

RADIO & TELEVISION NEWS

**SEPTEMBER
1953**

IN THIS ISSUE

R. F. POWER MEASUREMENTS

TRANSISTOR CHARACTERISTICS

**BALANCED
CRYSTAL-DIODE MODULATOR**

FLEXIBLE PLATED CIRCUIT

**VISUAL PROOF OF
PERFORMANCE MEASUREMENTS**

**THE STANDARD COIL
82-CHANNEL TUNER**


CERTIFIED RECORD REVUE

**"SUPER HORN"
A FOLDED HORN ENCLOSURE**

INEXPENSIVE NOVICE STATION

**KNOW YOUR 1954 ZENITH
TV RECEIVERS**

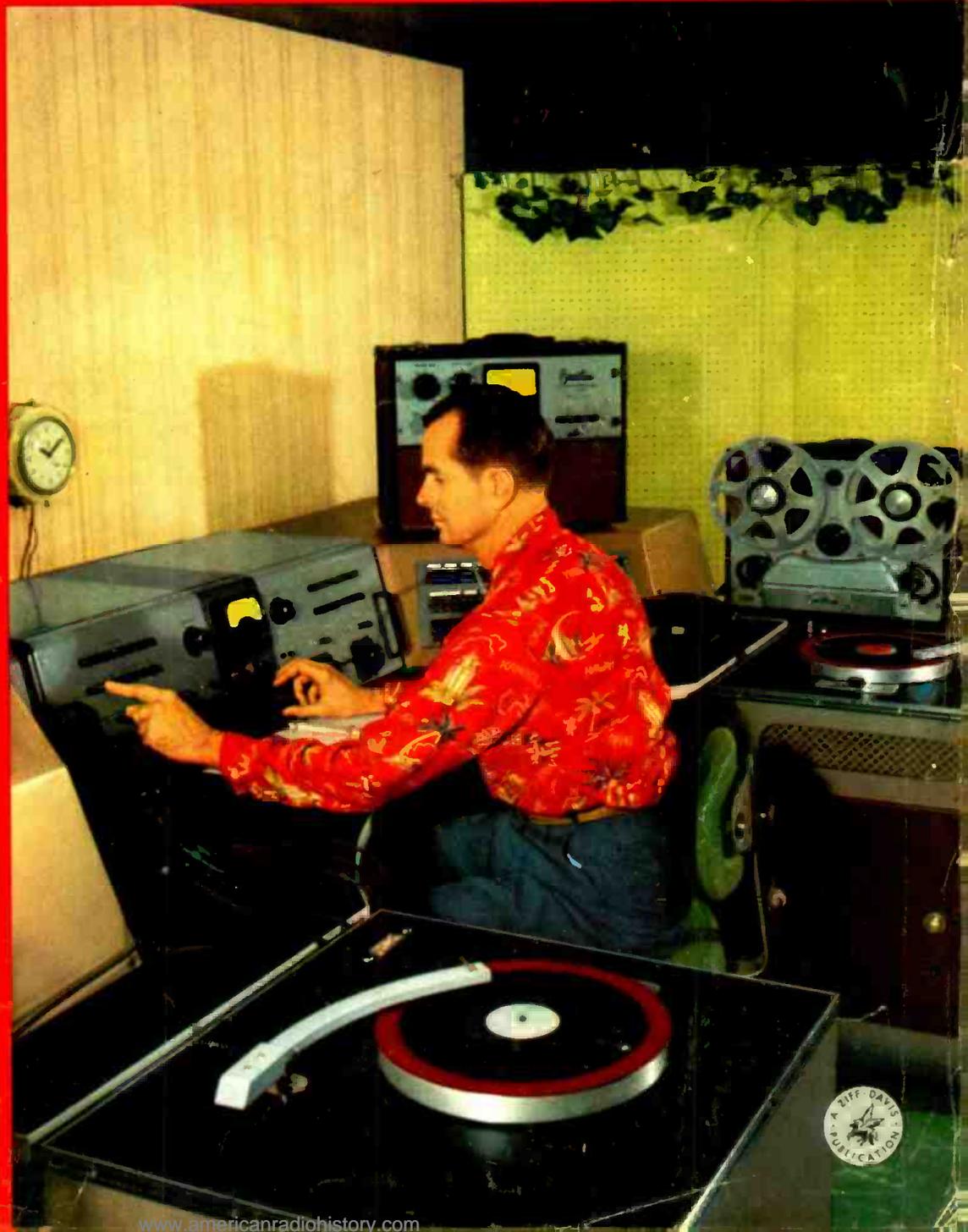**ELECTRONICS
GOES TO THE FAIR**
(See Page 73)



The "big moment"

...but whose big moment is it?

YOU FLICK THE SWITCH. This is the moment
... the final check.

And this is the big moment your customer
has been waiting for.

But, it's a big moment for you, too ...
because your reputation rests on the job
the new tubes do from this moment on.

Still, you have no worries ... for
your own experience has proven—
time and again—that the superior
quality of RCA Receiving Tubes is
your best measure of protection
against premature tube failures.

So, when your call is completed,
you can be confident that you've
won *another* steady customer.

Helping you to safeguard your
reputation is a vital, everyday serv-
ice of RCA Tubes. And that protec-
tion is yours at no extra cost.


"Sign up" for Success

Identify yourself with RCA! Ask your
RCA Tube Distributor today how you can
qualify for a Dealer
Identification Plaque
displaying your name.
He'll give you all the
exciting details on the
dynamic new RCA
promotion plan to
help you build your
business.



RADIO CORPORATION of AMERICA
ELECTRON TUBES

HARRISON, N. J.

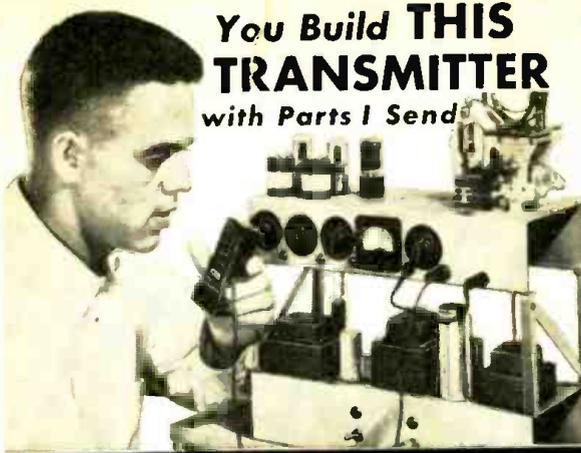

You Build **THIS TRANSMITTER**
with Parts I Send



Your FCC Operator's License can be your ticket to good jobs, security. I train you for it.

Learn RADIO-TV Broadcasting by Practicing at Home in Spare Time

Use parts I send for Actual Experience

My Training Leads to Jobs Like These

BROADCASTING: Chief Technician, Chief Operator, Power Monitor, Remote Control Operator, SHIP AND HARBOR RADIO: Chief Operator, Radiotelephone Operator, GOVERNMENT RADIO: Operator in Army, Navy, Coast Guard, Forestry Service Dispatcher, POLICE RADIO: Transmitter Operator, Service Technician, AVIATION RADIO: Plane Radio Operator, Airport Transmitter Operator, TELEVISION: Pickup Operator, Voice Transmitter Operator, TV Technician.




I TRAINED THESE MEN AT HOME

 "Am employed as transmitter engineer-studio operator at KPAT. Most important day of my life was when I enrolled with NRI." —Elmer Frewaldt, Madison, S. Dak.

 "I did not know a thing about Radio before I enrolled for your training. Now I have a job as Studio Engineer at Radio Station KMMJ." —Bill Delzell, Central City, Nebr.

 "A former employer recommended National Radio Institute training to me. Now employed as transmitter operator in Harrisburg." —Albert Herr, New Cumberland, Pa.

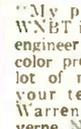 "My position with WNET is video control engineer on the RCA color project. I owe a lot of my success to your textbooks." —Warren Deem, Malverne, N. Y.

 "Am with WCOC. Happy with my job. NRI course can't be beat. Passed exam for 1st class Radio-phone license with no trouble." —Jesse W. Parker, Meridian, Miss.

AVAILABLE TO VETERANS UNDER G. I. BILLS

I Also Have a Course in Radio-TV SERVICING



If you prefer a career in Radio-Television Servicing, I'll train you at home for it. Course includes many Kits of parts. My book shows that many make \$10, \$15 a week EXTRA fixing sets while training.

The Communication Course I offer you is backed by NRI's 40 year record of training men at home. My well-illustrated lessons give you the basic principles you must have to assure success. My skillfully developed kits "bring to life" what you learn from my lessons, give you practical experience on circuits common to BOTH Radio and Television. You build the low-power Broadcasting Transmitter shown above (at left). You put this station "on the air," and conduct procedures required of Broadcasting Station operators. My book shows other valuable equipment you build and keep.

mitter Operators, Remote Control Operators, Service and Maintenance Technicians, etc. Mail Coupon. Find out, without obligation, what I offer. NRI training can assure you more of the better things of life; can help you qualify for high pay and promotion when times are good, enjoy greater security when jobs are scarce. Progressive, ambitious men consider Radio-TV an outstanding field for their life's work. My 64-page book, "How to Be a Success in Radio-Television," gives important facts about America's fast growing industry, details of job opportunities, tells about kits I furnish for practical experience, shows what my graduates are doing and earning. You don't have to leave home or give up your job to take NRI courses. You learn at home in your spare time, at low cost, on terms as low as \$5 a month. Many of my graduates make more than the total cost of my training in just two weeks. Mail coupon now. J. E. SMITH, President, National Radio Institute, Dept. 3JE, Washington 9, D. C. OUR 40th YEAR.



J. E. SMITH
PRESIDENT
National Radio Institute
For 40 years, the leader in training men at home.

Television's Rapid Growth Making Good Jobs, Prosperity

Radio is bigger than ever with over 3000 Broadcasting Stations on the air making good jobs for Chief Operators, Recording and Remote Control Operators, Power Monitors, Technicians, etc. Now there's Television, too. About 200 TV Stations are on the air with many more being built, construction of hundreds of additional stations authorized, and new TV Station applications being filed every month. Think of the demand this is creating from coast to coast for Pickup and Voice Trans-

Send for **FREE 64 Pg. Book**

Mr. J. E. SMITH, President, Dept. 3JE
National Radio Institute, Washington 9, D. C.


Mail me 64-page Book FREE. (No salesman will call. Please write plainly.)

Name Age

Address

City Zone State

VETS write in date of discharge

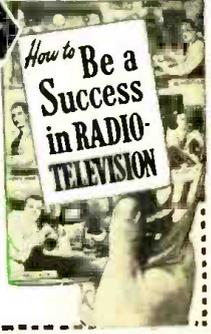

RADIO & TELEVISION NEWS is published monthly by the Ziff-Bass Publishing Company at 64 E. Lake St., Chicago 1, Ill. Entered as second-class matter, July 21, 1948, at the Post Office, Chicago, Ill., under the act of March 3, 1879. Authorized by Post Office Department, Ottawa, Canada, as second-class matter, SUBSCRIPTION RATES: Radio & Television News—one year, U. S. and Possessions, Pan-American countries, and Canada \$4.00; all other foreign countries \$5.00; Radio-Electronic Engineering Edition—one year, U. S. and Possessions, Pan-American countries, and Canada \$6.00; all other foreign countries \$7.00. Postmaster—Please return undelivered copies under form 3589 to 64 E. Lake St., Chicago 1, Ill.

Editor and Asst. Publisher
OLIVER READ, D.Sc., W1ETI

Managing Editor
WM. A. STOCKLIN, B.S.

Technical Editor
H. S. RENNE, M.S.

Service Editor
CHARLES TEPFER

Amateur Radio Editor
N. ROSA, W1NOA

Assistant Editors
P. B. HOEFER
M. C. MAGNA

Television Consultant
WALTER H. BUCHSBAUM

Short-Wave Editor
KENNETH R. BOORD

Staff Artist
FRANK SAYLES

Draftsmen
A. A. GANS, W2TSP
J. A. GOLANEK

Advertising Manager
L. L. OSTEN

Midwest Adv. Manager
JOHN A. RONAN, JR.

Western Adv. Manager
JOHN E. PAYNE

RADIO & TELEVISION NEWS

Reg. U. S. Pat. Off.

Radio News Trademark Reg. U. S. Pat. Office • Television News Trademark Reg. U. S. Pat. Office.

First in
radio-television-electronics

Average Paid Circulation over 200,000

CONTENTS

SEPTEMBER, 1953

New TV Grants Since Freeze Lift.....	16
The Standard Coil 82-Channel Tuner.....	Walter H. Buchsbaum 35
"Super Horn"—A Folded Horn Enclosure.....	Edward J. Gately, Jr. & Thomas A. Benham 38
Extended Class A Amplifier.....	Lloyd B. Hust 40
Electronic Counter.....	Erwin Levey 43
Assemble Your Own Hearing Aid.....	E. G. Louis 46
Keyed A.G.C. Systems.....	Milton S. Kiver 48
Counter Improves Tape Recorder.....	Richard H. Dorf 51
Inexpensive Novice Station (Part I).....	Larry Trombly, W0DCB, & Robert A. Hathaway, W0GTK 52
Break-in Without Relays.....	Bruce F. Brown, W6TWW 55
U.H.F. Test Equipment Adapter.....	Dan Lerner & Winston Starks 56
Certified Record Revue.....	Bert Whyte 58
Know Your 1954 Zenith TV Receivers.....	Brian J. Marohnic 59
A Square-Wave Shaper.....	George Ellis Jones, Jr. 63
Selenium Diode Applications.....	J. T. Cataldo 64
Obtaining Transistor Characteristic Curves.....	Warren Philbrook 66
A Transistorized Audio Oscillator.....	Louis E. Garner, Jr. 68
Automatic Input Switching Without Relays.....	Allan M. Ferres 70
A Multi-Band, Constant Impedance Antenna.....	Calvin R. Graf, W5LFM 72
Electronics Goes to the Fair.....	Robert Burdette 73
Speech Filters for Amateur Receivers.....	Hector E. French, W1JKZ 74
TV Receiver Sensitivity.....	John Rankin 76
Mac's Radio Service Shop.....	John T. Frye 78
Simple Sound Effects for Home Movie Makers.....	Jack Darr 98
Watch Those Heater Voltage Measurements.....	John K. Frieborn 134
Service Hints on Zenith TV Sets.....	138
New TV Stations on the Air.....	148
Radio-TV Service Industry News.....	162
"Converterless" 75-Meter Mobile Reception.....	Howard R. Shannon, VE7AGE 174

DEPARTMENTS

For The Record.....	The Editor 8	What's New in Radio.....	80
Spot Radio News.....	16	Technical Books.....	126
Within the Industry.....	24	Manufacturers' Literature.....	176
Short-Wave.....	K. R. Boord 75	New TV Products.....	186

COPYRIGHT 1953

(All Rights Reserved)

ZIFF-DAVIS PUBLISHING COMPANY

Editorial and Executive Offices

366 Madison Ave., New York 17, N. Y.

VOLUME 50 • NUMBER 3



Member
Audit Bureau of
Circulations

SUBSCRIPTION SERVICE: All communications concerning subscriptions should be addressed to Circulation Dept., 64 E. Lake St., Chicago 1, Ill. Subscribers should allow at least four weeks for change of address.

CONTRIBUTIONS: Contributors are advised to retain a copy of their manuscripts and illustrations. Contributions should be mailed to the New York Editorial Office and must be accompanied by return postage. Contributions will be handled with reasonable care, but this magazine assumes no responsibility for their safety. Any copy accepted is subject to whatever adaptations and revisions are necessary to meet the requirements of this publication. Payment covers all author's, contributor's, and contestant's rights, title and interest in and to the material accepted and will be made at our current rates upon acceptance. All photos and drawings will be considered as part of the material purchased.

RADIO & TELEVISION NEWS



COVER PHOTO: Part of the elaborate audio installation in the Radio-Television Building at the Los Angeles County Fair grounds in Pomona. All types of sound gear are available. (Ektachrome by P. J. Samerjan)

ZIFF-DAVIS PUBLISHING COMPANY

Chairman of the Board and Publisher
WILLIAM B. ZIFF

President
B. G. DAVIS

Secretary-Treasurer
G. E. CARNEY

Vice-Presidents
H. J. MORGANROTH
Production Director

H. G. STRONG
Circulation Director

BRANCH OFFICES

CHICAGO (1)
64 E. Lake St., AN 3-5200
LOS ANGELES (14)

Slatter Center, 900 Wilshire Blvd., Mich. 9856

Now IN YOUR OWN HOME Learn

TELEVISION RADIO ELECTRONICS

the Amazingly Effective
D. T. I. WAY

—with the aid of BOTH
HOME EQUIPMENT
and HOME MOVIES

NO PREVIOUS EXPERIENCE NEEDED


NOW... get
**EVERYTHING
YOU NEED**

for real Laboratory-
type training
AT HOME



**5 INCH
"SCOPE"**

Oscilloscope

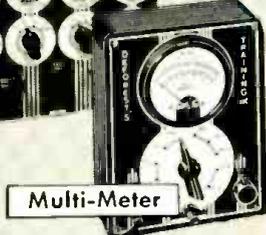

Multi-Meter



21 INCH

Build and keep this BIG DTI
engineered TV set—easily
converted to U.H.F.

1. Build over 300 fascinating experiments from 16 BIG SHIPMENTS of Electronic-Radio parts which you KEEP.
2. Build valuable commercial-type test equipment—as shown to the left—which you KEEP. This includes a quality 5 INCH oscilloscope and jewel bearing Multi-Meter—both highly useful for Television work.
3. Build and keep a big 21 INCH TV Set. (D.T.I. offers another home training in Television-Radio-Electronics, but without the TV set.)
4. Use a 16 mm. movie projector and new series of highly instructive movies—a wonderful aid to help you grasp important fundamentals faster... easier... better.
5. Enjoy well-illustrated, easy-to-read lessons with handy FOLD-OUT diagrams.
6. Get an honest-to-goodness EMPLOYMENT SERVICE to help you get a good job after graduating—or assistance in starting your OWN SALES AND SERVICE BUSINESS. Mail coupon today for the complete details.

Above:
Work over
300
fascinating
experiments
with this
equipment

What will mailing the coupon below do for YOU? Just this! You'll find out about one of today's most remarkable... practical ways to prepare to get into America's amazing billion dollar opportunity field of TELEVISION-RADIO-ELECTRONICS. You'll see how to get into fascinating work that pays well... that offers one of America's most promising futures... that enables you to start your own business almost "on a shoe string," if you prefer this to a job opportunity.

And above all, you'll get some GOOD NEWS especially welcomed by men anxious to earn REAL MONEY in this thrilling field. For you'll see that NOW you can get the kind of practical, laboratory-type training so desirable for making real progress in Television-Radio-Electronics AND WITHOUT LEAVING HOME.

You'll see that DeForest's Training, Inc. sends everything needed to set up your own HOME LABORATORY.

You get and keep the same type of basic electronic equipment used in our modern Chicago Training Laboratories. You get home training that includes the knowledge and experience gained from training thousands of students first hand in Chicago. And to top it all, you use DTI's amazingly effective and exclusive home training aid—INSTRUCTIVE MOVIES. But why not get the complete story? Mail coupon today for information-packed literature.


MODERN LABORATORIES

If you prefer, get all your preparation in our new Chicago Training Laboratories—one of the finest of its kind. Ample instructors, modern equipment. Write for details!

MILITARY SERVICE!

If you're subject to military service, the information we have for you should prove very helpful. Mail coupon today.

Get this
information-packed publication

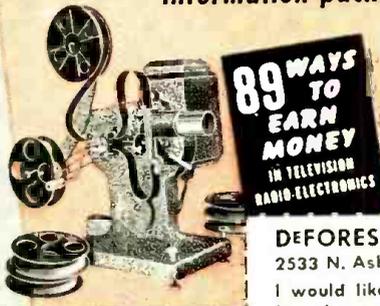

FREE!

Mail Coupon Today

"ONE OF AMERICA'S FOREMOST
TELEVISION TRAINING CENTERS"
— Established 1931 —



DEFOREST'S TRAINING, INC.

AFFILIATED WITH

DEVRY Technical INSTITUTE

CHICAGO 14, ILLINOIS


DEFOREST'S TRAINING, INC.

RN-9J

2533 N. Ashland Avenue, Chicago 14, Ill.

I would like your valuable information-packed publication showing how I can get started toward a good job or my own business in Television-Radio-Electronics.

Name Age
Street Apt.
City Zone State

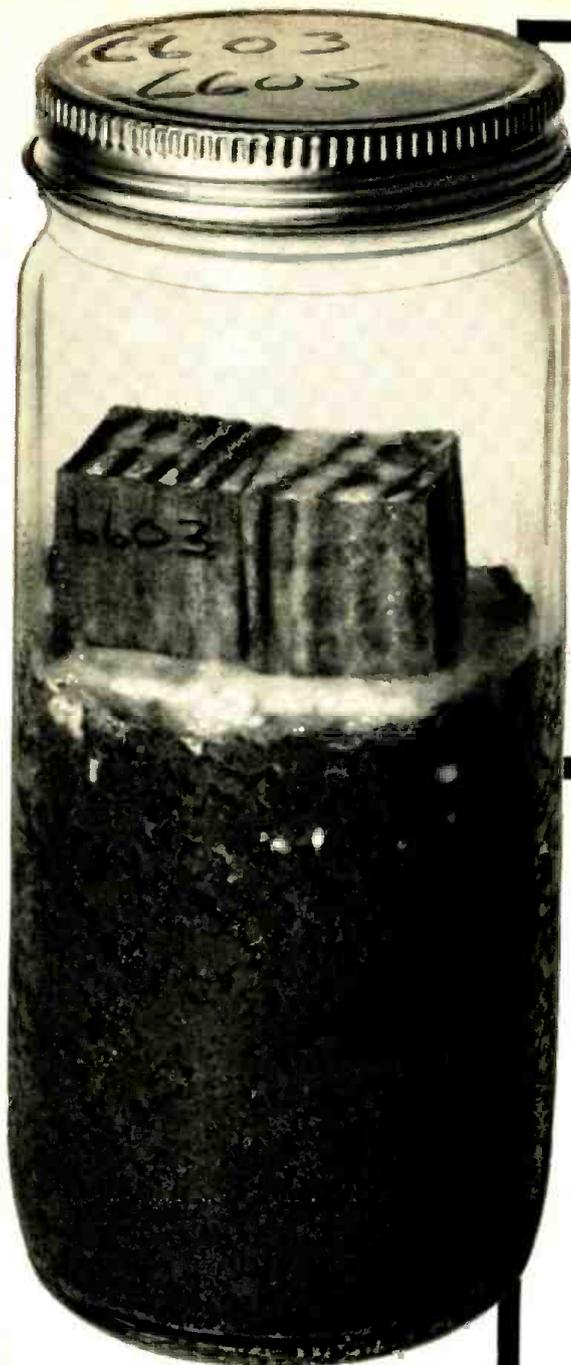

THIS BOTTLE TURNS SEVEN YEARS INTO SEVEN MONTHS

◀ *Test blocks of pole wood are fed to destructive fungi in bottles like this at Bell Laboratories. Wood rests on soil which controls moisture conditions and promotes fungus growth. Test speeds search for better preservatives.*

This year the Bell System is putting 800,000 new telephone poles into service. How effectively are they preserved against fungus attack and decay?

Once the only way to check a preservative was to plant treated wood specimens outdoors, then wait and see—for seven years at least. Now, with a new test devised in Bell Telephone Laboratories most of the answer can be obtained in seven months.

Cubes of wood are treated with preservatives, then enclosed in bottles with fungus of the most destructive kind, under temperature and humidity conditions that accelerate fungus activity. Success—or failure—of fungus attack on cubes soon reveals the best ways to preserve poles.

The new test has helped show how poles can be economically preserved for many years. It is another example of how Bell Telephone Laboratories works to keep down the cost of your telephone service.

A boring is taken from a pole section to see how far preservative has penetrated. For poles to last, it must penetrate deeply and be retained for a long time.



BELL TELEPHONE LABORATORIES

*Improving telephone service for America provides
careers for creative men in scientific and technical fields*

Check the specs...

Check performance...

Then, They'll Choose Hallicrafters




Model S-76

Double conversion receiver. Broadcast Band 538-1580 kc plus three short-wave bands covering 1720 kc-34 Mc.

Calibrated electrical bandspread for easy tuning. Double superhet with 50 kc second i-f and giant 4-inch "S" meter. Five position selectivity, one r-f, two conversion, two i-f stages. temperature compensated. 3.2 or 500 ohm outputs.

Satin black steel cabinet. 18½" x 8⅞" x 9½" deep. Nine tubes, voltage regulator, and rectifier. For 105/125 V. 50/60 cycle AC. Use R-46 speaker. **\$199⁹⁵**

SELECTIVITY CURVES, S-76

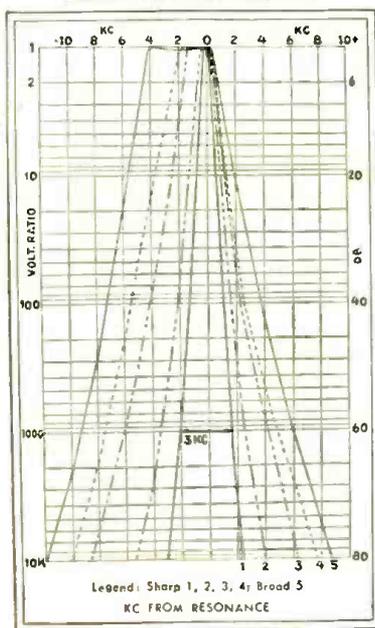

Do you know any better way, any other way, to judge SW equipment than to check the specifications and the performance? Frankly that's the only valid way we can think of to make sure you get your money's worth. Check these specs. Take a look at the selectivity curve for the S-76. It is typical of the outstanding value Hallicrafters offers in every price class.



Model HT-20. T.V.I. suppressed 100 watt AM-CW transmitter with all spurious outputs above 40 Mc at least 90 db. below full rated output.

All stages metered; single meter with eight position meter switch; output tuning indication. Frequency range of 1.7 Mc to 31 Mc continuous on front panel control. Seven tubes plus five rectifiers. For 105/125 V. 50/60 cycle **\$449⁵⁰**

Model SX-71. Covers Broadcast Band 535-1650 kc plus four short-wave bands covering 1650 kc-34 Mc. and 46-56 Mc.


Narrow Band FM one r-f, two conversion, and three i-f stages. Temperature compensated, voltage regulated. Three watt output (terminals for 500 and 3.2 ohms).

Satin black steel cabinet. 18½" x 8⅞" x 12" deep. 11 tubes plus regulator, rectifier. For 105/125 V. 50/60 cycle AC. Use R-46 speaker. **\$249⁹⁵**



Model R-46. Matching 10" PM speaker for use with Hallicrafters communications receivers SX-71, SX-76, SX-73 or SX-62. 80 to 5000 cycle range. Matching transformer with 500-ohm input. Speaker voice coil impedance, 3.2 ohms.

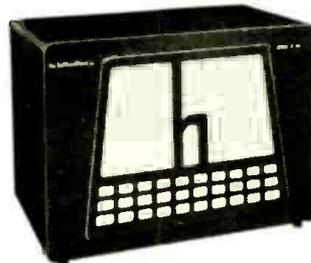Satin black steel cabinet matches all Hallicrafters receivers. Cloth covered metal grille. 15" x 10⅞" x 10⅞" deep. Ship. wt. 17 lbs. **\$24⁹⁵**



hallicrafters

World's Leading Exclusive Manufacturer of Communications and High Fidelity Equipment, Radio and Television

4401 West Fifth Avenue, Chicago 24, Illinois
Hallicrafters Ltd., 51 Camden Street, Toronto, Canada


**E-V ADDS THE MAGIC TOUCH
TO TV RECEPTION**

**NEW
all channel UHF
TV CONVERTER**



MODEL 3300

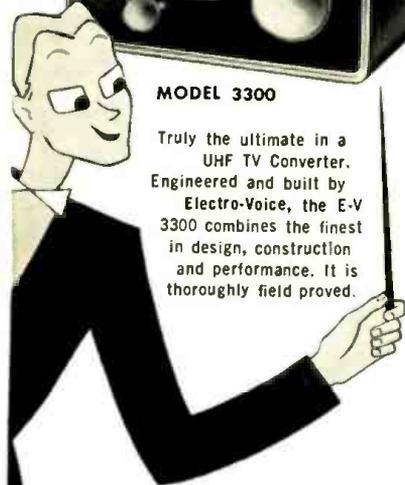Truly the ultimate in a UHF TV Converter. Engineered and built by Electro-Voice, the E-V 3300 combines the finest in design, construction and performance. It is thoroughly field proved.



Adds all UHF Channels to VHF Sets

Non-slip micrometer type tuning system* provides smooth, accurate, continuous tuning of all UHF channels 14-83. No band switches, strips or coils. New high-efficiency low-loss circuit. Operates with either separate UHF and VHF antennas or on all-channel (2-83) antenna. Adequate shielding. One control turns Converter and TV set "on" or "off" and switches to correct antenna. Utilizes channels 5 or 6 of VHF TV set as Intermediate Frequency. Does not affect VHF reception.

Installation is simple—connect to antenna input of VHF TV set and just plug in. For 105-125 volts, 50-60 cycles AC. Housed in small, attractive dark brown cabinet, 7 $\frac{3}{4}$ " x 5 $\frac{1}{4}$ " x 6 $\frac{1}{4}$ ". Completely self-contained, ready for installation.

MODEL 3300. List Price, \$39.50
*Patent Applied For

Send for Bulletin
No. 188

Electro-Voice

ELECTRO-VOICE, INC.
410 CARROLL STREET • BUCHANAN, MICH.
Export: 13 E. 40th St., New York 16, U.S.A. Cables: Arlob

For the **RECORD.**

BY THE EDITOR

HI-FI MAGICIANS

IT HAS seemed, in recent weeks, that hardly a day goes by that we don't recall the phrase. "Nothing is certain but death and taxes" and each time this phrase comes to mind we are more and more tempted to add "and the audiophile's dilemma." Sometimes we wonder just how far the audio industry can go in making all sorts of fancy performance claims for their products. The majority of manufacturers of audio equipment have apparently made a very honest attempt to follow an intelligent pattern and adhere to accepted engineering practice when publishing specifications for their equipment. Recently, however, there has been a steady influx of new companies entering the so-called high-fidelity market. All too often these manufacturers are guilty of misleading the public in their attempts to sell run-of-the-mill audio gear as high-fidelity equipment.

For example, we have just attended a press conference to see and hear a new tape recorder (one of three announced in four days) priced for mass-production and publicized as high-fidelity equipment. This machine, and we shall name no names, is manufactured by a well-known producer of photographic equipment; a company long respected in that field for its quality products. We spent the first moments of our visit in listening to some recorded classics from this new "Hi-Fi" portable. Being technically minded, we were most anxious to see the specifications for the new models. There were two; one employing a tape speed of 3 $\frac{3}{4}$ " /sec., the other, tagged as a "Hi-Fi" with a tape speed of 7 $\frac{1}{2}$ " /sec. We drew a mental comparison between many other tape recorders we had heard in the past and came to an immediate conclusion that the over-all frequency range was sadly lacking at the high and low ends.

In studying the published specifications for this "Hi-Fi" model, we were startled to find the following: "frequency response: 30 to 13,000 cycles." The specifications, however, did not qualify this claim by stating "plus or minus so many db" but simply stated "30 to 13,000 cycles." Our curiosity was greatly aroused when we came across the specifications showing the amplifier tube complement. The power tube is the well-known 6AQ5 having a power output of 3.2 watts.

Any audio engineer or experimenter worth his salt knows full well that a 6AQ5 beam power amplifier producing that output has a known total harmonic distortion of 8%. This is not "high-fidelity" in our book.

And, we have never in our experience been able to find a 6" x 9" elliptical loudspeaker, selling at catalogue prices for \$3.44, capable of producing the high-fidelity audio range stated by this manufacturer for this model to be from 30 to 13,000 cycles. We'd expect to pay many times that amount for a good 15" woofer to give us 30-cps. response, plus a good tweeter to reproduce 13,000-cps. response clearly.

Upon returning to our desk the next morning, we checked the specifications on seven leading tape recorders to determine what claims were made for their performance. Here are the results: Recorder A, 50-7000 cycles at 7 $\frac{1}{2}$ " /sec.; Recorder B, 40-10,000 \pm 2 db at 7 $\frac{1}{2}$ " /sec.; Recorder C, 40-12,000 cycles at 7 $\frac{1}{2}$ " /sec.; Recorder D, 50-9000 cycles \pm 2 db, 7 $\frac{1}{2}$ " /sec.; Recorder E, 50-7000 cycles \pm 2 db, 7 $\frac{1}{2}$ " /sec.; Recorder F, 60-15,000 cycles \pm 3 db, 7 $\frac{1}{2}$ " /sec.; and Recorder G, 70-7500 cycles, 7 $\frac{1}{2}$ " /sec. We averaged these specifications to find that our "composite recorder" would have a frequency response of 60 to slightly less than 10,000 cycles at 7 $\frac{1}{2}$ " /sec. Our "composite recorder" having this response would sell for \$397.93, this being the average cost of the seven models.

The recorder discussed in preceding paragraphs was intended to be marketed for approximately \$250.00. The point we should like to make is that the purchaser of an audio tape recorder could be very easily misled when comparing specifications of respective machines. He would come to the conclusion that he could purchase a home hi-fi tape machine having a frequency response of 30 to 13,000 cycles, using the same tapes and speed employed by the other machines and at a price far less than the others.

Even the "Cadillacs and Lincolns" of the tape recorder industry only claim a frequency response of 40 to 10,000 cycles at 7 $\frac{1}{2}$ " /sec.

This is but one of many examples we see and hear about each week in this business of technical publishing. There is a great need for a clear understanding within the industry and a code of ethics in advertising claims for what we call "high-fidelity."

The American public has always been a bit gullible when it comes to things technical or electronic. Let's quit calling every audio component and system "a new super ultra high-fidelity" product. If we don't pull in the reins pretty soon—the term will die out as an acceptable description of a quality sound reproducing system O.R.


NEW HOME OF ALLIED RADIO

ultra-modern facilities TO SERVE YOU BEST

FREE!

Get your
re-packed
**1954
ALLIED
268-PAGE CATALOG**

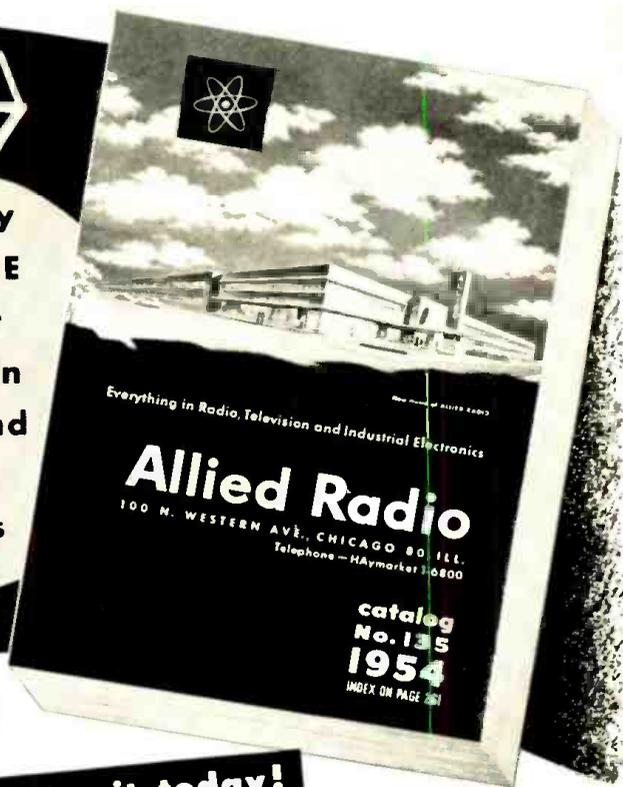the only
COMPLETE
catalog for
everything in
**TV, Radio and
Industrial
Electronics**



The World's Largest Stocks

- TV and Radio Parts
- Test Instruments
- High-Fidelity Equipment
- Custom TV Chassis
- AM, FM Tuners and Radios
- Recorders and Supplies
- P. A. Systems, Accessories
- Amateur Station Gear
- Builders' Kits, Supplies
- Equipment for Industry

**Fastest Service in
Electronic Supply**

Send for it today!



You'll want the *one* complete Buying Guide to *Everything in Electronics*—268 pages packed with the world's largest selection of quality equipment at lowest, money-saving prices. See all the latest releases in custom TV chassis, TV antennas and accessories; AM and FM tuners and radios; *everything* in High-Fidelity custom components; latest P.A. Systems and accessories; recorders and supplies; Amateur receivers, transmitters and station gear; specialized industrial electronic equipment; test instruments; builders' kits; huge listings of parts, tubes, tools, books—your choice of the world's *most complete stocks* of quality equipment. **ALLIED** gives you *every* buying advantage: speedy shipment, expert personal help, lowest prices, liberal terms, assured satisfaction. Get the 1954 **ALLIED** Catalog. Keep it handy—and save time and money. Send for your **FREE** copy today.

**SAVE ON EVERYTHING
IN ELECTRONICS**

**SEND FOR THE LEADING
ELECTRONIC BUYING GUIDE**

free

ALLIED RADIO
World's Largest Electronic Supply House

EASY-PAY TERMS

Use ALLIED'S liberal Easy Payment Plan—only 10% down, 12 months to pay—no carrying charge if you pay in 60 days. Available on Hi-Fi and P. A. units, recorders, TV chassis, test instruments, Amateur gear, etc.

TV and HI-FI SPECIALISTS

To keep up with developments in High-Fidelity and TV, look to ALLIED. Count on us for all the latest releases and largest stocks of equipment in these important fields. If it's anything in High-Fidelity or Television—we have it *in stock!*

ALLIED RADIO CORP., Dept. 1-J-3
100 N. Western Ave., Chicago 80, Illinois

Send FREE 268-Page 1954 ALLIED Catalog.

Name _____

Address _____

City _____ Zone _____ State _____

GENERAL ELECTRIC ANNOUNCES



Custom Music Ensemble

A new line of High-Fidelity Reproduction Equipment for Volume Sales...Record Profits!

HERE'S THE LINE of high-fidelity reproduction equipment that will bring customers to you! It offers the ideal answer to the growing demand for matched units in home sound systems. For the first time quality voice and music reception is available to every family... at prices they can afford!

The General Electric Variable Reluctance Cartridge started this business of high-fidelity. Today's G-E announcement of a new line of reproduction equipment completes the home sound picture. Your customers get the dual advantage of purchasing individual components or the complete ensemble for a home decorator installation.

Whether you sell or install high-fidelity sound equipment you'll want to have these units on hand. Be ready for the tremendous market they'll create...order today! Call the local General Electric distributor or write today to: *General Electric Company, Section 993, Electronics Park, Syracuse, New York.*

You can put your confidence in—

GENERAL  **ELECTRIC**



G-E DUAL COAXIAL
Model A1-400

New approach to coaxial speaker design—high sensitivity at low cost—exceptional balance between speaker with G-E baffle plate development. Revolutionary Tweeter Heart... wavefront shaping plug... provides smooth tweeter response.



G-E PREAMPLIFIER-CONTROL UNIT
Model A1-200

Combines functions of equalized pre-amplifier plus adjustable record compensation, program input selection, tone controls and volume control. Matching unit for the "Custom Music" amplifier. Self-powered for use with any installation.



G-E POWER AMPLIFIER Model A1-300

The G-E A1-300 is a medium power, compact amplifier designed to provide needed speaker power. An essential element in the new General Electric "Custom Music" Ensemble. It will deliver high-fidelity performance at very low cost.



G-E DELUXE TONE ARMS
Model A1-500 (12") Model A1-501 (16")

For home or broadcast station use. Compatible with the exceptional quality of G-E cartridges. Calibrated stylus pressure adjustment... 1 gram to 10 grams. They were developed to improve record reproduction in any home or broadcast studio installation.




G-E SPEAKER ENCLOSURE
Model A1-406 (6 cu. ft.)

Attractive corner or wall cabinet in hand-rubbed blond or mahogany veneers. "Distributed port" design offers tone realism from 40 to 15,000 cycles.

RADIO & TELEVISION NEWS

Here comes opportunity

...ready or not!

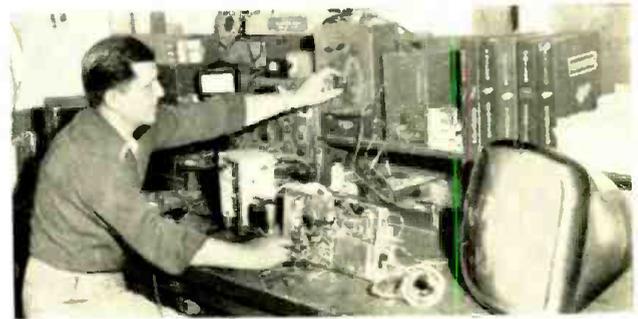

- Prepare now for the new Radio-TV-Electronics boom. Get in on VHF and UHF . . . aviation and mobile radio . . . color TV . . . binaural sound! The International Correspondence Schools can help you!

If you've ever thought about Radio or Television as a career . . . if you have the interest, but not the training . . . if you're waiting for a good time to start . . . NOW'S THE TIME!

No matter what your previous background, I.C.S. can help you. If Radio-TV servicing is your hobby, I.C.S. can make it your own profitable business. If you're interested in the new developments in Electronics, I.C.S. can give you the basic courses of training you need. If you have the job but want faster progress, I.C.S. can qualify you for promotions and pay raises.

I.C.S. training is *success-proved* training. Hundreds of I.C.S. graduates hold top jobs with top firms like R.C.A., G.E., DUMONT, I.T.&T. Hundreds of others have high ratings in military and civil service. Still others have successful businesses of their own.

With I.C.S., you get the rock-bottom basics and theory as well as the all-important bench practice and experimentation. You learn in your spare time—no interference with business or social life. You set your own pace—progress as rapidly as you wish.

Free career guidance: Send today for the two free success books, the 36-page "How to Succeed" and the informative catalog on the course you check below. No obligation. Just mark and mail the coupon. With so much at stake, you owe it to yourself to act—and act fast!

CHECK THESE SEVEN
FAMOUS I. C. S. COURSES
— ONE FOR YOU!

- PRACTICAL RADIO-TELEVISION ENGINEERING**—Foundation course for radio-television career. Basic principles plus advanced training. Radio, Sound, TV.
- TELEVISION TECHNICIAN**—To qualify you for high-level technical positions in television. Camera, studio, transmitter techniques. Manufacture, sale and installation of TV equipment.
- TELEVISION RECEIVER SERVICING**—Installation, servicing, conversion. Dealership. For the man who knows about radio and wants TV training.
- RADIO & TELEVISION SERVICING**—Designed to start you repairing, installing and servicing radio and television receivers soon after starting the course.
- RADIO & TELEVISION SERVICING WITH TRAINING EQUIPMENT**—Same as above but with addition of high-grade radio servicing equipment and tools.
- RADIO OPERATING COURSE**—Special course to help you pass the Government examination for operator's licenses. Code. TV. FM. Radio regulations.
- INDUSTRIAL ELECTRONICS**—Broad, solid background course devoted to the electron tube and to its many applications.

INTERNATIONAL CORRESPONDENCE SCHOOLS



BOX 2249-C, SCRANTON 9, PENNA.

Without cost or obligation, send me "HOW TO SUCCEED" and the booklet about the course BEFORE which I have marked X:

- | | | | | |
|---|--|---|---|---|
| <ul style="list-style-type: none"> <input type="checkbox"/> ART <input type="checkbox"/> Commercial Art <input type="checkbox"/> Magazine and Book Illustrating <input type="checkbox"/> Fashion Illustrating <input type="checkbox"/> Cartooning <input type="checkbox"/> Show Card and Sign Lettering <input type="checkbox"/> Automobile, Mechanic <input type="checkbox"/> Auto-Elec. Technician <input type="checkbox"/> Auto Body Rebuilding and Refinishing <input type="checkbox"/> Diesel—Gas Engines <input type="checkbox"/> AVIATION <input type="checkbox"/> Aeronautical Engineering Jr. <input type="checkbox"/> Aircraft Engine Mechanic <input type="checkbox"/> Airplane Drafting <input type="checkbox"/> BUILDING <input type="checkbox"/> Architecture <input type="checkbox"/> Arch. Drafting <input type="checkbox"/> Building Contractor <input type="checkbox"/> Estimating <input type="checkbox"/> Carpenter Foreman <input type="checkbox"/> Reading Blueprints <input type="checkbox"/> House Planning <input type="checkbox"/> Plumbing | <ul style="list-style-type: none"> <input type="checkbox"/> Heating <input type="checkbox"/> Steam Fitting <input type="checkbox"/> Air Conditioning <input type="checkbox"/> Electrician <input type="checkbox"/> BUSINESS <input type="checkbox"/> Business Administration <input type="checkbox"/> Certified Public Accountant <input type="checkbox"/> Accounting <input type="checkbox"/> Bookkeeping <input type="checkbox"/> Stenography and Typing <input type="checkbox"/> Secretarial <input type="checkbox"/> Federal Tax <input type="checkbox"/> Business Correspondence <input type="checkbox"/> Personnel and Labor Relations <input type="checkbox"/> Advertisin^g <input type="checkbox"/> Retail Business Management <input type="checkbox"/> Managing Small Business <input type="checkbox"/> Sales Management <input type="checkbox"/> Salesmanship <input type="checkbox"/> Traffic Management <input type="checkbox"/> CHEMISTRY <input type="checkbox"/> Chemical Engineering <input type="checkbox"/> Chemistry <input type="checkbox"/> Analytical Chemistry <input type="checkbox"/> Petroleum—Nat'l Gas <input type="checkbox"/> Pulp and Paper Making <input type="checkbox"/> Plastics | <ul style="list-style-type: none"> <input type="checkbox"/> CIVIL, STRUCTURAL ENGINEERING <input type="checkbox"/> Civil Engineering <input type="checkbox"/> Structural Engineering <input type="checkbox"/> Surveying and Mapping <input type="checkbox"/> Structural Drafting <input type="checkbox"/> Highway Engineering <input type="checkbox"/> Reading Blueprints <input type="checkbox"/> Concrete Construction <input type="checkbox"/> Sanitary Engineering <input type="checkbox"/> DRAFTING <input type="checkbox"/> Aircraft Drafting <input type="checkbox"/> Architectural Drafting <input type="checkbox"/> Electrical Drafting <input type="checkbox"/> Mechanical Drafting <input type="checkbox"/> Structural Drafting <input type="checkbox"/> Sheet Metal Drafting <input type="checkbox"/> Mine Surveying and Drafting <input type="checkbox"/> ELECTRICAL <input type="checkbox"/> Electrical Engineering <input type="checkbox"/> Electrician <input type="checkbox"/> Electrical Maintenance <input type="checkbox"/> Electrical Drafting <input type="checkbox"/> Electric Power and Light <input type="checkbox"/> Lineman <input type="checkbox"/> HIGH SCHOOL <input type="checkbox"/> High School Subjects | <ul style="list-style-type: none"> <input type="checkbox"/> College Preparatory <input type="checkbox"/> Mathematics <input type="checkbox"/> Commercial <input type="checkbox"/> Good English <input type="checkbox"/> MECHANICAL AND SHOP <input type="checkbox"/> Mechanical Engineering <input type="checkbox"/> Industrial Engineering <input type="checkbox"/> Industrial Supervision <input type="checkbox"/> Foremanship <input type="checkbox"/> Mechanical Drafting <input type="checkbox"/> Machine Design-Drafting <input type="checkbox"/> Machine Shop Practice <input type="checkbox"/> Tool Design <input type="checkbox"/> Industrial Instrumentation <input type="checkbox"/> Machine Shop Inspection <input type="checkbox"/> Reading Blueprints <input type="checkbox"/> Toolmaking <input type="checkbox"/> Gas—Electric Welding <input type="checkbox"/> Heat Treatment—Metallurgy <input type="checkbox"/> Sheet Metal Work <input type="checkbox"/> Sheet Metal Pattern Drafting <input type="checkbox"/> Refrigeration <input type="checkbox"/> POWER <input type="checkbox"/> Combustion Engineering <input type="checkbox"/> Diesel—Electric <input type="checkbox"/> Electric Light and Power | <ul style="list-style-type: none"> <input type="checkbox"/> Stationary Steam Engineering <input type="checkbox"/> Stationary Fireman <input type="checkbox"/> RADIO, TELEVISION, COMMUNICATIONS <input type="checkbox"/> General Radio <input type="checkbox"/> Radio Operation <input type="checkbox"/> Radio Servicing—FM <input type="checkbox"/> Television <input type="checkbox"/> Electronics <input type="checkbox"/> Telephone Work <input type="checkbox"/> RAILROAD <input type="checkbox"/> Locomotive Engineer <input type="checkbox"/> Diesel Locomotive <input type="checkbox"/> Air Brakes <input type="checkbox"/> Car Inspector <input type="checkbox"/> Railroad Administration <input type="checkbox"/> TEXTILE <input type="checkbox"/> Textile Engineering <input type="checkbox"/> Cotton Manufacture <input type="checkbox"/> Rayon Manufacture <input type="checkbox"/> Woolen Manufacture <input type="checkbox"/> Loom Fixing <input type="checkbox"/> Finishing and Dyeing <input type="checkbox"/> Textile Designing |
|---|--|---|---|---|

Name _____ Age _____ Home Address _____

City _____ Zone _____ State _____ Working Hours _____ A.M. to _____ P.M.

Occupation _____

Special tuition rates to members of the U. S. Armed Forces. Canadian residents send coupon to International Correspondence Schools Canadian, Ltd., Montreal, Canada.



NICE GUY... with a ⁿundeserved black eye

If you understood what your
RADIO AND TELEVISION SERVICE DEALER
 is up against, you'd buy him a steak for his eye

WE'LL WAGER DOLLARS to doughnuts you approach a TV-Radio Service Dealer with apprehension — feeling sure he's scheming to "dupe" you out of an unfair portion of your hard-earned money. This mental black eye given the TV-Radio Service profession by the public is undeserved. When TV-Radio Service Dealers were swept into the spectacular growth of the nation's fastest developing new industry, some made mistakes, but the misguided were mighty few. The vast majority of Television and Radio Service Technicians are capable, efficient, thoroughly trustworthy businessmen doing a magnificent job of keeping pace with a rapidly expanding new industry.

And we know what we're talking about. Since 1945 — that's way back before nationwide TV — the Raytheon Manufacturing Company, through several of America's largest surety companies has been Bonding the repair work of Radio and Television Service Dealers. More than 30,000 Registered Bond Certificates have been issued to service dealers all over the United States, and of the millions of jobs these qualified Bonded dealers have handled we've received less than 50 complaints. We consider this amazing record a marvelous indication of the skill, integrity and ability of these selected service dealers.

The service dealers that are bonded through Raytheon are nationally known as **RAYTHEON BONDED ELECTRONIC TECHNICIANS**. They must be skilled technicians, have modern, efficient test equipment, and a wealth of experience to qualify for this coveted classification. They adhere to a strict 8-point Code of Ethics designed to protect you. Here it is:

1. Guarantee all Radio and Television repair work for 90 days.
2. Use only parts of recognized quality.
3. Charge not more than list price for parts installed.
4. Test customers' tubes as accurately as possible.
5. Keep labor charges at a reasonable level.
6. Perform only such work as is necessary.
7. Maintain proper equipment for good repair work.
8. Maintain the highest quality service.

Whatever the make and model of your radio or television sets, next time you need service we'd like to suggest you call a *Raytheon Bonded Electronic Technician*. Look for his seal. It's the symbol of a service man whose work, way of doing business, and integrity are above reproach. We're sure he'll satisfy you.



Excellence in Electronics

RAYTHEON MANUFACTURING COMPANY, RECEIVING TUBE DIVISION
 NEWTON • CHICAGO • ATLANTA • LOS ANGELES



RAYTHEON MANUFACTURES TELEVISION AND RADIO TUBES, INDUSTRIAL AND POWER TUBES, TELEVISION AND RADIO SETS, GERMANIUM PRODUCTS, DIATHERMY EQUIPMENT, ELECTRONIC COOKERS, ELECTRONIC MARINE EQUIPMENT, ELECTRONIC DUPLICATORS, INDUSTRIAL EQUIPMENT, ULTRASONIC MACHINE TOOLS AND ELECTRONIC TUBES, SONAR, RADAR AND COMMUNICATIONS EQUIPMENT FOR THE UNITED STATES GOVERNMENT

Raytheon Is Telling Your Side of the Story to over

25,000,000 Readers of LIFE

The September 21st issue of LIFE will carry the full page, two color advertisement pictured above, telling your side of the Radio-TV Service story to LIFE'S vast audience. We gladly run this advertisement to help you combat the unjust attacks that have been made on

your profession and to give the public a true picture of the really good job you are doing. It's our way of saying "thank you" for your loyalty to *Raytheon Radio and Television Tubes*. We assure you their quality and performance will continue to meet your most exacting requirements.



Excellence in Electronics

RAYTHEON MANUFACTURING COMPANY

Receiving Tube Division

Newton, Mass., Chicago, Ill., Atlanta, Ga., Los Angeles, Calif.

RAYTHEON MAKES ALL THESE:

RECEIVING AND PICTURE TUBES • RELIABLE SUBMINIATURE AND MINIATURE TUBES • GERMANIUM DIODES AND TRANSISTORS • NUCLEONIC TUBES • MICROWAVE TUBES

RADIO & TELEVISION NEWS

*Compare these features
with any oscilloscope*

TRIPLET

3441

- **Vertical Sensitivity,**
10 MV with 2 MC band width.
4 MC band width at 20 MV.
- **Vertical Amplifier.**
Response usable beyond 4 MC.
Shows a 300 KC square
wave with no distortion.
- **Direct reading peak to peak
voltmeter** included, with
eight ranges.
- **Vertical reversing switch** for
changing polarity—wave form
shows in conventional manner.
- **Linear Time Base,** 10 cps to 60
KC seconds linear available
at panel.
- **Dual control** for perfect
focus over entire screen.
- **Phone jack on front panel**
connected to output or vertical
amplifier, so you can hear
as you see.

For this great combination
of service values, see this
oscilloscope with all the extra
features at your distributor's.



and now Compare Quality per Dollar

USA DEALER NET \$199.50

TRIPLET ELECTRICAL INSTRUMENT CO., BLUFFTON, OHIO

TRIPLET

3 New Electrical Advances!

CHANNEL MASTER'S all-new UHF BOW-FLECTOR

model no. 408

The highest gain Bow and Screen antenna ever developed — single or stacked!

1. **Enlarged Reflecting Screen.** 53% more reflecting area — higher, flatter gain level.
2. **Full-Wave Spacing** of stacked antennas. Provides highest stacking gain ever obtained in an antenna of this type.
3. **2-Stage Stacking Transformers** for broad-band impedance match. Delivers high stacking gain over entire UHF band.

New Mechanical Features


- Deep-embossed "rigidized" aluminum dipoles.
- Snap-in assembly. No U-Bolts.
- High-impact molded insulator.

"Free-Space" terminals that prevent picture dim-out caused by the accumulation of dirt, ice or rainwater between antenna terminals.



Only 20 seconds to install!

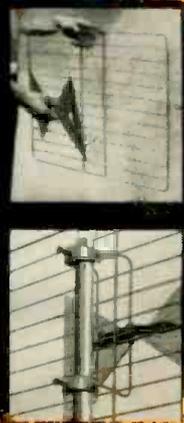
Just snap Bow into Screen, then fasten entire assembly to mast with Channel Master's exclusive "SPEED-NUTS." The antenna cannot move, twist, flutter, or vibrate! The light-weight Bow Flector is the most rugged, fastest-installing antenna of its type.




to 12 1/2 DB stacked

to 10 DB single

Terrific gain!

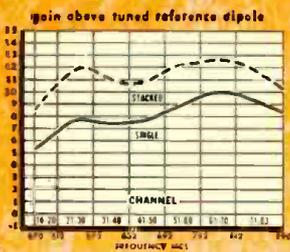

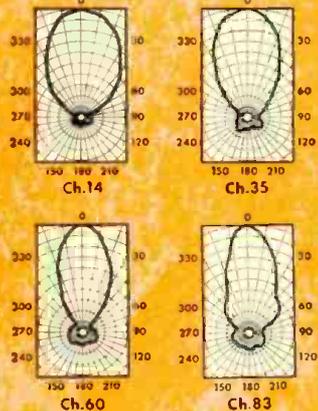Horizontal Polar Patterns (Relative Voltage)



One of 5 Great New Channel Master Products For Fall!

CHANNEL MASTER CORP.

ELLENVILLE, N. Y.



Ask your Channel Master distributor for complete technical literature.

You've never seen a mast like it!

CHANNEL MASTER'S


All-new

STRATO-MATIC

TELESCOPING MAST

for antenna installations
that are

- easier • faster
- safer

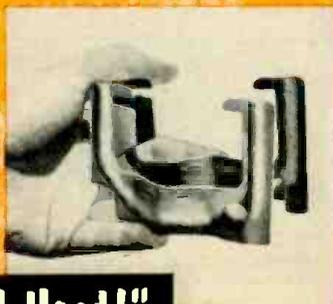

Featuring the Amazing "Third Hand!"

— an automatic, removable locking device that actually acts as your "third hand," holds mast sections up when you let go! The Third Hand converts each guy ring, in turn, into a "safety lock." This permits you to raise sections freely, using only one hand. And . . . sections cannot slide down when you let go.

Automatic Mast Extension

The Step-Up Key, inserted through the bottom of the mast tubing, automatically extends each mast section 6 inches. Mast sections are kept partially extended even after mast is placed in vertical position — without using hardware or locking bolts!

World's Finest Mast Protection!

16-Gauge Mast
HOT-DIP GALVANIZED

Most permanent type of mast corrosion protection available today. Sections are immersed in cauldron of molten zinc, until a thick layer of pure zinc is fused to inner and outer surfaces — so thick it actually adds to the weight of the mast; gives long-term protection!

ZINC IS SELF-HEALING!

When the protective zinc coating is scratched or broken, the surrounding zinc actually goes to work to "heal" the wound. Thus, the base metal is automatically protected against damage due to installation or handling. The only coating with this ability.


18-Gauge Mast
HEAVY ZINC ELECTRO-PLATING

Heavy layer of bright zinc, exceeding Army-Navy specifications, provides effective long-lasting protection against corrosion elements. A chromate dip adds brightness; increases corrosion resistance. The strongest, most durable protection jacket of its type.

One of 5
Great New
Channel Master
Products
For Fall!



Inter-Locked Sections

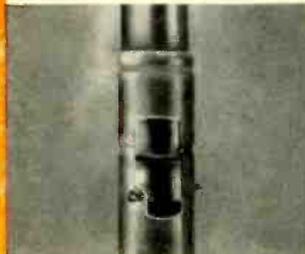

Safety Rings prevent sections from pulling out of each other. Notches in sections engage bolt — no twisting.

No Hidden Holes



Step-Up Key automatically extends mast sections high enough to provide easy access to bolt holes. You don't have to pull up next section to insert bolt!

Model No.		Sections	Lengths	Weights	
16-Gauge	18-Gauge			16-Gauge	18-Gauge
1620	1820	A, B	20'	16 lb.	13 lb.
1630	1830	A, B, C	30'	26 lb.	22 lb.
1640	1840	A, B, C, D	40'	38 lb.	33 lb.
1650	1850	A, B, C, D, E	50'	52 lb.	48 lb.

CHANNEL MASTER CORP. ELLENVILLE, N. Y.

Ask your Channel Master distributor for complete technical literature.






15 or 12 in.
Bass Reflex Cabinet

High Fidelity at moderate cost*

Every essential for superb tone— $\frac{1}{2}$ " wood sides, $\frac{1}{2}$ " acoustic lining, 4.3 cu. ft. capacity, heavy construction (wt. 31 lbs).

But moderate cost with leatherette covered sides. Hand rubbed solid mahogany or blonde hardwood around front adds genuine richness. Compare it with any other and see for yourself. Only \$45.00 net (slightly higher west of Rockies).

Send for **FREE Folder**

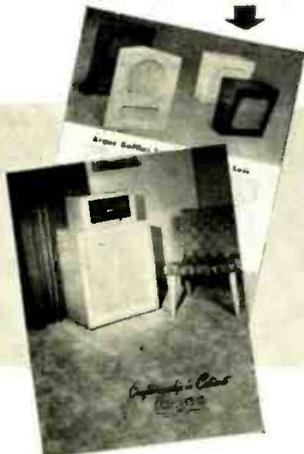

*By makers of famous TV Tube Caddy®

Argos
PRODUCTS COMPANY
310 MAIN STREET • GENOA, ILLINOIS

Spot Radio News

* Presenting latest information on the Radio Industry.

By RADIO & TELEVISION NEWS'
WASHINGTON EDITOR

THE COLOR AGE, heralded about two years ago after winking at destiny for years, and then spun back to oblivion, is now being boomed for a new glittering, golden debut before the year is out. The approval of two encyclopedic documents, petitioning the government for approval of compatible standards will signal the epic moment. At this writing one such monumental text is being studied by the Commission and another will be on the desks in Washington, just as this column goes to press. The former, prepared by RCA, represents an application from a manufacturer; the latter, a brief from industry in general, as members of the National Television Systems Committee.

The standards proposed in the first petition were described as technical signal specifications approved by outstanding engineers and scientists of the radio and television industry, including members of the petitioner's staffs, through the NTSC. In supporting the

plea for an OK, Mr. Sarnoff declared that his company and its broadcast unit are prepared to invest as much as \$15-million during color TV's introductory year to establish this new service on a solid foundation. Defending the early transmittal of the brief, before NTSC filed, attorneys for the company said that such a move was necessary in view of the barrage of statements accusing some of holding back color, commitments made in the Spring to the chairman of the Senate Interstate and Foreign Commerce Committee that a petition would be filed within six months or sooner if a system were ready, and a question of public law, it being doubted if the NTSC, as a body, had the legal authority to appear before the Commission with its standards. The latter point was argued by many who cited the standards evolved by the first NTSC group for black and white and approved by Washington; in that instance, it was admitted that the Commission had sought such standards and

NEW TV GRANTS SINCE FREEZE LIFT

Continuing the listing of construction permits granted by FCC since lifting of freeze. Additional stations will be carried next month.

STATE	CITY	CALL**	CHANNEL	FREQUENCY (mc.)	POWER* (Video)
Arizona	Phoenix	KOOL-TV	10	192-198	316
"	Phoenix	KOY-TV	10 (sharing air time with)	192-198	316
Arkansas	Little Rock	KARK-TV	4	82-88	100
"	Pine Bluff	7	174-180	24.5
California	Bakersfield	KERO-TV	10	192-198	11.7
"	San Jose	48	674-680	107
Connecticut	New Haven	WELI†	59	740-746	19.5
"	Stamford	27	548-554	19.48
Florida	Jacksonville	WJHP-TV	36	602-608	120
"	Pensacola	WEAR-TV	3	60-66	47.9
Illinois	Quincy	WGEM-TV	10	192-198	316
Indiana	Elkhart	WTRC-TV	52	698-704	215
Kansas	Topeka	WIBW-TV	13	210-216	95.5
Mississippi	Meridian	WTOK†	11	198-204	31
Missouri	Kansas City	KMBC-TV†	9	186-192	316
"	Kansas City	WHB-TV†	9 (sharing air time with)	186-192	316
"	Kansas City	KCMO-TV	5	76-82	100
New Mexico	Albuquerque	KOAT-TV	7	174-180	22.9
Ohio	Cleveland	WERE-TV	65	776-782	204
South Carolina	Camden	WACA-TV	14	470-476	78
Texas	Houston	KXYZ-TV	29	560-566	1000
"	Marshall	16	482-488	18.6
West Virginia	Beckley	21	512-518	19.5
Wisconsin	Milwaukee	WOKY-TV	19	500-506	17.4

*ERP = (effective radiated power, kw.).

** = Call letters to be announced

† = Temporary call letters.

**GOLD-COLORED ANTENNA...
 FULL-YEAR GUARANTEE AGAINST
 RUST AND CORROSION...
 ADVANCED HIGH-GAIN ANTI-VIBRATION
 DESIGN...**

These revolutionary features are your identification of the new JFD "Gold Shield" UHF antennas—introducing to the TV antenna field an unprecedented consumer attraction.



MODEL
UHF 902 PARA-STAK \$18.95 LIST



MODEL
UHF 400 GOLDEN MAXI-COR \$14.95 LIST




MODEL
UHF 900 PARA-BOW \$14.95 LIST



MODEL
UHF 633 GOLDEN MINI-COR WITH FREE JUMPERS \$7.50 LIST



MODEL
UHF 411 GOLDEN BRIDGE \$11.75 LIST

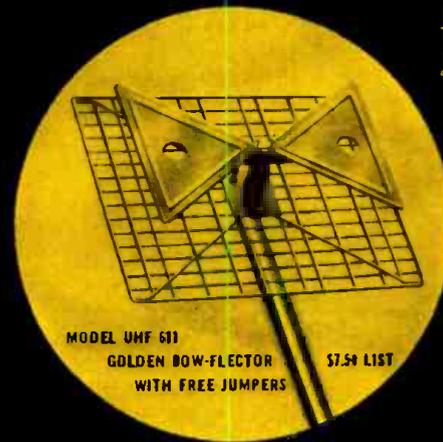

MODEL UHF 611
GOLDEN BOW-FLECTOR WITH FREE JUMPERS \$7.50 LIST



MODEL UHF 200 GOLDEN YAGI \$5.50 LIST
WITH FREE JUMPERS



Here's what the JFD "Gold Shield" UHF antennas offer you: An individual antenna for each installation requirement, ranging from the "Golden Para-stak" with 15 DB. gain and 20.5 DB. front-to-back ratio for fringe areas to the "Golden bow-flector" with 6.5 DB. gain and 10 DB. front-to-back ratio for local signal areas. Add "Bronzidite" protective plating, and you have the antennas for greater UHF profits—without call-backs. See them at your jobber.

JFD MANUFACTURING CO., INC.

BROOKLYN 4, N.Y.

World's largest manufacturer of TV antennas and accessories

B R O N Z I D I T E



"Of the very best!"

—HIGH FIDELITY MAGAZINE

FISHER

SERIES "50"

■ It is only natural that more than one manufacturer will claim *his* product is the best. For that reason it remains for *you* to be the judge. We say—*demand the specs.* Then check workmanship, performance and beauty of appearance. If you do all these things, the answer will inevitably be . . . THE FISHER SERIES "50." There is no finer made.

THE FISHER **Master Audio Control** MODEL 50-C

■ "One of the finest units yet offered to the enthusiast or audio engineer." —*Radio and TV News.* Can be used with *any* amplifier. IM distortion virtually unmeasurable. Complete, professional equalization settings and tone controls; genuine F-M loudness control; five inputs, five independent input level controls, two cathode follower outputs. Self-powered.

Chassis, \$89.50 • With blonde or dark cabinet, \$97.50

THE FISHER **FM-AM Tuner** MODEL 50-R

■ Features *extreme sensitivity* (1.5 mv for 20 db of quieting); *low distortion* (less than 0.04% for 1 volt output); *low hum* (more than 100 db below 2 volts output.) Armstrong system, *adjustable AFC* with switch, *adjustable AM selectivity*, separate FM and AM front ends (shock-mounted), cathode follower output, fully shielded, aluminum chassis, self-powered. \$164.50

THE FISHER **50-Watt Amplifier** MODEL 50-A

■ Truly the world's finest all-triode amplifier, yet moderately priced. A man's size unit! Less than 1% distortion at 50 watts (.08% at 10 watts.) IM distortion below 2% at 50 watts. Uniform response within .1 db from 20 to 20,000 cycles; 1 db. 5 to 100,000 cycles. Hum and noise more than 96 db below full output. Quality components throughout. \$159.50

Prices slightly higher west of the Rockies

WRITE TODAY FOR COMPLETE SPECIFICATIONS

FISHER RADIO CORPORATION • 39 EAST 47th STREET • N. Y.

asked industry to prepare them, and actually no general petition was involved.

Those at the helm of NTSC were deeply concerned with the prior filing, indicating that simultaneous or general petitioning would have been more prudent. Accompanying letters, particularly those explaining technicalities in the makeup and operation of the system, and employing a company identity, instead of NTSC, in referring to the system angered the industry color system headman. In one sizzling comment, the NTSC chairman declared . . . "such claims" . . . could result in . . . "controversy" . . . and it would be best if . . . "such claims were not made in the future, at least until the NTSC finishes its job."

The color system detailed in the company brief was said to meet all of the criteria established by the Commission for a satisfactory operation. Public reaction tests, for example, were cited as confirming the fact that the system offered a picture with a high degree of color fidelity, adequate apparent definition, good picture texture and was not marred by such defects as misregistration, line crawl, jitter, or unduly prominent dot or other structure. In a qualifying statement on picture texture, the brief pointed out that there are a number of factors that enter into the broad classification of this characteristic. In the system under consideration, it was noted, there are the same number of lines in the picture as in standard black and white TV, and the line structure is the same. Since this line structure has been satisfactory in the present service, there is no reason to believe that it will not be satisfactory for color, the petition continued. The diameter of an individual dot in the 16-inch tri-color picture tube was said to be about the same as about 70 per-cent of the thickness of a scanning line. Since lines are not usually visible at normal viewing distances, the individual red, green, and blue phosphors were described as even less visible.

Some minor misregistration as may, from time to time, be perceptible in present color receivers, will not, it was indicated, interfere with enjoyment of color pictures, and in addition is not a system limitation. In a comprehensive report on the subject, the petition reviewed why such misregistration might occur. In the camera used, although it is necessary to register accurately three scanning rasters, an unusual amount of success has been attained. Test pictures have been made by scanning a line and RTMA pattern; misregistration would be indicated by a thickening or multiplicity of some lines near the outer extremities of the pictures. Essentially no deleterious effects due to misregistration were observed, it was noted, although there may have been a slight tendency for a thickening of some lines near the outer edges, but there were no signs of multiple lines. In a questionnaire, it was


(Continued on page 170)

RADIO-ELECTRONIC *Engineering* SECTION

Reg. U. S. Pat. Off.

**RADIO &
TELEVISION
NEWS**

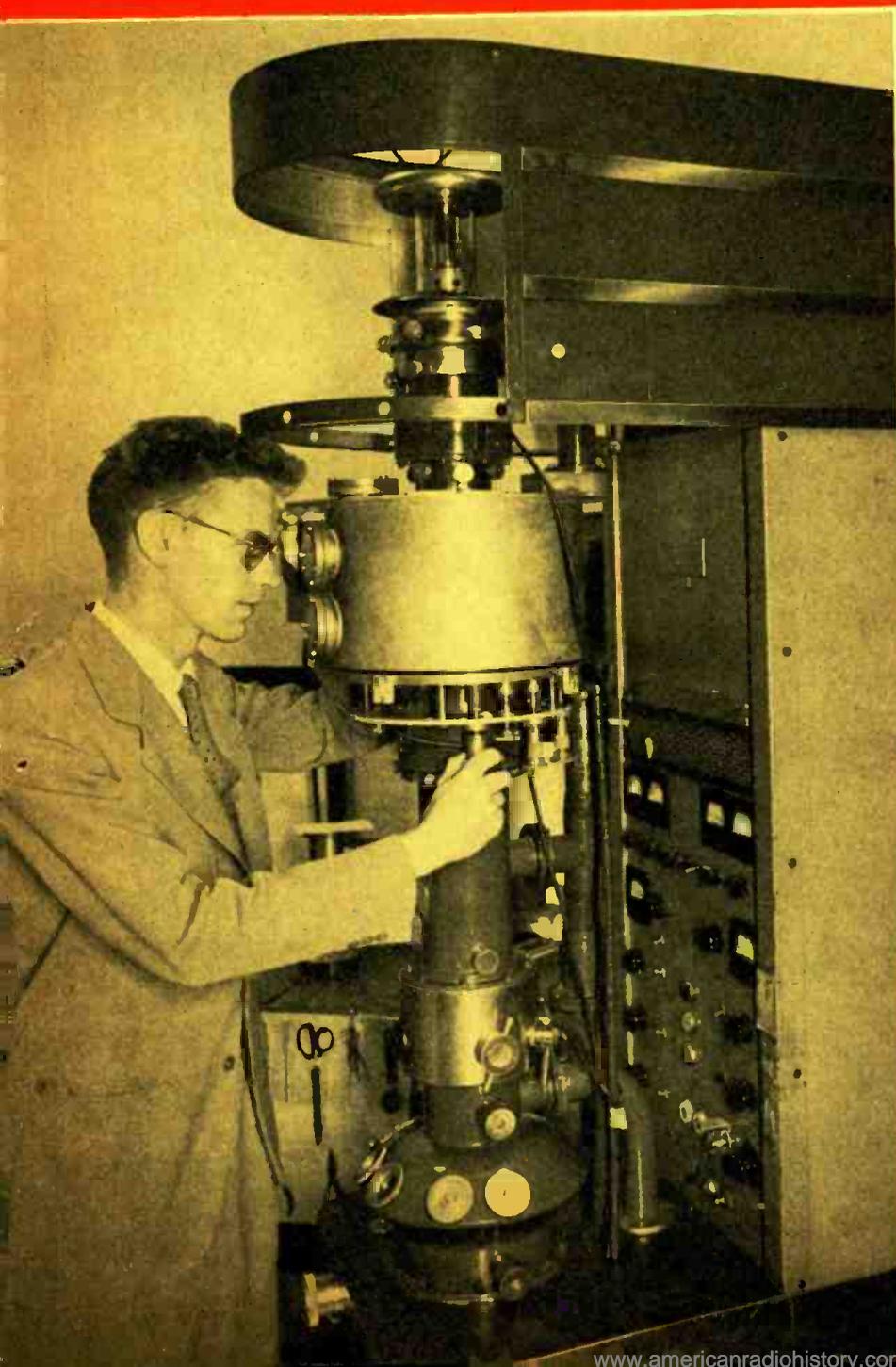TELEVISION • RADAR • ELECTRONICS • RESEARCH • COMMUNICATIONS • MICROWAVES



SEPTEMBER, 1953

ACCURATE
R.F. POWER MEASUREMENTS
3

TRANSISTOR CHARACTERISTICS
7

BALANCED
'CRYSTAL-DIODE MODULATOR'
10

A FLEXIBLE PLATED CIRCUIT
12

VISUAL PROOF OF PERFORMANCE
MEASUREMENTS
14

DEPARTMENTS

NEWS, BRIEFS	18
NEW PRODUCTS	20
LOOKING AT TUBES	22
PERSONALS	24
NEW LITERATURE	26
NEW TUBES	28
TECHNICAL BOOKS	30
CALENDAR	31



Copyright, 1953, by Ziff-Davis Publishing Company
RADIO-ELECTRONIC ENGINEERING is published each month as a special section in a limited number of copies of RADIO & TELEVISION NEWS, by the Ziff-Davis Publishing Company, 300 Madison Avenue, New York 17, N. Y.

Edited by H. S. RENNE
and the Radio & Television News Staff

In the National Bureau of Standards electron-beam interferometer, diffraction from extremely thin crystals is used to split and recombine electron beams. A conventional electron microscope is used for viewing the resulting interference fringe phenomena.



NEW "M" TYPE TOROIDS Maximum Q Minimum Size













UTC Permalloy Dust Toroids have been the standard of the industry for over 15 years. The MQ series of coils provide the highest Q factor in their class (see curves below), with miniaturized dimensions. All units are hermetically sealed to MIL-T-27 Specifications.

The stability is excellent. For the MQE-7 the inductance change is less than 1% for voltages from .1 to 3 volts. The MQA-13 change is less than 1% for applied voltages from .1 to 20 volts. The MQB-5 change is less than 1% for applied voltages from .1 to 50 volts. DC is permissible through the coil (values listed below). Inductance is virtually independent of frequency temperature and vibration.

Hum pickup is extremely low due to the toroidal winding structure, with windings uniformly spread over the core. The case is of high permeability, affording additional shielding such that close spacing of units can be effected, the coupling attenuation being approximately 80 DB.

Other values of Inductance than those listed are available on special order at the price of the next higher listed value.

TYPICAL Q CURVES

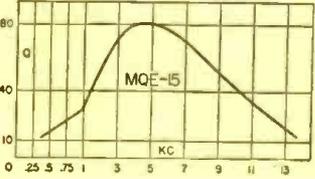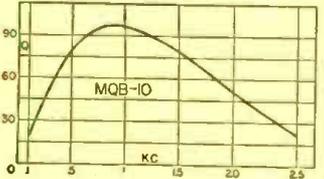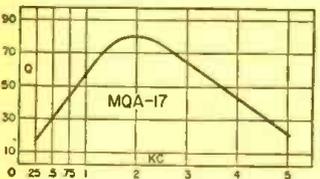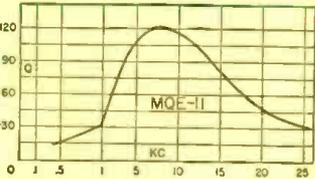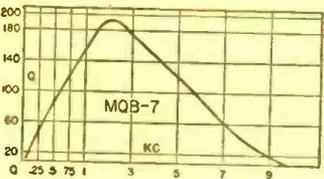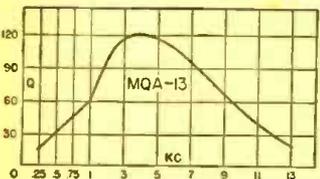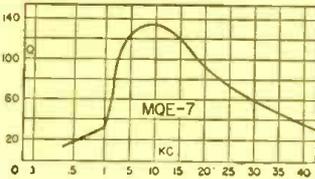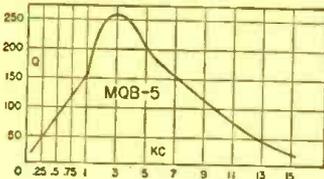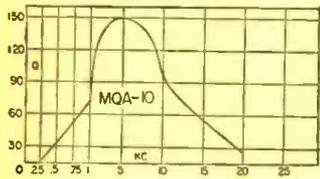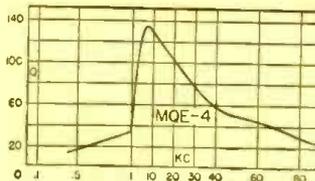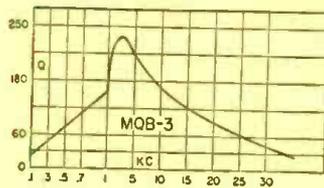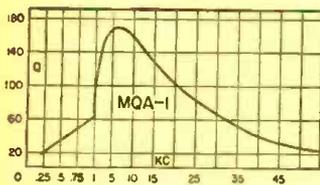

MQA TYPES

Type No.	Inductance	*DC Max.
MQA-1	7 mhy.	250
MQA-2	12 mhy.	200
MQA-3	20 mhy.	150
MQA-4	30 mhy.	125
MQA-5	50 mhy.	100
MQA-6	70 mhy.	80
MQA-7	120 mhy.	60
MQA-8	.2 hy.	50
MQA-9	.3 hy.	40
MQA-10	.5 hy.	30
MQA-11	.7 hy.	25
MQA-12	1 hy.	20
MQA-13	1.5 hy.	17
MQA-14	2.5 hy.	13
MQA-15	4 hy.	10
MQA-16	6 hy.	9
MQA-17	10 hy.	7
MQA-18	15 hy.	5
MQA-19	22 hy.	4

MQB TYPES

Type No.	Inductance	*DC Max.
MQB-1	10 mhy.	400
MQB-2	30 mhy.	250
MQB-3	70 mhy.	170
MQB-4	120 mhy.	120
MQB-5	.5 hy.	60
MQB-6	1 hy.	40
MQB-7	2 hy.	30
MQB-8	3.5 hy.	22
MQB-9	7.5 hy.	16
MQB-10	12 hy.	11
MQB-11	18 hy.	9
MQB-12	25 hy.	8

MQE TYPES

Type No.	Inductance	*DC Max.
MQE-1	7 mhy.	135
MQE-2	12 mhy.	100
MQE-3	20 mhy.	80
MQE-4	30 mhy.	65
MQE-5	50 mhy.	50
MQE-6	70 mhy.	40
MQE-7	100 mhy.	35
MQE-8	150 mhy.	30
MQE-9	.25 hy.	22
MQE-10	.4 hy.	17
MQE-11	.6 hy.	14
MQE-12	.9 hy.	12
MQE-13	1.5 hy.	9
MQE-14	2 hy.	8
MQE-15	2.8 hy.	7.2




MQE CASE

Length 1 1/16"
Width 1/2"
Height 17/32"
Unit Weight 1.5 oz.



MQA CASE

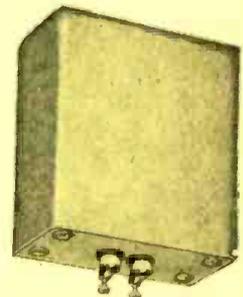Length 1 1/32"
Width 1 1/16"
Height 1 23/32"
Unit Weight 4 oz.



MQB CASE

Length 2 9/16"
Width 1 13/16"
Height 2 13/16"
Unit Weight 14 oz.


*This value of D.C. (MA) will drop the coil inductance 5%. Values of D.C. below this will show proportionately (linear) less inductance drop. For example, MQE-1 will drop 1/2% in L with 13.5 MA.

United Transformer Co.
150 VARICK STREET NEW YORK 13, N. Y.

EXPORT DIVISION: 13 EAST 40th STREET, NEW YORK 16, N. Y. CARLES MARLAR

www.americanradiohistory.com

ACCURATE R.F. POWER MEASUREMENTS

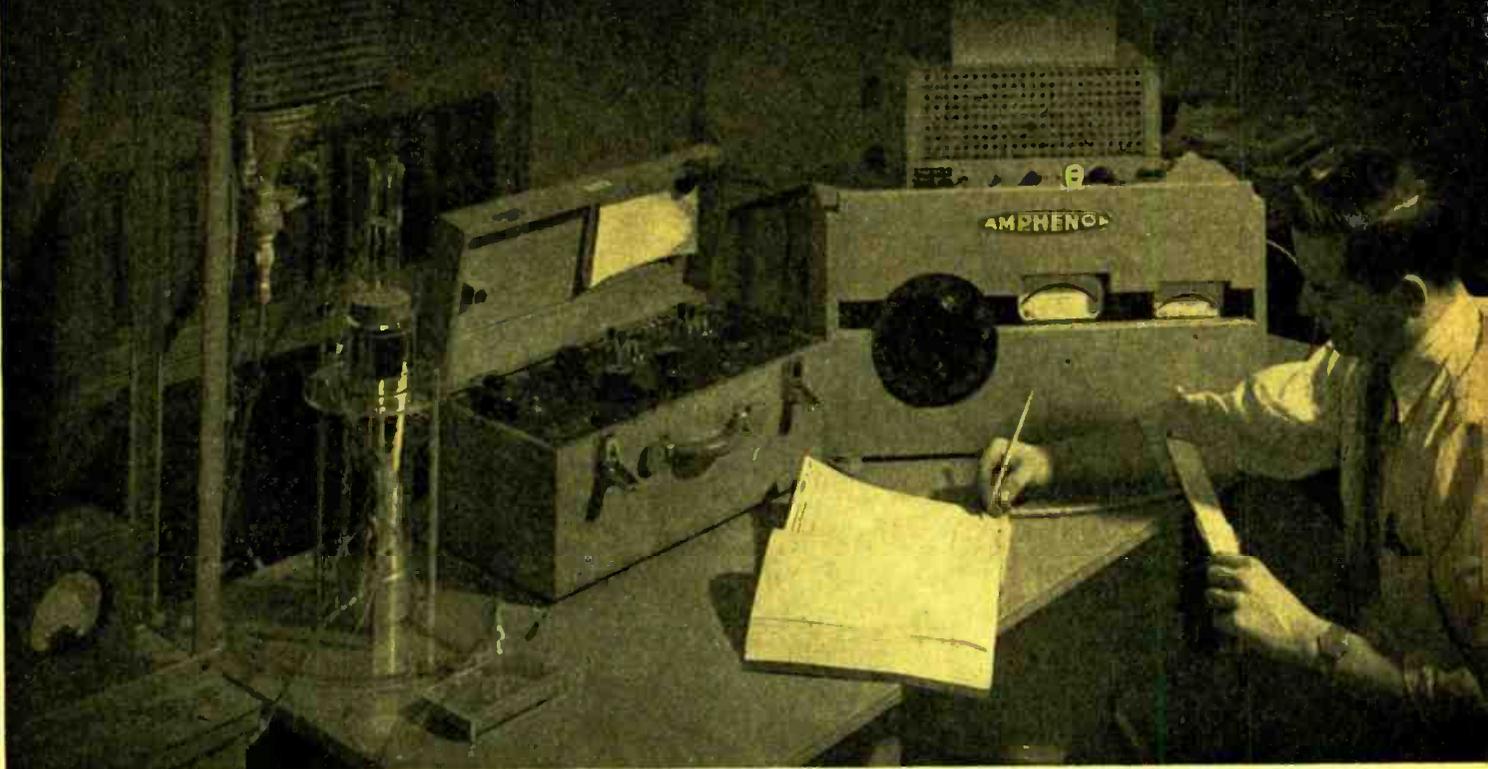

Setup for calorimetric calibration of water load and for making r.f. power measurements.

MEASUREMENT of radio frequency power in the range of 2 to 5000 watts is often accomplished by means of the temperature-rise or calorimetric method. Both input (through) and output (absorbed) power may be conveniently and accurately measured by this method, provided that proper impedance matching of the calorimeter to the component under test has been observed and that an accurate calibration of the water load exists. Need for the development to be discussed here arose in the course of measuring the r.f. power-handling capacities of coaxial cables having polyethylene, Teflon, and liquid dielectrics, and in the measurement of other components developed for airborne applications in the current miniaturization program. This article presents the results of an investigation by means of which a commercially available r.f. wattmeter load has been converted into a sensitive, closed-system calorimeter used for accurate r.f. power measurements up to 5000 watts.

Existing methods for measuring r.f. power have in common the conversion of r.f. energy into heat in some type of resistive material in which the effects of the dissipated heat are compared to equal effects produced by an easily measured a.c. or d.c. power

source. These existing methods may be classified as follows:

1. *Resistance change*—bolometers and thermistors having a range from one microwatt to several milliwatts
2. *Light*—lamp loads having a range from approximately 200 mw. to 200 watts
3. *Temperature rise*—calorimetric loads having a range from approximately 2 to 5000 watts

As the calorimetric or water-load method primarily measures output power, the load is usually inserted at the terminating end of the component being measured. Power is absorbed in a matching resistor which, in turn, is immersed in a circulating liquid cooling bath. The heat absorbed by the liquid is equal to the heat dissipated in the terminating resistor, and thus the rise in temperature of the liquid is a measure of power being dissipated.

If water is utilized as the circulating liquid, the power absorbed may be represented ideally by the equation:

$$P = 0.307 Wc (\Delta t) \dots\dots\dots (1)$$

where:

P = power absorbed = power dissipated, watts

W = weight rate of water flow, lb.-hr.⁻¹

c = specific heat of water, B.-lb.⁻¹ °F.⁻¹

Δt = temperature rise of water, °F

Although Eq. (1) is exact for the ideal case, where all the heat is absorbed by the circulating water, correction factors must be added to compensate for the heat losses due to radiation and convection from the calorimeter to the surrounding atmosphere. Deviations from the linear relationship of the dissipated power and the temperature rise of the cooling water are therefore caused by differences between the cooling water temperature and the

By **R. M. SORIA**, Director of Research, and
J. G. KRISILAS, Senior Research Mech. Engr.
 American Phenolic Corporation

Calorimetric method is used to measure r.f. power output and to calibrate an input power indicator.

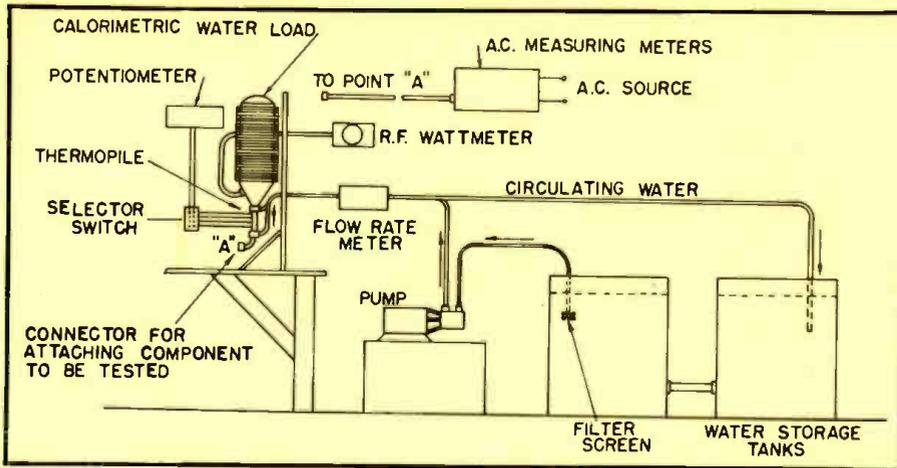


Fig. 1. Schematic diagram of the calorimetric equipment layout.

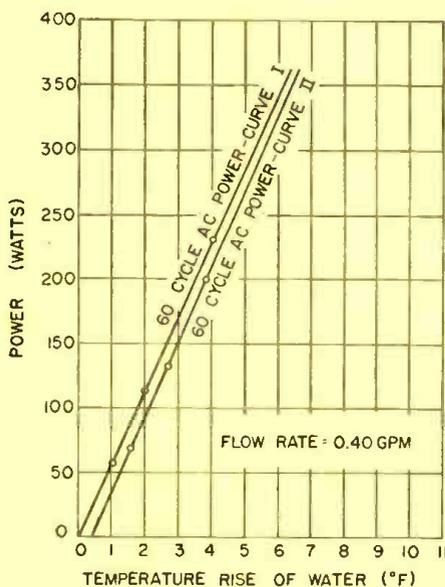


Fig. 2. Calorimeter calibration curves.

environment air temperature. If the cooling temperature is greater than the ambient temperature, the indicated temperature rise of the circulating water will be less than in the ideal case because of the heat losses to the environment caused by convection and radiation throughout the flow length

between the hot and cold junctions of the thermopile temperature indicator; and subsequent calculations of the dissipated power will thus be in error. Cooling water at a temperature lower than the ambient will cause similar errors. Optimum results are obtained when the cooling water is initially at room temperature and the temperature increases by only a few degrees as the water flows through the calorimeter.

The above calculations and the inherent errors may be circumvented by substituting a.c. power in calibrating the calorimeter. The temperature rise of the circulating water is first noted when r.f. power is being dissipated by the water load. The r.f. power source is then removed and the same temperature rise is produced in the circulating water by the dissipation of a.c. power. Accurate measurements of the flow rates are not necessary so long as the flow remains constant during both the r.f. and a.c. test runs.

Since the flow rate, the inlet temperature of the circulating water, and the temperature of the environment air are held constant for both cases, the a.c. power dissipated by the calorimetric load is equal to the r.f. power dissipated from the resistor for the

same cooling water temperature rise. A calibration curve may then be obtained of the power dissipated vs. the temperature rise of the circulating water.

As it is a requirement in the ideal case to have both the r.f. and a.c. resistors identical in physical dimensions and similarly located in the calorimeter, use of the commercially available r.f. water load in the power substitution method of measuring r.f. power eliminates a common source of error present in most laboratory calorimeters. For reasons of impedance matching, the a.c. calibrating resistor is mounted—in the usual laboratory calorimeter—externally to the r.f. portion of the calorimeter, so that identical heat transfer conditions are not available for both the r.f. and a.c. tests. Therefore, the cooling water temperature will increase in two unequal stages as it flows through the a.c. and r.f. portions of the system, causing a corresponding unequal cooling water temperature difference to be indicated for both the a.c. and r.f. test runs.


Experimental Installation


Two systems were designed and tested in the development of the calorimetric water load, one system permitting the use of the calorimetric equation for calculating the power values, the second and more useful system utilizing the power substitution method for obtaining r.f. power values. The latter system is described below.

A Model 67 Termaline wattmeter-load, manufactured by *Bird Electronic Corporation*, was adapted and calibrated for use as a calibrating calorimeter. The wattmeter has an operating range of 0-2500 watts arranged in three steps of 0-100, -500, and -2500 watts at a frequency range of from 30-500 mc.; this range can be extended to 1000 mc. with rapidly decreasing accuracy. The load can be air-cooled up to 200 watts and water-cooled for the higher power levels. Power being measured is absorbed in a terminating carbon-film-on-ceramic resistor enclosed in a bath of oil dielectric which transfers the heat from the terminating resistor to the water flowing in the coils immersed in the oil dielectric. Absorption of the power results in a temperature rise in the water flowing through the wattmeter-load.

The test installation, shown schematically in Fig. 1, consisted of the wattmeter-load, differential thermopile installation, a special a.c. connector to the wattmeter-load, an a.c. wattmeter and power source, and circulating cooling water contained in a closed system consisting of two 55-gallon containers with a positive displacement pump to maintain a constant flow rate.

Fig. 3. Sketches showing two different thermopile constructions.

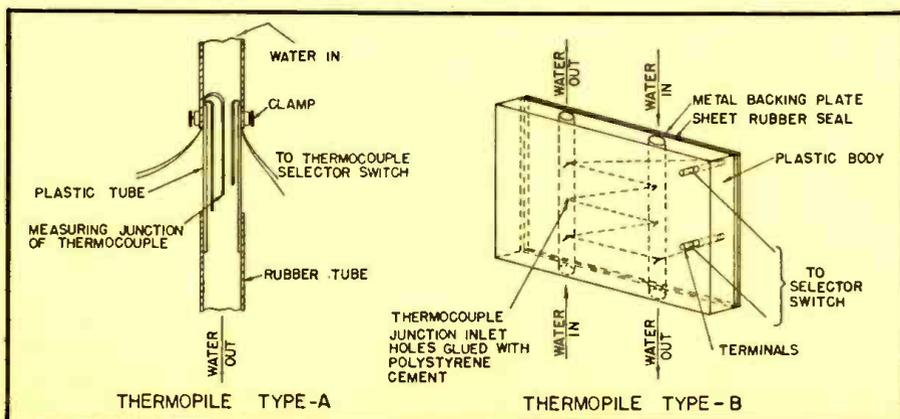

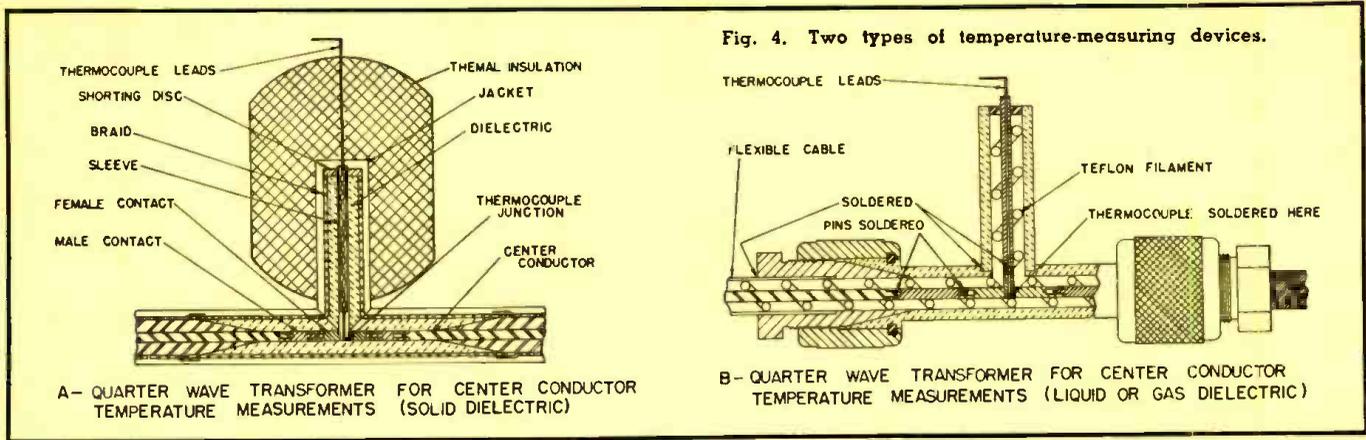

Two types of thermopile assemblies were developed for use with the calorimetric load to measure the cooling water temperature rise. In both of these assemblies, it was necessary to introduce the thermopiles into the inlet and outlet water streams and to make these points of entry leakproof against pressures of approximately 100 psi.

Thermopile Type A, shown in Fig. 3, was developed to prevent loss of heat from the flowing water while measuring the water temperature. Each tube contains a thermocouple for accurately measuring the water temperature as well as the thermopile for measuring the temperature differential between the two water streams. The thermopile is also used as a check on the thermocouple measurements. Since the thermocouple wire provides a path for heat losses, one to two inches of thermocouple wire should be enclosed in the water stream to insure accurate measurement of the true water temperature. Use of thermopile Type A makes possible utilization of Eq. (1) for calculating the power absorbed, provided that the environment temperature is close to the mean water temperature.

Thermopile Type B of Fig. 3 was developed for use when the calorimeter is being calibrated by the substitution of a.c. power. This method of construc-

tion is more rugged, the apparatus is easier to assemble, and it can withstand higher water pressures than thermopile Type A. The bulk of the thermopile body causes heat losses from the flowing water and thus indicates slightly lower temperature differences than those calculated from Eq. (1). However, it is not essential to measure the true water temperature since the temperature differences are correlated by means of the substituted a.c. power.

To insure a constant flow rate of water through the calorimeter, a constant-pressure or constant-head water supply is necessary. This may be attained by means of an open or a closed system.

A closed system was designed in which a positive displacement pump, having a capacity of 2 gpm and driven by a 1/3-hp. electric motor, was utilized to circulate the cooling water through the calorimeter. Various constant flow rates were obtained by adjustment of a valve while the flow rate was indicated rapidly and conveniently by a *Fischer and Porter* "Flowrater" meter. As a check on accuracy, however, the flow rates were also measured with a stop watch and container of known volume. Sufficient capacity was available with two 55-gallon drums coupled together to permit the water to cool to room tem-

perature before being recirculated through the calorimeter.

The a.c. calibrating installation consisted of a constant a.c. power source and an ammeter, wattmeter and variable resistance, which were assembled into a self-contained unit for ease in making the test measurements.

Experimental Results

The commercially available water load was calibrated by the a.c. power substitution method and a series of measurements was made to determine its performance as a calorimeter. Calibration test runs of the calorimeter with thermopile Type B are presented in Fig. 5; the a.c. power input to the calorimetric load is plotted as a function of the temperature rise in the circulating water with the various flow rates as parameters. Theoretical curves, calculated from Eq. (1), are also presented for comparison. The experimental results show that a greater temperature drop can be obtained due to the heat losses from thermopile Type B. The experimental curves of Fig. 5 were checked after the calorimetric load was in operation for a period of time, and these points are indicated by the symbol "B". It may be seen that excellent reliability and repeatability have been attained.

Fig. 5. Calibration of calorimetric water load at various flow rates, using thermopile Type B (Fig. 3). Theoretical and actual curves are given for three different water flow rates.


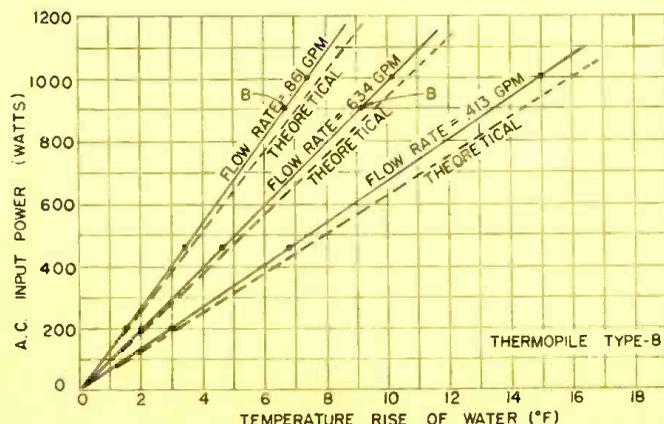


Fig. 6. Calibration of quarter-wave transformer by the braid temperature comparison method.

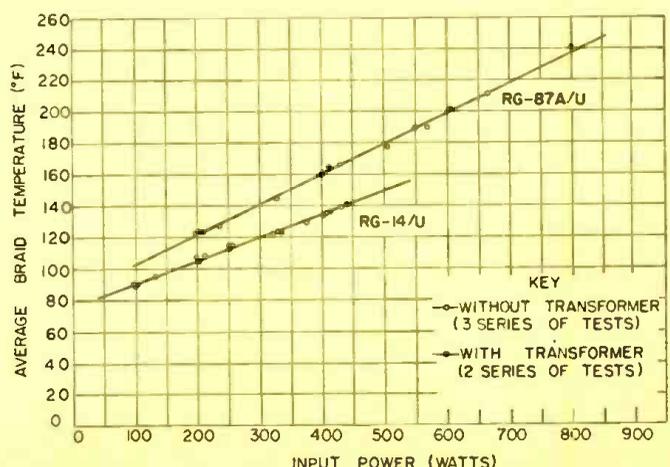


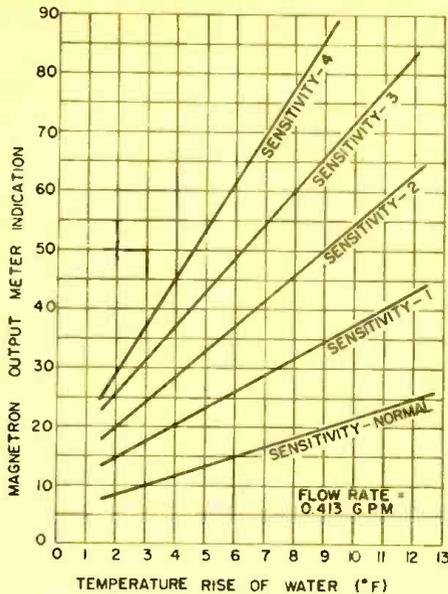


Fig. 7. Magnetron output meter variation with water temperature rise.

A series of tests was also made utilizing thermopile Type A in measuring the cooling water temperature difference, the results of which are presented in Fig. 2. Curve I is a plot of the power vs. the temperature difference as calculated from Eq. (1) for a flow rate of 0.40 gpm. The results of these test runs, in which the mean water temperature was equal to the environment air temperature, coincided with theoretical curve I, thus confirming the use of thermopile Type A when the power substitution method is not utilized in the calibration of the calorimeter. Curve II is a plot of the results obtained when the environment air temperature was greater than the mean water temperature. Since the amount of heat absorbed by the water from the environment air is approximately constant over the small temperature range, the effect of the environment air is manifested in an initial displacement of the curve.

It is desirable to obtain the power

Fig. 8. Calibration curve of magnetron input meter indication vs. the true output power.

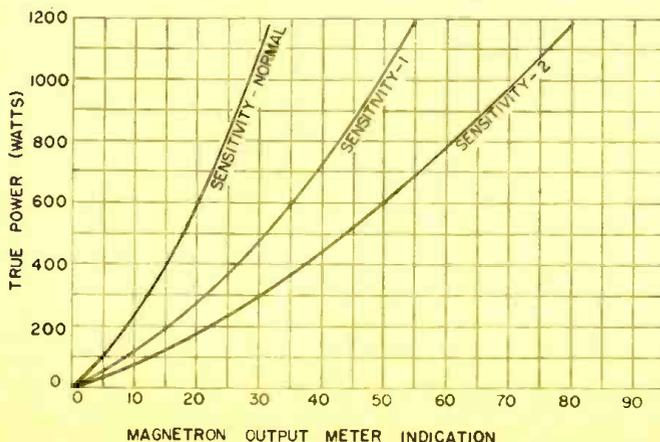

measurements using a flow rate which will give temperature differences of only a few degrees above the ambient temperature, so that heat loss errors to the environment will be kept at a minimum. In addition, the flow rate should be such that slight variations in it will not greatly influence the accuracy of the cooling water temperature difference. Optimum results have been achieved with flow rates maintained between 0.40 and 0.80 gpm.

Quarter-Wave Transformer

In conjunction with measurements of output or absorbed power, various indicating devices may be calibrated by the calorimeter for use as input or through power meters. A quarter-wave transformer with enclosed thermocouple was developed to measure accurately internal temperatures of r.f. components which contain solid, liquid or air dielectrics while transmitting r.f. power, and in addition, to indicate input power when so calibrated with the calorimeter.

This quarter-wave transformer was utilized to isolate electrically the effect of the thermocouple insertion into the component being tested. The condition of electrical similarity was achieved by constructing the transformer exactly like the component being tested. Thermal stability was achieved when necessary by the addition of thermal insulation (in the form of asbestos powder) to prevent heat losses from the quarter-wave stub from becoming greater than the heat losses from the component before the insertion of the transformer.

By assuming that the quarter-wave transformer would act like a cooling fin at the point of insertion into the component, a measure of the additional heat losses was obtained from theoretical calculations. The values of calculated surface temperatures along the quarter-wave stub were confirmed by actual measurements which showed that the transformer insertion would alter the condition of heat transfer and would indicate a lower center conductor temperature when solid and stationary liquid or gaseous dielectrics were utilized. Therefore, for precise center conductor measurements, thermal insulation should be added to the quarter-wave stub to decrease the heat losses to a negligible value. Insulation may be omitted when the

component utilizes a flowing liquid or gas which has a dual role as dielectric and coolant.

Two models of the quarter-wave transformer, developed particularly for the measurement of power-handling capacities of solid and liquid dielectric coaxial cables, are shown in Fig. 4. Similar quarter-wave transformers can be designed for other electronic components.

Two methods exist for the insertion of the particular quarter-wave transformer into the component circuit. The first method consists of custom-fitting the quarter-wave transformer into the component and then reconstructing the assembly to conform to the original, an example of which is shown in Fig. 4A. The other, and more general method, consists of constructing a transformer assembly with connectors on each end, as shown in Fig. 4B, to facilitate its insertion into any component circuit being tested.

The transformer (Fig. 4B) is connected to the center conductor of the component being tested by means of a double female contact having the same dimensions as the component center conductor. The quarter-wave stub, consisting of a brass sleeve 2.25" long, is screwed into the double female contact. The thermocouple (No. 30 AWG wire) is inserted through a 0.028" axial hole in the sleeve and soldered at the junction along the axis of the center conductor. The stub is then assembled exactly like the component in which it is inserted, provision being made for a shorting disc which is screwed to the sleeve and adjusted to the proper quarter-wavelength.

Construction of the quarter-wave transformer may be improved for large-size components by utilizing the center conductor of the component rather than replacing it with the double female contact. In the case of large-diameter coaxial cable, a tapered hole was first drilled through the jacket, braid and dielectric, exposing a small area of the center conductor surface. Using a bottoming tap, the center conductor was then tapped with a 0-80 thread. The vertical sleeve of the transformer was screwed directly into the center conductor of the cable, and the vertical portion of the transformer was then constructed as before. This procedure is especially recommended for power testing at high power levels where unequal thermal expansions of the various component materials may sometimes force the center conductor from the double female contact.

Limitations of space preclude the presentation of the electrical calibrations. It will suffice to state that the quarter-wave transformer is calibrated

(Continued on page 29)

TRANSISTOR CHARACTERISTICS*

By F. M. DUKAT

Raytheon Manufacturing Company

Production variations in the small signal and d.c. parameters of type PNP junction transistors.

THIS ARTICLE concerns the small signal and d.c. parameters of the Raytheon CK721 and CK722 transistors, the distributions of these parameters, and the effect of such distributions in the three amplifier connections. The parameters will be illustrated in the form of graphs which will indicate the spread in parameter values on a group of typical production units.

First of all, it might be well to acknowledge that at the present state of transistor development no manufacturing techniques are known which can control transistor parameters within close limits. Selection after manufacture is necessary. Therefore, if transistors are to be used commercially today, a knowledge of the extent of their variability is very important in order to minimize this variability by suitable circuit design.

Two Raytheon junction types are now available to the military and general trade: the CK721, which can be considered a relatively high grade unit; and the CK722, a medium grade unit which is useful in many applications. The basic difference between the CK721 and the CK722 is one of current amplification, the CK721 having an α of about .95 or greater while the α of the CK722 runs from about .85 to .95.

Distributions of the small signal

parameters and tentative limits, where applicable, are given in Figs. 1 through 7 for 100 units taken from the production line during the last quarter of 1952. It can be expected that both limits and distributions will change as manufacturing processes improve. All measurements except cutoff have been made with a fixed emitter current of 2 ma. d.c. and a collector voltage of -6 volts—an operating point that is not necessarily optimum but which has been selected as a reasonable compromise between small signal and large signal applications.

A distribution for emitter resistance, R_e , in both transistor types is shown in Fig. 1. It appears that in general the CK721 approaches more nearly the theoretical value of 25.9 ohm-ma. for an ideal unit.

The variation in base resistance (Fig. 2) indicates that the base resistance of the CK721 is higher than that of the CK722. This is in accord with observations that high alpha units generally have higher base resistance, although such is not always the case. Figure 3 gives alpha cutoff as a function of frequency. Approximately 50% of the CK721 transistors show an alpha cutoff greater than 800 kc. However, this does not imply that


good performance can be obtained up into these frequencies; alpha cutoff is only one of several factors governing high frequency performance.

Cutoff current, I_{co} , for both types is shown in Fig. 4. Cutoff current is an excellent indication of the surface cleanliness of the junction, and production has improved enormously in this regard since the present data was taken.

Figure 5 gives alpha distributions. Here is the major item that one buys in the CK721. While the CK721 curve cuts off quite sharply around .99, some units have been observed with an alpha as high as .999.

Distributions of collector capacitance, C_c , are presented in Fig. 6. The capacitance, as measured, is the output capacitance in the grounded base circuit. In the grounded emitter circuit, the effective output capacitance is much higher than that in the grounded base circuit because it is an inverse function of $(1-\alpha)$. This does not necessarily mean that the frequency response of the grounded emitter circuit is worse in audio service; the output resistance of the grounded emitter circuit is reduced by the same factor that the output capacitance has increased. Thus, for matched conditions, frequency response of the two connections is identical.

*This article is based on a paper presented at the 1953 Airborne Electronics Conference, Dayton, Ohio, May 11-13.

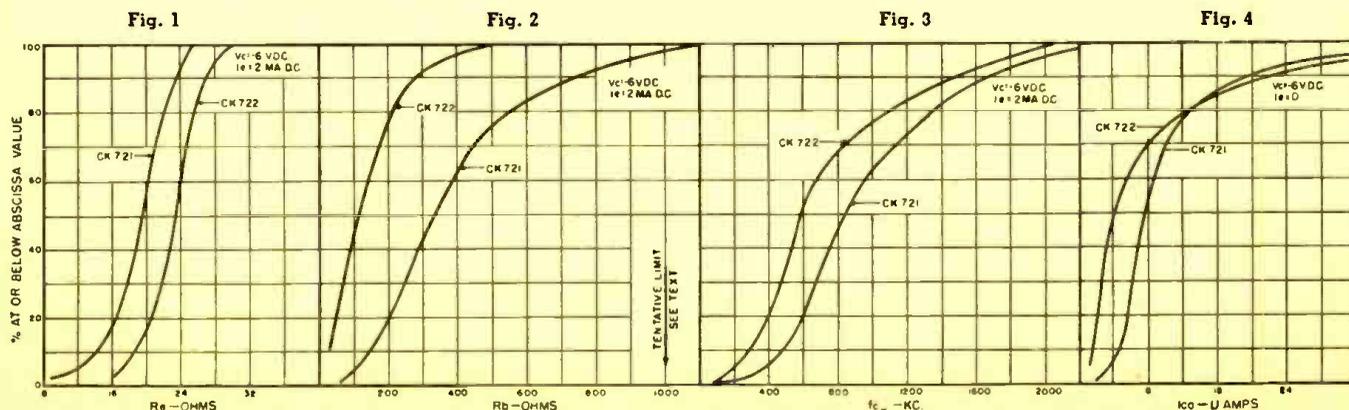

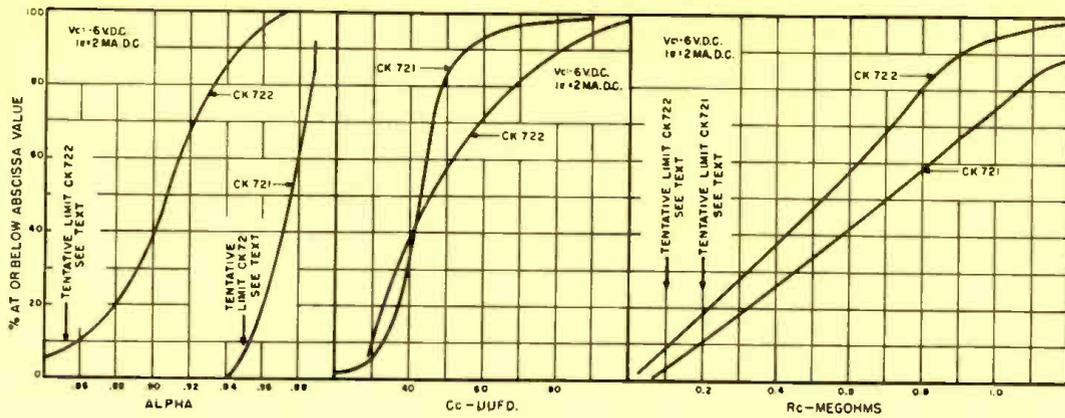


Fig. 5

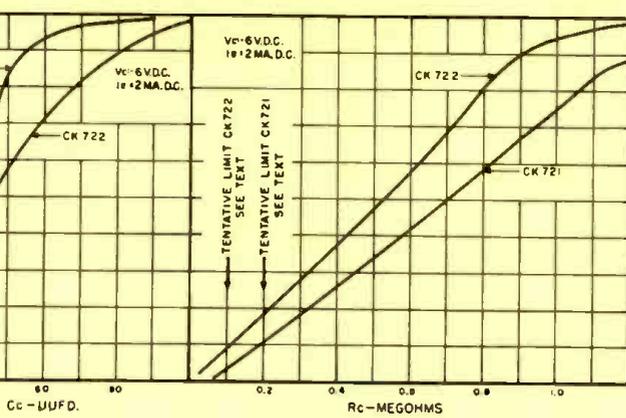


Fig. 6

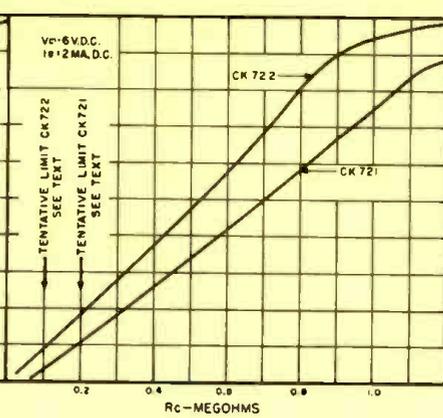


Fig. 7

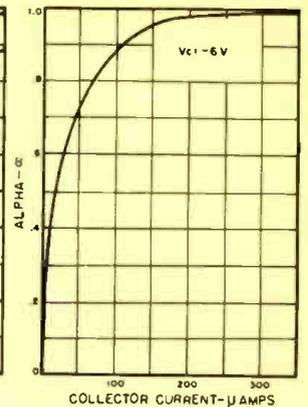


Fig. 8

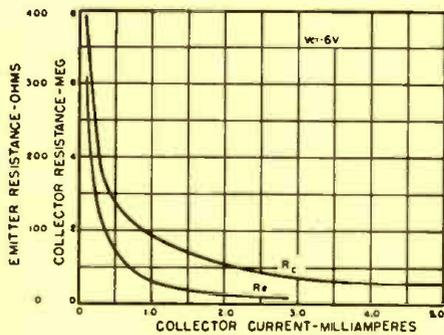


Fig. 9

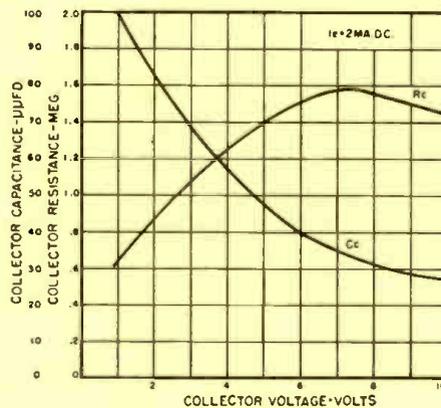


Fig. 10

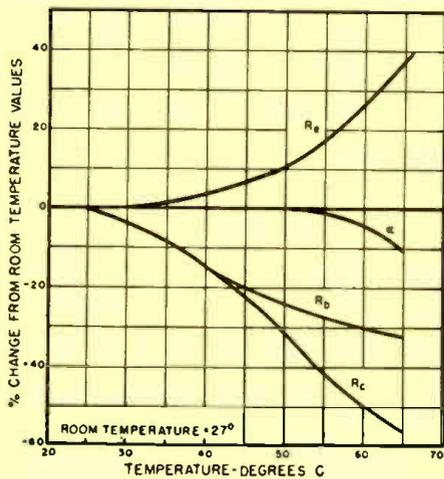


Fig. 11

The capacitance of the emitter junction when operated with reverse voltage should be noted. In these diffused

units, the area of the emitter junction is appreciably smaller than that of the collector, with the result that the emitter capacitance is about 25% of the collector capacitance.

Figure 7 shows the collector resistance, R_c . Improvements in I_c have also resulted in the elimination of most of the very low units that appear here. It should be realized that the values of certain of the parameters shown in Figs. 1 through 7 are functions of operating point. In Fig. 8, alpha is a function of collector current. Alpha holds up well down to about 200 μ a., but below this point it falls off rapidly and may be subject to a large unit-to-unit variation. Figure 9 presents the variations in R_c and R_e as functions of collector current on typical units; if high

R_c is desired, it can be obtained at lowered collector currents without loss in current amplification. Theoretically, R_c should be equal to $25.9 \times 10^{-3}/I_c$. The variation shown here with I_c approximates this relation quite closely. In Fig. 10, R_c and C_c are shown as functions of collector voltage V_c . R_c tends to maximize at various collector voltages, depending on the unit. C_c is theoretically proportional to $1/\sqrt{V_c}$.

Transistor parameters also depend on temperature. The variations in R_c , R_e , α , and R_b are given in Fig. 11. Alpha remains relatively constant with rising temperature, R_c decreases and R_e increases. R_b has a rather peculiar action as the temperature changes. Here it is shown as decreasing; however, examination of the low temperature range indicates that it also decreases in that region. Thus, R_c tends to be maximum at normal temperatures.

Before examining the circuit performance, it is essential to consider d.c. operating points. It is extremely important, from the standpoint of production use, that the external circuit and not the transistor itself govern the operating point. In the two-battery or tapped-battery circuit, the external circuit is in control—inasmuch as the resistance setting the emitter current is normally large compared to the d.c. emitter drop and, thus, primarily determines the emitter current. (It also

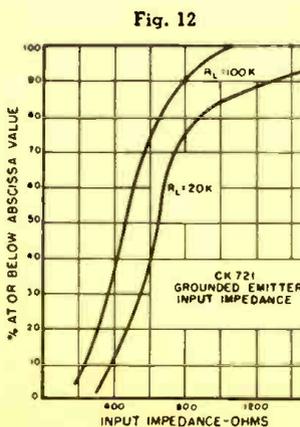


Fig. 12

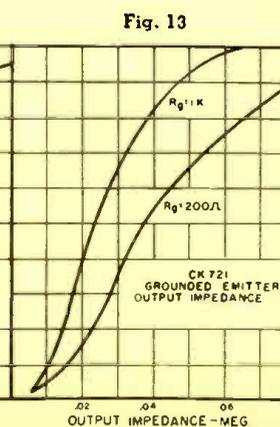


Fig. 13

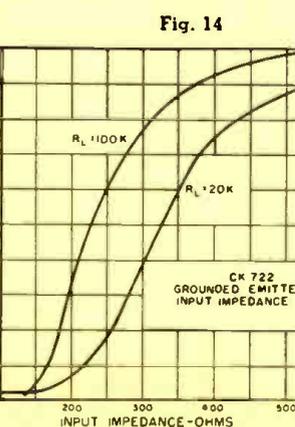


Fig. 14


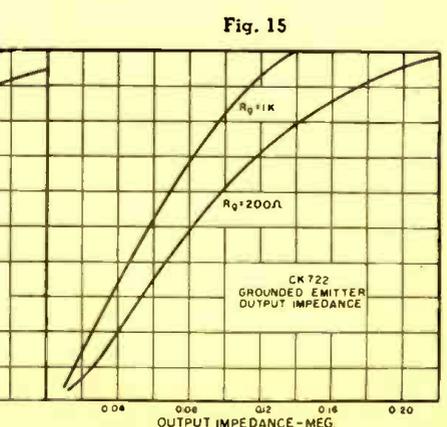


Fig. 15

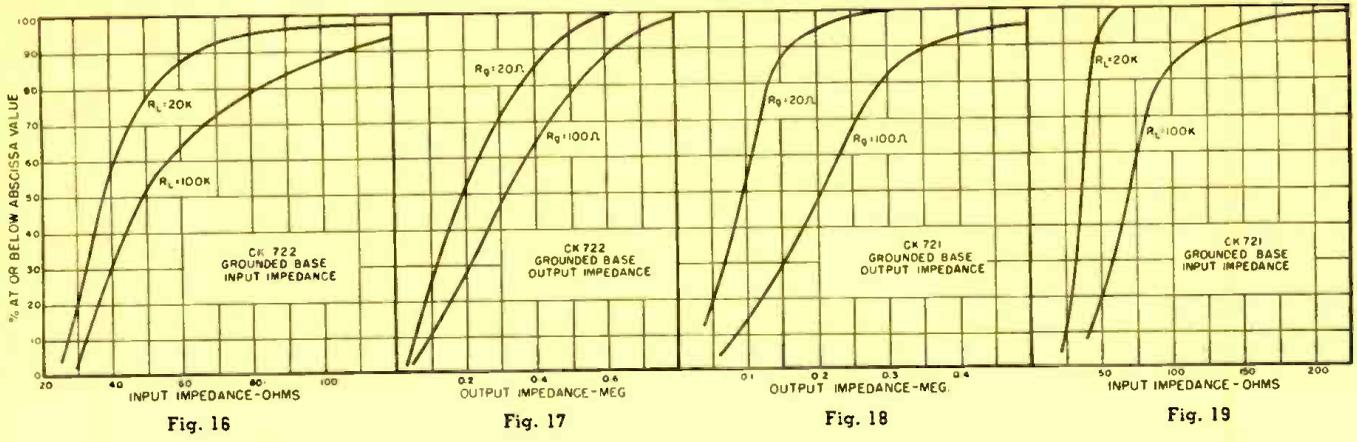


determines the collector current, for I_b and I_c are practically equal when I_b is large compared to cutoff current.)

On the other hand, single-battery operation is attractive, and one is first led to the simple circuit of Fig. 20A. In this circuit, the collector current is given approximately by:



$$I_c = \frac{I_b + I_{co}}{1 - \alpha}$$

The expression is approximate because α is a function of I_c . It will be evident that in this circuit I_c is subject to wide variations because I_{co} has rather wide limits and is comparable to I_b (the base current). In addition, $(1 - \alpha)$ may vary over 10:1 in the CK721. As Fig. 20A shows, the variation in the operating point is intolerable unless base resistances and transistors are matched, which constitutes an obviously undesirable process. Furthermore, if one wishes to hold collector current at, say, 500 μ a., it is impossible to do so in the circuit of Fig. 20A with units of even moderately high alpha and very reasonable cutoff currents. Figure 20B is a d.c.-stabilized circuit using three resistors in the manner described by Shea¹. The operating point is very nicely controlled at the expense of only a small amount of power being consumed by the stabilizing network. Networks of this sort also stabilize the operating point with temperature, which is of great advantage because of the sensitivity of cutoff current to

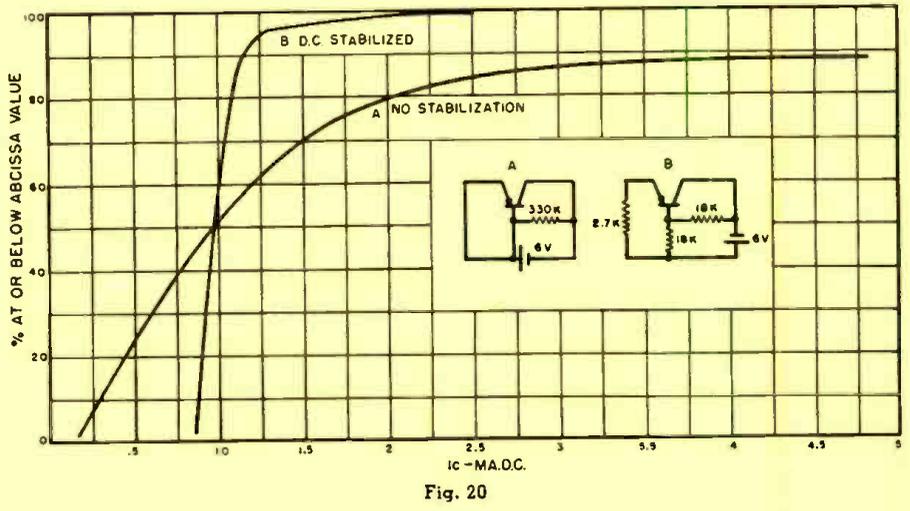

temperature variations. For example, at low cutoff currents, I_{co} has a temperature coefficient of about 7% per °C at 25°C. Incidentally, because the transistor doesn't know how it is connected, the d.c. stabilization circuit is the same and produces the same results no matter how it may be connected from an a.c. standpoint. Of course, one doesn't ever get something for nothing, and a disadvantage of this stabilization is that—depending on the degree of stabilization—the voltage available at the collector is always smaller than that available when a single base resistor is used.

(Continued on page 24)

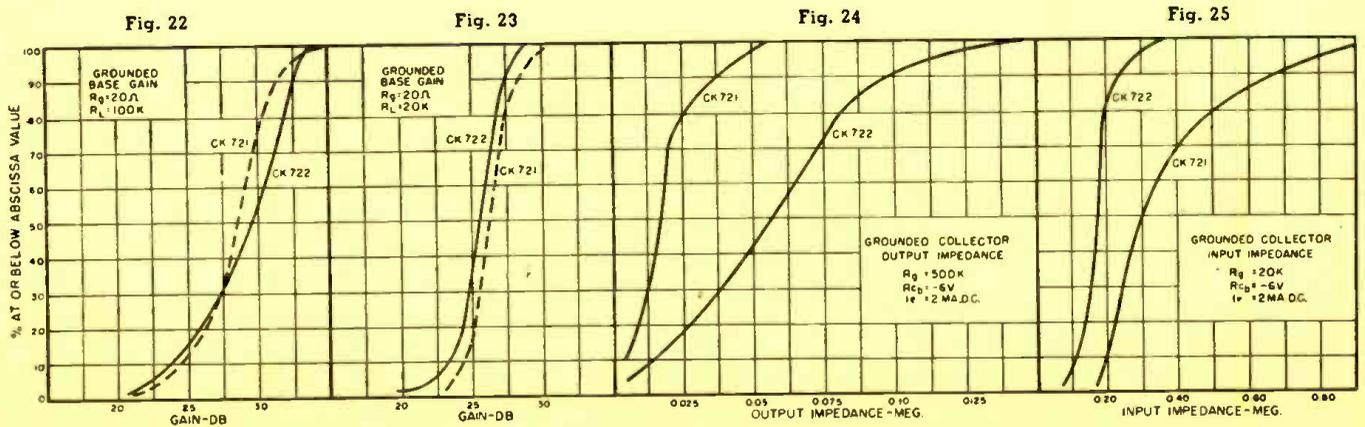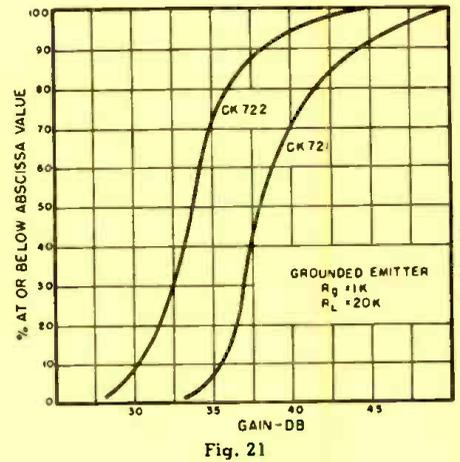

BALANCED CRYSTAL-DIODE MODULATOR*

By

WILLIAM F. BYERS

General Radio Company

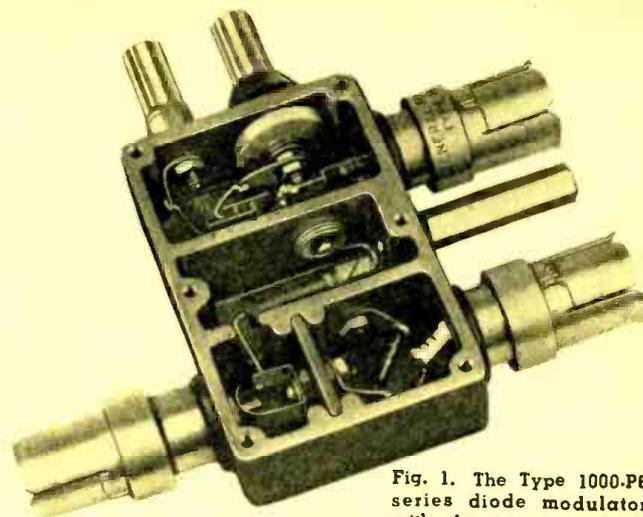


Fig. 1. The Type 1000-P6 series diode modulator with the cover removed.

Silicon diodes are used in a balanced modulator circuit to give up to 100% modulation of r.f. signals at 60 to 2500 mc.

IT IS well known that amplitude modulation can be accomplished by simultaneously applying radio and modulating frequencies to a nonlinear circuit element. Copper oxide rectifiers are commonly used as low-level modulators at audio and low radio frequencies, and silicon diodes are used at frequencies up to several thousand megacycles as modulators or mixers in receivers. This article will describe a balanced modulator utilizing silicon diodes which can be used to modulate the output of signal generators in the frequency range of 60 to 2500 mc.

The usual v.h.f. and u.h.f. signal generator consists of a carrier oscillator whose plate supply can be modulated. Such modulation inevitably results in considerable frequency modulation accompanying the desired amplitude modulation. For square-wave or pulse modulation, incidental FM is not usually a problem, but difficulty is encountered in obtaining fast rise time because of the time required for the oscillator to build up in amplitude to its maximum output.

Modulation of the output of an oscillator can be accomplished by a crystal diode if the signal level required is of

the order of 10 mv. or less. This output level is sufficient for many applications. The use of a modulator at the output of an oscillator greatly reduces or eliminates incidental FM and simplifies the problem of pulse modulation.

Figure 5 gives the volt-ampere characteristic of a typical 1N21-B crystal diode. As can be seen from this curve, the incremental resistance varies from about 5000 ohms with zero current to about 60 ohms at 1.2 ma. The small circles indicate the maximum spread of characteristics between ten 1N21-B units. With the range of resistance shown, it is evident that a reasonable degree of modulation can be obtained by inserting this crystal diode between a low impedance source and load as a series-modulated resistance. However, the high frequency impedance variation is less than that indicated by the d.c. volt-ampere characteristic, due principally to residual inductance and capacitance.


A crystal-diode modulator was developed a few years ago using a single diode as a series modulator. In the wiring diagram of this unit (Fig. 6), C_1 is a blocking capacitor which permits modulation and bias to be applied to

the diode but has a low impedance at the signal frequency. L_1 is the modulation feed choke. L_2 and C_2 constitute a simple high-pass filter, passing the signal frequency and attenuating the modulating frequency. A mixing pad provides a means of applying d.c. bias and modulation simultaneously. The bias is usually made adjustable and is set to give the desired operating point on the modulation characteristic. D.C. insertion can be supplied at the modulation terminals with the modulating signal if desired.

Figure 1 is a photograph of this modulator with the cover removed, displaying the arrangement of components. The crystal diode is contained within the r.f. input connector at the lower left. The tip of this diode can be seen projecting into the lower compartment of the casting, contacting a spring supported by an insulating strip. The r.f. path is then through the small capacitor at the right side of the compartment to the r.f. output connector at the lower right. In the center compartment is the modulation feed choke. The modulation input is at the upper right connector. The mixing pad is in the top compartment, and the bias terminals are at the top.

Modulation characteristics of this unit at various carrier frequencies are such that the depth of modulation decreases with increasing carrier frequency. For many applications, such characteristics are satisfactory. However, inability to get high percentages of modulation and the nonlinearity of the modulation characteristics limit the

Fig. 2. (A, left) Modulation characteristic of the Type 1000-P7 modulator. (B, ctr.) An 0.2- μ sec. r.f. pulse at a 60-mc. carrier frequency produced by Type 1000-P7 modulator. (C, rt.) Same as (B), but with a reduced amplitude.

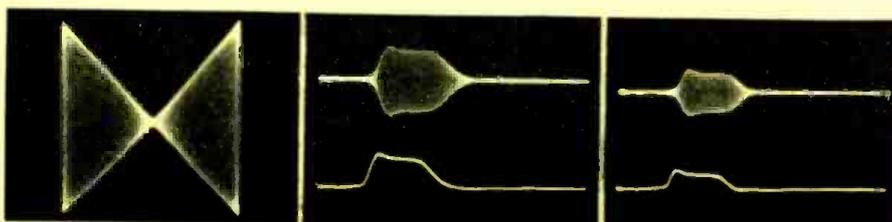

*This article is based on a paper presented at the 1953 Airborne Electronics Conference, Dayton, Ohio, May 11-13.

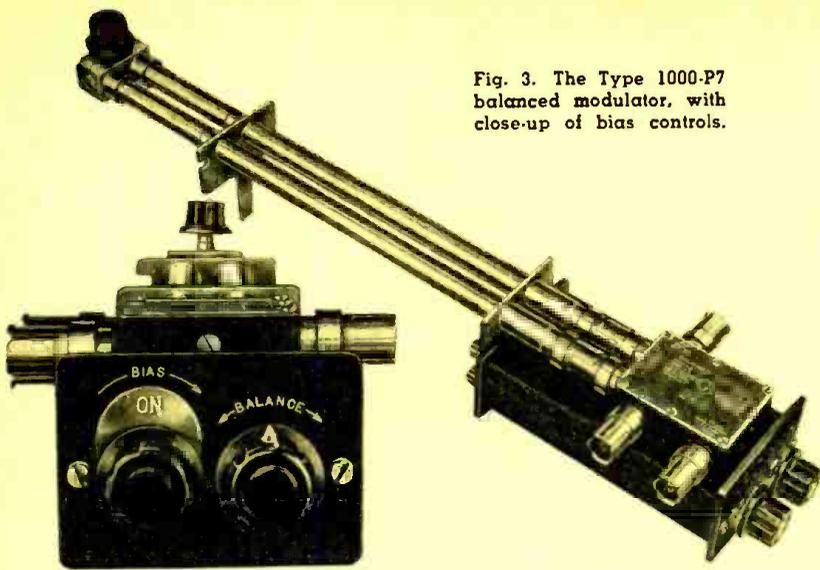


Fig. 3. The Type 1000-P7 balanced modulator, with close-up of bias controls.

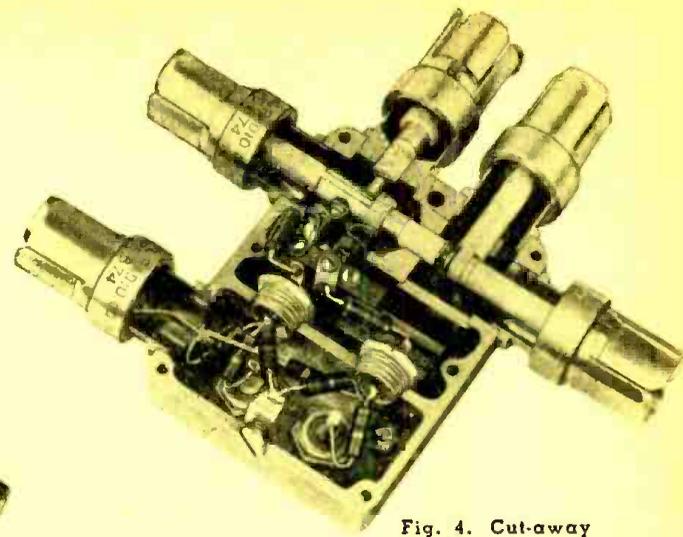


Fig. 4. Cut-away view of the Type 1000-P7 modulator.

application of a device of this kind. For most pulse work, the carrier level between pulses must be suppressed to a very small fraction of the pulsed level. Also, a higher degree of linearity and 100% modulation are often required. To overcome these limitations of the simple crystal-diode modulator, and to extend the operation to higher carrier frequencies, a balanced crystal-diode modulator has been devised.

Figure 7 is an elementary schematic diagram of the General Radio Type 1000-P7 balanced modulator. This is merely a combination of two crystal-diode modulators with an adjustable phasing line to supply two carrier signals which are 180° out of phase to the diodes. The outputs are connected in parallel. By adjusting the phasing line to an odd multiple of one-half wavelength and adjusting the relative bias of the two diodes, the combined output can be brought to essentially zero. The bias supply is arranged with a differential bias or balance control, and the phasing line is a "trombone" section of coaxial line. The two diodes are poled in such a manner that the application of a modulating signal increases the impedance of one and decreases the impedance of the other, permitting a

single-ended or grounded modulation source to be used.

The balanced modulator, complete with the adjustable phasing line, is shown in Fig. 3. A bias battery, consisting of four standard flashlight cells, is contained within the base of the instrument. Also shown is a view of the bias supply controls which permit setting the magnitude and balance of bias applied to the two crystal diodes.

In the cutaway view of the balanced modulator (Fig. 4), a detailed arrangement of components is displayed. The r.f. input connector is on the right. At the top are the adjustable phasing line connectors. The output connector is at the top, left. One signal path is through the diode unit (top center), and through a built-in coupling capacitor to the output connector. The other signal path branches near this diode and the external phasing line brings it to the other diode unit at the left adjustable line connector. A built-in capacitor brings the signal to the common output connector. The modulation and bias feed chokes are in the center compartment, and the resistive networks in the lower compartment mix the modulation input from the lower left connector with bias voltage supplied through feedthrough capacitors in the back of the case.

The modulation characteristic at a carrier frequency of 900 mc. is illustrated in Fig. 2A. This characteristic is essentially the same at all carrier frequencies from 60 to 2500 mc. Above 2500 mc. the residual impedances begin to swamp the modulated portion of the diode impedance, the balance becomes difficult to make, and the insertion loss increases rapidly. The photograph shows the r.f. envelope vs. instantaneous modulation voltage (positive to the right, zero in the center, and negative to the left). This characteristic represents balanced-

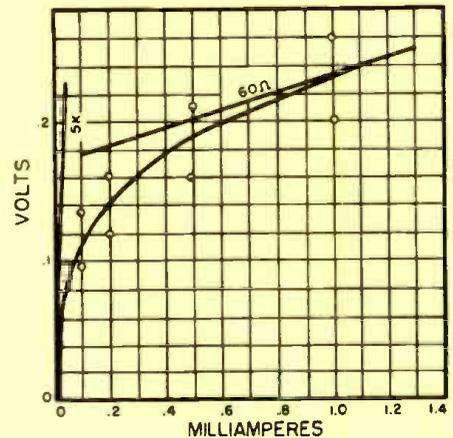


Fig. 5. Typical volt-ampere characteristic of a type 1N21-B crystal diode.

modulator operation, and when sine-wave modulation is applied, two sidebands are generated with the carrier suppressed.

A balanced modulator has desirable characteristics for pulse modulation. Application of a pulse of either polarity will result in an r.f. pulse in the output. The balance can be adjusted without much difficulty to give a carrier suppression between pulses of 60 db below the pulsed level, at all carrier frequencies. (Continued on page 27)

Fig. 6. Circuit of the Type 1000-P6.


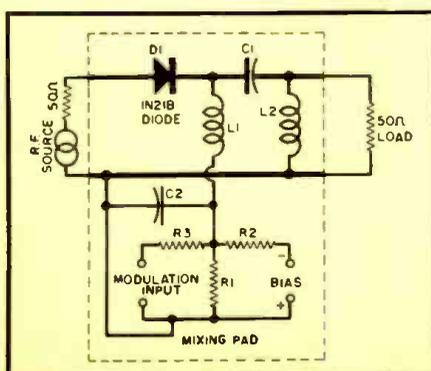


Fig. 7. Circuit of the Type 1000-P7.

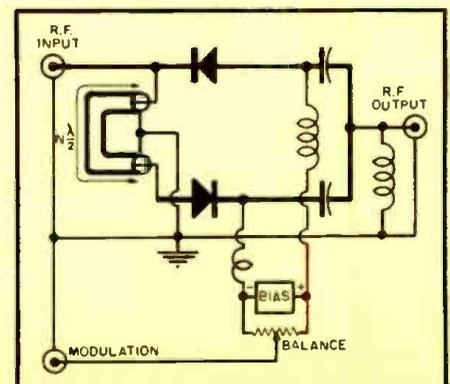

A FLEXIBLE PLATED

This cloth-backed plated circuit, produced by a new technique, is a versatile tool for engineers.

THE FLEXIBLE plated circuit appears to fit nicely into the general methodology of fabrication of electronic equipment. Some of the current forms of printed circuitry are rigid, and this rigidity is made use of in supporting small components. On the other hand, larger equipment is going to be chassis-bound for some time to come. Here, experience has shown that a state of fluctuation exists in individual terminal-to-terminal dimensions and elevations. Individual wires easily take this variation into account, as can pigtailed components. If the circuit is complex, it is not unusual for a number of small components to be subassembled on a terminal board where dip soldering can be used to advantage.

Production of a flexible plated circuit, simply stated, consists of silk screening a stop-off (i.e., an insulating lacquer) onto a stainless steel surface, copper plating the nonstopped-off area, and stripping the plating and stop-off from the stainless steel surface with an adhesive tape. This is illustrated in the flow diagram (Fig. 1), which will serve as an outline of the description to follow.

Type 316 or 347 stainless steel sheet, free from blemishes, flaws and fissures, is chosen because of its resistance to chemical attack in the copper plating solution and because it can be easily

maintained in the passive condition necessary for stripping the copper plating. The surface is given a mirror finish by polishing and buffing, and care is exercised in handling to avoid scratches. Surface roughness has a tendency to cause adhesion of copper plating to the steel, possibly by mechanical bonding, since this difficulty is noticed even with properly passivated steel. Individual scratches will be faithfully reproduced in the plating and, if sharp, will have a tendency to cause local mechanical weakness in the copper—probably as the result of a notch effect. After polishing and buffing, the surface is cleaned and passivated by anodic treatment in a conventional hot alkaline steel electrocleaning solution. (A solution suitable for this purpose is *Oakite #90*, manufactured by *Oakite Products, Inc.*)

Silk Screening

A reversed silk screen is prepared by conventional graphic arts procedure, using a fine mesh wire cloth (140 or 160 U.S. Standard) and a film which is resistant to the stop-off lacquer and thinner. The reversed screen is necessary because of the subsequent reversal when the circuit is stripped from the stainless steel.

The stop-off lacquer is a vinyl copolymer (*Unichrome Quick Dry Stop Off Lacquer #324*, manufactured by *United Chromium Inc.*). The original solvent is replaced with *n*-butyl acetate to give a lacquer with 16-20% solids and a viscosity of 200 poises. Care is taken in the screening to avoid holes or discontinuities in the lacquer film other than those of design. The evaporation rate of the solvent is adjusted in a compromise between rapid drying of the screened film and slow drying on the screen.

Electroforming

After the stop-off is dry, the wiring is formed by electroplating between 1 and 3 mils of copper onto the non-stopped-off stainless steel in an acid copper sulfate plating solution. A practical lower thickness limit exists in that deposits thinner than 0.7 mils have a tendency to tear when being stripped from the stainless steel. This is postulated to be due to a lower strength within the copper than in the weak bond between the copper and the stainless steel. An upper thickness limit is


Top view of an a.c.-d.c. receiver which utilizes the flexible plated circuit shown at top of p. 13.

Pressing the adhesive tape into contact with the copper plating and stop-off lacquer prior to the stripping operation.


By **E. R. BOWERMAN**

Physics Laboratories
Sylvania Electric Products Inc.

and **R. F. WALTON**

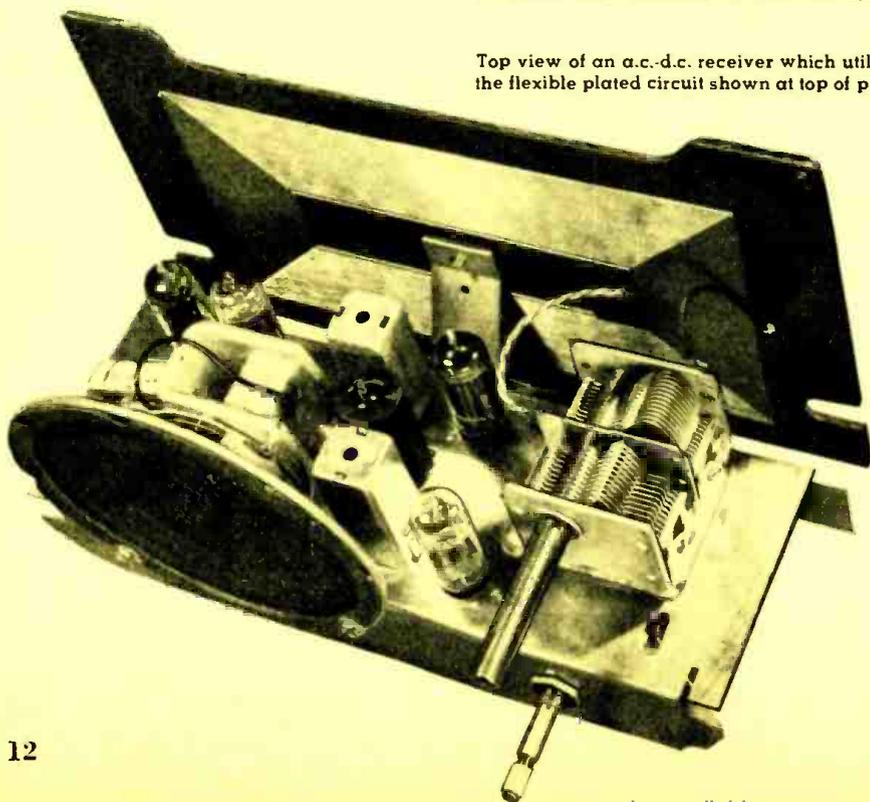

CIRCUIT*

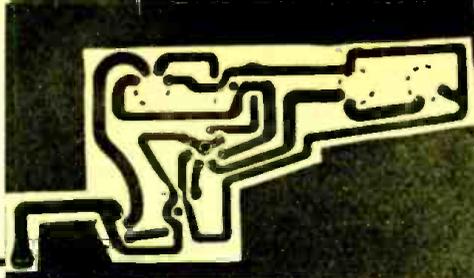

less easily defined, but as the thickness is increased, the flexibility of the copper decreases and the deposit tends to spread along the surface over the stop-off. If the wiring is closely spaced, bridging may occur between wires due to the spreading deposit.

For the circuitry investigated during the development of this process, loss in flexibility gave an upper limit at about 20 mils. The plating solution used for the investigative work contained 250 gms./liter $\text{CuSO}_4 \cdot 5\text{H}_2\text{O}$ and 75 gms./liter H_2SO_4 (sp. gr. 1.83). Before being used, the solution was filtered through activated carbon, and commercial electrolytic cathode copper was used as anode.

In this process, the stopped-off stainless steel is connected as cathode before immersion in the plating solution so that plating starts immediately on the passive surface. The cathode is agitated during plating and a cathode current density of 100 amperes per square foot is used. In 18 minutes, a 1.5-mil deposit is obtained which is suitable for $\frac{1}{16}$ "-wide wires in receivers having series string heater connections with 150-ma. currents. After plating, the cathode is water-rinsed to remove the plating solution and dried.

Stripping

An industrial cloth-backed adhesive tape is pressed against the copper plating and stop-off with sufficient pressure and time to obtain good contact to the adhesive. The tape and adhered circuit is then stripped from the steel sheet with a rapid, continuous, even pull. The stop-off also transfers and serves to cover the sticky areas of the tape not covered by the copper. (The particular tape used was Permacel EE3012, manufactured by Industrial Tape Corporation, compounded with a thermosetting adhesive which could be cured at 250°F before use or allowed to cure in equipment.) After stripping, the tape is trimmed and the required holes punched out. The stainless steel may be reused as long as the surface is maintained smooth, clean and passive.

Installation

The flexible circuit is forced over the fixed component and tie point lugs before the small components are installed. Flexibility of circuit harness speeds up

The complete plated circuit as it adheres to adhesive tape backing.

the installation due to the give and take possible in cloth fabrics. Some attention to the design of the lugs will pay off in easing the assembly and reducing the necessity for hole punching to accommodate lugs. On the other hand, if highly detailed work is not being produced, it is also possible to use a loose woven fabric for the adhesive tape backing which will permit the lugs to pierce it easily.

Coding

Since the electroforming of the copper will faithfully reproduce the surface finish of the stainless steel, it is possible to transfer certain types of designs to the copper surface beyond the obvious capabilities of outline identification techniques. Localized texturing of the stainless steel by, for example, shot blasting, etching or engraving, will give a visual coding to the plating. Only rounded and relieved designs may be employed to permit parting after plating. In addition, the deposit may have to be made a little thicker to obtain good strength for the parting operation.

A flexible circuit such as that described above has many advantages over rigid plated circuits. It may be flexed, warped, twisted, or otherwise deformed to accommodate itself to various mechanical designs. With proper precautions, the circuit can even be rolled up in tubular form.


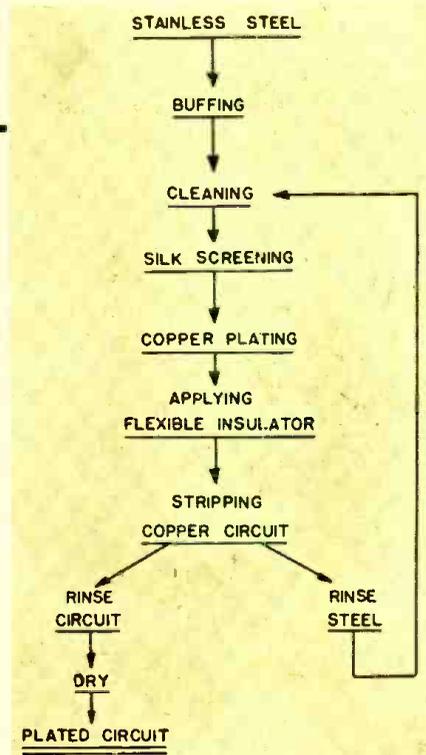


Fig. 1. Flow diagram of process.

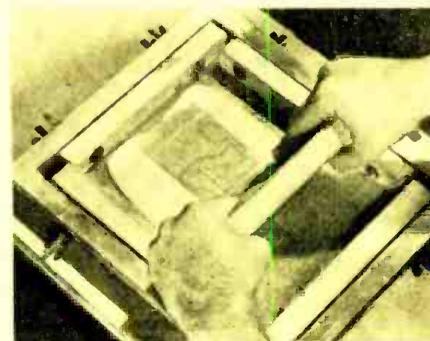

Application of the stop-off lacquer through the silk screen stencil.



Electroplating copper onto the steel plate. Power supply at left supplies plating current. Storage battery supplies power for agitating the solution.

*This article is based on a paper which was presented at the 1953 Airborne Electronics Conference, Dayton, Ohio, May 11-13.

VISUAL PROOF OF PERFORMANCE MEASUREMENTS

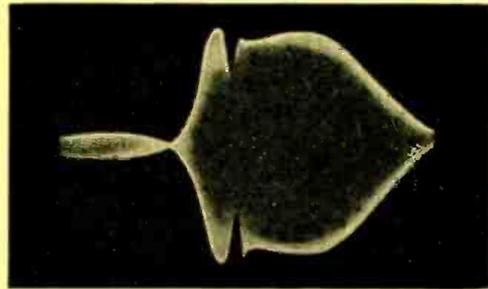


Fig. 1. Display from the Ruston wobbulator¹.

By

R. D. CHIPP, Director of Engineering
Du Mont Television Network

*Equipment and techniques used in making visual transmitter measurements to check TV operation**

SCTIONS 3.46 and 3.254 of the Rules of the Federal Communications Commission require that certain Proof of Performance measurements be made annually by standard AM and FM broadcasting stations. Although there are at present no such specific rules for television broadcasting stations, an initial Proof measurement is required in Form 302, the Application for New Broadcast Station License. Further, annual tests are implicit in Section II of Form 303, Application for Renewal of Broadcast

Station License, which calls for the date on which equipment performance measurements have been made, and specifically asks, "Do these measurements show the transmitting system performance to be in accordance with the Standards of Good Engineering Practice?" The Standards of Good Engineering Practice Concerning Television Broadcasting Stations, formerly a separate document, is now a part of the Rules.

Subpart E of Part 3 of the Rules covers the television broadcast service. Section 3.686 of this Subpart describes

the requirements for field strength measurements. Section 3.687 covers the measurements of transmitters and associated equipment, and Section 3.689 covers the determination of operating power. The measurements required by these three sections fall naturally into three major categories:

1. Field strength measurements
2. Performance of the aural transmission system
3. Performance of the visual transmission system

Field Strength Measurements

Field strength measurements may be made in two different ways. Mobile measurements, which involve continuous recording in a vehicle in motion, are preferred by the Commission. As an alternative, cluster or spot measurements may be submitted. Mobile measurements lend themselves readily to statistical analysis inasmuch as there are much more data available for study. However, it is often difficult to find highways that follow the radials used to show the topography in a station's service area. Cluster or spot measurements permit the use of higher receiving antennas, and provide better information for studies of diffraction.

Detailed information on the mobile method is available in the Proof of Performance measurements made by *Du Mont* for Station WTTG in Washington, D. C. Also, the mobile method as used at WEWS in Cleveland has been described by J. B. Epperson¹. Detailed information on the spot or cluster method is available in the Proof of Performance measurements made by *Du Mont* for Stations WDTV in Pittsburgh and WABD in New York².

Fig. 2. Waveform monitor for measuring significant amplitude levels.



*This article is based on a paper presented at the 7th Annual NARTE Broadcast Engineering Conference, April 29, 1953, in Los Angeles, Calif.

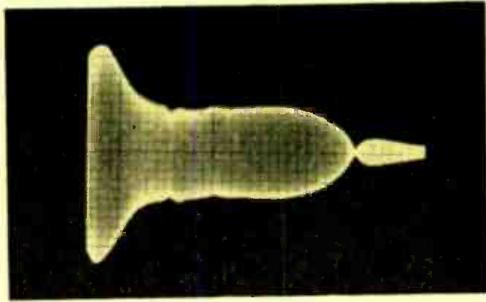


Fig. 3. Attenuation display with 4.5-mc. notch.

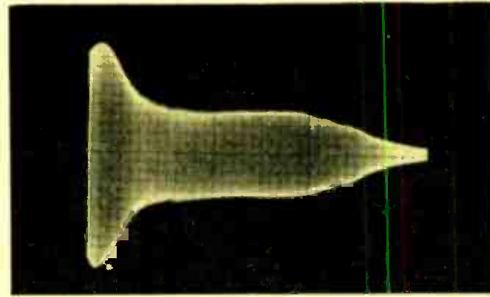


Fig. 4. Same as Fig. 3 without diplexer notch.

Aural Proof of Performance measurements for television stations are equivalent to the aural Proof of Performance measurements required for FM stations. A thorough and complete description of aural Proof of Performance measurements³ was presented before the NARTB Engineering Conference on April 15, 1950, by George Adair. This has been reprinted and is available through NARTB.

Visual Measurements

This article will discuss techniques and equipment used in making the visual transmitter measurements required by Section 3.687 and the power output measurements required by Section 3.689.

The upper sideband attenuation characteristic may be measured in at least two ways, either of which conforms to the Commission's Rules. The first method utilizes a composite video signal consisting of standard sync and blanking, with sine-wave modulation at selected discrete frequencies occupying the interval between blanking pulses. A typical test setup for such a measurement is shown in Fig. 5A.

A standard black picture is fed to the dummy load, and the transmitter is adjusted for rated output. Sync and

blanking levels are set to normal values with sync equal to 25% of the total modulation envelope. Proper setting may be determined by the r.f. waveform monitor that is usually a part of the station's monitoring equipment. Sine-wave modulation is generated in a video signal generator and is introduced into a line amplifier or stabilizing amplifier, usually included in the station's normal equipment. The axis of the sine-wave modulation is placed at a point equal to 50% of the sync peak amplitude, and video signal generator output at 100 kc. is then adjusted so that the maximum excursion of the sine wave reaches a point equal to 75% of the sync peak amplitude. Thus, in standard level measuring terminology, sine-wave modulation occupies the region between blanking level and 75% of reference white.


Blanking and sync level controls are not altered during the remainder of the test, and the amplitude of the sine wave is maintained within the limits specified. Video signal generator output voltage at 100 kc. is measured by a vacuum-tube voltmeter and recorded on a suitable form. The oscillograph is connected to the transmitter input and vertical gain adjusted to obtain suitable vertical

to 2½" on a 5" scope. Amount of deflection is recorded. The oscillograph is then switched from the transmitter input to the rectified transmitter output, and vertical trace deflection is recorded.

The measurement made at 100 kc. is the reference for the remainder of the test and is noted as 0 db. The oscillograph is now switched back to the transmitter input and the frequency of the signal generator is shifted to 500 kc. Output of the video signal generator is maintained at the value previously recorded, and vertical gain of the oscillograph is adjusted, if necessary, to maintain the deflection previously recorded. The oscillograph is then switched to the transmitter output, and vertical deflection is measured and entered in the appropriate column in the form. The ratio between the deflection at 100 kc. and at 500 kc. is entered in a differential column and converted to db. This test is then repeated at other frequencies; suggested values are 1.25, 1.5, 2, 2.5, 3, 3.5, and 4 mc.

The db differences are plotted on a rectangular coordinate display, similar to that shown in Fig. 7. This plot is the required attenuation characteristic. Figure 7 also shows the FCC ideal curve, as well as the upper and lower limits specified by the RTMA.

Fig. 5. (A) Setup for Proof of Performance measurement. (B) Alternate method. (C) Narrow-band receiver.

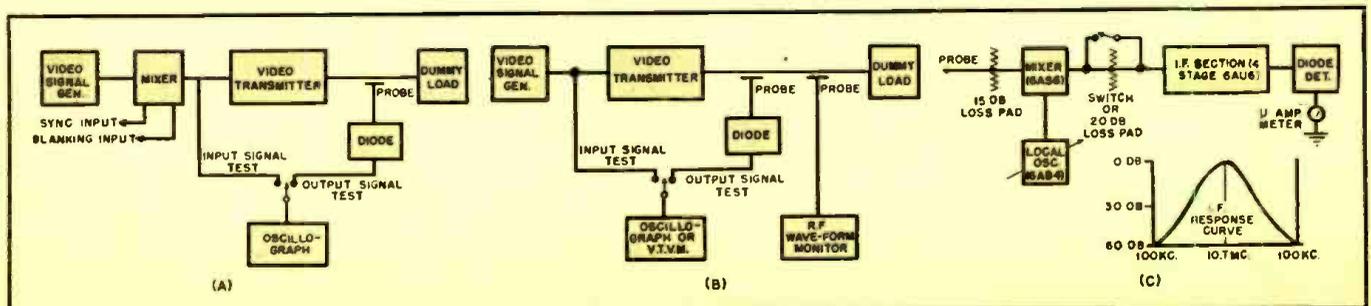

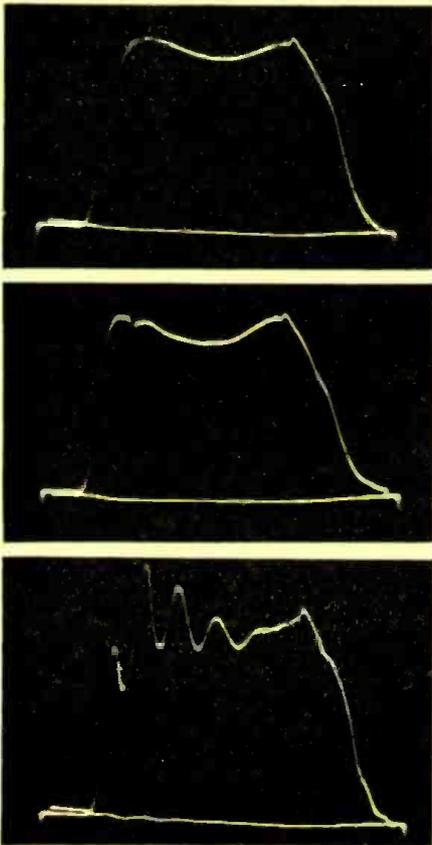


Fig. 6. Transmitter wobble curves. (A, top) Output into dummy load. (B, ctr.) Output into normal antenna system. (C, bottom) Output into defective antenna.

The alternate method for measuring the over-all attenuation characteristic involves use of a sine wave without sync and blanking. A typical equipment setup is shown in Fig. 5B. During this

measurement, any transmitter clamping circuits must be disabled and the d.c. level set manually for mid-characteristic operation. With the video input at zero, the r.f. drive is adjusted to dissipate rated average power in the dummy load—3 kw. for a 5-kw. peak power. The r.f. waveform monitor is then set so that the peaks are at 77.5%—the average value of voltage equivalent to the rated peak power output. Bias on the modulated stage is adjusted, still with no video modulation, until the r.f. peaks are at 45%; this 45% value represents the operating point and is midway between black level of 75% and white level of 15%. Now the video signal generator is set for 100 kc., and its output is adjusted for modulation peaks of 75% and troughs of 15% on the r.f. waveform monitor. Either a vacuum-tube voltmeter or an oscillograph may be used to measure a rectified sample of the output voltage; this value is recorded and represents 0 db. Output at other modulating frequencies is measured, recorded, converted to db, and may be plotted to give the over-all attenuation characteristic.

Another similar alternate method, which may be used to show the complete spectral response, involves the use of a narrow-band receiver and requires an r.f. signal generator as a calibrating instrument. By means of the r.f. waveform monitor, the transmitter is adjusted in the manner just described and modulated with 100-kc. sine waves. The receiver is tuned to locate either the upper or lower 100-kc. sideband, and meter deflection is noted. The receiver is then switched to the r.f. signal gen-

erator, which is tuned to the frequency of the receiver. Output of the signal generator is adjusted so that the receiver meter has the deflection previously noted, and the signal generator output at that point is recorded. This process is repeated for other modulating frequencies, and readings are taken of both the upper and lower sidebands. Recorded values of r.f. signal generator output may be converted to db and plotted, using the 100-kc. value as a reference. The curve shown in Fig. 8 is a recent spectral measurement made at WABD, New York; it also indicates transmitter performance with respect to the FCC rule that the lower sideband be 20 db down from the 100-kc. reference at frequencies of 1.25 mc. and higher.

From this complete spectral response, it is possible to derive the ideal demodulated curve, assuming negligible phase shift. This may be done by adding the values plotted for the lower sideband to the values plotted for the upper sideband. Several checks of this method have shown good correlation with the other methods of determining the ideal curve.


Throughout all of these measurements, it is necessary that power output be held constant. Transmitter power is generally measured by means of a dummy load, sometimes called a phantom antenna. There are two basic types of dummy load. The calorimeter type of load consists of a ceramic tube having a resistive coating which is cooled by a flow of water. The flow of water and its input and output temperatures are recorded. From these data, a simple calculation gives the average power dissipated in the resistor, and multiplication by 1.68 gives the peak power. It is important that sufficient time be allowed to permit temperatures to stabilize before taking readings with this type of load.

The other type of dummy load consists of a terminating resistor immersed in a tank of oil which is cooled by water. A portion of the voltage across the resistor is read by a meter, factory-calibrated by the calorimetric method to register watts. In general, dummy loads used at v.h.f. are accurate to within 5%. The same method of power determination is used at u.h.f., although in this range it is more difficult to be sure that the load does not present some reactive component to the transmission line.

Measuring equipment required for the foregoing tests is in most cases available commercially from several manufacturers and should be included in any station's regular test equipment complement. A vacuum-tube voltmeter, utilized for this type of measure-

(Continued on page 30)

Fig. 7. Over-all attenuation characteristics of the visual transmitter.

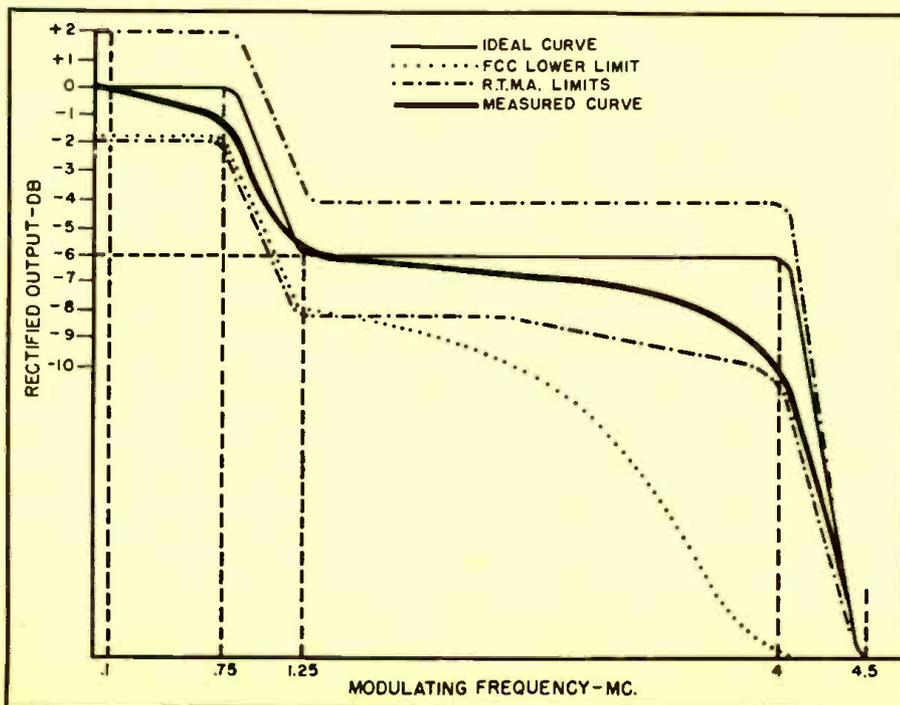

RCA MICROWAVE

RADIO-RELAY COMMUNICATION AND REMOTE CONTROL.



Over the years RCA MICROWAVE has proved it stays in service when you need communication most.

Most practical system, most complete service

RCA Microwave gives you as many voice channels as you need with minimum use of frequency space. It employs conventional tubes; familiar circuits not difficult to service. It interconnects with your telephone lines and switchboards.

Over the years the operating records of RCA MICROWAVE systems reveal a long history of successful operation through every kind of weather. Numerous RCA installations are now providing continuity of service in many applications.

RCA survey, construction and installation facilities are a complete, single-source, single-responsibility service.

For speedy, economical communication and for adequate, remote supervision, contact your local RCA Regional Office for information, or mail coupon below.

For dependable mobile communications, use RCA 2-Way Radio.

And remember, only RCA can provide the nation-wide service facilities of the RCA Service Company.



RADIO CORPORATION of AMERICA
COMMUNICATIONS EQUIPMENT

CAMDEN, N. J.



Radio Corporation of America
Communications Division
Dept. 157-U, Building 15-1
Camden, N. J.

Please send me your new, free booklet on:

- RCA Microwave
 RCA 2-Way Radio

Name _____

Title _____ Company _____

Address _____

City _____ Zone _____ State _____

NEWS BRIEFS

WIRE TWISTING DEVICE

Twisting the ends of stranded wire is speeded up with a device developed by the production department of the Brooklyn, N. Y., plant of *CBS-Columbia, Inc.*, television set manufacturing subsidiary



of the *Columbia Broadcasting System*. When the stranded wire ends are inserted in a "gripper" mounted on the shaft of a small motor, rotation of the motor shaft quickly twists the strands of wire.

RESEARCH CENTER

Plans for the construction of a functional two-story laboratory and headquarters in Kansas City, Mo., have been revealed by the Midwest Research Institute, technological and research center for middle western states. All operations of the Institute, which now occupies six scattered buildings, will be consolidated in the new structure. Actual construction on this 1¼-million dollar scientific center is expected to start some time in the fall.

ELECTRONICS DIVISION

An electronics division has been established by *Dade Brothers, Inc.* Known as the Engineering and Manufacturing Division, and located at Mineola, N. Y., it is currently engaged in design, development and production in connection with the military program. Elston H. Swanson, formerly on the engineering staff of *Airborne Instruments Laboratory*, is manager of the division.

BINAURAL TRANSMISSION

In an address before the American Institute of Electrical Engineers in June, Murray G. Crosby, President of *Crosby Laboratories*, Hicksville, N. Y.,

discussed a system of binaural sound transmission by FM multiplex which could result in third-dimension sound for FM and TV audiences.

Mr. Crosby presented a method of applying the two channels of the binaural system in which improved signal-to-noise ratio characteristics are obtained from the subcarrier channel which normally has a poorer signal-to-noise ratio than the main channel. His system also has advantages with respect to balancing the noise received on the main and subcarrier channels, and provides a "compatible" reception for listeners receiving on a monaural system.

RECORDING ANALYTICAL BALANCE

The recording analytical balance recently developed at the National Bureau of Standards automatically makes a continuous record of changes in weight. It is being used at the Bureau to record weight changes in samples of complex minerals during thermal decomposition, but is suitable for many other laboratory applications requiring a record of weight as a function of time.

Any weight change on the left side of the balance is promptly balanced by



automatic application of current to a solenoid that surrounds a permanent bar magnet suspended from the other side. A dual phototube (on top of balance case) senses unbalance in the illumination reflected from a mirror mounted on the balance beam; associated electronic circuitry consists essentially of a bridge circuit and two amplifiers. The current through the solenoid, which varies linearly as the weight be-

ing measured, actuates a strip-chart recorder (upper right).

G-E APPOINTMENTS

Three subdepartments have been created within the Commercial and Government Equipment Department of the *General Electric Company* at Syracuse, N. Y., and general managers have been appointed for each. This department is



one of four product units of the *G-E Electronics Division*.

William J. Morlock (shown at right) was named general manager of the Commercial Equipment Subdepartment; he will have responsibility for all engineering, manufacturing and sales activities relating to commercial products of the department. John J. Farrell (center) is the general manager of the Heavy Military Electronic Equipment Subdepartment, and Herman F. Konig (at left) is the general manager of the Light Military Electronic Equipment Subdepartment.

EXPANSION AT AEROVOX

Charged with basic research and engineering development for all divisions of *Aerovox Corporation*, this company's research laboratory continues to expand in facilities and personnel. Since moving into new quarters in *Aerovox Plant 2* at New Bedford, Mass., the laboratory has increased its space by five times.

Miss Elise Harmon, an outstanding physicist and chemist, now heads the printed circuit development at *Aerovox*; this development has already attained the level of pilot runs in the research laboratory, with actual production items being shipped to radio-electronic manufacturers. Prior to joining *Aerovox*, Miss Harmon was with the Bureau of Standards and the Naval Research Bureau in Washington, D. C.


CAPACITOR MANUFACTURING

Cornell-Dubilier Electric Corporation's giant new capacitor manufacturing plant being built at Sanford, N. C., is nearing completion. Production has already begun on paper tubular and electrolytic type capacitors.

Situated on a 27-acre tract, the new plant will have 270,000 square feet of operating space, including a two-story administration building. Facilities are being provided for a potential of some 2900 employees.

Ultra High Quality Sockets

FOR UHF APPLICATIONS

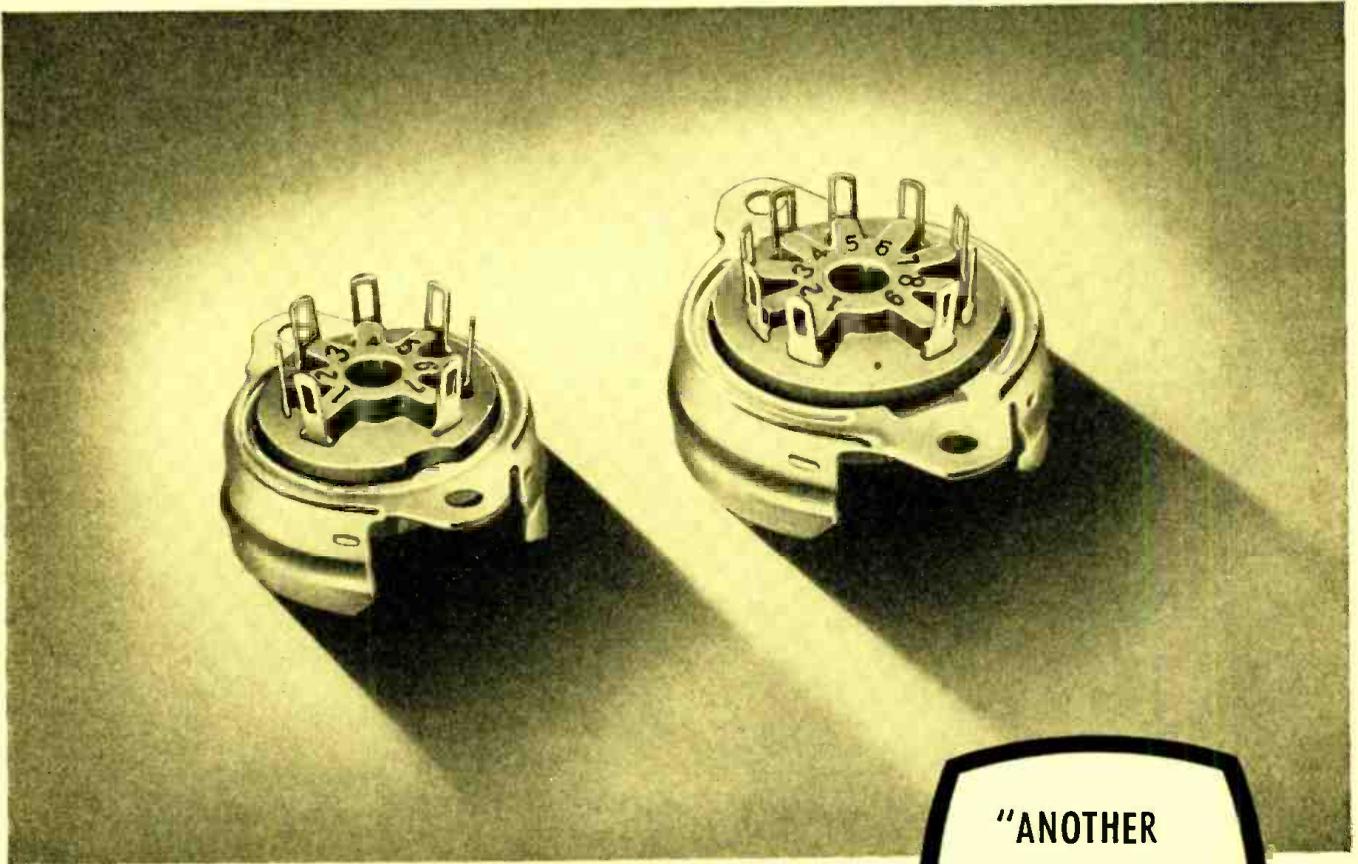

Sylvania now offers you highest quality sockets especially designed for UHF applications. Precision engineered throughout to assure minimum inductance.

Shielded bases and contacts are cadmium plated. Low-loss phenolic castings completely inclose tube pins to prevent shunted circuits.

You'll find it pays to insist on Sylvania ultra high quality parts for all your ultra high frequency requirements. For additional information and specifications, write: Sylvania Electric Products Inc., Dept. 3A-3509, 1740 Broadway, N. Y. 19, N. Y.

"ANOTHER
IMPROVED
PART...
BY SYLVANIA"



SYLVANIA


In Canada: Sylvania Electric (Canada) Ltd.
University Tower Building, St. Catherine Street, Montreal, P. Q.

LIGHTING • RADIO • ELECTRONICS • TELEVISION

NEW PRODUCTS

TRANSISTOR CURVE TRACER

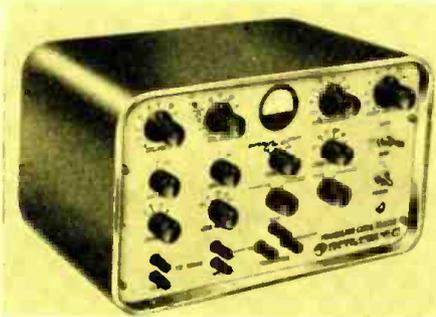Simple to operate, the automatic transistor curve tracer now being produced by *Magnetic Amplifiers Inc.* offers trouble-free circuitry and compact size. It tests NPN, PNP, junction and point-



contact transistors and features flexibility of design to accommodate new types of transistors. For complete specifications, write to *Magnetic Amplifiers Inc.*, 632 Tinton Avenue, New York 55, N. Y.

The curve tracer dynamically plots an entire family of curves simultaneously on a standard laboratory d.c. oscilloscope. A function switch selects the output and transfer curve in the grounded base or grounded emitter connection. Curves are displayed in any quadrant and the origin is always indicated.

POWER SUPPLY UNITS

Two high-voltage power supply units — Models LAB-40 and PN-60 — have been developed by the *Spellman Television Company, Inc.*, 3029 Webster Avenue, New York, N. Y. Detailed information on both of these units is available from the manufacturer.

Model LAB-40, which features a continuously variable regulated 25-40 kv.




d.c. power supply, has a 4-6 kv. focus tap for use with flying-spot kinescope recording tubes. This unit has a regulation of 0.5% at 1 ma.

Model PN-60 (shown in the photograph) is ideal for electrostatic paint spraying, capacitor charging and testing. Its reversible polarity r.f. d.c. power supply is continuously variable from 0-60 kv. Current output is 1 ma. at 60 kv.

ACTIVATED ROSIN FLUX

Insulation characteristics comparable to those of polyethylene have been successfully combined with extremely fast "take" in a newly developed rosin flux. Known as Lonco insulating rosin flux, this material is devoid of any free acid and is completely noncorrosive, thus providing (1) the fast fluxing action and smooth, even coating necessary in the dip tinning of printed circuits (see photograph), and (2) elimination of

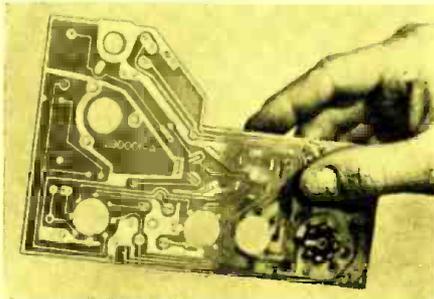

breakdown due to corrosion in the soldering of delicate u.h.f. components.

In addition, this flux is unusually resistant to high temperatures; its ability to withstand prolonged application of heat enables it to solder through badly oxidized copper surfaces and to solder hard-to-bond metals and alloys. For complete information, write to the *London Chemical Co., Inc.*, Dept. R5, 325 West 32nd Street, Chicago 16, Ill.

TRANSFORMER PANELS


Available in three models, the *SKL* Series 303 transformer panels are designed to be used with the *SKL* Series 300 variable electronic filters when a 600-ohm impedance is required. They can also be used when it is necessary to go from a 10,000-ohm impedance to a 600-ohm impedance. The transformers on each panel are arranged to provide either grounded, "floating," or balanced connections.

Model 303A supplies one 600-ohm output, Model 303B supplies two 600-ohm outputs, and Model 303C supplies two

600-ohm inputs and two 600-ohm outputs. For further information, write *Spencer-Kennedy Laboratories, Inc.*, 186 Massachusetts Avenue, Cambridge 39, Mass.

RADIATION MONITOR

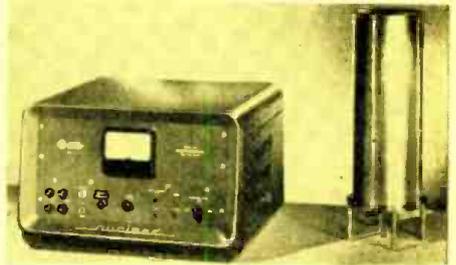Production of the Model 1310 "Remote Monitor," an area monitor developed at Oak Ridge National Labora-



tory, has been announced by the *Nuclear Instrument and Chemical Corporation*, 229 West Erie Street, Chicago 10, Ill. Consisting of an ion chamber and a main chassis, the system is used for measurement of relatively high gamma or neutron flux around reactors and accelerators.

The 4000-cc. ion chamber may be located either at the main chassis or up to 100 feet away, allowing its use in places of high radiation level without exposure of the operator. Visual indication of gamma or neutron radiation up to 125 mr/hr. is provided by a panel meter; a panel "alarm" light indicates any meter reading arbitrarily preset from 5 to 125 mr/hr.

RANDOM NOISE GENERATOR

The Type 811-A random noise generator announced by *Hermon Hosmer Scott, Inc.*, 385 Putnam Avenue, Cambridge 39, Mass., provides entirely random noise with very good normal or



Gaussian amplitude distribution. It is useful for tests in the design and production of sound apparatus and for calibrating acoustical instruments.

Random noise is generated by gaseous discharge in a 6D4 gas tube. Oscillation at high frequencies is eliminated by a magnetic field. Three noise ranges are provided, with a maximum open circuit output of 2 volts r.m.s. In the r.f. range, a constant spectrum level or

(Continued on page 27)

ENGINEERS:

**DOES YOUR
PRESENT JOB
GIVE YOU**

ALL THESE

RCA

CAREER

ADVANTAGES?

**POSITIONS NOW OPEN FOR
SENIOR DEVELOPMENT
AND DESIGN ENGINEERS:**

- ✓ ELECTRONIC . . .
- ✓ COMMUNICATIONS . . .
- ✓ MECHANICAL . . .
- ✓ COMPUTER . . .
- ✓ ELECTRON TUBE . . .

**PERSONAL INTERVIEWS ARRANGED
IN YOUR CITY.** A copy of our booklet
"Challenge and Opportunity," describing the role of the
engineer in RCA, will be mailed upon request. Please
send a complete resume of your education and
experience to:

MR. ROBERT E. McQUISTON, Manager
Specialized Employment Division, Dept. 204-1
Radio Corporation of America
30 Rockefeller Plaza
New York 20, N.Y.

CHECK SHEET

Yes No

- PROFESSIONAL RECOGNITION AND PRESTIGE?
- ADVANCEMENT IN STATUS?
- SECURITY AND STABILITY?
- CHALLENGE AND OPPORTUNITY?
- HIGH SALARY SCALE AND OPPORTUNITIES
FOR PROMOTION?
- EXCELLENT SUBURBAN HOUSING AT
REASONABLE COST?
- FACILITIES FOR PROFESSIONAL
ADVANCEMENT?
- UNEXCELLED TECHNICAL AND LABORATORY
FACILITIES?
- ASSOCIATION WITH TOP SCIENTISTS?
- TUITION REFUND PLAN FOR ADVANCED STUDY?
- MILITARY OR COMMERCIAL OPPORTUNITY?
- MODERATE COST OF LIVING?
- MODERN RETIREMENT PLAN?
- COMPANY-PAID LIFE INSURANCE?
- COMPANY-PAID LIBERAL HOSPITAL, SURGICAL
AND DISABILITY PLAN (FAMILY BENEFITS)?
- LIBERAL VACATION PLAN?
- LIBERAL HOLIDAY SCHEDULE?
- PROFESSIONAL STATUS AND UTILIZATION OF
YOUR EDUCATION AND EXPERIENCE?



RADIO CORPORATION of AMERICA

LOOKING at TUBES

By **WILFRID B. WHALLEY**

Adjunct Professor of Electrical Engineering
Brooklyn Polytechnic Institute

Picture reproducing tubes for color television.

UNTIL quite recently, all devices for reproducing color television could be considered as expedients of one form or another. The assemblies of three picture tubes—using various optical combining methods—have been cumbersome and limited in viewing angle, with image registration quite difficult to obtain, while the use of rotating color discs and drums has somewhat limited the maximum size of the color picture.

Tricolor Requirements

For full color reproduction by electronic control, without the addition of mechanical techniques and complex optical systems, it is desirable to have a single device which—during scanning by preferably only one electron beam—can give any one or a combination of primary colors. With scene brightness controlled by voltage variations on one electrode, it should be possible to change the hue by a change in voltage on another electrode or group of electrodes. In the experimental three-picture tube assemblies described last month, changes in color were controlled by changing

the three grid voltages of the three electron guns.

Also, if the light is to be released from a single surface, such as a multi-phosphor screen at the face of a picture tube, and yet provide equal resolution in each primary color as well as in white, the electron beam diameter must be smaller than for conventional monochrome picture tubes. This is necessary for any arrangement of color phosphors, whether they are in strips or in clusters of dots.

Television broadcasting will always contain a large percentage of black-and-white programs due to the high percentage of monochrome newsreel and feature films. Therefore, it is important that the tricolor picture tube also give good black-and-white pictures. Some tricolor tubes have been developed which give moderately good color pictures, but reproduce black-and-white pictures with low resolution and with variegated tints over the surface.

Early Color Tubes

Following his pioneer work in color television with rotating color discs, John L. Baird made possible the first electronic color reproduction by a relatively simple modification of a standard picture tube. The screen was divided into two sections, one half being settled with one color phosphor while the other was coated with a different color phosphor. The single electron gun could scan any portion of the whole surface.

The scanning system was so arranged that—in combination with the blanking signals on the electron gun—it gave two picture rasters side by side. By correct orientation of the yoke, each image was presented in a single color. Then two optical lenses were positioned in front of the images to project and combine the light on a single viewing surface.

This method of multiarea phosphor color reproduction has been tried many times since, usually with three color areas, but it presents several basic problems. First, the images on the picture tube are reduced in area by the square of the number of adjacent pictures; thus reducing the inherent resolution

of each image. Then, it is quite difficult to obtain separate images with accurately similar horizontal and vertical dimensions and scanning linearities. Combining the color images by the necessary optical systems requires critical adjustment for registration. Also, the total light on the final surface is low, due to the loss of light in such types of optical systems.

Multielectron Gun Tubes


Much of the development in tricolor picture tubes has been influenced by the interest of certain laboratories in "simultaneous" or parallel color systems; many engineers thought that the reproducing device should be capable of supplying light in each of the three primary colors at the same time.

Various proposals were made which endeavored to combine the properties of three separate picture tubes into one envelope. John L. Baird demonstrated a three-gun tube in which two electron beams scanned the front surface of a thin corrugated translucent structure while the third beam scanned the opposite side. The alternate faces of the ridged surface were coated with green and blue phosphor. Thus, one electron beam scanned the green section, the second excited the blue section, and the third beam—on the opposite side—produced light in the red region.

The next proposal was to use a screen made of a great number of small pyramid-shaped pieces. These three-sided pyramids were all oriented in the same direction, with the corresponding face of each coated with one color phosphor. The tube assembly had three electron guns displaced in three necks at approximately 120°, so that each electron beam would scan as closely as possible the same face of each pyramid.

Both of the latter types presented fundamental operating problems. Since the electron beams arrived at the same picture element from different angles, each deflection yoke required special waveforms for both the horizontal and vertical scans. Registration of three images formed on three similar picture tubes is sufficiently difficult; here the waveforms had to be different and yet be very precisely maintained. Also, it was difficult to avoid interaction between the fields of the three yokes.

As a further step in using three electron guns, yet avoiding three separate deflection yokes with the many associated waveforms, a "mask" type tube was developed as shown in Fig. 1. The three electron guns were equispaced around a common axis. Each of the three guns had a similar small tilt angle so that, with no extraneous field present, the three electron beams would coincide as closely as possible near the center of the tube face.

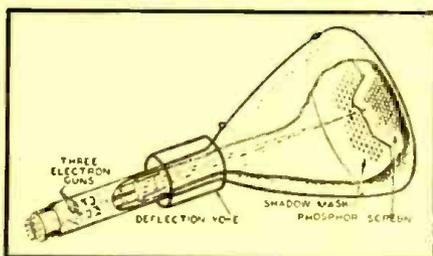


Courtesy of Proceedings of the I.R.E.

Fig. 1. Cut-away view of experimental shadow-mask color kinescope.

Fig. 2. Geometrical relations existing in the color tube shown in Fig. 1.

Courtesy of Proceedings of the I.R.E.

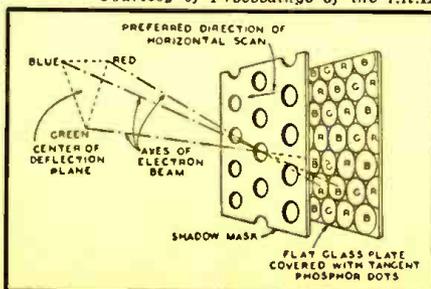

Toward the face of the tube there was a thin sheet of metal having a very large number of small holes. Parallel to this aperture mask was a glass sheet covered with clusters of three phosphor dots, one each for red, green and blue. As may be seen in Fig. 2, it was necessary that there be as many groups of phosphor dots as there were holes in the mask, and that they be accurately positioned to conform with the increasing scanning angle toward the edges of the screen. In this method of reproduction each electron beam passed through an aperture in the mask at a different angle from each of the other two beams, and could therefore excite the correct one of the three phosphor dots.

Since the electron guns were closely spaced, only electrostatic focusing could be used, requiring very careful electrode design. The large gun assembly required correspondingly larger neck and yoke diameters and increased power for deflection. Also, several fundamental problems existed. Since the three beams were displaced in volume at the entrance to the deflection yoke, they would disperse as the scanning angle was increased from the center of the tube. Hence, special deflection yokes, together with auxiliary convergence and "color purification" coils and small correction magnets, were necessary around the neck of the tube in order to provide some compensation. Any variation in second anode voltage required corresponding corrections in the currents through these various coils.

Setting up such a three-gun mask tube required quite critical adjustment of convergence voltages and coil currents, and alignment of the small magnets. This may be clearly realized when the small change in magnetic field necessary to shift one electron beam by one hole spacing is considered. Since the maximum field at the top or bottom of the vertical scan of the picture was only a few hundred gauss, an error in adjustment of one-fifth gauss could cause misregistration of the three electron beams. It might be noted that this field change is much less than that of the earth's magnetic field.

Despite the use of three electron guns, the light output was limited. The small apertures allowed only 10 to 15 % of the electrons to be useful in producing light, the remainder being collected by the mask. Also, there was a practical limit to the maximum scanning angle; if this limit were exceeded, color control would be lost at the edges of the picture. The scanning angle limit caused this type of tricolor tube to be about 1.8 times the length of a typical monochrome picture tube having the same useful picture area.

47 MICROSCOPIC TESTS



on all



RELIABLE SUBMINIATURE TUBES

Raytheon pioneered microscopic inspection of reliable tubes for missiles. The forty-seven microscopic tests were developed by Raytheon as a result of four years of intensive experience with visual inspection. This rigid multiple test procedure has been adopted as standard practice on every Raytheon Reliable Subminiature Tube. It assures utmost dependability.



All these Raytheon Reliable Subminiature Tubes must pass microscopic inspection

Type	Description	Heater		Plate		Grid		Screen		Amp. Factor	Mut. Cond.
		Volts	Ma	Volts	Ma	Volts	Ma	Volts	Ma		
CK5702WA	RF Amplifier Pentode	6.3	200	120	7.5	$R_k = 200$ ohms	120	2.5	—	5000	
CK5703WA	High Frequency Triode	6.3	200	120	9.4	$R_k = 220$ ohms	—	—	—	25.5	5000
CK5744WA	High Mu Triode	6.3	200	250	4.2	$R_k = 500$ ohms	—	—	—	70	4000
CK5783WA	Voltage Reference	Operating voltage approximately 86 volts between 1.5 and 3.5 ma.									
CK5784WA	RF Mixer Pentode	6.3	200	120	5.2	-2	120	3.5	—	—	3200
CK5787WA	Voltage Regulator	Operating voltage approximately 100 volts between 1 and 25 ma.									
CK5829WA	Dual Diode	6.3	150	Max. Peak Inverse 360 volts. $I_p = 5.5$ ma. per plate							
CK6021	Medium Mu Dual Triode	6.3	300	100	6.5	$R_k = 150$ ohms	—	—	—	35	5400
CK6111	Medium Mu Dual Triode	6.3	300	100	8.5	$R_k = 220$ ohms	—	—	—	20	5000
CK6112	High Mu Dual Triode	6.3	300	100	0.8	$R_k = 1500$ ohms	—	—	—	70	1800
CK6152	Low Mu Triode	6.3	200	200	12.5	$R_k = 680$ ohms	—	—	—	15.8	4000

Note: All dual section tube ratings (except heater) are for each section.

Write for New Edition of
RAYTHEON RELIABLE SUBMINIATURE TUBE BOOKLET



RAYTHEON MANUFACTURING COMPANY


Receiving Tube Division — for application information call

Newton, Mass. 02450 • Chicago, Ill. NAional 2-7770 • New York, N.Y. Whitehall 3-4980 • Los Angeles, Calif. Richmond 7-5324

RAYTHEON MAKES ALL THESE

RELIABLE SUBMINIATURE AND MINIATURE TUBES • GERMANIUM DIODES AND TRANSISTORS • NUCLEONIC TUBES • MICROWAVE TUBES • RECEIVING AND PICTURE TUBES

Personals

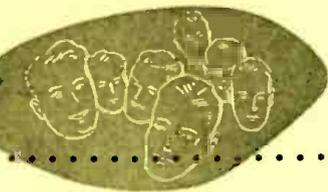

RODNEY D. CHIPP, director of engineering for the *Du Mont Television Network*, has been elected president of the Technical Societies Council of New York, Inc.; he served as director and treasurer during the past year. Associated with broadcasting since 1933, Mr. Chipp has been with *Du Mont* in his present capacity since 1948. He was the 1950-1951 chairman of the New York Section of the IRE and is a member of many other technical societies.



DR. WILLARD GEER, who invented one of the three recognized tubes in color television and is a patent holder of several other developments in the field, has been appointed a consultant on color in TV and military applications at the *Hoffman Radio Corporation* and *Hoffman Laboratories, Inc.*, Los Angeles, Calif. Dr. Geer is currently associate professor of physics at the University of Southern California and has been a faculty member there since 1943.



LEO G. KILLIAN has been appointed director of technical publications for *The Cook Research Laboratories*, a division of *Cook Electric Company*, Chicago, Ill.; he has been in charge of the preparation of technical reports, over-all project liaison and contract coordination since 1947. Holder of an M.S. degree in electrical engineering, Mr. Killian's past experience includes design, research and development work in the fields of radio, sound and electronics.



GORDON C. KNIGHT is the new manager of the Lodi, N. J., Television Transmitter Division of *Federal Telecommunication Laboratories, Inc.*, research associate of *IT&T*. Assistant to the president of *IT&T* since last August, Mr. Knight will now be responsible for the development and production of the Division's complete television line. He was formerly associated with the *Capehart-Farnsworth Corporation* in various capacities.



JOHN M. PEARCE, former president of *Phebeco, Inc.*, has joined the Electronics Division of *American Machine & Foundry Company* in Boston, Mass., as director of engineering. Active in radio and electronics since 1925, Mr. Pearce received the Presidential Citation of Merit for his contribution to the proximity fuse program at Johns Hopkins University during World War II. He was engaged in the development of guided missiles for many years.



W. WALTER WATTS has been elected a director of *Hydrocap Eastern Inc.*, Philadelphia, Pa., a subsidiary of *Industrial Research Inc.* of Miami, which specializes in newly developed catalyst storage battery caps. Col. Watts (U. S. Army Signal Corps) just recently was made vice-president in charge of technical products of the *RCA Victor Division*; his earlier associations were with *Montgomery Ward, Inc.*, and *Zenith Radio Corporation*.

Transistor Characteristics

(Continued from page 9)

Figures 12 through 26 (except Fig. 20) are distributions of performance for the CK721 and CK722 in the three amplifier connections. Units below the tentative limits shown on previous curves have been eliminated.

The input impedance of the CK721 in the grounded emitter circuit for two values of load is given in Fig. 12; Fig. 13 is the output impedance for two values of R_o . It may be seen that increasing the load resistance lowers the input resistance. Similarly, raising the generator resistance lowers the output resistance. In the grounded base circuit, the opposite is true. Figures 14 and 15 show the same data for CK722.

Relative gain distribution of the CK721 and CK722 in the grounded emitter circuit for one load and generator condition is given in Fig. 21. Gain as used here is defined as the output power delivered to the indicated load divided by the available power from the generator. In the grounded emitter connection, because gain is strongly dependent on $1/(1-\alpha)$, the CK721 is appreciably better than the CK722. Of course, the generator and load conditions favor the CK721, but it takes almost a 3:1 mismatch to cause a 1-db loss in power; so, to a certain extent, the mismatch is not serious.

Presented in Figs. 16 and 17 are the grounded base input and output resistances (CK722) for two values of R_L and R_o . 100K has been used as a load resistance—although the matched condition indicates a higher value—in deference to the fact that 100K is a more practical limiting value for the small transformers used in transistor circuits. Figures 18 and 19 show the same data for the CK721 and Figs. 22 and 23 compare the grounded base gain of the two types for two values of R_L . Note that the gain of the CK721 and CK722 under these conditions is quite comparable, and although the gain is less than that of the grounded emitter connection, the variation in gain is markedly reduced. (The average gain of the CK721 in the grounded emitter connection was about 38 db with a variation of 16 db while in Fig. 23, where $R_L = 20K$, it centers at about 26 db with only a 7-db variation.) The reduction in variability when the grounded base circuit is used is, of course, due to the fact that the alpha variation is small and that the gain, particularly under conditions of mismatch, tends to be more a function of R_o and R_L than of the transistor parameters.

Figure 24 is for the grounded collector circuit and shows output impedance of the CK721 and CK722 for

a generator resistance of 500K, while Fig. 25 shows input impedance for a load of 20K. In the interest of high input resistance, it is desirable to use a very high load resistance; unfortunately, the opposite is true if optimum gain is to be realized. A 20K load has been used here to hold up the gain, and it is, of course, more typical of what can be done with small transformers. Ordinarily, the grounded collector connection is preferred because it can provide high input resistance in an amplifier without the use of transformers. As the input resistance is a function of R_c and $1/(1-\alpha)$, it is desirable to operate with very high R_c —which, as has already been demonstrated, can be obtained at lower collector currents than 2 ma. without appreciable loss of alpha level.

Gain distributions for the grounded collector connection of the CK722 and CK721 are given in Fig. 26. The CK722 is obviously not recommended for this connection. Gain variability in this circuit is similar to that in the grounded emitter circuit.


The foregoing analysis may be summarized as follows:

1. Presently available transistors are quite variable in characteristics, and although more is being learned daily about control, units must still be selected after manufacture.
2. Some form of d.c. compensation is almost mandatory to control operating points.
3. Although the highest gains are available using the grounded emitter amplifier connection, the spread of gain in the grounded base amplifier is less.
4. Designers of transistor amplifiers for production purposes would do well to sacrifice appreciable stage gain by suitable feedback in order to reduce unit-to-unit variability.

REFERENCE:

1. Shea, R. F., "Transistor Operation—Stabilization of Operating Points," *Proceedings of the IRE*, November, 1952.

Fig. 26

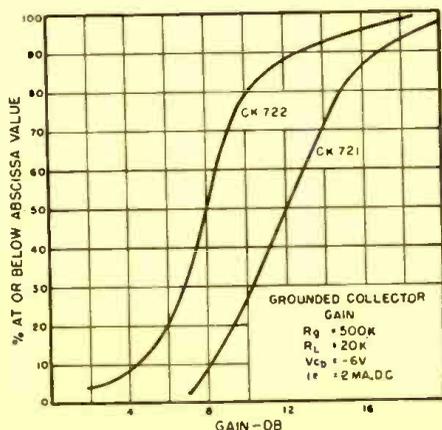

Introducing **KULGRID**

(NICKEL-CLAD COPPER WIRE)



...today's best answer to high temperature electrical-conductive problems

Electrical engineers in many industries now give Sylvania's Kulgrid the highest rating. This improved nickel-clad copper wire maintains excellent electrical conductivity at advanced temperatures. Its heavy nickel coating resists corrosion and guards the copper conductor against oxidation, flaking, brittleness or deterioration.

KULGRID RESISTS HIGH TEMPERATURES AND CORROSION... FIGHTS OFF BRITTLENESS



IDEAL FOR MANY APPLICATIONS

Kulgrid shows exceptional stability and performance in the high temperature operation of vacuum tubes. Other applications include: wiring of electric furnaces, industrial baking ovens, electric stoves, and numerous aircraft electrical installations, including jet engines.

AVAILABLE IN STRANDED FORMS

You can now obtain Kulgrid in stranded forms in various combinations of diameters and numbers of strands. Kulgrid welds readily to itself, nickel, copper, and can be welded to tungsten and molybdenum. New illustrated booklet gives detailed data. For your copy, address: Sylvania Electric Products Inc., Dept. 3A-3509, 1740 Broadway, New York 19, N. Y.



ANOTHER OUTSTANDING DEVELOPMENT BY SYLVANIA

SYLVANIA

LIGHTING • RADIO • ELECTRONICS • TELEVISION

In Canada: Sylvania Electric (Canada) Ltd., University Tower Building, St. Catherine St., Montreal, P. Q.

NEW LITERATURE

RESISTORS AND VARISTORS

Comprehensive data on two *IRC* products have been offered by the *International Resistance Company*, 401 N. Broad Street, Philadelphia 8, Pa.

Tubular and flat power wire-wound resistors are discussed in Catalog Bulletin C-1, a 12-page bulletin with photographs, detailed charts and graphs. Topics covered are adjustable features, brackets, characteristics, coating, dimensions, derating, insulation, specifications, tolerances and windings.

Catalog Bulletin SR-3 (available from the Special Products Division) is a six-page bulletin on varistors. Data on these nonlinear resistors include voltage-current characteristics, current ratings, temperature characteristics, typical applications and dimensions.

CAPACITORS

Bulletin AB-20A contains complete performance characteristics and test specifications on the new "Blue-Point"

molded plastic capacitors (patent pending.) It is available from *Astron Corporation*, 255 Grant Avenue, East Newark, N. J.

These capacitors are housed in molded plastic cases and are permanently sealed against heat and moisture by means of a solid, glass-like, thermosetting bond which also locks in the leads so that they cannot be pulled out. Neither lead, bond nor case is affected by flame or soldering iron heat, regardless of how closely they may be applied.

HIGH VACUUM PUMPS

F. J. Stokes Machine Company has issued an extensively revised edition of the 36-page catalog entitled "Stokes Microvac Pumps for High Vacuum." Known as Catalog No. 750, it includes: valuable tables of formulas, constants, and conversions frequently used in vacuum processing; solutions to problems of pump selection for typical vacuum systems; and useful information on continuous oil purification and other maintenance procedures for high vacuum pumps.

Copies of Catalog No. 750 may be obtained free on request to *F. J. Stokes Machine Company*, 5500 Tabor Road, Philadelphia 20, Pa.

CAPACITY MICROPHONE

In a four-page brochure, *International Research Associates*, 222 Warwick Avenue, Santa Monica, Calif., describes and illustrates the Model D-42 capacity type microphone. Small, sensitive and extremely linear, yet rugged enough to withstand shocks up to 200G, the Model D-42 is suitable for such applications as aircraft vibration detection, naval and medical research, and seismographic surveys. It reproduces acoustic levels in excess of 170 dbm and has a flat response from d.c. to 12.5 kc.

MODIFIED POLYSTYRENES

Characteristics and applications of *Koppers* modified polystyrenes are discussed in a 14-page technical bulletin which has been published by the Chemical Division of *Koppers Company, Inc.* Of the seven types of this thermoplastic material covered, four provide high elongation and high impact resistance while three provide medium elongation and medium impact resistance.

Information on parts manufacture,

injection molding, compression molding, extrusion and finishing is presented in Technical Bulletin C-3-161, which may be obtained on request from *Koppers Company, Inc.*, Chemical Division, *Koppers Building*, Pittsburgh 19, Pa.

MICROWAVE EQUIPMENT

A new line of microwave instruments and components is set forth in a four-page bulletin now available from *Narda, Nassau Research & Development Associates, Inc.*, 66 Main Street, Mineola, N. Y. Frequency meters, mixers, impedance meters, attenuators and other microwave equipment are listed.

SHOCK MACHINE

The Type 150-400 VD shock machine is designed to perform calibrated shock tests up to 77G peak acceleration, simulate the types of shock required for Government acceptance tests of airborne equipment, and carry out uniformly reproducible qualification tests for development engineering and quality control.

Barry Product Bulletin 533 gives detailed dimensions and construction features of this machine, operation and installation instructions, and calibrated performance data covering range of operation. It is available on request from *The Barry Corporation*, 870 Pleasant Street, Watertown 72, Mass.

CONTROL CENTERS

Federal Electric Products Company, 50 Paris Street, Newark 5, N. J., has issued a booklet on its "Noark" control centers. Each control assembly consists of a standardized, prefabricated steel enclosure, 20" x 20" x 94", in which are mounted *Federal* "Noark" motor starters of any required NEMA size, together with circuit breaker disconnect.

Besides listing specifications and enclosure sizes, the 16-page leaflet emphasizes the advantages of centralized control in a plant, describes exclusive features of these control centers, and shows photographic examples of typical installations.

FLEXIBLE DELAY LINES

A single-page bulletin has been released by *Richard D. Brew & Company, Inc.*, 106 Concord Avenue, Belmont 78, Mass., which describes and gives specifications for two types of flexible delay lines.

Type "A" lines are short lines in hermetically sealed stick form, with delays ranging from .1 μ sec. minimum to 3 μ sec. maximum; Type "B" lines are longer, in hermetically sealed cans, with delays ranging from 2 to 10 μ sec. Both are guaranteed to conform to delay specifications within $\pm .05 \mu$ sec.

In Stock at **TERMINAL**
for Prompt Delivery

- **CANNON** Connectors
- **CHICAGO** Transformers
- **PHASTRON** Ruggedized Meters
- **SOLA** Regulators
- **SUPERIOR** Powerstats
- **VICTOREEN**

Depend on **TERMINAL**

for ALL Your Electronic Needs!

FAST SERVICE—LOWEST PRICES—On all Standard Electronic Equipment for Industry, Laboratory, Communications. Literature on request.

FREE! NEW 1954 AUDIO CATALOG

Get your name on our Mailing List for this LATEST and GREATEST Audio Buying Guide of its kind! Write: Dept. RE-9.

Visit Our Salesrooms

Phone: WOrth 4-3311



Terminal
RADIO CORP.
85 Cortlandt St. • New York 7, N. Y.

New Products

(Continued from page 20)

flat frequency response exists to 1 mc., with the response sloping off thereafter at approximately 12 db per octave.

VARIABLE INDUCTOR

Improved stability is made possible through the use of a permanent-magnet bias in the Model PA-63 *Vari-L* variable inductor. In many FM and sweep applications, this feature eliminates the problem of assuring a well-regulated supply of d.c. to the control winding. The entire unit operates at a lower temperature, at high frequencies and high *Q*, without the constant presence of high saturating currents. Its sensitivity is shown by the fact that control-current changes of the



order of 0—10 ma. will accomplish inductance changes of several hundred per cent.

Described as a manually variable, high frequency, saturable-core reactor, the Model PA-63 also features provision for manual tuning—when desired—by movement of a metal slug to shunt the magnet bias. Complete details may be obtained from *The Vari-L Company, Inc.*, P. O. Box 1433, Stamford, Conn.

PHASE MONITOR

The *Andrew* Type 40-C phase monitor is a direct-reading phase-measuring instrument designed to facilitate adjustment and maintenance of broadcast directional antenna arrays. Phase angles are indicated directly in degrees on a single meter, permitting immediate observation of the effects of small antenna system adjustments. Relative amplitude of antenna currents can be quickly and accurately determined, the ratio appearing on a special current ratio scale on the indicating meter.

Available from the *Andrew Corporation*, 363 East 75th Street, Chicago 19, Ill., the Type 40-C contains no calibrated phase-shifting circuits which might become misadjusted. Six indi-

vidual input circuits accommodate directional systems utilizing as many as six towers; front panel switching permits rapid selection of any two input signals for comparison.

Balanced Modulator

(Continued from page 11)

frequencies within the range of 60 to 2500 mc. For ordinary amplitude modulation, the bias balance can be offset to insert the desired amount of carrier, and 100% linear modulation obtained.

Response vs. modulation frequency of the Type 1000-P7 is given in Fig. 8. The simplicity of the circuit makes it relatively easy to achieve a response flat to 20 mc.


Figure 2B is a photograph of an r.f. output pulse at a 60-mc. carrier frequency. The applied pulse also shown was 0.2 μ sec. long and had a 50-millimicrosecond rise time and about a 100-millimicrosecond fall time; it was faithfully reproduced in the r.f. envelope. The balanced modulator itself has a rise time of better than 20 millimicroseconds.

The setup that produced the pulse shown in Fig. 2B consists of a v.h.f. signal generator supplying the 60-mc. carrier, the balanced modulator, and a pulser with its own power supply. A flexible cable provides an extension of the phasing line. The trombone section

alone is suitable for 400 to 2500 mc., and flexible cable extensions are used at the lower carrier frequencies where the adjustable line alone has insufficient range.

Modulation characteristics of the balanced modulator are independent of signal level below 50-mv. input. Higher signal levels shift the operating points of the diodes and offset the balance. Operation at higher levels is possible if balance is set for each level. The Type 1000-P7 modulator is made to work with a generator of 50-ohms output impedance and into a 50-ohm load. Under these conditions and with a generator voltage of 50 mv., 10-mv. output on modulation peaks for linear amplitude or pulse modulation can be obtained.

Fig. 8. Modulating frequency characteristic of the Type 1000-P7 modulator.

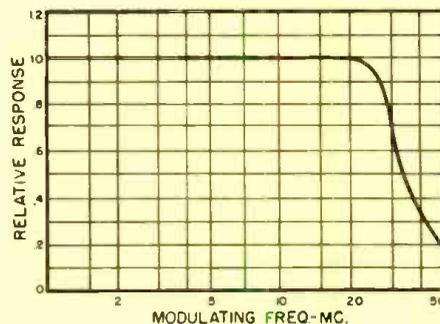

CLOSE-TOLERANCE CONSTRUCTION PLUS...

QUALITY CONTROL... brings you the best in paper tubes

PRECISION PAPER TUBES

Made of the finest dielectric kraft, fish paper, acetate, combinations or phenol impregnated materials, PRECISION Paper Tubes are die-formed under heat and pressure. Uniformity, strength, and light weight are assured. High manufacturing standards and rigid testing result in maximum insulation, heat dissipation, and moisture resistant characteristics.

Available in any shape, length, I.D. or O.D. Finished to your exact specifications.

SEND TODAY FOR FREE SAMPLE AND REQUEST NEW ARBOR LIST OF OVER 2000 SIZES.

PRECISION PAPER TUBE CO.

2063 W. CHARLESTON ST. CHICAGO 47, ILL.
 Plant No. Two, 79 Chapel St., Hartford, Conn.
 Also Mfrs. of Precision Coil Bobbins

TRANSMITTING AND SPECIAL PURCHASE TUBES

PERFECT AND GUARANTEED
STANDARD BRANDS
AT LESS THAN SURPLUS PRICES

Tube No.	NET, Each	Tube No.	NET, Each	Tube No.	NET, Each
1B22	\$2.95	217C	9.50	868A	1.45
1B23	9.50	218	39.50	869B	75.00
1B24	9.95	221A	1.50	872A	4.20
1B27	14.50	222	4.50	874	1.45
1B29	2.50	231D	4.50	878	9.95
1B32	3.75	237A	200.00	884	1.69
1P21	29.50	245B	8.50	891R	195.00
1P28	10.50	249C	9.50	892R	195.00
2AP5	9.50	250R	22.00	902P1	9.50
2C22	1.95	250TH	22.50	915	4.95
2C22	.29	250TH	19.00	918	2.85
2C26	.39	252A	19.00	923	1.85
2C26A	14.50	257B	10.00	924	2.10
2C34	.49	268A	4.50	931A	6.00
2C40	9.50	271A	4.50	950	1.25
2C43	14.50	174B	1.95	972	12.50
2021	1.80	276A	9.95	955	.69
2E22	1.95	282A	8.00	956	.69
2E24	3.95	282A	9.95	957	.69
2E26	5.25	284D	7.50	958A	.99
2E32	1.25	286A	9.50	972A	4.20
2E36	3.95	289A	4.95	973	12.50
2J22	9.00	289A	4.95	975A	9.95
2J26	25.00	294A	4.95	991	.49
2J27	23.00	297A	4.95	1602	1.95
2J30	25.00	317A	9.95	1603	1.95
2J31	29.50	304TH	19.50	1608	5.75
2J32	37.50	304TH	14.50	1612	2.50
2J33	35.00	304TH	14.50	1613	1.95
2J34	32.00	309A	4.95	1814	2.50
2J37	19.50	310A	9.50	1818	1.95
2J38	35.00	311A	9.50	1819	.49
2J48	35.00	313C	1.95	1820	6.60
2J49	75.00	316A	3.00	1821	1.95
2K20	75.00	317A	4.50	1822	2.60
2J48B	37.00	328A	9.50	1823	2.00
2J62	45.00	329A	9.50	1824	1.74
2K23	85.00	331A	14.50	1825	.49
2K25	25.00	336A	9.50	1826	.37
2K28	35.00	337A	7.95	1828	2.75
2K29	27.50	338A	7.95	1829	.45
2K33	265.00	350A	8.50	1830	1.95
3B22	3.50	350B	9.00	1831	1.65
3B23	4.95	352A	14.50	1832	.75
3B28	6.75	354C/D	22.50	1833	1.25
3B28	4.95	WE355A	22.50	1835	1.85
3BP1	4.50	357A	19.50	1836	3.00
3C22	80.00	359B	22.50	1838	5.00
3C24	1.75	367A	22.50	1842	.75
3CP1	4.50	368A5	.95	1844	.90
3C31	4.50	373A	4.95	1845	1.95
3C45	19.00	374A	4.95	1855	1.95
3DP1	7.50	375A	4.95	1665	1.75
3D21A	5.00	383A	4.95	1850	1.75
3EP1	4.95	385A	4.75	2050	1.75
3E29	14.00	387A	4.75	2051	.99
3FP7	2.75	388A	4.75	5926	4.95
3GP1	5.00	394A	4.25	5610	1.95
3JP7	20.00	398A	7.50	5654	3.95
3KP1	12.50	399A	2.50	5663	3.95
4FP10	4.50	400A	3.50	8870	9.50
4B24	9.50	401A	2.95	5686	7.00
4B25	7.50	408A	3.30	5687	4.70
4C27	45.00	417A	13.90	8722	6.40
4C35	25.00	450TH	50.00	3763	1.55
4D32	22.00	450TH	50.00	5814	3.25
4E27	19.00	471A	9.50	3629	3.95
4J26	99.50	527	15.00	5881	2.95
4J52	199.50	521	8.75	8005	9.50
4-125A	10.25	522A	3.95	8008	7.50
4-250A	41.25	575A	19.50	8011	1.75
5AP1	4.50	631P1	9.95	8012	2.75
5BP1	5.50	700B	20.00	8013A	4.95
5BP1A	12.50	700C	27.00	8020	100R
5BP4	8.50	701A	5.95	8025	2.20
5CP1	5.50	702A	4.95	F128A	80.00
5CP1A	22.50	703A	7.95	F137A	22.50
5CP7	10.75	704A	1.60	F568	135.00
5CP7A	25.00	705A	2.00	FG17	4.95
5O21	19.50	708A	19.00	FG27A	9.95
5FP7	4.50	708A	4.85	FG33	17.50
5FP14	19.50	708A	3.75	FG38A	9.95
5GP1	8.95	710A	10.50	FG97	9.95
5MP4	5.50	713A	1.95	FG104	19.00
5JP2	22.50	714A	8.50	FG105	22.50
5J23	22.50	714A	15.00	FG166	67.50
5J29	85.00	717	1.95	FG172A	35.00
5N1	8.00	718BY	49.50	GL15	20.00
6C21	24.50	721A	5.00	GL502A	1.75
7B1	8.00	722A	1.95	GL502	1.75
7BP7	8.00	722B	18.00	GL530	16.95
7C23	75.00	724A/B	3.25		
7C25	90.00	725A	9.75		
7DP4	14.50	726FY	24.50	HF60	8.50
7EP4	14.50	728FY	24.50	HF75	7.95
9C23	200.00	730A	35.00	HF100	7.95
9GP7	9.50	730A	8.00	HF120	9.95
9JP1	9.50	801	1.25	HF130	12.50
9L57	14.50	802	4.20	HF140	9.95
10CP4A	19.50	803	3.90	HF150	9.95
10V	14.50	805	4.95	HF200	17.50
12DP7	14.50	806	17.50	HF210	22.50
12FP7	14.50	807	1.50	HF250	15.00
12NP7	14.50	808	8.50	HK254	5.50
12KP4	19.50	809	4.00	HK354	22.50
12TP4/12LP4	19.50	810	13.50	HK37	3.95
15E	1.50	811	3.10	MY75	2.95
15P	1.50	812	5.00	RM47	3.95
16NP4	19.50	813A	12.00	RM53	1.45
17BP4A	24.50	813	5.28	RM60	1.95
20-4	.95	814	14.50	RM63	22.50
23B4	9.00	815	3.70	RM65	24.50
25T	9.00	816	1.50	RM72	9.95
35T	10.00	826	.75	RM73	.95
75TN	13.50	828	12.50	RM21	2.75
75TL	12.95	829	12.50	T20	4.95
100TH	9.50	829B	14.50	T40	2.50
100TS	9.50	830	4.50	W125	6.50
121A	3.50	832	8.50	T200	12.50
128	4.30	832A	9.00	T250	14.50
182B	4.30	834	13.50	T240	2.95
201C	12.50	836	5.35	UN50	4.50
205B	12.50	837	2.85	UN75	1.25
205F	12.50	838	8.50	VR90	1.25
207	195.00	841	.65	VR105	1.25
211	.95	842	1.95	W4411B	.50
215A	.15	845	12.75	WL460	17.50
		849	99.50	WL530	49.50
		851	49.50	WL530	49.50
		852	27.50	WL562	49.50
		856	27.50	WL762	99.50
		861	27.00	ZB3200	99.50
		865	2.75		

NEW TUBES

DECADE COUNTER TUBE

The "Vidicount-E1T" is a specially designed decade counter tube, based on cathode-ray tube principles, which has the dimensions of a radio receiving tube. Just announced by *Ampere Electronic Corporation*, 230 Duffy Avenue, Hicksville, L. I., N. Y., it makes possible the elimination of a number of tubes and components in decade circuits as well as a considerable reduction in power requirements.

According to the number of counting pulses applied, the ribbon-shaped electron beam of the tube passes through ten apertures of a cylindrical anode,

area junction results in rapid switching action and good high-frequency characteristics. In addition, these diodes are capable of withstanding high temperature-humidity ambient conditions.

TEMPERATURE-LIMITED DIODES

Complete specifications for six temperature-limited diodes having a stable emission characteristic are given in a four-page folder published by *Thermosen, Inc.* Three of the tubes incorporate a safety feature by which filament failure closes an external high-impedance circuit.

Copies of the folder, which includes illustrations of all the tubes, electrical and mechanical specifications, basing diagrams and basing designations, may be obtained by writing directly to *Thermosen, Inc.*, 361 West Main Street, Stamford, Conn.



SUBMINIATURE RECEIVING TUBES

Particularly suitable for military use, Types GL-6111 and GL-6112 subminiature receiving tubes are the latest additions to the *G-E* "Five-Star" line of high reliability tubes. Complete details on these tubes, both of which are designated for service under severe mechanical shock and vibration conditions and high ambient temperature, are available from the *General Electric Tube Department*, Schenectady 5, N. Y.

thus impinging on a fluorescent screen lining the envelope. Rectangular, luminescent spots corresponding to the number of pulses are read on the outside of the tube envelope opposite the figures from 0 to 9. As the last position is passed, the beam automatically resets to its zero position and a counting pulse is simultaneously applied to the following tube. With several such tubes in cascade, any number can be read directly.

The GL-6111 is a medium-mu twin triode designed for use in general-purpose amplifier applications. Each section has an individual cathode and is electrically independent. This tube may also be used as a combined oscillator and mixer in high-frequency circuits.

The GL-6112 is a high-mu twin triode suitable for use as an a.f. voltage amplifier or phase inverter. As a result of its low microphonic characteristics, the GL-6112 can be employed at relatively low signal levels.

SMALL-AREA JUNCTION DIODES

A line of small-area junction diodes has been announced by the Transistor Division of the *National Union Radio Corporation*, Hatboro, Pa. The three types currently available include: 1N106—a high back-voltage diode, 1N107—a high forward-current diode, and 1N108—a general-purpose unit.

Of extremely small size, the "Union" diodes have relatively high dissipation ratings and ratios of back-to-forward resistance an order of magnitude greater than those obtainable in conventional point-contact diodes. Use of the small-

SILICON DIODES

Eleven silicon diodes for microwave and video use are described in a four-page brochure available from *Micro-wave Associates, Inc.*, 22 Cumington Street, Boston, Mass. Designated as Catalog 53S, the brochure contains distribution charts and tables on diodes for use from 10 cm. to less than 1 cm. Special mention is made of new low-noise, uniform-impedance characteristic detectors for radar and the microwave relay frequencies.



MINIMUM
ORDER
\$10.00

RADIO SUPPLY CORP.
55 VESEY STREET • NEW YORK 7, N. Y.
Phone: Dlgby 9-1132

R.F. Power Measurements

(Continued from page 6)

to its proper length by first determining the exact frequency of the power source being used and then adjusting the length of the transformer accordingly.

The insulated quarter-wave transformer is thermally calibrated, and a test made of the effectiveness of the insulation, by using the braid of a coaxial cable or the metallic surface of other components as a reference. The braid temperature of a cable, the surface temperature of a connector, or any reference temperature other than the center conductor temperature is directly proportional to the center conductor temperature at any given power level after steady state conditions have been attained. Therefore, if this reference temperature in the vicinity of the quarter-wave transformer remains constant before and after the transformer insertion, the center conductor temperature also remains constant, and the insertion of the insulated transformer does not affect the true center conductor temperature.

A series of tests, in which the center conductor temperature of polyethylene and Teflon dielectric coaxial cables was measured, confirmed the above analysis.

Measurements were made at various power input levels and the reference temperatures measured. The insulated quarter-wave transformer was then inserted into the cable between the reference thermocouples, and the measurements of the reference temperatures were repeated at the various input power levels. Results of measurements made with an RG-9/U (polyethylene dielectric) and RG-87A/U coaxial cable (Teflon dielectric) are presented in Fig. 6. The reference temperatures before and after insertion at the same power level remained constant, indicating that the center conductor temperature also remained constant. The insulated transformer, therefore, did not affect the heat flow characteristics of the component into which it was inserted.

Since the quarter-wave transformer measures center conductor or—more generally—internal temperatures of r.f. components, it may also be calibrated as an input or through power meter by means of the calorimeter. The center conductor temperature rise at various power levels may be calibrated as a function of input power. A quarter-wave transformer, similar to Type B of Fig. 4, may be readily utilized with an air dielectric and rigid outer tube for use as a power indicator.

Applications

The calorimetric water load and the quarter-wave temperature indicator were successfully utilized in power rating tests of high temperature Teflon

and liquid dielectric coaxial cables recently developed for use in airborne installations at elevated temperatures. Although in the measurement of the power-handling capacities of coaxial cables it is necessary to measure surface and environment temperatures accurately in addition to input power, output power, (if attenuation data is required), and center conductor temperatures, this discussion is primarily concerned with the power and center conductor measurements.

Briefly, the cable to be power-rated was connected to a high power source (a *General Electric* magnetron heater capable of delivering up to 5000 watts at a frequency of 915 mc.) and terminated by the calibrated calorimeter. A quarter-wave transformer was inserted into the cable at the point of maximum center conductor temperature (determined by preliminary surface temperature measurements) to give maximum center conductor temperatures at the various input power levels.

The quarter-wave transformer, the magnetron output meter, a high power slotted line with susceptance stub, or an r.f. wattmeter can be utilized to measure input power when accurately calibrated with the calorimetric water load. Obviously, the most easily adapted procedure for this investigation was the use of the magnetron output meter, the sensitivity of which was increased by means of a resistor network. It was conveniently calibrated by attaching the calorimetric water load directly to the magnetron heater output. The calibration curves are shown in Fig. 7; the output meter indications for various power levels and sensitivities are obtained as a function of the cooling water temperature difference. These curves may then be combined with the calorimeter calibration curves of Fig. 5 to obtain the final working curve of the magnetron meter indication vs. the true r.f. power values shown in Fig. 8. Thus, the power input may be obtained by inserting the coaxial cable between the calorimeter and the magnetron, and reading the values directly. Use of the calorimeter for measuring output power may be eliminated by calibration of the r.f. wattmeter, which may be attached to the calorimeter and used in the same way as the output meter of the magnetron heater.

BIBLIOGRAPHY:

- Jakob, Max, "Heat Transfer," Volume I, John Wiley and Sons, Inc., 1949.
Montgomery, C. G., "Technique of Microwave Measurements," Radiation Laboratory Series XI, McGraw-Hill Book Company, 1947.
Soria, R. M., Krisilas, J. G., and Camillo, C. C., "High Power Transmission Through Liquid Dielectric Coaxial Cables of Small Diameter," Proceedings of the First Conference on Cooling of Airborne Electronic Equipment, and Engineering Experiment Station Bulletin No. 148, Ohio State University.
"UHF Power Measurements," *The Aerovoz Research Workers*, Vol. 21, No. 5, The Aerovoz Corporation.

WILEY Books

CIRCUIT THEORY OF ELECTRON DEVICES

By E. MILTON BOONE,
The Ohio State University

The author believes that the easiest way to understand most electron devices is by studying their over-all circuit behavior. For that reason, he emphasizes the circuit theory, rather than the physics, of electron devices. Outstanding features include: utilization of the concepts of four-terminal networks, generalized so as to apply to any electron device over any frequency range in which the device operates within the linear region of its characteristics... a complete chapter on the linear circuit theory of transistors... careful integration of tube and transistor circuit theory... thorough analysis of circuit behavior of electron devices.

1953 483 pages illus. \$8.50

FUNDAMENTALS OF ENGINEERING ELECTRONICS

2nd Edition

By WILLIAM G. DOW,
University of Michigan

A realistic presentation of the principles that govern the internal behavior of electronic devices. Completely revised and up-to-date.

1952 627 pages illus. \$8.50

FIELDS AND WAVES IN MODERN RADIO

2nd Edition

By SIMON RAMO, Hughes Aircraft Co.,
and JOHN R. WHINNERY,
University of California

All the electromagnetic theory you need for a practical understanding of fields and waves in present-day radio... presented in a simple yet thorough manner.

1953 576 pages illus. \$8.75

ESSENTIALS OF MICROWAVES

By ROBERT B. MUCHMORE,
Hughes Aircraft Co.

Fundamental laws... and applications of microwave equipment—all interpreted, described and judged on the basis of measurements that can be made.

1952 236 pages illus. \$4.50

STORAGE TUBES

AND THEIR BASIC PRINCIPLES

By M. KNOLL and B. KAZAN,
RCA Laboratories

Storage tubes discussed in terms of their common technical characteristics; their methods of operation are separated and classified in terms of fundamental processes.

1952 143 pages illus. \$3.50

Mail Coupon for FREE Examination

JOHN WILEY & SONS, Inc.
440 4th Ave., New York 16, N. Y.

Please ship books checked below for FREE examination. Within 10 days I will remit price plus postage for any I wish to keep, and return any I do not wish to keep.

- CIRCUIT THEORY OF ELECTRON DEVICES, \$8.50
 FUNDAMENTALS OF ENGINEERING ELECTRONICS, \$8.50
 FIELDS AND WAVES IN MODERN RADIO, \$8.75
 ESSENTIALS OF MICROWAVES, \$4.50
 STORAGE TUBES and Their Basic Principles, \$3.50

Name


Address

City..... Zone.... State.....


SAVE POSTAGE. Enclose check or money order now and we pay postage. Prompt refund on any books you return. REE93

NOW GIVE BETTER . FASTER SERVICE

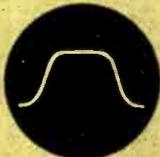
INVEST in KAY INSTRUMENTS THAT SAVE YOU TIME AND INCREASE YOUR PROFITS



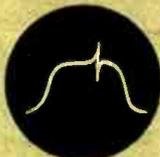
Calibrated MEGA-SWEEP
50 kc to 950 mc range
Sweep width at least 30 mc



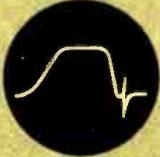MEGALIGNER—a calibrated
variable frequency
IF marker pip generator



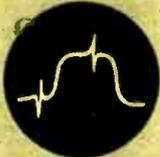MEGA-MARKER SR.
crystal controlled, 12-channel
TV RF sound carrier generator



DUAL MEGA-MARKER SR.—same
as Mega-Marker Sr. with RF
picture carrier generator added

Consult
this latest
64-page
catalog
FREE



Write . . .

KAY ELECTRIC CO.

12 MAPLE AVE. PINE BROOK, N. J.

TECHNICAL BOOKS

"ELECTRON OPTICS" by O. Klemperer, Ph. D. Second Edition. Published by *Cambridge University Press*; American Branch, 32 East 57th Street, New York 22, N. Y. 471 pages. \$9.50.

One of the Cambridge Monographs on Physics, this book gives a concise account of the most important principles, methods and applications of geometrical electron optics. Expanded to six times its original size, the present edition is intended to introduce the student to a specialized subject and to present the research worker or the designer of electron optical gear with essential information on the subject. An extensive bibliography is included as a guide to the literature; it lists some 500 papers.

The first five chapters give an outline of principles and facts about electron lenses. Lens errors are then discussed from an essentially experimental point of view. Following chapters discuss space charge and electron optics, emission systems, electron lenses and emission systems with line focus, and deflecting fields. Finally, a short survey is made of important applications of electron optics in both industry and research.

"DESIGN FOR A BRAIN" by W. Ross Ashby. Published by *John Wiley & Sons, Inc.*, 440 Fourth Avenue, New York 16, N. Y. 260 pages. \$6.00.

How does the brain produce adaptive behavior? "Design for a Brain" attempts to solve the origin of the nervous system's unique ability to do this, yet be mechanistic in nature.

Starting with first principles, requiring no specialized knowledge on the part of the reader, the book clarifies and relates various physical and psychological concepts, and shows how the problem can be stated with both generality and precision. It then develops the solution—the principle of ultrastability—which is defined and described in Chapter 8. The next two chapters apply this principle to the nervous system and show how it explains the organism's basic power of adaptation. The remainder of the book studies its developments.

Nonmathematical and complete in itself, the main account is given in Chapters 1-18. The appendix, in Chapters 19-24, contains the definitive theory in mathematical form. So far as was possible, the main account and the appendix were written in parallel to facilitate cross-reference.

Visual Proof


(Continued from page 16)

ment, should have good frequency response up to 5 mc. and should have low input capacity with high input impedance; cost is of the order of \$300. Oscillographs for video work vary in price from \$300 to \$900; it is assumed that most television stations will probably have at least one high quality oscillograph, equivalent to the *Du Mont* 303, for test purposes. The cost of the r.f. waveform monitor (shown in Fig. 2), which should also be part of a station's normal video monitoring equipment, is of the order of \$1000; this instrument is used during normal operation to measure significant amplitude levels—such as blanking, black peak, and white peak—and to assure maintenance of the proper percentage of sync. The video signal generator should have a frequency range of at least 100 kc. to 5 mc.; cost varies from \$600 to \$1000. Also available commercially are video sweep generators, sometimes known as wobblers, which may be set to fixed frequencies and used as video signal generators. Provision for calibrating markers is highly desirable; these devices are regularly used in the maintenance of a station's video equipment. Mixing amplifiers, dummy loads, and diode detectors are also—in most cases—a part of a station's regular equipment.

Narrow-band receivers with extreme selectivity are not generally available commercially. Figure 5C shows a block diagram of a receiver that was constructed by *Du Mont* for making spectral measurements. Cost is of the order of \$700. The response of this receiver is such that good resolution is obtained at 100 kc. off carrier. Similar receivers without as much selectivity can be used if 200 kc. is the reference point. Actually, it makes little difference whether 100 or 200 kc. is the reference inasmuch as the transmitter characteristic is flat at both points. R.F. signal generators are commercially available, at costs of \$600 to \$1000.

Certain precautions are always necessary in making measurements: (1) test equipment must be properly termi-

Fig. 8. Spectral analysis of the output of the visual transmitter.

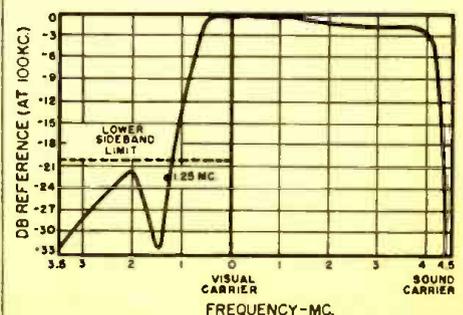

RESISTORS

- ALL MAKES
- ALL OHMAGES
- ALL TOLERANCES

1/2 WATT—1 WATT—2 WATT

AMERICA'S BEST

EB 1/2 W 10% .03 each
GB 1 W 10% .06 each
HB 2 W 10% .09 each
For 5% add 100%
Minimum per Item — \$2.00
Minimum per Order — \$10.00

LEGRI S COMPANY

158 West 99 Street, New York, N. Y.

nated with noninductive loads of the correct value; (2) equipment should be shielded to avoid the effect of stray r.f. fields; (3) diode detectors must be linear over the frequencies being measured, or known correction factors must be applied; (4) overmodulation or undermodulation of receivers used for measuring purposes must be avoided; (5) probes must receive sufficient energy to operate diode detectors or receivers in the linear region; (6) the transmitter should be set to operate at the proper modulation level; (7) test input levels and power output should be held constant during all measurements. Other points to remember include the following: video sweepers may not have constant output, and may generate some harmonics—for precise measuring, a low pass filter in the output may be necessary; vacuum-tube voltmeters are generally peak-reading devices calibrated in r.m.s. values, and correct readings are obtained only with sine waves having unity form factor; where notching duplexers are used, 4.5-mc. sine-wave modulation should not be applied, as the load resistor in the diplexer will overheat.

Although complete Proof of Performance measurements are made infrequently, it is believed essential that a television station make spot checks at least monthly. At the *Du Mont* stations, it is standard practice each week to wobble the transmitter into the dummy load and the antenna. Each transmitter has a built-in wobulator, essentially a low power r.f. generator which sweeps ± 5 mc. from the carrier. An oscillograph display shows qualitatively

the bandpass of various tuned stages as well as the final transmitter output. Crystal markers provide calibration points, and markers can be introduced at other frequencies to permit relatively accurate determination of the over-all characteristic. Three photographs of a typical wobble pattern are shown in Fig. 6. Figure 6A shows the transmitter wobbled into a dummy load; note the carrier frequency marker and the marker at 3.5 mc. Figure 6B shows the transmitter wobbled into the antenna; there is substantially no difference between antenna and dummy load. Figure 6C shows the wobble pattern taken at a time when, as it was later determined, two feed straps on a five-element antenna had broken off; the picture quality under these conditions was only slightly deteriorated, but the wobble test showed immediately that there was trouble.

A more recent type of built-in wobulator has been described by John Ruston'. This unit provides variable video input and has the advantage that the transmitter can operate under normal conditions of r.f. excitation and video modulation during its use. The output is a 15-kc. signal, the amplitude of which is proportional to the amplitude-frequency characteristic of the transmitter, and may be displayed on any general-purpose oscillograph. Figure 1 shows such a display.

Another type of spot check utilizes an external video sweep generator for modulating the transmitter. Output is detected and shown as a video signal on a wide-band oscillograph. Typical output with and without the use of a notch diplexer is shown in Figs. 3 and 4.

It is evident that visual transmitter Proof of Performance measurements, exclusive of field strength, can be made with readily available equipment. It is recommended that stations make frequent spot checks to assure continued compliance and to detect potential trouble or failure. These spot checks can be made with relative ease.

REFERENCES:

1. Epperson, J. B., "Television Field Intensity Measurements," *Electronics*, March, 1949.
2. Goldsmith, Thomas T., Jr., Wakeman, R. P., and O'Neill, J. D., "A Field Survey of Television Channel 5 Propagation of New York Metropolitan Area," *Proceedings of the IRE*, Vol. 37, No. 5, May, 1949.
3. Adair, George, "Aural Proof of Performance Measurements," *NARTB Engineering Conference*, April 15, 1950.
4. Ruston, John, "Measuring Television Transmitter Amplitude Characteristics," *Tele-Tech*, September, 1951.

Photo Credits

PAGE	CREDIT
3,	American Phenolic Corp.
10, 11,	General Radio Co.
12, 13,	Sylvania Elec. Prod. Inc.
14, 15, 16,	Du Mont Television Network

WHEN YOU ORDER

WELLS
COMPONENTS...



HERE'S WHAT YOU GET


- 1 IMMEDIATE DELIVERY FROM STOCK (in any quantity)
- 2 FINEST QUALITY OF FAMOUS BRANDS
- 3 GENERALLY LOWER PRICES
- 4 RETURN PRIVILEGE FOR FULL CREDIT IF NOT SUITED TO YOUR REQUIREMENTS

The valuable service Wells provides to the industry is being used by many of our greatest manufacturers as a matter of course.

Our vast stock (the world's largest) may contain just the components you need to fill urgent orders — at a substantial savings in time and cost.

ADEL CLAMPS • ANTENNAS, Insulators, Mast Sections • BINDING POSTS • BLOWERS • CABLE ASSEMBLIES • CHOKES • COILS • CONDENSERS Oil Filled, Bathtub, Hearing Aid, Transmitting Micas, Silver Micas, Ceramic, Variable, Trimmer • CRYSTALS • FILTERS • FUSES & MOUNTINGS • GENERATORS • GROUND RODS • HEADSETS • I.F. COILS • JACKS • JACK BOXES • KEYS, Telegraph KNOBS • LAMPS • LORD MOUNTS • LUGS MOTORS & BRUSHES • PLUGS • RECTIFIERS Selenium, Copper Oxide, Meter, Diode • RESISTORS—All Types • SELSYNS • SOCKETS • SWITCHES Aircraft, Micro, Switchettes, Toggle • TIMERS • TUBING—Flexible • TUNING SHAFTS • TRANSFORMERS All Types • VIBRATORS • WALKIE TALKIES

DYNAMOTORS

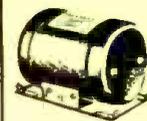

OVER 100,000
NEW DYNAMOTORS
IN STOCK!

DM 32A — DM 53A — PE 86 — PE 101C
DM 33A — D 101 — PE 94, etc.

Large quantities of brushes for all types of dynamotors and motors.

Write us for quotations. Advise us your requirements.

A complete Signal Corps stock number listing of items in our stock. Write for listing No. SG-200. (For government agencies and contractors only.)

Manufacturers and distributors—write for new Condenser Catalog C-10 now available.

Write, Wire, Phone Your Requirements
all phones: SEeley 8-4143

WELLS
SALES, INC.

33 W. Chicago Ave., Dept. R, Chicago 22, Illinois

CALENDAR of Coming Events

SEPTEMBER 1-3—International Sight and Sound Exposition, Palmer House, Chicago, Ill.

SEPTEMBER 14-16—Fourth Annual Convention and Manufacturer's Conference, NEDA, St. Louis, Mo.

SEPTEMBER 21-25—Eighth National Instrument Exhibit, Hotel Sherman, Chicago, Ill.

SEPTEMBER 28-30—National Electronics Conference, Hotel Sherman, Chicago, Ill.

OCTOBER 5-8—Fall Technical Meeting of USA and Canadian National Committees of URSI and the IRE Professional Group on Antennas and Propagation, National Research Council, Ottawa, Canada.

OCTOBER 26-28—IRE-RTMA Radio Fall Meeting, Toronto, Ontario.

NOVEMBER 13-14—Annual Electronics Conference, Kansas City Section, IRE, Hotel President, Kansas City, Mo.

FEBRUARY 4-6, 1954—Sixth Southwestern Conference and Electronics Show, Tulsa, Okla.

FREED

Instruments & Transformers

Famous
For

QUALITY • DEPENDABILITY • ACCURACY

FREED MINIATURE AUDIO TRANSFORMERS

PROFESSIONAL MINIATURE AUDIO TRANSFORMERS

These high quality, miniature transformers feature hermetic sealing for maximum protection from moisture penetration with subsequent electrolysis and corrosion of fine wires. While primarily intended for non-military equipment, these units are constructed in accordance with MIL-T-27 Specifications.


CATALOG NO.	APPLICATION	IMPEDANCE LEVEL OHMS		MAXIMUM POWER LEVEL V.U.*	RATIO	MAX PRI DC PER SIDE Ma.	D.C. UNBAL. Ma.	FREQ. RESPONSE C.P.S.	CASE NUMBER
		PRIMARY	SECONDARY						
PMA 1	Line or microphone to single or push-pull grids	50/200/500	60,000 C.T.	+8	1:11	0	0	±2.0 DB 30-20000	DM-12
PMA 2	Dynamic microphone or speaker voice coil to single or P.P. grid	4/8	60,000 C.T.	+8	1:86.6	0	0	±2.0 DB 30-20000	DM-12
PMA 3	Line or microphone to single or push-pull grids. Magnetically shielded.	50/200/500	60,000 C.T.	+8	1:11	0	0	±2.0 DB 30-20000	DM-12
PMA 4	Single triode plate to single or push-pull grids	15,000	60,000 C.T.	+8	1:2	0	0	±2 DB 30-10000	DM-12
PMA 5	Single triode plate to push-pull grids	15,000	60,000 C.T.	+8	1:2	2	2	±2 DB 200-10000	DM-12
PMA 6	Single triode plate to multiple line	15,000	50/200/500	+8	5.48:1	0	0	±2 DB 30-20000	DM-12
PMA 7	Single triode plate to multiple line	15,000	50/200/500	+8	5.48:1	2	2	±1 DB 200-10000	DM-12
PMA 8	Push-pull triode plates to multiple line	30,000 C.T.	50/200/500	+8	7.75:1	2	0.25	±2 DB 30-20000	DM-12
PMA 9	Crystal mike or pickup to multiple line	60,000	50/200/500	+8	11:1	0	0	±2 DB 30-20000	DM-12
PMA 10	Mixing or matching	50/200	50/200/500	+8	1:1.50	0	0	±2 DB 30-20000	DM-12
PMA 11	Parallel Feed Reactor * 1 mw. reference level.	40 hy.	3 ma dc,			3500 ohms D.C. resistance			DM-12



No. 1030
Low Frequency
"Q" Indicator



No. 10208
Megohmmeter

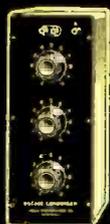

Decade
Inductors



No. 1040
Vacuum Tube Voltmeter



No. 1210
Null Detector &
Vacuum Tube Voltmeter



No. 1010
Comparison Bridge



No. 1110A
Incremental Inductance
Bridge



DM-12 CASE DIMENSIONS

FL - 1 1/2
FD - 1 1/32
W - 15/16
H - 1 15/32
M - 1 7/32

Screws - 4-40
Cut out - 7/8
Wgt. - 1.5oz.

Send for complete catalog on
Freed Instruments and Transformers

FREED TRANSFORMER CO., INC.

1719 WEIRFIELD ST. (RIDGWOOD) BROOKLYN 27, N.Y.

www.americanradiohistory.com

THIS WESTINGHOUSE UHF SERVICE KIT

YOURS AT NO COST

with purchase of
100 WESTINGHOUSE RELIATRON RECEIVING TUBES
OR
4 WESTINGHOUSE RELIATRON PICTURE TUBES
from your Westinghouse Tube Distributor



1 32-PAGE UHF CONVERSION HANDBOOK Tells How to Convert All Makes and Models

- Tells you all about:
Converters
Tuners
Strip Replacement
Antennas and Lead-In
- Written in easy-to-understand servicemen's language.
- More than 50 illustrations, diagrams.
- Makes UHF servicing easy and profitable.

2 SENSATIONAL NEW 3-FOOT HEAT-MOTOR WINDOW DISPLAY

Reproduces
Actual Moving
TV Troubles
in Lighted
Picture

Printed with
6 colors

Best display you
ever used



3 UHF WINDOW STREAMER Makes You UHF Conversion Headquarters

Attracts new
customers for
UHF conversion
business; turns
your UHF know-
how into quick
cash!

**DON'T MISS
UHF**
*Let us convert your set
to receive all stations*

We put **NEW LIFE** in your TV and radio set
with **NEW NEW NEW**
**Westinghouse
RELIATRON TUBES**

4 EXCITING LUMINESCENT "NEW LIFE" WINDOW STREAMER

YOU CAN BE SURE...IF IT'S
Westinghouse

5 FRAMED PRICE- POLICY STATEMENT

15 1/2" x 13" simulated wooden
frame with protective acetate
window permanently displays
your standard labor charges
or shop policy. Interchange-
able inserts provided.





Get this UHF Service Kit from your Westinghouse Tube Distributor **THIS WEEK**. It will mean extra money in your pocket through new customers. Offer is limited, closes Nov. 30th. Remember, there's no charge for this Kit. Just buy tubes from your Westinghouse RELIATRON Tube Distributor. Write Dept. G-209 for complete information.

EI-95029

RELIATRON TUBES

WESTINGHOUSE ELECTRIC CORPORATION, ELECTRONIC TUBE DIVISION, ELMIRA, N. Y.

NOW...more important than ever!

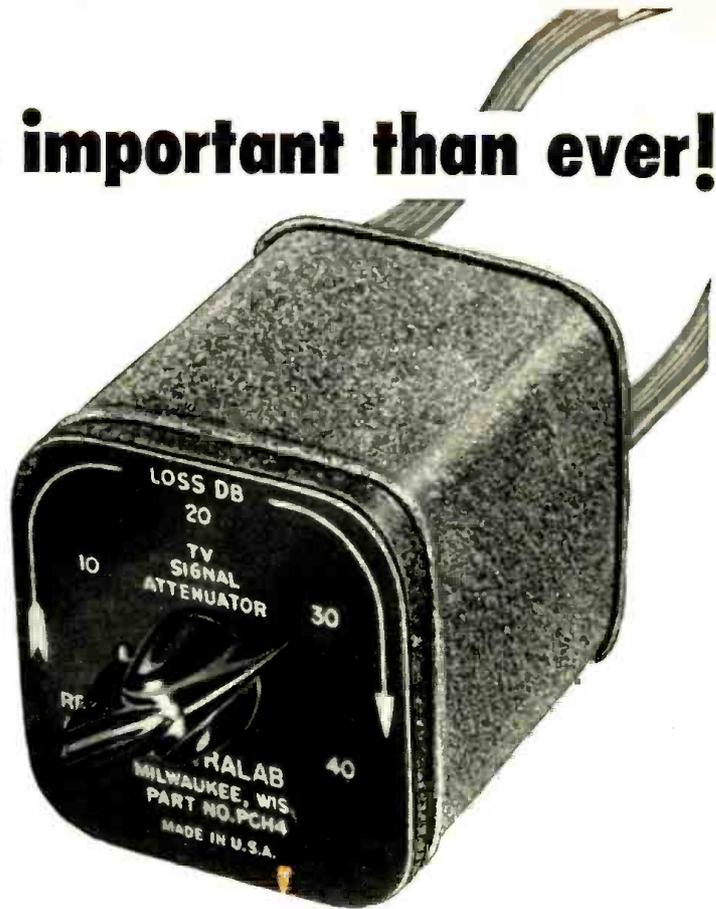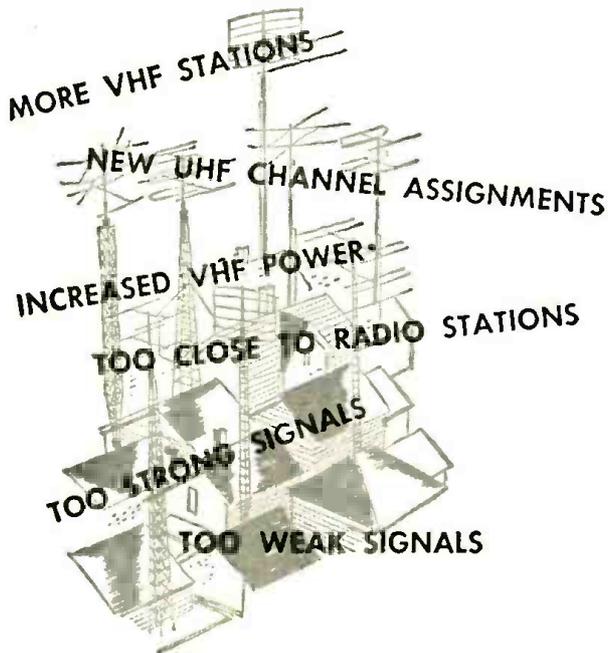

New service tool...PCH-4 TV ATTENUATOR assures best reception in multi-station areas

If you're in the thick of all the new channel assignments, both VHF and UHF, you know what a job it is to install H-pads for proper attenuation. Ordinary "cut-and-try" methods take too much time and there's always danger of overloading.

Even if you don't have attenuation problems now — you will later on! That's why it's smart to get the low-down on this brand-new Centralab TV Attenuator.



The switching arrangement makes it possible to attenuate each station as much or as little as necessary depending on daily conditions such as weather or existing interference, and allows for proper attenuation to balance two or more stations. It shows you the proper attenuation merely by turning a switch. You instantly match signal strength to requirements of receiver. Four different H-pads are mounted permanently to the at-

tractive metal case. All you do is hook up to the 300-ohm antenna twin lead and turn dial to the H-pad that gives you the proper attenuation. Then unhook leads and install the proper H-pad. Checking and installation takes only a few minutes.

If customers want permanent selective attenuation installation, this handy unit makes the job easier. And it's another sale for you!

Your Centralab distributor has these TV Attenuator Switches in stock for immediate delivery. Also ask him for a demonstration and complete data on dependable Centralab H-pads.

Always use Centralab H-pads — you'll prevent overloading, eliminate tearing of image, improve both audio and video results. Available in 10, 20, 30 and 40 db. Install in series with 300-ohm antenna.



Centralab

A Division of Globe-Union Inc.

910-1 East Keefe Ave. • Milwaukee 1, Wisconsin
In Canada, Box 208, Ajax, Ontario

MONEY BACK GUARANTEED

TO RECEIVE *All* UHF and *All* VHF STATIONS IN *All* DIRECTIONS FOR 60 MILES WITHOUT A ROTORMOTOR OF ANY KIND!!


WORLD'S MOST POWERFUL UHF—VHF TELEVISION ANTENNA

While antenna reception is guaranteed for 60 miles, perfect pictures have been consistently received as far as 160 miles from stations.

All NEW DESIGN FOR '54

- LOW-LOSS SWITCH
- LOW-LOSS PHENOLIC INSULATORS
- USES NEW 4-CONDUCTOR MATCHED IMPEDANCE LINE
- ONLY 10 INCH SPACING BETWEEN ANTENNA BAYS

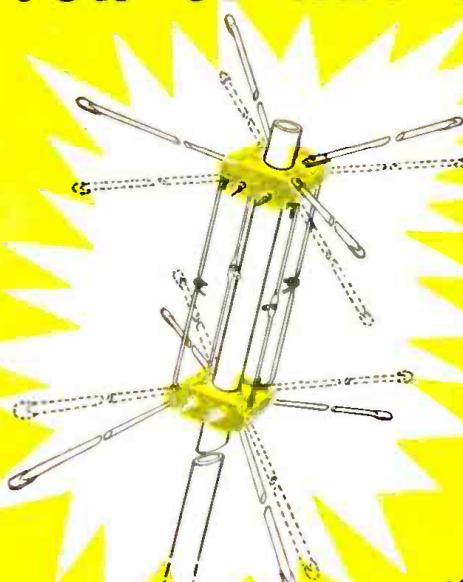ONE INSTALLATION ONE ANTENNA
ONE TRANSMISSION LINE



MODEL
**SUPER
60**

**SO NEW! SO DIFFERENT!
IT'S PATENTED!**

- # 2,585,670
- # 2,609,503
- # 2,625,655
- # 2,644,091


Money Back Guarantee

IN ALL LOCATIONS IN EVERY AREA

WITH STATIONS IN ALL DIRECTIONS

The new All Channel Model Super 60 is guaranteed to bring in, immediately on installation, every UHF and every VHF station within 60 miles in any direction, giving clearer and sharper pictures than any antenna or combination of antennas with or without rotor motors.

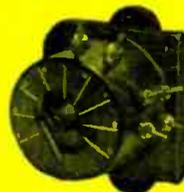If, immediately on installation, it fails to do this, we agree to refund to the jobber to whom we sold and shipped it, his full purchase price.



The 9 position selector switch electronically rotates the antenna in a stationary position.


LIST PRICE
\$36⁷⁵
SEE YOUR LOCAL
JOBBER

PRICE INCLUDES
Complete stacked array • 4 stacking bars • 9 position switch • Switch-to-set coupler • 3 - 7 1/2" stand offs • Individually boxed in mailable carton

BE READY NOW — FOR THE FUTURE

ALL CHANNEL ANTENNA CORP., 70-07 QUEENS BLVD., WOODSIDE 77, NEW YORK

Servicemen!

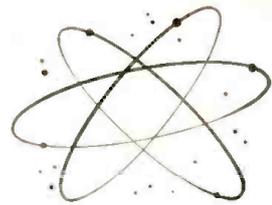

Field Strength Meter

Model M-8104. More new features than any other unit at this popular price. Reads signal strength directly from the dial from 10 to 100,000 microvolts. A serviceman's time saver to measure actual TV picture signal strength.

CHECK THESE PHILCO TEST EQUIPMENT FEATURES

- ✓ New Low Prices
- ✓ New Ruggedness
- ✓ New Circuitry
- ✓ New Versatility
- ✓ New Styling
- ✓ New Accuracy

Cross Dot Linearity Pattern

Model G-8004. Philco's new unit for the finest possible linearity adjustments when a station pattern is not available. It provides extreme versatility of performance and design at amazing economy of operation. Light, rugged and portable it's the new leader in test equipment.



NOW YOURS ON NEW EASY PAYMENT PLAN



VHF to UHF Signal Generator Adapter

Model G-8000. The most economical system yet designed to produce UHF signals for TV receiver tests. Through a conversion process using any VHF meter this unit produces from an input VHF signal, UHF signals having the same characteristics as the VHF signal.



Mutual Conductance Tube Checker

Model 7052. Tests more different type tubes than any unit on the market, from subminiature to acorn low power transmitting tubes. Shorts on tube elements can be easily determined, employs roll chart instead of cards, for use as a portable or counter top unit.



Dynamic Signal Tracer

Model 7031. An extremely versatile instrument... this unit is designed for fast diagnosis of radio trouble by audibly monitoring RF and AF circuits. Can be used to accurately check P.A. systems, microphones and phonograph pick-up circuits, also localizes distortion.



5-inch High Gain Oscilloscope

Model S-8202. This outstanding scope is built to the very highest standards of test instruments. . . It features the highest gain 10 millivolts/inch, and widest frequency range at its popular price. Wide sweep ranges allow extreme flexibility in sweep circuit trouble shooting.



3-inch TV Oscilloscope

Model S-8200. The most practical portable unit available for bench or field servicing. Preset horizontal and vertical sweep rates take the guesswork out of trouble shooting, aligning and measuring. Ideal for television because of its high sensitivity and wide response.



Philco Circuit Tester

Model 8102. A general purpose voltmeter that challenges comparison. Utilizes 1% resistors throughout to insure maximum accuracy. Tests AC voltage ranges of audio and high impedance AC circuits where a vacuum type voltmeter would normally be required.



Philco Circuit Master

Model 8100. Designed to the most rigid of engineering specifications, this rugged metal-cased vacuum tube voltmeter is by far the finest in its price class. Provides unmatched accuracy for measuring and aligning where plus and minus indications are required.



UHF Auto-Level Sweep Generator

Model G-8002. The most modern, most inexpensive UHF sweep generator on the market. Checks sweep alignment with *any* test oscilloscope. Its output is controllable and leakage is negligible . . . makes possible over-all trouble shooting and testing of low level units.



Cathode Ray Tube Checker

Model 7053. Will accurately test *all* picture tubes used in home TV receivers. Special cathode-ray tubes are easily checked by using plug-in adapters. Eliminates trouble shooting guesswork. Neon lamp indicates shorts and open elements in the electrodes of the gun.



Visual Alignment Generator

Model 7008. Combines in *one* economical instrument functions that can be approached only in a cumbersome collection of costly devices. No special scope connections are required for the most accurate visual alignment and calibration that is possible to achieve.



Appliance Tester

Model 5007. The ultimate in versatility. A one package, all purpose, portable appliance service unit. Permits over-all analysis of refrigerators, ranges, air conditioners and household appliances. With "pick-up" elements to determine temperature and built-in voltmeter.

MAIL THIS COUPON FOR NEW FREE BOOKLET
or see your Philco Distributor

PHILCO CORPORATION
Accessory Division
Allegheny Ave. & "A" St., Phila. 34, Pa.

I am interested in the Philco Test Equipment shown here. Please send me details of your SPECIAL PURCHASE PLAN for obtaining these units.

Please send FREE copy of your new booklet on Philco Test Equipment.



NAME

ADDRESS

CITY STATE

You can build a reputation on Tung-Sol® Quality



TUNG-SOL makes
All-Glass Sealed Beam Lamps,
Miniature Lamps,
Signal Flashers,
Picture Tubes, Radio, TV,
Special Purpose Electron Tubes,
Semiconductor Products.



TUNG-SOL ELECTRIC INC.
Newark 4, New Jersey

Sales Offices: Atlanta, Chicago, Columbus, Culver City (Los Angeles), Dallas, Denver, Detroit, Newark, Seattle

Within the INDUSTRY

GLEN McDANIEL, who served as the first paid president of the Radio-Television Manufacturers Association in 1951-52, has been elected temporary president of the organization pending the selection of another full-time paid president. He will also continue as general counsel of the Association.

The board of directors also elected Robert C. Sprague as chairman of the RTMA board for the next fiscal year. Mr. Sprague, who succeeds A. D. Plamondon, Jr. of Chicago, is past president of the Association and served as its chairman for two years in 1950-52.

Leslie F. Muter of Chicago was re-elected treasurer and Dr. W. R. G. Baker of *General Electric Company*, was re-elected director of the Engineering Dept.

NEDA has announced that the services of Donn Mason, widely known as "Minute Man of sales training," have been secured for its 1953 Convention and Manufacturers' Conference to be held in St. Louis, Sept. 14-16.

In view of the current shortage not only of trained help but of suitable people who can be trained, distributors report having to comb unlikely sources for prospective sales personnel.

Mr. Mason will provide new suggestions for getting, training, and keeping a fully-staffed operation, with emphasis on sales personnel.

EUGENE M. KEYS has been elevated to the post of president by the board of directors of *Edwin I. Guthman Co.* of Chicago, largest independent coil manufacturer in the country.

He was formerly executive vice-president of the firm and succeeds the late Edwin I. Guthman, president and founder who died last April.

Mr. Keys joined the company in 1942 as a member of the purchasing department. In 1945 he was named assistant sales manager and in 1947 he was promoted to the position of sales manager. In 1951 he was named vice-president in charge of sales and a year later was made executive vice-president of the firm.

MARTIN BETTAN, director of sales and engineering for *Radio Merchandise Sales, Inc.*, has been elected president of the Antenna Manufacturers Association.

Ben Snyder, of *Snyder Manufacturing Company* was named vice-presi-

dent and Edward Finkel of *JFD* will serve as secretary-treasurer of the trade group.

W. WALTER WATTS has been elected to the post of vice-president in charge of technical products for the *RCA Victor Division of Radio Corporation of America*.



He was previously vice-president in charge of engineering and is assuming the position formerly held by L. W. Teegarden who became executive vice-president of *RCA* last February. In his new assignment Mr. Watts will supervise the activities of both the Engineering Products Department and the company's Tube Department.

He joined *RCA Victor* after wartime service as a Colonel and Commanding Officer of the Signal Corps Distribution Agency and as a Signal Corps Procurement Director for which he was awarded the Legion of Merit.

SPRAGUE ELECTRIC COMPANY of North Adams, Massachusetts is building a new plant about seven miles from West Jefferson, North Carolina. About 250 workers will be employed when the plant reaches full production. It will be the company's seventh plant

... **TRACERLAB, INC.** is constructing a new \$100,000 plant in Richmond, California to house its Western Division. The building will contain approximately 15,400 square feet and will replace quarters the company has occupied in Berkeley since 1948. The building is scheduled for November completion

... **I. E. MANUFACTURING COMPANY** is undertaking an extensive expansion and modernization program designed to double its plant area. Completion is scheduled for next May

... **OAK MFG. CO.** has opened a new factory in Elkhorn, Wisconsin to serve as a feeder for its Chicago and Crystal Lake, Illinois plants. James L. von Harz will be in charge of the new facility

... **LOUIS M. HERMAN COMPANY** has opened a new branch store in Norwood, Massachusetts to service the Norwood, Framingham, Brockton, Taunton areas. The company handles a complete line of radio and television parts

... **AEROCOIL, INC.** has moved into larger quarters at 24 Cliff Street in Jersey City, N. J. ... The **RCA VICTOR DIVISION** has purchased land in Findlay, Ohio and will build a plant for the manufacture of electronic component parts for radio and TV home receivers. The first unit will be in op-



No matter where you live
or what you are doing now...

I WILL TRAIN YOU FOR A HIGH PAY JOB IN TELEVISION

L. C. Lane, B.S., M.A.
President: Radio-
Television Training
Association.
Executive Director:
Pierce School of
Radio-Television.

VETERANS! CIVILIANS!

Thousands of new jobs in TV are opening up in every state as new stations go on the air. You too can take your place in America's booming TELEVISION and Electronics Industry... enjoy the success and happiness you always wanted out of life! Now... prepare for a life-time career as a trained TV TECHNICIAN, often within months... using the same successful "learn-by-doing" home study methods that have helped hundreds of men with NO PREVIOUS TRAINING!

**NO EXPERIENCE NECESSARY
LEARN TELEVISION AT HOME
IN YOUR SPARE TIME!**

Giant Screen TV Receiver



21 IN

GET MORE! LEARN MORE! EARN MORE!

I give you ALL the equipment and training you need to prepare for the BETTER PAY jobs in TV. While training, many of my students make \$25.00 a week repairing Radio-TV sets in their spare time... start their own profitable service business.

MORE EQUIPMENT!

You build and keep this professional GIANT SCREEN TV RECEIVER complete with big picture tube (designed and engineered to take any size up to 21-inch). Also all units illustrated, plus additional equipment! Everything supplied complete with all tubes.

FREE FCC COACHING COURSE!

Prepares you at home for your FCC License. The best jobs in TV and radio require an FCC License. My FCC Coaching Course is given to you at NO EXTRA COST after TV Theory and Practice is completed.

BECOME A TV CAMERAMAN!

TV CAMERAMAN & STUDIO COURSE (Advanced training for men who have had radio & TV training or experience). I train you for an exciting, high pay job as the man behind the TV camera. Work with TV stars in TV studios or "on location" at remote pick-ups.

FM-TV TECHNICIAN TRAINING!

My FM-TV Technician Course will save you months of training, if you have previous Armed Forces or civilian radio experience. Complete with kits, BIG SCREEN TV RECEIVER, and FREE FCC Coaching Course.

NEW YORK ROUND TRIP!

Exclusive! Only RTTA gives you a ROUND TRIP TO NEW YORK CITY at NO EXTRA COST! Yes, from anywhere in the continental U.S. or Canada, I'll pay your way to New York and return after you finish your complete Radio-TV course. Get 2 FREE weeks, 50 hours of advanced study at our affiliated PIERCE SCHOOL OF RADIO & TV. Operate modern TV studio and camera equipment, go behind the scenes of New York's big Radio-TV centers! (Available only to students enrolled for complete Radio-TV Technician Course.)

RADIO-TELEVISION TRAINING ASSOCIATION

1629 Broadway, Radio City Station, New York City 19, N. Y.
LICENSED BY THE STATE OF NEW YORK

VETERANS!

MY SCHOOLS FULLY APPROVED TO TRAIN VETERANS UNDER NEW G.I. BILL! If discharged after June 27, 1950 - CHECK COUPON BELOW! Also approved for RESIDENT TRAINING in New York City... qualifies you for full subsistence allowance up to \$160 per month.



MAIL COUPON TODAY!

MY 4 FREE AIDS SHOW YOU HOW AND WHERE TO GET A BETTER PAY JOB IN TELEVISION!

See for yourself how my simple, practical methods make success easy.



NO SALESMAN WILL CALL!

Mr. Leonard C. Lane, President
RADIO-TELEVISION TRAINING ASSOCIATION
1629 Broadway, New York 19, N. Y. Dept. T-9A

Dear Mr. Lane: Mail me your NEW FREE BOOK, FREE SAMPLE LESSON, and FREE aids that will show me how I can make BIG MONEY IN TELEVISION. I understand I am under no obligation and no salesman will call.

(PLEASE PRINT PLAINLY)

NAME _____ AGE _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

I AM INTERESTED IN:

- Radio-TV Technician Course **VETERANS! Check here**
 FM-TV Technician Course for Training under NEW
 TV Cameraman & Studio Course G.I. Bill



Photo courtesy Herbert Smith (W8AIU), South Euclid, Ohio

Listen to the story of Brush headphone quality

Try out the best—and judge for yourself why the Brush Model BA-206 headphones are best suited for your individual application.

Acoustically—you'll enjoy the high fidelity and smooth frequency response which gives you all the lows and crisp clean highs.

Electrically—being capacitive in nature, they draw negligible power and only require modest driving voltages. Hence, these headphones are ideal for monitoring applications—may be used in either high or low impedance circuits and are extremely well suited for multiple installations.

Mechanically—you'll find them exceptionally light and comfortable. The advanced design gives your ear a smooth, comfortable, air-tight fit which is important for excellent bass response.

Listen for yourself—and then be surprised at the low cost of these superb headphones! Write for bulletin. Brush Electronics Company, Dept. UU-9, 3405 Perkins Avenue, Cleveland 14, Ohio.

BRUSH ELECTRONICS

INDUSTRIAL AND RESEARCH INSTRUMENTS
PIEZO-ELECTRIC MATERIALS • ACOUSTIC DEVICES
MAGNETIC RECORDING EQUIPMENT
ULTRASONIC EQUIPMENT



COMPANY

formerly
The Brush Development Co.
Brush Electronics Company
is an operating unit of
Clevite Corporation.

eration next Spring . . . The addition of a new 18,000 square foot warehouse has been announced by **RADIO MERCHANDISE SALES, INC.** The building is located at 945 Cortlandt Avenue in New York City . . . **MANNFRED ELECTRONICS CORP.** has moved to new and larger quarters at 21-38 36th Avenue, Long Island City 6, New York. The new facility offers off-the-street parking for the company's wholesale customers.

* * *

RALPH R. STUBBE has been named assistant chief engineer of *General Instrument Corporation* in line with the company's growing emphasis on u.h.f. television devices.



He will make his headquarters at the firm's home plant in Elizabeth, New Jersey. Mr. Stubbe has been connected with such firms as *Westinghouse, Hazeltine, NBC, and Hoffman* and will play a key role in *GI's* expanding production of u.h.f. tuners, converters, and other components it supplies to manufacturers and the government.

* * *

HAROLD B. RHODES of Paterson was re-elected president of the Radio and Television Servicemen of New Jersey, Inc. at the fourth annual meeting of the association.

Serving with Mr. Rhodes are: Fred E. Berdy, vice-president; J. Palmer Murphy, executive secretary-treasurer; and Jerome J. Gelman, counsel. All are from Paterson, N. J.

Mr. Rhodes pledged the Association's continued cooperation with the Greater Paterson Chamber of Commerce and the Paterson Better Business Committee during the coming year.

* * *

NATESA will hold its annual Fall convention October 9, 10, and 11 at the Morrison Hotel in Chicago. TISA-Illinois will be the host.

Present plans call for display booths, seminars, discussions, banquets, and entertainment. John Cecich, vice-president of TISA-Illinois is the convention chairman.

Further information on this meet is available from NATESA president, Frank J. Moch, 5908 Troy Street, Chicago 29, Illinois.

* * *

STANDARD TRANSFORMER CORPORATION of Chicago and the **CHICAGO TRANSFORMER DIVISION** of *Essex Wire Corporation* have been consolidated and will operate under the name of **CHICAGO STANDARD TRANSFORMER CORPORATION**. The new firm will retain and operate all present locations and facilities without any contemplated changes in personnel . . . Martin Corn has acquired the assets of **INTERNATIONAL CONNECTOR CORPORATION** of Paterson, New Jersey and will operate the new firm as **CORN ELECTRONICS**.
(Continued on page 120)

ADVANCE! Raise your earning power—learn RADIO-TELEVISION-ELECTRONICS by SHOP-METHOD HOME TRAINING

GOOD JOBS AWAIT THE TRAINED RADIO-TV TECHNICIAN

There is a place for *you* in the great Radio-Television-Electronics industry when you are trained as National Schools will train you at home!

Trained technicians are in growing demand at good pay—in manufacturing, broadcasting, television, communications, radar, research laboratories, home Radio-TV service, and other branches of the field. National Schools Master Shop-Method Home Training, with newly added lessons and equipment, trains you in your spare time, right in your own home, for these fascinating opportunities. **OUR METHOD IS PROVED BY THE SUCCESS OF NATIONAL SCHOOLS TRAINED MEN, ALL OVER THE WORLD, SINCE 1905.**

EARN WHILE YOU LEARN

Many National students pay for all or part of their training with spare time earnings. We'll show you how you can do the same! Early in your training, you receive "Spare-time Work" Lessons which will enable you to earn extra money servicing neighbors' and friends' Radio and Television receivers, appliances, etc.



Signal Generator

Audio Oscillator

T. R. F. Receiver

National Schools Training is All-Embracing

National Schools prepares you for your choice of many job opportunities. Thousands of home, portable, and auto radios are being sold daily—more than ever before. Television is sweeping the country, too. Co-axial cables are now bringing Television to more cities, towns, and farms every day! National Schools' *complete* training program qualifies you in all fields. Read this partial list of opportunities for trained technicians:

Business of Your Own • Broadcasting
Radio Manufacturing, Sales, Service • Telecasting
Television Manufacturing, Sales, Service
Laboratories: Installation, Maintenance of Electronic Equipment
Electrolysis, Call Systems
Garages: Auto Radio Sales, Service
Sound Systems and Telephone Companies, Engineering Firms
Theatre Sound Systems, Police Radio
And scores of other good jobs in many related fields.


TELEVISION TRAINING

You get a complete series of up-to-the-minute lessons covering all phases of repairing, servicing and construction. The same lesson texts used by resident students in our modern and complete Television broadcast studios, laboratories and classrooms!



MASTER ALL PHASES!

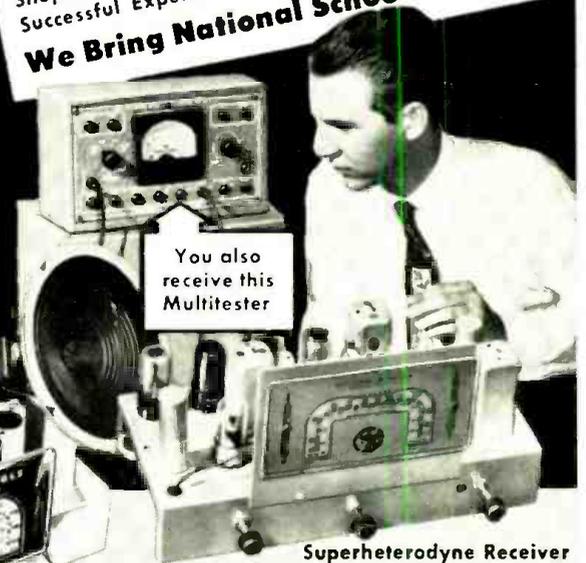Get Master Shop-Method Home Training from an Established Practical Resident School with its own Training Shops, Laboratories, Studios — almost 50 Years of Successful Experience in Training Ambitious Men.
We Bring National Schools To You!



You also receive this Multitester

Superheterodyne Receiver

LEARN BY DOING

You receive and keep all the modern equipment shown above, including tubes and valuable, professional quality Multitester. *No extra charges.*


FREE! RADIO-TV BOOK AND SAMPLE LESSON!

Send today for National Schools' new, illustrated Book of Opportunity in Radio-Television-Electronics, and an actual Sample Lesson. No cost—no obligation. Use the coupon now—we'll answer by return airmail.

This course also offered in Spanish and Portuguese

APPROVED FOR VETERANS AND NON-VETERANS
Check coupon below

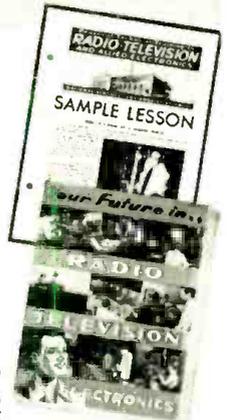Both Resident and Home Study Courses Offered!



NATIONAL SCHOOLS

LOS ANGELES 37, CALIFORNIA • ESTABLISHED 1905
IN CANADA: 193 E. HASTINGS STREET, VANCOUVER, B.C.

FIND OUT NOW—MAIL COUPON TODAY!

NATIONAL SCHOOLS, Dept. RH-93
4000 South Figueroa Street
Los Angeles 37, California

Mail in envelope or paste on postal card.

Send FREE Radio-TV Electronics book and FREE sample lesson. I understand no salesman will call on me.

NAME _____ AGE _____

ADDRESS _____


CITY _____ ZONE _____ STATE _____

Check here if released from service less than 4 years ago.

Check here if interested in Resident Training at Los Angeles.

another original!

Entirely New!

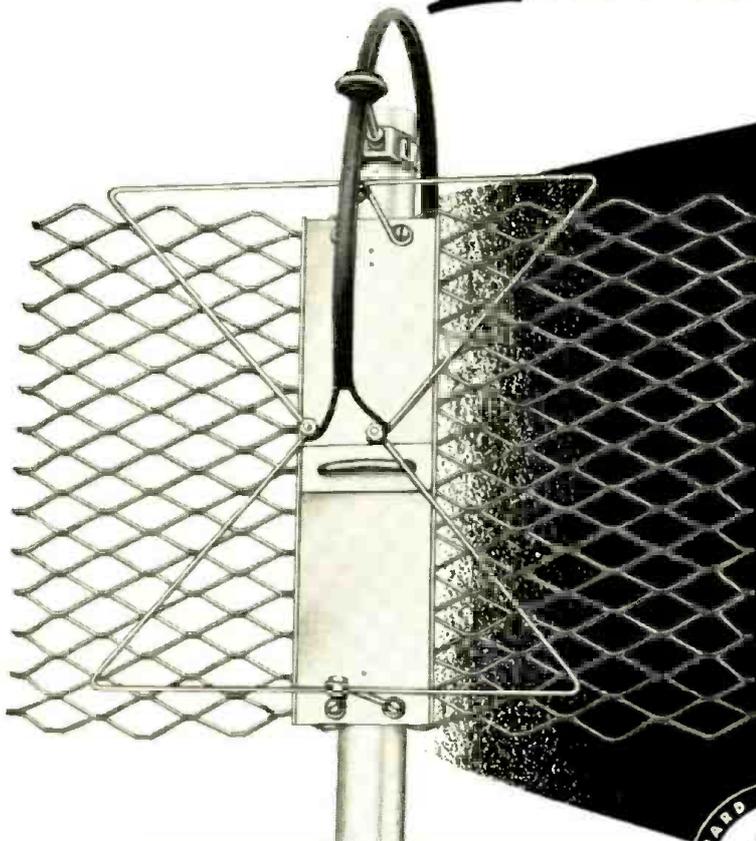

The last word in

UHF


TV Antennas

the

UW-2



Here's The One They've All Copied!

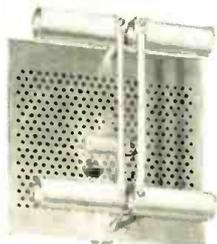

**...NOW
AT NEW
LOW PRICES**

**UHF
TV Antennas
MODEL U-4**

A superb quality UHF antenna featuring uniform gain with low vertical radiation (no ghosts), 300 ohm terminal impedance... measures 12x12x15 inches.

Here is another ORIGINAL... entirely NEW UHF TV antenna that far excels anything yet seen! It is a completely balanced broad band antenna covering ALL channels from 14 to 82 and terminating in 300 ohms with a very low voltage standing wave ratio! Some of the features include:

- Minimum wind resistance, (a double stacked UW-2 offers less wind resistance than many single bay antennas).
- The UW-2 assumes NO potential difference between itself and the mast, allowing MAXIMUM lightning protection when the mast is grounded.
- COMPLETELY FREE of insulators and their offending results.
- Excellent directivity, single lobe horizontal field pattern, 470 to 850 M.C.




SUBSIDIARY OF



THE RADIART CORPORATION CLEVELAND 13, OHIO

VIBRATORS • AUTO AERIALS • TV ANTENNAS • ROTORS • POWER SUPPLIES

RADIO & TELEVISION NEWS

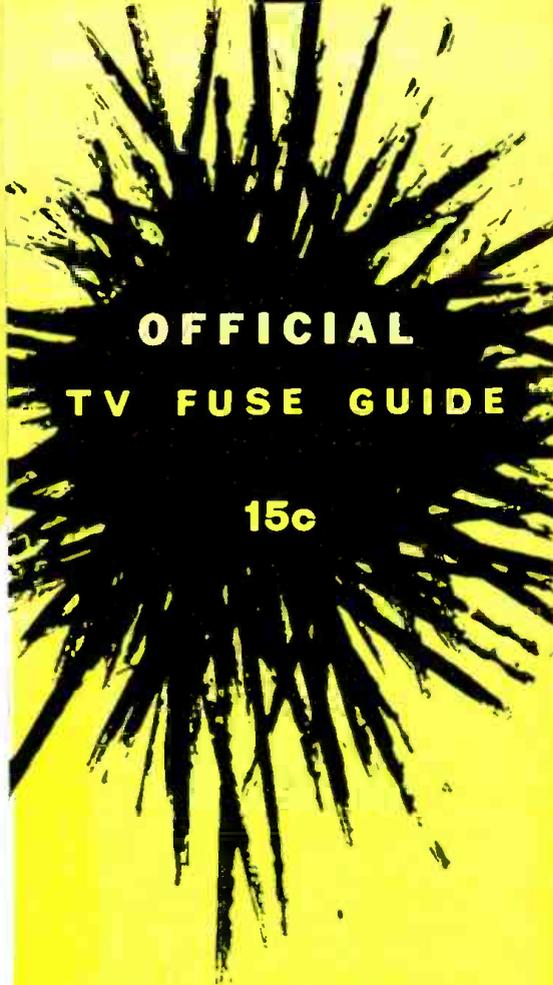

**OFFICIAL
TV FUSE GUIDE**


15c

LITTELFUSE

Littelfuse 1953 TV Fuse Guide enlarged to include latest models

Both New — Both Needed

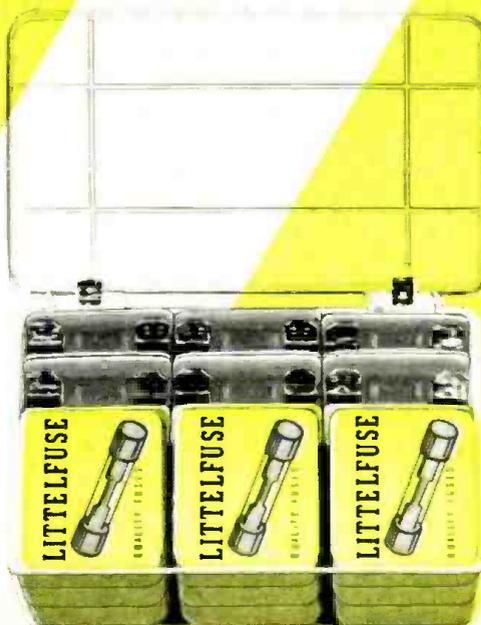
Littelfuse new One Call Kit adapted to include fuses being used in latest models—94 out of 100 times one call is all. Littelfuse Inc., Des Plaines, Ill.



PICKERING

PROFESSIONAL AUDIO EQUIPMENT

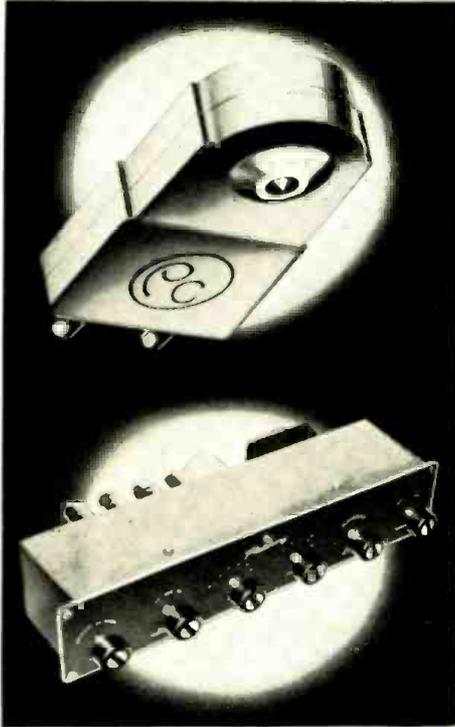BALANCED COMPONENTS / MAXIMIZE PLAYBACK PERFORMANCE



PICKERING CARTRIDGES . . .

are the choice of audio engineers throughout the world. They are universally acclaimed because of their high output, wide range performance and low distortion. They are used wherever a fine cartridge is required in radio stations, recording studios and for purposes of quality control by leading record manufacturers.


MODEL 410 AUDIO INPUT SYSTEM . . .

is designed to provide a complete audio control center. Model 410 may be used in any high quality playback system. Three input channels are provided—one for magnetic cartridges and 2 "flat" channels for other audio circuits. A 3-position equalizer network is built into the magnetic cartridge channel and provides accurate equalization for LP, AES and 78 rpm recording characteristics. Separate bass and treble controls are also provided. These are of the step-type and permit bass and treble adjustments in 2 db increments. The tone control circuits are intended to compensate for record characteristics and for listener-environment acoustical conditions. They are not intended to compensate for amplifier and/or loudspeaker deficiencies. Model 410 is intended for use with the highest quality professional type playback equipment. The output of the Model 410 is fed from a cathode-follower circuit and will work into any high quality audio or line amplifier having a high impedance input. It may also be used with a transformer for the purpose of feeding a 500 ohm line. Because of its flexibility, low noise and low distortion level, it is ideally suited for bridging and monitoring purposes and for critical listening applications.



THE MODEL 190 ARM . . .

is designed primarily for use with microgroove records. Its design has been recognized by leading audio engineers as that which incorporates all of the desirable tracking characteristics. Analysis has shown that for maximum performance with LP records the vertical mass of the moving arm element must be held to a minimum and further, that the arm must be counterbalanced about the vertical axis. This permits minimum stylus or tracking force and provides maximum record life. The Model 190 Arm embodies these all important features necessary for proper microgroove record playback.

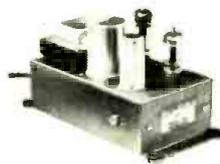

MODEL 230H EQUALIZER-PREAMPLIFIER . . .

is unique in its accuracy of equalization and frequency response. The intermodulation distortion is .2 per cent at normal output level. It is intended for use with high quality amplifiers having gain and tone controls. When used with the Pickering Model 132E Record Compensator the 230H is ideal for radio station and recording studio use and for applications requiring accurate low noise and distortion free playback.



MODEL 132E RECORD COMPENSATOR . . .

is designed to be used in conjunction with a magnetic cartridge preamplifier such as the Pickering 230H or any preamplifier which provides 6 db per octave bass boost. Six playback positions are incorporated:

- 1—European 78 rpm Records
- 2—Victor 45 rpm and Decca 78 rpm Records
- 3—No high frequency roll-off, 500 cycle turnover
- 4—All Capitol Records, new Victor 33 $\frac{1}{3}$, Audio Engineering Society Curve
- 5—Columbia, London and most LP Records
- 6—To remove the hiss from old noisy records

Precision elements are used in its construction to give accurate compensation. The 132E is inherently a low distortion R-C device.

PICKERING PROFESSIONAL AUDIO EQUIPMENT

"For those who can hear the difference"

...Demonstrated and sold by Leading Radio Parts Distributors everywhere.
For the one nearest you and for detailed literature, write Dept. C-2




PICKERING and company incorporated • Oceanside, L.I., New York


2 Good reasons

why it pays
to sell...

alliance
TENNA · ROTOR

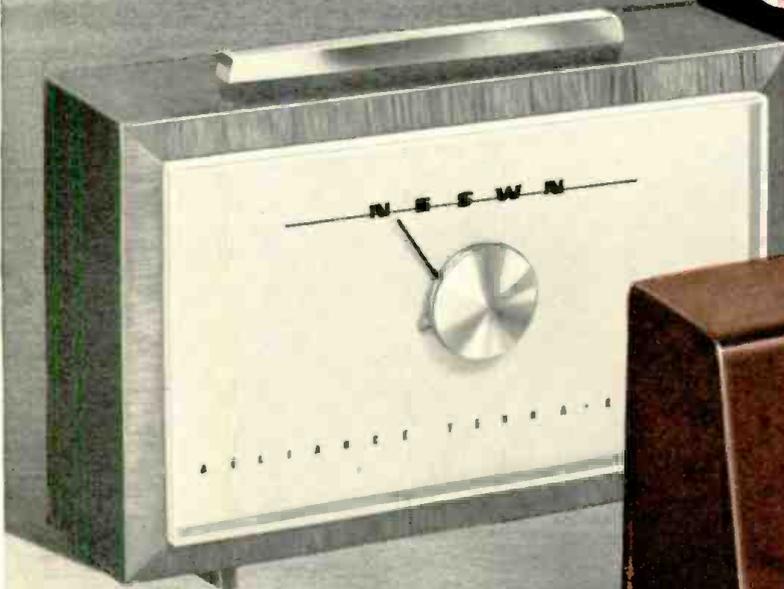

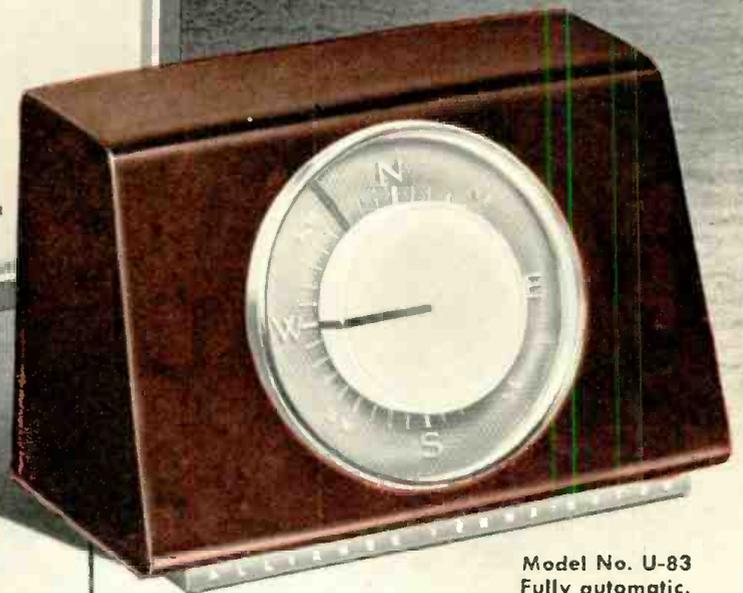Model No. T-10
Manual control.
Shows antenna direction.



Model No. U-83
Fully automatic.
Set it and forget it!

1

Complete new styling—modern—with new eye appeal. See how both manual and automatic models have been improved outside and inside. And remember, only Alliance has the rotator that's fully automatic!

2

More powerful pre-selling than ever—TV, magazines, newspapers. Sound reasons why Alliance Tenna-Rotors will continue to be the profit line for you! Better check your stock right now.

OVER ONE MILLION ALLIANCE TENNA-ROTORS HAVE NOW BEEN MADE

ALLIANCE MANUFACTURING COMPANY, ALLIANCE, OHIO

September, 1953

31

NEW

WALSCO *Imperial*

*

PROVEN THE MOST ADVANCED UHF CONVERTER IN AMERICA



NEW distinctive cabinet design available in beautiful assortment of COLORS

WITH EXCLUSIVE
Turretune

UP TO

GREATER POWER
GAIN

UP TO

88%

LESS NOISE
FACTOR

*** FACTS** from one of America's leading, independent research laboratories proved the WALSCO Imperial will out-perform all other UHF converters... anywhere!

	Average Power Gain dB			Average Noise Factor dB		
	500 mc	650 mc	800 mc	500 mc	650 mc	800 mc
WALSCO Imperial	10.0	9.5	9.5	15.0	15.5	16.0
Converter A	6.0	5.4	3.5	18.5	20.0	21.0
Converter B	7.0	6.5	5.0	18.0	18.5	20.0


WRITE FOR COMPLETE INFORMATION

WALSCO ELECTRONICS CORPORATION


3602 Crenshaw Blvd. • Los Angeles 16, California



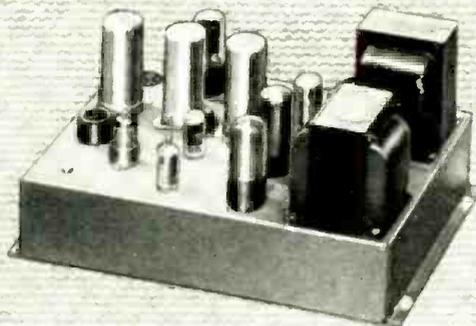THE FAMED LC-1A SPEAKER—for years the measure of perfection among users of professional-quality equipment. Now, more brilliant than ever with RCA's INTERMATCHED High-Fidelity. Now, cleaner than ever with ACOUSTIC DOMES on low-frequency cone DISPERSION VANES on hi-frequency speaker.



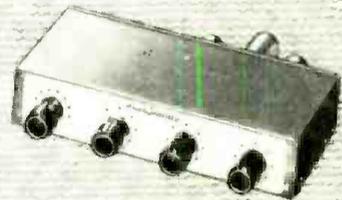DE LUXE AMPLIFIER—"power-proportioned" to the exact requirements of RCA INTERMATCHED High-Fidelity equipment. An unusual combination of power and balance for the most discerning high-fidelity enthusiast.



FULL-FUNCTION PRE-AMPLIFIER—carefully engineered to match RCA's DeLuxe 10- and 20-watt amplifiers—includes equalization for four types of recording characteristics—four input selector positions—volume control—bass and treble controls.

RCA Intermatched High-Fidelity A New Idea in Extended-Range Sound

Now HEAR high-fidelity as you've never heard it before—the thrilling extended-range reproduction of RCA's new INTERMATCHED High-Fidelity Systems.

Here is truly fine reproduction at every price level. Here is equipment designed *all the way through* to offer the finest in high-fidelity sound.

INTERMATCHED RCA High-Fidelity equipment offers you—for the first time ever—a wide selection of units designed to meet the music lover's needs. Intermatching lets you buy a fine—but reasonably priced—RCA system now, and progress to the finest—without fear of mismatching at any stage. Or you can buy the finest now with the assurance that all components are engineered to work as a system.

RCA—with its great background in all phases of professional-quality sound—has built into its intermatched line a combination of thorough engineering


and thorough understanding of good-music reproduction. Only RCA can offer you equipment so thoroughly intermatched that you can interconnect any RCA components you choose—merely by plugging one unit into another.

Now, ask your local RCA Electronics Distributor to let you hear true, high-fidelity through RCA's INTERMATCHED High-Fidelity Systems.



RCA INTERMATCHED CABINETS

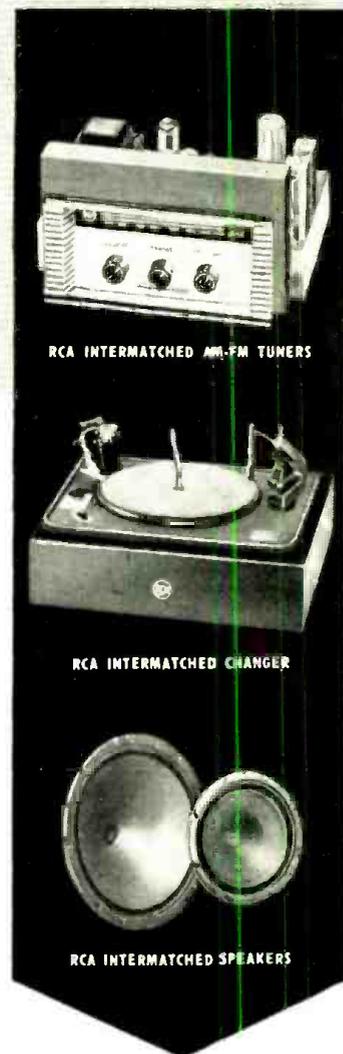Fine furniture—fine, high-fidelity units—styled to the requirements of RCA INTERMATCHED High-Fidelity System.



RCA INTERMATCHED AM-FM TUNERS

RCA INTERMATCHED CHANGER

RCA INTERMATCHED SPEAKERS

FOR FULL DETAILS AND ADDRESS OF YOUR LOCAL DISTRIBUTOR MAIL COUPON NOW

- RCA Engineering Products Dept. 221U, Building 15-1, Camden, N. J.
- Please send me your new booklet on RCA Intermatched High-Fidelity Equipment.
 - Please send me information on RCA Victor High-Fidelity "Victrola"® phonographs.

Name _____
 Address _____
 City _____ Zone _____ State _____



RADIO CORPORATION of AMERICA

ENGINEERING PRODUCTS DEPARTMENT,

CAMDEN, N. J.

©Tmks.

New! 7 INCH PUSH-PULL OSCILLOSCOPE

Only **EICO** Has All These Features:

- VERTICAL FREQ. RESPONSE: flat ± 2 db 10 cps - 1 mc
- VERTICAL SENS.: .01 volts rms/inch
- HOR. FREQ. RESP.: flat ± 0 db 10 cps - 200 kc, -4 db at 500 kc
- HOR. SENS.: .3 volts rms/inch
- SWEEP RANGE: 15 cps-100 kc
- 3-STEP FREQ.-COMPENSATED ATTENUATOR eliminates freq. distortion, overloading.
- CATHODE FOLLOWER inputs to both amplifiers
- PUSH-PULL outputs in both amplifiers
- RETURN TRACE BLANKING
- INT. VOLTAGE CALIBRATOR
- V & H TRACE EXPANSION & CENTERING: 1.5X full screen without distortion.
- DIRECT CONNECTION to vert. CRT plates.
- PHASING CONTROL of internal 60 cps sine wave sweep.
- AT FRONT PANEL: Intensity mod. input; 60 cps, sawtooth outputs.



MODEL 470K
KIT \$79.95. WIRED \$129.50.

Also Available:
425K 5" PUSH-PULL SCOPE KIT \$44.95. WIRED \$79.95.

- AC & DC volts: 0-5, 10, 100, 500, 1000 V (30 KV with HVP-1 probe).
- 5 ohm ranges from .2 ohm to 1000 megs.
- DC input Z 26 megs.
- 4 1/2" meter movement in can't-burn-out circuit.
- 1% mult. resistors.



221K VTVM KIT \$25.95. WIRED \$49.95.

- HIGH VOLTAGE PROBE \$6.95
- Extends range of VTVMs & voltmeters to 30 KV.



PIX TUBE ADAPTER for Tube Testers \$4.50. Checks TV picture tubes while in set.



625K TUBE TESTER KIT \$34.95. WIRED \$49.95.

- Illum. gear-driven "Speed Rollchart."
- New lever-action switches for individual testing of every element.
- Tests all conventional & TV tubes.

- Covers all TV & FM freqs. between 500 kc & 228 mc in continuous sweep.
- Sweep width variable 0-30 mc.
- Crystal marker oscillator, variable amplitude.



360K SWEEP GEN. KIT \$34.95. WIRED \$49.95.



214K VTVM KIT \$34.95. WIRED \$54.95.

- Large 7 1/2" meter, can't-burn-out circuit.
- AC/DC volts: 0-5, 10, 100, 500, 1000 (30 KV with HV Probe).
- 5 ohms ranges from .2 ohm to 1000 megs.
- DC input Z 26 megs.
- 1% mult. resistors.



950A-K R-C BRIDGE & R-C-L COMP. KIT \$19.95. WIRED \$29.95.

- Measures & tests all resistors; .5 ohm to 500 megohms.
- Every type condenser, 10 mmf to 5000 mfd.
- 0-500 DC voltage source for capacitor leakage testing.



145K SIG. TRACER KIT \$19.95. WIRED \$28.95.

- Audibly signal traces all IF, RF, Video & Audio circuits from ANT to SPKR or CRT in all TV, FM, AM, etc. without switching.
- Germanium crystal diode probe responsive to over 200 mc.
- Integral test speaker.

NOW! ONLY EICO - the largest manufacturer of its kind in the world - gives you **LIFETIME SERVICE & CALIBRATION GUARANTEE*** .. the Industry's greatest protection for your test equipment investment!

* at less than our cost of handling (see the EICO Guarantee Card enclosed with each Kit and Instrument).



NEW!
SCOPE VOLTAGE CALIBRATOR KIT
495K KIT \$12.95. WIRED \$17.95.

- Sq. wave output at power-line freq. with full-scale readings of .1, 1, 10 or 100 V. peak-to-peak.
- Accuracy $\pm 5\%$ of full-scale on each range.

NEW!
6V & 12V BATTERY ELIMINATOR KIT
1050K KIT \$29.95. WIRED \$38.95.

- DC output: 0-8 V or 0-16 V.
- Continuous current ratings: 10 A at 6 V, 6 A at 12 V.
- Intermittent current rating: 20 A at 6 V, 12 A at 12 V.
- Separate Voltmeter & Ammeter.



NEW!
DECADE CONDENSER BOX KIT
1180K KIT \$14.95. WIRED \$19.95.

- All capacitors precision silver mica, accuracy $\pm 1\%$.
- Range from 100 mmf - 0.111 mfd in steps of 100 mmf.
- Smooth-action positive detent ceramic switches.

Prices 5% higher on West Coast. Specifications and prices subject to change without notice.



536K MULTIMETER KIT \$12.90. WIRED \$14.90.

- 1000 Ω/V ; 31 ranges
- DC/AC volts: Zero to 1, 5, 10, 50, 100, 500, 5000.
- DC/AC Current: 0-1, 10 ma; 0.1, 1 A.
- Ohms: 0-500, 100 K, 1 meg.



377K SINE & SQUARE WAVE AUDIO GEN. KIT \$31.95. WIRED \$49.95.

- Complete sine wave coverage, 20-200,000 cps in 4 direct-reading ranges.
- Complete square wave coverage, 60-50,000 cps.
- Cathode follower output circuit.



565K MULTIMETER KIT \$24.95. WIRED \$29.95.

- 20,000 Ω/V ; 31 ranges.
- DC/AC Output volts: 0-2.5, 10, 50, 250, 1000, 5000.
- DC Current: 0-100 ua; 10, 100, 500 ma; 10 A.
- Ohms: 0-2K, 200K, 20 meg.



320K SIG. GEN. KIT \$19.95. WIRED \$29.95.

- Fundamentals 150 kc to 34 mc, harmonics to 102 mc.
- 5-step band switching.
- Colpitts audio oscillator generates 400 cps pure sine wave voltage.
- Permits pure RF, modulated RF, or pure AF.



1171K RES. DECADE BOX KIT \$19.95. WIRED \$24.95.

- Resistance values from 0 to 99,999 ohms with 0.5% precision.
- All resistors have 0.5% accuracy.



- Covers range of 75 kc to 150 mc.
- 7 calibrated scales: accuracy better than 1%.
- Bandspeed vernier tuning.
- 4-step RF shielded output multiplier: constant output Z.




Write NOW for FREE latest Catalog R-9

You build EICO Kits in one evening, but . . . they last a lifetime!
And you SAVE OVER 50%! See the famous EICO line TODAY, in stock at your local jobber.

ELECTRONIC INSTRUMENT CO., Inc., 84 Withers Street, Brooklyn 11, N. Y.

Fig. 1. The new Standard Coil 82-channel tuner. The front subchassis contains the u.h.f. coil strips. The tuner is about two inches longer than the 13-channel model and has the same width and height.

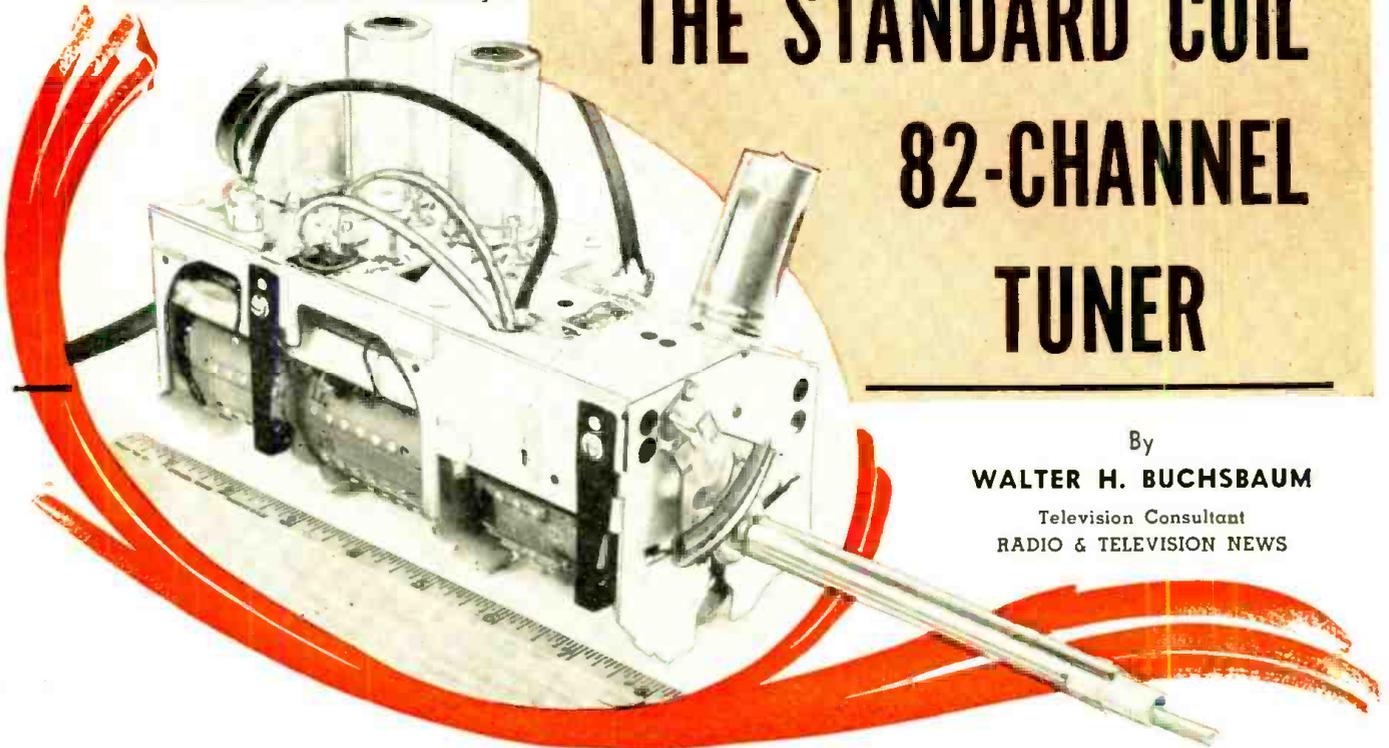

THE STANDARD COIL 82-CHANNEL TUNER

By
WALTER H. BUCHSBAUM
Television Consultant
RADIO & TELEVISION NEWS

WITH the rapid spread of u.h.f. television a large variety of converters, plug-in strips, and similar devices have appeared on the market, all designed to allow v.h.f. receivers to operate on the new channels. Some of the manufacturers have even built various types of u.h.f. converters into their receivers and a few are using a combination u.h.f.-v.h.f. tuner, consisting of continuously-tuned u.h.f. and switch-tuned v.h.f.

The latest development in tuners is actually the first true 82-channel step tuner, allowing the viewer to switch u.h.f. and v.h.f. channels with the same facility and accuracy.

The new *Standard Coil Products Co.* 82-channel tuner is the result of an extensive development program and contains many unique features. Using three tubes and a mixer crystal, this unit provides as much sensitivity on u.h.f. as on v.h.f., with excellent noise factors on both bands. Only slightly larger than the company's v.h.f. tuner, both u.h.f. and v.h.f. coil strips can be removed simply, and the entire drum assembly can be taken out for servicing without unsoldering or unscrewing anything.

As can be seen from Fig. 1, the tuner consists essentially of the v.h.f. chassis and drum with the u.h.f. section in front of it. The v.h.f. portion uses a 6BZ7 in a cascode r.f. amplifier and a 6U8 as a triode oscillator and pentode mixer. Twelve sets of coil strips tune in the v.h.f. channels and produce the i.f. signal. An improved cascode circuit permits better a.g.c. control over that stage and thus reduces the danger of overloading in strong signal areas. The u.h.f. portion

Complete description of the new turret tuner for both u.h.f. and v.h.f. reception, including service data.

uses a 6AF4 or 6T4 oscillator. The u.h.f. input is obtained through a built-in high-pass filter and then a double-tuned r.f. bandpass network. A 1N82 crystal mixer, mounted in a special socket at the top, provides the i.f. output signal from the u.h.f. tuner section. This i.f. signal is coupled to the v.h.f. section through a short shielded cable and plug. The r.f. bandpass network and oscillator tank circuit is switched through a set of eight coil strips, each containing the circuits for ten channels. Individual u.h.f. channels are tuned in through a 3-section concentric ceramic rotor which changes bandpass and oscillator frequencies as required. A fine tuning adjustment is provided for both v.h.f. and u.h.f., mounted on the same shaft but consisting of two different condensers. The u.h.f. oscillator tube is mounted on a slanted portion of the u.h.f. subchassis to help shorten leads.

The v.h.f. and u.h.f. antenna leads are brought to different terminals in the model shown in Fig. 1, but a coupling transformer will probably be used in later versions. All power connections are made to the v.h.f. chassis, and a simple plug and two wires bring heater and "B+" over to the u.h.f. chassis. This permits separate alignment and assembly.

As can be seen from Fig. 1, two different detent springs control the

motion of the u.h.f. and v.h.f. drums. When the v.h.f. drum turns, the u.h.f. drum stands still, but the ceramic rotor inside the u.h.f. chassis turns on the same shaft as the v.h.f. drum. Together with an ingenious internal cam arrangement, this permits very simple knob presentation. In effect, the customer simply turns the inner knob to tune the digits and v.h.f. Channels 2 to 13. When a u.h.f. station is selected, the outer knob is turned to show the tens. Thus, when Channel 24 is desired, the outer knob is set to 2 and then the inner knob is turned to 4. The numbers on the knob are so arranged that Channels 2 to 10 appear in one window while Channels 11, 12, and 13 appear both in the v.h.f. and u.h.f. window. Channel 14 appears only in the u.h.f. window. Tuning from Channel 13 to 14, or from Channel 83 to Channel 2, requires only a single turn, the internal changes being made automatically by the special cam. This mechanism is described in more detail later, but as far as the customer is concerned it really simplifies tuning tremendously.

When the u.h.f. channels are tuned in, the v.h.f. oscillator is disconnected and a special i.f. coil strip is switched into the v.h.f. circuit. This changes the 6BZ7 into a 41-mc. or 21-mc. amplifier and the pentode portion of the 6U8 operates as an i.f. stage. Because

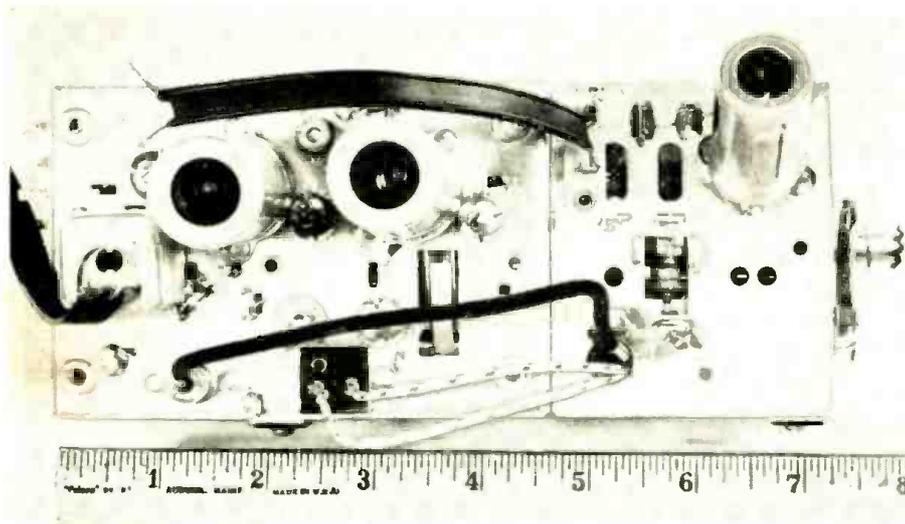



Fig. 2. Top view of the tuner showing the various adjustment points. See text.

of this unique arrangement, the u.h.f. sensitivity of this tuner is practically the same as for v.h.f.

The outermost shaft serves as fine tuning adjustment just as in present *Standard Coil* tuners. In Fig. 1, the friction drive for the fine tuning control can be seen together with its "off-center" shaft. Both the u.h.f. and v.h.f.

fine tuning rotors are mounted on this shaft. Both consist of a dielectric which moves between two stator plates. In the v.h.f. chassis the fine tuning stator plates are part of the local oscillator and mounted directly on that chassis. For u.h.f., the fine tuning uses a portion of the oscillator condenser plates which protrude outside the u.h.f. coil

Fig. 3. Complete schematic diagram of the 82-channel *Standard Coil* tuner. At the lower left is the u.h.f. oscillator; lower right, the i.f. coil section.

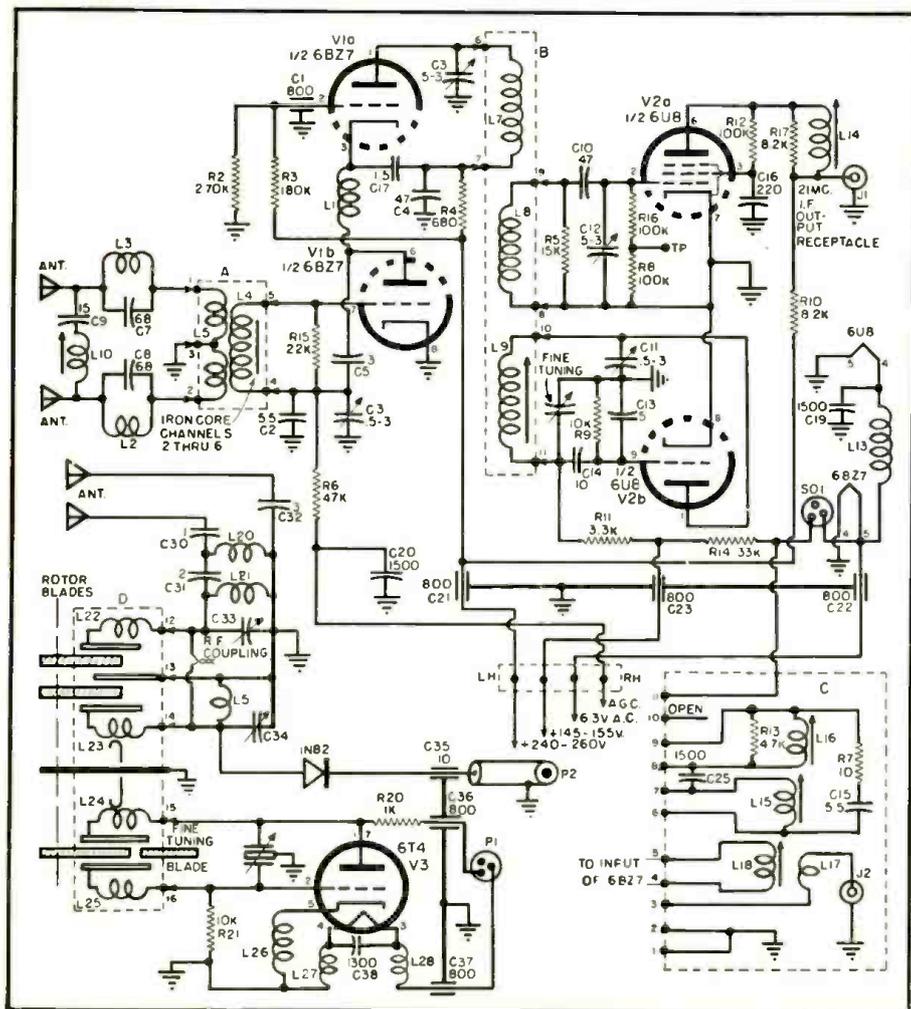

plates. In effect, the fine tuning is then in parallel with the ceramic rotor inside the drum.

Circuit Analysis

The complete circuit diagram of the tuner is shown in Fig. 3. The upper portion consists of the v.h.f. section which features balanced 300-ohm input with a tunable i.f. filter. This filter is contained in the small shield can at the left in Fig. 2. The 6BZ7 is connected in a series-type cascode circuit requiring 240 to 260 volts "B+". Current drain from this "B+" varies from 20 to 30 ma., depending on channels used. As in previous *Standard Coil* tuners, the antenna input coil is switched, permitting good bandwidth and impedance match for each channel. To avoid overload under excessively strong signals, the first cascode stage is controlled by a.g.c. bias.

The 6U8 mixer and oscillator represent some improvement over the older dual triode (6J6) in that the pentode mixer gives considerably more conversion gain while the triode section acts as a conventional oscillator. The pentode operates at the higher "B+" (240-260 v.) while the oscillator uses 145 to 155 volts. The current required from this "B+" varies between 12 and 17 ma. As in previous *Standard Coil* tuners, the r.f. mixer, and oscillator coils are mounted on a single coil plate, and the oscillator coil is slug-tuned. The oscillator tuning slug can be adjusted from the front of the tuner just as in the v.h.f. models, but this time a longer tool must be used since it has to pass through the u.h.f. chassis. Power connections to the tuner are made through a set of terminal lugs at the rear of the v.h.f. section.

The tuner described here is designed for 21-mc. i.f. The same tuner is also available for 41-mc. and is identical in all respects except for the i.f. and oscillator coils.

At the lower left of Fig. 3 is the u.h.f. circuit. The 300-ohm input goes through a high-pass filter which attenuates all frequencies below 470 mc. Coils L_{20} and L_{21} are small diameter air core coils and condensers C_{36} and C_{37} are part of an assembly of silver-plated metal and dielectric strips riveted together.

The u.h.f. r.f. bandpass network consists of an input coil L_{20} , and the coupling condenser formed by three plates and the ceramic rotor blades. The center plate of this condenser is grounded, keeping the total capacity quite low. L_{23} and L_{25} form a tapped coil arrangement tuned to match the impedance of the 1N82 crystal mixer to the r.f. bandpass network. The oscillator signal is coupled to L_{23} through a small piece of wire.

The u.h.f. oscillator uses a series-resonant circuit between plate and grid of the 6T4 (or 6AF4) tube. The center of this series circuit is a condenser whose plates are part of the u.h.f. coil strip and which is tuned by the ceramic rotor and the fine tuning control. The dotted section marked

"D" represents all the components which are part of each u.h.f. decade coil strip which is switched for every ten u.h.f. channels.

Stationary adjustments which are tuned for all u.h.f. channels include the r.f. bandpass condensers C_{10} and C_{11} and a split-stator oscillator trimmer condenser. The twisted wires marked "R.F. Coupling" form a small condenser which is adjusted at the factory.

The dotted box marked "C" on the diagram of Fig. 3, represents the 21- or 41-mc. i.f. coil section, which is switched in during u.h.f. operation. The contact numbers on section "C" correspond to the spring contacts made by the v.h.f. coil plates "A" and "B." When a u.h.f. channel is switched in, coil section "C" is depressed and connects to the stationary v.h.f. springs. At the same time these springs are bent away from the v.h.f. coil plates, so that only the components mounted on "C" are in the circuit.

Coils L_{17} and L_{18} form a transformer, coupling the output of the u.h.f. crystal mixer to the grid of the cascode amplifier. The network consisting of L_{17} , L_{18} , and associated condensers and resistors is a double-tuned broadband circuit between the output of the cascode and the input of the 6U8 pentode which acts as a regular i.f. amplifier. Contacts 10 and 11 take the place of the v.h.f. oscillator coil. By leaving 10 open, no plate voltage can reach the v.h.f. oscillator. At the same time, contact 11 shorts out the 33,000-ohm resistor, R_{11} , and places the 145-volt "B+", through R_{12} , on the plate of the u.h.f. oscillator. All "B+" and heater leads are isolated by means of r.f. chokes and special ceramic 800- μ fd. feedthrough condensers.

Mechanical Features

Height and width of the new tuner are approximately the same as for previous v.h.f. models, but the length has been increased about 2 inches. Shaft dimensions will depend on the cabinet and chassis designs of individual manufacturers.

The top view of the tuner (Fig. 2), shows the location of all adjustments, except for oscillator tuning for each channel which is done from the front. Starting at the left is the tunable i.f. interference trap, housed in a small shield can with two solder lugs for connection to the v.h.f. antenna. The tube next to it is the 6BZ7 with the input and output trimmer condensers on either side of it. At the lower edge is the connector plug and cable which brings the output of the crystal mixer to the v.h.f. section. The u.h.f. power plug with its heater and "B+" leads is to the right of this plug. Shown also is the cutout through which the v.h.f. fine tuning condenser protrudes. The remaining two trimmer condensers adjust the v.h.f. oscillator and the pentode mixer input tuned circuits. Between the two tubes, towards the upper edge of the chassis is the connection for the i.f. output to the TV

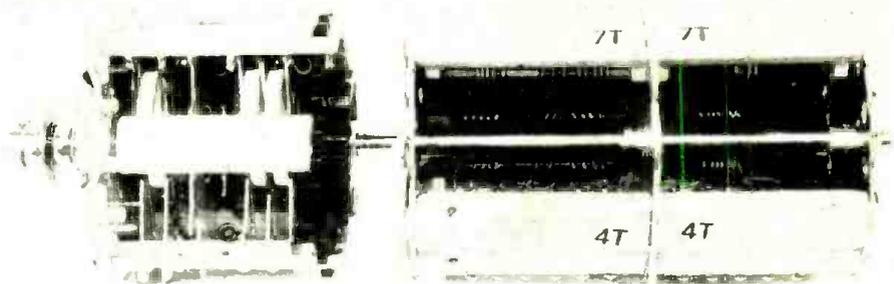


Fig. 4. The tuner drum. Section at left contains u.h.f. components, v.h.f. at right.

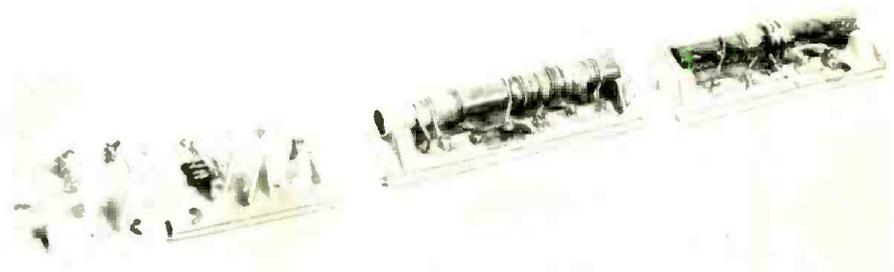


Fig. 5. Three strips from tuner. On left is u.h.f. strip, with v.h.f. strips at right.

chassis and, next to it hidden by the u.h.f. antenna line, is the slug-tuned i.f. output coil.


The smaller chassis in Fig. 2 contains all u.h.f. circuits. As can be seen from Fig. 1, the u.h.f. oscillator tube is mounted on a sloping portion of the chassis. Two slots in the chassis to the right of the u.h.f. antenna terminals permit adjustment of C_{10} and C_{11} (see Fig. 3), the tuning condensers for the u.h.f. bandpass network. Particularly interesting is the rectangular cutout which contains a special socket to hold the 1N82 crystal mixer. Because the lead length is so critical at u.h.f., and because it is sometimes necessary to change crystals during the production testing process, Standard Coil designed this crystal socket right into the tuner. The crystal can be removed by pulling the exposed end upwards and then withdrawing the other end from its round socket. Each coil strip has an oscillator adjustment accessible from


the front, located near the tuning shaft. This adjustment consists simply of a silver-plated screw which approaches the stator of the main tuning condenser. Fig. 4 shows these screws quite clearly, mounted on the metal detent plate on the front of the drum and reaching towards the stators.

In Fig. 4 is shown the entire u.h.f. and v.h.f. drum arrangement, with some of the coil plates removed to show the inside. The entire drum assembly can be removed from the tuner by removing three shaft locking springs. The smaller drum at the left is the u.h.f. portion. Notice the stator plates mounted in each coil section, and the three ceramic rotors which tune them to individual u.h.f. channels. Between the u.h.f. and v.h.f. drums, and forming one end of the u.h.f. drum, is a black plastic molding which contains the key to the unique

(Continued on page 180)

Fig. 6. Under chassis view of the tuner with drum removed to show the switch springs.

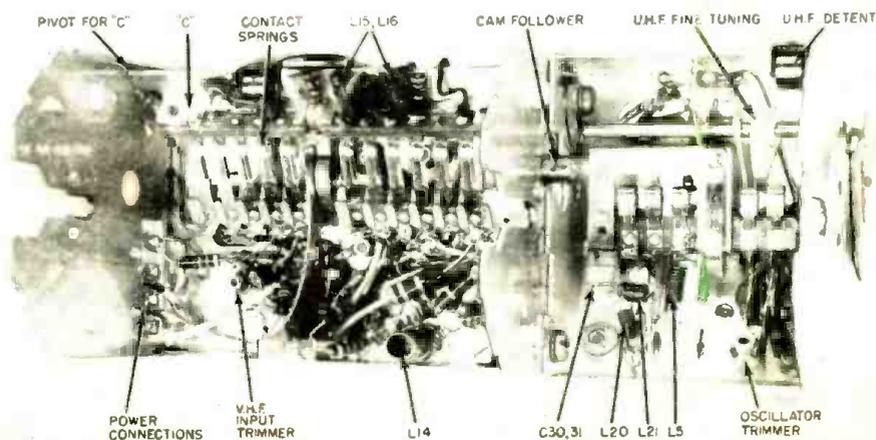

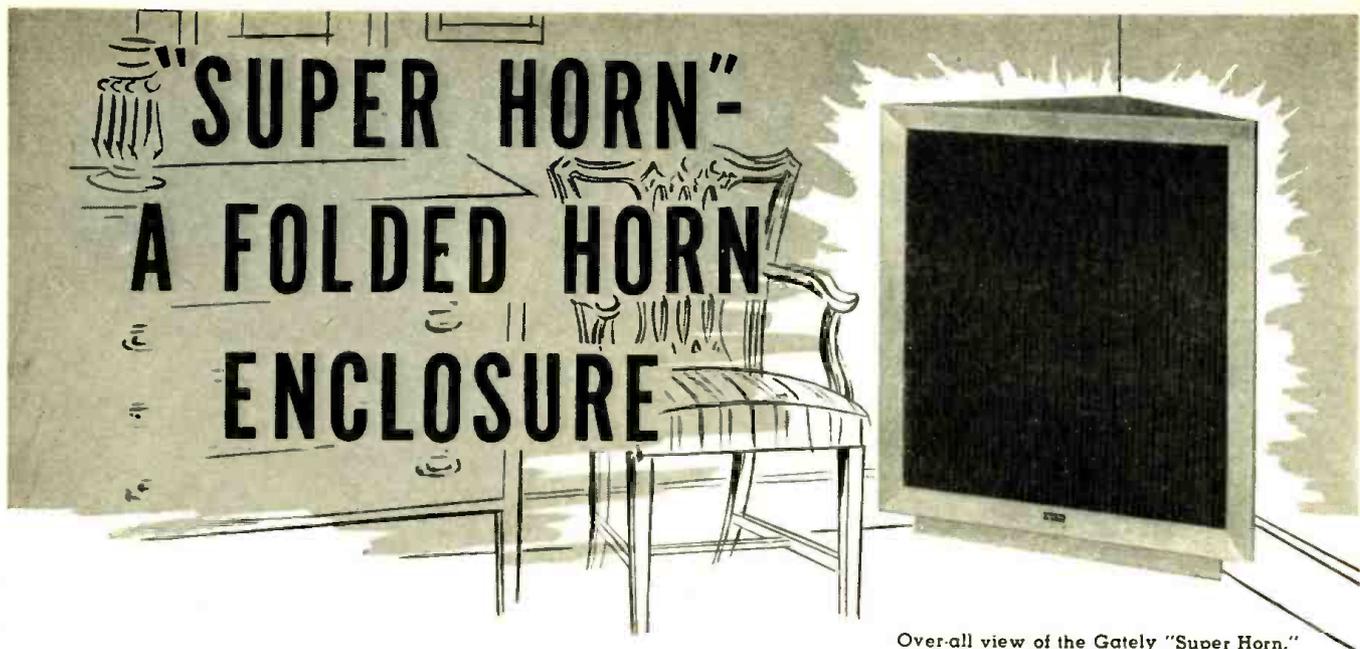

By **EDWARD J. GATELY, JR.** and **THOMAS A. BENHAM**
Gately Development Laboratory

Construction details on a reasonably-priced enclosure which is designed to accommodate either 12-inch or 15-inch speakers.

GOOD MUSIC reproduction requires that the product of the low and high frequency cut-off points must be approximately 600,000; that is, 40 x 15,000 cps. Some modern source materials cover this range. Electronic components have been developed to handle this range with low harmonic and intermodulation distortion. However, a satisfactory loudspeaker and enclosure that will do justice to the available material is the most expensive part of the phonograph reproducing system. A satisfactory, reasonably-priced enclosure, designated as the "Super Horn," has been developed to be used in conjunction with many of the better speaker systems to obtain good bass reproduction.

Attaining reproduction down to 40 cycles must not be accomplished with increase in distortion or at the expense of power handling ability of the system or transient response. Power handling of the extremely low bass tones can be accomplished only by moving large masses of air. A single 12-inch or 15-inch cone can not move the large masses of air required at low frequencies, unless the impedance of the air is properly matched to that of the mechanical vibrating system. Of course, a large number of 12-inch speaker elements, each operating at very low amplitude can equal the performance of a single speaker, properly loaded, but the resulting cost of multiple high-quality speakers and a cabinet to house them is prohibitively high. One means of properly loading a single speaker is to place it in an exponential horn. If the horn is correctly designed, it serves as a transformer to match the impedance

of the air which is to be moved to the vibrating system. However, a horn which is designed to reproduce low frequencies satisfactorily must have a low rate of flare and a large mouth area. The basic horn equation is

$$A = A_0 e^{mx}$$

where: A = area at any point along horn axis

A_0 = area of throat of horn

x = distance along axis of horn

$m = 4\pi f_0 / c$ constant denoting taper rate of horn

f_0 = cut-off frequency of horn

c = velocity of sound in air

The mouth area of the horn should equal approximately the area of a circle whose diameter is $1/\pi$ times the wavelength of the lowest frequency to be reproduced. For a horn having a theoretical cut-off at 40 cycles the area of the horn should double every 18 inches and the mouth should have an area of approximately 8400 square inches. If the horn is to be used with a 12-inch speaker which has an effective cone area of 75-square inches the horn would be approximately $10\frac{1}{2}$ feet long.

The physical length of a horn may be reduced by folding it. However, this folding process must be done in such a way as to prevent the production of standing waves within the horn. These standing waves impair the transient response of the system and introduce peaks and valleys in the response curve. The length of the horn can be reduced by designing it so that it may be placed in the corner of a room so as to use the walls and floor as extensions of the horn. Fig. 1 shows a "Super Horn" with front grille

Over-all view of the Gately "Super Horn," demonstrating its adaptability to either modern or traditional decorative schemes.

assembly removed, mounted in a corner of a room, and illustrates how images of the horn mouth are formed by the floor and walls of the room. Images I_1 , I_2 , and I_3 are real images, while I_4 and I_5 are virtual images. The existence of these images can be easily proved by setting up three hand mirrors in a mutually perpendicular configuration so that they represent the walls and floor of a room. Inserting a small piece of paper in the position the horn mouth would normally occupy will quickly illustrate the manner in which the acoustic images are formed.

The "Super Horn" (Patents Pending) was designed to include all the previously mentioned criteria, and yet be small enough to fit into the corner of the average living room. The total fold of the horn is only 90° . The fold is accomplished by use of panel 1 (see Fig. 1) which is arranged at 45° to the original path of sound from the throat. Since the angle of incidence is equal to the angle of reflection, any acoustic reflections must pass out the horn. This 45° arrangement of baffle 1 materially reduces the possibility of standing waves.

The enclosure greatly increases the air loading on the cone of the speaker at low frequencies. This may be proved as follows. Reduction of bass resonance of a speaker can be accomplished in one or both of the following ways. (1) Increasing the compliance of the cone suspension and/or (2) adding mass to the cone either in the form of cone material or increased air loading. The reduction of resonance by addition of mass as a function of the mass is expressed by the following relation:

$$M_e = \frac{F_{r_m}^2}{F_r^2 - F_{r_m}^2} M_0$$

where: F_{r_m} = effective resonance of

the cone with mass added (cps)
 M_c = mass of cone (grams)
 M_o = mass added
 F_r = free-cone resonance of speaker

A typical 12-inch speaker having a free-cone resonance of 54 cps and a cone mass of 50 grams will have its resonance reduced to 38 cps when used in this enclosure. The air load on a 12-inch, infinitely-baffled speaker is 12.5 grams. In accordance with the relation given previously the increase in air loading is approximately 36 grams. This increased air loading reduces the necessary motion of the speaker for a given power output and thus reduces distortion due to non-linear suspension and non-linear air gap flux. Placing the same speaker in an infinite baffle of the same cubic content as the "Super Horn" raises the resonance to 61 cps due to the stiffness of the cavity behind the speaker. Since a speaker can radiate power only down to its resonant frequency, it is indicated that the "Super Horn" increases the range of the speaker system by nearly an octave over that obtainable in the same cubic content totally-enclosed box (from 61 to 38 cps). No tuning, porting, or other tricks are used to extend the apparent range of the "Super Horn," as this would tend to spoil the transient response of the enclosure. Acoustic damping on the speaker cone is greatly increased by the improved air loading. This is illustrated by Figs. 3 and 4. Fig. 3 shows the impedance vs frequency curve of a 12-inch speaker in a "Super Horn," while the "impedance curve" for the same speaker in a well padded infinite baffle of the same cubic content is shown in Fig. 4. The reduction in amplitude of the resonant peak is evident. The suppression of this peak indicates clearly the increased acoustic damping afforded by proper impedance matching between the air of the room and the cone of the speaker.

The ultimate test of any reproducer is the listening test. AB comparisons with vented enclosure and infinite baffles of the same cubic content clearly show the advantages of this design and its effects on damping and the resultant increased bass range. The increased power handling ability of the speaker system, considered as an integrated whole, is immediately noticeable on high-level organ pedal tones. Bass transients such as plucked strings or tympani are cleaned up and move up and down the scale as intended. This is due to the increased damping and non-resonant character of the baffle.

The dimensions of "Super Horns" designed for 12- and 15-inch speakers are shown in Fig. 5. Home constructors are cautioned to use 3/4-inch wood and to securely screw and glue all joints. This can best be done by fastening glue strips to the top so that screws can be run into them from each side. Speakers can be best fastened

by installing anchor nuts on the front panel, and running screws through the mounting holes in the speaker into the anchor nuts. This eliminates the danger of rupturing expensive loudspeakers which can result when using a stud system of mounting. A finished 15-inch "Super Horn" is shown in Fig. 2 with top and grille cloth frame assembly removed. This indicates the relative positions of the internal baffles. A photograph of a "Super Horn" in a typical home installation demon-

strates (see facing page) how, although the cabinet itself has the clean lines which characterize modern furniture design, it fits in with period-type furniture and decor.

BIBLIOGRAPHY

- Olsen, H. F.: "Elements of Acoustical Engineering," D. Van Nostrand Co., Inc., New York.
 —: "Cabinets for High-Quality Direct Radiator Loudspeakers," RADIO & TELEVISION NEWS, May 1951.
 Gately, E. J.: "Design for Better Bass," Audio Engineering, October 1952. —30—

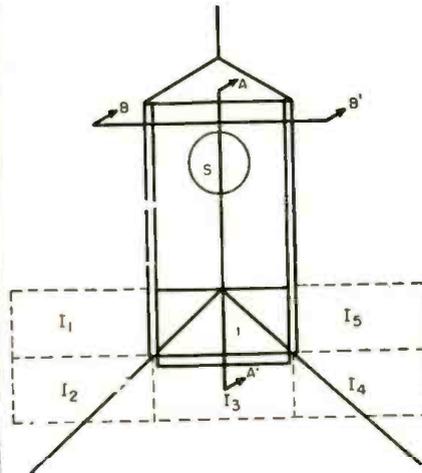


Fig. 1. Manner in which the walls and floor form images of the horn mouth.

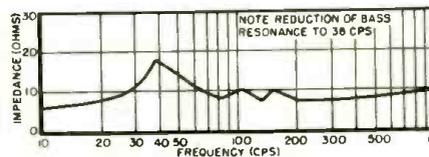


Fig. 3. Impedance vs frequency curve of 12" speaker in "Super Horn" enclosure.

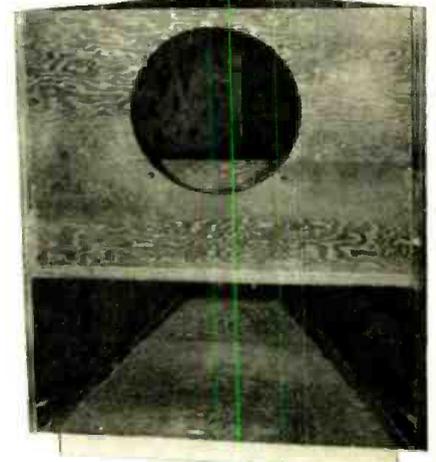


Fig. 2. Grille cloth frame assembly and top removed to show internal baffles.



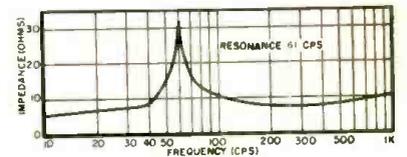


Fig. 4. Same speaker as Fig. 3 in enclosed box of same cubic content as "Super Horn".

Fig. 5. Dimensions for "Super Horn" enclosures to house 12- and 15-inch speakers.

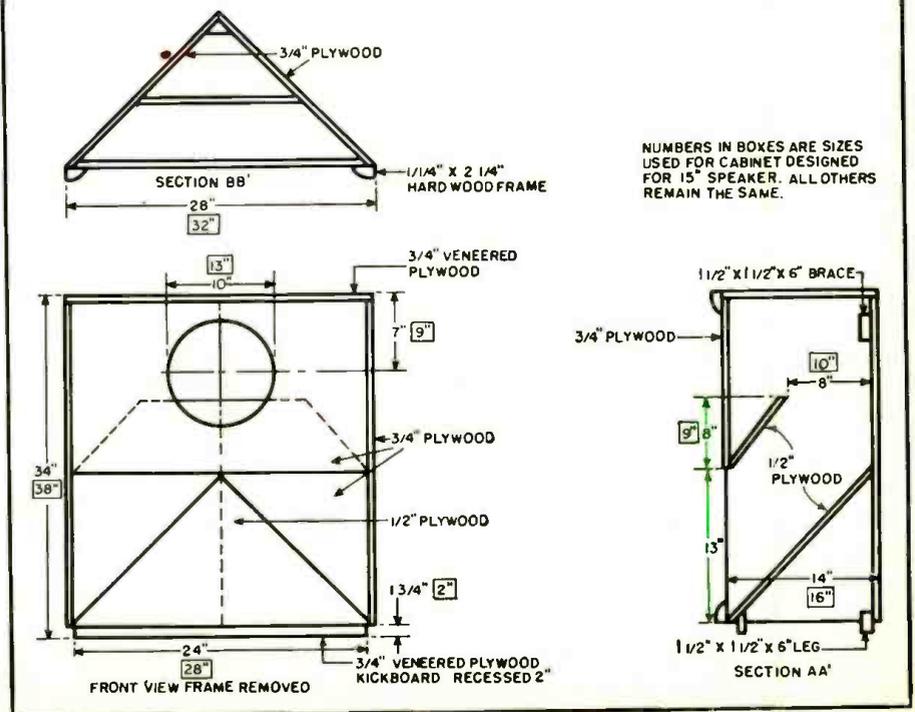

EXTENDED CLASS A AMPLIFIER

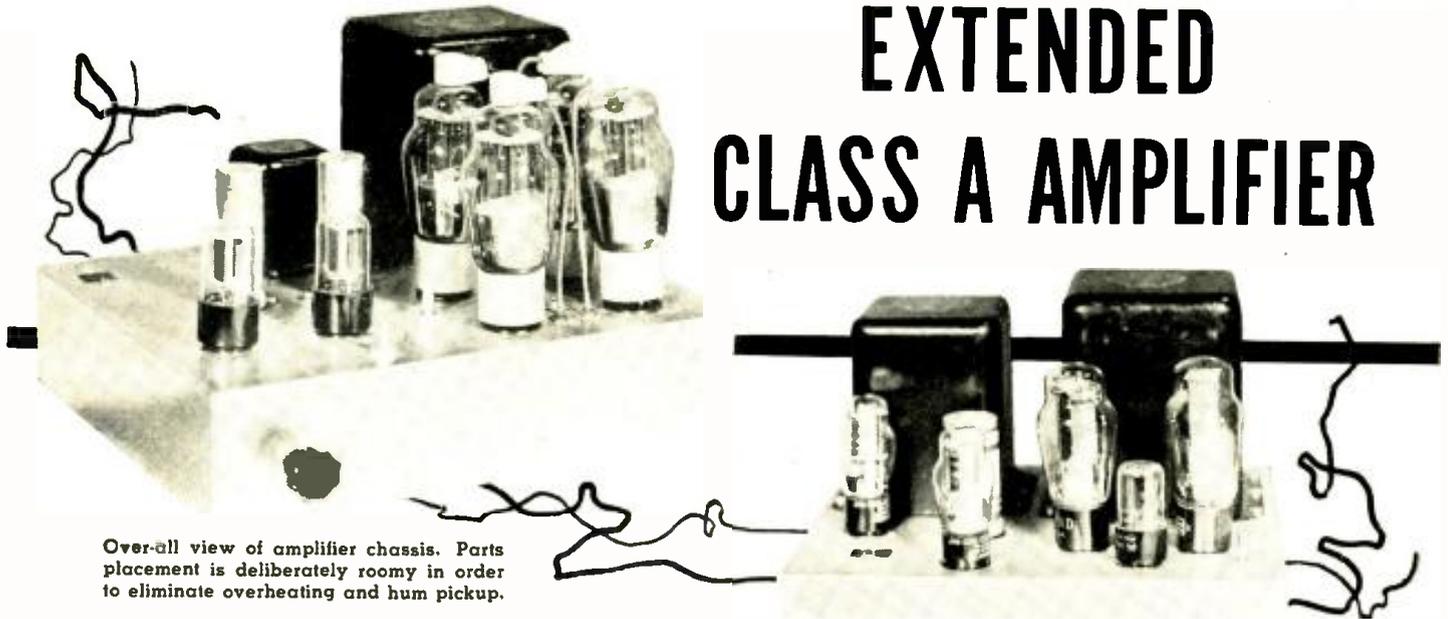

Over-all view of amplifier chassis. Parts placement is deliberately roomy in order to eliminate overheating and hum pickup.

The power supply chassis measures 10" x 12" x 3" and is separate from amplifier.

By LLOYD B. HUST

Triodes versus pentodes? Here's one answer. This 50-watt amplifier uses four beam power tubes—two connected as triodes, two as tetrodes—in push-pull parallel circuit.

THE range of development in the field of audio frequency amplification is of such tremendous scope that sometimes various methods of amplification and various systems with the claims made for them, tend to be rather confusing to the lay person. In fact, the proponents of different audio systems themselves often cannot agree as to the value of the various features of their systems. Perhaps the longest and most bitter feud has been between the advocates of triodes for power amplifiers *versus* the clique which claims that pentodes or tetrodes are superior. It is not intended in this article to add fuel to the flames of contention, but rather to acknowledge that both sides have some good points in their favor. The "RCA Receiving Tube Manual" states:

"Power tubes of the triode type in class A service are characterized by low power sensitivity, low plate-power efficiency, and low distortion. Power tubes of the pentode type are characterized by high power sensitivity, high plate-power efficiency, and relatively high distortion. Beam power tubes such as the 6L6 have a still higher power sensitivity and efficiency and have a higher power output capability than triode or conventional pentode tubes."

These facts have limited the use of triodes generally to amplifiers of rela-

tively low power, but low distortion, while pentodes, including beam power tubes, have been used in public address work and other applications where the highest fidelity is not of the greatest importance. This seems to substantiate the claims of the triode supporters that if one desires an amplifier of really "high quality" he must use triodes. The other faction points out that in order to have realism in the reproduction of music, certain passages call for surges of power in a range beyond that which can be economically supplied by triodes. In all probability the feud will never be settled, but there are some compromises which may give satisfaction to the advocates of each type. One such compromise is a system which uses *both* types of tubes, but in such a way that the advantages of each type can be realized, without the attendant disadvantages.

This system is called "extended class A" and is discussed by Howard T. Sterling in his article "Tube Applications in Amplifier Design" which appeared in the May, 1951 issue of the RADIO-ELECTRONIC ENGINEERING edition of RADIO & TELEVISION NEWS. In this type of operation, four beam power tubes—two connected as triodes and two as tetrodes—in a push-pull parallel arrangement are used. The bias voltage is such that under conditions of low power the tetrodes are cut off and the effect is the same as if a straight triode amplifier were being

used. However, when the signal voltage reaches such a level that high peaks of power are required, the pentodes conduct and satisfy the high power requirements of the amplifier. The tubes are operated under such conditions that at no time does their operation take them off the straight portion of the characteristic curve. Voltage and current requirements for 807's connected in such a system are as follows: plate voltage, 450; grid voltage, -45; screen voltage, 300; zero signal plate current, 110 ma. (triodes only conducting); maximum signal plate current, 256 ma. (all tubes conducting); power output, 47.5 watts.

The amplifier to be described in this article uses this mode of operation, and the extended class A feature does not introduce any problems which cannot be solved by the careful worker. It is necessary, for best results, to match the tubes, but that is the case with every high-quality amplifier. Tube types are not critical, and although the author used 807's as output tubes, many other types are suitable, including 6AR6's and 5881's.

The amplifier and power supply are built upon separate chassis, each 10" x 12" x 3". This method of construction eliminates many problems and makes testing very convenient. Of course, it would be possible to build the power supply on the same chassis as the amplifier, but precautions would have to be taken to guard against hum. The separate power supply method also has the advantage that the power supply can be used for experimental purposes with other equipment if desired.

It will be seen from the schematic diagram of the amplifier, Fig. 2, that it is actually a modified Williamson-type circuit. Some rather important changes have been made from the

original Williamson circuit, however. First, it will be noticed that the coupling between the first stage and the inverter is not direct coupling as in the Williamson circuit. This change was made in the interest of stability, particularly to obviate any unbalance developing in the circuit due to aging of the tube.

The phase-inverter circuit as used here can be thought to consist of three resistive elements in series, as is illustrated in Fig. 1. The first element consists of the 22,000 ohm plate-load resistor; the second consists of the plate resistance of the tube plus the bias resistance; and the third consists of the 22,000 ohm cathode-load resistor. This arrangement allows the biasing circuit to act as part of the tube resistance, and the only two elements which affect signal balance will then be the two 22,000 ohm resistors. Once these resistors are matched, the circuit will remain in balance, despite tube aging. The bias resistor, R_7 in Fig. 2, is shown as 3900 ohms. This value is not critical, but it does have some bearing on the signal balance as it will be seen that R_7 and R_8 act as a voltage divider as far as the signal voltage is concerned. If it is found that the signal voltage across R_7 is not the same as that across R_8 , then the value of R_7 can be changed until the two signal voltages are equal. R_7 may range anywhere between 2000 ohms and 5000 ohms.

As in any high-quality, push-pull amplifier, it is necessary to match the load resistors on each side of the circuit. This means that R_{15} and R_{16} should

be matched as should R_{15} and R_{16} . Two watt resistors were used as load resistors to minimize changes due to heating. The ones used by the author are *Ohmite* 10% resistors, pairs of which were carefully matched from a number of resistors. If the builder does not have equipment for matching resistors, it is suggested that he use 1% precision units for R_5 , R_6 , R_{15} , and R_{16} .

Although we often hear of the importance of matching load resistors in a push-pull circuit, little, if anything is said of the importance of matching coupling condensers. Although this may not be as important as the matching of resistors, it does have importance if good *over-all* balance is to be achieved in the amplifier. Condensers may differ in capacitance over a fairly wide range without too much effect at high frequencies, but at low frequencies, considerable unbalance may occur. Let us take the case of the condensers C_5 and C_6 , each of which is in one side of the push-pull circuit. Let us assume that these two condensers have a tolerance of $\pm 20\%$ which is common. Let us also assume that C_5 varies 20% in the positive direction and C_6 in the negative direction the same amount. The actual capacitance for C_5 would then be .3 $\mu\text{fd.}$, and C_6 would be .2 $\mu\text{fd.}$ The reactance unbalance at high frequencies would not be important because at high frequencies the capacitive reactance is low. However, a few simple calculations show us that at a frequency of 20 cycles, the reactance of C_5 would be about 26,500 ohms while


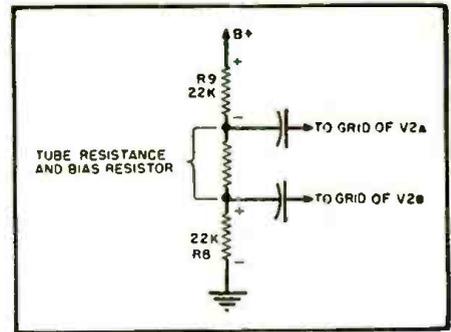


Fig. 1. How the inverter tube operates.

that of C_6 would be approximately 39,800 ohms. This difference of over 13,000 ohms would cause considerable signal unbalance at 20 cycles. Although it is unlikely that this extreme difference would exist with condensers chosen at random, it is entirely possible, and even much smaller differences in capacitance can be important at low frequencies.

Although the average experimenter does not possess equipment for matching condensers accurately, in most cases he can get this done at no cost. In most cities of medium or large size the high school laboratories will have capacitance and resistance bridges and those in charge of this equipment are usually willing to perform the service of matching a few pairs of resistors and condensers. In the smaller towns where the local high school does not have such equipment, one can usually make contact with the local telephone maintenance engineer. Even small telephone companies have accurate

Fig. 2. Schematic and parts list covering the amplifier section. Quality parts are used throughout to insure good performance. A cable connects this chassis to the power supply. Two Jones six-prong plugs are required for this cable. One pair of sockets and plugs could be eliminated by extending the wiring, cabled, between the amplifier and power supply. The four-prong socket is for connecting a preamp.

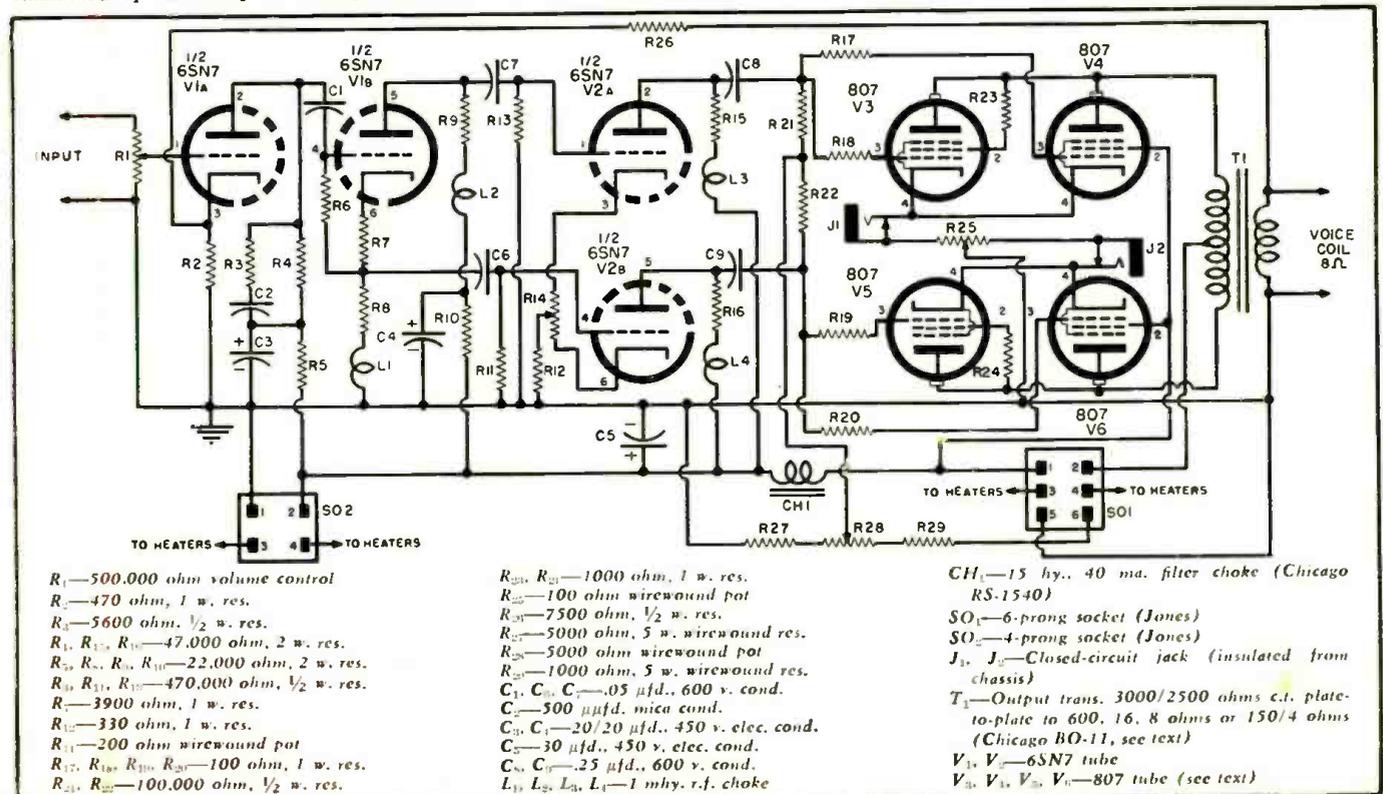

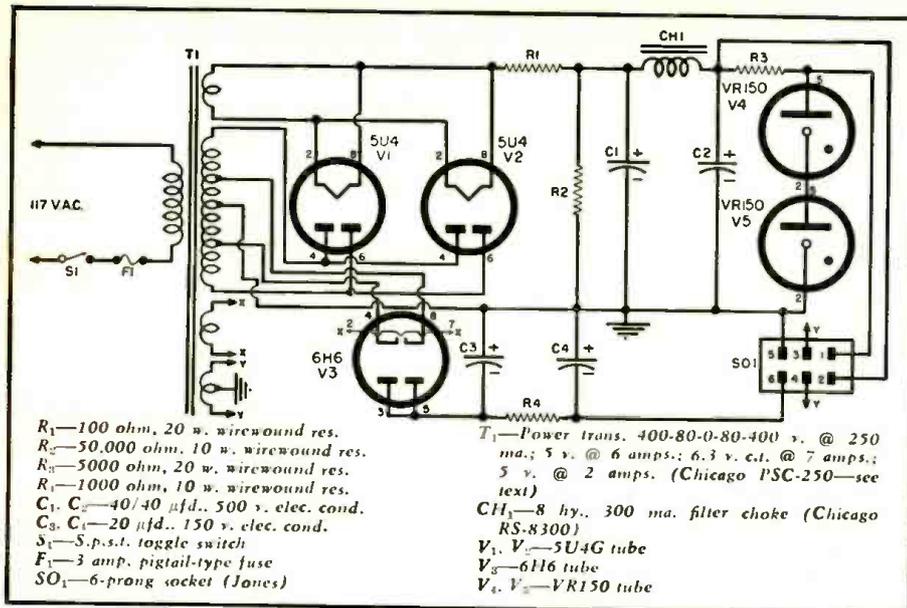


Fig. 3. Complete circuit diagram of the power supply. A separate chassis is used.

bridges and the officials of such companies are usually very cooperative.


Another innovation in this amplifier is the use of r.f. chokes in series with the load resistors. The purpose of these chokes is to offset the effect of tube and wiring capacitances which tend to reduce high frequency response. They are used in much the same way as the peaking coils in video amplifier circuits. One might think that the addition of such chokes would upset the stability of the amplifier, but such is not the case. Tests without the peaking chokes in the circuits compared with tests made after adding them indicated that they did not in any way reduce the stability of the amplifier.

The four output tubes are connected with a 100-ohm resistor in series with

each grid lead. This reduces the chance of oscillation in the output stage without reducing the gain of the amplifier. The plates could be isolated in the same manner, using 20-ohm resistors, but this was found to be unnecessary. Jacks are inserted in the cathode leads on each side of the circuit so that balancing of the output stage can be facilitated. It is important that these jacks be insulated from the chassis.

In any high-quality amplifier, if any one part is more important than any other, that part would be the output transformer. This is particularly true in the case of this amplifier because of the wide range of frequencies to be handled, and because of the high power output requirements. The extended class A type of amplifier using 807

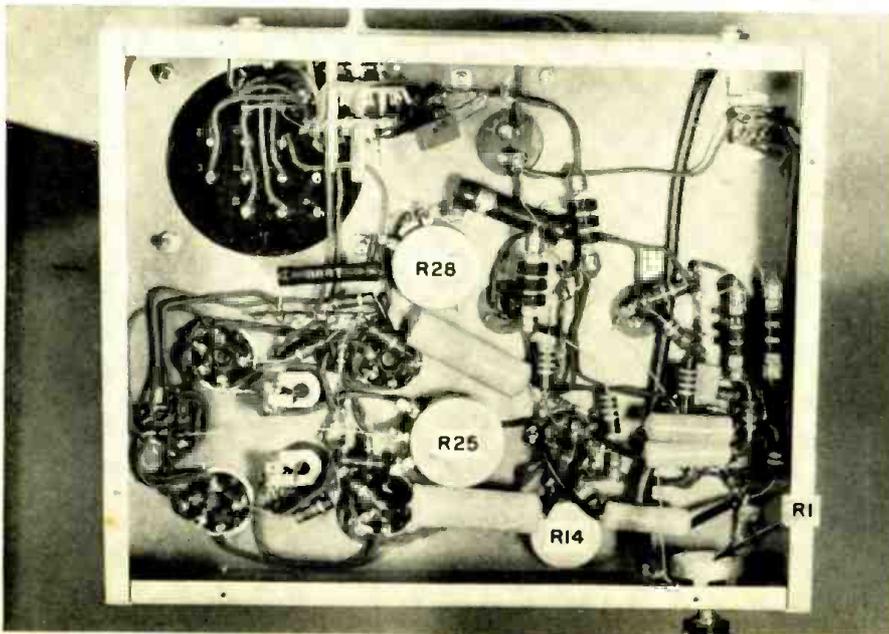Under chassis view of amplifier showing location of the various pots. The output impedance switch control, shown in Fig. 4, has been incorporated. Phone jack shown alongside selector switch and mounted on rear flange of chassis, is used to accommodate speaker phone plug. Jack on right rear flange of chassis is for input to amplifier.



tubes will require an output transformer with a plate-to-plate load resistance of 2500 ohms, and one that is capable of handling in the neighborhood of 50 watts of power. The Chicago BO-11 transformer was chosen because it met these requirements so suitably and because of its ability to handle a wide range of frequencies. This unit gives a range of output impedances of from 4 to 600 ohms which can add to the versatility of any amplifier.

A heavy-duty power supply, Fig. 3, is needed. In addition to the filament, plate, and screen voltages, it is necessary to provide a voltage supply for the fixed bias used in the output stage. This bias supply could be provided by a separate transformer, but the method shown in the schematic works very nicely, is simple in nature, and requires no additional transformer. The power transformer (Chicago PSC-250) supplies the bias through a special arrangement of taps on the high-voltage winding. Each of these taps is connected to a cathode of a 6H6 tube, and the plates of the tube are tied together, supplying a voltage which is negative in polarity with respect to the center tap of the transformer winding. This voltage is filtered and is fed to the grids of the output tubes through the voltage dividing potentiometer R_3 . This arrangement provides a very simple and convenient means of adjusting the output tube bias. The PSC-250 transformer has three heater windings, one which delivers 6.3 volts and two which deliver 5 volts each. One of the 5-volt windings is used for the heater of the 6H6, and although this tube's heater rating is 6.3 volts this slight difference in voltage does not impair the operation of the tube. Two 5U4G tubes are used as high-voltage rectifiers. The resistors R_1 and R_2 in the power supply are instrumental in protecting the condensers C_1 and C_2 from voltage surges during the warm-up time of the amplifier. The filter choke is a Chicago RS-8300 which will handle up to 300 ma., and which has a d.c. resistance of only 70 ohms. Excellent filtering is obtained with low voltage drop. This power supply very adequately meets the requirements of the amplifier. After several hours of operation the power transformer becomes only slightly warm, and what little heat is present seems to be acquired as much from the heat generated by the rectifier tubes as from within the transformer itself.

If low distortion is to be maintained during peak power, it is necessary that the voltage supplied to the screens of the output tubes be kept as stable as possible. Quite good stability could be obtained by means of a heavy bleeder circuit, but it was felt that somewhat better results could be obtained if voltage regulator tubes were used. Two VR150 tubes are used in series, and are fed from a 5000 ohm, 20 watt resistor, R_3 . This regulated

(Continued on page 146)

ELECTRONIC

COUNTER

By
ERWIN LEVY

A simple electronic unit which can be used for innumerable counting tasks. It may be elaborated at will by the builder.



ELECTRONIC counters are used in many new types of instruments and equipment that have been developed in the past few years. They are utilized in computers, radiation counters, precision timers, and automatic control systems for counting and sorting. Some of these devices, especially computers, require hundreds or even thousands of tubes. In order to simplify fabrication and maintenance, a unitized system of construction is often used. Small plug-in chassis which contain a number of tubes and their associated components are built as separate units. Identical prototypes can then be used to assemble the final machine. In addition, these units are often interchangeable in different pieces of equipment.

A basic counter unit built for experimental purposes is shown in Fig. 1. The tally of this four-stage prototype, which can count up to sixteen, is shown visually on the front panel by means of neon lamps. Only four indicators are needed since a binary rather than a decimal counting system is used. This will be explained separately in a later section of the article.

Most counters are derived from the basic Eccles-Jordan trigger circuit shown in Fig. 2. The circuit, which uses a dual triode, has two stable conditions of operation. In one, V_{1A} is conducting and V_{1B} is cut-off; in the other, V_{1A} is cut-off and V_{1B} is conducting. The circuit will maintain either of the two states until a signal is applied to reverse the action. Because of this unique characteristic it is frequently referred to as a "flip-flop."

Each stage functions basically as an amplifier. However, the plate of V_{1A} is directly coupled to the grid of V_{1B} by resistor R_3 , and the plate of V_{1B} is directly coupled to the grid of V_{1A}


by resistor R_4 . Actually, the circuit components form two voltage divider networks. This can be seen more clearly by reference to Fig. 3A where the circuit has been redrawn to accentuate this fact. Here, V_{1A} is cut-off and V_{1B} is conducting; this will be referred to as condition 1. The two grids are tied together through blocking condensers. If a negative pulse is applied to the input it will have no effect on V_{1A} since this tube is already cut-off. However, it will overcome the positive bias on the grid of V_{1B} and force this tube to stop conducting. As a result, the status of the two tubes will be reversed. When V_{1B} is biased to cut-off by the negative input pulse, the plate current will decrease and the plate voltage will increase. This positive voltage change impressed on the grid of V_{1A} will immediately cause the tube (V_{1A}) to conduct heavily. This in turn means a low plate voltage on V_{1A} . This drop in voltage is essentially negative when impressed on the grid of V_{1B} . This feedback pulse will augment the input signal to insure that V_{1B} will remain cut-off. The

voltages which exist in the circuit for this condition of operation are shown in Fig. 3B. With V_{1A} conducting and V_{1B} cut-off condition 2 exists. The circuit will remain in this state until another signal pulse is applied to the circuit. The negative pulse will always cause the conducting tube to cut off and thereby reverse the operating states. The change is produced instantaneously. A separate pulse is required for each change, two pulses are necessary to produce a complete cycle.

Visual indication is provided by a neon bulb connected from the plate of V_{1B} to ground through a series-limiting resistor, R_7 . A neon bulb requires approximately 60 volts for firing, that is, to be illuminated. In condition 1 (see Fig. 3A) when V_{1B} is conducting the plate voltage is lower than the critical value and the lamp is extinguished. In condition 2 (see Fig. 3B) V_{1B} is cut off and the plate voltage is high enough to light the lamp.

The explanation of the basic circuit serves to point out the important features of operation. However, the circuit shown has several limitations which tend to limit the stability of the system. Since the two grids are coupled together at the input, a "pulse-dodging" problem is encountered. When the negative input trigger is applied, it will tend to override the positive signal fed back to the other tube. As a result, the circuit is critical with respect to pulse amplitude and shape. In order to overcome this, several variations have been devised. The circuit used in the model constructed is shown in Fig. 4. A resistor common to each of the plate load resistors is added in the "B-plus" line. The signal is fed in at the junction of the plate load resistors and the series resistor, R_4 . This overcomes the mutual coupling of the grids and improves

Fig. 2. Basic Eccles-Jordan trigger circuit.

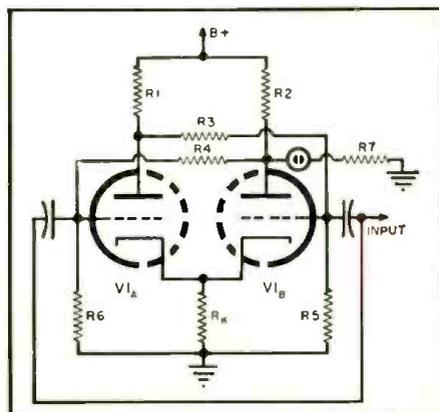

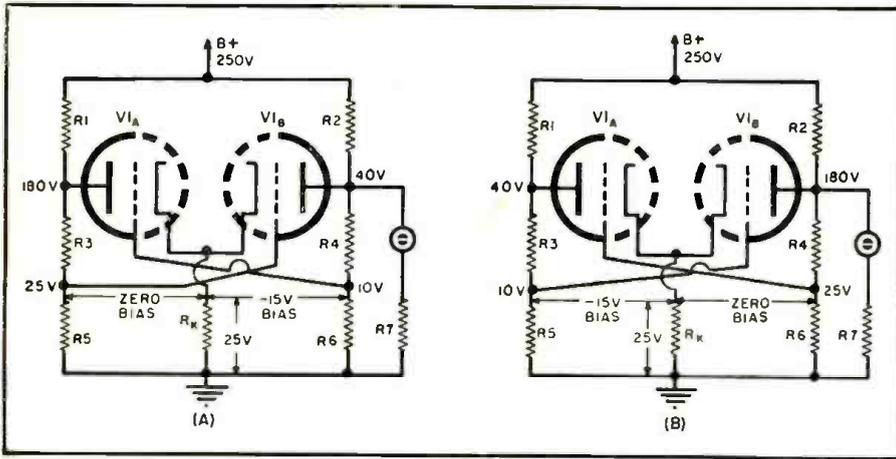


Fig. 3. (A) Trigger circuit in Condition 1. V_{1A} cut-off and V_{1B} conducting, neon lamp extinguished. (B) Circuit in Condition 2 with V_{1A} conducting, V_{1B} cut-off, lamp lighted.

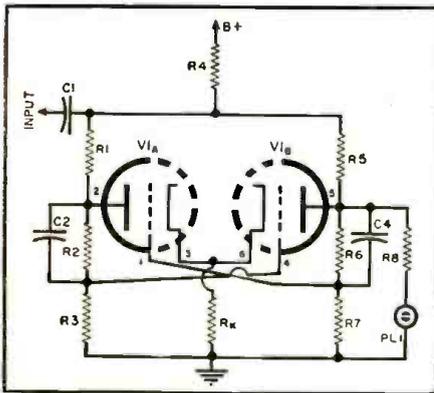


Fig. 4. Modified counter stage. The final unit is made up of four of these stages. They are identical with the exception of change in cathode circuit (Fig. 5). Refer to Fig. 5 for parts identification, values.

the stability. In addition, a small condenser is connected in parallel with each of the plate-to-grid coupling resistors in a single stage. This helps to sharpen the abrupt action of the changeover during operation. The complete circuit, which uses four identical counter stages is shown in

Fig. 5. (A more detailed description of trigger and counter circuits is given in the references listed at the end of this article).


The chassis is constructed from four pieces of aluminum. The upper and lower plates, made of heavy gauge metal, are $8\frac{1}{2}'' \times 2\frac{1}{2}''$; the front panel is $6'' \times 2\frac{1}{2}''$; the rear panel is $3\frac{1}{4}'' \times 2\frac{1}{2}''$. The individual parts are screwed together for final assembly. The sockets are spaced two inches on centers. From the photographs it can be seen that all the parts for an individual stage are mounted on a turret socket. The circuit diagram for each of the identical counter stages is shown in Fig. 4. Since a comparatively large number of components is used, the layout is simplified by using this method of construction. Wire the four individual stages on their sockets before mounting. The values of all similar resistors should be checked to insure that they are closely matched. The values should be within 10%; a 5% tolerance is even more desirable. (When the unit shown was first constructed this fact was overlooked and as a result it was necessary to replace

numerous parts to secure proper results). A check of all parts before mounting will eliminate many headaches when the unit is finished.

After the individual turrets are wired and checked they should be mounted; the connections between units can then be made. The next step is to mount the neon lamps. These are type NE-2 and are secured individually in $\frac{1}{4}''$ rubber grommets. The $\frac{1}{4}''$ holes for the grommets are $1''$ apart. The cathode resistor and bypass condenser are placed at the rear of the bottom plate. After all the parts are mounted on the individual plates the complete unit can be assembled. The external connections are made to an octal socket on the rear plate. Because of the type of layout, the circuit is relatively easy to assemble. The directions have been given in detail to simplify the process.

One feature not noted previously is that a counter must have provision for a "zero-set." That is, each time the circuit is put in operation the count must start from zero. In the circuit shown, this is accomplished in the cathode circuit. By referring to the circuit in Fig. 5 it can be seen that there are essentially two separate cathode circuits. The cathodes (pins 3 and marked X) are connected together, while the cathodes (pin 6, marked Y) are also connected together. These are brought to opposite sides of resistor R_{33} (47,000 ohms) marked respectively X and Y. This resistor is paralleled by a normally-closed "Microswitch" which shorts out the resistor during normal operation. The main cathode bias is provided by resistor R_k (5000 ohms) and its associated bypass condenser C_k (100 μ fd.). For reset, the switch is pushed momentarily. Resistor R_{33} is thereby inserted in series with one of the cathode circuits. The unequal bias on the tubes will force the left-hand triode of each tube to cut off (and thereby extinguish all neon lamps).

Fig. 5. Complete circuit diagram and parts list for the four-stage electronic counter. See Fig. 4 for detailed drawing of single stage.

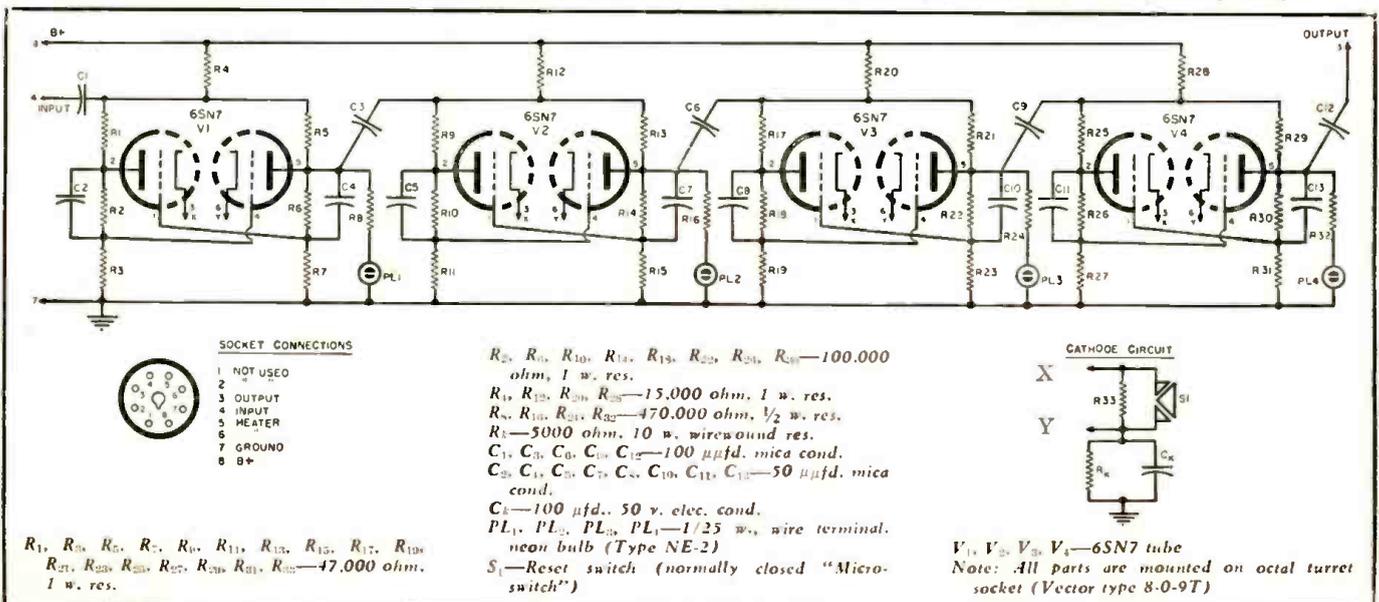

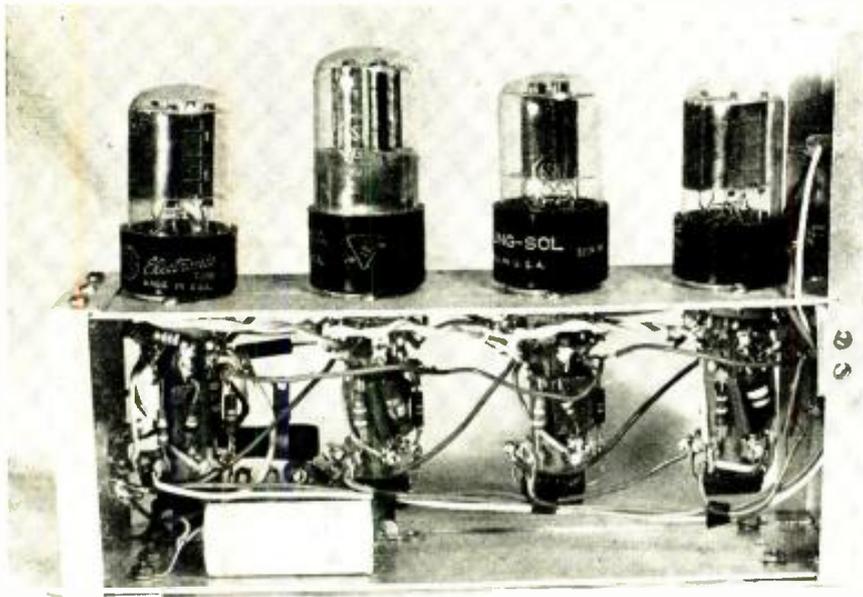


Fig. 6. Side view of the electronic counter. Note the turret socket construction.

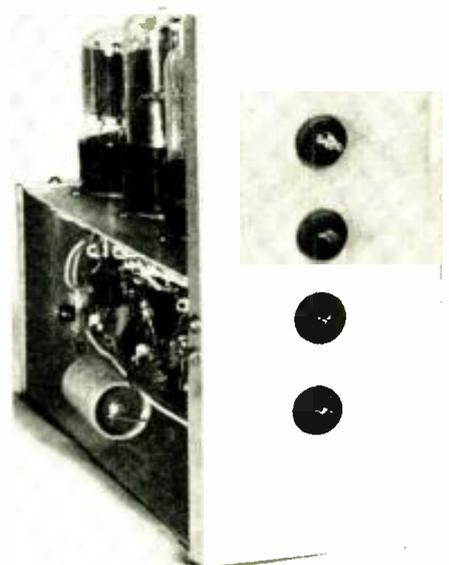


Fig. 7. Front view showing neon lights.

The reset switch does not show in the photographs. It is mounted at the rear of the counter chassis. However, it can be placed on the front panel below the neon indicator lamps. This is a more accessible position for normal use.

An input stage is usually required to provide the coupling between the original signal source and the counter itself. The circuit used depends upon the type of pickup device. In this case, a modified *Eccles-Jordan* trigger is used as a pulse shaper. The circuit is shown in Fig. 8. It is similar to the type originally illustrated in Fig. 2. However, in this case an unsymmetrical system is used. The grid leak resistor of V_{1A} (R_5) is much larger than the grid leak resistor of V_{1B} (R_3). With this arrangement V_{1A} will always be cut off. The pickup switch which activates the counter is a normally-open "Microswitch" connected across the grid leak resistor of V_{1A} . When the switch is actuated, the resistor is shorted; this reverses the operating states of the tubes. As soon as the switch is opened the circuit returns to its original state. A momentary push is sufficient to produce a pulse. The circuit operates as a single-shot pulser; only one input pulse is required for a complete cycle. The signal from the grid of V_{1A} provides a 150 volt negative pulse. The output from the plate of V_{1B} provides a 30 volt negative pulse. For the system described, the signal was coupled from the grid. (It is possible to operate a counter from any type of pickup device, the critical part is the input pulse-shaper).

The components for the pulse-shaper are mounted on a turret socket. The pulse-shaper and pickup switch are mounted in a small 4" x 4" x 2" utility box. The switch is placed on one of the side panels. Fig. 9 is a photograph of this unit. A well-filtered power supply which can supply about 250 to

300 volts at 50 ma. is required. If available, a regulated supply is even better.

After the circuit has been completely assembled and all wiring closely checked, the unit can be placed in operation. When the power supply is first turned on all four neon bulbs will probably be lit. As the tubes warm up some of them will flicker and then go out. After sufficient warm-up time (about one minute) push the reset switch. This will extinguish all lamps and represent a zero count.

Another word of caution. The four tubes should be closely matched. They do not all have to be new, but should have similar emission characteristics. A quick check on a tube checker is a good idea.

As mentioned in the beginning of the article, the binary system is utilized in the counter. Each circuit has two conditions of operation. These are shown by a neon lamp which is either on or off. This is indicated mathematically as 2^N , N stands for the

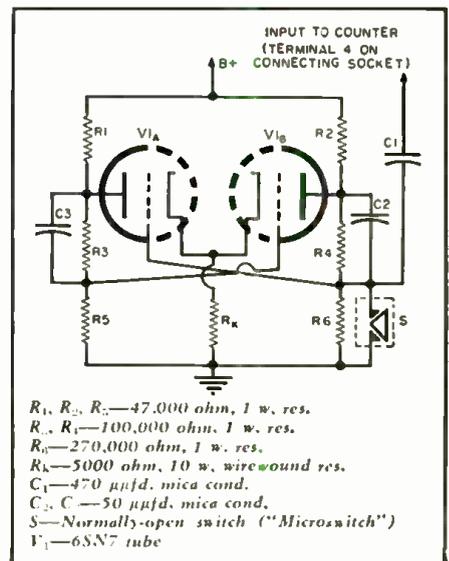


Fig. 8. Circuit of the pulse shaper which is used in conjunction with the counter.

number of stages, which in this case
 (Continued on page 114)

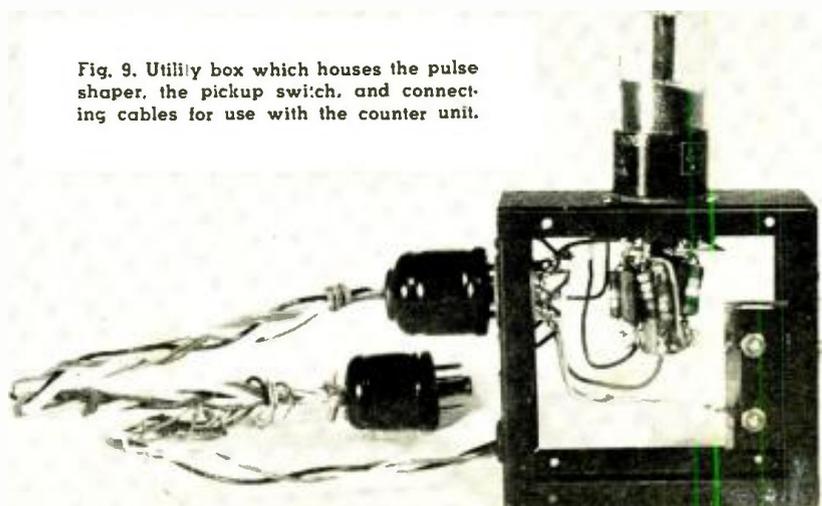


Fig. 9. Utility box which houses the pulse shaper, the pickup switch, and connecting cables for use with the counter unit.

ASSEMBLE YOUR OWN HEARING AID



By
E. G. LOUIS

Fig. 1. Over-all view of hearing aid. An even more compact assembly is possible.

Using a printed circuit and subminiature parts, this tiny instrument can be assembled in from four to six hours.

ALTHOUGH commercially-built hearing aids generally cost from \$75 to well over \$150, the basic electronic parts needed for the construction of a small hearing aid may cost less than \$35 at regular wholesale prices! Neither "special" components nor unusual skill is required to assemble such a unit. All the parts needed are commercially available at most wholesale radio supply houses, and the average technician should have little or no trouble completing the assembly of such a compact hearing aid, similar to the one shown in Fig. 1, in from four to six hours.


Even though "home-built," the hearing aid shown in Fig. 1 is quite small, as can be seen by comparing it to the package of king-size cigarettes. However, it can be assembled in a still smaller size if desired! Referring to the interior view of Fig. 4, it is readily apparent that considerable "waste space" is present inside the plastic case. If a smaller case had been available at the time of construction, the unit could have been assembled even more compactly, without appreciably more skill required for construction, or at any greater cost.

Probably the only major differences between the hearing aid shown and commercially-manufactured units are: (a) the use of a standard midget ear-

set in place of a "custom-molded" earpiece; (b) the use of a standard crystal microphone cartridge rather than a difficult-to-obtain subminiature microphone; and (c) the use of a plain plastic case.

However, the important characteristics of sensitivity (amplifier gain), power output, frequency response, and long battery life compare favorably with most commercially available units.

Fig. 2. Alternate circuits for hearing aid shown in Fig. 3. (A) Choke output for crystal earset. (B) Resistor output for crystal earset. (C) Transformer output circuit, required for low impedance earset.

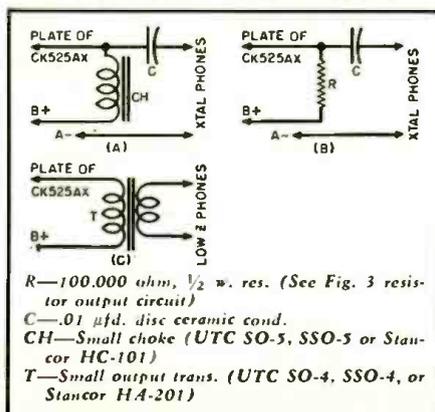

Circuit Description

As can be seen by reference to the schematic diagram given in Fig. 3, the complete hearing aid consists of a microphone, a three-stage audio amplifier, and an earphone output, with power supplied by small batteries. The amplifier itself is a complete printed circuit unit, with the only connections required by the builder shown outside the dotted line rectangle, that is, the builder need only wire the leads to R_1 and the "mike," to the volume control, to the tone control and headset, and to the batteries and "on-off" switch.

In operation, sound picked up by the microphone is converted into electrical signals and applied across grid resistor R_1 to the grid of the first voltage amplifier tube (CK512A). The amplified signal appearing in the plate circuit of this stage is applied through a .001 μ fd. d.c. blocking condenser to the volume control (R_2) and thence to the grid of the second voltage amplifier stage.

Additional gain is supplied by the second stage, with the audio signal appearing across the 1 megohm plate load resistor applied through another .001 μ fd. coupling condenser to the grid of the power output stage (CK525A). From here the signal is applied to the midget earset.

The tone control is a conventional high frequency "losser" type circuit and consists of C_1 and R_3 . As the value of R_3 is reduced, C_1 becomes more and more effective in bypassing the higher frequency components of the amplified signal.

A few characteristics of the printed circuit amplifier are worth noting. First, the two voltage amplifier tubes have their filaments connected in series, with the voltage drop acting to provide bias for the second stage. Bias for the output stage is obtained from the voltage drop across a 1500 ohm resistor between "B-" and circuit "ground." Stage decoupling is provided for the first voltage amplifier by a 700,000 ohm resistor and a .04 μ fd. bypass condenser in the "B" supply circuit.

Construction Hints

The entire assembly, including batteries, is mounted in a small plastic

case. Although the layout used by the author is easily observed in Fig. 4, this layout need not be followed exactly, if care is taken to keep the "input" and "output" leads of the amplifier well separated. In fact, "layout" becomes primarily a matter of conveniently fitting the necessary components into the case used.

Batteries are mounted in the model shown by cementing small metal strips along one side of the case for the "B—" and "A+" connections, and using an "expanded" *Fahnestock* clip and a small "L" bracket for the "B+" and "A—" connections, respectively. Small machine screws are used for mounting the clip and bracket in place.

Volume and tone controls are mounted using the small machine screws and nuts furnished with them. A mounting template is also furnished by the manufacturer with each of these two components, and it is only necessary to drill the indicated holes.

The "output" jack is a *Walsco* type 791 jack which was cut to about half its normal length before assembly. It is cemented in place using *Duco* cement or its equivalent. The microphone and printed circuit amplifier are similarly cemented to the plastic case.

It was necessary to replace the phone plug furnished with the *Telex* midjet earset with a *Walsco* type 790 plug to match the midjet output jack.

The microphone used by the author was purchased as a surplus item for less than \$1.50 from the *Leotone Radio Corporation*, 67 Dey Street, New York 7, N. Y. However, if this item is not available, any standard high impedance "mike" cartridge may be used instead—the *Shure* type R7 cartridge is excellent for use in this application.

Wiring Hints: When wiring sub-miniature components, certain precautions should be observed to avoid damaging parts. Use small diameter hook-up wire, preferably smaller than #22. Use a small soldering pencil and keep it well tinned. Complete the soldering as quickly as possible to avoid overheating.

Most connections are made as simple "lap" joints without attempting to make a good mechanical connection first (as is general practice in conventional wiring).

Once the wiring is completed, and before the unit is tried, a careful check of the wiring and of all connections should be made. Make sure that there are no errors in wiring, that no parts are accidentally shorted, and that excessive amounts of solder have not been used. If too much solder has been used on any terminals, carefully remove the excess using a clean soldering iron.

Circuit Modifications

A number of circuit modifications are possible to suit the individual requirements of the builder.

First, the tone control circuit may be left out completely if desired. Or,

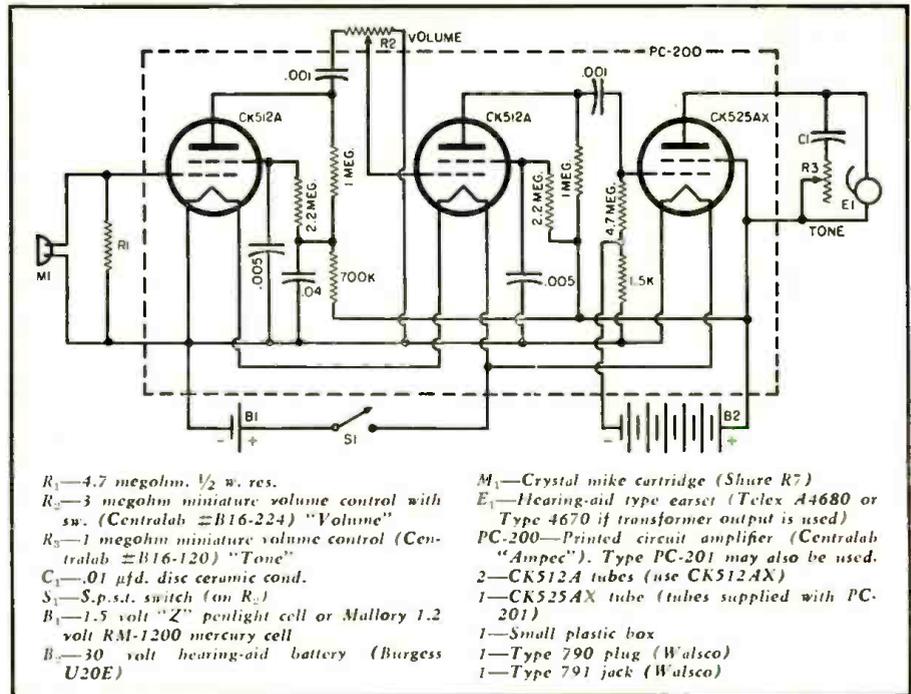


Fig. 3. Complete schematic. Circuit within dotted lines is a printed circuit amplifier.

if more effective control is preferred, *C*₁ may be replaced by a larger condenser—as high as .05 μ fd. may be used here.

Several output circuits which may be used instead of the circuit shown in the schematic diagram are illustrated in Fig. 2. Any of these circuits will give satisfactory results with the type of earphones suggested.

For a crystal earset, either the circuit shown in Fig. 2A or 2B is satisfactory. Somewhat greater gain is obtained with the choke output (Fig. 2A), but better frequency response is obtained with a resistor output (Fig. 2B).

If a low impedance earset is to be used, transformer output is mandatory, as illustrated in Fig. 2C.


Should the builder use a high im-

pedance output circuit, he may find it necessary to shield the amplifier to prevent feedback and oscillation. This step is best accomplished by using a small metal case rather than a plastic case when carrying out the assembly, taking care to mount any exposed parts on plastic to prevent shorts. The case is connected to "A—". Another alternative is to use aluminum foil or tinfoil to form an interior shield, cementing the foil to the case.

Either higher or lower "B" voltages may be used, with satisfactory results being obtained from as little as 15 volts to as high as 67½ volts. A 67½ volt supply should be used only with a resistor output. The lower "B" voltages will give better results when used with transformer output.

(Continued on page 161)

Fig. 4. Hearing aid layout. Parts placement is not critical and may be changed at will.

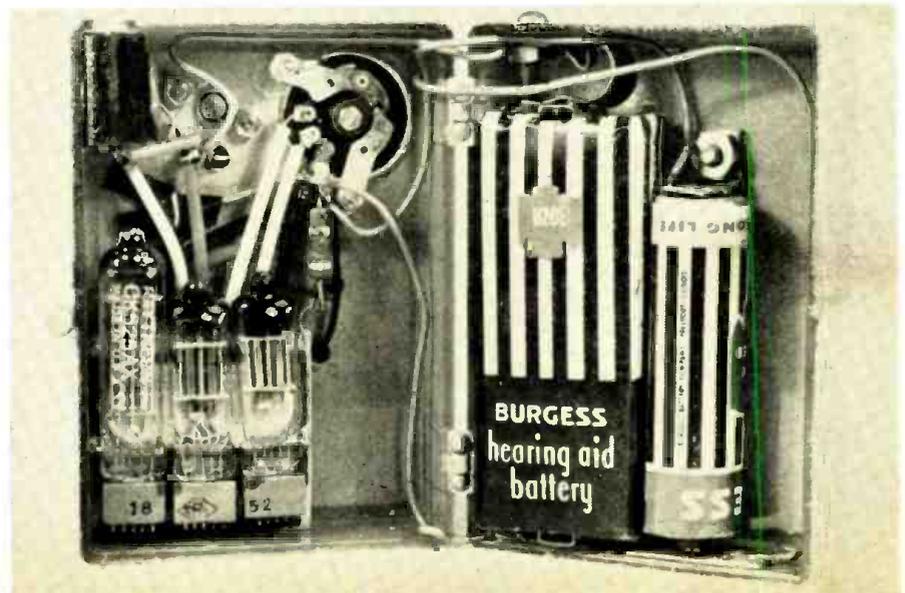

KEYED A.G.C. SYSTEMS

By MILTON S. KIVER

Pres., Television Communications Institute

Typical keyed a.g.c. circuits with explanation of how they operate to increase TV receiver noise immunity.

KEYED a.g.c. systems for television receivers have grown in popularity ever since their introduction several years ago. While many simpler a.g.c. systems exist, they do not possess the ability of the keyed system to react quickly to rapid fluctuations in signal strength nor can they equal the stability of the keyed system in the presence of noise pulses. Thus, while cost is an important factor in receiver design, it is partially sacrificed here in the interests of improved receiver operation.

In dealing with keyed a.g.c. systems, the service technician will find that although all are essentially similar, sufficient variations exist to require a careful analysis of each circuit before any service work is attempted. In this article the more popular keyed a.g.c. systems will be analyzed and discussed.

A simplified illustration of the basic keyed a.g.c. system is shown in Fig. 1. A 6AU6 pentode is so connected that a portion of the detected video signal is applied to its control grid. The signal is chosen with the sync pulses extending upward, *i.e.*, in the positive direction. The plate of the 6AU6 is connected to a winding on the horizontal output transformer and receives from this transformer a positive pulse of voltage at the end of each horizontal line.

Now, the 6AU6 is biased so that it will not conduct unless the grid and plate are simultaneously driven positive. If just one of these voltages is present, without the other, the 6AU6 does not ordinarily conduct.

The pulses applied to the grid are the incoming horizontal sync pulses. When these pulses arrive, the electron beam traveling across the face of the picture tube is about to start its retrace. At the moment this occurs, a large pulse of voltage is developed in the horizontal output transformer and a portion of this pulse is fed to the plate of the 6AU6. With both positive pulses of voltage present, the 6AU6 a.g.c. tube is keyed into conduction and the a.g.c. network bias is established.

Note the foregoing sequence of events carefully because they contain the key to the operation of this system. Positive pulses must be present at both control grid and plate of the 6AU6 in order for the tube to pass current and establish the proper a.g.c. bias. The plate receives no positive voltage other than that furnished by the horizontal output transformer.

Since the 6AU6 conducts only when the sync pulses are active at its control grid, and is inactive throughout the remainder of the video signal, it is evident that this tube and, consequently, the a.g.c. network is responsive to undesirable noise pulses for only a very short time. Actually, the sync pulses occupy but 5% of the composite video signal and therefore only 5% of the total noise can be effective.

Typical Keyed A.G.C. Systems

Typical of the simpler keyed a.g.c. systems in use is the one shown in Fig. 2. The video signal, with sync pulses positive, is tapped off the load resistor, R_1 , of the video amplifier and fed directly to the control grid of the 6AU6 keyed a.g.c. tube. The 39,000-ohm series resistor, R_2 , in this connecting line serves to isolate the input capacitance of the 6AU6 from R_1 . The video signal is in its d.c. form (*i.e.*, still retains both a.c. and d.c. components) because of the d.c. path from the output of the video second detector to the grid of the 6CB6 video amplifier tube.

Since the control grid of the 6AU6 is directly connected into the plate

circuit of the video amplifier stage, it possesses a positive potential. To offset this, both the cathode and screen grid of the keyer tube are given even greater positive voltages. The d.c. voltage between grid and cathode here is -15 volts and this is sufficient to prevent tube conduction, even when the plate receives a positive pulse. However, the peak-to-peak voltage of the video signal from the 6CB6 video amplifier is on the order of 25 volts and thus the bias is overcome when the sync pulses are active.

The required pulsing voltage for the keyer plate is obtained from a tap on the secondary of the horizontal output transformer. These pips have an over-all voltage value of 450 volts, which is more than sufficient to drive the tube.


When current does flow through the tube and plate circuit, a negative voltage is developed across R_3 and R_4 . This voltage is divided equally between the resistors, and that portion which R_4 receives is used as the a.g.c. bias. The r.f. amplifier, and the first and second video i.f. amplifiers are the tubes controlled. R_1 and C_1 form the principal filtering components, although other resistors and condensers aid in this purpose, too.

Zenith television sets (in 1951) employed a keyed a.g.c. system which differed slightly from the foregoing circuit. The Zenith circuit is shown in Fig. 3. The video second detector is a germanium crystal, a 1N64. The detected video signal is developed across R_{61} (4700 ohms) and applied via L_{55} to the grid of V_{10} . Although the manufacturer labels this tube as a noise limiter and inverter, it is essentially an amplifier, with the signal which is developed at the plate being fed to a second video amplifier.

The cathode resistor for V_{81} (R_{31} , 820 ohms) is also the cathode resistor for V_{121} , which is the keyed a.g.c. tube. Hence, the full video signal is applied to the cathode of the 6SN7 a.g.c. tube. The polarity of the video signal here is such that the sync pulses are negative.

The plate of V_{121} is connected to the cathode of the horizontal sweep oscillator. The voltage waveform developed here is a modified sine wave, with the positive peak somewhat more pronounced than the negative peak. When this oscillator is properly synced to the incoming signal, the

Fig. 1. Simplified block diagram of the basic components of keyed a.g.c. systems.

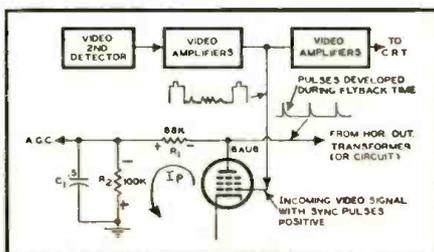

positive peak of the sine wave occurs at the same time that the sync pulses appear at the cathode of V_{12a} . Since negative pulses at the cathode are equivalent to positive pulses of voltage at the grid of V_{12a} , the tube is thus triggered into conduction and plate current flows. Condenser C_{29} charges up to a negative value determined by the strength of the current flowing. When the signal is strong, the negative voltage developed is high; when the signal is weak, less negative voltage appears. This a.g.c. voltage is then fed to the 1st, 2nd, and 3rd i.f. amplifiers and to the r.f. amplifier and converter as a control voltage.

An a.g.c. delay voltage is applied to the grid of V_{12a} . Its purpose is to permit adjustment of the amount of negative a.g.c. voltage which V_{12a} develops in order that this voltage may be set for the particular signal conditions prevailing at the receiver location.

The procedure for correctly setting this control is as follows: Connect a calibrated oscilloscope through a 10,000-ohm isolating resistor to the grid of V_{12a} . This will show you the video signal at this point. Select the strongest TV signal available and observe it on the screen. Adjust the a.g.c. delay control for 2.5 volts peak output.

A.G.C. with Diode Clampers

Since it is frequently desirable for the reception of weak signals that the negative bias on the r.f. amplifier be as low as possible, a number of manufacturers have been incorporating an additional diode tube (or a triode connected as a diode) into the a.g.c. system. The purpose of this tube is to keep the bias on the r.f. amplifier close to zero until the incoming signal reaches a moderate level. In this way the sensitivity of the set is high for weak signals, and properly reduced when the signal level is high. Diode clampers may be used with any a.g.c. system, keyed or otherwise.

A keyed a.g.c. circuit containing a diode clamber tube (as these tubes are called) is shown in Fig. 4. V_1 , the keyer tube, develops a negative bias voltage across R_1 , R_2 , and R_3 by means of the pulses of current that flow through these three resistors. The control bias for the i.f. stages is that developed across R_2 and R_3 . The r.f. amplifier receives less negative voltage because it obtains only the voltage developed across R_3 .

Consider, now, the circuit shown to the right of point "A." Here we find a fourth resistor (R_4) and a diode tube. Both of the new components are tied into the r.f. line and the manner in which they affect the voltage on this line depends upon the negative voltage which the a.g.c. tube develops. Let us, as a start, assume that in the absence of V_2 and R_4 , point "A" is negative by 1 volt. If, now, we add R_4 to the circuit, then R_1 and R_2 form a voltage divider network

across the 325-volt "B+" line and part of this positive voltage will appear across R_3 . To be exact, about 3 volts positive, due to the high value of R_1 and the relatively low value of R_2 . Thus, we have +3 volts across R_3 from the +325 volt line, and -1 volt from the a.g.c. tube. The net result is to make point "A" positive by 2 volts.


Now, all this did not take V_2 into account. Since the diode is connected from point "A" to ground, its plate will be made 2 volts positive with respect to its cathode, and conduction through the tube will occur. A diode conducting has a fairly low internal resistance so that, for all practical purposes, point "A" is brought to ground potential and the full 325 volts is dropped across the 3.3 megohm resistor.

Note that the key to this particular behavior is based upon two factors: First, the use of a high-value resistor between the "B+" point and the tube; and second, the fact that the internal resistance of V_2 is low when the tube conducts. This sets up a voltage divider network wherein practically all of the positive voltage is dropped across R_4 , leaving very little at point "A."

The r.f. amplifier tube is tied into point "A" and so, when the negative voltage that the a.g.c. tube produces is low, the r.f. tube receives essentially a zero bias. The i.f. tubes, under the same conditions, receive a negative voltage. This is because they are isolated from point "A" by R_2 (a 39,000-ohm resistor) and also because the line going to the i.f. tubes ties in at point "B," which is closer to the keyed a.g.c. tube and hence subject to a greater negative voltage.

When the incoming signal increases in strength, the negative voltage produced by V_1 rises, too. This means that the i.f. tubes are given a higher negative bias. At point "A," the diode will continue to conduct as long as the positive voltage (provided by the 325-volt line) exceeds the negative

Fig. 4. Keyed a.g.c. circuit using a diode for better r.f. gain control.

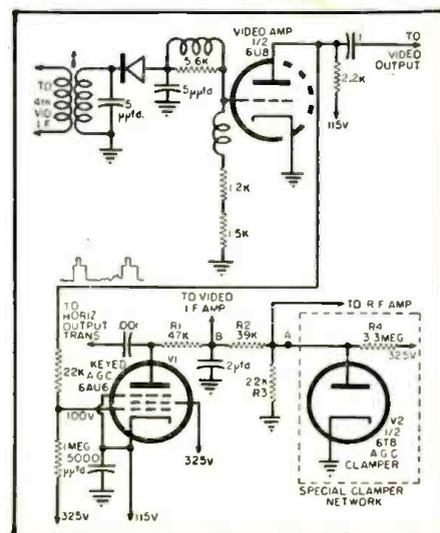

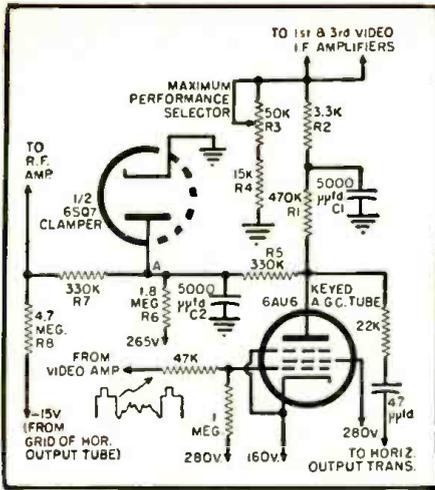


Fig. 5. Schematic of keyed a.g.c. circuit used by Hoffman in its model 21B116.

keyer tube, a negative voltage is developed across these resistors with the plate end of R_1 possessing the most negative potential. The video i.f. stages receive their bias from the voltage developed across R_1 and R_2 . R_3 is made variable in order that the i.f. bias may be adjusted for the particular location of the receiver. Reducing R_3 , by rotating its center arm, will lower the negative voltage applied to the i.f. stages and thereby increase their gain. This might be desirable in a weak signal area. When the signal level is high, more of R_3 is brought into the circuit, thereby raising the negative bias of the controlled video i.f. stages.

Leading off from the plate of the a.g.c. tube in a separate circuit is the bias line for the r.f. amplifier. R_5 and C_2 serve as a filter and isolating network, filtering the horizontal sync pulses present in the plate circuit and isolating the clamper tube from the a.g.c. tube and its i.f. line. The presence of R_6 and the diode maintain

point "A" at zero potential whenever the incoming signal is weak; when the signal becomes stronger, the potential at point "A" goes negative and the diode ceases to conduct.

Note, however, that point "A" does not connect directly to the r.f. stage, as it did in the previous circuit. Instead, between "A" and the r.f. amplifier there is another network consisting of R_7 (330,000 ohms) and R_8 (4.7 megohms). One end of R_8 is connected to the grid of the horizontal output tube where it receives a potential of -15 volts. If, now, point "A" is at zero volts, then the -15 volts will divide itself between R_7 and R_8 , with R_8 getting all but about -1.3 volts which goes to the r.f. amplifier tube grid as a biasing voltage.

Thus, as matters stand, the grid of the r.f. amplifier in this circuit can never become more positive than -1.3 volts unless the horizontal deflection system somehow becomes defective. With strong signals, point "A" is driven negative and this, in turn, raises the negative bias on the r.f. amplifier to above -1.3 volts.

Double-Delayed Keyed A.G.C.

A circuit which is known as a double-delayed keyed a.g.c. system is employed by Zenith in its 1953 line of television receivers. The operation of the keyer tube is somewhat reminiscent of the earlier Zenith circuit shown in Fig. 3. The rest of the circuit, however, is markedly different.

A diagram of the double-delayed a.g.c. system is shown in Fig. 6. The keyer tube is a triode ($1/2$ of a 12AX7). It receives the video signal at its grid with the sync pulses extending in the positive direction. The plate, in its turn, is connected to the grid of the discharge tube located in the horizontal deflection system. From this point, positive pulses are received by the plate of the keyer tube during the

horizontal retrace interval. Thus, the positive pulses at the plate and grid of the 12AX7 tube act in concert to produce a voltage in the output circuit of the tube that can vary from about $+8$ volts under weak signal conditions to -5 volts under moderate-to-strong signal conditions. Positive values of voltage are new to keyed a.g.c. systems and are brought about by (a) using a triode tube for the keyer tube instead of the more common pentode and (b) by carefully choosing the operating potentials for the various tube elements.

Now let us consider the over-all circuit operation under weak and strong signal conditions. When the incoming signal is weak, the output of the a.g.c. at point "A" is approximately 8 volts positive. This positive voltage is applied to the grid of the 1st video i.f. amplifier, a 6CB6. At the same time, the cathode of the 6CB6 has a positive potential of approximately 9.3 volts. 8 volts of this 9.3 volts is obtained from the drop across one of the cathode resistors of the 3rd i.f. tube. The remaining 1.3 volts is derived from the tube's current flow through L_{13} and R_{14} , located in its own cathode circuit. Thus, the grid of this first i.f. tube is actually 1.3 volts negative with respect to its cathode.

It will also be seen, from Fig. 6, that the second i.f. amplifier is in series with the first i.f. stage. Hence, any changes in the plate current of the first tube will also affect the second i.f. tube and thus both tubes are directly controlled by the a.g.c. bias.

During these same weak-signal conditions, the grid of the r.f. amplifier is run at a slight negative potential. It might appear from the diagram that the r.f. grid would be positive since it connects to point "A" on the now positive a.g.c. line. However, the 2.2 megohm resistor between the r.f. grid and point "A" is so high that the small amount of grid current (due to contact potential) from the r.f. amplifier is enough to produce a slight negative grid voltage.

When the receiver is used with normal-to-strong signals, the signal voltage applied to the grid of the a.g.c. tube will increase, causing the output of the a.g.c. tube to become 5 or more volts negative. This negative voltage will be applied to the r.f. grid through the 2.2-megohm resistor and decrease the gain of this stage. (With a negative voltage at point "A", no contact current flows through the 2.2-megohm resistor.)

The same negative voltage will also go to the grid of the first video i.f. stage. Under strong signal conditions, the cathode of this 6CB6 is not as positive as it was with a weak signal because it receives less positive voltage from the 3rd i.f. cathode resistor. The voltage at this latter point varies from 8 volts with no signal to 4 volts with strong signals.

The a.g.c. delay control is adjusted as previously described for Fig. 3.

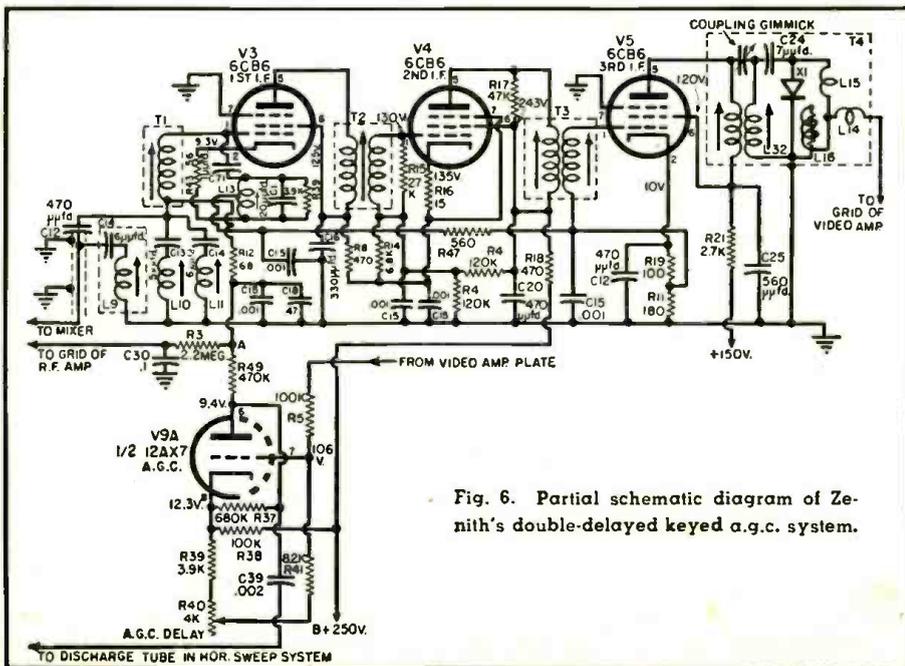


Fig. 6. Partial schematic diagram of Zenith's double-delayed keyed a.g.c. system.

COUNTER IMPROVES TAPE RECORDER

By
RICHARD H. DORF
Audio Consultant

TAPE recorders have many advantages over disc machines—erasability, noiselessness, long play, and so on—but they are lacking in one great convenience we have become accustomed to in the use of discs. That is the possibility of locating a given portion of the recording in quick order. In tape, if we want to play the second movement of the quartet, for example, we have to thread the tape, then roll it forward until we think we have hit the right place. It usually takes several tries and it is generally an annoying procedure—and all because we really have no good way of knowing just where we are on the 1200 or 2500 feet of the tape.

The counter arrangement shown in the photograph does away with this kind of headache once and for all. Not only is it an advantage for the ordinary home use of tape, but it is indispensable for the professional and semiprofessional user who edits tape or who (like the writer) records music on tape for later transfer to discs. The counter makes it possible to spot any point on the tape and later return to it within an accuracy of about 1 second; it also makes possible the timing of complete selections or portions of selections without playing anything but a few seconds of their beginnings and endings. This is done with the "Timing Chart".

The photograph of Fig. 1 shows a portion of the author's *Concertone* recorder with the timer installed, but the extremely simple system can be placed in the same way on almost any tape recorder which has the standard 5/16-inch center spindles for the reels. In the case of the *Concertone* the NARTB reel adapters cover most of the length of the spindles but there is still enough showing above the adapters to allow connection of the counters. In other machines the spindle may be almost entirely covered by the RTMA reel, but as long as there is a bare sixteenth of an inch showing it is enough.

Four elements make up the counter device. The counter itself is a standard *Veeder-Root* unit obtained by the writer for less than a dollar from *Herbach & Rademan*. The model number of the particular one at hand is A-0114214, but there are probably other models that will do as well. The essential characteristic is that it must have a shaft which advances

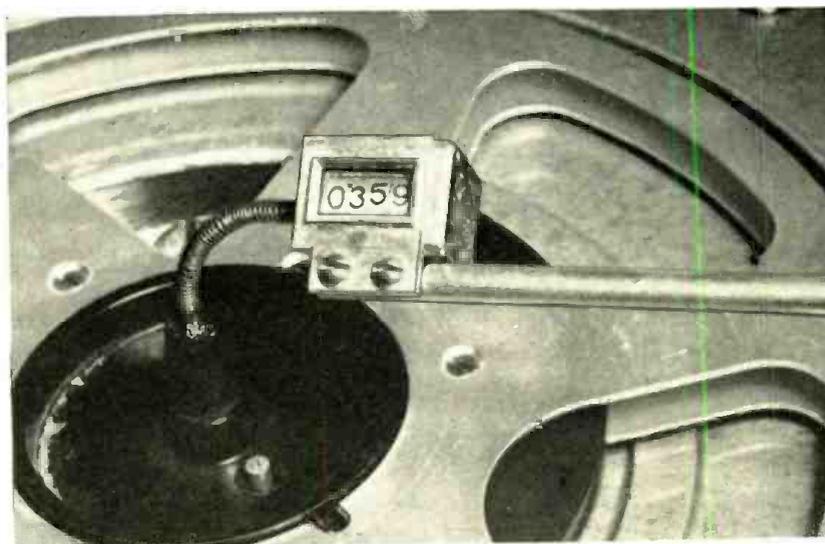


Fig. 1. Close-up view of counter mounted on brass rod. The rod is bent at right angle with lower end pushed into a hole in the wooden case. The counter shaft is connected by a spring to a rubber eyedropper bulb which slips over the take-up reel spindle.

Increase the versatility of your tape recorder by adding an inexpensive counter. All components are readily available.

the count by 1 each time it makes a complete revolution in the clockwise direction (looking at the shaft end) and reduces the count by one for each revolution in the other direction. A unit in good condition should be obtained, one which has negligible shaft friction and needs almost no power to drive it. If the counter is new (not used) it will be satisfactory. A 4-digit counter is necessary although only numbers up to a little over 1400 are used.

Item 2 is a small spring about 1½ to 2 inches long. The spring should be very light and flexible so that practically no force is required to bend it to a right angle. The spring


used by the writer was closewound and its flexibility was increased by pulling it out a little to separate the turns slightly.

The third piece is a rubber bulb from a medicine dropper. They come in different sizes. The one selected should have an inner diameter enough smaller than the outer diameter of the reel spindle so that when it is placed over the spindle it will grip tightly. A bulb with a bevel around the open end is best since that gives a thin wall at the spindle end and will work even with a very small amount of the spindle showing above the reel.

The last item is a length of quarter-

(Continued on page 159)

Fig. 2. Timing Chart. Use it to translate counter readings to time any recorder using the NARTB standard hub or reel and at speeds of 7½ or 15 inches-per-second. A similar chart for recorders with RTMA reels can be easily devised by the user.

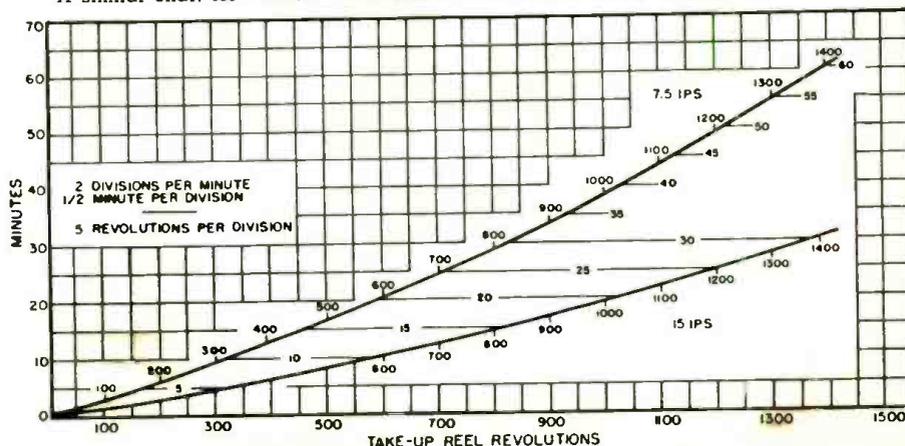


INEXPENSIVE NOVICE STATION

By

LARRY TROMBLY, W0DCB, & ROBERT A. HATHAWAY, W0GTK

Walter Ashe Radio Company

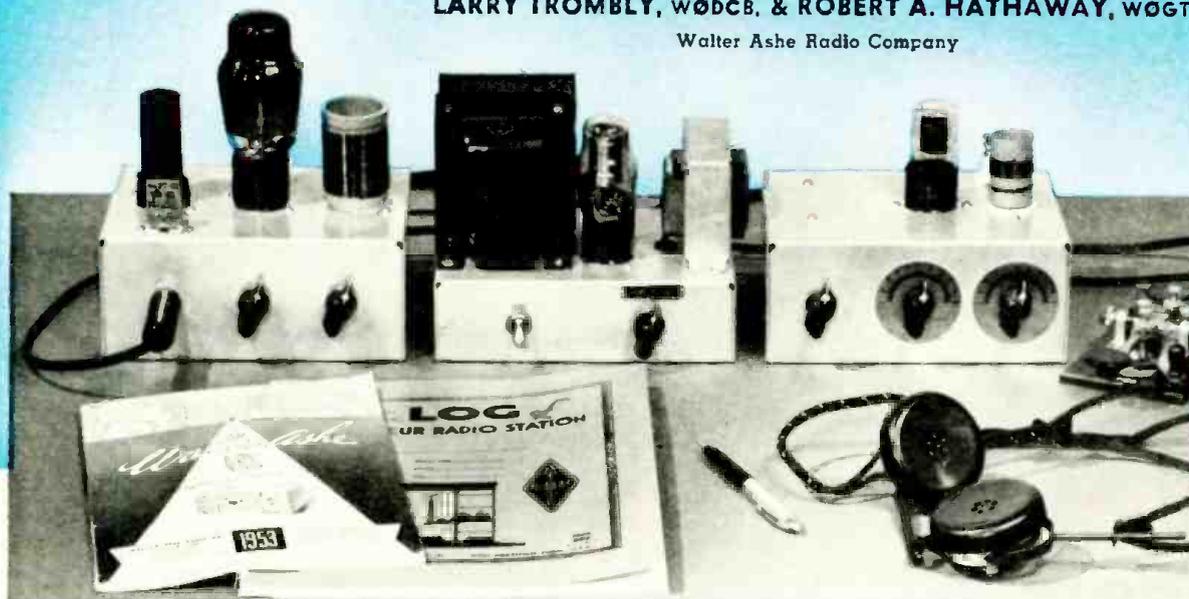

The complete Novice station: an efficient two-tube transmitter, a surprisingly effective simple receiver, and a single power supply for both. With the power supply switch in "receive" position, transmitter may be used for code practice.

Part 1. The transmitter and power supply of a complete station which can cost less than fifty dollars, including the receiver. The receiver will be described next month.

A GLANCE through radio catalogues or at the advertisements in radio periodicals may lead one to the conclusion that amateur radio is a fairly expensive hobby. In fact this belief has discouraged a number of beginners, particularly the younger ones whose supply of cash is limited. With this in mind, the writers have set out to show that it is still possible to get started in amateur radio with a very modest outlay. Twenty-two years ago, one of the writers got on the air after having spent about \$22.00. Considering the rise in the cost of living since that time, the cost of the equipment to be described here is comparable and performance is better. Certainly the \$22.00 outfit didn't provide you with a T9X signal.

With slight modifications of circuits found in *ARRL's* "How to Become a Radio Amateur" and "The Radio Amateur's Handbook" and using all new standard parts, a complete novice station was built at a cost of slightly less than \$50.00. This equipment consists of three units; transmitter, receiver, and power supply. The receiver will be described next month.

The transmitter uses a 6AG7 modified Pierce crystal oscillator which

has an untuned plate circuit using a small peaking coil whose inductance approaches self-resonance on 80 meters. The amplifier uses a 6L6 with a pi-section output circuit which permits use of random lengths of wire as antennas. Coil data for both 80 and 40 meters is given in the parts list. An 80-meter crystal can be used for both bands; however, the output is better when the 6L6 is used as a straight amplifier. Therefore a 40-meter crystal is recommended when the transmitter is used on that band.

Considerable effort was spent in an attempt to make this transmitter "foolproof" in that it will not oscillate with any setting of the controls when the crystal is removed from the socket. This insures that output will be crystal controlled and on the proper frequency, a condition which is quite often unobtainable in transmitters using high-gain tubes such as the 6AG7 and 6L6. The size of the 6AG7

EDITOR'S NOTE: Although the equipment in this and the coming receiver article can be constructed from parts readily available from any distributor, the units are supplied in complete kit form, with the chassis already punched, by the Walter Ashe Radio Company.

plate coil, 180 microhenrys (a Miller #6180 peaking coil), was critical in eliminating any sign of oscillation when the crystal was removed from its socket.

Complete TVI-proofing has not been provided in this transmitter; however, the type of construction used gives a good basis for such measures. Operated some 10 miles from a TV station on Channel 5, there was no disturbance to the picture with the transmitter and the TV receiver sitting side by side. Use of a metal 6L6, a coil shield, and a bottom plate on the chassis should eliminate TVI even in weak-signal TV areas.


The parts of the transmitter are mounted on a 5" x 7" x 3" chassis. The photographs will give an idea of the parts location which is not critical. Instead of a milliammeter, a pilot lamp PL_1 is used as a tuning indicator. It protrudes through a hole in the top of the chassis to the rear of the oscillator tube. A half-inch rubber grommet is fitted into the hole. The bulb is screwed into its socket and both the bulb and socket are held securely in place by pushing the bulb up through the grommet. Along the front edge of the chassis, from left to right, are mounted the keying jack and tuning condensers C_1 and C_2 . At the center of the inside back edge, a five-terminal tie strip is used to terminate the power cable, which enters the chassis through a hole fitted with a rubber grommet. This cable is shielded and ends in a five-prong plug which plugs into the

power supply. (The receiver power cable connector will be a four-prong plug. This arrangement eliminates the possibility of plugging the transmitter and receiver power cables into the wrong power supply outlets.) The heater leads should be of well-insulated hookup wire and should be kept close to the underside of the chassis. Keep all of the other leads as short as possible; in fact very little wire is required other than the leads on the components themselves and these are trimmed down in most cases.

In designing an economical novice station, the use of one power supply to furnish power for both receiver and transmitter seemed appropriate, especially since little more than a switch would have to be added to permit this operation. This supply delivers 350 volts at 100 ma. for the tube plates, and 150 volts regulated for the screen of the oscillator and for the receiver. The regulated voltage on the oscillator provides excellent keying and this 150 volts is supplied to the oscillator screen grid even when the "send-receive" switch is in the "receive" position, which permits the operator to spot his frequency on his receiver.

This arrangement is also ideal for code practice but, although very low power is used, it is advisable to disconnect the antenna from the transmitter before practicing. The previously discussed features hold true if the transmitter and power supply are used along with other makes of amateur receivers instead of the receiver to be described next month. The "send-receive" switch should be in the "receive" position for both frequency spotting and code practice, irrespective of the receiver being used.

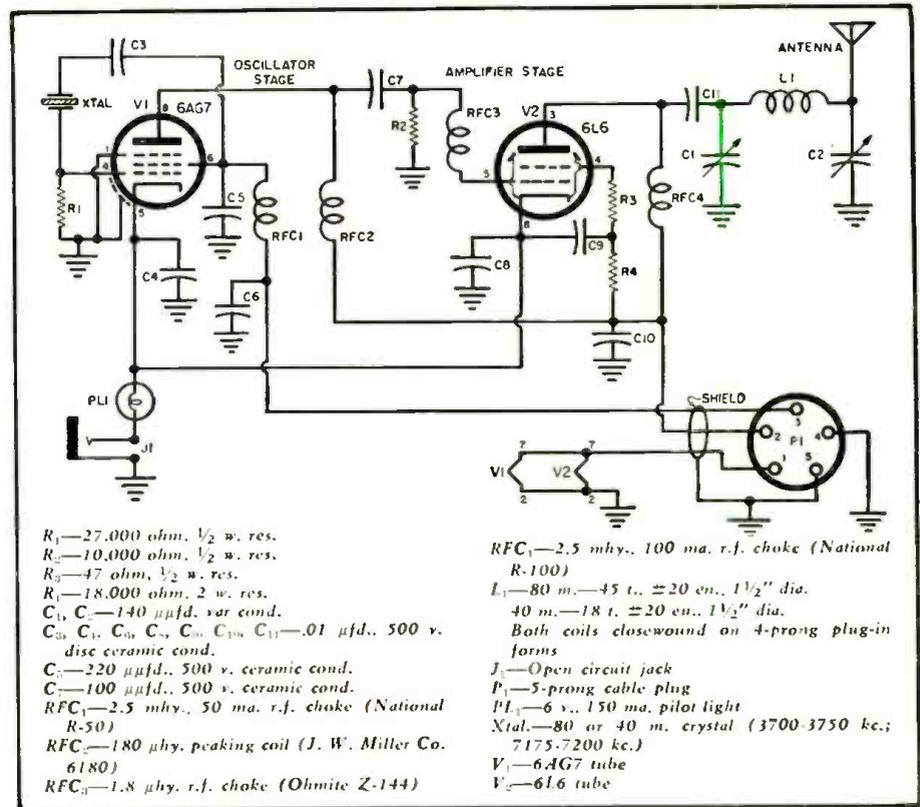The power supply parts are mounted on a 5" x 7" x 2" chassis as shown in the photograph. The "on-off" switch and the "send-receive" switch are mounted along the front




Schematic of the inexpensive transmitter. The separate power connection for the 6AG7 screen grid (P_1 , pin 3) provides a regulated voltage supply for the screen, resulting in improved oscillator stability and enabling oscillator to be used with a receiver for code practice and frequency spotting without putting the whole transmitter on the air. Two-tube circuit has many advantages over simpler rigs.

face of the chassis and the output sockets and line cord are mounted on the back face. A hole is cut in the chassis large enough to clear all the leads from the power transformer, and the leads from the choke are likewise fed through the chassis in a rubber grommet. Care should be taken in wiring up the "send-receive" switch; close inspection of its operation will indicate the correct terminals to use. The a.c. power cord is connected


through the internal jumper of the 0D3 as a safety measure (the supply is "killed" if the tube is removed); the connections to pins 3 and 7 of the 0D3 are not needed for the voltage regulating function.


After having carefully checked the wiring of both power supply and transmitter, you are ready to test these units. With the "send-receive" switch in the "receive" position, turn on the power supply. The 0D3/VR150

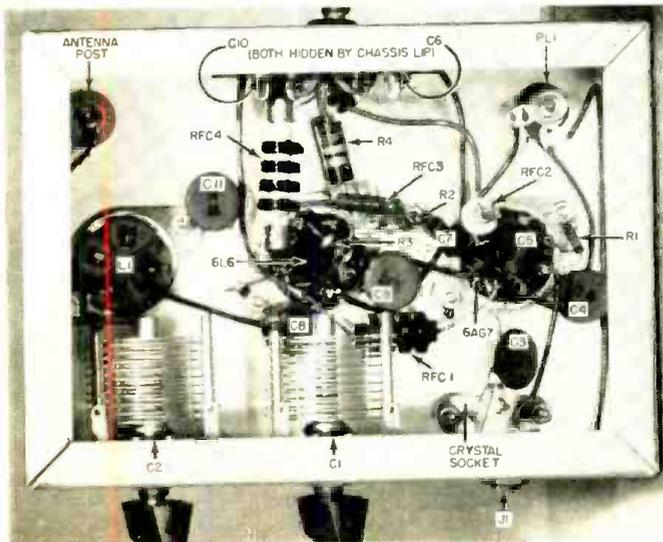Under-chassis view. Although a compact chassis is used, wiring is not crowded or difficult. Care should be taken not to overheat parts while soldering. Note that stator connections on the tuning condensers are made to ends of the stator bars rather than to the lugs (near chassis lip) to insure short leads.



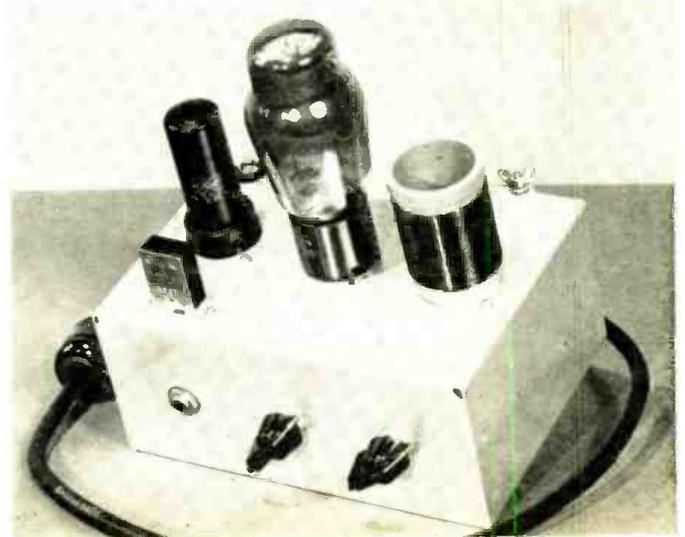The completed transmitter has a neat, businesslike appearance. Its power and performance are similar to those of "standby" rigs used by experienced amateurs. J_1 and knobs for C and C₂ are along front face of chassis; the tuning indicator bulb can be seen at left rear corner, antenna stand-off at right.



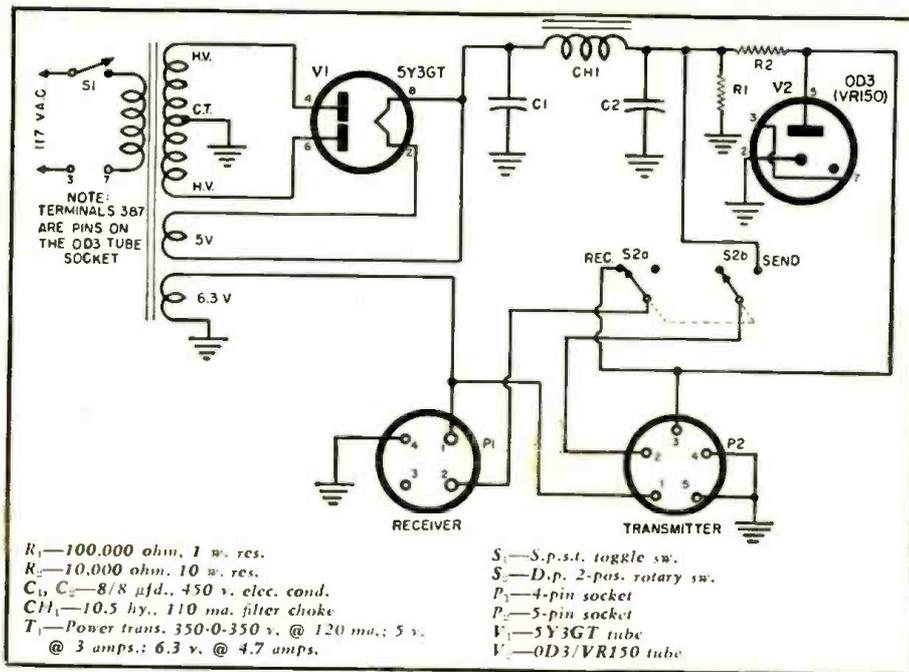

Schematic of the power supply for the inexpensive Novice station. As the screen grid of the 6AG7 transmitter oscillator is connected in both positions of S_2 , the tube can oscillate weakly and may be used with a receiver for code practice.

regulator tube should show a blue glow. On the receiver, tuned to the frequency of your crystal, you should hear a clean signal as you close the key. Next, with both tuning condensers set to maximum capacity, throw the "send-receive" switch to "send". The tuning lamp will glow brightly. Tune C_1 for a dip in the brilliance of the tuning lamp, PL_1 . This point indicates resonance of the 6L6 plate circuit. If all has gone well so far and you are a licensed amateur, you are ready to load the transmitter with an antenna.

Any piece of wire 60 feet or longer can be used for both 80- and 40-meter operation. The optimum length for the 40-meter Novice band is about 65 feet and for the 80-meter Novice assignment it should be 125 feet. With

the antenna connected to the transmitter, check for resonance by swinging C_1 slightly back and forth and watching PL_1 . Now slowly open condenser C_2 a little bit at a time and, after each change of C_2 , check for resonance with C_1 . You will find that the dip in the brilliance of the tuning lamp becomes less and less as you continue to open C_2 . When you have opened C_2 to a point where you can just detect a dip in the tuning lamp as you tune C_1 , the transmitter is fully loaded and ready to go.


As much tuning as possible should be done with the transmitter connected to a dummy load rather than to the antenna to prevent unnecessary QRM on the heavily loaded amateur bands. A satisfactory dummy load can be made with a 25-watt light

bulb and two short clip leads. The leads are soldered to each connection of the bulb and then one lead is clipped to the antenna terminal and the other one to the metal chassis of the transmitter. Tuning procedure is the same as that outlined before when feeding power to the antenna. The 25-watt light bulb will glow to nearly full brilliance if your transmitter is properly tuned. It should be noted that the setting of C_1 and C_2 quite likely will not be the same when operating the transmitter into the dummy load as when feeding the antenna. This is true unless by chance the antenna and dummy load present the same impedance to the transmitter.


This transmitter and its companion receiver have been used successfully on the 40- and 80-meter bands, including the crowded Novice portions of these two bands. Reports on the signal from the transmitter have been excellent and both coasts were worked with no difficulty. 579X reports at distances over 1000 miles have been consistently received and it was gratifying to be able to hold our own in competition with transmitters of much higher power. Naturally the best results will be obtained when the best possible antenna is used. Running 30 watts input, and with a little patience and some late night hours on your part, this transmitter is quite capable of producing foreign contacts.

Experienced amateurs will recognize the fact that the transmitter and power supply are not only well suited for the Novice, but that they can do a fine job as the regular rig for the old-time "c.w. hound". Many of the present day hams who have been weaned and raised on higher power will be surprised to see what can be accomplished with this small compact outfit. It is ideal for the high power man as an inexpensive standby rig in the event of rebuilding or breakdown of the "big rig", too much TVI, or high electric bills. (To be continued)

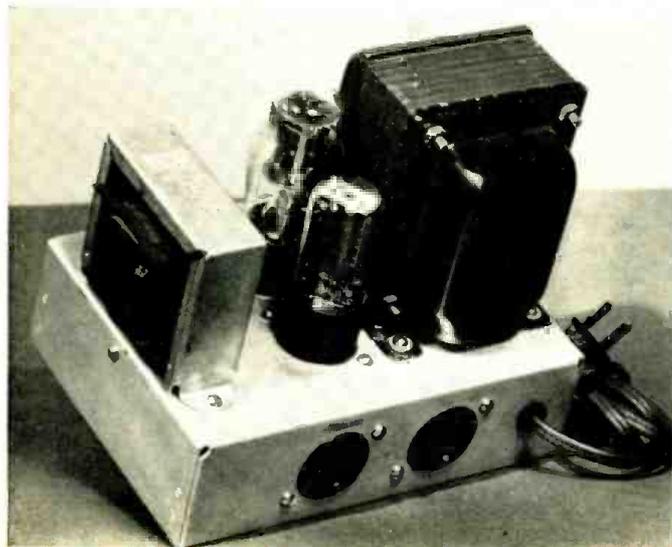Rear view of the power supply. Along the back edge, left to right, are the receiver and transmitter power sockets and the a.c. cord. The larger tube is the OD3 voltage regulator.



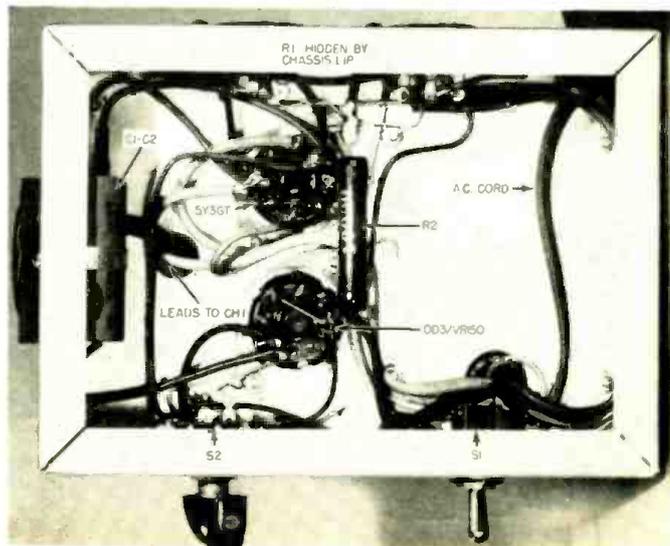Under-chassis view. Ground connections are made to lugs under socket mounting screws. Power transformer leads come through grommeted hole near S_1 at right. Wiring will be fairly easy.



BREAK-IN WITHOUT RELAYS

By BRUCE F. BROWN, W6TWW

VOICE-CONTROLLED break-in systems employing relays for transmitter and receiver control are slow-acting, causing undesirable clipping of first letters or syllables. In addition to acoustical noise in the "shack", relays cause distracting clicks and pops in the receiver and may even cause TVI.

The electronic break-in system to be described has none of the attendant disadvantages of relays, and it may be added to the station with little or no modification of existing control circuits. It is fast-acting, it makes clipping virtually undetectable, and it causes no distracting noise. Since the receiver is operative during every pause in speech the channel can be monitored for interfering signals. This same feature makes it possible to interrupt a station equipped with this system. The parts values in the system have been chosen so that the receiver cuts off before the transmitter is energized, and the transmitter cuts off before the receiver is re-energized. Any possibility of feedback is thus eliminated.

For the principle of operation, refer to the schematic. Audio is picked up from an existing speech amplifier and applied to the input circuit of V_{1a} . V_{1a} , in turn, amplifies the audio signal and applies it to V_{1b} which produces a rectified negative control voltage across R_1 and C_1 . This negative control voltage biases V_{2a} to cut-off causing V_{2b} and V_3 to conduct. The conduction of V_{2b} biases V_4 well past cut-off, thus removing screen voltage from the r.f. and i.f. screens of the receiver. When V_1 conducts, the 60-volt negative blocking bias produced at its cathode is shorted to ground thus unblocking the transmitter grids.

The time constant of R_1 and C_1 has been chosen so that with continuous talking the receiver will remain cut off and the transmitter will remain energized. However, at the ends of sentences or during any other break in continuous speech, the receiver will become operative, and the transmitter will be de-energized. If it is desired that the receiver be operative between words, the value of C_1 should be reduced. The correct capacity can be determined easily with a little experimentation. Switch S_1 disables the voice-control circuits when manual-control switching of the receiver and transmitter is desired.

In order to simplify the power supply, V_{1a} is operated with a grounded plate. This eliminates the need for a separate positive supply. A well-filtered




The all-electronic break-in system is small and is easily adapted to most stations using voice control. Well-filtered negative power supply is needed.

Voice-controlled break-in without relays switches receiver and transmitter without bothersome clicks or noise blasts.

negative power supply is necessary, however, since any ripple voltage appears as input to V_{1a} and would cause false operation of the circuit. Although the maximum heater-to-

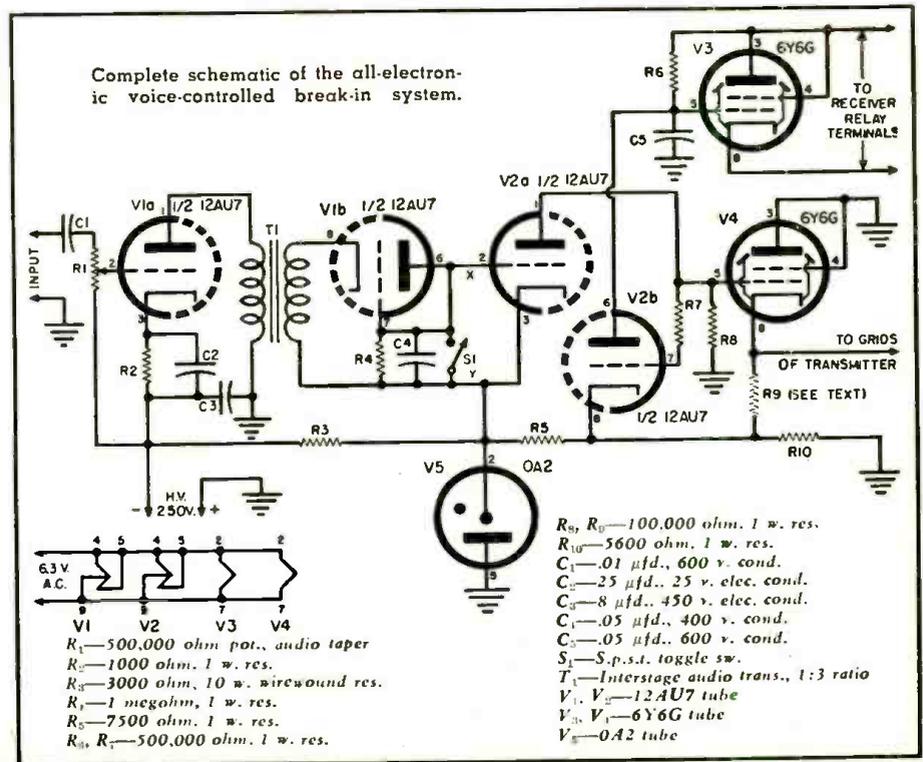cathode voltage ratings of V_1 and V_3 are exceeded, no trouble has been experienced. The purist, however, may wish to use separate heater supply windings. (Continued on page 132)



U. H. F. TEST EQUIPMENT ADAPTER



Fig. 1. The Philco adapter for converting v.h.f. service instruments to u.h.f. use.

You can adapt your v.h.f. signal or sweep generator to u.h.f. measurements with the unit described here.

DUE to the speed with which u.h.f. television was launched, there has been an urgent need in all service shops and laboratories for quality-engineered and low-priced u.h.f. service equipment.

The need for this type of equipment was foreseen by many electronic manufacturers. The result of a great deal of research and design work at Philco is a unit which prevents obsolescence of existing v.h.f. signal generators. This unit, the Philco Model G8000 v.h.f.-to-u.h.f. signal generator adapter (see Fig. 1), uses the Philco u.h.f. tuner as its heart.

This instrument will adapt any present v.h.f. signal or sweep generator, set at 60-mc. output, to any ultra-high frequency between 470 to 890 mc. This gives full channel coverage, from Channel 14 to 83. The adapter has sufficient handpass (15 mc.) to convert the entire sweep range of a sweep generator to u.h.f. frequencies. Markers may be fed into the adapter and measurements made the same as at v.h.f. Field strength meters may also be converted by the instrument to operate on u.h.f.

The adapter may also be used to convert any u.h.f. signal to Channels 2 or 3 on a TV receiver. Thus, it serves to check the over-all operation of u.h.f. converters and tuners rapidly.

As will be described later, this adapter has certain advantages over regular u.h.f. generators—and is less expensive. Basically, the G8000 employs a continuous-tuning variable condenser system to cover the u.h.f. channels by the superheterodyne prin-

ciple in which the oscillator frequency beats with a 60-mc. signal, and the resultant frequency sum is used as a u.h.f. signal. (See Fig. 4.) Since there are no vacuum tubes used in series with the signal, and since the mixing is done by a crystal, it follows that the adapter can be used in reverse to change u.h.f. to v.h.f.

A v.h.f. signal having a frequency of approximately 60 megacycles is fed into the 75-ohm input connector of the adapter, and is coupled by means of the low-impedance winding on transformer, T_2 , to the slug-tuned secondary of this transformer. (See Fig. 6.) From this point the signal is applied to the crystal mixer assembly, consisting of L_5 - L_6 and C_1 , and CD_1 . A signal generated by a local oscillator consisting of a type 6AF4 u.h.f. triode, V_1 , and its associated circuit, is introduced into the crystal mixer circuit by means of a 300-ohm miniature transmission line and the mutual coupling between L_7 - L_8 and L_5 - L_6 . This results in a beating together of the v.h.f. input signal and that from the local oscillator.

The beat frequency, which is equal to the sum of the local oscillator frequency and the v.h.f. input frequency, is passed on toward the u.h.f. output of the adapter by the mixer tank and tuned output tank circuits. All other beats and responses are greatly attenuated. The transfer of signal energy between the mixer assembly (or board) and the mixer tank circuit is accomplished by means of the mutual coupling between L_4 and L_5 , while signal transfer between the mixer and

By

DAN LERNER and WINSTON STARKS

Test Equip. Section, Philco Accessory Div.

the u.h.f. tank circuits is brought about by the mutual coupling between L_2 and L_3 and the stray capacitance, C_2 . From the output tank circuit, the u.h.f. signal is coupled, through a 150-ohm transmission-line matching section and two 680 μ fd. condensers, to the 300-ohm u.h.f. output terminals of the adapter.

The transformer-type supply provides a 6.3-volt a.c. power source for the heater of the local oscillator tube. A cathode-type full-wave rectifier tube, the 6X4, is used in conjunction with a resistance-capacitance filter to furnish a hum-free plate-supply voltage for the oscillator.

The use of the G8000 adapter is simple and straightforward in all of its applications. Whenever a v.h.f. signal is to be converted to u.h.f., it is simply fed through 75-ohm coaxial cable to the v.h.f. connector on the adapter. This signal must be at a frequency of 60 mc. for the dial calibration to hold true. Variation from 50 to 70 mc. is possible with a proportionate reduction in conversion efficiency, plus a loss of frequency calibration. The resulting u.h.f. signal appears at the u.h.f. connector. In this case, the u.h.f. connector is treated as the signal source.

When used to convert to u.h.f., the attenuator of the regular v.h.f. generator can still be used. To anyone who has ever tried to attenuate a u.h.f. signal, this feature will be welcomed as the logical solution for accurate and convenient control of u.h.f. signals.

Markers can be produced by v.h.f. generators coupled into the v.h.f. input cable to the adapter. The marker generator is handled just as if it were being used on a response curve at 60 mc.

Operation of the G8000 adapter in reverse is also a simple and straightforward procedure. A u.h.f. signal is fed into the u.h.f. antenna terminals. The v.h.f. output terminals are connected to whatever device is intended to accept the v.h.f. (at approximately 60 mc.). Then the u.h.f. dial is tuned to the incoming u.h.f. signal or for maximum v.h.f. output.

U.H.F. Test Hints

There are a number of precautions which should be taken whenever making tests at u.h.f. frequencies. It is necessary to use some new techniques

Certified RECORD REVUE

By **BERT WHYTE**

THE introduction of a record revue section in *RADIO & TELEVISION NEWS* may cause some lifted eyebrows, inasmuch as the editorial coverage of this magazine has always been on a technical plane. However, the results of a recent survey of our readership has convinced us of the need for this type of coverage. In this section the technical aspects of the recording will be fully covered, as to frequency response, dynamic range, distortion content, tracking, spindle hole eccentricity if present, surface noise, transient response, etc. Since the ultimate goal is the greater enjoyment of music, the section will include pertinent musical data about the recordings reviewed.

It will be the policy of this department to name the equipment used in the reviews, as well as the acoustical environment of the equipment. Each month the equipment used will be tested by an independent group of qualified engineers and "certified" as to the operating perfection of all elements, from pickup through loudspeaker.

Equipment used this month: *Weathers* FM pickup, *RekOkut* T12H, *Fisher* preamp equalizer, *McIntosh* 50 watt amplifier, *Jensen* G-610 "Tri-axial" in *Jensen* folded-horn corner enclosure. Speaker was placed in hard plaster corner, room has absorptive wall opposite speaker, carpeted floor, three reflective walls, hard ceiling, usual upholstered furniture. Reverberation time about 2 seconds, practically no slapback.

RESPIGHI

THE PINES OF ROME and THE FOUNTAINS OF ROME

The Minneapolis Symphony Orchestra conducted by Antal Dorati. Mercury 50011, 33 1/3 rpm, AES curve. Price \$5.95.

The Vienna State Opera Orchestra conducted by Argeo Quadri. Westminster 5167, 33 1/3 rpm, AES curve. Price \$5.95.

These offerings might be called the "dilemma of the db", or "which one has the mostest." Respighi wrote some of the most rip-roaring music in history. The loudness of his music is almost overshadowed by the loudness of the adherents of these discs. Seldom

has such vociferous controversy raged over phonograph records! Each camp is firmly convinced that the other is composed of members of that ignoble musical fraternity, Theta Epsilon Beta (Tin Eared Baboons)! Why all this uproar? Armed with both discs, I decided to listen and learn.

One thing is immediately apparent. Both the *Mercury* and *Westminster* discs are highly exciting recordings. Equally apparent is the difference in recording techniques. The engineers of both companies have tried to reach the same goal, but by totally different approaches. The *Mercury* people employed their by-now-famous, single *Telefunken* mike suspended at some optimum point over the conductor's podium. And *Westminster*? Well, I wasn't present when the recording was made (and *Westminster* ain't tellin') but I suspect they utilized a clever new version of an old technique used for "pop" dates! Each choir in the orchestra (brass, woodwind, etc.) is individually miked with reflecting or damping boards as dictated by acoustic outputs of the instruments, and then mixed by the engineer on the console. Usually an omni-directional mike is suspended for hall reverberation to enhance the liveness of the recording.

Both recordings are productive of some terrific sound. If you have a yen for the satisfying thump of bass drum and tympani, the crash of cymbals, then this is your meat. With controls set flat and with proper equalization for each disc, the *Westminster* seemed more strident than the *Mercury*, although string tone was generally well above average. It was in the last movement of the "Pines of Rome," which is fortissimo with a vengeance, that decided me in favor of the *Mercury* version. Now, I'm all for high-fidelity sound and the more cycles per, the better. But I think it is a cardinal sin to overlook the fact that we are still dealing with music, and that certain rules and a modicum of taste should be preserved. What I am referring to is the overblown dynamics and odd phrasing evident in the *Westminster* disc. Partly this is Mr. Quadri's sin, but the greater part is the overzealous "dial twiddling" of

the engineers. Had the tremendous climax come over completely free of distortion, it might have passed notice. But alas! the last few bars give far from mute testimony of the heavy hand on the controls. The dynamic range of the *Mercury* disc is unbelievable. I had the good fortune to hear the original tapes on the *Mercury*, "Pines." The transfer from tape to LP, via the sensational new *Miller* cutterhead was an astounding demonstration of what can be cut into a disc in terms of dynamic range, frequency response, and lack of distortion. Performance-wise, Dorati and the Minneapolis have far better command of the score; Dorati, often called a "cold" conductor, displays little of that attitude here and instead is highly evocative in the lyrical sections. Mr. Quadri does a competent job, within the limits of his insight into the score, but suffers from an orchestra far less disciplined than this colorful music demands. Surfaces of both recordings were very good. Summing up; a few years ago either disc would have been manna from heaven. Now with two very exemplary versions around, you've got a problem. Some people like vanilla and some like chocolate. I like the *Mercury*.

Note: Anent the reference to the *Miller* cutterhead most of the *Mercury* "Olympian Series" recordings originally cut with the *Gramplan* head have been recut with the *Miller* with results even more spectacular than the original. You can identify the new pressing by the letters "MF."

GOULD SPIRITUALS FOR ORCHESTRA GERSHWIN

PORGY AND BESS (arr. by Robert Russell Bennett)

The Minneapolis Symphony Orchestra conducted by Antal Dorati. Mercury MG50016, 33 1/3 rpm, AES curve. Price \$5.95.

Fabulous!! A more apt description of this recording would be hard to find. In many years of listening I have heard many great combinations of performance and score, recording technique and superb orchestras. In this recording a happy amalgam of all these factors has resulted in one of the outstanding listening adventures of this or any other year. The Gould "Spirituals," is the prize side on this disc and the side which I will review, although the "Porgy" is magnificent musically and technically.

I predict that "Spirituals" will supplant Varese's "Ionisation," as the demonstration record *par excellence*. Since the Gould score is also extremely interesting and listenable music, this will come as blessed relief to thousands of wild-eyed and long-suffering wives who have been under siege by 110 db of fire siren, assorted gongs and bells and of course, the lion's roar. As a demonstration piece for transient response and dynamic range, this disc has no peer. In five movements, "Spirituals," encompasses

(Continued on page 157)

THE 1954 Zenith television receivers utilize the following chassis: 19L25, 19L26, 19L27, 19L28, 21L21 and 22L20. These form the "Super K" or "L" series, designed for the best possible reception of both u.h.f. and v.h.f. TV signals in extreme fringe as well as local areas.

Tuner

The "Super K" chassis incorporates an improved signal-to-noise ratio, 12-position turret tuner, using a 6BK7A cascode-type r.f. amplifier, and a 6U8 triode-pentode used as a mixer and oscillator. The turret is shipped from the factory with twelve pairs of v.h.f. strips in place; however, it may be filled with any combination of twelve u.h.f. or v.h.f. pairs of strips. The tuner may be removed from the receiver without taking the chassis from the cabinet. Merely disconnect the fine tuning shaft, remove the antenna lead and plug-in connections, and then remove four small screws.

The complete circuit diagram of the tuner with the channel selector switch in a v.h.f. position is shown in the upper left of Fig. 1. The antenna is connected to a center-tapped primary. Two i.f. rejection traps, resonated to approximately the center of the i.f. bandpass, increase the i.f. rejection on Channel 2 and on u.h.f. These traps are designed so that additional resonant frequencies are not present in the u.h.f. band.

The r.f. grid coil is returned to ground through a trimmer condenser, C_5 , which is adjusted to approximately equal the value of the input capacitance of the 6BK7A.

The principal reason for using the 6BK7A cascode r.f. amplifier is to obtain the lowest possible noise figure on all channels. The cascode interstage is series-tuned near Channel 13 by means of a series coil, L_1 , connected between the first plate and second cathode. The two triode sections are connected in series and, therefore, have identical values of plate current. The grid of the second triode is held at a fixed potential by means of a voltage-divider network between "B+" and ground, thus giving a relatively rapid cut-off of the plate current of the first triode section, which is controlled by the a.g.c. voltage.

A pair of double-tuned circuits is provided between the r.f. amplifier plate and the mixer grid. The two coils are returned to ground through a common inductance, L_2 , which provides some coupling between the circuits on the high channels. On Channel 13 the coupling between the coils on the strip actually opposes this common inductance coupling slightly, while on the lower channels this common inductance coupling is reinforced in varying amounts by the coupling between the coils on the strip. All other coupling media between the circuits have been carefully avoided.

The mixer grid and r.f. plate coils are made identical by returning the



By

BRIAN J. MAROHNIC

TV Field Engineer, Zenith Radio Corp.

Complete service information on the new 1954 Zenith TV sets, including full schematic and alignment data.

converter grid through a 19 μ fd. series condenser, C_{10} . This simplifies the standardization of the coils, thus requiring fewer different types.

The oscillator tube is decoupled from the coil on the strip by means of a 5.5 μ fd. series condenser, C_{12} . This effectively increases the inductance value of the oscillator coil, and thereby minimizes the effect of contact and other stray inductances, and reduces the effect of tube voltage variation on the oscillator frequency. The variable condenser tapped on L_{10} , and designated as the fine tuning control, is used at the factory for standardizing the circuit, and as a fine tuning control by providing a stop which, after the factory trimming adjustment, permits the condenser to be turned only two turns out of the several in its complete range.

Where leads are brought out of the oscillator compartment for the "B+" and heater, feedthrough ceramic condensers and series r.f. chokes provide good isolation of all oscillator r.f. currents. Besides the normal shielding, some extra shielding is provided over the grid and cathode leads to the second triode of the 6BK7A which extends into the oscillator compartment.

All changes, going from v.h.f. to u.h.f., are made by simply turning the channel selector knob from a v.h.f. channel to a u.h.f. channel. The operation of the receiver is exactly the same on u.h.f. as it is on v.h.f., and there are no additional knobs or switches. The u.h.f. antenna, if required, is connected to the same tubular 300-ohm line, through an isolation filter, as that used to feed the v.h.f. signal to the receiver input terminals.

This tuner converts the u.h.f. signal


to the 40-mc. i.f. frequency used by the receiver. In the upper left-hand corner of Fig. 1 is shown the circuit of a u.h.f. strip. The u.h.f. strips are similar in size to the strips used for v.h.f. Incorporated on the u.h.f. channel strips is the u.h.f. preselector, the u.h.f. crystal mixer, which derives its local signal from a crystal multiplier between the mixer and v.h.f. oscillator, and coils for tuning the r.f. grid and plate, and the converter grid to the intermediate frequency. The converter output connection remains unchanged. These circuit changes are made entirely on the channel strip itself.

The triode of the 6U8, which is used as the v.h.f. oscillator, is also utilized as the oscillator on u.h.f. The oscillator tube, however, is operated on v.h.f., and its output is multiplied to u.h.f. by the crystal multiplier.

To feed the oscillator power into the crystal multiplier, which is inside the antenna compartment, a short coaxial cable is used. The possibility of coupling oscillator power to the antenna is avoided by providing a stator contact, #6, which has an effective ground finger on either side of it—and the best possible shielding around it. This contact is fed by means of the short coaxial cable, extending into the oscillator compartment to an extra stator contact, which is not used on v.h.f. For u.h.f., a small condenser is connected between this terminal (#11) and the plate end of the oscillator coil. Further isolation between the multiplier contact, #6, and the antenna is provided by the u.h.f. tuned circuits on the channel strip.

Coils LA and LB are preselector coils tuned to the incoming u.h.f. car-

Fig. 1. Complete schematic diagram of the Zenith 19L26 and 19L28 chassis. All other "L" series chassis use this diagram with some minor modifications. Note the schematic for a typical u.h.f. strip in upper left.

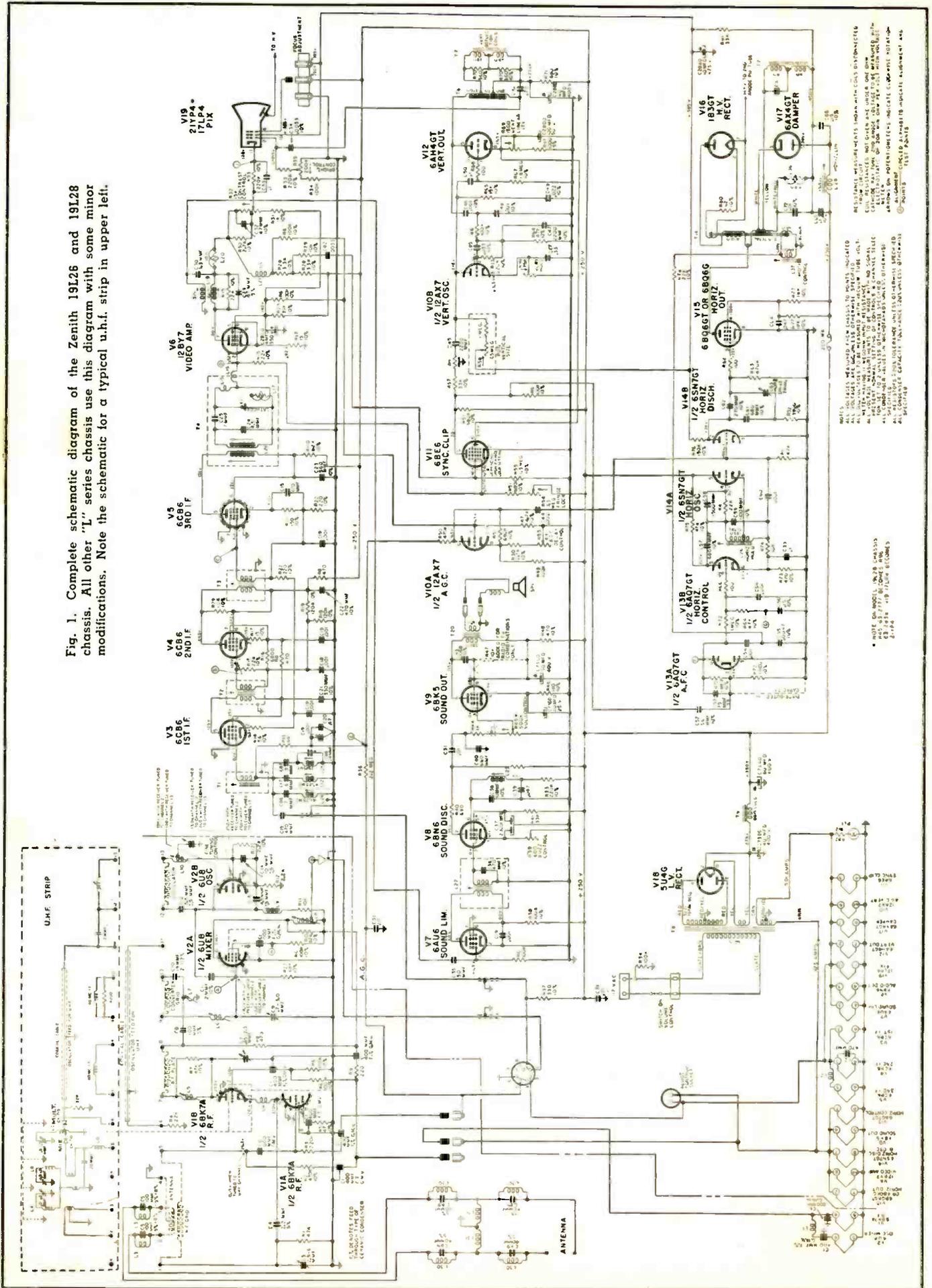

NOTE: ALL TUBES SHOWN ARE 9-pin tubes. ALL RESISTORS ARE 1/2 WATT UNLESS OTHERWISE SPECIFIED. ALL CAPACITORS ARE 50V UNLESS OTHERWISE SPECIFIED. ALL RESISTORS ARE 1/2 WATT UNLESS OTHERWISE SPECIFIED. ALL CAPACITORS ARE 50V UNLESS OTHERWISE SPECIFIED. ALL RESISTORS ARE 1/2 WATT UNLESS OTHERWISE SPECIFIED. ALL CAPACITORS ARE 50V UNLESS OTHERWISE SPECIFIED.

* 6BQ6 OR 6BQ7, 6BQ8, 6BQ9, 6BQ99, 6BQ100.

rier frequencies. Coil *LC* is a mixer coil which combines the multiplied oscillator frequency with the incoming signal to produce the 40-mc. i.f. Coupling between the antenna and the first tuned circuit is accomplished by means of a very small center-tapped loop, inductively coupled to the low potential end of the coil. Coupling from the second preselector circuit to the mixer is accomplished by a small loop, one side of which is returned to a 20 μ f. r.f. bypass condenser, and the other side is connected to the crystal. This r.f. bypass condenser also forms a part of the matching network to the 6BK7A grid. The other side of the mixer crystal connects to a tap on the multiplier coil, near the low potential end, to obtain oscillator excitation for the mixer. The multiplier crystal is connected to another tap, slightly higher on the multiplier coil. The other side of the multiplier crystal connects to the oscillator through the turret contact and shielded cable mentioned previously. The entire assembly is mounted in a metal casting, which provides excellent shielding for the preselector and multiplier circuits, both from each other and external influences.

The 40-mc. signal is applied to the 6BK7A grid through a pi network. Resistor, R_2 , supplies a steady $\frac{1}{2}$ milliampere of current through the crystal. The steady d.c. current creates a constant load at all times across the tuned circuits.

The main oscillator tuned tank is located in the tuner chassis. This tank circuit is in series with a small tun-

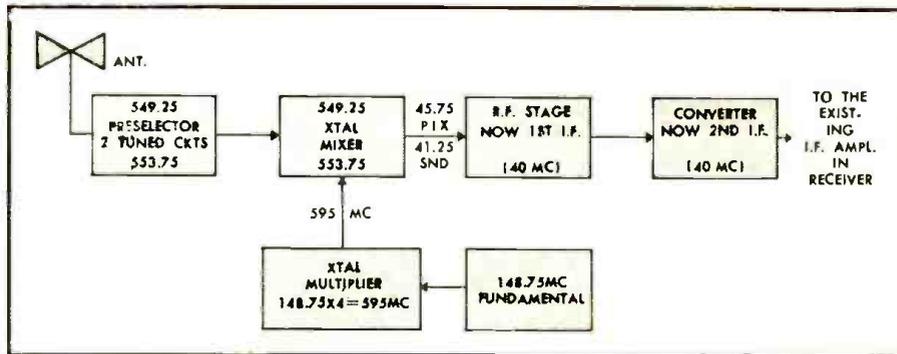


Fig. 2. Block diagram of the Zenith u.h.f. tuner strip conversion method showing how conversion to the receiver's i.f. is effected for Channel 27.

able coil, mounted on the strip, which adjusts the oscillator to the fundamental frequency desired. The sine-wave output of the oscillator circuit is fed to the germanium harmonic generator crystal. The crystal conducts only on the very peaks of the waves, and its output consists of sharp pulses which are rich in harmonics of the fundamental frequency. The oscillator tuned coil is adjusted to the desired harmonic frequency (by means of a metal screw which enters the coil and changes its inductance), and is excited at that frequency only. This is illustrated in Fig. 2, which is a block diagram of the operation of the tuner for Channel 27 (548-554 mc.). Here the fourth harmonic of the fundamental oscillator frequency, 148.75 mc., excites coil *LC* which is tuned to 595 mc., with the result that this frequency mixes with the video carrier frequency of 549.25 mc. to give the de-

sired video i.f. The actual conversion takes place in the mixer crystal, CK_{310} .

The 6BK7A and the 6U8 pentode section become i.f. amplifiers for u.h.f. by means of i.f. coils inserted into their circuits by the u.h.f. strip. The output of the 6U8 pentode section is fed to the regular i.f. section of the receiver.

The complete change to u.h.f. circuitry takes place as the u.h.f. strip clicks into position. The multiplier circuit can be tuned by connecting a voltmeter which has a full-scale reading of .2 or .3 volt to the turret contact for the 6BK7A grid. With the proper oscillator strip inserted, and the oscillator on the correct frequency, the multiplier tuned circuit can be adjusted for a dip in the voltmeter reading. Optimum excitation is that which causes the voltage across the crystal to drop to approximately

Table 1. Alignment procedure for the video i.f. and sound circuits of the Zenith "L" series chassis.

VIDEO I.F. ALIGNMENT						
STEP	SIGNAL GENERATOR FREQUENCY	CONNECT TO	OUTPUT INDICATOR	CONNECT TO	ADJUST	REMARKS
1			V.T.V.M.	Point E in Fig. 1	Bias to -2 volts	Use a 2-volt battery with potentiometer across it. Connect positive terminal to chassis.
2	43.5 mc. center frequency, 5 mc. deviation	Pin 1 of V_3 (Test point "C")	Oscilloscope through 10,000-ohm isolation resistor	Pin 2 of V_6 (Test point "D" and ground)	T_1 (top and bottom) for max. gain with 41.25 and 45.75 mc. markers in valleys of response curve	Adjust generator for 3-volt peak-to-peak detector output.
3	43.5 mc. center frequency, 5 mc. deviation	Pin 2 of V_2 (Test point "A")	Oscilloscope through 10,000-ohm isolation resistor	Pin 2 of V_6 (Test point "D" and ground)	L_{12} , L_{24} , and L_{25} for minimum marker amplitude at freq. shown in Fig. 1	It may be necessary to reduce bias to zero (or go slightly positive).
4	43.5 mc. center frequency, 5 mc. deviation	Pin 2 of V_2 (Test point "A")	Oscilloscope through 10,000-ohm isolation resistor	Pin 2 of V_6 (Test point "D" and ground)	T_2 , T_3 , T_4 , and L_6 for response curve below	Readjust bias to -2 volts
SOUND CIRCUIT ALIGNMENT						
5	Tune to on-the-air TV channel				L_{19} (top and bottom), L_{22} , L_{23} and R_{39} , for cleanest sound, min. buzz	Adjust step attenuator to level where "hiss" is heard.

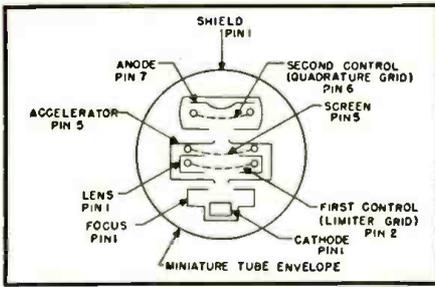


Fig. 3. Element arrangement of the 6BN6 used as the sound limiter-discriminator.

one-half the no-excitation voltage.

I.F., Sound, and Video Circuits

The intermediate frequency amplifier in the Zenith "Super K" chassis is of the 40-mc. type, and consists of three transformer-coupled 6CB6 stages.

A crystal diode, X_1 , is used to rectify the video and sound i.f. signals. The two i.f. carriers beat together in the diode detector producing a 4.5-mc. carrier, which is FM sound modulated. Both the composite video and sync signal and the 4.5-mc. sound carrier are applied to the 12BY7 grid. The sync pulses are negative with respect to ground. When replacing a crystal diode, the correct polarity of connection must be observed, otherwise, a negative picture will be obtained and sync troubles will develop. The crystal may easily be reached for test or replacement by lifting the top of the

last i.f. transformer metal shield can.

Many of the condensers and resistors in the i.f. circuit are of 10% tolerance. When replacing these components, use the same tolerance as the original part.

The video amplifier uses a new type 12BY7 pentode, and is directly coupled to the picture-tube cathode. The contrast control is in parallel with the plate load and directly controls the picture-tube cathode signal level.

The 4.5-mc. FM sound carrier is taken from the junction of C_{33} and the secondary winding of L_{10} , and is fed to the 6AU6 sound limiter grid. From this stage the 4.5-mc. signal of between three and about four volts goes to the grid of the 6BN6 sound limiter-discriminator.

The sound discriminator circuit used in the "Super K" chassis is one of the simplest ever designed. No discriminator transformer is required; the entire circuit depends for its operation on the 6BN6 tube. The tube is unconventional in element structure, operating on electron optics principles. Fig. 3 shows the element arrangement of this gated-beam tube.

Electrons from the cathode are formed into a beam by the grounded focus electrode and the positive accelerator. This beam is passed through the limiter grid when the latter is at zero or positive potential. However, when it is negative, it stops the beam which falls back on the accelerator. Since the limiter grid merely acts as

a gate, passing or obstructing the beam formed by the focus and accelerator elements, the size of its positive potential is irrelevant. The same beam will be passed whether the voltage on the limiter grid is 1-volt positive or 10-volts positive, resulting in very effective limiting.

The electron beam leaving the limiter grid next passes through the second accelerator and screen and from there goes through the quadrature grid to the positive anode. The quadrature grid is tuned to the signal frequency.

When the limiter grid is positive (one-half of each cycle of the input signal), it passes the electron beam to the quadrature grid. The quadrature grid obtains its potential from the periodic variation in the space charge in front of it, which produces about 5 volts across its tuned circuit. This grid clips the leading portion from the half-cycle pulse and passes approximately a quarter-cycle pulse of current to the anode.


The phase displacement between the voltage on the quadrature grid and the electron beam is affected by the modulation of the signal frequency. This, in turn, affects the length of the anode current pulse. The d.c. voltage drop across the plate load resistor (which is bypassed for i.f.) is proportional to the length of this pulse, and therefore, to the original modulation of the input signal.

A 220,000 ohm resistor, R_{33} , and .047 μ fd. condenser, C_{33} , in the circuit of the quadrature grid places a bias voltage on this grid to improve the noise immunity of the circuit. The variable resistor, R_{34} , sets the operating point of the 6BN6 to eliminate the 60-cycle vertical pulse from the sound.

The composite video signal at the grid of the video amplifier is fed to the first signal grid of the 6BE6 sync clipper. The sync pulses fed to this grid are negative in polarity, and the bias on the grid is so adjusted by means of R_{35} , the "Fringe Lock" control, that the sync tips do not cut off plate current in the tube. The current in the tube is normally controlled by a positive polarity composite video signal fed to the second signal grid from the output of the video amplifier. This voltage drives the 6BE6 into both plate saturation and cut-off. Operating bias of the tube is set by R_{35} and C_{32} from grid current drawn while signal voltage is applied, so that the sync pulse is clipped just above the black level. However, when a burst of noise appears in the composite video signal, the first signal grid is driven to cut-off, so that this noise does not appear in the output of the tube. Although the sync pulses may also be eliminated by this action, the oscillator continues on the flywheel effect, and will resync when the sync pulses reappear.

The sync pulses next go to the integrator and differentiator networks (Continued on page 106)

Fig. 4. Representative chassis layout for the Zenith "L" series TV receivers. Note the alternative focus and centering method used in some models (dotted).

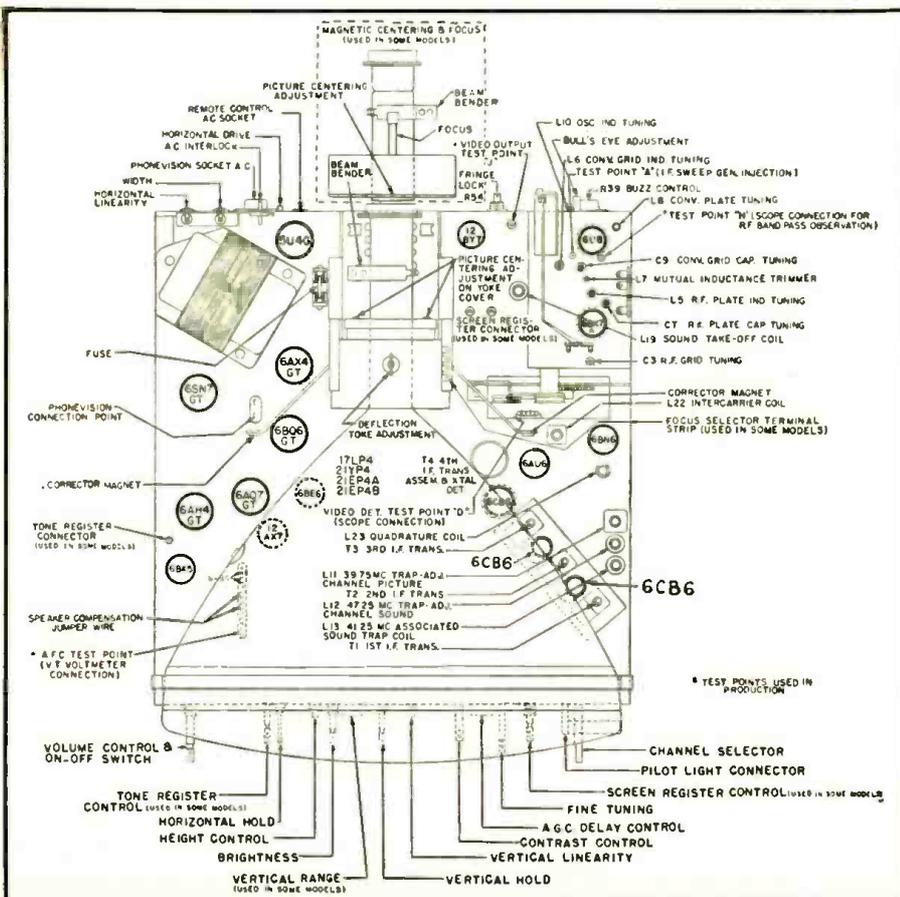

A SQUARE-WAVE SHAPER



By **GEORGE ELLIS JONES, JR.**
Dept. of Chemical Engineering
University of Pittsburgh


NOT ONLY will the use of square waves speed tests which can be made with other types of signal generators, but certain tests can be made using square waves that could not be made at all using sine waves. Transient response of an amplifier can be rapidly established by driving the amplifier with a square wave and observing its output with an oscilloscope. An additional use, not often discussed, is in the checking of tone control circuits. When the treble and bass controls are so adjusted that a 1000 cps square wave looks good and the best possible 100 and 10,000 cycle square waves are obtained, the tone controls are in their flat position.

The technician or experimenter who realizes the convenience of square-wave testing usually already has a sine-wave generator. The construction or purchase of the ordinary square-wave generator causes a duplication of parts and, generally, poorer performance than can be obtained by using a square-wave generator of the type described here. Most square-wave generators use a multivibrator circuit to develop a square wave of sorts which is then clipped and amplified. Frequency stability in such generators is notoriously bad. Furthermore the steep wavefronts are often slowed down and rounded off because the multivibrator circuit must suddenly charge or discharge the larger condensers necessary for timing the relatively long level sections of the square wave.

The unit which the author has designed amplifies and clips a sine wave input (derived from an external sine-wave generator) with one duo-triode stage. Further amplification and isolation is provided by a video-amplifier stage and a cathode-follower output stage. Fig. 1 is the schematic diagram of the unit. Waveforms appearing at various key points within the generator are shown in Fig. 2.

For those of us who generally work with class A amplifiers where the objective is to have the output waveform an enlarged version of the input waveform, complete and accurate in all detail, a stage-by-stage analysis of

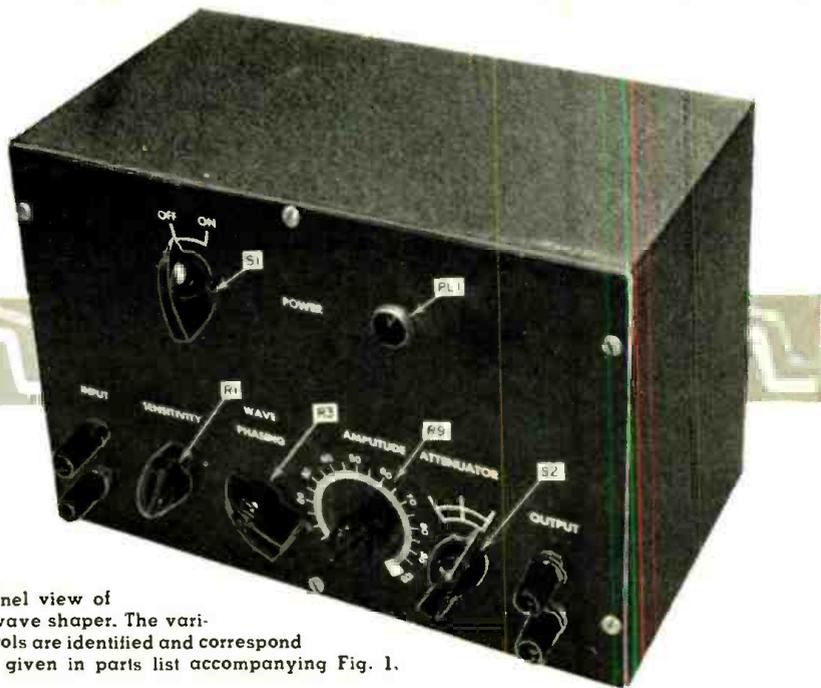Front panel view of square-wave shaper. The various controls are identified and correspond to those given in parts list accompanying Fig. 1.




The design, construction, and operation of an audio test unit which can be used in conjunction with a sine-wave generator.

this generator should prove interesting. Here each stage is driven either to cut-off or to grid current, and some of the tubes are driven from the one extreme to the other.

The amplifier tube V_{1B} is driven at both its cathode and its grid by V_{1A} in such a way that the two drives augment each other. When the grid

voltage of V_{1A} rises above some critical value (which is determined by the size of the cathode resistor, R_c) V_{1B} suddenly cuts off. When the V_{1A} grid voltage drops again, V_{1B} starts with equal rapidity to conduct again. Thus the sine-wave input (for all practical purposes) switches V_{1B} off
(Continued on page 116)

Fig. 1. Complete schematic diagram of the square-wave shaper built by the author.

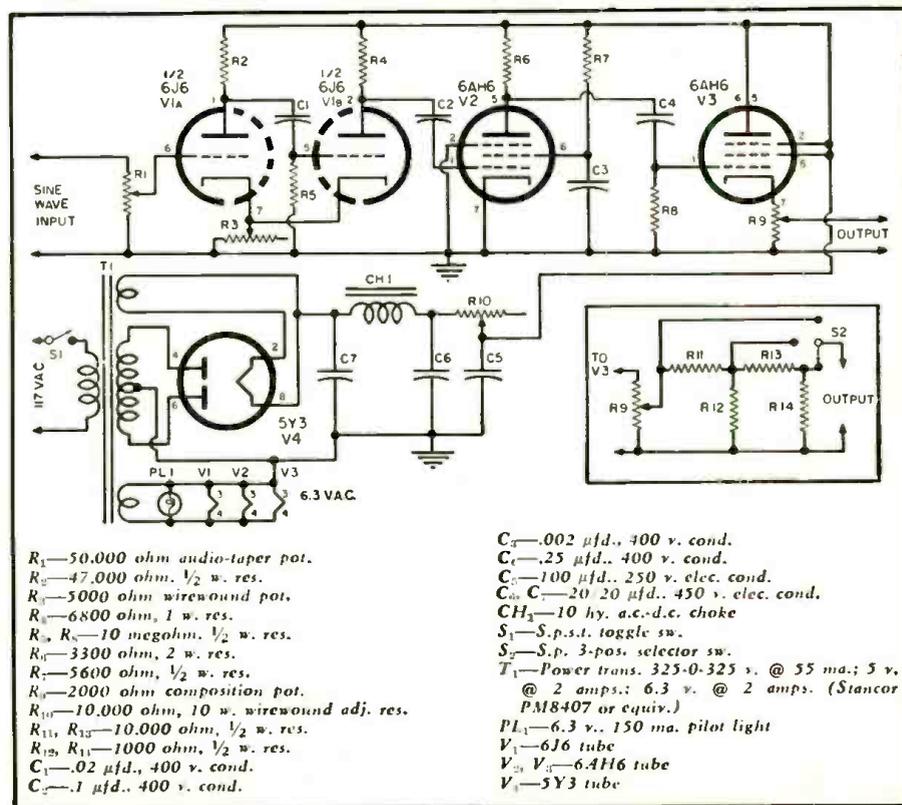

SELENIUM DIODE APPLICATIONS

By
J. T. CATALDO
 International Rectifier Corp.

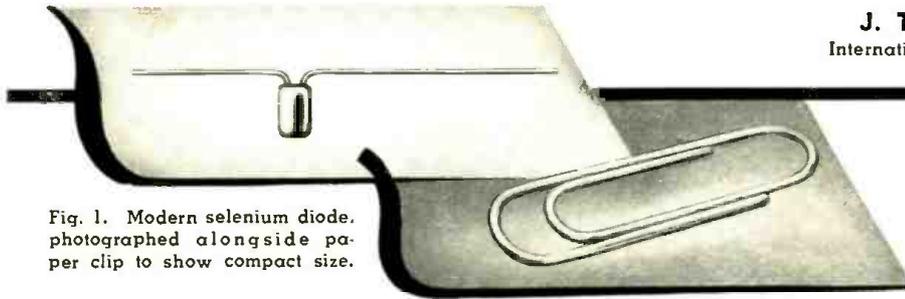


Fig. 1. Modern selenium diode, photographed alongside paper clip to show compact size.

The development of the selenium diode opens a whole new field of circuit design possibilities to the engineer.

THE development of the selenium diode offers the electronic design engineer a series of semi-conducting components heretofore not available. These units were developed, in part, to help fill the ever increasing demand for miniature diodes of the metallic family which was created with the advent of electronic computers and miniaturized equipment of all types. Germanium and silicon diodes were used almost exclusively in computers as well as in other electronic equipment such as hearing aids, electronic organs, bias supplies, sensitive d.c. relays, TV and radio receivers. Manufacturers have been sponsoring research and development activities since the first commercial production of selenium rectifiers. The development of the selenium diode, shown in Fig. 1, is the result of the progress made to date in the effort to miniaturize selenium rectifiers. The diode is photographed with a paper clip for comparison purposes.

Initial efforts to produce small rectifier cells were not very encouraging

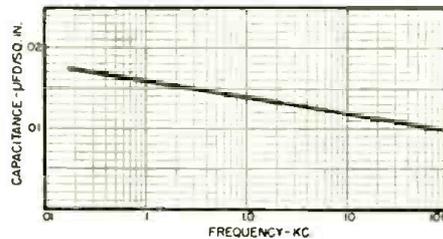


Fig. 2. Capacitance versus frequency curve.

because the many intricate and complex production processes were not well understood. However, with the gradual and continued improvement and control of production techniques and processes, a few selenium rectifier manufacturers started producing miniature rectifier cells. These small cells were assembled into various types of enclosures. A few of the many types of rectifiers produced are shown in Fig. 3. These units, although exceedingly satisfactory for many applications, were limited insofar as their frequency response is concerned. Unlike the silicon or germanium diode,

the selenium rectifier is an area type semi-conductor. As such, the selenium rectifier possesses a self-capacitance which is on the order of 0.018 microfarad per-square-inch at a frequency of 60 cycles-per-second. In Fig. 2 are plotted capacitance test data of an 0.250 inch diameter selenium rectifier cell in microfarads per-square-inch versus frequency. From this curve, the self-capacitance of an 0.250 inch diameter cell is calculated to be 500 $\mu\text{fd.}$ at 100 kc. and 900 $\mu\text{fd.}$ at 60 cycles. Since the capacitance of a selenium rectifier is a function of its area, it is obvious that reducing the area of the cell would, in turn, decrease the self-capacitance. Large scale production of smaller diameter cells was accomplished after continued research resulted in resolving the many difficulties previously encountered. Consequently, it is now possible to produce rectifier cells having an area of 0.003 square inch as compared to previous small cells having an area of 0.05 square inch. A decrease of capacitance of as much as 16 to 1 has been achieved by this reduction in rectifier cell size. The decrease of self-capacitance permits the use of these selenium diodes in circuits operating in a frequency range of 100 kc. to 200 kc. These research and development activities also resulted in operational improvements such as extreme stability and long life in high ambient temperatures and adverse environment conditions normally encountered in military applications. The resulting improvements are attributable to modifications made in several manufacturing processes and to the complete encapsulation of the rectifying element within a thermo-setting plastic.

Characteristics and Specifications

The present line of selenium diodes consists of three series: Series S, Series T, and Series U. The units are provided with pigtail leads to facilitate wiring into crowded chassis. Their small size (see Table 1 for dimensions) makes them ideal for use in electronic equipment where space is limited. They do not require any additional support because of their light weight.

The d.c. output current rating is 100 microamperes, 200 microamperes, and 1.5 milliamperes for the Series S, T, and U respectively. The Series S and T are produced for output voltages of 20 and 40 volts, while the

Table 1. Specifications on the Series S, Series T, and Series U selenium diodes.

	1S1	2S1	1T1	2T1	1U1	2U1	3U1	4U1	5U1	
Rated Forward Current	100 $\mu\text{a.}$	100 $\mu\text{a.}$	200 $\mu\text{a.}$	200 $\mu\text{a.}$	1.5ma.	1.5ma.	1.5ma.	1.5ma.	1.5ma.	
Max. Applied Voltage (r.m.s.)	26 v.	52 v.	26 v.	52 v.	26 v.	52 v.	78 v.	104 v.	130 v.	
Max. d.c. Output Voltage	20 v.	40 v.	20 v.	40 v.	20 v.	40 v.	60 v.	80 v.	100 v.	
Peak Inverse Voltage	60 v.	120 v.	60 v.	120 v.	60 v.	120 v.	180 v.	240 v.	300 v.	
Max. Surge Current (in ma.—1 sec.)	5	5	10	10	80	89	80	80	80	
Voltage Drop at Full Load	1 v.	2 v.	1 v.	2 v.	1 v.	2 v.	3 v.	4 v.	5 v.	
Max. r.m.s. Input Current	250 $\mu\text{a.}$		500 $\mu\text{a.}$		3.75 ma.					
Peak Rectified Current (in ma.)	1.3		2.6		20					
Reverse Current at Max. Applied Voltage	6 $\mu\text{a.}$		6 $\mu\text{a.}$		27 $\mu\text{a.}$					
Reverse Current at	-10 v.	-20 v.	-10 v.	-20 v.	-10 v.	-20 v.	-30 v.	-40 v.	-50 v.	
	.6 $\mu\text{a.}$.6 $\mu\text{a.}$		2.4 $\mu\text{a.}$					
Shunt Capacity at Max. Frequency	57 $\mu\text{fd.}$	29 $\mu\text{fd.}$	57 $\mu\text{fd.}$	29 $\mu\text{fd.}$	140 $\mu\text{fd.}$	70 $\mu\text{fd.}$	50 $\mu\text{fd.}$	35 $\mu\text{fd.}$	25 $\mu\text{fd.}$	
Max. Frequency	200 kc.		200 kc.		100 kc.					
Ambient Temperature Range:	-40 to 100 degrees C.									

Series U is available for output voltages of 20, 40, 60, 80, and 100 volts at rated output current. Higher output voltages are attainable with these selenium diodes at reduced output current. Static forward and reverse characteristics for the three available series are shown in Fig. 6. The characteristics shown are for the Type 1S1, Type 1T1, and Type 1U1. However, these curves are also applicable to the other diodes if the forward voltage and reverse voltage scales are multiplied by 2, 3, 4, or 5. For example, the Type 5U1 would have a maximum forward voltage drop of 6.0 volts when it is delivering an output current of 1.5 milliamperes. The characteristics in Fig. 6 are the minimum acceptable quality level for these diodes. Units in production all have characteristics well within the limits shown in Fig. 6. In other words, lower forward voltage drop and lower reverse currents can be expected of selenium diodes from regular production runs. Examination of this figure will disclose that a minimum forward-to-reverse resistance ratio of 5000 to 1 is obtainable when the reverse voltage on the unit is not more than 20 volts for the single cell units. This ratio is also attainable with a reverse voltage of 100 volts on the Type 5U1.

Forward voltage drop versus ambient temperature characteristics for various loads on a basic bridge are shown in Fig. 4. The bridge consisted of four Type 1T1 selenium diodes, one in each arm. The input voltage or voltage drop across the bridge was recorded for loads of half-, one-, and four-times rated for ambient temperatures of 0 to 100° C. Since selenium has a negative-temperature coefficient, a lower voltage drop exists at elevated temperatures. It will also be noted that the slope of the curves decrease with decreasing load.

These selenium diodes are being used in many novel circuits. An interesting application is as a clamping diode in a telemetering circuit, shown in Fig. 5. The purpose of this circuit in the telemetering equipment is to convert a signal voltage of fixed phase with the reference voltage into a d.c. voltage of 0-5 volts that is proportional to the amplitude of the signal voltage. In operation, the rectifier SR₁ rectifies the a.c. voltage existing at the cathode of the tube, V₁. Since there is no control on the magnitude of the input signal, the output voltage can exceed 5 volts thereby causing malfunctioning of the telemetering circuit. To preclude this condition, a Type 1U1 selenium diode is incorporated into the circuit as a clamper. With a clamping potential of 4.3 volts, clamping occurs when the output reaches 5 volts. In Fig. 5, SR₁ is an International Rectifier Corp. #V1HM rectifier and SR₂ is a 1U1 type. The circuit was supplied by the Raymond-Lindsey Co. of Gardena, Calif.

There are many other applications for these units. For example, the diodes have been designed into hearing

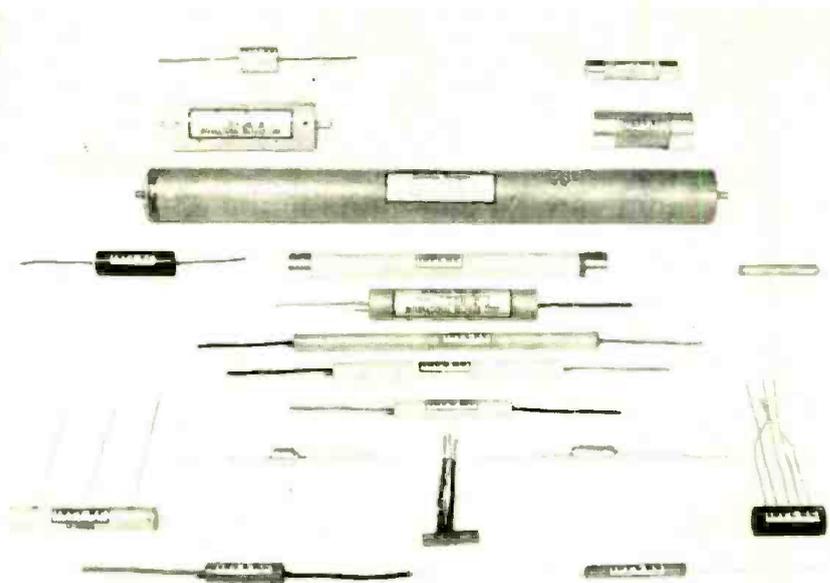


Fig. 3. Typical cartridge-type selenium rectifiers as made by International Rectifier.

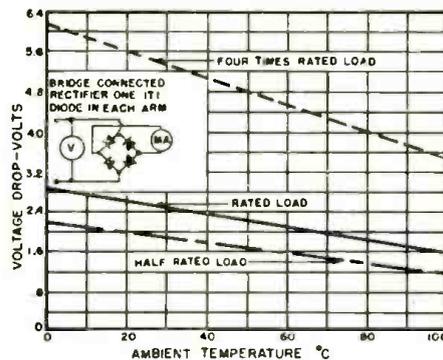


Fig. 4. Forward voltage drop vs ambient temperature characteristics for basic bridge.


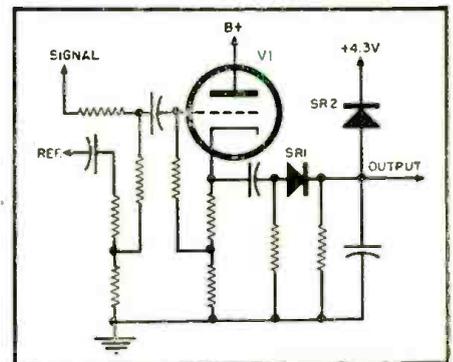


Fig. 5. Telemetering circuit showing selenium diode used for the clamping action.

aids, electronic organs, and numerous electronic instruments. The circuits of these applications cannot be disclosed at this time, since their disclosure may jeopardize certain patentable features. The most popular usage for

these diodes is to provide bias voltage in electronic equipment. Fig. 7 shows a typical application for providing fixed bias for the push-pull stage of an audio system. It is well to note that
(Continued on page 149)

Fig. 6. Static forward and reverse characteristics of Types 1S1, 1T1, and 1U1 diodes.

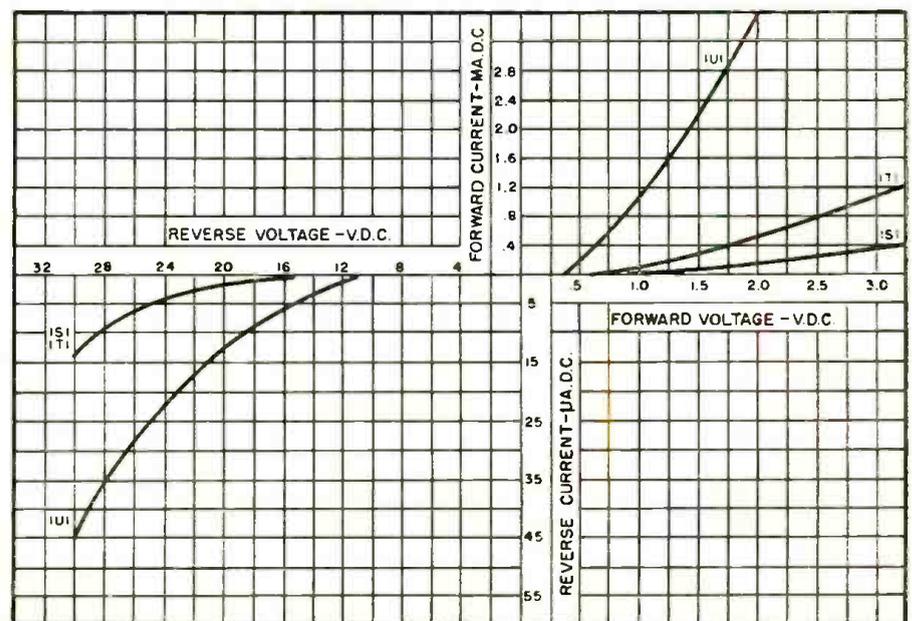

OBTAINING TRANSISTOR CHARACTERISTIC CURVES

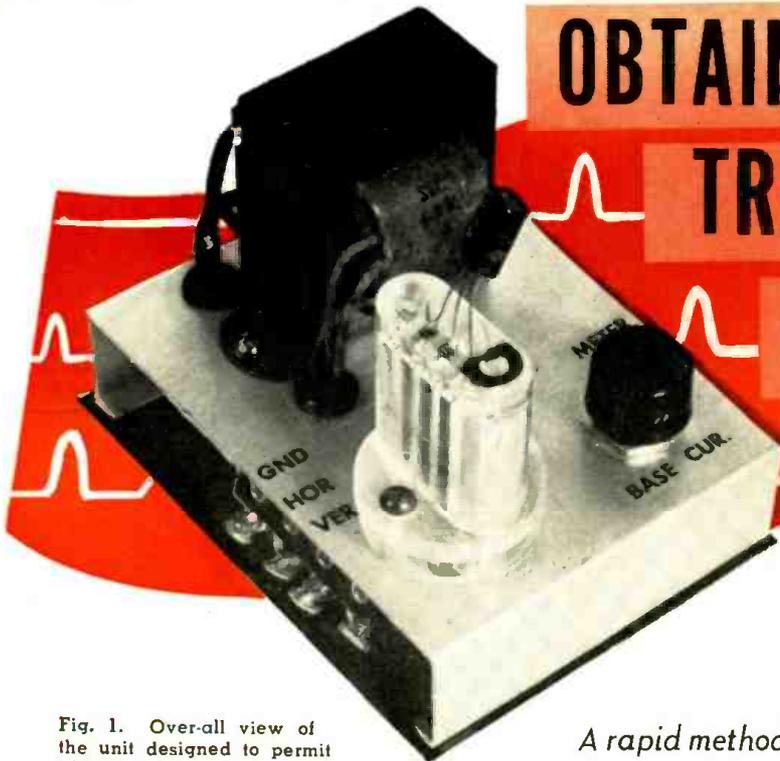


Fig. 1. Over-all view of the unit designed to permit plotting of transistor curves.

THE usual technique for obtaining a characteristic curve for a vacuum tube, transistor, or crystal diode is to set up the basic experimental circuit in breadboard fashion, making provision for both fixed and variable voltage sources. Where more than one voltage source is required for the particular characteristic curve desired, it is general practice to fix all voltage sources but one, then to vary that voltage in small increments, noting any variations in current.

In the case of a transistor, for example, a fixed base current may be allowed to flow, with the collector voltage varied over a range and changes in collector current noted. A number of "check" points may be obtained and the resulting data tabulated.

After a series of measurements have been completed, the resulting data might be plotted on a conventional graph scale, giving a "collector voltage vs collector current characteristic curve" for the particular transistor checked, and for the specific base current. If several complete sets of measurements are made, with different base current values, the resulting series of graphs, plotted on the same scale, represent a "family" of characteristic curves.

As can be easily seen, considerable time might be required to obtain sufficient experimental data to plot even a small "family" of curves. Where a number of individual transistors are to be checked, obtaining the experimental data alone may well represent many man-hours—with still more time required to plot the curves.

However, by using the small instru-

ment illustrated in Fig. 1, it is possible to obtain an accurate characteristic curve in less than a minute's time, including the time required for "setting up" the equipment! With proper accessory equipment, a complete "family" of curves can be obtained in well under five minutes' time!

Circuit Description

The complete schematic diagram of the "transistor waveform tracer" is given in Fig. 2. The meter M_1 is external to the small chassis shown in Fig. 1 and is connected to it with the leads identified by the word "Meter" on the chassis.

In operation, B_1 , a small penlight cell, supplies the desired base current

for the transistor, with the exact amount of base current adjusted by means of series resistor, R_1 , and indicated on the meter.

A pulsating d.c. voltage is applied between the emitter and collector terminals. This voltage is obtained by rectifying a 6.3 volt a.c. signal which is obtained, in turn, from the secondary of filament transformer T_1 . A half-wave selenium rectifier, $Rect. 1$, is employed.


A small resistor, R_2 , is connected in series with the collector terminal. The value chosen for this resistor (100 ohms) is low enough so as not to affect circuit operation. Since the voltage across any resistor is directly proportional to the current through it, observing the voltage waveform across R_2 gives an exact indication of the variations in collector current.

In practice, the pulsating voltage applied between the emitter and collector of the transistor is applied to the horizontal terminals of an oscilloscope. This gives a horizontal sweep directly proportional to variations in collector voltage.

The voltage across R_2 is applied to the vertical input terminals of the oscilloscope, giving a vertical deflection directly proportional to the variations in collector current.

The waveform of the pulsating voltage applied to the collector-emitter circuit is shown in Fig. 3, and can be observed by transferring the "Hor. Input" lead shown in Fig. 2 to the vertical input terminals of the scope and using the built-in linear sweep. However, when obtaining characteristic curves, the built-in sweep of the scope is not used. Be

Fig. 2. Complete circuit diagram of unit for checking transistor characteristics.

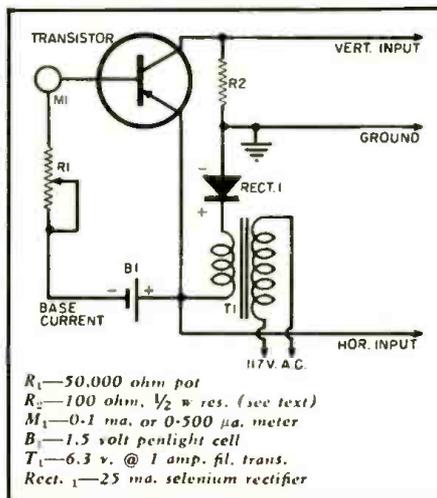

sure that the horizontal amplifier is switched to "Hor. Input."

Typical characteristic curves obtained by using this technique are illustrated in Figs. 4A and 4B. Fig. 4A was obtained using a base current of 100 microamperes, while Fig. 4B represents the curve obtained with a base current of 20 microamperes.

Construction Hints

The average technician should have no difficulty in assembling the circuit illustrated in about two or three hours' time and most of this time will be expended in laying out and drilling the small chassis. Where "breadboard" type construction is used, the entire circuit can be assembled and wired in less than an hour's time.

Terminals are provided for making the oscilloscope connections and two leads are brought out for the panel meter which is used to indicate base current.

All other components, including the penlight cell, are mounted directly on the small chassis shown. The chassis used by the author is a standard Bud CB-1617 chassis, but any small chassis base is suitable.

The transistor socket used in the model shown is a special unit and is not generally available commercially. However, the prospective builder may use any one of several substitute methods: a standard subminiature tube socket, a terminal strip to which temporary soldered "lap" joints may be made, a screw-type terminal strip, or even permanently-mounted spring clips to which quick connections of the transistor leads may be made.

No special pains need be taken in wiring the unit. However, if the transistor is to be soldered in position, care should be taken that the transistor leads are not overheated.

Circuit Modifications

The model shown in the photographs and in the schematic diagram is designed to obtain characteristic curves when used with Raytheon junction transistors of the *p-n-p* type over fairly limited changes in collector voltage. Where greater changes in collector voltage are desired, simply substitute another transformer for T_1 , which will provide a greater secondary voltage, for example, a 12.6 volt or a 25.2 volt transformer may well be used here.

If the engineer or experimenter wishes to obtain characteristic curves of the same type for point-contact transistors, the same basic circuit arrangement may be used, but with the necessary modifications in T_1 , as mentioned previously.

Where junction transistors of the *n-p-n* type are used, reverse the connections to the battery, B_1 , and to the selenium rectifier. This is necessary to insure that the proper voltages are applied to the transistor elements.

Although the circuit arrangement shown in Fig. 2 supplies collector current vs collector voltage characteristic curves, other types of curves may

be easily obtained by making minor variations in the circuit connections. For example, the pulsating voltage might well be applied between base and emitter, with a fixed voltage applied between emitter and collector. Any number of variations are possible, depending on whether "grounded-base", "grounded-emitter", or "grounded-collector" circuits are employed and upon which voltages (or currents) are made the independent variable.

However, whenever changing to different circuits, make sure that the polarity of the voltage connections is correct for the type of transistor being checked and for the type of characteristic curves desired.

The oscilloscope and meter connections are apparent in the schematic diagram (Fig. 2). A typical experimental set-up is shown in Fig. 7.

Once the proper connections have been made and the transistor connected in the circuit (or inserted in its socket), R_1 is adjusted for the desired base current, as indicated on meter M_1 . The "Vert. Gain" and "Hor. Gain" controls of the oscilloscope are adjusted until the desired image size is obtained.

The resulting characteristic curve (see Figs. 4A and 4B) is suitable for experimental study and school demonstration work. Where the curves obtained are to be used for engineering work, one or two additional steps are required in "setting up" for tests, however.

A transparent graph scale should be placed over the screen of the CRT and the "Vert. Gain" and "Hor. Gain" adjusted for a known amount of gain. In other words, the scope is "calibrated" so that the characteristic curve obtained may be actually checked in terms of milliamperes current and amount of applied voltage.

This calibration procedure is quite simple, and consists of applying a

(Continued on page 130)



Fig. 3. Waveform of a pulsating voltage applied to the collector-emitter circuit.

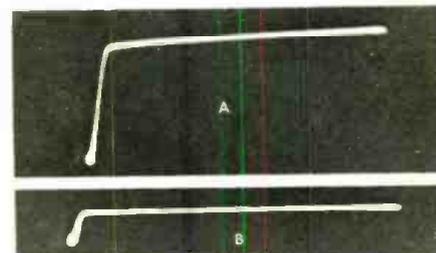


Fig. 4. Characteristic curves obtained with (A) base current of 100 microamperes, and (B) with base current of 20 microamperes.

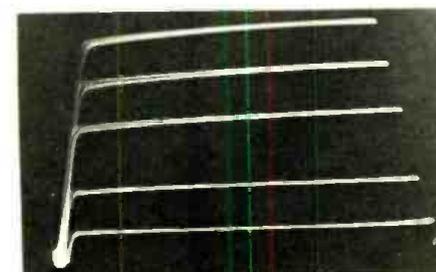


Fig. 5. Family of collector current vs collector voltage curves for Raytheon CK722 at base currents of 25, 50, 100, 150, and 200 microamperes respectively (bottom to top).

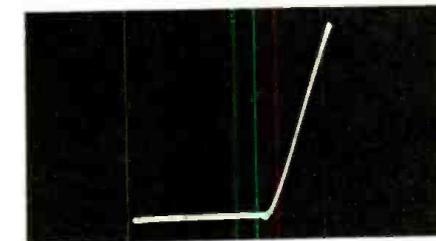


Fig. 6. Characteristic curve of a germanium diode which was tested with same circuit.


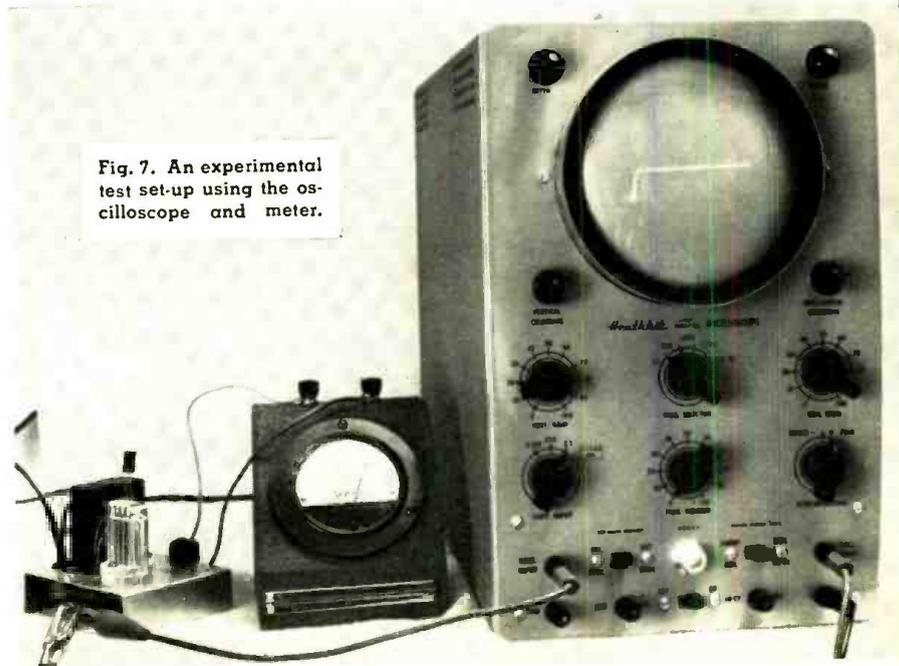


Fig. 7. An experimental test set-up using the oscilloscope and meter.

A TRANSISTORIZED AUDIO OSCILLATOR

Fig. 1. "Light-powered" audio oscillator which is housed in tiny pill box.

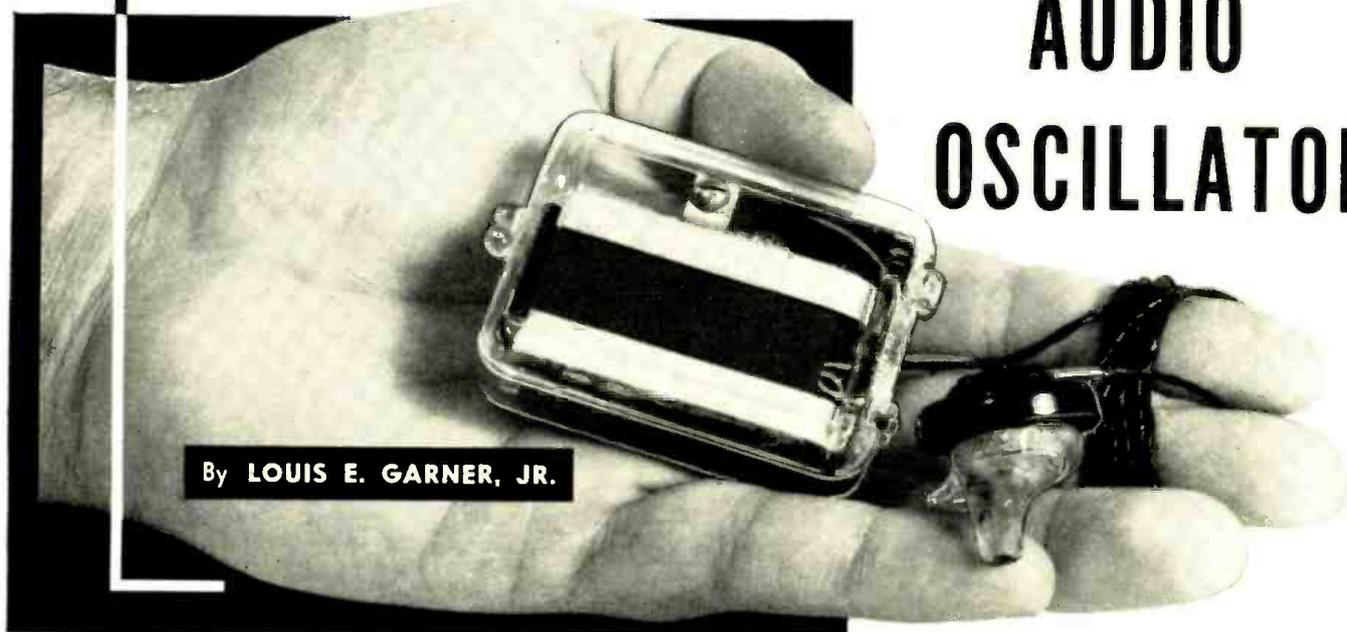

By LOUIS E. GARNER, JR.

A miniature test unit which requires neither batteries nor power lines. It has several unique service applications.

MOST electronic and electrical devices have one circuit in common—the power supply. In some cases, the power supply consists of one or more batteries, and may include additional components such as a vibrator, transformer, rectifier, and filter components. In other cases, the equipment is "line-operated," and the power supply may include a power transformer, rectifier (whether a vacuum tube or "dry disc"), and filter components.

But the audio oscillator shown in Fig. 1 (together with its small earphone) is completely self-contained and requires neither batteries nor "line plug-in" for operation! *All that is required for operation is for a reasonable amount of light to fall on its face.* While not quite "something for nothing," it is a close approach.

The unit shown is not an expensive "laboratory device" but a practical piece of equipment that can be easily duplicated by almost any technician or experimenter.

Its design and construction has been made possible by utilizing two semiconductor devices—a self-generating selenium photocell and a Raytheon type CK722 junction transistor.

Circuit Description

The complete schematic diagram for the *light-powered oscillator* is given in Fig. 2, while an interior view of the unit is shown in Fig. 3.

Referring to the schematic diagram, the transistor collector is connected

to the primary of a small "Sub-Ouncer" transformer, T_1 . The return lead is connected to the "negative" terminal of the self-generating photocell, PS .

The transformer secondary winding is connected between the transistor emitter and, through coupling condenser C_1 , to the transistor base. R_1 serves as a "base return" resistor and is connected to the negative terminal of the photocell.

An output signal is obtained through coupling condenser C_2 and applied to a standard crystal earphone, the lower lead of which connects directly to the transistor emitter. The "positive" terminal of the photocell is also connected to the transistor emitter.

In operation, light striking the photocell generates sufficient voltage to drive a small current through a low impedance load (the maximum current obtained with the photocell shown does not exceed a few hundred microamperes).

This current flows over two paths. Part of the current flows through the R_1 and base-emitter path, establishing the "bias current" for the transistor. Another part of the current flows through the primary of T_1 and the collector-emitter path.

As is readily apparent, the transistor itself is connected in a modified "tickler feedback" grounded-emitter oscillator circuit, with feedback obtained through the primary and secondary winding of T_1 . Current varia-

tions in the primary winding cause a.c. variations in the secondary winding through magnetic coupling. The signal thus developed in the secondary is applied to the base-emitter circuit of the transistor, where amplification takes place, resulting in further variations in the primary current (since this is equal to the collector current).

The oscillation obtained continues as long as sufficient light falls on the photocell.

With the parts values shown, there is a certain amount of "blocking oscillator" action, with the result that the frequency of operation varies with large changes in the amplitude of light falling on the photocell (and hence with changes in the amount of generated current). When the model shown is held in sunlight and gradually turned so that greater amounts of light strike the photocell, the tone gradually increases in pitch, then suddenly changes over to a low frequency "buzz."

Good results can be obtained under incandescent lights, but when the unit is used under fluorescent lamps, the 60-cycle line buzz modulates the normal signal, with the result that a "buzz" is heard in the earphone.

Construction is fairly straightforward and no particular difficulty should be encountered by the skilled technician. However, a few special suggestions appear to be in order.

The author's model has been assembled and wired in a small plastic box (an old "pill box"). As is easily seen in the interior view, Fig. 3, the inside of the box is mostly "empty space." If a smaller plastic box had been available at the time of construction, the entire unit could have really been "miniaturized."

Either a larger or smaller case may be used by the builder, as he prefers. However, two points should be kept in mind when selecting the case—first, it should be large enough so that the photocell used can be easily mounted. Secondly, if the builder plans to mount the photocell inside the case (as the author did), the case should be of clear (transparent) plastic.

This brings up an important point—obtaining the photocell. All parts used in constructing the small unit are commonly available and can be obtained from the majority of wholesale electronics parts distributors—except the photocell. Two possible sources of supply are open to the experimenter, (a) he can salvage a unit from a discarded or used photographic exposure meter, and (b) he can watch for “surplus” sale ads, where these units are sometimes offered at low prices. (*Concord Radio*, of New York, recently offered similar photocells at less than one dollar each.)

Once the photocell has been obtained, the polarity of lead connections must be identified. If these connections are not already marked on the photocell, a 0-1 ma. or 0-500 microammeter should be connected to the photocell and the unit held under a reasonably strong light. By noting whether an “up-scale” or “down-scale” deflection is obtained, the lead polarity can be quickly determined.

In the unit used by the author, the rear surface was positive and two narrow strips on the front (or light-sensitive) surface formed the negative terminals.

When mounting the photocell, make sure that the light-sensitive surface faces in the proper direction. Also make sure that positive contact is made to the photocell terminals. This contact is preferably made through spring surfaces (phosphor bronze is good material to use for this). No attempt should be made to solder directly to the photocell unless special terminals are provided for this on the unit itself.

Although the transistor could be wired directly into the circuit, using its leads, it is suggested that a standard 5-pin subminiature tube socket be used instead, as shown in the model. This step is necessary because the short lead lengths used in subminiature wiring might result in the transistor being overheated during soldering.

However, if the builder does not have the proper socket available, and cannot easily obtain one, the transistor may be soldered into the circuit if special care is taken to hold each transistor lead during soldering with a pair of flat-nosed pliers (the pliers should be on the “transistor side” of the soldered joint).

Both the transistor socket (where used) and the “Sub-Ouncer” transformer may be mounted simply by cementing them to the plastic case, using either “Duco” cement or any

general-purpose radio service cement.

Other parts are supported on their own leads.

Adjustment

Once the wiring is completed, the unit should be checked for operation by placing the earphone in the ear and holding the completed oscillator near a reasonably strong light source so that light falls directly on the photocell.

If oscillation is not obtained, try varying the size of R_1 . If necessary, a 250,000 ohm potentiometer may be temporarily connected in place of this resistor and an adjustment made. The value is then checked and a fixed resistor of approximately the same value permanently connected in place.


Should it be impossible to obtain oscillation, even by varying the size of R_1 , reverse the transformer secondary leads (the two black leads, Fig. 2) and again check for oscillation. If necessary, again try varying the size of R_1 .

Where the last step does not permit oscillation to be obtained, it may indicate that the photocell is defective or “weak.” Check this unit for operation by connecting a 0-1 ma. or a 0-500 microammeter across it and holding the unit under a strong light source; a current of at least 50 to 100 microamperes should be obtained, with as high as several hundred microamperes obtained from a really sensitive cell.

In an extreme case it may be necessary to try another transistor, but, in general, this should not prove necessary. The author tried this circuit with a number of different transistors (of the same type) and obtained satisfactory results in every case.

Applications

While the light-powered audio oscil-

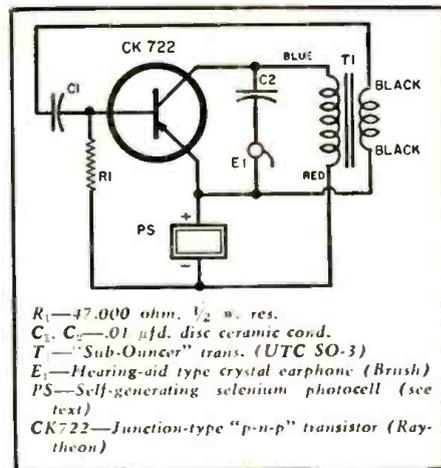

R_1 —47,000 ohm, $\frac{1}{2}$ w. res.
 C_1, C_2 —0.01 μ f. disc ceramic cond.
 T_1 —“Sub-Ouncer” trans. (UTC 50-3)
 E_1 —Hearing-aid type crystal earphone (Brush)
 PS —Self-generating selenium photocell (see text)
 $CK722$ —Junction-type “p-n-p” transistor (Raytheon)

Fig. 2. Schematic of audio oscillator unit.


lator, as shown in the photographs, is basically an experimental “gadget,” the unit does offer a number of practical applications. For example, by providing a hand-key in the emitter circuit, the unit could be used as an extremely compact and inexpensive-to-operate code-practice oscillator.

The unit could also be used by a blind person to determine if a room is lighted or dark. Since the tone pitch varies somewhat with light intensity, this would provide some indication as to the amount of light in a room and as to the light sources.

In addition to the applications of the audio oscillator, the use of “light-power” suggests many other possibilities. The author plans to eventually construct a small light-powered transmitter, a receiver, and possibly a small audio amplifier.


The reader can undoubtedly think of many additional applications of the light-powered audio oscillator, as well as other more general applications of light-powered “electronic” equipment.

Fig. 3. Internal view. Unit can be constructed in even smaller cabinet if desired.

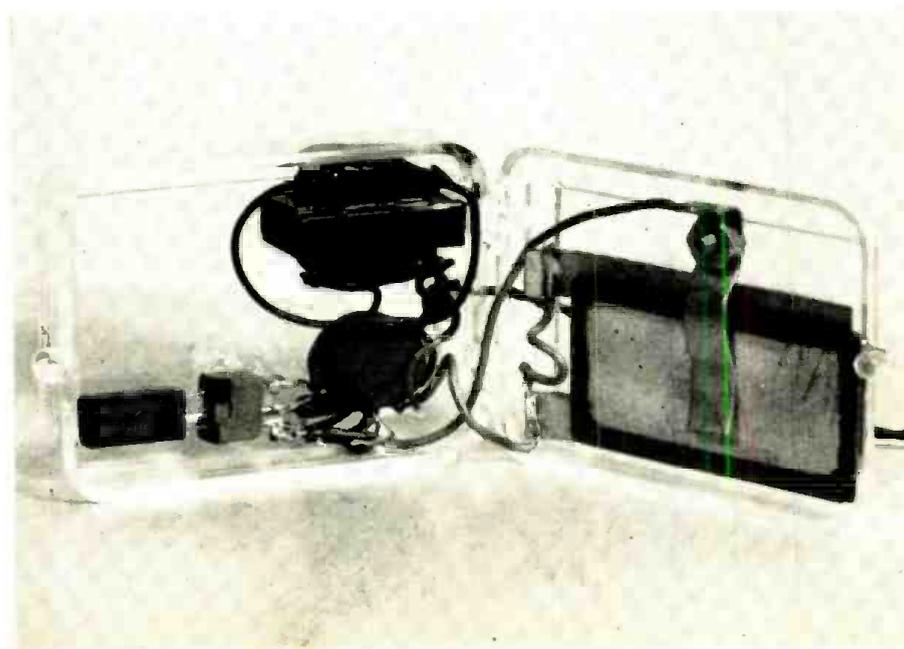

AUTOMATIC INPUT SWITCHING WITHOUT RELAYS

By ALLAN M. FERRES

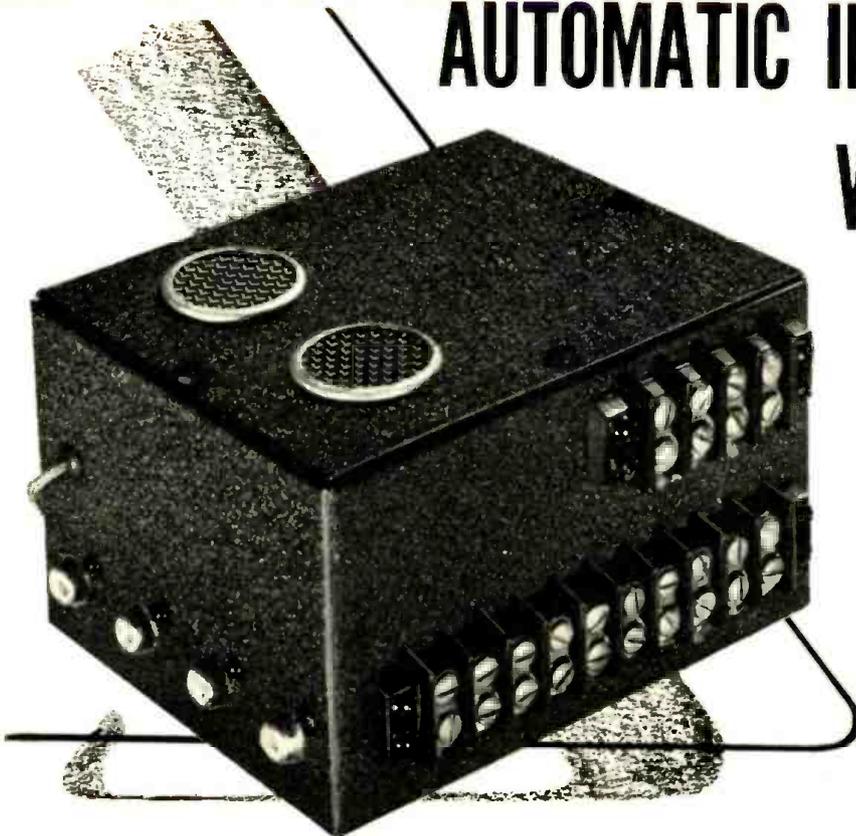

Over-all view of control unit. It is housed in 3" x 4" x 5" steel utility can. See text.

Construction details on a novel input control circuit for switching in the desired source—tuner, phono, TV, etc.

TOO many knobs" . . . and "I don't know how to work it" . . . "It's too complicated". If anyone in your family ever says these things about your radio/phonograph installation, then you are not getting full value from your investment in high-fidelity. Every member of the family should be able to enjoy it when they want to and so obtain from it the many hours of pleasure a really good system can furnish.

The "automatic input selector" can help you make the operation of your equipment easier. Here is how it was used in one fairly typical installation which was being re-designed with simplified operation in mind.


The equipment was installed in a deep-shelved bookcase built against one wall of the living room. The record player was placed on one open shelf a convenient forty-five inches from the floor, with the space below it containing the speaker and its housing. An AM tuner, an FM tuner, and the equalizing preamp were on another shelf of the same height.

Two open shelves below them were used for records and the bottom shelf was provided with doors to conceal the speaker crossover network, main amplifier, and power supply. Ten knobs and two switches were in daily use on the tuner/preamp shelf. All

the controls except those for the AM and FM tuners were grouped together on the preamp/control panel, each control essential, but the seven knobs in a row discouraged all but the technically-minded members of the family. The knobs lined up this way: on the AM tuner—"on-off" and volume and a tuning knob. On the FM tuner—volume, "on-off", tuning knob. On the preamp/control panel—input selector, bass, treble, low-frequency turnover, high-frequency cut, volume, "on-off" switch, and pilot light.

To reduce the number of controls, two methods of attack were used. The

Fig. 1. How the various components in the home entertainment system are connected into the automatic input switching unit.

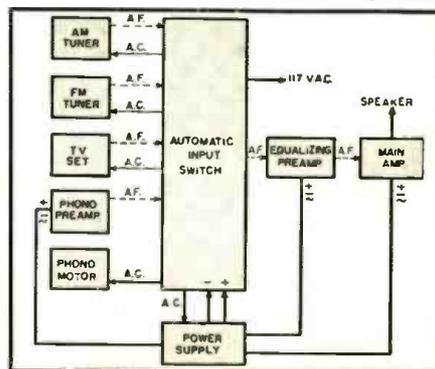

first was to have one knob serve two functions wherever possible and the second was to place specialized controls on the unit with which it was used. An example of both methods was to combine the low-frequency turnover and the high-frequency cut adjustments, which were used only for records, on one six-position switch and mount it alongside the record player. All this entailed was to build the phono preamp on its own two by two by four chassis instead of combining it with the equalizing/control preamp, and mounting it under the motor board so that the equalizer switch would appear near the back of the pickup arm. From an experimental viewpoint, it had the advantage of being readily available for modifications without the need for putting any other equipment out of service while it was being worked on. From the family's point of view, its location made it obvious that it needed manipulation only when records were being played.

The AM and FM tuning knobs on the separate tuners defied changing, for even if a combination AM/FM tuner were used, a bandswitch would be needed which still meant two knobs here.

Bass and treble controls still had to be separate, but if the input to the equalizing preamp could be selected automatically when the desired music source was turned on, one more control could either be eliminated or moved to a less crowded spot. It would, of course, be possible to use the input selector to turn on each input source as required, but with the tuners and the record player arranged as they were, the former method resulted in more logical operation. If another input source, such as a TV set or tape recorder, were located at a distance from the main installation, the reason for choosing this method would be even more obvious. As the only unusual item in the simplified installation was the automatic input selector, it is described here. The general arrangement is shown in Fig. 1.

The automatic input selector could have been included in the equalizing preamp, but it was made up on a separate chassis to reduce the extent of crippling of the whole system when future modifications were in order. As a separate unit, it can be readily

added to existing installations with only minor changes in each input source. Relays could have been used to select the desired input which was to be fed into the rest of the system, but by using the cathode followers, the distance between the selector and the equalizing preamp could be greatly extended without loss of high-frequency response or increase in susceptibility to hum pickup without additional complications.

The circuit (Fig. 2) is simple enough. It consists of four triodes connected as cathode followers, having a common cathode load resistor. In this case, two dual triodes, 12AU7's, are used. In these tubes, the cathode which is connected to pin 3 is heated by the section of the heater included between pins 4 and 9 and the cathode connected to pin 8 is heated by the section between pins 5 and 9. Each input source, tuner, TV set, tape recorder, or phono preamp is connected to a separate grid circuit and when the heater of this section is turned on by the regular a.c. switch of the input source, the signal is passed on by the tube and appears across the common cathode load resistor. As only one triode heater is turned on at a time, the other input circuits are effectively disconnected from the rest of the circuit. In order to eliminate the heat that would be caused by having a series dropping resistor in the heater circuit, a condenser is used to reduce the line voltage to the 6.3 volts required by each triode section. This idea was gratefully lifted from Mr. Richard Graham's article "A Novel Capacitance Relay" in the December 1952 issue of RADIO & TELEVISION NEWS. If each source of input had had its own 6.3-volt heater supply, this 6.3 volts could have been used to operate its respective triode section, although one additional conductor would have been required between the source and the input selector unit.

In the unit built by the author, the parts were mounted in a three by four

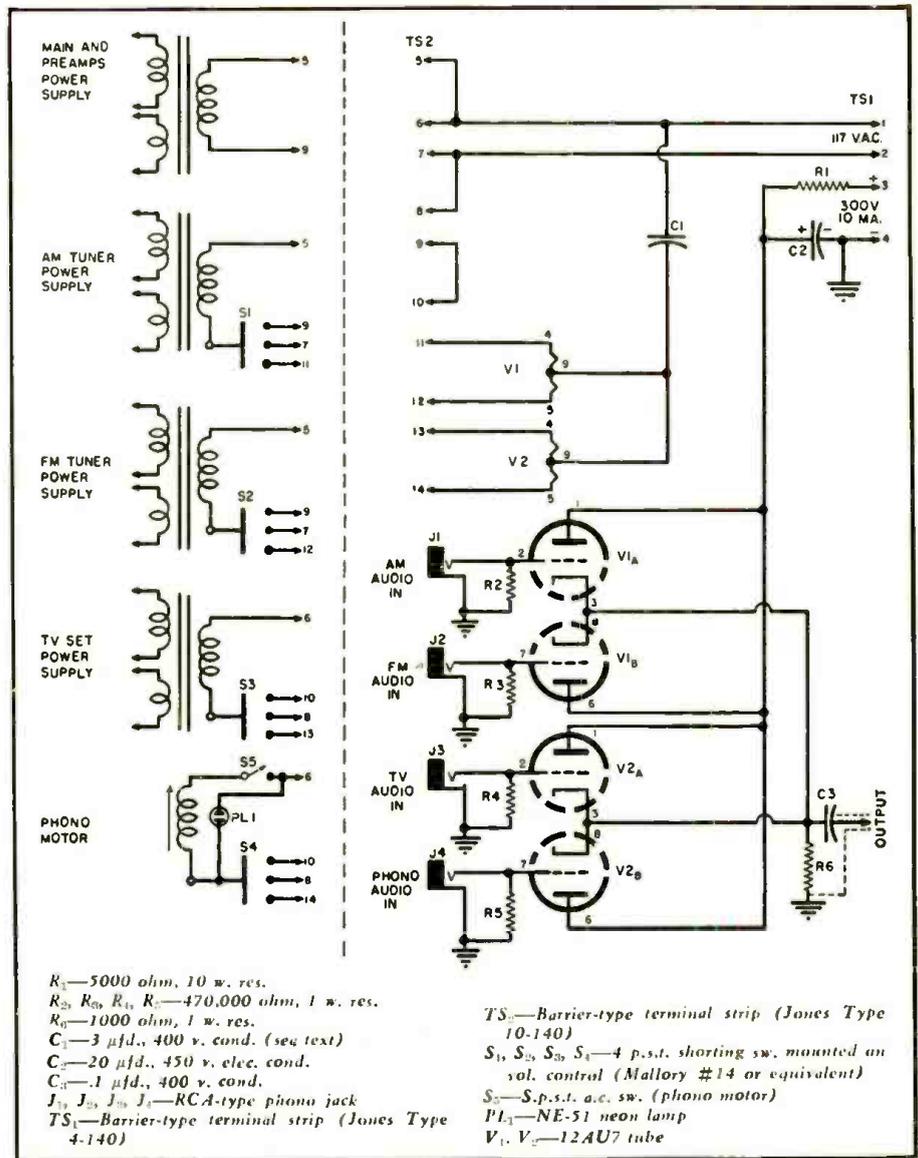




Fig. 2. Complete circuit diagram of the automatic input switching device.

by five steel utility can as shown in the photographs. The two tube sockets and the filter condenser were mounted on a piece of aluminum ap-

proximately five by two and three-quarter inches, with a half-inch fold on the two and three-quarter-inch (Continued on page 128)

Under chassis view. Few parts are required in the construction.

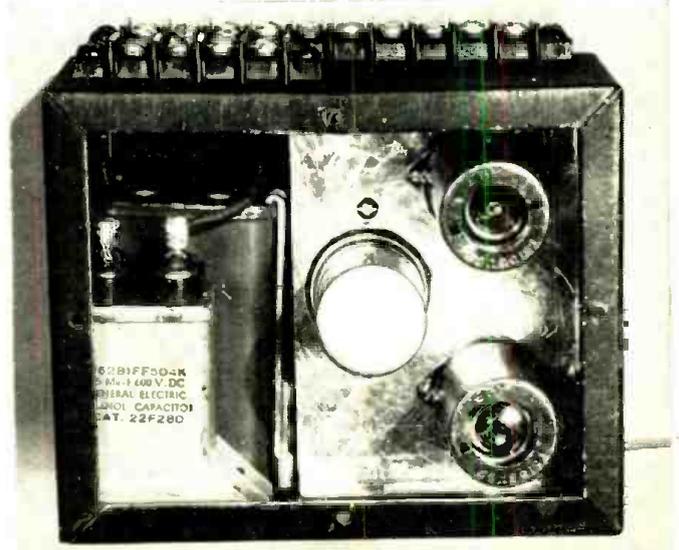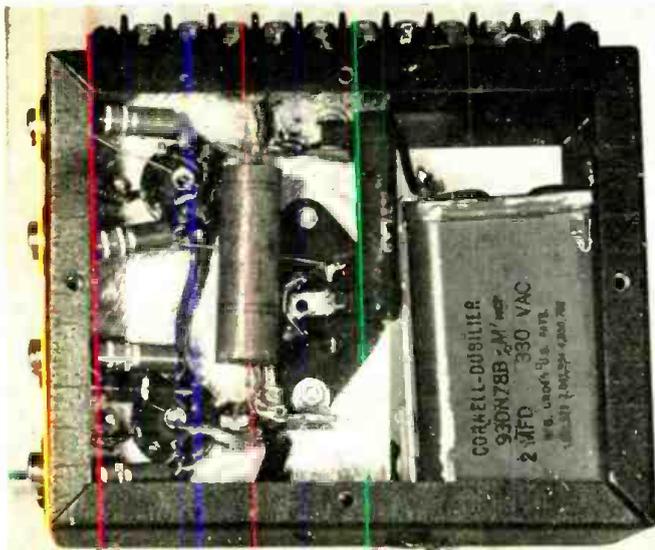Top chassis view. Provision is made for proper heat dissipation.



A MULTI-BAND, CONSTANT IMPEDANCE ANTENNA

By CALVIN R. GRAF, W5LFM

A simple modified "dipole" antenna can be used on all bands related to the fundamental frequency in steps of 1, 2, 4, 8, 16, etc. by choosing the correct feed point.

IN AN ARTICLE in this magazine several years ago,¹ it was shown that a transmission line could be matched to an antenna so that the antenna would operate on two bands. However, further investigation of the impedance-versus-length chart of the antenna shows that it is possible to work on several bands as long as they are related harmonically in steps of 1, 2, 4, 8, etc.

It is possible to find a point on an antenna that will present the same

impedance to the transmission line when operating on several different bands. Fig. 1, which is a logarithmic plot of impedance versus antenna length by bands, shows that there are many points on an antenna where the impedance is the same for different bands. Also, the points lie very near the 300-ohm line on the chart.

If point X in Fig. 1 is chosen, it can

¹ Dreher, Karl: "A Two-Band Piece of Wire" RADIO & TELEVISION NEWS, February, 1950.

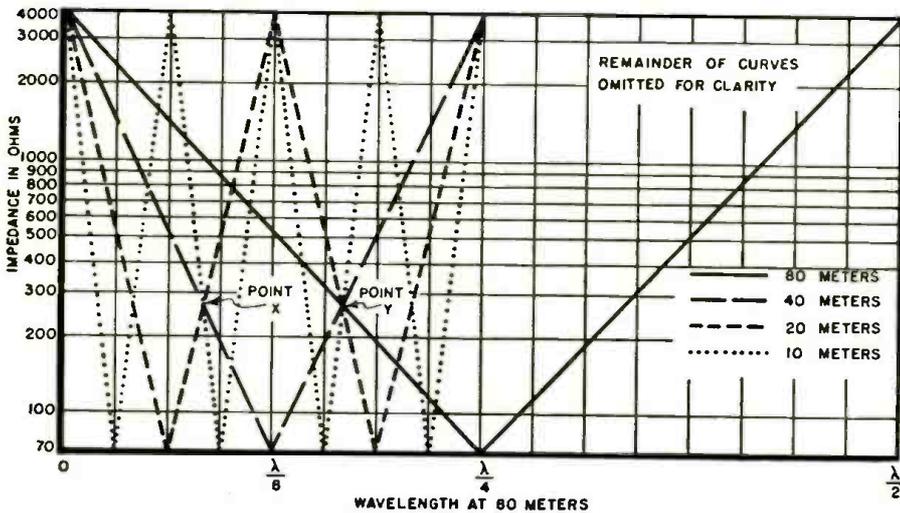


Fig. 1. Impedance vs wavelength for 80-meter antenna. See text on Points X and Y.

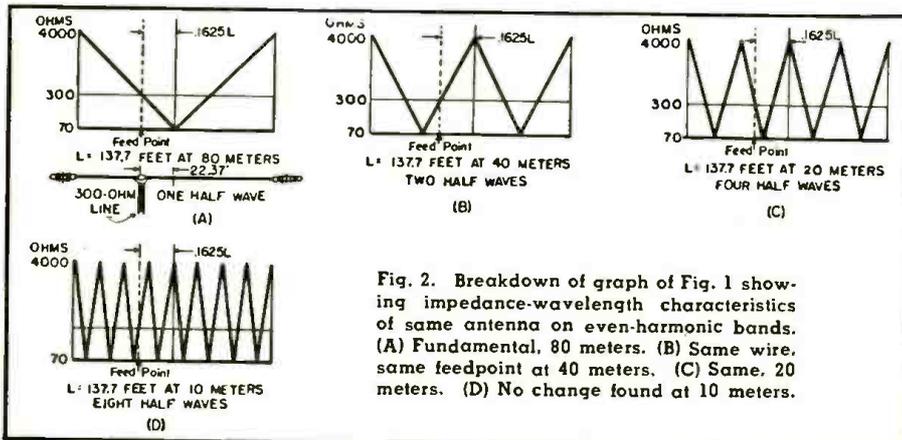


Fig. 2. Breakdown of graph of Fig. 1 showing impedance-wavelength characteristics of same antenna on even-harmonic bands. (A) Fundamental, 80 meters. (B) Same wire, same feedpoint at 40 meters. (C) Same, 20 meters. (D) No change found at 10 meters.

be seen that the fundamental of the antenna is not at the 300-ohm points. But if point Y is chosen, it includes the 300-ohm point of the fundamental and of all harmonics related in steps of 2, 4, 8, etc. Thus operation is possible not only on two bands, but on all bands that are related as indicated above. It becomes a simple matter of feeding a 300-ohm antenna with a 300-ohm line and this can be done on all bands without changing the feedpoint.

On its fundamental frequency, in our case 3.5 mc. (Fig. 2A), the antenna is fed off-center at one of the two 300-ohm points that exist on a half-wave dipole. This procedure is based on the assumption that the center radiation resistance of a half-wave dipole is approximately 70 ohms, rising to an approximate value of 4000 ohms at each end. Both values will vary somewhat, of course, depending upon the wire size and the proximity factors of the antenna.

When the antenna is operating on its second harmonic, 7 mc., and is a full wavelength long electrically (Fig. 2B), there exists a high impedance of 4000 ohms at the center instead of the usual 70 ohms. This 4000-ohm value will also be found at both ends of the wire. But, because of the position of the feedline, the antenna is still being energized at a 300-ohm point with a 300-ohm transmission line. Thus no standing waves result.


The same 300-ohm point is also used to feed the antenna on 14 and 28 mc., which are the fourth and eighth harmonics (Fig. 2C, 2D).

The 300-ohm transmission line can be any good-quality molded plastic or open-wire line.

We must now calculate the length of the antenna and the feeder tap point. The long wire formula $L = 492 (N - .05) / f$ is used to determine antenna length. L is length in feet, f is frequency in mc. for the highest band to be used, and N is the number of half-waves for the highest band to be used.

While in Japan, the author constructed an antenna such as this to be used on all bands from 80 through 10 meters. A frequency of 28.4 mc. for f was chosen since it allows the antenna to be tapped at the correct distance for proper operation in both the phone and c.w. portions of 10 and 20 meters. Operation on 40 and 80 will be satisfactory because of the lesser importance of the tap position at the lower frequencies. N in this case be-

(Continued on page 104)

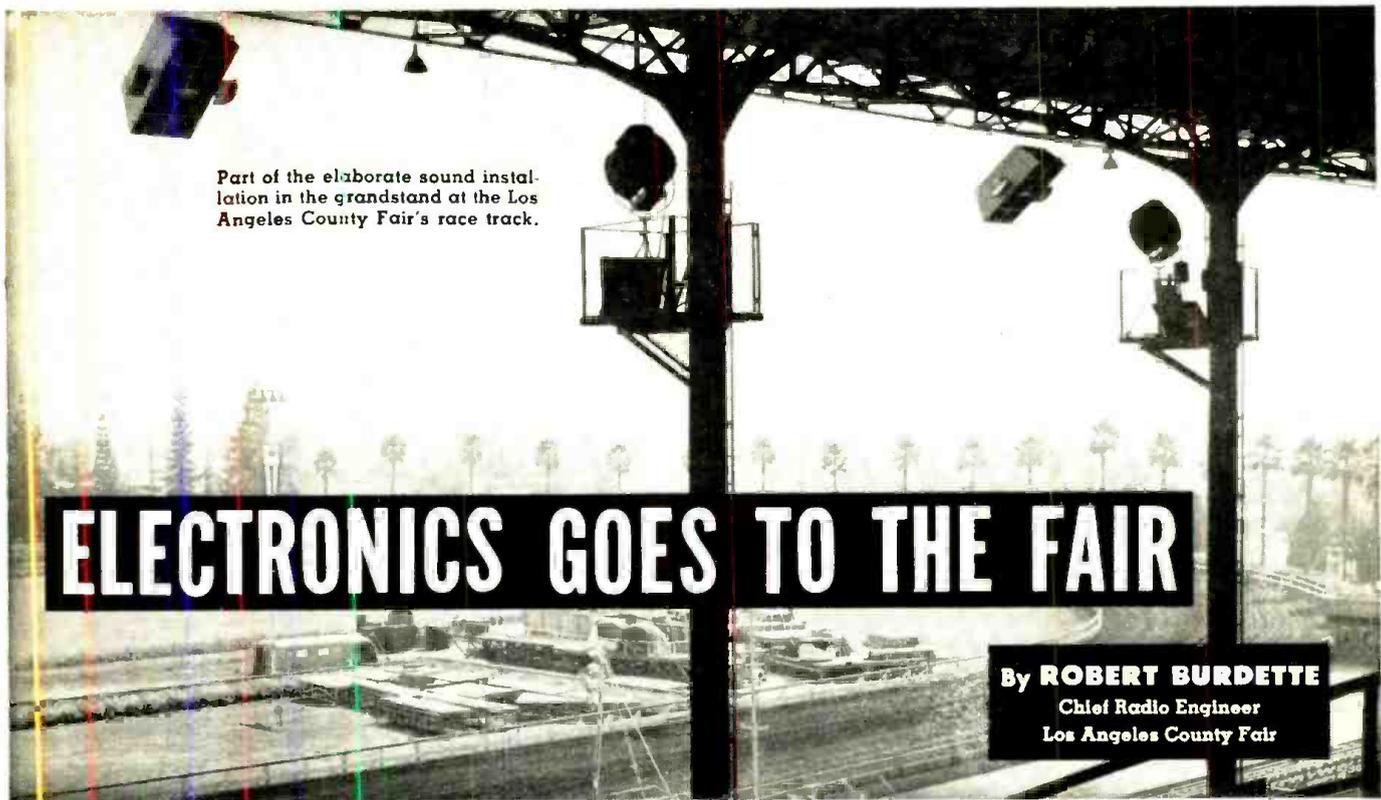

Part of the elaborate sound installation in the grandstand at the Los Angeles County Fair's race track.

ELECTRONICS GOES TO THE FAIR

By **ROBERT BURDETTE**
 Chief Radio Engineer
 Los Angeles County Fair

The sprawling grounds of the Los Angeles County Fair can shrink to backyard size because of an elaborate sound system which permits complete coverage.

IN OCTOBER, 1922 a popular young pharmacist, Mr. Jack C. Aflerbaugh of Pomona, California, conceived the idea of interesting a few of his fellow citizens in organizing an association, the purpose of which would be the exhibition of the products of the rich farm land and industries surrounding their thriving city.

Thus was born the Los Angeles County Fair, which has grown to be the largest in the world. From exhibits in tents spread over 40 acres of grain field, the Fair now covers 400 acres of ground with parking accommodations for 40,000 cars; one of the country's finest race tracks; and 200 permanent buildings housing exhibits brought from all over the world. More electricity is consumed daily at the Fair than is used by the entire city of Pomona, with its population of over 35,000 people.

Nineteen fifty-two, the twenty-fifth anniversary of the Fair, saw 1,068,000 people swarming through the grounds, consuming over 25 miles of hot dogs.

Protecting, guiding, and informing such a tremendous crowd involves public address and radio control problems of the first magnitude. The people must be able to hear clearly all sorts of material, from concerts in the grandstand (which seats 10,000 people) to the raucous calls of the Midway barkers.

Forty-two thousand individual exhibitors collect an estimated two miles of ribbons for prize-winning accomplishments in various fields including agriculture, livestock, fine arts and crafts, horticulture, domestic arts, and many others. Information regarding the activities must be gathered, edited, and broadcast by public address, radio, or telecast.

To accomplish this involves the simultaneous operation of over seventeen major public address systems, the broadcasting of over 600 radio programs of all types, and 75 hours of live telecasting, plus the release of many tape recordings for delayed broadcast.

This requires an enormous amount of electronic equipment, which must be set up, operated, and disassembled every year during the seventeen days the Fair is open.

Public address requirements may be divided into four classifications: the race-track installation, ground system, localized installations, and the mobile unit. The race-track installation consists of seven trumpet horns mounted in two clusters and directed to project sound across a 420 foot grandstand, which accommodates approximately 20,000 people. Two large baffle-type speakers are located directly in front of the grandstand to provide sound reinforcement for people standing at the edge of the track with two additional trumpet horns strategically mounted to cover the infield. Located in the center of the grandstand, upstairs rear, is a race announcer's microphone.

In front of the grandstand is a large stage equipped with seven microphones which is used for entertainment between races. Custom-built amplifiers furnish 150 watts of power. This installation is sponsored by the *General Petroleum Corporation*.

The ground system consists of speakers located throughout the grounds on towers approximately 60 feet in the air. These speakers are re-entrant-type trumpet horns with their amplifiers located in the Agriculture Building. Music, interspersed with public announcements, is continually originated at this point.

Custom-built amplifiers with 200 watts of power are located in the Agriculture Building. This system furnishes sound individually or simultaneously to the ground system and the speakers inside of the Agriculture Building, which is 400 feet wide, 800 feet long, with a 68 foot ceiling. Six *Jensen* "Hypex" chandelier-type speakers are used for sound projection. A stage, located at one end of this building, is equipped independently with its own amplification and baffle-type loudspeakers. This installation is also sponsored by the *General Petroleum Corporation*.

Localized installations are the main part of the public address operation with many units being operated simultaneously in approximately sixteen major locations. These installations cover the main auditorium, seating approximately 2000 persons, located in (Continued on page 183)

SPEECH FILTERS FOR AMATEUR RECEIVERS

By
HECTOR E. FRENCH, W1JKZ



The components needed for an effective filter are few, easily installed, and do not take up much room in the receiver.

Essential "intelligence" audio frequencies are emphasized and much interference rejected by a receiver speech filter.

WITH the amateur phone bands becoming more crowded each year, it is necessary to take advantage of every possible improvement in the entire communications link, from the microphone of the transmitter clear through to the speaker of the receiver. One of the easiest and most effective ways of improving this communications link is by using a speech filter.

Already, many transmitters include a filter circuit in the modulator, designed to eliminate the frequencies which lie outside the basic communications range of speech. By eliminating these frequencies, all the modulation energy can be applied to the most useful speech frequencies, with a resulting increase in the effectiveness of the modulation. When a speech clipper is being used in the modulator to increase the apparent percentage of modulation, a speech filter is required in order to eliminate the higher-order harmonic components generated by the clipping action. Failure to use a filter would result in severe distortion and spurious sidebands.

However, there is often little or no attention paid to the audio characteristics of the receiver when trying to reduce interference. This portion of the communications link can also benefit by careful design, since the signal fed to the speaker by the audio stage may include high-frequency heterodynes, converter hiss, splatter from a neighboring overmodulated carrier, or random noise from the background noise level on the band. To make it even worse, these interfering components are usually present two or three at a time. Since the generally-accepted limits of the effective speech frequencies are roughly 300 and

3000 cycles, it is obvious that a filter which rejects the frequencies outside these limits will improve the communications ability of the receiver when interference is present.

This type of interference is frequently made more severe by the characteristics of the speaker and its enclosure, and even by the position in the room where the speaker is mounted. Any resonances in this system outside the speech range will artificially re-inforce these unwanted frequencies, and reduce the effective signal-to-noise ratio. When it is remembered that the human hearing mechanism is most sensitive to the frequencies above 3000 cycles, it is plain that any effort to control this characteristic is a step towards more effective operation.

One popular and simple approach towards controlling the audio characteristics of the amateur communications receiver is to incorporate a resistance-capacity tone control somewhere in the audio circuit. This is of

some help in reducing the extremely high-pitched noise components, but the filtering action is usually too broad to be fully effective. With the tone control "full on," the important upper speech frequencies become attenuated so severely that the intelligibility is reduced by the tone control more than it would have been by the interference the tone control was designed to cure in the first place!

The only simple way of achieving the necessary sharp cut-off at the limits of the speech frequency range is by using a properly designed filter which has both inductance and capacitance. Designing the filter itself is somewhat complicated, but the greater complications are those which arise after the design is completed and the practical considerations of using the filter appear.


For example, there is the problem of size. A bandpass filter for the audio range can require more space than is available. Also, the electrical values required for the components almost always include some awkwardly impractical number of microfarads that must be "built up" by placing smaller values in parallel. It soon became evident that a conventional bandpass filter design was impractical, and this approach was discarded.

After calculation and experiment, it was found that the bandpass action could be obtained in two steps, by using a low-pass filter for the 3000-cycle cut-off, and by using the combination of a resistance-capacitance filter and an acoustic filter at the lower frequencies. Still further thought determined that for the greatest utility, the filter should be applicable to a receiver by merely inserting the circuit between the plate of a conventional "hi-mu" triode audio amplifier, such as the 6SQ7 triode section commonly used following the second detector, and the grid of the audio output stage which follows.

For convenience and economy, the filter was designed around the smallest and least expensive standard filter choke available. This turned out to be the Stancor No. C-1706, rated at 4.5 henrys at 50 milliamperes. By measurement, the inductance at zero current was found to be 5.3 henrys. By using this inductor with three


(Continued on page 124)

Fig. 1. Circuit of the filter. Numbered parts are the filter proper; labelled parts are typical or preferred receiver values.

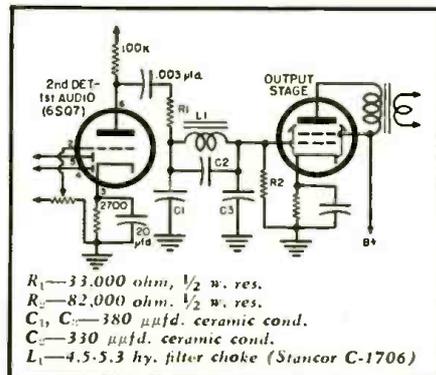



International SHORT-WAVE

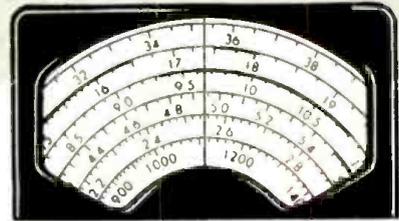

Compiled by KENNETH R. BOORD

ANSON BOICE has resigned as editor of the "United 49'ers Radio Society" and Mrs. Boice (Julia) has resigned as secretary, due to press of other duties. Bill Peters (W3NIT), 411 Pershing Ave., Collingdale, Pa., first editor of this club, has taken over the editor's job, and Mrs. Mabele Broome has been appointed secretary. Until further notice, all inquiries concerning the club should be sent to the president, Edward Broome, Box 371, Medford, N. J. (Boice, Conn.)

The "Newark News Radio Club" held its annual Convention Aug. 9 at the Montgomery County Sportsmen's Club, Green Lane, Pa.; this organization recently observed its 25th anniversary.

* * *

Around the World

Anglo-Egyptian Sudan—Radio Omdurman, 7.655A, tuned 1250 when had news in Arabic, then vocal Arabic music. (Pearce, England) Lists English for Friday 1230-1300, Sunday, Wednesday 1115-1130, and frequency as 7.600. (Riggle, Ohio)

Angola—Radio Clube de Huila, 10.48A, Sa da Bandeira, is fairly strong in Britain from around 1330 to close at 1604; CWQRM bad at times. (Monitor, England) Luanda, 11.862, is good level in Sweden 1500-1600 close-down. (GDX-aven, Sweden)

Australia—VLC9, 9.615—replacing VLC11, 11.810—to Eastern North America 0700-0845 is sending a greatly improved signal; DX session Sun. 0830. (Fox, Va.; Smits, Minn., others) Smith, Mich., notes excellent signal around 2300 from VLA15, 15.200.

Austria—Blue Danube Network, 9.617, Salzburg, noted 0200 with music; 0400 with news summary from the AFN newsroom, Frankfurt (Germany). (Pearce, England)

Balearic Islands—Radio Menorca, 7.410A, Mahon, noted in Sweden 1700-1720 sign-off. (Nattugglan, Sweden)

Belgian Congo—OTC, 9.655, Leopoldville, noted with English session relayed from ORU, Brussels, Belgium, 2000-2200 closedown. (Kelting, N. Y., others)

Brazil—A station on 11.965A around 1830 identifies in Portuguese as "Radio Record," Sao Paulo. (Niblack, Ind.) ZYB 32, 11.825, Recife, noted 1700 with call of "Radio Jornal do Comercio;" excellent level in Britain. ZYB8, 11.741.5, Sao Paulo, noted 1715 at good level. PSH, 10.224, Rio de Janeiro, heard relaying "Agencia Nacional"

session at 1750, fair level. (Catch) ZYB9, 15.155, Sao Paulo, noted in Portuguese at fair level 2100. (Hardwick, N. Z.) ZYR57, 9.745, has Japanese session ending around 1830; best day to try for this is Monday when HCJB, Quito, Ecuador, is off the air. (Bellington, N. Y., others) PRL7, Rio de Janeiro, noted recently with English announcements between 2130-2200. (Roberts, Conn.) Heard lately to past 0000. (Richmond, N. Y.)

Bulgaria—Sofia noted with English 1500-1515, 1615-1645 on 6.07, 7.670A. (Pearce, England) Excellent on 9.700 to North America 2000-2030. (Kelting, N. Y.) And in new period 1800-1815. (Dexter, Iowa, others) Now lists English for North America on 9.700 at 1800-1815, 2000-2030. (Crowell, Pa.)

Canada—CHNX, 6.130, Halifax, N. S., good level 0900. (Morrison, R. I.)

Canary Islands—Tenerife, 7.633A, noted 1700 in Spanish. (Alonso, Spain)

Cape Verde Islands—CR4AA, Praia, sent QSL card and gave channels as 5.895, 7.13 (but is now near 7.40), 400-3000 watts, at 1500-1700. (Pearce, England)

Ceylon—Colombo, 6.006, noted 0730 with musical program and news. (Sanderson, Australia) Commercial Service noted on 17.82A at 0615-0715 in English. (Ishikawa, Japan)

Chile—CE1173 is wandering around

(Note: Unless otherwise indicated, all time is expressed in American EST; add 5 hours for GCT. "News" refers to newscasts in the English language. In order to avoid confusion, the 24 hour clock has been used in designating the times of broadcasts. The hours from midnight until noon are shown as 0000 to 1200 while from 1 p.m. to midnight are shown as 1300 to 2400.)

The symbol "V" following a listed frequency indicates "varying." The station may operate either above or below the frequency given. "A" means frequency is approximate.

11.945AV lately; heard as early as 0730. (Stark, Texas; Niblack, Ind., others)

China—Radio Peking was measured 15.063A recently 2235 when was only fair level, a bit improved by 2247; in Chinese. (Ferguson, N. C.) Current schedule shows English at 0400-0430 on 6.100, 7.500, 9.040, 10.260, 11.690, 15.060, 15.170; 0830-0900, 11.690, 15.060; 2200-2230, 13.625 (new), 15.060. (Os-kay, Scheiner, N. J.)

Czechoslovakia—"The Voice of Peace," Prague, 9.504, noted signing on in English 1400 with news, music; off 1423. (Pearce, England) Heard on this channel 2315 with news, music. (Sanderson, Australia)

Denmark—Copenhagen, 15.165, heard signing on 0900 in Danish after clock chimes, anthem, to India, Malaya; closed with anthem 0959 (no English); at 1000 had ship's bells, then opened program for Danish seamen. (Pearce, England) Heard opening 1130 on this channel in Danish to Near East. (Takemi, Japan) Heard in both transmissions on 9.52 to North America 2030-2130, 2200-2300. (Gay, Calif., others)

Ecuador—HCRC1, 4.930, Quito, is scheduled Mon.-Fri. 0630-0800, 1200-1400, 1900-2215; Sat. 0630-0800, 1200-1400, 1900-2300; Sun. 1100-1300, 1900-2300. (Pearce, England) HC5GB, 4.780, Riobamba, noted signing off 2300. (Cushen, N. Z.)

Egypt—Cairo's new 11.965 channel noted opening 1000 with clock striking "5 p.m." The 6.085 channel appears parallel. (Pearce, England) Has been measured on 11.966 around 2335. (Ferguson, N. C.) Very strong in Virginia

(Continued on page 150)

This neat short-wave Listening Post is that of Yo Ishikawa, JA1DS, Tokyo, Japan, who is both an amateur and a SWL. Yo uses a home-made 11-tube superhet which has one r.f., three i.f., and two a.f. stages. Antenna is 10 meters long, 8 meters high.



TV RECEIVER SENSITIVITY

By

JOHN RANKIN



The "SensiMeter," manufactured by Service Instruments Co., measures TV receiver sensitivity when used with a v.t.v.m.

Importance of sensitivity measurements in improving TV sets and selecting the best receiver for fringe area operation.

ALTHOUGH television design engineers have been making great progress in increasing receiver sensitivity, realizing that this important factor enables the fringe areas to be extended farther from the television stations, very little information is available to the service technician on this subject. The majority of receivers now manufactured have approximately twenty times the sensitivity of receivers manufactured in 1948. However, due to production tolerances, tube aging, and rough handling during shipping, many receivers reach their destinations with decreased sensitivity and, unless the receiver is actually checked, poor reception is often blamed on local conditions or the antenna.

Very few factories check the sensitivity of all receivers leaving the plant, although every effort is made to see that the average sensitivity is kept high. If a receiver with below normal sensitivity goes to a primary service area, the owner would not know the difference; but if the same receiver goes to a fringe area, it might mean a very poor picture.

In many fringe areas where television signals are subject to fading, it is impossible to tell if a receiver has been satisfactorily repaired unless the sensitivity is actually measured.

Design engineers determine sensitivity by connecting a generator to the receiver antenna terminals, measuring the d.c. voltage developed across the video detector load resistor. The generator is not modulated, and has an output attenuator calibrated in microvolts. The attenuator is adjusted to give 1-volt d.c. across the video detector load resistor. This value is

used because, under actual operating conditions, if 1 volt d.c. is developed by the television signal a satisfactory picture will result. Some early receivers required an input as high as 500 microvolts to obtain 1 volt d.c. across the video detector load resistor. The receivers being produced today are capable of obtaining 1 volt with 20-microvolts input, with many even better.

The sensitivity figures mentioned are for Channel 2. This channel is used because the lower the channel, the higher the sensitivity, and unless one channel is used as a standard, the figures would become confusing. In modern receivers the sensitivity on Channel 2 is twice that of Channel 13, and the variation is almost linear on the other channels.

Sensitivity measurements help the service technician to improve reception in fringe areas. The following is an actual report on what can be done by measuring the sensitivity.

A receiver was checked and found to have a sensitivity of 100 microvolts. This was not good enough for fringe-area reception. The a.g.c. was a straight peak-operated diode type. Connecting the a.g.c. circuit through a changeover switch to operate from the negative voltage developed across the video detector load resistor, as shown in Fig. 1, brought the sensitivity of the set to 50 microvolts.

The "B+" was found to be low on the video i.f. amplifier tubes, so it was increased by shunting the feed resistors to the next higher "B+" source (an increase of 50 volts). This increased the sensitivity of the receiver to 25 microvolts.

The receiver used a *Standard Coil*

tuner, so the 3900-ohm resistor across the r.f. grid coil was changed to 22,000 ohms, resulting in a sensitivity of 20 microvolts.

In a 20-microvolt signal area this receiver gave excellent results. Sometimes, however, it is necessary to obtain a greater increase in sensitivity. If the receiver uses 6AU6 tubes as i.f. amplifiers, it is often possible to rewire one socket and use a 6AG5, increasing the sensitivity to 10 or 15 microvolts.

Due to manufacturing tolerances, all receivers, even of the same make, will not show the same increase with each step. Some receivers, with the changes mentioned, will not go below 20 microvolts; but others will go to 5 microvolts without developing a peaked curve due to regeneration.

Rectifiers supplying "B+" are one of the worst offenders causing low sensitivity—r.f. amplifier tubes come next. These tubes may be changed while the sensitivity is being measured without re-alignment of the receiver generally being necessary. Germanium diodes can also contribute to low sensitivity and, if they are accessible, they should be tried next; otherwise, the i.f. amplifier tubes should be replaced and the i.f. stages re-aligned.

Increasing the sensitivity by these methods will often save the work involved in erecting stacked antennas, and will eliminate the need for a booster.

Since all u.h.f. signals are ultimately converted to a v.h.f. signal, and also since u.h.f. signals are usually much weaker than v.h.f., it is important to know the maximum receiver sensitivity on a low v.h.f. channel before poor reception is blamed on the converter or u.h.f. strips. Unless a check of this type is made, the service technician may spend much time on the antenna installation without much improvement in picture quality.

The "SensiMeter" is a generator designed expressly for measuring the sensitivity of television receivers. This unit has a unique attenuator which is

the most critical part of equipment of this type; a cross sectional diagram of the attenuator is shown in Fig. 2. The oscillator coil "A" is housed in a seamless metal bellows "B." When the bellows is opened or closed, the output coil "C" moves with it. The attenuation remains constant with variations in oscillator frequency, and is free from the usual difficulties associated with variable-resistance type attenuators. The attenuator also provides shielding and matching for the output circuit and even with the attenuator in the 5-microvolt setting, the cable may be grasped without any charge in reading. The output impedance is 300 ohms at all settings of the attenuator, and the calibrations are extremely accurate. Also, the oscillator tube may be replaced without recalibrating the instrument.

To measure sensitivity with the "SensiMeter," the two clips on the output cable are connected to the receiver antenna terminals; the receiver channel selector is set to Channel 2, or if Channel 2 is operating in the area Channels 3 or 4. The meter on the front panel is then set to center scale to compensate for any variation in line voltage. A v.t.v.m. (or 20,000 ohms-per-volt meter) set on the low-voltage d.c. range is connected across the video detector load resistor, and the channel dial on the "SensiMeter" tuned for a peak on the v.t.v.m. The microvolt dial is then adjusted until the v.t.v.m. reads 1 volt. The figure on the microvolt dial at this setting is the sensitivity of the receiver. The scale of the microvolt dial is divided into three parts—"Very Sensitive Receiver," "Medium Sensitivity," and "Insensitive Receiver," to allow the operator to quickly determine the condition of the set.

Measuring sensitivity in this manner duplicates the receiver operating conditions in fringe areas where the pictures are mostly tuned with the video carrier on top of the curve. If it is required to know the receiver sensitivity under operating conditions in a primary area, the microvolt figure would be multiplied by 2, since the video carrier would be tuned to the 50% point of the receiver response curve.

While sensitivity is being measured, the channel dial on the "SensiMeter" should be turned slowly, watching the pointer of the v.t.v.m. If the receiver is properly aligned, the pointer will slowly rise and fall, tracing out the curve of the receiver, as shown in Fig. 3A.

Some receivers may show very good sensitivity, but the check described in the preceding paragraph may indicate a sharp peak, as shown in Fig. 3B.

This is often caused by regeneration. Most manufacturers recommend that battery bias be used during alignment, and after alignment the curve may look normal when viewed with a sweep generator and oscilloscope. However, when very little or no a.g.c. bias for the i.f. amplifiers is

developed in fringe areas, regeneration may occur in the i.f. strip, resulting in large snow particles and poor sync. The regeneration can be caused by wrong lead dress in the i.f. amplifier strip, long leads on i.f. bypass condensers, or the use of tubes with too high a gain for the amount of shielding provided. Connecting the suppressor of 6AU6 tubes to the un-bypassed cathode resistor instead of to ground is another common cause of regeneration.

Many manufacturers have test points for the video detector load accessible without removing the receiver from the cabinet, so it is possible to check the sensitivity of a receiver rapidly before it is sent to a fringe area. In this way a "hot" receiver may be selected for a difficult area.

A further use for the "SensiMeter" is to check the field strength of the television signal on Channels 2, 3, and 4. To do this, connect the antenna to a television receiver, short-circuit the a.g.c., and measure the voltage across the video detector load resistor. Then connect the "SensiMeter" to the receiver input. Adjust the microvolt dial until the voltage across the video detector load is the same as that produced previously by the signal coming down the antenna. The reading on the microvolt dial is the field strength. If this reading is 15 microvolts, then a receiver with a sensitivity of at least that amount must be used.

The preceding methods of measuring sensitivity do not include the video amplifier and picture tube which also play their parts in producing the picture. The video amplifier, whether it be one or two stages, must amplify the signal from the video detector load to a level which will operate the picture tube.

Two terminals on the right-hand side of the "SensiMeter" provide 1 volt peak-to-peak. This is connected across the video detector load resistor and if the video amplifier has adequate gain and if the picture tube is good, a black bar will appear on the screen.

Although it is not necessary, the actual gain of the video amplifier may be measured by connecting a peak-to-peak voltmeter between the picture tube cathode and grid. The reading in peak-to-peak volts is the gain of the video amplifier.

Although this article has stressed the importance of receiver sensitivity in fringe areas, sensitivity becomes

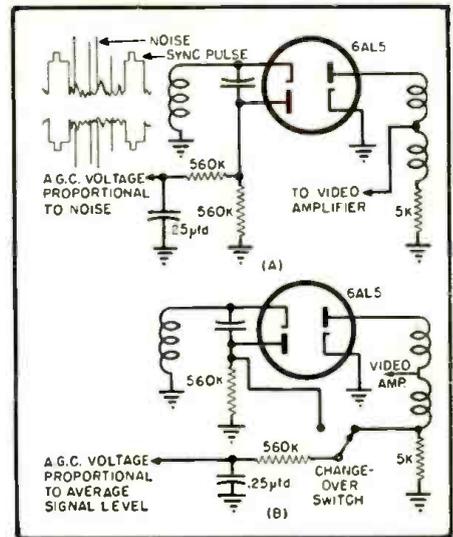


Fig. 1. (A) A diode a.g.c. system which develops a.g.c. voltage in proportion to the peak level of the received signal. In fringe areas where the noise peaks often exceed the level of the sync pulses, the noise pulses develop a.g.c. voltage which is too high. The addition of a local-distance switch shown in (B) avoids this situation.


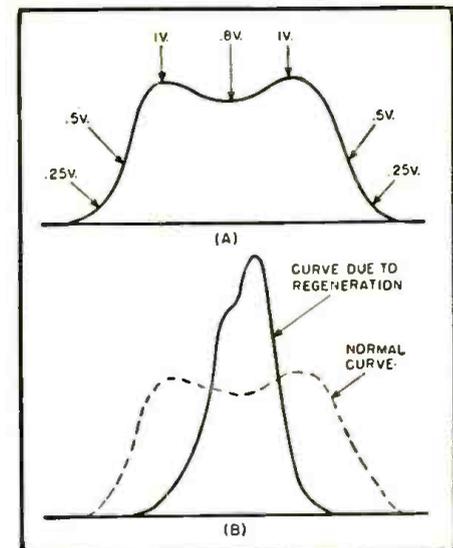


Fig. 3. (A) TV receiver response curve traced out from v.t.v.m. readings as channel dial of "SensiMeter" is tuned. (B) Faulty-type curve.

very important in primary areas when receivers are installed in apartment buildings where outside antennas are not permitted. In such instances, many sales have been lost due to insensitive receivers.


-30-

Fig. 2. Simplified schematic of the critical circuits of the "SensiMeter" showing the "bellows" attenuator, which gives constant output attenuation for all frequencies.

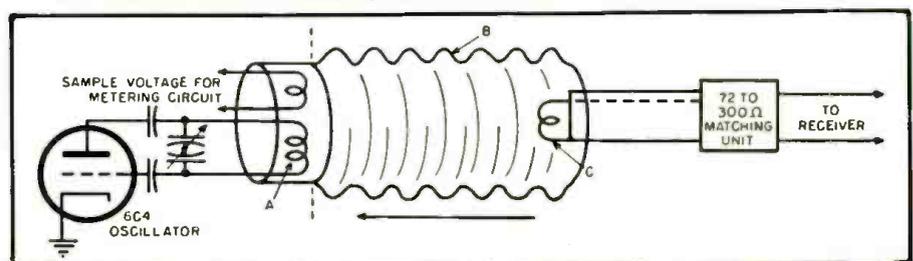

MAC'S RADIO SERVICE SHOP

By JOHN T. FRYE

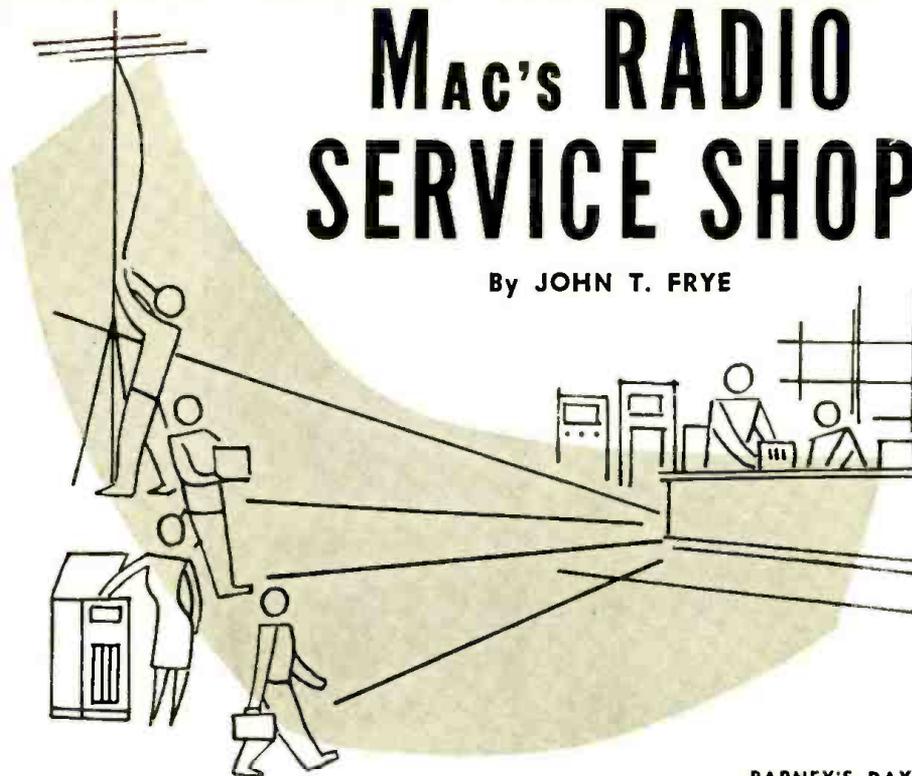

BARNEY'S DAY

A SMUG little smile was playing around Barney's mouth as he marched into the service shop and tossed the book he was carrying onto the service bench. Mac, his boss, eyed him out of the corner of his eye for a little while and then said, "All right; wipe the cat-that-ate-the-canary grin off your mug and out with it! What do you think you've got on me?"

"Oh it's nothing, really nothing at all," Barney said airily; "only it just so happens I was chewing the fat on 75 phone last night with a ham up in Connecticut and a friend of his by the name of Howard who was there with him in the shack. We got to talking about test instruments, and I sounded off on that business you were giving me a while back about how the 20,000 ohms-per-volt voltmeter loads a circuit less than a v.t.v.m. whenever you are measuring a voltage from about 500 volts up. Howard agreed this was so as long as you use the instruments without high voltage probes or if you use probes merely designed to extend the highest scale of either instrument to 30,000 volts.

"However, he pointed out that some v.t.v.m. manufacturers use a probe that increases the total resistance and all ranges of the v.t.v.m. by a ratio of 100 to 1. In theory, this would extend the top range to 100,000 volts or so, but of course you would never try to measure such a voltage. What you do, though, is switch to say a 300-volt scale and read up to 30,000 volts on it. Changing ranges of the v.t.v.m. has no effect on its fixed input resistance of 10 megohms, and so you can thus have a total meter-and-probe resistance of around 1000 megohms."

Mac mulled this over for a moment, and then a sheepish grin spread over his face. "And Howard is absolutely right!" he confessed. "I'm giving myself a big black mark for forgetting about those high-resistance probes. We were not giving the v.t.v.m. a very fair shake, were we?"

"You were not," Barney said with exaggerated emphasis on the pronoun. "Why a fellow could use a 10,000 to 1 probe and read the 3-volt scale and so get a resistance total of 100,000 megohms for measuring 30,000 volts!"

"Not in practice, he couldn't," Mac disagreed. "When you get past 1000 megohms of multiplier resistance, the resistance of the probe insulation would become a serious factor. Not to change a disagreeable subject, though, how did you manage to tear yourself away from your beloved comics long enough to try to read a book? What have you got there: *Tom Swift and His Giant Cannon* or *The Return of Tarzan*?"

"This book," Barney said with great dignity, "is *Cybernetics* by Professor Wiener."

"Whoberwhatics?" Mac asked with a puzzled frown.

"Cybernetics," Barney repeated, obviously enjoying his employer's bewilderment. "Surely you know what that is."

"This is certainly not my day," Mac said with a deep sigh. "Would you condescend to explain in as simple words as you can to an ignorant old man what cybernetics might be?"

"Well," Barney began with obvious relish, "cybernetics has been defined as the study of control and communication in the animal and the machine, but I like to think of it as a sort of correlation of the physical sciences of

mathematics, statistics, and electronic engineering with the biological science of neurophysiology."

"You do?"

"Yes; but you might understand it better if I said it occupies a kind of middle ground between men and machines, and looks in two directions: on the one hand it is interested in building machines that will do some of the tasks of computing or controlling that now are usually done by human beings. At the same time it studies the problems and failures of such machines and so arrives at a better understanding of the nervous system of the human body by which such jobs are done."

"I get it now," Mac said. "You are talking about the brand-new science that builds electronic brains like the one we saw on television election night."

"The word is new but the science is not," Barney explained. "We had cybernetic machines long before we had vacuum tubes. The governor of a steam engine is a good example. This gadget tends to keep the speed of the engine constant under varying loads. It consists of two iron balls on pendulum rods attached to opposite sides of a rotating shaft driven by the engine. As the balls are swung out from the shaft by centrifugal force they work a valve that controls the amount of steam entering the engine. If the engine tries to speed up, the governor cuts down on its steam; if it tends to slow down, the governor admits more steam. This is a dandy example of the negative feedback principle that is of major importance in cybernetics."

Mac looked completely baffled. "Negative feedback in a non-electronic machine?" he questioned.

"Sure; feedback is merely a term applied to information fed back from a controlled mechanism to the controlling force to let it know how the action is progressing. In the case of the steam engine, the change in speed of the engine 'reports back' by causing the iron balls of the governor to change their position."

"But you said 'negative feedback.'"

"That's right. The use of the word 'negative' means that the feedback tends to buck whatever the system is already doing. If the engine speeds up, the governor slows it down, and *vice versa*. It is the same thing in an amplifier. 'Negative feedback' here simply means that we cause a portion of the output of the amplifier to oppose the input."

"Yes, I suppose it does," Mac muttered feebly. "You've been telling me about machines that act like men; what has cybernetics done in discovering how men act like machines?"

"A good question, and I'm glad you asked it," Barney said glibly. "Dr. Jose Delgado of the Yale Medical School recently thrust as many as forty tiny electrodes, only 1/200 of an inch in diameter, deep into the brain

(Continued on page 167)

*Depend on Mallory
for
Approved Precision Quality*



“...and BE SURE



the VIBRATORS are MALLORY!”

That's the best way to be sure your service jobs stay "sold". You can depend on Mallory Vibrators to give more years of service. Their precision quality is the answer to time-wasting call backs. These are just two of the reasons why 5 out of 6 service men prefer Mallory for all their service work.

And the preference doesn't end there. They are more widely used as original equipment than all other makes combined. The patented, tuned mechanism in Mallory Vibrators gives better performance because:

*Slow contact make ...
means less wear*

*High contact pressure ...
means low resistance*

*Fast clean break ...
means reduced arcing*

The next time you order vibrators ... be sure to ask for Mallory. You'll get better vibrators, available in a complete line, meeting original equipment specifications ... yet they cost no more. You can be sure that every service job is done right the first time.


P. R. MALLORY & CO Inc
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

'SCOPES ARE "GOLD MINES"

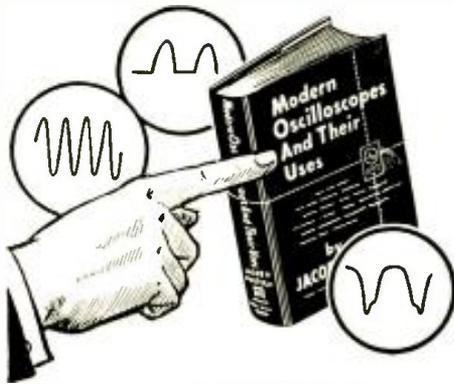... when you know how
to use them fully on all
types of service jobs



... AND THIS BOOK
MAKES IT EASY TO LEARN
ALL ABOUT THEM!

No question about it! The cathode ray oscilloscope is the handiest, most useful instrument in radio-TV servicing today. Servicemen who master it get the best jobs—make the most money—work lots faster—and are headed for even bigger things in the future!

MODERN OSCILLOSCOPES AND THEIR USES

By Jacob H. Ruiter, Jr.
of Allen B. DuMont Laboratories, Inc.
326 pages. 370 illustrations. \$6.00

- ✓ When, where, why and exactly how to use them
- ✓ How to interpret patterns
- ✓ How to handle tough jobs easier and faster

Now the oscilloscope won't "stump" you—not when you have the clear explanations given by this famous book! It contains no involved mathematics—no puzzling and complicated discussions. Instead, it goes right to work explaining oscilloscopes fully and showing you exactly how to use them in lab work and on AM, FM and TV service work—from locating troubles to handling tough realignment jobs. Each operation is carefully explained including determining where and how to use the 'scope; making connections, adjusting circuit components, setting the controls and analyzing patterns fast and accurately. About 370 illustrations including pattern photos make things doubly clear.

No other type of specific service method training can mean so much to you in terms of efficiency and greater earning power! Send for it today. See for yourself how this book can help you—before you buy!

READ IT 10 DAYS . . . at our risk!

Dept. RN-93 RINEHART BOOKS, Inc.,
Technical Division,
232 Madison Ave., New York 16, N.Y.

Send MODERN OSCILLOSCOPES AND THEIR USES for 10-DAY EXAMINATION. If I decide to keep the book, I will then remit \$6.00 plus a few cents postage in full payment. If not, I will return book postpaid and owe you nothing.

Name.....

Address.....

City, Zone, State.....

Employer's Name & Address.....

OUTSIDE: U. S. A.—Postage \$6.50 cash only.
Money back in 10 days if book is returned.

WHAT'S

New in Radio

For additional information on any of the items described herein, readers are asked to write direct to the manufacturer. By mentioning RADIO & TELEVISION NEWS, the page and the issue number, delay will be avoided.

CONSTANT CURRENT CONVERTER

Electronic Research Associates, Inc., Box 29, Caldwell, N. J. is now offering the Model CC-60 constant current converter for transistor applications.

The new instrument is designed to convert a standard power supply into a constant current generator for transistor and other applications where



constant current is required. The unit is connected externally in series with the standard supply and no rewiring or other modifications are necessary.

The design makes use of the high impedance of a pentode when operating above the knee of the I_b-E_b curve to present a constant impedance to the input voltage source. Thus, substantially constant current is maintained independent of a wide range of load variation. In addition, inverse current feedback is utilized which further increases the internal impedance and provides for long-term current stability.

The company will forward a data sheet on the Model CC-60 on request.

EVACUATED TRANSISTOR

CBS-Hytron of Danvers, Massachusetts has announced a new evacuated junction transistor.

Sealing each transistor in a vacuum is a further improvement on the original hermetic sealing of transistors, as announced recently by the company. The new process removes all polar molecules that in time might deposit themselves upon the junction boundary line, thus eliminating unwanted leakage of applied currents and the gradual breakdown of the units.

Additional information on the evacuated transistors is available on request.

HIGH-FIDELITY EQUIPMENT

Pilot Radio Corporation, 37-06 36th Street, Long Island City, N. Y. has announced the addition of several new units to its high-fidelity equipment line.

Among the new units now being marketed are the company's Models AF-723 and AF-824 FM-AM tuners, the Models AA-901 and AA-902 amplifiers, the Model PA-912 preamplifier, the Model CV-602 u.h.f. converter, the Model TV-524 24" television chassis, and the Model TV-527 27" television chassis.

A data sheet giving complete specifications on all of these units is available from the company on request.

RCA PORTABLE TAPE UNIT

The Engineering Products Department of *Radio Corporation of America*, Camden, New Jersey has unveiled a new portable tape recorder designed for the consumer market.

Packaged in an aviation luggage carrying case, the recorder weighs 25 pounds. Its over-all size is 14" x 12" x 9". The dual-speed machine can record or play back up to two hours and can rewind in approximately 2¾ minutes. It will accommodate all sizes of tape reels up to 7".

Push-button controls are used to operate the machine and tape threading may be accomplished in a matter of seconds. The unit also has a jack to permit easy attachment to phonographs, radio receivers, and p.a. systems.

The recorder is now available at RCA distributors, competitively priced.

REMOTE CONTROL UNIT

Rauland-Borg Corporation, 3515 West Addison Street, Chicago 18, Illinois has introduced a unique remote control unit which has been trademarked "Libretto".


This remote control-preamp is fashioned in the form of a lavishly bound book in padded leatherette with metallic gold-finished backbone and sides.



The backbone lifts on a piano hinge giving access to convenient tuning controls. It can be operated in either horizontal or vertical position.

The "Libretto" is completely self-powered and capable of operating up to several hundred feet from the amplifier. The unit measures 8¾" x 11"

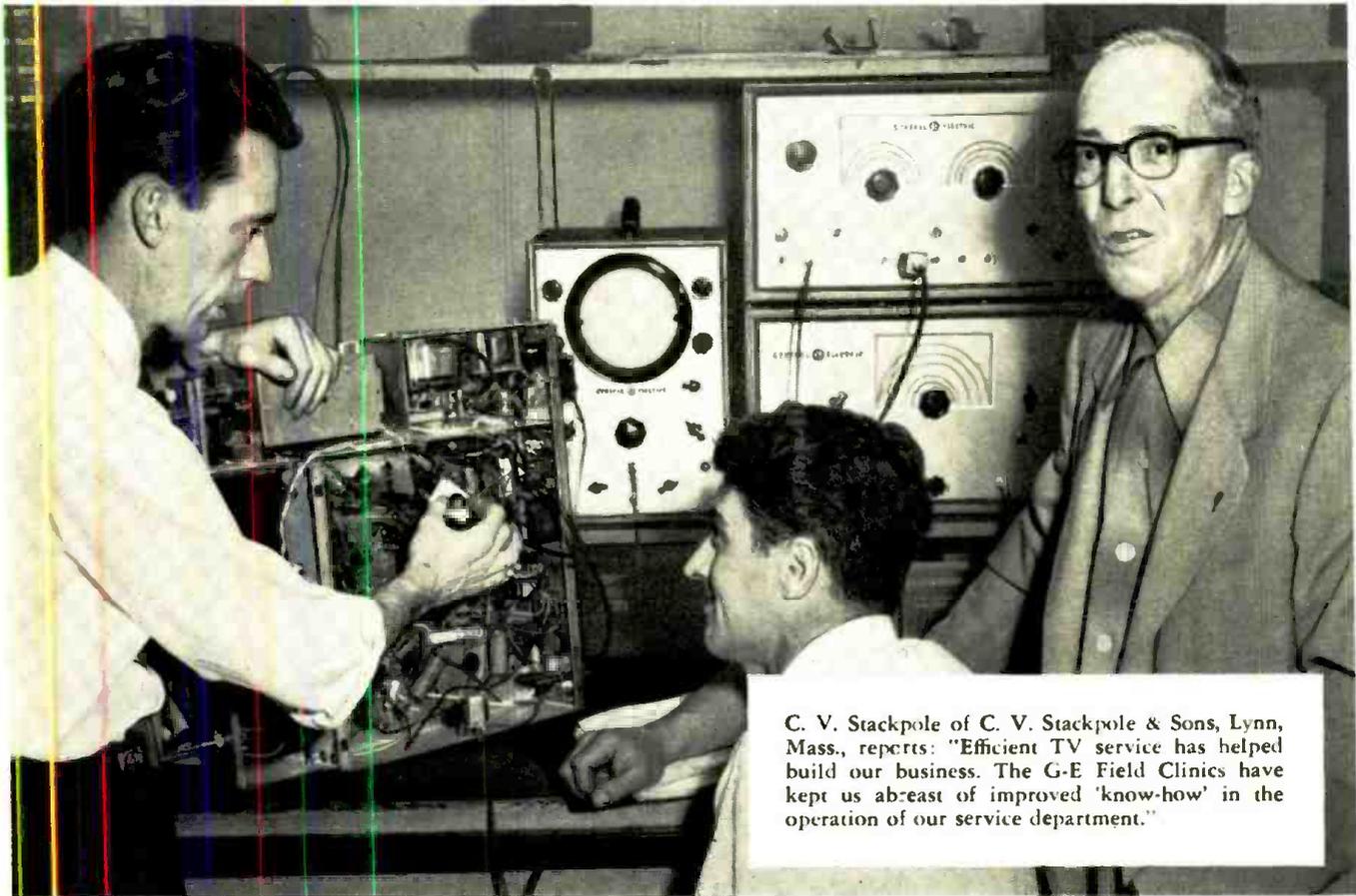G-E FIELD CLINICS SHOW WAY TO INCREASED EFFICIENCY IN TV SERVICE



C. V. Stackpole of C. V. Stackpole & Sons, Lynn, Mass., reports: "Efficient TV service has helped build our business. The G-E Field Clinics have kept us abreast of improved 'know-how' in the operation of our service department."


Left to right—Danny O'Connell, Arthur Drolet, C. V. Stackpole.

General Electric Field Engineers are holding Clinics throughout the Country—Open to all TV Servicemen—Without Charge

● An efficient service department is a vital factor in building a profitable television business. Like C. V. Stackpole, you'll find it well worth your while to attend one of the G-E Field Clinics. G-E engineers demonstrate simple ways to diagnose and correct TV troubles with special emphasis on UHF. They will show you how to install and adjust the various kinds of UHF antennas and tuners—and answer your questions on all phases of TV service.

Ask the Service Manager at your G-E TV distributor to sign you up for the next G-E Field Clinic in your area.

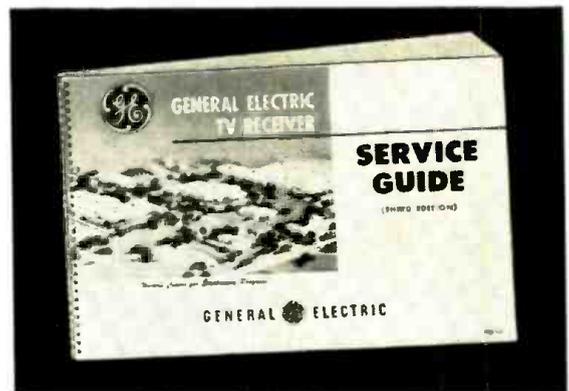General Electric Company, Radio & TV Department, Syracuse, N. Y.



● The Third Edition of the G-E TV Receiver Service Guide has just been released. Order your copies today through your General Electric TV Distributor.

You can put your confidence in—

GENERAL  **ELECTRIC**

WE HAVE THE LARGEST STOCK OF MILITARY EQUIPMENT IN THE WORLD. ALL RECONDITIONED AND CHECKED OUT TO ORIGINAL SPECS. IN OUR OWN COMPLETELY EQUIPPED SHOP.

RADAR—COMMUNICATIONS—TEST EQUIPMENT

APS-2 S-band search radar
 APS-3 X-band search & homing radar
 APS-4 X-band search & homing radar
 APS-6 X-band search & gun laying radar
 APS-10 X-band search & navigation radar
 APS-15 X-band navigation & blind bombing radar
 SO-13 S-band marine radar
 SQ-10 CM portable radar
 TPS-1 portable search radar
 TPS-3 long range early warning ground radar
 VC-VE-VF-VG remote PPI radar indicators
 UPN-162 S-band toratron radar beacon
 SCR-602 early warning portable radar
 APN-19 airborne S-band radar beacon
 APQ-5 low alt. bombing attachment
 APA-10 panoramic adaptor
 APA-11 pulse analyzer used with APR equip.
 APA-17 automatic bearing indicator used with APR equip.
 APA-23 automatic sig. strength & time recorder
 APA-38 panoramic adapter 30 MC input used with APR equip.
 APR-1 radar search rec. 38-1000 MC
 APR-2 radar search rec. 85-1000 MC
 APR-4 radar search rec. 38-4000 MC
 APR-5 radar search rec. 1000-3100 MC
 APR-6 radar search rec. 6000-10000 MC
 APT-4 radar jammer 165-780 MC
 APT-5 radar jammer uses 3C22 osc.
 APN-4 airborne loran
 APN-9 airborne loran
 CPN-8 10 CM high pow. ground radar beacon

APN-1 altimeter
 CRT-3 du l freq. victory girl
 PPN-1 Reflex transmitter used with APN2
 ARQ-5 automatic panoramic rec. 18-80 MC
 ARN-7 automatic radio direction finder
 SCR-555 direction finder 18-85 MCS
 SCR-284 portable field radio station
 AN TR-2 remote control equipment
 SCR-619 freq. mod. field radio 120 channel
 AN/ARC-1 radio tele. trans./rec.
 SCR-522 V.H.F. trans./rec. 100-156 MCS
 SCR-269G automatic R.D.F.
 AN/ARN-7 automatic R.D.F.
 SCR-291 radio direction finder
 AN/TRC-1 V.H.F. radio tele. relay station
 RC-261 radio remote control with RM-53, 52
 BC-639 rec. 100-156 MC with RA42 power supply
 BC-902 port. marker beacon xmitter 75 MCS
 RC-103 instr. landing system
 SCR-718C high altitude radio altimeter
 SCR-536 hand-talkies 3-6 MC batt. oper.
 AN/CRC-7 V.H.F. hand-talkies 1-2 MC
 RC-191 transmitter
 BC-325 airport high pwr. xmitter 50 watt
 BC-640 xmitter 100-156 MC
 DAK automatic direction finder marine
 RAK-7 rec. w/p.s. 15-500 KC 110 w. 60 eye.
 TCS marine equipment 1.5-12 MCS
 BC-348 rec. 1700 KC-18 MC & 200-400 KC
 BC-342 rec. 1700 KC-18 MC 115 v. 60 eye

TS- 3/AP S-band pwr. & freq. mtr.
 TS- 10/AP altimeter test set
 TS- 12/AP X-band VSWR test set
 TS- 13/AP X-band sig. gen. pwr. & freq. mtr.
 TS- 14/AP S-band sig. gen. & pwr. mtr.
 TS- 15/AP fluxmeter
 TS- 16/AP altimeter test set
 TS- 23/APN SCR-718 test set
 TS- 24/ARR2 test set
 TS- 32/AP TRC-1 test oscillator
 TS- 33/AP power test meter
 TS- 34/AP portable stroboscope
 TS- 35/AP X-band sig. gen. pwr. & freq. mtr.
 TS- 36/AP X-band pwr. mtr. batt. oper.
 TS- 45/AP X-band sig. gen. pwr. mtr.
 TS- 56/AP L-band slotted line
 TS- 59/APN altimeter test set
 TS- 61/AP S-band echo box
 TS- 62/AP ARN5 I.L.S. test set
 TS- 67/AP cavity type freq. mtr.
 TS- 69/AP voltage divider
 TS- 88/AP pulse voltage divider
 TS- 102/AP wavelength calibrator
 TS- 111/AP S-band wave meter
 TS- 114/AP APS2 radar test set
 TS- 125/AP S-band pwr. pwr. mtr.
 TS- 127/AP U freq. meter 300-750 MC
 TS- 148/UP 3 CM spectrum analyzer
 TS- 155/UP S-band sig. gen. pwr. freq. mtr.
 TS- 170/ARN5 I.L.S. field test set
 TS- 184/AP echo box & attenuator
 TS- 226/AP pwr. mtr. 300-1000 MC to 1 kW peak
 TS- 268/UP crystal diode test set
 I-100 radio compass test set
 I-208 tank radio test set
 CW-60/ABM S-band freq. meter
 BC-221 Freq. mtr. Mod. & unmod.
 IE-19 ARC-1 SCR-522 comp. test set
 IE-36 SCR-322 test set

FAMOUS MAKE PANEL METERS
 2" sq., any range milliammeter, d.c. voltmeter, r.f. ammeter. Large selection available.
\$295 EA.
 WHILE THEY LAST!!

SPECIAL Give Away Offer
EIMAC TYPE 100TH TUBES
3 FOR \$15.50
 NEW - - - GUARANTEED

ONE MILLION TUBES
In Stock At Low Prices
 Receiving, Transmitting, Special Purpose, Cathode Ray, Klystrons, Magnetrons, Crystal Diodes. New, Standard Brands, Guaranteed.

EXPORTERS • GOVERNMENT AGENCIES • LABORATORIES • SCHOOLS!!
 Consult us. Come to the source. Warehouses of our own stock. We will buy, sell or swap in any quantity. Space limits complete listings. Write for our catalog.
RADIO HAM SHACK, INC.
 Cable: "Hamshack N. Y."
 New York 13, N. Y. **CAnal 6-8446-7-8-9**

x 2" and uses three 12AX7 tubes. It comes complete with a 7 foot power cord and 7 foot connector cable and plug. It incorporates five controls: crossover, roll-off, volume, bass tone, and treble tone.

The company will forward a data sheet on request.

NEW V-M CHANGERS
 V-M Corporation of Benton Harbor, Michigan is now offering a high-fidelity record changer, the Model 935HF, to the trade.

The new unit features an exclusive die-cast aluminum tone arm which is rigid and resonance-free to eliminate tonal distortion, two plug-in tone arm



heads (less cartridges), a laminated turntable with precision-formed concentricity and heavy flocking, a four-pole four-coil motor which is said to eliminate the source of electronic hum and rumble during operation, and a muting switch for absolute quiet during the change cycle.

A brochure on this changer is available from the company on request.

MORE QUIETROLE
 TRADE MARK REG. U.S. PAT. OFF.
 is purchased by
MORE USERS
 than ever before...

Because it does more for the user than any other product of its kind. It is the original non-conductive, non-inflammable liquid that works magic on noisy TV and radio controls and switches. The choice of those who want the best, the standard since 1947. Keeps customers happy, puts money in your pocket.



Carried by leading jobbers everywhere!
 manufactured by
QUIETROLE COMPANY
 Spartanburg, South Carolina



"Mr. Elkins, this floors me... a genuine JENSEN DIAMOND NEEDLE!"


(Advertisement)

SERVICE TESTER
 Electronic Measurements Corporation, 280 Lafayette Street, New York, N. Y. has announced the addition of a new tube-battery-ohm-capacity tester to its line of test equipment.

The Model 207 features a large, easy-to-read, 7 1/2" meter for counter use. It is a durable instrument that gives direct readings for all tubes through the standard emission method of testing. Four-position, lever-type switches are used and it is housed in a hand-rubbed portable oak carrying case with removable hinge cover. The counter model is the 207C while the portable case unit has been designated as the 207P.

BOGEN AUDIO EQUIPMENT
 David Bogen Company, Inc. of 29 Ninth Avenue, New York 14, New York has added an FM-AM radio receiver and an FM-AM radio tuner to its line.

The 10-tube radio receiver has been designated as the Model RR500. It provides both AM and FM reception, has an output of 10 watts at 3 percent distortion, and furnishes separate bass and treble tone correctors. The FM circuit features a triode r.f. amplifier and triode mixer for minimum noise and a balanced ratio detector. Sensitivity is 7 microvolts input for 30 db quieting and the frequency response is ± 2 db from 30 to 18,000 cps. Frequency response on AM is ± 3 db from 40 to 4000 cps.

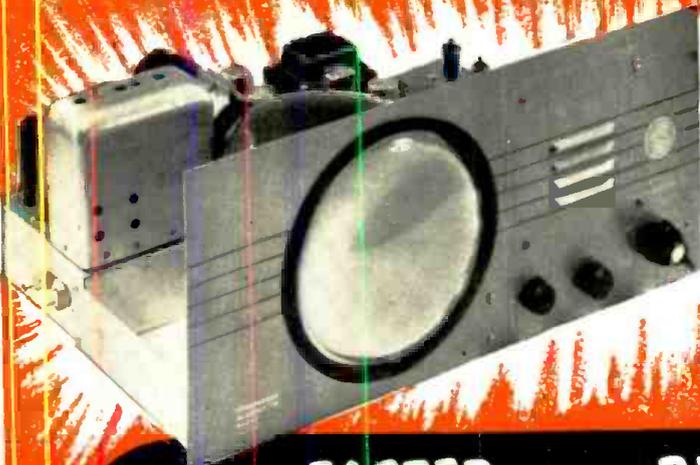

TRAIN **FASTER**—TRAIN **BETTER**—TRAIN **EASIER**
 IN 10 MONTHS—OR LESS—FOR
RADIO-TELEVISION

Our 21st Year Training Men for Greater Incomes and Security in Radio-Television

**I SEND YOU
 18 BIG KITS**

of Radio Television parts and equipment. Much of your training will be actual construction and experimentation . . . the kind of truly PRACTICAL instruction that prepares you for your Radio-Television career.




Frank L. Sprayberry
 President
 Sprayberry Academy
 of Radio

NEW! NO OBLIGATION PLAN

**You Have No Monthly Payment Contract to Sign
 Pay For Your Training as You Earn and Learn**

You can get into Radio-Television, today's fastest growing big money opportunity field, in *months* instead of years! My completely new "package unit" training plan prepares you in as little as 10 months or even less! *No monthly payment contract to sign—thus NO RISK to you!* This is America's finest, most complete, practical training—gets you ready to handle any practical job in the booming Radio-Television industry. Start your own profitable Radio-Television shop . . . or accept a good paying job. I have trained hundreds of successful Radio-Television technicians during the past 21 years—and stand ready to train you, even if you have no previous experience! Mail coupon and get all the facts—FREE!

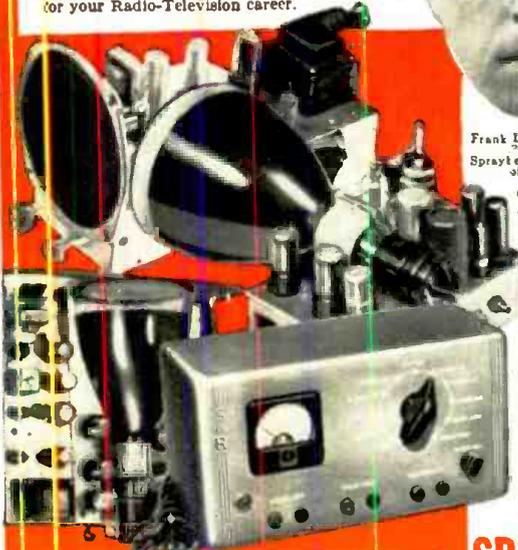

**Valuable Equipment Included
 With Training**

The new Sprayberry "package" plan includes many big kits of genuine, professional Radio-Television equipment. You perform over 300 demonstrations, experiments and construction projects. You build a powerful 6-tube 2-band radio set, multi-range test meter, signal generator, signal tracer, many other projects. All equipment and lessons are yours to keep . . . you have practically everything you need to set up your own profitable Radio-Television service shop.

Earn Extra Money While You Learn!

All your 10 months of training is IN YOUR HOME in spare hours. Keep on with your present job and income while learning. With each training "package" unit, you receive extra plans and "Business Builder" ideas for spare time Radio-Television jobs. New television stations everywhere, open vast new opportunities for trained Radio-Television Technicians—and those in training. If you expect to be in the armed forces later, there is no better preparation than practical Sprayberry Radio-Television training.

YOU BUILD

the Television set and the powerful superhet radio receiver shown above. IN ADDITION to the other test units shown here (many are not shown because of lack of space). All equipment I send you is **YOURS TO KEEP.**

Approved for Veterans under the G. I. Bill

SPRAYBERRY ACADEMY OF RADIO 111 NORTH CANAL ST.
 Dept. 25-A, Chicago 6, Ill.

**MAIL COUPON
 TODAY!
 NO OBLIGATION**

I invite you to get all the facts—
**FREE TO YOU 3 BIG
 RADIO-TELEVISION BOOKS**

I want you to have ALL the facts about my new 10-MONTH Radio-Television Training—without cost! Rush coupon for my three big Radio-Television books: "How to Make Money in Radio-Television." PLUS my new Illustrated Television Bulletin PLUS an actual sample Sprayberry Lesson—ALL FREE. No obligation and no salesman will call. Mail coupon NOW!

**SPRAYBERRY ACADEMY OF RADIO, Dept. 25-A
 111 North Canal St., Chicago 6, Ill.**

Please rush to me all information on your 10-MONTH Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Be sure to include 3 books FREE.

Name..... Age.....

Address.....

City..... Zone..... State.....

the new H. H. Scott "99"

\$99.95
net



THE TYPE 99-A TRANSCRIPTION AMPLIFIER

"That amplifier of yours is fantastic". So said a leading expert, hearing the "99" perform against amplifiers costing several times as much. Even we are flabbergasted (but happy) at the response — "When can I have one?", "That I want.", "Save me one of the first". The "99" is unique — a complete amplifier in one compact case with 4-position input selector, separate turn-over and rolloff record equalizers, treble and bass controls, adjustable loudness compensation and pickup-level control. See and hear an H. H. Scott amplifier at only 99.95 — the phenomenal "99".

FREE BOOKLET R-53

The tuner is known as the Model R300 and features separate bass and treble controls, automatic frequency control, and compensated preamp for use with magnetic pickups.

WEBCOR PHONOGRAPH

Webster-Chicago Corporation of Chicago, Illinois has recently introduced a high-quality, table-model phonograph which has been trademarked "Musicale."

According to the company, this new unit provides uniform audio response from 50 to 12,500 cps. It incorporates a 5-tube amplifier which includes a preamplifier for the G-E reluctance pickup with which the phonograph is



equipped. A loudness control is used to improve tonal quality at low levels.

The set uses three separate speakers, one 4-inch unit to handle the higher frequencies and two 6-inch speakers. The 4-inch speaker is mounted in the front of the case while the others are mounted on the sides. With this arrangement the high frequencies are still audible even when the listener moves at an angle from the speaker.

The "Musicale" is currently available in blonde korina and in mahogany finishes.

AMATEUR DESK SIGN

Hawkins Distributing Co., Paquetuck Terrace, East Moriches, New York is now offering a new amateur desk sign which features a sturdy, crystal-clear, plexiglas base and red or black polystyrene injection-molded letters 1 1/2" high.

The new sign is durable and may be washed in lukewarm water with mild soap when it becomes soiled.

A quantity price is available to radio clubs ordering lots of three or more. An order blank, giving full details on these units, will be forwarded on request.

SMALLEST PERSONAL PORTABLE

Emerson Radio and Phonograph Corporation of 111 Eighth Avenue, New York 11, New York has just introduced what is said to be the world's smallest personal portable receiver, the "Pocket Radio".

Catalogued as the Model 747, the unit weighs less than 1 pound and measures 6 inches in width and 1 1/4 inches in depth. It is small enough to

(Continued on page 110)

RADIO & TELEVISION NEWS

99 **HERMON SCOTT, INC.** **99**
"PACKAGED ENGINEERING"
385 PUTNAM AVE. • CAMBRIDGE 39, MASS.

AMPERITE

Studio Microphones at P.A. Prices

Ideal for BROADCASTING RECORDING PUBLIC ADDRESS

"The ultimate in microphone quality," says Evon Rushing, sound engineer of the Hotel New Yorker.

- Shout right into the new Amperite Microphone—or stand 2 feet away—reproduction is always perfect.
- Not affected by any climatic conditions.
- Guaranteed to withstand severe "knocking around."

Models
RBLG—200 ohms
RBHG—Hi-imp.
List \$42.00

"Kontak" Mikes
Model SKH, list \$120.00
Model KKH, list \$18.00

Special Offer: Write for Special Introductory Offer and 4-page illustrated folder

AMPERITE Company, Inc.
561 BROADWAY • NEW YORK 12, N. Y.
Canada: Atlas Radio Corp., Ltd., 560 King St. W., Toronto

New		Standard	
Guaranteed	TUBES	Standard	Brands
0A2	\$1.00	4-125A	22.50
0A3 VR75	1.10	4X150A	22.50
0A4G	1.00	4X500A	75.00
0B2	1.40	5B1	4.50
0C3 VR105	1.00	5C22	42.00
0D3 VR150	1.90	5D21	15.00
1A3	1.00	5FP7	1.95
1B23	8.95	5R4GV	1.25
1B24	9.50	5T4	1.50
1B26	2.30	6AL5W	1.75
1B27	12.50	6AN5	2.90
1N21B	2.50	811	10.95
1N22	1.25	812	2.75
1N23	1.25	815	3.95
1N23B	3.25	829	8.95
1N34A	7.50	829B	9.95
1N38	1.50	830B	2.75
1N58A	1.25	832A	9.50
1N63	2.15	836	1.45
1N69	1.89	837	1.45
1N70	2.59	849	29.50
2D215	4.25	852	19.95
2C39	19.95	6A56	2.30
2C39A	22.00	6BL6	69.50
2C40	7.25	6F06	69.50
2C42	19.95	6F4	5.25
2C44	1.19	6J4	5.25
2C46	19.95	6K4	3.50
2C51	4.50	1SE	.89
2C52	4.95	1SR	.89
2D21	2.49	FG17	3.95
2D21W	1.95	FG32	12.32
2E22	4.95	FG57	14.95
2E24	4.95	FG95	2.00
2E25A	3.25	RK60 1641	2.25
2E26	32.50	FG104	24.50
2K23	28.50	VT-127A	2.95
2K25	75.00	100TH	9.50
2K26	32.00	250TH	16.50
2K28	32.00	304TH	7.95
2K34	179.50	304TL	7.95
2K41	110.00	307A RK75	3.95
2K45	110.00	310A	4.95
2K48	99.50	350B	3.95
3A4	7.50	394A	3.95
3A5	1.25	417A	8.50
3B23	4.95	446A	44.49
3B24	4.75	450TH	44.49
3B25	4.95	527	11.50
3B26	3.95	575A	13.95
3B28	6.50		
3C22	72.50		
3C23	32.95		
3C24/24G	1.50		
3C33	9.95		
3C45	11.95		
3E29	11.95		
3FP7	1.95		
3IP1	3.95		
3HP7	3.95		
3K30	299.50		
4B24	6.95		
4C27	17.50		
4C28	35.00		
4C35	22.00		
4E27	14.50		
4-65A	17.00		
703A	4.50		
705A	1.50		
707B	14.95		
715B	8.95		
715C	18.00		
717A	9.00		
722A	1.95		
723A B	16.95		
724B	2.75		
726B	45.00		
726C	69.70		
801A	3.99		
803	3.95		
807	1.65		
808	2.95		
809	2.95		
811	2.90		
813	10.95		
814	2.75		
815	3.95		
829	8.95		
829B	9.95		
830B	2.75		
832A	9.50		
836	1.45		
837	1.45		
849	29.50		
852	19.95		
860	4.50		
861	14.95		
866A	1.50		
872A	3.25		
884	1.40		
931A	5.50		
957	.33		
958	.49		
959	.49		
959A	.69		
959B	2.45		
1005	.39		
1006	.69		
1616	2.75		
1625	.90		
1626	.39		
1626	.39		
2051	1.10		
2050	1.40		
2051	1.10		
5651	2.75		
5670	2.00		
5677	4.30		
5718	2.95		
5719	8.95		
5726	8.95		
5749	2.25		
5814	2.50		
5844	4.50		
8005	5.95		
8012	1.95		
8014A	55.00		
8025A	4.95		
9001	1.25		
9002	1.25		
9003	1.50		
9004	.49		
9005	1.50		
9006	.49		

WE PAY HIGHEST PRICES FOR YOUR SURPLUS!

Vacuum Capacitors

Complete line of Receiving Tubes. Thousands of other types of Transmitting Tubes. If you don't see it, WRITE. Prices subject to change without notice. Californians add sales tax. Add postage to order.

Jsh ELECTRONICS
Dept. R-25
7552 Melrose Ave.
Los Angeles 46, California

12 reasons why it pays to replace with SYLVANIA PICTURE TUBES

Independent laboratory tests show these 12 outstanding qualities of Sylvania Picture Tubes

- | | |
|---|---|
| 1. No tube failures (after 1500 hours). | 7. No stray emission. |
| 2. No trend toward slumping emission or low light output. | 8. Low electrical breakdown. |
| 3. No excessive leakage. | 9. Very good color control. |
| 4. No excessive gas present. | 10. Excellent spot centering. |
| 5. Excellent grid control. | 11. Low screen burning (no rejections). |
| 6. Excellent emission characteristics. | 12. Excellent physical conditions. |

**Only Sylvania showed
no tube failures**

Here is proof that Sylvania Picture Tubes are *first* in long life and *finest* in all around performance of all tubes tested.

The above record was established in comparison tests of the tubes of 9 different manufacturers. All tests were conducted under identical conditions by an outside testing agency.

See owners everywhere are being told again and again about Sylvania's superiority on the big, nationwide TV show "Beat the Clock."

The Picture Tube for Reliable Replacement

Of course, the name Sylvania has always stood for highest quality. Now, more than ever before, Sylvania Picture Tubes mean better business for jobbers and service-dealers alike. If you would like the full story of these recent tests to show your customers how Sylvania Picture Tubes won over all others tested, simply mail the coupon now.



Send
for this
report



Sylvania Electric Products Inc.
Dept. 3R-2109, 1740 Broadway, N. Y. 19, N. Y.

Please send me the official report of the tests made on Sylvania Picture Tubes in competition with other makes.

Name _____

Company _____


Street _____

City _____ Zone _____ State _____

SYLVANIA

LIGHTING • RADIO • ELECTRONICS • TELEVISION

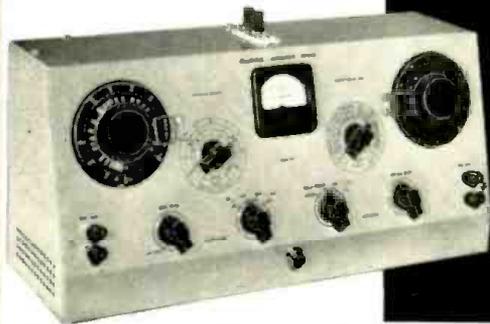In Canada: Sylvania Electric (Canada) Ltd., University Tower Bldg.
St. Catherine St., Montreal, P. Q.



Heathkit IMPEDANCE BRIDGE KIT

MODEL IB-2

\$59⁵⁰

SHIPPING WT.
15 LBS.

Another new, outstanding instrument design so typically characteristic of Heathkit operation in producing high quality instrument kits at the lowest possible price. A new, improved model Impedance Bridge kit featuring modern cabinet styling, with slanted panel for convenience of operation and interpretation of scales at a \$10.00 price reduction over the preceding model. Built-in adjustable phase shift oscillator and amplifier with all tubes of the battery operated type completely eliminates warm-up time. The instrument is entirely AC line operated. No bothersome battery replacements.

The Heathkit IB-2 Impedance Bridge Kit actually represents four instruments in one compact unit. The Wheatstone Bridge for resistance measurements, the Capacity Comparison Bridge for capacity measurements, Maxwell Bridge for low Q, and Hay Bridge for high Q inductance measurements. Read Q, D, DQ all on one dial thereby eliminating possible confusion due to the incorrect dial reference or adjustment. Only one set of instrument terminals nec-

essary for any measurement function. Panel provisions provided for external generator use.

A newly designed two section CRL dial provides ten separate "units" switch settings with an accuracy of .5%. Fractions of units are read on a continuously variable calibrated wire-wound control. A special minimum capacity, shielded, balanced impedance matching transformer between the generator and the bridge. The correct impedance match is automatically switch selected to provide constant load operation of the generator circuit. The instrument uses 1/2% precision resistors and condensers in all measurement circuits.

The new Heathkit IB-2 provides outstanding design features not found in any other kit instrument. The single low price includes the power supply, generator, and amplifier stages. No need to purchase separate instrument accessories in order to obtain the type of operation desired.

Features

- Simpson 100-0-100 microampere meter.
- Completely AC operated.
- Built-in phase shift generator and amplifier.
- Battery type tubes, no warm-up required.
- Newly designed two section CRL dial.
- Single knob D, Q, and DQ functions.
- Special impedance matching transformer.
- New modern cabinet styling.
- 1/2% precision resistors and silver mica condensers.

Heathkit AUDIO WATTMETER KIT



MODEL AW-1

\$29⁵⁰

SHIPPING WT.
6 LBS.

A new Heathkit design for the audio engineer, serious hi fi enthusiast, recording studio, or broadcast station; the Heathkit Audio Wattmeter Kit. This specialized instrument instantly indicates the output level of the equipment under test without requiring the use of external load resistors. All readings are taken directly from the calibrated scales of a 4 1/2" 200 microampere Simpson meter.

The Heathkit Audio Wattmeter features five full scale power measurement ranges from 5 milliwatts up to 50 watts with db ranges of -15 db to +48 db. The instrument has a power measurement rating of 25 watts continuous and 50 watts maximum for intermittent operation. Non-inductive resistance load impedances of 4, 8, 16, and 600 ohms are provided through a panel impedance selector switch. Frequency effect is negligible from 10 cycles to 250 kc. A conventional VTVM circuit utilizes a 12AU7 twin triode tube. The meter bridge circuit uses four germanium diodes for good linearity.

With the Heathkit AW-1 desired information can be obtained instantly and conveniently without bothering with the irksome setups and calculations usually required. Useful for power curve measurements, frequency response checks, monitoring indicator, etc. Convenient calibration directly from 110 volt AC line source. This new instrument will help to supply the answers to your audio operating or power output problems.

Heathkit LABORATORY GENERATOR KIT



MODEL LG-1

\$39⁵⁰

SHIP. WT.
16 LBS.

Another welcome new addition to the popular line of Heathkit instruments, the Heathkit Laboratory Generator. Specifically designed for flexibility of operation, accuracy and versatility beyond the performance level provided by the conventional service type generator. Frequency coverage of the Colpitts oscillator is 150kc to 30mc in five convenient ranges with provisions for internal or external modulation up to 50% and .1 volt RF output throughout the frequency range. Panel mounted 200 microampere Simpson meter for RF "set reference level" to provide relative indication of RF output. Individually shielded oscillator and shielded variable and step attenuator provide flexible control of RF output.

The circuit features a 6AF4 high frequency oscillator, a 6AV5 amplifier with grid modulation, 12AU7 400 cycle oscillator and modulator, OB2 voltage regulator tube, and a selenium rectifier for the transformer operated power supply. The smart professional instrument appearance and over-all flexibility of operation will prove a decided asset to any industrial or educational laboratory. The Heathkit Laboratory Generator sets a new level of operation, far superior to any instrument in this price classification.

HEATH COMPANY • Benton Harbor 15, Mich.

CHECK THESE *Features*

- ✓ New 5U1 CR tube
- ✓ Re-trace blanking
- ✓ Voltage regulation
- ✓ Extended band width
- ✓ Peak-to-peak calibrating provisions
- ✓ Good square wave response
- ✓ Astigmatism control
- ✓ New heavy duty shielded power transformer

NEW 5" *Heathkit*
**OSCILLOSCOPE
KIT**

MODEL O-9

\$59⁵⁰

SHIPPING
WT. 28 LBS.



Announcing the latest addition to a brilliant series of Heathkit Oscilloscopes, the new Model O-9. This outstanding instrument incorporates all of the features developed and proven in the production of well over 50,000 kits, in addition to a host of many new design features for truly outstanding performance. This new scope features a brand new (no surplus) commercially available 5U1P1 cathode ray tube for fine focusing, high intensity, and freedom from halation. The 5" CR tube is the standard size for design and industrial laboratories, development engineers, and service men. The only size CR tube offering a wide range of types, colors, phosphors, and persistence. The answer to good oscilloscope performance lies in improved basic design and operating characteristics, and not in the use of larger CR tubes.

VERTICAL AMPLIFIER — New extended band width vertical amplifier with sensitivity of .025 volts per inch down 3 db at 2 mc, down only 51 db at 5 mc. Three step vertical input attenuator, quality ceramic variable capacitors for proper input compensation, provisions for calibrated 1 volt peak-to-peak reference, with calibrated screen for direct reading of TV pulses.

HORIZONTAL AMPLIFIER — New input selector switch provides choice of horizontal input, 60 cycle sweep input, line sync, internal sync, and external sync. Expanded horizontal sweep produces sweep width several times the cathode ray tube diameter. New blanking amplifier for complete retrace blanking and new phasing control.

POWER SUPPLY — New high voltage power supply and filtering circuit for really fine hairline focusing. New heavy duty power transformer with adequate operating reserve. Voltage regulated supply for both vertical and horizontal amplifiers for absolutely rock steady traces and complete freedom from bounce and jitter due to line variations.

The acid test of any oscilloscope operation is the ability to reproduce high frequency square waves and the new Heathkit O-9 will faithfully reproduce square waves up to 500 kc. This is the ideal all around, general purpose oscilloscope for educational and industrial use, radio and TV servicing, and any other type of work requiring the instantaneous reproduction and observation of actual wave forms and other electrical phenomena.

Heathkit **LOW CAPACITY
PROBE KIT**



NO. 342
\$3⁵⁰ SHIP. WT.
1 LB.

Oscilloscope investigation of high frequency, high impedance, or broad bandwidth circuits encountered in television work requires the use of a low capacity probe to prevent loss of gain, distortion, or false service information. The Heathkit Low Capacity Probe features a variable capacitor to provide the necessary degree of instrument impedance matching. New probe styling with bright polished aluminum housing and polystyrene probe ends.




NO. 337-B
\$3⁵⁰
SHIP. WT. 1 LB.

Heathkit
**SCOPE DEMODULATOR
PROBE KIT**

In applications such as trouble shooting or aligning TV, RF, IF, and video stages, the frequency ranges encountered require demodulation of signals before oscilloscope presentation. The newly-styled Heathkit Demodulator Probe in polished aluminum housing will fulfill this function and readily prove its value as an oscilloscope service accessory. Detailed assembly sheet provided, including instructions for probe operation.

Heathkit
VOLTAGE CALIBRATOR KIT

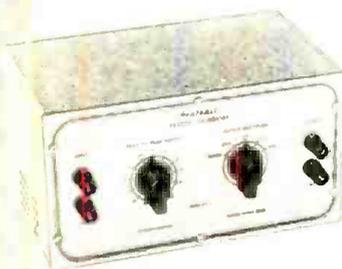

MODEL VC-2
\$11⁵⁰
SHIPPING WT.
4 LBS.

The Heathkit Voltage Calibrator provides a convenient method of making peak-to-peak voltage measurements with an oscilloscope by establishing a relationship on a comparison basis between the amplitude of an unknown wave shape and the known output of the voltage calibrator. Peak-to-peak voltage values are read directly on the calibrated panel scales. To offset line voltage supply irregularities, the instrument features a voltage regulator tube.

With the Heathkit Voltage Calibrator, it is possible to measure all types of complex wave forms within a voltage range of .01 to 100 volts peak-to-peak. A convenient "signal" position on the panel switch bypasses the calibrator completely and the signal is applied to the oscilloscope input thereby eliminating the necessity for transferring test leads.

Heathkit
**ELECTRONIC SWITCH
KIT**



MODEL S-2
\$23⁵⁰
SHIP. WT. 11 LBS.

The basic function of the Heathkit S-2 Electronic Switch Kit is to permit simultaneous oscilloscope observation of two separate traces which can be either separated or superimposed for individual study. A typical example would be observation of a signal as it appears at both the input and output stages of an amplifier. It will also serve as a square wave generator over the range of switching frequencies, often providing the necessary wave form response information without incurring the expense of an additional instrument.

Continuously variable switching rates in three ranges from less than 10 cps to over 2,000 cps. Individual controls for each input channel and a positioning control. The five tube transformer operated circuit utilizes two 6SJ7, two 6SN7, and one 6X5 tubes. Buy this kit and enjoy increased versatility of operation from your oscilloscope.

HEATH COMPANY • Benton Harbor 15, Mich.



Heathkit VACUUM TUBE VOLTMETER KIT

MODEL V-6

\$24⁵⁰

SHIPPING WT. 6 LBS.

The beautiful Heathkit Model V-6 VTVM, the world's largest selling kit instrument, now offers many outstanding new features in addition to retaining all of the refinements developed and proven in the production of over 100,000 VTVM's. This is the basic measuring instrument for every branch of electronics. Easily meets all requirements for accuracy, stability, sensitivity, convenience of ranges, meter readability, and modern styling. It will accurately measure DC voltages, AC voltages, offers tremendous ohmmeter range coverage, and a complete db scale for a total of 35 meter ranges.

New 1½ volt full scale low range provides well over 2¼" of scale length per volt. Upper DC scale limit 1,500 volts. DC ranges 0-1.5, 5, 15, 50, 150, 500, 1,500 volts full scale. AC ranges 0-1.5, 5, 15, 50, 150, 500, 1,500 (1,000 volts maximum). Seven ohm-

meter ranges from .1 ohm to 1,000 megohms. For added convenience a DC polarity reversing switch and a center scale zero adjustment for FM alignment.

The smartly styled, compact, sturdy, formed aluminum cabinet is finished in an attractive gray crackle exterior. The beautiful two-color, durable, infra-red, baked enamel panel further adds to the over-all professional appearance.

Top quality components used throughout. 1% precision resistors — silver contact range and selector switches — selenium rectifier — transformer operated power supply. Individual calibration on both AC and DC for maximum accuracy. DB scale printed in red for easy identification, all other scales a sharp, crisp black for easy reading. A variety of accessory probes shown on this page still add further to over-all instrument usefulness.

Features

- ✓ New 1½ volt full scale low range
- ✓ 1,500 volt upper limit DC range
- ✓ Increased accuracy through 50% greater scale coverage
- ✓ High impedance 11 megohm input
- ✓ Center scale zero adjust
- ✓ Polarity reversal switch
- ✓ 1% precision resistors
- ✓ Clearly marked db scales

Heathkit 30,000 VOLT DC PROBE KIT

For TV service work or any similar application where the measurement of high DC voltage is required, the Heathkit Model 336 High Voltage Probe Kit will prove invaluable. A precision multiplier resistor mounted inside the two-color, sleek, plastic probe body provides a multiplication factor of 100 on the DC ranges of the Heathkit 11 megohm VTVM. The entire kit includes precision resistor, two-color plastic probe, tip connector spring, test lead, phone plug panel connector, and complete assembly instructions.



No. 336

\$4⁵⁰

SHIP. WT.
2 LBS.

No. 338-B

Heathkit PEAK-TO-PEAK PROBE KIT



\$5⁵⁰

SHIP. WT. 2 LBS.

Now read peak-to-peak voltages on the DC scales of the Heathkit 11 megohm VTVM. Readings can be directly made from the VTVM scale without involved calculations. Measurements over the frequency range of 5 kc to 5 mc. Use this probe to extend the usefulness of your VTVM in radio and TV service work. The Peak-to-Peak Probe Kit features the new polished aluminum housing with two-color polystyrene probe ends. Detailed assembly sheet including instructions for probe operation.

Heathkit RF PROBE KIT

The Heathkit RF Probe used in conjunction with any 11 megohm VTVM will permit RF measurements up to 250 mc. ± 10%. A useful, convenient accessory for those occasions when RF measurements are desired. The RF probe body is housed in the new, smartly-styled polished aluminum probe body featuring two-color polystyrene probe ends and a low capacity flexible shielded test lead. The kit is complete with all necessary material and a detailed assembly sheet as well as instructions for probe operation.



No. 309-B

\$3⁵⁰


SHIP. WT. 2 LBS.

Heathkit AC VACUUM TUBE VOLTMETER KIT

MODEL AV-2

\$29⁵⁰

SHIPPING WT.
5 LBS.

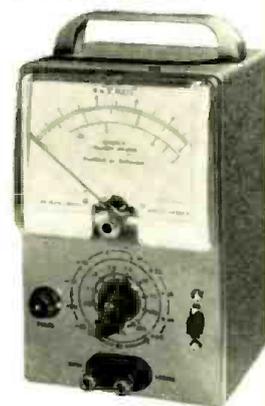

The new Heathkit AC VTVM that makes possible those sensitive AC measurements required by laboratories, audio enthusiasts, and experimenters. Especially useful for hum investigation, sensitive null detection, phono pick-up output measure-

ments, making frequency response runs, gain measurements, ripple voltage checks, etc. Low level measurements are easy to make because of the complete voltage coverage of the instrument and the one knob operation.

The large 200 microampere Simpson meter has clearly marked and easy to read meter scales. Ten voltage ranges covering from .01 rms full scale to 300 volts rms full scale, with frequency response ± 1 db from 20 cycles to 50,000 cycles. Instrument input impedance 1 megohm, ten db ranges from -52 db to +52 db. For stability and good linearity characteristics the meter bridge circuit features 4 germanium diodes. Attractive instrument styling, a companion piece for the popular Heathkit VTVM and the new AW-1 Audio Wattmeter.

HEATH COMPANY • Benton Harbor 15, Mich.

CHECK THESE *Features*

- ✓ 20,000 ohms per volt DC sensitivity, 5,000 ohms per volt on AC
- ✓ Polarity reversal switch
- ✓ 1% precision multiplier resistors
- ✓ 50 microampere 4½" Simpson meter
- ✓ Meter ranges for service convenience
- ✓ New resistor ring-switch assembly
- ✓ Total of 35 meter ranges
- ✓ New Modern cabinet styling

NEW *Heathkit*
**MULTIMETER
KIT**

MODEL MM-1
\$26⁵⁰
SHIPPING WT. 6 LBS.



The most important Heathkit announcement of the year, the new 20,000 ohms per volt Heathkit Multimeter, Model MM-1. The universal service measuring instrument, accurate, sensitive, portable, and completely independent of AC line supply. Particularly designed for service use incorporating many desirable features for the convenience of the service man. Full 20,000 ohms per volt sensitivity on DC ranges — 5,000 ohms per volt sensitivity on AC — polarity reversal switch, no bothersome transferring of test leads — 1% precision multiplier resistors — large 4½" recessed non-glare 50 microampere Simpson meter — conveniently slanted control panel — recessed safety type banana jacks — standard universally available batteries — rugged practical sized cabinet with plastic carrying handle, and a total of 35 calibrated meter ranges.

RANGES

Voltage ranges selected entirely for service convenience. For example 1½ volt full scale low range for measuring portable radio filament voltages, bias voltages, etc., 150 volt full scale range for AC-DC service work, 500 volt full scale range for conventional transformer operated power supply systems. Complete voltage ranges AC and DC, 0-1.5—5—50—150—500—1,500—5,000 volts. DC current ranges, 0-150 microamperes—15 milliamperes—150 milliamperes—500 milliamperes—15 amperes. Resistance measurements from .2 ohms to 20 meg-

ohms x 1 x 1,000 x 10,000.
DB coverage from -10 db to +65 db.

CONSTRUCTION


Entirely new design permits assembly, mounting and wiring of precision resistors on a ring-switch assembly unit. The major portion of instrument wiring is completed before mounting the ring-switch assembly to the panel. No calibration procedure is required, all precision resistors readily accessible in event of replacement.

CABINET

Strikingly modern cabinet styling featuring two piece construction, durable black Bakelite cabinet, with easy to read panel designations. Cabinet size 5½" wide x 4" deep x 7½" high. Good cabinet physical stability when operated in vertical position.

The Heathkit MM-1 represents a terrific instrument value for a high quality 20,000 ohms per volt unit using all 1% deposited carbon type precision resistors. Here is quality, performance, functional design, and attractive appearance, all combined in one low priced package.

Heathkit
BATTERY TESTER KIT

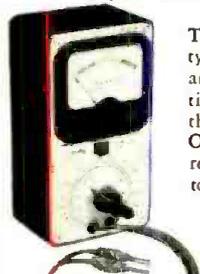

MODEL BT-1
\$8⁵⁰
SHIP. WT.
2 LBS.

The Heathkit Battery Tester measures all types of dry batteries between 1½ volts and 150 volts under actual load conditions. Readings are made directly on a three color Good-Weak-Replace scale. Operation is extremely simple and merely requires that the test leads be connected to the battery under test. Only one control to adjust in addition to a panel switch for "A" or "B" battery types. The Heathkit Battery Tester features compact assembly, accurate meter movement, and a three deck wire-wound control, all mounted in a portable rugged plastic cabinet. Checks portable radio batteries, hearing aid batteries, lantern batteries, etc.

Heathkit
HANDITESTER KIT



MODEL M-1
\$14⁵⁰
SHIPPING WT.
3 LBS.

The Heathkit Model M-1 Handitester readily fulfills major requirements for a compact, portable volt ohm milliammeter. Despite its compact size, the Handitester is packed with every desirable feature required in an instrument of this type. AC or DC voltage ranges full scale: 0-10—30—300—1,000—5,000 volts. Two ohmmeter ranges, 0-3,000 and 0-300,000. Two DC current measurement ranges, 0-10 milliamperes and 0-100 milliamperes. The instrument uses a Simpson 400 microampere meter movement, which is shunted with resistors to provide a uniform 1 milliampere load on both AC and DC ranges. Special type, easily accessible, battery mounting bracket — 1% deposited carbon type precision resistors — hearing aid type ohms adjust control. The Handitester is easily assembled from complete instructions and pictorial diagrams. Necessary test leads are included in the price of this popular kit.

HEATH COMPANY • Benton Harbor 15, Mich.



New *Heathkit* 12 Volt BATTERY ELIMINATOR KIT

MODEL BE-4

\$31⁵⁰

SHIPPING WT.
18 LBS.

CHECK THESE *Features*

- ✓ Either 6 or 12 volt operation
- ✓ Continuously variable voltage output
- ✓ Constant ammeter and voltmeter monitoring
- ✓ Automatic overload relay — self-resetting
- ✓ Two 10,000 mf condensers
- ✓ New 18 disc split type heavy duty rectifier unit
- ✓ Fuse protection

Here is the new Heathkit Battery Eliminator necessary for modern, up-to-date operation of your service shop. The Heathkit Model BE-4 furnishes either 6 volts or 12 volts output which can be selected at the flick of a panel switch. Use the BE-4 to service the new 12 volt car radios in addition to the conventional 6 volt radios.

This new Battery Eliminator provides two continuously variable output ranges, 0-8 volts DC at 10 amperes continuously, or 15 amperes maximum intermittent; 0-16 volts DC at 5 amperes continuously or 7.5 amperes maximum intermittent. The output voltage is clean and well filtered as the circuit uses two 10,000 mf condensers. The continuously variable voltage output feature is a definite aid in determining the starting point of vibrators, the voltage operating range of oscillator circuits, etc. Panel mounted meters constantly monitor voltage and cur-


rent output and will quickly indicate the presence of a major circuit fault in the equipment under test. The power transformer primary winding is fuse protected and for additional safety an automatic relay of the self-resetting type is incorporated in the DC output circuit. The heavy duty rectifier is a split type 18 plate magnesium copper sulfide unit used either as a full wave rectifier or voltage doubler according to the position of the panel range switch.

Here is the ideal battery eliminator for all of your service problems and as an additional feature, it can also be used as a battery charger. Another new application for the Heathkit Battery Eliminator is a variable source of DC filament supply in audio development and research. More than adequate variable voltage and current range for normal applications.

Heathkit VIBRATOR TESTER KIT

Your repair time is valuable, and service use of the Heathkit Vibrator Tester will save you many hours of work. This tester will instantly tell you the condition of the vibrator being checked. Checks vibrators for proper starting and the easy to read meter indicates quality of output on a large Bad?-Good scale. The Heathkit VT-1 checks both interrupter and self rectifier types of vibrators. Five different sockets for checking hundreds of vibrator types.

The Heathkit Vibrator Tester operates from any battery eliminator capable of delivering continuously variable voltage from 4 to 6 volts DC at 4 amperes. The new Heathkit Model BE-4 Battery Eliminator would be an ideal source of supply.

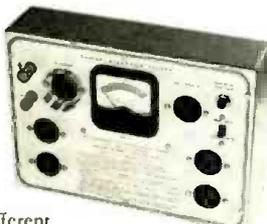

MODEL VT-1

\$14⁵⁰

SHIPPING WT.
6 LBS.

NEW *Heathkit* VARIABLE VOLTAGE ISOLATION TRANSFORMER KIT


The new Heathkit Isolation Transformer Kit provides line isolation for AC-DC radios (not an auto transformer), thereby eliminating shock hazard, hum problems, alignment difficulties, etc. The output voltage is variable from 90 to 130 volts AC and is constantly monitored by a panel mounted AC voltmeter. Use it to increase AC supply voltage in order to induce breakdown of faulty components in circuits thereby saving service time. Use it also to simulate varying line voltage conditions and to determine the line voltage level at which oscillator circuits cease functioning, particularly in three-way portable radios. Rated at 100 watts continuous operation and up to 200 watts maximum intermittent operation. A useful radio and TV service tool.



MODEL IT-1


\$16⁵⁰

SHIP. WT. 9 LBS.

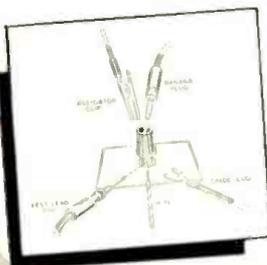

Heathkit BINDING POST

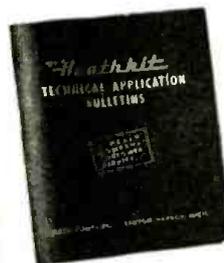Binding post kit now available so that standardization of all instrument connectors is possible. This new, five-way binding post will accommodate an alligator clip, banana plug, test lead pin, spade lug, or hook-up wire. Sold in units of 20 binding post assemblies. Each assembly includes binding post, flat and shoulder fiber washers, solder lug, and nut. 120 pieces in all. Kit 362, \$4.00.



Heathkit

TECHNICAL APPLICATION BULLETINS

An exclusive Heathkit service. Technical application bulletins prepared by recognized instrument authorities outlining various combinations of instrument applications. Available now with 40 four-page illustrated bulletins and an attractive flexible loose-leaf binder. Only \$2.00. (No c.o.d. on this item, please.)

HEATH COMPANY • Benton Harbor 15, Mich.

CHECK THESE *Features*


- ✓ INCREDUCTOR controllable inductor sweep
- ✓ TV and IF sweep deviation 12-30 mc
- ✓ 4 mc- 220 mc continuous frequency coverage
- ✓ Oscillator operation entirely on fundamentals
- ✓ Output in excess of 100,000 microvolts
- ✓ Automatic amplitude circuit
- ✓ Voltage regulation
- ✓ Simplified operation

NEW *Heathkit*
**TV ALIGNMENT
GENERATOR
KIT**

MODEL TS-3

\$44.50

SHIPPING WEIGHT
18 POUNDS

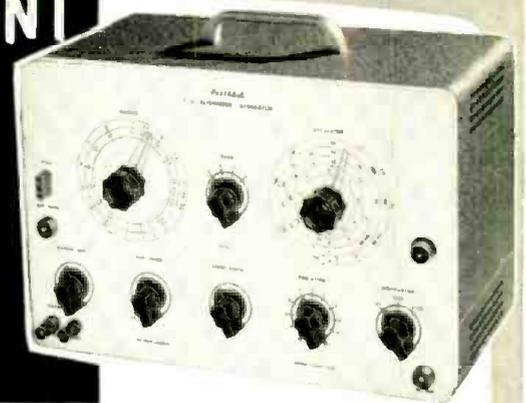

Proudly announcing an entirely new, advanced model TV and FM Sweep Generator, the Heathkit Model TS-3. This new design provides features and combinations of functions not found in any other service type instrument. Every design consideration has been given to the requirements of the TV service man to provide a flexible, variable sweep source with more than adequate RF output and complete frequency coverage throughout the TV and FM spectrum.

The frequency range of the TS-3 is from 4 mc to 220 mc in four switch selected ranges. All frequency ranges are overlapping for complete coverage. A particularly important feature of the instrument is that the oscillator operates entirely on fundamentals, thereby providing complete freedom from spurious oscillation and parasitics normally encountered in beat frequency type oscillators. This circuitry assures a much higher total RF output level and simplifies attenuation problems.

The new TS-3 features an entirely new principle of sweep operation. Sweep action is entirely electronic with no moving parts or electro-mechanical devices so commonly used. The heart of the sweep system is a newly-developed INCREDUCTOR controllable inductor. With this system, the value of inductance of each oscil-

lator coil is electrically varied with an AC control current, and the inductance variation is achieved by a change in the magnetic state of the core on which the oscillator coils are wound. This system provides a sweep deviation of not less than 12 mc on all TV frequencies, and up to a maximum of 30 mc on TV IF frequencies. The high RF output level throughout the instrument frequency range overcomes the most common complaint of the older type sweep generators. A new, automatic amplitude control circuit maintains the output level flat to ± 2 db throughout the instrument range. For convenience of operation a low impedance 50 ohm output is used.

Operation of the instrument has been simplified through the reduction of panel controls and separate panel terminals provide for external synchronization if desired. The circuit uses a voltage regulator tube to maintain stable instrument operation. A built-in variable oscillator marker further adds to flexibility of instrument operation. Provisions are also made for the use of an external marker, such as your service type signal generator, if desired. Use the Heathkit TS-3 for rapid, accurate TV alignment work, and let it help you solve those time consuming, irksome problems so frequently encountered.

NEW *Heathkit*

SIGNAL GENERATOR KIT

MODEL SG-8

\$19.50

SHIPPING WEIGHT
8 POUNDS



Announcing the new Heathkit Model SG-8 service type Signal Generator, incorporating many design features not usually found in an instrument in this price range. The RF

output is from 160 kc to 100 mc in five ranges, all on fundamentals, with useful harmonics up to 200 mc. The RF output level is in excess of 100,000 microvolts throughout the frequency range.

The oscillator circuit consists of a 12AT7 twin triode tube. One half is used as a Colpitts oscillator, and the other half as a cathode follower output which acts as a buffer between the oscillator and external load. This circuitry eliminates oscillator frequency shift usually caused by external circuit loading.

All coils are factory wound and adjusted, thereby completely eliminating the need for calibration and the use of additional calibrating equipment. The stable low impedance output features a step and variable attenuator for complete control of RF level. A 6C4 triode acts as a 400 cycle sine wave oscillator and a panel switching system permits a choice of either external or internal modulation.

The transformer operated circuit is easy to assemble, requires no calibration, and meets every service requirement for an adjustable level variable frequency signal source, either modulated or un-modulated.

NEW *Heathkit*

BAR GENERATOR KIT

MODEL BG-1

\$14.50

SHIPPING WEIGHT
6 POUNDS



The Heathkit BG-1 Bar Generator represents another welcome addition to the fast growing line of popular Heathkits. The

bar generator is the logical answer to the TV service man's problem in obtaining quick, accurate adjustment information without waiting for test patterns.

The Heathkit BG-1 produces a series of horizontal or vertical bars on a TV screen. Since these bars are equally spaced, they will quickly indicate picture linearity of the receiver under test. Panel switch provides "stand-by position" — "horizontal position" — "vertical position." The oscillator unit utilizes a 12AT7 twin triode for the RF oscillator and video carrier frequencies. A neon relaxation oscillator provides low frequency for vertical linearity tests. The instrument will not only produce bar patterns but will also provide an indication of horizontal and vertical sync circuit stability, as well as overall picture size.

Instrument operation is extremely simple, and merely requires connection to the TV receiver antenna terminal. The unit is transformer operated for safety when used in conjunction with universal or transformerless type TV circuits.

HEATH COMPANY • Benton Harbor 15, Mich.



NEW *Heathkit* TUBE CHECKER KIT

MODEL TC-2

\$29⁵⁰

SHIP. WT. 12 LBS.

The new Model TC-2 Heathkit Tube Checker features many circuit improvements, simplified wiring, new roll chart drive and illumination of roll chart. The instrument is primarily designed for the convenience of the radio and TV service man and will check the operating quality of tubes commonly encountered in this type of work. Test set-up procedure is simplified, rapid, and flexible. Panel sockets accommodate 4, 5, 6, and 7 pin tubes, octal and loctal, 7 and 9 pin miniatures, 5 pin Hytron and a blank socket for new tubes. Built-in neon short indicator, individual three-position lever switch for each tube element, spring return test switch, 14 filament voltage ranges, and line set control to compensate for supply voltage variations, all represent important design features of the TC-2. Results of tube tests are read directly from a large 4½" Simpson three-color meter, calibrated in terms of Bad?-Good. Information that your customer can readily understand. Checks emission, shorted elements, open elements, and continuity.

The use of closer tolerance resistors in critical circuits assures correct test information and eliminates the possibility of inaccurate test interpretation. Improvement has been made in the mechanical roll chart drive system, completely eliminating diagonal running, erratic operation, and backlash. The thumb wheel gear driven action is smooth, positive, and free running. As an additional feature, the roll chart is illuminated for easier reading, particularly when the tube checker is used on radio or TV home service calls.

Wiring procedure has been simplified through the extended use of multi-colored, color coded wires, providing a harness type installation between tube sockets and lever switches. This procedure insures standard assembly and imparts that "factory built" appearance to instrument construction. Completely detailed information is furnished in the new step-by-step construction manual, regarding the set-up procedure for testing of new or unlisted tube types. No delay necessary for release of factory data.

The new Heathkit Tube Checker will prove its value in building service prestige through usefulness — simplified operation — attractive professional appearance. Don't overlook the fact that the kit price represents a savings of \$40.00 to \$50.00 over the price of a comparable commercially built instrument. At this low price, no service man need be without the advantages offered by the Heathkit Tube Checker.

CHECK THESE NEW *Features*

- ✓ Simplified harness wiring
- ✓ Improved, smooth, anti-backlash roll chart action
- ✓ Optional roll chart illumination
- ✓ Individual element switches
- ✓ Portable or counter style cabinet
- ✓ Spare blank socket
- ✓ Contact type pilot light test socket
- ✓ Simplified test set-up procedure
- ✓ Line adjust control
- ✓ 4½" three-color meter

New

HEATHKIT

PORTABLE TUBE CHECKER KIT

MODEL TC-2P

\$34⁵⁰

SHIP. WT. 14 LBS.



The portable model is supplied with a strikingly attractive two-tone cabinet finished in rich maroon, proxylin impregnated, fabric covering with a contrasting gray on the inside cover. Detachable cover, brass-plated hardware, sturdy plastic handle help to impart a truly professional appearance to the instrument.

PORTABLE TUBE CHECKER CABINET as described above will fit all earlier Heathkit TC-1 Tube Checkers. Shipping weight 7 lbs. Cabinet only, 91-8, \$7.50.



Heathkit TV PICTURE TUBE TEST ADAPTER

The Heathkit TV Picture Tube Test Adapter used with the Heathkit Tube Checker will quickly check for emission, shorts, etc., and determine picture tube quality. Consists of standard 12 pin TV tube socket, four feet of cable, octal socket connector, and data sheet.

No. 355 **\$4⁵⁰**
Ship. Wt. 1 Lb.

Heathkit POWER SUPPLY KIT



MODEL PS-2

\$33⁵⁰

SHIPPING WT.
17 LBS.

The Heathkit Laboratory Power Supply features continuously variable, regulated voltage output with good stability under wide load variations. A 4½" Simpson plastic enclosed panel mounted meter provides accurate meter output information of voltage or current. All panel terminals completely isolated from the cabinet. Separate 6.3 volt AC supply at 4 amperes for filament requirements. Ripple component exceptionally low; stand-by switch provided to eliminate warm-up time of the five tube circuit.

LABORATORY AND SERVICE SHOP BOOKLETS



"Planning Your Service Business" by John T. Frye, and "Establishing the Industrial Electronics Laboratory" by Louis B. Garner, Jr., are booklets available to Heathkit customers at no charge. These booklets, written by nationally recognized authorities, outline the various requirements and considerations for establishing your own service business or for setting up an industrial electronics laboratory. Full attention is given to various details that are frequently overlooked when projects of this nature are undertaken. Just write in to the Heath Company requesting your free copy, or attach a memo to your next order.

HEATH COMPANY • Benton Harbor 15, Mich.

CHECK THESE *Features*

- ✓ Visual and aural signal tracing
- ✓ Two channel input
- ✓ High RF sensitivity
- ✓ Unique noise locator circuit
- ✓ Calibrated wattmeter
- ✓ Substitution test speaker
- ✓ Utility amplifier
- ✓ RF, audio probes and test leads included

Heathkit VISUAL-AURAL SIGNAL TRACER KIT

MODEL T-3
\$23⁵⁰

SHIPPING WEIGHT
10 POUNDS



An entirely new type of signal tracer incorporating a combination of features not found in any other instrument. Designed expressly for the radio and TV service man, particularly for the servicing of AM, FM, and TV circuits. Here in a five tube, transformer operated instrument are all of the useful functions so necessary for speedy, accurate isolation of service difficulty.

This new signal tracer features a special high gain RF input channel, used in conjunction with a newly-designed wide frequency range demodulator probe. High RF sensitivity permits signal tracing at the receiver antenna input. A separate low gain channel and probe available for audio circuit exploration. Both input channels are constantly monitored by an electron ray beam indicator, so that visual as well as aural signal indications may be observed. The instrument can also be used for comparative estimation of gain per stage.

A decidedly unusual feature is a noise localizer circuit in conjunction with the audio probe. With this system, a DC potential is applied to a suspected circuit component and the action of the

voltage in the component can be seen as well as heard. Invaluable for ferreting out noisy or intermittent condensers, noisy resistors, controls, coils, IF and power transformers, etc. A built-in calibrated wattmeter circuit is very useful for a quick preliminary check of the total wattage consumption of the equipment under test. Separate panel terminals provide external use of the speaker or output transformer for substitution purposes. Saves valuable service time by eliminating the necessity for speaker removal on every service job. The terminals also permit the utilization of other shop equipment, such as your oscilloscope or VTVM. The T-3 Signal Tracer can be used as a high gain amplifier for checking tuners, record changers, microphones, phono crystals, etc.

Don't overlook the interesting service possibilities provided through the use of this new instrument and let it work for you by saving time and money. The kit is supplied complete with all tubes, circuit components, demodulator probe, audio probe, and additional test leads.



Heathkit DECADE RESISTANCE KIT

MODEL DR-1
\$19⁵⁰
SHIP. WT.
4 LBS.
The Decade Resistance Kit provides individual switch selection of resistance values using twenty 1% resistors providing a choice of 1 to 99,999 ohms in 1 ohm steps. Ceramic wafer switches, silver-plated contacts, smooth, positive detent action, baked enamel panel, and handsome, polished birch cabinet.

Heathkit DECADE CONDENSER KIT

The Heathkit Decade Condenser Kit features silver mica, precision condensers with a rated accuracy of $\pm 1\%$. Capacity values are arranged in three decades from 100 mmf to .111 mf in steps of 100 mmf. Ceramic wafer switches with silver-plated contacts and smooth detent action. Useful in laboratory work, for circuit development.

MODEL DC-1
\$16⁵⁰
SHIP WT
4 LBS.




Heathkit RESISTANCE SUBSTITUTION BOX KIT



MODEL RS-1
\$5⁵⁰
SHIP. WT.
2 LBS.
The Heathkit Resistance Substitution Box provides individual switch selection of any one of 36 RTMA 1 watt 10% standard value resistors, ranging from 15 ohms to 10 megohms. Many applications in circuit development work, and also in radio and TV service work. Ideal for experimentally determining resistance values and for quickly altering circuit operating characteristics. Entire unit housed in attractive Bakelite cabinet, featuring the new universal type Heathkit binding posts to simplify circuit connections.

Heathkit CONDENSER CHECKER KIT

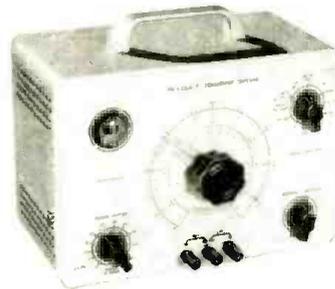

MODEL C-3
\$19⁵⁰
SHIPPING WT.
8 POUNDS

Use the Heathkit C-3 Condenser Checker to quickly and accurately measure those unknown condenser and resistor values. All readings are taken directly from the calibrated panel scales without requiring any involved calculation. Capacity measurements in four ranges from .00001 mf to 1,000 mf. Checks paper, mica, ceramic, and electrolytic condensers. A power factor control is available for accurate indication of electrolytic condenser measurements. A leakage test switch with switch selection of five polarizing voltages, 25 volts to 450 volts DC, will indicate condenser operating quality under actual load condition. The spring return leakage test switch automatically discharges the condenser under test and eliminates shock hazard to the operator.

Resistance measurements can be made in the range from 100 ohms to 5 megohms. Here again all values are read directly on the calibrated scale. Increased circuit sensitivity coupled with an electron beam null indicator increases overall instrument usefulness.

For safety of operation the circuit is entirely transformer operated and the instrument is housed in the attractive, newly-styled Heathkit cabinet, featuring rounded corners, and drawn aluminum panel. The outstanding low kit price for this surprisingly accurate instrument includes necessary test leads. Good service shop operation requires the use of this specialized instrument, designed for the express purpose of determining unknown condenser values and operating characteristics.

HEATH COMPANY • Benton Harbor 15, Mich.

Heathkit AMATEUR TRANSMITTER KIT

MODEL AT-1

\$29.50

SHIPPING WEIGHT
16 POUNDS



CHECK THESE NEW Features

- ✓ Single knob band switching
- ✓ Pre-wound coils
- ✓ Metered operation
- ✓ 52 ohm coaxial output
- ✓ Crystal or VFO excitation
- ✓ Built-in power supply
- ✓ Rugged, clean construction

Here is the latest Heathkit addition to the ham radio field, the AT-1 Transmitter Kit, incorporating many desirable design features at the lowest possible dollar-per-watts price. Panel mounted crystal socket, stand-by switch, key click filter, AC line filtering, good shielding, etc. VFO or crystal excitation—up to 35 watts input. Built-in power supply provides 425 volts at 100 ma.


This kit features pre-wound coils, single knob band switching, 52 ohm coaxial output, plug in chassis provisions for VFO or modulator and rugged clean construction. Frequency range 80, 40, 20,

15, 11, and 10 meters. Tube line-up 6AG7 oscillator-multiplier, 6L6 amplifier-doubler, 5U4G rectifier. Physical dimensions 8 1/8" high x 13 1/8" wide x 7" deep.

This amazingly low kit price includes all circuit components, tubes, cabinet, punched chassis, and detailed construction manual. The ideal kit for the novice just breaking into ham radio. It can be used later on as a stand-by rig or an all band exciter for higher powered transmitter.

NEW Heathkit ANTENNA COUPLER KIT

New Heathkit Antenna Coupler, specially designed for the Heathkit AT-1 Transmitter. The Antenna Coupler can be used with any 52 ohm coaxial input—up to 75 watts power. Low pass filter with cut-off frequency of approximately 36 mc — L section tuning network—neon tuning indicator—rugged, compact construction—transmitter type variable condenser, and high Q coil are all outstanding features. The AC-1 has both inductance and capacity tuning for maximum operating versatility. Dimensions 8 1/8" wide x 4 3/8" high x 4 3/8" deep.

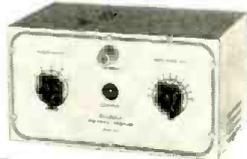

MODEL AC-1

\$14.50 SHIP. WT. 3 LBS.

Heathkit ANTENNA IMPEDANCE METER

Use the Heathkit Antenna Impedance Meter for measuring antenna impedance for line matching purposes—adjustment of beam antennas—phone monitor, etc. It will determine antenna resistance at resonance, match transmission line for minimum SWR, determine receiver input impedance, and provide a rough indication of SWR. Precision resistors, germanium diode, 100 micro-ampere Simpson meter. Dial calibrated from 0-500 ohms. Shielded aluminum cabinet. 7" long x 2 1/2" wide x 3 1/4" deep.

\$14.50

SHIP. WT. 3 LBS.



MODEL AM-1

Heathkit COMMUNICATIONS RECEIVER KIT

MODEL AR-2

\$25.50 SHIP. WT. 12 LBS.



Here is the new receiver kit you have repeatedly asked for, the Heathkit Communications Receiver. The perfect companion piece for the AT-1 Transmitter kit. Many outstandingly desirable features have been incorporated in the design of the AR-2; such as, electrical bandspread

for logging and tuning convenience—high gain miniature tubes—IF transformers for high sensitivity and good signal to noise ratio—separate RF gain control with optional automatic volume control or manual volume control, in addition to the conventional audio gain control. Noise limiter—stand-by switch—stable BFO oscillator circuit—headphone jack—transformer operation, etc., all contribute to a high performance standard.

Frequency coverage is continuous from 535 kc to 35 mc in four ranges. For added convenience, various ham bands have been separately identified in respect to their relative placement on the slide rule tuning scale. A chassis mounted, 5 1/2" PM speaker is included with this kit. Tube line up 12BE6 mixer oscillator, 12BA6 1F amplifier, 12AV6 detector AVC audio, 12BA6 BFO oscillator, 12A6 beam power output, 5Y3GT rectifier.

RECEIVER CABINET

Proxilyn impregnated, fabric covered, plywood cabinet with aluminum panel designed expressly for the AR-2 Receiver. Part 91-10, shipping weight 5 lbs., \$4.50.

IMPROVED Heathkit GRID DIP METER KIT

\$19.50 SHIP. WT. 4 LBS.

MODEL GD-1B

The invaluable instrument for service men, hams, and experimenters. Useful in TV service work for alignment of traps, filters, IF stages,

peaking compensation networks, etc. Locates spurious oscillation, provides a relative indication of power in

transmitter stages, use it for neutralization, locating parasitics, correcting TVI, measuring C, L, and Q of components, and determining RF circuit resonant frequencies. With oscillator energized, useful for finding resonant frequency of tuned circuits. With the oscillator not energized, the instrument acts as an absorption wave meter. Variable meter sensitivity control, head phone jack, 500 microampere Simpson meter. Continuous frequency coverage from 2 mc. to 250 mc. Pre-wound coil kit and rack, new three prong coil mounting. 6AF4 high frequency triode.

Two additional plug-in coils are available and provide continuous extension of low frequency coverage down to 355 kc. Dial correlation curves included. Shipping weight 1 lb., kit 341, \$3.00.



HEATH COMPANY • Benton Harbor 15, Mich.


CHECK THESE *Features*

- ✓ First popular priced Q Meter
- ✓ Reads Q directly on calibrated scale
- ✓ Oscillator supplies RF frequencies of 150 kc to 18 mc
- ✓ Calibrate capacitor with range of 40 mmf to 450 mmf with vernier of ± 3 mmf
- ✓ Measures Q of condensers, RF resistance, and distributed capacity of coils
- ✓ Many applications in design and development work
- ✓ Useful in TV service work for checking deflection yokes, coils, chokes, etc.

Heathkit "Q" METER KIT

MODEL QM-1
\$44.50

SHIPPING WT. 14 POUNDS

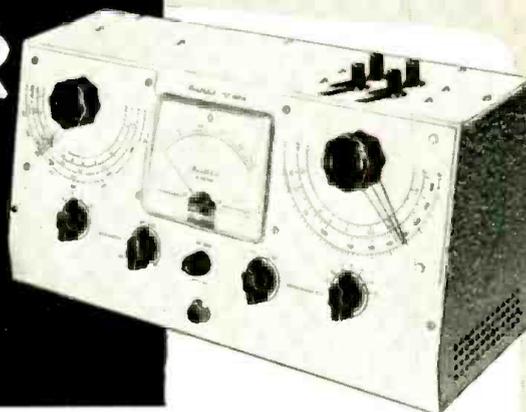

Another outstanding example of successful Heathkit engineering effort in producing a Q Meter Kit within the price range of TV service men, schools, laboratories, and experimenters. This Q Meter meets RF design requirements for rapid, accurate measurement of capacity, inductance, and Q at the operating frequency and all indications of value can be read directly on the meter calibrated scales. Oscillator section supplies RF fre-

quencies of 150 kc to 18 mc. Calibrate capacitor with range of 40 mmf to 450 mmf, with vernier of ± 3 mmf.

Particularly useful in TV service work for checking peaking coils, wave traps, chokes, deflection coils, width and linearity coils, etc. At this low kit price research laboratory facilities are within the range of service shops, schools, and experimenters.

Heathkit INTERMODULATION ANALYZER KIT



MODEL IM-1
\$39.50

SHIPPING WT.
17 POUNDS

The Heathkit IM-1 is an extremely versatile instrument specifically designed for measuring the degree of inter-action between two signals in any portion of an audio chain. It is primarily intended for making tests of audio amplifiers, but may be used in other applications, such as checking microphones, records, recording equipment, phonograph pick-ups, and loud-speakers. High and low test frequency source, intermodulation unit, power supply, and AC vacuum tube volt meter all in one complete instrument. Per cent intermodulation is directly read on the calibrated scales, 30%, 10%, and 3% full scale. Both 4:1 and 1:1 ratios of low to high frequency easily set up. With this instrument the performance level of present equipment, or newly developed equipment can be easily and accurately checked. At this low price, you can now enjoy the benefits of intermodulation analysis for accurate audio interpretation.

Heathkit AUDIO GENERATOR KIT

A Heathkit Audio Generator with frequency coverage from 20 cycles to 1 mc. Response flat ± 1 db from 20 cycles to 400 kc, down 3 db at 600 kc, and down only 8 db at 1 mc. Calibrated, continuously variable, and step attenuator output controls provide convenient reference output level. Distortion is less than .4% from 100 cps through the audible range. The ideal controllable extended frequency sine wave source for audio circuit investigation and development.



MODEL AG-8
\$29.50
SHIP. WT. 11 LBS.

Heathkit AUDIO OSCILLATOR KIT

Sine or square wave coverage from 20 to 20,000 cycles in three ranges at a controllable output level up to 10 volts. Low distortion, 1% precision resistors in multiplier circuits, high level output across entire frequency range, etc., readily qualify this instrument for audio experimentation and development work. Special circuit design consideration features thermistor operation for good control of linearity.



MODEL AO-1
\$24.50
SHIP. WT. 11 LBS.

Heathkit AUDIO FREQUENCY METER KIT



MODEL AF-1
\$34.50
SHIP. WT. 12 LBS.

The Heathkit Audio Frequency Meter provides a simple and convenient means of checking unknown audio frequencies from 10 cycles to 100 kc at any voltage level between 3 and 300 volts rms with any non-critical wave shape. Instrument operation is entirely electronic. Just set the range switch, feed an unknown frequency into the instrument, and read the frequency directly on the calibrated scale of the Simpson 4 $\frac{1}{2}$ " meter.

Heathkit SQUARE WAVE GENERATOR KIT



MODEL SQ-1
\$29.50
SHIP. WT. 12 LBS.

The Heathkit Square Wave Generator provides an excellent square wave frequency source with completely variable coverage from 10 cycles to 100 kc. This generator features low output impedance of 600 ohms and the output voltage is continuously variable between 0 and 20 volts, thereby providing the necessary degree of operating flexibility. An invaluable instrument for those specialized circuit investigations requiring a good, stable, variable square wave source.

HEATH COMPANY • Benton Harbor 15, Mich.



Heathkit
WILLIAMSON TYPE
**AMPLIFIER
KIT**

MODEL W-2

Particularly designed for custom installations, featuring separate cable connected units for simplicity of installation. Sheet metal work finished in attractive gray hammer-tone for smart appearance. All control shafts of the adjustable length break-off type.

\$69.50

PRICES OF COMBINATIONS

- W-2 Amplifier Kit including main amplifier, power supply, and WA-P1 Preamplifier Kit. Shipping Weight 37 lbs. Shipped Express only. **\$69.50**
- W-2M Amplifier Kit includes main amplifier and power supply. Shipping Weight 29 lbs. Shipped Express only. **\$49.75**
- WA-P1 Preamplifier Kit only. Shipping Weight 6 lbs. Shipped Express or Parcel Post. **\$19.75**

When selecting an amplifier for the heart of your high fidelity audio system, investigate the outstanding advantages offered by the Heathkit Williamson Type Amplifier. Meets every high fidelity audio requirement and makes listening to recorded music a thrilling new experience. This outstanding amplifier is offered with optional output transformer

operation, providing either the conventional triode output circuit or the new extended power circuitry in which the screen supply voltage is obtained from separate transformer primary taps. Frequency response within ± 1 db from 10 cycles to 100 kc. Tube complement—6SN7 cascade amplifier and phase splitter, 6SN7 push pull driver, two 5881 push pull power amplifiers, one 5U4G cathode type rectifier. Matching preamplifier available providing three switch selected inputs, correct compensation, and individual bass and treble tone controls. Uses 12AY7 (or 12AX7) preamplifier—12AU7 tone control amplifier. Particularly designed for the novice kit builder and requires no specialized knowledge or equipment for successful assembly and operation.

NEW *Heathkit* 20 WATT
High Fidelity AMPLIFIER KIT

MODEL A-9A




\$35.50

SHIP. WT. 18 LBS.

A new 20 watt high fidelity amplifier, designed especially for custom audio installations demanding clean reproduction, adequate power, and flexibility to meet individual requirements. Separate treble and bass tone controls provide up to 15 db boost or cut. Four switch selected inputs, each with the necessary compensation for the service desired. Output transformer impedances of 4, 8, and 16 ohms.

Preamplifier, tone control, and phase splitter circuits utilize 9 pin twin triode miniature tubes for low hum and noise level. Two 6L6 push pull power output tubes provide full 20 watts power. Frequency response ± 1 db, 20-20,000 cycles. Total harmonic distortion 1% (at 3 db below rated output). Tube line-up: 12AX7 pre-amplifier, 12AU7 voltage amplifier and tone control, 12AU7 voltage amplifier and phase splitter, two 6L6 push pull pentode power output, 5U4G rectifier. Truly outstanding amplifier performance coupled with low cost.

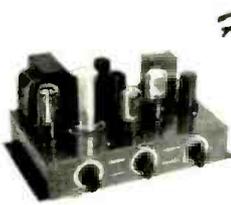

MODEL A-7B

\$15.50

SHIP. WT. 10 LBS.

Heathkit ECONOMY 6 WATT
AMPLIFIER KIT

The new Heathkit Model A-7B Amplifier offers many unusually fine features not normally expected in this low price range. Either of the two input circuits may be individually switch selected for phono or tuner operation. Separate bass and treble tone controls. Output impedances of 4, 8, and 15 ohms. Push pull beam power output stage for balanced reproduction. Excellent voltage gain characteristics, good frequency response, and full 6 watts power output. 12J5 amplifier, 12SL7 second amplifier and phase splitter, two 12A6 beam power output, one 5Y5 GT rectifier.

A-7C incorporates preamplifier stage with special compensated network to provide necessary gain for operation with variable reluctance or low output level phono cartridge. Circuit is properly compensated for microphone operation. \$17.50.

NEW *Heathkit*
BROADCAST BAND
RECEIVER KIT

Another new Heathkit for the student, beginner, or hobbyist. If you have ever had the urge to build your own radio receiver, this kit warrants your attention.

New high gain miniature tubes and IF transformers provide excellent sensitivity and good signal to noise ratio. A built-in ferrite core rod type antenna has been provided. A chassis mounted 5 1/2" PM speaker provides excellent tone and volume. Convenient phono input. Can be operated either as a receiver or tuner. Simplified construction manual outlines circuit theory. Ideal for students. Tube line-up: 12BE6 mixer oscillator, 12BA6 IF amplifier, 12AV6 detector-AVC-first audio, 12A6 beam power output, 5Y3GT rectifier.




MODEL BR-2

\$17.50 SHIP. WT. 11 LBS.

CABINET—Proxilyn impregnated fabric covered plywood cabinet. Shipping weight 5 lbs. Part number 91-9, \$4.50.

Heathkit
FM TUNER KIT

The Heathkit FM-2 Tuner was specifically designed for simplified kit construction. Can be operated through the "phono" portion of your radio or with a separate amplifier. The kit features a pre-assembled and adjusted tuning unit, three double tuned IF transformers, and a discriminator transformer in an 8 tube AC operated circuit. Frequency coverage 88 to 108 mc. Experience the thrill of building your own FM tuner and at the same time enjoy all of the advantages of true FM reception.

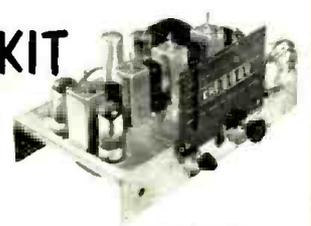

MODEL FM-2

\$22.50

SHIP. WT. 9 LBS.

Free CATALOG

Write for free catalog containing latest price information, schematics, specifications, and descriptions of all Heathkits.

HEATH COMPANY • Benton Harbor 15, Mich.

SIMPLE SOUND EFFECTS FOR HOME MOVIE MAKERS

By JACK DARR
Ouachita Radio Shop


For fun or as a money-making sideline, these sound effects can be set up using readily-available household equipment.

24 HOUR
DELIVERY
FROM STOCK!

RELAYS

Our stock of more than a million relays — in over a thousand different types — is the world's largest. Don't delay your production for want of large or small quantities of relays of any type.

Telephone, wire or write for quotations.

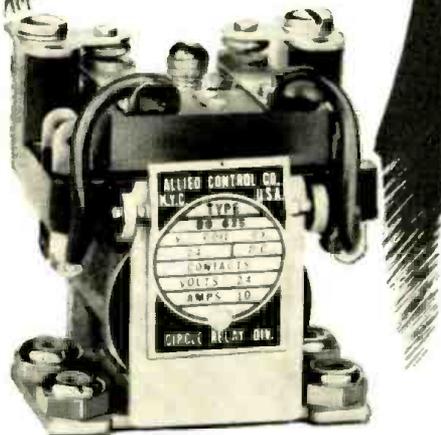

NEW AND MORE
COMPREHENSIVE

**1953
RELAY SALES
CATALOG**

NOW READY

Be sure to send for your copy



Telephone

SEeley 8-4146

**Relay
Sales**

833 W. CHICAGO AVE.
DEPT. 8, CHICAGO 22, ILL.

A WHOLE new market for wire or tape recorders can be opened up around your home town if you'll get out and round up some of the local "home-movie" bugs. The home-type wire or tape recorders, referred to hereafter as "recorders," to save time, can be used to make real professional-sounding sound-tracks and sound effects. Any of these are easily made at home, with a little practice. Special sound effects, shots, automobile or airplane engines, trains, or anything, can be "dubbed in," by using two or more recorders.

Recording of sound, dialogue, etc., simultaneously, as the pictures are being shot is easy; the sound can later be transferred to another tape. This could be done on occasions such as banquets, speeches, athletic events, etc., which could not be repeated. To make dramatic scenes, such as in a play, the actors can say the lines; after the film has been developed and edited, it can be run off, while the characters say the lines for the final sound track. "Bridge" music and special effects may be put on at this time. Of course, for a simple indoor or outdoor scene where the action is stationary, this wouldn't be necessary; the main value of this method lies in shots where the sound would be very difficult to record; moving cars, etc. This can be used to make scenes such as the common ones found in Western pictures; the hero and heroine, with supporting characters, are riding over the plains, singing happily to the accompaniment of a full orchestra, apparently riding in an invisible stage-coach! Shoot the picture from the back of a car, while the actors pretend to be singing; then, with the orchestra and chorus, dub in the sound later. Horses' hoofs, etc., may be dubbed in from another sound track. The popular "cartoons" are all made in this way, as a matter of fact.


Some hilarious comedy effects are possible with this method; loud "bongs" when someone is hit over the head, horn-squawks when somebody gets a punch in the nose, tearing cloth as an actor bends over, and of course, the well-known "Boinnngggg!" when man sees beautiful gal. There are a million possibilities, and still more

will occur to the "producer" as he goes along.

The first requirement is at least one recorder and a couple of tapes. Two or three would be much better, as this will permit dubbing and mixing sound effects, background music, bridges, (the music which is used during a fade between scenes) and other special effects. This is done with a simple mixing harness. (See Fig. 1A.) If the recorder in use has only one input, a mixer made up of standard volume controls and jacks will do very well. (See Fig. 1B.) When using this hookup, a few test runs will give you the proper level settings for each particular sound effect. One very convenient feature of magnetic recordings is their "erasability." If a scene isn't just right the first time, it can be erased and repeated until perfect.


Just for instance, a love scene is being recorded. The microphone, which is connected to the "Mike" input of the "final" recorder (Rec. 1) picks up the voices of the actors. Recorder No. 2 is playing soft background music into the #2 input of the mixer. If other sound effects are necessary, for instance a car driving up outside, they may be added by another unit connected to the #3 input of the mixer. The output of the mixer is fed to the "High Level" input of Recorder #1. Monitoring of the final recorder may be done by attaching headphones to the output of the amplifier. Some machines have this connection available, and it may easily be installed, if not. Using this method requires at least two operators for the sound

Fig. 1. (A) Simple connection harness for two recorders. (B) Unit for mixing outputs of two recorders into input of final machine. The resistance values are not critical.

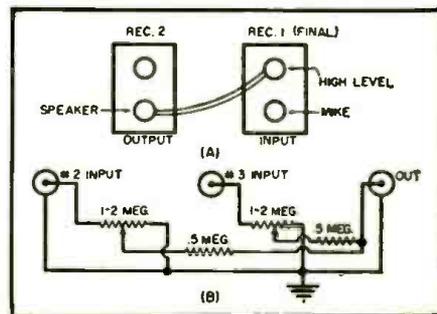

RADIO & TELEVISION NEWS


You can see the difference...

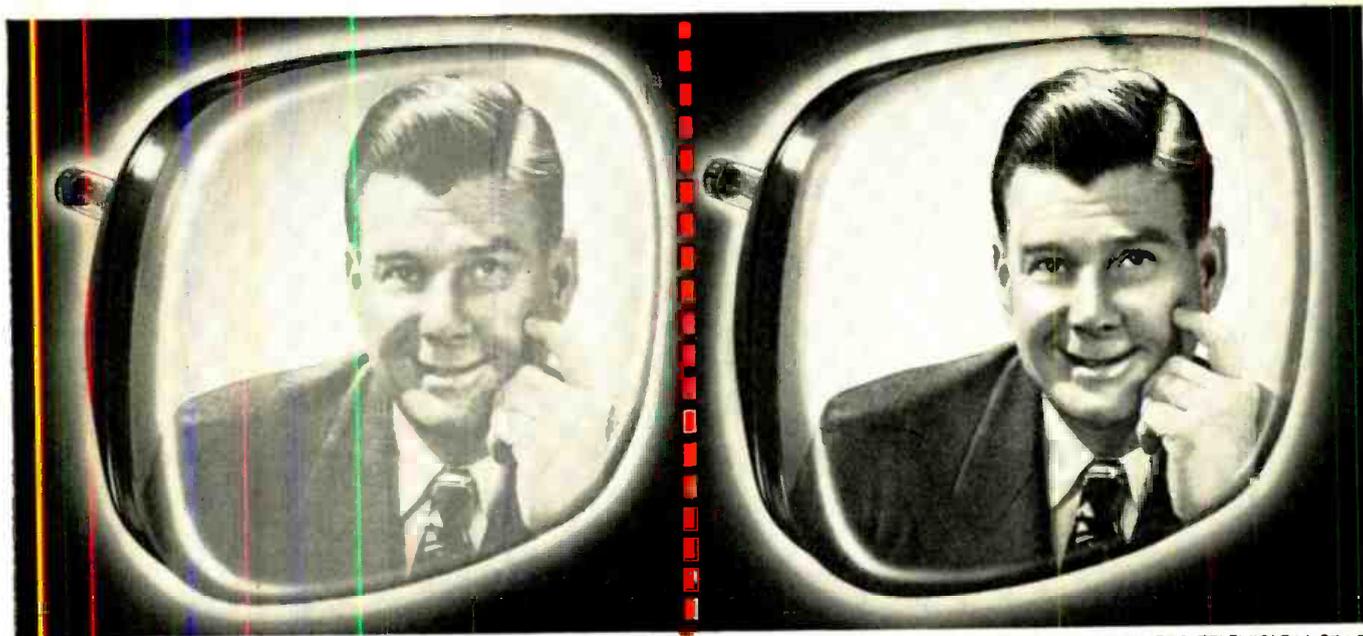

ARTHUR GODFREY, FAMOUS CBS-TELEVISION STAR

NOW CBS-HYTRON **MIRROR-BACK** BIG-SCREEN TUBES 27EP4 . . . 24TP4 GIVE YOU BRIGHTER PICTURES!

HOW MIRROR-BACK TUBES ARE MADE

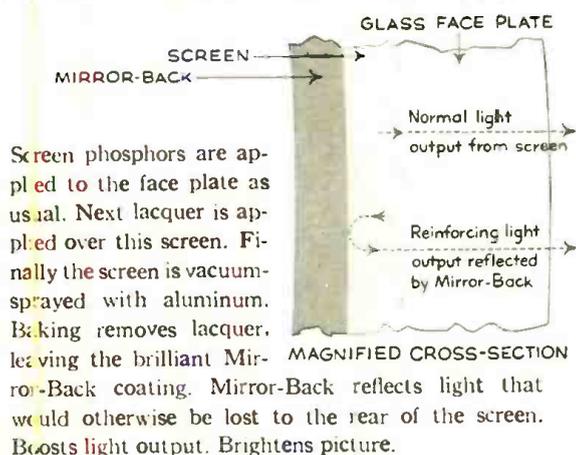

ADVANTAGES OF CBS-HYTRON MIRROR-BACK TUBES

1. Stepped-up light output.
2. Brighter picture.
3. Greater contrast.
4. Reduced strain on component parts.
5. Full effective screen potential maintained by metallic contact between anode and screen.
6. Longer life . . . drain on cathode materially reduced.

Leading TV set makers demand maximum brightness from their large-screen sets — without strain on component parts. For them, CBS-Hytron introduced its Mirror-Back 27EP4 and 24TP4 (both spherical, electromagnetic types). Mirror-like effect of their aluminum-backed screens reinforces light output. Gives brighter, sharper pictures.

You, too, will want CBS-Hytron Mirror-Back big-screen tubes for replacement. In 27- and 24-inch sizes, they are a must. Take a tip from leading TV set makers. Try the CBS-Hytron 27EP4 and 24TP4. See the difference for yourself. Let your customer see it too. Order performance-tested Mirror-Back tubes from your CBS-Hytron distributor.

New . . . FREE CBS-HYTRON TRANSISTOR MANUAL Just what you have been looking for: A down-to-earth, complete, 8-page introduction to transistors. In three parts: 1. Theory. 2. Data. 3. Application. CBS-Hytron Transistor Manual is profusely illustrated. Contains nine basic transistor applications. Explains by vacuum-tube analogy both point-contact and junction transistor operation . . . conduction by "holes" . . . P-N-P and N-P-N transistors . . . advantages and limitations of transistors.

An easy-to-take introduction to how transistors work . . . their characteristics . . . and how to apply them, this CBS-Hytron Transistor Manual is also *free*. Get it from your CBS-Hytron distributor. Or write direct today.




Manufacturers of
Receiving Tubes Since 1921

CBS-HYTRON Main Office: Danvers, Mass.

A Division of Columbia Broadcasting System, Inc.

Insure Yourself FASTER, EASIER Installations AT LOWEST COST

NEW SUPER-FRinge MOTORLESS

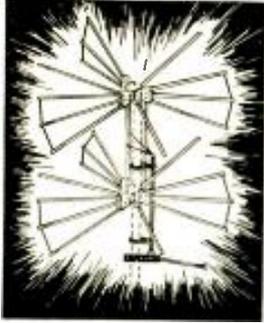

- DIRECTRONIC**
- 24 Elements
 - New High Gain
 - Clearer, Sharper Pictures
 - Electronically Beamed in All Directions
 - New Low-Loss Tubular Tri-X Cable
 - Eliminates Ghosting Interference

New Improved Hi-Gain super Directronic offers sensational advantages over motorized antennas—less installation cost—less upkeep. The new 24-element Directronic is beamed to any transmitter in fringe as shown. New 6-position Directronic switch located at receiver. Twenty-four elements provide high gain in all directions. New Tri-X low-loss tubular cable minimizes attenuation. Serviceman's kit contains 21 hi-tensil aluminum elements, including 6 reflectors, Directronic 6-position switch, 100 ft. Tubular Tri-X, 3 matched stacking bars, Universal U-Clamps.

Model AX-524 **\$24.95**

Switch located at receiver. Twenty-four elements provide high gain in all directions. New Tri-X low-loss tubular cable minimizes attenuation. Serviceman's kit contains 21 hi-tensil aluminum elements, including 6 reflectors, Directronic 6-position switch, 100 ft. Tubular Tri-X, 3 matched stacking bars, Universal U-Clamps.



For Ultra-Fringe Reception, Use the "Power Master"

New 48-element Motorless Directronic provides higher gain than any other broad band antenna. Proved reception at 100 miles from transmitter in average location. Serviceman's kit provides 48 aluminum elements, 100' tubular Tri-X, 6-position beam selector, matched stacking harness, Universal U-Clamps.

Model AX-548 **\$41.50**

SAVE WITH ROCKET 35 FT. MAST KITS
Economy mast kit contains 3-10' seamless TRI-COATED 1 1/2" O.D. masts, one 5' mast, 300 feet of 3/20 galvanized steel guy wire, and everything else needed including guy rings, mast connectors, insulators, cable clamps, guy hooks, and swivel mounting base.

35-foot Mast Kit **\$15.95** 25-foot Mast Kit **\$11.95**

- Lowest Prices on Antenna Accessories**
- Mast Steel (Duplicated 5' crimped) 1 1/4" O.D. **\$1.05**
 - Mast Steel (Duplicated 10' 1 1/4" O.D.) **1.95**
 - Mast Connectors for 1 1/4" O.D. Mast **.59**
 - Chimney Mount Complete with Straps **1.19**
 - Peak Roof Saddle (will take up to 1 1/2" O.D.) **1.59**
 - Lightning Arrestor—TV **.69**
 - Galvanized Steel Guy Wire—0 20' **2.4c ft.**
 - Rocket Twin-Lead—7/28 stranded **2c ft.**
 - UHF Tubular Twin-Lead Lo-Loss 100' Coil **4.95**
 - Mast Stand-off Insulators—3" **.10**
 - Screw Type Stand-off Insulators—3" **.03**

ROCKET BROAD BAND YAGIS

- SENSATIONAL GAIN
- SENSATIONAL PICTURES IN FRINGE AND ULTRA FRINGE AREAS



Switch in Yagi Broad Band Hi-Gain Antennas! These new Yagis give you Yagi reception on the 7 low-band and 7 hi-band channels—no restriction to one single channel! A two-by array will outperform even a 10 or 12-element single channel Yagi. Price is sensationally low. Complete serviceman's array includes 1 Double Reflector, 2 folded dipoles, 3 directors, Universal mast clamp, Easy-to-assemble quick fit construction.

Model RB2—6 Ch. 2 thru 6 **\$10.95 Ea.**
Model RB7—13 Ch. 7 thru 13 **5.95 Ea.**
Matched stacking bars **1.25 Pr.**

NEW HIGH GAIN UHF YAGI

Good UHF reception in fringe areas now assured with new Rocket Broad-band UHF Yagis. Compact, easy to stack for all the gain required anywhere. Three models cover all UHF channels. Rocket UHF Yagis are completely pre-assembled—you simply tighten mast clamp. Serviceman's array includes two reflectors, 2 dipoles, 4 directors and Universal mast clamp.



Model UHF-1A—Ch. 14 thru 48 **\$4.25**
UHF-1B—Ch. 27 thru 62 **3.75**
UHF-1C—Ch. 47 thru 83 **3.75**
Single **54.25**
Lots of 6 **3.75**
Matched stacking bars—12 wave **.75 pr.**

UHF STRIPS—Now available for Standard Coil tuners. To order, specify channel No. and series designated by letter, such as F, G, Q, etc., stamped on each strip of your present tuner. (Set consists of osc. & ant.) **\$750 Ea.**

Hi-Gain Single Channel Yagis

5 element—Ch. 2, 3, 4... **\$7.95** Ch. 5 or 6... **\$6.95**
Ch. 7-13... **\$3.95**

Specify exact channel number required.

NEW FALL AND WINTER CATALOG AVAILABLE

ALL PRICES F.O.B. CLEVELAND, OHIO
Do not remit more than complete purchase price. Pay shipping charges on receipt of goods. 25% deposit on all C.O.D. orders, please. Money-back guarantee. Prices Subject to Change Without Notice.

National Electronics OF CLEVELAND
THE HOUSE OF TV VALUES
109 Delco Building Cleveland 3, Ohio

equipment, but around a project of this nature, there is usually a surplus of eager personnel, so that will be no trouble.

The basic hookup for this arrangement is not as complicated as it looks. Actually it is rather simple; Recorder No. 1 is making the final sound track; it is picking up the dialogue, and also the sound effects fed into it from the mixer. Background sounds are fed into the mixer by the other two recorders, on "playback," of course, and the resultant combination is all recorded upon the final tape. Monitoring is essential, so that the levels of different sounds may be adjusted to give the correct proportions. It is best to make a couple of "dry-runs" in order to check this.

Home-Made Sound Effects

There is no end to the possibilities of making home-made, realistic sound effects. We'll list a few, and your imagination can supply the rest.

Pistol shots: Slap a flat plastic or leather cushion with a flat stick, like a yardstick.

Machine-gun: Same cushion; make a "flapper" out of a tricycle wheel, etc., by fastening several pieces of leather to the rim, then spinning the wheel, so that the flappers strike the cushion.

Ricochets: Slap cushion and whistle.

Automobile effects: Take the mike or recorder out to the curb; while an accomplice starts, stops, slams door, etc., on the family car, record sounds needed. Hint: leave blanks of several seconds between each sound effect. These are necessary for rapid "cueing."

Train sounds: Take the recorder down to friend's house near tracks, or to depot.

Airplane sounds: Try a piece of medium-stiff cardboard and a small electric fan. Vacuum cleaner and a stiff plastic brush can make some interesting sounds, also electric razors.

Marching men: Make several small blocks of wood, like pieces of broomstick, about six inches long; drill hole through one end. String them on stiff wire, in two rows. Tap them on table, in cadence.

Door slamming, opening: Open and slam door. (Don't laugh; this is about the only way to get a realistic door slam sound!)

Rain: Large sheet of tin, about 12 x 24 inches; pour coarse sand or dried peas, as it is held in a slanting position.

Hail: Same; use larger peas.

Thunder: Bass drum or tympani, if obtainable; if not, use piece of tin mentioned before. Hang it by one edge, and shake gently. (This is the old "thunder-sheet" used in theaters for years. The bigger the piece of tin, the better the effect.)

Fire, wood burning: Crush cellophane in hands close to mike.

Wooden house or the like falling down: Break strawberry box or other pieces of very thin wood in hands close to mike.

Editors and Engineers PUBLICATIONS

BETTER TV RECEPTION

New 2nd Edition.
IT COVERS ALL YOU WANT TO KNOW ABOUT fringe and low-signal areas

BETTER TV RECEPTION has become the standard guide for the installation technician and a popular text for TV enthusiasts.



Book No. E&E-TR2
\$2.50 per copy * (paperbound) at our store

For Additional Coverage

RADIOTELEPHONE LICENSE MANUAL. Typical study questions with concise answers for any commercial U.S.A. radiotelephone operators license. Book No. E&E-RL1... **\$3.75***

RADIO HANDBOOK, GIANT 13TH EDITION. A one-volume library of radio information with extensive, simplified theory. Detailed how-to-build-it data on dozens of items of practical radio equipment. Book No. E&E-RH13... **\$6.00***

SURPLUS RADIO CONVERSION MANUAL, VOL. 1. Practical conversions. Write for list of contents. Book No. E&E-SM1... **\$2.50***

SURPLUS RADIO CONVERSION MANUAL, VOL. 2. Companion to Volume 1. Book No. E&E-SM2... **\$2.50***

*Plus any tax.

BUY FROM YOUR DISTRIBUTOR
ADD 10% ON DIRECT MAIL ORDERS TO EDITORS AND ENGINEERS, LTD., BOX 689A, SANTA BARBARA, CALIF.
Book orders under \$100 BAKER & TAYLOR, MILWAUKEE, WIS.

Look for the

PHOTOGRAPHY ANNUAL

Everybody likes good pictures, and this big value is a treasurehouse of them. . . . Contains the best work of today's photographers in every field. . . . Concise notes in the back of the book tell the technical story behind each striking photograph.

NOW ON SALE

See Your Favorite News Dealer



there are **4** points to a triangle...

THE POINT OF APPLICATION

determines the type of loudspeaker best capable of providing optimum performance at lowest possible cost. There are over 50 different University models to choose from... each designed to serve most efficiently and economically in its intended application.

- Radial type projectors and paging speakers with 360° dispersion for maximum coverage at lowest cost and ease of installation.
- Reflex trumpets in various sizes for incomparable efficiency, distance, and noise penetration.
- Wide-angle and bi-directional types, marine and submergence models for heavy industry.
- Paging and "talk-back" speakers in numerous sizes, power and frequency characteristics and mounting arrangements.
- "Explosion-proof", blastproof, and even super-power types from 100 to 720 watts capacity.
- High fidelity, full-frequency response types for indoor and outdoor use.

University Loudspeakers are application-engineered to assure customer satisfaction, avoid waste of amplifier power and speaker capacity and reduce initial equipment and installation costs. University helps you to sell more sound jobs... make more profit you can pocket. Why spend more for more than you need—CHECK UNIVERSITY FIRST!




UNIVERSITY LOUDSPEAKERS • INC.
80 SOUTH KENSICO AVENUE, WHITE PLAINS, N. Y.

FREE—new 1953 copy of the University Technilog • Complete up-to-date manual of sound theory, application and installation requirements • SEND for your copy today.



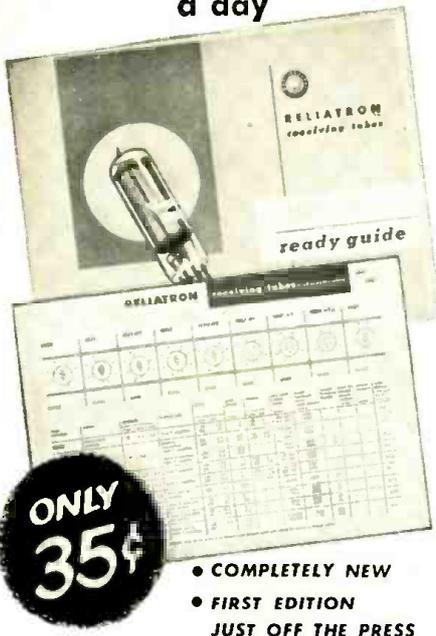This book will save you
30 Minutes
 a day



**FIND TUBE RATINGS,
 CONNECTIONS IN SECONDS**

This big new Westinghouse Ready-Guide is a completely new kind of handbook of receiving tube data. Designed to save time for busy servicemen and engineers. Eliminates "squinting" at tiny data listings.

BIG — BOLD — CLEAR

Just 9 tube types are listed on each 8½" x 11" page. Not 30 or 40 tiny type listings as in most condensed data books. Best of all, large clear base diagrams are located on the same page as ratings. Bothersome cross referencing, footnotes cut to the bone.

COMPLETE, ACCURATE, UP-TO-DATE

This new Westinghouse Ready-Guide lists complete data on receiving tubes which account for more than 98% of tube usage. 48 pages. 385 pictures and diagrams. 342 types listed.

SPECIAL: 3 for \$1.00

This Ready-Guide is being sold at less than cost as an introductory offer only. Price is only 35¢—3 for \$1.00. Order from your nearest RELIASTRON Tube Distributor or mail coupon below.

ET-95038

**RELIASTRON
 TUBES** TM

Westinghouse

Westinghouse Electric Corporation
 Electronic Tube Division, Dept. G-209
 Box 284, Elmira, N. Y.

..... Enclosed is \$1.00 for 3 copies of Ready-Guide
 Enclosed is 35¢ for 1 copy

NAME.....
 ADDRESS.....
 CITY..... STATE.....
 Please Print

Phone ringing: Get accomplice to call you, then record actual ring, picking up of phone, "Hello" etc. Telephone company is just a bit touchy about recording of actual conversations. To get effect, record other half of conversation on one recorder; connect output to actual telephone receiver; then play this and record whole thing.

Kiss: Recording of actual sound is more fun, but if performer is bashful, kiss back of your own hand close to mike. Comedy kiss, with loud "plop," made by putting forefinger in mouth, closing lips, then pulling out rapidly.

Footsteps: Surprisingly good footsteps may be made by putting mike on hard-topped table, then "walking" your fingers up to and past it. Variation in timbre of sound may be made by putting handkerchief on table.

Echo effects: Record the desired voice, etc., then go to a building with a long, hard-surfaced hall, while it is empty. Courthouse, school building, factory, etc. Set up one recorder at each end of hall; play sound loud enough to echo, record on other machine. For extra echoes, play back

recording just made, and re-record. (A peculiar effect may be made by making a recording of a voice, copying it, then playing both into the final recorder, so that one is just a fraction of a second out of phase; experiment with it.)

These are only a few of the hundreds of possible sound effects; the number is limited only by your imagination. Crickets or frogs chirping at night, for instance, can probably be picked up just outside your house, any summer night, unless you live in a very large city; in this case you'll have to go to the park or zoo. The zoo should furnish some wonderful sounds, if you can get them! Old auto-horns of the bulb-type are an indispensable adjunct of the sound man, as are cowbells, siren whistles, police whistles, wood blocks, and gongs. An old auto brake drum makes a wonderful gong.

As we've said repeatedly, there is no limit to the effects you can make, or the fun you can have with a setup like this, and if you're a radioman, you can make some good money selling the equipment. Have fun!

-30-

NOVEL DESK-STAND FOR MICROPHONE

By ARTHUR TRAUFFER


THIS novel, economical, and easily built desk-stand for microphones, was specially designed for those who use their mikes on glass-topped desks, or on other smooth or polished surfaces. Besides acting as a soft shock-absorbing base for the mike, this stand allows the mike to be "stuck" to the desk top so it cannot slide around or be knocked off the top of the desk.

Buy a large rubber vacuum cup with a ¼"-20 bolt in it; these are used for holding luggage racks on the tops of automobiles and sell for about 23¢ at auto supply stores. Also buy a male microphone-cable-connector; these sell for about 21¢ net at most radio supply houses. Twist the bolt securely into the neck of the vacuum cup and then saw off the head of the bolt. Remove the cord-

protecting spring in the cable connector, and twist the connector into the socket in the bottom of the mike. Now slip the connector over the bolt in the vacuum cup and tighten the set-screw in the connector. The opening in the connector is a little large for the bolt, so if you wish, you can wrap a couple of turns of friction tape around the bolt to increase its diameter before slipping on the connector. As shown in the photo, the writer placed a rubber faucet washer between the top of the cup and the connector; this improved the appearance of the unit somewhat. This desk stand is not recommended for use with microphones much larger than the Turner Model-CD shown in the photograph. However, the modern trend is towards smaller and lighter microphones.

-30-

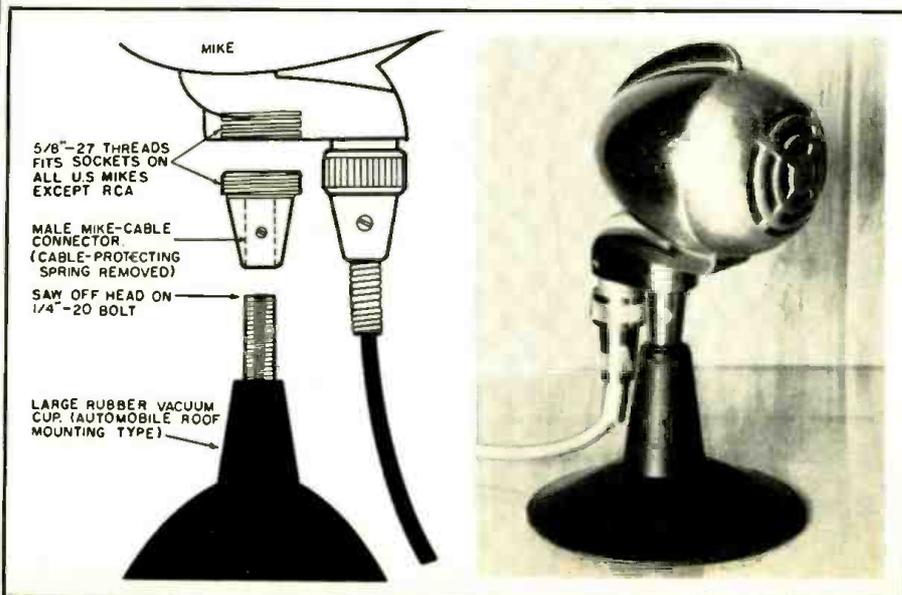Mechanical details for building desk-stand and photo of completed unit.



BUILDING INEXPENSIVE DECADE BOXES

By RICHARD FRIEDMAN

WHILE seeking an economical method for making home-made decade resistance and capacitance boxes, I hit upon the scheme to be described.

The chief advantages of these techniques are that only four resistors or condensers are required for each decade box and that stock selector or push-button switches may be used.

A sample decade box is shown in Fig. 1B. It covers the range of 1000 to 9000 ohms. Similar decades can be made up to cover other ranges such as 10 to 90

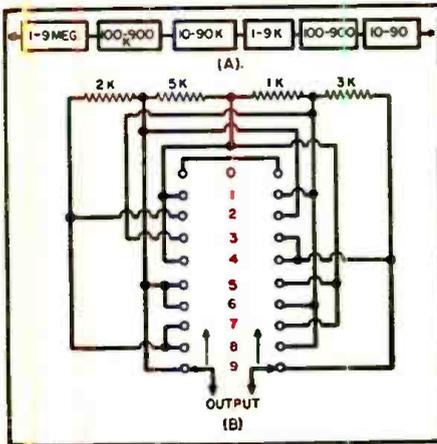




Fig. 1. (A) Method for connecting resistors and (B) a sample resistance decade circuit.

ohms; 100 to 900 ohms, etc. Any number of these units can be made up and connected in series, as shown in Fig. 1A, to give a greater range.


Connect condenser decades in parallel as shown in Fig. 2A. A sample decade is shown in Fig. 2B. It is recommended that the values of the condensers used be selected with the aid of a bridge. Incidentally, if electrolytics are employed be sure to observe polarity so that they are not reversed during the switching operation.

-30-

Fig. 2. (A) How condensers should be connected. (B) One usable circuit arrangement.

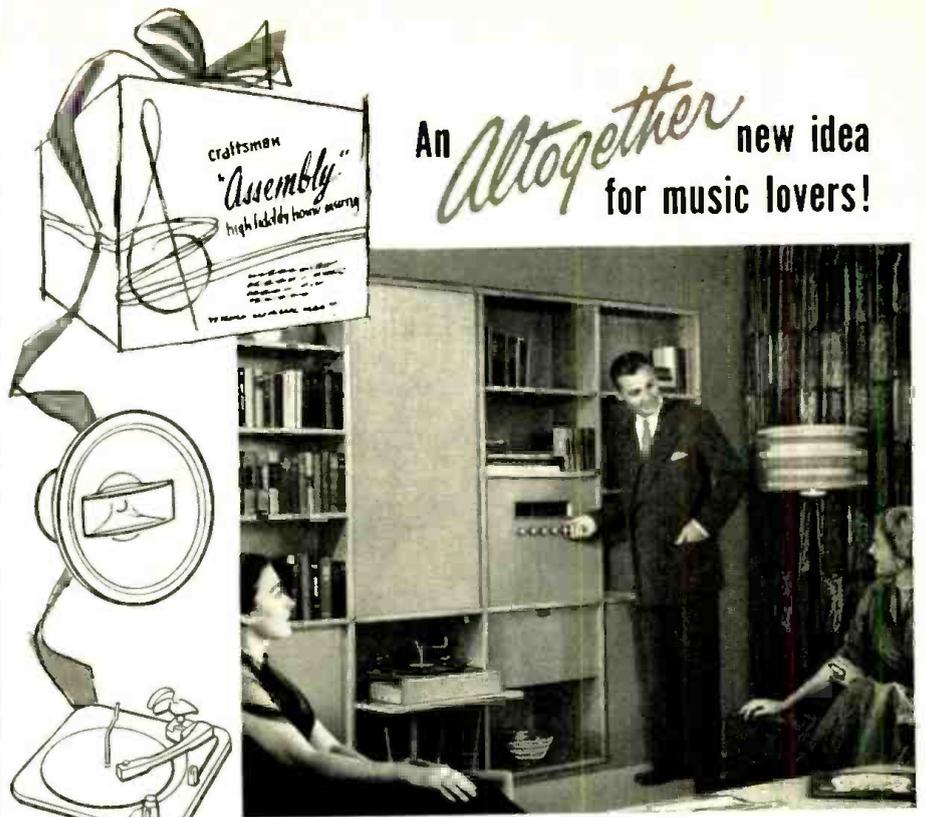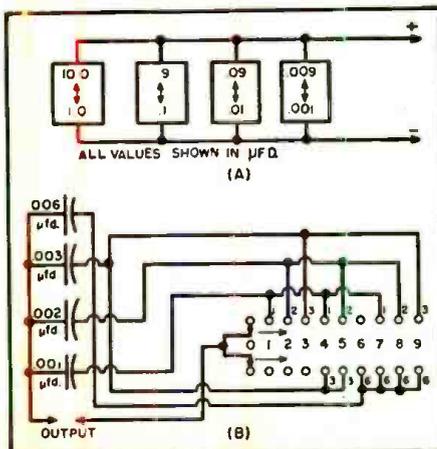

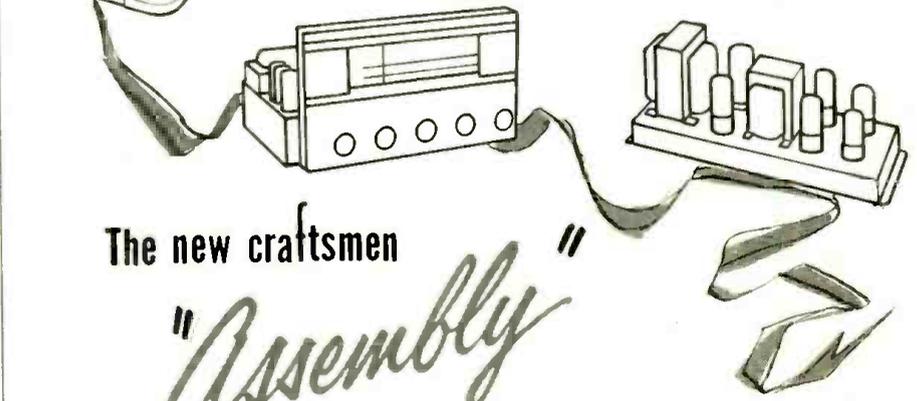An *Altogether* new idea for music lovers!



The new craftsmen

"Assembly"

high fidelity home music system

DID YOU KNOW that buried away in your own phonograph records there's a treasure of beautiful music you probably have never heard? It's true! Today's High Fidelity recording (and broadcasting) techniques bring you music with a clarity and tonal range never before possible outside the concert hall.

To enjoy this full measure of realism, you need an instrument capable of reproducing all the music without distortion—a High Fidelity home music system.

Now, in one package, the world's most respected name in High Fidelity brings you a complete system of perfectly matched units—the Craftsmen "ASSEMBLY."


You get the performance-proved Craftsmen FM-AM Tuner and Amplifier

... two new Craftsmen speakers coaxially mounted and 3-speed record player with dual sapphire magnetic pick-up... many accessories, too.

The Craftsmen "ASSEMBLY" is waiting for your critical ear in the sound rooms of a Radio Parts Supplier near you. Drop in today for a demonstration of distinctly better listening.

Send for this booklet on High Fidelity by DEEMS TAYLOR

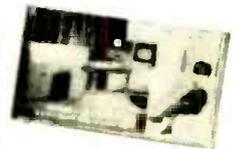Ask your Supplier for a copy of this 24-page booklet by Deems Taylor—or write to us, enclosing 10¢ to cover handling and mailing.



high fidelity by craftsmen means distinctly better listening

The Radio Craftsmen, Inc., Dept. R-9, 4401 N. Ravenswood Ave., Chicago 40, Illinois

THESE BOOKS HELP YOU EARN MORE IN TV SERVICING

"How to Understand and Use TV Test Instruments"



Provides basic explanations of how each test instrument operates. Covers: VT Voltmeters, AM Signal Generators, Sweep Signal Generators, Oscilloscopes, Video Signal Generators, Field Intensity Meters, Voltage Calibrators. Describes each in detail; explains functions; tells proper use in actual servicing; shows how to avoid improper indications. Helps you get the most from your instruments; saves you time, helps you earn more. 175 pages, 8 1/2 x 11".

ORDER TN-1. Only..... \$3.00

"TV Servicing Short-Cuts"

Describes a series of actual TV service case histories, giving step-by-step explanations of how the service technician localized and tracked down each problem. Shows how these frequently recurring troubles can be tracked down and solved in any set. Explains how to apply proper time-saving servicing techniques — gives you the successful experience of experts, to make your service work easier, quicker, more profitable. 100 pages, 5 1/2 x 8 1/2".

ORDER TK-1. Only..... \$1.50



"Servicing TV in the Customer's Home"



Saves you time, work and chassis-hauling on outside TV service calls. Shows you how to make successful repairs on the spot using these methods: employing VTVM and capacitor probe to trace down trouble; "tube-pulling" to diagnose trouble by observing audio and picture effects; performance tests through analysis of test pattern; adjustment techniques developed for field servicing. Saves time, avoids chassis removal. 96 pages, 5 1/2 x 8 1/2".

ORDER TC-1. Only..... \$1.50

"Television Tube Location Guides"

VOL. 3. Shows tube positions and functions in hundreds of important TV sets. Helps save servicing time. Often, looking at the picture or listening to the sound, provides the clue to the trouble. Frequently, a tube failure is the cause. This guide, with its clear, accurate tube placement and function diagrams, makes trouble diagnosis and tube replacement quick and easy, without removing chassis. 192 pages. All new diagrams continuing coverage from Vol. 2.

ORDER TGL-3. Only..... \$2.00

VOL. 2. Over 200 pages of tube placement diagrams not included in Vols. 1 and 3.

ORDER TGL-2. Only..... \$2.00

VOL. 1. Over 200 pages of diagrams not in Vols. 2 and 3. ORDER TGL-1. Only..... \$1.50



"Photofact Television Course"



A full, easy-to-understand explanation of TV principles, operation and practice. Covers Cathode Beam Formations and Control, Beam Deflection Systems, Beam Mod. and Synch.; analyzes CR tubes, camera tubes, voltage supplies, saw-tooth generators, sync. circuits, control functions, antenna circuits, RF input tuning, IF systems, AGC, DC restoration, etc.; with full bibliography and glossary. 208 pages, 8 1/2 x 11".

ORDER TV-1. Only..... \$3.00

HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber today, or write direct to Howard W. Sams & Co., Inc. 2203 East 46th Street, Indianapolis 5, Ind.

My (check) (money order) for \$..... enclosed. Send the following books:

- TN-1 TK-1 TC-1
 TGL-3 TGL-2 TGL-1 TV-1

Name.....

Address.....

City..... Zone..... State.....

Multi-Band Antenna

(Continued from page 72)


comes 8 because if the antenna is a half-wave at 80 meters, it will be two half-waves at 40, four at 20, and eight at 10 meters. Since a half-wave at 80 meters is over 130 feet, we know approximately what the exact length should be.

The length of the antenna is equal to $492 (8 \div .05) / 28.4$ which is 137.7 feet. The antenna is fed at a point 16.25% of its length either side of the center. That is to say, the two 300-ohm points on a half-wave will be found to be .1625 of its total length either side of center. The mid-point of the antenna is at 68.85 feet and either of the desired 300-ohm points is found 22.37 feet from the center. That is, $137.7 \times .1625 = 22.37$ feet. The wire is cut, an insulator inserted, and the 300-ohm line attached as with a center-fed dipole. A short, straight-sided feeder spreader is the best mechanical type of insulator for this application. The lead-in should run at a sharp right angle to the insulator so that no fanning effect can take place, as shown in Fig. 3.

As the feeders tie in at a rather low voltage point insulation is not too important. All excess line should be removed so as to reduce standing waves that may arise if the excess line is allowed to coil on the floor or wall. (Standing waves will exist in such an instance between the mismatched coiled section and the transmitter because of the discontinuity of characteristic impedance.) The line can then be attached to any link-coupled final tank circuit and will operate with virtually no standing waves.

It should be remembered that a transmission line which matches an antenna perfectly will reflect only a resistive load into the final tank circuit. When the loading is varied from minimum to maximum, the final tuning condenser does not have to be varied to tune out any reactance that would ordinarily be reflected into the tank circuit by an improperly matched line. This method was used and it was impossible to find a further dip of the final plate current when varying the loading on bands from 80 through 10 meters.

Fig. 3. The 300-ohm feedline is attached to the multi-band antenna without "fanning," which would upset the impedance relationship. Insulator is a ceramic feeder spreader. The horizontal pieces of feeder, taped to the spreader, become part of the antenna.

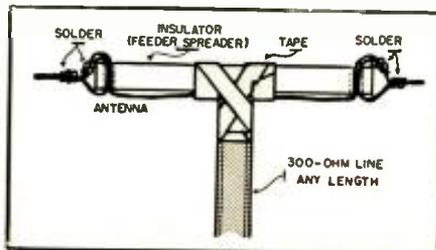

Loading will vary with precipitation, as do all antennas and lines made of molded plastic, because of the increased line capacitance per unit length.

The antenna can be a half-wave on any band and will operate on any higher band harmonically related to the fundamental in steps of 2, 4, 8, etc. If it is a half-wave at 80 meters, 40, or 20, it will not operate satisfactorily on 15 meters because the feedline now ties in at a high impedance point and standing waves will result.

The antenna requires approximately one half-hour to construct and is especially useful for contests or "field days" because the antenna connections do not have to be touched when changing bands.

If the final amplifier does not load enough with a two- or three-turn link, wind a separate pick-up link, increasing the number of turns until the antenna loads to the proper value.

Even though the antenna is fed off-center, the difference in line current is not measurable with a meter inserted in each line.

One important thing to bear in mind is that the feedpoint must be determined for the highest-frequency band to be used as this is where the impedance curve varies most rapidly for any variation of feedpoint location.

The radiation patterns of this antenna are identical to those of any long-wire antenna and signal reports have shown the pattern to be quite sharp on the higher frequencies. —30—

ROCKY MOUNTAIN MEET

ESTES PARK in the Rocky Mountains was the scene of the 1953 Convention of the Rocky Mountain Division of the ARRL recently.

The Denver Radio Club this year sponsored the meetings which drew local communicators, scientific personnel, and interested amateurs from widely separated points to share in an annual exchange of technical information. Visitors from both coasts and as far away as the Isthmus of Panama and the Johnson Islands were in attendance.

A diversified program, both technical and social, was provided for the edification of conventioners. —30—

PAGING OLD-TIMERS

WE ARE pleased to report that the item "Wireless Ops of Old" which appeared in the July issue (page 127) has elicited a favorable response from our readers.

Records from the West Coast disclose the names of several "Old Timers" we would like to locate: Art Baxter, George Baxter, C. H. Bowers, G. S. Corpe, E. W. Lovejoy, B. C. MacDonald, C. R. Parker, Felix Sehadessack, and P. J. Townsend.

These men were prominent commercial operators about 1912, and we would like to know their present status. If some career highlights can be obtained on these Old Timers, we would like to print a thumb-nail sketch of such and thus honor these "Pioneers of the Pacific." Let's hear from you men! —30—

GET DEPENDABLE PERFORMANCE IN TV TEST EQUIPMENT!



**...Accurate Measurements
and Increased Profits, Too!**

COMBINED use of these G-E units takes guesswork out of test measurements. With good linearity and amplitude characteristics G-E equipment eliminates misleading results from distorted patterns. Your technicians will handle more work...handle it more efficiently...add to your profits and your reputation!

Sweep Generator ST-4A. Outstanding in performance and varied in application. Adjustable linear sweep that is all-electronic...no moving mechanical parts. Covers all broadcast TV channels. Good attenuation and extremely low leakage plus continuously variable center frequency.

Marker Generator ST-5A. Marks all the critical frequencies on a pass band as well as having continuous coverage. Designed to give fast manipulation with crystal controlled accuracy for outstanding performance. Features separate crystal on each TV channel with simultaneous picture, audio and trap markers on both channel and intermediate frequencies.

Oscilloscope ST-2A. Reports from thousands indicate this scope does the job they need in TV circuit work. Used in conjunction with the G-E Sweep and Marker you have an unbeatable combination. Special features include wide frequency response plus DC amplifier to adapt the equipment to other applications.

Balanced Output Adaptor ST-8A. Converts single-ended Sweep Generator output to balanced output for 300 ohm television receiver work.



Model ST-4A



Model ST-5A



Model ST-2A



GENERAL  ELECTRIC

General Electric Company, Section 993
Electronics Park, Syracuse, N. Y.
Please send me complete specifications on G-E
TV Test Equipment.

NAME.....
COMPANY.....
ADDRESS.....
CITY..... STATE.....

BARGAINS · BARGAINS · BARGAINS

BARGAINS · BARGAINS · BARGAINS

Famous
STEVE-EL
BRANDED

TUBES

All Brand New
Individually Boxed
FAR BELOW WHOLESALE COST!

1A7	\$.59	6AT6	\$.37	6SA7	\$.52	12AT6	\$.48	25L6	\$.48
1B3	\$.63	6AX4	\$.52	6SG7	\$.49	12AT7	\$.68	25Z6	\$.42
1P5	\$.54	6B8	\$.45	6SK7	\$.52	12AU7	\$.48	35C5	\$.47
1R5	\$.56	6BA6	\$.45	6SL7	\$.52	12AV6	\$.56	35L6	\$.48
1S5	\$.48	6BC7	\$.58	6SN7	\$.42	12AX7	\$.69	35W4	\$.37
1U4	\$.48	6BC7	\$.86	6SQ7	\$.74	12AZ7	\$.94	35Z5	\$.33
1U5	\$.48	6BE6	\$.48	6SR7	\$.42	12BA7	\$.59	50C5	\$.48
1X2	\$.53	6BG6	1.21	6T8	\$.74	12BB6	\$.46	50L6	\$.48
3V4	\$.47	6BG6	\$.62	6U6	\$.57	12BE6	\$.59	60	\$.47
5U4	\$.46	6B16	\$.74	6V8	\$.46	12B7	\$.52	117Z3	\$.38
6A7	\$.62	6C4	\$.34	6V8	\$.46	12C7	\$.52		\$.36
6A8	\$.51	6CB6	\$.48	6W4	\$.45	12S7	\$.49	SPECIAL DISCOUNTS	
6AC5	\$.52	6CD6	1.21	6W6	\$.52	12SN7	\$.42	50 Asst.	5%
6AK5	1.14	6F6	\$.49	6X4	\$.37	14AF7	\$.59	100 Asst.	10%
6AL5	\$.41	6J5	\$.37	6X5	\$.42	14N7	\$.64		
6AU6	\$.43	6J6	\$.79	7C5	\$.52	19T8	\$.78		
6AV6	\$.37	6K6	\$.41	7K7	\$.62	25B06	\$.77		
6AS5	\$.49	6L6G	\$.89	7X7	\$.48	25W4	\$.48		
6AQ5	\$.39	6E4	\$.44	12A6					

INTERCOM SPECIAL



Now you can own an intercom that has a thousand uses at a price you would normally pay for a kit. This intercom comes housed in wooden cabinets completely wired and ready to operate. Outfit consists of one master, one sub station and fifty feet of two wire cable. Ideal for home as baby sitter. Perfect for office or factory. Order now as quantities are limited.

\$15.95

YOUR COST COMPLETE only...

SUPREME TESTERS



Model 600
— Tube &
Tester **\$89.95**

Model 616
— Tube &
Battery
Tester **\$69.95**

WEN ELECTRONIC SOLDERING GUN



250 Watts.
Choice
of red,
green,
black. **97¢** each
Lots of 3 **\$8.64**

Write for new Fall catalog just off the press.

Visit our new store, 166 Washington St., N. Y. C.

Minimum order \$5.00.

STEVE-EL ELECTRONICS CORP.

Dept. N-9 61 Reade St., New York 7, N. Y. Cortland 7-0086

COMPARISON PROVES

EICO OFFERS GREATEST V-O-M values!



GET the MOST for your money — Before you buy, see chart below!

World-renowned **EICO**
VOLT-OHM-MILLIAMMETERS

- * #536 KIT \$12.90. Wired \$14.90
- * #526 KIT (with 1% multipliers) only \$13.90. Wired \$16.90

VERIFY AT YOUR DEALER'S	EICO \$12.90-up (KIT)	Co. A	Co. B	Co. C	Co. D
31 ranges?	YES	No	No	No	No
Full-size 3-inch meter?	YES	Yes	Yes	Yes	No
400 ua sensitivity?	YES	Yes	Yes	Yes	No
Zero to 1 v. range on both AC and DC?	YES	No	No	No	No
5000 v. range on both AC and DC?	YES	Yes	No	Yes	No
AC/DC sens: 1000 a /v.?	YES	Yes	Yes	Yes	No
DC and AC Current Ranges?	YES	No	No	No	No
In KIT and Wired form?	YES	Wired Only	Wired Only	Wired Only	Wired Only
Lowest cost in the industry?	YES See Above	No	No	No	No

Write for FREE Catalog MR-9 & name of local dealer. Prices 5% higher on West Coast.

ELECTRONIC INSTRUMENT CO., Inc.
84 WITHERS STREET, BROOKLYN 11, N. Y.

Electron

Tube

Technicians

We now have openings for work in the fabrication and processing of experimental electron tubes.

Applicants should be high school graduates with a natural aptitude for making small parts. Experience in electronics, precision machine work and experimental tube work is desirable.

Address resume of experience and training to

Hughes

RESEARCH AND DEVELOPMENT LABORATORIES

Technical Personnel Department
Culver City, Los Angeles County,
California

1954 Zenith TV Sets (Continued from page 62)

where they are separated for the vertical and horizontal sweep circuits.

A 6AQ7GT duo-diode-triode is used in a conventional a.f.c. circuit for the horizontal oscillator. The duo-diode section compares the phase of the horizontal output pulse with the sync pulse, and furnishes the triode control section with a d.c. voltage proportional to the phase difference. A change in phase between the two compared waveforms changes the d.c. voltage to the triode section of the 6AQ7GT, and this changes the latter's internal resistance. Since this triode section is connected in series with condenser C_{55} , across the horizontal oscillator tank coil, a change in the triode's plate-to-cathode resistance will change the oscillator's frequency. If the internal resistance of the triode section is increased, the value of C_{55} is, in effect, reduced, and the oscillator frequency increases, and vice versa.

Condenser C_{56} and resistor R_{64} at the grid of V_{15H} form an anti-hunt circuit which reduces the overswing which exists when a correcting voltage is applied to a control circuit.

The horizontal oscillator is a conventional *Hartley* circuit using one-half of a 6SN7GT. The oscillator applies a positive pulse to the second section of the 6SN7GT, the horizontal discharge tube, initiating the production of the saw-tooth waveform applied to the horizontal output tube, a 6BQ6GT. A conventional high-voltage circuit, using an autotransformer, develops the high voltage for the picture tube as well as the horizontal deflection voltage for the yoke coils.


A.G.C. Circuit

The a.g.c. amplifier is of the "gated" type, in which the a.g.c. voltage developed is proportional to the amplitude of the transmitted sync pulses, and not to the average of the composite video and sync.

The tube used is one-half of a 12AX7 (the other half is used as the vertical oscillator). Fixed bias is applied to the cathode by connecting it to a voltage divider network consisting of R_{65} , R_{66} , and R_{67} . The resistor R_{65} is adjustable so that the cathode may be operated at the proper value for "gating" of the 12AX7 on the sync pulses only, and not on the pedestal. The grid is held at a fixed potential by means of another voltage divider network which consists of R_7 and R_{68} . R_7 connects to the 12BY7 video amplifier plate circuit and to "B+" through the video amplifier plate load resistors. This network also supplies the grid with the composite video and sync signal. However, as mentioned before, only the sync pulses cause conduction in the 12AX7 since the pedestal and video are below the grid cutoff potential point. The sync pulses at the 12AX7 grid are in the positive

TRIO

AMERICA'S MOST DEPENDABLE TV ROTATOR

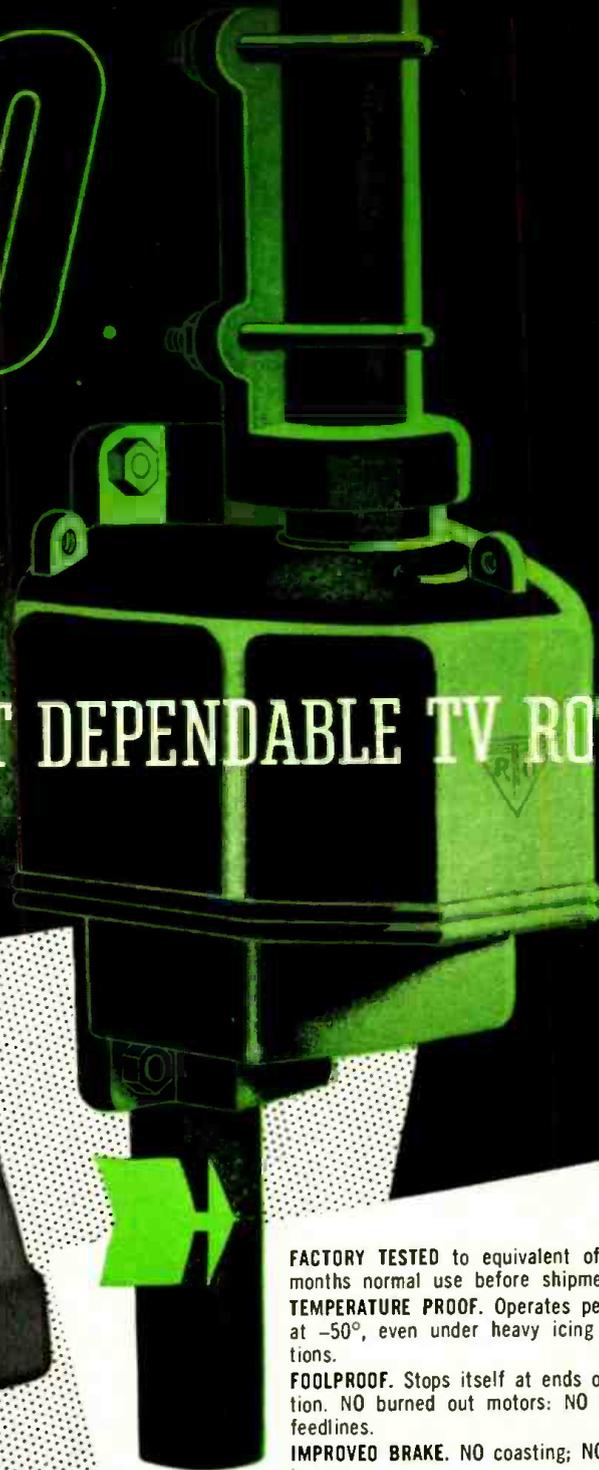

FACTORY TESTED to equivalent of three months normal use before shipment.

TEMPERATURE PROOF. Operates perfectly at -50° , even under heavy icing conditions.

FOOLPROOF. Stops itself at ends of rotation. NO burned out motors; NO broken feedlines.


IMPROVED BRAKE. NO coasting; NO drifting.

TWO MOTORS. Separate motor for each direction of rotation.

SMART—EASY TO USE Control unit. Indicates direction without turning rotator.

TWO YEAR GUARANTEE instead of the usual one.

**Write for literature.*

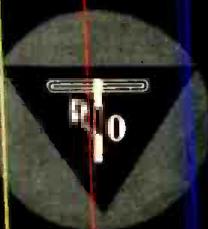

TRIO Manufacturing Co.

GRIGGSVILLE, ILLINOIS

Latest Books for TV "KNOW-HOW"!



TV MANUFACTURERS' RECEIVER TROUBLE CURES VOL. 1, VOL. 2, VOL. 3 and VOL. 4

Positive cures for TV troubles! Gives you exact directions for correcting TV receiver performance "bugs". Each cure is official, factory-authorized, direct from the receiver's manufacturer. Listings by manufacturer and model or chassis number. Helps correct the most difficult faults—picture jitter, hum, instability, buzz, tearing, etc.

- Vol. 1, 115 pages (5¼ x 8¼").....\$1.80
Covers 12 brands, Admiral through Dumont
- Vol. 2, 117 pages (5¼ x 8¼").....\$1.80
Covers 11 brands, Emerson through Jackson
- Vol. 3, 119 pages (5¼ x 8¼").....\$1.80
Covers 16 brands, Kaye-Halbert through Philco
- Vol. 4, over 115 pages (5¼ x 8¼").....\$1.80
Covers 10 brands, Philharmonic through Shaw TV

VOLUME 5 COMING SOON!

Prominent manufacturers not in first 4 volumes
ONE SERVICE JOB WILL MORE THAN PAY THE COST OF THIS SERIES OF BOOKS!

OBTAINING AND INTERPRETING TEST SCOPE TRACES

by J. F. Rider

Over 500 actual photographs of test scope traces. Shows how to use scopes and what traces mean. Valuable for servicing TV receivers, FM and AM radio receivers, audio systems and test equipment. Specific test equipment set-ups shown with each application. No other book like it! Over 140 pages... Only \$2.40

HOW TO USE METERS

by J. F. Rider

Panel type, volt-ohm-milliammeters, vacuum tube voltmeters for servicing radio and TV receivers, audio amplifiers, power supplies; for use and repair of ham transmitters. Written for the service technician, the TV and Radio student and hams.
Over 140 pages.....Only \$2.40

TV SWEEP ALIGNMENT TECHNIQUES

by Art Liebscher, Test Equipment Specialist

Never before has there been a book such as this on TV sweep alignment! An expert gives you accurate time-saving methods—and tells you how they work. Introduces the new Supermark method. Chock-full of sweep curve pictures. Valuable for servicing in UHF signal areas. 123 (5½ x 8½") pp., illus.....\$2.10

HOW TO USE SIGNAL AND SWEEP GENERATORS

By J. R. Johnson

First book on all types of signal and sweep generators. Gives test uses and discusses problems and their solutions in using this equipment. Applications of all signal and sweep generators in AM, FM radio and TV servicing.
Over 120 (5½ x 8½") pages.....\$2.10

GUIDE TO AUDIO REPRODUCTION

By David Fideiman

A to Z explanation of the reproduction of sound. Design, construction, assembly and testing of sound systems and their components. Valuable for service technicians, engineers, amateurs.
Over 250 (5½ x 8½") pp., illus.

RADIO TROUBLESHOOTING GUIDEBOOK

By J. F. Rider and J. R. Johnson

Here is a troubleshooting guidebook that covers the more than 100 million radio receivers now in use! Explicit information about troubles and possible causes. Completely practical for the radio service technician and student. Over 140 (5½ x 8½") pages.

Write for information on all RIDER books.

Buy these books now from your jobber... bookstore
If not available from these sources, write to:

JOHN F. RIDER Publisher, Inc.
Dept. RN 9 480 Canal Street, New York 13, N. Y.

direction, with respect to ground.

The 12AX7 plate load resistor, R_{51} , is returned to the cathode and its voltage divider. A 15,750-cycle pulse, approximately 100 volts in peak value, is taken from the grid of the horizontal discharge tube and applied to the 12AX7 plate through C_{11} . If the horizontal oscillator is operating at 15,750 cps, and is in phase with the transmitted horizontal sync pulse, the oscillator pulse will be applied to the 12AX7 plate at the same instant that the sync pulse is applied to its grid. The plate will be driven in a positive direction and the tube will conduct down through R_{51} . Since the plate is conducting heavily at this time, the potential will swing in the direction of ground. This negative excursion will be applied through R_{50} to C_{19} and C_{20} , and through R_{50} to C_{31} . These condensers will accumulate a negative charge. The time constant of the a.g.c. filter is comparatively long and, since the charging process repeats each time a horizontal sync pulse appears at the 12AX7 grid, the average voltage on the a.g.c. line, with respect to ground, will be negative. The degree of conduction in the 12AX7 is determined by the amplitude of the positive sync pulse applied to its grid, therefore, the negative a.g.c. voltage will vary in proportion to the sync pulse amplitude which, in turn, is proportional to the strength of the signal being received.

In a weak signal area, very little a.g.c. voltage will be developed since the sync pulse applied to the 12AX7 grid will be low in amplitude, and will not drive the tube into heavy conduction. Consequently, the gain of the r.f. and i.f. amplifiers will increase. When the signal is very weak, the 12AX7 plate, being returned through R_{51} to cathode and through R_{10} to "B+", will swing in a positive direction and the a.g.c. voltage, with respect to ground, may actually be of a positive polarity. The 6BK7A r.f. amplifier grid, however, is returned to the a.g.c. line through a 2.2-megohm resistor (R_{30}) and, due to contact potential, will be maintained slightly negative even though the a.g.c. line may be positive. The 6CB6 first i.f. amplifier has some bias applied to its cathode (the cathode is returned to ground through a 56 ohm and two 220 ohm resistors, R_{11} and R_{22}), and the a.g.c. voltage is permitted to swing positive by this amount. This arrangement is designed to provide a good noise figure both on very weak and moderately weak signals. When the signal level increases to the point where the a.g.c. voltage passes through zero, the noise figure of the r.f. amplifier is no longer important, and the 6BK7A is then rapidly cut off by a further increase of a.g.c. voltage in a negative direction. This type of a.g.c. circuit is known as a "double delayed" a.g.c. system.

Some television technicians experience great difficulty in locating trouble in gated a.g.c. circuits. Much of this


confusion is caused by the fact that defects in some other circuit will be indicated as an apparent fault in the a.g.c. As an example of what might happen, a receiver overloads on a strong local signal and the a.g.c. delay control has little or no effect. The technician undoubtedly would try a new 12AX7 tube before proceeding further. If this did not eliminate the trouble, it is possible that the defect could be located in the i.f. strip, the crystal diode detector, the video amplifier, the horizontal oscillator, or the a.g.c. circuit itself. If the overloading is severe, the picture probably would be negative; the sync would be compressed and possibly inverted. An oscilloscope examination of the diode output would be of little value except to confirm this.

Probably the best procedure for servicing gated a.g.c. systems would be as follows: first, make certain that the 12AX7 a.g.c. amplifier, the 12BY7 video amplifier, and the 6CB6 first i.f. amplifier tubes are good. The second step would be to disable the a.g.c. by applying from -3 to -6 volts to the a.g.c. line. This fixed voltage can be supplied by a small "C" battery, the positive terminal of which should be connected to chassis (ground). The application of the fixed bias should stabilize the circuit, at least to the extent where intelligent measurements can be made. It should be possible to stabilize the sweep oscillator. If the vertical stabilizes but the horizontal does not, it probably indicates some fault in the horizontal oscillator circuit. As described before, the plate voltage pulse for the 12AX7 is taken from the grid of the horizontal discharge tube. If this pulse is low in amplitude, the a.g.c. tube plate will not be driven sufficiently positive and very little a.g.c. voltage will be developed. If trouble in this circuit is suspected, the peak voltage value of the pulse at either the horizontal discharge tube grid or the a.g.c. tube plate may be measured and compared against the value shown on Fig. 1. If there is much difference in the pulse amplitude measured at pin 1 of the 6SN7 and pin 6 of the 12AX7, condenser C_{11} may be open. If the a.g.c. line is positive with respect to ground, or if the circuit continues to overload with the battery bias connected, C_{11} , in series with the coaxial line from the tuner to the i.f. input, may be leaky or shorted. If the peak value of the composite sync signal at pin 7 of the 12AX7 is low, the defect may be in the video amplifier, but is more likely to be a defective crystal diode.

Alignment

The alignment procedure for the video i.f. and sound circuits of the Zenith "Super K" chassis is given in Table 1.

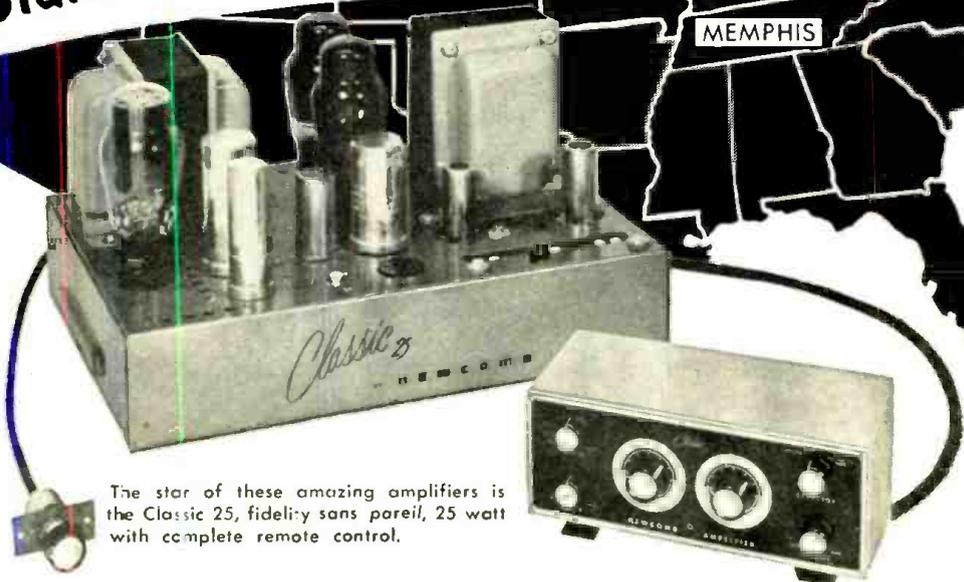When aligning the sound circuits, the signal to the receiver must be below the limiting level of the 6BN6. A "hiss" will accompany the sound



The star of these amazing amplifiers is the Classic 25, fidelity sans pareil, 25 watt with complete remote control.

AMERICA'S FINEST HOME MUSIC AMPLIFIERS

Everywhere they are shown these new amplifiers by Newcomb create a positive sensation. Everyone has a good word for them. Acclaimed at the shows and fairs in New York, Chicago, Memphis and California for their noticeably better sound, unique new features and unbelievable values in every price group. Thousands who have seen them make enthusiastic comments like this:


... "the first really new amplifiers in years" ... "the best record reproduction I've ever heard" ... "they solve the toughest installation problems" ... "the Audi-balance feature really does away with tube balancing problems" ... "Adjusta-panel makes cabinet mounting a breeze" ... "I've never seen anything so beautifully designed for the home" ... "women will love them" ... "I find the A.E.S. response position very pleasing" ... "I want the Classic 25 for myself" ... "the finest coverage yet, there's something here for everyone" ...

Those are the good words everywhere. If you have

not yet seen them for yourself, there's a treat in store for you.

Substantial installation savings

Exclusive Newcomb features make all eight of these new amplifiers easier to install and make possible substantial savings in cabinetry and labor. Models with complete remote control offer a unique design which eliminates the usual necessity of a remote control being near the amplifier, tuner and changer. This permits installation savings frequently greater than the cost of the amplifier itself. These items can now be installed in any out of the way location, leaving only the remote unit and the speaker in the living room, with no messy confusion of wires. All models have "Adjusta-panel" feature to extend control shafts instantly up to 3/4" for easy cabinet mounting. Investigate all the amazing advantages of these amplifiers. You will be thrilled with their outstanding improvements.

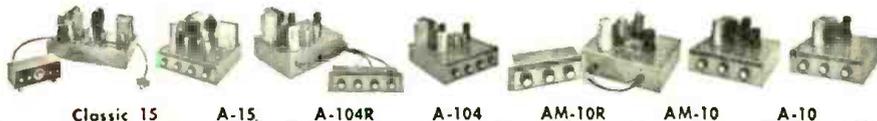

Send for catalog of 8 completely new amplifiers priced from \$39.50 to \$269.50 audiophile net.

Newcomb
15 years of quality leadership

NEWCOMB AUDIO PRODUCTS CO. DEPT. F 6824 LEXINGTON AVENUE, HOLLYWOOD 38, CALIFORNIA

September, 1953

109

BUILD 15 RADIOS

AT HOME ONLY

With the New Improved 1953 **\$19.95**

Progressive Radio "EDU-KIT"

NOW INCLUDES

**SIGNAL TRACER
and
CODE OSCILLATOR**

- FREE TOOLS WITH KIT
- ABSOLUTELY NO KNOWLEDGE OF RADIO NECESSARY
- NO ADDITIONAL PARTS NEEDED
- EXCELLENT BACKGROUND FOR TELEVISION
- 10-DAY MONEY-BACK GUARANTEE



WHAT THE PROGRESSIVE RADIO "EDU-KIT" OFFERS YOU

The "Edu-Kit" offers you a Home Radio Technician Course at a rock-bottom price. You will learn how to identify Radio Symbols and Diagrams; how to build radios using regular radio schematics; how to wire and solder in a professional manner. You will learn how to operate Receivers, Transmitters, and Audio Amplifiers. You will learn how to service and trouble-shoot radios. You will learn code. You will receive training for F.C.C. license. In brief, you will receive a basic education in Radio exactly like the kind you would expect to receive in a Radio Course costing several hundred dollars.

THE KIT FOR EVERYONE

It is not necessary that you have even the slightest background in science or radio. The "Edu-Kit" is used by young and old; by radio schools and clubs; by the Veterans' Administration for Vocational Guidance and Training. No instructor is required. Instructions are complete, simple and clear. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD

The "Edu-Kit" uses the principle of "Learn by Doing." Therefore you will build radios, perform jobs, and conduct experiments to illustrate the principles which you learn. You begin by learning the function and theory of each of the radio parts. Then you build a simple radio. Gradually in a progressive manner, you will find yourself constructing more advanced multi-tube radio sets, and doing work like a professional Radio Technician. The "Edu-Kit" Instruction Books are exceedingly clear in its explanations, photographs and diagrams. These sets operate on 105-125 V. AC-DC.

The Progressive Radio "EDU-KIT" Is Complete

You will receive every part necessary to build fifteen different radio sets. Our kits contain tubes, tube sockets, chassis, variable condensers, electrolytic condensers, mica condensers, paper condensers, resistors, line coils, selenium rectifiers, tie strips, coils, hardware, tubing, hook-up wire, solder, etc. Tools are included, as well as an Electrical and Radio Tester. Complete, easy-to-follow instructions are provided. In addition, the "Edu-Kit" now contains lessons for servicing with the Progressive Signal Tracer, F.C.C. instructions, quizzes. The "Edu-Kit" is a complete radio course, down to the smallest detail.

TROUBLE-SHOOTING LESSONS

Trouble-shooting and servicing are included. You will be taught to recognize and repair troubles. You will build and learn to operate a professional Signal Tracer. You receive an Electrical and Radio Tester, and learn to use it for radio repairs. While you are learning in this practical way, you will be able to do many a repair job for your neighbors and friends and charge fees which will far exceed the cost of the "Edu-Kit." Our Consultation Service will help you with any technical problems which you may have.

FREE EXTRAS IN 1954

- Electrical and Radio Tester • Electric Soldering Iron • Book on Television • Radio Trouble-Shooting Guide • Membership in Radio-Television Club • Consultation Service • Quizzes • Training for F.C.C. License.

Send me the "Edu-Kit" with Money-back Guarantee—include ALL FREE extras.

- Check or M.O. enclosed—postage prepaid
- C.O.D. (U. S. Only)—I will pay postage
- Send further information

Outside U.S.A.—cash orders only; send international M.O. or check on U.S. bank. Postage Prepaid. "Edu-Kit" for 210-250 V. AC/DC \$22.45.

NAME _____

ADDRESS _____

PROGRESSIVE ELECTRONICS CO.

497 Union Ave., Dept. RN-22, Brooklyn 11, N. Y.

when the signal is below this level. To obtain this signal condition, a step attenuator should be used. Also, be certain to prevent leakage by using short leads between the attenuator and antenna terminals on the receiver. Use approximately six feet of 300-ohm shielded line between the antenna transmission line and the attenuator. The shield from the transmission line should be connected to the attenuator, and the attenuator itself grounded to the TV chassis.

What's New in Radio

(Continued from page 84)

fit into a woman's purse like a compact or be tucked into a man's breast



pocket. It is smaller than a miniature camera and can be held comfortably in the palm of the hand.

The circuit uses subminiature parts throughout and is powered by self-contained batteries. The set has a full-vision dial with large easy-to-read numbers, automatic volume control, and a full-volume "super speaker".

SERVICE TOOL

Aviation Service Supply Co., Stapleton Field, Denver, Colorado has introduced a new precision-made nut and screw starter to aid technicians in starting small nuts as well as screws in difficult, hard-to-reach places.

Designed for use in the radio, electronic, communication, and instrument fields, the tool has a special lever mechanism in the handle which controls the movable blades and adjusts them for gripping all standard sizes of small nuts and screws.

The unit has a pair of movable blades projecting from a sleeve attached to the handle. As these blades are pushed into the sleeve, the mechanism inside the handle causes them



to rotate inward thus forming a "V" shaped end, which grips the screw head and maintains the necessary tension to hold it until the screw is started.

It is available in six different sizes to accommodate nuts and screws from #6 to 1/4" nut and from a #4 to a #10 screw. Special sizes are available on a custom basis.

GERMANIUM DIODES

A new line of germanium diodes featuring vacuum tight, moisture-resist-

ant seals as well as good mechanical stability is now being offered by Bomac Laboratories, Inc. of Salem Road, Beverly, Mass.

According to the company, the use of a ceramic case insures stable electrical characteristics and complete isolation from adjacent circuitry. The diodes consist of a small, low-loss ceramic case into which two end caps are threaded. Metallization of the case surfaces allows vacuum tight ceramic-metal seals to be made. The specially-treated germanium pellet and tungsten whisker are precisely adjusted for optimum performance by use of force-fitting, knurled, nickel pins.

The use of nickel terminal pins and flexible, tinned leads permits the unit to be either clipped into spring holders or soldered directly for circuit applications.

The Semi-Conductor Department of the company will provide complete information on request.

"LAVALIER" MIKE

Electro-Voice, Inc. of Buchanan, Michigan has introduced a small-sized lavalier-type dynamic microphone designed for chest, desk, or hand use in public address work.

The Model 647 offers full-range E-V dynamic microphone quality, rugged-



ness, and performance characteristics for indoor and outdoor use, according to the company. Frequency response is from 60 to 13,000 cps, specially compensated for chest resonance. Slightly rising characteristic is specifically calculated to provide crisp, clear pick-up and reproduction when used against the chest. Output level is -57 db.

For further information, write for Bulletin 201.

PARTS KITS

Carl Cordover & Co., 100 Warren St., New York 7, New York has introduced five new parts kits for service technicians, amateurs, laboratory men, dealers, experimenters, and engineers.

The line includes one resistor and four condenser kits. All assortments are selected to include the most-often used sizes for replacement work. The resistor kit (RK-100) contains 100 resistors; the ceramic condenser kit

MORE for your Kit Dollar!

All Collins Tuner Kits are complete with punched chassis, tubes and all other necessary materials. Sub-assemblies; tuning units, IF amplifier, etc. wired, tested and aligned. Join thousands of satisfied Collins users... order today!

BUY DIRECT AND SAVE

COLLINS

AUDIO PRODUCTS CO.

'PRE-FAB' TUNERS and COMPONENTS




COLLINS AUDIO PRODUCTS CO. is in no way affiliated with Collins Radio Co.

FM/AM Tuner Kit

The original 15 tube deluxe FM/AM pre-fab kit redesigned on a smaller chassis. The tuner now measures 14" wide by 12" deep by 7 1/2" high. This attractive new front and dial assembly opens up new applications where space is at a premium. Kit includes everything necessary to put it into operation — punched chassis, tubes, wired and aligned components, power supply, hardware, etc. Kit comprises FMF-3 tuning unit, IF-6 amplifier, AM-4 AM tuning unit, magic eye assembly and complete instructions. All tubes included. Shipping weight 19 lbs.

\$77.50

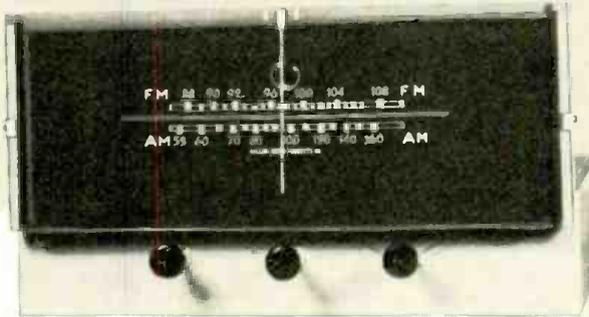

FM Tuner Kit


The FM-11 tuner is available in kit form with the IF Amplifier mounted in the chassis, wired and tested by us. You mount the completed RF Tuning Unit and power supply, then after some simple wiring, it's all set to operate. 11 tubes: 6J6 RF amp, 6AG5 converter, 6C4 oscillator, 6BA6 1st IF, (2) 6AU6 2nd and 3rd IF, (2) 6AU6 limiters, 6AL5 discriminator, 6AL7-GT double tuning eye, 5Y3-GT rectifier. Sensitivity 6 to 10 microvolts, less than 1/2 of 1% distortion, 20 to 20,000 cycle response with 2DB variation. Chassis dimensions: 12 1/2" wide, 8" deep, 7" high. Illustrated manual supplied. Shipping weight 14 lbs.

\$55

AM Tuner Kit

A twin for the FM-11! A wide-band T.R.F. high fidelity AM tuner kit with special features. A new Collins design for those who desire the very finest AM performance. Tuning range: 530 KC to 1650 KC; Bandpass: 20 KC Distortion: less than 2%; Frequency response to 10,000 cycles; whistle filter; R.F. circuits wired and aligned. You mount the power supply and dial and it's ready to go. Operates into any high fidelity pre-amplifier control unit or standard single chassis amplifier. No tone controls. Six tubes. Shipping weight 14 lbs.

\$59.50

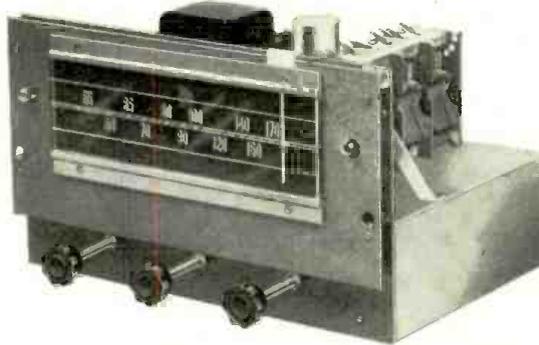

Selected Basic Components For Special Applications

FMF-3

The best for FM. The most sensitive and most selective type of "front end" on the market. 6 to 10 microvolts sensitivity. Image ratio 500 to 1. 6J6 tuned RF stage, 6AG5 converter, 6C4 oscillator. Permeability tuned, stable and drift-free. Chassis plate measures 6 1/2" x 4 1/2". In combination with the IF-6 amplifier, the highest order of sensitivity on FM can be attained. Tubes included as well as schematic and instructions. Draws 30 ma. Shipping weight FMF-3: 2 1/2 lbs. Dial available @ \$3.85.

IF-6

A remarkable value! 6 tubes are used in the IF amplifier: 6BA6 1st IF, (2) 6AU6 2nd and 3rd IF's, (2) 6AU6 limiters and 6AL5 discriminator. High gain, wide-band response (200 KC) for highest fidelity. 20 to 20,000 cycles. Distortion less than 1/2 of 1%. Draws 40 ma. @ 220 volts. Chassis plate dimensions: 11-5/16" x 2 1/2".


Shipping weight: 3 lbs.

AM-4

Tops in AM superhet performance! A 3-gang tuning condenser gives 3 tuned stages with high sensitivity and selectivity. Assembly is completely wired, tested and aligned ready for immediate use. Frequency coverage 540 KC to 1650 KC at a sensitivity of 5 microvolts. Tubes 6BA6 RF amplifier, 68E6 converter, 6BA6 IF amplifier and 6AT6 detector. Draws 30 ma @ 220 Volts. Mounts on a chassis plate measuring 4" x 7 3/8". Shipping weight 2 1/2 lbs. Dial available at \$3.85.

Slide Rule Tuning Dial

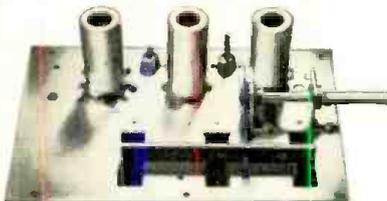available separately — for use with FMF-3 or AM-4. **\$3.85**



FMF-3 Tuning Unit

\$15.25



IF-6 Amplifier

\$19.75



AM-4 Tuning Unit

\$24.50

MAIL COUPON TODAY

To: Collins Audio Products Co. Inc.
P. O. Box 368, Westfield, N. J.
Tel. WESTfield 2-4390

FM Tuner Kit FM/AM Tuner Kit AM Tuner Kit
 FMF-3 Tuning Unit IF-6 Amplifier AM-4 Tuning Kit
 Slide Rule Dial

NAME

ADDRESS

CITY STATE

Amount for Kit \$ See weights, add shipping cost \$

Total amount enclosed \$ Check Money Order

WHEN YOU THINK OF TUNERS, THINK OF COLLINS AUDIO PRODUCTS

Windsor TUBES

RADIO & TV RECEIVING

TESTED and GUARANTEED for PEAK PERFORMANCE!

TO MERIT YOUR CONFIDENCE—to insure your satisfaction—Every tube we ship has been tested in a radio or TV set for PEAK PERFORMANCE. Each tube is attractively packaged in individual carton—and, Each WINDSOR Tube you buy carries the full RTMA GUARANTEE!

Type	Each	Type	Each	Type	Each	Type	Each	Type	Each
1A7GT	\$.61	6AK5	\$.95	6CB6	\$.53	7A4/XXL	\$.57	7Q7	\$.62
1B3GT	\$.63	6AL5	\$.40	6CD6G	1.85	7A5	\$.70	7R7	\$.70
1C6	\$.96	6AO5	\$.46	6E5	\$.65	7A6	\$.57	757	\$.90
1E7GT	\$.99	6AO7	\$.68	6F5GT	\$.49	7A7	\$.58	7V7	\$.92
1H5GT	\$.57	6AR5	\$.38	6J5GT	\$.40	7A8	\$.56	7X6	\$.62
1L4	\$.46	6AS5	\$.50	6J6	\$.62	7AD7	1.05	7Y4	\$.45
1L6	\$.60	6AT6	\$.38	6K6GT	\$.41	7AF7	\$.63	7Z4	\$.50
1N5GT	\$.57	6AU6	\$.43	6L6G	\$.80	7AG7	\$.65	12AT6	\$.48
1R5	\$.56	6AV6	\$.37	6L6GA	\$.80	7AH7	\$.65	12AT7	\$.68
1S4	\$.61	6AX4	\$.65	6Q7GT	\$.50	7AJ7	\$.70	12AU6	\$.43
1S5	\$.47	6BA6	\$.45	6S4	\$.46	7B4	\$.54	12AU7	\$.53
1T4	\$.56	6BA7	\$.60	6S8GT	\$.68	7B5	\$.51	12AV6	\$.37
1T5GT	\$.71	6BC5	\$.53	6SA7GT	\$.52	7B6	\$.52	12AV7	\$.79
1U4	\$.55	6BD5GT	\$.89	6SC7	\$.57	7B7	\$.58	12AX4	\$.65
1U5	\$.46	6BD6	\$.49	6SF5GT	\$.60	7C4	1.05	12AX7	\$.61
1X2A	\$.67	6BE6	\$.46	6SH7GT	\$.47	7C5	\$.56	12AY7	1.95
2X2	1.29	6BF5	\$.60	6SK7GT	\$.50	7C6	\$.50	12BA6	\$.45
3Q4	\$.60	6BF6	\$.39	6SL7GT	\$.62	7C7	\$.58	12BA7	\$.60
3Q5GT	\$.65	6BG6G	1.34	6SN7GT	\$.54	7E5	\$.85	12BD6	\$.46
3S4	\$.55	6BH6	\$.57	6SQ7GT	\$.42	7E6	\$.65	12BE6	\$.47
3V4	\$.56	6BJ6	\$.48	6T8	\$.77	7E7	\$.85	12BH7	\$.63
5R4GY	\$.91	6BK5	\$.69	6U8	\$.78	7F7	\$.69	12SA7GT	\$.52
5U4G	\$.40	6BK7	\$.88	6V3	\$.99	7F8	\$.97	12SK7GT	\$.50
5V4G	\$.75	6BL7GT	\$.85	6V6GT	\$.46	7G7	\$.85	12SL7GT	\$.61
5Y3GT	\$.29	6BN6	\$.89	6W4GT	\$.45	7H7	\$.61	12SN7GT	\$.54
5Y4G	\$.39	6BQ6GT	\$.89	6W6GT	\$.57	7J7	\$.85	12SQ7GT	\$.42
6AB4	\$.46	6BQ7	\$.84	6X4	\$.34	7K7	\$.85	14A7	\$.58
6AG5	\$.54	6BZ7	\$.99	6X5GT	\$.33	7L7	\$.85	14AF7	\$.48
6AH4	\$.62	6C4	\$.37	6Y6G	\$.58	7N7	\$.62	14B6	\$.50
								117Z3	\$.39



WRITE FOR Additional Tube Types and Prices. We also stock Special Purpose and Transmitting Tubes at similar savings!

25% Deposit with Order. All Merchandise F.O.B. New York City. For orders less than \$10, add \$1 handling cost. Deduct 2% if full remittance accompanies order. All merchandise subject to prior sale and price change without notice. Dept. N-9

Windsor ELECTRONIC TUBE CO.
1515-N SHEEPSHEAD BAY ROAD, BROOKLYN 35, N. Y.

Now! HANDLE UP TO 90% OF TV TROUBLES

by the easy

PICTURE ANALYSIS METHOD!



PIX-O-FIX TV TROUBLE FINDER GUIDE

By Ghirardi & Middleton

Cut hours of tedious TV troubleshooting to minutes! Make repairs twice as fast! Operation of Ghirardi's new PIX-O-FIX TV TROUBLE FINDER GUIDE is simply itself. Covers all TV receivers. Just turn dial until actual TV screen photo appearing in PIX-O-FIX "window" matches distorted picture on set being repaired. PIX-O-FIX then gives you all possible causes for this trouble and just where they are likely to be found. But that's only the beginning!

WHAT TO DO—HOW TO DO IT

Step-by-step repair instructions follow. Components likely to be faulty are specified. Quick tests are outlined. PIX-O-FIX guides you every step of the way! Remember! PIX-O-FIX is NOT a "fix-it-yourself" gadget for consumers. It is a truly professional device for servicemen, apprentices and students—prepared by two of the nation's foremost service instructors—A. A. Ghirardi and It. G. Middleton.

MONEY BACK IF YOU'RE NOT SATISFIED!

Simply pin a \$1 bill to this ad. Mail with your name and address to the publisher. If not satisfactory, return PIX-O-FIX in 10 days and your \$1 will be refunded promptly. (Price outside U.S.A. \$1.25. Same money-back guarantee!)

Only \$1.

Covers 24 common troubles identified by actual screen photos

• • • 190 possible causes of these troubles localized to receiver stage or section where they are most likely to occur.

• • • 253 step-by-step remedies for these troubles.

• • • 4,500 words in CAUSE AND REMEDY section to show just what to do.

Dept. RN-93, RINEHART BOOKS, Inc., Technical Div., 232 Madison Ave., New York 16, New York

STOP

Volume Control Noise!



"NO NOISE"

Contains the amazing new

PERMA-FILM

- ★ **CLEANS!** Gets rid of dirt and oxidation immediately on contact.
 - ★ **LUBRICATES!** One drop eliminates scratch, hum and noise.
 - ★ **PROTECTS!** NEW Perma-Film assures continued top performance.
- The **PERFECT Contact Restorer**
Cleans and restores volume controls, band switches, push button assemblies, electrical contacts.
- **NOT A CARBON TET SOLUTION**
NO NOISE is a scientific formula especially compounded for contacts!
- 2 oz. Bottle
Net to Servicemen \$1.00
Available in 8 oz. bottles, quart cans and 6 oz. spray can.

Nearest Distributor or order direct from
ELECTRONIC CHEMICAL CORP.
813 Communipaw Ave., Jersey City 4, N. J.


(CK-35) has 35 ceramic units; kit MK-50 contains 50 mica condensers; kit TK-25 offers 25 molded tubular condensers in various capacities; and LV-10 contains an assortment of 10 low-voltage electrolytics.

For further information, contact the company direct.

UNIVERSITY ENCLOSURE

University Loudspeakers, Inc., 80 S. Kensico Ave., White Plains, N. Y. has recently introduced a line of high fidelity corner enclosures for 12" speakers.

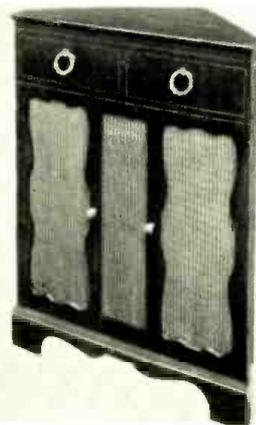The enclosures combine authentic furniture styling with quality sound



reproduction and are available in modern, traditional, or provincial furniture styles. The cabinets are available in a variety of wood finishes. Enclosure dimensions are 37" high, 28" wide, and 15" deep.

Although especially designed to house the company's Model 6201 coaxial speaker, the Model 6200 extended range, or the wide-range "Diffusicone-12", the "Musicorner" can serve as the enclosure for most 12" speakers. Simplified integral construction of both the interior and exterior makes for easy installation.

SELF-POWERED PREAMP


Brook Electronics, Inc., 34 DeHart Place, Elizabeth, N. J. is currently offering a self-powered preamp, the Model 7.

The unit is finished in gold-aluminate enhanced with highly polished walnut end blocks. All of the features of the company's Model 4B have been retained in the new unit with the addition of a built-in power supply. Hum



level is said to be extremely low, well below the thermal noise of the tubes.

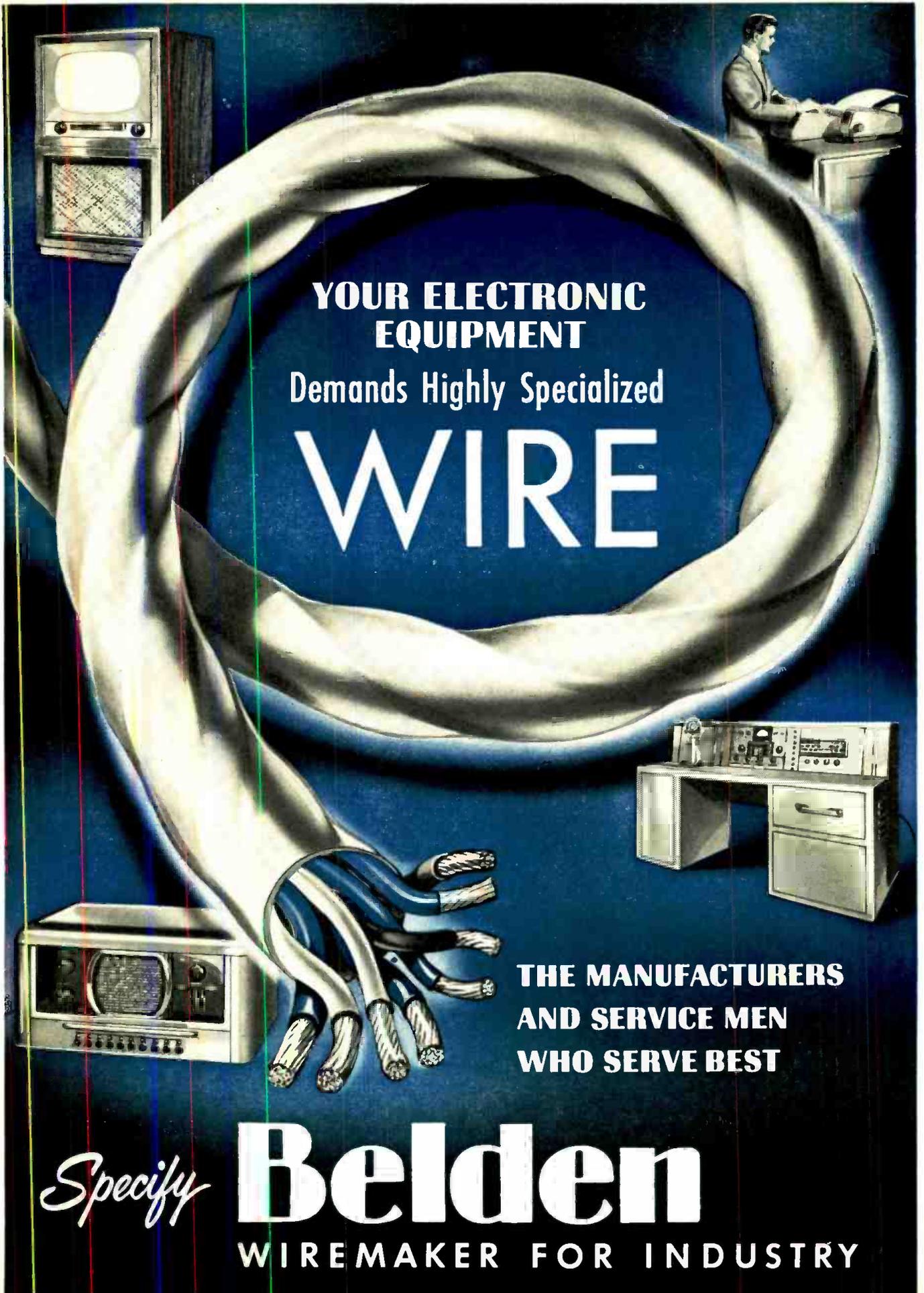Other features include a record playback characteristic control which permits a theoretically exact match of the recording characteristics so



YOUR ELECTRONIC
EQUIPMENT
Demands Highly Specialized
WIRE

**THE MANUFACTURERS
AND SERVICE MEN
WHO SERVE BEST**

Specify

Belden

WIREMAKER FOR INDUSTRY

Train IN
Great COYNE shops
for big pay jobs



IN Television
- Radio



OR
Electricity
- ELECTRONICS

Learn on REAL EQUIPMENT!
in Best Equipped School of its
kind in U. S.

Prepare for your future NOW! Come to the Great Shops of Coyne. Get practical training in opportunity fields—TELEVISION-RADIO—ELECTRICITY—ELECTRONICS. Prepare for a better job in Industry or better service rating if drafted.

WE TRAIN YOU IN CHICAGO

At Coyne you learn on real, full-size equipment. Trained instructors show you how, then you do shop jobs yourself. No previous experience or advanced education needed.

Approved for Veterans

Finance Plan—Enroll now, pay most of tuition later. If you need part-time work to help out with living expenses while at Coyne, we'll help you get it. Special tuition plan for men of draft age.

FREE BOOK Clip coupon for Big Free Illustrated Book. No salesman will call. Act Now.

COYNE
SCHOOL

810 S. Paulina St., Dept. 63-85H
Established 1899
APPROVED for VETERANS

B. W. COOKE, Pres.
COYNE School
810 S. Paulina St., Chicago 12, Ill., Dept. 63-85H
Send FREE BOOK and full details on:

TELEVISION-RADIO ELECTRICITY

NAME

ADDRESS

CITY.....STATE.....



that the tonal balance of bass, middle, and high frequencies will be correct. This control has nine positions to match the better-known makes of records.


Over-all frequency response is within 1 db from 15 to 30,000 cycles.

A data sheet covering the Model 7 is available on request.

RCA TRANSISTORS

The Tube Department of Radio Corporation of America has announced the commercial availability of four types of transistors.

Two point-contact and two junction

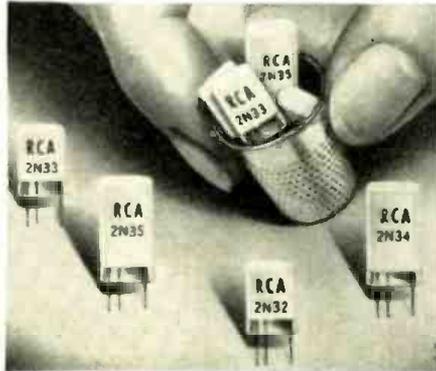


types are now in production. The RCA-2N32 is a point-contact type for large signal applications. The RCA-2N33 is a point-contact type for use as an oscillator up to 50 mc. The 2N34 and 2N35 are junction types, p-n-p and n-p-n respectively. Both are designed for low-power, audio frequency applications.

Further information on these four units is available from the company's tube distributors.

POWER BOOSTER

Kuar Engineering Corp., Middlefield Road, Palo Alto, California has announced a new power booster which is said to increase the power output of any 10-watt mobile radiotelephone transmitter six times.

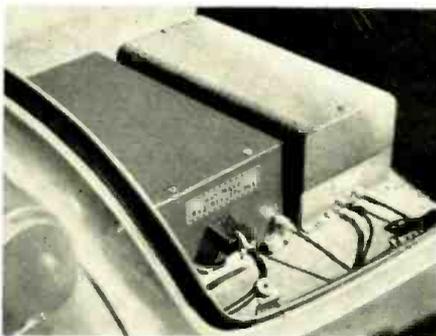The booster is inserted between the low power transmitter and antenna.



The power desired is selected by a switch on the dashboard and the booster is activated when the microphone button is pushed. Because the unit is "instant heating", added power is not drawn from the battery until the mike button is pushed.

The unit may be used with any make of radiotelephone operating in the 152-174 mc. band. It is said to

increase the effective range of the equipment considerably while conforming to the FCC good engineering requirements by using maximum power for such transmissions only when needed.

Electronic Counter

(Continued from page 45)

is four. Since 2^4 equals 16 it means that the counter circuit shown can count up to sixteen. (The zero count also represents a number.) With a decimal system eight tubes would be required for a count of sixteen. This points out the advantages of the binary system, less tubes are required for an over-all count. The visual binary count is shown diagrammatically in Fig. 10. Each vertical row represents the four neon lamps. The different columns show the count from one to fifteen (and also zero).

One of the prime advantages of electronic counters is high-speed operation. The prototype described in this article can perform at a maximum rate of about 100,000 counts-per-second. However since the tally limit is sixteen the master sum could not be

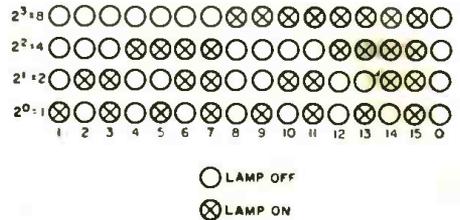


Fig. 10. Indicated count in binary system. Each vertical row represents four lamps on counter panel. When all lamps are extinguished the reading is zero.

indicated at this rate. In addition, the pickup switch could not function at this rate. Other types of counters have been developed which can perform efficiently up to 10,000,000 counts-per-second. For this purpose special unitized decade counters are used which stop at a forced count of ten. With this arrangement, identical prototypes are cross-connected for counting and indicating in the decimal system. One prototype is used for units, another for tens, another for hundreds, another for thousands, and so on. It is only necessary to connect the output of each subassembly in the input of the next higher decade and thereby build up to any degree required. These units also employ the basic four-stage circuit described in this article.

BIBLIOGRAPHY

- Phelps, B. E.: "Dual-Triode Trigger Circuits," *Electronics Engineering Manual*, Vol. 4.
- Potter, J.: "A Four-Tube Counter Decade," *Electronics*, June 1944.
- Blume, R. J.: "Predetermined Counter for Process Control," *Electronics*, February Counters," *Electronics*, March 1948.
- Sharpless, T. K.: "High-Speed N-Scale" 1948.

Free

Midwest

NEW 1954

MIDWEST

TELEVISION
and RADIO Catalog
Featuring a Completely
NEW Line of Magnificent



21" and 27"
TELEVISION
CONSOLES • TABLE MODELS
CHASSIS

ALL-CHANNEL RECEIVERS
with new **UHF**
built-in


EASY TERMS 30 DAYS TRIAL

Here is a brilliant new line of magnificent long-distance 21" and 27" Television receivers in beautiful console, table models and complete chassis — to mark Midwest's 34 years of leadership, 30 Days Trial... Easy Terms... Low Factory Prices. Send coupon for 1954 Catalog TODAY!

Also — Powerful New 1954 World-Ranging
MIDWEST Series 16 RADIOS
In Beautiful Consoles and Complete Chassis



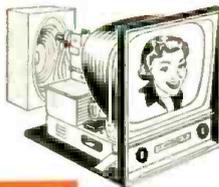Once again Midwest offers its famous series 16 five band AM-FM radio chassis and the magnificent new Symphony Grand Radio-Phonograph with 3-Speed Automatic Inter-Mix Record Player. Also, a complete line of clock radios, table radios, and portables.



MIDWEST 21" Television Chassis. Complete with 12" Speaker.



MIDWEST 21" Table Model Television Receiver.



MIDWEST Luxurious 27" Television Console.

LOW FACTORY PRICES

WRITE IN NAME AND ADDRESS (PLEASE PRINT) ON COUPON OR 2c POSTCARD

MIDWEST RADIO & TELEVISION CORP.
Dept. A-37, 909 BROADWAY • CINCINNATI 2, OHIO
Please send me your new FREE 1954 Catalog.

NAME _____

ADDRESS _____

CITY _____

ZONE _____ STATE _____

MIDWEST RADIO & TELEVISION CORP.

DEPT. A-37, 909 BROADWAY, CINCINNATI 2, OHIO

MONEY MAKERS!

FOR MOBILE-RADIO SERVICE ENGINEERS!

Provide for future expansion in this profitable field, with Lampkin frequency- and modulation-measuring equipment.



For Any Number of Frequencies, AM or FM. The Type 105-B MFM.

The Type 105-B Micrometer Frequency Meter, or MFM, measures center-frequency on any number of nearby transmitters, AM or FM, 0.1 MC. to 175 MC. Performs as signal generator for mobile receivers. 20 MC. up. Meets FCC requirements for mobile services, with accuracy guaranteed better than 0.0025%. Can be checked against WWV. Price \$220.00 net.



The Type 205 FM Modulation Meter for Multiple Mobile Frequencies.

Instantly tunable anywhere, 25 MC. to 200 MC., the Type 205 measures maximum FM deviation due to modulation, as required by the FCC. Indicates 0-25 KC. deviation. Simple to use, easy to carry. No charts or tables. Price \$240.00 net.

Send name and address for literature

Name
 Address
 City State

LAMPKIN LABORATORIES, INC.
 MFM DIVISION
 BRADENTON, FLORIDA



Let MILTON S. KIVER Help You Prepare For U.H.F.-TV And...

TELEVISION SERVICING

Easy to TRAIN AT HOME This Practical Way!

Men with the right training in Television Servicing are in big demand . . . pull down big pay. T.C.I. TRAINS YOU RIGHT with easy-to-follow technical training designed by servicemen for servicemen! You learn practical, professional type Television Servicing without leaving your present job. Included are money-making extras such as set conversion, master antenna installation, U.H.F.-TV and field servicing short cuts. You can start earning Television money after the first few lessons. You learn to test, trouble shoot and repair all types of TV sets the proven, practical way!

HERE'S HOW YOU GET EXPERIENCE!


You train on your own large screen modern television receiver, furnished as part of your course. This set is yours to keep! As an optional feature you can get two weeks of actual field experience out on service jobs and on the repair bench for Chicago's largest independent servicing organization. You learn Television Servicing by actually doing Television Servicing . . . you get the practical know-how you need to qualify for BIG MONEY in this fast-growing field! Age is no barrier, Many TCI students are over 40!

VETERANS!
 T.C.I. is approved for G.I. training under Public Law 550. Check coupon.

ACT NOW! Mail coupon for FREE Catalog and SAMPLE LESSON. Write TODAY!

TELEVISION COMMUNICATIONS INSTITUTE

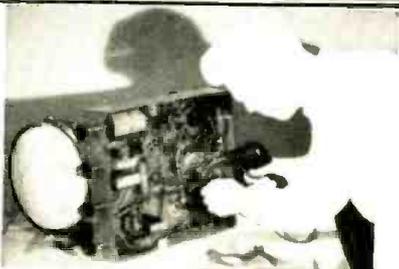205 W. Wacker Dr., Dept. L-AP Chicago 6, Ill.



YOU GET and keep modern large screen Television receiver.

YOU DO actual testing, servicing, trouble shooting and repairing

BEGINNERS! LEARN ABOUT NEW BASIC TV COURSE!
 You don't need radio experience for practical, home-study training in Basic Television. Start earning money in TV after first few easy lessons. Check coupon for details.

MAIL NOW FOR FREE BOOKLET

MILTON S. KIVER, President
 TELEVISION COMMUNICATIONS INSTITUTE
 205 W. Wacker Dr., Dept. L-AP, Chicago 6, Ill.
 Rush full facts on practical TV training. I am not obligated. Salesman will not call.

Name Veterans; check here
 Address
 City Zone State
 BEGINNERS check here for information on Basic Television Course.


Square-Wave Shaper (Continued from page 63)

and on. This sine-wave input should be between seven and ten volts.


The video amplifier stage, V_2 , rests at zero bias. No grid coupling resistor is used. Leakage through the coupling condenser, C_2 , keeps the grid from drifting negative, and grid current in V_2 will prevent the grid from drifting positive. When this grid is driven by V_{1B} through the coupling condenser, C_2 , rectification occurs and the grid of V_2 is driven between zero bias and a large negative voltage. Only a fraction of this grid voltage is needed to drive V_2 from zero bias to cut-off. The screen of V_2 is lightly bypassed so that its plate responds more rapidly to the sudden rise and fall in the grid drive. This bypassing of the screen produces a little pip on the negative section of the square wave appearing at the plate of V_2 . No similar pip appears on the positive half since the positive segment results from the cut-off of both plate and screen current. The output of V_2 is coupled into the grid of V_3 by the ordinary method. This final stage, in addition to providing a low impedance output, eliminates the unwanted pip present on the negative segment of the output voltage from V_2 . Since V_3 is a self-biased cathode follower (the entire voltage across its cathode load resistor providing bias voltage) and since the drive to its grid is large, it is cut off by the negative section of its drive.

At very low frequencies the positive segment of the output waveform tends to drift down slightly instead of remaining flat. This decay is caused by the discharge of coupling condenser, C_3 , through the grid resistor, R_3 . To

Fig. 2. Waveforms at various key points.

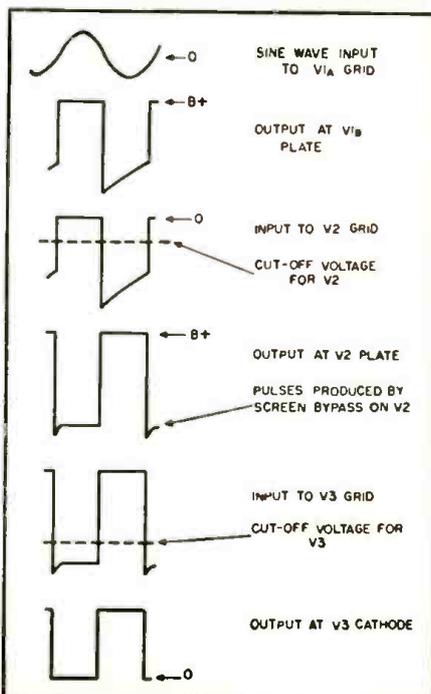

LOOKING FOR A NEW MODEL?

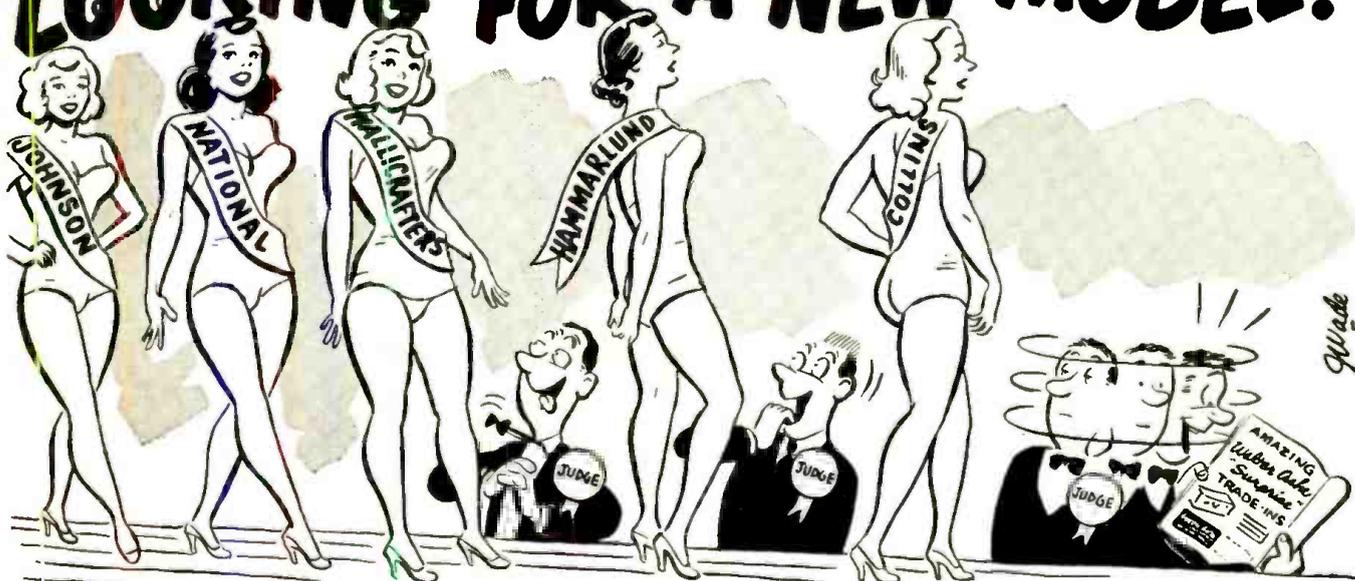

JOHNSON VIKING II Transmitter Kit.
Shpg. wt. 85 lbs. Net \$279.50
JOHNSON VIKING II Wired and Tested. Net \$337.50


If you're ready now for that new receiver, transmitter or test instrument—or simply "window shopping" at present—you'll do yourself a big, money-saving favor by obtaining Walter's "SURPRISE" Trade-In offer on your used test or communication equipment. Allowances were never more generous! Stocks of all the big-name brands are complete. Deliveries are prompt. Wire, write, phone or use the handy coupon today.



HAMMARLUND HQ-140-X
Less Speaker. Shpg. wt. 60 lbs.
Net \$264.50



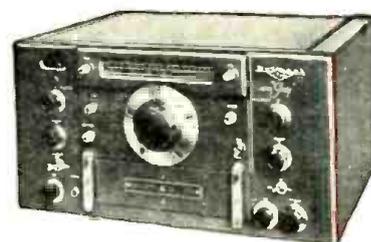COLLINS 75A-3 with 3 KC Mechanical Filter.
Less speaker.
Net \$530.00



NATIONAL HRO-60-T
Less Speaker. Shpg. wt. 90 lbs.
Net \$483.50



HALLCRAFTERS SX-71. Less Speaker. Shpg. wt. 51 lbs.
Net \$224.50

All prices f. o. b. St. Louis

Phone CHEstnut 1125

Walter Ashe
RADIO CO.
1125 PINE ST. • ST. LOUIS 1, MO.

FREE CATALOG!

R-9-53

WALTER ASHE RADIO COMPANY
1125 Pine Street, St. Louis 1, Missouri

Rush "Surprise" Trade-in Offer on my _____

for _____ (show make and model number of new equipment desired)

Send for latest Catalog.

Name _____

Address _____


City _____ Zone _____ State _____

Send
for
your
copy
today

KESTER



FASTER
ACTING

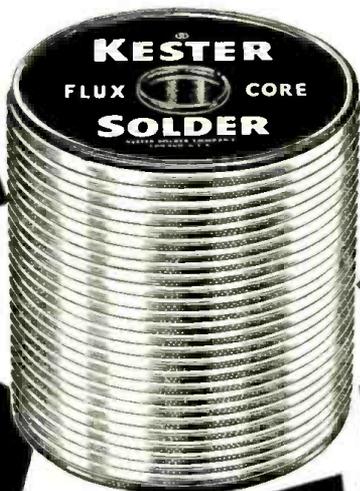

Since the most important single step in Radio-Television Servicing is soldering... it's just plain good sense to use the best — KESTER SOLDER... Key Name in Solder for More Than 50 Years.



THE
BEST



LONGER
LASTING

KESTER SOLDER COMPANY
4235, Wrightwood Avenue • Chicago 39, Illinois
Newark 5, New Jersey • Brantford, Canada

SOLDER

STAY ON THE AIR
WHEN POWER FAILS...with
an ONAN Electric Plant



Model 10EL, 10KW A.C.

When storms, floods, or fires interrupt electricity and force you off the air, you lose listeners and income. Guard against loss, assure vital public service during emergencies by installing an Onan Electric Plant. Onan Standby Electric plants serve many network and private stations. Automatic models to 35,000 watts.



PORTABLE ELECTRIC PLANTS FOR MOBILE RADIO USES
Supply A.C. power for broadcasting at scene of events. Light in weight. Can be carried by hand or in trunk of car. A.C. models: 400 to 3,000 watts.

Write for FREE Folder



D. W. ONAN & SONS INC.
7897 University Avenue
Minneapolis 14, Minnesota



THE *Case* WITH A
1,000 APPLICATIONS

This all-purpose case is ideal for housing meters, controls and switches of all types.

Made of heavy molded black plastic with matching phenolic panel.

Easy to drill and saw.

Available in two sizes;
5-1/4" x 6-7/8" x 2-5/16"
3-3/4" x 6-1/4" x 2"

Ask your Distributor for Waldom's Plastic Case.

WALDOM
ELECTRONICS INC.

911 Larrabee St., Chicago 10, Ill.

compensate for this droop the screen and plate loads for V_2 have been selected to be, in combination, smaller than the cathode load for V_2 . As a result the decrease in current when V_2 is cut off is not entirely offset by the simultaneous increase in current through V_2 when it starts to conduct. The net decrease in current causes the supply voltage to rise as the filter condenser, C_2 , takes on more charge. This increase in supply voltage bucks out most of the deterioration of the output waveform. This design expedient seems somewhat more economical than using all push-pull, direct-coupled circuits.

When constructing the unit the three variable resistors should be considered front panel controls. Potentiometer R_3 may be used to adjust the amplitude of the sine-wave input. The variable cathode resistor, R_4 , adjusts the relative length of the positive and negative pulses. Amplitude of the output signal is controlled by R_5 .

The addition of a switch and four resistors after R_5 will give step-wise attenuation with R_5 serving as a vernier. The inset in Fig. 1 shows such an arrangement in detail. This addition is well worthwhile, since it is thus much easier to control very low output levels. Furthermore, on the second and third switch positions (-20 db and -40 db) the output impedance is substantially independent of the setting of R_5 . Since these positions give maximum outputs of about 5 and 0.5 volts peak-to-peak, they will be the positions most often used. Having a constant output impedance is more than just a convenience when testing with pulse type signals. Unless the output impedance is constant the waveform shape will change as its amplitude is varied.

Should a different power transformer be used, R_5 should be adjusted to give a supply voltage (at the plate of V_1) of between 100 and 150 volts. About 20 milliamperes of current will be drawn with a 150 volt supply. Generally speaking the higher supply voltage will give a larger output signal but will require a larger sine-wave drive. The author's unit with a 160 volt supply requires 7 volts of drive.

Without a sine-wave generator this unit as it stands is not of much use. However, if you do have a sine-wave generator, the device here described will provide an excellent square wave over the entire frequency range of your sine-wave generator. —30—

LONG ISLAND HAMFEST

THE Federation of Long Island Radio Clubs will hold its 17th annual Hamfest and Dance on Friday evening, Oct. 9, at Lost Battalion Hall, 93-29 Queens Boulevard, Elmhurst, N. Y. The program will begin at 8.00 p.m. and will include activities for amateurs with special interests (DX, v.h.f., traffic, etc), entertainment and favors for the ladies. Tickets are available from J. N. Jablin, W2QPQ, 147-14 Charter Road, Jamaica 35, N. Y. —30—

Everybody's talking about the new Pyramid Imp!



See Us At
Western Electronic Show
Booth No. 1715

All over the country service-engineers are praising the newest and finest molded tubular paper capacitor—the Pyramid IMP!

here's why—



IMPS ARE REALLY RUGGED!
The tough thermo-setting plastic will take an astounding amount of abuse—yet IMPS will still look and perform like new!

IMPS WON'T FREEZE OR MELT! They'll operate faithfully in temperatures ranging from -40° C. to $+100^{\circ}$ C. (212° F.)—and that's the boiling point of water!



IMP LEADS CAN BEND AND BEND! Tinned leads that are really securely anchored — you'll be amazed at how much punishment they'll take without breaking!

IMPS ARE MOISTURE-PROOF! No moisture can get through the varnished plastic case, or even through the lead anchor-points.



IMPS are available in all popular ratings in 200, 400 and 600 volt ranges. See your local distributor.

If you haven't tried the new IMP, send for your free sample today—


PYRAMID ELECTRIC COMPANY
1445 HUDSON BOULEVARD • NORTH BERGEN, NEW JERSEY

This Month's Special

- ARC-3 PARTS
- T-206 Output XFMR. #55320.....\$2.75
- T-101 Mike XFMR. #55548.....1.50
- T-102 Driver XFMR. #55545.....1.75
- T-103 Audio XFMR. #55546.....1.75
- T-104 Modulation XFMR. #55547.....3.25
- T-105 Side-Tone XFMR. #55544.....1.85
- Driver Transformer for RT-13, T-202.....1.29
- Side-Tone Transformer for ART-13, T-203.....1.19
- Modulation Transformer, ES-691025 for BC 456.....1.19
- AN-104A Antennas for SCR 522......95
- BC 929 Indicators, p/o APN-2.....32.50
- BC 451 Trans. Control Box, p/o SCR 274N.....1.85
- C-30/ARC-5 Control Box.....1.65
- FT-225-A Mounting Racks.....1.65
- FT-227-A Shock Mount Racks.....1.65
- J-22/ARC-5 Junction Boxes.....1.75
- J-17/ARC-5 Junction Boxes.....2.75
- MD7/ARC-5 Modulators, all Tubes.....5.95
- MC 211 Right Angle Drives......21
- BC 433B Compass Revs., Used, Excellent.....32.50
- ART-13 Barometer Limit Switch.....8.75
- BC 306 Antenna Loading Unit for BC 375.....3.00
- RL-7 Interphone Amplifiers, Used, Excellent, Less Tubes.....3.75
- SA-4A APA-1 Motor Driven (28 VDC) Yagi-Antenna Switch.....24.50
- MT-36-C Ant. Loading Unit for TA-2J XMTR.....35.00
- A-62 Phantom Antenna for use with Mobile XMTRS. 20-38.9 MC 40 Watts.....3.95
- RT-19/ARC-4 Trans.Receivers, 24 VDC, covers Amateur 2-Meter Band, Complete with Tubes and Crystals.....39.50
- Radar Trainer, Type IS-C, Consists of 4 separate XMTRS. Operating 380-500 MC., 1-Pulse Gen. I—Power Supply, all Cables, 2 Inst. Books.....215.00
- Rubber Inserts, M-300 for HS-30 Headsets, 3.25/M.....
- BC 496A Dual Control Boxes (Receiver) for SCR 274N.....1.35
- T-30 Throat Microphones......69
- National XS-3 Double-Down Insulators, fits 2 3/4" Hole, All Hardware included......65
- IN-84 Double Cone Insulations.....\$12 for 1.00
- ARC-5 PLUGS

#5842.....35c	#7027.....45c
#5577.....35c	#7025.....45c
#PL 154.....70c	#PL 152.....65c
#PL 154A.....70c	#6418.....35c
- C-114 Loading Coils......85
- Overload Breaker: 500 MA @ 1000VDC Manual Reset, Heinemann AM 1610—5.....1.45
- Voice Coil & Diaphragm Assy. (Spares) for Beachmaster Sneaker Assy. Will handle 50 W. Audio......85

PLATE TRANSFORMERS

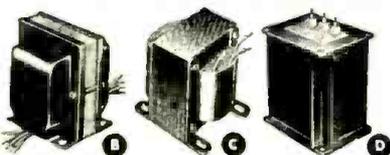

(All primaries are 110 v. 60 cps, single phase) DC ratings are approximate values obtained at output of a 2-section choke input filter using MV rect. tubes.

TYPE	VOLTS A.C. R.M.S.	D.C. VOLTS	D.C. MA.	FIG.	PRICE
PT 175	550-550	400	150	A	\$ 6.43
PT 157	660-660	500	250	B	8.42
	550-550	400			
PT 158	1080-1080	1000	125	B	10.00
	500-500	400	150	B	
PT 159	900-800	750	225	B	9.70
	800-800	600			
PT 167	1400-1400	1200	300	C	24.10
	1175-1175				
PT 168	2100-2100	1750	300	C	30.58
	1800-1800	1500			
PT 062	2900-2900	2500	300	D	47.04
	2385-2385	2000			

Simultaneous ratings

FILTER CHOKES

(Smoothing)

TYPE	IND. HYS.	CUR. MA.	DCR (OHMS)	TEST VOLTS	FIG.	PRICE
181	10	200	140	3000	A	\$4.70
182	10	250	125	3000	B	6.47
183	8	300	80	3000	B	6.76
Swinging input chokes						
187	4-16	150	120	3000	B	3.82
189	4-16	250	125	3000	B	6.47
190	3-14	300	80	3000	B	6.76

DYNAMOTORS

ALL BRAND NEW—ORIGINAL PACKING INPUT OUTPUT

TYPE	VOLTS	AMPS	VOLTS	AMPS	PRICE
PE 86	28	1.25	250	.070	\$4.25
DM 416	14	6.2	330	.170	6.75
DM 33A	28	7	540	.250	3.95
BD AR 93	28	3.25	375	.150	7.50
23350	27	1.75	285	.075	3.95
B-19 Pack	12	9.4	275	.110	8.95
			504	.050	
DA-3A*	28	10	300	.260	6.95
			150	.030	
			14.5	5.	
S053	30	14	250	.060	3.95
PE 73 CM**	18	19	1000	.350	**
337	14	8	425	.160	7.95

* Replacement for PE 94.
** Price sent on request.

ALL MERCHANDISE GUARANTEED. EVERY ITEM IS NEW UNLESS STATED OTHERWISE

Send M.O. or Check. Shipping Chgs. C.O.D.
COMMUNICATIONS EQUIPMENT CO.
131 Liberty St. Dept. N-9 New York City 7, N. Y.

Within the Industry

(Continued from page 26)

TRONICS, division of **CORN ELECTRIC COMPANY** in Stamford, Conn. . . **K. W. JOHNSON & CO., INC.** has been formed in Dayton, Ohio to engineer, design, test, and manufacture complete shock and vibration systems for industry and military purposes. K. W. Johnson, formerly chief engineer of the Mechanical Section of the Components and Systems Laboratory at Wright Field, heads the new firm which has headquarters at 1805 Webster Street in Dayton . . . **FEDERAL CHEMICALS CORPORATION**, 210 Wythe Avenue, Brooklyn, New York has been formed to supply the plastisol and organisol fields . . . **INTERNATIONAL RESISTANCE COMPANY** of Philadelphia has purchased **GORMAN MANUFACTURING CORPORATION** of Los Angeles. The California firm will continue to manufacture its line of encapsulated wire-wound resistors . . . **THE DAN J. CONNOR CO.** has incorporated as **DANCO CORPORATION**. The firm which represents many well-known electronics firms will continue to maintain its offices at 1346 Suburban Station Bldg., Philadelphia 3, Pa. . . A new electronics supply house which will operate under the name of "HEADQUARTERS" has been opened in Austin, Texas. Lyle Hammer, manager of the new firm, has been in the radio field for over thirty years.

LAWRENCE J. CERVONE has been promoted to the post of general sales manager of **Gates Radio Company** of Quincy, Illinois. He was formerly head of the company's New York office and has been with the firm since 1947. He was previously associated with both **Westinghouse** and **RCA**. He served in the Navy during World War II. He replaces the late Fred O. Grimwood who passed away in 1952. John M. Haerle, head of the defense contracts department for the company, will head the New York office which is located at 51 East 42nd Street.



T. R. MATHEWS has been named assistant general sales manager of the **Raytheon** Television and Radio Division at the Chicago headquarters. He was formerly eastern regional sales manager for the firm . . . **Sylvania Electric Products Inc.** has named **E. FINLEY CARTER** vice-president and technical director of the firm and **HOWARD L. RICHARDSON** as vice-president in charge of engineering operations . . . **HARRY SCHECTER** is the new general manager of **CBS-Columbia Distributors, Inc.**, the New York factory branch handling the distribution of the company's radio and television receivers in the Metropolitan area . . . **STANLEY**

L. ABRAMS, director of purchases for **Emerson Radio and Phonograph Corporation**, has been promoted to the post of director of the material division of the firm . . . **General Electric Company** has created three sub-departments within its tube department and has appointed general managers for each. **ROBERT O. BULLARD** will head the industrial and transmitting tube sub-department; the receiving tube sub-department will be handled by **L. BERKLEY DAVIS** while the cathode-ray sub-department will have **ROBERT E. LEE** as its manager . . . **PERCY L. SCHOENEN**, former president of **Olympic Radio & Television, Inc.** of Long Island City, passed away suddenly at his New York City home. He was 61. He retired as president of the firm in April of this year after having been associated with the company since its founding in 1935 . . . **J. HARVEY PICKET** is the new chief engineer for the Capacitor Division of **Aerovox Corporation**. He has been with the firm's Canadian subsidiary since 1935.

HARRY E. McCULLOUGH has been named general sales manager for television and radio of the **Crosley Division** of **Avco Manufacturing Corp.** He succeeds E. W. Gaughan who has been transferred to the staff of W. A. Bles.




Mr. McCullough has been associated with the firm since 1948, taking over as Cincinnati regional manager in early 1949. He has served successively as Cleveland regional manager and then as assistant to Mr. Bles, from which position he was promoted to product sales manager of radio and television and, later, sales manager for radio and television.

RTMA has announced that TV set production for the first five months of this year topped all previous January-May periods on record. During the first 21 weeks 3,309,757 TV sets and 6,102,711 radios were manufactured as against 1,957,083 and 4,469,432 TV and radio sets, respectively, produced during the same period in 1952.

DR. W. R. G. BAKER, vice-president and general manager of **General Electric Company's** Electronics Division, is the recipient of the 1953 Medal of Honor awarded annually by the Radio-Television Manufacturers Association to the person making the most outstanding contribution to the nation's radio-television-electronics industry.

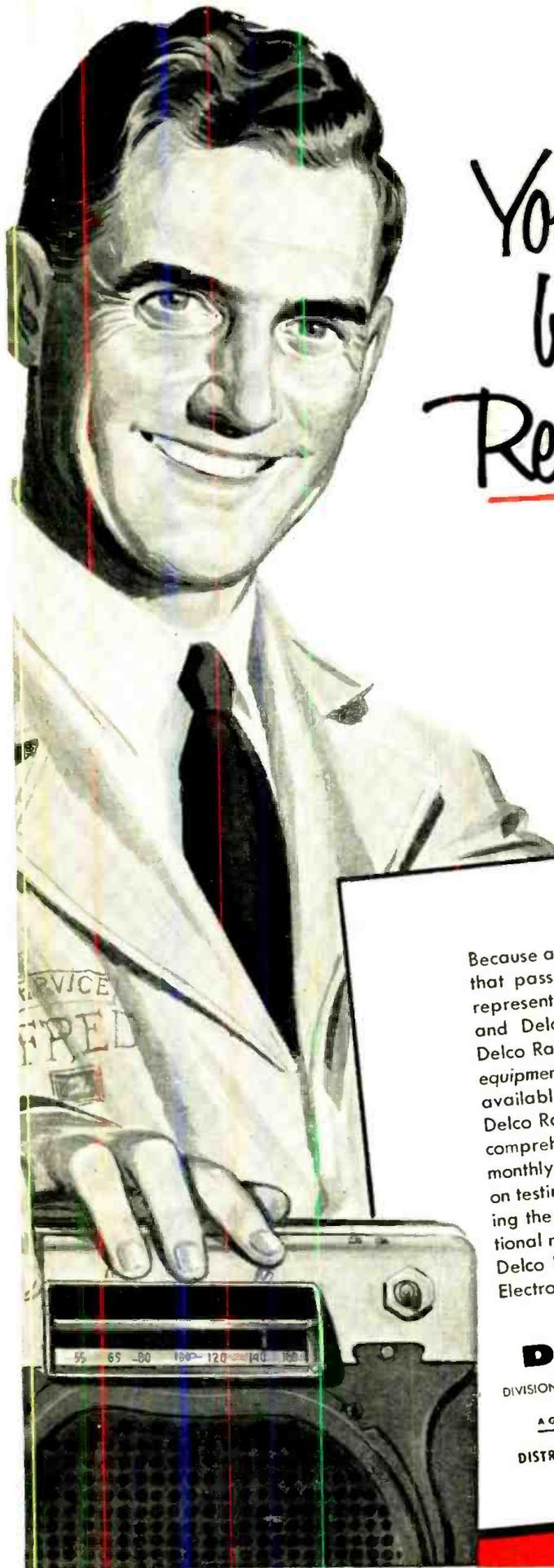A leader in the electronics industry for more than 30 years, Dr. Baker is chairman of the National Television Systems Committee which worked out the FCC-approved standards for the present black-and-white television system and is currently developing standards for a compatible color television system.



You can build a better Auto Radio Repair Business!

Because a majority of the radio-equipped cars and trucks that pass your door have Delco radios, their servicing represents a great business-building opportunity . . . and Delco Radio's service program offers real help! Delco Radio alone is the source for Delco Radio original equipment and universal replacement parts—readily available through United Motors Electronics Distributors. Delco Radio alone can supply you with its complete and comprehensive Service Manual and its "Testing Tips," a monthly bulletin giving you the latest factory information on testing and repairing Delco radios—including the Delco models equipped with the sensational new Signal-Seeking Tuner! To get on the Delco Radio team contact your United Motors Electronics Distributor today!

DELCO RADIO

DIVISION OF GENERAL MOTORS CORPORATION, KOKOMO, INDIANA

A GENERAL MOTORS PRODUCT   A UNITED MOTORS LINE

DISTRIBUTED BY ELECTRONICS WHOLESALEERS EVERYWHERE



REG. \$117.50 SUPREME TUBE TESTER—V.O.M. ON SALE AT McGEE FOR \$64.95


WITH ROLL CHART—7 INCH METER—BUILT IN BATTERY TESTER

Supreme Model 616 Tube Tester and Battery Tester. This is the same instrument as the model 600 except it has no volt-ohm and milliamp scale. However, it's a top quality tube tester, with illuminated roll chart and a complete dry battery tester. Made to sell for \$87.45 dealers' net. Our price of \$49.95 is good only as long as the limited supply lasts. Shipping weight 24 lbs. Sale price, \$49.95.

MODEL 616
REG. \$87.45
\$49.95

SUPREME MODEL 600 \$64.95

Supreme Model 600 tube tester, dry battery tester, volt ohm meter. All in one gray metal portable carrying case, 14" x 12" x 7 1/2". Large 7" meter, easy to read. Calibrated good-bad scale for tube testing with easy to read volt-ohm and milliamp scale. Most people can operate this meter without glasses, the printing is so large, as you would expect with a 7" meter. Illuminated roll chart. Push button tube checker operation. Easy to learn how to operate. Battery tester will check all dry batteries under proper load. Has 5 resistance ranges from .1 to 20 megohms, 6 AC-DC volt ranges from 0 to 2500 volts, 6 milliamp ranges from 1 to 1000 and 0 to 10 amps. This meter had a regular net price of \$117.50. Our special purchase makes this \$64.95 price possible. Think of it, the battery and VOM part is worth one-half our sale price. Stock No. 600 Supreme tube-set tester on sale for only \$64.95 at McGee. Only a limited supply is available. Shipping weight 24 lbs.

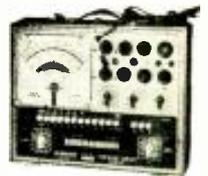

SUPREME MODEL 600


INDIVIDUALLY CARTONED ELECTRONIC RADIO & TV TUBES

McGee offers you a wide selection of good quality TV and Radio tube types, Individually cartoned. Our private brand. These are not set mfg's. cuts, but a carefully inspected private line of tubes with a full 6 months' guarantee. Types listed are in stock in good quantity at this time. Thousands sold. Order 25 tubes and take 10% off the listed prices.

02A	\$.09	6BA7	\$.69	6T8	\$.79	12K8GT	\$.59
1A7GT	\$.59	6BC5	\$.59	6U8	\$.79	12Q7GT	\$.59
1B3GT	\$.79	6BD6	\$.49	6V6GT	\$.59	12SF5GT	\$.69
1M5GT	\$.59	6BF5	\$.59	6W4GT	\$.59	12S17M	\$.59
1L4	\$.59	6BF6	\$.59	6X4	\$.39	12S17GT	\$.59
1R5	\$.59	6BG6G	1.29	6X5GT	\$.49	12SN7GT	\$.69
155	\$.59	6BM6	\$.59	7A7	\$.69	12SL7GT	\$.79
1T4	\$.59	6BJ6	\$.59	786	\$.69	1986GG	1.79
1U4	\$.59	6BK7	\$.99	7H7	\$.79	25B06GT	\$.99
1U5	\$.59	6BQ6GT	\$.99	7Y4	\$.69	25L6GT	\$.59
3Q4	\$.59	6C4	\$.39	12AL5	\$.59	32L7GT	\$.79
3CSGT	\$.69	6C6	\$.59	12ASGT	\$.69	35B5	\$.59
3S4	\$.59	6CD6G	1.49	12AT6	\$.49	35C5	\$.59
3V4	\$.59	6HG6T	\$.59	12AT7	\$.69	35W4	\$.59
5U4G	\$.49	6K7GT	\$.59	12AU6	\$.59	35L6GT	\$.59
6A4	\$.69	6L6G	1.09	12AU7	\$.69	43	\$.79
6AK5	\$.89	6S4	\$.59	12AV6	\$.59	47	\$.89
6AL5	\$.49	6SA7GT	\$.59	12AV7	\$.89	50B5	\$.59
6AQ5	\$.49	6SH7GT	\$.59	12AX4GT	\$.59	50C5	\$.59
6AT6	\$.49	6SF5GT	\$.59	12AX7	\$.69	50L6GT	\$.59
6AU6	\$.69	6SK7GT	\$.39	12BA6	\$.59	70L7GT	\$.99
6AV6	\$.49	6SL7GT	\$.69	12BF6	\$.59	11Z73	\$.39
6AX4GT	\$.69	6SN7GT	\$.69	12BD6	\$.59		
6BA	\$.49	6SU7GT	\$.69	12BF6	\$.79		

ESPEY 12-TUBE FM-AM CHASSIS, \$59.95

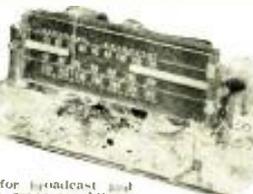- ★ BUILT-IN PRE-AMP FOR G. E. VARIABLE RELUCTANCE PICK-UP
- ★ WIDE RANGE AUDIO
- ★ WHY NOT ORDER WITH A COAXIAL SPEAKER AND A RECORD CHANGER? SEE OUR SPECIAL OFFERING



McGee's new 1953 model 12-tube FM-AM chassis. Latest design with phono inputs for all types of record players, crystal or G.E. variable reluctance. Receiver's standard broadcast 550 to 1700 kc and FM—10 to 108 mc. Wide range audio response push-pull 6V6 output and two-beat tone control. Loop antenna for broadcast band. 300 ohm line type FM antenna may be standard in chassis. All-tube type lighted slide rule dial. Chassis size, 13 1/2" x 9" high and 9" deep. Complete with tubes, 6BA6, 6BA7, 12AT7, 6SL7, 6AL5, 6SQ7, 6SU7, 12AT7, 2-6V6GT and 533GT rectifier. Shipping weight 29 lbs. Stock No. 7C-X Espey 12-tube FM-AM chassis. Sale price, \$59.95, less speaker. Output matches voice coil of our 12" or 15" coaxial speakers.

ESPEY DEAL (1), \$99.95

Espey 7C chassis complete with 12" coaxial PM speaker CU-14Y and VM-950 G.E. 3-speed changer equipped with a G.E. turnabout variable reluctance cartridge. A better home music system than ordinarily available. Espey Deal #1. Sale price \$99.95. With 15" coaxial PM speaker P-13CS instead of CU-14Y, \$10.00 extra.

ESPEY DEAL (2), \$118.95

Espey 7C chassis complete with 12" coaxial PM speaker CU-14Y and the Emch-Garrard 3-speed changer equipped with a G.E. variable reluctance turnabout cartridge. Our best home music system. Espey Deal #2. Sale price \$118.95. With 15" coaxial PM speaker P-13CS instead of CU-14Y, \$10.00 extra.

AMERICA'S FINEST 28 WATT—50 WATT AND 10 WATT P.A. VALUES

\$69.95 BUYS A 28 WATT \$150.00 LIST VALUE PORTABLE P.A. SYSTEM

(Illustration B)

**3-SPEED PHONO TOP—TWO 12-INCH SPEAKERS
7-TUBES PUSH PULL 6L6'S HEAVY LEATHERETTE COVERED PLYWOOD PORTABLE CASES
CRYSTAL MIKE \$8.95 EXTRA**

STOCK NO. AP-28X. Portable 28 watt public address system. You get a 7-tube heavy duty push-pull 6L6 amplifier with inputs for 2 mikes either crystal or dynamic with separate mixing volume controls. One phono input. Fully variable tone control high fidelity, wide range frequency response. The heavy duty output transformer has taps for 4, 8, 16, 125, 250 and 500 ohm speaker connections. Two heavy duty 12 inch alnico V P.M. speakers, each with 25 feet of speaker cable. Each speaker is mounted in separate carrying cases. Each case has a snap on back and is large enough to give good speaker baffling. Each case is 21 x 14 x 13 inches. One is used to carry the amplifier. A 3-speed phono motor and pick-up is mounted in the top of the amplifier to play 33 1/3, 45 and 78 RPM records.

This portable PA system will put out 20 watts all day long and 25 to 30 watts peak audio. McGee offers you this \$150.00 list portable PA system at a terrific saving.

STOCK NO. AP-28X complete portable PA system with 3-speed phono and 2 mikes \$150.00 list value. Stock No. AP-10X. 10-watt portable P.A. system Electro Voice model 910 \$28.50 list crystal mike with 20 feet of cable and desk stand \$8.95 extra.


Floor type mike stand instead of desk stand \$4.95 extra.

10-WATT PORTABLE P.A. ON SALE \$42.95

3-SPEED PHONO TOP—10" ALNICO PM SPEAKER

(Illustration C)

5-tube portable 10-watt (14-watt peak) public address system. (Push-pull 7C5) U. L. approved amplifier with wide range response. Inputs for microphone and phono, with separate mixing type volume controls. Tone control. 10" Alnico V PM speaker is housed in a leatherette case 21"x13"x13" which holds the amplifier for carrying. 3-speed turntable and pickup arm to play all records 33 1/3, 45 and 78 RPM is mounted in the top of the amplifier. List value \$40.00. Stock No. AP-10X. 10-watt portable P.A. system has only one case and one 10" speaker, less microphone. Sale price, \$42.95. Shipping weight 41 lbs. Shipped via Express or Truck only. Crystal microphone with non-removable desk stand, \$3.95 extra when ordered with the AP-10X portable P.A. system.

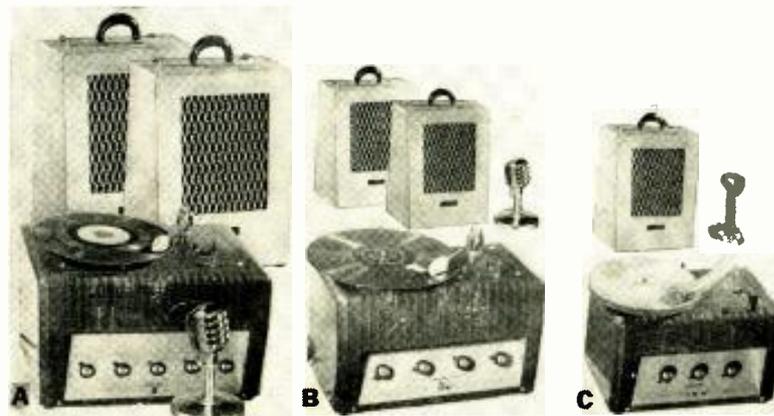

50-WATT PORTABLE P.A. ON SALE \$99.95

3-SPEED PHONO TOP—TWO 12" SPEAKERS

(Illustration A)

10-tube portable 50-watt public address system. 4-6V6 push-pull parallel output tubes. Inputs for 2 microphones, either crystal or dynamic, with separate mixing volume controls. Twin bass and treble tone controls. High fidelity wide range output transformer with taps at 4, 8, 16, 125, 250 and 500 ohms. Complete with 2 super heavy duty 12" PM speakers and 25 ft. cables mounted in separate leatherette-covered carrying cases, 21"x21"x13". The amplifier fits in one of the cases for carrying. This amplifier will put out 40 watts all day long and 50 to 60 watts peak with ease. 3-speed turntable and pickup arm to play all records 33 1/3, 45 and 78 RPM is mounted in the top of the amplifier. Stock No. AP-50X. 50 watt portable P.A. system similar to the 28-watt model pictured above, less microphone. Sale price, \$99.95. Shipping weight, 100 lbs. Shipped via Express or Truck only. Regular \$45.00 list. Electro-Voice 610 dynamic microphone with 20 ft. cable and desk stand, \$11.95 extra. For floor stand instead of desk stand, add \$4.95.

McGEE RADIO COMPANY

Prices F.O.B. K.C. Send 25% Deposit with Order, Balance Sent C.O.D. With Parcel Post Orders, Include Postage

TELEPHONE VICTOR 9045. WRITE FOR FLYER
1422 GRAND AVE., KANSAS CITY, MISSOURI

McGEE OFFERS YOU TERRIFIC VALUES IN T. V. BOOSTERS—AMP'S AND KITS

STANDARD COIL SUPER CASCADE TUNER \$19.95 UHF STRIPS \$7.50 EXTRA

The Cascade Circuit of the Standard Tuner offers a new development of this famous TV front end assembly which affords a 2-to-1 improvement in gain and a 35% to 50% reduction of noise over the Pentode tuner. Other advances include easy conversion to UHF reception by interchange of channel inductors; increased sensitivity for TV sets in fringe areas; elimination of booster use; and a high profit item for the serviceman as a replacement unit. Standard TV-2000 TV tuner, comp., with tubes 6BK7 or 6BQ7 and a G3B. Shaft length 3 1/4". Secord UHF (specify channel) strips supplied in pairs for above cascade tuner, \$7.50 per set.



FRINGE AREA TV RECEPTION IS BETTER WITH OUR McMURDO SILVER TV BOOSTER \$10.95—TWO FOR \$20.00



Read the article on pages 32 and 53 of the December "Radio & TV News." You will see how a booster like McMurdo Silver Super Somic was used for fringe area TV reception. We can't guarantee this unusual reception, but we will guarantee this booster to be a sensational value. Continuously variable inductance type tuner from channel 2 including the FM band through channel 13. Self-powered for 110 volts AC operation, incorporates a 6BQ tube. Input for 300 ohm TV line and 300 ohm output to TV set. Single knob tuning. Attractive plastic case. McMurdo Silver Super Somic TV-FM booster. Stock No. GB-6H, shipping weight 5 lbs. Sale price, \$10.95 each or two for \$20.00.

14-Inch Conversion Kit \$25.95 WITH G.E. TUBE

14-inch conversion kit: You get a 14-inch black face, 1 year guarantee G.E. 14" picture tube, a 70" deflection yoke with matching 14,000 volt flyback and a 1 1/2" plexiglas gold trim safety mask, plus conversion instructions. Stock No. 14C-01, Sale price, \$25.95.

17-INCH CONVERSION KIT \$25.95

17-inch conversion kit with a 17BP4A, 17" rectangular blackface electro-magnetic focus picture tube with 8 months' guarantee, plus a matched 70" cosine yoke, a G.E. built 14,000 volt flyback and a 1 1/2" rectangular gold trimmed plexiglas mask and safety shield. Suggested diagram furnished. Shipping weight, 30 lbs. via Express or Truck only. Stock No. 17-AXL, 17" conversion kit. Sale price, \$25.95. Kit Price with GE or Raytheon 1 year guarantee picture tube, \$5.00 extra.

20-Inch Conversion Kit \$29.95

20" conversion kit includes a 6-month guaranteed 20HP4 20" rectangular blackface picture tube, plus a 14,000 volt G.E. built high voltage cosine yoke, plus a matched 70" cosine yoke, plus a 20" rectangular gold trimmed plexiglas mask and safety shield. The picture tube is the latest electro-static focus type that requires no focus coil. Shipped via express or truck only. Ship. weight, 40 lbs. Stock No. 20-TP, net price, \$29.95. Price with Raytheon or GE 1 year guarantee picture tube, \$10.00 extra.

SPEAKER AND BAFFLE SALE 8" SPEAKER AND BAFFLE \$4.95

Stock No. 818. Tan leatherette covered, plywood slant type wall baffle, plus an 8" Oxford, 2 1/2" dia. Alnico V magnet PM speaker. A terrific McGee value for only \$4.95 each, or \$4.70 each in lots of 3 or more.

10" SPEAKER AND BAFFLE \$6.50

Stock No. CA-10. Tan leatherette covered plywood slant type wall baffle, plus 10" Alnico V PM speaker. Only a few hundred to sell at \$6.50 each, or \$6.25 each in lots of 3 or more.

12" SPEAKER AND BAFFLE \$7.95

Stock No. CA-12. Tan leatherette covered plywood slant type wall baffle, plus a 12" Alnico V magnet PM speaker. A terrific McGee value for only \$7.95 each, or \$7.50 each in lots of 3 or more.

3 STATION INTERCOM MASTER \$16.95 SUB STATION \$3.95



3-station intercom master housed in chrome plated metal cabinet 7 1/2" x 6" x 5" sloping front. Full 3-tube amplifier for 110 volt AC-DC operation. Press-to-talk switch is on top of the cabinet and volume control with on-off switch and station selector switch are on either side. May be used with from one to 3 sub-stations. See matching cabinet chrome plated sub-station No. PM-A5. Master is quiet at all times except when press-to-talk switch is pressed at the master or call-back switch at the sub. Uses 3-wire intercom cable. 3-station intercom master MPM-A3, shipping weight 10 lbs. Sale price, \$16.95 each, sub-station chrome plated intercom cable, 100 ft. for \$1.95, 500 ft. for \$8.95.

1000 INTERCOM SUB-STATIONS TO SELL AT \$3.95 EACH




Chrome plated, with call back switch for a 3-wire intercom master. Size 7 1/2" x 6" x 5" sloping front. 5" Alnico V PM speaker. Intercom dealers buy at less than present production cost. Limited quantity. Stock No. PM-A5, ship. weight 8 lbs. Sale price, \$3.95 each or 3 for \$10.00. Stretched 3-wire plastic intercom cable, 100 ft. \$1.95, 500 ft. for \$8.95. Brown leatherette covered chrome plated sub-station with call back switch for use with 3-wire intercom masters. 5" square and 2 1/2" deep. Has new plastic grill cloth. Alnico V PM speaker. A true McGee value. Stock No. NE-5, ship. weight, 1 1/2 lbs. Sale price \$3.95 each or 3 for \$10.00. 3-wire plastic intercom cable, 100 ft. for \$1.95, 500 ft. for \$8.95.

3-TUBE SARKES-TARZIAN T.V. TUNER \$9.95

This popular Sarkes-Tarzian Type 3 tuner is widely used, 13 channel rotary type switch with individually tuned coils. Price is complete with diagram and three tubes: 6C4 osc., 6BH6 R.F. and 6AR5 mixer. Regular factory cost is twice our price. Each tuner is wired ready to hook up to a video and sound IF strip. May be used with either inter-carrier or separate sound IF circuits. Has built-in converter coil, built in fine frequency control. Sarkes-Tarzian TV tuner, with 3 tubes. Net price, \$9.95 each. Shaft length, 2 1/4".

50-WATT BOOSTER AMPLIFIER

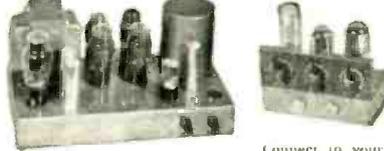

50-WATT BOOSTER AMP, \$39.95

2-Mike Pre-Amp \$12.95 Extra. Not a Kit, but a Manufactured Amp.

50-watt booster amplifier. A sensitive 50 watt booster amplifier with push-pull parallel 816 output tubes. Connect to your present amplifier as a booster or use with the PR-2X Pre-amp to add the use of 2 mikes and gives 50 watts of audio. The booster has a 6 lb. bottled case high fidelity output transformer, matches speaker with 4-8-16 ohm voice coil, also 60 ohm and 250 ohm line. Booster has a 225 mill power supply with 324 rectifier. The tone is free floatable. The two variable controls are for master volume control and bass boost tone control. Size 8 x 6 1/2 x 14 1/2. Stock No. PA-50N. Shipping weight 26 lbs. Sale price \$39.95 ea.

2-MIKE PRE-AMP

Pre-amplifier plugs in directly to the PA-50N booster amplifier. It enables use of 2 Crystal or Dynamic Mikes plus one level input. Furnished with 4 foot cables and plugs for remote control of the 55 watt Booster Amplifier. Small chassis size 5 x 3 1/4 x 4". Stock No. PR-2X, with tubes 7F7 and 7N7. Net price \$12.95 ea.

McGEE'S \$62.50 LIST 15" COAXIAL SPEAKER, \$23.95



15" COAXIAL SPEAKER, \$23.95

McGee offers the new 1953 Model 15" coaxial PM speaker. Quality you would put in your finest sets if you were a manufacturer. 12 tweeter has 6.8 ohm Alnico V magnet, tweeter is coaxially suspended and has a metal diffuser. High pass filter is under the pot cover. Only two wires to connect your radio or audio amplifier, 8 ohm with 18 watt peak and 10 watt average. Shipping weight 8 lbs. Response from 30 to 17,500 cps. Stock No. CU-14Y. Sale price \$23.95 each; 2 for \$25.00.

12" JENSEN PM, \$15.95

Another McGee Secord Jensen Concert 12", 14 1/2" dia. Alnico V magnet PM speaker. 8 ohm voice coil. Will take 25 watt audio. You save dollars on this speaker. Just 100 to sell. Shipping weight 8 lbs. Stock No. P-12P. Sale price \$15.95; 2 for \$30.00.

G.I. 3-SPEED CHANGER WITH G.E. \$22.95

VARIABLE RELUCTANCE TURN-ABOUT CARTRIDGE

Another tremendous McGee Secord Brand new General Instrument 3-speed automatic record changers. Complete with RPX-050 G.E. variable reluctance cartridge with turn-about stylus. Plays all 3 3 1/2, 4 1/2 or 5 inch records. Has eject button. Repeats last record. Base size, 12" x 12 1/2". Shipping weight 14 lbs. Stock No. 700-6E. Secord price, \$22.95. G.I. 3-speed changer same as above, but with Webster flip-over twin needle cartridge. Stock No. 51-700. Sale price, \$21.95 each.

COMPLETE RADIO, TELEVISION AND AMPLIFIER KITS AT McGEE

3-WAY PORTABLE KIT \$15.95

New 1952 Model 3-way personal portable radio kit. Operates on 110 volts AC-DC or 67 1/2 B plus 1 1/2 volt self-contained batteries. Leatherette covered case size, 5 1/2" x 3 1/2" x 2 1/2". Receives broadcast 250 to 1450 KC. conventional 2-gang superhet circuit with 75 KC iron core I.F. Incorporates the new super gain stick loop antenna. All fitted chassis. Lab. approved circuit—matched parts. Price includes all parts, tubes, diagram, Alnico V PM speaker. A factory quality kit. Stock No. PN-4T, shipping weight 7 lbs. The complete kit, less batteries, \$15.95, 67 1/2V. B. \$15.99, 1 1/2V. 3cc extra.

8-Tube Hi-Fi Amplifier Kit \$29.95

A complete kit, including tubes 6X4, 6AR5, 2-12AX7, 2-triode plus rectifier, 6A5, 6AV6 and photos. Inputs for radio tuner and any kind of pressed at the sub. Uses 3-wire intercom cable. 3-station intercom master MPM-A3, shipping weight 10 lbs. Sale price, \$16.95 each, sub-station chrome plated intercom cable, 100 ft. for \$1.95, 500 ft. for \$8.95.

10-TUBE RADIO KIT \$29.95

10 tube broadcast radio chassis—12 tubes, complete with tubes: 6AR5, 6AV6, 2-6X4, 3-6SN7, 1-6BE6, 2-6V6 plus 5Y3 pre-equalizer. 4 1/2" x 4 1/2" x 4 1/2" chassis size. 12" x 10" x 10" rule dial. Chassis size, 12 1/2" x 10" x 10" high. Features push-pull 6V0 high fidelity output, output matches 3 to 8 ohm intercom cable speakers. Inputs for G.E. variable reluctance or crystal phono pickup and crystal or heavy duty power transformer. Model HK-10 kit less speaker, shipping weight 18 lbs. Net \$29.95.

6-TUBE 2-BAND KIT \$14.95

Popular with schools and colleges for training. 6 tube AC-DC band radio kit with plastic cabinet. Repeats automatically and 6 to 18 mc. coverage. Full 2 gang superhet with 5" speaker and a slide rule dial. A complete kit with tubes: 12SK7, 12K8, 12SK7, 12SQ7, 50L8 and 35Z5, diagram and instructions. Factory quality. Cabinet size 13" x 6 1/2" x 6 1/2". Shipping weight, 12 lbs. Model ME6-2. Net \$14.95.

Build Your Own \$7.95 Phono-Mike Broadcaster

Kit Model DE-6R. With this simple kit, you can build a 3-tube phono oscillator that also has a mike input. Will broadcast over any radio within your home, (about 75 feet) from 1000 to 1500 kc. Inputs for crystal mike or crystal phono pickup. Ejector button. Volume from mike to record. Ideal for a home P.A. system, baby listener and home entertainment. A complete kit with 3 tubes, 2 tubes. Kit Model DE-6R. Net price, \$7.95. I.E.-61WT, wired and tested. Net price, \$9.95. Crystal mike and desk stand, \$4.95 extra. Concentrated microphone unit, only 1 1/2" diameter and 1 1/2" thick. Specify hidden price when ordering. Stock No. T-001. Net, \$3.95 extra.

WRITE FOR McGEE'S 1953 CATALOGUE

56 PAGES OF BARGAINS—EVERYTHING FOR THE TELEVISION AND RADIO SERVICE MAN. UP TO DATE UHF TELEVISION MATERIAL. WRITE FOR YOUR COPY TODAY.

17, 20" T.V. Kit \$59.95 Less Tubes

A complete kit of parts to build an AC transformer operated television chassis for use with a 17" or 20" rectangular picture tube. The 17" channel Sarkes-Tarzian tuner is ready wired, as is the 4 tube video IF strip. Circuit is of the conventional design. Do not buy this unless you understand television. It is difficult to wire. We furnish schematic. Kit Model WH-20, ship. wt. 40 lbs. less all tubes. Net \$59.95. Cascade tuner \$10.00 extra, 12" speaker \$2.95 extra. Kit of 10 tubes, less picture tube \$10.95. 17" 17BR4A \$17.95, 20HP4 \$25.00.

AC POWERED BROADCAST TUNER KIT \$12.95

A self-powered, 3-tube superhet tuner kit with R.F. stage. This complete kit is furnished with a transformer, photos and tubes. 6BA6 R.F., 6BE6 oscillator R.F., 6BA6 I.F. detector, 5A5 diode, AVC, plus rectifier. Connect to any audio amplifier. Ideal for use with our S-2020 or 7x5 amplifier kits. Chassis size, 9 1/2" x 4 1/2" x 4 1/2". Shipping weight, 7 lbs. Broadcast tuner kit Model BT-38X. Net price, \$12.95.

McGEE RADIO COMPANY

Prices F.O.B. K.C. Send 25% Deposit with Order, Balance Sent C.O.D. With Parcel Post Orders, Include Postage. TELEPHONE VICTOR 9045. WRITE FOR FLYER 1422 GRAND AVE., KANSAS CITY, MISSOURI

SPECIAL OF THE MONTH

HIGH VOLTAGE MICA CONDENSERS
 .001 Mfd. 4000 V.D.C., 6 amps @ \$295
 1000 Kc. Ea.

NON-INDUCTIVE RESISTORS **59¢**
 Ohmite, 250 Ohm, 100 Watt.
 Special. 5 for \$2.50

SOLA CONSTANT VOLT. TRANSFORMER
 Pri. 95-125 volts, 60 cy. Sec. Regulated
 at 115 volts. 30 VA. \$ 9.95
 60 VA. \$14.95 120 VA. \$22.50

PLATE TRANSFORMER
 1000-0-1000 Volts @ 400 mills, 115 v., 60 cy.
 pri. Removed from equipment but guaranteed
 perfect. ea. \$8.95

6 HY, 400 MA FILTER CHOKE
 Made by Acme. Only 30 Ohms DC Res. \$250
 3000 Volt INS. ALL BRAND NEW.

0-150 MICROAMP METER
 G.E., 2" Rush Bakelite case, Scale 0-150
 Microamps. BRAND NEW. A Terrific Value. \$4.95

FILAMENT TRANSFORMER
 10 Volts center tapped @ 6 amps, 115
 V., 60 cy. Primary. ONLY \$295 Ea.

MOBILE DYNAMOTORS
 MADE BY PIONEER AND EIGOR
 6 Volts Input, 425 Volts at 375
 MA Output. 6 3/4" Long. 4" Di-
 ameter. Weight 10 lbs. List
 Price Approx. \$70.00. \$2495
 BRAND NEW. ONLY.

CARTER SUPER DYNAMOTOR
 12 Volts Input, 400 V. Output @ 200 MA Con-
 tinuous or 375 MA Intermittent duty. Model B420.
 Designed for Police, Aircraft and Ma-
 rine Use. Small, rugged and effi-
 cient. \$2495 Each
 BRAND NEW. ONLY.

CONTINENTAL MOBILE DYNAMOTORS
 11.5 Volts input, output 270 V. @ \$8.95 Each
 70 mills
 11 Volts input, output 475 V. @ \$19.95 Each
 210 mills

12 VOLT D.C. RELAY
 DPDT \$1.75 Each

G. E. RELAY CONTROL
 (Ideal for Model Controls, Etc.)
 Contains a sigma midget 8,000 ohm. relay (strips
 at less than 2 MA), high impedance choke, bi-
 metal strip, neon pilot and many useful parts.
 The sensitive relay alone is worth much more
 than the total \$1.25 Each 10 for \$9.90

Panel Meters
 NEW GOVT SURPLUS
 STANDARD BRANDS
 2" METERS
 DB meter—10 to
 +20 \$3.49
 0-500 ma DC 3.49
 3" METERS
 0-50 Microamps \$8.95
 0-100 Microamps 7.95
 0-200 Microamps 6.95
 0-400 Microamps 5.95
 0-500 Microamps 5.95
 0-10 Milliamm 4.50
 0-150 Milliamm 4.50
 0-200 Milliamm 4.50
 0-300 Milliamm 4.50
 0-500 Milliamm 4.50
 0-1000 Milliamm 4.50
 0-50 Volt DC (1 MA) 4.95
 0-150 V. DC (1 MA) 4.95
 0-1.5 Volts AC 4.95
 0-3 Volts AC 4.95
 0-150 Volts AC 7.50
 4" METERS
 0-200 Microamps \$8.95

WIRE WOUND RESISTORS
 Stock too long to list. We can supply most sizes,
 so order what you need.
 5 Watts, From 1 Ohm to 40K Ohms. Ea. \$.09
 10 Watts, From 1 Ohm to 70K Ohms. Ea. .15
 20 Watts, From 4 Ohms to 50K Ohms. Ea. .20
 25 Watts, From 1 Ohm to 100K Ohms. Ea. .30
 50 Watts, From 5 Ohms to 100K Ohms. Ea. .40
 100 Watts, From 50 Ohms to 100K Ohms. Ea. .50
 ADJUSTABLE SLIDER, WIRE WOUND
 10 Watts from 1 Ohm to 10K \$.25
 25 Watts from 20 Ohms to 2.5K35

VACUUM CONDENSERS
 50 mmf. 5 KV. General Electric. \$ 5.95
 50 mmf. 20 KV. Jennings 7.95
 100 mmf. 20 KV. Jennings 12.95
 150 mmf. 20 KV. Jennings 16.95

1 MEGOHM, 1% W.W. PRECISION RESISTORS,
 SMALLCROSS. 97c ea. 10 for \$8.95

BAKELITE CASED MICAS
 MFD VDC Price MFD VDC Price MFD VDC Price
 .001 600 \$.18 .01 1 KV \$.45 .02 2 KV \$.90
 .002 600 .24 .002 1200 .35 .005 2500 .55
 .01 600 .26 .024 1500 .65 .002 2500 .45
 .02 600 .26 .033 1500 .75 .004 2500 .50

Min. Order \$3.00—25% with Order

PEAK ELECTRONICS CO.
 66 West Broadway, New York 7, N. Y.
 Phone WOrth 2-5439

Speech Filters (Continued from page 74)

tiny ceramic condensers which are also inexpensive and readily available, a complete low-pass filter section can be made which takes up a negligible amount of space inside a receiver. The photograph shows how small the filter and its terminating resistances actually are; a man's fountain pen is of telegraph-pole size by comparison.

To obtain the sharpest possible cut-off, an *m*-derived filter section was used. While this type of filter can give a much sharper cut-off than could be obtained with a more familiar design, it is done at the expense of a different type of attenuation curve as the frequency is raised. Unlike the more familiar circuits, an *m*-derived section does not have an ever-increasing attenuation as the frequency is raised, but instead has a point just above the cut-off frequency at which the attenuation is extremely high, and then has somewhat less attenuation as the frequency is raised still further. In some applications, this "leak-through" of the extremely high frequencies could be very undesirable. In this case, however, there should be no difficulties, because of the frequencies involved. With an *m*-derived filter cutting off at 3000 cycles, the response of all but the highest-fidelity loudspeakers will have dropped off before the attenuation of the filter starts to deteriorate at the high frequencies.

The final filter circuit is shown in Fig. 1, as it appears in a conventional receiver, complete with the 82,000 ohm terminating resistance at the input and output of the filter. The load or output termination is shown in the diagram at the grid of the output stage. The source impedance is furnished by the plate resistance of the 6SQ7, the 100,000 ohm load resistance in series with the filter, which combined make up an effective 82,000-ohm source impedance.

The high-frequency end of the response curve shown in Fig. 2 represents the measured response of this filter section in the circuit shown. It is evident that the high-frequency cut-off is extremely sharp, much sharper than could ever be obtained with a conventional resistance-capacitance tone control circuit. Its effectiveness is indicated by the speed with which a c.w. note drops out completely as its audio tone passes the upper limits of the filter. In addition, the tone control circuit of the receiver was found to have become completely worthless, for the filter does the job so much more effectively that advancing the control to cut down any remaining high-frequency interference will instead reduce the intelligibility of the speech before any useful noise reduction is obtained.

In this design, the low frequencies

Reliance Specials

SOUND POWER PHONES
 Sound Powered Handset
 TS-10 TYPE
 Uses no batteries or external power source. Ideal for TV installation work, farms, construction projects, connecting outbuildings, extensions, etc., includes 3 ft. cord. \$18.95
 Pair

SOUND POWERED HEAD & CHEST SET
 Navy type M head and chest set. Brand new. For work requiring free use of hands. Heavy duty—consists of headset with 3 phones and chest mike. Includes 20 ft. rubber cord. Each \$14.88

COAXIAL CABLE CONNECTORS

Full line of JAN approved coaxial connectors in stock.



RR-1AC	\$0.42	PL-271	\$1.10	JG-88/U	\$0.90
RR-1AP	.30	PL-275	2.10	UG-89/U	1.10
RR-1B	.35	UG-218/U	1.45	UG-102/U	.80
RR-1F	1.10	UG-13/U	1.70	UG-103/U	1.40
RR-1H	.12	UG-148/U	1.05	UG-104/U	1.50
RR-1HP	.22	UG-208/U	1.60	UG-105/U	1.15
RR-1J	.73	UG-21/U	1.00	UG-107B/U	2.75
RR-1R	.40	UG-218/U	1.05	UG-146/U	2.00
RR-1RTV	.65	UG-21/U	1.75	UG-167/U	3.75
RR-1SP	.45	UG-21/U	1.30	UG-175/U	.12
RR-1SPN	.50	UG-22/U	1.30	UG-174/U	.12
RR-2AP	1.30	UG-22A/U	1.60	UG-185/U	.95
RR-2B	1.20	UG-22B/U	1.20	UG-196/U	1.65
RR-2AP	1.65	UG-22B/U	1.50	UG-200/U	.65
RR-22P	1.95	UG-22B/U	1.20	UG-224/U	1.15
RR-22P	2.10	UG-24/U	1.30	UG-251/U	1.95
RR-22R	1.40	UG-27/U	1.25	UG-260/U	.85
RR-22SP	.80	UG-27A/U	2.95	UG-261/U	1.10
RR-22T	1.95	UG-27B/U	2.95	UG-273/U	1.45
RR-148	1.20	UG-27C/U	2.95	UG-274/U	2.30
RR-185	.12	UG-30/U	2.30	UG-281/U	.95
CW-123A	.45	UG-37B/U	1.85	UG-308/U	2.65
M-358	1.20	UG-58/U	1.10	UG-314/U	1.95
M-359	.30	UG-58A/U	.90	UG-318/U	1.25
M-359A	.65	UG-59A/U	1.90	UG-325/U	1.35
PL-258	.45	UG-83/U	1.75	UG-325/U	1.35
PL-259	.45	UG-87/U	1.40		

NEW COAXIAL CABLES JAN APPROVED

RG 8/U	Price Per Ft.	RG 58/U	Price Per Ft.
RG 11/U12 1/2c	RG 59/U7 1/2c
RG 22/U19c	RG 62/U9c

Deduct 20% 500 ft. or more of a type.

RG-8/U Unmarked 100 ft. coil.....\$5.95

SPECIAL FILAMENT TRANSFORMER

SEC. 3V 190A. PRI. 105-125 VAC. 60 cy. 1 Phase .07 KVA, 35 KV. RMS insulation test. 7"x10"x12"; weight 80 lbs. Ideal for use as arc welder. ONLY \$29.50

HARDWARE ASSORTMENT—Five Pounds
 Mixed nuts, bolts, washers, rivets, solder lugs, & what not. An experimenter's nightmare. \$2.00

GIANT RESISTOR KIT
 200 assorted 1/2 W. American made resistors—all insulated. ONLY \$2.50

GEAR ASSORTMENT
 100 small assorted gears, bushings, & shafts. Most are stainless, or brass. An experimental treasure. \$6.50

OIL FILLED CONDENSERS

MFD	VDC	PRICE	MFD	VDC	PRICE
4	1000	\$1.59	4	2000	1.30
1	2000	1.95	1	3000	2.75
3	3000	7.95	8	2000	8.95
12	2500	15.80	32	4000	29.50
2	4000	4.88	1	15KV	45.00
1	6000	9.95	1	10KV	8.95
1	7000	1.79	1	20KV	19.95
1	8000	6.50	1	50KV	24.50
1	10KV	29.50	1	50KV	42.50
1	15KV	45.00	1	50KV	85.00
1	10KV	8.95	1	50KV	85.00
1	15KV	19.95			
1	20KV	24.50			
1	25KV	29.50			
1	30KV	34.50			
1	35KV	39.50			

FILTER CHOKE — 10 HY
 400 MA. 90 OHMS \$488
 3500 VDC. TEST
 HERMETIC SEALED

Selayn Motors 50V-50 cy. 3/8" D X 5/8" L. Connect in series for use on 110 V-60 cy. Like new. Only \$12.95

TERMS—Cash with Order or 25% Deposit—Balance C.O.D. Net 10 Days to Rated Accounts. All Prices are Net F.O.B. our Warehouse.

RELIANCE MERCHANDISING CO.
 2219 ARCH ST., PHILA. 3, PA.

below the speech range were attenuated in three different ways.

First, the coupling condenser at the plate of the 6SQ7 is operating in a circuit whose impedance at low frequencies is twice the impedance required by the filter, or 164,000 ohms. With a value of .003 μ fd., the response of the complete circuit between the 6SQ7 plate and the following grid starts to drop off below the lower limit of speech frequencies at six decibels-per-octave.

Second, a simple acoustic filtering process was used to increase still further this low frequency attenuation. The loudspeaker was removed from its cabinet and mounted in the exact center of a square baffle a few inches less than three feet on a side, and the baffle mounted out in the open, away from any adjoining wall. With this size baffle, the distance from the front of the speaker cone to the back of the speaker cone averages a half wavelength somewhere between 250 and 300 cycles, and introduces another attenuation of six decibels-per-octave which is effectively added to the similar attenuation introduced by the coupling condenser in the filter circuit. This simple acoustic filtering is valid for any size of speaker, providing the speaker is not so small that its fundamental free air resonance is up in the speech range of frequencies.


The third source of low-frequency attenuation is furnished by the human hearing mechanism itself. At the usual levels of reproduction, the ear becomes progressively less sensitive as the frequency is lowered. This particular attenuation, however, depends on so many other variables that it is difficult, if not impossible, to express precisely. Therefore, the response curve of Fig. 2 shows only the effects of the electrical filtering.

With this filter circuit, and with the speaker mounted in the center of the square baffle, the speech response takes on an added crispness which is very pleasing.

A final added benefit was obtained which was not expected. The tone control no longer performs any useful function, since the filter does the job automatically, and with much more precision. Guesswork and "fiddling" are eliminated. The operator can now be sure that if the speech can be brought out of the QRM by any process of audio filtering, he will hear it.

-30-

Fig. 2. Response curve of the receiver speech filter. Note sharp drop at 3000 cps.

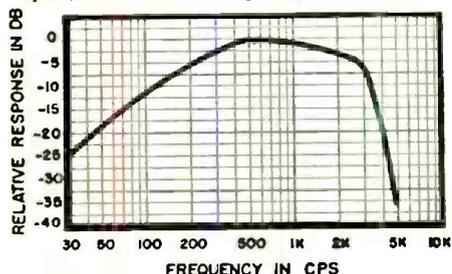

Facts listed are published through the courtesy of Mr. Anthony Todaro, part owner of a thriving radio and TV shop in Monessen, Pa.... Monessen Radio and Television. Mr. Todaro's growing business is based upon a policy of "the best" in material and service.

When reputations rely upon quality... **PERMA-TUBE** stands the test!

HERE'S THE PERMA-TUBE RECORD AT *MONESSEN RADIO AND TELEVISION


- 1 1800 installations without a single antenna mast failure.
- 2 Not a single claim for rusted, bent, twisted, or broken masts since PERMA-TUBE was adopted in 1949.
- 3 PERMA-TUBE installations show no wear after 41 months (average antenna life 27 months).
- 4 Storm that flattened 100 antennas failed to buckle PERMA-TUBE masts.
- 5 PERMA-TUBE supports shop's fine reputation for high-quality work.

Here's why PERMA-TUBE backs up quality service

- 1 PERMA-TUBE IS STURDY . . . it's made of special, high-strength, J&L steel.
- 2 PERMA-TUBE IS CORROSION-PROOF . . . it's treated with vinsynite—then coated inside and outside with a metallic vinyl resin base.
- 3 PERMA-TUBE IS EASILY INSTALLED . . . it's the only mast with both ends of the joint machine fitted.

Here's proof of how Perma-tube resists corrosion

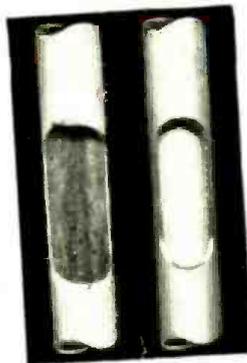Section of ordinary conduit tubing used for TV masts after 96 hours in a salt spray test (A.S.T.M. Designation B-117-49T) to accelerate corrosion. Extensive rust inside the mast has reduced strength—caused rusty water to drain onto the owner's home.



Section of PERMA-TUBE after 500 hours salt spray test shows no evidence of corrosion. Strength has been retained and the chance of rust streaks on owner's home is eliminated. Note sturdier wall thickness of PERMA-TUBE sample.

PERMA-TUBE IS AVAILABLE IN STANDARD LENGTHS . . . DIAMETERS . . . WALL THICKNESSES. FOR COMPLETE INFORMATION MAIL THIS COUPON



Jones & Laughlin Steel Corporation
495 Gateway Center, Pittsburgh 30, Pa.

Without charge, please send me: Name of nearest distributor Complete information on PERMA-TUBE

Name _____
Company _____
Address _____

NEWARK

YOUR KEY TO
★ BARGAINS
★ SPECIAL VALUES
★ SAVINGS



YOU SAVE \$30
on this ESPEY 512C
FM-AM TUNER

New Low Price \$69.50

High Fidelity Tuner Chassis. Completely self-powered tuner. Featuring full tonal range with increased selectivity and sensitivity. Tuned RF stage and two high gain IF stages. Built-in pre-amplifier for all magnetic cartridges with switch for selecting crystal phono. Circuit is drift compensated. Uses 9 tubes including 3 dual purpose types, plus 5Y3GT rectifier. 6 gang tuning condenser. High and low level audio outputs. Phono input on rear of chassis. Complete with tubes AM and FM antennas, hardware and eschecheon. For 105/125 volts, 60 cycle. Size: 13 1/2" W x 8 1/2" H x 9" D. wt., 16 lbs.

96F031. NET.....**\$69.50**



FAMOUS NAME ★
MIDGET CONTROLS
10 of one type.. ONLY \$1.75

Save while quantities last! Flat 2" shaft with all fittings and hardware. All are linear taper except *audio and *series or cathode. Wt., per 10, 1 lb.

No.	Ohms	No.	Ohms	No.	Ohms
U-12	5,000*	U-33	50,000*	U-46	250,000
U-14	5,000	U-34	50,000†	U-48	500,000*
U-18	10,000*	U-35	50,000	U-50	500,000
U-19	10,000†	U-36	75,000*	U-51	750,000*
U-20	10,000	U-39	100,000*	U-53	1 Meg*
U-21	15,000*	U-40	100,000†	U-54	1 Meg
U-22	15,000†	U-41	100,000	U-55	2 Meg*
U-24	20,000*	U-42	150,000*	U-56	2 Meg
U-26	20,000	U-43	200,000	U-57	3 Meg*
U-28	25,000†	U-44	250,000*	U-59	3 Meg
U-29	25,000	U-45	250,000†	U-65	5 Meg*

TAPPED MIDGET CONTROLS

No.	Ohms	Tap	No.	Ohms	Tap
UT-420	250,000	50,000	UT-443	1 Meg	450,000
UT-425	350,000	70,000	UT-448	2 Meg	250,000
UT-427	500,000	100,000	UT-450	2 Meg	125,000
UT-429	500,000	50,000	UT-451	2 Meg	900,000
UT-431	500,000	225,000	UT-454	2 Meg	400,000

★ **Newark Specials** ★

2 Mfd. 600 VDC. General Electric Pyranol-filled capacitor. Flange type mounting. Ceramic pillar terminals. 10/32" studs. Size, 2x2 1/4x1". Wt., 1 lb. **54G006. 10 for 3.00 Each 39c**

5 Mfd. 1000 VDC. Type BAR. Oil filled. Solder terminals. Size, 3 1/2x3 1/4x1 1/4". Wt., 1 lb. **54G400. 10 for 7.50 Each 98c**

1 Mfd. 5000 VDC. General Electric Pyranol-filled filter capacitor. Large ceramic terminals. With ntc. clamps. Size, 4 1/2x3 1/2x4 1/4". Wt., 3 lbs. **54G004. Special Price 4.95**

35 ohm, 50-watt Pot. Ohmite Type "J" wire-wound pot. Heavy ceramic form. 1/4" shaft for 3/8" mtg hole. 1 lb **54G587. 10 for 5.50 Each 69c**

Thordarson T-45166 Output Transformer. Single G6 to 2-4-8-500 ohms voice coil. Case size 2 1/4x2 1/2x3" high. Shpg. wt., 5 lbs. **54G581. 10 for 12.00 Each 1.50**

Driver Transformer. P.P. 2A3's to grids. Case size, 3 1/4x2 1/2x3" high Shpg. wt., 5 lbs. **54G111. 10 for 15.00 Each 1.95**

Dept. R-9 . . . FOB Chicago

Send for FREE Catalog

NEWARK

ELECTRIC COMPANY

223 W. MADISON ST. CHICAGO 6, ILL.

Technical BOOKS

"ELEMENTS OF ELECTRICITY" by William H. Timbie. Published by *John Wiley & Sons, Inc.*, New York. 624 pages. Price \$5.50. Fourth Edition.

Any person who has ever taken a radio or electricity course without encountering Prof. Timbie's "Elements of Electricity" is a rare exception indeed. This revised edition of a work which has been known to several generations of students is a welcome addition to the literature.

Like the previous editions of this book, the material is presented at an elementary level and provides the student with the fundamentals so necessary to a thorough understanding of the subject.

Beginning with an exposition of Ohm's Law, the text progresses naturally and logically through electrical power and energy, wire, the measurement of resistance, magnets and magnetism, the magnetic circuit, the generator, operation of d.c. generators, electric motors, batteries and electrochemical action, the simplification of circuits, inductance, capacitance, alternating currents, electronics and electron tubes, and electrostatic behavior. Nine tables are presented in the appendix to give the reader all of the supplementary data required in his studies.

Students seeking an authoritative and readable text on the subject of electricity would do well to investigate this up-to-date work by one of the country's leading engineers.

* * *

"BRITISH RADIO COMPONENTS" compiled and published by *Radio & Electronic Component Manufacturers Federation*. Available from The Radio Industry Council, 11 Garrick St., London W. C. 2, England. 210 pages. Price 1 shilling.

This publication is the official catalogue and buyer's guide issued by the Radio Components Show held recently in London. It is intended to be used as a reference and handbook to the radio components available from various British firms.

The catalogue is thoroughly indexed and includes, in addition to technical data on the parts, two articles, one on the show and the other on the ever-increasing use of electronic components.

Since well over 400,000 English pounds' worth of British components were exported to the United States in 1952, the value of this handbook to American users is obvious.

* * *

"PRINCIPLES AND PRACTICES OF TELECASTING OPERATIONS" by Harold E. Ennes. Published by *Howard W. Sams & Co., Inc.*, Indianapolis. 600 pages. Publication date October 1, 1953.

Well-known to readers of this publication, Mr. Ennes covers all phases

of telecasting operations from networks and remote links through monitors, cameras, control rooms, studio transmitters, and even production planning.

The publication will be non-technical in that no knowledge of advanced theory or mathematics is required for an understanding of the text material. It is suitable for all personnel connected with the technical production of video and audio program material from camera, mike, or projector through the transmitter. Students will also find it of value.

Department 107 of the publisher, 2201 East 46th Street, Indianapolis 5, Ind., will supply full details on this book upon request.

* * *

"ELECTRONIC CIRCUITRY FOR INSTRUMENTS AND EQUIPMENT" by Milton H. Aronson. Published by *Instruments Publishing Co.*, 921 Ridge Ave., Pittsburgh 12, Pa. 305 pages. Price \$4.00.

The material appearing in this valuable home-study text originally ran serially in the magazine "Instruments" and contains a wealth of pertinent data in non-mathematical, concise style.

The text is divided into fifteen chapters which cover fundamentals, vacuum tubes, gas-filled tubes, rectification and power supplies, amplifier circuits, solid-state amplifiers, oscillator circuits, signal-shaping circuits, electrical and electronic test equipment, r.f. communication and television, scientific and industrial instruments, and military electronics.

The book also carries 450 multiple-choice questions so that the student can check his grasp of the subject matter.

As a comprehensive source book on instrument circuitry, this one will be hard to beat.

-30-

SERVICE ACCOUNTING

READERS of this magazine may now obtain a free copy of a new service publication, "Accounting Procedures for Radio and TV Service Technicians" by Donald B. Shaw, vice-president of *Howard W. Sams & Co., Inc.*, 2201 E. 46th St., Indianapolis 5, Ind.

Prepared as an aid for the small service operator, this handy booklet outlines simplified accounting procedures which permit the owner of the small shop to ascertain his financial condition at any time.

The booklet shows how to prepare a balance sheet of varying degrees of elaborateness to meet the requirements of various sized businesses. How such a balance sheet is to be used in doing business is explained in some detail.

The second part of the booklet explains the profit and loss statement, how it is prepared, and how it is to be used in conducting a successful servicing operation.

Readers desiring a copy of this publication may have one without charge by writing to the publisher direct.

-30-



Edward H. Guilford
Executive Vice President

Want To DOUBLE YOUR PAY?

How To Pass FCC COMMERCIAL RADIO OPERATOR EXAMINATIONS FCC LICENSE



TELEVISION ENGINEERING
Included in our
Training and coaching

GET THIS AMAZING NEW BOOKLET FREE!

TELLS HOW...

WE GUARANTEE
TO TRAIN AND COACH YOU AT
HOME IN SPARE TIME UNTIL YOU GET
YOUR FCC LICENSE

If you have had any practical experience—Amateur, Army, Navy, radio repair, or experimenting.

HERE IS YOUR GUARANTEE

If you fail to pass your Commercial License exam after completing our course, we guarantee to continue your training without additional cost of any kind, until you successfully obtain your Commercial license, provided you first sit for this examination within 90 days after completing your course.

TELLS HOW...

**Our Amazingly Effective
JOB-FINDING SERVICE**

Helps CIRE Students Get Better Jobs

Here are a few recent examples of Job-Finding results:

GETS CIVIL SERVICE JOB

"Thanks to your course I obtained my 2nd phone license, and am now employed by Civil Service at Great Lakes Naval Training Station as an Equipment Specialist."
Kenneth H. Lelser, Fair Oaks, Md. Del., Melherry, Ill.

GETS STATE POLICE JOB

"I have obtained my 1st class ticket (thanks to your school) and since receiving same I have held good jobs at all times. I am now Chief Radio Operator with the Kentucky State Police."
Edwin P. Healy, 264 E. 3rd St., London, Ky.

GETS BROADCAST JOB

"I wish to thank your Job-Finding Service for the help in securing for me the position of transmitter operator here at WCAE in Pittsburgh."
Walter Koschik, 1442 Ridge Ave., N. Braddock, Pa.

GETS AIRLINES JOB

"Due to your Job-Finding Service, I have been getting many offers from all over the country, and I have taken a job with Capital Airlines in Chicago, as a Radio Mechanic."
Harry Clare, 4537 S. Drexel Blvd., Chicago, Ill.

TELLS HOW...

**Employers Make JOB OFFERS Like These
to Our Graduates Every Month!**

Letter from nationally-known Airlines, "We would also appreciate if you would place the following additional advertisement in your bulletin—Wanted—Superintendent of Communications . . . Salary \$666.66 per month."

Letter from nationally-known airplane manufacturer, "We need men with electronic training or experience in radar maintenance to perform operational check-out of radar and other electronics systems . . . starting salary . . . amounting to \$329.33 per month."

Letter from nationally-known Airlines, "We are contemplating placing . . . an Airline Ground Radio Engineer." Starting salary \$385 per month.

These are just a few examples of the job offers that come to our office periodically. Same licensed radioman filled each of these jobs . . . it might have been you!

**HERE'S PROOF FCC LICENSES ARE OFTEN
SECURED IN A FEW HOURS OF STUDY WITH
OUR COACHING AT HOME IN SPARE TIME**

Name and Address	License	Lessons
Lee Worthy 2210 1/2 Wilshire St., Bakersfield, Calif.	2nd Phone	16
Clifford E. Vogt Box 1016, Dania, Fla.	1st Phone	20
Francis X. Foerch 38 Beucler Pl., Bergenfield, N. J.	1st Phone	38
S/Sgt. Ben H. Davis 317 North Roosevelt, Lebanon, Ill.	1st Phone	28
Albert Schoell 110 West 11th St., Escondido, Calif.	2nd Phone	23

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
Carl E. Smith, E. E., Consulting Engineer, President
Desk RN-56, 4900 Euclid Bldg., Cleveland 3, Ohio

**OURS IS THE
ONLY HOME
STUDY COURSE
WHICH SUP-
PLIES FCC-TYPE
EXAMINATIONS
WITH ALL LES-
SONS AND FINAL
TESTS.**



Your FCC Ticket is recognized in all radio fields as proof of your technical ability.

MAIL COUPON NOW

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
Desk RN-56—4900 Euclid Bldg.
Cleveland 3, Ohio
(Address to Desk No. to avoid delay.)

B I want to know how I can get my FCC Ticket in a minimum of time. Send me your FREE booklet, "How to Pass FCC License Examinations" (does not cover exams for Amateur License), as well as a sample FCC-type exam and the amazing new booklet, "Money-Making FCC License information."

Be sure to tell me about your Television Engineering Course.

Name.....
Address.....
City..... Zone..... State.....

Paste on two cent postcard or send air mail.

DO YOU USE ...

ERIE

... the Most Complete Line of Ceramic Replacement Capacitors

ERIE FEED-THRU CERAMICONS



STYLE 362

STYLE 327


ERIE BUTTON SILVER MICA CAPACITORS



STYLE CB

STYLE FA

ERIE DISC and PLATE CERAMICONS

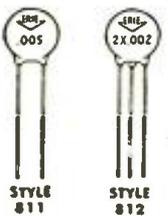

STYLE 005

STYLE 2X002

STYLE 811

STYLE 812

ERIE CERAMICON and TUBULAR TRIMMERS



STYLE TD2A

STYLE TS2A

STYLE 557

STYLE 532

ERIE Electronic Components have long enjoyed the reputation of being always of the highest quality. They are produced by experienced craftsmen, in a factory equipped with the finest machinery, much of which was designed and built especially for ERIE. Leading builders of radio and TV sets have approved ERIE components and have been using them for 25 years.

ERIE components are stocked by leading electronic distributors everywhere.

ERIE CERAMICONS

STYLE L




STYLE 334

ERIE UNIVERSAL 20KV CERAMICONS



STYLE 413

ERIE PRINTED CIRCUITS

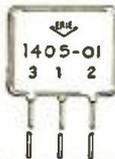

1405-01
3 1 2

ERIE STAND-OFF CERAMICONS



STYLE 325

STYLE 326

STYLE 2336

STYLE 323

STYLE 324

ERIE

RESISTOR CORP.

ERIE RESISTOR CORPORATION . . . ELECTRONICS DIVISION

Main Offices: ERIE, PA.

Sales Offices: Cliffside, N.J. • Philadelphia, Pa. • Buffalo, N.Y. • Chicago, Ill. • Detroit, Mich. • Cincinnati, Ohio • Los Angeles, Calif.

Factories: ERIE, PA. • LONDON, ENGLAND • TORONTO, CANADA

!!WANTED!!

In order to supply government and industrial requirements, we are paying top dollar for all types of radio and electronic surplus. We specialize in test equipment and complete radios, such as:

APA, APN, APQ, APR, APS, APT, ARB, ARC, ARN, ART, ATC, BC, DY, I, IE, LM, MG, PE, PU, SCR, TCS, TN, TS, and many others.

WE ESPECIALLY NEED: APA10, APN9, APR4, APS4, ARC1, ARC3, ART13, ATC, BC221, BC342, BC348, BC611, BC721, DY12, DY17, I100, LM10 to LM18, MG149F, MG149H, PUI4, R5/ARN7, R5A/ARN7, SCR718C, TCS, TN16, TN17, TN18, TN19, TN54, TS3, TS13/AP, TS33, TS35, TS45, TS75, TS76, TS102, TS147/UP, TS148/UP, TS173, TS174, TS175, TS250, TS251, TS323, (ICT, IF, IG, 5CT, 5DG, 5F, 5G, 6DG, 6G 115V, 60 c.p.s. Selsyns), and all types of Hewlett Packard, General Radio Co., Measurements Corp., Boonton Radio, Ferris, Leeds & Northrup, and other test equipment.

Please state accurate description, condition, and your lowest price. Explain modifications, if any. We pay freight charges.

PURCHASING AGENTS, ENGINEERS, EXPORTERS, INDUSTRIAL BUYERS, DEALERS, AND INDIVIDUALS, Please send us your requirements.

New Catalog Now Available


PHOTOCON SALES

417 N. Foothill Blvd.
Pasadena 8, California

SYcamore 2-4131
RYan 1-6751

Compo EASY-HANDLING MAGNETIC TAPE REELS

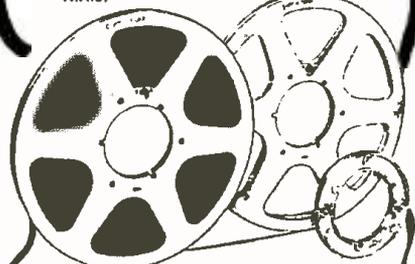Precision manufactured in accordance with the exacting standards set by the N.A.B.



- Easy to handle because:
1. Burrs and sharp edges are smoothed away.
 2. Components assemble quickly, easily.
 3. Aluminum flanges stay flat. Eliminate tape rubbing.
 4. Hubs are die-cast to close tolerance.
 5. Grey, "write-on" finish available for editing notes.

TAPE REELS, STORAGE CANS, AND SHIPPING CASES FOR EVERY PROFESSIONAL REQUIREMENT ALWAYS IN STOCK

Write for descriptive literature and price list

COMPO CORPORATION

Manufacturers of fine products for the Audio-Visual industry.

2251 W. St. Paul Ave. Chicago 47, Illinois

Input Switching

(Continued from page 71)

sides. The series heater condenser was made up of a 2 μ f. and two .5 μ f. condensers in parallel due to their being on hand, though, of course, any parallel combination of condensers totalling 3 μ f. can be used. They should be rated at 400 volts d.c.. If more than four inputs are required, as many additional triode sections as needed can be added to the assembly without any change in the cathode or filter resistors as only one section is drawing current at any one time. If an odd number of inputs is required, the odd triode may be a type 6C4, which is similar to one section of the type 12AU7.

A ventilating plug was mounted in the cover over each tube and rubber feet were attached to the bottom of the case by tapping the holes intended for the self-tapping screws that hold on the bottom plate. A one-quarter inch roundhead machine screw was passed through the hole in the rubber feet and this screw used to secure both the feet and the bottom plate. If the usual wiring precautions of keeping the grid circuits far away from the heater wiring are taken, no hum troubles will be encountered. The heater leads and the output lead were shielded as an additional hum prevention. It will be found that reversing the a.c. plug in the wall outlet will affect the hum level, so the connection which gives least hum should, of course, be used. Plate voltage was obtained from the main amplifier power supply. The insertion loss of this coupling unit is about 4 db when working into a 500,000 ohm load, little enough so that it can be easily compensated for by the spare gain usually available in home radio systems.

As the output impedance is low, the shielded cable between the unit and the following amplifier can be any length normally required in home installations, up to perhaps a hundred feet or so.

One point often misunderstood is that although the output impedance of a cathode follower may be in the neighborhood of 500 ohms, the load offered to the follower by the next amplifier can be the customary 500,000 ohms. It does not have to match the output impedance of the follower any more than it would have to match the output of any voltage amplifier.

A 4-pole, single throw shorting switch was mounted on the back of the FM tuner volume control and the a.c. toggle switch was removed. On the AM tuner, the original single-pole, single-throw switch on the volume control was replaced by a single-throw unit. These two tuners could now be operated simply by turning up the volume control, the way radio sets have been turned on during

BUY TEST EQUIPMENT ON THIS RADICALLY NEW TIME PAYMENT PLAN

NO INTEREST!! - NO CARRYING CHARGES!!

USE CONVENIENT TIME PAYMENT ORDER BLANK BELOW

Superior's New Model 770

VOLT-OHM

MILLIAMMETER


Sensitivity—1000 ohms per volt

Uses latest design 2% accurate 1 Mil. D'Arsonval type meter. • Same zero adjustment holds for both resistance ranges. It is not necessary to readjust when switching from one resistance range to another. This is an important time saving feature never before included in a V.O.M. in this price range. • Housed in round-oriented, molded case. • Beautiful black etched panel. • Depressed letters filled with permanent white insures long-life even with constant use.

- SPECIFICATIONS:**
- 6 A.C. VOLTAGE RANGES: 0-15 30-150 300-1500 3000 Volts.
 - 6 D.C. VOLTAGE RANGES: 0-7.5 15-75 150-750 1500 Volts.
 - 4 D.C. CURRENT RANGES: 0-1 15/150 MA. 0-1.5 Amps.
 - 2 RESISTANCE RANGES: 0-500 Ohms. 0-1 Megohm.

The Model 770 comes complete with self-contained batteries, test leads and all operating instructions.

\$14.90 NET

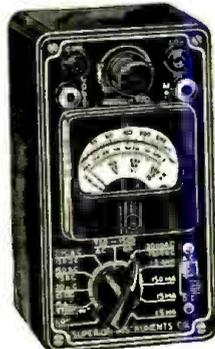

Model 770 is an accurate pocket-size V.O.M. Measures only 3 1/2" x 5 7/8" x 2 1/4".

Superior's New Model TV-11 **TUBE TESTER**



Operates on 105-130 Volt 60 Cycles A.C. Hand-rubbed oak cabinet complete with portable cover

\$47.50 NET

• Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-11 as any of the pins may be placed in the neutral position when necessary. • Uses no combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket. • Free-moving built-in roll chart provides complete data for all tubes. • Phono jack on front panel for plugging in either phones or external amplifier detects microphonic tubes or noise due to faulty elements and loose external connections.

Superior's New Model 670-A

SUPER-METER

A COMBINATION VOLT-OHM MILLIAMMETER PLUS CAPACITY REACTANCE INDUCTANCE AND DECIBEL MEASUREMENTS

- SPECIFICATIONS:**
- D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500 7,500 Volts.
 - A.C. VOLTS: 0 to 15/30 150/300/1,500 3,000 Volts.
 - OUTPUT VOLTS: 0 to 15/30 150/300/1,500 3,000 Volts.
 - D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5 15 Amperes
 - RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms
 - CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd. (Quality test for electrolytics)
 - REACTANCE: 50 to 2,500 Ohms. 2,500 Ohms to 2.5 Megohms
 - INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries
 - DECIBELS: -6 to +18 +14 to +38 +34 to +58

\$28.40 NET

ADDED FEATURE: The Model 670-A includes a special GOOD-BAD scale for checking the quality of electrolytic condensers at a test potential of 150 Volts.



Comes housed in rugged, rackie-finished steel cabinet complete with test leads and operating instructions. Size 6 1/2" x 9 1/2" x 4 1/2".

Superior's New **TV BAR GENERATOR**

THROWS AN ACTUAL BAR PATTERN ON ANY TV RECEIVER SCREEN!!



TV Bar Generator comes complete with shielded leads and detailed operating instructions. Only

\$39.95 NET

CONNECTS DIRECT TO ANTENNA POST
NO CONNECTION INSIDE RECEIVER

Features.—Can be used when no stations are on the air. • Provides linear patterns to adjust vertical and horizontal linearity. • Provides vertical and horizontal sweep signals. • Provides signal for testing video amplifiers.

Superior's Model 660-A—A NEW A.C. OPERATED

SIGNAL GENERATOR

Provides Complete Coverage for A.M.—F.M. and TV Alignment



• Tubes used: 1-6BE6 as R. F. Oscillator, mixer and amplifier, 1-6BE6 as Audio Oscillator, 1-6H6 as Power Rectifier. The Model 660-A comes complete with coaxial cable test lead and instructions. NET

\$42.95 NET

• Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 220 Megacycles on powerful harmonics. • Accuracy and stability are assured by the use of permeability trimmed Hi-Q coils. • R. F. available separately or modulated by the internal audio oscillator. • Built in 400 cycle sine wave audio oscillator used to modulate the R. F. signal also available separately for audio testing of receivers, amplifiers, hard of hearing aids, etc. • R. F. Oscillator Circuit: A high transconductance heptode is used as an R. F. oscillator, mixer and amplifier. Modulation is effected by electron coupling in the mixer section thus insulating the oscillator from load changes and affording high stability. • A. F. Oscillator Circuit: A high transconductance heptode connected as a high- μ triode is used as an audio oscillator in a high-C Colpitts Circuit. The output (over 1 Volt) is nearly pure sine wave. • Attenuator: A 5 step ladder type of attenuator is used.

NEW TIME PAYMENT PLAN ORDER BLANK

MOSS ELECTRONIC DISTRIBUTING CO., INC. Dept. B-73, 38 Murray Street, New York 7, N. Y.

Please send me the units checked below. I am enclosing the down payment with order and agree to pay the monthly balance as shown. It is understood there will be no carrying interest or any other charges, provided I send my monthly payments when due. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

- MODEL 770 \$2.00 down payment. Balance \$2.00 monthly for 6 months. Total Price \$14.90
- MODEL TV-11 \$11.50 down payment. Balance \$6.00 monthly for 6 months. Total Price \$47.50
- MODEL 670-A \$7.40 down payment. Balance \$3.50 monthly for 6 months. Total Price \$28.40
- TELEVISION BAR GENERATOR \$9.95 down payment. Balance \$5.00 monthly for 6 months. Total Price \$39.95
- MODEL 660-A \$12.95 down payment. Balance \$5.00 monthly for 6 months. Total Price \$42.95
- I enclose \$..... as down payment.
- Ship C.O.D. for the down payment.

Signature.....

Name.....

Address.....

City..... Zone..... State.....

HARVEY

WHERE YOU
FIND the FINEST



THE ORIGINAL WILLIAMSON HR-15 AMPLIFIER KIT



The famous, original Williamson HR-15... still acclaimed the leader... in kit form, with the original Partridge output Transformer. Assemble this kit, and in 3 hours or less, enjoy the finest sound you ever heard. Operates from a tuner, phono-preamp, crystal pick-up, or other signal source. Absolute gain is 70.8 db with 20 db of feedback. Frequency response: ± 5 db, from 10 to 100,000 cps. Output impedances to match all speakers from 1.7 to 109 ohms. Kit is complete with 5 tubes (1-5V4, 2-6SN7, and 2-5881 (or 807 if requested), 2-Punched Chassis, 2-Resistor Mounting Strips, Sockets, Partridge WWFB Output Transformer, Assembly Instructions, and All Other Necessary Parts for Amplifier and Power Supply. **\$76.50**

HR-15 as above, but with Partridge CFB Output Transformers (hermetically sealed) **\$90.00**

PARTRIDGE OUTPUT TRANSFORMERS available separately. WWFB **\$26.00** CFB **\$40.00**

NOTE: HR-15 Kits may be had with British KT-66 Output tubes for \$3.00 additional.

McINTOSH HI-FI UNITS

Model C104
PHONO
PREAMPLIFIER
and
EQUALIZER



Provided with five inputs and selector switch, and accommodates FM-AM Tuner, crystal pickup, low level and high level magnetic pickups, low level microphone, and other signal sources. Phono section has three-position switch for selecting correct turnover, and a versatile treble control to provide required roll-off, to match most record characteristics. Separate bass and treble, boost and attenuation controls are effective on all input channels. A master power switch and volume control complete the attractive 5-knob panel. Power is obtained from main amplifier. Supplied with tubes and power cable.

Less Cabinet (with knobs and panel) **\$49.50**
In Mahogany Finish Cabinet **\$57.50**

30 Watt
AMPLIFIER
Model A-116



Incorporates the famous patented McIntosh output circuit for extremely high quality performance. Frequency response at 30 watts is $\pm .5$ db from 10 to 50,000 cycles. Harmonic distortion is less than .5% at 30 watts from 20 to 20,000 cycles. Inter-modulation distortion, with peak below 60 watts, is less than 1%. Has two high impedance inputs for .25 and 2.5 volt signals, and four outputs: 4, 8, 16, and 600 ohms. Power supply is built in, with provision for furnishing power to McIntosh and other preamplifiers. Uses 6BG6 output tubes.

Complete with Tubes **\$139.50**

NOTE: Prices Net, F.O.B., N.Y.C.
Subject to change without notice.



Harvey
RADIO COMPANY, INC.

103 W. 43rd St., N.Y. 36, N.Y. • JU 2-1500.

the years preceding high fidelity in the home. The dial lights on each tuner served to indicate that the system is on. This made the pilot light on the equalizing preamp unnecessary, thus eliminating one more part on what had been the central control panel.

A volume control, with its switch, and a pilot light were mounted alongside the phono preamp equalizer control, completing this part of the job.

A new panel of quarter-inch plywood, painted to match the shelves of the bookcase, and cut out for the two tuner dials and their tuning and volume control knobs, was mounted in front of the tuners. The former central control panel which had been reduced to holding only the bass and treble controls was installed between the two tuners so that the symmetry was preserved.

Another installation was made which also employed this automatic switching circuit. In this one it was found to be more convenient to mount just the double-pole, single-throw switches on each of the input sources, a tape recorder, TV set, FM tuner, and a record player, and use only one volume control mounted between the bass and treble knobs.

You will find, as the author has, that the time and effort expended on simplifying the operation of your home radio/phonograph installation will be amply repaid by the additional use of the equipment made by the family, thus giving you a better return on your investment.

Transistor Curves (Continued from page 67)

known a.c. voltage to the "Vert. Input" and "Hor. Input" terminals of the scope and adjusting the "Vert. Gain" and "Hor. Gain" controls, respectively, for a given deflection.

As an example, an a.c. voltage having a peak-to-peak amplitude of six volts could be applied to the "Hor. Input" terminals of the scope and the "Hor. Gain" control adjusted for a deflection of 3 inches. The horizontal sensitivity then becomes 2 volts/inch.

If an a.c. voltage having a peak-to-peak amplitude of 0.6 volt is applied to the "Vert. Input" terminals of the scope and the "Vert. Gain" control adjusted for a deflection of 3 inches, the vertical sensitivity is then 0.2 volt/inch.

Once the "Hor. Gain" and "Vert. Gain" controls have been set in this manner, no changes should be made in their settings while a particular characteristic curve (or group of curves) is obtained.

The characteristic curves obtained with the scope controls preset as described may be compared in terms of actual collector current and voltage, and, when recorded, are sufficiently accurate for many types of engineer-

CRYSTALS

LARGEST
STOCK



IN THE
WORLD

In FT 241-A Hold. crs.— $\frac{1}{2}$ in. Pin SFC. These are designated 54th or 72nd Harmonic MC freq. Listed by fundamental freq. with fractional increments.

370	396	419	443	466	491	513
372	397	420	444	468	492	514
374	398	422	445	469	493	515
375	400	423	446	470	494	516
376	401	424	447	472	495	518
377	402	425	448	473	496	519
379	403	426	450	474	497	520
380	404	427	451	475	498	522
381	405	429	452	476	499	523
383	406	430	453	477	501	525
384	407	431	454	479	502	526
385	408	433	455	480	503	527
387	409	434	456	481	504	529
388	411	435	457	483	505	530
390	412	436	458	484	506	531
391	413	437	459	485	507	533
392	414	438	462	486	508	536
393	415	440	463	487	509	537
394	416	441	464	488	511	538
395	418	442	465	490	512	540

All above crystals sent postpaid. Also available in complete sets for SCR-608, SCR-528, SCR-628, and TRC. Foreign, wholesale, and dealer inquiries invited. Write for LARGE QUANTITY DISCOUNTS.

COMPLETE SET—80 CRYSTALS
In above gradations from 370-516 Kc., 54th Harmonic, INCLUDING 500 Kc. & 455 Kc. crystals. Only...Per set **\$12.50**

COMPLETE SET—120 CRYSTALS
In above gradations from 370-540 Kc., 72nd Harmonic, PLUS 500 Kc. & 455 Kc. crystals. Only...Per set **\$16.95**

200 KC. CRYSTAL.....Ea. \$2.25
500 KC. CRYSTAL.....Ea. 1.25
1,000 KC. CRYSTAL.....Ea. 3.25

All crystals sold us 18.

MISCELLANEOUS BEST BUYS

EE-8 FIELD PHONE. In good working cond. Each unit **\$14.95**

6 V. WET CELL BATTERY. NF-6, Heavy plastic case. $3\frac{1}{2} \times 2\frac{1}{2} \times 1\frac{1}{4}$ in. New... **\$2.49**

ARC-4 TRANSCEIVER. Excellent 2-meter rig. Less tubes and dynamotor. Only... **\$10.95**

12-24 V. DYNAMOTOR. For above unit. Excellent cond. Specially... **\$7.50**

APS-13 TRANSCEIVER. Complete with tubes and dynamotor. Easily converted to 420 MC. Excellent cond. **\$22.50**

RL-42 REVERSIBLE MOTOR & CLUTCH. Used, good condition. A HOT buy at only **\$2.95**

6 V. WET CELL BATTERY. In heavy, polyethylene plastic case. $6 \times 4 \times 4$ inches. New... **\$4.95**

COMPLETE 2-WAY SOUND POWERED COMMUNICATION SET. Consists of single unit on each end PLUS 50 ft. of wire. The set COMPLETE only **\$3.35**

All prices are net F.O.B. Los Angeles.

All items subject to prior sale.



J.J. GLASS ELECTRONICS CO.
1615 S. MAIN STREET
LOS ANGELES 15, CALIF.

Say You Saw It In RADIO & TELEVISION NEWS

Unlimited Opportunities in

RADIO ENGINEERING

DEGREE IN 27 MONTHS

Complete Radio Engineering course, including Telev., U.H.F. and P.M. Bachelor of Science Degree also in Mech., Civil, Elect., Chem., and Aero. Eng.; Bus. Adm., Acct. Extensive campus, modern buildings, well equipped labs. Low cost. Prep courses. Personalized, practical instruction. Founded 1884. Placement service. Growing shortage of engineers. Prepare now for unlimited opportunities ahead. Approved for Korean vets. Enter September, January, March, June. Write for catalog.



TRI-STATE COLLEGE

1693 College Avenue. ANGOLA, INDIANA

RADIO & TELEVISION NEWS

ing measurements and calculations.

As an example, assuming the scope controls preset using the values given before, let us suppose that a curve having a peak amplitude of 1 inch and a width of 3 inches is obtained. The peak vertical input voltage is 0.2 volt. Since this represents the drop across a 100-ohm resistor (R_s , Fig. 2), the peak collector current is 2 milliamperes. The peak collector voltage is 6 volts.

The graph scale permits the collector current for any given collector voltage to be determined in a similar manner.

Recording the Curves

In many cases, the characteristic curve displayed on an oscilloscope screen is of little value unless a record is made of it. Two methods may be used.

A simple tracing of the curve may be made, using either plain or graph paper.

A better technique, however, is to photograph the scope pattern. If desired, the graph scale may be photographed also, so that the transistor characteristic curve appears superimposed on a graph scale in the final photograph.

One technique that has been used to accomplish this is to "de-focus" the oscilloscope beam so that the entire CRT screen glows behind the graph scale. An exposure is made of this. The beam is then refocused and the desired pattern obtained. Another exposure, on the same film, is made of the final curve, thus superimposing the characteristic curve on the previously photographed graph scale—a deliberate double exposure!

A complete family of characteristic curves may be obtained very easily by means of the "multiple exposure" technique. Before taking the first photograph, a small piece of tape is affixed to the CRT screen to serve as a "zero" point so that a series of curves may be properly "lined up."


The first curve is then photographed, after being lined up with the small piece of tape, using the vertical and horizontal centering controls.

Base current is then adjusted to a new value and the new curve lined up properly, again using the vertical and horizontal centering controls—the "Gain" controls should not be touched, however. Another exposure, on the same piece of film, is then made.

This process is repeated until the desired "family" of curves is obtained. A typical "family", photographed using this technique, is shown in Fig. 5. These are collector current vs collector voltage curves for a Raytheon type CK722 junction transistor at base currents of 25, 50, 100, 150, and 200 microamperes, respectively (from bottom to top).

(Note: For those photographers who may be interested in repeating this technique, the following information may be of value. A $2\frac{1}{2} \times 3\frac{1}{4}$ Speed Graphic camera was used, lens setting

September, 1953

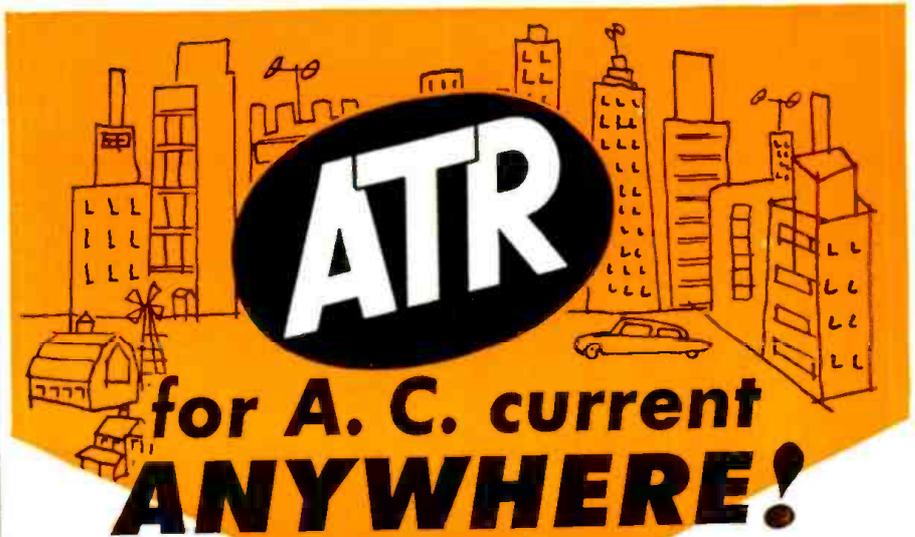

for A. C. current
ANYWHERE!




AT NEW
LOW COST

\$25⁵⁵
And Up
Retail Price

INVERTERS

For Inverting D.C. to A.C. . . . Specially Designed for operating A.C. Radios, Tape Recorders, Wire Recorders, Record Changers, Television Sets, Amplifiers, Address Systems, Radio Test Equipment and most small electrical and electronic devices from D. C. Voltages in Vehicles, Ships, Trains, Planes and in D. C. Districts.

Type	Input DC Volts	A.C. Output 60 Cycles	Output Int.	Wattage Cont.	Consumer Net Price
6-LIF	6	110 volts	40	35	\$25.55
12-LIF	12	110	50	35	25.55
* 6-RSD	6	110	85	75	39.25
*12-RSD	12	110	125	100	39.25
32-RSD	32	110	150	100	39.25
110-RSD	110	110	250	150	39.25
*12T-HSC	12	110	250	200	96.45
110AT-RHE	110	110	325	250	56.95

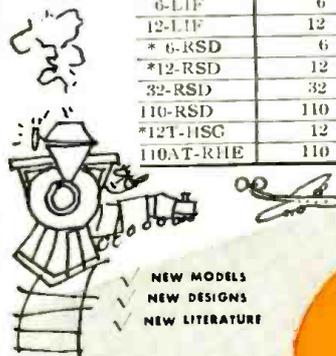

See your jobber
or write factory



There is an ATR model for most any application.
* Available with leather carrying handle at \$1.00 additional—optional.

"A" Battery Eliminators, DC-AC Inverters, Auto Radio Vibrators

AMERICAN TELEVISION & RADIO Co.

Quality Products Since 1931

SAINT PAUL 1, MINNESOTA—U. S. A.

BECOME AN ELECTRICAL ENGINEER



Bachelor of Science Degree in 36 months.

Major in Electronics or Power. Now, prepare for a career in these rapidly expanding fields.

This school will prepare you to become an engineer, technician or service man. Previous military, academic or practical training may be evaluated for advanced credit.

Enter Both Radio and Television

In 12 months you can attain the Radio-Technician's certificate. An added 6 months course qualifies you for the Radio-TV Technician's certificate and the Degree of "Associate in Applied Science." The Technician's course is the first third of the program leading to a Bachelor of Science Degree in Electrical Engineering with a major in Electronics.

Also offered: 12-month Radio-TV service course; 12-month Electronics or Electro Technician Courses; 6-month Electrical Service Course and 3-month refresher and general preparatory classes.

Terms Open Oct., Jan., April, July

Famous for its Concentric Curriculum. Faculty of specialists. 50,000 former students. Annual enrolment from 48 states and 23 overseas countries. Non-profit. 50th year. Courses approved for Veterans. Residence courses only.



MILWAUKEE SCHOOL OF ENGINEERING

MILWAUKEE SCHOOL OF ENGINEERING
Dept. RN-953, 1025 N. Milwaukee
Milwaukee 1, Wisconsin

Send: Free 45-page "Your Career" booklet describing Electrical Engineering Courses;
 Booklet on Careers in Radio-TV.

I am interested in..... name of course

Name..... Age.....

Address.....

City..... Zone..... State.....

If veteran, indicate date of discharge.....

/4.5, shutter speed 1/25 second, "Super XX Pan-Chromatic" film-pack. Room lights were turned off while making the series of "quintuple" exposures.)

Other Applications

As mentioned previously, this technique may be extended to obtain characteristic curves other than collector current vs collector voltage simply by rearranging the pulsating d.c. and steady d.c. supplies, and by changing the scope connections.

There is still another possible application of the unit shown, however. It may be used to obtain characteristic curves of germanium diodes with equal facility. In fact, the author obtained the characteristic curve of a type 1N34 crystal diode simply by "plugging" it into the transistor socket so that its cathode lead was connected in place of the transistor's collector lead, and so that the "plate" lead was connected in place of the emitter lead. The characteristic curve obtained is shown in Fig. 6. -30-

Electronic Break-in

(Continued from page 55)

Since most receivers have relay terminals on the back which are in series with the r.f. and i.f. tube screen grids, V_2 can be connected directly across the terminals provided, of course, that the correct polarity is observed. This will parallel V_2 across an existing control circuit, thus requiring no modification of such circuit. A drop of only about eleven volts appears across V_2 when it is conducting. Any receiver can stand this small drop in screen voltage with no detectable loss of sensitivity.

In a few receivers disabling is accomplished by breaking the power-supply center tap. In these cases it

Nowak, Edward F.: "Voice Controlled Break-In . . . And a Loudspeaker." QST, May 1951

will be necessary to bring out the r.f. and i.f. screen leads. This, however, is no disadvantage, because oscillator stability will be improved as the oscillator will operate continuously.

For keying the transmitter or exciter, blocked-grid type keying is suggested. If this type of keying is already in use, the grid-blocking voltage will be supplied by the transmitter or exciter. In this case the resistor R_2 may be omitted from the circuit, and the cathode of V_1 may be connected to the blocking bias to be keyed.


If blocked-grid keying is not in use, R_2 will be necessary. In this case, the cathode of V_1 should be connected to a buffer-amplifier grid observing the precaution of using an r.f. choke to prevent any r.f. from going astray.

Voice-controlled operation is equally effective on AM, FM, and single-sideband transmitters. When used with AM or FM transmitters, the receiving operator should turn off his a.v.c. and operate the receiver at reduced r.f. gain. This adjustment of the receiver eliminates blasts of noise when the carrier being received turns off. In operation, adjust R_1 for the highest possible gain consistent with the avoidance of false triggering from background noise.

If loudspeaker operation of the receiver is desired, an excellent article¹ has appeared in the past on this subject. Since the circuit referred to in the footnote produces a positive control voltage, it will be necessary to transpose the audio inputs in order to obtain the negative control voltage required by V_2 . The circuit referred to in the footnote may be connected at points "X" and "Y".


The time spent in building and installing this type of circuit will be well repaid in the operating pleasure it will afford, not to mention the "lost" transmissions it will save, which were formerly lost due to unheard QRM on the frequency. -30-

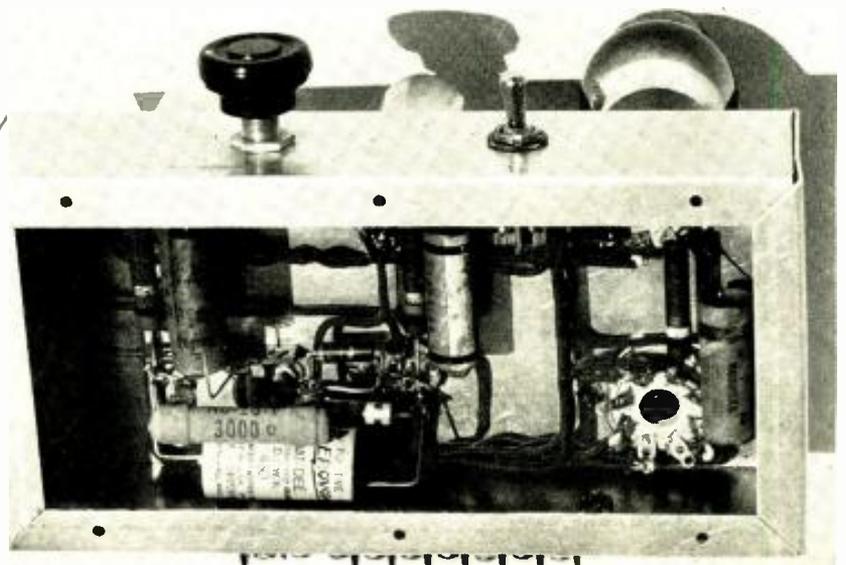Under chassis view of the voice-controlled break-in unit. No relays are required.



YOU CAN'T BEAT AIREX'S ...LOW, LOW PRICES!

ONLY \$169⁹⁵ GETS YOU THE

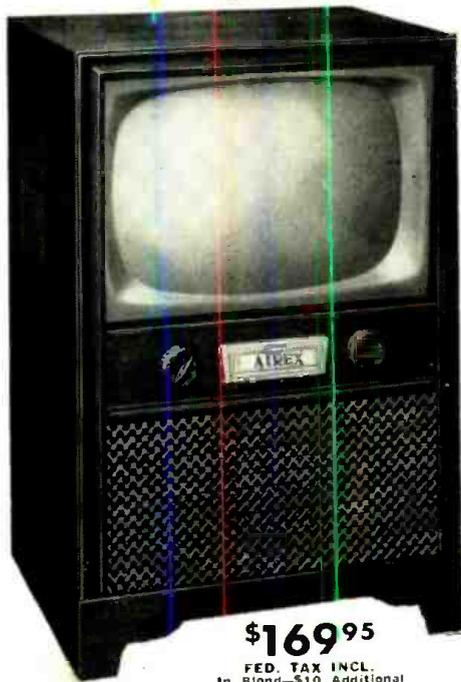

\$169⁹⁵

FED. TAX INCL.
In Blond—\$10 Additional

TOPS IN INTERMEDIATE AREA TV RECEPTION

Airex complete 21 inch
Console Model...Just
plug in and play...

You'll enjoy the sensational
clarity of picture quality and
the lovely tone of this specially
designed set. It gives you the
ultimate in reception in Metro-
politan and Suburban areas.
The finest of parts are used to
assure you trouble free oper-
ation.

SENSATIONAL FEATURES FOUND ONLY IN HIGH PRICE SETS

- Limiter ratio detector—FM Sound
- Separate high & low sync clippers
- Standard coil 4 circuit tuner
- Retrace Blanking Circuit
- 3 1/2 watts audio output
- Automatic Gain Control
- Built-in antenna
- 3 stage 6CB6 IF system
- Automatic frequency control
- Easily adaptable to UHF

• Beautiful Mahogany all wood cabinet

1 INCH TABLE MODEL—\$139.95 FED. TAX INCL.
21 INCH TABLE MODEL—\$159.95 FED. TAX INCL.

1 YEAR PICTURE TUBE WARRANTY. 3 MONTHS RMA GUAR. TUBES & PARTS

SPECIALS—SAVE UP TO 70%

- RCA ACCORDION CONE SPEAKER
7 inch, 21 oz. magnet, #MI 1382.
Removed from original equip. \$5.88
- AIR KING 6 TUBE SUPER-MET
Receiver chassis. 5" speaker. Complete with
loop antenna and all tubes. Removed from
original cabinet. \$11.95
- IRISH MAGNETIC TAPE—7" REEL
Fresh stock. 1250 ft. reel. \$1.99
- UHF SLUGS—ALL CHANNELS
For standard coil tuner. Send code initial of
present strip \$7.95
- GI 3 SPEED AUTOMATIC CHANGER
WEBSTER 3 SPEED—latest mdl., T.O. Cart. \$19.95
Automatic stop \$31.88
- GARRARD 3 SPEED Changer \$37.95
- MAHOGANY WOOD BASES for above changers
GI — \$3.89; Webster — \$4.95; Garrard — \$5.50
- FM-AM TUNER FOR 630 CHASSIS
Fits into well. Complete with tubes &
instructions \$29.95
- AM TUNER FOR 630 CHASSIS
Fits into well. Complete with tubes &
instructions \$14.95
- TUBES—UP TO 70% OFF LIST
All types receiving tubes. 90 day guar.
Write for free list.
- Eico #360 TV FM SWEEP GENERATOR
Fully wired. Less carrying case \$34.50

TV PICTURE TUBE SALE

Standard Brands. Fact. New.
Guar. 1 full year.

- 16" Tube \$19.95
- 17" Tube \$27.95
- 20" Tube \$34.95
- 21" Tube \$39.95
- 24" Tube \$79.95
- Ring and Sleeve for 24" \$7.50

TV Gold Plastic Masks

- 16" and 17" \$ 4.95
- 20" and 21" \$ 7.95
- 24" \$14.95

Bargain Cabinet Buy!

Beautiful mahogany console
Cabinet cut for 630
FA-2 Chassis. Complete
with mask, glass & tube
brackets. In Blond \$49⁹⁵
\$59.95

SEND FOR FREE NEW TV PARTS & HI-FI CATALOG

All merchandise is brand new, factory fresh & fully guaranteed. Mail & phone orders filled upon receipt of certified check or money order for \$25 as deposit on TV chassis. 20% on other items. Balance C.O.D., F.O.B. N. Y. Prices & specifications subject to change without notice. NO FED. TAXES TO PAY.


AIREX RADIO CORP.

SHOWROOM: 171 Washington St., N. Y. 7, N. Y.
Gramercy 7-9245
MAIL ORDER DEPT.: 400 Lafayette St., N. Y. 3

FREE DELIVERY* On 630 FA-2 Chassis
And Cabinets

3 MONTHS

RMA
GUAR.
ON ALL
PARTS

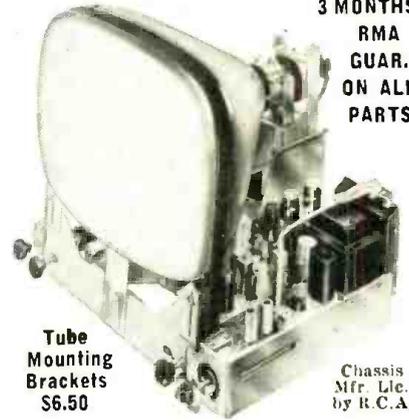

Tube
Mounting
Brackets
\$6.50

Chassis
Mfr. Lic.
by R. C. A.

New 1953 Co-Channel

630 FA-2 . . . with genuine

FM Armstrong sound system

Here is the most powerful fringe area
chassis on the market today . . . the one
TV engineers and servicemen are buying
for themselves. Clear, sharp, exceptional
reception up to 200 miles.

CHECK THESE EXCLUSIVE FEATURES

- 10 WATT push-pull audio output. Frequency range from 40 to 12,000 cycles • Standard Coil Cascode Tuner prevents radiation • Retrace Blanking Circuit allows you to raise the brightness without the annoying vertical retrace lines • Heavy duty front focus control • Automatic gain control potentiometer allows you to adjust the threshold sensitivity as low as 4 microvolts & still keep the full 4MC band width
- Improved sync amplifier • Improved automatic brightness control • Set aligned for 21.9 MC. New Ham band will not interfere • Improved fused high voltage power supply gives full 14.5 KV under load. Will handle all picture tubes up to 24 inch with full sweep • Improved video amplifier has a gain of 40 • All moulded plastic condensers give long life & trouble-free operation • Easily adapted to new UHF stations in 2 minutes by just changing a strip in the tuner • Extra heavy duty power transformer with large safety factor • 6CB6 tubes in Video IF to give full gain • Extra filtering in power supply for hum & ripple-free operation • Phono Connection & switch on chassis allows you to play your phonograph or tuner through the built-in 10 watt hi-fidelity amplifier • Extra heavy duty focus coil, which runs cool • Full focus cosine yoke.

THE ONLY CHASSIS WITH
PUSH-PULL AUDIO OUTPUT AT

\$169⁹⁵

Fed. Tax
Included

Less C.R. Tube
and Brackets


Complete with 12" ROLA Hi-Fi Speaker
Detailed Service Manual & Schematic—\$1

* Offer Limited to U. S. Only


OVER 100 BARGAIN-PRICED
CABINETS FOR TV AND
AUDIO INSTALLATIONS

Send for FREE folder and price list. Full
line table models, consoles, consolettes and TV-
Radio Phono combinations. Many styles, Mahog-
any, blonde, etc.

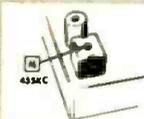
**NEW FEATURES MAKE
PHOTOFACT
more useful than ever
for faster, more profitable servicing**



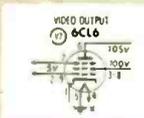
Alignment Frequencies
right on photos adjacent to adjustment number—to speed up adjustment.



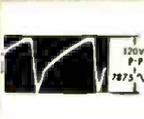Voltages on Schematics
to help speed voltage analysis for quick location of trouble.



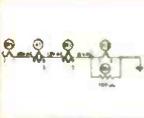Waveforms on Schematics
reproduced right on the diagram at vital points for rapid analysis by 'scope.



Series Filament Schematic
for quick reference when receiver employs series or series-parallel combination filament string.



Blank Pin or Locating Key
shown on each tube in placement chart (top view) to aid in substituting and replacing tubes without chassis removal.

NEW "EXTRAS"

- Tube types on chassis top photo views
- Tube failure check chart in TV Folders
- Fuse location on tube placement chart
- TV Trouble-Shooting Aids Chart
- Tips on TV servicing in the field
- Color code on transformer lead

NOW! GET THE PROOF FOR YOURSELF!

FREE

We'll send you a Free Photofact Folder on any receiver covered in Sets No. 101 and following

Learn for yourself—at our expense—how PHOTOFACT pays for itself by earning bigger profits for you! Select any Folder appearing in PHOTOFACT Sets Nos. 101 and following, from the PF Index. (If you haven't a copy, see your distributor.) When you write for your Free Folder, be sure to state Photofact Set and Folder Number as shown in the Index (offer limited to Folders in sets subsequent to No. 101). Get your Free Folder now. Examine, use, compare—see why PHOTOFACT belongs in your shop!

HOWARD W. SAMS & CO., INC.
2203 E. 46th St., Indianapolis 5, Ind.

HOWARD W. SAMS & CO., INC.

WATCH THOSE HEATER VOLTAGE MEASUREMENTS

By JOHN K. FRIEBORN

Avoid expensive meter burnouts by observing a few simple precautions when making voltage measurements in TV sets.

CAN you burn out a meter measuring the heater voltage of a 6.3-volt tube using the 10-volt a.c. range of the meter? You can, in certain television receivers, unless you take the proper precautions. Probably you don't actually find it necessary to measure the heater voltages of individual tubes very often, so when you do you may not be prepared for some of the surprises which can occur.

Most television receivers have parallel heaters with one side of each heater grounded, so that the heater voltages can be measured with the common lead of the meter connected to the chassis, just as it usually is in measurements of d.c. voltages on plate, screen, etc. Even if, through unfamiliarity with the receiver or carelessness, you measure the voltage between the chassis and the grounded heater terminal, or the heater ground point turns out to be the transformer winding center-tap, it won't do any harm and you'll soon catch on.

So where's the risk? It is in

measuring between the chassis and one side of a heater which has a high d.c. voltage with respect to ground. Well, you say, of course you know better than to measure the heater voltage of a power supply rectifier or damper tube that way; is that all? It isn't.

Probably you have noticed that many television receivers of the past couple of years have the cathodes of one or more tubes, other than rectifiers and dampers, positive with respect to the chassis a hundred volts or more. Many of these receivers have the heaters of the same tubes at about the same d.c. potential. Two typical examples are *Motorola Chassis TS-236* and *Crosley Chassis 356-1*, partial schematics of which are shown in Figs. 1 and 2, respectively. Other manufacturers who have used similar arrangements are: *Bendix, Hoffman, Magnavox, RCA Victor, and Raytheon*. The tubes involved are: the audio output (most often), the sound i.f. (sometimes), and other tubes such as

Fig. 1. Partial diagram of Motorola TS-236.

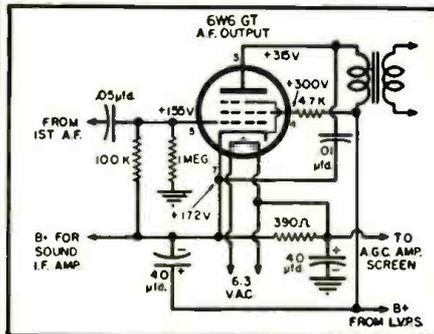


Fig. 2. Crosley's 356-1. partial schematic.


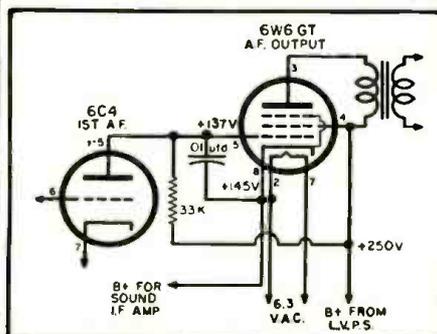


Fig. 3. Partial schematic, Sylvania 1-502-1.

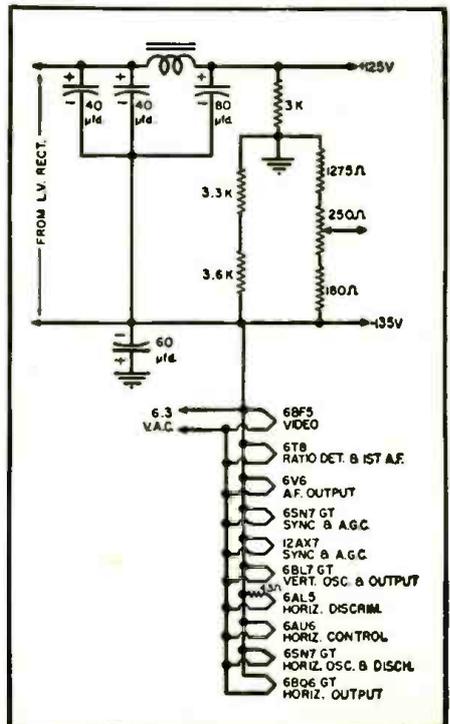

12,080 HOURS OF ENGINEERING TO BRING YOU THE

NEW... AMAZING precise OSCILLOSCOPE

(IN KIT AND WIRED FORM)

THE OSCILLOSCOPE YOU'VE BEEN SEEKING . . . NO OTHER OSCILLOSCOPE AT ANY PRICE—HIGH OR LOW — WITH THESE DESIRABLE FEATURES — IN BOTH KIT AND WIRED FORM:



MODEL 630

RF-AF-TV AND MARKER GENERATOR. For the first time in the history of the industry . . . SO MUCH FOR SO LITTLE. 110 MC on fundamentals, 330 MC on harmonics; Pre-tuned RF (within 1%) head†; AF from 20 to 20,000 cycles; variable ♂ and Ext. Mod.; Cathode Follower and Constant Z output; Stepping attenuator; Speech Amp.; Xtal Marker with Amp. control; RF and AF Standby; Wien Bridge AF; Colpitts RF; illuminated Drum Dials; Coax output; Separately tuned coils; Filtered AC; Vernier tuning; Separate RF; Shielded; 8" x 11" x 5"; Etched panel. Model 630K †Model 630KA . . . \$38.95 (pre-assembled head) **\$33.95** Model 630W . . . \$53.95 (Factory wired)




PRECISE MODEL 300

VERTICAL—Vertical-flat (3db) DC through 5 megacycles with sensitivity of greater than 10 millivolts push-pull (3.94 Millivolts/cm); Constant Resistance; Push-Pull input immediately converted to single-ended normal or reverse phase by shorting bar at inputs 1 and 2; Frequency compensated vertical stepping attenuator selects AC or DC inputs; Push-pull DC amplifiers from input through output; Internal electronic mixing through inputs 1 and 2; five-way binding posts.
POSITIONING—Bridge type positioning on vertical and horizontal does not vary tube characteristics.
HORIZONTAL—Frequency compensated stepping attenuator in horizontal amplifier; Push-pull Horizontal out.
BLANKING—Internal (return trace blanked), external (return trace not blanked); 60 cycle or 120 cycle Blanking through Blanking amplifier circuit.
SYNCHRONIZATION—External, Internal Positive, Internal Negative, Internal 60 cycle or Internal 120 cycle synchronization.
SWEEP RATE—Driven or non-driven linear sweeps; from 1 cycle to 80KC in five ranges (1-10 cycles uses external C circuit); Trigger potentiometer.
MAGNIFIER—Electronic magnifier and magnifier positioner allows any part of a signal to be magnified up to ten times (equivalent to 70 inches of horizontal deflection).
CALIBRATION—Internal square wave calibrator and potentiometer for using oscilloscope as a VTVM on Peak to Peak measurements.
CALIBRATION SCREEN—Edge-illuminated scale and gratule may be turned on or off; filtered screen.
OUTPUTS ON FRONT PANEL—Plus Gate output; Sawtooth output; 60 cycle phasing output; 60 cycle unphased output; Calibration output.
FOCUSING—Astigmatism, focus and intensity control.
CRT—NEW 7" Tube, normally supplied is medium persistence type 7VP1, or 7JP1 may also be used (oscilloscope green trace)—high persistence types available at additional cost.
DIRECT—Deflection Plates available from rear of cabinet.
INTENSITY MODULATION—2 modulation through modulation amplifier.
GENERAL—Low loss components; Over-designed fused power supply for additional circuitry; Deeply etched aluminum panel; New parts from original manufacturers—(NO SURPLUS); Steel cabinet; 11" x 14" x 17"; complete with instruction book and all components; Accessories: Model 912T(MM) Demodulator Probe and Model 960 Capacity Attenuator Probe available at extra cost—please see specifications on following pages. There are many additional features and circuits in kit form, which may be added to the Model 300. Please write us for descriptive literature. **\$94.95**
300K—kit form . . . **\$199.50**
300W—factory wired . . . **\$199.50**



MODEL 635

UNIVERSAL AF SINE, SQUARE AND PULSE GENERATOR. For accurate testing audio and video circuits; 1% Ceramic precision resistors; Wien Bridge; variable Z and cathode-follower output; minimum overshoot and roundoff through 100,000 cycles; sine waves through 200 KC. Model 635K Model 635W . . . \$52.50 (Factory wired) **\$33.50**

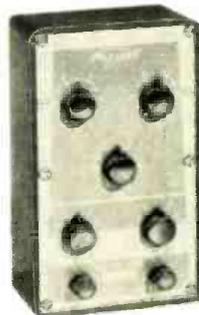

MODEL 468

PRECISE AGAIN LEADS THE FIELD with its New Low-Priced Resistance Decade Box. Ideal for specialized service work. Compact in size for Bench Drawers and Tool Boxes. Engineered with the customary Precision Accuracy and Dependability.


5 Separate Switches, 11 Positions on Each; plus or minus better than 1%; for Extreme Accuracy; Readings from 10 OHM to 1,111,110 OHM in 5 Decades. Deeply etched Aluminum Panel; Rugged Construction; Complete with famous Precision Simplified Construction Manual. 3" x 6 1/4" x 2".

468K . . . kit form . . . **\$18.95**
468W . . . factory wired . . . **\$24.95**
478K—CAPACITY DECADE BOX (Not illus.) kit only **\$18.95**
478W—CAPACITY DECADE BOX (Not illus.) factory wired . . . **\$24.95**



MODEL 909

VACUUM TUBE VOLTMETER. 1% Ceramic precision Resistors; Coax DC connector; FM zero alignment scale; burn-out proof circuit. Rugged oversize 4 1/2" meter. Model 909K Model 909W . . . **\$44.98** (Factory wired) **\$25.98**

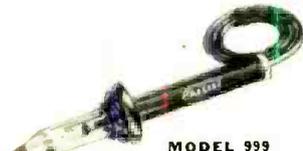

MODEL 999

HIGH VOLTAGE PROBE. Designed for high voltage measurements with special emphasis on Safety, Operational Simplicity and Rugged Construction. Exclusive Features: MULTIPLE INSULATION. MECHANICALLY SHOCKPROOF; CHANGEABLE TIPS; SWIVEL connection. Odds are billions of billions to 1 that no breakdown will occur! **\$6.98**
INTERCHANGEABLE RESISTORS . . . Wired Only



MODEL 907

OELUXE VACUUM TUBE VOLTMETER. Another PRECISE First! Vertical or Horizontal construction. GIGANTIC 7 1/2" meter movement; all the unusual values and features of Model 909 in a really OELUXE version. Model 907K Model 907W . . . **\$57.98** (Factory wired) **\$38.98**

MODEL 912

RF PROBE. LOWEST PRICED. factory wired. Probe in the industry. Individually calibrated at 75 MC for accuracy, impedance and shunt capacity. Wired Only. **\$4.25**

MODEL 960 CAPACITY ATTENUATOR PROBE. Reduces input C. and loading effects of an oscilloscope by 10 to 1. Adjustable for any scope. Lowest priced in the field, but still using highest quality components. Wired Only. **\$5.95**



MODEL 610

RF SIGNAL GENERATOR. The lowest priced signal generator in the field offering:—Same RF head as Model 630; 110 MC on fundamentals; 330 MC on harmonics; 60 and 400 cycle AF; Cathode-follower output; Ext. Mod.; Speech Amp.; Individually tuned coils. Model 610K Model 610KA . . . **\$28.95** (pre-assembled head) **\$23.95** Model 610W . . . **\$39.95** (wired)

SEND FOR COMPLETE CATALOG

Send 20% deposit with order, balance C.O.D., or, check or money order in advance.

TEE-VEE Supply Co.

3211-13 Washington Street
Jamaica Plain 30, Mass.

TV Receiver Sensitivity Measurements made Simple with

The New "SensiMeter" *
 Portable
 ... a "must" in fringe areas



Net \$129.50
 *Pat. Applied For


Approved by leading television manufacturers!

Consult your Jobber or write for further information

- * Takes the guesswork out of TV service
- * Checks receiver from antenna terminals to picture tube
- * Microvolt scale is divided into 3 sections as a guide for the servicemen
- * Sensitivity testing is accepted by servicemen as the best method of determining the cause of bad pictures

SI SERVICE INSTRUMENTS COMPANY
 422 South Dearborn Street, Chicago 5, Illinois

WANT THE BEST IN CAPACITORS?

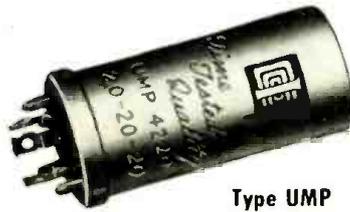

Type UMP

• Many, many notable advances in the art of capacitor design and manufacture have been made by the ILLINOIS CONDENSER COMPANY. As an example, ILLINOIS CONDENSER COMPANY has recently been awarded a patent on their unique and exclusive molded capacitor construction as featured in the UMP types.

For almost two decades, ILLINOIS CONDENSER COMPANY has been building quality capacitors and regular users include most all of the largest manufacturers of TV and radio sets. Their names literally comprise the "blue book" of electronics.

To meet the ever increasing demand for ILLINOIS electrolytic capacitors, ILLINOIS CONDENSER COMPANY has built new plants and greatly increased production. Why don't you, too, discover why ILLINOIS capacitors are "first choice" of so many!

Write for Catalog!



ILLINOIS CONDENSER CO.
 1616 NORTH THROOP STREET • CHICAGO 22, ILL.

a.g.c. keyers (in a few cases). Some Sylvania models, such as Chassis 1-502-1, have the heaters of about half of the tubes more than a hundred volts *negative* with respect to the chassis. (See Fig. 3.)

Measuring between the chassis and either side of the heater in the cases mentioned will put the high d.c. voltage across a meter which is set for a low a.c. voltage. Some meters would not be harmed; would yours?

One way to avoid the risk is to make all heater voltage measurements in unfamiliar receivers between the heater terminals on the tube sockets. That does not apply to series heater arrangements; they present a different type of danger, as you probably know. An open heater of a series string has almost the entire a.c. line voltage between its terminals when the circuit is completed by a high-resistance voltmeter.

-30-

RECEIVER AS MODULATOR

By George R. Anglado

A BROADCAST receiver can be used for modulating a flea-power transmitter when a modulator is unavailable. The diagram shows how the output stages of a broadcast set are used for this purpose. Our receiver had a phono jack which served for connecting the microphone. The s.p.d.t. switch shown in the diagram is part of the "radio-phonograph" switch in some models, while others do not have it and require the radio to be tuned to a quiet channel for using the phonograph. If the switch is added, the leads and switch should be shielded and the switch mounted as close as possible to the first a.f. tube.

Although a carbon microphone may be used, with a suitable battery and transformer as in the inset diagram, crystal mikes have been used successfully in the phono input.

A heavy-duty universal plate-to-voice-coil transformer is used to couple the audio to the transmitter. Its secondary is connected across the secondary of the receiver output transformer, and its primary is connected in series with the transmitter "B-plus." The taps are chosen on both windings to match the output impedance of the receiver and the estimated plate impedance of the transmitter final tube. An approximate match is good enough. The reason for the s.p.d.t. switch is obvious. The power of this "modulator" depends, of course, on the power output of the receiver audio section.


-30-

"SOMETHING FABULOUSLY BEAUTIFUL ...

... Amazed by new purity of sound... clarity... clean definition!"

says noted Record Reviewer

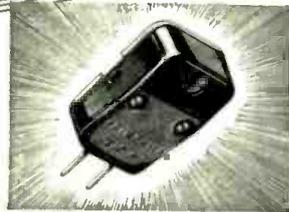FAIRCHILD
 SERIES 215
HIGH COMPLIANCE
 Diamond Cartridge



NOW ONLY \$37.50
 WITH FINEST DIAMOND STYLUS FOR 33, 45 OR 78 RPM RECORDS

First to achieve near-perfect lateral compliance—freedom of stylus to yield to rapid deflections of sensitive microgroove recordings—the amazing new Fairchild Series 215 provides all these exciting improvements:


- ★ New shades of tone color from fine recordings! ★ New clear timbre in high volume piano chords! ★ Rich low-frequency tones never previously heard! ★ Needle talk, record hiss, base concentration caused by arm resonance—reduced to a new low low! ★ Stylus wear vastly reduced, record quality preserved! ★ And above all—TRACKING DISTORTION ELIMINATED!

ORDER FROM YOUR AUDIO DEALER or Mail Coupon for FREE "HI-FI Facts" folder

Fairchild Recording Equipment Corp.
 8th Ave. & 154th St., Whitestone, L.I., N.Y.
 Please mail folder "Hi-Fi Facts" to:


Name _____
 Address _____
 City _____ State _____

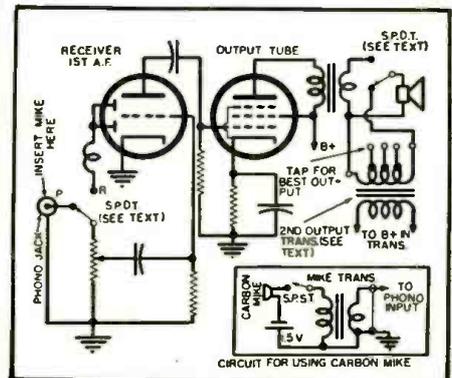Using a b.c. set to modulate transmitter.




RADIO & TELEVISION NEWS


paul klipsch-designed

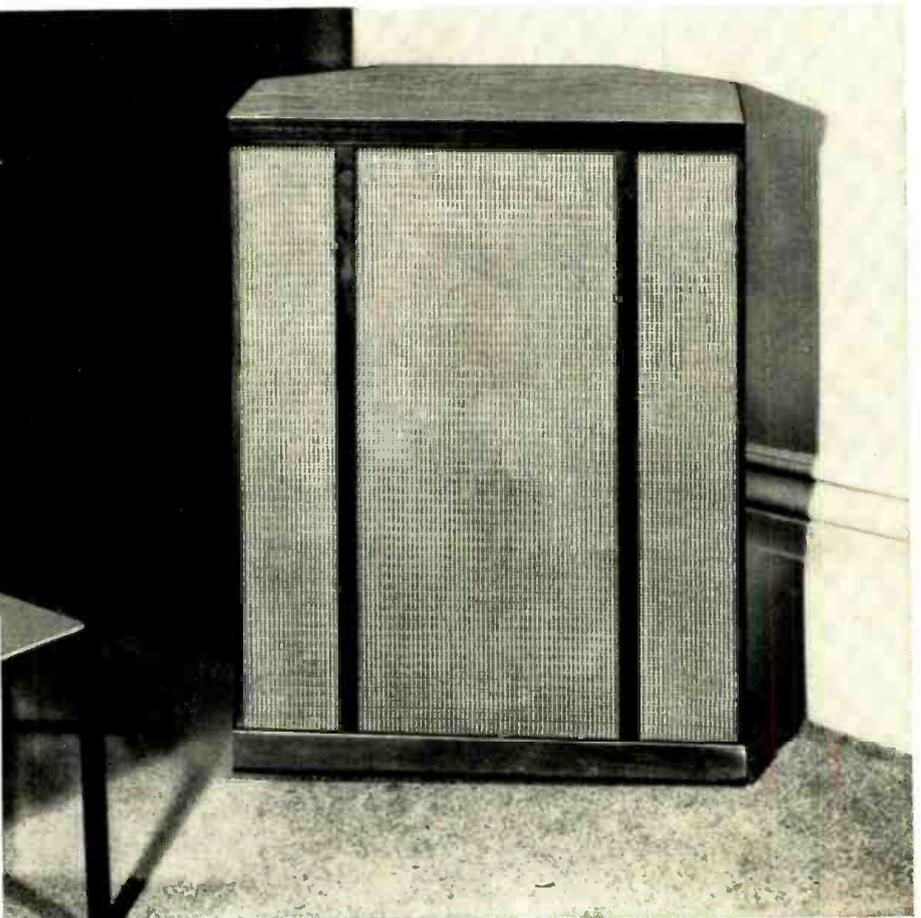

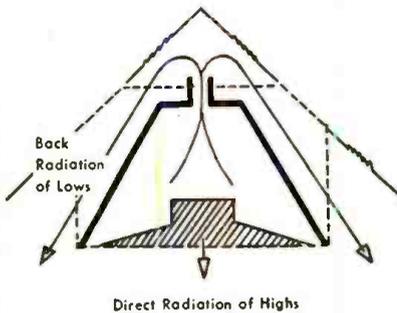**SO MUCH VALUE...
...AT SO LITTLE COST**



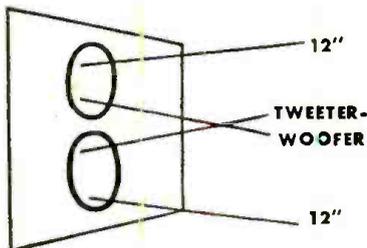- Large enclosure performance within minimum area achieved through principle of "backloading", which increases path length and provides better reproduction of lows.
- Direct radiation of high frequencies cuts out "Masking".



- Two-way system performance. So flexible in design so as to provide you wide latitude in determining your listening requirements. Removable panel allows for a variety of speaker combinations. For example, in the 12" Klipsch you can install a single 12", two 12" speakers or a tweeter-woofer combination.

**THE
REBEL IV
by
CABINART**

Attractively styled to blend with any interior decor, the Klipsch Rebel IV by Cabinart comes in Limed Oak, Honey Walnut, French Mahogany and Black Lacquer.

**\$69.00 Net for 12" model
\$87.00 Net for 15" model**

"popularly priced!"

AVAILABLE AS KITS IN

BIRCH, UNFINISHED

Build your own Klipsch and save money—identical in acoustic design to assembled units and easily put together with a minimum of tools.

\$36.00 Net for 12" model

\$42.00 Net for 15" model

**SEE IT AND HEAR IT AT YOUR LOCAL PARTS DISTRIBUTOR.
WRITE RN9 FOR COMPLETE TECHNICAL DATA.**



**MANUFACTURED BY
G & H WOOD PRODUCTS CO.**
75 NORTH 11th STREET, BROOKLYN 11, N.Y.

Pioneers in radio furniture for high fidelity equipment

LET THESE
Professional
SERVICE METHODS
Boost Your
Earning Power!



Ghirardi's new 1-vol. training course helps you handle jobs more efficiently—in less time!

COMPLETELY NEW!
Radio and TV Receiver
TROUBLE SHOOTING AND REPAIR

820 pages,
417 illustrations, only \$6.75

For the beginner, this NEW Ghirardi book is a complete, up-to-the-minute training course in servicing by modern professional methods. For experienced servicemen, it is a quick way to brush up on specific types of work, to develop improved troubleshooting techniques or to find fast answers to puzzling problems.

Components, their troubles, their replacement and even their repair are fully analyzed. Modern testing methods including both "static" and "dynamic" tests using signal tracing and injection techniques are carefully explained. You learn how to set up an efficient service procedure and to interpret data fast and accurately. Four big chapters show how to handle TV, FM and AM alignment jobs in less time and with a minimum of equipment. Dozens of unique new "step-by-step" charts explain complicated servicing details almost at a glance.

THE HOW-TO-DO-IT
GUIDE TO M-o-d-e-r-n
SERVICE METHODS!

Nowhere else will you find troubleshooting procedure and servicing operations explained so clearly or so understandably! Dozens of service "tips" are equally helpful.

You learn to analyze many television troubles without laborious testing.

You learn what to do about those puzzling intermittent troubles; how to service difficult 3-way portable filament circuits; how to handle ac/dc and transformerless power supply heaters professionally; how to remedy fading and propagation troubles . . . and many more.

No really practical service procedure has been omitted—and all are explained so clearly you can't fail to understand them! Use coupon for 10-day examination.



LICENSE EXAMS
Won't "Stump"
You!

This is the ideal book to help you pass servicing licensing examinations now pending in many places.

Remember: Ghirardi books are more widely used for school, military and home study training than any others of their type! This new book is the latest, most helpful of all for boosting your service profit!

MAIL ORDER! 10-DAY EXAMINATION

Dept. RN-93, RINEHART BOOKS, INC.,
Technical Division,
232 Madison Avenue, New York 16, N. Y.

Send Ghirardi's Radio & TV Receiver TROUBLE-SHOOTING AND REPAIR for 10-day examination. If book is what I want, I will then promptly remit \$6.75 plus a few cents postage or return book to you postpaid.

Name

Address

City, Zone, State

Employers' Name & Address

OUTSIDE U.S.A.—Price \$7.25, cash only.
Same 10-day return privilege with money refunded.

SERVICE HINTS ON ZENITH TV SETS

27F20, 28F20, 28F21, 28F22, 28F23, 28F25, & 29G20

Insufficient width.

This condition is most prevalent in low line voltage areas and may be particularly noticed on 12-inch picture tubes.


To increase the width, connect a .047 μ f., 600 volt condenser across the terminals of the width control. A higher capacity unit (up to .1 μ f.) may be required on some receivers.

Inverted picture.

This condition is usually caused by a defective blocking oscillator transformer (T_1). Also check condenser, C_{12} , the .047 μ f. unit in the plate circuit of the blocking oscillator. See diagram below. Replace with a similar type of condenser if defective.

Poor vertical linearity.

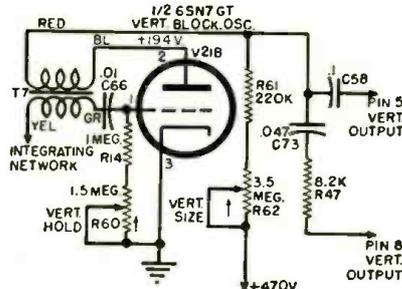This condition may or may not be accompanied by foldover. If the vertical size control, R_{62} , is connected to the 340 volt "B+" line



(as in early production receivers), remove it from this line and connect it to the 470 volt "B+" line through a 47,000 ohm, 1/2 watt resistor. The junction of the size control and the 47,000 ohm resistor should be bypassed to ground through a 10 μ f., 475 volt electrolytic condenser. See diagram for original circuit.

Foldover and distortion at top of picture.

When this condition occurs, check the 20 μ f. electrolytic condenser (C_{67}) through which the primary of the vertical output transformer returns to ground.

Oscillator frequency shifts.

This may be caused by fine shavings which break loose from the oscillator adjustment screw, and lodge in a channel strip of the tuner. These shavings cause a change in the strip adjustment condenser when the turret is switched from channel to channel. To correct this condition, remove

the adjustment screw and blow out the excessive shavings (with an air gun, etc.). Crimp the two ears on the *Tinnerman* clip so that it will hold the slug shaft securely. Re-insert the slug, and adjust for proper tuning.

Brightness control has little or no effect.

This may occur when the 6200 ohm, second video amplifier plate load resistor, R_{10} , increases in resistance. If this has occurred, replace this resistor with the proper value unit.

When replacing this resistor, mount it approximately one-inch from the 3000 ohm wire-wound resistor (R_{10} , connected to the horizontal deflection coils) in order to obtain better heat dissipation.

Also check the 6AU6 sync amplifier plate bypass condenser, C_{62} . This condenser should be 220 μ f., 600 volts.


Sound from speaker affects picture.

This condition is usually caused by a microphonic 6AC7 reactance tube. It may also be caused by a defective 6J6 r.f. oscillator tube. Check by replacing these tubes.

Horizontal instability.

This may be caused by the following:

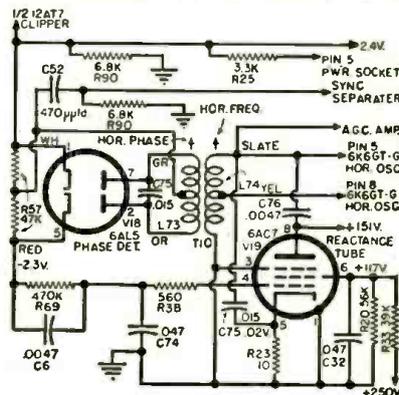
1. Drift in the .015 μ f. condenser, C_{18} , connected between pin 5 of the 6AC7 reactance tube and inductance, L_{11} . If defective, replace this unit with a *Sprague* .015 μ f. condenser, *Zenith* part #22-1850.
2. Change in the value of the 56,000 ohm, 1/2 watt resistor, R_{24} , between pin 6 of the 6AC7 reactance tube and ground.
3. Change in the value of the



3300 ohm, 1/2 watt resistor, R_{28} , between pin 1 of the 6AL5 phase detector tube and pin 5 of the power socket.

THE Original

WRENCH WITH THE SCREWDRIVER ACTION!

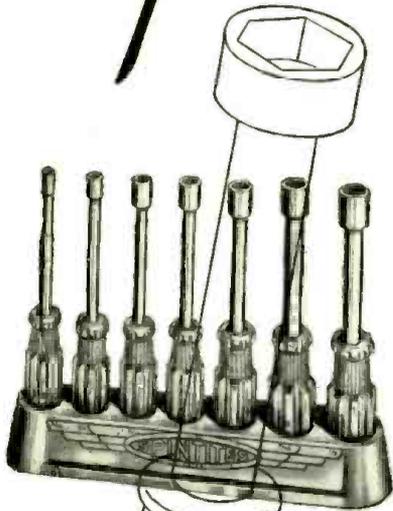

SPINTITE

REG. U. S. PAT. OFFICE

120 STYLES and SIZES

for

- ASSEMBLY WORK
- REPAIR WORK
- RADIO
- TELEVISION
- INDUSTRIAL
- AIRCRAFT




STEVENS WALDEN, Inc.
WORCESTER 4, MASS.

4. Change in the value of the 6800 ohm, ½ watt resistor, R_{50} , between pin 1 of the phase detector tube and ground. See diagram (page 138).

23G22, 23G23, 23G24, 24G22, 24G23, 24G24, 24G25, & 24G26

To improve fringe-area reception.

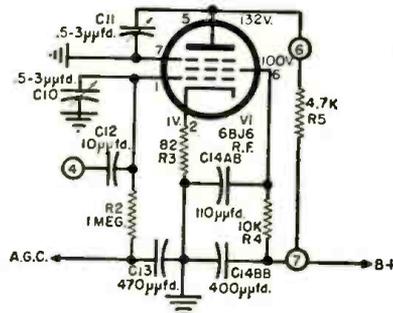- Considerable improvement in reducing snow in fringe areas can be made by the following modifications in the r.f. amplifier stage:
1. Replace the 6BJ6 tube with a 6AK5. (No socket changes are necessary.)
 2. Replace the 10,000 ohm screen resistor, R_1 , with a 27,000 ohm, ½ watt unit. See diagram.



3. Parallel a 2.5 μ fd. ceramic condenser (Zenith part #22-1891) with the plate tuning condenser, C_{11} .
4. Tune in a weak signal, and adjust the plate condenser, C_{11} , for the best picture with the least snow.

Overheating of the 25Z6 rectifier tube.

When this condition occurs, check the 50 μ fd., 500 volt ceramic condenser, C_{31} , in the plate circuit of the 12AT7 intercarrier sound amplifier.

The Zenith replacement for this condenser is part #22-1761, which should have a green durez coating. Condensers with a brown durez coating should not be used in this circuit.

Instability in the sound channel.

If the sound channel breaks into oscillation when adjusted, do the following:

1. Replace the sound take-off coil, L_{75} , at pin 1 (the plate) of the 12AU7 video amplifier, with a Zenith S-16854 assembly.
2. Replace the 10 μ fd. condenser, C_{55} , in the grid circuit (pin 2) of the 12AT7 intercarrier sound amplifier with a .01 μ fd., 500-volt condenser.
3. Add a 470 ohm, ½ watt resistor between the black lead and the chassis.


Horizontal instability.

This condition may be caused by one of the following:

1. An open or leaky 100 μ fd. condenser, C_{65} , at the cathode of the 6AL5 phase detector tube. When this condenser is defective, a positive voltage

appears at the plate (pin 7) of the phase detector, instead of the normal negative 8 volts.

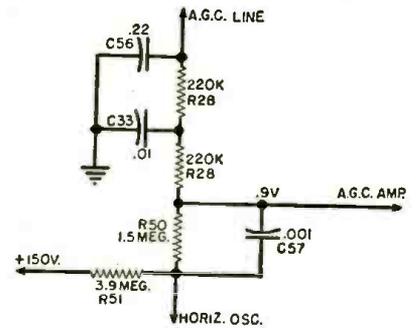2. Loose rivets on the "Phonevision" connector plug. Solder the shorting bars to the rivets to correct this.
3. A shorted 470 μ fd. condenser, C_{65} , at the plate (pin 5) of the 6SN7 horizontal control tube.
4. Overheated 56,000 ohm resistors (R_{15}) in the a.f.c. return (from the horizontal output transformer connection 1, to "Phonevision" socket). These resistors are normally ½ watt; however, use 1 watt resistors as replacements.
5. If the receiver cannot be adjusted to snap into horizontal sync when switching from




channel to channel, replace the .001 μ fd. condenser, C_{55} , in the a.g.c. circuit with a .047 μ fd., 500 volt ceramic unit. See diagram.

22H20, 23H22Z, 24H20, & 24H21

Poor vertical sync in weak signal areas.

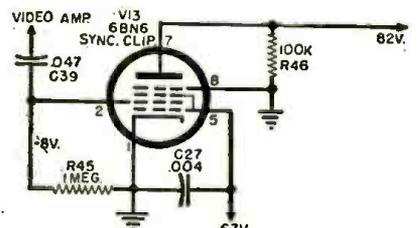The vertical sync may be improved by lowering the value of resistor, R_{15} , in the grid circuit of



the sync clipper (6BN6) from its normal 1 megohm value. Values as low as 10,000 ohms may be used. Too great a reduction of this resistance may introduce horizontal distortion into the picture on some signals.

Washed-out picture.

If this condition persists after all normal adjustments have been made, the cause may be low detector output due to a defective germanium crystal. Test the crystal with an ohmmeter for front-to-back resistance ratio (with the crystal disconnected). The resistance in one direction should be lower than 400 ohms, and at least 25 times this value, or 10,000 ohms, in the other direction. Any ratio less than 1:25 indicates a below-standard crystal.

START ON THE ROAD TO SUCCESS

Study the RCA TV Servicing Course in your spare time

ARE YOU SATISFIED with the position you now hold? Do you feel you're worth more money? Are you pleased with yourself, your work, your associates . . . and your future? What does the next year hold for you . . . and the year after that?

Are you content merely to plod along through the best years of your life . . . or do you want to get into more pleasant work . . . hold a well-paid job . . . perhaps establish your own business?

If you are looking for a REAL opportunity . . . If you want to GROW with a GROWING INDUSTRY . . . If you want to grasp the success that should be yours, *then we say to you, study TV Servicing.*

Everyone knows that Television is the fastest growing industry today. Opportunities are going begging for men who have the training and ability to grasp them. *Now is the time to start on the road to success in TV Servicing.*

Study at Home in your spare time

The RCA Institutes Home Study Course in TV Servicing is easy to learn. You progress rapidly, step by step, as you learn the procedure of servicing and trouble-shooting TV receivers and installing TV antennas. Hundreds of pictures and diagrams help you understand the how-it-works information and the how-to-do-it techniques.


A Service of Radio Corporation of America

The RCA Institutes TV Servicing course was written and planned by instructors with years of specialized experience in training men. You get up-to-the-minute information, too, because you study right at the source of the latest developments in Television. Your lessons are carefully examined and accurately graded by competent teachers who are interested in helping YOU to succeed.

RCA Institutes is licensed by the University of the State of New York . . . an affiliate member of the American Society for Engineering Education . . . approved by leading Radio-Television Service Organizations.

It costs so little to gain so much

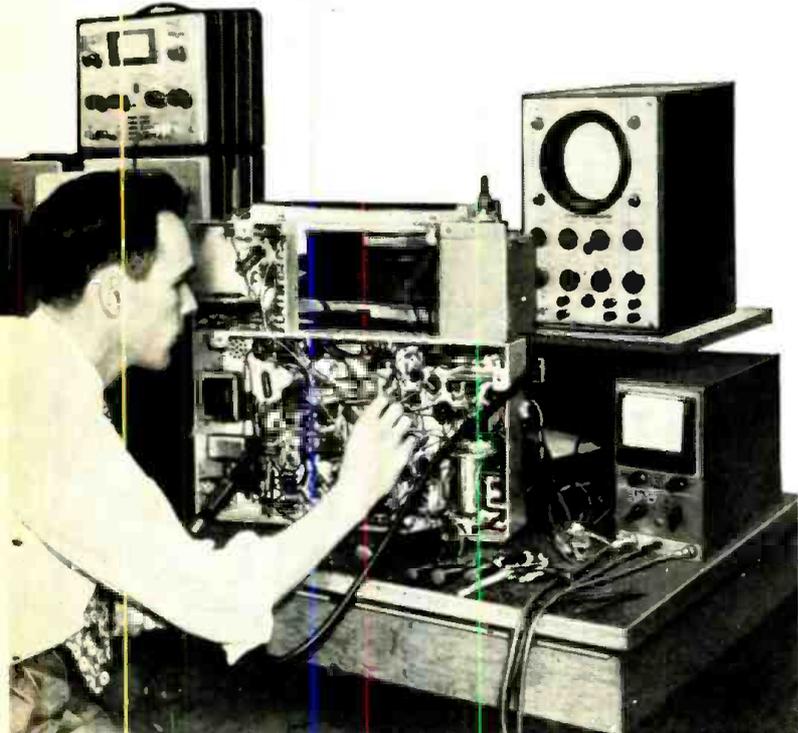RCA Institutes makes it easy for you to take advantage of the big opportunities in TV Servicing. The cost of the TV Servicing Home Study Course has been cut to a minimum. You pay for the course on a pay-as-you-learn unit lesson basis. *No other home study course in TV Servicing offers so much for so little cost to you.*



RCA Institutes conducts a resident school in New York City offering day and evening courses in Radio and TV Servicing, Radio Code and Radio Operating, Radio Broadcasting, Advanced Technology. *Write for free catalog on resident courses.*



RCA INSTITUTES, INC.
A SERVICE OF RADIO CORPORATION of AMERICA
350 WEST FOURTH STREET, NEW YORK 14, N. Y.

SEND FOR FREE BOOKLET—Mail the coupon—today. Get complete information on the RCA INSTITUTES Home Study Course in Television Servicing. Booklet gives you a general outline of the course by units. See how this practical home study course trains you quickly, easily. Mail coupon in envelope or paste on postal card.



MAIL COUPON NOW!

RCA INSTITUTES, INC., Home Study Dept. RN953
350 West Fourth Street, New York 14, N. Y.

Without obligation on my part, please send me copy of booklet "RCA INSTITUTES Home Study Course in TELEVISION SERVICING." (No salesman will call.)

Name _____ (please print)

Address _____

City _____ Zone _____ State _____

for ALIGNING UHF FRONT ENDS

A LOW COST UHF SWEEP GENERATOR



Here are the essential specifications:

- Frequency Range... 450 to 900 mc (Single Range)
 - Sweep Width... 0 to at least 30 mc over entire band
 - Output Voltages... 0.01 to 1.0 volts into a 75 ohm load
- A balun is available for 300 ohm balanced load

\$265

f.o.b. New London, Connecticut

At last the service man gets a break! Most laboratory instruments are priced so high that anyone without a big company backing him can only dream of them.

Not so New London's Model 130! Combining laboratory precision with practical design, the 130 is priced so you can afford it.

Moreover, the 130 is easy to use. Frequency is in a single range. A minimum of controls are provided. And the return sweep is blanked, thus providing a zero level baseline.

for further details or to place your order write to

New London Instrument Company
Dept. C
NEW LONDON, CONNECTICUT

ADCO JOE SAYS:

Here are just a few of our 10,000 Bargains
SAVE MONEY—ORDER BY MAIL!

SELENIUM RECTIFIERS

350 ma. — \$1.75
500 ma. — \$2.02

Additional 10% discount on lots of 12 assorted.

PHILCO FLYBACK NO. 32 - 8509

Reg. price \$11.10. OUR SPECIAL PRICE \$3.75

PHONO-XTAL

Most popular of all crystal cartridge replacements. 3V. output.

\$1.95 each in lots of 3

TV TUBE SOCKETS with leads 45c	TV LINE CORDS 29c	SPRAY KLEEN Contact Cleaners 99c
--------------------------------	-------------------	----------------------------------

6"x9" or 7" PM auto type replacement speaker
\$2.50

TV PICTURE TUBE BRITENER
\$1.30 ea.

Vertical output transformer—3 wire, universal type... \$1.49


10" & 12" FLYBACK TRANSFORMER Special—\$1.75

20% deposit on all orders—Bal. C.O.D. All Shipments F.O.B. Baltimore.

AMERICAN DISTRIBUTING COMPANY

1200 N. FULTON AVE. — BALTIMORE 17, MD.

PREMAX Mobile Mountings

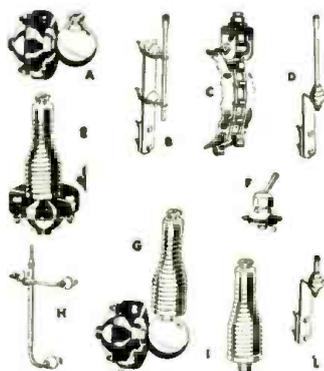

Premax Mobile Mountings withstand stress and shock under all conditions. A complete line with collet-type lock which fits any 1/4" rod or, by removing it, the mounting fits any 3/8" 24-thread rod. Send for special bulletin and prices.

PREMAX PRODUCTS
DIVISION CHISHOLM-RYDER CO., INC.

5304 HIGHLAND AVE., NIAGARA FALLS, N. Y.

19K20, 19K22, 19K23, & 21K20

Ringing or white stripes in picture.


This condition can usually be corrected by re-adjusting the horizontal drive control, or by replacing the 6CD6 horizontal output tube.

In some cases it may be necessary to dress the peaking coil in the second video amplifier plate circuit, L_{22} , and the contrast and picture control leads as far from the sweep transformer cage as possible.

Also, insert a parallel network consisting of a 1000 ohm, 1/2 watt resistor, a .0047 μ fd., 400 volt condenser, and a peaking coil (Zenith part No. S-17911) in series with the red-white lead of the sweep transformer.

Airplane flutter.

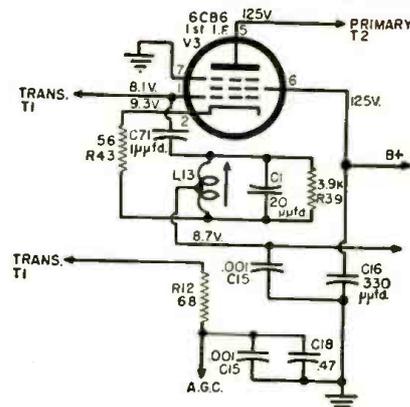
Rapid changes in signal level may be caused by signal fading due to



airplane reflections. To improve the a.g.c. action of the receiver to eliminate this flutter, replace the .47 μ fd. condenser, C_{18} (see diagram), with a .047 μ fd., 600-volt molded unit. In addition, make the change noted below under "Horizontal pull."

Picture flicker.

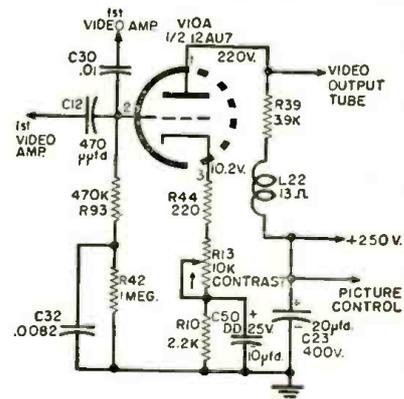This may be caused by fluctuations in line voltage, and may be corrected by increasing the second video plate decoupling electrolytic



condenser, C_{23} , from 20 to 100 μ fd. (See diagram.)

Horizontal pull on top of raster.

This may at times occur only with certain types of transmitted sig-

MAIL YOUR ORDER TODAY—OLSON WILL RUSH IT RIGHT AWAY!

24 DRAWERS
12 1/2" High, 12 1/2" Wide,
6" Deep
72 COMPARTMENTS
STOCK NO. X-334
SINGLE
EA. \$7.95
LOTS OF 3, EACH. **\$6.95**

BRAND NEW ALL-METAL PARTS CHESTS

Olson gives you a chance to load up on these famous make Paris Chests for less than HALF THE REGULAR PRICE. Case is heavy, welded Dura Steel, strong and sturdy with handsome grey enamel finish. Drawers are ALL-ALUMINUM—1 1/4" deep, 2 1/2" wide, 5 1/2" long. Each drawer has 2 removable sliding partitions. Index cards provided for insertion in card holder on front of each drawer.

Order your share while they last. Keep all those small things handy—such as Nuts, Bolts, Screws, Small Parts, Condensers, Resistors, etc. Chests may be assorted for quantity price. Shpg. wt. X-334, 9 lbs.; X-335, 18 lbs.

ONLY WILCOX-GAY Recordio TAPE RECORDER
with PREST-O-MATIC push-button keyboard
gives Maximum performance for Lowest cost!

DUAL SPEED—Records at 1 1/2" and 3 1/4" per second

STOCK NO. AMP-17

\$99.50

RYTEL PICTURE TUBE REJUVENATOR

STOCK NO. T-113
SPECIAL PRICE WHILE THEY LAST

\$7.95

Olson gives you first crack at these famous Rytel Rejuvenators at almost a 50% reduction. A Service Shop and Dealer Must. Give new life to those low emission picture tubes by increasing cathode current. For use on any size picture tube. Handsome black crackle metal case with full instructions. Make Money Rejuvenating Picture Tubes. Reg. Wholesale Price \$14.95. Shpg. wt. 3 lbs.

This is the famous DeLuxe Wilcox-Gay Recorder that retails all over the country for \$179.95. Naturally they are all brand new, in factory sealed cartons and Guaranteed 100% by Wilcox-Gay and Olson.

How can we sell this outstanding value for such an amazing low price? . . . our main purpose in this business is to offer the highest quality for the lowest cost . . . and the Recordio is a perfect example.

Record those treasured "Family Highlights" . . . or your favorite music, broadcasts, friends or parties. Use it in your business for dictation, meetings, speeches, etc. Portable Recordio is also a valuable aid in Schools, Churches, and Clubs.

Remember . . . it's completely Automatic . . . the finger-act controls are so simple even a child can operate it. And we're offering the finest Recorder we've ever featured at LESS than Dealer's Cost.

INSTANTANEOUS RECORING OR PLAYBACK. 2-SPEEDS. RECORDS. PLAYS BACK. ERASES. LOOK AT THESE QUALITY-PACKED FEATURES:

"Prest-o-matic" Controls allow instant choice of all operating functions . . . High speed forward and reverse, record, stop, and playback. Handles up to 7" reels. Neon Indicator shows Normal and Overload levels. Full Range Variable Tone Control allows maximum brilliance to a deep, rich tone. Volume Control has and trouble compensated for best reproduction. COMPLETELY READY TO OPERATE. Included: Heavy-duty Controlled Rectifier, Microphone, Radio, Phone, TV Input Jack permits recording from radio, piano or TV speaker voice coil by means of patch cord. External Speaker for external speakers, automatic disconnects internal 5" x 7" elliptical P.M. Speaker, 4 Tubes, 6SR7, 6AQ5, 6AV6, 6X4, 6X4. Reelifier, 7 ft. Cord, Handsome Removable Cover, Operating Instructions. Size: 12" x 14" x 8". Weight: 23 lbs. complete. 110-120 Volt 60 Cycle AC. U.L. Approved.

Sets a record! But Gently
3-SPEED GENERAL INSTRUMENT AUTOMATIC RECORD CHANGER WITH GENUINE ASTATIC "TURNOVER" CARTRIDGE

Changes All Sizes—7, 10, 12" All Speeds—33 1/3, 45, 78 RPM

This General Instrument Record Changer has turned out to be the OLSON'S ALL TIME "BEST SELLER" For Good Reasons. Good It performs like the Pace-Setter it is the smoothest running changer on the market today. Records slide gently down the spindle—no chance of damaging those valuable records. Simple to operate—because it is precision-built by craftsmen who have had years of experience, thus insuring years of trouble-free performance.

Changer may be connected to any Radio, TV or Amplifier. Clever "touch-plate" allows you to reject a record at will. Genuine Astatic "Turnover" Cartridge is included at this fabulous low cost. Of course they're Brand New, in original factory-sealed cartons, and guaranteed 100% by Olson and the manufacturer.

Operates on 115 Volt AC, 60 Cycle. Base size 12" x 12 1/2", 5 1/4" above plate and 3 1/2" below.

BRAND NEW PLASTIC BASE RECORDING TAPE

600 Ft. REEL 1200 Ft. REEL

STOCK NO. X-275 Single, ea. \$1.29 Lots of 10 \$11.99

STOCK NO. X-249 Single, ea. \$2.19 Lots of 10 \$21.99

RELAYS CHOICE—ONLY \$1.99 EACH

STOCK NO. CON. TACTS OHMS USE

SW-30 SPDT 30 6 to 12V

SW-41 SPST 3000 Plate Sens

SW-24 SPST 5000 Plate Sens

SW-29 DPDT 6000 Plate Sens

Made by Allied and Potter-Bromfield. Silver contacts. Size: 1 1/2" x 1 1/2" x 2". Shpg. wt. each 1 lb.

CONVERT 5V DC TO 110V AC
STOCK NO. RA-104 ONLY **\$10.63**

Now you can have all the advantages of a 110V AC power supply in YOUR OWN CAR! Converts 5V DC to 110V AC 60 cycle with capacity to 45-50 watts. Fully filtered. Just plug in cigar lighter and operate portable phonos, radios, dictating machines, lights, electric shavers, etc. Slightly larger than cigarette pack! Ideal for Picnics, camping, summer traveling pleasure. Shpg. wt. 5 lbs.

HI-FI DELUXE MODEL

Equipped with "Turnover" cartridge and dual needle—both for 33 1/3 and 45 RPM discs and the other side for 78 RPM discs. Both sides equipped with precision metal tone-lasting tips. Regular retail price \$52.50. Shpg. wt. 1 lb.

Stock No. RA-113

Single, each \$22.99

Ea., Lots of **\$21.99**

Operates on 115 Volt AC, 60 Cycle. Base size 12" x 12 1/2", 5 1/4" above plate and 3 1/2" below.

12" CO-AXIAL SPEAKER

\$12.95

Stock No. S-168

Our new 1953 Model. Guaranteed to outperform any speaker in its price class. Equipped with two "high concentration" Alnico 5 magnets and a high frequency diffuser. The 12" section delivers the bass while the inner 3" tweeter speaker section delivers the treble tones. Together they give you "living tone." This speaker is unconditionally guaranteed to satisfy even the most critical user. Olson promises to refund your money. Only two wires to connect to any radio or amplifier. Voice coil impedance 8 ohms. Frequency response 30 to 17,500 cps. Ship. wt. 10 lbs.

6-TUBE CUSTOM AUTO RADIOS

Here's your chance to save plenty on these nationally famous CUSTOM AUTO RADIOS. Simple to install—no cables, no brackets, no holes to drill. Install in 3 to 4 minutes. Custom-built to fit in dash of each model car listed. Six tubes including rectifier—2 being dual purpose—thus you really get 8-tube performance. Dynamic speaker with powerful Alnico 5 permanent magnet. Easy vision slide-rule dial. Beautiful hamper-tone finish. Shpg. wt. 16 lbs.

\$41.97

STK. NO.	MAKE OF CAR	YEAR MODEL
RA-300	Chevrolet	1949-1950
RA-351	Chevrolet	1951-52
RA-142	Chevrolet	1953
RA-200	Dodge	1949-1950
RA-251	Dodge	1951-52
RA-124	Dodge	1953
RA-100	Ford	1949-1950
RA-151	Ford	1951
RA-152	Ford	1952

STK. NO.	MAKE OF CAR	YEAR MODEL
RA-144	Ford	1953
RA-451	Hudson	'48-49-50-51-52
RA-751	Henry J.	1951-52
RA-143	Mercury	1952-53
RA-200	Plymouth	1949-1950
RA-651	Plymouth	1951-52
RA-125	Plymouth	1953
RA-551	Studebaker	1950-1951-1952

10 WATT HI-FI PUSH-PULL AMPLIFIER

• Built-In Pre-Amplifier • G-E Cartridge Input

• Treble and Bass Boost • All-Aluminum Chassis

• Push-Pull Output • Multiple Speaker Impedances WITH BOMBSHELL VALUE! It's unbelievable! A full 10 watt HI-FI Amplifier completely assembled and ready to play. Has built-in PRE-AMP for G-E, and similar types of magnetic pickup. 4 inputs: 1 crystal phono, 1 magnetic phono, 1 radio, 1 mike. 4 Controls: 1 Bass, 1 Treble, 1 Volume, 1 Phono-radio Switch. Output Impedances: 4, 8, 16 ohms. Peak Power output 17 watts.

Order this amplifier today and see what brilliant real tone it will deliver. Supply is limited. Even our factory seal cartons. You couldn't buy the parts alone for this price. Remember this: Every one in history and custom. Frequency response 20 to 20,000 is a full size amplifier, transformer operated, not an AC-DC job. Frequency response 20 to 20,000 cps at least than 1/2 of 1% distortion. Tubes—6BE7, 1-6SC7, 2-6AV6, 1-6X3. Complete with cps at least than 1/2 of 1% distortion. Shpg. wt. 15 lbs. Can be used with any phono or speaker but you should take advantage of the Combination Deal offered below.

COMBINATION DEAL!

10 WATT HI-FI PUSH-PULL AMPLIFIER COMPLETE WITH 12" CO-AXIAL SPEAKER

Stock No. AS-67

Both for **\$39.95** WITH TUBES

Only **\$39.95** Completely wired. Not a kit.

RCA TV LINE COUPLER

Stock No. RA-132

\$1.99 EACH

Made by RCA and used on their production lines. Copper Case 3 1/2" x 3 1/2" x 2. Fully shielded with built-in deck and removable covers; 2 amphenol silver plated co axial plugs; 1—RCA 616 tube, socket and shield; 3—1 mid. 400 volt tubular condensers; 2 mica condensers; 5 resistors, padder, choke and slug tuned to 1. Shpg. wt. 3 lbs.

3-SPEED AUTOMATIC PORTABLE RECORD PLAYER

Complies With Latest Model VM Changer, Amplifier, Speaker and Portable Carrying Case.

STOCK NO. RA-145 **\$45.95**

Regular \$84.50. Changer Plays twelve 7" discs (33 1/3 or 45 RPM); Twelve 10" or ten 12" discs (33 1/3 or 78 RPM). 100% automatic in operation. Just stack on the records. Motor shuts off after last disc. Turnover cartridge for playing all speeds. Two osmium tipped long life needles. Alnico 5 PM heavy duty speaker. Volume and tone controls. Simulated Alligator case 17 1/2 x 8 1/2" 115V, 60 cy. AC. Factory sealed cartons. Shpg. wt. 21 lbs.

PRICES SLASHED TO BITS ON OLSON RESISTOR KITS

GIANT "SUPER-ASSORTMENT" KIT—232 RESISTORS

Olson Offers You a Price-Busting Assortment of Brand New, Fully Guaranteed Most Popular Resistors At the Lowest Price in Our History. Without a doubt this is the Biggest Resistor Bargain to be found in America Today. Every Kit is chock full of Popular Values—sizes you need and use every day in TV and Radio Servicing. Invaluable to hams and experimenters. Many leading brands of resistors are included such as IBC, Clarostat, Centralab and other top-notchers. KIT CONTAINS: 200—1/2 Watt Resistors, 20—1 and 2 Watt Resistors, 12—5 to 25 Watt Wirewounds. A total of 232 Assorted Popular Resistors worth at least \$23.50. Every Kit is unconditionally guaranteed to please or you get your money back. Every Resistor is RMA Code Coded or stamped with value. Tolerances are 5%, 10% and 20%. This amazing offer will not be repeated when our stock is gone. Shpg. wt. 2 lbs.

\$3.95 STOCK NO. AS-84

PERMEABILITY TUNED AM FRONT END

BRAND NEW! PARTS ALONE WORTH \$4.50. Used in standard broadcast receivers in place of variable condenser associated parts. Self contained—includes antenna, tuned r-f and oscillator coils, dual trimmers. Designed for linear dial calibration through approximately 340° rotation by means of concentric cam and lever drive. Connects directly to mixer grid and r-f grid to make complete receiver. Mounted on plate 5 1/4" x 3 3/4". Instructions included. Shpg. wt. 1 lb.

3 for **\$5.50**

\$1.89 EACH

STOCK NO. L-46

How to Order

Order directly from this ad. State quantity desired, stock number, description and price. You may send remittance with order. (Add for Postage: Estimate at least \$1.00 of order value.—10c for each \$1.00 if you order more than 1,000 miles away. We refund every cent not used) or if you prefer SEND MONEY ORDER. We will ship C.O.D. and you may pay mail or express—no merchandise and postage.

OLSON'S BIG NEW BARGAIN CATALOG FREE!

Get Olson's LOWER-than-wholesale prices from this famous book. STANDARD BRANDS—FRESH STOCK. IMMEDIATE DELIVERLY. Catalog is two colors—40 full pages of unbelievable bargains each mailing. Simply note on your order or write today for your free copy from: OLSON RADIO WAREHOUSE, 275-D EAST MARKET ST., AKRON 8, OHIO.

COMPLETE TV ANTENNA

A complete stacked array. Made by a famous manufacturer whose name and brand is on every factory sealed carton. Look what you get: 2 Six-element conical bays, 1 pair "Q" bars, 2 Five-foot mast sections, 60 ft. 300 ohm twin line, 5 Standard insulating base, 1 guy ring, 1 clamp, hardware. Elements are highest quality aluminum. Reg. list price is \$31.95. Shpg. wt. 15 lbs. Express only.

Stock No. AU-24

\$12.99 Complete Set

OLSON STORES TO SERVE YOU IN:

CLEVELAND, OHIO 2020 Euclid Avenue

CHICAGO, ILLINOIS 623 W. Randolph Street

If you live in or near either of these cities visit our Bargain Stores where you'll find these and hundreds of other Olson Buys.

PLEASE: MINIMUM ORDER \$3.00

OLSON RADIO WAREHOUSE 275-D EAST MARKET ST., AKRON 8, OHIO

FIX 3 OUT OF 4 Television and Radio Receivers



Just by
reading
this one
book!

Here's the practical television and radio repair book for you—easy, plain, and simple, and written for the man with no technical training.

Just think—without math or heavy circuit theory, you can start doing actual repair work even before you finish the book! No trick methods—only the sound, correct, safe way to do things. Read it and—so quickly it will surprise you—you can fix your own and friends' sets . . . get a service shop job . . . even start your own money-making business. Here's the reason you'll learn so quickly: You deal only with the things that go wrong in sets—the parts—instead of spending long weeks studying circuits and doing lab work.



TELEVISION AND RADIO REPAIRING

556 pages
225 illus.
\$7.95

by John Markus
Assoc. Ed. Electronics

- Gives all these helps:**
- How to run your own business
 - How to test and replace tubes
 - How to test tubes without equipment
 - How to eliminate receiver noises
 - How to improve dim TV pictures
 - How to solder
 - How to repair, replace and adjust:
 - power supplies
 - carbon and wirewound resistors
 - controls and switches
 - condensers, coils, and transformers
 - tuning devices
 - How to fix phono pickups
 - How to repair wood and plastic cabinets
 - How to install, adjust, and repair different types of antennas and many others

Simple! Easy-to-read!
For every television and radio part, no matter what make the set is, Markus shows you how to recognize symptoms of trouble . . . how to test to make sure . . . how to order the new part . . . and how to install it. He explains everything in plain language and uses pictures throughout so you actually see what he's talking about.

Be a well-paid repairman—Even start your own business

Here's your chance to share the big money going to servicemen today—without investing a good deal of cash—and by starting right in your own home or working for a service outfit.

The book tells you what few tools to buy, how to make a service call, how to collect the bills. It shows you how to test television and radio parts with a multimeter.

Just one repair job pays for the book!

10-DAY FREE TRIAL


McGRAW-HILL BOOK CO., Dept. RTN-9
327 W. 41 St., New York City 36

Send me Markus' TELEVISION AND RADIO REPAIRING for 10 days' examination on approval. In 10 days I will remit \$7.95, plus few cents for delivery, or return book postpaid. (We pay for delivery if you remit with this coupon; same return privilege.)

(Print)
Name
Address
City Zone State
Company
Position RTN-9

(This offer applies in U. S. only)

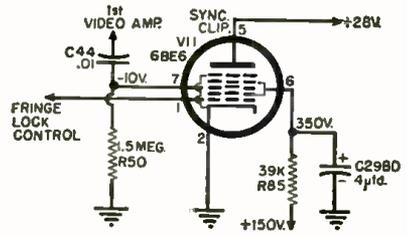nals, or on some community distribution systems. To correct this



condition replace C_{11} , the .01 μ fd. coupling condenser in the grid circuit of the 6BE6 sync clipper. (See diagram.) The new condenser should be a .0022 μ fd., 600-volt molded unit.

19K20, 19K22, 19K23, 19K24, & 21K20

Picture shrinks horizontally.

This condition may be caused by an increase in value of R_{11} , the 150,000 ohm resistor in the plate circuit (pin 2) of the 6SN7GT horizontal discharge tube. To correct this, replace the resistor with another 150,000 ohm, 1 watt, 10% tolerance unit.

21K20

Arcing between 1X2A tube and adjacent components.


High-voltage breakdown may occur between the 1X2A tube and adjacent components (particularly the 6SN7GT horizontal oscillator and discharge tube) in areas of high humidity. To correct this condition, install a polystyrene corona shield around the 1X2A tube and socket assembly. The Zenith part No. for such a corona shield is 83-2102.

K SERIES TUNERS

Poor performance on u.h.f.

Poor performance on u.h.f. may be caused by excessive leakage in the coaxial cable which is used to inject the oscillator signal. (See diagram.)

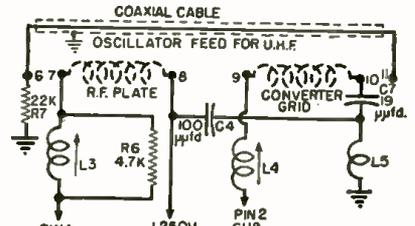To check this cable, switch the tuner to a v.h.f. position, unsolder the ground end of the 22,000 ohm resistor, R_{11} , and check for leakage, using the highest megohm



scale on a vacuum-tube voltmeter. If the meter shows anything but infinite resistance, replace the cable.

REMOTE CONTROL UNIT S-17268

Locking of the manual control.

This can be caused by failure of the worm drive gear to disengage, as a result of a weak solenoid armature actuating spring, or because of misalignment of the magnet mounting bracket. The mounting bracket may be aligned through the slotted mounting holes.

Excessive buzz.

This may be due to improper seating of the solenoid clapper plate on the magnet core. —50—

WORLD'S LARGEST TUBE WAREHOUSE OPENED

ELABORATE dedication ceremonies attended by civic and industry leaders of the Midwest marked the opening of the world's largest tube warehouse by General Electric Company.

Located at 3800 N. Milwaukee Ave. in Chicago, the new building provides two acres of warehousing facilities for industrial, transmitting, receiving, and cathode-ray tubes.

Laboratory, application engineering,

and sales facilities are also housed at this new tube center.

Besides storage and office space and the laboratory, the building houses sections for tube testing and packing, a medical dispensary, and an employee's cafeteria.

Sheltered loading docks in the new structure provide space for loading five large truck trailers and four railroad freight cars simultaneously. —50—

Two views of the new G-E tube warehouse in Chicago. To the right are parts of the lab facilities while picture below shows portion of the huge loading area for handling all the tube shipments.



CREI prepares you quickly for success in

The future is in your hands!

The signs are plain as to the future of the trained men in the electronics industry. It is a tremendous industry, and—at the *present time* there are more jobs than there are trained men to fill them. But—when there's a choice between a trained and untrained applicant, the trained man will get the job. Your biggest problem is to decide on—and begin the best possible training program.

CREI Home Study . . . The Quick Way to Get There.



Since 1927, CREI has given thousands of ambitious young men the technical knowledge that leads to more money and security. The time-tested CREI procedure can help *you*, too—if you really want to be helped. CREI lessons are prepared by experts in easy-to-understand form. There is a course of instruction geared to the field in which you want to specialize. You study at *your* convenience, at *your* rate of speed. Your CREI instructors guide you carefully through the material, and grade your written work personally (not by machine).

Industry Recognizes CREI Training.

CREI courses are prepared, and taught with an eye to the needs and demands of industry, so your CREI diploma can open many doors for you. Countless CREI graduates now enjoy important,

good-paying positions with America's most important companies. Many famous organizations have arranged CREI group training for their radio-electronics-television personnel. To name a few: All America Cables and Radio, Inc.; Canadian Aviation Electronics, Ltd.; Canadian Broadcasting Corporation; Columbia Broadcasting System; Canadian Marconi Company; Hoffman Radio Corporation; Machlett Laboratories; Glenn L. Martin Company; Magnavox Company; Pan American Airways, Atlantic Division; Radio Corporation of America, RCA Victor Division; Technical Appliance Corporation; Trans-Canada Air Lines; United Air Lines. Their choice for training of their own personnel is a good cue for *your* choice of a school.



Benefits Felt Right Away.

Almost immediately, you feel the benefits of CREI training. Your employer, when informed of your step toward advancement (only at your request), is certain to take new interest in you and in your future. What you learn in CREI Home Study can start helping you do a better job immediately.

- BROADCASTING
- TELEVISION
- MANUFACTURING
- COMMUNICATIONS
- SERVICING
- AERONAUTICAL ELECTRONICS



CREI also offers Resident Instruction

at the same high technical level—day or night, in Washington, D. C. New classes start once a month. If this instruction meets your requirements, check the coupon for Residence School catalog.

INFORMATION FOR VETERANS

If you were discharged after June 27, 1950—let the new G. I. Bill of Rights help you obtain resident instruction. Check the coupon for full information.

Get this fact-packed booklet today. It's free.

Called "Your Future in the New World of Electronics," this free illustrated booklet gives you the latest picture of the growth and future of the gigantic electronics world. It includes a complete outline of the courses CREI offers (except Television and FM Servicing) together with all the facts you need to judge and compare. Take 2 minutes to send for this booklet right now. We'll promptly send your copy. The rest—your future—is up to you.



CAPITOL RADIO ENGINEERING INSTITUTE

An Accredited Technical Institute • Founded in 1927

3224 16th Street, N.W.

Washington 10, D. C.

MAIL COUPON TODAY

CAPITOL RADIO ENGINEERING INSTITUTE

Dept. 119 3224 16th St., N.W., Washington 10, D. C.

Send booklet "Your Future in the New World of Electronics" and course outline.

CHECK FIELD OF GREATEST INTEREST TV, FM & Advanced AM Servicing Aeronautical Radio Engineering Practical Radio Engineering Broadcast Radio Engineering (AM, FM, TV) Practical Television Engineering

Name.....

Street.....

City.....Zone.....State.....

Check— Residence School Veteran

TOWN

Simpson

MODEL 488 FIELD STRENGTH METER

Saves service time in JV antenna installation—makes service profits longer....Whether installation is fringe in the hills or in the bounce-filled canyons of the city, Model 488 gives you the best location quickly, accurately....Location of maximum signal areas, antenna orientation, comparison of antenna systems, adjustment of boosters and checking of antenna and lead-in installations are only a few of the many functions of Model 488.

You're losing profits without one....Dealer's net price including operating instructions and shoulder strap, \$115.00

See your jobber for full information or write Simpson Electric Company, 5200 West Kinzie Street, Chicago 44, Illinois. Phone EStebrook 9-1121.

In Canada: Bach-Simpson, Ltd., London, Ont.

Another reason why Simpson is the world's largest manufacturer of test equipment



Country

SAVE UP TO 60% ON PICTURE TUBES

Add To Your Profit By Letting NATIONAL Rebuild Your Duds

Exchange old tubes direct with the factory and double your profits on tube replacements. Our new process gives you a tube with a new phosphor screen, new inside dag, new electron gun. Exhausted to highest standards. All tubes meter and set tested.

EVERY TUBE CARRIES A 1-YEAR NEW TUBE WARRANTY.

How To Order

Send old tubes direct to National, together with check or money order for quantity desired at prices quoted here. We ship you new tubes immediately. All tubes sold F.O.B. Blue Springs, Mo., but we pay incoming freight on tubes shipped to us in quantities of 5 or more.

LOOK AT THESE
**LOW
PRICES**

Over 17-inch to
21-INCH TUBES

18.85

Plus 10% Fed. Excise Tax
Up to and Including
17-INCH TUBES

14.85

Plus 10% Fed. Excise Tax

National Picture Tube, Inc., Blue Springs, Mo.

Class A Amplifier (Continued from page 42)

voltage is used for the voltage amplifier and driver stages as well as for the screens of the output tubes. An additional small choke (*Chicago RS-1540*) rated at 15 henrys and 40 ma. with associated condensers supplies additional filtering for these stages. Since there is sufficient power available, a 4-prong *Jones* socket is provided on the amplifier chassis to supply heater current and filtered plate voltage for a preamplifier. The power supply is protected by means of a 3 amp. pigtail-type fuse, wired in the primary circuit of the power transformer.

The builder should have little difficulty assembling and wiring the amplifier and power supply. However, a few suggestions here might help. Since the transformers have a relatively large area devoted to terminal space, they require rather large openings in the chassis. These can best be made by means of a circle cutter in a slow turning drill press. However, a hand brace could be used with the circle cutter to make these openings. Terminal strips should be used in convenient places to facilitate the supporting of the various small components. If the wiring is kept symmetrical, with approximately equal lead lengths on each side of the push-pull circuit, instability and hum problems will be minimized. Care should be taken in the grounding of the various leads so that hum pickup due to ground loops will not be encountered. Room should be provided near the output tubes for the placement of the balancing potentiometer R_{25} and jacks J_1 and J_2 . The balancing potentiometer for the driver stage is mounted near its associated tube. The under-chassis view of the amplifier shows the placement of these units.

The schematic diagram of the amplifier shows only one output impedance provided. This was in the interest of simplicity for those who may have need for only one impedance. However, the *BO-11* transformer makes available impedances of 8, 16, and 600 ohms and it can be connected so that impedances of 4 and 150 ohms can be obtained. The builder can modify this part of the amplifier to suit his own needs. One method of switching for various impedances is shown in Fig. 4. It will be noticed that separate feedback resistors are used for each value of output impedance. This could be eliminated by having the feedback come from one tap on the output transformer for every impedance used, but if good speaker damping is to be achieved, it is best to have the feedback come from the winding attached to the voice coil. It will be seen that two different positions are given for the 600-ohm impedance. One supplies a lower degree of feedback than the

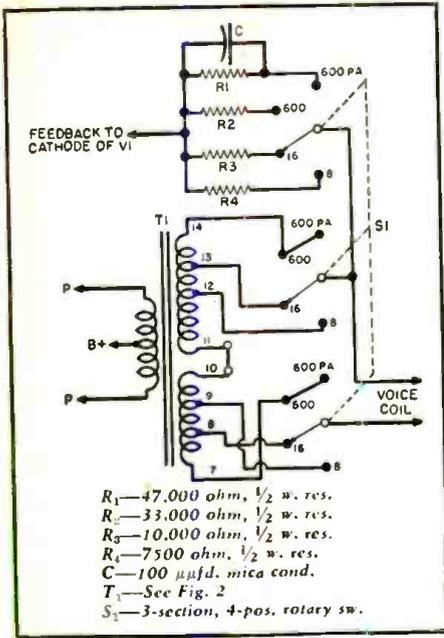


Fig. 4. Switching circuit for 600, 16, and 8 ohms. Fig. 2 is for 8-ohm voice coil.

other and can be used for public address work or some similar service where maximum feedback may not be as important as increased gain.

The adjustment of the finished amplifier is not difficult, but it should be carefully done. After a warmup period has been allowed, the bias voltage on the grids of the output tubes should be set to -45 by adjusting R_{25} . The four output tubes chosen should be as nearly matched as possible. The final balancing of the output stage is accomplished by means of R_{25} . The pentode sockets are left empty for this adjustment and a pair of triodes are tried. The current drawn by each tube can be observed by plugging a milliammeter into the jack associated with that tube. The potentiometer, R_{25} , is adjusted until the current drawn by each tube is equal. These tubes are marked and set aside while various other tubes are tried in the same sockets with the same settings of R_{25} until another pair which matches is found. One of these pairs is used in the triode section and one is used in the tetrode section. Of course the tetrodes could be balanced in their own sockets if the bias were changed or if a signal of sufficient intensity were supplied to the grids. However, the method here outlined works very nicely. If the circuit is operating properly and all voltages are correct, the current in each of the triode tubes will read about 55 ma. with no signal.

The driver stage can now be balanced. This is simple and consists simply of adjusting R_{11} until the voltage at each plate of the driver tube is equal when measured with a vacuum-tube voltmeter. A check can then be made on the signal balance of the amplifier, stage-by-stage, by feeding a sine wave into the input and measuring the signal voltage at each grid on each side of the circuit. This measurement can be made with the a.c. range


**SETCHELL-CARLSON
BEACON RECEIVER
BC-1206-C**
 Receives A-N beam signals.
 Tunes 195 to 420 Kc. Size
 4 1/4 x 6 3/8 x 4 1/2 in.
 Complete with 5 tubes.
BRAND NEW \$13.50
 Used, less tubes \$8.95

SENSATIONAL Smash Value!


**NEW COMPLETE
I.F.F. Equipment
RC-188-A**

Bargain opportunity of a lifetime! This I.F.F. equipment originally cost about \$20,000

... now buy it for a tiny fraction of cost! Easily converted for Television. Complete assembly consists of Control unit with 5 C.R. Tube, transmitter and receiver assembly (157 to 185 Mc.), indicator unit, and Power Supply (450 watts), operating on 110 volts, 60 cycles AC. All assembled, ready to operate. 62 Tubes included: 8—6V6GT, 9—6SL7GT, 14—6SN7GT, 1—5CP1, 2—9006, 1—6Y6G, 2—6E5, 1—100TH, 2—6J5, 2—2C26, 1—3E29, 1—6H6, 7—6AG5, 3—6AK5, 1—6C4, 3—2X2, 1—6X5GT, 3—5U4GT. Overall size 55" high, 28" wide, 20 1/2" deep. Shpg. weight 855 lbs. Your cost, complete, **\$350.00** BRAND NEW in original packing.

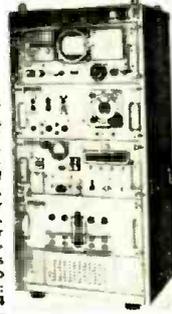


**McElroy
Automatic
KEYER
BRAND NEW**

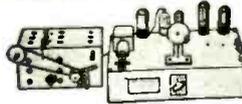

Suitable for keying transmitter, or for code practice. Has photoelectric cell and sensitive relay. Variable speed motor operates on 110 volts, 60 cycles AC, or DC, complete with 2—11726 and 1—117L7 tubes, your cost **\$27.95**

80 VOLT A.C. INVERTER

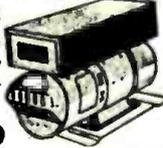Sig. Corps PE-206A. Terrific Value! 80 Volts AC Output, 800 cy. 28 V DC Input 6000 RFM. Complete with Filter.



Value \$100.00. Your Cost **\$12.50**

DYNAMOTORS

TYPE	INPUT Volts	OUTPUT V	A	Excellent USED	BRAND NEW
PE-#6	28	250	@ .06	5.295	5.550
DM-28	28	224	@ .07	4.95	10.50
PE-101C	12/24	400	@ .13	2.75	4.85
PE-103	6/12	500	@ .16	22.50	34.50
PE-94	28	300	@ .2	4.95	7.95
DM-32	28	250	@ .06	4.90	8.95
DM-21	14	230	@ .09	6.85	16.50
BD-77	12	1000	@ .35		27.50

ARMY FIELD PHONES

Type EEB—Talk as far as 17 miles. Dependable 2-way communication at low cost. Ideal for home, farm, field. Up to six phones can be used on one line. Each phone complete with ringer. Originally cost Govt. \$65.00 each. Excellent Condition. Your cost **\$22.25**



WILLARD 6-VOLT MIDGET STORAGE BATTERY
 3-amp hr. BRAND NEW. 3 3/8" x 1-13/16" x 2 3/8" Uses standard electrolyte **\$2.65**

WILLARD 2-VOLT STORAGE BATTERY
 20 AMP. HR. BRAND NEW **\$2.69**
 1-QUART ELECTROLYTE FOR ABOVE. BOTTLE **\$1.45**
 ENOUGH FOR TWO CELLS
 7-PRONG 2-VOLT VIBRATOR, FOR PORTABLE AND FARM SETS (ICE LB530) **\$1.49**

Please include 25¢. Deposit with order—Balance C.O.D. MINIMUM ORDER \$3.00. All Shipments F.O.B. Our Warehouse N.Y.C.

G & G RADIO SUPPLY COMPANY Dept. N9

Phone COrtlandt 7-4605
 51 VESEY STREET • NEW YORK 7, N. Y.
 Branch: 7123 Bryn Mawr Ave., Chicago, Ill.

MICROPHONES Excellent BRAND USED NEW
 T-45 Lip Mike, navy type \$0.49 \$1.45
 T-30 Throat Mike .49 .85

CARBON HANDMIKE
 Genuine Sig. Corps Mike. 200 ohm, single button, has pressure-to-talk switch, 4-ft. rubber cable, amphenol plug. Beautiful satin chrome finish. BRAND NEW **\$5.95**

HEADSETS Excellent USED BRAND NEW
 HS-23 high impedance \$2.95 \$4.75
 HS-33 low impedance 2.45 5.75
 HS-30 low imp (featherwt) 1.49 2.45
 H-105 U high imp (2 units) 4.95 4.95
 CD-307A cords, with PL55 plug and JK26 jack, 8' long 1.19

BC-645 TRANSMITTER-RECEIVER
 15 Tubes 435 To 500 MC
 Set can be modified to use for 2-way communications, voice or code, on following bands: ham band 420-450 mc, citizens radio 460-470 mc., fixed and mobile 450-460 mc., television experimental 470-500 mc. 15 tubes (tubes alone worth more than sale price): 4—7F7, 4—7H7, 2—7E6, 2—6F6, 2—955 and 1—WE316A. Now covers 460 to 490 mc. Brand new BC-645 with tubes, less power supply in factory carton. Shipping weight 25 lbs.
\$49.50 each
 CONVERSION DIAGRAM INCLUDED!

PE-101C DYNAMOTOR for above BC-645 **\$4.85**
 UHF ANTENNA ASSY, for above BC-645 **\$2.45**

SCR-274N COMMAND & ARC-5 EQUIPMENT
 Excellent BRAND USED NEW
 Type BC-453 Rcvr. 190-550 Kc. \$28.50 \$44.50
 BC-454 Rcvr. 3-6 Mc. 12.50 24.95
 BC-455 Rcvr. 6-9 Mc. 12.95 17.95
 BC-456 Modulator 2.75 5.75
 BC-457 Xmtr. 4.5-3 Mc. 18.50 29.50
 BC-458 Xmtr. 5.3-7 Mc. 17.50 27.50
 BC-459 Xmtr. 7-9.1 Mc. 19.95 24.50
 BC-450 3 Rcvr. control box 1.49 2.45
 BC-451 Xmtr. control box 1.25 1.95
 3 Receiver rack 1.79 2.98
 2 Transmitter rack 1.59 3.25
 Single Transmitter rack

ARC-5/T-23 Transmitter
 With tubes, Brand New **\$59.50**

BC-221 FREQUENCY METER
 Reconditioned. PERFECT! Complete with tubes and crystal **\$129.50**

TRANSMITTER BC-223-AX
 Ideal for 80-meter band! 801 osc., 801 P.A., 2—4G modulators, 1—4G speech amp., 4 ktal freq. and master osc., on selector switch, 10 to 30-watt output, tone, voice or C.W. Black wrinkle case, complete with freq. chart, 3 tuning units and tubes in original cases, less xtals. Specially low price, shpg. wt. 80 lbs. **\$99.50** BRAND NEW


B-29 BOMB SIGHT
 ASSEMBLED BY SPERRY GYROSCOPE CO.

HUNDREDS OF USES THOUSANDS OF VALUABLE PARTS

- Experimenters
- Physicists
- Schools
- Research Men
- Mechanics
- Opticians
- Laboratories
- Tech Institutes
- Engineers
- Repairmen
- Manufacturers
- Electricians

Recently declared a war surplus item this bomb-sight is now selling at a ridiculously low price! As parts or as precision units, this P-4 Computer can be used to make instrument and machinery repairs, in manufacturing and assembling, in home and industrial workshops. It can be used in teaching aeronautics, engineering, navigation, physics, optics, mechanics, etc.
 Comes in three units—the main body and two attachable periscopes, 22 and 68 inches high, alternate parts of an intricate optical system made by Eastman-Kodak Co. Main body is 35x25x14 inches. Contains at least 8 27 VDC motors, electric heater and temp. control, precision sextant, dozens of switches and controls, hundreds of fine gears and driving rods all types. Shipping wt. 250 lbs.
Cost to U. S. Govt. \$21,000. \$295.00
 Your Cost BRAND NEW

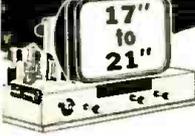Let me show you how EASY it is to
LEARN TV
the practical way..



ASSEMBLE A
**TRANSVISION
TV KIT**

Pay as You Wire \$**39**
Down Payment

I WILL HELP YOU to start learning TV the practical way — by assembling a TRANSVISION TV KIT in EASY STAGES. For only \$39 you get PACKAGE #1 (standard first pkg. for all of our kits). This package gives you the BASIC CHASSIS and over 450 TV COMPONENTS with complete Instructions, Drawings, Photos, Service Booklet, and a year's subscription to my "TV and Electronics Notes". When ready, you order the next stage (pkg. #2), etc. Low prices make your complete kit a terrific buy!



FREE CATALOG

Shows 6 Great TV Kits:
EXCLUSIVE: Only Transvision TV Kits are adaptable to UHF. Ideal for FRINGE AREAS. No Previous Technical Knowledge required. Write now!

TRANSVISION, INC., Dept. RN9
NEW ROCHELLE, N. Y.

— MAIL THIS COUPON TODAY —

Mr. D. Gnessin, Educational Director
TRANSVISION, INC., NEW ROCHELLE, N. Y. Dept. RN9

I'm enclosing \$_____ deposit. Send standard kit PACKAGE #1, with all Instruction Material. Balance C.O.D.

Send FREE copy of your new TV Kit Catalog.

Name _____
Address _____
City _____ State _____

Tremendous Opportunities in
COIN TV
and **COMMERCIAL TV**

TRANSVISION offers the only specially designed line of Coin-Operated and Commercial TV with the **FREEVIEWER*** ATTACHMENT (Pat. Pend.)



This field offers rich rewards to enterprising servicemen or dealers — on part time or full time basis. *The Electronic Freeviewer is a patented device which makes coin operation really pay off in a big way. Boosts revenue by "sampling" — by giving a short freeview of TV programs to prospective customers. Works like magic in enticing sales.

Get details now.
TRANSVISION, INC.
NEW ROCHELLE, N. Y.

— MAIL THIS COUPON TODAY —

TRANSVISION, INC., NEW ROCHELLE, N. Y. Dept. RN9

Rush full details on COIN OPERATED TV.

Name _____
Address _____
City _____ State _____

of a v.t.v.m. or with an oscilloscope. The oscilloscope has the advantage of showing the waveform as well as the amplitude. If all units in each side of the push-pull circuit are matched properly, this signal voltage will be the same on the grid of V_{2A} as on the grid of V_{2B} . It will also be the same on the grids of V_3 and V_4 as on the grids of V_5 and V_6 . If such is not the case, it may be necessary to try different tubes in the voltage amplifier and driver stages until tubes are found, the sections of which are balanced.

The results obtained with this amplifier are very gratifying. In the first place, the hum level is extremely low — a condition which is necessary if good results are to be obtained. The frequency range of the amplifier extends to several hundred kilocycles, and is relatively flat to over 200,000 cycles. Sine-wave distortion within this range is undiscernable on the scope, even as maximum output is approached. The author does not have equipment for measuring intermodulation distortion, but listening tests in-

dicates a pleasing clean quality, even at maximum output.

One interesting experiment was made in connection with listening tests. It was desired to observe the quality of radio music, and since no FM station was in the vicinity, a simple crystal detector was connected to a coil and condenser, giving very broad tuning. This was connected to the input of the amplifier and was tuned to the local AM radio station. The results were amazing. Both the highs and lows were reproduced in a very pleasing manner and, to the average ear, the results were comparable to those that would be obtained from an FM signal. It is realized that in such a signal the sidebands are cut, but with the broad tuning used, the effect was that of a fairly wide-band signal.

If the builder desires a high-quality amplifier and is not satisfied with the relatively low output of the average Williamson amplifier, it is strongly recommended that he try this "extended class A" amplifier.

NEW TV STATIONS ON THE AIR

(As of August 25, 1953)

The following new stations bring the lists published in previous issues up to date.

STATE, CITY	STATION	CHANNEL	FREQUENCY RANGE (IN MC.)	VIDEO WAVELENGTH (IN FT.)	VIDEO POWER (IN KW.)
Arizona Yuma	KIVA	11	198-204	4.93	29
California Chico	KHSL-TV	12	204-210	4.79	12
Los Angeles	KUSC-TV†	28	554-560	1.77	46
San Diego	KFSD-TV	10	192-198	5.08	316
Connecticut Waterbury	WATR-TV	53	704-710	1.40	245
Georgia Macon	WETV	47	668-674	1.47	20
Idaho Boise	KIDO-TV	7	174-180	5.61	51
Illinois Decatur	WTVP	17	488-494	2.01	17
Iowa Ford Dodge	KQTV	21	512-518	1.92	23
Kansas Wichita	KEDD	16	482-488	2.04	200
Louisiana Monroe	KFAZ-TV	43	644-650	1.53	25
Monroe	KNOE-TV	8	180-186	5.43	250
Minnesota Austin	KMMT-TV	6	82-88	11.8	18
Missouri Kansas City	KCMO-TV	5	76-82	12.74	100
St. Joseph	KFEQ-TV	2	54-60	17.8	52
Nevada Las Vegas	KLAS-TV	8	180-186	5.43	28
New York Buffalo	WBUF-TV	17	488-494	2.01	166
Oregon Medford	KBES-TV	5	76-82	12.74	19
Pennsylvania Easton	WGLV-TV	57	728-734	1.35	83
Harrisburg	WTPA-TV	71	812-818	1.21	175
Pittsburgh	WENS	16	482-488	2.04	89
South Carolina Greenville	WGVL-TV	23	524-530	1.87	17
Tennessee Johnson City	WJHL-TV	11	198-204	4.93	108
Texas Abilene	KRBC-TV	9	186-192	5.25	22
Longview	KTVE	32	578-584	1.70	20
Tyler	KETX	19	500-506	1.96	2
Virginia Hampton	WVEC-TV	15	476-482	2.06	200
Newport News	WACH-TV	33	584-590	1.68	20
Washington Tacoma	KMO-TV	13	210-216	4.65	120
Yakima	KIMA-TV	29	560-566	1.75	55
Wisconsin Oshkosh	WOSH-TV	48	674-680	1.46	1

*From Station CP application. †Educational, U. of Southern California. The frequency of the video carrier = 1.25 + channel lower freq. limit. Total number of television stations now on the air: 238 (67 of which are u.h.f.)

to the

E. E. or

PHYSICS GRADUATE

with an interest
or experience in

RADAR or ELECTRONICS

Hughes Research and Development Laboratories, one of the nation's large electronic organizations, are now creating a number of new openings in an important phase of operations.

Here is what one of these positions offers you

OUR COMPANY

located in Southern California, is presently engaged in the development of advanced radar devices, electronic computers and guided missiles.

THESE NEW POSITIONS

are for men who will serve as technical advisors to the companies and government agencies purchasing Hughes equipment.

YOU WILL BE TRAINED

(at full pay) in our Laboratories for several months until you are thoroughly familiar with the equipment that you will later help the Services to understand and properly employ.

AFTER TRAINING

you may (1) remain with the Laboratories in Southern California in an instruction or administrative capacity, (2) become the Hughes representative at a company where our equipment is being installed, or (3) be the Hughes representative at a military base in this country—or overseas (single men only). Adequate traveling allowances are given, and married men keep their families with them at all times.

YOUR FUTURE

in the expanding electronic field will be enhanced by the all-around experience gained. As the employment of commercial electronic systems increases, you will find this training in the most advanced techniques extremely valuable.

How
to
apply

If you are under 35 years of age and have an E.E. or Physics degree and an interest or experience in radar or electronics,

write
to

HUGHES

RESEARCH AND DEVELOPMENT
LABORATORIES

Scientific and Engineering Staff

Culver City,
Los Angeles County, California

Assurance is required that the relocation of the applicant will not cause the disruption of an urgent military project.

Selenium Diodes (Continued from page 65)

fixed bias offers several advantages over the conventional cathode bias provided that the cathode resistor is not intended to obtain degeneration. It should be noted that the greatest advantage of fixed bias is for class AB₁ push-pull amplifiers. When used in this type of circuit, fixed bias provides higher power output, increased stability, and reduced distortion for a given output tube plate current. A good example is a push-pull circuit for 2A3, 6A3, or 6B4 tubes. When fixed bias is used, the power output is increased by about 50% and the distortion is decreased by 50% for the same current rating. The fixed bias (Fig. 7) for the output tubes is ob-

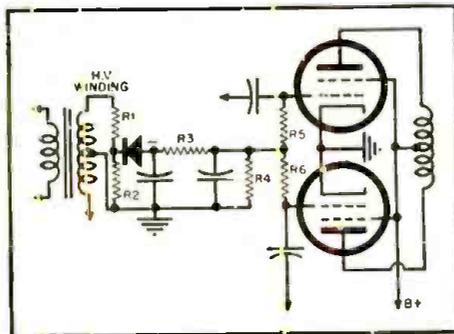



Fig. 7. Push-pull stage with fixed bias.

tained from the high voltage winding of the power transformer with a voltage divider, a selenium diode, and a filter network. There is no need to consider the loading effect on the high voltage transformer winding, since the additional current drawn by the grids of the tubes or the voltage divider is negligible.

Fixed bias for the output and r.f. stages of an a.c. radio receiver can be simply accomplished by the use of a selenium diode and associated resistors and condensers. A typical example of such a circuit is shown in Fig. 8. The a.c. input to the rectifier network may be obtained from the 6.3 volt filament winding on the power transformer.

Because selenium diodes range in input voltages from 26 to 130 volts r.m.s., the number of bias voltages that can be provided is practically unlimited when proper voltage dividers are used. For another example, it may be well to note that the power supply of TV receivers can be simpli-


Fig. 8. Fixed bias supply circuit for audio stage and r.f. stages of an a.c. receiver.

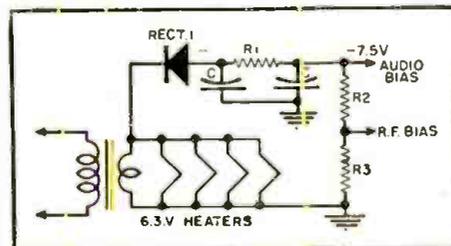

L. Veltri, busy service-dealer of Westchester, N. Y., reports:

I SAVED \$940*
by making a \$59 INVESTMENT
in a Transvision
FIELD STRENGTH METER

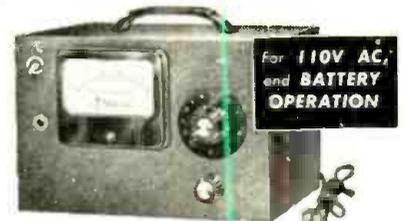*Says Mr. Veltri: "... The way I figure, in the last 6 months I saved that much money in installation time alone ..."



FIELD STRENGTH METER
Saves 50% of Installation Cost
Pays for itself on 3 or 4 jobs

NO TV SET NEEDED

Works from antenna ... Measures actual picture signal strength directly from antenna. Shows antenna orientation maxima. Compares gain of antenna systems. Measures TVI on all channels. Checks receiver re-radiation (local oscillator). Permits one man antenna installation.



PREVENT WASTE OF SERVICING TIME!

By checking antenna performance with the Field Strength Meter, the serviceman can determine whether the TV set or antenna, or both, are the source of trouble. Call backs are eliminated.



Wide range: Measures field strength from 10-50,000 microvolts. Has Fringe Area Switch for weak signal areas. 13 channel selector. Individually calibrated on every channel.

ADAPTABLE for UHF

Model FSM-2, for 110V AC only. Complete with tubes. Wt. 13 lbs. net \$59.

Model FSM-3B, for 110V AC and Battery Operation (all batteries and cables included). Wt. 22 lbs. net \$79.

Order direct from factory:

TRANSVISION INC., NEW ROCHELLE, N. Y.

FREE: Sample copy of "TV and Electronics Notes". Or send 50¢ for year's subscription.



10 DAY TRIAL

Buy and try this fine instrument for 10 DAYS. Then, if you wish, you may return it. Your purchase price less 10% (our cost of handling and re-packaging) will be promptly refunded.

TRANSVISION, INC. NEW ROCHELLE, N. Y.

DEPT. RN-9F

() Send me Model FSM-2; _____ FSM-3B

() Enclosed find \$_____ deposit. Balance C.O.D.


() Enclosed find \$_____ in full.

I accept your 10 Day Trial terms.

Name _____

Address _____

City _____ State _____

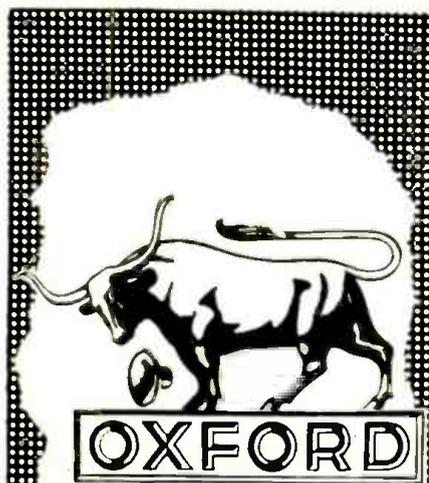

OXFORD

Speakers



There is an application for every Oxford Speaker . . . and an Oxford Speaker for every application.

**OXFORD
ELECTRIC
CORPORATION**

3911 S. Michigan Ave.
Chicago 15, Illinois

EXPORT: ROBURN AGENCIES
NEW YORK CITY

Preferred for original equipment
... Proven for replacement!

International Short-Wave (Continued from page 75)

from 1100 to after 1830 in Arabic Service. (West) Cairo, 11.815, now appears to run to 1700 daily. (Bellington, N.Y.)

El Salvador—YSS, 9.555, San Salvador, good level with popular music 2250, closing 2300. (Morrison, R. I.; Boice, Conn.)

England—MSF, Rugby, has been testing for about one hour at 1800 on 2,500, 5,000, and 10,000; call-sign is given in slow c.w. followed by voice announcement and 1000-cycle tone; requests reports to The National Physical Laboratory, Teddington, Middx., England. (ISWC, London)

Ethiopia—Radio Addis Ababa, 15.050V, "Voice of Ethiopia," some days at least has news 1315 followed by a commentary. Should close 1430. (Pearce, England, others)

Fiji—ZJV, 3.980, Box 163, Suva, states reports on tests have been received from as far away as Sweden, Norway, and USA; will stay on 3.980 for some time to come since is best frequency yet tested. Studios are in Cable and Wireless buildings, Victoria, Fiji Broadcasting Commission, 2 kw. on 930 kc., 500 watts on s.w.; schedule is now 1400-1600, 1900-2100, 0030-0500, Sun. only at 0030-0500; station staff consists of four members—manager, two announcers, and E. K. Broadbridge, technician-announcer. (Cushen, N. Z.) Excellent level in N. Z. on 3.980. (Hardwick) Usually is poor around 0300 in Australia. (Williams)

French Equatorial Africa—Brazzaville, 11.97, has news for Far East 1100. (Pearce, England) Heard with news 1550-1600; CWQRM. (Grace, Conn.) And at 1745. (Esser, Pa.) Good on 15.595 at 1430-1525 sign-off. (Saylor, Va.) Brazzaville noted calling Paris 0830 using 15.416; later played popular music; good level. (Catch, England) Radio A.E.F., 9.970A, noted 1400 with call in French, then news in that language, closing 1524 with "La Marseillaise." (Pearce, England)

French Morocco—Rabat noted on new measured channel of 7.220 at 0730 in French, good level in Britain. (Catch)

French West Africa—Radio Dakar, 9.560, noted signing on 0200 after interval signal; call in French by woman, light musical recordings. (Pearce, England) Heard closing on this frequency 1715 with "La Marseillaise." Officials of Radio Dakar say Radio Conakry, French Guinea, operates daily 0715-0730 on the 40-m. band, no frequency given; that a new station is Radio Cotonou, Dahomey, no further details; that Dakar will have a new 30 kw. transmitter next year to replace the 12 kw. one, a 50 kw., and a 10 kw. tropical band station, that Radio Abidjan, Ivory Coast, may increase power to 20 kw. soon. (Scheiner, N. J.)

Germany—Stuttgart, 6.030, noted

RADIO & TELEVISION NEWS

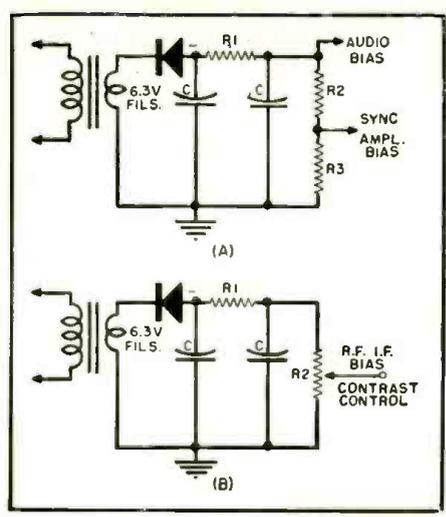


Fig. 9. Two TV circuits illustrating selenium diode applications. (A) In audio and sync amplifier bias circuits, and (B) in the r.f. and i.f. bias circuits of set.


fied by supplying individual bias for the audio, synchronization, r.f., and i.f. stages. This is also desirable since it eliminates the possibility of load changes in one circuit affecting the other circuits which was often the case in earlier TV receivers. The circuits shown in Fig. 9 are two possibilities. On the other hand, they may be combined as shown in Fig. 10, depending upon the choice of the design engineer.

It is believed that the Type 5U1 selenium diode is the most versatile of the line. This unit is rated for a maximum input voltage of 130 volts r.m.s. and can consequently be connected directly to a 117-volt line for its source of voltage. It is obvious that this unit is ideal for use in equipment that does not have any transformer winding such as an a.c.-d.c. radio set. The circuit would be similar to Fig. 7. The resistance of R_1 plus R_2 should be on the order of 150,000 ohms or more.

For higher output voltages, several of these selenium diodes may be connected in series. For example, three Type 5U1 diodes connected in series can be used to deliver 300 volts d.c.

It is believed that the selenium diodes thus far developed have made available a series of new components to the design engineer for consideration in his future circuit designs. The examples given are merely intended as illustrations of a few such possibilities and it is hoped that they may stimulate the imagination and ingenuity of the circuit design engineer. —30—

Fig. 10. Biasing for four stages in TV set.

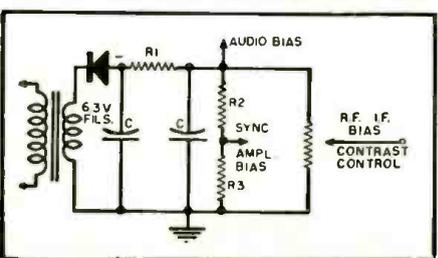

Compare... prove EMC superiority




model 206 MUTUAL CONDUCTANCE TUBE TESTER

- Checks mutual conductance on calibrated microhmo scale • Checks tubes for gas content • Detects both shorted and open elements • Tests all tubes from .75V to 117 filament volts • Tests all local, actual and miniature tubes • Checks individual sections of multi-purpose tubes • Built-in roll chart • Uses lever type switches.

MODEL 206P—With hand-rubbed oak carrying case (illustrated)

\$83.50

MODEL 206C—Slipping counter case
\$79.50

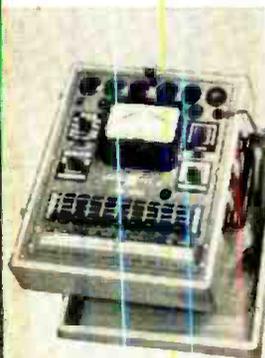

model 205 TUBE TESTER

- Tests all tubes including Noval and sub-miniatures • Completely flexible lever type switching arrangement • Tests all tubes from .75 volts to 117 filament volts by standard emission test • Tests all cold cathode, magic eye, voltage regulator and ballast tubes • Has pilot light indicator • Line voltage control compensates for line variations between 105 and 135 volts • Checks for shorts and leakages • Three-color hammerstone panel.

MODEL 205P—with hand-rubbed oak carrying case (illustrated)

\$47.50

MODEL 205C—Slipping counter case
\$46.50



model 204 TUBE-BATTERY-OHM CAPACITY TESTER

- Tests all tubes including Noval and sub-miniature • Tests all batteries under rated load • Emission testing method gives easy, direct readings • Tests resistance to 4 megohms • Tests condensers from .01 to 1 mfd • Uses four-position lever type switches • Checks condenser leakage.

MODEL 204P—Portable oak case, removable cover (illustrated)

\$55.90

MODEL 204C—Slipping counter case
\$54.90

— See them at your Jobbers —

EMC

WRITE DEPT. RN-9
FOR FREE
COMPLETE
CATALOG OF
THESE AND OTHER
INSTRUMENTS

ELECTRONIC MEASUREMENTS CORPORATION
280 LAFAYETTE STREET • NEW YORK 12, N. Y.

EXPORT DEPARTMENT 106 LIBERTY STREET, N. Y. C. 6, N. Y.

high
fidelity
music

wherever
you wish
to enjoy:

beautiful
furniture
styles



V-M tri-o-matic 555
High Fidelity Phonograph
Mahogany \$139.95*
Lined Oak \$144.95*

tri-o-matic® 555 HIGH FIDELITY PHONOGRAPH

Just plug it in, and the V-M 555 will faithfully reproduce every note in your favorite albums with full, realistic beauty and majestic power. It adds beauty to any room with your choice of glowing mahogany or modern lined oak furniture finishes. Golden grille of expanded metal protects three 5" ultra-wide range speakers.

V-M MODEL 555 FEATURES

High fidelity audio system provides 20 to 15,000 cycles tonal reproduction. It includes three 5" ultra-wide range speakers and powerful 4-tube (plus electronic rectifier) amplifier with dual purpose tube to give you 5-tube performance. Rigid, resonance-free aluminum die cast tone arm has special "flip-under" cartridge with two sapphire needles. Enjoy the convenience of Siesta Switch that shuts off everything (amplifier too) after last record plays. The 555 plays records of all three sizes and speeds automatically.

*Slightly higher in the west.

PLEASE MAIL COUPON

V-M Corporation,
Benton Harbor 4, Michigan

Please send me illustrated literature telling all about the V-M Model 555 High Fidelity Phonograph.

Name _____

Address _____

City _____, State _____

TUNING FORK ACCURACY



with the *Concertone* 1502

Driving the tape directly from the shaft of a two-speed hysteresis synchronous motor, this new Concertone recorder combines precise timing accuracy with unsurpassed sound reproduction. Concertone Model 1502 ... \$445.00

WRITE FOR BULLETIN 201

Manufactured by

Berlant Associates

4917 W. Jefferson Blvd. • Los Angeles 16, Calif.



0100 with call in German, then news in that language; Munich, 6.160, noted 0800 with news in German, also at 1200, and at 0100; Frankfurt, 6.190, has news in German 0100 and 1345. *Overseas Service*, Cologne, noted on 5.98 at 0830 with dance music, also with dance music 1700; with news in German 0100. (Pearce, England) This channel is used parallel 7.29 to North America 2030-2330. (Bellington, N. Y.; Morrison, R. I., others) Heard on 11.795 at 1700. (Scheiner, N. J.)

Holland—Radio Nederland by now should be using a new 19-m. channel, probably 15.245. (ISWC, London, others) Noted with news to North America 1645 on 11.73, 9.59, 6.025. (Zerosh, Pa., others)

Hong-Kong—ZBW3, 9.525, Victoria, heard 0515 with *English* session of recorded music. (Sanderson, Australia) Noted irregularly with news 0500. (Balbi, Calif.) Has newscast 0930. (Navarro, Philippines)

Hungary — Budapest noted with *English* 1600-1630 on 9.833, 11.91. 7.22. (Pearce, England) Mailbag session Sun.; reports requested. (Catch, England)

India—Delhi, 11.95, noted to West Indies 1830. (Catch, England; Niblack, Ind.) Has replaced 11.85 and has news 1930. (Bellington, N. Y., others) Delhi, 15.35, noted 0245 with news. (Sanderson, Australia)

Indo-China (Vietnam) — Radio France-Asie, 15.420, Saigon, is readable now around 0700 although some days has bad QRM from a N. Y. commercial phone station. (Bishop, Ohio) Heard well with news 0500. Also with news 2035 on 11.925. Heard on 9.745A at 0615 with French session of news, music. Hanoi, 7.405A, heard 0630 with French news and music, fair level. (Sanderson, Australia) "Voice of Vietnam," 9.620, Saigon, noted 0500-0630 in Vietnamese and *English*; good level in Tokyo. (Ishikawa)

Iran—EPB, 15.100, Teheran, has news 1500. Russian 1515, closes 1530 when clock strikes 1200. (Pearce, England, others) Has Turkish 1345-1400; Persian 1400-1430; German 1430-1445; French 1445-1500. (ISWC, London)

Israel—Tel Aviv, 9.010A, has news 1415; French 1430-1515, and "Voice of Zion" session in *English* 1515-1600 closedown. (ISWC, London, others)

Italy—Rome noted signing on with news 0400 on 17.80, 15.40, 11.905. (Pearce, England) Noted in *English* to North America 1920 on 9.575A. (Esser, Pa.) With news 2145 on 9.575A and 11.810. ("The Knob Twisters," Iowa) Is strong on 15.40 in Spanish 2020. (Niblack, Ind.)

Lebanon—Beirut, 8.036, noted 1600 in French, 1625A with news in Arabic, and closing 1630 with march (not "La Marseillaise"). (Pearce, England; Ferguson, N. C.)

Libya—Forces Radio Station, 4.785A, Tripoli, noted around 1400-1600 closedown, when gives time as "11 p.m.," and plays "God Save the Queen;" announces as 4.782 and says will return at "6:30 a.m." (2330 EST). Often has

RADIO & TV TUBES

1B3	.65	6CD6G	1.29
1X2	.60	6SN7	.49
5U4G	.41	12AT7	.56
6AU6	.38	12AU7	.43
6BG6G	1.19	12AV7	.59

Many more types available at attractive prices, including transmitting tubes. WRITE FOR COMPLETE PRICE LIST TODAY.

CONDENSERS

20-20	150V	10 for \$2.95
40-40	150V	10 for \$3.24
50-30	150V	10 for \$3.24

RESISTORS—STANDARD BRAND

1/2 Watt	20%	\$ 8.95 per 1000
1 Watt	20%	\$15.95 per 1000

RESISTOR SPECIAL

1/2 Watt, 1 Watt, 2 Watt, some 10 Watt resistors. Sold only in assorted lots of 200 for \$1.98 un-insulated. Few duplications.

HEAD PHONES

5 ft. moisture proof cord and phone tip terminals. Low impedance. \$2.98 per set.

TUBE REJUVENATOR

Increases the life of fading picture tubes. \$1.63 each.

ELECTRONIC LINE FILTER

Just plug filter into outlet, and plug television into filter, eliminates interference noise from all electrical appliances. Prices .75 each. In lots of 10 or more .65 each.

ANTENNAS


"Braeh" Radar tenna UHF corner reflector. \$10.77. We carry a complete line of BRACH radio and TV antennas.

Hi-Lite Electronic Sales Co.

DEPT. RN, 837 18th AVE.
IRVINGTON 11, NEW JERSEY

South River NEWS

CHIMNEY CORNER GUARD

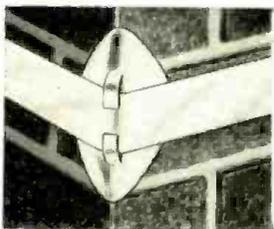

Box of Six . . . 49c

An exclusive South River device for protecting, strengthening, and safeguarding chimney and strapping. Prevents chipping of chimney. Permits uniform tightening of banding. Safeguards mounting equipment. South River Antenna Mounting Accessories are carried by every leading TV Parts Jabber from coast to coast.

Write for your copy of our new 1953 catalog.

In Canada A. T. R. Armstrong Co., Toronto

SOUTH RIVER METAL PRODUCTS CO., INC.
SOUTH RIVER, N. J.

PIONEER AND OUTSTANDING PRODUCER OF FINEST LINE OF ANTENNA MOUNTS

BBC recorded features. (Pearce, England; Cushen, N. Z.) Uses 250 watts to a dipole running east-west; reports requested to No. 1, FBS, Tripoli, Middle East Land Forces, Libya. (*Radio Sweden*)

Luxembourg—Radio Luxembourg 6.090, noted 1700 with call in French, then dance music; another day at 1325 with news in French. (Pearce, England)

Madagascar—Radio Tananarive noted closing 1200 on Sat. and 1230 Sun. in Malgache program on 7.374A; uses "La Marseillaise" at sign-off.

Malaya—BFESB, Singapore, noted on 11.82 at 1045 when gave frequencies of 15.435, 11.820, 11.955, 7.120; listed schedule at 1130 closedown as 0800-0900 on 15.435; 0915-1030, 11.820; 1030-1130, 15.435 and 11.820 for India-Pakistan; 0800-0815, 7.120; 0900-1130, 11.955 and 7.120 for Burma-Thailand. (Pearce, England) Is fair level on 15.435 around 1100 daily. (Boice, Conn.) *Radio Malaya*, 4.825, Singapore, heard 0615 with news, commentary, music. (Sanderson Australia)

Martinique—Radio Amateur, London, says Hardwick, N. Z., has "squeezed a QSL out of FNRI, Fort-de-France on 9.700, which is indeed another nice item for his collection. We are pleased to note that this station is at least still active on this channel." Not reported as heard in USA for a long, long time!

Nicaragua—YNOW noted on 6.077 lately up from 6.055, identifies in Spanish 0800; has QRM from YSC. 6.078. El Salvador; is on before 0730 and goes to 2300A. (Stark, Texas)

Northern Rhodesia—Lusaka sent schedule of 0700-1400, 4.826; 0700-1200, 7.220; 1215-1400, 3.914. (Pearce, England)

Norway—Radio Norway, LLG. 9.610, is good to Eastern North America 2000-2100; extends schedule to 2120A on Sunday when has English session "Norway This Week." (Ferguson, N. C., others) Heard to Western North America from 2300. (Niblack, Ind., others)

Outer Mongolia—Ulan Bator, 6.325, noted in N. Z. opening 0100 at weak level. (*Radio Amateur*, London)

Philippines—The Far East Broadcasting Co., Manila, "The Call of the Orient," recently observed its 5th anniversary; broadcasts to Asia, the Middle and Near East, and Europe in 36 languages now over 7 transmitters. (*Radio Sweden*) DZH9, 1.855, good, DZH7, 9.73, good 0315 with news. (Balbi, Calif.) DZH2, 9.64, noted 0500-0730 at good level; DZH3, 9.500, fair 0630-0800; 9.690, good at 0700-0830 in English. (Ishikawa, Japan)

Pitcairn Island—Scheiner, N. J., has received word that there is a new radio station on this island; was built by a New Zealander and transmitter is called the "Transarctic"; will use an Australian wind charger to provide necessary power; call will be ZBP and will use English with 500 watts power between 1.5-13 mc. on the s.w. band. No further details.

SEE LEO FIRST FOR . . .

hallicrafters

I can SAVE you money . . . Liberal Trade-ins



SEE US FIRST FOR THE NEW SX-88 RECEIVER . . . \$499.95



\$199.95

S-76 RECEIVER

Extra selectivity with double superheterodyne circuit. One RF, two conversion and 3 IF stages. Range 550-1550 Kc, 1.7-34 Mc in four bands. 8 tubes plus voltage regulator and rectifier. Complete with tubes, less speaker.



\$249.95

SX-71 RECEIVER

Double Conversion sharp selectivity, plus built-in NBFM at moderate cost. 11 tubes plus voltage regulator and rectifier. Low down payment.

NAME YOUR TERMS • LOW DOWN PAYMENTS • PERSONALIZED SERVICE

HALLICRAFTERS RECEIVERS AVAILABLE FOR IMMEDIATE SHIPMENT

S-81	\$59.95	S-408	\$129.95	ST-83	\$129.95
S-82	\$59.95	S-53A	\$99.95	S-78A	\$89.50
A-84	\$99.50	S-72L	\$119.95	SX-62	\$349.95
S-38C	\$59.95	S-77A	\$129.95	S-72 Portable	\$109.95

R-46 Speaker \$24.95 HT-20 XMTR \$449.50



JUST OFF THE PRESS!

Big New WRL 1954 Catalog

Offering the greatest selection of radio & television equipment, parts, and supplies, from "The World's Largest Distributor of Amateur Radio Transmitting Equipment." Order with confidence from WRL—the world's most personalized radio supply house.

Send for FREE Copy

WRITE—WIRE
PHONE 7795

WORLD RADIO LABORATORIES
744 West Broadway
Council Bluffs, Iowa

R-9

Please send me:

- Radio Map 25¢ WRL XMTR Info
 New Catalog SX-71 Info
 Used Equipment List S-76 Info
 New Log Book

Name

Address

City

State



Biggest
AUDIO
and
HI-FI
Event of
the Year!

AUDIORAMA 1953

Presented by THE AUDIO FAIR

The annual event in the Audio field of utmost interest to Government and Military Agencies, Broadcast Engineers, Recordists, Sound-On-Film Men, Hobbyists, High Fidelity Enthusiasts, and Distributors and Dealers of Audio and High Fidelity equipment. THE AUDIO FAIR is the largest and most concentrated exhibition of Audio Equipment held under one roof! Every up-to-the-minute development will be represented, seen and heard.

SPONSORED BY



The General Public
Is Invited to Attend

NO ADMISSION CHARGE

AUDIORAMA is presented by THE AUDIO FAIR
HARRY N. REIZES, Managing Director, 67 W. 44 St., N. Y.

TIME:
Oct. 14, 15, 16, 17

PLACE:
Hotel New Yorker
New York City
Registration On
5th, 6th
and 7th Floors

**"ON TOP
OF-THE-STATION
RECEPTION"**
in the
**FRINGE
AREAS**


OUT PERFORMS

all other
VHF
Antennas!

BJ-2

These "BIG JACK"* Antennas are performing with outstanding success in many areas. Near-station installations of the BJ-1 provide a higher gain and clearer picture on all VHF channels in range. The BJ-2, for fringe area installations, has provided excellent reception where other antennas have failed.

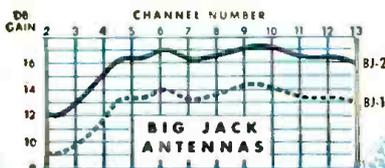Kay-Townes superior constructions and engineering details plus fringe area "Know-How" make the BIG JACK series the greatest high-gain VHF antennas ever built.



Kay-Townes Antennas and Accessories are available in all areas. Select your nearest wholesaler or retailer. Contact your jobber or write for name of nearest distributor.

*Pat. Pending

**THE BEST SET IS ONLY
AS GOOD AS ITS ANTENNA!**

**KAY-TOWNES
ANTENNA CO.
BOX 586, ROME, GA.**

Poland—Warsaw noted with *English* 0130-0200 on 9.555 and 7.105A; with *English* 1730-1800 near 5.93; at 1200-1230 on 9.555, 7.175, and repeated 1230-1300 on 9.555, 7.145. (Pearce, England) Has quite powerful signal on 9.57 with *English* 1400. (Bishop, Ohio) Heard opening 1715 on 11.74 in *English*. (Bellington, N. Y.) On same channel with *English* 1945. (Scheiner, N. J.)

Portugal—Lisbon's new 11.835 channel noted signing on 1230 with news in Portuguese, parallel 11.99A. (Pearce, England) Good on 11.99A at 1622 tune-in. (Bishop, Ohio) Heard closing 1840 on 11.924 and 11.960 parallel, and separately on 11.996. (Catch, England) Heard to North America in Portuguese 1900-2100 on 9.745A (Zerosh, Pa.) And parallel on 5.973A. (Saylor, Va.) Verifies quickly now with a new, attractive QSL card. (Stenson, Sweden)

Portuguese India—Radio Goa at present operates on 6.025, 5 kw., 9.610, 10 kw., at 2100-1230, and on 557 kc., 2.5 kw., 0230-1430; shortly will also use 15.235, 17.795, 21.685; the 3.425 channel, 5 kw., is still used *experimentally*. (WRH)

Sao Tome—CR5SC, 4.807, noted with news in Portuguese 1545, closing 1602 with "A Portuguesa;" CR5SB, 17.677, noted *Sunday* 0700-0800 close-down. (Pearce, England)

Saudi Arabia—Djeddah, 11.845 and near 9.650, heard with interval signal 1030, signed on with march-anthem 1036; all-native. (Pearce, England)

Somalia—Radio Mogadiscio officials list the transmitter as an Imcaradio (Italian), 300 watts, with a doublet antenna, omni-directional, on 7.420 at 0445-0530 Italian; 0915-1015, 1100-1200 Somali; 1200-1300 Italian. (Scheiner, N. J.)

Switzerland—Berne, 9.665, noted at good level in *English* 1445. (Esser, Pa.) Heard closing North American transmission 2300 on 6.165. (Hathaway, Ill.) HEI5, 11.615, excellent level in N. Z. in Spanish 1930. (Hardwick)

Syria—Damascus, 11.910A, has news 1645 and 1715; off 1730. (Baetz, Ill., others)

Taiwan (Formosa)—BED4, 11.920, "Voice of Free China," Taipei, noted 1325 with news, off with national an-

**INTERNATIONAL
RECTIFIER
CORPORATION**

EL SEGUNDO
CALIFORNIA

Selenium

Diodes



Actual Size

DIAMETER:
From 1/4" to 13/32"
LENGTH: From 1/4" to 1/2"
RMS applied voltage:
From 26 volts to 208 volts
DC output voltage:
From 20 volts to 160 volts
DC output current:
avg. from 200 microamperes
to 11 milliamperes

Reverse Leakage at 10 volts RMS:
0.6 microamperes to
2.4 microamperes
Potted in thermosetting
compound
Temperature Range:
From -60° C to 100° C
Available in 1, 2, 3, 4, 5, 6, 7
and 8 cell Diodes.

WRITE FOR BULLETIN SD-1

**INTERNATIONAL RECTIFIER
CORPORATION**

1521 E. Grand Ave., El Segundo, Calif. Phone: OREGON 8-3778
CHICAGO: 205 W. Wacker Drive. Phone: Franklin 2-3889
NEW YORK: 501 Madison Avenue. Phone: Plaza 5-8665

them 1500. (Pearce, England) Ishikawa, Japan, says is heard on 11.735 and 9.775A at 0400-0900 in Chinese, Japanese, English, good level. Sanderson, Australia, notes BED32, 9.778A at 0345 with Western music, Chinese news. Saylor, Va., recently heard BED26, 10.080, at 0100-0215.

Thailand (Siam)—Bangkok's HSK7, 11.910, noted 0515 with news and music, then Thai session. (Sanderson, Australia) By now may have new 50 kw. transmitter on air with news services to Europe 1700-1800, and to North America 2200-2300, in English; not known what frequency will be used, but possibly will be 11.700A. Plans a regional station set up soon, may have two stations in this service in operation next year. (Scheiner, N. J.)

Tangier—Pan American Radio. 7.405A, noted mixed with Athens (Greece) Forces Station to 1703, then in clear to fade-out 1745. (N. Z. DX Times) Radio International, 6.110, heard around 1600. (Alonso, Spain)

Trieste—The British Forces Station has an experimental transmission on 15.125 at 1100-1800. (ISW, London, others) Fairly good level in N. Y. (Legge) Heard from 1400 onwards. (Saylor, Va.)

USI (Indonesia)—Djakarta now uses 11.735 parallel 15.15 to Europe in English 1400-1500. (N. Z. DX Times; Pearce, England) The Indonesian Air Force Station still operates on 11.945 and is strong in N. Z. around 0500. (Radio Amateur, London)

Venezuela—YVKD, 4.890, Caracas, noted 1800 with news in Spanish, good level. YVLA, 4.780, Valencia, fair level 1815. (Catch, England) YVLK, 4.970, Caracas, is good in English session 1800-1900. (Kroll, N. Y., others) YVKF, Barquisimeto, noted on 9.510 at 2000-2030 with classical music; all-Spanish. (Middleton, Ohio)

Yugoslavia—Radio Yugoslavia, Belgrade, uses a new channel of 9.615A from 2230. (N. Z. DX Times, others) Heard with English 0130 on 6.100, 9.505; 1:00, 6.100; 1315 and 1645, 6.100, 6.150. Mickelsson, Sweden)

Press Time Flashes

Etersvej, Sweden, reports transmissions from Katmandu, Nepal, begin at 2330, 0310, and 0830 on 7.370; (Continued on page 156)



Germanium Transistors and Diodes

POINT CONTACT TRANSISTORS

Available in a variety of stable controlled types suitable for both fast and medium speed switching circuits and high frequency amplifiers.

JUNCTION POWER DIODES

Useful in power supplies, magnetic amplifiers and telephone systems, etc., they have the characteristics of large plate-type power rectifiers and size and weight of a small circuit component.

PNP JUNCTION TRANSISTORS

Tiny, stable high gain units, most economical of power, may be soldered in place or socketed in a recommended RTMA transistor socket. Suitable for audio amplifiers, servo amplifiers and transformer coupled carrier amplifiers. In plastic or hermetically sealed in metal and glass.



Unit illustrated at right hermetically sealed.

Coming Soon...


RRP JUNCTION POWER TRANSISTORS
RRP PHOTO TRANSISTORS

Our engineers will be glad to offer suggestions regarding your Germanium Transistor and Diode applications without obligation... Write to Section RT 1.

Sales and Service

RADIO RECEPTOR CO., INC.

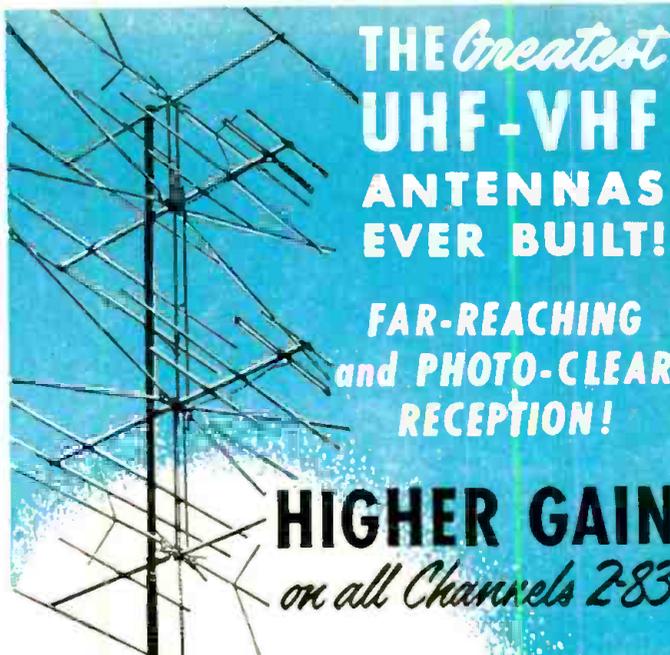Since 1922 in Radio and Electronics
Sales Dept.: 211 W. 14th St., New York 11, N. Y.
Factory: 84 North 7th St., Brooklyn 11 N. Y.



THE Greatest UHF-VHF ANTENNAS EVER BUILT!

FAR-REACHING and PHOTO-CLEAR RECEPTION!

HIGHER GAIN on all Channels 2-83

Original, revolutionary design... FIXED IMPEDANCE Term System provides All-Channel High Gain reception with a single transmission line.

BJU-2




Kay-Townes' BJU Antennas are the recognized leaders in the field of clear-picture, high-gain, trouble-free UHF-VHF antenna performance! Simplified but more exacting and effective engineering has resulted in "bug-free" antennas that provide photo-clear reception. One lead-in wire only. No matching pads or isolation filters... no coils or condensers... which tend to cut down signals.

"THE BEST ALL CHANNEL UHF-VHF ANTENNA AVAILABLE!" says

Leading Alabama Dealer

Henry N. Bailey of Mobile says: "We have tested more than 25 different antennas in our search for a good performer on UHF channel 48 and our local VHF channel 10... and your BJU-1 all-channel UHF-VHF antenna did the job that others failed to do... and in addition performed superbly as a fringe antenna on channel 6, New Orleans... over 150 miles away!"

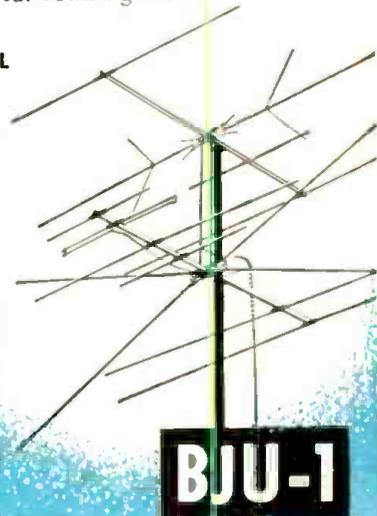K-T Antennas are sold through selected distributors only... write for name of your nearest jobber.



BJU-1

THE BEST SET IS ONLY AS GOOD AS ITS ANTENNA!

*Pat. Applied for

KAY-TOWNES ANTENNA CO.

BOX 586, ROME, GA.

Here's the new SHURE SLIM-X


All-Purpose Crystal MICROPHONE



MODEL 777
List Price \$18.95
MODEL 777s
(with switch)
List Price \$20.95

(Price includes cradle for mounting on stand)

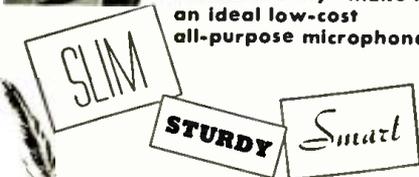Its Versatility and "Hand-a-Bility" make it an ideal low-cost all-purpose microphone



LIGHT! The new "777" Slim-X Microphones are rugged little microphones weighing only 6 ounces! They are designed for good-quality voice and music reproduction. Their versatility and "hand-a-bility" make them ideal for use by lecturers, announcers, instructors, and Hams; for audience participation shows; carnivals; panel and quiz shows; and use with home-recorders. When mounted on either cradle or swivel, the "777" can be removed in a flash (no tools necessary)—simply by lifting it out of the holder. This makes it an ideal "walk-around" hand-held microphone.

TECHNICAL INFORMATION: Smooth frequency response—60 to 10,000 c.p.s.; special-sealed crystal element—for long operating life; high impedance; 7' single-conductor cable, disconnect type. Dimensions: (Microphone only) Length, 4½"; Diameter 1". Finish: Rich satin chrome overall.

NOTE: Lavalier cord for suspension of Microphone around neck is available. (optional).

ACCESSORIES FOR "777"

MODEL S38 STAND is a heavy die-cast base. Includes metal screw machine stud for connecting microphone adaptor to stand base.

List Price: \$3.00

MODEL A25 SWIVEL ADAPTOR features a long-life, high-quality swivel connector. Is lined with a long-life nylon sleeve—for noise-free and scratch-free insertion and removal of microphone.

List Price: \$5.00



SHURE BROTHERS, Inc.
MICROPHONES and ACOUSTIC DEVICES

225 W. Huron St., Chicago 10, Ill., Cable: SHUREMICRO

not confirmed. *Radio Amateur*, London, says a station announcing as Katmandu, has been reported testing on 9.856 in Hindi, Pathani, Tamil, and French around 0630.

ZL2, 9.54, Wellington, New Zealand, noted 0300. (Frazier, Texas) Heard over ZL9, 11.810, and ZL3, 11.780, from around 2250 to after 0000 with good level on former, fair on ZL3. (Baetz, Ill., others)

A new channel of *Radio Thailand* (Siam) is HSK9, 11.700, heard 0500 with news, music, good level in Australia. (Sanderson) May be the new 50 kw. transmitter.

The BBC, London, has been testing 0430-0800 on 15.390, 15.400. (*N. Z. DX Times*) According to announcement, by now the 1015-1030 news session from *Radio Pakistan* should be on 9.484, 5.990. (Pearce, England) *Radio France-Asie*, Saigon, Indo-China (Vietnam), tests to Europe on 11.950A at 1035-1100 in French, 1100-1130 in English; reports requested to Box 412, Saigon. (*Etersrep*, Sweden, others) *Radio Luxembourg's* new 50 kw. transmitter is in use on 6.090 at 0040-0930, 1045-1800, mostly in French. (Mickelsson, Sweden) When this was compiled, the VOA relay at Salonika, Greece, was scheduled with tests to Europe on 6.040 at 1245-1655; on 7.270 at 0900-1645.

Clandestine *Radio Espana de Independencia* still noted around 1750 with "news" in Spanish on 10.280. (Catch, England) *Radio Sweden* says *Deutsche Welle*, Cologne, the *German Overseas Service*, is on this new schedule—2030-2330, 11.795; 0530-0830, 15.275; 0930-1230, 1300-1600, 17.845; 1700-2000, 11.795.

Revised schedules of *Radio Pakistan's* External Service are 2015-2100, 11.885, 15.335 to Southeast Asia; 2315-2400, 15.335, 11.770 to East and South Africa; 0440-0600, 9.645, 15.335 to South Asia; 0630-0715, 15.335, 17.770 to Indonesia; 0830-0915, 11.674 to Burma; 1100-1200, 6.235, 7.010 with Afghan-Persian Service; 1215-1300 same channels with Iranian Service; 1310-1330

General Overseas Service (dictation-speed news in English), 11.650, 7.010 (or 9.645?); 1330-1430 same channels for Arabic Service; 1445-1530 to Turkey and 1530-1615 to the United Kingdom, 9.645, 11.650 (*Radio Australia*, others) Djeddah, Saudi Arabia, seems back on 7.255A again from 7.305AV; noted 2143; has QRM now. (Washington, N. J.) The Nicaraguan on 6.197A seems to be YNVP up from 6.185 and 6.188; announces "En Managua, Las Emisoras de Radio Mil;" has gone to 2335 sign-off. (Stark, Texas)


Zurich sunspot count predictions are—Sept.—15; Oct.—14; Nov.—13; Dec.—13. (Ferguson, N. C.) *Radio Hirondelle*, Hanoi, Indo-China (Vietnam), noted on 7.410A opening 0500 with news in French or Vietnamese to 0515, then Western music; starts to fade out by 0600. The *Thai Army Signal Corps Radio Service*, HSIJS, 4.875, noted daily 0630-0700 with weak signal in Australia; DZ17, 6.080, Manila, noted in English 0500 relaying DZMB; *Radio Peking's* new 12.620A channel noted in English 2200-2215 but with bad CWQRM. (Williams)

A new Brazilian station is *Radio Universidade do Rio Grande do Sul*, Porto Alegre, 3.944, with 1 kw. Port Stanley, Falkland Islands, is reported now on 580 kc. and 6.100 in addition to 3.440; further details desired; not confirmed. "Radio Liberation," Munich, Germany, heard on 15.105 at 1400-1415, with news in Azerbaidjani followed by an Armenian program 1415-1430. The Technical School of Istanbul, Turkey, closed its s.w. station in June and probably will return to the air in October, presumably on same channel—6.690. (WRH)

Acknowledgment

Thanks for your fine reports. Keep them coming in during the fall and winter DX season to Ken Boord, 948 Stewartstown Road, Morgantown, West Virginia, USA. ISW DEPARTMENT monitor's certificates will be sent to any contributor free on request. K.R.B.

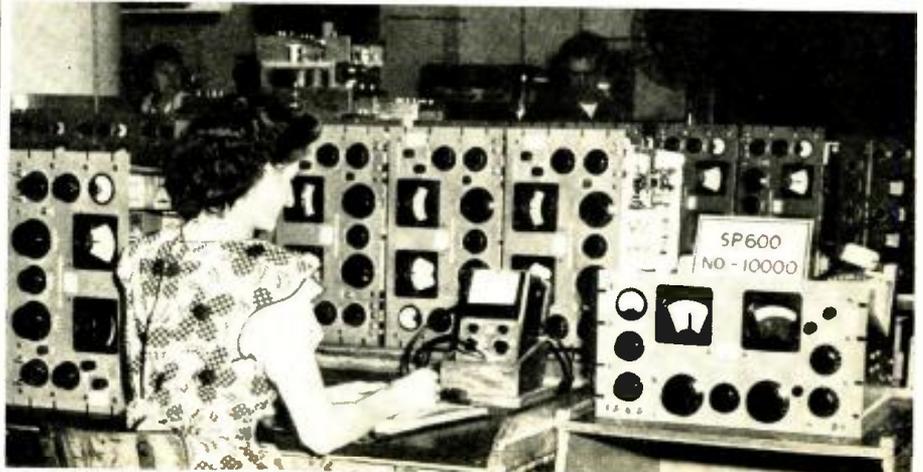The Hammarlund Manufacturing Co., Inc. of New York recently produced its 10,000th "Super-Pro 600" communications receiver. The receiver, which is in use by all the military services as well as by governments and commercial groups all over the world, has been in production since 1950. It is used in the Presidential Communications car.



Certified Record Revue
(Continued from page 58)

an incredible range of orchestral colorings. From the opening snare flourish and sharply accented bass drum, through the wonderful pizzicati and xylophone of the third movement, to the tremendous tympani explosions and savage drum rolls of the movement called "Protest," this is a grand and glorious feast of transients! Believe me the "Protest" movement is well named. Watch your gain control or you'll find the speaker cone in your lap! With controls set for AES equalization, no touch up of bass or treble, cut or boost was required. Surfaces were exceptionally good, in spite of the super-wide dynamic range.

Musically, this is certainly the best thing Dorati and the Minneapolis have done to date for the Mercury "Olympian Series." Dorati is one of the best orchestral craftsmen around. His meticulously detailed reading of this complex score bears witness to this prowess. The orchestra responds sensitively to Dorati's deft direction, with sumptuous string tone and extraordinary percussion.

If you enjoyed "Spirituals" in the old Rodzinski version on Columbia, you will find this up-to-date recording superior in every aspect and well worth your investment.

WAGNER
SIEGFRIED'S RHINE JOURNEY and FUNERAL MUSIC and PRELUDE AND LIEBESTOD (from Tristan und Isolde)

The Pittsburgh Symphony Orchestra conducted by William Steinberg. Capitol "FDS" \$8.185, 33 1/3 rpm, AES curve. Price \$5.72.

Here are two standard "warhorses" brought up-to-date with Capitol's slick new "Full Dimensional Sound." I've always admired Steinberg's conducting, especially since hearing him do the Verdi "Requiem" at the Ravinia Festival in Chicago some seasons back. He is on familiar ground with the "Siegfried" work, and evokes some splendid sonorities from the orchestra. Soundwise, this is a very luminous "big hall" type of recording, very live and with sufficient detail to hold it together. Strings are very clean and percussion sharp and crisp. My only quibble is that the big climaxes seem to lack the punch and weightiness we associate with this music. Otherwise, this is certainly the best "Siegfried" at the present. In the "Tristan," Steinberg's competent and musically, the recording excellent. However, this score still seems to be the property of Stokowski, who has a way with this music, and whose recording remains unmatched.

WALTON
FACADE
LAMBERT
HOROSCOPE (Ballet Suite)
The London Philharmonic Orchestra conducted by Robert Irving. London

September, 1953

Introducing

THE New

PERMOFLUX
Super **ROYAL**

HIGH Fidelity SPEAKER

The finest speaker ever made by Permoflux . . . retaining all the exceptional features of the famous Royal Line . . . plus new developments in design giving you a performance which is *Virtually Distortionless*. It has *Full Range Response* (to the limits of audibility), and *Superior Damping* with *Maximum Sensitivity*.

This unsurpassed performance is due to exclusive Permoflux features, such as ★T.S.C. (treated slotted cone) for extended distortionless low frequency response. ★Latest design in magnetic structure utilizing heavy Alnico 5 ring magnet for maximum flux density. ★Specially designed single cone radiator for full high and low frequency response, without the phase distortion due to separate speakers for high and low frequencies.

Available in 3 sizes - 8, 12 and 15 inch

See and hear the Super Royal at your High Fidelity Dealer

For descriptive literature write to . . .

Permoflux CORPORATION
4918 West Grand Avenue, Chicago 39, Illinois
236 S. Verdugo Rd., Glendale 5, California

FACTS YOU SHOULD KNOW ABOUT UHF CONVERTERS

Many converters on the market today are unsatisfactory in fringe and shadow areas where signal strength is low. Before you install a UHF converter in these areas you should know these facts:

- 1** Signal power loss in the preselector seriously affects picture quality. Most UHF converters use sliding-contact shorted line tuners in the preselector with a fixed power loss of 6 db. The Turner converter uses High Q coaxial cavity tuners with no sliding contacts. Signal power loss is cut to 3 db. The resulting low noise figure keeps picture quality high.
- 2** Oscillator radiation often causes disturbing interference with neighboring sets. In the Turner converter the oscillator tube socket and all associated circuits are inside the coaxial cavity, self-shielded. Removable covers provide a second shield against radiation.
- 3** High amplifier noise figure can further damage picture quality. The Turner converter uses a special broadband amplifier with Cascode circuit. It retains the preselector signal savings without appreciably increasing the noise figure. The Turner amplifier noise figure is only 4 db.

Whether you're selling converters for installations in shadow or fringe areas or putting one in your own home, remember . . . the Turner converter often means the difference between good reception and bad.

EXCLUSIVE TURNER FEATURES

- Higher sensitivity
- Extremely low noise figure
- Exceptional frequency stability
- Double shielding
- Hi-Q silver plated coaxial cavities
- No sliding contacts

OTHER MAJOR TURNER FEATURES

Continuous single-knob tuning. Illuminated slide-rule dial. Smaller size: 8"x6"x6". Use with UHF or combination antennas. Self powered, uses channels 5 or 6. Complete installation instructions for 110-120 volts 50-60 cycles AC. Schematic included.



List price \$49.50

In VHF fringe and shadow areas, the Turner Booster is a superior performer, too.

THE TURNER COMPANY

901 17th St., N.E., Cedar Rapids, Iowa
 Export: Ad Auriemo, Inc.,
 89 Broad St., New York 4, N. Y.
 Canada: Canadian Marconi Co.,
 Toronto, Ont. & Branches

ffer LL771, 33 1/3 rpm, London ffer curve. Price \$5.95.

London has just issued a spate of music by English composers in what they call the "Special Commemorative Coronation Series." In spite of this mouthful, this is a very noteworthy collection of the works of some of England's most highly regarded musical talent. The disc here reviewed is the one most likely to appeal to hi-fi fans. The Walton "Facade" is racy, impudent music, chock full of the things dear to the audiophile's heart. Snarling snare drums, bells, and triangles in profusion, really high register flutes and piccolo, and in one section some wonderful castanets. A superb job of recording. The only thing I missed was the fantastic and amusing poetry of Edith Sitwell, for whom Walton wrote this music. However, many will prefer this orchestral version over the difficult-to-follow edition with the spoken words. Lambert's "Horoscope Ballet" is a frothy trifle, very pleasant to listen to and with enough dissonance here and there to make it interesting. Sharp, brilliant recording, especially fine woodwind playing. Robert Irving conducts both of these works with a sure and knowing hand and gets the best from a good orchestra.

VAUGHN WILLIAMS

A PASTORAL SYMPHONY

The London Philharmonic Orchestra conducted by Sir Adrian Boult. London ffer LL721, 33 1/3 rpm, London ffer curve. Price \$5.95.

Another disc in the "Special Coro-

nation Series," this is a notable "first" for London. Those who have patiently waited over the years for some enterprising company to give them a recording of this great work will rejoice in the splendid job that has been done. Very frankly, this is not the kind of recording preferred by the hi-fi crowd. There are no tricky effects, no bombast. There is, however, a very wonderful recording of a most unusual work. The score has a strange and mystic quality, a sort of "other worldliness" which even the most hardened hi-fi fan can't fail to be interested in and attracted to. Sir Adrian is thoroughly at home with Vaughan Williams and his reading is powerful without being pedantic. Silken string tone, some huge sonorities and a quiet surface add to the attractiveness of this "off-the-trail" disc. Well worth your attention.

EDITOR'S NOTE: This new column is presented as a "bonus" to our audio readers. It will be continued and expanded in scope if reader interest indicates a demand for this type of review. Your letters, either "pro" or "con," will be appreciated and will serve to guide your editor in the conduct of this department.

May we have your comments? -50-

MIDWEST RELAY

A. T. & T. has announced the completion of a new radio-relay system between Chicago, Milwaukee, and Minneapolis.

It will provide 400 additional long distance phone circuits and a TV channel between Chicago and Milwaukee.

ELECTRONIC FLASH PROJECT

CAPTAIN J. E. BROYLES, F. E. Warren Air Force Base, Wyoming, has reported on the success of a building project undertaken by the personnel responsible for the operation of the MARS amateur radio station at the base.

The group built the electronic flash unit described in the March, 1953 issue of RADIO & TELEVISION NEWS ("Build This Electronic Flash") and are so enthusiastic over its performance that they sent in a photograph of the completed unit.

According to Captain Broyles, the flash is housed in a mahogany box no larger than a lady's "cosmetic case." The cabinet contains both the battery pack and the a.c. power supply. The group had to make a few changes in the circuit diagram as printed because of the unavailability of parts. They used three 75 ma., 125 volt selenium rectifiers in place of the two 20 ma. rectifiers specified in the original parts list. They substituted an NE-51 neon lamp for the NE-1 shown and added a 2 amp. fuse in the primary of the power transformer.

The cabinet was built with the side width slightly less than the front width with the depth about the same. The internal parts are accessible by means of a hinged cover which is fastened by a brass trunk-type lock. Both switches and the fuse holder are conveniently located on the front. The indicators, the a.c. light, and the neon lamp are located on the top of the hinged lid. The back of the box carries the two parallel plugs wired for the flash lamp and an extra unit

which can also be used. In addition, a plug is provided to connect the two-wire connector that goes to the synchronizing switch on the camera. -50-

Airman George A. Lehmkuhl poses with the electronic flash unit constructed by the MARS station (K7FAO) group at the F. E. Warren A. F. Base in Wyoming. The reflector is a standard Kalart flash modified slightly to take the 4-prong plug and flash lamp. The camera Mr. Lehmkuhl is using with the electronic flash is a Leica.



RADIO & TELEVISION NEWS

Tape Recorder Counter

(Continued from page 51)

inch brass rod. Twelve-inch lengths of solid brass rod are a standard radio hardware item at any parts jobber.

Assembling the Counter

The spring is first assembled to the rubber bulb. The end result of this operation is seen in Fig. 1. The easiest way is first to select a screw which can be driven into the end of the spring, using the coils of the spring as threads. Then pierce the closed end of the bulb as near the exact center as possible. Push the screw through the hole, with the head of the screw inside the bulb; use a washer if the screwhead is not large enough to insure that it won't itself come through the hole.

Next place a good-sized nut, or a washer and a nut, on the screw, over the top of the rubber bulb. At this point we should have a bulb with a screw firmly fastened into it, threads pointing up through the top. Now fasten the spring to the screw by threading its end over the screw threads and tightening. A little *Duco* cement spread around the top of the bulb and allowed to dry will avoid any possibility of the arrangement coming apart.

Attention goes now to the brass rod and the counter. Fig. 1 shows how the assembly will be mounted. Select the mounting point and dimensions for the particular recorder first. With the *Concertone* the lower end of the rod was simply pushed into a 1/4-inch hole in the edge of the wood case and the over-all rod length is 8 1/2 inches. Use a ruler, or preferably a metal measuring tape, to figure over-all length once the rod has been bent, so that the counter at the rod's end will sit about 2 inches above the upper face of the take-up reel and about 1 inch from the center of the spindle. Then cut the rod to this length, locate the bending point, and bend the rod in a vise. Bend it gently, using if possible a round-edge piece of stock in the vise so that the bend has a good, big radius. This rod can be broken.

Placing the counter experimentally on the inner end of the rod, determine the best angle from which to view the numbers. Then mark the rod and drill two holes at this angle by which to mount the counter. The counter skirt has two holes tapped for 4-40 screws and they can be used as if available screws are just long enough to come flush with the skirt surface of the rod. The writer did it the other way, however, drilling out the threads and threading the brass rod holes for 4-40 screws which were placed through the top. If taps are not at hand, drill ordinary holes and use lockwashers and nuts under the rod to hold the screws.

Now mount the rod-counter assembly. The easiest way is that shown—simply a 1/4-inch hole in the wood case, into which the lower end of the rod is pushed. This also allows the rod to be swung out of position if necessary, without demounting it.

The inner diameter of the spring should, if possible, be slightly less than the outer diameter of the counter shaft, so that the spring can simply be pushed over the shaft. If the spring is too large, make a sleeve to fit over the counter shaft. A little tape or thin metal or foil is usually sufficient. There will be no occasion to remove the spring from the counter so it can be made solid by any necessary means.

The assembly is now complete. After a take-up reel is in place on the spindle, the counter is engaged by pushing the rubber bulb down over the spindle end. When the reel is to be removed, just pull off the bulb, and let it dangle at the end of the spring.

On the *Concertone* the center hole of the plastic NARTB reel adapter was countersunk about 1/16 inch with a half-inch drill; this revealed a little more of the spindle for better seating of the rubber bulb. The same can be done with adapters or reels on other machines if it is an advantage.

Using the Counter

It is desirable to be able to locate a given point on a reel of tape by winding to the same counter number no matter how many times the reel is removed from the recorder and replaced. Therefore, we set up one rule of procedure which works as follows:

Place the full reel of tape on the supply spindle or adapter. Thread the end into the notch of the take-up reel. Now give the take-up reel one counterclockwise turn by hand, reaching the point when the second layer of tape just begins. At this point stop the reel. With the counter at 0000 place the rubber bulb over the take-up spindle. Then begin operations. This insures that the zero count is always just at the same point on every tape and on a given tape every time.

The bulb should remain on the spindle until the end of operation when the supply reel is again full and the counter back to zero. In this way it always indicates exactly what section of tape is against the heads, since it travels with the tape in forward and reverse operation as well as in fast forward and rewind. If the take-up reel is to be removed when full, as is true when using both tracks of most dual-track machines, the counter will be far from zero. Either omit to use the counter in these cases or first rewind the reel, disconnect the bulb, then get the tape back to the take-up reel with fast forward.

The ideal way to connect a counter would be so that each count would indicate a specific length of tape. This would mean connecting it to the capstan, in which case it would fall out of step on rewind and fast for-

A MONTH OF SPECIALS!

SPECIAL! No need to worry about high transportation costs, for Platt will cheerfully refund your local cartage with any purchase at either store listed below.

SPECIAL!

Merit M-345 VTVM

4 1/2" meter with adjustable pointer to zero center for TV & FM discriminator alignment. AC-DC Range: 0-2/10/100/500/1000 V. 5 Resistance Ranges: 2 ohms-1000 megohms. DIB scale for audio and gain measurements. Completely wiped, tested—ready for use—SPECIAL WHILE THEY LAST! **\$19.95**

MULTI-TESTER FOUNDATION BIAS METER I-97A

Complete, Brand New. Special! **\$5.95**

TUBES BRAND NEW! JAN! BOXED! TUBES

SPECIAL! Add only 10% to the price of any tube you buy and receive two at a sensational saving!

1022	69c	114B	29c	841	29c
1023	53.75	215A	09c	843	17c
2022	49c	221A	29c	863	19c
2026	09c	318A	20c	1020	19c
2027A	09c	388A	59c	7103	19c
3022	\$1.19	471A	\$1.19	0002	69c
3100	39c	532A	\$1.19	F114B	45c
7C4	39c	722A	99c	RK34	99c
12KB5	39c	801A	19c	VR02	14c
15H	39c	820	39c	VT127	15c
30/44	29c				

HEADSETS

HS-23 high impedance. BRAND NEW with ear pads. **\$5.95**

HS-33 low impedance. BRAND NEW with ear pads, cord and PL54 plug. **6.45**

HS-35, used. **1.89**

CS-307A Cordis, 8 ft. NEW. **\$1.49**

H-10/U high impedance. Includes two receiving units. **3.95**

HS-16 high impedance—used. **.98**



BC-221 Frequency Meter

Real Value! QUANTITY IS LIMITED—so first come, first served. They are just like new, with original calibration charts. Range 125-20,000 KC with crystal check points in all ranges. Complete with crystal and tubes. **\$139.50**

MODULATED TYPE **\$169.50**

MODULATED TYPE WITH AC Power Supply **189.50**

These Frequency Meters are factory treated, checked for frequency alignment and GUARANTEED.



SCR-27AN COMMAND and ARC-5 EQUIPMENT

RECEIVERS USED EXCELLED NEW

BC-453—190 to 550 KC.	\$29.95		\$49.95
BC-454—3 to 6 MC.	6.95 (8515)		24.95
BC-455—6 to 9 MC.		\$13.95	19.95
1.5 to 3			34.95

TRANSMITTERS

A-958—2.1 to 3 MC.			29.95
BC-457—4 to 5.3 MC.		14.95	29.95
BC-458—5.3 to 7 MC.	9.95	14.95	29.95
BC-459—7 to 9.1 MC.			24.95
T-15 ARC 5—500 to 800 KC.			29.95

ADDITIONAL EQUIPMENT

BC-456 Modulator			7.29
BC-450 Control Box (3 Receiver)	1.49	1.95	2.75
BC-451 Control Box (Transmitter)	1.29	1.79	2.39
BC-442 Relay Unit (ANT)			5.69
Plugs: PL-147, 148, 151, 152, 153, 154, 156 EACH			1.25
Flexible Shafting with gear to fit receivers			2.69
3 Receiver Rack	1.79	2.29	2.98
2 Transmitter Rack	1.69	2.39	3.97
Single Transmitter Rack		2.95	3.95
DM-33 Dynamotor for Command Set.		1.95	

MOUNTS for Above Racks.

ARMY TEST UNIT 1-236

Meter is contained in a metal box 5 1/2" long x 3 3/4" wide x 3 1/4" deep. Comes complete with test leads and instruction book. Can be used for testing between AC and DC measuring resistance of circuits, checking fuses and testing capacitors.

SPECIAL \$4.19



SPECIAL!

20 LBS. of ASSORTED RADIO PARTS

A terrific buy at only **\$1.99**



FIELD TELEPHONES

Army surplus, completely reconditioned and electrically tested, using 2 flashlight cells and a pair of interconnecting wires. GUARANTEED.

New \$28.95. LIKE NEW **\$22.95**



MINIMUM ORDER \$2.00

Immediate Delivery—Send 25% deposit on C.O.D. orders. All shipments F.O.B. N.Y.C. (N.Y.C. residents add sales tax to your remittance.)

PLATT ELECTRONICS CORP.

Dept. A, 489 Broome St., N. Y. 13, N. Y.

PHONES: WO 4-0827 and WO 4-0828

BRANCH STORE: 159 Greenwich St., N.Y.C.

The ideal replacement cartridge!

TITONE

Revolutionary High-Fidelity CERAMIC PICKUP

No other pickup offers all these great advantages

Only 2 models replace 89% of all present cartridges • Ideal for records of all speeds • Hundreds of thousands already used by leading manufacturers as original equipment • No preamplifier or equalizer needed • Unaffected by temperature or moisture • Long life on shelf and in use • Wide adaptability and simple replacement • High sensitivity • Wide frequency range • Low distortion • No hum pickup • Superior tracking ability • Proper groove fit

Replacement Chart and Literature Available



TITONE PLAYAL

— for all records. With replaceable 1- or 3-mil sapphire or 2-mil osmium needle.

\$7.50 List



TITONE TURNOVER

—with unique, replaceable dual sapphire needle assembly. (Only needle rotates).

\$9.50 List

Electronic Applications Division

SONOTONE CORPORATION

Elmsford, New York

ward, or using a separate roller, which would create the danger of wow and flutter.

The present method of connection—to the take-up reel—means that the count is not proportional to tape length. At the start each turn of the take-up reel pulls a rather small amount of tape. Toward the end of the tape, when the effective outer diameter of the reel is rather large, each revolution takes up a much larger length of tape.

The "Timing Chart" of Fig. 2 allows the operator to time selections by using the counter, despite this non-linearity. It is calibrated for use with an NARTB take-up reel or hub and for speeds of 7½ and 15 inches-per-second. The horizontal axis is calibrated in take-up reel revolutions as indicated on the counter; the vertical axis shows time in minutes. Both calibrations are repeated along the curve to save time and temper in tracing graph lines back to the axes.

Suppose a selection is to be timed. The beginning is located on the tape and the counter number recorded—suppose it is 100. Then the end of the selection is found and its counter number jotted down—say 650. Assuming the tape speed was 7½ inches-per-second, reference to the chart

shows that 100 is equivalent to 3 minutes and 650 is equal to 22½ minutes. Subtracting 3 from 22½, we find that the time for the selection is 19½ minutes.

The counter is useful for purposes other than timing. Sometimes, for example, several selections are on a tape but only some of them are to be transferred to a disc. The usual procedure would be to edit the tape by cutting and splicing. This waste of time and tape can be avoided merely by noting the counter numbers at the ends of the wanted selections and the beginnings of the following desired selections. When dubbing to disc, the gain controls are closed when the first selection ends, the tape is rolled fast forward until the counter indicates the next desired selection is ready, then recording resumed. With a little practice the "dead air" during the forward roll is at a minimum. Broadcasters will also find the counter useful for cueing and for timing, all without the necessity of cutting and pasting tape.

For a very small investment of time and money, the counter saves a good deal of wear and tear on nerves and temper, and opens up new fields for every tape recorder owner.

—30—

IMPROVING INTERCARRIER SOUND SYSTEMS

By CHARLES ERWIN COHN

THE usual intercarrier sound system used in low- and medium-priced TV sets comprises a pentode driver stage followed by a ratio detector feeding the audio amplifiers, with the ratio detector being depended upon to eliminate the AM impressed on the sound carrier during the intercarrier heterodyning process. However, since the limiting properties of the usual ratio detector are far from perfect, some buzz is unavoidably present. What is needed to eliminate this is positive limiting action in the driver stage, which can be provided by replacing the pentode driver with a 6BN6 limiter, as shown on the accompanying schematic.

The 6BN6 gated-beam is usually used as a combined limiter and discriminator, but if the existing ratio detector is in satisfactory condition there is no reason to replace it with the full 6BN6 circuit. Therefore, this tube is used here as a limiter only.


On the schematic, all unlabeled components are those which are already in the set, so only a few new components are needed. It is necessary to add a 1000 ohm potentiometer for buzz control, which must be mounted on the rear of the chassis where it is accessible for adjustment. The screen and plate dropping resistors R_1 and R_2 may also have to be changed to apply the correct operating voltages to the 6BN6. R_1 should be sufficient to keep the accelerator voltage at 100 volts or less at a current of 10 ma. For example, 2200 ohms is a good value for a 120-volt supply. R_2 , however, serves only a filtering and decoupling function since the plate voltage rating is high, and thus should be around 1000 ohms or less. All grid leaks and condensers are removed, so that the grid can have a d.c. path to ground through the take-off coil.

The grid input (terminal 2 of the 6BN6) goes to the sound take-off coil in the TV set.

Alignment and adjustment are simple but, like all intercarrier alignment, should be done with an actual TV signal to insure accuracy. The ratio detector transformer is aligned in the usual manner, after which the signal is attenuated by some means until it is below the limiting threshold and noise appears. Then the sound take-off coil is peaked up and the signal then restored to normal. The buzz control is then adjusted for minimum buzz. Since the optimum adjustment of this control depends on signal level, it should be adjusted under operating conditions on the worst channel.

This circuit will do an excellent job of eliminating buzz, and is also effective on impulse noise. However, it will not be effective on signals which are below the limiting threshold, nor will it eliminate excessive downward modulation. Due to its improved properties, it might also be an effective circuit for use with FM receivers and separate-sound TV sets. —30—

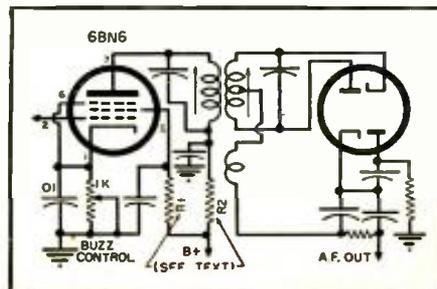A simple circuit change for intercarrier television receivers which provides positive limiting action in the driver stage.



RADIO & TELEVISION NEWS

Hearing Aid (Continued from page 47)

When a 22½ volt "E" battery is used, adjust the bias by connecting a 5000 ohm, ½ watt shunt resistor between "A—" and "B—" (effectively shunting the 1500 ohm bias resistor for the output stage).

The penlight cell used as an "A" battery may be replaced with one of the newer mercury cells, either to obtain a more compact layout or to obtain longer battery life (depending on the size mercury cell chosen). For the maximum in "A" battery life, use the Mallory type RM-1200 cell.

If the reader desires to achieve the most compact design feasible for easy home construction, it is suggested that the following modifications be made, and that the smallest case which will hold the various components be obtained. (1) Omit tone control circuit; (2) Use transformer output with a UTC type SSO-4 transformer; (3) Use a 15 volt "B" battery (Bugess U10); (4) Use a Mallory RM1000 "A" battery; (5) Use the smallest microphone available to the builder; and (6) Omit the output jack and wire the earset directly into the circuit.

Centralab recently announced a new 3-stage printed circuit amplifier which is even smaller than the type PC-200 used in the model shown. The use of the later version would permit an even further reduction in over-all size. However, the author was unable to obtain one of these newer amplifiers, even after contacting a number of distributors, and it appears likely that the PC-200 will be the most readily available unit for some time.

In this article, the author has presented the information necessary for a skilled technician to assemble a basic hearing aid; however, no individual should indiscriminately build and use a hearing aid without competent medical advice. Whether or not a hearing aid is required should be determined by a physician.

In operation, the tone control is generally adjusted so that speech is intelligible or so that music and other sounds seem realistic to the user. The volume control is adjusted to provide the minimum gain necessary for adequate volume and sensitivity; the "ideal" setting is where the individual's hearing, compensated by the amplifier, becomes normal. With this adjustment, there is a minimum of "blasting" from loud sounds, yet good sensitivity is maintained.

Often, where the individual's hearing with one ear is much weaker than with the other, the earpiece is placed on the weaker ear so that the hearing aid acts to bring the weaker ear up to "normal."

While battery life is fairly long due to the low current requirements of the subminiature tubes, the life may be extended even further by turning the unit "off" whenever it is not needed for long periods of time.


Only ROHN TOWERS ARE PROVED IN CONSTRUCTION DESIGN, USE & SALES

3 standard self-supporting ROHN steel towers for your every need!



Famous ROHN FOLD-OVER TOWER
(Pat. Pending)

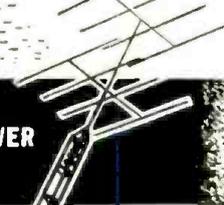Fold Over Tower uses standard tower sections plus an inexpensive easy-to-use "fold-over" kit. The perfect answer to this type tower requirement.



ROHN TELESCOPING MASTS

NO. 5—A 9-in. triangular designed tower especially designed for TV needs. Can be used up to 40-ft. non-guyed or guyed to 80-ft. An economical, yet sturdy, permanent tower. Can be climbed as can all ROHN Towers.


NO. 10—The standard 12-in. design—heavy duty tubular steel, electric welded and heavily cross-braced throughout. Used by thousands coast-to-coast. Up to 50-ft. non-guyed—guyed to 120-ft.

NO. 20—Uses a 14-in. triangular design—the heavy duty tower. Ideal for communications and where greater height is required.

All ROHN towers in 10-ft. sections for easy erection and transportation.

Come in 20, 30, 40 and 50 ft. sizes. Easily erected. Heavy-duty seamless steel tubing throughout.

PLUS A COMPLETE LINE OF ACCESSORIES:

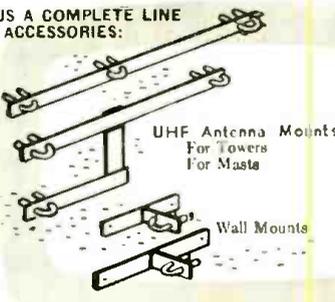

Also House brackets, guy brackets, etc., all Rohn designed!

Contact your ROHN distributor for FREE catalog and Prices or write:

ROHN MANUFACTURING COMPANY

DEPT. RTN
116 LIMESTONE
BELLEVUE,
PEORIA,
ILLINOIS



RADIO CONTROL YOUR MODELS

DELUXE MIDGET 1" RADIO CONTROL. COMPLETE WITH DELUXE FREE BAND TRANSMITTING RADIO, A RECEIVING RADIO & A CONTROLLING BEARING LONG RANGE TO OPERATE MODEL AIRCRAFT, BOAT & AUTO MODELS. ALL THREE UNITS ABOVE SHOWN ASSEMBLY WITH OUR PATENT & TRADE MARK DETAILED INFORMATION & RADIO CATALOG. 25¢ SPECIAL "SUPPLY DIRECTORY" & SUPPLY COUPON. Shipping and Postage Extra \$1.00

DELUX MIDGET 1" RADIO CONTROL \$9.98

RADIO MODELS, BOX 35, DEPT. RT BALTIMORE 6, MARYLAND

MORE CASH

Att.: Schools, Labs, Hams!

Cash in on your surplus Radio Parts & Equipment! We pay more—or trade for something you really need. TV Sets, Mobile Equipment Available for Trade. Write Now!


MARJO SALES CO.
4109 Burbank Blvd.
Burbank, Calif. Cable MARJO

TOPS in TV TRAINING

WANT to get into TV? Then don't settle for LESS THAN THE BEST. Get FULL FACTS FREE about our highly SUCCESSFUL TV Train-at-Home Plan. We TELL you and SHOW you how to Build your own big TV Set (with parts we supply). Learn how to Install, Repair, Service, Resistors, Signals—everything a Top-Flight TV Expert must understand. TWENTY KI'S of Parts, Professional Equipment and Tools included. Make a TV Set operate as smoothly as a precision-made watch. Be ready for a Big-Pay TV Job—and a Big-Pay TV Job will be ready for YOU. Don't confuse CII Home-TV-Training with ordinary home-study courses made up of radio lessons with some TV lessons tacked on. The CII Train-at-Home Plan is MODERN, SPECIALIZED 100% TV INSTRUCTION. Over 24 MILLION TV Sets in use and more thousands sold every week make TV TODAY'S Big BOOMING Opportunity. Get the RIGHT Training—NOW! Then accept a Big-Pay Job—or have a business of your own. Thousands CASHING IN with our Proved Methods. Send for Big FREE Book, "You Can Succeed in Television."

Commercial Trades Institute, Dept. T-19-9, 1400 Greenleaf Ave., Chicago 26, Ill.

CANNON PLUGS

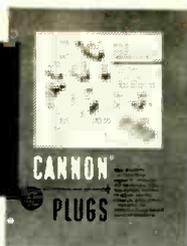

Send for Cannon Bulletin RJC-6
... a special condensed catalog

Covers the Radio, Sound and Miniature Connectors that are available to you through Franchised Distributors, Electrical Wholesalers and Radio Parts Distributors.

TYPE **XL**



FITTINGS: For audio, instrument and related uses. 3 contacts. 15a max., 14 basic shapes. Latchlock coupling. Available at your Radio Parts Distributor.

TYPE **P**



FITTINGS: For audio, TV and instrument uses. 2 to 8 contacts, 30a max., 16 basic shapes. Universally used in sound and allied applications.

TYPE **O**



FITTINGS: 3-contact oval-shaped plugs and receptacles, equipped with latchlock device. For microphones and related uses. 6 basic shapes. 30a max.

TYPE **UA**



FITTINGS: Designed in cooperation with RMA Committee, combining all features of P, O and XL Series. Gold plated contacts. Rubber relief collar and bushings.

TYPE **45-E**



TEST POINT JACKS: High quality phone tip jacks to accommodate ATMA phone tip for laboratory uses. Rugged construction, nylon insulation precision-made for long life.

TV CONNECTORS:

Specialized "LK" and "LKT" plugs used on television cameras and related equipment.

TYPE **U**



SUB-MINIATURE SERIES: Hermetic sealed, vitreous insulated receptacles and Silcan insulated plugs for instruments, relays, transformers and other sealed components.

TYPE **D**



SUB-MINIATURE SERIES: Gold plated contacts. Rack-and-panel or cord mounted disconnect for portable radio and related equipment. Hermetic sealed if desired.

Additional related audio and power Cannon connectors include Types X, XK, M1, GB and BP, all available through selected Cannon Franchised Distributors. See your classified telephone directory.

CANNON ELECTRIC

Since 1915



CANNON ELECTRIC CO., LOS ANGELES 31, CALIF.
Factories in Los Angeles, Toronto, New Haven. Representatives in principal cities. Address inquiries to Cannon Electric Company, Department I-145, Los Angeles 31, California.

RADIO-TV Service Industry News

AS REPORTED BY THE TELEVISION TECHNICIANS LECTURE BUREAU

THE one thing about TV service on which everyone is agreed is that independent service badly needs a dynamic public relations program to remove the fog that beclouds it in the eyes of the average set owner. The public, reading about TV service gyps, assumes that all service businessmen are shady characters who leech a living from those who own TV sets. "Just imagine," said one set owner indignantly to her neighbor, "these TV service people want five dollars just to come out and see what's wrong with our set!" Talk to the next fifty average TV set owners you meet and you will find they all harbor the same feeling.

Day after day, TV technicians working on home service calls take a terrific pounding from set owners about service charges. While it's easy to talk about being nice to customers who speak caustically about service and its costs, it is difficult for a technician to match wits with the vagaries of TV circuitry and with consumer ignorance and consistently maintain a pleasant decorum. It is understandable that customers who have bought "lemons" will sometimes trigger the resentment in a service technician and get told what kind of a set he thinks they bought.

Regardless of who is at fault, it is known that TV set owners are inclined to expect more service out of sets than was built into them in the first place. They have been misled on the need for service and misinformed on what they should expect to pay for competent service when it is needed.

This all adds up to a public relations (PR) job of first magnitude and one that should be of concern to every segment of the industry.

The recognition of the need for a major public relations job in the interests of TV service quite naturally brings up the subject of how it can best be accomplished. Some people feel that an immense program should be launched on a national scale. This idea, however intriguing, fails to take into account the two most basic factors of the problem. The first of these is that any effective public relations program, to be successful, must be geared to the peculiarly local needs of

every TV area. The second factor is the prohibitive cost of a national program that could be localized to meet metropolitan and urban requirements.

Service executives who have studied this problem have reached the conclusion that the best initial attack on it should be made at local or sectional levels. At the present time there are several excellent national campaigns underway sponsored by individual manufacturers, but it has been obvious to service businessmen that even these programs would accomplish little if they are not bulwarked by effective local level public relations programs.

However, regardless of whether you plan a local campaign or a national program, it costs money to do the right kind of a PR job. The question always arises, "Who is going to foot the bill?"

In an attempt to find a workable answer to the problem of financing a badly needed PR program in the greater Chicago area, a group of service operators got together earlier this year and formed the Greater Chicago TV Service Industry Committee to develop a PR program and to find some way to finance it.

A Service PR Program

In Philadelphia, where the Joint Electronic and Radio Committee on Service (JERCS) has been functioning effectively for several years, a sound method for raising funds to finance an effective PR program in the interests of service has been evolved.

The Philadelphia committee is made up of representatives of all segments of the industry in that area. Although there are several organizations in that city whose members are engaged in TV service, practically all of these groups cooperate whole-heartedly in the JERCS planning and in following through to help make selected programs successful.

The basic merit of the JERCS fundraising program is that it provides an opportunity for all elements of the industry to participate, and for each participant to gain some definite promotional value in return for his cooperation.

The Joint Committee has developed

RADIO & TELEVISION NEWS

BUSINESS REPLY CARD

No Postage Necessary if Mailed in U. S. A.

3c Postage will be Paid by

FIRST CLASS

Permit No. 37110

Sec. 349, P. L. & R.

NEW YORK, N. Y.

Radio - Electronic Engineering

EDITION OF RADIO & TELEVISION NEWS

366 MADISON AVENUE
NEW YORK 17, NEW YORK



Enter A Subscription For:

RADIO-ELECTRONIC
Engineering

EDITION OF
RADIO & TELEVISION NEWS



NAME _____

ADDRESS _____

CITY _____ ZONE _____

STATE _____

POSITION _____

COMPANY _____

9-53

I'll pay when Billed

Remittance enclosed

Canada, Mexico, South
America same as U. S. A.
For all other countries add
\$1.00 for each year.

3 years \$10⁰⁰

2 years \$9⁰⁰

1 year \$6⁰⁰

a consumer show which will be given in the Convention Hall in Philadelphia next November. The show will feature prominent TV stars and perhaps recording artists whose services will be made available by the television manufacturers who sponsor their programs. Income from the show will be derived from the sale of admission tickets.

Interest in the show will be built to a high pitch through the use of tickets by set dealers and service operators who will purchase blocks of tickets and use them in special business promotion programs during the Fall months. Dealers will plug the show in their TV receiver newspaper ads and service businesses will promote it in their advertising and direct mail campaigns.

The JERCS program is being handled by Paul V. Forte, an experienced public relations counsel. It is directed by a committee comprised of representatives of the set distributors, parts distributors, set dealers, service dealers, and electronic technicians with the cooperation of manufacturers' representatives and manufacturers in the Philadelphia area.

It is the JERCS' plan to employ the proceeds from this show to carry out an expanded public relations program in the interests of service during the 1953-54 season.

Which Way U.H.F.?

There has been a lot of loose, uninformed talk lately about u.h.f. going down the road to oblivion in the wake of FM. All of this seems to come from areas where u.h.f. pictures have had to compete with good, established v.h.f. service. It fails to take into consideration that u.h.f. has gotten better consumer acceptance in new TV areas than v.h.f. was accorded in its early days.

Of course, u.h.f. has not proven to be the business bonanza that every one hoped it would be and it didn't keep the industry from going into the usual seasonal doldrums when summer weather set in. Perhaps this experience with u.h.f. will finally teach us that "boom" business in television is definitely a thing of the past; that new developments will merely represent a slow, orderly expansion of the industry without boom proportions.

Unfortunately, many of the people who have much to gain from a growing acceptance of u.h.f. on the part of the set owning public in their areas have retarded that acceptance through their uninformed, negative statements about it.


Manufacturers, broadcasters, dealers, and service people all have much to learn about u.h.f. and its peculiar individual requirements to produce good TV pictures. Many dealers have killed interest in u.h.f. by telling customers interested in converters that they wouldn't recommend them—they would only recommend new sets already equipped to tune u.h.f. stations. Many people do not want to trade sets

ORDER BY MAIL FROM "WHOLESALE RADIO"

Equal to \$50 Aerial Systems All Directional TV AERIAL 360° DIRECTRONIC SYSTEM

Exclusive Snyder Engineering and designs cut cost to **\$18.95**

COMPLETE with three 31/2 ft. masts, 75 ft. 3 cond. cable, beam selector sw., guy rings and mtg. base. Electrically beams complete 360° rotation to give clear pic on all channels. You choose direction with directronic selector sw. mounted on or near TV set. Complete double stacked array with 18 hi tensil. double alloy aluminum elements. AX-591 same as TX-599 less masts, guy ring & mtg. base **16.95**

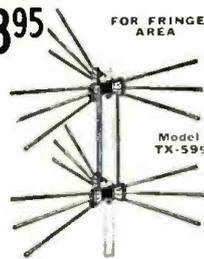

Model TX-599

Beats Any Antenna . . . Anywhere! SUPER 4 BAY DIRECTRONIC! 48 ELEMENTS! ALL DIRECTIONAL! FOR ULTRA FRINGE!

Complete with 6 pos. beam selector sw., 150' tubular tri-x cable, Universal U clamps. Model AX-548. **\$44.95**

Cover All VHF Channels with 2 Arrays SNYDER BROAD BAND YAGIS

- Higher Gain Than Conventional Yagis
- For Fringe and Ultra Fringe

High signal level for sharp, bright pictures. Hi-tensil. aluminum elements; 7 on low bands, 9 on high band. Complete with universal U clamps. Easy to assemble. Space-saver design.



RB-6 for Ch. 2 thru 6 **\$9.95**
RB-13 for Ch. 7 thru 13 **\$4.95**

Stancor CR Tube Brightener

Gives CRT's Longer Life!
No Soldering Needed!



Light and compact. Requires no connecting to AC line. Extra long 18" leads. Install anywhere in set. Autotransformer type with hi-lo sw. Choice of 2 degrees of brilliancy. Complete with bracket and screws for mounting. **\$2.94**
P-8192

RESISTOR & CONDENSER BARGAINS
100 ASS'T RESISTORS, 1/2-1-2 W. \$1.95
50 ASS'T MICA COND. 5mmf to .001 mf. 1.95

SPECIAL! PRICES SMASHED!

Westinghouse Gamma Counter Tubes

Was \$50. Alpha, Beta and Gamma Counter tubes. Self-quenching. #5979 BS-1 **\$8.95**

Was \$35. Gamma Counter tubes. Self-quenching. #5980 BS-2 **\$4.95**

FREE! Write for new value-packed "FYI" bulletin #115. Write for our big audio guide, "Hi-fidelity Magic."

WHOLESALE RADIO PARTS CO., Inc.

311 W. BALTIMORE ST., BALTIMORE 1, MD.

CODE BENDING SPEED
RECEIVING

Be a "key" man. Learn how to send and receive messages in code by telegraph and radio. Commerce needs thousands of men for jobs. Good pay, adventure, interesting work. Learn at home quickly through famous Candler System. Qualify for Amateur or Commercial License. Write for FREE BOOK.

CANDLER SYSTEM CO.
Dept. 2-K, Box 928, Denver 1, Colo., U.S.A.

FACTORY REPAIRS
ON ALL MAKES AND TYPES OF
TEST EQUIPMENT
Write for BIG NEW FREE Catalogue
GENERAL ELECTRONIC DIST. CO.
98 PARK PLACE, NEW YORK 7, N. Y.

Compare With Any Scope At Any Price! SENSITIVITY—LESS THAN 10 mv.

PRECISE 300 K 7" SCOPE KIT

Immediate Delivery!

Has true electronic sweep magnifier. Automation control. Push-pull vertical beam input thru output; push-pull horizontal; internal blanking and Z modulation with blanking amplifier. Driven and non-driven sweep. Over 3 MC flat response (3 db). DC amplifiers. Cathode follower input on vert. and horiz. Internal calibrator. Horiz. and vert. step-ping attenuator. NEW 7" tube. Highest sensitivity. COMPLETE WITH ALL TUBES, HARDWARE AND STEP-BY-STEP CONSTRUCTION BOOK.



MODEL 300 K

\$94.95

More Famous PRECISE Kits!

630K RF-AP-TV & MAPKER GENERATOR KIT. \$33.95
(630KA pre-assembled head \$38.95) (630W wired) **\$53.95**
635K UNIVERSAL AF SINE, SQUARE & PULSE GENERATOR KIT **\$33.50**
(635W wired) **\$52.80**
610K RF SIGNAL GENERATOR KIT **\$23.95**
(610KA pre-assembled head \$28.95) (610 wired) **\$39.95**
907K VTVM KIT WITH 7 1/2" METER **\$38.98**
(907 wired) **\$57.98**

For Greater Record Enjoyment G.E. RECORD COMPENSATOR

Five selective settings including two scratch filter positions. Noticeable high freq. distortion and background noise greatly reduced. Easily connected between pick-up car-tridge and pre-amp input. **\$8.95**



SPECIAL! 12" PM SPEAKERS

Excellent fidelity! Atlas V PM speakers. Special purchase from maker, specially priced to you. **\$4.95**
10 watts peak output

Famous FAIRCHILD DIAMOND CARTRIDGES




Replace any modern pickup with this new cartridge and enjoy music as never before.
215A—1.0 mil LP stylus. **\$37.50**
215B—2.5 mil stylus LP.
215C—5.0 mil stylus LP.

Why Waste Time Waiting for Test Pattern

RMS TV BAR GENERATOR

Makes Actual Bars on Any TV Screen

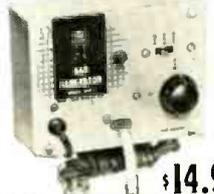

\$14.95

Make accurate, on-the-spot linearity adjustments. No chassis removal necessary. Operates directly into ant. terminals. Adj. number of horiz. & vert. bars. Complete unit. Order RMS BAR-L.

FREE! U.H.F. and "THE VERSATILE CRYSTAL PROBE"

Solve your U. H. F. ANTENNA PLACEMENT and ORIENTATION problems the easy way!

★
Get maximum picture strength - eliminate ghosts - no more roof-top shouting - no expensive field strength meters needed!
ONE MAN CAN DO IT!

★
Write for FREE bulletin today and other information about KLIPZON products.


UNITED TECHNICAL LABORATORIES
203 LITTLETON RD. ★ MORRISTOWN, N. J.

Discover WHAT INCREASED AIR-LOADING DOES FOR YOUR SPEAKER

Super Horn[®] LOUDSPEAKER ENCLOSURES

A unique principle of acoustical engineering . . . exclusive with Super-Horn . . . gives peak free, smooth bass response. Superbly designed in beautiful dark or natural mahogany, or blond finish, Super-Horn enclosures are available for 12 inch and 15 inch speakers.

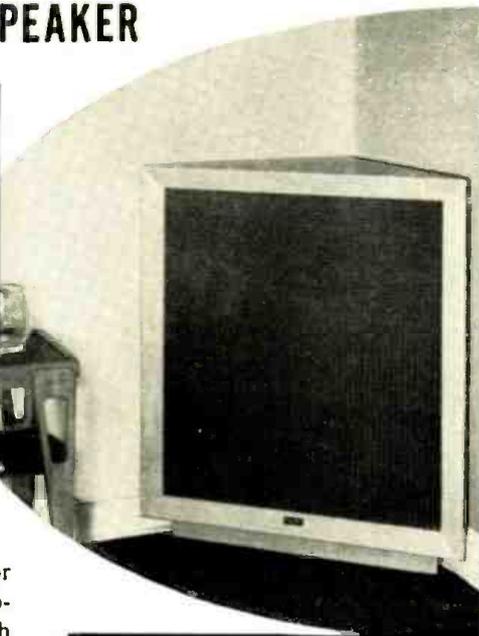WRITE FOR TECHNICAL LITERATURE, CATALOGS & PRICE LIST



GATELY
DEVELOPMENT LABORATORY
BARRINGTON, NEW JERSEY

now—they feel that color television will be available soon and when they trade they will want a color TV receiver—but they would like to buy a converter for the present set to receive a newly added u.h.f. station. A negative attitude on the part of a dealer toward conversions will not sell a new dual set and it may certainly kill the customer's interest in u.h.f.

The u.h.f. broadcaster's biggest problem is to build up a viewing audience as rapidly as possible to be able to get top programming. Where v.h.f. broadcasters are entrenched, they are going to do everything in their power to hold back, if not kill, that competition for their TV audience.

From a purely selfish standpoint, the service industry stands to gain most by helping to sell every new TV service that is offered. The sale of a converter means another service possibility in the user's home—a bigger market for service.

The pattern of interest in u.h.f. among service dealers and technicians is following that of the early days of v.h.f. Service people do not take a really active interest in u.h.f. until a station is practically on the air and then there is a mad scramble to learn something about it. This has resulted in independent service having to share the responsibility for the troubles of u.h.f. as reported in all of the surveys of present u.h.f. markets.

There is no reason why a service businessman cannot develop a high degree of proficiency in his technicians on u.h.f. long before they have to work with broadcast programs and sets in the customers' homes. Many simple devices can be easily built that will enable technicians to work with signals in the u.h.f. band to check antennas, transmissions lines, and converters. With all of the equipment and information currently available, service people should be right on top of this whole u.h.f. problem.

Color Television

Late in June, RCA-NBC filed a petition with the FCC for approval of their compatible color television system. The industry-wide group, the National Television Systems Committee, completed their report and filed their petition with the Commission a short time afterward. Since the technical standards proposed in both petitions are said to be identical it is generally felt that the FCC will set an early date for hearings that will result in the acceptance of this industry-endorsed compatible color TV system by the first of the coming year.

Industry opinions vary considerably as to the length of time it will take to get color television receivers into large scale production.

RCA, which is the most optimistic, anticipates the production of only about 2000 tri-color tubes per month, six to nine months after standards are set by the FCC. While it is expected that imminent prospects for color television will slow down sales of new sets

The COMPLETE line

DR Double-Reentrant Projectors

Paging & Talk-Back Speakers

ALNICO-V-PLUS Driver Units

Dual Speakers

for EVERY

Public Address need!

Tweeters

FULL-GRIP, VELVET-ACTION Mike Stands

WRITE NOW for FREE Catalog 553

ATLAS SOUND CORP.
1446 39th St., Brooklyn 18, N. Y.
In Canada: Atlas Radio Corp., Ltd., Toronto, Ont.

ALNICO MAGNET SPECIALS! Type (8 1/2" sq. x 5/16" dia.) Excl. for Wire or Tape Erase; spkr. or phone magnet . . . 49c 12 5.00
BAR MAGNET (1 1/2" x 3/4" x 1/2") polished . . . 39c 12 4.00
ROUND BAR (1 1/2" x 5/8" x 1/2") polished . . . 69c 6 3.50
ALNICO CHIP MAGNETS—small irreg. shapes, approx. 80pes.oz. per oz. 15c 51.50 lb.
ALNICO MAGNET KIT of 10 assorted Rods, etc. . . \$1.98
(WRITE FOR LATEST "ALNICO" SUPPLEMENT)

CRYSTAL DIODES—1N21 . . . ea. 89c 10 57.95
1N23—ea. \$1.29; 1N21B—ea. \$2.49

12V. VIBRATOR—400ma. 0.1b. 200V. . . \$1.49

16" TV LUCITE MASK-ESCUTCHEON (rnd. sides) gray edge masking. Shpg. wt. 3 lbs. . . 1.69

14" RECT. TV FRAME—gold finish metal98

DPDT BAT TOGL SWITCH—(A/125V, ea. 49c) 12 5.00

1/40 HP AC MOTOR (Hobbs & Myers) 115V, 1650 RPM, with capacitor & switch (7 lbs.) . . . 4.95

HI-FI CRYSTAL HAND MIKE—hi-impedance, mounted bakelite case, 5 1/2" ft. cable . . . 3.95

HAND MIKE CASE only—mounted black bakelite, rubber mouthpiece, 2" 1 1/2" . . . ea. 49c; 12 5.00

HEADPHONES—sensitive Alnico powered, adjustable forks, 5 ft. taped cord . . . 2.49

SPONGE RUBBER PHONE CUSHIONS—per pair49

HB-7 HEADPHNS. leather, less blnd. ea. 69c; 10 7.50

PL-54 JK-26 CONNECTORS . . . set 39c; 10 3.50

33 CONTACT CONNECTORS (Jones 2-1131)—Cable female; panel male, 5ft. cables . . . set \$1.29; 5 5.00

T-44A MAGNETIC MIKE—complete, brand new .98

LUMINOUS TAPE—GLOWS IN DARK (1 1/2" x 10")39

2000 OHM LAB. POTENTIOMETER (Dialux) 5% accuracy, w/w. 2 1/2" bakelite shaft—ea. 98c; 12 10.00

MIDGET PUNCHED CHASSIS for 4 min. tubes 61x20x1 1/2" . . . ea. 29c; 4 1.00

"BUY OF THE MONTH"—New "Jumbo" RADIO ELECTRONICS PARTS KIT—DON'T MISS THIS BARGAIN! In inventory odds & ends: COILS, RESISTORS, CONDENSERS, WIRES, SOCKETS, CONTROLS, SWITCHES, etc., etc. Shpg. wt. 20 lbs. \$3.95

W.E. PHONE UNIT (Type P-11), 1000 ohms DC, Nickel plated case each \$2.49

BARGAIN ASSORTS! 1. **MOLDED BAKELITE CONDENSERS** (Micamold), 20mmf.-2mf. 200-600V. Kit of 50 assid. \$1.98; 100 2.98

ELECTROLYTIC tub. 77 cap. Kit 8 assid. . . . 1.98

RADIO HARDWARE TREASURE—Full lb. can of Nuts, Screws, Washers, Lamps, etc. . . . 89c; 3 lbs. 2.49

MICA TRIMMERS—Incl. ceramic, 1.5 assid.69

ROTARY SELECTOR SWITCHES—Incl. multideck, 1 1/2" shaft . . . Kit of 5 assid. . . 1.75

W.W. RESISTORS—3W-20V. Kit of 10 assid. . . .98

"DIRECT FACTORY SPEAKER REPAIRS SINCE 1927"
Min. order \$3.00. 20% deposit req. on all C.O.D.'s
Please add sufficient postage—excess refunded.

LEOTONE RADIO CORP.
67 Day Street
New York 7, N. Y.

in all TV areas, this would not become a really serious problem if the TV retail industry will become sales-minded and sell the product as it can and should be sold.

The decided advantage of the NTSC system is that it is completely compatible with the present monochrome system. No one who now owns a TV set will have to discard it when broadcasters change to color telecasting. It will accept the color TV signal and produce a better black-and-white picture from it than is now available from the average telecasting station. There is a very simple reason for that. The basic signal in a colorcast under the NTSC standards is a high resolution monochrome interpretation of the picture. Color is added by a second signal which is fitted into the present 6 mc. channel. Color information is interspersed between the black and white picture information. Present TV receivers will accept the high resolution monochrome part of the signal but will reject the frequencies that represent the color information. The result is a very fine black-and-white picture on present sets from an NTSC system color telecast.

TV service technicians could render a signal service to the entire industry if they would present the color television story properly to the people who will be asking them about color TV. Most set owners are greatly influenced in their feeling about what to buy and what not to buy in TV sets or

equipment by the information they get in reply to questions they put to the service technicians who call to fix their sets. As the RCA and NTSC system moves toward acceptance by the FCC it will undoubtedly get increasing attention in the daily papers and, of course, feature writers will have a field day writing articles on it for the consumer weeklies and monthlies. Set owners will be interested, of course, and there may be a tendency toward wanting "temporary" repairs to failing TV sets because the owner thinks he may soon be able to trade the old one in on a new color TV receiver. The public is like that. They skimp on automobile maintenance and repairs for a year in anticipation of trading the old jalopy on a new model.

What should a TV technician say to a set owner who inquires about color TV and how soon it would be available?

The best thing, of course, is to tell the truth. The truth in this instance would be phrased like this:

"Mr. Set Owner, no one can tell you for sure when you will be able to buy a color television receiver at a price you would be willing to pay. Color is the glamor phase of TV but to add that glamor a great many very complicated production problems must be solved.

"But there is one thing that color television broadcasts will do for you on this very fine set you now own. They will give you the best black-and-

white pictures you ever have seen on this set. And you won't have to spend a cent to get those extra good pictures on this set.


"In a few years perhaps, color television sets will be sold at a reasonable price and then I'm sure you will want to buy one. But even then, you will probably want to keep this set as a second or spare set to use when your more complicated color set is tied up for service."

Customer Relations

Many parts distributors perform a real service for their service customers by sending out a locally prepared news bulletin in the form of a house organ. Where the news is prepared by competent local writers it usually carries a fast analysis of national developments that have a special significance in the distributor's local market. This monthly house organ also serves as a showcase for products the distributor has stocked for special sale that his service customers might not otherwise have known about.

One of the most informative house organs of this type is the "Almo Broadcaster," a monthly four-page bulletin mailed to its customers by the Almo Radio Company of Philadelphia. This company, headed up by Morris Green and Al Margolis, is a merchandising-minded distributing firm that now operates eight stores located in Pennsylvania, New Jersey, Delaware, and Maryland.

Just Cut

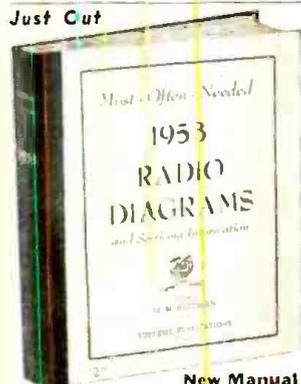

New Manual

Be prepared to repair quickly all new 1953 radio receivers. In this big single volume you have easy-to-use, extra large schematics, needed alignment data, replacement parts lists, voltage values, and information on stage gain, location of trimmers, and dial stringing. Get almost every 1953 radio. Giant size, 8 1/2 x 11 1/2" manual style, sturdy binding. Price, only **\$2.50**

New Supreme 1953 Radio Manual

Now you can benefit and save money with Supreme amazing scoop of 1953. This one giant volume has all the service data you need on all recent radio sets. A full year of models of all popular makes, home and auto sets, portable radios, combinations, changers, all included. The full price for this mammoth 1953 manual is only \$2.50, nothing else to buy for a whole year. Other Supreme radio service volumes for previous years (mostly at \$2), TV, and UHF manuals are described below and at right.




SUPREME RADIO MANUALS FOR PREVIOUS YEARS

Use Supreme manuals to repair all radios faster, easier, save time and make more money. Here is your lowest priced service data. Covers all years, from 1926-28 to 1953 models, in 15 volumes. Used by 141,000 street servicemen. Most volumes only \$2 each, see coupon. Average volume 192 large pages, 8 1/2 x 11 inches. Quality printing, manual-style binding. Amazing values. Be wise, use these manuals to get all needed diagrams, parts lists, alignment facts, and service hints, at the smallest cost. Sent no-risk coupon.

SUPREME TELEVISION SERIES

Here is your complete source of TV and UHF service data. These manuals at only \$3, \$2, and \$1.50 each are amazing bargains and defy competition. Each manual covers a whole year of models, using original factory material. Include giant double-spread circuits and blueprints, alignment procedure, voltage charts, test patterns, wave forms, factory revisions, and helpful service hints. Select volumes from list below and send no-risk coupon.

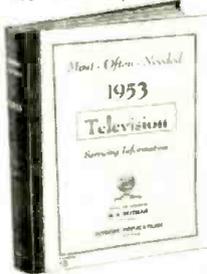

1953 TV, \$3

New giant volume of TV factory data has everything you need on recent sets. 192 pages, 8 1/2 x 11", + double-spread blueprints. Only...\$3

- 1952 TV Manual \$3
- 1951 TV Manual \$3
- 1950 TV Manual \$3
- 1949 TV Manual \$3
- 1948 TV Manual \$3
- 1947 FM & TV, \$2
- 1953 UHF Units \$1.50

RADIO-ELECTRONICS

NEW AMAZING HOME-STUDY COURSE OFFER



Large, 3-volume course

Here is the most amazing bargain in electronic training. For only \$3.95 (full price) you receive a complete course of 24 large lessons. Covers every topic of radio, electronics, with large lessons on TV, FM, audio, etc. As an extra, every page has teacher-comments to guide you and supply additional help. Includes self-testing questions, 427 drawings, pictures, and diagrams. Compare lessons by lesson with the best \$200 home-study correspondence courses. Price complete, 3-in-1 volume, 53 lessons, only **\$3.95**

Supreme Publications
Sold by all Leading Radio Jobbers

September, 1953

NO-RISK TRIAL ORDER COUPON

SUPREME PUBLICATIONS, 1760 Balsam, Highland Park, ILL.

Radio Diagram Manuals

- New 1953 Manual, \$2.50
- 1952 Radio
- 1951 Diagrams } EACH
- 1950 Manual } \$2.50
- 1949 Radio
- 1948
- 1947
- 1946
- 1942
- 1941
- 1940
- 1939
- 1926-1938 Manual, \$2.50

PRICED AT ONLY **\$2** EACH

Send Radio Manuals checked at left and TV Manuals below. Satisfaction guaranteed or money back.

- Practical Radio & Electronics Course...\$3.95
- 1953 TV Manual, \$3. 1953 UHF Units, \$1.50
- 1952 Television Manual, \$3. 1951 TV, \$3.
- 1950 Television Manual, \$3. 1949 TV, \$3.
- 1948 TV, \$3. 1947 TV & FM, only \$2.

- I am enclosing \$..... Send postpaid.
- Send C.O.D. I am enclosing \$..... deposit.



Name:

Address:

Music Lovers and Professionals

RECOGNIZE THE INIMITABLE

MODEL 12A4
1C WATT

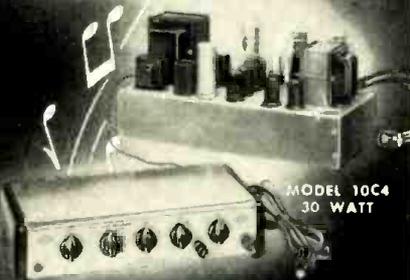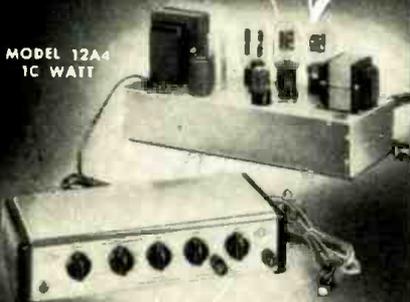

MODEL 10C4
30 WATT

Naturalness
IN SOUND
REPRODUCTION



MODEL 7
SELF-POWERED PRE-AMP

AFFORDED ONLY

BY

BROOK

HIGH QUALITY
AUDIO AMPLIFIERS

Write today for complete technical data;
also name of nearest dealer. Dept. RJ-3

BROOK ELECTRONICS, INC.

First in the High Quality Audio Field Since 1934
34 DeHART PLACE, ELIZABETH, N. J.

The news features of the "Almo Broadcaster" are written especially for it by competent writers. A typical example of the timeliness of its articles is the following story prepared by Paul V. Forte about G-E's summertime service business program based on a contest:

"General Electric is running a contest for service operators. All you have to do, in fifty words or less, is tell the company how you would spend \$2500 to improve your service business and, presto, you may get a check in that amount from G-E to do so. Of course, the fifty words go on a special blank which you pick up at your G-E distributor, usually with the purchase of G-E parts or equipment.

"To my mind, this is a wonderful contest, even if you don't win the main prize or one of the numerous lesser ones. The mental exercise it should give every service dealer and operator is something he should undertake, whether G-E gives a prize for it or not. After all, there's the bigger prize of getting more and better television service business which a lot of service people could use right now.

"Since I am not a service dealer or operator, I have no right to be in the contest. However, I have this little space in the 'Almo Broadcaster' and, with no hope of winning any prizes, I'm going to tell G-E what I would do with that \$2500.

"First, I would recognize that any kind of service business is based on the extent to which the public has confidence in me, my company, and the company which I keep. I would surround myself with name brands and ride the coattails of name brand national advertising. I would obtain, imprint with my own name, and distribute all the literature that name brand manufacturers are constantly making available.

"Second, I would spend part of that \$2500 to provide myself with adequate but economical addressing and mailing machines, place the name and address of every TV owner I could locate on plates, and proceed to make Uncle Sam my best salesman via the post office. My mailing would go out regularly and be interspersed with mimeographed special offers and observations on the intricacy of television, as well as its need for expert service of the kind I offer.

"Third, I would get thousands of copies of 'Service Management's' national average price chart, with my imprint, and send them out to every customer before his next service call. I would attach one to every bill that I render and, in this way, persuade the customer to understand and accept fair prices for honest, high grade service and parts.

"Fourth, I would become an active member in my local TV service association and work hard to help it do the job, in behalf of myself and my fellow businessmen, which I cannot do as an individual. I would recognize that the public is quick to accept the service

operator who can be readily identified with a code of ethics in association with other responsible operators.

"Fifth, I would be my own best public relations man and become a member of every possible civic organization in my community.

"Sixth, I would, of course, back this all up with the best in service personnel and equipment that is available.

"There it is. G-E. We'll be interested in hearing who wins the big prize." -30-

NETWORK FACILITIES

FIVE years ago the Bell System opened for commercial use 916 miles of television channels to provide network service to twelve stations in five cities.

These facilities have now been extended to some 34,000 channel miles enabling more than 130 stations in 87 cities to receive live network television programs. Another 13,000 channel miles will be added to the system between now and the end of the year.

Both coaxial cables and microwave radio-relays are used to provide the network service. -30-

NEW YORK AUDIO FAIR

MORE than 20,000 music lovers, audiophiles, and sound engineers are expected to attend this year's Audio Fair to be held at the Hotel New Yorker October 14, 15, 16, and 17.

Paralleling a new high in attendance will be a record-breaking number of exhibitors, more than one hundred of whom have already engaged display space. The Fair this year will occupy three floors instead of the two floors which have sufficed in previous years.

RADIO & TELEVISION NEWS will, as in past years, be represented by its editors. The place: Room 504.

The Audio Engineering Society's annual convention will be held at the same time as the Fair. Technical papers on a wide variety of audio subjects will be presented to the AES membership.

This year's Audio Fair will be open to all interested parties, professional and amateur, free of charge. -30-

Miss Pat Marand, singing star of Broadway's "Wish You Were Here" has been named "Miss Audio Fair 1953" by the Fair's Advisory Committee of Exhibitors.



RADIO & TELEVISION NEWS

Mac's Service Shop
(Continued from page 78)

of an anesthetized rhesus monkey and brought out leads to miniature tube sockets fastened to the animal's body. The monkey recovered quickly from the operation and showed no bad effects, but Dr. Delgado was able to measure the brain waves coming from the electrodes and to send tiny electrical currents deep into the brain of the animal. He found out that by passing a current through different parts of the cortex he could make a resting monkey raise his paws, turn around, yawn, scratch himself, or try to catch imaginary insects. A funny thing was that he could even change the monkey's emotions by passing current through certain parts of the brain. Current through the frontal lobe turned the animal against his favorite bananas. Current through a point midway between the ears in the brain of a savage rhesus monkey changed him into a gentle creature, but the instant the current was cut off he tried to bite.

"The interesting part of all this is that it was possible to assume a certain amount of control over the human machine from without. To a degree, it was possible to control the animal with electrical currents exactly the same as if he were a machine."

"If I may be so bold as to ask," Mac said, "does it look as though these wizard machines are going to take the place of man's brain-cells in the near future?"

"Not in the near future," Barney reassured him, "but there are some who think that eventually cybernetics will do for mediocre brains what the Industrial Revolution did for muscle. Machines will undoubtedly take over many of the simple mental tasks now performed by human beings. So far, though, nature is able to pack a lot more communication and control equipment into a given space than our scientists can. Take an earthworm, for example, and its ability to detect and turn away from light. We could make a machine that would do the same thing by using several photocells, amplifiers, servo-mechanisms, power supplies, etc.; but we would never be able to build all this into the chassis of an earthworm. Dr. Wiener calculates that to duplicate mechanically the million-odd nerve fibers that exist in a human brain would require a machine ten feet high spread over a space equal to 222 football fields."


"Our steady progress toward miniaturization is in the right direction," Mac pointed out. "Transistors ought to help."

There was a considerable silence, which Barney finally broke.

"Say, Mac, I'll not deny that I haven't got a kick out of being the one who does the 'telling' around here

GRAND OPENING!

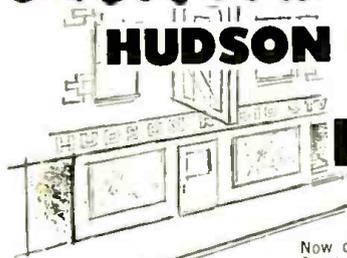HUDSON RADIO & TV CORP.
OPENS SALESROOMS IN
NEWARK, N. J.
at 35 WILLIAM STREET



Now offering to the New Jersey area, the same Huge Stocks and Fast Service that have distinguished our two great New York City Salesrooms!

YOU'RE INVITED TO VISIT US!

We invite our Jersey patrons to drop in, get acquainted, and look over our vast facilities. You'll find complete stocks of all leading brands, Thousands of Special Buys at our Giant Bargain Counters, and a corps of courteous personnel to serve you fast and well! Free souvenirs to all! Come in today!

Audio Headquarters in N. J.
Hi-Fi "Studio 35"
at our Newark Salesrooms

"You Never HEARD It So Good" . . . as you'll hear it in our ultra-modern "Studio 35"! See, Hear, and Compare ALL the Leading Makes of High Fidelity and Sound Equipment!

SENSATIONAL PRICE SLASH!

BRAND NEW Norelco PA2A projection TV Adapters at a price far below wholesale cost! Provides CHOICE of direct view picture on your present set (IR Projects Giant 3'x4' Home Movie Size TV from almost any 10", 12" or 16" set. Ideal for clubs, taverns, schools, churches. EASILY INSTALLED! Supplied complete, ready to set up, with 3NP4 Proj. Tube, 25KV power supply, all tubes, and all accessories, plus detailed instructions. Nothing Else to Buy! In mahogany cabinet 23x26x20" Deep. 87 lbs. **DIRTY-RIFIC LOW PRICE** Reg. Price \$219.50

\$59.50

37"x50" Aluminized Screen \$17.25
*Specify your make and model TV set when ordering.

Famous Norelco DUO-VUE PROJECTION TV



TERRIFIC BUY!

BLOWER
115 Volt, 60 Cycle
SPECIAL LOW PRICE **\$8.95**
Cat. No. S-5075
Please include postage.

If you need a blower, grab this one—it's a BIG BUY! All BRAND NEW, PERFECT, LIMITED QUANTITY. Overall 6x6x5". 2 3/4" intake, 2 3/8x2 1/2" outlet. Wt. 7 lbs. 110 CFM; 3100 RPM. Supplied with 4 Mfd Starting Capacitor.

Write for our Latest BARGAIN SUPPLEMENT No. H-27 Just Out!

HUDSON
RADIO & TELEVISION CORP.

3 GREAT SALESROOMS to Serve You!

Dept. A-9
Adjoining Radio City Downtown N. Y. C.
48 West 48th St. 212 Fulton St.
New York 36, N. Y. • CI 6-4060 • New York 7, N. Y.
In NEWARK, N. J.: 35 William Street.

RADIO ENGINEERING DEGREE IN 27 MONTHS

Radio engineering is a big field. There's room for you in it—if you're good. Get first-class training at Indiana Tech. Intensive specialized course, including strong basis in mathematics and electrical engineering, advanced radio theory and design, television, electronics, Modern Laboratories. Low rate. Also B.S. DEGREE IN 27 MONTHS in Aeronautical, Chemical, Civil, Electrical and Mechanical Engineering. C.I. Government approved. Enter September, December, March, June. You can earn part of your expenses right here in Fort Wayne while you are studying.

INDIANA TECHNICAL COLLEGE

993 E. Washington Blvd., Fort Wayne 2, Indiana
Please send me free information on B.S. Engineering Degree in 27 months as checked.

Radio-Television Aeronautical
 Civil Mechanical Electrical

Name _____
Address _____

SCHEMATICS—CONVERSIONS FOR SURPLUS GEAR

NEW LIST! MANY ADDITIONS!

Send stamped, self addressed envelope for List C. Add 25c for chart explaining AN nomenclature.

R. E. BOX 1220
GOODHEART BEVERLY HILLS, CAL.

WE ARE QUICK AND CASH BUYERS

We're looking for surplus inventories of all types of electronic parts—receiving, transmitting and special-purpose Tubes. Anything in the Radio, TV and electronic field.

SMALL OR LARGE QUANTITIES—SEND US YOUR LIST
Submit samples where possible, amount of each item and prices.

NAT ADELMAN
168 Washington St. New York 6, N. Y.

PAY LESS FOR TUBES

INDIVIDUALLY BOXED • FULLY TESTED • EACH TUBE GUARANTEED FOR SIX MONTHS

Type	Price	Type	Price	Type	Price	Type	Price
1B3GT	\$.69	6A55	\$.50	6K6GT	\$.41	12A27	\$.70
1H5GT	.46	6AT6	.38	6L6C	.80	12BA6	.45
1L4	.57	6AU6	.43	6L6GA	.80	12BE6	.47
1N5GT	.57	6AV6	.38	6S4	.46	12BH7	.63
1R5	.56	6B4C	.96	6SA7GT	.52	12BZ7	.75
1S5	.47	6BA6	.45	6SJ7GT	.47	12SA7GT	.52
1T4	.56	6BC5	.53	6SK7GT	.50	12SK7GT	.50
1T5GT	.71	6BD5GT	.89	6SL7GT	.62	12SL7GT	.61
1X2	.67	6BE6	.47	6SN7GT	.54	12SN7GT	.54
3Q5GT	.65	6BF5	.60	6SQ7GT	.42	12SQ7GT	.44
3S4	.55	6BG6	1.34	6T8	.78	19B6G	1.39
3V4	.56	6BH6	.57	6U8	.85	19C8	.94
5U4G	.43	6BJ6	.48	6V6GT	.46	19T8	.79
5V4C	.73	6BK7	1.10	6W4GT	.45	25B06	.89
5Y3C	.34	6BL7	.83	6W6GT	.57	25L6GT	.48
5Y3GT	.30	6BQ6	.89	6X4	.34	25Z6GT	.42
6AB4	.46	6BQ7	1.10	6X5GT	.33	35A5	.48
6AF4	1.40	6BZ7	1.10	7N7	.59	35B5	.47
6AG5	.54	6C4	.34	12AT6	.52	35C5	.47
6AK5	.95	6C4	.34	12AT7	.68	35L6GT	.47
6AK6	.63	6CB6	.53	12AT7	.68	35W4	.31
6AL5	.40	6CD6	1.85	12AU6	.43	35Z5GT	.30
6AN4	1.30	6FGCT	.45	12AU7	.55	50B5	.47
6AQ5	.46	6HGCT	.49	12AV6	.38	50C5	.47
6AQ6	.42	6JSCT	.40	12AV7	.80	50L5	.47
6ARS	.38	6J6	.62	12AX7	.61	117Z3	.39
						117Z6	.68

Motorola Ballast Tube #17A48545930


Each tube is performance-proven. 25% deposit must accompany all orders. Balance C.O.D. All prices F.O.B., N.Y.C. If remittance is made with order, you can deduct 2%. \$1.00 handling charge for orders under \$10.00. Subject to Prior Sale. Importer inquiries invited.

PHILLIPS TUBE COMPANY

2281 Nostrand Ave.
BROOKLYN 10, N. Y.
CLoverdale 3-8010-1-2

AUDEL'S TV-RADIO SERVICE LIBRARY

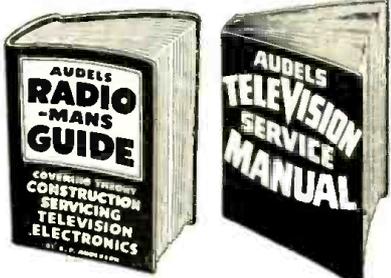HERE IS LATE INFORMATION IN A HANDY FORM FOR RADIO & TELEVISION REPAIRMEN, SERVICEMEN & STUDENTS



2 VOLTS. \$6 COMPLETE \$1.00. PAY ONLY \$1.00. IT PAYS TO KNOW!

AUDEL'S T.V.-RADIO SERVICE LIBRARY presents the important subjects of Modern Radio, Television, Industrial Electronics, F.M. Public Address Systems, Auto, Marine & Aircraft Radio, Phonograph Pick-Ups, etc. Covers Basic Principles—Construction—Installation—Operation—Repairs—Trouble Shooting. Shows How to get Sharp, Clear T.V. Pictures. Install Aerials—How to Test. Explains Color Systems & Methods of Conversion. 1001 Facts—Over 1260 Pages—625 Illustrations—Parts & Diagrams—Valuable for Quick Ready Reference & Home Study. Tells How to Solve T.V. & Radio Troubles—Answers T.V. & Radio Questions.

Get this information for Yourself.
7 DAY TEST—ASK TO SEE IT!

MAIL ORDER

AUDEL, Publishers, 49 W. 23 St., N.Y. 10
Mail AUDEL'S T.V.-RADIO SERVICE LIBRARY 2 Vols. \$6 on 7 days free trial. If O.K. will remit \$1 in 7 days and \$1 monthly until \$6 is paid. Otherwise I will return them.

Name _____
Address _____
Occupation _____
Employed by _____

Radio War Surplus SAVE UP TO 85%




MIDGET TYPE NT-6 WILLARD 6-V STORAGE BATTERY DRY CHARGED

3 amp hour rating. Transparent plastic case. Size 3 3/4" x 1-13/16" x 2 3/4". Weight approx. 1 1/4 lbs. Uses standard electrolyte. Regularly lists at \$12.00 each. Now sensationally priced. **\$2.49 ea.** 4 For \$8.50 postpaid. New, Unused.

TUNER FROM NAVY "BN" EQUIPMENT

Simply modified into 2-meter converter for car or communications receiver. Uses 1-6.16, 1-6SH7, 1-9006, 1-6.15 (Not Furnished). Slug is tuned from 157 to 187 Megacycles. Includes schematic diagram for "BN" equipment. Now—A New LOW Price. ea. **\$3.95**

CRYSTALS

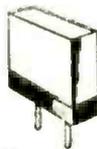

... in FT 241-A Holders—1/2" Pin SPC. Marked 54th OR 72nd Harmonic MC Freq. Listed below by fundamental frequency with fractions omitted.
500 KC Crystals ea. **\$1.95**
1000 KC Crystals ea. **\$3.95**
200 KC Crystals ea. **\$3.95**

Write for our complete list of crystals and prices.

POWER TRANSFORMER

Primary 125 volts tapped at 105 and 115 volts, 50 to 425 cycles. Secondaries: 5.1 v. at 3.0 amps. 325-0-325 v. at 0.175 amp., 5.4 v. at 8 amp., 6.4 v. at 10.3 amp., 2.5 v. at 3.0 amp., 4500 v. at .005 amp., 2.5 v. and 4500 volt windings insulated for 6000 volts. All other windings insulated for 1500 volts. Cost government more than \$12.00—a real bargain at Each **\$3.95**

ALL EQUIPMENT F.O.B. PASADENA LESS OTHERWISE SPECIFIED. PLEASE ENCLOSE FULL AMOUNT WITH ORDER.

C & H SALES CO.

2176 E. Colorado St. • Pasadena 8, Calif.
Box 356-ST East Pasadena Station • Pasadena 8, Calif.

for a change; but I guess it was rather a cheap trick for me to bone up on an off-trail subject and then lord it over you on the strength of it. I probably should have been reading about sync circuits and u.h.f. converters instead of spending so much time with books and magazine articles on cybernetics, but the subject fascinates me and I just can't seem to leave it alone."

"Wait up there!" Mac interrupted. "You certainly have no reason to apologize after having done me two of the most important favors one person can do for another in a single afternoon: first, you showed me where I was mistaken; second, you gave me something new and interesting to think about. As soon as you are finished with that cybernetics book, I want to borrow it.

"As for your reading up on a subject that does not contribute directly to your work, I'm all for it. If all a guy knows is how to do his job, he's pretty poor company—for himself as well as other people. His kind of intellect will be the first to be replaced by a machine someday. But the man whose brains are constantly alert to grasp and analyze and digest new ideas, the fellow who has fun with his intellect, no machine will ever take his place."

TEST BENCH TIP

By PHIL WEISS

HERE'S a practical solution to the problem of grounding the instruments on the test bench, without getting into trouble with "hot chassis" radios or TV sets.


Lay a piece of sheet metal on top of the bench, to which all the instruments are securely grounded. Mount a 117 volt, 6 watt lamp over the bench in a conspicuous position. Connect one side of the lamp to the metal bench top, and the other side to a water pipe, or other good ground. Now everything is grounded to earth through the cold resistance of the lamp, about 200 ohms.

When a hot chassis is placed on the bench and turned on, watch the lamp. If it glows, turn over the a.c. plug. When the lamp is out, it means the chassis and instruments are at ground potential.

Now all measurements are made relative to chassis, without bothering to connect to "B—" in the set.

Caution. It is a good idea not to use the "on-off" switch in a hot chassis set, since this switch is usually in the ground circuit. Instead, install an extra a.c. outlet and a double-pole switch on the bench, for turning sets on and off.

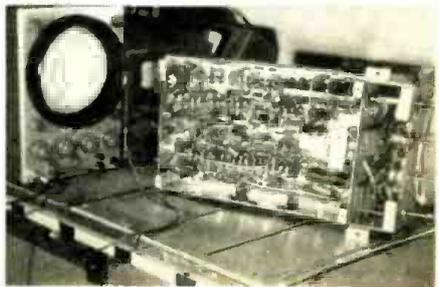
How metal plate is used to obtain common ground for test units and a TV chassis.



NOW ON SALE!

an exciting array of the world's greatest pictures as selected by the Editors of PHOTOGRAPHY magazine.

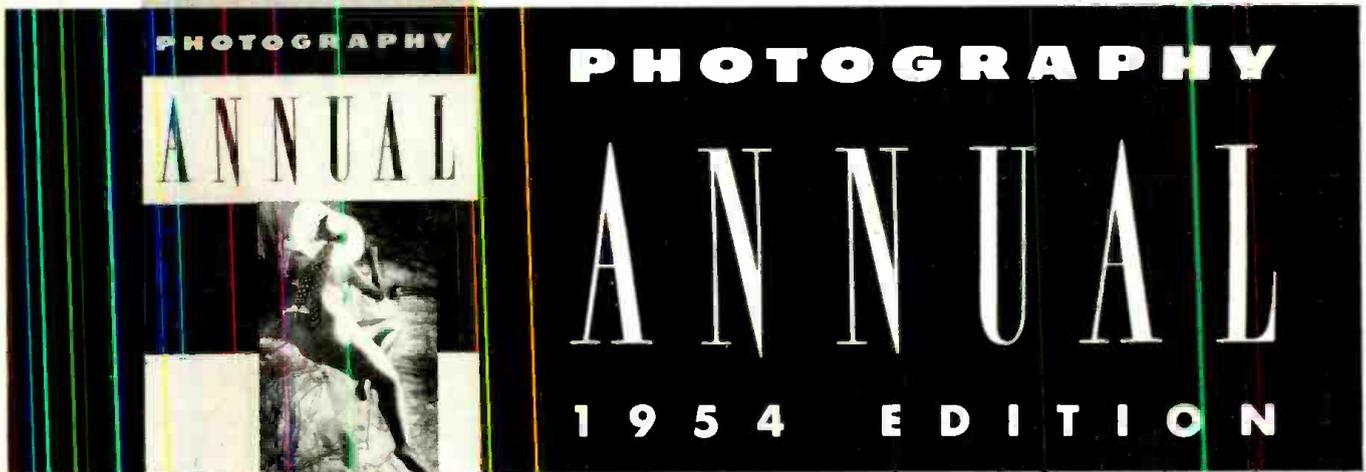with a symposium on Photography Today by the distinguished judges of PHOTOGRAPHY magazine's \$25,000.00 Picture Contest for 1953; Norris Harkness—Wilson Hicks—Irving Penn—Arthur Rothstein—W. Eugene Smith—Frank Zachary.



OVER 250 PICTURES! —

Complete technical data on every picture! Each basic technique thoroughly explained.

24 PAGES OF BRILLIANT COLOR!

PORTFOLIOS BY FAMOUS PHOTOGRAPHERS!

5 BIG SECTIONS LOADED WITH KNOW-HOW, INSPIRATION, NEW IDEAS!

- Camera Techniques...the shutter...the aperture... lenses, what they do... points of view... offbeat effects... technique of color...
- Light at Work... Daylight-down to dusk... after dark... flash, floods and spots... electronic flash... available light... filters... lighting for color...
- In the Darkroom... printing problems... darkroom magic...
- Top Amateur Color... slides... stereos...
- The Approach to Pictures.

PHOTOGRAPHY ANNUAL — THE PERFECT GIFT — THE IDEAL ADDITION TO EVERY PHOTOGRAPHIC LIBRARY.

Reserve your copies at your Newsdealer—Camera Store—Bookshop



ZIFF-DAVIS Publishing Company, Publishers of: PHOTOGRAPHY magazine—PHOTOGRAPHY Annual—MODERN BRIDE—FLYING—RADIO & TELEVISION NEWS—RADIO-ELECTRONIC ENGINEERING Edition of RADIO & TELEVISION NEWS—FICTION GROUP—G.I. JOE Comics.

PHOTOGRAPHY ANNUAL • 1954 EDITION

New Portable Battery-Operated Spring-Motor Tape Recorder



The Magnemite*

For all field recording without AC power! Smaller and lighter than a portable typewriter, the Magnemite* actually makes field recordings that can be played on any studio console equipment. Completely self-powered, the Magnemite* does away with bulky and cumbersome generators, storage batteries and rechargers.

Just check these unusual features:

- Noiseless and vibrationless governor-controlled spring-motor assures constant tape speed.
- 100 operating hours per set of inexpensive flashlight-type dry cell batteries.
- Earphone monitoring while recording, and earphone playback for immediate quality check.
- Operates in any position, and is unaffected by movement or vibration during operation.
- Warning indicator tells when to rewind, and shows when amplifier is on.
- Broadcast models weigh 15 pounds. Slow-speed models weigh only 10 pounds.
- Requires no more desk space than a letter-head, measuring only 11 x 8½ x 5½ inches.

There's a choice of 5 different models for any recording need. High fidelity units, meeting primary and secondary NARTB standards, which record and play back frequencies up to 15,000 cycles, are available for broadcast stations, critical music lovers, and scientific research. For investigation, missionaries, reporters, and general dictation while traveling, there are units which play up to 2 hours per reel of tape.

Write Dept. RN today for complete descriptive literature and direct factory prices.



AMPLIFIER CORP.
of AMERICA

398 Broadway, N. Y. 13, N. Y.

*Trade Mark Reg

Spot Radio News (Continued from page 18)

revealed that 18 per-cent of the viewers found misregistration not observable.

In an additional analysis of picture texture, it was pointed out there are approximately 900 colored phosphor dots along a line in a 16-inch tri-color tube, and about 700 from the top to the bottom of the normal raster area. As noted, this would mean that the diameter of an individual dot is about 70 per-cent of the thickness of a scanning line. In answer to a query of whether viewers could observe any dot pattern, 93 per-cent, it was said, said no.

One of the highlights of the brief is detailed descriptions of the color receivers developed for compatible pickup. Available for reception of the standard or the ultra-high bands, one new chassis features an intercarrier 41.25 i.f. system, noise inversion sync separation, electrostatic convergence and focus, along with dynamic modulation of the picture tube plates, quartz-crystal a.f.c. color synchronization, low level color demodulation using quadrature techniques, picture-tube grid drive with d.c. restoration, and a color killer to disable the color channel during black and white transmissions. Particularly interesting in the new tri-color chassis is the picture i.f. channel, designed for a 45.75-mc. picture carrier, 42.17-mc. color subcarrier, and 41.25 mc. sound carrier. The amplifier consists of six stages, using a single 6BQ7A, four 6CB6's, and one 6CL6. In the second detector is a 1N60 crystal operated at 6 volts peak output level to preserve linearity.

At the ultra-highs, the noise factor of the tuner in the set depends primarily on the noise contributed by the crystal mixer and by the first i.f. amplifier following the mixer circuit. Thus, a low noise driven grounded-grid stage is used for this i.f. amplifier which uses a 6BQ7A; it is fed from the crystal mixer by means of a single-tuned circuit. The output network is a link-coupled bridged-T, *m*-derived bandpass circuit with a rejection trap tuned for accompanying sound or 41.25 mc. To reduce cross modulation, the sound carrier is attenuated as soon as possible in the i.f. amplifier.

The video section of the color receiver is also unusual, consisting of three separate functions: luminance channel, chrominance channel, and a matrix which combines the two channels. The luminance (*Y*) channel serves to amplify the luminance information to a level satisfactory for application to a picture tube, information being applied *via* the matrix. The chrominance channel serves to recover the color difference information contained in the color subcarrier and its accompanying sidebands. By a process of synchronous detection in phase quadrature, two independent signals are recovered from the color subcarrier; these signals are called *I* (in phase) and *Q* (quadra-

ture phase). Both of these channels are band limited. That is, the *Q* channel passes information up to approximately .5 mc., and the *I* channel passes information up to about 1.8 mc. While band limiting of these channels prevents crosstalk, it necessitates equalization of signal delay time since the channels have different bandwidth characteristics. Similar equalization is required in the luminance channel.

The color picture tube requires simultaneous excitation with red, green, and blue signals; the matrix provides these simultaneous signals by combining predetermined proportions of the *Y*, *I*, and *Q* information. To synthesize the color drive signals, a fixed resistive mixing type of feedback amplifier is employed. Using one triode section of a 12BH7, in conjunction with three fixed matrix resistors for red, green, and blue adder stages, linear addition of *Y*, with the proper amplitude and polarity of *I* and *Q* is accomplished. The added luminance and chrominance signals are then amplified by output amplifier stages (second half of a twin triode 12BH7) to a level satisfactory for application to the grids of the picture tube. Unequal picture-tube drive signals are required due to the unequal phosphor deficiencies of the tri-color tube. Red requires about 100 volts, while blue and green use about 50 to 70 volts of drive. Over-all gain controls for the green, red, and blue channels are provided.

Color synchronization, also an extremely important factor in picture control, is thoroughly analyzed in the petition. To recover the color information contained in an NTSC type signal, it is necessary to generate a local subcarrier of proper frequency and phase. To accomplish this, phase reference information is transmitted as a component of the composite color video signal. This color sync information is transmitted in the form of a *burst* of approximately 8 cycles of the color subcarrier frequency and appears immediately following each horizontal sync pulse in the composite signal.

This *burst*, the discussion points out, is separated from the composite video signal and is used in establishing two continuous wave signals of color subcarrier frequency having a 90° phase displacement from each other. These two signals are generated by a quartz crystal oscillator whose exact frequency is controlled by a reactance tube. This tube derives its control information from an error signal proportional to the difference in phase between the transmitted *burst* and the local crystal oscillator output.

The color sync channel includes a keyed *burst* amplifier stage, phase detector-3.579-mc. driver and color phasing amplifier, crystal oscillator, reactance tube, and quadrature 3.579-mc. amplifier.

In a color tube, convergence is a key item. Center convergence of three beams is accomplished in this chassis by adjusting the d.c. potential of a convergence electrode for best super-

Presenting . . . at most moderate cost . . .

ESPEY

25th Anniversary "Trophy" Models AM-FM CHASSIS • TUNERS • AMPLIFIERS



In commemoration of twenty-five years' experience in the manufacture and development of high-fidelity audio equipment, Espey is proud to present its distinguished "Trophy" models. Renowned for beauty of styling and excellence of performance, the new Espey models are so reasonably priced that for the first time magnificent listening pleasure is within the means of all lovers of fine audio reproduction.

Descriptive literature on the new Espey AM-FM chassis, tuners and amplifiers is now available . . . your inquiry is invited.

SYLVAN A. WOLIN & ASSOCIATES SALES CORP., 409 GRAND AVENUE, ENGLEWOOD, N. J.

Communications Receivers

Special
\$ **69** 50

KIT PRICE EACH

COMPLETE KIT—This kit is complete with every part necessary to assemble into a finished receiver, including tubes and cabinet. Chassis is punched and macked. Mount the parts, wire it, align it and you have a fine receiver of commercial appearance, that can't be beat for 3 or 4 times the price. Parts layout, schematic diagram and alignment instructions are supplied.

FEATURES:

- 2 Watt F.P. Audio
- Amplified AVC
- Voltage Regulated Oscillator Supply
- Noise Limiter
- Beat Cancellor
- Air Flared R.F. Trimmers
- 2 Stage Permeability Tuned 455 KC I.F. Plus Crystal Filter
- Phone Jack—Built-in Stand-by Relay
- Operation on 135 to 125 volts AC or DC Power Source
- Frequency Range 200 KC to 400 KC and 490 KC to 19 MC in Six Bands
- 40:1 Geared Ratio Dial Drive
- 11 Tubes Plus Selenium Rectifier
- 6SQ7 RF AMP.
- 6S87Y Mixer
- 2-6SQ7 I.F.
- 6H6 2nd Det & N.L.
- 6SF7 AVC AMP.
- 6SL7 BFO & 1st Audio
- 6SL7 Phase Inverter
- P.P. 25L6GT Audio
- VR-75 Voltage Regulator
- Full Vision Calibrated Dial Cabinet 19 1/2" long x 10 1/2" high x 12 1/2" deep
- Finished in fine grain black wrinkle
- Front panel silk screened to identify each control
- Smps. weight 45 lbs.
- Shipped Express Only.

FRONT PANEL CONTROLS

- Tuning
- R.F. Gain
- Audio Gain
- BFO-AVC Switch
- BFO Pitch
- Power On-OH
- Stand-by
- Noise Limiter On-OH and Control
- Antenna Trimmer
- Crystal Filter On-OH
- Crystal Phasing
- Selectivity
- Band Change Switch
- Calibrated Dial Face



Contains All Components

WEBSTER CHICAGO CHANGER Model 121

Automatically plays all records, all sizes, 12", 10", 7", all speeds—78, 45, and 33 1/3 RPM. Simple to operate. Automatically shuts off and tone arm returns to rest after last record has been played. Minimum mounting space required, 14 1/2" W., 13 1/2" D., 8 1/2" H., with 6 1/4" above mounting board. Wt. 14 lbs. **\$29.95**

Brand new 78 r.p.m. PHONO MOTOR without reduction, 1,000 r.p.m. **49c**

All American Tube Kits

12AT6, 12BA6, 12BE6, 35W4, 50B5, 5 Tubes for **\$2.59**
50L6GT, 35Z5GT, 12SQ7GT, 12SK7G, 12SA7G, 5 Tubes for **\$3.22**

ORDER TODAY!

TERMS: 25% Deposit with order. Balance C.O.D. Include postage with parcel post orders. All prices F.O.B. Chicago and subject to change without notice. All merchandise subject to prior sale.

DUMONT TV TUNERS


Favorite continuous tuner covering TV Channels 2 through 13 and the RR to 108 m.c. FM band. 3 Tube (6AH1-6AK5-6J0) Tuner for Dumont models R-119A & R-112A & R-113. Model R-119A complete with calibrated glass dial. Model R-112A & R-113 complete except for dial. Brand new. Use them for TV tuners, H.F. converters, etc. continuous tuning range from 52 to 216 MC. Tuner for R-119A **\$10.95**
Tuner for R-112A and/or R-113 **9.95**

AMPHENOL Double Stacked TV ANTENNAS

Amphenol 114-322 double stacked T.V. antenna with 100 ft. of twin lead and 5 ft. mast. Regular **\$18.95** \$22.75 value for only **\$12.95**

FREE GIFT If you visit our store and bring this ad with you

Philmore 2-tube AC-DC Radio Kit

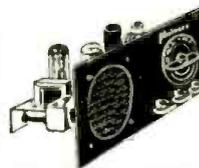

Includes simple instructions and diagrams, complete less tubes, headset, wire and solder. 115V AC or DC. **\$7.35**

Set of tubes: 35Z5 and 12SJ7. . . . **\$1.51**

3-TUBE AC-DC RADIO KIT

2 band including short wave. Easy to assemble; with good 4" PM Speaker. 550-1700 KC on broadcast band; 3-18MC on short wave. 115V AC or DC. Complete with speaker. **\$11.76**
Set of tubes: 35Z5, 50L6, 12SK7. . . . **\$2.39**

We have all PHILMORE kits in stock . . .

BOULEVARD ELECTRONICS, INC.

DE 2-4458

808 10 W JACKSON BOULEVARD • CHICAGO 7, ILLINOIS

RADIO AND TELEVISION SUPPLIES

STAN-BURN E-D-A-R-K-E

CATHODE RAY TUBE SPECIALS One Year Guarantee

G. E.		STAN-BURN	
* 5TP4	\$44.95	* 10BP4A	\$11.00
* 71P4	17.10	* 12LP4A	14.20
* 10BP4A	19.25	* 14CP4	17.00
* 10FP4A	24.00	* 15DP4	19.50
* 12KP4A	27.10	* 16AP4	21.60
* 12LP4A	21.70	* 16FP4	19.60
* 12UP4B	28.25	* 16GP4	21.60
* 14CP4	24.50	* 16EP4A	22.60
* 16AP4A	30.95	* 19AP4	23.90
* 16DP4A	28.20	* 16DP HP4A	20.60
* 16CP4	31.25	* 16KP4	18.50
* 16KP4/16RP4	28.20	* 16LP4	20.60
* 17BP4A	23.90	* 16LP4A	21.60
* 17CP4	23.90	* 17BP4	18.50
* 19AP4A	39.45	* 17CP4	21.60
* 20CP4	32.50	* 19AP4	23.90
* 20LP4	37.50	* 19AP4A	25.90
* 21EP4A	37.35	* 20CP4	29.50
* 24AP4A	78.50	* 21EP4	32.50

ANTENNAE SPECIALS

* RED DOUBLE TV Antenna	1-5	6 or more
* 10 ELEMENT CONICAL DOWELED INSERTS	\$2.19	\$1.98
* Folded Hi Straight Low Quick Rig	2.98	2.79
* WINDOW CONICALS	4.25	3.25
* WINDOW CONICALS	4.95	3.75
* 5 FOOT SWEGED MASTS	.79	.69
* 10 FOOT PLAIN NEPCO MASTS	1.39	1.29
* 42 Mil. TV WIRE		
* 55 Mil. 300 OHM		\$ 9.95 M Ft.
* 72 OHM COAXIAL		11.95 M Ft.
		35.00 M Ft.
* 12 Heavy Six Speaker		Special \$3.98

WIRE RECORDERS IN STOCK

* PENTRON Model 9T3C - 2 Reel Tape Recorder		Write for Price
* RADIO CRAFTSMAN Model C400 - Hi-Fi Amplifier		Net 42.90
* Model C10 - AM-FM Tuner		Net 131.50
* Model C500 - Williamson Amplifier		Net 99.50
* We also carry MASCO-BOGEN-PILOT, etc. Amplifiers, Pre-Amps, FM Tuners and WEBSTER Tape Recorders.		
* 6x9 PM Speaker	\$ 3.98	630 Vert. output dotted 1.29
* 7" PM Speaker	3.98	630 Vert. Blocking .89
* 77J1 G.E. Flyback	1.98	OSC. XForm .89
* 70 Yoke	1.98	Cascade Tuners 19.95
* 630 Vert. output upright	1.98	Standard Tuners 17.95
		Dumont 21.25 mc. 14.95

AUTHORIZED DISTRIBUTORS

for General Electric, Kenrad, Tunja-Sol, National Union, Oc Wald, Regal, Automatic and General Motors.

Automatic Custom-Built Radios for Plymouth, Ford, Chevrolet and many others, always in stock.

We carry a Complete line of HI-FIDELITY and sound equipment. Send us your requests.

We also carry a complete line of popular makes of Radio Tubes at 50% discount. Also many other special purpose and transmitting types, and all electronic parts and equipment at lowest prices. Send us a list of your requirements for prompt quotations.

Terms: 20% with order. Balance C.O.D. All prices F.O.B., NEW YORK Warehouse. Minimum order \$5.00. Write for our latest price list and Hi-Fi catalog to Dept. RN-9.

STAN-BURN RADIO and ELECTRONICS CO.
(C.B.S. THEATRE BLDG.)
1697 BROADWAY • NEW YORK 19, N.Y.

positioning. That error which still exists is due to the mechanical inaccuracies of gun alignment and is corrected by the use of individual-beam convergence magnets. To effect overall beam coincidence, dynamic convergence is employed. Reviewing this technique, the brief declares that since the phosphor plate and shadow mask are flat surfaces, the distance the beams must travel from the deflection plane to the central area of the shadow mask is less than the distance they must travel when the beams are deflected away from the central area. If the potential on the convergence electrode, necessary to produce center convergence, remained unchanged, the three beams would then cross over at some point before reaching the shadow mask. This would result in a mis-registered picture. To correct this condition, it is necessary to modulate the d.c. potential on the convergence electrode in such a manner as to produce a larger convergence electrode voltage as the deflection angle increases. This condition also exists with respect to focus.

A dynamic convergence voltage and focus modulation voltage, each with the proper waveform, amplitude and synchronism with deflection, are generated by the use of a pair of tapped transformers and a single triode amplifier, one half of a 6BL7. These dynamic voltages are produced by linear addition of horizontal and vertical waveforms derived from the cathodes of respective deflection output stages. The composite alternating output voltage is coupled to the picture-tube convergence electrode and focus electrode through their respective output transformer taps.

While the brief submitted by RCA is extremely complete and thorough, the NTSC report will offer an even more exhaustive review covering engineering and statistical data compiled by many panels with scores of sub-committees whose membership totals

hundreds. To illustrate, in one field report, results obtained during over 3000 observations were recorded, and such studies covered co-channel interference, lower and upper adjacent channel troubles (if any), random noise, sine-wave interference, and multipath problems. In addition, a variety of receivers were under study during these tests; in some examinations, as many as thirty receivers were scrutinized for picture quality, flicker, general compatibility, brightness, contrast, picture texture, adequacy of sync, and even sound reproduction. Another report covers broadcasting over direct, microwave, and coax facilities with scores of observations by experts from receiver and transmitter manufacturers, as well as broadcast stations.

As this is being written, two questions are spinning about Washington: Will anyone oppose either the RCA or NTSC appeals? Will the patent situation be taken in stride or subjected to a microscopic inquiry not only by the Commission, but by our legislators? Some feel that Dr. Du Mont might object to the standards, for he has declared on several occasions that he didn't feel that the system was currently strong enough. Others say that he'll go along, notwithstanding his earlier remarks. It is also believed that CBS, whose wheel system had been approved, will now follow the compatible march. While the Commission, as an official body, has been silent on its views, it has been reported that some of the members have been impressed with advancements made with the new compatible color TV system. During the recent RTMA conclave in Chicago, one Commissioner was quoted as declaring that compatible color will be approved before Christmas. That will be quite a headliner for the Yuletide season.

A BIRTHDAY, the first anniversary of the lifting of the freeze, highlighted

Regency

**LARGEST SELLING
BOOSTER**

at any price!

the end of the fiscal year in Washington. During those twelve months, station permits were routed to some 300 cities throughout the land. Of the post-freeze approvals, 256 were for ultra-high stations and 142 for standard bands, with educational groups receiving seventeen of the allotments, or thirteen for u.h.f. and four for v.h.f.

Texas, California, Pennsylvania, and New York led the parade in grants, with Texas receiving 41 approvals (25 v.h.f. and 16 u.h.f.), New York 36 (15 v.h.f. and 21 u.h.f.), Pennsylvania 34 (9 v.h.f. and 25 u.h.f.), California 33 (24 v.h.f. and 9 u.h.f.).

All states except Vermont now have station authorizations, and some in New England, such as New Hampshire and Maine have but one and two, respectively. However, Massachusetts has received OK's for twelve, with two for present-band operation and ten for the upstairs use.

The hearing calendar is still a crowded one, with over 600 applications awaiting approval at this moment, and more and more petitions coming in daily.

ONE OF INDUSTRY'S stalwart pioneers, a bold crusader whose vigorous drives for better broadcasting won the acclaim of the nation, is dead. Lewis Allen Weiss, who served as chairman of the board of the *Mutual Broadcasting System*, and headman of the *Don Lee* network on the Pacific coast, committed suicide a short while ago, after learning that he was suffering from an incurable ailment. Everyone will miss the sparking wisdom of this inspiring leader. . . . L.W.

WCOS-TV ON NETWORK

SOUTH Carolina's first television station, WCOS-TV in Columbia has been connected into the Bell System's nationwide television network.

It is connected to a section of the intercity facilities which carries net programs from Charlotte, N. C. to Jacksonville, Florida.

-30-



FOLLOW ARROW FOR BIGGEST STOCK AT LOWEST PRICES

- RADAR—TRANSMITTERS
- RECEIVERS — TUBES — PARTS

234-258 MC RECEIVER

11-tube UHF tunable receiver with schematic. Like new.

\$17.95

Rack\$3.50
Control Box.. 1.50

UHF Transmitter

450-710 MC. Tunable Transmitter. 10 W. output. Two 300-type tubes as push-pull oscillators. Wide band Alder amplifier. Less tubes, with schematic. Excellent condition. . . . \$8.95

RADAR TEST EQUIPMENT

TS-3, TS-12, TS-15, TS-33, TS-34, TS-35, TS-36, TS-45APM3.

R.F. Modulator

Complete Tunable 205 MC. Test Set With 110 V. 60 cps. power supply. 3-stage audio amplifier. Terrific chassis for experimentation. With schematic. Like new. . . . \$9.95

FOLLOW ARROW TO GET HIGHEST PRICES FOR YOUR NEW AND USED RADIO GEAR! What have you to sell? WRITE TODAY!

INTERPHONE AMPLIFIER BC-709-B

A 2-position single stage audio amplifier. Uses 1 tube and operates from self-contained batteries. With Instruction Manual and Schematic. . . . \$3.95
NEW (less batteries).....

Monthly Specials!

EC-604 30 W. FM TRANSMITTER. For 20-27 MC. band. Ideal for 10-11 meters. Complete with tubes, temperature controlled crystal oven and control manual with all instructions for BC-604 and BC-604. Less dynamotor and crystals. Excl. cond. . . . \$12.95

ARC-4 TRANSCEIVER

140-144 MC. Complete with control box, tubes. 12/24 VDC dynamotor with schematic. This is a special reduction for this month only. . . . \$32.50
Like new . . . \$36.00
MT 101 ARC-4. Rack. . . . \$6.00

GA-C 2 V. VIBRATOR. New. Each.	39c
MT 101	\$3.50
MT 77 10 BC-412. New.95
MT 68-E for RFA-1B. New.	P.U.R.
MT 290A ARC-1 for ARC-1. New.	P.U.R.

COMMAND EQUIPMENT (SCR-274N)			
	Used	New	
BC-442 ANTENNA RELAY. Less cond.	\$1.95	3.95	
BC-451 TRANSMITTER CONTROL BOX with cond.		5	3.50
BC-450 3-RECEIVER REMOTE CONTROL BOX		2.95	
WC-215 MECHANICAL DRIVE SHAFT. Perf. form		2.95	
BC-496 2-POSITION RECEIVER CONTROL BOX		2.95	
BC-455 6-9 MC RECEIVER. With tubes	9.95	14.95	
MC-211 90° ANGLE COUPLING UNIT.			New \$0.95
FT-234 MOUNTING RACK for single transmitter		\$2.95	3.50
FT-226 MOUNTING RACK for 2 Communicators			3.95
FT-221 MOUNTING PLATE for FT-220; FT-220 MOUNTING RACK for 3 receivers			1.50
FT-225 MOUNTING PLATE for BC-456 BC-456 MODULATOR. For SCR-274.		2.25	3.95
Complete set of 4 tubes for transmitter		5.75	1.25

G.A.P. SPECIAL BC-625 VHF TRANSMITTER

Freq. range 100-150 MC. With modulation section. Less tubes & crystals, with conversion d.p.p. U.S.C. good condition. \$9.95

UHF 420 MC TRANSCEIVER

Complete transmitter-receiver unit with 5 stages of 6B6 AF amplifier. This unit is the famous AFS-13 Radar Set. Less tubes and dynamotor. With Schematic. Excl. cond. . . . \$12.95

UHF MOBILE DIRECTIONAL ANTENNA

Complete with directors, reflectors, and mounting plates. Made for use with accompanying AFS-13 transceiver. New 95c

Miscellaneous Specials!

H-16U HEADSET. 8,000 ohms.	\$3.95	PE-125 POWER SUPPLY: Operates on 12 or 24 v. battery. NEW	\$17.95
HS-18 HEADSET. New	2.45	CD-307 EXTENSION CORD. For HS-23-33. NEW95
HS-23 HEADSET. High imp. New.	4.95	RS-38 MIKE. Excellent cond.	3.95
HS-30 HEADSET. Featherweight type. Low Imp. NEW.	\$2.49	SCR-625 MINE DETECTOR. New.	59.50
HS-33 HEADSET. Low imp. New.	6.95	BC-605 INTERPHONE AMPLIFIER. With dual mike input circuit. NEW	5.95
HS-3H HEADSET. USED. excel. cond.	1.49	TELEPHONE REPEATER AMPLIFIERS:	
NEW	3.50	EE-99. New, with tubes	17.95
T-32 DESK STAND MIKE. New	5.95	EL-89. New.	12.95
T-48 DESK STAND MIKE. New.	4.95	FL-8 RANGE FILTER.	1.95
LIP MIKE. Navy type. New.98	PL-68 MIKE PLUG. New.79
MP-22 MOBILE ANTENNA. MOUNTING RACK. (C.R.) with hardware. Per Pair \$4.95.	Ea. 2.95	PL-55 HEADSET PLUG. New.59
TU-17 TUNING UNIT. (2-3 MC.) For BC-223. Amt. Used	2.95	IN-48 L.F. TUNING METER. Used.	3.95
TU-25 TUNING UNIT. (3.5-5.2 MC.) For BC-223. Amt. Used	2.95	FL-5 RANGE FILTER.	1.25
I-70 "S" TUNING METER. NEW.	2.50	TS-10 SOUND POWERED HAND SET—Used. excel. cond. Per Pair. 12 V input. 500 VDC @ 210 mls. output. New.	14.50
WOBLATOR See p. 43. Inc. '51 RADIO NEWS	5.95	PE-53 DYNAMOTOR 12 V input. 500 VDC @ 210 mls. output. New.	24.50
BC-1023 75 MC. MARKER BEACON RECEIVER. Complete with tubes, mts. rack. NEW.	10.95	FIELD TELEPHONE. PE-8. Complete BRAND NEW.	27.50
		DC OVERLOAD RELAY. West. 0.2-1.0 amps.	6.50

ID6 APN-4

Complete with tubes and crystal. Excl. cond. \$47.50
Only

250 TL TUBES—Limited Quantity!
Only \$9.95 each
Save \$2.00! Order 2 for only \$17.00

INDUSTRIAL CORPORATIONS

We carry one of the most complete stocks in U. S. of Military Electronic Equipment, Test Equipment, and Aircraft Electronics. Call or write for free catalogue.

\$5.00 MINIMUM ORDER ACCEPTED. All items subject to prior sale. All shipments F.O.B. warehouse. Calif. residents add tax with remittance. 20% deposit required. Please specify shipping instructions with order. EQUIPMENT WANTED! Highest prices paid for all types of Electronic Gear!

ARROW SALES, INC.

Cable Address: ARROWSALES POPlar 5-1819

Mailing Address:
P. O. Box 3878-R, N. Hollywood, Calif.

Office-Warehouse:
7460 Yermo Ave., N. Hollywood, Calif.

Mailing Address:
P. O. Box 3878-R, N. Hollywood, Calif.

Office-Warehouse:
7460 Yermo Ave., N. Hollywood, Calif.

WORLD'S LARGEST MANUFACTURER
OF CUSTOM BUILT TELEVISION

MATTISON

SILVER ROCKET 630 CHASSIS
• with TUNEABLE •

BUILT-IN BOOSTER
for Better DX Reception

Featuring NEW CASCADE TUNER
made for UHF interchangeable
tuning strips and COSINE YOKE

Tube
Complement:
28 tubes
3 rectifiers
1 CRT

32



All Channel Booster

• Broad band single knob control pre-amplifier built in to eliminate long leads which may cause regeneration and attenuation of signal.

• ONLY THE MATTISON 630 CHASSIS HAS AN ALL CHANNEL TUNEABLE BUILT-IN BOOSTER THAT INCREASES SIGNAL STRENGTH UP TO 10 TIMES. THE SILVER ROCKET WILL OUTPERFORM ANY CHASSIS MADE AND IS PRICED RIGHT TO SELL FAST WITH AN EXTRAORDINARY MARGIN OF PROFIT FOR YOU. ALSO AVAILABLE WITHOUT BOOSTER.

AVAILABLE FOR IMMEDIATE DELIVERY!
SILVER ROCKET FOR 27" OPERATION

ANNOUNCING
the New
AMBASSADOR
for 1954



The only open
face console
made in every
expensive
decorator
finish . . . on
guaranteed
genuine ma-
hogony, walnut,
oak and other
rare woods!

The AMBASSADOR 21" and 27"
Best Looking . . . Best Value, Too!

Full size console for eye level television. Available in every expensive decorator finish. Featuring removable safety glass. ALL CABINETS MADE IN MATTISON'S OWN CABINET FACTORY.

DEALERS! SERVICE DEALERS! Here is your opportunity to become the "important" TV Dealer in your area for THE FINEST CUSTOM-BUILT LINE OF TV RECEIVERS. FREE!! Write for Mattison's merchandising portfolio explaining the "UNASSEMBLED PLAN" and "\$1,000,000 FLOOR PLAN."



Manufactured with integrity

When you buy from Mattison you need only one source of supply! You can buy a Mattison Chassis, a Mattison Cabinet or a complete Mattison TV Set!

Mattison Television & Radio Corp.

10 West 181st St., Dept. RN, N.Y. 53, N.Y.

"CONVERTERLESS"

75-METER MOBILE RECEPTION

By HOWARD R. SHANNON, VE7AGE

An easy modification of your car broadcast set, that does not harm broadcast reception, gives you 75-meter coverage.

IF YOUR CAR is equipped with a good broadcast receiver, you will find that it can be made to work on 75 meters without loss of efficiency on the broadcast band. This will please the XYL and save much-needed space for the transmitter, v.f.o., or what-have-you in the front end of your car.

First, let's take a look at one of the permeability-tuned coils used in nearly all late-model car receivers and consider the effect of adding a second coil in parallel. The tuning range will now be higher and can be extended to 75 meters.

With the two coils in parallel, any change of inductance in one will change the inductance of the whole tuned circuit; in other words, the iron slug that moves in and out of the coil to tune the broadcast band may now be moved in the same way to tune the higher frequencies. The new range should be from 3825 to 4000 kc. Since the added coil has less inductance than the other, we can get the band-spread required for easy tuning.

In making the change, first connect a new coil across the antenna coil, calculating the number of turns so that the two coils together, with the slug out, tune to the high end of the 75-meter band (1500 kc. on the dial). Then with the dial turned and the slug in, the coils will tune to the low end of 75 meters. For the author's


receiver, the required coil turned out to be 27 turns of No. 22 enamel close-wound on a 1-inch diameter form.

A coil is similarly added to the mixer and a third to the oscillator. The new coil connects across the "tuned" part of the oscillator coil (not including the feedback winding). The oscillator will continue to operate with ample output for good mixing, regardless of the type of oscillator circuit used in the car set. The normal oscillator coil has, by comparison with the other radio frequency coils, few turns and high fixed capacity; similarly, the new "double" oscillator coil will have effectively fewer turns yet a high capacity. By keeping the ratio correct, tracking problems can be avoided.

The added mixer coil had 26 turns of No. 22, closewound, and the added oscillator coil had 9 turns, closewound, each on a 1-inch diameter plastic form. Small peaking padders across the new coils are switched in and out along with the coils when changing bands.

Both C_1 and C_2 in the diagram are 7-150 μfd . padders. The value of C_2 should be determined experimentally, to cause the oscillator to tune from 3825 kc. plus the intermediate frequency to 4000 kc. plus the intermediate frequency. For a 456-kc. i.f., as used in the author's set, the cor-

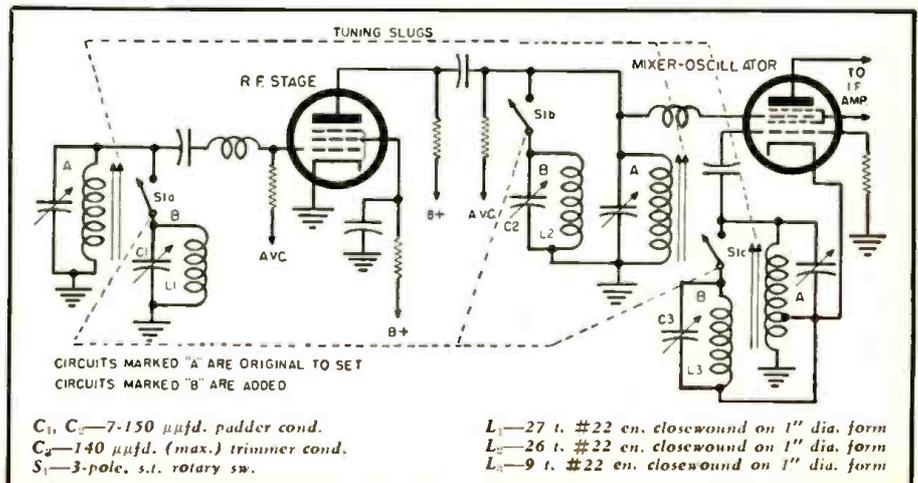Broadcast receiver circuit changes for "converterless" 75-meter reception. Coils and condensers are switched into the circuit across the slug-tuned r.f. mixer, and oscillator coils to change their tuning characteristics to cover the amateur band.



rect value will be found somewhere in the range of 85-140 micro-micro farads. This value will cause the oscillator to tune from approximately 4281 to 4456 kc. For lower i.f.'s, it should only be necessary to add an extra turn or two to the new oscillator coil, using the same condenser.

We need, then, for the new two-band receiver only three coils, three padders, and a simple bandswitch (since in changing bands only one side of each coil must be connected or disconnected). Custom sets pretty well take care of engine noise over the broadcast band, and their design in this regard shows their merit on 75 meters too. You will find no undesired signals, just the ones that should be there.

The author's set is custom-built by *General Motors* and the coils shown are the ones used in it. The band-switch is on the back of the set but is not hard to reach even while driving. I have tried other makes of sets with equal success, and feel that the system should work on 40 meters as well as on 75—possibly on 20 or 10.

SOME PORTABLE RADIO SERVICE HINTS

By JACK DARR

THERE is no substitute for experience in rapid portable radio servicing. The hints below may serve to bolster the service technician's own experience in servicing such sets and make such work more rapid and, hence, more profitable.

SILVERTONE 101.802-1

This portable came into the shop with almost no volume. The trouble turned out to be an open plate resistor in the 1L5 circuit, a one-megohm unit, which has been found bad in several of these sets. Another source of trouble in these sets is the 3.3-megohm screen resistor of the same tube. Replace this unit if its value has increased by about 20%.

WESTINGHOUSE H-105

This set came into the shop with the volume extremely weak. It would just barely get the local station, and others not at all. All tubes were good, all supply voltages up to normal. Eventually, the a.v.c. voltage was checked. Over most of the bus the voltage was normal, but about 10 volts negative appeared on the input grid of the 1R5 mixer-oscillator. This voltage was observed to rise and fall as the set was tuned from one end of the dial to the other. The oscillator coil in this set uses a few turns open-ended as a "gimmick" coupling for the oscillator grid. This gimmick was shorted to the rest of the coil, which returned through a 10-megohm resistor to the a.v.c. bus. This caused the oscillator grid voltage to feed through into the a.v.c., reducing the sensitivity. The gimmick was cut off, and a small mica condenser was connected from the oscillator grid to the hot end of the coil. After realignment, good performance was restored.

PHILCO 46-350 AND 47-350

If these sets have low sensitivity and the tone is poor, look for a bad screen resistor on the 1U5 tube. These are 3.3-megohm matchstick units. Also, check the 1-megohm plate load resistor on the same tube.

September, 1953

1 = 4 with RCP Model 324

Because the Radio City Products Model 324 "DO-ALL" Tube and Battery Tester packs into one instrument the performance of four...

Facilities to Test

1. **All TV and Radio Tubes**
Sockets for all standard 4, 5, 6, 7, octal, loctal, miniature and subminiature are provided. Tests transmitting, hearing aid, ballast, pilot light, gaseous rectifiers and tuning indicator types. All readings are indicated on a large easily read meter.
2. **Cathode Ray Tube**
Checks all magnetic deflection types right in the set or carton. Will locate and isolate all shorts or leaks.
3. **Batteries**
Tests popular portable battery types under load. Indicates true condition of battery under check.
4. **All This and a Reactivator Too—**
Gives extra life to otherwise dim or bad picture tubes.



Two Styles to Meet Your Service Needs—

Model 324C—Counter model with open style metal case. Size: 13 3/4" x 12 1/4" x 4". Weight: 10 lbs. Price: \$69.95.

Model 324P—Combination portable—counter model. Smart looking, hand-rubbed carrying case with slip-hinge cover—includes battery test leads. Size: 16 1/4" x 14 1/4" x 5". Weight: 12 lbs. Price: \$79.50.

Remember You Can Do More With A "DO-ALL" See it at your Parts Distributor today Write Dept. RN-9 for RCP '53 catalogue

RADIO CITY PRODUCTS CO., Inc.
151 WEST 25th STREET • NEW YORK 1, N. Y.

USED RECORDING TAPE (PLASTIC BASE)

\$1.99 for 7"—1200 foot
1.09 for 5"—600 foot
.59 for 4"—300 foot
.29 for 3"—150 foot

Plastic reels included with all above sizes.

Money cheerfully refunded if you do not find this tape cleanly erased and as good as new. (If you are skeptical and from Missouri send us 12¢ in stamps and we'll roll you a sample.)

New empty plastic reels in boxes for easy labelling 3"-10c; 4"-22c; 5"-24c; 7"-30c ea. EMPTY BOXES: 3"-3c; 4"-5c; 5"-5c; 7"-10c ea.

We carry new recorders, recording blanks, tape, tape recorders, etc. at large savings. PLEASE INCLUDE SUFFICIENT POSTAGE.

COMMISSIONED ELECTRONICS CO.
2503 Champlain St. N. W., Washington 9, D. C.

EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.

ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

INSTRUCTOGRAPH COMPANY
4711 SHERIDAN ROAD, CHICAGO 40, ILLINOIS

MANUFACTURERS' LITERATURE

Readers are asked to write directly to the manufacturer for the literature. By mentioning RADIO & TELEVISION NEWS, the issue and page, and enclosing the proper amount, when indicated, delay will be prevented.

CD PUBLICATIONS

Cornell-Dubilier Electric Corporation, South Plainfield, New Jersey has issued a catalogue on its TV rotor line, including the TR-2, the CDR rotor models TR-11 and TR-12, as well as accessories to the rotors, including the automatic clock.

Also available is a new catalogue on the company's full line of u.h.f. and v.h.f. antennas for both indoor and outdoor installation.

A third publication is a supplement to the "Vibrator Replacement Guide" which gives complete and up-to-date listings.

A series of promotion aids for the television rotor, including illuminated and animated displays, envelope enclosures, and window streamers are also available, according to the company.

SWITCH BULLETIN

A comprehensive selection of inexpensive line and slide switches for radios, TV sets, appliances, small motors, toys, instruments, and similar equipment is described in a new 16-page bulletin released by the Electronic Components Division of the *Stackpole Carbon Company*, St. Marys, Pa.

Bulletin RC-9B includes complete specifications, dimensions, and helpful application data on seven new line switches recently developed for use with the company's variable composition resistors. In addition, similar data is given for a wide variety of slide switches including several new heavy-duty types for fractional horsepower motors.

Copies of this bulletin are available on letterhead request.

MAILING PIECE

G & H Wood Products, 75 North 11th Street, Brooklyn 11, New York has issued a new mailing piece on its "Cabinart" line of interior styled, high-fidelity cabinets and kits.

Equipment cabinets, speaker enclosures, and combinations are listed in relation to wood and style so that they can be properly matched at the right price. Custom builders, dealers, and audio enthusiasts will find the catalogue of interest.

Copies may be obtained from local parts distributors or from the company direct.

ELECTRONIC TUBES

Amperex Electronic Corporation, 230 Duffy Avenue, Hicksville, Long Island, New York has issued a con-

densed catalogue covering its line of electronic tubes for communication, industrial, rectifier, radiation detection, electro-medical, amateur, and special applications.

This 24-page catalogue is intended as a quick reference guide to the correct tube for any given application. More detailed data sheets on the listed tubes are available on request.

Please write the company direct for copies of this publication.

REPLACEMENT PARTS

An up-to-date, revised replacement catalogue has been issued by *Sprague Products Company*, 51 Marshall Street, North Adams, Massachusetts.

Catalogue C-609, a 20-page booklet, contains detailed listings of all standard stock condensers and the company's "Bulplate" printed circuits for radio and television service, lab applications, amateur radio, and experimental purposes.

An unusually complete line of condensers is included with more than 375 ratings in voltages from 300 to 20,000 volts d.e.

Copies of this publication are available either from the company's distributors or from the company direct.

STANDARD TUNER DATA

Parts prices and descriptions and installation and performance data on the company's new television tuner and u.h.f. coil strips are included in the new 8-page brochure just released by *Standard Coil Products Co., Inc.* of Chicago.

Available from the company's wholesale distributors, the brochure gives a detailed circuit diagram of the tuner, trimmer location, and mounting dimensions. How to adapt the company's "Super" cascade tuner and the new pentode tuner to split-sound i.f. systems is also explained.

TUBE BOOKLET

An educational picture booklet of photographs, cut-away drawings, and exploded views showing structural details of electron tubes has been published by the Tube Department of *Radio Corporation of America*.

The "Tube Picture Book" was prepared especially for use as a visual instruction aid in schools. The tubes "dissected" in the booklet include: typical glass, metal, and miniature types; a subminiature triode; a thyatron; a high-voltage rectifier; a power triode; a super-power triode; television picture tubes; studio and industrial types of television camera tubes;

RADIO & TELEVISION NEWS

Heard...

but not Seen

American's

25th year of leadership

in the design and manufacture of quality microphones. Pioneers of the attractive "full-vision" design of quality microphones to be heard but not seen. Enjoy perfect performance... plus... full vision for both artist and audience.



D 33
BROADCAST
D 22 P.A.

DR 330
BROADCAST
DR 332 P.A.
RIBBON & DYNAMIC
CARDIOID

Write for Free Catalog 46

American

MICROPHONE CO.

370 S. FAIR OAKS AVE., PASADENA 1, CALIF.

pencil-type tubes; and a multiplier phototube.

The booklet is priced at 25 cents a copy and is obtainable from Commercial Engineering, RCA Tube Department, Harrison, N. J.

"REPS' ROSTER"

"The Representatives" of Electronic Products Manufacturers, Inc. has announced publication of its new 1953 National Membership Roster.

Copies are available without charge to any manufacturer, distributor, or other industry person by request on business letterhead. Write the national headquarters office at 600 South Michigan Avenue, Chicago 5, Illinois for copies.

JTC CATALOG

United Transformer Company, 150 Varick Street, New York 13, New York is currently offering copies of its catalogue 530 covering transformers, reactors, and filters.

This 24-page publication is completely indexed and contains specifications and prices for the company's entire line of audio, power, and filament transformers; chokes; Williamson amplifiers and amplifier kits; high-fidelity equipment; toroids; equalizers and filters; etc.

Write the company direct for copies of this publication.

RECTIFIER STACKS

A new bulletin on miniature selenium rectifier stacks for electronic circuit applications is now available from the General Electric Company, Schenectady 5, New York.

The illustrated, four-page publication contains data on the applications, construction features, and electrical characteristics of small selenium rectifiers. Included are tables of ratings and dimensions, plus graphs on the effect of temperature and life expectancy of the various types of stacks.

When writing for this bulletin, please specify publication GEA-5935.

ATLAS SOUND EQUIPMENT

Atlas Sound Corp. of 1449 39th Street, Brooklyn 18, New York has released its 1953 catalogue describing its line of p.a. speakers and accessories and mike stands and accessories.

The catalogue illustrates and lists specifications for such products as projectors, radials, pagings, talk-backs, tweeters, baffles, driver units, transformers, etc. in its loudspeaker section and floor stands, desk stands, boom stands and brackets, sky hooks, cable hangers, etc. in its microphone section.

LOW-COST SPEAKER DATA

Ultrasonic Corporation of 61 Rogers Street, Cambridge, Massachusetts will forward a four-page data sheet on its new high-fidelity speaker unit to those requesting such information.

The publication describes and pictures the company's Model U-25 speaker and its compact cabinet. The system is based on the Baruch-Lang

SPECIAL BUYS!



Radar Indicator unit for conversion to test scope or for use as a modulation monitor. Complete with tubes. But, less 5BP1. Parts alone are worth much more. **\$9.95**



CRYSTALS

Low Freq.—FT 241 A for 55B, lattice filler, 1/2" spc.	54th harm channels listed by fund.	Fractions omitted.
370 388 407 425 444	462 481 501	
372 390 409 427 446	464 483 503	
374 392 411 429 448	466 485 505	
375 394 412 431 450	468 487 507	
377 396 414 433 451	470 488 509	
379 398 416 435 453	472 490 511	
381 400 418 437 455	474 492 512	
383 401 420 438 457	475 494 514	
385 403 422 440 459	477 496 516	
387 405 424 442 461	479 498	

49c each
10 for
\$4.00

WHILE THEY LAST!

350 ft. of 50 ohm coaxial cable.....	\$ 9.95
Attenuator—one cavity type.....	7.95
TS13 Hand Sets, excellent condition.....	5.95
TS Type, exc. less cord.....	2.45
TEB Portable Telephone exc. cond.....	18.95
2 for	35.00
SURPRISE PACKAGE , 15 lbs. of assorted good radio parts.	\$1.95
A real value at.....	

MONTHLY SPECIAL!

Brand New

R-1 ARR-1—220 mc converter with minor alterations becomes a high gain converter with two stages of H. F. amplification—see "Radio & TV News," Jan. 1949..... **\$4.95**
TS-1—Test Set for above..... **4.95**

TUBES

304TL, 5BPI, 5CPI \$5.95 ea.

DYNAMOTORS: The best dynamotor for conversion to 6v. Multiple windings! After conversion you get choice of 100 or 350 v. at 50 MA or 250 v. at 100 MA. Complete doc sheet furnished. **\$4.65**
BRAND NEW (See "CQ" Aug. Issue).....

TRANSCIEVER—140-144 mc, 2 meter, used, excellent condition, less dynamotor, less tubes, only \$17.95

HP-34 APS 13 Transceiver used as a tall warning radar on 412 MC. Containing a 6UMC IF Strip and various other parts, these units have been stripped of IF sections and all tubes, but are an excellent buy if only for parts and IF Strip..... **\$ 4.95**

BROADCAST BAND & AERO

Ideal for Use in Boats, etc.

MIN-26-C Remote Controlled Navigational Direction Finder and communications receiver. Manual DF in any one of three freq. bands, 150 to 1500 KC, 24 V. Self contained dynamotor supply. Complete installation, including receiver, control box, loop azimuth control, Left-Right Indicator, plugs, loop transmission line and hex shafts..... **\$89.50**
LIKE NEW..... **69.50**
MIN-26-Y 150 to 325 KC, 325 to 605 KC, 3-4 to 7 megacycles, comb. installation..... **69.50**
Receiver alone..... **35.95**
MIN-26-C alone, like new..... **39.50**
MIN-26-C or MIN-26-Y as is less tubes..... **13.95**
With tubes, used good..... **24.95**
MIN-20-E Loop, Brand New..... **6.95**
MIN-52 Crank drive, New..... **2.50**

MIKES and HEADSETS: MS-33 Low Impedance Headset..... exc. \$2.95 new \$5.95
MS-23 Headset..... used 2.95 new 4.95
CD-307 1st. cord for MS-23-33..... like new .79
Throat Mike-T-30..... new .98
Lip Mike-Navy Type..... new 1.95
CW-4950 High Impedance headset complete with headband..... used **98c**
HP-7 Headband..... used, exc. \$1.29 new \$1.98
MS-38 Headset..... exc. 1.95 new 2.29
MS-30, miniature headset..... used 1.49 new 2.49

Shipments F.O.B. warehouse. 20% deposit on orders. Minimum order \$5.00. Illinois residents, add regular sales tax to remittance. Prices subject to change without notice.

	AS IS	EXC. USED	NEW
BC-454 Receiver, 3 to 6 mc.....		\$11.95	
BC-455 Receiver, 6 to 9 mc.....	\$4.95	9.95	
BC-456 Modulator.....	2.95	4.95	\$7.95
BC-457 Transmitter, 3 to 6 mc.....		4.95	
BC-458 Transmitter, 5.3 to 7 mc.....		4.95	
BC-459 Transmitter, 7 to 9 mc.....	7.95	14.95	
Control boxes, racks, receivers for above in stock—write.			
SCR-625—Mine Detector—New.....			\$59.50
BC-357—Exc. L/T.....			5.95
BC-709—Inter. Amp. New.....			3.95

WANTED: All TS, APR, AP5, ARC, ARN, SCR, R89 and BC equipment! Write today! Quote lowest prices in your first letter

TUBES

10 assorted for \$3.00
954, 955, CH1005, 1625, 1626, 1613, 1619, 32, 33, 34, 9002, 9004, 9006, 627G, 1N5GT, 6J5G, 12A6, 12S17G7, 12S47G7.

MISCELLANEOUS EQUIPMENT

FL-8 used, exc..... \$1.19 BC-347 each..... used 95c
BC-906 each..... 9.95

RT7 APN-1 TRANSCIEVER UNIT—Used as an altimeter it may be converted for signaling control circuits, etc. Complete with 14 tubes and dynamotor they are in good used condition at the amazing low price of..... **\$29.95**
Used, less tubes, as is..... **4.95**

AR2 Receiver—214 to 258 mc, less tubes..... **\$10.95**
BC-624 receiver SCIT 522, less tubes, used **14.95**
100-136MC

WOBULATOR

BUILD TV-FM-AM SWEEP GENERATOR

You can build Versatile Sweep Frequency Generator with APN-1 magnetic units..... **\$ 6.95**
BC-1200 Beacon Receiver..... **9.95**
MIN-261B Receiver exc..... **59.50**
RCA Sound Powered Phones..... brand new..... **12.95**
two for **24.95**
TS-184 AP Test Set..... **69.50**
APN-2 Radar Search Receiver, 85-1000MC..... **195.00**
APN-1 Radar Search Receiver, 38-4100MC..... **199.00**
Tuning Unit—TN16, TN17, TN18..... each **200.00**
HP-19A-SCR522 Test Unit..... used **295.00**
MG-123 Inverter..... used **69.50**
I-222-Signal Generator..... Used, exc. **125.00**
AN-APT5 Transmitter..... Like new **189.50**

SELSYN TRANSMITTER: Autodyn Transmitter Assembly for matching to I-R2 Indicator. Used, excellent condition. **ONLY \$7.95.** Complete with Indicator..... **\$14.95**

RL-42 Reversible Motor with antenna reel and clutch, used..... **\$ 2.95**

BC-433 RADIO COMPASS RECEIVER, 200 to 1700 KC, used, excellent condition with tubes..... **39.95**
used, exc. less tubes..... **24.95**
used, as is, less tubes and cover, exc. for parts..... **8.95**

RW ELECTRONICS

Dept. N, 1712-14 S. Michigan Ave., Chicago 16, Ill.

PHONE: HARRISON 7-3177

RKAI
world's finest radio kits
Write for free Brochure
RADIO KITS, INC., 120 Cedar St., N. Y. 6

GET INTO TV SERVICING

Send for free 24-page illustrated booklet which tells you how to become a successful TV technician. America's leading TV servicing school offers you a specialized training program that omits non-essential math & design theory. You concentrate on radio & TV servicing only. You get professional training & experience right in our fully-equipped shops & laboratories. Send for this booklet today. Write Dept. H-93. No obligation—no salesman will call.

Approved for Veterans
WESTERN TELEVISION INSTITUTE
341 W. 18th St. Los Angeles 15, Calif.

ALTERNATOR—GEN. (NEA-2D)

For IKW Emergency Plant • Mobile • Amateurs • Marine Radio & Power • Test Bench & Shop Power

Output 108VA @ 115V, 800 cy. & 24 VDC @ 25A at any speed from 2400 to 4200 rpm. Speed clutch holds from 2% designed to operate @ 1500 rpm for FULL RATED output at 600 cy. & 12VDC @ 25A. Alternator, less clutch, 6 1/2" D x 7" H. Overall lg. w/clutch 12". Wt. 42 lbs. Instructions furnished.

Excellent Cond. **\$18.95** New..... **\$24.95**
Used.....

25% with C.O.D. orders. Satisfaction guaranteed. F.O.B. Los Angeles.

POSSNER CO.

1223 Venice Blvd., Los Angeles 6, Calif.

now!

INTERMODULATION DISTORTION

0.09%

AT AVERAGE LISTENING LEVELS

FOR ONLY \$109.95

The **NEW Shields**
Model SPA-25
AMPLIFIER

- Outstanding sound quality at a record low price.
- A power output of 25 watts with less than 0.7% intermodulation distortion. Power response from 18 cps. to 40 kcs. plus or minus one db.
- Internal output impedance of less than one ohm.
- A compact, sturdy unit adaptable to almost any high fidelity system.

**GET THE FACTS —
MAIL THIS COUPON TODAY!**

Shields Laboratories, Inc.

Please send me your bulletin on the new SPA-25 Power Amplifier.

NAME

ADDRESS

CITY

STATE

RTVN-953

Shields LABORATORIES, INC.
810 N. LINCOLN AVENUE
PITTSBURGH 12, PA.

principle which permits high quality performance from a compact unit.

DU MONT PUBLICATIONS

Allen B. Du Mont Laboratories, Inc. has announced the availability of three new publications of interest to service technicians.

The first is a spiral-bound service information book containing schematics, parts lists, alignment data, and miscellaneous service data on all of the company's television receivers. This publication is available from Du Mont parts distributors.

The second publication is a thirty-two page guide of original television parts and picture tubes for replacement in the company's TV receivers. The cross-indexed guide also includes electrical values of the components. It is available from the company's parts jobbers.

The third offering is the eighth edition of the company's "Picture Tube Data Chart". Printed on heavy stock suitable for hanging on the wall or folding into a notebook, this chart lists complete specifications for more than 150 picture tubes of all manufacturers. Parts distributors are handling this item.

TV TUBE RENEWAL

Eisler Engineering Co., Inc., 750 South 13th Street, Newark 3, New Jersey is currently offering copies of its new catalogue, "Equipment Required to Renew Burned Out Television Tubes".

This 8-page publication contains 70 illustrations of the various items needed by television tube manufacturers.

Copies of catalogue TV-RN-53 are available on request.

AUTO RADIO DATA

Thordarson-Meissner of Mt. Carmel, Illinois has announced the release of its new 1953-1954 "Automobile Radio Replacement Guide".

The new publication lists replacements for vibrator transformers, interstage transformers, output transformers, oscillator coils, input and output i.f. transformers, and ratio detector i.f. transformers.

All makes of automobile radios are listed in this informative and compact guide. Copies are available from Dept. C of the company.

FREE TOOL GUIDE

United Catalog Publishers Inc., 110 Lafayette St., New York 13, N. Y. has recently released a 36-page "Handi-Guide" covering a wide assortment of tools for the repair and maintenance of radio, television, and electronic equipment.

This handy reference book for technicians, engineers, experimenters, amateurs, and purchasing agents is available without charge. It contains detailed specifications, illustrations, technical data, and prices on tools made by 17 leading manufacturers. Included are TV alignment tools, chassis punches, pliers, screw and nut

CRYSTALS

FOR ALL PURPOSES

LOW FREQ.—FT 241A for SSB, lattice filter, 1/2" spc. 54th or 72nd harm channels (listed by fund. Fractions omitted).	SCR. 522 1/2" sp	BC-610 2 banana plugs 1/4" spc.
370 392 412 433 494 515	400 459	5910 2030 2415
372 393 413 434 495 516	440 461	6370 2045 2435
374 394 414 435 496 518	441 462	6450 2065 2442.5
375 395 415 436 497 519	442 463	6470 2105 2532.5
376 396 416 437 498 520	445 465	6522.9 2131 2557.5
377 397 418 438 501 522	446 466	6547.9 2145 3202.5
379 398 419 481 502 523	447 468	6610 2155 3215
380 401 420 483 503 525	448 469	7360 2220 3237.5
381 402 422 484 504 526	450 470	7390 2258 3250
383 403 423 485 505 527	451 472	7480 2260 3250
384 404 424 486 506 529	452 473	7580 2280 3510
385 405 425 487 507 530	453 474	7810 2282.2 3520
386 406 426 488 508 531	454 475	7930 2290 3550
387 407 427 490 509 533	455 476	2300 3570
388 408 429 491 511 534	456 477	2305 3580
390 409 430 492 512 536	457 479	2300 3945
391 411 431 493 513 537	458 480	2360 3955
514 538		2390 3995
49¢ EA—10 for \$4.50	99¢ each	200 or 50 KC
	10 for \$9.00	1 IN FT 241 A HOLDER
		1/2" SPC. \$1.95 EA.

FT 243—1/2" P IN SPC.

4190 6140 7806	1015 5760 5906 6340 6540 6706 7640	
5030 6206 7840	3735 5773 5940 6373 6573 6740 7650	
5485 6773 7873	5305 5800 5973 6406 6575 7440 7673	99¢
6040 6873 7906	5677 5806 6273 6450 6606 7506 7706	EA—10
6073 7773 7940	5706 5840 6306 6473 6640 7573 7973	for \$39.00
	5725 5873 6325 6506 6673 7606 8240	
	5740	
49¢ EA—10 for \$4.50		

Special Purchase! FM RADIO CHASSIS

88-108 MC—complete with 6 tubes, built-in antenna and speaker. Product of famous radio and TV maker whose name we promised not to mention. **\$16.95**
Maroon plastic cabinet for above \$5.95.



**DO NOT SEND POSTAGE;
We Ship the Best Way. Collect.**

TWO-STATION INTERCOM SYSTEM



Consists of master and remote station, 20-ft. of 3 wire cable, 115 V operation, AC or DC. Extra wire .06 per ft. **\$16.97**

NOTICE TO ALL HAMS
TRADE-IN your used communications gear on new Hamblers. National IRE, Hammarlund, Sonar, Elmac, Gonset, Etc. equipment. Write for FREE ESTIMATE, attention "Pick"—W3PPQ.

FREE QUOTATIONS
on hi-fi equipment yours on request. All famous brands of amplifiers, tuners, changers, pick-ups, speakers, etc. Just tell us how much you want to spend and we'll recommend the best matched system your budget will allow!

Sun

PARTS DISTRIBUTORS, LTD.

520 TENTH ST., N.W. - WASHINGTON, D.C.

The Next Big
**FACT FILLED EDITION of
RADIO & TELEVISION NEWS**

Will Be On Sale Sept. 25.

Reserve Your Copy TODAY!

**AUDIO (SOUND) ENGINEERING COURSE
HOME STUDY TRAINING**

Prepare yourself, in your spare time for a BIG PAY JOB as an AUDIO ENGINEER. Practical, easy-to-understand lessons, written by nationally recognized Audio Engineers and Educators. Prepare for a SUCCESSFUL CAREER in the TELEVISION, RADIO, DISC and TAPE RECORDING, ELECTRONICS.

Training will not interfere with present employment.

**EARN WHILE YOU LEARN
WRITE FOR COMPLETE DETAILS—TODAY**
HOLLYWOOD TECHNICAL INSTITUTE
15228 Ventura Blvd. Sherman Oaks, Calif.

RADIO & TELEVISION NEWS

drivers, soldering irons and guns, tool kits, wire strippers, etc.

TELEVISION HARDWARE

A 12-page catalogue which describes and illustrates its complete line of television mounts, hardware, and accessories is now being offered by *I. E. Manufacturing Company*, 325 N. Hoyne Street, Chicago 12, Illinois.

The self-bound catalogue, No. 16, lists the features of each unit together with detailed specifications and retail prices.

Copies are available on request. -30-

SOUTH JERSEY HAMFEST

The South Jersey Radio Assn. will hold its annual hamfest on Sunday, September 13th at Locust Grove Farm on Almonesson Road near Westville, N. J.

The program starts with registration (\$1.00 per family) at 10 a.m. Each family should bring its own picnic lunch. Free soft drinks will be furnished.

Mobiles should contact K2AA on 2, 10, and 75 meters for driving instructions. Bill Bowers, W2EGP, 303 Lakeview Ave., Haddonfield, N. J., will supply additional information. -30-

ELIMINATING FOLDOVER

By ELMER FISCHER


WHILE converting to a larger screen for a critical customer, the author encountered the problem of obtaining rapid enough flyback to avoid foldover. After exhausting all possibilities of doing it the easy way, a vacuum-tube circuit, as follows, was developed.

Positive-going flyback pulses were obtained from the plate of the vertical-output tube and the a.g.c. winding of the horizontal-output transformer. These pulses were applied to the grids of a 6J6 through .01 μ fd. condensers, no grid resistors being necessary. The 6J6 plates were connected directly to "B+", and the two cathodes and the kinescope cathode were tied together and returned to the brightness control through a 15,000-ohm resistor.

About 90-volts peak-to-peak mixed blanking voltage appeared at the kinescope cathode.

Resistor values in the brightness-control circuit may have to be changed slightly as compensation for the 15,000-ohm resistor and the 6J6 current. -30-

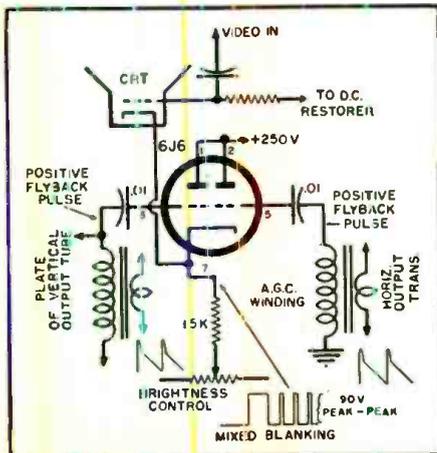Method for increasing flyback pulse rate.



September, 1953

YOUR BIGGEST DOLLAR VALUE IN RECEIVERS!



THE *Mighty Midget* SW-54

COVERAGE: Entire frequency range from 540 kc. to 30 mc. in 4 bands. Voice, music or code.

FEATURES: Sensitive and selective superhet circuit, using new miniature tubes. Slide rule general coverage dial with police, foreign, amateur and ship bands clearly marked. Unique plastic bandsread dial is adjustable to assure logging accuracy over entire range. Built-in speaker and power supply. Volume, Receive-Standby, Band-switch, AM-CW, Speaker, Phones. Smart, unbreakable grey metal cabinet 11" x 7" x 7".

\$49.95*



for radio's crowning achievements

THE *World-Master* NC-88

COVERAGE: Entire range from 540 kc. to 40 mc.

FEATURES: Calibrated bandsread for 80, 40, 20, 15, 11 and 10 meter bands! Eight min. high gain tubes in advanced A.C. superhet circuit. Tuned R.F. stage. Two I.F. stages. Built-in spkr. Ant. trim. Separate high freq. osc. Sensitivity control. Noise limiter. Delayed A.V.C. Headphone jack. Standby-receive switch. Tone control. **\$119.95***

*Slightly higher west of the Rockies



National


National Company, Inc., Malden, Mass.



PC 2362

MEASURE: INDUCTANCE, CAPACITY, DISTRIBUTED CAPACITY & MUTUAL INDUCTANCE.

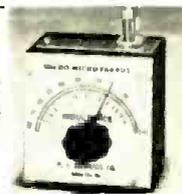Use this CALIBRATED CAPACITOR with a grid dip meter or VTVM and signal generator for an engineering approach to service and experimental work. Price \$5.00. Write for information. **P. E. HAWKINS CO.** 3208 E. 56th St. N. KANSAS CITY 16, MO.



BARGAIN HUNTING? RADIO SERVICEMEN!
Write for SENSATIONAL CATALOG
HENSHAW RADIO SUPPLY
3619 TROOST KANSAS CITY, MO.

CASH FOR SELSYNS

Navy or Army Ordnance type #0 cycle types as follows: \$35.00 for 1DG, 1D, 1F, 1G, 1DF, 1CT; \$20.00 for 5DG, 5G, 5F, 5CT, 5D, 6DG, 6G, 6CT; \$25.00 for 7G, 7F, 7CT, 7DG. ALSO NEED: GE Selsyns Models 2J5HA1, 2JD5HA1, 2J5LA1; Autosyns AY100 or 200 series; Diehl Control Motors 49-7, 25-11, etc.; Delco and GE PM Motors, Inverters, Tubes, and other Electronic Components. All Merchandise Subject to Inspection. Send Lists—Will advise Price.

Electro Sales Co., Inc.

Depl. RN 58 Eastern Ave Boston 13

more
and more
replacement
problems
are being
solved
this way



for complete
information
write-

SARKES TARZIAN, INC.
RECTIFIER DIVISION

15 N. COLLEGE AVE., BLOOMINGTON, INDIANA

Standard Coil Tuner

(Continued from page 37)

u.h.f.-v.h.f. changeover switching. The outer fingers of this molded piece hold the u.h.f. coil sections in place, the inner portion forms a double-action cam in which a follower rides and this, in turn, is linked to the u.h.f.-i.f. coil section "C" in Fig. 3.

The appearance of three typical coil sections as they were removed from the drums is shown in Fig. 5. In front is the u.h.f. coil section with the two front stators and coils forming the oscillator tank circuit. Between the oscillator tank circuit and the u.h.f. r.f. bandpass network is a small wire link which couples the oscillator voltage to the mixer. This link is on the outside of the coil form, see Fig. 4. The center coil section in Fig. 5 is the v.h.f. oscillator and mixer strip with the slug-tuned oscillator coil and the slug retainer spring visible in the front. The last coil strip carries the 300-ohm balanced v.h.f. input circuit. A better view of the operation of the u.h.f. and v.h.f. switching section can be had in Fig. 6, showing the inside of the tuner with the drums removed. The cam follower which accomplishes the u.h.f.-v.h.f. switchover can be seen right at the partition of the two chassis. Its linkage extends to the pivoted section "C" which contains the coils for changing the v.h.f. into an i.f. amplifier. Also visible in this photograph is the u.h.f. fine tuner, the u.h.f. oscillator tube socket, and split-stator master trimmer just below it.

The v.h.f. circuitry shown in Fig. 6 is conventional except for the use of ceramic feedthrough condensers to isolate "B+" and heater leads. Note the extra long contact springs. For v.h.f. channels contact with the drum coil sections is made at the approximate center of each spring. For u.h.f. operation, coil section "C" is tilted forward in the illustration by the action of the cam follower and linkage, and this puts pressure on the contacts at the far end of the springs, pushing

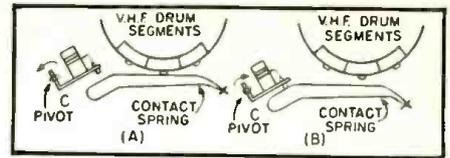


Fig. 8. Simplified drawing of the operation of the pivoted i.f. coil section, (A) in v.h.f. position, (B) in u.h.f.

these springs away from the v.h.f. coil segments and, instead, connecting them to the i.f. coil section "C." This coil section can be seen better in Fig. 7. Here is shown the u.h.f.-i.f. input cable, connector, and lead to L_{10} (see Fig. 3). L_{15} and L_{16} are slug-tuned and also mounted on coil section "C." As shown in Fig. 7, this coil section is tilted away from the spring contacts and only v.h.f. stations would now appear. The simplified sketch in Fig. 8 shows the two positions of coil section "C" as seen from the rear of the tuner.


Another feature which cannot readily be shown in photographs is the rocking motion which takes place each time a channel is switched. This motion is due to the design of the cam and serves to wipe all v.h.f. contacts to keep them clean and noise free.

Although individual manufacturers will use different types of knobs, the channel presentation is dictated by the operation of the tuner itself.

Assume that Channel 37 is desired. Simply turn the middle knob to 3 and then turn the inner knob until the 7 appears next to the 3, showing 37. Then adjust the outermost knob for fine tuning. To tune in Channel 8, turn the middle or u.h.f. knob until the v.h.f. window shows some number. Looking at the v.h.f. window, turn the v.h.f. or inner knob until 8 appears. Adjust the outermost knob for fine tuning. If the set is tuned to Channel 15, for example, it is not necessary to tune through all intermediate channels to get Channel 79. Simply turn the u.h.f. knob from 1 to 7 in either direction, then turn the inner or v.h.f. knob from 5 to 9 in either direction.

The 6.3-volt a.c. heater bus re-

Fig. 7. Another view of tuner chassis showing the pivoted i.f. coil section.

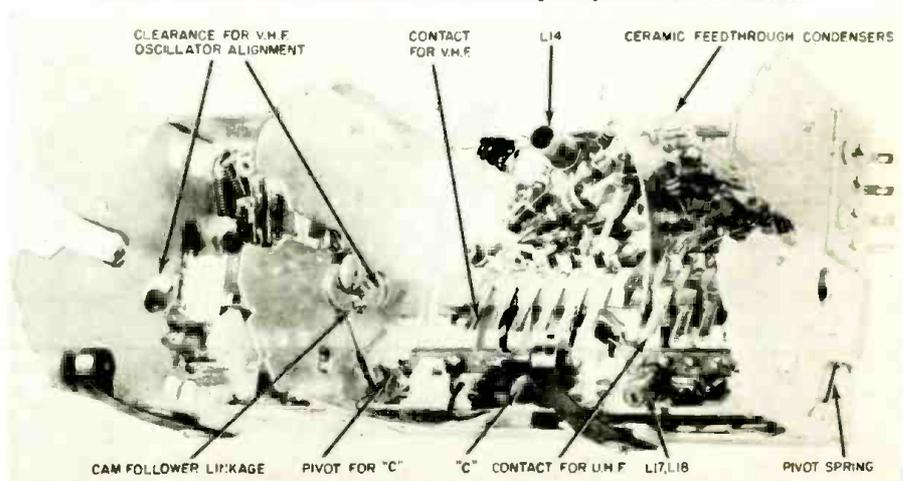

GROMMES AMPLIFIERS



WRITE FOR CATALOG

PRECISION ELECTRONICS, Inc.
 8101 King Avenue, Franklin Park, Ill.

Be UP-TO-DATE—Read

RADIO & TELEVISION NEWS

Every Month



17" Table
\$122.68

Pl. \$12.27 Fed. Excise Tax

20" Table
\$134.50

Pl. \$13.45 Fed. Excise Tax

Check these luxury features: Ultra sensitivity, dynamic range control, UHF adaptability. Duo power supply. Acoustic-clear sound system... all in a beautiful Mahogany finish cabinet.

20" Console
\$149.95

Pl. \$15.00 Fed. Excise Tax

21" Console
\$164.95

Pl. \$16.50 Fed. Excise Tax

ALSO AVAILABLE TV CHASSIS

All sets have full 1-yr. factory picture tube warranty, and standard 90-day RTMA parts warranty. Mail and Phone Orders Filled. \$25 deposit, balance C.O.D., Shipping Charges Additional.

STEPHEN SALES CORP.

45 Crossby St., N.Y. 12, N.Y. Phone: WO 4-8233

Dealer Inquiries Invited

quires a total of 1.075 amps. The a.g.c. bias voltage may vary from 0 to 5 or even 6 volts on very strong signals. Naturally any variation in bias will also vary the d.c. current drawn by the 250-volt "B+" since the bias controls the 6BZ7. "B+" current from the 250-volt bus varies from 20 to 30 ma. as the bias changes from 1.5 volts to zero. When more than 3 volts of bias are applied, the gain of the tuner is reduced by about 12 db and the current will drop to about 12 ma.

Current through the 150-volt "B+" remains at 17 ma. for u.h.f. operation, and 12 ma. for v.h.f. Neither the 150 nor the 250-volt "B+" values are critical as long as a minimum of 140 and 230 volts respectively is available.

The most important characteristic of any tuner is its noise figure. Because a low-noise cascode input circuit is used, the v.h.f. noise figure of the tuner described here is excellent. Production samples of this tuner give noise figures below 4 db on Channels 2 to 6, and below 6 db on the higher v.h.f. channels. The noise figures for u.h.f. are not so uniform since they are, to a great extent, dependent on the 1N82 mixer crystal. Representative measurements, however, show that individual channels or groups can be aligned to less than 10 db noise figure, while the worst noise figure for any channel is below 14 db.

Although these figures do not look as attractive as the v.h.f. noise characteristics, they are based on the limits of crystal noise, impedance matching, and other circuit parameters. In actual field tests, the noise performance of the 82-channel tuner on u.h.f. compared very favorably with other tuners and converters.

Next to noise, the over-all conversion gain of the tuner is of interest. Exact figures on this are not yet available but, from the circuit itself, it is apparent that the v.h.f. gain is somewhat better than in current v.h.f. tuners, due to the use of a pentode mixer. For u.h.f. the loss in the r.f. bandpass network is on the order of 1 or 2 db, but the i.f. gain through the 6E27 and 6U8 considerably boosts the over-all gain until it is almost the same as for v.h.f. An approximate over-all gain figure is about 40 to 50 db, depending on i.f. bandwidth, a.g.c. bias, and "B+" voltage supplied. Because of this high gain it is possible to use only two or three i.f. stages after the tuner and still have a very sensitive receiver.

Bandpass characteristics for the v.h.f. channel are the same as in any other v.h.f. turret tuner, i.e., 6 mc. between peaks with less than 3 db valley on any channel. For u.h.f. such narrow bands are not practical and are not used. On the lower u.h.f. channels the r.f. bandwidth of the input circuit is approximately 20 mc. between peaks, while at the higher u.h.f. channels the bandwidth increases up to 35 mc. Because the crystal mixer is part of the load across the r.f. input

SHARPER PICTURE BETTER *all around* PERFORMANCE!

CHANNELS 2 TO 83

UHF & VHF


VU-1

RECEPTION *in* METROPOLITAN AND PRIMARY AREAS

BE "ALL SET" WHEN UHF
 COMES TO YOUR CITY!

- One lead-in wire for all channels.
- Reception up to 50 miles, depending on terrain and power of transmitter.
- Quality construction throughout... double plate dipole holders... heavy cast aluminum mast clamp... heavy gauge aluminum cross arms... 7/16" aluminum tubing for extra strength and long life... micarta insulator... over-all lightweight and partial pre-assembly mean easy assembly and erection.

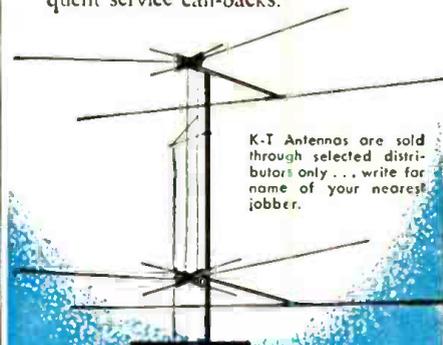The "best by test"... according to leading technicians in areas now receiving both UHF and VHF! No matching pads or isolation filters... no coils or condensers which tend to cut down signals and increase cost of installations. K-T engineering has eliminated the "bugs" and the possibilities of frequent service call-backs.



K-T Antennas are sold through selected distributors only... write for name of your nearest jobber.

VU-2

KAY-TOWNES ANTENNA CO. BOX 586, ROME, GA.

THE BEST SET IS ONLY AS
 GOOD AS ITS ANTENNA

Let these antenna experts help you

To be sure of getting the most out of the antenna system at any site, use Noll and Mandl's



Television and FM Antenna Guide

Both a practical installation handbook and a clear, understandable text on v.h.f. antenna theory, this book gives you all the information you need to choose the best antenna for a particular site and install it for best performance.

You'll be equipped to deal with the many individual problems you meet in weak signal and fringe areas and other difficult sites. You'll know, without trial and error and with minimum testing, which type of antenna will give best reception, how to place it to best advantage, and how to reduce interference, overcome ghost reception, boost signal strength, etc.

The authors, both well known writers on TV service problems, have made extensive tests on antennas. The data they give here on antenna characteristics and comparative performance is complete and ACCURATE.

Is this book on your work shelf?



Mandl's Television Servicing

THE NEW REPRINT of this widely used service guide includes new data on the cascade tuner, servicing newer types of i.f. systems, automatically focused tubes, UHF station listing and antenna calculations, transistors and other recent developments. All faults likely to occur, including those hard-to-find troubles, are dealt with in the clearest, most practical way. A master index enables you to turn directly to procedures for locating and correcting any particular flaw in sound or picture.

SEE THEM ON APPROVAL

The Macmillan Company, 60 Fifth Ave., N. Y. 11

Please send me the book(s) checked below. I will either remit the full price plus small delivery charge, or return the book(s) in 10 days. (Save: Enclose check or money order and we pay delivery charge).

TV & FM Antenna Guide, \$5.25 Mandl's TV Servicing, \$5.50

Signed _____

Address _____

This offer good only within continental limits of U.S.A.

circuit, the amount of crystal current will affect the "Q" and, therefore, shape of the r.f. bandpass. Average crystal current is on the order of 1 to 2 ma. so that the valley in any response curve will be less than 2 db. Actual wave shapes show a very flat and symmetrical bandpass characteristic.

The u.h.f. and v.h.f. oscillators are both tuned above the incoming signal by 41 mc. or 21 mc., depending upon the i.f. For v.h.f. operation, the v.h.f. oscillator is adjusted just as in current v.h.f. models, through a hole in the front. By passing a long fiber alignment tool through this hole a brass or aluminum slug may be turned inside the oscillator coil which tunes it to a particular channel. The hole for the alignment tool goes clear through the u.h.f. tuner section only when v.h.f. is tuned in. On u.h.f. channels no clearance is available, and only the u.h.f. oscillator itself can be aligned. As shown in Fig. 4, the u.h.f. oscillator adjustment consists of a screw which protrudes through the u.h.f. detent plate into the region of the oscillator condenser stator plate.

The i.f. coils mounted on section "C" are tuned by powdered iron slugs

which are accessible from the bottom of the tuner. All other adjustments are available from the top of the tuner and can be made with the tuner in the set. The range of the v.h.f. fine tuning adjustment is approximately 1 mc., while the u.h.f. fine tuning control shifts the u.h.f. oscillator frequency by only 2 to 3 mc. This latter shift is relatively small at these high frequencies, but if it were any greater serious mistuning would be possible by the unskilled viewer. As it is, it does not permit tuning in the wrong channel through the fine tuning, if the u.h.f. oscillator screw is adjusted correctly.

Undoubtedly many improvements will be made on this and successive tuner models, and it is foreseeable that a single r.f. amplifier, oscillator, and mixer will soon be used for all 82 channels. In such a tuner the decade and digit switching system, together with the changeover cam arrangement, would be of real value. Until tubes are available which can amplify u.h.f. and v.h.f. equally well, the tuner described here will certainly find wide and successful application in many different TV receivers.

-30-

AN IMPROVEMENT FOR OLDER TV SETS

By CHARLES ERWIN COHN

ALTHOUGH all present-day TV sets use some form of a.f.c. in their horizontal sweep circuits, many older sets did not have such circuits, but used triggered sweep, which has since been abandoned due to its extreme noise susceptibility. However, many of these older sets are still quite serviceable, and it may be desirable to improve the horizontal action, but a complete conversion to an a.f.c. circuit is a major operation and might not be worthwhile on an old set. However, with the modification to be described here the noise immunity can be greatly improved with very little work, if the set uses a multivibrator in the horizontal circuit.

The nature of the modification can be seen from Fig. 1A, and consists of placing a tuned "ringing" circuit in series with the cathode resistor. L₁ can be a commercial ringing coil such as the Miller 6210, while C₁ can be about 3900 μfd .

Adjustment of the circuit is very simple and can be done without instruments. To do it, first short out the tuned circuit and also short the grid of the first triode to "B+", cutting out the sync. Then adjust the horizontal hold control until the picture is synced in as nearly as possible. Then without changing anything else, remove the short from the ringing circuit. This will make quite a change in the image, but you can then adjust the slug in the ringing coil until the picture is again synced in, leaving the hold control at its original setting. Then remove the short from the first triode grid and the modification is complete.


The action of this circuit can be seen from Fig. 1B. Waveform "A" shows the grid-cathode voltage of the first triode without the ringing circuit. Here the dotted line is the cut-off level below which triggering takes place. It can be seen that a noise pulse (shown dotted) coming in between the sync pulses has

no trouble in triggering the circuit and causing tear-out of a line. However, as shown in waveform "B," the ringing circuit superimposes a sine wave on the sync pulses and thus, as shown, hinders the false triggering of the circuit by a stray noise pulse.

This simple modification cannot be expected to give the same accurate sync as a standard a.f.c. circuit, especially on weak signals, but it does give an improvement which makes it well worthwhile to install.

-30-

Fig. 1. (A) Modification to add a "ringing" circuit. (B) Circuit waveforms. See text.

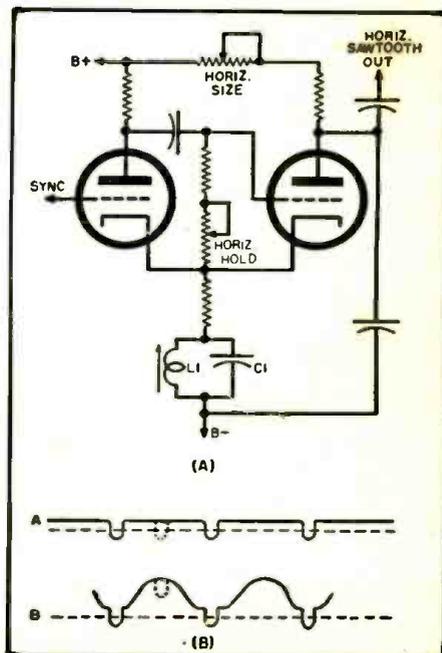

Electronics at the Fair (Continued from page 73)

the Radio-Television Building, the outdoor amphitheater, the Mexican Village, and the school exhibit, along with the various livestock judging rings.

The equipment used in the Radio-Television Building auditorium consists of a high-fidelity installation with two complete amplifying systems. The high-frequency system employs RCA re-entrant-type trumpet horns, while the low-frequency system uses Western Electric type 728-B bass reflex speakers with audio power obtained from two RCA 30-watt high-fidelity amplifiers. A four-channel Western Electric 22E amplifier is used to feed these two high-fidelity amplifiers simultaneously.

Typical outdoor installations throughout the rest of the Fair grounds include RCA re-entrant-type trumpet horns and RCA amplifiers. A system located in the stable area notifies the jockeys and trainers of the next race. Since the stable covers considerable area, large RCA re-entrant trumpet horns are used, along with powerful amplifiers.


Children, who are lost, are placed in a small Austin roadster and driven through the grounds while their parents are being paged through loudspeakers mounted on top of the car.

During the run of the 1952 Fair, nightly musical entertainment was provided by the well-known pianist, "Liberace." These performances were held on a large stage erected in front of the grandstand and required a high-fidelity, theater-type installation to cover sound reproduction over an area 420 feet wide, 65 feet high, and 120 feet deep. To accomplish this, five special Stephens "Tru-Sonic" reproducing systems were installed. Each system consisted of a double folded horn 80 inches long, 40 inches high, and 30 inches deep and two low-frequency driver units. On each side of the folded horn was mounted a 2 by 5 multi-cellular high-frequency driver unit. These speaker banks, when assembled, weighed approximately 400 pounds each and presented quite a problem to mount 65 feet in the air. This was done by block and tackle, hoisting the units up to steel crossmembers supporting the grandstand roof and then securing them in place by chains at the correct elevation to distribute sound evenly throughout the entire grandstand with no dead spots.

Amazing lifelike reproduction was accomplished through the use of the Stephens 500-D direct-drive amplifier, which eliminates the output transformer. Power is delivered from the cathode of the amplifier output tubes through a 600-cycle crossover network to specially wound 500-ohm voice coils of the high- and low-frequency units. Frequency response of

METER AND MULTI-METER BARGAINS

These gorgeous meters are made in Japan to the highest U.S. standards for meters made to sell at double these prices. We had Bureau Veritas (International Inspection Agency) test and inspect them for us at source. They report that the tolerances are MUCH BETTER than the MAXIMUM permissible deviations shown below. Therefore we offer them with an IRON-CLAD, MONEY-BACK GUARANTEE. Both models come with instruction sheet, test leads, and internal dry battery of standard American size, shape, and type. Ideal for service work, experimenters, students, home builders, and the fellow who would rather leave his expensive lab-standard equipment behind when he goes on rough field trips.

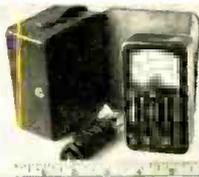

(left)
**Pocket Model
TK-30 Tester**

In genuine leather
carrying case.

\$11.95
Only

(Plus 25c shipping)

RANGES: AC and DC volts 0-15/150/750. 1%. DC MA 0-150. 4%. Ohms 0-100K, 10%. In rugged black bakelite case and leather carrying case.

(right)

**MODEL 27-Z
TESTER**

\$9.95
Only

(Plus 25c shipping)

RANGES: AC and DC volts 0-5/25/250/500. DC MA 0-1/10/100/250. Ohms 0-10K, 100K. Black bakelite panel, metal case. Manufacturer claims extreme accuracy and our spot checks show them to be within 1%. Here is a meter to be proud of!

MODEL MO-52 0-1 DC MILLIAMETER

(Not shown)

Standard 2" round panel-mounting meter with hair-line needle indicator. Spot-checks better than 1% accuracy. White face with black calibrating. Graduations every 0.02 MA (250 μ A). **ONLY \$3.95** (Plus 25c shipping charge)

12 VOLT RECEIVER DYNAMOTORS. Deliver 250 vdc, 60 ma. Shipping wt. 4 lbs. **EXCELLENT USE \$7.95**

274N PLUG. 7-prong male plug to fit back of command reverb. and xmtrs. This is the same plug as used in the racks. NEW, each 21c. Five for **\$1.00**
Local Control Adapter Parts for 274N or AHC-5 reverb. Exact pot, switch, knob, etched plate, and instruction data. Ready to mount. **\$1.29**

MOBILE VHF ANTENNA KIT

Famous make, designed for two-way police and taxi operation. Complete with 16" chrome plated detachable rod, base fitting, 10" coax, dome sheet. **BRAND NEW, ONLY 98c** (Shipping weight, 2 lbs.)

PE-101-C DYNAMOTOR. Brand new. **\$4.95** (Shipping weight, 13 lbs.)

OUTPUT TRANSFORMER. 5000 ohms input to TWO outputs, 300 ohms or 3-5 ohms. Use as output for 12A6, 6V6, etc., or to match speaker or headset. **NEW, shipped, shielded. 79c**

ANTENNA MAST SECTIONS. MS-49, 50, 51, 52. **39c** new, original packing. Each

CRYSTAL MICROPHONE GIVEAWAY!
Sensitive hearing aid capsule sealed in neat, compact, flat container with lined terminals. Crisp, clear, high level output. Ideal for lapels, ties, tuck-aways. Individually tested and guaranteed. **ONLY 98c**

G. L. ELECTRONICS 905 S. VERMONT AVE. LOS ANGELES 6, CALIF.
ALL PRICES F. O. B. LOS ANGELES, CALIF. BUYERS ADD SALES TAX

\$2.95 EACH OR 2 FOR \$5.00



Upright Telephone complete with cord in Tested and Guaranteed condition. For inter-communication or extension. Complete list of telephone parts, inter-communication sets, switchboards, handsets, magnets and dial telephones, etc. Write for list, F.O.B. Simpson, Pa. C.O.D. shipments accepted.

TELEPHONE ENGINEERING CO.

Dept. G. SIMPSON, PA.

**SALE OF ELECTRONICS
NOTICE TO PROSPECTIVE BIDDERS:**
The State of Wisconsin, Department of Public Instruction, Division of Surplus Property, will offer for sale, by sealed bid offering, several lists of new electronic properties.
Bid lists, inspection procedures, and method for submitting bids, will be provided upon application. Inquiries and requests for bid lists should be addressed to:
Palmer O. Johnson, Supervisor, Department of Public Instruction, Division of Surplus Property, 147 North State Capitol, Madison 2, Wisconsin.

SENSITROL RELAY

WESTON SENSITROL, coil sensitivity only 10 micro-amps. Built like meter. AC 110v. needle swings over into permanent magnet which grips it to close contacts rated 1 ampere. Perfectly damped; vibration will not close contacts. Built-in reset unlatches contacts when 12 to 24 volts AC or DC is momentarily applied to reset leads. The Sensitrol works directly from photocells, thermocouples, or any source of min. use current. No electronic amplifier needed. **\$12.95**
A \$69.50 precision device for only

SENSITIVE POLARIZED RELAY

This is the device that the services use to replace relays. Now offered to the public for the first time! SP/DT. All contacts normally open. The POLARITY of an applied 1% VDC, 5 MA current determines which contact closes. Use for micro-switching, remote control, model control, etc. Our free data sheet shows you just how to use it. In metal box with two other heavier duty relays. NEW slightly dirty. **\$6.95**
(Shipping weight, 4 lbs.)

SUPER SENSITIVE RELAY BK-7-B

Single pole, double throw. Coil 4000 ohms. Sensitivity accurately adjustable on calibrated scale. At 5 on scale sensitivity is 1/2 millamp (1 milliwatt, 2 volts) and from 5 to 40 on scale the sensitivity decreases linearly to 1.5 ma (9 milliwatts, 6 volts). Thousands of uses: telemetering, voice-operated, capacity operated or thermocouple operated circuits, sequence circuits, etc. Fully enclosed, 1 1/2" x 3 3/4" x 1 1/2" deep. Weight, 6 oz. White hinged contacts, inspection door and screwdriver adjustable stationary contacts. Brand New, Only \$1.95 each, 10 for \$17.50 (Shipping Weight, each, 1 lb.)

A SENSITIVE RELAY!

Closes at 4 to 5 ma. (Extra set of SP/ST contacts for additional sequence, close at 0.5 ma.) Coil 6000 ohms. Only 1 1/2" x 2 1/4" x 1 3/4" overall. Dozens of applications and offered at a "stock up" price. Removed from clean equipment. **ONLY 98c each, 3 for \$2.75**

PRECISION CALIBRATING CRYSTAL

200 KC. Same as used in late model Collins Autotune Xmtrs. In FT-241-A holder 1 1/2" x 1 1/2" x 1 1/2" in size. Use in Pierce untuned oscillator circuits to get check points very close together all the way up the spectrum. **BRAND NEW \$2.95**

12 CHANNEL T-V TUNER

Complete front end, famous make "Silver Circle," furnished with original factory instructions, less tubes, dozens of uses: frequency converters, etc. The TV bargain of the year for builders, amateurs, students. These are factory selected for minor \$5.00 damage. **ONLY \$1.95 each, 3 for \$5.00** (Shipping Weight, each, 3 lbs.)

49c FOR AC AMPS

Read AC current to appliances, receivers, etc., for quick check, servicing by connecting this gadget externally to your AC voltmeter, 0-100 AC amps, or use two for 0-20. Postpaid, with instructions. **49c**

MINIATURE 6 VOLT WET BATTERY

Just arrived! The famous NT-6 2.4 Ah 6 V battery. A standard for model control, etc. Plastic case, only 3 1/2" long, 1-13/16" wide, 2 1/2" high. Uses standard electrolyte. **ONLY \$2.49** or 4 for **\$6.50** (Shipping wt. 1 lb.)

BROADCAST BAND & AERO

MN-26-C Remote Controlled navigational direction finder and communications receiver. Manual DF in any one of three freq. bands, 150 to 1500 KC, 24 V. Self-contained dynamotor supply. Complete installation, including receiver, control box, loop, azimuth control, Left-Right Indicator, plugs, loop transmission line, and flex shaft. **BRAND NEW, ORIG. PACK \$69.50** (Shipping Wt. 75 lbs. Express Collect.)

HI-FI HEADSET

Uses annular grooved plastic fibre cones with voice coils as in speakers, and padded chamfer ear muffs to obtain spacing for correct acoustical load. Gives finest music reproduction, flat far beyond upper and lower limits of auditory perception. Pair in series has measured impedance of 600 ohms at 1000 cycles, obtained with built-in high quality transformers. Checked out with freshly laundered ear pads. **\$7.95** (Shipping weight, 3 lbs.)

6 V VIBRATOR KIT. Vibrator, plus non-avne transformer, two resistors, 700 μ F, 50 ma for plates; 15 V for bias. Can deliver 320 V at 130 ma. (Shipping wt. 6 lbs.) **NEW \$2.89**

EASY MONEY!

We're still buying surplus gear. Tell us what you've got, its condition, and your price. If we like it you'll get our check quick.

GET INTO ELECTRONICS



You can enter this uncrowded, interesting field. Defense expansion, new developments demand trained specialists. Study all phases radio & electronics theory and practice: TV; FM; broadcasting; servicing; aviation, marine, police radio. 18-month course. Graduates in demand by major companies. U.S. or equivalent required. Begin Jan. March, June, Sept. Campus life. Write for catalog.

VALPARAISO TECHNICAL INSTITUTE
Dept. RD Valparaiso, Indiana

NOW!

**TEST SERVICE
12v. AUTO RADIOS**



**New DC Power Supply
Model C-12**

0-16 Volts from 0-8
Amperes Continuous Output. Up
to 12 Amperes Intermittently



"For Both 12V. and 6V."

Only 3% Ripple at full load!

Completely variable output, makes it possible to test equipment under any voltage input condition. Provides filtered adjustable DC voltage for testing and servicing 12 volt and 6 volt auto radios from AC lines. Operates electronic equipment used on trucks, tanks and other mobile units; low voltage devices. Utilizes Superior Powerstat Voltage Control (Model 10) for extremely fine voltage adjustments.

See Your Nearest Parts Jobber!

Write for FREE BULLETIN!

- MODEL BJ 6 Volts, 1-12.5 Amps. 5% Ripple
- MODEL B 6 Volts, 1-20 Amps. 3% Ripple
- MODEL N 0-28 Volts, 1-15 Amps. 8% Ripple
- MODEL NF 0-28 Volts, 1-15 Amps. 1% Ripple

ELECTRO PRODUCTS LABORATORIES

4501-Nc No. Ravenswood Ave., Chicago 40, Ill.
CANADA: Atlas Radio Corp., Ltd., Toronto, Ont.

this amplifier is $\pm 1/4$ db from 20 to 70,000 cps with distortion less than one-half of one per-cent. This method of coupling is so efficient that only 20 watts is required to drive each one of the five banks of four speakers to the maximum output. The output of each bank of speakers was phased and connected to a separate amplifier, inputs of which were phased and terminated together and fed at a zero level by a Western Electric 22-E, four-position remote amplifier.

Microphones used on the stage for the pick-up were the Stephens C-1 condenser and American DR330 "Cardioid." The results obtained were most gratifying and tape recordings made during the musical extravaganza were equal to those obtained from any fine acoustically-treated sound stage. An engineer, located between the grandstand and the stage, mixed the sound for the musical production.

Open time is allocated by local Los Angeles radio stations to broadcast various types of radio programs direct from the Fair grounds. As these programs are planned they are channeled into the radio and television program office headed by Mr. Lisle Sheldon, who checks the available time and assigns it to the proposed program. Upon confirmation of the program, an announcer is assigned from this same office and a broadcast time notification is sent down to the master control room to allow the assignment of an engineer and equipment to handle the pick-up.

The radio control center is the heart of all radio and tape recording activities. It is located in front of the Radio-Television Building and enclosed behind plate-glass windows, which allow Fair patrons to witness engineering operations. A studio is built on each side of the control room for the broadcasting of news, interviews, and disc-jockey shows. These studios are individually equipped with their own remote amplifiers and microphones and terminate at the master control patch bay. The master control room is equipped with an RCA type 76B console, two custom-built turntables, and four "Concertone" tape recorders. Since a great many of the programs broadcast are recorded and released by tape, two "Concertone" network recorders are mounted on each side of the control desk for convenient operation by the engineer.

Outlying remote points of origin, such as the race track, the main auditorium, the Agriculture Building, Mexican Village, etc., are connected to the master control room by telephone lines and terminated on a patch bay. This allows instant, finger-tip control for the engineer to select incoming programs to be sent direct by special broadcast lines to Los Angeles radio stations or channeled through to the tape recorders for recording and subsequent rebroadcasting.

With finger-tip control, it is possible for the engineer to have five

**AUTUMN SALE
PRICES SLASHED**

T.V. TUBES—ROCK BOTTOM PRICES

In lots of 6 each No. only
6B6G .89c 6C86 .39c 6A05 .38c 6T8 .59c
198G6 .89c 6AK5 .69c 6C6E .51c 1L4 .45c
12AX7 .47c 6BQ6 .57c 6S4 .49c 1T4 .45c

Tube Special—Broken Keys—Electrically Perfect
12A6 .29c; 4 for \$1.00 12K8 .49c; 7 for \$3.00
Tube Sale—2A7-55-27-85-31-56. No Mixed Ass't
of any Type \$2.25

Heavy Duty Shielded P.P. Input Trans. \$1.00
H.D. Silver Contact Trans. Keys 1.00

Bat Handle S.P.S.T. or D.P.S.T. Toggle Switch. 25c
Isolantite Octal Panel Clamp Sockets. 3c ea.

100 Assorted Resistors \$1.95
1 Mid. 1,000V Oil Filled Cond.75c

2 Gang Var. Cond. 456 K.C. with Osc. Section
2 3/4 in. Pulley on 3/4" Shaft 49c

Westinghouse Kuprox Rectifier 0.64 Amd. 2P
Volts. Reg. 511.00 ea. Special \$1.95

BRAND NEW 10" PHONO RECORDS—Ass't
Jazz—Popular, Rhythm—Blues, Record sheetfy.
12 for \$1.75 or 24 for \$3.00 or 50 for \$5.75

Single Pole—10 Pos. 2 Gang Switch. 29c
Grind your own Crystals. Pure Brazilian Quartz. Vari-
ous sizes and thicknesses. 3/4 lb. Pk. \$1.00

4 Tube Drilled Chassis. 4 1/2"x6 1/2"x1 1/2". 29c each
Signal Corps Phones—2 M. Ohms (8 M. Ohms
Imp.) \$1.25

2 Ft. Ext. Cord (and Plug) 40c
2 3/4"x4" Bake. Panel Mounting—5 Res.; 6 Mica Cond.;
2 Choke Coils. 49c

2 1/2" M.H. R.F. Choke Coil 27c ea.; 4 for \$1.00

TOBE TUBULAR ELECTROLYTICS
20-20 MFD. 150 V. 49c 30-30 MFD. 150 V. 57c
10-40 MFD. 150 V. 59c

Low-Loss Short Wave
Lock Type Air Trimmer
Variable Condensers

5 Pl.—20 Mmfd. 16c
7 Pl.—25-30 Mmfd. 18c
8 Pl.—30-35 Mmfd. 20c
14 Pl.—56 Mmfd. 28c

3 GANG T.R.F.
VARIABLE CON-
DENSERS
D E N S E R S
0000365 Con. 65c

D.P.D.T. SLIDE
TOGGLE
SWITCH 15c

1,000 OHM WIRE WOUND POTENTIOMETER 15c
30 HY-FILTER CHOKE SHIELDED. 3 for \$1.25

PIEZO CRYSTAL HOLDERS. 12 for \$1.00—\$6.00 per C

RCA Band Switches—
3 gang, 3 pos. 3 band. 30c 6 gang, 4 pos. 4-5 band. 40c
Trimmer-Pads—Ass't.—all isolantite—singles, dual
triples—100 each. \$2.25

ATTENTION: Prospectors, Explorers or Hidden Treasures!
Construct a U.S. Army Type of Metallic Mine Detector
Amplifier unit only (less tubes and bat-
teries) with cables, headphone cord and fact. Army
wiring diagram. Type AN/PRS-1 \$1.95

Philco push button Rotary Switch Double Pole. 35c
8 or 9 Gang Push button Switch 49c

DRILLED CHASSIS FOR 5-6 tubes 5"x10"x1 1/2". 25c
PHONE JACKS—OPEN & CLOSED AUTO. 18c
156-1 RATIO VERNIER DIALS—1 in. Dia. Hub. 35c

SALE—PHONO RECORD ALBUMS—12" comp.—15c;
10"—3 comp.—15c; 4 comp.—20c; 12 comp.—50c


VULCAN HEAVY DUTY 100 WATT SOLDERING IRON.
Built for U.S.N.—Brand New—Equip. sets for
\$8.50. OUR PRICE \$3.25

MINIMUM ORDER \$3.00—NO C.O.D.
SHIPMENTS—PLEASE INCLUDE POSTAGE

NEWARK SURPLUS MATERIALS CO.
324 Plone Street, Dept. SE, NEWARK 1, N. J.

HI-GAIN TUNER-BOOSTER

LESS TUBES WITH DIAL

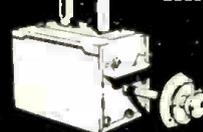

\$4.75

COMPLETE WITH TUBES

\$6.00

Solve poor T.V. reception with a Hi-Gain
Booster. Banish weak fringe areas, reduce
snow. This unit comes to you as a highly
serviceable High-Gain Tuner. Uses 6J6
Tubes in very efficient Hi-Q Circuit. Has
8 tuned circuits using pure silver induct-
ances and individual compensation provid-
ing high gain on all channels. Built in 5:1
Vernier Drive. This is a complete departure
from ordinary tuners.

All necessary parts and instructions are
included to convert this unit in a few min-
utes to one of the highest gain boosters on
the market regardless of price.

100 ASSORTED RESISTORS

Carbon insulated. New in
current RMA Values 5%,
10% and 20% in 1/2, 1 and
2 watt **\$1.00**

Shipments sent postpaid when full payment is en-
closed with order. 25% deposit on C.O.D. ship-
ments. Open account privileges to rated firms.
Send for our new bulletin listing many T.V. Com-
ponents at terrific price reductions.



11842 WEST JEFFERSON BOULEVARD
CULVER CITY, CALIFORNIA

programs in operation at the same time, namely: Studios A and B located in the control room feeding programs to Los Angeles over direct telephone lines; tape recording the daily races originating at the grandstand; tape recording a program by telephone line from a remote point of origin, such as the Agriculture Building, for rebroadcasting at a later time; or releasing a previously tape-recorded program over a direct telephone line to Los Angeles. Programs may also be channeled direct through the master control patch bay.

Tape recording plays a major part in the broadcasting activities at the Los Angeles County Fair as it affords flexibility in the recording and rebroadcasting of various radio programs. Field tape recording equipment, consisting of "Concertone" portable tape recorders, allows programs to be made at any location on the Fair grounds where broadcast lines are not readily available. When necessary, remote broadcasts originating from such locations as the Agriculture Building, Mexican Village, Floral Building, Sportsman's Area, and the Live Stock Judging Rings may be channeled directly through the master control room and handled by the engineer at the point of origin.

Since the Fair ground covers such a large area and activities are geared to such a fast pace, it is imperative that a rapid method of transportation be available at all times to carry an engineer and equipment to any part of the 400 acres in a matter of minutes. To accomplish this, special-built electric "Autoettes" are used.

Telephone order wires connected to the radio control center are located throughout the Fair grounds in thirteen locations, which allow immediate communication and the assignment of an engineer, if necessary, to originate a program in the field.

A completely-equipped control room is located on one side of the stage in the main auditorium allowing the origination of local and network radio programs. When programs emanate from the auditorium, they are bridge fed through the dual, high-fidelity public address installation for the benefit of the audience.

Broadcasting equipment includes a Western Electric 22-E, four-position mixer along with various types of microphones used for different stage presentations.

Through television, Fair activities were witnessed by thousands of Southern Californians.

Thus, electronics plays a very important part in the world's largest county fair by allowing patrons to hear the various Fair activities through sound reinforcement and by bringing many of its features into the homes of thousands of people through the medium of radio and television.

EDITOR'S NOTE: Interested audio readers in the area are urged to visit the installation at the forthcoming Fair in Pomona.

SOUND POWERED HEAD AND CHEST SET

Navy Type—No Batteries Required—Ideal for TV Antenna Installations and many other uses. 20 Ft. Cord. Used—Tested..... \$5.95 EA.



RE-64 FIELD TELEPHONE Used—Tested..... \$12.95

TELEPHONE WIRE FOR USE WITH EITHER OF ABOVE:

COBMBAT TYPE—2 Cond. Twisted, Rubber Covered, Medium Weight, W-130..... @ .01c per Ft.
FIELD WIRE—2 Cond. Twisted, Weather-proof, Heavy Duty, W-110—\$25 Ft. Roll..... \$4.75
COPPER WELD WIRE—Weatherproofed, 2 Cond. Solid, 1200 Ft. Roll, \$10.00, Per Ft. @ .01c per Ft.

COAXIAL CABLES:

RG-8/U (SPECIAL) 51.5 ohms. Same size as RG-8/U. Prices: 1 to 100 ft. @ 7c per ft.—100 to 500 ft. @ 7 1/2c per ft.—500 to 1000 ft. @ 7c per ft.—1000 ft. Rolls @ 6 1/2c per ft.
RG-34/U 71 ohms, 145 ft. length..... \$15.00

DYNAMOTORS:

INPUT:	OUTPUT:	STOCK No.:	PRICE:
110 V.D.C.	330 V. 135 MA.	DM-330	\$7.95
110 V.D.C.	250 V. 50 MA.	DM-25	8.95
110 or 24 V.D.C.	500 V. 50 MA.	USA/0515	4.95

PE-103 DYNAMOTOR

6 or 12 Volt input; output 500 Volts 160 MA. Complete with battery cables, circuit breakers, and filter base. Prices:..... NEW: \$39.95—USED: \$29.95
OUTPUT CABLE 1/PE-103—8 ft. CD-501..... \$2.95

PE-101C DYNAMOTOR

6 OR 12 VOLT (Reprints of original CO conversion articles—Oct. and Dec., 1952 issues furnished.)
This is the Dynamotor the Hams have been talking about! Easily adapted to supply 625 V. @ 150 MA. and 325 V. 125 MA. at 12 Volts—or 300 V. 100 MA. and 160 V. 110 MA. at 6 Volts. NEW \$4.95

BATTERY SWITCHING UNIT and METER

Used to switch load from one battery to another—or 6 to 12 Volts. Contains 2" Meter —3-15 Volt DC Scale for reading battery voltage. 20 Amp DPDT Switch and Indicator. Case size: 4" x 6 1/2" x 2 3/4"..... NEW: \$2.95

BLOWERS—115 VAC 60 CYCLE

SINGLE TYPE: (Illustrated at left) 100 CFM. 2 1/2" intake; 2" outlet. Complete size: 5" x 6". Order No. 1C939..... \$8.95
DUAL TYPE: 100 CFM. 4" Intake; 2" Dis. Each Side. Complete Size: 8" x 6". Order No. 1C880..... \$13.95
COMPACT TYPE: 108 CFM. Motor built inside squirrel cage. 4 1/2" intake; 3 1/2" x 3" Dis. Complete size: 4 1/2" W x 8 3/4" H x 8 3/4" D. Order No. 2C067..... \$14.50
FLANGE TYPE: 140 CFM. 3 1/2" Intake; 2 1/2" Dis. Complete size: 7 1/2" W x 7 1/2" H x 6 3/4" D. Order No. CB07..... \$13.95
FLANGE TWIN: 275 CFM. 4 1/2" Intake; 3 1/2" x 3" Dis. Complete size: 11 3/4" W x 8 3/4" H x 8-1/16" D. Order No. 2C069..... \$21.95

Address: Dept. RN • Minimum Order \$5.00 • Prices F.O.B., Lima, O. • 25% Deposit on C.O.D. Orders

FAIR RADIO SALES 132 SOUTH MAIN ST. LIMA, OHIO

SPEAKER RECONING

Complete line Cones, Spiders, Rings and Voice Coils. Custom Built Voice Coils. Low prices. Write for Parts List and Reconing information.

WESTERN ELECTRONICS CO.
3104 West Colfax Denver 4, Colo.

RCA INSTITUTES, INC.

A service of Radio Corporation of America
350 West 4th St., New York 14, N. Y.

OFFERS COURSES IN ALL TECHNICAL PHASES OF RADIO, TELEVISION, ELECTRONICS

Approved for Veterans
Write Dept. RN-53 for Catalog

COMMAND RECEIVERS & TRANSMITTERS

BC-454 REC.—3 to 6 MC. Used—Tested..... \$14.95
BC-455 REC.—6 to 9 MC. Used—Tested..... \$14.95
BC-456 MODULATOR—Used: \$3.95—New: \$6.95
BC-457 TRANS.—4 to 5.3 MC.—Used..... \$12.95
BC-458 TRANS.—5.3 to 7 MC.—Used..... \$12.95
PLUG—Male, 1/Rear Rec. or Trans. 75c



POGO-STICK

TRANS.—REC.—PORTABLE, READY TO OPERATE. BC-745 TRANS.—REC.: Crystal Controlled, covers Freq. 3 to 6 MC. by use of Plug-in Coil, with PE-157 Power Supply, BB-54 2 Volt Battery, Speaker, Antenna, Mic., and Crystal for 5030 KC. Set size: 5"x5"x6", mounted on Staff 30" Lg. Power Supply operates from 2 Volt Wet Battery rechargeable from 6 Volts and houses Speaker. Price: Used—\$49.95 Tested—Complete..... \$49.95
T-39 CHEST SET—Has Speaker & Space for Dry Cells..... \$4.95
BC-745 TRANS. & REC.—CHASSIS ONLY—No Cover, Staff or Antenna, but w/Trans.—NEW..... \$14.95
ANTENNA—Telescoping, for above set..... \$2.00

RECEIVER AND TRANSMITTER

RECEIVER BC-229 or 429—TRF Receiver with 3 Plug-in Coils to cover Freq. Range 201 to 398, 2500—4700, 4150—7700 KC. With 6 Tubes: 1/37—1/38—3/39. Power Supply required, 6 or 12 Volt & 256 Volts. Size: 16"x8"x7". Schematic included..... USED: \$8.95
TRANSMITTER BC-230—Voice modulated Trans. with 5 Plug-in Coils to cover Freq. Range 2500 to 7700 KC. With 4 Tubes: 2/10y—2/45 & RF Meter 0-1.5 Amps. Power Supply required, 6 or 12 Volt & 350 Volts. Size: 13"x8"x7". Schematic included..... USED: \$8.95

Special Buy—Both Rec. & Trans.: \$15.00
TRANS. CONTROL BOX BC-232 w/Plug..... \$1.50
REC. CONTROL BOX BC-231 w/Plug..... \$1.50
PLUG 1/Rec. PL-61..... 75c F/Trans. PL-64..... 75c

ANTENNA EQUIPMENT

MAST BASES—INSULATED:
MP-132 BASE—Illustrated at left—1" heavy coil spring, 2" insulator. Overall length: 11 1/2". Weight: 2 3/4 lbs. Price..... \$3.95
MP-S-33 BASE—Insulated type with heavy coil spring and 6 1/2" dia. insulator. Requires 2" hole for mounting. Weight: 9 lbs. Price..... \$5.95
MAST SECTIONS FOR ABOVE BASES
Tubular steel, copper coated, painted, in 3 ft. sections, screw-in type. MS-53 can be used to make any length with MS-52-51-30-49 for taper. Any section..... 50c Each
Larger Diameter Section: MS-54..... \$1.25

TRANSFORMERS—110 V. 60 CYCLE PRIMARIES: 5 Volt CT-25A—10.000 V. Ins. OPEN FRAME—6" x 5" x 4 1/2"..... \$7.95
6.3 V. 1 Amp..... 1.25 24 V. 1 Amp..... 1.95
24 V. 1/2 Amp..... 1.50 24 V. 6.5 Amp..... 5.95
6-24—or 30 Volt 8 Amp..... 5.95

BC-709 PORTABLE AMPLIFIER—One Tube uses 67 1/2 V. and 1.5 Volt Batt.—NEW..... \$4.95

STANDARD BRAND TUBES—Most Types Are Jans and FULLY GUARANTEED

1A7GT	.50	523	.40	6H6	.45	2A4	.65
1B3GT	.60	524	.40	6H7	.45	2A5	.65
1C5GT	.65	6A8	.50	6J6	.75	31	.75
1E7GT	.95	6A87	.75	6K6	.50	34	.95
1L4	.50	6A7	.65	6L6 G.	.65	38	.50
1L6	.40	6A76	.50	6A	.95	39 44	.50
1LH4	.80	6A75	.60	6SL7	.60	43	.45
1LN5	.40	6A77	.95	6SN7GT	.60	46	.60
1R5	.50	6A78	.65	6X4	.75	50	.75
1S5	.50	6A15	.45	6V6GT	.45	50B5	.60
1T4	.45	6A76	.42	6W4GT	.55	59	.75
2A3	.65	6A78	.65	6X5GT	.45	12SL7GT	.85
3A4	.60	6A76	.45	6Y6G	.60		
3A5	.75	6B40	.75	All Loktal			
3B7	.40	6B6GG	1.70	Type Tubes			
3D6	.40	6B76	.60	at 70% off			
3Q4	.50	6C4	.50	12AT7	.85	Most Type	
354	.50	6C66	.60	12AU7	.60	Tubes. Our	
5U4G	.50	6F6	.60	22	.75	Price 70%	

Write for other types not listed. Special Purpose Trans mitting types Crystal Diodes. Minimum order \$5.00 F.O.B. N.Y.C. 25% deposit with order will facilitate delivery

ALLIED ELECTRONIC SALES, Dept. G
74 Cortland St., New York 7, N. Y. Barclay 7-5839, 5840

4 for 53 NEW Trav-Electric CONVERTERS

CHANGE 6 OR 12 VOLT D.C. TO
110 VOLT A.C. 60 CYCLE
Just plug into Cigar Lighter on Dash.



**Trav-Electric
Super**
Model 6-71160
60 cycle
60-75 Watts
\$37⁹⁵
LIST

Size
4" x 5" x 6"

Operates

- Wire Recorders
- Dictating Machines
- Amplifiers
- Turntables
- Soldering Iron
- Small Electric Drill



**Trav-Electric
Master**
Model 6-51160
60 cycle
40-50 Watts
\$24⁹⁵
LIST

Size
4" x 5" x 6"

Operates

- Curling Irons
- Small Dictating Machines
- Radios
- Test Equipment, etc.
- Turntables
- Portable Phonographs



**Trav-Electric
Senior**
Model 6-11160
60 cycle
35-40 Watts
\$15⁹⁵
LIST

Size 2 1/2" x 2 1/2" x 4 1/2"

Operates

- Test Equipment
- Short, Long Wave Radios
- Turntables
- Portable Phonographs
- Lights
- Electric Shavers, etc.



**Trav-Electric
Midget**
Model 6-11160
60 cycle
10-15 Watts
\$11⁹⁵
LIST

Size 2" x 2" x 3 1/2"

Operates Test Equipment, All Electric Shavers

Fully Guaranteed

See Your Jobber or Dealer

TERADO COMPANY
MFRS. OF PRECISION EQUIPMENT

1068 RAYMOND AVE. • ST. PAUL 14, MINN.

In Canada write: Atlas Radio Corp., Ltd.

560 King St. West, Toronto 28, Ont.

Export Sales Division: Scheel International, Inc.,

4237 N. Lincoln Ave., Chicago 18, Ill., U. S. A.

Cable Address—Harscheel

NEW TV PRODUCTS on the Market.....

U.H.F. TUNER

Radio Receptor Co., Inc. of 251 West 19th St., New York 11, N. Y. has developed a new u.h.f. tuner circuit



which has been tradenamed the "Cavi-Tuner".

The new circuit has also been incorporated into a second unit which serves as a u.h.f. converter. The "Cavi-Tuner" is designed as an original equipment component to provide both v.h.f. and u.h.f. reception while the converter has been designed to be used as an accessory for existing v.h.f. receivers.

The "Cavi-Tuner" consists of three cavities—two functioning as a band-pass preselector while the third controls the local oscillator frequency. The preselector is essentially an over-coupled, double-tuned transformer. Two antenna inputs are available for use with 300 ohm twin-lead or shielded 75 ohm coax. Mixing takes place in a low-noise diode with an i.f. appearing at v.h.f. Channels 5-6. A single knob functions both as a channel selector and fine tuning control.

TRANSMISSION LINE

Rego Insulated Wire Co., Inc. of 830 Monroe Street, Hoboken, N. J. has introduced a new 300-ohm transmission line with #18 copper or Copper-weld.

Especially designed for u.h.f. and v.h.f. applications, this line has pure polystyrene spacers 4 1/2 inches apart. According to the company, the line performs well in both local and fringe areas and matches the input of all sets tested. No transformer is required.

"PACKAGE" TV STATION

General Electric Company of Syracuse, New York has announced a low-cost "package" television station, designed to expedite the advent of television in 1100 small cities (under 50,000) allotted channels by the FCC.

The new "package" station requires only a single technical operator to prepare and broadcast film and network programs. The "package" sta-

tion will be available for either v.h.f. or u.h.f. telecasting and in several different power ratings.

Complete details on this new transmitter "package" are available from the company's broadcast equipment division.

NEW TUBE FOR TV

Sylvania Electric Products Inc.'s Radio Tube Division has released a new tetrode beam power amplifier, the Type 6BQ6G.

The new tube has been designed for service as a horizontal deflection amplifier in television receiver sweep circuits. It is similar to the company's Type 6BQ6GT except for increased bulb size.

The new amplifier is contained in a ST-12 bulb, thus providing a greater safety margin for dissipation. As a horizontal deflection amplifier, a d.c. plate supply voltage of 600 volts and a peak positive plate voltage of 6000 volts are allowable.

TV SIGNAL GENERATOR

Radio City Products Co., Inc., 152 West 25th St., New York, N. Y. has developed a new u.h.f.-v.h.f. signal generator which has been designated as the company's Model 750.

Covering all u.h.f. and v.h.f. channels for TV and FM, the new unit contains test facilities for use as a pattern generator, marker generator, and signal generator. The instrument features an "Inductuner" which insures accuracy within 1/2 of 1% over the entire range of 9 mc. to 900 mc., according to the company.

All v.h.f. frequencies are on fundamentals. The horizontal-vertical bars and crosshatch pattern are individually produced on all channels.

NEW U.H.F. ANTENNAS

JFD Manufacturing Co., Inc., 6101 16th Ave., Brooklyn 4, N. Y. is in production on the Model UHF611 "Bow-tie-Flector" antenna. Featuring rigid wire-frame screen reflectors that minimize vibration, the new unit also carries the company's "Bronzidite" plating that prevents rust and corrosion of non-aluminum parts.

LaPointe Electronics Inc. of Rockville, Conn. has added the "Corner Reflector, Model COR-U." to its "Vec-D-X" line of u.h.f. antennas. Fiber-glas booms provide strength without weight and permit the use of small diameter solid aluminum rod to prevent icing. A compact, swing-open design requires less than 30 seconds for assembly.

Q-Line Manufacturing Corp., 1362 61st Street, Brooklyn 19, N. Y. is mar-

N.J.R.T. TUBES

LOWEST TUBE PRICES

Dependable N.J.R.T. Tubes for 70% to 90% off list

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
1A7GT	.45	6BA6	.41	12AT7	.54
1B3GT	.47	6BA7	.57	12AU6	.38
1H5GT	.38	6BC5	.42	12AU7	.41
1L4	.44	6BE6	.37	12AV7	.57
1L6	.41	6BG6G	.92	12AX4GT	.46
1LC5	.49	6BH6	.44	12AX7	.49
1LN5	.49	6BJ6	.41	12BA5	.36
1N5GT	.44	6BL7GT	.60	12BA7	.44
1R5	.43	6BQ6GT	.57	12BE6	.37
1S5	.37	6BQ7	.61	12BH7	.61
1T4	.43	6BZ7	.93	12SA7GT	.42
1U4	.43	6C4	.39	12SK7GT	.46
1U5	.37	6CB6	.42	12SN7GT	.50
1X2	.52	6CD6G	1.09	12SQ7GT	.42
3A4	.43	6F6G	.37	12SR7MET	.47
3Q4	.46	6F6GT	.35	19B6AG	.96
3O5GT	.47	6J6	.50	19T8	.77
3S4	.44	6K6GT	.35	25BQ3GT	.60
3V4	.45	6L6G	.62	25L6GT	.37
5U4G	.45	6L6GA	.62	25W4GT	.45
5Y3GT	.30	6S4	.37	25Z6GT	.35
5Y4G	.33	6S8GT	.51	35A5	.50
5Z3	.37	6SA7GT	.41	35B5	.38
6A3	.57	6SD7GT	.39	35C5	.37
6AR4	.42	6SK7GT	.39	35W4	.35
6AG5	.41	6SL7GT	.46	35Z5GT	.35
6AF4	1.06	6SN7GT	.50	.42	.40
6AJ5	.48	6SQ7GT	.35	.43	.53
6AK5	.73	6T8	.54	.45	.53
6AL5	.36	6U8	.59	5C85	.37
6AO5	.37	6V8GT	.37	5CC5	.37
6AO6	.35	6W4GT	.42	5CL6GT	.39
6AT6	.35	6W6GT	.45	70L7GT	1.07
6AU6	.36	6X4	.35	.76	.42
6AV6	.35	6X5GT	.35	117Z3	.35
6AX4GT	.57	12AT6	.35	807	.97

MANY 7 VOLT TYPES NOT LISTED

ALL TUBES BOXED AND FULLY GUARANTEED.
MINIMUM ORDER \$10.00.
TUBES OFFERED SUBJECT TO PRIOR SALE.
PRICES SUBJECT TO CHANGE.
ORDERS SHIPPED PREPAID IF CHECK IS ENCLOSED.
25% DEPOSIT REQUIRED ON C.O.D. SHIPMENTS.

NEW JERSEY TELEVISION SUPPLY CO.
906 Westfield Ave. Elizabeth, N. J.
Phone Elizabeth 3-6166

MOVING?

Please allow at least 60 days for address change. Notify **RADIO & TELEVISION NEWS** Circulation Department at 64 E. Lake St., Chicago 1, Ill.

100 ASSORTED 1/2 WATT RESISTORS

100 Assorted, American made, insulated resistors, packaged in a beautiful clear polyethylene bag.

All resistors bear our 100% guarantee.

Price ea. **\$1.99**

Capitol Commodities Co.

1229 W. Washington Blvd., Chicago 7, Ill. TA-9-7393

ON THE SPOT BATTERY RECORDER

WALKIE-RECORDALL. 8 lb. miniature BATTERY RECORDER-PLAYBACK. Continuous, permanent, accurate, indexed recording at only 1¢ per hr. Instantaneous, permanent playback. Picks up sound up to 60 ft. Records conferences, lectures, dictation, 2-way phone & sales talks; while walking, riding or flying. Records in closed briefcase with "golden mike"! Write for Detailed Literature.

MILES REPRODUCER CO., INC.
87 BROADWAY, Dep't RR-9, NEW YORK, N.Y.

keting a pre-assembled, vibration-proof u.h.f. corner reflector, the Model 150. The antenna features a unique three U-bolt mounting which eliminates vibration by anchoring the center and ends of the reflector to the mast. The company has literature available on this unit for those requesting it.

Radio Merchandise Sales, Inc., 2016 Bronxdale Ave., New York 60, N. Y. is currently introducing the "RMS Bo-Tenna", Model BT-10, a flexibly constructed bow tie and reflector antenna. The bow tie element and reflector section are standard fitted units, each of which is available separately. The reflector is comprised of tuned elements to help eliminate ghost pickup.

Television Hardware Mfg. Co., 919 Taylor Ave., Rockford, Ill. is offering a new series of antennas for u.h.f. The "Telco" units are available in both single- and two-bay styles.


Telrec, Inc. of Asbury Park, N. J. is now offering a "Duo-Band" array, an all-channel antenna which is said to provide high gain coverage of Channels 2 through 83 with one major in-line lobe, constant center impedance, and high signal-to-noise ratio. The Model 420 requires a single transmission line and needs no lossy filter or isolation networks. Stacked arrays, Model 440, are also available.

SELENIUM RECTIFIERS

International Rectifier Corporation, 1521 E. Grand Ave., El Segundo, California has developed a complete line of selenium rectifiers for use in television, radio, TV boosters, and u.h.f. converters.

Units are rated for 130 volts r.m.s. maximum input for load currents of 20, 30, 40, 50, 65, 75, 100, 150, 200, 250, 300, 350, 450, and 1000 ma.

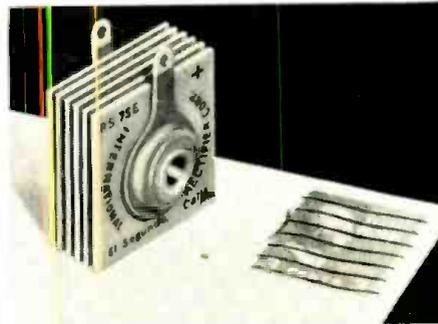The rectifier illustrated is the Type RS75E rated at 130 volts maximum; 380 volts maximum peak inverse; 75 ma. maximum output current. A series resistor of at least 22 ohms is recommended as a current limiter when



used with a capacitive filter. Over-all dimensions of this unit are 1" wide by 1 1/4" high by 3/4" deep and provided with a clearance hole for a number 8 machine screw for mounting.

Complete information on the full line is available from the company.

CLOSED-CIRCUIT TV

Radio Corporation of America is currently introducing its "Private-

NEW!

NICHOLS NEVER-STAIN

Aluminum TV AND RADIO GROUND WIRE


RUST PROOF



- ★ High Electrical Conductivity
- ★ Inconspicuous — Low Reflectivity
- ★ Pliable — Specially Tempered
- ★ Etched finish — clean
- ★ STD. No. 8 B & S Ga. (.128" dia.)

Aluminum TV ANTENNA GUY CABLE

RUST PROOF

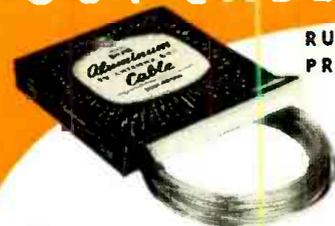

- ★ Seven — 18 Ga. Stranded Wires
- ★ Flexible — Specially Tempered
- ★ High Strength Aluminum Alloy for all Types of Antennas.
- ★ Approx. break strength — 500 lbs.



*Packed 2-500 ft. continuous coils per carton marked every 100 ft. with bright red tape.



PACKAGING DATA

ITEM	PKG. NO.	DESCRIPTION
TV Grd. Wire	8	100 ft. coil per box, 10 boxes per ctn.
TV Grd. Wire	9*	2-500 ft. continuous coils.
TV Cable	50	100 ft. coil per box, 10 boxes per ctn.
TV Cable	60*	2-500 ft. continuous coils.

Order from your jobber or write us direct. Address Dept. TVN-3

NICHOLS WIRE & ALUMINUM CO.
DAVENPORT, IOWA
World's Largest Manufacturer of Aluminum Rolls

"In music, listening quality is everything . . .

1 It is the No. 1 MUST. Without it everything else becomes meaningless. The AUDAX CHROMATIC has that quality to a degree not equalled by any other pickup" . . . so says violinist David Sarser, of *MUSICIAN'S* amplifier fame (Toscanini's NBC Symphony).

2 Every stylus has a limited life-span, be it diamond or sapphire; the diamond lasting the longer. Obviously then, replaceability of the stylus—at home—is of the greatest importance. ONLY AUDAX PROVIDES REPLACEABILITY—AT HOME—OF EITHER STYLUS, INDEPENDENTLY OF THE OTHER.

★ ★ ★ ★ ★

Now YOU can tell
WHEN to change
STYLUS



A microscope will show a tiny flat on any diamond after 40 or so hours of play—yet, the jewel is in good playing condition. Hence, in diagnosing wear, it is not the flat but detection of actual cutting edges that is of vital importance. This makes a microscope—(\$15.00 to over \$100.00)—almost useless to an untrained observer. He can see, but he can't judge. The Audax Company has developed the STYLUS-DISK which makes home-testing of any jewel point very simple. If worn or defective the stylus will scrape the delicate surface of the STYLUS-DISK, leaving a visible indication. With proper care, this new STYLUS-DISK should have a life-span of at least 20 styli. Yet it costs only \$6.50 list, \$3.90 net.

If your favorite store hasn't yet received a shipment of STYLUS-DISKS, write to us.

AUDAX COMPANY

500 Fifth Avenue New York 36


Fine Audio-Electronic apparatus for over 25 years

"The Standard by Which Others Are Judged and Valued"

Line" camera chain which has been designed for schools, hospitals, prisons, stores, small factories, and even homes.

Featuring low price, small size, and simplified operation, this newest and most compact closed-circuit television system yet offered by the company has been tradenamed "TV-Eye".

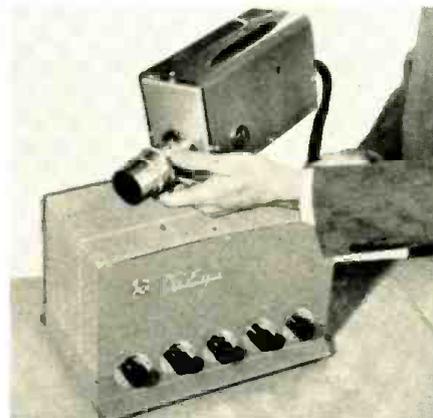The unit is designed to utilize any standard home-type receiver as a monitor and can be tuned to an other-



wise unused channel without interfering with reception on other channels. The complete unit, including the camera and control box, weighs less than 20 pounds.

RESISTOR OUTLET

A new, simplified resistor outlet box has been developed by *Blonder-Tongue Laboratories*, 526-536 North Avenue, Westfield, N. J., for providing isolated TV outlets in all types of master TV systems.

The new unit, Model RO1, will tap off from RG/11U or 59U with only ½ db insertion loss. Signal attenuation of 17 db at the TV outlet terminal prevents interaction among sets in the system.

The detachable face plate contains all cable connections and will fit any standard outlet box. Screw terminals provide a 75 or 300 ohm outlet to the set. Center conductors are attached to inner screw terminals and coax shields are grounded by the clamp.

TV FUSE KIT

Littelfuse, Inc., 1865 Miner Street, Des Plaines, Illinois has brought its popular "One Call Kit" up-to-date to meet the requirements of television service technicians and set manufacturers.

The revised kit represents the latest usages of fuses as indicated by set makers and technicians. It is estimated that service technicians can handle 95 per-cent of their fuse replacement requirements from this single unit.

TELEVISION CONDENSERS

Sangamo Electric Company of Marion, Illinois has developed a new molded paper tubular condenser especially for television applications.

By using "Humiditite", a new molding compound with unusually high

moisture resistance characteristics, the new molded tubular will meet the minimum moisture resistance requirements of MIL-C-91A (proposed), while the new impregnant holds the condenser to rated capacity under all conditions and provides additional strength.

An engineering data sheet TEL and further information on the new "Telechief" condensers is available from the company.

OPEN LEAD

Imperial Radar and Wire Corp., New York 66, N. Y. has developed an open lead with a nominal impedance of 250-275 ohms with either 4½ or 6 inch spacing.

The new transmission line can be used with 300-ohm equipment without concern for mismatch. The narrower spacing for 250-275 ohms is said to be more desirable at the u.h.f. frequencies. Its low-loss characteristics, .35 db dry line loss in 100 feet at 500 mc., make it adaptable for both u.h.f. and v.h.f. installations.

The product is being handled through distributors in 100 and 250 foot spools.

U.H.F. "AUTOBOOSTER"

Industrial Television Inc., 359 Lexington Ave., Clifton, New Jersey is marketing a new booster for u.h.f., the IT-124A "AutoBooster".

Factory pretuned for a single u.h.f. channel, the booster is a two-stage high-gain, low-noise amplifier which utilizes the 6AJ4 grounded-grid triode in a unique design.

Automatic operation is retained by the use of a magnetic relay. In multiple u.h.f. areas combined operation of several of these units may be used by means of switching or combining networks.

V.H.F. TV BOOSTER

Electro-Voice, Inc. of Buchanan, Michigan is in production on an improved Model 3002-A, three-tube "Tune-O-Matic" all-channel v.h.f. television booster.

The new multi-power low noise circuit has three tubes in broadband balanced stages, including a power multiplier stage. It provides extra



gain with minimum internal noise and higher signal-to-noise ratio, according to the company. The unit can also be used at the output of a u.h.f. converter to increase signal strength of the first i.f.

The 3002-A is automatically self-

tuned to all v.h.f. channels. No separate tuning of the booster is required. It turns "on" or "off" with the television receiver switch. Input and output is to 300-ohm twin-lead.

Bulletin 182 covering this unit is available from the company on request.

TV COUPLER

The Tube Department of Radio Corporation of America, Harrison, N. J. has announced the development of an inexpensive coupler unit which makes possible the quick installation of a secondary receiver.

The TV-set coupler, RCA-240A1, can also be used in combinations of two,



three, and four units for the operation of as many receivers from a single antenna.

Designed for use with antennas having 300-ohm, ribbon-type transmission line, the coupler is a quick-service item. It requires only a screwdriver and a few minutes' time for installation and features a self-contained woodscrew which facilitates mounting on wall or baseboard.

The company's tube distributors are handling this item.

"FILTER TESTER"

Vidaire Electronics Mfg. Co. of Lynbrook, N. Y. has introduced an unusual piece of test gear, the "Fil-Test".

This new wave trap meter permits the technician to determine which type of filter and/or wave trap to install. The unit covers the entire i.f. and r.f. range of TV and employs a unique switching arrangement. Any interfering signal reaching the set through either the a.c. supply line or the antenna may be located by switching in the correct filter number on the "Fil-Test". In each instance the indicator shows which filter or wave trap to install.

"CUSTOM-BUILT" TV

A new custom-built 630-type television chassis designed for 27" and 30" picture tubes as well as the new 24" rectangular tube has been announced by Tech-Master Products Co., 443 Broadway, New York 31, New York.

Known as the Model 2430-9, the new unit features the latest type high-voltage and sweep circuits, 22 kv. second anode voltage, polyethylene enclosed high-voltage socket, new and

September, 1953

MEET *Telechief!*

SANGAMO'S NEW PREMIUM TUBULAR CAPACITOR — designed to give

better TV performance!



EXTRA VALUE
at NO EXTRA COST!

Sangamo combines an amazing new molding compound with a new impregnant to bring you a completely new paper tubular capacitor — developed by request to meet rigid specifications so tough that no previously existing paper tubular could approach them.

Thousands of Telechiefs have been tested under actual service conditions... have proved their ability to outlast and outperform all other tubulars.


The new molding compound, Sangamo Humiditite, greatly

lengthens capacitor life. It has been proved, by severe tests, to give the best seal against moisture of any molding compound in the industry.

The new Sangamo impregnant holds rated capacity under all conditions and makes the Telechief really rugged.

Because we know that service men want only the best replacement parts—the new Telechief has been released to the service trade. Get in touch with your Jobber.

Those who know... choose Sangamo

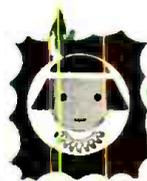

SANGAMO ELECTRIC CO. MARION ILLINOIS

.....
SAVE MONEY! SAVE SERVICE CALLS!
CHECK ALL TV, RADIO & PICTURE TUBES
 with this VISULITE TV TUBE CHECKER
 NO TECHNICAL KNOWLEDGE REQUIRED
 Simple Instructions Furnished
SAFE—QUICK—FOOLPROOF
 Most Radio set failures are due to burned out tubes. Just plug tube into socket provided and Neon Lamp indicates this condition instantly. Operates on 110 Volt AC or DC. PERFORMS 1001 ELECTRICAL CHECKS. Checks continuity of resistors, appliances, motors or any Electrical device. Sturdily built for long life of trouble shooting. Test Leads included. —Nothing else to buy.
SOLD ON 10-DAY MONEY-BACK GUARANTEE. See it at your distributor today. If he can't supply, order direct from factory. \$3.95 Postpaid anywhere in the U.S.
 Only \$3.95
 Complete
 Dept. RN-9 423 Broome St., N. Y. 13, N. Y.
 VISULITE CO.



110V. AC POWER SUPPLY FOR ANY 274-N RECEIVER

Just plug it into the rear of your 274-N RECEIVER... any model Complete kit and black metal case, with ALL parts and diagrams. Simple and easy to build in a jiffy. Delivers 24 volts plus B voltage. No wiring changes to be made. Designed especially for the 274-N receiver. Only \$8.95. Filament trans. for 274N receivers. Pri. 110V. 110 cy. AC. Sec. 2-1V @ .6A. An excellent buy at \$1.95 ea

SPLINED TUNING KNOB FOR 274N RECEIVERS



An exclusive O-K item manufactured for us. Fits BC-453, BC-454 and other 274N receivers. This is a really hard-to-obtain item. Only .89c ea.

OFFENBACH-REIMUS
1564 Market Street, San Francisco, Calif.

**CRYSTALS!
LOWEST PRICES!**

ONLY 79¢ EA. **ACT NOW**

In PT 241-A Holders—1/4 in. Pin SPC. These are designated 54th Harmonic MC freq. Listed by fundamental freq. with fractions omitted.

370	392	414	437	494	477	505
372	394	416	438	496	479	507
374	396	418	440	498	481	509
375	398	420	442	461	483	511
377	400	422	444	462	485	512
379	401	424	446	464	487	514
381	403	425	448	466	488	516
383	405	427	450	468	490	518
385	407	429	451	470	492	520
387	409	431	453	472	494	522
388	410	432	454	473	495	523
390	412	435	457	475	503	525

5 CRYSTALS \$2.00 for \$8.50 Assorted ONLY \$2.75
10 for \$4.50 for \$18.50

COMPLETE SET:—RD crystals covering above basic freq. including a 500 Kc. crystal. Lowest Price in United States! Write in for terrific buy!

SPECIAL 500 Kc. Crystal \$1.25
1000 Kc. Crystal 2.25
5000 Kc. Crystal 3.25

All above crystals sent postpaid in U. S. only. Also available in complete sets for SCIT-608, SCIT-528, SCR-628, and TRC. Foreign, wholesale, and dealer inquiries invited. Write for LARGE QUANTITY DISCOUNTS.

SUPREME MODEL 600
Illuminated TUBE & SET TESTER

Tests all latest tubes. Seven in. multi-tester tests DC 0-2,500 V. in 7 ranges; AC 0-2,500 V. in 6 ranges; DC current ranges: 0-1,000 microamps, 0-1,000 ma., and 0-10 amps. Ohmmeter 5 ranges: 0-20 megohms. Output meter and battery tester which tests auto batteries under load. Comes with test leads and Gray metal Hammerloid case. Size: 11x15x6 1/2 in. Factory guarantee includes 1 year of free time setting service. **BRAND NEW IN ORIGINAL BOXES.** You know this set is destined to net for \$117.50. While they last, our price—the country's lowest, only. **\$69.95**

METERS Guaranteed

2" Rd. Weston 0-25 MA \$2.95
 2" Rd. Westinghouse 0-1 MA with multimeter scale 4.95
 2" Rd. Westinghouse 0-9 amp. R.F. 2.95
 3" Rd. Roller-Smith 0-15 VAC 2.95

CONDENSERS New Guaranteed

10 mfd. 600 VDC Oil Filled \$2.79
 2x8 mfd. Tolu. Ester-misc. 1.95
BATHTUB CONDENSER ASSORTMENT 10 for 2.29

GLOBAR 600 ohm 100 W. Non-inductive resist. 50.98
2-METER WHIP ANTENNA. With coax plug in base 1.19
AUTO SYN MOTORS, 0-24 VAC 60 cyc. FH for Antenna Indicators, Per Pair 8.95
MINIATURE 8 V. WET CELL BATTERY. With 6 V. reversible DC motor. Ideal for R/C boat. New size: 3 1/2x2 1/2x1 1/2 in. Weight dry: 1 1/4 lbs.
 Battery less motor 1.49
 Battery plus motor 2.99

TUBES New Bored 803 \$3.49
2AP1 \$7.95 807 1.25

AIRCRAFT, HAMS & MARINE MEN!
SCR-183 12 V. RECEIVER & TRANSMITTER! Covers aircraft, marine and ham bands! Complete with 2 coils, control boxes, tuning head, flex cable, rack and shock mount! Plus 12 V. Dynamotor! Individual parts worth \$25.35. Approx. 2-w. output. **EXCEL. COND., COMPLETE! Never before sold at this sensationally low price. \$15.95**

ARC-5 OR 274-N TRANSMITTERS

2-1/3 mcs. Brand new	\$19.95
3-1/4 mcs. With tubes	25.00
4-5/8 mcs. With tubes	8.95
5-3/7 mcs. With tubes	6.95
7-0-1 With tubes	14.50

ARC-5 OR 274-N RECEIVERS

Equipped with tuning knobs	\$19.95
10-55 kc.	24.50
1-5/8 mcs. Brand new	22.50
3-6 mcs. Brand new	10.95
3-6 mcs. With tubes	7.95
0-9-1 mcs. With tubes. Used	22.50
New	6.50
6-9-1 mcs. Used. Less tubes	3.95
BC-456 274-N Modulator. Less dynamotor. Excel. cond.	12.95
12 V. COMMAND RECEIVER DYNAMOTOR. New	12.95

Plus All Accessories Needed for Above.

SHY? Are you shy of ready cash? Get dough NOW by selling yer new and used radio gear. Write yer own ticket—but write US!

Write Today—and ask for FREE CATALOGUE!
 All orders F.O.B. Los Angeles. 25¢ deposit required. All items subject to prior sale.

COLUMBIA ELECTRONIC SALES
 522 South San Pedro St. Los Angeles 13, Calif.

TRAIN FOR A SUPERVISORY POSITION IN ELECTRONICS

Thorough 2-year course covers electrical circuits and machinery, basic electronics and industrial electronics. Franklin Technical Institute graduates are in demand as junior engineers for research and test work, sales engineering, supervisory work on production lines and drafting room design work. Other engineering and technical courses. Coed. Day, evening, 45th year. Write for catalog.

FRANKLIN TECHNICAL INSTITUTE
 46 Berkeley Street Boston 16, Mass.

exclusive quick retrace autotransformer, full horizontal and vertical sweep even under low-voltage line conditions, variable vertical linearity and height controls, edge-to-edge focus, and the latest 90 degree ferrite cosine yoke.

The chassis comes completely wired, aligned, and factory tested with all tubes except the picture tube.

"SOLID" TV LINE

All channel reception in both u.h.f. and v.h.f. bands, irrespective of weather, is being offered by means of a new form of low-loss insulation—Foamed Polyethylene—by *Anaconda Wire & Cable Co.*, Hastings-on-Hudson, New York.

Known as ATV-270 FOAM, the new line is easy to terminate, all that is needed is a skilled hand and a pen-knife. Developed to solve the problem of internal moisture condensation, the new product provides one-piece insulation which virtually eliminates the problem and considerably improves the line's attenuation characteristics.

FIELD STRENGTH METER

Radion Corporation, 1130 W. Wisconsin Avenue, Chicago 14, Illinois is currently offering a new battery-operated field strength meter, the Model FSM-5000.

This compact unit features continuous one-knob tuning for Channels 2 to 83, direct, accurate reading in microvolts of either the video or audio portion, and extreme sensitivity ranging from 5 to 50,000 microvolts on v.h.f. and 50 to 100,000 microvolts on u.h.f.

The FSM-5000 is powered by standard "A" and "B" dry cell batteries and battery condition is shown at all



times on the dial. Microvolt readings are not affected by line voltage variations.

Full details on this unit are available from the company. Address your request to Dan O'Connell in care of the firm.

TEST SOCKET ADAPTER

Pomona Electronics Company, 524 West Fifth Avenue, Pomona, California is currently introducing its TVS-1 duo-decal test socket adapter to the trade.

The new unit is designed to permit operating tests, while the set is in

operation, on all circuits going in to the television tube socket. It is inserted between the CR tube base and its socket to complete the circuit



and make all connections readily accessible to meter test leads.

Measurements can be made without tracing circuit wiring to test points below the chassis, thus saving valuable service time by giving an immediate answer without removing the chassis from its cabinet.

For further information on the TVS-1 and a complete list of products made by the company, write to the firm direct or consult your local distributor.

TURNER'S U.H.F. CONVERTER

The Turner Company of 909 17th Street, Cedar Rapids, Iowa, is currently marketing a new u.h.f. television converter especially designed for low signal area installations.

The new unit features a two-section preselector with two silver-plated coaxial cavity tuners, a double-shielded fundamental oscillator, and a broadband amplifier with cascode circuit. According to the company, signal power loss in the preselector is reduced to 3 db. The noise figure is a maximum 17 1/2 db and a minimum of 15 1/2 db.

The converter has an illuminated slide-rule dial, continuous single-knob tuning from 470 to 890 mc. using Channels 5 or 6, and measures 8" x 6" x 6". It may be used with either a u.h.f. or combination antenna. It is self powered.

BROADBAND ANTENNAS

Two new broadband antennas, one for v.h.f. and the other for v.h.f.-u.h.f. reception, have been introduced by *Best Electronics Corporation* of 2254 Colby Avenue, Los Angeles 64, California.

According to the company, the new antennas have good directivity and a gain of up to 15 db over a standard reference dipole. A unique feature is the elimination of insulators at the lead-in terminals in all of the company's "Double-Diamond" models. In this way performance of the antennas is not affected by heavy rain, ice, fog, snow, or dust storms.

The v.h.f. design, Model 213, covers Channels 2 through 13. The second unit, for v.h.f.-u.h.f. reception, is available in three models. All are similar

in shape and performance characteristics to the v.h.f. design except that no crossarms are required. The Model 1440 covers Channels 14 through 40. Model 3570 provides high-gain reception of Channels 35 through 70, and Model 6083 covers Channels 60 to 83. Each model weighs slightly over one pound.

Details on any or all of these antennas are available from the company on request.

PROGRAM TIMER

International Register Company, 2620 West Washington Boulevard, Chicago 12, Illinois is currently offering a new electric timer which will follow the desired time schedule day after day without resetting.

Called the "Time-All", the timer is unique in that it does not have to be reset after each "on-off" cycle has been completed and can be used to control home appliances as well as radio and television programs.

TV REMOTE CONTROL

An inexpensive remote control unit for television that operates from a single connecting cable and can be installed in less than 15 minutes is now being offered by *Industrial Development Engineering Associates (I.D.E.A.)* of Indianapolis, Indiana.

The new "Regency" remote control performs four major functions: it selects stations, adjusts fine tuning, and controls contrast and volume. All of these operations are performed with the single cable connecting the TV set and the control unit. Tests show that the control will operate up to 150 feet from the set.

STAG HAMFEST

THE Greater Cincinnati Amateur Radio Assn. will sponsor its annual Stag Hamfest on Sunday, September 13th at Ash Grove on Winton Road, Cincinnati.

As is customary, refreshments, dinner, and supper will be included in the share-the-cost plan. The fee will be \$2.00 at the gate.

For additional details write W81VE or W40MW.

PHOTO CREDITS

Page	Credit
35, 36, 37, 110	Standard Coil Products Co.
38, 39	Gately Development Laboratory
52, 53, 54	Walter Ashe Radio Co.
56, 57	Phileo Corporation
60, 61, 62	Zentith Radio Corporation
64, 65	International Receiver Corp.
73	P. J. Samerlan
76	Service Instruments Company
144	General Electric Company
156	Hammarlund Manufacturing Co., Inc.
166	New York Audio Fair

ERRATUM

The radar unit shown on our July cover and described on page 35 was erroneously identified as the product of Electric Service Co. of Seattle. The unit was originally made by Raytheon and later modified by Electric Service Co. to operate on the 3 inc. commercial band.



Same Day Service!

TOP TUBE BUYS

70% to 90% off list!

All Tubes Individually Boxed! Check this list for Fully 1 Year Guaranteed Tubes Order Today

Another RAD-TEL Extra!
200 ASSORTED RESISTORS \$1.39
Carbon, Wire Wound, Carbon Film, Standard RMA Color Code or Value Printed. Uninsulated Type. 1/2 Watt, 1 Watt, 2 Watt and Some 10 Watt. Very Few Duplications or Odd Values!

Type	Price	Type	Price	Type	Price
1A5GT	.30	6B8J	.30	12BA6	.50
1A6G	.30	6B8K	.59	12BA7	.60
1A7GT	.47	6B8L	.39	12BD6	.45
1AB5	.30	6B8M	.39	12BE6	.39
1B3	.55	6B8P	.59	12BF6	.39
1B5	.30	6B8Q	.95	12BH7	.63
1B7GT	.30	6B8T	.95	12BQ7	.65
1C8GT	.43	6C4	.37	12BZ7	.63
1E7	.29	6C5GT	.39	12C8	.34
1G4GT	.24	6C6	.58	12F5GT	.34
1G6	.30	6C8G	.24	12J5GT	.42
1H4G	.30	6C8E	.44	12J7GT	.34
1H5GT	.40	6C8GG	1.11	12K7GT	.34
1H6	.24	6D6	.45	12L7	.70
1I6	.24	6E5	.49	12SA7GT	.44
1L4	.46	6F5GT	.39	12SF5	.50
1L5	.51	6F6	.37	12S7GT	.52
1N5	.46	6F8G	.24	12S7J	.44
1P5	.57	6G6	.52	12SK7GT	.48
1Q5	.54	6H6GT	.41	12SL7GT	.47
1R5	.45	6H8GT	.37	12SN7GT	.52
1S5	.39	6I6	.52	12SQ7	.44
1T4	.45	6J7G	.45	12SR7	.45
1T5	.53	6K7	.30	12T7	.30
1U4	.45	6K5	.47	14W7	.30
1U5	.35	6K6GT	.37	19B6GG	.95
1V7	.60	6L7	.64	19C4	.84
1X2	.63	6L5	.24	19T8	.79
2A3	.70	6L6	.64	19V8	.89
2A4G	.24	6M7	.64	20A	.63
2X2	1.50	6S4	.38	23AV5	.83
3A4	.45	6S8	.53	23B6GGT	.62
3E5	.45	6SA7GT	.43	23L6GT	.59
3D4	.48	6SD7GT	.41	23W4	.56
3Q5GT	.49	6SF5GT	.46	23Z5	.40
3A4	.47	6S7GT	.45	23Z6GT	.40
5U4G	.45	6S8	.73	28	.45
5V4	.73	6SJ7GT	.41	27	.39
5W4	.50	6SK7GT	.43	28L7	.89
5X4	.40	6SL7GT	.4R	3B5	.40
5V3GT	.32	6SN7GT	.52	3C5	.39
5Y3GT	.32	6SO7GT	.45	3SL6GT	.41
5Y4G	.35	6SR7GT	.42	3SW4	.37
5Z3	.46	6T8	.42	3Z4	.39
6A7	.59	6U4	.50	3Z5GT	.37
6AR	.62	6U5	.44	41	.42
6B4	.44	6U6	.63	42	.42
6B5	.43	6U7	.63	43	.55
6AJ5	.90	6V6GT	.39	45	.55
6AK5	.75	6W4GT	.44	45Z5	.49
6AL5	.38	6X5GT	.44	50B5	.39
6A05	.39	6X4	.37	50C5	.39
6A06	.37	6X3GT	.37	50C6	.59
6A5	.37	6Y4	.61	50L6GT	.41
6A55	.50	6Y6G	.4R	50Y7	.50
6A76	.37	7A4	.47	53	.24
6A8U	.38	7AF7	.53	54	.64
6AV6	.83	7C6	.44	57	.58
6AX4	.37	7C6	.40	58	.60
6AX6G	.53	7E6	.30	70L7GT	1.09
6B4G	.24	7K7	.70	75	.44
6B4	.64	12A8	.61	76	.44
6B8B	.39	12AL5	.37	77	.57
6B8C	.57	12AT6	.57	78	.47
6B8D	.44	12AT7	.56	80	.35
6B8E	.34	12AU6	.38	83	.68
6B8F	.59	12AU7	.43	85	.59
6B8G	.45	12AV6	.39	117L7	.39
6B8H	.39	12AV7	.59	117Z3	.39
6B8J	.41	12AX4	.48	1274	1.19
6B8K	.37	12AX7	.48	2050	.99
6B8L	1.25	12AZ7	.69	813	1.85

TERMS: A 25% deposit must accompany all orders—balance C.O.D. All shipments F.O.B. Irvington warehouse. Orders under \$10—\$1.00 Handling Charge. Subject to prior sale. Don't Delay... Order Today!

RAD-TEL TUBE CO.

"Integrity Is Our Chief Asset"

Phone: Essex 5-2947
Dept. RN9

115 Coit Street
IRVINGTON 11, N. J.

Selected Surplus Components

For INDUSTRY • AMATEUR • SERVICEMEN
Completely Guaranteed

SIGNAL Corps flame proof. Key-J5A NEW—boxed ea. 98c	WESTON 301 0-20 Micro-amp DC Mfgd. for Test Set. T562, K59490 ea. \$9.95
CROSS POINT Indicator. 2A—NEW—boxed ea. \$4.95	SPIT Stator Variable Condensers. 11v gap. 25 mmfd ea. section. \$1.25 50 mmfd ea. section. 1.50
BAND PASS Filters 60, 90, or 150 cycle Navy Type-Casid -53069, 70, 71 ea. \$1.95	PANELS removed from Computers. Loaded with valuable parts, etc. Large—\$1.50 ea. Small—98c ea.
WESTERN Electric RF Filter—D171738 115v-100w 15kc-30mc. ea. \$2.95	SOCKETS
HI-VOLTAGE Condenser .001mf-75.000vdc Aero 375028X. ea. \$49.50	7PR for 1625-G for \$1.00 Octals—Seat. 16 for 1.00 Octals—Bake. 16 for 1.00 Min 7PR Mica 16 for 1.00

SPECIAL PURPOSE TUBES

866/A	\$1.45	2E24	\$2.50
847	1.59	2E26	2.75
82A	3.95	8298	9.95
304TL	7.95	2C39A	19.95
3A29	14.95	R11308	5.00

25% with order. Balance C.O.D. unless well rated. F.O.B. N. Y.

LARGE LISTING—WRITE—INQUIRE

GREENWICH SALES CO.
59 Cortlandt St., New York 7, N. Y., Digby 9-3813

THE NEW TV DYNATRACER



TRACES TV SIGNALS AND VOLTAGES

LOCATES DEFECTIVE COMPONENTS INSTANTLY

REQUIRES NO ADDITIONAL EQUIPMENT

Makes Television Servicing Easier, Faster and More Accurate—AT LOW COST

\$4.95

plus P.P.D. or C.O.D. + Chgs.

Ideal for trouble-shooting television in the field or on the bench. Used under actual operating conditions, will out-perform more expensive testers.

A MUST FOR EVERY ALERT TV TECHNICIAN! SPECIFICATIONS: The "DYNATRACER" is a self-powered quality instrument designed to trace TV signals through any Video, Sound, Sync, AFC or VERTICAL and HORIZONTAL Sweep Circuit—will isolate trouble to a stage or component.

ADDED FEATURE: The "DYNATRACER" will also trace voltages and instantly locate open, shorted or intermittent condensers, resistors, coils, speakers, transformers, etc.

COMPLETE INSTRUCTION BOOK ENCLOSED 10-DAY MONEY BACK GUARANTEE

Clip adv., write name and address in margin, attach \$5 bill. Check or M.O. and mail to

Century ELECTRONICS CO.

8509-21st Ave., Dept. 204, Brooklyn 14, N. Y.

STANDARD BRAND SPECIALS


Tube Orders Over \$8.00. with full remittance. Prepaid To You in USA.

Stock up on these excellent values in Standard-Brand, Dated G.E., Sylvania, RCA, T.S., N.U. etc., TV Tubes. Prices are below wholesale cost. Quantities available from stock. Fully guaranteed on a 100% replacement-money-back guarantee.

024	.55	6A7	.50	6T8	.99
1B3	.63	6AU6	.49	6U5	.83
1L4	.40	6AX4GT	.66	6U8	.75
1NSGT	.60	6BC5	.62	6V3	.95
1R5	.50	6BE6	.50	6V6GT	.66
1U4	.70	6BF5	.69	6W4GT	.59
1S5	.60	6BG6G	1.40	6W6GT	.62
1T4	.55	6B6	.80	7B5	.60
1N34A	.69	6BK5	.70	7H7	.70
1N48	.50	6BK7	.99	12A7	.63
1X2	.85	6BL7GT	.89	12A7	.72
2E24	2.25	6BN6	.89	12AU6	.73
2X2	.43	6BO6	.85	12AU7	.57
3Q4	.80	6BQ7	.95	12AV7	.75
3Q5GT	.85	6BZ7	.99	12AX7	.65
3S4	.55	6C4	.47	12BA6	.50
3V4	.75	6CB6	.55	12BE6	.50
5U4G	.49	6CD6-G	1.55	12BH7	.98
5V4G	.90	6F6M	.68	12BY7	1.03
5W4	.88	6H6	.58	12SA7	.69
5Y3GT	.45	6J5GT	.45	12SG7	.75
6ABGT	.75	6J6	.59	12SL7	.63
6AB4	.60	6J7	.68	12SN7GT	.66
6AC7	.77	6K6GT	.58	14F7	.75
6AG5	.65	6K7	.65	19BG6G	1.30
6AG7	1.10	6L6GA	.98	35B5	.50
6AH4	.70	6S7	.70	50B5	.50
6AJ5	1.00	6SK7GT	.60	50C5	.50
6AK5	.69	6SL7GT	.59	304TH	7.75
6AL5	.48	6SN7GT	.57	866A	1.28
6AQ5	.58	6S4	.50	5654	1.10
6A07	.70	6S07	.62	5814	1.75

Above is a partial listing of our large stock. You may order types not listed at approx. the same savings.

SELENIUM RECTIFIERS

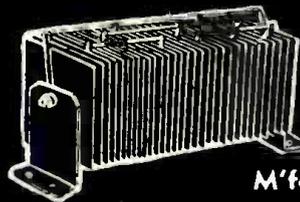

Buy Direct From Manufacturer

Full-Wave Bridge Types

Current (Continuous)	18/14 Volts	36/28 Volts	54/42 Volts	130/100 Volts
1 Amp.	\$1.35	\$2.15	\$3.70	\$7.50
2 Amps.	2.20	3.60	5.40	10.50
2 1/2 Amps.			6.00	13.00
4 Amps.	4.25	7.55	12.95	25.25
6 Amps.	4.75	9.00	13.50	33.00
10 Amps.	6.75	12.75	20.00	40.00
12 Amps.	8.50	16.25	25.50	45.00
20 Amps.	13.25	25.50	39.00	79.50
24 Amps.	16.25	32.50	45.00	90.00
30 Amps.	20.00	38.50		
36 Amps.	25.00	48.50		

We can manufacture other Selenium Rectifiers, Selenium Rectifier Supplies, XFMRs., & Chokes.

New Selenium Rectifier Transformers

PR1: 115 V., 60 cycles in. 4 Amps. \$8.75
 SEC: 9, 12, 18, 24, and 36 } 12 Amps. 16.75
 volts } 24 Amps. 35.75
 Continuous Ratings } 50 Amps. 59.75

● New Selenium Rectifier Chokes
 4 Amps.—.07 Hy.—.6 ohm \$7.95
 12 Amps.—.01 Hy.—.1 ohm \$14.95
 24 Amps.—.004 Hy.—.025 ohm \$29.95

BARRY ELECTRONICS CORP.

136 F Liberty Street, N.Y. 6, N.Y. REctor 2-2562

Terms: 25% with order, balance C.O.D. All merchandise guaranteed. F.O.B. N.Y.C.

INDEX OF

Advertisers

SEPTEMBER 1953

While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of this index.

ADVERTISER	PAGE	ADVERTISER	PAGE
Adelman, Nat.	167	McGee Radio Company	122, 123
Airex Radio Corp.	133	McGraw-Hill Book Co., Inc.	144
All Channel Antenna Corp.	21	Mallory & Company, P. R.	4th Cover, 79
Alliance Manufacturing Company	31	Mattison Television & Radio Corp.	174
Allied Electronic Sales	185	Midwest Radio & Television Corp.	115
Allied Radio Corp.	9	Miles Reproducer Co.	187
American Distributing Company	142	Milwaukee School of Engineering	132
American Microphone Co.	176	Mass Electronic Distributing Co., Inc.	129
American Television & Radio Co.	131	National Co.	179
Amperite Company Inc.	84	National Electronics of Cleveland	100
Amplifier Corp. of America	170	National Picture Tube Co.	146
Arky Radio Kits	177	National Radio Institute	3
Argos Products	116	National Schools	27
Arrow Sales, Inc.	173	Newark Electric Company	126
Ashe Radio Company, Walter	117	Newark Surplus Material Co.	184
Atlas Sound Corp.	164	Newcomb Audio Products Co.	109
Audak Company, Inc.	188	New Jersey Television Supply Co.	187
Audio Fair Corporation	153	New London Instrument Company	142
Audel, Publishers	168	Nichols Wire & Aluminum Co.	187
Barry Electronics Corp.	192	Offenbush & Reimus	189
Belden Mfg. Company	113	Olson Radio Warehouse	143
Bell Telephone Laboratories	6	Onan & Sons, D. W.	118
Berlant Associates	152	Oxford Electronics	150
Boulevard Electronics, Inc.	171	Peak Electronics Co.	124
Brush Electronics Company	26	Permolux Corporation	157
Brook Electronics, Inc.	166	Phileo Corporation	22, 23
C B S Hyrton	99	Phillips Tube Company, Incorporated	168
C & H Sales Company	168	Photo Sales	128
Candler System	163	Pickering & Company	30
Cannon Electric Company	162	Platt Electronics Corp.	159
Capitol Commodities, Inc.	187	Possner Electronics	177
Capitol Radio Engineering Institute	145	Precision Electronics, Inc.	181
Centralab	20	Premax Products	142
Century Electronics Co.	191	Premier Radio-TV Supply	139
Channel Master Corporation	14, 15	Progressive Electronics Co.	110
Cleveland Institute of Radio Electronics	127	Pyramid Electric Company	119
Collins Audio Products Co., Inc.	111	Quietrol Company	82
Columbia Electronics Sales	190	RCA Audio Equipment	33
Commercial Trade Institute	161	RCA Institute, Inc.	141, 185
Commissioned Electronics Co.	175	R W Electronics	177
Communication Equipment Co.	120	Radiart Corporation	28
Compo Corporation	128	Radio City Products, Inc.	175
Concord Radio	193	Radio Corporation of America	2nd Cover
Coyne Electrical School	114	Radio Craftsmen, Inc.	103
DeCray & Assoc., Frank W.	184	Radio Receptor Co., Inc.	155
DeForest's Training, Inc.	5	Radio Shack Corporation	82
Delco Radio Corporation	121	Radio-Television Training Association	25
Editors & Engineers Limited	100	Rad-Tel Tube Co.	191
Electro Products	184	Raytheon Mfg. Company	12
Electro Sales	179	Regency	172
Electro Voice	8	Relay Sales	98
Electronic Chemical Corp.	112	Reliance Merchandising	124
Electronic Instrument Co., Inc.	34, 106	Rider Pub., Inc., John F.	108
Electronic Measurements Corp.	151	Rinehart Books, Inc.	80, 112, 138
Eric Resistor Corporation	128	Rohn Mfg. Co.	161
Espey Manufacturing Co., Inc.	171	Sams & Co., Inc., Howard W.	104, 134
Fairchild Recording Equipment	136	Sangamo Electric Co.	189
Fair Radio Sales	185	Sarkes-Tarjian, Inc.	180
Fisher Radio	18	Schott Company, Walter L.	32
Franklin Technical Institute	190	Scott, H. H.	84
G & G Radio Supply Company	147	Service Instruments Co.	136
G & H Wood Products Co.	137	Shields Labs., Inc.	178
G. L. Electronics	183	Shure Brothers, Inc.	156
Gately Development Labs.	164	Simpson Electric Co.	146
General Electronic Dist. Co.	163	South River Metal Products Co., Inc.	152
General Electric	10, 81, 105	Sonotone	160
Goodheart, R. E.	167	Sprayberry Academy of Radio	83
Greenlee Tool Co.	193	Stan Burn Radio & Electronics Co.	172
Greenwich Sales Company	191	State of Wisconsin	183
Gull Model Airplane Company	161	Stephan Sales Corp.	181
Hallcrafters	7	Steve-El Electronics Corp.	106
Harvey Radio Company	130	Stevens Walden, Inc.	140
Harjo Sales Co.	161	Sun Parts Distributors, Ltd.	100
Hawkins Name Plate Company	179	Supreme Publications	165
Heath Company	86, 87	Sylvania Electric Products, Inc.	85
Henshaw Radio Supply	179	TAB	193
Hi-Lite Electronic Sales Co.	152	Tee-Vee Supply Co.	135
Hollywood Technical Institute	178	Telephone Engineering Co.	183
Hughes Research & Development Laboratories	106, 149	Television Communication Institute	116
Hudson Radio & TV Corp.	167	Terado Company	186
Illinois Condenser Co.	136	Transvision, Inc.	148, 149
Indiana Technical College	167	Triplet Electrical Instrument Co.	13
Instructograph Company	175	Tri-State College	130
International Correspondence Schools	11	Trio Manufacturing Company	107
International Rectifier Corporation	154	Tung-Sol Electric Inc.	24
J. J. Electronics	130	Turner Company, The	158
J F D Mfg. Co.	17	United Technical Laboratories	163
J S H Sales Co.	84	University Loudspeaker, Inc.	101
Jensen Industries	82	V-M Corp.	151
Jones & Laughlin Steel Corporation	125	Valparaiso Technical Institute	183
Kay-Townes Antenna Company	154, 155, 181	Visulite Company	189
Kester Solder Company	118	Waldon Electronics, Inc.	118
Lampkin Laboratories	116	Ward Products Corp.	3rd Cover
Leeds Radio Co.	193	Western Electronics Co.	185
Leotone Radio Corp.	164	Western Television Institute	177
Littelfuse, Inc.	29	Westinghouse Electric	19, 102
MacMillen Company	182	Windsor Electronics Tube Co.	112
		World Radio Laboratories	153
		Wholesale Radio Parts Co., Inc.	163

Classified

Rate 50c per word. Minimum 10 words

RADIO ENGINEERING

COMPLETE radio, electronics theory & practice: television: broadcasting: servicing: aviation, marine, police radio. 12 or 18 months. Catalog. Valparaiso Technical Institute, Dept. N, Valparaiso, Ind.

ELECTRONIC engineers with minimum of 3 years research or developmental work in field of Electronic Control Systems needed immediately in a permanent capacity by rapidly expanding firm located near Dallas, Texas. Varo Mfg. Co., Box 638, Garland, Texas.

ELECTRICAL Engineer. Large gulf coast chemical company has opening for graduate electrical engineer. 25-35 years of age. Communications experience desirable. Supervisory position. Salary open. Reply Box 536, Radio & Television News, 64 E. Lake St., Chicago 1, Ill.

FOR SALE

G.E. MODEL 910 Projector. Used three weeks. Complete or in parts. Write to: Caya's Radio Shop, Main St., Northbridge, Mass.

TWO National NC-183 Communications Receivers, factory wired for diversity operation, \$250 each. Nagrodsky, 85 Shields Ave., Williston Park, N. Y.

TAPE Recorders, Tapes, Accessories. Unusual Values. Dressner, 621-R East 20th St., N.Y.C. 9.

TUBES and equipment bought, sold, and exchanged. For action and a fair deal, write B. N. Gensler, W21.N1, 136 Liberty, New York 6, N. Y.

NEW RCA 3AP1A original cartons, \$8.75 each. Tubes, surplus—bought, sold. Free list. Write, Mark, Box 14, New York City 72.

DIAGRAMS—Radio \$1.00; record changers, recorders \$1.25. Television with service data \$2.00. Where model unknown, give part numbers. Kramer's Radio Service, Dept. S53, 36 Columbus Ave., New York 23, N. Y.

TV-PM antennas. All types including UHF. Mounts, accessories. Lowest prices. Wholesale Supply Co., Dept. H, Lunenburg, Mass.

300 ohm TELEVISION lead-in, 1,000 feet \$11.00; RG-29/U coax 100 feet \$4.00; Postpaid to 600 miles. Van Dick, Little Falls, New Jersey.

NEW 1953 Heath model V-6 VTVM wired, tested, calibrated; \$44.95 complete. Jerry Cohen, 340 Frost Street, Brooklyn 22, N. Y.

TELEVISION high pass filter, Guaranteed, only \$1.00 Postpaid. Box 8, Hillside Manor Branch, New Hyde Park, N. Y.

WANTED

AN/APR-4, other "APR," "ARR," "TS," "IE," ARC-1, ARC-3, ART-13, everything surplus; Tubes, Manuals, Laboratory equipment. Describe, price in first letter. For Sale: Reconditioned Watthour Meters, four for \$10.00. Engineering Associates, 431 Patterson Rd., Dayton 9, Ohio.

WILL buy all ART-13 type T-47A \$200.00; ART-13 type T-47, \$150.00; BC-348 unmodified \$65.00; BC-348 modified \$50.00; APN-9 \$200.00; ARC-3 complete \$600.00; R77 Receivers \$300.00; ARC-1 \$300.00; BC-312 \$60.00; BC-342 \$60.00. Ship via Express C.O.D., subject to inspection to: H. Finnegan, 49 Washington Avenue, Little Ferry, N. J.

WANTED used coin operated radios, good condition. Quote best price. B. Kugler, % Chas. C. Giles, Clinton, South Carolina.

CORRESPONDENCE COURSES

USED correspondence Courses and Books sold and rented. Money back guarantee. Catalog free. (Courses bought.) Lee Mountain, Pisgah, Ala.

USED correspondence courses and educational books bought. Sold. Rented. Catalog free. Educational Exchange, Summerville, Ga.

PATENT ATTORNEYS

ATTENTION: Inventors of Electronic, Electrical, Audio, Automobile Products. Will buy or pay royalties on any manufacturable ideas if inventions are possible money makers. We manufacture. Please write Box 535, % Radio & Television News, 64 E. Lake St., Chicago 1, Illinois. Advise arrangement for discussion.

MISCELLANEOUS

SPEAKERS repaired, wholesale prices, guaranteed workmanship. Amprite Speaker Service, 70 Vesey St., New York City 7.

KITS assembled; units constructed from schematics. Audio amplifiers our specialty. Neil Laboratories, IA, 164 Prospect Place, Brooklyn, N. Y.

IT'S READY NOW!

SEND FOR YOUR GIANT NEW Concord Catalog

FALL 1953 EDITION



IT'S GOT
EVERYTHING!

- Standard Lines
- Special Buys

and

IT'S FREE!

Concord Radio
55 Vesey Street, New York 7, N. Y.

Phone DLgby 9-1132

Repeated
by Popular Demand

MAGNIFICENT
BRITISH
HI-FI 5" PM
SPEAKERS



A sensational value! 50-12,000 CPS range. Outperforms most 8" and 10" units. Highly efficient for general use in amplifiers, radios, TV sets and custom combinations. 4.6 ohms impedance—1.5 oz. Alnico magnet. Buy now—while we still have stock on hand!

Stock No. 99-A-850P.
Singly \$1.69.

\$1.59

In lots of 4—Each
"All-American" Tube Kit
"Portable" KIT

12SA7, 12SK7, 12SQ7,
35Z5,
50L6— **\$2.99**

1R6, 1U4, 1U5, 35A
\$2.95

MINIMUM ORDER \$5.00

CONCORD RADIO, 55 Vesey St., New York 7, N. Y. Dept. N-9
Send Giant New FREE Concord Catalog at once to:

Name _____
Address _____
City _____ Zone _____ State _____

Easy, fast
way to cut
"Key" and "D"
openings
in chassis



...with new GREENLEE
Radio Chassis Punches

Now, in 1½ minutes or less make perfect "Key" or "D" holes for sockets and other equipment. Simply insert GREENLEE Punch and turn with an ordinary wrench... get a "clean" opening in a hurry! Write today for details on these as well as GREENLEE Radio Chassis Punches for round and square openings. Greenlee Tool Co., 1889 Columbia Ave., Rockford, Illinois



No. 732 "Key" Punch



No. 733 "D" Punch

TOOLS FOR CRAFTSMEN
GREENLEE

POLYSTYRENE

ROD— 12" or 48" lengths.

Dia.	12"	48"	Dia.	12"	48"
1/8"	\$.03	\$.12	3/4"	\$.80	\$ 3.20
3/16"	.06	.24	1"	1.55	6.20
1/4"	.10	.40	1-1/8"	2.00	8.00
5/16"	.16	.64	1-1/4"	2.30	9.20
3/8"	.21	.84	1-3/8"	3.00	12.00
7/16"	.30	1.20	1-1/2"	3.30	13.20
1/2"	.40	1.60	1-3/4"	4.50	18.00
5/8"	.57	2.28	2"	5.90	23.60

SHEET - masking paper both sides.

Thickness	Size	Price
1/16"	12" x 12"	\$ 2.50
3/32"	12" x 12"	2.75
1/8"	12" x 12"	3.00
3/16"	12" x 12"	3.75
1/4"	12" x 12"	4.60
1/16"	12" x 24"	4.90
3/32"	12" x 24"	5.25
1/8"	12" x 24"	5.90
3/16"	12" x 24"	7.25
1/4"	12" x 24"	8.25
1/32"	20" x 20"	7.75
1/16"	24" x 24"	9.50
3/32"	24" x 24"	10.25
1/8"	24" x 24"	11.75
3/16"	24" x 24"	14.00
1/4"	24" x 24"	16.00
5/16"	20" x 20"	14.50
3/8"	20" x 20"	16.00
3/8"	24" x 24"	23.75
1/2"	20" x 20"	21.50
1/2"	24" x 24"	31.88
5/8"	20" x 20"	34.50
3/4"	20" x 20"	41.00
1"	20" x 20"	55.50

TUBING — 12" or 48" lengths.


O.D.	I.D.	12" lgth.	48" lgth.
1/4"	1/8"	\$.07	\$.28
5/16"	3/16"	.10	.40
3/8"	1/4"	.13	.52
1/2"	3/8"	.18	.72
5/8"	1/2"	.23	.92
3/4"	5/8"	.29	1.16
1"	7/8"	.38	1.52
1-1/2"	1-1/4"	1.13	4.52
2"	1-3/4"	1.50	6.00

All prices F.O.B. our warehouse New York


LEEDS RADIO CO.
75 Vesey St. Dept. A New York City 7




Up! Up! Up! — Up go your Sales! Up go your Profits — to a new NEW HI — with the complete WARD line of Television Antennas and Accessories that outdistances tomorrow — that makes today look far behind! Creations of the world's finest research laboratories . . . produced by the oldest and greatest of TV and Radio Antenna manufacturers . . . WARD Antennas will keep you far in advance of your competition. Climb aboard, Partner — and zoom to greater profits!

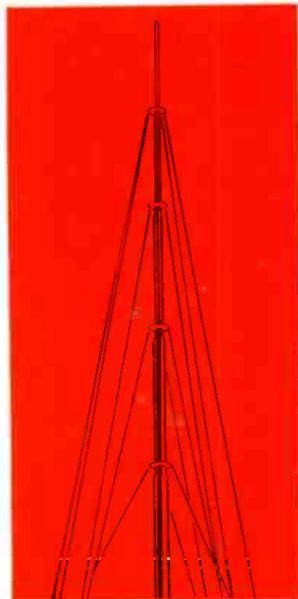

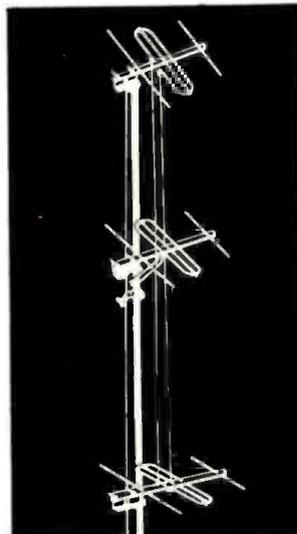
ZIP-HI MAST — Corrosion-proof 16 gauge permotube . . . easily assembled . . . in 2, 3, 4, 5 section models.



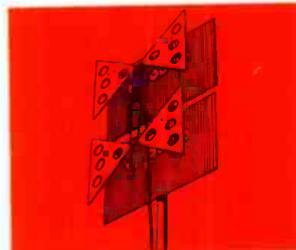3 X 3 — Original development for UHF band composed of 3 stacked 3 element beams. Full wave spacing between boys . . . clean cut pattern with sharp forward lobe and no side lobes . . . cut to frequency . . . unsurpassed for near fringe and fringe areas.



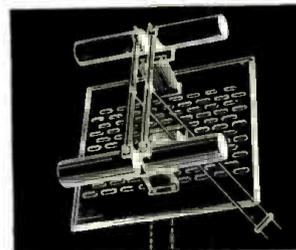
BOW TIE — Peak-A-Bow design with the only adjustable screen on the market . . . Available in single and stacked models.




CAN.CAN — New lazy H design for entire UHF band . . . uni-directional pattern . . . sturdy compact unit . . . field tested and thoroughly proven.



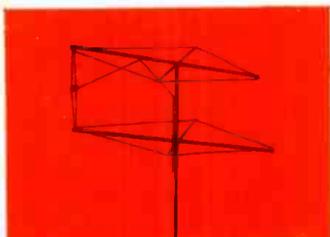
CORNER REFLECTOR — For semi-fringe areas . . . ruggedly designed to eliminate ghosts and vibration.



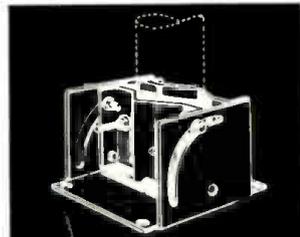
RHOMBIC — Highest gain of all UHF antennas . . . for fringe and super fringe areas.



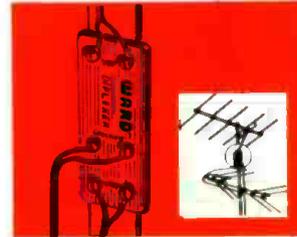HEAVY DUTY BASE — Ruggedly constructed to fit all masts from 1 1/4" to 2 1/4" O.D.



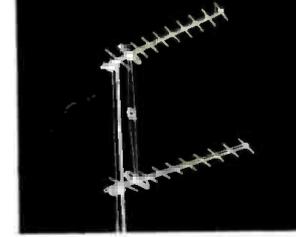DIPLEXER — For separate UHF-VHF antennas . . . or for set and converters with separate UHF-VHF terminals . . . Foolproof . . . easily installed.



10 ELEMENT YAGI — Multi-channel series of 10 element UHF Yagis . . . Excellent for fringe areas . . . very directional . . . completely pre-assembled — single and stacked models.



THE **WARD** PRODUCTS CORP.

DIVISION OF THE GABRIEL COMPANY

1148 Euclid Avenue • Cleveland 15, Ohio • in Canada: Atlas Radio Co., Ltd.

Depend on Mallory
for
Approved Precision Quality



The
MALLORY UHF Converter
can mean
EXTRA PROFITS
when UHF television comes
to your area

Where UHF television has already gone on the air, the Mallory Converter has proven to be one of the fastest moving items in the new UHF market. And for good reason too.

- The Mallory Converter will equip any TV set to receive *all* channels—old and new.
- Picture definition is excellent... tuning is easy.

Another outstanding feature of the Mallory Converter is that it tunes in *all* channels in *any* area. The customer who has one has nothing more to buy, no adjustments to make... even if he moves to another broadcast area.

YOUR MALLORY DISTRIBUTOR will be glad to show you the Mallory Converter... tell you how successful it has been for dealers in other areas. Get complete information today, so you can make the most of the new UHF market tomorrow.

**Installation is
FAST and EASY**

... and it can be done right in your customers' homes in a matter of minutes. Simply connect the antenna leads and power lines from the Converter to the set. That's all there is to it.

P. R. MALLORY & CO., Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA