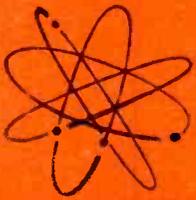



SERVICE DEALER

AUGUST
1956

50¢



and ELECTRONIC SERVICING

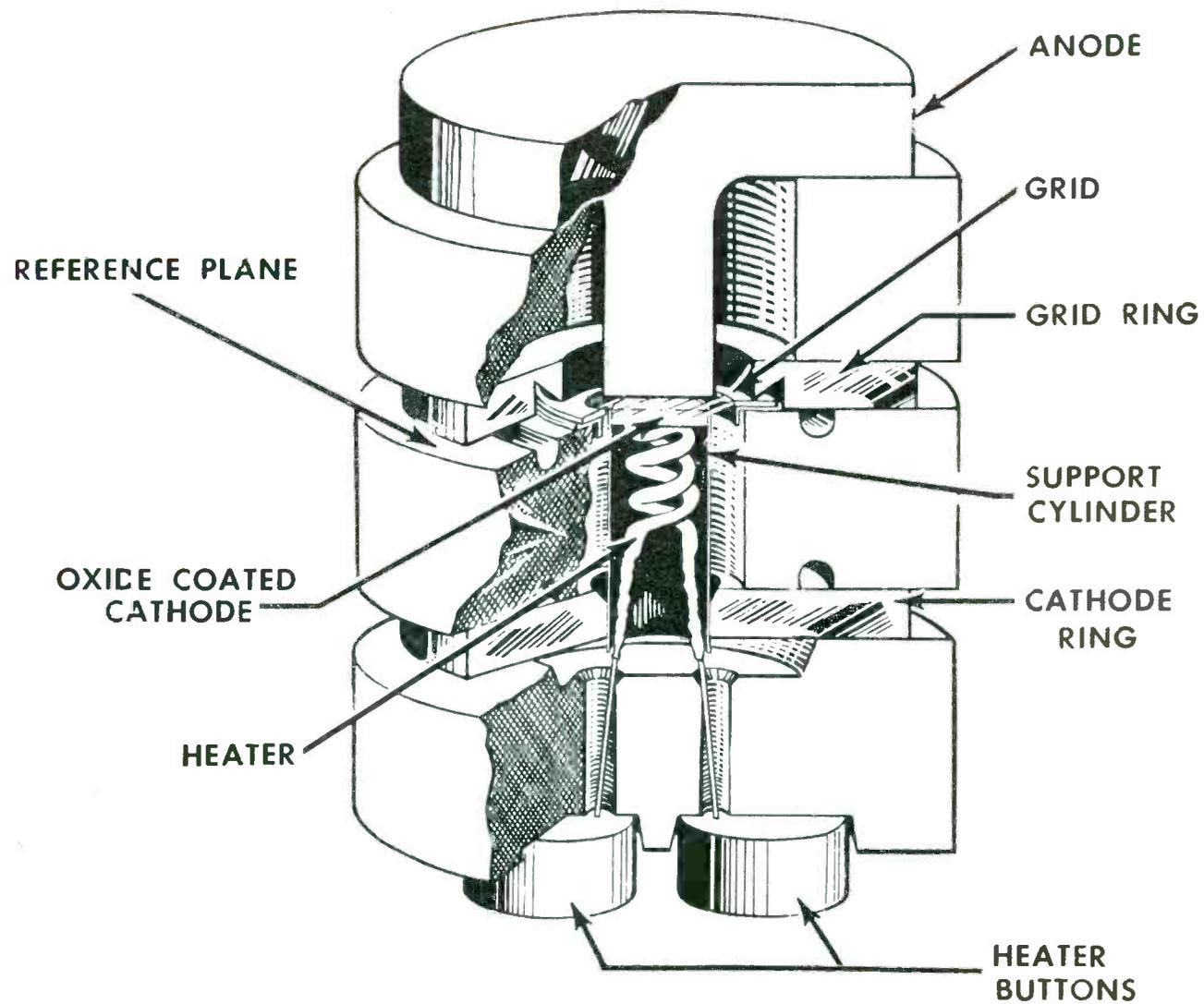

MICRO-MINIATURE CERAMIC TUBE

Photo explanation on page 1

In This Issue:

The Marine Electronics Business
Troubleshooting the Yoke and CRT
Oscilloscope Probes

A Modern Cathode Ray Tube Checker
Complete Mfrs. Schematics
Color Detectors


**"A TV network
can't afford
to take chances
on tube quality"**

As Garry Moore tells over five million women on the CBS Television Network...

"CBS tubes are made by the tube manufacturing division of Columbia Broadcasting System. So we *know* how dependable they are. That's why we use them here in our own cameras and other equipment."

Garry also points out that CBS tubes have the Good Housekeeping Guaranty Seal. That means a lot to women . . . and women are your customers.

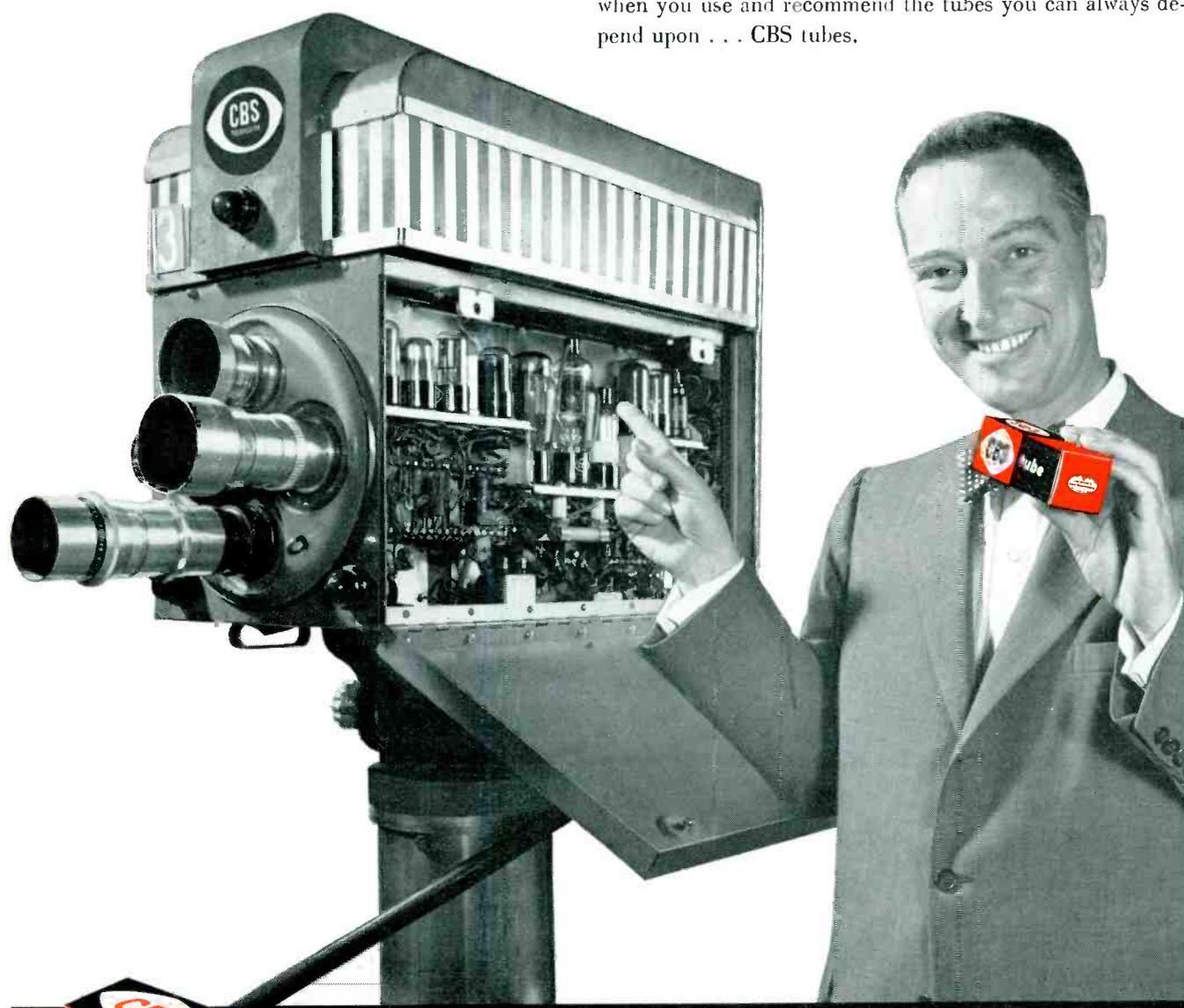In fact, if you're like most service technicians, more and more women are asking you for CBS tubes. Because Garry Moore has convinced them that there are no better tubes made. Yes, you'll find it's easy to build customer satisfaction when you use and recommend the tubes you can always depend upon . . . CBS tubes.



Garry Moore sells you and your expert service, too. Have you seen him?

CBS-HYTRON, Danvers, Massachusetts
A Division of Columbia Broadcasting System, Inc.

EDITORIAL STAFF

Sanford R. Cowan	Publisher
Samuel L. Marshall	Editor
Oscar Fisch	Assistant Editor
Charles W. Gardner, Jr.	Editorial Production Manager
San D'Arcy	Contributing Editor
Robert T. Dargan	Contributing Editor
Paul Goldberg	Contributing Editor
Elbert Robberson	Marine Communications Editor
Lawrence Fielding	Hi-Fi & PA Editor

BUSINESS STAFF

Advertising Sales

New York and East	Richard A. Cowan Jack N. Schneider 67 West 44th Street New York 36, N. Y. MUrray Hill 7-2080
Chicago and Midwest	Jim Summers 400 North Michigan Ave. Chicago 11, Illinois SUperior 7-1641
West Coast	Ted E. Schell 2700 West 3rd Street Los Angeles 57, Calif. DUnkirk 2-4889

David Saltman Advertising Production Mgr.

CIRCULATION

Harold Weisner	Circulation Manager
Carol J. Binderman	Ass't Circulation Mgr.
Mady Weinbaum	Circulation Processing

SERVICE DEALER and ELECTRONIC SERVICING (formerly Radio-TV Service Dealer) is published monthly by Cowan Publishing Corp., 67 West 44th Street, New York 36, New York, MUrray Hill 7-2080. Subscription Price: \$3.00 one year, \$5.00 two years in the United States, U.S. Possessions, Canada and Mexico. Elsewhere \$1.00 per year additional. Single copies 50¢. Second Class Mail privileges authorized at New York, N. Y.

POSTMASTER: SEND FORM 3579 TO SERVICE DEALER and ELECTRONIC SERVICING. 67 WEST 44TH STREET, NEW YORK 36, N. Y.

SERVICE DEALER



and **ELECTRONIC SERVICING**

VOL. 17, NO. 8

Member

EPA

AUGUST, 1956

FEATURE ARTICLES

- The Marine Electronics Business, Part 3**, by Elbert Robberson 4
Boat electrical systems described.
- Trouble-Shooting the Yoke and CRT, Part 2**, by B. Jarmalow 10
Discussion of Yoke construction, operation and trouble shooting; also CRT troubles.
- Oscilloscope Probes**, by Robert G. Middleton 14
How to use the scope demodulator probe for various circuit tests.
- A Modern Cathode Ray Tube Checker**, by J. Frank Brumbaugh 20
Description of a CRT checker with unusual features.
- Color Detectors**, by Bob Dargan and Sam Marshall 28
Discussion of the various types of detector circuits employed in color TV receivers.

CIRCUIT AND SERVICE FORUM

- Service Dealer Complete Manufacturer's Schematics**
- Westinghouse Ch. V2340, V2350, V2342, V2352, V2343, V2341, V2351 23
G.E. "S" line 25
- Workbench**
- CBS Color Chassis 205 34
Motorola Color Chassis BP-902A-01 35
- Video Speed Servicing Systems**
- Motorola Chassis 1S-326B 37
Silvertone Chassis 128-16 39
- The Answerman**
- Connecting a VU meter to a tape recorder 41
Travler 46A3—burnt out contrast control 41
Hum in TV receivers (not caused by open filters) 43
Reducing strong TV signals 44

DEPARTMENTS

- S. R. Cowan Ad Libs** 2 **New Antennas** 27
- Rider Speaks** 12 **Trade Flashes** 32
- Guest Editorial** 18 **Association News** 36
- New Semi-Conductors** 22 **Buyer's Directory** 45
- Advertiser's Index** 49

THIS MONTH'S FRONT COVER

The new G.E. "micro-miniature" ceramic triode 6BY4 for UHF TV sets.

Entire Contents Copyright 1956, Cowan Publishing Corp.

COWAN PUBLISHING CORP., 67 West 44th Street, New York 36, N. Y.

SERVICE DEALER and ELECTRONIC SERVICING • AUGUST, 1956

AMPHENOL

TWIN LEAD HANKS

Now . . . 25 FOOT HANKS

25 FEET GENUINE AMPHENOL no. 214 056 FLAT TWIN LEAD NET PREASSEMBLED WITH LUGS ON ONE END! AMERICAN PHENOLIC CORPORATION CHICAGO 50, ILLINOIS

For Better TV Pictures USE NEW ANTENNA WIRE AMPHENOL YOUR GUARANTEE OF DEPENDABLE PERFORMANCE

make your Selling job EASIER!

in addition to 50, 75, 100 ft. put-ups

At your request AMPHENOL now provides new 25 foot hanks in two popular types of Twin Lead. Add these to your AMPHENOL Twin Lead Display Board—and watch your sales and profits increase while your selling job gets easier! Your growing Twin Lead market includes: those who buy a second set (black & white or color) or replace worn-out lead-in or need extra lengths for moving sets.

Don't wait for your customers to ask—stock and display AMPHENOL Hanks in all the popular sizes listed below.

Part No.	Description	Available in Hanks of			
		25 ft.	50 ft.	75 ft.	100 ft.
214-318	Indoor*—60 mil, 7/28 pure copper cond.	✓	✓	✓	✓
214-056	Standard—60 mil, 7/28 pure copper cond.	✓	✓	✓	✓
214-559	Steelcore—72 mil, 7/28 copperweld cond.		✓	✓	✓
214-298	Rotator—4 conductor—7/28 pure copper cond.		✓	✓	✓
214-100	Century—100 mil, 7/28 pure copper cond.		✓	✓	✓

Now Available in Coils

214-271	Air-Core**—U.S. Pat. 2543696 7/28 pure copper cond.		✓	✓	✓
---------	---	--	---	---	---

*Indoor is the newest AMPHENOL Twin Lead. It's made of pure virgin natural polyethylene to harmonize with any interior.

**Now famous AMPHENOL Air-Core is available in pre-cut coils.

Remember: for finest quality, virgin polyethylene is used in all AMPHENOL Twin Leads.

AMPHENOL ELECTRONICS CORPORATION

chicago 50, illinois

AMPHENOL



S. R. COWAN

Ad Libs

The Votes Are In

You will recall that in April we announced that starting in May this magazine would go to "King-Size" and we explained in a superficial manner why that change would take place. Now, because so many subscribers have asked us to do so, we will give you fuller details as to the reasons for the change.

During the last quarter of 1955 we made a survey and asked every tenth reader of our magazine, (nearly 7,000 of the 70,000), a series of questions. For example, we asked the nation's servicemen what they liked about our magazine and other servicemen's magazines, what they disliked about our magazine and the other servicemen's magazines, and finally we asked for their suggestions as to what we could do as a publication to help them.

Almost 5,000 replies came in and strangely enough nearly 4,600 service shop owners remarked that the greatest contribution we


This combination of **CDR ROTORS**
and the **Biggest TV Spot Campaign**


in our history

PRE-SELLING your customers

opens the door

for you to

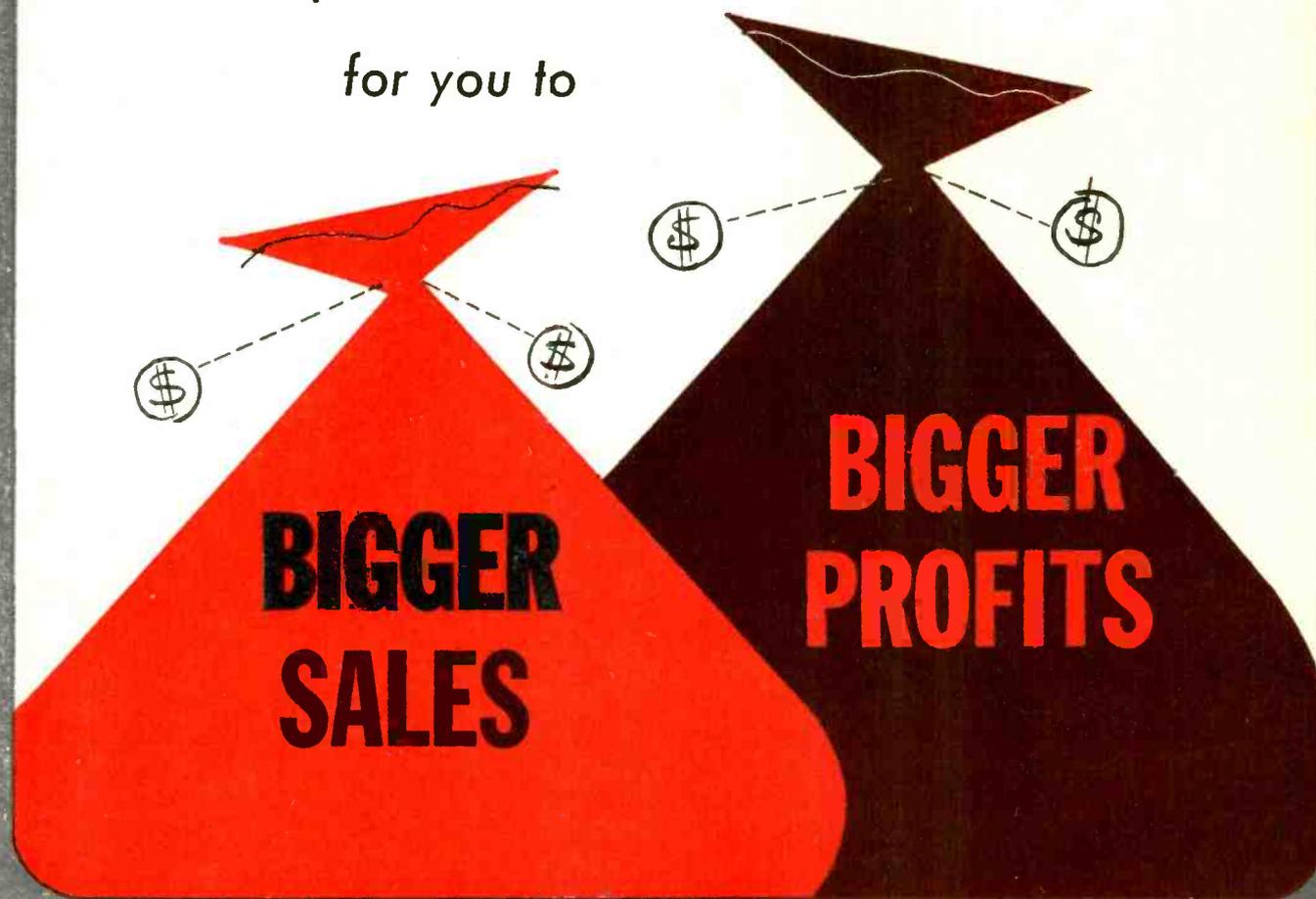

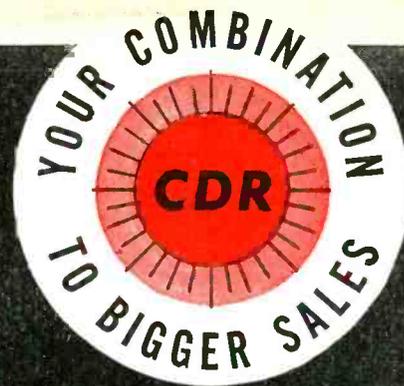


There's more in store
for you... when you feature
CDR ROTORS

Proven the popular favorite
the complete line...
a model for every need!



AR-1

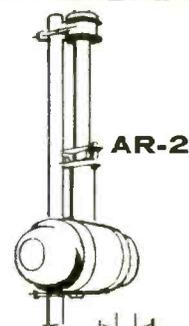

AR-2



AR-22

featuring

CDR AUTOMATIC Rotors

An outstanding group of rotors... three proven and tested models... ALL 40% SHARPER TUNING than ANY other automatic rotor. Handsome cabinet... dependable performance... proven and tested by thousands and thousands of satisfied users.

TR-12 a special combination value consisting of complete rotor, including thrust bearing. Handsome new modern cabinet with meter control dial, uses 4 wire cable.

TR-11 same as TR-12 without thrust bearing.

TR-4 the heavy duty rotor complete with handsome modern cabinet with METER control dial, uses 4 wire cable.

TR-2 the heavy duty rotor with plastic cabinet featuring "compass control" illuminated perfect pattern dial, uses 8 wire cable.



CORNELL-DUBILIER South Plainfield, N. J.



The **RADIART** Corporation, Cleveland 13, Ohio

www.americanradiohistory.com


could make would be to show them how to make more money by opening new fields of endeavor for them. That overwhelming, simple and pointed request was the determining factor in our decision to open new service vistas for our readers.

Of course only 10% of our readership was involved in the survey and the other 90% did not know what was happening until our format - change announcement appeared in the April issue. Subsequently, since the May issue reached our subscribers, our mail has been rather heavy, and we feel that you are entitled to know what our readers' reaction has been.

The first 18 letters we received came from service shop owners who voiced strong indignation and objection to our new format. 17 of the 18 men stated that the new magazine was so big that it did not fit on their shelves. During the next few weeks scores of other letters arrived and amongst them was only an occasional letter of criticism, the bulk of the letters being congratulatory. Now, just two months later I am happy to report that a total of 31 letters of criticism about our new format have reached me while 179 unsolicited letters complimenting us on our new format and broadened editorial scope have also arrived.

Strangely enough, of the 31 critical letters received, only 2 were written on business letterheads; all the others being written on either postcards or plain paper. However, of the 179 letters favoring our new format, only 6 were on plain paper or postcards and 173 were on professional letter-

[Continued on page 7]

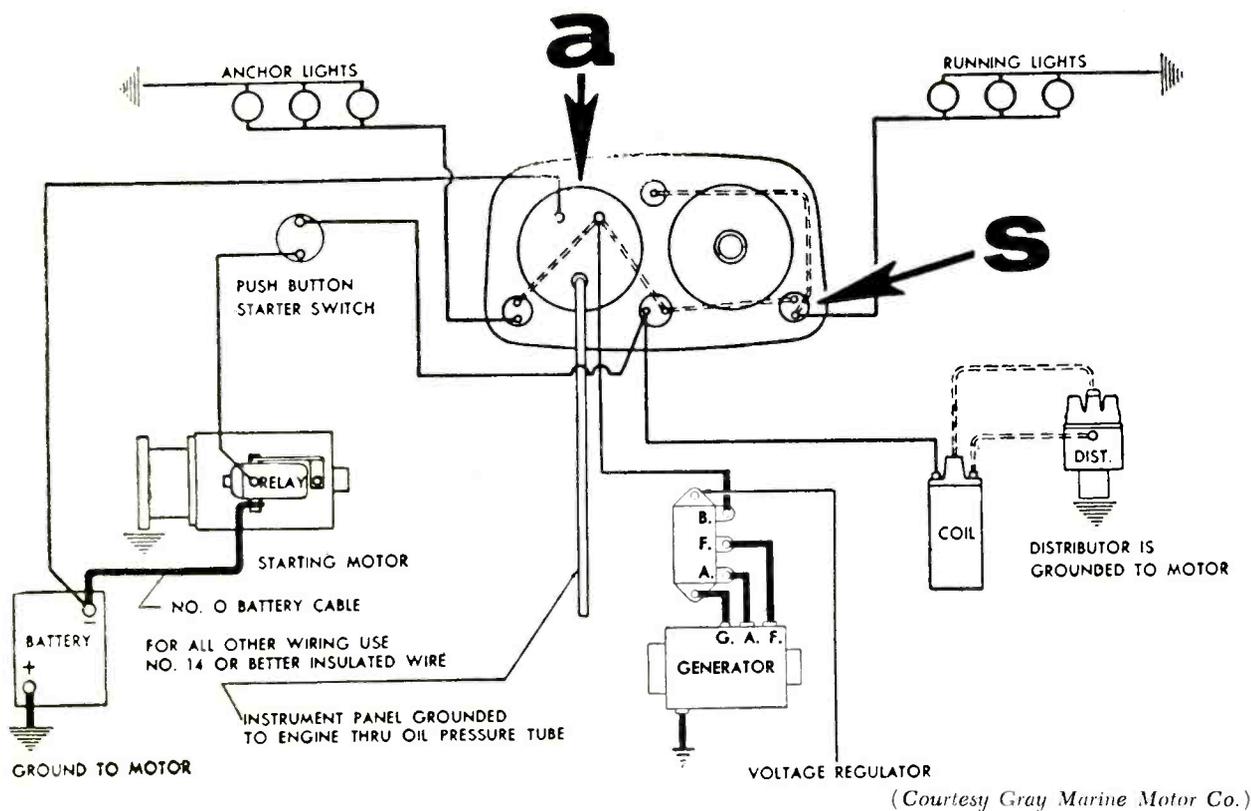

► Fig. 1—Typical boat engine-battery system. (a) indicates ammeter, (s) switches.


Various electrical wiring systems used in typical boat installations are discussed in this installment. Precautions for the prevention of accidents are also discussed.

PART 3—BOAT ELECTRICAL SYSTEMS

by **ELBERT ROBBERSON**
Marine Electronics Consultant



The Marine Electronic Business

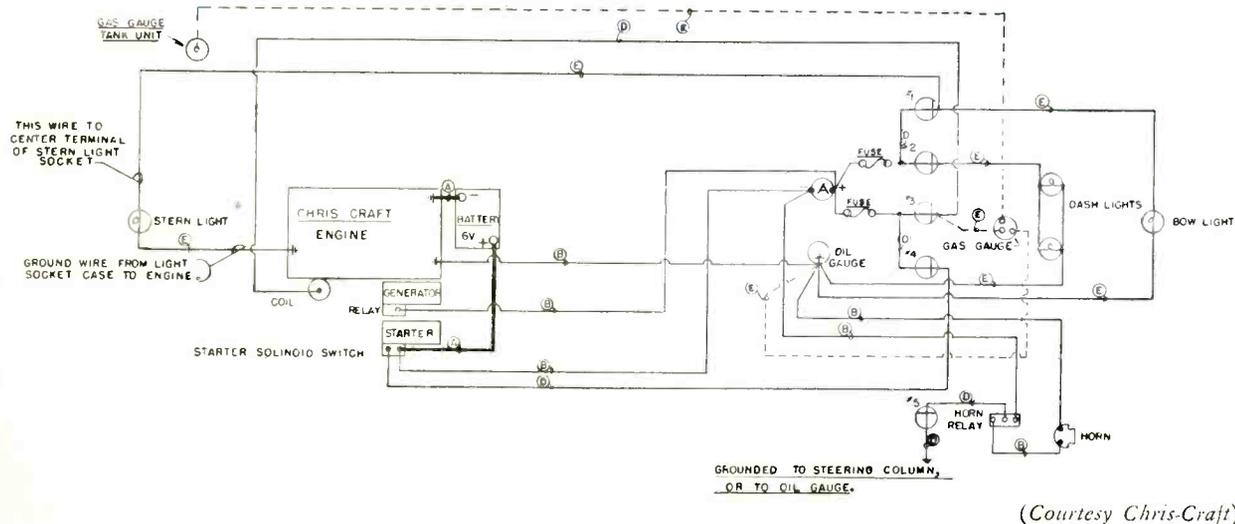

► Fig. 2—Circuit of more elaborate boat wiring system.

TOTE a piece of electronic equipment into a man's home and nobody has the least trepidation about plugging it into an electrical outlet.

But step foot over the side of the same man's boat, and you're in a different world. To the person accustomed to shore circuits, where Underwriters' and power-company rules keeps things fairly well in order, the usual small-boat electric system will seem like chaos.

You'll find power feed lines for different devices hooked onto the engine battery, the electric starter, the dashboard ammeter and (of all places) *the engine oil gage!*

But once you know how these lashups are derived, you can safely connect your own contribution to the boat's equipment. In badly confused situations, you might suggest a little electrical reorganization to the owner, which will make for a more reliable system.

Following this thought a little further, a service

man who becomes an expert in this field may gain considerable extra business by taking care of the more complex electrical needs of a number of small shipyards and boat dealers. Usually, there just isn't enough electrical work at any one small yard to sustain a specialist. So one of the engine mechanics is called upon to double as electrician. The bad results of having electrical work performed by alumni of the corner gas station are evident wherever you find boats.

Simple Battery Systems

Aside from the personnel involved, most confusion in the boat electrical systems stems from the fact that the majority of today's boat engines are beefed-up automobile engines. In the interest of economy, automobile wiring practice is followed, with one side of the battery grounded to the engine, and the engine block and various other masses of metal connected to it acting as ground returns. The polarity of the battery ground varies between engine manufacturers, and may change from year to year. In practice, it does not matter which side is grounded, just as long as there are no cross-polarity connections.

Fig. 1 shows a typical boat engine-battery system. One pole of the battery (in this case positive) and the ground returns of the charging generators, engine starter, ignition system, etc., are all connected to the engine block. Note that this ground and the lead over to the starting-motor solenoid switch are the only heavy conductors from the battery. Because of the high starter current there are no fuses in this heavy line.

The "hot" power feed for auxiliary and lighting circuits is a single wire run from the ungrounded terminal of the battery, as shown, to the dashboard ammeter, or more often this wire is connected to the solenoid. The wire, and branches from here on out, may be as light as No. 14 gage. Load circuits, and the generator, are connected to the other side of the ammeter, so that current going into or out of the battery makes the meter register "charge" or "discharge."

The simplest installations have no fuses or circuit breakers other than a toggle switch on the control panel. Although the schematic shows only the hot wire running out to the lights, with the return to ground at that point, two wires are actually used. One of them is the hot wire and the other the ground return. And here is where some odd connections may be found, such as terminals on the oil gage (which on the surface seems to have nothing to do with electricity). It has been common practice to ground auxiliary return circuits to any piece of hardware that connects metallically to the engine. Thus, steering columns, clutch controls, pressure gages connected to the engine by a copper tubing, and what-not will be found "doubling" as electrical conductors.

When a boat having such a system is originally

delivered, it may be entirely bare of any other electrical gadgets. However, the new skipper invariably loads on the equipment. Windshield wipers, horns, cabin lights are the starting point. As circuits are added, they may be connected to the ammeter until the terminal is full, and not one more wire can be squeezed under the nut. Then wires begin doubling up on the ignition switch and any other "hot" points that can be found. Things installed in the engine compartment, such as an electric bilge pump, are usually connected to the "hot" solenoid terminal or the battery. Thus, the electrical system turns into quite an amazing growth.

Semi-Protected Battery Systems


Figure 2 shows the circuit of a somewhat more elaborate boat wiring system. Note that load circuits are protected by fuses as well as having "on"-off switches. Some boats have the fuses behind the dashboard wherever room is found—the better jobs have a switchboard, installed in a cabinet or provided with a protective cover.

Note that the electric horn is fed from the battery side of the ammeter, rather than on the "load" side used for other circuits. This is because horn current is so high it would damage the ammeter. And, as in the case of the engine-starting motor, the horn is not fused.

Two or three-engine boats have complete battery systems for each engine, along the lines of either of the preceding. Although boats large enough to have more than one engine usually carry an auxiliary battery system for lighting and power, some loads, such as the dashboard and navigating lights, will still be operated from the engine batteries. In this case, the circuits may be split up—for instance with the battery of one engine supplying dashlights, and the battery of the other furnishing electricity for running lights, etc.

In the interests of safety, some boats are wired with heavy (100-ampere or more) knife or inclosed switches in the main battery leads to disconnect all load when the boat is not manned. And some have double-throw switches here, arranged so either battery can be used to start either engine in an emergency. Because of the voltage loss in lengthy high-current cables, such switches are as close to the engines as possible—sometimes directly at the batteries.


Great caution is, of course, necessary when working around open switches (and all of the other battery-circuit terminals, for that matter). Six or twelve volts may sound "tame" to the technician accustomed to working in the thousands—but a heavy short circuit can cause hundreds of amperes to flow in a hurry. This is enough to blow up a tool in your face, melt a ring on your finger, or a wrist-watch band on your arm: very unpleasant, not to mention fire danger.

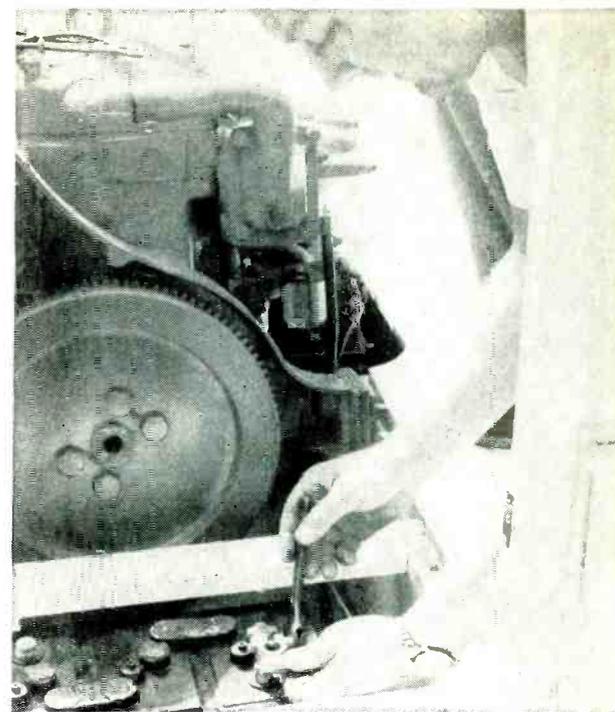

▶ On small boats, heavy current equipment is connected directly to the battery.

Remember that gasoline fumes are terrifically explosive, and easy to ignite. The engine room of a boat is no place to test batteries or circuits by "spark-ing" wires together. When a boat starts to "blow" there are only milliseconds to get out, and very few people have made it without injury.

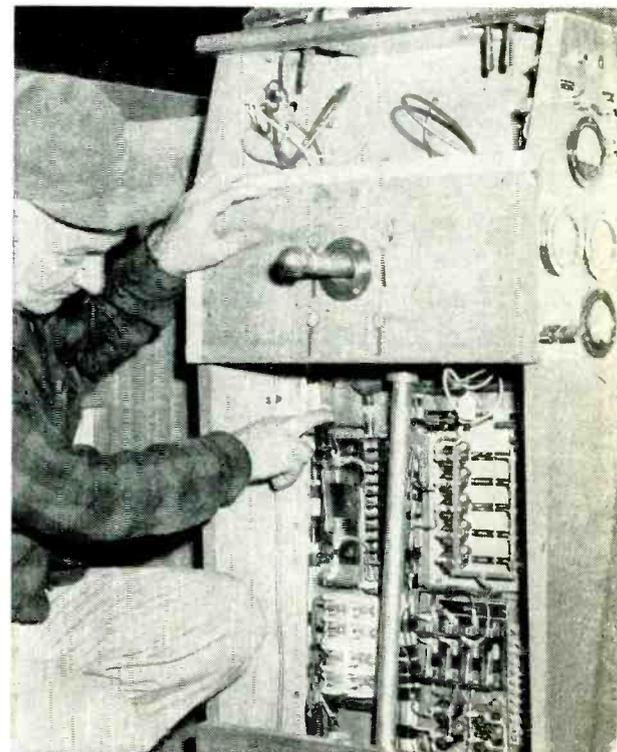There have been a few twin-engine boats built



▶ Example of panel on 50 foot boat. Not suitable for very heavy-current equipment.



Well-engineered boats have separate circuits and junction boxes as illustrated above.

with the battery for one engine positively grounded, and the other engine battery negatively grounded. This arrangement provides two separate six-volt sources of power, and 12 volts for higher-current equipment between the "hot" sides of the two batteries. Naturally, the 12-volt lines cannot be used to operate any device which is designed with one of its input legs grounded, since this would short-circuit one battery.

It is obvious that only equipment having very low current requirements can be tapped into the usual boat circuits because of the small wire used, and the fact that circuits are very likely overloaded by the time you get there. Standard practice is therefore to connect electronic gear directly to the battery with heavy cable or, better yet, to the solenoid "hot" terminal and to the same stud on the engine that the battery ground connects to. The latter connection is safer, since the person servicing the batteries cannot mis-connect the cables as easily as if four or more wires were involved.

On low-voltage feed lines, such as for radiotelephones, heavy motors, etc., fuses are almost never used. The reason is that at currents of 25 or 50 amperes, which are common, the voltage drop across the fuse is sufficient to affect operation of the equipment. This fact demands that all such circuits be most carefully designed, installed, and worked around, so there is no chance whatever of a short circuit. The bilge or behind the panelling of a boat is not the place for burning insulation and melting copper.

Auxiliary Battery Systems

Most boats over 35 feet or so in length have auxiliary battery systems, and generators, separate from the engine system. Voltages are 12 or 32 and on the largest vessels, 110 volts. The auxiliary generator may

be run from one of the engines by a V-belt, or it may be a separate gasoline or diesel engine-driven unit. Conventional *dc* machines are most common, but some of the newer units have alternators and selenium rectifiers. Usually the negative side of the system is grounded, because the generators are built that way, but there are cases in which systems have been converted to positive ground to conform to the ground polarity used on the engine, or in the belief that this will give less electrolysis danger.

There should be no intermingling of engine and auxiliary electrical circuits, although the engine generating unit may be arranged to switch over and charge the propulsion engine batteries.

Although it is sometimes done as a matter of expedience, battery banks should not be partially tapped, to operate lower-voltage devices. This will overwork some of the batteries, leading to their possible failure earlier than the rest. Equipment put on a boat should be chosen for the full voltage of the bank from which it is to be operated.

Auxiliary battery systems are generally better engineered than engine systems, with switchboards and fuses for different branches, and very often reserve positions for future installations. Sometimes terminals will be reserved for radio equipment—however, it is quite common that the wire to these terminals is not heavy enough and will have to be replaced or ignored.

Even more care should be taken in working on auxiliary battery systems than in working on the engine batteries because of the danger of arcs. A high voltage arc will "draw" out quite a distance and may be difficult to extinguish before a lot of hardware has melted.

On any boat electrical system watch out for leakage current, which is indicative of insulation failure or a cross-ground connection. With everything aboard turned off, there should be no current flow from the battery—if there is, locate the source by disconnecting wires until flow stops, and correct the defect before doing anything else. Otherwise, there is danger of fire or electrolysis damage, a scourge which will be covered in detail later.

Alternating Current

A few years ago, *ac* on a boat was unheard of. But with more and more docks being equipped with shore power lines, and with the development of compact, efficient, quiet and reasonably priced *dc-to-ac* converters, it is becoming commonplace. The result is that many new boats are wired for *ac* as well as *dc*.

One simple arrangement is the installation of a converter unit which operates from 110-volt shore *ac*, changing it to the boat's normal voltage, such as 6, 12, or 32 volts, and rectifying it. This *dc*, is "floated across" the battery, to supply extra current and charge the batteries during "resting" periods.

A variation of this type of converter disconnects the batteries from the load and supplies low-voltage *ac* directly to the boat's lighting circuits. Naturally, *dc* devices cannot be used while the shore *ac* is in the boat lines.

Still other boats have two entirely separate lighting systems, one fitted with low-voltage *dc* fixtures, and the other having 110-volt *ac* lights and appliances. In fact, dual lighting fixtures for this kind of operation are often used.

But with these systems, leaving the dock means the end of such diversions as "hi-fi" and TV. For this reason some boats are coming around to generating their own *ac*.

Some have engine-driven alternators, but this requires operation of the engine to get electricity. The more popular means of getting alternating current is through use of a converter, operating from the boat's batteries.

There are two kinds. One, the rotary type, is simply a *dc* motor and an alternator on the same shaft. These are fairly efficient, and will handle any desired amount of power, but they are mechanically noisy, and without special filtering, cause electrical interference. On top of this, some of them require periodic lubrication; and brushes, commutators and slip rings all have to be kept in shape.

More recently developed, and becoming popular, is the vibrator-type converter. In these, an expendable chopper makes *ac* from battery current, and steps it up to 110 volts with a transformer. An example of this type of unit is the Cornell-Dubilier "Powercon," one series of which is engineered specifically for marine application, with capacity up to 375 VA.

Caution To Be Observed

Some conventional *ac* equipment can be operated from shore power, or from converters, on a boat.

[Continued on page 42]



Cornell-Dubilier Powercon converter supplying 110 V.A.C. household power from boat battery system to dictation machine.

AD LIBS

[from page 3]

heads. It would seem to me that the more progressive and businesslike type of service firm operator has recognized the efforts we are expending on behalf of all professional servicemen much more so than those servicemen who do not even deem it worthwhile to use professional letterheads. However, to the latter group, and to all those who at present still feel a little "put out" because of our magazine's larger size, may we suggest that they just keep reading it and see if they don't eventually agree that they are getting a better magazine than heretofore.

Moch Resigns From TESA

The Television Electronic Service Association of Chicagoland was established 8 years ago, largely through the efforts of Frank J. Moch who became its first President and who has held that position until recently when he resigned. In the meanwhile, Mr. Moch was very active in the formation of NATESA (National Alliance of Television & Electronic Service Associations) and he also assumed, and still retains, the presidency of that organization.

In the publicity release announcing Mr. Moch's relinquishment of his title with the local Chicago Servicemen's association he stated that as time passed the demands of the association work had become so overwhelming as to almost necessitate that the executive head devote his full time to it. We have noted that the same condition exists in several other parts of the country where the Presidents of

[Continued on page 8]

CHANNEL MASTER

Explodes a Spectacular Campaign of

NATIONAL CONSUMER MAGAZINE ADVERTISING

THE FIRST PROGRAM OF ITS KIND IN TV ANTENNA HISTORY

**2-Page Spreads . . . Full-Page Ads . . .
Full-Color Ads . . .**

reaching into millions of American homes on
the pages of these outstanding magazines:



CHANNEL MASTER REVOLUTIONIZES ANTENNA MERCHANDISING! With large-scale national advertising and traffic-building local promotions, Channel Master now places TV antennas on the same retail level as traffic appliances. It's actually a NEW WAY for you to sell antennas — and sell more of them. Climb aboard the Channel Master brandwagon and tie in with these profit-making promotions. Get details from your Channel Master distributor.

NEW MARKETS . . . NEW CUSTOMERS . . . FOR THESE 2 GREAT NEW ANTENNAS

the respective servicemen's associations have out of the goodness of their hearts and with complete sincerity, almost lost their own businesses in their efforts to coordinate the efforts of the associations which they headed.

It thus becomes obvious that for an association to be truly effective it must find a way or means of paying its top men, call them the Coordinators or Presidents, as you will, some fee to reimburse them for the services they are rendering when taking losses from their normal business occupation.

Tube Developments

Hardly a day passes wherein some engineer does not conceive of the need for some new type of electronic tube. Only a few years ago tube manufacturers and radio-TV receiver equipment designers agreed that the 680-odd tube types then available would suffice to meet any need in the then foreseeable future. In fact, there was a movement for a while to eliminate a great many tube types in the belief that many of those that were then available had already become obsolete.


Progress will not stand still and for that reason the idea of reducing the number of tube types in production was abandoned and from that day until this more and more new tubes have been conceived and put into production, and as this is written many other new ideas are in the drawing board stage.

Late last Fall General Electric announced the release of a tiny "Micro-Minature" Ceramic Triode for UHF television receivers. The new all-metal and ceramic tube, which is about

CHANNEL MASTER®

T-W

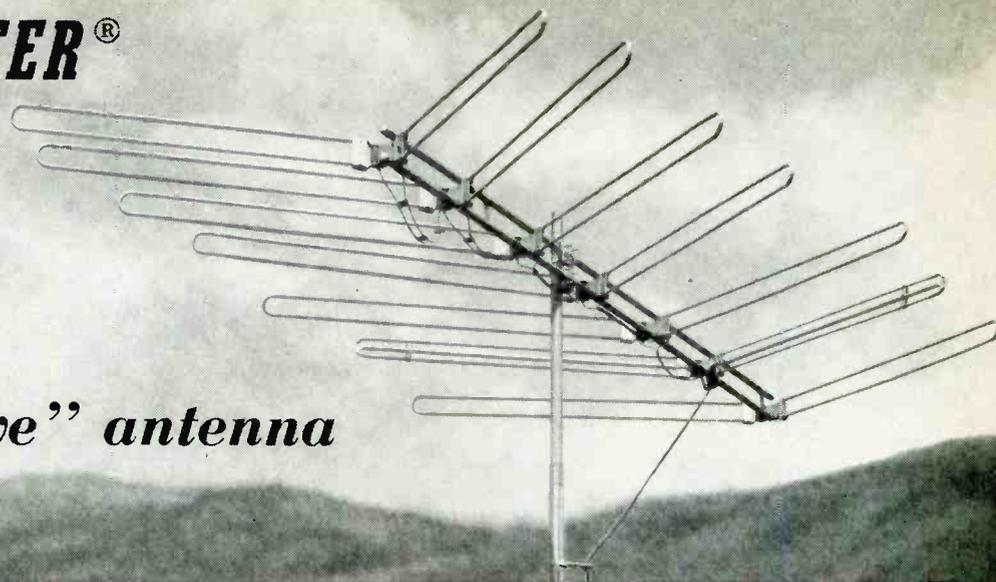the world's first "Travelling Wave" antenna






WHAT THE "TRAVELLING WAVE" PRINCIPLE MEANS—

- ideal phase relationships on all channels
- optimum impedance matching on all channels
- equal flow of current in all dipoles on all channels
- fullest use of transmitted energy on all channels

IN SHORT — FABULOUS PERFORMANCE
ON ALL CHANNELS

SENSATIONAL 3- AND 5- ELEMENT MODELS!

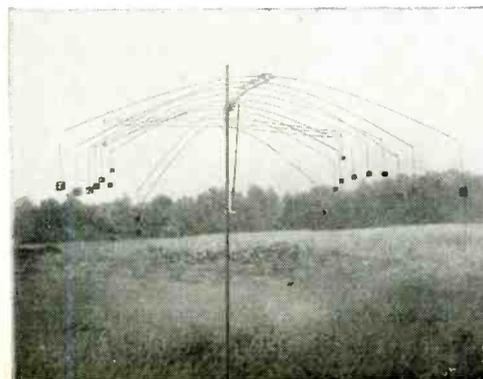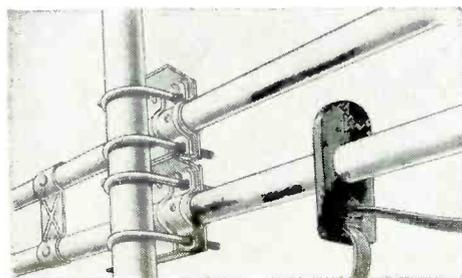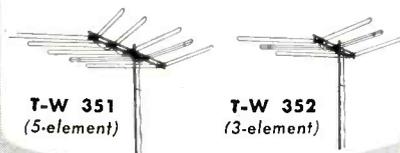Amazing T-W performance for suburban and near-fringe areas, too! Wonderfully compact and rugged!



revolutionary new design provides picture quality never before possible

After two years of research—a completely new kind of VHF antenna, operating on revolutionary new electronic principles. The T-W is Channel Master's greatest antenna achievement.

ALL THREE — IN ONE ALL-CHANNEL ANTENNA

1 HIGHEST GAINS

Most powerful all-channel antenna ever developed. A single-bay T-W 350 (7-element) actually **OUTPERFORMS—**



any wide-spaced 5-element Yagi on each low band channel.



any stacked 10-element Yagi on each high band channel.

2 TOP FRONT-TO-BACK RATIOS

Low Band:

Better than 10:1 on every channel. **HIGHER THAN ANY 10-ELEMENT SINGLE CHANNEL YAGI ON ALL CHANNELS!**

High Band:

From 5:1 to 12:1. **HIGHEST RATIOS OF ANY SINGLE ALL CHANNEL ANTENNA.**

3 GREATEST MECHANICAL STRENGTH

The most rugged antenna ever built. "Twin Truss" design amplifies the strength of every component. And new mechanical features add still greater durability . . .

"Twin Booms" . . . Two full-length crossarms—really rugged and rigid.

2 "Super-Nests" One heavy-duty mast clamp on each crossboom .
A TOTAL OF 4 U-BOLTS! Antenna cannot move.

"Line-Lok" Twinlead can't possibly tear away from terminals..

PROOF OF THE SUPERIORITY OF "TWIN-TRUSS" CONSTRUCTION

Look at the dramatic result when equal weights are hung on a T-W and a standard 10-element Yagi!


Write for complete technical literature,

© Trade Mark Reg. U.S. Pat. Off.

CHANNEL MASTER® "Showman"

new "Metro-Dyne" tuning
obsoletes

"Rabbit-Ears"

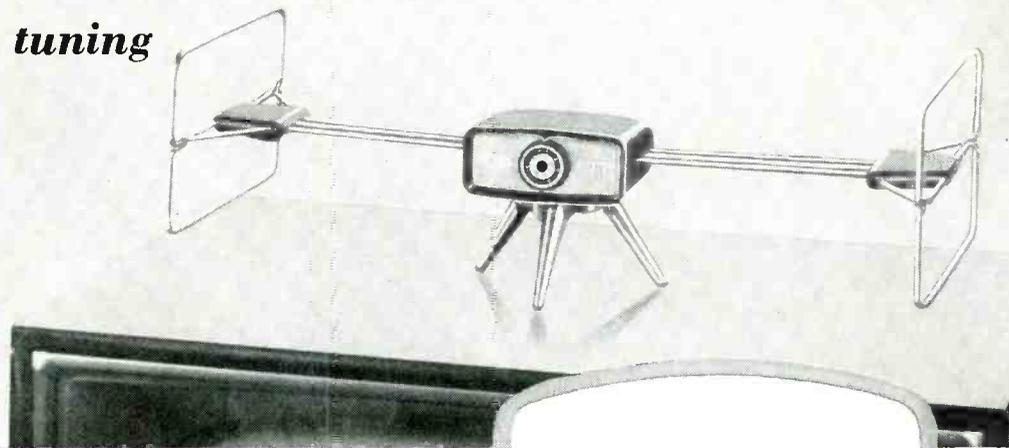

the first basic indoor antenna improvement in over 10 years

Channel Master sets an exciting new trend in TV antennas with the Showman. In appearance (so important in the sale of indoor antennas) the Showman is in a dazzling class by itself. Yet, it's a complex electronic instrument—the most powerful indoor antenna yet developed by modern science!

The SHOWMAN is perfect for color reception, tops for black-and-white. And, it provides excellent FM reception, too!

ACTUALLY TUNES OUT "GHOSTS" AND "SNOW"! MORE EFFECTIVE THAN ANY OTHER INDOOR ANTENNA!



With ordinary
indoor antennas

With the
Showman

Metropolitan areas, where indoor antennas are most frequently used, are often subject to the most severe "ghosting" problems. Only the SHOWMAN, with its sensational new Metro-Dyne tuning, can overcome this difficulty. You'll be amazed at the job it does on all kinds of interference. Test it for yourself! Demonstrate it for your customers!


Channel Master stands squarely behind every SHOWMAN you sell. An unconditional money-back guarantee assures your customer of complete satisfaction.

**UNCONDITIONAL
MONEY-BACK
GUARANTEE**

Available in three "decor designs"—
to blend with any setting.

Mahogany and Gold	Blond and Gold	Ebony and Silver
model no. 3900	model no. 3901	model no. 3902

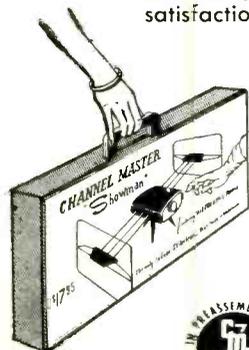"High fashion"
packaging.
Attractive,
convenient,
Ideal for
display.



CHANNEL MASTER CORP. ELLENVILLE, N. Y.
the world's largest manufacturer of television antennas and accessories

Copyright 1956, Channel Master Corp.


what makes the
"Showman" different?

FABULOUS "METRO-DYNE" TUNING!

The Metro-Dyne 12-Channel "Variable Inductance" Tuner

Ordinary switch-type antennas work by connecting various element into different combinations. METRO-DYNE tuning, on the other hand, is "variable inductance" tuning, using the same tuning principles as any TV set. It is the first broad band antenna which can be tuned to a specific channel so that it exhibits the band width characteristics of a single-channel Yagi. This selectivity cuts down tremendously on "electronic noise" and interference. A built-in auto transformer maintains a constant 300 ohm impedance match.

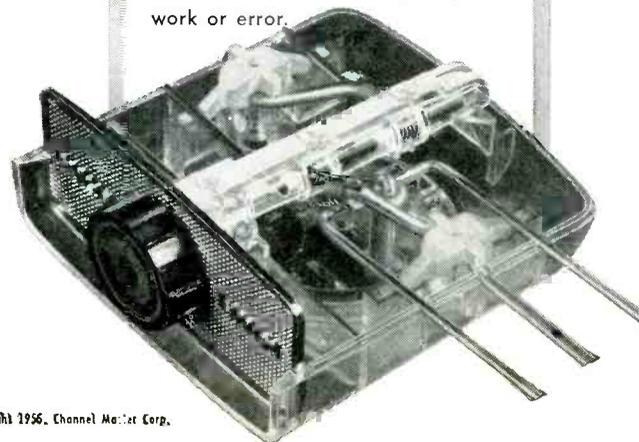EASY OPERATION: the Showman is calibrated by channels. Just turn it to the same channel number as the TV set. No arms to adjust; no guess-work or error.




$\frac{3}{8}$ " long and $\frac{5}{16}$ " in diameter, was given the type number 6BY4. This particular tube was rated to operate with a noise factor of approximately 8 db and a power gain approximating 15 db when operated at 900 mc.

As one can see by glancing at our front cover this month the 6BY4 tube features micro spacing of elements and a grid of approximately 1,000 turns per inch. The simplified design permitted a relatively low list price.

The particular tube under discussion is simply the forerunner of an entirely new engineering concept and line of tiny electronic tubes from diodes to complex multi-element tubes, all of which will have application in mobile and industrial communications equipment, airborne and mobile radar, industrial controls, etc. Because of its ruggedness this type of design permits further exploration in the Guided Missile program, but even more important is the present day application of the tube in UHF circuits. Because at present the FCC is becoming more and more conscious of the potential of UHF in television, (not that we agree with their philosophy) it is incumbent upon all developmental engineers to reinvestigate and continue their research into the development of components that will be required for combination UHF-VHF television transmission and reception usage.

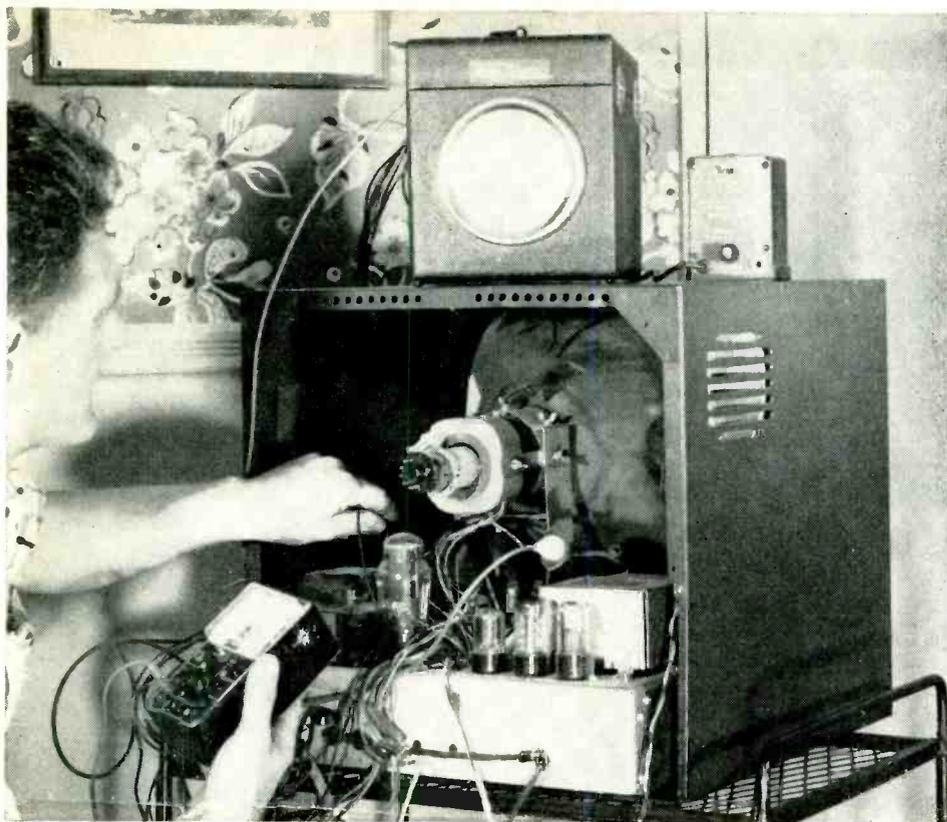It is said that history repeats itself. How true! Not very long ago the entire industry was trying to meet the demands for UHF tuners. Then UHF came upon bad days and it was only recently that a revitalization program became mandatory.



TROUBLE SHOOTING THE YOKE AND CRT



by B. Jarmalow

Chief Engineer Telematic Industries, Inc.

▶ Convenience of trouble shooting receiver with a CRT and yoke substitution tester is illustrated above, showing instruments being used.

Yoke Network

Since there are different stray capacitances existing from different points of the horizontal yoke windings to ground, a balancing capacitor is connected across the high side to offset this condition and prevent ringing. The latter takes the form of light and dark vertical bars at the extreme left of the screen and which diminish gradually towards the center.


Typical balancing capacitors for 70 degree yokes are 47, 56, and 68 $\mu\mu\text{f}$. 90 degree yokes use capacitors of the order of 100 $\mu\mu\text{f}$. They also use a higher capacitance to offset the greater stray capacitance resulting from the use of a yoke with a wider flare and greater inductance.

A replacement yoke must have a balancing capacitor with the same capacitance as the original, if ringing is to be prevented. The two resistors connected across the vertical windings (generally, 560 or 1 K ohms) are used to prevent the vertical windings from breaking into oscillation. Although the size of

these resistors is not critical, lower than normal ohmic values could result in reduced picture height.

Identifying Horizontal and Vertical Windings

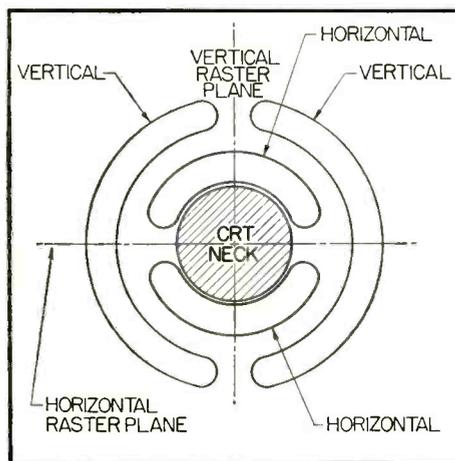When checking or replacing a yoke, the horizontal and vertical leads must be identified. One way of doing this is



▶ Fig. 4—Cross section of yoke and CRT neck showing windings only with relation to CRT neck.

by identifying the horizontal and vertical windings. The relative positions of both windings are the same for all yokes and these are shown in Fig. 4. The horizontal and vertical windings lie in the vertical and horizontal planes, respectively. This is done since the CRT electron beam is deflected at right angles to the magnetic fields which are produced by the windings. Note also, from Fig. 4, that the horizontal windings are closer to the CRT neck, so that they have the greater effect on the electron beam. In some yokes, however, such as for G. E., the vertical windings are placed closer to the CRT neck.

The illustration in Fig. 4 might very well represent the front-view of a yoke. A plastic spacer between each set of windings prevents shorting from the horizontal to the vertical windings. To identify the yoke windings, with the yoke back cover removed, refer to Fig. 5. The windings which are visible (inner ones) are the horizontal; the vertical windings are hidden by the plastic spacer. A schematic representa-

tion of the yoke is also shown in Fig. 5, so that the relationship between it and the rear view may be discussed.

The yoke has two terminal strips and each has four terminals. The terminals are either numbered on the strips or etched on the casing. The terminal numbers indicated in Fig. 5 are typical of most yokes. Compare these numbers with those shown on the schematic representation. Capacitor *CI*, across terminals 1 and 2, is the yoke balancing capacitor, which is connected across the horizontal winding on the high side. Many yokes have *CI* connected across terminals 3 and 7. Resistors *R1* and *R2*, the damping resistors, are connected across each vertical winding (terminals 4-5 and 6-8). The two horizontal windings are connected together by a jumper lead from terminal 2 to 7; the vertical windings are connected by the jumper lead from terminals 5 to 8.

The yoke lead which connects to capacitor *CI* is the horizontal winding high-side lead (terminal 1). The two leads which connect to resistors *R1* and

A thorough coverage of yoke construction, operation, and trouble shooting procedures. Chart is provided.

Part II

$R2$ are the vertical winding leads. The high and low sides of the yoke are difficult to determine, although terminal 4 is usually the high-side. The fourth remaining unidentified lead connects to the horizontal winding low side (terminal 3). Although set manufacturers do not follow any lead color code in particular, it will be found that many use blue (high side) and red (low side) for the horizontal and brown (high side) and green (low side) for the vertical.

Some yokes incorporate a resistor (about 1K) in series with the balancing capacitor. See $R3$ in Fig. 6A. Still other yokes omit the damping resistors, $R1$ and $R2$. In direct-drive yokes, resistors $R1$ and $R2$ are not used. Instead, a capacitor (about 270- $\mu\mu\text{f}$) is connected

between the horizontal and vertical windings ($C2$ in Fig. 6B) which minimizes yoke cross-talk. Cross-talk results in a moveable, dark horizontal hum bar(s) in the picture. Some direct-drive yokes, such as Motorola's have the vertical and horizontal windings jumped (terminals 3 and 8, in Fig. 6C) and capacitor $C2$ is not used.

Many of the yokes used in newer sets have five leads. The fifth lead connects to the center point of the horizontal winding, through a resistor, about 1K, as shown in Fig. 6D. This lead connects to the flyback transformer to provide better yoke balancing. To make the replacement yoke equivalent to the five-lead yoke, simply connect an additional lead to the horizontal winding center-tap. In most cases, the balancing ca-

pacitor, $C1$, will be included. Some manufacturers, such as Magnavox and Philco, leave these capacitors out. Sylvania and G.E., among others, connect the two horiz. windings in parallel (Fig. 6E), which eliminates the need for a balancing capacitor. This yoke operates in the same way as two horizontal windings connected in series. Consequently, a replacement yoke, which has two horizontal windings in series, may replace this yoke by connecting it to the same taps on the flyback. In this case, a balancing capacitor must be connected across the high side of the horizontal winding to eliminate ringing. Several different values may have to be tried.

Removing a "Frozen" Yoke


Yokes which are defective, or which have not been disturbed for a very long period of time, tend to adhere, or "freeze," to the CRT neck. They should not be forced, lest the CRT be broken. One way to loosen the yoke is to apply 115 volts *ac*, for about 10 seconds, across the horizontal windings after the yoke leads have all been disconnected. The yoke will become warm, and twisting it while pulling it away from the CRT should free it. If necessary, repeat this procedure several times.

Yoke Troubleshooting Chart

The chart on page 12 may be used as a reference to identify yoke troubles quickly. The causes and remedies of the various troubles are also indicated.

Using 5AXP4 for 24 or 27 inch CRTs

High voltages, of the order of 20 kv, are usually needed to operate 24 or 27 inch, 90-degree CRTs. When the 5AXP4 is used as a temporary substitute for such a tube, the high voltage may damage it permanently. Furthermore, it is necessary to properly load down the flyback circuit of the receiver. To satisfy these conditions, it has been found that a 150 megohm voltage divider network must be used, as shown in Fig. 7. Fifteen 10 meg, 1w, resistors form the divider. Mounting the resistors on a terminal board will make the divider more compact and reduce the chances of arcing between resistors. An alligator clip is attached to each end of the string

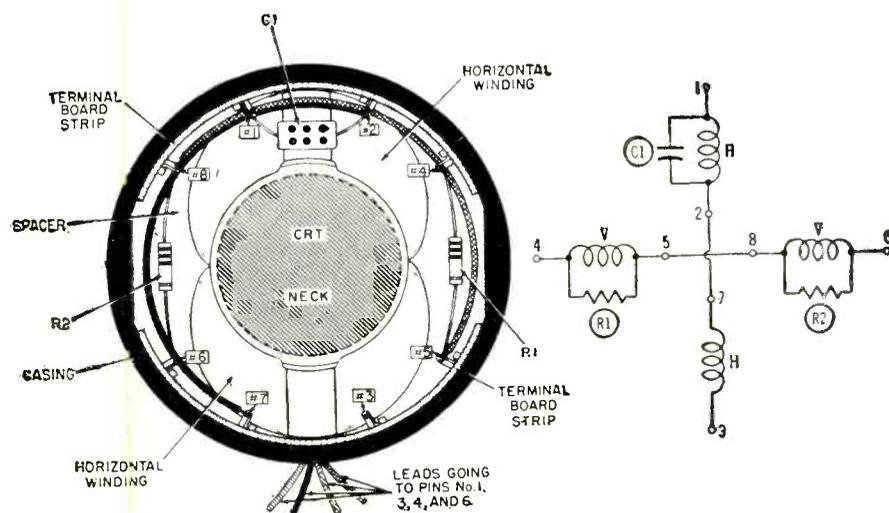

(Courtesy: Reprinted from Howard Sams "Servicing TV Sweep Systems," by J. Dines)

Fig. 5—Similar cross section as that of Fig. 4; in this case all parts are shown with corresponding schematic on the right.

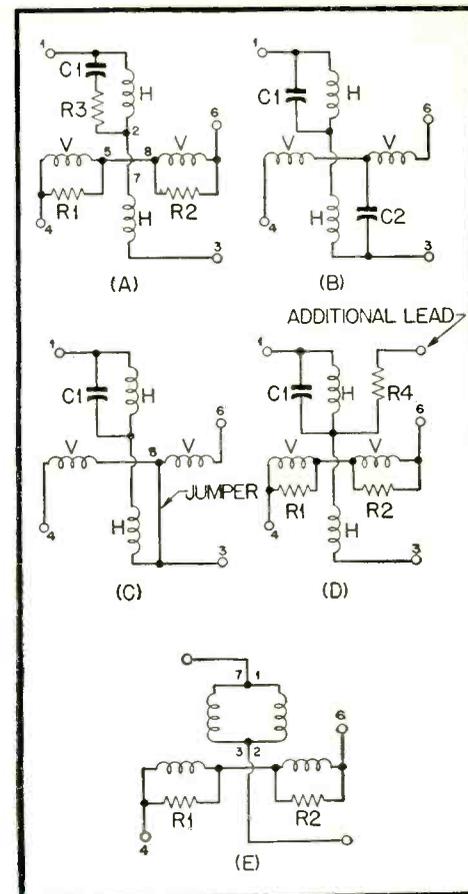


Fig. 6—Connections for different yoke types.

and a high voltage wire (with 2nd anode suction cap) is attached to the junction of the fifth and sixth resistors. The entire resistor string is then taped with high-voltage plastic, such as vinyl.

For a 24 inch CRT, whose high voltage requirement is less than that of a 27-inch CRT, alligator clips #1 and #2 are connected to the set *hv* lead and chassis ground, respectively. This de-

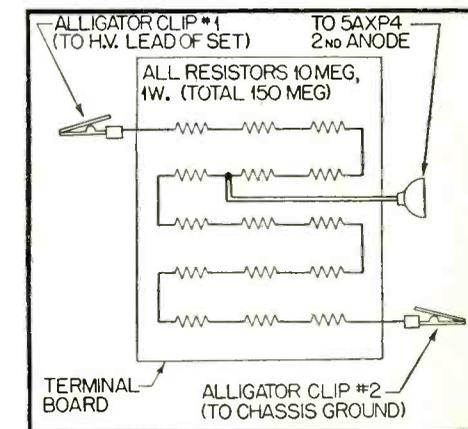


Fig. 7—Voltage divider for using 5AXP4 tube as a substitute for 24" and 27" high voltage tubes.

livers about 2/3 of the available voltage to the 5AXP4. For 27-inch CRTs, the connections to clips #1 and #2 are reversed. Now only about 1/3 of the available h-v from the set feeds the 5AXP4 2nd anode. In some cases, blooming (a poor focusing, low-brightness picture resulting from insufficient high-voltage) will occur, but this should not hinder the troubleshooting to any appreciable extent.

C.R.T. Troubles

A defective CRT is easy to detect where the fault is obvious, such as an open heater or a screen marred by an ion burn. Often, however, symptoms occur which, from both experience and reasoning, appear to be the result of trouble in the circuitry of the receiver, and do not seem to have any connection with the CRT at all.

When electrical leakages or shorts occur between elements of the CRT gun assembly, voltages are coupled from one circuit into another. This causes symptoms to appear which are similar to indications of defective blacking or bypass condensers or other components in the set. If the CRT seems to be in good condition, judging from the brightness and focus, one might start looking anywhere but there for trouble.

An example might be the case where 1st or 2nd anode voltages leak to the control grid, overcoming the normal bias and placing a positive potential thereon. In most sets the raster brightness would become excessive and irreducible to zero. In some older sets however, where the sync signal is taken from the CRT grid circuit, compression of the pulses would occur resulting in sync instability.

A CRT cathode-heater leak in some models would produce a 60-cycle hum pattern (horizontal half-shading) of the raster and in sets where the video is cathode fed to the CRT a loss of video could be expected.

In brightness control schemes where the CRT cathode is tied to the low voltage line and the heater is at ground, a cathode to heater short would knock out the front end and I.F. supply voltage, resulting in loss of both picture and sound.

Unless all indications definitely point

TROUBLE	CAUSE	REMEDY
Ringing	No capacitor (or improper value) across horizontal winding; yoke mismatch	<i>Insert proper yoke balancing capacitor; use properly matched yoke</i>
Keystoning and reduced height (trapezoid)	Short in vertical windings or damping resistors	<i>Replace damping resistors or yoke</i>
Keystoning and reduced width (trapezoid)	Short in horizontal windings or balancing capacitor	<i>Replace balancing capacitor or yoke</i>
Upside-down picture	Vertical winding leads reversed	<i>Reverse vertical winding leads</i>
Horizontally reversed picture	Horizontal winding leads reversed	<i>Reverse horizontal winding leads</i>
Arcing in yoke	Short in a winding	<i>Replace yoke</i>
Barrelling (bulging raster)	Conventional wound yoke used in place of cosine or cosine-squared yoke	<i>Use cosine, or cosine-squared yoke</i>
Pincushioning (caved-in raster)	Cosine, or cosine-squared yoke used in place of conventional yoke	<i>Use conventional-wound yoke, or install anti-pincushion magnets</i>
Tilted, off-center picture	Yoke not properly oriented	<i>Reorient relative yoke position; readjust set controls</i>
Neck shadow	Yoke not snug against picture tube; incorrect angle yoke used	<i>Position yoke snug against picture tube; use proper angle yoke</i>
Bow-tie pattern	Yoke wired incorrectly internally	<i>Replace yoke</i>
Horizontal foldover and/or horizontal nonlinearity	Improperly-matched, or defective yoke	<i>Replace with properly matched yoke</i>
Horizontal line (usually wavy)	Open in vertical winding or connecting leads	<i>Repair open circuit or replace yoke</i>
Vertical line (usually wavy) or no raster	Open in horizontal winding or connecting leads	<i>Repair open circuit or replace yoke</i>
No raster	Short in yoke	<i>Replace yoke</i>

▶ Trouble shooting chart that may be used for identifying yoke troubles.

elsewhere, a quick substitution of the CRT before proceeding further might

save needless probing and much valuable time. ■■



It is said that events occur in cycles. Let's begin early in July. I'm driving the family chariot, with my wife aboard, to Westchester to play with three golf sharks. Halfway to the club I notice that the ammeter does not indicate charge, nor does it indicate discharge when the engine is idling. However, the engine is running, so we continue on our way. I suspect that the generator is not functioning, but of even greater concern is the fear that perhaps this condition has existed long enough to run down the battery. Traffic isn't light and I have visions of the engine stopping when the car comes to a halt; there we'd sit, in the middle of the parkway with a hundred thousand cars lined up behind us.

So we get off the parkway at a point where I know a service station is not too far distant. I tell my tale of woe to a guy who is said to be the mechanic. He lifts the hood and asks to have the engine revved so that he can verify what I was watching for about 18 miles. The ammeter does not indicate charge or discharge, even with the unloaded engine turning over so rapidly that I am sure the fan belt will leave the pulley at any moment. The mechanic is now convinced that my eyesight is good.

He walks over to the front of the car, bangs the generator with the handle of a screwdriver and tells me to stop the engine. I suggest that maybe the battery is run down and that it may be a problem to start the engine again. "Don't worry about it," he says, so I don't. I turn off the ignition.

SPEAKS

by JOHN F. RIDER

"Dean of America's Radio Servicemen"

He removes the regulator box cover, peers at the relays and pushes one of them while I'm looking at the ammeter. It shows a momentary discharge. Now he says, "Start the engine." I try. A few weak grunts of the starter—then nothing. Now comes a profound comment from the genius. "The battery is dead" (as if I didn't know it). His next remark is even better. "I think you ruined the battery; you'll probably need a new one," says he. "You also need a new generator" is the inevitable follow-up.

After a few moments spent trying to recover my breath, I suggest that we substitute a charged battery for mine to get the engine started. He agrees and goes inside the shop. Shortly thereafter, he returns and calmly tells me he's fresh out of charged batteries, but he has one on the line that will be usable in about 30 minutes.

By this time I am 20 minutes late for my date and my wife is slightly perturbed, which is a polite way of saying it. But we wait, and finally the venture is crowned with success. He shunts the old battery with the charged one and the car is running, but the ammeter shows nothing. So I suggest that maybe it would be a good idea to measure the output from the generator to find out whether it is generating anything more than the wind from the ventilating fan. My mechanic friend doesn't think it is necessary; he insists that he knows his business. Anyway, he has no equipment for checking the voltage.

Now I'm one hour late for my date
[Continued on page 47]

WESTERN UNION "OPERATOR 25"



Raytheon Bonded Dealers are listed with Western Union "Operator 25". Potential customers needing TV or Radio repairs need only call Western Union by number and ask for "Operator 25". She'll give them the name and phone number of the Raytheon Bonded Dealer nearest the customer. More business for Bonded Dealers.

NATIONAL ADVERTISING



10 million readers a month will be urged to use Raytheon Bonded Electronic Technicians for their TV and Radio repairs. A powerful, exclusive advertising campaign designed solely to stimulate service business for Raytheon Bonded Dealers.

only **RAYTHEON** BONDED DEALERS
have all these business-building assets

RAYTHEON BONDED BACKING



The Bonded Electronic Technician guarantee on all radio and television repair work and parts is backed by a bond issue through one of America's largest insurance companies. This important support creates customer confidence and results in more customers — more profit and more prestige.

EXCLUSIVE RAYTHEON BONDED DEALER PROMOTION MATERIAL



Raytheon Bonded Dealers receive a registered Bond Certificate, Decals, ID Cards, Creed Displays — all designed to bring attention to their Bonded status. Special ads, mailing pieces and countless sales and shop aids are available exclusively to Raytheon Bonded Dealers.

Your sponsoring Raytheon Tube Distributor will be happy to discuss the Raytheon Bonding program with you. Better call him today.

RAYTHEON MANUFACTURING COMPANY

Receiving and Cathode Ray Tube Operations

Newton, Mass. • Chicago, Ill. • Atlanta, Ga. • Los Angeles, Calif.

Raytheon makes all these } Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes, Semiconductor Diodes, Power Rectifiers and Transistors, Nucleonic Tubes, Microwave Tubes



Excellence in Electronics

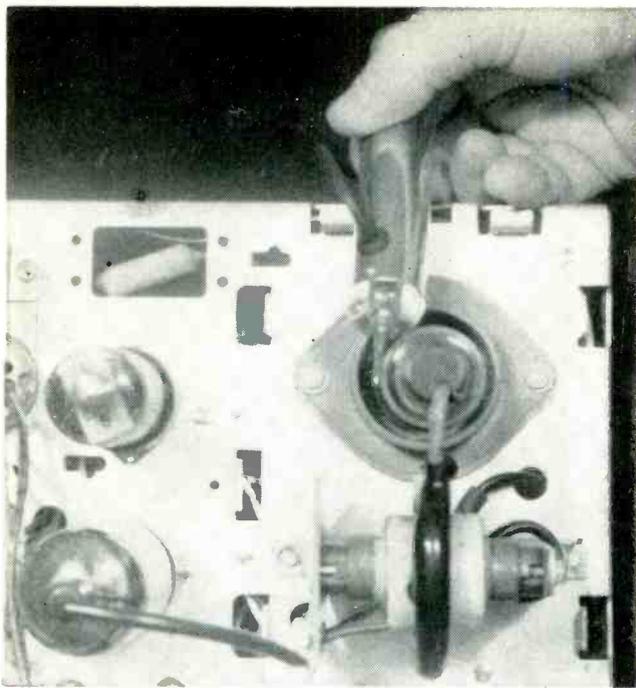


Fig. 1A—Checking level of flyback waveform with demodulator probe and voltmeter.

Construction, test applications, and limitations of the scope demodulator probe. Various examples and measurement techniques are discussed and illustrated.

Oscilloscope Probes

by Robert G. Middleton

Chief Field Engineer,
Simpson Electric Co.

MANUFACTURERS of oscilloscope probes receive many inquiries concerning the application of probes in radio and television service. Today, nearly all technicians have a complement of scope probes available, but the use of these probes is not always completely understood. It is the purpose of this article to outline the general techniques which find daily application at the bench.

Application of the Detector Or Demodulator Probe

Figure 1 shows applications of a detector probe of the demodulator type, which is used with an oscilloscope. This probe utilizes a voltage-doubler circuit arrangement, which effectively doubles the sensitivity of indication; the circuit is shown in Fig. 2.

A demodulator probe for scope use differs from a detector scope used with a VTVM in one essential respect: the demodulator probe is arranged to rectify and filter the *carrier* component of the signal, but passes the *modulation* component of the signal to the scope. A VTVM detector probe, on the other hand, rectifies and filters *both* the carrier component and the modulation

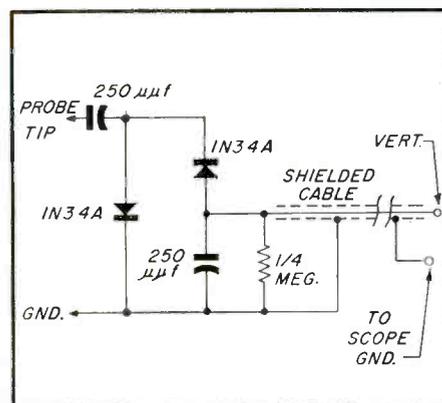


Fig. 2—Circuit arrangement of voltage-doubler demodulator probe.

component of the signal. The circuit arrangement of a VTVM detector probe is shown in Fig. 3.

A scope demodulator probe finds its most popular application in signal-tracing procedures. For example, with a fairly strong TV signal applied to the antenna-input terminals of a TV receiver, the demodulator probe can be used to check the progress of the signal from the output of the *rf* tuner up to the input of the picture detector. Thus, dead or weak *if* stages can be quickly localized.


There are some limitations in this signal-tracing procedure which should

be recognized. First, the amount of scope deflection which is obtained is not necessarily an accurate measure of the stage gain, because the probe loads the *if* circuit substantially, and the value of signal voltage delivered by the probe is sometimes less, and sometimes more, than the true signal voltage. The probe has appreciable input capacitance, which detunes the stage under test to some extent. If the detuning happens

to occur in a direction which peaks up the amplifier response, the apparent signal voltage is increased. But if the detuning occurs in a direction which broadens the over-all response, the apparent signal voltage is decreased.


Because of the detuning action of the probe, it is advisable to make a double check at each tube—one check at the grid terminal, and another check at the plate terminal. In a few cases, a satis-

Fig. 1B — Checking video signal level to picture tube with probe.

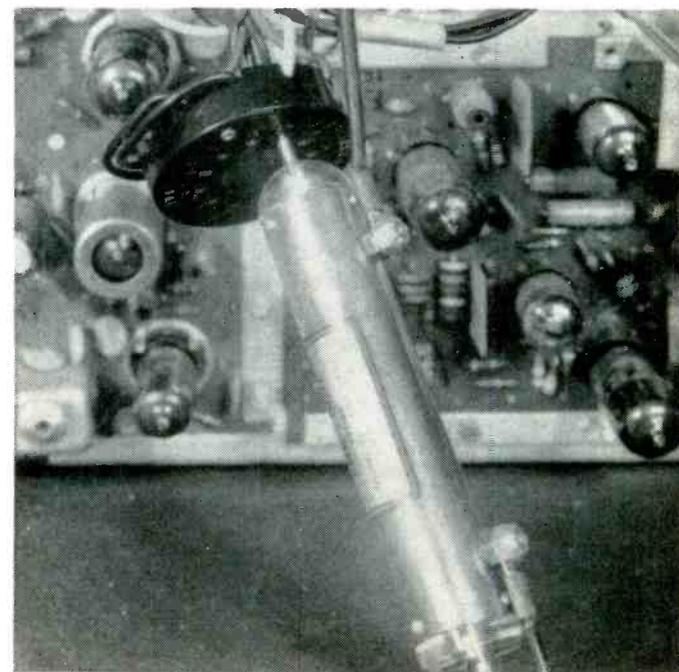

factory test may be obtained at the grid, whereas at the plate the application of the probe causes the amplifier to break into oscillation. Oscillation has the same appearance on the scope screen as a dead stage, but a VTVM at the output of the picture detector will show a large jump in *dc* voltage when the probe is applied. Experience is the best teacher in this regard, and makes it possible to obtain satisfactory preliminary tests with a signal-tracing probe and scope.

Another limitation in the signal-tracing procedure is the attenuation of the high-frequency component of video signal which is incurred in its passage through the probe. It will be noted that the vertical sync pulse comes through and is displayed in reasonably undistorted form on the scope screen. But the horizontal sync pulse is both attenuated and integrated, and appears as a low-level sawtooth waveform. For this rea-

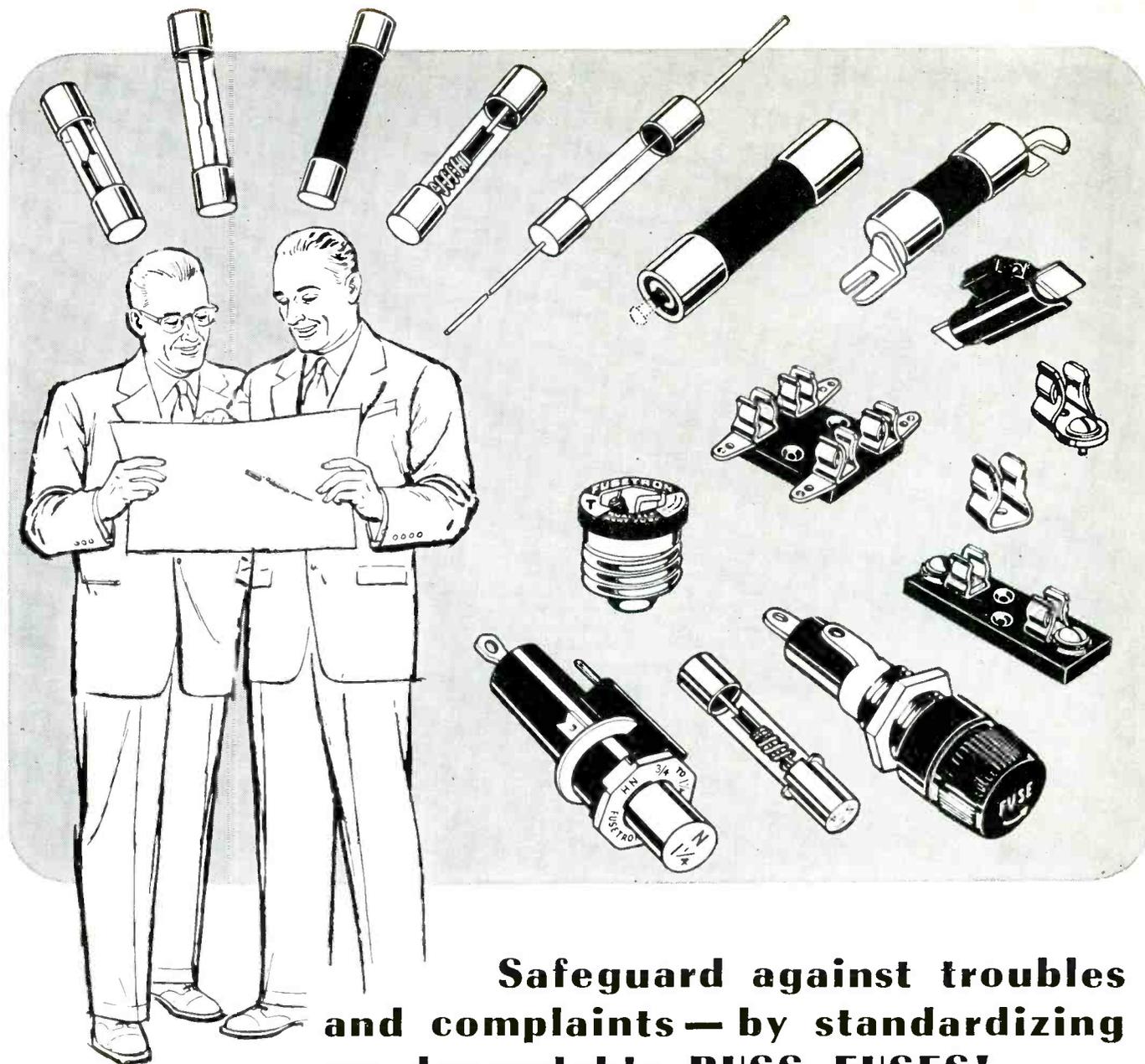

Safeguard against troubles and complaints — by standardizing on dependable **BUSS FUSES!**

BUSS fuses give you double protection against loss of customer goodwill because . . . BUSS fuses blow only to protect — never needlessly. To make sure of proper operation, BUSS fuses are tested in a sensitive electronic device that automatically rejects any fuse not correctly calibrated, properly constructed and right in all physical dimensions.

When you sell or install BUSS fuses . . . you are safeguarding the users of equipment against irritating, useless shutdowns due to faulty fuses blowing needlessly. And you are providing them with maximum protection against damage caused by electrical faults.

Most important, the dependability of BUSS fuses helps you avoid costly,

unnecessary callbacks. And the proper operation of BUSS fuses helps safeguard your reputation for quality and service.

Why settle for anything less than BUSS quality in fuses? The complete BUSS fuse line includes: standard types, dual-element (slow blowing), renewable and one-time types — in sizes from 1/500 amp. up . . . plus a companion line of fuse clips, blocks and holders.

For more information available on BUSS and Fusetron small dimension fuses and fuse-holders . . . Write for bulletin SFB.

BUSSMANN MFG. CO. (Div. of McGraw Electric Co.)
University at Jefferson, St. Louis 7, Mo.

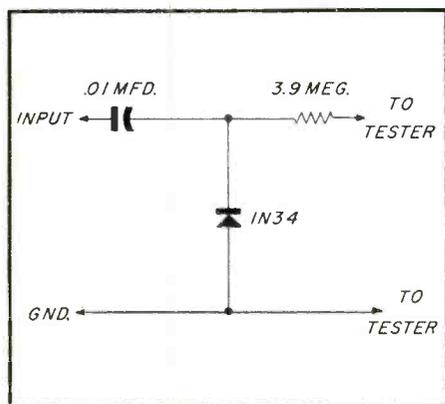


Fig. 3—Circuit arrangement of a typical VTVM detector probe.

son, signal-tracing procedures are accomplished to best advantage when the scope is deflected horizontally at a 60-cycle rate.

A more satisfactory method of signal-tracing is realized when the receiver is energized by the output from an AM or FM generator. The signal level is then under the operator's control, and the modulation frequency does not exceed 400 cycles, so that the maximum efficiency of the demodulator probe is realized. If an AM generator is utilized, the modulated *rf* output (at the channel frequency) is applied to the antenna-input terminals of the receiver, and the output level is advanced until

Makers of a complete line of fuses for home, farm, commercial, electronic, automotive and industrial use.

855

"COLOR TV TRAINING MANUAL"

THE NEW BOOK THAT PREPARES YOU FOR SUCCESSFUL COLOR TV SERVICING

Written by C. P. Oliphant and Verne M. Ray, of the Howard W. Sams editorial staff, in practical, down-to-earth language you can understand. Presented in 3 comprehensive sections. SECTION I: Principles of the Color TV System (includes chapters on Colorimetry; Requirements of the Composite Signal; Make-Up of the Color Picture Signal). SECTION II: Color Receiver Circuits (chapters on RF and IF Circuits; Video, Sync and Voltage Supply Circuits; Bandpass-Amplifier, Color-Sync and Color-Killer Circuits; Color Demodulation; Matrix and Output Circuits). SECTION III: Servicing the Color Receiver (chapters on Setting Up the Color Picture Tube; Aligning the Color Receiver; Trouble-Shooting; Test Equipment Required). Appendices include Equations, Vectors, Color-blocks, Colorplates, Glossary. A comprehensive training course that helps you qualify for Color TV servicing. 260 pages, 8½ x 11"; profusely illustrated.

Postpaid, only \$695

Sams books cover every phase of Electronics for the service technician, engineer, student or experimenter. Listed below are a few of the many valuable Sams books available at electronic parts distributors and leading book stores.

USE THIS ORDER FORM

COLOR TELEVISION TRAINING MANUAL \$695

- Analyzing and Tracing TV Circuits. Presents a new approach to TV servicing. 168 pages, 8½ x 11". \$3.00
- TV Service Data Handbook. Most frequently needed charts, tables and formulas required in TV servicing and installation. 112 pages, 5½ x 8½". \$1.50
- Principles & Practices of Telecasting Operations. Discusses equipment and techniques. Covers such subjects as: TV Cameras; Control Rooms; Fundamentals of Studio Lighting; Relay Systems; Maintenance Practices; Technical Production; etc. 600 pages; 6 x 9"; illustrated. \$7.95
- Radio Receiver Servicing. Covers the basic receiver types—gives time-saving hints for solving basic troubles, such as dead set, weak set, noisy set, etc. 192 pages; 5½ x 8½". \$2.50
- So You Want to Be a Ham. Tells you what you need to know about getting your license and acquiring equipment. Covers such subjects as: Conquering the Code; Getting Your Ticket; Going on the Air; Electronics as a Career; etc. 196 pages; 5½ x 8½"; illustrated. \$2.50
- Servicing TV Sweep Systems. Describes the operation, circuit function and circuit variations of vertical and horizontal sweep systems common to most TV receivers. Tells how to analyze circuits; trouble-shoots for you. 212 pages; 5½ x 8½"; illustrated. \$2.75
- The Recording and Reproduction of Sound. Widely used by Audio engineers, Hi-Fi enthusiasts, broadcasting stations and recording studios. Authoritative chapters cover: behavior of sound waves; basic recording methods; lateral disc recording; micro-groove recording; phono reproducers; microphones; home music systems; P.A. systems; amplifiers; tuners; etc. 810 pages; 6 x 9"; illustrated. \$7.95

HOW TO UNDERSTAND AND USE TV TEST INSTRUMENTS

- Completely revised and enlarged to include latest data on instruments used for Color TV Servicing. Covers use of VTVM's Signal Generators, Sweep Signal Generators, Scopes, Video Signal Generators, Field Intensity Meters and Voltage Calibrators. 208 pages, 8½ x 11". \$3.50
- Photofact Television Course. Gives a clear complete understanding of TV principles, operation, practice. Used by thousands of students. 208 pages, 8½ x 11". \$3.00
- Atomic Radiation, Detection and Measurement. Provides basic understanding of nuclear science and its applications. Thoroughly covers and illustrates circuitry and operation of the many types of detection devices. 200 pages; 5½ x 8½". \$3.00
- Basic Radio Manual. Provides all the basic facts on theory, definitions, components. Includes section devoted to actual projects that translate theory into practice. 248 pages; 8½ x 11"; illustrated. \$5.00
- Attenuators, Equalizers and Filters. Describes design, application and theory of operation of every type of Attenuator, Equalizer and Wave Filter. Covers all types of equalization and attenuation used in audio recording and reproducing systems, both professional and home-type. Includes chapters on Hi-Fi crossover networks. Provides time-saving charts which permit easy determination of component values required in designing equalizers and filters. Invaluable to audio technicians and engineers. 176 pages; 5½ x 8½"; fully illustrated. Deluxe hard binding \$4.00 Paper-bound edition \$2.75

There is an authoritative Sams book on virtually any Electronic subject in which you're interested. Check below for FREE Book List describing all Sams books.

Send Book List



Look for SAMS BOOKS on the "Book Tree" at your Parts Distributor

HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber today, or mail to Howard W. Sams & Co., Inc., Dept. 4-H6 2201 East 46th St., Indianapolis 5, Indiana.

Send books checked above. My (check) (money order) for \$..... is enclosed.

Name.....

Address.....

City..... Zone..... State.....

(outside U.S.A. priced slightly higher)

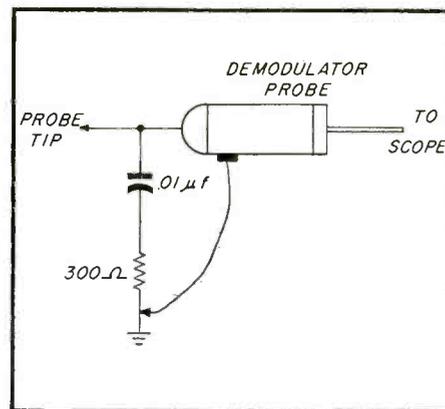


Fig. 4—Network across probe input permits response curve visualization on the scope screen.

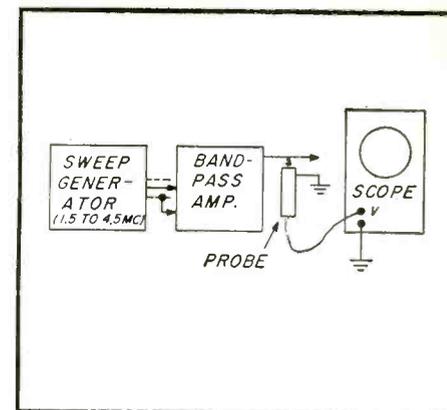


Fig. 5—Demodulator probe may be used to check the frequency response of bandpass amplifier.

an indication is obtained at the output of the *rf* tuner. Most AM generators utilize 400-cycle sine-wave modulation, so that the indication obtained on the scope screen is a sine waveform.

If an FM generator is utilized in the test, a sweep signal is applied to the antenna-input terminals of the receiver at channel frequency. The blanking control of the generator is turned on, to provide a zero-volt reference line. The *rf* output level is advanced, as before, until an indication is obtained with the probe at the output of the *rf* tuner. The display observed on the scope screen is that of the over-all frequency response of the circuits up to the point of test, wherever the probe may be applied in the *if* amplifier. Note, however, that the true response curve will not be obtained with the unaided probe, due to loading and detuning. To observe the true frequency response up to the test point, the input to the probe should be damped by a capacitor and resistor, as shown in Fig. 4.

A demodulator probe is also very useful when checking the frequency response of color-TV circuits, such as the chrominance bandpass amplifier, as shown in Fig. 5. In this application, the probe in combination with the scope will reveal the frequency response curve of the video-swept signal in the bandpass amplifier. Similar frequency response checks can be made of the color-difference detector circuits in a color-TV receiver.

A somewhat similar technique to determine the frequency response of a video amplifier is made possible by the demodulator probe. Fig. 6 shows how

the outputs from a sweep and a marker generator can be applied at the input of a video amplifier, with the demodulator probe at the output, to display the video-frequency response curve on a scope screen.

The preferred method of sweeping the video amplifier (illustrated in Fig. 6) is to apply an *if* sweep signal and an unmodulated *if* signal to the input of the picture detector, which beats a video-sweep voltage through the picture detector. A demodulator probe is applied at the output of the video amplifier, and the response curve is displayed on a scope. A puzzling characteristic of the display is that often a small notch only is observed at zero frequency, whereas when a video sweep signal is applied directly at the input of the video amplifier, a deep notch is seen at zero frequency. The reason that the notch is shallow for the set-up shown is that the demodulator probe cannot respond completely to the very sharp notch that is actually present.

The various frequency points along the video response curve can be determined by "walking" the curve along the base line of the scope. This is done by turning the AM generator dial in 0.5 or 1 *mc* steps, as shown in Fig. 7, which shows an example of how frequencies are determined accurately along the video response curve. At A is shown a video response curve in standard form, with the zero-frequency point at the end of the base line. If the dial of the instrument is rotated 2 *mc* to bring point "1" to the zero-frequency point, as shown at B, the frequency of point "1" in A is then 2 *mc*. Likewise,

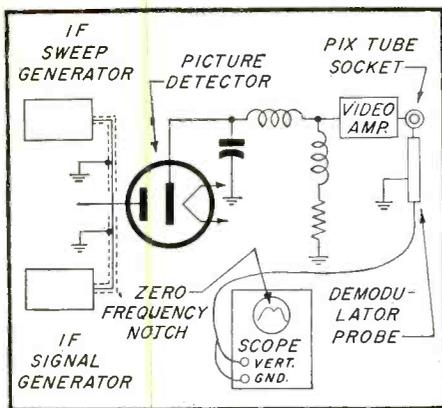


Fig. 6—Demodulator probe may be used to check frequency response curve of a video amplifier.

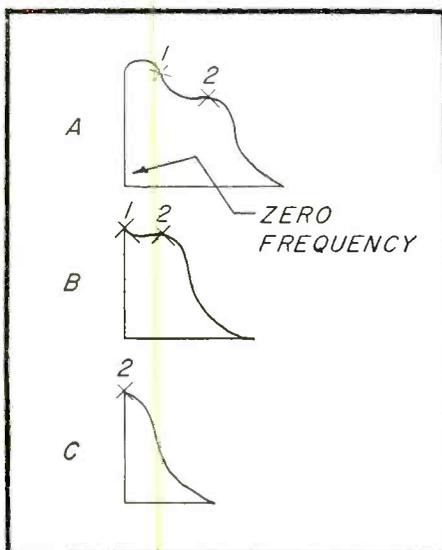


Fig. 7—Use of a video-frequency marker box is not necessary when "curve walking" technique is used to determine frequency points.

if the dial of the instrument is rotated 4 mc to bring point "2" to the zero-frequency point, as shown at C, the frequency of point "2" in A is 4 mc. This "trick" simplifies the marking problem in low-frequency signal circuits, and avoids the complication of external marker boxes. ■ ■


MOVING?

Please Mail Us Your Change of Address 5 Weeks Before Moving

Also include old address and code line, if possible. Thanks.

**SERVICE DEALER
and ELECTRONIC SERVICING**
67 West 44 St., New York 36, N. Y.

TUNG-SOL 1956 TECHNICAL DATA BOOKS

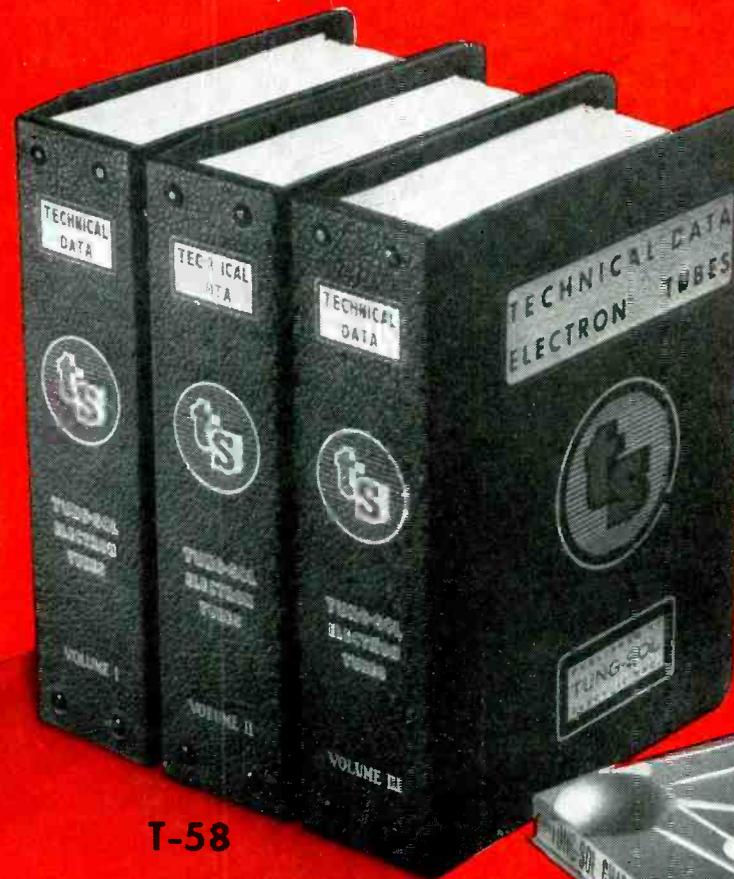

The new 1956 Tung-Sol Electron Tube Technical Data books are the most practical set of reference books in the entire industry. They contain all the information you need for everyday use. Clearly indexed and streamlined for fast reading, they open flat for rapid on-the-job reference. Ask your Tung-Sol supplier how you can get your set.

TUNG-SOL ELECTRIC INC.
Newark 4, N. J.

Sales Offices: Atlanta, Columbus, Culver City, Dallas, Denver, Detroit, Melrose Park (Ill.), Newark, Seattle.




T-31




T-70

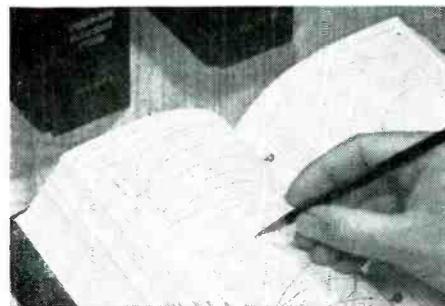ALL THE INFORMATION... AT YOUR FINGER TIPS!



T-58 1250 pages— 1000 tube types.

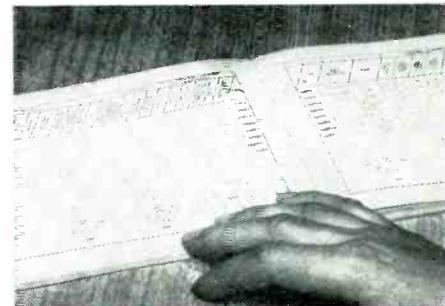

T-70 More than 250 pages of data on CR tubes, receiving and special purpose tubes and dial lamps.



T-31 Over 350 blueprint base diagrams for 1400 tube types.





by R. D. HERSHEY

If it's worth Engineers' time . . .

. . . It's worth Engineered Cable

Belden

INTERCOMMUNICATING
AND
SOUND SYSTEM CABLES

Indoor-outdoor, phones
or speakers—there is a
Belden engineered cable
to meet your needs for
a permanent, trouble-
free installation.

"Items from the
Complete Belden Line"

*The TV station, the systems for
music, paging, and intercom-
munication in the new
Prudential Insurance Company
of America's Building in Chicago
have been—wired by Belden.*

Belden

WIREMAKER FOR INDUSTRY
SINCE 1902
CHICAGO

8-8

Magnet Wire • Lead and Fixture Wire • Power Supply Cords, Cord Sets and Portable Cord • Aircraft Wires
Welding Cable • Electrical Household Cords • Electronic Wires • Automotive Wire and Cable

THE field of electronics has made many tremendous strides in the past few years. We have seen television grow from an idea to one of the major industries of the United States. Along with television, the electronic service profession also has grown to major proportions and YOU, Mr. Service Technician, are a member of this important profession. Through self-improvement, attendance to lectures and schools and practicing good business ethics, YOU have raised the electronic service profession to its rightful place with the other leading professions in your community. With this rapid growth in the field of electronics and the development of new and more complex electronic devices, the electronic service profession has become a field only for highly skilled service technicians. There is no longer a place for just plain service men, tube jerkers or tinkerers. The electronic equipment of today and tomorrow requires—yes, demands the highest technically trained men to provide the necessary maintenance.

For the service profession to maintain and further its position, each service technician must become a well trained service engineer. He must be completely familiar with the use and application of test equipment and, of extreme importance, know how to interpret what the test equipment tells him. . . . He must be thoroughly familiar with all basic circuitry as used in radio and television receivers. . . . He must be able to apply this basic knowledge to

EDITORIAL

Service Manager
Receiver Division
Philco Corporation

new circuitry thereby gaining an understanding of its operation and purpose. . . . He must learn new servicing and trouble shooting techniques and be adept at using these newly learned skills.

How does a service technician achieve this goal? Not by being satisfied with his present knowledge and ability. Not by assuming that theory and application of circuit theory is unnecessary and a waste of time. Not by blaming a manufacturer for a component failure which he is incapable of locating and repairing; and certainly not by procrastinating as to when would be the right time to start furthering his education. I have many times heard the remark, "I can't take time during the day to study any new circuits or try new service procedures. I've got to keep on the job or we can't make money." I can agree with part of this statement. . . . "I've got to keep on the job or we can't make money." This is true. A service technician must take full advantage of his time since "time" is one of the major commodities which he is selling. However, has this man ever stopped to realize that by understanding the new circuitry which he is attempting to trouble shoot or by learning new and advanced servicing procedures he may very well double his daily work output thus making his time far more valuable?

A few minutes spent every day in furthering your technical knowledge and skill can result in hours of saved
[Continued on page 33]

THOUSANDS OF SERVICE DEALERS

**SATISFY CUSTOMERS
SAVE REPEAT CALLS**

MAKE MONEY EVERY DAY with B&K



DYNA-QUIK MODEL 500
DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER

Tests over 95%

OF ALL POPULAR TV TUBES*— IN SECONDS

It's easy and profitable to check all the tubes in a TV set with DYNA-QUIK—on every service call. Cuts servicing time. Creates more on-the-spot tube sales. Saves repeat calls, protects service guarantee.

DYNA-QUIK 500 measures true dynamic mutual conductance, completely checks tubes with laboratory accuracy under actual operating conditions right in the home.

Tests each tube for shorts, grid emission, gas content, leakage, dynamic mutual conductance and life expectancy. One switch tests everything. No roll charts. No multiple switching. Makes complete tube test in as little as 12 seconds. Large 4½-inch plastic meter shows tube condition on "Good-Bad" scale or in micromhos on scales calibrated 0-6,000 and 0-18,000. Used in home or shop, DYNA-QUIK is a proved money-maker!

*Including new 600 mil series tubes.


NET **\$109⁹⁵**

Dyna-Quik 500. Easily portable in luggage-style carrying case. Size: 15¼ x 14¼ x 5¼ in. Weighs only 12 lbs. Has 7-pin and 9-pin straighteners on panel.

DELUXE—PORTABLE

CRT MODEL 400

Tests and repairs
TV Picture Tubes

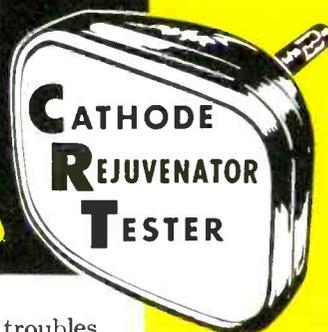

**CATHODE
REJUVENATOR
TESTER**

Quickly spots and corrects picture tube troubles right in the home, without removing tube from set. Restores emission, stops leakage, repairs interelement shorts and open circuits. Life test checks gas content and predicts remaining useful life. Grid cut-off reading indicates picture quality customer can expect. Eliminates tube transportation, cuts service-operating costs. Also saves money on TV set trade-in reconditioning. Earns dollars in minutes—pays for itself over and over again.

NET **\$54⁹⁵**

Deluxe CRT 400. With 4½-in. plastic meter. Weighs only 5 lbs. Luggage style carrying case. Size: 11 x 7½ x 5".


Also available in economy model CRT 200 with 3-in. meter at \$39.95 net.

Proved in Use by Servicemen Everywhere.

See your B & K Distributor or send for facts on "Profitable TV Servicing in the Home" and Informative Bulletins 500-104-D.



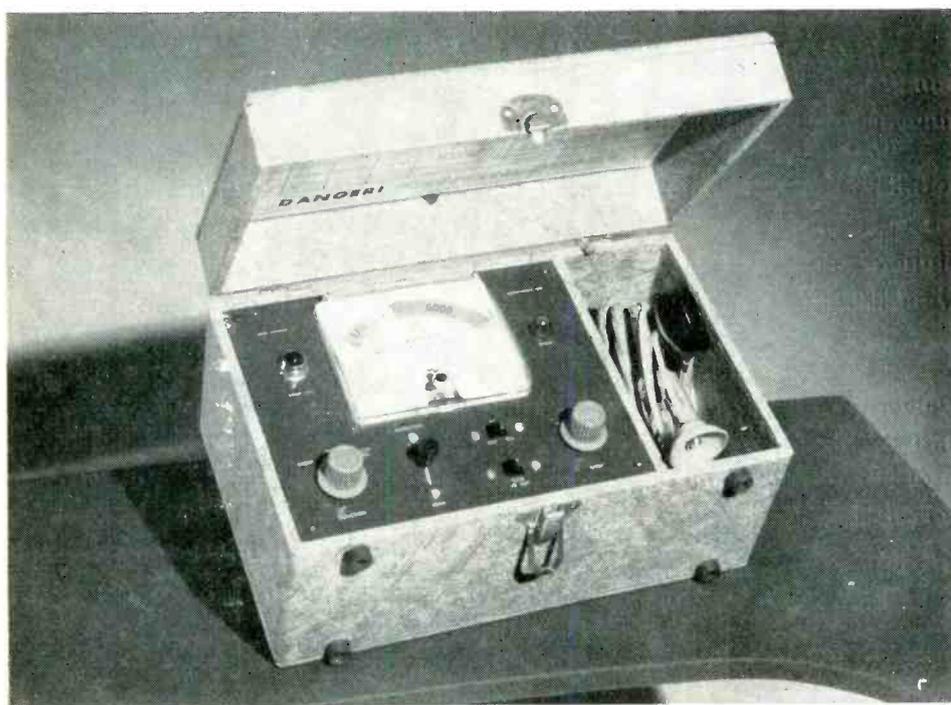B & K MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois



▶ Heathkit Model CC-1 Cathode Ray Tube Tester

10 megohms, provides for magnified visual inspection of the gun aperture and enables examination of the relative condition of the phosphor coating on the screen. Completely self-contained in an attractive portable cabinet, it is *ac* operated and supplies all necessary voltages to the cathode ray tube being tested.

Theory of Operation

Referring to *Fig. 1*, the power transformer supplies *ac* voltages of 6.3, 450 and 1200 to the cathode ray tube being tested.

With the instrument connected to the tube to be tested, turned on and the FUNCTION switch in the SHORT position, the SHORT switch may be rotated. This applies 450 volts *ac* in series with the short test circuit between any element and all other elements. If a short exists between any two elements, the neon SHORT indicator will glow. Even a leakage path of as much as 10 megohms resistance will give a strong indication.

In the TEST position, the FUNCTION switch opens the short test circuit, ties the control grid to the cathode, applies 450 volts *ac* between these elements and all other elements and 1200 volts *ac* to the high voltage anode through current-limiting resistors and the SLIDE-TO-TEST switch. The SLIDE-TO-TEST switch must be activated to the right to complete the high voltage circuit for BEAM and SHADOW-GRAPH tests. This requires the simultaneous use of both hands and is designed as a safety factor to eliminate the possibility of inadvertent contact with the high voltage.

A Modern Cathode Ray Tube Checker

by J. FRANK BRUMBAUGH

Project Engineer
Heath Company
Benton Harbor, Michigan

Description and operation of a cathode ray tube tester with many unusual features.

THE service man has had available for some time a large assortment of cathode ray tube testers, adapters, rejuvenators, et al, ranging from the inexpensive—and ineffectual “gimmick” to the more elaborately designed—and priced—CRT “do-all.” Many of these have fallen by the wayside and as many more have risen to take their place. The Heath-

kit Model CC-1 Cathode Ray Tube Tester is a recently developed instrument designed expressly to assist the television service man in rapidly locating weak or defective “picture” tubes, and is invaluable in convincing the customer of the advisability of purchasing a new tube when this is necessary.

In order to save much of the service man’s valuable time, the instrument has been so designed as to allow testing of any cathode ray tube which the attached socket will fit, as long as deflection is electromagnetic, and all tests may be made without removing the tube from the set or the carton. Only enough warm-up time is necessary for the heater in the cathode ray tube to reach operating temperature, approximately 90 seconds or less, and all testing may easily be accomplished in less than a minute. The Model CC-1 provides an overall quality test, a beam current test, indicates shorted elements and leakages to in excess of

The BEAM-EMISSION switch, when activated to the BEAM position, inserts the meter in series with the supply voltage and the meter indicates the level of total cathode current.

In the EMISSION position, the BEAM-EMISSION switch removes the 1200 volts *ac* from the high voltage anode circuit and again inserts the meter in series with the supply voltage. The meter now indicates the level of cathode current *minus* the beam current.

In the SHADOW-GRAPH position, the FUNCTION switch applies 450 volts *ac* between the cathode-control grid and all other elements, shorts out a portion of the current limiting resistance, and applies 1200 volts *ac* to the high voltage anode through the SLIDE-TO-TEST switch. (The meter is not connected into the circuit for this test and observation of the face of the tube is required.) With the FUNCTION switch held in the SHADOW-GRAPH

SERVICE DEALER




and **ELECTRONIC SERVICING**

NEW SEMI-CONDUCTORS

SUB-MINIATURE RELAY RECTIFIER

A new versatile sub-miniature selenium relay rectifier to energize *dc* relay coils is now in production at International Rectifier Corporation. This new Unit, type 60-9267, is a full wave center tap rectifier and may be used either as a center tap full wave rectifier or as a half wave and "back wave" rectifier combination. The unit is rated for 66 volts maximum *ac* input and will deliver 22 *ma dc* as center tap or 11 *ma dc* as a half wave rectifier.

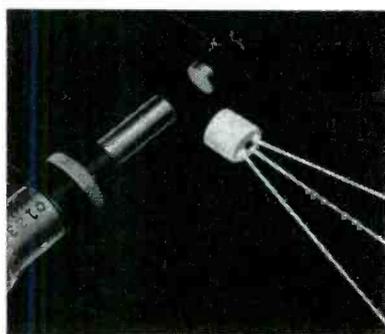
(Check 807 on inquiry card for more information)



G.E. SILICON RECTIFIERS

The General Electric Company has announced two new silicon rectifiers designed to meet stringent military requirements. The new rectifiers, designated as 1N537 and 1N538, are rated at a maximum *dc* output current of 250 milliamperes at 150°C. The devices may be designed into circuits for outputs of up to 750 milliamperes where lower temperatures are encountered. Maximum leakage over the temperature range is 0.5 milliamperes.

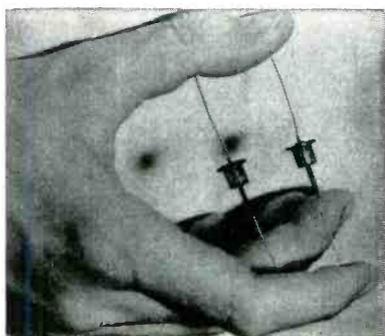
(Check 802 on inquiry card for more information)



CBS-HYTRON POWER RECTIFIERS

A new series of silicon power rectifiers, CBS types 1N503 through 1N526, featuring an exceptionally large handling capacity for their size has been developed by CBS-Hytron. These new silicon rectifiers are capable of operating with extremely high reverse voltages and accompanying low reverse currents. This feature, together with a very low forward voltage drop, enables the rectifier to deliver large power to the load with relatively little dissipation.


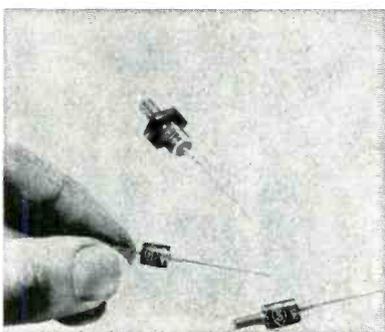
(Check 804 on inquiry card for more information)



G.E. SILICON RECTIFIER

The new G.E. high current silicon rectifier, designated 7J 15, is a compact device occupying a total volume of 1.0 cubic inches including mounting stud. It is capable of operating at 50 amperes forward current per cell at 200 volts, peak inverse voltage. Depending on whether the rectifier is connected in a single phase, three phase or six phase circuit, maximum forward current is rated at 50 amperes, 46 amperes, or 35 amperes, respectively.

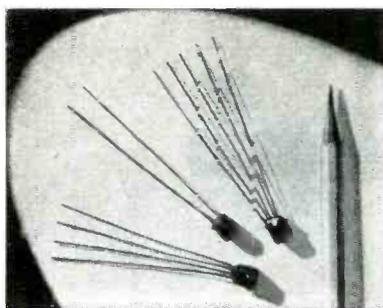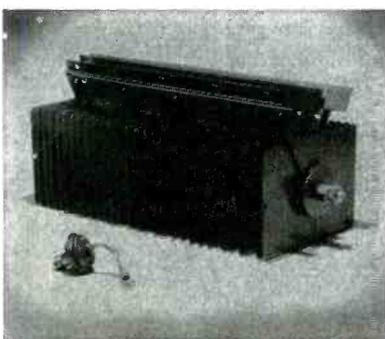(Check 809 on inquiry card for more information)



MINIATURE RECTIFIERS


A new line of sub-miniature selenium rectifiers has been announced by Bradley Laboratories of New Haven, Conn. These rectifiers will find wide application in portable and airborne communications and other electronic equipment where space and weight limitations are major factors. Important features are low forward drop, low reverse leakage, uniformity of electrical characteristics and the ability to perform as rated at high ambient temperatures.

(Check 805 on inquiry card for more information)

SILICON POWER DIODES

The International Rectifier silicon power diodes are rated for 300 *ma dc* rectified output current when mounted by leads in free air at ambient temperatures up to 100°C. The rectifying barrier of this silicon diode is formed by the fused junction principle, which results in excellent electrical and mechanical stability. This junction is hermetically sealed in an all-welded, shockproof housing with pigtail leads firmly welded to the terminals.

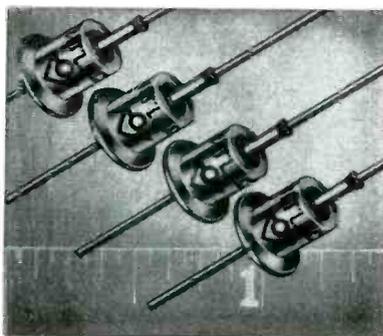
(Check 803 on inquiry card for more information)



R.C.A. JUNCTION TRANSISTOR

The RCA 2N175—a hermetically sealed, germanium alloy junction transistor of the p-n-p type—is designed especially for use in the preamplifier or input stages of transistorized audio equipment operating from extremely small input signals. Because of its extremely low noise factor of 6 *db* maximum, and its freedom from microphonism and hum, the 2N175 makes possible higher small-signal sensitivity of transistorized audio equipment.

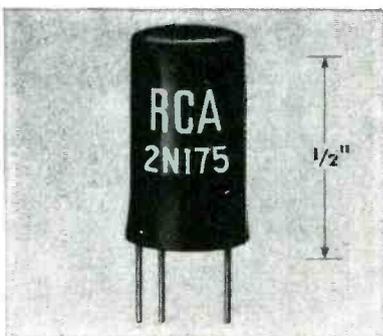
(Check 808 on inquiry card for more information)



POWER RECTIFIER STACKS

A line of germanium rectifier power stacks, with a new design which results in better heat dissipation while combining light weight and superior rigidity, has been developed by Federal Telephone and Radio Co. The new Federal germanium stacks are smaller than previous designs by an estimated one-third, as a result of improved convection and cooling. A special base plate design makes the stacks mechanically interchangeable with types now on the market.

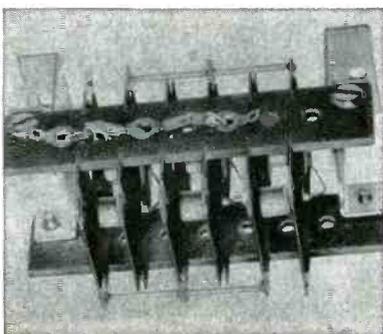
(Check 806 on inquiry card for more information)





DC CONVERTER TRANSISTOR

The Amperex Electronic Corporation has announced the addition of a new switching-type transistor to their extensive semi-conductor line. Designated as type OC76, the new transistor was developed particularly for *dc* converter applications. Some of the important uses of the new OC76 as a *dc* converter will be in high voltage supplies of portable and mobile radio sets, transistorized photo-flash units and Geiger counters.

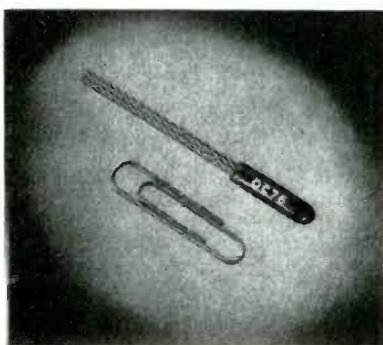(Check 801 on inquiry card for more information)



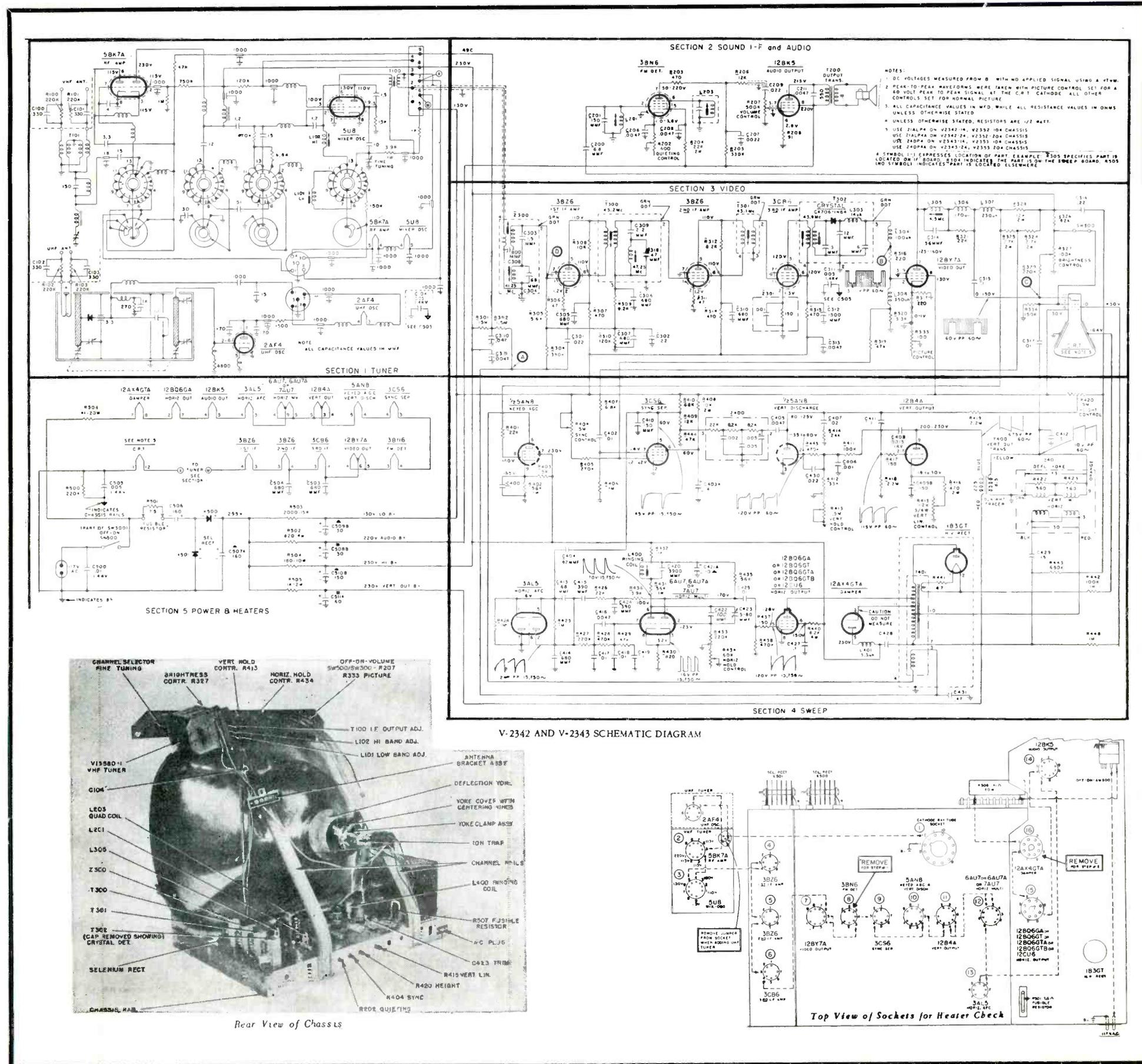

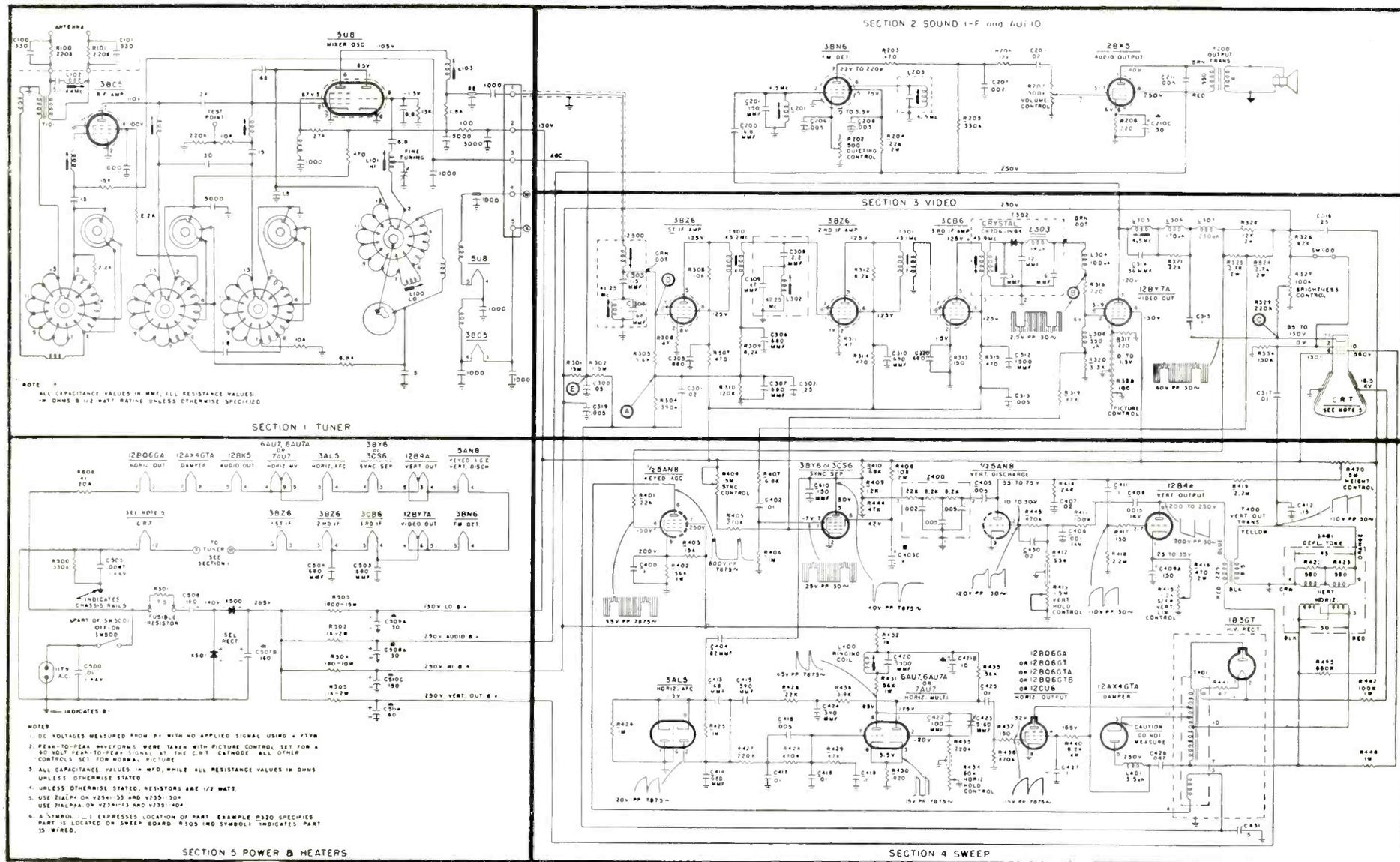

Schematic Diagram for Chassis Assemblies
V-2341, 35, V-2341-45, V-2351-304 and V-2351-404

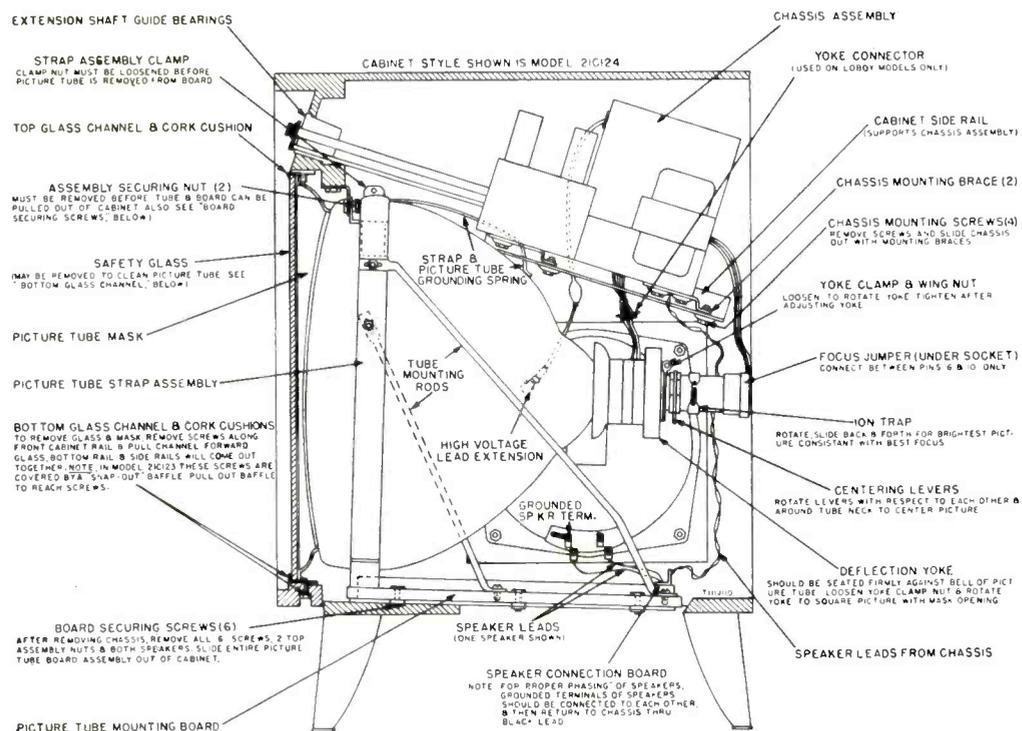


FIGURE 1. CUT-AWAY VIEW OF LOBOY MODELS

INSTALLATION ADJUSTMENTS

GENERAL: These receivers are shipped from the factory with the picture tube installed and all controls pre-adjusted for normal operation. It is necessary, therefore, to merely plug in the receiver and, where required, connect it to a suitable antenna system. The various operating controls should then be checked for proper operation.

On the rear of the receiver immediately above the antenna terminals is located a local-distant switch. This switch is normally left in the distant position except in cases of severe cross modulation caused by one or more strong stations interfering with the signal received. It may be necessary, therefore, to switch from distant to local in these areas.

As shown in figure 1, the chassis of Models 21C123 and 21C124 is mounted above the picture tube. The chassis, in all other models in the "S" line, is mounted beneath the picture tube, as shown in Figure 2.

If it becomes evident that one or more of the preset controls are out of adjustment due to handling, adjust the necessary controls according to the following information.

It is recommended that the receiver be permitted to operate for at least 15 minutes before the final raster adjustments are made. Refer to Figures 1 and 2.

ION TRAP:

Power should not be applied to the receiver for any great length of time without the ion trap being properly adjusted. Rotate and slide the ion trap on the tube neck for position of maximum picture brightness consistent with best focus. As maximum brightness with trap is approached, re-adjust the brightness control as required, to keep picture brightness moderate during trap adjustment.

YOKE POSITION (Picture Tilt):

Loosen yoke clamp wing nut and push deflection yoke to seat firmly against bell of picture tube. Rotate yoke and clamp to correct picture tilt (squaring of picture within picture mask). Tighten wing nut after adjustment.

PICTURE CENTERING:

A lever and ring assembly used for picture centering, rests behind the deflection yoke. Move the levers toward or away from each other until picture is centered within picture mask. The centering assembly should rest up against rear of yoke clamp.

FOCUS:

On the base of the picture tube is located a focus jumper. This jumper should be placed between picture tube pins 6 and 10 and the ion trap should be adjusted for best focus per above.

HEIGHT & VERTICAL LINEARITY:

These controls (R210 & R214), see Fig. 2, should be adjusted simultaneously to provide proper picture height consistent with good vertical linearity. The final adjustment should extend the picture approximately 1/8 inch beyond the mask limits.

REMOVAL AND REPLACEMENT OF PICTURE TUBE (LOBOY MODELS)

If it becomes necessary to remove the picture tube, adhere to the following procedure. Refer to Figure 1.

1. Disconnect and remove speakers.
2. Disconnect chassis speaker leads, picture tube socket, yoke connector and high voltage anode connector.
3. Remove front control knobs and four chassis mounting screws.
4. Slide out chassis, together with both mounting braces.

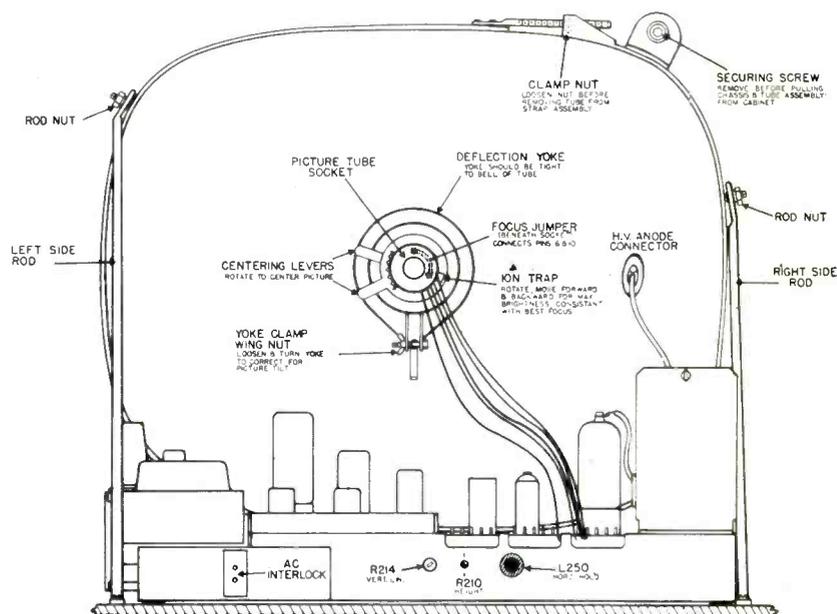


FIGURE 2. REAR VIEW, PICTURE TUBE AND CHASSIS BOARD ASSEMBLY

5. Loosen and remove both securing nuts above picture tube assembly.
6. Remove six screws arranged along edge of picture tube mounting board and slide entire tube assembly from cabinet. Remove yoke, centering assembly and ion trap, loosen clamp nut and remove tube.

When replacing tube, reverse above procedure. Be sure to "phase" speakers properly according to note in Figure 2, or according to label affixed to cabinet.

To clean picture tube without removing it:-

1. Remove screws arranged along cabinet front rail. (For Model 21C123, first remove "snap-out" baffle.)
2. Pull out bottom glass channel and glass. Mask and side rails will also come out, leaving tube face exposed.

REMOVAL AND REPLACEMENT OF PICTURE TUBE (STANDARD MODELS)

- Refer to Figure 2 during this procedure.
1. Remove knobs. Disconnect and remove speaker.
 2. Remove six screws arranged along edges of board assembly.
 3. Remove securing screw atop tube assembly.
 4. Remove entire tube and chassis board assembly.
 5. Disconnect high voltage lead and picture tube socket. Remove ion trap, centering assembly, and yoke.
 6. Loosen clamp nut and remove tube.

To clean picture tube, use LOBOY procedure above, or remove entire chassis and tube assembly board.

NOTE: When replacing chassis on braces or board after removal for service work, do not tighten chassis screws more than necessary. Excessive tightening of screws may damage bottom chassis screw clip projections.

CAUTION: DO NOT REMOVE 7A77 HORIZONTAL OSCILLATOR WITH SET TURNED ON. DAMAGE TO 6BQ6 TUBE WILL RESULT. BEFORE REPLACING 6BQ6, FIRST CHECK 7A77 TO PREVENT DAMAGE TO NEW TUBE.


HORIZONTAL PHASE BALANCE ADJUSTMENT:
This is not considered an installation adjustment but should be performed whenever the horizontal phase detector, oscillator or output tubes are changed. Use barely visible signal.
1. Turn L250 horizontal hold control counter-

clockwise so that picture is out of sync by 8 bars using VTVM, set R251 on top of chassis, Figure 11, so that voltage at Test Point VI reads -.5 volt. (Maintain 8 bar condition by additional adjustment of L250).
2. Turn L250 clockwise until picture just pulls in and then continue knob rotation 45 degrees further clockwise. Check lock-in stability on normal signal.

SOUTH RIVER CHIMNEY MOUNTS

In keeping with South River Metal Products Co.'s policy of manufacturing products that permit maximum safety when working in precarious positions, they have recently redesigned the entire SNAP-IN line of chimney mounts and wall brackets. A specially designed "U" bolt is now used with all SNAP-IN antenna mountings which permits one hand spintite fastening. The installer inserts the special U bolts instead of the customary nuts and screws.

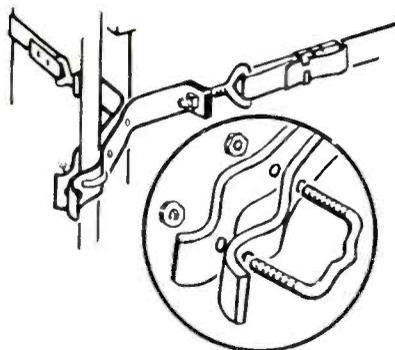(Check 816 on inquiry card for more information)



R-COLUMBIA COUPLER

In line with the trend to "do-it-yourself" departments in radio and television stores, R-Columbia Products Co. Inc., has developed a new two set coupler that can be sold by the Service Dealer. Available in three models, HK 1 for normal signal gain with normal interference rejection; HK 2 for exceptional signal gain with normal interference rejection; HK 3 for maximum interference rejection with normal signal gain. It can be installed on the antenna mast.


(Check 818 on inquiry card for more information)



TACO TRAPPERS

Technical Appliance Corporation, in announcing their new Stay-Lok assembly, stated that Taco Trappers and Super Trappers were now available to the trade in two designs. The original models employing the tension booster design are continued in the line, being supplemented by Models 2880, 2885 and 2890 which utilize the new element design. With these new models elements are automatically locked in without using any tools.

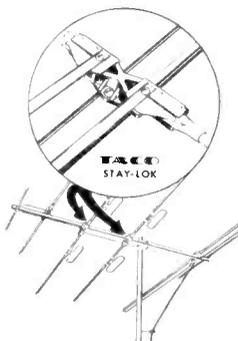
(Check 811 on inquiry card for more information)



JERSEY SPECIALTY COLORED WIRE

Jersey Specialty has announced to the trade that they are now in production on all colors—300 ohm twin lead television wire (red-white-blue-green-pink-yellow-gold-silver-brown-clear). Installers can now match the outside color paint on homes or can match woodwork, wallpaper or even the rug on the floor. It even brightens the appearance of the room in place of the usual brown twinex. The color price is the same as for the brown twinex.

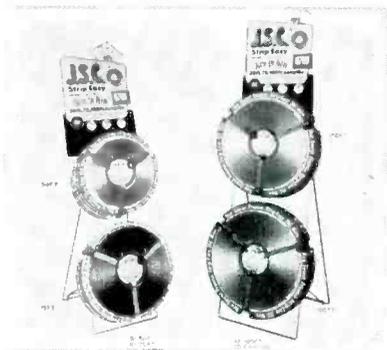
(Check 814 on inquiry card for more information)



BAKER "YUG"

A new 5' tower has been announced by the Baker Manufacturing Co., as an answer to the dealer's desire to eliminate guy wires on antenna installations up to 20' above the roof. It resembles, but is much larger than the successful 3' tower introduced previously which permits antenna mountings up to 12' without guys. Both towers are now nicknamed YUGS, a letter reversal of the word *guy*. The absence of guys means safer, faster roof installations.

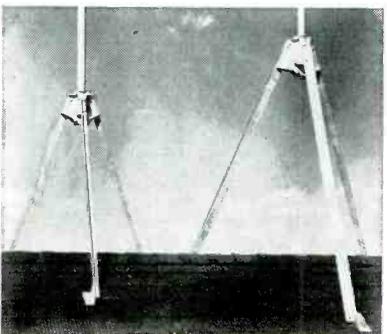(Check 815 on inquiry card for more information)



SERVICE DEALER




and **ELECTRONIC SERVICING**

NEW ANTENNAS

CHANNEL MASTER FILTER

Introduction of a completely re-designed model of its UHF-VHF inter-action filter, the "Ultra-Tie," has been announced by Channel Master Corp. The filter joins together VHF and UHF antennas of all types for use with a single transmission line to the set. The "New Ultra-Tie" performs this function with leads of any length. Transmission wires between the two antennas and the filter need not be cut to a specifically prescribed measurement.

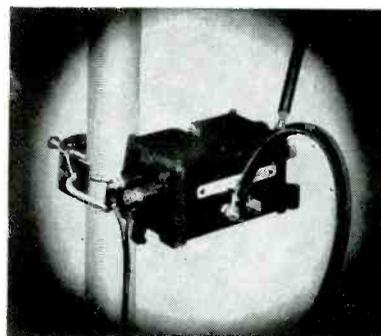
(Check 817 on inquiry card for more information)



TELCO ANTENNA

"Switch-O-Matic" is the name of a new high gain indoor TV antenna just developed by Telco Electronics Mfg. Co. It's a refinement on the basic "rabbit ears" style and said to provide new sensitivity on all viewing channels from 2 to 83. The "Telco Golden Switch-O-Matic" has two features that give it unusual power—six-phase tuning and a slide adjustment. The six-phase switch on the antenna's base provides improved reception.

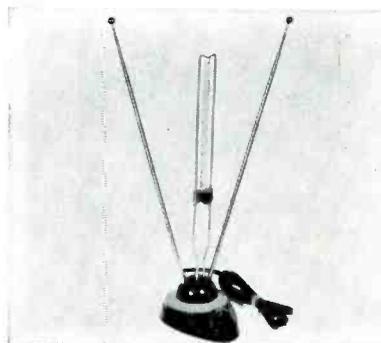(Check 813 on inquiry card for more information)



DYNAMIC ELECTRONICS ACCESSORIES

Dynamic Electronic's complete new line of accessories in the tentenna series for fm-uhf, vhf and color TV are to be sold through electronic parts jobbers and distributors as service aids to improve reception where problems exist even when the receiver is operating to the accepted standards of its manufacturer. In such cases reception can be improved by using a properly designed accessory.


(Check 812 on inquiry card for more information)



WELCO ZEE-X

The Welco Mfg. Co., of Burlington, Iowa, has recently presented the Zee-X Model Z-4 television antenna which is said to exhibit exceptional low and high band antenna response patterns. Welco's arrangement of its exclusive Zee-X elements offers an efficient Direction System—full half-wave director action on both VHF bands, the low channels up to 6 and the high channels from 7 to 13. This permits excellent VHF reception.

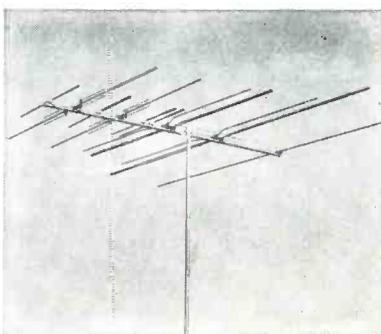(Check 819 on inquiry card for more information)



Discussion and analysis of the various types of detectors used in color TV receivers. Several circuits are illustrated.

COLOR DETECTORS

by BOB DARGAN and
SAM MARSHALL

From a forthcoming book entitled
"Fundamentals of Color Television"

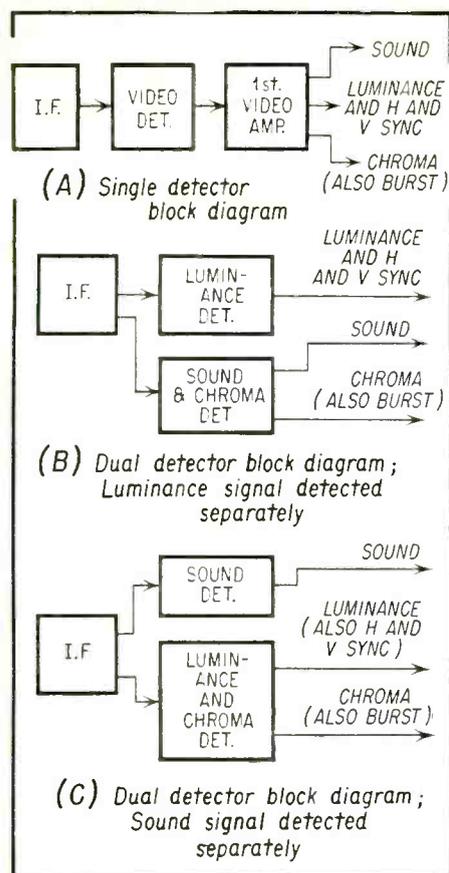


Fig. 1—Block diagrams of various types of color detector circuits.

zontal and vertical sync signals. If we were to consider the horizontal and vertical sync signals separately we would have six signals. These signals have the frequency ranges shown below.

Signal Takeoff Systems

Three signal takeoff systems are employed for extracting the individual signals listed above. These systems are shown in rather simple block diagram form in Fig. 1 and were introduced to the reader originally at the beginning of this chapter (see *May Service Dealer & Electronic Servicing* Pg. 16). Referring to Fig. 1:

FIVE different signals are contained in the composite video signal presented to the video detection circuit. These signals are the chroma, luminance, color burst, sound, and hori-

Figure 1 (A) shows a block diagram of a Single Video Detector type where the entire composite video *if* signal is demodulated in a single detector. The output of this detector feeds the first video amplifier tube following which the various signals are processed in succeeding circuits.

Figure 1 (B) shows a block diagram of a Dual Detector type where the luminance signal is demodulated in one detector and the combined sound and chroma signals are demodulated in another detector.

Figure 1 (C) shows a block diagram of a Dual Detector type where the combined luminance and chroma signals are demodulated in one detector, and the sound signal in another detector.

It will be observed, from a study of Fig. 1, that in all cases the color burst signal is fed along with the chroma signal following detection. In subsequent circuits these two signals are separated from each other. It will also be observed that following detection, the sync signal which contains the hori-

Signal	Center Frequency	Upper Limit	Lower Limit
Chroma	3.58 mc	4.08 mc	2.08 mc* or 3.08 mc
Luminance	—	3.2 mc**	0
Color Burst	3.579545 mc***	—	—
Sound	4.5 mc	4.5 mc + 25 kc	4.5 mc - 25 kc
Horizontal Sync Pulse	15.734 cps	—	—
Vertical Sync Pulse	59.94 cps	—	—

*For I/Q receivers the lower limit is 2.08 mc., and for R-Y/B-Y receivers the lower limit is 3.08 mc.

**The response at the higher frequencies falls off considerably as compared to the lower video frequencies. The luminance signal must be sufficiently attenuated at 3.58 mc. to reduce dot pattern and the resultant moiré effect.

***Consists of 8 to 11 cycles on the back porch of each horizontal sync pulse.

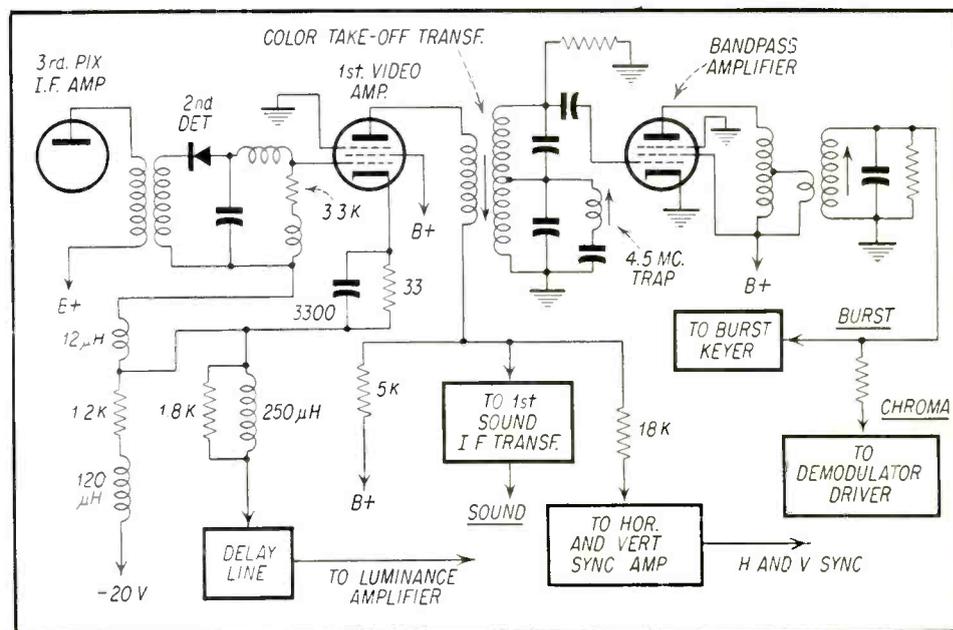


Fig. 2—Partial schematic of receiver using a single detector for the composite video I.F. signal. Separation of the various component signals is effected by employing selective circuits as shown in the above diagram.

zontal and vertical sync information is fed along with the luminance signal. These two sets of signals are duly processed in subsequent circuits wherever separation is required.

Single Detector Analysis

In Fig. 2 we observe a simplified partial schematic of the RCA 21CT661-4 color TV receiver showing how the signal from the 3rd *if* is fed into the crystal 2nd detector. The demodulated output of this detector is then fed into a video amplifier tube where the process of extracting the various signals enumerated above are begun.

Notice that the luminance signal is taken off the cathode circuit of the video amplifier. The chroma signal is taken off the secondary of a Color-Takeoff transformer. The opposite end of the primary of this transformer, which is maintained at an *rf* potential above ground by a 5K resistor, provides the take-off point for the sound and sync (horizontal and vertical) signals. Separation of the sync signals from the sound signal is effected by means of a tuned 1st *if* sound transformer. The sound signal is subsequently removed from the sync signals in the sync amplifier circuits.


Dual Detector-Separate Luminance Detector Analysis

A circuit employing dual-detection in which one of the detectors is used for luminance and the other for chroma and sound is shown in Fig. 3 which is a partial schematic of the Emerson Model C502A color receiver. Notice that the plate of the 4th *if* tube feeds parallel signals to T-7 and T-6. T-7 is a transformer which picks off the *if* signal preparatory to demodulation of the signal by crystal XTAL-2, the luminance detector. The output of this detector provides the signals for the luminance section as well as the horizontal and vertical sync amplifier.

In T-6 we observe a transformer which provides the sound takeoff signal across terminal No. 3 and ground. The tap on the transformer (terminal No. 5) connects through a 6.8K resistor and a 3K control for variable sound rejection of the system. From terminal No. 2 we obtain the chroma signal


Video speed Servicing Systems Vol. 2

is now available

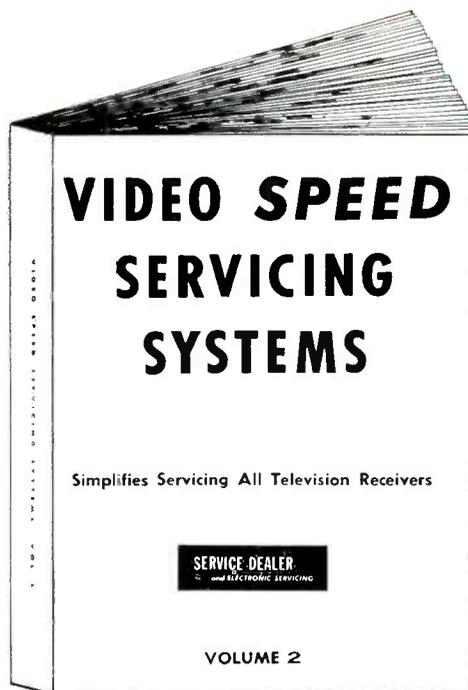

- Volume 2 of VSSS is completely new and does not cover any of the items published in volume 1.
- Volume 2 of VSSS contains most of the data sheets published since May 1953 plus several hundred new data sheets that have not been published heretofore and which will not be published anywhere else.
- Although published as a hard paper cover bound volume each page in VSSS Vol. 2 is marked so the pages can be inserted into a loose leaf ring binder or into our VSSS Vol. 1 cloth-covered ring-binder edition.

Order Your Copy Today

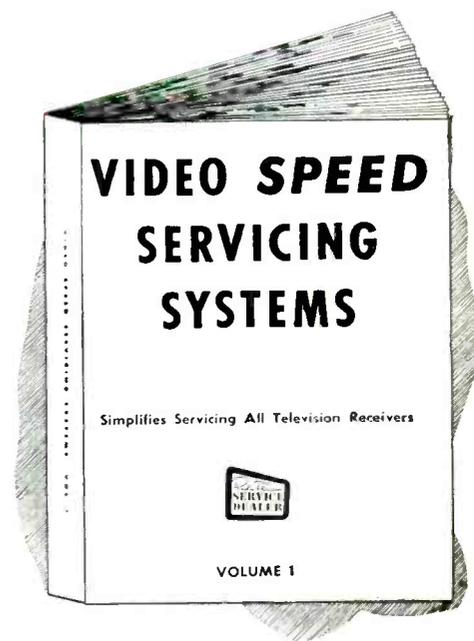

VOL. 1 and VOL. 2 VSSS Paper Bound Editions
\$2.95 Postpaid.

Vol. 1 Ring-Binder Edition **\$4.95** Postpaid.

- Each edition of Video Speed Servicing Systems is guaranteed to simplify servicing all TV sets. Each edition contains over 600 service items covering the most-serviced TV models now in use. All leading manufacturers' lines and models are covered.
- The VSSS data sheet for any particular TV set maker's model or chassis number gives: 1—the section of the set affected; 2—the symptom; 3—the cause of complaint; 4—the solution.

CUT OUT AND MAIL

COWAN PUBLISHING CORP., 67 WEST 44TH STREET, NEW YORK 36, N. Y.

Please send me postpaid Video speed Servicing Systems Vol. 1 in Paper Bound Edition for \$2.95

" " " " " " " " " Vol. 1 in Hard Cover Ring-Binder Edition for \$4.95

" " " " " " " " " Vol. 2 in Paper Bound Edition for \$2.95

My Check for \$ is enclosed. (If you reside in New York City add 3% to cover city sales tax.)

Name

Address


City Zone State

What About Color TV?

There has been much talk about Color TV — and about whether or not available TV equipment is suitable for Color TV reception. Whatever other conditions prevail — one thing is certain . . .

ALL **B-T LABS** TV PRODUCTS ARE ENGINEERED for COLOR

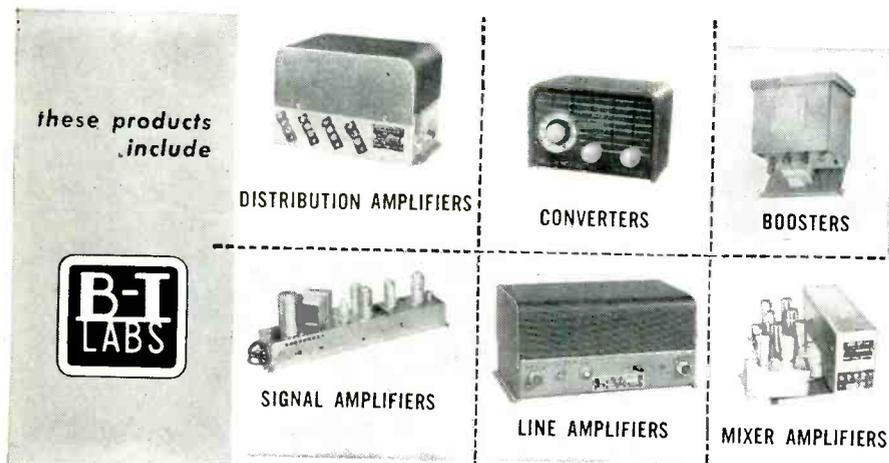Every piece of Blonder-Tongue equipment ever built, sold and in use — or ever to be used — is designed with color in mind . . . with the flat, broad output required for color.



. . . and all B-T impedance matching devices, equalizers, couplers, attenuators, connectors and tap-offs.

For example:

The **2-SET COUPLER** Model TV-42

is the only type approved by engineers for color — with a flat response from 0 to 900 mc.

Every **B-T LABS** Master TV System now in operation is designed to meet the exacting demands of Color Television . . . today and tomorrow.

Keep abreast of the Latest Developments. Apply for your **FREE** subscription to the **B-T BULLETIN**.



Write today, to Dept. OH-7

BLONDER-TONGUE LABS., INC. Westfield, New Jersey

In Canada: Telequipment, London, Ontario

The largest manufacturer of TV Signal Amplifiers, UHF Converters and Master TV Distribution Systems.

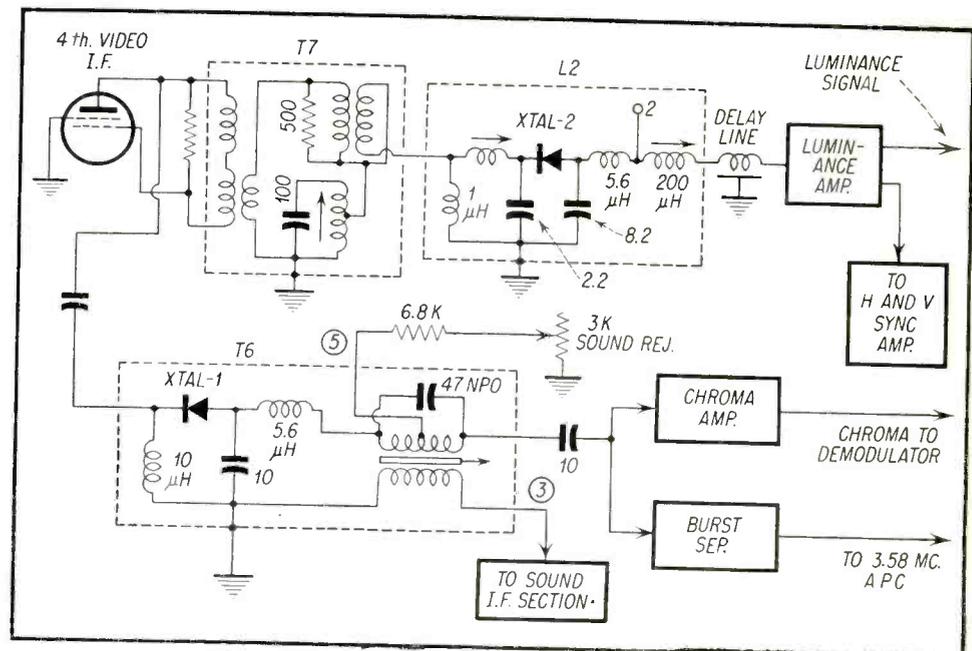


Fig. 3—Partial schematic of a dual detector receiver. The luminance signal is detected separately in one of the detectors. The sound and chrominance signals are detected together in another detector as shown above.

which is fed into the chroma section for further processing.

In the CBS-Columbia 205 receiver the video detector and signal takeoff circuit, as shown in Fig. 4, provides a separate crystal detector for the sound signal, and another for the chroma and luminance signals. Here we observe that the video *if* signal from the plate circuit of the 5th video *if* ampli-

fier is divided into two paths. One path feeds the sound detector as shown, coil *L9* being tuned to 4.5 mc.

In the other branch of the detected signal the video *if* signal is sent through a sound trap of the "Sound Reject" type described in the May 1956 issue of Service Dealer and Electronic Servicing on page 32. The video *if* information comprising the chroma and luminance

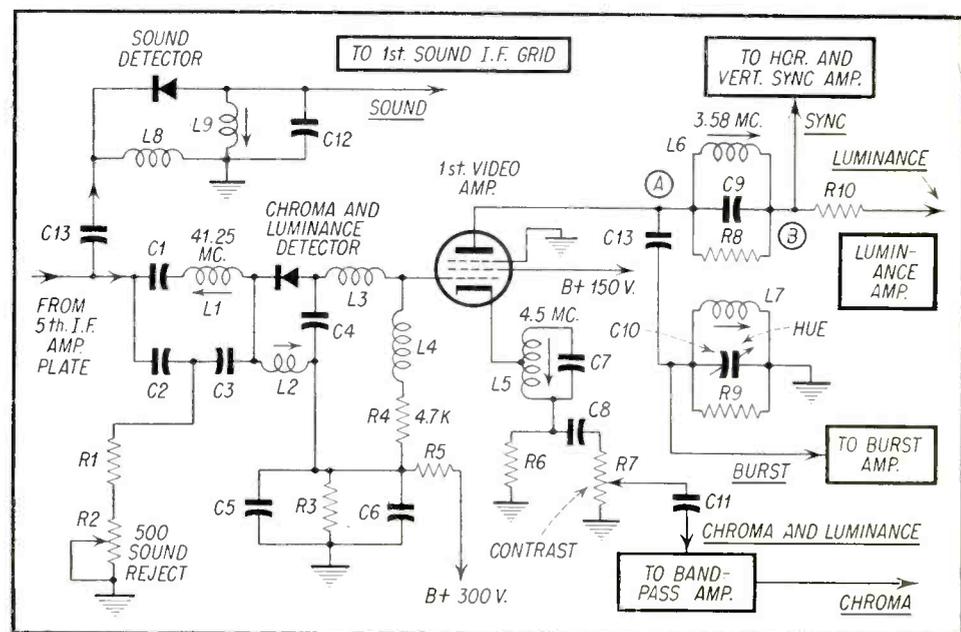


Fig. 4—Partial schematic of a color receiver using a separate detector for the sound signal and another detector for the chroma and luminance.

signals are demodulated together and fed into a video amplifier. The output of the latter provides three divisions of the detected signal. These divisions take place as follows:

The chroma signal is taken off at the cathode. Here a 4.5 mc trap provides further sound attenuation and the signal is sent into the bandpass amplifier via a contrast control. The bandpass amplifier which is tuned between 2.08 mc and 4.08 mc serves to attenuate the useful luminance signal, passing only the chroma information.

The plate circuit of the video amplifier feeds the video signal across L6 and C9 which is a parallel resonant circuit tuned to 3.58 mc. Because of its parallel resonant nature at 3.58 mc the color burst signal develops a high voltage at point A and is forced through C13 to the Burst Amplifier where it is processed as described in previous installments.

Signal frequencies other than 3.58 mc, of which the luminance and sync signals are examples, find an easy path through L6 and C9 and are transferred on to point B. At point B the signal divides again, making its way into the luminance amplifier and into the horizontal and vertical sync amplifiers where appropriate signal processing extracts the desired signal.

Summary

Extraction of the various signals contained in the composite video *if* signal takes place in the section of the color receiver immediately preceding or immediately following detection.

Three detection systems are generally to be found. These consist of a single detector for all of the component signals; a dual detector in which one detector demodulates the sound *if* and the other the chroma and luminance *if* signals; and a dual detector in which one detector demodulates the luminance *if* signal and the other the chroma and sound *if* signals.

Methods used to separate one signal from another where they appear in a common circuit is generally accomplished by means of tuned coils or transformers which accept the desired signal and reject the undesired signal. ■ ■



**Let's slug it out with
the tube Racketeers!**

**Together we can give 'em
the knockout blow!**

PHILCO

Tube Racket-Smashing Campaign

Last year Philco sponsored the industry's first Tube Racket-Smashing Campaign. The results . . . wonderful cooperation from service dealers and praise from thousands of TV and radio owners who had been "taken over" on replacements.

Now, after one year of slugging, the tube racketeers are staggering . . . and we're ready to "knock 'em out" with another great Tube Racket-Smash-

ing Campaign. During the month of August, Philco Distributors will credit you with 5c for old, worn out tubes you bring in, toward the purchase of new Philco receiving tubes. *Your old tubes will be smashed right before your eyes.* Join the Tube Racket-Smashing Campaign today . . . for the good of the industry . . . for extra profits for *you*. See your Philco Distributor.



PHILCO CORPORATION
ACCESSORY DIVISION
PHILADELPHIA 34, PENNA.



trade flashes

A plaque honoring Ray R. Simpson's "leadership and inspiration" during his 50 years in the electronic instrument field was presented to the Chicago industrialist recently.



The presentation was made at a dinner sponsored by sales representatives of Simpson Electric Company, Chicago, founded by Simpson. The 35-pound copper and wood plaque was presented by John M. Forshay of New York City on behalf of the 100 sales representatives attending the affair at the Congress Hotel.

An unprecedented contract between General Electric Company's Communication Equipment Section and Ryder System, Inc., one of the country's largest transport firms, calling for the widespread leasing of mobile radio units as regular trucking gear, was announced jointly by the two companies. Under the unique agreement, General Electric will lease two-way radio units for installation in trucks owned by Ryder Truck Rental Systems, a subsidiary of Ryder System. Ryder Truck Rental in turn will offer radio-controlled pickup and delivery to customers obtaining transport equipment from the Ryder organization on a lease basis.

The Washington County, Maryland Board of Education, with headquarters here, announced plans for installing the nation's first large scale closed-circuit television institutional program throughout an entire public school system.

Superintendent of Schools, William M. Brish, disclosed that the program will be instituted when school opens in September, with more than 6,000 pupils in two high schools and six elementary schools receiving an important part of their daily instruction by television. Present plans call for the extension of the program to the entire Washington

County school system by September 1958, with all 47 schools supplied with closed-circuit equipment and approximately 20,000 benefitted from direct instruction by television.

Under the plan outlined by Mr. Brish all necessary equipments for school installations during the life of the project, presently planned for five years, will be contributed by the nation's leading electronic manufacturers through their official trade association, the Radio-Electronics-Television Manufacturers Association (RETMA). Funds to provide for the training of personnel and for supervising the program will be granted by the Fund for the Advancement of Education, an independent agency established by the Ford Foundation.

DOUGLAS H. CARPENTER, formerly chief engineer of JFD Mfg. Co. Inc., Brooklyn, New York, announces the opening of offices at 19 West 44th Street, New York City. Mr. Carpenter's firm will deal with various organizations in the electronic and electro mechanical industries on a consulting basis, in addition to public relations work in association with another New York organization.


The Hickok Electrical Instrument Company announces the opening of a new San Francisco Branch at 2585 Shattuck Avenue in Berkeley, California. George Ksander, Sales Engineer with Hickok for 10 years, has been appointed West Coast Manager for Hickok's complete line of electrical and electronic test equipment and electrical indicating instruments.

A 25th anniversary celebration in honor of the Snyder Mfg. Co., makers of auto radio and TV antennas and automobile accessories, will be held in the Beverley Hilton Hotel in Los Angeles. Key West Coast Snyder distributors will pay tribute to Ben and Gus Snyder, founders of the company. A supper party will be followed by an advance showing of all Snyder fall lines in the Presidential Suite of the hotel.

A new engineering development program has been added by Raytheon Manufacturing Company to encourage its employees to advance professionally by attending evening college classes and obtaining scientific training to qualify them for engineering positions. The program begins this fall.

Participants will be granted tuition, fees, and a stipend for books for study at accredited colleges and universities with evening divisions, such as Boston University and Northeastern University. Grants will be made on a yearly basis, renewable for a second year.

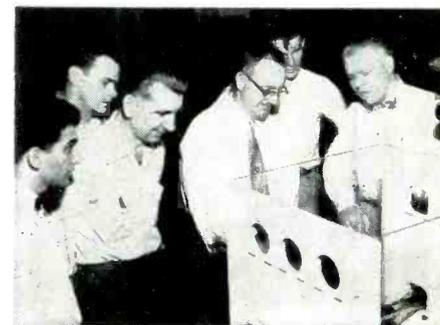Dan Johns, Moses Radio-Electronics Co., Hartford, Conn.; William Osterhaut, Bob's Electric Co., Winsted, Conn.; John Hurchala, Stafford Electric Co., Stafford Springs, Conn.; Robert Kelly, Radio Service Laboratory, Hartford, and Dennis Dandara, Bob's Electric Co., are shown receiving pointers from Herbert Evander, Tung-Sol Electric Inc. commercial



engineer, during groups' recent trip to three Tung-Sol tube plants in Newark, N. J. Mr. Johns escorted the four winners of the Moses Co. bonus plan contest. The one-day trip included an hour-long session with Louis Rieben, Tung-Sol president.

According to the Radio & TV Guild of Long Island News, the Detroit City Council passed unanimously an ordinance requiring a license to conduct a business of installing and servicing television equipment. The ordinance is aimed at "irresponsible sales methods," "inferior installation, maintenance, and repairs."

[Continued on page 42]

GUEST EDITORIAL

[from p. 19]

time and a higher quality of service work. When a new or unfamiliar receiver comes into your shop, stop for a few minutes before you begin to service the set. Take out the manufacturer's service information on the set. Study the overall circuitry of the receiver. If there are any new or unusual circuits, read the circuit description of that portion of the receiver. Glance through the scope wave forms illustrated and note from where they are taken. Observe any special notations as to voltage readings, alignment or servicing procedures. All this takes but a very few minutes out of each day and will reward the service technician with a full working knowledge of every receiver he may be called upon to service. In turn, he is then in position to provide his customers with the most complete, most competent and highest quality service available.

To supplement this self-improvement program of the service technician, most major Radio & Television Manufacturers have made available to the service profession: training courses, schools, home study material, and monthly technical publications. Avail yourself of these opportunities to broaden your education for, as with any other major profession, you must continually strive to increase your technical knowledge and improve your servicing ability. ■ ■



**Radio - TV
Hi Fi-Audio
Communications
Electronics**

SERVICEMEN

SERVICE DEALER

and ELECTRONIC SERVICING

is YOUR magazine.

Subscribe to it now. Reap its benefits!

**Now every serviceman engaged in every phase of radio-TV
and Industrial Electronics servicing will find:**

SUBSCRIPTION RATES: 12 Issues \$3; 24 Issues \$5 (In the U.S.A., U.S. Possessions, Canada and Mexico). Elsewhere add \$1 per year.

COWAN PUBLISHING CORP.

67 W. 44 St., New York 26, N.Y.

NEW

RENEWAL

Sirs: I remit herewith \$..... Enter a subscription for..... years as follows:

Name.....

Address.....

City..... Zone..... State.....

Name of firm.....

Firm's business address.....

City..... Zone..... State.....

CHECK YOUR CLASSIFICATION

- | | |
|--|---------------------------------------|
| <input type="checkbox"/> Independent Radio-TV Serviceman | <input type="checkbox"/> Owner |
| <input type="checkbox"/> Radio-TV Service Organization | <input type="checkbox"/> Employee |
| <input type="checkbox"/> Retail Store having Service Department | <input type="checkbox"/> Service Mgr. |
| <input type="checkbox"/> Industrial Electronic Service Firm | <input type="checkbox"/> Student |
| <input type="checkbox"/> Firm having electronic equipment which I service and maintain | |

If some other type of company describe:.....

A TYPICAL ISSUE COVERS

- Latest TV Installation and Maintenance Techniques for VHF and UHF
- Auto Radio Installation and Service
- Mobile Communications, 2-Way Radio, Ship-to-Shore Radio Installation and Service Techniques
- Industrial Electronics Equipment Servicing Data
- Advanced Data on New Circuitry
- Production Changes and Field Service Data on Receivers
- New Tubes
- New Test Equipment, Operation and Application Data
- P.A. Installation and Service
- Hi-Fi Installation and Service
- New Developments, Such As Transistors, Color, UHF, etc.
- News of the Trade
- Service Short Cuts and Shop Notes
- Explanation of Difficult Circuits
- M'fgr's Complete Line of TV Schematics
- Video Speed Servicing Systems

DON'T Just say capacitors

Ask For Sprague By Catalog Number
Know what you're getting... get exactly what you want. Don't be vague... insist on Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 71 Marshall Street, North Adams, Massachusetts.

SPRAGUE

WORLD'S LARGEST CAPACITOR MANUFACTURER

NEW

PHAOSTRON PROBE-LITE

ILLUMINATED TEST PROBE
SELF-CONTAINED
SEE WHAT YOU ARE TESTING!


\$250
LIST

It is just like having an extra hand. Simply insert the probe from your tester into the jack of the Probe-lite and the Probe-lite becomes alive to instantly give you a brilliant, pre-focus spotlight on the area that you are testing plus a long, extra slender, probe tip for making electrical contact in difficult places which previously were inaccessible. It could pay for itself the first time you use it.

GET A FREE PROBE-LITE

If you are the fortunate owner of a Phaostron "555" or "555A" VOM, we will send you a Probe-lite free. Mail us the warranty page you will find in your instruction manual. We will send you a new Probe-lite and return your warranty. Be sure you include your correct name and address.

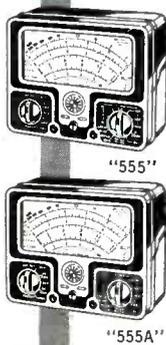This offer is good until October 1, 1956.



PHAOSTRON

PHAOSTRON INSTRUMENT & ELECTRONIC CO., 151 Pasadena Avenue, South Pasadena, Calif.

THE WORK BENCH

Unusual Service Problems And Their Solutions

by PAUL GOLDBERG
Service Manager

This Month's Problem:
Color Receivers

THIS month's installment concerns problems in color receivers. A knowledge of color receiver theory and circuitry is necessary in solving these problems. This article has been written with the hope that the reader has been reading the very informative articles on color by Dargan and Marshall in this magazine.

CBS Color Chassis 205

The receiver was turned on and it was noted that the black and white picture was normal; however, during color transmission there was an absence of red and the picture seemed to be dominated by the colors green and purple. This usually indicates the malfunctioning of the I channel in the color section of the receiver. The absence of the color signal passed by the I channel usually gives this effect; in which case the Q

and Y (luminance) signals are the only signals reaching the picture tube red, green, and blue control grids.

The diagram was now studied. It was observed that the 6BY6, V23, I demodulator, and the 6AN8, V24 A & B, I amplifier and phase splitter were the tubes that would affect only the I band of color signals. These two tubes were replaced individually, but had no effect.

The purpose of the demodulator is to separate the chrominance information into the I and Q signal voltages. This is accomplished in the I demodulator, V23, by applying the chrominance signal to the pin #1 grid and applying the I reference oscillator signal (3.58 megacycles) to the pin #7 grid. Synchronous detection then occurs.

The I signal then passes through the filter network C23-4, L23-1, C23-3, R23-3. The filter passes a band of frequencies

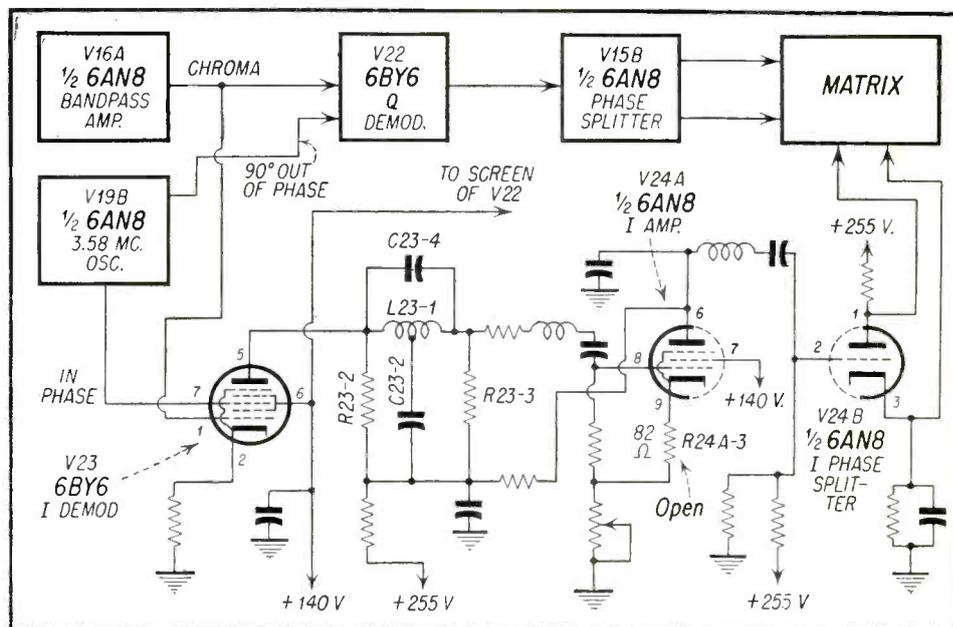


Fig. 1—Partial schematic of CBS 205 Color TV receiver.

from 0 to about 1.5 mc and eliminates any high frequency brightness information. The I signal then enters the I amplifier V24a, 1/26AN8. The signal is here amplified to a value proportional to the Q signal voltage. This is necessary since only one sideband of I, between .5 and 1.5 mc., is transmitted as compared to Q which has two sidebands. (The Q sidebands add in the Q demodulator producing twice the amplitude of I in the I demodulator.) The signal then leaves the I amplifier and enters the I phase splitter stage, V24A, 1/26AN8. This stage produces negative as well as positive I voltages at its plate and cathode which are coupled to the matrix section.

Aware of these facts, quick voltage checks were made at the plate, screen and cathode of V23, V24A and V24B. When a voltage measurement was taken at the cathode, pin #9, of V24A, the meter read about 60 volts positive instead of about 5 volts. Thinking that this cathode was open, a resistance measurement was made from cathode to ground of V24A. The meter read infinite. The circuitry was examined and R24A-3, 82 ohms was found to be burned open. Replacing R24A-3, the receiver was turned on and checked on a station transmitting color. It now operated normally with all colors being reproduced properly. As no other cause could be found for the open R24A-3, V24, 6AN8 was replaced as a precautionary measure.

Motorola Color Chassis— Model BP-902A-01

The receiver was turned on and it was observed that black and white pictures were being received properly; however, during color transmissions the picture had horizontal bands of color moving vertically. It was deduced therefore that there was no color synchronization; that is the 3.58 mc CW oscillator was not being synchronized with the transmitted burst signal.

The color sync section is made up of V24 A & B (color *afc*), V28A, 1/212AT7 (reactance), and V28B, 1/212AT7 (3.58 mc CW oscillator). V24 and V28 were replaced individually, but had no effect.

[Continued on page 46]

the new
Jensen

PROFESSIONAL SERIES

the complete line for
**INDUSTRIAL,
COMMERCIAL
and INSTITUTIONAL**
sound systems

... indoors or out—there is a
JENSEN PROFESSIONAL SERIES
loudspeaker that will do the job
*better, more dependably and
more economically* than ever before.

Here is a *complete* new line of
loudspeakers to meet every sound
system need for both entertainment
and efficient, effective communication.

Catalog 1070 describes all of
these new Jensen products.
Send for your free copy today.

Jensen

**MANUFACTURING
COMPANY**

6601 South Laramie, Chicago 38

Division of The Muter Co. • In Canada: Copper Wire Products, Ltd.



DD-100



D-40



D-30

LIFETIME DRIVERS
100 WATT 40 WATT
30 WATT

(Lifetime guaranteed against failure)



RT-2C



H-150
H-200
H-240



R-242

HORNS
RECTANGULAR,
ROUND and RADIAL



HF-100




VH-91



VR-11

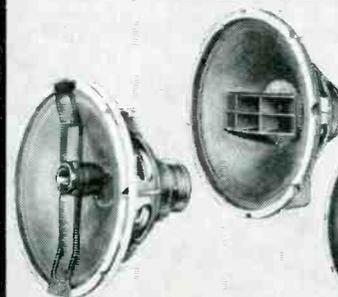Complete PROJECTORS
FOR HIGH FIDELITY
and HIGH EFFICIENCY



TRIAxIAL*

High Fidelity 3-way
unitary loudspeakers.
3 coaxial 2-way hi-fi
unitary loudspeakers.

*T.M. Registered



**EXTENDED
RANGE**

4" to 15". Quality
performance in a "one-way"
speaker.



**SPEECH
MASTER**

Highly efficient
PM speaker for
speech reproduction.



**TRANS-
FORMERS**

Constant Volt-
age and Impedance Match-
ing types.



Complete **SERVICE KNOWLEDGE**

AT UNBELIEVABLY LOW COST!


RIDER MANUALS—THE ONLY FULLY FIELD-TESTED, FACTORY-APPROVED SERVICE DATA—IS AVAILABLE TO YOU AT AN INCREDIBLE PER CHASSIS COST OF 8¢! AT A PER-MODEL COST OF ONLY 2¢ . . .

Now available...

TV 18

Limited Printing...
order your copy NOW!

Only \$19.80

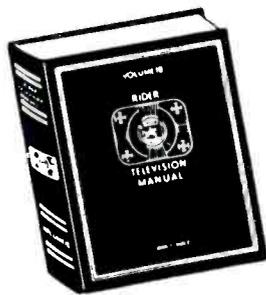

HANDBOOK OF 630-TYPE TV RECEIVERS

by Miller & Bierman

Deals with all versions of the famous 630-type receivers made up to 1955. Explains modifications and circuit improvements made by various manufacturers, and includes 26 pages of troubleshooting charts. A book every technician can use to major advantage! Soft Cover, 200 pp., 5½ x 8½", illus.

#174 Only \$3.50

RECEIVING TUBE SUBSTITUTION GUIDE

by H. A. Middleton

Lists 2,500 radio-TV tube substitutions. Also lists ratings and wiring instructions, original and substitute tube socket illustrations. Soft Cover, 224 pp., 8½ x 11", illus.

#135 Only \$3.00

FIRST SUPPLEMENT: Lists 750 new and different tube substitutions, not listed in the original edition. Soft Cover, 48 pp., 8½ x 11", illus.

#139 Only \$.99

SECOND SUPPLEMENT: Features 134 TV picture tube substitutions as well as over 190 AM-FM-TV receiver tube substitutions. This set of Three books is the most complete coverage available on the subject. Soft Cover, 48 pp., 8½ x 11", illus.

#139-2 Only \$.99

PICTURE BOOK OF TV TROUBLES

by Rider Lab. staff

A series of books, each covering a different part of the TV receiver, and showing typical troubles, their symptoms and causes. All material is from actual case histories. These books do your troubleshooting for you! Soft Covers, 5½ x 8½", illus.

VOL. 1: HORIZONTAL AFC-OSCILLATOR CIRCUITS

#168, 80 pp. Only \$1.35

VOL. 2: VERTICAL SWEEP-DEFLECTION CIRCUITS

#168-2, 96 pp. Only \$1.80

VOL. 3: VIDEO IF & VIDEO AMPLIFIER CIRCUITS

#168-3, 96 pp. Only \$1.80

VOL. 4: AUTOMATIC GAIN CONTROL CIRCUITS

#168-4, 96 pp. Only \$1.80

VOL. 5: HORIZONTAL OUTPUT AND HIGH POWER CIRCUITS

#168-5, 103 pp. Only \$1.80

HOW TO USE TEST PROBES

by A. Ghirardi & R. Middleton

The only book of its kind, it covers all types of test probes used with VOM's, VTVM's, and scopes. Complete step-by-step explanations, with practical examples of results and effects. Soft Cover, 176 pp., 5½ x 8½", illus.

#165 Only \$2.90

TELEVISION—HOW IT WORKS

(2nd Edition)

by J. Richard Johnson

A completely rewritten, up-to-the-minute edition of an authoritative and informative book. It is the newest and most comprehensive text on the subject, and follows the progress of the received signal from the antenna to the picture tube and loud-speaker. Leather Finish MARCO Cover, 352 pp., 5½ x 8½", illus.

#101 Only \$4.60

#101-II, Cloth Bound Only \$5.50

RIDER MANUALS

AND THE FAMOUS

LINE OF ECONOMICAL

RIDER BOOKS

ARE AVAILABLE AT

YOUR PARTS JOBBER.

LOOK FOR THE

RIDER BOOKSELLER.



FREE CATALOG ON REQUEST

If your jobber does not sell Rider Manuals order them from us.

JOHN F. RIDER PUBLISHER, INC.

480 Canal Street, New York 13, N. Y.

In Canada:
Charles W. Pointon, Ltd.
6 Alcina Ave., Toronto, Ontario
Prices approx. 5% higher.

ASSOCIATION NEWS

by SAMUEL L. MARSHALL

Television Service Dealer Association of San Mateo County

Recently, celebrating its first year anniversary, the Television Service Dealers Association of San Mateo County had its annual dinner dance at Bob's Place on Broadway in Burlingame.

Headlining the distinguished guests that were present was Frank Moch, president of NATESA, who flew from Chicago to install the newly elected officers.

The new president of TSDA is Eddy Mitchell. W. D. Haines was elected vice-president. TSDA secretary is Jack Gardner, and treasurer is Jetti Hill.

Dick Dowlwig, California State Assemblyman, Rex Yeager, president of the San Francisco Service Guild and H. Lawrence Schmitt, president of the Radio and Television Association of Santa Clara Valley were among the honored guests.

As guest speaker, Frank Moch confined his comments to television service industry problems of a national character.

Over 150 people heard Moch say that factory service company competition is becoming more of a problem in the East. "The large companies are going to compete because they realize that the service industry can be profitable." Moch closed his talk with the thought that "only the local associations can handle the biggest problem of all; establishing good relations with the public."

Radio Television Guild of Long Island

With the organization of a full working committee, plans for the Long Island Electronics Fair swing into high gear.

The first task of the committee was the formation of a brochure. Included in the brochure will be the purpose of the Fair, the facilities that are available, the participation rate and other

pertinent information to attract lectures and exhibitors.

The Long Island State Agricultural Institute, where the Fair will be held, has pledged full support. As an added attraction to visitors, the Institute intends to conduct guided tours through the University itself.

Exhibit facilities consist of a large building, 130 x 90', which will comfortably accommodate 50 to 75 booths. The Institute has also made available three lecture halls accommodating up to 150 people which will be used for the presentation of technical papers. Included in the facilities available are a cafeteria, a large parking lot, ample lighting, public address systems and motion picture equipment.


Of interest to both exhibitors and visitors will be the information that the Electronics Fair is to run as a non-profit venture. Charges both to visitors and exhibitors will be small and are only intended to cover expenses.

Association Radio-Television Servicemen of New York, Inc. (ARTSNY)

In addition to the ARTSNY Clinic Color Course, ARTSNY has obtained a series of technical lectures to be given by one of the finest lecturers in the field. Samuel Marshall, author, teacher, lecturer, and editor of SERVICE DEALER AND ELECTRONIC SERVICING MAGAZINE, will present a series of lectures on Color TV. This same course was presented to a teacher group in New York City and is to be given in its entirety over a period of ten months. The course will start from the theory and operation, and progress to the servicing of color TV and the instruments used, and will provide the necessary knowledge for servicing color sets. This course will be free to all members of ARTSNY,

[Continued on page 38]

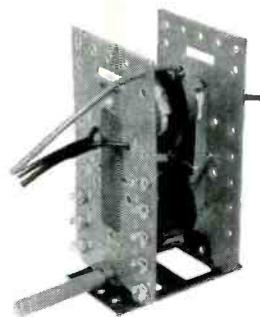MERIT, first in exact and universal replacement transformers, yokes, coils —the only manufacturer of transformers, yokes and coils who has complete production facilities for all parts sold under their brand name.



HVO-49 FOR EXACT REPLACEMENT IN AIRLINE, RAYTHEON, TRUETONE. Another in the complete MERIT line of exact and universal replacements —the only single source for all your transformer and coil requirements.

Merit

MERIT COIL & TRANSFORMER CORP.
4427 NORTH CLARK STREET
CHICAGO 40, ILLINOIS



Mfg: Motorola Chassis No. TS-326B


Card No. MO326-1

Section Affected: Raster

Symptom: Insufficient width, buzz, and vertical roll.

Cause: Defective component.

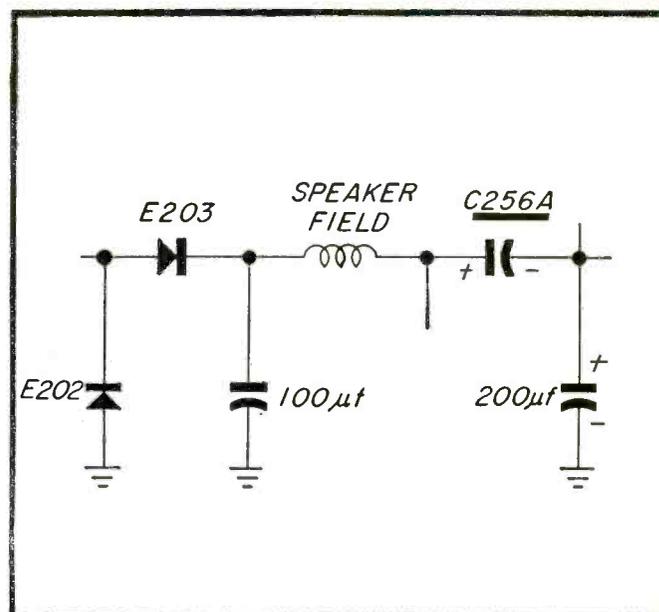What To Do:
Replace: C256A (200), which is leaking.



Mfg: Motorola Chassis No. TS-326B


Card No. MO326-2

Section Affected: Raster

Symptom: Vertical jumps.

Cause: Defective component.

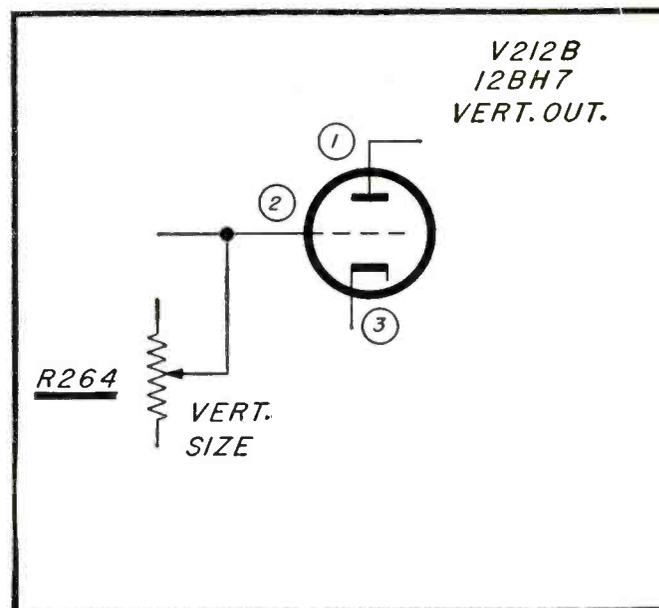What To Do:
Replace: R264 (5 meg.), vertical size control; arcing.



Mfg: Motorola Chassis No. TS-326B


Card No. MO326-3


Section Affected: Raster

Symptom: Bad vertical sweep.

Cause: Defective component.

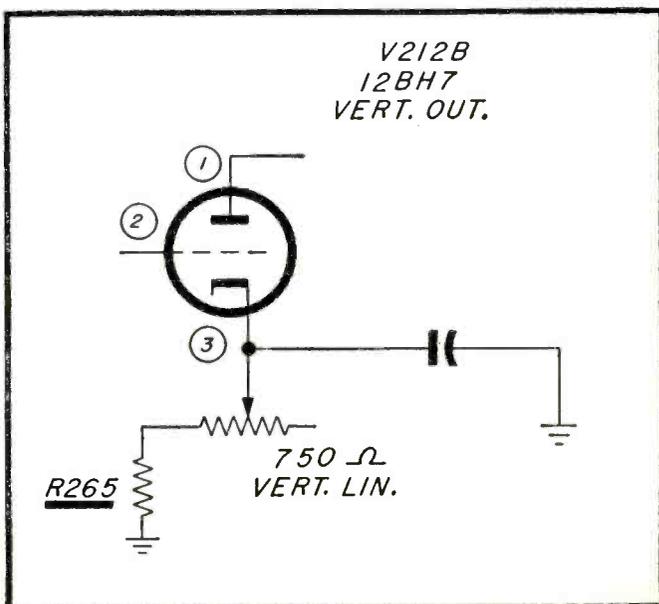What To Do:
Replace: R265 (8.7K), which is open.



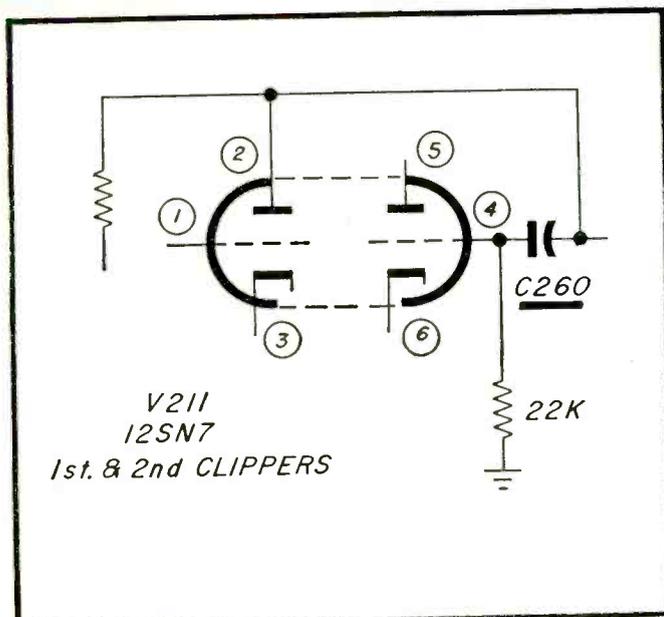

Mfg: Motorola

Chassis No. TS-326B

Card No. MO326-4


Section Affected: Sync.

Symptom: Critical vertical and horizontal hold.

Cause: Defective component.

What To Do:

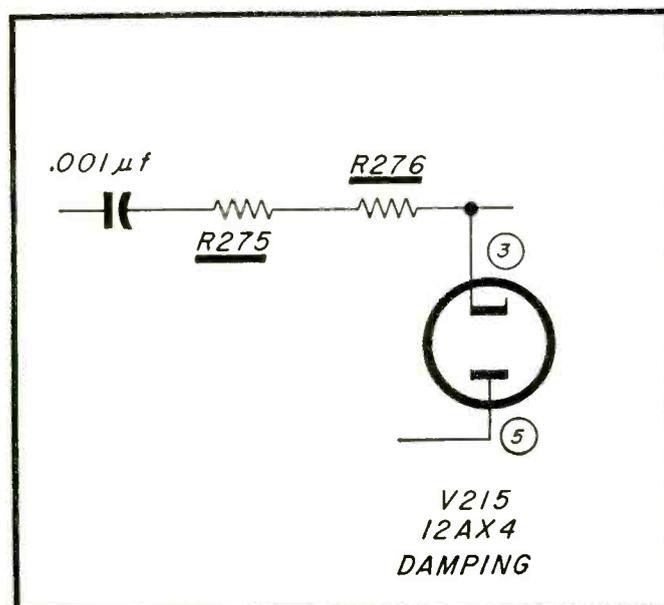Replace: C260 (.05 μ f), which is leaking.



Mfg: Motorola

Chassis No. TS-326B

Card No. MO326-5


Section Affected: Sync.

Symptom: Critical horizontal sync.

Cause: Defective components.

What To Do:

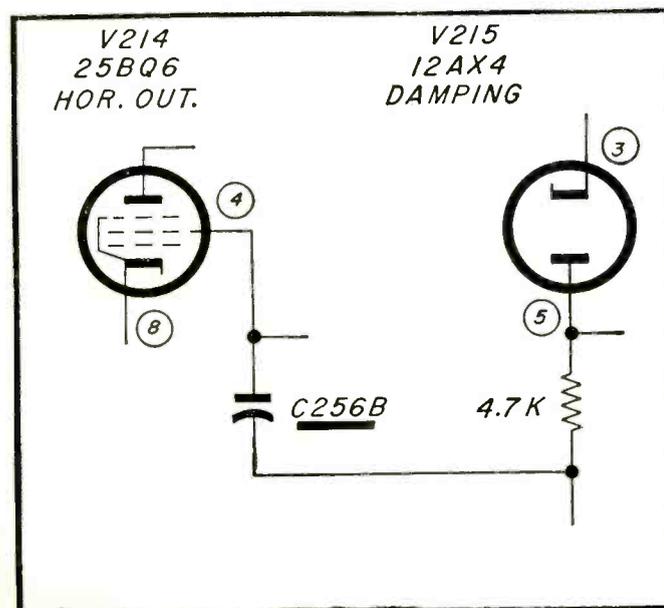Replace: R275 (150K), R276 (150K), which have increased in value.



Mfg: Motorola

Chassis No. TS-326B

Card No. MO326-6

Section Affected: Raster

Symptom: Insufficient width and sound distorted

Cause: Defective component.

What To Do:

Replace: C256B (5 μ f), which is shorted

ASSOCIATION NEWS

[from page 36]

A proposition was presented to the Associated Radio and Television Service of New York, Inc. by the Nationwide Insurance Co. It was a plan to help service the membership of the television association. It was by no means an insurance selling scheme, but rather a phase of the Brooklyn division of Nationwide to become part of the community it serves.

For the first time statistics of the industry which has numerous hazards will be compiled. The problem of one serviceman is the problem of hundreds of others. The Associated Radio and Television Servicemen of New York working with the Nationwide company has started a new vogue. The heavyweight working with the little fellow is a remarkable combination because it becomes a mutual service pact.

Associated Radio and Television Servicemen, Illinois (ARTS)

The ASSOCIATED RADIO & TELEVISION SERVICEMEN, Illinois, have created two new positions in their organization. One is that of Trade and Press Representative, and the other is that of Historian. Mr. Stephen (Steve) Jacyna, owner of Logan Square Radio has been appointed Trade and Press Representative. Mr. Anthony (Tony) Mallin, owner of Devon Radio Service has been appointed Historian. Because of the growth of the ARTS organization, the need for these positions has been recognized. Also they create the basis by which the members can share in the responsible work of the organization, and have the opportunity to assume work which will prepare them for more important administrative duties later.

High Point Radio & TV Technician's Association

The High Point (North Carolina) Radio & TV Technician's Ass'n. has been in operation for about three years. Major activity to date has been an opportunity for local shops to get to know

each other better and to exchange credit information. Meetings are held at local Y.M.C.A. on first & third Tuesday evenings, each month. First meeting is a business meeting, second a supper meeting.

Officers are Jim Hornaday, Pres., G. V. Fendor, V-Pres., Bob Baird, Sec.-Treas. Correspondence should be addressed to Bob Baird, 500 Mint St., High Point, North Carolina.

At a meeting in Greensboro, N. C. on June 14 the groundwork was laid for an association of TV-Radio service shops in the central part of the State. The meeting, called by the High Point Radio & TV Technician's Association, was attended by about 30 men from Greensboro, High Point and Winston-Salem. For the time being the group will be known as the Tri-City Technician's Ass'n.

Temporary officers to serve for three months were elected. These were Jim Hornaday, High Point, Pres.; Van Sickles, Winston-Salem, V-Pres.; Joe Woods, Greensboro, Sec.; and C. B. Steele, Greensboro, Treas. All full-time shops in the area are invited to join. Membership is not limited to the three cities mentioned. It is hoped that in the future this group may serve as a basis for a State-wide organization.

Houston Association of TV-Electronics Servicemen, Inc.

"The Houston Association of TV-Electronics Servicemen, Inc., an affiliate of the National Alliance of TV-Electronics Service Association has finally completed drafting of a Texas State Electronics Licensing Bill, which is now being incorporated into the platforms of several candidates for the new Legislature, and which will be considered for passage into law by the Texas Legislature," according to F. B. (Bob) Koepnick, President of the Houston Association, and a Director of the National Association. "The measure is not a control, nor regulatory bill, but provides that any person who engages in the servicing, or repairing of television or electronic equipment, will be required to take a State supervised Civil Service type examination. . . . Upon satisfactory passing he will be eligible to obtain a License, good anywhere in the State. . . . The law is designed to

Mfg: Silvertone

Chassis No. 128-16

Card No. SI128-1


Section Affected: Raster

Symptom: Intermittent ticking noise in sound and in raster.

Cause: Defective component.

What To Do:

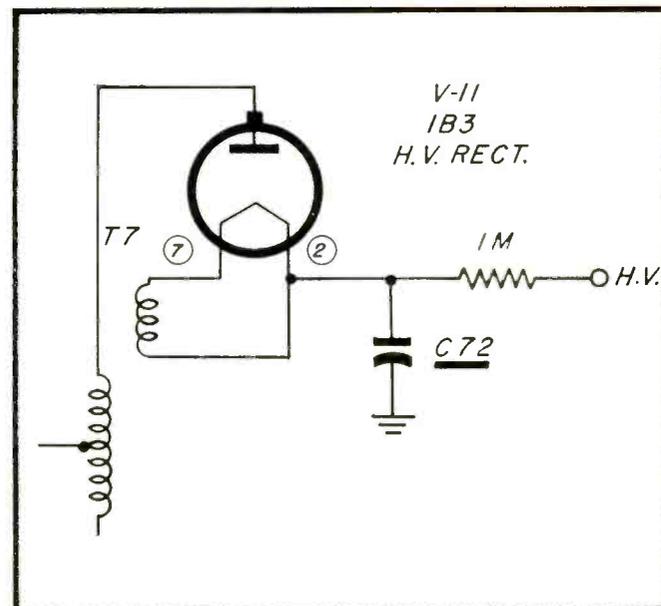Replace: C72 (330 $\mu\mu\text{f}$, 12.5KV), which is breaking down.



Mfg: Silvertone

Chassis No. 128-16

Card No. SI128-2


Section Affected: Sync.

Symptom: Vertical hold drifts out of range.

Cause: Defective component.

What To Do:

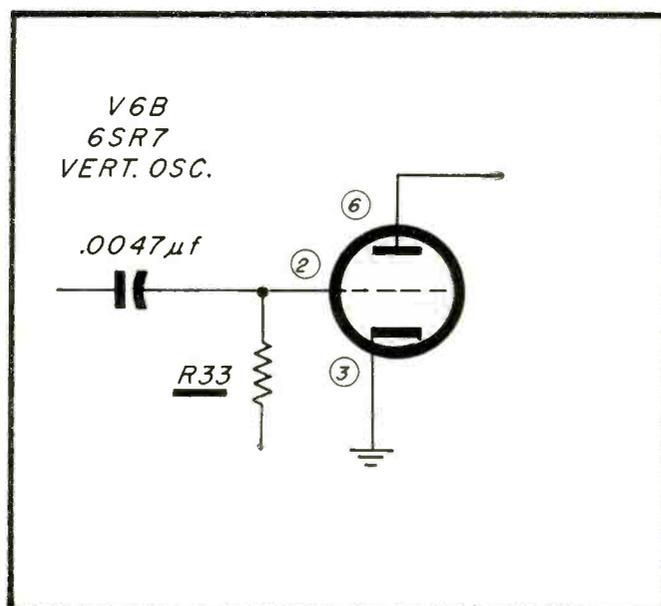Replace: R33 (1 meg.), which has increased in value.



Mfg: Silvertone

Chassis No. 128-16

Card No. SI128-3


Section Affected: Sound


Symptom: No sound and R66 is burned.

Cause: Defective component.

What To Do:

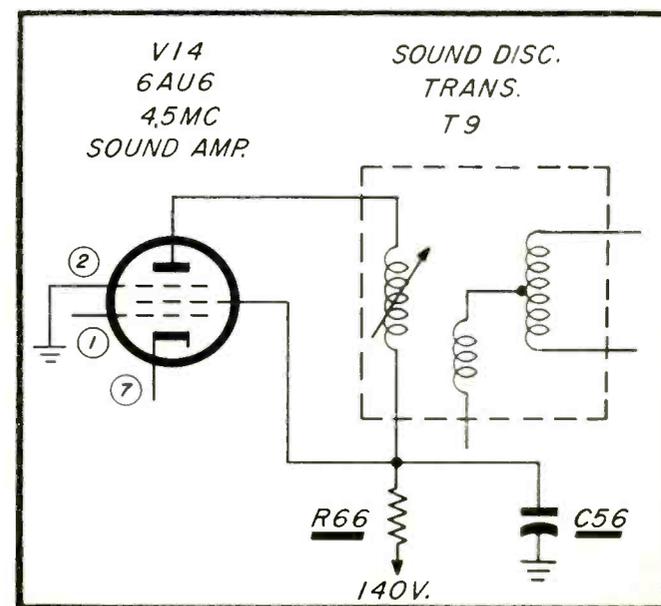Replace: C56 (.01 μf), which is shorted and R66 (1K), which is burned.



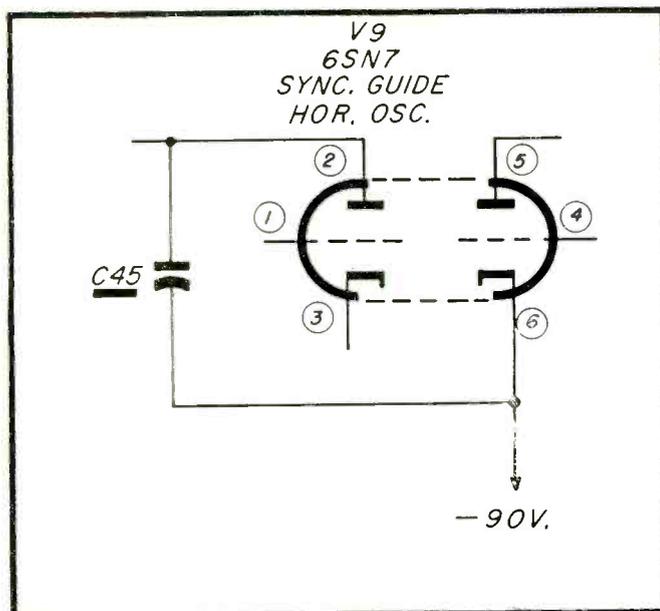

Mfg: Silvertone

Chassis No. 128-16

Card No. SI128-4


Section Affected: Sync.

Symptom: Horizontal frequency drifts intermittently.

Cause: Defective component.

What To Do:

Replace: C45 (.047 μ f), which is leaky.

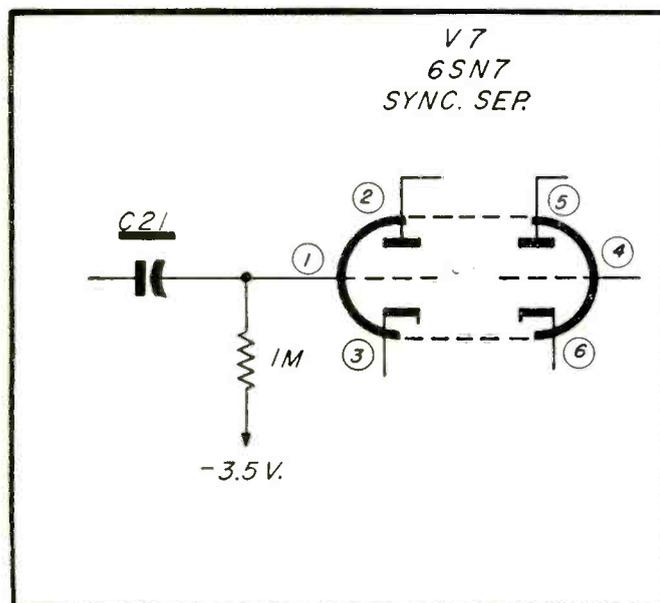

Mfg: Silvertone

Chassis No. 128-16

Card No. SI128-5


Section Affected: Sync.

Symptom: Poor vertical and horizontal hold.

Cause: Defective component.

What To Do:

Replace: C21 (.047 μ f), which is leaky.

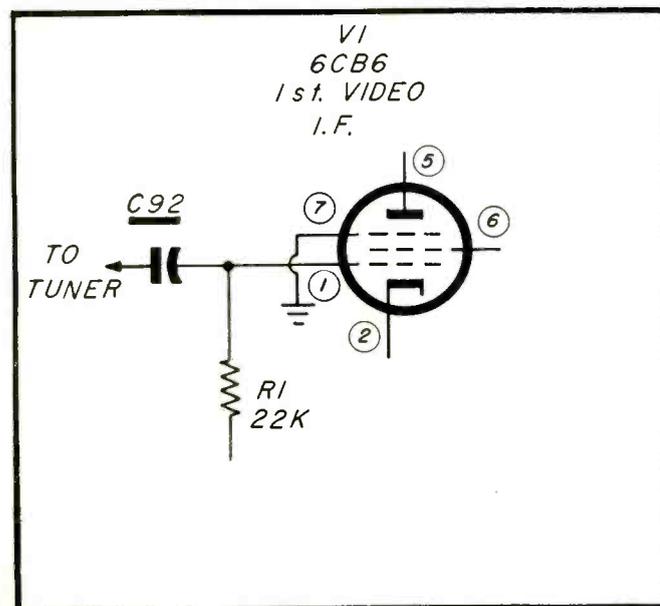

Mfg: Silvertone

Chassis No. 128-16

Card No. SI128-6

Section Affected: Pix

Symptom: Video overload.

Cause: Defective component.

What To Do:

Replace: C92 (270 μ f), which is leaky.

assist the public in cleaning up a lot of mess now existing in the business, and will provide penalties for those found guilty of damage and fraud to consumers' property."

Television Electronic Service Association, Saint Louis (TESA)

Charles Luensmann and Vince Lutz of TESA made a trip to New Madrid, Mo., for the June meeting of the Radio Television Association of South East Missouri. Charlie and Vince were made to feel welcome by this new group, which has only been organized for three months.

The story of how an individual shop owner could be represented on a local, state, regional and national level was explained and how small shops could benefit on advertising, educational, technical, credit and insurance problems through affiliation with TESA—Missouri and NATESA was described. Shop owners in outlying areas have much trouble setting up good technical meetings, purchasing insurance on group rates and being able to get high class advertising service at low cost. The present and future plans of NATESA to furnish these services to all affiliates was encouraging to the eighteen shop owners attending the meeting. Many of these men drove thirty or forty miles to attend. The association has a total of twenty-one members.

Radio Television Association of Santa Clara Valley (RTASCV)

Of news to the RTASCV membership is the fact that the new Westinghouse color receiver will be shown at the next general meeting to be held at the Napredak Hall in Cupertino. Don Johnson, Westinghouse dealer training supervisor will be present at the Aug. 14 meeting to describe the new Westinghouse color set.

Technical aspects and service procedures will be covered as well as set up and installation.

Business at the July 10 meeting included a report on the licensing bill that is proposed for the Santa Clara County. Members of the RTASCV will be asked to approve a bill that will be presented to the County Board of Supervisors. ■ ■

THE ANSWERMAN

Inquiries Sent To The Answerman Will Be Acknowledged Only If Accompanied By Radio-TV Service Firm Letterheads Or Similar Identification.

BY SERVICE DEALER & ELECTRONIC SERVICING TECHNICAL STAFF

Dear Sir:

I come across a job to add a VU meter to a tape recorder in connection with a mixer for a Hi-Fi fan. The recorder has a "Magic Eye" volume indicator only.

Maybe the "Answer Man" or Mr. Lawrence Fielding will mention a proper information in his "The Service Dealer and Hi-Fidelity."

W. R.
Brooklyn, N. Y.

Inserting a VU meter in a tape recorder may be accomplished in accordance with Fig. 1. A properly damped VU meter should be used, although so-called "power-level" meters will do a fair job. The former cost about \$42.00

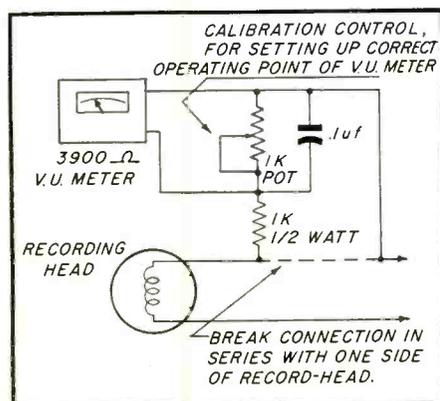


Fig. 1—How to connect a VU meter to tape recorders.

list, whereas the latter may be obtained at a list of about \$17.00 or 18.00.

The potentiometer is suggested in the circuit because not all recording heads require the same energizing current. Since you did not specify the type of recorder in question, I am suggesting a value of potentiometer which will cover most commercially available units. Your job will be to CALIBRATE the meter so that it reads just below full scale at the point of tape overload, but since you have the eye indicator, this should prove to be fairly simple.

Dear Sir:

I have a problem that has mystified me and may interest some of your readers. The receiver is a Travler 46A3. The receiver was examined and it was found that the contrast control was burned open. This looked simple enough. There was no picture or sound.

The audio take-off is in the plate circuit of the video amplifier which explains the lack of audio. I thought at first the problem was only going to involve an open contrast control. I replaced the control and turned on the receiver. Still no sound and no picture. The new contrast control burned in a short time.

I referred to the schematic, looked it over, measured a couple of voltages and

[Continued on page 43]

SPECIAL OFFER TO OUR READERS!

By special arrangement with John F. Rider Publisher, Inc., SERVICE DEALER and ELECTRONIC SERVICING now brings you a COMPLETE diagram service to help you do a faster, easier servicing job!

ALL COMPLETE! ALL FACTORY
PREPARED! ALL FACTORY
AUTHORIZED!

✓ Just \$1.25 for COMPLETE SERVICING INFORMATION on any TV receiver . . . any year, any make, any model . . . from 1946 on!

✓ Just 75¢ for COMPLETE SERVICING INFORMATION on any radio . . . any year, any make, any model . . . from 1941 on!

TAKE ADVANTAGE OF THIS SPECIAL
OFFER . . . MAIL THE COUPON TODAY!

COWAN PUBLISHING CORP.
67 W. 44 Street, New York 36, N. Y.
Please RUSH me the the following diagrams:

TV DIAGRAMS @ \$1.25 EACH

CHASSIS ≡	MAKE	MODEL ≡

RADIO DIAGRAMS @ 75¢ EACH

CHASSIS ≡	MAKE	MODEL ≡

MAKE CHECKS & MONEY ORDERS PAYABLE TO
COWAN PUBLISHING CORP.

(For all New York City orders, please submit additional 3% sales tax.)

Name _____

Address _____

City _____ State _____

XCELITE Hand Tools
PREFERRED BY THE EXPERTS

**NEW TWIST
in REAMING!**

Extra leverage—just insert 3/16" blade or pin

The new XCELITE No. 39 chrome plated reamers give you extra capacity—up to 1/2" reaming—chrome-hard cutting edges—plus this handy 3/16" leverage hole. Just insert 3/16" screwdriver or pin—you have the leverage of a T-type reamer plus the convenience of the famous XCELITE handle! Get No. 39 (with fixed handle) or 99-39 (fits your 99 Kit handle — your distributor stocks it with his new No. 99 replacement kit). An ideal addition to your 1/8" to 3/8" XCELITE SUPER-REAMERS!

**BIG
1/2"
CAPACITY**

No. 39 reamer fixed in handle

No. 99-39 detachable reamer

XCELITE, Incorporated
Dept. R
Orchard Park,
New York

For Originality
Look to XCELITE

**For Originality
LOOK TO XCELITE**

**Mr. Electronic
Service
Technician**

**FOR LONGER SERVICE LIFE
you can rely on...**

LYTICAP* ELECTROLYTIC CAPACITORS

You can recognize PLANET LYTICAPS by their shiny red cardboard jackets and their general neat workmanlike appearance. Available in all frequently used capacities from 3 to 500 volts, they are ideal for all types of service work—radio—television—industrial.

PLANET LYTICAPS are 100% tested for capacity and leakage; they receive a rigid mechanical inspection. Like all Planet products, they are fully guaranteed for one year. No wonder so many set manufacturers use them as original equipment!

*Registered

Ask for PLANET LYTICAPS by name at your regular parts jobber.

PLANET SALES CORP.
BLOOMFIELD, N.J.

TRADE FLASHES [from page 23]

Requirements for a service dealer's license are that he must have a certified technician's license or regularly employ a full-time certified technician.

It does not apply to any employee of a licensed service dealer under direction of a certified technician. That is to say, only one certified technician is required.

Students or apprentices accompanied and supervised by a certified technician are not required to have licenses but must carry identification cards.

As approved, the ordinance is a compromise between proposals made earlier requiring that all engaged in doing repair work or running a business be licensed and those proposals opposing licensing entirely. The television service association advocated the licensing proposal.

The requirements of a certified technician are that he must be over 21 years old, have four or more years of experience in servicing equipment, or have technical training (trade, college or correspondence school) equivalent to two years, with a minimum of one year's practical experience.

A service dealer's annual license fee is \$25 and a certified technician's \$10.

A board of examiners is to be selected and provision made for administration and enforcement of the ordinance. Members of the examining board will include three service dealers, an instructor of a TV school and an engineer from one of the local TV stations.

Industry-wide plans for the observance of National Television Week, Sept. 23-29, began to jell as manufacturers, dealers and broadcasters spelled out their individual and collective sales promotion campaigns.

Celebration of the Week again will be under the joint sponsorship of the Radio-Electronics-Television Manufacturers Association (RETMA), the National Association of Radio and Television Broadcasters (NARTB), the National Appliance and

Radio-TV Dealers Association (NARDA), and the Television Advertising Bureau.

RETMA and the other sponsoring organizations adopted the following slogan for this year's promotion campaign: "National Television Week—Celebrating the Finest Home Entertainment in Sight".

With the termination of Capehart's Television-Radio and High Fidelity Production and Sales—Mr. F. B. "Ted" Ostman, Director of Capehart-Farnsworth Company Service Operations will join the Federal Electric Corporation, another I T & T Division. Mr. Ostman will be Staff Consultant to Major General Francis H. Lanahan, Executive Vice-President.

Robert C. Kocmoud is the new sales promotion manager of General Cement Mfg. Co., Rockford, Illinois, and all that firm's sales divisions. The appointment was made recently by Stanley B. Valiulis, G-C president. Mr. Kocmoud brings to his new position several years' work with the advertising department of a large mail order company.

The two-way radio communications industry, through the Radio-Electronics-Television Manufacturers Association, announced plans looking toward the inauguration of an extensive educational and liaison program for the industry.

In accordance with this program, Carroll M. White, who has had many years experience in military, municipal and industrial communications, has been employed as Manager of Mobile Radio Communications by RETMA. In his new position, Mr. White will conduct a varied and extensive campaign to acquaint the government, industry and the public with the contributions made by the land mobile communications industry to the over-all economy and safety of the country. He will be stationed in Washington at RETMA headquarters.

MARINE ELECTRONICS [from page 6]

However, unless it has been specifically engineered for marine use, no ac equipment should be grounded in any way, because of the danger of causing electrolysis. This applies especially to battery chargers, some of which employ auto-transformers. Connecting them to a boat's batteries (while the batteries are still connected to boat circuits) is an invitation to rapid electrolysis. More on this in a succeeding chapter.

CORRECTION

The reader's attention is called to two corrections that should be made in Fig. 1 of the June installment of "The Marine Electronic Business" on page 15. The rectifier protective resistor is 22 ohms, not 22K; and the filter resistor is 500 ohms, not 500K. These corrections will render the diagram correct in every detail.

ANSWERMAN [from page 41]

found that instead of having, as the print called for, 135 volts at the cathode circuit of the 6V6 audio output tube I had nearly 400 volts. Tracing down the circuit I found that a large voltage was being applied to the contrast control when it should have been much less than 135 volts. I went back over the circuit diagram and found a condenser, EC-17B which was the filter condenser from the bottom of the audio output transformer to the cathode circuit of the audio output tube. Again, I thought, this is an easy one. The 40 μ f condenser is shorted and putting too much B plus on the 135 volt line. I checked the condenser. Needless to say, it was good.

I still haven't found why the contrast control has such a high voltage on it or 400 volts exists at the cathode of the 6V6 audio output tube.

I hope you can help me in this.

P. C.

Philadelphia, Pa.

In examining the B plus system and the power supply circuit as shown in Fig. 2 of the Travler 46A3 TV chassis it can be noted that there is another way in which 400 volts can appear at the cathode of the audio output tube besides with a shorted 40 μ f condenser (not considering a shorted 6V6 audio output tube). That is, if a short occurs in the power transformer filament windings. If the 5 volt filament winding for the 5U4 tube should short to the 6 volt winding, as shown in Fig. 2 the 400

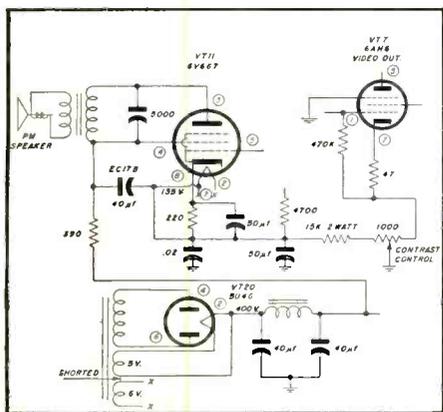


Fig. 2—Partial schematic of Travler 46A3 chassis showing power supply, audio, and video output.

volts on the 5 volt filament winding would also be applied to the 6 volt winding for the 6V6 tube and thus to its cathode circuitry. This is more than likely the cause of the difficulty.

Mr. Answerman:

What can be causing the low hum in the audio output from a television receiver I have been servicing. When the volume control is turned down the hum is still present from the speaker. It is not very loud but could possibly be considered objectionable.

Naturally, the first thing checked was tubes, then B plus filters. They were all found to be normal. Now what?

I have noticed that when I bring my hand in near the audio circuits there is a change in amplitude of the hum depending upon the position of my hand. Some locations cause the hum to increase and others reduce the hum.

Would very much appreciate a suggestion as to what to try next.

T. R.


Dallas, Texas

More than likely your problem is due to lead dress. In some receivers the ac leads that run to the on-off switch on the volume control pass along side of the audio stages. These leads can very easily induce 60 cycle voltages into the grids, or across the grid leak resistors. Lead dress in this section is more important than many technicians believe. Fortunately, it is usually solved in the experimental models and the technician is not too often bothered with lead dress problems.

When a hum is present as stated, one of the first steps to locate its cause would be to examine the ac lines running near the volume control and most particularly near the grid leak resistors. Another possibility of this difficulty may be the vertical deflection leads, such as those that feed the vertical output transformer. These wires must definitely be placed away from audio stages.

Also, contrast control or video signal leads running near audio circuits


\$3.25
each

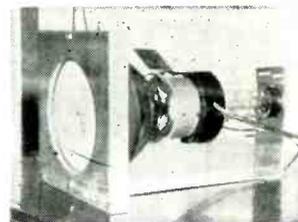

QUICK-CHANGE 5AXP4 HOLDER

Permits Speedy Yoke Changing

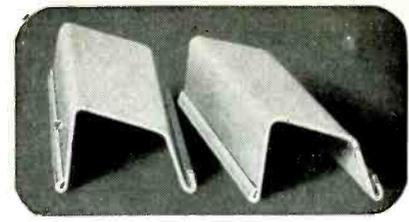TELE-SCOPIC PRODUCTS, INC. 215 W. 33rd St. • New York 1, N.Y.



CHASSIS HOLDERS

FOR HANDLING CHASSIS
WITHOUT CUTTING FINGERS

\$1.00

pair

Why "The Man On The Roof"


prefers *South River*



for making superior television antenna installations

Take "Snap-In" Type CHIMNEY MOUNTS and WALL BRACKETS for instance . . .

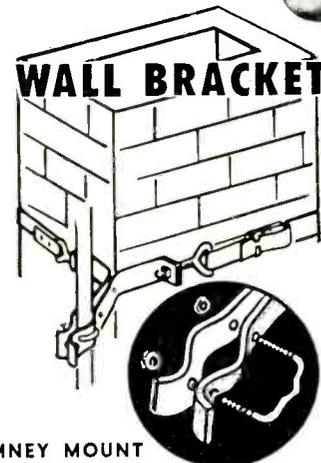Unique U Bolts instead of two screws make for quick, simple, antenna installation. Spring tension on steel mast retainers holds antenna mast while Special U Bolts are inserted and tightened. Saves installer time — permits greater safety. Same features are included in Snap-In Wall Brackets.



SN-50 CHIMNEY MOUNT (Two To A Set)

"Special U Bolt is far superior to two screws"

"Hot-Dip Galvanized for rust resistance . . . prevents ugly rust streaking"

"Need only one hand and spintite for securing mast"

"One hand can be used to hold on to the mast, ladder or mounting for greater safety"

"Saves time fumbling with screws and screwdriver. Only one man needed on roof"

Mr. Installer:

DON'T BE SWITCHED—IT'S YOUR TIME AND SAFETY

Your Distributor has these in stock or can order and receive them immediately. If your distributor does not handle South River products, please write us on your business letterhead. We'll

see him at once and tell him the story of South River superiority. Products made better by design — with the installer in mind **MAKE IT EASY FOR YOURSELF** . . . Better for your Customers

Insist on mountings and accessories made by

South River **METAL PRODUCTS CO., INC.**
South River, New Jersey

PIONEER MANUFACTURER AND OUTSTANDING PRODUCER OF THE FINEST LINE OF ANTENNA MOUNTING ACCESSORIES

WRITE FOR OUR 1956 CATALOG

for service and lab. work

Heathkit PRINTED CIRCUIT OSCILLOSCOPE KIT FOR COLOR TV!

① Check the outstanding engineering design of this modern *printed circuit* Scope. Designed for color TV work, ideal for critical Laboratory applications. Frequency response essentially flat from 5 cycles to 5 Mc down only 1½ db at 3.58 Mc (TV color burst sync frequency). Down only 5 db at 5 Mc. New sweep generator 20-500,000 cycles, 5 times the range usually offered. Will sync wave form display up to 5 Mc and better. Printed circuit boards stabilize performance specifications and cut assembly time in half. Formerly available only in costly Lab type Scope. Features horizontal trace expansion for observation of pulse detail — retrace blanking amplifier — voltage regulated power supply — 3 step frequency compensated vertical input — low capacity nylon bushings on panel terminals — plus a host of other fine features. Combines peak performance and fine engineering features with low kit cost!



MODEL
0-10
\$69.50
Shpg. Wt.
27 lbs.



MODEL
TS-4
\$49.50
Shpg. Wt.
16 lbs.

Heathkit TV SWEEP GENERATOR KIT ELECTRONIC SWEEP SYSTEM

② A new Heathkit sweep generator covering all frequencies encountered in TV service work (color or monochrome). FM frequencies too! 4 Mc — 220 Mc on fundamentals, harmonics up to 880 Mc. Smoothly controllable all-electronic sweep system. Nothing mechanical to vibrate or wear out. Crystal controlled 4.5 Mc fixed marker and separate variable marker 19-60 Mc on fundamentals and 57-180 Mc on calibrated harmonics. Plug-in crystal included. Blanking and phasing controls — automatic constant amplitude output circuit — efficient attenuation — maximum RF output well over .1 volt — vastly improved linearity. Easily your best buy in sweep generators.



When signal conditions
demand a **TOWER...**
choose one built by **AERMOTOR**



AERMOTOR TOWERS have proven their excellence in thousands of installations . . . installations exposed to the most severe weather and wind loading conditions.

AERMOTOR steel antenna towers are self supporting . . . require no cumbersome guy wires. Each part is heavily galvanized *after* fabrication to insure complete protection from exposure.

Towers are shipped knocked down in convenient bundles; well designed parts make section-by-section assembly easy.

AERMOTOR 3-post antenna towers are available in heights of 33, 47, 60, 73, 87 and 100 feet.

WRITE FOR ADDITIONAL INFORMATION ABOUT THE AERMOTOR TOWERS AND A DEALER FRANCHISE IN YOUR TERRITORY.

SINCE 1888, MANUFACTURERS OF QUALITY BUILT TOWERS

• **AERMOTOR COMPANY** •

2500 W. ROOSEVELT RD.—CHICAGO 8, ILLINOIS U.S.A. DEPT. 33U8

or leads to audio circuits should be considered as the possible cause of hum in audio systems. Of course this would only occur on channel. The large video voltages present can easily couple a buzz into audio leads. The amplitude of these video signals is easily demonstrated by bringing a scope probe in the vicinity of the video stages and observing the video pulses that will be picked up without making a direct connection. Large coupling condensers are particularly good radiators of video signals.

Most likely, a close examination of the leads from the volume control to the audio amplifier grid and audio output grid circuits will reveal the source of the induced hum voltage. It is frequently helpful to twist the *ac* leads that run to the on-off switch so that the fields radiated by these wires are more or less cancelled, or at least reduced to a minimum.

Dear Mr. Answerman:

In certain areas of our city I have received many complaints in regard to reception of our local TV station which is Channel 2. Due to a recent change-over from one antenna to another, a decidedly ultra strong signal is now present in these areas. The symptoms clearly indicate an over-driven too great a signal being applied to the receivers. This is particularly of concern with new model receivers.

Could you suggest a means of rectifying this situation and would this corrective measure pertain to all types of sets.

J. J. S.
Allison Park, Pa.

With the high amplification ability of present day receivers and the large amounts of power being radiated by some channels a problem is sometimes prevalent that was not experienced on the older receivers they are replacing. This overload problem comes into particular concern when the TV receiver is in an area where the transmitter signal strength is increased or is of a large magnitude.

Unfortunately, many technicians seem to be unfamiliar with the solution of this problem. Technicians feel that the set manufacturer should have designed a

good *agc* system to handle the very strong signals. This is not always the situation. Some TV sets use only simplified *agc* circuits that are not capable of governing the amplification under very strong signal conditions. Most frequently they favor the weak signal reception conditions. Thus the problem arises. And the technician all too frequently does not recognize it as one to be corrected outside the receiver and often may consider it as a fault or a failure in the circuitry.

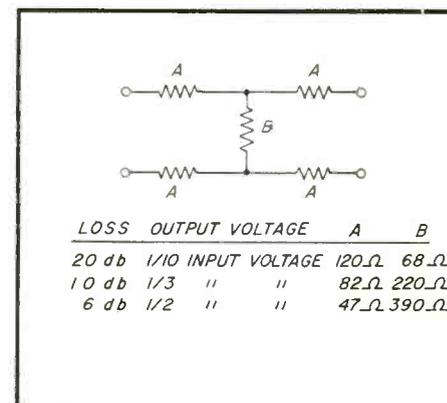


Fig. 3—Attenuator pad values.

Fig. 3 shows a basic H pad and the values of resistors that will provide different amounts of attenuation. It is desirable to have a set of these pads to use for checking purposes when new antennas are installed in strong signal areas. The insertion of one of these attenuation pads can easily remove buzz from some receivers due to an over-driven condition as well as correct for over-driven pictures.

The unfortunate thing about this is that many technicians refuse to believe that in certain cases of antenna installations pads are necessary and required to reduce the signal as applied to the receiver. This is even more important when a channel puts up a new antenna or increases its radiating power. This problem is also very important when making antenna installations for color receivers. Excessive signals can cause considerable difficulty with color receivers. This is of such concern that color receiver manufacturers are providing attenuation pads at the rear of their receivers with switch arrangements for changing the insertion loss with different pads.

AMPLIFIERS—(Audio, Hi-Fi, P. A.)

Allied Radio Corp.	100 N. Western Ave., Chicago 80, Ill.
Blonder-Tongue Labs, Inc.	526 North Ave., Westfield, N. J.
Bogen & Co., Inc., David	29 Ninth Ave., New York 14, N. Y.
Transvision, Inc.	360 North Ave., New Rochelle, N. Y.

ANTENNAS

Amphenol Electronics Corp.	1830 S. 54th Ave., Chicago 50, Ill.
Channel Master Corp.	Ellenville, New York
Clear Beam Antenna Corp.	Canoga Park, Calif.
Cornell-Dubilier Electric Corp.	South Plainfield, New Jersey
Electrend Products Corp.	St. Joseph, Mich.
Finney Company, The	4612 St. Clair Ave., Cleveland 3, Ohio
Hi-Lo TV Antenna Corp.	3540 N. Ravenswood Ave., Chicago 13, Ill.
Holloway Electronics Corp.	Fort Lauderdale, Fla.
JFD Manufacturing Co., Inc.	6127 16th Ave., Brooklyn 4, N. Y.
Philco Corp.	Philadelphia 34, Pa.
Radiart Corp.	3455 Vega Ave., Cleveland 13, Ohio
Radio Merchandise Sales, Inc.	2016 Bronxdale Ave., New York 60, N. Y.
Snyder Mfg. Co.	22nd & Ontario Sts., Philadelphia 40, Pa.
Technical Appliance Corp.	Sherburne, New York
Telco Electronics Mfg. Co.	919 Taylor Ave., Rockford, Ill.
Telrex, Inc.	Asbury Park, N. J.
Walsco Electronics Corp.	3602 Crenshaw Blvd., Los Angeles 16, Cal.
Winegard Company	3000 Scotten Blvd., Burlington, Iowa

ANTENNA ACCESSORIES

Alliance Manufacturing Co.	Alliance, Ohio
Amphenol Electronics Corp.	1830 S. 54th Ave., Chicago 50, Ill.
Blonder-Tongue Labs, Inc.	526 North Ave., Westfield, N. J.
Channel Master Corp.	Ellenville, New York
General Cement Mfg. Co.	919 Taylor Ave., Rockford, Ill.
I. E. Manufacturing Co.	325 N. Hoyle Ave., Chicago 12, Ill.
JFD Manufacturing Co., Inc.	6127 16th Ave., Brooklyn 4, N. Y.
Jontz Manufacturing Co.	1101 E. McKinley Ave., Mishawaka, Ind.
Kenwood Engineering Co.	265 Colfax Ave., Kenilworth, N. J.
Mosley Electronics Corp.	8622 St. Charles Rock Rd., St. Louis 14, Mo.
Mueller Electric Co.	1583 E. 31st Street, Cleveland 14, Ohio
Philco Corp.	Philadelphia 34, Pa.
Radiart Corp.	3455 Vega Ave., Cleveland 13, Ohio
Radio Merchandise Sales, Inc.	2016 Bronxdale Ave., New York 60, N. Y.
South River Metal Products Co., Inc.	South River, New Jersey
Superec Electronics Corp.	6 Radford Place, Yonkers, N. Y.

BATTERIES

Burgess Battery Co.	Freeport, Illinois
RCA (Tube Div.)	Harrison, New Jersey

BOOKS & MANUALS

Cisin, Harry G.	Amagansett, N. Y.
Cowan Publishing Corp.	67 West 44th Street, New York 36, N. Y.
Electronic Publishing Co.	180 N. Wacker Drive, Chicago 6, Ill.
Rider, John F., Publisher	480 Canal Street, New York 13, N. Y.
Sams, Howard W. & Co., Inc.	2201 E. 46th Street, Indianapolis 5, Ind.
United Catalog Publishers	110 Lafayette Street, New York 13, N. Y.

BUSINESS ORDER FORMS

Electronic Publishing Co.	180 N. Wacker Drive, Chicago 6, Ill.
Oelrich Publications	4308 N. Milwaukee Ave., Chicago 41, Ill.

CAPACITORS

Aerovox Corp.	New Bedford, Mass.
Astron Corp.	255 Grant Ave., East Newark, N. J.
Centralab, Div. of Globe-Union	900 E. Keefe Ave., Milwaukee 1, Wis.
Cornell-Dubilier Electric Corp.	South Plainfield, New Jersey
Eric Resistor Corp.	Eric, Pa.
Illinois Condenser Co.	1616 N. Throop St., Chicago 22, Ill.
Planet Sales Corp.	225 Belleville Ave., Bloomfield, N. J.
Pyramid Electric Co.	1445 Hudson Blvd., North Bergen, N. J.
Sprague Products Co.	71 Marshall Street, North Adams, Mass.

CHEMICALS, SPRAYS, LUBRICANTS

Electronic Chemical Corp.	813 Communipaw Ave., Jersey City 4, N. J.
General Cement Mfg. Co.	919 Taylor Ave., Rockford, Ill.
Great Eastern Mfg. Co.	165 Remsen Ave., Brooklyn 12, N. Y.
Krylon, Inc.	Ford & Washington Sts., Norristown, Pa.
Quietrol Co., Inc.	Spartanburg, South Carolina
Superec Electronics Corp.	6 Radford Place, Yonkers, N. Y.
Telematic Industries, Inc.	16 Howard Ave., Brooklyn 21, N. Y.
Walsco Electronics Corp.	3602 Crenshaw Blvd., Los Angeles 16, Cal.

CHOKES, COILS & TRANSFORMERS (RF)

Acme Electric Corp.	468 Water Street, Cuba, New York
Chicago Standard Transformer Corp.	3501 Addison Street, Chicago 18, Ill.
Merit Coil & Transformer Corp.	4427 N. Clark Street, Chicago 40, Ill.
Miller, J. W. Company	5917 S. Main Street, Los Angeles 3, Cal.
Superec Electronics Corp.	6 Radford Place, Yonkers, N. Y.
Triad Transformer Corp.	4055 Redwood Ave., Venice, Calif.

CHOKES, COILS & TRANSFORMERS (Audio and Line Freq.)

Acme Electric Corp.	468 Water Street, Cuba, New York
Chicago Standard Transformer Corp.	3501 Addison Street, Chicago 18, Ill.
Delco Radio (Div. of General Motors Corp.)	Kokomo, Indiana
Merit Coil & Transformer Corp.	4427 N. Clark Street, Chicago 40, Ill.
Perma-Power Company	4721 N. Damen Ave., Chicago 25, Ill.
Triad Transformer Corp.	4055 Redwood Ave., Venice, Calif.

CHOKES, COILS & TRANSFORMERS (Deflection & Focusing)

Acme Electric Corp.	468 Water Street, Cuba, New York
Chicago Standard Transformer Corp.	3501 Addison Street, Chicago 18, Ill.
Great Eastern Mfg. Co.	165 Remsen Ave., Brooklyn 12, N. Y.
Merit Coil & Transformer Corp.	4427 N. Clark Street, Chicago 40, Ill.
Perma-Power Company	4721 N. Damen Ave., Chicago 25, Ill.
Ram Electronic Sales Co.	Irvington, New York
Superec Electronics Corp.	6 Radford Place, Yonkers, N. Y.
Triad Transformer Corp.	4055 Redwood Ave., Venice, Calif.

CONNECTORS, PLUGS

Blonder-Tongue Labs, Inc.	526 North Ave., Westfield, N. J.
Cannon Electric Co.	P. O. Box 275, Los Angeles 31, Calif.
Eby Sales Co. of N. Y.	130 Lafayette Street, New York 13, N. Y.
General Cement Mfg. Co.	919 Taylor Ave., Rockford, Ill.
Mosley Electronics	8622 St. Charles Rock Rd., St. Louis 14, Mo.
Radio Merchandise Sales, Inc.	2016 Bronxdale Ave., New York 60, N. Y.

FUSES

Bussmann Mfg. Co.	University and Jefferson, St. Louis 7, Mo.
Littelfuse, Inc.	4751 N. Ravenswood Ave., Chicago 40, Ill.

SERVICE DEALER and ELECTRONIC SERVICING • AUGUST, 1956

BUYER'S DIRECTORY OF ADVERTISED PRODUCTS

• This department is an additional service to our readers and advertisers. It is not intended to cover all products in all categories, nor is it intended to cover all products made by any manufacturer.

• The classifications are broad. Under each is listed the name and address of only those manufacturers who have, in the recent past, or who are currently advertising these particular products in this publication.

• This service is not a part of the advertiser's contract. The listings may change in future issues. Every reasonable precaution is taken to avoid errors and omissions.

HARDWARE

I. E. Manufacturing Co.	325 N. Hoyle Ave., Chicago 12, Ill.
Kenwood Engineering Co.	265 Colfax Ave., Kenilworth, N. J.
Mueller Electric Co.	1583 E. 31st Street, Cleveland 14, Ohio
South River Metal Products Co., Inc.	South River, New Jersey
Television Hardware Mfg. Co.	919 Taylor Ave., Rockford, Ill.
Walsco Electronics Corp.	3602 Crenshaw Blvd., Los Angeles 16, Cal.

MICROPHONES, Stands & Accessories

American Microphone Co.	370 S. Fair Oaks Ave., Pasadena 3, Cal.
Atlas Sound Corp.	1446 39th Street, Brooklyn 18, N. Y.
Shure Bros., Inc.	222 Hartrey Avenue, Evanston, Ill.

PHONOGRAPH NEEDLES

Jensen Industries, Inc.	342 S. Wood Street, Chicago 12, Ill.
Permo, Inc.	6415 N. Ravenswood Ave., Chicago 26, Ill.
Reotone Corp.	52-35 Barnett Ave., Long Island City 4, N. Y.
Walco-Electrovox Co., Inc.	60 Franklin Street, East Orange, N. J.

PHONOGRAPH PICKUPS & CARTRIDGES

American Microphone Co.	370 S. Fair Oaks Ave., Pasadena 3, Cal.
Electro-Voice, Inc.	Buchanan, Michigan
Shure Brothers, Inc.	222 Hartrey Avenue, Evanston, Ill.
Sonotone Corp.	Elmsford, New York

POWER SUPPLIES (Converters & Inverters)

American Television & Radio Co.	300 East First St., St. Paul 1, Minn.
Electro Products Labs, Inc.	4501 N. Ravenswood Ave., Chicago 40, Ill.
Perma-Power Company	4721 N. Damen Ave., Chicago 25, Ill.
Vokar Corporation	Dexter 2, Michigan

RESISTORS & CONTROLS

Aerovox Corp.	New Bedford, Mass.
Centralab, Div. of Globe-Union	900 E. Keefe Ave., Milwaukee 1, Wis.
Claroostat Mfg. Co., Inc.	Dover, New Hampshire
Delco Radio, Div. of General Motors Corp.	Kokomo, Indiana
Eric Resistor Corp.	Eric, Pa.
International Resistance Co.	401 N. Broad St., Philadelphia 8, Pa.

SEMI-CONDUCTORS

CBS-Hyltron	100 Endicott Street, Danvers, Mass.
Federal Telephone & Radio Corp.	100 Kingsland Road, Clifton, N. J.
General Electric Co.	Schenectady, New York
Philco Corp.	Philadelphia 34, Pa.
RCA (Tube Div.)	Harrison, New Jersey
Raytheon Mfg. Company	Newton, Mass.
Tarzian Inc., Sarks	415 N. College Ave., Bloomington, Ind.
Tung-Sol Electric, Inc.	95 Eighth Ave., Newark 4, N. J.

SERVICING AIDS

Allied Radio Corp.	100 N. Western Ave., Chicago 80, Ill.
American Phenolic Corp.	1830 S. 54th Ave., Chicago 50, Ill.
Belden Manufacturing Co.	4647 W. Van Buren St., Chicago 80, Ill.
Blonder-Tongue Labs, Inc.	526 North Ave., Westfield, N. J.
Colman Tool & Machine Co.	P. O. Box 7026, Amarillo, Tex.
Columbia Wire & Supply Co.	2850 Irving Park Road, Chicago 18, Ill.
Electric Soldering Iron Co.	Deep River, Conn.
Electronic Publishing Co.	180 N. Wacker Drive, Chicago 6, Ill.
General Cement Mfg. Co.	919 Taylor Ave., Rockford, Ill.
Mall Tool Company	7740 South Chicago Ave., Chicago 19, Ill.
Oelrich Publications	4308 N. Milwaukee Ave., Chicago 41, Ill.
Quietrol Co., Inc.	Spartanburg, South Carolina
Ram Electronic Sales Co.	Irvington, New York
Tele-Scopic Products, Inc.	215 W. 33rd Street, New York 1, N. Y.
Ungar Electric Tools, Inc.	P. O. Box 312, Venice, Calif.
United Catalog Publishers	110 Lafayette Street, New York 13, N. Y.
Vaco Products Co.	317 E. Ontario Street, Chicago 11, Ill.
Wall Mfg. Co.	Grove City, Pa.
Weller Elec. Corp.	160 N. 15 St., Phila., Pa.
Wen Products, Inc.	5806 Northwest Highway, Chicago 31, Ill.
Xcelite, Inc.	Thorne Ave. and Bank St., Orchard Park, N. Y.
Yeats Appliance Dolly Sales Co.	2133 N. 12th Street, Milwaukee 5, Wis.

SPEAKERS (including phones)

Atlas Sound Corp.	1446 39th Street, Brooklyn 18, N. Y.
Delco Radio, Div. of General Motors Corp.	Kokomo, Indiana
Jensen Mfg. Company	6601 S. Laramie Ave., Chicago 38, Ill.

North American Philips Co., Inc.	100 East 42nd Street, New York 17, N. Y.
Oxford Electric Corp.	3911 S. Michigan Ave., Chicago 15, Ill.
Philco Corp.	Philadelphia 34, Pa.
Quam-Nichols Company	Marquette Rd. & Prairie Ave., Chicago 37, Ill.
Telex	Telex Park, St. Paul, Minn.
University Loudspeakers, Inc.	80 S. Kenosca Ave., White Plains, N. Y.

SPEAKER ENCLOSURES

Jensen Mfg. Company	6601 S. Laramie Ave., Chicago 38, Ill.
Transvision, Inc.	460 North Ave., New Rochelle, N. Y.
University Loudspeakers, Inc.	80 S. KENSICO AVE., White Plains, N. Y.

TEST EQUIPMENT & INSTRUMENTS

American Scientific Development Co.	334 S. Main St., Fort Atkinson, Wis.
B & K Manufacturing Co.	3731 N. Southport, Chicago 13, Ill.
Central Electronics, Inc.	1247 Belmont Ave., Chicago, Ill.
Electronic Instrument Company (EICO)	84 Withers Street, Brooklyn 11, N. Y.
Electronic Test Instrument Corp.	13224 Livernois Avenue, Detroit 38, Mich.
General Electronic Research Co.	Whitewater, Wis.
Heath Company, The	Benton Harbor, Michigan
Hickok Electrical Instrument Co.	10533 Dupont Ave., Cleveland 8, Ohio
Hyon Electronics, Inc.	320 S. Arroyo Parkway, Pasadena, Calif.
Jackson Electrical Instrument Co.	16 S. Patterson Blvd., Dayton 2, Ohio
Leitch Engineering Co.	326 Lincoln St., Manchester, N. H.
Moss Electronic Distributing Co., Inc.	38 Murray Street, New York 7, N. Y.
Phaestron Company	151 Pasadena Ave., South Pasadena, Calif.
Philco Corp.	Philadelphia 34, Pa.
Precision Apparatus Co., Inc.	70-31 84th Street, Glendale 27, L. I., N. Y.
Probescope Co.	44-05 30th Ave., Long Island City 3, N. Y.
Radio City Products Co., Inc.	Centre & Glendale Sts., Easton, Pa.
Research Inventions & Mfg. Co.	617 F Street, N. W., Washington 1, D. C.
Seco Mfg. Co.	5015 Penn Avenue, South, Minneapolis, Minn.
Simpson Electric Company	5200 W. Kinzie Street, Chicago 44, Ill.
Superior Instruments Co.	2435 White Plains Rd., New York 67, N. Y.
Telematic Industries, Inc.	16 Howard Ave., Brooklyn 21, N. Y.
Teletest Instrument Corp.	31-01 Linden Place, Flushing 54, N. Y.
Triplet Electrical Instrument Co.	Bluffton, Ohio
Weston Electrical Instrument Corp.	614 Freligh Avenue, Newark 5, N. J.
Winston Electronics, Inc.	4312 Main Street, Philadelphia 27, Pa.

TOOLS

Electric Soldering Iron Co.	Deep River, Conn.
General Cement Mfg. Co.	919 Taylor Ave., Rockford, Ill.
Ohmite Manufacturing Co.	3640 W. Howard Street, Skokie, Illinois
Philco Corp.	Philadelphia 34, Pa.
Krauter & Co., Inc.	583 18th Avenue, Newark, N. J.
Mall Tool Company	7740 S. Chicago Ave., Chicago 19, Ill.
Tele-Scopic Products, Inc.	215 W. 33rd Street, New York 1, N. Y.
Ungar Electric Tools, Inc.	P. O. Box 312, Venice, Calif.
Vaco Products Co.	317 E. Ontario St., Chicago 11, Ill.
Wall Mfg. Co.	Grove City, Pa.
Walsco Electronics Corp.	3602 Crenshaw Blvd., Los Angeles 16, Cal.
Weller Elec. Corp.	160 N. 15 St., Phila., Pa.
Wen Products, Inc.	5806 Northwest Highway, Chicago 31, Ill.
Xcelite, Inc.	Thorne Ave. and Bank St., Orchard Park, N. Y.

TUBES—CRT & RECEIVING

Barry Electronics Corp.	512 Broadway, New York 12, N. Y.
CBS-Hyltron	100 Endicott St., Danvers, Mass.
Ceco Electronics Co.	Columbia Ave. and 18th, Irvington 11, N. J.
Delco Radio, Div. of General Motors Corp.	Kokomo, Indiana
Federated Television Mart	513 Rogers Ave., Brooklyn 25, N. Y.
General Electric Co.	Schenectady, N. Y.
Philco Corp.	Philadelphia 34, Pa.
RCA (Tube Div.)	Harrison, N. J.
Raytheon Mfg. Company	Newton, Mass.
Tung-Sol Electric, Inc.	95 Eighth Ave., Newark 4, N. J.

VIBRATORS

American Television & Radio Co.	300 E. First Street, St. Paul 1, Minn.
Cornell-Dubilier Electric Corp.	South Plainfield, New Jersey
Delco Radio, Div. of General Motors Corp.	Kokomo, Indiana
Radiart Corp.	3455 Vega Ave., Cleveland 13, Ohio
Vokar Corporation	Dexter 2, Michigan

WIRE—CABLE—HARNESSES

American Phenolic Corp.	1830 S. 54th Ave., Chicago 50, Ill.
Belden Manufacturing Co.	4647 W. Van Buren St., Chicago 80, Ill.
Columbia Wire & Supply Co.	2850 Irving Park Road, Chicago 18, Ill.
Eby Sales Co. of N. Y.	130 Lafayette St., New York 13, N. Y.
Federal Telephone & Radio Corp.	100 Kingsland Road, Clifton, N. J.
Jersey Specialty Co.	Burgess Place, Mountain View, N. J.

Ask For Sprague By Catalog Number

Know what you're getting... get exactly what you want. Don't be vague... insist on

Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 71 Marshall Street, No. Adams, Mass.

DON'T JUST SAY CAPACITORS

SPRAGUE®
WORLD'S LARGEST CAPACITOR MANUFACTURER

SERVICE DEALER

and ELECTRONIC SERVICING

AS ADVERTISED IN
STANDARD RATE & **BPA**
DATA SERVICE.

69,265*

CIRCULATION

*(Publisher's Statement, December 31, 1955, submitted to BPA and subject to audit. Over 47,000 of this 69,000 is paid circulation.)

At present, and in 12 of the past 16 years, SERVICE DEALER and ELECTRONIC SERVICING has provided advertisers with much more monthly circulation amongst:

Radio-TV service firm owners

Dealers operating service departments
Independent radio-TV servicemen
Electronics equipment servicemen
Communications equipment servicemen

than any other service field publication.

SERVICE DEALER and ELECTRONIC SERVICING is the only magazine reaching upwards of 95% of the nation's service shop owners, dealers operating their own service departments, and independent full-time servicemen.

SELLING THE MARKET

If your products are used in any type of radio, TV, industrial electronics or commercial communications equipment . . . if you want to sell your products to the service firms and servicemen who maintain the many thousands of equipments now in use . . . from a radio or TV set to ship-to-shore or 2-way mobile radios or complex electronics devices of all types—then advertise in SERVICE DEALER and ELECTRONIC SERVICING.

RADIO-TV SERVICING

Our readers accounted for 84% of all radio-TV service work done last year. This group of professional servicemen bought for use and resale as replacements, and for their shop operations, over \$1 billion worth of tubes, components, accessories and test equipment during the past year.

INDUSTRIAL ELECTRONICS

Aside from home, auto radio and TV servicing, almost 2,000 paid subscribers to SERVICE DEALER and ELECTRONIC SERVICING are engaged solely in servicing and maintenance of industrial electronics and commercial communications equipment. This highly specialized group of "industrial electronics servicemen" — as differentiated from the regular category of radio-TV servicemen—also bought almost \$1 billion worth of tubes, components, instruments, etc., last year in performing their routine duties.

EDITORIAL SCOPE & STAFF

Our editorial staff, each man having from 14 to 29 years of practical experience as radio-TV servicemen (plus many years of electronic teaching background) is the largest and most qualified group of its kind now editing any serviceman's publication. SERVICE DEALER and ELECTRONIC SERVICING is the only publication regularly covering every phase of radio, television, industrial electronics and commercial communications servicing. It is the only technical serviceman's magazine using the "King-Size" format.

COWAN PUBLISHING CORP.,
67 WEST 44TH STREET,
NEW YORK 36, N. Y.

NEW-NEW-NEW

Get your copy of the

ERIE

D-56 CATALOG

Now Available at
ERIE DISTRIBUTORS
Everywhere




More complete than ever, the new ERIE D-56 Catalog not only describes and illustrates the complete line of ERIE Electronic Components but also includes CORNING GLASS and ERIE-

TEFLON items, that are available through ERIE Distributors. Get your copy of the ERIE D-56 Catalog now at your ERIE Distributor; if he cannot supply it, write us, giving his name.

ERIE
electronics

ERIE ELECTRONICS DISTRIBUTOR DIVISION
ERIE RESISTOR CORPORATION
Main Offices: ERIE, PA.
Factories: ERIE, PA. • LONDON, ENGLAND • TRENTON, ONTARIO

WORKBENCH [from page 35]

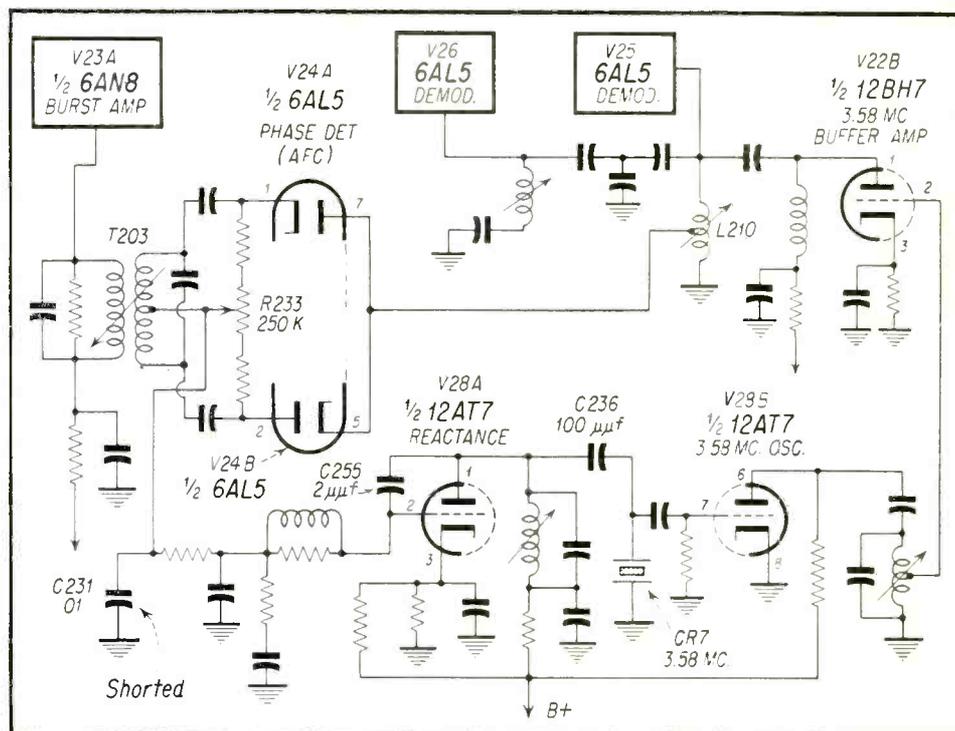

V28B is a shunt fed crystal stabilized 3.58 mc oscillator. The oscillator signal voltage is fed through C236 to the plate of the reactance tube, V28A, and arrives at the grid, pin #2, through C255, 2 μf. Due to capacitor action the oscillator signal voltage at the grid leads the oscillator signal applied at the plate. A leading plate current is thus produced which makes the entire reactance tube appear as a condenser to the crystal oscillator. A larger reactance tube plate current, for example, is caused by a more positive control grid voltage which causes the tube to act as a larger condenser and tunes the crystal oscillator to a lower frequency. The phase detector (afc), V24 produces a dc output voltage when the phase and/or frequency of the local 3.58 mc oscillator is not exactly that of the color burst synchronizing signal. The local oscillator signal is amplified by the buffer amplifier V22B and is fed by means of a tap on L210 to the phase detector V24A & B. (The output of the buffer amplifier is also fed to the demodulators V25 and V26.)

During the color transmission the burst signal is also fed to the phase detector through the tuned transformer T203. The simultaneous injection of the

two ac signals creates resultant voltages (added vectorially) which affect the two diodes differently. The resultant dc output voltages is supplied to the control grid of the reactance tube whose tuning action pulls the oscillator into correct phase and frequency.

Knowing all these facts voltages were measured first at the plates and cathodes of V28A & B. The voltages measured correctly at these points, R233, 250K, the afc balance potentiometer was adjusted, but would not bring the color picture into synchronization. It seemed to have no effect. R233 was next resistance checked. A reading of zero ohms was measured on the meter from the center arm to ground. Condenser C231 (.01 μf) was then clipped off the center arm connection. The center arm was again resistance checked to ground. The meter now read infinite. C231 was measured and found to be shorted. This condenser obviously shorted the dc corrective voltage supplied by the phase detector, V24A & B to ground. C231 was replaced with a new .01 μf condenser. R233, the afc balance control was adjusted for a normal color picture, (so that there were no horizontal bands of color moving vertically). The receiver now functioned properly.

3 big reasons why **QUIETROLE**
Reg. U. S. Pat. Off.

is "The Choice of Better Service Dealers Everywhere"

1 MERIT
2 QUALITY
3 RELIABILITY

The original product for quieting noisy controls and switches . . . the universal lubricant-cleaner for TV and radio . . .

Say "QUIETROLE" to your distributor . . . be sure you get it.

NO GUM!
NO GOD!
NO GRIME!

Carried by recognized jobbers . . . everywhere!

manufactured by

QUIETROLE COMPANY INC.
Spartanburg, South Carolina

IN CANADA: Active Radio & TV Distributors
58 Spadina Ave., Toronto 28, Ont.

UNITED COMMUNITY CAMPAIGNS
Give...the United way

RIDER SPEAKS

[from page 13]

and my wife is slightly more perturbed. I decide that maybe the best thing to do is to go to the club and call another mechanic after I get there. So we disconnect the charged battery and, lo and behold, the engine continues running and we go to the club.

Now I call another mechanic and describe my difficulty. Within 30 minutes he's at the car. After looking at the ammeter and banging the voltage regulator box cover, he declares the generator bad; it must come off. Being stubborn, I ask him if he would check the generator output. No, he has no measuring device, but he knows the generator is bad and must be replaced.

I remain stubborn. Two days later I get the car back to town and to my regular mechanic. I still have the same battery and the same generator, but a new set of brushes; the car runs like new.

Don't go away, there's more.

The day I get the car fixed my wife asks me to visit a watch repairman with her. (Several years ago I demonstrated my appreciation of her endurance in living with me for 25 years by buying her a watch from a very reliable establishment.)

Something had happened to the watch early in June and it needed repair. I suggested that she take it back to the store where I had purchased it. This she did but (unknown to me), when told the repairs would take two weeks, she took it to a watch repairman in the neighborhood. He operated on it, and within a brief period of four weeks she had made four separate visits to him, picking up the watch and returning it. It would run for about 48 hours, and then stop. Each time he got it started again he gave a one-year guarantee. She now owned four guarantees on a non-functioning watch that was

New **PERFO** System TV tube tester
CANNOT BECOME OBSOLETE!




DynaMatic tube tester uses perforated plastic cards to automatically set up socket pin connections & test voltages.

For the first time AUTOMATION comes to TV service! No more waiting for new roll charts for 6 months to a year, every time new tubes come out. And no more multiple socket panels that become obsolete as soon as a new tube is made. The DynaMatic's 'PERFO-System' allows you to test the newest tubes and all future tubes as soon as they're out!

- Speed! Tests complete set of tubes in 15 minutes!
- Compact! Smallest and lightest mutual conductance tester made! Easy to carry.
- Permits full-complement tube testing which must result in increased tube sales.

SEE IT AT YOUR JOBBER IN SEPT.

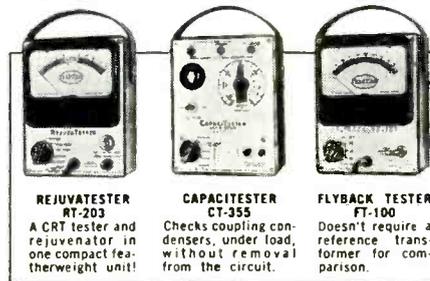

REJUVANATOR RT-203
A CRT tester and rejuvenator in one compact featherweight unit!

CAPACITESTER CT-355
Checks coupling condensers, under load, without removal from the circuit.

FLYBACK TESTER FT-100
Doesn't require a reference transformer for comparison.

TELETEST

Teletest Instrument Corporation
121-08 14th Road
College Point 56, New York

FREE LITERATURE REQUEST FORM

Valid for 6 weeks only, expires **9/1/56**
Business Card **MUST** be attached

Circle numbers for Free Technical Literature or Information on New Equipment:

801 802 803 804 805 806

807 808 809 810 811 812

813 814 815 816 817 818

If you want more details on products advertised in this issue fill in below:

Page Product

Page Product

Page Product

Name

Title


Company

Co. Address

City Zone

State

IDEA OF THE MONTH

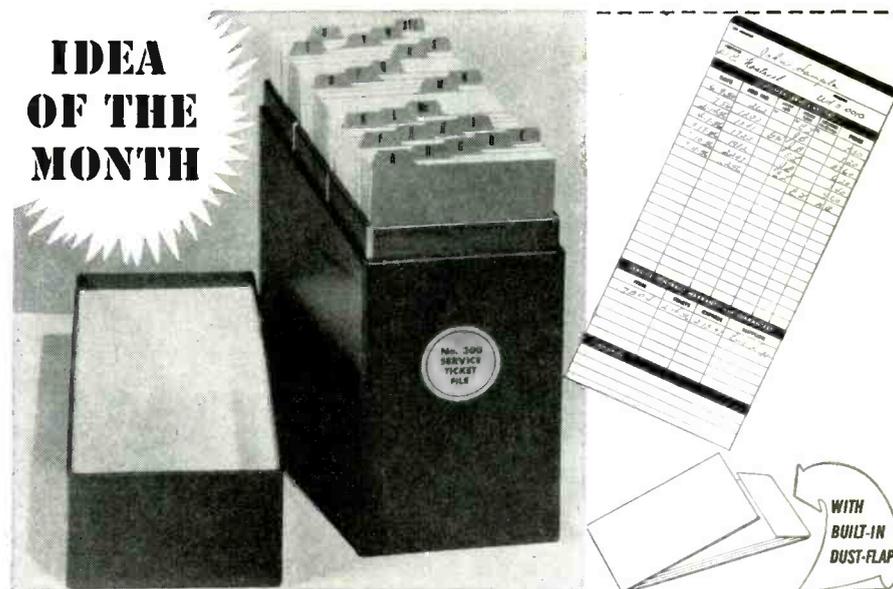

#300 SERVICE TICKET FILE

A new practical low cost system for filing customers service call and shop job tickets alphabetically in individual file folders. For instant reference a form is printed on the face of each folder for summarizing contents. File case is of heavy cardboard construction in attractive brown simulated leather finish. File folders are of heavy cream tag stock with extra flap feature for fast reference (see inset) . . . smartly printed in brown. A to Z file guides are heavy press board. **FILE CASE SIZE 4 7/8" x 10 1/8" x 12 1/2"**

AT YOUR ELECTRONIC PARTS JOBBER

(200 FOLDER CAPACITY)

- #300 SERVICE TICKET FILE SYSTEM \$7.40 (includes case, guides and 100 folders)
- #301 BOX OF 100 FILE FOLDERS \$2.95
- #302 SET OF FILE GUIDES \$1.95

OEIRICH PUBLICATIONS
4308 N. MILWAUKEE AVE. • CHICAGO 41, ILL.
Send me FREE sample file folder and catalog.

Name
Address
City Zone State

Only the 5 TOP-QUALITY brands of

STANDARD BRAND TUBES

AT SENSIBLE PRICES

• 90 Day RETMA Guarantee • Brand New
• 1st quality only • Individually boxed

FREE! Newest handy air-mail order form for your ordering convenience.—Free!
• Lists ALL popular TV & radio types.
• Makes mail-ordering a real pleasure.
• Orders over \$25.00 (with remittance) postpaid

0Z4	.50	6AS6	2.25	7F8	1.20
1AX2	.15	6AS8	1.20	7G7	1.15
1B3GT	.95	6AT6	.60	7H7	.85
1H5GT	.80	6AT8	1.10	7J7	1.35
1L4	.85	6AU4GT	1.10	7K7	1.20
1L6	1.10	6AU5GT	1.25	7L7	1.15
1L8	1.00	6AU6	.75	7N7	.95
1L8A	1.00	6AU7	.90	7Q7	1.00
1LB4	1.00	6AV5GT	1.20	7R7	1.30
1LC5	1.00	6AV6	.60	7V7	1.30
1LC6	1.00	6AW8	1.20	7W7	1.30
1LD5	1.00	6AX4GT	.90	7X7	1.00
1LE3	1.00	6AX5GT	.90	7Y4	.70
1LG5	1.00	6BA6	.70	7Z4	.70
1LH3	1.00	6B7	.90	12A4	.85
1LNS	1.00	6BC4	1.60	12AL5	.70
1Q5GT	.95	6BC5	.75	12AQ5	.75
1Q5GT	1.15	6BC7	1.25	12AT6	.65
1R4	1.00	6BD5	1.40	12AT7	1.00
1R5	.85	6BD6	.75	12AU6	.70
1S4	1.00	6BE6	.75	12AU7	.85
1S5	.75	6BF5	.90	12AV6	.65
1T4	.85	6BF6	.70	12AV7	1.05
1T5GT	1.05	6BGG	1.85	12AW6	1.00
1U4	.80	6BH6	.90	12AX4GT	1.00
1U5	.75	6BJ6	.85	12AX7	.90
1V	.95	6BK5	1.15	12AY7	1.75
1V2	.70	6BK7A	1.15	12B7	.70
1X2B	1.00	6BL7GT	1.25	12BA4	.90
2AF4A	1.40	6BN6	1.15	12BA6	.70
2D21	1.00	6BQGTA	1.45	12BA7	.95
2X2	.50	6BQ7A	1.30	12BD6	.75
3A3	1.10	6BX7GT	1.25	12BB6	.75
3A4	.55	6BY5G	1.30	12BF6	.70
3A5	.80	6BZ6	.80	12BH7A	1.00
3AL5	.70	6BZ7	1.35	12BK5	1.10
3AUG	.75	6C4	.60	12B96GTB	1.45
3AV6	.65	6C5	.80	12BX7	.90
3BA6	.75	6CB5	4.50	12BY7A	1.05
3BC3	.90	6CBH	.75	12C7	1.10
3BE3	.75	6CD6G	1.90	12CA5	.80
3BN6	1.05	6CF6	.90	12CUG	1.45
3BY6	.90	6CG7	.90	12CL6	.80
3BZ6	.80	6CL6	1.20	12SA7GT	1.00
3CB6	.85	6CM6	.85	12SC7	.80
3CF6	.85	6CS6	.75	12SJ7	.75
3CS6	.80	6CU6	1.45	12SK7GT	1.30
3LF4	1.20	6DC6	.95	12SL7GT	1.00
3Q4	.85	6DE6	.80	12SN7GTA	.85
3Q5GT	1.00	6F5	.85	12SO7GT	.75
3S4	.80	6FGG	.80	12V6GT	.80
3V4	.85	6H6	.75	12W6GT	.95
4B07A	1.30	6J4	3.95	14A3	1.00
4BZ7	1.35	6J5	.75	14A5	1.50
5AM8	1.05	6J6	.70	14A7	.85
5AN8	1.10	6K6GT	.75	14A7F	1.00
5AQ5	.75	6K7	.90	14B6	.85
5AS8	1.10	6K8	1.25	14C7	1.00
5AT8	1.10	6L6GA	1.30	14E7	1.20
5AY3	1.15	6L6M	1.75	14E7F	1.30
5AW4	1.15	6M7	1.00	14F7	1.00
5AZ4	.60	6Q7	1.00	14F8	1.30
5BK7	1.10	6S4	.70	14H7	1.00
5J6	.95	6SR7	1.10	14N7	1.00
5T4	1.75	6SA7GT	.90	14Q7	.95
5T8	1.10	6SC7	1.00	14R7	1.30
5U4G	.70	6SF5	.75	14S7	1.25
5U4GB	.75	6SF7	.95	14W7	1.35
5U8	1.10	6SG7	1.00	19T8	1.20
5V4G	1.00	6SH7	.95	25AV5GT	1.30
5V6GT	.70	6SJ7M	.85	25AX4GT	1.10
5W4GT	.70	6SK7GT	.85	25B5	1.10
5X4G	.80	6SL7GT	1.00	25B06GTB	1.45
5X8	1.05	6SN7GTA/B	.90	25CD6GA	1.85
5Y3GT	.60	6SQ7GT	.75	25CU6	1.45
5Y4G	.65	6SR7	.75	25LG7	.75
5Z3	.90	6T4	1.30	25W4GT	.85
5Z4	1.25	6T8	1.10	25Z5	.80
6ARGT	1.10	6U8	1.10	25Z6GT	.85
6AB4	.70	6V3A	1.50	35A5	.75
6AC5GT	1.15	6V6GT	.75	35B5	.70
6AC7	1.15	6V6M	1.35	35C5	.70
6AD7G	1.55	6W4GT	.80	35L6GT	.65
6AF4	1.35	6W6GT	.95	35W4	.55
6AF6G	1.20	6X4	.55	35Y4	.75
6AG5	.80	6X5GT	.95	35Z5	.60
6AC7	1.35	6X8	1.20	41	.85
6AH4GT	1.00	6Y6G	.95	42	.75
6AH6V	1.05	7A5	.95	43	.85
6AJ5	1.75	7A6	.80	50A5	.75
6AK5	.80	7A7	.85	50B5	.75
6AK6	.60	7A8	.80	50C5	.75
6ALS	.85	7A9T	1.00	50L6GT	.75
6AL7GT	1.65	7AH7	1.00	50X6GT	.90
6AM4	1.55	7B4	.80	50Y6GT	1.00
6AM8	1.15	7B5	.70	50Y7GT	.90
6AN4	1.50	7B6	1.00	70L7GT	1.55
6AN5	3.50	7B7	.80	80	.65
6AN8	1.20	7B8	.90	117L7GT	2.50
6AQ5	.75	7C5	.80	117N/P7	2.00
6AQ6	.60	7C6	1.00	117Z3	.80
6AQ7GT	1.25	7C7	.85	117Z4GT	1.15
6AR5	.75	7E7	1.20	117Z6GT	1.15
6ASS	.80	7F7	.90	5642	1.00

We stock over 1000 types including Diodes, Transistors, transmitting and Special Purpose types.

TERMS: 25% with order, balance C.O.D. All merchandise guaranteed. F.O.B., N.Y.C.

BARRY ELECTRONIC CORP.
Dept. SD

512 Broadway, N. Y. 12, N. Y.

Call us day or night
24-hour telephone service
Walker 5-7000

back for repair for the fifth time.

So I go with her and get the fifth guarantee. This time the watch runs for less than 24 hours. This is the last straw for her (for me too), and she takes the timepiece back to the place where I had bought it. They send it to the factory. She waits two weeks, and peace reigns at home once more.

Don't go away, there's more.

My married daughter just moved into a new home. She reads advertisements and has equipped the house with a well known brand of kitchen appliances. (You know, refrigerator, washing machine, dishwasher—everything.) But the dishwasher wasn't installed, so she called the dealer who had sold her the equipment. He sent the repairman pronto, but the repairman could do nothing because he had no equipment with him. Said he would be back the next day.

Correction!

The June, 1956 issue of Service Dealer and Electronic Servicing on page 49 contained an erroneous description of the TeleTest Capacitester in the article, "Condenser Checkers." Part 2, by Steve Travis. The correct description of this device appeared in the October, 1955 issue of this magazine in the article entitled, "The Capacitester," by Sol Heller. The correct operation of the Capacitester, quoted in part from this article, is as follows:

"The leakage testing section of Capacitester employs a unique test set-up that is interesting enough to warrant description. This set-up is shown in simplified form in Fig. 1. A 'magic-eye' 6AF6 tube is used as an indicating device in conjunction with the condenser circuit under test. This circuit is shown in Fig. 2. Here point A corresponds to the B+ Jack Connection of Fig. 1; point B corresponds to the Grid Jack Connection; and ground corresponds to the B— Jack Connection. If the grid return of the stage

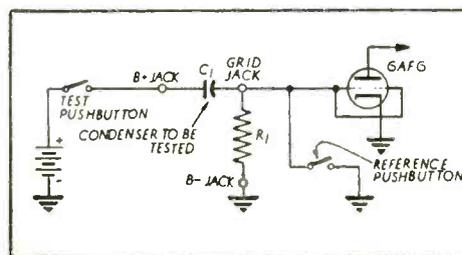


Fig. 1—Simplified circuit

A new man came, but he could do nothing, because the first guy had told him nothing about what had to be done, and he had no tools with him. Now my daughter called me. Could I do something? Did I know someone who could do something?

I don't know anything about dishwashers, but I do know someone in the firm that made the equipment. So I call my friend and he gets in touch with their service department right away. The man arrives two days later, but can't install the dishwasher because he has no equipment with him! Yes, it's installed now—about five weeks after all this started.

What's all this talk about incompetent TV service technicians? Sure, we have a few, but hardly enough to give us a monopoly.

Anyway, I'm glad July is coming to a close.

does not go directly to the ground, the B— Jack lead connects to the 'low' side of the grid resistor. Changes in the shadow-angle of this eye-tube are produced when leakage exists in the component under test."

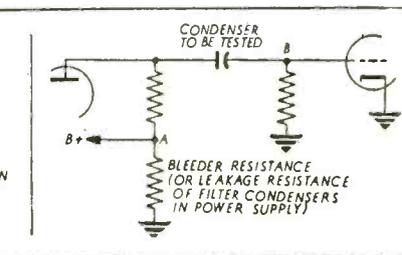


Fig. 2—Equivalent circuit

SERVICEMEN
WHO PUT PRIDE
IN THEIR WORK
"ALWAYS
SPECIFY
STANCOR"



CHICAGO STANDARD TRANSFORMER CORPORATION

3511 Addison Street • Chicago 18, Illinois

ASK FOR SPRAGUE BY CATALOG NUMBER

Know what you're getting... get exactly what you want. Don't be vague... insist on Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 71 Marshall Street, North Adams, Massachusetts.

DON'T JUST SAY
CAPACITORS
SAY

SPRAGUE

WORLD'S LARGEST CAPACITOR MANUFACTURER

SERVIS-ADES

by

TELE-SCOPIC PRODUCTS, INC.

215 W. 33rd St. • New York 1, N.Y.



ADJUST-
ABLE
3rd ARM

FOR HOLDING
CHASSIS IN
POSITION ON
WORK BENCH

\$5.50
each

Send checks or money orders only

Advertisers' Index

Aermotor Company	44
Amphenol Electronics Corporation	1
B & K Manufacturing Co.	19
Barry Electronics Corp.	48
Belden Manufacturing Co.	18
Blonder-Tongue Laboratories, Inc.	30
Bussmann Manufacturing Co.	15
CBS-Hytron	Cover 2
Channel Master Corp.	7, 8, 9
Chicago Standard Transformer Corp.	48
Cornell-Dubilier Elec. Corp.	2, 3
Erie Resistor Corp.	46
Heath Company	44
Jensen Manufacturing Company	35
Merit Coil & Transformer Corp.	37
Oelrich Publications	47
Phaestron Company	34
Philco Corporation	31
Planet Sales Corp.	42
Quietrol Company	47
RCA Batteries	Cover 4
Radiart Corporation	2, 3
Raytheon Manufacturing Co.	13
Rider, John F. Publisher	36
Sams, Howard W. & Co.	16
South River Metal Products Co.	43
Sprague Products Company	33, 45, 48
TeleTest Instrument Corp.	47
Tung-Sol Electric, Inc.	17
Weller Electric Corp.	Cover 3
Xcelite, Inc.	42

YOUR ELECTRONIC PARTS DISTRIBUTOR INVITES YOU TO



PARDNERS, HERE'S YOUR CHANCE . . . round up that old soldering gun or iron. Regardless of brand, age or condition it is worth \$2.00 TRADE-IN if you act now.

WANTED

all old soldering guns or irons
any brand or condition

**\$200 TRADE-IN
REWARD**

offer is limited . . . you must act now

REWARD

\$2.00 trade-in allowance on a
professional model D-550 gun

OFFERED

on every old soldering gun or iron

DEAD OR ALIVE

no matter what make or condition



CHECK YOUR GUNS

Get ready for the
Fall service rush.
Get ~~this~~ regular \$11.95
value for only \$9.95
AND SAVE \$2.00.

PROFESSIONAL MODEL D-550

**WELLER
Soldering Gun**

only **\$9.95** dealer net
with trade-in of any old soldering tool

DUAL HEAT • 200/275 WATTS



WELLER ELECTRIC CORP. • 601 Stone's Crossing Road, Easton, Pa.



Get your share of vacation dollars...

STOCK, PROMOTE AND SELL RCA RADIO BATTERIES NOW

Plenty of long, sunny vacation weeks—and battery-selling weeks—still to come. Matter of fact, portables are becoming a year-'round item and battery business is following suit. This clean, rapid turnover business is even easier when you sell 'em the radio-engineered batteries with the name they know—RCA. Now's the time to take inventory to be sure you're not out of stock on the popular types. Use RCA's sales-building promotional material. Put the RCA cartons out front—your quality-conscious customers will do the rest.



RADIO BATTERIES
RADIO CORPORATION OF AMERICA • HARRISON, N. J.

COWAN PUBLISHING CORP., 67 West 44th Street, New York 36, N. Y.

SERVICE DEALER
and **ELECTRONIC SERVICING**

IA 6F 244 16 SEP 57A
HERB'S TV
H A KAURANEN PROP
11666 HUBBELL
DETROIT 27 MICH