

Oct. 27 1934

A NEW AUTO SET

Price 15c Per Copy

# RADIO

REG. U.S. PAT. OFF.

# WORLD

The First National Radio Weekly  
657th Consecutive Issue — Thirteenth Year

## Ingenious Mobile, Universal PA System

### Superiority of Choke Input

# CRAFTSMANSHIP IN AN ALL-WAVE RECEIVER




An enormous amount of engineering work was put into the construction of this custom-built all-wave superheterodyne. See article on pages 12 and 13.
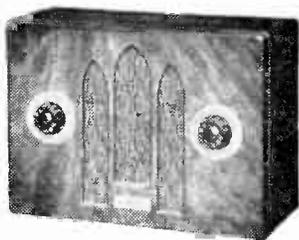
# 110 kc to 20 mgc Wired Set \$16.64 Complete with RCA Tubes 16

HERE is a tuned-radio-frequency model DIAMOND OF THE AIR for covering from 110 kc to 20 mgc, therefore truly all-wave, and costing you only \$16.64. And if you don't want such wide wave coverage, say, want only short waves, or only the broadcast band, the cost is even less. The difference is due to the cost of extra coils, that's all. The Series 1040 DIAMOND OF THE AIR is just the thing for those who want real reception at low cost, and who are willing to use plug-in coils, because in that way the cost of constructing the set is kept down. The results are of a high order.

This model uses one 25Z5 rectifier, one 43 tube, one 44 tube and one 77 tube. And the wired receiver is supplied completely equipped, ready for operation, with four RCA tubes and built-in speaker, in cabinet.



The series 1040 DIAMOND OF THE AIR is an all-wave instrument contained in an attractive midget cabinet and has tuning control and volume control. By using adapters operation may be enjoyed on 6-volt d-c supply, on 32-volt farm lighting systems, or on 220 volts a-c or d-c. The standard model is for 90-120 volts a-c operation, any commercial frequency, or on 90-120 volts d-c. Shipping weight, 8 lbs. Net price, complete, in cabinet, wired... \$16.64

Extreme pains have been taken to make this inexpensive all-wave DIAMOND OF THE AIR a truly worth-while product, despite the exceptionally low cost. We believe that it is the lowest-priced all-wave receiver in the world. And we know that users are fully satisfied with results. The instrument is really high grade.

Some examples of how pains were taken: The speaker used is a real dynamic. The broadcast-band coverage is from 540 to 1,710 kc, complete coverage, and even into some police frequencies. Antenna is built in. There is provision for phonograph or ear-phone attachment. The steel shield cabinet is of burl walnut Bakelite finish. The receiver is made to function well on 90-120 volts of any commercial frequency, i.e., 25, 40 or 50-60 cycles. The filtration is so good that operation on even 25 cycles is entirely satisfactory.

This receiver is sold only in cabinet, wired, and complete. No separate chassis is obtainable.

The adapters permit operation on automobiles, boats, farm light plants, steamships, etc.


Model 1040-A. 4-tube universal wired receiver, complete with four RCA tubes, and coil for the broadcast band only; contained in attractive midget cabinet; dynamic speaker; phonograph connecting posts. Shipping weight, 8 lbs. Net price... \$10.77

Model 1040-B. Same as above, except that four coils are supplied for the short waves only, 1,500 kc to 20 mgc. Shipping weight, 8 lbs. Net price... \$14.68

Model 1040-C. Same receiver, with broadcast coils, also low-frequency coils (to 110 kc) and short-wave coils (1,500 kc to 20 mgc). Shipping wgt., 8 lbs. Net price... \$16.64
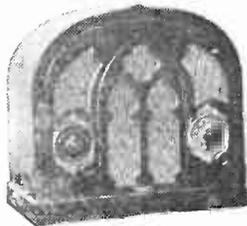
## 540-1,900 kc Set for AC Operation \$12.91

FOR those who are interested only in the broadcast band we have a splendid ac t-r-f model DIAMOND OF THE AIR that tunes from 540 to 1,900 kc, and therefore gets some police and amateur calls as well; that has frequency-calibrated and illuminated airplane dial; and that can be bought, complete with tubes, all wired and ready for operation of




Take your choice between the Model 1041-DL five-tube t-r-f broadcast DIAMOND OF THE AIR in a de luxe Gothic cabinet (shown above) at 59c extra, net price \$13.50, or exactly the same receiver in the oblong cabinet illustrated at right.

its self-contained dynamic speaker, at only \$12.91 net, for 50-60 cycles a.c., 105-120 volts. Model 1041-DL, at left, and Model 1041 at right, are the same sets except for cabinets. Not only may the receiver be bought already in its cabinet, but separately as a wired chassis, with speaker and tubes (less only cabinet). Besides, there is a model for 25 cycles a.c., 90-120 volts, and another for 220 volts a.c., 50-60 cycles. This is a tuned-radio-frequency receiver, five-tube model, using two 6D6, one 6C6, one 42 and one 80. It will be noticed that the economical and electrically strong 6-volt series tubes are used in the receivers proper. The primary power consumption is 55 watts. Not only is this a fine receiver, but it is made right, and every attention has been paid to detail. The airplane type dial is frequency-calibrated, so that the frequencies are read directly. There is provision for phonograph connection. The cabinet is walnut. And the performance, from the viewpoint of sensitivity and electricity, is adequate even for exacting needs, despite the sensationally low price, only \$12.91 net. This price admittedly seems out of all reason, compared to satisfactory performance, and yet the answer is found in the great popularity of this particular model. And, just as a hint, it makes a dandy and appreciated gift.



The oblong cabinet in which the 1041 is housed. The complete receiver, with speaker and tubes, costs only \$12.91 in the cabinet illustrated above. The price is F.O.B. Sandusky, O., which applies to all prices quoted. See notice at bottom of this advertisement. Study the lines of the two cabinets into which the same chassis is put and select the one that better suits your living room, parlor, bedroom or den.

## DUAL-WAVE DIAMOND OF THE AIR

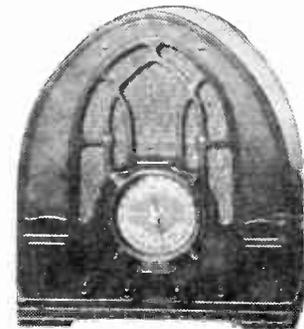

Dual-wave DIAMOND OF THE AIR, Model 1043. Covers broadcast band and also one short-wave band, 55 to 18 meters. Equipped with automatic volume control, manual volume control, airplane illuminated dial calibrated in frequencies, tone control, wired and supplied in Gothic cabinet with five RCA tubes, 50-60 cycle, 105-120-volt operation. Model 1043 net price F.O.B. Sandusky, O. \$18.80


THE most popular receiver today is the dual-wave type that covers the broadcast band and one short-wave band. On that one short-wave band are found the most important foreign stations. The coverage of the Model 1042 receiver is: broadcast band (550 to 1,500 kc) and short-wave band (5,500 to 16,000 kc). Therefore the short waves are tuned in from 18 to 55 meters, and that is the band on which the most important foreign program transmitters are working. Anybody who has not had his taste of short-wave reception will do well to be initiated with either of these two dual-band receivers. Model 1043 is illustrated at left, and is a superheterodyne for foreign and domestic reception. There are also the following valuable features: built-in antenna, frequency-calibrated dial, separate short-wave switch (no plug-in coils), dynamic speaker, figured walnut cabinet with figured Oriental overlays. And the price of Model 1042 (at right) is only \$18.21 net, F.O.B. Sandusky, O. (Shipping weight, 10 1/2 lbs.)

Model 1043, illustrated at left, has an airplane frequency-calibrated and illuminated dial, and besides can be obtained for battery operation and 32-volt operation. It is a superheterodyne of the switch type, covering the broadcast band and 18 to 55-meter short-wave band. It has automatic volume control and tone control. It is for 105-120 v. 50-60 cycle operation. Primary power consumption 60 watts; shipping weight, 17 1/2 lbs. Net price... \$18.80

Same as above, except for 25-cycle operation, order Model 1042-25. Net price... 20.27

Battery model (less batteries). Model 1042-B... 18.80

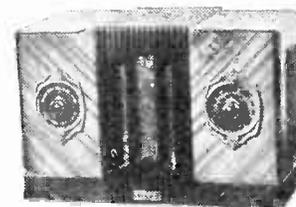32-volt model (for farm lighting plants; a.c.f. operation). Model 1042-FLO... 23.52



Dual-wave DIAMOND OF THE AIR. Model 1042, in a handsome oblong cabinet, 11 3/4 inches wide by 7 1/2 inches high by 6 1/4 inches front to back. This covers the broadcast band and also one short-wave band by switching, 55 to 18 meters. The net price of the illustrated model is \$18.21. The chassis, speaker, tubes may be obtained (complete less cabinet), by ordering Model 1042-CH @ \$14.97. A 220-volt adapter may be obtained at 88c extra. The receiver is a superheterodyne and provides splendid results both on the broadcast band on short waves.

### Ten Years of Experience Behind These Sets

The factory is at Sandusky, O., and all prices quoted are F.O.B. factory. You pay the transportation charges from Sandusky in all instances. You may select what carrier you desire and we will ship according to directions. Otherwise shipments will be made by Railway Express Agency. In asking for shipment by other means, please add transportation cost to the prices quoted. Express shipments are sent collect for the amount of the transportation charges. You will get receivers of the very highest type backed by 10 years' experience in making radio receivers. Remit to New York office full amount of net prices. If C.O.D. shipment is preferred, send 25% of net prices. Shipment will go C.O.D. for balance, at 2% above quoted net prices.

**GUARANTY RADIO GOODS CO., 145 West 45th Street, New York, N. Y.**



# Choke Input Superior For B Rectifier—Hum Increase Easily Overcome

IT is generally known that when choke-input filter is used improved regulation with lower peak current will be obtained. This is equivalent to removing  $C_1$  in a condenser-input filter, Fig. 1. The disadvantage of this omission is slightly larger hum distortion and a drop of the output voltage in the order of 20%. However, both these difficulties may be easily overcome.

The voltage loss may be made up by increasing the secondary voltage. With such an arrangement the power loss in the tube itself will be about the same or even less.

The choke-input increases the life of the rectifier tube and permits the use of a tube whose emission has fallen below the point at which the tube would be useful in a capacity-input filter. Since the current drain may vary considerably, the choke-input gives the much needed better regulation (Fig. 2).

### Value of Increased Capacity

The filtering action of  $C_1$  may be replaced in the other sections by increasing  $C_2$  and  $C_3$ , so that the overall filtering remains the same. It is of interest to know the value of  $C_x$  that must be added both to  $C_2$  and  $C_3$  to accomplish this.

The ratio of voltage fluctuation to the total voltage at the terminals of  $C_1$  may be expressed nearly by the equation:



$$\frac{E_r}{E} = \frac{1}{RfC_1}$$

where

- R = load resistance
- f = frequency of the rectified current
- $C_1$  = capacity in farads

and if the resistance of the choke is small compared to the load resistance, as the case usually is.

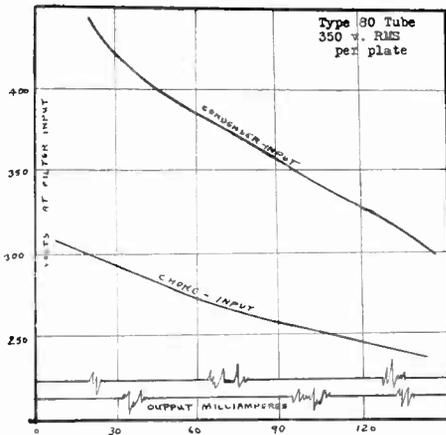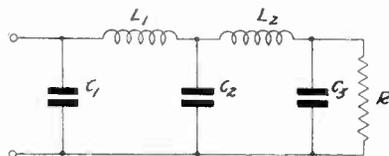For simplicity it may be assumed that all chokes and condensers are equal in value respectively. Then the ratio of voltage fluctuations to the total voltage



At top, Fig. 1, a condenser-input filter. At bottom, Fig. 2, a comparison of voltage output for the condenser and the choke input methods. The choke characteristic is about 20% lower in voltage, easily atoned for at the secondary.

in either choke condenser (such as  $C_2$ ,  $L_1$ ) combination may be expressed by the following formula:

- $L = L_1 = L_2$  = inductance in henries
- $C = C_2 = C_3$  = capacity in farads
- $E_r$  =

$$E = \frac{R + 6.28 fL (1 + 6.28 fRC)}{R}$$

### Equation Set Up

In the condenser-input filter the overall filtering action will be equal to the

product of the filtering action of  $C_1$ ,  $C_2$ ,  $L_1$  and  $C_3$ ,  $L_2$ , or mathematically:

$$\left( \frac{1}{RfC} \right) \left( \frac{R}{R + 6.28 fL (1 + 6.28 fRC)} \right)^2$$

If in the choke-input filter the overall filtering action is made equal to the above by increasing the capacities by  $C_x$ , then its overall filtering action may be expressed as:

$$\left( \frac{R}{R + 6.28 fL (1 + 6.28 fR [C + C_x])} \right)^2$$

Since the last two expressions are equal, they may be set up as an equation. This equation may be solved for  $C_x$ , giving this answer:

$$C_x = \sqrt{RfC} \left( \frac{1}{39.4 L} + \frac{1}{6.3 R} + \frac{C}{L} \right)$$

### Case of Average Set

In an average receiver we may assume:

- R = 3,000  $\Omega$
- C = 4 mfd.
- L = 15 henries
- f = 120 cy. in a full-wave rectifier

This will make  $C_x$  somewhat less than 1 mfd. This shows that it is possible to obtain greater filtering action using a total of 10 mfd., divided equally between  $C_2$  and  $C_3$ , than is obtainable with 12 mfd. divided equally among  $C_1$ ,  $C_2$ , and  $C_3$ , the chokes being the same in both cases.

From the above discussion one realizes that choke-input is superior in almost all respects to the condenser-input.


### AUDIO OSCILLATOR HINT

If a tube is used as audio oscillator, with transformer coupling, it is always well to use grid leak and condenser if the bias is positive, zero or slightly negative. The stability is improved. Also, by resistor and capacity selection, the frequency of generation can be controlled considerably.
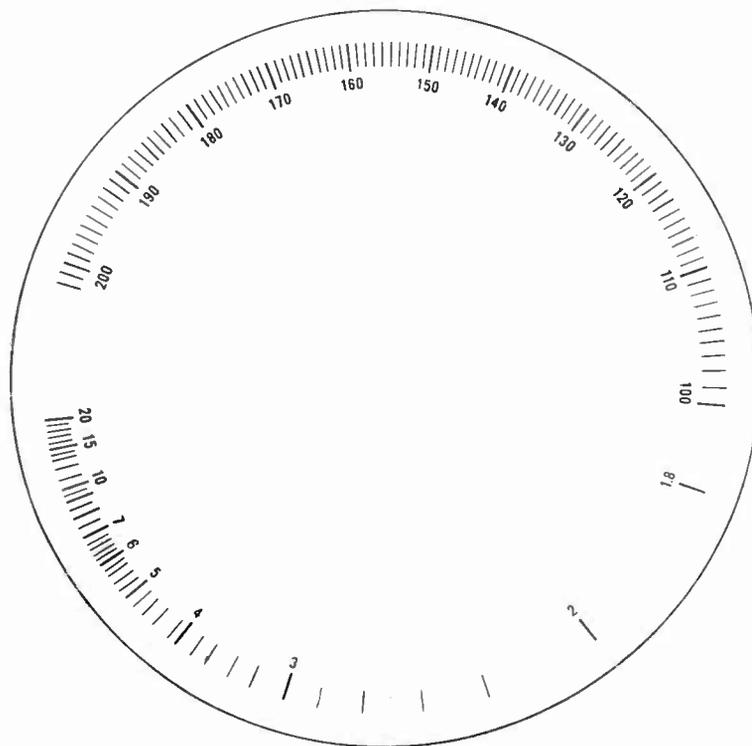
## Harmonic Counter Scale Visualized

If a signal generator covers low frequencies it can be used for measuring high frequencies harmonically in several ways, one of them being the introduction of the automatic electric harmonic counter system. By this method one starts at a given point, say, at 100 kc, and thus can measure frequencies that are multiples of 100 kc, or 0.1 mc.

It can be seen that the fundamental range of 100 to 200 kc can be attained on practically a straight frequency line basis. If the harmonic counter system is applied, the fact that the higher the frequency of the unknown, the nearer to the starting point will be the next response frequency, is utilized. Hence imagine a double pointer, one end indicating 100 kc, the other end in perfect alignment. Then as the pointer is moved the least bit one comes to a mark "20 mc". Note that from 10 to 20 mc the jumps are 1 mc, while at the other extreme, 1.8 mc up, differences of 0.2 mc are far apart. Hence this method, good for relatively low frequencies, does not yield sufficiently close results for high frequencies, as jumps of 1 mc are intolerable.



# An All-Wave Generator

## Switch-Type Instrument Uses Fundamentals 50 kc. to 20 mgc., Works on A.C. or D.C.

By Herman Bernard

**T**HE rule applying to short-wave and all-wave sets, that they should be as simple as possible, also applies to an all-wave signal generator. The model 337-A diagramed herewith has the minimum number of parts consistent with the performance required.

The first requirement is all-wave coverage on fundamentals. Here we have the lowest frequency as 50 kc. It would seem that so low a frequency is not absolutely required. Perhaps that is true at the moment. But to reduce noise in all-wave and short-wave sets, the expediency is being tried of having a stage of high intermediate-frequency amplification, using an extra local oscillator to lower the frequency, and then amplify more quietly at that low frequency. At present around 100 kc or so is the frequency used, but there is no telling whether the vogue will catch on, and the second i.f. be reduced still more. It is extremely unlikely that it will be made less than 50 kc, and so the lowest limit of the present model is a safeguard against obsolescence.

### Inductance Values

The first band, 50 to 160 kc, has about the same tuning ratio as the two next succeeding bands, where Band 2 covers 150 to 500 kc and Band 3 covers the broadcast spectrum, 500 to 1,700 kc. For coverage to the broadcast band, honeycomb coils are used, while for the broadcast and three short-wave bands the inductances are solenoids. All six coils are tapped, the tap position not being critical, although for the low-frequency coils less comparative inductance is required between tap and ground than for the high-frequency coils. The inductance values are:

Band 1 (50-150 kc), 25 millihenries, tapped at 10 millihenries.

Band 2 (150-500 kc), 2.8 millihenries, tapped at 1 millihenry.

Band 3 (500-1,600 kc), 250 microhenries, tapped at 30 microhenries.

Band 4 (1.5-5 mgc), 30 microhenries, tapped at 10 microhenries.

Band 5 (5-10 mgc), 2.5 microhenries, tapped at 1 microhenry.

Band 6 (10-20 mgc), 0.62 microhenry, tapped at 0.3 microhenry.

The honeycombs necessarily are commercial coils. The four solenoids may be wound on 1-inch outside diameter tubing, according to the following directions:

Band 3: 137 turns No. 32 enamel wire, tapped at 35 turns from ground end.

Band 4: 29 turns No. 32 enamel wire, tapped at 15 turns from ground end.

Band 5: 8¾ turns No. 20 enamel wire, tapped at 4 turns from ground end.

Band 6: 4 turns No. 18 enamel wire, tapped at 2 turns from ground end.

The directions are for close winding.

### Frequency Ranges

The tuning condenser used has a maximum capacity of 404 mmfd., and has no trimmer. The circuit capacity is 13 mmfd. The condenser minimum is 20 mmfd. So the effective capacity range is from 33 mmfd. to 417 mmfd., since the condenser's minimum disappears for increased capacity settings.


It will be noticed that approximately the full frequency range is utilized for the bands

up to and including the broadcast band, a ratio of more than 3 to 1. In fact, the actual frequency ratio obtained for the broadcast band was 3.6, though not all of it is included in the calibration. To provide adequate overlap the maximum capacity theoretically taken was 400 mmfd., and the inductances selected accordingly, although checked also at the high-frequency end of each band for frequency generation with a capacity of 33 mmfd.

There is, therefore, no missout, and a higher ratio of frequency is utilized for the first four bands, while the ratio for the two high-frequency bands is reduced to 2 to 1. This is done without any compensation save selection of the inductance on the basis of tuning beginning at 400 mmfd. total capacity, so only that part of the condenser between 400 and 100 mfd. is used. This is done because the spread-out is much better at the higher capacity settings, and the practice of omitting special compensating methods is consistent with simplicity. The 2-to-1 ratio utilizes 110 degrees out of 180, or 61 per cent. of the dial.
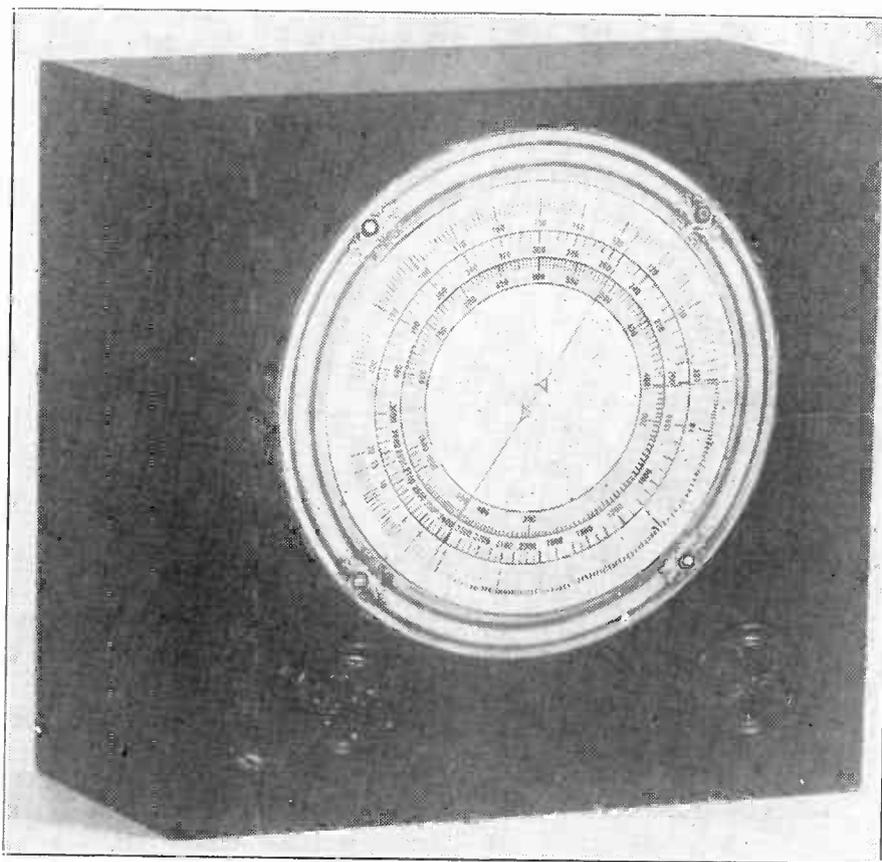
### Switch Considerations

The bands are changed by front-panel switching. A two-deck, six-position switch is required. Switches made by Central Radio Corporation, Yaxley, Soreng-Man-




The all-wave signal generator, Model 337-A, has a frequency-calibrated air-plane dial, direct-frequency reading from 50 kc to 20 mgc. One knob is for turning the dial, the other is for the combination on-off switch and attenuator.

gold and Oak Manufacturing Company are entirely satisfactory, and besides all have low contact capacity, of the order of 1 mmfd., and low contact resistance, a few thousandths of an ohm. The capacity must be low, otherwise a frequency-calibrated scale would not apply with 1% accuracy.

It would seem that there is no adjustment of the circuit, that one simply has to put in the parts, and take what frequencies result. This is not true. The common practice of using a compression type trimmer across the tuning condenser leads some to believe that therefore no compensation is provided. However, the 0.2 meg. (200,000-ohm) resistor in the plate leg (Grid No. 2) may be changed, also the condenser across it, shown as 0.0001 mfd., to coincide the circuit for any particular band, using a high frequency of that band, and then the circuit is adjusted for the purposes of the other bands, because only the inductance has to be accurate then to assure tracking a frequency-calibrated dial. It must be remembered that only a particular tuning condenser can be used even with the accurate inductances for the generated frequencies to coincide with the scale.

The circuit proved an interesting one to engineer. The triode section of the 6A7 tube is used as the generator. The circuit  
(Continued on next page)

# New All-Wave Signal Generator

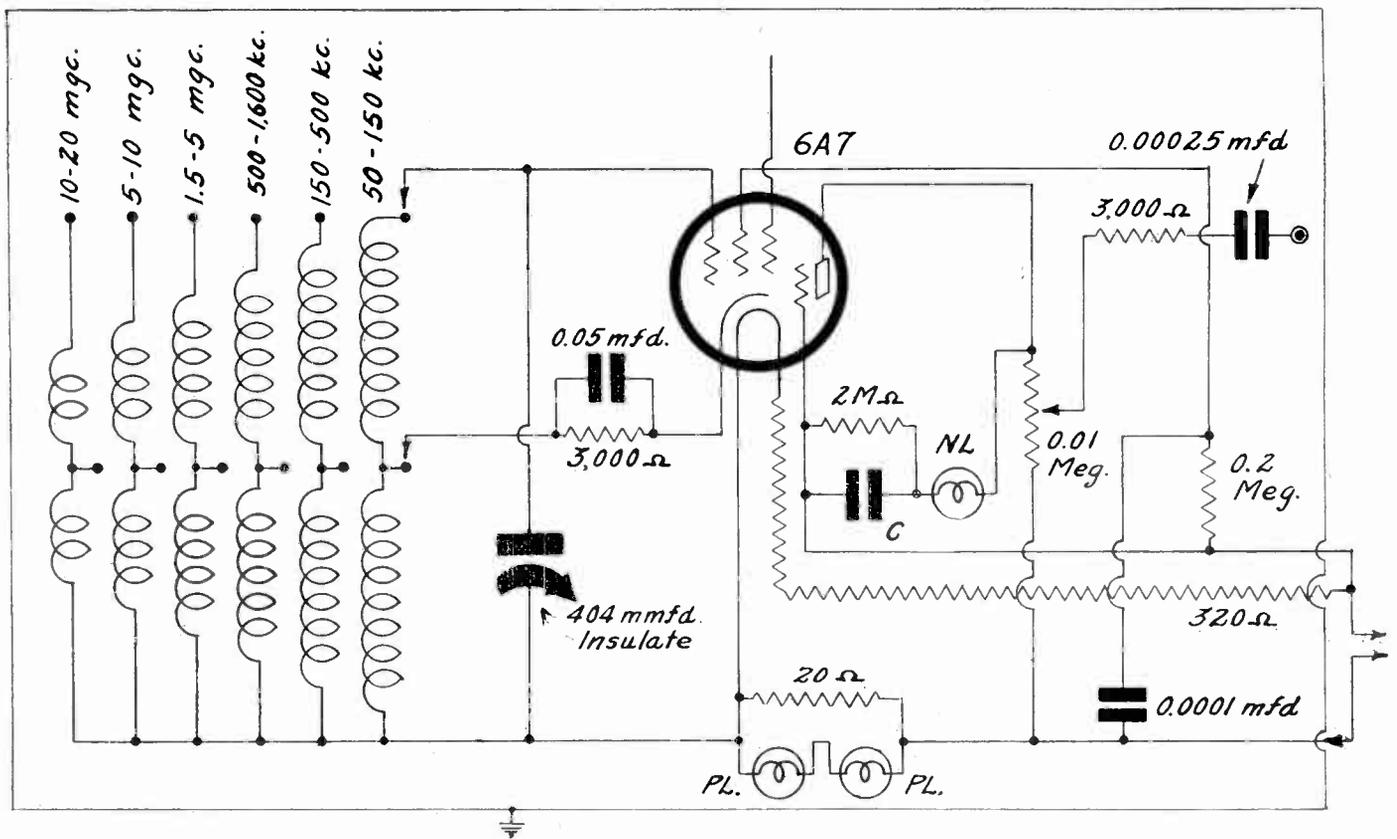

Precision results were obtained by circuiting an all-wave signal generator as diagramed. The grid shown as free may be grounded as an extra capacity adjustment (increase of capacity).

(Continued from preceding page)

is a Hartley, with cathode to coil tap, so that between cathode and ground is the feedback winding, while in the grid circuit is the entire winding, hence an auto-transformation effect is present.

To take off the oscillation the conventional plate circuit of the pentode of the 6A7 is used, but return of load resistor grounded. Thus does one have electron coupling. It is important to have such coupling, or other method for holding the frequency of generation immune from the effects of the circuit being measured.

## Right Coupling

Some users of generators must have noticed that as the attenuator is turned, the frequency of generation shifts. This is due to the close relationship of the impedances, one acting upon the other. That is, the primary of the antenna coupler of a set, for instance, becomes a part of the generator. That strictly is not wanted. Hence electron coupling. And yet one may have too much coupling of whatever kind, and something of the same vice of detuning by the measured circuit will prevail. It will be noticed that the conventional control grid of the pentode is left free. Were this tied to the oscillator control grid the capacity effect would be relatively large and the screening destroyed. As a capacity adjustment one has the option of grounding the element. Were Grid No. 4 tied to the conventional plate as part of the output circuit the relationship between generator and output would be too close, and there would be the detuning effect mentioned. Were it tied to the plate of the oscillator (Grid No. 2) or to the screen (Grids Nos. 3 and 5) there would be large grid current in a circuit not intended to carry it, tube life would be shortened, and power wasted. So the method outlined proved the best, and there was no detuning no matter what the position of the attenuator.

Considering the output, there is another

possible trouble. While the frequency may be safeguarded in the generator against change due to external causes affected by the attenuator, nevertheless the generator attenuator may act as a volume control on the receiver itself. This is not wanted, either. The vice lies in the fact that the receiver loses sensitivity when the generator control is set to a value intended for low output, while most accurate tests are made with receiver at maximum sensitivity and generator near minimum output. The 3,000-ohm series output resistor took care of that, for no matter if the attenuator has arm grounded, the input to the measured circuit is not shorted, as there are 3,000 ohms across the measured circuit, as a minimum. As a maximum there are 13,000 ohms across the measured circuit, when full generator output is utilized.

## High Stability

The circuit, moreover, is remarkably stable. It is not true that the type of tube helps a great deal. In fact, used as a grid-leak-condenser type generator, without limiting plate resistor, the plate current changed considerable over the tuning range of any band. Putting in the 0.2 meg. limiting resistor helped stability a lot. Even with self-bias operation by cathode-resistor voltage drop, the stability was poor. When the 0.2-meg. plate limiting resistor was included the stability was of a high order, better than one part in 10,000.

The test for frequency stability, in qualitative terms, may be made by putting a by-passed milliammeter in the plate circuit (Grid No. 2) and tuning over the entire span of any one band, or all bands, and noting whether the needle moves. When the circuit is completely stable there is practically no movement.

A listening method is to tune in a station, on a set, start the generator, tune the generator to the frequency of the station, then detune the generator a bit, so that a high-

pitched note is heard, easily distinguished from the program which for the present purpose constitutes interference, and then listen for fifteen minutes. The pitch should not change in any manner discernible by the ear. If the frequency of the station is 1,500 kc, that is, 1,500,000 cycles, and no change of pitch can be heard, then the change, if any, is 100 cycles or less, and the stability is better than one part in 15,000. Better stability than this is not required of generators, and there are few, if any, generators used as commercial instruments that have anything even approximating such stability.

## What Stability Means

By stability we mean that when the generator is set to generate a certain frequency it continues to generate only that frequency and does not drift to some other frequency.

Since a heater type tube is used, all tests and measurements should be made only after the emission has risen to its full value. Also, as an extra precaution, it is well to wait until the generator has been going for two minutes.

The generator works on a.c. or d.c., 90-125 volts. On a.c. the hum of the line is the modulation, heard only at resonance. On d.c. a neon tube is used as audio oscillator. The resistor that aids this oscillation is marked on the diagram as 2 meg., but may be almost any value equal to or larger than that, without limit, the condenser C being selected so that the tone of modulation is whatever one desires. When 2 meg. was used with C equal to 0.001 mid. the note was around 3,000 cycles. Circuit conditions other than the time constant of C and 2 meg. affect this frequency.

Instead of putting the heater limiting resistor inside the generator cabinet it is feasible to use an a-c cord that has heater element inside the covering. The cord then gets warm but not hot. The resistance value should be around 320 ohms, and as the dissipation is nearly 33 watts, a resistor of 50

LIST OF PARTS

Coils

Six tapped oscillation coils as follows: two honeycomb coils of total inductances of 25 and 2.8 millihenries; four solenoids of total inductances of 250, 30, 2.5 and 0.62 microhenries.

Condensers

One 0.000404 mfd. (404 mmfd.) tuning condenser without trimmer.  
 One 0.05 mfd. fix tubular fixed condenser.  
 One 0.001 mfd. fixed condenser (C).  
 One 0.0001 mfd. mica fixed condenser.  
 One 0.00025 mfd. mica fixed condenser.

Resistors

Two 3,000-ohm pigtail resistors.  
 One 0.2-meg. (200,000-ohm) pigtail resistor.  
 One 2.0-meg. (2,000,000-ohm) pigtail resistor.  
 One 0.01-meg. (10,000-ohm) potentiometer with a-c switch attached.  
 One 320-ohm 50-watt resistor (or built into a a-c cable unit).  
 One 20-ohm wire-wound resistor.

Other Requirements

One seven-hole medium-sized socket.  
 One frequency-calibrated airplane dial with two pilot brackets.  
 Two 6-volt pilot lamps.  
 One a-c cable and plug (or with 320-ohm, 50-watt resistor built in).  
 One two-deck, six-position switch.  
 Two knobs.  
 One switch-position index plate.  
 One attenuator index plate.  
 One shield cabinet and one chassis.  
 One 6A7 tube.  
 One output post.  
 One small neon lamp without limiting resistor built in.

watts rating is used, whether inside the cabinet or as part of the cord outfit.

Two Pilot Lamps

If the resistor is built into the cord covering, then there are three wires at the free end, one connected to pilot lamp, one to other heater side, and remaining one to intended B plus connections. It so happened the cord used has an unusual code: black was for positive, common with one end of the limiting resistor; red for negative; white for the side of the heater to which resistor is connected.

If any trouble arises due to oscillation failure on either or both of the high-frequency bands, then a mica-dielectric condenser of 0.001 mfd. or thereabouts may be connected across the heater at the tube.

The reason for the two pilot lamps is that brackets for them are built into the airplane dial, to illuminate both semi-circles.

Harmonics

Because the shield cabinet has to be insulated from conductive connection to the line, to avoid possibility of shorting the line if a grounded wire is accidentally connected to cabinet when the cabinet would be the hot side, the frame of the tuning condenser is insulated from the cabinet by putting a block under it. The condenser is attached to this block with three No. 8/32 machine screws 1/2 inch long, and the block is attached to the chassis by wood screws. Since the airplane dial is a conductive mechanism, and the cabinet would be connected to line through condenser shaft and dial frame, despite the previous precaution, an insulating extension shaft is used on the condenser. This device receives the 1/4-inch shaft of the condenser and extends in the opposite direction a 3/8-inch shaft for the dial hub. A notation for the insulation of the condenser



# Mixers for Battery Sets; R-F Stage Advisable

Two mixers are shown, both for battery operation. One has antenna connected to the primary of the coil which constitutes the transformer feeding the first detector control grid. This is not good practice, as there should be some tuning ahead of the modulator input. The other diagram does not show whether the antenna stage or an r-f stage feeds the IC6, but it is better practice to have an r-f stage do that feeding.

The grid leak and condenser, R1 and C3, in the one diagram, connected to control grid of the pentode, are for constituting the pentode the detector. The other diagram shows negative bias detector arising from "signal grid bias," meaning a battery of some 4.5 to 6 volts. The grid leak method is more sensitive, but the battery method will stand a greater input and therefore cause less likelihood of overloading.

Both diagrams represent the use of the IC6 pentagrid converter tube. This is an improvement over the 1AC, in fact, the emission is just about doubled. Hence there is better performance at the higher frequencies, should short waves be a goal. The 1A6 did not amount to much above 10 mcg. The IC6 was brought out particularly to give decent response for frequencies from, say, 10 to 25 mcg.

For the battery-bias diagram C4 may be 0.0001 mfd., while R1 may be 50,000 ohms. One reason for keeping the leak value relatively low, in battery sets, is to avoid excessive voltage drop in the leak, as from one point of view there is a drain on the tube by high leak values, caused by the fact it does take power to run the leak. While theoretically the larger the leak the greater the drop and the greater the sensitivity, where does the sensitivity come in if the tube stops oscillating?

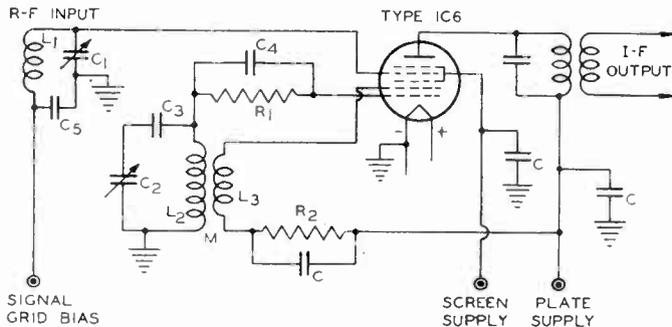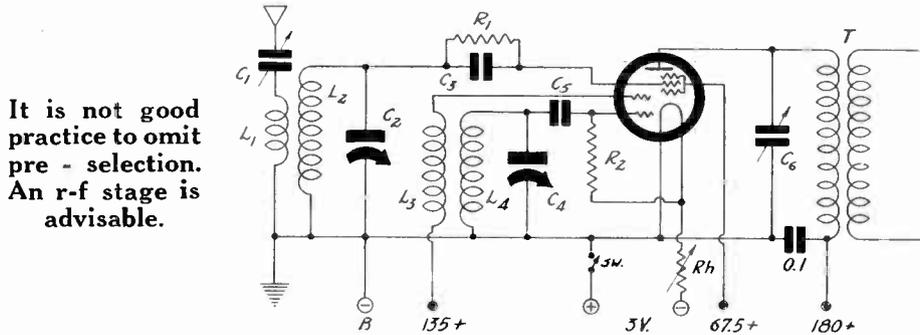

from the cabinet appears on the schematic diagram, but no notation of the insulation of the airplane dial from the condenser, as the dial is not a part of the wiring proper.

Since the generator covers all frequencies, 50 kc to 20 mcg, on fundamentals, there is no intention that harmonics be used. Therefore the harmonic generation has been suppressed to a considerable extent. It will be found, for instance, that the low-frequency band yields small, if any, response between 50 and 80 kc when tenth harmonics are used for 500 to 800 kc measurements. However, as stated, there is no intention of introducing such use. For the fundamental range between 50 and 80 kc, for instance, the response is adequate.

The harmonics, in general, are useful up to the fifth, and therefore the 10 to 20 mcg range may be used for measurements of 20 to 40, 30 to 60, 40 to 80, and 50 to 100 mcg. The harmonic-confusion-elimination methods described in the October 13th issue may be followed for that purpose, especially the harmonic-order method.

However, harmonics may be used as a check, principally as the lower frequencies are more readily handled on an accuracy basis. For instance, using a fundamental, register a particular frequency, say 5,000 kc. The accuracy will be better if when one

turns the switch for broadcast-band coverage and uses 1,000 kc generation, the fifth harmonic serving as a check. The registered frequency as attained on a fundamental may be checked by dividing by 2, 3, 4, or 5 and using next a low frequency equal to that quotient.

## Heat Method As Used For Measuring Sound

Sound is measured usually on the pressure basis. Now engineers of the Round Hill station of Massachusetts Institute of Technology have a way of measuring sound by the heat that it produces. Metal strips one-millionth of an inch thick are stacked up, and the electrolytic action causes current to heat the dissimilar electrodes, and the heat varies a resistance introduced into a very sensitive amplifier. The response of the system is said to be keen enough to yield a reading of one one-hundred-millionth of a volt.

At present measurements are confined to frequencies up to 10,000 cycles a second, which is near the upper limit of hearing. Soon it is expected to make heat measurements of radio frequencies up to 300 kc, and after that even of higher frequencies.

# Making the Oscillator Track

## In All-Wave Superheterodynes;

### Simplified Formulas Stated

**S**UPERHETERODYNE receivers of today must be tuned with a single adjustment. The accomplishment of this with a receiver covering a certain frequency range requires that one or more tuned r-f circuits must be adjusted over that range while, at the same time, the oscillator circuit must be caused to "track" at a constant frequency difference from the r-f circuits. It is universal practice to use a "gang" of variable capacitors operated by a common shaft to tune both the signal and the oscillator circuit.

The most popular design of the present-day superheterodyne circuit includes for each of the signal circuits, a fixed inductor, an initially adjustable minimum capacitor, and a variable tuning capacitor. To obtain approximately the necessary frequency difference, the oscillator will include values of inductance and minimum capacitance different from those of the signal circuits, a fixed capacitor in series with the inductor, and a variable capacitor the same as those used with the signal circuits.

#### Less of the Cut and Try

The present popularity of multi-range receivers has increased the need for a simple method of designing these circuit elements. A simple method of design requiring no charts or other tools, except possibly a slide rule, is presented. This method is based on a mathematical analysis flexible enough to cover any frequency range and any intermediate frequency. It is sufficiently accurate to provide the required circuit values and to reduce greatly the necessity for experimental cuts and tries.

The circuits most frequently used to obtain alignment of oscillator and radio-frequency circuits are illustrated by Figs. 1 and 2. Fig. 1 represents the radio-frequency circuit consisting of inductance  $L$  and capacitance  $C$ .  $C$  is variable over a sufficient range to cover the desired range of frequencies. The minimum capacitance of the circuit, including that of the tubes and other elements, is considered as included in  $C$ . For the solution of the problem to be considered, it is necessary to know either the value of  $L$  or the value of  $C$  at some particular frequency. If the value of  $C$  at a frequency  $F_0$  is expressed as  $C_0$ , the corresponding value of  $L$  is given by the expression:

$$L = 25330/C_0 F_0^2 \quad (1)$$

in which  $L$  is expressed in microhenries,  $C_0$  in micro-microfarads, and  $F_0$  in megacycles. These are generally the most convenient units to use in the solution of the problem under consideration.

#### Shunt Capacity

Fig. 2 represents the oscillator circuit. In this circuit, the capacitance  $C$  is to be varied simultaneously with  $C$  of Fig. 1 and is to have the same value as  $C$  of Fig. 1 at all adjustments. The rate of variation of  $C$  with condenser setting is not important as long as the r-f tuning condenser and oscillator tuning condenser change at the same rate.

The capacitance  $C_s$  represents the difference in minimum capacitance between the oscillator tuning capacitor and the radio-frequency tuning capacitor. Under certain conditions, the oscillator minimum may be the smaller (particularly, if  $C_s$  is large); in this case,  $C_s$  must be assigned a negative value. In most cases,  $C_s$  will be positive. The capacitor  $C_s$  is the series tracking capacitor, sometimes called the padding condenser. The

capacitance  $C_s$  is always present in a real circuit, since the distributed capacitance of the coil appears in this position. However, if  $C_s$  is small compared to  $C_0$ ,  $C_s$  may be considered as a part of  $C_0$ . This may be done in practically all cases in which the intermediate frequency is lower than the signal frequency.

When the required shunt capacitance  $C_s$  is large and the series capacitance  $C_0$  is small,  $C_s$  must be taken into account. Also, in some cases, the adjustable shunt capacitor may be placed in the position of  $C_s$ . When  $C_s$  must be considered, either  $C_s$  or  $C_0$  must be known approximately. This is not a serious restriction, since usually only one of these capacitances is adjustable. The other represents distributed capacitance of a coil, capacitance of wiring, input capacitance of a tube, or other similar factors and combinations; all of these may be estimated with sufficient accuracy. A small error in this estimate is compensated in practice by adjustment of the other shunt capacitor.

#### Three Tie-down Points

The desired relation between the resonant frequencies of the circuits of Fig. 1 and Fig. 2 is given by the relation:

$$f_1 = f + f_0 \quad (2)$$

where  $f_1$  is the resonant frequency of the oscillator circuit,

$f$  is the resonant frequency of the radio-frequency circuit, and

$f_0$  is the intermediate frequency.

When the circuit of Fig. 2 is used this relation cannot be satisfied at all frequencies. Instead, there are, in general, three frequencies at which equation (2) is exactly satisfied. The departure from this equation is in the regions between and just beyond these frequencies. The three values of the signal frequency (the "tracking frequencies") are designated as  $F_1$ ,  $F_2$ , and  $F_3$ . These frequencies should be chosen in advance for each band under consideration.  $F_2$  should be chosen near the center of this band;  $F_1$  and  $F_3$ , for best results, should be placed near but not at the ends of the band.

On the following page is a summary of the formulas for calculating superheterodyne-oscillator constants. The Appendix contains the mathematical derivation of these formulas. For practical use in design problems, the summary sheet gives all necessary information to determine  $L_1$ ,  $C_2$ , and  $C_3$  or  $C_4$  for the circuit shown in Fig. 2. It is assumed that the following design information is available.

- I. The intermediate frequency,  $f_0$ .
- II. The tracking frequencies,  $F_1$ ,  $F_2$ ,  $F_3$ .
- III. The inductance,  $L$ , or the capacitance,  $C_0$ , at frequency,  $F_0$ .
- IV. The capacitance,  $C_s$ , or the capacitance,  $C_0$ .

Equations (24), (25), (26), and (27) may be used to check the results obtained. Also, these equations may be used to determine the oscillator frequency when circuit constants are known.

#### Examples Cited

Two examples illustrating the use of these formulas follow:

##### Example I

Design a circuit covering the receiving frequency range from 150 kc to 420 kc and using an intermediate frequency of 465 kc. Given: For frequency of 150 kc,  $C = 400$  mmfd.

Arbitrarily chosen: Tracking frequencies of 175 kc, 260 kc, and 380 kc.

Each of the cases will be worked out with given data as follows:

Case 1: Where  $C_s = 0$ .

Case 2: Assume tube is connected across coil to give maximum voltage at grid of tube.  $C_s$  will include tube input capacitance and distributed capacity of coil. Assume  $C_s = 12$  mmfd.

Case 3: Assume that trimmer of capacitor has been adjusted to match minimum capacitance of r-f section. Consequently,  $C_s = 0$ . The adjustment of minimum capacity is made by varying  $C$ .

Case 4: Same as Case 3, except that oscillator minimum trimmer has been removed from tuning capacitor. Minimum capacity of oscillator section is assumed to be 20 mmfd. less than the minimum of the r-f circuit. Consequently,  $C_s = -20$  mmfd.

Frequencies are expressed in megacycles in order to give small numerical quantities.

Given:  $f_0 = 0.465$   $2f_0 = 0.930$   $f_0^2 = 0.2162$   
 $F_1 = 0.175$   $F_2 = 0.260$   $F_3 = 0.380$   
 $F_0 = 0.150$   $C_0 = 400$   $C_0 F_0^2 = 9.00$

Then:  $a = 0.175 + 0.260 + 0.380 = 0.815$   
 $b^2 = (0.175 \times 0.260) + (0.175 \times 0.380)$   
 $+ (0.260 \times 0.380)$

$= 0.0455 + 0.0665 + 0.0988 = 0.2108$

$c^3 = 0.175 \times 0.260 \times 0.380 = 0.01728$

$d = 0.815 + 0.930 = 1.745$

$l^2 = (0.2108 \times 1.745 - 0.0173)/0.930$

$= (0.3680 - 0.0173)/0.930$

$= 0.3507/0.930 = 0.377$

$m^2 = 0.815 \times 1.745 + 0.216 + 0.377 - 0.211$

$= 1.423 + 0.005 + 0.377 = 1.805$

$n^2 = (0.01728 \times 1.745 + 0.2162 \times 0.377)/1.805$

$= (0.0302 + 0.0815)/1.805 = 0.1117/1.805$

$= 0.0618$

#### Case 1

$C_2 = 9.00(1/0.0618 - 1/0.377)$   
 $= 9.00(16.18 - 2.65) = 9.00 \times 13.53$

$= 121.8$  mmfd.

$C_3 = 9.00/0.377 = 23.9$  mmfd.

$L_1 = L(0.377/1.805)(145.7/121.8) = 0.2496L$

#### Case 2

$C_s = 12$  mmfd.

$A = 9.0(1/0.0618 - 1/0.377) = 121.8$

$C_2 = 121.8(\frac{1}{2} + \text{square root of quantity } \frac{1}{4}$

$+ 0.0985)$

$= 121.8(0.500 + \text{square root of } 0.3485)$

$= 121.8(0.500 + 0.590)$

$= 132.8$  mmfd.

$C_3 = 9.00/0.377 - 12 \times 132.8/144.8 = 23.9$

$- 11.0$

$= 12.9$  mmfd.

$L_1 = L(0.377/1.805)(145.7/144.8)$

$= 0.210L$

#### Case 3

$C_s = 0$

$C_2 = 9.0/0.0618$

$= 145.7$  mmfd.

$C_4 = 9.0/(0.377 - 0.062) = 9.0/0.315$

$= 28.5$  mmfd.

$L_1 = L(0.377/1.805)(145.7/174.2)$

$= 0.2088L$

#### Case 4

$C_s = -20$

$B = 9/0.377 + 20 = 23.88 + 20$

$= 43.88$

$C_2 = 9/0.0618 + 20 = 145.7 + 20$

$= 165.7$  mmfd.

$C_4 = (165.7 + 43.88)/121.8$

$= 59.7$  mmfd.

$L_1 = L(0.377/1.805)(1 + 5.7/225.4)$

$= 0.1348L$

The example chosen was selected to show

wide divergency between values of  $C_2$  and  $L_1/L$  for the various cases. When  $C_2$  is larger, the differences between cases are much less pronounced.

The check formulas give for Case 4:  
 $l^2 = 9/(-20 + 43.8) = 0.377$   
 $m^2 = 9/0.1348(52.7 - 22.7) + 9/0.1348 \times 37.0 = 1.803$   
 $n^2 = 9/145.7 = 0.0618$   
 $f_1^2 = 1.805 (f^2 + 0.0618)/(f^2 + 0.377)$

**Calculations of Values**

Check calculations tabulated for end frequencies, tracking frequencies, and two others will be found in the tabulation at bottom of columns 2 and 3. In this tabulation the value  $f_1 - f$  shows that tracking is very good except at the extreme high-frequency end.

**Example II**

Design a circuit covering the receiving range of 10 to 23 megacycles and using an intermediate frequency of 465 kc.

Since the signal frequency is considerably greater than the intermediate frequency, the equations of Case 1 ( $C_4 = 0$ ) will be used.

Given: For frequency of 10 megacycles,  $C = 400$  mmfd.

Arbitrarily chosen: Tracking frequencies of 12, 16 and 20 megacycles.

Given:  
 $f_0 = 465$      $2f_0 = 0.93$      $f_0^2 = 0.216$   
 $F_1 = 0.12$      $F_2 = 18$      $F_3 = 20$   
 $F_0 = 10$      $C_0 = 400$      $C_0 F_0^2 = 40000$

Then:  
 $a = 48$   
 $b^2 = 192 + 240 + 320 = 752$   
 $c^3 = 3840$   
 $d = 48.93$   
 $l^2 = 752 \times 48.93 - 3840 = 32960$   
 $m^2 = 234.8 + 0.2 + 32960 - 752 = 35560$   
 $n^2 = (184000 + 712)/35560 = 5.19$   
 $C_2 = 40000 (0.1927 - 0.00003) = 7708$  mmfd.  
 $C_3 = 40000/32960 = 1.21$  mmfd.  
 $L_1 = L (32960/35560) (7709/7708) = 0.927L$

In this case,  $C_2$  is so large compared with the tuning capacitor that  $C_2$  could be omitted; a small correction of the inductance value would then be required. The resultant capacity of 400 mmfd. and 7700 mmfd. in series is 380 mmfd.; if the series capacity is omitted, inductance  $L_1$  must be reduced to correspond to the increase in  $C$ .  $L_1/L$  is then equal to  $0.927 \times 380/400 = 0.88$ . An increase in the value of minimum capacity will complete the correction.

With the series capacity  $C_2$  omitted, exact tracking occurs at only two points; however, tracking will be so close to the conditions of Example II that the difference is of little consequence.  
 (Copyright 1934, by RCA Radiotron Co., Inc.)

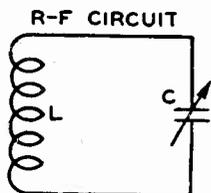


FIG. 1

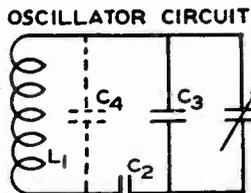


FIG. 2

Frequencies expressed in megacycles  
 Inductances " " microhenries  
 Capacitances " " micromicrofarads

**Basic Considerations and Relations**

$f_0$  = Intermediate frequency  
 $F_1, F_2, F_3$  = Frequencies at which exact tracking is to be obtained.

$a = F_1 + F_2 + F_3$  (3)

$b^2 = F_1 F_2 + F_1 F_3 + F_2 F_3$  (4)

$c^3 = F_1 F_2 F_3$  (5)

$d = a + 2f_0$  (6)

$l^2 = (b^2 d - c^3)/2f_0$  (7)

$m^2 = l^2 + f_0^2 + ad - b^2$  (8)

$n^2 = (c^3 d + f_0^2 l^2)/m^2$  (9)

$C_0$  = Tuning capacitance at frequency  $F_0$

$L = 25330/C_0 F_0^2$ , or if  $L$  is known, then  $C_0 F_0^2 = 25330/L$  (1)

$A = C_0 F_0^2 (1/n^2 - 1/l^2)$  Required only for Case 3 (16)

$B = (C_0 F_0^2 / l^2) - C_3$  Required only for Case 4 (20)

**Case 1: When  $C_4 = 0$ , or  $C_4 \ll C_2$  (the usual case).**

$C_2 = C_0 F_0^2 (1/n^2 - 1/l^2)$  (10)

$C_3 = C_0 F_0^2 / l^2$  (11)

$L_1 = L (l^2 / m^2) (C_2 + C_3) / C_2$  (12)

**Case 2: When  $C_3 = 0$ .**

$C_2 = C_0 F_0^2 / n^2$  (13)

$C_4 = C_0 F_0^2 / (l^2 - n^2)$  (14)

$L_1 = L (l^2 / m^2) C_2 / (C_2 + C_4)$  (15)

**Case 3: When  $C_4$  is known.**

$C_2 = A (1/2 + \sqrt{1/4 + C_4/A})$  (17)

$C_3 = (C_0 F_0^2 / l^2) - C_2 C_4 / (C_2 + C_4)$  (18)

$L_1 = L (l^2 / m^2) (C_2 + C_3) / (C_2 + C_4)$  (19)

**Case 4: When  $C_3$  is known.**

$C_2 = (C_0 F_0^2 / n^2) - C_3$  (21)

$C_4 = C_2 B / (C_2 - B)$  (22)

$L_1 = L (l^2 / m^2) (C_2 + C_3) / (C_2 + C_4)$  (23)

\* \* \* \* \*

**Check Formulas**

Equation for oscillator frequency:

$f_1 = m \sqrt{(f^2 + n^2)/(f^2 + l^2)}$  (24)

Equations for  $l^2, m^2$ , and  $n^2$ , in terms of oscillator constants:

$l^2 = C_0 F_0^2 / (C_3 + \frac{C_2 C_4}{C_2 + C_4})$  (25)

$m^2 = C_0 F_0^2 / (L_1 / L) (C_4 + \frac{C_2 C_3}{C_2 + C_3})$  (26)

$n^2 = C_0 F_0^2 / (C_2 + C_3)$  (27)


|                      |        |        |        |        |        |        |        |
|----------------------|--------|--------|--------|--------|--------|--------|--------|
| $f$ .....            | 0.150  | 0.175  | 0.220  | 0.260  | 0.320  | 0.380  | 0.420  |
| $f^2$ .....          | 0.0225 | 0.0306 | 0.0484 | 0.0576 | 0.1024 | 0.1444 | 0.1764 |
| $f^2 + 0.0618$ ..... | 0.0843 | 0.0924 | 0.1102 | 0.1294 | 0.1642 | 0.2062 | 0.2382 |
| $f^2 + 0.377$ .....  | 0.400  | 0.408  | 0.425  | 0.445  | 0.479  | 0.521  | 0.553  |
| $f_1^2$ .....        | 0.380  | 0.409  | 0.468  | 0.526  | 0.619  | 0.714  | 0.778  |
| $f_1$ .....          | 0.616  | 0.640  | 0.684  | 0.725  | 0.787  | 0.845  | 0.882  |
| $f_1 - f$ .....      | 0.466  | 0.465  | 0.464  | 0.465  | 0.467  | 0.465  | 0.462  |

# A Ham Speech Amplifier

## 56 First AF, 56 Push-Pull Driver and 46 Parallel-Push-Pull Output

By Russell De Jonge

W8DIB, Zeeland, Mich.

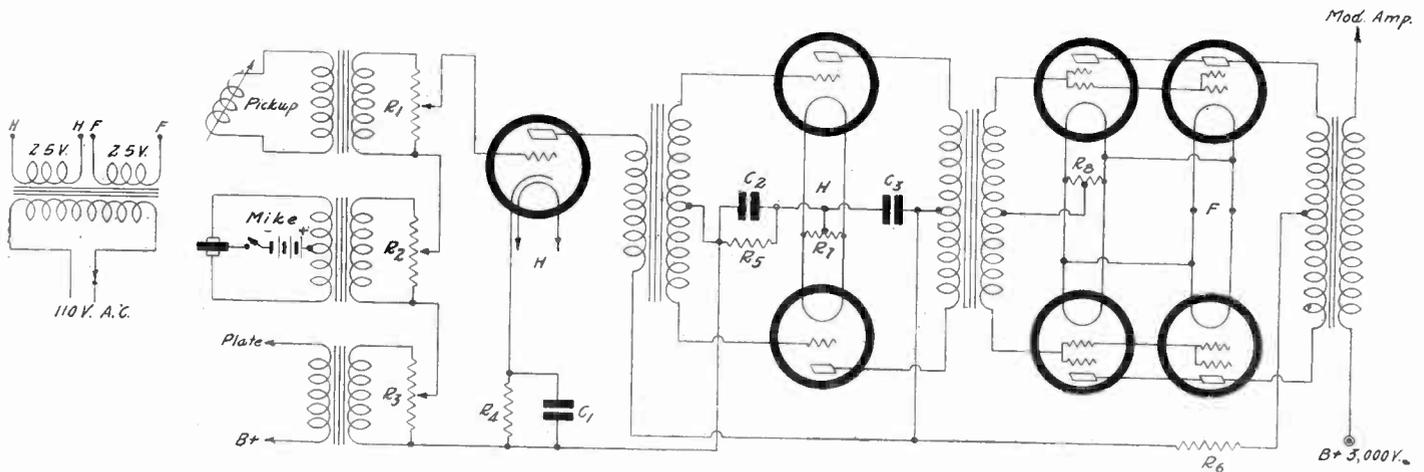

Speech amplifier for a high-class amateur transmitting installation.

THE radio-frequency generator and associated amplifier, as well as power supply for an entire amateur transmitter, were described last week, issue of October 20th. This article describes the speech amplifier and modulator unit which converts the continuous-wave (code) transmitter into a modern amateur radiophone station.

The first principal part of this unit is the microphone. It changes audible voice frequencies or music into minute electrical pulsations. Another converter of sound vibrations into electrical pulsations is the magnetic pickup, the needle of which is vibrated at sound frequencies by the irregularities in the groove of a record, the coil changing the sound into electrical pulsations. The third input is the land line from remote places which might be a telephone line but in this case is the output of a radio receiver. The microphone is the only input requiring a battery, which in this circuit is a 6-volt storage battery. When the microphone is not being used the battery should be disconnected by opening the switch.

### Class A 2A3 Output

Each of these B "interpreters" has its individual volume control connected across the secondary of the step-up audio transformers. The primaries are connected as is shown in the accompanying diagram.

The output of the faders are connected directly to the grid of a type 56 tube whose automatic bias is 13.5 volts. The output of this tube is transformer coupled to a pair of 2A3 triode amplifiers. The 2A3 tubes are run Class A. The coupling transformer is a step-up transformer whose primary is matched to the plate circuit of the 56, the step-up ratio is 5 to 1.

The grid bias for these tubes is obtained by the automatic bias method. This stage is the driver stage, being so called because it "drives" the final or modulator stage.

### 46 Parallel Push-Pull

The driver is transformer-coupled to the modulator stage by a transformer whose turns ratio is 1 to 1. Two pairs of 46

tubes connected in parallel push-pull combination are used as modulators. The purpose of the modulator is to superimpose an audio frequency upon the continuous-wave signal. The audio frequency may be either voice or music, according to the selection of the volume controls preceding the first speech amplifier.

A heavy-duty modulation transformer is connected as shown in the diagram. In order that the high voltage will not cause puncture or short circuit the transformer should be insulated for at least 3,000 volts. The secondary winding is inserted into the plate lead of the type 60. This lead also supplies the screen voltage of the 60. This lead must be cut and permanently connected to the secondary winding. The voltage developed across the secondary winding should be equal to that developed in the final radio-frequency stage. The percentage of modulation is one hundred per cent. when these voltages are equal.

Since both the 2A3 and 46 tubes are the filament type tubes, separate filament windings are necessary so that the correct bias can be supplied to the tubes. Both of these secondary windings supply 2.5 volts. Secondary No. 1 is connected to the 56 and 2A3 tubes and secondary No. 2 is connected to the four type 46 tubes.

### High-Class Equipment

The negative as well as the positive of 400 volts is common to both of the units, the radio-frequency amplifier and the modulator and speech amplifier. Two hundred and fifty volts positive is supplied to the type 56 tube and 2A3 tubes from the 400-volt terminal through a series resistor R6.

With a complete outfit, such as has been described, the radio amateur today can rest assured that he has the equipment equalling any other rig as to stability and quality. It is not, however, the most powerful on the air, because its output is limited to 200 watts. The Government will license it for 1,000 watts. If, however, one is desirous of increasing the output to 1,000 watts he may do it with the addition of a 1-kilowatt tube operated in a linear manner. With this

addition the transmitter will be as powerful and as reliable as any amateur installation.

With the rig as I have described the amateur will be able to contact stations otherwise out of his reach, provided that he has a reliable receiver.

### License Necessary

Before this unit is operated an amateur must obtain from the United States Government a license to operate the equipment. The Government has set aside several bands of frequencies in which the amateurs are allowed to operate. The laws concerning the operation of such stations can be had by requesting them from the Federal Communications Commission, Washington, D. C.

An amateur, according to the regulations, must have equipment to check his frequency. He must check the frequency before every transmission. To do this he must have modern equipment. The most important is a frequency meter.

The values of the resistors and condensers in the diagram are tabulated below:

|    |       |             |              |
|----|-------|-------------|--------------|
| R1 | ..... | 25,000 ohms | low wattage  |
| R2 | ..... | 25,000 ohms | low wattage  |
| R3 | ..... | 25,000 ohms | low wattage  |
| R4 | ..... | 2,700 ohms  | low wattage  |
| R5 | ..... | 1,500 ohms  | high wattage |
| R6 | ..... | 2,200 ohms  | high wattage |
| R7 | ..... | 20 ohms     | high wattage |
| R8 | ..... | 20 ohms     | high wattage |
| C1 | ..... | 0.1 Mfd.    |              |
| C2 | ..... | 0.1 Mfd.    |              |
| C3 | ..... | 1.0 Mfd.    |              |

### FAREWELL TO STATIC!

Static is as unsteady and indeed as unreliable as its name does not suggest. Anything static is something that stands still, but the static we know in radio is restless. Very pronounced at long waves, it becomes negligible in the broadcast band, then becomes severe to about 17 meters, after which it disappears. If it would disappear at zero frequency or infinite wavelength and never come back nobody would complain.

**A THOUGHT FOR THE WEEK**

**YOU KNOW JULE DELMAR**, of course; or, if you don't, you acknowledge that you don't know show business. Jule has just become associated with the WOR Artists Bureau, located in that station's studio at 1440 Broadway, New York City.

A history of the American stage and the world of native entertainment would not be complete without something concerning the experience and ability of Jule Delmar. Starting a good many years ago in the smaller towns and on less important circuits of the country, he at last reached that point of importance and usefulness where he was needed by the Keith-Albee Circuit and later by the R.K.O. He was practically the czar—though a most reasonable and human one—of the Southern part of the big R.K.O. Circuit, and the managers of those houses below the Mason & Dixon Line and the players who appeared in them will tell you that Jule Delmar knew his business from A to Z and that they trusted him to do the right thing at the right time and in the right way.

Broadway and Radioland are glad that Jule Delmar's light is shining again—although permit us to remark right here that his light really never has gone out.

Radio certainly is bringing the big men of the theatre into its fold—and one of the best of all these is our old friend and townsman, Jule Delmar.—R.B.H.

**Literature Wanted**

Readers desiring radio literature from manufacturers and jobbers should send a request for publication of their name and address. Address Literature Editor, RADIO WORLD, 145 West 45th Street, New York, N. Y.

- Gregory H. Diez, 950 N. Clinton Ave., Rochester, N. Y.
- Edward Arnold, 42 West Fordham Road, The Bronx, New York City.
- Harry Latta, Jr., 116 St. Mary's St., Raleigh, N. C.
- R. C. Ashcraft, 226 North Signal St., Ojai, Calif.
- Alexander Pacelt, 1552 Buena Vista West, Detroit, Mich.
- Chas. J. Adams, 3435 Finlaw Ave., Pensauken, N. J.
- Ole Anderson, 819 Weller St., Seattle, Wash.
- C. H. Annis, 1702 So. 52nd St., Tacoma, Wash.
- Charles W. Anderson, Grantsville, Utah.
- Julius Jacobson, Vashon, Wash.
- Chas. E. Barns, 11741 Mansfield, Detroit, Mich.
- H. H. Bouson, 623 Insurance Bldg., Seattle, Wash.
- Oscar Bradford, 1814 N. Fayette St., Saginaw, Mich.
- Lawrence Solie, Nome, No. Dak.
- G. Arthur Black, Clinton, S. C.
- E. F. Boran, 820 Doyle Ave., West Homestead, Penna.
- Earl G. Bartels, Sidlo, Simons, Day & Co., First National Bank Bldg., Denver, Colo.
- Arthur D. Calvert, Chicora, Penna.
- R. E. Cotton, 12905 Imperial Ave., Cleveland, Ohio.
- Edward G. Craft, 2055 "S" St., Lincoln, Nebr.
- Geo. G. Caldwell, 4000 - 5th St., N.W., Washington, D. C.
- Carl Cadwallader, Radio Service Dept., Thos. J. Wadson & Son, Hamilton, Bermuda.
- W. T. Dice, Fowler Radio Shop, 816 Merced St., Fowler, Calif.
- Warren J. Daugherty, Kincaid, Kans.
- D. Dootson, P. O. Box 280, Port Alberni, B. C., Canada.
- H. F. Dickten, 2550 N. Webster St., River-Grove, Ill.
- Richard B. O'Connor, 30 Ninety-first Street, Brooklyn, N. Y.
- Raymond Brennan, 6136 Lebanon Ave., Overbrook, Philadelphia, Pa.
- Bertram Reinitz, 18 Twenty-first Street, Brooklyn, N. Y.

**CORPORATE REPORTS**

**ZENITH RADIO CORPORATION**—Net loss for the quarter ended July 31, 1934, \$36,573, after depreciation expenses, taxes, and other charges; compared with a net profit of \$8,336 last year, before federal taxes. In August Hugh Robertson, vice-president and treasurer, reported to stockholders a profit.

# Large PA System on Rack and Panel

**THEATRE INSTALLATION**

For large halls, auditoriums, theatres and the like, the public address system may assume considerable physical proportions. The service to be rendered is a large one, and therefore more apparatus is needed, for furnishing greater power, and the rack-and-panel type of construction becomes attractive.

The assembly illustrated herewith is suitable for any type of microphone, except a carbon type, as there is no energizing force for driving such a transducer. However, even a carbon microphone could be used, as all that would be needed would be a small battery to potentialize the buttons.

Some of the microphone types that have the best acoustical qualities are not the most sensitive devices, and therefore a pre-amplifier is used. This consists of stages of amplification preceding the main amplifier. Thus the voltage amplification is divided into two parts. On the top shelf only voltage amplification is used. On the middle shelf, where the main amplifier is housed, all the amplification is of the voltage type up to the output stage, which is a power amplifier. Double push-pull 56 Cascaded stages are used for loading up the push-pull 2A3 output tubes.

To keep hum well below the 5 per cent. allowable limit, special pains are taken as to filtration. Hence the B supply for the pre-amplifier is situated below, and this same nether component takes care of the excitation of the fields of the two dynamic speakers used. The speakers are baffled in a separate compartment and are not shown.

On the front panel are three adjustment controls and a switch and an earphone jack. Thus the operation may be monitored from the rack; that is, the volume adjusted on the basis of the operator listening to what the amplifier is reproducing.

Such a piece of apparatus as this is to be used in connection with a microphone, as when somebody is to speak and it is the serious intention of the management that the speaker be heard all over the house. Some who address the public do not realize this necessity. The public-address system makes up for the deficiency.

Also, music is to be played in the hall or theatre. By placing speakers in suitable locations, such as sound engineers can spot with trained ears, the distribution of sound is made more uniform and the reproduction louder and more realistic.

The installation illustrated herewith is the design work and product of Harvey Sampson, sound specialist and operator of Harvey's Radio Shop, New York City. His amplifiers are used by the most noted singers and orchestras.



Rear view of a rack-and-panel public-address system developed by Harvey Sampson, of Harvey's Radio Shop, New York City. The top shelf holds the pre-amplifier, for building up the microphone level, and thus permitting use of a crystal microphone. The mid-section houses the power amplifier proper. Below is the power supply for the pre-amplifier, and a field exciter. This type of installation is used in theatres.

## Pro or Con—Which Shall It Be?

**SHALL WE HAVE GOVERNMENT RADIO CENSORSHIP?** You can't make up your mind on the subject by reading the speeches made during the annual assembly of the National Advisory Council on Radio in Education held recently in Chicago. A number of men whose convictions are interesting even if not conclusive and still more prominent educators and microphone declaimers disagree quite thoroughly over the pros and cons of the case. Many of them missed a most important angle of the subject—for no matter why or when or by what administration radio censorship is established there al-

ways remains the positive danger that a big percentage of our population will claim that a synonym for censorship is propaganda.

Again, and for the seventh time, let us proclaim to the whole world that radio can save the expense, resentment and unpleasant features of censorship only by keeping its skirts clean and sending out nothing over the air-waves that calls for censorship. Who shall decide? Why, the same duo that decides most things at home and in national life—good, old Dr. Decency and his partner, Dr. Commonsense.

They make a strong team.





| TYPE | NAME                                | BASE         | SOCKET CONNECTIONS | DIMENSIONS MAXIMUM OVERALL LENGTH X DIAMETER | CATHODE TYPE # | RATING             |         |            | USE Values to right give operating conditions and characteristics for indicated typical use | PLATE SUPPLY VOLTS               | GRID VOLTS <sup>1</sup> | SCREEN VOLTS | SCREEN MILLI-AMP. | PLATE MILLI-AMP. | A-C PLATE RESISTANCE OHMS | MUTUAL CONDUCTANCE MICRONS | VOLTAGE AMPLIFICATION FACTOR  | LOAD FOR STATED POWER OUTPUT OHMS | POWER OUTPUT WATTS   | TYPE |     |     |     |
|------|-------------------------------------|--------------|--------------------|--|----------------|--------------------|---------|------------|---|----------------------------------|-------------------------|--------------|-------------------|------------------|---------------------------|----------------------------|---|-----------------------------------|--|------|-----|-----|-----|
|      |                                     |              |                    |  |                | FILAMENT OR HEATER | PLATE   | SCREEN     |   |                                  |                         |              |                   |                  |                           |                            |   |                                   |  |      |     |     |     |
|      |                                     |              |                    |  |                | VOLTS              | AMPERES | MAX. VOLTS |   |                                  |                         |              |                   |                  |                           |                            |   |                                   |  |      |     |     |     |
| 1A6  | PENTAGRID CONVERTER                 | SMALL 8-PIN  | FIG. 20            | 4 1/2" x 1 1/8"                              | D-C FILAMENT   | 2.0                | 0.06    | 180        | 67.5  | CONVERTER                        | 180                     | -3.0 min.    | 67.5              | 2.4              | 1.3                       | 50000                      | Anode Grid (#3) 135 max. volts, 2.3 ma. Oscillator Grid (#1) Resistor, 50000 ohms. Conversion conductance, 300 micromhos. | 1A6                               |  |      |     |     |     |
| 1C6  | PENTAGRID CONVERTER                 | SMALL 8-PIN  | FIG. 20            | 4 1/2" x 1 1/8"                              | D-C FILAMENT   | 2.0                | 0.12    | 180        | 67.5  | CONVERTER                        | 180                     | -3.0 min.    | 67.5              | 2.0              | 1.5                       | 75000                      | Anode Grid (#3) 135 max. volts, 3.3 ma. Oscillator Grid (#1) Resistor, 50000 ohms. Conversion conductance, 325 micromhos. | 1C6                               |  |      |     |     |     |
| 2A3  | POWER AMPLIFIER TRIODE              | MEDIUM 4-PIN | FIG. 1             | 5 1/2" x 2 1/8"                              | FILAMENT       | 2.5                | 2.5     | 300        | ---   | CLASS A AMPLIFIER                | 250                     | -45          | ---               | 60.0             | 800                       | 5250                       | 4.2   | 2500                              | 3.5  | 2A3  |     |     |     |
| 2A5  | POWER AMPLIFIER PENTODE             | MEDIUM 6-PIN | FIG. 15A           | 4 1/2" x 1 1/8"                              | HEATER         | 2.5                | 1.75    | 250        | 250   | CLASS A AMPLIFIER                | 250                     | -16.5        | 250               | 6.5              | 34.0                      | 100000                     | Power Output is for 2 tubes at stated load, plate-to-plate  | 5000                              | 10.0   | 7000 | 3.0 | 2A5 |     |
| 2A6  | DUPLEX-DIODE HIGH-IMP. TRIODE       | SMALL 8-PIN  | FIG. 13            | 4 1/2" x 1 1/8"                              | HEATER         | 2.5                | 0.8     | 250        | ---   | TRIODE UNIT AS CLASS A AMPLIFIER | 250                     | -1.35        | ---               | 0.4              | ---                       | ---                        | Gain per stage = 50-60  | ---                               | ---  | ---  | --- | 2A6 |     |
| 2A7  | PENTAGRID CONVERTER                 | SMALL 7-PIN  | FIG. 20            | 4 1/2" x 1 1/8"                              | HEATER         | 2.5                | 0.8     | 250        | 100   | CONVERTER                        | 250                     | -3.0 min.    | 100               | 2.2              | 3.5                       | 360000                     | Anode Grid (#3) 200 max. volts, 4.0 ma. Oscillator Grid (#1) Resistor, 50000 ohms. Conversion conductance, 520 micromhos. | 2A7                               |  |      |     |     |     |
| 2B7  | DUPLEX-DIODE PENTODE                | SMALL 7-PIN  | FIG. 21            | 4 1/2" x 1 1/8"                              | HEATER         | 2.5                | 0.8     | 250        | 125   | PENTODE UNIT AS R.F. AMPLIFIER   | 100                     | -3.0         | 100               | 1.7              | 5.8                       | 300000                     | 950   | 285                               | ---  | ---  | --- | 2B7 |     |
| 6A4  | POWER AMPLIFIER PENTODE             | MEDIUM 6-PIN | FIG. 8             | 4 1/2" x 1 1/8"                              | FILAMENT       | 6.3                | 0.3     | 180        | 180   | CLASS A AMPLIFIER                | 100                     | -4.5         | 50                | 0.65             | ---                       | ---                        | ---   | ---                               | ---  | ---  | --- | 6A4 |     |
| 6A7  | PENTAGRID CONVERTER                 | SMALL 7-PIN  | FIG. 20            | 4 1/2" x 1 1/8"                              | HEATER         | 6.3                | 0.3     | 250        | 100   | CONVERTER                        | 250                     | -3.0 min.    | 100               | 2.2              | 3.5                       | 360000                     | Anode Grid (#3) 200 max. volts, 4.0 ma. Oscillator Grid (#1) Resistor, 50000 ohms. Conversion conductance, 520 micromhos. | 6A7                               |  |      |     |     |     |
| 6B7  | DUPLEX-DIODE PENTODE                | SMALL 7-PIN  | FIG. 21            | 4 1/2" x 1 1/8"                              | HEATER         | 6.3                | 0.3     | 250        | 125   | PENTODE UNIT AS R.F. AMPLIFIER   | 100                     | -3.0         | 100               | 1.7              | 5.8                       | 300000                     | 950   | 285                               | ---  | ---  | --- | 6B7 |     |
| 6C6  | TRIPLE-GRID DETECTOR AMPLIFIER      | SMALL 6-PIN  | FIG. 11            | 4 1/2" x 1 1/8"                              | HEATER         | 6.3                | 0.3     | 250        | 100   | SCREEN GRID R.F. AMPLIFIER       | 250                     | -3.0         | 100               | 0.5              | 2.0                       | 800000                     | 1225  | exceeds 1.5 meg.                  | Plate coupling resistor 250000 ohms. Grid coupling resistor 250000 ohms. | ---  | --- | --- | 6C6 |
| 6D6  | TRIPLE-GRID SUPER-CONTROL AMPLIFIER | SMALL 6-PIN  | FIG. 11            | 4 1/2" x 1 1/8"                              | HEATER         | 6.3                | 0.3     | 250        | 100   | SCREEN GRID R.F. AMPLIFIER       | 250                     | -3.0 min.    | 100               | 2.0              | 8.2                       | 800000                     | 1600  | 1280                              | Oscillator peak volts=7.0.   | ---  | --- | --- | 6D6 |

# Grids #3 and #5 are screen. Grid #4 is signal-input control-grid.

1 Applied through plate coupling resistor of 200000 ohms.

\*\*For grid of following tube.

x Applied through plate coupling resistor of 250000 ohms.

|       |                        |              |         |                 |              |     |       |     |      |                               |     |       |     |      |      |        |      |     |       |       |     |       |
|-------|------------------------|--------------|---------|-----------------|--------------|-----|-------|-----|------|-------------------------------|-----|-------|-----|------|------|--------|------|-----|-------|-------|-----|-------|
| 6F7   | TRIODE-PENTODE         | SMALL 7-PIN  | FIG. 27 | 4 1/2" x 1 1/8" | HEATER       | 6.3 | 0.3   | 100 | ---  | TRIODE UNIT AS R.F. AMPLIFIER | 100 | -3.0  | --- | ---  | 3.5  | 17800  | 450  | 800 | ---   | ---   | --- | 6F7   |
| 100-A | DETECTOR TRIODE        | MEDIUM 4-PIN | FIG. 1  | 4 1/2" x 1 1/8" | D-C FILAMENT | 5.0 | 0.25  | 45  | ---  | GRID LEAK DETECTOR            | 45  | ---   | --- | ---  | 1.5  | 30000  | 666  | 20  | ---   | ---   | --- | 100-A |
| 01-A  | DETECTOR TRIODE        | MEDIUM 4-PIN | FIG. 1  | 4 1/2" x 1 1/8" | D-C FILAMENT | 5.0 | 0.25  | 135 | ---  | CLASS A AMPLIFIER             | 90  | -4.5  | --- | ---  | 2.5  | 11000  | 725  | 8.0 | ---   | ---   | --- | 01-A  |
| 10    | POWER AMPLIFIER TRIODE | MEDIUM 4-PIN | FIG. 1  | 5 1/2" x 2 1/8" | FILAMENT     | 7.5 | 1.25  | 425 | ---  | CLASS A AMPLIFIER             | 350 | -31.0 | --- | ---  | 16.0 | 5150   | 1550 | 8.0 | 11000 | 0.9   | 10  |       |
| 11    | DETECTOR TRIODE        | WD 4-PIN     | FIG. 12 | 4 1/2" x 1 1/8" | D-C FILAMENT | 1.1 | 0.25  | 135 | ---  | CLASS A AMPLIFIER             | 90  | -4.5  | --- | ---  | 2.5  | 15500  | 425  | 6.6 | ---   | ---   | --- | 11    |
| 12    | DETECTOR TRIODE        | MEDIUM 4-PIN | FIG. 1  | 4 1/2" x 1 1/8" | D-C FILAMENT | 1.1 | 0.25  | 135 | ---  | CLASS A AMPLIFIER             | 135 | -10.5 | --- | ---  | 3.0  | 15000  | 440  | 6.6 | ---   | ---   | --- | 12    |
| 19    | TWIN-TRIODE AMPLIFIER  | SMALL 6-PIN  | FIG. 25 | 4 1/2" x 1 1/8" | D-C FILAMENT | 2.0 | 0.26  | 135 | ---  | CLASS A AMPLIFIER             | 135 | -3.0  | --- | ---  | 2.5  | 15000  | 440  | 6.6 | 10000 | 2.1   | 19  |       |
| 20    | POWER AMPLIFIER TRIODE | SMALL 4-PIN  | FIG. 1  | 4 1/2" x 1 1/8" | D-C FILAMENT | 3.3 | 0.132 | 135 | ---  | CLASS A AMPLIFIER             | 90  | -16.5 | --- | ---  | 3.0  | 8000   | 415  | 3.3 | 9600  | 0.045 | 20  |       |
| 22    | R-F AMPLIFIER TRIODE   | MEDIUM 4-PIN | FIG. 4  | 5 1/2" x 1 1/8" | D-C FILAMENT | 3.3 | 0.132 | 135 | 67.5 | SCREEN GRID R.F. AMPLIFIER    | 135 | -1.5  | 45  | 0.6* | 1.7  | 725000 | 375  | 270 | ---   | ---   | --- | 22    |
| 24-A  | R-F AMPLIFIER TRIODE   | MEDIUM 5-PIN | FIG. 9  | 5 1/2" x 1 1/8" | HEATER       | 2.5 | 1.75  | 275 | 90   | SCREEN GRID R.F. AMPLIFIER    | 180 | -3.0  | 90  | 1.7* | 4.0  | 400000 | 1000 | 400 | ---   | ---   | --- | 24-A  |
| 26    | AMPLIFIER TRIODE       | MEDIUM 4-PIN | FIG. 1  | 4 1/2" x 1 1/8" | FILAMENT     | 1.5 | 1.05  | 180 | ---  | CLASS A AMPLIFIER             | 90  | -7.0  | --- | ---  | 2.9  | 8900   | 935  | 8.3 | ---   | ---   | --- | 26    |
| 27    | DETECTOR TRIODE        | MEDIUM 5-PIN | FIG. 8  | 4 1/2" x 1 1/8" | HEATER       | 2.5 | 1.75  | 275 | ---  | CLASS A AMPLIFIER             | 180 | -14.5 | --- | ---  | 6.2  | 7300   | 1150 | 8.5 | ---   | ---   | --- | 27    |
| 30    | DETECTOR TRIODE        | SMALL 4-PIN  | FIG. 1  | 4 1/2" x 1 1/8" | D-C FILAMENT | 2.0 | 0.06  | 180 | ---  | CLASS A AMPLIFIER             | 135 | -9.0  | --- | ---  | 3.0  | 10300  | 900  | 9.3 | ---   | ---   | --- | 30    |

\*For Grid-leak Detection—plate volts 45, grid return to + filament or to cathode.

• Applied through plate coupling resistor of 250000 ohms or 500 henry choke shunted by 0.25 megohm resistor. \*Maximum


|       |                                     |              |         |                 |              |     |      |     |      |                            |     |       |      |      |      |        |      |     |       |       |     |       |
|-------|-------------------------------------|--------------|---------|-----------------|--------------|-----|------|-----|------|----------------------------|-----|-------|------|------|------|--------|------|-----|-------|-------|-----|-------|
| 31    | POWER AMPLIFIER TRIODE              | SMALL 4-PIN  | FIG. 1  | 4 1/2" x 1 1/8" | D-C FILAMENT | 2.0 | 0.13 | 180 | ---  | CLASS A AMPLIFIER          | 135 | -22.5 | ---  | ---  | 8.0  | 4100   | 925  | 3.8 | 7000  | 0.185 | 31  |       |
| 32    | R-F AMPLIFIER TRIODE                | MEDIUM 4-PIN | FIG. 4  | 5 1/2" x 1 1/8" | D-C FILAMENT | 2.0 | 0.06 | 180 | 67.5 | SCREEN GRID R.F. AMPLIFIER | 135 | -3.0  | 67.5 | 0.4* | 1.7  | 950000 | 640  | 610 | ---   | ---   | --- | 32    |
| 33    | POWER AMPLIFIER PENTODE             | MEDIUM 5-PIN | FIG. 6  | 4 1/2" x 1 1/8" | D-C FILAMENT | 2.0 | 0.26 | 180 | 180  | CLASS A AMPLIFIER          | 180 | -18.0 | 180  | 5.0  | 22.0 | 55000  | 1700 | 90  | 6000  | 1.4   | 33  |       |
| 34    | SUPER-CONTROL R-F AMPLIFIER PENTODE | MEDIUM 4-PIN | FIG. 4A | 5 1/2" x 1 1/8" | D-C FILAMENT | 2.0 | 0.06 | 180 | 67.5 | SCREEN GRID R.F. AMPLIFIER | 135 | -3.0  | 67.5 | 1.0  | 2.8  | 600000 | 600  | 350 | ---   | ---   | --- | 34    |
| 35    | SUPER-CONTROL R-F AMPLIFIER TRIODE  | MEDIUM 5-PIN | FIG. 9  | 5 1/2" x 1 1/8" | HEATER       | 2.5 | 1.75 | 275 | 90   | SCREEN GRID R.F. AMPLIFIER | 180 | -3.0  | 90   | 2.5* | 6.3  | 300000 | 1020 | 305 | ---   | ---   | --- | 35    |
| 36    | R-F AMPLIFIER TRIODE                | SMALL 5-PIN  | FIG. 9  | 4 1/2" x 1 1/8" | HEATER       | 6.3 | 0.3  | 250 | 90   | SCREEN GRID R.F. AMPLIFIER | 100 | -1.5  | 55   | ---  | 1.8  | 550000 | 850  | 470 | ---   | ---   | --- | 36    |
| 37    | DETECTOR TRIODE                     | SMALL 5-PIN  | FIG. 8  | 4 1/2" x 1 1/8" | HEATER       | 6.3 | 0.3  | 250 | ---  | CLASS A AMPLIFIER          | 90  | -6.0  | ---  | ---  | 2.5  | 11500  | 800  | 9.2 | ---   | ---   | --- | 37    |
| 38    | POWER AMPLIFIER PENTODE             | SMALL 5-PIN  | FIG. 9A | 4 1/2" x 1 1/8" | HEATER       | 6.3 | 0.3  | 250 | 250  | CLASS A AMPLIFIER          | 100 | -9.0  | 100  | 1.2  | 7.0  | 140000 | 875  | 120 | 15000 | 0.37  | 38  |       |
| 39-44 | SUPER-CONTROL R-F AMPLIFIER PENTODE | SMALL 5-PIN  | FIG. 9A | 4 1/2" x 1 1/8" | HEATER       | 6.3 | 0.3  | 250 | 90   | SCREEN GRID R.F. AMPLIFIER | 90  | -3.0  | 90   | 1.6  | 5.6  | 375000 | 960  | 360 | ---   | ---   | --- | 39-44 |

\*For Grid-leak Detection—plate volts 45, grid return to + filament or to cathode. # Either A, C, or D, C, may be used on filament or heater, except as specifically noted. For use of D, C, on A-C filament types, decrease stated grid volts by 1/2 (approx.) of filament voltage.

• Applied through plate coupling resistor of 250000 ohms or 500-henry choke shunted by 0.25 megohm resistor.

• Applied through plate coupling resistor of 100000 ohms.

\*Maximum

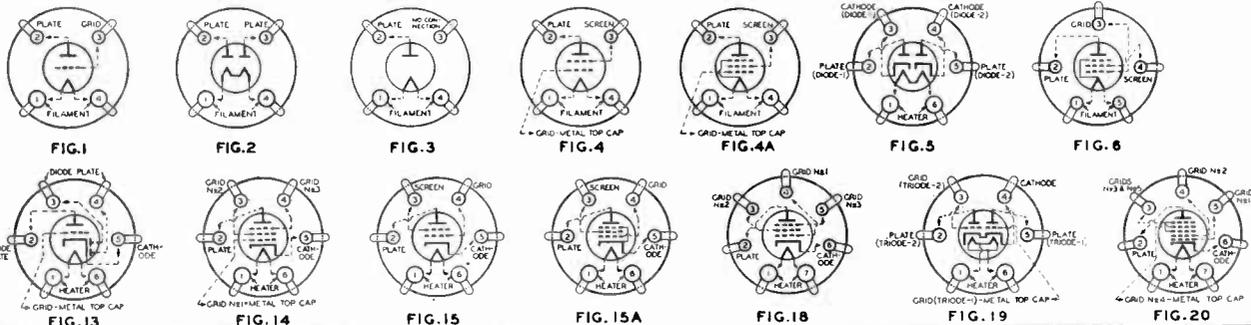

| INDEX OF TYPES BY USE AND BY CATHODE VOLTAGE |                              |   |                                |                                |                                 |            |               |
|--|------------------------------|---|--------------------------------|--------------------------------|---------------------------------|------------|---------------|
| CATHODE VOLTS                                | POWER AMPLIFIERS             | VOLTAGE AMPLIFIERS Including Duplex-Diode Types | CONVERTERS IN SUPERHETERODYNES | DETECTORS                      | MIXER TUBES IN SUPERHETERODYNES | RECTIFIERS | CATHODE VOLTS |
| 1.1  | ---                          | 11, 12  | ---                            | 11, 12                         | ---                             | ---        | 1.1           |
| 1.5  | ---                          | 26  | ---                            | ---                            | ---                             | ---        | 1.5           |
| 2.0  | 19, 31, 33, 49               | 30, 32, 34                                      | 1A6, 1C6                       | 30, 32                         | 1A6, 1C6, 34                    | ---        | 2.0           |
| 2.5  | 2A3, 2A5, 45, 46, 47, 53, 59 | 2A6, 2B7, 2A-A, 27, 35, 55, 56, 57, 58          | 2A7                            | 2A6, 2B7, 2A-A, 27, 55, 56, 57 | 2A7, 2A-A, 35, 57, 58           | 82         | 2.5           |
| 3.3  | 20                           | 22, '99   | ---                            | '99                            | ---                             | ---        | 3.3           |

| TYPE | NAME                            | BASE         | SOCKET CONNECTIONS | DIMENSIONS OVERALL LENGTH X DIAMETER | CATHODE TYPE | RATING             |       |        | USE Values in right give operating conditions and characteristics for indicated typical use | PLATE SUPPLY VOLTS               | GRID VOLTS        | SCREEN VOLTS            | SCREEN MILLI-AMP. | PLATE MILLI-AMP.  | A-C PLATE RESISTANCE OHMS | MUTUAL CONDUCTANCE MICRO-MHMS | VOLT-AGE AMPLIFICATION FACTOR | LOAD FOR STATED POWER OUTPUT OHMS | POWER OUTPUT WATTS    | TYPE                 |              |    |
|------|---------------------------------|--------------|--------------------|--------------------------------------|--------------|--------------------|-------|--------|---|----------------------------------|-------------------|-------------------------|-------------------|-------------------|---------------------------|-------------------------------|-------------------------------|-----------------------------------|-----------------------|----------------------|--------------|----|
|      |                                 |              |                    |                                      |              | FILAMENT OR HEATER | PLATE | SCREEN |   |                                  |                   |                         |                   |                   |                           |                               |                               |                                   |                       |                      |              |    |
| 40   | VOLTAGE AMPLIFIER TRIODE        | MEDIUM 4-PIN | FIG. 1             | 4 1/2" x 1 1/2"                      | D-C FILAMENT | 5.0                | 0.25  | 180    | —   | CLASS A AMPLIFIER                | 135 M<br>180 M    | —                       | —                 | 0.2<br>0.2        | 150000<br>150000          | 200<br>200                    | 30<br>30                      | —                                 | —                     | 40                   |              |    |
| 41   | POWER AMPLIFIER PENTODE         | SMALL 8-PIN  | FIG. 15A           | 4 1/2" x 1 1/2"                      | HEATER       | 6.3                | 0.4   | 250    | 250   | CLASS A AMPLIFIER                | 100<br>180<br>250 | —7.0<br>—13.5<br>—18.0  | 100<br>150<br>250 | 1.6<br>3.0<br>3.5 | 9.0<br>18.5<br>32.0       | 103500<br>81000<br>68000      | 1450<br>1850<br>2200          | 150<br>150<br>150                 | 13000<br>9000<br>7600 | 0.33<br>1.50<br>3.40 | 41           |    |
| 42   | POWER AMPLIFIER PENTODE         | MEDIUM 8-PIN | FIG. 15A           | 4 1/2" x 1 1/2"                      | HEATER       | 6.3                | 0.7   | 250    | 250   | CLASS A AMPLIFIER                | 95                | —16.5                   | 250               | 6.5               | 34.0                      | 100000                        | 2200                          | 220                               | 7000                  | 3.00                 | 42           |    |
| 43   | POWER AMPLIFIER PENTODE         | MEDIUM 8-PIN | FIG. 15A           | 4 1/2" x 1 1/2"                      | HEATER       | 25.0               | 0.3   | 135    | 135   | CLASS A AMPLIFIER                | 95<br>135         | —15.0<br>—20.0          | 95<br>135         | 4.0<br>7.0        | 20.0<br>34.0              | 45000<br>35000                | 2000<br>2300                  | 90<br>80                          | 4500<br>4000          | 0.90<br>2.00         | 43           |    |
| 45   | POWER AMPLIFIER TRIODE          | MEDIUM 4-PIN | FIG. 1             | 4 1/2" x 1 1/2"                      | FILAMENT     | 2.5                | 1.5   | 275    | —   | CLASS A AMPLIFIER                | 180<br>250        | —31.5<br>—50.0<br>—56.0 | 180<br>250<br>275 | —                 | 31.0<br>34.0              | 1550<br>1510                  | 2125<br>2175                  | 3.5<br>3.5                        | 7000<br>3900          | 0.82<br>1.60         | 45           |    |
| 46   | DUAL-GRID POWER AMPLIFIER       | MEDIUM 8-PIN | FIG. 7             | 5 1/2" x 2 1/2"                      | FILAMENT     | 2.5                | 1.75  | —      | —   | CLASS B AMPLIFIER                | 300<br>400        | 0<br>0                  | —                 | —                 | —                         | —                             | —                             | —                                 | —                     | 5200<br>5800         | 16.0<br>20.0 | 46 |
| 47   | POWER AMPLIFIER PENTODE         | MEDIUM 8-PIN | FIG. 8             | 5 1/2" x 2 1/2"                      | FILAMENT     | 2.5                | 1.75  | 250    | 250   | CLASS A AMPLIFIER                | 250               | —16.5                   | 250               | 6.0               | 31.0                      | 60000                         | 2500                          | 150                               | 7000                  | 2.7                  | 47           |    |
| 48   | POWER AMPLIFIER TETRODE         | MEDIUM 8-PIN | FIG. 18            | 5 1/2" x 2 1/2"                      | D-C HEATER   | 30.0               | 0.4   | 125    | 100   | CLASS A AMPLIFIER                | 96<br>125         | —19.0<br>—20.0          | 96<br>100         | 9.5               | 52.0<br>56.0              | —<br>3900                     | —<br>—                        | —<br>—                            | 1500<br>1500          | 2.0<br>2.5           | 48           |    |
| 49   | DUAL-GRID POWER AMPLIFIER       | MEDIUM 8-PIN | FIG. 7             | 4 1/2" x 1 1/2"                      | D-C FILAMENT | 2.0                | 0.12  | 180    | —   | CLASS B AMPLIFIER                | 135<br>180        | —20.0<br>0              | —                 | —                 | —                         | 4.0<br>4.75                   | 1125                          | 4.7                               | 12000                 | 3.5                  | 49           |    |
| 50   | POWER AMPLIFIER TRIODE          | MEDIUM 4-PIN | FIG. 1             | 6 1/2" x 2 1/2"                      | FIL. HEAT    | 7.5                | 1.25  | 450    | —   | CLASS B AMPLIFIER                | 300<br>400<br>450 | —54.0<br>—70.0<br>—84.0 | —                 | —                 | 35.0<br>55.0              | 2000<br>1800<br>1800          | 1900<br>2100<br>2100          | 3.8<br>3.8<br>3.8                 | 4600<br>3670<br>4350  | 1.6<br>3.4<br>4.6    | 50           |    |
| 53   | TWIN-TRIODE AMPLIFIER           | MEDIUM 7-PIN | FIG. 24            | 4 1/2" x 1 1/2"                      | HEATER       | 2.5                | 2.0   | 300    | —   | CLASS B AMPLIFIER                | 300<br>0          | 0<br>0                  | —                 | —                 | —                         | —                             | —                             | —                                 | —                     | 8000<br>10000        | 8.0<br>10.0  | 53 |
| 55   | DUPLEX-DIODE TRIODE             | SMALL 8-PIN  | FIG. 13            | 4 1/2" x 1 1/2"                      | HEATER       | 2.5                | 1.0   | 250    | —   | TRIODE UNIT AS CLASS A AMPLIFIER | 135<br>180<br>250 | —10.5<br>—13.5<br>—20.0 | —                 | —                 | 6.0<br>6.0                | 8500<br>8500                  | 975<br>975                    | 8.3<br>8.3                        | 25000<br>20000        | 0.075<br>0.160       | 55           |    |
| 56   | SUPER-TRIODE AMPLIFIER DETECTOR | SMALL 8-PIN  | FIG. 8             | 4 1/2" x 1 1/2"                      | HEATER       | 2.5                | 1.0   | 250    | —   | CLASS A AMPLIFIER                | 250               | —13.5                   | —                 | —                 | 5.0                       | 9500                          | 1450                          | 13.8                              | —                     | —                    | 56           |    |
| 57   | TRIPLE-GRID DETECTOR AMPLIFIER  | SMALL 8-PIN  | FIG. 11            | 4 1/2" x 1 1/2"                      | HEATER       | 2.5                | 1.0   | 250    | 100   | SCREEN GRID R.F. AMPLIFIER       | 250               | —3.0                    | 100               | 0.5               | 2.0                       | —                             | —                             | —                                 | —                     | —                    | 57           |    |

\*For Grid-leak Detection—plate volts 45, grid return to + filament or to cathode.  
 †Requires different socket from small 7-pin.  
 ‡Grid next to plate tied to plate. ††Two grids tied together. †††For grid of following tube.  
 ‡‡Applied through plate coupling resistor of 25000 ohms.

| TYPE         | NAME                                | BASE                    | SOCKET CONNECTIONS | DIMENSIONS OVERALL LENGTH X DIAMETER | CATHODE TYPE | FILAMENT OR HEATER | PLATE | SCREEN | USE | PLATE SUPPLY VOLTS               | GRID VOLTS        | SCREEN VOLTS            | SCREEN MILLI-AMP. | PLATE MILLI-AMP.  | A-C PLATE RESISTANCE OHMS | MUTUAL CONDUCTANCE MICRO-MHMS | VOLT-AGE AMPLIFICATION FACTOR | LOAD FOR STATED POWER OUTPUT OHMS | POWER OUTPUT WATTS    | TYPE                   |              |    |
|--------------|-------------------------------------|-------------------------|--------------------|--------------------------------------|--------------|--------------------|-------|--------|-----|----------------------------------|-------------------|-------------------------|-------------------|-------------------|---------------------------|-------------------------------|-------------------------------|-----------------------------------|-----------------------|------------------------|--------------|----|
| 58           | TRIPLE-GRID SUPER-CONTROL AMPLIFIER | SMALL 8-PIN             | FIG. 11            | 4 1/2" x 1 1/2"                      | HEATER       | 2.5                | 1.0   | 250    | 100 | SCREEN GRID R.F. AMPLIFIER       | 250               | —3.0                    | 100               | 2.0               | 8.2                       | 80000                         | 1600                          | 1280                              | —                     | —                      | 58           |    |
| 59           | TRIPLE-GRID POWER AMPLIFIER         | MEDIUM 7-PIN            | FIG. 18            | 5 1/2" x 2 1/2"                      | HEATER       | 2.5                | 2.0   | 250    | 250 | CLASS A AMPLIFIER                | 250               | —28.0                   | —                 | —                 | 26.0                      | 2300                          | 2600                          | 6.0                               | 5000                  | 1.25                   | 59           |    |
| 71-A         | POWER AMPLIFIER TRIODE              | MEDIUM 4-PIN            | FIG. 1             | 4 1/2" x 1 1/2"                      | FILAMENT     | 5.0                | 0.25  | 180    | —   | CLASS A AMPLIFIER                | 90<br>180         | —19.0<br>—43.0          | —                 | —                 | 10.0<br>20.0              | 2170<br>1750                  | 1400<br>3.0                   | 3000<br>4800                      | 0.125<br>0.790        | 71-A                   |              |    |
| 75           | DUPLEX-DIODE HIGH-MU TRIODE         | SMALL 8-PIN             | FIG. 13            | 4 1/2" x 1 1/2"                      | HEATER       | 6.3                | 0.3   | 250    | —   | TRIODE UNIT AS CLASS A AMPLIFIER | 250 M             | —1.35                   | —                 | —                 | 0.4                       | —                             | —                             | —                                 | —                     | Gain per stage = 50-60 | 75           |    |
| 76           | SUPER-TRIODE AMPLIFIER DETECTOR     | SMALL 8-PIN             | FIG. 8             | 4 1/2" x 1 1/2"                      | HEATER       | 6.3                | 0.3   | 250    | —   | CLASS A AMPLIFIER                | 250 M             | —13.5                   | —                 | —                 | 5.0                       | 9500                          | 1450                          | 13.8                              | —                     | 76                     |              |    |
| 77           | TRIPLE-GRID DETECTOR AMPLIFIER      | SMALL 8-PIN             | FIG. 11            | 4 1/2" x 1 1/2"                      | HEATER       | 6.3                | 0.3   | 250    | 100 | SCREEN GRID R.F. AMPLIFIER       | 250               | —1.5<br>—3.0            | 60<br>100         | 0.4<br>0.5        | 1.7<br>2.3                | 65000<br>150000               | 1100<br>1250                  | 715<br>1500                       | —                     | —                      | 77           |    |
| 78           | TRIPLE-GRID SUPER-CONTROL AMPLIFIER | SMALL 8-PIN             | FIG. 11            | 4 1/2" x 1 1/2"                      | HEATER       | 6.3                | 0.3   | 250    | 125 | SCREEN GRID R.F. AMPLIFIER       | 90<br>250         | (—3.0) min.             | 90<br>125         | 1.3<br>1.7        | 5.4<br>7.0                | 315000<br>800000              | 1275<br>1450                  | 408<br>1100                       | —                     | —                      | 78           |    |
| 79           | TWIN-TRIODE AMPLIFIER               | SMALL 8-PIN             | FIG. 19            | 4 1/2" x 1 1/2"                      | HEATER       | 6.3                | 0.6   | 250    | —   | CLASS B AMPLIFIER                | 160<br>135        | 0<br>—                  | —                 | —                 | —                         | —                             | —                             | —                                 | —                     | 7000<br>14000          | 5.5<br>8.0   | 79 |
| 85           | DUPLEX-DIODE TRIODE                 | SMALL 8-PIN             | FIG. 13            | 4 1/2" x 1 1/2"                      | HEATER       | 6.3                | 0.3   | 250    | —   | TRIODE UNIT AS CLASS A AMPLIFIER | 180<br>250        | —10.5<br>—13.5<br>—20.0 | —                 | —                 | 6.0<br>6.0<br>8.0         | 8500<br>8500<br>7500          | 975<br>975<br>8.3             | 20000<br>20000                    | 0.160<br>0.350        | 85                     |              |    |
| 89           | TRIPLE-GRID POWER AMPLIFIER         | SMALL 8-PIN             | FIG. 14            | 4 1/2" x 1 1/2"                      | HEATER       | 6.3                | 0.4   | 250    | 250 | CLASS A AMPLIFIER                | 100<br>180<br>250 | —10.0<br>—18.0<br>—25.0 | 100<br>180<br>250 | 1.6<br>3.0<br>5.5 | 9.5<br>20.0<br>32.0       | 104000<br>80000<br>70000      | 1200<br>1550<br>1800          | 125<br>125<br>125                 | 10700<br>8000<br>6150 | 0.33<br>1.56<br>3.40   | 89           |    |
| V-99<br>X-99 | DETECTOR AMPLIFIER TRIODE           | SMALL 4-MUB SMALL 4-PIN | FIG. 10<br>FIG. 1  | 3 1/2" x 1 1/2"<br>4 1/2" x 1 1/2"   | D-C FILAMENT | 3.3                | 0.063 | 90     | —   | CLASS A AMPLIFIER                | 90                | —4.5                    | —                 | —                 | 2.5                       | 15500                         | 425                           | 6.6                               | —                     | —                      | V-99<br>X-99 |    |
| 112-A        | DETECTOR AMPLIFIER TRIODE           | MEDIUM 4-PIN            | FIG. 1             | 4 1/2" x 1 1/2"                      | D-C FILAMENT | 5.0                | 0.25  | 180    | —   | CLASS A AMPLIFIER                | 90<br>180         | —4.5<br>—13.5           | —                 | —                 | 5.0<br>7.7                | 5400<br>4700                  | 1575<br>1800                  | 8.5<br>8.5                        | —                     | —                      | 112-A        |    |

\*For Grid-leak Detection—plate volts 45, grid return to + filament or to cathode.  
 †Either A. C. or D. C. may be used on filament or heater, except as specifically noted. For use of D. C. on A-C filament types, decrease stated grid volts by 1/2 (approx.) of filament voltage.  
 ‡Requires different socket from small 7-pin.  
 ‡‡Grid #1 is control grid. Grid #2 is screen. Grid #3 tied to cathode.  
 ††Grid #1 is control grid. Grids #2 and #3 tied to plate. †††Applied through plate coupling resistor of 25000 ohms.  
 ‡‡Grids #1 and #2 connected together. Grid #3 tied to plate. †††For grid of following tube.

RECTIFIERS

|                  |                     |              |         |                 |          |      |      |   |   |                                    |                  |   |   |   |   |   |   |   |   |   |                  |
|------------------|---------------------|--------------|---------|-----------------|----------|------|------|---|---|------------------------------------|------------------|---|---|---|---|---|---|---|---|---|------------------|
| 523              | FULL-WAVE RECTIFIER | MEDIUM 4-PIN | FIG. 2  | 5 1/2" x 2 1/2" | FILAMENT | 5.0  | 3.0  | — | — | Maximum A-C Voltage per Plate..... | 500 Volts, RMS   | — | — | — | — | — | — | — | — | — | 523              |
| 1223             | HALF-WAVE RECTIFIER | SMALL 4-PIN  | FIG. 22 | 4 1/2" x 1 1/2" | HEATER   | 12.6 | 0.3  | — | — | Maximum D-C Output Current.....    | 250 Milliamperes | — | — | — | — | — | — | — | — | — | 1223             |
| 2525             | RECTIFIER-DOUBLER   | SMALL 8-PIN  | FIG. 9  | 4 1/2" x 1 1/2" | HEATER   | 25.0 | 0.3  | — | — | Maximum A-C Plate Voltage.....     | 250 Volts, RMS   | — | — | — | — | — | — | — | — | — | 2525             |
| 1-V <sup>9</sup> | HALF-WAVE RECTIFIER | SMALL 4-PIN  | FIG. 22 | 4 1/2" x 1 1/2" | HEATER   | 6.3  | 0.3  | — | — | Maximum D-C Output Current.....    | 125 Volts, RMS   | — | — | — | — | — | — | — | — | — | 1-V <sup>9</sup> |
| 80               | FULL-WAVE RECTIFIER | MEDIUM 4-PIN | FIG. 2  | 4 1/2" x 1 1/2" | FILAMENT | 5.0  | 2.0  | — | — | Maximum A-C Plate Voltage.....     | 350 Volts, RMS   | — | — | — | — | — | — | — | — | — | 80               |
| '81              | HALF-WAVE RECTIFIER | MEDIUM 4-PIN | FIG. 3  | 6 1/2" x 2 1/2" | FILAMENT | 7.5  | 1.25 | — | — | Maximum D-C Output Current.....    | 50 Milliamperes  | — | — | — | — | — | — | — | — | — | '81              |
| 82               | FULL-WAVE RECTIFIER | MEDIUM 4-PIN | FIG. 2  | 4 1/2" x 1 1/2" | FILAMENT | 2.5  | 3.0  | — | — | Maximum A-C Voltage per Plate..... | 500 Volts, RMS   | — | — | — | — | — | — | — | — | — | 82               |
| 83               | FULL-WAVE RECTIFIER | MEDIUM 4-PIN | FIG. 2  | 5 1/2" x 2 1/2" | FILAMENT | 5.0  | 3.0  | — | — | Maximum D-C Output Current.....    | 125 Milliamperes | — | — | — | — | — | — | — | — | — | 83               |
| 84<br>also 822   | FULL-WAVE RECTIFIER | SMALL 8-PIN  | FIG. 13 | 4 1/2" x 1 1/2" | HEATER   | 6.3  | 0.5  | — | — | Maximum A-C Voltage per Plate..... | 500 Volts, RMS   | — | — | — | — | — | — | — | — | — | 84<br>also 822   |

†Mercury Vapor Type. \*Interchangeable with Type 1.

| CATHODE VOLT | POWER AMPLIFIERS        | VOLTAGE AMPLIFIERS Including Duplex-Diode Types       | CONVERTERS IN SUPERHETERODYNES | DETECTORS                             | MIXER TUBES IN SUPERHETERODYNES       | RECTIFIERS  | CATHODE VOLTS |
|--------------|-------------------------|---|--------------------------------|---------------------------------------|---------------------------------------|-------------|---------------|
| 5.0          | 112-A, 71-A             | 01-A, 40, 112-A                                       | —                              | 00-A, 01-A, 40, 112-A                 | —                                     | S23, 80, 83 | 5.0           |
| 6.3          | 6A4, 38, 41, 42, 79, 89 | 6B7, 6C6, 6D6, 6P7, 36, 37, 39-44, 75, 76, 77, 78, 85 | 6A7, 6P7                       | 6B7, 6C6, 6P7, 36, 37, 75, 76, 77, 85 | 6A7, 6C6, 6D6, 6P7, 36, 39-44, 77, 78 | 1-V, 84     | 6.3           |
| 7.5          | 10, 50                  | —   | —                              | —                                     | —                                     | '81         | 7.5           |
| 12.6         | —                       | —   | —                              | —                                     | —                                     | 1223        | 12.6          |
| 25.0         | 43                      | —   | —                              | —                                     | —                                     | 2525        | 25.0          |
| 30.0         | 48                      | —   | —                              | —                                     | —                                     | —           | 30.0          |

Tube symbols and bottom views of socket connections have pin numbers according to the new system recently standardized by Radio Manufacturers Association, Inc. Courtesy RCA Radiotron Co., Inc. Copyright, 1934.





# Station Sparks *By Alice Remsen*

## CROONERS AND THE TOOTHACHE

**M**Y SISTER IVY, who lives in London, England, sends me an English weekly, "The Radio Times." Some of their comments on American programs are very amusing. This week there is a cartoon entitled "Baying At the Moon," and this comment follows: "It is a very good drawing of a negro sitting in a swamp apparently baying at the moon, and it looks to us very much like a visual conception of the people who croon with the dance bands. At least, we have often imagined that only a very melancholy negro sitting in a swamp with a bad toothache could produce some of the sounds we hear." . . . And speaking of amusing things, the housewives of the nation will no doubt be pleased to hear that Allan Prescott, the Wife Saver, is to continue his activities, via the NBC-WJZ network each Monday and Wednesday at 11:00 a. m., under the sponsorship of Fels and Co. This youngster manages to pack a lot of humor into the broadcasting of such prosaic things as "How to Turn Your Husband's Socks"—and "What to Do When the Milk Turns Sour." Associated with Prescott will be, of course, Ray Heatherton, the romantic baritone, and Oscar, the pianist, who is really Irving Miller; and do they have a good time together! Well, rather!! . . . There is a new morning commercial on three times weekly that you should enjoy; it is called "The Land of Beginning Again," featuring the poems and philosophic comment of Rod Arkell, the singing of Ruth Everest and Harrison Knox, the music of Lew White at his organ, and an instrumental ensemble. Each Monday, Wednesday and Friday morning at 10:30 a. m. over an NBC-WEAF network. Also, on Sunday the program will be on the air for a half-hour, with Louis Katzman's Orchestra furnishing the musical background instead of White and the ensemble, and with Arkell and the same soloists, at 4:30 p. m., over an NBC-WJZ network. . . .

## TIGERS AND BIRDIES

Frank Buck, Ali, Tim and the other jungle adventurers heard in Frank Buck's Pepsodent program, have moved from Chicago to New York, and will hereafter broadcast from Radio City. Charlie Range and Hal Woods, the sound effect men who are responsible for the trumpeting of elephants, the roar of tigers, chirping of tropical birds, and other jungle sounds, and Ferrin Fraser, the novelist, who writes the adventures for radio presentation, accompanied Buck to New York. . . . Josephine Gibson, celebrated cooking expert and head of the home economics department of the Heinz Company, is back on the air over an NBC-WJZ network with her Hostess Counsel talks each Monday, Wednesday and Fri-

day at 10:00 a. m. Miss G. speaks from the Heinz Auditorium, Pittsburgh, and is accompanied by Milton Lomask, violinist and concertmaster of the Pittsburgh Symphony, and Louis Miller at the organ. . . . Sunday afternoon at 2:00 p. m. brings us Anthony Frome, tenor, and Alwyn Bach, narrator, in a new series of fifteen-minute broadcasts under the sponsorship of the M. J. Breitenbach Company, over an NBC-WJZ network. Frome, who is known as the Poet Prince, brings a romantic cycle of songs from all over the world, with Bach setting the scene for each melody; we wander in fancy with the Poet Prince through many countries, while he sings folk songs in the native language of each country visited. . . .

## UNCLE EZRA ON DECK

City slickers of the East now have a chance to listen to a brand of rustic humor and philosophy that has captivated westerners, for old Uncle Ezra, long-time favorite of National Barn Dance audiences, has a series of thrice-weekly programs of his own. Under the sponsorship of the Dr. Miles Laboratories, Uncle Ezra now operates his own mythical small town, five-watt radio station over an NBC-WEAF network each Wednesday and Friday at 7:30 p. m., and each Sunday at 7:15 p. m. He is supported by a large cast of actors including his wife, Nora Gunneen. . . . Angelo Ferdinando and his orchestra have taken to the air for another winter from the Hotel Great Northern. Four times weekly over an NBC-WJZ network. . . . Isn't it grand!!!! Sherlock Holmes is coming back! The first broadcast will be on Sunday afternoon, November 11th, at 4:00 p. m. over an NBC-WJZ network. Richard Gordon will again impersonate Holmes, and Leight Lovell, veteran British stake artist, the vere beloved Watson. Joseph Bell, of course, will be heard in his old role, and it will be sponsored again by the George Washington Coffee concern, and I offer thanks here and now for the treat which I know is in store for me!! . . . Winter is upon us, at least it seems that way when cough drops start going on the air. This time it's Luden's. They have a jolly good show for you, too—Dick Liebert's Musical Revue, featuring Dick, of course, at the organ; Robert Armbruster and Milton Kraus, at two pianos, a novelty quartet and Mary Courtland, contralto. November 2d is the opening date, 8:15 p. m. the time, and WJZ the station—oh, yes, and the blue network. . . . Armbruster, by the way, is in charge of the dovetailing of musical fragments, original and otherwise, to be used in the sequences of the Lux Radio Theatre presentations, each Sunday at 2:30 p. m. over an NBC-WJZ network. . . .

## HERE COMES TITO GUIZAR

Over at CBS Tito Guizar has started his new series for Brillo, each Sunday at 12:30 p. m. . . . and those famous "Og, Son of Fire" stories are being dramatized for the kids three times a week, Mondays, Wednesdays and Fridays at 5:00 p. m. These stories, as you probably know, were originally written by Irving Crump for the "Boys Lie" magazine; now they are being used to advertise the Libby, McNeill & Libby products. . . . Another popular series has returned to CBS—"Marie, the Little French Princess," five times weekly, at 2:00 p. m. . . . The Curtis Institute of Music, Philadelphia, will present its sixth annual series of vocal and orchestral concerts over the Columbia network beginning Wednesday, October 24th, at 4:15 p. m. . . . The garage of

America's Little House, at Park Avenue and 39th Street, is being used as a broadcasting studio by CBS; one of the programs heard regularly from there is the Triangle Club, sponsored by Benjamin Moore and Co.; each Wednesday at 11:30 a. m. starting on October 24th. . . . Leon Belasco and his orchestra are back on the air from the Casino de Patee; twice weekly, Sundays at 11:30 p. m. and Wednesdays at 11:00 p. m. CBS. . . . It is Alexander Gray who is pinch-hitting for Everett Marshall on the Broadway Varieties show these Wednesdays at 8:30 p. m. Everett is having his tonsils out. . . . The American School of the Air opens again on WABC and network for its sixth consecutive season, on Monday, October, 22d, and each day thereafter except Saturday and Sundays, at 2:30 p. m. . . . Gordon, Dave and Bunny, the Oxol Trio, have had their contract renewed, and may still be heard each Monday and Wednesday at 5:45 p. m. . . . Another popular program to return to the air is Columbia's Dramatic Guild, Sundays at 10:30 p. m. . . . Waring's Pennsylvanians are all set for a five-week vaudeville tour beginning November 2d. They will play Cleveland, Pittsburgh, Washington, Baltimore, and Philadelphia. So look for them in your home town. . . .

## ABS SPREADS OUT

The American Broadcasting System now boasts of eighteen stations in its tie-up. Burt McMurtrie, director of program operations for ABS, is planning an extensive schedule of well-known names in the radio and theatrical field which he will present this winter over the newly formed network. Well, the more networks the merrier, so far as the artist is concerned; it means that much more work. . . . An old WLW artist, Tony Cabooch, and his daughter, Jimmy Dew, have been signed by ABS for a five-time weekly schedule. . . . Brad Browne, an old friend of CBS fame, will also be heard in the "Wild Goose Chase," which is nothing more nor less than the old "Nitwit" hour—our pals, Lord Ashcart, Professor R. U. Musclebound, Aphrodite Godiva, Madame Mocha de Polka, etc., will be heard with Brad; Mondays at 10:00 p. m. . . . Trixie Friganza has also been coralled by ABS as the Mistress of Ceremonies on their "Americana" program, which may be heard for a full hour each Saturday night at 9:00 p. m. . . . Another old time variety actress, Marie Hartman, has been signed by ABS to appear in a series entitled "Furnished Rooms," written especially for her by Ned Joyce Heaney. These sketches will be heard each Monday, Wednesday and Friday at 8:45 p. m. over the ABS-WMCA network. . . .

## STUDIO NOTES

Johnny Green and Betty Barthell are the latest vaudeville combination to be recruited from radio. . . . David Ross was the first person around the CBS studios to show up wearing his winter spats. . . . Elsie Thompson, formerly organist at the Brooklyn Paramount Theatre, has joined the CBS staff as pianist and organist. . . . Peter Van Steeden, NBC orchestra leader, is a handball enthusiast. . . . John Seagle, NBC baritone, was born in Paris. . . . You should taste Jimmy Melton's lemon chiffon pie. Yes; he makes it himself. . . . Frank Black's parents were Dutch Quakers. . . . Ralph Kirby is receiving instructions in flying from Jack Ericson, "the flying bandsman." . . . Irene Beasley never sings before breakfast. . . . Jack Benny smokes on an average of twenty cigars a day. . . . Frank Parker skips rope every morning for fifteen minutes. . . . A short featuring the Pickens girls is now being shown in theatres. Little Patti plays the ingenue lead. . . .

## STATIONS SEEK NEW TALENT

Stations are seeking new artists, new songs and new dramatic pieces. Some hold auditions in the form of competition.

## RADIO

### ENGINEER OR JUST HANDYMAN?

Why study courses costing three times as much and hit only the "high spots" of what you want?

Here's a Radio and Television home-study course that will give you sound engineering principles. Not just elementary instruction but advanced training that's vital—yet a beginner can master it!

Ask about our fair price. Less than

**\$1.25 a Week**

for a few, short weeks! Write

**Radio Technological College**

1202 OMAR AVE. HOUSTON, TEXAS

## Quick-Action Classified Advertisements

5 cents a word. 50 cents minimum.

**WORK AT HOME:** Men, women make good money. Particulars for stamp. Chas. Link, 3286 East 116th St., Cleveland, Ohio.

**INVENTIONS WANTED,** Patented or unpatented, any size, any material, for any legitimate purpose. Now is the time to act. Send us your ideas. A square deal assured. Bosley Mfg. Co., 79 High Street, Torrington, Conn.

**COMPLETE TRAINING FOR AMATEUR LICENSE,** \$1.50 weekly. N. Y. Wireless School, 4 West 105th Street, New York City; phone: CLarkson 2-7456.

**POEMS SET TO MUSIC**—Send poems to McNeil, Bach. of Music. 1582 West 27th St., Los Angeles, Calif.

**"GATEWAY TO RADIO"** by Maj. Ivan Fifth and Gladys Shaw Erskine. An intimate exposition by experienced authors, directors and players, of the radio broadcasting industry, with helpful hints on gaining success as a radio author or actor. Contains much of interest to sponsors, program-builders, studio directors, advertising agencies and listeners. Contains reprints of manuscripts of successful air plays. Price \$2.50. Book Dept., Radio World, 145 W. 45th St., N. Y. City.

**TECHNICAL SCHOOL GRADUATE** wants position in radio factory or laboratory. Factory experience. Write B. Mac-Holmes, Box 132, Corona, N. Y.

**SPECIAL**—500 business cards, \$1.25. QSL cards, lowest prices. Cumberland Printing Co., Box 2145, Knoxville, Tenn.

**CAST ALUMINUM RADIO CHASSIS.** Send 10-cent stamp for blueprint. Valentine, Stewartsville, New Jersey.

**RADIO WORLD AND RADIO NEWS.** Both for one year \$7.00. Foreign \$8.50. Radio World, 145 W. 45th St., N. Y. City.

## U. S. GOVERNMENT SHORT-WAVE STATION LIST

2,400 short-wave stations listed by frequency, wavelength, with call, location, and power. Some time-tables included. All the short-wave phone transmitters on earth (except amateurs)! Distance map for world application printed right in the book!

### THE CONTENTS:

**Station Identification:** List of the most popular short-wave program stations of the world that use characteristic "air signatures."

**Foreign Alphabetic Pronunciation:** How the letters of the alphabet and numbers 1 to 50 are pronounced in English, French, Spanish, German and Portuguese.

**Short-Wave Broadcasting and Police Radio Stations by Countries:** The calls, location and frequencies are given for the whole world. It repeats data found in the main grouping of the 2,400 stations by frequencies.

**Distances to Foreign Cities:** A textual and map-illustrated explanation of how to determine how far any one city on earth is from some other city.

**Short-Wave Radiophone Stations by Frequencies:** This is the comprehensive, never-before-available list of the 2,400 or more stations, including all the program stations on earth that send on short waves, using phone (speech and music) but not including amateurs. A treat unparalleled in radio history—the most accurate list of its kind man has ever produced!

**Time Zone Chart:** This insert (stitched right in the book) is a black and white reproduction of a colored chart issued by the Hydrographic Office, Navy Department.

Send \$1.00 for 8-weeks subscription for RADIO WORLD and ask for "World Short-Wave Radiophone Transmitters" sent post-paid as premium.

**RADIO WORLD**

145 WEST 45th STREET,  
NEW YORK CITY

# Presenting the New... POWER TONE Signal Generators



## Model 77 DeLuxe Type SIGNAL GENERATOR

- Calibrated Frequency Range 115-3000 K.C. with a 1000 cycle Modulated Signal.
- Operates efficiently on A.C. or D.C. Current.
- The Model 77 signal generator is the ideal for simplicity and accuracy in service oscillators.


Another startling feature in the Signal Generator is the new Egert dial employed. This new dial allows the serviceman to absolutely read accuracies as close as 500 cycles at any point of the broadcast band. This dial in conjunction with the electron coupled oscillator gives a standard as close as 1/10 of 1% of frequency. The appearance of the unit is beautiful in every respect. The entire unit is completely enclosed in a handsome black metal etched portable carrying case. A calibrated curve with a complete set of operating instructions are supplied with each oscillator. Also instructions are given how to add an attenuator.

Battery Model: Size 6x5x9".  
Weight 4½ pounds.

List Price \$25.00.  
Cat. No. PO-77. **\$ 10.95**  
NET

THE tubes employed are a 6A7 and a '37. The 6A7 operates in a unique circuit which generates audio and radio frequencies from this same tube. The radio frequency circuit uses an electron coupled type oscillator which is inherently extremely stable. This circuit generates powerful harmonics which are available down to 10 meters. The .F. modulated signal can be employed for checking intermediate frequencies and for testing the general overall gang of All-Wave frequency circuits. The audio frequency note generated by the 6A7 is fixed at 1,000 cycles and is brought out to tip jacks on the front panel. This signal may be employed to check speech amplifiers, condensers, coils and etc., as well as being capable of supplying an audio signal which is always of use about the service laboratory. By this arrangement it is possible to use the audio frequency note separately. In this way the instrument allows the user to obtain either pure R.F., pure radio or modulated R.F.

## BERNARD SIGNAL GENERATOR

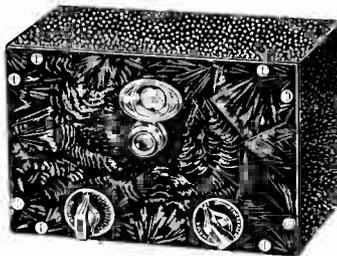


### High Stability; Accuracy 1%

HERE IS THE FIRST NEWS of our exclusive battery-operated Signal Generator, designed by Herman Bernard, and using his frequency-calibrated scale for fundamentals of 135 to 280 kc. with all popular intermediate frequencies inscribed right on the dial, and with calibration, also directly on the dial, for the broadcast band. Thus coverage from 135 to 1,520 kc is read. Higher frequencies, almost without limit, also can be measured without confusion. And the price is the world's lowest for such an instrument.

### No Charts! Scale is Directly Read in Frequencies

This laboratory-tested Bernard precision instrument, Model 336-SG, uses a 34 r-f oscillator in a stabilized circuit, has attenuator that contributes NO DETUNING, and has optional modulated-unmodulated service by switching. The audio oscillator is a 30. Electron coupling is used between a.f. and r.f., and also between output and measured circuit. Accuracy is 1 per cent. Model 336-SG is in a crinkle-finish black shield cabinet, 9" wide, 6" high, 5" front to back, weighs 7½ lbs. complete. It has bar-handle control of volume and modulation. It is useful for lining up super-heterodyne i-f channels, also the r-f channels of any receivers, and can be used satisfactorily for peaking on short waves as well. Instruction sheet supplied. Order Cat 336-SG, wired, complete with 22.5v. B battery, 4.5v. A battery, and tubes, ready to operate, (shipping weight, 8 lbs.) Cat. No. **\$7.95**  
336-SG. NET

## TEST OSCILLATOR With Output Indicator

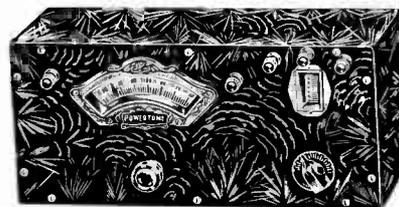

ACCURATELY calibrated with direct reading of major frequencies on full vision tuning dial. Rigid design and special oscillator circuit guarantee a clean steady output signal, which will not drift or shift under any conditions. Supplied in three models: A.C., A.C.-D.C. universal and Battery.

Extreme care has been taken in its construction and accuracy is guaranteed to be better than 2%. This rating is extremely conservative. In many instances accuracy better than 1% is obtained. The primary scale is calibrated from 50 to 150 k.c. The bars are 1 k.c. apart from 50 to 80 k.c. and 2 k.c. apart from 80 to 150 k.c. Therefore when used with TRF receivers (using the 10th harmonic) the separation as registered by the calibration points is 10 k.c. from 500 to 800 k.c. to 1500 k.c.

On the upper or secondary scale the popular intermediate frequencies are clearly marked: 175, 260, 400 and 450 k.c. with 177.5-175-172.5 spotted. Frequencies not marked can be obtained by means of harmonics, by simply dividing the desired frequency by small whole numbers to obtain the nearest scale frequency.

Strong harmonics are present due to the character of the oscillator circuit employed. In actual practice sufficient signal is available for checking purposes up to the 50th harmonic and beyond. In many cases strong steady signals have been obtained up to the 150th harmonic.

Output indicator consists of a built in glow tube, which is extremely sensitive and follows every variation in frequency and intensity of the signal impressed on the indicator. **\$10.95**  
All Models

New 192 Page  
Short-Wave and  
P. A. Manual 50c

TRY-MO RADIO CO., Inc.  
85-RW CORTLANDT STREET  
179 GREENWICH STREET  
NEW YORK CITY

VISIT OUR  
BARGAIN  
BASEMENTS

# Instructions for Servicing Automobile Receivers

The Diamond of the Air auto set, described on opposite page, is a six-tube superheterodyne using the latest type of high-efficiency tubes and newest super circuit, giving exceptional sensitivity and tone quality, in a compact design, easy to install and service.

## Installation Procedure

1. After the set has been unpacked, remove the four screws from bottom of cabinet, remove the front cover by carefully inserting screw driver at either side and exerting slight twisting pressure, slide chassis forward out of cabinet and inspect tubes to make sure if they are completely down in their sockets, after which replace chassis, front of cabinet and four screws as they were originally.
2. Determine most satisfactory mounting position on bulkhead which should be at the left-hand side or directly in front of steering column. Spot the mounting bolt location and drill 1/2 inch diameter hole. Insert bolt through hole and assemble washer and nut on engine side. Hang receiver over bolt head and tighten nut.
3. Attach flexible shafts to control unit by first inserting shaft as far in as possible and then tighten set screws of shaft housing, being careful they are not so tight as to cause shaft to bind in housing.
4. Mount control unit on steering post in approximately correct position. Set pointer to "530" on the dial. Turn upper control on set to extreme clockwise position. Carefully place right hand shaft in position on upper control of set and tighten screws. Next turn lower control of set to left until switch snaps, remove left-hand knob from control head by turning to correct position, place left-hand shaft in position on lower control of set and tighten set screws securely.
5. Adjust control unit position so that shafts leave set with least amount of bend possible and fasten securely in this position. Trial of controls will show best location for smooth operation.
6. Attach heavy rubber-covered lead to ammeter terminal.
7. Connect pilot light wire from control

head to short black wire on set, making connection close to set, and tape up joint. Ground shield by loosening screw under nearest corner of set and connecting wire therefrom to end of shield and tighten up screw.

8. Disconnect ignition leads from spark plugs, attach one suppressor to top of each plug and reattach the ignition lead to free end of suppressor. Disconnect center wire from distributor head, and substitute distributor suppressor, then plug center wire into free end of suppressor.

9. Attach generator bypass condenser to generator frame by means of screw holding cut-out. Connect wire from condenser to generator side of cut-out switch.

10. A roof antenna is usually best, although antenna beneath the car will usually be found satisfactory. Connect shielded lead from set to antenna lead-in. Lead-in should be shielded its complete length and this shield grounded to car as near the antenna as possible and the other end connected to shielded loom coming from the set. Thick covering between sheath and conductor is necessary to avoid loss due to capacity to ground.

11. Turn left-hand knob on control head to right. If connection directions have been correctly followed, dial should become illuminated immediately and the tubes reach correct operating temperature in approximately 30 seconds.

12. Operation: The right-hand knob is the tuning control. The left-hand knob is a combination switch, volume control and key which locks the set when turned completely to left and pulled out.

## Service Notes

If the radio fails to operate when unpacked, or stops working after a few days, proceed as follows: (1) Have tubes checked. (2) Remove chassis and check for loose connections. (3) Give the set a check-over entirely.

The circuit diagram on opposite page gives all necessary resistance and capacity values for servicing the set.

Balancing intermediate frequency coils. These are peaked to 175 kc, and are trimmed through the top of the tall cans by means of a small screwdriver and a 5/16-inch socket wrench. Chassis must first be removed from cabinet and signal from test oscillator fed into grid cap of the 6A7 tube.

Balancing R-F Coils. The tuning control must first be attached to tuning condenser shaft with pointer set to 530 when tuning condenser is turned to maximum. Tune in a weak signal at its proper dial marking near 1,400 and adjust first the second trimmers on variable from front of chassis for loudest signal. If signal does not come at proper dial setting carefully adjust rear trimmer on variable to shift signal to its proper location and then readjust first and second trimmers. After reinstalling set in car slightly readjust first trimmer through hole in top of cabinet.

Ignition Noise. Fouled plugs or plugs with improperly adjusted gaps will affect the operation of the set. Burned or improperly adjusted breaker points will also impair the performance. In some cases a .5 mfd. or 1 mfd. condenser connected from ammeter to car frame will be required. Also, in some installations using a roof antenna, a .5 mfd. condenser connected from car frame to dome lamp lead at point where it leaves bulkhead will be required. It is usually necessary to connect a .5 mfd. condenser from primary of ignition coil to ground and from relay switch on generator to ground. Ground all of the control rods going to the instrument board of the car by soldering to each rod a length of copper braid and connecting same to the motor head. Isolate the battery lead to the ignition coil by running same through a grounded shield. In some cases it may be necessary to solder a short piece of copper braid from the shaft of the tuning condenser of set to the common ground point on the chassis just below the shaft.

Tubes should be tested at regular periods and replaced if necessary in order to maintain best performance. Each tube may be checked by comparison with a new one of the same type in its place.


"B" power supply should require little or no attention. A full wave vibrator in connection with the primary of a transformer and the 6-volt storage battery furnishes the means of obtaining the proper "B" voltage. With the power turned on a slight buzz should be heard which indicates proper operation of vibrator. Failure to observe this buzz will denote a faulty condition, in which case the complete set should be subjected to a close test and inspection.


## How to Obliterate Receiver Hum

Since the question of hum arises so often in regard to simple short-wave sets, the question is whether the universal type of receiver can be free from hum. Indeed it can. It will work just as quietly as any other a-c receiver. One way to be sure of this result is to use two separate chokes, and plenty of filter capacity. In the diagram the two chokes are 30 henries each, and are not on the same core. This is a mistake some make. They read such a diagram as implying that the two windings are on the same core. If they are on the same core, there may be more hum if both windings are used than if only one is used, and also more hum if the mid-section 8 mfd. condenser is included than if it is omitted.

An audio choke load for the detector is also advisable. This may be the secondary of an old audio transformer. Some additional filtration is obtained in this way.

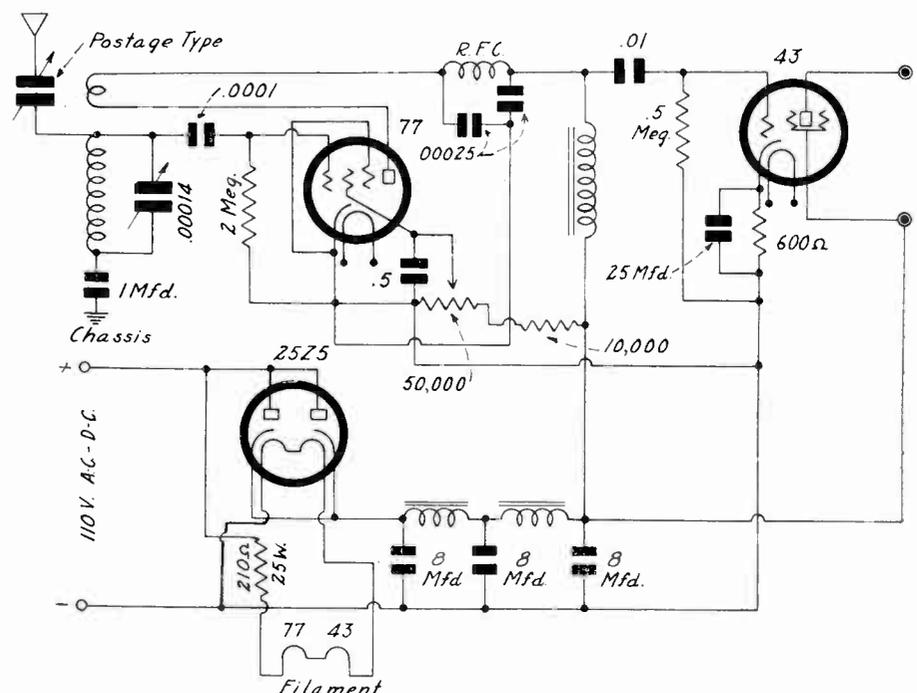
In connecting to the line care should be exercised that positive of the receiver goes to positive of the line and negative of the receiver to negative of the line, as a wrong connection might damage the first electrolytic condenser.



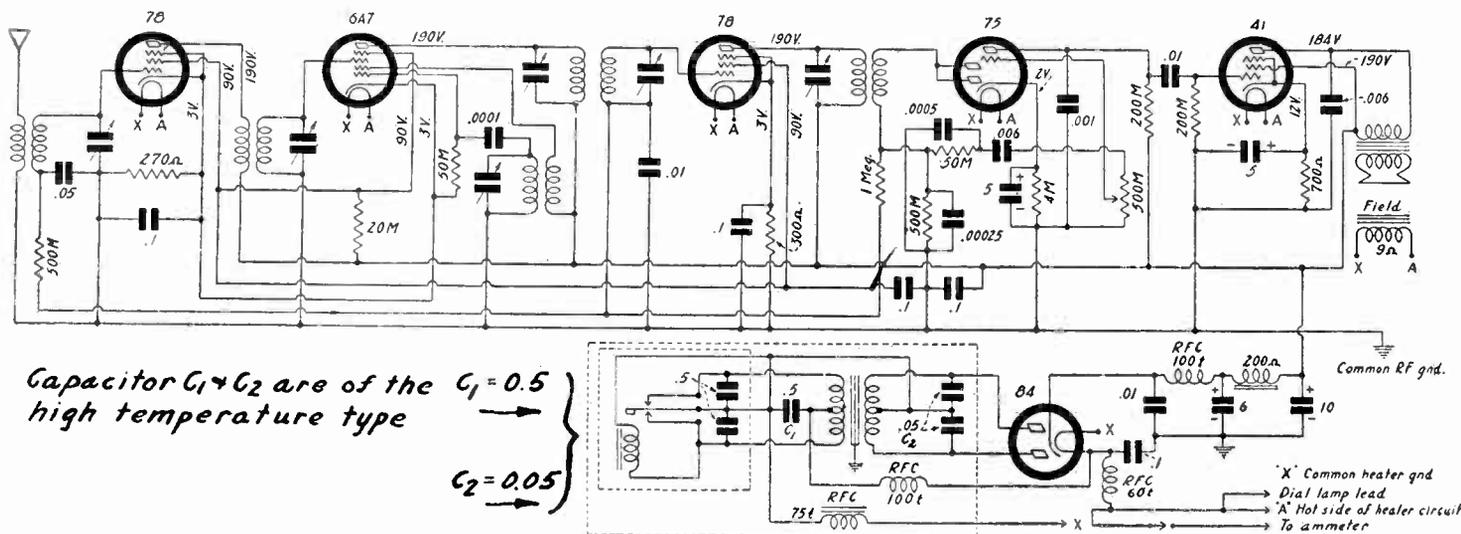

Capacitor  $C_1$  &  $C_2$  are of the  $C_1 = 0.5$  high temperature type  
 $C_2 = 0.05$

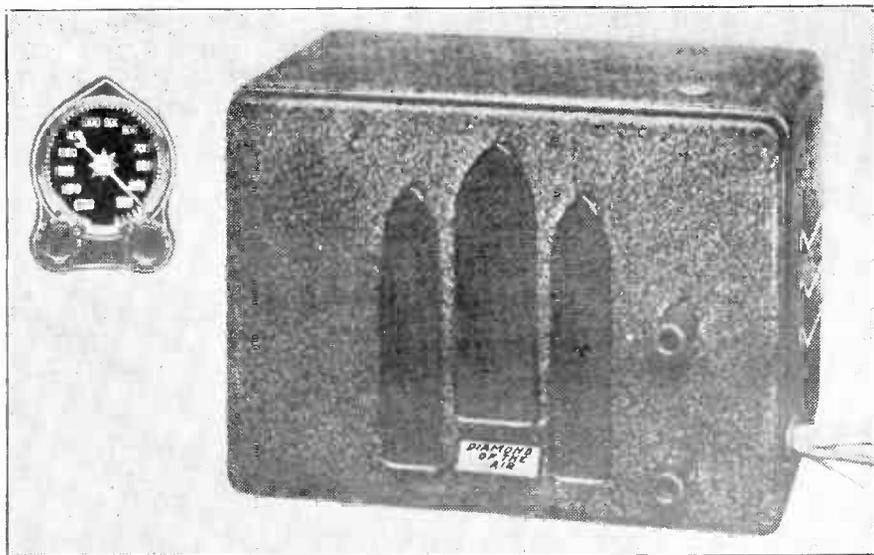The circuit diagram of the Diamond of the Air automobile receiver. At left are shown the small cabinet housing the set, and the remote tuning-volume control.



the success of this particular solution. So, after the filtration was made all that was necessary, the shielding was made even more than was absolutely necessary, and we have the actual case of shield within shield, so that there will be no interference from the opposite direction, that is, due to interaction arising from disturbances coming into the set.

**High-Temperature Condensers**

Moreover, it must be known that quite some heat develops in part of the circuit where condensers are placed, and instead of putting just the run of condensers there, high-temperature type condensers were used. These are identified as such on the diagram, two to the left of the plates of the 84, and one to the left of the primary of the transformer feeding the 84.

The circuit is a standard one. It has been found that most "highly original" circuits do not give much satisfaction, except mental satisfaction in the accomplishment of a scientific feat. The sets to build are those that are orthodox, and to which much pains has been given to make the engineering of the highest practical type. So we have here a stage of tuned-radio-frequency amplification ahead of a pentagrid converter tube, with a stage of high-gain intermediate-frequency amplification, a diode second detector, a triode driver and a 41 output tube. This is a very satisfactory pentode for car use.

# Six-Tube Auto Receiver Uses a Vibrator Unit

THE gradual increased demand for convenience and reduction of expense has made the selection of the B-batteryless type automobile receiver almost unanimous.

There are two general types of auto B eliminators: the vibrator and the converter. The vibrator makes and breaks a circuit, and due to the associated coil system, varying electro-magnetic fields are set up. The variation in the magnetic field, or spurt and collapse, constitutes a.c. Therefore the output of the vibrator's primary can be communicated to a secondary and fed to a rectifier tube, like the 84, and we can obtain a high-voltage rectified value. The d.c. output in the circuit diagrammed, which is the 6-tube Diamond of the Air car set, is 190 volts.

**R-F Waves Squelched**

Not only must the audio-frequency ripple be filtered out, but also the radio-frequency strays arising from the action of the vibrator. As is well known, the vibrator is a very effective type of B eliminator for car sets, but the filtration must be good, otherwise there would be more interference than from a motor generator, filtration values equal in both instances. Also, the strays referred to are familiar aspects of shock-excitation voltages, for the strays are of practically all frequencies. Therefore a radio-frequency choke coil is used with condensers to get rid of

this type of interference, and the result is that there is quiet and pure-tone operation, and the nuisance of the B batteries is swept aside.

Mastering the problems associated with motor generator or vibrator-unit types of B eliminators is part of the job of the car set designer, and to a considerable extent the success of the set depends on


## Franklin Transformers "Most Sock Per Dollar"

A few of the many outstanding values that can be secured at your nearest jobber or direct if he does not stock them.

**GENERAL REPLACEMENT**

|   |        |
|---|--------|
| No. 210—Pri 110 v. Sec. 300-0-300—40 M.A. 2.5 V 5.5 Amp. 5 V 2 Amp. ....  | \$1.11 |
| No. 209—Pri 110 v. Sec. 330-0-330—60 M.A. 2.5 V 8.75 Amp. 5 V 3 Amp. .... | 1.80   |
| No. 1103—Single plate to P.P. grids. ....                                 | .98    |

Net Dealers Price

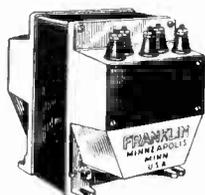

**SOUND**

|  |      |
|--|------|
| No. 521-B—Double button mike to grid. ....                     | 1.32 |
| No. 802—P.P. 45 plates to 8-15 ohms. ....                      | .95  |
| No. 6131—Pri. for D.B. mike, 500 ohm line and tube plate. .... | 3.30 |

**AMATEUR**

A very complete line by Mr. Boyd Phelps. Illustration shows one type.

**WRITE FOR CATALOGUES**

(No. 70 contains a large number of up-to-date amplifier circuits.)  
 No. 51—General Replacement No. 70—Sound No. 52-C—Amateur


**FRANKLIN TRANSFORMER MFG. CO.**

607-609 22nd Avenue, N. E., Minneapolis, Minn.
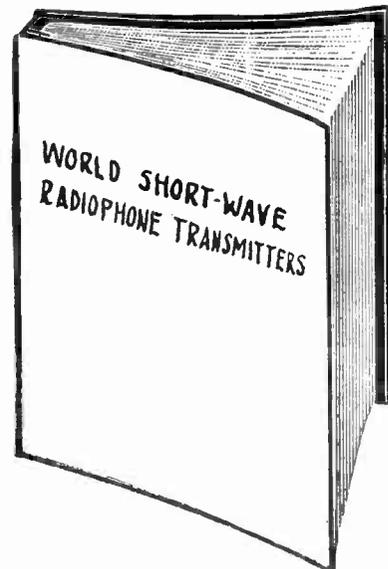
# YOU MUST HAVE— the World's Outstanding Short-Wave Station List and Time-Zone Map-Chart

INTO ninety-six pages, 8 x 10¼ inches, has been put the very information that all short-wave enthusiasts have been awaiting—all the radio phone short-wave transmitters of the world, listed by frequencies, with equivalent wavelength given in every instance, the call letters, the location, and in many instances also the time schedule being given. So complete and accurate a compilation has never before been published. The compilation was made from official publications of the Bureau de l'Union Internationale des Telecommunications, the British Broadcasting Corporation and the U. S. Federal Communications Commission, as well as from unofficial sources of information. There are MORE THAN 2,400 LISTINGS made by the U. S. Department of Commerce.

Nowhere—never—has there been such a massing of the most vital information that radioists want. And remember, this is the most complete work of its kind available anywhere! The list is as comprehensive as human care and ingenuity could make it!



## See What's in This Most Valuable Radio Book!

### THE CONTENTS:

**Station Identification:** List of the most popular short-wave program stations of the world that use characteristic "air signatures," so you can identify the stations by their "signatures."

**Foreign Alphabetic Pronunciation:** How the letters of the alphabet and numbers 1 to 50 are pronounced in English, French, Spanish, German and Portuguese. Familiarity with these pronunciations aids in station identification, that is, knowing what call letters are being announced, or what frequency or wavelength is mentioned.

**Short-Wave Broadcasting and Police Radio Stations by Countries:** The calls, location and frequencies are given for the whole world. This is a geographical classification and expedites station-finding and identification. It repeats, geographically classified, data found in the main grouping of the 2,400 stations by frequencies.

**Distances to Foreign Cities:** A textual explanation of how to determine how far any one city on earth is from some other city. A Department of Commerce map gives direction of shortest distances (measured on great circle). This map is right in the book. Besides, there is a table of distances between key cities of the United States for guiding determinations of world distances, as well as a table of world distances for principal cities.

**Short-Wave Radiophone Stations by Frequencies:** This is the comprehensive, never-before-available list of the 2,400 or more stations, including all the program stations on earth that send on short waves, using phone (speech and music) but not including amateurs. A treat unparalleled in radio history—the most accurate list of its kind man has ever produced! Both frequencies and wavelengths.

**Time Zone Chart:** This insert (stitched right in the book) is a black and white reproduction of a colored chart issued by the Hydrographic Office, Navy Department.

## Amazing Offer—Greatest We've Ever Made!

Let's get this pound-and-a-half of vital, comprehensive, authentic and valuable information in the mails to you right away!

Send only \$1.00 for an 8 weeks' subscription for RADIO WORLD, 8 issues, one each week (regular rate), and you will receive postpaid the great volume, "World Short-Wave Radiophone Transmitters," with the reduced time map stitched in.

**ACT NOW! SEND THAT DOLLAR**

**GET THAT GREAT 96-PAGE BOOK AND THAT TIME-CHART MAP**


**Never Miss an Issue! That's How to Keep Posted on Radio!**

RADIO WORLD is a weekly technical radio magazine, in its thirteenth year, one of the oldest radio magazines on earth. It prints intimate details on latest circuits, tubes, test equipment, trouble-shooting, servicing, merchandising and has a weekly "column" about program stars and station personnel. Latest news of all branches of radio is published, including corrections and amendments of station lists, all waves. RADIO WORLD is the all-wave radio authority. RADIO WORLD is on sale at news-stands, 15c per copy.

**RADIO WORLD, 145 West 45th Street, New York, N. Y.**

[Owing to unprecedented demand promptness in filling orders depends on the ability of the government to handle the vast orders.]

# DIAMOND OF THE AIR DUAL-WAVE SUPERS

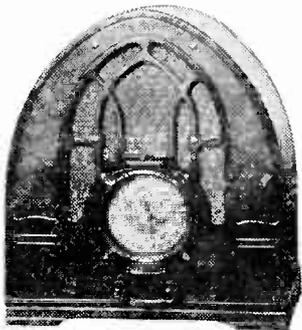

The 1010 chassis in a Gothic model table cabinet; wired, with dynamic speaker; five RCA tubes. Cat. 1010-G. \$17.51

THE principal foreign short-wave stations are on waves between 18 and 55 meters. Therefore we have a five-tube a-c superheterodyne for covering the broadcast band (550-1,500 kc) and the principal short-wave bands, a dual-wave receiver of excellent performance. Band selection by front-panel switching.

This is our Model 1010, obtainable as a wired chassis, with speaker and five RCA tubes; or in either of two table model cabinets, or in a console. The same receiver is used in all four instances.

The tubes used are one 6A7, one 6D6, one 75, one 42 and one 80. The illuminated airplane dial has a double pointer and is calibrated in kilocycles. Automatic volume control is included. There is provision for phonograph pickup connection or earphones. A tone control and manual volume control are provided. A dynamic speaker is used. The primary power rating is 60 watts.

Principal foreign stations are brought in with simple ease and remarkable clarity. The Gothic cabinet illustrated above, with wired set, speaker, complete with tubes, is Cat. 1010-G. Cabinet is 19 inches wide, 14 1/2 inches high, 7 inches front to back. Shipping weight, 17 1/2 lbs. **\$17.51**


The same receiver in the de luxe model table cabinet, illustrated below, Cat. 1010-DL. **\$18.65**

The same receiver in modernistic console. Shipping weight, 45 lbs. Cat. 1010-CON **\$27.25**

Wired chassis, tubes, dynamic speaker, Cat. 1010-CH **\$15.38**

Above models are for 50-60 cycles, 110 volts. Models for 25 cycles, \$1.50 extra, net. Add the number 25 to the catalogue number. Or, for 50-60 cycles, 220 volts, add 60 cents net, and add the number 220 to the catalogue number. Battery Model. We can supply the 1010 model in the same cabinets, at the same price as for a.c., but for battery operation. The prices do not include batteries. Add the letter B after the catalogue numbers.

World-wide reception is enjoyed on the 1935 Series Diamond of the Air Receivers. The series, besides the 5-tube models listed above, also includes an 8-tube all-wave model, 150 kc to 22 mae, using the 1008 Chassis, obtainable in modernistic table model cabinet or in console, and a six-tube, high-gain automobile set in a single unit, with remote tuning-volume control. Send for circular on 8-tube models and on auto set.

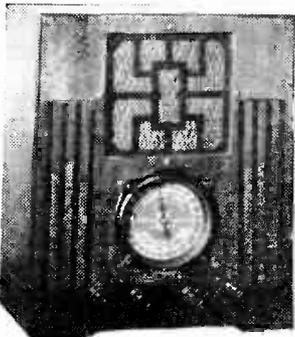



The 1010 chassis in a modernistic, de luxe table model cabinet, complete with dynamic speaker and five RCA tubes. Cat. 1010-DL. \$18.65

Remit with order to benefit by the low prices quoted. State what carrier you prefer or shipment will go by express. You pay transportation. C.O.D. orders accepted on basis of 25% remittance with order, but net prices are 2% higher than those quoted.


**Guaranty Radio Goods Co.**  
145 W. 45th St. New York City
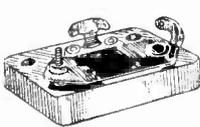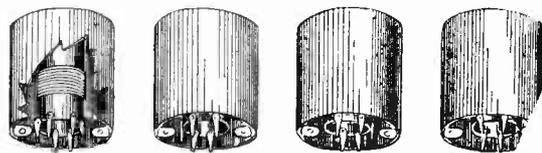
## DUAL-BAND TUNING UNIT

FOR broadcast reception, plus coverage to higher than 4,000 kc, thus yielding a total span of 540 to higher than 4,000 kc. We have an exceptionally precise combination, consisting of three r-f coils, one of which is used as antenna coupler, and one oscillator coil, also the necessary four-gang condenser and the correct padding condenser (Hammarlund adjustable type). The tuning coils for the r-f level have secondaries tapped so that the condenser stator may be switched from full inductance to just enough inductance to pick up the broadcast band where the full inductance left off. The oscillator coil is appropriately tapped, also, for this purpose. A four-pole, double-throw switch would be required (not furnished). Coils aluminum shielded, 2-1/16" outside shield diameter by 2.5 inches high.




The four-gang condenser is very compact (5 x 2.25 x 2.75 inches). All material is specially made for this premium offer and is of highest calibre. Order Cat. PR-BCTU-465 for use with 485 kc intermediate, and enclose \$9 for 18-month subscription (78 issues, one each week), and four-gang condenser, four coils, and 350-450 mmfd. padding condenser, but no switch, will be sent. Small transportation charges collect.

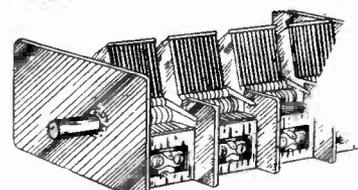

Same as above, same terms, except oscillator is for 175 kc and padder is 850-1,350 mmfd. Order PR-BCTU-175.

## TUNING UNIT FOR TEST OSCILLATOR

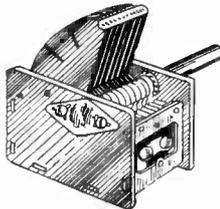

HERE is your very first opportunity to get the parts for constructing a universal, modulated test oscillator to cover fundamentals from 135 to 389 kc, and read higher intermediate frequencies and the entire broadcast band, by harmonics, all imprinted right on the dial. That is, the oscillator will be direct frequency-reading. The parts consist of one metal-etched scale, one metal enclosure, one 0.000406 tuning condenser with trimmer built in, one oscillation transformer (secondary inductance accurate to 0.1 per cent.), and one knob for condenser. Circuit diagram by one of America's premier precision radio parts manufacturers. Quantity at left.

supplied for universal model modulated test oscillator (80-120 volts a.c., d.c. or batteries, same oscillator works on all three). Instruction sheet for lining up at broadcast and intermediate frequencies included. Line up the oscillator with one adjustment on broadcast band, beating with some station on 1,200 to 1,400 kc. Whole dial then will track. Order PRE-TUTO and send \$6.00 for one-year subscription for (52 issues). Sent postage prepaid.

## MICA-DIELECTRIC Intermediate Transformers

For 465 kc or 175 kc i.f. we offer doubly-tuned transformers, with mica-dielectric condensers built in, all enclosed in 4-inch high aluminum shield, 2-1/16-inch diameter. Quantity is at left. Sent postpaid.

### Single Transformer

- (1) PRE-MD-465... \$2.00 subscription, 16 issues
- (2) PRE-MD-175... \$4.00 subscription, 34 issues
- (3) PRE-MDD-465... \$6.00 subscription, 52 issues
- (4) PRE-MDD-175... \$6.00 subscription, 52 issues

## Complete Selection of Tubes



The following highest-grade, licensed, brand-new, 10-day-replacement-guarantee tubes are offered as premiums.

One Tube for \$1.00 Subscription, 8 Issues.  
01A, 01AA, 1V, 12Z3, 112A, 24A, 26, 27, 30, 31, 35, 36, 37, 38, 39, 45, 47, 51, 56, 71A, 80, 82.

Any two of above tubes for \$2.00 Subscription (16 Issues), any three for \$3.00 Subscription (26 Issues), any six for one-year Subscription (52 Issues).

## AIR-DIELECTRIC Intermediate Transformers

For unequalled maintenance of the frequency to which the intermediate channel is adjusted, air-dielectric tuning condensers must be provided. These are supplied on Isolantite forms, and are made by one of America's premier precision radio parts manufacturers. Quantity at left.

- (1) PRE-AD-465... \$6.00 subscription, 52 issues
- (2) PRE-AD-175... \$12.00 subscription, 104 issues
- (3) PRE-ADD-465... \$18.00 subscription, 156 issues
- (4) PRE-ADD-175... \$18.00 subscription, 156 issues

One Tube for \$1.50 Subscription, 13 Issues.  
1A6, 5Z3, 2A5, 2A6, 2A7, 2B7, 6A4, 6A7, 6B7, 6F7, 25Z5, 22, 32, 33, 34, 41, 42, 44, 46, 49, 53, 55, 57, 58, 59, 67, 75, 77, 78, 83, 83V, 84, (8Z4), 85, 89, 483, 485.  
Any two of the \$1.50 group for \$3.00 Subscription (26 Issues), any four for \$6.00 Subscription (52 Issues).

TUBES SENT POSTAGE COLLECT.

## VITAL BOOK

The biggest help any one can get who desires to wind radio-frequency coils for any frequency from just below the audio range to the fringe of ultra frequencies is to have a book that tells just what inductance is required for the condenser one possesses, and just how many turns of any kind of wire on any sensible diameter are needed to produce that inductance. "The Inductance Authority," by Edward M. Shiepe, gives you just that information, to an accuracy of 0.1 per cent. Send \$4.00 for an eight-months subscription (39 issues) and order PRE-IA sent postpaid.

**POWER TRANSFORMER**  
Primary—105-130 volts.  
Secondary A—2.5 volts, center-tapped.  
Secondary B—110 volts, no center tap.

Splendid for powering a-c test oscillator or any other rectifier for not more than three small tubes.

Order PRE-SPTR and send \$1.50 for three-month subscription (13 weeks) postpaid.

**RADIO WORLD, 145 WEST 45th STREET, NEW YORK, N. Y.**

## SOME EXCELLENT RADIO BOOKS

- "This Thing Called Broadcasting" by Alfred N. Goldsmith and Austin C. Lescarbourea, \$3.50
- "Audio Power Amplifiers," Anderson, Bernard 1.50
- "Radio Frequency Measurements," by E. B. Moullin 12.50
- "Short Waves," by Charles R. Leuts and Robert B. Gable 3.00
- "Perpetual Trouble Shooter's Manual," No. 1, by Rider 7.50
- "Perpetual Trouble Shooter's Manual," No. 2, by Rider \$6.50
- "115 Latest Commercial Set Diagrams," by Rider 1.00
- "Drake's Radio Cyclopaedia," by Manly 6.00
- "Elements of Radio Communication," by Morecroft 6.00

RADIO WORLD, 145 West 45th Street, New York, N. Y.

## Generator with Amplifier Stage

### Shipment Absolutely Guaranteed!

Frequencies are commonly given only their wavelength equivalents, and for true likewise. So a Signal Generator, that enables determinations in both is the thing. That service is what the new Bernard Signal Generator Model

of general purpose of lining up superheterodynes at intermediate, broadcast and peaking tuned-radio-frequency sets, it may be used as an all-wave Station-Finder, and Dual Measurement and Combination Use make this Signal Generator most valuable. Fundamental frequencies and wavelengths are direct-reading. There are no charts to strain the dial is accurately calibrated and the Signal Generator accurately adjusted. These fundamentals are 99.9 kc. (1 kc. separation); 140 to 500 kc. (5 kc. separation); 540 to 1,600 kc. (10 kc. separation); 1,400 to 5,000 kc. (20 to 50 kc. separation); 3,010 to 3,600 meters (25 and 50 meter separation). The bands are selected by turning a front-panel switch. There are four switch stops. The low-frequency band and the wavelength band cover the same range, the same stop being used, though there are two scales for this band, wavelength and frequency.

Any frequencies or wavelengths as listed above are present as fundamentals and are read directly. A new method, simple to apply, enables measurements from 4,500 kc. to 99.1 mc., also wavelengths from 3,010 meters to 0.1 meter. The extension of the fundamental ranges is accomplished by a startling method that opens up new possibilities of extensive and accurate measurements.


Model 333-A Signal Generator, for 90-120 volts a.c., d.c. or batteries; designed by Herman Bernard, accurately calibrated and adjusted, for all-wave service, 83 kc. to 99.1 mc., 3,600 meters to 0.1 meter; equipped with output attenuator, on-off switch, modulation switch for d.c. and battery use, Chromium-plated control and band-index scales, positive-contact, low-resistance band-selector switch, a.c. cable and plug, black wrinkle-finish shield cabinet, 34 and 30 tubes, neon tube, and instruction sheet included. Ready for immediate use.

Model 333-A (shipping weight, 7 lbs.)  
List Price .....\$49.60

**NET PRICE \$19.95**

Model 333-AK. Instructions (less tubes), complete kit; list price, \$32.00.  
Net price .....\$16.00

## THREE TUBES!

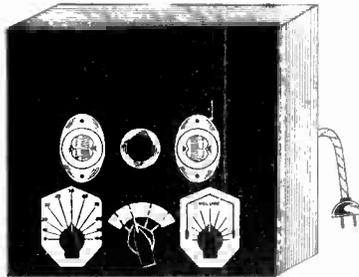

### DIRECT RADIO CO.

145 West 45th Street, New York, N. Y.

## SHORT-WAVE AND PUBLIC ADDRESS MANUAL

**FREE**

192 pages, 400 illustrations, costing \$4,000 to produce. And yet a copy of this manual will be sent to you free if you send \$1.00 for an 8-weeks subscription for RADIO WORLD. Existing subscribers may extend their subscriptions under this offer.

Bound in cardinal red leatherette, this manual includes articles on the construction of short-wave receivers from one to nine tubes, inclusive, and all values between, supers and t-r-f, with the clearest imaginable illustrations both photographic and draughting. Besides the usual plain circuit diagram there is a pictorial diagram for each circuit. And all the photographs are brilliantly lighting and informative. Portable short-wave sets, design and winding of coils for short waves and broadcasts (intimately illustrated), list of short-wave stations with meters and kilocycles and hours on the air; trouble-shooting, and forty other topics, all done well.

The public address section contains data on different systems, how to use them, and offers opportunities to turn public address work to profit. Besides, there are articles on testing and servicing not encompassed by the title of the manual—signal generators, broadcast home and portable sets, analyzers, formulas, capacity data. Everything plainly told, simple language, from microphones to speakers.

Send \$1.00 now and get RADIO WORLD for 8 weeks and the manual free. Ask for Cat. PR-SPAM.  
RADIO WORLD, 145 W. 45th St., New York, N. Y.

## SUBSCRIBE NOW!

YOU CAN GET TWO FULL YEARS—  
104 ISSUES—ONE EACH WEEK—FOR \$10.00

RADIO WORLD, 145 West 45th St., New York City. Enclosed please find my remittance for subscription for RADIO WORLD, one copy each week for specified period.

- \$10.00 for two years, 104 issues.
- \$6 for one year, 52 issues.
- \$3 for six months, 26 issues.
- \$1.50 for three months, 13 issues.  
\$1.00 extra per year for foreign postage.
- This is a renewal of an existing mail subscription (Check off if true)

Your name .....

Address .....

City .....

## John F. Rider's Vol. IV Perpetual Trouble Shooter

**S**ERVICING during 1934 will be more complicated than at any time during the past 14 years of radio activity. Volume IV is your means of combating the numerous highly scientific problems of design introduced by the receivers sold during 1933.

"I do not hesitate to say that Volume IV is the most important of all the manuals I have issued. Volumes I, II and III found their place in the servicing world as important aids to the service man . . ."

"Volume IV is destined to be more than just an important aid. . . It will be a vital necessity. . . I am firm in the belief that because the contents of Volume IV cover the most scientific and complicated radio receivers ever produced in the history of the radio industry—its ownership will mean the difference between success and failure when servicing the 1933 crop of radio receivers. John F. Rider."

Volume IV has in it 1040 pages in the loose leaf binder; about 20 pages in a separate supplement and the index, covering all of the manuals, totals about 40 pages, making a grand total of approximately 1100 pages.

The binder used in Volume IV is identical to that employed for Volume III. It is loose leaf employing the finest of materials. Aligner bar "instant removal" mechanism is employed.

Volume IV, Price \$7.50, postpaid

|  |        |
|--|--------|
| Also:  |        |
| Volume I, Rider's Perpetual Trouble Shooters Manual                  | \$7.50 |
| Volume II—Does not duplicate Vol. I                                  | 6.50   |
| Volume III   | 7.50   |
| Rider's Combination "3 in 1" Manual, now ready (Vols. I, II and III) | 21.50  |
| Rider's Combination "3 in 1" Manual, with carrying handles           | 25.00  |

Address: BOOK DEPT.

### RADIO WORLD

145 W. 45th St., New York, N. Y.

## 115 DIAGRAMS FREE

115 Circuit Diagrams of Commercial Receivers and Power Supplies supplementing the diagrams in John F. Rider's "Trouble Shooter's Manual." These schematic diagrams of factory-made receivers, giving the manufacturer's name and model number on each diagram, include the MOST IMPORTANT SCREEN GRID REVERSERS.

The 115 diagrams, each in black and white, on sheets 8 1/2 x 11 inches, punched with three standard holes for loose-leaf binding, constitute a supplement that must be obtained by all possessors of "Trouble Shooter's Manual" to make the manual complete.

Circuits include Bosch 54 D. C. screen grid; Balkite Model F. Crosley 30, 31, 33 screen grid; Eveready series 18 screen grid; Wria 194 A.C. screen grid; Pearless Electrostatic series; Philco 76 screen grid.

Subscribe for Radio World for 3 months at the regular subscription rate of \$1.50, and have these diagrams delivered to you FREE!

Radio World, 145 West 45th St., New York, N. Y.



### Dial-Calibrated

## OSCILLATORS

1% Accuracy. Grid Stabilization.  
WORK ON AC OR DC  
Designed by Edward M. Shiepe

**MODEL 37-S.** Neon tube supplies modulation to 37-tube oscillator. Scale direct reading in kilocycles. Fundamental range 135-380 kc. 60-cycle modulation on AC and neon tube modulation on DC. Dial also calibrated in 4th harmonic for broadcast band, 540-1500 kc. Complete with both tubes in black cracked steel cabinet for only .....  
Shipping wt. 3 lbs. **\$9.50**

**MODEL 37-D.** Dual Range. Two oscillators in one. One range 132-380 kc. Switch changes to 530-1500 kc. all fundamental frequencies. Larger than Model 37-S. Neon tube modulator. Engraved bakelite panel on black cracked steel cabinet. Complete with two tubes and ready to operate for only .....  
Shipping Wt. 4 lbs. **\$14.50**

### COIL BOOK

New book by Edward M. Shiepe, B.S., M.E.E., gives number of turns for any inductance on a series of 48 accurate charts for any single-layer coil from 1/2" to 3" diameter. All insulations covered in charts. Complete with large chart supplement relating inductance, capacity and frequency.....  
Shipping wt. 1 lb. **\$2.00**

All Orders Filled Immediately  
or Money Refunded

## DIRECT RADIO CO.

145 West 45th Street New York, N. Y.

## BATTERY-OPERATED Signal Generator Free!



High  
Stability;  
Accuracy  
1%

**H**ERE IS THE HOT NEWS of our exclusive battery-operated Signal Generator, designed by Herman Bernard, and using his frequency-calibrated scale for fundamentals of 135 to 380 kc. with all popular intermediate frequencies inscribed right on the dial, and with calibration, also directly on the dial, for the broadcast band. Thus coverage from 135 to 1,520 kc is read. Higher frequencies, almost without limit, also can be measured without confusion. And the price is the world's lowest for such an instrument.

## NO CHARTS! SCALE IS DIRECTLY READ IN FREQUENCIES

This laboratory - tested Bernard precision instrument, Model 336, uses a 34 r-f oscillator in a stabilized circuit, has attenuator that contributes NO DISTORTING, and has optional modulated - unmodulated service by switching. The audio oscillator is a 30. Electron coupling is used between a.f. and r.f. and also between output and measured circuit. Accuracy is 1 per cent.

Model 336 is in a wrinkle-finish black shield cabinet, 9" wide, 6" high, 5" front to back, weight 7 1/2 lbs. complete. It has bar-handle control of volume and modulation. It is useful for lining up superheterodyne i-f channels, also the r-f channels of any receivers, and can be used satisfactorily for peaking on short waves as well. Instruction sheet supplied. Order Cat. 336, wired, complete with 22.5v. B battery, 4.5v. A battery, and two tubes, ready to operate.

Send \$12. for a 2-year subscription for Radio World (104 issues, one each week), and order Cat. 336 sent as a premium. Add postage to remittance or you pay expressage. (Shipping weight, 8 lbs.)

### RADIO WORLD

145 West 45th Street New York City