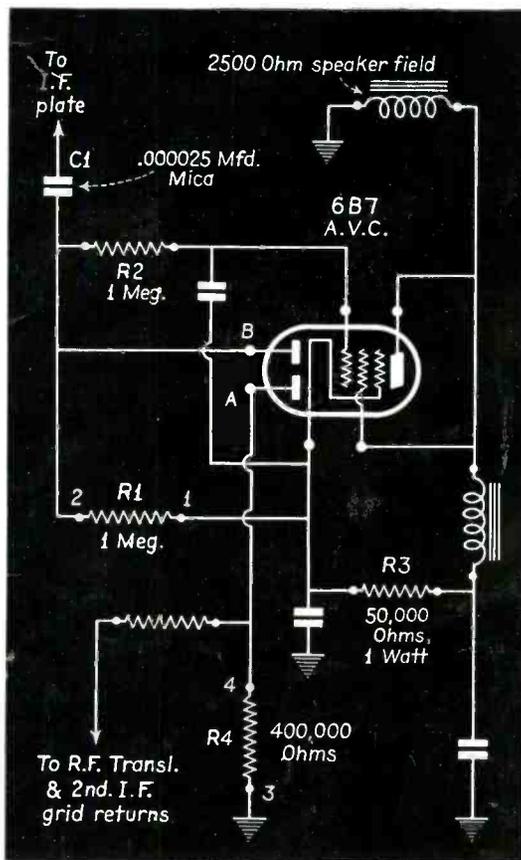




SERVICE

A MONTHLY DIGEST OF RADIO AND ALLIED MAINTENANCE



Novel 6B7 AVC Circuit

(See page 183)

PER COPY
25 CENTS

MAY
1934

ELECTRAD

Serves Service Men


THE biggest factor in the performance of a radio set, after it leaves the retailer, is SERVICE. The service man, therefore, is one of the most important links in the chain of customer satisfaction, extending from the manufacturer to the final purchaser.

That is why ELECTRAD serves the service man with helpful ideas and replacement parts which save his time, labor and money, and which reflect credit on his skill and knowledge.

If you haven't an ELECTRAD Catalog handy for consultation, mail coupon for a FREE copy.

Here's a 10-Watt That Stands Up

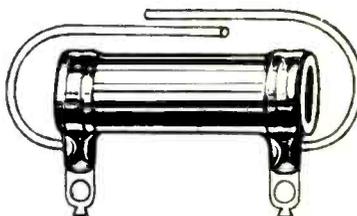Stop guessing about resistors! This ELECTRAD 10-Watt is compact, wire-wound and vitreous-enameled. It is non-porous and moisture-proof. It has positive electrical contacts and non-corrosive Monel metal contact bands and lugs. Its resistance is stable. And it comes in 41 values at only 35c each, list. Also in larger sizes and ratings.



TRUVOLTS

Have a Safety Factor
of 1,000 VOLTS


And in addition, these exclusive features: (1) Patented design permits larger wire and open-air cooling. (2) Double-spiral winding insures perfect electrical contacts. (3) Sliding clips provide exact adjustments. (4) Full-length fibre protective guard. All Standard Sizes.



RESISTOR
SPECIALISTS
Since the
Birth of Radio

Two-Purpose Volume Controls

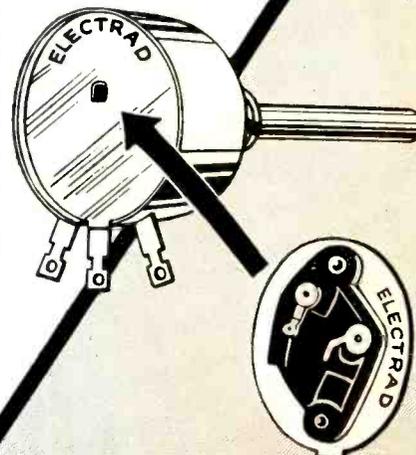A standard volume control, or combined with power-switch. Just snap out the plain end cover and snap in the switch assembly. All done in a moment without disconnecting wiring. A great time and labor saver in replacement work. Only five types in the service kit will fit 799 standard receiver models. Long ALUMINUM shafts easily cut to desired length.



FREE
Vest-Pocket
Volume Control
GUIDE

175 Varick St., New York, N.Y.
ELECTRAD
INC.



ELECTRAD, INC., Dept. S-5
175 Varick St., New York

... Check here for FREE General Catalog.


... Check here for FREE Vest-Pocket Volume Control Guide.

Name

Address

SAY YOU SAW IT IN SERVICE

for Auto Radios

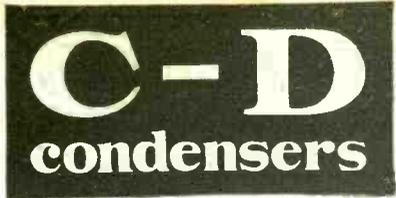

—Meeting EVERY REQUIREMENT

PAPER • MICA • OIL • ELECTROLYTIC



Type DT, DWARF TIGER condensers. Small sized, finely constructed tubular units. Electrical characteristics far outshine the many nondescript types on market.



Type 3W. MICA condensers. Very small, bakelite-cased units fitting in tight places. Work efficiently and effectively. Cost so little in comparison to their intrinsic value.



Type IC-4050 GENERAL UTILITY condensers. The unit that will eliminate generator interference noises. A .5 mfd. 400-volt condenser that "can take it" and stand up under all conditions. Your BEST bet!



Type ED ELECTROLYTIC condensers. Cartridge or tubular units that fit into the picture of things and serve their long useful purpose to good advantage. Complete range of capacities and voltages.



Type XB VIBRATOR condensers. All sizes and shapes to meet the varied requirements of "B" supply units used on auto sets. One shown is popular item—at a popular price.

Noise elimination on auto-set installations is a most important item which confronts the service man with increasing regularity at this time. Perplexing problems are easily solved only by a careful analysis of the many and varied factors which have to be considered. Most important of all is the proper selection of condensers required in different circuits. You WILL get markedly better results by using CORNELL-DUBILIER throughout.

Take for instance our special XB units. These are available in .01, .015, .02 and .03 mfd. capacities with a safe rated working voltage of 1000 w. v. (3500 max. surge V.) in both cardboard and metal containers. Made small and compact. Reliable. Easily "stand the gaff" on any make vibrator. Ask your supplier about them.

—and for All-Wave Radios

Type JHM, the "300" line Junior "HANDY-MIKE" condensers. Beautifully made. Mounted in tiny silver-coated cardboard containers. No mistaking polarity of leads. Ideal for all circuits requiring maximum working voltage condenser of 250 V.D.C., 300 V. Peak. Available in 4, 8, 10 and 12 mfd. units.

Type RHM, the "525" line Regular or General Utility "HANDY-MIKE" units. Small, silver-finished rectangular containers. Equipped with colored wire leads that stay put. Unit can be used where a minimum of space is available and where a dependable condenser will stand up at 450 V.D.C., 525 V. Peak. Sizes in 1, 2, 4 and 8 mfd.

Type HM, the "600" line "HANDY MIKE" condenser. The condenser that's got 'em all beat! Working voltage 475 V.D.C., 600 V. Peak. For those sets that have a tendency to kick up a high surge or transient voltage before filaments get good and hot, these condensers will hold more than their own. In 1, 2, 4 and 8 mfd.

"300"

"525"

"600"

"HANDY-MIKE" UNITS

There are many makes of electrolytic condensers. And there are many degrees of excellence. Cornell-Dubilier electrolytics are time-proven—they are accepted as standard by manufacturers of radio and precision equipment. WHY?—Not just because—BUT, only as the experience gained through a quarter of a century of quality condenser manufacture can give us.

You, Mr. Service Man, will save money and do a better job by using

CORNELL-DUBILIER CONDENSERS

THE MOST COMPLETE CONDENSER LINE

Ask Your Supplier for Them!

CORNELL-DUBILIER CORPORATION

Jobbers' Division

4375 BRONX BOULEVARD

NEW YORK CITY



SERVICE

A Monthly Digest of Radio and Allied Maintenance

MAY, 1934
Vol. 3, No. 5

EDITOR
M. L. Muhleman

ASSOCIATE EDITOR
Ray D. Rettenmeyer

EDITORIAL CONTENTS

FEATURES

Community Aerials	173
New All-Wave Aerial.....	176
Novel 6B7 AVC Circuit.....	183
"Public-Address" for the Service Man By Frank Lester.....	189
Service-Man's Notebook	187
The S. W. Converter Market By Ellis Cohen.....	182
Wurlitzer Model SA-133.....	178

ANTENNA (Sales and Service).....	170
----------------------------------	-----

ASSOCIATION NEWS.....	194
-----------------------	-----

AUTO RADIO

Auto-Receiver I-F Peaks.....	186
Majestic 66 Protection.....	186
Philco Model 800.....	185

CIRCUITS

Community Aerials	173
Knight Model W All-Wave.....	184
New All-Wave Aerial.....	176
Novel 6B7 AVC Circuit.....	Front Cover
Philco Model 800.....	185
Portable Storage-Battery Amplifier.....	189
Self-Powered S. W. Converter.....	182
Universal Feeder Circuit for Dynamic Speakers.....	188
Wurlitzer Model SA-133.....	178

FORUM	198
-------------	-----

GENERAL DATA

Airline No. 62-20.....	188
Knight Model W All-Wave.....	184
Novel 6B7 AVC Circuit.....	183
Peerless 65 and K-65.....	188
Philco Model 58.....	183
Sparton "A" and "AX" Receiver Models.....	184
Testing Rectifier Tubes.....	188
The S. W. Converter Market.....	182
The 1C6 Tube.....	184
Using Oscillator Harmonics.....	187
Wurlitzer Model SA-133.....	178
6C6, 6D6 and 76 Tubes.....	183

HIGHLIGHTS	190
------------------	-----

MANUFACTURERS	200-202
---------------------	---------

ON THE JOB

Airline No. 62-20 By J. M. Osenton.....	188
Peerless 65 and K-65 By S. F. Pusey.....	188
Testing Rectifier Tubes.....	188
Universal Feeder Circuits for Dynamic Speakers By Bernard Ephriam.....	188

PUBLIC ADDRESS

"Public-Address" for the Service Man By Frank Lester.....	189
Testing Rectifier Tubes.....	188
Type 42 and 2A5 Tubes.....	192

SERVICE-MAN'S NOTEBOOK (Using Oscillator Harmonics)	187
--	-----

BRYAN S. DAVIS
President

JAS. A. WALKER
Secretary

Chicago Office—919 N. Michigan Ave.—L. F. McClure, Mgr.

Cleveland Office—10515 Wilbur Ave.—J. C. Munn, Mgr.

San Francisco Office—155 Sansome St.—R. J. Birch, Mgr.

Published Monthly by the

Bryan Davis Publishing Co., Inc.
19 East 47th Street
New York City

SANFORD R. COWAN
Advertising Manager

A. B. CARLSEN
Circulation Manager


Los Angeles Office—846 S. Broadway—R. J. Birch, Mgr.

St. Louis Office—505 Star Bldg.—F. J. Wright, Mgr.

Wellington, New Zealand—Tearo Book Depot.



Melbourne, Australia—McGil's Agency.

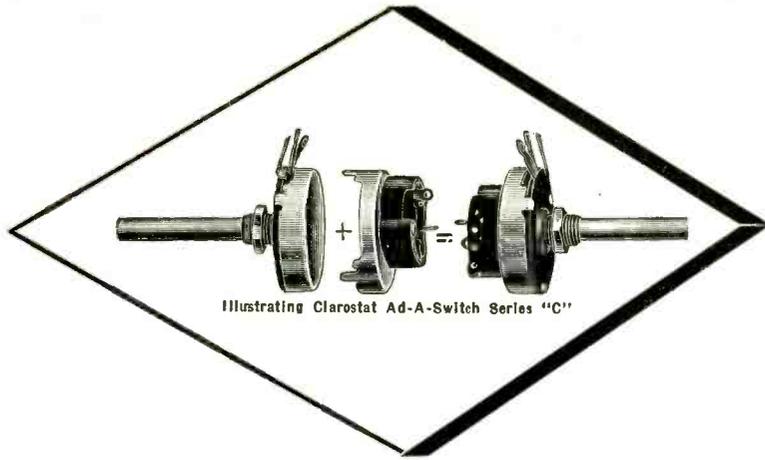Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price \$2.00 per year in the United States of America; 25 cents per copy. \$3.00 per year in Canada and foreign countries; 35 cents per copy.




The **CLAROSTAT** line of replacement controls  is the most complete

and dependable line available. 477 RECEIVERS CAN BE SERVICED WITH ONLY 4

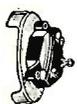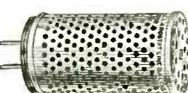CLAROSTAT CONTROLS  +  = . Line Ballasts  to limit

the line voltage fluctuation for all makes of receivers permit Servicemen to make an

additional profit \$\$\$ on every call. Tone Controls , Flexible Resistors

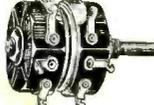 , "T" and "L" Pads  for Public Address applications, Wire Wound

Grid Resistors —all these components, manufactured to Clarostat's rigid require-

ments afford Servicemen with a single, dependable source of supply.



CLAROSTAT'S CONTROL REPLACEMENT GUIDE SENT FREE UPON REQUEST

CLAROSTAT MFG. CO., Inc.

287 North 6th Street

Brooklyn, N. Y.

"AD-A-SWITCH" was originated by Clarostat

THE ANTENNA...

SALES AND SERVICE

EVERY self-respecting Service Man who considers radio servicing a profession is justified in any attempts he may make to keep his business free and clear of rank commercialism. A Service Man is likened to a doctor, and though this simile is worn to a frazzle, it still holds good. It will continue to hold good so long as Service Men keep their business clean.

Ordinarily we would hesitate in going too deeply into this "Service Man—Doctor" likeness, but the present case seems to call for a complete understanding on the part of all just what a Service Man is, what he should and should not do, and lastly, what his future may be.

There are more obligations attached to the medical profession than there are to the profession of radio servicing. This is obvious, since a broken-down human being represents a more serious case than does a broken-down radio receiver. The doctor should provide his services free if necessary, because of the human element; a Service Man should not, because no human element is involved. The doctor should make sacrifices, the Service Man should not, for the Service Man is not a public servant.

Super-idealists have carried the likeness between doctor and Service Man too far, with the result that there are many men in the radio field who consider that their department should be identical with that of the doctor's and that, like the doctor, their professional pride should prevent them from selling anything beyond their normal services.

It is quite true that the average doctor does not sell medicines, crutches, artificial legs, etc. He sends his patients to the proper men who do sell these items. Even so, a doctor may often accept some form of commission on the sale of medicines and equipment, though this is not the general rule and is frowned upon by the profession. The point is, most doctors do not have to commercialize themselves in such a manner in order to produce a living income. There is enough money in doctoring alone without a medico seeking added sources of revenue.

It should—and does—cost more to service a human being than to service a radio receiver. Since a Service Man is not a public servant in the manner that a doctor is, he should look to "commercialism" for some of his profits. It is natural that he should, yet there are so many men who feel that anything dealing with merchandising is not to be considered equal in any respect to the business of servicing. This attitude is in many cases due to overzealous manufacturers and dealers who have seen in the Service Man the "perfect merchandising outlet." This has resulted in some warped viewpoints.

What a few of these men may fail to realize is that a perfect service is not rendered the customer unless an honest endeavor is made to provide everything required. As an example, if a customer makes inquiry

regarding tone quality over and above that which his set is capable of producing, or indicates a healthy interest in short-wave reception, it is more or less the duty of the Service Man not only to inform the customer what can or cannot be done but also to sell and install the equipment. This is his duty for the reason that there are still a goodly number of radio stores of one sort or another that will sell anything irrespective of its worth or its adaptability to the case. In some cases, such sales are purely dishonest; in other instances they are made because of the stupidity of salesmen who have no technical understanding of radio.

If you will stop to think things over, you will realize that doctors are up against much the same proposition. It is the duty of the doctor to prevent medical quacks from selling their wares to an unsuspecting public. A Service Man cannot save a life by prescribing to a customer, but he can save a lot of grief and ill-feeling. Every worthless piece of apparatus sold, or every piece of apparatus improperly adapted, does harm to the entire radio industry. Why should not the Service Man function as the guardian at the sales gates?

We have long felt that the Service Man should serve the industry as well as his customers. We know that at the present time both manufacturers and broadcasters are more than usually interested in the Service Man as an individual who can contribute immeasurably to the creation of public good-will by functioning as an advisor, much in the same manner as does a doctor. The more advising the Service Men do, the better conditions will be, for all of us, and the better will be the Service Man's standing in the field.

Now, then, why try to be a doctor all the way? You have a living to make and there is no reason why you shouldn't sell all manner of merchandise when, as, and if it is wanted. If you cannot, or do not wish, to carry a line of merchandise yourself, why not make arrangements with a reliable local dealer so that you may function as his agent on a commission basis? Such an arrangement where you remain, so to speak, a "freelance," precludes any possibility of the dealer forcing you to enter into high-pressure selling. At the same time it affords a source of extra profit well worth considering.

Reliable manufacturers and dealers are not trying to make supersalesmen out of Service Men. As a matter of fact, the nearer a Service Man comes to being a typical salesman, the less opportunity he has of actually selling the customer. The Service Man's selling opportunity lies in his inherent sincerity and integrity. If you have a good reputation and you tell a customer that such-and-such a product is the best, the customer will believe you, where he will not believe a salesman.

There are thousands of Service Men who make a good thing of sound merchandising. We see no reason why all Service Men shouldn't do the same.

A NEW INSTRUMENT FOR RADIO SERVICE

THE **TOBE** CONDENSER ANALYZER


The TOBE CONDENSER ANALYZER

is a scientifically designed electrical testing instrument developed especially for quick and accurate condenser analysis in the field of radio service.

The TOBE CONDENSER ANALYZER

performs these much needed tests on all types of condensers including: electrolytic, paper dielectric, mica, and oil:

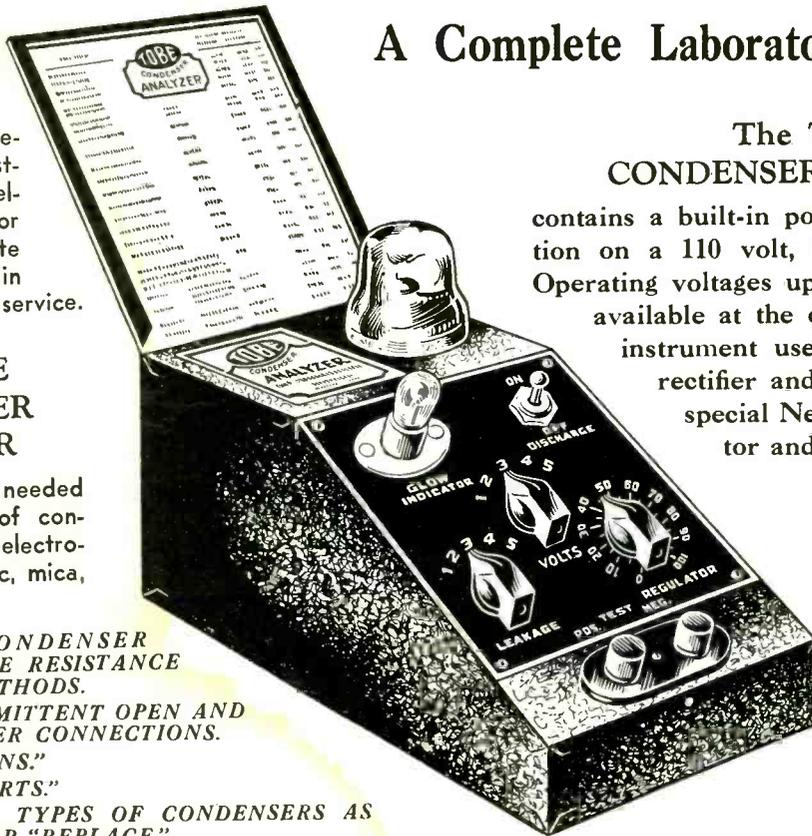1. MEASURES CONDENSER "QUALITY" BY THE RESISTANCE AND LEAKAGE METHODS.
2. DETECTS INTERMITTENT OPEN AND CLOSED CONDENSER CONNECTIONS.
3. INDICATES "OPENS."
4. INDICATES "SHORTS."
5. IDENTIFIES ALL TYPES OF CONDENSERS AS "SATISFACTORY" OR "REPLACE."



A Complete Laboratory Instrument

The TOBE CONDENSER ANALYZER

contains a built-in power supply for operation on a 110 volt, 60 cycle A.C. supply. Operating voltages up to 700 volts D.C. are available at the output terminals. The instrument uses one 01-A tube as a rectifier and is equipped with one special Neon Glow Tube Indicator and 6 ft. of cord and plug.

The TOBE CONDENSER ANALYZER

is enclosed in a heavy metal case finished in attractive black Damaskene wrinkle. Size of case only 3 3/4" x 4 1/2" x 7 1/2".

● AMAZINGLY LOW PRICED ●

Dealers' net price of the TOBE CONDENSER ANALYZER complete with operating instructions and valuable information on condenser testing, less 01-A tube, only **\$11.40**
Price \$11.70 in Denver and the West Coast.

The Tobe Deutschmann Corporation being principally a manufacturer of replacement condensers has developed this product as an aid to the solution of condenser problems encountered in radio service, and for its indirect value in the merchandising of TOBE condensers. For this reason the instrument is being offered at an unusually low figure.

USE THIS COUPON—ORDER TODAY
TOBE DEUTSCHMANN CORPORATION
CANTON—MASS.

TOBE DEUTSCHMANN CORPORATION
Canton, Massachusetts

Gentlemen:

Enclosed find check money order for \$11.40 plus for postage. (Shipping weight of instrument 6 lbs.) Kindly send me one TOBE CONDENSER ANALYZER complete with operating instructions.

NAME

STREET

CITY STATE

My parts jobber is

Address

MISTER!
 YOU JUST CAN'T
 AFFORD TO
 MISS A WORD
 OF THIS!



Making Summer Profits With PUBLIC ADDRESS!

Ten to twenty-five dollars per day profit! It sounds pretty good, doesn't it . . . yet you can make this much easily on many days by renting P.A. units this summer. Conventions, fairs, lawn festivals, athletic events of all kinds; church, fraternal and social events . . . all can return a nice profit to you—if you are alert to the opportunity.

Here at Radio Headquarters we have every type of latest P.A. permanent or portable equipment at prices to meet every budget requirement . . . quality to satisfy the most discriminate. Amplifiers, power supply units, tuners, transformers, speakers, trumpets, remote control, microphones, phono-pick-ups . . . in fact everything you may need for P.A. work at lowest wholesale prices!

The Lafayette 6 volt P.A. system is low in cost, compact, yet extremely efficient. Can be adapted to any truck or passenger car . . . even a coupe! It is a model of completeness consisting of 2 large Lafayette Trumpets with cone units, model 25 Lafayette microphone, complete with desk stand and cable, a senior mike in-put stage, and the


famous Lafayette 6 volt 15 watt Amplifier complete with tubes.

This Amplifier is a big improvement over anything ever offered before. It has 4 stages of amplification, providing a tremendous gain. Tone quality is superb even at peak output of 17.5 watts while current drain at maximum output is only 11 amp. It employs the latest tubes while "B" supply is self-contained.

This Lafayette system is suitable for practically any purpose for it is powerful enough to operate up to 8 speakers. Installation is extremely simple and can be completed within one hour. \$45.00

Price of Lafayette 6 V. Amplifier, less tubes **45**
 Kit of matched tubes..... \$6.94
 Complete Lafayette system for battery operation with 2 trumpets, 2 cone units, senior in-put stage, etc. as described above including the amplifier **129.95**

6v. P.A. Battery System

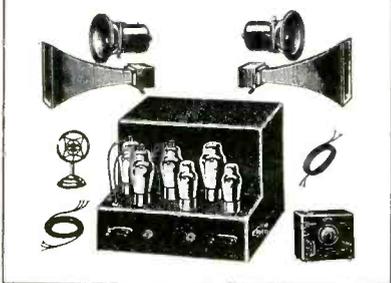

A NEW BOOK ON SOUND



The serviceman who wants to make real money on P.A. needs this new book, **SOUND, Its Fundamentals and Methods of Application.** It is profusely illustrated showing amplifiers and complete systems for every P.A. use. Get a few copies. Place them in the hands of Club, Church or Social Secretaries, Politicians, Yacht Club Members, Boat Owners, etc. Let them read the book and they will sell themselves on the advantages of Public Address. Written in simple non-technical language anyone can understand! The price is only 25c a copy which only partially covers the cost of printing. This book will make money for you. . . Be sure to get a few copies!

6v. Battery Amplifier



★ **A Brilliant
 NEW CATALOG
 from RADIO
 HEADQUARTERS
 will be ready
 for you
 JUNE FIRST
 Send for your copy NOW**

A NEW WORLD OF LATEST RADIO ACHIEVEMENTS

Here is a catalog *timed to the minute! Geared to the season!* It's not an ordinary catalog for it concentrates on those Radio Specialties that sell fastest during the summer months!

Most companies issue one, or at most two catalogs per year. Thus in these very catalogs you'll find merchandise which has been out-moded, out-distanced by the latest developments in the fast moving world of radio.

Wholesale Radio Service Co. alone keeps stride with the times by issuing 4 Big Bargain Books each year! Why buy from a catalog which is 6 to 11 months old when Radio Headquarters gives you the latest, newest developments? In 1934 we have already issued catalogs 55A, B and C. Now comes

Summer Supplement 55D packed from cover to cover with timely, seasonable merchandise.

You'll find portable AC-DC sets, portable phonoradio combinations, portable S.W. sets, Portable P.A., a whole section on Auto Radios and Accessories; Marine Radio and equipment; S.W. kits for those who wish to build during their leisure time this summer. All this in addition to an amazing array of replacement parts, sets, kits, tubes and accessories from the largest stock in the world! This great book is the last word! Our catalogs 55A, B and C have brought you the latest innovations as they have appeared. Now this new 55D brings you right up to the minute. Together they constitute an Encyclopedia of 1934 Radio Bargains . . . at America's Lowest Wholesale Prices!

WHOLESALE RADIO SERVICE CO., INC.
 100 Sixth Avenue, New York, N.Y.
 New Branch
 219 Central Avenue, Newark, N.J.

MAIL THIS COUPON NOW . . . TODAY!

WHOLESALE RADIO SERVICE CO.
 100 Sixth Ave., New York, N. Y. Dept S-54.
 Send me your newest Catalog 55D.
 I enclose . . . cents for . . . copies of SOUND.
 Send me further information on Lafayette 6 v. P.A. system.

NAME

ADDRESS

CITY STATE

SERVICE

A Monthly Digest of Radio and Allied Maintenance

FOR MAY, 1934

COMMUNITY AERIALS

WITH spring here and summer not far behind, it is time for the Service Man to give thought to aerial installations. Not just the common garden variety of aerial, but the new type "community antennas" which permit a number of receivers to operate from a single wire.

Apartment-house owners have gone on a spree of cleaning up and modernizing their buildings, mainly because of increased competition in the realty field. And, if these owners are out for "pre-tying up" their buildings, one of the first things they ought to do is clean up the roofs which are coming more into use as spots for sun bathing and garden parties. But the average apartment roof is an eye sore in the first place, and unfit for use as a place to "sit out" because of the maze of aerial wires strung in all directions.

This is where the Service Man comes in. Such a jumble of wires can easily be replaced by a few well-strung aerials which will serve as signal feeders for every radio receiver in an apartment building—and provide far superior results in the bargain. These "community aerials" are easily installed, can be extended as a complete and permanent system for every apartment in a building, and will provide noise-free reception for the simple reason that shielded transmission lines are employed.

AVAILABLE SYSTEMS

There is a large variety of "community antenna systems" available, some quite simple and others more complex. The small systems are quite satisfactory for the average size apartment building, and are also perfect for use in private homes where a number of radio receivers are in use. This is another angle of the business the Service Man should not overlook. Many people have two, three, and even four sets located in different parts of the house, such as the living room, kitchen, the "bar" or "game" room in the cellar, workshop, etc. Either separate outdoor aerials are used, which are admittedly

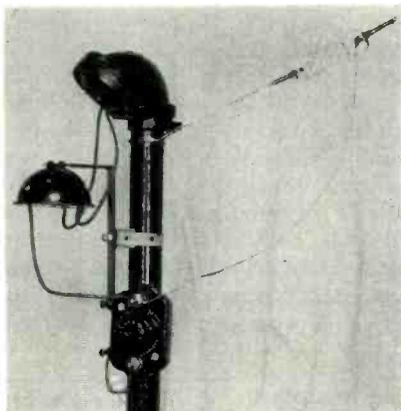


Fig. 5. The aerial lead termination, with antenna transformer, lightning arrester and conduit.

eye sores and cause just so much more concern relative to the dangers from lightning, or the small receivers are operated from some form of indoor, make-shift aerial which provides a comparatively low signal voltage at the receiver input and thereby increases noise troubles. With all receivers coupled to a single, shielded antenna provided with the necessary coupling units, each receiver is favored by the increased signal pickup of the single antenna wire and each receiver is protected from lightning by a common lightning arrester.


To Service Men wishing to install and service such antenna equipment, it is believed that a better understanding of the principles involved in the functioning of such aerials will be of considerable value in determining which type of system should be used to meet specific conditions. Let us first consider the good, old transmission line which is the backbone of the "noise-reducing" part of a "community aerial" system.

THE TRANSMISSION LINE

All antenna systems are built around the transmission line, whose function is simply to conduct the radio-frequency currents over appreciable distances with a low loss. In general, there are two

types of transmission lines, namely, the balanced line¹ and the unbalanced line.² The balanced line consists of a twisted pair, and as its name might suggest it is balanced to ground. Referring to Fig. 1-A, it is evident that both wires of the balanced line will be effected similarly by nearby interference fields so that voltages of identical phase and magnitude will be induced in each. The directions of the voltages are indicated by the arrows, and it can be seen that they oppose each other in transformers T_1 and T_2 and hence are drained off to ground. This results in the absence of any interference voltage in the secondary of either transformer, providing, of course, that both line and transformers are perfectly balanced. Now, if some of the lines of magnetic force do pass between the two wires, a condition results in which the induced currents are in such a direction that they flow around the circuit instead of being drained off to ground. However, if the lines are transposed as shown in Fig. 1-B, it is evident that the voltages in the adjacent sections of the line are opposed so that no interference current will flow in the circuit at all. Obviously the greater the number of transpositions the better the chances of current balance becomes. Twisted wire, then, in conjunction with well-balanced trans-

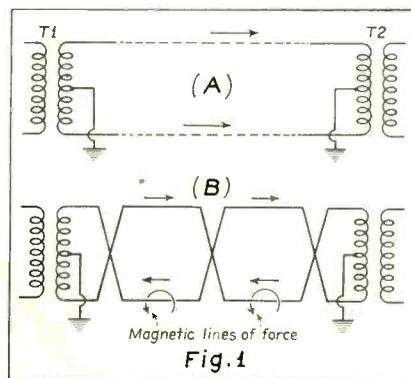¹Service, August, 1932, pp. 198.
²Service, June, 1932, pp. 125, and Service, August, 1932, pp. 193.



Balanced line lead-in systems, indicating direction of current in wires.

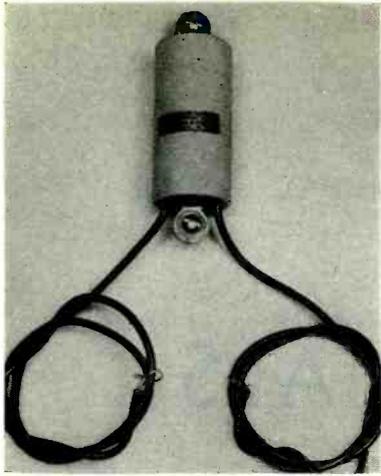


Fig. 6. One of these coupling devices is used for each receiver connected to the common aerial lead.

formers, constitutes a nearly interference-proof transmission line.

UNBALANCED LINES


The unbalanced line generally takes the form of a shielded wire, or as it is sometimes called, a coaxial conductor line. In this case the interference currents are induced in the shield and are simply drained off to ground in the usual manner, and without inducing any interference current in the central conductor. If the impedance of the exposed portion of the shield to ground is zero—i. e., a perfect shield—or if the current is uniformly distributed around the outside of the shield and all points on the outer surface of the shield are equidistant from the central conductor, then it is obvious that the field due to the current in any thin strip of shield is balanced out by an equal field from a similar current diametrically opposite. Fig. 2 shows how the fields from two opposite strips of shield balance out so far as a central space is concerned.

Obviously, concentricity will not be maintained in long lengths of shielded

conductor. Consequently a continuous shield is necessary which is either frequently grounded or of low resistance. However, if either a lead shield or a heavy copper braid is used, the interference pickup is nil. Therefore, as far as results are concerned, there is no choice between balanced and unbalanced lines, provided each are built with equal care.

SIMPLE SYSTEM

Fig. 3 illustrates the simplest types of antenna systems. The balanced transmission line always requires a transformer at each end. Generally both transformers have static shields between primary and secondary, as may be seen from Fig. 3-A, to prevent capacity coupling which might destroy the balance of the system. Further, shields may be employed with the ordinary shielded wire line (Fig. 3-B shows a typical shielded wire line without static shields), although they are of less importance in this application. Now, the impedance ratio of the transformers are usually about 60 to 1000 ohms. Again, some manufacturers recommend connecting as many as 10 receivers to a

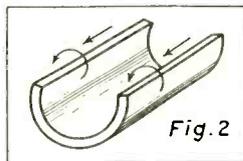

How the fields in a conductor shield balance out when an unbalanced line is used.

system of the type shown in Fig. 3-C. In some instances small coupling transformers are used to connect the receivers to the line, in other cases series resistances, and in other instances the receivers are connected directly across the line. All three systems should operate satisfactorily with no interaction between sets. However, if certain types of superheterodyne receivers are con-


nected to such a system some of the oscillator voltage may be fed back into the line to be picked up by other receivers as a beat note on certain stations. Trouble of this sort will occur only when some of the older and cheaper types of supers are used. There is no remedy except the removal of the particular receiver, as any coupling impedance, either condenser or resistance, would cause too high a loss to the set under question, if any measure of relief were to be afforded the others.

SIGNAL LOSS

While the systems of Fig. 3 are very simple and inexpensive, there is always some loss between receivers and antenna. For the average case, about 30 per cent of the induced antenna voltage is lost at the antenna transformers. If good transformers are used their losses are negligible. The antenna voltage is stepped down to the transmission line to about 25 per cent of its value across the transformer primary. Thus if the induced antenna voltage were 1 volt, about .7 volt would appear across the transformer primary, and .175 volt would be applied to the transmission line. About 10 per cent of this remaining voltage is lost for every 100 feet of transmission line. Now if at the end of 100 feet of the line the voltage is stepped up through a good transformer, about .6 volt would be applied to the set. If sets are applied directly across the line, of course, only 17 per cent of the induced antenna voltage will be applied to their terminals and this only when the input impedance of the sets are sufficiently high that their shunting effect is negligible. This does not represent a serious signal loss, since a change of 50 per cent in signal strength is barely noticeable to the average ear. It is evident, however, that series resistances or small capacities should not be used in series with the sets connected directly to the line. If lines of only 100 feet are used the termination resistance can usually be dispensed with, while for longer lines it should always be used. Otherwise standing waves may be set up on the line causing serious losses at certain frequencies.

COMPLEX SYSTEMS

Obviously the only disadvantage of the simple systems so far discussed lie in the fact that regenerative sets or poorly designed supers may feed energy back into the line to cause squeals in the other connected receivers. This could be reduced if high-loss coupling elements, such as small condensers or large series resistors, were inserted in series with each set, and this can be done if sufficient amplification is inserted between the antenna and sets.

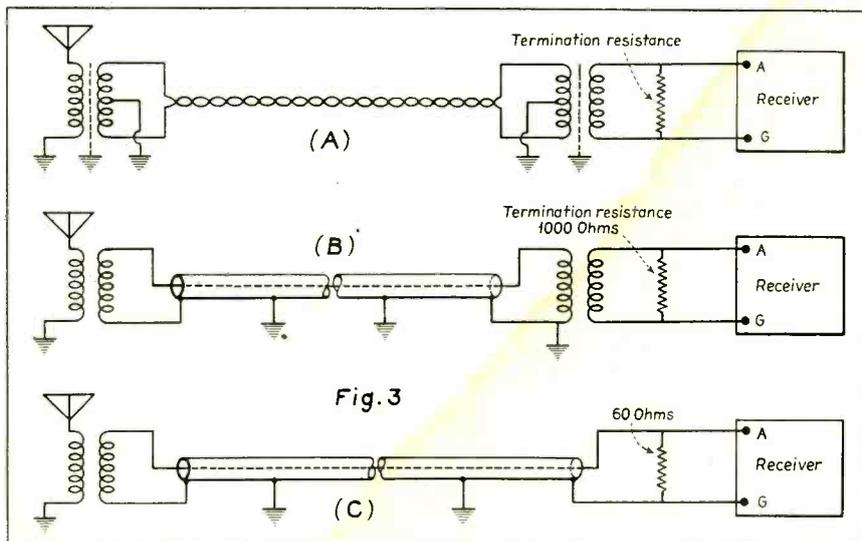

Illustrating three different transmission-line arrangements which may be used for noise reducing. These types of lines are used with community aerial systems.

There are at least two manufacturers (RCA and W. E.) producing such systems. These are illustrated schematically in Fig. 4. In general, several hundred radio receivers may be served in this manner with little or no loss in signal from antenna to receiver and with almost complete isolation of each receiver from the others connected to the system. The RCA system of this type (Fig. 4-A) employs from one to five amplifiers located near the antenna to feed 50 receivers each, while the Western Electric system of the same type (Fig. 4-B) employs four amplifiers, each feeding 750 receivers. The amplifiers in this latter system may be connected through a 750-foot transmission line to the antenna. The essential differences of these two systems are evident from the figures, and their principal virtue lies in the fact that several hundred receivers may be served from one system.

Some of the older systems, which are more or less obsolete now, were similar to the systems illustrated in Fig. 4, except that the coupling elements were single-stage amplifiers instead of resistors. While such means of coupling are technically satisfactory, it is inherently more expensive than the systems shown. In addition, care must be taken in systems employing amplifiers to prevent overload from nearby transmitters, for such overloads may cause so-called phantom stations to be produced at the sum or difference frequencies of two strong stations, or the usual cross-modulation. Wavetraps similar to those shown in Fig. 4-B are the most effective remedy for this trouble.

SMALL INSTALLATIONS

Amy, Aceves & King and Arthur H. Lynch, Inc., have produced a system that is quite suitable for smaller installations such as small apartments and homes. This system is limited to 12 receiver outlets and may be installed either inside or outside. An antenna transformer, similar to the one shown in Fig. 5, is required with each aerial, the latter being from 40 to 75 feet in length. Also a coupling device is placed directly across the downleads, and the downleads may be run a total length of 400 feet. Such a coupling device is clearly shown in


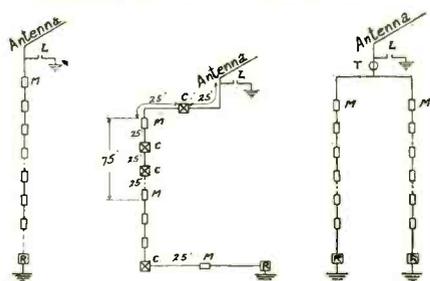


Fig. 8. Three riser connections. Other arrangements can be made, depending upon the size of the complete job.

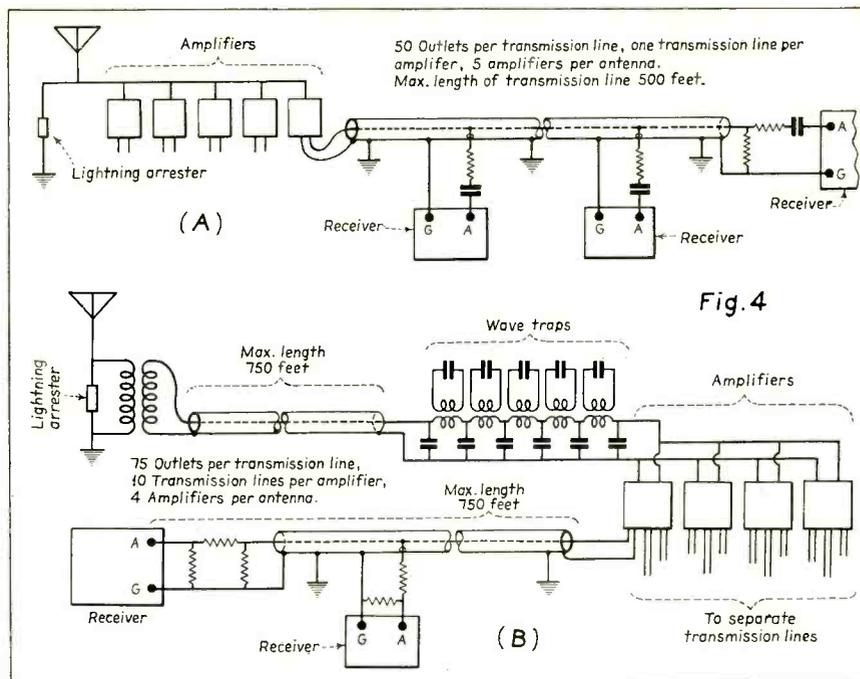

Radio-frequency distribution system for very large installations. In both A and B, amplifiers are used for each set of lines. Note the wave traps in system 4-B.

the illustration of Fig. 6. The important feature of this system is that the feeder wires may be run in armored or lead-covered cable.

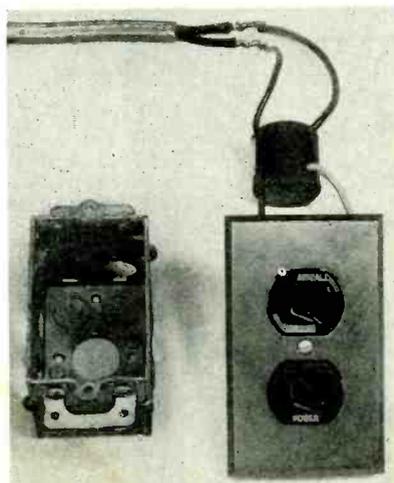


Fig. 7. A typical radio receptacle for community aerial installations. A small coupling transformer is shown connected in the shielded cable circuit.

OUTSIDE SYSTEM

These companies have, also, an outside system of particular interest that permits a total of 24 receivers. In this system each antenna consists of a single wire 50 to 75 feet in length, supported about 20 feet above the roof, a lightning arrester being installed for each aerial and mounted at the head of the downlead (Fig. 5) in accordance with the requirements of the Board of Fire Underwriters. Where the roof space is limited and it is impossible to construct an aerial 50 feet long in a straight line, satisfactory results may be had by

making the aerial up into two or more sections connected at one end and fanned out at the other.

The downlead wire is supported at the top and the bottom by small strain insulators, and it is located outside the windows, allowing the shortest connection to the radio sets. This downlead is held out from the wall by means of standoff insulators, located a few inches below the coupling unit. These coupling units are required for each set.

The lead-in wire of the coupler is brought in through a hole in the window-sill, and is then run to the surface mounting receptacle through wire mold or along or in back of the baseboard. Ground connections are picked up from a water or radiator pipe and run in the same manner to the ground connection of the receptacle. For each downlead a terminal resistance (R) is required and must be connected between the end of the downlead and a good ground. This is shown in the antenna arrangements in Fig. 8. The terminal resistance is 1000 ohms and rated at 30 watts.

CONDUIT SYSTEM

A similar description of a conduit or inside type antenna system of the same companies is thought to be of interest. The one which will be described allows a total of 20 receivers to be connected with an average antenna, the antenna being of standard copper wire located as high above the roof as possible and a lightning arrester being installed for each aerial. Two vertical risers (three different riser diagrams are shown in Fig. 8) may be connected

(Continued on page 183)

New All-Wave Aerial

AS we all know, there is at the present time a great deal of interest in all-wave receivers, and unless all indications are wrong there is likely to be a great deal more, due to the large amount of valuable information and entertainment on bands other than the broadcast band. Now, along with the advent of these multi-band receivers a great deal of difficulty was experienced with antenna systems.

ANTENNA DIFFICULTIES

The ordinary antenna that worked fine for the old broadcast receivers has been found to be inadequate for short-wave reception due, in part, to the greater noise pickup at the high frequencies and to the antenna length. Now the effectiveness of an antenna depends upon its length, the length determining the point at which it will be resonant. The result is that a good broadcast antenna is too long for good short-wave reception, and the usual short-wave antenna—which is not efficient on all the short-wave bands anyway—is entirely too short for satisfac-

tory reception on the broadcast band. Hence, there is a distinct need for some type of antenna system that will be effective at a number of different points; namely, the 16, 19, 25, 31, and 49 meter bands, as well as the broadcast band, and while separate antennas with some sort of switching arrangement might be employed to cover these bands, the installation difficulties, the inconvenience of the switching arrangement and the cost of such a system would be prohibitive.

THE "DOUBLE-DOUBLET"

The RCA in their World-Wide Antenna System have combined a number of antennas into one simple system. In general, this system is of the "double-doublet" type using a balanced transmission line of a length to match the doublet antenna, and the receiver matching transformer, the latter being designed to match the receiver impedance to the line, and to eliminate noise pickup on the transmission line.

It can easily be seen from Fig. 1 that the antenna is made up of four sections of different lengths, namely, 29- and

16½-foot sections. A 29-foot section will tend to tune toward the 49-meter band, the 16½-foot section will tend to tune toward the 16-meter band, and the connection of both doublets to the transmission line has a tendency to give a smooth match over the entire short-wave band. A switch is located on the receiver transformer which eliminates the primary and one side of the twisted pair when thrown to the "STD" position. Thus the antenna is converted into the conventional "flat top" or "inverted L" for broadcast reception.

A close inspection of Fig. 1 will reveal a number of interesting features concerning this antenna system. First, the 29-foot sections are horizontal, being connected to their respective supports by strain insulators, while the 16½-foot sections are placed at an angle determined by sighting along the line AD or CB. This is shown in the enlarged view of the crossover insulator, in Fig. 1, which also reveals that the 29-foot section on one side is connected to the 16½-foot section on the opposite side, the connections for the


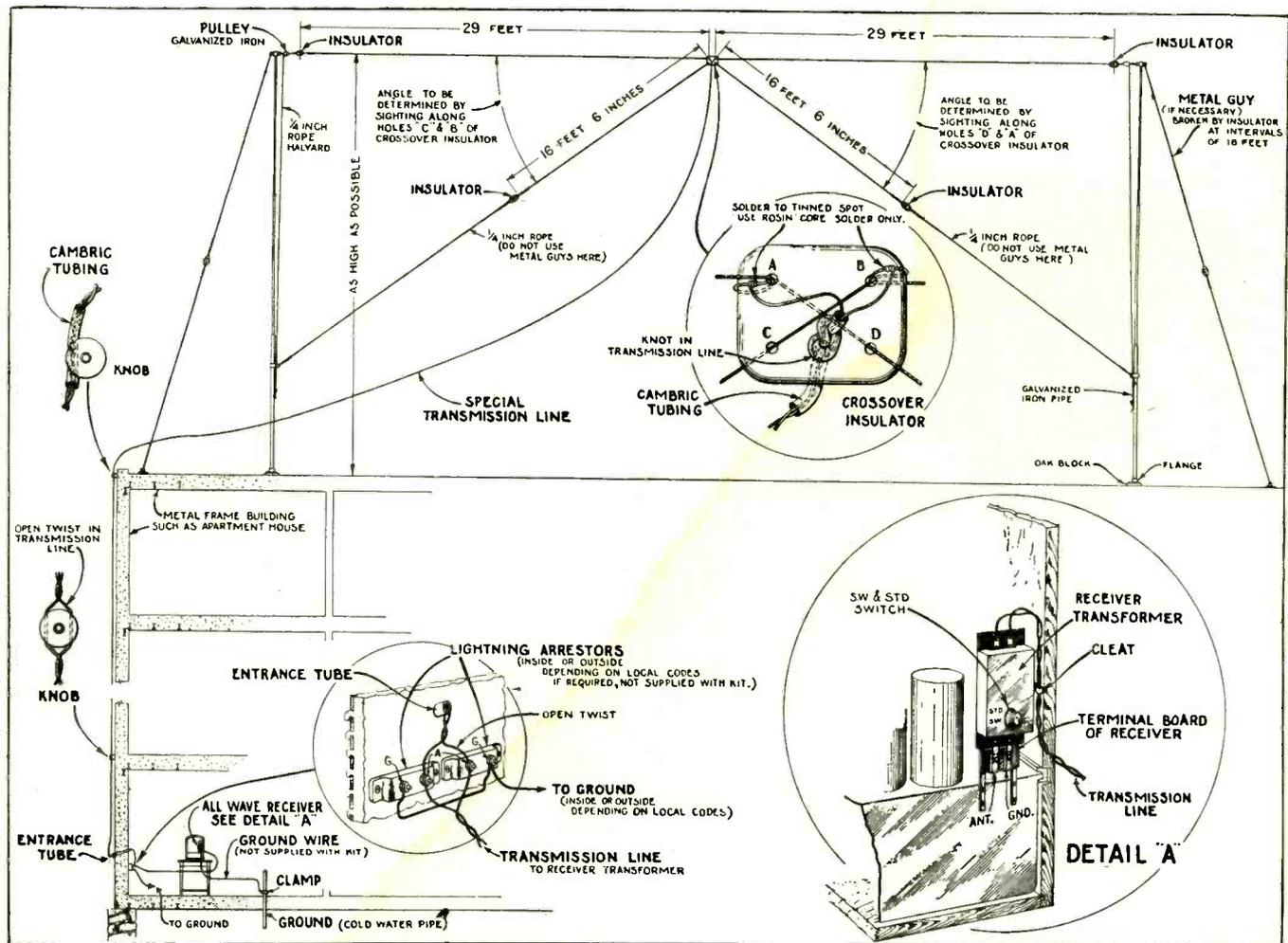


Fig. 1. Details of the RCA Victor "World-Wide Antenna System."

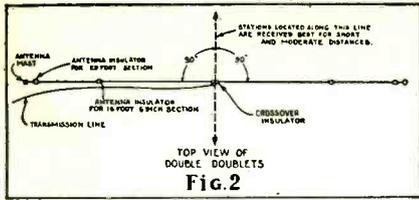

Indicating the correct angle between the two parts of the doublet span.


balanced transmission line being taken from the points A and B.

DIRECTION OF SPAN

Fig. 2 indicates the correct angle between the two parts of the doublet span; i. e., 180°. It should be kept in mind, also, that those stations that are on a line perpendicular to the span will be received best. Again, maximum reduction of interference will be obtained when the span points toward the source of the station interference. However, if it is necessary, the doublet may be placed at an angle of 90° as shown in Fig. 3, though this results in a decrease in signal of about 30 per cent. In still other cases where a 60-foot span cannot be obtained, loading coils (RCA Stock No. 6958) may be used as shown in Fig. 4 and Fig. 5. This permits the reduction of the span to approximately 34 feet, or if the space is still not sufficient, a vertical doublet may be used as illustrated in Fig. 5. A vertical doublet has the advantage of being non-directional, though it will not give as good a signal-to-noise ratio as the horizontal doublet.

HEIGHT OF SPAN

Since the signal strength varies with the height above ground, the height of the span is another very important consideration. The height of a doublet of this type is taken as the distance from ground to the center of the span, and this distance should not be less than 30 feet. The location of the ground will depend, of course, upon where the antenna is located. For example, if the antenna is located on top of a building with a grounded metal frame, the height from ground will be the height from the top of the building; while on the other hand, if the location is on a

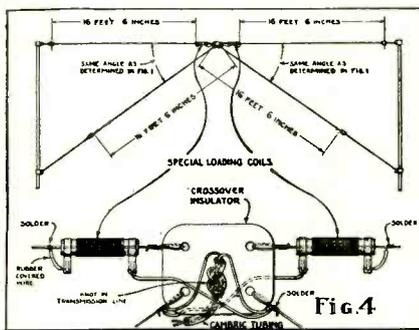

If the full length of the doublet cannot be used, loading coils may be connected in series, as shown.

frame dwelling the height may be taken from the actual ground.


CLEARANCE

Further, the antenna system should be kept clear of wires, buildings, highways, electrical machinery, and the like, for two very good reasons; namely, the prevention of the possibility of shadows being cast upon the antenna, and the reduction of interference pickup on the antenna. The balanced transmission line, of course, prevents practically all of the interference liable to be picked up on the lead-in. Then, too, another aid to the avoidance of interference lies in the transmission line, as it may be up to 500 feet in length—allowing quite a bit of choice, generally, in the location of the antenna. However, the shortest length of transmission line used is 110 feet, and any remaining length is to be coiled—it must not be cut. For distances greater than this, additional lengths of line must be added in multiples up to two times. After 220 feet, however, additional lengths can be added in any desired length up to 500 feet. This is shown in the accompanying table:

Line Run to Receiver from Doublet in Feet	Line Length Used in Feet	Number of Lengths of 110 Feet	Length to be Coiled in Feet
95	110	1	15
150	220	2	70
210	220	2	10
300	300	3	No coil necessary. Cut off unused portion if desired.
500	500	5	

MATCHING TRANSFORMER

The matching transformer is used to couple the transmission line to the receiver, and it is so designed that it may be used as an electrostatic shield to balance out the transmission line to ground. The transformer is designed to mount directly on the antenna-ground terminal board of RCA Victor All-Wave receivers such as Models 140, 240, 120, 121, 320, and 321, giving as a result the shortest connection to the antenna and ground terminals. The installation of the transformer to a Model 140 is shown in Fig. 1, and it should be noted that the length of the ground connection of the special transformer is critical. To insure maximum noise reduction, this connection should be kept the shortest possible distance (not over one inch) from the chassis ground. On other manufacturers' receivers, having the chassis grounded, the transformer should be mounted on the side of the cabinet (by utilizing holes, spacers and screws provided) in such a manner as to permit having the transformer ground connector, when bent, slip under the ground terminal or a chassis nut. If this is not possible, make the ground connection absolutely as short as possible.

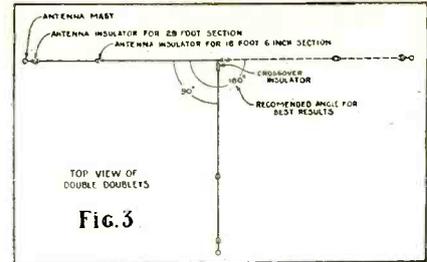


The doublet may be placed at an angle of 90 degrees, but this will decrease the signal about 30 per cent.

ALIGNMENT

On the RCA Victor Model 140 (All-Wave) the connection of the receiver matching transformer tends to throw the antenna circuit for band "D" out of alignment. This should be checked in the usual manner by the use of the tuning wand and realigned with the range switch at "D" and the station selector turned to the 25-meter band. If no station or oscillator signal can be used, use background noise as a basis of line-up.

It will be noticed that on most converter types of short-wave receivers, such as the RCA Victor Universal Radiola RO-23, the use of this system reduces serious cross-modulating effects from nearby code, airport, or amateur stations.

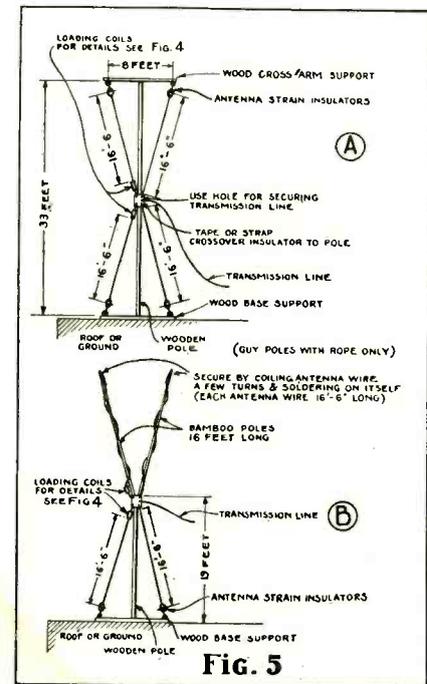In order not to affect the receiving qualities of the antenna system, wood poles and rope guys should be used wherever possible. If guy wires are necessary, lengths of over 16 feet should be broken by insulators, one for every 16 feet.



(A) and (B) show vertical doublets, which are non-directional, but have less efficiency than the horizontal doublet.

THE CHANNEL CONTROL SYSTEM

To the right of the AGC tube in the main diagram are the two type 57 tubes involved in the channel control system. The first 57 is the actual channel control tube and the second is the silencing tube which controls the type 56 tube in the first a-f stage.

The channel control system insures correct tuning, and eliminates interstation noise. This system functions to silence the audio channel under certain predetermined conditions, and to unlock the audio channel under certain other conditions.

Referring to the diagram of Fig. 4, the tubes involved in the operation of this channel control system are, a channel control tube, C, a silencing or relay tube, S, and the first a-f tube. The operation of the system is as follows:

When the arm of the 15,000-ohm channel control adjustor, 8, is retarded to the negative side, there is zero bias on the channel control tube and this tube draws plate current irrespective of signal conditions in its grid circuit. This plate current through resistor 4-9 biases tube S to cut-off, resulting in normal bias on the first a-f tube. Under these conditions the channel control is inoperative, and the entire receiver functions as a conventional superheterodyne with AGC.

However, as the arm of the channel control adjustment is advanced toward the positive side, the bias on tube C increases to, and beyond, cut-off. When cut-off bias is applied to tube C and the plate current through resistor 4-9 stops, the bias on tube S returns from cut-off to normal, allowing plate current to flow in the plate circuit of tube S (through resistors 2-4 and 11-12). The current through resistor 2-4 produces a voltage in series with the normal bias developed across resistor 2-14, and these combined voltages bias the first a-f tube to cut-off, thus silencing the audio channel.

If a signal of sufficient strength is applied to the grid of tube C this tube will draw plate current, biasing tube S to cut-off and returning the audio channel to normal operating conditions. The

signal strength required to perform this operation is determined by the degree past cut-off to which tube C is biased.

The signal to actuate the channel control circuits is induced in a tuned tertiary winding of the third i-f transformer so coupled to the primary that the selectivity at the grid of tube C is considerably more than the selectivity at the grid of the second detector. As a result of this greater selectivity the signal at the grid of tube C will be insufficient to unlock the audio channel unless the receiver is tuned almost exactly to the carrier. However, this extreme selectivity does not impair the high-frequency response, as the received signal does not pass through this very selective control circuit.

An interesting and important feature of this channel control circuit is, that as the ratio of noise to signal increases it becomes more difficult for a signal to unlock the audio channel. An explanation of this peculiar phenomenon follows.

SIGNAL-NOISE SELECTION

Reference to the diagrams of Fig. 1 and Fig. 4 will indicate that the signals that operate both the AGC and channel control circuits are derived from the plate circuit of the second i-f tube. Any signal impressed on the grid of the AGC

tube tends to reduce the sensitivity of the receiver. Any signal impressed on the grid of tube C (Fig. 4) tends to unlock the audio channel. The conductance of the AGC coupling circuit is a direct function of frequency. The conductance of the channel control coupling circuit is practically zero except at the frequency to which the i-f transformer is tuned, at which frequency the conductance is high. If a voltage of any frequency other than the i-f (such as noise) appears in the plate circuit of the second i-f stage this voltage will be transferred to the grid of the AGC tube and effect a reduction in sensitivity of the receiver. However, this voltage will not be transferred to the grid of the tube C owing to the frequency discrimination of the channel control coupling circuit and, therefore, will have no effect on the channel control circuit.

To sum up—only a voltage whose frequency is equal, or very nearly equal, to the frequency to which the i-f transformer is tuned will have any effect upon the channel control circuits. The AGC circuits function to maintain a constant voltage across the plate load of the 58 second i-f tube with almost no regard for the frequencies present in that voltage.

An illustration might clear up any possible misunderstanding: The AGC circuits function to maintain a constant voltage across the plate load of the second i-f tube. If this voltage is comprised of only the i-f signal, a certain voltage will be transferred to the grid of tube C. If, however, this voltage is comprised of equal parts of signal and noise, and is of the same value as in the first case, only half as much voltage will be impressed on the grid of tube C. If this voltage is comprised wholly of noise, the AGC circuits function to


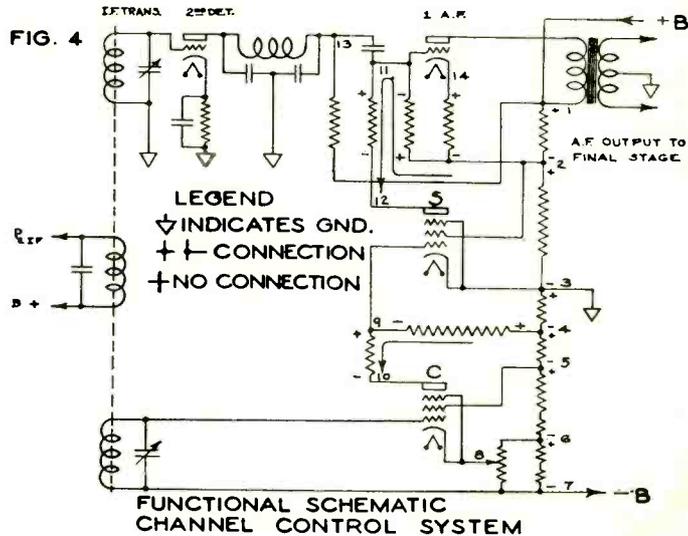


FIG. 3

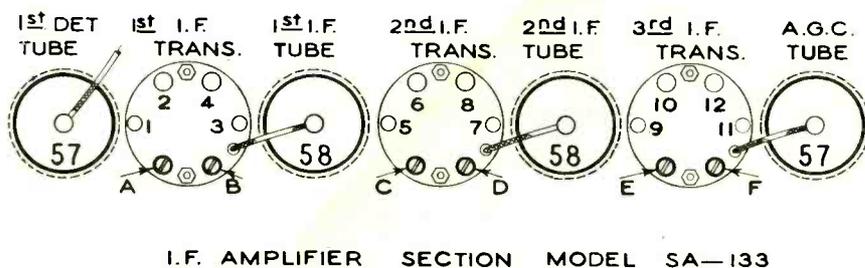

maintain this voltage at practically the same value as if it were at i-f, but the channel control coupling circuits transfer none of this voltage to the grid of tube C, and the audio channel remains silent.

The circuit of Fig. 5 shows the channel control circuits and the values of the various elements.

ALIGNMENT PROCEDURE


In order to insure correct operation of the receiver and of the channel control in particular, it is essential that the entire alignment procedure be performed with utmost caution in order to maintain a very high order of precision.

In view of the difficulty of correctly aligning the i-f stages, the Service Man is warned against tampering with the adjustments unless a thorough investigation definitely proves them to be in need of attention.

The difficulty in correctly aligning the i-f stages is a result of the design of the i-f transformers. In order to obtain a high degree of selectivity without sacrificing tone quality, these transformers have been designed to provide a very narrow resonance curve with an essentially flat top. This is accomplished by over-coupling these transformers enough to obtain a double peak (or double bumps) the correct distance apart. With these transformers over-coupled it is impossible to correctly align them; therefore, it is necessary to decouple each i-f transformer while it is being aligned. This is accomplished by shunting one winding with a 20,000-ohm resistor and aligning the other winding.

In the event that the i-f stages need alignment, proceed as follows:

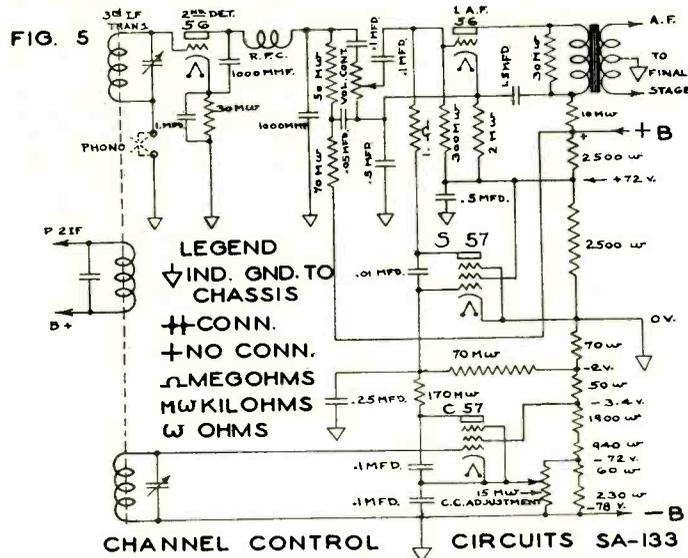- (1) Attach output meter from plate to plate of the 2A5 tubes.
- (2) Remove the silencing tube of the channel control circuit.
- (3) Attach the local oscillator, tuned to exactly 175 kc, to the control grid of the first detector, using some type of coupling device that provides a d-c path to ground. *In all ganging operations use the weakest signal that will give a satisfactory indication on the output meter.*
- (4) Attach a resistor across the secondary of the first i-f transformer (by inserting the leads in holes 3 and 4—See Fig. 3) and adjust screw A for maximum indication on the output meter.
- (5) Remove the resistor from the secondary of the first i-f transformer and place it across the primary (holes 1 and 2) and adjust screw B for maximum indication on the output meter. *Leave*



this resistor where it is for the balance of the alignment procedure.

- (6) With a second resistor repeat operation 4 (holes 7 and 8, screw C).
- (7) With this second resistor repeat operation 5 (holes 5 and 6, screw D).
- (8) With a third resistor repeat operation 4 (holes 11 and 12, screw E).
- (9) With this third resistor repeat operation 5 (holes 9 and 10, screw F).
- (10) Adjust the channel control pad (screw adjusting trimmer under chassis pan near third i-f transformer (adjustable through hole in chassis pan bottom cover)) for minimum (dip) indication on the output meter. This dip is not very pronounced, and unless extreme care is exercised it may be passed over without being noticed. *Note:* Be sure the resistor leads make good contact when inserted in holes in transformers. For all above hole numbers and adjuster screw letters, refer to the diagram of Fig. 3.

CALIBRATION PROCEDURE

- (1) Adjust the dial mechanism (if necessary) so that with the plates entirely enmeshed the dial will indicate 525 kc.
- (2) Set the dial to the point where a station (or oscillator) of known frequency, about 600 kc, should be received and adjust the oscillator pad (screw adjustment under hole in chassis pan between oscillator section on gang condenser shields) until desired signal is heard.
- (3) Set the dial to the point where a station (or oscillator) of known frequency, about 1400 kc, should be received and adjust the oscillator trimmer (screw adjustment, top of gang condenser, third from front) until the desired signal is heard.
- (4) Re-check operations 2 and 3.
- (5) Check the calibration at, or near,

1200 kc and correct (if necessary) by bending outer oscillator section rotor plates.

- (6) Repeat operation 5 at, or near, 950 kc.
- (7) Repeat operation 5 at, or near, 650 kc.
- (8) A thorough re-check of the foregoing 7 operations to insure perfect calibration is recommended. If the alignment procedure to this point has been performed correctly the calibration will be accurate to within 2 kc at all points on the dial.

R-F ALIGNMENT

- (1) Attach the output meter from plate to plate of the 2A5 tubes.
- (2) Attach the local oscillator to the antenna and tune to set at each test frequency.
- (3) At 1400 kc, adjust the antenna, link, and r-f trimmers (screw adjustments, top of gang condenser—see main diagram) for maximum indication on the output meter using the weakest signal that will give a satisfactory indication.
- (4) At 1200 kc, bend the plates of the antenna, link and r-f rotors to give maximum indication on the output meter.
- (5) Repeat operation 4 at 950 kc.
- (6) Repeat operation 4 at 650 kc.
- (7) Repeat operation 4 at 570 kc.
- (8) Re-check operations 3 and 8 inclusive to insure perfect alignment.
- (9) Remove resistors from the i-f transformers.
- (10) Remove output meter and oscillator, attach antenna, set dial to a point where no signal is being received and turn channel control adjustment counter-clockwise just far enough to silence the static and inter-station noises. The receiver is then ready for operation.

THE S. W. CONVERTER MARKET

By Ellis Cohen*

AT no time within the past few years has there been such widespread interest in the reception of short-wave foreign broadcasts and the local police and airplane signals. The public has become "short-wave" conscious as evidenced by the increased sales of dual-wave and all-wave receivers.

There are about 18,000,000 radio receivers in the United States. All the owners of these receivers are not going to buy new sets, even with short-wave reception put out as an enticement, for the simple reason that there are thousands of people too well satisfied with their old sets to make any change. Yet, it is quite evident that a large percentage of the people who own these 18,000,000 receivers would like to experience the thrill of pulling in foreign stations and the ever-exciting police signals.

SHORT-WAVE SALES

It is here where the Service Man fits into the picture. He is in a position, when making a service call, to demonstrate just what a modern short-wave converter can accomplish—a converter using the new type tubes and with a satisfactory coupling system which will permit it to be used effectively with most any type of broadcast t-r-f or superheterodyne receiver.

It has already been demonstrated that many people are more inclined to purchase a short-wave converter than an all-wave receiver because the converter adds to a remarkable degree to the capabilities of old broadcast receivers to which the owners have become attached. It gives the owner something

*Sales Manager, Insuline Corp. of America.

to talk about and supports his belief that "the old set is a world beater."

If the Service Man, when he completes a job of repairing a set, would simply attach a good short-wave converter and tune in on one of the short-wave bands, he can show the set owner that he is getting something that he cannot possibly get with the old set. My suggestion is that a converter should be left with the set owner for a day or two for an actual demonstration. The reception of London or Berlin will whet his appetite, and these two stations are comparatively easy to pick up.

Summer is really a very good time to sell short-wave converters, because the high frequencies are not troubled with much static and reception is quite often better than at other times of the year. Summer is also a good time to sell all-wave antenna systems, for installation is more convenient. While it is not advisable to try to sell too many things at one time, there is always the opportunity for a Service Man to call back again after a converter is sold and make a new sale of an all-wave antenna system.

AN ALL-AROUND CONVERTER

Now comes the question as to what sort of a short-wave converter the Service Man should attempt to sell. First of all, there is a better chance of a sale if the price of the converter is not too high. Fortunately, good, low-priced converters are obtainable on which the Service Man can make a good profit. These units are small and quite simple in operation.

Next in importance is the design of

the converter. It should preferably be of a type which is self-powered and will operate equally as well on a-c as on d-c. With a converter of this type, all that is necessary in any case is to plug it into the line, change the aerial connection, and attach the output of the converter to the input of the broadcast receiver. Furthermore, the converter should have a switch which will permit the aerial to be changed from the converter input to the broadcast receiver input so that the installation and connection will be permanent.


The circuit of a converter of this type is shown in the accompanying diagram. This unit uses a type 37 tube as a half-wave rectifier in the power-supply, and a type 6A7 tube as first detector and oscillator. Since there is no power transformer or complicated coils and switching system, the cost of the unit is kept low. The absence of a switching system might be considered a drawback on first thought, but it must be remembered that plug-in coils are far superior, and in such a simple unit it is best to keep losses as low as possible. The consequent increase in efficiency makes the converter that much more sensitive to weak signals.

The usual inconvenience of plug-in coils is practically eliminated by the use of a fairly large capacity tuning condenser—used in conjunction with a vernier dial to make tuning easy. Only two coils are therefore necessary, one coil to cover the waveband from 20 to 60 meters and the other to cover the band from 60 to 200 meters. Since the average short-wave listener usually stays in one band for a considerable length of time, the coil changing is no real inconvenience.

EXTERNAL POWERED CONVERTER

If it is believed that there is a good market for an even cheaper converter, there is the type which obtains its heater and "B" supply directly from the power-supply in the broadcast receiver. This type is quite satisfactory providing it uses no more than one or two tubes, for in this case it places no heavy drain on the receiver power-supply unit. Most converters of this type are supplied with an adapter which may be placed over the prongs of the power tube in the broadcast set—the most logical place to pick up the voltage supply. Installation of this type of converter, therefore, is equally as simple as the self-powered type.

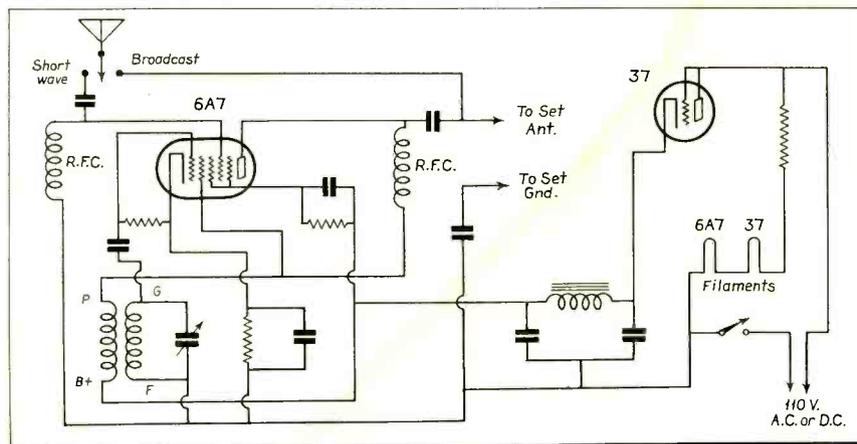The writer believes that the Service Man has a real opportunity to cash in on the publicity being given short-wave radio if he will go ahead with the home demonstration idea. It's certainly worth a fling.



Circuit diagram of a simple self-powered short-wave converter which may be used with any type of broadcast receiver. Plug-in coils are used.

NOVEL 6B7 AVC CIRCUIT

(See Front Cover)

The Silvertone (Sears Roebuck) Models 1722X and 1732X twelve-tube receivers employ a novel type of AVC system entirely divorced from the second detector circuit and working directly from the output of the last i-f tube.

Referring to the circuit on the front cover, note that a 6B7 tube is used solely for automatic volume control action. A study of the diagram will show, first, that the cathode circuit of the tube includes the 50,000-ohm resistor, R-3; a choke, which in the complete circuit is in relation to the tuning flasher system; and the 2500-ohm speaker field the low end of which is grounded. For the purpose in hand all three units may be considered as a single cathode bias resistance. Second, note that the diode plate B of the 6B7 tube is connected to the plate of the i-f tube through the condenser C-1. Therefore, a certain percentage of the i-f signal voltage is impressed on diode plate B. Third, the actual AVC voltage is developed in the circuit of diode plate A, and is taken off at point 4 and fed to the controlled tubes through the resistor in series with the lead from point 4.

OPERATION OF CIRCUIT

Now let's get down to the actual operation of the AVC system. Again referring to the diagram on the front cover, it will be seen that if there were no plate current through the 6B7, its cathode would be negative with respect to diode plate A by the amount of the voltage drop across the 2500-ohm speaker field. However, because of the 6B7 plate current and consequent voltage drop across the 50,000-ohm resistor R-3, the cathode potential of the 6B7 is raised so that it is approximately 15 volts positive to diode plate A.

As previously pointed out, a portion of the i-f signal is fed through condenser C-1 to diode plate B. The resulting current, flowing through R-1 creates a voltage drop across it with point 1 positive with respect to point 2. This voltage is impressed through R-2 on to the control grid of the 6B7. This increased negative control grid bias decreases the plate current and the voltage drop across R-3. As a consequence the cathode bias with respect to ground decreases. This is equivalent to saying that diode plate A becomes positive with respect to the cathode. Current therefore flows from diode plate A to the cathode, creating a voltage drop across R-4 with point 3 posi-

tive with respect to point 4. Since the grid returns of the r-f, translator and second i-f stages are connected to point 4, the voltage drop across R-4 is impressed on the control grids of these tubes. This negative bias, which varies in step with the strength of the signal, controls the amplification of these tubes. An increase in signal strength is offset by a decrease in tube amplification so that the output of the i-f stage tends to remain at a constant value.

Because the cathode of the 6B7 tube is 15 volts positive with respect to diode plate A (the AVC plate) the AVC action is delayed until the received signal is strong enough to cause diode plate A to go positive with respect to the cathode. In this way the full sensitivity of the receiver is maintained for stations too weak to give full output from the receiver.

COMMUNITY AERIALS

(Continued from page 175)

to the same antenna provided the total number of outlets does not exceed 25, unless, of course, an exceptionally good antenna is used. In this case an antenna transformer (T) is installed between the antenna and branch risers, as shown in the right diagram of Fig. 8 and also in the illustration of Fig. 5.

The wiring used with this system is enclosed in a rigid conduit and consists of two straight copper wires rubber-insulated and covered with a paraffined braid. One wire is used as the down lead feeder from the antenna, to which the couplers in that riser are connected. The end of this wire is connected through a terminal resistance to ground in the basement. A typical radio receptacle for this type of system is shown at the right in Fig. 7.


When the length of the conduit between the radio outlets, or the distance between the top of the conduit on the roof of the building and the first radio outlet, is more than 50 feet, loading coils are required. A loading coil should be installed approximately every 25 feet in series with the downlead. Also for each downlead a terminal resistance is used. This resistance is connected between the end of the downlead and a good ground.

After the installation, a continuity test of both the aerial downlead and the ground wire should indicate approximately 1000 ohms for each terminal resistance. Since the resistance of the coupler units are negligible, the resistance of the aerial to ground for a single downlead should measure around 1000 ohms. For two downleads in parallel this value should be 500 ohms.

6C6, 6D6 and 76 Tubes


RCA Radiotron, E. T. Cunningham have released the technical data on the 6C6, 6D6 and 76 tubes. The tube symbols and bottom views of the socket connections are given herewith.

6C6 and 6D6

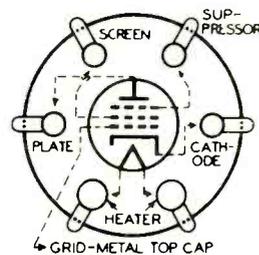

Since the Service Man has no particular use for the specific characteristics of tubes, such as inter-electrode capacity, etc., we believe it will suffice to state in these cases that the 6C6 is the 6.3-volt version of the 57 tube, the 6D6 the 6.3-volt version of the 58, and the 76—a particularly new tube on the horizon—the 6.3-volt version of the 56.

76

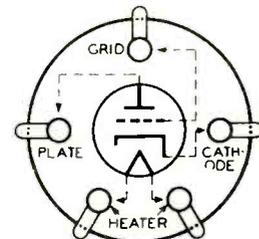

All three tubes have the usual heater current of 0.3 ampere, and are operated at the same values of plate and screen voltages as their 2.5-volt sisters.

Philco Model 58

Model 58 is a four-tube superheterodyne receiver, very similar to Model 57. It uses the same tubes, circuit, and most of the same electrical parts as the Model 57. However, the cabinet is somewhat different, and a pilot light has been added. The illuminated dial and volume indicator are similar to those used in Model 54-C.

The center tap of the filament winding goes to B—instead of to ground. This connection (to B—) is also used on all Model 57's except the earliest production.

Also the connections on the oscillator pick-up coil have been changed from the Model 57. In the Model 58 one end of this coil goes directly to the cathode of the detector-oscillator tube, and the other end to the 8000-ohm resistor and .001-mfd condenser, the other ends of these two units being grounded.

Knight Model W All-Wave

The diagram of this 8-tube Knight (Allied Radio) superheterodyne, with all values and voltages, is given on this page.

A type 78 tube is used as first detector and a 37 tube as oscillator. Wave changing in these circuits is accomplished by a five-position tandem switch. Separate coils are used for each waveband and one section of the tandem switch selects a colored light for each position or waveband. The lights are supplied by the same winding on the power transformer which feeds the tube heaters.

There are two i-f stages following the first detector, each stage employing a type 78 tube. These i-f tubes obtain their initial bias from the voltage drop in the 300-ohm resistors in series with the cathode circuits. The grid return circuits of the i-f tubes are connected to the automatic volume control line terminating in the output of the diode second detector.

The diode section of the type 85 tube supplies signal voltage to the triode section. The control grid of the 85 triode is biased from the same source as the control grids of the type 42 power pentodes; namely, the drop in voltage across the resistor network shunting the speaker field. Since the speaker field is in the negative leg of the power-supply system, the voltage developed is negative with respect to ground.

The volume control is in the grid circuit of the 85 triode. The tone control is in the grid circuit of the power tubes.

The i-f stages are carefully peaked

at 456 kc and should not require adjustment under ordinary circumstances. However, if adjustment is found necessary, feed a 456-kc signal from a test oscillator to the grid cap of the 78 tube located at the rear end of the tuning condenser; then adjust the double trimmers in the top of the coil cans nearest this tube—also the single trimmer in the top of the coil can near the type 85 tube, to loudest volume, being sure to keep the oscillator signal at a low volume level. In trimming the frequency bands, first set the dial to the third group of figures from the right-hand end. Trim the "red" band first by adjusting the trimmers on top of the tuning condensers until a signal of the proper frequency applied to the built-in aerial is heard at its loudest. Next, trim the "orange" band by adjusting the 3-plate trimmers, located on the under side of the chassis, to loudest volume with proper signal frequency applied to the antenna. Finally, trim the "blue" band by adjusting the 2-plate trimmers located adjacent to the 3-plate trimmers, in the same manner. In trimming the various bands, be sure that the band switch is set to the proper band as indicated by the color of the dial lamp. Also, keep the oscillator signal to as low a volume level as possible for accuracy.

PHONOGRAPH CONNECTIONS

If it is desired to employ the audio amplifier of the receiver for the reproduction of phonograph music, mount a single-pole toggle switch and two insulated pin jacks in the rear of the chassis near the type 85 tube socket; connect

one side of the switch to one pin jack, the remaining pin jack to one outside terminal of the volume control and the remaining switch terminal to the other outside terminal of the volume control. Plug the phonograph pickup leads into the pin jacks.

Spartan "A" and "AX" Receiver Models

The Spartan receivers Models 75-A, 475-A and 478-A use the same chassis. These are all-wave receivers manufactured for the domestic market and are equipped with an inter-station noise suppressor system.


The 75-AX, 475-AX and 478-AX receivers are export models, all using the same chassis. This chassis differs from the chassis used in the "A" models in that there is no inter-station noise suppression and there is added a radio-phonograph switch and pickup jacks.

The i-f peak in all these receivers is 456 kc.

The 1C6 Tube

The 1C6 tube is of the 2-volt filament type. It is a five-grid, electron-coupled, detector-oscillator tube with a high conversion gain and was designed to displace the 1A6 in battery receivers of the all-wave type. It readily oscillates at frequencies in the upper band of 10 to 24 megacycles.

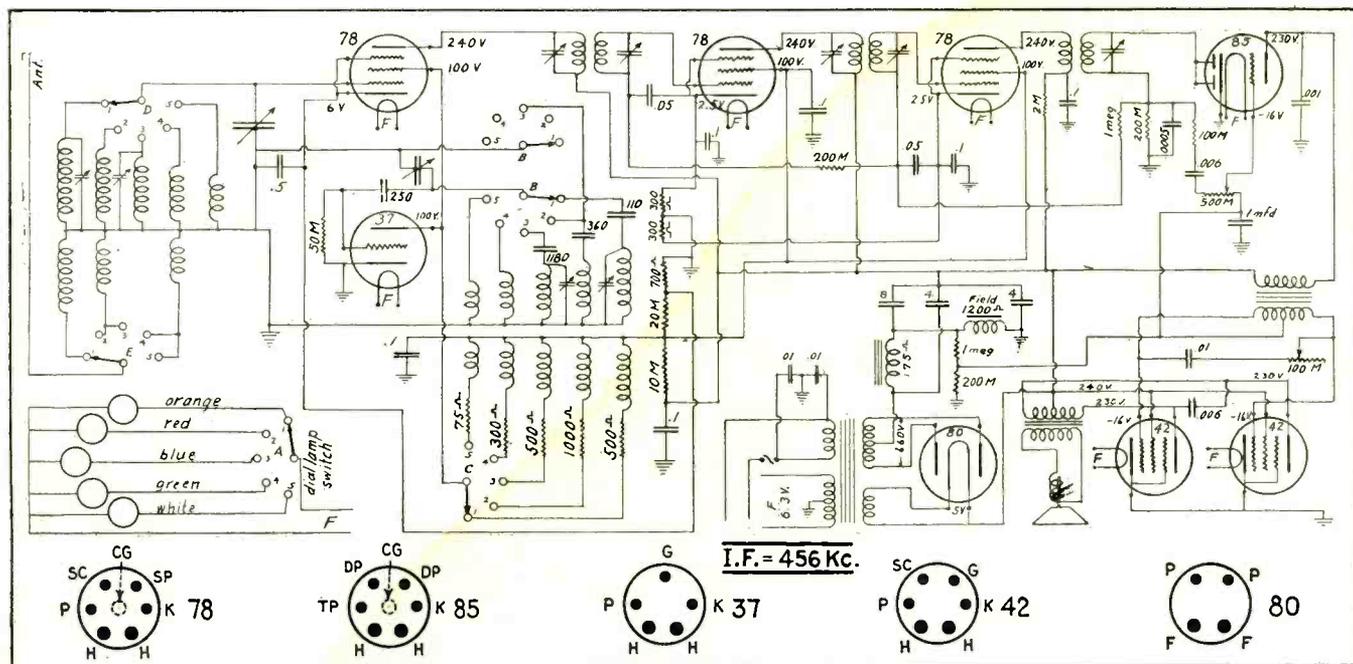The interchanging of the 1A6 with the 1C6 is recommended only in circuits where the ballast lamp or filament series resistor can be changed to accommodate the .120-ampere filament drain of the 1C6.



Complete circuit of the Knight (Allied Radio) Model W All-Wave Receiver.

Auto-Radio . . .

Philco Model 800

A new style i-f transformer, complete with padders, is used in the Model 800. The padders are placed in the top of the shield can one above the other.

The primary padder is adjusted by means of the screw slot, accessible through the hole in top of the shield can. The secondary padder is adjusted by means of the small hex nut, also accessible through the hole in top of the can. (See Fig. 2.)

The coil windings terminate in leads instead of terminal lugs. The plate lead is white; B plus, red; grid, black; and grid return, green.

THE CIRCUIT

A type 39 or 44 tube is used in the r-f stage. This is inductively and capacitively coupled to the 6A7 mixer-oscillator tube. There is one stage of i-f peaked at 260 kc, using a 39 or 44 tube, which feeds a type 75 diode-triode used as second detector, AVC and a-f. Resistors (32) and (33) are a part of the diode load circuit and the AVC lines leave at this point. Full control is placed on the r-f and mixer tubes, and partial control is placed on the i-f tube, through the connection from the midpoint of the two resistors just referred to. The volume-control potentiometer (30) really parallels resistors (32) and (33). A connection dot should be shown where the potentiometer lead crosses the lead from resistor (28) to resistor (32).

Make the change now before you forget it.

The 75 triode is resistance coupled to a 37 used as a driver for the type 79 Class B output tube. The tone control is in the plate circuit of the driver tube.

ADJUSTMENTS

It is essential that adjustments be made very carefully in this receiver. A good test oscillator must be used.



Remove the speaker lid from the receiver and disconnect the antenna. Then

remove the grid connection from the 6A7 tube. The location of this tube is given in Fig. 2.

Set up the oscillator and adjust it exactly to 260 kc. Connect the oscillator lead to the grid cap of the 6A7. The output meter must be connected by means of an adapter to the small prong of the speaker plug and to the chassis.

Set receiver volume control approximately full on and the attenuator on the oscillator at a point which gives a half-scale reading on the output meter.

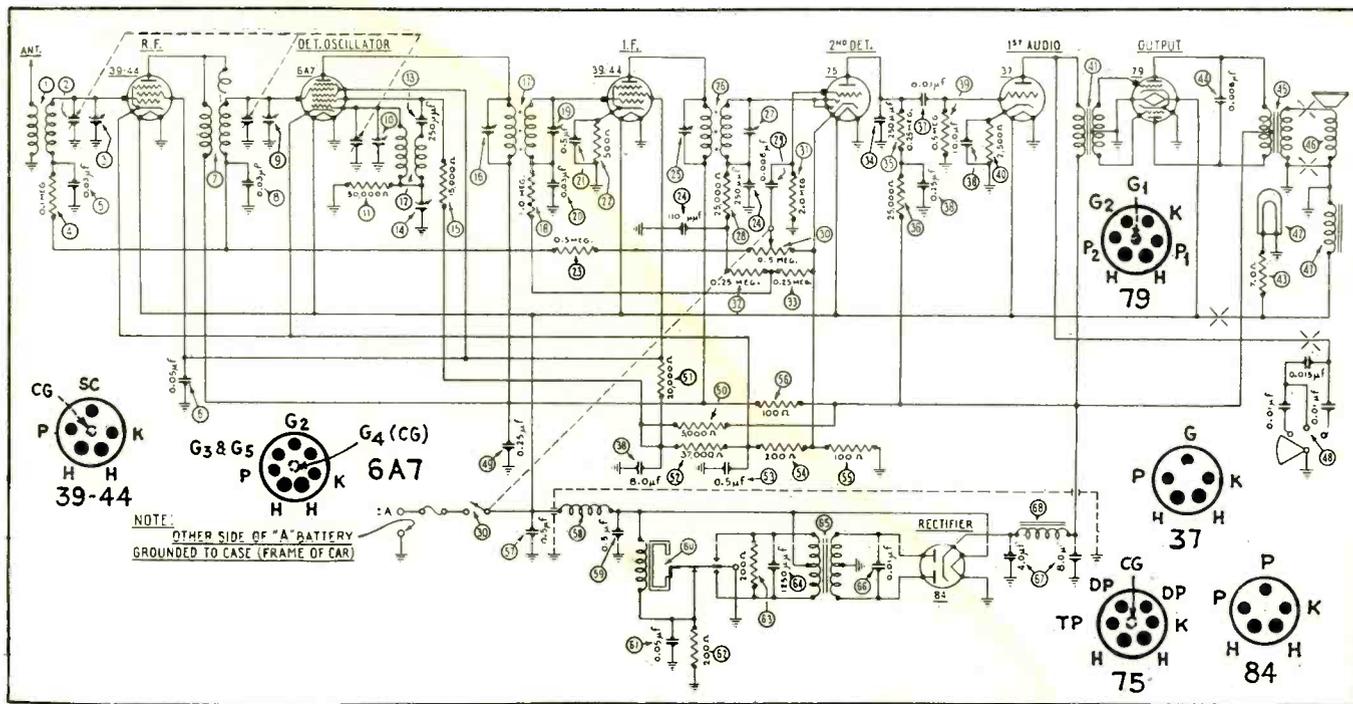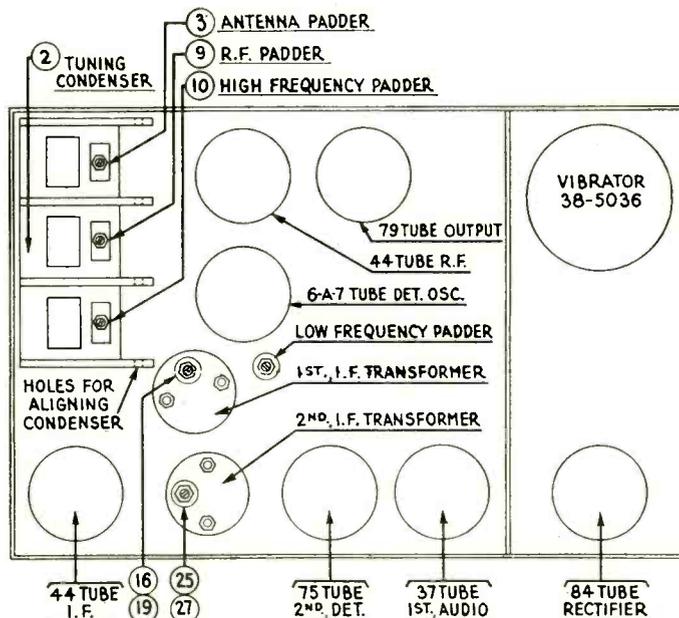The padders (25) and (27) are adjusted first (See Figs. 1 and 2). Turn the adjusting screw (25) all the way in. A metal screw driver can be used for this. Then, with oscillator attenuator set so there is approximately half-scale reading, adjust the nut (27) with a fibre



AUTO-RADIO—continued

wrench for maximum reading in output meter.

Then adjust the screw (25) for maxi-

mum reading. This adjustment is critical. Note the maximum reading obtainable and then turn the screw in again

and readjust, just bringing the adjustment up to the maximum reading. *Do not pass it and then back off.*

Repeat the above procedure with the condensers (16) and (19).

After padding the first i-f stage, remove the oscillator lead from the 6A7 and put back the grid connection on this tube. Also connect the antenna lead to the receiver. Set the oscillator at 1500 kc and then connect the oscillator lead to the antenna lead.

There are four holes in line, one in each of the sections of the tuning condenser housing (See Fig. 2). Place a nail of the size that fits snugly through the holes and then turn the condenser plates out of mesh until they strike against the nail.

With the tuning condenser in this position adjust the high-frequency padder (10) until the maximum reading is obtained. This is the true setting for 1500 kc, 150 on the dial scale.

Next turn the condenser plates in mesh to 140 on the scale (1400 kc), and set the oscillator at 1400 kc. The r-f padder (9) and the antenna padder (3) are next adjusted for the maximum reading.

Turn the condenser plates in mesh to 60 on the scale (600 kc), and readjust the oscillator to this frequency. Adjust the low-frequency padder (14) for maximum reading.

Majestic 66 Protection

The Majestic Model 66 auto radio must be carefully protected from moisture, or the set may become inoperative for no apparent reason. Moisture may leak in through the top of the set if the louvers in the cover point forward when the set is in position, or even when they are reversed, if the car in which the set is installed has a leaky cowl.

The moisture gets into the i-f trimmers, changing their capacity or shorting them outright; into the tuning condensers, shorting them; and around the tube prongs, causing a peculiar, moist substance to form, which shorts out any r-f energy which may get that far. This substance is similar in appearance to the copper sulphate which forms on storage batteries, but the writer has been unable to determine its composition. It must be removed, however, the set dried in a warm place overnight, and morning will find it as good as ever.

Attention should be given this matter in the case of convertibles and older model cars having cowl ventilators.

IRVING SEIDEMAN,
89-25 Parsons Blvd.,
Jamaica, L. I., N. Y.

AUTO-RECEIVER I-F PEAKS

Manufacturer	Model	I-F Peak
Air King Products Corp.	400, 500	175
All American Mohawk Corp.	U-50	485
All American Mohawk Corp.	U-500	456
American Television & Radio Corp.	Duo, 61	175
Arvin-Noblitt Sparks Industries	10-A	175
Arvin-Noblitt Sparks Industries	20-A, 30-A	182.5
Atwater Kent Manufacturing Co.	91, 91-B, 91-C	260
Atwater Kent Manufacturing Co.	424, 666, 816, 926, 936	264
Atwater Kent Manufacturing Co.	534	450
Atwater Kent Manufacturing Co.	636, 756, 756-B	262.5
Audiola Radio Co.	6, 7, A-6, S-6, S-7	177.5
Audiola Radio Co.	345	456
Autocrat Radio Co.	Dictator 5	456
Auto-Vox Radio Co.	75	175
Auto-Vox Radio Co.	80	262
Belmont Radio Corp.	660	175
Cadillac Motor Car Co.	06W, 072, 56V1	262
Car'uso-Laurehk Radio Mfg. Labs.	AE-79	175
Central Radio Corporation	560, 561	256
Central Radio Corporation	261	175
Crosley Radio Corporation	95, 96, 98, 99, 102, 103	181.5
Colonial Radio Corporation	150	480
Colonial Radio Corporation	106B, 164, 164B, 182, 182B	175
Delco Radio Corporation	3026	175
Dewald-Pierce Airo, Inc.	61	456
Dewald-Pierce Airo, Inc.	52	175
Electric Auto Lite Co.	062-A, 072-A, 3722	262
El Rey Radio Mfg. Co.	A, B, C,	465
Emerson Radio & Phonograph Corp.	678	172.5
Erla-Elect. Research Labs.	521	175
Erla-Elect. Research Labs.	601, 602, 5600, 6000	265
Erla-Elect. Research Labs.	4400	370
Fada Radio & Electric Corp.	101 (RK), 102, 104-B	175
Fada Radio & Electric Corp.	104	470
Franklin Radio Corp.	100, 102, 200	175
Freed Radio & Television Corp.	A-7, A-9	456
Gulbransen Company	362, V6Z2, 06-W, Z6Z1	262
Hoodwin Company, Charles	970	175
Jackson Bell Company, Ltd.	24, 205	456
Kayo Manufacturing Co.	Super 4	175
Kayo Manufacturing Co.	Super 5	262.5
Larkin Company	90, 91	175
Lyric, Rudolph Wurlitzer Mfg. Co.	A-60	485
Lyric, Rudolph Wurlitzer Mfg. Co.	460	175
Majestic-Grigsby Grunow Co.	66, 114, 116	175
Melburn Radio Mfg. Co.	40, 45, 50	465
Mission Bell Radio Co.	10-A, 19, 19-A	262
Montgomery Ward Co.	670	175
Motorola-Galvin Mfg. Co.	7-T-47-A, 61, 88	175
Motorola-Galvin Mfg. Co.	44, 55, 66, 77, 77A, 77B	456
Moto-Meter Gauge & Equipment Co.	10-A	175
Packard Radio Corp.	5, 46	470
Philco Radio & Television Corp.	5	460
Philco Radio & Television Corp.	7, 8, 12	175
Philco Radio & Television Corp.	6, 9, 10	260
RCA-Victor Company, Inc.	M30, M32, M34, M105, M116	175
Radio Chassis, Inc.	2, 5	175
Sparks Withington Company	33, 34	172.5
Stewart Radio Corporation	60	262
Stewart-Warner Corporation	R-112	456
Stromberg-Carlson Tele. Mfg. Co.	33	260
Stromberg-Carlson Tele. Mfg. Co.	(Compact Police)	175
Transformer Corporation of America	AR-100	465
United American Bosch Corporation	100, 150, 108 (Police)	175
United Motors (B O P)	2035, 4036, 4037	262
Wells-Gardner & Company	5V, 6V, 6U, 062, 6Z1, V6Z2, Z6Z4, 06-W	262
Wholesale Radio Service Co., Inc.	6-Tube Super	262
Zenith Radio Corporation	460, 461	485

—Courtesy Hygrade-Sylvania "Auto-Radio Installation and Servicing"

USING OSCILLATOR HARMONICS

THE table printed on this page is made up of the fundamental radio frequencies from 125 kc to 4500 kc and the harmonics of these frequencies through the seventh. This table may be used when it is desired to determine rapidly what fundamental frequency a test oscillator should be set at to provide a harmonic at some specific frequency not within the fundamental range of the oscillator. Or the process may be reversed: For example, suppose we wish to make an adjustment on an all-wave receiver at 9000 kc. A quick glance through the table will show that 9000 kc is the sixth harmonic of 1500 kc. Therefore, if the test oscillator is set at 1500 kc, its sixth harmonic may be used to make the receiver adjustment at 9000 kc. Now, suppose that the frequency desired is 9100 instead of 9000 kc. A glance at the table will show that 9100 kc is the seventh harmonic of 1300 kc. Therefore, if the test oscillator is set at 1300 kc, the seventh harmonic will be heard when the receiver adjustment hits 9100 kc.

CHECKING HARMONICS

If you will run through the table of figures you will find that the harmonics of some frequencies are very close to the harmonics of others. Thus, the second harmonic of 126 kc is only 2 kc away from the second harmonic of 125 kc. Also, as another example, the fourth harmonic of 2500 kc is also the fifth harmonic of 2000 kc, i. e., 10,000 kc. It is seen, therefore, that errors can be made if the oscillator is not well calibrated, or an error may be made through confusion of harmonics. The accompanying table is handy in this respect, too, as it indicates where errors could well be made.

Here is a way to check the harmonic: Suppose we wished to check an all-wave or short-wave receiver at 12,000 kc. First set the test oscillator at 2000 kc and the receiver at 4000 kc. When the receiver reaches 4000 kc the second harmonic of the test oscillator will be picked up. It would be pretty hard to go wrong on this. Now tune the receiver to 12,000 kc, at which point the sixth harmonic of the 2000-kc test oscillator signal will be heard. Now, by leaving the receiver adjustment as it is and re-setting the test oscillator to 3000 kc we can check the latter harmonic, for at the 3000-kc setting we should again hear the oscillator note because 12,000 kc is the third harmonic of 3000

as well as being the sixth harmonic of 2000 kc. A further check can be made at 4000 kc, for 12,000 kc is the third harmonic of this frequency. This pro-

cedure insures us that we were using the correct harmonic so that the test oscillator may then be set again at 2000 kc and the receiver adjustment made.

Fundamental Frequency	Harmonics					
	2nd	3rd	4th	5th	6th	7th
125	250	375	500	625	750	875
126	252	378	504	630	756	882
127	254	381	508	635	762	889
128	256	384	512	640	768	896
129	258	387	516	645	774	903
130	260	390	520	650	780	910
131	262	393	524	655	786	917
132	264	396	528	660	792	924
133	266	399	532	665	798	931
134	268	402	536	670	804	938
135	270	405	540	675	810	945
170	340	510	680	850	1020	1190
171	342	513	684	855	1026	1197
172	344	516	688	860	1032	1204
173	346	519	692	865	1038	1211
174	348	522	696	870	1044	1218
175	350	525	700	875	1050	1225
176	352	528	704	880	1056	1232
177	354	531	708	885	1062	1239
178	356	534	712	890	1068	1246
179	358	537	716	895	1074	1253
180	360	540	720	900	1080	1260
200	400	600	800	1000	1200	1400
220	440	660	880	1100	1320	1540
240	480	720	960	1200	1440	1680
260	520	780	1040	1300	1560	1820
261	522	783	1044	1305	1566	1827
262	524	786	1048	1310	1572	1834
263	526	789	1052	1315	1578	1841
264	528	792	1056	1320	1584	1848
265	530	795	1060	1325	1590	1855
280	560	840	1120	1400	1680	1960
320	640	960	1280	1600	1920	2240
350	700	1050	1400	1750	2100	2450
400	800	1200	1600	2000	2400	2800
450	900	1350	1800	2250	2700	3150
500	1000	1500	2000	2500	3000	3500
550	1100	1650	2200	2750	3300	3850
600	1200	1800	2400	3000	3600	4200
650	1300	1950	2600	3250	3900	4550
700	1400	2100	2800	3500	4200	4900
750	1500	2250	3000	3750	4500	5250
800	1600	2400	3200	4000	4800	5600
850	1700	2550	3400	4250	5100	5950
900	1800	2700	3600	4500	5400	6300
950	1900	2850	3800	4750	5700	6650
1000	2000	3000	4000	5000	6000	7000
1100	2200	3300	4400	5500	6600	7700
1200	2400	3600	4800	6000	7200	8400
1300	2600	3900	5200	6500	7800	9100
1400	2800	4200	5600	7000	8400	9800
1500	3000	4500	6000	7500	9000	10500
2000	4000	6000	8000	10000	12000	14000
2500	5000	7500	10000	12500	15000	17500
3000	6000	9000	12000	15000	18000	21000
3500	7000	10500	14000	17500	21000	24500
4000	8000	12000	16000	20000	24000	28000
4500	9000	13500	18000	22500	27000	31500

ON THE JOB . . .

UNIVERSAL FEEDER CIRCUIT FOR DYNAMIC SPEAKERS

It is quite often found impractical to run four lines to supply the voice-coils and fields of remotely located loudspeakers. It is possible, by the use of the circuit shown, to use only two lines and send the d-c and a-c over the same line without producing interference. This is accomplished by merely putting in two 1-mfd condensers as shown, the condensers naturally not permitting the d-c to pass. Hence both the d-c field-excitation current and the a-c voice-coil current can be made to pass over the same line. Such a system is well adapted up to distances of 2000 feet, but it is necessary, of course, to take the line drop, resistance, and the like, into consideration at such distances.

In the accompanying diagram, the output-to-line transformer, T-1, has 400 ohms on the output side. The line-to-speaker transformer, T-2, has 400 ohms on the line side and 15 ohms on the speaker side. In series with both transformers are 1-mfd condensers which limit the d-c excitation to the resistor and field circuits. The resistor is variable from 0 to 250,000 ohms and is across a 500-ohm line. This resistor naturally gives any value to the field excitation current that may be desired, with a similar effect upon the amount of a-c flowing through T-2. Other values may be substituted when necessary or desirable.

BERNARD EPHRAIM,
Repres, Calif.

Testing Rectifier Tubes

It is an advisable precaution, when testing a customer's tubes, to pay somewhat more than normal attention to the rectifier tube, for failure of the rectifier tube can, and sometimes does, cause damage to the set. After testing the rectifier for plate current, it is well to

inspect the stem to determine whether any marked amount of electrolysis has taken place.

ELECTROLYSIS

Electrolysis is defined as the chemical decomposition of a substance due to an electric current. Through the glass stem tubing of the rectifier tube pass the plate and filament leads. The spacing between these leads is relatively small; the stem temperature during operation is high and the potential difference existing between the leads is large. All three of the above conditions cause electrolysis to a greater or less degree.

This electrolysis manifests itself as a black growth on the plate lead, or leads, in a rectifier where these leads pass through the glass stem. This black growth is evidence of a decomposition of the glass in the stem and when it has progressed sufficiently far, an arc may occur between the plate and the filament, or it may impair the stem to such an extent that air is admitted to the tube through a microscopic leak. If an arc occurs between the plate and the filament, and the radio set is unprotected by a fuse, there is quite a possibility that the power transformer will be burned out. It is for this reason that one should, when testing tubes, pay particular attention to the rectifier and see that the tube is replaced before electrolysis has progressed to such a point that it may soon damage the receiver.

DEGREE OF DEPOSIT

As stated above, the evidence of electrolysis is found in the black growth surrounding the plate lead. Inspection of a new tube will reveal that, while the surface of the glass stem may be blackened to some extent, still, the point where the lead wires go through the glass stem will usually be clear, or at least, milky in appearance. Inspection

of a rectifier tube, which has been used for 1000 hours, or so, in a radio receiver, will readily reveal that surrounding the plate lead wires in the stem is a black deposit. It is impossible to lay down a hard and fast rule as to just how large this deposit may safely be before the tube should be thrown away, but the degree of blackening permissible should probably not be greater than the diameter of the lead wire.

Airline No. 62-20

When an Airline No. 62-20 seven-tube superheterodyne receiver was turned on, with the manual volume control turned to the lowest position, any station came in with full volume for a minute or so, and since the set was used in a hotel it became quite bothersome. Since the manual volume control affects the control grid of the AVC tube, the trouble was remedied by putting in a quicker heating 24-A (AVC) tube.

REALIGNING SUPERS

In realigning superheterodynes at the high frequency end of the dial (around 1400 kc), which use one stage or one tube as AVC and 2nd detector, or for that matter whatever the combination may be, always keep the signal from the external oscillator very low in order to keep below the AVC action in the set. A much sharper and more accurate peak can be obtained in this way.

CHEVROLET MOTOR CAR SETS

I have had about 18 Chevrolet car sets, Model 364441 (United Motors), in which the vibrator failed. Most of these were in use around 4 months.

To correct, remove chassis and then remove vibrator points. Use a thin carborundum stone to dress up the points, and adjust them very close to the center points.


J. M. OSENTON,
Osenton's Radio Service,

Peerless 65 and K-65

Peerless Courier 65 and K-65 (United Reproducers Corp.). Trouble with plate bypass condensers. They should be replaced with 400-volt, 0.1-mfd condensers.

Recently increased the volume of a number of these sets by shorting out the portion of the voltage divider between r-f plate lead (red) and first a-f plate lead (yellow), then changing first a-f bias resistor to 1500 ohms, and detector bias resistor to 25,000 ohms.

S. F. PUSEY,
Madera, Pa.

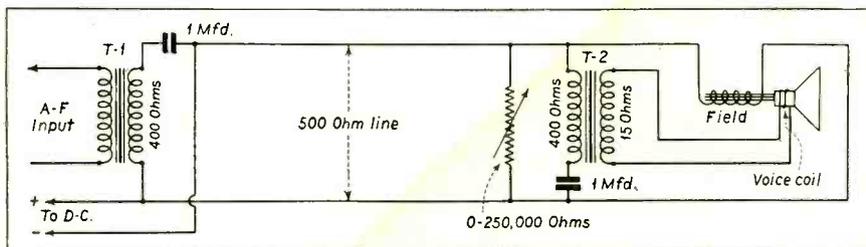

Circuit arrangement which permits the feeding of signal and power to a dynamic speaker over a single pair cable.

Public Address . . .

"PUBLIC-ADDRESS" FOR THE SERVICE MAN

• The second of a series of three articles on the sale, rental and use of public-address equipment. The present article deals with outdoor equipment of the mobile type and includes the technical data on a storage-battery-operated job with 15 watts output.

By Frank Lester*

IN the outdoor public-address field more than in the indoor field, aggressiveness is a prime requisite. The wise Service Man with an eye for business will read his local newspaper and the newspapers of surrounding towns very carefully, and will clip out all items referring to carnivals, circuses, American Legion gatherings, fairs, auto races, organization picnics or outings, church festivals, swimming meets, beauty and baby parades, and even outdoor weddings. The two theatrical magazines, "Variety" and "The Billboard," copies of which can be picked up at most railroad stations, should also be consulted. If you expect to sell or rent P-A outfits for outdoor work, you've got to know who and where your prospective customers are.

Many traveling road shows carry their own P-A stuff, so perhaps it is best to stick to your own territory. Write, telephone or visit the commander of the Legion post, or the chairman of the entertainment committee of the fraternal lodge, or the promoter of the auto race or parade, as far in advance of the date of the affair as possible, and tell him what you have to offer. A P-A system invariably makes a big hit at affairs of this kind, as the neighborhood clown gets a chance to perform, the community Lily Pons does a little yodeling, the local politician does a little electioneering, and everybody has a good time.

RENTAL BUSINESS

Of course, the possibility of selling P-A units for work of this kind is pretty remote. The "gravy" is renting them for the occasion at a lump sum. Fees of \$10 to \$25 per day are pretty easy to get, as this money represents only a small part of the total cost of most outdoor shows of various kinds. Figuring a complete outfit to cost about \$150 (including amplifier, mike, controls, two speakers and phonograph turntable), a live-wire Service Man should be able to clear the entire in-

vestment between May and October, and from then on all income, less comparatively small deductions for maintenance, is pure profit. There is no reason why the sales effort should be relaxed even during the winter, for ice skating contests are highly popular in many sections of the country and draw large crowds.

PORTABLE P-A OUTFITS

When I speak of "portable P-A outfits," I refer exclusively to 6-volt storage-battery-operated units. Formerly the orphans of the sound business, portable amplifiers have today reached a rather high degree of perfection, thanks to the introduction of versatile, low-drain tubes, the development of high-gain, high-power, Class "B" circuits and the availability of economical high-voltage dynamotors. Rack and panel amplifiers and tons of expensive "B" batteries, once required for the purpose, are no longer needed for outdoor service. A 15-watt amplifier, with self-contained plate generator, can now be obtained in the form of a single unit so small it can be hung under the dashboard of a light passenger car! And if

you don't think 15 watts of audio signal is a lot of signal, you should be near the speakers with the gain control all the way up!

With compact, efficient amplifiers of this kind, the problem of transportation presents no difficulties at all. A complete P-A outfit can be loaded into most any coach, sedan or touring car, or even a rented horse-drawn wagon, if the Service Man has no car of his own. Of course, it is important to have a husky, fully-charged battery at the start of a day's work; some men even carry a spare. If the regular car battery is of respectable size, there is no reason why it cannot be used, as the total current drain of the typical amplifier mentioned is only about 11 amperes.


As batteries are pretty cheap, it is a good idea to have a separate 120-hour unit for the amplifier, and the car battery can then be used in a pinch if the amplifier must be operated for more than a whole day. This is not likely, but it pays to be prepared.

PRECAUTIONS

If you get the P-A job for a picnic or any other outdoor affair, be sure to look the grounds over before you drag out any equipment. In some cases, it is possible to leave all the apparatus in the car, parked near the speaker's stand or headquarter's tent, and to run the mike and speaker wires out from it. Some protection for the amplifier and its accessories must be provided, otherwise it will disappear piece by piece in the hands of souvenir collectors. Keep an especially wary eye on the microphone, as this is a great attraction for people who have never before seen one close up.

For a crowd of several hundred people, one or two speakers is sufficient.

(Continued on page 192)

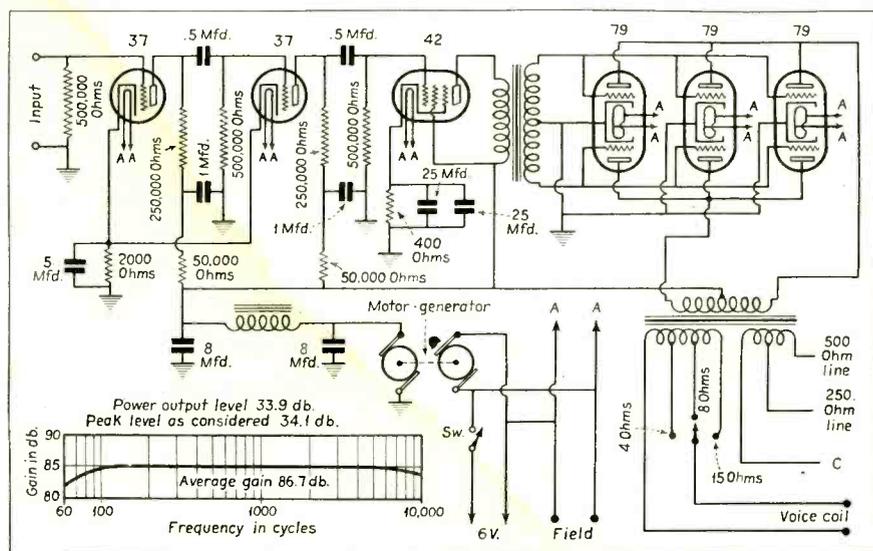

Circuit and frequency curve of a storage-battery-operated Class B amplifier.

*Engineer, Wholesale Radio Service Co., Inc.

HIGHLIGHTS...

Service-Man's Notebook

Who can move these days without realizing that 1934 has reached the spring of its life and is budding profusely on all sides? We noticed it recently, and decided on the spot that since everything else seemed to be filled with new life—including business—that SERVICE should be touched by the fingers of spring, too. So—we finally decided to start a new department, the idea for which has been fermenting in the cask of our brain ever since repeal.

Well, the new department is here, and we've named it the "Service-Man's Notebook."

For the present at least this new department will be confined to a single page, and will include only such items as tables, graphs and calculations which we believe of special value to the Service Man. We have a number of items lined up for forthcoming issues, but are plenty open to suggestions. Maybe you have something in mind which you would wish to have tabulated, graphed or otherwise fingerprinted for quick survey. Something like a wavelength-frequency chart, or a graph for the quick calculation of the value of resistors in parallel. Or what?

If you don't let us know what you want, we'll go our own way and may end up by running dope on how to make your own wine—which wouldn't be so bad, but a bit out of place.

Rider Manual Volume IV

Another addition has been made to the Rider's Manual series. Volume IV made its appearance during the last week in March.

Volume IV picks up where Volume III left off. From reports furnished by the publisher, the new Rider Manual includes schematics and service data covering radio receivers issued as late as February, 1934.

The complete manual, inclusive of a Special Section, totals about 1060 pages. Of special interest is a section of about 24 pages which is devoted to explanations of the path of the signal currents found in some of the highly complicated receivers listed in Volume IV. No doubt Rider realized the need for explanations covering the operation of some of these special circuits. Some of the items mentioned in this Special Section to Volume IV are: Automatic sensitivity control; automatic tone control; delayed AVC; duo-diodes, triodes and pentodes; phase changer tubes; QAVC; reflexed pentodes; various flasher systems, etc.

The index accompanying Volume IV is also unique. It is a separate printed volume of about 40 pages. (In time to come the index will be as voluminous as the manuals themselves!) Of particular interest is the fact that this index covers all of the Rider Manuals ever issued, inclusive of the early Volumes I and II sold by the publisher and also distributed by National Union in connection with tube deals, and also the RCA Radiotron-Cunningham "Combination Rider Manual," which contained Volumes I, II and III.

The revised Volumes I and II and all of the Volumes III and IV sold by the publisher or disposed of by some of the tube companies in connection with tube deals are indexed in this single complete index.

As is to be expected, Rider made every effort to present the most complete picture and there are about 135 manufacturers and trade names listed in Volume IV. The addition of this volume to the previously issued Volumes I, II and III makes a total of about 4,000 pages in Rider's Manual.

Sylvania Auto-Radio Book

Hygrade Sylvania Corporation, Emporium, Pa., have on the presses the new "Auto-Radio Installation and Servicing" manual—and by the time you read this it will probably be ready for distribution.

We have before us as we write the complete page proofs of this manual, and it is undoubtedly the best and most complete compilation of auto-radio data we have so far run across.

The book opens with a number of pages on general engineering information on the calculation of resistor and condenser values. These pages are followed by installation notes on receivers and antennas, with antenna top construction data, and a lengthy treatise on the suppression of ignition interference.

The long chapter on service hints should prove of great value. The hints refer to makes of receivers and the listing is alphabetical. This is followed by further hints listed alphabetically by makes of cars. More hints are given under special headings, such as installation, interference suppressors, power-supply units, tubes and parts, and tube requirements for all makes of receivers. A table is also included, showing which auto-radio tubes are interchangeable.

In the back of the book are tables listing the characteristics of all Sylvania auto-radio tubes, and their base connections.

A copy of this book may be obtained free of charge by writing to Hygrade Sylvania. It's well worth having.

Short Wave Handbook

Standard Publications, Inc., 1123 Broadway, New York, N. Y. (the publishers of the excellent magazine, "Short Wave Radio") have brought out the "Short Wave Radio Handbook," by Clifford E. Denton. There are 122 actual pages of text and tables, and one of the nice things about the book is that there is no introductory section telling how a magnet works and showing you a picture of the thing to convince you of the fact.

The book is primarily intended for the short-wave experimenter who likes to roll his own, but there is so much data on tube applications, coil winding data, simple formulas, etc., that it should also appeal to the Service Man.

The book also contains constructional data on short-wave t-r-f and superheterodyne receivers, converters, super-regenerative receivers, single-signal sets, power-supply units, an i-f oscillator, short-wave oscillators, etc.

\$1 for March SERVICE

Copies of SERVICE prior to December, 1934, are scarcer than hen's teeth. Mr. H. A. Shannon, of Shannon Radio Service, Mount Vernon, New York, is a nervous wreck from trying to hunt down a copy of the March, 1932, issue. Now he gives up, and will be glad to pay anyone a dollar for one of these copies.

Who wants to make a dollar? Well, write Mr. Shannon.

"Unit-Matched" P-A.

The Operadio Manufacturing Co., St. Charles, Ill., subscribe to the old belief that when you buy a new suit, by rights the pants ought to match the coat and the vest. We think so too . . . that is, if you're not an Englishman.

With this logical premise in hand, they also figured that if a fellow is going to buy public-address equipment, by rights all the units ought to match up if the thing is to work the way it should.

Thereupon they worked out various types of amplifiers, microphones, pickups, control units and speakers which, when used with the right units will work at maximum efficiency. Thus, no headaches or dissatisfied customers.

Operadio has a bulletin on this new idea, titled "A Sound Argument." Copies may be had free upon request.

New Cornell-Dubilier Catalog

Cornell-Dubilier Corporation, 4377 Bronx Boulevard, New York, have just issued Catalog No. 125 which is available to the trade free of charge. This catalog is especially for the Service Man and is replete with information regarding the most common and popular types of electrolytic, paper and mica condensers used in all types of radio receivers, auto-radios, a-c, d-c midgets, large consoles and all-wave sets.

New Kenyon Catalog

Kenyon Transformer Co., Inc., has just released their new Spring catalog.

It is somewhat changed in form from earlier issues, as it appears in two parts. The Laboratory Standard, the Portable, the Transmitting, and the All-Purpose lines appear in one catalog of twenty pages, and these are presented with full detailed information in tabular form. The Replacement line is covered in a separate eight-page folder and contains many new items, both in the power transformers and audio line.

Copies may be procured through your local dealer, or directly.

Trouble Manual

The Servicemen's Publishing Co., 136 Liberty St., New York, N. Y., have brought out a nice husky pocket manual (which will really fit the pocket) called "Actual Troubles in Commercial Radio Receivers." There are 173 pages of notes on characteristic troubles and cures gained through the experience of Mr. Bertram M. Freed who has worked for large dealer-service companies. The book opens with "Amrad" and closes with "Zenith." It's quite complete, and should be of value to the Service Man who can't waste too much time with Jonah's.

Compact "All-Waver"

The Freed Television and Radio Corp. has the only All-Wave "Midget" receiver we have ever seen. It's the Model 366 SW, and covers the complete band from 15 to 560 meters.


The set is designed for operation on 110/120 volts a-c, and uses a 6D6, two 78's, a 77, a 42 and an 80.

AUTO-RADIO PROBLEMS

simplified

New **SYLVANIA** Service Book reveals short-cuts on 29 different counts!

TABLE OF CONTENTS		Page
FOREWORD		3-4
GENERAL ENGINEERING INFORMATION		5-7
INSTALLATION:		8
Introduction		8
Automobile Battery Grounds		8-9
Antenna Installation		10-14
Top Construction		10-14
Slat		10-11
Fabric		11
Poultry Wire		11-12
Metal Braced		12
Folding		12-13
Running Board and Under-Car		13
Automobile Antenna Equipment		14
INTERFERENCE SUPPRESSION:		
Primary Methods		15-16
Secondary Methods		17
Chassis Pick-up		17-20
Antenna Pick-up		20-21
Static Discharges		21-22
Summary		22-23
SERVICE HINTS:		
By Makes of Receivers		24-33
By Makes of Cars		34-37
I. F. Peak Frequencies		38-39
MISCELLANEOUS INFORMATION:		
Installation Hints		40-42
Interference Suppression		42-45
Power Supply Units		45-47
Receiver Hints (General)		47-48
Tubes and Parts		49-51
TUBES:		
Tube Requirements for Auto-Radios		52-59
Interchangeable Auto-Radio Tube Types		60-61
Characteristics of Tubes for Auto-Radios		62
Tube and Base Diagrams		63

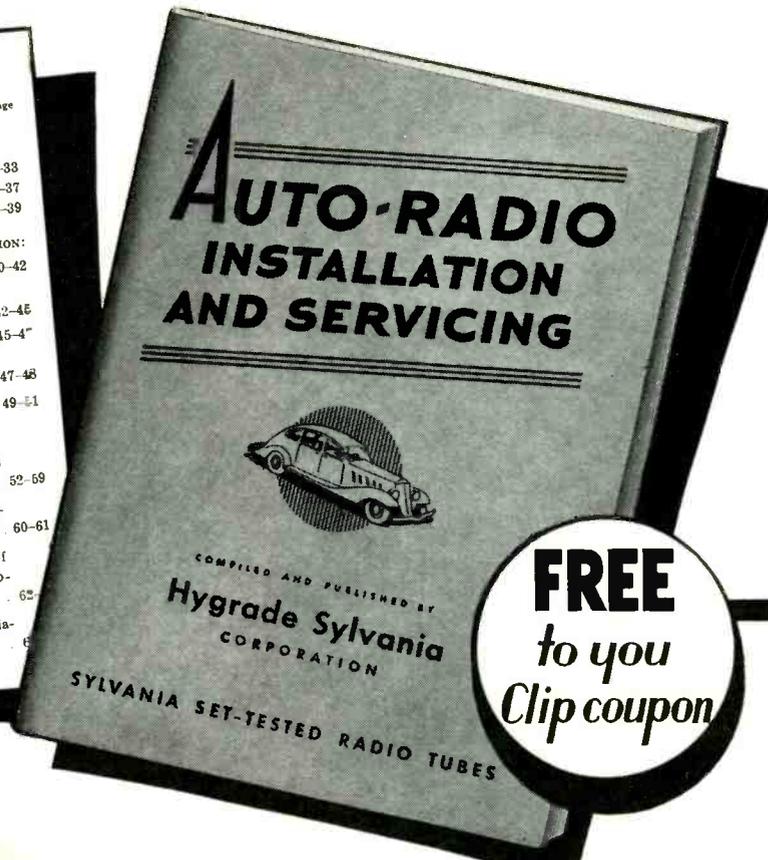

● Now Sylvania engineers have prepared a reference book devoted solely to auto-radio. This handy pocket manual, written in the service man's terms, contains tested information on suppression of ignition interference, tells which pole of the storage battery is grounded, what car makes and models have antenna installed at the factory . . . and answers other problems you will meet in auto-radio installation and servicing.

Send for your free copy of this new book that will help to put you in on the ground floor of the fast-growing auto-radio industry—a worthwhile business in itself, when you realize that 724,000 sets were sold in 1933, and it is estimated that 1,000,000 sets will be installed in 1934! Sylvania engineers themselves, with their development of the 6.3 volt tube, are responsible to a large extent for the advance of auto-radio. HYGRADE SYLVANIA CORPORATION.

Sylvania
REGISTERED U. S. PAT. OFF.
 THE SET-TESTED RADIO TUBE

Makers of
 Sylvania Tubes
 Hygrade Lamps
 Electronic Devices

Factories
 Emporium, Pa.
 St. Mary's, Pa.
 Salem, Mass.
 Clifton, N. J. © 1934. H. S. C.


HYGRADE SYLVANIA CORPORATION C-12 
 Emporium, Pa.
 Please send free, without obligation, your new service book, "Auto-Radio Installation and Servicing".

Name.....
 Address.....
 City..... State.....

(Continued from page 189)

For convenience in connection, try to keep them on top of the car, or on poles or trees close by. For most temporary set-ups it rarely is necessary to extend the speaker leads any distance. A little experimenting with the speakers in relation to the microphone will quickly determine the best set-up for freedom from howling due to acoustic feedback.

A phonograph turntable and a plentiful supply of records are essential. Incidentally, make sure to include a record of the National Anthem. This is particularly important for semi-military and patriotic organization affairs. Let the chairman or the head of the affair know what your record stock consists of, and try to work out a definite program in advance. Careful arrangement of the musical part of the program will do much to make the event a success. Also determine who is or is not to be allowed the use of the microphone.

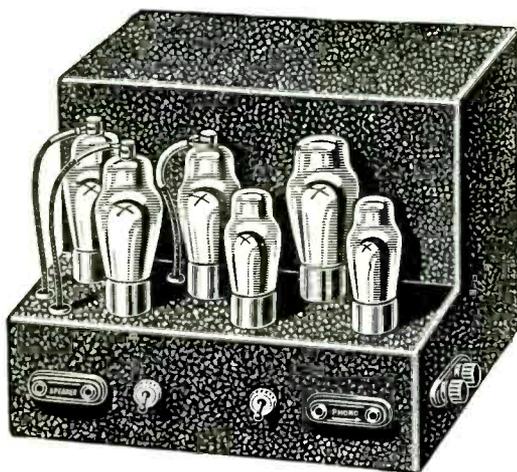

The chassis of the storage-battery-operated Class B amplifier, the circuit of which is shown on page 189. This unit employs three type 79 tubes in the output. These are connected in parallel and operated push-push.

Everybody will want a chance at it, and unless some person of authority lays down the law, the mike will be assailed by giggling sopranos, boy orators, would-be crooners and so on.

COLLECTING FEES

One important little detail must not be overlooked, and that is the matter of collecting for your services. First agree with the promoters of an affair as to your fee (don't be afraid to ask for plenty; you can always come down a little, and then your customer will think he has done his organization a good turn), and then determine when and how you are to be paid. Demand at least half of your fee in advance, the balance to be paid before or immediately at the close of the affair. If you think you can demand it, try and get the whole sum in advance. Many social and fraternal affairs start out with a big splash and end up with a deficit, so

don't depend on promises. If you don't collect immediately you will invariably be out of luck later. Many a well-meaning club secretary says, "Oh, you'll be paid just as soon as we tally up the receipts," but if the receipts don't cover the beer and the hot dogs, and if you didn't get a deposit in advance, you're likely to go home with a dead battery, a feeling of chagrin, and a lot of apologies.

TYPICAL SIX-VOLT AMPLIFIER

The Service Man with suitable equipment at his disposal can undertake any ordinary outdoor P-A job with complete confidence. Six-volt amplifiers are now as dependable as any a-c jobs, and really more economical than many of them. An excellent example of present-day trends in this direction is a 6-volt mobile amplifier, which has a 15-watt output rating (17 watts peak) and a self-contained "B" supply in the form

sists of six tubes. Their elements are connected in parallel to provide the equivalent of three tubes in half of the stage. The unusual method of connection is responsible not only for the 15-watt output, but also for remarkably clear amplification, the wave-form distortion being only 7 per cent. This figure was not merely calculated, but was measured by means of a cathode-ray oscillograph.

Two input posts, connecting directly to the grid-cathode circuit of the first 37 tube through a half-megohm resistor, are provided. When a regular double-button microphone is to be employed, the use of a small control box containing a suitable coupling transformer and gain control is recommended. A high-impedance phonograph pick-up may, of course, be connected directly to the input posts on the amplifier.

An unusually large and heavy universal output transformer is contained in the amplifier. This has two secondaries; one, with 250- and 500-ohm windings, is for transmission line work; the other, with 4-, 8- and 15-ohm windings, is for direct connection to loud-speaker voice coils. The three sections of the latter secondary are instantly available, being selected by a three-position switch on the front of the amplifier chassis.

THE DYNAMOTOR

The plate dynamotor, which is enclosed in an upright compartment behind the tube lineup, is equipped with a two-section filter consisting of a 15-henry choke coil and two 8-mfd condensers. The six-volt side is controlled by a snap switch which also controls the current to the field windings of the speakers used with the amplifier.

In connection with the use of outdoor P-A amplifiers in general, the writer wishes to emphasize the importance of using trumpets. It is highly inadvisable to use ordinary dynamic speakers, as they scatter the sound too much and cause considerable acoustic feed-back trouble. Trumpets concentrate the sound in the area where it is needed most.

(To be continued)


Type 42 and 2A5 Tubes

There has been some question as to the interchangeability of the type 42 and 2A5 tubes. Both types have exactly the same characteristics with the exception of the heater voltage. Therefore, any amplifier using one type may equally as well use the other providing the heater voltage is altered.

of a highly reliable dynamotor, and yet which is actually smaller than the standard 120 ampere-hour storage battery with which it is intended to operate. The steel chassis measures overall only 14 $\frac{5}{8}$ inches wide, 8 $\frac{1}{2}$ inches deep and 10 $\frac{1}{2}$ inches high, and contains, in addition to the plate dynamotor, a complete four-stage amplifier using three type 79's, two 37's and one 42. These tubes are of the 6.3-volt automobile class, and are known for their great ruggedness.

CLASS B AMPLIFIER CIRCUIT

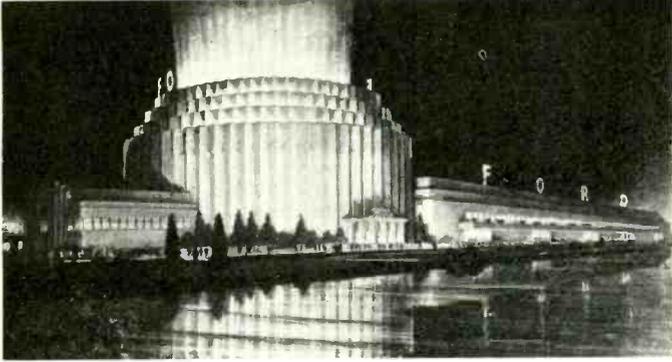The accompanying schematic diagram shows the circuit arrangement of this amplifier. A 37 feeds another 37, which in turn works into a 42, resistance-capacity coupling being employed. The 42 is transformer coupled into a push-pull output stage comprising three type 79's. The 79 is a double triode in one envelope, so the output stage really con-



SOUND AMPLIFICATION BY WEBSTER-CHICAGO

To you service men who read this advertisement and think of it in terms of the sound amplification equipment you are going to sell, which you should, it may seem like a long haul from the equipment necessary for a \$1,500,000 Exposition Building to the little 3 tube Amplifier.

In a way it is, but the most outstanding thing about it is that it places in your hands the kind of selling talk you may need most in securing whatever job of sound amplification you're after. To be able to point out that the unit you are going to use in providing sound amplification for the smallest hall is the same kind as that selected by the most exacting group of engineers possible to get together, is a whale of a sales argument.

For this little 3 tube WEBSTER-Chicago Amplifier is made with the same exacting, laboratory-controlled production methods; the same sound engineering practice that produces installations for great Exposition Halls.



THREE TUBE AMPLIFIER
Type SA-2, for general purpose public address systems of small and medium size requirements. Complete with 8" Dynamic Speaker; 4 ft. cord with plug and 6 ft. power cord.

And, this same little 3 tube job should make it more certain than ever before that you can get into this most profitable business of Sound Amplification or Public Address, whichever you prefer to call it, in a big way . . . with little money and the certainty of making such satisfactory installations that your business will grow and prosper.


Let us send you the Webster Catalog and supplementary bulletins of the finest Permanent; Portable; large and small Sound Amplification units possible to buy.

**THE
WEBSTER
COMPANY**
CHICAGO
U. S. A.

3827 WEST LAKE STREET

MAY, 1934 •

SAY YOU SAW IT IN SERVICE

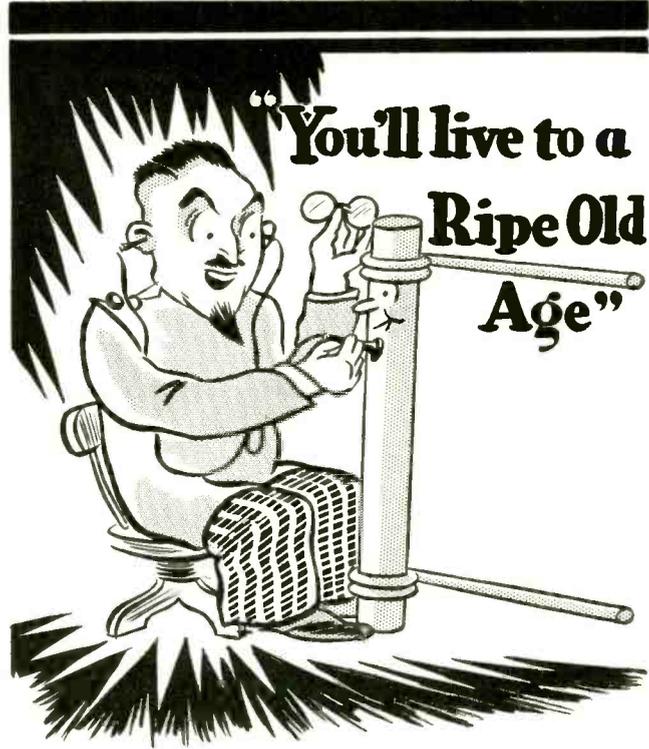

Nothin' wrong with this boy. If you ask us he's a tough hombre . . . he ought to be . . . for he was "Baptized with Fire" at 2700 degrees and he's vibration proof, heat proof and moisture proof.

On that next replacement job try a CENTRALAB FIXED RESISTOR and note the difference. Good business too . . . for the customer won't be coming back with a squawk.

At your jobber. . . .

Every Radio Service Man
should be a member of the
Institute of Radio Service Men

Centralab RESISTORS

CENTRAL RADIO LABORATORIES
MILWAUKEE, WISCONSIN

ASSOCIATION NEWS . . .

R. T. A. (San Francisco)

We have just received the first printed issue of the R. T. A. News, put out by the Radio Technicians' Association of San Francisco. It looks like real business, and reads like it, too.

The gang out there made a special trip to the RCA Communications station, at Bolinas, California, on Sunday, February 18th. We think one of the fellows thought the tape in the automatic transmitter gave stock quotations, and tried reading it. We were listening to Bolinas on the eighteenth and the "ditter" had hysterics, to say nothing of the transmissions.

Who was the guy breaking the tape? Or was that KEE sending a program to Koko Head?

I. R. S. M. Additions

Listed below are the new I. R. S. M. Sections and Chapters recently formed, and with the names and addresses of the recently elected officers.

BALTIMORE SECTION

Albert O. Rabassa, Chairman, 2920 East Baltimore, St., Baltimore, Md.

F. J. Weipert, Secretary, 408 Calvin Ave., Baltimore, Md.

CEDAR RAPIDS SECTION

Donald Anderson, Paramount Radio Shop, 1232 5th Ave., S. E., Cedar Rapids, Iowa.

CHICAGO SECTION

Chas. K. Failing, 3336 N. Oak Park Ave., Chicago, Ill.

Russell V. O'Byrne, Secretary, 7134 Ridgeland Ave., Chicago, Ill.

LAKE COUNTY CHAPTER

Martin J. Findling, Chairman, 426 Clinton St., Hammond, Ind.

Mike Jancik, Sec'y.-Treas., 4245 Johnson St., Hammond, Ind.

COLORADO SPRINGS CHAPTER

Francis M. Harvey, 15½ E. Pikes Peak Ave., Colorado Springs, Colo.

DENVER SECTION

Wyman C. McKelvy, Sec'y., Federal Radio & Service Shop, 3022 W. 38th Ave., Denver, Colo.

KANSAS CITY SECTION

P. N. Connet, Chairman, 4053 Broadway, Kansas City, Mo.

Fred M. Myers, Secretary, 7439 Lydia, Kansas City, Mo.

LOUISVILLE SECTION

Wallace M. Smith, Chairman, 2304 Wrocklage Ave., Louisville, Ky.

Allan W. Panke, Secretary, 2205 W. Ormsby Ave., Louisville, Ky.

MIDWEST SECTION

Ralph W. Pitt, 543 S. Douglas Ave., Belleville, Ill.

MILWAUKEE SECTION

Cedric E. Heller, Chairman, R. R. No. 2, Nashotah, Wis.

Wm. E. Hough, Secretary, 1854 N. 27th St., Milwaukee, Wis.

NEW YORK SECTION

L. Howard Sack, 40 Lexington St., Newark, N. J.

Forest B. Arnold, Secretary, 303 Vanderbilt, Brooklyn, N. Y.

BROOKLYN CHAPTER

James L. Kearns, Chairman, 9531 4th Ave., Brooklyn, N. Y.

Moe Asch, Secretary, 565 Columbus Ave., New York City, N. Y.

QUAD CITY SECTION

R. E. Rote, Chairman, 2016 16th St., Rock Island, Ill.

D. G. Erickson, Secretary, 4303 15 Ave., Rock Island, Ill.

ROCK RIVER SECTION

Floyd S. Ward, Chairman, 1121 18th St., Rockford, Ill.

Carl H. Gustafson, Secretary, 542 Merrill Ave., Rockford, Ill.

SPRINGFIELD, MO., CHAPTER

Wayne A. Clay, Chairman, 402 E. Elm St., Springfield, Mo.

Virgil F. Anderson, Secretary-Treasurer, 305½ East Walnut St., Springfield, Mo.

TRI-STATE SECTION

Ray D. Johnson, Chairman, 118 Jefferson St., Burlington, Iowa.

Byron B. Jeffrey, Secretary-Treasurer, 214 N. Main St., Burlington, Iowa.

New York Section I.R.S.M.

Another angle on the seasonally important subject of auto-radio will be presented by Mr. Murray Yoemans, of the Galvin Manufacturing Co., when he delivers a paper on "Auto-Radio Installation and Service" on Monday, June 11. The Service Forum, conducted by Herb Zvorist, will be devoted to auto-radio problems.

Noise reducing antennas are becoming more and more necessary with the increasing interest in high-fidelity reception, short-wave and television, and hence a talk by Mr. Arthur H. Lynch, President of Arthur H. Lynch, Inc., on the subject of "Correct Installation of Noise Reducing Systems" has been arranged for Monday, June 25. Come and get first-hand information on this important and timely subject.

Both of the above meetings are to be held in the Pennsylvania Hotel, 33rd Street and 7th Avenue, at 8 o'clock, on their respective Monday evenings.

Moe Asch to Represent I.R.S.M.

The Institute of Radio Service Men will be represented by Mr. Moe Asch, of Brooklyn, N. Y., on the Joint Standards Committee of the I.R.E. and R.M.A. This committee determines standards affecting receiver design, its several members co-operating to standardize the various parts and the form of circuit and other information so as to be of greatest benefit to Service Man, Dealer, Manufacturer and Engineer alike.

Mr. Asch, in addition to being a member of the I.R.S.M. is the secretary of the Brooklyn chapter of that organization, he also has conducted business in Brooklyn for several years under the name of "Radio Laboratories" and specializes in dealer service work.

New York Chapter N.R.I. Alumni Association

The initial meeting of the New York Chapter of the National Radio Institute Alumni Association was held in the North Ball Room of the New Yorker Hotel on Friday evening, April 27.

Mr. Phillip J. Murray, the Executive Secretary of the Alumni Association, opened the meeting and explained the aims

and purposes of the Association and its relationship to other organizations. Mr. James L. Kearns, Chairman of the Brooklyn Chapter of the I. R. S. M., and a member of the Alumni, also addressed the meeting.

A charter was presented to the chapter by Mr. Murray and temporary officers were elected as follows: J. L. Kearns, chairman; Forrest B. Arnold, secretary; and a financial committee was elected comprising the secretary, Louis Giannone, and Bert Shapiro. These officers will serve until a regular election can be held.

Service Men Attaining Professional Status

That Service Men have attained professional and business status in most communities is the observation made by Walter Jones, Tube Commercial Engineer of the Hygrade Sylvania Corporation, who contacts Service Men's organizations throughout the country.

"The Real Service Man is certainly coming into his own," states Mr. Jones. "He is no longer a radio experimenter, dabbler or backyard mechanic; nor does he work nights and in spare time to pick up a few spare dollars. The true Service Man is in business, working full time, making a fair living.

"That radio set and tube manufacturers fully realize the changed status of the Service Man is evidenced by the growing collection of technical literature and service notes being issued. Service Men are kept posted on circuit and tube techniques by wide-awake manufacturers.

"And following in the footsteps of the automobile industry, certain set manufacturers are now appointing authorized Service Agencies or Service Men in various territories, so that owners of such sets may know where to secure dependable service. This seems particularly true of automobile radio sets, because this class of equipment is far more critical than the home category. Authorized service agencies and the true Service Men are by now provided not only with the necessary knowledge and skill, but also with good test equipment for use both in the shop and out in the field. Reasonable stocks of spare parts are also carried for immediate repairs.

"Too much cannot be said regarding the splendid efforts of the Institute of Radio Service Men, in promoting not only the technical standards but also the business methods of member Service Men. We can look forward to a striking merchandising activity by these fellows who gain access not only to homes but also to the confidence of their trade.


"In certain territories broadcasting stations are collaborating with Service Men in gaining public recognition and support. In Buffalo, Chicago, Detroit, Cleveland and Pittsburgh, only to mention a few, broadcasting stations are featuring regular programs on behalf of local Service Men's organization, thereby impressing the radio listeners with the value of genuine radio service. The NRA code as applied to radio servicing further strengthens the true Service Man in his business and professional standing, his public acceptance and his well-earned profits," concludes Mr. Jones.

THESE ARE
Genuine
OHIOHM
SUPPRESSORS

ACCEPT NO OTHER



Model WP (Plug)

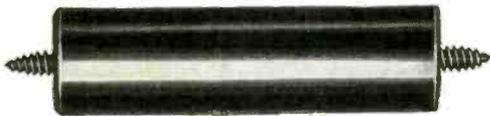

Model Z (Universal)



Model WD (Distributor)

153,000 CAR MILES
Without a failure!

OHIOHM SUPPRESSORS

Have achieved such a record under conditions of 95% relative humidity, a temperature of 140° F., and connected in series to an ignition system operating at the equivalent of 60 M. P. H. for 2,550 consecutive hours.


Also Available in Complete Sets

consisting of necessary suppressors and condenser to fit all makes of cars.

Get them from Your Jobber or directly from



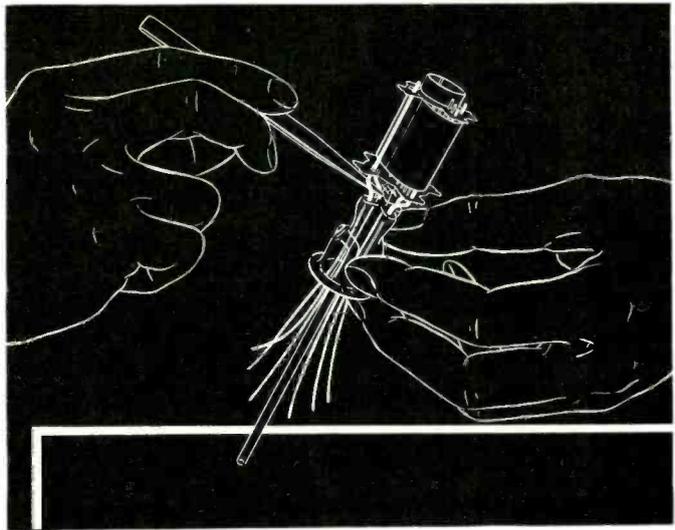THE OHIO CARBON CO.
 12511 BEREA ROAD CLEVELAND, O.



BEHIND THE FINGERS,
THE PURPOSE

FINGERS can be skilful and yet fashion nothing of practical importance. They must be guided by a purpose — a vision of perfection, the desire to create something better.

It is such a purpose that guides the many manual operations in the assembling of Raytheon 4-pillar Radio Tubes. For these tubes are made by workers steeped in the watchmaker's tradition of precision. Even the machines, employed in several stages of their manufacture, are fashioned for an express purpose — the construction of the 4-pillar principle of support which holds the vital elements in a Raytheon secure from damage through vibration.

Every operation through which the raw materials for these tubes pass, reflects that guiding purpose. The result is a tube that performs to perfection under the most rigorous circumstances. That is why police departments, air transportation companies, polar expeditions and millions of set owners everywhere, use Raytheon 4-pillar Tubes and nothing else. When you put a Raytheon 4-pillar Tube in a set, you are assured of perfect tube performance and customer satisfaction.

RAYTHEON
4-PILLAR RADIO TUBES

RAYTHEON PRODUCTION CORPORATION
 30 E. 42nd Street New York City
 445 Lake Shore Drive Chicago
 55 Chapel Street Newton, Mass.
 555 Howard Street San Francisco



Volume I Will Be Out of Print Soon!

The supply of Rider's "Perpetual Trouble Shooter's Manual," Volume I, now in the hands of our distributors in the United States is very definitely limited!

After the present edition is exhausted, Volume I will not be reprinted. If you or your friends have not as yet secured your copy—NOW is the time to buy your Volume I.

This valuable Manual covers radio receivers announced and sold up to April, 1931. . . . Many millions of radio receivers now in use and which will find their way into your shop are included in this manual. . . . Years of service are still in this Manual. . . . Your shop needs Volume I!

Due to an unforeseen accident—many of the plates used for the printing of Volume I were destroyed. . . . If you have any intentions of buying this volume—NOW is the time to act. . . . If you wait too long—you will not be able to secure your copy.

DON'T DELAY.....BUY TODAY!

Volume I of Rider's Manual—as long as it lasts \$7.50

Here It Is!

The **NEW**

Larger—Entirely Rewritten

Servicing Superheterodynes

BY

JOHN F. RIDER

Now on the press. Ready for delivery in June

The original volume published first in 1931 was acclaimed over night as being the finest, most comprehensive and easy to understand practical volume covering the servicing of superheterodyne receivers.

The **NEW** revised book announced in this advertisement has been rewritten. . . . It is better than the original in every respect. . . . It is brand new. . . . Right-up-to-the-minute. . . . In this **NEW** book you will find the most comprehensive explanations of the principles underlying the operation of all types of superheterodyne receivers—broadcast—short wave—all wave—converters—electron coupled mixer-oscillators—wave changing systems—AVC and QAVC used in superhets—demodulators—special circuits, etc.

The most complete information covering alignment operations on old and new superheterodynes—inclusive of special condenser arrangements—will be found in the **NEW** "Servicing Superheterodynes" by Rider. . . . Peculiarities in these receivers accompanied by practical trouble shooting is a feature of this volume. 200 pages.

*Absolutely no service station handling superheterodyne receivers can afford to be without the **NEW** "Servicing Superheterodynes."*

Price \$1.00 Postpaid

Place your orders with us or with your dealer.

JOHN F. RIDER

1440 BROADWAY

1936

SAY YOU SAW IT IN SERVICE

NEW YORK CITY

• SERVICE FOR

NOW—the New Volume IV Rider Manual

1040 pages
\$7.50
Postpaid


"I do not hesitate to say that Volume IV is the most important of all the manuals I have issued. Volumes I, II and III found their place in the servicing world as important aids to the service man. . . ."

Volume IV is destined to be more than just an important aid. . . . It will be a vital necessity. . . . I am firm in the belief that because the contents of Volume IV cover the most scientific and complicated radio receivers ever produced in the history of the radio industry—its ownership will mean the difference between success and failure when servicing the 1933 crop of radio receivers.

You will witness a new era in radio servicing during 1934 . . . and it is only the start of complex radio service problems. . . . Research laboratories in contact with receiver manufacturers forecast increased science applied to radio receiver design. . . . We are passing out of the three and four tube receiver stage—back into the 8, 10 and 12 tube stage with highly complicated electrical networks. . . . Hourly use of radio service data will be imperative. . . ."

John F. Rider

No service man, or service organization, can operate effectively without Volume IV. . . . Advances in radio receiver design have been so numerous within the past twelve months that no ordinary text is able to keep abreast of these new ideas. . . . Volume IV, by including receivers as recent as February, 1934, affords you service data coverage on—dual oscillator systems—bucking bias voltages—automatic noise control—reflexed i-f and 2nd detectors—reflexed r-f, detector and a-f amplifiers—combination rectifier-power pentodes—electron coupled oscillators—single envelope multi-tubes—automatic noise gates and tuning indicators—compensated volume controls—continuously variable frequency compensation circuits—phase shifting tubes—voltage doubler rectifier circuits, etc.

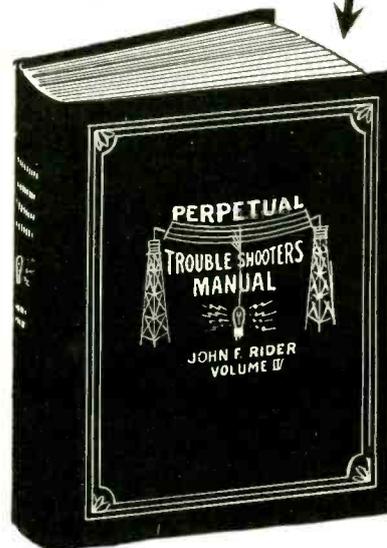


Now is the time to secure those volumes which you lack to make up the complete series. . . . You'll need them—every one of them . . . and they now are available at the lowest prices.

VOLUME II

800 Pages, \$6.50


This volume covers the period between early 1931 and the middle of 1932. It also includes some older receivers, which were not available when Volume I was printed. Point-to-point data is to be found in this volume.

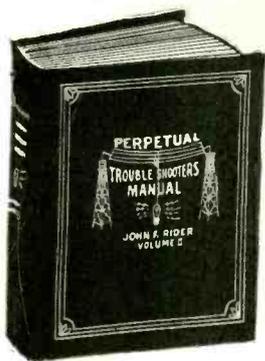

VOLUME III

1185 Pages, \$7.50

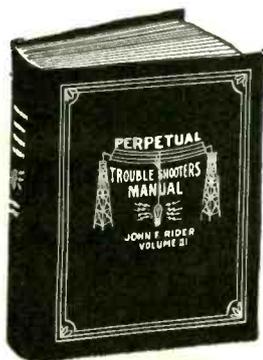
This volume covers the period between middle 1932 and about June of 1933. It also includes some old receivers which were secured subsequent to the publication of Volumes I and II. Volume III also contains some point-to-point data and the world's only set catalog identifying about 8,000 models.



Combination Manual

3000 Pages, \$25.00

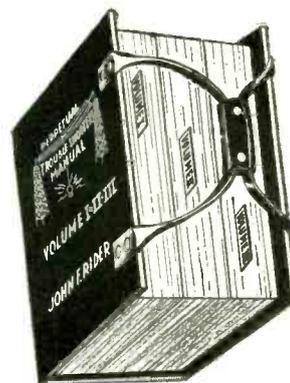Contains Volumes I, II and III under one cover. Available in two types. Without carrying handle \$21.50. With carrying handle \$25.00.



All of these manuals contain schematic wiring diagrams, socket layouts, chassis diagrams, voltage data, photographic views, resistor data, condenser data, electrical values, alignment notes, i-f peaks, trimmer location, continuity test and point-to-point data, etc., etc. All manuals are loose leaf bound in "instant-removal" type binder and contain cumulative index.

Sold With a Money Back Guarantee

JOHN F. RIDER

1440 BROADWAY



NEW YORK CITY

MAY, 1934 •

SAY YOU SAW IT IN SERVICE

197

THE FORUM . . .

Interference and Fading

Editor, SERVICE:

We have experienced the interference and fading (condition occurs only at night during the winter) problems mentioned in your editorial columns. For example, there is continued hash from two or more stations on the same frequencies, stations fade out to be supplanted by others on the same channel hitherto covered up (sometimes 3 or 4 programs will be heard in 5 minutes), and particularly annoying is a 40 or so cycle heterodyne between two carriers. This makes reliable DX impossible. Further, these effects are not caused by the receivers as they appear in all sets used in the same location, so we tell our customers that skip distance and the 11-year sun spot cycle are the causes.

We have no trouble in separating WGN and WOR, with cross talk only on high audio frequencies.

F. R. ASHLEY,
Stamford, Conn.

Broadcast Interference

Editor, SERVICE:

I have read with a great deal of interest the recent letters published in The Forum, regarding broadcast interference, and inasmuch as I have noticed a similar condition in this locality, a report may be in order to aid in clearing up the mystery(?).

In the first place I think that Mr. Ralph P. Worden's letter in the April issue regarding the propagation of skywaves has pretty well covered that phase of the matter insofar as the sun spot cycle affects the intensity of signals. (Although I do not quite agree with one of Mr. Worden's statements, i.e., "Night reception is produced by skywave only.") Another governing factor, no doubt, is that in some localities the broadcast stations may be at fault, as pointed out by Mr. J. Glen Kirstie in the March issue. It is a generally known fact that the frequency of a broadcast station, under certain conditions, is likely to "creep" even though crystal controlled. True, this condition is restricted to a very narrow margin and a "creeping" frequency is not likely to interfere with its frequency neighbor. We must remember however that there are hundreds of small stations throughout the nation that share channels with some of the larger stations. Under favorable conditions some of these smaller stations come through with remarkable volume and are likely to snatch a vacant place on the tuning dial when the desired station has faded to oblivion. This condition is liable to be noticed on any type of set but as sets equipped with straight AVC will hang on to a station until it is practically inaudible, it is only natural that such sets will be much more susceptible to this annoyance, for the simple reason that when the desired station fades to inaudibility, the circuit is thrown "wide open" and any station lurking in the background on approximately the same frequency will be pulled in, to be blanketed out again when the desired station swings back to normal. The same condition would exist on a non-AVC set if the volume were pushed to maximum in following the fading station.

A sharply tuned receiver is a great help

in lessening this condition. Therefore it is always advisable and good service practice to properly align all circuits using a well-calibrated oscillator and a sensitive output meter.

So much for broadcast interference.

I would like to hear from some of your readers regarding their experiences with what is generally termed "fading distortion." This is a condition that I think is far more annoying than the aforementioned interference. Then, too, I have formed theories regarding its cause that I would like to have corroborated. More about this in another letter.

H. B. BENNETT,
623 Fairfax Ave.,
Norfolk, Va.

(Have any Service Men experienced similar interference difficulties in connection with receivers having delayed AVC? We should like reports on interference from other parts of the country, too, if any other localities are suffering from similar cases. THE EDITORS.)

Aerial Installations

Editor, SERVICE:

Going over some old files I ran across a copy of an order issued by the Tenement House Department of the City of New York, forwarded to me under date of June 20, 1932, attached to a covering letter by John P. Finnerty, First Deputy and Acting Commissioner.

The order refers to radio aerials on certain types of apartment buildings and reads as follows:

"On April 4, 1932, the Governor signed the Potter-Burchill bill which added subdivision 2 to section 62 of the Multiple Dwelling Law, and which is in relation to radio antenna or other wires placed over the roofs of multiple dwellings. The following departmental regulations shall apply:

A. There shall be headroom of not less than 10 feet between the roof and all portions of such antenna or other wires.

B. Such antenna or other wires shall be so placed as not to obstruct any required means of access to the said roof.

C. All radio antenna or other wires so placed above the roof of a multiple dwelling shall be properly supported, and such supports shall be sufficiently strong and adequate for the purpose required.

D. No radio antenna or other wires, or the supports which carry them shall be secured to any pipe which is a part of the plumbing or drainage system of such buildings, or to any portion of a fire-escape or other required secondary means of egress.

E. All radio antenna or other wires and supports of the same when placed above the roof of class A multiple dwellings, shall be kept clear of bulkhead doors, scuttle openings, gooseneck ladders or other means of egress for said dwelling.

F. All radio antenna and lead-in wires from same, or any wire which is placed above the roof of a class A multiple dwelling, the purpose of which is to carry an electrical charge, shall be properly insulated from contact with all portions of said roof."

Now if we could get this order enforced

I think it would at least do something in New York City to solve the unemployment among radio men. How about some of the organizations contacting their influential friends on this one?

CARL D. SHORT,
2715 E. Tremont Ave.,
Bronx, N. Y.

(It would be a fine thing if the order referred to was enforced, not only for the sake of Service Men and better reception, but also for the sake of people who use the roofs. The aerial situation is absolutely lousy everywhere and it is about time something was done. Every city and village should have some form of regulation in respect to aerial installations, and we would raise a couple of cheers if service organizations would get busy on this matter in their respective localities.—THE EDITORS.)

Poor Taste

Editor, SERVICE:

I think the tone of Mr. Burkholder's letter in the April issue is uncalled for. I understand the Forum is for readers to discuss problems and suggestions for your magazine.

I don't think it is very good form to be insulting and sarcastic when replying to some letters published in The Forum.

We can't all be super radio engineers.

FRANK PALMER,
Edgewater, Colo.

(The poor taste rests with us. It is quite possible that the interference difficulties experienced by so many Service Men are not apparent in Mr. Burkholder's locality. Presumably this led him to believe that the entire matter is so much tommyrot, which, of course, is not the case.—THE EDITORS.)

Diagram Improvement

Editor, SERVICE:

An article, "Self-Reading Diagrams," in the "Highlights" section of the February issue of SERVICE, requested the reaction of Service Men toward the Wurlitzer diagram, shown in that issue, with reference to tube element indications.

This method is better than your previous diagrams. However, on page 50 of the same issue may be seen a diagram of the Spartan Model 82 receiver in which a still better method of tube element indication is shown. This method suits my taste better than any I have seen heretofore, and could be still further improved if the tube cap would be indicated as shown—each prong indication being numbered.

I would appreciate your kindness in putting this type of diagram before the field for its approval (or disapproval), and if deemed practical, incorporating it in all your future diagrams.

THEODORE R. SAYRE,
1136 Woodruff Ave.,
Hillside, N. J.


(What do you think? Remember that in some cases it may be necessary to sacrifice "readability"—but then it is a question whether most Service Men find the reading of a diagram necessary.—THE EDITOR.)

Service Engineers' 1934-B REPLACEMENT TRANSFORMER


Catalog!

8 pages 8 1/2" x 11"—fits your price manual or ready reference file.


General Power Transformers

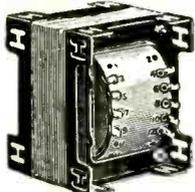


TYPE "U"

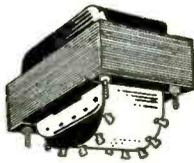

TYPE "P"

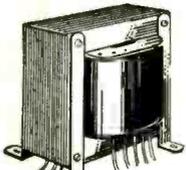

TYPE "H"

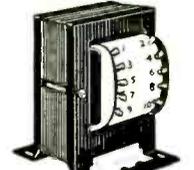

TYPE "E"



TYPE "F"



TYPE "G"

Lists power transformers shown for any set from 4 tube midgets to 12 tube super-power, 110-120 V, 220-240 V, 50-60 cycle—or 115 V, 25-40 cycle.

GIVES COMPLETE INFORMATION REGARDING

"Multi-Tap" UNIVERSAL TRANSFORMERS

5 units for any of 1937 models of radios—
from smallest to largest high-powered sets.

EXACT DUPLICATES FOR 500 MODELS OF THE MOST POPULAR SETS

Auto Radio Multi-Tap "B" power and single and synchronous vibrators.

Class B amplifier and Amateur broadcasting equipment.

Also — Outputs, Input Audios, Interstage coupling chokes for every need.

Tube testing microphone, Step-down and Step-up transformers.

Free for the Asking!

The most comprehensive manufacturers' catalog of power supply units for replacements or for new set building, will please you. Illustrations—units listed, giving code word, dimensions, technical description, shipping weight, and list price of each.

MAIL THIS COUPON TODAY!


GENERAL TRANSFORMER CORP.
502 South Throop Street, Chicago, Ill.
Please send me, without obligation, your 1934-B Catalog and address of nearest distributor.

NAME
ADDRESS
CITY STATE

GENERAL TRANSFORMER CORPORATION
502 South Throop Street : : Chicago, Illinois

Replace Faulty Auto-Radio "B" Packs

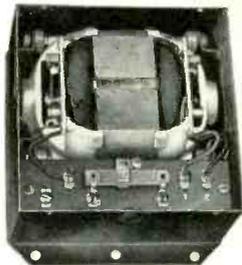PIONEER Gen-E-Motors for Sound Amplifiers



High voltage D. C. for sound amplifiers may be obtained from 6, 12, 32, and 110 volt D. C. power sources with these PIONEER Gen-E-Motors.

Used by leading amplifier manufacturers for sound truck and other installations where A. C. power is not available. Let PIONEER engineers help solve your problems. Write, giving full details of your power needs, and you will receive complete power data without obligation.


PIONEER D. C. to A. C. Converters

110 volts A. C. for operating radio receivers, sound amplifiers, and electric appliances may be secured from 6, 12, 32, or 110 volt D. C. sources with the new PIONEER Converters. Heavy duty design with conservative ratings—yet offered at remarkably low prices. Write for price list today!


with this NEW Pioneer Model JW Gen-E-Motor

Here at last is a complete solution of all auto-radio "B" power troubles. The new PIONEER Model JW Gen-E-Motor replaces vibrator type power units on all popular auto-radio receivers.

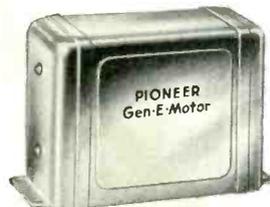It is so compact, measuring only 4 1/8" high x 5 1/2" wide x 2 7/8" deep, that installations may be made within the auto-radio housing



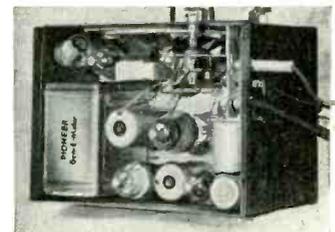The leading 1934 auto-radios are PIONEER Gen-E-Motor Equipped!



in the space vacated by removal of the vibrator unit. Installation is extremely simple. Only three connections and the Gen-E-Motor is ready to bring noise-free, dependable power.

No adjustments, no lubrication, no servicing to cut your profits. Guaranteed ONE YEAR!

The Model JW-25 Gen-E-Motor delivers 225 volts at 50 m.a. with only 3.8 amps. battery drain. The Model JW-50 delivers 250 volts at 50 m.a. with a battery drain of 4.2 amps.

List price only \$13.00

ALSO—new compact models, complete with filter, measure only 5-7/16 x 5-7/16 x 2 7/8 in. Write for price list.

Write for full information—today!

Pioneer Gen-E-Motor Corp.,
460-C W. Superior St., Chicago, Ill.

Send full information about the new PIONEER Replacement Gen-E-Motor and net prices to servicemen.

Name
Address
My Jobber is

THE MANUFACTURERS . . .

TOBE CONDENSER ANALYZER

With the advent of electrolytic condensers, radio sets have been increasingly difficult to service; particularly so during the past two years because of circuit designs incorporating the use of multiple and concentrically wound condensers.

Many aids have been available to the Service Man in an assortment of testing devices which check continuity, resistance, voltage, current, and other such electrical characteristics. However, no practical device has been produced to accurately determine the "quality" and efficiency of electrolytic and paper condensers. The Service Man has encountered much difficulty and delay in his work due to the unsatisfactory and sometimes unreliable methods of testing condensers.



The Tobe Deuschmann Corporation continuing its policy of close co-operation with the service field, has spent considerable time in developing a condenser analyzer which satisfies the most exacting requirements. With this instrument practically any commercial paper and electrolytic condenser can be quickly and accurately tested and its quality directly determined, it is stated.

The condenser analyzer detects defective condensers according to the leakage-resistance-voltage method used by the majority of manufacturers in determining the quality of their products. It is an accepted fact that a condenser not having sufficient dielectric leakage-resistance and not capable of withstanding a definite voltage will not operate satisfactorily.

The fundamental principle of the analyzer is to test condensers under normal operating conditions. This is accomplished by means of a specially designed adjustable power supply which is an essential part of the device. The quality of the various condensers is determined by a simple setting of three controls which adjust the circuit for the allowable electrical characteristics.

The condition of the condensers is directly indicated as good or defective by a sensitive Neon Glow Tube. This instrument quickly and efficiently locates practically any type of defective condenser without removing the condensers from the radio set.

A complete analysis of the entire condenser installation can be accomplished in

a few minutes, thereby improving the ultimate value of the repair job.

The condenser analyzer is furnished complete with instructions and valuable data on condensers and condenser testing.

SHIELDED WEATHERPROOF TUBING

The Shielded Low Capacity Weatherproof Tubing shown in the accompanying illustration is manufactured by the Lenz Electric Manufacturing Company, 1751-57 N. Western Avenue, Chicago, Ill. This



tubing, they state, is excellent for shielding the output of signal generators and, in addition, the small outside diameter permits easy assembly in corner posts of autos as a shield for the antenna lead-in. The inside diameter of this low capacity tubing is 3/16 inch, with an outside diameter of approximately 3/4 inch, and it may be obtained in either 50- or 100-foot coils, the respective weights of these coils being 2.0 and 4.0 lbs.

ALL-WAVE OSCILLATOR

The Radio Products Company, Dayton, Ohio, recently announced an all-wave signal generator—the Series 32—that enables the Service Man to align any radio set on intermediate, broadcast, and short-wave frequencies. Continuous frequency alignment without use of harmonics, a vernier dial that may be used in "flat topping" intermediates, extremely wide range of output voltages made available through the use of a three-section attenuator, unusual stability through the use of a "high C" circuit, an individually calibrated chart that is easily read by hairline sliders, and a switch for unmodulated and modulated signals, calibration



being the same for each position, are the features given for this signal generator. In addition, the unit, which is shown here, is completely shielded and filtered, shielded connector leads being included, while stability is obtained through the use of bat-

teries. The frequency range is from 100 to 13,000 kc, this being gained through the use of six separate coils covering the following bands: 100 kc-220 kc, 220 kc-485 kc, 485 kc-1100 kc, 1100 kc-5750 kc, and 5750 kc-13,000 kc.

NEW "DEPENDABLE" SWITCHES

A new line of switches is being produced by the Radio City Products Co., 48 West Broadway, New York, N. Y. These switches, it is stated, fulfill all requirements for a quality product where demands are exacting, and they are unusually rugged in design and construction which safeguards against decrease in efficiency after continued use.

The discs are made of high grade bakelite with a low moisture content, the electrical conductors are made of a special alloy giving high conductivity and a small amount of wear, and the moving arm makes a positive and wiping contact which is self cleaning.



The shaft is entirely insulated from the contact arm, (bakelite shafts being supplied upon order for ultra short-wave use), and the capacity between contacts is low.

These units require only a single hole for mounting (3/8-inch bushing), numbered dial plate and knob being included with each switch which is individually boxed. While the switch illustrated here is of the 12-point type, they may be had in ranges from 3- to 12-point in single or multi-gang up to seven gangs.

"UNIVERSAL" DETECTIVE LISTENING EQUIPMENT

Detective Listening-in Equipment has just been placed on the market by the Universal Microphone Co., Inglewood, Cal., in a specially constructed carrying case. It may be used as a portable outfit, or kept in one location as permanent equipment.

Technically the outfit has two stages of amplification, a volume control, a high and low switch, two pairs of earphones and comes supplied with six microphones of an ultra-sensitive type.

The instrument is said to be practically foolproof. There are no complicated adjustments. Plug in the phones and it is ready to operate. There are 800 feet of lead-in wire which is so small it cannot easily be seen or discovered. The outfit has volume, power and exceptional tonal quality, it is stated.

LE BOURG AERIAL TOWERS

A. LeBourg, 602 South 11th Street, Gadsden, Alabama, has made available a new type aerial support. These metal Aerial Towers, which are light in weight, may be fastened to any type of roof, without any resulting damage, by means of the loops in the feet of the support. On wood or composition roofs staples may be

LENZ RADIO WIRE

Products For Auto Set Installation
Three Most Generally Used Items

A NEW LEAD-IN SHIELD

Shielded tubing for auto aerial lead-in. 3/16" inside diameter. Approximately 1/4" outside diameter. Low capacity weatherproofed tubing with tinned copper shield applied. Small O.D. permits convenient installation. Used by many prominent manufacturers of auto radios.



AUTO RADIO SHIELDED CONTROL, SPEAKER AND BATTERY CABLE



Two to six conductors. Cotton braids on individual conductors thoroughly moisture-proofed and color coded. Closely braided tinned copper shield applied overall.

Also supplied with cotton braid over shield.

TINNED COPPER SHIELDING AND BONDING BRAID

Following widths available:

3/16", 13/64", 3/8",
9/16", 11/16"



Used for general shielding and bonding purposes.

The above products are available on spools and coils in convenient lengths. Send for Lenz Radio Products (illustrated) catalogue No. 20 today showing complete line for Auto Radio installations and replacements.



LENZ ELECTRIC MFG. CO.

1751 No. Western Ave.
Chicago, Ill.



The Most COMPLETE Tube Tester

in the moderately priced class

JACKSON

MODEL 427

Direct Reading



Every important feature you have wanted in your new tester—and more. This tester has been scientifically planned to meet modern, exacting requirements.

Checks every tube—has line voltage control to assure accuracy—complete neon test for shorted elements and leakage between elements. Also the exclusive Jackson test system for locating "open elements."

Precision D'Arsonval type meter with colored scale. Operating the tester is simple and rapid. Housed in attractive leatherette case with complete instructions.

You cannot afford to be without this Instrument!

Price **\$28.40** (Net to Dealer)

See Your Jobber—or Write Today

THE JACKSON ELECTRICAL INSTRUMENT CO.

432 KISER STREET

INCORPORATED

DAYTON, OHIO



SHORT WAVE CONVERTERS

EASY TO CONNECT AND OPERATE
WORK WITH ANY ELECTRIC SET

The "MARVEL" for A.C. Sets

A Brand new low priced converter which brings any A.C. electric set up-to-date! Connects in a moment without wiring change. The Marvel utilizes the entire circuit of your present set plus power pack making it a super-hot all wave receiver. Comes in beautiful bakelite case. Wave length, 20-200 meters. A source of genuine pleasure—it lives up to its name! Our Low List Price less tube, \$9.50.
Your net cost at 40% off..... **\$5.70**



The "SCOUT" for Either A.C. or D.C. Sets

For DeLuxe performance the Scout has no peer. Efficient with any make radio. Utilizes a No. 37 tube as rectifier; and 6A7 Pentagrid converter tube. Gets Europe easily. Comes in beautiful walnut cabinet complete with both tubes and 2 plug in coils covering band from 20-200 meters. List price complete, \$17.50.
Your net cost at 40% off..... **\$10.50**



ORDER TODAY

from your jobber or favorite Mail Order House at 40% discount. If we cannot supply you write us direct. Be sure you get our big FREE Catalog listing hundreds of IC quality S.W. parts and accessories... today!

WARNING

Be sure you ask for and get ICA quality products. Accept no substitute for the value ICA offers you. All ICA products come packed in ICA containers. They never are sold loose or in bulk. Insist upon the container bearing the ICA trade mark and you will be assured of satisfaction.

INSULINE CORP. OF AMERICA
23-25 PARK PLACE NEW YORK, N.Y.

Department V-54

Send me details of the Marvel The Scout Converter
 Send me name of nearest jobber.
 Send me your FREE S.W. Catalog.

Name
Address
City State

Sold by
more
Servicemen
than
Any Other
Make
EXTRA!

Month of June only! Clough-Brengle Electron Coupled Test Oscillator FREE on special tube purchase offer. Quantity limited. Get details.

Superior Tubes
More Profit
Higher List Price
Free Equipment
Service Aids
Sales Aids
Complete Jobber Stocks

National Union Radio Corp. of N. Y.
400 Madison Ave., N. Y. C.

Send me details about:

..... S-5
Name
Street
City State



used to fasten the tower, while for tile or slate roofs, wires running along the ridge from tower to tower and passing through the loops may be used. In case the middle of the tower should sag it is easy to use a third support.

A. T. R. FULL-WAVE VIBRATORS

The American Television and Radio Co., St. Paul, Minn., have full-wave vibrators of the inverter and self-rectifying inverter types for use in 6- and 32-volt "B" power units.



The full-wave inverter is designed for use with a transformer to deliver a-c current for rectification by means of a tube, such as the 84 type, at a minimum efficiency of 61 percent, and for use with any circuit regardless of whether or not the B- is grounded. It may also be used with just the transformer for supplying current to a-c operated devices.

The self-rectifying inverter is of the full-wave synchronous type, and is designed to deliver high voltage direct current when used with a transformer at a minimum efficiency of 70 percent. It is usually used with circuits having the B- grounded when operated from a common battery supply.

CONDENSER MICROPHONES

Several refinements, involving mechanical construction and frequency response characteristics, are present in the current production of Model 40C Condenser Microphones by Shure Brothers Company, 215 West Huron Street, Chicago.

All condensers and resistors are mounted in a catacomb; and are double shielded, protected, and mechanically rigid. The cable to the tube sockets and the output transformer are the only visible elements.

An interesting feature of the new instrument is "valve-control" of barometric compensation to equalize performance under varying air pressures. The range of compensation has been greatly extended, insuring constant performance under widely varying conditions of weather and altitude and improving the frequency characteristic, they state.

Accessibility of amplifier tubes and the four terminals for the adjustment of the output impedance have been retained. They are readily available under the back cover which unlocks with a twist of a tiny chrome lever.

JEFFERSON REPLACEMENT TRANSFORMERS

In their new catalog No. 341-R, the Jefferson Electric Company announces the addition of a great many replacement and manufacturers' style transformers, including audio, input, output, filament, microphone, line and power, as well as a complete line of chokes, radio fuses, and fuse blocks. Copy of the catalog, together with quotations, may be obtained by applying to the Jefferson Electric Company, Bellwood, Illinois.

LYNCH AUTO ANTENNA SYSTEMS

The Lynch Radio Laboratories, Inc., 51 Vesey Street, New York, N. Y., has recently introduced an antenna system for auto-radios. This system is procurable in three kits; namely, Kit A-1, Kit A-2, and Kit A-3.

Kit A-1, which is made up of the antenna parts only, is for installation under the car. It is triangular in shape, may be folded back on itself, and is fastened to the flywheel housing and the two rear springs. The lead-in is taken from the flywheel end of the triangle.

Kit A-2 is a coupling system that may be used on existing installations and consists of a receiver transformer, an antenna transformer, and ten feet of shielded cable, the latter acting as a low-loss transmission line.

Kit A-3 is the combination of A-1 and A-2, giving the complete antenna system, including insulators, antenna, coupling cable, and transformers.

WECO GENERATORS

The Weco Manufacturing Company, Inc., 520 Second Avenue, Seattle, Wash., announce a new alternating-current generator, in which voltage regulation is accomplished automatically within the generator itself without the use of moving parts or resistances. The principle upon which the unit is based may be incorporated in generators of any size or voltage, either single or polyphase, they state.

The generator is a 60-cycle, 110-120-volt, 500-watt (350-watt equipment) unit that is radio shielded and self excited. It requires no batteries and weighs about 60 pounds. It can, they state, be used in the open and under all climatic conditions. A special cooling system is provided.

KESTER ALUMINUM SOLDER


The Kester Solder Company recently announced a flux-filled aluminum solder which, they say, successfully meets the requirements for proper aluminum soldering.



This solder, which is of special alloy, has an efficient flux sealed in the core or center opening of the solder. It is sold in small tins for repair work, and in one pound spools for commercial use.

"PROD-LITE"

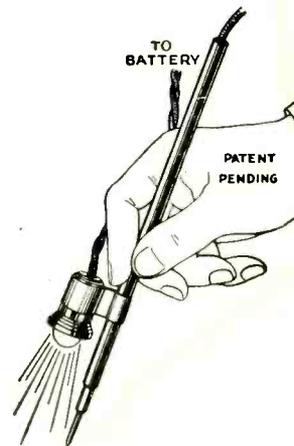The "Prod-Lite," a new device of the Radio City Products Co., 48 West Broadway, New York, N. Y., is a complete system to illuminate test prods without interfering with the normal test procedure, it is stated.



As shown in the accompanying illustration, the lamp socket is clamped to the test prod, adjustment to any position on the prod being quickly obtainable; and it is furnished complete with bulb, flexible cord and standard flashlight battery which is contained in a case that may easily be carried in the pocket. An additional feature of the unit lies in the fact that there are no protruding contacts on the case, a slight movement of the cover switching the light on or off as desired.

NEW SHURE MICROPHONES

Shure Brothers Company, 215 West Huron Street, Chicago, Ill., have announced three new microphones.

The Model 5B is a two-button full-size microphone weighing 15½ ounces. This chromium plated unit has a maximum current rating of 21 ma. per button and an equivalent internal impedance of 200 ohms. The frame diameter is 3 inches and the frame thickness 11/16 inches.

The Model 3A is a two-button microphone suitable for paging systems, portable public-address, and the like. The maximum current rating for this unit is 10 ma., the equivalent internal impedance is 200 ohms, the frame diameter is 2½ inches, the frame thickness ½ inch, and the net weight 5½ ounces.

A maximum current rating of 10 ma., an equivalent internal impedance of 100 ohms, a frame diameter of 2½ inches, a frame thickness of ½ inch, an overall diameter of 3⅜ inches, and a net weight of 5 ounces are the specifications for the single-button Model 2A microphone which was designed to be used on amplifiers that will only accompany a single button unit.

CURTIS CONDENSER CATALOGUE

The Curtis Condenser Corporation, 3601 W. 140th St., Cleveland, Ohio, have released a new catalogue covering their complete line of electrochemical condensers. A copy may be had free on request.

Here's the NEW DAYRAD TUBE TESTER!

... portable, moderately priced, test all tubes!

The handiest tube tester made. Makes complete test of all tubes using basic circuit as applied by leading tube makers. Selector switch method and combination sockets make it very flexible for future type tubes. Cathode Release Short Tests, originated by Dayrad. Tests all types of Dual Tubes. English reading dial. Enclosed in neat case. Operates on 100 to 135 volts, 60 cycle.

ORDER NOW! This modern tube tester leaves nothing to be wanted. Order yours today. You will find it the most accurate versatile and convenient tube tester you have ever used. Order, or write for further information.

Only
\$22.50

25 Cycle
\$2.00
additional.



Cover, hinging at top, not shown here.
Size: 9 3/4" x 8 3/4" x 4 1/2"

THE RADIO PRODUCTS CO., 125 Sunrise Place, Dayton, Ohio



SERVICEMEN!

REDUCE THE HIGH COST OF
KEEPING UP-TO-DATE

Here in one inexpensive 28-lesson *post-graduate* course—the only one prepared *exclusively* for active servicemen—Sprayberry gives ALL the dope on modern radio servicing. Covers every detail—Testing, Repairing (AVC, short wave, all wave, auto radio, P.A., etc.); Parts Testing and Trouble Shooting—also tubes, modernizing set analyzers and selling. No "fluff," mathematics or costly bindings—just a practical, how-to-do-it course that will save hours of reading in scattered sources. Only \$10 for course alone or \$15 with personal instruction and answers to questions by Mr. Sprayberry. Money back guarantee. Write for FREE details!

F. L. SPRAYBERRY,

132 BRYANT ST., N.W.,
WASHINGTON, D. C.

OHMITE "DIV DOHM" RESISTORS



The DIVIDOHM semi-variable resistors were the first vitreous enameled units offered for service work. They incorporate many original features including the patented percentage-of-resistance scale. DIVIDOHMS make ideal replacement voltage dividers as several adjustable lugs may be used without "shorting out" much resistance.

TURN
OVER
A
NEW
LEAF
IN THE
OHMITE
1934
RESISTOR
CATALOG

Use the coupon
for your copy!

COUPON

OHMITE MANUFACTURING CO.
627 N. Albany Ave., Chicago, Ill.

Please send me a copy of the 1934 Resistor Catalog as soon as it comes off the press.

Name
Address
City State



Ohmite RED DEVIL cement coated resistors are the leading universal replacement units; starting from scratch two years ago these resistors have become a prime favorite with servicemen everywhere; their five-to-one factor of safety assures trouble-free operation and eliminates return calls.

OHMITE
Manufacturing Company

Group Subscriptions at SUBSTANTIAL SAVINGS!

- The Regular Subscription price for SERVICE is now \$2.00 per year.

You, no doubt, know many other Service Men who would like to receive SERVICE every month. Probably several other Service Men in your acquaintance are already subscribers.

Here are two plans whereby you can save money for yourself and your friends:

- 1—Subscriptions (new or renewals) can be purchased in groups of ten or more for \$1.00 per year each.
- 2—Subscriptions (new or renewals) can be purchased in groups of five to ten for \$1.50 per year each.

If your subscription is about to expire show SERVICE to five or ten of your friends. They, too, will want it. If they are already subscribers, they will want to renew or extend their subscriptions.

If you wish to *extend* your subscription at these savings, get five or ten others to subscribe at the same time.

Be sure to print clearly the name and address of all the subscribers, and send a check or money order covering the exact amount, noting in each case whether the subscription is a new one or a renewal.

All Offers are Subject to Withdrawal Without Notice

Bryan Davis Publishing Co., Inc.
19 East 47th Street New York, N. Y.

A New Device

A "CHUCKKER" enables radio men to localize any radio trouble, in any radio receiver, in a few minutes right in the field. Successful on 1,000 actual service jobs. Comes complete with instructions and schedule of flat rate prices which you can quote at once regardless of the repair necessary. Flat rate schedule based on \$1.50 per hour for labor and list prices for parts. Introductory Price \$1.00 Postpaid.

FREED'S RADIO CO. (Dept. S)

5053 Baltimore Ave.

Philadelphia, Pa.

When Seeking a Radio School

Consider the advantages afforded by the long-established RCA Institutes

The beginner or the experienced man who seeks instruction in any branch of radio will find courses designed for him . . . either at the resident schools in New York and Chicago or in the RCA Institutes Extension Courses for Home Study.

Following Units Especially Recommended to Readers of "Service":
Elementary Radio Mathematics—Advanced Radio Mathematics—Advanced Radio Servicing—Sound Amplification

Resident schools are fully equipped, conveniently located, low weekly tuition rates. Home Study Courses are on the "no obligation" plan. Free post-graduate practical training period at a resident school.



Catalog on Request

RCA INSTITUTES, Inc.

Dept. SV-34

75 Varick Street, New York
1154 Merchandise Mart, Chicago

In Memoriam

To an advertiser whose copy arrived too late—who now has to wait another month before telling you about his products.

June advertising copy must reach us by June 10th



WET AND DRY ELECTROLYTIC PAPER AND MICA CONDENSERS

RECOGNIZED FOR SUPERIOR QUALITY IN ALL CLIMATES THE WORLD OVER

SOLD BY LEADING JOBBERS EVERYWHERE

SOLAR MFG. CORP.
599 BROADWAY
NEW YORK

BEST BY TEST!
ASK FOR CATALOG OF EXTREMELY COMPACT TYPES HANDY FOR SERVICE

SERVICEMEN!

Do you want an

INDEPENDENT
RADIO SERVICE
CODE

?

Here is your Chance!

Whether you are a member of the Institute or not, Executive Secretary Ken Hathaway advises that *all* Radio Service Men are requested to co-operate in this nation-wide movement for an INDEPENDENT RADIO SERVICE CODE by filing the declaration at the foot of the page.

If the Radio Service Men in your section have not already filed with the Institute a declaration for an Independent Code for the radio service industry, then this is your opportunity to join hands with those who have done so, by either using the reproduction of the "Declaration Card" which you see below, or by copying it and sending it to the headquarters of the Institute of Radio Service, Inc., 510 North Dearborn Street, Chicago, Ill. You will thus let the United States Government know that the Service Men are capable of self-government and that they are united back of this Independent Code.

Promptness on your part will make it possible for your industry to be placed under *independent code control quickly*.

INSTITUTE OF RADIO SERVICE, INC.

510 North Dearborn Street,
Chicago, Ill.

FILL IN AND MAIL TODAY!

ASSENT TO INDEPENDENT ARTICLES AND CODE FOR THE RADIO SERVICE INDUSTRY

To The Institute of Radio Service, Inc.

I believe the RADIO SERVICE industry is entitled to its own independent NRA Code of Fair Competition. It is capable of self-government, if given this opportunity.

I have been connected with radio service since 19..... My business (in 1934) gives employment to a total of..... people, including owners.

I am willing to do my part to bring recovery to the Radio Service industry. I will cooperate with the Local Code Administration Board when duly elected by this territory and recognized by the National Code Authority Board. I approve and assent to the independent NRA Radio Service Code of Fair Competition and to the Articles of Organization of the Institute of Radio Service, Inc., incorporated under the Code of the District of Columbia.

FIRM NAME Corporation

ADDRESS Partnership

STREET NO. CITY STATE Proprietorship

Signed by Dated 1934

TITLE



ALL-NEW—Not Only For Today, But For All Time

Wave OSCILLATOR

ELECTRON COUPLED. ZERO TO MAXIMUM OUTPUT
With No Frequency Shift

ALIGNMENT FROM 100 TO 10,000
KILOCYCLES 3000 TO 30 METERS

Without Harmonics

Utilization of Harmonics permits Alignment
to One Meter—Wave Length

270 DEGREE DIAL—SEVEN RANGES

No. 1	Dial 100 to 300 K. C.
No. 2	Dial 300 to 600 K. C.
No. 3	Dial 600 to 1600 K. C.
No. 4	Dial 1600 to 3000 K. C.
No. 5	Dial 3000 to 4500 K. C.
No. 6	Dial 4500 to 6500 K. C.
No. 7	Dial 6500 to 10,000 K. C.

Equip now for complete all time
future service with this master
unit - - - - It Pays

SPECIAL FEATURES:

Permits use of Pure R. F., or 100% Modulated R. F. for alignment by the old (modulated) or new (unmodulated) methods.

When using modulated R. F., output may be METER READ AT DETECTOR, or any AUDIO FREQUENCY STAGE.

ACCURATE SELECTIVITY MEASUREMENTS

Output continuously variable in four ranges from less than one-tenth Microvolt to over one-tenth volt.

Built in Standard Antenna Loading Capacity . . . Shielded Output Leads.

Line test meter and Voltage Control permits constant operating voltage.

Tube Type 41. Indirectly heated cathode.

Minimizes Frequency and Output Variations with Fluctuations in Line Voltage.



Size 11 x 8 x 4 1/2"

Using unmodulated R. F., any stage or group of consecutive stages may be meter aligned and tested independently.

	HEATER VOLTS	PLATE VOLTS	PLATE CURRENT M.A.	SCREEN VOLTS	SCREEN CURRENT
Rated	6.3	167.5	17.0	167.5	3.00
Operated	4.3	10.0	.15	10.0	.03

This light loading of the Tube results in almost indefinite life and extreme stability.

Each Wave Band has its own separate coil . . . All coils, except the one being used are completely disconnected from the Oscillating Circuits and Grounded.

No Mica Tuning Condensers which change capacity with variations in humidity, temperature, etc., are used on any intermediate or broadcast frequency range . . . PURE INDUCTIVE AND AIR CAPACITY ONLY.

Output Meter automatically connected into the proper circuit to read Modulated or Pure R. F., Output.

Each Oscillator is Accurately calibrated at the Factory and this calibration data is included in addition to complete detailed operating instructions.

Calibrated Dial permits instantaneous setting of the Fundamental of any Frequency from 100 Kilocycles to 10,000 Kilocycles.

Harmonics of the Fundamentals of the No. 6 and 7 scales have sufficient output to permit ready alignment of Receivers to One Meter or 300,000 Kilocycles.

APPROVED—GUARANTEED—DESIGNED AGAINST ALL FUTURE OBSOLESCENCE

These Features all combine to provide an Oscillator that will meet the demands for the accurate servicing of any receiver ever built or that may be expected to be built for many, many years to come.

List Price \$85.00 Dealer's Net Price \$51.00
West Coast Prices Slightly Higher

THE HICKOK ELECTRICAL INSTRUMENT CO., 10516 DUPONT AVE., CLEVELAND, O.

SAY YOU SAW IT IN SERVICE



WE are pleased to announce that up to May 2nd we had received over 25,000 dealer applications for appointment as Retail Agents under the RCA Radio Tube Agency Plan ★ ★ ★ Since the keynote of the Agency Plan is . . . BETTER DISTRIBUTION — NOT MORE DISTRIBUTION . . . we must necessarily proceed carefully in the approval of Agency contracts. Even with all District Sales Offices and the Home Office Headquarters working at capacity, this process of examining and passing on applications naturally requires some time. ★ ★ ★ We ask all applicants for appointment as Retail Agents to bear with us while this arduous task is being completed.

RCA RADIOTRON COMPANY, INC.
CAMDEN ★ NEW JERSEY

SAY YOU SAW IT IN SERVICE