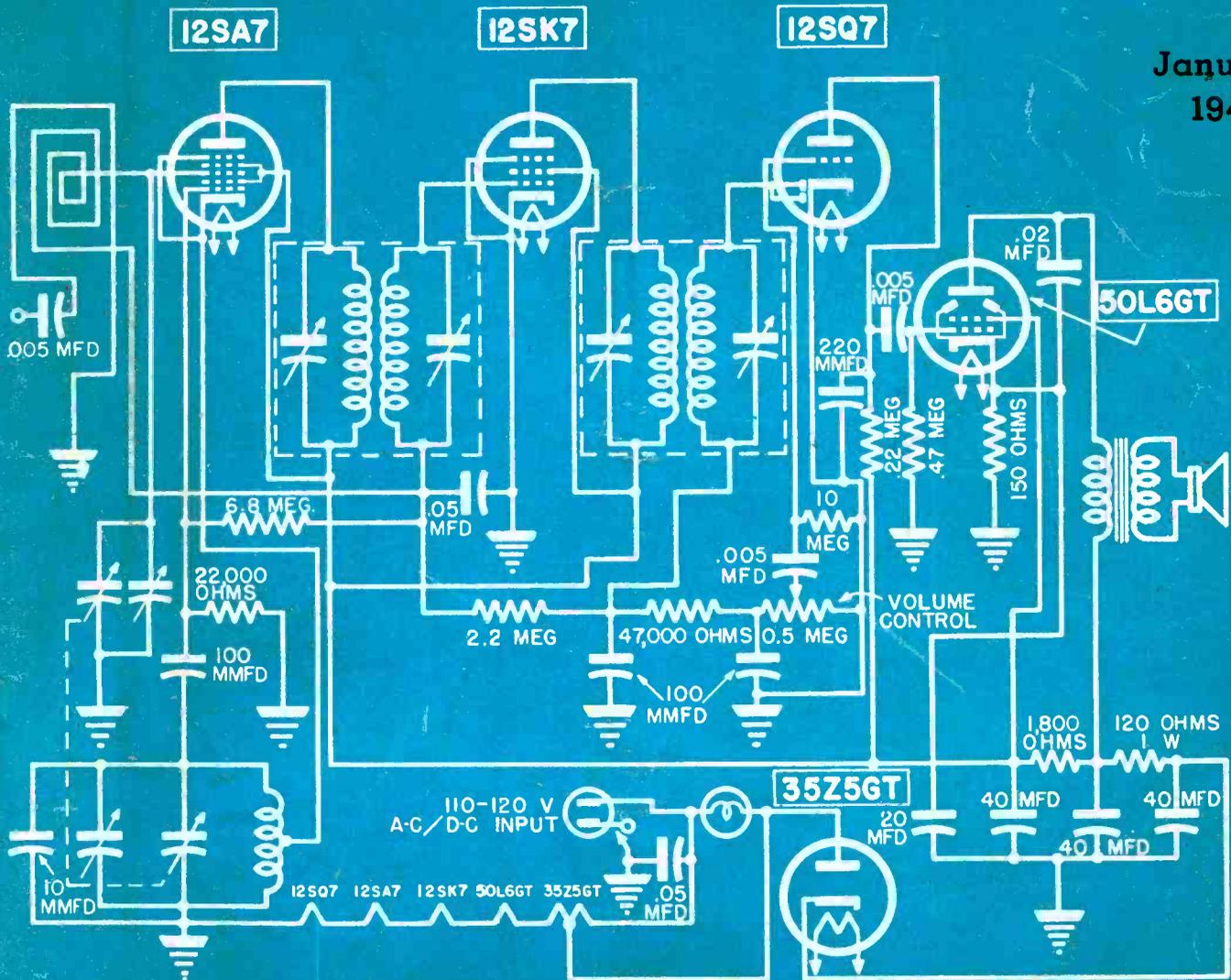


RADIO • TELEVISION • ELECTRONIC

SERVICE

January
1946




Postwar 5-tube a-c/d-c superheterodyne featuring a 2-stage resistance filter and high-Q i-f transformers. (See page 47.)

Annual Index.....Pages 34 to 36

A MONTHLY DIGEST OF RADIO AND ALLIED MAINTENANCE

Felix strikes a happy note-

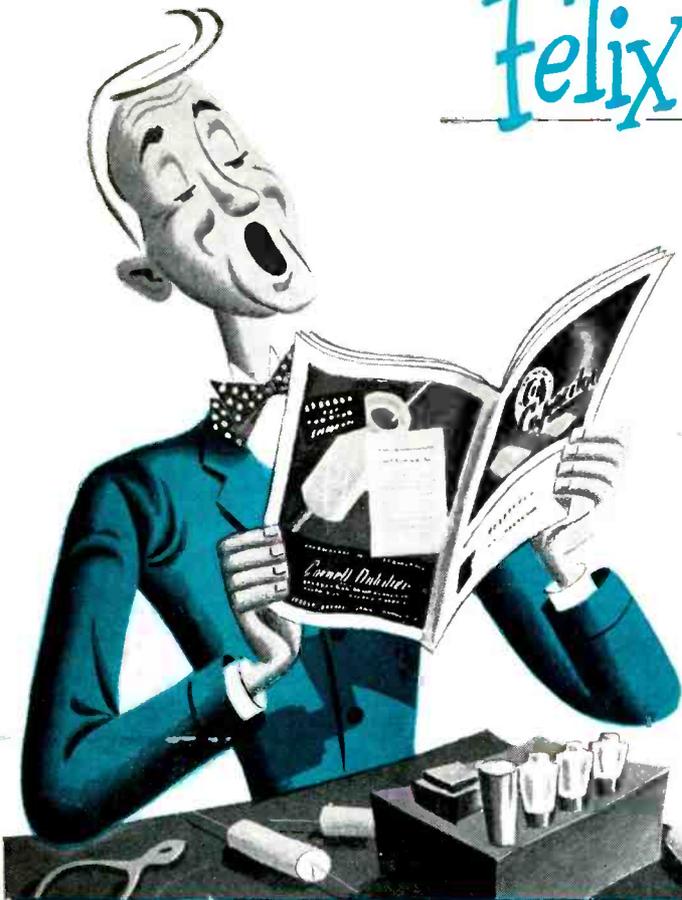

Felix has his share of worries, just like every other radio man . . . work piling up, parts hard to get; overhead mounting, hours shrinking into minutes. In fact, when you think about it, this should be a picture of a well-disgruntled service man.

Then, what's the smile for? Last month Felix read about the C-D Capacitor and straight 'way had his name added to our mailing list. (Didn't cost him a cent). Now look at him, after reading only one issue! What did he discover? A practical service story that opened his eyes to a quick, easy way of cracking a tough-nut problem. What a break!


Maybe you'd like to join our happy family of Capacitor readers? Then do as he did. Write to "The Capacitor", Cornell-Dubilier Electric Corporation, South Plainfield, New Jersey.

COLOR-CODE CHARTS FOR YOU!



Another C-D help. These charts are available in two useful sizes; one for your wall and one for your pocket. Both include Army-Navy coding and RMA standards. Ask your local jobber for a set.

DO YOU HAVE THIS CATALOG?

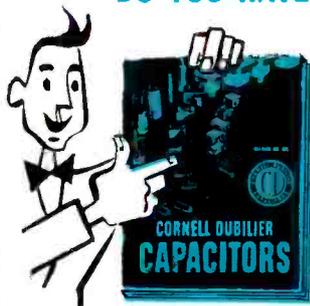

Here at your fingertips is all the information you need on capacitors. Smart servicer's remember only one line . . . one name for their capacitor needs: Cornell-Dubilier. Send for Catalog #195.



STOUT HEARTED BEAVERS



Small in physical dimensions; giants in quality. Even when you use them in heat and high humidity, these little Blue Beavers are "all there". They're Johnny-in-the-spot for small space mounting, too. Ask your jobber.



MICA • DYKANOL

PAPER • ELECTROLYTICS

CORNELL-DUBILIER
World's Largest Manufacturer of
CAPACITORS

JOBBER DIVISION: NEW BEDFORD, MASS. Other plants at So. Plainfield, N. J., Worcester, Mass. and Providence, R. I.

An army

of salesmen is
working for
you...



...when you handle  radio tubes

SOUNDS too good to be true, eh? But it's a fact—this is why: . . . Ever stop to think how many homes have one or more G-E lamps, fans, irons, refrigerators, and other appliances, aside from G-E radio sets? *The G-E monogram is everywhere*—famous sign of quality and owner satisfaction. Right in your area, thousands of G-E products, by their dependable performance, are *pre-selling*

radio owners on the fact that tubes carrying the G-E monogram are the **BEST!** . . . As a G-E radio tube dealer, put this army of 24-hour home salesmen to work for *you*—then watch profits increase! Don't delay. Write for information about G-E tube selling rights to:

*Electronics Department,
General Electric Company,
Schenectady 5, New York.*

Every tube dealer and service man should have G.E.'s handy, fact-filled Tube Characteristics Booklet ETR-15. Write for your free copy today!

GENERAL  ELECTRIC
176-E1-0850

EDITORIAL

WHILE polls or surveys have never been taken too seriously by many of the technical group, significant data presented in recent projects appear to have changed these views. For the surveys have proved that they provide an effective guide to not only purchasing requirements, but to important trends and plans.

An enterprising Service Man proved this quite effectively recently. Before expanding his shop, he decided to survey the community to both determine prospective servicing sources and what additional equipment might be necessary for any new servicing efforts.

It was believed that while homes offered a substantial medium for servicing there were other interests that could be served. As a result, offices, schools, hospitals, taxis, garages, hotels, auditoriums and a few public buildings were polled.

While the survey consumed many days and was not too simple to conduct, the results proved the effort well worth while. For this Service Man found that quite a few of the plans he had made and believed quite necessary would have to be completely revised. He found, for instance, that only certain types of receivers were in immediate need of servicing; antennas were a major servicing factor in certain parts of the community; intercommunication systems in plants and offices were in need of repairs and a maintenance service; and the local school system had been in need of repairs for months. In contrast, the Service Man found that taxis would not need a repair service now, because of the possibility of new cab shipments. He had also assumed that the hospital system would require a complete overhauling. He was right, but funds would not be available for at least a year. Many other similar important income-producing facts were disclosed. As a result it was possible to prepare an evaluation of the services that might be offered and equipment that might be needed. The receivers and associated equipment that were to be serviced dictated the purchase of the proper assortment of components, accessories and tubes, and test equipment.

While all surveys are dated, they do serve as a barometer and prevailing conditions can be used as a guide to accuracy.

Whether conducted in an elaborate or simplified procedure, the survey offers basic information that is certainly more useful than that obtained in a guesswork procedure. Try it!

SERVICE

A Monthly Digest of Radio and Allied Maintenance

Reg. U. S. Patent Office

Vol. 15, No. 1

January, 1946

LEWIS WINNER

Editorial Director

ALFRED A. GHIRARDI

Advisory Editor

F. WALEN

Managing Editor

	Page
Analyzing Intermittents. By Willard Moody.....	32
Annual Index For 1945.....	34
AVC Systems in Communications Receivers. By Thomas T. Donald.....	16
Deflection Circuits in Television Receivers. By Frank G. Strong.....	10
Ohm's Law (A Simplified Analysis). By L. A. Mohr.....	14
Old Timer's Corner.....	38
Postwar Receivers.....	26, 31, 47
Ser-Cuits. By Henry Howard.....	26
Servicing Helps.....	47
Television And The Service Man. By R. B. Carwood.....	9
Volume And Tone Control Resistors (Repairing, Reconditioning and Circuit Substitutions...Part XI). By Alfred A. Ghirardi.....	22
Circuits	
Andrea 1F5 (Deflection Circuit).....	10
DuMont 14" Television Model (Deflection Circuit).....	12
G.E. HM 225B/226B (Deflection Circuit).....	12
Hallicrafters SX28 (AVC).....	17
Hammarlund SP 200-X (AVC).....	18
Philco 38-7.....	32
Philco 90.....	33
RCA TRK5 (Deflection Circuit).....	11
RCA BT6.....	33
Stewart-Warner 9002-A, B, P and R.....	26
Templetone E-510, 519 (Cover).....	47
Cover	
Postwar 5 tube A-C/D-C Receiver (Templetone E-510, 519).....	47
Servicing Helps	
RCA 5T.....	47
Index to Advertisers	
	48
Manufacturers	
News.....	40
New Products.....	44
Jots and Flashes.....	48

Copyright, 1946, Bryan Davis Publishing Co., Inc.

Published monthly by Bryan Davis Publishing Co., Inc.

52 Vanderbilt Avenue, New York 17, N. Y. Telephone MUrray Hill 4-0170



Bryan S. Davis, President

Paul S. Weil, Vice Pres.-Gen. Mgr.

James C. Munn, 10515 Wilbur Avenue, Cleveland 6, Ohio: Telephone SWeetbriar 0052

Pacific Coast Representative: Brand & Brand, 1052 W. Sixth St., Los Angeles 14, Calif.; Telephone Michigan 1732



A. Goebel, Circulation Manager

F. Walen, Secretary

Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price: \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.

AC RADIO SERVICE



Here's
where
your
profits
start!



RAYTHEON
Bonded
ELECTRONIC
TECHNICIANS




RAYTHEON
MANUFACTURING COMPANY

Right on your door, every visitor will see this smart, modern decal—and know your shop is operated by Bonded Electronic Technicians. Here, where your profits start, your doorway becomes a sales-aid. And this is only the beginning. Wall banners, displays, job record cards—the Raytheon Bonded Electronic Technician will have plenty of these to help build a substantial, money-making radio service business. See your Raytheon distributor today. Find out how you can qualify to become a Bonded Electronic Technician. Join the practical, responsible business men known to their communities as Bonded Electronic Technicians.

Another reason why it pays to qualify as a Raytheon Bonded Electronic Technician.

Excellence in Electronics
RADIO RECEIVING TUBE DIVISION
NEWTON, MASS. • NEW YORK • CHICAGO

The Mark of Quality

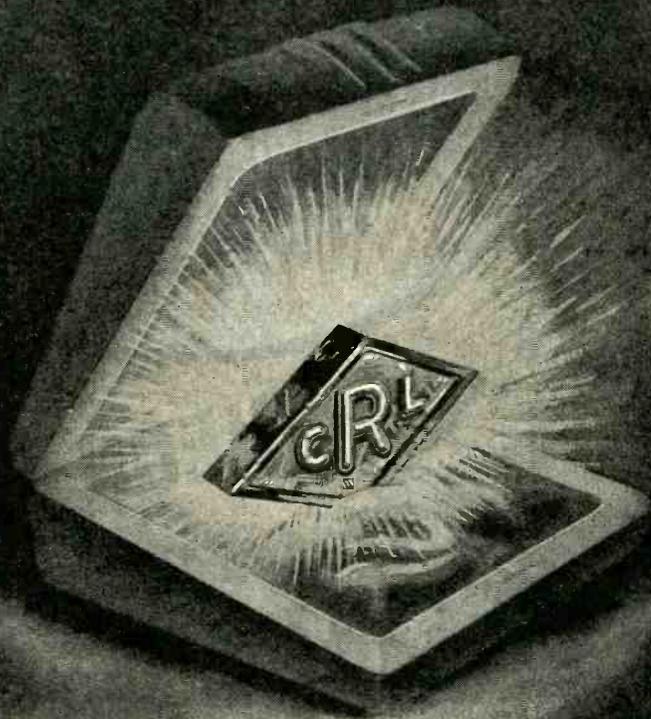

The initials "CRL" in the Diamond stand for Centralab

They are an integral part of the Centralab name, and for more than a quarter of a century have represented the utmost in engineering skill and precision . . . the height of manufacturing perfection.

Both in original equipment and in replacements, the symbol "CRL" is the Mark of Quality.

... Always specify Centralab.

Ceramic High Voltage Capacitors
Bulletin 814

Centralab

Division of GLOBE-UNION INC., Milwaukee

PRODUCERS OF


Ceramic High Voltage Capacitors
Bulletin 814



Ceramic Trimmers
Bulletin 625



Variable Resistors
Bulletin 692

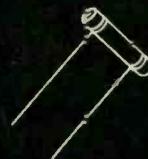

Tubular Ceramic Capacitors
Bulletins 630 and 586



Selector Switches
Bulletin 722




SOME family trees may boast more branches, but our fruit's all hand-picked. There are no lemons in the Stamford "60" line. Even the smallest are built like giants; you couldn't want a stouter crop of transformers. We designed the 60 transformer types that covered all your replacement needs in

quality as well as quantity. Ask to see the Stamford "60"! Give them a try! You'll do a better service job; you'll know real satisfaction in using the finest parts made. For the address of your nearest Stamford "60" jobber and other information, write: Stamford Electric Products Co., Inc., Stamford, Connecticut.

stamford
transformers



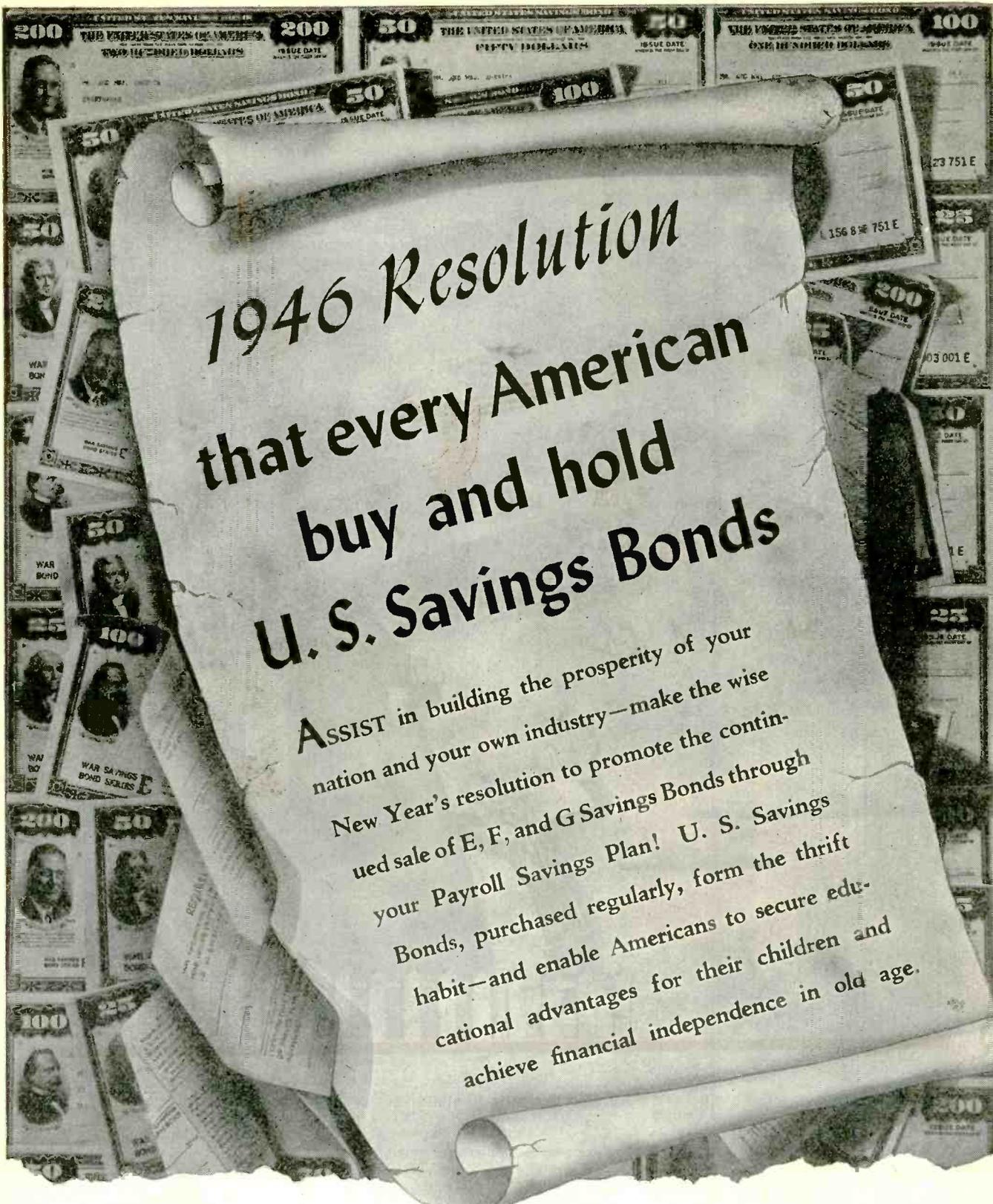

1946 Resolution
that every American
buy and hold
U. S. Savings Bonds

ASSIST in building the prosperity of your nation and your own industry—make the wise New Year's resolution to promote the continued sale of E, F, and G Savings Bonds through your Payroll Savings Plan! U. S. Savings Bonds, purchased regularly, form the thrift habit—and enable Americans to secure educational advantages for their children and achieve financial independence in old age.

The Treasury Department acknowledges with appreciation the publication of this message by

SERVICE

This is an official U. S. Treasury advertisement prepared under the auspices of the Treasury Department and War Advertising Council

SPRAGUE TRADING POST

A FREE Buy-Exchange-Service for Radio Men



A PERSONAL MESSAGE TO EVERY USER OF THE SPRAGUE TRADING POST

With the gradual reappearance on the market of peacetime radio parts and equipment, it becomes obvious that the four-year-old Sprague Trading Post has outlived its usefulness. Rather than buy old materials, you will want factory-fresh new ones. Instead of trading obsolete equipment, you will now want to avail yourself of the many developments that wartime engineering has produced.

Thus, we are sure that the thousands of radio men, amateurs, experimenters, instructors and those in the nation's armed forces who have benefited through this free buy-trade-sell advertising service will fully understand our reasons for discontinuing it with the December issues of the six leading radio magazines wherein it has appeared.

In closing this chapter of Sprague cooperation with our friends throughout Radio, it is interesting to recapitulate briefly:

During the life of the Sprague Trading Post, approximately 12,000 individual classified advertisements were run absolutely free of charge. As a result, hard-to-get equipment was made rapidly available through those who no longer had need for it. Tubes, test equipment, manuals, receivers, transmitters, and dozens of other items including complete service shops were bought, sold and exchanged in tremendous quantity. So many ads were sent in to us that, on several occasions, we

* Trademark Reg. U. S. Pat. Off.

had to increase our advertising budget in order to buy enough magazine space in which to accommodate them all. All told, we invested over \$70,000.00 to make this special wartime service as effective as was humanly possible.

What does the Sprague Products Company expect to get out of all of this? Well, the answer to that one is easy. It is simply that we believe that anything we can do to help our friends is good business for us. Now that Sprague Capacitors, *Koolohm Resistors and Test Equipment are again becoming available in complete lines, we believe we can count on the loyal support of every radio man we tried to help when the going was tough. We believe we can count on you to use Sprague materials wherever possible—and if you do, we assure you that you will be getting the best, most dependable units money can buy.

Meanwhile, should any new opportunity for a cooperative service such as the Trading Post present itself, you can count on Sprague to render it to the utmost. Not only this, but I'll personally welcome suggestions and correspondence along this line from all of you who have benefited even a little through the Sprague Trading Post effort during the hectic wartime years.

Harry Kalcker
SALES MANAGER

SPRAGUE PRODUCTS CO., NORTH ADAMS, MASS.



CAPACITORS FOR EVERY SERVICE, AMATEUR AND EXPERIMENTAL NEED

SERVICE, JANUARY, 1946 • 17

SYLVANIA NEWS

RADIO SERVICE EDITION

JAN. Published by SYLVANIA ELECTRIC PRODUCTS INC., Emporium, Pa. 1946

RADIO SERVICEMEN KNOW THEIR BUSINESS; HAVE COUNTRY'S COMPLETE CONFIDENCE, SURVEY SHOWS

National Research Bureau Reports Findings to Sylvania

A recent nationwide, independent survey — conducted by one of America's leading market research organizations — reveals that not only do 93% of the thousands of set owners interviewed firmly believe that the radio serviceman does a good

job, but also that 89% say he charges a fair price for his work!

That's a flattering record — since the ground covered was scientifically selected, both from the geographical distribution standpoint and income group.

WHAT THIS MEANS TO YOU

To radio servicemen this means they are virtually assured of the continuance of this public trust in the busy years ahead. For, if this confidence was main-

tained throughout the past *difficult* period, it certainly may be expected to continue — and grow — in the following years, when the millions of radio tubes and parts needed will be *available*.

All of this spells opportunity for the radio serviceman. Knowing that he has the public confidence, he can combine the other ingredients of quality components and high class equipment, backed by aggressive promotion, to form an unbeatable recipe for success.

**SYLVANIA
SERVICEMAN
SERVICE**
by
FRANK FAX

Now that the war's over, radio tube production is rapidly getting into its stride. All the pre-war tubes should be available gradually — and along with them will come the newly developed tubes, or improvements and modifications of some of the older ones.

So to keep you in step with the latest tube characteristics and base diagrams, we at Sylvania are having prepared a brand new Radio Tube Characteristics Sheet as well as an up-to-date Base Chart.

You can get both your copies — free — from your Sylvania Jobber or send your request direct to me at Emporium, Pa.

**YOU SAY
WE DO GOOD WORK**

A NATIONWIDE SURVEY
CONDUCTED FOR US
AMONG THOUSANDS OF
RADIO SET OWNERS REVEALS...

93% SAY
REPAIRS MADE ON THEIR
RADIOS WERE SATISFACTORY

89% SAY
THE CHARGES FOR THE
SERVICE WERE REASONABLE

**LET US SERVICE YOUR RADIO
EXPERT WORK AT REASONABLE COST
WE USE SYLVANIA RADIO TUBES**

This is the
special poster — in color —
mailed to radio servicemen with *Sylvania News*

SYLVANIA ELECTRIC

Emporium, Pa.

MAKERS OF RADIO TUBES; CATHODE RAY TUBES; ELECTRONIC DEVICES; FLUORESCENT LAMPS, FIXTURES, WIRING DEVICES; ELECTRIC LIGHT BULBS

TELEVISION AND THE SERVICE MAN

by R. B. CARWOOD

WHILE television at present is in a state of flux, the Service Man will find it to his advantage to become acquainted, even superficially, with some of the problems of this new field.

The FCC rules governing the broadcast of television signals contain many facts of interest to Service Men.

FCC Rules

Thirteen channels have been assigned for television broadcast, six between 44 and 88 mc, and seven between 174 and 216 mc, chart 1. Channel 1 (44-50 mc) has been assigned exclusively to *community stations*. By FCC definition . . . "A *community station* is designed primarily for rendering service to the smaller metropolitan districts or principal cities." The other twelve channels are assigned to *metropolitan stations*, or stations located in large cities, or serving high population areas.

Thus far, the largest number of station channels have been assigned to the New York-northern New Jersey area, Los Angeles, and Chicago, where seven channels each are available. Next comes San Francisco-Oakland with six, and other large population areas with five channels. It does not necessarily follow that all these channels will come into immediate use, since these channels have been assigned to areas, and not to specific stations. In addition, present television receivers cannot receive stations assigned above 88 mc. For example, in the New York area only channels 2, 4, and 5 will be immediately available. It would be to the Service Man's advantage, therefore, to ascertain what is being done to establish television service in his service area, so as to be able to answer customer queries on this subject honestly.

Community stations will be permitted a maximum radiated power of 1000 watts, and *metropolitan stations*, 50,000 watts, at maximum antenna heights of 500' above the average terrain. Where television antennas are

higher than 500', the permissible power will be reduced, so that the signal coverage will be equal to that of an antenna 500' high, at a signal strength of 50,000 watts. This would correspond to an average effective signal radius of approximately 35 miles.

Transmitting hours for each station will be in the neighborhood of six hours per day. At present, the few television stations that are in operation transmit infrequently, and then only for a few hours, two or three at the most. Most of these transmissions take place after 8:00 P.M., except for week-end sporting events. The Service Man should find out what the exact schedules of transmission are, now and in the future. In this way, any contemplated television service work or checking can be assigned to the proper hours.

It is difficult to predict what the public will expect from television. Some of the new receivers give excellent results in black and white images, under ideal reception conditions. How much deviation from the ideal will be tolerated by the television set owner is unknown. From observation, many people will accept television even when it is not perfect. From personal observation among men, sporting events such as boxing and football games go over big, even though the present results on prewar receivers are not very good. Few television stations have made an effort to present well-staged studio programs. For this rea-

son it has not been possible to establish public reaction to a good television program. However, anyone who has seen television has evinced a positive interest in it.

From the Service Man's viewpoint, the installation of television antennas may turn out to be his biggest problem. Reflectors will undoubtedly be necessary. However, the problem of how to construct an antenna with directional qualities, so that it can pick up signals from 7 different directions, and spread out over a band extending from 44 to 216 mc is a problem that is going to require a lot of thought and ingenuity. In addition, the problem of *ghosts* and shielding effects are bound to be trying. In apartment houses, the problem will be further complicated by the installation of numerous television antennas, and unless some method is found to solve this problem, it will be necessary for the Service Man to adjust all the other antennas every time a new antenna is put up.

The next problem faced by the Service Man is the presence of car ignition interference on receivers installed at street or second floor levels. Power and telephone line interference may also be present, particularly in areas where the signal level is low. The Service Man's approach here would be to determine just what is the attitude of television set owners and how much interference will be tolerated by the consumer. To determine public reaction to television Service Men could place a sign in their store window reading:


"Do You Own a Television Set? Come Inside for Pertinent Information."

Since present frequencies are to be reassigned, and new stations will undoubtedly spring up, it will become necessary for these set owners to have their sets realigned. Therefore, in addition to bringing in business, it will be possible to find out their reaction to television, determine what con-

Channel	Mc.	Channel	Mc.
1	44-50	7	174-180
2	54-60	8	180-186
3	60-66	9	186-192
4	66-72	10	192-198
5	76-82	11	198-204
6	82-88	12	204-210
		13	210-216

Chart 1

(Continued on page 21)

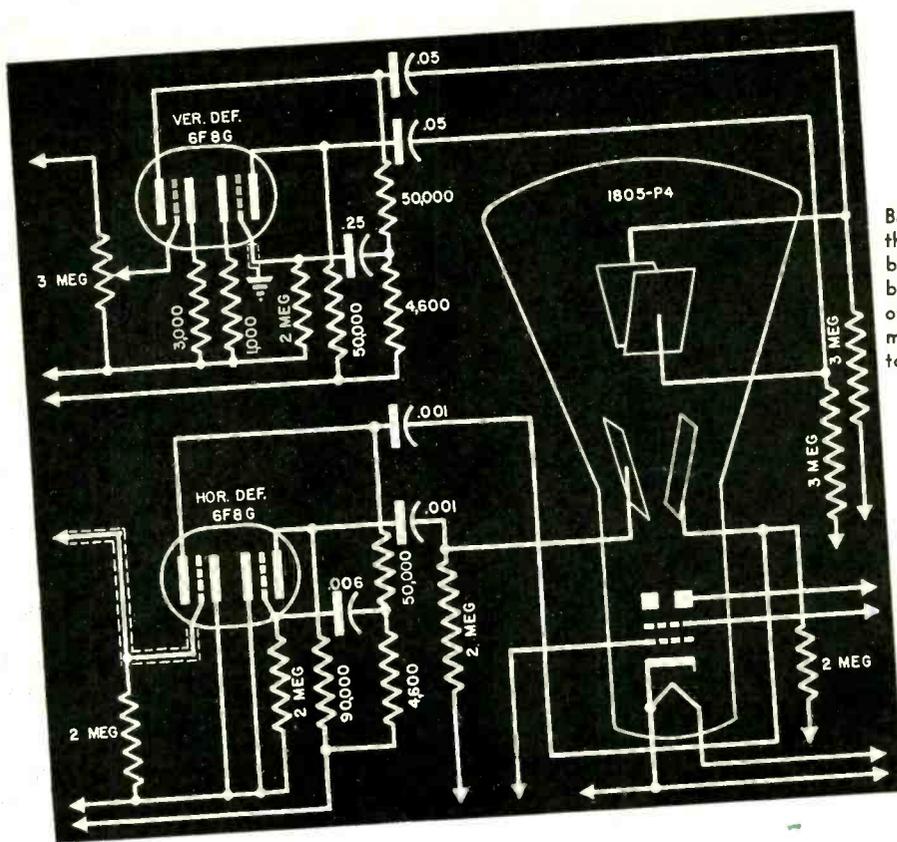

Balanced electrostatic deflection circuits of the Andrea IF5 television receiver. In a balanced push-pull amplifier working into balanced deflecting plates, we use only 1/2 of the *B* voltage of an unbalanced, common tube connection system. That is, the total deflecting voltage is the sum of the two output voltages.

DEFLECTION CIRCUITS IN

ONE of the most interesting and important circuits in the television receiver is the deflection circuit. It is this circuit, linked to the picture tube, that controls the video response to provide acceptable pictures.

There are two general methods of deflecting the beam of a cathode-ray tube; electrostatic method in which the deflection is produced by a pair of parallel plates within the tube, and the magnetic method which makes use of deflecting coils or yokes wrapped around the outside of the tube. The two methods require radically different deflection circuits, although other circuits in the television receiver, including the synchronizing system remain the same for either deflection system.

Electrostatic deflection is familiar to most Service Men since it is commonly used in most oscillographs.

Electrostatic Deflection

In electrostatic deflection circuits we have a high-impedance system where a high voltage of the order of 500 or more (peak-to-peak) is applied

by

FRANK G. STRONG

to a pair of deflection plates to produce a uniform electrostatic field between the plates with a little fringing beyond them. When the plates are sections of horizontal planes, the field produced is vertical, providing vertical deflection of the electron beam. This deflection is based upon the fundamental law of charged bodies: like charges repel, opposite charges attract. The beam, being formed of negative electrons, are repelled from the plate which is momentarily negative and attracted to the plate which is momentarily positive.


In television receivers we must have balanced deflection systems. This necessitates separate terminals for all deflection plates. A balanced system may be produced by a push-pull amplifier or a center-tapped transformer, the latter being good for the lower frequencies only. The important feature is to maintain the same average potential on the plates as on the second plate,

balancing the voltages on a pair of plates with respect to that plate. In inexpensive oscillographs, there is usually a common connection between one plate of each set and the second plate. This causes the deflection sensitivity to decrease with a positive voltage and increase with a negative voltage applied to the free plate. Thus accurate measurement is not always possible. Focussing is also disturbed by the common connection. A type of astigmatism is produced, causing distortion of the normally round spot.

Deflection Sensitivity

As the beam leaves the electron gun it is aimed at the center of the screen and can be displaced only by stray or intentional electrostatic or magnetic fields in its path, which can be identified as deflection sensitivity. This factor is proportional to the peak voltage on the plates, length of the static field and distance from the plates to the screen material. It is inversely proportional to the separation of the plates and the accelerating plate potential. We can control only the deflecting voltage and plate voltage. The other

Fig. 2. Deflection system used in the RCA TRK-5. The coupling system in this television receiver is similar to that used in the Andrea model shown in Fig. 1, with a 6F8G used for the horizontal output and a 6N7 for the vertical. In this circuit, the horizontal plate load consists of a 47,000-ohm resistor and a .005-mfd capacitor. The vertical load is 220,000 ohms.

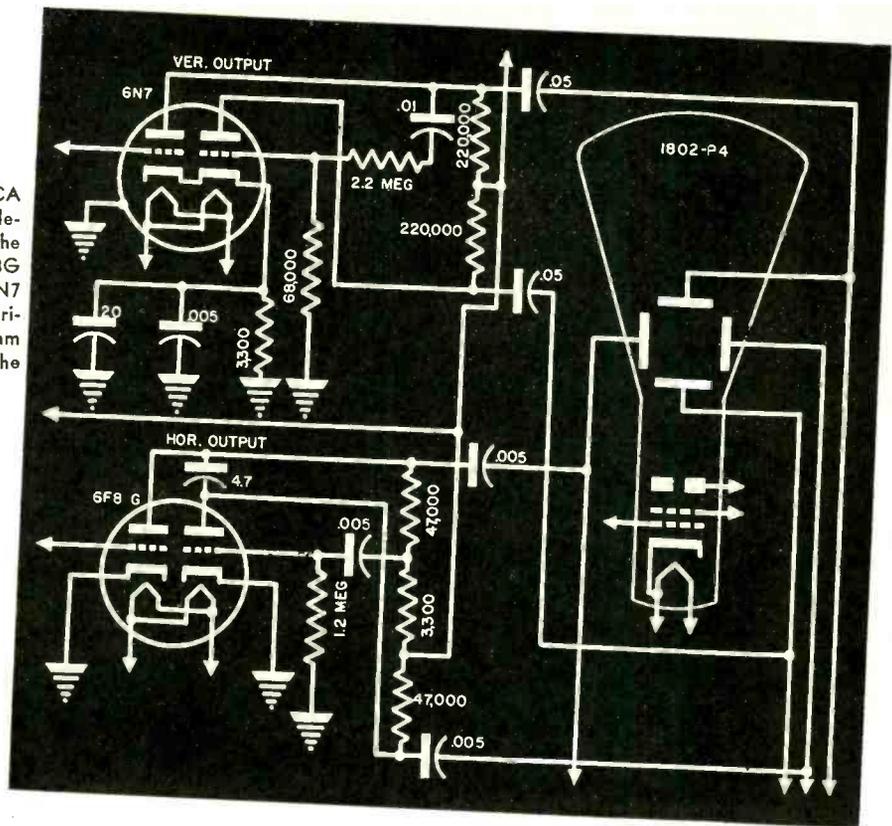

TELEVISION RECEIVERS

factors are inherent in the tube. Expressed as a formula:

$$\text{Amount of deflection} = \frac{V_a \times l \times \text{distance}}{2 \times E_a \times d}$$

where: V_a is the peak voltage between deflecting plates
 l is the length of the plates (length of the field)
 distance is measured from the center of the plate to the screen
 E_a is the second plate accelerating voltage
 d is the distance between the pair of plates
 dimensions are in centimeters

The path of the beam curves while it is acted upon by the static field. The deflection produced upon the screen is directly proportional to the voltage applied; i. e., the system is linear. A tolerance of about $\pm 20\%$ in deflection sensitivity is allowed between tubes of a given type. This is usually allowed for in circuit design. Electrostatic tubes have a deflection angle limited to approximately 35° as compared to 55° for magnetic tubes. This requires a longer tube for a given screen size which, in turn, requires higher voltage for the same brilliance.

The power requirements for electrostatic deflection are not great, and

much less than in magnetic systems. A linear voltage output up to 500 or more is the main necessity for the amplifier, although there is some leakage current, as well as about 10 mmfd of capacity to offset.

Some receivers require compensators or trimmers for tube-to-tube variations. Centering controls operate at a high potential requiring very good insulation and, sometimes, insulated couplings. Service Men must exercise caution in handling these controls.

Magnetic Deflection

Magnetic deflection systems are inherently low-impedance systems requiring coupling transformers for impedance matching between the output amplifier tubes and the deflecting coils. The beam is deflected by motor action. This is the action of a magnetic field on a conductor carrying current, the conductor being the beam itself. The design of magnetic deflecting circuits is much more difficult than electrostatic circuits, because a sawtooth current is required in the deflection coils. To obtain such a current waveform, a negative pulse must be superimposed

upon a sawtooth voltage, just before the start of the sawtooth rise, to offset a surge caused by collapse of the magnetic field in the yoke.

In this system, we have a horizontal amplifier handling 15-kc. In the vertical amplifier 60 cycles are used. Thus the control problem is quite acute in the horizontal amplifier.

Both yoke and coupling transformer must have sufficient insulation to handle the great inductive kick due to the collapse of the magnetic field when the current suddenly returns to zero during the return sweep. At 15 kc with 10% return time, this voltage has a peak value of 2,000-4,000 and, for shorter returns, it is still higher. Damping is required to prevent oscillations following the surge of the return sweep. The speed of return depends upon well engineered transformers and coils having a minimum of distributed capacity. The linearity requirement also demands the best in matching transformers.


Because of the power requirements of the yokes, losses due to damping circuits, and severe surges, power tubes with plenty of tube insulation are employed. Special power tubes

For use in any department and all laboratories where instruments are employed and their performance must be carefully checked

MARION Multi-Range

METERTESTER

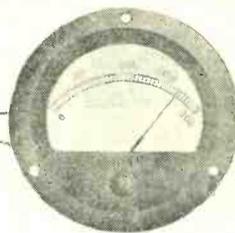With self-contained power supply and control equipment for operation on 110 volts, AC, 60 cycles . . . for production testing, and calibration of DC instruments



No additional accessories are required. Merely connect the two clips to the instrument under test, and proceed to analyze its accuracy and general performance.

INCLUDES . . .

- Regulated Power Supply
- Stepless Vacuum Tube Voltage Control
- Large 8½" Mirror Scale Standard Instrument, Hand Calibrated
- Decade of .1% Accurate Manganin Wire Wound Resistors

After having been successfully used for four years in our own plant, the **Marion MeterTester** is now ready for marketing. It is designed with many operational features which will definitely improve the production rates of any meter inspection department. Moreover, its accuracy is such that it may be used for checking purposes in any department and all laboratories employing instruments. It may also be used as a source of DC current and voltage.

The **MeterTester** is provided with a simple, but effective, Vacuum Tube Voltage Control using a type 6N7 as a grid controlled variable resistor for complete and smooth control of the power to the standard from 0-110 volts, DC. This obviates the use of cumbersome rheostats which oftentimes are unsatisfactory for the wide range of current and voltage covered by the **MeterTester**.

Range of this unit is 25 microamperes full scale to 10 milliamperes full scale, with the first scale division reading ¼ microampere, and 0-100 volts full scale. Overall accuracy is better than ½ of 1%. Basic sensitivity of the Mirror Scale Standard Instrument is 10 milliamperes. The complete unit is housed in a hand-rubbed, solid oak carrying case.

Additional Details Supplied Upon Request

Marion also manufactures a complete line of Electrical Indicating Instruments

**Ideal
Counter Display
for
Meter
Jobbers**





MARION ELECTRICAL INSTRUMENT CO.

MANCHESTER, NEW HAMPSHIRE

Jobber Sales Division: Electrical Instrument Distributing Co.
458 BROADWAY NEW YORK, N. Y.

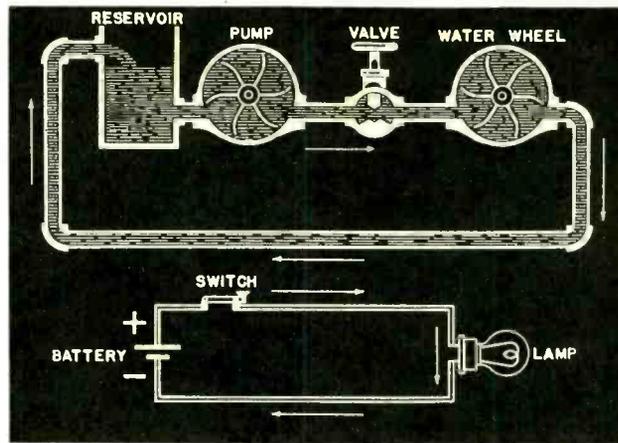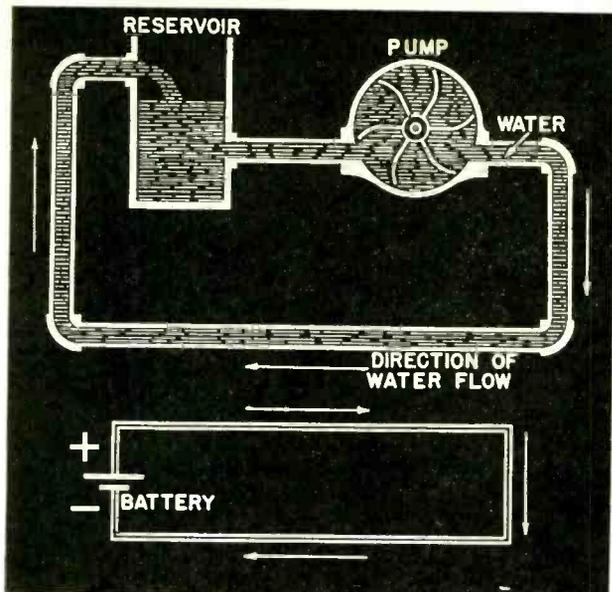EXPORT DIVISION • 458 BROADWAY • NEW YORK 13, N. Y., U. S. A. • CABLES: MORHANEX



Figs. 1 (left) and 2 (above). Fig. 1. Analogy of the continuous water system and the electrical circuit. The battery in the electrical circuit is equivalent to the reservoir and pump of the water system. Fig. 2. Here we see an analogy of the work accomplished by water and electrical systems. The pump drives the water from the reservoir against the water wheel, which turns, due to the pressure against its vanes. The water then returns to the reservoir.

O H M ' S L A W

A SIMPLIFIED ANALYSIS

by L. A. MOHR

THE three basic elements of the electric circuit are *current*, *voltage* and *resistance*. Since there is a close kinship between the behavior of electricity and water, the action of the electrical circuit can be explained by a water analogy.

Current, which is measured in amperes, is the flow of electricity, usually along a conductor, and may be likened to the flow of water through a pipe, measured in gallons per minute.

Voltage, which is measured in volts, is the force which pushes the current, and may be compared to the pressure exerted on the water flowing through the pipe, measured in pounds per square inch.

Resistance, which is measured in ohms, is a static force opposing, or slowing down the flow of electrical current, and is comparable to the type or size of pipe used in the water analogy; Fig. 1.

Current

In measuring the flow of water, a time element is involved, in that we say that 10 gallons, or 15 gallons, or 20 gallons of water are flowing past some preselected point in the space of one minute. If comparisons were to be made between two or more pipes

and their effect on the flow of water, we could compare the flow of water in each by using some time base, such as one second, or one minute, or one hour.

Suppose that an agreement had been reached that in measuring water flow, a basis of one minute would always be used. Then we could say that the flow in one pipe was 10 gallons, in another 16 gallons, etc., with the added expression *per minute*, understood. Similarly, when we say that a current of one ampere is flowing in a circuit, we mean a measured amount of electricity, which takes one second to flow past some point. The term ampere is therefore one which embodies within itself not only a definite quantity, but also a definite time element.

Voltage

Referring again to the water analogy, one influence which governs the amount of water passing a given point is the pressure exerted at the source. Any increase in the pressure will increase the flow of water, and conversely, a decrease in the pressure will decrease the flow.

Water pressure is indicated in pounds per-square-inch. Similarly, the volt represents the unit of electrical pressure, and variations in voltage produce corresponding variations in current or amperes. To summarize, the ampere represents the amount of electricity flowing in a circuit, and

the volt represents the force responsible for that flow.

The Ohm

The third element in the analogy is the *ohm*, or unit of resistance. For water there is no term which adequately defines resistance to the flow of water. However, we can define the resistance offered to the flow of water in a pipe in a general way, since we know that a small pipe will not deliver as much water as a large pipe, even though the pressure on the two is equal. In other words, the dimensions of the water conductor influence the amount of water flow.

Wire Size and Current Flow

In much the same way, the size of the electrical conductor determines the amount of electricity, or amperes, which will flow through it when a pressure, or voltage is exerted on it. That is, for the same force, a large electrical conductor will permit a greater flow of current than a smaller one; this brings up other influences on current flow.

Pressure

For a given pressure, the longer the pipe, the slower will be the flow of water, and the resultant quantity of water emitted at the end of the pipe will be less. That is, if two similarly

(Continued on page 42)

"BIG C"



in new dress!

Take a look at her—



1 She's decked out in the old, familiar blue and orange—but vivid and sharply cut.



2 "Big C" is telling the world she's an *ELECTRON TUBE*—ready for what today *and tomorrow* will bring.

3 She's got her type numbers *out front*—in black, bold type—on the carton top, for easy identification on stock shelves.

What's more, "Big C" is exclusive. She's strictly for Radio Service-Dealers. And you can be sure that her 30-year reputation for quality and top performance will roll up the profits.

Ask your Cunningham Tube Distributor for full details today.

**A QUALITY PRODUCT FOR RADIO SERVICE-DEALERS
BY THE RADIO CORPORATION OF AMERICA**

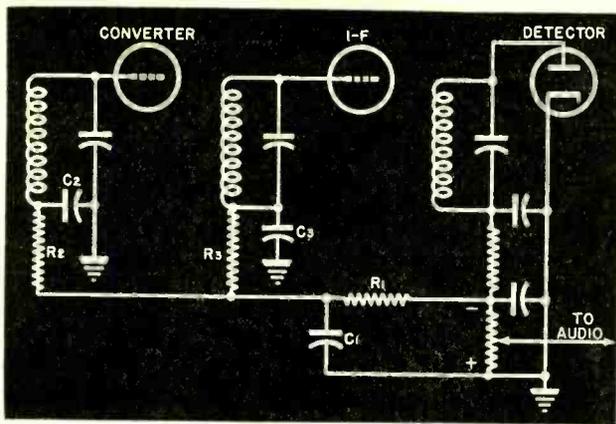


Fig. 1 (above right). Three graphs to illustrate audio output versus signal input. Curve A shows the response of a receiver with no avc system. Curve B is the response curve for the average midget receiver of the 5 tube a-c/d-c type. Curve C is an idealized version of receiver response, with uniform gain for input to a predetermined point, and constant output for increased input beyond this point.

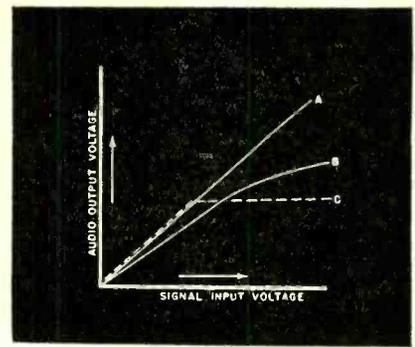


Fig. 2 (left). The avc system of a typical midget receiver. The time constant for the circuit is determined largely by the values of R_1 and C_1 . R_1C_1 also act to filter the audio component of the rectified signal voltage developed across the volume control, which acts to bias the converter and i-f stages.

AVC SYSTEMS IN

by

THOMAS T. DONALD

THE avc systems of communications receivers are basically identical in function to those employed in home receivers, but on a more elaborate scale. Avc systems are employed to keep the audio output level fairly constant for a wide variety of station signal levels, and to compensate to some extent for fading signals. In communications receivers they are doubly important, because the set is invariably being tuned over a band of frequencies, and dx is an important factor.

In Fig. 1 is shown a simplified graph of avc action. Curve A shows the audio-response level for a receiver with no avc, Curve B is the response curve for a receiver with simple avc, such as in 5-tube a-c/d-c receivers, and curve C is an idealized response curve. Curve C indicates that the audio output of the receiver would increase uniformly with input for weak signals, with no avc action taking place until a predetermined signal input level had been reached. Any increase in input signal beyond this level would produce no appreciable increase in audio output.

Fig. 2 shows the simplest form of avc. Here, the signal voltage rectified by the diode detector develops a d-c voltage across the volume control. The amplitude of this voltage will be a function of the amplitude of the r-f signal applied to the detector. Since this voltage will vary at audio frequency, an additional filter consisting of R_1 and C_1 is used to level off or filter the recovered signal. This voltage is then applied as additional grid bias to the r-f and i-f tubes. Decoupling filters are used in these control grid

feeds (R_2 , R_3 , C_2 and C_3) to prevent feedback. In addition, R_1 and C_1 serve to establish a time constant for the avc action.

The time constant is due to the fact that a capacitor shunted by a resistor takes a finite time to charge or discharge. Thus, by shunting a capacitor with a high value resistor and charging the capacitor with a voltage, the capacitor will take longer to discharge than when shunted by a low value one.

Since the capacitors in the avc system are charged by the rectified signal, and since this voltage is applied to the r-f and i-f control grids to reduce stage gain, it can be seen that the time constant should be slow enough so as not to be affected by audio variations in amplitude, yet fast enough to respond to variations induced by signal fading. The time constant used depends on the service for which the receiver is designed. In high-fidelity receivers, the time constant is kept slow, about $\frac{1}{4}$ to $\frac{1}{2}$ second, so that the bass response is unaffected. If the time constant of the avc system were faster, the avc voltage might respond to low audio-frequency modulation of the rectified signal. Thus at peak low audio amplitudes the signal level at the detector would be reduced, and vice versa. This action would tend to remove low-frequency notes. However, in receivers designed for short-wave reception, the time constant is made faster, about $\frac{1}{10}$ second or

less, to instantly compensate for fading characteristics. (Time constant = R [in megohms] $\times C$ [in mfd] seconds.) The formula for computing the time constant of an avc system becomes quite complicated due to the presence of the decoupling filters, but may be roughly estimated from the product of the original filter, such as R_1 and C_1 of Fig. 2.

Since it is sometimes desirable to prevent avc action until a signal of predetermined level is being received, the avc action may be delayed, Fig. 3. Here, a second diode is coupled to the detector diode with its cathode at a positive potential above ground. D_2 will not conduct until the incoming signal exceeds the value of cathode potential. Therefore, no avc will be applied to the r-f section until the signal at the detector is in excess of the delay diode-cathode voltage. Most delay systems operate on a similar principle, that is, a voltage applied to a cathode prevents rectification below a given voltage level.

Fig. 4 shows the circuit of an amplified form of avc. This type of circuit is used extensively in communications type receivers, and has several advantages over simpler forms of avc. First, it will be noted that the avc amplifier tube does not have avc controlling its amplification. Thus, it will respond to increased signal strength to a greater extent than would the diode detector. This action would tend to keep the signal output at a more constant level. In addition avc systems that are derived from detectors tend to load or shunt the audio circuit, producing distortion. The system in Fig. 4 does not affect the audio re-


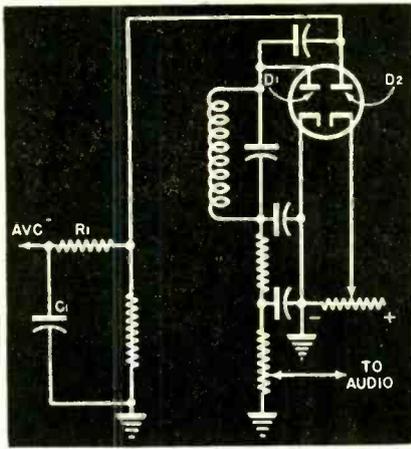


Fig. 3 (above). A simple form of delayed avc. The application of a d-c voltage to the cathode of the delay diode, D_2 , prevents rectification until the signal voltage exceeds the cathode voltage. All delay systems employ some version of this principle.

Fig. 4 (right). A generalized form of amplified avc. In effect, the avc amplifier and diode duplicate the i-f and detector system of the receiver, designed with special emphasis on avc action. Improved avc is provided by the cathode-type bias on the avc amplifier, and the untuned coupling transformer.

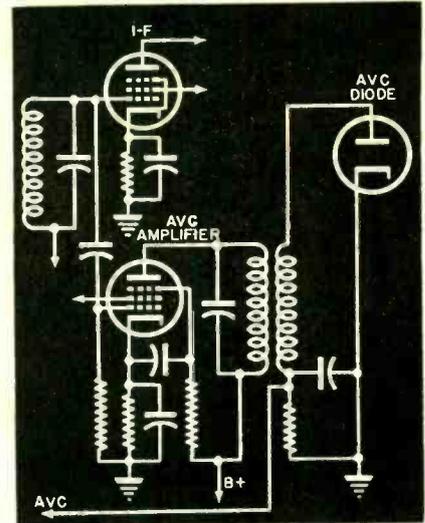

COMMUNICATIONS RECEIVERS

sponse at all. A third benefit is that the avc circuit is being fed from a fairly broad signal source point in the receiver, usually the first i-f stage input. This permits aural tuning of the receiver, since detuning of the signal causes a sharp drop in audio volume level. This sharp drop in audio level is due to the fact that while the signal is being detuned, the avc voltage tends to remain at a uniform level, since it is derived from a broadly tuned signal point. In ordinary avc systems, detuning of the receiver would cause a drop in avc voltage, which would tend to keep the signal at a constant level, even when detuned.

Hallicrafters SX-28

Amplified avc is sometimes used in conjunction with detector type avc systems to improve the uniform response characteristic of communications receivers. One such system is shown in Fig. 5, Hallicrafters SX 28. Here, the avc amplifier tube, a 6B8, is used to supply the avc voltage for the first and second r-f stages, and the first detector. At the same time, it is also used as an amplifier for the a-n-l system. The detector supplies the avc voltage for the first i-f stage. The second i-f stage operates at a fixed bias. The entire avc system represents several principles involved in avc design.

The signal is fed to the avc amplifier from the input to the first i-f

stage, a broadly-tuned signal point. The secondary of the avc i-f transformer is untuned so as not to increase the selectivity of the voltage to be used for avc purposes. The control grid of the 6B8 avc amplifier is grounded through a .5-megohm resistor, with no avc applied, thereby increasing its efficiency as an avc amplifier. The two diodes of the rectifier portion of the 6B8 return to ground through the cathode resistor. Therefore, any volt-

age developed by the diodes across the avc feed resistors, due to contact potential, is more than overcome by the drop across the 6B8 cathode resistor. This voltage also represents a modified form of delayed avc voltage, since a slightly positive voltage is being applied to the grids of the r-f section until a signal strong enough to exceed this cathode voltage is received. It will also be noted that the avc voltage applied to the first de-

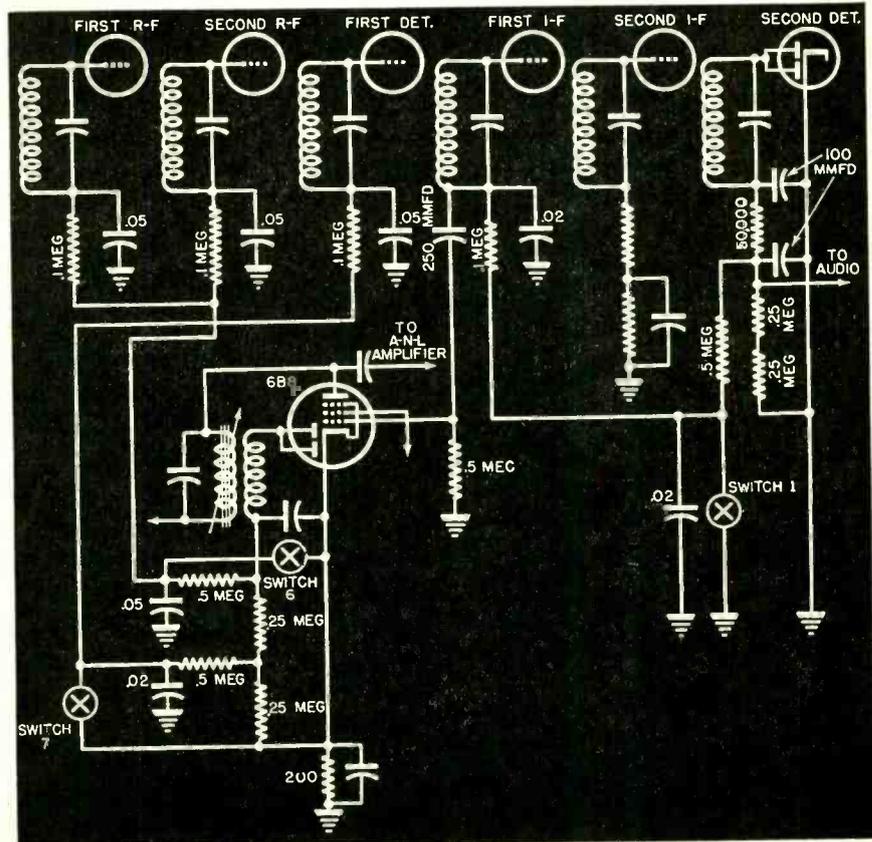


Fig. 5. Avc system of the Hallicrafters SX28. The 6B8 not only acts as an avc amplifier and detector, but also amplifies the r-f signal for the automatic noise limiter. The audio detector supplies avc voltage for the first i-f. The first detector is biased at a lower avc voltage to prevent cross-modulation.



BEFORE THE WAR

Accepted as the foremost manufacturer of quality transformers in the communications industry.



DURING THE WAR

The largest manufacturer of communications transformers in the world.



POSTWAR

Still leading the field in high quality transformers for broadcast applications, specialty fields and volume users.

United Transformer Corp.

150 VARICK STREET

NEW YORK 13, N. Y.

EXPORT DIVISION: 13 EAST 40th STREET, NEW YORK 16, N. Y. CABLES: "UTWAR"



● These Aerovox twist-prong-base electrolytics are again available to you. And they're still extra-good because: (1) They are tightly sealed. Note the unique rubber-sleeved terminals. (2) Rigid terminals, due to eyeletted construction. (3) Special provisions such as hi-purity aluminum foil throughout, minimize corrosion. Post-war listings provide outstanding selection of popular single and multiple section units in required capacities and voltages.

● Ask Our Jobber . . .

Ask for these extra-good Aerovox Type Ar electrolytics. Ask for our post-war catalog. Or write us direct.



FOR RADIO-ELECTRONIC AND INDUSTRIAL APPLICATIONS

AEROVOX CORP., NEW BEDFORD, MASS., U.S.A.
Export: 13 E. 40th St., New York 16, N.Y. • Cable: 'ARLAB'
In Canada: AEROVOX CANADA LTD., Hamilton, Ont.

AVC SYSTEMS

(Continued from page 18)

the grid bias only becomes more negative. On the positive halves, the negative grid voltage is cancelled, and the plate draws current, the amount of current depending on the degree of cancellation. This action creates a voltage across the plate dropping resistor, R_1 , with point A negative in relation to point B . The greater the signal input, the more current the plate draws, and the higher will be the voltage drop. The receiver ground is shown in dotted form in Fig. 7b, to show the voltage relationships in the original circuit. The input signal voltage is developed between the control grid of the 6SJ7 and ground. However, the high value capacitances in

the plate and screen grid circuits actually bring point C to r-f ground.

Servicing AVC Systems

Many receiver troubles arise in the avc system; fading and intermittent conditions to distortion. A fading receiver should first have its avc system checked. This can be done by shorting out the avc system to see if the trouble is coming from this portion of the receiver, Fig. 8. If C_1 were defective, instead of developing the stage voltage gain across the secondary of transformer, T_1 , the gain would be divided between the transformer and R_1 . This would result in a drop in stage gain. If R_1 were open, or increased greatly in value, the voltage on the control grid of the tube would depend to a great extent on the voltage charge on C_1 . This would result in periodic variations in volume, depending on how fast the capacitor

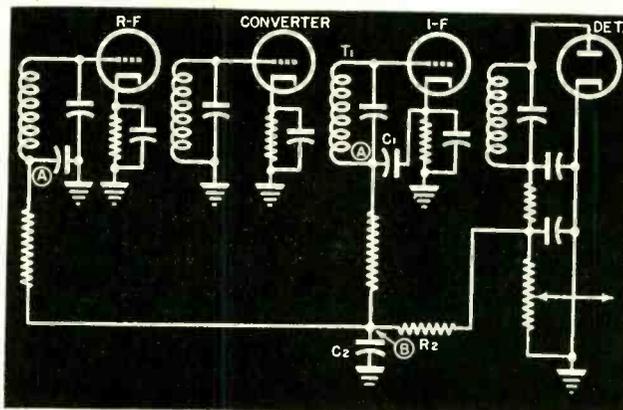


Fig. 8. A standard avc system, showing possible points of failure. To check whether avc system is causing trouble, points marked A should be grounded. A short to ground from point B will cause receiver to distort on strong signals.

SPEED UP REPAIRS WITH THESE G-C AIDS!



FREE STEEL CABINET

G-C Dial Belt Kits

Every Serviceman needs a G-C Dial Belt Kit. Save money—be ready for that repair job. Finest woven fabric replacements. Easy to install—no stretch—no adjustments. Supplied in kits of 25, 50, 100, 200 or 300 Belts in sturdy metal box with slide-in drawer. Free Belt Guide and measuring device.



G-C Dial Drive Cables

G-C has a complete line of Dial Drive replacement cables. Available by the spool for prompt servicing of all sets. Every Serviceman should have a complete assortment. Best quality—extra strength. Preferred by Radio Men everywhere.

G-C Radio Service Cement



The best Cement for Speaker and Radio Work. Especially suitable for cementing replacement cones and repairing rattling and torn cones. Also used on glass, to seal adjustments, hold wires in place, etc. Dependable, vibration proof, water-proof and fast drying.

Write for New G-C Catalog No. 146 and G-C Dial Belt and Service Book

Immediate Delivery on all G-C Products

Order From Your Radio Parts Jobber ALWAYS ASK FOR G-C PRODUCTS



GENERAL CEMENT MFG. CO. ROCKFORD, ILLINOIS

discharged. The symptoms would be similar to that of an open grid.

In checking whether the avc system is at fault, it is necessary that all stages fed by the avc system be grounded, not at the source of avc voltage, but at point *A* in Fig. 8. This precaution is necessary, since the trouble point may be C_1 or R_1 , both of which remain in the circuit if the avc system is grounded at point *B*.

If R_2 were to open, or if either R_2 or C_2 were to be intermittent, the set would react similarly. The trouble may not be in the parts themselves, but in soldered connections at these points. This condition has been found in several receivers. Again, in those receivers employing an avc tube, fading was traced to the tube.

Distortion in the receiver may sometimes be traced to a grounded avc system, or some portion of it. The distortion arises from the fact that the signal applied to the control grid is greater than the bias. Where no avc action is present, this stage will rectify, or draw grid current when the signal exceeds the bias, thereby distorting the signal. In one receiver, the audio volume control could only be advanced slightly, and the receiver would blast out at full volume. The trouble was traced to a partial ground after the avc RC filter. The voltage developed across the volume control was so high, that only a slight advance of the control was necessary to derive the full driving voltage for the first audio stage.

TELEVISION

(Continued from page 9)

stitutes satisfactory reception from the public's point of view, and also what reception is like in the area. The distribution of a printed or typed card of local television station hours will help keep the Service Man's name near the television receiver. It is also suggested that a record be made of all television set owners for future reference.

Too much stress cannot be placed on the dangers involved in television servicing. Some of the new receivers contemplate voltages ranging to 30,000. In addition, the dangers attendant in breaking the CR tube, with its accompanying hazard of flying glass introduce new problems in service.


The Service Man should become thoroughly acquainted with the television field and its problems before he attempts to establish a television service. But such a service, carefully planned with a sound background of information will pay real dividends.



MAKE your transformer replacements more profitable by specifying STANCOR Uni-dapt units. More adaptable because over 80% of all radio transformers now in use are replaceable with a standard Uni-dapt item.

It's this adaptability that makes STANCOR design complete, fulfilling the exact needs of radio serviceman, amateur, and electronic engineer in an economical manner.

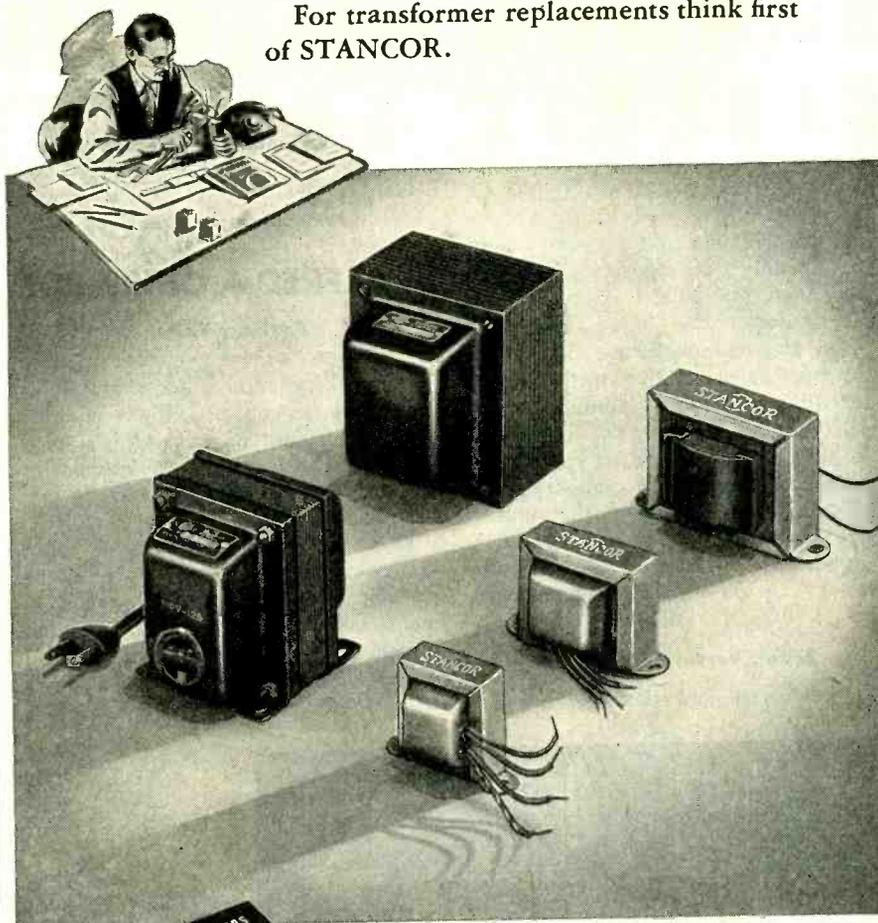For transformer replacements think first of STANCOR.



STANCOR

STANDARD TRANSFORMER CORPORATION
1500 NORTH HALSTED ST., CHICAGO 22, ILLINOIS

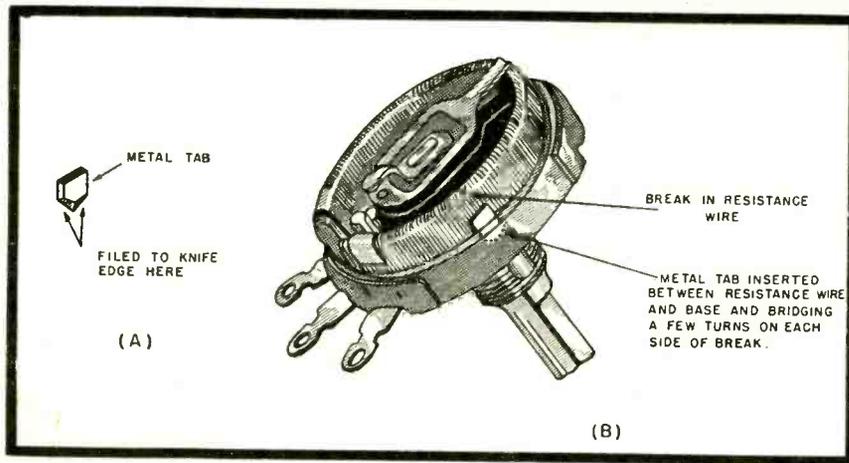


Fig. 1. How a small metal tab may be inserted to bridge *open* wire in a wire-wound control. At *A* appears a view of the tab, that can be cut from old tube shields. The lower edge must be cut to a pointed shape and filed almost to a smooth knife edge.

VOLUME AND TONE CONTROL RESISTORS

REPAIRING, RECONDITIONING AND CIRCUIT SUBSTITUTIONS

[Part Eleven of a Series]

by **ALFRED A. GHIRARDI**

Advisory Editor

MODERN good-quality volume and tone controls are remarkably inexpensive, compact, smooth in mechanical operation and free of noise, when new. Extensive design and manufacturing experience, and efficient production methods employed by the leading manufacturers of such controls are largely responsible for this. However, after the many thousands of operation cycles they receive in a radio receiver that undergoes several years of continual use, volume and tone controls become subject to various troubles¹—principally that of *noisy* operation.

Repair Versus Replacement

There is no doubt but that the best

service policy is to *replace* a faulty volume or tone control with a suitable replacement unit whenever this is possible. A repaired unit seldom continues to give as long or satisfactory service as a new one.

However, as every Service Man knows, it often is not convenient or possible to quickly obtain a replacement control that matches the original in resistance value, taper, physical dimensions, etc. This is particularly true when a *special* unit is encoun-

tered. In such cases, it is necessary to: (1) Repair the faulty control as well as possible to obtain further use from it; and (2) make an *almost-as-good* substitution. This situation was quite prevalent during the war when volume and tone controls were scarce. However, even though they now are more plentiful and the policy of exact replacement should be adopted whenever possible, the Service Man should know how to repair and recondition a volume or tone control whenever it is necessary, for he still will encounter many instances where a suitable new replacement control is not readily obtainable.

Many Repair Methods

The methods of repair that are suggested in this installment are those generally used by Service Men for the majority of types of controls. However, they are by no means the only methods that can be employed! Experienced Service Men seem to develop an amazing amount of ingenuity and resourcefulness when they are confronted with the necessary repair of volume and tone controls, and many perfectly satisfactory *pet* repair meth-

(Continued on page 24)


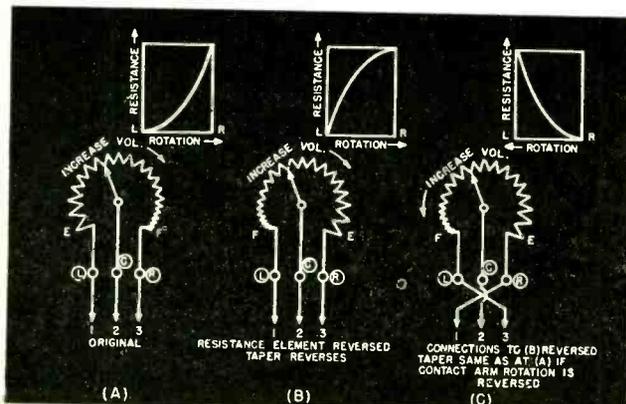


Fig. 2. What happens to a volume control having unsymmetrical taper when position of resistance element is reversed.

¹Part 10, December 1945, SERVICE.

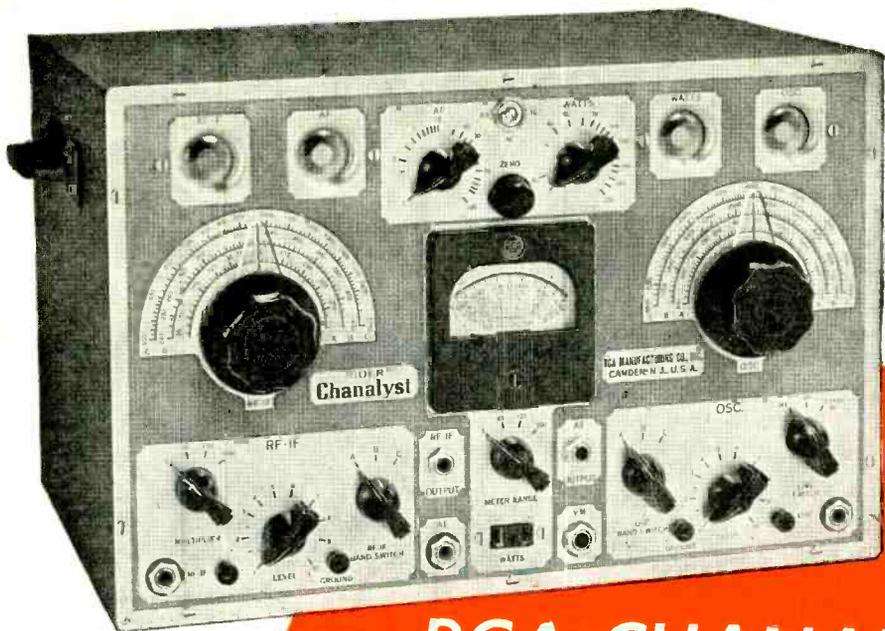

**TYPE 162-C
Rider Chanalyst**

**HOW this
RCA CHANALYST helps
you test radios faster**

THE RCA Type 162-C *simplifies and speeds* up many types of radio trouble-shooting, testing, and repair jobs—saves worry, work, and time.

Because it analyzes the *signal* itself in any part of a radio receiver, the same method of analysis can be used with *all* receivers, old or new, simple or complicated. You can locate quickly and without guesswork the precise stage where distortion, hum, noise, low sensitivity and other defects first appear.

This instrument even helps to solve the

problem of intermittent troubles by indicating how far the signal has passed through the receiver when the intermittent develops. All tests can be made without introducing distortion or otherwise interfering with the operation of the set.

Service records show that several months' use more than pays for the cost of this labor- and money-saving instrument. Be sure to get your name on your RCA Distributor's reservation list so that you will be among the first to get one of the Chanalysts now in production.



GET OUT THE SCISSORS—TODAY

Radio Corporation of America
Test and Measuring Equipment Section
Box 76-A, Camden, New Jersey

Please send me your publication on the RCA 162-C Chanalyst which tells what this instrument does and how to use it.

Name _____
Street Address _____
City _____ Zone _____ State _____



TEST AND MEASURING EQUIPMENT

**RADIO CORPORATION
of AMERICA**

ENGINEERING PRODUCTS DIVISION, CAMDEN, N. J.

STANDS UP IN HARD SERVICE




IT'S
ENGINEERED WITH
HI-Q
COMPONENTS

Every engineer knows that failure starts with the little parts. That's why more and more development engineers place their dependence on Hi-Q Ceramic Capacitors, Wire Wound Resistors and Choke Coils. They know through their own actual tests, that Hi-Q Components stand up under every condition of temperature, humidity, vibration and shock. Test these sturdy components in your own applications. Send your specifications for samples and complete data.



CERAMIC CAPACITORS

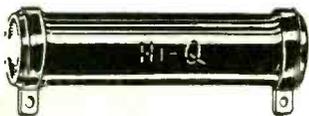Made of titanium dioxide (for temperature compensating types). Tested for physical dimension, temperature coefficients, power factor and dielectric strength.



WIRE WOUND RESISTORS

Immediately available in standard ratings or precision built to any tolerance or value.



CHOKE COILS

Sturdy Construction. Insulated or bare types. Quantity production available at once.

ELECTRICAL REACTANCE CORPORATION

FRANKLINVILLE, N. Y.

VOLUME AND TONE CONTROLS

(Continued from page 22)

ods in addition to those outlined here are in use.

Repairing and Reconditioning Wire-Wound Controls

1. *Open:* (a)—Wire-wound controls which become open due to a break in the resistance wire often may be repaired quickly and effectively by cutting a small metal tab which is then wedged in between the fine-wire element and the phenolic-molded base, as illustrated at (B) of Fig. 1, thus bridging the broken turns. The metal strip should be as thin as possible, tinned and clean, and should be cut wide enough to bridge only several turns on either side of the break. Tabs cut from tube shields are excellent for this purpose. They may be inserted easily and without tearing the fine resistance wire, if the lower edge is first cut to a pointed shape as shown at (A) of Fig. 1, and filed almost to a smooth knife edge with a fine-toothed file.

(b)—If the break has been caused by wearing away of the wire where the contact arm slides along it, the foregoing repair procedure is not recommended, since the fact that the wire has worn through at one point indicates the likelihood that the whole resistance element is badly worn and susceptible to subsequent break-through at other points.

In such cases, it is preferable (when possible) to remove the resistance element from the groove in the phenolic base and turn it upside down so the worn surface rests in the supporting groove and the contact arm slides along the new, unworn surface made available. This new surface should be cleaned with very fine sandpaper until it is smooth and bright. It should also be lubricated with one of the special contact lubricants (see Fig. 3) made for such controls. The break in the winding can be repaired (before inserting the element in the groove) by unwinding one turn to provide the necessary wire and twisting the broken ends together, soldering the joint if possible. The resistance element usually will have to be wedged or cemented back into place in the groove.

If the control employs an unsymmetrical resistance taper, this method of repair cannot be employed. Study of the three illustrations in Fig. 2 will reveal the reasons. When the resistance element shown at (A), which has the left-hand resistance taper characteristic indicated in the insert at the upper right, is turned upside down, its

LAKE'S

RADIO Cabinets, Parts and Equipment!


Now
Available

Postwar 2-Post Record Changer




In luxurious brown leatherette portable case, 15" L x 15" W x 10" D. Latest electronic developments make

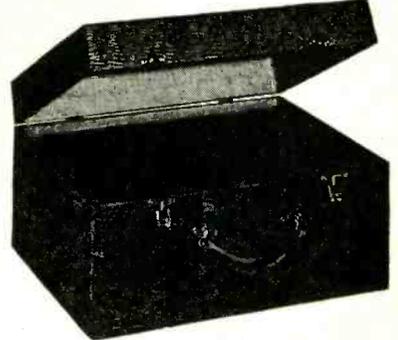this modern record-changer the finest on the market today! List price \$49.95. Dealer's net\$29.97



Portable Phonograph Case of sturdy durable plywood, in handsome brown leatherette finish. Inside dimensions 16½" long, 14" wide, 9½" high. Has blank motor board. As illustrated above, specially priced at **\$6.95**

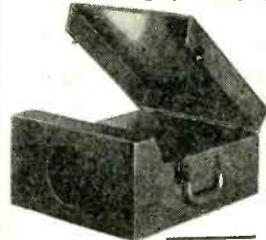Portable Phonograph Case in brown leatherette covering. Inside dimensions 17½" long, 13" wide, 7½" high. Has blank motor board and opening for speaker. As illustrated at left, specially priced at



\$7.95

Also blank table cabinets of walnut veneer in the following sizes, with speaker opening on left front side:

(Note: *7 has center speaker grill.)

#1	—8½"	L x 5½"	H x 4"	D \$1.95
#2	—10½"	L x 6½"	H x 5"	D \$2.75
#3	—13½"	L x 7½"	H x 6¼"	D \$3.25
#7*	—10¾"	L x 7"	H x 5½"	D \$2.50
#8	—17"	L x 9"	H x 9½"	D \$4.50
#9	—21"	L x 9¼"	H x 10½"	D \$5.50

*Speaker Opening in center of front side. Cabinets available in ivory color and Swedish Modern. Write for prices.



All types of radio cabinets, equipment and parts are available at Lake's lower prices. A large stock is listed in our catalog.

SERVICEMEN!

Join our customer list today. Write for Our Free New 12-page, elaborate, illustrated Catalog! Order From Lake! You'll Make No Mistake! Dept. D

Lake Radio Sales Co.

615 W. Randolph Street
Chicago 6, Ill.

two ends *E* and *F* and the tapered portion of its winding reverse in position, as shown at (*B*). Hence its taper also reverses as indicated at the upper right of (*B*), which of course is undesirable. Reversing the connections to the left and right-hand terminals of the control to obtain the correct taper again does not solve the problem, for if this is done, as shown at (*C*), the shaft will have to be turned counter-clockwise for increased volume and vice versa. Such reversed manipulation of the control is confusing and undesirable.

2. Noisy or Erratic Operation: (*a*)—Noisy, erratic operation is sometimes caused by loose terminals on the control. The rivets on these may be tightened, or they may be re-riveted.

(*b*)—If the resistance element has loosened in the groove, causing it to make erratic contact with the contact arm, it may be cemented back in place or, in some constructions, paper shims may be inserted between the element and the phenolic base to make it fit tightly in place again.


(*c*)—Wire-wound volume controls often become very noisy long before they are actually worn out. This may be caused by any one or more of several conditions. A non-conducting glazing of oxidized lubricant and particles of worn-away metal may form on the contacted surface of the resistance element, the contact surface of the arm, or the slip ring and wiper arrangement which makes electrical contact to the shaft or contact arm. This coating causes imperfect contact, and results in noises in the output of the receiver. The obvious remedy is careful removal of the offending substance, plus replacement of the lubricant. Several methods are in vogue for accomplishing this.

Carbon-element, as well as wire-wound controls, often may be quieted (usually only temporarily) by merely rotating the shaft back and forth repeatedly while the entire unit is immersed in a grease solvent such as carbon tetrachloride (Carbona), Ener-

(Continued on page 28)

Fig. 3. Applying *Lube-Rex* lubricant to the cleaned rubbing surface of a noisy wire-wound volume control.


(Courtesy General Cement)

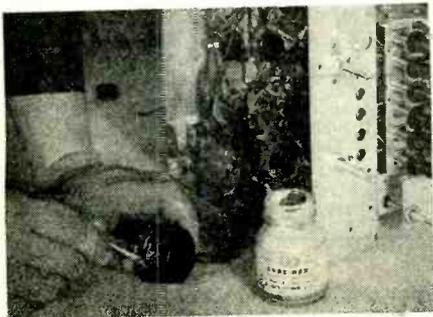

**Greater Signal Strength
Low-Loss, High Efficiency
Tops in Weather Resistance**

Amphenol's "Twin-Lead" is a solid dielectric line that transmits signals from antenna to FM and Television receivers with extremely low loss. It's tough . . . inexpensive . . . easy to install . . . repels water . . . and is unaffected by acids, alkalies and oils because the dielectric is Amphenol Polyethylene.

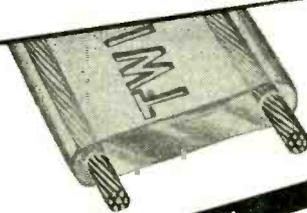
In temperatures as low as -70°F . Twin-Lead Transmission Line stays flexible and does not become brittle after continuous aging in sunlight. In such outstanding qualities Amphenol's "Twin-Lead" is a wire of exceptional efficiency, life and utility.



U. H. F. Cables and Connectors •
Conduit • Fittings • Connectors (A-N,
U. H. F., British) • Cable Assemblies •
Radio • Antennas • Plastics for Industry

AMERICAN PHENOLIC CORPORATION
Chicago 50, Illinois • In Canada • Amphenol Limited • Toronto

SERVICE, JANUARY, 1946 • 25

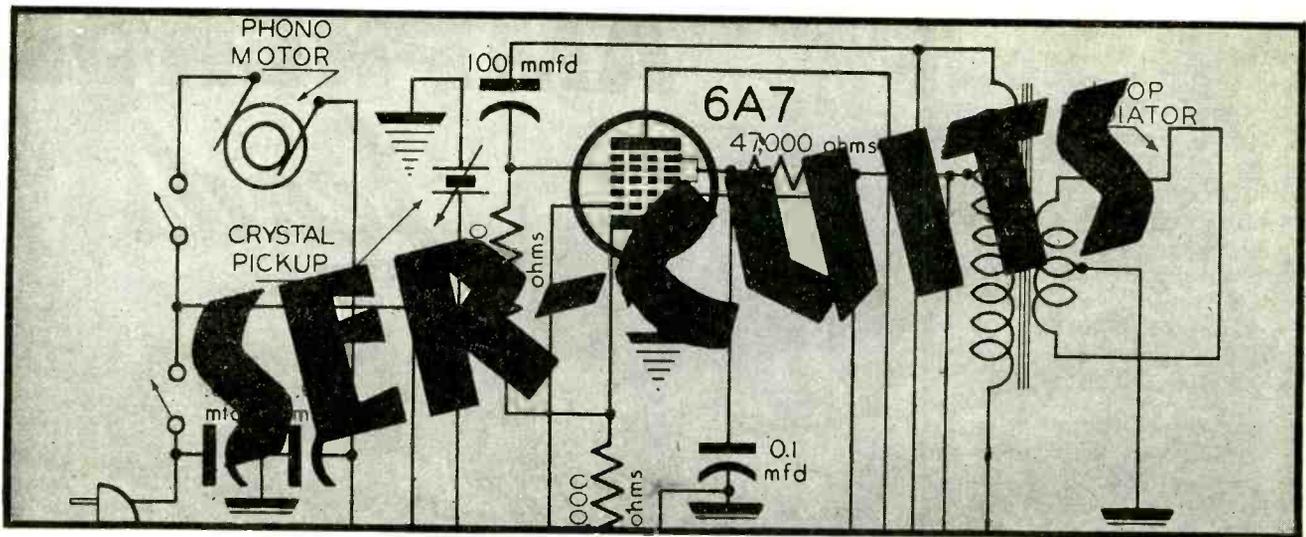

POSTWAR models, just released by Stewart-Warner, reveal many novel circuit developments, particularly in the antenna system. In these models all loops are balanced to ground, with the center at ground potential. Instead of being directly tied to the first grid the loops are coupled to the grid through an iron-core coupling transformer. Thus the loops have a lower impedance than a direct-coupled loop which, with the balanced feature, minimizes capacity coupling with its attendant noise pickup. Another advantage is that the loop may be placed further away from the chassis without the loading effects of long leads. Because of the lower capacity from input grid to ground, the loop will peak at a higher frequency and maintain a better Q through the band. These advantages are obtained only when the coupling transformer has a high coupling coefficient at all frequencies and is otherwise well designed and constructed.

Oddly enough there is a disadvantage to a well-balanced, well-engineered loop system in broadcast re-

by HENRY HOWARD

ceivers. This is the improvement in directional characteristics. While of extreme importance to radio compasses

and direction finders, this directional effect may prove annoying to some because the set (or the loop) has to be frequently rotated to avoid a directional minimum when tuning from station to station.


Another interesting feature of the postwar Stewart-Warner sets is a tuned r-f amplifier. It serves to eliminate many types of interference, including code signals from commercial stations, crosstalk from strong local stations and a multitude of squeals and squeaks from harmonic combinations. The gain in the broadcast band is of the order of 10 to 20, not to be compared with an i-f stage, but substantial.

Instead of the popular dual diode-triode, detector-avc-first audio tube of the 6SQ7 family, these receivers use the 6SF7-12SF7 diode-super-control pentode amplifier type for the i-f amplifier and detector-avc, and a 6SK7-12SK7 for the first audio stage. The pentode audio amplifier permits the use of a novel method of screen grid inverted feedback from the voice coil of the 'SK7 screen. The lower end of

(Continued on page 30)

CONDENSERS	
3A-3B-3C	Condenser—variable gang (with drum)
7	Condenser—mica—50 Mmfd. 500 Volt
9	Condenser—1 Mfd. 200 Volt
10	Condenser—2 Mfd. 200 Volt
12	Condenser—.25 Mfd. 200 Volt
19	Condenser—mica—110 Mmfd. 500 Volt
21	Condenser—.0008 Mfd. 400 Volt
22	Condenser—mica—110 Mmfd. 500 Volt
27	Condenser—.05 Mfd. 200 Volt
31	Condenser—.004 Mfd. 400 Volt
34	Condenser—.01 Mfd. 400 Volt
35A-35B	Condenser—electrolytic
	A-40 Mfd. 150 Volt
	B-20 Mfd. 150 Volt
38	Condenser—.02 Mfd. 400 Volt
41	Condenser—.05 Mfd. 400 Volt
RESISTORS	
4	Resistor—carbon 390 Ohms 1/4 Watt
5	Resistor—carbon 22,000 Ohms 1/4 Watt
11	Resistor—carbon 220,000 Ohms 1/4 Watt
13	Resistor—carbon 4700 Ohms 1/4 Watt
15	Resistor—carbon 47 Ohms 1/4 Watt
16	Resistor—carbon 3.3 Meg. 1/4 Watt
18	Resistor—carbon 47,000 Ohms 1/4 Watt
18	Resistor—carbon 47,000 Ohms 1/4 Watt
20A-20B	Volume control 500,000 Ohms (with switch)
24	Resistor—carbon 10 Meg. 1/4 Watt
25	Resistor—carbon 2.2 Meg. 1/4 Watt
26	Resistor—carbon 2200 Ohms 1/4 Watt
29-30	Resistor—carbon 220,000 Ohms 1/4 Watt
32	Resistor—carbon 470,000 Ohms 1/4 Watt
33	Resistor—carbon 130 Ohms 1/4 Watt
37	Resistor—carbon 1500 Ohms 1 Watt
42	Resistor—carbon 33 Ohms 1/2 Watt

Fig. 1. Stewart-Warner 5-tube and rectifier a-c/d-c single-band receiver, model 9002-A, B, P and R. Sharper tuning is provided by tapping the secondary of the transformer that couples the r-f amplifier and the 12SA7 converter. Parts list above.

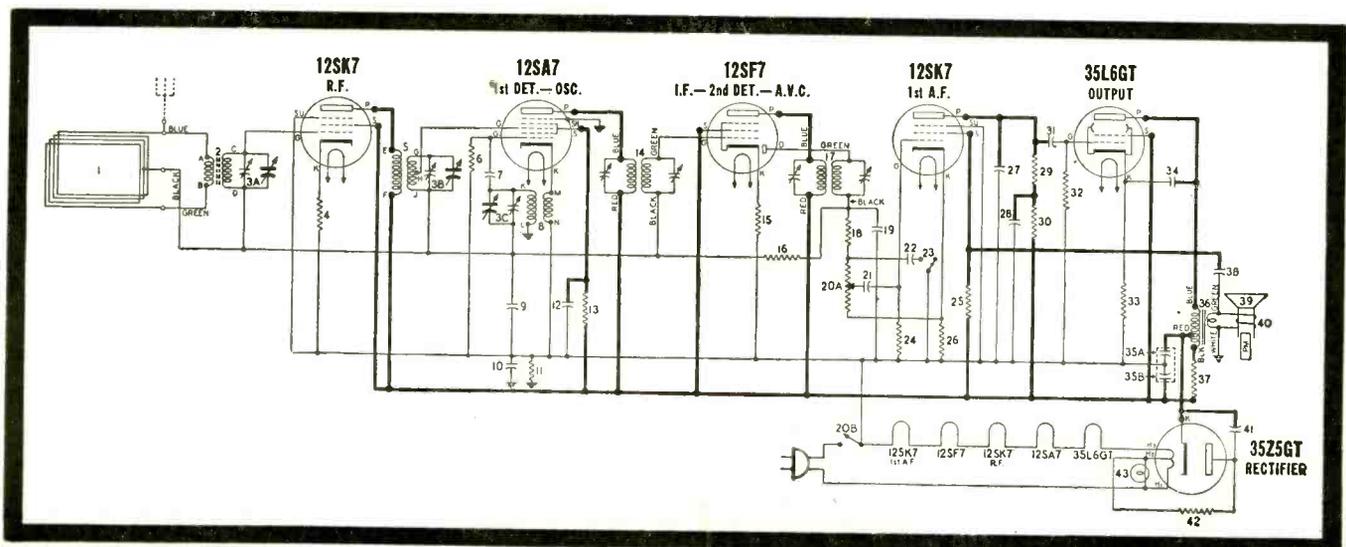

**THERE IS NO OTHER
RADIO MANUFACTURER
LIKE HALLICRAFTERS**

hallicrafters
*manufacturers of high precision, high
frequency radio and electronic equipment.*

Hallicrafters is the world's largest exclusive manufacturer of short wave radio communications equipment. In all the exciting history of the development of the science of radio communications in America there is no story like the Hallicrafters story.

Before the war Hallicrafters built high frequency receivers and transmitters used by 33 governments and sold in 89 countries. Now, in a world that will necessarily be held together by improved communications, Hallicrafters will be demanded by hundreds of thousands—here and around the world.

Hallicrafters receivers and transmitters will be used in all sorts of transportation communications systems—land, sea and air. This equipment will be used as a scientific control and research instrument as FM and television experiments move onward and upward, and it will be in great popular demand by discriminating radio listeners who want distance, clarity, sensitivity and stability combined to a degree that no other radio can offer.

In Past Performance

In Engineering

In Outlook

In Future Possibilities



hallicrafters RADIO

THE HALLICRAFTERS CO., MANUFACTURERS OF RADIO AND ELECTRONIC EQUIPMENT, CHICAGO 16, U. S. A.
COPYRIGHT 1945 THE HALLICRAFTERS CO.

SERVICE, JANUARY, 1946 • 27

Attention GI JOE!

Here's Your Opportunity to be First to
**Start Your Own
RADIO SERVICE
SHOP**

Complete Starting-in-Business
Package Stocks of

**TEST EQUIPMENT
TUBES, PARTS, TOOLS** **\$350 up**

Act quickly! Meet the pent up demand for radio service. Turn your special service training into a profitable business of your own. No fuss. No worry. Here's everything you need—\$350 up. Details upon request! Write, wire or phone



TRIPLETT Volt-Ohm-Milliammeter

A. C.-D. C. Volts
0-10-50-250-1000-5000
at 1000 ohms per volt.
D. C. Milliamperes
0-10-100-500
Ohms 0-300-250,000
Case Black molded
3 1/2" x 5 1/4" x 2 1/4"

\$16.00 net

Good News! ALL
PRIORITIES LIFTED

HALLICRAFTERS SX-28A




\$223

SUPER DEFIANT	SX25	\$94.50
SKY CHAMPION	S20R	60.00
SKYRIDER MARINE	S22R	74.50
SKY RANGER	S39	110.00
ECHOPHONE	EC1A	29.50

ORDERS FILLED AS RECEIVED!!!

AMPLIFIERS

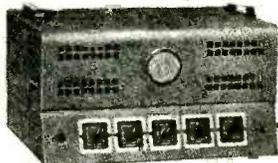

Complete
with tubes.

17 Watt	30.30
25 Watt	42.60
35 Watt	54.60
50 Watt	70.50
17 Watt with Phono-top	42.30
25 Watt with Phono-top	52.20
35 Watt with Record-changer	89.10

PHILCO BEAM OF LIGHT

Selenium Cell only, no holder 1.80

20% deposit required on all C.O.D. orders. 2% transportation allowance on orders of \$25.00 or more accompanied by payment in full.

RADIO SUPPLY & ENGINEERING CO., Inc.
126 SELDEN AVE DETROIT 1, MICH.

Write for
FREE CATALOG

VOLUME AND TONE CONTROLS

(Continued from page 25)

gine, or white (non-leaded) gasoline. Another method, often used for temporary relief, is to use an eye-dropper to force some carbon tetrachloride into the control at the terminal lugs and where the shaft enters the mounting bushing. These procedures are not recommended for permanent relief from the trouble, since they do not allow for thorough cleaning, or for replacement of the lubricant on the rubbing surfaces.


The only really satisfactory method of quieting noisy wire-wound controls entails removal of the attachable switch or dust cover from the back so as to make the vital parts of the control accessible and permit visual inspection of the surfaces of the resistance element, contact, etc. If the condition of the control is really bad, the split retainer washer pressed into the groove in the shaft should next be removed by clamping the shaft in a vise, leaving just enough of it exposed to work on the washer. The washer should then be removed and the contact arm and shaft pushed out through the mounting bushing.

The rubbing contact surfaces on the resistance element, contact arm, wiper and slip ring, etc., should now be inspected. One method of cleaning consists of immersing the disassembled parts in a grease solvent (carbon tet., white gasoline, Energine, etc.) and brushing the rubbing surfaces thoroughly with a 1/2-inch soft paint brush. Then allow to dry. The rubbing surfaces should then be carefully polished with an ordinary pencil eraser (never use sandpaper) until they are brightly polished without scarring. All traces of the eraser dust must then be brushed away. It is advisable at this point to increase the tension of the various springs by a little careful bending. These should not be bent too far, or excessive pressures and wear will result.

Next, a suitable lubricant should be

Fig. 4. Applying *Grafoline*, a combination cleaner and lubricant, to a noisy wire-wound control.

(Courtesy General Cement)

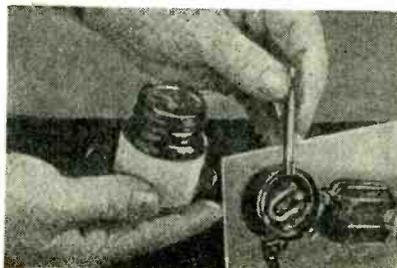

For Soldering in
Tight Places . . .

DRAKE

No. 400 Soldering Iron

Smallest Industrial Iron
Ever Designed

60 Watts — 1/4 in. Tip
Only 9 in. long. Wt. only 8 oz.

This mighty mite is backed by DRAKE's 25 years of soldering iron manufacturing experience. The high quality and long-service of DRAKE soldering irons have made them outstanding favorites with all types of radio men everywhere. The DRAKE No. 400 is an outstanding value at



Only \$4.50

List

Drake Has an Iron
for Every Purpose.
Ask Your Radio
Parts Jobber

DRAKE ELECTRIC WORKS, INC.

3656 LINCOLN AVE., CHICAGO 13, ILL.

FREE

TO
YOU



COLOR CODE
and OHMS LAW CALCULATOR

Great Time Saver

Burstein-Applebee of Kansas City offers you this great convenience FREE. Easy to work. Solves many problems in a jiffy. FREE to Radio men, electronic engineers and others in the business. Attach coupon to your letterhead.

MAIL COUPON NOW



BURSTEIN-APPLEBEE CO.
1012 MCGEE ST.
KANSAS CITY 6, MO.

Send me FREE Color Code and Ohms Law Calculator along with latest catalog.

I am _____
STATE CONNECTION IN INDUSTRY

NAME _____

ADDRESS _____

TOWN _____

STATE _____

applied sparingly to these rubbing surfaces by means of an ordinary match stick, finally wiping over the contact surfaces with clean fingers. White (uncarbolated) vaseline, or Russian mineral oil is satisfactory. So is *Lube-Rex*,* a lubricant that can be used on volume and tone controls, push-button and all-wave switch contacts, the Philco mystery control, etc., Fig. 3. Oil or graphite grease should never be used, since the first cannot be depended upon to remain where it belongs and the second contains a conducting substance.

Some Service Men prefer to use a combination cleaner and lubricant in one, such as *Grafoline*,* on wire-wound controls. Fig 4 illustrates how this may be applied. This cleaner-lubricant may also be used for the contacts of push-button and all-wave switches, tube prongs, etc., or any application where good contact and lubrication must go hand in hand.

Another excellent combination cleaning and lubricating solution can be made by dissolving one-half level teaspoonful of white (uncarbolated) vaseline in two ounces of carbon tetrachloride (both are obtainable at any drug store). They should be thoroughly mixed and allowed to stand overnight. The solution may be applied as above, finally wiping over the contact surfaces with clean fingers.

The control should then be reassembled and the split washer pushed into place on the shaft and squeezed shut with a pair of pliers.


In most cases, an astonishing improvement in noisy wire-wound controls results from such simple cleaning and lubricating. The contacts on noisy *switch-type* tone controls may be cleaned and lubricated in the same way.

*General Cement Mfg. Co.

[To be concluded in February]

Fig. 5. Touching up with *Carbon-A*. Liquid is used on worn and noisy spots on the resistance elements of carbon volume or tone controls.

(Courtesy General Cement)

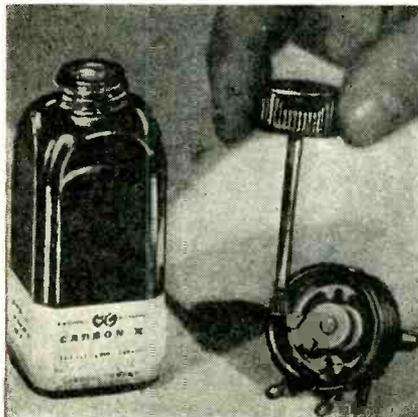

WE'LL PROVE this 4 lb. book IS WORTH ANOTHER MAN in your shop!

\$5

Saves You Time on 4 Jobs Out of 5

Don't confuse A. A. Ghirardi's 3rd Edition **RADIO TROUBLE-SHOOTER'S HANDBOOK** with books on servicing theory! It simply isn't that kind. You don't study the **HANDBOOK!** You just look up the Make, Model, and Trouble Symptom of the Radio to be repaired — and go to work!

TELLS EXACTLY WHAT TO DO!

Clear instructions tell exactly what the trouble is likely to be — **EXACTLY** how to fix it. This big, 4 pound, 744-page manual brings you quick, specific repair data for every radio in use — Over 4,800 models of Home and Auto Radio receivers and Automatic Record Changers of 202 manufacturers! Pays for itself the first time you use it. In

addition, there are hundreds of pages of repair charts, data on tuning alignment, transformer troubles, tube and parts substitutions, etc. etc. — all indexed for quick easy reference.

WE'LL PROVE IT

The **HANDBOOK** is the ideal book for training new helpers repairing either cheap or expensive sets profitably, substituting tubes and parts accurately, eliminating useless test time and equipment. Because it helps you fix **TWO SETS IN THE TIME YOU'D NORMALLY TAKE FOR ONE** it's every bit as valuable as another helper in your shop — and we'll prove it. Send for the book now! Let it work for you for 5 full days. If not more than satisfied, return it and we'll refund every cent of your money. Take us up on this offer now!

... and this 1300 Page Book is worth every cent of a **COMPLETE RADIO-ELECTRONIC SERVICING EDUCATION**



Every Conceivable Service Subject!

A. A. Ghirardi's big 1300-page **MODERN RADIO SERVICING** is the finest, most complete instruction book on Radio-Electronic service work for either the novice or the professional Radio-Electronic Serviceman — bar none! Actually, it gives a **COMPLETE MODERN EDUCATION** in truly professional service work that is an Open Sesame to real opportunities in post war Radio-Electronic Service work where the call will be for **TRAINED** men with a **BROAD** knowledge of modern test equipment and testing techniques . . . and not poorly-trained screw-driver mechanics.

TEST INSTRUMENTS — TROUBLE-SHOOTING — REPAIR

Read from the beginning, it is a complete servicing course from A to Z. Used for reference, it is an invaluable means of "brushing up" on any work that puzzles you. Gives complete information on all essential service instrument types; how they work (with wiring diagrams), how, when, and why to use them; how to build your own; preliminary

trouble checks; circuit and parts analysis; parts repair, replacement, substitution; obscure troubles; aligning and neutralizing; interference reduction — and **HUNDREDS** of other subjects including How to Start and Operate a Successful Radio-Electronic Service Business. 706 illustrations; 720 self-testing review questions. Only \$5 complete (\$5.50 foreign).

MONEY-SAVING OFFER!

Get **BOTH** the *Handbook* and *Modern Radio Servicing* — radio's most famous complete service library totaling over 2030 pages — at a bargain combination price. See coupon.

5-DAY MONEY-BACK GUARANTEE

MURRAY HILL BOOKS, Inc. Dept. S-16, 232 Madison Avenue, New York 16, N. Y. Enclosed find \$..... for books checked; or [] send C.O.D. (in U.S.A. only) for this amount plus postage. If not fully satisfactory, I may return the books at the end of 5 days and receive my money back.

- [] **RADIO TROUBLE SHOOTER'S HANDBOOK** \$5 (\$5.50 foreign)
- [] **MODERN RADIO SERVICING** \$5 (\$5.50 foreign)
- [] **MONEY SAVING COMBINATION**. Both books for only \$9.50 (\$10.50 foreign)

Name

Address


City & Dist. No. State

(Please print or write plainly.)

Everything FOR THE SERVICE DEALER

We have, ready for immediate delivery, a complete stock of tools, replacement parts, inter-communication systems, public address systems, test equipment . . . everything in radio equipment for the progressive service dealer. For big profit items . . . for quick delivery . . . place your order now with Leo.

6 TUBE AC-DC KIT

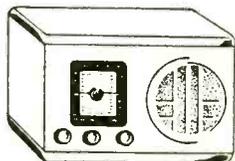

Complete, ready for assembly.

\$23.75

Cat. No. 7-691

A two-band, superheterodyne kit with all tubes, speaker, chassis, and all parts for easy assembly. Broadcast band from 540 to 1620 KC. Short wave from 5.7 to 18.3 MC. Cabinet, \$5.25.


WRL MULTITESTER

All purpose tester. Money back guarantee.

\$18.75

less leads

Cat. No. 16-439

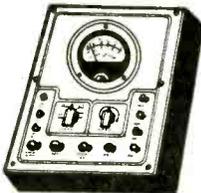


Handles AC DC Voltmeter, DC Milliammeter, high and low range Ohmmeter. 3" meter with sturdy D'Aronsva movement. Size 5½x8x3¼.

Exclusive at WRL!

Our latest flyer . . . 12 page V-J edition of merchandise and radio values. FREE.

Handy Tube-Base Calculator . . . 25c

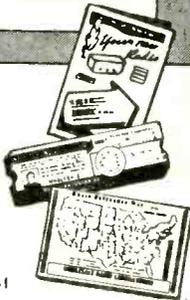Giant Radio Reference Map, 3½x4½ ft. . . 15c



MAIL TODAY 5c

Wholesale Radio Laboratory
744 West Broadway Council Bluffs, Iowa

Rush _____ WRL Multitesters. Cost, \$ _____

Send _____ 6-tube AC DC Kits and cabinets. Cost, \$ _____

I want a tube-calculator. 25c enclosed.

Ship me your radio map. 15c enclosed.

Send me your new V-J Flyer free.

Enclosed is \$ _____; Balance C.O.D.

Name _____

Address _____

Town _____

State _____

I am an amateur; experimenter; service man.



We invite industrial inquiries for electronic equipment and devices of all kinds.

QUICK SERVICE FROM LEO
"same day" delivery service from the heart of the nation . . . on anything in radio. Order today.

**Wholesale
RADIO LABORATORIES**

SER-CUITS

(Continued from page 26)

the voice coil is grounded and the high end is connected to the screen through a blocking capacitor and across a resistor-straight resistance coupling. The constants differ in the various models but the circuits are the same.

Stewart Warner 9002-A, B, P, R

In Fig. 1 appears a 5-tube and rectifier a-c/d-c single-band model, 9002-A, B, P, R, with the external antenna directly connected to the loop. The coupling transformer between the r-f amplifier and 12SA7 converter has a secondary tap for the signal grid for sharper tuning. A cathode tickler type oscillator is used. All tuning capacitors as well as transformers and loop center tap are returned to the avc bus instead of B- or ground. The B- is grounded through a .2-mfd capacitor and 220,000 ohms in parallel.


As previously mentioned, the 12SF7 i-f amplifier contains the single diode used for detector and avc. A 47-ohm resistor from cathode to B- provides a bit of bias. The detection capacitor of 110 mmfd returns to B-, while the detector load resistance composed of 47,000 ohms and a ½-megohm volume control returns to the first audio cathode and then to B- through a 2,200-ohm bias resistor. The audio pick-off is through a .002-mfd capacitor to grid and a 10-megohm grid leak. Since the signal voltage is supplied between grid and cathode directly, no bypass capacitor is required across the cathode bias resistor, there being no common coupling between grid and plate return circuits.

A hum and decoupling filter of 220,000 ohms and .05 mfd is used for the 12SK7 first audio plate. A 2.2-megohm screen supply resistor serves also as a coupling resistor for the degenerative feedback loop from the output transformer through a .02-mfd blocking capacitor and screen bypass.

Power Amplifier

A 35L6 power amplifier has a 130-ohm unbypassed resistor for bias, a .01-mfd output capacitor and p-m speaker load. The output transformer primary is tapped for hum bucking. This permits the 35L6 plate to be supplied directly from the 35Z5 rectifier. Hum, or filter ripple, is attenuated in the same manner as in a push-pull amplifier where the primary is tapped so that ripple currents travel in opposing directions through the winding, causing their cancellation. Here, the out-

M U E L L E R

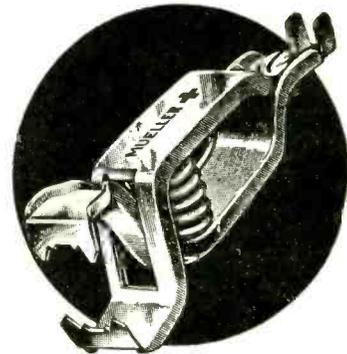

CLIPS

For Quick Temporary Connections

- Made in 10 sizes—from the tiny wee-pee-wee to the 300 ampere Big Brute.
- Offered in both steel and solid copper.
- Red and black rubber insulators to fit each size.
- A complete line with

A CLIP FOR EVERY PURPOSE

Send for free samples and catalog 810

Mueller Electric Co.

1565 E. 31st St. - Cleveland, Ohio

FILTER CONDENSER Bargains!



Thousands of rugged, oil-filled, oil-impregnated condensers at ridiculously low prices. Write for list! New Time Payment Plan if desired.

BIG NEW CATALOG!

By mailing us your name and address, you will be among the first to get a copy of our own big new catalog, plus latest announcements of new and bargain components and equipment. Write today! Address Dept. S of nearest Newark branch.



CHICAGO
Newark ELECTRIC Company

115-117 W. 45th St. NEW YORK 19 323 W. Madison St. CHICAGO 6

put tube load is balanced against the total drain of all plates and screens (except the 35L6 plate) through a 1,500-ohm filter and audio load resistor. A 33-ohm anti-surge resistor and .05-mfd r-f bypass are associated with the 35Z5 power rectifier.

(Continued on page 46)


POSTWAR RECEIVERS




Above, Farnsworth portable loop type, single-band receiver, type EP-351. Below, Farnsworth table model television receiver.



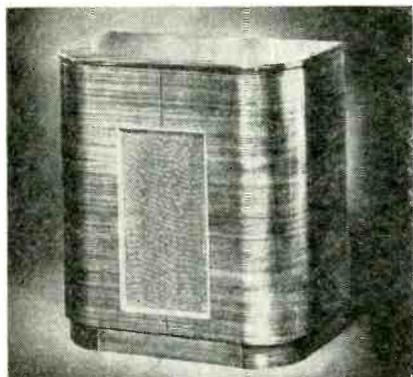Below, Farnsworth 6-tube automatic record changer console, type EX-263.



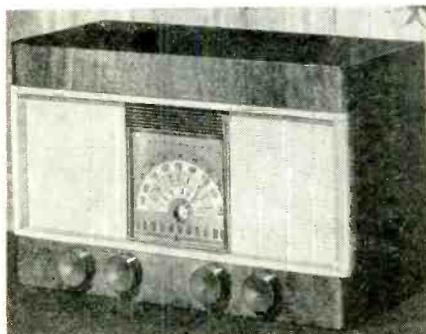Below, Echophone 5-tube, 3-band a-c/d-s table model, type EC-103.



Wait for these new


HICKOK

Radio Service Instruments

*If It Isn't A Hickok Indicating
Micromhos It's Not
Dynamic Mutual Conductance*



Model 532
Tube Tester

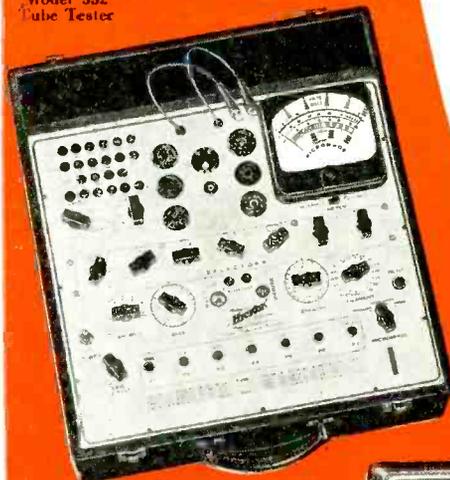

Model 534
All Purpose Tube and Set Tester

Your patience in waiting for these new 1946 HICKOK models will be richly rewarded for these new HICKOK tube and set testers make still closer tests, with finer accuracy, rejecting tubes that might get by with an ordinary tester.

Now you have 7 selector switches instead of 2. That aims to prevent obsolescence. Isn't that worth waiting for?

What's more, Dynamic Mutual Conductance, indicated in Micromhos, is a duplicate of the manufacturers' method of checking when he makes the tubes. Remember, if it isn't a HICKOK Indicating Micromhos, it isn't Dynamic Mutual Conductance.

The new Electronic Volt-Ohm-Capacity Milliammeter Model 203 reads as low as 1.0 mmf and up. It will measure at frequencies to over 10 mc with no frequency error and the ohm meter will measure up to 10,000 megohms.


Keep patiently in touch with your jobber and you will soon get the instruments that are held in highest esteem.



Model 203
Electronic Volt-Ohm Capacity Milliammeter

THE HICKOK ELECTRICAL INSTRUMENT CO.

10521 Dupont Avenue
Cleveland 8, Ohio

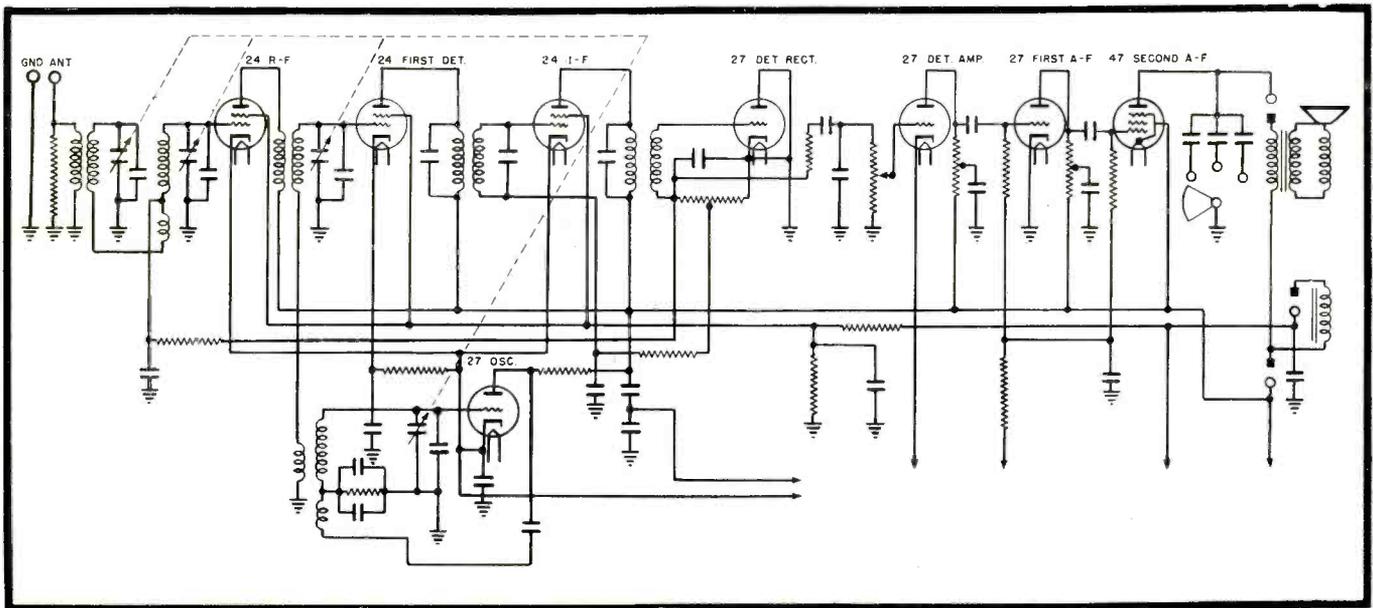

Figs. 1 (left) and 3 (above). Fig. 1. Circuit of the Philco 38-7. This diagram is used to illustrate the possible sources of intermittent operation. Three such sources are padder capacitors, particularly mica types, defective wiring or cold solder joints, or a loose voice-coil connection. The use of a signal tracer facilitates the localization of the particular circuit responsible. Fig. 3. Philco model 90. In this receiver, breakdown of the bypass capacitors causes a high-pitched squeal, and intermittent reception. The defective capacitor may be found by bridging the suspected capacitor with a .25-mfd. capacitor and noting if the receiver returns to normal.

INTERMITTENTS

should be directed to move only one part or element of the set at a time, since excessive vibration or jarring may extend throughout the set and make it difficult to locate the real cause of the intermittent operation.

If wriggling the bandswitch causes noise and intermittent operation, the contacts of the switch should be cleaned with carbon tetrachloride or an equivalent solvent. The soldered joints on the switch should be *gone over* with a hot soldering iron. Noise and cutting on and off at the low-frequency end of the dial, while the high frequency end is all right, indicates that rubbing and shorting tuning capacitor plates are causing the low-frequency trouble. Should the set cut on and off as the volume control is adjusted, it's likely the control itself is defective and in need of replacement.

In some sets of this kind, where a sharp break in reception occurs, the wires leading from the loudspeaker to the rectifier and output tube circuits may not be securely soldered, and the

make and break of the end of a wire or wires will cause intermittent operation that shows up when the speaker cable or wiring is *wiggled* by hand. In some cases the wires themselves are defective, due to rotted insulation causing short circuits between the wires or between the wires and chassis.

A loose connection anywhere in the set may cause noise as well as intermittent reception. The trimmers in the

antenna and oscillator circuits or the padder in the Philco 38-7, Fig. 1, could cause such trouble. A loose voice-coil connection could be responsible and some peculiar intermittents have been traced to such sources. Many such faults may be located by carefully inspecting the wiring and chassis, using a small penlight or flashlight which augments the regular shop lighting or
(Continued on page 39)

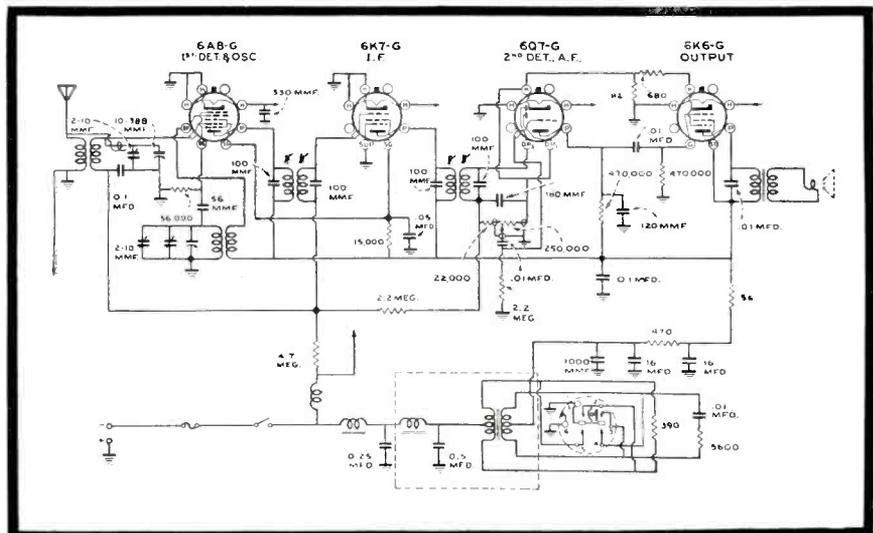


Fig. 2. RCA auto receiver, model 94 BT6. Most intermittents in auto receivers can be traced to the vibrator and power supply system. Two frequent offenders are the 1000-mmfd. and the .01-mfd capacitors in the vibrator circuit.

JANUARY, 1945 — DECEMBER, 1945

AMPLIFIERS

4-Plant Transformer-Type Volume-Level Control Unit Aug.
 20 Watt Mobile P-A (Silvertone 8919) Sept.
 60-Watt Amplifier Aug.
 A-F Amplifier Testing. *By Willard Moody*. Mar.
 Air King 4034 (I-F Amplifier) Nov.
 Allied D-366 (I-F Amplifier) Nov.
 Amplifiers and Systems, Intercommunicator. *By A. A. Ghirardi*. Jan.
 Amplifiers, I-F. *By R. L. Martin*. Apr.
 Amplifier Terminal Connections for Audiograph Oct.
 Amplifier Terminal Connections for Erwood Oct.
 Amplifier Terminal Connections for Magnavox Oct.
 Amplifier Terminal Connections for Operadio Oct.
 Amplifier Terminal Connections for RCA Oct.
 Amplifier Terminal Connections for Stromberg-Carlson Oct.
 Amplifier Terminal Connections for Webster-Rauland Oct.
 Audiograph Amplifier Terminal Connections. Oct.
 Bogen Amplifier Terminal Connections. Oct.
 G.E. 60 (I-F Amplifier) Nov.
 G.E. L-243 (I-F Amplifier) Nov.
 I-F Amplifiers. *By L. E. Edwards*. Nov.
 High Fidelity Amplifier (Magnavox A-3001 C) Nov.
 Marine P-A Systems. *By Martin W. Elliott*. Sept.
 Mixer Circuit Aug.
 P-A Output Amplifier Design. *By W. Moody*. May
 Phase Inverters, and Push-Pull Amplifiers. *By E. Arthur*. May
 Power Amplifiers Aug.
 Push-Pull Amplifiers and Phase-Inverters. *By E. Arthur*. May
 Separate Room Amplifier Aug.
 Silvertone 8935-8942 (35-w Amplifier) Aug.
 Silvertone 8950 (30-w Amplifier) Feb.
 Spiegel 1-40 (I-F Amplifier) Nov.
 Stromberg-Carlson 515 FM (Amplifier Sections Only) Aug.
 Terminal Connections for Unlabeled Amplifiers (Audiograph, Bogen, Erwood, Magnavox, Operadio, RCA, Stromberg-Carlson, Webster-Rauland) Oct.
 Ward 04WG-2672 (I-F Amplifier) Nov.
 Ward 62-262 (Mixer) Nov.
 Ward 62-319 (I-F Amplifier) Nov.
 Wells-Gardner A-7 (I-F Amplifier) Nov.
 Westinghouse M 104 (I-F Amplifier) Nov.
 Westinghouse WR 678 (I-F Amplifier) Nov.

ANTENNAS

Air King 4136 (Input Circuit) Sept.
 Allied D174 (Input Circuit) Sept.
 Antennas, F-M. *By W. Moody*. Jan.
 Belmont 533 (Input Circuit) Oct.
 Continental C7 Input Circuit Sept.
 Detrola (Input Circuit) Oct.
 Firestone S-7400-1 (Input Circuit) Sept.
 G.E. L642 (Input Circuit) Oct.
 General Television 530 (Input Circuit) Sept.
 Input Circuits (Part II). *By L. E. Edwards*. Oct.
 Lafayette BB9 (Input Circuit) Oct.
 Meek Industries RC-5C5 Loop Receiver Nov.
 Philco 42-853 (Input Circuit) Oct.
 Philco 42-854 (Input Circuit) Sept.
 Philco 42-1004 Input Circuit Sept.
 Receiver Input Circuits. *By L. E. Edwards*. Sept.
 Scott, Laurette Model (Input Circuit) Sept.
 Traps, Wave. *By W. Moody*. July

CONDENSERS

Auto Sets for Home Use, Simplified Conversion of. *By J. George Stewart*. July
 Condenser Servicing, Variable (Part I). *By E. Arthur*. July
 Variable Condenser Servicing. (Part II) *By E. Arthur*. Aug.

CONVERTERS

F-M Converters May
 Meissner 9-1047 (F-M Adaptor) Mar.

CHARTS

Ceramic, (RCA) Capacitor Color Code Charts May

COVER DIAGRAMS

5-Tube Postwar Receiver (Stromberg-Carlson 1000 H, J-1100H) Dec.
 30-watt Amplifier (Silvertone 8950) Feb.
 Emerson CJ449 (Record Player Circuit) June
 Emerson GL-457 (2-w Phono-Amplifier) Oct.
 G. E. HM 225B/226B (Television I-F System) July
 Magnavox A-205 (Record Player) Apr.
 Magnavox A-3001C (High Fidelity A-F Amplifier) Nov.
 Philco 41-R-6 (Record Player) Jan.
 Silvertone 8919 (20-w P-A) Sept.
 Stromberg-Carlson 515 FM (R-F and I-F Amplifier Section of a 7-tube F-M Receiver) Aug.
 Television Deflection Circuit (RCA TRK-12) Mar.

EDITORIALS

Allotment of Replacement Parts; Misrepresentation May
 F-M Allocations; Radio Fundamentals Books; Video Sets July
 Hiring Service Men; Set Failures; Time Records Apr.
 Housing Development Servicing Opportunities; Letters of Questions Offering Problems; Miniature Receivers Oct.
 Opportunities for 1946 Dec.
 Part Shortages; Need for F-M Studies by Service Men June
 Postwar Aircraft Expansion; Postwar F-M Receivers Nov.
 Postwar Receivers Dec.
 Production Line Methods in Servicing Jan.
 Receiver Failures; Repair Charges Sept.
 Receivers and Accessories; F-M Broadcasting Aug.
 Service Charges and Hearing Aid Servicing Feb.
 Sound System Servicing Mar.

ELECTRONIC APPLICATIONS

Cathode-Ray Tubes. *By S. J. Murcek*. July
 Cells, Photoelectric. *By W. Moody*. Oct.
 Direct Viewing Television July
 Electronic Alarm Systems. *By W. Moody*. Nov.
 Electronic Spotwelding Timers. *By S. J. Murcek*. Apr.
 F-M Discriminators. *By J. G. Stewart*. Aug.
 Indicators, F-M Tuning. *By J. G. Stewart*. Oct.
 Oscillographs, C-R. *By S. J. Murcek*. Sept.
 Servicing The Oscillograph. *By S. J. Murcek*. Dec.

FEATURES

350-Speaker P-A System Dec.
 A 6-Plant Sound System. *By Harold Lewis*. June
 A Dealer in Buzz-Bomb Alley. *By A. W. Lines*. Jan.
 A-F Amplifier Testing. *By Willard Moody*. Mar.
 Annual Index (1944) Jan.
 Automatic Noise Limiters. *By Thomas T. Donald*. Dec.
 Auto Set Dial Cord Installation Notes (For Chrysler C-1708; Ford F-1740; Lincoln L-1760, 61; Studebaker S-1722, S-1726) Feb.
 AVC-Detector-AF Systems. *By Robert L. Martin*. Dec.
 C Biasing. *By Edward Arthur*. Mar.
 Cathode-Ray Tubes (Part I) (Design, Application, Servicing). *By S. J. Murcek*. July
 Cathode Ray Tubes (Design, Application Servicing). *By S. J. Murcek* (Part II) Aug.
 Communications Receivers' Beat Frequency Oscillators. *By Thomas T. Donald*. Oct.
 Connections for Unlabeled Amplifier Terminals (Audiograph, Bogen, Erwood, Magnavox, Operadio, RCA, Stromberg-Carlson, Webster-Rauland) Oct.

Cross Modulation, Beat Notes and R-F Modulation. *By A. M. Ross*. Dec.
 Crystal-Controlled Oscillators. *By J. George Stewart*. Nov.
 Crystal Filters Used in Communications Receivers. *By Thomas T. Donald*. Nov.
 Crystal Pickups (Data for 17 RCA Types) Feb.
 C-R Oscillographs (Applications—Servicing, Part III). *By S. J. Murcek*. Sept.
 C-R Oscillographs (Applications—Servicing, Part IV). *By S. J. Murcek*. Oct.
 C-R Oscillographs (Applications—Servicing, Part V). *By S. J. Murcek*. Nov.
 Direct Viewing Television July
 Electronic Alarm Systems. *By Willard Moody*. Nov.
 Electronic Spotwelding Timers. *By S. J. Murcek*. Apr.
 Extending Ammeter Ranges with Shunts. *By Lewis J. Boss*. May
 Fixed Resistors (Part 1). *By Alfred A. Ghirardi*. Mar.
 Fixed Resistors (Troubles and Service Hints, Part II). *By Alfred A. Ghirardi*. Apr.
 Fixed Resistor Replacement and Substitutions (Part III). *By Alfred A. Ghirardi*. May
 F-M Antennas. *By Willard Moody*. Jan.
 F-M Converters May
 F-M Discriminators. *By J. George Stewart*. Aug.
 F-M Limiters. *By J. George Stewart*. Sept.
 High Fidelity. Recorded Music Reproduction. *By Willard Moody*. Feb.
 Hiring Service Men. *By Charles and H. A. Middleton*. Feb.
 Hum (Its Causes and Cures). *By Edward Arthur*. Apr.
 I-F Amplifiers. *By Robert L. Martin*. Apr.
 I-F Amplifiers. *By L. E. Edwards*. Nov.
 Input Circuits (Part II). *By L. E. Edwards*. Oct.
 Interstation Noise Suppression. *By J. George Stewart*. Dec.
 Intercommunicator Amplifiers and Systems. *By A. A. Ghirardi*. Jan.
 Loudspeaker Additions for Improved Tone Quality. *By Willard Moody*. June
 Loudspeaker Matching. *By E. B. Menzies*. Jan.
 Marine P-A Systems. *By Martin W. Elliott*. Sept.
 Old Timers' Corner Jan.
 Old Timers' Corner Feb.
 Old Timers' Corner Mar.
 Old Timers' Corner Apr.
 Old Timers' Corner May
 Old Timers' Corner June
 Old Timers' Corner July
 Old Timers' Corner Aug.
 Old Timers' Corner Sept.
 Old Timers' Corner Oct.
 Old Timers' Corner Nov.
 Old Timers' Corner Dec.
 Output Design in P-A Amplifiers. *By Willard Moody*. May
 Past, Present and Future Status of Tone Quality. *By Arnold Peters*. Mar.
 Photoelectric Cells. *By Willard Moody*. Oct.
 Postwar Receiver Components and Accessories. *By Donald Phillips*. Feb.
 Postwar Receivers Oct.
 Postwar Receivers Dec.
 Power Amplifiers Aug.
 Power Transformer Replacements and Substitutions. *By Edward Arthur*. June
 Power Transformer Servicing. *By Arnold D. Peters*. May
 Power Tube Substitutions. *By B. W. Kay*. Aug.
 Push-Pull Amplifiers and Phase Inverters. *By Edward Arthur*. May
 RCA Ceramic Capacitor Color Code Charts. May
 Receiver Input Circuits. *By L. E. Edwards*. Sept.
 Second Detector and AVC Systems. *By Robert L. Martin*. Aug.
 Ser-cuits. *By Henry Howard*. Jan.
 Ser-cuits. *By Henry Howard*. Feb.
 Ser-cuits. *By Henry Howard*. Mar.
 Ser-cuits. *By Henry Howard*. Apr.
 Ser-cuits. *By Henry Howard*. May
 Ser-cuits. *By Henry Howard*. June
 Ser-cuits. *By Henry Howard*. July
 Ser-cuits. *By Henry Howard*. Aug.
 Ser-cuits. *By Henry Howard*. Sept.
 Ser-cuits. *By Henry Howard*. Oct.
 Ser-cuits. *By Henry Howard*. Nov.
 Ser-cuits. *By Henry Howard*. Dec.
 Service Helps. *By Edward Arthur*. Feb.
 Service Helps Mar.
 Servicing Helps Apr.

Servicing Helps	May
Servicing Helps	June
Servicing Helps	July
Servicing Helps	Aug.
Servicing Helps	Sept.
Servicing Helps	Oct.
Servicing Helps (Recentering Loudspeaker Cones)	Nov.
Servicing Helps	Dec.
Servicing The Oscillograph	Dec.
Simplified Conversion of Auto Sets for Home Use	July
Sub-Miniatures	Dec.
Superheterodyne Mixers (Part I)	Oct.
Superheterodyne Mixers (Part II)	Nov.
Test Equipment in the Postwar Era	Jan.
Use of Resistors in Tube Substitutions	June
Use of Resistors in Tube Substitutions	July
Variable Condenser Servicing (Part I)	July
Variable Condenser Servicing (Part II)	Aug.
Volume and Tone-Control Resistors	Aug.
Volume and Tone Control Resistors (Part VIII of a Series on Receiver Components)	Sept.
Volume and Tone Control Resistors (Part VIII of a Series on Receiver Components)	Oct.
Volume and Tone Control Resistors (Part IX of a Series on Receiver Components)	Nov.
Volume and Tone-Control Resistors (Part X)	Dec.
Volume Control Circuits (Part I)	June
Volume Control Circuits (Part II)	July
Wave Traps	July

HUM

Hum	Apr.
-----	------

INTERCOMMUNICATORS

G.E. FM 41 (Intercommunicator)	Jan.
Operadio 4208-12 (Intercommunicator)	Jan.
Remler 2030 (Intercommunicator)	Jan.
Remler 2050 (Intercommunicator)	Jan.
USL-300 (Intercommunicator)	Jan.
USL-303 (Intercommunicator)	Jan.

LIMITERS, DISCRIMINATORS, AVC; AFC AND DETECTORS

AVC-Detector-AF Systems	Dec.
Detrola 408 (AVC/Detector/A-F)	Dec.
Discriminators, F-M	Aug.
Emerson FM-460 (Magic Eye Circuit)	Oct.
Espey 2170 (Magic Eye Circuit)	Oct.
Espey F-M (F-M/I-N-S)	Dec.
F-M Limiter, Freed 40	Sept.
F-M Limiter, Emerson 460	Sept.
F-M Limiter, G.E. 40	Sept.
F-M Limiter, Motorola FM 82	Sept.
F-M Tuning Indicators	Sept.
Freed 57-71 (Magic Eye Circuit)	Oct.
Freed 57A-71A (F-M/I-N-S)	Dec.
G.E. J FM 90 Discriminator	Aug.
G. E. L 651 (AVC/Detector/A-F)	Dec.
G. E. 20 (AVC/Detector/A-F)	Dec.
Hallcrafters SX-28 (A-N-L)	Dec.
Hammarlund SP-200X (A-N-L)	Dec.
Limiter, F-M, Emerson 460	Sept.
Limiter, F-M, Freed 40	Sept.
Limiter, F-M, G.E. 40	Sept.
Limiter, F-M, Motorola FM 82	Sept.
Limiters, F-M	Sept.
Meissner 9-1053-4 (F-M/I-N-S)	Dec.
National NHU (A-N-L)	Dec.
National NC-44B (AVC/Detector/A-F)	Dec.
Pilot 300 (Discriminator)	Aug.
RCA QB1 (AVC/Detector/A-F)	Dec.
RCA QU 52C (AVC/Detector/A-F)	Dec.
RME 31-42 (A-N-L)	Dec.
RWT B 92 (AVC/Detector/A-F)	Dec.
Second Detector and AVC Systems	Aug.
Stromberg-Carlson 25 (Discriminator)	Aug.

Ward BR-474 (AVC/Detector/A-F)	Dec.
Ward 62-271 (AVC/Detector/A-F)	Dec.
Zenith 12H678 (Discriminator)	Aug.

NOISE

Automatic Noise Limiters	Dec.
Cross Modulation, Beat Notes and R-F Whistles	Dec.
Interstation Noise Suppression	Dec.

OSCILLATORS

Continental G4 (Mixer Circuit)	Oct.
Coronada C6D18 (Mixer Circuit)	Oct.
Garod 1C712 (Mixer Circuit)	Oct.
G.E. JCP596 (Mixer Circuit)	Oct.
G.E. L540 (Mixer Circuit)	Oct.
Hallcrafters SX 28 (Beat-Frequency Oscillator)	Oct.
Lafayette C-37 (Mixer)	Nov.
Mixers, Superheterodyne	Oct.
National NHU (Beat-Frequency Oscillator)	Oct.
Oscillators, Beat Frequency, Communications Receivers	Oct.
Oscillators, Crystal-Controlled	Nov.
Philco 41 KR (Mixer Circuit)	Oct.
RME 41-43 (Beat Frequency Oscillator)	Oct.
Silvertone 7091-7093 (Mixer Circuit)	Oct.
Superheterodyne Mixers (Part I)	Oct.
Superheterodyne Mixers (Part II)	Nov.

PARTS

Crystal Pickups	Feb.
Fixed Resistor Replacement and Substitutions	May
Fixed Resistors	Mar.
Fixed Resistors	Apr.
Postwar Receiver Components and Accessories	Feb.
Resistors, Use of, in Tube Substitutions	June
Resistors, Volume and Tone Control (Part VIII)	Oct.
Tone and Volume Control Resistors	Sept.
Use of Resistors in Tube Substitutions	July
Volume and Tone-Control Resistors	Aug.
Volume and Tone Control Resistors	Nov.
Volume and Tone Control Resistors	Dec.

PHOTOCELLS

Photoelectric Cells	Oct.
---------------------	------

PHONOGRAPHS, PICK-UPS, RECORD PLAYERS, ETC.

Crystal Pickups	Feb.
Emerson CJ-449 (Wireless Record Player)	June
High-Fidelity Recorded Music Reproduction	Feb.
Magnavox A-205 (Record Player)	Apr.
Philco 41-RP-6 (Record Player)	Jan.
Two-Stage Record Player (Emerson GI 457)	Oct.

POWER SUPPLIES

Power Transformer Replacements and Substitutions	June
Spotwelding Timers, Electronic	Apr.

RECORDING

High-Fidelity Recorded-Music Reproduction	Feb.
---	------

RECEIVERS

Auto Sets for Home Use, Simplified Conversion of	July
Beat Frequency Oscillators of Communication Receivers	Oct.
Coronada C1100 (11 tube—5 bands) Receiver	Oct.
Crystal Filters Used in Communications Receivers	Nov.
Detrola 568 (Postwar Model)	Nov.
Detrola 568 (a-c/d-c 2-band)	Nov.
Emerson 460 (F-M Limiter)	Sept.
Emerson 363 (2-band a-c/d-c Portable)	May
Emerson EX 386 (3-band a-c/d-c)	May
Fada 204 (2-band)	Aug.
Farnsworth BT-22 (2-band) Receiver	Oct.
Freed 40 (F-M Limiter)	Sept.
Garod 3P 1812 (A-M/F-M/S-W Receiver)	Apr.
Garod 3P 1812 (A-M/F-M/S-W Receiver)	May
Garod High Fidelity Receiver	Nov.
G.E. LB 530 A-C/2-Volt Battery Receiver	Sept.
G.E. RHJS-10005 (3-Band Receiver)	May
Hallcrafters S-36A (F-M/A-M)	June
Hallcrafters SX 18 (Crystal Filter)	Nov.
Hallcrafters SX 28 (Crystal Filter)	Nov.
Hammarlund Super-Pro (Crystal Filter)	Nov.
Input Circuits, Receiver	Sept.
Meck Industries RC-5C5 (Postwar Model)	Nov.
Motorola 59 BP1/2 (4-tube Portable)	July
Motorola B150 (3 tube) Receiver	Oct.
Motorola FM-82 (F-M 42.50 mc Band)	Apr.
Motorola FM 82 (F-M Limiter)	Sept.
Motorola 61L11/61L12 (Input Circuit)	Sept.
Motorola 65 BP 1-2-3-4 (6-tube a-c/d-c/battery)	Dec.
National NC 100 XAB (Crystal Filter)	Nov.
Philco 41-609 (3-band, light beam)	Feb.
Philco 42-245 (3-band, 7-tube)	Feb.
Philco 730A (t-r-f Receiver)	Feb.
Receivers, Postwar	Oct.
Receiver Sales, Servicing and Repairs	Sept.
RCA 26BP (t-r-f Portable)	Aug.
RCA VHR-212 (2 band)	June
RME 41-43 (Crystal Filter)	Nov.
Sentinel 237 (a-c/Battery Receiver)	Apr.
Scott F-M Tuner	June
Silvertone R81 (Television Receiver)	Feb.
Stromberg-Carlson 1000H, J-1100H (5-tube a-c/d-c)	Dec.
Truetone D-1042 (11-tube a-m Hi-fidelity) Mar.	
Truetone D1182 (a-c/d-c Battery Portable)	Sept.
Ward 93 WG-1000/1001 (10-Tube High-Fidelity)	Dec.

RECTIFIERS

Detrola 571 (a-c/d-c 4 Tube and Rectifier Unit)	Nov.
Electronic Spotwelding Timers	Apr.

SERVICE HINTS AND KINKS

A-F Amplifier Testing	Mar.
Auto Set Dial Cord Installation Notes	Feb.
Arwin 302	Mar.
Columbia SG 8	July
Components and Accessories, Postwar Receiver	Feb.
Condenser Servicing, Variable (Part II)	Aug.
Crosley 1336	Mar.
DeWald 555	Feb.
Dial Drive Installation Notes	Dec.
Emerson 109, Chassis U4A	July
Emerson 1941-42 Portables	Mar.
Emerson CR-243	Mar.
Emerson 255	June
Fada 207 APT	Feb.
G.E. 60	Dec.
G.E. I1639	Mar.
G.E. L500 Series	Oct.
Grunow 1151	Feb.
Magnavox CR-171	Feb.
Magnavox C178	Aug.
Majestic 91	Mar.
Mopar 600 (Chrysler)	Mar.
Motorola 9-44M 9-49	June
Motorola 51F11	Feb.
Motorola 51X12	Mar.
Motorola 161L12	Feb.
Philco 38-39	Mar.
Philco 610	Aug.

Philco C1450. *By David B. Chambers*. Aug.
 Power Transformer Servicing. *By A. D. Peters*. May
 Resistors, Fixed (Part II). *By A. A. Ghirdardi*. Apr.
 Silvertone 1970. *By Edward Goldschmidt*. June
 Sparton 410, 420. Dec.
 Stewart-Warner 07-511. *By George Ryan*. Mar.
 Stewart-Warner R137. *By David B. Chambers*. Aug.
 Synchronous Motor Record Players. Dec.
 Terminals, Connections for Unlabeled Amplifier. Oct.
 Truetone 13746. *By David B. Chambers*. Aug.
 U. S. Radio and Television 28. *By Edward Goldschmidt*. July
 Variable Condenser Servicing. (Part I). *By E. Arthur*. July
 Zenith 6C 301. *By Willard Moody*. May
 Zenith 6D 410, 411, 413, 414, 425, 426, 427, 446, 455 (Chassis 5659, 5660, 5663, 5664). From Zenith Shop Notes. Apr.
 Zenith 6R683. *By Edward Arthur*. Feb.
 Zenith 6 S 439, 469 (Chassis 5678) From Zenith Shop Notes. May
 Zenith 7S432, 33, 34; 449, 50; 458; 460; 461, 2; 487, 88 (Chassis 5724) From Zenith Shop Notes. Mar.
 Zenith 7 S 633, 634, 637 (Chassis 7801) From Zenith Shop Notes. May
 Zenith 8S432, 434, 449, 450, 458, 459, 460, 461, and 462 (Chassis 5810). *By Edward Goldschmidt*. July
 Zenith 703, 06, 07; 711, 750; 712; Chassis 2052. *By Edward Goldschmidt*. July

SOUND

350-Speaker P-A System. Dec.
 Marine P-A Systems. *By M. W. Elliott*. Sept.
 P-A Amplifiers, Output Design in. *By W. Moody*. May
 Sound System, A 6-Plant. *By H. Lewis*. June

SPEAKERS

6-Plant Sound System, A. *By H. Lewis*. June
 Loudspeaker Additions for Improved Tone Quality. *By H. Moody*. June
 Loudspeaker Matching. *By E. B. Menzies*. Jan.
 P-A Systems, Marine. *By Martin W. Elliott*. Sept.

Recentring Loudspeaker Cones. *By F. C. Keene*. Nov.

TELEVISION

G.E. HM 225B/226B. (Television I-F System). July
 RCA TRK-12 (Television Receiver). Mar.
 Silvertone R81 (Television Receiver). Feb.
 Television, Direct Viewing. July

TEST EQUIPMENT

Ammeter Ranges, Extending with Shunts. *By L. J. Boss*. May
 C-R Oscillographs. *By S. J. Murcek*. Sept.
 G.E. TC-3, 3P (Tube Checker). Mar.
 G.E. UM-3 (Portable Utility Tester). Jan.
 Oscillographs, C-R. (Part V). *By S. J. Murcek*. Nov.
 Servicing the Oscillograph. *By S. J. Murcek*. Dec.
 Test Equipment in the Postwar Era. *By L. A. Goodwin, Jr.*. Jan.

TOPE COMPENSATION

Tone Quality, Loudspeaker Additions for Improved. *By W. Moody*. June
 Tone Quality, Past, Present and Future Status of. *By A. Peters*. Mar.
 Volume and Tone Control Resistors (Part VIII). *By Alfred A. Ghirdardi*. Oct.
 Volume and Tone-Control Resistors (Part X). *By Alfred A. Ghirdardi*. Dec.

TRANSFORMERS

Transformer, Power, Replacements and Substitutions. *By E. Arthur*. June
 Transformer Servicing, Power. *By A. D. Peters*. May

TUBES

C Biasing. *By E. Arthur*. Mar.
 Oscillographs, C-R (Part IV). *By S. J. Murcek*. Oct.
 Power Tube Substitutions. *By B. W. Kay*. Aug.
 Sub-Miniatures. *By Roger Etton*. Dec.
 Tube Substitutions. *By Willard Moody*. May
 Tubes, Cathode-Ray. *By S. J. Murcek*. July
 Tubes, Cathode-Ray. *By S. J. Murcek*. Aug.
 Tuning Indicators, F-M. *By J. G. Stewart*. Oct.

VOLUME CONTROLS

Tone and Volume Control Resistors (Part VIII). *By Alfred A. Ghirdardi*. Oct.
 Volume and Tone-Control Resistors (Part X). *By Alfred A. Ghirdardi*. Dec.
 Volume Control Circuits. *By R. L. Martin*. June
 Volume Control Circuits. *By R. L. Martin*. July

WARTIME SERVICING

Condenser Servicing, Variable. (Part I). *By E. Arthur*. July
 Erwood Amplifier Terminal Connections. Oct.
 Extending Ammeter Ranges with Shunts. *By L. J. Boss*. May
 Magnavox Amplifier Terminal Connections. Oct.
 Operadio Amplifier Terminal Connections. Oct.
 Power Tube Substitutions. *By B. W. Kay*. Aug.
 RCA Amplifier Terminal Connections. Oct.
 RCA Ceramic Capacitor Color Code Charts. May
 Resistor Replacement and Substitutions. *By A. A. Ghirdardi*. May
 Resistors, Volume and Tone-Control. *By A. A. Ghirdardi*. Aug.
 Stromberg-Carlson Amplifier Terminal Connections. Oct.
 Tube Substitutions, Power. *By B. W. Kay*. Aug.
 Use of Resistors in Tube Substitutions. *By A. A. Ghirdardi*. June
 Variable Condenser Servicing (Part II). *By E. Arthur*. Aug.
 Webster-Rauland Amplifier Terminal Connections. Oct.

AGAIN AVAILABLE!

RADIO · TELEVISION · ELECTRONIC

SERVICE

GROUP SUBSCRIPTION PLAN

12 ISSUES ONLY \$1

Saves Fifty Per Cent of the Subscription Price if Four or More Orders, Including Your Own, Are Properly Entered on This Form

Name
 Address
 City-State
 Occupation
 Title (Service Mgr., etc.)
 Employed by
 State whether Employer is a Service Organization, Dealer, Jobber or Manufacturer

Name
 Address
 City-State
 Occupation
 Title (Service Mgr., etc.)
 Employed by
 State whether Employer is a Service Organization, Dealer, Jobber or Manufacturer

Name
 Address
 City-State
 Occupation
 Title (Service Mgr., etc.)
 Employed by
 State whether Employer is a Service Organization, Dealer, Jobber or Manufacturer


Name
 Address
 City-State
 Occupation
 Title (Service Mgr., etc.)
 Employed by
 State whether Employer is a Service Organization, Dealer, Jobber or Manufacturer

Please enter annual subscriptions (12 issues) for each of the above for which payment is enclosed at the rate of \$1.00 each. (This rate applies only on 4 or more subscriptions when occupations are given.)

SERVICE, 52 Vanderbilt Ave., New York 17, N. Y.

DON'T SETTLE FOR LESS THAN:

the Best

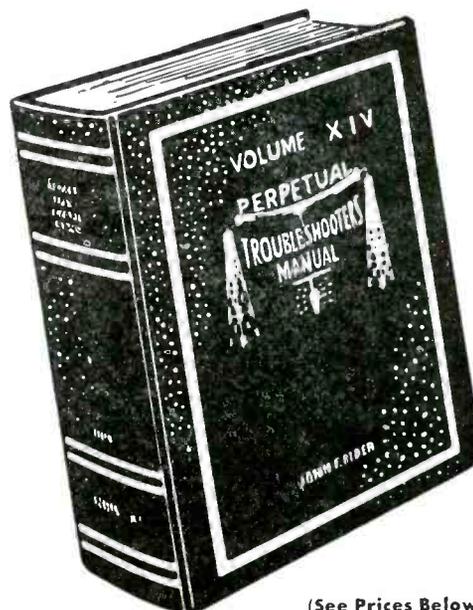

(See Prices Below)

When you must service any and all models of radio sets, only Rider Manuals can fill the need.

For sixteen years Rider Manuals have been furnishing complete and authentic servicing data on American radio receivers. Today they represent the only single source upon which you can depend for all the information you need on such vital material as receiver schematics, voltage data, alignment data, resistance values, chassis layouts and wiring, trimmer connections—in fact all the things that lead to quick diagnosis of troubles in ailing receivers.

—And they're complete! Since the publication of Volume I over 42,000 models have been covered—only Rider Manuals contain wiring diagrams on Scott receivers. (These diagrams were received officially from the E. H. Scott Radio Labs., Inc.)

There are good reasons why better servicing shops have waited during the war until they could get their Rider Manuals. There are better reasons today why you should not settle for less than "The Best." For, the flow of Rider Manuals is again approaching normal.

See your jobber and place your order today to guarantee fastest possible delivery.

GET ON THE MAILING LIST FOR "SUCCESSFUL SERVICING"

A monthly paper, dedicated to the financial and technical advancement of the electronic and radio maintenance man. Free distribution—Just

MAIL COUPON

JOHN F. RIDER PUBLISHER, INC.
404 (b) FOURTH AVE., NEW YORK, N. Y.

NAME _____

ADDRESS _____

CITY _____

STATE _____

YOU MUST STUDY TO KEEP UP TO DATE

Just Out "INSIDE THE VACUUM TUBE" . . . 424 Pages, \$4.50

RIDER MANUALS (14 VOLUMES)

Volumes XIV to VII . . . \$12.50 each volume
 Volumes VI to III . . . 9.50 each volume
 Abridged Manuals I to V
 (1 volume) . . . \$15.00
 Automatic Record Changers and
 Recorders . . . 7.50
 The Cathode Ray Tube at Work
 Accepted authority on subject . . . 4.00

Frequency Modulation
 Gives principles of FM radio . . . \$2.00
 Servicing by Signal Tracing
 Basic Method of radio servicing . . . 4.00
 The Meter at Work
 An elementary text on meters . . . 2.00
 The Oscillator at Work
 How to use, test and repair . . . 2.50
 Vacuum Tube Voltmeters
 Both theory and practice . . . 2.50

Automatic Frequency Control Systems
 —also automatic tuning systems . . . \$1.75
 A-C Calculation Charts
 Two to five times as fast as slide rule . . . 7.50
 Hour-A-Day-with-Rider Series—
 On "Alternating Currents in Radio Receivers"
 On "Resonance & Alignment"
 On "Automatic Volume Control"
 On "D-C Voltage Distribution" . . . 1.25 each

JOHN F. RIDER PUBLISHER, INC. 404 FOURTH AVE., N. Y. 16, N. Y.

Export Division: Rocke-International Electric Corp. 13 E. 40th Street, New York Cable: ARLAB

*—and Don't
Forget*

RIDER MANUALS

*are Now Complete
in 14 Volumes*

They Provide Schematics and Essential Servicing Data on American Made Radio Receivers.

RADIO PARTS ELECTRONIC EQUIPMENT



FREE! CONCORD Victory Clearance Flyer

Ready now! 32 Bargain-packed pages listing thousands of standard-make, top-quality radio parts and electronic supplies—now available without priority at low VICTORY CLEARANCE prices. The values listed below are typical of the important savings offered in Meters, Condensers, Transformers, Resistors, Controls, Relays, Switches, Test Equipment, Generators, Microphones, Tools, and hundreds of Repair, Replacement, and Accessory Parts.

<p>D.C. Milliammeters</p>  <p>2 1/4" flange mtg. type. Metal case dull black finish. C.E. 0-200 M.A. CI0650. Specially priced. \$4.95</p>	<p>Output Transformer</p>  <p>Hermetically sealed. Six studs, 1, 2, and 3 are pri. 4, 5, and 6 the sec. Pri. ind. at 5 V. 1000 cy.: 20 H. Ratio sec. to pri. 3.02:1. Size: 3 1/4 x 2 1/4 x 1 1/4". 5B5045 Your cost... \$1.95</p>
--	--

Immediate Shipment from
CHICAGO or ATLANTA

Huge stocks in two convenient warehouses—one in CHICAGO and one in ATLANTA—are ready to supply you quickly with needed parts of dependable nationally-known quality—and at VICTORY CLEARANCE prices that mean real savings. Mail the coupon below NOW for your FREE copy of CONCORD'S VICTORY CLEARANCE Flyer.

CONCORD

RADIO CORPORATION

Lafayette Radio Corporation

CHICAGO 7, ILL. ATLANTA 3, GA.
901 W. Jackson Blvd. 265 Peachtree Street

CONCORD RADIO CORPORATION
901 W. Jackson Blvd.
Dept. S-16, Chicago 7, Ill.
Please RUSH FREE copy of
CONCORD'S new 32-page VICTORY CLEARANCE Flyer.

Name.....
Address.....
City..... State.....



OLD TIMER'S CORNER

by **SERVICER**

SEEMS as if many feel that luck plays an important role in business. Well it may help, but hard work and sound business judgment is quite helpful too. A visit to Jerry's Radio Shoppe the other evening certainly proved this point.

I had been dropping into Jerry's store now and then to talk, but never questioned too much. On this particular evening I found Jerry in back of his well-stocked store hard at work putting some very nice-looking housekeeper's marketing pads into some very attractive envelopes. The pads consisted of about a hundred single sheets of printed lists with spaces for the woman of the house to check off what she needed to buy from the grocer and butcher. The pad was backed with stiff cardboard, and a hole for mounting the list was punched in the back.

Jerry was also putting a thumb-tack for the pad into the envelopes. At the top of the list and again on the envelope was Jerry's name and store address, together with a statement that when the radio went out "Call Jerry" and he would fix it.

I asked Jerry what was the big idea. Was he going into a big publicity stunt? How was he going to distribute them? What, besides the advertisement, was the purpose?

"It's this way," said Jerry. "I got the idea from my wife who used to get one of these from her grocery store. He got them from a breakfast food manufacturer. But somehow in the rush of war, the manufacturer did not come through, and so they stopped coming. I looked over her old one, or rather what was left of it, and decided that here was a fine medium with which to sell my service.

"So she and I got together and made up our own list. I put our advertisement on the front and then she suggested that I include a thumb tack so that the housewife would only have to put the pad up, and not search for any means with which to do it."

"In the first place," continued Jerry, "the housewife has the list in front of her every day. She picks out what she has to buy. On the list I inserted the reminders. 'Call Jerry to fix the radio set' and 'Call Jerry to fix the iron, washing machine, lamp, etc.', and I included our phone number.

"I distribute these myself. Here's how I do it. I take a minimum of 6 hours a week to call on the housewives, which amounts to about an hour a day. Sometimes I call in the evening, sometimes in the morning. It all depends on how the work goes in the shop. I ring door bells.

"Of course a lot of women won't talk to me at all. They are busy and don't

want to be disturbed. For those, who let me in or who talk to me, I have a brief message.

"After the woman answers the door-bell, I tell her who I am—actually the proprietor. Then I reveal that I have a marketing list for her which I will give her absolutely free of charge if she will answer a few questions for me. When she asks me 'Why the questions?' I tell her truthfully that I am making a survey so that I will know what to stock in my store.

"If she agrees to answer the questions, I ask her very few, marking the answers down on a pad I carry for the purpose. I ask: Name, and the name of her husband (or head of the household); number of persons in the family; is there a radio set in the house, or more than one; brand names; approximate date when the receivers were bought; electrical appliances about the house; approximately when were they acquired; and last, would she be interested in seeing any new radios or appliances when they are available?

"Just before I leave, I ask if the radio is working properly and if the appliances are all right. If they aren't I make a note of it and tell her that if she wants me to repair them, I'll return during business hours the next day. If she refuses to have me make the repairs, I still smile and say 'Thank you'. Then I give her the marketing list and leave.

"When I get back to the office, I make up a list of the homes I called on. As a result, I have compiled very useful data. I know what radios are around, which ones are out of order and which ones the owners will have replaced or repaired. I also know a lot about the families. All this is valuable material for future sales campaigns.

"For instance, I have a list of all the larger families who do not own washing machines. They are logical prospects. If there are only two in the family, say man and wife, they usually send their laundry out. These are poor prospects. They are not very good prospects for a new radio since they are not home a lot. But with large families, there is ample opportunity to sell one or more radio sets as well as appliances. Since I know which homes are without working radios and appliances, I can tell where I can hope to do business. I also know where my competitors are too firmly entrenched to be displaced, for in those places I have been told that I cannot make any repairs or replacements.

"Meanwhile I have made valuable contacts. In many homes, I find that if you call at the door and offer to repair the radio set, there is some fear and doubt as to your identity. To offset that, I always use the company's truck or have business cards with me. I offer to have the housewife call the local bank or police station to verify that I am as represented. I also carry a flock of identification cards. If that does not satisfy, I tell the housewife to call the shop, looking up the number in the phone book. Then I either come out the next day or send out my helper.

"And believe it or not, I have not only made the price of printing the lists many times over, but I have been getting an ever increasing share of the radio service and new business in this town."

That's why I have come to know that Jerry is an uncommonly good business man, and not "jest lucky" as the boys say.

ANALYZING INTERMITTENTS

(Continued from page 33)

bench lamp. An open in the mixer grid circuit coil of the 6A8G might cause loss of sensitivity, yet still allow the receiver to play, after a fashion, even though reception might be very poor. Tapping the coil or its leads might restore operation momentarily. A defective coil or soldered joint on a terminal lug could cause the condition to develop.


The signal could be checked with a signal tracer. The gain of the stage would be much lower than normal with an open in the grid circuit. A gain of about 2 to 10, depending on the set design, normally would be expected from the antenna to the first grid circuit. For an auto set, the gain might be somewhat higher, about 10 to 50.

An auto type receiver is shown in Fig. 2. In such receivers, excessive noise accompanied by intermittent reception may be caused by a defective vibrator, 100-mmfd filter capacitor or .01-mfd vibrator secondary filter capacitor, or possibly a leaky or intermittently opening grid capacitor. Further, the filters might be defective. The excessive leakage in the filters might cause vibrator overheating and sticking of the contacts, making the vibrator operation critical and uncertain. The output of the *B* supply, in such a case, could be checked with a cathode-ray oscillograph to get a picture of the condition of the supply. An alternative method would be to substitute, temporarily, a battery supply or a *B* eliminator, and to localize the trouble in that way.

In some cases oscillations could be caused by an intermittent in a capacitor. The set might play, break into oscillation, drowning out reception, and then, suddenly return to normal. In the Philco 90, Fig. 3, this might be caused by faulty capacitors in the plate circuit of the output tube, or an open in a capacitor in the screen grid circuit of the i-f tube. Allowing the set to squeal or whistle, a .25-mfd., 400-volt capacitor could be bridged across the suspected unit and the results observed. If the oscillation cleared up and the set snapped back to normal operation, replacement could be tried. However, to make certain the job is a success, the receiver should be allowed to play for several hours continuously.

The time element is a clue to the trouble. If the set cuts off in three minutes or less, it may be a tube or poor connection that is causing the trouble. •If three to five minutes time

(Continued on page 45)

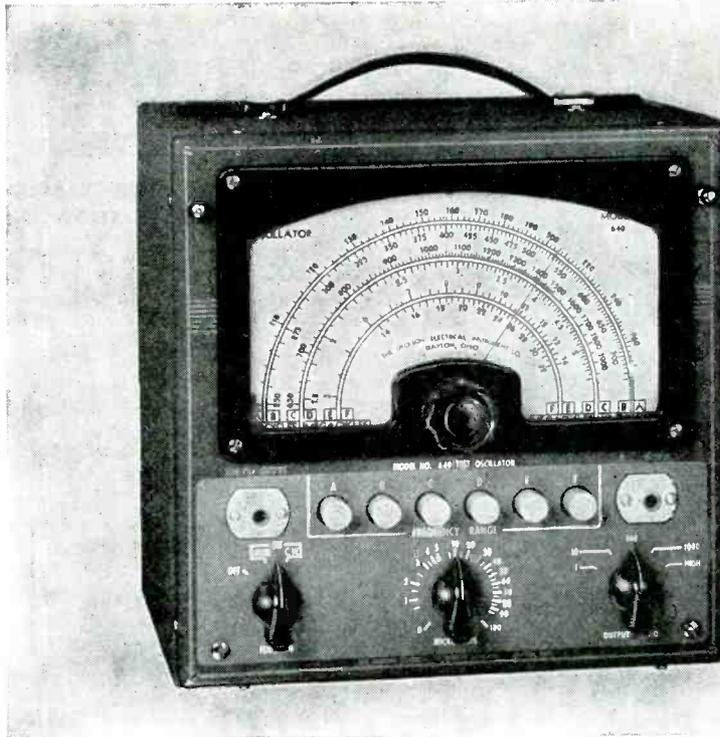

TEST OSCILLATOR Model 640

A COMPLETE "standard type" oscillator for all general purpose work. Has full range direct reading dial from 100 KC up to 30 megacycles. No skips or harmonics calibrated. All ranges are fundamental frequencies.

Push Button selection of all ranges makes speedy and accurate operation possible.

Glass Enclosed Dial—prevents dust and avoids possibility of damage to pointer.

Two Circuit Attenuator provides variable ratio and also vernier control.

Has Powerful Signal output which may be used either as pure R.F. or Modulated R.F. The A.F. voltage is available for external use. Carrier is modulated at approximately 30%.

Accuracy Guaranteed to 1/2 of 1% on all ranges. Operates from 110 volt 60 cycles. Uses three tubes (rectifier, oscillator and modulator).



The Jackson "Service Lab"


Back again, when steel is more plentiful—Jackson Service Labs. assembling in one handy unit your choice of standard sized Jackson instruments! Watch for them.

JACKSON

Fine Electrical Testing Instruments

JACKSON ELECTRICAL INSTRUMENT COMPANY, DAYTON, OHIO

SERVICE, JANUARY, 1946 • 39

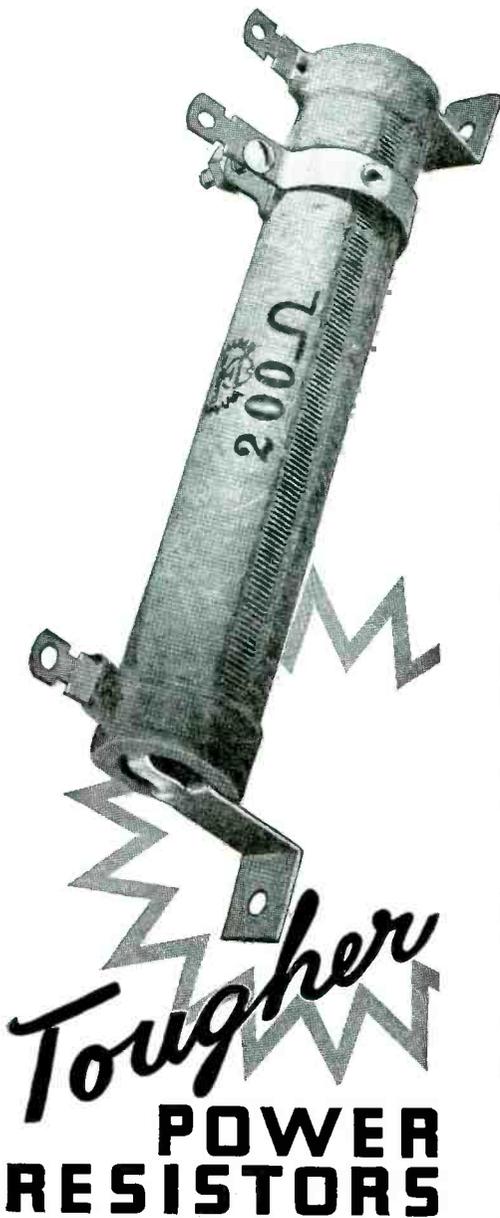

★ Yes, Clarostat Greenohms are definitely tougher power resistors. That's why you find those green-colored power resistors in high-grade radio-electronic assemblies that simply must stand the gaff. It will pay you to use Greenohms for those new assemblies, just as it pays to use these "stay-put" power resistors for repair jobs.

★ Ask Our Jobber . . .

Ask him about Greenohms. Better yet, try a few in your own work. Ask for our latest catalog—or write us direct.



CLAROSTAT MFG. CO., Inc. • 285-7 N. 6th St., Brooklyn, N. Y.



**KENNETH C. PRINCE APPOINTED
RADIO PARTS SHOW G-M**

Kenneth C. Prince has been named general manager of the Radio Parts and Electronic Equipment trade show scheduled for May 13-16 at Hotel Stevens, Chicago. Mr. Prince recently returned from active duty with the Navy, where he held the rank of Lieutenant.

Prior to entering the Navy, Mr. Prince was legal counsel for the Electronic Parts and Equipment Manufacturers Association.

The show corporation has established office headquarters at 221 North LaSalle Street, Chicago.

BLACKLIDGE NOW STANCOR G-S-M

James M. Blacklidge has been named general sales manager of the Standard Transformer Corporation, Chicago. Mr. Blacklidge was formerly sales manager of the industrial division.

Earl T. Champion has joined Stancor's distributor sales division.



**MOULTHROP JOINS RADIO TELE-
VISION SUPPLY CO.**

Jack Moulthrop has been appointed vice president and general manager of the Radio Television Supply Company, 1509 South Figueroa Street, Los Angeles. Mitchell Hirsch has retired due to illness.

Mr. Moulthrop, for the past ten years, has been manager of the electronic division of the San Francisco division of the Leo J. Meyberg Company.



NEWS OF THE REPRESENTATIVES


The New York chapter of The Representatives elected Leo Freed president during a recent meeting. Samuel Eggert was named vice president, and William Gold, secretary-treasurer.

E. G. Hendrickson, 121 S. Monroe Street, Spokane 8, Wash. has joined the Pacific Northwest chapter of the Representatives.

Hal F. Corry, 3522 Gillon Avenue, Dallas 5, Texas, was elected to the office of secretary-treasurer of the Southwestern chapter. The other officers of that chapter are: A. L. Berthold, president, and Ernest L. Wilkes, vice president.

The J. T. L. Sales Co., are now located

AN ENTIRELY NEW LINE

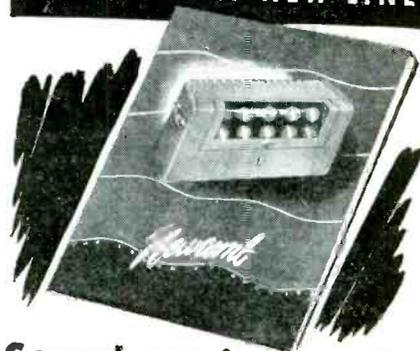

**Sound equipment by
NEWCOMB**

Our newest amplifiers offer greater excellence in sound reproduction than ever before available to the public address field. Designed by an organization devoted exclusively for seven years to the perfection of sound equipment, they embody all the benefits of today's most advanced electronic achievements.

Send for the catalog . . . you'll find no other amplifier has so many advantages.



**New MODEL 450
TUBE TESTER**

Designed especially for the service man who wants to give better service. Speedy operation is assured by newly designed rotary selector switch which replaces the usual snap, toggle or lever action switches. Tests all tubes up to 117 volts including 4, 5, 6, 7L, Octals, Locfals, Magic Eye, Hearing Aid, Thyratrons, Single Ended, Floating Filament, Mercury Vapor Rectifiers, also Pilot Lights. Tests shorts and leakages up to 3 Megohms in all tubes. Tests both plates in rectifiers. Has many other new features and advantages that any good service man will appreciate after five minutes use. Immediate Delivery.

Only **\$39.50**

Write for latest bulletin showing hundreds of other hard-to-get items at money-saving prices.



at 120 Liberty Street, New York, N. Y. Members of the firm are Jules T. Levy and Nat Rubin.

Harry B. Segar, veteran manufacturers representative, died recently. He is survived by his widow, Mrs. Carolyn L. Segar, who is carrying on her late husband's business.

JULIAN K. SPRAGUE AND DR. PRESTON ROBINSON BECOME SPRAGUE VICE PRESIDENTS

Julian K. Sprague and Dr. Preston Robinson have been elected vice presidents of the Sprague Electric Company, North Adams, Mass. Mr. Sprague joined the company in 1926. He was one of the original group of four employees at the old Quincy, Mass., plant where he served as production manager. Dr. Robinson has been with the company since 1929, serving as chief engineer and director of research.

L. R. O'BRIEN NOW G-S-M OF RAYTHEON RECEIVING TUBE DIV.

L. R. O'Brien has been appointed general sales manager of the radio receiving tube division of Raytheon Manufacturing Co.



MARION INSTRUMENT CATALOG

A 28-page catalog, describing standard and hermetically sealed electrical indicating instruments, has been published by the Marion Electrical Instrument Company of Manchester, N. H.


COL. SOULES NAMED ELECTRO-VOICE SALES MANAGER

Lt. Col. Webster F. Soules, now on terminal leave from the Army Signal Corps, has been appointed sales manager of Electro-Voice, Inc., South Bend, Ind.



GHIRARDI BOOK DISPLAY

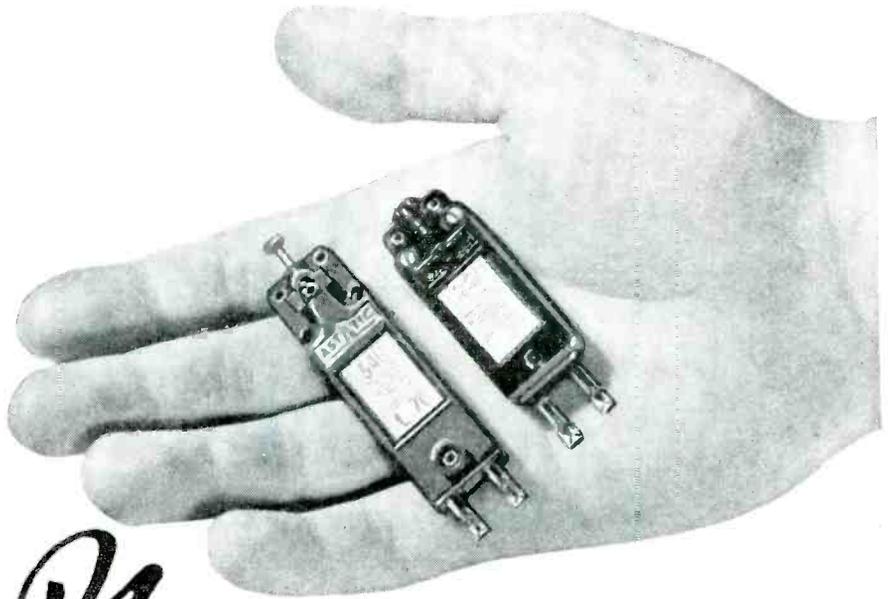A combination book display 12½" wide by 9¾" deep for Ghirardi radio books has been designed for distribution to dealers.



New Astatic Cartridges

Improve Phonograph Reproduction

INTENDED for use with both automatic record changers and manually operated equipment, these new Astatic Cartridges, in MLP and L-70 Series, assure a degree of fidelity heretofore unparalleled in the reproduction of recorded sound. All new Astatic Phonograph Pickup Arms will include these finer Cartridges.

L-70 Series Cartridges are of the replaceable needle type, are designed with streamlined housing, high output voltage and low needle pressure.


MLP Series Cartridges are of the permanent or fixed stylus type and are engineered to operate at one-ounce pressure, with increased vertical compliance, higher output voltage and reduced needle talk.

"You'll HEAR MORE from Astatic"

• Astatic Crystal Devices manufactured under Brush Development Co. patents.

THE Astatic CORPORATION
 CONNEAUT, OHIO
 IN CANADA. CANADIAN ASTATIC LTD, TORONTO, ONTARIO

First Choice

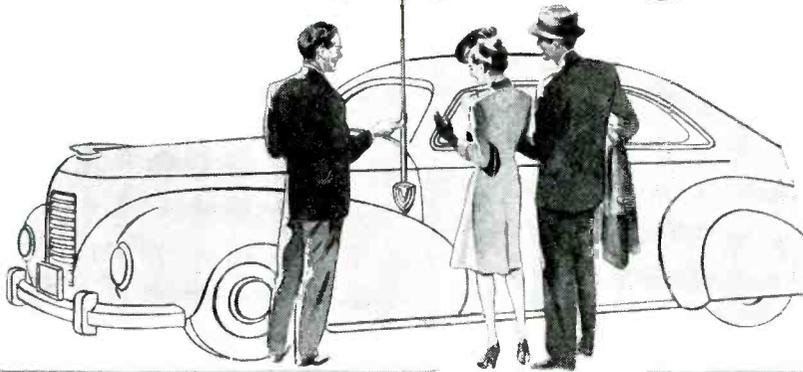

... OF AMERICA'S AUTO DEALERS

The same precision workmanship and the same fine quality mark Ward Antennas now as before the war. But now there are added reasons of new design and newly-engineered efficiency which will give Ward Antennas an even greater margin of preference with America's auto dealers. For extra profits that satisfied customers always bring, order Ward—world's finest antennas for car and home.

Buy Victory Bonds
THE WARD PRODUCTS CORPORATION
 1523 E. 45th St., Cleveland 3

WARD

Antennas



UNIMETER

This unit fulfills an extremely important need for general utility portable service equipment. It has wide range coverage for both a-c and d-c measurements of voltage, current measurements on d-c and the popular ranges on resistance.

The UM-3 is designed to clearly indicate all the functions which aid in the prevention of application of high voltages when preparing for current or resistance measurements.

Other G-E units for better servicing include: Tube Checker TC-3, Unimeter UM-4, and Oscilloscope CRO-3A.

For details write: *Electronics Dept., Specialty Division, General Electric Company, Syracuse, New York.*

Electronic Measuring Instruments



GENERAL ELECTRIC



UM-3

UM-3

177-E1

OHM'S LAW

(Continued from page 14)

dimensioned pipes were connected to a common source, and one was longer than the other, the amount of water coming out of the longer pipe would be less than for the shorter one. (One point should be noted; the rate of flow of the water will be the same at any point along the line of flow, or at the mouth of the pipe.) The reason for the reduced flow in the longer pipe is the greater friction loss in the longer pipe. In the same way, the longer an electrical conductor is, the smaller will be the current flow. In other words, less current will pass a given point for the same amount of time.

Again, for water, given two pipes of the same dimensions, both length and inside diameter, but with the inner wall of one smoother than the other, more gallons per minute will flow through the smoother one, since it offers less resistance to the flow of water. The same is true of electrical conductors. Two electrical conductors of identical dimensions, but constructed of different metals, will offer different resistances to the flow of electrical current.

The Closed Circuit

Using the water analogy again, an electrical circuit may be represented as a continuous system, in which the water is constantly circulating, within a closed circuit, and with some outside force, such as a pump supplying the motive force. If the circulation of the water were interrupted, for example by a stop valve, there would be no current flow. Here, the water analogy breaks down. Both water and electricity systems require continuity. However, in the water system we insert a stop to prevent the flow of water. In the electrical system we *open* the circuit to stop the flow of current. Although the effects are similar, the terms are different. A more apt analogy in this instance would be a draw bridge, which cuts

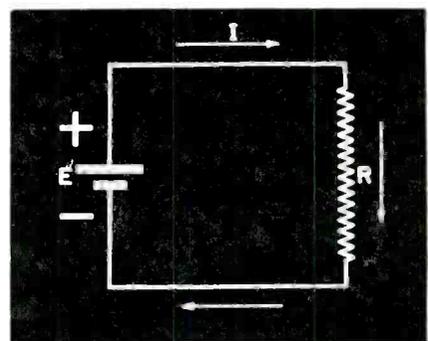


Fig. 3. Graphical representation of a closed electrical circuit. *E* represents the voltage source; arrows the accepted direction of current flow, and the resistance is designated by *R*. The wire connections are here shown as straight solid lines.

off the flow of traffic across it when it is open; Fig. 2.

A continuous water system would have two terminals, one the intake, the other the outlet. In a similar manner, voltage sources have two terminals. The outlet is called the plus or positive terminal, and the intake the negative or minus terminal. In the early days of electricity, current was thought to flow from the terminal designated as *positive* to that called negative, and all meters, batteries, and circuits were so marked. Modern electrical theory has proved the opposite to be true. However, all meters and circuit designations in use today still cling to the old system. A more complete explanation will be furnished later.

Ohm's Law

Ohm's law states that . . . "in any closed electrical circuit, the flow of electrical current is directly proportional to the force producing it, and inversely proportional to the resistance in the circuit." Stated mathematically: $I = E/R$, where I = current in amperes, E = force in volts, and R = resistance in ohms.

In this manner, all three quantities are defined in terms of each other. The same expression, or formula, may be expressed mathematically as $E = IR$, or $R = E/I$.

Examples

A simple circuit which represents the operation of this law is shown in Fig. 3. To find the value of any one of the three terms, the other two must be known.

Suppose we have a source voltage of 8 volts, and a circuit resistance of 2 ohms, and we wanted to know what current will flow in the circuit.

Substituting in the mathematical representation of Ohm's law:

$$I = \frac{E}{R}, I = \frac{8}{2}, \text{ or } I = 4 \text{ amperes.}$$

Now suppose we have a current of 3 amperes and a circuit resistance of 5 ohms, and we wanted to know the source voltage. Using the second form of ohm's law:

$$E = IR, E = 3 \times 5, \text{ or } E = 15 \text{ volts.}$$

Let us now take an example where we have a source voltage of 12 volts, and a circuit current of 6 amperes, and the circuit resistance is to be found. Here, the third form of Ohm's law is applied:

$$R = \frac{E}{I}, R = \frac{12}{6}, \text{ or } R = 2 \text{ ohms.}$$

[To be continued]



MR. RADIOMAN: You Can Use These "Tools" To Build a Better Job and a Secure Career in RADIO-ELECTRONICS

CREI Home-Study Training in Practical Radio-Electronics Engineering Combined with Your Own Experience Assures You of Job Security and an Interesting, Profitable Career

What's ahead for *you* in the field of Radio Electronics? One thing is certain. Now that peace is here, Radio-Electronics will surge forth as one of America's foremost industries, offering promising careers for radiomen with modern technical training.

NOW is the time to take the time to prepare yourself for these important, career jobs in radio-electronics engineering. CREI can show you the way by providing you with the "tools" to build a firm foundation of ability based on a planned program of technical training.

In our proved home-study course, you learn not only *how* . . . but *why!* Easy-to-read-and-understand lessons are provided you well in advance, and each student has the benefit of personal guidance and supervision from a trained instructor. This is the successful CREI method of training for which thousands of professional radiomen have enrolled since 1927.

Your ability to solve tough problems on paper and then follow-up with the necessary mechanical operation, is a true indication that you have the *confidence* born of *knowledge* . . . confidence in your ability to get and *hold* an important job with a secure, promising post-war future. Investigate now the CREI home-study course best suited to your needs, and prepare for security and happiness in the New World of Electronics! *Write for all the facts now.*



**WRITE FOR
FREE 36-PAGE
BOOKLET**

*"Your
Opportunity in
the New World of
Electronics"*

If you have had professional or amateur radio experience and want to make more money, let us prove to you we have something you need to qualify for a better radio job. To help us intelligently answer your inquiry — PLEASE STATE BRIEFLY YOUR BACKGROUND OF EXPERIENCE, EDUCATION AND PRESENT POSITION.

CAPITOL RADIO ENGINEERING INSTITUTE

HOME STUDY COURSES IN PRACTICAL RADIO-ELECTRONICS
ENGINEERING FOR PROFESSIONAL SELF-IMPROVEMENT

Dept. S-1, 3224 16th Street, N.W., Washington 10, D. C.

Contractors to U. S. Navy — U. S. Coast Guard — Canadian Broadcasting Corp.
Producers of Well-trained Technical Radiomen for Industry.

MEMBER, NATIONAL COUNCIL OF TECHNICAL SCHOOLS

NEW SOLDERING GUN

THE SPEED IRON*



100 Watts 115 Volts 60 Cycles

Soldering Heat in 5 Seconds

Wherever you have a soldered joint in radio, electrical or electronic repair and service work, the Speed Iron will do the job faster and better.

The transformer principle gives high heat—in 5 seconds—after you press the trigger switch. Convenient to hold with a pistol grip handle, the compact dimensions of this new soldering tool permit you to get close to the

*T.M. Reg. U. S. Pat. Off.

joint. The copper loop soldering tip permits working in tight spots. The heat is produced by the high current flowing through the soldering tip—permitting direct and fast transfer to the soldered connection.

If you want to save time on soldering jobs with a tool that is ready to use in 5 seconds, get a Speed Iron today. See your radio parts distributor or write direct.

WELLER MFG. CO.

514 NORTHAMPTON ST., EASTON, PA.

5 Minutes to install a RAD-EL-CO AERIAL

- Factory Assembled
- No Conversion Parts
- Aircraft Connectors
- Polyethylene Cable
- Ceramic Insulators

RAD-EL-CO MFG. CO.


6300 EUCLID AVE.,
CLEVELAND 3, OHIO

NEW PRODUCTS

PRECISION MULTI-RANGE V-T VOLTMETER

A portable vacuum-tube multi-range tester, type EV-10-P, with direct-reading megohmmeter, milliammeter, ammeter, and db meter ranges, has been announced by the Precision Apparatus Company, 92-27 Horace Harding Blvd., Elmhurst, N. Y.

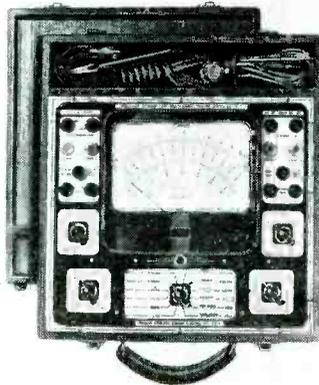Has a 7" size rectangular meter. Uses a stabilized bridge circuit with a 6C5, 6X5 and VR-150. The meter is said to be zero-center on all ranges when used



in the vtvm circuit, indicating both polarity and magnitude without reversing the prods or use of a polarity switch.


Eight zero-center vtvm ranges from ± 3 volts d-c to $\pm 6,000$ volts d-c full scale; six resistance ranges from 0-2,000 ohms to 0-2,000 megohms; eight a-c and eight d-c ranges from 600 microamps to 12 amperes; eight output ranges from 3 to 6,000 volts and eight db ranges from -26 to +70 db. Overall dimensions 12" x 13" x 6".

BARKER AND WILLIAMSON R-F SIGNAL GENERATOR

A high-level r-f signal generator covering 400 kc to 60 mc range in six steps has been announced by Barker and Williamson, 235 Fairfield Avenue, Upper Darby, Pa. Modulation of 30% at 1,000 cps is optional by means of a panel switch. Output is 3 volts (rms) at all frequencies and is read directly from a panel voltmeter. Output is through an output jack and coaxial cable terminated in a 75-ohm resistive load.

Calibration is said to be accurate to better than $\frac{1}{2}$ of 1% and is read from a calibrated chart mounted on the lid of each cabinet.

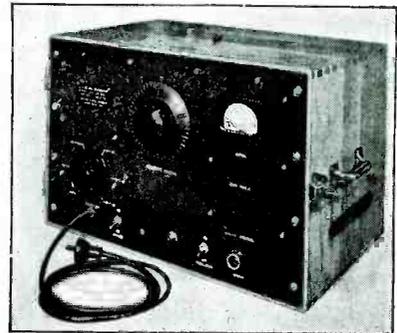Six ranges are: 400 to 1,000 kc; 1,000 to 2,500 kc; 2,500 kc to 6 mc; 6 to 13 mc; 13 to 28 mc, and 28 to 60 mc.



RCP POCKET MULTITESTER

A pocket multitester, model 448, featuring 6 instruments in one, is now being offered by Radio City Products Co., 127 West 26th Street, New York.

Db range is calibrated for a line of 500-ohm impedance. For lines of other impedance, correction charts are supplied. Size is $5\frac{7}{8}$ " x $3\frac{1}{16}$ " x $2\frac{1}{8}$ "; weight $1\frac{3}{4}$ pounds with batteries.

FARNSWORTH RECORD CHANGERS

Automatic record changers, type P-50, using three shelves, have been announced by the Farnsworth Television and Radio Corporation, Fort Wayne, Indiana.

Plays either ten twelve-inch records or twelve ten-inch records.

Incorporated is an automatic stop which shuts off the unit after the last record has been played; simultaneously the tone arm swings off and away from the turntable which permits removal of the records for reloading.

The tone arm has a one-ounce needle pressure and will take any standard pickup cartridge. The turntable rotates on ball thrust bearings.

Baseplate size, 12" x 14"; required clearance above and below the baseplate is $6\frac{1}{4}$ " and $1\frac{3}{4}$ ".

HICKOK TUBE AND SET TESTERS


All-purpose tube and set testers with

a dynamic mutual conductance circuit have been developed by the Hickok Electrical Instrument Company, 10521 Dupont Avenue, Cleveland 8, Ohio.

Models 532C, (counter model) and 532P (portable) that tests and rejects all bad tubes, are fitted with scales having micromho ranges from 0-3,000, 0-6,000, 0-15,000 with legends indicating *replace*, *doubtful*, and *good*. This unit also provides for noise, gas, and hot and cold shorts tests. Diodes are tested separately with low voltage to prevent paralysis of the elements. Line voltage is indicated on a test meter, from 100 to 130 volts. Rectified current is used to energize plates and grids using two rectifiers and tests can be made of grid controlled rectifier tubes. Filament voltage is in steps to 117 volts. A roll chart is included. Tester is 17" x 18" x 8½". Operates on a power supply of 110-130 volts from 50-60 cycles.

The unit uses an 83 and a 5Y3GT.

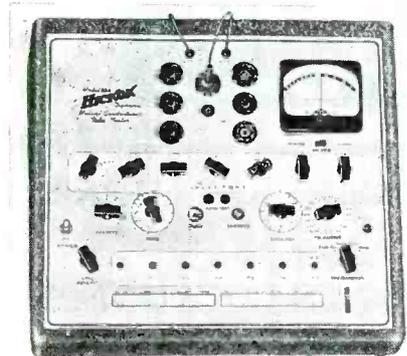Tests octal, loktal, miniature, ballast, magic eye and standard tubes.



NATIONAL UNION MINIATURES

A miniature type (2¾" bulb) half-wave high vacuum rectifier, the 1Z2, with voltage handling capabilities of 20,000, has been announced by National Union Radio Corporation, Newark, N. J. In addition to its application as a half-wave rectifier at line frequencies, the tube is also adaptable for fly-back pulse rectifiers, and r-f supplies for television circuits.

Filament (thoriated tungsten) voltage, 1.5 a-c or d-c; filament current, 300 ma; peak inverse plate voltage, 20,000 volts max.; peak plate current, 10 ma max.; average d-c plate current, 2 ma max.

Maximum overall length, 2.70"; maximum seated height, 2.45"; maximum diameter, 0.75"; bulb, T-5½; base, miniature button 7-pin; mounting position, any.

Typical operation, as half-wave rectifier: a-c plate supply voltage, 7,800; filter-input capacitor, 0.1 mfd; d-c output current, 2.0 ma; d-c output voltage, 9,200.

SHALLCROSS 0.5-WATT HERMETICALLY-SEALED RESISTORS

Hermetically-sealed resistors, type 1101, rated at 0.5 watt and 7/8" long x 7/8" in diameter have been announced by the Shallcross Mfg. Co., Jackson and Pusey Avenues, Collingdale, Pa.

Maximum resistance value when wound with nickel chromium wire is 350,000 ohms; maximum voltage, 420.

SHURE LEVER-TYPE PICKUP CARTRIDGES

A crystal pickup cartridge with the

6 TEST INSTRUMENTS IN HIS COAT POCKET*

• The R.C.P. Model 448 Pocket Multifester combines six essential instruments in a case only 5-7/8" x 3-1/16".

This versatile multimeter is remarkably accurate and combines low and high ranges. It's tops for general circuit testing and to speed trouble shooting. Despite its compact size, it uses a 3 inch square meter for easy reading, with a movement of 200 microamperes and a 5000 ohms per volt sensitivity.

MODEL 448 POCKET MULTIFESTER

Weight only 1¾ lbs. Size, 57/8" x 3-1/16" x 2 1/8". In metal case. Complete with self contained batteries, ready to operate in snap spring contact holders.

Price \$24.50

RANGES: dc Voltmeter: 0/5/50/250/1000 volts—First scale division—0.1 volt ★ ac Voltmeter: 0/5/50/250/1000 volts—First scale division—0.1 volt ★ Output Voltmeter: 0/5/50/250/1000 volts—First scale division—0.1 volt ★ dc Milliammeter: 0.5/10/100/1000 ma—First scale division—0.1 ma ★ Ohmmeter 0/1000, 0/10,000, 0/.1 meg ★ Decibel meter: -6 to +10, -14 to +26, -28 to +40, -40 to +52 db. Db scale is calibrated for a range of 500 ohm impedance. For other impedance ranges, correction charts can be supplied.

RADIO CITY PRODUCTS CO., INC.

127 West 26th Street,




New York 1, N. Y.

crystal driven by a lever has been announced by Shure Brothers, Chicago.

Lower needle point impedance is said to be obtained. The lever arrangement is said to absorb the full impact of sudden jars to the cartridge or needle. Needle force of ¾ to 1½ ounce is attainable with the output voltage from 1.6 to over 3.

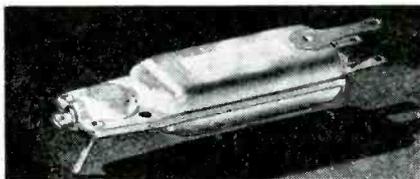Cartridge is available in an aluminum case. Weight, .43 ounce. It is also furnished in steel, weighing .85 ounce.



ANALYZING INTERMITTENTS

(Continued from page 39)

elapses before development of the intermittent, you should look for faulty carbon resistors, especially in cathode circuits of output tubes. If over five minutes are required for the defect to develop, suspect audio transformers, the primaries of first i-f transformers, r-f transformers, chokes, etc.

In any event, listening carefully to the customer's complaint may prove very helpful. Final judgment may be reserved, but if you know what you're looking for, it's easier to find than to look for something that is vague.

POSTWAR A-C/D-C RECEIVER

(See front cover)

A POSTWAR 4-tube-and-rectifier a-c/d-c compact receiver, recently announced by Temple-tone, E-510 to 519, appears on the front cover this month.

The 2-stage resistance power-supply filter is more generous than usual, minimizing hum level. The 12SK7 i-f amplifier has a fixed minimum bias supplied by the oscillator. The loop primary has a .005-mfd series capacitor. A cathode-tapped oscillator uses a fixed 10-mfd compensator. A 6.8-megohm bias resistor from the oscillator grid to the i-f grid return, supplements the a-c bias. The amount of fixed bias depends upon the Q of the oscillator circuit which may be made to vary with frequency, a sort of automatic sensitivity control. Where oscillation troubles are encountered near the low-frequency end of the tuning range, the Q may be made to increase at that end, reducing i-f sensitivity to stop the undesired oscillation.

The r-f demodulation products from the detector are filtered out by a π filter using two 100-mfd capacitors and a 47,000-ohm resistor. The filter and

$\frac{1}{2}$ -megohm volume control serve as the diode load resistance.

The power filter uses a pair of 40-mfd capacitors and a 120-ohm resistor for the first section which feeds the 50L6 plate, and 1,800 ohms and another 40-mfd capacitor for the 50L6 screen and other tubes. A 20-mfd cathode bypass shunts a 150-ohm bias resistor.

SERVICING HELPS

RCA 5T

Dead or with intermittent, not due to tube: Usually one of the tubular capacitors is open. In most cases the faulty capacitor can easily be found by testing each of the leads for looseness. On some models I have found the defective capacitor by tapping each lightly with an aligning tool, while set is on. Set will cut on and off when defective unit is tapped.

Claude M. Prev

RADOLEK


Radio-Electronic Service Parts



Large stocks assure the finest and most complete selections of all available items at lowest prevailing prices. Thousands of active buyers depend on us for their entire Radio repair and replacement requirements. Because we understand service problems, every order is expedited for delivery in double quick time. Everything we do is planned for convenience and satisfaction to our customers. You will find it profitable to make Radolek your buying headquarters.

FREE BUYING GUIDES

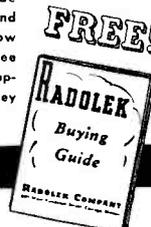Because of existing conditions we keep our customers right up to the minute on available merchandise by releasing supplements frequently instead of sending our regular Big Profit Guide once a year. Send the coupon now to get these Free Buying Guide Supplements as they are issued.




FAST SERVICE!

RADOLEK CO., Dept. S-110
601 W. Randolph St., Chicago 6, Ill.

Please send FREE Buying Guide Supplements

NAME _____
ADDRESS _____

ORDER FROM RADOLEK

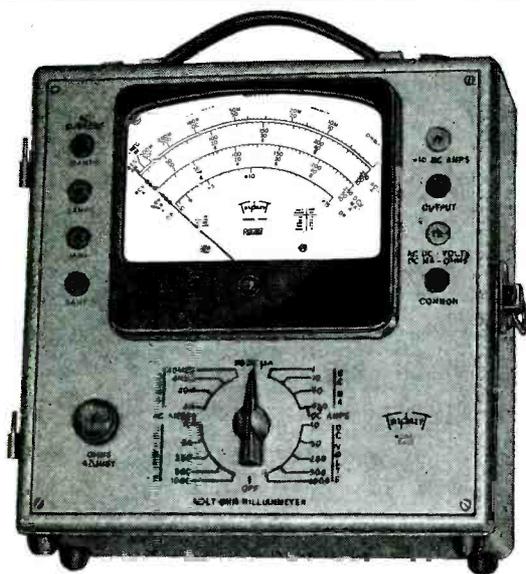

NEW ENGINEERING • NEW DESIGN • NEW RANGES 50 RANGES

- Voltage: 5 D.C. 0-10-50-250-500-1000 at 25000 ohms per volt.
- 5 A.C. 0-10-50-250-500-1000 at 1000 ohms per volt.
- Current: 4 A.C. 0-.5-1-5-10 amp.
- 6 D.C. 0-50 microamperes — 0-1-10-50-250 milliamperes—0-10 amperes.
- 4 Resistance 0-4000-40,000 ohms—4-40 megohms.
- 6 Decibel -10 to +15, +29, +43, +49, +55
- Output Condenser in series with A.C. volt ranges.

Model 2400 is similar but has D.C. volts Ranges at 5000 ohms per volt.

Write for complete description

MODEL 2405

Volt-Ohm-Milliammeter

25,000 OHMS PER VOLT D.C.



SPECIFICATIONS

NEW "SQUARE LINE" metal case, attractive tan "hammered" baked-on enamel, brown trim.

- PLUG-IN RECTIFIER—replacement in case of overloading is as simple as changing radio tube.
- READABILITY—the most readable of all Volt-Ohm-Milliammeter scales—5.6 inches long at top arc.
- RED-DOT LIFETIME GUARANTEE on 6" instrument protects against defects in workmanship and material.

Triplet

ELECTRICAL INSTRUMENT CO.

BLUFFTON, OHIO.

Radio Headquarters

for 25 years



We ship at once—parts, equipment, whatever you need!

This house began its career almost as early as Broadcasting itself! Today, 25 years later, we're the world's largest radio supply house with a constant stock of well over 10,000 parts! Just tell us what you need and we'll ship it!

Standard Lines: National, Hammarlund, R.C.A., Hallicrafters, Bud, Cardwell, Bliley, and all the others you know so well!

SUPERSPEED SERVICE Orders shipped out same day received.

ENGINEERING SERVICE If your engineering problem requires special equipment, we'll make it.

WHOEVER YOU ARE... industrial organizations, laboratories, purchasing agents, radio dealers and service men, training schools, amateur operators and experimenters—we'll supply you fast and economically.

Originators and Marketers of the Famous *Lafayette Radio*

Radio Wire Television Inc.

NEW YORK 13 BOSTON NEWARK

FREE! New 1946 Flyer packed with all the things you need right now. Mail coupon below!

R. W. T. Dept. FA-6

100 AVENUE OF THE AMERICAS, NEW YORK 13

I want your latest free 1946 Flyer.

NAME _____

ADDRESS _____

HAM? (CALL LETTERS) _____

ENGINEER? SERVICE MAN? STUDENT?

JOTS AND FLASHES

POSTWAR receivers now in production reveal many circuit innovations. An interesting analysis of these developments appears in Henry Howard's discussion of *Ser-Cuits* this month on page 26. . . . Ivan G. Easton is now in charge of the New York office of General Radio at 90 West Street. . . . John Altmayer is president of a new company, the Asco Corporation, 874 East 140 Street, Cleveland 10, Ohio. . . . Ben Joseph has been named eastern representative for the British Industries Sales Corporation, 401 Broadway, New York City. William Carduner organized the company to handle Garrard record changers, Ersin multicore solder and Solon soldering irons, British products. . . . Stanley A. Morrow is now assistant manager of advertising and sales promotion of Farnsworth. . . . John R. Hughes has been named assistant sales manager of Farnsworth sales. . . . Russ Owens has been appointed manager of the Shelby Woodcrafters, Shelbyville, Indiana, a subsidiary of Hallicrafters. . . . R. E. Samuelson, vice president in charge of Hallicrafters engineering, has been named chairman of the marine section of the RMA. . . . John M. Cage is now manager of the industrial electronic division of Raytheon, with headquarters at Waltham, Mass. . . . The needle resharpener service department of the recording blank division of Gould-Moody, 195 Broadway, New York City, has been expanded. . . . George D. Rice is now acting assistant chief engineer of the radio division of Lear, Inc. . . . E. F. Erickson has joined Carter Motor Company, 1608 Milwaukee Avenue, Chicago, Ill., as purchasing agent. . . . Sylvania has purchased the Wabash Appliance Corporation, 335 Carroll Street, Brooklyn, N. Y., makers of photoflash and incandescent lamps. . . . Edwards Sales Company have moved to 504 Erie Building, Cleveland, Ohio. . . . Charles B. Kennedy has become branch manager of the West Central district of Westinghouse Electric Supply at Dayton, Ohio. . . . Louis Alweis has returned to Garod Radio as a sales representative. . . . Walter Widlar is now general manager of the MecRad division of Black Industries, Cleveland, Ohio. . . . S. B. Levaur has been named sales manager of television receivers at Du Mont. . . . Cmdr. G. Robert Mezger has rejoined Allen B. Du Mont Labs., Passaic, N. J., as manager of instrument sales. . . . Comdr. Ralph T. Brengle has been appointed district sales manager of the Aero Needle Company, Chicago, for Indiana, Illinois and Wisconsin.

ADVERTISERS IN THIS ISSUE SERVICE INDEX—JANUARY 1946

AEROVOX CORPORATION	20
Agency: Austin C. Lescarboura & Staff	
AMERICAN PHENOLIC CORP.	25
Agency: Evans Associates, Inc.	
THE ASTATIC CORPORATION	41
Agency: Wearstler Advertising, Inc.	
BURSTEIN-APPLEBEE CO.	28
Agency: Frank E. Whalen Adv. Co.	
CAPITOL RADIO ENGINEERING INSTITUTE	43
Agency: Henry J. Kaufman & Associates	
CENTRALAB DIV. GLOBE-UNION INC.	4
Agency: Gustav Marx Adv. Agency	
CLAROSTAT MFG. CO., INC.	40
Agency: Austin C. Lescarboura & Staff	
CONCORD RADIO CORP.	38
Agency: E. H. Brown Adv. Agency	
CORNELL-DUBILIER ELECTRIC CORP.	
Agency: Reiss Advertising	
DRAKE ELECTRIC WORKS, INC.	28
Agency: William Hoffman & Associates	
ELECTRICAL REACTANCE CORP.	24
Agency: Scheel Adv. Agency	
GENERAL CEMENT MFG. COMPANY	20
Agency: Turner Adv. Agency	
GENERAL ELECTRIC COMPANY	4, 42
Agency: Mason, Inc.	
HALLICRAFTERS COMPANY	27
Agency: Burton Browne Advertising	
HICKOK ELECTRICAL INSTRUMENT CO.	31
Agency: White Adv. Co.	
JACKSON ELECTRICAL INSTRUMENT CO.	39
Agency: Kireher, Helton & Collett, Inc.	
LAKE RADIO SALES COMPANY	24
Agency: Sanler Rodkin Adv. Agency	
LIFETIME SOUND EQUIPMENT COMPANY	40
Agency: The Miller Agency Co.	
McELROY MFG. CORPORATION	46
Agency: Shappe-Wilkes Inc.	
M. V. MANSFIELD COMPANY	46
MARION ELECTRICAL INSTRUMENT CO.	13
Agency: Shappe-Wilkes Inc.	
MUELLER ELECTRIC COMPANY	30
MURRAY HILL BOOKS, INC.	29
Agency: The Harry P. Bridge Company	
NATIONAL RADIO DISTRIBUTORS	46
Agency: Burke & Wayburn Adv. Company	
NATIONAL UNION RADIO CORP.	Back Cover
Agency: Hutchins Adv. Co., Inc.	
NEWARK ELECTRIC COMPANY	30
Agency: Charles Brunelle	
NEWCOMB AUDIO PRODUCTS COMPANY	40
Agency: Gail Hall Advertising	
RAD-EL-CO MFG. COMPANY	44
RADIO CITY PRODUCTS CO., INC.	45
Agency: Reiss Advertising, Inc.	
RADIO CORPORATION OF AMERICA	15, 23
Agency: J. Walter Thompson Co.	
RADIONIC EQUIPMENT COMPANY	46
Agency: Hishon-Garfield Co.	
RADIO SUPPLY & ENGINEERING COMPANY	28
Agency: Karl G. Behr Adv. Agency	
RADIO WIRE TELEVISION, INC.	48
Agency: S. T. Seidman & Co.	
THE RADOLEK COMPANY	47
Agency: Turner Adv. Company	
RAYTHEON MFG. COMPANY	3
Agency: Burton Browne Advertising	
JOHN F. RIDER PUBLISHER, INC.	37
Agency: Lansford P. King Advertising	
SOLAR CAPACITOR SALES CORP.	
Agency: O. S. Tyson & Co., Inc.	
SOUTHWEST WHOLESALE RADIO	46
SPRAGUE PRODUCTS COMPANY	7
Agency: The Harry P. Bridge Co.	
STAMFORD ELECTRIC PRODUCTS COMPANY	5
Agency: Reiss Advertising	
STANDARD TRANSFORMER CORP.	21
Agency: Burnet-Kuhn Adv. Company	
SYLVANIA ELECTRIC PRODUCTS INC.	8
Agency: Newell-Bennett Company	
TRIPLETT ELECTRICAL INSTRUMENT CO.	47
Agency: Western Adv. Agency, Inc.	
U. S. TREASURY DEPT.	6
UNITED TRANSFORMER CORP.	19
Agency: Shappe-Wilkes Inc.	
THE WARD PRODUCTS CORP.	42
Agency: Burton Browne Advtg.	
WELLER MFG. COMPANY	44
Agency: Beaumont, Heller & Spertling, Inc.	
WHOLESALE RADIO LABORATORIES	30
Agency: Pfeiffer Adv. Agency	

You can't put the *squeeze* on "Sealdtite" Capacitors

Take a genuine "Sealdtite" capacitor and try to squeeze it. No "soft spots." Why? Because this Solar capacitor has its high purity paper-and-foil-winding ingeniously molded into a cylinder of solid wax.

No atmospheric moisture can penetrate this protective housing to attack the capacitor element. In genuine wax-molded "Sealdtite" capacitors, there just is no possibility of those twin omens of trouble — soggy cardboard tubes and moisture-filled hollows.


For real reliability, specify Solar "Sealdtites" on your next order.

P.S. If you haven't a copy of our Catalog SC-1, get one from your Solar distributor, or drop us a penny postcard today.




SOLAR CAPACITOR SALES CORP.
285 Madison Avenue • New York 17, N. Y.

Ⓢ1000

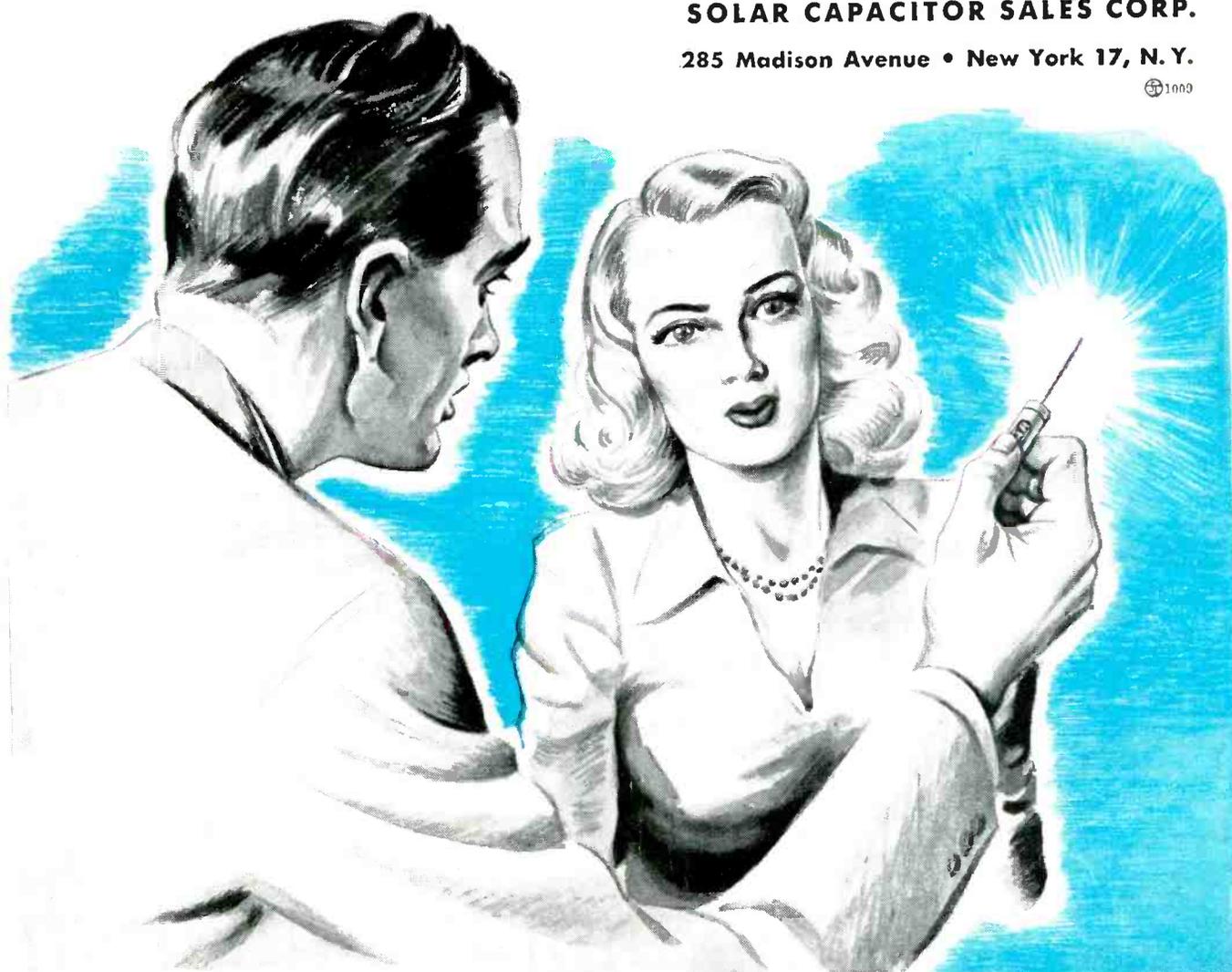

N. U. BATTERIES

by the Carload!

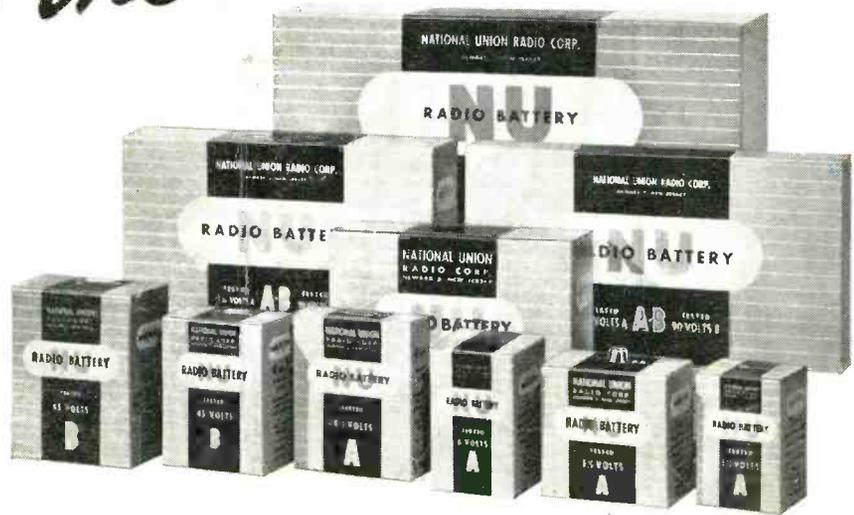

Get Immediate Deliveries of All Types for Standard Radio and Other Replacements

Now you can bring many thousands of good, serviceable battery-powered radio sets *back to life*. Portables—Farm Radios—"carry-about" sets! Here are the batteries you need to bring in this flood of profitable service and parts business. Order now and *tell* your customers to come on the run for the batteries they need.

In batteries as in other products, N. U. quality helps you build for the future. The patented construction of N. U. Batteries permits more active materials—more service hours per dollar. Every N. U. Battery is engineered to the highest initial equipment standards and is designed for universal replacement.

PLACE YOUR BATTERY ORDER TODAY—with YOUR N. U. DISTRIBUTOR

Renew with N. U. . . . the quality line that brings repeat sales at full profit to radio service men!

NATIONAL UNION RADIO CORPORATION, Newark 2, New Jersey

NATIONAL UNION RADIO TUBES AND PARTS

Transmitting, Cathode Ray, Receiving, Special Purpose Tubes • Condensers • Volume Controls • Photo Electric Cells • Panel Lamps • Flashlight Bulbs

