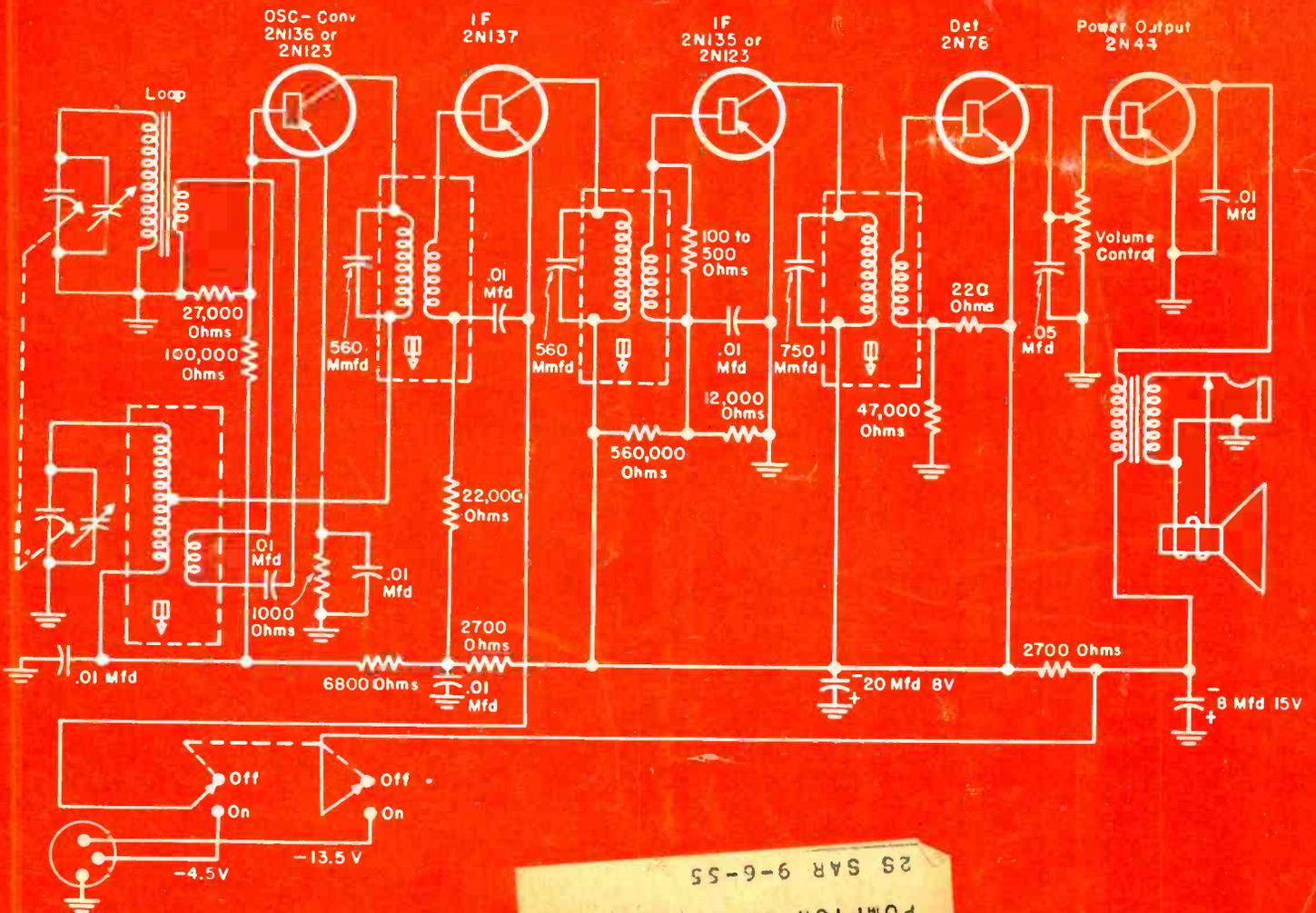



SERVICE

The Technical Journal of the Television-Radio Trade



Transistorized pocket radio with used junction-type transistors. See circuit analysis, this issue

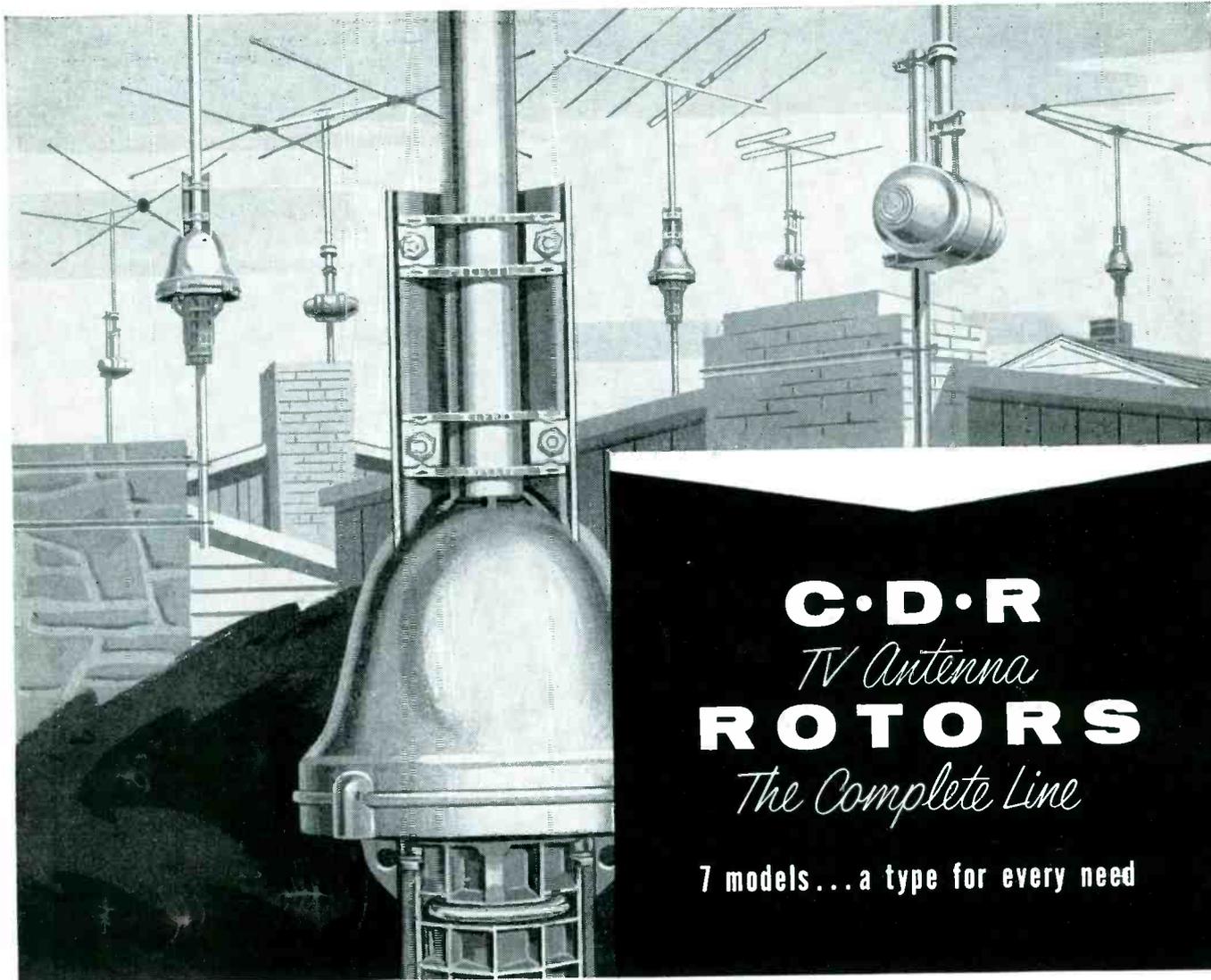2S SAR 9-6-55
 R TURSE
 CLARKE LANE,
 POMPTON LAKES, N.J.
 10-57



C·D·R
TV Antenna
ROTORS
The Complete Line

7 models... a type for every need

featuring **C·D·R automatic ROTORS**

Here they are . . . the fastest selling line of rotors . . . complete in every detail . . . including three models in completely AUTOMATIC rotors! The AR-1 and AR-2 and the AR-22 which is the automatic version of the famous TR-2. ALL FIELD TESTED AND PROVEN BY THOUSANDS OF SATISFIED USERS!


TR-2 The heavy duty rotor with plastic cabinet featuring "compass control" illuminated perfect pattern dial . . . uses 8 wire cable.

TR-12 Complete rotor INCLUDING thrust bearing. Handsome modern cabinet with meter control dial, uses 4 wire cable.

TR-4 The heavy duty rotor complete with handsome new, modern cabinet with METER control dial, uses 4 wire cable.

TR-11 Same as model TR-12 without thrust bearing.

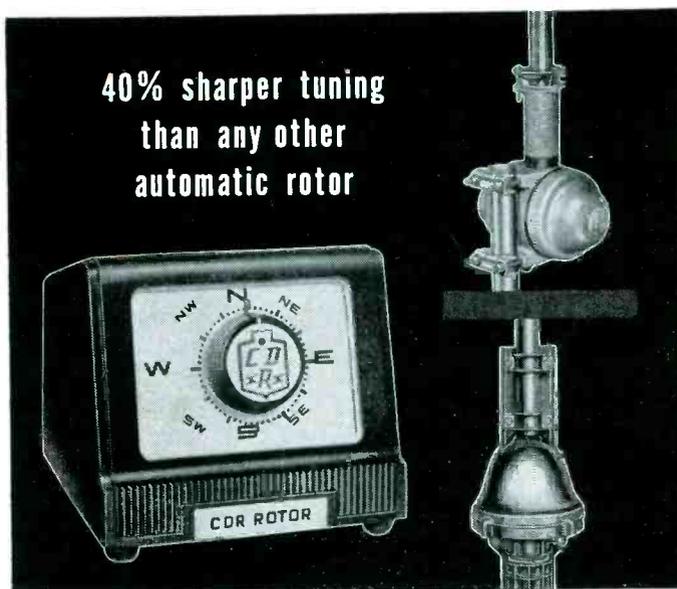pre-sold PRE-SOLD to millions with the greatest concentration of TV Spots in our history.



40% sharper tuning than any other automatic rotor



CORNELL-DUBILIER
 SOUTH PLAINFIELD, N. J.



THE RADIART CORP.
 CLEVELAND 13, OHIO

20 7 WATT RESISTORS


SELECTED POPULAR VALUES



RESIST-O-CARD

\$6.20
NET

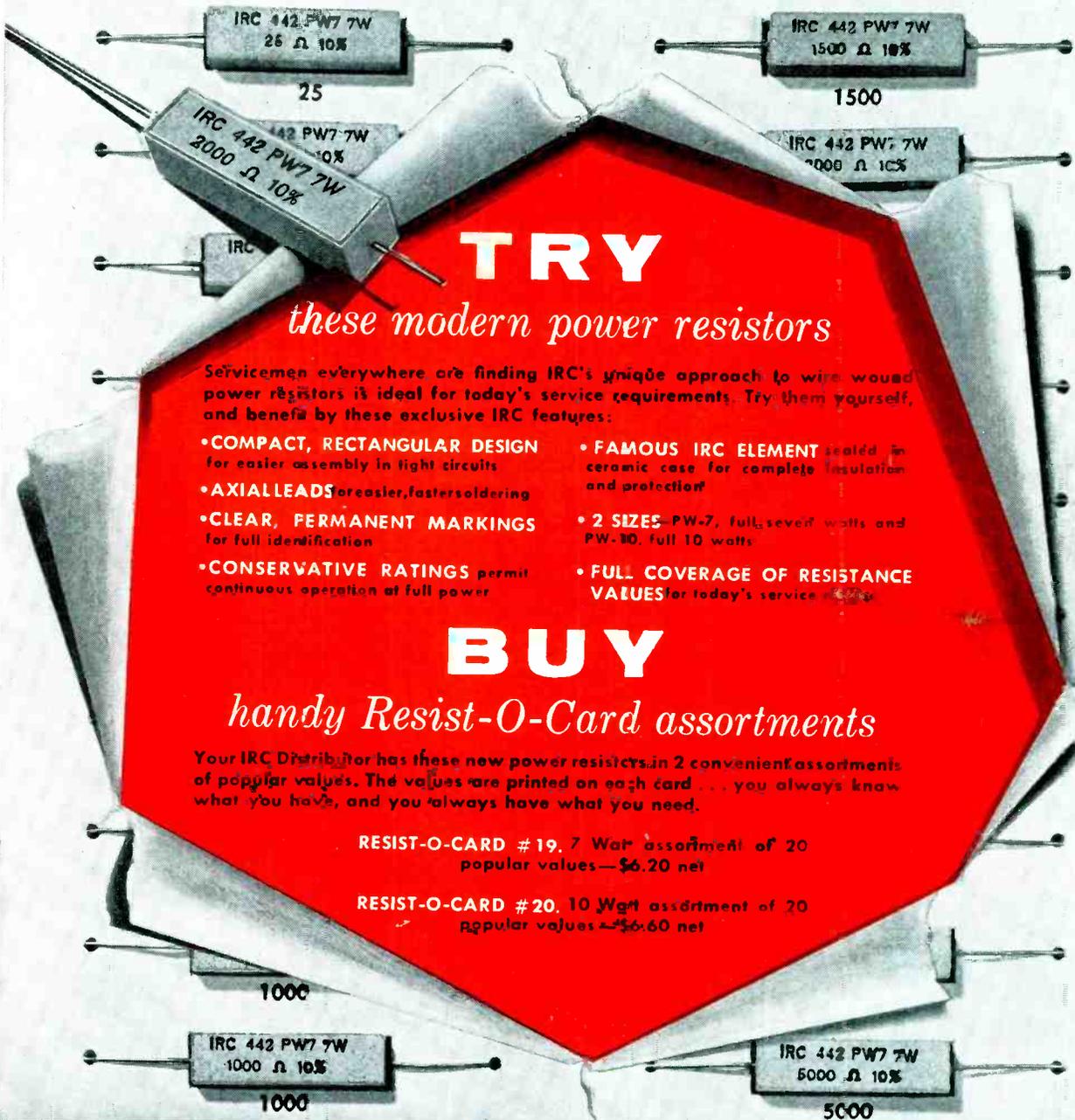NEW TYPE PW-7 WIRE WOUND POWER RESISTORS • FULL 7 WATT RATING



TRY

these modern power resistors

Servicemen everywhere are finding IRC's unique approach to wire wound power resistors is ideal for today's service requirements. Try them yourself, and benefit by these exclusive IRC features:

- **COMPACT, RECTANGULAR DESIGN** for easier assembly in tight circuits
- **AXIAL LEADS** for easier, faster soldering
- **CLEAR, PERMANENT MARKINGS** for full identification
- **CONSERVATIVE RATINGS** permit continuous operation at full power
- **FAMOUS IRC ELEMENT** sealed in ceramic case for complete insulation and protection
- **2 SIZES** PW-7, full 7 watt and PW-10, full 10 watts
- **FULL COVERAGE OF RESISTANCE VALUES** for today's service

BUY

handy Resist-O-Card assortments

Your IRC Distributor has these new power resistors in 2 convenient assortments of popular values. The values are printed on each card . . . you always know what you have, and you always have what you need.

RESIST-O-CARD # 19, 7 Watt assortment of 20 popular values—\$6.20 net

RESIST-O-CARD # 20, 10 Watt assortment of 20 popular values—\$6.60 net

INTERNATIONAL RESISTANCE CO.

Philadelphia, Penna.

ASSORTMENT 19


FOR 10 WATT POWER RESISTOR REQUIREMENTS SPECIFY IRC ASSORTMENT #20. ASSORTMENT #20 INCLUDES 20 PW-10 RESISTORS IN SELECTED VALUES—\$6.60 NET.

New!


Technician's
Quickie bench

TRADE MARK

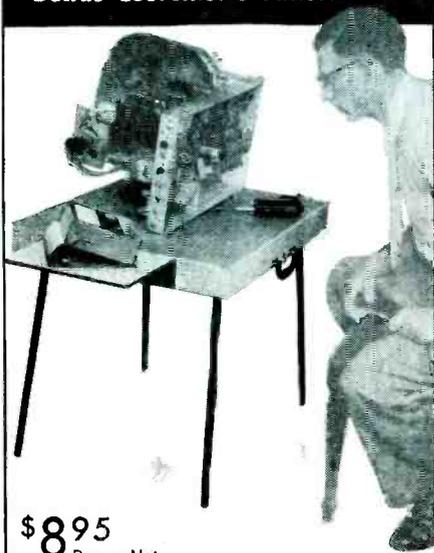**Speeds Repairs On the Spot
Increases Profit Per Call
Builds Customer's Satisfaction**




\$895
Dealer Net

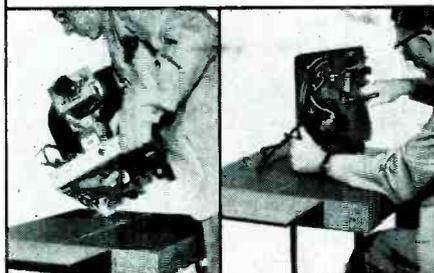

STRONG
with "Craftsmanship in Cabinets."

VERSATILE
use for any repairs.

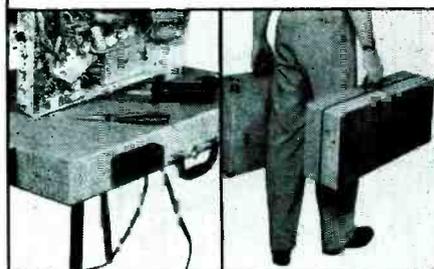

EXTRA GADGETS
can easily be added. Not incl.

CARRIES EASILY
only 26x11x6 1/4"
Can fit under arm.

**ASK YOUR PARTS DISTRIBUTOR
OR WRITE FOR FOLDER**

Argos
PRODUCTS COMPANY
230 MAIN STREET - GENOA, ILLINOIS

SERVICE

The Technical Journal of the Television-Radio Trade

Including SERVICE—A Monthly Digest of Radio and Allied Maintenance; RADIO MERCHANDISING and TELEVISION MERCHANDISING. Registered U. S. Patent Office.

COVER CIRCUIT

Transistorized Printed Circuit Pocket Radio (G.E. 675) 22

FEATURES

Views and News Lewis Winner 17

SERVICE . . . The National Scene 18

The Independent Service Man In The Rural Areas Jack Darr 20

Transistorized Printed Circuit Pocket Radio (G.E. 675) 22

Power Wire-Wound Resistors Esmond E. Johnson 24

Wide-Band Chroma Signal Amplifier for Color-TV G. S. Ryant 26

Servicing Helps T. L. Gilford 28
(Auto Headlight-Control Circuit Modification . . 90° Tube Linearity Adjustments)

The NCTA Western Regional Conference F. M. Randolph 32

Operation-Maintenance of High-Band 2-Way Sets Albert R. Sinclair 35

21-Inch Wide-Band 41-Mc B-W TV Receiver (Ser-Cuits) R. D. Wengenroth 38

Phono-Tape Motor Design-Repair F. R. Sailes 42

Phono Needle Replacement (Audio Installation-Service) Maxwell Alberts 47

VHF/UHF Transistors (Tube News) A. M. Kelwood 53

UHF/VHF TV Antenna Digest Ralph G. Peters 54

Schematics In This Issue 62

DEPARTMENTS

Association News 10

Ten Years Ago in SERVICE 11

TV Accessories . . . Parts 59

Bench-Field Tools 60

Instruments 61

News 62

Personnel 63

Components 64

Catalogs and Bulletins 65

Jots and Flashes 66

Index to Advertisers 65

Entire Contents Copyright 1955, Bryan Davis Publishing Co., Inc.

Second-Class mail privileges authorized at New York, N. Y.; additional entry at the Post Office, Norwalk, Conn.

Subscription price: \$2.00 per year in the U.S.A. and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.



EDITOR

Lewis Winner

Assistant Editors: **D. E Pearsall II**
R. D. Wengeroth
J. Dines

Art Director: **Anthony R. Alliff**

Supervisor, Circuit Diagrams:
M. D. Bellezza

Editorial Production: **A. Kelly**

CIRCULATION DEPARTMENT

Circulation Manager: **A. Goebel**

Ass't Circulation Mgr.: **A. Kiernan**

ADVERTISING DEPARTMENT

Business Mgr.: **F. W. Boyd**

East: **Jerome J. Brookman**

Mid-West Mgr.: **Stuart J. Osten**
333 N. Michigan Ave.
Chicago 1, Ill.
Tel.: DEarborn 2-3507


East-Central Rep.: **James C. Munn**
2253 Delaware Dr.
Cleveland 6, O.
Tel.: ERview 1-1726

Pacific Coast Rep.: **Brand & Brand**
1052 W. 6th St.
Los Angeles 17, Cal.
Tel.: MADison 6-1371

Published Monthly By



Bryan Davis Publishing Company, Inc.
52 Vanderbilt Ave., New York 17, N. Y.
Tel.: MUrray Hill 4-0170

B. S. Davis, Pres. F. W. Boyd, Sec'y

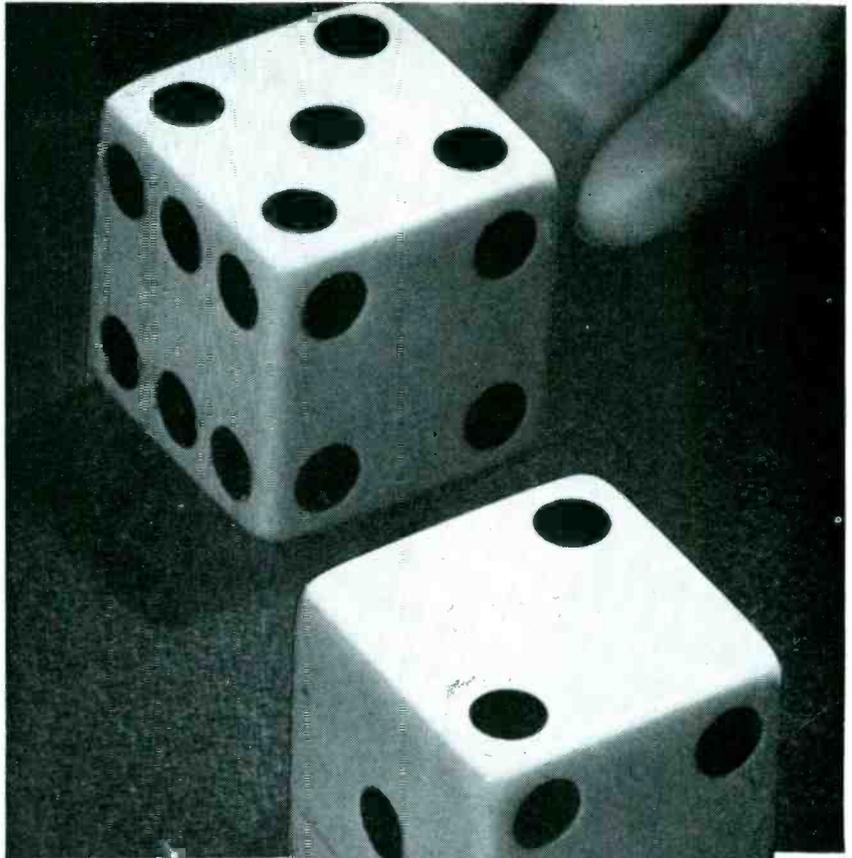

A NATURAL

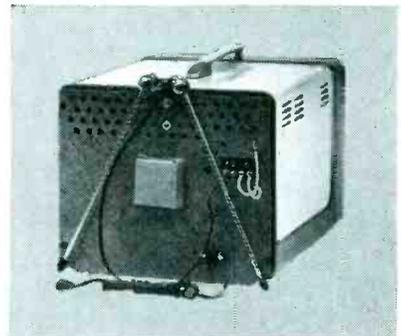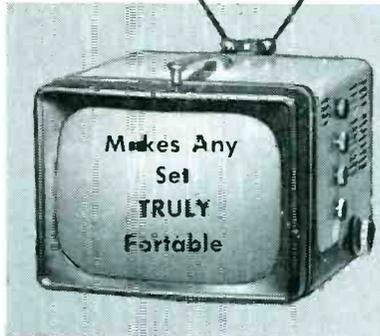The No. 900 "BUILT-ON" ANTENNA.. List \$5.95
Attached easily with just two screws.... Folds neatly out of way



* For the Second Set Market
for Replacement Antenna Sales

for Home Demonstrations
for Rental Sets



THE RADION CORP., 1130 W. WISCONSIN AVE., CHICAGO 14

SERVICE, OCTOBER, 1955 • 3

RCA

SELENIUM

RECTIFIERS

Now, RCA offers you a top-grade line of selenium rectifiers for general replacement use in TV, radio receivers, and phonographs. Advanced design, select raw materials, and superior workmanship give you a *dependable line of selenium rectifiers for virtually all service jobs.*

Advanced Design for Dependable Performance and Long Life

Note the wide-open plate spacing for elimination of solid center "hot spot." Design utilizes corrugated spacers for *excellent heat dissipation and rigid construction for rugged service.*



NEW—smaller size . . . for any given current, they are smaller than other types.

NEW—quicker installation . . . integral mounting stud.

NEW—wide-open design . . . insures maximum heat dissipation, cooler operation . . . no center "hot spots."

NEW—rigid construction . . . for rugged service.

RCA SELENIUM RECTIFIERS—a *comprehensive line*—for consistently good performance, easier installation, longer life and customer satisfaction. **ORDER FROM YOUR RCA DISTRIBUTOR TODAY!**

—one comprehensive line for virtually all replacement requirements!

WIDE SELECTION OF 12 TYPES		
Max. Output ma	Max. Input volts	RCA Type
65	130	205G1
75	130	200G1
100	130	206G1
150	130	201G1
200	130	207G1
250	130	208G1
300	130	202G1
350	130	209G1
400	130	203G1
500	130	204G1
400*	130	210G1
500*	130	211G1

*Special thin types for use where available space will not permit the use of type 203G1 or 204G1.



RADIO CORPORATION of AMERICA
ELECTRONIC COMPONENTS
HARRISON, N. J.



SYLVANIA SILVER SCREEN 85

more profit for you in
"Silver Screen 85's"

Stepped-Up
Selling Power

Sylvania puts you in the driver's seat and backs you with more promotional horsepower than ever before. This Fall, it's all out on all fronts to make your selling job easier and your servicing job more profitable. Here's how:

Stepped-up TV power—"Beat the Clock's" fabulous prize contest makes all your customers and prospects potential prize winners. 10 new prizes, 10 new winners every week. Week after week you'll win new customers who come to you for their free entry blank. And as a Sylvania Dealer only you can supply them with an official entry blank.

Stepped-up magazine power—Sylvania's selling the "Silver Screen 85" in the biggest consumer magazine campaign of 1955. Full schedules in *This Week* and *TV Guide* will presell your customers on the three outstanding features of the "Silver Screen 85" picture tubes. 11 million readers are reached by *This Week* through the combined distribution of 35 great American newspapers. Over 3 million TV viewers use *TV Guide* every week for TV news and program listings.

Stepped-up promotional power for you. A complete package of Sylvania promotion material is available so you can fill in the important final link in this promotional chain reaction. Window and counter displays, new direct-mail material, the important "Silver Screen 85" booklet, and new ad mats are included to help you capitalize on the prize contest and national magazine program.

Stepped-up profits for you. Sylvania supplies selling power that adds up to more profit for you. Think with Sylvania—work with Sylvania—promote with Sylvania—and you can't help but profit with Sylvania.

SYLVANIA ELECTRIC PRODUCTS INC.
1740 Broadway, New York 19, N. Y.

In Canada: Sylvania Electric (Canada) Ltd.
University Tower Bldg., Montreal

LIGHTING • RADIO • ELECTRONICS
TELEVISION • ATOMIC ENERGY



SYLVANIA®

... fastest growing name in sight



Turn to BUSS for all your fuse needs

COMPLETE LINE

It is easy to select a BUSS fuse to do the job right. The BUSS fuse line includes: dual-element (slow blowing), renewable and one-time types — in sizes from 1/500 ampere up . . . plus a companion line of fuse clips, blocks and holders.

BUSS FUSES ARE MADE TO PROTECT — NOT TO BLOW NEEDLESSLY

To assure unfailing dependability — every BUSS fuse normally used by the Electronic Industries is tested in a sensitive electronic device. Any fuse not correctly calibrated, properly constructed and right in all physical dimensions is automatically rejected.

With the cost of a fuse being so insignificant compared to the value of the equipment it protects and the value of your good name — it is just good business to refuse to take a chance on anything less than BUSS quality in fuses.

IN SALES AND SERVICE, PROFIT BY THE BUSS TRADEMARK



Millions upon millions of BUSS fuses for home, industry and automotive use have firmly established BUSS as the *Known* brand. Handling quality products, like BUSS fuses, help you maintain your reputation for quality and service.

More information is available on BUSS and FUSETRON small dimension fuses and fuseholders . . . Write for bulletin SFB.

Makers of a complete line of fuses for home, farm, commercial, electronic, automotive and industrial use.

BUSSMANN MFG. CO. (Division of McGraw Electric Co.)
UNIVERSITY AT JEFFERSON ST. LOUIS 7, MO.

S-1055

Never before — an antenna
with such utterly . . .

Fantastic

front-to-back ratios

Low Band: from 20:1 to 50:1 relative VOLTAGE
(2500:1 relative power)

High Band: up to 13:1 relative VOLTAGE
(169:1 relative power)

"Super-sembled"
— with
Channel Master's
trigger-fast
Snap-Lock Action.

CHANNEL MASTER'S

new
"K.O."
all-channel antenna

Available 3 ways!

Broad Band model—model no.1023
(includes HI-LO Matching Harness)

Low Band only—model no.1026

High Band only—model no.1073

Full descriptive literature available from your
Channel Master distributor.


Knocks out venetian blinds and co-channel interference!

Channel Master's new "K.O." has the highest front-to-back ratios ever recorded for any TV antenna! The sensational "K.O." actually sets up an INVISIBLE BARRIER to signals coming in from the rear. Working with supreme efficiency on both VHF bands, it totally REJECTS rear signals, preventing venetian blinds and other picture problems caused by co-channel interference.


Spectacular High Gain!

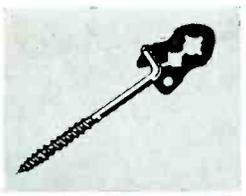Low Band, 7 to 9 DB, single bay; High Band, 8.5 to 10.5 DB, single bay. True Yagi performance, combined with completely independent High and Low Band operation for maximum efficiency.






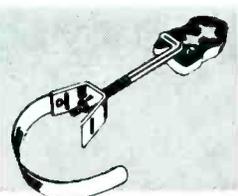TELCO-E-Z "SWING-IN" STAND-OFF
Wood screw type, 3 1/2", UHF-VHF
No. EZ-8027 \$4.80 C



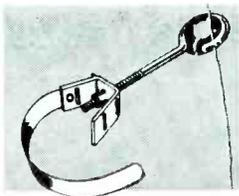TELCO E-Z "KANT-STRIP" STAND-OFF
"Swing In" type, 3 1/2", 9" strap
No. EZ-8253 \$0.13




TELCO "KANT-STRIP" STAND-OFF
Round insulator, 3 1/2", 9" strap
No. 8253 NET \$0.11



TELCO 3-WAY STAND-OFF
For 3-line use, 7 1/4" wood screw
No. 8397 NET \$0.21



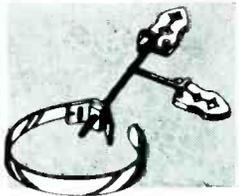
TELCO NUT-TYPE STAND-OFF
Welded 10-23 nut, 3 1/2", 9" strap
No. 8253-N \$0.12



TELCO E-Z NUT-TYPE STAND-OFF
Tougher, inline duplex, 7 1/2", 9" strap
No. EZ-8258-N \$0.24



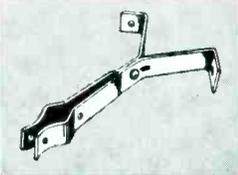
TELCO CHIMNEY QUICK MOUNT
Easy to install, complete
No. 8005 NET \$1.35




TELCO SNAP-IN CHIMNEY MOUNT
Fits masts to 1 3/4" complete
No. 8610 NET \$1.71



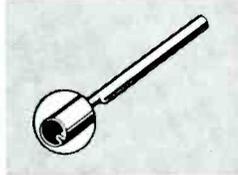TELCO PEAK MOUNT
Masts to 1 3/4" 30" lower support
No. 8625 NET \$2.37



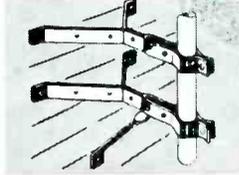TELCO GALVANIZED ANTENNA MASTS
1 1/4" OD x 5' crimped end
No. 9013 NET \$0.78



TELCO DELUXE SNAP-IN WALL MOUNT
Extra sturdy, 12" clearance
No. 8312 NET \$2.10



TELCO UNIVERSAL LIGHTNING ARRESTOR
Easy to install, UL approved
No. 8642 NET \$0.75



TELCO UHF-VHF GLOBE-TENNA
Handsome 12" globe plus built-in antenna
No. A-9265 \$11.97


Ask For These

SERVICE AIDS

...at Your Jobber



TELCO UHF-VHF LIGHTNING ARRESTOR
Universal type, UL approved
No. 9242 NET \$0.42

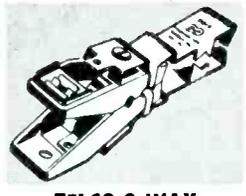


TELCO 3-WAY TV LINE KLIP
For straight, side or plug-in
No. 9015 NET \$0.12



TELCO LOW-LOSS LINE KLIP
All one piece, plastic, metal ends
No. 9055 NET \$0.15



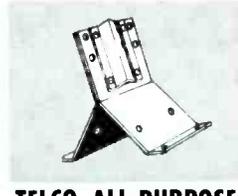TELCO HINGED TYPE RIDGE MOUNT
Fits masts to 1 1/2" assembled
No. 9021 NET \$1.17



TELCO ALL-PURPOSE MAST BRACKET
Fits masts to 1 3/4" use every where
No. 8575 NET \$1.65




TELCO MAST HANDY MOUNT
For masts to 1 1/2", extra support
No. 8800-U \$0.33




TELCO SPECIAL WALL MOUNT
For close-in (4") mounting
No. 9241 NET \$0.45



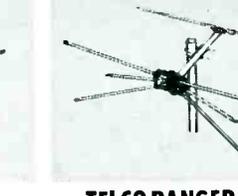
TELCO MASTER-LINE VHF CONICAL ANTENNA
Single bay, 10 element, all-channel
No. A-8700 \$4.20



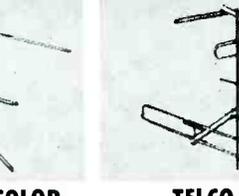
TELCO RANGER-COLOR CONICAL ANTENNA
Single bay, 8 element, VHF-UHF
No. A-110 NET \$3.45



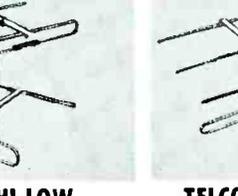
TELCO HI-LOW DIPOLE ANTENNA
VHF, covers channels 2 to 13
No. A-250 NET \$4.41



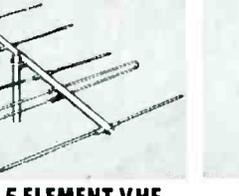
TELCO 5 ELEMENT VHF YAGI ANTENNA
12 models, custom cut to each.
No. A-302 Ch 2 \$7.35
No. A-313 Ch 13 4.35



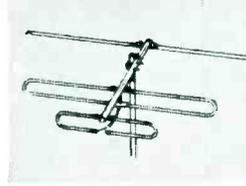TELCO UHF-VHF DOUBLE V ANTENNA
Covers channels 2 through 83
No. A-9017 \$3.15



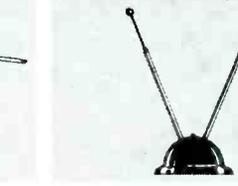TELCO VHF INLINE ANTENNA
Channels 2-13, 1/2" seamless elements
No. A-9046 NET \$5.97



TELCO INDOOR UHF-VHF ANTENNA
DeLuxe brass, nickel-plated elements
No. A-8160-TP \$2.97

FREE!

Your copy of the complete, illustrated TELCO Catalog. Send postcard today.


TELEVISION HARDWARE MFG. CO.

Division of General Cement Mfg Co. 901 TAYLOR AVENUE • ROCKFORD, ILLINOIS




TRIO®

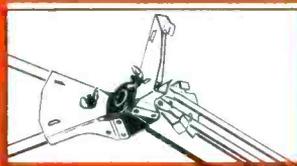**Will Not Sacrifice Quality
FOR PRICE!**



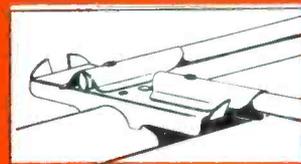Insta-Lok Head—216% more resistance to vibration and breakage. Flip out elements—they're locked in place.



Insta-Lok Clamp—Swing elements into position—that's all!

TRIO
Model 74

Sharpshooter

CONICAL

\$3.95
LIST

14

POPULAR MODELS
—ALL COMPLETELY
PRE-ASSEMBLED

Quality materials plus advanced TRIO automation give you the finest conicals ever built.

*Sharpshooter's Quality Features
Obsolete Un-assembled Antennas*

TRIO

Sharpshooter

YAGI

DRAW A BEAD ON QUALITY



*Only TRIO SHARPSHOOTER
Yagis Have These
Quality Features*

5 ELEMENT
(CHANNEL 6)
\$7.45
LIST

5 ELEMENT
HIGH BAND
\$3.95
LIST

10 ELEMENT
(CHANNEL 6)
\$13.65
LIST

10 ELEMENT
HIGH BAND
\$6.88
LIST

INSTA-LOK CLAMPS—Perfect alignment, positive lock, superior strength, lessened vibration and breakage. No finer yagis regardless of price!

EFFICIENT ELECTRICAL DESIGN—TRIO high channel models use a ratio type dipole for better impedance match, higher gain, sharper directivity.

RIVETED CONSTRUCTION—Introduced by TRIO for faster assembly, better picture quality.

BETTER VALUE—Because TRIO produces practically every part used in their products, including their own aluminum tubing.

Ask your distributor for complete literature on the new SHARPSHOOTER Conicals and Yagis.




TRIO® Manufacturing Company
GRIGGSVILLE, ILLINOIS

COPYRIGHT 1955—TRIO MANUFACTURING COMPANY

EXPORT SALES DIV., SCHEEL INTERNATIONAL INC., 4237 N. Lincoln Ave., Chicago, U.S.A. Cable Address: HARSHEEL

SERVICE, OCTOBER, 1955 • 9

"I NEVER HEAR COMPLAINTS..."

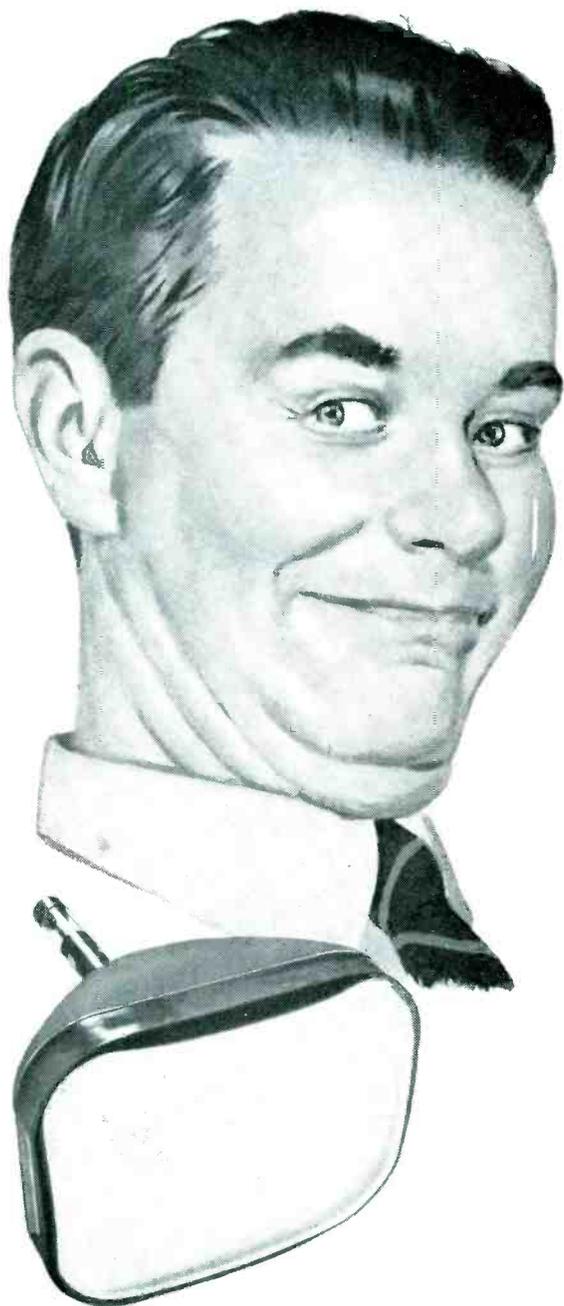

"... when I use Tung-Sol Tubes for replacement jobs! These dependable, long-lasting tubes stay put. Instead of wasting time on callbacks, I'm out servicing new business!"

 **TUNG-SOL**[®]
dependable
PICTURE TUBES

TUNG-SOL ELECTRIC INC., Newark 4, N. J. Sales Offices: Atlanta, Chicago, Columbus, Culver City, Dallas, Denver, Detroit, Newark, Seattle.

Associations

ARTS, Chicago, Ill.

A SCHEDULE of fall and winter lectures has been prepared by the Associated Radio and TV Servicemen, Chicago. One of the talks will feature a report by *Emerson J. Morris*, vice-president of the National Bank of Commerce of Chicago, on installment financing for the small radio and television service shop, and what to know about selling on credit.

Richard Harasek, of the radio division of Motorola, will appear at another meeting and discuss printed circuits and how they are produced. He will offer pointers in the servicing and repair of such circuits.

L. J. Couch, sales service engineer of Sylvania Electric Products, Inc., will be a speaker at another lecture and cover transistors; what they are, how they work, and where they may be going.

• • •

TISA, Chicago, Ill.

THE TELEVISION Installation Service Association, Chicago, Ill., has changed its name to the Television Electronic Service Association or TESA-Chicagoland.

• • •

ETA, Jamestown, N. Y.

TO ACQUAINT set owners with the unusual problems encountered in servicing, the Electronic Technicians Association, Jamestown, New York, have prepared a *friendly-message* card, explaining service guarantees, which is left at home or distributed in the shop by all members.

The card tells set owners that ETA members take pride in their work and strive at all times to do a top-flight job. Noting that ETA members guarantee parts and workmanship against normal service failure for a period of 90 days, customers are also informed that due to the complexity and nature of electronic equipment, many defects which seem identical can be caused by one of several individual parts or circuits; thus they explain it is not possible to assume responsibility for any portion of the instrument (parts, tubes or circuits) on which service has not been performed.

The invoice, the ETA card points out, shows work performed and parts replaced on which the guarantee is based.

Plane-load of Detroit service association delegates who attended recent uhf antenna clinic session at Taco's plant in Sherburne, N. Y.: Ralph L. Carew, **University Radio and TV Service, (Electronic Service Association);** Leander R. Rivard, **Triangle Television, Inc., (Macomb County Electronics Association);** F. William Vigelius, **Electronic Service Co., (Oakland County Electronics Association);** Mike Mosier, **Berkley Electronics, (South Oakland County Television Association);** and William O. Mattingly, **Matts Radio and TV Sales and Service,** Charles D. Judd, **Judd Electronics,** and Jack Barton, **Barton's Radio and TV Co.,** all representing **Television Service Association of Michigan.** Also on the plane was Ralph E. Sloan, director of publicity of the operations committee of the **Detroit Educational TV Foundation operators of the uhf station in Detroit (channel 56)** and Taco rep John Merchant. Technical sessions were directed by **Kendrick H. Lippitt,** Taco's chief engineer, assisted by **Norman Rea,** field engineer.



PR SMA, Philadelphia, Pa.

RICHARD G. DEVANEY will serve as president of the Philadelphia Radio Service Men's Association for '55-'56.

Devaney has been a member of the PR SMA advisory board and previously served two terms as vice president.

Samuel Brenner has been elected vice president; James T. Daly, recording secretary; Stanley W. Myers, treasurer; and William P. Humes, corresponding secretary.

RTTG, Miami, Florida

IN A REVIEW of the positive and negative aspects of licensing, in a recent issue of a monthly bulletin issued by the Radio and Television Technicians Guild of Florida, Charles Pierce declared that a majority of Service Men, recently polled, noted that they would be in favor of a properly written and administered licensing law.

Commenting on the present situation, Pierce said that now there are no duly authorized and appointed TV Service Men. Noting that there is no recognized authority to appoint master Service Men and allgrades in between down to apprentice, the RTTG member said that this condition does not bring about public confidence and trust. All respected professional trades have had licensing by examination for some time it was emphasized, and are much better off because of it.

The license law proposed would be administered by the county or state; not individual cities. According to the measure, there would have to be a master Service Man in charge of each shop who would be held responsible for the work performed by that shop; licensed journeymen doing bench work and making service calls; apprentices working under the supervision of masters and Service Men. A license would be granted after successfully passing a theoretical as well as a practical examination given by examiners qualified to render such exams. No one could apply for examination, it was stressed, who has not been a resident of the county for more than six months. All examination papers would be made available to any and all interested parties up to 30 days after taking such examination, so that qualified men will not be kept out and unqualified men will not get in through some political means. All persons now in business legitimately would be granted a license under the proposed law.

TEN YEARS AGO IN SERVICE

THE TREMENDOUS installation-servicing demands that the projected large-scale housing programs will create were viewed as a boon to the Service Man by industry and associations. This big job, association officials pointed out, will require extensive facilities, such as complete single-manned shops for each building and larger community operations to handle many buildings. To expedite repairs, it was suggested that shops feature specialists on receivers and antennas, and use portable and fixed instrument setups for apartment or bench multiple-set servicing. The instruments, housed in a rack mounting, could be so arranged, it was noted, that they would be plugged into position for fixed use or removed, via multi-pin plug jacks, for portable work. . . . Many types of miniature radios, of the pocket-sized style, using multi-element tubes and hearing aid earpieces were, it was disclosed, scheduled for a big push by manufacturers; a number of instrument makers were described as planning compact testers to check the new small tubes and components included in these tiny portables. . . . The first May parts and equipment show, sponsored by the parts division of the RMA, NEDA, Association of Electronic Parts and Equipment Manufacturers and the Sales Managers Club (Eastern Division), was announced for the Hotel Stevens, Chicago; the dates, May 13, 14, 15 and 16, 1946. . . . Newark Electric Company added 7,000 square feet of floor space to its store in Chicago. . . . R. B. Stuart was appointed sales manager of the Radel Manufacturing Co., Cleveland, O.


"IT SOUNDS BETTER THAN EVER..."



"... since my service man fixed it! Complicated sets are scarcely my cup of tea, but I do know this: he used Tung-Sol Tubes and my set's never worked better."


 **TUNG-SOL**[®]
dependable
TUBES-DIAL LAMPS

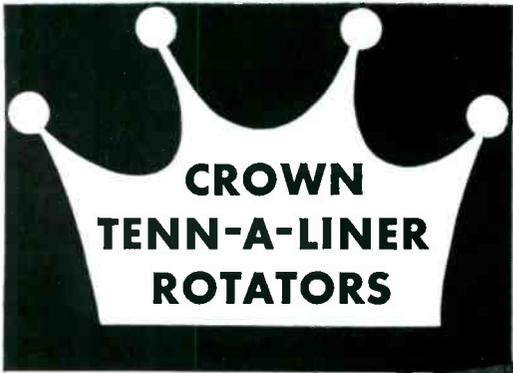TUNG-SOL makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.



BEST

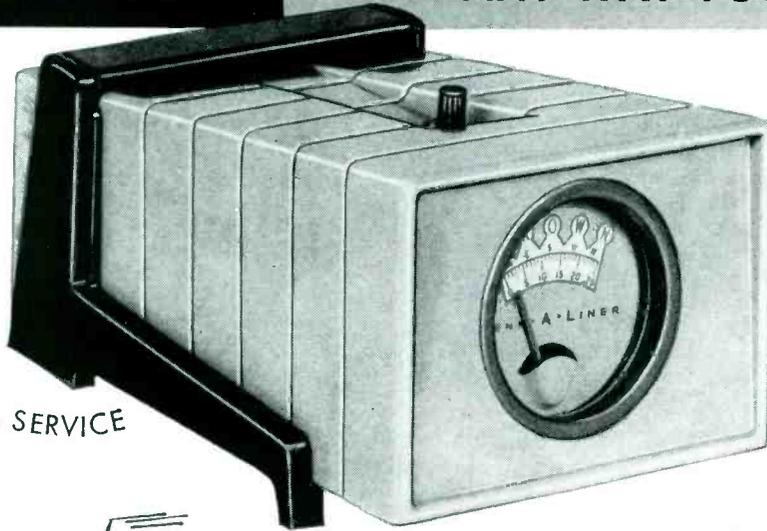IN ANTENNA ROTATION
ANY WAY YOU LOOK AT IT!



... SERVICE






PROFIT ..



... CUSTOMER
SATISFACTION

PERFORMANCE ...

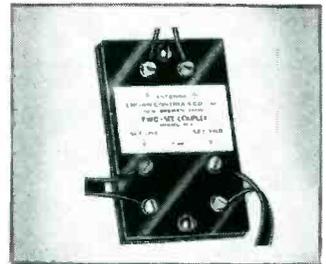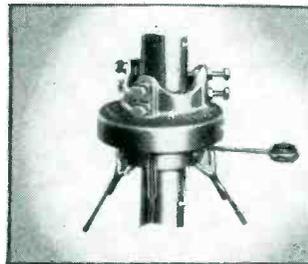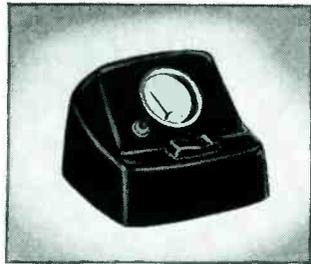

Right now is the time to get ready to cash in during the peak selling season ahead . . . get the complete story on the bigger profits possible with Crown Tenn-A-Liner Rotators. Available in two decorator-styled models, Crown Tenn-A-Liners give you the highest profits in the TV antenna rotator field. Crown's ruggedness and dependability increase customer satisfaction and reduce profit-consuming call backs . . . in fact,

only 1.06% of all Crown units sold require service. A guaranteed product, Crown's exclusive replacement policy keeps customers happy.

Crown also provides a complete line of TV accessories — the Crown TV Planter for use with the CAR6B Tenn-A-Liner, the Roller Bearing Guy Ring, and the Two Set Coupler — sure ways to make those extra sales that come from impulse buying.

For bigger profits this year . . . **SELL WITH CONFIDENCE, SELL CROWN!**

CROWN® CONTROLS Co., Inc. NEW BREMEN, OHIO

Canadian Subsidiary Crown Controls Mfg. Ltd. Export Division, 15 Moore St., New York, N. Y., Cable—"Minthorne"

Auto-Radio Technicians:

DELCO RADIO

TRAINING COURSES MEAN MORE BUSINESS FOR YOU



Working in small groups under factory-trained Delco instructors, alternate lecture and lab periods keep radio technicians up to date on latest radio and repair developments at a General Motors Training Center Delco Radio course.



Typical of the thirty General Motors Training Centers across the country is this one at Tigard, Oregon, a Portland suburb. Ample parking areas help to make this center popular throughout the Northwest.

Week-long courses for experienced service technicians provide latest radio and repair information—enable you to do the job faster and more efficiently.

Quick, accurate auto radio diagnosis and repair to factory specifications boosts your profits. That's why so many qualified auto radio technicians attend these Delco Radio training courses at no cost for tuition, school supplies, or equipment.

Factory-trained instructors, using latest equipment and instruction methods, conduct these intensified week-long courses, designed to familiarize repairmen with modern auto radio developments and factory-approved repair techniques.

The Delco Radio diploma, awarded only to those who successfully complete the course, is proof that you're equipped to give more and better service to more people—and that means more business.


If you're an auto radio service dealer, come yourself, or send your technicians. There's one of 30 GM Training Centers near you. Apply through your local Delco Electronic Parts Distributor or write Delco Radio Division of General Motors, Kokomo, Indiana.

DELCO RADIO
DIVISION OF GENERAL MOTORS
KOKOMO, INDIANA

HERE'S THE COURSE OF STUDY — (1) Circuitry differences between home and auto radios. (2) Dead radio trouble-shooting procedure and lab. (3) Noisy radio trouble-shooting and lab. (4) Weak radio trouble-shooting and lab. (5) Distorted radio trouble-shooting and lab. (6) Intermittent trouble-shooting and lab. (7) Push-pull lock-up tuner lecture and lab. (8) Mechanical operation of Signal Seeking Tuner. (9) Electrical operation and trouble-shooting of Signal Seeking Tuner. (10) Autronic-Eye operation trouble-shooting procedure and lab. (11) Autronic-Eye installation and adjustment procedure. (12) Transistors and printed circuits.

Simpson IN-CIRCUIT CAPACITOR LEAKAGE TESTER

model 383

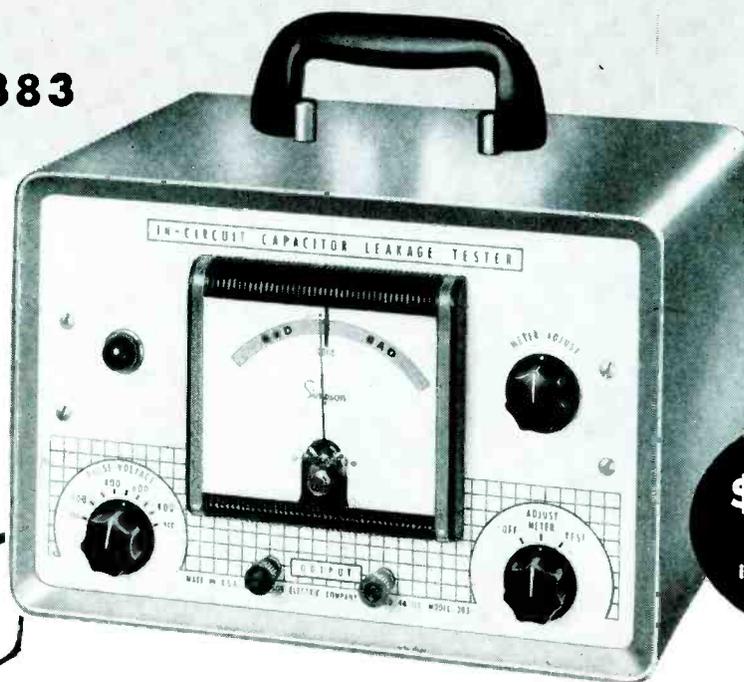

only
\$79⁹⁵

Including probe leads
and manual



**World's first tester that truly checks
paper, mica, and ceramic capacitors . . .
WITHOUT DISCONNECTING THEM
FROM THE CIRCUIT!**

Here's a new dimension in electronic instrumentation. Detects leakage in paper, mica, or ceramic capacitors, while connected in the circuit. No disconnections of any kind. Checks leakage, even when the shunting circuit resistance is only 1% or less of the leakage resistance value. Uses a new Simpson discovery (patent applied for).

Only two simple test leads to apply. Indication is on a "Good-Bad" scale—your customer can see *why* new capacitors are needed. Tests capacitors from 1 uuf to 0.25 uf in a jiffy. Indicates leakage resistance from "shorts" to hundreds of megohms. Also detects the presence of unstable *resistors* right in the circuit.

Be the first technician in your area to cash in on this fabulous Simpson tester. Sell *preventive* maintenance . . . fix "dog" sets in one-tenth the usual time. Double . . . yes, even triple your service income.

ask your jobber, or write . . .

Simpson ELECTRIC COMPANY

5220 W. Kinzie St., Chicago 44, Illinois


Phone: EStebrook 9-1121

In Canada: Bach-Simpson Ltd., London, Ontario

WORLD'S LARGEST MANUFACTURER OF ELECTRONIC TEST EQUIPMENT

WORLD'S MOST *Exciting* TV ANTENNAS

Originals by **WINEGARD**

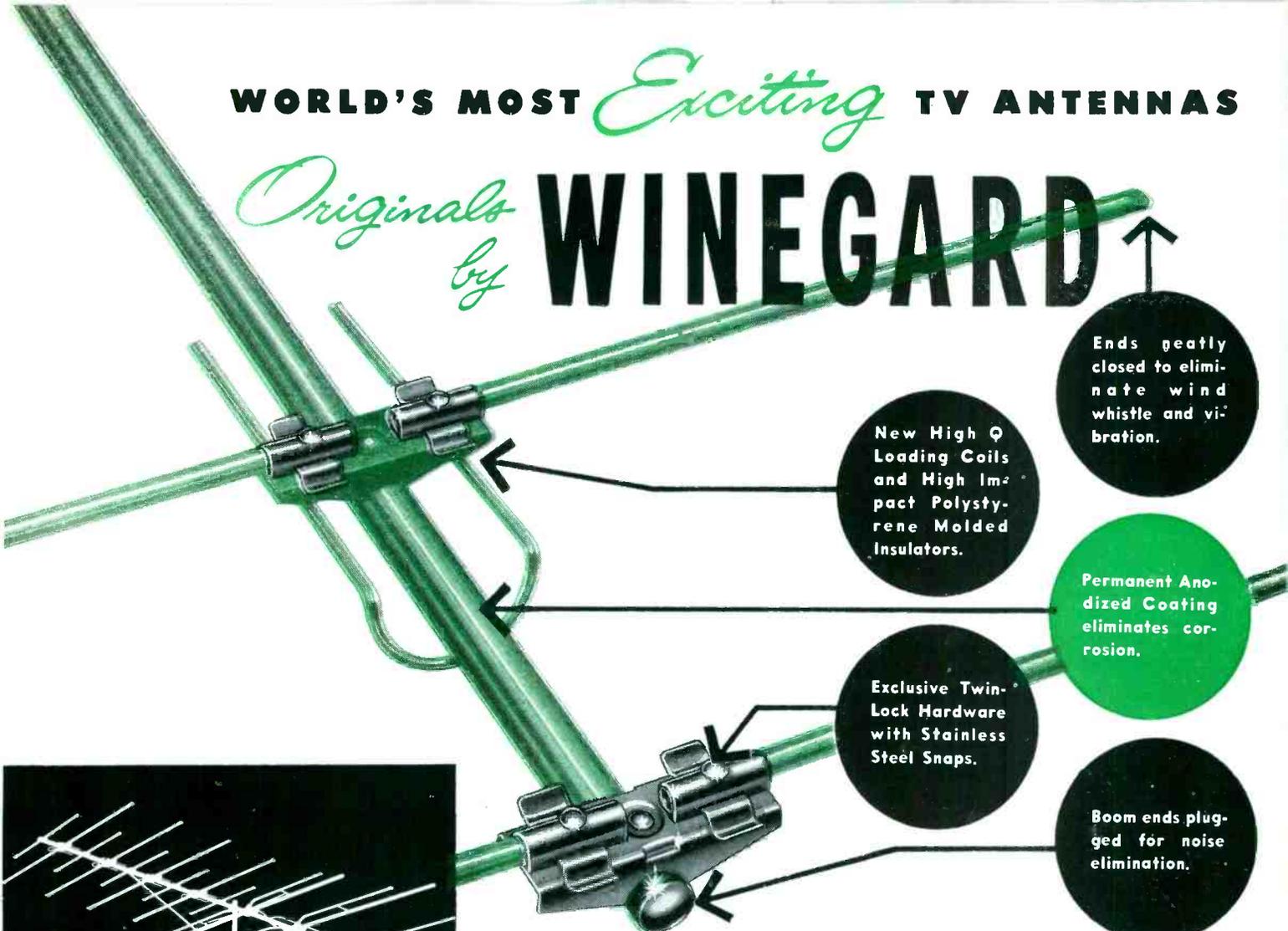


Ends neatly closed to eliminate wind whistle and vibration.

New High Q Loading Coils and High Impact Polystyrene Molded Insulators.

Permanent Anodized Coating eliminates corrosion.

Exclusive Twin-Lock Hardware with Stainless Steel Snaps.

Boom ends plugged for noise elimination.

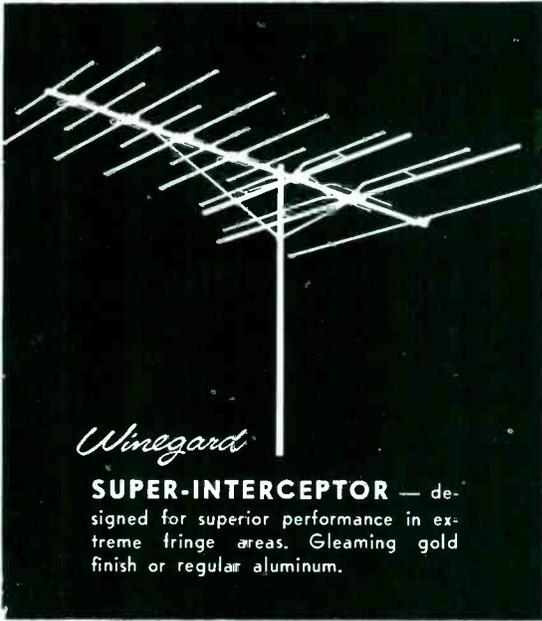

Winegard

SUPER-INTERCEPTOR — designed for superior performance in extreme fringe areas. Gleaming gold finish or regular aluminum.



Winegard

INTERCEPTOR — world's most imitated all-channel Yagi. Available in beautiful metallic shades of red, blue, green and gold.

Colors so Bright... They Sell on Sight

When it comes to antennas, you, as a technician, are naturally interested in gain, directivity, front-to-back ratios — all of the electrical and mechanical features that make antennas tick. But think of it from your customer's viewpoint. He is interested in only two things: (1) performance — getting the best possible pictures on his TV set; and (2) appearance — how the antenna looks on his roof. **Only Winegard Interceptor TV Antennas give you both unequalled performance plus neat, colorful appearance.**

Color is something people understand and *want!* That's why you should start installing Winegard anodized Interceptors NOW! Wait till people see these shimmering metallic colors sparkling in the sun! One installation and you'll have the whole neighborhood talking — asking who did the job. **You'll sell at least a dozen Winegard Interceptors from each one you install!**

Ask your jobber or clip coupon



Mail Today

WINEGARD COMPANY, Dept. B
3000 Scotten Boulevard, Burlington, Iowa

Please rush bulletin No. WL21455 Send complete technical information on Anodized Antennas Send complete technical information on Winegard Interceptors

FIRM NAME _____

ADDRESS _____

CITY _____ STATE _____

SIGNATURE _____

WHAT

have you got

that other



TV-Radio servicemen

haven't got?

When you are a *Raytheon Bonded Electronic Technician*, the answer is simple. You have the exclusive tool, the *only* tool in the industry that creates customer confidence — *draws customers to your shop.*

Under the Raytheon Bonding plan, your work and parts guarantee is backed by a Bond issued through one of America's largest insurance companies. Customers appreciate the value of this extra protection and, all else being equal, give their business to the Raytheon Bonded Dealer.

If you can qualify for the Raytheon Bond, it won't cost you a penny. Call your Sponsoring Raytheon Tube Distributor today for the whole story.



Excellence in Electronics

RAYTHEON MANUFACTURING COMPANY

Receiving and Cathode Ray Tube Operations
Newton, Mass., Chicago, Ill., Atlanta, Ga., Los Angeles, Calif.

RAYTHEON MAKES ALL THESE:

RECEIVING AND PICTURE TUBES • RELIABLE SUBMINIATURE AND MINIATURE TUBES • SEMICONDUCTOR DIODES, POWER RECTIFIERS AND TRANSISTORS • NUCLEONIC TUBES • MICROWAVE TUBES

SERVICE

The Technical Journal of the Television-Radio Trade

Prepare Now for Color TV

COMBINED EFFORTS of the TV network and set manufacturers, which went into high gear this fall, have lifted color TV off the ground and ushered in a field bouncing with opportunities for the Service Man.

Set makers are now planning to produce nearly a quarter of a million color chassis during the next twelve months. And a year from now industry experts believe that both the tube and set manufacturers will be sorely pressed to supply the demand. In '57 the production of nearly a million and a half units is expected. Beyond that year no one can be found who will hazard a guess as to the upward trend of output and sales.

Everyone is equally as optimistic regarding costs, noting that prices will drop and bring sets within reach of the buying potential of a large

percentage of the present b-w TV set owners.

All of this means big business for the Service Man. Those aware of these enormous possibilities are preparing themselves *now* for this gala color era.

Since early summer, SERVICE has been paving the way for the color push, offering complete information on sets and instruments. Next month, the *prepare-now* program will receive headline attention; SERVICE will publish an exclusive technical color-TV progress report that will reveal for the *first* time new circuitry trends for sets and test gear, new color picture and receiving tube developments and the latest bench-field installation-repair techniques.

Don't miss this all-important field report, exclusive in SERVICE.

A Must for Phonos: Periodic Inspection and Service

IN NO SYSTEM in the electronic family is periodic inspection and service so vital as in the phono, because of its network of expendable components. Here practically every item has a wear factor, requiring policing and replacement on a consistent basis.

Up front in this replacement chain is the needle; even the diamond finds itself roughed up by the abrasive action of a record. In the cartridge there are a number of items that can deteriorate with age, one of the most critical being the damping material. When this becomes damaged due to aging, peaking and subsequent distortion occur.

Then there is the speaker, whose cone is always affected by changes in temperature and humidity, as well as dust particles in the air. And, of course, the motor and turntable are always suspects for wear and tear.

In a number of phonos, capacitors and resistors, packed tightly in contained areas and enveloped by tube heat, are also subject to aging breakdown.

Every element in the phono chain is actually an expendable part that demands the closest periodic inspection and complete replacement to insure fidelity results that will match the quality output originally available.

The Readers Run the Show

EACH YEAR, at this time, we observe an important anniversary; the birthday of ABC, the Audit Bureau of Circulations, in which we have had a long-time record of continuous membership for over twenty years.

We belong to ABC to give advertisers an independently audited circulation count and an accurate description of the circulation audience they reach when their sales messages appear in our journal.

While the major objective of the bureau is to give advertisers accurate, verified information about the net paid circulations of all publisher members, its work has also a very real importance to our readers.

*Design-application field reports on needles, cartridges and motors, detailing how they should be screened for every phono job, appear in this issue on pages 42 to 49.

Our ABC reports serve us as editorial guides. The reports reveal the business or occupation in which our readers are engaged, and thus we can arrange our editorial coverage to serve their interests most effectively.

All of the other factual information in the report serves to guide us in our editorial planning—to bring our readers a useful, interesting publication of the type they want.

The needs of our readers keep us on our editorial toes; we must help and serve them to merit their continued patronage.

By subscribing, by renewing their subscription and by reading SERVICE, our readers keep us on top, as an editorial leader—to make sure that they will always agree that to them, we are worth the price of admission.—L.W.

SERVICE... The National Scene

PICTURE TUBE REPLACEMENT MARKET SOARING--The 30-odd million TV sets that have been in the field for over a year--many have been in use for nearly five years--have developed a bulging market for replacement picture tubes, that next year is expected to create a demand for over 60 per cent of all of the tubes being made. . . . Production records of this year and last dramatically reveal this marked trend. Currently, about a 50-50 basis obtains for the manufacture of pix tubes for replacements and original equipment. A year ago, almost 70 per cent of the tubes were being made just for new chassis. . . . The recent significant advancements in tube design, offering a parade of improvements in picture quality, are also serving to generate growing interest in replacements. And, in addition, industry spokesmen have disclosed, their superior performance is highlighting the advantages offered by nationally-advertised standard-brand tubes. Commenting on this important fact, one specialist said that in these tube plants, not only is every process supervised with meticulous care, but all materials are subjected to critical quality control, and every piece of equipment used in tube fabrication is closely guarded and kept hospital-clean to avoid any air or liquid contamination that could affect the life and results.

EXPERIMENTAL POST-ACCELERATION RECTANGULAR COLOR PICTURE TUBE DEMONSTRATED--A lab type 22-inch rectangular three-gun post acceleration color tube, using electron optical masking rather than shadow masking, was unveiled recently at a progress-report demonstration. In this tube electron beams, directed at vertical color-phosphor stripes inside the face of the tube, were, it was pointed out, accelerated after passing through an array of parallel wires located close to the screen. . . . The grille of parallel wires, called a color-selecting electrode, was described as having a high transparency, permitting a substantial percentage of the electrons ejected from the gun to strike the screen, thus contributing to picture brightness. For equal high-voltage power input, it was said, this tube theoretically offered about six times more brightness than the shadow-mask tube. . . . Since the three beams are all in one plane, both static and dynamic convergence are required for only the two outside beams. This design, it was felt, would reduce the relative complexity of the convergence problem in each of the four functions of horizontal dynamic amplitude, horizontal phasing, vertical amplitude and vertical tilt. . . . Scientists on the project estimated that at least another year of development work would be required before the tube would be ready for the set market.


VHF CALLED SUPERIOR BAND BY FCC COMMISSIONER--The veryhigh channels were recently viewed as the best bet for overall reception by a member of the Federal Communications Commission. He based his opinion on nationwide results which indicated that the vhf signals can travel further than the ultrahighs without deteriorating and are also easier to control at the transmitter and receiver. . . . To capitalize on these features, the Commissioner proposed an extension of vhf to 342 mc and movement into the 132-174 mc bands, shifting present tenants to above 500 mc. This might be done, he said, by relaxing the present separation rules and also creating another TV service providing for low-power stations in small-town areas.

TV AUDIO SPURS INTEREST IN FM--The exceptional quality available from the sound channel of TV receivers, thanks to FM, has sparked new interest in FM receivers. . . . As a result, Service Men are now being called on with greater frequency not only to maintain and repair FM sets, but recommend new models designed to provide that better sound on FM's wide-band noise-free channels. . . . Many feel that FM, often tagged the faltering medium, is really out of the woods and on its way to popularity row where it belongs.--L. W.

All New!
RCA WO-91A
5" 'SCOPE FOR
BLACK and WHITE
and COLOR TV

Only \$229⁵⁰
 User Price (Optional)

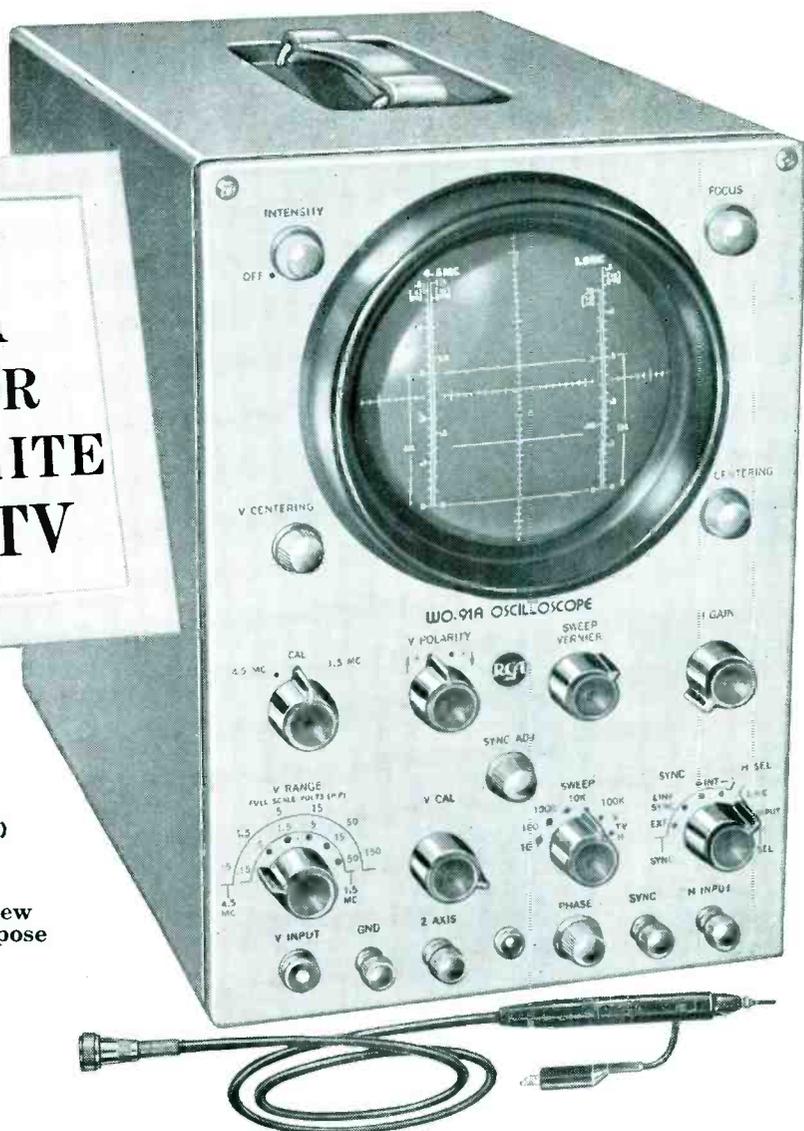RCA WO-91A 5" OSCILLOSCOPE
 Complete, ready-for-use, including new
 WG-300A low-capacitance, dual-purpose
 probe, shielded input cable and
 instruction book.



NOW—AN ALL-NEW OSCILLOSCOPE with features usually found only in more expensive instruments. It has all the 'scope functions you need to do both black-and-white and color TV service work . . . speedily and with top-grade results! Check a few of these work-simplifying features . . . "low-capacitance/direct" probe . . . preset "V" and "H" sweep positions . . . automatic probe-disconnect calibration control. And look at the added features of this instrument:

- *Dual-band response. Response flat to 4.5 Mc in wide-band position.*
- *Voltage-calibrated, frequency-compensated, 3-to-1 step attenuator for "V" amplifier.*
- *Simplified, semi-automatic voltage calibration for simultaneous voltage measurement and waveshape display.*
- *VTVM-type graph scales marked in peak-to-peak volts—read voltage amplitude directly from screen.*
- *Vertical-polarity reversal switch for "upright" or "inverted" trace display.*
- *Sturdy one-piece low-capacitance/direct probe minimizes circuit loading.*
- *Z-AXIS input facilities permit direct modulation of the cathode-ray tube grid.*
- *Preset "V" and "H" sweep positions for speedy, automatic lock-in at "vertical" and "horizontal" frequencies.*
- *"Plus" or "minus" internal-sync selector.*
- *Shielded vertical-input connector and shielded cable for minimizing hum and stray field pick-up.*
- *Positive-lock internal sync.*

FREQUENCY RESPONSE: Wide-band position, within-1 db from 10 cps to 4.5 Mc; Narrow band position, within-1 db from 10 cps to 0.5 Mc; within-6 db at 1.5 Mc.

SENSITIVITY: 0.05 volt peak-to-peak per inch (0.018 volt rms) in narrow-band position; 0.15 volt peak-to-peak per inch (0.053 volt rms) in wide-band position.



RADIO CORPORATION of AMERICA
 TEST EQUIPMENT
 HARRISON, N. J.

See the ALL-NEW
 WO-91A at your
 RCA Distributor.
 Order now for
 early delivery.

The Independent Service Man



A Field Study of the Complete

by the Small

(Left)

Delivery car, which doubles as a sound truck. Horns are mounted on a detachable carrier and are removed when vehicle is used for delivery purposes.

SMALL-TOWN SERVICING is no longer a limited operation. Today, shops in the smaller communities are involved in installing, maintaining and repairing almost the same lineup of equipment found on big-city service benches. For instance, in our shop we not only service table model, console, portable, auto and straight battery radios and TV sets of all sizes, shapes and kinds, old and new, but transistorized gear, phonos, from *kid-die-players* up through home consoles to hi-fi rigs. And we've also been called on to take care of home movie projectors, intercom and pa systems, wire, tape and disc recorders, radio-operated garage door openers, and an assortment of electronic devices, ranging from complicated gas-fired boiler controls with photocells, to simple *moisture-meters* used in testing lumber for dryness. The list is a long one, and covers all phases of the art; one must be prepared to tackle any kind of a job, no matter how far away he lives.

Radio-TV dealers in the small town seldom maintain their own service departments; most of them pre-

fer to use the facilities of the independent Service Men and their seasoned experience. The practice has not only been found to be technically superior to an on-the-premise operation, but a wise one economically. Most of the small-town radio-TV merchants are actually appliance and hardware dealers handling white goods, stoves, refrigerators and radios, with TV as a sideline; their installation-service volume is rarely sufficient to warrant the expense involved in setting up and operating a special service department. Therefore, the independent Service Man profits by doing this work for them.


In our town, where there are five service shops, two specialize in handling installation and repair for dealers.

Dealers are generally given discounts on service calls and installation work, and calls made for warranty work; such discounts range from ten to twenty per cent. Some dealers pick up sets and bring them to the shop, also delivering them; others merely call the Service Man and turn the call over to him.

Replacement of parts and tubes on warranty can be a headache, unless one is very careful. New parts must be replaced from stock, the defective parts being turned in to the state distributor, located in another city. This requires packing and shipping at least once a month. If this practice is neglected, one can sustain a serious loss, for the warranty period could expire and the parts are then unreplaceable. It has been found that the best way to handle this problem is to issue a charge for all parts used to the dealer, allowing a good discount, and then let him take care of the packing and shipping. When parts are replaced to the dealer, credit can then be applied on the current month's bill.

Rural Service Men are also faced with the long service-call problem; ten or twenty miles out of town. While there is no universal solution, we have found that the practice of charging on a call-charge plus-mileage basis works out very well. Our fees, in this area, are \$5.00 for an out-of-town call, plus ten cents per mile, both ways. In our territory,

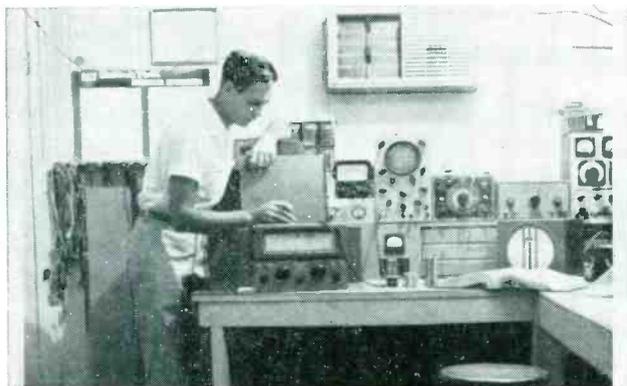Corner of rural service shop where test equipment for radio repair is mounted.



Checking sets in over the counter. Shop is visible through picture window behind operator.



In The Rural Areas


by JACK DARR

Facilities and Services Provided

Town Radio-TV Shop

(Right)

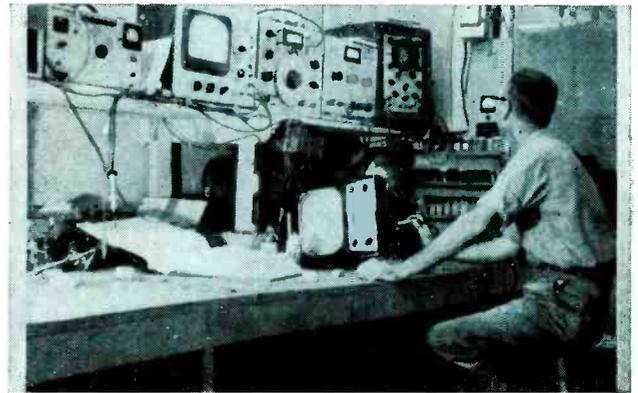The TV service bench section of Darr's shop, with its complete lineup of test instruments.



many customers bring their sets to the shop.

With the growth of TV, small-town Service Men have been faced with the same situation which appeared in big-city shops a few years ago; conversion of the shop from radio to radio plus television. This has necessitated not only a change in education, but in the physical layout of the shop. Instrumentation, tools, service bench and data department; all must be worked over, if the shop is to operate at maximum efficiency. Our own old shop, for instance, was well set up for general radio repairing. The bench was 9' long, and 20" wide; test equipment was mounted in panels, about 6" above the bench, fixed more or less permanently in place. Six fluorescent lamps, in two fixtures, gave adequate illumination. This was fine, until the first TV sets came in. The huge chassis hung precariously off the edge of the bench, while the pix tube completely obscured the test equipment; we were forced to peer around the ends of the chassis to read meters! We completely redesigned the service bench to cope with this changed set of working requirements.

Our new bench is 19' long, with a four-four L-shaped section at the back. Equipment is no longer fixed in place, but rests upon a shelf, two feet wide, at a height of two feet above the bench. This has provided us the needed clearance to see over TV chassis; if it is necessary, pieces of test equipment may be rearranged at any time, to facilitate checks and repair. The old bench was faced with a panel board on which were mounted test-speaker jacks and meters. These had to be moved and now occupy individual small panels, placed near the spot where they will

be used. Total width of the new bench is exactly four feet; the shelf covers two feet of this, but is open underneath, so that TV sets can be pushed partially under it. Even so, it could have been at least six inches wider; this might have made it difficult to reach the test equipment, so that the final width is more or less a compromise.

An isolation transformer and wattmeter have been mounted on the wall at the TV end of the bench; this enables the servicing of *line-connected* chassis without too much shock hazard. For convenience, receptacles connected to this are brought down the bench to two different locations. The wattmeter is fused, with a 5-ampere unit, for protection against overloads.

At the back of the bench, on the L-shaped section, radio test equipment is located. These instruments are on a lower shelf, about 8" high, for added convenience. This provides the needed separation for the two *branches* of the work, and allows us to leave TV sets on the bench, while doing radio work. Before, one TV set covered up practically all of the available space, and had to be

moved, if anything else was to be done.

A drastic change in instrumentation was also necessary; instead of one *vtm*, two are now in use. One is used for radio (the older model) and a newer model (equipped to read peak-to-peak voltages with center zero-scale for *dc*) is used for TV service work. Added equipment included a sweep generator and another 'scope. The new 'scope was selected for TV work; the older model is used for radio alignment work, testing vibrators, etc. In between the two *departments*, we installed a microvolter signal-generator and a frequency-deviation monitor for two-way FM communication system repair and maintenance.




The special gadgets, which we had in the old bench, were transferred to the new one and remounted. These include a universal test speaker, with a set of extension jacks at three different positions, an auto-radio power supply converted to handle either 6 or 12-volt radios, and an auto-transformer which, in conjunction with a small electric battery eliminator, is used to test battery radios. There are

(Continued on page 50)

Another section of shop in which service manuals and technical data files are kept, and supply of tubes and batteries are stocked.



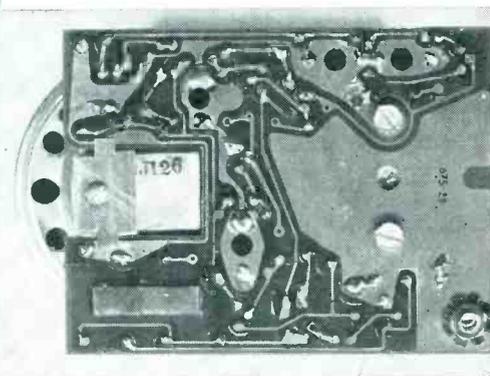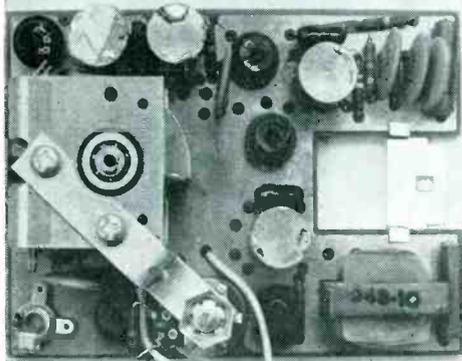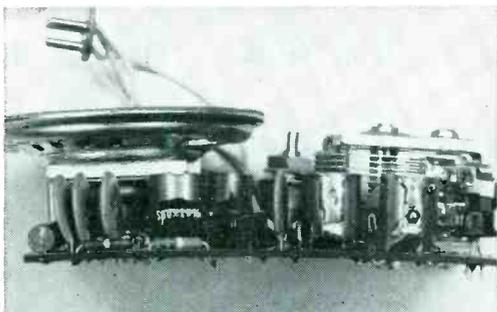Transistorized Printed Circuit Pocket Radio



[See Front Cover]

(Left)

Side, top and underside views of transistorized pocket set.

THE DEVELOPMENT of hermetically-sealed fused junction-type transistors, for all-stage use in radios, has made it possible to design and produce completely transistorized pocket-sized receivers, with a number of circuitry innovations, as illustrated on the cover and in Fig. 2.†

In this model five transistors are used; four *pnp* and one *nnp* type. These are almost identical, except that the direction of all currents and voltages is reversed. The *nnp* transistor corresponds to an electron tube with ordinary (negative) electrons as charge carriers; the *pnp* transistor corresponds to a tube that would have positive instead of negative electrons. In this set the *pnp* transistors function as oscillator-converter (2N123 or 2N136), *if* amplifiers (2N137; 2N135 or 2N123), and audio output (2N44), while the *nnp* transistor serves as the detector (2N78).

Oscillator-Converter

The oscillator-converter (2N136 or 2N123) stage is similar in operation to the vacuum-tube converter circuit shown in Fig. 1. As in all superhet circuits, the *if* transformer accepts the proper frequency from the many frequencies in the output of the converter and passes this frequency to the first *if* stage. In this chassis a built-in tuned iron-core loop antenna

†Based on information prepared by the Technical Publication Group, Radio and Television Department, General Electric Company.

feeds received signals into the oscillator-converter.

IF Amplifier


It is relatively simple to design a multi-stage *if* amplifier for vacuum tubes, because there is relatively little reflection from the output side to the input side of each amplifier.

A transistorized *if* amplifier is a little more difficult to work out since the input side is closely coupled to the output side through the transistor. Actually, any change in the final output circuit will be reflected to all of the preceding stages. Also, the input impedance of a transistor stage is much lower than its output impedance.

Tuned Primaries

In this model only the primary of the *if* transformers is tuned. The *if* transformer primaries are high impedance and are slug tuned. The secondaries are low impedance to match

Fig. 1. Vacuum tube oscillator-converter circuit, which is basically similar in operation to that used in transistor radios.

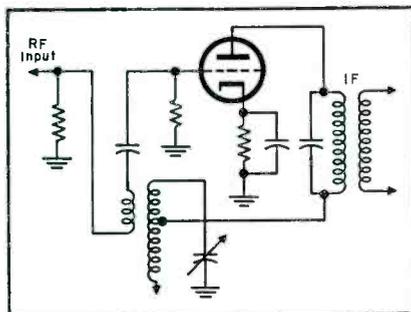

the transistor input impedance, and are not tuned.

As mentioned, any change in a transistor circuit will be reflected to all previous stages. Because of this, a change in the second *if* stage will be reflected back into the first *if* and converter stages. Thus, we can see that the 100-470 ohm resistor (R_7), in the grid of the second *if* amplifier (2N135 or 2N123) will affect the overall gain of the *rf* and *if* system of the receiver. Therefore, the value of R_7 in each receiver has been chosen so it is high enough for maximum gain, but not too high to cause the *rf* and *if* system to regenerate.

The first *if* amplifier (2N137) has a fixed emitter bias so that the *agc* control on the collector and base will control the gain of this stage. A pair of resistors (560,000 and 12,000 ohms; R_8 and R_9) form a voltage-divider network to bias the base of the second *if* amplifier (2N135 or 2N123). Another pair of resistors (47,000 and 220-ohms; R_8 and R_{10}) form a divider network to furnish bias for the base of the detector (2N78).

Second Detector and Audio Output

The second detector (2N78) is similar in operation to a vacuum tube plate detector. The base is biased at nearly *cutoff* so that the transistor will only conduct when a signal is applied between the base and the emitter, and then only on the positive half of the *rf* cycle. This, of course,

‡G. E. model 675.

gives us rectified *rf* in the collector circuit, which is bypassed to ground leaving only the intelligence contained in the envelope.

This audio voltage is applied across a 5,000-ohm volume control (R_{11}). Because the 2N78 detector draws current while receiving a signal, there will be a voltage drop across the volume control, the polarity of which is negative, and the amount in proportion to the setting of the control and the strength of the received signal. This negative voltage biases the base of the 2N44 output transistor and delivers the audio signal to this stage.

Thus we can now see that the 2N44 power-output stage will draw current directly proportional to the strength of the received signal and the volume-control setting. The output of the 2N44 is taken from its collector and fed through the output transformer (T_6) to the loudspeaker. The transformer is necessary to match a 16-ohm speaker to the high output impedance of the 2N44.

Automatic Gain Control

The purpose of *agc* in a radio receiver is to maintain the carrier voltage at the second detector approximately constant. Its function is to counteract strong signals by reducing the gain of the *rf* or *if* amplifiers. In a vacuum-tube radio this is accomplished by biasing the grids of the

Analysis of New G.E. Circuit Developed For Portable

Chassis Using Fused Junction PNP and NPN Transistors.

by WYN MARTIN

tubes in these stages with a *dc* voltage derived by rectifying the carrier. An increase in signal increases the negative bias, which reduces the gain of the unit and vice versa.

In a transistorized radio receiver the *agc* system must perform the same duty as in a vacuum tube set, but, because of the transistors, it must be accomplished in a different manner.


In the 2N78 detector stage, the emitter bias comes from the B- supply (-13.5 v) through a 2,700-ohm resistor (R_{12}). The 2N78 does not draw current until a signal is received. Therefore, with no signal the voltage drop across the 2,700-ohm resistor is created only by the current drawn by the previous *rf* and *if* stages. When a signal is received, the 2N78 draws current proportional to the strength of the signal, and the voltage drop across the 2,700-ohm resistor will increase. Effectively then,

the bias (negative) to the converter and *if* amplifiers will be less negative on a strong signal than it is on a weaker signal. This changing bias supply will change the gain of the 2N137 first *if* amplifier greatly, since it changes the bias of the base and collector, with respect to the emitter which has a fixed bias from the battery. On the other hand, the converter (2N136 or 2N123) and second *if* amplifier (2N135 or 2N123) will only be controlled slightly since the bias on all elements of these transistors change in unison.

Thus we find that when a strong signal is received the 2N78 detector will draw more current, increasing the drop across the 2,700-ohm resistor and lowering the bias for the converter and *if* amplifiers. The first *if* amplifier (2N137), having a fixed emitter bias, will be controlled by

(Continued on page 51)

Fig. 2. Schematic diagram of G.E. 675 transistorized portable radio.

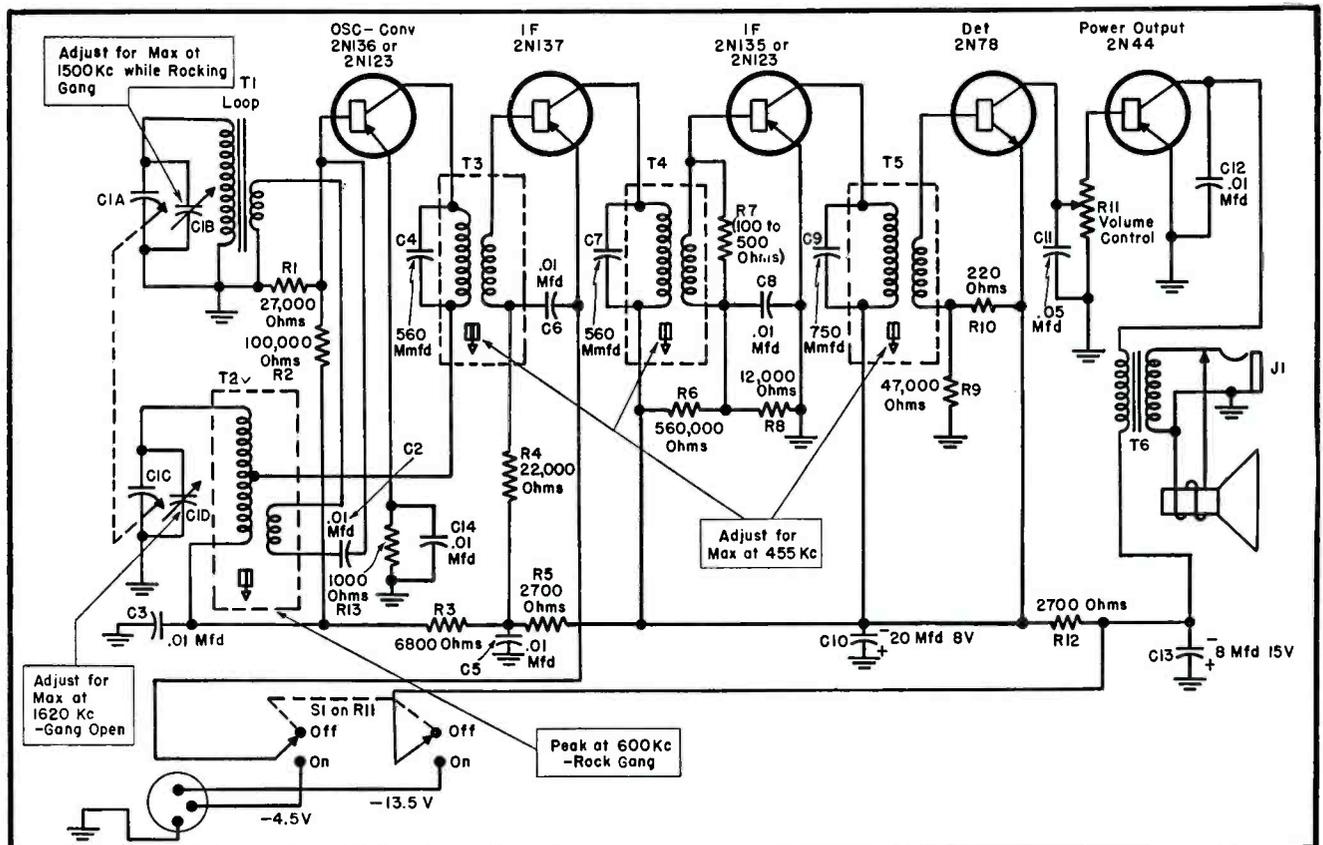

Power Wire-Wound Resistors

Their Construction . . . Application . . . Tips on Installation

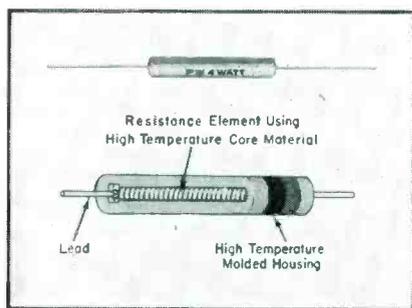


Fig. 1. Molded 4 watt power wire-wound resistor and its construction.

Fig. 2. Flat type molded power wire-wound resistors.


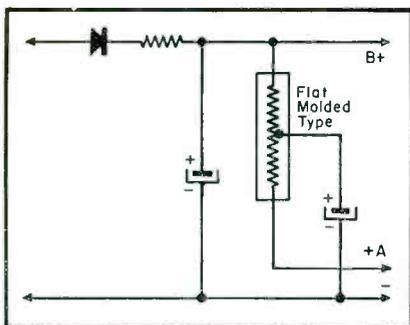
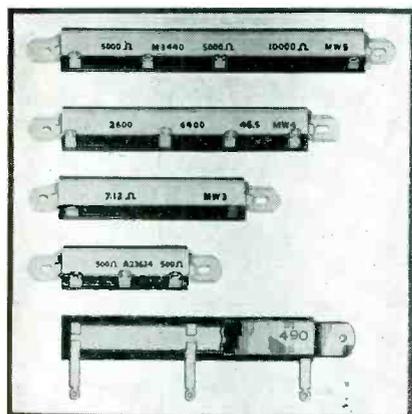


Fig. 3. Partial schematic showing application of flat molded-type power wire-wound resistor as the resistance element in a resistance-capacitance filter and as a voltage dropping resistor for the series filament string in a typical 3-way portable radio.

Fig. 4. Examples of 7 and 10 watt cement-embedded type power wire-wound resistors.

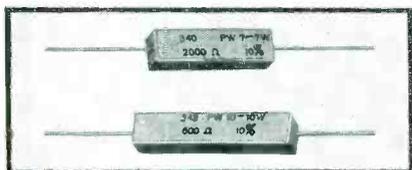

POWER WIRE-WOUND resistors are used in radio, TV and communication receivers, as well as industrial electronic equipment, where a power dissipation of more than 2 watts is required. Normally they are large enough to permit a manufacturer to stamp his part number and the resistance value and wattage rating on the unit. Besides coming in a multitude of colors (such as blue, green, gray, red, and sand), the resistors also come in a variety of shapes, as solid cylinder, round-tubular, oval-tubular, square, flat-rectangular, and *dog-bone*.

Molded Power Wire-Wound Types

Where the power dissipation is near or greater than two watts, under high ambient temperature conditions, it is necessary to use molded wire-wound resistors that are rated at 4 watts. One such type is illustrated in Fig. 1. Typical applications include *r-c* filter networks, used in auto sets where the ambient temperature is high.

A second version of this type is shown in Fig. 2. Here the resistance element consists of a strip of insulation over which wire is wound; the wire size and the amount of turns produce the resistance desired. Terminals are attached to both ends of the strip and the completed subassembly is then molded.

This version is manufactured in body lengths of from two to five inches, and covers a power range of from approximately 4 to 10 watts in free air, and approximately 8 to 18 watts when mounted on an average-sized television chassis. The resistor is mounted by means of a metal strip which holds the flat side of the resistor firmly against the chassis. This is done to provide better heat dissipation through the chassis, and accounts for the increase in this resistors' power rating over that of one in free air.

Still another version of this type of resistor has an additional resistance element encased in a metal housing with a strip of insulating material separating the resistance winding from the housing. Such resistors are used extensively in 3-way portable receivers as both the resistance element of an *r-c* filter network and a voltage-dropping resistor for series filaments. A typical circuit using this type of resistor is shown in Fig. 3.

Cement-Embedded Type


There's another type of resistor which uses a resistance element similar to that of the molded power wire-wound type, but instead of being molded, it is first encased in an open-sided ceramic shell and then completely embedded in a special cement. This allows operation at a much higher temperature, which, in turn, permits its overall size to be relatively small (for a given resistance). Typical 7-watt and 10-watt sizes are shown in Fig. 4.

In another version of this type, the resistance element is placed within a ceramic tube and the ends are sealed with cement. Cement-embedded resistors are used extensively in hi-fi equipment, as well as radio-TV receivers.

Round- and Oval-Tubular Types

The round-tubular type of resistor is familiar to old timers, since it has been used in electronic gear for more than 25 years. The internal construction of the oval-tubulars is similar to the round-tubulars, with a winding


Fig. 5 (right). Oval tubular-type power wire-wound resistors found in all types of electronic equipment. In a 22-watt model is illustrated (this model is also found in a 15-watt size with a 1/4" long core and in all other sizes shown in b for the adjustable type); 63, 47, 37 and 22 watt models are shown, from left to right in b.

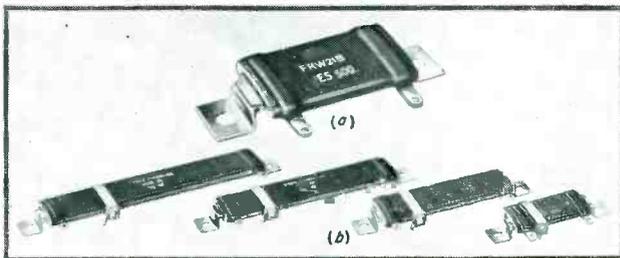

Service Engineer, International Resistance Company

(Right)

Fig. 6. Typical sizes, types and methods of mounting for round tubular type power wire-wound resistors. A 5-watt model is shown in a; in b is an 8-watt unit; a 10-watt type with single end mounting is shown in c; a 10-watt adjustable model with single end mounting appears in d; e shows a 20-watt model; f illustrates a 50-watt adjustable model with 3 types of mounting; g is a 45-watt adjustable model with through-bolt type mounting; a 40-watt tapped model is shown in h and in i is a 50-watt model with ferrule terminals for clip-type mounting. Models shown in c and d are also used with same terminals as 5- and 8-watt sizes.

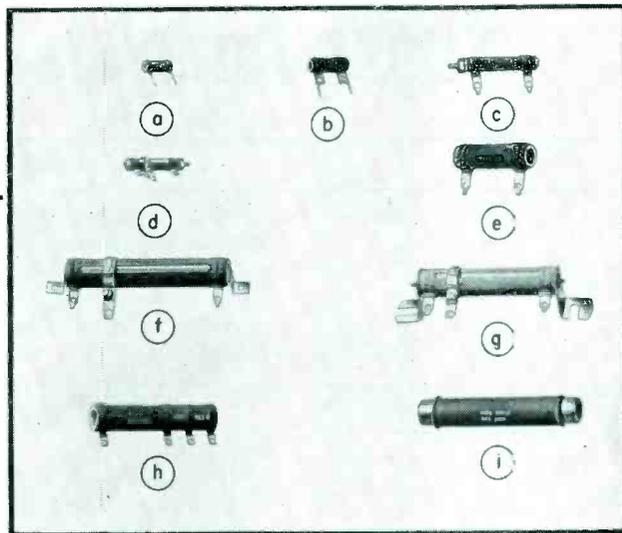

forming the resistance element (as in the cement-embedded type). The windings are covered with a special coating to protect them from mechanical damage, as well as environmental conditions, such as temperature and humidity.

The larger-sized units of both types can be provided with taps, so that they can be used as voltage dividers, or with an open slot and slider which make them adjustable.

The round-tubular types come in sizes ranging from 5 watts, with a dimension of 1" x 5/16" od (outside diameter) and a maximum resistance value of 3000 ohms, to 225 watts with a dimension of 12" x 1 1/8" od and a maximum resistance of approximately .5 megohm.

The oval-tubular type is provided in sizes of from 1 1/4" core length, for a power rating of 15 watts and a maximum resistance of 15,000 ohms, to a 6" core length, for a power rating of 75 watts and a maximum resistance of .14 megohm. Figs. 5 and 6 show typical examples of round- and oval-tubular sizes, types, and methods of mounting.

The oval-tubular resistor is used where high power dissipation is required, such as in bleeder circuits, and where there is limited space. This is made possible by using the mounting bracket as a heat conductor to the chassis. These resistors can also be stack-mounted, as illustrated in Fig. 7.

In some electronic circuits a power-type resistor with a low inductance value is required. When manufactured by standard methods, both the round- and oval-tubular type power wire-wound resistors have very high inductances. However, when a special type of winding, the Ayrton-

Perry winding, is used (Fig. 8) low inductance obtains. Two windings are used here, with the total resistance of both windings twice the required resistance. One winding is wound in an opposite direction from that of the other, and both windings are connected in parallel. This results in a reduction of the two inductances, since the magnetic fields set up by each winding oppose each other, thus reducing the effective inductance.

Tips on Installation

It must be remembered that the power wire-wound resistor operates at a very high surface temperature and can give a very painful burn upon contact. Also, it may damage the wiring or other component parts if it is mounted too close to them. Fig. 9 shows a typical temperature rise curve versus percentage of rated load for round- and oval-tubular types. This plot reveals that when these resistors are operated at their full rated load, a temperature rise of approximately 300° C prevails. This,

(Continued on page 56)

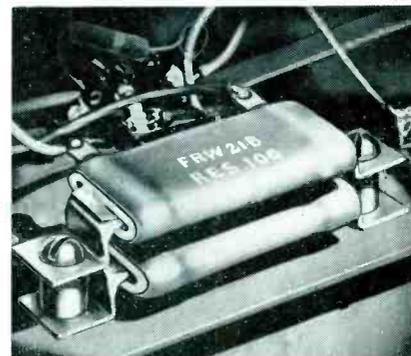


Fig. 7. Method of stacking oval tubular type power wire-wound resistors to obtain higher power dissipation in a limited space

Fig. 8. Ayrton-Perry method of winding round and oval tubular-type power wire-wound resistors to reduce inductance.

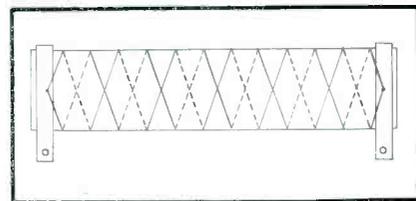


Fig. 9. Approximate temperature rise for power wire-wound resistors mounted in free air

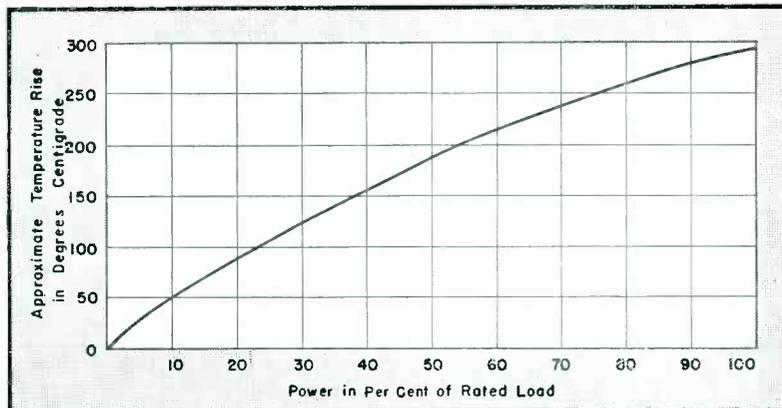



Chart Analysis of Wide-Band Chroma

Design Features	Purpose in Amplifier	Performance Factors
Input coupling network. (11)	A series coupling capacitor prevents the entry of <i>dc</i> voltage to the grid of the 6AN8, which would disturb the operating bias. The capacitor permits application of the <i>ac</i> chroma signal to the grid.	The value of C_6 , with respect to the value of R_3 , determines the lowest frequency which can be applied without attenuation to the grid. When C_6 is doubled in size, the low frequency limit is extended by a 2-to-1 factor. See circuit at right; circle (11).
Cathode bias network. (12)	Space current through the 6AN8 produces a voltage drop across R_4 which is utilized by the circuit as cathode (grid) bias. C_7 provides a low-impedance <i>ac</i> path to ground, thus avoiding degenerative signal attenuation.	The value of R_4 is chosen to provide an operating point at the middle of the linear portion of the grid-plate characteristic. The value of C_7 must be larger than C_6 , because R_4 is smaller than R_3 . See circuit at right; circle (12).
Series peaking network. (13)	L_1 holds up the mid-band response of the circuit, by resonating with the circuit capacitance in the 2-mc region. Damping resistor R_5 broadens out the response to provide the required spread of the resonant peak.	An adjustable core in L_1 permits the peak response to be shifted somewhat, to obtain maximum uniformity of response, in spite of manufacturing and tube tolerances. See circuit at right; circle (13).
Shunt peaking network. (14)	L_2 resonates at a frequency somewhat above 4 mc, and holds up the high-frequency end of the response. Its inductance is correspondingly smaller than that of L_1 .	L_1 and L_2 , in combination with the plate and grid-circuit capacitances form a low-pass filter network, which has a practically flat pass band up to the cut-off frequency between 4 and 5 mc. See circuit at right; circle (14).
Plate load resistor. (15)	R_7 determines the low-frequency response of the chroma amplifier, up to .5 or 1 mc.	The value of R_7 is somewhat critical, and the low-frequency response changes rapidly with change in value of R_7 . A $\pm 5\%$ tolerance is advised. See circuit at right; circle (15).
Coupling network to triode section of tube. (16)	Purpose of network is same as noted in (1).	The same performance factors apply as noted in (1).
Cathode bias and feedback network. (17)	The cathode resistor is center-tapped to provide a suitable grid bias to the triode section of the tube. The unbypassed resistor provides negative feedback in circuit.	It will be noted that the <i>ac</i> signal from the grid does <i>not</i> flow into R_8 and R_{10} , because R_8 has a high value; 1.5 megohms. Only a <i>dc</i> voltage path exists between grid and cathode. Negative feedback helps to linearize the triode. See circuit at right; circle (17).
Series peaking coil. (18)	Purpose of network is the same as noted in (3).	The same performance factors apply as noted in (3). The second stage is utilized to obtain the desired gain figure. See circuit at right; circle (18).
Load resistor and output circuit. (19)	The purpose of the network is basically the same as noted in (5). However, the load is connected directly to the series-peaking coil because the relatively large value of output capacitance makes use of series-peaking coil of small advantage.	A series-peaking coil cannot be used to advantage unless the ratio of input to output capacitances in the circuit are suitable to low-pass filter response. The output circuit is somewhat load-sensitive, particularly with respect to capacitance. The value of R_{11} shown provides flattest response for a capacitance of 10 mmfd, when looking into the probe or other device being driven. See circuit at right; circle (19).
Power-supply circuit. (10)	A small voltage-doubler power supply utilizing selenium rectifiers is used in the interest of compactness.	The value of the output voltage determines the signal swing which can be handled by the chroma amplifier. However, the upper limit is determined by the rated dissipation of the 6AN8. See circuit at right; circle (10).


‡From a field report submitted by Robert G. Middleton, Simpson Electric Company.

Signal Amplifier for COLOR-TV

by G. S. RYANT

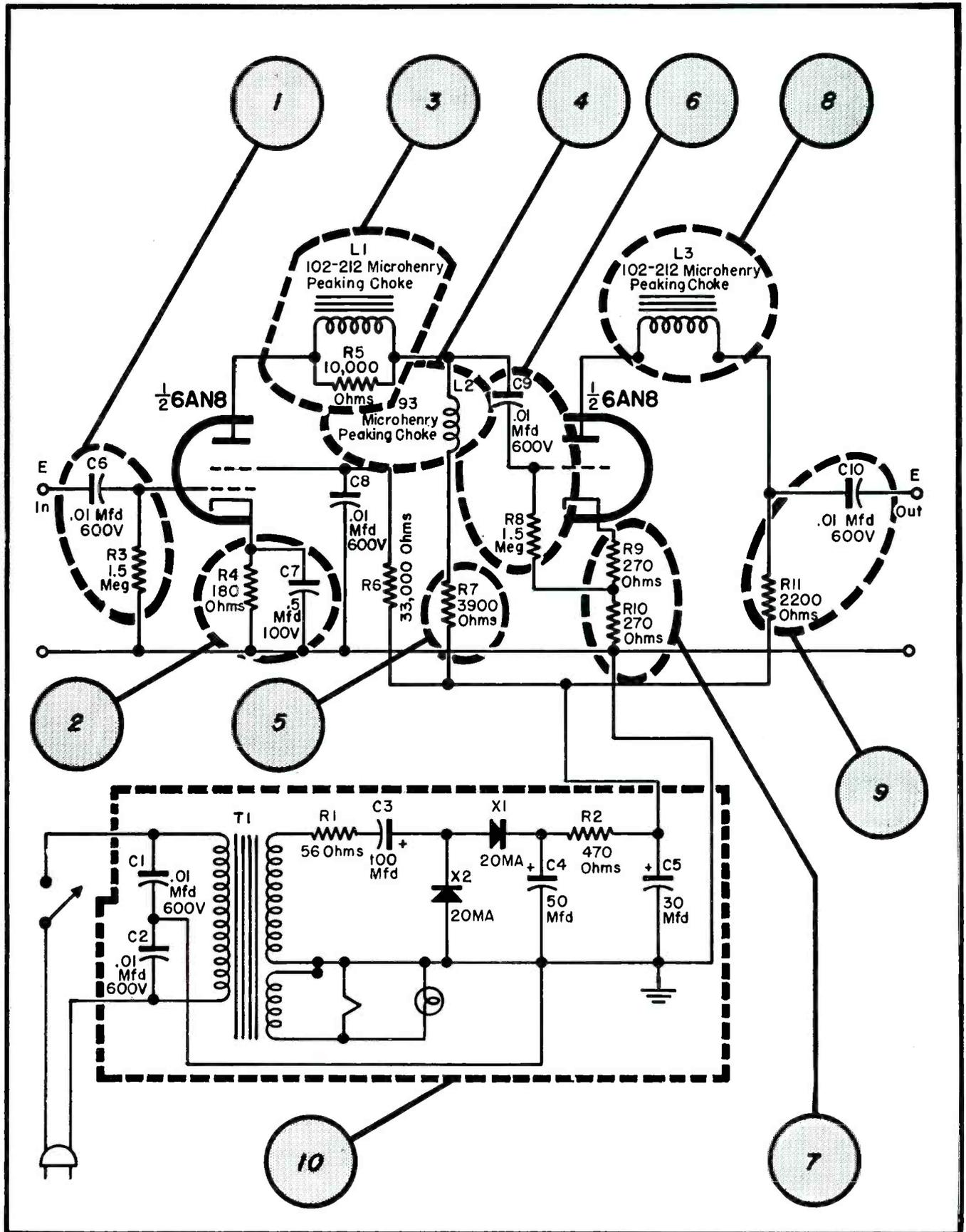

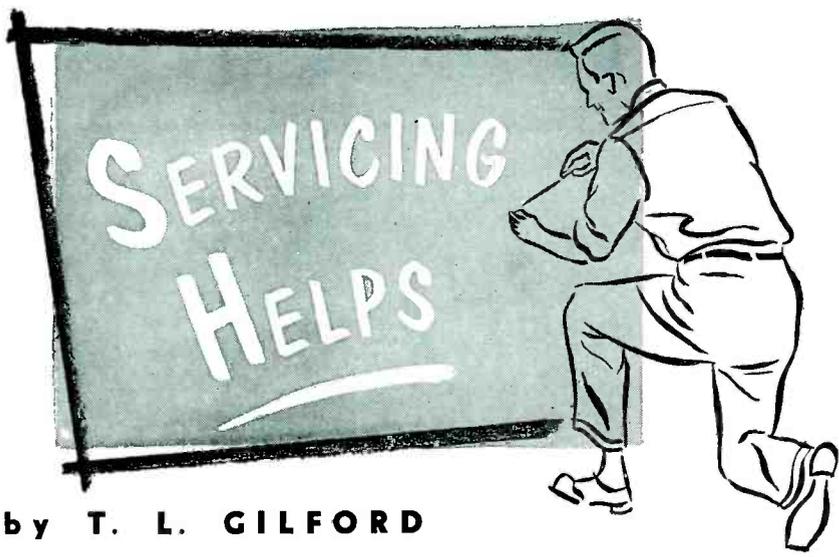Circuit of wide-band chroma amplifier used as preamp for demodulator probe and similar preamp applications. Response is flat within ± 1 db from 7.5 kc to 4 mc, and gain is approximately 35 times. When bypass and coupling capacitors are appropriately increased in value, preamp response is lowered and is flat ± 1 db from 60 cycles to 4 mc, and can be used for low-frequency work.



by T. L. GILFORD

EVER since electric headlamps were first used on autos, glare has been a problem. A beam illuminating the road far ahead for safe driving is too bright for an approaching driver. At first there were only one-beam lamps which were dimmed by switching a resistance in and out of a circuit. Later lamps were designed with two beams; an upper beam for clear road driving and a lower beam for reducing glare when approaching another car at night. Over the years headlamps have been standardized and improved in accuracy, and inspection and service facilities developed until the glare problem has become one of proper headlamp usage by the driver. However, many drivers are not willing to devote the close attention and rapid reaction required under present highway conditions.

In studying the situation it was found that it would be necessary to


develop a device that would automatically control dimming of the lower beams at a safe distance. Satisfactory sensitivity was achieved by using a multiplier phototube, which is capable of about one million times the sensitivity of standard phototubes. As sensitivity was increased, it was found that extreme variations in brightness of oncoming headlamps was not nearly as serious as anticipated, because few roads are straight and level for any great distance. However, as sensitivity was increased, other problems in the fields of optics and electricity had to be solved.

One problem encountered was the variation in the reflectivity of road surfaces. Headlamps illuminate the road ahead and the road brightness reflecting back to the driver varies from almost nothing from wet asphalt to a considerable amount from dry gravel or fresh snow. A device sensitive enough to retain the lower

beam after an approaching driver dims, would necessarily be sensitive enough to be greatly affected from road reflection, unless the downward response angle was carefully controlled. If too much light from the road were permitted to reach the phototube, the device would stay on the lower beam. At the same time, the sensitivity response angle must extend enough below horizontal so that the device will function properly under conditions of normal car loading. These problems were solved through the development of the *Autronic Eye* which employs a lens and mask system to provide a sharp lower cutoff. The cutoff is aimed as low as possible without incurring interference from road reflection. This aim is low enough to stand the upward tilting caused by normal car loading without bundle loss in sensitivity.

Most electronic devices require a moderate warmup time, and during this period they do not provide automatic control. This period of no control must be considered in design, because usually vehicles are operated in areas of opposing traffic during the warmup period and it is desirable to have a fixed lower beam until the automatic control is functioning. In the *Autronic-Eye* 10 to 15 seconds warmup time is required for the rectifier and amplifier tubes. The rectifier tube controls the high voltage to the phototube, and the amplifier tube provides the current to a sensitive relay; this relay is in the lower beam position when the amplifier tube current is off. The rectifier tube circuit has been so designed that the tube warms up ahead of the amplifier tube, so that the phototube is in control before the amplifier tube can operate the sensitive relay to the upper beam position.

Fig. 1. Modified Autronic Eye circuit, in which the hv rectifier has been eliminated. Point X illustrates wire break in system when used in Oldsmobile; new wiring is shown by dotted lines. Automatic operation is made available at headlight switch. The starred resistors, 270,000 and 180,000 ohms, also appear in the modified circuit, replacing the 1-megohm and 560,000-ohm units used originally.

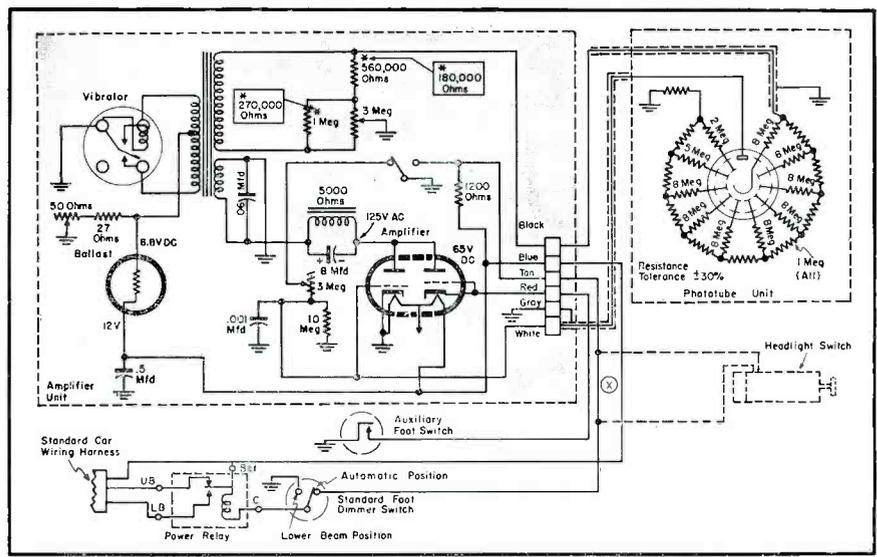

Regulating Control

Insensitivity to changes in battery voltages has also been built into the control system. Car battery voltages vary from 11 to 15 volts or $\pm 15\%$ from the midpoint. Multiplier phototubes are very sensitive to voltage changes; in fact, a 10% increase in voltage will double the output. To obtain satisfactory performance on a car, the automatic control had to be designed with voltage regulation; this has been obtained by using a current regulator (ballast tube) in the pri-

†Based on copyrighted data appearing in the *Instruction and Training Manual Guide for the Autronic Eye*, published by the *Guide Lamp Division of General Motors Corp.*

mary of the transformer. The dimming distance varies $\pm 5\%$.

Energy for the automatic control is provided by the car electrical system through the standard light switch. This voltage is applied through an *amplifier disconnect block* and the ballast tube to the primary winding of the transformer, and then through a vibrator to the ground. The transformer has two secondary windings, one producing approximately 1150 volts *ac* and the other approximately 150 volts *ac*. The higher voltage is rectified to produce approximately 1000 volts *dc* across a load resistor network.

A high voltage control is adjusted to supply the necessary voltage for the phototube unit. A sensitivity control in the phototube unit adjusts the high voltage to compensate for variations in phototubes. The voltage is applied to the various dynodes in the phototube through a voltage divider network.

The 150-v secondary winding of the transformer supplies power for the amplifier tube and the sensitive relay. In the absence of light on the phototube, the amplifier tube passes enough current through the sensitive relay to close it. Light causes the phototube to pass a current through a load resistance which develops a negative bias voltage on the amplifier tube control grid. This causes the amplifier tube to reduce the current through the sensitive relay. When the current is reduced sufficiently, the sensitive relay opens. When the sensitive relay opens, a much larger load resistance is switched into the phototube circuit and the device thus becomes about ten times as sensitive in the lower beam position as it is in the upper beam position.

The optical system of the phototube unit consists of a condensing lens which focuses light through an amber filter and through an opening in a mask to a multiplier phototube. The condensing lens is corrected for spherical aberration and focuses the light from approaching headlamps to a point in the plane of the mask.

The vertical and horizontal angles through which the device responds to light are limited by the size of the opening in the mask, and the sensitivity cuts off abruptly when the point of focused light passes the edge of the mask opening.

Modifications

In the early part of this year a few modifications were made to the original control circuit, and the schematic

Modified Circuitry for Automatic Auto-Headlight Control †

. . . Curbing 90° Deflection Problems . . . Vertical Hold Improvements

of the altered system is shown in Fig. 1.

A high-voltage rectifier was eliminated. The *ac* voltage is now connected directly to the phototube, so that when light strikes the phototube it acts as a half-wave rectifier during the negative half of the *ac* cycle. In this manner, negative *dc* voltage is still applied to the grid of the amplifier tube. A capacitor is connected between the grid and ground to reduce ripple.

Shielding Now Used

Since *ac* voltage is present in the black high-voltage lead, inductive interaction between this wire and the white wire leading to the grid of the amplifier tube would result, without proper shielding. The negative half of the *ac* cycle induced into the white wire would be great enough to apply enough negative voltage to the grid to shut off current through the section of the tube, putting the headlamps on continuous low beam regardless of the light on the phototube. To prevent this, an improved shielding system is now provided between the black and white wires.

To increase further the shielding possibilities, all circuits of the amplifier tube section return to ground in-

stead of the 12-v line. The armature of the sensitive relay is now grounded instead of being connected to the 12-v line, requiring a new power relay. One side of the coil of the new power relay is connected internally to the 12-v line or battery terminal. The other side is connected to a C terminal. Current flows through the power relay, when the C terminal is connected to ground through the *automatic* position of the standard foot dimmer switch, tan wire and to the armature of the sensitive relay, when in *open position*. Lower beam terminal of the standard foot dimmer switch is also connected to ground. When the standard foot dimmer switch is in the *lower beam* position, the terminal of the power relay is grounded, thus putting the headlamps on lower beam.

Oldsmobile now offers a *manual-automatic* control at the light switch by providing a means of breaking the tan wire. In *manual* position the tan wire is open and the terminal of the power relay cannot be grounded through the armature of the sensitive relay. In this condition the standard foot dimmer switch provides manual operation of the headlamps.

The *dim* and *hold* sensitivity adjustment procedure for the new circuit is in reverse to previous models

(Continued on page 30)

Fig. 2. TV troubleshooting guide chart featuring use of 'scope and square-wave patterns. (Courtesy RCA).

INPUT TO VIDEO AMPLIFIER	SHAPE OF OUTPUT WAVE SEEN ON SCOPE SCREEN	EFFECT ON TELEVISION PICTURE	DEFECT	CHECK THESE CIRCUIT COMPONENTS
SQUARE WAVE (ABOUT 60 CYCLES)		PICTURE NORMAL	NO DEFECTS. GOOD LOW-FREQUENCY RESPONSE AND NEGLIGIBLE PHASE SHIFT	
		GRADUAL CHANGE IN PICTURE SHADING FROM TOP TO BOTTOM OF PICTURE. (THIS EFFECT CAN BE MINIMIZED BY DC-RESTORER ACTION)	LEADING LOW-FREQUENCY PHASE SHIFT. USUALLY ACCOMPANIED BY A LOSS OF LOW-FREQUENCY GAIN.	COUPLING CAPACITORS, SCREEN AND CATHODE, BY PASS CAPACITORS, LOW-FREQUENCY COMPENSATION CIRCUITS, SCREEN AND GRID RESISTORS.
			LAGGING LOW-FREQUENCY PHASE SHIFT. USUALLY CAUSED BY OVER COMPENSATION.	
SQUARE WAVE (ABOUT 25 KC)		PICTURE NORMAL	NO DEFECTS. GOOD HIGH-FREQUENCY AND TRANSIENT RESPONSE.	
		PICTURE DETAIL IS POOR; SHARP CHANGES IN PICTURE SHADING ARE FUZZY.	POOR HIGH-FREQUENCY RESPONSE	PEAKING COILS, LOAD RESISTORS, LEAD DRESS OF PEAKING COILS AND COUPLING NETWORKS.
		FINE VERTICAL BLACK AND WHITE STRIATIONS FOLLOWING A SHARP CHANGE IN PICTURE SHADING.	EXCESSIVE HIGH-FREQUENCY RESPONSE AND NON-LINEAR TIME DELAY; ALSO HIGH-FREQUENCY CUTOFF MAY BE TOO SHARP.	PEAKING COILS, LOAD RESISTORS, DAMPING RESISTORS SHUNTING PEAKING COILS, LEAD DRESS.
		WHITE BORDER FOLLOWING A BLACK-TO-WHITE TRANSITION; BLACK BORDER FOLLOWING A WHITE-TO-BLACK TRANSITION.	EXCESSIVE OR NOT ENOUGH MID-FREQUENCY RESPONSE AND NON-LINEAR TIME DELAY.	PEAKING COILS, LOAD RESISTORS, DAMPING RESISTORS SHUNTING PEAKING COILS, LEAD DRESS.

OHMITE® REPLACEMENTS

WON'T boomerang
into call backs




NEW OHMITE FUSE RESISTOR

FOR REPLACEMENT IN ALL
TELEVISION RECEIVERS

The FR-7.5 Fuse Resistor is provided with 1½" tinned wire leads for easy installation directly in the circuit. Can also be soldered to the plug-in terminal strip which is provided.



7.5 OHMS

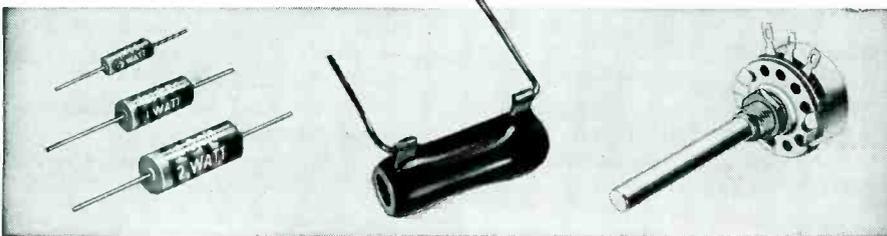

Little Devil® COMPOSITION RESISTORS

Tiny, yes . . . but what dependability, ruggedness, and stability! Rated at 70C rather than 40C. Completely sealed and insulated by molded plastic, they meet all MIL-R-11A requirements. Little Devils are available in ½, 1, and 2-watt sizes in all standard RETMA values.

BROWN DEVIL® AND DIVIDOHM® RESISTORS

Brown Devil fixed resistors and Dividohm adjustable resistors are favorite vitreous-enamelled units! Resistance wire is welded to terminals. Brown Devils are available in 5, 10, and 20-watt sizes; Dividohm and fixed resistors in 10 to 200 watts.

TYPE AB NOISE-FREE POTENTIOMETERS

Because the resistance material in these units is solid-molded—not sprayed or painted on—continued use has practically no effect on the resistance. Often, the noise-level decreases with use. They give exceptionally long service. Rated at 2-watts.

Servicing Helps

(Continued from page 29)

which had a fixed *dim* grid resistance at the grid of the amplifier tube, with the *hold* resistance variable. The modified *hold* resistance is a fixed 10-megohm resistor, while *dim* resistance is varied by a *dim* control connected in parallel with the resistor in the *closed position* of the sensitive relay. The *hold* must be adjusted first and can be adjusted only by the potentiometer which adjusts the high voltage applied to the phototube. This potentiometer is called the *hold control*. After *hold* is adjusted the *dim* may be adjusted by the *dim control*.

Shortly after production started on 1955 models a minor change was made in the amplifier wiring circuit. The 47-ohm, 2-watt filament resistor was removed from the section-one filament (pin 5) of the amplifier tube. The section-two filament (pin 4) of the amplifier tube, was disconnected from the regulated 6.8-v line, and the ground connection removed from the filament center tap (pin 9).

The two filaments have been connected in series across the 12-v line. The two resistors have been changed to 270,000 and 180,000 ohms, 2 watts.

90° Linearity Adjustments¹

ADJUSTMENT of picture size and linearity, require close control of horizontal drive, width and linearity. These adjustments affect not only horizontal linearity, but *vertical linearity*. *B-boost* voltage, a product of the horizontal flyback circuit, is the supply voltage for the vertical oscillator.

Faulty horizontal adjustment can cause excessive current in the horizontal output tube, resulting in fuse burnout, early tube failure and component failure in the horizontal output circuit.

In adjusting these controls the width core should be placed at the maximum counterclockwise position. Then the horizontal drive trimmer should be moved counterclockwise two turns from tight position, or until an overdrive line appears; then clockwise until it just disappears.

A 0-500 *ma* meter should then be inserted in place of the high-voltage fuse and the horizontal-linearity control adjusted for minimum indication on the meter. After this the horizontal drive trimmer should be readjusted once more. The width core should then be adjusted so that it slightly overscans the picture area. If an over-

¹Based on notes from RCA Service Co.

GET THEM FROM YOUR
ELECTRONIC PARTS
DISTRIBUTOR

Write for
Stock Catalog
No. 24



OHMITE MANUFACTURING CO.
3642 Howard St., Skokie, Ill.
(Suburb of Chicago)

Be Right with
OHMITE®
DEPENDABLE RESISTANCE UNITS

drive line appears the drive should be decreased.

In models without a horizontal-linearity coil the width core should be placed at the maximum counterclockwise position, and the driver trimmer turned counterclockwise two turns from tight or until just before the overdrive line appears. The width core should then be adjusted for sufficient width to overscan slightly the picture area, and the drive trimmer adjustment repeated.


Since these adjustments may have an effect on other controls, the vertical height and linearity, and centering adjustments, and position of the ion trap should be checked after horizontal setup.

As an alternate method of obtaining minimum current in the horizontal-output tube, a pilot lamp may be inserted in the plate lead of the tube. This can be done at the point where the plate lead is connected to the cap on top of the tube. A number 45 or 44 pilot lamp, connected in this manner, will light up and become bright when the current is maximum, or dim when the current is minimum. If the light becomes dim at two settings of the linearity control, the one indicating minimum current should be chosen.

Vertical Hold Control Improvement

DUE TO RESISTOR TOLERANCES in the vertical circuitry of Stromberg-Carlson X 21-22 sets, it has been noted that the vertical controls in some receivers had a tendency to move electrically near one end of the control. A production change has been made to remedy this condition; effective with serial number T48914. Resistor R_{222} (820,000 ohms/½ w) has been changed to 1 megohm/½ w.

REPLACEMENT SPEAKERS

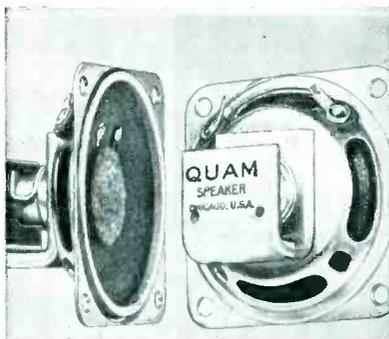

Two and one-half inch replacement-improvement speaker for personal portable radios, intercom equipment and other applications. Speaker is 1¼" deep. Maximum input is 2 watts. Has .65 ounce alnico V magnet and four mounting holes on rim. Voice coil impedance is 3.2 ohms. (Model 25A07; Quam-Nichols Co., Chicago, Ill.)

**Radio-TV
and
Electronic
Dealers**

**make more sales-
more money
with GENERAL
BATTERIES**

MORE PROFIT-OPPORTUNITIES

WITH THE COMPLETE LINE OF MERCURY BATTERIES

General Mercury Batteries are surge-welded for whisper-quiet service . . . give greater satisfaction to users . . . result in more sales, more money for you!

SIX-TWENTY-FIVE . . . 1.3 VOLTS. Smaller than a dime. World's most powerful miniature, commercial battery.

RG-1 . . . 1.3 VOLTS. Powerful, long-lived service for whisper-quiet operation.

B-1 . . . 2.6 VOLTS. Two RG-1 cells for use where low resistance is a must.

B-2 . . . 2.6 VOLTS. Three cells high (one is a dummy). Lower voltage to cut down output power.

B-3 . . . 3.9 VOLTS. Three cells high and 3-cell voltage. Full power output without noise.

B-4 . . . 1.3 VOLTS. Two cells in parallel. Gives twice the service life of the RG-1.

NOTE: You will want the new 3RG3, 4 volt mercury pack for semi-transistor portable radios. Order today from your distributor or write direct to the factory for details.



RADIO AND INDUSTRIAL TYPES OF DRY BATTERIES

A complete line for all current radio sets and industrial testing equipment.

General is a dependable source for all sizes and types of mercury and dry batteries for all purposes. Put in your order now!



General

DRY BATTERIES, INCORPORATED

13000 ATHENS AVE., CLEVELAND 7, OHIO, BOulevard 2-0030

The NCTA Western Regional Conference

TAKING THEIR cue from the first National Community TV Association Western regional meeting, held last fall in San Francisco, planners of the second annual conference and exhibition at Colorado Springs have arranged two days of sessions¹ where informal open forum discussion will be the rule.

Among the discussion topics scheduled to generate lively *give and take* at the conference sessions is the challenging subject of illegal-radiator operation, particularly in the Pacific Northwest where controversial satellites and boosters have been most active in recent months. NCTA spokesmen at the meeting will spell out the competitive advantages of community television, operating entirely within the framework of legal regulations, as the most practical and economical means of bringing quality reception and program choice to walled-in areas.

The use of common carrier microwave relay facilities will be explored as an increasingly widespread means of making TV available to those operating, in many cases, far from signal sources. *Closed circuit* operation, in which a cable company may lease an otherwise unused channel of its system to another firm interested in local program origination, will also come in for its share of attention. Such service is being contemplated by com-

¹Tuesday and Wednesday, October 25 and 26; Antlers Hotel, Colorado Springs, Colorado. Equipment will be on view in the General Palmer Room.

munity operators whose systems serve those towns and cities where there is no outlet for local TV, and no apparent prospect for TV broadcasting activity to fill such a need. In this instance the program-originating company would specialize in catering to local needs and interests, without diminishing the amount of *outside* program fare being distributed to subscribers of the cable company.

Representatives of community-TV equipment manufacturers will deal with such technical posers as radiation measurement and control, while other sessions will be devoted to business aspects of the industry.

George J. Barco² will serve as moderator of a discussion based on the new NCTA-sponsored code of business ethics for community-TV operators. Other aspects of business to be discussed will include recommended advertising and promotion efforts aimed at expanding cable service to new subscribers.

Legal aspects of the community television industry will be reviewed by E. Stratford Smith, NCTA executive secretary as well as the association's general counsel.

All sessions of the first day's conference will be presided over by

²Meadville Master Antenna, Meadville, Pa.

³Pottsville Trans-Video Corp.

⁴Community TV System of Wyoming.

NCTA president Martin Malarkey,³ Bill Daniels,⁴ NCTA vice prexy, will preside over the concluding sessions.

The problems of *preventive maintenance*, of such intense interest at the annual meeting in New York, will receive additional coverage at the western session. Up for discussion will be a number of the points stressed by Caywood Cooley.

At the New York meeting, it was noted that three basic measurements on amplitude distortion, signal-to-noise ratio, and picture resolution should be established in a p-m program, and then one can proceed toward the system extremities beginning at the antenna site. The objective in such a check would be to locate any obvious sources of troubles, eliminating these, so that the first measurements at the system extremities would be indicative of those we could expect on a properly operating system. As we proceed, it was brought out, it would then be desirable to record and log all input and output levels; such a step serves to measure the attenuation of all cables and the associated accessories. All feeder line inputs and termination voltages should also be measured. These measurements would provide a guide on troubleshooting required, if and when, such a move becomes necessary.

A tube-maintenance program, also proposed by Cooley, will be examined further at the western meeting.

Officers and members of the board of the National Community Television Association, left to right: Bill Daniels, NCTA vice prexy; Glenn H. Flinn; Fred J. Stevenson, Martin F. Malarkey, prexy of the association; George J. Barco; A. J. Malin; W. Randolph Tucker, and Ned W. Cogswell.



BIG NEWS!

Now Available in

ALUMINUM COATED STEEL

Alprodco's

NEW CUSTOM TELESCOPING SLIP-UP MAST
and **NEW** 10-FOOT CUSTOM TV MASTS

NOW—through a revolutionary new process that bonds aluminum to steel—ALPRODCO is able to offer you the finest TV masts ever put on the market!

The new masts are made from ALPRODCO'S famous temper-proof, high-carbon content alloy which has been hot-dipped in aluminum. The finished product combines the strength and rigidity of steel with the lasting beauty and corrosion resistance of aluminum.

Tests show ALPRODCO'S new Aluminum coated steel masts have




3 times the life
of galvanized steel—

Cost Approximately
10% More!

ALUMINUM-DIPPED 10-FOOT MASTS

Featuring:

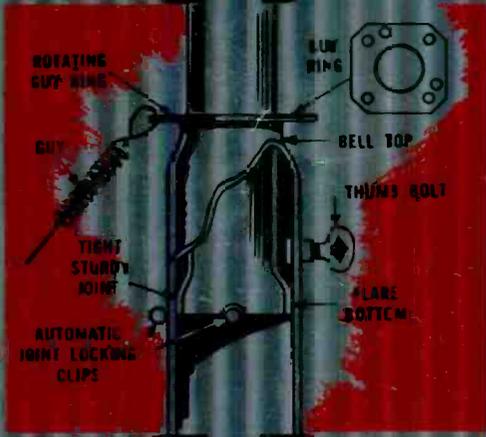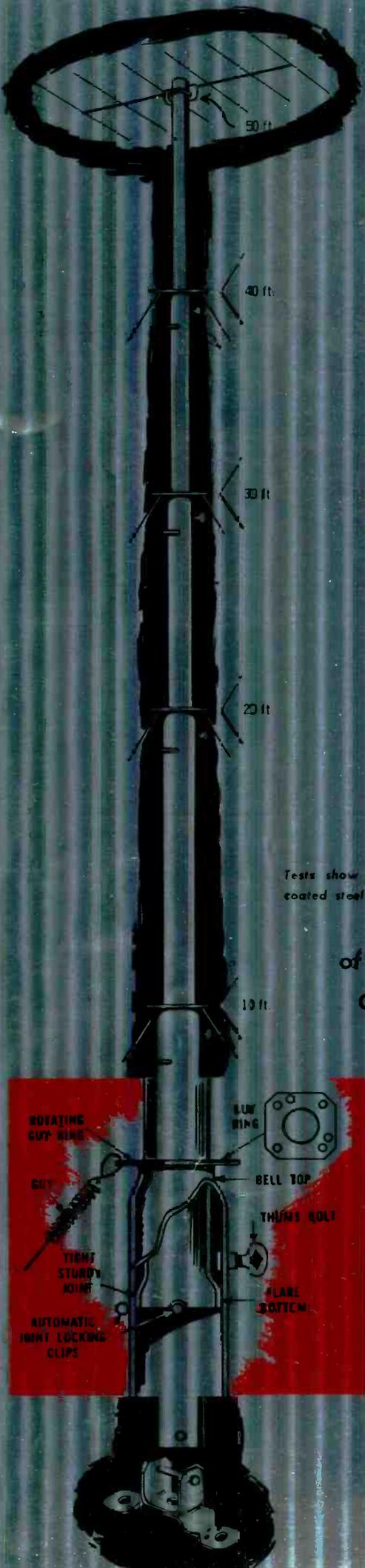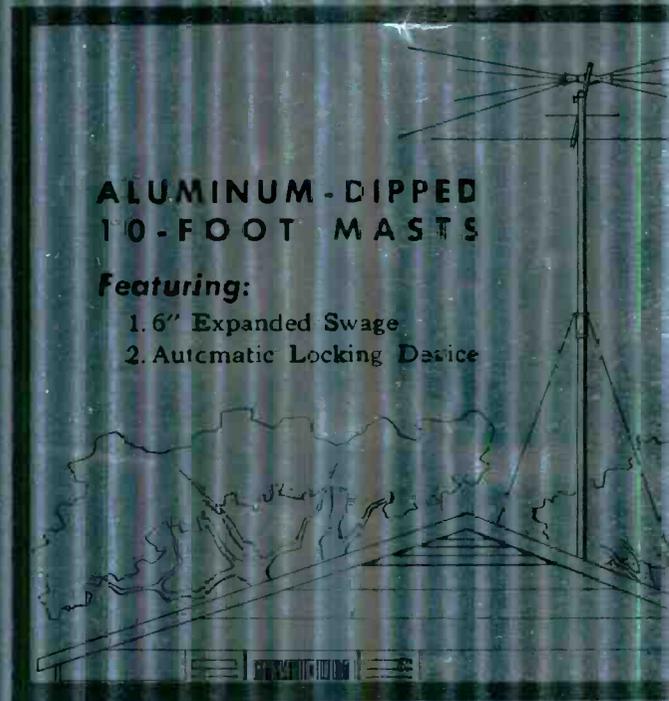- 1. 6" Expanded Swage
- 2. Automatic Locking Device



Alprodco

The nation's largest producers of telescoping slip-up masts

**MORE
BIG
NEWS!**

Automatic
Positive
Locking
Device

6-Inch
Expanded
Swage for
Strength

Same Tempered
Hot Dipped
Galvanized Steel


Alprodco's
10' CUSTOM TV MASTS

M-10-15 Heavy Weight

M-10-17 Utility Weight

Available From Your

Authorized **Alprodco** Distributor

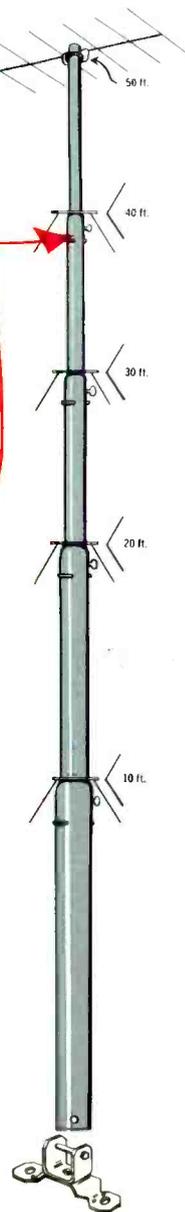

Service Engineering

field and shop notes

by **ALBERT R. SINCLAIR**

Communication Engineer, General Electric Company

IT WASN'T TOO long ago when only hams used frequencies above 100 megacycles. Tubes wouldn't oscillate in this region, amplifier efficiencies were low and many other drawbacks prevented commercial use of these frequencies. However, the development of new types of *vhf* tubes and circuits have solved a number of these problems. And today we have 2-way commercial *vhf* gear that is not only extremely reliable, but not too difficult to maintain and service. Of course, servicing *vhf* communications equipment may not be as easy as radio and TV repair, but the assignment is easier to handle now than it was in the past.

The *vhf* receivers used in 2-way systems are very unique. There has been a trend since '46 to provide more selectivity, instead of more sensitivity.

In addition, fixed receivers have been designed so that they are interchangeable with the mobile unit. This makes it unnecessary to stock a special spare for large or small systems. Also, it is now possible to change from wide band to narrow band operation when the FCC so directs. And

the current type receiver does not receive adjacent or neighboring channel signals nor can it be desensitized by them. Receivers also have *if* and *rf* transformers that are very stable. A receiver that incorporates these features is illustrated in Fig. 1.

Tuned Circuit Front End

Neighboring signal troubles have been solved by using a front end (*rf* amplifiers and high *if* stages) with tuned circuits where they do the most good. In the receiver diagrammed there are two tuned circuits before the first *rf* grid and three between the *rf* amplifier and the mixer. These tuned circuits have very high *Q* and have been designed to minimize the desensitization from nearby channels. Another advantage of high-*Q* tuned circuits at this particular point is that intermodulation is minimized in the front end. Earlier, in these reports, intermodulation was described as the mixing of two signals to form the third. This mixing takes place in a non-linear circuit such as an *rf* amplifier. So if we can reject as much of the first two signals, then

very little intermodulation will be present.

A comparison of the selectivity that obtains in the new models and those made in '54 is shown in Fig. 2 (p. 36); the curve is for the antenna transformer as compared to cavity resonators. In the high band set of curves, at ± 2 mc using the '54 approach, it will be noted that the selectivity is only down .2 db, while the '55 design affords an increase of approximately 17 db or over 7 times that of typical '54 receivers. Two *rf* stages have been used in the past, primarily to obtain high image response ratios, rather than for gain requirements. In the new receivers this is not necessary, due to new antenna circuits. The gain is more than sufficient to override first converter noise and the selectivity provides better than 100 db image rejection. Delayed *agc* has been used to reduce intermodulation. This has been accomplished by biasing the tube so that it will operate on the linear portion of its $E_p I_p$ curve. The *agc* is delayed so that full *rf* gain is available for reception of threshold signals.

The receiver features the use of a multiplier in the first conversion oscillator, which is unusual. By using a fundamental crystal in the 12-mc range, instead of one which operates on a mode, it has been found possible to obtain better stability with ample rubbering (ability to vary the crystal frequency). The oscillator output is multiplied three times four, twelve times in all, to reach the injection frequency.


A high intermediate - frequency amplifier has been incorporated; it is tuned to 8.7-mc. It consists of a four coil transformer, a 6BH6, and a two-coil transformer, coupling the output into the second converter. The combination of selectivity and the right amount of gain in the front end makes it extremely difficult for off-channel signals to desensitize the second converter.

Low IF Amplifier

The receiver employs two stages of *if* amplification at 290 kc. Most of the gain and selectivity is built into the low *if*'s. A six-coil transformer is utilized to obtain most of the selectivity. Inasmuch as each circuit in the six-coil transformer is tuned to center frequency, each coil is resistive at resonance and loads the adjacent tuned circuits. This loading provides the broad response needed

(Continued on page 36)

Fig. 1. Block diagram of G.E. Progress receiver designed for 2-way installations.

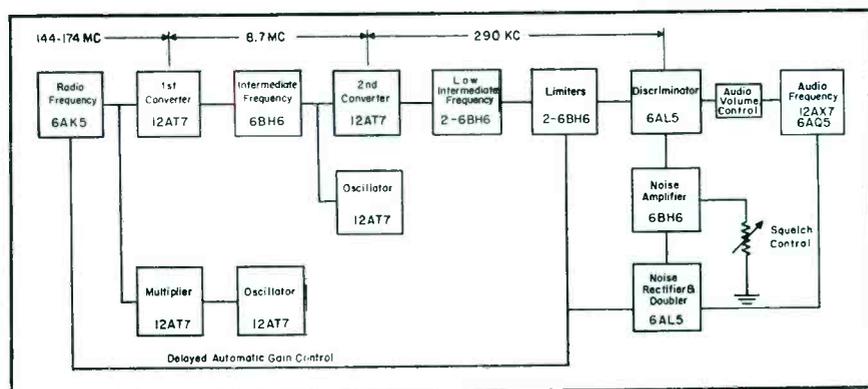

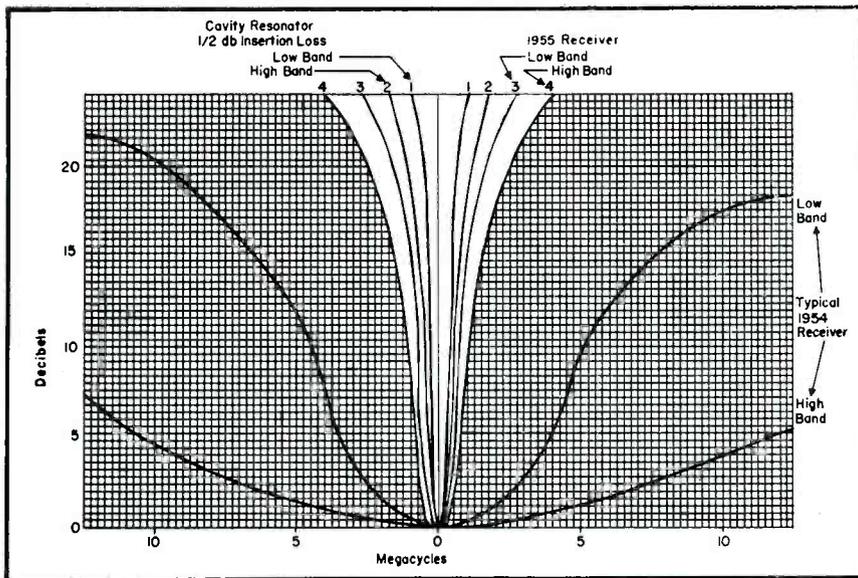


Fig. 2. Comparison of selectivity offered by 2-way system receivers designed in '54 and '55. Curve illustrates results achieved with antenna transformer and cavity resonator.

on the nose of the selectivity curve for full pass-band at threshold signal levels. At frequencies other than center frequency the circuits are reactive and present a low-impedance path, thus effectively bypassing them. This action provides a nearly perpendicular selectivity curve that is needed to operate on local-area adjacent channels. One might conclude that it is difficult to align a six-coil transformer; actually it is not. All that is needed is a stable generator and an *ac vtvm*. The procedure would be to place the voltmeter on the plate of the *if* amplifier and apply an on-frequency signal into the receiver.

In the alignment process (Fig. 2a), we short out coil 2 and peak 1 for maximum reading, remove the short on 2 and short 3, and tune 2 for a dip in the voltmeter. Next, we remove the short on 3 and short 4 and tune 3 for a peak in the voltmeter. In the following step 5 is shorted and the short on 4 is removed and we tune for a dip. This procedure is continued until all coils have been tuned. The voltmeter used in this alignment procedure must have a low input capaci-

ty or it will detune the first plate coil. The bandwidth of the amplifier is determined by the spacing between the tuned circuits. This coupling can be either set in the factory or in the field to give a narrow or a wide band type of operation. The coupling can be varied by the mounting holes in the transformer identified by *N* for narrow and *W* for wide.

The terminology *narrow* and *wide* band is derived from the move that will provide more spectrum space by splitting the width of the present channels. At present the high band (152-174 mc) channel is 60-kc wide; in the future it may either be 30, 20 or 15-kc. This high band model has been designed with this change in mind. The one six-coil transformer can be adjusted to give good adjacent channel performance on 30-kc channels, but should the split be to 20 or 15, or should one still desire more selectivity, then a second six-coil transformer can be added in the holes provided, following the second low *if* tube. The method of varying the selectivity by changing the coup-

ling will mean less headaches for the service engineer. The 290-kc amplifier exhibits higher selectivity, as compared to a 455-kc amplifier of equal quality, using the same number of tuned circuits (12). In the six-coil *if* transformer each pair of coils is individually shielded from the others within the enclosing structure. This insures a minimum of mutual coupling, thereby increasing the *Q* of each circuit.

Other important features are precise temperature compensation and mechanical stability of the coils. Any coil will change its inductance when subjected to temperature variations, but it can be compensated by the use of temperature-compensated capacitors, provided the inductance retraces its temperature versus inductance curve *exactly*. The coils in this receiver will retrace accurately due to special treatment in manufacture. This feature permits the use of shields over the *if* transformers to prevent the temptation of unauthorized personnel from retuning these transformers. The tuning range of the *if* coils is sufficient to permit retuning for split-channel operation without having to replace either the first or the second oscillator crystal.

The squelch circuit in *vhf* receivers must be capable of allowing weak signals to be received without clipping them, or distorting the audio, yet it must be capable of good sharp cutoff after the carrier is removed. To accomplish this the voltages are balanced against one another in a see-saw fashion. The noise that is inherently present in all high gain stages is used; it is amplified and fed to a rectifier doubler circuit. Positive voltage from the rectifier is used to drive a *dc* amplifier. This amplifier cuts the first audio stage off, when the positive voltage is present. When a weak carrier (which is the worst condition for squelch circuits) is present, the first limiter grid conducts, developing a negative bias across its

(Continued on page 52)

(Below)

Fig. 2a. Simplified schematic of 290-kc *if* amp, illustrating steps required to align six-coil transformers.

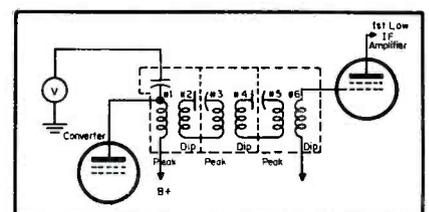


Table 1. Vhf receiver troubleshooting chart, detailing symptoms and checks.

Symptom	Check
Squelch will not open manually.	<ol style="list-style-type: none"> 1) One should test to see if the second limiter current is normal; it should not be lower than minimum established value. If so, tubes should be replaced to bring up to normal. 2) The 6AL5 rectifier should be removed. Noise should be present in speaker. If not, it will be necessary to replace the 12AX7 <i>dc</i> amplifier and audio.
Cannot squelch receiver.	<ol style="list-style-type: none"> 1) The 6BH6 noise amplifier or 6AL5 rectifier, whichever is bad, should be replaced.

INTRODUCING THE

New **GEOMATIC** TV ANTENNAS

(pat. pend.)

BY **FINCO**®

with exclusive **Fidelity Phasing***


* Dictionary: the highest degree of accuracy in the reproduction of a signal




Model B-1
Metropolitan
and Suburban




Model B-2
Suburban and
Semi-Fringe Area

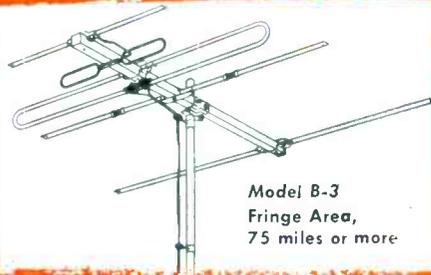

Model B-3
Fringe Area,
75 miles or more

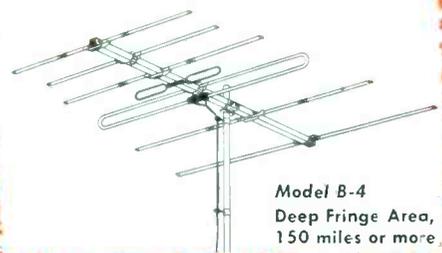

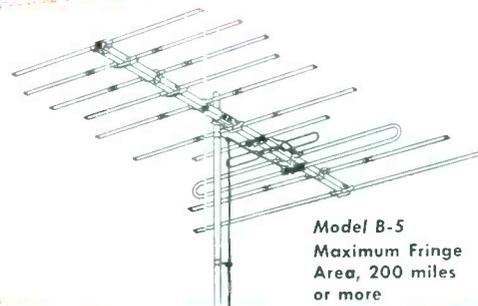Model B-4
Deep Fringe Area,
150 miles or more



Model B-5
Maximum Fringe
Area, 200 miles
or more

GEOMATIC means customized for your locality

Now For The First Time —

Regardless of channels, distance from station, or terrain FINCO can deliver a model that is perfectly suited for your area — at no extra cost!

Write, wire or phone
The FINNEY Company

Henderson 2-2150 4612 ST. CLAIR AVENUE
CLEVELAND 3, OHIO

Dept. 5105

Copyright, 1955
The Finney Company

21-Inch ATR Wide-Band 41-Mc B-W TV Receiver

by ROBERT D. WENGENROTH



See Pages 40 and 41 for Complete Schematic of TV Chassis

THE TREND toward improved picture fidelity through the use of aluminized picture tubes has prompted the development of a new family of circuitry improvements, involving 41-mc wide-band *if*, cascode tuners, high-gain video amplifiers, and precision interlace. The schematic of a receiver with such circuit features is shown in Fig. 1; pages 40 and 41.

In this chassis, we have a four-stage intermediate frequency amplifier with a design bandwidth of 3.9 mc, and a video carrier frequency of 45.75 mc. The first stage employs a 6AU6 (V_8); the next three are 6CB6s (V_9 , V_{10} , and V_{11}). Improved bandwidth is attained through the use of six transformers with three traps. Four of the transformers utilize tube

and wiring capacities for resonance; between the first and second stages the coupling is a complex network including two shunting traps and two series arms. All are slug tuned. Gain is maintained for the required bandwidth, and in addition, relative phase shifts for frequencies through the band are controlled to provide an overshoot-free picture.

4.5-Mc Trap Circuit

The output from the second detector, an IN60, includes the video signal with the sync negative, and the aural signal at 4.5 mc. The video load of the detector is a series-shunt-series peaked circuit providing the highest possible video load impedance to the detector. A series-resonant circuit serves as a 4.5-mc trap to the video signal, by transferring the sound energy to the sound *if* amplifier.

The Video Amp


The video amplifier, a 12BY7 (V_{12}) amplifies and inverts the video signal, and provides contrast control. (This tube has a transconductance of 12,000 micromhos, with a video load impedance of 3300 ohms, and gain of 40.) The circuit is a conventional series-peaked video amplifier with a 4.5-mc trap to eliminate the last traces of the sound carrier. The amplified video signal is applied to the cathode of an aluminized picture tube, 21AMP4A.

The picture tube operates at 18 kv and utilizes *pm* focus. The brightness control, in the grid circuit, includes a section of the power switch so that the spot on the screen is


extinguished when the set is turned off.

A second amplifier parallels the video amplifier. Its purpose is to provide amplification of the *dc* component of the video signal and the synchronizing signal. In this way no *dc* restorer is required, while the main video amplifier is available for contrast control; thus improved picture quality results. Because of the larger plate-load resistor and the lack of peaking, this amplifier has high gain in the lower frequency range where the synchronizing information exists, while short noise pulses are given much less amplification. The tube used is a 6AU6 (V_{13}) biased by the output of the detector. An unby-

(Continued on page 40)

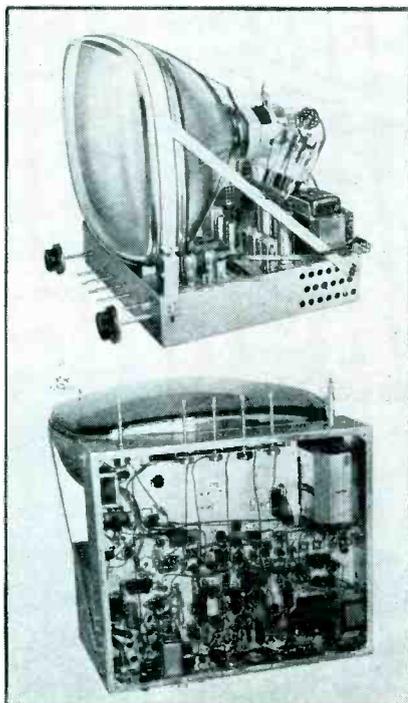

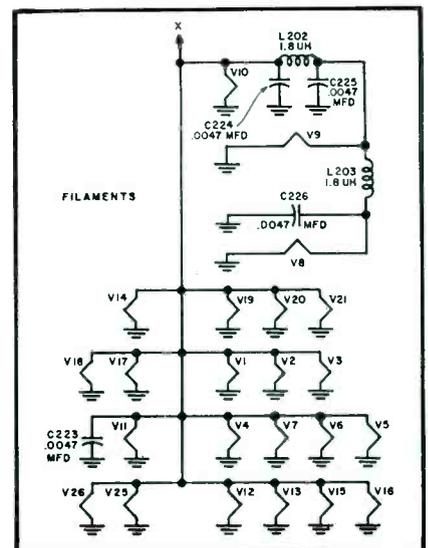(Left)
Top and underside views of ATR chassis.
(Below)
Filament circuitry of ATR TV chassis 2600; see pages 40 and 41 for complete diagram of set.




†American Television and Radio Co., model 2600.

She: *But, how do I know this is a good tube?*

You: *Because, this is a CBS aluminized Mirror-Back picture tube. There aren't any better.*

She: *And I see it has the Good Housekeeping Guaranty Seal, too. That's proof enough for me.*

Customer confidence really counts when it comes to the big tube. That's when CBS tube advertising helps you most. For CBS tubes have the Good Housekeeping Guaranty Seal and are nationally advertised to 76.9% of your customers . . . the women of America. And 53% of these women are influenced in their purchases by that seal of approval. You protect yourself and gain your customer's good will when you install a new CBS aluminized Mirror-Back picture tube.

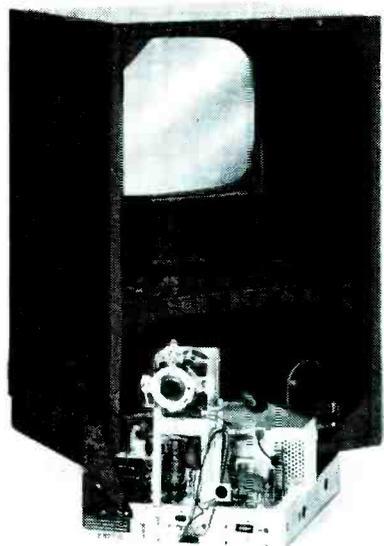

Show her the CBS carton with the Good Housekeeping Guaranty Seal.



CBS-HYTRON, Danvers, Massachusetts . . . A DIVISION OF COLUMBIA BROADCASTING SYSTEM, INC.


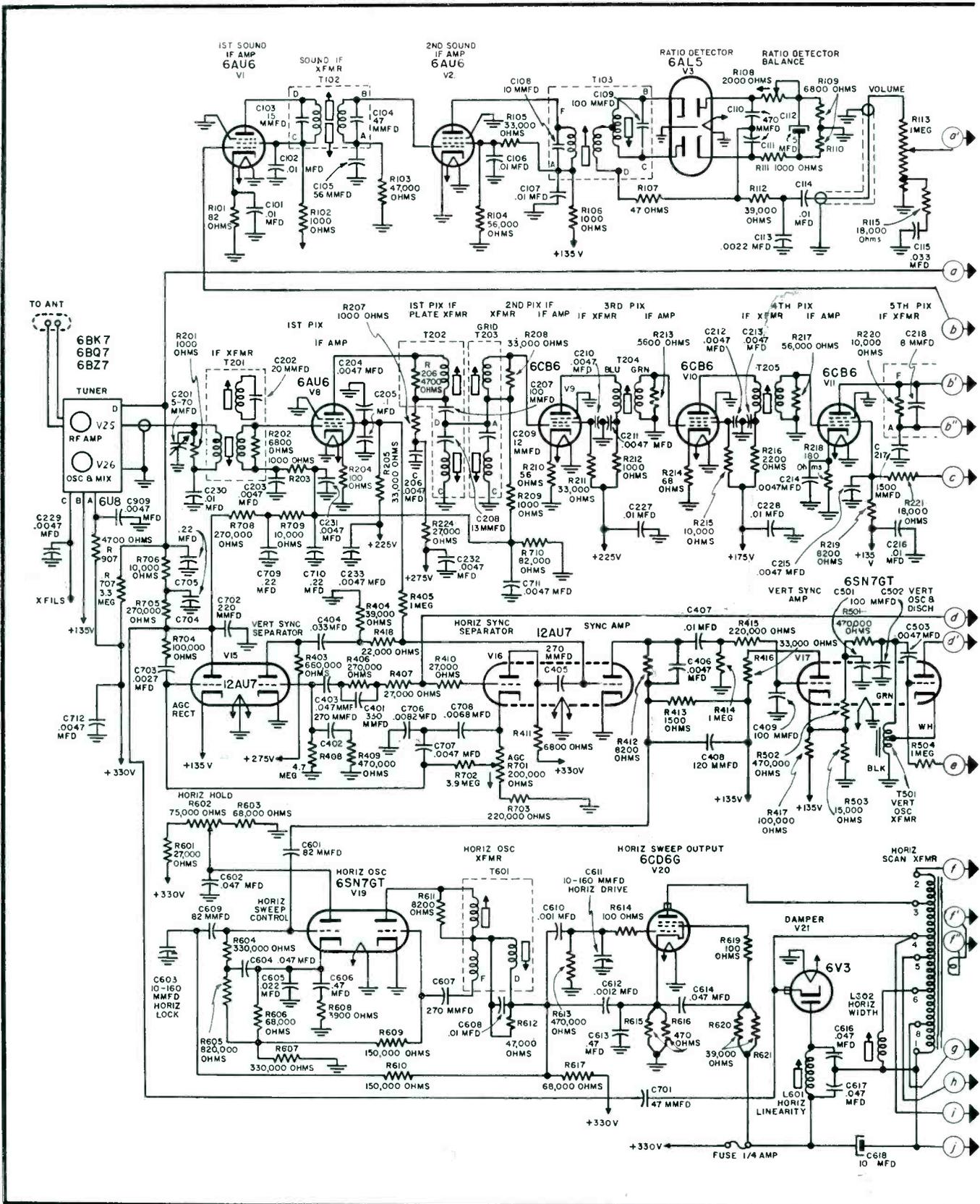


Fig. 1. Schematic of the ATR 41-mc wide-band chassis (model 2600) which features high-gain video amps. In chassis now being

passed cathode resistor provides both non-signal bias and gain stabilization. The outputs from a pair of sync separators are recombined at the grid of the second half of a 12AU7 (V₁₅). This tube section is a sync amplifier, and provides a high-level

sync pulse to the vertical sync amplifier, to the horizontal sweep control tube, and to the *agc* circuit. Its grid is biased through a 1-megohm resistor from the screen of the first picture *if* amplifier. It should be noted that this

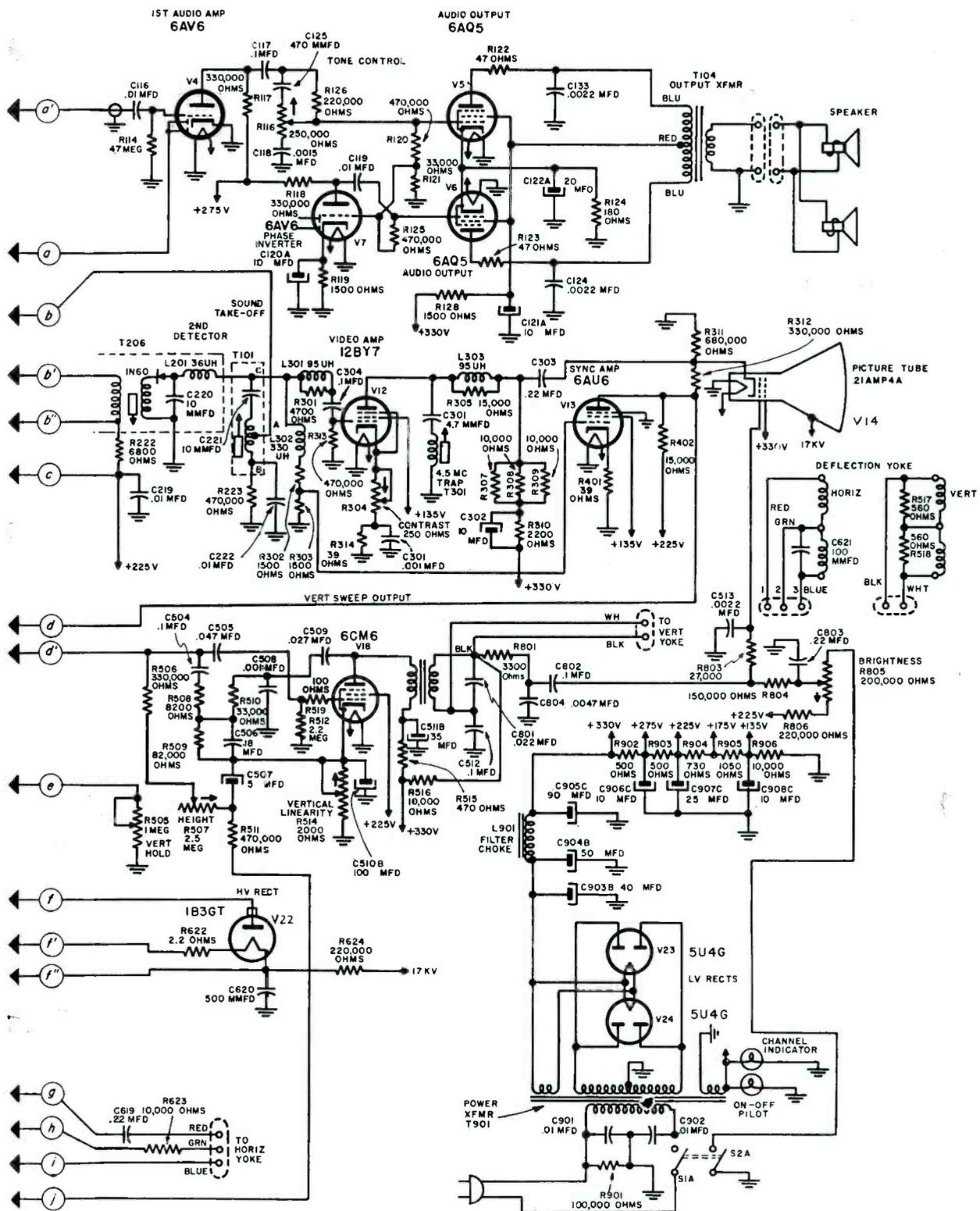is only a bias lead to the sync amplifier, not a signal lead back to the *if* amplifier. The positive-bias return holds the tube in a heavily-conducting condition, until a sync pulse occurs. This provides a maximum gain



made, the high voltage for the picture tube is 18 kv, and there is a 1-mfd capacitor in series with the voice coil of the hf speaker.

and amplitude range for sync pulses.

The sync pulses were recombined to attain a fast rise on the vertical sync pulse at the time of each horizontal sync pulse. In this way the vertical oscillator can actually be trig-

gered by a horizontal pulse gated into the vertical oscillator circuit by the vertical sync pulse. The result is precision interlace.

The vertical sync amplifier and the vertical oscillator and discharge tube

are the two halves of a 6SN7GT, V₁₇. The vertical sync amplifier is a cathode follower, with a two-stage integrating network, coupling it to the grid of the vertical oscillator. The vertical oscillator is a blocking oscil-

(Continued on page 57)

AUDIO Maintenance- Service Tips

by F. R. SAILES

Operational Characteristics of PHONO and TAPE MOTORS (Shaded-Pole Induction . . . Universal . . . Sync and Torque) and Their Maintenance and Repair


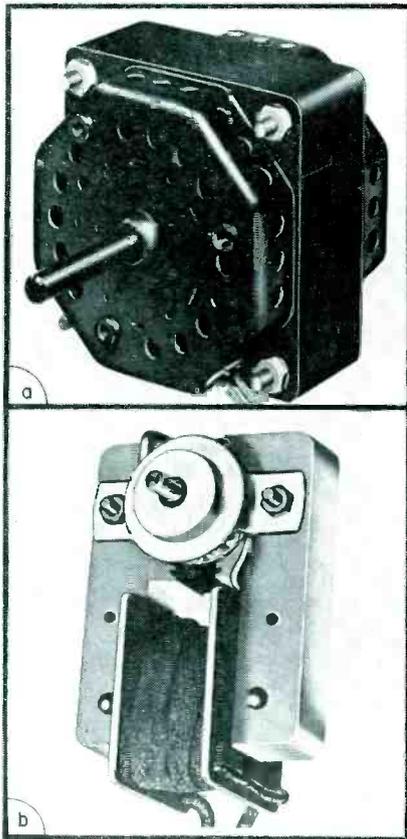


Fig. 1. Typical shaded-pole induction motors. A two-pole induction type is shown in (a); a four-pole induction model in (b). (Courtesy Alliance Mfg. Co.)

Figs. 2 and 3. A rim-drive three speed turntable is shown in Fig. 2. The proper pulley is positioned against the idler by the turret plate which is shifted by the lever protruding from under the turntable. Fig. 3 illustrates a rim-drive three-speed turntable utilizing a stepped-diameter motor shaft. The idler is moved vertically to engage the proper diameter step on the shaft. Note the wide rim on the turntable. (Courtesy General Industries Co.)

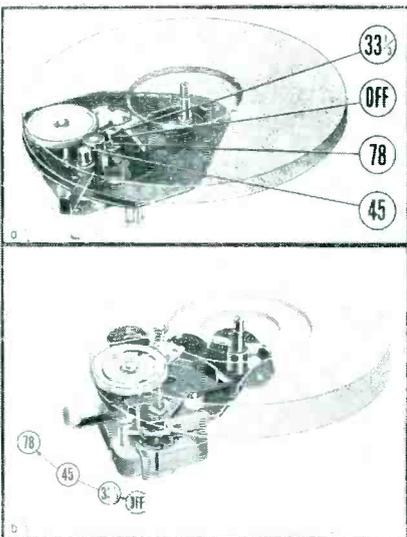

Motors play a vital role in phono and tape machines, and their installation or maintenance and repair require a thorough familiarity with the assorted types that are used, plus skilled handling of the units on the job.

Four basic types of motors are used for record players or tape recorders; shaded-pole induction, universal, synchronous and torque. The shaded-pole induction motors are the most common for record players, while sync and torque motors are often used on tape recorders.

Operating Principles


The shaded-pole induction motor employs a copper strap around part of each pole to produce a field which rotates; the rotor is a squirrel-cage affair which has current induced in it by the moving field. This induced current supplies the magnetization which makes the rotor move. So that rotor current will be induced, torque must be supplied; this is accomplished by seeing to it that the rotor rotates at a speed slower than the rotating field. Therefore an induction motor runs at less than synchronous speed. Typically, the speed is near 1740 rpm (less than 1800 rpm) for 4-pole motors, and near 2900 rpm (less than 3600 rpm) for 2-pole motors. This type motor

needs no brushes, its speed depending upon its load. In record players the load is light enough and nearly enough constant so that adequate performance is obtained.

The rotating field required in the shaded-pole induction motor is produced by the action of the shaded pole. As noted earlier, a shaded pole consists of a pole with its winding and an auxiliary one-turn copper strap around a portion of the pole. Because the copper strap is a shorted turn, the magnetic field cannot build up so rapidly in the portion of the pole which it surrounds as in the remainder of the pole. Similarly, as the magnetic field in the pole decreases, the field in the surrounded portion cannot decrease so rapidly. As a result, the surrounded portion acts as an independent pole lagging the main pole by nearly 90°. By placing the shaded portion between the normal poles, the electric field is made to move uniformly from unshaded to shaded, to next unshaded, to next shaded pole. Therefore, the magnetic field applied to the rotor appears to rotate. In a number of the higher-priced or higher-power shaded-pole motors, capacitors are utilized to shift the phase of the current supplied to the poles half way between the directly-connected poles in the

(Continued on page 44)

Fig. 4. Illustration of the construction of a two-pole shaded-pole induction motor (a) and its rotating field (b). The rotating field is produced by induced current in the short-circuited one-turn copper strap.

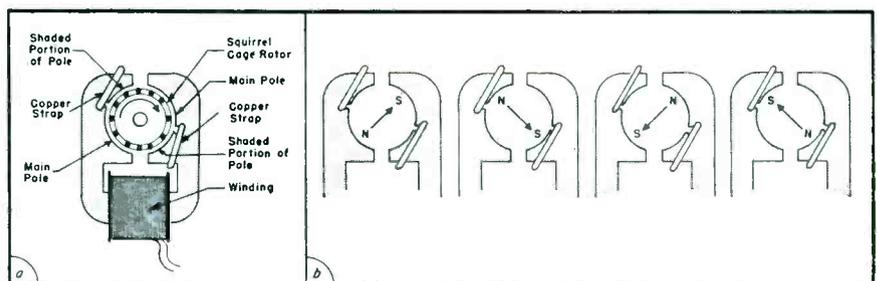

Another ANTENN-GINEERED Original

by **Snyder**
PHILADELPHIA

TORQUE-T-ANTENNA

WITH EXCLUSIVE INTERCEPTOR DISCS




WEIGHS ONLY 27 OUNCES

- NEWEST ELECTRONIC DISCOVERY
- OUTMODES OLD FASHIONED ANTENNAS
- EQUAL/BETTER THAN ANY CONICAL
- QUICKER/LASIER I-MAN INSTALLATION
- STACKS FOR FRINGE AREAS

**SAVES SPACE
FACTORY PREASSEMBLED
GOES UP FAST**

and Costs Less!

Unfold - Tighten - Erect

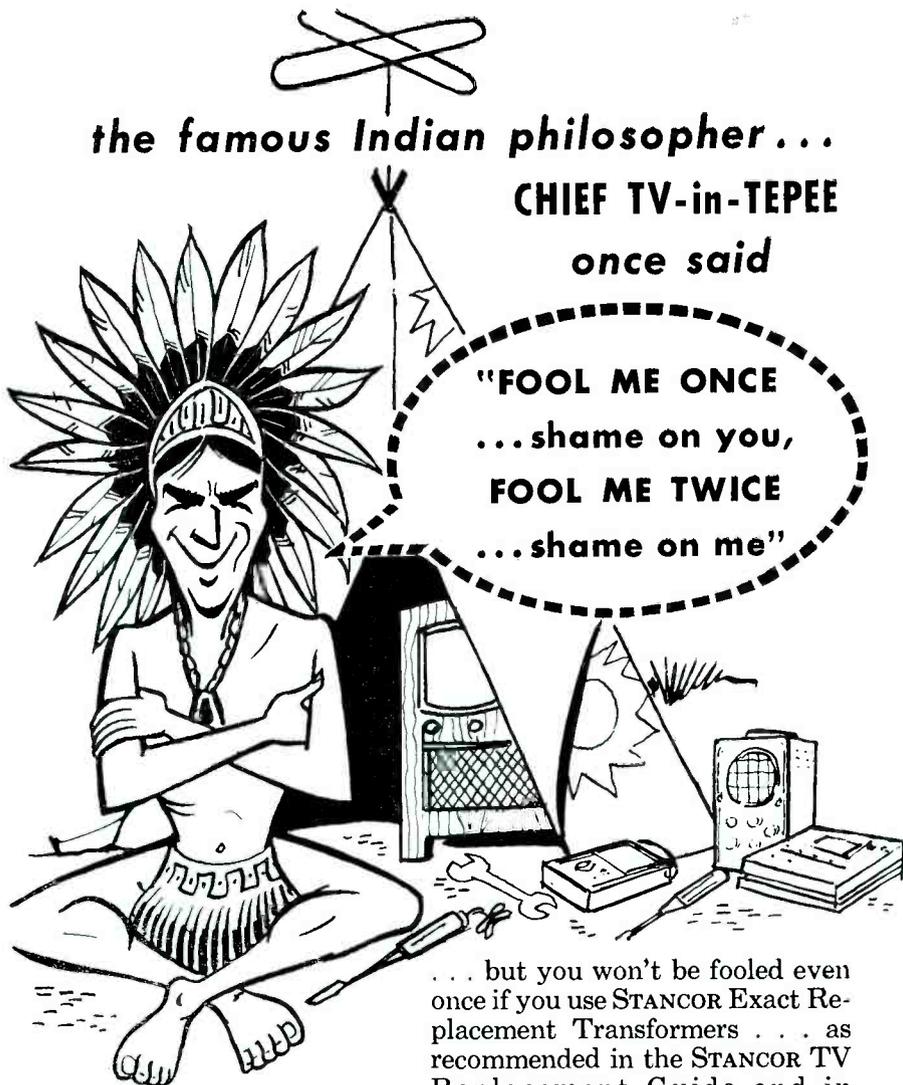

the famous Indian philosopher . . .

**CHIEF TV-in-TEPEE
once said**

**"FOOL ME ONCE
...shame on you,
FOOL ME TWICE
...shame on me"**

EXPORT SALES:
Roburn Agencies, Inc.
431 Greenwich St.
New York 13, N. Y.



**CHICAGO
STANDARD
TRANSFORMER
CORPORATION**

3588 ELSTON AVENUE . CHICAGO 18, ILLINOIS

. . . but you won't be fooled even once if you use STANCOR Exact Replacement Transformers . . . as recommended in the STANCOR TV Replacement Guide and in Counter-Facts . . . because every unit is a **VERIFIED** exact replacement, designed from the original manufacturer's specifications and tested by actual installation and operation in the recommended chassis.

FREE—54 page STANCOR TV GUIDE. Lists over 8000 TV models and chassis and over 150 exact replacements. Available from your STANCOR distributor or from Chicago Standard.

Audio Maintenance

(Continued from page 42)

motor. Such motors are known as split-phase type, which are not common in home-type reproducing equipment.

There are variations of the shaded-pole models. Where, for instance, a variety of frequencies and voltages are encountered, geared center-drive units are used. One such type has been designed for 50 or 60 cycle use, with voltages between 100 and 250 volts. A governor controls the speed

by changing the load on the system. The motor operates at 1130 rpm, well below the synchronous speed of 1800 rpm, and changes speed considerably for a small change in torque. The governor is able to absorb changes in load torque and developed torque, while permitting only a small change in speed.

Universal motors are similar in appearance to the motors described, being typically geared center-drive units. The governor is essential in their use since their speed changes

rapidly for changes in load. A major disadvantage of a universal motor is the need for brushes to supply current to the wound rotor. This type of motor is built, however, to operate on 100 to 250 volts, *dc* to 60 cycles, and only a tap change is required for the change from the 110 to the 220-volt range.

Synchronous motors are similar to induction types. However, the rotor is constructed of material which will retain its magnetism; the rotor becomes a permanent magnet and rotates in synchronism with the rotating field. Its speed is locked to line frequency, so long as the load does not exceed *pullout*, the maximum load the motor can handle.

Torque motors are induction motors designed to be operated *stalled*. They are used for takeup and rewind on tape recorders, where they serve to maintain tape tension by operating at low voltage, and to rewind by applying full line voltage; in rewind, the motor operates as an induction motor.

The available torque of typical phono motors is in the order of 1 to 5 ounce-inch; the power ratings run between 1/500 and 1/40 *hp*. Higher-torque motors are also in use, principally in high-priced equipment.

Record player drives fall into two broad classifications. The majority of American-produced units are rim-drive, utilizing a rubber-rim idler wheel between the motor or auxiliary shaft and the rim of the turntable. Many foreign units are center-drive, with gear speed-reduction.

Multiple-speed record players almost always utilize a change in the drive mechanism, rather than a change of motor speed to obtain the required speeds. The common means of changing speeds is to utilize three drive shafts, belt driven at different speeds, or driven at the same speed but having different diameters. One which produces the proper turntable speed is positioned to engage the idler by the speed-change lever. Another means of changing speeds is to utilize stepped diameters on the motor shaft, and shift the idler up or down the shaft so that it engages the proper diameter section. In gear-drive motors, the gearing is changed, while in governor-controlled motors moderate variations can be made by changing the governor setting to change the motor speed.

Maintenance

Some types of motors and many record changers need occasional oiling. The instruction manual for the particular instrument requiring atten-

tion should be consulted before it is oiled. Service men should note that improper oiling can do substantial harm. For example, one motor manufacturer¹ points out that the idler support plate should never be oiled. The load on this part is sufficiently light that even light oil will actually increase friction. In general, small phono-motors are built with bearings which will not run dry during the life of the motor.

The principle cause of slowing down or erratic operation are dirt and oil on critical parts. It has been found that carbon tet is very good for idler wheel cleaning.² Dust and lint must also be removed from the surface driven by the idler; the rim of the turntable. The motor and pulley shafts on multiple-speed drives must be free of oil. No oil should get on the surfaces driving the idler. If care is taken, so that oil is applied only on the bearings, one drop of number 10 or 20 oil on each motor bearing may quiet for a considerable time a noisy motor or free a motor which was running slow. However, the importance of avoiding oil on the drive shafts, idlers, and turntable rim cannot be overemphasized.

The idler wheel suffers from another possible trouble. On systems which do not relieve the pressure on the idler, flats can develop when the unit is not operated for a considerable time. In most cases, after 15 to 20 minutes of operation the flattened portion will return to normal. If the flat appears to be permanent, it will then be necessary to replace the idler. An attempt to remachine the idler tire will probably result in *wow*. In production, idler-wheel concentricity is held to extremely close tolerance, in the order of one ten-thousandth of an inch, by special techniques. It is unlikely that one can find a machine shop which can do as well.

More serious troubles, such as damaged windings or bent assemblies are items which the Service Man can best serve his customer by complete replacement. Rewinding the motor generally is not economical. It may be possible to solder a break in the top layer of a motor winding, but repairs of this sort are seldom satisfactory. It becomes necessary in the case of difficult repairs, to estimate whether the satisfactory repairs can be done for less than the price of a new part. Quite often replacement is not only more satisfactory in terms of performance, but also in cost to both the customer and the Service Man.

¹General Industries.

²From Alliance Manufacturing.

**Avoid makeshifts...
use function-fitted**

AEROVOX Hi-Q[®] CERAMIC CAPACITORS



Ceramic capacitors serve in the more critical applications. That's why the Aerovox Hi-Q line is outstandingly complete. You get that function-fitted number every time. Which means you don't waste time, effort and money, improvising with the usual limited selections.

There are General Purpose (including By-Pass and Coupling) and Temperature-Compensating Ceramics. Aerovox furnishes both categories in Tubular and Disc types. Also many special-purpose types—Stand-Offs, Feed-Thrus, High-Voltage Cartwheels and Plate Assemblies.

Avoid makeshifts! Use function-fitted Aerovox Hi-Q Ceramic Capacitors. Stocked by your Aerovox distributor for your convenience.

Latest Aerovox Catalog contains the outstanding selection of ceramic capacitors. Available free of charge only from your Aerovox distributor.

AEROVOX CORPORATION



**DISTRIBUTOR SALES DIVISION,
NEW BEDFORD, MASS.**

In Canada: AEROVOX CANADA, LTD., Hamilton, Ont.
Export: Ad. Aurisma, 89 Broad St., New York, N. Y. • Cable: Aurisma, N. Y.

Federal's

Silver-Q

COMMUNITY TV CABLES

... with NON-CONTAMINATING JACKET!

Federal's original "silver" high-molecular polyethylene provides
20-YEAR LIFE EXPECTANCY!

CHECK THIS CHART
for all CTV single and
double shielded needs

"SILVER-Q" COMMUNITY TV CABLES

also feature separator of
anti-oxidant carbon black
polyethylene... to extend
life and step-up signal
transmission performance!

The longer the cable life... the longer your
profit on Community TV operations - and the
better the quality... the better the customer is
satisfied with reception.

Get the facts about Federal's "Silver-Q" cables
with long-life, non-contaminating jacket... Give
your system the finest... for initial installation
or replacement...!



K-135 Primary N-R Lead-in (RG11/U)



K-136 Secondary N-R Lead-in (RG-59/U)



K-171 Aux. Secondary N-R Lead-in (RG-6/U)



K-133 Secondary Lead-in (RG-59/U)



K-134 Primary Lead-in (RG-11/U)

NOW YOU CAN BUY K-14DS for COMMUNITY TV

Federal's famous "Conqueror of Canyons" is Community TV's top primary lead-in... engineered and manufactured for long-life long-distance runs... fewer amplifiers... low line loss... "Super Service" year-round signal transmission... over the toughest terrain!



(Also available as K-14 - Single-Shielded)


For more information on any of the above cables, see your Federal Distributor. If you require special technical data, write to Federal:

Address your inquiry to Dept. D-856

Federal Telephone and Radio Company

A Division of INTERNATIONAL TELEPHONE AND TELEGRAPH CORPORATION
COMPONENTS DIVISION • 100 KINGSLAND ROAD • CLIFTON, N. J.

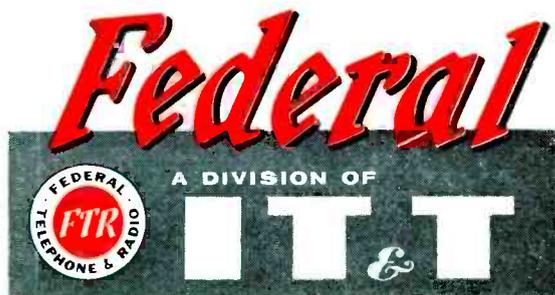In Canada: Standard Telephones and Cables Mfg. Co. (Canada) Ltd., Montreal, P. Q.
Export Distributors: International Standard Electric Corp., 67 Broad St., New York





by MAXWELL ALBERTS

OFTEN, SERVICE MEN ask why it is necessary to carry so wide a variety of needles to suit the various pickups now in use. The answer is not as involved as many argue. In audio we are faced with a very simple fact; audio is a perfectionist's hobby and thus any chance of achieving standardization, that would reduce the number of needle types, is a pretty hopeless task. Even the manufacturer who caters to audio must be a perfectionist who can never be trampled by standardization.

We have the great variety of needles for phonograph pickups because pickup designers and manufacturers are constantly seeking to achieve an improvement in reproduction. Every pickup has been designed to provide its best performance with a particular type of stylus. For this reason, when the stylus is replaced, it is extremely important that one selects the *correct* shape and size as a replacement.

The variable reluctance pickup offers an excellent example of complementary stylus-cartridge design. In this cartridge we have an armature that moves between the poles of a magnetic circuit and is very close

to the stylus itself; actually the armature moves with the needle instead of being driven by it through the arm.

The three most common forms of stylus (excluding the type used in the *v-r* pickup) are shown in Fig. 1.

The simplest shape, merely a modification of the old-fashioned needle, is illustrated in *a* of Fig. 1. This drawing reveals the important effect that the shape of the needle and the material of which it is made can have on performance. Even the old acoustic phono exhibited different tonal qualities, when assorted brands of needles were inserted, because of the change in needle length, rate of taper, and the quality of steel of which it was made. Now that the quality of reproduction has advanced a long way from that of the old acoustic phonograph, this principle is even more important.

In replacing even the simple type of needle, one must be careful to see that the correct dimensions and material are considered. If a needle with a precious stone tip, such as sapphire or diamond, is used to replace a shorter-lived metal-alloy type, its dimensions must follow the recommendation for the particular type of

Acoustical Characteristics
to Needle Performance . . .
Requirements of Cartridge
Design to Match Needle
Structures

pickup to maintain a correct frequency-response characteristic.

The other two types, shown in Fig. 1, merely differ in the manner that the shank holder moves in the pickup. In each case there are two important dimensions to take into consideration, besides giving attention to the fit of the shank in its holder, which should be a good push or snug fit, so that there is no room for vibration at this point; the radius of the stylus movement (shown as *r* in Fig. 1) must be correct, and also the length of the shank for inserting into its holder.

These factors are important to insure faithful movement of the stylus in the record's grooves at all frequencies. The stylus can depart from its correct movement in a variety of ways. One possibility of such deviation is shown in Fig. 2; the small double-ended arrows, underneath the end view of the stylus, represent possible directions of movement.

Desirable Needle Movement

The desirable one is shown at the extreme left, immediately underneath the stylus. Since the stylus is to some extent flexible in the vertical direction, it is also possible for the stylus to move, relative to the pickup, in a vertical direction as shown in the second position. These two forms of movement should be quite independent; the lateral direction should follow the waves in the groove, and the vertical direction, if it occurs at

Figs. 1 and 2 (below): Fig. 1 shows three common forms of needle, excluding the *v-r* type. In each, apart from the shank fitting snugly into its holder, the following dimensions are important: (a) the length and rate of taper; (b) and (c), radius of stylus movement, *r*, and the shank length, *l*. Fig. 2 illustrates end view of stylus arm of type (b) shown in Fig. 1, showing possible modes of stylus movement.

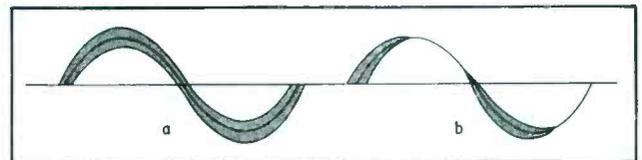
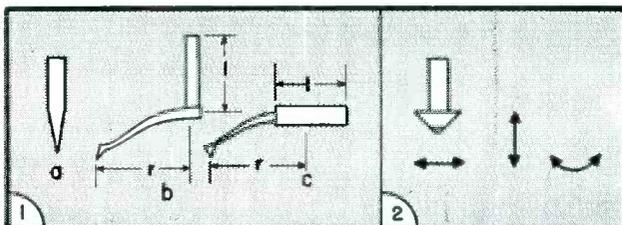


Fig. 3. The last mode of movement shown in Fig. 2 causes a combined wave, as at (a), to lose some of its high-frequency component, as at (b), which is a bad form of intermodulation.

NOW 2 B&K CRT Money-Makers

TEST and REPAIR TV PICTURE TUBES

NEW DELUXE CRT 400 with 4½" Plastic Meter

This portable Cathode Rejuvenator Tester quickly locates and corrects picture tube troubles in a few minutes, right in the home, without removing tube from set! Restores emission, stops leakage, repairs inter-element shorts and open circuits. Life-test checks gas content and predicts remaining useful tube life. Grid Cut-Off reading indicates picture quality customer can expect. Earns servicing dollars in minutes. Cuts operating costs, eliminates tube transportation. Saves money on TV set trade-in reconditioning. Pays its way from the very first day.

Weighs only 5 lbs. mounted in rugged, luggage style, carrying case covered with handsome, durable leatherette. Size: 11 x 7½ x 5".

Model 400. Net \$54.95



Over 20,000 CRT'S NOW IN DAILY USE ACROSS THE NATION



NEW ECONOMY CRT 200

A quick profit maker priced low enough for every serviceman to cash in on picture tube repairs. Performs most of the functions of the CRT 400. Has 3" meter. In leatherette carrying case. Size: 11 x 7½ x 5". Weighs 5 lbs.

Model 200. Net \$39.95



Send for Bulletin 104-S

B & K MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois



Audio

(Continued from page 47)

all, should merely allow the stylus to follow any vertical undulations in the groove, due to record warpage. There should be no coupling between the two forms of movement.

Unbalance Problems

If the pickup is well designed, and the stylus fits it correctly, no such coupling will exist, but if an incorrect stylus is fitted into the cartridge, the movement may be thrown out of

balance so that some kind of coupling will occur between the two forms of movement. The third arrow shows a rocking type of movement that can occur due to unbalance in a vertical direction. The stylus, instead of moving purely from side to side, introduces a rocking movement simultaneously. This can cause a serious deviation from the desired frequency response; but this is not the only defect possibility that can result from this poor combination.

Sometimes two resonances occur, and they are in a form of multiple

relationship, so that a lateral movement at one frequency will excite a vertical movement, at some harmonically-related frequency. As a result, the stylus performs a figure of eight, or some other kind of Lissajous pattern. This kind of movement causes the stylus to bounce in and out of the groove, instead of following along the groove's base. Since program material contains a wide range of frequencies at the same time, such movement will not only cause distortion of the frequency that generates the trouble, but also produce intermodulation of any other frequency present, as shown in Fig. 3; page 47.

The wave at (a) represents the reproduction as it should appear, while the wave at (b) shows the result when the needle or stylus jumps out of the groove during segments of the lower frequency wave. The stylus cannot follow the high frequency undulations superimposed on the low-frequency wave, and hence they get lost for part of the latter, giving a choppy or dithery effect to high-frequency reproduction.

One should not assume, that if this effect does not show up when a single record is played as a test, that it will not occur on some other program material. If there is some unbalance in the pickup, due to use of a wrong stylus, this effect can occur at some frequency and will show up when the particular note that causes the Lissajous pattern is played on the disc; only when this particular note is played, will that dithery effect appear.

These effects are most likely to occur if a stylus using the wrong shank length is employed, because this will upset the leverage, transferred to the pickup, and also the balance of the movement.

Now let's consider the effects that occur when we use styli that have the wrong radius of tip movement. Two different stylus arm lengths at the end of a tone-arm are illustrated in Fig. 4. Assuming that the compliance, which is usually a piece of damping material somewhere in the cartridge itself, is the same in each case, a change in the stylus arm length will cause a change in the effective compliance to the movement of the tone arm at its resonant frequency; it will, incidentally, shift the resonant frequency. This change occurs because the longer stylus arm allows a larger movement, for the same degree of distortion in the compliance material.

This means that, if a short stylus happens to be the correct one, a long-


er stylus will result in a lower frequency of rolloff and a peak occurring before rolloff, as shown at Fig. 5 (curve B), causing undue emphasis of rumble and the lower frequencies in the record and creating unnatural reproduction, particularly on voice. If the longer stylus arm is the correct one for the particular pickup, use of a shorter stylus arm will result in restriction of the low-frequency response, as shown in curve C of Fig. 5.

Another possible result of incorrect stylus length or even incorrect construction of the stylus itself, high-frequency response, is illustrated at Fig. 6. The length of the stylus dictated by the designer of the cartridge always takes into account the compliance provided and various other characteristics of the pickup. The kind of movement that the stylus arm should follow, in tracing out a wave in the groove, is shown in *a* of Fig. 6. If the reaction produced by the pickup at the pivot point does not induce enough damping to the stylus, it may set up a different kind of vibration, at some frequency toward the high end, such as that shown at *b*. This is a natural resonant vibration of the stylus arm itself. If the pickup provides the correct damping, this natural resonant frequency will not occur, and the movement will be as shown at *a*, the same as at all other frequencies; but with insufficient damping to this particular resonance of the stylus, the movement changes to that shown at *b*.


The important thing to remember is the relationship between the angle of movement at the pivot, which is what determines the output in most cartridges. The resonance increases the angle of movement, provided by the same displacement of the stylus point at the lefthand end.

It should be remembered that the pickup cartridge, as well as its stylus, is an expendable item. This was the reason for introducing detachable cartridge elements, in place of the earlier units built right into the tone-arm.

Fig. 4. How the radius of stylus movement can affect tone-arm resonance effects. The relative lengths of the arrows show the relative movement at tone-arm resonance, other things being equal.

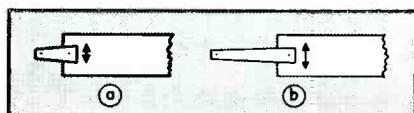

**G.E.'s Pacer "40"
4-inch cup speaker**

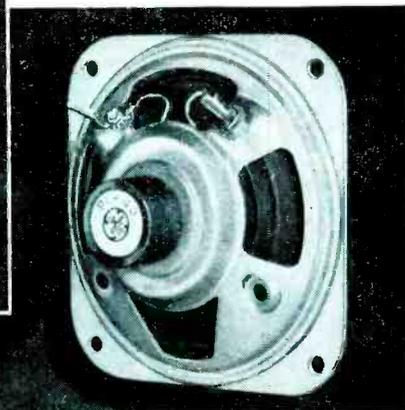

**LOW COST,
NO YOKE,
LESS BULK**

G.E.'s NEW POWDERED IRON MAGNET SPEAKER

Is easier to install, delivers all the quality of speakers twice its magnet weight!

HERE'S a high-quality speaker that is more compact—easier to install—yet carries a low price tag. An ideal replacement unit for standard or portable radios or TV sets, intercoms, or mobile radio installations.

A NEW CONCEPT OF SPEAKER ENGINEERING

The PACER "40" combines unusual strength with compact design. High energy Alnico 5 magnet material, teamed with a powdered iron structure, greatly reduces flux leakage, and because the yoke is eliminated, less space is needed. Result—a compact, all-purpose speaker with an efficiency rating comparable to yoke-type units with twice the magnet weight.

Aluminum base voice coil assures reliable all-weather performance, provides excellent heat dissipation, and high power handling capacity. Felt dust cap prevents air gap contamination, minimizes distortion. Chipboard gasket, two-way lug type terminals.


NOW A WIDE RANGE OF G-E SPEAKERS

G. E. catalogs a full line of loudspeakers for general replacement, PA systems, drive-ins, and hi-fi needs. In this wide line of superior speakers you will find the right model for your needs. See the quality line—the G-E line, today. Or, write: *General Electric Co., Radio & TV Dept., Section R3102, Electronics Park, Syracuse, N. Y.*

Progress Is Our Most Important Product


GENERAL  ELECTRIC

Fig. 5. Effect of incorrect stylus arm length (radius of movement) on lf response: A represents correct response; B is result of a stylus arm giving a longer radius of movement; and C is result of too short a stylus arm.

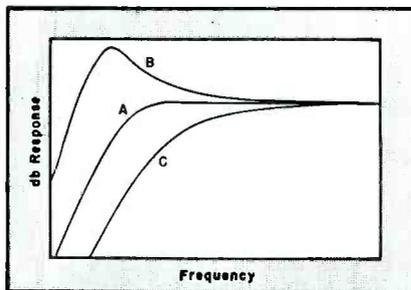


(Below)

Fig. 6. The wrong combination can also result in spurious stylus arm resonance, as shown in (b). By comparing the angle of movement for the same stylus displacement at its tip, it will be seen that the rotation at the pivot is accentuated at this frequency.

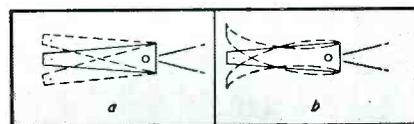

KESTER

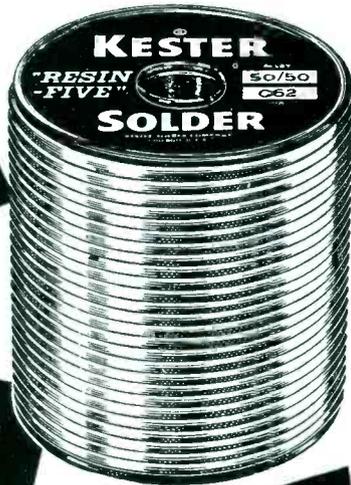

Absolutely non-corrosive and non-conductive, KESTER "RESIN-FIVE" CORE SOLDER contains an activated type of resin that gives you that fast, positive action on all your jobs . . . including the most difficult.



KESTER SOLDER COMPANY
 4844 Wrightwood Avenue • Chicago 39, Illinois
 Newark 5, New Jersey • Brantford, Canada

SOLDER

Independent Service Man

(Continued from page 21)

still many battery sets in use, even in farm homes with electricity, and servicing them has been profitable for us. Using the auto-transformer, battery voltage may be lowered at will, to simulate the effect of the battery running down. At a voltage of 1.1, the oscillator tube may cut off. If this cutoff takes place appreciably above this value, the set will quit before the battery is fully discharged, with a resultant loss. It then becomes necessary to replace the oscillator tube; the oscillator should still work, even down as far as 1.05 volts. This demonstration, which is very rapid, can be used to convince one of the need for a new tube; the voltage is simply run down until the old tube stops oscillating, and a new tube can be installed to show that it will operate on the required voltage. This gadget is also used to test three-way portables; an ac voltmeter was recently added for quick checking. Here too, if the sets do not remain in operation down to an applied line voltage (around 105 volts) trouble will appear. Replacement of either the oscillator tube or the rectifier will usually remedy this complaint.

Other service aids we've installed include a picture tube, with yoke assembly, mounted on the bench to avoid removal of cabinet-mounted picture tubes. Special extension harnesses can be made up or purchased for the same purpose, to use the set's own tube.

Because of the variation in overhead expenses, an entirely new rate

Servicemen everywhere are saying...

MOST VALUABLE TV SERVICE INSTRUMENT EVER MADE!

\$181 in INSTRUMENTATION FUNCTIONS for only **\$49⁹⁵**

7 Performs these VITAL FUNCTIONS

COMPLETELY CHECKS:

- ← Flybacks and Yokes
- ← Selenium Rectifiers
- ← Continuity
- ← Condensers
- ← Picture Tubes
- ← Series Filament Tubes — for Newest TV Sets
- ← Reactivates Pic. Tubes

TV COMPONENT TESTER
 by **TRANSVISION**

SOLD ONLY THRU SELECTED DISTRIBUTORS

DISTRIBUTORS:
 Some areas still available. Write, wire, phone for complete program.

Write for the name of the one in your area.

TRANSVISION, INC., NEW ROCHELLE, N. Y. S-10

Rush name of your nearest Distributor

Send _____ TV Component Testers. Enclosed find \$_____ deposit, balance C.O.D.

Name _____

Address _____

City _____ State _____

"It just isn't fair . . . she's using JENSEN NEEDLES!"

DON'T JUST SAY CAPACITORS • DON'T JUST SAY CAPACITORS • DON'T JUST SAY CAPACITORS

Ask For Sprague By Catalog Number

Know what you're getting . . . get exactly what you want. Don't be vague . . . insist on Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 61 Marshall Street, North Adams, Mass.

SPRAGUE

WORLD'S LARGEST CAPACITOR MANUFACTURER

DON'T JUST SAY CAPACITORS • DON'T JUST SAY CAPACITORS • DON'T JUST SAY CAPACITORS

structure prevails in the smaller towns. To arrive at this schedule in our town, all of the Service Men agreed on a nominal set of charges for various jobs, such as antenna installations, tube replacements, etc.

We have found that most customers object to *hour-charges*; Service Men in our community have found far less *price-resistance* to prices quoted by the job, even though they work out to exactly the same amount.

This ties in with another facet of small-town life, not so prevalent in the cities. In the small town, everybody knows everybody else, and the most potent form of advertising known is merely *word-of-mouth*. It far exceeds in effectiveness any other form of advertising. One small word of either praise or condemnation from a neighbor will do more for you than all of the other advertising you could possibly use. It works both ways, too, so one must be careful and always do a top-notch job.

Transistor Radio

(Continued from page 23)

this lower bias and have a lower amplification factor, thus reducing the gain of the receiver and accomplishing the overall aim of *agc*.

Troubleshooting

At present there is only one way to check a transistor; by substitution. Unlike a vacuum-tube radio then, it is best to check the circuit thoroughly before attempting to check the transistors.

The cause of transistor failure is moisture getting through the seal. Since the transistors used in this set are hermetically sealed, failures should be few. This should govern you in a direction just the opposite of the vacuum-tube radio philosophy; suspect the transistor only as a *last resort*.

Normal service procedures can be followed in troubleshooting transistorized radios. With a voltmeter the battery supply should be checked first. If this is okay, any well-known troubleshooting procedure can be tried. The stage-by-stage interruption method, starting at the output stage, works well. The signal-tracing method works equally well and may be a little better. It is up to individual preferences which method should be used.

The foregoing checks will only give you the stage in which the trouble is located; resistance and voltage tests must be employed to find the defective part. If this procedure fails to disclose a defective component,

Better
Restore the Original Sound
with **Better** Replacement Speakers

OXFORD
SPEAKERS
are **Better**

Because:

Oxford specializes in the designing and manufacturing of a complete line of speakers and has been doing so for many years.

Since speakers is our business . . . since we supply more of the BEST manufacturers of original equipment . . . since we have quality replacement speakers for any and every application . . . you will actually better the original sound with OXFORD SPEAKERS.

Why wait . . . find out TODAY why more and more servicemen are switching to OXFORD SPEAKERS . . . truly the BETTER SPEAKERS in every way!

OXFORD

ELECTRIC CORPORATION

3911 SOUTH MICHIGAN AVENUE
CHICAGO 15, ILLINOIS

EXPORT — ROBURN AGENCIES NEW YORK CITY
IN CANADA — ATLAS RADIO CORP. LTD., TORONTO

Our latest catalog
is available . . .
write today!
...at better jobbers!



the transistor can be blamed as the cause of trouble and should be replaced.

While checking voltages you will note that they are exceptionally low; the total B— supply in this model is -13.5 v. The collectors on all of the *pnp* transistors are negative with respect to their emitters and bases, so don't be worried when the polarity is just the reverse of that in a tube radio.

At present, the five transistors are soldered into the circuit. If it becomes necessary to remove or replace a transistor, extreme caution should be used with your soldering iron, be-

cause excess heat will permanently damage the transistor.

If it is found necessary to replace the converter or first and second *if* amplifier transistors, it may be necessary to change the value of R_7 (100-470 ohms) in the second *if* amplifier for optimum receiver sensitivity, consistent with no regeneration.

One should always make sure that the battery is fresh and delivers the full 13.5 v; then start with R_7 at 470 ohms. If the set regenerates, the next lower value resistor should be tried and the procedure repeated until the resistance *just below* the lowest value where regeneration occurs is found.

1st with all prices

Dave Rice's Official Pricing Digest answers a need long-felt by Servicemen—List or resale prices for every replacement part or component at your fingertips.

Over 300 pages; covers more than 60,000 items

Compiled like a telephone book (1) Alphabetical by Manufacturer (2) Alphabetical by Product Category (3) Numerical by Part Number. Price and identify any replacement item in seconds—as easy as 1-2-3.

1st handy sized reference in the industry

9 3/4" long by 3 3/4" wide . . . convenient for counter, pocket, tool box or tube caddy.



1st completely revised four times each year

Publication dates are October, January, April and July. Prices will be current on each publication date.

1st in savings

Time and money savings—no wasted effort—no calls to your distributor to check prices. No undercharges—no overcharges when you price your tubes and parts from the Official Pricing Digest.

1st issue October, 1955

PRICE \$2.50 PER COPY—will pay for itself many times over by giving you CORRECT PRICES where and when you need them.

available exclusively thru your parts distributor

See him now and place your order for the first issue.

Electronic Publishing Co., Inc.
180 North Wacker Drive
Chicago 6, Illinois

Service Engineering

(Continued from page 36)

grid resistor. This voltage is fed to the rectifier's doubler circuit and cancels some of the positive noise voltage. The amplified noise drops to a lower magnitude, due to the quieting of the receiver. As a result of this carrier present, the *dc* amplifier conducts less and lets the first audio stage conduct and amplify any audio present.

One might think that control of the volume is an easy matter; one simply inserts a potentiometer in the grid of the first audio tube. However, one must remember that this receiver is in the mobile control head and is actually separated from the receiver by a 17' or 20' cable; with this in mind one can see it becomes difficult to run audio leads through a 20' cable and not pick up hum and noises.

A fixed value of resistance could be inserted in the grid of the audio amplifier and the output attenuated with a constant-impedance network, which is commonly known as a pad. This pad would act as the volume control. But these pads are invariably noisy and require frequent cleaning or replacement. Another method that is commonly used is to vary the *dc* plate and screen voltage to the second limiter tube. This does eliminate hum and noise, but the volume cannot be adjusted to zero. The chief disadvantage in this method is that the position of this control affects the operation of the squelch circuit, which depends upon noise from the discriminator. There is also high voltage on the controls; thus servicing control head is a hazardous chore. These objectional features have been overcome by replacing the last resistor in the receiver deemphasis network by a variable resistor. This method utilizes a two-lead connection between the receiver and the control lead, which permits balancing out any hum or noise due to any other leads in the control cable.

The complete unit has been built with the operator and service engineer in mind. For example, in the receiver there are pin jacks to check the oscillator and multiplier-grid voltages, second low *if*-grid voltage, first and second limiter grid voltages, discriminator and plate-supply voltages, and primary source voltage. Any 20,000 ohm-per-volt meter having a three-volt scale can be used. Simple multipliers are used so that the service engineer can readily determine the actual voltages or currents. This design permits metering two or more circuits simultaneously.

PERMO'S SALES INDEX

A factor of the relative national rate of movement of each type of needle to other types

Permo Number	Std. Price	Index	Index per Std. Price	Index per Std. Price	Type of Needle	Permo Type	Material & Size
A-300	\$7.50	\$1.50	\$1.47	7.9	33 1/2 & 45	Shurcut Jewel	001 RCA
A-304	1.50	.90	.88	7.3	33 1/2 & 45	Parametrol	001 Permo
B-310	1.00	.50	.49	136.2	33 1/2 & 45	Parametrol	001 Shure RCA
A-314	1.50	.90	.88	1.3	33 1/2 & 45	Parametrol	003 Shure RCA
C-320	1.50	.90	.88	17.9			
B-324	2.50	1.50	1.47	6			
B-324D	25.00	15.00	14.70				
C-360	7.50	1.50	1.47	0			
C-360D	25.00	15.00	14.70	11.0			
A-311	1.50	.75	.73	30.2			
A-312	1.50	.75	.73				
C-312	25.00	15.00	14.70				
C-312D	25.00	15.00	14.70				
AC-313	3.00	1.80	1.76	4.7	33 1/2 & 45	Parametrol	
AC-313D	26.50	15.90	15.58				
A-314	2.00	1.20	1.18	1.4	33 1/2 & 45	Parametrol	
A-314D	25.00	15.00	14.70				
AC-315	2.50	1.50	1.47	6.7	33 1/2 & 45	Parametrol	


Keeps you from being "STUCK" with once-a-year sellers . . .

PERMO PHONO NEEDLES

PERMO, INC. CHICAGO 26

ATLAS Cobra-Jectors

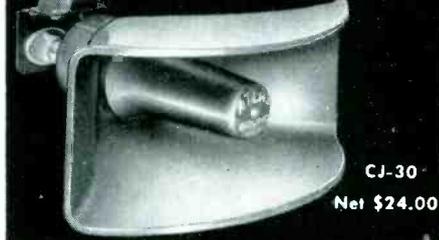- wide angle dispersion
- indestructible fiber-glass
- all-weather construction



CJ-30
Net \$24.00

CJ-14
Net \$16.80

Designed for wide angle coverage, paging, high efficiency intercom, sensitive talk-back. Tops in articulation. Convenient omnidirectional mounting bracket. In appearance, they're "beauts".

SPECIFICATIONS	CJ-30	CJ-14
Input pwr (cont.)	15 w	5 w
Input imp.	4 or 8 Ω	4, 8 or 45 Ω
Response (cps)	250-9,000	400-10,000
Dispersion	120° x 60°	120° x 60°
Bell Size	14" x 6"	9 1/2" x 5 1/2"
Over-all length	14"	8 1/2"

Amazing "power packages"—use the Cobra-Jectors for the "tough" jobs.

ATLAS SOUND WRITE FOR COMPLETE CATALOG
ATLAS SOUND CORP.
1442 — 39 St., Bklyn. 18, N. Y.
In Canada: Atlas Radio Corp., Ltd., Toronto, Ont.

Tube News

by A. M. KELWOOD

UNTIL ONLY a short while ago, transistors were used mainly in hearing aids. Recent advancements in their design and construction made it possible to include them in pocket radios, and achieve highly efficient results; as reported on page 22 of this issue.

To extend further the range of applications, transistor experts have now pushed the frequency utility of these pea-sized items way up into the megacycle range. As a result, it has become possible to develop many unusual devices, including transistorized test gear and even 2-way equipment.

The test unit is a portable voltmeter† covering frequencies from 20 cps to 1 mc.

The voltmeter, which has printed circuits, has a peak sensitivity of 0 to 1 millivolt and any of 12 decade (10 db) ranges may be switched on the front panel; 10-megohm input impedance on all ranges is included to prevent disturbances to circuits under test. Output terminals are provided so that the unit can be used for monitoring of the voltmeter's amplifier output with any device having 50,000-ohm or greater input impedance. Power is supplied by three standard batteries which provide over 35 hours continuous operation.

The 2-way item is a 40-50 mc walkie-talkie 12-transistor FM package, designed for the military, which can be carried in a shirt pocket. Field tests have indicated that two-way communication over a quarter mile is possible with this novel transistorized transceiver.

For radar and ultrahigh TV application, there has been developed a *junction tetrode* type of transistor* that will operate in the 1000-mc range. This has been accomplished by the addition of a fourth electrode to the basic junction transistor.

The junction tetrode transistor has been made to perform at high frequencies by reducing the width of the germanium bar and the central *p*-layer and by adding the fourth electrode. New techniques for producing the thin middle layer for all types of transistors have made possible an almost ten-fold reduction in its width; in the tetrode transistor,

†Alto Scientific Co., Palo Alto, Calif.

*Bell Laboratories.

**Amperex Electronic Corp.; type 2N115.

**NO SPEAKER
INSTALLATION
PROBLEMS**
with
QUAM
Adjust-a-Cone[®]
SPEAKERS

QUAM speakers have transformer mounting brackets welded to the baskets.

There is a universal mounting bracket packed with every QUAM 3½", 4", 5", 5¼", 6½", 4" x 6" and 5" x 7" Adjust-a-Cone speaker, **AT NO EXTRA COST.**

In addition there are four threaded mounting holes in the pot . . . besides the usual mounting holes in the speaker basket.



A good hi-fi speaker need not be expensive.

Prove it to yourself by listening to QUAM extended range and coaxial speakers.

They can't be beat for small budget hi-fi installations.

Write for QUAM Hi-Fi Catalog No. 69.

**QUAM
HI-FI
SPEAKERS**

for fine audio reproduction at low cost

ask for QUAM, the quality line, for all your speaker needs
QUAM-NICHOLS COMPANY
232 EAST MARQUETTE ROAD • CHICAGO 37, ILLINOIS

this layer is less than two ten-thousandths of an inch wide.


To fill the growing need for transistors with greater power, a *pnp* junction power transistor, which delivers 5 watts push-pull output with a 6-volt supply, has been developed.**

This transistor has a very high current rating with a low voltage drop across it; the relationship between its base and collector currents is extremely linear. The output impedance is low enough for a 5-ohm speaker voice coil to be used directly as the collector load in the *af* output stage.

Transistorized portable voltmeter.



Troubleshooting Community-TV Systems†

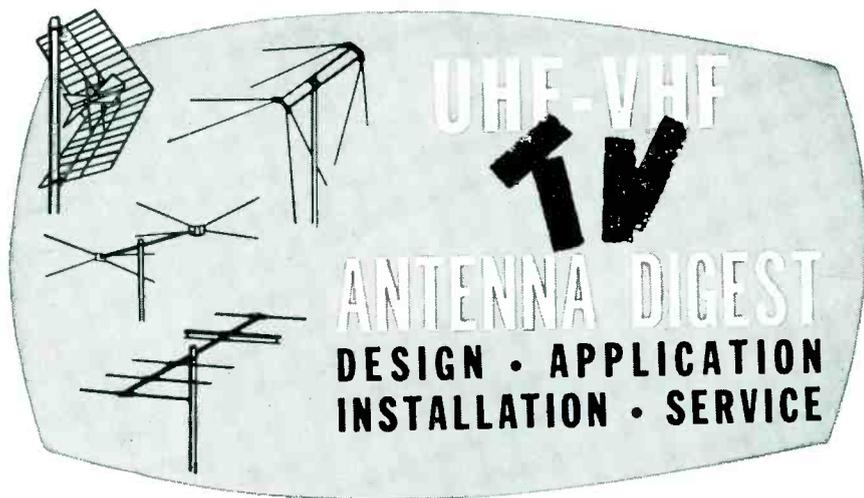

by RALPH G. PETERS

THERE ARE four vital tools required in the community-TV maintenance-repair kit; a lightweight TV chassis, *vtvm* or 20,000 ohm-per-volt meter, sweeper and field-strength meter.

The TV set serves to check the quality of reception at the antenna, amplifier locations, and distribution points. Any sudden marked changes in reception offer a positive indication of trouble and the type of pix trouble will reveal what's wrong with the system.

The *vtvm* or 20,000 ohms-per-volt meter is required to check the *agc* of single channel and broadband amplifiers and also to measure line voltage. A sweeper with good linearity will show response of single channel amplifiers and also permit spot checking of broadband equipment.

Field strength meters with continuous tuning are preferred. A 6-db pad should be used between meter and measuring point to min-

imize standing-wave ratio. Sometimes the meter detector will not completely rectify peak pulse signals on the picture carrier. This results in a reading lower than actual available signal.

After making field repairs such as tube replacement, replacement of power supply parts, gain controls, etc., one should inspect units for gain with a field-strength meter, a switch attenuator and an *rf* signal source. The *rf* signal can be conveniently obtained by tapping off the cable system. The attenuator switches should be set so that the db attenuation approximates the amplifier's db gain. Field-strength meter input readings should equal output readings.

Sometimes, gain of amplifiers will be found to be low as a result of low *ac* line voltage. To correct, a

†Based on data prepared for the *Blonder-Tongue Master TV Installation Manual*.


voltage-regulating transformer is recommended, with the wattage rating equal to or slightly less than the total wattage of the equipment to be regulated. Overloading the regulating transformer by 5% assures maximum regulation. Voltage regulating transformers should be ordered with *wave form correcting networks* to restore the peaks of the *ac* sine wave, providing the proper B+ voltage and amplifier gain.

Typical troubles encountered in a community system include multiple ghosts or smears, due to an open circuit or short circuit in transmission line, improper line or equipment termination, incorrect terminal connection or jumper position on one of the units, or ghost in received signal.

An overloaded line amplifier or distribution amplifier, or unbalanced signals in the line will cause complete picture breakup and often *ride-through* of one channel into several others. To correct overloading of amplifiers, gain must be reduced and attenuator pads should be used; amps should also be spaced further apart.

Often diagonal lines, or light heringbone, venetian blind and swirling patterns will appear. The causes are many: *Rf* interference due to FM stations or other radio services, local TV set oscillator radiation, line amplifier oscillation, co-channel or adjacent channel interference from another TV station. Local TV set oscillation can be cured only by checking individual sets and tapoffs for proper connections, and for at least 12-db isolation at the tapoff. Increasing the amount of isolation at the tapoff to the troublesome receiver will often eliminate the problem.

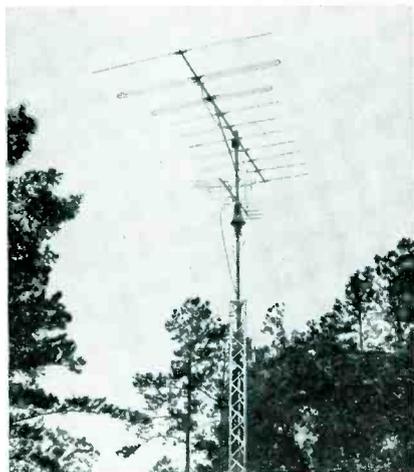Three types of antenna systems installed in fringe and deep-fringe areas. At left is a rotor-controlled stacked tower-mounted antenna set up for co-channel problems. Center view shows roof-top mounted yagi with a rotator for fringe-zone use. And at right is another tower-mounted rotator-controlled stacked yagi for the super-fringe country involved in co-channel trouble. (Jack Darr)



BLACK AND WHITE TV

COLOR TV

TRANSISTOR RADIOS
FM RADIOS

AM RADIOS

AMPLIFIERS AND TUNERS
AUTO RADIOS

RECORD CHANGERS



WHAT'S YOUR SERVICE PROBLEM?

PHOTOFACT HELPS YOU SOLVE IT

FASTER, EASIER, BETTER, MORE PROFITABLY!

**THE WORLD'S
FINEST SERVICE DATA**



THESE GREAT FEATURES ARE EXCLUSIVE IN PHOTOFACT—THEY HELP YOU EARN MORE DAILY, HELP INSURE CUSTOMER SATISFACTION

PHOTOFACT Service Data is the *only* service information based upon first-hand examination of the actual production-run receivers and equipment. It is authentic, uniform data developed through actual study and analysis by service engineers in the Howard W. Sams Laboratories. PHOTOFACT is the *only* data prepared from the practical point of view of the Service Technician.

Thousands of Service Technicians use PHOTOFACT daily for time-saving, profit-boosting service operations. If you've never used PHOTOFACT, you've never realized your full earning power—you've never given such complete customer satisfaction. So get the proof for yourself. Try PHOTOFACT—use it on any job. Your Parts Distributor has the Folder Sets you need for any of the 17,000 TV and radio receivers, changers, recorders, etc., covered in PHOTOFACT. Once you use this great service, we know you'll want the complete PHOTOFACT Library.

FREE Send for the PHOTOFACT CUMULATIVE INDEX IT'S VALUABLE!

Send for it! Your guide to virtually any model ever to come into your shop; helps you locate the proper PHOTOFACT Folder you need to solve any service problem on any model. Once you have the make and chassis number, it takes just 60 seconds to find the applicable PHOTOFACT Folder. Send coupon now for your FREE copy of the valuable Cumulative Index to all the PHOTOFACT Folders you need.



FREE

FULL SCHEMATIC COVERAGE

1. Famous "Standard Notation" uniform symbols are used in every schematic.
2. The same standard, uniform layout is used for each schematic.
3. Diagrams are clear, large, easy to read, easy to handle.
4. Wave forms are shown right on the TV schematics for quick analysis by 'scope.
5. Voltages appear on the schematics for speedy voltage analysis.
6. Transformer lead color-coding is indicated on the schematic.
7. Transformer winding resistances appear on the schematic.
8. Schematics are keyed to photos and parts lists.

FULL PHOTOGRAPHIC COVERAGE

9. Exclusive photo coverage of all chassis views is provided for each receiver.
10. All parts are numbered and keyed to the schematic and parts lists.
11. Photo coverage provides quicker parts identifications and location.

ALIGNMENT INSTRUCTIONS

12. Complete, detailed alignment data is standard and uniformly presented in all Folders.
13. Alignment frequencies are shown on radio photos adjacent to adjustment number—adjustments are keyed to schematic and photos.

TUBE PLACEMENT CHARTS

14. Top and bottom views are shown. Top view is positioned as chassis would be viewed from back of cabinet.
15. Blank pin or locating key on each tube is shown on placement chart.
16. Tube charts include fuse location for quick service reference.

TUBE FAILURE CHECK CHARTS

17. Shows common trouble symptoms and indicates tubes generally responsible for such troubles.
18. Series filament strings are schematically presented for quick reference.

COMPLETE PARTS LISTS

19. A complete and detailed parts list is given for each receiver.
20. Proper replacement parts are listed, together with installation notes where required.
21. All parts are keyed to the photos and schematics for quick reference.

FIELD SERVICE NOTES

22. Each Folder includes time-saving tips for servicing in the customer's home.
23. Valuable hints are given for quick access to pertinent adjustments.
24. Tips on safety glass removal and cleaning.

TROUBLE-SHOOTING AIDS

25. Includes advice for localizing commonly recurring troubles.
26. Gives useful description of any new or unusual circuits employed in the receiver.
27. Includes hints and advice for each specific chassis.

OUTSTANDING GENERAL FEATURES

28. Each and every PHOTOFACT Folder, regardless of receiver manufacturer, is presented in a standard, uniform layout.
29. PHOTOFACT is a *current* service—you don't have to wait a year or longer for the data you need. PHOTOFACT keeps right up with receiver production.
30. PHOTOFACT gives you complete coverage on TV, Radio, Amplifiers, Tuners, Phonos, Changers.
31. PHOTOFACT maintains an inquiry service bureau for the benefit of its customers.

EASY-PAY PLAN TO FIT YOUR BUDGET

Ask your PHOTOFACT Distributor . . . he'll show you how you can now own the PHOTOFACT Library through a unique Easy-Pay Plan that exactly fits your needs. Pays for itself as you EARN MORE.

HOWARD W. SAMs & CO., INC.

Howard W. Sams & Co., Inc., Dept. 5-K5
2201 E. 46th St., Indianapolis 5, Ind.

Send FREE Photofact Cumulative Index.


Name.....

Address.....

City.....Zone...State.....

HELPS YOU EARN MORE DAILY

and NOW a NEW

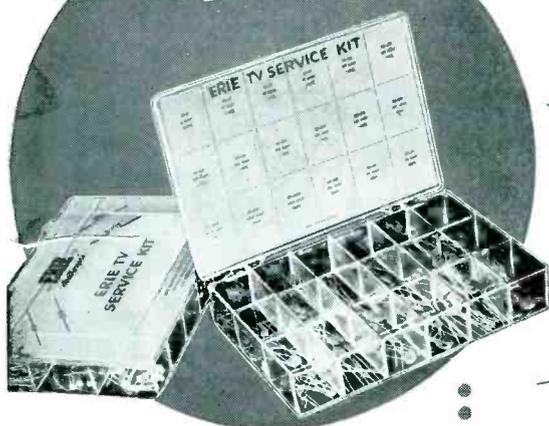

ERIE CERAMICON®
TV SERVICE

Kit

HERE'S WHAT YOU GET

- ① 63 High Stability ERIE Disc or Tubular Ceramicons
- ② 18 Popular Values
- ③ Handy, Convenient 18 Section Plastic Storage Case
- ④ Exceptional Value


HERE'S WHAT YOU SAVE

REGULAR PRICE
63 Piece ERIE Ceramicon Assortment \$15.00
18 Section Plastic Case 1.75
Total Value \$16.75
YOU PAY \$10.65
YOU SAVE \$ 6.10

ORDER NOW
From Your
ERIE
DISTRIBUTOR



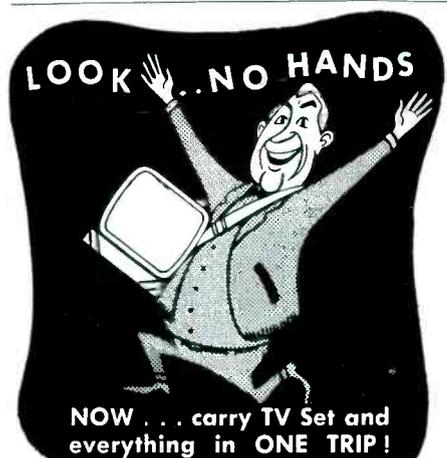ERIE ELECTRONICS DISTRIBUTOR DIVISION
ERIE RESISTOR CORPORATION
Main Offices: ERIE, PA.
Factories: ERIE, PA. • LONDON, ENGLAND • TRENTON, ONTARIO



NOW . . . carry TV Set and everything in ONE TRIP!

TV HAMMOCK

Save time . . . Save trips . . . carry TV set safely with both hands free. Heavy durable harness webbing with adjustable strap. 24x24 inches.

DeLuxe Model 24 List Price \$4.95
Economy Model 18 List Price 2.95

SAVE-UR-MIKE COVER

Special impregnated white celanese cover. Fits and protects all microphones. Keeps out mist, rain, dust and mike can be used covered with only slight loss of highs. . . . List Price \$1.25



See your dealer or write for complete details and where to buy.

S. I. Jacobson Mfg. Co.
1414 S. Wabash Ave. • Chicago 5, Ill.

Wire-Wound Resistors

(Continued from page 25)

plus an ambient temperature of 25° C, produces a surface temperature of 325° C. Since ambient temperatures in most equipment are higher than 25° C, it is necessary to derate the resistor used. Thus, if 50° C is considered as the ambient temperature, which is typical of many TV receivers, then the resistor should be used only at approximately 87 per cent of its rated power.

Most equipment manufacturers consider this factor in their design and seldom operate a wire-wound resistor at its full power rating. For example, a manufacturer may call for a 10-watt resistor to do a job when, actually, only 5 to 7 watts are being dissipated.

Adjustable Wire-Wound Applications

When using an adjustable-type wire-wound resistor, that portion which is used should be required to dissipate only a corresponding part of the full power rating. For example, let us suppose a 2,600-ohm, 10-watt resistor is required, but is not


available. Instead, a 3,000-ohm adjustable wire-wound resistor is available. To use the 3,000-ohm resistor, it should have a higher rating than 10 watts. Specifically, the rating should be 3,000/2,600 x 10, or 11.5 watts. Inasmuch as the next highest power rating available is 25 watts, a 25-watt resistor must be used. Selecting a resistor whose actual power rating is approximately 50% greater than its calculated power rating, to compensate for ambient and excessive surface temperatures, is in accordance with standard practice.

The cost of a replacement part, as well as time, can be saved by replacing only the opened or burned out section of a multi-section, or tapped resistor, with a single fixed resistor of approximately the same resistance value and power requirement as the damaged section.

Exact Replacement Factors

One must always use the exact replacement, in resistance and inductance, (or one proven to be satisfactory) for a power wire-wound resistor, when it is used as part of the video output tube plate load. This practice must obtain because a variation in inductance can change the video response characteristic, thus impairing picture quality. Fig. 10 illustrates what happens when an incorrect 5,000-ohm 10-watt resistor is substituted for the original in the video amplifier circuit. If a round tubular type were used, its inductance would be approximately 100 uh or a large portion of the total inductance in the circuit including the 370 uh peaking coil. On the other hand, if a core-type 10-watt resistor were used as a replacement, the inductance would then be at least one-tenth that of the round tubular type, and improper as a replacement.

Fig. 10. Schematic of TV video output stage showing effect of using other than recommended replacement for 5,000-ohm, 10-watt resistor.

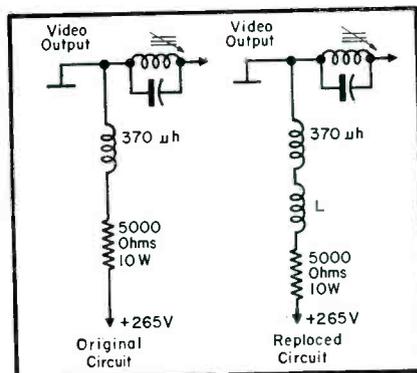

Ser-Cuits

(Continued from page 41)


lator utilizing cathode feedback through a tapped transformer. It is similar to the well known Hartley oscillator except that the transformer is untuned.

The current pulse from the vertical oscillator discharges a 1-mfd vertical sweep capacitor (C_{504}), which recharges through the height control, toward the boosted B+ supplied from the horizontal damper circuit. The height control limits the rate of charging of this capacitor, and thus the magnitude of the sweep voltage when the next discharge pulse occurs. The networks connected to the vertical sweep capacitor shape the waveform supplied to the vertical output tube in order to obtain a linear sweep. The vertical-sweep output amplifier is a conventional circuit utilizing a 6CM6 (V_{18}), transformer-coupled to the vertical-deflection coils of the deflection yoke. A negative blanking pulse is derived from the retrace voltage across the vertical deflection coils of the yoke, and applied to the grid of the picture tube.

For the horizontal sweep, at the output of the second sync amplifier (the second half of V_{18}), the synchronizing signal is differentiated, to eliminate the vertical sync pulses, and applied to the grid of the horizontal sweep control tube, the first half of a 6SN7GT (V_{19}). The second half of V_{19} is a blocking oscillator with a partially resonant transformer in a grounded-cathode Hartley-oscillator circuit. The grid-blocking voltage, applied to the blocking oscillator, is controlled by the horizontal sweep control tube in response to the combined sweep and sync voltages applied to the grid. This is a typical *afc*-horizontal circuit. The current pulse from the blocking oscillator discharges an adjustable 10-160 mmfd capacitor, used as a horizontal drive control (C_{811}). When this capacitor recharges, the voltage across it drives the horizontal-sweep output tube.

The horizontal sweep output circuit is conventional; a 6CD6G (V_{20}) driving the deflection yoke through an output transformer, while a 6V3 (V_{21}) damps the ringing of the output circuit by converting the excess energy to boosted B+. The flyback high-voltage supply utilizes a 1B3GT (V_{22}) to supply 18 kv for the picture tube. The remainder of the circuit, such as the linearity and width controls, are also conventional.

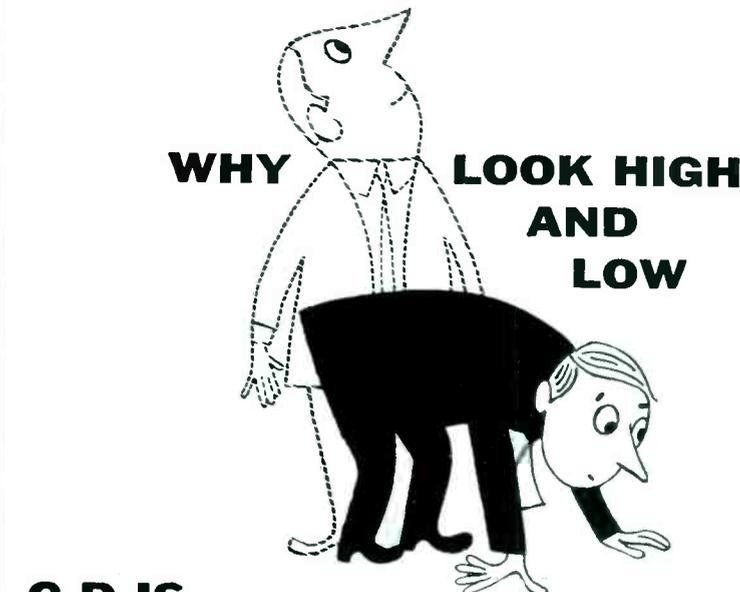The automatic-gain control circuit is keyed by a positive flyback pulse




C-D IS THE ONLY COMPLETE LINE OF ELECTROLYTICS

No matter what you need in electrolytic capacitors—C-D has it. Every type, shape and rating . . . all of consistent high quality proven by outstanding field performance. C-D capacitors are always reliable . . . and readily available—because Distributors *who know*, carry the complete Cornell-Dubilier line.

Free! TV Capacitor "Replacement Guide"—and C-D Twist Prong Cross Index from your C-D Distributor. He's listed in your local Classified Telephone Directory.

C-D's "UP" twist prong

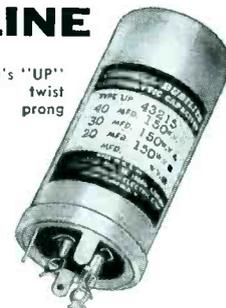

C-D's Blue Beaver

There are more C-D capacitors in use today than any other make.



CONSISTENTLY DEPENDABLE
CORNELL-DUBILIER CAPACITORS

PLANTS IN SOUTH PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER AND CAMBRIDGE, MASS.; PROVIDENCE AND HOPE VALLEY, R. I.; INDIANAPOLIS, IND.; SANFORD AND FUQUAY SPRINGS, N. C.; SUBSIDIARY: THE RADIART CORPORATION, CLEVELAND, O.

from the horizontal transformer. The positive pulse is applied to the plate of the *agc* rectifier, the first half of a 12AU7 (V_{18}). Sync pulses, which come from the horizontal sync separator, are applied to its grid. A 200,000-ohm potentiometer (R_{701}) in the cathode of the horizontal-sync separator serves both as a cathode load across which the sync voltage applied to the *agc* circuit is developed, and as a source of adjustable bias for the *agc* rectifier. (The sync amplitude supplied to the *agc* circuit is not affected by this control since a .0082

and .0068-mfd capacitive divider (C_{706} and C_{708}), with a .0047-mfd coupling capacitor (C_{707}) bypass the control.

The positive keying pulse from the horizontal deflection circuit is applied to the plate of the *agc* rectifier. The amount of current drawn depends upon the amplitude of the positive sync pulses applied to the grid. This current flowing through three resistors (R_{705} , R_{706} and R_{707}) with values of 270,000 and 10,000 ohms and 3.3 megohms, respectively, to B+ of 330

(Continued on page 58)

for service and lab. work

Heathkit PRINTED CIRCUIT OSCILLOSCOPE KIT FOR COLOR TV!

① Check the outstanding engineering design of this modern printed circuit Scope. Designed for color TV work, ideal for critical Laboratory applications. Frequency response essentially flat from 5 cycles to 5 Mc down only 1½ db at 3.58 Mc (TV color burst sync frequency). Down only 5 db at 5 Mc. New sweep generator 20-500,000 cycles, 5 times the range usually offered. Will sync wave form display up to 5 Mc and better. Printed circuit boards stabilize performance specifications and cut assembly time in half. Formerly available only in costly Lab type Scope. Features horizontal trace expansion for observation of pulse detail — retrace blanking amplifier — voltage regulated power supply — 3 step frequency compensated vertical input — low capacity nylon bushings on panel terminals — plus a host of other fine features. Combines peak performance and fine engineering features with low kit cost!

Heathkit TV SWEEP GENERATOR KIT ELECTRONIC SWEEP SYSTEM

② A new Heathkit sweep generator covering all frequencies encountered in TV service work (color or monochrome). FM frequencies too! 4 Mc — 220 Mc on fundamentals, harmonics up to 880 Mc. Smoothly controllable all-electronic sweep system. Nothing mechanical to vibrate or wear out. Crystal controlled 4.5 Mc fixed marker and separate variable marker 19-60 Mc on fundamentals and 57-180 Mc on calibrated harmonics. Plug-in crystal included. Blanking and phasing controls — automatic constant amplitude output circuit — efficient attenuation — maximum RF output well over .1 volt — vastly improved linearity. Easily your best buy in sweep generators.

MODEL 0-10
\$69.50
Shpg. Wt. 27 lbs.

MODEL TS-4
\$49.50
Shpg. Wt. 16 lbs.

Heath COMPANY
A SUBSIDIARY OF DAYSTROM, INC.
BENTON HARBOR 11, MICH.
WRITE FOR FREE CATALOG
...COMPLETE INFORMATION

(Continued from page 57)

v determines the average voltage at which the circuit operates. Since R_{707} is a 3.3-megohm unit, a current of .1 milliampere is sufficient to place the average voltage at ground.

This .1 mil current is supplied by the *agc* rectifier when a small sync pulse on the grid drives the tube out of cutoff, when the keying pulse occurs. With a slightly larger pulse applied, more current is drawn, and the average voltage becomes negative, with respect to ground. A relatively small change in sync-pulse amplitude will produce a large change in average voltage; the resultant change in gain of the receiver provides a system with very close control of the amplitude of the video signal.

R_{708} and R_{709} , in conjunction with a pair of .22-mfd capacitors, C_{704} and C_{705} , filter out the positive pulse, leaving a *dc* bias to be applied to the tuner. To prevent the bias from going positive, this bias supply is clamped by the double diodes of a 6AV6 (V_1). Contact potential of these diodes actually maintains the *agc* bus always negative by at least ½ volt. Another filter consisting of two resistors and two capacitors (270,000 and 10,000 ohms, and .22 mfd (R_{708} , R_{709} , C_{706} and C_{710}) is in the *agc* bias line to the first and second picture *if* stages. An 82,000-ohm resistor (R_{710}) forms a voltage divider with R_{708} and R_{709} , which reduces the magnitude of the *agc* voltage to one-fourth that applied to the tuner. The different characteristics of the tubes used in the tuner and in the *if* amplifiers require this difference, so that the gain reduction for strong signals will be properly proportioned among the controlled stages to prevent overload.

The audio output of the ratio detector is deemphasized by R_{112} and C_{113} , (39,000 ohms and .0022 mfd), and fed to the audio amplifier through the tone-compensated volume control.

A floating *paraphase* inverter, another 6AV6, supplies the signal to a push-pull circuit. It should be noted that this circuit is inherently quite independent of tube characteristics, because of feedback from plate to grid through 470,000 and 33,000 ohm resistors, R_{126} and R_{121} . This feedback also makes the circuit self-balancing.


A transformer type supply, with high current capacity in dual 5U4C rectifiers, provides well-filtered B+ to all of the stages of the receiver. A bleeder provides the five different values of B+ for optimum set operation. Bypass capacitors are placed from the power leads to the chassis to help reject interference caused by razors, mixers, and the many other home noise sources.

NOT VERY BIG!

in fact...the one truly miniaturized clip in this age of miniaturization! The new

M U E L L E R

MINI-GATOR

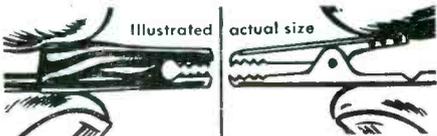

Separate skin-tight vinyl plastisol insulator covers right down to the nose. Will not tear. Slotted "lip action" tip permits full jaw opening without "baring" teeth.

Steel (cadmium plated) or solid copper, 1-1/16" long. Jaws open 3/16". Solder connection. Clinching ears for cord strain relief. For No. 20 or smaller wire.

Simply stated in Electronic terms, it's



(Mini-gator : Alligator :: Transistor : Tube)

SIMPLIFIES TESTING OF ALL MINIATURIZED AND SUB-MINIATURIZED EQUIPMENT.

Provides the quick convenience of a test clip in spots that are otherwise inaccessible.

FREES THE HAND THAT HELD THE PROD!

WRITE TO FACTORY FOR **FREE SAMPLES!**
Mueller Electric Co. 15737 E. 31st STREET
CLEVELAND 14, OHIO

Coming Events

Northern California Audio Show
September 30, October 1 and 2
Sheraton-Palace Hotel, San Francisco

Institute of Hi-Fi Manufacturers Show
November 4, 5 and 6
Benjamin Franklin Hotel, Philadelphia

Don't just say CAPACITORS

Ask For Sprague By
Catalog Number

Know what you're getting... get exactly what you want. Don't be vague... insist on Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 61 Marshall Street, North Adams, Massachusetts.


SPRAGUE

WORLD'S LARGEST
CAPACITOR MANUFACTURER

TV Parts... Accessories

TRIAD REPLACEMENT FLYBACKS

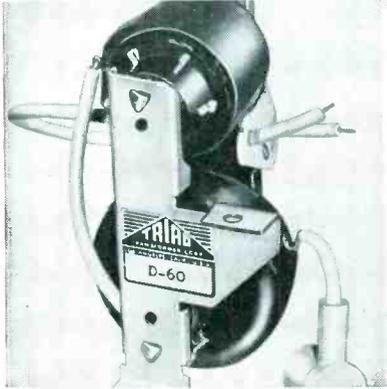Five replacement flyback transformers, for use in RCA, Travler and Zenith TV sets, have been announced by Triad Transformer Corp., 4055 Redwood Ave., Venice, Cal.



MERIT HORIZONTAL-HVO TRANSFORMER REPLACEMENTS


Six horizontal and high-voltage output replacement transformers have been announced by Merit Coil and Transformer Corp., 4427 N. Clark St., Chicago, Ill.

One unit, *HVO-41*, has been designed for Airline, Coronado, Truetone, Arlington, Firestone, Wells-Gardner, Silvertone and Warwick receivers; another, *HVO-42* for CBS-Columbia sets; *HVO-44* for Airline, Coronado, Firestone, Truetone and Wells-Gardner chassis; *HVO-45* for Westinghouse models; *HVO-47* for Andrea, Arvin, Du Mont, Hoffman, Kaye-Halbert, Pacific Mercury, Packard-Bell, Silvertone, Stromberg-Carlson and Tech-Master sets, and *HVO-48* for Magnavox receivers.

EICO TV ALIGNMENT CRYSTALS

A package of TV alignment crystals has been introduced by Electronic Instrument Co., Inc., 84 Withers St., Brooklyn 11, N. Y.

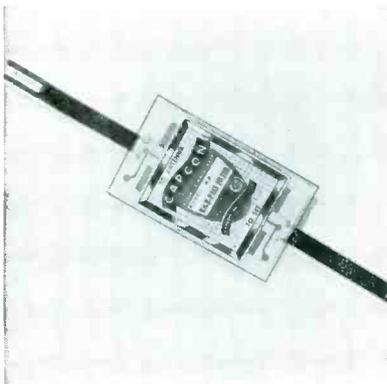Holds five 4.5 and five 5-mc crystals applicable to TV sweep generators and marker oscillators.



For the
Finest TV Master or Community System

Send us Your
Installation
Problem for
FREE

Engineering Advice

FREE:

Write for "Technical Information Pamphlet" on TV Master and Community Systems.

TRANSVISION
Master Systems
have been proven

**BEST IN
PERFORMANCE**

LOWEST IN COST

in hundreds of im-
portant installations

**BEST IN PERFORMANCE
BECAUSE Transvision
Master Units have spe-
cialized Broadband
and individual Chan-
nel Amplifiers for each
purpose.**

SOLD THRU SELECTED DISTRIBUTORS

Write for the name of the one in your area.

SPECIALIZED BROADBAND UNITS

with 1 or 2 outputs—each with full power
Built-in cable loss equalization on com-
munity broadband units. Largest line of
strip amplifiers, channel changers, etc.
Send us your problem.

Transvision offers you the choice of the
best Broadband Amplifier — at lowest
cost—for any particular community TV
job.



DISTRIBUTORS: Some areas still available.
Write, wire, phone for complete program.

TRANSVISION, INC. • NEW ROCHELLE, N. Y.

TRANSVISION FIELD STRENGTH METER

For Battery Operation and 110 V AC

Saves 50%
of installa-
tion cost



Model FSM-5B, for Battery Opera-
tion and 110 V AC. Weight 22 lbs. **\$89**
net

TRANSVISION, INC., NEW ROCHELLE, N. Y. S-10

Please send name of your nearest Distributor.
 FREE copy of Pamphlet on TV Master Systems.

Name _____

Address _____

City _____ State _____

(Left)
**Printed-circuit three-section high-pass
filter. Contains six coils and four ca-
pacitors. Designed to filter out inter-
fering signals below 54 mc. Enclosed in
transparent case.** (Capcon, Inc., 25
Willett St., N. Y. 2, N. Y.)

(Right)
**Multi-set couplers available as two-way
and three-way splitting devices. Housed
in weatherproof cases, couplers are de-
signed for installation on the exterior
of building. Couplers are of voltage-
splitting type. In high-signal strength
areas, units may be used in tandem
to serve as a TV distribution system.**
(Model 825; Technical Appliance Corp.,
Sherburne, N. Y.)



This is the 2-Set TV COUPLER

Rated No. 1

... by a nationally known independent product quality rating group as the result of tests made on 10 leading two-set couplers for:

- IMPEDANCE MATCH
- SIGNAL TRANSFER
- TWO-SET ISOLATION

MOSLEY 902



List Price \$3.95

Rated **FIRST** in overall quality for weak signal reception means; the MOSLEY 902 Dual Match 2-Set TV Coupler can be sold and installed in practically any TV area with full confidence that your customers will be completely satisfied!

Available at Radio and Television Parts Distributors — coast-to-coast.



GUN-TYPE SOLDERING TIPS

An assortment of gun-type soldering tips is now being marketed by Electric Soldering Iron Co., Inc., Deep River, Conn. Included is a tip 1/16" thick for soldering tight spots and deep chassis connections.

Tips, it is said, will not bend, anneal or develop surface residue, even though left on circuit beyond operating cycle.


Included in the assortment are tips for soldering connections to small prongs and for thin channel-type lug connections.

Bench-Field Tools . . .

XCELITE REAMERS

Chrome plated hand reamers, 38, with 1/2" to 3/4" capacity in wood, plastic and sheet metal, have been announced by Xcelite, Inc., Orchard Park, N. Y.

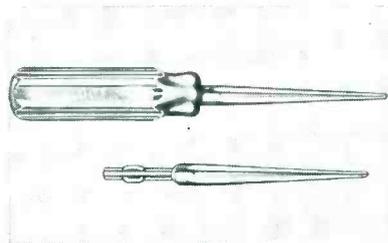Available with handle or to fit detachable handle in model 99 multi-purpose tool kit.



R-COLUMBIA CLEANER-LUBRICATOR

A tool, *TrolMaster*, developed to clean and lubricate TV or radio controls, without removing chassis, has been announced by the R-Columbia Products Co., 305 Waukegan Ave., Highwood, Ill.

To operate, knob is removed at front of control, device is filled with solvents, tool is screwed onto the control, and plunger is pushed in. By the addition of an adapter which screws on, unit can also be used to clean and lubricate auto radio controls.

Nine inches long overall. Made of solid brass.


Recommended for use with device is Kleontrol solvent; a non-inflammable fluid. Further details in bulletin 21.

ARGOS PORTABLE BENCH

A portable work bench, the *Quickie Bench*, for in-the-home repairs has been introduced by Argos Products Co., Genoa, Illinois.

When folded for carrying, bench resembles suitcase; 26" x 11" x 6 1/4" thick. Set up it provides a work surface (ma-sonite) 26" x 22" about 25" high. In addition there is an extension shelf 9" x 12" on one end.

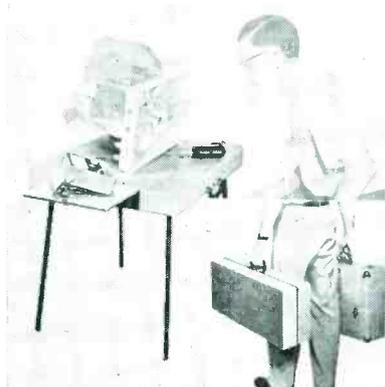Sides of bench are covered with tweed-gray fabric.



ask the
"Man-on-the-Roof"
why he prefers

South River



TWO
TO A
SET

RATCHET TYPE CHIMNEY MOUNT

Model RT (Galv. Banding)
Model RT-ST (Stainless Banding)

**FASTEST, SIMPLEST, MOST
CONVENIENT EVER
MANUFACTURED**

Mounts in 2 simple steps. Completely factory assembled with no eyebolts, banding clips, nuts, etc., to handle. Furnished with flat-lay, non-coiling banding, heavy gauge embossed, welded steel construction. Forged, heat treated Alum. ratchets.

Write for 1955 Catalog

SOUTH RIVER
METAL PRODUCTS CO., INC.
South River, New Jersey

pioneer &
outstanding
producer of
finest line
of antenna
mounts


SERVICE PARTS RACK

A heavy duty parts rack, for storage and display of radio and TV parts, has been introduced by Service Parts Systems, Inc., 13380 E. Nine Mile Rd., East Detroit, Mich.

MASTRA TOOL-TUBE CARRIERS

Three radio and TV tube and tool carriers, 11, 33 and 55, are now being produced by The Mastra Co., 2032 Euclid Ave., Cleveland, Ohio.

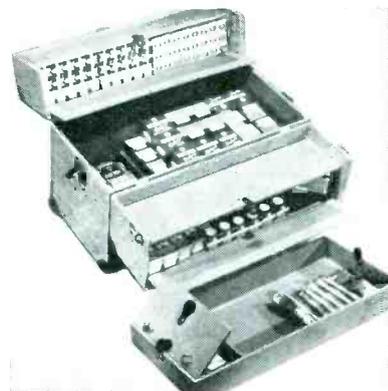Model 11 has room for 45 small, 44 medium and 21 large tubes, plus assortment of tools. Model 33 has a removable tool tray and partition for tester; holds 100 small, 60 medium and 30 large tubes. Model 55 features side pockets and removable tray.



Instruments

HICKOK VOM

A portable multimeter (model 455), with a self-disconnect that operates a reset button when a dangerous overload is applied, has been developed by The Hickok Electrical Instrument Co., 10521 Dupont Ave., Cleveland 8, Ohio.

Meter sensitivity is 20,000 ohms/volt *ac* and *dc*. A single selector switch is used for function and range settings. Batteries are housed in a compartment which is accessible without removing case.

Audio model (456) with a sensitivity of 20,000 ohms/volt *dc* and 1,000 ohms/volt *ac* and including *db* ranges is also available.



PHILCO VTVM

An *ac/dc* voltmeter-ohmmeter (model 6100) has been announced by Philco Corp., Philadelphia, Pa.

Six voltage ranges afford *ac* and *dc* voltage measurements up to 1,000 *v*; six resistance ranges from .5 ohm to 1,000 megohms. *Ac* frequency range extends from 20 to 20,000 *cps*. An accessory *hv* probe permits *dc* voltage measurement to 30,000.

HEATH LINEARITY GENERATOR

A linearity pattern generator (LP-1), covering TV channels 2-13, providing a free channel for adjustment, has been developed by Heath Co., 305 Territorial Rd., Benton Harbor, Mich. Produces vertical (6 to 12) or horizontal (4 to 7) bars, and cross hatch or white dot patterns. Horizontal and vertical frequency controls are provided for synchronizing and establishing aspect ratio. Attaches to receiver antenna terminals through a clip on shielded output cable. Uses 6X4, OA2, two 6J6s and a 12AT7. Can also be used to check sound.

G-C SERIES-FILAMENT TUBE CHECKER

Series-filament tube checkers for detecting burned-out tubes by plugging into proper tester socket (model 9270) are now available from General Cement Manufacturing Co., Rockford, Ill. Unit plugs into TV interlock or cheater cord.

Service man's DREAM COME TRUE

TIP . . . smallest ever, ideal for tight spots and deep chassis. Heats quickly.

TRIGGER distributes pull over several fingers, actuates heat and twin spotlights.

GRIP shaped to hand for untiring easy use.

FREE Introductory offer! Your choice, absolutely FREE of an Esico LUGER special alloy tip. Select it today from the ESICO Tips display on your distributor's counter. Fill out and take coupon below to your distributor. That's ALL!

NOW . . . Esico, the name known to the radio and electronics industries for quality soldering equipment for 28 years, bring you the newest achievement in electric soldering guns made expressly to serve servicemen's needs. No matter what soldering gun you now use, you'll want an Esico LUGER, with its wide selection of tip sizes and shapes which do not anneal, bend, or develop surface residue, even though kept on circuit beyond operating cycle. Here at last, is the smallest tip ever (only 1/16" thick) to service heretofore-impossible-to-reach remote connections without dissembling products and parts. **CONVENIENCE** plus! Imagine a point that permits you to pry or loosen wires while hot. Quick heat with easy triggering; well ventilated housing for cool, molded-to-hand grip and fatigue-free balance in any position for easy use. Twin spotlights focus on work. Light, compact for kit or pocket. Rests on side . . . no stand needed. No serviceman's kit is complete without an Esico LUGER . . . see, buy now!

ELECTRIC
Soldering Iron Co., Inc.
Deep River, Conn.

TAKE COUPON TODAY TO YOUR DISTRIBUTOR	(offer subject to withdrawal)	Electric Soldering Iron Co., Inc. 6255 Elm Street Deep River, Conn.
		I want Tip # _____ My distributor is _____ at _____ Signed _____ Address _____ City _____ State _____
		MR. DISTRIBUTOR: Esico guarantees your normal profit on this tip. Send coupon to us.



Phaostron vtvm

PHAOSTRON VTVM


A *vom* (777) featuring illuminated scales and provision for peak-to-peak measurements, has been developed by The Phaostron Co., 151 Pasadena Ave., S. Pasadena, Cal.

Two jacks are used for measurements on 42 ranges. Accuracy is said to be 3% *dc* and 5% *ac*. Uses separate range and function switches. It has two zero-center scales for FM discriminator alignment.

Accessories include a high-frequency coax cable and *dc* probe. Unit and accessories are housed in a leather carrying case.

NEW! Arrow's T-25 Staple Gun for Low Voltage Wire!

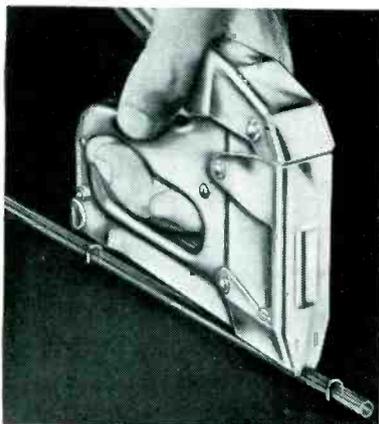For Wire Up To 1/4" in Diameter . . . Bell, Thermostat, Radiant Heat, Telephone, Inter-com, Burglar Alarm, etc.



Tapered striking edge gets into tight corners!

T-25 AUTOMATIC STAPLE GUN for wires up to 1/4" in diameter. Uses 7/16" and 9/16" round crown staples, galvalloy-coated for high rust resistance. Also available in rust-proof Monel wire.

LIST \$15.

SAFE!

Can't damage wire because staples automatically stop at right height! Won't even break 1/4" hollow glass tubing.

FAST!

Proved by test 6 times faster than old hammer method. Saves you 70% in fatigue and efficiency . . . saves many dollars a year.

HOLDS!

New staples get tremendous holding power from tack points that spread to lock themselves into wood!

Write for catalog and information.

ARROW FASTENER CO., INC.
ONE JUNIUS STREET, BROOKLYN 12, N. Y.

Schematics In This Issue

	Page
Tube Oscillator-Converter; Equivalent of Transistor Circuit	22
G.E. 675 Transistor Pocket Radio (Cover)	23
3-Way Portable Series-Filament String Using Wire-Wound Resistors	24
Wide-Band Chroma Amplifier in Demodulator Probe Preamp	27
Modified Autronic-Eye Circuit	28
G.E. Progress Receiver for 2-Way Use	35
G.E. Six-Coil 290-Kc IF Amp for 2-Way Receiver	36
ATR Filament Circuitry for Model 2600 TV Chassis	38
ATR 41-Mc 21-Inch TV Chassis; Complete Circuit	40, 41
TV Video-Output Stage Illustrating Use of Resistors	56

WHEN YOU CHANGE YOUR ADDRESS

Be sure to notify the Subscription Department of SERVICE at 52 Vanderbilt Avenue, New York 17, N. Y., giving the old as well as the new address, and do this at least four weeks in advance. The Post Office Department does not forward magazines unless you pay additional postage, and we cannot duplicate copies mailed to the old address. We ask your cooperation.

JFD WINS FCDA PUBLIC SERVICE CERTIFICATE

The Federal Civil Defense Administration has awarded a Public Service Certificate to JFD Manufacturing Co., Inc., for its recent role in the '55 Civil Defense atomic test program at the AEC Nevada test site.

GENERAL CEMENT CONSOLIDATES PLANTS

The General Cement Manufacturing Co., Rockford, Ill., and its five subsidiaries (G-C Electronics, Television Hardware Mfg. Co., Telco Electronics, Gearing Mfg. Co., and Wood Specialty Mfg. Co.) have moved into a five-story, 180,000 square foot building at 400 S. Wyman St., Rockford, Ill.

LINE OF ALUMINIZED PICTURE TUBES DEVELOPED BY RCA

A line of 25 types of aluminized Silverama television picture tubes, has been announced by the RCA Tube Division.

Included are 10, 12, 16, 17, 20, 21, 24, and 27-inch tube sizes, which it is said, will perform the functions of 114 types now on the market.

PRETELECAST CONFAB



Key figures in recent northwest speedboat race telecasts, sponsored by Channel Master. Left to right: Stan Sayres, owner of the boat Slo-mo-shun; Lee Naylor, Channel Master western district sales manager, and Bill O'Mara, sports director of KING-TV who directed the telecast.

10-MILLIONTH TV TUBE



Sylvania executives witnessing company's 10,000,000th TV picture tube wing its way to completion over a tube conveyor system in the Seneca Falls plant. Left to right: Willis C. Toner, plant manager; Matthew D. Burns, vice president-operations; Don G. Mitchell, chairman and president; W. H. Lamb, divisional general manager.

FINCO-LINE PROMOTION MEETING



Aaron Fox, Finco ad-agency account executive, delivering personalized zipper case containing introductory promotional material on Finco Geomatic line to M. L. Finney, Jr., Finco general sales manager. Looking on, left to right, Howard Freed, agency production manager and Bill Zagar, agency art director.

PERSONNEL



JACK M. GUTZEIT is now national sales manager of Rogers Electronic Corp., New York, N. Y.



Jack M. Gutzeit



Robert W. Felber

ROBERT W. FELBER, former national service manager for Stewart-Warner, has joined the sales organization of American Phenolic Corp., Chicago Ill., as head of a new community-TV division.

* * *

RUSSELL D. GAWNE has been named sales manager of G-C Electronics Manufacturing Co., a division of General Cement Manufacturing Co., Rockford, Ill.



Russell D. Gawne



Douglas Vining

DOUGLAS VINING has become a field engineer at Technical Appliance Corp., Sherburne, N. Y.

* * *

PHILIP A. PORTNOY has been named vice president of Electronic Instrument Co., Inc., 84 Withers St., Brooklyn 11, N. Y.

* * *

BENJAMIN C. BOWKER has been appointed public relations manager of Allen B. Du Mont Laboratories, Inc., 750 Bloomfield Ave., Clifton, N. J. . . . JACOB H. RUITER is now director of advertising and sales promotion of the technical products division.

* * *

WEST COAST SHIPPING DEPOT



Astron Blue Point capacitors going to west coast distributors from Astron's new Los Angeles warehouse.



IT'S PORTABLE

WEIGHT ONLY 1C LBS.

WHEN YOU COMPARE YOU'LL CHOOSE THE BEST

the **VITAMETER**
OVER 20,000 IN USE

AN INSTRUMENT DESIGNED TO MAINTAIN, IMPROVE and VITALIZE OPERATION OF CATHODE RAY TUBES

Unique reactivator function is accomplished by dynamic sweep between cathode and grid . . . removing gas ions and stale emitting material from surface of cathode tube.

the **VITAMETER**

The VITAMETER is precision designed and housed in rugged steel case to insure long and dependable service. It is light, compact, portable and therefore can be used on picture tube while it is still in the cabinet. Just plug in and attach instrument socket to C.R. Tube . . . easy to read indicators tells the whole accurate story at a glance. VITAMETER repairs tubes right-on-the-spot. NO GUESS WORK.


SEE YOUR DISTRIBUTOR OR WRITE

ELECTRONIC TEST INSTRUMENT CORP.
13224 LIVERNOIS AVENUE DETROIT 38, MICHIGAN

- analyzes performance characteristics
- locate and remove inter-element shorts
- repairs open elements
- welds open filaments
- restores or improves emission quality
- estimates tube life expectancy

\$6995 COMPLETE

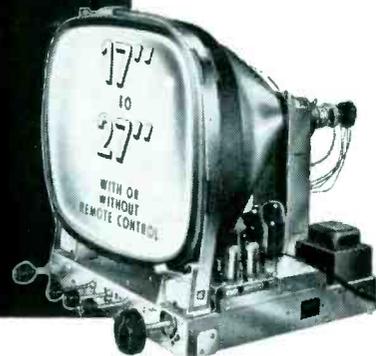For **CUSTOM**
and **HI-FI**
Installations



The **FINEST** in TV WIRED CHASSES

FRINGE AREA CIRCUITS
SUPERIOR PERFORMANCE
LOW IN COST

FEATURES include: Cascode Turret Tuner with individual antenna coils for each channel . . . Heavy duty power supply (2-5U4G) and scanning circuits. Uses power transformer, not selenium rectifiers . . . Fine quality, conservatively rated parts . . . Connection to plug into HI-FI system . . . Superior intercarrier circuit with special reflex sound system . . . AFC, AGC, vertical retrace blanking . . . Separate IF plate with 4 IF stages . . . Complete set of service and alignment information.

For **COIN OPERATION** . . . write for complete line of coin boxes, coin operated TV units and Master Systems.

by **TRANSVISION**

**SOLD ONLY THRU
SELECTED DISTRIBUTORS**

Write for name of the one in your area.

DEALERS: Write for Circuit Information and new low dealer prices

TRANSVISION, INC., NEW ROCHELLE, N. Y. S-10

- Rush name of your nearest Distributor
- Send circuit info on TV Wired Chasses

Name _____

Address _____


City _____ State _____

TRANSVISION, INC., NEW ROCHELLE, N. Y.

Your TRIAD parts distributor can supply your TV replacement needs

with TRIAD'S complete line of television replacement transformers

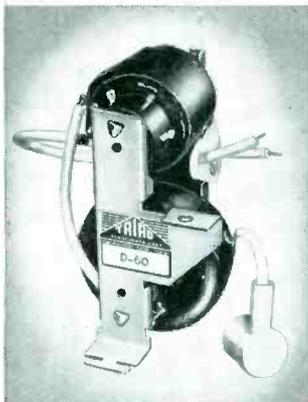*including these 5 new *correct replacements just added to the TRIAD line*



TRIAD
D-60
Zenith
*Correct
Replacement

- D-54 List Price \$6.50 *Correct Replacement for RCA 77833.
- D-57 List Price \$9.00 *Correct Replacement for Travler TV-X-107, 108, 110, 113, 114.
- D-58 List Price \$9.00 *Correct Replacement for Zenith S-21219.
- D-59 List Price \$9.00 *Correct Replacement for Zenith S-22154.
- D-60 List Price \$9.00 *Correct Replacement for Zenith S-22130.

TRIAD *CR (Correct Replacement) television transformers are mechanically and electrically correct ruggedized versions of mfr's items — and wherever possible COMPOSITE REPLACEMENT to fill a number of requirements where mechanical and electrical specifications are identical. All items are listed in Sams Photofact folders and Counterfacts.

write for Catalog TV-155L



4055 Redwood Ave. • Venice, Calif.



Components

C-D TUBULAR PAPER CAPACITORS

Polykane impregnated tubular paper dielectric capacitors, *Royal Cub*, designed for use under severe conditions of heat, cold, moisture and humidity, have been developed by Cornell-Dubilier Electric Corp., South Plainfield, N. J.

Units feature high insulation resistance, low power factor and a temperature range from -55°C to $+100^{\circ}\text{C}$. Available in .001 to 1-mfd capacitances and from 100 to 1000 *wvdc*.



* * *

G-C/STACKPOLE CARBON RESISTORS

Carbon resistors, in color-coded plastic boxes, have been announced by G-C Electronics Manufacturing Co., Rockford, Ill., and Stackpole Carbon Co., St. Marys, Pa.

The line, coded G-C 60, is available in assortments of six, four and three to a box in $\frac{1}{2}$, 1 and 2 watt types, respectively; in 77 RETMA values, with tolerances of 20%, 10%, and 5%.



Richard G. Ellis, vice president and general sales manager of General Cement and Dick Bond, distributor sales manager of Stackpole Carbon watching Russ Gawne, G-C electronics sales manager, demonstrate G-C/Stackpole carbon resistor jobber display. Looking on is Stanley B. Valiulis, G-C president.

* * *

CAPCON MINIATURE AND SUBMINIATURE CAPACITORS

A line of miniature and subminiature capacitors, for use in transistor assemblies, printed circuits, hearing aids, miniature radios and transmitters, and portable and color TV sets, has been announced by Capcon, Inc., 25 Willett St., New York 2, N. Y.



POCKET UTILITY PROBE

PR-200

- Series Filaments
- Parallel Filaments
- Electronic Components



\$3.25
LIST
Complete with Instructions

TUBE TESTER CONTINUITY TESTER

Rapid positive tests for SERIES and PARALLEL filaments in all types of TELEVISION, A.C.-D.C. RADIOS and PORTABLES. Tests all types of tubes, OCTAL, LOCTAL, 7 PIN MINIATURES, 9 PIN MINIATURES and CATHODE RAY TUBES. Continuity tests can also be made on all types of electronic components, appliances, electrical and automotive equipment. Unlike most series filament and continuity testers, the PR-200 Pocket Probe is designed to easily fit the serviceman's pocket and tool box. The PR-200 probe is entirely shock-proofed and utilizes any 110V. AC-DC line.

EBY SALES CO. of N.Y.
130 LAFAYETTE STREET
NEW YORK CITY 13, N. Y.

Coming Event

Hi-Fi Audio Show
February 8-11, 1956
Los Angeles, Calif.

don't just say capacitors

Ask For Sprague By Catalog Number

Know what you're getting . . . get exactly what you want.

Don't be vague . . . insist on

Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 61 Marshall Street, North Adams, Mass.

SPRAGUE

WORLD'S LARGEST CAPACITOR MANUFACTURER

ADVERTISERS IN SERVICE
OCTOBER, 1955

	Page
Aerovox Corp.	45
Alprodc Co.	33, 34
American Television & Radio Co.	66
Argos Products Co.	2
Arrow Fastener Co.	62
Atlas Sound Corp.	52
B & K Mfg. Co.	48
Blonder-Tongue Labs, Inc.	65
Bussmann Mfg. Co.	6
CBS-Hytron	39
Channel Master Corp.	7
Chicago Standard Transformer Corp.	44
Cornell-Dubilier Electric Co.	57
Crown Controls Co., Inc.	12
Delco Radio, Div. General Motors Corp. 13	
Eby Sales Co. of N. Y.	64
Electric Soldering Iron Co., Inc.	61
Electronic Publishing Co., Inc.	52
Electronic Test Instrument Corp.	63
Erie Resistor Corp.	56
Federal Telephone & Radio Corp.	46
The Finney Co.	37
General Cement Mfg. Co.	8
General Dry Batteries, Inc.	31
General Electric Co.	49
The Heath Co.	58
International Rectifier Corp.	66
International Resistance Co.	1
S. I. Jacobson Mfg. Co.	56
Jensen Industries, Inc.	50
Kester Solder Co.	50
P. R. Mallory & Co., Inc. Inside Back Cover	
Mosley Electronics, Inc.	60
Mueller Electric Co.	58
Ohmite Mfg. Co.	30
Oxford Electric Corp.	51
Permo, Inc.	52
Quam-Nichols Co.	53
The Radiart Corp. Inside Front Cover	
Radio Corp. of America .4, 19, Back Cover	
The Radion Corp.	3
Raytheon Mfg. Co.	16
Howard W. Sams & Co. Inc.	55
Simpson Electric Co.	14
Snyder Mfg. Co.	43
South River Metal Products Co.	60
Sprague Products Co.	50, 58, 64
Sylvania Electric Products, Inc.	5
Television Hardware Mfg. Co.	8
Transvision, Inc.	50, 59, 63
Triad Mfg. Co.	64
Trio Mfg. Co.	9
Tung-Sol Electric Inc.	10, 11
Winegard Co.	15

Catalogs - Bulletins

VACO PRODUCTS CO., 317 E. Ontario St., Chicago 11, Ill., has released a 4-page illustrated brochure listing gift-packaged, personalized tool sets available for use as promotional good-will builders.

GENERAL ELECTRIC EQUIPMENT CO., P.O. Box 347, Easton, Pa., has published a brochure, describing instruments and instrument kits that are available through distributors. Included are 'scopes, tube testers and multimeters.

EAGLE ELECTRIC MANUFACTURING CO., Inc., 23-10 Bridge Plaza South, Long Island City 1, N.Y., has published a 68-page catalog listing electrical wiring devices, extension and cord sets, fuses, wall plates, push buttons, flashing devices, nichrome wire and elements and staples.

NEWARK ELECTRIC CO., 223 W. Madison St., Chicago, Ill., and 4736 W. Century Blvd., Inglewood, Cal., has issued a 260-page catalog covering electronic parts, tubes, equipment, tools and accessories. Included is a 64-page section devoted to high-fidelity systems and components.

MERIT COIL AND TRANSFORMER CORP., 4427 N. Clark St., Chicago 40, Ill., has released an 80-page TV transformer replacement guide (No. 408), listing replacements for 12,000 models and chassis, cross referenced with original manufacturer's part number.

CHICAGO STANDARD TRANSFORMER CORP., Addison and Elston Sts., Chicago 18, Ill., has published a 52-page TV transformer replacement guide listing replacements for more than 7,000 models and chassis. Units are arranged in alphabetical order by set manufacturer.

ERIE ELECTRONICS DISTRIBUTOR DIVISION, Erie Resistor Corp., Erie, Pa., has issued revised catalog sheets covering fixed glass capacitors, midget rotary trimmers, and 4-w glass resistors.

GENERAL ELECTRIC CO., 1 River Rd., Schenectady 5, N. Y., has published a 10-page booklet, *Capacitors for the Electronics Industry*, (GED-2620) describing basic characteristics of specialty capacitors for use in electronic systems.

PRICE GUIDE



DAVE RICE'S OFFICIAL PRICING DIGEST (VOL. 1—No. 1): A resale pricing guide containing prices for over 60,000 replacement parts. Pocket-sized, with over 330 pages of consumer-price information. Will be revised every three months.—3 3/4" x 9 3/4", priced at \$2.50; *Electronic Publishing Co., Inc., 180 N. Wacker Dr., Chicago 6, Ill.*

ALL-CLEAR TV PICTURES

with the new

B-T LABS ANTENNA BOOSTER

(BROADBAND VHF)

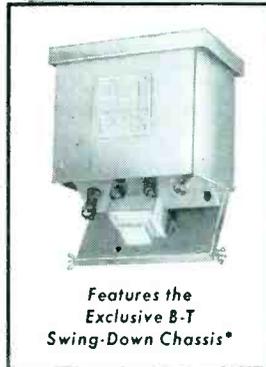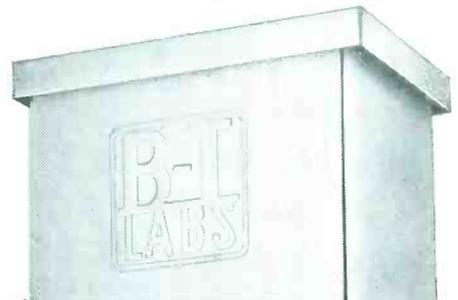

MODEL AB

4 TUBES
25DB
GAIN
\$95.00
LIST
WITH
MULTI
VOLTAGE
POWER
SUPPLY

Features the
Exclusive B-T
Swing-Down Chassis*

- Low-noise, all-triode circuit
- Easy mast-mounting
- Automatic 'on/off' from set
- 24 and 110v AC available plus step-ups for long-line drop
- Single lead line carries power 'up' and signal 'down'

• For Servicing and Maintenance . . . chassis swings down — trap door fashion — for easy handling and tube replacements.

For complete details, use this coupon



BLONDER-TONGUE LABORATORIES, INC.
Dept. GK-8 Westfield, New Jersey

Please send complete specs of your new Antenna Booster. I am also interested in:

- TV Amplifiers UHF Converters
 Master TV Systems


Name

Address

City Zone State

AMERICAN TELEVISION & RADIO CO. ST. PAUL, MINN.

introduces the
new

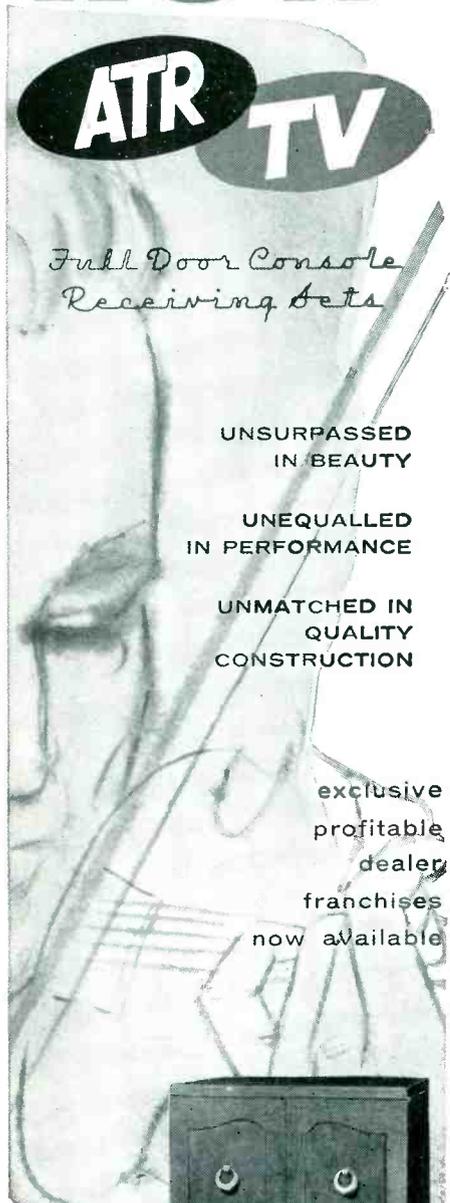

ATR TV

*Full Door Console
Receiving Sets*

UNSURPASSED
IN BEAUTY

UNEQUALLED
IN PERFORMANCE

UNMATCHED IN
QUALITY
CONSTRUCTION

exclusive
profitable
dealer
franchises
now available



*designed
with the
Serviceman
in mind
... easy to
get at*

WRITE TODAY FOR COLORFUL
BROCHURE SHOWING THE
NEW LINE OF ATR TV SETS

ALSO MANUFACTURERS OF DC-AC INVERTERS,
"A" BATTERY ELIMINATORS, AUTO RADIO VIBRATORS

ATR AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA-U. S. A.

JOTS AND FLASHES

DESIGN TECHNIQUES that will help curb interference from high-power fixed radio transmitters serving mobile units, which occasionally affects TV set performance in certain metropolitan areas throughout the country, are now under study by set manufacturers, employing test facilities of RCA. The tests are expected to reveal whether production models meet standards necessary to discriminate against the radiating signals, or what additional shielding may be required to provide adequate discrimination. Set performance data will be compiled and submitted to RETMA who will prepare a report for the FCC for its information and possible guidance on an interference ruling. . . . Colonel Richard H. Ranger has been elected president of the Audio Engineering Society, succeeding Albert A. Pulley of RCA. Walter O. Stanton, Pickering Co. proxy, has been named executive vice president. . . . Elgin National Watch Co., has established warehouse and distribution facilities at Elgin, Ill., for mid-west and eastern distributors handling products of American Microphone Co., and Advance Relay Co., of Pasadena and Burbank, Calif. . . . As a part of a program for the accelerated production of color TV picture tubes, RCA has completed arrangements to purchase an additional 285,000 square feet of building space at Lancaster, Pa. . . . Service Instruments Co., has moved from 422 S. Dearborn St., Chicago, to 171 Official Road, Addison Industrial District, Addison, Ill. . . . Times Wire and Cable Co., Inc., has moved its offices and manufacturing facilities to Hall Ave., Wallingford, Conn. . . . The United Transformer Co., has opened a west coast plant at 4008 West Jefferson Boulevard, Los Angeles, Calif. . . . Gramer Yarbrough, sales manager of American Microphone Co., will head the committee for the '56 Los Angeles High Fidelity Music Show, which will be held February 8-11, and will be jointly sponsored by the Institute of High Fidelity Manufacturers and the West Coast Electronic Manufacturers Association. . . . S. Prall Culviner has joined the public relations department of Sylvania Electric Products, Inc., 1740 Broadway, New York 19, N. Y., as a project manager. . . . G. Leonard Werner has been appointed director of sales of Astatic Corp., Conneaut, Ohio. . . . John P. Yohe has been named director of purchases. . . . John L. Bradley has been appointed assistant manager of advertising and sales promotion of Ampex Corp., Redwood City, Calif. . . . John F. Glump has been elected sales and advertising vice president of Viking Instruments, Inc., East Haddam, Conn. . . . Richard Johnson has been promoted to manager of the Syracuse sales office of International Resistance Co. Thomas E. Davis is now on the office sales staff. They will cover the New York State area, excluding N. Y. City.

INTERNATIONAL'S

NEW
TV RECTIFIER
REPLACEMENT
BONUS
PACK!



FREE!

NYLON TV TOOL

With every pack of 4 TV
Selenium Replacement Rectifiers...
A PAIR and a SPARE PAIR!

You can't miss with International's New "BONUS PACK"! You'll get the *best* in TV replacement rectifiers. Each BONUS PACK contains a pair for immediate use, and a spare pair for your next job—PLUS a Nylon TV Alignment Tool worth \$1.00—ABSOLUTELY FREE!

SPECIFY INTERNATIONAL RECTIFIERS for long, dependable performance—the Widest Range in the Industry! Best for you... Best for your service customers!



Ask your distributor
for details about
"Bonus Pack" today!

**International
Rectifier**

C O R P O R A T I O N

1521 East Grand Avenue, El Segundo, California • ORegon 8-6281
IN CANADA: Atlas Radio Corp., 50 Wingold Ave. W., Toronto, Ontario

**WORLD'S LARGEST SUPPLIER
OF INDUSTRIAL METALLIC RECTIFIERS**

P. R. MALLORY & CO. INC.
MALLORY

P. R. MALLORY & CO. INC.
MALLORY
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. INC.
MALLORY
APPROVED PRECISION PROD



Dr. FIXIT,
BA,
MSR,
DSIP*

It takes a highly educated, thoroughly trained technician to capably test and repair that amazingly complicated mechanism of your TV set. As a result, the successful TV serviceman has to invest plenty of time, money and effort in order to gain the "know-how" to do his job well. Then, to use his training and skill to the best advantage, this expert needs the finest tools, instruments and parts available. Aware of that, many servicemen use Mallory precision built electronic components—Resistors, Capacitors, Rectifiers, Controls.



AERIAL CIRCUS

At last all you're liable to get from a solo antenna-adjusting expedition is a better view of the neighborhood! That's a job for an expert—a man who knows your television set inside and out. He's your TV serviceman—the fellow who has spent plenty of time and money learning to do everything from tracing intricate circuits to adjusting your antenna just right for good reception.

He's selective in his choice of tools and equipment, too. To make sure you get the best possible results from repairs to your set, many servicemen use Mallory precision-built Controls, Resistors, Capacitors, and Rectifiers.

When you see your serviceman using Mallory parts, you can be sure he is providing you with the finest... they are the same Mallory precision parts used by most TV set manufacturers.

P. R. MALLORY & CO. INC., INDIANAPOLIS 6, INDIANA

P. R. MALLORY & CO. INC.
MALLORY

MISSING UHF PROGRAMS?
Make your present set an all-channel receiver with the Mallory UHF Converter. Its performance has been proved in every UHF area. Call your serviceman or TV dealer.

How Mallory Does A Selling Job For You...

Right in Your Customers' Homes

MORE than three million readers of TV GUIDE will see ads like these again this year—ads that sell your specialized abilities and experience to your customers and prospects.

You can count on Mallory for this extra sales support just as you can count on Mallory precision electronic components for the kind of dependable performance that keeps your customers satisfied.

You can count on Mallory . . . always!

NEW... For Your Shop

We have prepared a colorful counter display card based on the Mallory TV Guide advertising—your advertising. You may obtain this display card by writing Mallory, P. O. Box 1558, Indianapolis 9, Ind. Enclose 25c for postage and handling.



P. R. MALLORY & CO. INC.
MALLORY
APPROVED PRECISION PRODUCTS


P. R. MALLORY & CO. INC.
MALLORY
APPROVED PRECISION PROD

P. R. MALLORY & CO. INC.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

How to "tame" a TV Sync Circuit *FAST*

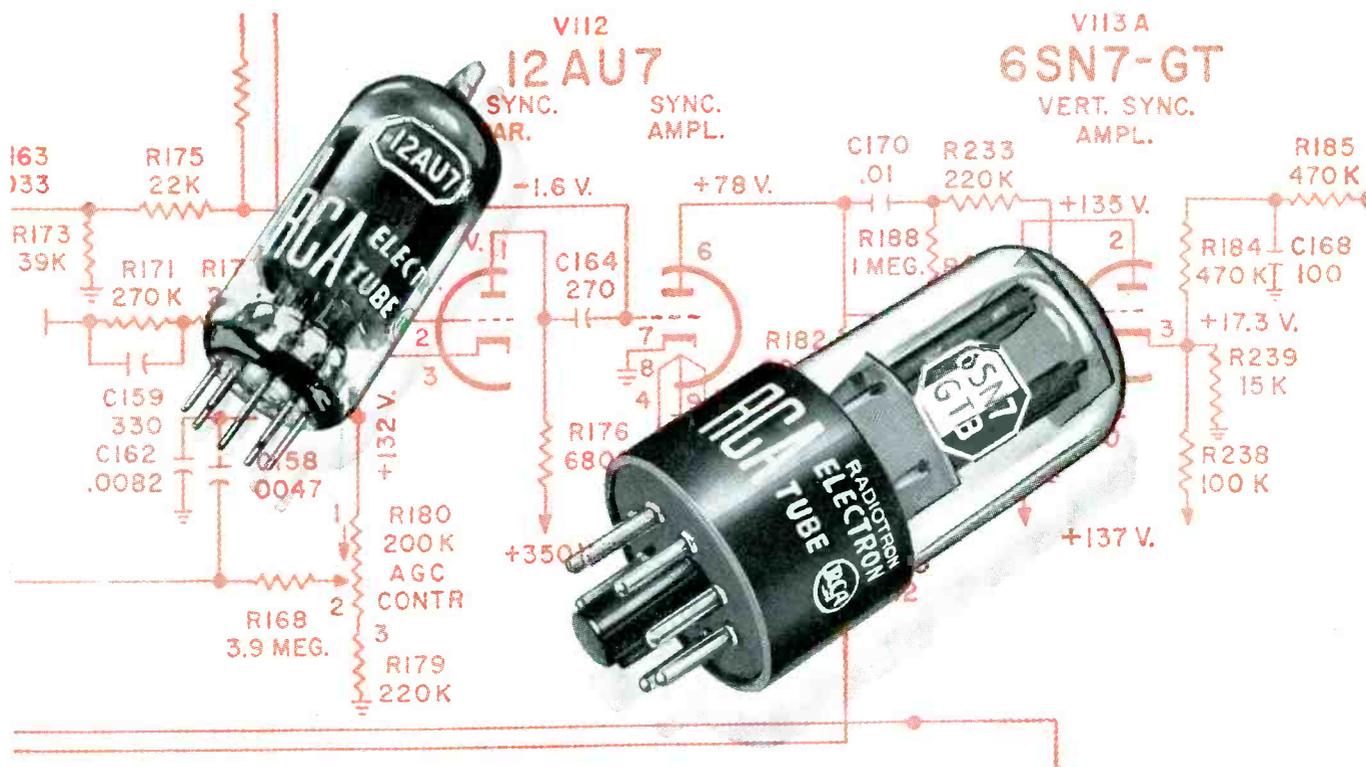


Use RCA Tubes with Built-In Quality!

For instance, RCA-12AU7's and 6SN7-GTB's are known for their close manufacturing tolerances. Microphonics are minimized. Plate current cutoff is closely controlled. Result: High tube stability—even during variations in heater voltages!

It's a fact—you can rely on RCA Tubes to give your customers stable TV pictures. That's because RCA Tubes are designed and manufactured specifically to meet the close tolerance requirements of TV circuitry.

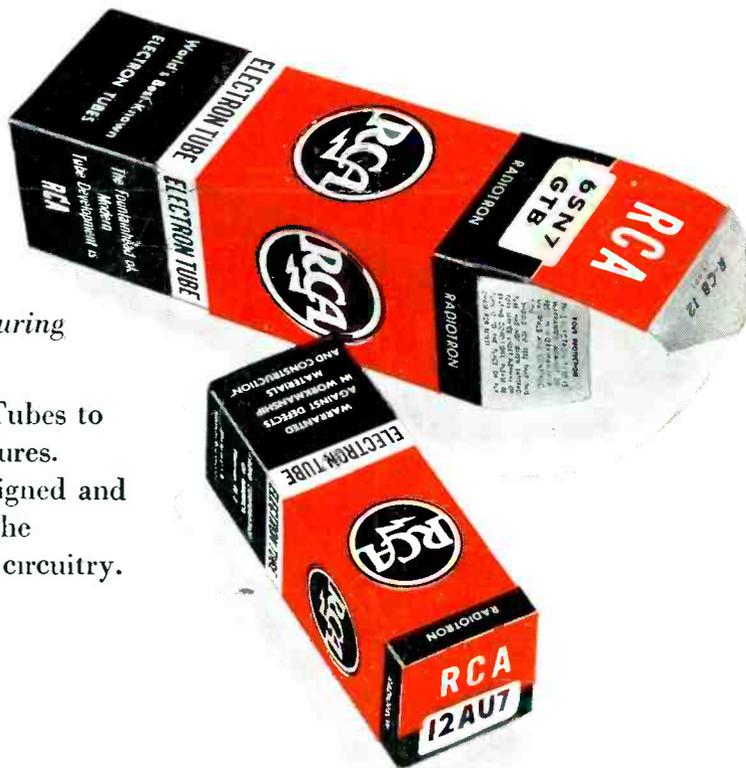So, insist on RCA Receiving Tubes for *all* your service work.



RADIO CORPORATION of AMERICA
ELECTRON TUBES

HARRISON, N.J.

First Choice for TV Circuits... dependable RCA Tubes