



Before you send your next order to us by post, take a look and see if there's a Maplin shop near you. In our shops you'll find that personal service that even the best mailorder operations cannot match. And you can look at the products before you buy. If you're coming for a particular item, a quick phone call will enable you to be certain the shop has everything you want in stock.

Our shops are pleased to accept Access, Barclaycard, American Express and Mapcard, and also cheques up to £50 with a cheque guarantee card. We'll even accept ordinary money as well!

All our shops are close to excellent parking facilities, meters in London and Manchester, and free elsewhere.

The South

In the South our Southampton store is conveniently placed for easy access from all parts of Hampshire and surrounding counties and is just 15 minutes from Portsmouth.

London

Our London store situated just to the west of the pedestrian shopping centre in Hammersmith, is just 5 minutes from the end of the M4 and only a short walk from the District, Piccadilly and Metropolitan lines' Hammersmith station.

The Midlands

In the Midlands our Birmingham store is just 5 minutes from the M6 on the A34, and only a little farther from the M5 (junction 1) on the A4040.

The North

Our self-service store in Manchester serves the North and is just off the Mancunian Way, opposite the BBC, about 5 minutes from the end of the M602 or junction 10 on the M63.

South-East

Essex and Kent are served by our

Southend shop which is right on the A13, just 2 minutes before you reach the centre of Southend. And we're only 30 minutes from the M25 (junction 29) as well.

All our shops are open from 9 a.m. to 5.30 p.m. Tuesday to Saturday (closed all day Sunday and Monday) and do *not* close for lunch.

There's a friendly welcome in store for you at any Maplin shop. Our helpful staff may often be able to help with a technical problem or a constructional difficulty.

Call in at a Maplin store and get what you want today. We look forward to serving you. Volume 5 Number 20



PROJECTS

Weather Satellite Decoder.....




The second item of equipment for the Weather Satellite receiver system is the Decoder which enables the satellite picture to be displayed on a monitor by a home computer, from either a signal being directly received by the Receiver. or from a recording on cassette.

Infra Red Proximity Defector 20




An infra red heat detector specialising in short range applications. It will serve as a detector guarding doorways and corridors, etc. Ideal as a heat or movement detector where coverage of room sized areas is not required.

Fibre-Optic Audio Link..... 37

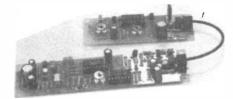

Uses special on-board sending and receiving devices to transmit AC signals in the audio band along up to 20 metres of fibre-optic cable. Separate Transmitter and Receiver boards are used for coupling remote items of equipment. Although the project is aimed at educational and experimental applications, it may prove invaluable, for example, in electrically noisy environments.

Amstrad 8-Bit Input Port.. 48

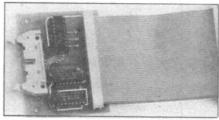

A simple 8-bit parallel input port for use with the CPC 464, and 664 and 6128 range of Amstrad computers. Can be used to interface to the Weather Satellite Decoder also in this issue.

Low-Z Microphone Preamplifier 54

For 200 Ω to 600 Ω impedance balanced or unbalanced microphones. The screened module also includes gain adjustment.

FEATURES




The newcomer to electronics cannot fail to have noticed the bewildering variety of different shapes, colours and specifications of all the range of capacitors available - even if they do happen to be of the same value. Why should the construction and composition of the different types, ostensibly so similar in value and voltage rating, be so diverse? Be prepared for some surprises . . .

Mains Power Control with TRIACS 24

The TRIAC has effectively revolutionised AC power control in recent times. However, powerful as these devices may be. they are not infallible. Before attempting to design such a control system some fundamentals have to be worked out first to ensure safe operation. This article presents a detailed insight into the internal workings of the modern TRIAC.

The Story of Radio 44

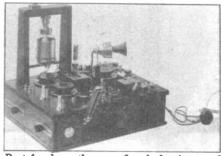

Part 4, where the new-fangled science of the invisible rays quickly came of age during the Great War. Those involved in other similarly fast growing technologies. aviation for example, took to it immediately, as did the Royal Navy for whom it was to become a valuable and indispensible tool. Traditionalists couldn't, or wouldn't, understand how it could be properly used.

Test Gear and Measurements 50

Part 2 continues this series with some indepth studies of how errors and tolerances are negated when taking measurements of real electrical properties. The principle of the measurement bridge circuit illustrates its wide range of applications.

Machine Code Programming with the Z80 59

Part 4 of this series describing the instructions for the ubiquitous Z80 CPU continues with conditional jumps, conditional calls and returns from subroutines, restarts, interrupts and the control group.

REGULARS

the state of the s	
Catalogue Amendments	34
Classified Advertisements	64
Corrigenda	29
Project Servicing Rules	64
New Books	
Order Coupon	
Price Changes List	31
Price List of Items Since Catalogue	30
Subscriptions	36
Top 20 Books	30
Top 20 Kits	29
Voyager Competition Results	58

Mail Order

P.O. Box 3, Rayleigh, Essex SS6 8LR. Telephone: Retail Sales: (0702) 554161. Enquiries: (0702) 552911. Production Manager Trade Sales: (0702) 854171. Enquiries: (0702) 862961. General: (0702) 554155. Cashtel: (0702) 552941.

Shops: See inside front cover. All shops closed Mondays.

Editorial & Production

Editor Technical Editors **Art Director Art Assistant Technical Artists**

Secretary

Roy Smith Mike Holmes Robert Kirsch, Dave Goodman Peter Blackmore

Great Buckley John Dudley, Lesley Foster Angela Clarke

Published by Typesetting by

Printed by

Distributed by


Maplin Electronic Supplies Ltd. Essex Process and Engraving Co. Graphic House, Stock Road, Southend-on-Sea, Essex. Mayhew McCrimmon Ltd. Star Lane, Great Waltering, Essex. Spotlight Magazine Distribution Ltd., 1-11 Benwell Rd, London N7.

Copyright. All material is subject to world wide copyright protection, and reproduction or imitation in whole or part is expressly forbidden. All reasonable care is taken to ensure accuracy in preparation of the magazine, but Maplin Electronic Supplies Ltd. cannot be held legally responsible for its contents. Where errors occur corrections will be published as soon as possible afterwards. Permission to reproduce printed circuit board layouts commercially or marketing of kits must be sought from the publisher.

© Copyright 1986 Maplin Electronic Supplies Limited.



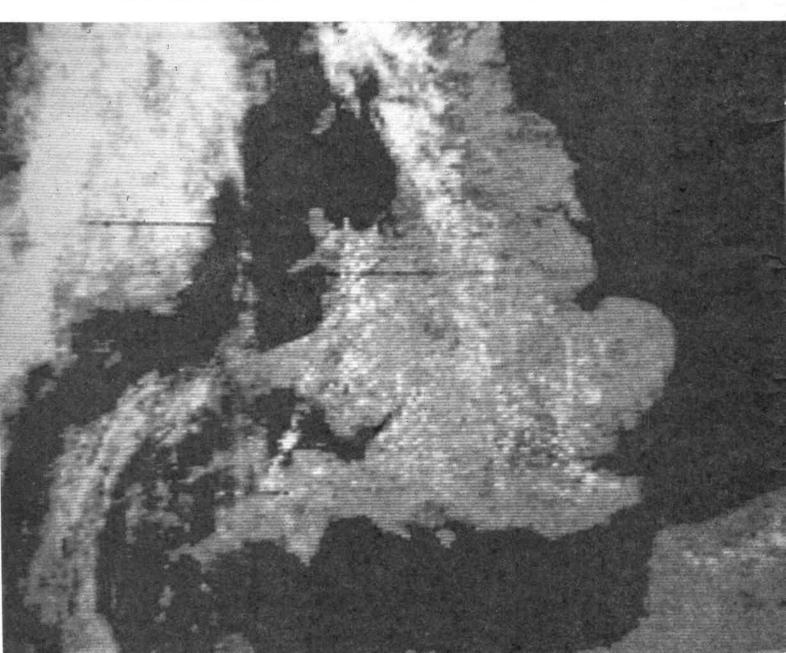- * Full 8-bit Digital Output
- * Picture Slip Control
- * Black and White Level Controls
- * Input Level Meter
- * Peak White and Black Indicators
- * Optional Line Sync Card
- * Sync Timing for TIROS Satellites Provided
- * Programmable Sync Cards for Other Satellites
- ★ Bullt-in Power Unit (Also Supplies Receiver)



SATELLITE DECODER

by Robert Kirsch Part 2

The Decoder


This article describes the Decoder needed to demodulate the APT (Automatic Picture Transmission) signals transmitted from most of the orbiting and geostationary weather satellites. These signals can be received using the Receiver described in Part 1 of this series.

The Decoder accepts audio signals either from tape or directly from the receiver and converts them into an 8-bit digital format with necessary synchronising pulses for connection to a suitable computer or frame store for display on a television or monitor. Controls are provided to enable the contrast of the picture to be adjusted and various types of synchronisation may be selected to suit different satellites. Power for the decoder comes from an internal power unit which will also supply the receiver.

The APT Format

Pictures transmitted by most VHF
American and Russian orbiting weather
satellites, as well as WEFAX transmissions from the GOES series satellites (e.g.
ESA METEOSAT 2), use the APT format.
The radio frequency carrier is frequency
modulated by a 2.4kHz subcarrier whose
amplitude is modulated by the picture
information and synchronising signals.
Figure 1 shows the subcarrier envelope
for a typical line of APT information.

Peak white, it will be noted, corresponds to maximum subcarrier level, and black to the minimum. Picture lines are transmitted either 2 or 4 times a second, each line having 600 cycles of subcarrier, thus the maximum horizontal definition is 600 pixels. The TIROS satellites send alternate lines of infra-red and visible information (when viewing the Earth in daylight) each line being preceded by synchronising pulses. Channel 1 (visible) sends 7 pulses at 1040 pulses per second and channel 2 (infrared) sends 7 pulses at 832 pulses per second. Meteosat sends 7 pulses at 840 pulses per second at the start of every line, as well as a 300 pulses per second start and a 450 pulses per second stop signal for frame synchronisation.

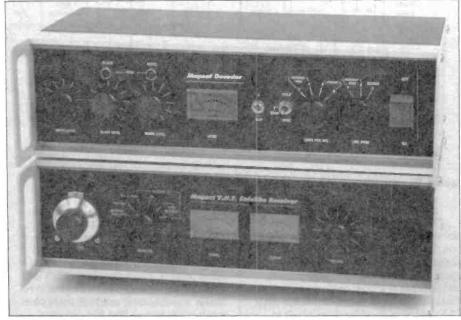

Decoder with the Receiver

The Russian Meteor satellites send approximately 2 lines per second with a synchronising tone of 300Hz for every line. The decoder described in this article produces line synchronising pulses by dividing the 2.4kHz subcarrier digitally, using a programmable divider to obtain the correct periods for various types of satellites. These pulses may be manually adjusted to correctly position the picture on the screen. (When using the optional sync tone decoder card this is achieved automatically.)

Circuit Description

Figure 2 shows a block diagram of the decoder, synchronising unit and power supply. Figure 3 shows the circuit diagram for the main circuit board. Live or recorded signals, selected by the receiver, enter via the 6-pin DIN socket and are first fed to a master level control. The signal at this point splits into three paths; the first goes to the A/D converter, the second to the Level Meter and AM detector circuit, and the third to the Phase Locked Loop carrier regeneration circuit.

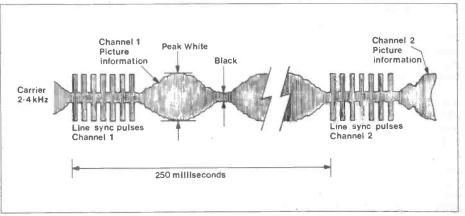


Figure 1. Typical APT information.

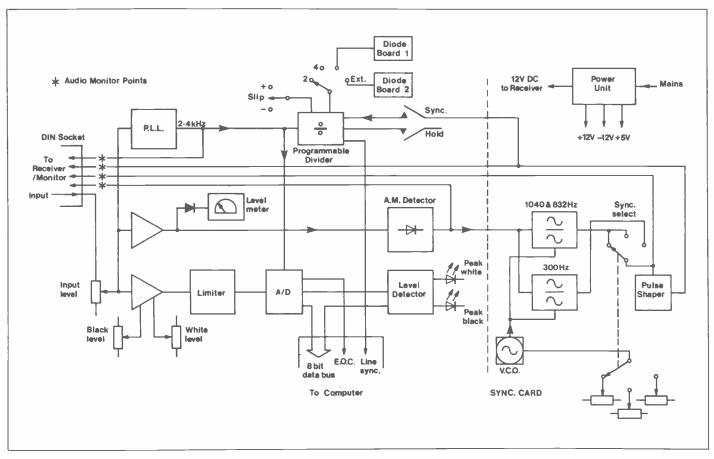


Figure 2. Decoder Block Schematic.

The conversion from the analogue subcarrier level to a digital code is accomplished by IC2, an 8-bit A/D converter. This device requires two inputs, one is the analogue information, and the other is a 'start conversion pulse'. The analogue input range of IC2 is from 0 to 2.5 volts to give codes from black to peak white. It is therefore important to adjust the level of the incoming signal in order to obtain correct contrast on the displayed picture. This function is provided by the op-amp ICla. The gain of this device is adjusted by RV5 in the feedback circuit, this sets the white level. The output from ICla is about ± 2.5 volts but only the positive half cycle is fed to the A/D converter. RV4 sets the DC reference of the op-amp, and this offset is used to adjust the black level of the picture. Note, there is always a small amount of carrier at black level for synchronising purposes, so this circuit enables this level to produce true black on the display. The black and white level controls may also be used to enhance pictures particularly when only a few grey levels are available from the computer or frame store used.

The two light emitting diodes LED1 and LED2 are used to obtain the correct setting for the black and white level controls. The most significant bit from the output of the A/D converter is monitored and, when this bit goes high, TR2 turns on and causes LED2 to light, this indicates a level approaching peak white. All 8 bits are fed to the NOR gate IC5. When all 8-bits are low the output of this gate turns

TR1 on, causing LED1 to light and indicate black level.

The second op-amp, IClb, is fed with the incoming signal via the input level control. The output from IClb is rectified by D3 and D4 to drive the level meter which should read full scale on a peak white signal. The AM detector formed by D1 and D2 is also fed from the output of IClb and this audio signal is fed to the sync tone decoder card.

The phase locked loop, IC3, is fed with the incoming modulated signal and locks to the 2.4kHz subcarrier. The clean square wave output produced is used to generate the 'start conversion' pulse for the A/D converter and it is also fed to the programmable divider to produce line synchronising pulses.

The three counters IC6, 7 and 8 form the programmable divider whose division ratio is set by the data on pins 3, 4, 5 and 6 of each IC. The rotary switch S2 selects one of two preset ratios (1200 for 2 lines per second and 600 for 4 lines per second) and also two ratios that may be set by programming the optional diode cards, the circuit of which is shown in Figure 4. The SLIP control S3, temporarily raises or lowers the division ratio to enable the picture to be moved in relation to the line sync pulse thus shifting the display left or right in relation to the television screen. The phase locked loop will produce an output even when no input is present, and therefore line sync pulses will also occur. For this reason the HOLD switch is provided to stop the


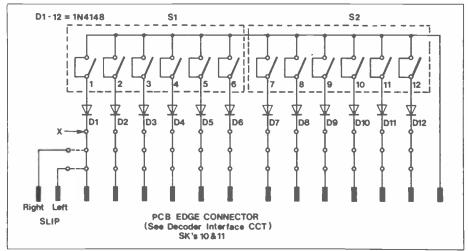


Figure 4. Diode Card Circuit.

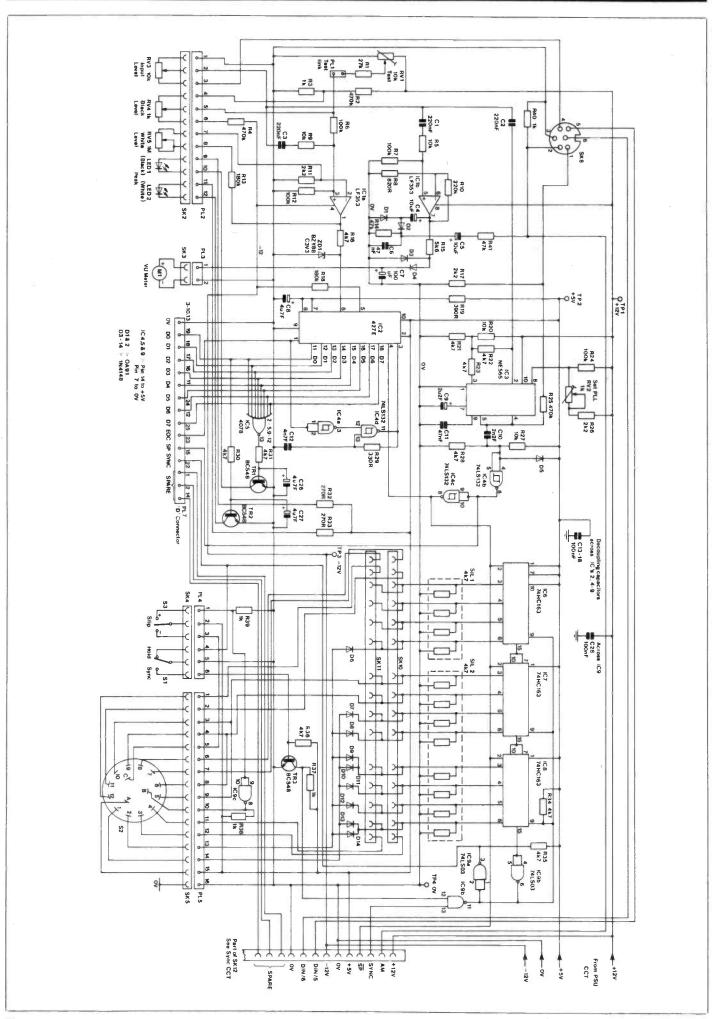


counter, thus preventing the current picture from being lost.

Four audio monitor points in the decoder are connected back to the receiver in order to help in setting up and testing. One of these is connected to the 2.4kHz output from the phase locked loop and another to the output of the AM detector. The remaining two monitor points coming from the optional sync tone card.

The preset RV1, along with the TEST LINK are provided to help in testing and setting up the A/D converter, computer hardware and software. This potentiometer provides an adjustable source of voltage to the input of IC1a which will simulate signal levels from black to peak white.

Sync Tone Card

This card is used to detect the line synchronising tone at the beginning of each picture line. Figure 5 shows its circuit, and it will be noted that a MF10 switched capacity filter (IC2) is used to select the tones. The frequency of this type of filter is determined by the frequency of the oscillator fed into pins 10 and 11 of the IC, in this case it is 100 times the required filter frequency. The two separate halves of IC2 have different bandwidths for optimum reception of different types of sync tones. The

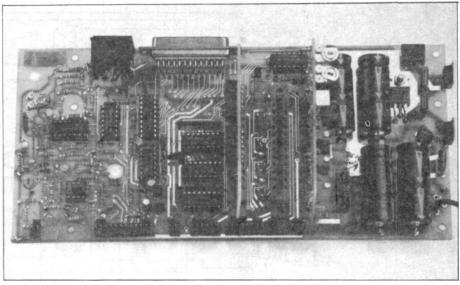

Decoder Board

frequency of the voltage controlled oscillator, IC1, is controlled by the three multi-turn potentiometers RV3, 4 and 5 which are selected by S4 on the front panel.

The input level of IC2 is preset by RV1 and RV2, and the filtered output is buffered by TR1 and TR2. TR3 with D1, 2 and 3 form a threshold switching circuit whose output is used to reset the divider on the main board when the LINE SYNC switch is operated.

Construction

Referring to the Parts list and component overlay on the three circuit boards, Figure 6 shows the legend of the main decoder board, Figure 7 gives the tracks and overlay of the Sync tone card, as does Figure 8 for the Diode board; insert and solder all components in the following order: fixed resistors, capacitors, diodes and bridge rectifier, SIL resistors, IC holders, transistors and regulator IC's; veropins, preset resistors

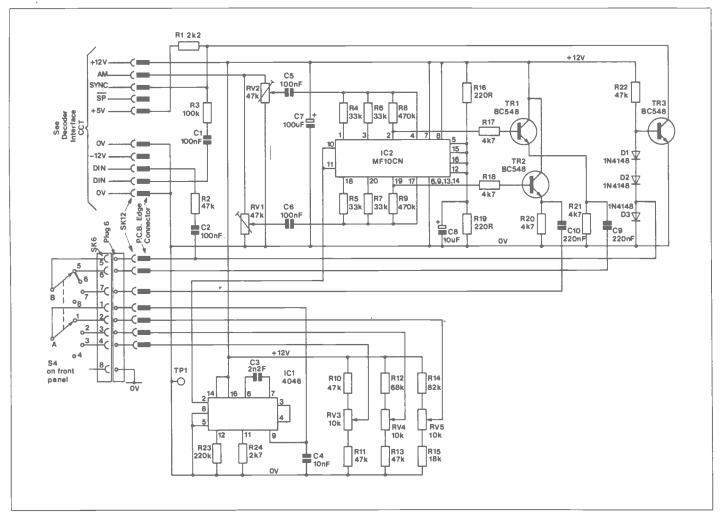


Figure 5. Sync Tone Circuit.

and finally plugs, sockets and edge connectors. **NOTE** - observe the correct polarity of transistors, regulators, diodes, LED's, meter, electrolytic capacitors and the bridge rectifier. The white dot marked at one end of the SIL resistor package should correspond to the white dot on the board overlay. The tags of the Minicon plugs should be to the rear of the circuit board. The white rings on the overlays indicate where the boards should be soldered on both sides; in addition TR1 on the sync card should be soldered on both sides also.

Insert the keys into the edge connectors, referring to the wiring diagram Figure 9. Carefully insert all integrated circuits into their correct holders ensuring that pin 1 marked on the board aligns with pin 1 of the IC. Carefully fit the clip-on heatsink to REG2.

Use the stick-on front panel as a template to mark out the front plate of the box, before drilling and cutting out, see Figure 11. Remove the protective backing from the front panel and carefully position it on the prepared front plate, pressing down evenly all over, making sure there are no air bubbles trapped underneath. Mount all controls and switches on the front panel. Referring to the wiring diagram Figure 9, connect all level controls, toggle and rotary switches, LED's and the meter to their appropriate Minicon housings via the ribbon cable provided, allowing approximately 5 inches of cable from each housing to the front panel. Note that the Minicon housings will have their lugs towards the rear of the circuit board when installed. (Refer to the Receiver article for details of how to make terminations to the Minicon connectors, Maplin Magazine Issue 18.)

Mount the toroidal transformer with the rubber washers provided on either side and place a solder tag under the fixing screw, the PSU circuit is shown in Figure 10. Insert the rubber grommet into the hole in the transformer bracket and pass the red, blue, grey, and yellow wires from the transformer through the grommet. Referring to Figure 11, mark and drill the base plate and mount the transformer bracket, placing the mains label in a visible position on this bracket. You can make your own bracket if you wish according to the dimensions shown in Figure 12. Drill and cut out the rear plate of the box and mount the fuseholder. (Check that when the case is finally assembled, the fuseholder tags will be clear of any obstructions.)

Pass the mains cable through the strain relief grommet and then through its hole in the rear plate and secure grommet in position, then refering to Figure 9, connect the brown wire via the fuseholder to the mains switch. The blue wire connects straight to the mains switch and the green/yellow wire to the earth tag under the transformer mounting screw. Terminate the two orange primary wires from the transformer at the




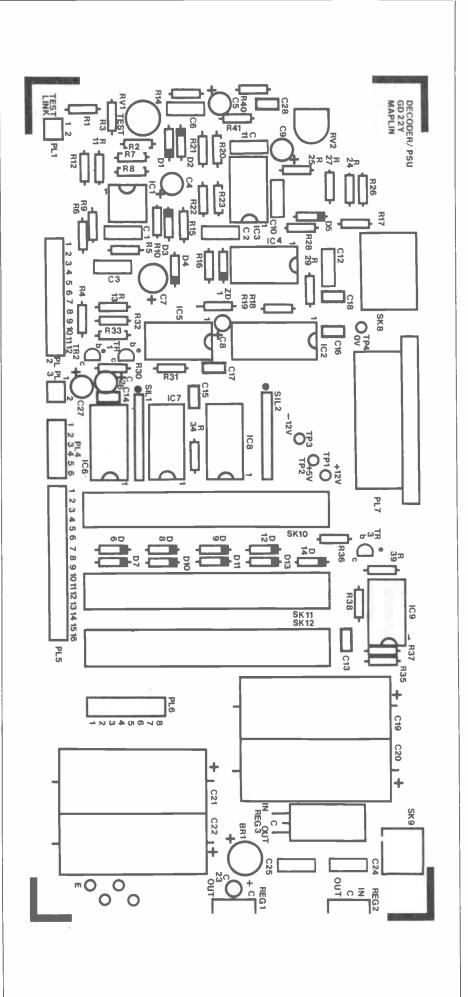


Figure 6. Decoder PCB Overlay.

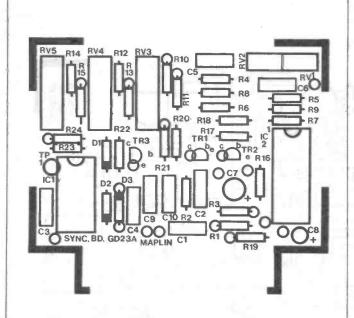

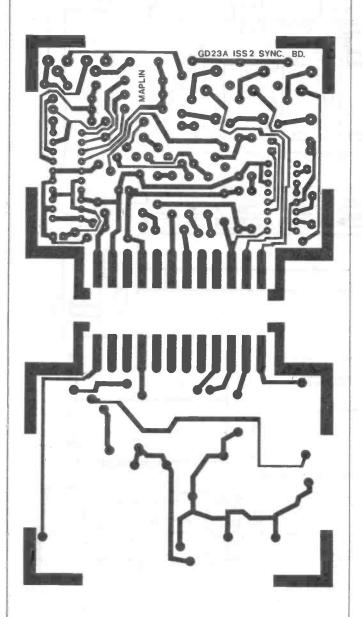

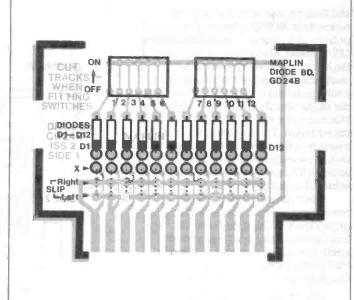


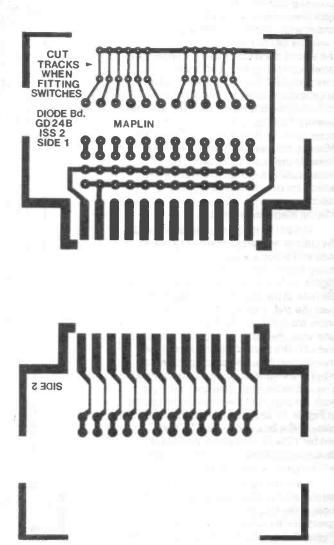


Figure 7. Sync Tone Tracks and Overlay.

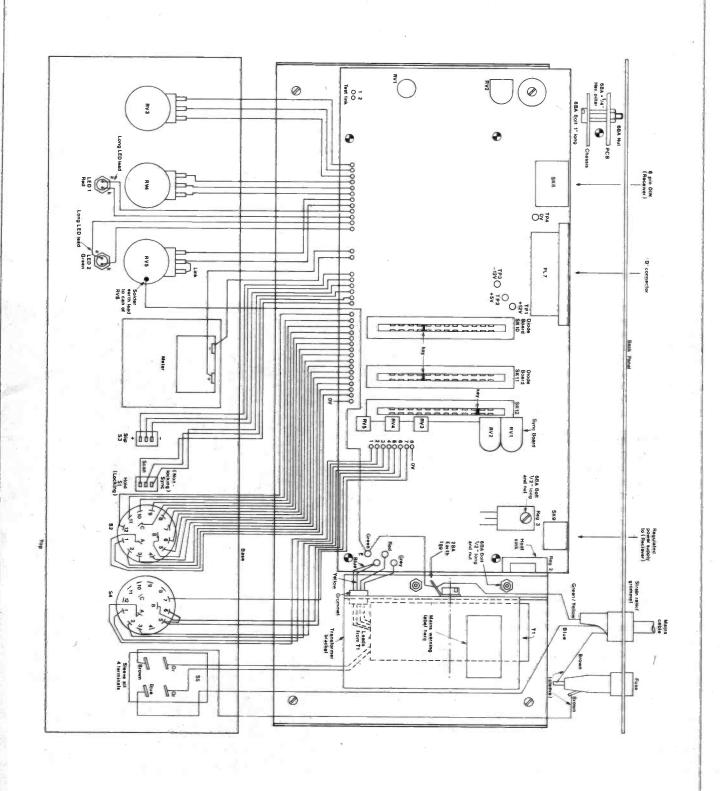

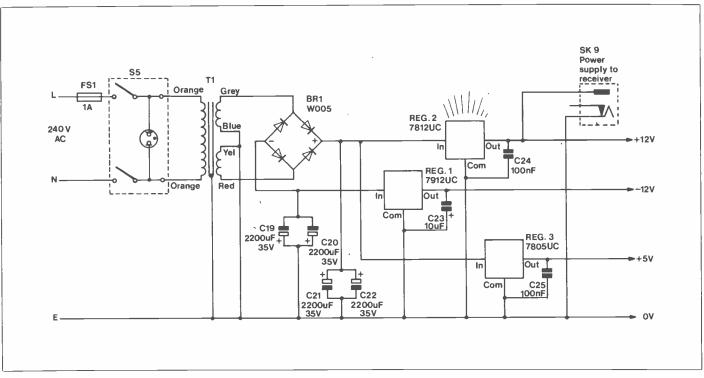


Figure 10. Power Supply Circuit.

mains switch. Insulate all exposed mains connections. Fix the main circuit board to the base plate, and solder the transformer secondary wires onto their respective pins.

The case may now finally be assembled and the front panel connectors plugged onto the circuit board. The decoder is now ready for testing.


Setting-Up and Testing

warning - Take care when working on the decoder with the mains supply connected. NOTE - Do not connect the computer, framestore or receiver until the following tests have been carried out.


Set all three front panel level controls anticlockwise. Insert the 1 Amp fuse and connect the Decoder to the mains supply. Switch on. The mains indicator light in the power switch should glow and the red 'Peak Black' LED should be illuminated. Using a suitable multimeter check the power supply outputs at the test points provided to obtain the following readings (to within ±0.5 volts). All readings are relative to 0 volts (TP4) or chassis. TP1: +12 volts, TP2: +5 volts, TP3: -12 volts.

If these readings are correct, connect the Decoder to the parallel I/O port of the computer/framestore and run the appropriate software. (When using the Amstrad or BBC software provided in this article, set the horizontal resolution to 4.) Set the TEST preset (RV1) fully clockwise and the sync switch to SCAN. The lines per second switch should be set to 2. Join the two TEST LINK pins (PL1) together and note that the 'Black Peak' LED remains alight.

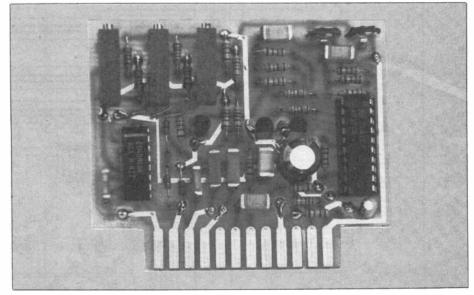Slowly rotate the TEST preset anticlockwise whilst observing the monitor screen. The brightness of the scan lines moving up the screen should be seen to



Sync Tone Card

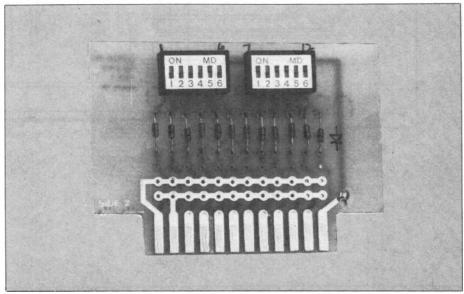

Diode Board


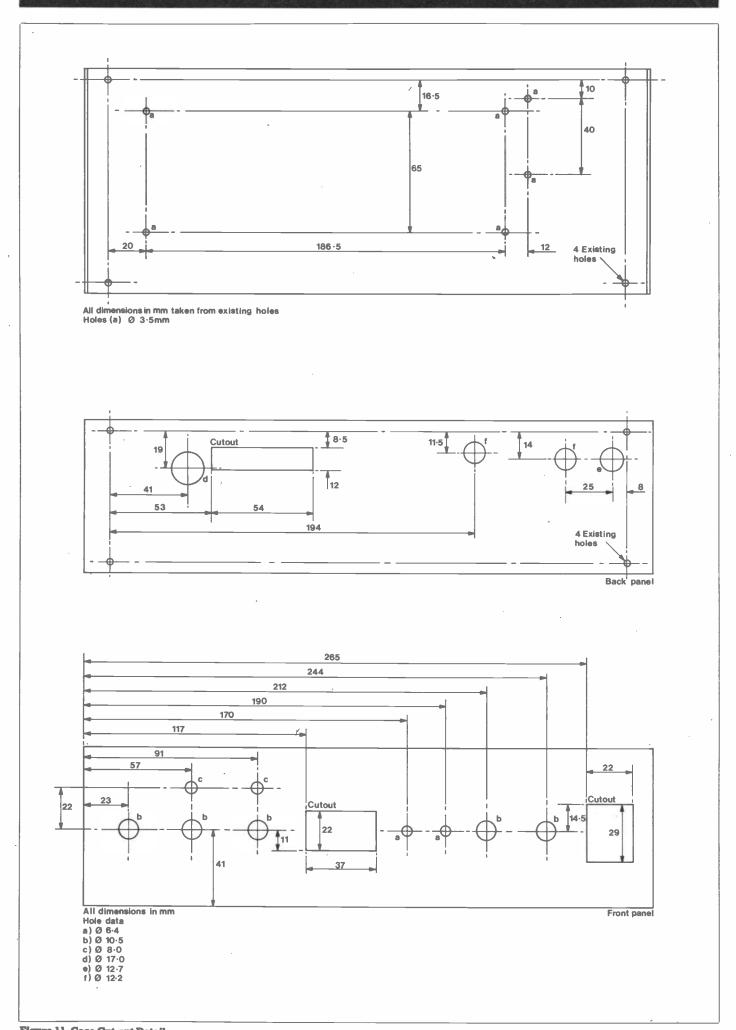


Figure 11. Case Cut-out Details.
September 1986 Maplin Magazine

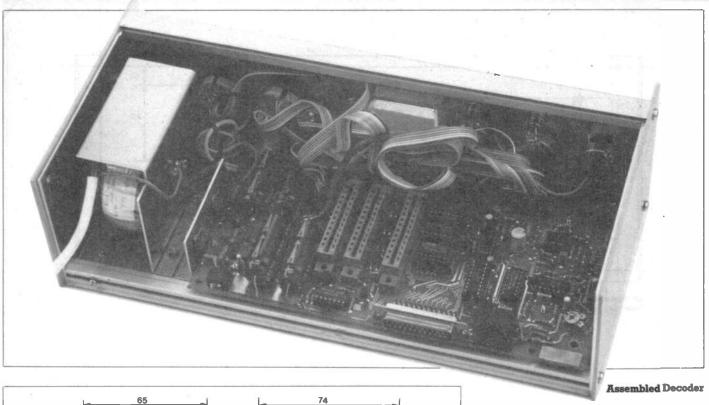

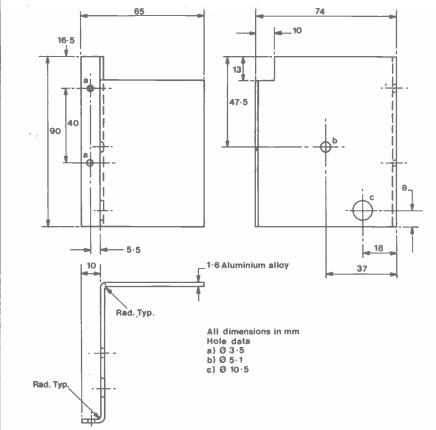


Figure 12. Transformer Bracket.

Sync Tone Switch Position	Frequency of Tone	Frequency at TP1 of Sync Tone Card
TIROS 1 (Channel A)	1040Hz	104 kHz
TIROS 2 (Channel B)	832 Hz	83·2 kHz
METEOR	300Hz	30 kHz

Figure 13. Sync Card Frequency Settings.

progressively increase as the control is rotated. Repeat this test and note that the 'Black Peak' LED goes out before the first grey level appears on the screen and that the 'White Peak' LED comes on as the maximum white is approached. When the full number of crev levels appear on the screen move the scan switch to 'HOLD' (this should stop the picture being scanned) and check that the correct number of levels appear on the screen depending upon the type of display system in use. (The Amstrad and the framestore should produce 16 levels including black and white, and the BBC 8 levels including black and white). The "TEST" link pins may now be disconnected.

The following tests should be carried out by using a good quality recording of the NOAA 6 or NOAA 9 satellites. Connect the Decoder to the Receiver via the 6-way audio DIN lead and the power lead. Connect the tape recorder to the Receiver, referring to the previous article (Issue 18). Play the recording of the satellite. Select TAPE, OUT on the MONITOR switch of the Receiver and adjust the VOLUME to a comfortable level. Set the Decoder INPUT LEVEL control to minimum. Switch between TAPE OUT and PLL on the MONITOR switch, and adjust the preset RV2 on the Decoder board until the tone from the PLL is the same as that of the satellite's subcarrier.

To check this setting, the INPUT LEVEL may now be increased and the Black Level' LED should now flash or go out. Check that the LEVEL meter responds as the INPUT LEVEL control is increased.

The basic Decoder is now ready for use but if the sync tone card has been installed the following setting-up is

required. The three multi-turn presets on the tone card are best adjusted using a frequency counter, with reference to Figure 13. Where no frequency counter is available, this adjustment may be carried out by using the audio monitor test points provided in the Receiver unit in the following manner.

When playing a recording of the NOAA satellites, the characteristic 'clip-clop' of the synchronising tones will be noted. The first two positions of the LINE SYNC switch ("TIROS") select one or other of these two tones, the third position is for the Russian Meteor satellites.

Play the recording as before and adjust the INPUT LEVEL to give about half scale on the LEVEL meter. Select the first position of the sync detector on the MONITOR switch. Switch the LINE SYNC switch to TIROS 1, and set the two presets RV1 and RV2 on the sync card to their mid-position, and adjust RV3 to obtain the loudest output for the higher tone.

Repeat this procedure with the LINE SYNC switch set to TIROS 2, and adjust RV4 to obtain the maximum output for the lower tone (RV5 may be adjusted in the same way when playing a recording of a Meteor satellite with the SYNC switch in the METEOR position).

Switch to the second sync detector position on the MONITOR switch and adjust RV2 on the sync card to obtain a short burst of noise that corresponds to every second sync tone of the recording. Check this setting in the other (TIROS) position of the SYNC switch. For the METEOR position of the SYNC switch, adjust RV1 to obtain the noise burst for every sync tone when playing a recording of the satellite.

Decoder in Use

The following information refers to the use of the decoder with the BBC B and Amstrad computers. (Information for using the Frame Store will be published later).

Program 1 is for the BBC model B. Program 2 is the machine code created by the GENA 3 assembly program from Amsoft. From Program 2 you can create your object file which can then be loaded by Program 3. When loaded and run, these will ask for the Horizontal Resolution to be entered; this value determines not only the definition of the displayed picture, but also the proportion of the total picture width displayed across the screen. The first time a recording is run, select full width (4), and then any intèresting parts may be re-run with a lower setting to obtain greater detail. The SHIFT switch may be used to move the picture to the desired position at the beginning of the run, and if required, the full scan may be re-started by holding the space bar. (The sync when set is not lost until the tape is stopped or the signal fails.) Synchronisation to the start of a line is provided by the Sync Tone Card. The

Satellite	DIL 1 2								on 12	Slip Switch	Connections Right
# 1	1	1	1	1					4	9	8
# 2	1	1	1			1	1	1		8	6
# 3	1	√	1	/						9	8

Figure 14. Settings for Russian Satellites.

LINE SYNC switch selects the type of satellite and channel to be synchronised. With the recording running and the appropriate position of the LINE SYNC switch set, synchronisation is achieved by a short operation of the non-locking SYNC toggle switch.

The INPUT LEVEL control should be set to give an average reading of about half scale on the LEVEL meter. (Note that if a known peak white signal is being received, the level should be adjusted to give a full scale reading on the meter.) Advance the 'White Level' control until the peak white LED just starts to flash, then adjust the 'Black Level' until the black LED is just flashing. This setting should give a fairly good picture, but some experimentation with the settings of these controls is required to achieve the best results.

The LINES PER SECOND switch should be set to 2 lines per second for NOAA pictures, as channel A and channel B are sent alternately. The 4 lines per second position is used for satellites such as Meteosat when part lines are displayed to improve the aspect ratio and increase the vertical resolution.

The two preset positions of this switch are used for satellites with other line rates, and are programmed by using the diode cards. The Diode Card may either be fitted with DIL switches, or with diodes in a pre-selected matrix. When the DIL switches are fitted, cut the shorting tracks under the switches, and fit all diodes. The correct setting for a satellite is found by switching the LINES PER SECOND switch to the A position, inserting a diode card, with DIL switches installed, in position (nearest to the sync card) and trying different settings of the switches until a synchronised picture is

obtained. Figure 14 shows some settings for Russian satellites that have been found to synchronise correctly. When the setting has been determined, the code may be 'copied' onto a blank diode card by inserting diodes only in positions that correspond to the positions of those diodes that connect to the switches that are in the ON position on the original (DIL switch) Diode Card. The shorting tracks are left intact. The connections to the SLIP switch also appear on the Diode Card, and these are made by inserting wire links below the diodes. The method of setting these links is as follows:- Find the correct setting for the DIL switches as before, connect a short length of wire to the 'left' track and connect the other end to one of higher numbered pads marked X that does not have its associated switch in the ON (up) position. Run the tape and operate the SLIP switch to the LEFT position and note the effect on the picture. The correct setting is where the picture moves left at a controllable rate.

Once this connection point has been found, determine the position to the left of this connection where there is a switch in the ON position. Connect the RIGHT track to the 'X' connection of this position, and turn the switch OFF. Try running the recording again and check that when the SLIP switch is held in the RIGHT position, the picture moves to the right at a comfortable rate.

When the correct positions for the two connections have been found, permanent wire links may be fitted.

The picture scanning may be stopped at any time by using the HOLD switch. (This does not lose synchronisation if the incoming signal is uninterrupted.)

DECODER DIODE BOARD PARTS LIST

SEMICONDUCTORS
D1-12 1N4148 12 (QL80B)
MISCELLANEOUS
S1.2 DIL Switch SPST 6-Way 2 (FV44X)

MISCELLANEOUS
S1,2 DIL Switch SPST 6-Way 2 (FV44X)
Diode PCB 1 (GD24B)

A complete kit of all parts is available for this project:

Order As LM09K (Decoder Diode Board Kit) Price £5.95

The following item in the above kit list is also
available separately, but is not shown in the 1986 catalogue:
Decoder Diode PCB Order As GD24B Price £3.25

```
Program 1.
                                                                         97¢ LSR SMPL
 10 MODE 7
                                                                         9BO BCS UNE
 20 CLS: PRINT: PRINT
                                                                         990 INC SMPL
 30 PRINT"INPUT HORIZONTAL RESOLUTION (1-4)";
                                                                         1000 JMP WTBUSY
 40 INPUT HRES
                                                                         1010 .UNE
 50 MODE 2
                                                                        1020 LDA DOTBSE
1030 SEC
 60 VDU 23;8202;0;0;0
 70 PRINT
                                                                         1040 SBC #&08
 80 DIM CODE% 500
                                                                         1050 BCS
                                                                                   TWO
 90 ROWBSE=&70
                                                                         1060 DEC DOTBSE+1
100 ?ROWBSE=((HIMEM+20479) MOD 256)
110 ?(ROWBSE+1)=((HIMEM+20479) DIV 256)
                                                                         1070
                                                                              . TWO
                                                                         1080 STA DOTBSE
120 DOTBSE=&72
                                                                         1090 LDA ROWBSE+1
    ?DOTBSE=((HIMEM+20479)MOD 256)
130
                                                                         1100 STA RWBSSH+1
    ?(DOTBSE+1)=((HIMEM+20479)DIV 256)
140
                                                                         1110 LDA ROWBSE
150 SMPL=&74
                                                                         1120 STA
                                                                                   RWBSSH
160 TEMP=&75
                                                                         1130 SEC
170 RWBSSH=&76
                                                                         1140 SBC
                                                                                   #128
180 FINSCN=&78
                                                                         1150 BCS THREE
190 OVBRT=&7A .
200 ?FINSCN=((HIMEM)MOD 256)
210 ?(FINSCN+1)=((HIMEM)DIV 256)
                                                                         1160 DEC RWBSSH+1
                                                                         1170 .THREE
1180 STA RWBSSH
1190 DEC RWBSSH+1
220 PORT=&FE60
230 FOR P=0T02 STEP 2
                                                                         1200 DEC
                                                                                   RWBSSH+1
240 P%=CODE%
                                                                         1210 LDA DOTBSE+1
1220 CMP RWBSSH+1
250 [OPT P
260 LDA #&02
270 LDX #&00
                                                                         1230 BNE WTBUSY
                                                                         1240 LDA DOTBSE
280 JSR &FFF4
                                                                         1250 CMP RWBSSH
290 .INIT LDA #&00
300 LDX #&00
310 LDY #&00
                                                                         1260 BNE WTBUSY
                                                                         1270 TYA
1280 PHA
320 SEI
                                                                         1290
                                                                              TXA
330 CLD
                                                                         1300 PHA
340 STA &FE62
                                                                         1310 LDA #481
350 STA SMPL
360 STA TEMP
                                                                         1320 LDX
                                                                                   #&00
                                                                         1330 LDY
                                                                                   #8.00
     .WTSYNC
                                                                              JSR &FFF4
                                                                         1340
380 LDA PORT
                                                                         1350
                                                                               TYA
390 AND #64
                                                                         1360 BNE NEWLNE
400 BEQ WTSYNC
                                                                         1370 PLA: PLA: JMP EIGHT
410 .FINSYNC
                                                                         1380 . NEWLNE PLA
420 LDA PORT
                                                                         1390 TAX
430 AND #64
                                                                         1400 PLA
440 BNE FINSYNC
450 .WASTE BIT PORT
                                                                         1410 TAY
                                                                         1420 LDA ROWBSE
460 BMI WASTE
                                                                         1430 SEC
470 .PING BIT PORT
                                                                         1440 SBC #&01
480 BPL PING
                                                                         1450 INY
490 INX
                                                                         1460 BCS FOUR
500 CPX#01
510 BNE WASTE
520 LDX #&00
                                                                         1470 DEC ROWBSE+1
                                                                         1480 .FOUR
                                                                         1490 STA ROWBSE
530 .WTBUSY
540 BIT PORT
                                                                         1500 STA DOTBSE
                                                                         1510 LDA ROWBSE+1
550 BMI WTBUSY
                                                                         1520 STA DOTBSE+1
560 .WTSMPL
570 BIT PORT
                                                                         1530 CPY
                                                                                    #&08
                                                                         1540 BEQ SIX
580 BPL WTSMPL
                                                                         1550 JMP WTSYNC
590 INX
600 .RESH CPX #&02
                                                                         1560
                                                                               .SIX
                                                                         1570 LDA ROWBSE
610 BNE WTBUSY
                                                                         1580 LDY #&00
620 LDA PORT
                                                                         1590 SEC
630 AND #&OF
                                                                         1600 SBC #
640 LDX #&00
                                                                         1610 BCS FIVE
650 STX
          TEMP
                                                                         1620 DEC ROWBSE+1
660 LSR A
                                                                         1630 DEC DOTBSE+1
670 ROL TEMP
                                                                         1640 .FIVE
1650 STA ROWBSE
 68¢ ROL
          TEMP
690 ROL
                                                                         1660 STA DOTBSE
 700 ROL A
                                                                         1670 DEC ROWBSE+1
1680 DEC ROWBSE+1
710 ROL
720 ROL
                                                                         1690 DEC DOTBSE+1
 730 ROL A
                                                                         1700 DEC DOTBSE+1
1710 STY SMPL
 740 ROL
 750 ROL OVERT
                                                                         1720 LDA ROWBSE+1
 760 ROL A
                                                                         1730 CMP FINSCN+1
1740 BEQ SEVEN
 770 ROL TEMP
 780 ROL
           TEMP
                                                                         1750 BCC SEVEN
 790 RDL A
                                                                         1760 JMP WTSYND
 800 ROL
          TEMP
 810 LSR OVBRT
820 BCC TEST
                                                                          1780
                                                                               JMP EIGHT
                                                                         1790 LDA ROWBSE
1800 CMP FINSCN
 830 LDA#21
 840 STA TEMP
850 .TEST L
                                                                         1810 BEQ EIGHT
              LDA SMPL
                                                                          1820 BCC FIGHT
 860 LSR A
                                                                         1830 JMP WTSYND
 870 BCC ODD
880 ASL TEMP
                                                                          1840 .EIGHT
                                                                          1850 CLI
 890 LDA TEMP
                                                                          1860 RTS
 900 ORA (DOTBSE,X)
910 STA (DOTBSE,X)
                                                                          1870
                                                                          1880 NEXT P
1890 IF HRES>O AND HRES<5 THEN ?(RESH+1)=HRES
 920 JMP NEWDOT
 930
      . ODD
                                                                          1900 CALL CODE%
 940 LDA TEMP
950 STA (DOTBSE, X)
                                                                          1910 GOTO 90
 96¢ . NEWDOT
```

Program 2.

Hisoft GENA3.1 Assembler.

	A028		10		ORG	41000
	A028		20		ENT	\$
	FBF0	•	30		EQU	#FBF0
	9C40 9C41		40 50	TEMP:	EQU	40000 40001
	9C42		60	XREG:	EGU	40002
	9C44				EQU	40004
	9046			HXREG:	EQU	40006
	9048		90	BLKADD:	EGU	40008
	A028	3E00	100		LD	A,#00
	AO2A	32479C	110		L.D	(HXREG+1),A
	A02D A030	CDOEBC 219F00	120	RERUN:	CALL	HL,159
	A033	224290	140	IXC.XOIV	L.D	(XREG),HL
	A036	210700	150		LD	HL,199
	A039	22449C	160		LD	(YREG), HL
	VO3C	DD2142A1	170		LD	IX, BYTEAD+15
	A040	3EOF	180		LD	A, #OF
	A042	32409C	190	COLSET:	LD LD	(TEMP),A A,(IX+O)
	A045 A048	DD7E◊◊ 47	210	COLSETT	L.D	B, A
	A049	4F	220		LD	C, A
	AO4A	3A409C	230		LD	A, (TEMP)
	AO4D	CD32BC	240		CALL	#BC32
	A050	21409C	250		LD	HL, TEMP
	A053	35	260		DEC	(HL)
	A054 A057	FA5CAO DD2B	27¢ 28¢		JP DEC	M,WTFRM IX
	A059	C345A0	290		JP	COLSET
	AO5C	CD19BD		WTFRM:	CALL	#BD19
	A05F	CD19BD	310		CALL	
	A062-	F3	320	L00P1:	DI	
	A063	01F0FB	330		LD	BC, #F8F0
	A066	ED78		LINE:	IN	A, (C)
	A068	CB77	350		BIT	6, A
	AOGA AOGC	28FA ED78	360	ENLIN:	JR IN	Z,LINE A,(C)
	A06E	CB77	380	EI4E114.	BIT	6, A
	A070	20FA	390		JR	NZ, ENLIN
	A072	160A	400		LD	D, 10
	A074	15	410	DELAY:	DEC	D
	A075	20FD	420		JR	NZ, DELAY
	A077	F3		L00P2:	DI	m
	A078 A07A	1602 01F0F8	440 450		LD LD	D,2 BC,#F8F¢
	A07D	ED78		SMPL:	IN	A, (C)
	AO7F	CB7F	470	J	BIT	7, A
	A081	20FA	480		JR	NZ, SMPL
	A083	ED78		ENSMP:	IN	A, (C)
	A085	CB7F	500		BIT	7, A
	A087	28FA	510		JR	Z, ENSMP D
	A089	15 20F1	520 530		DEC JR	NZ,SMPL
	AOBC	2011		GETLUM:	31	142 y 31 W C
	AOBC	ED78	550	OL I LOIII	IN	A, (C)
	AOBE	E60F	560		AND	#OF
	A090	32419C	570		LD	(LUM),A
`	A093	1F	580		RRA	
	A094	CB18	590		RR	В
	A096 A097	1F CB18	600		RRA RR	В
	A099	1F	620		RRA	ь
	AO9A	CB19	630		RR	С
	A09C	1F	640		RRA	
	AO9D	CB18	650		RR	В
	A09F	1600	660		LD	D, O
	AOA1	CBOO	670		RLC	В
•	EAOA	CB1A	680		RR	D
	A0A5 A0A7	CB1A CB00	690 700		RR RLC	D B
	AOA9	CB1A	710		RR	D .
	AOAB	CB1A	720		RR	D
	AOAD	CBO1	730		RLC	C
	AOAF	CB1A	740		RR	D
	AOB1	CB1A	750		RR	D
	AOB3 AOB5	CBOO CB1A	760 770		RLC RR	B
	AOB3	3A429C	780		LD	A, (XREG)
	AOBA	1F	790		RRA	
	AOBB	3003	800		JR	NC, NOLFT
	AOBD	B7	810		OR	Α
	AOBE	CB1A	820		RR	D
	AOCO	32469C		NOLFT:	LD	(HXREG),A
	AOC3 AOC4	7A 32409C	84¢ 85¢		LD LD	A,D (TEMP),A
	HVU4	JZ7V30				S 152111 / J 151

```
LD
                                      HL.#5000
AOC7
      210050
                   860
                   870
                                 LD
                                      A, (YREG)
AOCA
      3A449C
                   880
                                 SRL
AOCD
      CB3F
                   890
                                 SRL
AOCF
      CB3F
                   900
                                 SRL
AOD1
      CB3F
AOD3
      5F
                   910
                                 LD
                                      E,A
AOD4
      1600
                   920
                                 LD
                                      D, O
AOD6
      0608
                   930
                                 LD
                                      B.8
                   940 MULT:
                                 ADD
                                      HL.HL
AODR
      29
                   950
                                 JR
                                      NC, NOADD
      3001
AOD9
      19
                   960
                                 ADD
                                      HL, DE
AODB
       10FA
                   970 NOADD:
                                 DJNZ
                                      MULT
AODC
AODE
      22489C
                   980
                                 LD
                                       (BLKADD) . HL
AOE1
      3A449C
                   990
                                 LD
                                      A, (YREG)
A0E4
      CB27
                  1000
                                 SLA
                                      Α
                  1010
                                 SLA
                                      Α
AOF6
      CB27
AOEB
      CB27
                  1020
                                 SLA
AOEA
      E638
                  1030
                                 AND
                                       56
AOEC
      67
                  1040
                                 LD
                                      Н,А
AOED
      2E00
                  1050
                                 LD
                                      L,O
                                       BC, (RLKADD)
AOEF
      ED4B489C
                  1060
                                 LD
                                      HL.BC
AOF3
      09
                  1070
                                 ADD
                                      BC, #C000
AOF4
      0100C0
                  1080
                                 LD
                  1090
                                 ADD
                                      HL, BC
AOF7
      09
AOFB
      ED4B469C
                  1100
                                 LD
                                       BC, (HXREG)
AOFC
       09
                  1110
                                 ADD
                                      HL,BC
                                       A, (TEMP)
      3A409C
AOFD
                  1120
                                 LD
      DD21429C
                                       IX. XREG
A100
                  1130
                                 1 D
                                 BIT
                                      0, (IX+0)
A104
      DDCB0046
                  1140
A108
       2001
                  1150
                                 JR
                                       NZ, PLOT
A10A
      B6
                  1160
                                 OR
                                       (HL)
A1 OB
       77
                  1170 PLOT:
                                 LD
                                       (HL),A
A1QC
      010100
                  1180
                                 LD
                                       BC, #0001
                                      HL, (XREG)
A10F
      2A429C
                  1190
                                 LD
      B7
                  1200
                                 OR
A112
A113
      ED42
                  1210
                                 SBC
                                      HL,BC
       3806
                  1220
                                 JR.
                                       C, NEXY
A117
       22429C
                  1230
                                 LD
                                       (XREG), HL
A11A
      C377A0
                  1240
                                 JP.
                                       LOOP2
                  1250 NEXY:
                                 t D
      219F00
                                       HL . 159
A11D
       22429C
                  1260
A120
                                 LD
                                       (XREG), HL
A123
       2A449C
                  1270
                                 LD
                                       HL, (YREG)
A126
       в7
                  1280
                                 QR
A127
      ED42
                  1290
                                 SBC
                                      HL, BC
A129
      3002
                  1300
                                 JR
                                       NC, NEWL IN
      FB
A12B
                  1310
                                 ΕI
A12C
      C9
                  1320
                                 RET
A12D
      22449C
                  1330 NEWLIN:
                                       (YREG), HL
                                 LD
A130
      C362A0
                  1340
                                 JP
                                       L00P1
A133
                  1350 BYTEAD:
A133
      00010204
                  1360
                                 DEFB 0,1,2,4
      05060B0A
                                 DEFB 5,6,8,10
A137
                  1370
      OCOE1012
A13B
                  1380
                                 DEFB 12, 14, 16, 18
       1416181A
                  1390
                                 DEFB 20,22,24,26
A13F
```

BYTEAD A133 COLSET A045 BLKADD 9C48 DELAY A074 ENLIN AO6C **ENSMP** E80A GETLUM AOBC HXREG 9046 LINE A066 L00P1 A062 LODP2 A077 LUM 9C41 **NEWLIN A12D** MULT AOD8 NEXY A11D NOADD AODC NOLFT PLOT A10B AOCO F8F¢ RERUN A030 SMPL A07D PORT TEMP 9C40 WTFRM AQ5C XREG 9042 YREG **9C44**

307 350 from Table used: Executes: 41000

Program 3.

5 MEMORY 30000: MODE 2 10 LOAD"wefax1.obj"

20 INPUT"enter horizontal resolution 1-4"; resh 30 IF resh>0 AND resh<5 THEN POKE &A079,


resh ELSE CLS:GOTO 20

40 CALL 41000

50 CALL &A030

60 GOTO 50

SATELLI	TE DECODER PAR	TS	LIST	S3 S5	Switch Sub-Min Toggle SPDT Switch Dual Rocker Neon	(D) 1	(FH03D)
RESISTORS: AL	ll 0.6W 1% Metal Film			FS1	Fuse LA A/S	1	(YR70M) (WR19V)
R1	27k	1	(M27K)	PL1,3	Minicon latch Plg 2-Way	2	(RK65V)
R2,4,25	470k	3	(M470K)	PL2	Minicon latch Plg 12-Way	1	(YW14Q)
R3,37,38,39,40	lk	5	(M1K)	PL4	Minicon latch Plg 6-Way	1	(YW12N)
R5,9,20,27	10k	4	(M10K)	PL5,6	Minicon latch Plg 8-Way	3	(YW13P)
R6,7,12,24	100k	4	(M100K)	PL7	R.A. 'D' Range 25-Way PCB P		(FG68Y)
R8	820Ω	1	(M820R)	SK1,3	Minicon latch Housing 2-Way		(HB59P)
R10	220k	- 1	(M220K)	SK2	Mincon latch Housing 12-Way		(YW24B)
R11,17,26	2k2	3	(M2K2)	SK4	Minicon latch Housing 6-Way		(BH65V)
R13	180k	1	(M180K)	SK5,6	Minicon latch Housing 8-Way Minicon Terminal		(YW23A)
R14,41	47k	2	(M47K)	SK8	6-Pin PCB DIN Socket	46	(YW25C)
R15	5k6	1	(M5K6)	SK9	Power Socket D.C. 2.5mm	1	(FA90X) (FK06G)
R16,21,22,23,28,		- 1		SK10-12	2x12-Way P.C. Edgeconn	3	(BK74R)
30,31,34,35,36	4k7	10	(M4K7)		Polarising Key 0.156in	3	(FD08])
R18 R19	180k 390Ω	1	(M180K)		Bolt 6BA x lin	1 Pkt	(BF07H)
R29	330Ω	1	(M390R)		6BA x 1/4 in Threaded Spacer	1 Pkt	(FD10L)
R32.33	270Ω	2	(M330R)		Nut 6BA	1 Plct	(BF18U)
SIL 1,2	SIL 4k7	2	(M270R) (RA29G)		Tag 2BA	1 Pkt	(BF27E)
RV1	10k Cermet	1	(WR42V)		Bolt 6BA x ½in	l Pkt	(BF06G)
RV2	lk Hor. S-Min Preset	1	(WR55K)		Mains Warning Label	1	(WH48C)
RV3	10k Pot Lin	1	(FW02C)		Cable Min Mains White	1 mtr	(XR02C)
RV4	lk Pot Lin	1	(FW00A)		Ribbon Cable 20-Way	l mtr	(XR07H)
RV5	IM Pot Lin	1	(FW08J)		Grommet Small	1	(FW59P)
			(2 11 00))		S.R. Grommet 6W-1	1	(LR49D)
CAPACITORS		250			Sleeving Heatshrink CP95 Clip-on TO220 Heatsink	l mtr	(YR17T)
C1-3	220nF Poly Layer	3	(WW45Y)		Decoder PCB	1	(FG62G) (GD22Y)
C4,5	10μF 16V Minelect	2	(YY34M)		Veropin 2141	1 Plet	(FL21X)
C6,11	47nF Poly Layer	2	(WW37S)		DIL Socket 8-pin	1	(BL17T)
C7	100μF 25V P.C. Electrolytic	1	(FF11M)		DIL Socket 14-pin	4	(BL18U)
C8,26,27	4μ 7F 35V Minelect	3	(YY33L)		DIL Socket 16-pin	3	(BL19V)
C9	2μ2F 63V Minelect	-	(YY32K)		DIL Socket 18-pin	1	(HQ76H)
C10 C12	2n2F Poly Layer	1	(WW24B)		Safuseholder 20	1	(RX96E)
C13-18,28	4nTF Poly Layer	1 7	(WW26D)		Knob K10B	5	(RK90X)
C19-22	100nF Minidisc	1	(YR75S)		Transformer Mounting Bracke	t 1	(FD09K)
C23	2200μF 35V Axial Electrolytic 10μF 16V Tantalum	1	(FB90X) (WW68Y)		Constructor's Guide	1	(XH79L)
C24,25	100nF Polyester	2	(BX76H)	OPTIONAL			
01 1,00	10014 1019 GSIGE	2	(DALGE)	OFTIONAL	Instrument Case NM2H		CVARIEN
SEMICONDUC	TORS				Decoder Front Panel	1	(YM51F) (FD05F)
D1,2	OA91	2	(QH72P)		Araldite	1	(FL44X)
D3-14	IN4148	12	(QL80B)		DIN Plug 6-pin	2	(HH29G)
ZD1	BZY88C3V3	1	(QH02C)		Standard Power Plug 2.5	2	(HH62S)
LED 1	Red LED Chrome large	1	(YY60Q)		Cable Single Core Screened ((XR13P)
LED 2	Green LED Chrome large	1	(QY47B)		Multi-Core 6-Way	1 mtr	(XR26D)
TR1-3	BC548	3	(QB73Q)		Decoder Interface Cable	1	(FD17T)
BRI	VV005	1	(QL37S)				
REG1	μA7912UC	1	(WQ93B)	A co	mplete kit of all parts, excluding o	ptional ite	ms.
REG2	μA7812UC	1	(QL32K)		is available for this project		
REG3	μA7805UC	1	(QL31J)	Order	As LM07H (MAPSAT Decoder K	it) Price £	79.95
IC1	LF353	1	(WQ31J)	The following	lowing items included in the above	kit list are	e also
IC2	ZN427E	1	(UF40T)	available	separately, but are not shown in the	ne 1986 cat	talogue:
IC3 IC4	NE565	1	(WQ56L)	Sub-	Min Toggle SPDT Order As FH020	12 Daige C1	.20
104	74LS132	1	(YF51F)		n PCB DIN Socket Order As FA90	o Fince al	
		-	COVOCED			X Price 5	Opp
IC5	4078 744C163	1	(QX28F)		dgeconn Polarising Key Order As	X Price 50 FD08J Pri	0p ice 1 2p
IC5 IC6-8	74HC163	3	(UB42V)	⅓in x €	dgeconn Polarising Key Order As BBA Threaded Spacer Order As F	X Price 50 FD08J Pri D10L Price	0p ice 1 2p
IC5		3		⅓in x €	dgeconn Polarising Key Order As BA Threaded Spacer Order As Fi ecoder PCB Order As GD22Y Pri	X Price 50 FD08J Price D10L Price ice £12.95	0p ice 1 2p e 88p
IC5 IC6-8	74HC163 74LS03	3 1	(UB42V)	⅓in x € D MAPSAT	dgeconn Polarising Key Order As BA Threaded Spacer Order As Fi ecoder PCB Order As GD22Y Pri Decoder Front Panel Order As F	X Price 50 FD08J Pri D10L Price ice £12.95 D05F Price	0p ice 12p e 88p e £3.95
ICS IC6-8 IC9 MISCELLANEC M1	74HC163 74LS03	1 3 1	(UB42V)	¼in x 6 E MAPSAT Transforr	dgeconn Polarising Key Order As BA Threaded Spacer Order As Fi ecoder PCB Order As GD22Y Pri Decoder Front Panel Order As F ner Mounting Bracket Order As F	FD08J Pri FD08J Pri D10L Pric ice £12.95 D05F Pric D09K Pric	0p ice 12p e 88p e £3.95 e £1.20
ICS IC6-8 IC9 MISCELLANEO M1 T1	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V	1 1 7 1	(UB42V) (YF03D)	¼in x 6 D MAPSAT Transforr Instru	dgeconn Polarising Key Order As BA Threaded Spacer Order As Fi ecoder PCB Order As GD22Y Pri Decoder Front Panel Order As F ner Mounting Bracket Order As F nent Case NM2H Order As YM51	X Price 50 FD08J Price D10L Price ice £12.95 D05F Price D09K Price £1	0p ice 12p e 88p e £3.95 e £1.20 4.95
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (6	1 1 7 1	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C)	1/4in x 6 MAPSAT Transfort Instrut Decode	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Filecoder PCB Order As GD22Y Pridecoder Front Panel Order As Filecoder Front Panel Order As Filecomer Mounting Bracket Order As Filecomer Case NM2H Order As YM51 ler Interface Cable Order As FD1	X Price 50 FD08J Price D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £	0p ice 12p e 88p e £3.95 e £1.20 4.95 6.85
ICS IC6-8 IC9 MISCELLANEO M1 T1	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V	1 1 7 1	(UB42V) (YF03D) (LB80B) (YK11M)	1/4in x 6 MAPSAT Transfort Instrut Decode	dgeconn Polarising Key Order As BA Threaded Spacer Order As Fi ecoder PCB Order As GD22Y Pri Decoder Front Panel Order As F ner Mounting Bracket Order As F nent Case NM2H Order As YM51	X Price 50 FD08J Price D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £	0p dce 12p e 88p e £3.95 e £1.20 4.95 6.85
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (Switch Rotary 3-pole 4-way	1 7 1 7 1 C)1 2	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF78S)	44in x 6 E MAPSAT Transforr Instruit Decode	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Filecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder Front Panel Order As Finer Mounting Bracket Order As Finent Case NM2H Order As YM51 ler Interface Cable Order As TD1 tructor's Guide Order As XH79L 1	X Price 50 FD08J Price D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (6	1 7 1 7 1 C)1 2	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF78S)	44in x 6 E MAPSAT Transforr Instrut Decod Cons	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Fivecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder Front Panel Order As Finer Mounting Bracket Order As Finer Case NM2H Order As YM51 ler Interface Cable Order As TD1 tructor's Guide Order As XH79L 10nF Poly Layer	X Price 50 FD08J Price D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (c Switch Rotary 3-pole 4-way	1 7 1 7 1 C)1 2	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF78S)	Vain x 6 E MAPSAT Transforr Instrut Decod Cons C4 C7	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Fivecoder PCB Order As GD22Y Prid Decoder Front Panel Order As Finer Mounting Bracket Order As Finer Mounting Bracket Order As YM51 ler Interface Cable Order As YM51 tructor's Guide Order As XH79L 100µF Poly Layer 100µF 16V Minelect	X Price 50 FD08J Price D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (c Switch Rotary 3-pole 4-way	1 7 1 7 1 C)1 2	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF78S)	Vin x 6 D MAPSAT Transforr Instru Decod Cons	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Flecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder Front Panel Order As Finer Mounting Bracket Order As Finer Case NM2H Order As YM51 ler Interface Cable Order As TD1 tructor's Guide Order As XH79L 1 10nF Poly Layer 100µF 16V Minelect 10µF 16V Minelect	X Price 50 FD08J Pric D10L Pric ice £12.95 D05F Pric D09K Pric F Price £1 TT Price £ Price 25p	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55K) (YY34M)
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (c Switch Rotary 3-pole 4-way	1 7 1 7 1 C)1 2	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF78S)	Vain x 6 E MAPSAT Transfort Instrut Decod Cons C4 C7 C8 C9,10	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Fivecoder PCB Order As GD22Y Price Decoder Front Panel Order As Finer Mounting Bracket Order As Finer Mounting Bracket Order As YM51 ler Interface Cable Order As YM51 ler Interface Cable Order As TD1 tructor's Guide Order As XH79L 1 10nF Poly Layer 100µF 16V Minelect 10µF 16V Minelect 220nF Poly Layer	X Price 50 FD08J Price D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (c Switch Rotary 3-pole 4-way ER SYNC TONE BOLLST	1 7 1 7 1 C)1 2	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF78S)	Vain x 6 E MAPSAT Transfort Instrut Decod Cons C4 C7 C8 C9,10 SEMICONDU	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Filecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder Pront Panel Order As Finer Mounting Bracket Order As Finer Mounting Bracket Order As YM51 ler Interface Cable Order As YM51 ler Interface Cable Order As TD1 tructor's Guide Order As XH79L 1 10nF Poly Layer 100µF 16V Minelect 10µF 16V Minelect 220nF Poly Layer	X Price 50 FD08J Pri D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £ Price 25p	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RASSK) (YY34M)
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS I RESISTORS: All	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (Switch Rotary 3-pole 4-way ER SYNC TONE BO LIST 1 0.6W 1% Metal Film	1 7 1 7 1 C)1 2	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF76S)	Vain x 6 E MAPSAT Transforr Instrum Decod Cons C4 C7 C8 C9,10 SEMICONDU D1-3	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Flecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder Front Panel Order As Finer Mounting Bracket Order As Finer Case NM2H Order As YM51 ler Interface Cable Order As YM51 ler Interface Cable Order As XH79L Interface Cable Order As XH7	X Price 50 FD08J Pri D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £ Price 25p	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RASSK) (YY34M)
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS I RESISTORS: All R1	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (6 Switch Rotary 3-pole 4-way ER SYNC TONE BOLIST 1 0.6W 1% Metal Film 2k2	1 1 / 1 (C)1 2 PAR	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF75S)	Vin x 6 D MAPSAT Transforr Instrut Decod Cons C4 C7 C8 C9,10 SEMICONDU D1-3 TR1-3	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Flecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder Front Panel Order As Finer Mounting Bracket Order As Finer Mounting Bracket Order As YM51 der Interface Cable Order As YM51 der Interface Cable Order As XH79L 1 10nF Poly Layer 100µF 16V Minelect 10µF 16V Minelect 220nF Poly Layer ICTORS 1N4148 BC548	X Price 50 FD08J Pri D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £ Price 25p	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55E) (YY34M) (WW45Y) (QL80B) (QB73Q)
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS RESISTORS: All R1 R2,10,11,13,22 R3 R4-7	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (c) Switch Rotary 3-pole 4-way ER SYNC TONE BOLIST 1 0.6W 1% Metal Film 2k2 47k	1 1 / 1 (C)1 2 PAR	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FT78S)	Vin x 6 D MAPSAT Transforr Instrut Decod Cons C4 C7 C8 C9,10 SEMICONDU D1-3 TR1-3 IC1	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Flecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder Front Panel Order As Finer Mounting Bracket Order As Finer Mounting Bracket Order As YM51 der Interface Cable Order As YM51 der Interface Cable Order As TD1 tructor's Guide Order As XH79L 1 10nF Poly Layer 100µF 16V Minelect 10µF 16V Minelect 220nF Poly Layer ICTORS 1N4148 BC548 4046BE	X Price 50 FD08J Pri D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £ Price 25p	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55K) (YY34M) (WW45Y) (QL80B) (QB73Q) (QW32K)
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS I RESISTORS: All R1 R2,10,11,13,22 R3 R4-7 R8,9	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (c) Switch Rotary 3-pole 4-way ER SYNC TONE BC LIST 1 0.6W 1% Metal Film 2k2 47k 100k 33k 470k	1 1 / 1 (C)1 2 PAR	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF78S)	Vin x 6 D MAPSAT Transforr Instrut Decod Cons C4 C7 C8 C9,10 SEMICONDU D1-3 TR1-3	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Flecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder Front Panel Order As Finer Mounting Bracket Order As Finer Mounting Bracket Order As YM51 der Interface Cable Order As YM51 der Interface Cable Order As XH79L 1 10nF Poly Layer 100µF 16V Minelect 10µF 16V Minelect 220nF Poly Layer ICTORS 1N4148 BC548	X Price 50 FD08J Pri D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £ Price 25p	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55E) (YY34M) (WW45Y) (QL80B) (QB73Q)
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS RESISTORS: All R2,10,11,13,22 R3 R4-7 R8,9 R12	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (Switch Rotary 3-pole 4-way ER SYNC TONE BC LIST 1 0.6W 1% Metal Film 2k2 47k 100k 33k 470k 68k	1 1 / 1 (C)1 2 PAR	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF78S) (M2K2) (M47K) (M100K) (M33K)	C4 C7 C8 C9,10 SEMICONDU D1-3 TR1-3 IC1 IC2	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Fivecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder PCD Panel Order As Fivecoder PCD Panel PCD Panel PCD Panel PCD Panel PCD	X Price 50 FD08J Pri D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £ Price 25p	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55K) (YY34M) (WW45Y) (QL80B) (QB73Q) (QW32K)
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS I RESISTORS: All R1 R2,10,11,13,22 R3 R4-7 R8,9 R12 R14	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (Switch Rotary 3-pole 4-way ER SYNC TONE BO LIST 1 0.6W 1% Metal Film 2k2 47k 100k 33k 470k 68k 82k	1 1 / 1 (C)1 2 PAR	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF75S) (M2K2) (M47K) (M100K) (M33K) (M470K)	Vin x 6 D MAPSAT Transforr Instrut Decod Cons C4 C7 C8 C9,10 SEMICONDU D1-3 TR1-3 IC1	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Flecoder PCB Order As GD22Y Pridecoder PCB Order As Energy Decoder Front Panel Order As Finer Mounting Bracket Order As Finer Mounting Bracket Order As Finer Interface Cable Order As YM51 der Interface Cable Order As XH79L Intructor's Guide Order As XH79L Intructor's G	X Price 50 FD08J Pri D10L Price £12.95 D05F Price D09K Price £1 TT Price £1 TT Price £2 Price 25p	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55K) (YY34M) (WW45Y) (QL80B) (QB73Q) (QW32K) (QY38Q)
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS RESISTORS: All R1 R2,10,11,13,22 R3 R4-7 R8,9 R12 R14 R15	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (6 Switch Rotary 3-pole 4-way ER SYNC TONE BC LIST 1 0.6W 1% Metal Film 2k2 47k 1000k 33k 470k 68k 82k 18k	1 1 / 1 (C)1 2 PAR	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF75S) (M2K2) (M47K) (M100K) (M33K) (M470K) (M68K)	C4 C7 C8 C9,10 SEMICONDU D1-3 TR1-3 IC1 IC2	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Filecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder Front Panel Order As Filecoder	X Price 50 FD08J Pri D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £ Price 25p 1 1 1 2 3 3 1 1 1 1 Pkt	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55E) (YY34M) (WW45Y) (QL80B) (QB73Q) (QW32E) (QY38Q)
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS I RESISTORS: All R1 R2,10,11,13,22 R3 R4-7 R8,9 R12 R12 R14 R15 R16,19	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (in Switch Rotary 3-pole 4-way) ER SYNC TONE BC LIST 1 0.6W 1% Metal Film 2k2 47k 100k 33k 470k 68k 82k 18k 220Ω	1 1 / 1 (C)1 2 PAR	(M2K2) (M2K2) (M47K) (M100K) (M470K) (M68K) (M68K) (M82K) (M18K) (M120R)	C4 C7 C8 C9,10 SEMICONDU D1-3 TR1-3 IC1 IC2	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Filecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder Front Panel Order As File Polaris Process of Panel Order As File Interface Cable Order As TM51 der Interface Cable Order As TM51 der Interface Cable Order As TM51 der Interface Cable Order As XH79L 1 10nF Poly Layer 100µF 16V Minelect 10µF 16V Minelect 220nF Poly Layer ICTORS 1N4148 BC548 4046BE MF10CN EOUS Veropin 2145 Sync 1 PCB	X Price 50 FD08J Pri D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £ Price 25p 1 1 1 2 3 3 1 1 1 Pkt 1	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55K) (YY34M) (WW45Y) (QL80B) (QB73Q) (QW32K) (QY38Q) (FL24B) (GD23A)
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS I RESISTORS: All R1 R2,10,11,13,22 R3 R4-7 R8,9 R12 R14 R15 R16,19 R17,18,20,21	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (6 Switch Rotary 3-pole 4-way ER SYNC TONE BO LIST 1 0.6W 1% Metal Film 2k2 47k 100k 33k 470k 68k 82k 18k 220Ω 4k7	1 1 / 1 (C)1 2 PAR	(M2K2) (M100K) (M2K2) (M47K) (M100K) (M33K) (M470K) (M82K) (M82K) (M82K) (M10K) (M82K) (M82K) (M10K) (M82K) (M82K) (M10K) (M82K) (M10K) (M82K) (M10K) (M10K) (M10K) (M10K) (M10K)	C4 C7 C8 C9,10 SEMICONDU D1-3 TR1-3 IC1 IC2	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Filecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder Front Panel Order As Filecoder	X Price 50 FD08J Pri D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £ Price 25p 1 1 1 2 3 3 1 1 1 1 Pkt	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55K) (YY34M) (WW45Y) (QL80B) (QB73Q) (QW32K) (QY38Q) (FL24B) (GD23A) (FL24D)
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS I RESISTORS: All R1 R2,10,11,13,22 R3 R4-7 R8,9 R12 R14 R15 R16,19 R17,18,20,21 R23	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (Switch Rotary 3-pole 4-way ER SYNC TONE BC LIST 1 0.6W 1% Metal Film 2k2 47k 100k 33k 470k 68k 82k 18k 2200 4k7 220k	1 1 / 1 (C)1 2 PAR	(M2K2) (M100K) (M2K2) (M47K) (M100K) (M33K) (M470K) (M68K) (M82K) (M18K) (M220R) (M4K7) (M220R)	C4 C7 C8 C9,10 SEMICONDU D1-3 TR1-3 IC1 IC2	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Filecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder PCB Order As Filecoder Front Panel Order As File Decoder Front Panel Order As File Interface Cable Order As YM51 Ider Interface Cable Order As TD1 tructor's Guide Order As XH79L Interface Cable Order As XH79L Interface Interfa	X Price 50 FD08J Pric D10L Pric ice £12.95 D05F Price D09K Pric F Price £1 TT Price £ Price 25p i 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55K) (YY34M) (WW45Y) (QL80B) (QB73Q) (QW32K) (QY38Q) (FL24B) (GD23A)
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS I RESISTORS: All R2,10,11,13,22 R3 R4-7 R8,9 R12 R14 R15 R16,19 R17,18,20,21 R23 R24	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (c) Switch Rotary 3-pole 4-way ER SYNC TONE BC LIST 1 0.6W 1% Metal Film 2k2 47k 100k 33k 470k 68k 82k 18k 220Ω 4k7 220k 2k7	1 1 1 C)1 2 2 1 1 1 2 2 4 1 1 1	(M2K2) (M100K) (M2K2) (M47K) (M100K) (M33K) (M470K) (M68K) (M82K) (M18K) (M220R) (M4K7) (M220R) (M2K7)	Vin x 6 E MAPSAT Transform Instrum Decod Cons C4 C7 C8 C9,10 SEMICONDU D1-3 TR1-3 IC1 IC2 MISCELLAN	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Fivecoder PCB Order As GD22Y Pridecoder PCB Order As Finer Mounting Bracket Order As Finer Mounting Bracket Order As YM51 der Interface Cable Order As YM51 der Interface Cable Order As YM51 der Interface Cable Order As XH79L Intructor's Guide Order As YH79L Intructor's Guide Or	X Price 50 FD08J Pri D10L Price ice £12.95 D05F Price D09K Price F Price £1 TT Price £ Price 25p 1 1 1 2 3 3 1 1 1 Pkt 1 1 Pkt 1	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55K) (YY34M) (WW45Y) (QL80B) (QB73Q) (QW32K) (QY38Q) (FL24B) (GD23A) (FL24B) (HQ77J)
ICS IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS I RESISTORS: All R1 R2,10,11,13,22 R3 R4-7 R8,9 R12 R14 R15 R16,19 R17,18,20,21 R23 R24 RV1,2	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (Switch Rotary 3-pole 4-way ER SYNC TONE BC LIST 1 0.6W 1% Metal Film 2k2 47k 100k 33k 470k 68k 82k 18k 2200 4k7 220k 2k7 47k Vert S. Preset	1	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF75S) (M2K2) (M47K) (M100K) (M33K) (M470K) (M68K) (M68K) (M82K) (M18K) (M120R) (M220R) (M4K7) (M220K) (M2K7) (WR70Q)	Vin x 6 E MAPSAT Transfort Instrut Decod Cons C4 C7 C8 C9,10 SEMICONDU D1-3 TR1-3 IC1 IC2 MISCELLAN A con	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Fivecoder PCB Order As GD22Y Pridecoder PCB Order As Fiver As GD22Y Pridecoder PCB Order As Fiver As Fiver As GD22Y Pridecoder PCB Order As Fiver As	X Price 50 FD08J Pri D10L Price £12.95 D05F Price D09K Price £1 TT Price £ Price 25p 1 1 1 2 3 3 1 1 1 Pkt 1 1 Pkt 1 cor this proj	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55K) (YY34M) (WW45Y) (QL80B) (QB73Q) (QW32K) (QY38Q) (FL24B) (GD23A) (FL24B) (HQ77J) ect:
IC5 IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS I RESISTORS: AII R1 R2,10,11,13,22 R3 R4-7 R8,9 R12 R14 R15 R16,19 R17,18,20,21 R23 R24 RV1,2 RV3-5	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (c) Switch Rotary 3-pole 4-way ER SYNC TONE BC LIST 1 0.6W 1% Metal Film 2k2 47k 100k 33k 470k 68k 82k 18k 220Ω 4k7 220k 2k7	1 1 1 C)1 2 2 1 1 1 2 2 4 1 1 1	(M2K2) (M100K) (M2K2) (M47K) (M100K) (M33K) (M470K) (M68K) (M82K) (M18K) (M220R) (M4K7) (M220R) (M2K7)	Vain x 6 E MAPSAT Transfort Instrut Decod Cons C4 C7 C8 C9,10 SEMICONDU D1-3 TR1-3 IC1 IC2 MISCELLAN A con Order	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Fivecoder PCB Order As GD22Y Pridecoder PCB Order As Finer Mounting Bracket Order As Finer Mounting Bracket Order As YM51 ler Interface Cable Order As YM51 ler Interface Cable Order As XH79L Intructor's Guide Ord	X Price 50 FD08J Pri D10L Price £12.95 D05F Price D09K Price £1 TT Price £ Price 25p 1 1 1 2 3 3 1 1 1 Pkt 1 1 Pkt 1 c) r this proj it) Price £	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55K) (YY34M) (WW45Y) (QL80B) (QB73Q) (QW32K) (QY38Q) (FL24B) (GD23A) (FL24B) (HQ77J) ect:
IC5 IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS I RESISTORS: All R1 R2,10,11,13,22 R3 R4-7 R8,9 R12 R14 R15 R16,19 R17,18,20,21 R23 R24 RV1,2 RV3-5 CAPACITORS	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (Switch Rotary 3-pole 4-way ER SYNC TONE BC LIST 1 0.6W 1% Metal Film 2k2 47k 100k 33k 470k 68k 82k 18k 2200 4k7 220k 2k7 47k Vert S. Preset 10k 23-Turn Cermet	1	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF75S) (M2K2) (M47K) (M100K) (M33K) (M470K) (M68K) (M68K) (M82K) (M18K) (M120R) (M220R) (M4K7) (M220K) (M2K7) (WR70Q)	Vin x 6 D MAPSAT Transforr Instrut Decod Cons C4 C7 C8 C9,10 SEMICONDU D1-3 TR1-3 IC1 IC2 MISCELLAN A con Order	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Filecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder Front Panel Order As Filecoder Front Panel Order As TM51 der Interface Cable Order As TM51 der Interface Cable Order As TM79L Intructor's Guide Order As XH79L Intructor's Gui	X Price 50 FD08J Pri D10L Price ice £12.95 Control Price £12.95 F Price £1 TT Price £ Price 25p 1 1 1 2 3 3 1 1 1 Pkt 1	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55K) (YY34M) (WW45Y) (QL80B) (QB73Q) (QW32K) (QY38Q) (FL24B) (GD23A) (FL92D) (HQ77]) ect: 12.95
IC5 IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS I RESISTORS: All R1 R2,10,11,13,22 R3 R4-7 R8,9 R12 R14 R15 R16,19 R17,18,20,21 R23 R24 RV1,2 RV3-5 CAPACITORS C1,2,5,6	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15VS witch Sub. Min. Toggle SPDT (Switch Rotary 3-pole 4-way) ER SYNC TONE BOLIST 1 0.6W 1% Metal Film 2k2 47k 100k 33k 470k 68k 82k 18k 2200 4k7 220k 2k7 47k Vert S. Preset 10k 23-Turn Cermet	1 1 1 1 2 2 3 4 4 1 1 2 2 3	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF76S) (M2K2) (M47K) (M100K) (M33K) (M470K) (M68K) (M82K) (M18K) (M220R) (M4K7) (M220R) (M4K7) (W220K) (M2K7) (W270Q) (WR49D)	Vin x 6 D MAPSAT Transforr Instrut Decod Cons C4 C7 C8 C9,10 SEMICONDU D1-3 TR1-3 IC1 IC2 MISCELLAN A con Order A available	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Filecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder Front Panel Order As Filecoder Front Panel Order As File Decoder Front Panel Order As File Interface Cable Order As YM51 der Interface Cable Order As XH79L Intructor's Guide Order As XH79L Intructor's G	X Price 50 FD08J Pric D10L Priccice £12.95 Construction F Price £1 TT Price £ Price 25p 1 1 1 2 3 3 1 1 1 Plat 2 Plat 3 Plat 3 Plat 3 Plat 4	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55K) (YY34M) (WW45Y) (QL80B) (QB73Q) (QW32K) (QY38Q) (FL24B) (GD23A) (FL92D) (HQ77]) ect: 12.95
IC5 IC6-8 IC9 MISCELLANEO M1 T1 S1 S2,4 DECODE PARTS I RESISTORS: All R1 R2,10,11,13,22 R3 R4-7 R8,9 R12 R14 R15 R16,19 R17,18,20,21 R23 R24 RV1,2 RV3-5 CAPACITORS	74HC163 74LS03 DUS Signal Meter Transformer Toroidal 30VA 15V Switch Sub. Min. Toggle SPDT (Switch Rotary 3-pole 4-way ER SYNC TONE BC LIST 1 0.6W 1% Metal Film 2k2 47k 100k 33k 470k 68k 82k 18k 2200 4k7 220k 2k7 47k Vert S. Preset 10k 23-Turn Cermet	1 1 1 C)1 2 2 2 1 1 1 2 2 3 3	(UB42V) (YF03D) (LB80B) (YK11M) (FH02C) (FF76S) (M2K2) (M47K) (M100K) (M33K) (M470K) (M68K) (M68K) (M82K) (M18K) (M220R) (M4K7) (M20K) (M2K7) (WR70Q) (WR49D)	Vin x 6 D MAPSAT Transforr Instrut Decod Cons C4 C7 C8 C9,10 SEMICONDU D1-3 TR1-3 IC1 IC2 MISCELLAN A con Order A available	dgeconn Polarising Key Order As EBA Threaded Spacer Order As Filecoder PCB Order As GD22Y Pridecoder PCB Order As GD22Y Pridecoder Front Panel Order As Filecoder Front Panel Order As TM51 der Interface Cable Order As TM51 der Interface Cable Order As TM79L Intructor's Guide Order As XH79L Intructor's Gui	X Price 50 FD08J Pric D10L Priccice £12.95 Construction F Price £1 TT Price £ Price 25p 1 1 1 2 3 3 1 1 1 Plat 2 Plat 3 Plat 3 Plat 3 Plat 4	Op ice 12p e 88p e £3.95 e £1.20 4.95 6.85 NV (WW29G) (RA55K) (YY34M) (WW45Y) (QL80B) (QB73Q) (QW32K) (QY38Q) (FL24B) (GD23A) (FL92D) (HQ77]) ect: 12.95

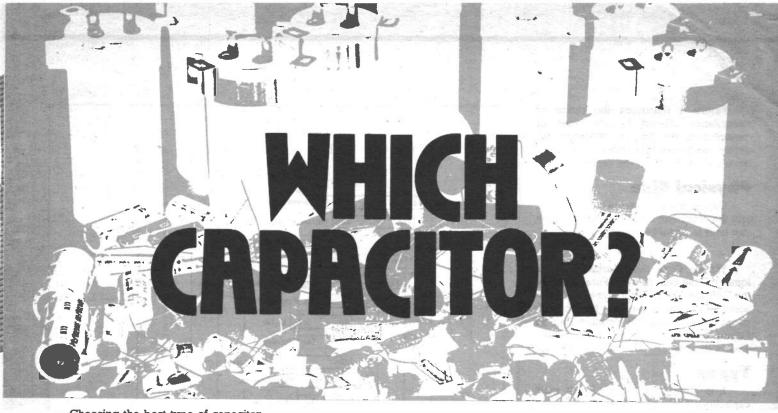

Choosing the best type of capacitor for a circuit is not always easy. Manufacturers' data sheets are packed with helpful information like "Insulation resistance.>5000 M Ω ", and "Power factor <0.013 at 10kHz", but unless you know what it all means - and why it matters you might just as well pick the cheapest component with an adequate voltage rating and hope for the best.

If you need a $0.1\mu F$ capacitor, for example, the Maplin catalogue gives you twelve to choose from, see Table 1. They range from a tantalum electrolytic the size of a dried pea, right up to a polystyrene component as big as a cigar butt. Why are there so many different types? The answer, of course, is that each has been carefully optimised for one of the many different roles capacitors have to fill - coupling in audio circuits, interference suppression, tuning RF oscillators, decoupling digital logic circuits, and so on.

Value

Capacitors are generally sold as preferred values in the range from 1pF to about $10,000\mu F$. The lower limit is set by the inevitable stray capacitance around the component when it is used, and at the upper end of the range the components can store so much energy for such long periods that they are virtually batteries. Indeed, a 1 Farad capacitor is made especially to act as a short-term emergency power supply for computer memory boards.

The range of preferred values in each decade are often just 1, 1.5, 2.2, 3.3, 4.7, and (sometimes) 6.8, with a tolerance of typically 10%. This rather limited range is not always as restricting as it seems; after all, it doesn't really matter if the value of a decoupling capacitor is slightly higher than it need be. Capacitors intended for use in circuits where precision is important - like filters and oscillators, for example - are available in a much wider range of values and with tighter tolerances.

September 1986 Maplin Magazine

by J.K. Hearfield

Туре	Price	Materiai	Working Voltage	Toi. %	Power factor %	insulation Resistance Ω	
Minidisc	10p	Ceramic	16	+80 -20	<7	·>10 ¹⁰	-1
Połystyrene	54p	Polystyrene	63	±5	<0.05 @1MHz	>10 ¹¹	-0.016 ±0.008
Tant	15p	Tantalum	35	±20	<10	>3.10 ⁷ (see text)	+0.1
Monocap	54p	Multilayer ceramic	50	±10	2.5	>10 ¹¹	-1
Disc	6р	Ceramic	40	+80 -20	<5	>5.10 ⁹	-1
Minelect	10p	Electrolytic	63	±20	<9	>2.10 ⁷ (see text)	+0.2
Monores	40p	Multilayer Ceramic	100	±10	<2.5	>10 ¹⁰	-1
Mylar	6р	Polyester	100	±10	<0.01 @1kHz	>1010	+0.02
Poly Layer	15p	PETP	250V DC 100V AC	±5	<0.8 @1kHz	>7.5.10 ¹⁰	+0.02
Polyester	9р	PETP	250	±10	<0.013 @1kHz	>3.10 ¹⁰	+0.033
IS Cap	35p	PETP	250V AC	±20	≤0.013 @10kHz	>15.10 ⁹	+0.03
HV Cap	80p	Polyprop- ylene	1000V DC 500V AC	±10 ^	<0.015 @1kHz	>10 ¹¹	-0.02

Table 1. 0.1μ F capacitors summary.

Family	Capacitance Range	Power Factor %	Tempco %°C	Working Voltage Range
Ceramic	1pF – 1μF	5	-1	50 - 1000
Plastic Electrolytic	10pF – 1μF 100nF – 100,000μF	0.01 10	+0.02 +0.2	100 - 400 10 - 450

Table 2. The three main families of capacitor.

Figure 1 illustrates the range of capacitance offered by the types of capacitor in the Maplin catalogue, together with current prices for components at each end of the range.

Physical Size

Capacitors are used to store charge, and the maximum amount of charge each can hold is given by its CV product:

$$Q = C \times V$$

Where Q is the charge (in coulombs), C the capacitance (Farads) and V the voltage. One might expect a capacitor's physical size to be roughly proportional to its CV product, but as Figure 2 shows, this is by no means always the case.

Types

It is clear from Figure 2 that most capacitors belong to one of just three families: ceramic, plastic, or electrolytic. The important characteristics of each family are illustrated in Table 2.

Table 2 shows that, although the ceramic and electrolytic families between them cover the whole range from lpF to $10,000\mu\text{F}$, capacitors with plastic dielectrics are a much better choice when the application requires high stability or low loss.

Identification

Like resistors, some capacitors carry gaily coloured stripes to indicate their nominal values; the colour code is the same as for resistors. But it is much more common for capacitor manufacturers to print the component's value on its case along with its rated working voltage and the manufacturer's name. The value may be expressed as a three-digit code for example, "154" would not mean 154pF, but 15,0000pF ('15' plus '4' zeros): that is, 150nF.

Voltage

Manufacturers specify the maximum voltage that may be applied across their capacitors without damaging them, and it is essential to observe this limitation. But in the same way as a resistor is more reliable if it is not allowed to get too hot, a capacitor (especially an electrolytic) tends to last longer if the voltage across it is kept well below its rated voltage. It's also important to ensure that the voltage across any electrolytic (and tantalum) type is of the correct polarity. As a rule of thumb, it is prudent to choose a capacitor with a working voltage about 20% greater than the voltage it will actually see in practice.

Temperature

Capacitance varies with temperature, although usually not very much. Its temperature dependence is known as its 'Tempco' (short for 'Temperature Coefficient,' though it sounds more like the name of a secretarial staff agency!).

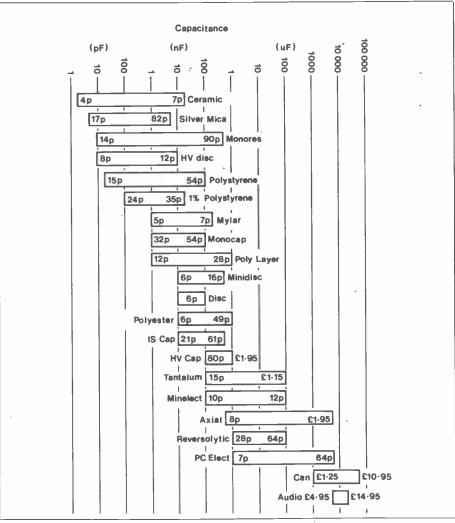


Figure 1. Capacitance range offered by different types.

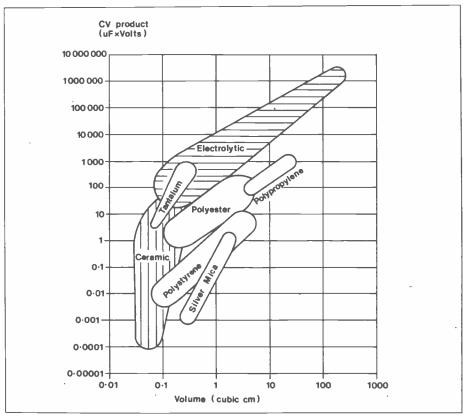


Figure 2. CV product and volume of capacitor range.

Tempco is measured in parts per million per degree C (ppm/°C) or as the percentage variation from its value at room temperature. Table 1 shows that plastic film capacitors are the most stable – their value changes by less than 1% between 0 and 50 degrees C. Over the same temperature range, electrolytics might vary by 5% or so, but ceramic-based capacitors could be as much as 25% less in value at 0° and at 50° than they are at room temperature!

Imperfections

The impedance of a perfect capacitor is always inversely proportional to frequency; its insulation resistance is infinitely large, and it never absorbs energy from the ripple current flowing through it. Unfortunately, perfect capacitors exist only in textbooks, and real capacitors suffer from all these defects to a greater or lesser extent. The capacitor's equivalent circuit, see Figure 3, shows how the imperfections can be modelled as series and shunt resistances, and series inductance.

Insulation Resistance

Some applications demand a capacitor having a very high effective parallel resistance – timing circuits, or sample-and-hold circuits, for instance. But as Table 1 illustrates, all except electrolytic types have an insulation resistance measured in thousands of Megohms.

Electrolytic and tantalum types have a small but continuous leakage current flowing through them. This current increases with temperature (reaching about twice its room temperature value at 50°C), and also with applied voltage.

Self-Resonance

The inductance of a length of straight wire is about 15nH per cm. Simple theory says that if each lead of a perfect $0.1\mu F$ capacitor is 5mm long, the resulting tuned circuit will resonate at a frequency of 4MHz. At frequencies below resonance, impedance falls as frequency rises and the combination behaves like a capacitor. But at frequencies above resonance the impedance rises with frequency: the capacitor behaves like an inductor! At the other end of the scale, if the component in question is a real $100\mu F$ capacitor instead, then self-resonance occurs at just a few tens of kHz.

The moral is to use the smallest component with the lowest practical value, and to keep the leads (not forgetting the wiring and/or the PCB track) as short as possible if the self-resonant frequency must be high.

Power factor and tan d

Manufacturers don't usually quote the size of the Effective Series Resistance (ESR) for their capacitors directly. September 1986 Maplin Magazine

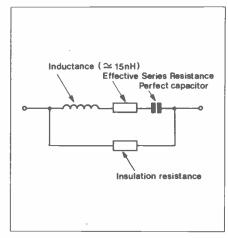


Figure 3. Capacitor equivalent circuit.

Instead, they define the component's power factor, where:

Power factor = Effective Series Resistance
Total impedance

Or more commonly, its dissipation factor: Dissipation factor = tan d

tan d = Effective Series Resistance

Capacitive Reactance

The two terms are almost identical provided ESR is small. Both are obviously frequency-dependent; they are often specified at a frequency of lkHz or l0kHz.

It is straightforward to extract a value for ESR from the power factor. The $0.1\mu F$ Poly Layer capacitor, for example, has a power factor quoted as 0.008 at 1kHz. At this frequency the capacitive reactance is 1590Ω , so:

 $ESR = 0.008 \times 1590 = 13 \text{ ohms.}$

Any current flowing through the capacitor flows also, by definition, through the ESR. Suppose the capacitor is carrying a ripple current of 50mA at lkHz. The power dissipated in the ESR – and, hence, in the component – is then:

 $P = 0.05 \times 0.05 \times 13 = 33 \text{mW}$

Electrolytic & Tantalum

Though they pack a lot of capacitance into a very small space, electrolytics are not precision components. They are generally sold with a tolerance of $\pm 20\%$, or even +50%/-10%. They are polarised, and therefore are intended to work in situations where a constant DC bias appears across them (though some can withstand a small continuous reverse bias); the bias voltage causes a leakage current of typically $1\mu A$ or so to flow continuously through them. Electrolytics are made in values from $0.1\mu F$ upwards, although the high-frequency performance of the larger ones is often poor. A high frequency, for an electrolytic, can be as low as only a few kHz.

Ceramic

The properties of a ceramic capacitor depend very much on the type of

dielectric that it employs. So-called "low-K" types are available at 5% tolerance from a few pF to a few nF. They have excellent temperature stability and a low dissipation factor.

"High-K" types by contrast may show a startling decrease in capacitance from the value quoted at room temperature. They are available in values from a few nF to 1μ F, and are used mainly in decoupling applications where their loose tolerance (10% or 20%) and poor dissipation factor are less important than their compactness, low inductance and low cost.

Polyester and Polycarbonate

Metallised film and foil capacitors are manufactured in values from 100pF to a few μF , usually at 10% tolerance. Their chief attraction is their low dissipation factor, particularly at low frequencies, but their performance may be good enough for some filter applications despite their relatively high Tempco (typically 300 ppm). They are often much cheaper than ceramic types, albeit physically larger.

Polystyrene

Their high stability and tight tolerance make polystyrene capacitors the obvious choice for precision work. They are available in 1% and 5% tolerances, from a few tens of pF up to 100nF. They have a moderate Tempco (typically –150ppm) and a low dissipation factor, even at high frequencies. At small values they can be much more expensive than equivalent ceramic types, but from about 1nF upwards they have no real competition.


Silver Mica

Silver mica capacitors also have good stability and tight tolerance but their high price makes them difficult to justify for most applications. Like low-K ceramic types, they are available in values from a few pF to a few nF. The two types are physically much of a size, especially at low values, but silver mica capacitors can cost more than twice as much.

Summary

Each of the capacitor types described in this article is ideal for some particular task – and woefully inadequate for others. Picking the most suitable type involves deciding which properties matter most for the application you have in mind. Must the component fit into a very small space? Must its value be stable over a wide range of temperatures? Must it have very low loss? Armed with the answers to these questions, you can use the catalogue to identify just the component you need. Of course, it may not yet exist.....



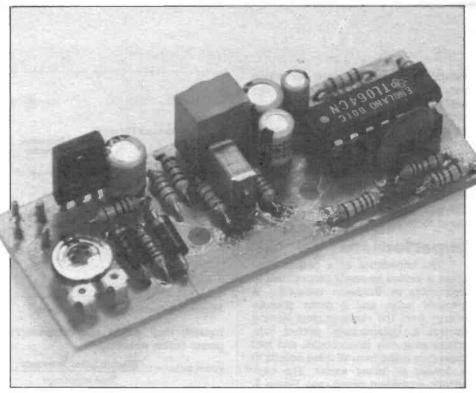

- * Low Cost, Short Range, Heat/Movement Detector.
- * Ideal for Doorways, Stairs and Proximity Systems.
- * Low Power Consumption for Long Battery Life.

ommercially available body heat, movement detection systems, although very sophisticated in their operation, can be rather expensive for use in limited applications where short range coverage is required. This I/R proximity detector has been designed as a simple low cost system for detecting heat changes, movement of a warm body, etc., such as those emitted from the human body. The unit responds to a definite change or disturbance in ambient - or background - heat levels and could be placed across a doorway or stairs to indicate movement in those areas.

Pyroelectrics

The F001P sensor uses a ceramic, ferroelectric element made from Lead Zirconate Titanate (PZT), which has the property of producing an electrical change at its surface when the temperature changes, due to a change in polarization intensity. If a moving object enters the field of view of this sensor, changes in infra red energy levels occur due to a difference in temperature between this object and the background. Infra red energy is converted into heat by the surface electrode of the element, thus causing a change in temperature within the element itself, and a small electric charge is created as a result (see Figure 1).

This small charge appears across the gate resistance Rg in Figure 2, and is impedance buffered by the FET source follower, where a change in voltage appears across source resistance Rs. A small DC bias voltage (IDRs) is produced

by Dave Goodman

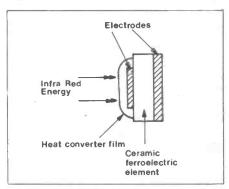


Figure 1. Pyroelectric Element.

by the quiescent current (ID) flowing through the FET while no signal is present, as Figure 3, and output signals from the source terminal overlap this level with a +Ve voltage swing.

In use, the voltage swing is very small, its amplitude being determined by the amount of incident energy available, which becomes smaller with increasing distance.

Done with Mirrors!

A negligible amount of energy is emitted from the human body which limits the effective working range of the module down to four feet or so. This range could be extended by increasing the sensitivity of the amplifier and developing velocity related filter circuits which would determine a given range of movement speeds and size of body.

An even more effective method is employed on commercial systems, in the form of collecting lenses and optical

Maplin Magazine September 1986

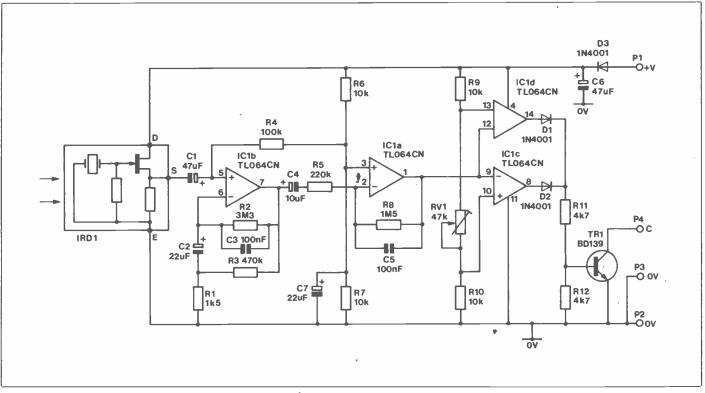


Figure 2. Sensor Circuit.

amplifying concave mirrors. Problems associated with energy collecting systems are: movements in the air, sunlight 'modulated' through curtains and even small animals generating fluctuations in the infra red energy background. To help overcome these sorts of problems, a multi-faceted, concave mirror is often used, which has the effect of expanding (or narrowing) the field of view into bands.

As an infra red emitting source crosses the field of view, radiated energy bounces off these facets in a sequence. The sensor responds with a series of related output pulses, and detection electronics can determine the size, velocity and direction of the source while it is moving. Quite a sophisticated achievement, and such a system is available in our catalogue, being more suitable for security and alarm uses than this particular system.

However, many applications exist where a simpler system is called for, especially for the home constructor!

Circuit Description

The circuit, shown in Figure 4, consists of two amplifying stages, with low pass filtering and a comparator threshold stage. Output voltage swings from the IRD are amplified by IClb, which is configured as a non-inverting amplifier. The IRD receives energy from many sources, and a mixed waveform would be produced at IClb output, therefore C3 integrates continuous low level signals and acts as a low pass filter.

The somewhat unusual arrangement of resistors R1 and R4 allow C2 to charge slowly during initial power up. C2 is necessary for isolating IC1b -Ve input from the 0V supply rail. With single supply op-amps, it is common to gen-September 1986 Maplin Magazine

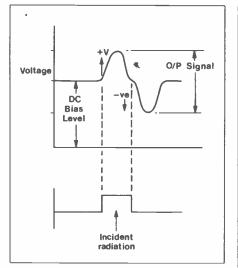


Figure 3. Source Output Voltage Swing.

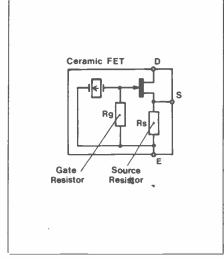


Figure 4. Proximity detector Circuit.

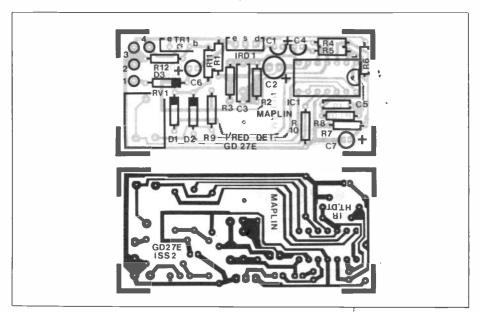


Figure 5. PCB Artwork.

erate a half supply DC voltage reference to bias the differential inputs, thus allowing output voltage swings about this level. The effect of integration on the continuous input signals produces a very low frequency output signal, which is applied to C2.

The charge across C2 varies with the magnitude of the output signal (from pin 7), and limits heavy transients from saturating this stage.

ICla is a standard inverting amplifier, again voltage referenced to half supply by R6 and R7. C7 decouples the reference voltage to prevent comparator supply spikes from being introduced into the stage. ICld and IClc serve as a simple comparator. The threshold voltage reference, determining when the comparators will trigger, is set by RVI in the potential divider chain R9 and R10.

Positive voltage swings from ICla trigger the ICld comparator causing D1 to conduct, while negative swings trigger IClc causing D2 to conduct. From Figure 3 it can be seen that the output voltage swing from the IRD is, firstly, in a positive direction and then secondly in a negative direction. The ultimate effect from the comparator output at R11 is therefore not one but two pulses turning on transistor TR1.


Either one of diodes D1 or D2 could be removed for single pulse output and which particular one to remove must be decided under full operational conditions. TR1 is an open collector switch, and will sink external loads (sourced from their own external +V supply) to the 0V common rail when conducting.

Construction

For information on building details and components, refer to Figure 5 for the board layout and to the 'Constructor's Guide' supplied with this kit (if you do not intend to purchase the complete kit then see the Parts List for the order code of the Constructor's Guide, price 25p). Identify and insert resistors R1 to R12. Solder these components and remove excess wire before continuing.

Mount diodes D1 to D3, and insert veropins at Pin 1 to Pin 4 in the holes marked with white circles. Next, insert a 14-pin IC socket in position IC1, and bend a few legs over the track pads to hold it in position. The PCB is quite small with tracks running close together, so care must be taken whilst soldering, as short circuits between tracks can easily occur.

Identify and insert capacitors C1 to C7. Polylayer type C3 should be fitted carefully to prevent breaking the lead out wires from each end of the package. Fit preset RV1, and solder all components in position. Again, cut off all excess leads, then fit TR1 and the sensor IRD1 shown in Figure 6. One side of TR1 has a metal, heat transfer mounting plate fitted. Insert TR1 with this plate facing outward towards the edge of the pcb. The sensor IRD1, shown in Figure 7, could be

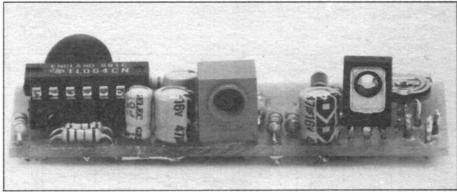

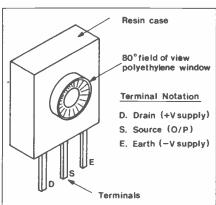


Figure 6. Sensor pin-outs.

mounted vertically from the pcb, or horizontally off the pcb as detailed. Mount the sensor as close as possible – in both cases – to the pcb in order to reduce noise induced into this area.

Either mounting position will have to take into account the boxing (case) requirements, and this is left to the fitting as required by the constructor. Solder any remaining components, cut off all excess wires and clean up the track area to facilitate inspection.

Testing

Supply requirements for the module are 9V DC @ 2mA. Current consumption is low, which allows long periods of use from small battery packs such as the PP3. Connect the battery +Ve to Pin 1, and -Ve to Pin 2; diode D3 prevents damage to components in the event of accidentally reversed battery polarities.

Check the supply current with an milliammeter, which will be around 2.5mA for a minute or so, dropping to 1 – 1.5mA after this period. Current consumption increases by approximately lmA while the comparator stages are operating.

The output transistor TR1 does not source current, but being open collector will sink current from an external supply load. Figure 8 suggests various methods of switching external loads, and diagram (a) could be used for testing purposes. Connect the LED cathode (k) to collector Pin 4, and wire the battery to one end of a $lk\Omega$ resistor connected to the LED anode (a).

If using the same battery for both module supply and LED supply, then the second battery -Ve connection is not

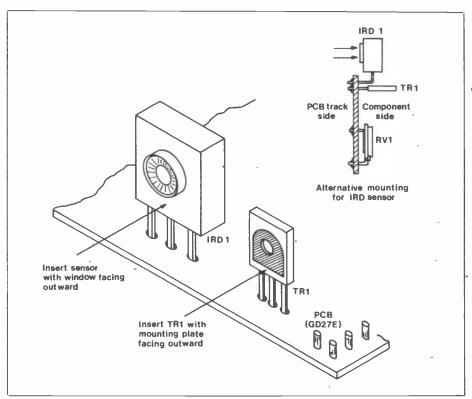


Figure 7. Mounting arrangements.

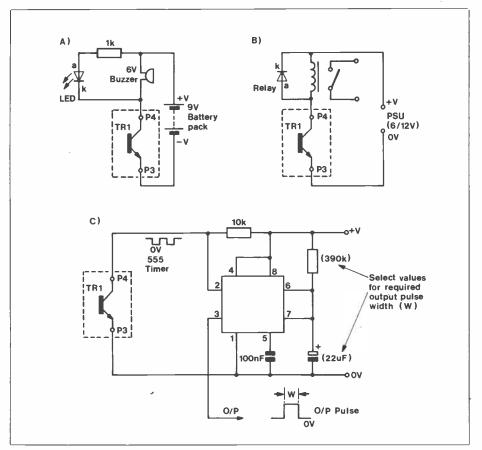


Figure 8. External Circuit Connections.

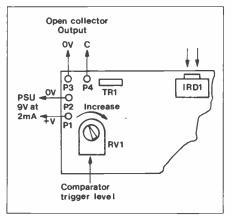


Figure 9. External PCB Connections.

required. Turn the comparator threshold control, RV1, to half travel (Figure 9), and after the initial 'warming up' period, move your hand across the sensor window. Do not poke the window with fingers as grease deposited will reduce sensitivity and may prevent operation completely! Figure 10 shows the spectral response expected in the window. The LED will light for a few seconds. If the LED is permanently aglow, turn the trigger level down by moving RV1 wiper anti-clockwise.

Using the Module

TR1 is not capable of switching

heavy loads and should be used on external systems up to 12V DC, and current levels below 100mA. Relays could be used for controlling larger voltage/current devices (Figure 8b), or a timer could be employed to generate long operating periods once triggered (Figure 8c). On the prototype, a 6V @ 35mA buzzer was used, on a separate supply, to good effect. Any battery supplying the electronics should not be used for supplying the external devices as well, if more than a simple LED arrangement is to be used. Battery connections to Pin 1 and 2 should be kept short - a PP3 clip lead is ideal for this and mount both module and battery together in the same housing with a suitable ON/OFF switch.

Sensing range is 4 to 5 feet, depending upon the sensor's field of view and variations in the light/heat background levels. A whole room, for instance, could not adequately be covered by this system, but doorways, narrow hallways and corridors are suitable areas. Another use for the module could be in a shower cubicle, using a timer circuit for controlling the water pump. Obviously, low voltage switching systems are important in this application.

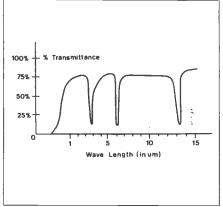


Figure 10. Window Spectral response.

SEMICONDUCTORS INFRA RED PROXIMITY DETECTOR D1-3 1N4001 PARTS LIST TR1 BD139 IC1 TL064CN RESISTORS: All 0.6W 1% Metal Film IRD1 F001P (M1K5) Rl 1k5 **3M3** (M3M3) R2 MISCELLANEOUS (M470K) R3 470k I/R Detector PCB (M100K) **R4** 100k Veropins 2145 R5 220k (M220K) DIL Socket 14-Pin R6,7,9,10 10k (M10K) Constructor's Guide (M1M5) RS 1M8 (M4K7) R11.12 4k7 A complete kit of all parts is available for this project: 47k Hor. Sub-min Preset (WR60O) RV1 Order As LM13P (I/R Detector Kit) Price £10.95 The following items in the above kit list are also CAPACITORS available separately, but are not shown in the 1986 catalogue: C1,6 47μF 16V Minelect 2 (YY37S) I/R Detector PCB Order As GD27E Price £1.95 C2,7 22µF 16V Minelect (YY36P) I/R Detector F001P Order As FD13P Price £5.95 C3 C4 100nF Polyester 10μF 16V Minelect (WW41U) Constructor's Guide Order As XH79L 25p NV (YY34M) 100nF Minidisc (YR75S)

(QL73Q)

(QF07H)

(RA66W)

(FD13P)

(GD27E)

(FL24B)

(BL18U)

(XH79L)

There are many useful devices, from greenhouse heating controls, through motor speed controllers to disco lights, that need some way of controlling mains power by means of low-level signals, either analogue or digital. Relays can be used for simple on/off control, and recent developments have made switching current ratings of the order of 20A available in small relays of reasonable cost. For many applications, however, solid-state control devices are preferable, on the grounds of physical size or cost, or because proportional control is required.

Thyristors are used for DC, and high-power AC/rectifier applications, while for other AC applications the triac, being a bi-directional device, is better. It can control powers up to at least 10kW (single-phase), and substantially higher powers in multi-phase systems.

High power bipolar and MOS transistors are also available, at reasonably competitive prices, for power-control applications, and are useful with high-frequency supplies, or where controlled turn-off is required: in these cases gate-turn-off (GTO) thyristors are also used for powers up to about 100kW.

In this article, however, we shall concentrate on a qualitative explanation of the working of the triac, and a look at design methods in some typical, basic applications.

Construction of the Triac

The triac is a four-layer semiconductor, but, being bi-directional, its structure is at first sight somewhat complex. We can build up an explanation of the structure and operation by first considering the thyristor.

The thyristor can be modelled by an interconnected complementary pair of bipolar transistors, as shown in Figure 1. From equation A.1 of Appendix 1, the current in response to a positive voltage on the p-n-p emitter (anode) relative to the n-p-n emitter (cathode) is critically dependent on the product of the DC current gains, and becomes unlimited when the product is equal to 1. This occurs at quite low values of the collector currents, in the region where the current gains are proportional to the collector currents. A small current injected at either base can therefore trigger the device into conduction. The n-p-n base, or 'gate', shown in Figure 1, is known as a cathode gate. A low power, four-layer device, BRY39 (page 294 of the 1986 Maplin Catalogue), is available which gives access to both anode and cathode gates. The device is very versatile, offering many small signal switching applications, but these are outside the scope of this article.

For full-wave AC power control, two of these model devices would be required, connected in inverse parallel. Luckily, it is possible to integrate the two devices on a single die, and an example of such a triac structure is shown

by J.M. Woodgate B.Sc.(Eng.), C. Eng., M.I.E.E., M.A.E.S., M.Inst. S.C.E.

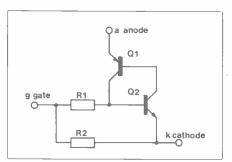


Figure 1. 2 transistor equivalent of a Thyristor

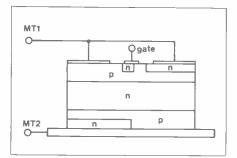


Figure 2. Centre-gate Triac structure

diagrammatically in Figure 2. This is a centre-gate structure; other structures are manufactured, and the geometry has significant effects on the device characteristics.

Electrical Characteristics of Triacs

If the anode to cathode voltage applied to the model device of Figure 1 is increased sufficiently, the increased leakage currents will themselves raise the current gains to the critical values, and the device is then said to have 'broken down'. This is not a normal mode of operation however, and conduction is usually started by applying to the gate terminal a positive voltage (in the case of the model device) relative to the cathode.

The characteristics of the semiconductor materials used in a triac are different from those of a bipolar transistor (for example, the same region has to work both as a collector and as a base),

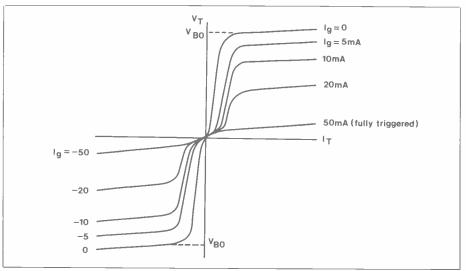


Figure 3. Triac main voltage/main current characteristics with gate current as parameter

Maplin Magazine September 1986

and the gate input characteristics are rather different from those of a 'conventional' base-emitter junction.

Part of this difference can be represented by the resistors R1 and R2 in Figure 1. These differences in characteristics raise the gate voltage at, say, 10mA gate current from the 600mV of a typical silicon transistor junction to about 900mV. The presence of R1 means that conduction in the main circuit cannot be stopped by connecting the gate to cathode or MT1; thus the gate current can be applied in the form of a short pulse. Conduction is normally stopped by allowing or forcing the main circuit current to fall below the minimum value necessary to hold the current gains at or above their critical values. This current is known as the holding current IH, and, in AC applications, the current normally falls below this value as a matter of course once every half-cycle.

If the gate current is increased slowly from zero, with a resistive load in the main circuit (see Figure 3), the voltage across the main terminals falls, eventually to a low value, represented in the model by the saturation voltage of the p-n-p transistor plus the base-emitter voltage of the n-p-n transistor, or vice versa for an opposite supply polarity. This is the normal on-state of the device, and operation at lower values of gate current than is necessary to achieve it should normally be avoided, because the power dissipation in the device is considerably increased by this. Thus it is wise to ensure that, subject to the limits of peak and average gate dissipation, the worst-case gate current available from the trigger circuit comfortably exceeds the gate current required to trigger a least-sensitive device.

Capacitance within the device, between the main terminals and the gate, can cause the triac to trigger if the mainterminal voltage rise rate (dV/dt) is sufficiently fast. This, too, is normally an undesired effect, but can be avoided by correct design. Some types of triac are very resistant to this sort of false triggering, having maximum dV/dt values of several hundred volts per microsecond, but are limited in their triggering modes (see below). Where the load is inductive, and the triac is required to go from the conducting to the non-conducting state, the maximum permissible dV/dt is dependent on the current flowing in the main circuit and its rate of fall (-dI/dt), a high current or rate of fall reducing the permissible dV/dt, which is then known as 'commutation dV/dt'.

If we look at the main circuit voltage/current characteristics in Figure 4, we can see significant hysteresis: the main circuit current has to rise to I_L , the latching current, before the gate loses control, whereas the current can fall to I_H , the holding current, before conduction substantially ceases.

The off-state leakage current I_D is sufficient to disqualify the triac as a circuit isolator, and a mechanical isolator September 1986 Maplin Magazine

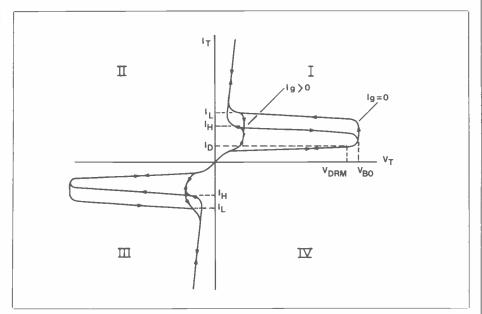


Figure 4. Dynamic main current/main voltage characteristics

switch should always be provided for maintenance and/or service operations!

The quadrants of the V/I graph are conventionally numbered I to IV. Operation in quadrant I is satisfactory with the gate either positive or negative with respect to MT1; and in quadrant III with a negative gate, but for a positive gate in quadrant III the gate sensitivity is, for most types of triac, much reduced, and this triggering mode may not be recommended by the device manufacturer. The latching current may also be different in the two quadrants, and decreases somewhat with increasing gate-current pulse width (see below). The data sheet values, rather than measured values, should be accepted for design work.

When the gate current is in pulse form, as is the case in many practical circuits, the rather large capacitance between the gate and MTl effectively makes triggering dependent on the total charge at the gate, i.e. for a square pulse, the product of gate current and application time. The precise nature of this dependence is not linear however.

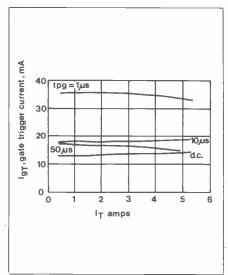


Figure 5. Peak gate trigger current as a function of trigger pulse duration

Typical characteristics are shown in Figure 5. Very short pulses of less than $1\mu s$ duration should be avoided, because only part of the die area may be triggered. This will cause a hot-spot to form, and may destroy the device. The manufacturer may specify a pulse width, which should be regarded as a recommended minimum value. Once the device is properly triggered, complete conduction is established typically in about $1\mu s$. There is, however, a delay time of several microseconds before conduction begins, as shown in the timing diagram of Figure 6.

A group of characteristics which is not usually mentioned in data sheets describes the effects of the anode voltage and the main circuit current on the gate voltage. The gate drive circuit has to have a high impedance for these to be observed. For example, the continuity of the load in the main circuit can be confirmed, while the triac is in the blocking state, by monitoring the gate voltage. This is particularly of value where the load is a projector lamp,

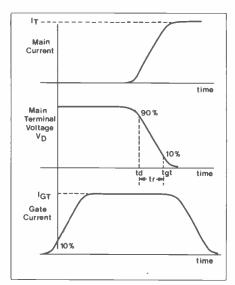


Figure 6. Timing diagram for the triggering process

whose failure might spoil an audio-visual presentation, and the use of this technique is advocated in a draft international standard ¹.

The gate voltage in this condition is due to the capacitance between the gate and MT2. This is usually large enough to be practically useful only for triacs of 10A rating or greater, smaller triacs requiring an unreasonably high impedance at the gate. The effects of main circuit current on the gate characteristics depend on the triac geometry. When the gate voltage is of the same polarity as the MT2 voltage, the existence of main-circuit current simply reduces the gate current produced by a given voltage, see Figure 7a.

A transient appears at the onset of main circuit current, due to the gate to MT2 capacitance. If the gate polarity is opposite to that of MT2, (I- and III+ modes), there is spectacular disturbance of the gate voltage caused by transients in the main terminal voltage waveform, see Figures 7b and 7c. This characteristic can be traced by applying an alternating voltage through a resistive load to the main circuit, and an out-of-phase current to the gate. Figure 7b shows the Ig/Vg characteristic of a TIC226D, which has a high dV/dt rating but is not characterised in the III+ mode. Figure 7c shows the behaviour of another type, which is characterised for all modes, but has a lower dV/dt rating. Figure 7d shows that the gate voltage of the TIC226D is affected by the MT2 voltage, even if the external trigger gate current is insufficient to trigger the device. The occurrence of fast pulses of reverse polarity gate voltage due to capacitive effects, and of negative resistance regions in the gate characteristics, can give rise to considerable r.f. interference. This suggests that operation in the reversepolarity modes (I- and III+) should be avoided, where possible, for all triacs, even if they are characterised for this service.

Thermal Characteristics

There are limits to both the peak power and the average power that can be dissipated at the gate, and care is necessary to design the gate drive such that fast and reliable triggering is achieved without exceeding these limits. This should always be verified by taking measurements.

The main power loss in the device is due, naturally enough, to the main-circuit voltage drop during conduction, and the manufacturer normally provides data on this, for both half-wave and full-wave operation, as well as for various triggering points along the waveform. When the power loss has been determined, an electrical analogue circuit, see Figure 8, can be used to calculate the heat-sink requirements (see Appendix 2).

The performance of the chosen heat-sink design, in its final environment or housing, should always be measured,

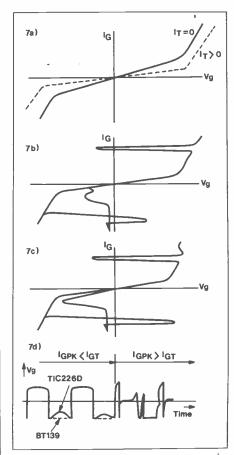


Figure 7 (a). Gate dynamic characteristics with gate and main currents in phase.
(b). Gate dynamic characteristics of TIC226D with gate and main currents in phase opposition.

(c). Gate dynamic characteristics of BT139 with gate and main currents in phase opposition.

(d). Gate voltage waveforms in untriggered and triggered conditions.

allowing for worst-case conditions of load current, ventilation and ambient temperature.

Gate Drive Techniques

For a simple switching circuit, it is possible to supply gate triggering current from a resistor connected between

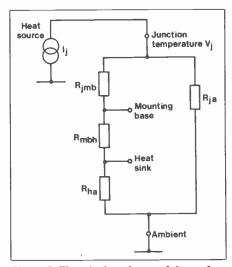


Figure 8. Electrical analogue of thermal circuit

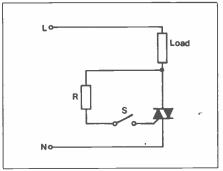


Figure 9. Simple Triac switch

gate and MT2, as shown in Figure 9. The device is switched on by closing the (low-power) switch. As the load current falls through zero each half-cycle, control is regained by the gate, so the load current will cease at the end of the half-cycle during which the switch is opened. This circuit has the advantage of simplicity and is widely recommended in American textbooks.

But with a British 240V mains supply, it may be difficult to ensure reliable triggering of least-sensitive devices without exceeding the permitted peak gate dissipation. It is preferable to apply gate current in pulse form, and one common way of doing this is to use a device known as a diac, or Silicon Bilateral Switch (SBS).

This is the solid-state equivalent of a neon-tube, that is to say as far as its electrical behaviour is concerned, and has a V/I characteristic as shown in Figure 10, with prominent negative resistance regions. Its action can be likened to a bi-directional zener diode. Connected as a relaxation oscillator, shown in Figure 11, a series of current pulses are produced in the resistor R2,

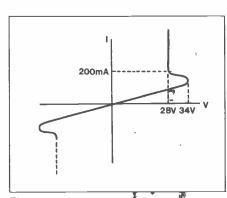


Figure 10. Typical Diac characteristic

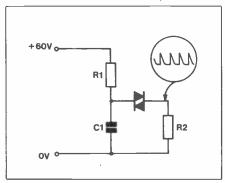


Figure 11. Diac relaxation oscillator

Maplin Magazine September 1986

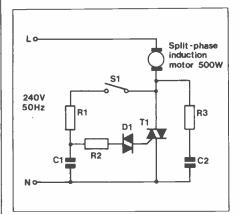


Figure 12. Practical Triac switch for a motor-driven appliance (for component values see Appendix 3).

representing the triac gate. For measurement of the gate-current pulse-width, an actual triac should be connected in place of R2, because the impedance at the gate is very non-linear and cannot be satisfactorily represented by a fixed resistor.

Figure 12 shows the resulting triac switch circuit. Normally the triac fires on the first gate pulse, but if it does not, trigger pulses continue to be applied until firing occurs. This is particularly significant with inductive loads, since the current may not rise above IL, the latching current, until some milliseconds after the triac has first been fired. Operation of this circuit with highly inductive loads may in any case be unsatisfactory for other reasons. With partially inductive loads, the snubber network R3, C2, is necessary. C2 reduces the rise rate of the MT2 voltage (dV/dt) at current cut-off, while R3 controls the current dumped from C2 into the triac as it begins to conduct.

With resistive loads, it is necessary to add interference suppression components. The interference r.f. is generated by the rapid collapse of the voltage across the triac as it fires. The detailed design of this circuit is dealt with in Appendix 3.

A unijunction transistor may also be employed as a trigger-pulse generator, but this will require a DC supply. Note that to avoid operation (or non-operation!) in the III+ mode, any single-polarity gate drive should consist of negative-going pulses.

In the triac switch circuit, it is necessary for the triac to fire as early in each half-cycle as possible, so as to minimise the loss of load power. Conversely, by varying the delay between the start of the half-cycle and the time at which the triac fires, the load power can be controlled. This can be done by varying the phase relationship of the gate voltage to the main terminal voltage, and this method is therefore called 'phase control'. Simple household dimmers use this technique, which has the considerable disadvantage of generating a great deal of r.f. interference, due to the sudden fall in the voltage across the triac as it fires. Suppression components L1, C4 are essential, and a typical circuit is shown in Figure 13.

This is one of those circuits whose operation is more complex than appears at first sight. If the components R2, R3 and C2 were omitted, the dimmer control R1 would suffer from considerable hysteresis. The lamp comes on suddenly, and quite brightly, as the control is advanced (reducing the resistance). When the control is turned the other way, the lamp becomes much dimmer, until it finally goes out at a control position noticeably different from that at which it came on. This effect is due to the loss of charge from C1 into the triac gate when the diac breakover voltage is only just exceeded

Suppose that the resistor R1 is set to a value such that the diac breakover voltage of, say, 34V is just not exceeded. The capacitor Cl charges to +34V on one half-cycle, then discharges to zero and charges to -34V on the next halfcycle, giving a change of capacitor voltage of 68V. If the resistor R1 is then slightly reduced, so that the diac conducts, this quickly reduces the voltage across the capacitor to, say, 28V. Thus, on the following half-cycle, the change in capacitor voltage is only 62V, so that the breakover voltage is reached at an earlier 'epoch' (i.e. time during the halfcycle), and, when the steady-state is reached, breakover is occurring considerably before the end of the halfcycle, and the lamp is quite bright.

Increasing R1 then smoothly reduces the conduction angle (firing time approaches the start of the half cycle). and, hence, the brightness of the lamp is reduced. This effect can be overcome with the additional components R2, R3 and C2. Gate current is drawn from C2. which is recharged via R2 from the much larger C1, with hardly any effect on the voltage across C1 and consequently on the firing epoch. R3 serves to limit the discharge current from C2, which is desirable on reliability grounds anyway, and reduces the recharging demand made of C1. With these additional components, 'backlash' is practically eliminated. This circuit also works well as a speed-controller for series-wound commutator motors, such as are found in power tools. Speeds can be reduced by around 10 times without an unacceptable loss of torque. A snubber network, R4 and C3, is included to avoid false triggering due to excessive dV/dt from the inductive load and the commutator noise spikes, is necessary. However, the circuit is not ideal for phase-control of loads having significant inductance, because if the firing epoch is not precisely the same for both polarities of supply voltage, then the load current will contain a DC component due to the unbalance, and this may cause undesirable effects due to the saturation of the magnetic circuits of the load.

When resistive loads of greater than about lkW dissipation have to be switched or controlled, the r.f. interference generated by the circuits described above becomes a serious problem. For such applications as stage and discolighting, there are few alternative techniques, and relatively costly filters are used to eliminate the interference. But for heaters with a large thermal inertia, burst-firing with synchronous switching can be used.

Synchronous Switching

Synchronous switching is a technique for minimising the amplitude of the voltage transient across the triac as it fires, and it works best when the latching current of the triac is very much less than the full load current. Gate drive is applied in pulse form, the leading edge of the pulse occurring at, or preferably before, the zero-crossing of the supply voltage, so that the triac remains conducting as the load current falls below the holding current and goes through zero. The pulse must, of course, last long enough to maintain the device in the 'on' condition for the load current to rise in the next half-cycle, to a value exceeding the latching current.

There is then no voltage transient, and consequently no r.f. interference. The technique can also be applied to phase control, where detection of the zero-crossing of the supply voltage is used as a reference for timing the trigger pulses more accurately, and more controllably, than can be achieved with RC phase-shift networks.

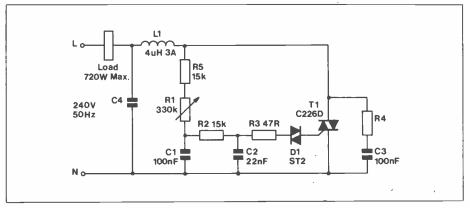


Figure 13. Lamp-dimmer or speed-controller for an AC series commutator motor

Synchronous switching circuits can be designed using discrete transistors², but integrated circuits are now available which offer improved performance, and usually a number of additional features. An example is the TDA 1024. This is an advanced phase-control device especially suitable for very low-differential temperature control or speed-control of series commutator motors. It can be powered either directly from the mains supply via a suitable voltage dropper, rectifier and stabiliser circuit, or from a local DC supply, and will control the conduction angle of the associated triac in accordance with a DC voltage, which may be obtained from a tacho-generator or a temperature sensor, for feedback control, or from a potentiometer, for open-loop control.

Synchronous switching also provides a solution to the problem, mentioned above, of firing-point asymmetry causing DC saturation in phase-controlled inductive loads. In this case, it is particularly important to use a synchronous switching circuit, or zero-crossing detector, which does not itself suffer from asymmetry. Most of the current integrated circuits satisfy this requirement.

Burst Firing

Burst firing, with synchronous switching, is a technique for controlling load power without generating r.f.i. Instead of varying, as in phase control, the fraction of each half-cycle for which load current is allowed to flow, the current is allowed to flow for an exact number of half-cycles, followed by an interval, also an exact number of half-cycles in duration, when no current is permitted.

Isolated Driving Circuits

It is essential for safety reasons that low-level drive signals derived from microprocessors, remote sensors etc., should not be applied directly to the triac, if it is, as usual, connected directly to the mains supply. All low-level circuits must be isolated from the mains. If they are earthed, the isolated coupling (opto-isolator, pulse transformer etc.) must withstand 2000V for 60 seconds, but if not, then circuit isolation to withstand 3000V for the same period is necessary. It should be noted that many opto-couplers and low-cost pulse trans-formers will not

meet these requirements!

Of the two devices mentioned, the opto-coupler is perhaps simpler to incorporate in a design, and there is little difference in cost. Furthermore, for AC applications, an optically-triggered triac is much easier to use than a coupler with a bipolar output device. Such a device is the Triac Isolator (Maplin Stock Code: QQ10L), and this can directly replace the switch S1 in Figure 12 and in similar circuits. The input of this device can be driven directly from TTL logic, and easily interfaced with CMOS. There is also a version, Order Code RA56L, which includes a zero-crossing detector.

References

- 1. IEC Publication 574-3A: Audiovisual, video and television equipment and systems. Part 3A: Connectors for automatic slide-projectors with built-in triacs, for audiovisual applications. International Electrotechnical Commission, Geneva. (To be published.)
- D.R. Armstrong, 'Zero-crossing detector circuits', Mullard Technical Communications No.132 Page 63-68. October 1976.

Appendix 1

In the model circuit, (Figure 1):

$$\begin{split} I_{m} &= I_{c1} + I_{c3} \\ I_{c1} &= I_{ceo1} + I_{b1}h_{FE1} \\ &= I_{cbo1} \left(1 + h_{FE1}\right) + I_{c2}h_{FE1} \end{split}$$

Similarly:

$$\begin{split} I_{c2} &= I_{cbo2} \left(1 + h_{FE2} \right) + I_{c1} h_{FE2} \\ I_{c2} &= I_{cbo2} \left(1 + h_{FE2} \right) + \{I_{cbo1} \left(1 + h_{FE1} \right) \\ &+ I_{c2} h_{FE1} \} h_{FE2} \\ I_{c2} \left(1 - h_{FE1} h_{FE2} \right) &= I_{cbo2} \left(1 + h_{FE2} \right) \\ &+ I_{cbo1} \left(1 + h_{FE1} \right) h_{FE2} \end{split}$$

Similarly:

$$\begin{split} I_{c1} \left(1 - h_{FE1}h_{FE2} \right) &= I_{cbo1} \left(1 + h_{FE1} \right) \\ &+ I_{cbo2} \left(1 + h_{FE2} \right) h_{FE1} \\ \\ \text{So, } I_{c1} + I_{c2} \\ &= I_{\underline{cbo2}} \left(1 + h_{\underline{FE2}} \right) \left(1 + h_{FE1} \right) + I_{\underline{cbo1}} \left(1 + h_{\underline{FE1}} \right) \left(1 + h_{\underline{FE2}} \right) \\ &\quad 1 - h_{FE1}h_{FE2} \\ &= \underbrace{ \left(1 + h_{FE1} \right) \left(1 + h_{FE2} \right) \left(I_{\underline{cbo1}} + I_{\underline{cbo2}} \right) }_{1 - h_{FE1}h_{FE2}} \end{split}$$

Appendix 2

- l. From a graph similar to Figure A.2.1, which will be found in the triac data sheet, find the power, P_T , dissipated by the triac at the given value of load current, I_T , and conduction angle a.
- 2. From the data sheet, substitute values in the electrical equivalent circuit, Figure 8.
 - R_{j-a} = thermal resistance of triac junction to ambient.
 - R_{j-mb} = thermal resistance of triac junction to mounting-base.

 R_{mb-h} = thermal resistance between the mounting-base and the heat-sink. Allow 1°C/W for a mica washer, 1.5°C/W for contact resistance without thermal jointing compound, 1°C/W for contact resistance with silicone grease, and 0.5°C/W for

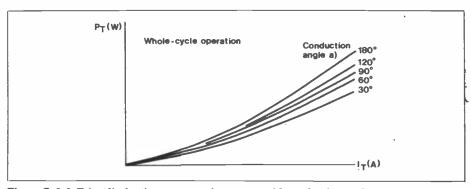


Figure A. 2. 1. Triac dissipation verses main current, with conduction angle as parameter.

contact resistance with oxide-loaded thermal jointing compound. These values apply for TO-220, TO-3 and similar encapsulations.

We have to find $R_{ha} \stackrel{!}{=}$ thermal resistance of the necessary heat-sink.

3. Substitute $I_j = P_T$, also $V_j = (T_j _{max} - T_{amb})$, where $T_j _{max}$ is the maximum permitted junction temperature of the

triac, from the data sheet, and T_{amb} is the maximum value of ambient temperature (35°C for the normal household environment). Preferably, reduce the value of V_j by 10°C, for greater reliability.

4. From the equivalent circuit:

$$I_{j} = -\frac{V_{i}}{R_{j-a}} + \frac{V_{i}}{R_{J-mb} + R_{mb-h} + R_{h-a}} \label{eq:interpolation}$$

This is just Ohm's Law. For many devices and applications, R_{j-a} can be neglected (thereby adding a safety factor).

Then
$$R_{h-a} = (V_j/I_j) - R_{j-mb} - R_{mb-h} =$$

$$\left\{ \begin{array}{c} \frac{(T_{j \text{ max}} - T_{amb})}{P_T} \end{array} \right\} - R_{j-mb} - R_{mb-h}$$

Appendix 3

Referring to Figure 12, the triac, T1, is chosen to have a V_{BO} rating greater than the peak voltage of the supply. For 240V mains, a V_{BO} of 400V must be regarded as a minimum. The I_T rating obviously depends on the required load current. It is wise to choose a generously-rated device, because this does not usually increase the cost greatly, and often gives a lower thermal resistance as a bonus. For example, a TIC226D, rated at 400V/8A r.m.s., could be chosen for this circuit, and is quite inexpensive.

We next look at the snubber network, R3 and C2. In the absence of these components, the series inductive component L_{IL} of the load impedance will cause a voltage spike to appear across the triac when it switches off. This spike may exceed the dV/dt rating of the triac and cause it to remain conducting! To avoid this, C2 is added to slow down the transient and reduce its amplitude, and R3 is included to ensure that the tuned circuit L_I/C2 is, at least, critically damped.

Unfortunately, the value of L_L is often not known, and it is not easily measured because, being dependent on an iron-cored component, it varies with the applied voltage and frequency. Under

these conditions, it is usual to choose an initial value for C2, such as 100nF, and to examine the resultant voltage transient with an oscilloscope. Any necessary adjustment, to achieve a desired value of dV/dt, can then be easily made. If L_L is known, then:

$$C2 > 2V_s^2/\{L_L(dV/dt)^2_{max}\}$$

Similarly, the value of R3 depends on that of L_L :

$$R3 > 2 L_{\text{\tiny I}}/C2$$

and, in practice, is adjusted so that the voltage transient is observed to be well damped.

C2 should be rated for 250V AC working, and a self-healing 'X-type' capacitor should be used.

R3 has to pass a current transient greater than 3A if power is applied to the circuit at a voltage maximum, and should be chosen accordingly. Some low-cost metal-film resistors are unsuitable.

Dl, the diac, can be chosen from the few types (e.g. ST2 (QL08])) available. The symmetry of the breakover voltage is important in minimising the DC component in the load current. It is worth noting that the prices of rather similar devices of this type vary considerably.

Cl is chosen to store enough charge to supply the gate current required for reliable triggering. Most samples of triac require typically one-tenth of the triggering current given in the data sheet, so an experimental approach is unwise here. Cl should not be made too large, as this will delay the triggering and cause loss of load power and increased r.f.i. A value of 47nF is satisfactory in this circuit. Again, a 250V AC rated component of 'X-type' is preferred.

Rl should have a resistance much lower than the impedance of Cl, so that the triggering delay is minimised. But if Rl is made too low, a short-circuit in, or across, Cl may cause such a severe overload in Rl that it burns the printed-circuit board and adjacent components. A simple fault may thus destroy the circuit. Luckily, a value of $18k\Omega$ will avoid this problem, without delaying the trigger point unacceptably.

R2 is required to adjust the trigger current pulse duration to exceed the minimum recommended value, which is $20\mu s$ for the TIC226D. A value of 47Ω is satisfactory.

The switch S1 can be any form of low-current switch, such as a light-touch push or a reed switch, but it must be insulated for use in direct connection with the mains supply.

We can determine the heat-sink requirements using the final result from Appendix 2. From the device data-sheet, $T_{\rm j~max}=110^{\circ}\text{C}$, $P_{\rm T}=2\text{W}$ at $I_{\rm T}=2.08\text{A}$, and $R_{\rm j-mb}=1.8^{\circ}\text{C/W}$. Allowing for a mica washer, without thermal jointing compound, $R_{\rm mb-h}=2.5^{\circ}\text{C/W}$, $T_{\rm amb}=35^{\circ}\text{C}$ and the derated $T_{\rm j~max}=100^{\circ}\text{C}$.

Then
$$R_{ha} = \frac{(T_{j \text{ max}} - T_{amb})}{P_{T}} - R_{j-mb} - R_{mb-h}$$

$$= \left(\frac{-65}{2}\right) - 4.3 = 28.2^{\circ}\text{C/W}$$

By comparison, $R_{j-a}=62.5^{\circ}\text{C/W}$, from the data-sheet. This is not negligible compared with the heat-sink requirement, and would allow the use of a heat-sink having a thermal resistance of 50°C/W rating. The final design should be checked by measurement.

CORRIGENDA

Vol. 1 No. 1

Combo Amplifier: In the power supply section of the Control Board circuit the junction of C89/C80 should connect to pin 9, junction of D8/D9. Also the arrow going to the PSU supply from the junction of R72/R75 should be designated +15V.

Vol.5 No. 19

Amstrad PSU: In Figure 8, the legend of pcb GD07H is incorrect. The circular shape designated REG1 should be BR1, and the rectangular shape designated BR1 should be REG1. In addition, in the text it is suggested that transformer YK10L could be used. Do not use YK10L as the maximum unregulated DC voltage must be less than +2TV.

Mixer PSU: In the Parts List, a heatsink Penta (FG64) is called for; this is changed to two heatsinks Plastic types (FL68N).

MAPLIN'S TOP TWENTY KITS

	LAST		DESCRIPTION OF KIT	ORDER CODE	KIT PRICE	DETAILS IN PROJECT BOOK
1.	(1)	44	Live Wire Detector	LK63T	£3.50	14 (XA14Q)
2.	(5)	*	U/Sonic Car Alarm	LK75S	£17.95	15 (XA15R)
3.	(2)	_	100W Mosfet Amplifier	LW51F	£17.95	Best of E&MM
4.	(3)	-	Partylite	LW93B	£9.95	Best of E&MM
5.	(7)	-	8W Amplifier	LW36P	£5.95	Catalogue
6.		_		LW78K	£7.95	4 (XA04E)
	(6)		Car Burglar Alarm			
7.	(4)	-	Ultrasonic Intruder Detector		£10.95	4 (XA04E)
8.	(8)	-	Car Battery Monitor	LK42V	£7.50	Best of E&MM
9.	(11)	•	Stepper Motor and Driver	LK76H	£15.95	18 (XH18U)
10.	(9)	-	PWM Motor Driver	LK54J	£9.95	12 (XA12N)
11.	(-)	•	TDA 7000 Radio	LK32K	£11.95	9 (XA09K)
12.	(17)	•	Noise Gate	LK43W	£10.95	Best of E&MM
13.	(14)	•	Burglar Alarm	LW57M	£59.95	2 (XA02C)
14.	(12)	-	Logic Probe	LK13P	£14.95	8 (XA08J)
15.	(16)	•	Light Pen	LK51F	£8.95	12 (XA12N)
16.	(10)	•	15W Amplifier	YQ43W	£6.50	Catalogue
17.	(-)	•	Car Digital Tacho	LK79L	£18.95	Best of E&MM
18.	(-)	•	Syntom	LW86T	£13.95	Best of E&MM
19.	(-)	•	Servo and Driver	LK45Y	£10.95	11 (XA11M)
20.	(20)	*	DXer's Audio Processor	LK05F	£9.95	7 (XA07H)

Over 150 other kits also available. All kits supplied with instructions. The descriptions above are necessarily short. Please ensure you know exactly what the kit is and what it comprises before ordering, by checking the appropriate Project Book mentioned in the list above – see inside back cover for details

╵╸┍┸┪[╵]╱╵┦╸══┦╻╢┞╸╕┍┸ ן :

- Loudspeaker Enclosure Design and Construction. (WM82D) Cat. P52.
- **International Transistor Equivalents** 2. (4) Guide, by Adrian Michaels. (WG30H) Cat. P45.
- Remote Control Projects, by Owen 3. (3) Bishop. (XW39N) Cat. P50.
- Power Supply Projects, by R.A. Penfold. (XW52G) Cat. P49.
- 5. (11) Electronic Music Projects, by R.A. Penfold. (XW40T) Cat. P53.
- How to Design and Make Your Own PCB's, by R.A. Penfold. (WK63T) Cat. P48.
- Radio Control for Beginners, by F.G. 7. (6) Rayer. (XW66W) Cat. P50.
- 8. (10) How to Use Op-amps, by E.A.Parr. (WA29G) Cat. P47.
- 9. (13) Counter Driver & Numeral Display Projects, by F.G. Rayer. CXW34M) Cat. P52.
- IC555 Projects, by E.A. Parr. (LY04E) 10. (9) Cat. P51.
- Mastering Electronics, by John 11. (7) Watson. (WM60Q) Cat. P48.
- 12. (16) How to Get Your Electronic Projects Working, by R.A. Penfold. (WA53H) Cat. P48.
- 13. (-) **Electronic Science Projects,** by O. Bishop. (WA49D) Cat P50.



- 14. (15) Audio Amplifier Construction, by R. A. Penfold. (WM31J) Cat. P52.
- 15. (12) 50 Simple LED Circuits Book 2, by R.N. Soar. (WG43W) Cat. P82.
- Oscilloscopes: How to use them, how 16. (-) they work, by Ian Hickman. (WG34M) Cat. P51.
- Audio Projects, by F.G. Rayer. (WG46A) Cat. P52.
- 18. (14) Electronic Security Devices, by R.A. Penfold. (RL43W) Cat. P50.
- 19. (20) Questions and Answers on Electric Motors, by A.J. Coker and P. Chapman. (RR02C) Cat. P43.
- 20. (-) Easy Add-on Projects for Commodore 64, VIC20, BBC Micro and Acorn Electron, by Owen Bishop. (WP29G) Cat. P64.

These are our top twenty best selling books based on mail order and shop sales during April, May and June 1986. Our own magazines and publications are not included. The Maplin order code of each book is shown together with page numbers for our 1986 catalogue. We stock over 500 different titles, covering a wide range of electronics and computing topics.

UF73Q Amstrd Test 2716/M11. XH65V Amstrad Booklet. XH79L Constructors Guide.

YM15R Gen. Purpose Input

YM168 Gen. Purpose Input

Module (Mono).

Module (Stereo)

Price \$5.96

Price £3.95

Price £6.40

Price £1.50 NV

Price 25p NV

MS P CEI

GD05F Amstrad Controller PCB. Price £11.95 GD06G Amstrad 6x8 Bit Port PCB.

GD07H Amstrad Expansion PSU PCB.

GD10L Play Along Mixer PCB. Pri GD11M Hi-Z Mic (Mono) PCB. Pri GD13P Lead Acid Bat Charger PCB.

GD14Q Stepper Motor PCB. GD18U Active Aerial PCB. GD19V ATU PCB.

GD21X ADA Echo PSU PCB.

GD26D Active Aerial Screen.

LE78E ASCII Keyboard Kit.

LK81C General Purpose Input Kit

LK82D General Purpose Input Kit.

LK84F Tone Control Kit (Stereo). P. LK85G Peak Overload Detector Kit

(Stereo).

LK83E Tone Control Kit (Mono).

LKR9W Headphone Monitor Kit.

LK93B Play Along Mixer Kit. LK94C Hobbyist's Temperature

LEGE Digitiser Controller Kit. LEGTF Amstrad ROM Card Kit.

LKSSG Amstrad Motherbd Kit.

LEGOX Mixer PSU Kit.
LEGOX Hixer PSU Kit.
LEGOX Hi-Z Mic Stereo Kit.
LEGOZA Hi-Z Mic (Mono) Kit.

LESSD Video Digitiser Kit

GD20W ADA Echo PCB

GD2SC Mixer PSU PCB.

LESST Mixer Amp Kit. LESTU Line Amp Kit. LESSV VU Meter Kit.

Controller Kit.

Price £10.95

Price £2.95

Price £1.95

Price £1.95

Price £1.75

Price £1.45

Price £11.95 Price £3.50

Price £5.95

Price £2.50 Price £3.95

Price £1.10

Price £3.50

Price £3.95

Price £4.95

Price \$2.20

Price £4.75 Price £3.95

Price £8.95

Price £6.95

Price £16.95 Price £8.50 Price £4.95

Price £13.95

Price £41.95

Price £29.95 Price £39.95

Price \$29.95

Price \$59.95

The following is a list of all items introduced since our 1986 catalogue, excluding new items in this issue.

AERIALS

YM56L Hi-Tech TV Aerial. Price £10.95 BOOKS .

WP35Q LIN CMOS Design Book. Price £5.60 NV

WP36P Radio Stations Guide. Price £2.95 NV

WP375 Comp Progs Running.

Price £2.50 NV

WP38R Comptr Music Projets.
Price £2.95 NV WP39N Digital IC Equivalents

Price £4.95 NV WP40T Linear IC Equivalents

Price £4.95 NV

WP41U Proj in Microelect. Price 54.95 NV WP42V Wrd Proc Amstrad 8256, 8812. Price 55.95 NV

WP43W Add-on Proj for Amstrad 464, 664 6128 & MSX. WP44X More Adv Elec Music Price £2.95 NV

Price £2.95 NV

WP45Y Linear & I/F Circuit Price £8.00 NV WP46A Top Pocket Micro-Elec

Dictionary. Price
WP47B Scanners. Price
XW30H Cost Effective Construction. Price £1.50 NV Price £7.95 NV

EW31J Projects for Car/Garage.
Price \$5.50 NV

BOXES

YM51F Instrument Case NM2H.

Price £14.95

Price £5.95 NV

CAPACITORS Price 95p UF71N Fltr 10.7MHz/50kHz. CONNECTORS Price £4.95

FASTU 2x25 way Edge Con. FA90X PCB 6 pin DIN Skt. FA93B Gold Phono Line Skt. FA94C Adaptor W. OPTO ELECTRICAL

FA95D Plastic Lens

Price 58p Price 65p

Price 48t

UF72P Ultrabri Red LED Min. PCB EQUIPMENT

XH66W Transfer Sheet 1 Price 45; Price 45p XH67X Transfer Sheet 4. XH68Y Transfer Sheet 8. Price 45p XH69A Transfer Sheet 9. XH79M Transfer Sheet 14. Price 45p Price 45p XH71N Graphic Sheet Black Price 45p Price 45p XH72P Graphic Sheet White. XH73Q 2.5mm Transfer Sheet Bla

Price 45p XH74R 2.5mm Transfer Sheet White.

Price 45p XH75S 3.5mm Black No's Resist Transfers.

Price 45p XH76H 3.5mm White No's Regist Transfers

XH777 4.2mm Alpha-Numeric Black Resist Price 45p XH78K 4.2mm Alpha-Numeric White Re Price 45p

YM62S 200g Positive PCB Photoresist Price £3.98

PROJECTS AND MODULES

FA85G Temperature Controller Front Panel. Price £1.80 FA86T 50 way Amstrad Cable Price £7.99

Price 55p Price 45p Price £3.95 FASSV Amstrad Front Panel. FA89W Amstrad Rear Panel. FA91Y Mapsat Front Panel. FA92A Mapsat Bracket.
FA99H Active Aerial Front Panel. Price 80g Price £3.95

FD07H ATU Switch Mounting Plate Price 78p

FD10L 6BA x 1/4in. Threaded Spacer. Price 88n Price £3.95 Price £8.50 FD11M Tuner Front Panel GB96E ASCII Keyboard PCB. Pr. GB97F IBM Golfball Printer I/F PCB.

GB99H Amstrad Extendiboard. GD00A Hobbyist's Temp. Controller PCB. Price £2.95 Price £2.95 GD01B High Volts PCB. GD02C Digitiser PCB.
GD03D Digitiser Controller PCB. Price £11.95

GD94E Amstrad Motherboard.

LK99E Sat Receiver Kit.
LM00A Sat Aerial Kit.
LM01B L/Acid Bat Chrgr Kit. Price £39.95 Price £19.95 LM02C Amstrad 6x8 Bit Port Kit. Price £24.95 LM03D Amstrad Expansion PSU Kit. LM04E ADA Echo Kit LM05F Active Aerial Kit. LM06G ATU Kit.

Price £4.95 Price £54.95 Price £44.95 Price £29.95 RASSG Programmed Golfball EPROM 2716/M10. Price \$9.95

YM17T Tone Control Module (Mono).
YM18U Tone Control Module (Stereo). YM19V Peak Overload Detector Price \$7.75 TM20W Mixer Amp Assembled Price \$8.50 Price \$5.50 YM21X Line Amp Assembled. YM22Y VU Meter Assembled. Price £10.95 YM23A Headphone Monitor A mbled Price £8.95 YM24B Mixer PSU Assembled. Price £19.95 Price £9.95 Price £5.95 Price £59.95 YM25C Mic I/P Stereo Assem. YM26D Hi-Z Mic Mono Assem YMS7M Amstrad Contril: Asm. YMS8N Aerial Rod. Price 80p YM59P Set Recvr PCB Ass YM61R Pre-drilled Tube. Price \$44.95 **PROTECTION** YM52G The Fly. YM53H The Spid Price \$24.95 Price £34.95 Price £44.95 YM54] Alarm Cash Box. YMSSK Alarm Jewellery Box. SEMICONDUCTORS OY80B 8186 I/O Ports, 256 byte RAM and 14 bit programmable Timer IC. Price £1.95 SWITCHES AND RELAYS FA97F 1-Pole 12-Way Stackable PCB Mounting Rotary Wafer. Pric FA98G PCB Mounting Rotary Wafer Price £1.45 Price 50p Coupling Shaft. TEST GEAR FA96E Min Probe Clip Set. YJ82D MF100 Freq Counter. Price £2.95 Price \$89.95 WOUND COMPONENTS FD00A Toko CAN1A380EK. FD01B Toko RWR331208. FD02C Toko KANK3333R. Price 88p Price 58p Price 55p

Maplin Magazine September 1986

FD03D Toko KANK3334R

TALOG

The price changes shown in this list are valid from 11th August 1986 to 8th November 1986. Prices charged will be those ruling on the day of despatch.

For further details please see 'Prices' on catalogue page 15.

Price Changes

All items whose prices have changed since the publication of the 1986 catalogue are shown in the list below. Those where the price has changed since the last Price Change Leaflet (dated 12th May 1986) are marked 'e' after the price.

A complete Price List is also available free of charge - order as XF08J.

Key

Not yet available. NYA

DIS TEMP

Discontinued.
Temporarily unobtainable.

Out of stock; new stock expected in month shown. FEB An additional £5.50 carriage charge must be added. NV

Indicates that item is zero rated for VAT purposes. See 'Amendments To Catalogue'. Note that not all

items that require amendments are shown in this list.

1986 VAT Catalogue Inclusive Page No. Price	1986 VAT Catalogue Inclueive Page No. Price	1986 Catalogue Page No.	VAT Inclusive Price	1986 Catalogue Page No.	VAT Inclusive Price	1986 Catalogue Page No.	VAT Inclusive Price
AERIALS	BOOKS	Page 71 YRSSH PCB Brackets	DISA	Page 80 BH16S Systofiex 4mm White	DISa	K803D Wizerd of Wor Disk K899H Armour Assault Disk	DIS
Page 30 XQ23A Mushkitler FM1063£14.49	Page 43 R022Y Book NB345TEMP+ XW12N Book NB365TEMP+ WA44X Undrstnding Auto Elec£13.50 NV+	YRSSH PCB BracketsFX98E Cestors	£3.96	BH17T Systoffex 4mm Yellow Page 81	DIS•	BO97F Battle Shiloh Disk	DIS
X025C Mushkiller FM 1085 £22.30 \$X027E Mushkiller FM 1087 £29.45 e X029G Trucolour TC10 Brp A £11.25	Page 44	CABLES		BH28D Safix 4	9p	BG82D Midway Campaign Disk BG84F NA Convoy Raider Dsk.	DIS
X030M Trucolour TC10 Grp B	WA20W Understding Electrics£13.50 NV= WA21X Understding Dig Elec£13.50 NV= WG11M Book JW748£11.45 NV= WK81R Electrics for Techs£8.50 NV	Page 74 PASSL 100m Bell Wire Bik	62.00	CAPACITORS		KR02C Tigers in Snow Disk	DIS
XG23A Trucelour TC10 Grp E	Page 45	PAS7M 100m Bell Wire Blu PAS8N 100m Bell Wire Brn PAS8P 100m Bell Wire Grn	£2.00			Page 106 BG66W Acquire Cessette YL33L Fest Gemmon KF79L Kids 3 (4 progs) Dis Page 106	DIS•
Page 31	WA24B Undrating Communities £13.50 NV= WP28F Data Communications £13.50 NV= WM59P Linear Electronics £8.50 NV= R088A Book F1985	PASIR 100m Bell Wire Orn PASIR 100m Bell Wire Red	£2.00	Page 86 WX02C Mica 5pF WX030 Mica 10pF WX05F Mica 22pF WX07H Mica 33pF WX08K Mica 47pF	22p •22p •22p •	KE43W Music Leasons Diek	DIS
X038P Trucolour TC18 Grp B	Page 46	PA63T 100m Bell Wire Yel BL46A L/C Wire Black	£2.00	WX07H Mica 33pF WX08K Mica 47pF	22p •22p •22p •22p •22p •22p •	BG91Y Stocks and Bonds Css. KF56L Typo Cart	DIS •
XU38R Extragain XG5	RH35Q Book BP202 TEMP◆ RL08G Book N80740 £5.50 NV RH05F Book BP7 950 NV RH21X Book BP27 950 NV RH53H Book BP160 £2.50 NV			WX13P Mica 100pF WX14Q Mica 120pF	26p •	BG11M Bob's Business Cass	DIS
XQ40T Extragain X68 GroupB	RH21X Book BP27 950 NV RH53H Book BP160 £2.50 NV	BL50E L/C Wire Gray	98p •	WX18S Mics 180pF WX17T Mica 220pF	26p •	BG12N Bob's Business Disk BG08J Mini Word Procr Cass BG09K Mini Word Procr Disk YG52G Statistics Cassette	£4.95
Page 32	WA10L TI Linear Circuits £10.00 AV WA14Q TI TTL Data £10.00 AV WP31J TTL Data BDOK £9.00 AV WA18U TI Dig IC Guide DIS WG58N Book FT1199 £14.20 AV	BL48C L/C Wire Brown BL49D L/C Wire Green BL50E L/C Wire Green BL50E L/C Wire Grey BL51F L/C Wire Print BL52G L/C Wire Print BL53H L/C Wire Print BL53H L/C Wire Violet BL55L L/C Wire Violet		WX09K Mica 47p F WX113P Mica 88p F WX13P Mica 100p F WX14Q Mica 100p F WX14B Mica 150p F WX18S Mica 150p F WX18T Mica 150p F WX19T Mica 250p F WX19T Mica 230p F WX19T Mica 230p F WX19T Mica 230p F WX23A Mica 470p F WX23C Mica 1000p F WX23C Mica 1000p F	35p+	VGASA Convergation Spenish	nic
X0526 Caratenna CA7 £10.456 8W42V Univ. Clamp Type 1 £1.706 8W43W Mast Bracket Type 2 £2.406 X053H Mast Bracket Type 3 £7.956 X054J Mast Bracket Type 8 £12.456	WA18U TI Dig IC Guide	BL55K L/C Wire White BL56L L/C Wire Yellow BL00A 7/0.2 Wire 10M Blk	98p ቀ	**************************************	42p ♥	YG68A Pilot Consumer BG64U The Next Step Disk	DIS
X053H Mast Bracket Type 3	WA15R TI 9900 Data£12.00 NV	PA28F 1000m 7/0.2 Wire Bik		Page 90 ★FB53H Axial 100uF 200V	£1.56	KF88V Graphics Machne Disk KF90X Instedit Disk	DIS
BW44X Mest Bracket Type 14	WA08G TI MDS Memory Data£10.20 W/• WA13P TI Interface Deta£10.80 N/V WG87U Book BP101	PA46A 100m 7/0.2 Wire Blu PA29G 1000m 7/0.2 Wire Blu	£2.40	Page 92 WL89A Trimmer 10pF WL70M Trimmer 22pF WL72P Trimmer 85pF	24p •	KF71N Charctr Graphes Disk KF73Q GTIA Grphes 9-11 Dis KF76S Sound Effects Disk	DIS
X057M Lashing Kit Type 7£17.96◆ X058N Lashing Kit Type 8£12.46◆	RR27E Book NB2026 DIS	PA47B 100m 7/0.2 Wire Bm PA30H 100m 7/0.2 Wire Bm	£2.40	Page 94		KF78S Sound Effects Disk KF78H Memory Map Tutri Cas KF77J Memory Map Tutri Cas KH59P Sam Tutorial Disk/At KH69W Basic Prog Tools Disk	DIS•
X0800 Mast 0 £3.86 X083T Mast M £8.50 XX081R Mast E £7.45 XX081R Mast E £1.859	WM600 Mastering Electronic£3.96 NV Page 49	BL03D 7/0.2 Wire 10M Grn PA48C 100m 7/0.2 Wire Grn	£2.40	HX600. Crystal Socket 25u HX61R Crystal Socket 6u		KH86W Basic Prog Tools Dsk KH85V Fancy Fonts Disk /At	DIS
Page 33	R029G Book BP49 £2.50 NV RH25C Book BP32 DIS XW52G Book BP76 £2.50 NV	PA31J 1000m 7/0.2 Wire Grn BL04E 7/0.2 Wire 10M Gry PA49D 100m 7/0.2 Wire Gry		COMMUNICATIONS		Page 107 BC38P Cave Hunter	DIS
XB54.J Aerial Rotator £49.95 e BW46A Masthead UP1300/W £14.95 BW48D Masthead UP1300/V £14.95 BW50E Power Unit PU1244 £18.95	Page 50 WGMO Rook RP95 £1 95 AV	PA32K 1000m 7/0.2 Wire Gry BL05F 7/0.2 Wire 10M Drn PA50E 100m 7/0.2 Wire Orn	£21.95	Page 95 XG10L 12V 3A Power UnitYB00A Low-Pass RF Filter	DIS+	BC34M Cosmic Invaders BC79L Galex Attax Cart BC35Q Ghost Attack BC33L Meteoroids	DIS
Page 34	WG18U Book HD748 DIS WK45Y Undrstn Phone Eletrn £13.50 N/Ve WG94C Book FT1349 DISe	PA33L 1000m 7/0.2 Wire Drn BL06G 7/0.2 Wire 10M Pnk	£21 95	Page 96		Page 108	
YX73Q Amp XB1U £23.50 BK086 Amp VX18 £23.50 YQ22Y Xtra Set Amp £23.50 BK75S Xtra Set 3 Amp £27.95 BK76H TV Amp XB12 £17.95	Page 51			LB72P Intercom 2-Station		KL62S Word Proc Ces (32) KL66W Number Gulper Ces 32. KL75S Forth Cess (32) BC61R Crsh Crmbl Chmp Disk. BC57M Temple Of Apshai Dis	DIS
BK76S Xtra Set 3 Amp	XW07H Book BP57 DIS RH18U Book BP24 TEMP	BL07H 7/0.2 Wire 10M Red	£2.40 £21.95	COMPUTERS	DIS	BC81R Crsh Crmbl Chmp Disk. BC57M Temple Of Apshai Dis. BC58N Uppr Rchs Apshal Dis.	DIS
*BW51F Diplexer UF22	RF12N Book BP42 £1.95 AV WG43W Book BP87 £1.35 AV WP00A Fb Dp Laser Handbk £18.20 AV WA0BJ Ti Dptp Data £5.00 AV LY05F Book BP45 £1.96 AV	PASSH 100m 7/0.2 Wire Vio PASSP 1000m 7/0.2 Wire Vio	£2.40	Page 100	COR 15	KS03D M5 Tank Battalion KS04E M5 Step Up KH56L Pool Cass (SP) KK36P VIC Aggressor Cert	DIS
Page 35	WA08J TI Opto Data	PAS4J 100m 7/0.2 Wire Wht PA37D 1000m 7/0.2 Wire Wht	<u>£2.40</u>	YJ34M MPF-1P Speech Synth Page 101 XG84U TV Monitor V7001		Page 109	
HX87U Surfaca Co-Ax Outlet 9800 BW56K Flush Co-Ax Outlet £1.550 BW56L Fish Dbi Co-Ax Outlt £2.650	Page 53	BL10L 7/0.2 Wire 10M Yel PA56K 100m 7/0.2 Wire Yel PA36R 1000m 7/0.2 Wire Yel	£2.40	XG65V TV Monitor CM14 Page 102	£239.95◆	KK10L Crah & Cmp + 16K Cass KK09K Sword Frgoal 16K Cass. AC96E VIC Writer Olsk BC12N Know Your Own IQ BC14Q Know Yr Parsonality	DIS
Page 36	WG82D Book FT1364 £9.45 AV WG88A Book AG902 £10.95 AV WG40T Book BP05 DIS XW40T Book BP61 DIS XW40T Book BP74 £2.50 AV	FA26D 16/0.2 Wire 10M Blk PA64U 100m 16/0.2 Wire Blk FA27E 16/0.2 Wire 10M Blu	£4.00	YX67U S/S D/D Disk 5.25 YJ00A 10 S/S D/D Disk 5.25 FT80B D/S D/D Disk 5.25 YJ70M 10 D/S D/D Disk 5.25 FT81C S/S Q/D Disk 5.25	£1.75+ £15.95+ £1.95+	BC12N Know Your Own IQ BC14Q Know Yr Parsonality	DIS
YG41U 27MHz Rubbar Duck	Page 54	PA65V 100m 16/0.2 Wire Blu FA28F 16/0.2 Wire 10M Bm	64.00	YJ70M 10 D/S D/D Disk 5.25 FT81C S/S Q/D Disk 5.25 YJ71N 10 S/S Q/D Disk 5.25	£18.95+	BC22Y MM Date 1	DIS •
Page 38 Y.185W 1Ah Land Acid Bet 6V	WASOX Book NB112DIS RF18U Book BP43DIS	PA87X 100m 18/0.2 Wire Gm	£4.00	FT82D D/S Q/D Disk 5.25 YJ72P 10 D/S Q/D Disk 5.25	£2.50 •	KM52G VIC Pixel Power Cass AC55K Programmers Aid	DIS •
YJ67X 1.2Ah Ld Acid Bet 8V £7.95® XG78K 15Ah L/Acid Bet 12V £41.96® XG79L 24Ah L/Acid Bet 12V £48.96® XG80B 38Ah L/Acid Bet 12V £74.95®	Page 55 R033L Book BP52 DIS	FA30H 18/0.2 Wire 10M Bry PA68Y 100m 18/0.2 Wire Bry FA31J 16/0.2 Wire 10M 0rn PA69A 100m 16/0.2 Wire 0rn	50p • £4.00	YJ730. 10 S/S D/D Disk 3.5 YJ74R 10 D/S D/D Disk 3.5 Page 103	£28.95 •	CONNECTORS	
Page 39	WA61R Book FT1408	FA32K 16/0.2 Wire 10M Pnk	50p♥	Addressed Free Pro 6 of 14 of the	£8.95	Page 111 HF45Y 2mm Socket Blue HF34M 4mm Petch Cord	20p
FKS4J Blue Seal R03B 24p FKS5K Blue Seal R8B 20p FKS6L Blue Seal R14B 33p FKS7M Blue Seal R20B 37p FKS6N Blue Seal R20B 37p FKS6N Blue Seal R20B 7p	Page 56 WM88V Fault Diag Dig Syst£8.00 NV	PA70M 100m 16/0.2 Wire Pnk FA33L 16/0.2 Wire 10M Red PA71N 100m 16/0.2 Wire Red FA34M 16/0.2 Wire 10M Vio	£4.00 50p ♥ £4.00	UG06F Atari User Grp Mag 5 UG08G Atari User Grp Mag 6	£1.00+	Page 112	
FK57M Blue Seal R208 37p FK58N Blue Seal PP38 73p FK81R Silver Seal R20S 53p		PAZE TUQITI 10/U.2 VVIEW VIO		KB32K Dregon's Eye Disk	DIS	FT94C 2.5 Stereo Ches Skt FT93B 2.5 Stereo Line Skt	DIS•
FK82S Silver Seal PP3S	XW986 Book FT1070£14.20 NV RD02C Book Sybex C207 £19.95 NVe	FA360. 16/0.2 Wire 10M Wht PA730. 100m 16/0.2 Wire Wht FA36P 16/0.2 Wire 10M Yel PA74R 100m 16/0.2 Wire Yel	£4.00 50p ● £4.09-	KF02C Helifire Wrrior Cess KF03D Helifire Wrrior Disk	DIS	Page 115 HH07H Co-ex Plug AlyYW08J Co-ex Plug PlasHH08L Co-ex Socket Page	32p◆
FK86V Gold Seel LR14		Page 75		BQ83E Crush Crumble Cass BQ84F Crush Crumble Disk	£4.95	HH08J Co-ax Socket Pan HH09K Co-ax Socket Flush YW09K Co-ax Line Skt HH11M Co-ax Conn	35p • 35p • 40p •
FIGSTX Bold Seal 8LF22 £2.05 FIGSY Gen Purpose No.8. 41p FIGSA Gen Purpose 1289 85p YJISU Gen Purpose PJ986 £2.55	XW808 Book C202 £16.95 NV XW81C Book D302 £13.96 NV XW70M Book M3. £19.95 NV WKC30H Programming 6809 £15.96 NV+	XR39N Zip Wire XR60Q HD Loudspeaker Cable XR72P HIFI Loudspkr Cable XR89W 4-Wira Burgler Cable	9p • 40p •			Page 116	
V.J19V Gen Purpose 991	Page 59	Page 76		KF15R Morioc's Tower Disk BQ21X Rescue Rigel Cass BQ24B Star Warrior Cass KB35Q The Nightmere Disk	DIS	HH18S FM Aeriel Plug HH17T BNC Plug FJ72P BNC R/A Plug HH18U SNC Socket QY22Y BNC Earth Teg	£1.20+
		XR86W 4-Wire Phone Cable PA78H 100m 4-Wire Phone XR74R Flat IDC Cable 20wey XR75S Flat IDC Cable 34way	12p	KB35Q. The Nightmera Diak B965V Space Shuttle Mod 1	DIS	HH18U BNC Socket QY22Y BNC Earth Teg	£1.05*
YJ23A Gen Purpose HP992	Page 60 £14.95 NVe XW79L Book C300 £14.95 NVe WG48C Book HD162 £15.25 NV XW90D Book HD782 £12.75 NV WK66V BBC Assembly Lang £8.95 NV WK88V Mechine Code BBC TEMPe	XR75S Flet IDC Cable 20way XR76H Flat IDC Cable 26way	39p •	BG60E Angle Worms Cassette. KF66W Ardi-Sub Patrol Cass KF67X Ardi-Sub Patrol Disk. KF64J Attck Ep-Cyg-4 Cart KB75S Beja Buggles Disk	DIS	YW00A BNC Square Socket YW02C BNC Straight Adaptor. YW03D BNC T Adaptor	£1.05• £1.95•
FM04E Trans Pwr PP7 9V£1.54	WM53H DIY Robotics BBCDIS	XR77J Flet IDC Cable 40way XR79L Flet IDC Cable 50Way XR808 Cir Cd IDC Cable 16W	64n e	KF54J Attck Ep-Cyg-4 Cart KB75S Beja Buggles Diek	DIS	FA11M Phono Skt/BNC Plg BW81C Plug PL259	£1.10+
YJ248 Trans Pwr PP8 6V	Page 61 WM74R Interfece Proj BBC	PA39N 30m Cir Cd IDC 16W XR81C Cir Cd IDC Cable 20W	£31.50 •	KB62S Bug Off Disk		FA11M Phono Skt/BNC Pig BW81C Plug PL259 FJ730. UHF R/A Plug BW82D UHF Reducer Smell BW83E UHF Reducer Large HJ95D RA PL259 Plug BW84F UHF Socket Round	24p •
YJ248 Trans Pwr PP8 8V £5.55 FM06F Trans Pwr PP8 8V £1.56 FM066 Trans Pwr PP1 4.5V2 £2.25 FM13P Gold Seal LR1	Page 62 WM71N Atari 600XL Prog BkDIS	XR82D		Page 105 KB80B Clwns & Ballons Disk	DIS+	BW84F UHF Socket Round BW85G Socket S0238	85p •
FM08J Photo Batt BLR122	Page 63	XR84F Cir Cd IDC Cable 40W PA43W 30m Cir Cd IDC 40W XR85G Cir Cd IDC Cable 50W	98p+ £77.95+	KB808 Clwns & Ballons Disk KF57M Fortune Hunter Cart BQ84U Ghost Hunter BG78K Guns Fort Defiance BG38R Haunted Hill Cass	DIS	Page 117	
Page 40	WA40T Your Atari Computer£19.95 NV WK40T Spctrm Benners M/CDIS Page 84	PA44X 30m Cir Cd IDC 50W	£97.95Φ	ROST K-Razy Sht Out Cart	DIS	BW87U UHF Straight Adaptor BW88V UHF T Adaptor RK0DA UHF Female Y Adaptor. RK01B UHF Adaptor FFLA RK02C UHF Adaptor FMLA YW04E Adaptor 239 YW05F Adaptor 239	£2.95 e £2.95 e £1.96 e
FM140 Merc Bett PX1/RMIN £1.22e FM19U Merc Batt PX/RM625 65pe FM20W Merc Batt PX675 55pe FM21X Merc Batt RM13H 34pe FM22Y Merc Batt RM13H £1.04e	WM04E Intro Spec Machina	XRIGK HD Mains BlackXRIGK HD Mains BlackXRIGK HD Mains WhiteXRIIM HD Mains Orange	54p •	BG49D Lunar Lander Disk KF01B Monster Maze Cart KF45Y Mountain King Cart	DIS	RK02C UHF Adapter FMLA YW04E Adapter 239 YW05F Adapter 259	£2.25•
		★BL72P Stretchflex 6A	54p • £4.95	KB14Q Neutilus Disk	DIS	FJ79L N Type Chessis Skt FJ80B N Type Chess Skt Sq	£1.95+
FM25A Merc Bett BP675	WG61R Book HD192£14.35 NV	Page 78 XR15R Min Screened	18p+	KB08J Preppie Disk KF56K Princess & Freg Cart KB48C Rear Guard Disk	DIS	FJ82D N Male to BNC Adent.	£2.95+
FV88A Ni-ced C 1200mAh£2.45●	BOXES Page 66	Page 79		BQ38P Shoot Gallery Cass BG97F Shootout Galaxy Cass KF27E Sky Blazer Disk	DIS	FJ84F BNC Female to N Fem. Page 118	
Page 41 FV70M Ni-cad D 1200mAh£2.85 Y6030 Ni-cad D 4000mAh£4.80 £4.80	**YK48C Snep Box B1	XR21X Cable TwinXR23A Cable Qued	45p ◆ £16.95	KB56K Space Games Cass KB54J Stratos Disk	DIS	FJ70M 8 Pin EIA Plug FJ71N 8 Pin EIA Skt. FJ41U Scart Plug (21 way) PV89W SCART Socket. RK52G 10 Way Line Skt.	£2.75 • £2.50 • £1.24 •
HF27E Clips PP9 27p HF28F PP3 Clip 12p		XR87U White Low-loss Coex	20p •	BG18U Threshold DiskBQ37S Thunder Island	DIS	FV89W SCART Socket RK52G 10 Way Line Skt	48p • £2.90 •

1906 Catalogue ^l Page No.	VAT Indiusive Price	1986 VAT Cetalogue Inclusive Page No. Price	1985 Catalogue Page No.	VAT Inclusive Price	1986 Catalogue Page No.	VAT Inclusive Price	1986 Catalogue Page No.	WG Incheles Price
RK53H 10 Way Line Plug FM60E Lite Audio Plug 2-Way FK22Y Lite Audio Skt 2-Way	£3.70 e	Page 150 HK23A HD-1250 Dip Meter	Page 179		LICSAM 2.8kW Pwr Critir ICt LICS60. Fluor Tube Dryr ICt	£19.95	Page 258	
FK22Y Lkg Audio Skt 2-Way FM51F Lkg Audio Plug 3-Way FK23A Lkg Audio Skt 3-Way		Page 152	HK87X PS2406 Hand-Fre	nter£139.95 q PSU£12.95 nne£8.95	Page 231	£0.05	Page 259	
FM528 Lkg Audio Plug 4-Way FK248 Lkg Audio Skt 4-Way	66p •	HC91Y Hearthkit CD-1015	Page 180 HK960 16-4244 Osc Calib	rtr£149.95	GP000 2716/M5 GB06F Connect PCB	£4.95	GR21X CM	e Wire Det Kit
FM53H Lkg Audio Plug 5-Way - FK25C Lkg Audio Skt 5-Way FM54J Lkg Audio Plug 6-Way	80p#	Page 153 HK80B NE-2112 Heat Sniffer£19.950	HT526 Heathlitt IP-2780. HK53H IP-2718 Tri-Otpt P HK360. IP-2728 Low-Volt	£179.95 SU£118.96 PSU£49.95			Page 260 LK066 Sw	weo Osc ICt
FK26D Lkg Audio Skt 6-Way FK27E Lkg Audio Plug 7-Way FK26F Lkg Audio Skt 7-Way	BEnd	Page 154 HK02C GD-49 Ultra Intruder	Page 181 HG46A Heathkit IP-2717/	£188.95	LW82D Digi-Tel Main Kit UG78 Digi-Tel Expdr IGt	£129.95 £148.95•	GB30H Pro GB31J Pro LK13P Loc	be Upper PCB
FK30H Lkg Audio Skt 8-Way	£1.40=	HC05F Heathkit GD-1183£19.95	HK36L ID-4001 Weather	Cmpr£398.95	Page 232 XX478 Train Corri Front Pol BA72P Train Common PCB		Page 261	pic Probe Kit£14.95 ser PCB£1.80
FT91Y Lkg Audio Plg 10-Way FT92A Lkg Audio Skt 10-Way	£7.95+	HK11M ETW-31008 Assembled£184.95e Page 158	KNOBS Page 182		GA758 Train Receiver 2 PCB LW81R Train Common/PSU IQL	£1.20		q Cnt Front Panel
Page 119 BW89W XLR Line Plug	£7.05+	HM06F EE-1003 Anig Dan Crs£88.65 Page 159 HM27E EE-110 Laser Course£98.95	RX018 Knob NK2 Page 183	54p*	LW62S Train Control Kt LW63T Train Revr1 ML926Kt LW64U Train Revr2 ML826Kt	£11.95		q Ctr Display PCB
	£2.40•	Page 160	HB28F Knob R51 HB29G Knob R52		LW88Y Train Royr1 ML827Kt LW89A Train Royr2 ML927Kt GAB4F Remote Data Ltch PCB.	£10.95* £10.95*	Page 282 6B09K Mo GB10L Mo	dem Main PCB£5.95 dem PSU PCB£1.80
Page 120 YXSOX PC DIN Skt 2-pin	22p •	HM32K ETS-4200 Laser Trnr	HB31J Knob R54 HB32K Knob K105 Page 184		GASS Data Encoder PCB GASST Data Decoder PCB	62.00	Page 263	dem Krt£54.96
Page 121 RK800. D-Range 9 Way Plug BK58N D-Range 15-Way Plug	57p◆	HK91Y EWA-3400 Assembled £279.95 HM15R EC-2001 Cmptr Fndmnt £98.95 MD28D Heathkit EC-2002 £39.95	*RX29G Spindle Coupler RX30H Ext Spindle	£1.20	GA87U IR Tx PCB		GB84F Ma LK88Y Ma LK17T RS:	ins Tx/Rx PC8£2.95+ Ins Tx/Rx Dryr IQt£32.95+ 232/TTL Cnystr kit£8.90
YQ48C D-Range 25-Way Plug FV71N D-Range 37-Way Plug	£1.08 • £1.55 •	Page 164 MD31J Heethkit EC-2003	MICROPHONES		Page 233 FT40T Cntrl-A-Train Fr Pan	£1.85	Page 264	
RK61R D-Range 9 Way SktBK58P D-Range 15-Way Skt	88p+	Page 166	Page 186 FK43W Omni Insert Dyn D	NIS £1.10	LK84U Control-A-Train Kit GB77J Mains Cntrllr PCB Page 235	£13.96	GB39N BB	CPU Module PCB
Y0480 D-Renge 25W Socket FV72P D-Renge 37-Way Skt FV75S D-Renge 50-Wey Skt	£1.60+	HS806 ETS-18 Hero Assembld£2149.90 HM28D ET-18-9 Hero 1 Basic£48.95 Page 169	Page 187 YB33L Electret Casette N		GA19V Batt Mon PCB LK42V Car Batt Monitor	£1.30	LK10U Dra	gon I/O PCB£5.50
F925C RA D-Range 8-Way Skt	£1.35+	KA00A Hero Jr Kit RTR-1-1£299.95 Page 170	Page 188 YW77J Mic Hidr Screw-F	ix DIS	XX41U Ign Mtg Plets		Page 285 GB45Y Orio	C Talkback PCB£4.95 C Talkback IQt£21.95
FG27E RA D-Ringe 25-Wey Skt FG86W RA D Range 9 Way Pig FG87X RA D Range 15 Wy Pig	£1.50•	MD38P Heethkit RTC-1-9	YW78K Mic Hidr Adhesiv Page 189		Page 236 GASSG Car Burgler Airm PCB LW78K Car Burgler Airm PCB	£1.40	GB56K Orio LK40T Orio	C Ma-Mo L/F PCB£4.50 C Maplin Mo IFace£11.95 •
FG68Y RA 0 Range 25 Wy Pig Page 122	£2.40+	Page 172 HM11M EB-6140 C of E Text	YW71N UM Tie-Clip Mic Page 192		EW78K Car Burgir Alarm Kit BA40T Car Aerial Ester PCB GB93B U/Sonic Car Airm PCB.	£1.80		8/M8 EPROM Shp IF
*YRSEN Edge Conn Foot Open Page 123	24р	HM14Q EB-6140-30 C E Parts	YW78H Extra Hgt Mic Sta XB46Y 5-Foot Mic Stand	ndDIS	Page 237 GA78H MPS Meter Main PCB	£2.20	Page 266 0Y57M 271	6/M7 £9.05
*BX98E Minicon Latch PI 2w *BX98E Minicon Latch PI 3w *YW11M Minicon Latch PI 4w	18p 24p 28p	HM18S EB-6101 DC Elec Text£19.95 AV HM17T EB-6101-40 DC Wkbk£10.95 AV HM18U EB6101-50 DC instr£9.95 AV	MUSICAL & EFFE	CTS	BA77J MP6 Meter Disply PCB. LW87X MP6 Meter ICt	£1.80 £84.95*	LIC21X Spc	trev/R\$232 Intf kt
*YW12N Minicon Letch PI 5w	35p 36p	HD55K Heathkit EEA-3101A£19.95 HM19V EB-6101-30 DC Perts£24.95	Page 194 X683E G. Equier + Analy	ser£139.95•	GB83E 4 Ch Servo Cntrl PCB	£7.95	TIMOTO OPE	rm I/O Critri Asem£19.96
*YW13P Minicon Letch PI 9w *RK88W Minicon Letch PI 10w *YW14Q Minicon Letch PI 12w	80b	HM22Y EB-6102 AC Elec Text	Page 195 AFIG DE1200 Digital De	lay£224.95*	LK61R 4 Ch Servo Cntrir Kt Page 238 LK46Y Servo & Driver Kit		Page 267 LIC26D Spe	ectrum ADC IQt£32.95 ·
★BH61R Minicon Latch PI 17w ★BK86G Minicon Latch PI 18w ★FY92A RA Leh Minicon PI 2w	80p 85p	HD50N Heathick EEA-3102A £19.95 HM25C EB-6102-30 AC Parts £19.95 AV HM26F EB-6103 Semicnd Text £19.95 AV	OPTO-ELECTRICA	L	FJ54J TU 1000 Rear Penel GB67X RTTY Terminal PCB	£10.95 £2.59 £9.95	go-/o ape	C PCB
★YW15R RA Lch Minion Pt 3w ★FY91Y RA Lch Minion Pt 4w	42n	HM29G EB-6103-40 Sami Withk£10.95 AV	Page 197 FF67X Fluted Lhidr Clear	DIS=	Page 239		GB40C Spe LK29G Spe	ictrum Kbd Con Pcb£2.20 ictrum Kybd Klt£36.95 e im Kybd Adptr Klt£8.95
⇒RK67X RA Lch Minion PI 5w ⇒FB99H RA Lch Minion PI 6w ⇒YW18U RA Lch Minion PI 6w	48p 58p 64p	HD61R Heathkit EEA-3103A £19.95 HM31J E8-6103-30 Semi Part. £19.95 HM34M EB-6104 Elc Cir Text £19.95 AV	Page 198 WL76H Bulb MES 3.5V	380	GB50E TDA 7000 Radio PCS LK41U 80m Conv fb: Kit Page 240	£19.95◆	LK16S ZX8	11 1K RAM Extrasion£7.95
*RK68Y RA Lch Minion Pl 10w *YW19V RA Lch Minion Pl 12w *FT87X RA Lch Minion Pl 17W	86p	HM360, EB-6104-40 Elec Withk£10.95 AV HM36P EB8104-50 Elec Instr£3 96 AV	WL78K Bulb MES 6V 0.6V FM99H Reader's Light	/	XG15R Stereo Amp Chassis GA71N Stereo Amp PCB	£7.95	LICZZY VIC	20 Extendiboard £34.95 20 Talkback PCB £3.95 20/RS232 Intice £3.80
#HR59P Maco Itch Hea 2way	98p	HM40T EB-8105 Test Eq Text£19.95 NV HM41U EB-8105-40 Test Wkbk£10.95 NV	Page 199	£12.95	BA78K Stereo Amp Sw PCB LW71N 25W Stereo Amp ICt LW77J Amp Remote Cntrl ICt	£89.95+	Page 269	
*BX97F Mncn Ltch Hsg 3-way Mncn Ltch Hsg 4way *BH66W Mncn Ltch Hsng 5-way Mncn Ltch Hsng 5-wa	9p 10p 12p	HM42V EB6105-50 Test Instr	±0.Y866 Ultrabri LED Red 8 ±0.Y866 Ultrabri LED Red 8 Page 201	itd	Page 241 XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX	£2.20	LW72P ZX8 GA90X I/O LW78H ZX8	11 Ext Kyboard PCB
★YW23A Minon Litch Henri 8-wey	18n	HM46A EB-6106 Commun Text £19.96 NV HM47B EB-6106-40 Comm Wkbk £10.95 NV	BY65V Red Bergraph Dai YB33L Green Bargraph D	py£2.25 slpy£2.25	Page 242 LR15R HQ Mixer PCB No.2		Page 270	1) Sound Gen Pcb
★YW24B Mncn Ltch Hsng 12way ★RK69A Mncn Ltch Hsng 17way	24p 36p	HM48C EB6106-50 Comm Instr£9.95 NV HD68Y Heethkit EEA-3106A£19.95 HM49D EB-6106-30 Comm Pert£34.96	Page 206				UK02C ZX8	Snd/inv Vid PCB
*YW28D Minicon Skt 3-way *YW27E Minicon Skt 4-way *YW28F Minicon Skt 6-way	28p 40p	HM490 EB-6106-30 Comm Part. £34.95 HM526 EB-6201 Digital Text £24.95 AV HM53H EB-6201-40 Digi Wkbk£11.95 AV HM54 EB6201-50 Digi Instr £8.95 AV	Page 207 HY19V 5KV Leser PCB		LR16S HQ Mixer PCB No.5 LR35Q HQ Mixer PCB No.25 LR22Y HQ Mixer PCB No.7 Page 243	£2.40	QY52G 271	6/M6£3.95
*YW30H Minicon Skt 8-way	58p	HM54J EB8201-50 Digi Instr	ORGAN COMPON		LR248 HQ Mbser PCB No.9 LR25C HQ Mbser PCB No.10 LR260 HQ Mbser PCB No.14	£2.40 £2.40	Page 271 0Y58N 271	6/M8£9.95
Page 125 FJ82S Centronix Type Con R BK98E 34 Wy IDC Skt + Chie	£4.95 £3.30	HS25C Heathkit EB-6001-50 69 95 AV	Page 210		Page 244	61.10	GB90X Tru	11 Hi Res Grph PCB£14.95 11 Hi-Res Graphics£34.95 ndle Sensor PCB£2.80
Page 128 RW61R Cas Lead Paros		HS28D Heathkit EB-0001-30 £10.86 HS27E Heathkit EB-0002 £19.96 NV HS28F Heathkit EB-0002-40 £10.96 NV	YL17T Reverb PSU Mode Page 213		LK49W Noise Gate Kit	FA 95	FT41U Tru	ndle Motor Ass£4.45
FT37S Fused Euro Ch PigPage 129	£1.40	HS296 Heathkit EB-8002-50	BR21X S Tab Gedeckt 8'. BR26F S Tab Selicional 8 BR32K S Tab String 8' BR34M S Tab Tremulant		Page 245		PROTEC	TION
BW99H Euroconn Lead		HM58L EB-6401 Micro Text	Page 214		GA30H Compander PCB	£3.50 £44.95	Page 273 WR93R Fus WR00A Fus	e 20mm 50mA
HI.30H Mains Plug SA2019A HI.31J Mains Socket SA2020 HI.37S Mains Socket P836	DIS	HM61R EB-6402 Intrace Text	BR42V Drawber White BR98G Drawber Blue BR88H Drawbar Green	£1.500	Page 246		WR94C Fus	e 20mm 160mA12p◆
Page 131 *FV94C Small Locking Plate	£1.55•	HM61R EB-6402 Intrace Taxt £24.95 NV HM62S EB-6402-40 Intt Withk £10.95 NV HM63T E86402-50 Intt Instr £3.95 NV HM64U EB-6402-30 Intt Part £24.95 NV HM67X EB-8088 18-Bit Taxt £24.95 NV	PCB EQUIPMENT		LK89A Active Crasvr Kit			, TAPE & VIDEO
Page 133 *FG30H Printer Cable 1			Page 218 BK83T Verobloc Kit	FB.45	BY73Q 8W Amp PCB	£5.95	Page 277 HR15R Ctro HR16S Ctro	dg Goldring G850£10.95 • dg Goldring G800£13.95 •
#F631J Printer Cable 2	£8.96	HS730 Heathkit EB-8405	Page 220 XG20W CM100 PCB Kk		Page 249		Page 278	
ELECTRICAL Page 137		HS75S Heathkit EB-8405-50 £9.96 /W HS78H Heathkit EB-8405-30 £54.95 HM81C EB-1801 Robotic Taxt £28.95 /W HM82C EB1801-40 Robot Width £14.96 /W HM82B EB1801-50 Robot Inst £9.96 /W	Page 222	400	LW350. 50W Amp lGt		Page 279	dg Goldring G800E£19.95+ Tenorel T2001ED£11.95+
RW88Y Dis Board 4-way Page 138	£8.95	HM82D EB1801-40 Robot Witch: £14.95 NV HM83E EB1801-50 Robot Inst£9.95 NV HM84F EB-1801-30 Robot Prt £44.95	HX46A Transfer Sheet 2 HX47B Transfer Sheet 3 HX48C Transfer Sheet 4 HX48D Transfer Sheet 5	45p 45p	Page 251		*HR39N BSI *HR51F Ror	R TC8
HL78K Shaver Skt Isolated FQ10L 250W Rotary Dimmer	£21.95 £8.95	HS88A Heathkit EB-1812	LIVERY Tonned - Charles	Aff -	GA28F 100W MDSFET Amp PCI LW51F MDSFET Amp Kit	£17.95	★FV27E BSI ★HR25C Acc ★HR87U Phi	R TC8 65p rette BF40 98p R ST4 98p as GP91-1SC £1.25 lips AG3308 £1.25
Page 139 LB83T Bayonet L/Hidr FQ05F Celling Rose		HS71N Heathkit EB-1812-50	HX68U Transfer Sheet 7 HX68V Transfer Sheet 8 HX68V Transfer Sheet 9 HX67X Transfer Sheet 10.	48p	LIKUSU MYUSPET Bridging KR	£2.96	*HR42V BSI *YX27E Sor	otone 9TAHC £1.25 R ST10 £1.26 Ny ND15P £5.96 Dis GP91-1 £1.25 Trard KS40A £1.25
Page 140		HM730. EB6100-50 BASIC Inst	HXBSY Transfer Sheet 11 HXBSE Transfer Sheet 12		Page 252		⇒FV28D Acc ⇒HR53H Gar	os GP91-1£1.25 rrard KS40A£1.25
XYOSK Extr Leed 13A		MID 34M MERINGE ER-BRIDS-PD ER RE MA	HX84F Transfer Sheet 13 HX44X Transfer Kit	45p	B881C Disco Pre-Amo Tn PCB. BB19V Disco PSU PCB B828D Motor Switch PCB Light Mod Bd	£2.95 £1.50	★HR31J Acc ★HR47B BSI ★HR74R BSI	ps GP104 £1.25 R ST17 98p R ST21 98p R ST21 98p £1.25 cos Luxor 98p
HARDWARE Page 142		MD350 Heathirt EB-8003-30 £19.95 HE11M Heathirt EB-801 £19.95 AV MO41U Heathirt EB-801-40 £10.95 AV HE12N Heathirt EB-801-50 £9.95 AV HE13P Heathirt EB-801-30 £24.95	PROJECTS & MO Page 224	DULES			★FQ45Y Ger ★HR81C Vac ★FV19V Shu	Tard GDD1
LR63T isotag M4	28p e	HE13P Heathkit EB-801-30£24.95 MD18U Heathkit EB-2001£19.95 MD19V Heathkit EB-2001-40£10.95 MV	XG086 Burgler Alarm Bor GA46A Break Contact PC LW57M Burgler Alarm Kt. LW58N Ext Horn Kt	t£11.96 B£2.20	GA42V Partylite PCB. XF11M Steree Synth Book. BB41U Synth Mixer PCB BB44X Synth VCA PCB BY90X Synth Smpl & Nae PCB.	£1.95 NV £8.50	★FV30H Shu ★FV31J Shu ★HR45Y BSI	rra N75-8. 28.95 rra N75-ED £15.95 rra N75-EJ £11.46 rra N75-EJ £11.46 £ \$715 £1.25 C R\$030 £5.95
Page 143 LR03D Terry Clip 1/2in		MD18U Heathick EB-2001 £19.95 MD19V Heathick EB-2001-40 £10.95 AV MD20W Heathick EB-2001-50 £9.95 AV MD22Y Heathick EB-2002 £19.95 MD23A Heathick EB-2002-40 £10.95 AV	LW57M Burgler Alerm ICt. LW50N Ext Horn ICt Page 225	£42.95•	BY90X Synth Smpl & Nse PCB. BB43W Synth Trns Gen 1 PCB BB45Y Synth Trns Gen 2 PCB	£3.90 ; £4.95 ;	*YX086 AD: *FV25C AD:	C RSQ30
YH99M Transfer 1/8in Black	C1 E0		GASIC Channel/PSU PCB GAS2D Extra Channel PCS	£1.80	BY82D Synth Rvrb & Phs PCB BY83E Synth VC Pn & AncPCB BR48C Synth Fxt I/P's PCR	£4.50 £11.95	*FV248 Fuji *FV22Y San *HR90X Phil	Onkyo£4.96 nyo STG6£1.25 hps GP400£3.96
XH407 Transfer 1/8in Red XH41U Transfer 1/8in White XH42V Transfer 1/4in Black XH43W Transfer 1/4in Red	£1.50 £1.50	MD27E Heathikt EB-2003 £19.95 MD28F Heathikt EB-2003-40 £10.96 AV MD29B Heathikt EB-2003-50 £9.96 AV MD30H Heathikt EB-2003-50 £29.95	GA81C Channel/PSU PCB GA82D Extra Channel PCI LW75S Radar Extr Ch Mo LW83E Usonic Xcelver I LW84F Usonic Interface I	E4.95 • £10.96 • £3.45	BB478 Synth Otpt Stge PC8	£3.30	★FM76H Hits ★FV33L Shu ★FV20W Teb	C RS033 £14 95 Onkyo £4 95 Onkyo £4 95 yo ST188 £1.25 English £1.25 En
XH44X Transfer 1/4in White	DIS	Page 175 HT83T Heathkit HS-317-10	Page 226 LK73Q. Floodlight Alarm K LW97F Panic Button Kt		6A03D Spectrum PSU PCR	£2.80 1	*FV34M Shu *FQ51F Ten *FQ526 Ten	ire N97-HE £30.95
XH46Y Penel Transfer Black XH46A Penel Transfer Red XH47B Penel Transfer White	£1.50	Page 175	Page 227	w	GA36P Spectrum VCO PCB GA55K Spectrum Cntrlir PCB XH56L Spectrum Synth Book	£1.20 NV=	≠FUS26 Ten ≠BK19V Star ≠HR89W Phil	nton D5107Ai,
		HG12N Heathkit IG-5282	LK600 Expleve Gas Airm LK140 Codeleck l0t GB768 Musical D.Bell PC LK57M Musical Announce	£24.96 £21.96= B£2.95	Page 255	£22.95	★FM70M Gar ★HR97F San ★HR48C Gold	Tard GKS25 £1.25 nyo 2611K £4.95 dring D110SR 53.45
HEATHKIT Page 146		Page 177	Page ZZ8		GB72P Computadrum PCB	£11.95	*HR77J Bold *HR76H Gold	rition DS107AL 69.95 lips GP206. 78p rard GR525 F1.25 rard GR525 F1.25 fc/fing D110SR 52.46 dring D110SR 52.46 dring D110F 52.96 dring D120SR 52.46 dring D120SR 52.4
HK81R HW-5400 Syn HF Xcvr Page 147	.£549.95	HG13P Heathkit IT-5283	LW85V Stopwetch Kit	£44.95	LW87U Symtom Kit		★HR490 Gok ★FV29G Pan ★HR61R Son	esonic EP\$36
HT27E Heethkit SW-7800	.£298.95 £84.95	HS800_ GD-1703 Bat Test Kit£16.95	GB84U Enlarger Exp Mtr F	CB£1.20	LK15R Synchime Kit	£22.95 •	★HR95D San ★HR96H She ★FV32K Shu	sui SN28 £3.95 rp STV717 £4.95 rs N70-8 £8.50 chi ST103 £8.95
Page 148 HT30H Heathlit HD-1986 Page 149	£44.95	HEBBS Heathkit IT-5230 £149.95 MD096 Heathkit ITA-5230-1 £29.95 HEBBE Heathkit IHA-180 £279.95 HK326 IN-3117 Resisting Box. £289.95	G878K Flash Meter PCB GA62S Timer Switch Boar GA63T Timer Relay PCB GA64U Timer Front Panel	£1.96	Page 267			
HK25C HD-1234 Antenna Sw HC53H Heathilt SA-2080A HC51F Heathilt HL-2200	£22.96 .£299.95	11/4200 1464-10 DC LL006"""" F 10'80	rage Z3U	£4.90	LW89W Auto Swell Kit	£2.40	#8K12N Aud	### ##################################
HC51F Heethilk HL-2200	DIS+	HT51F Heathkit IM-5215	GA25C Power Control PCE	£1,10	LIC74R Guitar Equaliser IQt	£29.96	*F994C Sha	rp STV123

1906 Cetalogue Page No.	VAT Inclusive Price	1986 Catalog Page N		VAT Inclueive Price	1986 Catalogue Page No.	VAT Inclusive Price		6 nlogue e No.	VAT Inclusive Price	1998 Cetalogue Page No.	VAT Inclusivo Prico
Page 282 FRSOE Gram Speed Indicator	DISe	UF22Y +UF36P	45998 E	£1,98 =	YF140 74LS20YF16S 74LS22		Pag OX2	je 323	20-	Page 407 \$XB82D Crotech 3031	£225 00 a
Page 283	£2.98 •	UF33L UF34M ★QQQ2C	45998 E	······································	rage 306	25p	Pag	3P 74HC4316 3e 324		YK01B RF Frequency Meter	£325.00•
RB07H Rota-Rack Page 284		OX37S YF00A OX38R	7400 74LS00	25p	QX50E 7430 YF20W 74LS30 YF07H 74LS08	259 280 250 250 250	AHG COOR		£3.40 97p	Page 408 YB81C Signal Generator	£34.96
CT00A Scotch BX-C80	94p =	* QX38N	7401 74LS01 7402	25p	QX44X 7411 YF08K 74LS11 YF13P 74LS15	25p	Pag	10 225		Page 410 *YJ09K Multimeter M-5050E Page 411	£34.95
CT07H Scotch CX-C90	£1.10 •	*YF02C YF03D QX40T	74LS02 74LS03 7404 74LS04 7405	25p 25p 28p		25e DIS 25e	QW: QW: UF2	22Y 40328E	DIS •	★YJ78K Push Button DMM Page 412	
CT21X Scotch XSII-C80	£1.450	YF04E DX41U YF05F	74LS04 7405	25p 28p	Page 307 +0x39N 7402	25p	Pac	10 325		YJ79L Multi-purpose DMM Page 413	£84.96
CT33L Scotch XSMIV-C90	£1.10m	0X75S 0X76H YF07H	74LS05	58p •44p	*YF22Y 74LS33 QX808 7425 QX48D 7427	25p 25p 26p 37p	11790	00A 74122 4J 74LS122 01B 74123 0C 74LS123 1T 74LS221	62p 82p 68p	*YK81C Fluke Meter Holster Page 414	
CT03D TDK D-80	£1.35+ £1.70+	YF08J QX44X	74LS09 74LS10 7411	38n e	YF18U 74LS27		Pag	it	74p	LH80B Clamp Meter	£44.95
CT15R TDK AD-X80	£1.95+	YF09K YF10L QX45Y	74LS127413	25p 25p 40p	Page 308		Pag	72C 74LS829=74LS124 328 7X NE5639	£1.35	TOOLS	
CT248 TDK SA-90	£2.35 • £1.90 • £7.95 •	YF11M QX46A YF13P	74LS13	34p	YF27E 74LS51		Pac	o 329		Page 416 YW92A Retchet Socket Set	nis.
CT30H TDK HXS-80	£2.60+ £3.30+	YF14Q QX48C YF15R	74LS15 74LS20 74LS21 74LS21		UW50E 4085BE		RA7 QL2 Pac	4R DP-27GNB DW uA708C	£4.50 • 45p •	Page 417 FY21X Std Lep-joint Cutter	
CT34M TDK MA-80	£3.95=	VELEC	741 522	DISA	Page 309 WH03D 74132 YF51F 74LS132 0X45Y 7413	69p	QH3 RA7	60 LH0042C	£9.95 42p •	Page 419 FT44X Cutter/Stripper Tool	
CT39N TDK MA-R90	£4.95 • 82p • £1.05 •	YF17T QX49D	7425 7426 74LS26 74LS27	DIS	YF51F 74LS132 QX45Y 7413 YF11M 74LS13		BRO	ge 335 2C 5W Amp PCB	£2.20	Page 420 ★FY45Y Adjust Spanner 150 ★FY46A Adjust Spanner 200	£4.95
CT10L Mexell UD1-C80	£1.40@	YF18U QX50E YF20W	74LS277430	25p	0X46A 7414 Page 310 0X40T 7404		BRO	je 337 4E LM381 PCB IF LM382	£3.45	Page 423 *YW65V Mini Melns Drill	£15.95
CT18U Mexell XLI-C90 CT19V Mexell XLI-S80	£1.80=	YF21X *YF22Y YF23A	74LS32 74LS33 74LS37	25p	OYA1U 7406	28n	Paç	10 SAA1088	NYA	Page 424	
CT12N Maxell UDII-C80 CT2SC Maxell UDII-C90	£1.55 m	YF25C OX56K	74LS40	25p	YH12N 74LS386	25p 58p •	Pag ORS	je 350 BN ML927	£4.50+	QY86W Metric Drill 1.4mm FR018 Element Type CN FR02C Handle Type CN	£3.75 95p •
CT28F Mexell XLII-C80 CT41U Mexell XLII-S80 CT42V Mexell XLII-S90	£Z.35 •	QQ53H YF27E	74LS48		YH140 74LS366 QX21X 4049UBE QX76H 7407	48p	YY7	je 363 10. lm336z	£1.85	FY950 Element CS 240V FY68Y CS Kit SK5	£3.75
CT37S Maxell MX-C90	£2.50●	YF28F QX56L QX57M	74LS51	DIS 55p 48p	YH13P 74LS365YH3P 74LS367	48p	FY90 YY90	je 355 IX Crystal 6.5536MHz IB ICM70464P1	£2.55+	PRIOR 129 Iron MILAS	
Page 285 CT40T D Micro MC-80YJ46A Video Tapa Hd Cinr	<u>£2.</u> 95 o £1.35	YF30H YY83E	74LS73		YF50E 74LS128	42p	QYO	N 74C925		FY97F Element MLXS 12V FR15R Element MLX12 #FT08K Finger Hook XS/MLXS RK33L Sponge ST4	£3.75 £3.96
YJ46A Video Tepe Hd Cinr	£2.95●	YF31J QX80Q YF32K	74LS74	32p	Page 311 YF90X 74LS243YF88V 74LS241	92p	+UF3i	3P 4702B je 361		RK33L Sponge ST4 Page 426	37р
FJ09K Video Belts VSK9708 FJ10L Video Belts VSK9794	£2.95 =	OX81R YF33L	74/37 74\S73 74\S74 74\S74 74\S75 74\S75 74\S75 74\S75 74\S75 74\S75 74\S76 74\S76 74\S76	46p	*QQ56L 74LS244 YP91Y 74LS245	95p • £1.00 28p	Pag	IS ICL7680CPA po 362		YESSE Solder Station TCS111	£85.95
FJ11M Video Belts VSK9805 FJ12N Vdeo Belts VSK9835 XG59P Video Enhencer VH807	£2.95 •	OX85G OX84U YF38R	74LS90	46p	Page 312		Pag	n 364		FT13P 30 West Iron CSTC FT28D CSTC Element FT28F 40 West Iron XSTC FT27E XSTC Element	£12.38 £21.50 £12.38
		OX86T OX87X YE39N	7491	74n m	YF31J 74LS74 YY83E 74ALS74 YF75S 74LS175 WH11M 74174	\$2p e 69p	Y04 Y04 Y04	9N 0.1A Reg PSU PCB 0T 0.5/1A Reg + V PS PCB 1U 0.5/1A Reg - V PS PCB 1U 0.5/1A Vareg Pos PCB 5K 0.5/1A Vareg Neg PCB	£1.80 £1.10 £1.10	FT10L Sponge Tray TCSU-1 XG57M Solder Station TCSUD. FT12N 50 Watt Iron XSD	£1.73 £94.96 £21.96
RESISTORS Page 287		YF40T 0X87U	7492 74LS92 74LS93 7496	51p	YF/4R /4LS1/4 YH19V 7AI S978	nis			£1.10	FT19G XSD Element FT11M Spenge Tray TCSU-D	£12.36
~ XL06F Colour Wheel	45p •	0X71N 0X88V YF45Y	74107 74109 74LS112 74118	DIS • 69p 46p	YH00A 74LS273YH16S 74LS374YH18U 74LS377	90p 90p £1.15	*0.00	je 366 2C 6502 je 367	£7.95	FT08J Sponge TCSU-D	£1.38
YY13P Resnet 220R YY14Q Resnet 470R	68p	0X72P WH00A 0.054J	74118 74122 74LS122	5/P	Page 313 QX56L 7470 QX57M 7472 QX58N 7473 YF30H 74LS73 QX61R 7476	55р	YHSI	DE 8256A DSD Z80A-P10	£3.65	CDD00 Div 000	E4 20
YY18U Resnet 10k RA24B SIL Resistor 220R	88p 34p	WH01B YF48C YF49D	74123 74LS123 74LS125	82p	DX58N 7473 YF30H 74LS73		Pag UF33	je 370	£1.70	FRO7H Bit 821 FR08J Bit 822 FT01B Bit 202 C FT02C Bit 302 C	£1.36 £1.36 £1.38
RA25C SIL Resistor 330R RA26D SIL Resistor 470R RA27E SIL Resistor 1k	34n	W/Moan	74LS126	42p	QX71N 74107		WU	IM (6264-150ns) I2V MCM4027 250ns Ie 371	£4.50	FT03D Bit 10 C	£1.38
RA27E SIL Resistor 1k	34p	YF51F YF52G YF53H	74LS132 74LS138 74LS138 74LS138	60p 40p 55p	QX88V 74109 YF45Y 74LS112 YH01B 74LS279		0.77	IR 41256 - 150ns	£5.50 £8.50	L100AA BU 1105	& 1.38
RA31J SIL Resistor 47k RA32K SIL Resistor 100k	34p	WH05E	74141	90n	0X72P 74118	£1.10	Pag	je 372 9K 2764 350ns		FR30H Bit 1106	£1.36
Page 290 FW44X Sw Pot Lin 47k	£1.35	D 2	0.7		YF73Q 74LS173		QY7	BV 27128 5S 27256 - 250ns	£3.45	FR17T Bit No. 51 FR18U Bit No. 52 FT06G Bit 14A XS	£1.38
CEMICONDUCTORS		Page 2 YF56K DX89W	74LS145	£1.00	YF32K 74LS75 QW82D 4508BE YH15R 74LS373	43p £1.45 90p £1.00 £1.98 £1.35	YH3	je 374 BR 8038 CCPD je 378		Page 427	
SEMICONDUCTORS Page 294		YF56L YF57M YF59P	74LS151		YF97F 74LS259 UF2ZY 4599BEYF72P 74LS170	£1.00 £1.98*	YHS	je 378 9P ICL7109 je 381	£29.95•	FR63T Desidr Washer Type 2. HY13P Desidr Nozzle Type 2	DIS
QB0QA AA119 QB19V AF139 QF10L BF167 QF15B BF200 QQ20W BF495	12pe 54pe				Page 315		FRE	2G Clip on T0220	45р	Page 430 YJ91Y Flex Rubber Sealant FA81C Thermalbond Compour	£2.80 e
QF15R BF200 QQ20W BF495 *YH95D BT149M	DIS	YF63T YF66W	74LS158	78p •	WH13P 74194 YF82D 74LS194 YF83E 74LS195 YH23A 74LS395 QW62S 40104BE		FG6	je 382 3T – Dip Sink 40 pin je 383		Trois Tribination sompour	-
*YH950 BT149M 0F41U BY126 YH59P ICL7109 YY755 ICL7680CPA YY93B ICM7045IPI	20p •	YF67X YF68Y YF69A	74LS184	£1.06 £1.00	[13/8711 7.498	92n	YB2	8D Heatsink 600N	DIS	WOUND COMPONER	NTS
YY93B ICM7045IPI Page 295	£16.95•	YF71N YF72P YF73Q	74LS169	£1.00 £1.35	OX86T 7491 YF67X 74LS164 YF68Y 74LS165			EAKERS & SOUNDI	ERS	Page 431 LB42V Dust Core Type 6 Page 432	28ρ●
QH35Q LH0042C YY73Q LM335Z	£9.95	WHIIM YF74R YF75S	74174	£1.10	YF69A 74LS166	£1.00	Pag YM4	e 387 3W SC Xtd Freq Sterophn 4X SC V/cntrl Sterophon	TEMP	★WH25C Choke 8.22uH ★WH27E Choke 8.47uH	48p
QH35Q LH0042C	£1.98= DIS	YF78K YF79L	74LS170 74LS173 74LS173 74LS174 74LS174 74LS175 74LS190 74LS191 74LS181 74LS181 74LS182 74LS182 74LS182 74LS183	86p	YF89A 74LS16 Page 317 YF39R 74LS90 QX67X 7492 YF39N 74LS92 WH09K 74150 YF78K 74LS190 WH12N 74192 YF80B 74LS192 YF80B 74LS192 QW83E 4510BE QW83E 4510BE	63p	Pag	e 389	1EMP	#WH25C Choke 0.22uH. #WH27E Choke 0.47uH. #WH29G Choke 1.0uH #WH30H Choke 1.5uH #WH31J Choke 2.2uH	48p 48p 48o
QY81C MV2108 Vericap YY87X NE5539 QH72P 0A91	£1,45	WH12N YF80B YF81C	74192	£2.20 86p 86p	YF63T 74LS160 YF78K 74LS190	78p •	Pag	e 391	£11.95	*WH33K Choke 3.3uH *WH33L Choke 4.7uH *WH34M Choke 6.8uH *WH36D Choke 10.0uH *WH36P Choke 15.0uH	48p
QH75S DA202 RA74R DP-27GNB	12p =	WH13P YF82D	74194	90p	WH12N 74192 YF80B 74LS192 YF84F 74LS198					★WH36Q Choke 10.0uH ★WH36P Choke 15.0uH	48p
RA81C SAA1099		YF83E YF84F YF85G YF86T	74LS195	86p	QW83E 4510BE YF40T 74LS93 YF66W 74LS163		SW	/ITCHES & RELAYS • 394			48p 48p 48p
QL20W uA709C WQ98G VN88AF QL37S W005		VERRV	74L S241	920	YF71N 74LS169 YF79L 74LS191 YF61C 74LS193	51p 69p £1.00 63p 85p	FH10 FH11	DL Std Toggle SPST	98p •	★WH41U Choke 100uH ★WH45Y Choke 470uH ★WH47B Choke 1mH	48p
QL37S W005 QL38R W01 QL39N W02 QL40T W04 QL50E ZTX304		* QQ56L YF91Y YF92A	74LS243	£1.00 £2p	YF85G 74LS197 YH22Y 74LS393 QQ44X 4528BE QW20W 4029BE		Pag	in 395		Page 434	
0L50E ZTX304	28p •	YPOSD	741 C257	82n	QQ44X 4526BE QW20W 4029BE Page 318				£2.50 £2.50 £2.50	WB096 Min Tr 6V	£4.50 £5.75
Page 296		YF99H YH00A	74LS258 74LS259 74LS266 74LS273 74LS279	28p 90p	Page 318 QWe1R 40103BE QY55K 4419BE	£2.25 £3.20	*FT58 FH57 Pag	P PCB NA Rotary 3x3 PM Rotary Mains je 400	£2.50 88p	WB11M Min Tr 9V WB10L Min Tr 12V YK28F Tr 12V 0.5A	
QR46A 2N4062	DIS	YH01B YH02C YH06G	74LS279 74LS283 74LS296 74LS385 74LS386	80p	Page 319 0W89W 4532BF	74n	*FH67	TX Latchswitch 2-pole IY Latchswitch 4-pole		WB25C Tr 12V 1A. WB28D Tr 12V 2A. LY03D Tr 10VA 15V. WB15R Min Tr 15V.	£5.75 £7.95 • £4.25
±0008J 2732 350ns D009K 2784 350ns	£3.95	YH11M YH12N YH13P	74LS386	48p 48p 48n	YF54J 74LS139 YF59P 74LS155 QW9QX 4555RF	55p 62p	*BW1	ie 400 X Latchswitch 2-pole. I Latchswitch 4-pole Latchswitch 6-pole Latchswitch 6-pole IM Latchsoft 2-pole IN Latchsoft 2-pole IN Latchsoft 2-pole IN Latchsoft 4-pole Latchsoft 4-pole Latchsoft 4-pole Latchsoft 4-pole I Latchsoft 4-pole R Meins Latchswitch R Meins La	55p	WB15R Min Tr 15V	
YH88V 27128	£3.45 £5.50 £2.95•	YH140 YH15R YH16S	74LS367 74LS368 74LS373 74LS374 74LS377		YF53H 74LS138 WH05E 74141	55p	#FH72 #FH74 FL36	R Mains Latchswitch P Rd Latchbutton Chrm		WB20W Min Tr 24V Page 435 YJ52G PCB Tr 0-6 0-6 0.5A	
				£1.15	YF56K 74LS145 Page 320	£1.40• £1.00	Pag LB91	e 401 Y Resher Unit 2-Wey	DIS	YJ53H PCB Tr 0-9 0-9 0.3A YJ54J PCB Tr 0-12 x 2 .25A YJ56K PCB Tr 0-15 x 2 0.5A	£3.75
0W26D 4038BE	DIS =	YH23A WH02C QQ63T	74LS393 74LS395 74LS829=74LS124 74LS829=74LS124	£1.35	QW85G 4614BE QX56K 7447A QQ53H 74LS47 QQ53H 74LS48 QX31J 4511BE	£1.20 £1.80	F)(24 F)(28	e 403 B Open Relay 12V D 2p Sub-Min Relay 6V	£4.95	LW33L Tr 240V Isotran	UIS
QX23A 4086BE = FD1079DS		QY08J #UF13P	74LS884 74C925 74HC4318 8038 CCPD 8255A	£3.40 £8.95 £2.75	QQ53H 74LS48 QX31J 4511BE		FX27 FX30 FX30	E 2p Sub-Min Relay 12V H 4p Sub-Min Relay 12V	£2.95 e	Page 436 *YK33L Toroidal 24/100V	
OW526 40898E	£2.25	Page 3	ns .		Paga 321		P(5)	F Reed Relay 9 to 12V e 404	£2.70®	Page 437 ★LK78H Stppr Mtr + Drvr Kit	£15.95
OVERY AA19RE	£3 20	OX37S YFOOA	7400	25p	YF95D 74LS257 YF96E 74LS258 YH06G 74LS298	54p 55p 62p DIS	FX91 FX93	Y Dil Reed Relay 2p12V B Dil Rd Riy 1p C/012V	DIS •	MISCELLANEOUS	
QW82D 4508BE QW83E 4510BE QW31J 4511BE QW84F 4512BE	63p 63p 63n	OX38R YF01B YF03D	7400	25p 25p 25p	VEX7M 741 C152	746				Page 439	
OW85G 4514BF	£1.20	DYRIC	7428	DIS	YF56L 74LS151 YF92A 74LS251 QW84F 4512BE QX89W 74150			ST GEAR • 405		Page 440	
QQ44X 4528BE UF24B 4527BE QW89W 4532BE QW90X 4566BE	74p 57p	YF08J YF10L	74LS26 74LS37 74LS10 74LS12	25p 25p	Page 322 *QW34M 4051BE	57р		V Test Prod Black W Test Prod Red		YX86T Flow Sensor FT30H UHF Modulator UM123 BK86W UM1286 Modulator	£4.95 • 3£4.95 • £7.95 •
Contombos 1000 Ma											

AMENDMENTS TO 1986 CATALOGUE

PLEASE NOTE that the telephone number of MPS (Maplin Professional Supplies) is 0702-552961.

VHF/UHF DIPLEXER BW51F (Page 34).
Diplexer UF20 has been replaced by
Diplexer UF22 which is a masthead
(fastening to mast by nylon strap) or
surface mounting diplexer for combining
UHF/TV and VHF/FM signal from antennæ
downleads. Bandwidth: (FM) 87-108MHz;
(UHF) 470-860MHz. Channel isolation:
(FM) 22dB; (UHF) 38dB. Insertion loss: (FM
and UHF) 0.5dB.

SNAP-TOGETHER PLASTIC BOXES
YK48C - YK51F (Page 68). These boxes
are now supplied with the base and top
sections in cream, with the two end plates
now in brown.

COILED MAINS CABLES BL72P (Page 77). The extended length of Stretchflex 6 Amp is 3 metres.

AXIAL LEAD ELECTROLYTIC FB53H (Page 90). The working voltage of this $100\mu F$ axial electrolytic is now 200V not 280V.

KINGDOM GAME CASSETTE (Page 104). This cassette game for the Atari has been listed as having the stock code KB9TF, whereas it should be YGSSK. SCREENED CENTRONICS PLUG FJ61R (Page 121). The 38-way contacts are not of the IDC type as stated in the catalogue, but are solder terminals.

EDGE CONNECTOR FOOT (CLOSED)
FI.91Y (Page 122). The Edge Connector
End Bracket (YR58N) available for the
Card Frame Edge Connectors is an open
ended (slotted) type. FL91Y is now also
available and is a closed type, i.e. suitable
for use as a pcb guide. Price 24p.

0.1in. SERIES PCB CONNECTORS
RE657 - YW30H (Page 123). Please note
that although these minicon latch connectors are described as having 0.1in.
spacing, the actual spacing is 0.098in. or
2 8mm

TELEPHONE WALL SOCKETS' LOCK-ING PLATE FV94C (Page 131). The Small Locking Plate is for use with the Surface Mounting Jack Units 2/4A and 2/6A, and not 1/4A and 1/6A.

PRINTER CABLES FG30H & FG31J (Page 133). These 26-way and 20-way ribbon cables have had their lengths quoted as 30cm, they should be 1m as before.

STRAIN RELIEF GROMMETS LR4TB -LR50E (Page 143). Please note the amended sizes of these strain relief grommets. All dimensions in millimetres:

Type	В	A	D
3P-4	9.9	11.0	10.3
5M-3	11.7	12.7	11.0
6W-1	11.8	12.7	11.0
7K-2	19.6	22.2	19.0

GRAPHIC AND PANEL TRANSFERS

(Page 144). A new range of transfer sheets are available as follows: 2.5mm letters and numbers in black or white; XH73Q Transfer 2.5 Black, XH74R Transfer 2.5 White. 3.5mm numbers only in Black or White; XH75S Transfer 3.5 Black, XH76H Transfer 3.5 White. 4.2mm letters and numbers in black or white; XH77J Transfer 4.2 Black, XH78K Transfer 4.2 White. Sizes 2.5 and 3.5 are in medium typeface, size 4.2 is in light typeface.

Two new graphic panel sheets are available: XH71N Graphic Sheet Black, XH72P Graphic Sheet White. All of the above priced at 45p per sheet.

SPINDLE COUPLER RX29G (Page 184).

The length of this brass coupler is 15mm and not 22.5mm.

and not 22.5mm.
ULTRA-BRIGHT RED LEDs QY84F,
QY85G (Page 199). It is the anode and not
the cathode that is denoted by the flat of

the package and the shorter of the two leads.

5x7 LED ARRAY FT61R (Page 201). The dimensions of the 5x7 LED array have been erroneously omitted from the catalogue. The dimensions of the array are 53 x 38 x 8.5mm deep excluding pins. PCB TRANSFERS (Page 222). A new range of PCB transfers are now available There are 14 sheets in the range, some will replace existing stock, others are completely new. Old Transfer Sheets 1 (HX45Y), 4 (HX48C), 8 (HX65V), 9 (HX66W) are discontinued. To replace them new transfer sheet numbers have been allocated thus: Transfer Sheet 1 = XH66W, Transfer Sheet 4 = XH67X, Transfer Sheet 8 = XH68Y, Transfer Sheet 9 = XH69A and a new Transfer Sheet 14 = XH70M. The Transfer Kit (HX44X) now contains all 14 sheets A brief run-down of each sheet follows:

Sheet 1: 2176 circle pads 1.6×0.38 mm. Sheet 2: 20 straight lines 170×1.61 mm. Sheet 3: 260 circle pads 2.54×0.45 mm. Sheet 4: 351 circle pads 3.6×0.79 mm. Sheet 6: 210 transistor pad sets, each circular pad is 2.4×0.32 mm. Sheet 6: 45 rows of 16 pad DIL IC's spaced at 0.3×0.1 inch, each circular pad is 2.16×0.32 mm.

Sheet 7: 90° bend lines, fifteen bends 2.25mm wide, twelve bends 3.0mm wide. Sheet 8: 8 rows of 68 pairs of pads with between-pad' tracks, pads are 2.54mm diameter.

Sheet 9: 77 sets of 8 pads 1.6×0.34 mm with through tracks.

Sheet 10: 0.1 inch spaced edge connector fingers, 12 rows of 32 fingers. Sheet 11: 21 straight lines 170 \times 0.68mm. Sheet 12: 90° bend lines, 24 bends 0.65mm

thick. 24 bends 1.61mm thick.

Sheet 13: 33 sets of DIL IC pads with leads and offset holes.

Sheet 14: 7 straight lines 170 x 3.0mm, 8 straight lines 170 x 2.25mm.

XH67X to XH70M are priced at 45p each. STEREO SYNTH BOOK XF11M (Page 283). Please note that details of metalwork and cabinet are no longer available and are not shown in the book.

THERMAL FUSE RA18U (Page 274). Note that the Thermal Fuse 169C is no longer being manufactured. It is replaced with type 167C which for most purposes is suitable for the same applications as type 169C.

REPLACEMENT STYLI (Page 279). The prices for the styli shown on pages 279 and 280 of the 1986 catalogue have been omitted. For prices refer to a copy of the current price list.

CASSETTE CARE KIT BK28F (Page 282). Please note that the cleaning head of the cassette in this Cassette Care Kit no longer includes a demagnetiser.

ALL ROTARY POTENTIOMETERS (Page 290, 291). The shaft length of all types (single, single with switch and dual gang) is 50 ±0.8mm minimum. Also the thread length of the single and dual gang is 9mm and not 7mm. Note that the body length of the switched types is 22mm not 20.8mm, and that the switch rating is 4A at 250V AC and not 2A.

4702B PROGRAMMABLE BIT RATE GENERATOR (Page 296). The order code for this device is UF36P, not UF35Q. 74HC4316 UF13P (Page 297). In the semiconductors index on page 297, the 74HC4316 IC has been listed as being described on page 328, it is in fact to be found on page 323.

THYRISTOR BT149M YE95D (Page 302). Replacement device TAG 84 may be supplied, please note that the anode and cathode are reverse of that shown for the BT149M.

BT149F YH94C (Page 302). Please note that thyristor BT149F is now no longer in manufacture, and has been replaced by this device BT149B. The specifications are identical except that PIV is rated at 200V instead of 50V. The specifications are: Case T092f, PIV 200V, I_{T (max)} 1A, I_{T (av)} 0.64A, V_{CT (max)} 0.8V, I_{CT (max)} 0.2mÅ, I_H (max) 5mÅ.

7402, 74LS02, 74EC02 AND 4001BE,
4001UBE QX39N - QL03D (Page 307). The

captions for the pin-out diagram of the TTL devices have been accidentally transposed with those for the CMOS diagram. 74LS244, 74HC244, 74HC744 OCTAL BUFFERS QOSGL, UB65V, UB66W (Page 311). In the pin-outs diagram for these octal buffers note that the control input via pin 19 should have an inverting input symbol at the control input buffer.

4040BE, 74HC4040, 4060BE,
74HC4060 RIPPLE COUNTERS (Page
318). The pin-outs diagrams for these ICs
have the wrong captions. The 4060BE and
74HC4060 devices are actually the 14stage ripple counter with oscillator, and
the 4040BE and 74HC4040 devices are the
12-stage ripple counter.

4051BE, 74HC4051, 74HC4351 (Page 322). The captions on the pin-out diagrams for these 1-pole 8-way analogue switches should be transposed.

AUDIO POWER AMP IC's OH39N. WQ33L, WQ66W, WQ67X, YY70M (Pages 335 – 337). Please note that although these devices are described as having heatsink mounting tabs that do not need to be electrically insulated from a chassis, this is on the condition that the chassis is the same potential as the most negative supply pin of the IC. The mounting tab is connected to the IC substrate, and it is required that this be equal to or up to 0.6V more negative than the negative supply pin voltage. If chassis = IC 'ground' potential, then the omission of an insulating kit will satisfy this condition, but do not overlook the possibility of earth related instability problems. If you intend to use a split-rail power supply, you must not bolt the tab direct to chassis without an insulating kit! TEMPERATURE COMPENSATED TWO

TEMPERATURE COMPENSATED TWO STEP LEAD ACID BATTERY CHARGER (Page 364). In the circuit diagram a value is missing for R14, it should be 4k7. 6502 MICROPROCESSOR QQ02C (Page 366). The device being supplied is the

2732 EPROM QQ08J (Page 371). The programming voltage $V_{\rm pp}$ at pin 20 of this IC should be 21 volts, not 25 volts. MID-RANGE SPEAKER WT15R (Page 389). This mid-range unit is for use in systems up to 25W and not 40W. RIGHT-ANGLED PCB ROTARY SWITCHES FTS6L, FTSTM, FTS8N & FTS9P (Page 395). The specifications of these switches should be amended as follows – FTS6L is 1-pole 12-ways, FTS7M is 4-pole 2-ways (4-pole changeover), FTS8N is 2-pole 6-ways, and FTS9P is 3-

PUSH BUTTON LATCHSWITCHES
FH67I - FH74R (Page 400). The operation of these switches has changed slightly. For push-on/push-off locking action the switches operate as before, but for momentary push-on non-locking, or for interlocking action with the use of a latchbracket, the locking/retainer clip must be replaced with the nylon retainer provided with each switch, otherwise the moving portion containing the moving contacts will entirely withdraw from the switch body. This may be useful for

contact cleaning purposes.

TJ09K (Page 410). In that part of the description relating to measurements from centre zero scale, it should read 'In addition the meter pointer can be positioned to the centre of the scale so that + and - DC readings may be taken,' In the table, the line 'DC' volts' etc. should be followed with 'From centre zero ±f.s.d;

PUSE BUTTON DIGITAL MULTIMETER M6000 TJ78K (Page 411). Note that the table of resistance ranges has been erroneously omitted from the catalogue. The resistance ranges for the M6000 are as follows, written as 'Range, Resolution,

 ± 150 mV, ± 0.6 , ± 1.5 , ± 6 , ± 15 , ± 60 , ± 150 ,

Accuracy': 200 Ω , 100m Ω , \pm (0.5% of rdg + 1d); $2k\Omega$, 1Ω , \pm (0.3% of rdg + 1d); $20k\Omega$, 10Ω , \pm (0.3% of rdg + 1d); $20k\Omega$, 10Ω , \pm (0.3% of rdg + 1d); $20k\Omega$, 10Ω , \pm (0.3% of rdg + 1d); $20m\Omega$, $10k\Omega$, \pm (1.5% of rdg + 1d). Max open circuit voltage drop across probes, <3V. Overload protected to 280V DC or rms AC.

FLUKE METER HOLSTER YK81C (Fage 413). This holster no longer has a neck strap.

ADJUSTABLE SPANNERS FT45Y, FT46A (Page 420). The dimensions of these spanners have changed slightly. The small adjustable is now 150mm in length with a maximum jaw opening of 19mm, and the large adjustable has an overall length of 200mm with a maximum opening of 200mm.

BOX SPANNERS FY41U & FY42V (Page 420). Please note that these box spanners are no longer 4BA and 6BA respectively as stated in the catalogue, but are now metric M4 and M2.5.

SATURN MAINS DRILL YW65V (Page 423). Please note that the specifications in the catalogue are not quite correct. The mains supply voltage range is actually 220 – 250V, the off-load speed is 12,000 r.p.m, and the 3-jaw pin chuck has a maximum capacity of 2.9mm and not 1/sin.

SOLDERING IRON HOOK FT09K (Page 425). This clip-on hook/finger guard will fit the KS and MLXS soldering irons only, and not the CS type.

not the CS type.

RF CHOKES WH25C - WH47B (Page 432). Please note that due to a change of supplier these RF chokes will be supplied with colour code bands to denote the value, as stocks of the black bodied types become exhausted. The colour codes operate in the same way as the resistor 3band colour codes, except that the unit value is the microhenry and not the ohm. For example: Red, Red, Silver = 20 + 2 x 0.01 μ H; Brown, Black, Gold = 10 + 0 \times 0.1 μ H; Orange, Orange, Gold = 30 + 3 x 0.1 μ H; Brown, Green, Black = 10 + 5 x 1 μ H; Brown, Black, Brown = $10 + 1 \times 10 \mu H$; Brown, Black, Red = $10 + 2 \times 100 \mu H$; etc. A fourth band is always silver.

TOROIDAL TRANSFORMER YK33L (Page 436). In the case of the toroidal transformer with 0-24, 0-24, 0-100V secondaries, the wire colour codes for the 100V secondary have been omitted. They are: start of winding, Black. Finish of winding. White.

TRANSFORMER KITS (Page 436). The turns ratio quoted for the 20, 50, and 100 watt transformer kits are in the wrong order. Correct turns/volts ratios are as follows:-

follows:-20VA — 6.04 turns per volt, +1% for each multiple of 10VA loading.

50VA - 4.8 turns per volt, +1% for each multiple of 10VA loading.

100VA - 4.16 turns per volt, +1% for each

multiple of 10VA loading.

STEPPER MOTOR HIT LK76H (Page 437). This kit now includes a pcb, GD14Q.

Maplin Magazine September 1986

ORDER COUPON



If ordering by Credit Card please sign:

Expiry date of Credit Card

P.O. Box 3, Rayleigh, Essex SS6 8LR. Telephone, Credit Card Sales (0702) 554161; Enquiries (0702) 552911.

A different postal code is correctly shown on the reply paid envelopes.

	-
Customer No	*****
Name	
Address	
Post Code	

In any correspondence please quote your customer number. Date

Block capital letters please.

Keep a copy of your order.

Description (for your information only) Current Price List (Please write 1 in quantity, if required)		Order Code Quantity			Quantity	Price Each	£ Total p		
		F	0	8	J		FREE	0	00
Price Change Leaflet (Please write 1 in quantity, if required)		A	9	9	Н		FREE	0	00
									-
	-								
	-								
	-							-	
	\perp								-
	+					-			
	+	-							+
	+								+-
	+			20110					
					L				-
	+				-				-
	+								+
5	+			-					
	+								
	+				_				+-
	То	tal this	s she	et			3		
Overseas customers including Channel Isles and Eire, please deduct Office Use Only DOR CQ CA PO	To	tal oth	ner sh	eet(s)			3		
VAT where applicable and tick this box. Total Export Order Total							etal for goods £		
horise you to debit my credit card account for the cost of goods despatched.	Ha £5	andling , mak	g Cha e tota	rge. I I here	total up to	for goods be £5. If less th	etween £4.50 and an £4.50, add 50p.		
dit Card Number	De Er	educt v	value the n	of Cre umbe	edit N	ote No Credit Note w	ith this order.		
ess/American Express/Mapcard/Visa/ Delete as required. e. Goods will be despatched only if the address above is the cardholder's address.	Ple	ease a	add 5	Op Ca	rriage	and Packin	g order placed	0	

Total £

FOR A WHOLE YEAR'S SUBSCRIPTION TO 'ELECTRONICS - THE MAPLIN MAGAZINE'

ONLY.

- **★ Every issue sent to you as soon as it's printed,** post free.
- ★ Packed with interesting and novel projects that you can build with all components easily obtainable.
- **★** Many features on electronics subjects to keep you up-to-date with latest developments.
- **★ More pages to read than the monthly magazines.**
- ★ And much, much cheaper too. Many of the monthlies are now £1 or more per issue!

BUYING A SUBSCRIPTION IS THE BEST WAY TO BUY 'ELECTRONICS'

'Electronics' is different from any other electronics magazine for two reasons:

- 1. It's quarterly, so it's hard to remember when a new issue is due out both for you and your newsagent.
- 2. We don't carry any advertising, which means that having lots of copies sitting on the newstands waiting for casual sales is of no advantage to us. The newsagent will normally have plenty in stock of those magazines which advertise because in almost all cases, he can return them if they are not sold so he doesn't pay for them.

'Electronics' has no advertisers to pay for unsold copies, nor does it need to have an impressively large circulation, so the newsagent must buy all of his delivery of 'Electronics' and cannot return those he doesn't sell. Therefore, he may not want to take stock of too many. Before you know where you are, 'Electronics' has sold out!

That's why you'll need to place a firm order with your newsagent to be sure of obtaining each new issue. Better still, place the order directly with us by sending £3.00 now and we will send you every issue for a year, post free.

Despite having very few casual sales, 'Electronics' sells as many copies as the top selling monthly magazines. So we can justly claim if not quite the largest, definitely the largest committed readership in the U.K. of any electronics magazine.

Address

.....Post Code.....

 Order as many copies as you wish, you will not be affected by future price increases until your subscription ends.



CRDER NOW! From issue 21 the cover price of 'Electronics' will increase, so now is your chance to buy your advance copies on subscription for the current price of 75p each. So don't delay, order now!

he Fibre Optic Audio Link serves as an interesting alternative to the traditional pair of wires carrying audio signals from one point to another. Fibre optics are used extensively these days in the fields of communications, TV and Radio, computer data transmission, medicine and even motor vehicles – to name but a few!

Optical Fibre

The light guide itself may consist of many strands of fine, drawn, glass fibres or a single, solid fibre made from polymethyl-methacrylate and enclosed with a polymer cladding and protective sheath. Unlike cables and wires, the fibres do not carry an electric current, but instead reflect light waves along their length.

Therefore electrical signals must be converted into light and sent along the guide. At the far end, the light waves are re-converted back into electrical signals, closely resembling the original. Unfor-

Characteristics

Frequency

Response - 50Hz to 20kHz (-6dB) Flat

from 150Hz to 3kHz

Max I/P and

O/P Levels

- 0dB (775mV rms) @ 1kHz

Minimum
I/P Level

- - 28dB (30mV rms) for

rated O/P

Noise Level

- 10mV

Signal to

Noise Ratio – 35dB T.H.D. @ 1kHz – 1.0%

P.L.L. Carrier

Frequency - 95 to 120kHz (110kHz nom)

PSU (Tx) 4.8 to 6V DC @ 30 to 50mA

(Average)

Recommended, +5V DC @ 38mA

PSU (Rx)

4.8 to 12V DC @ 5 to 12mA Recommended, +9V DC @ 8mA

finations and to the survivation

All specifications apply to the prototypes and may vary between different modules. Use recommended supplies for optimum performance.

tunately, fibres exhibit the luminal equivalent of resistance which increases proportionately with length and limits the maximum length of guide which can be used in any particular system. Attenuation effects can be measured at 1.2dB per metre, or approximately a 20% reduction with the light guide recommended for use with this project (XR56L).

The maximum useable range of these modules is limited to 20 metres (65 feet approx) provided that the fibre ends are 'polished' for optimum light transfer.

Fibre Optic Couplers

A simple system for connecting the light guide to each module is shown in Figure 1. Both Emitter and Detector units contain an Infra Red PIN Diode and lens contained in the FLCS housing. Prepared light guide ends are inserted through the cap, which is then screwed onto the housing, up to finger tightness. The cap contains a compression ring which grips the light guide tightly and prevents it from being easily pulled out, see Figure 2.



* Transmits over fibre optic light guide with up to 20M range

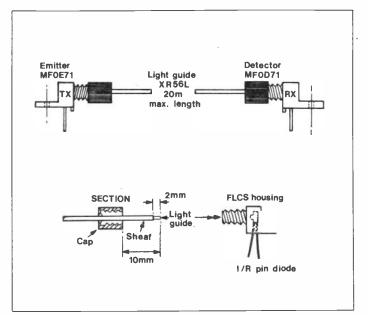


Figure 1. Connecting Light Guide.

Preparation of Light Guide

Both FLCS couplers are designed for use with 1000 micron (1mm) core plastic fibre, which can be found in our catalogue or parts list (XR56L). Remove a short piece of sleeving from one end of the light guide, as shown in Figure 3, by gently cutting around the circumference, or by using 18 gauge wire strippers. Great care should be taken when cutting through the covering sheath, to prevent scoring the fibre core inside!

Remove the end covering and cleanly cut the fibre core two millimetres long. Try to make a single, straight cut thus keeping the end as smooth as possible, this being important for maximum light transfer to the couplers. Use a sharp knife for this. Very fine emery paper, or the striking edge of a matchbox (but not glasspaper types!) can be gently rubbed, squarely across the cut fibre end to polish the surface. Liquid metal polish also helps to develop a smooth finish and could also be used to finish off.

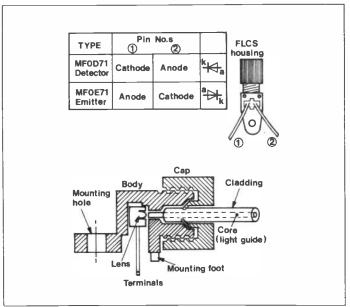


Figure 2. Emitter and Detector Pin-out and Construction.

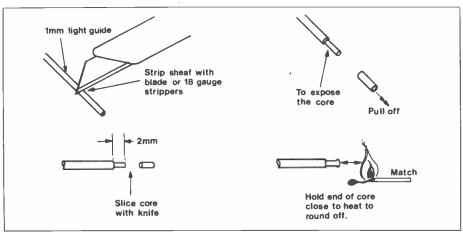


Figure 3. Preparing the Light Guide.

Alternatively, the cut fibre end could be placed close to a naked flame for a few seconds until the end begins to round off. Excessive heat will melt the fibre completely, and this should be avoided. This latter method has the advantage of producing a near perfect finish and develops a 'lens' in the fibre —

ideal for good light transfer. Whichever method is employed, aim for a mirrorlike finish on the fibre end if maximum range is required.

Circuit Description

The system has been developed for use with audio signals of a reasonably

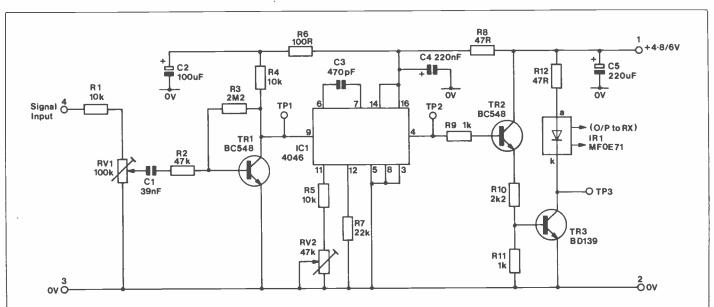


Figure 4. Transmitter Circuit.

high level to begin with. High impedance microphones could be coupled directly to the input of the Tx module, as could cassette or amplifier line outputs.

TR1 on the transmitter module (Figure 4) pre-amplifies the incoming signal and RV1 is adjusted to suit the input signal level from Pin 4. Because a low voltage supply is used here (4.8 – 6V) the input range dynamics are somewhat limited and C1 has been chosen to roll off low frequency signals, which would otherwise produce distortion from the receiver output.

The low power, CMOS, Phase Locked Loop device, IC1, is used as a voltage controlled oscillator, operating at a centre frequency of 110kHz. Audio signals from TR1 collector swing the VCO each side of the 110kHz centre frequency, thus frequency modulating the 'carrier' signal. At test point TP2, a 5V square wave representing the modulated carrier is available, this being buffered by an emitter follower TR2 to the current switch TR3.

The Light Guide Emitter MF0E71 is an infra-red PIN diode, which is switched on and off, at the carrier frequency, by transistor TR3. R12, of 47Ω , limits current through the PIN diode at an average 40mA. The diode is capable of taking up to 100mA, made possible by reducing the value of R12 down to 22Ω or so, but power supply demands are then greater. If using a 4 cell nicad pack (5.2V) then the lower 40mA current drain is preferable for longer battery life. The advantage of increasing current through the PIN-diode comes from an increased light output; the signal to noise ratio is improved and greater transmission distances are possible, although by only a few metres, but this is only practicable given the appropriate power supply.

Hence R12 is here optimised at 47Ω for a 40mA collector current. Timing components C3 and R7 determine the VCO centre frequency and RV2, R5 allow a 25kHz adjustment approximately over a 95kHz to 120kHz range. Light transmitted from the MF0E71 is in the infra-red band at a peak, spectral wavelength of 820nM; the full bandwidth extends from 400 to 1000nM (nano-metres) with an 80% reduction in qutput power.

Receiver

Audio signals in the form of frequency modulated, infra-red light now have to be amplified, detected, demodulated and filtered to reconstitute the original waveform. A matching infra-red detector, MF0D71, is used in reversed-bias mode with current limiting resistor R1 (see Figure 5). Output current to TR1 is extremely small, so the front pre-amplifing stages have a very high gain. TR1 and TR2 are configured as a DC coupled amplifier, self biased by R2. C3 is the main AC feedback component, and this stage has a frequency response of up to 0.5MHz.

With such a high gain, wide band pre-amplifier, noise levels are increased,

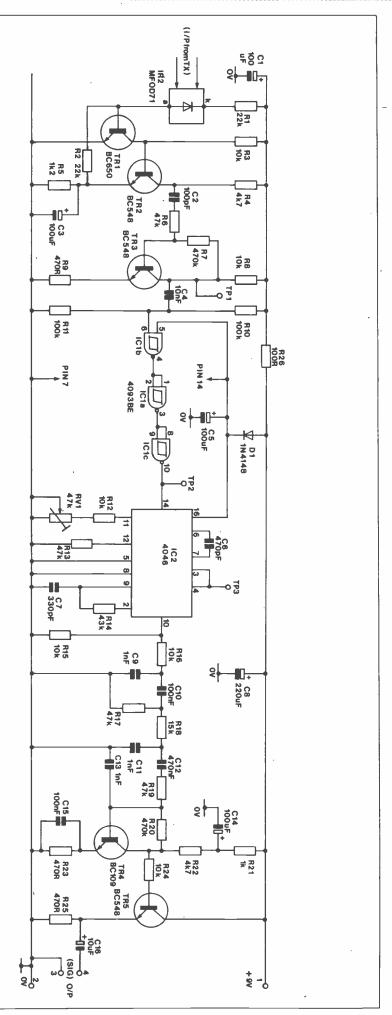


Figure 5. Receiver Circuit.

originating from the optical fibre itself, in addition to self-generated noise – therefore buffering amplifier TR3 is coupled by C2 and R6, which filter out much of the lower frequency noise signals. IC1 is a schmitt trigger-NAND package used for 'cleaning up' the pre-amplified carrier signal, and the supply for this and IC2 is separated from the main supply rail by reversed supply protection diode D1 and C5

The carrier square wave is made available at TP2, which is also one of the Phase Locked Loop's phase comparator inputs. The comparator output controls a voltage controlled oscillator, via R14 and C7 which filter out harmonics and maintain a 90° phase shift at the VCO centre frequency. VCO timing components are C6, R13 and RV1. With no carrier signal applied to the receiver input, the VCO is free running at 110kHz; this frequency can be varied by RV1. The VCO square wave output from pin 4 feeds back to a second phase comparator input at pin 3.

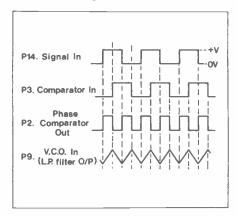


Figure 6. Waveforms.

With a 110kHz carrier signal present on Pin 14, a digital error signal is output to the filter and VCO input Pin 9 (Figure 6). Signals well outside of the carrier frequency do not produce the error signal, and the loop (VCO-comparator) does not 'lock on'. The values of R14 and C7, therefore, are important and determine the loop capture range and bandwidth.

The low pass filter output is taken from Pin 10, which is a buffered output from Pin 9. R15 serves the internal FET buffer source load and R16, C9 form a first stage filter for the audio and carrier output. A further two stages of low pass and high pass filters are necessary to reconstitute the audio waveforms and remove much of the 110kHz carrier signal. TR4 amplifies the filtered signal and TR5, emitter follower, buffers the signal for a low impedance output at Pin 4

Transmitter Construction

For information regarding component identification, assembly methods and soldering, please refer to the 'Constructors Guide' supplied with this

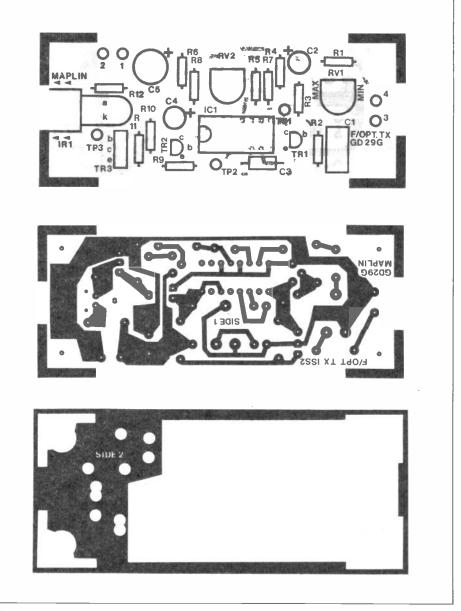


Figure 7. Transmitter Track and Legend.

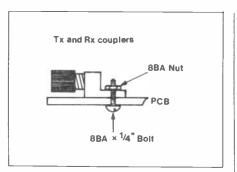


Figure 8. Coupler Mounting.

kit (if you do not intend to purchase the complete kit then see the Parts List for the order code of the Constructor's Guide, price 25p). Begin construction by referring to Figure 7 and inserting seven vero pins, pins 1 to 4 and TP1 to 3. Pin 2 (0V - PSU) should be soldered to both side 1 and side 2 of the pcb in order to connect the screening earth plane on both sides. Referring to Figure 8, mount the emitter coupler MF0E71 on side 2.

Ensure both terminal leads pass completely through the pcb and both locating pegs enter their holes. Insert an 8BA x 1/4 in bolt through the tab provided and tighten down with an 8BA nut. Do not overtighten, as excessive force is not necessary and the plastic body may be damaged.

Refer to Figure 9 and fit power transistor TR3 (BD139). This device must be fitted correctly, with the metal heatsink mounting surface facing toward TP3 and the front edge of the pcb. Push all three leads down into the holes leaving a clearance of 3mm between pcb and the base of the package of TR3. Solder all these five leads in place and cut off excess ends.

Now identify and insert resistors R1 to R12, and capacitors C1 to C5. When fitting C1, take care not to damage the leads on each end of the device, as they are very easily broken off. Note polarity markings on electrolytic and tantahum capacitors and insert correctly (consult the Constructor's Guide if in difficulty). Solder these components and again, remove excess wire ends.

Mount the 16-pin IC socket and TR1, TR2. Bend a few legs of the socket over beneath the pcb to prevent it from falling

out. Mount RV1 and RV2 – note that their values are not identical so be sure to put the correct value in the required position – finally solder all remaining component leads, remove excess wire ends and clean the pcb tracks, before inserting the P.L.L. device, IC1.

Transmitter Testing

A few checks can be made at this stage to ensure that the transmitter module is operating properly. Connect a 5V power source to Pin 2 (0V) and +Ve via a milliammeter to Pin 1. Set the wiper of RV2 to approximately half travel, and turn on the power source.

A current reading of approximately 30 to 40mA should be obtained. Any readings well outside of this may well point to a fault, unless the test meter is not connected properly or the wrong range selected; double check and repeat the procedure. If the error is genuine and a frequency counter or oscilloscope is available, connect either to test point TP2. Adjust RV2 for 110kHz, which will be some 45° displacement of the wiper of RV2 from its central position. The output stage can be monitored with a 'scope on

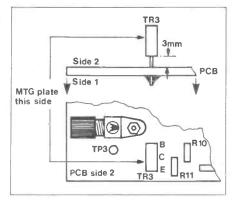


Figure 9. Mounting TR3.

TP3, where a 9μ s square wave of 3.25V amplitude is present. The lower edge of the square wave will be approximately 0.7V above 0V, and the upper edge at +4V.

If this waveform is not present and the VCO is running, then it is possible that the actual infra-red coupler devices could have been mixed up! Both devices look the same, except for an identification code printed along one side of the body housing – if it turns out to be the wrong device then swop it for the other and repeat the testing procedure.

With testing completed switch off the power source and continue with the Receiver.

Receiver Construction

In similar fashion to the transmitter module, refer to Figure 10 and insert 7 vero pins in the holes marked with white rings, and mount the infra-red detector coupler, as Figure 8. Identify and insert resistors R1 to R26, then solder their leads on side 1 of the pcb. Three of these resistors, R5, R9 and R11, additionally have one of their leads soldered on side 2, the component side, of the pcb, see Figure 11. Do not omit this as it extends the earth plane to 0V.

Insert diode DI, taking care not to damage the glass case, and semiconductors TR1 to TR5. TR2, TR3 and TR5 are identical devices and look similar to TR1, but must not be mixed as TR1 has a different leadout configuration. TR4 has a silver, metal case with a marker tab against the emitter lead; push these devices down to within 3mm clearance between pcb and base of the package.

Next, fit capacitors C1 to C16, noting polarity markings on electrolytic types.

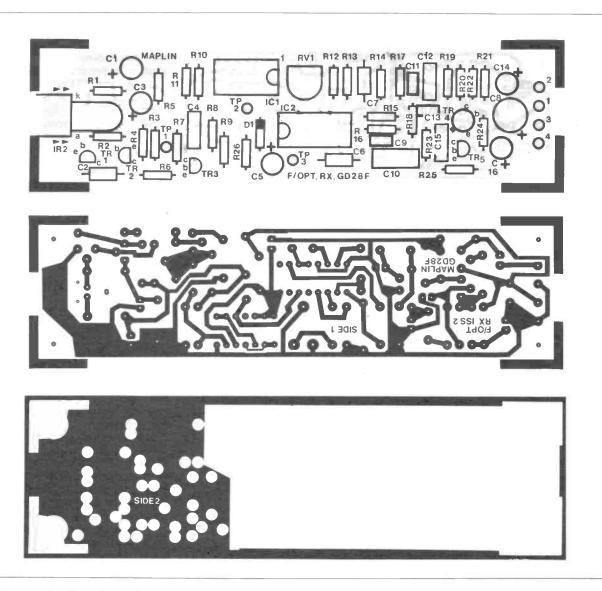


Figure 10. Receiver Track and Legend. September 1986 Maplin Magazine

Poly-layer capacitors should be handled carefully to avoid their leads breaking off, as this is easily done.

Mount preset RVI and a 14-pin IC socket at IC1 position, and 16-pin socket at IC2 position. Solder all components and leads and remove excess wire ends before inserting IC1 and IC2 into their sockets.

A careful inspection of all resistors and track areas is advisable at this stage, and cleaning side 1 of the pcb is recommended.

Receiver Testing

Basic checks and adjustments can now be made on the receiver module. Connect a 9V power source with 0V to Pin 2 and +V via a milliammeter to Pin 1. A PP6 9V battery pack is useful for this. Set the wiper of RV1 to approximately half travel, and turn on the power source.

A current reading of 7 to 9mA should be obtained. With a frequency counter or oscilloscope, monitor the test point TP3, and adjust RV1 for a frequency of approximately 110kHz. The exact setting is not that critical, since the PLL will lock onto the transmitter signal (once detected) and pull the VCO within range. If monitoring TP3 with a 'scope, then a square wave form (\approx 50% duty cycle) should be evident of at least 8V in amplitude with a 9 μ s period. Check that TP2 is at logic 0 (0V) whilst no carrier signal is present, and TP1 is at approximately +2 to +4V.

Monitoring the audio output, Pin 4, may produce a certain amount of carrier

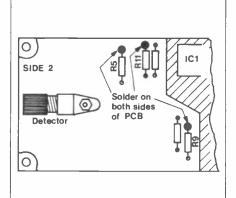


Figure 11. Some resistors are soldered both sides.

'breakthrough' signal (at 110kHz) which can be reduced by turning RV1 clockwise. The signal is present due to a lack of input carrier to the receiver and is removed when the PLL locks onto the incoming signal. Remove the 9V test power source.

Connecting the System

Figure 12 details both modules and should be referred to for the following. If the Fibre Optic Light Guide has not yet been prepared, then refer back to the Preparation of Light Guide section and Figures 1 to 3.

Slide a fluted cap from the coupler over the light guide – it will be quite a tight fit – leaving about 1cm of prepared end protruding. Push the prepared end into the coupler, and offer up the cap. Tighten the cap with fingers only – do not use any tools to do this! Repeat the

procedure on the opposite end so that both Tx and Rx modules are secured to the light guide. It must be emphasised that careful preparation of the light guide core end is of vital importance if maximum range is required. Poorly prepared ends will produce noisy Rx output and may well limit useable cable length to below 10 metres or less!

When installing fibre optic light guide in a permanent position, be careful with bends, see Figure 13. The absolute minimum radius of any bend in the fibre should not be less than 20mm. Exceeding this limit will result in cracking of the fibre, which will completely refract light and result in zero throughput. If using clips to hold the guide in position, be careful not to pinch or damage the outer sheath in any way. Light will escape and/or enter from pierced sheathing and again poor results are inevitable. Excessive heat and some chemical solvents will also damage the guide and should be avoided.

Final Testing

Apply power sources to both modules and connect a suitable signal source to the transmitter input Pins 4 and 3 (0V). Turn RV1 clockwise to approximately one-quarter of its travel and monitor the receiver output Pins 4 and 3 (0V). RV2 on the transmitter should be adjusted slightly for optimum signal level from the receiver, and RV1 on the Rx pcb can be turned clockwise if background noise level is excessive. The Tx input attenuator can be turned clockwise to

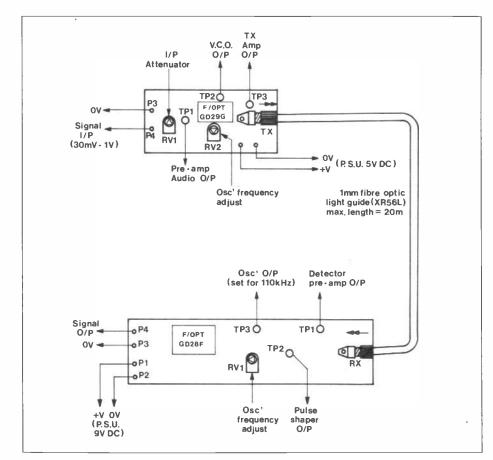


Figure 12. Connecting up the System.

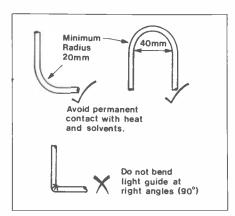


Figure 13. Bending the Light Guide.


increase the audio signal level through the system, but too high a level will produce a distorted audio output from the receiver.

Input signal levels to the transmitter should be kept as high as possible (at least 250mV to 500mV) for best signal to noise performance if using long (20 metre) lengths of light guide, although a fair amount of gain is available from the Tx input pre-amp.

Tests on the prototype produced quite good results using a Hi-Fi cassette player line output as the signal source, and the line/Aux input of a Hi-Fi tuner amp for the output of the receiver, with approximately 500mV average signal

level applied. Very low frequency transients are limited by the input stage filtering, middle and upper ranges are reproduced very well.

The modules are not designed to Hi-Fi standards, but as a fairly low cost introduction to fibre optics for personal and educational uses. Really useful practical applications would be in comenvironments through munications plagued with electrical noise and powerful electro-magnetic fields to which conventionally carried screened signals cannot remain immune. Much scope exists for the enthusiast to improve on the basic system. For example, an audio compressor could be used to limit and average-out applied signals to the transmitter. The pre-amp gain could then be increased for better signal to noise

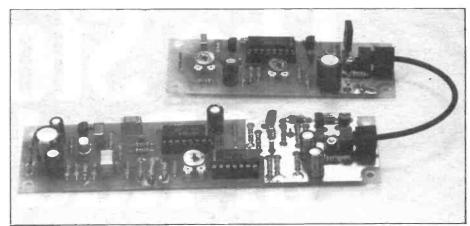

performance, especially if an expander is used at the receiver output.

Another application could include computer data transmission. The system bandwidth will not allow very high baud rates, but this could be improved on by removing much of the receiver output filtering components as required, and is a matter for some further experimentation by the enthusiast.

FIBRE OPTIC LINK Rx PARTS LIST

RESISTORS: All	0.6W 1% Metal Film		
R1,2	22k	2	(M22K)
R3,8,12,15,16,24	10k	6	(MIOK)
R4,22	4k7	2	(M4K7)
R5	1k2	1	(M1K2)
R6,13,17.19	47k	4	(M47K)
R7.20	470k	2	(M470K)
R9,23,25	470Ω	3	(M470R)
R10.11	100k	2	(M100K)
R14	43k	1	(M43K)
R18	15k	1	(M15K)
R21	1k	1	(MIK)
R26	100Ω	1	(M100R)
RV1	47k Hor S-min Preset	1	(WR60Q)
CAPACITORS			
C1,3,5,14	100 µF 10V PC Electrolytic	4	(FF10L)
C2	100pF Polystyrene	1	(BX28F)
C4	10nF Polylaver	- 1	(WW29C)
C6	470pF 1% Polystyrene	1	(BX53H)
C7 -	330pF 1% Polystyrene	1	(BX51F)
28	220µF 16V PC Electrolytic	i	(FF13P)
C9,11,13	InF Ceramic	3	(WX68Y)
C10,15	100nF Polylayer	2	(WW41U)
C12	470nF Polylayer	1.5	(WW49D)
C1 6	10μF 50V PC Electrolytic	1	(FF04E)
SEMICONDUCT	ORS		
DI	1N4148	1	(QL80B)
rr1	BC650	1	(QB74R)
TR2,3,5	BC548	3	(QB73Q)
rr4	BC109C	1	(QB33L)
Cl	4093BE	1	(OW53H)
C3	4046BE	1	(QW32K)
R2	F/Optic Detector MFOD71	1	(FD12N)
MISCELLANEOU	US		
	F/Optic Rx PCB	1	(GD28F)
	Veropins 2148	1 Pkt	(FL24B)
	DIL Socket 14-pin	1	(BL18U)
	DIL Socket 16-pin	1	(BL19V)
	8BA x 1/ain Bolt	1 Plat	(BF08])
	8BA Nut	1 Plet	(BF19V)

A complete kit of all parts is available for this project:

Order As LM11M (Fibre Optic Rx Kit) Price £8.50

The following items in the above kit list are also available separately, but are not shown in the 1986 catalogue: Fibre Optic Detector MFOD71 Order As FD12N Price £1.98

Fibre Optic Rx PCB Order As GD28F Price £1.80

FIBRE OPTIC LINK TX PARTS LIST

RESISTORS: A	il 0.6W 1% Metal Film		
R1,4,5	10k	3	(M10K)
R2	47k	1	(M47K)
R3	2M2	1	(M2M2)
R6	100Ω	1	(M100R)
R7	22k	1	(M22K)
R8,12	47Ω	2	(M4TR)
R9,11	lk	. 2	(MIK)
R10	21x2	1	(M2K2)
RV1	100k Hor S-min Preset	1	(WR61R)
RV2	47k Hor S-min Preset	1	(WR60Q)
CAPACITORS			
Cl	39nF Polylayer	1	(WW36P)
C2	100μF 10V PC Electrolytic	1	(FF10L)
C3	470pF 1% Polystyrene	1	(BX53H)
C4	220nF 35V Tantalum	1	(WW86L)
C5	230µF 16V PC Electrolytic	1	(FF13P)
SEMICONDUC	TORS		
TR1,2	BC548	2	(QB73Q)
TR3	BD139	1	(QF07H)
IR1	F/Optic Emitter MFOE71	1	(FD14Q)
IC1	4046BE	1	(QW32K)
MISCELLANE			
	F/Optic Tx PCB	1000	(GD29G)
	DIL Socket 16-pin	1	(BL19V)
	Veropins 2148	1 Pla	(FL24B)
	8BA x 1/4 in Bolt	1 Pkt	(BF08J)
	8BA Nut	1 Pkt	(BF19V)
	Constructor's Guide	1	(XH79L)
OPTIONAL			
	F/Optic Light Guide	As req	(XR56L)

A complete kit of all parts, excluding optional item, is available for this project:

Order As LM12N (Fibre Optic Tx Kit) Price £6.50

The following items included in the above kit list are also available separately, but are not shown in the 1986 catalogue: Fibre Optic Emitter MFOE71 Order As FD14Q Price £2.35

Fibre Optic Tx PCB Order As GD29G Price £1.25

Constructor's Guide Order As XH79L Price 25p NV

The Story of Radio

n 1899, Marconi gave a demonstration of wireless telegraphy on Salisbury Plain. Present at this event were representatives of the Post Office, the Royal Navy and the Army, the latter including an officer of the Royal Engineers. As a result, some wireless sets were despatched to South Africa to help in the Boer War, which they failed to do and so were transferred to ships. The early military attitude to wireless was lukewarm; at best it might be considered an adjunct to the cavalry. Consequently, at the outbreak of war in 1914, the British Army was not particularly well equipped with the new technology.

By 1903, all ships of the Royal Navy had been fitted with Marconi wireless equipment.

The situation in the Royal Navy was much better. Some of their ships had been fitted with wireless as early as 1899 and, in 1900, a contract with the Marconi Company was signed for the supply of two shore stations and twenty-six shipboard installations. By 1903, all ships of the Royal Navy had been fitted with Marconi wireless equipment. The use of wireless had also become universal in the U.S. Navy, and quite widespread in the German Kriegsmarine.

Wireless with Wings

There was of course, in Britain at least, no separate air force prior to World War One. But experiments had been carried out to take wireless equipment aloft. The Royal Engineers, from which the Royal Flying Corps and, later, the Royal Air Force, emerged carried out some tests with their balloons. In 1907, Lieutenant C.J. Ashton ascended in a captive balloon and became the first person to receive signals from the ground. In the following year, two-way communication was established with a free balloon, the Pegasus, when signals were received from Aldershot, twenty miles away.

by Graham Dixey
C.Eng., M.I.E.R.E.

Part Four—
The First World War

From balloons to airships was a natural step and, in 1911, the airship Beta was used, equipped with a transmitter and receiver. Captain Leroy of the Royal Engineers went up in her and made contact with the ground at distances up to thirty miles. A slight snag was that the airship's engines had to be stopped during reception! However, the value of the 'eye in the sky' was shown during exercises in 1912, when the airship Gamma reported consistently on the movements of the 'enemy' below. It pointed the way for the value of wireless in the conflict


to come, though during the Great War the Army used aeroplanes in the spotting role, as airships close to the ground were far too vulnerable.

The feasibility of equipping an aeroplane, as opposed to an airship, with wireless had been shown quite recently, in 1910 in fact. The demonstrations had taken place on both sides of the Atlantic. McCurdy in a Curtiss had effected two-way communication at Sheephead Bay, New York, while the well known British actor, Robert Loraine, had taken up a transmitter in his Bristol during the Salisbury Plain manoeuvres, and made contact with a receiver on the ground.

In 1907, Lieutenant C.J. Ashton ascended in a captive balloon and became the first person to receive signals from the ground.

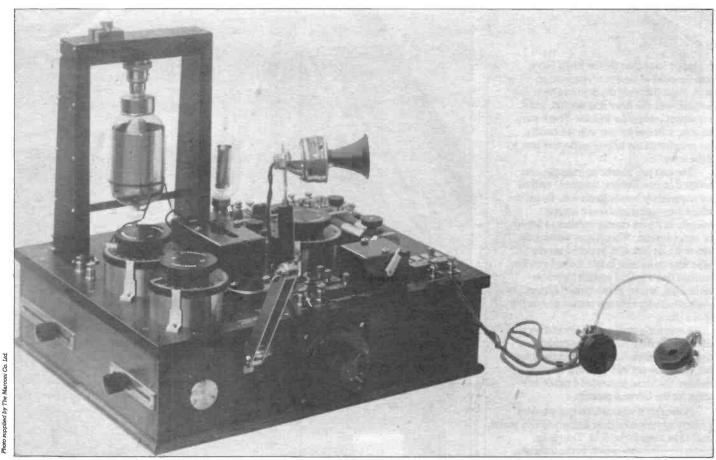Message transmitted from an aircraft to the ground, September 1910 over Salisbury Plain.





Set used by Marconi during telephone experiments between vessels at anchor 10 kilometres apart in Italy 1914.

Not to be left out of the picture, the Royal Navy were busy putting wireless sets into some of their aircraft and, in 1912, there occurred the first instance of the rescue of an aircrew downed in the drink, as a direct result of wireless. This came about when Lieutenant Fitzmaurice and Commander Samson suffered an engine failure in their Short seaplane and had to put down on the sea. Because of the signals they sent when the trouble developed, they were soon rescued by the ship Hermes.

In the Beginning

During the opening months of World War One, the whole country was caught up in the most incredible spy mania. Most people, including those in positions of authority, had little idea of the potentialities of wireless and there was the fear that anyone who owned anything remotely connected with this 'dark art' was likely to be a German agent. As a result, everyone was required by law to register any equipment in their possession, even a simple crystal set! One young man who was an avid experimenter was found to have a roomful of apparatus and so languished in gaol for nine months because he hadn't registered it!

By the outbreak of war in August 1914, wireless had not developed sufficiently for Britain to possess transmitters with a world wide range. But, she did have an Empire and a number of cables. The combination of the two made communication with the Royal Navy possible, wherever the ships were to be found. So it was that, on August 3rd 1914, the following messages were received by ships of the Royal Navy.

'Admiralty to all ships – Urgent message. The war telegram will be issued at midnight authorising you to commence The value of the 'eye in the sky' was shown during exercises in 1912, when the airship Gamma reported consistently on the movements of the 'enemy' below.

hostilities against Germany but in view of our ultimatum they may decide to open fire at any moment. You must be ready for this.'

Followed by a few hours later:

'Commence hostilities against Germany.'

Both the Royal Navy and the German Kriegsmarine had full wireless contact with their ships at sea. Cipher was used in the passing of messages of course but, right at the beginning of the war, the British gained an enormous advantage over their enemy by the most incredible stroke of luck.

At the beginning of September 1914, the German light cruiser, Magdeburg, was wrecked in the Baltic. The body of an unter-offizier was hauled out of the sea by the Russians a few hours later and, clasped firmly in his arms, held there by rigormortis, were the German Navy's cipher and signal books, together with detailed maps of the North Sea and the Heligoland Bight!

The whole country was caught up in the most incredible spy mania; most people had little idea of wireless and there was the fear that anyone who owned anything remotely connected with it was likely to be a German agent. The Russians felt that Britain, as the leading naval power, should have the use of these important documents and so they were handed over to us.

As a result, we were able to monitor all communications between Germany and her warships for the early part of the war (until it was realised why we always knew where the German ships were!) and decipher them at ease. Then the Germans changed their codes.

Find the Direction

However, by the time that had happened, wireless was being applied in a new role, that of direction finding. DF stations were set up on the east coast, for example at Aberdeen, Flamborough and Lowestoft, and with them it was possible to pinpoint the activities of enemy vessels. This could only be done if the ships were actually transmitting, of course, but as it happened the Germans had not learnt the value of wireless silence.

In fact, the battle of Jutland came about because the British could follow the passage of the German High Seas Fleet and so were able to put to sea to intercept it.

Submarines were also equipped with wireless in order to maintain contact with their bases and, although the transmissions were brief, they were sufficient to allow the DF stations to plot the course of the German U-boats. By co-operating with the aircraft of the Royal Naval Air Service, it was possible to vector a seaplane or flying boat onto the enemy, with a fair chance of finding and destroying it.

Field Radio

As already mentioned, the British Army entered World War One in a much

less happy state than did the Royal Navy, from the point of view of wireless equipment. What the army did have had been designed with the Boer War in mind, and it was almost useless for its task. There were ten sets, supplied for use with the cavalry, that prestigious but largely ineffective arm of the army.

The cart set, to take an example, was mounted on two limbers, weighed two tons and required six horses to draw it. To get the station fully operational was a lengthy process, as it took twenty minutes to set up the aerial system. When it was working the selectivity, or lack of it, imposed severe limitations on its use. In fact, so bad was the situation that a special system had to be worked out, known as the 'period system', in which effectively only one station was on the air at a time!

It was not a system that worked very well and so it did little to inspire confidence in the use of wireless. Another problem was that, when the set was used in a 'forward' position, the aerial presented a rather nice target for the German gunners.

However, it was obvious that wireless properly developed and applied would be a useful asset to an army in the field. Telephone lines were used extensively in the trenches, but they were easily cut, and could also be tapped into. What was required was a shortrange portable set so, in August 1915, the British field wireless set was ordered.


These were first used at the Battle of Loos and actually worked very well. This set had a range of 4000 yards when it was used with a 180 foot long aerial, supported on 12 foot high masts, but gave a better range on a *longer* aerial! A crystal detector was used. It is interesting to note that, in London where Dr. W.H. Eccles was working on the use of the thermionic valve for wireless, he was able to pick up the transmissions from the Western Front in Flanders.

The early transmitters were of the spark type but when later, in 1917, it became possible to generate continuous oscillations (called CW for Continous Wave), CW transmitters appeared on the Western Front which gave a range of 6000 yards with an aerial system only 30 feet long and 2 to 3 feet high.

The big problem with wireless in the army was not the equipment as such, but the general attitude to its use. It simply wasn't trusted by those in command and, consequently, was never employed to the extent that it could or should have been. Nevertheless, it did have one particular use which was exploited effectively, and that was for artillery observation. In this application aircraft were used as spotters for the artillery, directing the fall of shot.

Wireless Aeroplanes

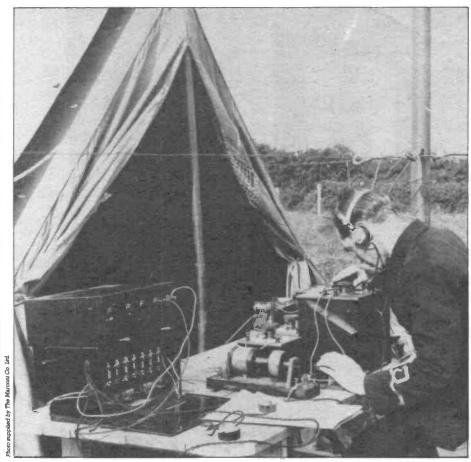Two wireless sets were designated for aircraft use, known as the type L and L1 respectively. The former weighed 50lb and had a range of 15 miles for a power rating of 40W; the latter had the very much greater range of 80 miles, achieved using an aerial power of 500W, but weighed 200lb, which made it an unlikely proposition for the



Mobile wireless set 1916.

typical artillery observation aeroplane whose payload was very limited. However, of a number of methods tried for communicating the desired information to the ground, the use of wireless telegraphy turned out to be the most effective.


There were still some of the old problems though of mutual interference due to lack of selectivity. The answer was to use sets of low power and a minimum spacing of about 2000 yards between adjacent 'wireless aeroplanes'. An example of this type of set was the Sterling, which was manufactured by the Sterling Telephone Co Ltd to the designs of Lt. Leroy, an RNVR officer serving with the RNAS. It weighed only

It took twenty minutes to set up the aerial system . . . When the set was used in a 'forward' position, the aerial presented a rather nice target for the German gunners.

20lb, which made it possible for an observer to be carried, who could deal with its operation, leaving the flying to the pilot. Hitherto the pilot had had to handle the aeroplane, observe the effects of the artillery bombardment and pound out the relevant information in morse code at the same time!

A special wireless unit was built up, which later became No.9 Squadron, Royal Flying Corps. Later still every battery of guns had its own spotting plane. By the end of the war about 600 British aircraft were fitted with wireless telegraphy equipment, and there were some thousand or so ground stations.

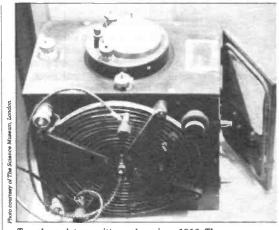
Wireless 'telegraphy' meant, of course, morse code. However, there were experi-



Trench spark transmitter and receiver, 1916. The receiver aerial is laid along the floor of the trench while part of the transmitting section was hoist on a bayonet in the Parapet.

ments with radio telephony (RT) as early as 1914. A Captain Dowding, later Lord Dowding of Battle of Britain fame, while with No. 9 Sqdn. RFC, took a Maurice Farman biplane aloft, which was fitted with a telephony transmitter. He was assisted by a professional wireless engineer, one C.E. Prince, and was able to lay claim to being the first person in England to receive an airborne radio telephone transmission. The War Office decreed that such impracticable experiments must cease, but evidently relented later because, by 1915 a working RT set had been put into service which had a special microphone capable of working close to the aeroplane's engine.

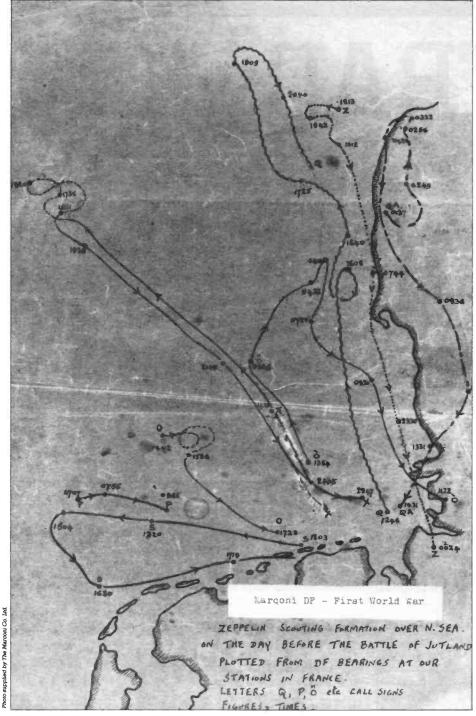For a long time transmission was a oneway affair, because the high noise level in the air made it difficult to understand messages received from the ground. However, by shouting into his microphone the operator could get a good enough



 ${\it DF bearings of Zeppelins over the North Sea.}$

The body of an unterofficier was hauled out of the sea by the Russians a few hours later and, clasped firmly in his arms, were the German Navy's cipher and signal books

signal/noise ratio to make one-way working practicable. The other problem with airborne reception was the way in which the vibration of the airframe affected the stability of the contact between the 'cat's whisker' and the crystal. The introduction of balanced carborundum crystals improved this situation.

Another weapon of war appearing at this time was the tank. To direct the tank force effectively also meant control from the air. RT was tried, but the range was too limited to be effective. WT was much better but here there was also a slight snag. The

tank had to stop and set up an aerial whenever it wanted to communicate! There is much we take for granted today.

Signal Corp

Throughout the various theatres of operations of World War One, wireless was employed with a greater or lesser degree of usefulness, but it seems that the former was more prevalent because, by the middle of 1918, the army 'brasshats' realised that a separate organisation was needed to control the use of wireless, both WT and RT. Though too late to see service in the First World War, the Royal Corps of Signals was formed in 1920.

For the first time the civilians, well away from the battle lines, became involved in a major conflict between combatant powers. This was one of the less desirable by-products of the new age of aerial transportation. The Germans, as well as the

British, built some heavy bombers with a moderate war load and respectable range. However, the Germans, just across the Channel had an advantage, which they followed up.

While a substantial number of air raids were carried out on English towns, with the consequent loss of life and extensive damage to property, it is the Zeppelin that has captured the public imagination rather than the Gotha and Friedrichshafen bombers. Perhaps it is their immense size that accounts for this, the huge gas-filled envelopes droning above the cloud cover, dropping their explosive cargoes indiscriminately.

WT was much better but here there was also a slight snag. The tank had to stop and set up an aerial whenever it wanted to communicate!

Wireless was used by both sides in this form of warfare. The Zeppelins could only be attacked if the element of surprise could be achieved. This meant knowing sufficiently well in advance the likely course and height of the intruders. Thus, DF was used to plot the enemy's course and the use of wireless communication directed the defending fighters onto him. Although the little singleseater scouts used for air defence were nimble, the giant airships could rise very rapidly out of range, just by jettisoning ballast, carried in the form of water. It was very much a 'cat and mouse' game, but in the end the Zeppelins were too vulnerable. Although 'radar' had to wait for another war to bring it into existence, wireless played a similar and vital role during the Great War.

The Germans used wireless for communication between airships (and aeroplanes), for communication with their bases and also for navigation. For the latter purpose, the Germans set up a network of DF stations, able to take bearings on signals transmitted from an airship, that could provide a fix for an airship commander. It was, of course, this very provision that allowed the British to plot the enemy's

The Germans set up a network of DF stations, able to take bearings on signals transmitted from an airship, that could provide a fix for an airship commander.

incoming track and so scramble the defending fighters in time!

As wireless had assisted the purposes of war, in the end it was used to announce to a tired and waiting world the most welcome news of all.

On top of Marconi House in London a constant vigil was kept to listen out for the transmissions of the French station FL on the Eiffel Tower in Paris. At 0500 hours on November 11th, the following message was received and despatched to Downing Street.

'From Marshal Foch to All Allied Commanders – Hostilities will cease at 11.00 o'clock.' AMSTRAD
8 BIT
INPUT
PORT

his article describes a simple 8-bit input port which plugs into the expansion connector on the rear of the Amstrad CPC 464/664/6128 range of computers and allows information from the outside world to be read and stored by the computer. It may be used, for example, to interface the weather satellite decoder described elsewhere in this issue with the Amstrad computers.

Circuit Description

In Figure 1, IC1 decodes \overline{IORQ} and A5 - A7 to produce \overline{IOSEL} , which is active for any valid external I/O address, enabling IC2 when \overline{RD} is active and A4 is high.

This locates the port within the second block of 16 addresses in the valid external I/O area starting at \$F8E0, although the constraints imposed on the design complexity by the low cost specification precluded complete address decoding, so there are 'ghost images' of the port in the other I/O areas. For this reason, the port address may also be located at any two addresses within the block of sixteen by fitting one of the eight links as shown in Table 1.

By carefully choosing the link required, it should be possible to avoid overlapping the port with any other external I/O mapped device used within the system.

Finally, IC3, when enabled via the link fitted, gates any data present on P_0 - P_7 onto the data bus to be read by the processor.

Construction

Referring to the Parts List and the legend, as shown in Figure 2, fit and solder the IC sockets, ensuring that the notch on each socket aligns with the legend. Locate and solder the three

by Mark Brighton

- ★ Inexpensive Easy to Build and Fit
- * Compatible with BBC User Port Socket

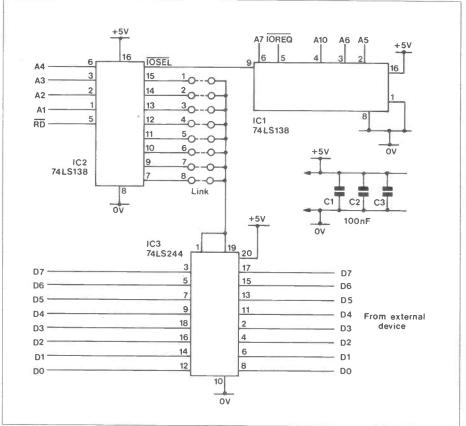


Figure 1. Circuit Diagram.

 $0.1\mu F$ decoupling capacitors. Then fit PL1 and the IDC cable of your choice, with the stripe on the cable at the pin 1 end of the legend! Lastly, fit the link previously selected from Table 1, and proceed to solder all connections and check the PCB for dry joints, short circuits, etc. Fit all ICs into their sockets, noting correct orientation. Figure 3 shows PL1 pin connections looking into the connector, onto the pins.

Testing

There is a choice of cables given in the Parts List, but you will probably use cable FD22Y for most applications. Plug the IDC cable into the expansion connector on the Amstrad, with the stripe on the left side when viewed from the front of the computer. If an external disk drive or other peripheral is to be used, plug this into the socket mid-way along the alternate IDC cable (FD24B) which must be used in conjunction with our Reversiboard (GD37S) to ensure that the peripheral is connected correctly, see Figure 4.

Switch the computer on, switching off again immediately if the computer fails to initialise in the normal way of displaying the 'ready' prompt.

If all is well, reading the address chosen with an 'INP' command should return the number set-up on the port inputs (if nothing is connected to the port, 255 will be read).

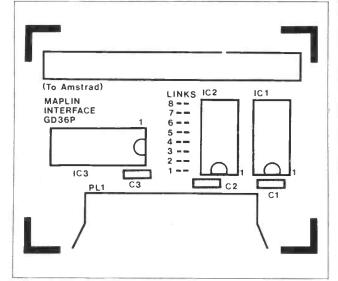


Figure 2. Board Layout.

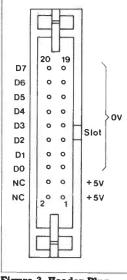


Figure 3. Header Plug.

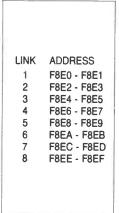


Table 1.

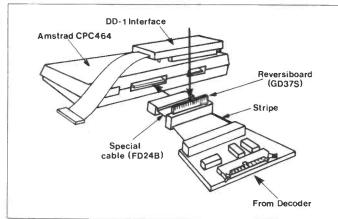


Figure 4. Alternate cable.

AMSTRAD 8-BIT I/P PORT PARTS LIST

-			
CAPACITORS C1-3	100nF Minidisc	3	(YR78S)
SEMICONDUC.	PORS		
IC1,2	74LS138	2	(YF53H)
1C3	74LS244	1	(QQ86L)
MISCELLANEO	US	MAG	
	Amstrad Interface PCB	1355	(GD36P)
PL1	20-way IDC Header R/A	1	(FT72P)
	DIL Socket 16-way	2	(BL19V)
	DIL Socket 20-way	1	(HQ77))
	Bolt 6BA x 1/2"	1 Pkt	(BF06G)
	Nut 6BA	l Pkt	(BF18U)
OPTIONAL			Assistant Control
	Cableform Amstrad/Interface	1	(FD22Y)
The same of	Cableform Amstrad/Disc/Interface	1	(FD24B)

A complete kit of all parts, excluding optional items, is available for this project:


Order As LM14Q (Amstrad 8-bit I/P Port Kit) Price £9.50

The following items included in the above kit list are also available separately, but are not shown in the 1986 catalogue:
Amstrad Interface PCB Order As GD36P Price £5.95

Amstrad/Interface Cable Order As FD22Y Price £7.20

Amstrad/Disk/Interface Cable Order As FD24B Price £12.15

Reversiboard Order As GD37S Price £2.50

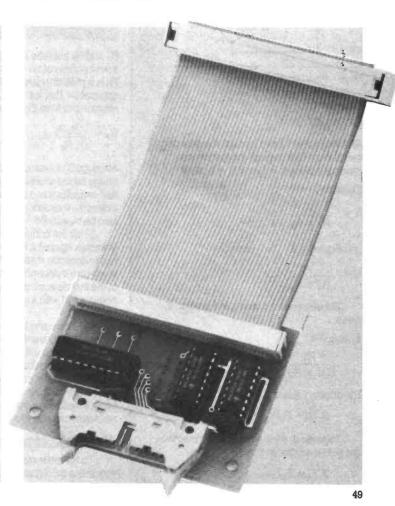

TEST GEAR AND MEASUREMENTS

by Danny Stewart Part 2

aving established some internationally recognised standard units of measurement in Part 1 of this series, we shall now take a look at some actual practical methods of measuring electrical properties.

Wheatstone Bridge

A basic bridge circuit is shown in Figure 1, where D is a detector, usually a galvanometer or any other sensitive current meter. The bridge is balanced when the voltage across the detector is zero volts and there is no current flowing through it. This can be expressed as:

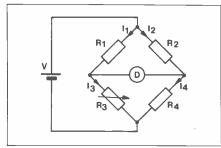


Figure 1. Basic Bridge.

Equation 1.

$$I_1R_1 = I_2R_2$$

And if no current flows through the detector, then it must flow through the resistance dividers making $I_1 = I_3$ and $I_2 = I_4$, also:

Equation 2

$$I_1 = -\frac{V}{R_1 + R_3}$$

and Equation 3.

$$I_2 = \frac{V}{R_2 + R_4}$$

Substituting for I_1 and I_2 in Equation 1 gives:

Equation 4


$$\frac{R_1}{R_1 + R_3} = \frac{R_2}{R_2 + R_4}$$

Simplifying Equation 4 gives Equation 5:

$$R_1R_4 = R_2R_3$$

In general, if the arms of the bridge are not pure resistances then:

$$Z_1Z_4 = Z_2Z_3$$

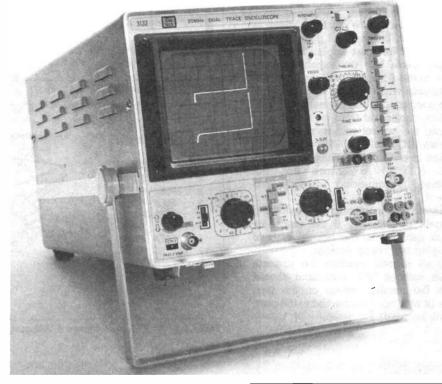

 R_1 and R_2 are ratio arms and are switchable from fractions of an ohm to several megohms. R_3 is a precision standard which is also selectable. This leaves R_4 as the unknown resistor and from Equation 5, Equation 6:

$$R_4 = \frac{R_3 R_2}{R_1}$$

Although this example illustrates the use of a bridge for measuring resistance, inductors and capacitors can also be measured. Indirectly, frequency and phase angle can also be measured.

Since the bridge method compares the unknown against a fixed standard, this is a highly accurate method. Also the measurements are independent of the characteristics of the null detector as long as the detector can detect a null with a reasonable degree of sensitivity.

Therefore any lack of accuracy will be attributed to tolerance of the three resistors and any *heating effect* of the current through the resistors, particularly for low values of resistance. Inaccuracy can also be due to an insensitive null detector. Inspite of all this, the basic Wheatstone Bridge is used to measure resistors from one ohm to one Megohm.

Kelvin Bridge

To measure resistor values below 1 ohm requires a modification to the basic

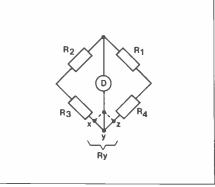


Figure 2. Measuring Resistor Values below 1Ω .

Wheatstone Bridge. Figure 2 shows the problem. The resistance of the leads become significant in measuring the unknown resistance.

Connecting the detector to either x or z means increasing the resistance in the respective bridge arms. But if the detector is connected to point y such that:

$$\frac{Rxy}{Rvz} = \frac{R_2}{R_1}$$

then the bridge balance conditions are met and:

$$R_4 = \frac{R_1}{R_2} R_3$$

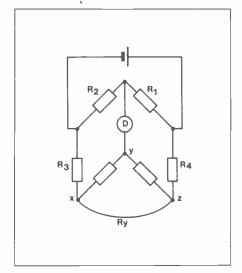


Figure 3. Kelvin Double Bridge

where R4 could be the unknown resistor.

Figure 3 shows a Kelvin double bridge, so called because it contains an additional pair of ratio arms to eliminate the effect of wire xz. As before:

$$\frac{Rxy}{Ryz} = \frac{R_2}{R_1}$$

The Kelvin Bridge can be used to measure resistors down to 0.00001 ohm. If R_3 is the standard resistor then it could be arranged in steps of 0.001 ohm, as shown in Figure 4. A manganin bar of 0.0011 ohm provides a sliding contact for small adjustments and for good accuracy as much of the standard resistance must be included in the circuit. This depends on the ratio of R_1 to R_2 . As for the Wheatstone Bridge, R_1 and R_2 are switchable in decade steps.

Murrary Loop Test

A modified form of the Wheatstone Bridge is used to detect wires shorting to earth in a telephone cable.

If a wire is shorting to earth at point x, Figure 5, it is connected to a good wire at the far end and both wires connected to a Wheatstone Bridge. In this way both wires will contribute towards two arms of the bridge, with point x the dividing point. The balance condition is given by:

$$\frac{R_1}{R_2} = \frac{R_L - R_X}{R_X}$$

where R_L is the total resistance of the two wires, R_X is the resistance from the bridge to point x.

Therefore,
$$R_x = \frac{R_2 \cdot R_L}{R_1 + R_2}$$

length is proportional to resistance, so we can replace R_{X} and R_{L} above.

$$Lx = \frac{R_2 (L_1 + L_2)}{R_1 + R_2} \setminus$$

Also $L_1 = L_2$

Hence Lx =
$$\frac{R_2}{R_1 + R_2}$$
 · 2L

and the distance to the faulty point can be calculated.

September 1986 Maplin Magazine

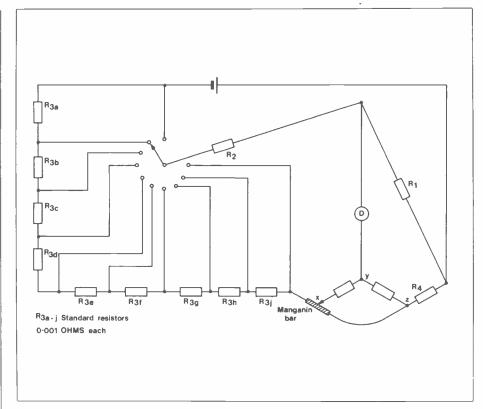


Figure 4. Stepped Resistors.



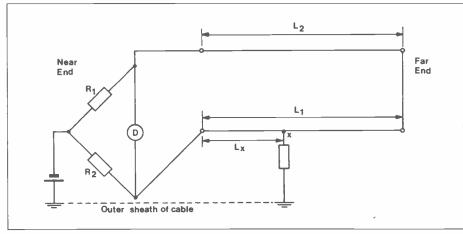


Figure 5. Murrary Loop Test.

Varley Loop Test

This is a further modification of the Wheatstone Bridge and is also used to detect cable faults, e.g. crossed connections, short circuits or earth faults. This test is usually used to locate a fault down to a cable section and is capable of locating within 500 feet in a 50 mile section. The Murrary test can then be used to locate within the section, therefore the Murrary test set is usually of the portable variety, employing batteries.

The Varley test is a more complex test than the Murrary test and employs three wires with different connection arrangements, see Figure 6a, b, c.

Compared to the Murrary Bridge, the Varley has resistors in three arms instead of two and the variable resistor is placed in the third arm. The ratio arms R_1 and R_2 are varied by a dial to give a ratio from 0.001 to 1,000 in decade steps.

Analysis of the circuits in Figure 5 yield:

$$\begin{aligned} Lx &= & \frac{R_1 \, \cdot \, (B - A)}{R_1 \, + \, R_2} \\ (L_1 - Lx) &= & \frac{R_1 \, \cdot \, (C + B)}{R_1 \, + \, R_2} \end{aligned}$$

Substituting the results of the measurements in the above two equations gives the distance to the fault. It can be seen that one equation provides a check on the other.

A.C. Bridges

An a.c. bridge will require an a.c. power source and an a.c. detector, and is used for measuring inductors, capacitors, frequency, i.e. anything other than resistance which is the domain of d.c. bridges.

An a.c. bridge then, will have the general format of Figure 7, where the Z values are capacitors or inductors with their associated resistive components. the detector can be a pair of headphones or magic eye (electron ray tube).

At low frequencies, the domestic mains supply is an adequate source but at higher frequencies an oscillator must be used at the frequency for which the component is designed.

For bridge balance, the potential difference across the detector has to be zero, as for d.c. bridges. This will occur when the potential difference across Z_1 is the same as that across Z_2 in both magnitude and phase.

i.e.
$$I_1Z_1 = I_2Z_2$$

also $I_1 = \frac{V}{Z_1 + Z_3}$
and $I_2 = \frac{V}{Z_2 + Z_4}$

Substituting for I1 and I2 gives:

$$Z_1Z_4 = Z_2Z_3$$


or using admittances


$$Y_1Y_4 = Y_2Y_3$$

In complex rotation, the magnitudes are multiplied and the phases angles added:

$$Z_1Z_4 / (\Theta_1 + \Theta_4) = Z_2Z_3 / (\Theta_2 + \Theta_3)$$

and for balance, not only must $Z_1Z_4 = Z_2Z_3$ but $f(\Theta_1 + \Theta_4)$ must equal $f(\Theta_2 + \Theta_3)$.

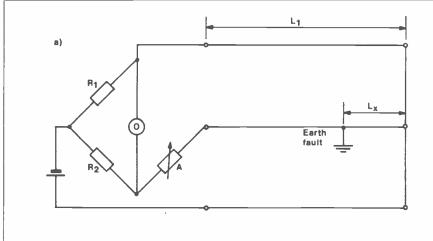

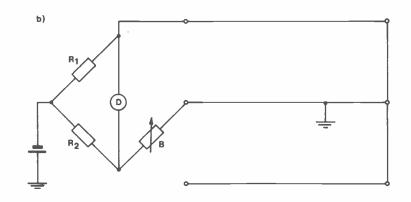

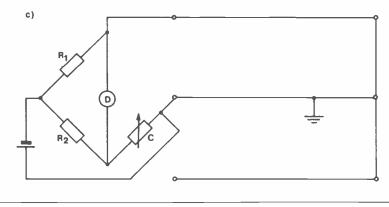


Figure 6. Varley Loop Test.

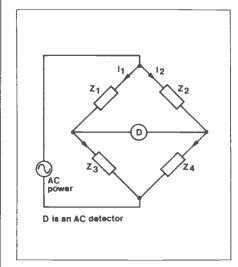


Figure 7. A.C. Bridge.

Capacitance Bridge

Figure 8 shows a bridge arrangement for measuring capacitance where Cx is the unknown capacitor and Rx its associated leakage resistance. These two components are reflected on the other side of the equation by standard capacitor Cs and a variable resistor Rs.

Now
$$Z_1 = R_1, Z_2 = R_2,$$

 $Z_3 = R_S - \frac{j}{wC_S}, Z_4 = Rx - \frac{j}{wC_X}$

Substituting in $Z_1Z_3 = Z_2Z_4$

$$\begin{aligned} &\mathsf{R}_1 \left(\frac{-\mathsf{R}\mathsf{X} - \mathsf{j}}{\mathsf{w}\mathsf{C}_\mathsf{X}} \right) = \mathsf{R}_2 \left(\frac{-\mathsf{R}_\mathsf{S} - \mathsf{j}}{\mathsf{w}\mathsf{C}_\mathsf{S}} \right) \\ &\mathsf{R}_1 \mathsf{R}_\mathsf{X} - \mathsf{R}_1 \ \frac{\mathsf{j}}{\mathsf{w}\mathsf{C}_\mathsf{X}} = \mathsf{R}_2 \mathsf{R}_\mathsf{S} - \mathsf{R}_2 \frac{\mathsf{j}}{\mathsf{w}\mathsf{C}_\mathsf{S}} \end{aligned}$$

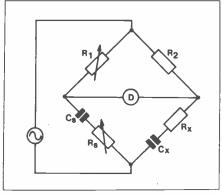


Figure 8. Bridge for Measuring Capacitance.

Such equations are solved by equating real and imaginary expressions separately. Equating real terms:

$$R_1R_x = R_2R_S$$

Equation 7.

$$Rx = \frac{R_2R_S}{R_1}$$

Equating imaginary terms:

$$\frac{jR_1}{wC_X} = \frac{jR_2}{wC_S}$$

Equation 8.

$$C_X = \frac{C_S R_1}{R_2}$$

 $C_{\rm X}$ is a precision standard capacitor that cannot be adjusted and since $R_{\rm S}$ does not appear in Equation 8, it can be made adjustable. One other variable component is required in order to balance the above two equations. Unfortunately, the choice is between $R_{\rm 1}$ and $R_{\rm 2}$ which appear in both equations.

If R_1 is chosen, then R_1 and R_8 need to be changed alternately for minimum sound in the headphones until balance is obtained. This is called convergence.

Schering Bridge

Figure 9 shows a Schering Bridge which is one of the popular bridges for measuring capacitors and insulators.

For measuring insulation (phase angle nearly 90°), C_S is an air dielectric capacitor. Otherwise, C_S is a mica capacitor which also has low loss and therefore, a phase angle of 00°

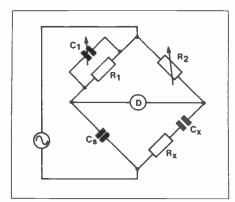


Figure 9. Schering Bridge.

September 1986 Maplin Magazine

Substituting in the balance equation

$$\begin{split} Z_{x} &= \quad \frac{Z_{2} \ Z_{3}}{Z_{1}} \\ \frac{R_{X} - j}{wC_{2}} &= \quad \left(\frac{R_{2} - j}{wC_{S}}\right) \left(\frac{1 + jwC_{1}}{R_{1}}\right) \\ \frac{R_{X} - j}{\widetilde{w}C_{X}} &= \quad \frac{R_{2} \ C_{1}}{C_{S}} - \frac{jR_{2}}{wC_{S}R_{1}} \end{split}$$

Equating real terms $R_X = \frac{R_2 C_1}{C_S}$

Equating imaginary terms $C_x = \frac{C_S R_1}{R_2}$

Inductance Bridge

The general form of an inductance bridge is shown in Figure 10 where Lx is the unknown inductor and Rx its resistive component. To balance these on the other side of the equation, the standard is in two parts, Ls and Rs.

Circuit analysis yields:

$$Rx = \frac{Rx \cdot R_2}{R_1}$$

$$Lx = \frac{Ls \cdot R_2}{R_1}$$

In an inductor, the resistive component is larger than that in a capacitor, so the resistive adjustment must be made first.

When measuring inductors, Q values must be taken into account. The Q of a coil is

WL and the Q of a capacitor 1 wCR. For Q walues above 10, a Hay bridge is used and for Q between one and ten, a Maxwell bridge is used. The reason for this will become clear

Hay Bridge

below.

Figure 11 shows a Hay bridge. The impedances of the arms are:

$$Z_1 = R_1 - \frac{j}{wC_1}$$
,
 $Z_2 = R_2$, $Z_3 = R_3$, $Z_x = Rx + jwLx$.

Substituting in $Z_1Z_x = Z_2Z_3$

$$\frac{(R_1 - j)}{wC_1}(Rx + jwLx) = R_2R_3$$

$$R_1 Rx = jwLxR_1 - \frac{jRx}{wC_1} + \frac{Lx}{C_1} = R_2R_3$$

Equation 9.

Equating real terms $R_1Rx + \frac{Lx}{C_1} = R_2R_3$

Equation 10.

Equating imaginary terms $wLxR_1 = \frac{Rx}{wC_1}$

Equations 9 and 10 each contain both Rx and Lx, therefore these equations need to be solved as simultaneous equations, yielding:

Equation 11.

$$Rx = \frac{wC_1^2R_1R_2R_3}{1 + w^2C_1^2R_1^2}$$

Equation 12.

$$Lx = \frac{C_1 R_2 R_3}{1 + w^2 C_1^2 R_1^2}$$

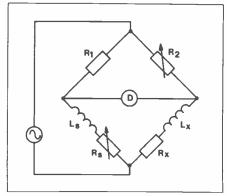


Figure 10. Inductance Bridge.

Substituting
$$Q = \frac{1}{\text{wCR}}$$
 in Equation 12:

Equation 13.

$$Lx = \frac{C_1 R_2 R_3}{1 + \left(\frac{1}{Q}\right)^2}$$

If Q = 10 then $(1/Q)^2$ = 0.01 and is insignificant and Equation 13 reduces to: Lx = $C_1R_2R_3$.

This final equation is the same as that for a Maxwell bridge, which has a different component arrangement.

Maxwell Bridge

A Maxwell bridge is suitable for coils with a Q between one and ten. Figure 12 shows the arrangement of components in a Maxwell bridge.

Now
$$Z_1 = \frac{R_1 \left(\frac{1}{jwC_1}\right)}{R_1 + \frac{1}{jwC_1}}$$

$$= \frac{\frac{R_1}{jwC_1}}{\frac{jwC_1R_1 + 1}{iwC_1}} = \frac{R_1}{jwC_1R_1 + 1}$$

$$Z_2 = R_2$$
, $Z_3 = R_3$, $Zx = Rx + jwLx$

Substituting in Z_1 $Z_x = Z_2Z_3$

$$\left(\frac{R_1}{jwC_1R_1+1}\right)(Rx+jwLx) = R_2R_3$$

Equating real terms:

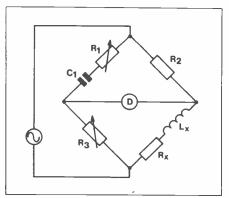


Figure 11. Hay Bridge.

Continued on page 62.

eneral purpose microphones are usually supplied as either high impedance or low impedance versions and occasionally, both. In the past, high Z (where 'Z' represents 'impedance') microphones have been the most commonly used in non-studio applications, especially for stage mixing and PA amplification. Modern technology has allowed for very high quality Low Z microphones to be more readily available at much lower prices.

Matching these devices to High Z system inputs poses a problem, due to the inherent low signal levels, and resulting lack of high frequency response. In the absence of Low Z input facilities on amplification equipment, a pre-amplifier is required to match the mic' output impedance and amplify signals to a level suitable for driving into high Z inputs.

The Low Z mic' pre-amp module is intended for this purpose, and is available either in kit form, for home constructors, or as a ready-built module complete with its own screening case.

Impedance

The term impedance, abbreviated to 'Z', is commonly used in electronics and the expression describes the joint opposition to the flow of current, caused by the presence of resistance and reactance, in the circuit. With microphones, be they dynamic or condenser types, it is

by Dave Goodman

- * Use with Balanced and **Unbalanced Microphones**
- \star 300 600 Ω Low Level Input, High Level Output
- * Very Low Noise and Distortion
- * Low Supply Current Drain

Low Z Mic **Pre-amp Module**

MODULE SPECIFICATIONS

Input

Impedance

 600Ω Balanced

 $(300 - 0 - 300\Omega)$

Typical

Signal Levels

1.25V out for

lmV in

Maximum **Output Level**

2V r.m.s (5.6V Pk)

Input/Output

Gain

30 to 50dB

Variable

Signal to

Noise Ratio Distortion

80dB

(@ lkHz)

0.02%

Frequency Response

50Hz to 30kHz (-ldB)

PSU Requirement - 9V @ 3mA

necessary to know the capabilities of the transducer, under specific operating conditions.

For instance, if a microphone output is designed to deliver 10mV of signal into a $47k\Omega$ load, then decreasing the load to $100k\Omega$ or more (remembering that a larger resistance is a lighter load) would allow a higher signal voltage, greater than 10mV, to be developed. Alternatively, increasing the load to 600Ω or less would greatly reduce the signal level developed.

To standardise these variations, microphone specifications typically state voltage (signal) levels with a particular impedance value; usually $47k\Omega$ for high Z mic's and 600Ω for low Z mic's. With high impedance microphones, frequency is important when driving into a reactive circuit. Inductive and capacitive reactances effect the microphone signal level dramatically, and specifications often apply to voltage and impedance values at a frequency of lkHz.

Low Z Balanced Lines

Figure 1 shows two typical configurations for balanced and unbalanced line connections to this module. Because Low Z mic signal levels are very low, in the order of 100 to $500\mu V$, induced noise and hum becomes a very real problem especially where long connecting cables are used. Not all microphones have the facility for balanced line connection

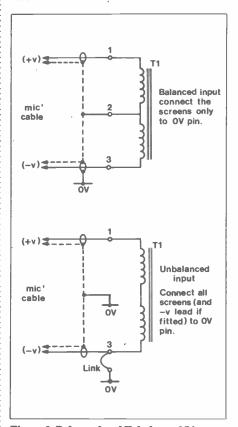


Figure 1. Balanced and Unbalanced Lines.

however, and in this case the unbalanced system must be adopted, although with degraded noise performance. The step up transformer, T1, can be used in either balanced or unbalanced systems with 600 and 300Ω microphones. 200Ω unbalanced lines can also be used, although output signal levels will be reduced by a few dB.

Circuit Description

Figure 2 shows ICI which is a very low noise, instrument grade op-amp offering wide bandwidth, high slew rates and reduced low frequency noise performance.

For improved component noise figures, gain determining components, R2 and R3, have low values of resistance and C2 prevents RF breakthrough problems associated with local radio transmissions. Capacitor C1 limits HF response and R1 with T1 secondary determine the input impedance for optimum performance of IC1.

The preset potentiometer RV1 allows gain adjustment over a 20dB range, with resistor R6 selected at $27k\Omega$. The signal output impedance is approximately 600Ω , but at a much amplified level, making for compatibility with high impedance equipment inputs, and DC isolation is maintained by C5. Diode D1 prevents circuit damage in the event that the power supply connections may be reversed, and the divider made up from R4, R5 provides a local '0V' central to the positive/negative supply rails, for the purpose of biasing the inputs of IC1. Input and output signals are consequently referenced to this 0V tap, and not the negative rail, which is connected to a top earth plane of the PCB to ensure stability.

September 1986 Maplin Magazine

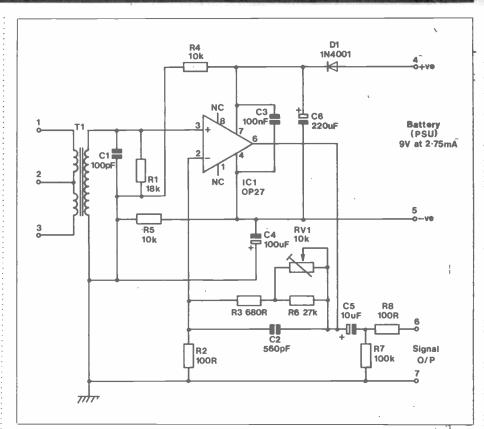


Figure 2. Circuit Diagram.

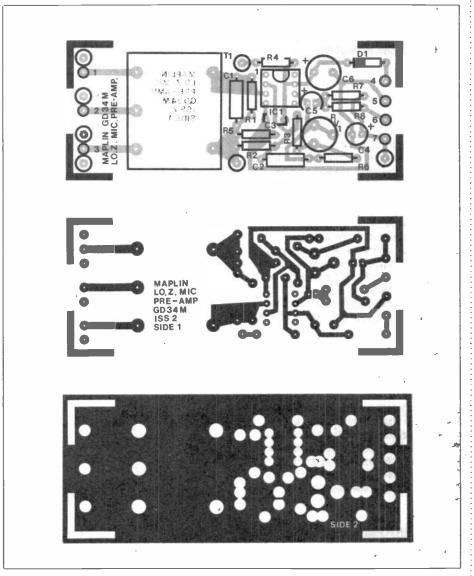


Figure 3. Track and Overlay.

Construction

Reference should be made to the 'Constructor's Guide' supplied with this kit (if you do not intend to purchase the complete kit then see the Parts List for the order code of the Constructor's Guide, price 25p), and Figure 3 which shows the PCB track and legend.

Component assembly is quite straight forward and is best begun by inserting 14 vero pins as detailed in Figure 4. Fit each pin into holes marked with a circle, from track side 1 and solder all pin heads. Seven of these pins require to be soldered on both sides of the PCB for connection to the earth plane.

Identify and insert resistors R1 to R8, and capacitors C1 to C6. Observe the polarity rules with electrolytics, and ensure there is adequate clearance between the leads of these components and the earth plane areas on top of the PCB.

Fit diode D1 and solder these components in position, removing excess wires, Mount IC1 directly into position on the board and insert RV1. Carefully solder these components and mount transformer T1 firmly onto the board and solder in place. Do ensure that the five terminating posts on T1 do not touch the earth plane or short across to any components. Clean the track areas and inspect all joints, looking for short circuits, etc.


Testing


A signal source is required, such as a microphone or AF signal generator, and also an amplifier or oscilloscope for monitoring the module output. Power supply requirements are low so a 9V battery, such as a PP3 can be used for this project. Connect the negative supply to Pin 5 (Figure 4) and positive supply via a milliammeter to Pin 4. With 9V applied, the current consumption is approximately 3mA; any large deviation from this figure will point to a fault condition such as D1 or IC1 fitted incorrectly, so switch off immediately and recheck. If all is well, connect a signal source across Pins 1 and 3, and wire Pin 3 to an adjacent 0V terminal.

Take the signal output from Pin 6 to a 'scope, or to an amplifier. Pin 7, connected to 0V, is the ground return connection for the 'scope or amp' cable screen/earth return. When using a signal generator, keep the peak-to-peak signal level at 5 to 10mV maximum, to avoid excessive distortion of the audio output. Turn RV1 clockwise for increased output signal or anticlockwise to decrease. When satisfied that the module is working, fit the screening case as follows.

Case Mounting Details

With reference to Figure 5 place a layer of insulating material cut to the size of the PCB (85 x 33mm) over the inside

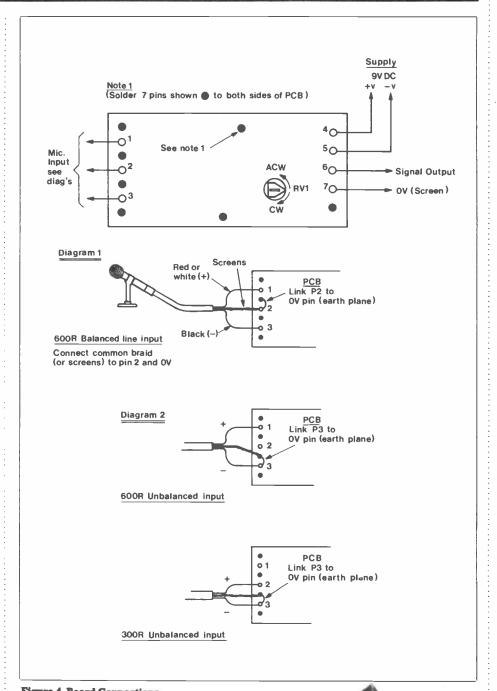

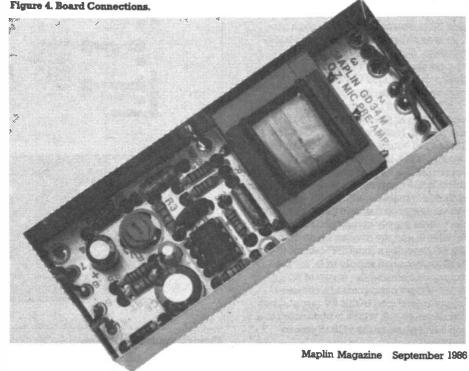

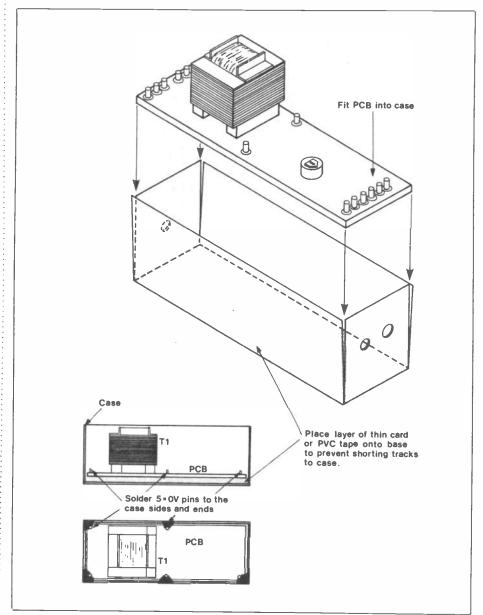


Figure 5. Mounting Module into Case.

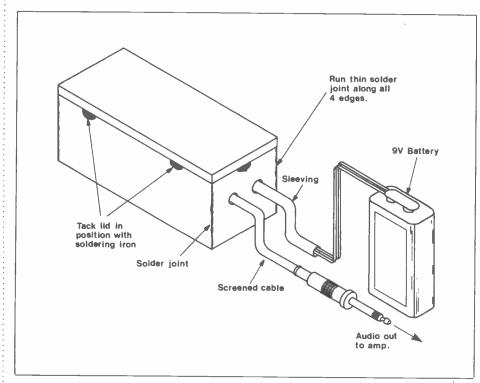


Figure 6. Final Assembly.
September 1986 Maplin Magazine

base area of the case. The material could be thin card, polythene or a few layers of PVC insulating tape. This insulation prevents the PCB tracks and joints from shorting to the case bottom. Insert the working module into the case with Pins 1 to 3 facing the case end panel that is drilled with a single hole only. If the module is a tight fit then the side plates can be spread apart or the PCB sides may be filed slightly to remove high spots, to help with this operation.

Push the module down towards the base until the transformer T1 just clears the top of the case, and does not obstruct the lid. Test that the module is still working correctly, and then apply small solder joints between all the 0V pins and the case sides as shown. Do not overheat the earth plane area, or put excessive amounts of solder onto the board. All that's required is a few small joints connecting the case to 0V, and to hold the PCB in position. The four corner edges can have a thin film of solder run along them, but electrically, this should not be necessary, especially if the module is required to be removed from the case later on.

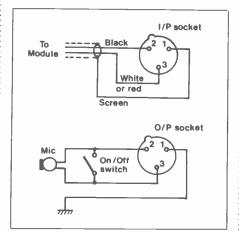


Figure 7. Wiring XLR Connectors.

Final Assembly


Input/output cables and battery/PSU connections can be made through the end panel holes of the case. Heat shrink sleeving can be fitted over thin wires to prevent them from chafing on the hole edges. Be careful when soldering wires to the PCB pins, as solder can run down onto the earth plane and cause a short circuit.

The input cable (from the microphone) screening braid can conveniently be soldered directly to the outside of the case as can the screened output cable from module to amplifier. Once wiring has been completed, fit the lid in position and distribute a few solder joints around the edges to seal the case, see Figure 6.

Figure 7 details various XLR plug and socket wiring arrangements for reference purposes; the terminals shown are standardised for most microphone/ mixer systems, and these connectors are recommended where small signal, low noise terminations are required.

LOW-Z MIC PRE-AMP PARTS LIST

LWIG I	100m以为10mm,10mm。10mm。10mm。	N THE SECOND	
RESISTORS: All	0.6W 1% Metal Pilm		
RI	18k	1	(M18K)
R2,8	100Ω	3	(M100R)
R3	690Ω	1	(M880R)
R4,5	10k	2	(MIOK)
R6	27k	1	(M27K)
R7	100k	1 4	(M100K)
RV1	10k Cermet		(WR42V)
CAPACITORS			
Cl	100pF Polystyrene	1	(BX28F)
C2	560pF 1% Polystyrene	1	(BX84I)
C3	100nF Minidisc	1	(YR78S)
C4	100µF 10V PC Electrolytic	1	(FF10L)
C8	10µF 16V Minelect	1	(YY34M)
C8	220µF 16V PC Electrolytic	1	(FF13P)
SEMICONDUCT	ORS		
IC1	OP-27GNB	1 4	(RA74R)
DI	1N4001		(QLT3Q)
MISCELLANEO	us		
Tl	Mic Transformer 600/20	1	(FD23A)
	Low-Z Mic Pre-emp PCB	1	(GD34M)
	Low-Z Mic Pre-amp Case		(FD20W)
	Veropins 2148	1 Pkt	(FL24B)
	Constructor's Guide		(XH79L)
OPTIONAL		The Day of	
	2mm Systoflex Black	As req	(BH06G)
	PP3 Battery Clip	1	(HF28F)

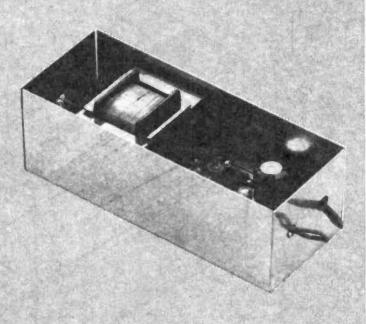

A complete kit of all parts, excluding optional items, is available for this project:

Order As LK80B (Low-Z Mic Pre-amp Kit) Price £14.95

The following items included in the above kit list are also available separately, but are not shown in the 1986 catalogue:

Low-Z Mic Pre-amp PCB Order As GD34M Price £1.80

Low-Z Mic Pre-amp Case Order As FD20W Price £1.50

Mic Transformer 600/20 Order As FD23A Price £5.95

Constructor's Guide Order As XH79L Price 25p NV

A ready-built version of this Kit is available: Order As YM14Q (Low-Z Mic Pre-amp Assem) Price £16.95

The Maplin Voyagers' Bounty is Shared

Pictured below on the right is Mr S. Grimmer of Middleton in Manchester, who is the lucky winner of the recent Maplin shop customer competition. Seen shaking hands with Keith Evans, the Manchester Shop Manager, Mr Grimmer was surprised to find that his entry had been judged as the most accurate. He was nevertheless very pleased to accept the prize voucher saying that he may use it to get an upmarket home computer, something he has been wanting for some time.

Mr Grimmer was a regular Maplin mail order customer until Maplin opened a shop in Manchester. It was on one of his recent visits, getting parts to complete the Maplin burglar alarm project, that he was able to stake his claim in the competition. The solutions to the competition questions were as follows:

- The Maplin Voyager was heading in a North Easterly direction.
- 2. There were 200 crew on board.



- 3. The treasure was found at the South Polar Zone.
- 4. Hebroth IV is 58 light years away from Earth.


Mr Grimmer was correct on the first three questions and only 2 light years out on the fourth!

Second Prize was won by Mr J.E. Cousin of Highgate in London.

The five Runners-Up, who each receive a Maplin Digital Multimeter were:

Mr S.R. Flooks of Hedge End in Southampton; Mr A. Dance of Springfield, Chelmsford in Essex; Mr C.P. Morrison of Harlesden in London; Mr K. Burford of Great Barr in Birmingham; Mr J. Houghton of Warrington in Cheshire.

MACHINE CODE PROGRAMMING WITH THE Z80

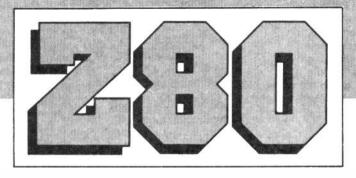

by Graham Dixey C.Eng., M.I.E.R.E. Part Four

More Jumps

The true jumps are JR and JP, discussed last time, but a number of related operations are included for convenience in the same table.

There is the CALL instruction, which is used when you want to access a subroutine. In assembly language, the operand for CALL is the label or symbolic address by which the subroutine is known. For example, a subroutine that develops a fixed time delay might be known simply by the label DELAY, and be located at an address &5CC0. In assembly language we get:

CALL DELAY which, in machine code, is CD C0 5C.

However, CALL is much more useful than just that. The CALL to the subroutine can be made unconditionally (as in the above example) or subject to one of a number of conditions (carry, noncarry, zero, non-zero, etc.) just as for the jumps JP and some JRs. This raises an obvious question. If there is so much similarity between CALL and JP, what's the real difference? It's an important question and the answer is as follows.

When a jump, whether JP or JR, is made, the contents of the program counter PC are simply replaced by the address of the destination for the jump.

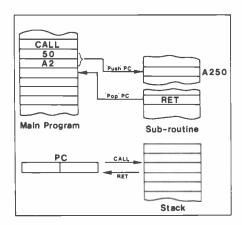


Figure 1. Use of the CALL and RET

September 1986 Maplin Magazine

The old PC contents are lost and thus there is no provision for returning from whence you came. Usually this doesn't matter otherwise jumps would be of little use. The CALL instruction, on the other hand, recognises the fact that the main program is only being left temporarily (to execute the sub-routine) and a return is intended. Thus, CALL does two things. It changes the PC contents to access the area of memory where the sub-routine resides and saves the old PC by 'pushing' it onto the 'stack'. This provides an opportunity to introduce another instruction from the set, RET (obviously short for RETURN), which must be included at the end of the sub-routine for, when it is executed, it 'pops' the old PC off the stack and the program continues from right after where it left originally when told to by the CALL instruction. Incidentally, the RET instruction is unconditional or subject to exactly the same choice of conditions as the CALL instruction. Figure 1 shows the use of CALL and RET.

There is a particularly useful instruction in this group, which has the mnemonic DJNZ (Decrement and Jump if Non-Zero). Decrement what? The answer is the B register. This register can be set up as a counter, loaded with any value from &00 to &FF that determines how many times the loop is to be executed. DJNZ is included within the loop and acts as a relative jump back to the beginning of the loop as long as B is not zero. Since, every time that DJNZ is encountered, B is automatically decremented, the program will eventually exit the loop when B becomes zero. Here's an example.

	LD	B,&0A	Load B with ten (&0A)
	LD	C,&0C	Load C with twelve (&0C)
LOOP:	LD ADD	A,&00 A,C	Set A register to zero
2001.	DJNZ		Decrement, jump
	LD	DUMP,A	Send result out

This simple program causes A to increase in value by a fixed amount (twelve) each time it goes round the loop. Thus, by going round the loop a given number of times (in this case ten), the product of these two numbers is obtained. Obviously the application is limited but it does illustrate the way in which the DJNZ instruction works.

There are just two instructions left in this set, RETI and RETN, which are both return instructions similar to RET discussed previously. However, they relate to 'return from interrupt' rather than from a sub-routine

So just what is an interrupt? In brief, it's a way of getting the computer to run a particular program and yet be able to handle peripherals, apparently at the same time. Suppose there are three peripherals, known as A, B and C, as in Figure 2. Each of these is connected via a wired-OR configuration to an 'interrupt pin' on the CPU. Each of these peripherals has a flag which is connected to an input port line on the computer. Suppose the latter is happily working away on some task and peripheral A has some data that it wants to send to the computer for processing. How can it let the computer know this? By interrupting!

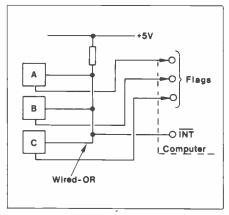


Figure 2. Three peripherals A, B and C connected to a common interrupted line.

It takes the interrupt line low and this initiates a secuence of events that includes pushing the PC (and usually other registers as well) onto the stack and going to an Interrupt Service Routine. But the computer has to decide which of the peripherals actually interrupted, which it does by testing the flags, since the peripheral that interrupted will have its flag 'high'. Then having identified the interrupting peripheral, it will go to a service routine for that peripheral. The sequence is very much like that when a sub-routine is called. But there are important differences. The manner in which it is initiated is quite different. Also the peripherals can be assigned different priorities, thus ensuring that if two or more interrupts occur at once, the most important will be serviced first. Once the service routine is complete a return must be made to the original program. This is accomplished by using the RETI instruction, which 'pops' the PC and other registers off the stack.

However, this hasn't explained what the RETN instruction does. Well, it does the same thing as RETI but for what are called 'non-maskable interrupts'. The term 'mask' is used here in the sense of inhibiting an action, i.e. preventing an interrupt from having any effect on the CPU. Does this seem a strange thing to want to do? Not at all. If there are several peripherals, one of which has interrupted and is being serviced and another, less important one, decides to interrupt also, it shouldn't be allowed to until the previous peripheral has finished. Thus a mask bit is set to prevent this. However, if there is an emergency situation, this must be given top priority, which is done by assigning it to a non-maskable interrupt. The Z80 has two separate interrupt pins. Pin 16, INT, is where the regular interrupt line is connected. Pin 17, NMI, is used for the high priority non-maskable interrupts. The rule is, use RETI for INT interrupts, and RETN for NMI interrupts.

Skew Operations

This group of operations includes the 'shift' and 'rotate' instructions. The first four rotations are RLC, RRC, RL and RR. Rotations may be made to the left or to the right, and may be 'through the carry' or 'with the branch carry'. Figure 3 shows how the operations are carried out. There is a general pattern about them so, once one is understood, the rest follow easily enough.

Taking the rotations first, RLC is a 'circular left rotation', in which all bits shift left and bit 7 goes into the carry flag CY as well as 'round the loop' into bit 0. RRC is simply a rotation in the opposite direction with bit 0 ending up in the carry flag. These rotations may be compared with the next two, RL and RR, in which the carry flag is 'in series' with the rotation. In RL, whatever is in the carry flag goes into bit 0 and bit 7 goes into the carry flag; in RR the exact reverse happens. There are four instructions RLCA, RRCA, RLA and RRA that duplicate the four just desc-

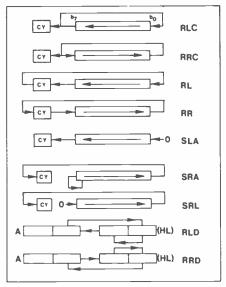


Figure 3. Effects of the 'skew' operations.

ribed but act on the A register only. They are a hangover from the 8080 from which the Z80 was developed. The Z80 instructions allow all of the registers to be operated upon as well as memory locations addressed by HL, IX or IY.

Now for the shifts. These may be to the left or the right and also involve the carry flag. However, there is no closed loop, just a series chain. For example, SLA is the Arithmetic Shift Left; all bits shift left one position, bit 7 is 'caught' by the carry flag and a zero enters bit 0.

The carry flag CY is often called a 'carry link' because it allows one register to be linked to another and data passed serially between them. For example:

LD A,&00 LD C,&0FF LD B,&08 LOOP: SLA C RL A DJNZ LOOP

This program will serially shift the contents of register C into register A with eight consecutive left shifts determined by the DJNZ instruction. However, serial shifting between registers (which includes memory locations) is not all that can be done. Every left shift multiplies a number by two, as the following sequence shows.

Original byte - 00001011 = 11 (denary)

1st shift left 00010110 = 22 2nd shift left 00101100 = 44 3rd shift left 01011000 = 88 4th shift left 10110000 = 176

At which point the carry flag must be used to link this byte to another register to avoid the m.s.b. falling off the end!

SRA is the Shift Right Arithmetic instruction, which is not a simple reversal of SLA. The difference lies in that, instead of a zero entering bit 7, the current value

of this bit remains unchanged, thus preserving the 'sign' of the number. The remaining seven bits can be transported across to another memory location, via the carry link, but using the RR instruction on the other location. Each successive shift right divides the number by two, for positive numbers only and only if no ones fall off the rightmost bit position a simple but limited means of performing binary division.

The difference between SRA and SRL is that the latter is a Logical Shift Right, and a zero enters bit 7 when shifting.

The two instructions RLD and RRD stand for Rotate Digit Left and Right respectively. They are used in Binary Coded Decimal (BCD) arithmetic, in which the digits 0-9 are encoded as four-bit binary groups (0000-1001) or 'nibbles'. They act on data in the A register and a memory location pointed to by HL. Figure 3 clearly shows the re-arrangement of nibbles that occurs for each RLD or RRD instruction, all data moving simultaneously.

Bit Manipulation Group

The instructions in this group allow bits in various registers or indirectly addressed memory locations to be tested for their value (BIT), set to logic 1 (SET) or reset to logic 0 (RES). This is done by specifying the bit number (0-T) and the register. For example:

SET 2,C

Will set bit 2 of register C to logic 1.

RES 5,A

Will reset bit 5 of the A register (to logic 0), while:

LD HL,&A200 BIT 3,(HL)

Will test bit 3 of memory location &A200 and will set the zero flag in the flags register F if the bit is found to be zero.

The ability to manipulate or test bits in registers or memory locations on an individual basis is a very useful one.

General Purpose AF Group

There are just five instructions in this group, which are concerned solely with the A register or the flags (F) register.

The first of these, Decimal Adjust A register (DAA) is used when arithmetic is to be done in BCD. The problem arises because the CPU can only work in binary and special provision must be made to compensate for errors that may arise when working in another system. As we know, BCD uses four bits to encode the denary digits 0-9, i.e. uses the groups 0000 to 1001. But what about the remaining possible groups, 1010 - 1111? These can obviously occur in binary addition and subtraction yet have no meaning in BCD - they are 'illegal' codes.

It is possible to skip over these six illegal codes by adding six to the result whenever such a code occurs. Consider the following BCD addition of 35 and 22.

+ 0011 0101 (35) - 0010 0010 (22) - 0101 0111 (57)

The answer 57 is obviously correct.

Now see what happens with the sum of 35 and 25.

+ 0011 0101 (35) - 0010 0101 (25) - 0101 1010 (5?)

The second nibble of the result is one of the illegal codes.

Now add 6 to the result and see what happens.

+ 0101 1010 0110 0000 (60)

The corrected result is now right. Fortunately we don't have to worry about when to add six or whether it should be added to the low nibble or the high one, or even both. On receipt of DAA, the CPU tests the flags and decides for itself what to do.

The DAA instruction should follow when operating in BCD with any of the following instructions, ADD, ADC, INC, SUB, SBC, DEC, NEG.

CPL is a useful single-byte instruction which complements the contents of the A register, that is swaps Is for 0s and vice-versa.

> LD A,&2C CPL

The above example means that the A register is loaded with 00101100 (2C) which, after the CPL instruction, becomes 11010011 (D3).

NEG means 'negate the A register', e.g. if the number held is a positive one, then form the two's complement of it.

&0F (+15) becomes &F1 (-15) &E2 (-30) becomes &1E (+30)

The final instructions in this group are CCF (Complement Carry Flag) and SCF (Set Carry Flag). CCF inverts the value of the carry flag, while SCF forces it to logic l.

Restarts

This group of eight instructions is a special set of sub-routine calls, whose origin addresses are &00, &08, &10, &18, &20, &28, &30 and &38. Commonly used sub-routines can be called from these addresses and require only a single-byte instruction.

For example, RST 20 calls the subroutine whose origin is at the address &0020. Somewhat confusingly these restarts are sometimes referred to by their denary values, i.e. RST 32 may be used instead of RST 20.

September 1986 Maplin Magazine

Control Instructions

The first instruction in this group is NOP, which stands for No OPeration, meaning that the CPU does precisely nothing during the time of this instruction. It can be useful, however, to insert a few NOPs into programs sometimes, so that program changes can be accommodated more easily by changing them to active instructions. They can also be put into a loop to act either as a short time wasting program, or where an interrupt is anticipated and the machine must be idle, such as in keyboard input routines, thus:

WAIT: NOP JR WAIT

The CPU obediently cycles back and forth between the two lines until the interrupt breaks into the loop. HALT could be used instead, since this will stop the operation of the CPU until either an interrupt is received or the reset pin (pin 26) is taken low. The remaining five instructions are all concerned with interrupts and work as follows:

DI and EI stand for 'Disable Interrupts' and 'Enable Interrupts' respectively. Earlier it was said that various interrupts can have different priorities. Thus, if a high priority interrupt wishes to ensure that it cannot be over-ridden by one of lower priority, the first thing it does when it goes into its Interrupt Service Routine is to disable further interrupts with the DI instruction. Then, when it has completed its routine it will issue the EI instruction to allow further interrupts to be acknowledged by the CPU. The last three instructions are concerned with the interrupt modes of the Z80 and require more detailed discussion.

IM0 sets mode 0. This can be referred to as the 8080 mode, since it is compatible with the older 8080 CPU. In this mode, when an interrupt is received, the PC is pushed onto the stack and the Z80 passes control of the data bus to the interrupting peripheral. The latter responds by placing an instruction on the data bus, which is usually a sub-routine call to execute the service routine for that particular peripheral. One of the restart instructions may be used for this.

IM1 sets mode 1, which is the 'polled response mode'. When an interrupt is received the CPU calls a sub-routine located at the restart address &0038. This will then poll the various peripherals to ascertain which one interrupted and then will service that peripheral.

IM2 is the most powerful of the Z80 interrupt modes. It uses a register, the I or Interrupt Vector register, which has to be loaded with the high byte of the interrupt vector. The low byte is supplied by the interrupting device itself. This complete vector then points to two consecutive locations

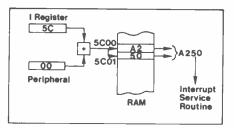


Figure 4. The Z80 Mode 2 interrupts.

that give the start address for the service routine. This is not as complex as it may sound and is illustrated in Figure 4.

The Input-Output Group

And so to the final set of instructions for the Z80, those that deal with the transfer of data between the CPU and the outside world through interface chips such as the Z80 PIO.

Unlike the 6502, the input/output ports on a Z80 system are not memory-mapped, i.e. they do not have memory addresses on the main memory map of the computer. Instead they are identified by 'port addresses', which are usually in the range &00 – &FF (which allows for 256 separate ports). In theory it is possible to have 65536 individual ports – the mind boggles! This is done by combining the number held in the A register (the high byte) with the operand of the instruction (the low byte) to give an address range for the ports from &0000 – &FFFF.

To fetch data from a port, the IN instruction is used together with the destination register and the port address, thus:

IN A, &02

Will fetch the data at port &02 and place it in the A register.

Data is sent to the port by using the OUT instruction, the port address and the destination register, so that:

OUT &02, A

Will send the contents of the A register to port &02. The other general purpose registers can also be the subject of IN and OUT instructions, but by means of register indirect addressing, using the C register. Thus, to send data from the D register to port &02 and then input data from port &03 into the E register, the following program could be used.

LD C, &02 OUT (C), D INC C IN E, (C)

There is also a range of block transfers for IN and OUT, that work in essentially the same way as the block transfers described in Part Three. INI is used to fetch data from a port and load it into a block of sequential memory locations and vice-versa for OUTI. In both cases the I stands for Increment. If, instead, the instruction INIR or OUTIR is

issued the process of transferring data and incrementing to the next address is done automatically until the whole block has been transferred. In this type of transfer HL is first loaded with the start address of the block, B with the number of bytes to be transferred and C with the port address. Consider the following program:

LD HL, &A200 LD B, &32 LD C, &02

This will load the block of memory

&A200 - &A231 with the fifty bytes of data, specified by the B register, from port &02.

If INI is used instead of INIR only one byte is transferred, but HL is incremented and B decremented ready for the next INI.

In both cases the transfer is complete when B=0 though, in the case of INI, this must be ascertained by testing the Z flag after each transfer to see if it now equals 1.

Analogous to INI, INIR, OUTI and OTIR are IND, INDR, OUTD and OTDR. The D. of course, stands for Decrement and refers to the fact that at each transfer HL is 'decremented' instead of being incremented. As a result, HL initially holds the 'top' address of the memory block, which is then loaded 'downwards'.

Some of the descriptions may have been fairly brief, but all of the Z80 instructions have now been discussed. This means that future articles can deal entirely with the writing of a variety of programs in Z80 code, on the assumption that all mnemonics may now have some meaning, even if it does sometimes mean a quick look back to earlier issues.

TEST GEAR & MEASUREMENTS Continued from page 53.

Equation 14.

$$Rx = \frac{R_2R_3}{R_1}$$

Equating imaginary terms:

Equation 15.

$$Lx = C_1R_2R_3$$

Since R_3 is common to both Equations 14 and 15, adjustment of R_3 to balance the inductor, upsets the resistive balance. Using R_1 and R_3 in turn results in successive balance points such that convergence is obtained towards final balance.

The other bogey man of bridge circuits is stray capacitance between bridge arms. Up to now we have assumed that the arms of the bridge contain lumped impedances. In practice, stray capacitance couples the various arms and upsets the balance giving a false reading.

One way out of this is the Wagner ground where all the arms are shielded and the screens connected to ground. This does not get rid of the capacitances but does make them constant in value enabling them to be included in the calculation.

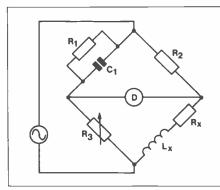


Figure 12. Maxwell Bridge.

Wien Bridge

This is a very useful bridge for measuring frequency, Figure 13. One of the drawbacks is that it requires a pure sinusoid, and any harmonics tend to upset the balance.

The Wien bridge is versatile and has been used in modified forms in oscillator circuits as well as notch filters in frequency analysers for extracting a particular frequency.

$$Z_{3} = \frac{R_{3}}{jwC_{3}R_{3} + 1}$$

$$Z_{2} = R_{2}$$

$$Z_{4} = R_{4}$$

$$Z_{1} = R_{1} + \frac{1}{jwC_{1}}$$

Substituting in $Z_1Z_4 = Z_2Z_3$

$$\begin{pmatrix} R_1 + \frac{1}{jwC_1} \end{pmatrix} R_4 = R_2 \left(\frac{R_3}{jwC_3R_3 + 1} \right)$$

$$R_1R_4 + \frac{R_4}{jwC_1} = \frac{R_2R_3}{jwC_3R_3 + 1}$$

$$R_1R_4(jwC_3R_3 + 1) + \frac{R_4}{jwC_1} (jwC_3R_3 + 1)$$

$$= R_2R_3$$

$$jwC_3R_3R_1R_4 + R_1R_4 + \frac{R_4}{jwC_1} + \frac{R_4R_3C_3}{C_1}$$

= R_2R_3

Equating imaginary terms:

$$w^{2}C_{3}C_{1}R_{1}R_{3}R_{4} = R_{4}$$

$$w^{2}C_{3}C_{1}R_{1}R_{3} = 1$$

$$w^{2} = \frac{1}{C_{2}C_{1}R_{1}R_{2}}$$

if
$$C_1 = C_3$$
 and $R_1 = R_3$

then
$$w^2 = \frac{1}{C^2R^2}$$

 $w = \frac{1}{CR}$

Equation 16.

$$f = \frac{1}{2\pi CR}$$

Equating real terms:

$$\begin{aligned} R_1 R_4 + \frac{R_4 R_3 C_3}{C_1} &= R_2 R_3 \\ \frac{R_1 R_4}{R_3} &+ \frac{R_4 C_3}{C_1} &= R_2 \\ \frac{R_1}{R_3} &+ \frac{C_3}{C_1} &= \frac{R_2}{R_4} \end{aligned}$$
 As before, if $C_1 = C_3$ and $C_1 = C_3$

Equation 17.

then
$$\frac{R_2}{R_4} = 2$$

This means that if R_2 is twice the value of R_4 , then R_1 and R_3 can be ganged together and altered in equal steps to achieve balance. Therefore only one control is sufficient, and can be calibrated in frequency according to Equation 16.

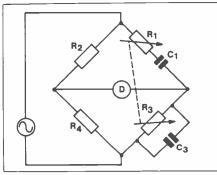


Figure 13. Wien Bridge.

A Universal Bridge

A portable impedance measuring instrument complete with handle and lid is standard in most development laboratories. In order to measure resistance, inductance and capacitance, such an instrument needs d.c. and a.c. power supplies as well as d.c. and a.c. detectors.

For a d.c. power supply, battery packs are used, and a.c. is supplied from an oscillator via RC networks to select the frequency. A frequency of 10kHz is the usual standard.

A suspension galvanometer with a sensitivity of $0.5\mu\mathrm{A}$ per division is used as a d.c. detector in resistance measurements. An electron ray tube (magic eye) is used as an a.c. detector. There is usually an external facility for connecting headphones, as well as an a.c. mains power supply input.

Now to the actual measurements themselves. What is the minimum number of bridges we can get away with? For inductance measurements, both the Hay and Maxwell bridges are required for Q above ten and less than ten respectively. For resistance measurements a Wheatstone bridge is adequate and a bank of standard capacitors is required for capacitance measurements. So about half a dozen different bridges will serve most requirements.

New Books

Getting the Most from Your Printer

by J.W. Penfold

It is probable that a large majority of dot-matrix printer owners only ever use a fraction of the possible features offered by their machines. Often this is because the manual supplied tends to be a bit on the technical side and lacking in really helpful explanations of the printer's capabilities.

This book has been written for dotmatrix printers commonly in use with most popular home computers including the BBC and Acorn Electron, Amstrad, Sinclair Spectrum and QL, Commodore, Memotech, MSX and Enterprise. It will help the user to realise more of the afore-mentioned capabilities of his dot-matrix by illustrating exactly how to achieve given effects in word processing, using printed listings as an aid to program design (it is said by many users who virtually a programmable orchestra. The major part of this book provides details of how to interface most of the popular home computers with MIDI systems, including all circuit diagrams with operational detail, plus examples of programming used to drive the interface. Machines catered for include the Amstrad CPC464 and 6128, CBM 64 and VIC-20, BBC Model B, MTX and MSX computers, and the Sinclair QL, Spectum and ZX81.

The book also includes examples of interfacing MIDI equipment to analogue and percussion synthesisers. 178 x 112mm, 103 pages, illustrated. Order As WP49D (MIDI Projects)

Price £2.95 NV

Introduction to Electronics

by Pam Beasant

This book is an introduction to the basic principles of electronics, and

ponent works. This ranges from the very basic using light bulbs and batteries, through an introduction to transistors, choice and use of tools and how to solder, to circuit assembly on veroboard. A potted history of the science is also included. A must for anyone totally unfamiliar with real electronic components, and a useful supplement to the text books.


240 x 170mm, 48 pages, illustrated in colour.

Order As WP50E (Intro Elec)
Price £2.25 NV

Audio Projects and Circuits

by Graham Bishop

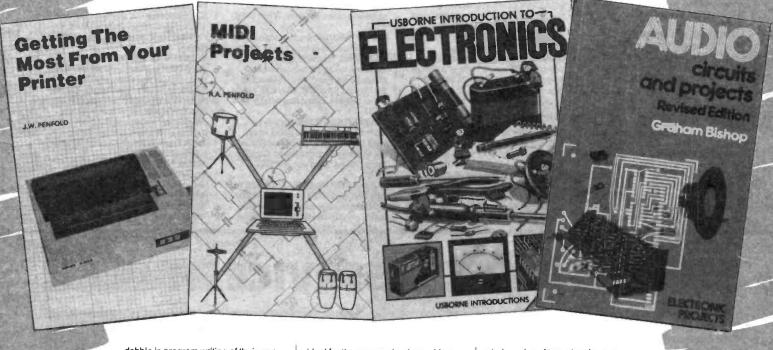No matter how sophisticated your audio system, there are circuits here that will improve it – if not in sound quality, then in convenience. There are projects to cater for the musician too. A



dabble in program writing of their own that they wouldn't like to think about how they would have managed in the days before the printer was eventually added into the system), as a peripheral used by the user's own programs, and how to print graphics effectively.

178 x 112mm, 88 pages, illustrated.

Order As WP48C (Get Most from Your Printer)

Price £2.95 NV

MIDI Projects

by R.A. Penfold

MIDI interfacing enables any so equipped instruments, regardless of manufacturer, to be easily interconnected and used as a complete, sophisticated system. The MIDI interface also permits easy computer control of such a system, and a few MIDI compatible instruments together with a suitable computer and interface can provide the user with what is

September 1986 Maplin Magazine

ideal for the younger beginner. Many introductory text books deal mainly with the electronic theory alone, with little, if any, really useful, down to earth practical illustration of how a soldering iron should be used. For the new amateur enthusiast as well as for the professional student, the gulf between the calculations and diagrams on paper, and assembling (and making work!) the real hardware itself is always a shock. Here a host of hitherto unforeseen problems, sometimes of a more 'mechanical' nature, lie in wait. Electricity is ever fickle, and at the outset the book states its purpose to show how this energy must be controlled.

The bulk of the book comprises many simple, practical experiments copiously illustrated in full colour. Each experiment is designed to illustrate an important principle of electronics and demonstrate how each different com-

whole series of tested projects, easy and inexpensive to build, are shown together with full constructional details. The first part of the book includes projects for audio amplifiers, preamplifiers and signal correction/processing, with designs ranging from single transistor circuits to a 100W power amp design. The second part covers musical instruments such as synthesisers, rhythm generators and organs, including effects devices such as sound to light modulation and other 'fun circuits'.

All the projects can be built onto veroboard, and components lists and relevant semiconductor information is included. Even if you do not wish to build all or any of the designs as they are, the book certainly contains many thought provoking ideas.

215 x 138mm, 194 pages, illustrated.

Order As WP51F (Audio Ccts & Proj.)

Price £6.95 NV

CLASSIFIED

VARIOUS FOR SALE

PAPER TAPE PUNCH mechanism (Creed) £2.50. Reader mechanism 75p. New paper tapes 50p. Audiovisual post in slot cassette unit with amplifier £3. Coin operated telemeter unit £3. 0689 68868.

ONE VALVE TUNER AMP. Valves seem OK but unit doesn't work. £8. Buyer collects. Phone Graham on Edenbridge (Kent) (0732) 862089. HEATHKIT SW717 SW radio £48. VDU cabinet with keyboard and VDU pcb (will hold computer pcb) £48. Maplin M-8060E electronic multimeter £25. Maplin Wordmaker speech synthesiser incl. PSU £50. AY-3-891 Sound Generator on pcb £6. Vero 17 inch racking cabinet with PSU £48. Computer speech recognition system £25. Watford Drum Rythm generator £35. Tel: Lowestoft (0502) 66026. RTTY MAPLIN TU1000 built and

MTTY MAPLIN TU1000 built and working, tested by Maplin, see page 228 of 1986 catalogue for photo.

Complete with case, cost to build £57, yours for £48 post free! 061 231 3028.

THERMAL COPIER £10. Oscilloscopes; Solartron CT316 £30, Tektronix \$48A (but with EHT fault) £78. Mufax D649GA facsimile receiver plus manuals, £78. Roneotronic 400T stencil cutter £90. Ditto, requiring transformer, £40 plus carriage. Porthtowan (0209) 890688.

MAPLIN XENON FLASE TUBE DRIVER built and tested, no case, £14.80 (P+P included). Callwrite to M. Dutta, 178 Bramhall Moor Lane, Hazel-Grove, Stockport, Cheshire SK7 8BE. Tel: 061 483 8659.

COMPUTERS

COLOUR GENIE 32K. Dust cover, dual joysticks and keypads, cassette recorder, LC24 data stabiliser, leads, filing box, £250 worth of software, 11 Genie magazines. In original boxes – £115 ono. Tel: A. Fowler (063783) 2100. BURNDEPT CYFAS \$885 controller pcb fully populated. 2K RAM, 4K ROM, blown monitor ROM, UART, parallel port, diagrams. Unused, still in anti

If you would like to place an advertisement in this section, here's your chance to tell Maplin's 200,000 customers what you want to buy or sell, or tell them about your club's activities – absolutely free of charge. We will publish as many advertisements as we have space for. To give a fair share of the limited space, we will print 30 words free of charge. Thereafter the charge is 10p per word. Please note that only private individuals will be permitted to advertise. Commercial or trade advertising is

strictly prohibited in the Maplin Magazine.

Please print all advertisements in bold capital letters. Box numbers are available at £1.50 each. Please send replies to Box Numbers to the address below. Please send your advertisement with any payment necessary to: Classifieds, Maplin Mag., P.O. Box 3, Rayleigh, Essex SSS ST.D.

For the next issue your advertisement must be in our hands by 6th October 1986.

static bag. Any offers 0252 542703 after 6pm.

COLOUR MONITOR. Rediffusion system Alpha. RGB and composite video inputs. Built-in audio amp/speaker.

New April '96. Sell £180 or swap portable colour TV. Tel: '021 706 3883.

MAPLIN 300 BAUD MODEM cased, tested, reliable. Including cables, disk and ROM software for BBC micro. £80.

D.R. Boyd, Treuddyn Mill, Mold, Clwyd, CHY ABD.

VIC20 CARTRIDGE AREA
MEMORY EXPANSION KIT for
machine code use, etc. Includes board
and instructions. Just add 2K RAM or
2-4K PROM. Only £4.95 from J. Seddom,
63 Portland Road, Birmingham.
HERO 1 ROBOT with voice recognition and 48K memory. Lots of software.
Bargain at £2000 o.v.n.o. 01-240-0668
day.

CLUBS

EI-FI CLUB OF CAPETOWN South
Africa issues monthly newsletter for
members Worldwide. Join S. Africa's
Audio Chub for 2 LR.C.'s to P.O. Box
18262, Wynberg 7824, South Africa.
MECHANICAL LOW DEFINITION
TELEVISION revived 1976, offers
interesting inexpensive hobby. Narrow
Bandwidth Television Association (sub-

scription £3.00) provides quarterly newsletters and technical help. Write:— Doug Pitt, 1 Burnwood Drive, Wollaton, Nottingham.

MUSICAL

YAMAEA CS01 and Boss DR55, both in mint condition and fully working. Boss DR55 fitted with separate outputs. Offers! Tel: Dave on Southampton (0703) 433871.

ENSONIQ MIRAGE owner seeks other users in the Southend area, to exchange ideas, samples – Tony (0702)

MES 53 ORGAN plus auto organ, 2 x 49 note keyboards, reverb, Leelie rotator, pedalboard, twin 80W amps & speakers in home made mahogany effect cabinet, circuits with construction details. Cost £700, take £250 o.n.o. Buyer collects. Phone Canterbury 67021

MAPLIN PIANO plus amplifier.
Professionally built. Polished wood
case. Brilliant tone. Offers over £100.
Mr. Stanley, 9 Princes Street, Connahs
Quay, Clwyd. Tel: Deeside (0244)

MAPLIN 600 NOTE SEQUENCER use with 3800 and 5600S synthesisers. All pcb's made, case and hardware £50. Instructions included. Mike, 24 Sutherland Ave, Sunbury-on-Thames, Middle-

MAPLIN HARMONY GENERATOR built, cased and fully tested, never used after testing, £20. Maplin Computadrum pcb, built and fully tested, excellent condition (no case) £12.80 (P+P inchded). Call/write to M. Dutta, 178 Bramhall Moor Lane, Hazel-Grove, Stockport, Cheshire SK7 5BE. Tel: 061 483 5659.

WANTED

COULD SOMEONE SELL DT Scope, working or not, to person of limited means. Contact Mr. Matthews, 63, The Oval, Otley, West Yorkshire, LS21 2EE. WANTED TELETERT DECODER in kit, pcb or ready built form. Write with details to J. Heywood, 19 Molyneux Road, Maghull, Liverpool L31 3DX. YAMAHA CS70M data cards wanted, any number, preset or blank - if you have any please 'phone Dave on Southampton (0703) 433871. WANTED BY PENSIONER Maplin organ 51, leaflets, MES53, XH04E, and MESS4, XH31J. Willing to buy. Scott, 'Lilden', Lydfords Lane, Gillingham,

WANTED CIRCUIT DIAGRAM or any information on the Hartley Electromotives Ltd. Oscilloscope type 13A Ref No. 105/831. N. Bradbrook, 38 Orchard Park, Laugharne, Carmarthen, Wales.

WANTED HANDBOOK FOR AIRMEC Oscillator type 888. Price etc to Rodley, 19 Warwicks bench, Guildford, Surrey. Tel: Guildford 38796. WANTED INSTRUCTION MANUAL for D62 Telequipment 'scope, or any relevant information at all. Contact Paul Topping, 100 Longhill Road, Ovingdean, Brighton BN2 7BD, or tel: Brighton (0273) 31817.

WANTED 2716/M3 ROM for 5600 sequencer, or complete unit working or not, with ROM. Also any data book etc. on M108 organ. L.C. Millhouse, 7 Bentinck St, Mansfield. Tel: 0623 688234

MAPLIN SERVICE

With most electronic projects, performance will depend on the conditions of use. Recommendations and suggestions made in the articles in this magazine are for guidance only, since conditions of use are beyond our control.

Repairs and Get-You-Working Service

Our 'Get-You-Working Service' is available for any of the projects published in this magazine, provided they are constructed on our ready-etched printed circuit boards, and that they use a majority of components supplied by us. We regret we cannot extend this service to the 'interest' circuits, for which we do not provide ready-made boards, or supply as projects or kits; nor for projects or kits that have been customised or modified by the constructor.

We cannot enter into correspondence with regards to fault-finding, and recommend you return the unit to us for servicing if you are unable to rectify the fault yourself.

Project Servicing

If the problem has been caused by a faulty component supplied by us, then there will be no charge for the work performed or the components used. If the fault has been caused by error(s) in



construction, then there will be a charge for the work performed at a rate of £10 per hour, or part of an hour plus the cost of any damaged components which need to be replaced. If no fault is found on the unit, then there will still be a charge of £10 per hour or part of an hour for the time involved in establishing this fact.

Projects returned for repair should be addressed to:-Service Department Maplin Electronic Supplies Ltd

P.O. Box 3 Rayleigh Essex SS6 8LB

DID YOU MISS THESE ISSUES?



Project Book 1 Universal Timer. Programmable mains controller. Combo-Amplifier. 120W MOSFET power amp. Temperature Gauge. 10°C - 100°C, LED readout. Pass The Bomb! Pass-The-Parcel with a difference. Six easy-to-build Projects on Vero-board. Car batt. monitor; Colour snap game; CMOS Logic Probe; Peak Level meter; Games timer; Multi-colour pendant. Order As XA01B (Maplin Project Book No. 1) Price 75p NV.

Project Book 2 Digital Multi-Train Controller. Controls up to 14 model trains. Home Security System. Six in-dependant channels. Digital MPG Meter. With large LED display, a must for more economical motoring.

Order As XA02C (Maplin Project Book No. 2) Price 75p NV.

Project Book 3 ZX81 Keyboard. 43 keys, plugs directly into ZX81 with no soldering. Stereo 25W MOSFET Amp. 25W r.m.s per channel; Disc, Tape, Tuner & Aux. Radar Intruder detector. 20 metres range, may be used with our security system. Remote Control for Train Controller. Remote control by infra-red, radio or wire. Order As XA03D (Maplin Project Book No. 3) Price 75p NV.

Project Book 4 Telephone Exchange. Up to 32 extensions on 2-wire lines. Remote Control for Amplifier. Volume, balance and tone controlled via infra-red link. Frequency Counter. 8 digit DFM, 10Hz - 600MHz range. Ultrasonic Intruder Detector. Areas up to 400 square feet can be covered.

Order As XA04E (Maplin Project Book No. 4) Price 75p NV.

Project Book 5 Modem. 300 baud transmission speed over normal telephone lines. Inverter. 240V AC 60W from 12V car battery. ZX81 Sound Generator. 3 tone generators fully controlled from BASIC. Central Heating Controller. Optimised performance with this advanced system. External Horn Timer. Exterior intruder alarm. Panic Button. Add on to our Home Security System. Model Train Projects. Add on to our Multi-Train Controller. Interfacing Micro processors. How to use parallel I/O ports, with circuits

Order As XA05F (Maplin Project Book No. 5) Price 75p NV.

Project Book 6 VIC20 & ZX81 Talkbacks.
Speech synthesis projects. Scratch Filter.
Tunable active circuit 'reclaims' scratched
records. Bridging Module. Converts two 75W
MOSFET amps to one 400W full bridge amplifier.
Moisture Meter. Finds damp in walls and floors.
ZX81 TV Sound and Normal/Inverse Video. TV
sound and inverse video direct. Four Simple
Veroboard Projects. Portable Stereo Amp; Sine
Generator; Headphone Enhancer and Stylus
Organ.

Order As XA06G (Maplin Project Book No. 6) Price 75p NV.

Project Book 7 CMOS Crystal Calibrator.
For amateur radio receiver calibration. DX'er's
Audio Processor. Improved sound from Communications Receivers. Enlarger Timer.
An accurate timer for the darkroom. Sweep
Oscillator. Displays AF frequency response on an oscilloscope screen. VIC20 and ZX81 Interfaces.

RS232 compatable.

Order As XA07H (Maplin Project Book No. 7) Price 75p NV.

Project Book 8 Spectrum Modem/RS232 Interface. 2400 baud self contained operating system. Synchime. Simulates bells, gongs and other chiming sounds. Dragon 32 RS232/Modem Interface. Plugs into ROM expansion port. Codelock. Programmable electronic lock. CMOS Logic Probe. Digital display shows logic states. Minilab Power Supply. Versatile unit for the test bench. Dragon 32 I/O Ports. Two 8-bit ports. Doorbell for The Deaf. Flashing lamp attracts attention.

Order As XA08J (Maplin Project Book No. 8) Price 75p NV.

Project Book 9 Spectrum Keyboard. 47 full travel keys. VIC Extendiboard. Three expansion ports, one switchable. Oric Talkback. Speech synthesiser for the Oric 1. TDA7000 FM Radio. Complete FM receiver on a chip. ZX81 High Resolution Graphics. 256 x 192 fine pixel display. Nine Projects! Personal Stereo Dynamic Noise Limiter; Logic Pulser; TTL/RS232 Converter; Pseudo Stereo AM Radio; and more. Order As XA09K (Maplin Project Book No. 9) Price 750 NV.

Project Book 10 Spectrum Easyload. Helps cassette loading with the Spectrum. 80m Receiver. Simple SSB direct conversion receiver. Fluorescent Tube Driver. 8W 12V for camping and caravanning. Auto-Waa. Automatic waa-waa effects unit. Digi-Tel Expansion. Expands Maplin Telephone Exchange to 32 extensions. Oric 1 Modem Interface. Adapts the Oric 1 to the Maplin Modem. Dragon 32 Extendiport. Makes the Dragon's cartridge socket more accessible. Order As XA10L (Maplin Project Book No. 10) Price 75p NV.

Project Book 11 Mapmix. Six channel audio mixer. Xenon Tube Driver. Xenon flash tube module with strobe. Enlarger Exposure Meter. Simple inexpensive tool for the darkroom. 8 Channel Fluid Detector. Check/control fluid level in up to 8 containers. Servo & Driver Module. Servo mechanism with driver module kit. Mk II Noise Reduction Unit. Improves signal/noise ratio of tape recordings. Cautious Ni-Cad Charger. Controlled charging of ni-cad cells. Motherboard for The BBC Micro. Gives easy access to ports.

Order As XA11M (Maplin Project Book No. 11)
Price 75p NV.

Project Book 12 RTTY Unit. The TU1000 receives/transmits Radio Teletype; connects to computer via RS232. Computadrum. Use your computer as a drum synthesiser. Light Pen. Draw onto the TV screen or select menu options. PWM Motor Drive. Reversible model motor driver for 6V and 12V.

Order As XA12N (Maplin Project Book No. 12) Price 75p NV.

Project Book 13 Explosive Gas Alarm.
Flammable gas detector. Flash Meter. Get your exposure right when using your flash gun.
Musical Announcer. A doorbell with a difference.
Mains Controller. An add-on for the 8-Channel Fluid detector.

Order As XA13P (Maplin Project Book No. 13)

Price 75p NV.

Project Book 14 Live Wire Detector.
Invaluable aid for the handyman. Trundle. The
line follower robot as featured on Channel 4. 4Channel PWM Controller. Digital control of
motors and servos. Display Driver Module. How
to use our LED bargraph display ICs. Control-ATrain. Full inertia control of model trains.
Spectrum I/O Controller. Buffered 2-way 8-bit
data bus and 8 control lines.

Order As XA14Q (Maplin Project Book No. 14) Price 75p NV.

Project Book 15 Z80 CPU Module.
Expandable CPU based controller. Sharp MZ-80K
Serial Interface. Get into communications with
this project. Ultrasonic Car Alarm. Stop car
thieves. Active Crossover. Includes matched
output power amplifiers. Guitar Equaliser.
Specifically for six string electric guitatrs.
Fabulous Five. A selection of interesting circuits.
Order As XA15R (Maplin Project Book No. 15)
Price 75p NV.

Project Book 16 Floodlight Controller. Both power supply and mains switching unit for the Infra-red Intruder Detector Kit. Spectrum Parallel/Serial Interface. Provides 8-bit I/P and O/P parallel or serial transfer with programmable UART. Mains Tx/Rx Data Communications System. Sends or receives data via the mains wiring. 16-Channel Logic IC Tester. Simultaneously displays logic states for any logic IC of up to 16 pin-outs on your oscilloscope. Order As XA16S (Maplin Project Book No. 16) Price 75p NV.

Electronics Issue 17 Video Digitiser. Interface a TV camera to your computer. Mixing It. A comprehensive range of audio amplifier modules. Hobbyist's Temperature Controller. General purpose electronic mains power thermostat. ASCII Keyboard. Professional computer keyboard with standard ASCII output. Play Along Mixer. Play along to your favourite records and tapes on your own instrument.

Order As XA17T (Maplin Magazine Volume 5 Issue 17) Price 75p NV.

Electronics Issue 18 Weather Satellite
Receiver. Display regional weather systems on
your TV or monitor. Mixing It Part 2. Mono/stereo
Hi–Z mic input, mixer and line amplifiers;
VU/headphone driver. Stepper Motor Driver.
How to build and start using the Stepper Motor
Kit featured in the Catalogue. Amstrad Expansion
System. The Maplin Amstrad External ROM Card
System for the CPC 464, CPC 664 and 6128.
Sealed Lead Acid Battery Charger. Special high
stability output with automatic trickle charge
mode for sealed lead acid batteries. Fantastic
Five. Veroboard projects comprising HF tremelo
unit, crystal checker, clap switch, low–Z
ohmmeter, snooze timer.

Order As XA18U (Maplin Magazine Volume 5 Issue 18) Price 75p NV.

Electronics Issue 19 Active Aerial and Aerial Tuning Unit. get more from SW. Amstrad Expansion System. 6 x 8-bit parallel I/O card and PSU. ADA Digital Echo. RAM based low cost echo machine. Mixing It. Mixer Modules' PSU. Order As XA19U (Maplin Magazine Volume 5 Issue 19) Price 75p NV.



MODEL 5010EC

A versatile digital multimeter with a 0.5in. 31/2 digit LCD display and a host of useful additional facilities.

- Continuity buzzer.
- Conductance measurement.
- Diode testing capability h_{FE} transistor tester.
- Digital thermometer probe.
- Capacitance tester.
- Capacitance range 1pF to 20µF
- DC volts up to 1,000V.
- AC volts up to 750V
- DC AC current to 10A. Resistance 100m() to 20M() and 2.8V or 500mV drop across probes.
 - Fully overload protected.

Order As YJ79L Price £64.95



A fully auto-ranging digital multimeter with 0.5in. high 31/2 digit LCD display. Includes low battery, overange, polarity, auto mode and range ■ 10MΩ-100MΩ input impedance. selected indicators.

- Range hold mode available. Memorise lead resistance.
- DC volts up to 1,000V.
- AC volts up to 750V.
- DC/AC current to 10A.
- Resistance $100 \text{m}\Omega$ to $2 \text{M}\Omega$.
- Continuity buzzer. Supplied with battery, safety test leads and operating instructions.

Order As YJ80B Price £39.95





MODEL M105 LOW COST DIGITAL

Compact easy to use digital multimeter at an affordable price. Full overload protection.

- 31/2 digit LCD display.
- Basic accuracy 0.5% Screened against RFI.
- 10M() input impedance.
- DC volts up to 1,000V, AC to 750V
- DC current to 2A FSD.

MAPLIN ELECTRONIC SUPPLIES LTD. P.O. Box 3, Rayleigh, Essex SS6 8LR.
Tel: (0702) Sales: 554161; Enq: 552911.

Access, Barclaycard, Amex, Mapcard - phone before 2.00 p.m. for same-day des

Or call in at one of our shops: or can mar one or our snops: Birmingham, London, Manchester, Southampton, and Southend-on-Sea.

- Resistance 111 to 2M1. 2.8V maximum drop across probes
- all resistance ranges. One handed operation
- Supplied with battery, safety test leads and operating instructions.

Order As YJ77J Price £26.95

Maplin Gold



MODEL M6000 PUSH BUTTON DIGITAL

Push button operated digital multimeter with 0.5in high 31/2 digit LCD display which includes low battery and overload indicators. Battery life and overload indicators, battery life can be as much as 2,000 hours using an alkaline PP3.

- Fully overload protected
- 10MΩ input impedance.
- Ohe handed operation.
- DC volts up to 1,000V
- AC volts up to 200V. DC and AC current to 20A.
- Resistance 100mg to 20Mg. Switchable 3V or 0.6V maximum drop across probes all resistance
 - Diode test capability

 - Supplied with battery, safety test Bench tilt stand. leads and operating instructions. Order As YJ78K Price £39.95



HOBBY MULTIMETER

A rugged, easy to use general purpose instrument offering 10,000 V DC and 4000 V AC.

- DCIAC volts up to 1,000V. DC current up to 500mA.
- Resistance 212 to 10M1.
- Decibels 20dB to 62dB.
- Overload protection. Supplied with battery, test leads and operating instructions. Order As YJ76H Price £8.95

All prices are valid until 8th November 86 and inc. VAT

Also available in the Maplin Precision Gold range

Y J06G General purpose pocket analogue multimeter £6.95 YJ07H Wide range analogue multimeter M-102BZ with continuity buzzer and battery YJ08J Professional analogue

multimeter M-2020S with transistor, diode and LED tester £19.95

YJ09K Professional quality FET input electronic analogue multi-meter M-5050E £34.95 YJ10L M-5010 high performance digital LCD multimeter, ranges start at 2011, 20 µA or 100 MV AC DC FSD. 10Ms1 input impedance £41.95