

# MODERN WIRELESS



June.

1/-

Vol. III. No. 1.

Edited by JOHN SCOTT-TAGGART, F.Inst.P., A.M.I.E.E.

June, 1924.



J. L. KARSAY

Vol. III.

# No. 1

**AN ST100 SET WITH TWO H.F. VALVES.**


**HOW TO BUILD A TWO-VALVE HIGH-TENSIONLESS RECEIVER.**

**A FIVE-VALVE LONG-DISTANCE RECEIVER.** *By Percy W. Harris.*

**HIGH-TENSIONLESS CIRCUITS EXPLAINED.** *By John Scott-Taggart, F.Inst.P., A.M.I.E.E.*

**UNUSUAL FAULTS.** *By G. P. Kendall, B.Sc.*

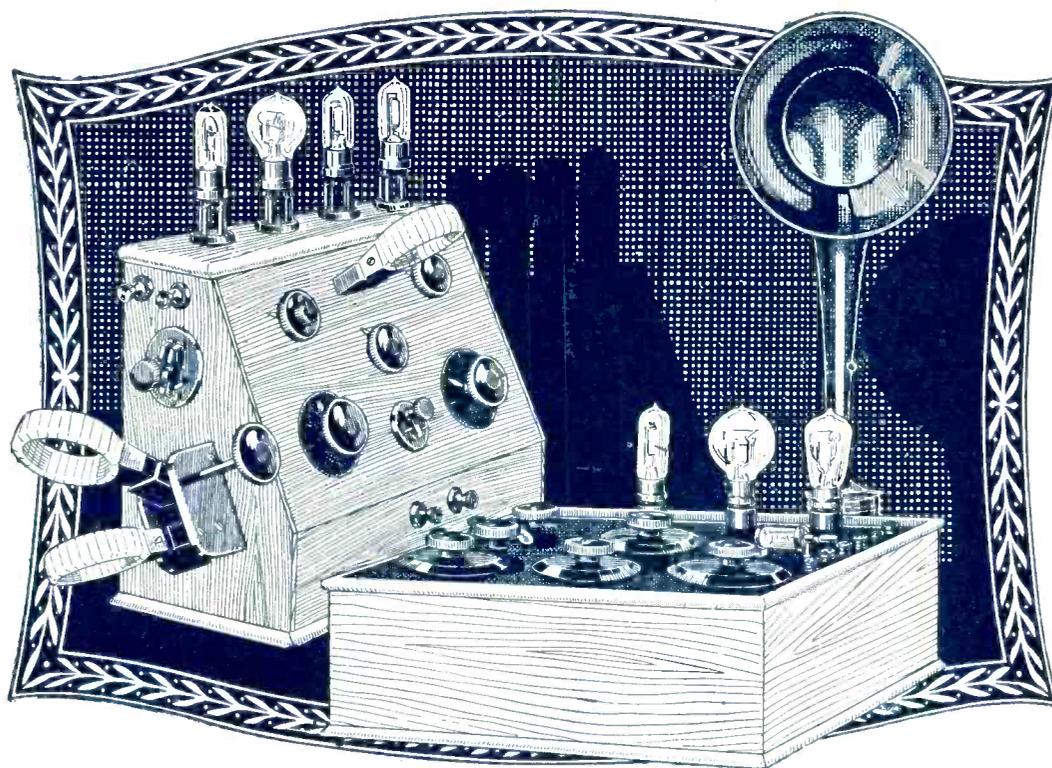**How to Build: A New Crystal Set—A Single-valve Set—A Two-Valve Set.**



No previous Radio experience needed.

EVERY Receiving Set described in this Book has been actually built by the Author and its performance thoroughly tested under various conditions.

The result is that any man wishing to make up a Set can read through the Book, study his local conditions, gauge his anticipated expenditure and make his choice. And when he gets down to the actual building he will find every item fully described just as if he were working side-by-side with the Author himself.

In addition, the Book also furnishes a complete

course on set building—commencing with simple, inexpensive, yet thoroughly efficient, Crystal Sets and progressing to more ambitious multi-valve Receivers capable of spanning the Atlantic.


No matter how great or how little your Radio experience may be there is certain to be a Receiving Set described which will fit your pocket and provide you with many hours of satisfaction and pleasure. Any Bookseller will supply "Wireless Sets for Home Constructors" or it can be obtained direct from the Publishers (postage 2d. extra).

**SHOWS HOW TO BUILD:**

- Simple Crystal Receivers.
- An inductively-coupled Crystal Set.
- A two-valve Low frequency Amplifier.
- A two-valve Broadcast Receiver.
- A three-valve Regenerative Receiver.
- A single-valve Reflex Receiver.
- A three-valve Broadcast Receiver.
- A four-valve Universal Receiver.

Together with information as to the testing and operation of Receiving Sets.

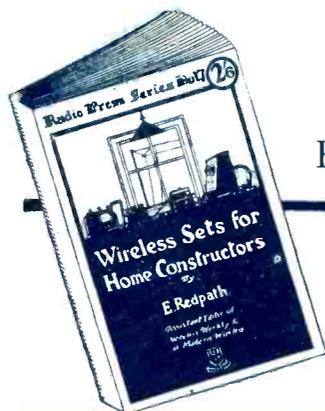RADIO PRESS LTD., DEVEREUX CT., STRAND, W.C. 2



**Wireless Sets for Home Constructors**  
By E. Redpath.

2/6

Radio Press Series No 17.



# Contents

*Editor :*  
**JOHN SCOTT-TAGGART,**  
 F.Inst.P.

*Joint Assistant Editors :*  
**PERCY W. HARRIS,**  
**E. REDPATH.**

*Staff Editors :*  
**E. H. CHAPMAN,**  
 M.A., D.Sc.  
**A. D. COWPER, M.Sc.**  
**G. P. KENDALL, B.Sc.**  
**R. W. HALLOWS, M.A.**  
**S. G. RATTEE.**

	PAGE		PAGE
Frontispiece ... ..	2	A Crystal Receiver ... ..	48
Adding a High-Frequency Valve to the S.T.100 ... ..	3	With Special Tuning. ... ..	
By THE EDITOR.		Regular Programmes from British and Continental Broadcasting Stations ... ..	55
In Passing ... ..	10	Readers' Experiences ... ..	56
Some Unusual Faults ... ..	12	An Efficient Single-Valve Receiver ... ..	53
By G. P. KENDALL, B.Sc.		By HERBERT K. SIMPSON.	
The "Transatlantic Five"—A Multi-Valve Set with Range and Volume ... ..	15	Why Constructors Sometimes Fail ... ..	67
By PERCY W. HARRIS.		By THE EDITOR.	
High-Tensionless Receivers ... ..	23	Tested by Ourselves ... ..	71
By JOHN SCOTT-TAGGART, F.Inst.P., A.M.I.E.E.		The Use of Taps in Wireless Work ... ..	77
A Two-Valve Cabinet Receiver ... ..	30	By R. W. HALLOWS, M.A.	
By STANLEY G. RATTEE, Member I.R.E.		Further Notes on the 10-Valve Armstrong Supersonic Heterodyne ... ..	81
Above and Below the Broadcast Wavelengths ... ..	34	By KENNETH ALFORD.	
The "Modern Wireless" High-Tensionless Receiver ... ..	38	Reflex Wireless Receivers in Theory and Practice... ..	83
By HERBERT K. SIMPSON.		By JOHN SCOTT-TAGGART, F.Inst.P., A.M.I.E.E.	
The Cowper High-Tensionless Circuit ... ..	47	Trouble Corner ... ..	92

*Scientific Adviser :*  
 Prof. G. W. O. HOWR,  
 D.Sc., M.I.E.E.

*Advisory Editors :*  
 Prof. R. WHIDDINGTON,  
 M.A., D.Sc.  
 Prof. C. L. FORTESCUE,  
 M.A., M.I.E.E.  
 Tel.—Central 3763.

*Advertisement Managers :*  
 SCHEFF PUBLICITY ORGANISATION, LTD.  
 125, Pall Mall, London, S.W. 1.  
 Tel.—Regent 2440.


# MODERN WIRELESS

All correspondence relating to contributions is to be addressed to the Editor of "Modern Wireless."

**Radio Press Ltd**  
 PUBLISHERS OF WIRELESS WEEKLY  
**DEVEREUX COURT.**  
 • STRAND, W.C.2 •  
 Tel.—Central 3763.

Nothing contained herein is to be regarded as permission or encouragement to infringe any patent rights.

# A Millionaire's Station.

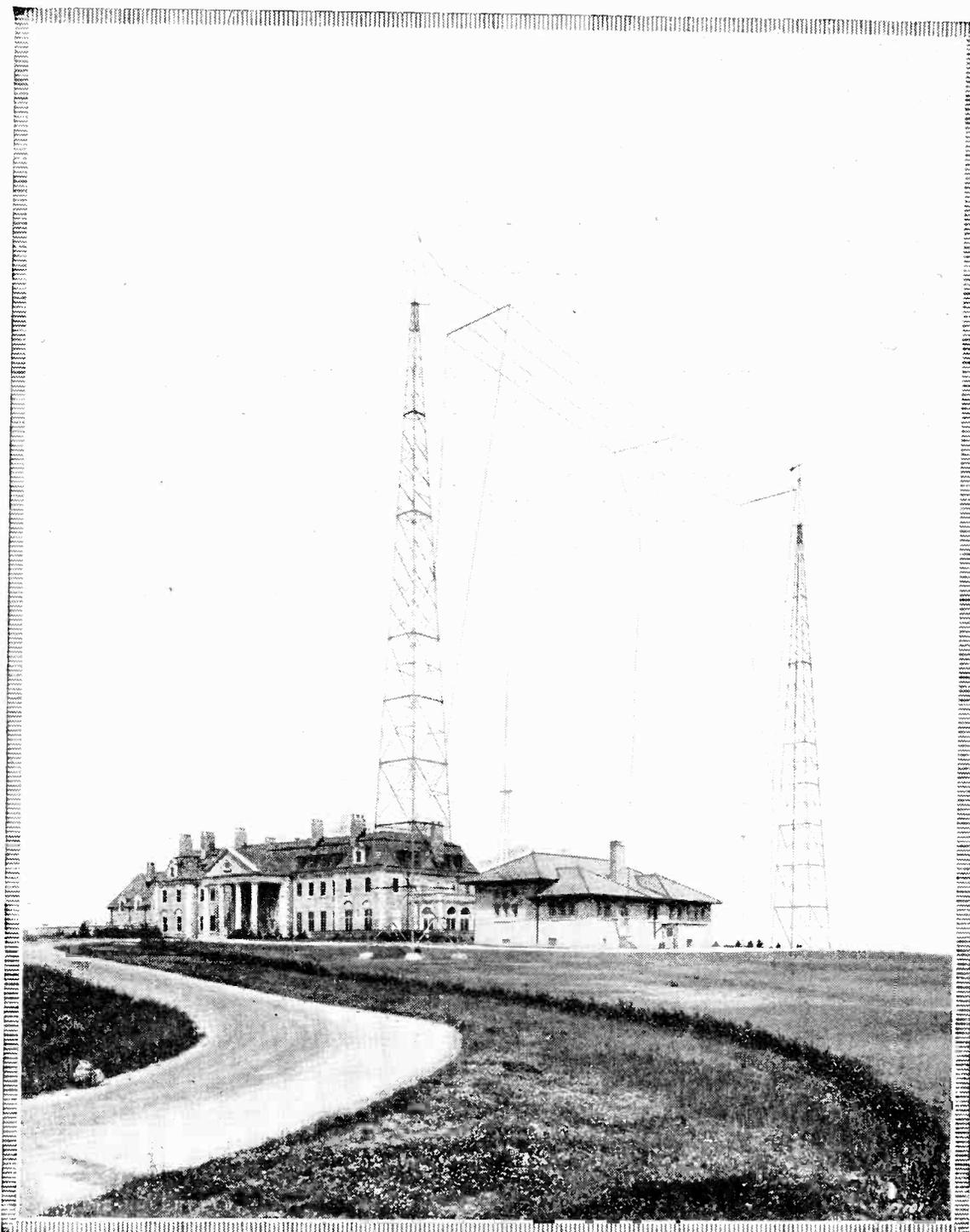

*This splendid aerial equipment, and the station beneath, are the property of an American millionaire, who possesses a broadcasting licence and sends out regular concert programmes for the benefit of listeners.*

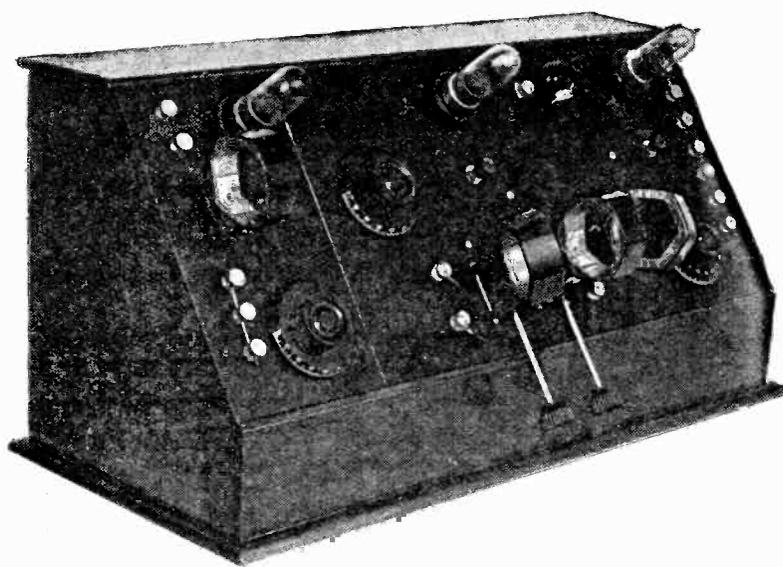


Fig. 1.—The set is built into the conventional sloping front cabinet.

*To those who have tested the S.T. 100 circuit the following description of a set with an extra high-frequency amplifier will prove interesting. Those without experience of the S.T. 100 are advised to try that circuit first.*

THE exceedingly large volume of sound obtainable from the S.T. 100 circuit has made the latter popular among those who like to have ample power to work a loud-speaker. This volume decreases fairly rapidly, however, at distances of over 50 miles from a broadcasting station, and many readers have expressed their desire for a circuit incorporating one more valve in order to bring in more distant stations with certainty at good strength.

The addition of a high-frequency amplifying valve will increase the range of the circuit and will make the reception of the distant stations an easier proposition.

The present set, a photograph of which is seen in Fig. 1, has been designed to give the maximum results, and the lay-out has been carefully considered, in order to prevent, as far as possible, any interaction between the parts. In the photograph a white line is shown drawn on the panel to indicate that on the left is the high-frequency amplifying portion, and on the right is the usual S.T. 100 with a modification, which will be discussed later.

A single-pole double throw switch serves to cut out the extra high-frequency valve if desired, the ordinary circuit being then in

use. The terminals on the left are those controlling the aerial circuit, enabling constant aerial, series, or parallel tuning to be employed at will.

The condenser  $C_1$  on the extreme left of Fig. 2 is the aerial tuning condenser, used when the high-frequency valve is working, while the condenser  $C_3$  above the three-coil holder, to the left, is that tuning the secondary of a high-frequency transformer, coupling the first and second valves, which is formed by the coils  $L_2$  and  $L_3$ , these being the left-hand movable socket, and fixed socket of the coil-holder, respectively. When the extra high-frequency valve is cut out by bringing the switch  $S_1$  over to the X side, the extreme left-hand condenser  $C_1$  and the coil  $L_1$  are out of circuit, as is also the left-hand socket  $L_2$  in the coil-holder, and this coil must either be withdrawn or moved well away from the other two; the condenser  $C_3$  to the right of the white dividing-line now becomes the aerial tuning condenser. The right-hand socket  $L_4$  of the coil-holder and the condenser  $C_4$  on the extreme right of the receiver are those in the anode circuit of  $V_2$ , which is the first valve of the ordinary S.T. 100 circuit. The crystal detector is situated between the second and third valves of this receiver, and is of a

## Adding a High-Frequency Valve to the S.T. 100

A Highly Powerful Set Designed by  
THE EDITOR

particularly neat and efficient type, known as the "Eccentro."

### Circuit Diagram

A diagram of the circuit arrangement of this receiver is given in Fig. 3, and it will be seen that the aerial circuit comprises the coil  $L_1$  and the condenser  $C_1$ , the small fixed condenser C.A.T. being included in order that constant aerial tuning may be applied. The valve  $V_1$  acts purely as a high-frequency amplifier, the amplified oscillations being passed on, *via* the coil  $L_3$ , which is closely coupled to  $L_2$  in the anode circuit of  $V_1$ , to the grid of  $V_2$ . The high-frequency oscillations are further amplified by the valve  $V_2$ , and are then rectified by means of the crystal detector D. The rectified signals then pass through the transformer  $T_1T_2$  back to the valve  $V_2$ , where they are magnified by this valve, and pass on to  $V_3$  by means of the transformer  $T_3T_4$ , the low-frequency oscillations being thus further magnified. The receiver thus acts as a five-valve set, having two stages of high-frequency amplification, a rectifier, and two stages of note magnification, with the difference that the rectifier is a crystal, and one valve—namely,  $V_2$ —does the work of two. A great saving in valves and current is thus effected.

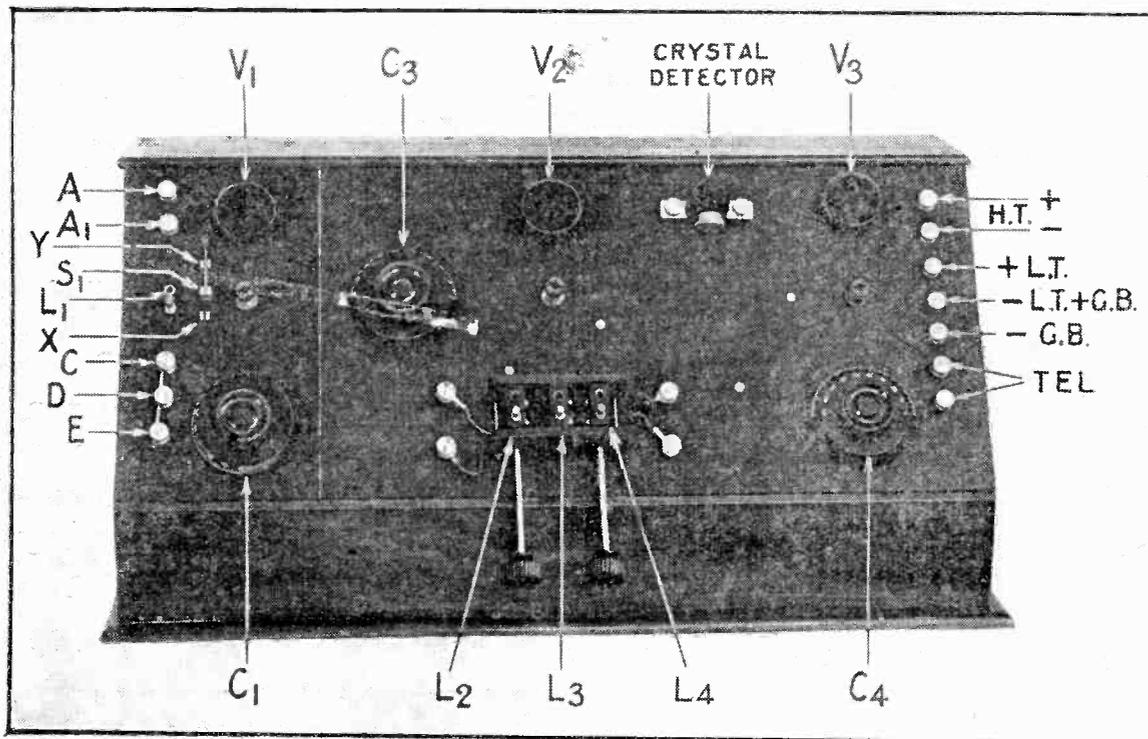


Fig. 2.—Front of the cabinet, with valves removed and the various components lettered.

**Stabilising Resistance**

It will be noticed that the stabilising resistance included in the usual design of S.T. 100 set has been omitted from this receiver. Should the constructor find that it is necessary, when using two valves only, to have this resistance, he may include a variable anode resistance of the order of 50,000 to 100,000 ohms by joining the grid of the second valve  $V_2$  to one end and the positive of the low-tension battery to the other end of the resistance. A reliable make of fixed resistance may be used if desired, and in this case the value should be about 80,000 ohms.

Another modification of the original S.T. 100 circuit which has been introduced in this set is the condenser  $C_5$ , which is connected across the O.P. and O.S. of the low-frequency transformer  $T_3T_4$ . The object of this condenser is to increase the purity of the received signals, and it was found necessary with the transformer used that its value should be  $0.001 \mu F$ . This value will vary with different transformers, and in some cases perhaps the condenser may be dispensed with altogether.

The method of coupling the extra high-frequency valve to the S.T. 100 circuit was suggested to us in April by Mr. H. L. Meyer, of Cavendish Square, who has obtained successful results with this type of circuit.

**Reversal of Coils**

It is desirable to reverse the direction of the coil  $L_2$ , in the anode circuit of  $V_1$ , in order to ascertain in which position the best results are obtained, and, in the set described, provision for such reversal has been made. Flexible rubber-covered leads join the socket of the coil-holder to two terminals on the panel, thus rendering the reversal of the coil a simple operation. Similar provision has been made in respect of the reaction coil  $L_1$ , in accordance with a practice frequently advocated in this journal.

**Constant Aerial Tuning**

Constant aerial tuning may be applied to the three-valve circuit by joining the aerial lead to terminal A, earth to E, and joining C, D, and E together by means of a piece of wire. The switch  $S_1$  must be turned so as to make contact with the upper point Y. A circuit diagram showing the three valves in use with constant aerial tuning is given in Fig. 4.

Parallel tuning may be used instead of constant aerial tuning by joining the aerial lead to terminal  $A_1$ , leaving A free, earth to E, and

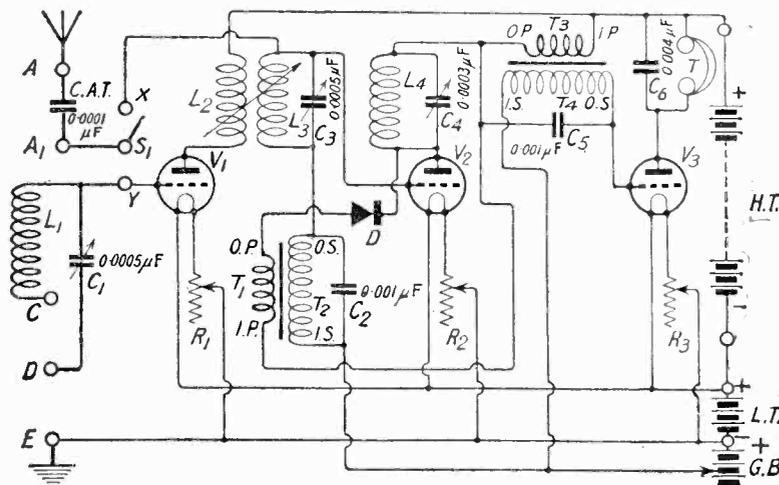


Fig. 3.—The circuit arrangement of the receiver.



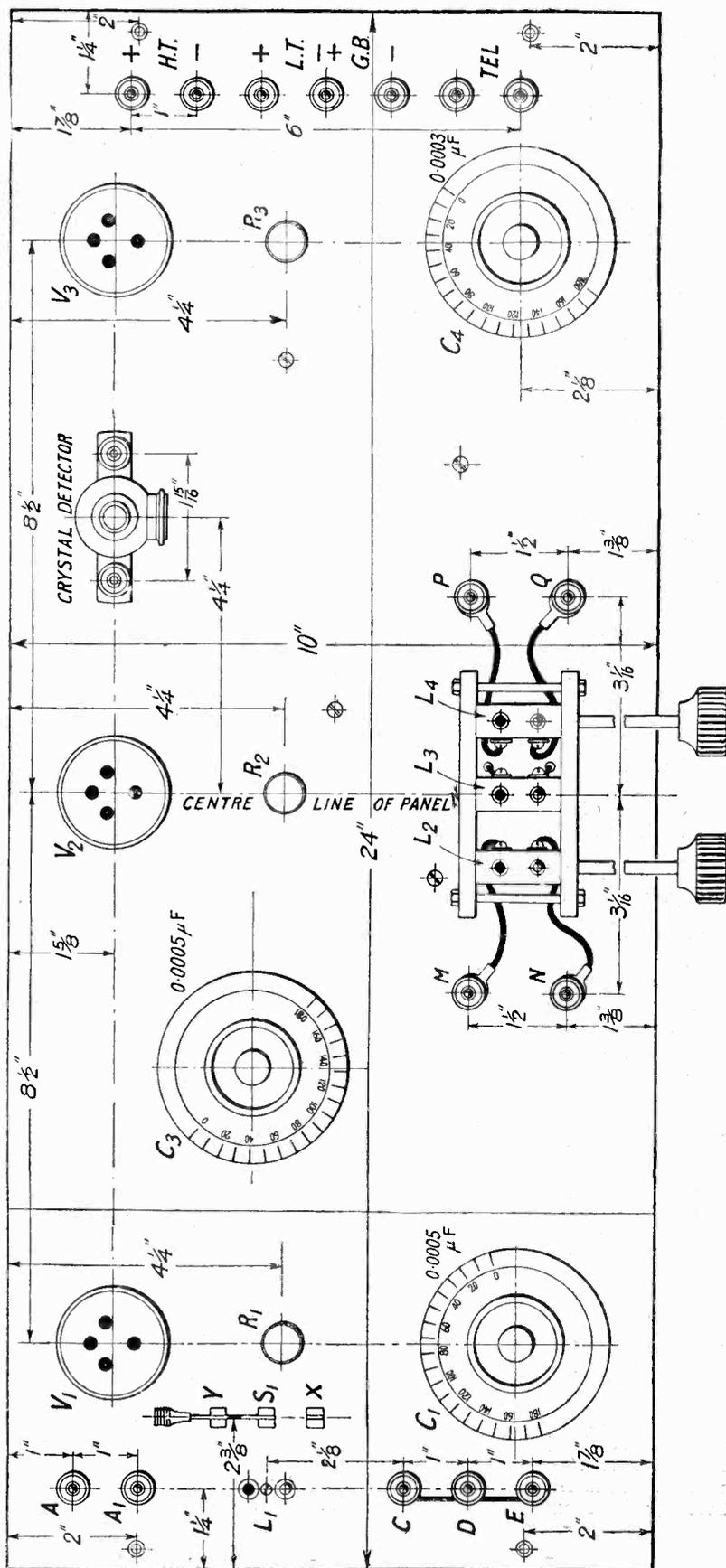


Fig. 5.—A scale drawing of the top of the panel, showing the positions of all the necessary holes.

time in changing drills. The holes shown are in the correct positions for the components used, but care must be taken, if parts other than those specified are employed, that the holes are drilled of the correct size for these parts. Four holes are drilled, two in each of the shorter sides, by means of which the panel is secured to the cabinet. The positions of these holes are seen in Fig. 5.

**Mounting the Parts**

When all holes have been drilled, the various parts should be mounted up, and it is recommended that they be placed in position according to weight. For example, start with the terminals, then proceed with the valve holders, filament resistances, and so on, leaving such parts as variable condensers and transformers until the last, thus keeping the weight down as much as possible while the panel is being turned about in the process of tightening nuts, and so on.

**Wiring Up**

Having mounted all the necessary parts, the constructor should proceed to tin thoroughly all points to which a wire has to be soldered, and then commence the actual wiring up of the receiver. The square-section wire used gives a very neat appearance to the back of the panel, and also there is less capacity between wires than when systoflex-covered wire is used. With a little care in bending the wire to fit exactly between the terminals, the constructor should find this wire almost as easy to work as the older method of thinner wire covered with insulated sleeving. The leads to the two movable coils on the coil-holder consist of rubber-covered flexible wire, secured under the screw-heads on the respective sockets, and terminating in spade tags, which are secured to the correct terminal on the panel. The leads to the fixed socket consist of the ordinary wire used for wiring up, pushed through holes in the panel immediately underneath this socket.

A wiring diagram is given in Fig. 7, and when this is consulted no difficulty should arise out of the wiring. Two photographs of the back of the panel are shown in Figs. 6 and 9, and give a good idea of the neatness of the wiring, besides helping to clear up any little points of uncertainty.

**The Cabinet**

The panel is mounted in a polished mahogany cabinet of the sloping front type, thus completing the handsome appearance of the

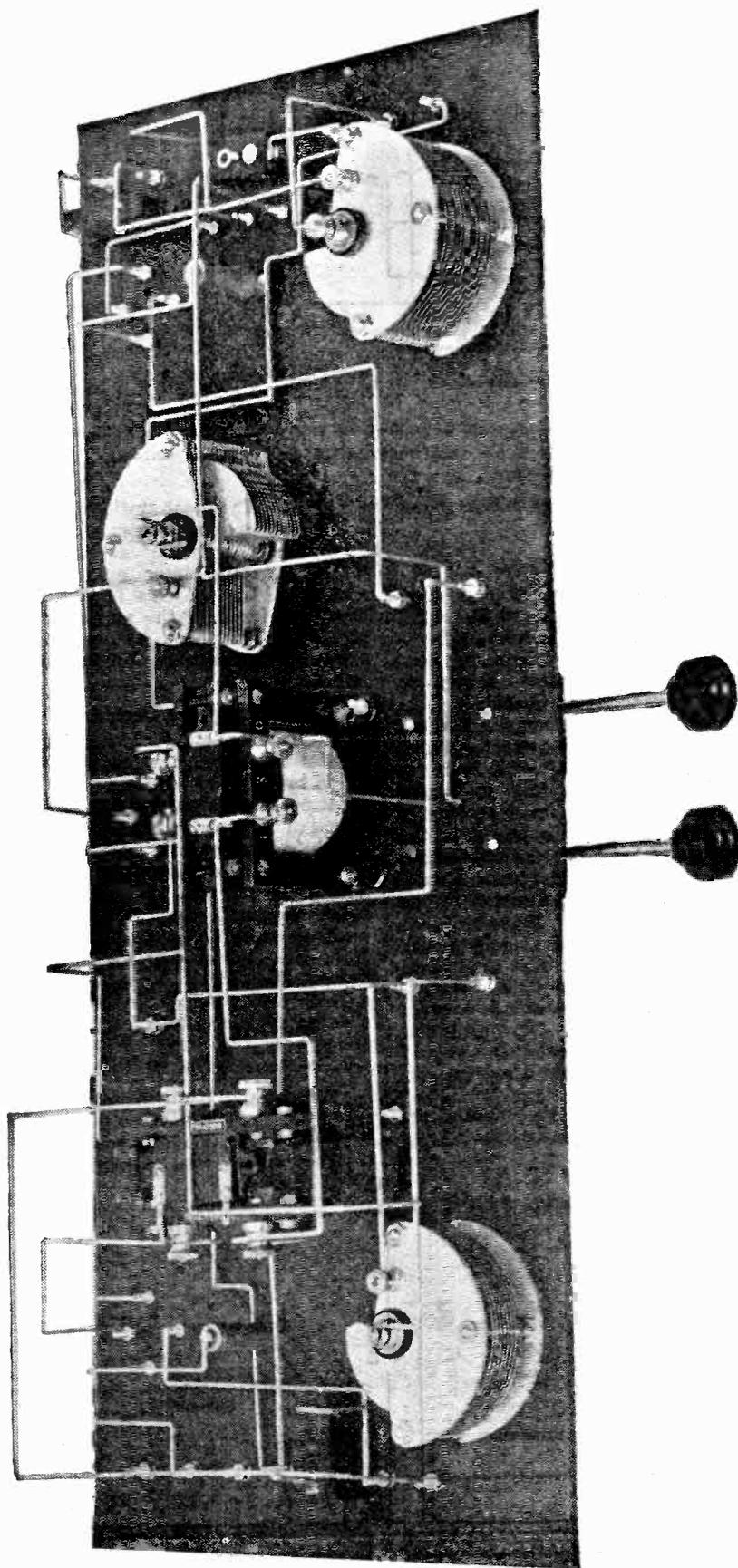


Fig. 6.—The underside of the panel, showing the wiring.

receiver. The cabinet, a dimensioned drawing of which is given in Fig. 8, was obtained from Messrs. Wright and Palmer, of Forest Gate, and is the same cabinet as was used in the Three-Valve Dual Receiver mentioned previously. For those who intend to make their own containing box the drawing given should furnish all the necessary information. The work is carried out in  $\frac{3}{8}$  in. finished mahogany, the wood being cut according to the dimensions given. The two side pieces are best cut to size,  $11\frac{1}{8}$  in. by  $9\frac{1}{2}$  in., as a rectangle first, the bevel being cut off afterwards, with both the sides firmly clamped together, thus ensuring that the slope is the same on both pieces. As seen from the figure, small fillets of wood are secured to the inside of the front of the cabinet, to provide additional support for the panel, preventing the latter from sagging.

#### Coils and Valves

When using all three valves with the constant aerial tuning arrangement, the coil  $L_1$  on the extreme left of the panel may be a Lissen No. 50 for broadcast wavelengths below 420 metres, above which a Lissen 75 may be used. The left-hand coil  $L_2$  in the three-coil holder may be a Lissen 75, the fixed one  $L_3$  a No. 50 (or a 75 may be tried for wavelengths over 420 metres), and the right-hand coil  $L_4$  a 50 or a 75, according to whether the wavelength to be received is below or above 420 metres. When two valves only are in use, the middle socket on the coil-holder becomes the aerial coil, and when using constant aerial tuning, this should be either a No. 50 or 75, as explained above. The coil  $L_4$  in the right-hand socket of the coil-holder remains a 50 or 75.

Any good make of valve may be used. Three Ediswan A.R. valves were used when the following Test Report was prepared.

#### Batteries

A high-tension battery of 100 volts should be used, in order to obtain the best results from the set, and this is connected, positive and negative respectively, to the top two terminals on the right-hand side of the receiver. The low-tension positive is connected to the third terminal from the top, and L.T. - to the fourth. A grid bias battery should be used, and its positive connected to the same terminal as the negative of the low-tension accumulator, the negative of the grid battery being connected to the fifth terminal in

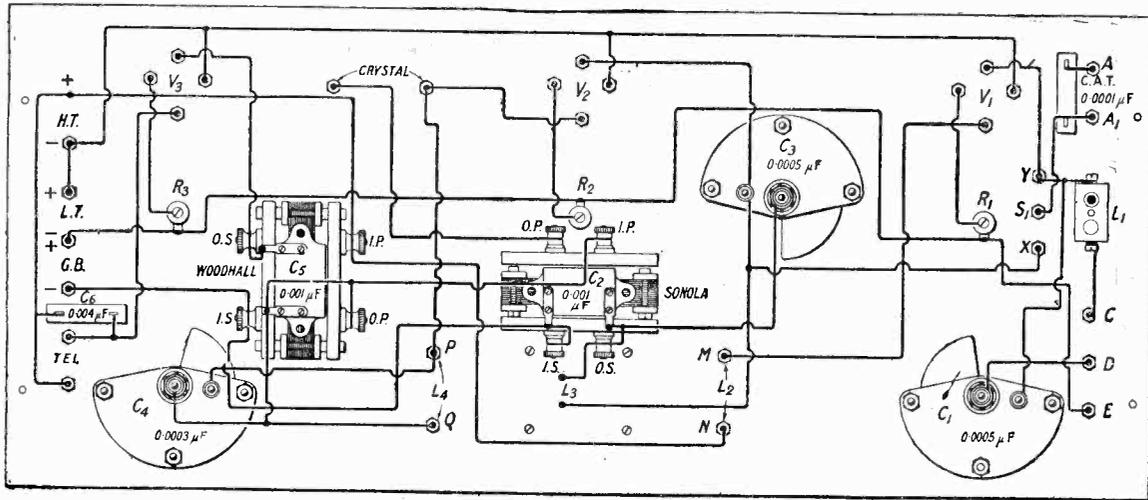


Fig. 7.—The wiring of the receiver. The lettering of the condensers, etc., corresponds with the circuit diagram.

the row. The loud-speaker is connected to the bottom two terminals in this row.

The grid battery, which appears to be somewhat of a mystery to some readers, may conveniently consist of a 15-volt high-tension unit, of the type in which tapings at every three or so volts are provided. Actually about  $4\frac{1}{2}$  volts negative grid bias is usually ample, and very often no extra grid bias is necessary, the terminals G.B. — and L.T. — G.B. + being shorted. The small Ever-Ready cell, size O, is eminently suitable for making up a grid bias battery, each cell having a voltage of 1.5 volts, thus allowing tapings to be taken from the battery at 1.5, 3, 4.5 and so on, providing a more or less even control of grid voltage. Ordinary flash-lamp batteries may conveniently be employed.

When using bright emitter valves, a 6-volt accumulator should be used, and it is advantageous to use an accumulator with dull emitter valves, as the discharge current is much more steady than is that of dry cells. In this case

a 4-volt accumulator will be found satisfactory.

**Testing the Set**

When complete, the receiver may be connected up to the aerial and tested. The filament and high-tension batteries should be connected, as explained above, to their respective terminals. In order to test whether the S.T.100 part of the set is in correct working order, start testing with constant aerial tuning on the two-valve circuit when the local station is operating. Insert a 50 coil in the middle socket  $L_3$  of the coil-holder, and a 50 in the right-hand socket. No coils are to be inserted in the sockets  $L_1$  and  $L_2$ . Make sure that the cat-whisker is touching the crystal, and turn the single-pole switch  $S_1$  so that it is pointing downward and making contact with the point X. The grid bias terminals G.B. + and G.B. — should be shorted when first using the set. Turn on the filaments of the valves  $V_2$  and  $V_3$ , leaving  $V_1$  switched off, and tune on the condensers  $C_3$  and  $C_4$ , keeping the coil  $L_1$  well away

from  $L_3$ . The local station should be heard at good strength, and should become louder as the coil  $L_1$  is brought closer up to the fixed coil  $L_3$ . If this is not the case, the leads to the moving coil should be reversed by changing over the connections to the terminals PQ.

**Operating the Detector**

The Eccentro is a totally enclosed crystal detector, the cat-whisker being brought up to the crystal by rotating a knob on the top of the barrel of the instrument, the crystal cup being inserted in the front of the barrel and being rotatable. The knob on the top has a red mark engraved upon it, and this mark must be brought as far away from the crystal cup as possible before the latter is rotated, or damage will result. The knob on the top of the detector should be slowly rotated until a sensitive spot on the crystal is found.

**Testing the High-Frequency Amplifier**

When the S.T.100 part of the receiver is operating efficiently, the

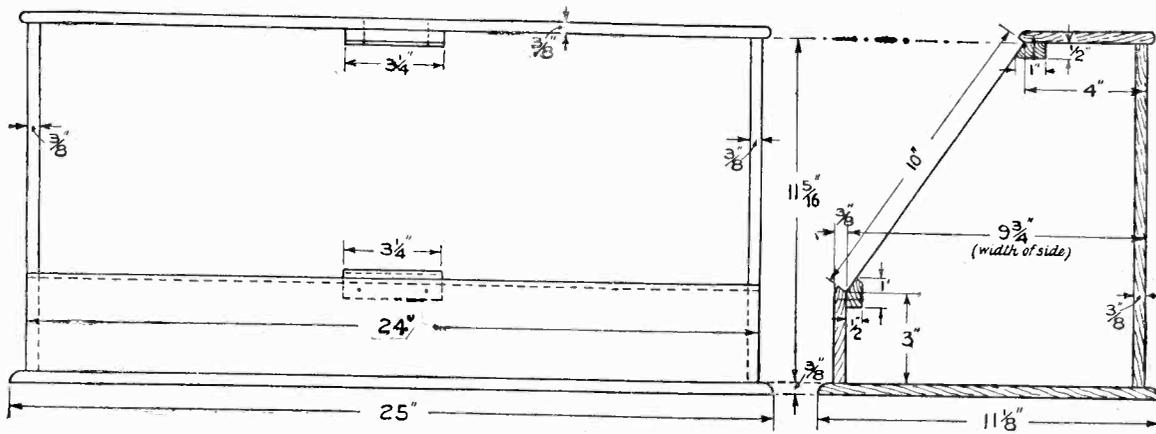


Fig. 8.—Two views of the cabinet, with full dimensions.





### Unrest

**T**HERE is considerable unrest in the world of wireless men at the present time. By this I do not mean that they are thinking of rebelling against the regulations or of tarring and feathering the Postmaster-General, or anything of that kind. I mean simply that about 99.9 per cent. of them are engaged in rebuilding their sets. Now rebuilding a set is not half such a simple business as the uninitiated might suppose. In fact, it brings out the quality of indecision which we noble males claim does not as a rule form part of our character. You know how we are accustomed to laugh quietly at our wives when they are in the throes of choosing new garments. "I can go to 'my' tailor's" say we, "and in the brief space of twenty minutes choose the cloth for three suits and be measured for them. Now you take a whole morning over buying a scarf or a pair of gloves." Werubin in rather a superior way the manner in which our wives will have a whole draper's store turned upside down for them, departing eventually with a winning smile and packet of pins whilst the salesman sinks groaning to the floor and cries aloud for first aid. But the indecision of a woman even when she is choosing a hat is as nothing to that displayed by the average man when he is endeavouring to select the ideal circuit for his new set. He comes home every evening with his pockets crammed full of wireless books and papers. He writes to every manufacturer for a catalogue. He visits all his friends and consults them. He makes up his mind three times a day and changes it as often. He fares forth and purchases an ebonite panel as big as a table top, marks it out, and then repents. With infinite labour and the use of vast quantities of emery paper he removes his scribed lines. Then he begins all over again. At last he has something which seems nearly perfect.

He scratches with his scriber; he plies his trusty breast drill; he mounts up most of his components, only to find that unless he fixed the first L.F. transformer to the underside of the A.T.C. or something of that kind, there is no possibility of getting them all in.

### A Soft Job

With a sign of resignation he decides that the spoilt ebonite will come in quite handy for making up small gadgets later on. Another monster slice is purchased, and this time he resolves that he will not rush at things. It is usually at about this time that he reads in the papers that in three days the finest wireless programme of the year will be put on, whilst his wife informs him that she has invited a dozen friends to come and hear it. In a frenzy he rushes to his workshop, flings things together almost anyhow, and probably produces a set that surpasses his fondest expectations by its performances. This, of course, is only a temporary affair which must come to pieces at once when its work has been done. You will find that most wireless enthusiasts have enormous supplies of ebonite for gadget making! Meantime the manufacturers of this beautiful insulating material prosper and wax fat and drive about the country in Rolls-Royce cars. A hard-up ebonite manufacturer is a rarer bird than a dead donkey. It has been calculated by Professor Goop that if all the panels discarded during the last twelve months were piled into one enormous heap, it would be nearly as tall as the stories told by our most enthusiastic receivers of trans-atlantic broadcasting.

### A Friendship Severed

It is this troublesome business of choosing a new set which has been responsible for the terrible civil strife that is now raging in our little town. Two of the most prominent members of the wireless

club are Rear-Admiral Whiskerton-Cuttle and General Blood Thunderby, who, until recently, have been the closest of cronies. There has always been as one might expect a friendly rivalry between the representatives of the fighting services, but the warrior and the salt formed a close alliance with the object of proving to the rest of us that mere civilians were simply nowhere. Naturally they both took up wireless in its early days. The Admiral is an expert at splicing ropes and hoisting spars and heaving ho and things like that, so that it was natural for him to help the General in the erection of his aerial. The soldier man, on the other hand, has more workshop skill than the other, and used always to do the sailor's little drilling jobs and so on. Whilst they were going through the early stages of radio-mania all was well.

### Progress

They progressed in perfect amity from crystals to single valves, and then went on to make bigger and bigger straight circuits. The coming of the Armstrong and Flewelling circuits dealt their friendship rather a shrewd blow, for Blood Thunderby became a strong Armstrongite, whilst Whiskerton Cuttle pronounced emphatically in favour of Flewelling. Night after night they would meet in one or the other's sanctum to argue the matter out. They would demonstrate to each other the wonderful capabilities of their super sets, whilst the rest of us had to close down owing to the whistles and banshee wails with which the local ether was filled. And if the ether was filled with sound, so was the air later in the evening as they conducted their argument.

And all night long the noise of battle rolled,

From out the windows of the wireless den.

There was something like a reconciliation between the two when we had our little row at the

wireless club, for then the two joined forces in attacking the committee, the General asserting loudly that the club was going to the dogs, and the Admiral urging us in what the newspapers call bluff breezy sailor talk to sack the lot. We thought for a time that they were going to patch it up for good and all, and I think that they might have done so had it not been for the flood of complicated circuits which were shortly afterwards let loose upon the world. Each of the pair began at once feverishly to redesign. Unable to make up his own mind the General determined to make up the Admiral's for him, whilst Whiskerton-Cuttle, equally undecided, left no stone unturned to convince the warrior that the indecision which he showed was unworthy of the traditionals of the army and that it was imperative that he should construct a colossal Super pliodyne. The rest of us strove to persuade them both to go in for something simpler, for we foresaw that the welkin-rending properties of untamed super circuits in the hands of fierce fighting men might well make it necessary for us to give up wireless altogether. Alas, it was of no avail. They both built these terrible things, and each has reported the other to the Postmaster-General as a violent and confirmed oscillator. The strife rages fiercely and there are no signs that peace is very likely to reign. They cut each other dead in the street, and at the club the General never misses the chance of referring scathingly to well-meaning but wooden-headed sailors, whilst the Admiral usually gets out something about the amazing lack of common-sense which he asserts is the hall-mark of the junior service.

#### For this Relief . . .

I am glad to say that the mania for super-supers did not last long, and we can now hear ourselves think once more when our sets are working. It has been succeeded by constructivitis in a very marked and satisfactory form. Each of the rivals is now so busy in building new sets and new gadgets that he has no time at all for "broad-catching." No set ever reaches completion; therefore we are safe. Just as the finishing touches are about to be added it occurs to the maker that it would be vastly improved by the addition of a switch here or a potentiometer there. He promptly pulls it to pieces and begins anew. General Blood Thunderby comes to the wireless club and tells us that he


will have his set working on the following evening. Then we keep him talking whilst an emissary is sent to fetch Ponderby, who is always full of new ideas. Ponderby, who knows what is expected of him, strolls in quite casually and says, "Evening, General, how is the set getting on?" "Finished to-morrow," says the warrior proudly and proceeds to describe it. Ponderby listens intently until he pauses for want of breath. Then he adroitly says, "Ah, but had you not thought of fitting variable grid-leaks?" That does it. Blood Thunderby swears that variable gridleaks are no use, but we know that the seed has been sown and that it will bear fruit. On the morrow if you visit his workshop you will find him altering the positions of his components to make room for them, and drilling holes for their reception. He posts an order for them, and we have a respite of at least three days, during which time Ponderby thinks of something else to suggest.

#### The Problem of Whisker Cuttle

The Navy is a little more difficult to deal with, for somehow or other the admiral has got wind of our methods of keeping the General in order, and sympathises thoroughly with them. In fact, we have had several most valuable suggestions from him; one of them kept Blood Thunderby busy for nearly a fortnight. It consisted of an entirely unworkable addition to his circuit which took him a week to make, whilst he spent the best part of another trying to find out why it would not function. The way in which, metaphorically, of course, we sit upon the admiral's head is most effective, and if it is a little expensive at times, it is well worth it. He, I should explain, is what we may call a local patriot. He never buys things out of the town, but orders them always through the small electrical shop in the High Street. It was this habit of his which gave Gubbsworthy the inspiration which has delivered him into our hands. We formed a secret society, the S.K.R.A.B. — The Society for Keeping Rear-Admirals Busy. Our first step was to see that he was elected chairman of every possible organisation, from the parish council to the committee of boy scouts. This ensures that he has not more than two days a week to himself. Next we sent a deputation to the aforementioned electrician and hatched a conspiracy with him. If the admiral

orders a panel 54 in. by 33 in.— "and, mind you, it must be exact because I have got the cabinet made"—it is delivered at the end of three days an inch too small all round. He takes this back livid with fury, and demands another in its stead. The second, when sent round, is found to be more diamond-shaped than rectangular. The S.K.R.A.B., of course, pays for the spoilt panels, which are cut up and divided amongst the members. In the same way, if he wants a .001 variable condenser, he gets a fixed one of three times that value, and the mistake cannot be rectified in less than a week. Sometimes he goes into the shop and actually sees the order written, so that he knows that it is right this time. When this happens he is horrified to hear some days later that the gadget he requires is out of stock, but that they are making him one, which he may expect to receive in about a month. Naturally he raves at the club about the stupidity of local tradesmen. When this happens, Ponderby, Gubbsworthy and General Blood Thunderby, who has been made a member of the S.K.R.A.B., urge him strongly to give up attempting to deal in the town and to purchase all his requirements by post. The very fact that Blood Thunderby supports this suggestion is quite sufficient to make the Admiral turn it down at once. Such is his local patriotism that he will go on buying from the shop in the High Street till the cows come home, and so long as he does so life is worth living for the rest of us. It is really great to be beckoned across the road by the Admiral, who whispers into your ear some perfectly fiendish new idea for his rival's set, and later on meet Blood Thunderby, who, after making the secret sign of the S.K.R.A.B., unfolds briefly his latest plan for interfering with the Navy's supplies of raw materials. It is sad, of course, that a long standing friendship should have been broken up, and when the first breach occurred, we all endeavoured to bring them together again. But now we glory in the strife, for we see in it the only way of ensuring peace and tranquillity for ourselves.

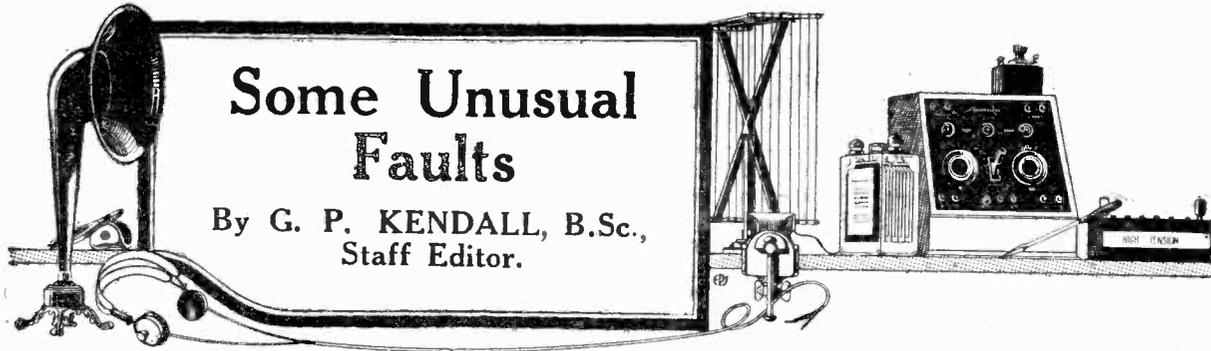BUY  
WIRELESS WEEKLY  
EVERY WEDNESDAY  
SIXPENCE.  
EVERYWHERE.



# Some Unusual Faults

By G. P. KENDALL, B.Sc.,  
Staff Editor.

**A**MONG the things which sometimes deter the beginner, and sometimes even the more experienced experimenter, from starting upon the construction of a new set perhaps the most serious is a feeling that there is always a chance that the set won't work when finished. The constructor usually knows, either from his own painful experience or that of one of his friends, that it is quite possible to follow a perfectly reliable design with entire accuracy, using materials of good quality, and yet find oneself possessed of a set with some obscure fault at the end of one's work. Skill in fault-finding being an accomplishment usually possessed only by the fairly experienced constructor, it is not surprising that the relative novice occasionally hesitates to start building a set, very naturally disliking the possibility of placing himself in the humiliating position of having to make a set and being unable to find out why it doesn't work.

No doubt experience alone can give that confident feeling possessed by the old hand, of being able to locate and clear any fault, however obscure, but a few hints on the general methods of trouble-tracing do a good deal to remove the sensation of helplessness which afflicts the novice in a difficult case. It is outside the scope of the present contribution to consider methods of fault-finding in detail, and it must suffice to say that there are four chief classes of faults:—

- (1) An error in wiring.
- (2) A defective connection (a badly soldered one, for example).
- (3) A defective component.
- (4) A defective accessory, such as a valve, tuning coil, 'phones, etc.

The location of the first type is usually easy, being merely a matter of comparison with the original wiring diagram, but the second usually calls for special

methods of testing, one of the most useful of which I propose to detail later. The fault can often be located by anyone possessing sufficient knowledge to recognise the symptoms to which it gives rise, but lacking such experience systematic testing is the only course.

Similarly, with a case of trouble in a component part, such as a "shorted" fixed condenser, or a break in the windings of a low-frequency transformer, tests are usually necessary, although the alternative method of systematic substitution of parts known to be in order for those under suspicion may sometimes be preferable. This latter method is probably the best to adopt in the case of the fourth type of fault, since such accessories as valves are almost impossible for the user to test, and by far the best plan is to substitute

however, it is first necessary to explain one of the simple methods of testing which I employ—namely, the 'phones and dry cell method.

### Testing with Dry Cell and 'Phones

This method of testing is chiefly of use in detecting broken connections and short circuits, but other applications will present themselves to the user. It is probably the simplest and easiest method of testing a defective set, and a little ingenuity enables one to locate all sorts of faults by its aid. The reader will be aware that if the tags of a pair of telephones are joined across a dry cell strong clicks will be heard on making and breaking the circuit, and this is the indication which we use in testing. One tag of the 'phones is permanently connected to one terminal of the dry cell, and the

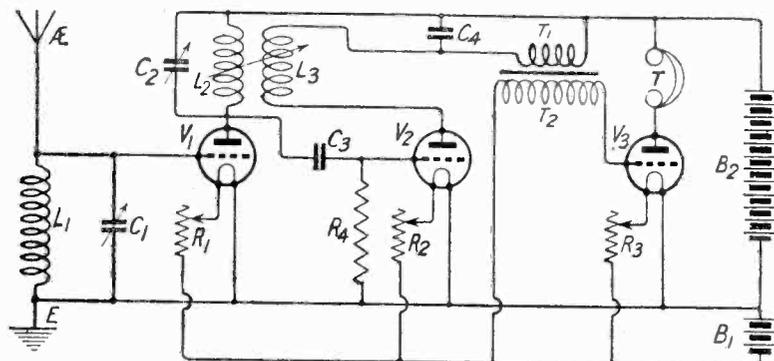


Fig. 1.—A circuit in which a break in the aerial circuit may produce very peculiar symptoms.

others known to be in working order.

The purpose of this contribution is really to give a series of examples of the more difficult type of fault, all these cases being ones which I have actually met with recently, since a study of typical cases is of the greatest assistance to anyone who is faced with a difficulty, and I propose to explain in each case the methods which led to the detection of the fault. In order to do this,

other is left free. The free tag and a wire from the other terminal of the dry cell can then be touched upon all the points in the circuit which ought to be joined together, and clicks should be obtained. If no breaks are found in the wiring, one then proceeds to test all the points which ought not to be joined together; a click (other than a faint one) in this case denotes a short circuit. This understood, we can proceed to consider

some instructive and unusual faults.

### Case No. 1

About a month ago a three-valve set closely resembling the "all-concert" set was brought to me which presented some very peculiar symptoms. Signals were weak, and the set was apt to oscillate in an uncontrollable manner, but the most curious phenomena were observed in the aerial circuit, where it was observed that it was quite immaterial what size of coil was used. Further, it was presently discovered that no difference was made by removing the coil altogether! The only effect produced by varying the aerial condenser was to weaken signals as the capacity was increased, the strongest signals being obtained at the zero end of the scale, irrespective of the size of coil in use.

Since the trouble was evidently located in the aerial circuit the first step was to test this circuit for continuity, and the dry cell and pair of 'phones were brought into action. A coil was inserted in the aerial socket to complete the circuit, and the free 'phone tag was touched upon the aerial terminal and the wire from the dry cell upon the earth. Dead silence, indicating a break. The panel was then taken off and detailed tests were made of each part of the wiring of the aerial circuit.

The circuit of this set is given in Fig. 1, while the wiring of the aerial circuit is illustrated in Fig. 2.

The first test was between the aerial terminal (A in Fig. 2) and the grid (G) of the first valve, a good click being obtained. Tests between A and the point B (fixed plates of aerial condenser), between the earth terminal (E) and the moving plates (C), and between E and the point F (one pole of the coil socket) were then made, and showed no fault. When the test was applied between A and the point D (other pole of aerial coil socket), however, it was found that no click could be obtained and break in the circuit being thereby indicated. Examination of the soldered joints showed them to be O.K., and therefore attention was directed to the coil socket, and here the trouble was found: the screw under whose head the wire was fastened was so short that by the time it had been withdrawn far enough to permit of the insertion of the wire its inner end no longer made contact with the metal part of the coil socket, but merely gripped in the ebonite.

### Case No. 2

This example will illustrate the fact that the combination of two perfectly simple faults may produce phenomena which are so exceedingly puzzling that they may set one looking for exceedingly improbable defects, unless one possesses some simple means of testing. The receiver in question employs practically the same circuit as the one which we have just been considering, and the following symptoms were observed. There was a total absence of signals, but a continuous rushing and crackling noise was heard. This, in itself, was puzzling, since those faults

and then it was found that the noise entirely ceased, indicating that one of the quite common faults was present in combination with some other which was responsible for the absence of signals. Since there was no break of any point in the circuit, as indicated by the telephone test, and none of the condensers were shorted, it was evident that some fault must be present of a type whose presence would not be revealed by the telephone test. Practically the only point at which such a fault could exist were the various condensers, since the telephone would only reveal here a shorted

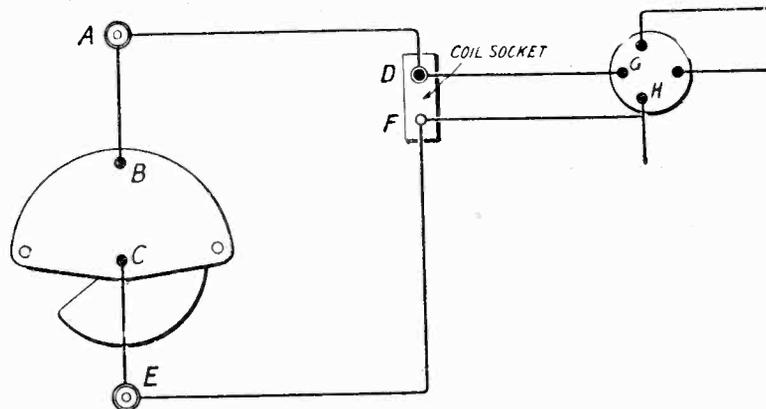


Fig. 2.—Part of the wiring of the set whose circuit is given in Fig. 1.

which usually result in crackling noises are not in themselves sufficient to entirely prevent the reception of signals. Common causes of such noises, for example are a defective high-tension battery, bad insulation at some point upon the panel or in the valve sockets, a defective grid leak, or a partial break in the windings of either the telephone receivers or a low-frequency transformer.

Substitution of other valves, coils, high-tension battery and telephone receivers showed that the trouble was in the set itself, and therefore the wiring was slightly altered so as to cut out the low-frequency valve, leaving only the high-frequency and rectifier in circuit. The noise continued, and therefore the low-frequency circuits were exonerated.

The telephones and dry cell test was then applied over the whole of the circuit, without the slightest indication of a break or a short circuit at any point, and the matter became more puzzling than ever. The next step, obviously, was to try in a rather haphazard manner eliminating some of the possibilities which might be giving rise to the noise. Eventually the grid leak was removed from circuit,

component. They do not indicate a break between the external terminals of the condensers and the plates within, and therefore the experiment was tried of replacing the grid condenser which was the most likely to be giving trouble, with a condenser which was known to be in order, and signals were immediately received as well as could be expected without a grid leak. The insertion of a good leak was then sufficient to enable the set to give the results which had been hoped for. Cases so involved as this one, of course, are not very common, but it is well to be prepared for them.

### Case No 3

This case is perhaps scarcely correctly included under the heading of "Some Unusual Faults," but it has such a valuable and obvious moral. The subject was a reflex receiver employing three valves, the first being a combined high- and low-frequency amplifier, and the second a rectifier. The set was giving very poor signals, and the owner was very much perturbed by the fact that he had discovered that he could turn out the filament of the rectifying valve without making the slightest difference to

the signals. He imagined that there must be some very serious mistake in his wiring to produce such a state of affairs, but the trouble was really very much simpler. The cause was actually rectification on the part of the first valve, so that little or no high-frequency amplification was obtained, and the set was simply functioning as a poor rectifier, followed by one stage of low - frequency amplification, this latter being given by the third valve. Questions elicited the fact that ordinary all-purpose receiving valves were being used, with a plate potential of 60 volts, and that a negative bias of about 5 volts was being applied to the first valve, and this might, and indeed has been known to, give rise to just such effects as this. Increasing the H.T. voltage to 120 volts completely removed the trouble.

Another case in which just the same phenomena were observed was the result of the employment of a soft Dutch valve as the first combined high- and low-frequency amplifier, together with an unsuitable plate voltage.

Case No. 4

This receiver was one possessing only two valves, one detector with reaction and one low-frequency amplifier. Although only one stage of low - frequency amplification was used most persistent low-frequency howling was occurring. It should perhaps be explained at this stage how it was decided that the howling was taking place in the low-frequency circuits, since this discrimination is one which often has to be made.

The discrimination is made by bringing the reaction coil right out from the aerial coil, and observing whether alterations of filament current of the low - frequency valve make any difference in the pitch of the note. If the howling is taking place at low-frequency such variations in pitch will usually take place, and, further, alterations of aerial tuning will leave it quite unaffected.

The particular fault which was present in this case is one which it is exceedingly difficult to locate by means of any system of testing, but it is one which having once been experienced is never forgotten. I had previously discovered that the use of a very high internal resistance high-tension battery will produce just this effect in a circuit of this type, and therefore the first accessory which I investigated was this battery. The method of testing was quite simple, but un-

fortunately one which is not usually possible to the experimenter. Measurement of the high-tension voltage was first made by means of a volt-meter of very high internal resistance. The result was practically the full reading which might have been expected from a number of cells in use. Upon a further reading being taken with a comparatively low internal resistance volt-meter (this being simply one of the cheap types sold at 7s. 6d.) scarcely any deflection at all was observed. The obvious inference was a high internal resistance in the battery, but its location proved unusually difficult.

The battery consisted of an assembly of separate flash-lamp refills, connected together by means of some of the patent strip connectors now upon the market. Each individual refill tested out quite satisfactorily by means of a small flash-lamp bulb, and it therefore seemed that the trouble must be in one of the connections. The trouble was ultimately found by the use of another low resistance volt-meter, reading up to 12 volts, applied across the ends of two of the refills at a time, the expected readings being 9 volts. A pair was ultimately found which gave scarcely any reading at all upon this volt-meter, although their individual readings were quite up to standard. Closer examination then revealed the fact that there was a patch of verdegis immediately beneath the clamping screw of one of the connecting strips, and upon the removal of this the fault was cleared.

Case No. 5


The receiver in this instance was the Transatlantic 5-valve set, employing two high-frequency valves, a rectifier and one or two stages (optionally) of low-frequency amplification. The set was being used in the Midlands, and the owner found that he could receive Aberdeen, Glasgow, Newcastle, and Birmingham quite satisfactorily, but only the weakest of signals could be obtained from London, Cardiff and Manchester. Upon these shorter wavelengths, also, tuning was exceedingly flat, and no reaction could be obtained.

Correspondence revealed the fact that all his good results were obtained by means of a home-made basket-coil of 50 turns, but that for shorter wavelengths he used a No. 35 of a make which shall be nameless. The substitution of this No. 35 coil being the only change which was made to receive the shorter wavelengths, I asked the

experimenter to send me his No. 35 coil, and found that it did actually give in any set with which I could try it only the very poorest of results. Its windings were continuous, as indicated by the telephone test, and therefore suspicion fell upon the quality of the insulation of its plug. The coil was removed from the plug, and the plug itself was placed in series between the telephones and a high-tension battery. Quite loud clicks were obtained between the two metal parts, thus showing that the insulation of the material was exceedingly low. Remounting the coil upon another plug restored the coil to normal functioning.

Extending the Spindles of Variable Condensers

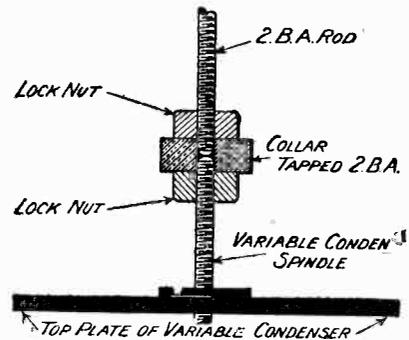It is often desirable for various reasons to extend the moving plate spindle of a variable condenser. A very simple method of doing this is shown in the diagram given below. A further length of 2 B.A. rod is secured to the 2 B.A. spindle by means of a brass collar which is tapped 2 B.A. A 2 B.A. nut is then tightly clamped on either side of the collar, as shown.




These nuts, acting as lock nuts, firmly grip the two lengths of rod, and there is no possibility of them becoming loosened with use.

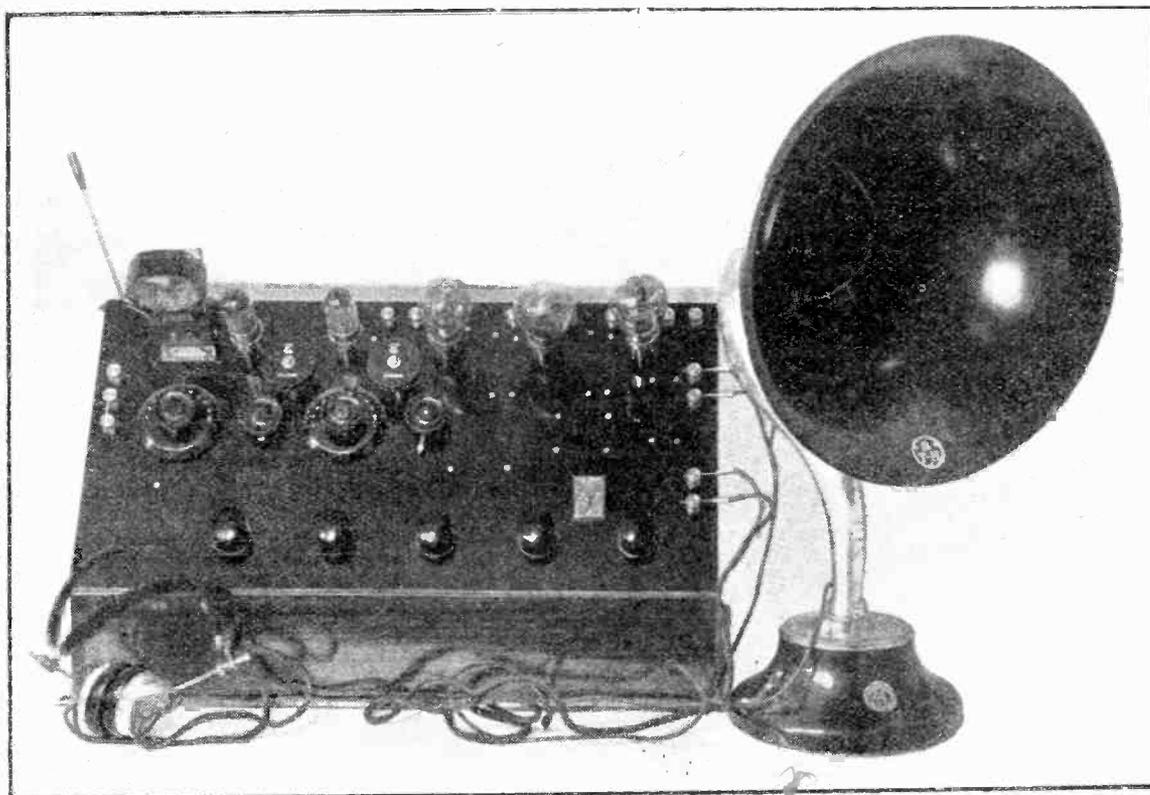H. B.

TO NEWSAGENTS

Radio Press are preparing a complete list of blue prints. Send a post-card if you have received enquiries.



## The "Transatlantic Five"—A Multi-Valve Set with Range and Volume

By PERCY W. HARRIS, Assistant Editor.

*This Receiver is a modification of the original "Transatlantic" design, and includes the Note Magnifiers on the same panel.*

**I**N November last, following a large number of requests for such a set, I described in these pages a three-valve wireless receiver containing two stages of high-frequency and a detector valve. The set in question, as many readers will remember, was designed to use the tubular types of valve known as the V. 24 and Q.X., whilst the tuning of the two stages of high-frequency—always rather a difficult matter—was simplified by the use of a double condenser. Largely owing to the fact that up to this time no simple set with two stages of high-frequency had been described for home construction, the "Transatlantic" receiver, as it was called, was built in large numbers, and I am pleased to know excellent results have been obtained with it in all parts of the country. In the following month (December) I described a two-valve amplifier

which could be attached to the "Transatlantic" as making with the previous unit a five-valve receiver of high efficiency.


The design of a good set with two stages of high-frequency is not a particularly simple matter, owing to the fact that unless we take great precautions there will be interaction between the stages of tuned high-frequency, and self oscillation will be set up on the slightest provocation. It was in order to reduce the interstage coupling to the lowest limit that the tubular low capacity type of valve was used. Incidentally, it may be remarked that the new Myers valves work admirably in the Transatlantic set. Many readers, however, have asked whether it is possible to make up the set with the ordinary four pin valves which are more readily obtainable and, incidentally, are only half the price of the V.24 and Q.X. Further,

the very low consumption dull emitters are only obtainable in the four-pin type, and many people are so situated that such valves are highly useful to them.

The present set is a re-designed "Transatlantic" receiver with a number of improvements which have suggested themselves since last November. I have found it possible, by taking certain precautions which will be explained later in the article, to utilise the four-pin valve in this set, thus giving the reader a very wide choice in the valves he may use.

Let us examine first of all the particular features of the present set, to see wherein it resembles, and in what it differs from, the original Transatlantic design. Here are the chief features tabulated:—

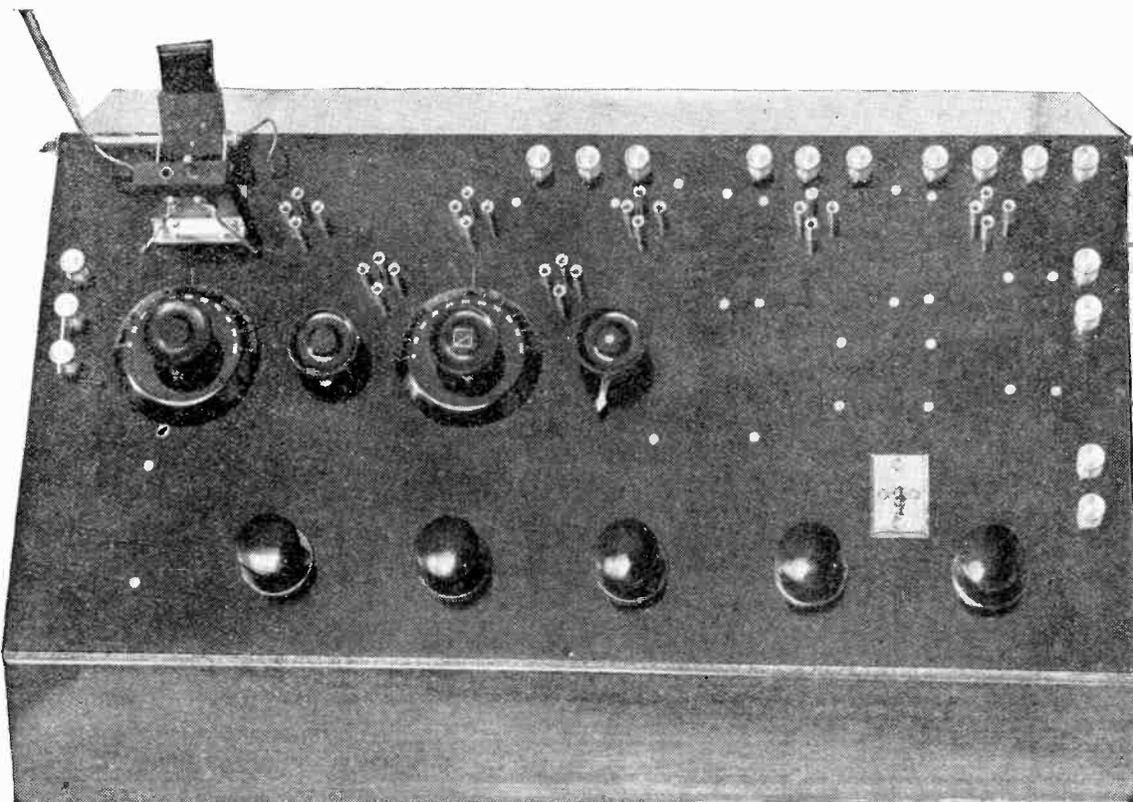1. Four-pin valves are used throughout in low capacity mountings.
2. Double filament resistances



*Reaction on to the aerial coil is rarely needed, as sufficient reaction control is generally obtainable on the potentiometer. If, however, with very poor aerials magnetic reaction is found necessary, the shorting plug in the reaction socket is replaced by a small coil.*

are used to enable the reader to use bright or dull emitters in any of the sockets.

3. An original form of switching is incorporated so that in one position we may listen on three valves (two high-frequency and a detector) in the telephones, whilst in the other position of the switch we listen on five valves (two high-frequency, detector and two note magnifiers) on the loud-speaker. Telephones and loud-speakers are kept permanently connected to their respective terminals so that having tuned-in in comfort on the telephones we can change in a moment to the loud-speaker without touching any leads. The switch also controls the lighting of the filaments of the last two valves.

4. Terminals are provided so that four volts I.T. can be used on the first three valves (for dull emitters) and six volts on the last two valves (for power valves or bright emitters), using one accumulator throughout.

5. Four high-tension terminals are provided, giving us an opportunity to use one voltage of high tension on the first three valves, a different voltage on the first note-

magnifying valve, and a still higher voltage on the last valve. Thus power valves may be used in the last two sockets.

6. Separate grid bias terminals are provided for each of the two stages of note magnifying so that we can adjust the particular valves used to the best working positions.

7. Resistance capacity coupling is adopted for the note magnifying stages.

This form of coupling has come into prominence in the last few months owing to the fact that for telephony it gives remarkable purity. There are arguments both for and against resistance coupling. In the main they are as follows.


*For* :—Great purity is obtainable—a purity only equalled by the best of intervalve transformers correctly used. The cost of the coupling is low so that, excluding valves, we may say roughly that the two stage resistance amplifier costs no more than a single stage transformer amplifier. There is much less risk of interaction between stages and consequent howling.

*Against* :—The amplification per valve is not so great as with transformer coupling. The differ-

ence may be roughly stated to be that with three stages of resistance amplification no greater magnification is obtainable than would be possible with two stages of transformer amplification.

About 50 per cent. higher plate voltage is required with resistance coupling.

One of the reasons for choosing resistance coupling in the present receiver was that experience with the original Transatlantic set and its two note magnifiers showed that only very rarely indeed was it necessary to use the second stage of note magnification to bring in practically any station on the loud-speaker. Furthermore, many readers have commented on the remarkable purity of signals obtainable with the original Transatlantic, and it was thought that there would be less difficulty for many to retain this purity when amplifying if resistance coupling were used. Others, however, may desire to use transformer amplification in the present set, and provided they are satisfied with the transformers they are at present using there is no reason why they should not give just as good results.

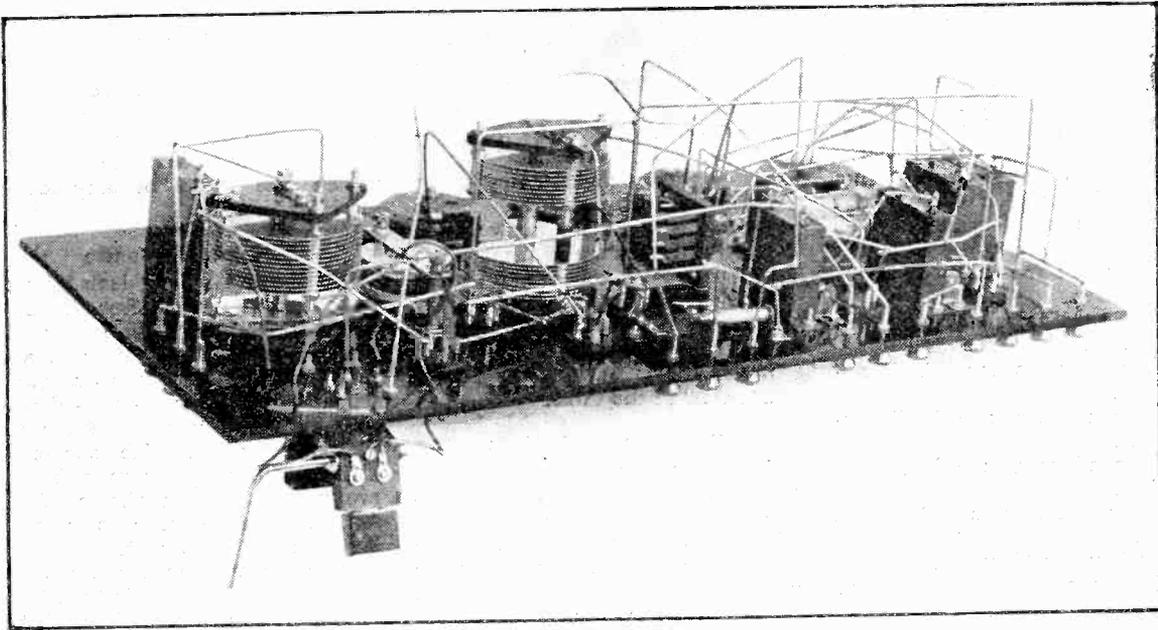

This photograph shows how the various components stand in relation to one another.

#### What Cannot be Done with This Set

It should be pointed out at once that the man who wants a set with every possible switching combination and who desires to perform "stunts" with his receiver will not find the present apparatus to his liking. As I have pointed out on many occasions, efficiency in high-frequency stages is very largely dependent upon the shortest and most careful wiring. If we were to introduce a switch so that either one or two stages of high-frequency could be used, not only would the wiring be complicated, but the efficiency would drop quite a considerable degree. In any case, it will be found for local work that on switching off one or both of the high-frequency valve filaments sufficient energy will get through to the detector valve to give good signals. It will also be noticed that we are bound to use both of the stages of note magnification or none at all. Again, there are reasons for this. Two stages of high-frequency amplification and a detector valve will bring in practically anything in comfortable telephonic strength, particularly when reaction is carefully controlled. Amplification added to this by the two stages of note magnification will work the loud-speaker. In the great majority of cases it will be found that one stage of note magnification will give signals too strong to be comfortable in the telephones, but not quite strong enough to work a loud-speaker. Last, but not least, if all kinds of change-over arrange-

ments are desired, it is far better to lay out the apparatus on an experimental bench, so that every possible arrangement can be tried. The present instrument is designed to give good reliable results *all the time and every time* with the minimum of adjustment and trouble. I do not think it will be found to fail in this respect.

#### General Arrangement

The whole of the apparatus is mounted on a single ebonite panel measuring 22 in. by 11 in. The actual instrument described uses a sloping front cabinet of conventional design, but many readers will desire to build the panel into a bureau or some special box. The fact that everything is mounted on a panel makes it quite a simple matter to fit it in any convenient position either vertically or horizontally. Many readers may think the construction of a five-valve set of this type is both an ambitious and an expensive proceeding. It will be found, however, that if the set is built up from components of good quality throughout, using a bought french-polished mahogany cabinet of the correct size, the total cost will not exceed £12, excluding, of course, valves and batteries, telephones and loud-speaker. This figure is not high when it is considered what can be done with the receiver.

#### Components Required

The list of components is given below. In accordance with the usual practice in this magazine,

the actual make used by the author is given in brackets, but of course any similar component of good quality may be utilised.

The use of square law condensers is recommended in this set, for they greatly facilitate the calibration of the instrument and, furthermore, give much greater ease in tuning. The ordinary type of condenser has a congestion of wavelengths in the first portion of the scale, and the reverse at the upper end. In a square law condenser the wavelengths are equally distributed throughout the whole scale. This means that if we plot a "curve" with wavelengths on a vertical scale and condenser degrees on a horizontal scale, then the line joining the points of intersection of the different condenser readings and the different wavelengths corresponding will be straight. In practice the effect of this is that if we pick up any two different stations, the wavelengths of which we know, then the two points of the chart can be joined with a ruler and the line extended right across the chart. We can then find the position of any other wavelengths by noticing the points of intersection. Those readers who desire to use the ordinary form of condenser will not find the signal strength any different. The sole and very important difference between the two forms of condenser lies in the explanation given above.

We need, then:—

- 1 variable condenser, .0005  $\mu\text{F}$  (Bowyer-Lowe square law).
- 1 double condenser, the two halves

of which are each .0003  $\mu$ F. (Bowyer-Lowe square law). NOTE.—Experience with the instrument has shown me that the two halves of .0002  $\mu$ F. would be quite big enough for the broadcast band of wavelengths, as if the set is made exactly as described it will be found that the plug-in transformers rated as from 300 to 600 metres will actually run from 235 to about 750 metres.

- 2 fixed condensers, .0003  $\mu$ F. (Dubilier).
  - 3 fixed condensers, .25  $\mu$ F. (Mansbridge).
  - 1 fixed condenser, 1  $\mu$ F. (Mansbridge).
  - 1 fixed condenser, 2  $\mu$ F. (Mansbridge).
  - 5 filament resistances (Burndept dual).
  - 1 potentiometer (Igranic).
  - 3 grid leaks, 2 megohms (Dubilier).
  - 14 terminals, 4 B.A.
  - 7 sets of valve sockets. (See note below.)
  - 1 two-coil holder (Burne-Jones Magnum).
- Matched plug-in H.F. transformers. (I have several makes of these at hand, and have used McMichael, Bowyer-Lowe and Ediswan, which are all good. Gent's also make this type.)
- 1 4-pole double-throw anticapacity switch (Utility).
  - 2 80,000 ohm anode resistances (Dubilier large type).
  - 3 sets of grid leak clips.
  - 1 panel-mounting on-and-off switch (Connecticut).

Ebonite panel, 11 in. by 22 in. by  $\frac{1}{4}$  in.

Suitable cabinet (that shown was made by Wright and Palmer).

Quantity of No. 16 square tinned-copper bus-bar wire (this is sold by a number of firms, including Sparks Radio and Bowyer-Lowe).

Suitable plug-in coils for the ranges it is desired to receive. Those readers who do not know which coils to buy should consult the MODERN WIRELESS coil table published in our last issue. Only one set of coils will be needed, those required being indicated under the heading "Aerial Socket" in the table.


**Constructional Work**

I have endeavoured to make the constructional work as simple as possible, and it will be found that with the solitary exception of the hole in the panel necessary for the particular type of on and off switch everything else can be mounted by means of ordinary drilled holes. Fortunately, the manufacturers are gradually adopting the wise policy of supplying with the component parts suitable drilling templates. Thus, the condensers, double filament resistances, and the potentiometer are all provided with paper drilling templates. Blue prints are available for both front and back of this receiver, so that the laying out of parts will not be found at all difficult. The largest drill required will be  $\frac{3}{8}$  in. diameter for the central spindle of the condensers, filament resistances and potentiometer, as well as the hole for the single hole mounting Utility switch. I hope the Igranic Com-

pany will forgive me for changing the knob of their potentiometer. The reason for this was that it did not match the knob of the Utility switch, which is a standard knob, whereas the Igranic use a special knob of their own which does not match the knob of any other manufacturer.

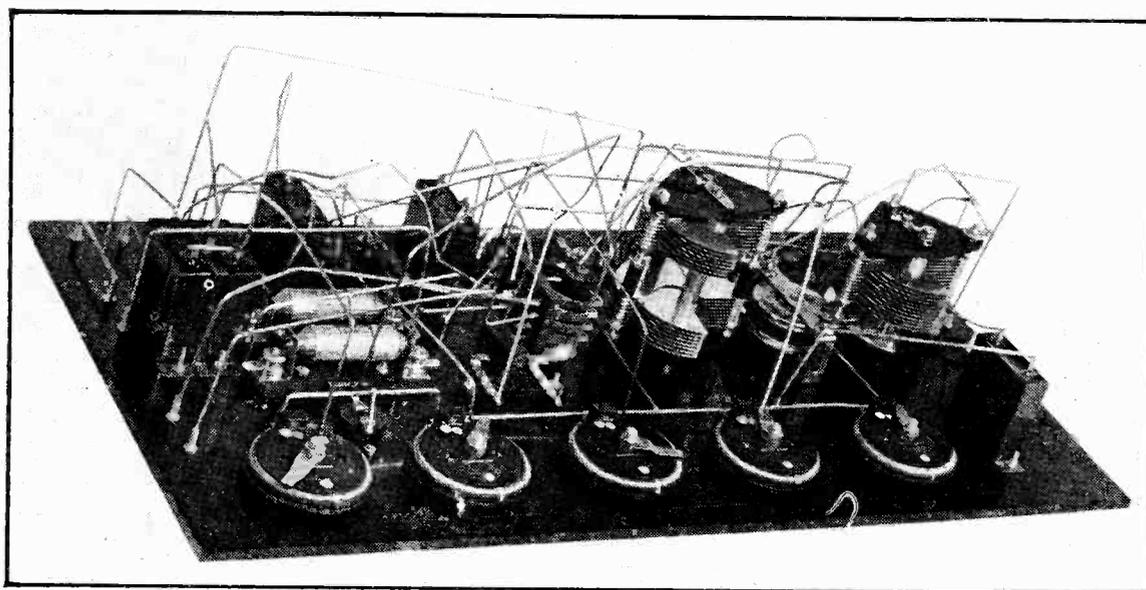**A Note on Ebonite**

We are still in the dark ages as far as ebonite is concerned. This material varies enormously in quality, and in the main is still manufactured in a manner which, whilst satisfactory for pre-wireless uses, is quite unsuitable for the present purpose. The sheets of ebonite during their manufacture are rolled between sheets of tin foil. As the ebonite is a combination of rubber with sulphur this latter substance attacks the tin foil and the result is that there remains upon the surface of the ebonite an invisible compound of tin foil and sulphur which is more or less of a conductor. If then we mount our component parts on the ebonite as bought there will be a great deal of surface leakage, and we may lose all our signals, or at least part of them, and hear at the same time a very disagreeable frying noise. It is for this reason that I always recommend readers to remove the surface of the ebonite with emery paper, rubbing carefully so as to give a good matt surface. There is no virtue in a matt surface as such, and if only the manufacturers would make the ebonite in such a way as to avoid surface leakage, then we could use it with



Another helpful view showing the five resistances controlling the filament current.


its original polished surface. In the United States, such highly polished panels entirely free from surface leakage are available at any dealers. In this country practically all the ebonite sold has a leaky surface. There are, however, some kinds of ebonite available which are guaranteed free from surface leakage. Unless you can obtain such a guarantee with your ebonite remove the surface with emery paper.

At first glance the wiring of the set looks a very complex matter, but further examination will show that the complexity is entirely confined to the audio-frequency side, the wiring of the radio-frequency side being exceedingly

( $\mu\text{F.}$ ), but a spare  $.25\mu\text{F.}$  was handy and was accordingly used. The size is not a critical matter and any condenser of a capacity of .001 or larger will do. Indeed, if it was omitted no great difference would be noticed.

The Connecticut on and off switch will require a 1 in. hole in the panel. This can be cut either with a fretsaw or by scribing a circle of 1 in. diameter, and drilling a number of holes round the circumference until the centre piece drops out. The hole can then be smoothed off with a file. This particular switch will carry if necessary 10 amperes, and as we may desire to use bright emitters throughout this set which may

most detrimental in high-frequency amplification. In the present receiver I used separate valve legs which are attached to the panel without nuts or washers. This is done by drilling clearance holes with a template for the four valve pins and screwing them into ebonite discs on the opposite side of the panel, these discs being threaded with holes to take the pins. Just as good results can be obtained, however, by threading holes instead of making clearance holes for the valve pins in the panel. If then the separate legs are screwed into the threaded holes (4 B.A.) we can dispense with nuts and washers, which all add to the capacity. The valve legs used should not

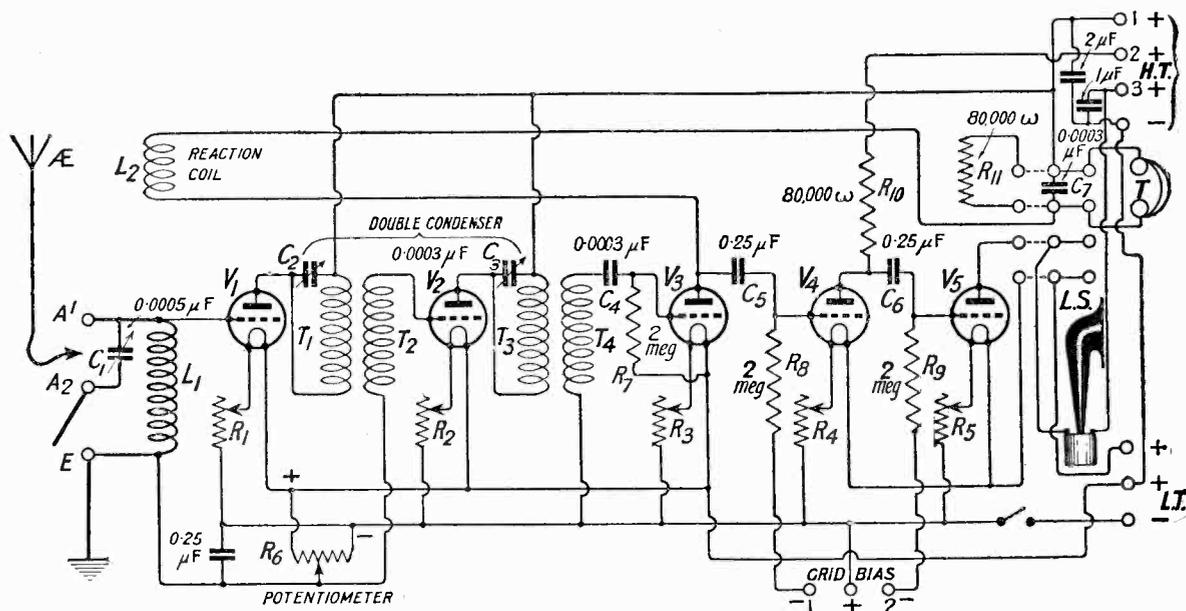

The theoretical diagram. The twelve white dots near  $R_{11}$  and  $C_7$  represent the switch contacts. The blades are shown as full lines on the right. They can be changed over to the dotted positions on the left.

simple. Be sure in wiring up to make your leads as short as possible on the high-frequency side. The complication on the audio-frequency half is due to the introduction of four-pole two-way switch. Those readers who find it difficult to use square wire and to bend it accurately on this part of the receiver may care to use the thinner tinned copper wire and insulating sleeving. This, however, should not be used on the radio-frequency side, but only after the detector.

Some readers may wonder what is the object of the  $.25\mu\text{F.}$  condenser on the radio-frequency side of the instrument. This is slanted across the active portion of the potentiometer so that the radio-frequency currents do not pass through any inductive windings here. A much smaller condenser would have done here (say .001

average over half an ampere each, it will be seen that a switch with good current carrying capacity is required. I do not recommend the use of a cheap switch here. In any case the Connecticut is not dear.

The Dubilier anode resistances are supplied complete with clips mounted on an ebonite strip. This ebonite strip has two holes so that it can be attached to a panel with ordinary metal screws and nuts. I do not recommend the reader to take the clips off the ebonite strip to which they are attached. The whole strip should be mounted on the underside of the panel.


**Special Note on Valve Sockets**

In this instrument the ordinary ebonite sheathed valve socket should not be used. These sockets have a very large capacity between pins, and this is a capacity which is

have flanges and should be as thin as possible, as it is upon small details such as this that the efficiency of a high-frequency set depends. Do not therefore use the conventional composition or ebonite sheath valve socket and expect to get the same results. There are already several good low capacity valve sockets on the market, and in the future I think there will be more, when the importance of low capacity in valve sockets is fully realised.

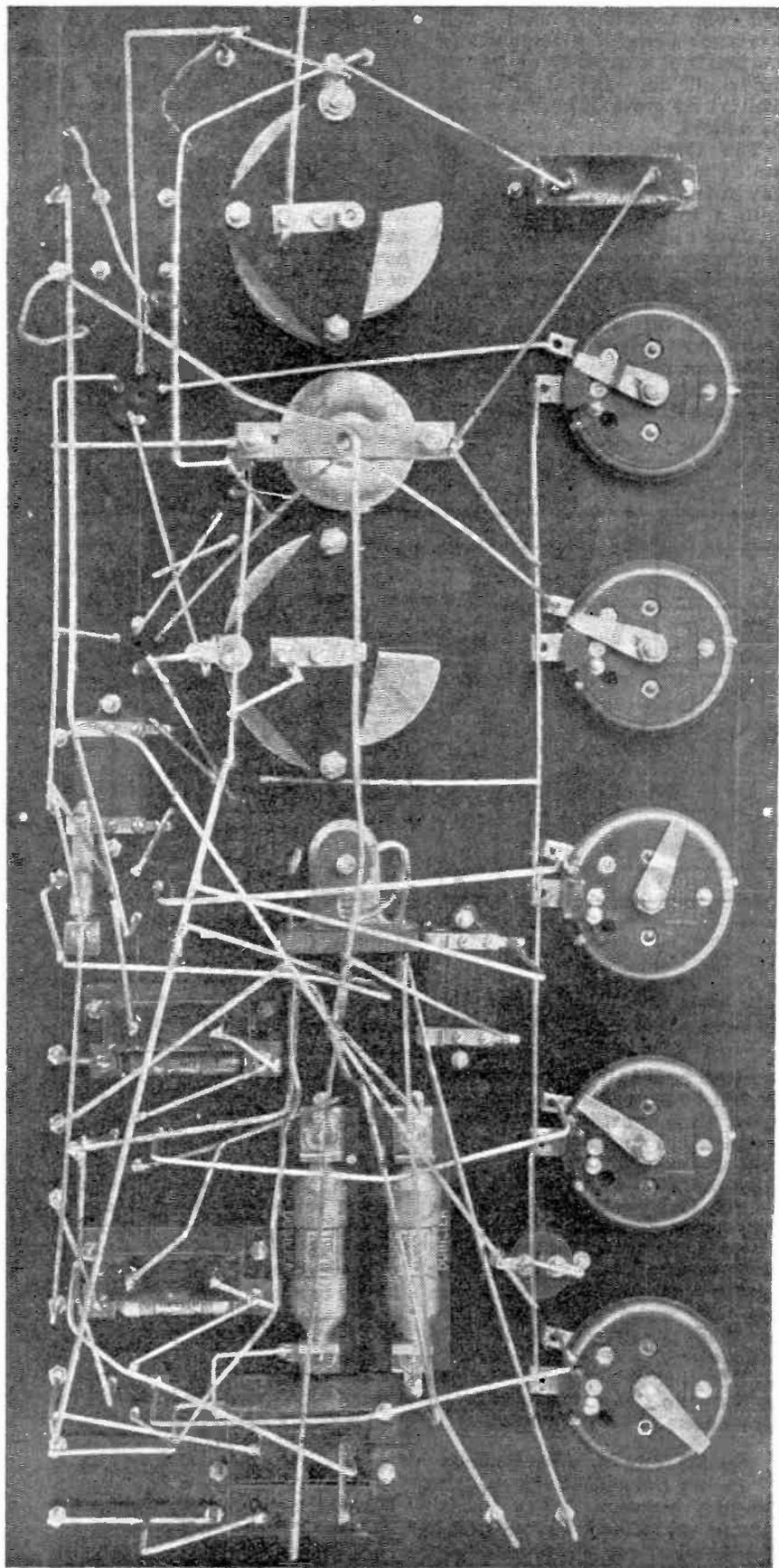**Wiring Up**

When all the components have been mounted remove the tops of all brass screws and points that have to be soldered with a fine smooth file, and carefully tin each point before the wiring up is commenced. Wiring up with stiff wire is quite a simple matter when you get the



*Looking from above, the wiring is not difficult to follow*

knack of it, and success largely depends upon bending each piece of wire to its shape before attempting to solder it. If you try to bend the wire after you have soldered one end you will find that it will probably break off the soldered connection. In wiring up follow the diagram carefully and see that each piece of wire is clear of any other where it crosses. I admit that the wiring up of the switch is not so easy as the other parts, but it is worth taking a little trouble with. Do not attempt to "rush" your wiring in an endeavour to get the set finished rapidly. Go steadily with the work and you will find that the extra pains will well be repaid.

The enquiring reader may wonder why the grid leak of the detector circuit is not placed directly across the .0003  $\mu\text{F}$  condenser as it is transformer coupling. The reason for this is that later the reader may desire to use resistance coupling on the high-frequency side for longer waves, and if the leak is wired up as shown it will be possible to use the plug-in resistance capacity units recently described in these pages for use with the original Transatlantic design.


**Some Special Points**

With the particular form of coil holder used it is necessary to bring flexible leads from the front of the panel to the back. Long flexible leads are always a nuisance and to avoid any trouble in this regard I have introduced into the panel two 6-B.A. metal screws secured with nuts. To these screws are soldered the leads which normally would go to the reaction coil. This secures the stiff wires firmly in place. The flexible wires in front of the panel are now brought through and soldered to the stiff wires at the back thus enabling the shortest possible flexible leads to be used.

It will be noticed that there are two large condensers across the high tension. It might be thought that only one would be necessary. The reason for using two is that in using different high tension tappings it is impossible to make one condenser serve for all. We therefore have a 2  $\mu\text{F}$  condenser shunted across the high-tension battery which supplies the first three valves and 1  $\mu\text{F}$  shunted across the portion of the battery which supplies the last valve. It has not been found necessary to add one across the second high-tension tapping.

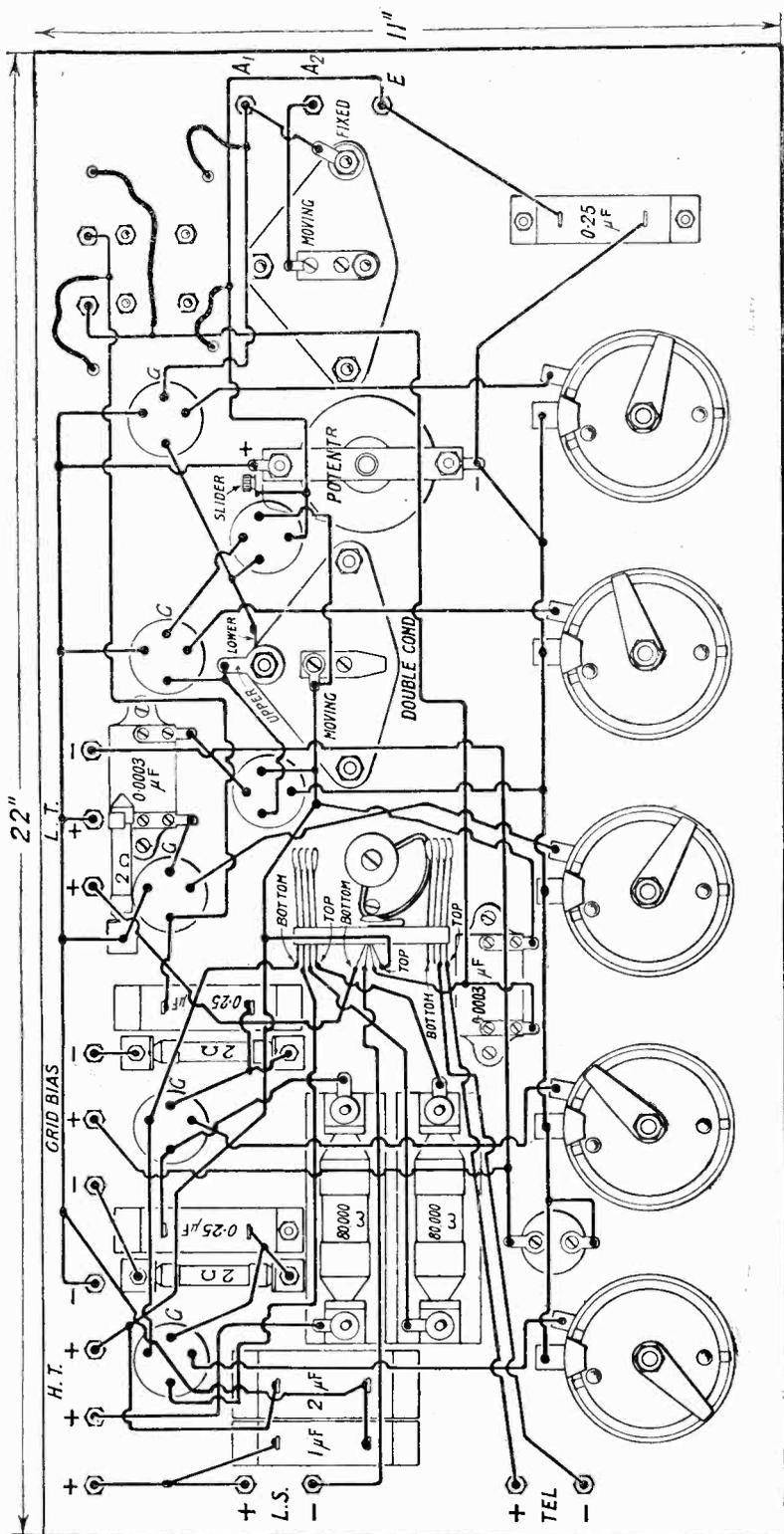**Note on the Switch**

The appearance of the wiring to the switch may at first confuse



Complete wiring diagram. A full-sized blue print of this is available. (Ask for No. 43B).

drawing I have marked top and bottom for each of the rows. "Top" in this case is the uppermost lug when the panel is laid face downwards on the table. The moving portions of the switch are not drawn in detail and therefore the reader is not advised to pay too much attention to them. If this part of the switch had been drawn very fully it would have given more complication to the drawing without elucidating any points.

**Testing and Joining Up**

When the set is finished and you have carefully tested it to see that all leads are free of one another place the panel in its cabinet and examine the front. You will see on the left hand side of the front panel drawing three terminals marked respectively A<sub>1</sub>, A<sub>2</sub> and E. These are to enable you to use the aerial tuning condenser either in series or in parallel. Parallel connection is recommended in most cases save where the aerial is extremely large or where it is desired to receive very short wavelengths. For parallel join A<sub>2</sub> and E with a link or piece of wire, joining aerial to A<sub>1</sub>, and earth to E. For series connection open up the link, join aerial to A<sub>2</sub>, leaving earth as before. The condenser will now be in series. You will also see that there are three terminals for the low-tension, marked negative (common), positive (valves 1, 2, and 3) and positive (valves 4 and 5). The reason for having the terminals so marked is that many readers may desire, from the point of view of current economy, to use dull emitters in some parts of the circuit if not everywhere. You may, for example, use three .05 ampere valves in the first three sockets for high-frequency and detecting. To operate these valves you require only 4 volts from an accumulator or dry cells. To get really loud and powerful signals when using the note magnifying stages it is often desirable to use bright emitters or even power valves. These with the filament resistances supplied will require 6 volts. Say, for example, we put three dull emitters in the first socket, say an R valve in the first note magnifying socket, and an L.S.<sub>5</sub> power valve in the last socket. We can now use a 6 volt accumulator of say 40 ampere hour capacity, joining the negative to the common negative terminal, taking a tapping from 4 volts to the positive for the first three valves and the 6 volt terminal to the

the new constructor, but if the diagram is carefully examined it will be found a comparatively easy matter to wire up. The switch in question is sold for panel

mounting in the one hole fixing manner. There is a vertical plate on the switch carrying twelve projecting soldering lugs, already tinned for soldering. On the

positive terminal for the last two valves. We shall then get 4 volts on the first three and 6 on the last two. If, however, we desire to use bright emitters throughout then the two positive L.T. terminals can be joined by a wire and taken to the 6 volt terminal of the accumulator. The filament resistances of the dual type are so arranged that when we turn the knob clockwise we first of all run over a sector of the resistance of a wire of suitable size to cut down the voltage on the dull emitters. We then pass on to a section of thicker wire which will pass enough current to the bright emitters. Therefore, when using dull emitters the first half of the resistance is used and with bright emitters the second half.

**High Tension Terminals**

There are four terminals for the high tension. The first is negative (marked common) the second is

use a power valve, we may desire to use as high as 200 volts, whereupon we shall take the tapplings from the correct socket for this. If we are using ordinary bright emitters throughout, say 5 valves of the "R" type, then we can use say 70 volts for the first three and 100 for the last two, in this case the last two terminals being joined together by a wire and taken to the 100 volt tapping. It would, of course, be an added refinement to add a separate tapping for the detector valve, but in practice we must stop somewhere in complications, and it was not found necessary to add this terminal.


**Grid Bias**

Three terminals are provided, as will be seen, for grid bias. The centre terminal is the positive from the grid bias battery. This may be one of the ordinary tapped high tension batteries if power valves are used. Let us imagine

for the last valve. If of course we use the same type of valve in the last two sockets with the same high tension, then the two negatives can be linked by a wire and taken down to the tapping which happens to suit.

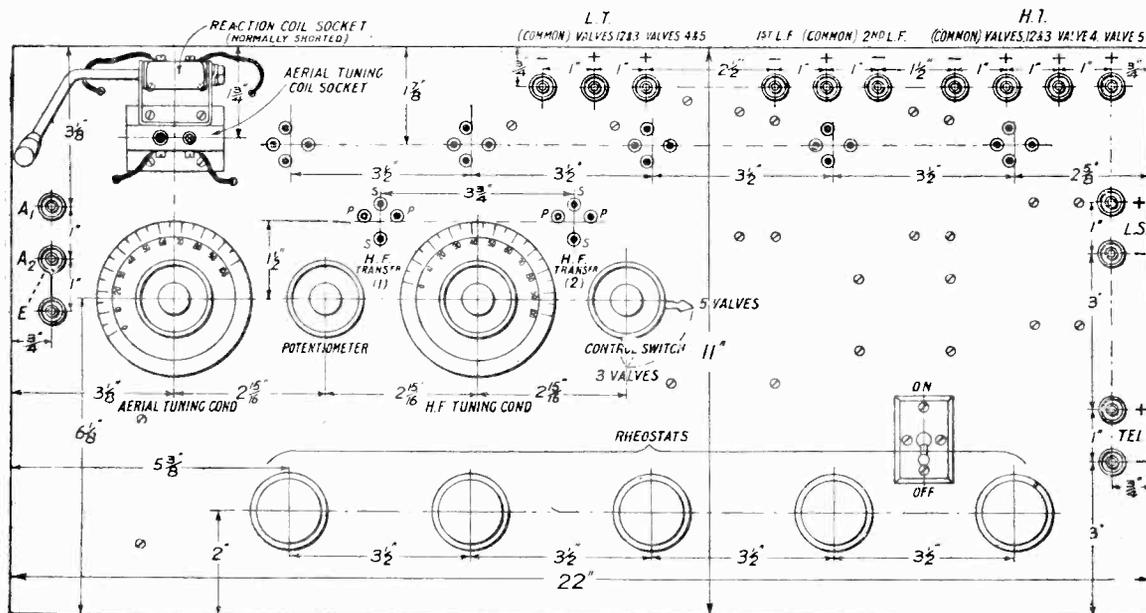**Starting Up**

When you have thoroughly mastered the terminal arrangements you can place a short-circuiting plug into the reaction coil socket (you will rarely need to use reaction with this set) and you can place in the aerial tuning coil socket a suitable coil for your local broadcast station. Turn the switch to the 3-valve position, turn off your filament resistances all along, turn on the filament switch and then light each of the first three valves by turning the filament resistances to the right until the correct degree of brightness is obtained for the valves you are using. The potentiometer should now be turned anti-clockwise as far as it will go. Now plug into the transformer sockets a pair of matched transformers to cover the wave-length range you desire, and turn the high-frequency tuning condenser to about the halfway position. Now on the aerial tuning condenser turn this backwards and forwards until you hear your local station at the best strength, whereupon you can further increase the strength by moving the high-frequency tuning condenser to its best position—which will be readily found. If you are fairly close to



A full-sized blue-print of this panel is available (No. 43A).

the positive for the first three valves, the third the positive for the first note magnifying valve and the last the positive for the final valve. These are used as follows. If, for example, we desire to use .05 ampere valves in the first three sockets we take a tapped high tension battery and join its negative to the common negative terminal. We then take a tapping at 40 volts (say) to the first positive terminal. We will perhaps use an ordinary bright emitter "R" valve in the first note magnifying stage. We can then take for this a tapping at say 70 or 80 volts. Finally, if we

we have a tapped battery of say 30 volts. The positive end is connected to the middle positive terminal. If we are using say 100 volts on an "R" valve in the first note magnifying socket, then about 4 volts grid bias will probably suit. To obtain this we take a tapping at 4 or 4½ volts and connect this to the negative terminal marked "first L.F." valve. If we are using say 200 volts on an L.S.5 for the last valve, then we shall require about 16 volts grid bias, to obtain which we take a tapping at 16 volts (or the nearest voltage to this) to the grid bias negative terminal marked

meter should now be turned anti-clockwise as far as it will go. Now plug into the transformer sockets a pair of matched transformers to cover the wave-length range you desire, and turn the high-frequency tuning condenser to about the halfway position. Now on the aerial tuning condenser turn this backwards and forwards until you hear your local station at the best strength, whereupon you can further increase the strength by moving the high-frequency tuning condenser to its best position—which will be readily found. If you are fairly close to

(Continued on page 74.)

# High-Tensionless Receivers

By JOHN SCOTT-TAGGART, F.Inst.P., A.M.I.E.E.

Author of "Thermionic Tubes in Radio Telegraphy and Telephony," "Elementary Textbook on Wireless Vacuum Tubes," "Wireless Valves Simply Explained," "Radio Valves and How to Use Them," "Practical Wireless Valve Circuits," "More Practical Valve Circuits," etc., etc.

This article reviews the whole position of the possibility of eliminating the high-tension battery, and numerous new circuits are given for this purpose.

A GREAT deal of interest has been aroused recently by the publication of accounts in the general Press suggesting that high-tension batteries are now things of the past, and that we might expect the whole technique of radio to change.

After allowing for the enthusiastic extravagance which usually attaches to Press reports when dealing with technical subjects, there is sufficient basis for an investigation into the matter from a dispassionate point of view.

At first sight the words "No More High-tension Batteries," "Amazing Invention," "Revolutionary Development," etc., might not only cause manufacturers to shake in their shoes, but also create some concern to experimenters and constructors. As for the high-tension battery manufacturers, one's sympathies are only tempered by recollecting their astonishing lack of enterprise.

I think it is desirable to calm the fears of those interested by rashly prophesying that the high-tension battery industry will not be

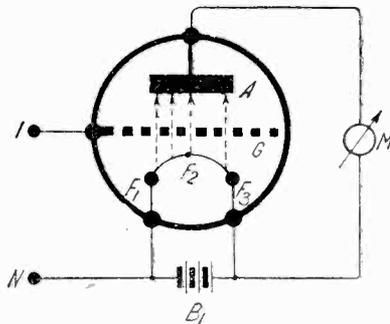


Fig. 1.—How the filament battery acts as an H.T. battery.

abolished, and that radio technique will not undergo a revolutionary change.

It would be as well, before discussing the technical prospects, to examine the fundamental question of whether the high-tension battery may be eliminated.

Messrs. G. V. Dowding and K. D. Rogers have not confined them-

selves to their own interesting example of a high-tensionless receiver, but have made such sweeping statements that they invite friendly correction.

They state that, "according to the accepted theory of wireless

The object of a high-tension battery in a wireless receiver is fundamentally to draw electrons, which are shot off from the filament of a valve, to an anode, and produce what is called the anode current. The strength of the anode current affects the signal strength obtained with a receiver, or, rather, the variation of the anode current affects the signal strength. If there is a small anode current and an incoming signal varies it between zero and maximum, a certain signal strength will be obtained. If, now, we increase the anode current and also vary it between zero and maximum, the signal strength will increase. It is, of course, not possible to obtain something out of nothing, and the same applies to wireless valves. We cannot obtain signals unless we have an anode current of varying amplitude. If the total current flowing through a valve is only a small fraction of a milliampere, it is theoretically, and practically, impossible to get adequate signal strength. The average current flowing in the anode circuit of a valve may be said to be modulated

## The Article in Brief.

The following conclusions are arrived at by the author of this article—

- 1.—That high-tensionless receivers are not new in themselves. Fullest results are given of his own work, for which no particular credit is claimed, but which indicates the successful results obtained without a high-tension. References to publications three years old are given.
- 2.—That present design will not undergo modification as a result of the interesting circuit developed by various investigators, but that these circuits form an addition to the already innumerable circuits available to the experimenter.
- 3.—That, in his opinion, the high-tension battery circuits will give better results than one using no high-tension battery, and that after the first valve the disparity becomes greater and greater with the addition of every extra valve.
- 4.—That high-tensionless circuits are of chief interest in the case of portable sets.
- 5.—That, in his opinion, standard broadcast apparatus will not be modified and that there is nothing to justify any alteration.
- 6.—That any existing sets, commercial or otherwise, may be converted to high-tensionless receivers at the expense of signal strength. Suggestions are given.
- 7.—That, ultimately, the interest which has been shown in high-tensionless receivers may lead valve manufacturers to design valves requiring a smaller amount of high-tension voltage.
- 8.—That the expression "high-tensionless" is really a misnomer because some high-tension voltage is essential for the proper working of a valve, although this voltage may come from the filament battery. The problem of reducing the value of the high-tension voltage is exactly the same as the problem of the so-called elimination of the high-tension battery.
- 9.—That high-tension batteries will not be abolished.

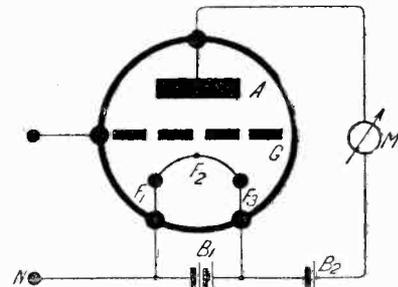


Fig. 2.—The previous circuit re-arranged.

reception," the elimination of the high-tension battery is impossible. The fact that wireless receivers without high-tension batteries have in the past been employed is probably the best reply to this, but nevertheless there are certain fundamental facts in connection with valves which no invention, however amazing, can confound.

by the potentials applied to the grid. When the grid is made positive the anode current increases, and when the grid is made negative the anode current decreases.

To establish the normal anode current it is necessary to give the anode a substantial voltage. To produce an average current of,

say, 3 milliamperes, it may be necessary to have 100 volts on the anode of the valve. Positive impulses on the grid, if sufficiently large, may increase this average current momentarily to 6 milliamperes, while negative impulses on the grid might reduce it to zero. Such variations would produce very loud results in a loud-speaker. If the steady anode

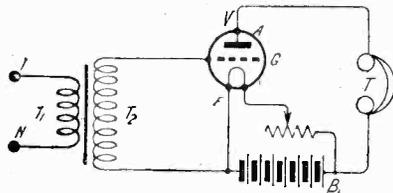


Fig. 3.—An L. F. Amplifier circuit without H.T.

current were much smaller, by using a lower anode voltage, for example, the maximum output obtainable would naturally be smaller.

It is therefore essential to have some anode voltage to produce a real flow of electrons from the filament to the anode, although the amount of this voltage will depend upon the type of valve used.

The question naturally arises, "Why is a large anode voltage necessary?" The reason, briefly, is that the resistance of the valve is so high, or, to use a better expression—since we shall be dealing with fluctuations of current—the impedance of the valve is so great. If we reduce the impedance of the valve, we shall be able to use a

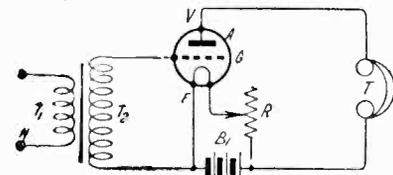


Fig. 4.—An arrangement for ordinary valves.

much lower anode voltage. The resistance, or impedance, of a valve is due, not to the fact that there is a vacuum, but to an effect due to what is termed the "space-charge." A vacuum is an ideal medium for the passage of electrons from the filament to the anode, and we might therefore at first think that a very low anode voltage would be sufficient to draw up a large number of electrons shot off from the filament. To explain why this is not so we must examine closely the effect of a space-charge.

When a stream of electrons is flowing from the filament to the anode the space between these two electrodes is filled with a cloud of negative particles of electricity.

This cloud acts exactly in the same way as any other negative charge, except that, instead of the charge being on a body, it is a charge in space, and it is therefore called a space-charge. This space-charge, since it possesses the properties of any other negative charge, will tend to repel the electrons emitted from the filament.

Now the number of electrons emitted by the filament depends solely, in the case of a given valve, on the temperature of the filament. Except by altering the temperature of the filament, we cannot alter the number of electrons given off per second, but we can alter the number of electrons which pass to the anode. When an electron is shot off from the filament on account of the internal vibrations in the filament, two influences affect it. One influence is the electrostatic

force of the space-charge, while others come out of the filament at a relatively low speed and are unable to overcome the repulsion of the space-charge. The effect of the space-charge varies at different distances from the filament; close to the filament the space-charge repulsion on a newly emitted electron is greatest. Moreover, near the filament the attractive force of the anode is weakest. The newly emitted electron experiences a strong repulsion from the negative charge very close to it, and an attraction, due to a larger positive charge at the anode, which is situated, however, at a very much greater distance from it. Under ordinary conditions, the slower moving electrons find the repulsion of the space-charge greater than the attraction of the anode, and they are consequently

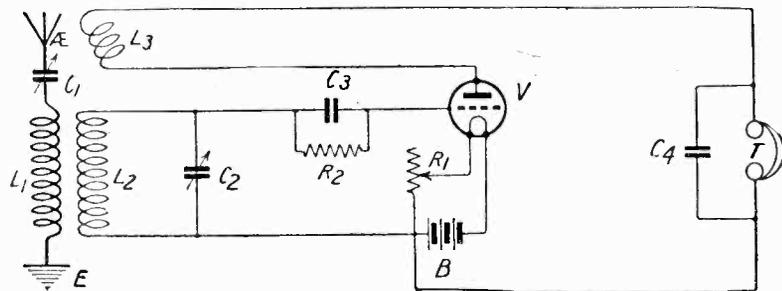


Fig. 5.—An arrangement introduced by the General Electric Co. of America.

field produced by the anode; the anode being positive with respect to the filament, the electron, which is a negative charge, tends to move from the filament to the anode according to the ordinary laws of electricity. The other force is one due to the repulsion exercised by the mass of electrons which exist between the newly emitted electron and the anode. The large total negative charge in the space between the filament and anode, due to the electrons on their way to the anode, makes it difficult for the newly emitted electrons to emerge from the neighbourhood of the filament and to join in the main stream to the anode. The electron does one of two things; it either goes back again to the filament, or joins in the main stream to the anode. When the anode voltage is small the majority of electrons remain near the filament, but as the anode voltage is increased more of them pass to the anode.

The reason for this is that the electrons are not all emitted from the filament at the same speed; some of them are shot off at high speed and travel a further distance than others, in spite of the repul-

made to return again to the filament. Speedier electrons, however, are shot out a further distance, since their additional speed enables them to penetrate the heavy space-charge cloud surrounding the filament and to enter a zone where the attractive force of the anode is greater than the repulsion exercised by the space-charge. Once they get through this cloud they are all right, and they are able to proceed to the anode.

This is so for two reasons; firstly, they approach the anode and so come under its attractive influence more; and secondly, once they have proceeded some distance towards the anode they are helped on their way by the negative space-charge behind them, which tends to push them on towards the anode; moreover, the space-charge ahead of them gradually gets weaker and weaker. It is almost as though the electron were like a person travelling to a certain place through a thick fog, which is very thick at first but gradually gets clearer. Once he is out of the heaviest part of the fog he can proceed on his way.

Another comparison which may

help the reader a little is one which considers a rifle bullet being fired through a thick plank of wood at a target ahead. If the bullet is shot from the gun at a slow velocity it will not pass through the wood. If, however, the bullet leaves the gun at a high speed it will pass through the wooden plank, and, once through, will pass on and hit the target. The gun may be compared to the filament, the wooden plank to the space-charge and the target to the anode of the valve.

These comparisons, of course, do

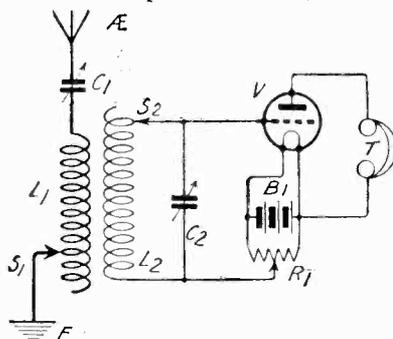


Fig. 6.—The successful 1918 high-tensionless circuit.

not show the whole picture, but they may be of assistance.

If we desire to obtain a substantial anode current with a low anode voltage, we have to reduce the space-charge effect. The ordinary way of overcoming the space-charge effect is to increase the high-tension voltage, but since we are assuming that we are to use a very low anode voltage, we must adopt some means of reducing the space-charge. One method of doing this is to reduce the diameter of the anode and grid, but mechanical considerations limit the size of the anode, because in any case the grid has to come between the filament and the anode if the normal construction of the valve is adhered to. It might be mentioned here, incidentally, that this defect has been overcome by having the grid in the form of a flat plate on one side of the filament, and the anode on the other side, both electrodes being very close to the filament. With such an arrangement quite good results have been obtained in Germany, using only a few volts on the anode. It will be remembered that details of this arrangement were published in the *Radio Review* a long time before that publication was discontinued.

The best example, probably, of a valve designed to operate without a high-tension battery is that produced by the General Electric

Company of America in 1918. A very small anode was employed, and the voltage of the accumulator which lit the filament was used to supply the anode of the valve. The actual circuit was similar to that illustrated in Fig. 6. No attempt was made to overcome the space-charge effect in the valve by giving the grid a positive potential; the effect is obtained solely by reducing the diameters of the anode and grid.

Even before this an effective arrangement was produced by myself; a description of it appears later.

Another method of attacking the problem consists in providing a separate grid in the valve, and connecting this grid to the positive terminal of the filament battery, the object being to introduce a positive potential of about +six volts very close to the filament in the particular zone where the space-charge exists, and thereby counteracting, to a considerable extent, its effect. The principle of this solution dates back, I believe, to the middle of 1914, and it has been regularly employed on the Continent, particularly in Holland and France, where double-grid valves for this purpose have been manufactured for a considerable period.

Before actually describing different specific arrangements, I should like to consider a few preliminary matters in connection with the expression "high-tensionless." There is, in fact, no such thing as a high-tensionless receiver, or a valve capable of amplifying which does not require some high-tension E.M.F. The term "high-tension," of course, becomes even more ridiculous when considering only a few volts, but it is used as conveying the E.M.F. which is applied to the anode of a valve. This E.M.F. is absolutely essential to the operation of an amplifying valve. To get the maximum results out of an ordinary valve, a substantial anode voltage, or high-tension battery, is required, but the actual value depends largely upon:—

- (1) The purpose for which the valve is used, *i.e.*, rectifying or amplifying.
- (2) The size of the electrodes in the valve.
- (3) The potentials applied to the grid.
- (4) The specific means adopted for reducing the space-charge effect.

A valve, for example, while giving quite good results as a detector for working telephone

receivers, would be totally incapable of producing the output currents necessary to operate a large loud-speaker. For the reception of weak signals requiring only a feeble or moderate output, a small steady anode current is all that is needed. When dealing, however, with a substantial degree of amplification, substantial anode currents are necessary.

An attempt has been made to suggest that the elimination of the high-tension battery is a different problem from its reduction. This, however, is not so. The problem of "eliminating" the high-tension battery is exactly the same as that of reducing the high-tension battery. No set yet produced will work without a high-tension battery; all that is being done is to reduce its size to about six volts, and to use the high-tension battery to pass a current through the filament for the purpose of heating it. In other words, the filament battery is used both for heating the filament and providing the high-tension, or anode, voltage.

This may be explained by reference to Fig. 1. This figure shows an ordinary three-electrode valve in which a milliammeter, or microammeter, M is included in the anode circuit of the valve between the anode and the positive terminal of the six-volt accumulator B<sub>1</sub>. The anode will now have a potential of +six volts with respect to the filament. Speaking a little more accurately, we should say that the anode has a potential of +six volts with respect to the end F<sub>1</sub> of the filament, while the potential with respect to the end F<sub>3</sub> is zero. With respect to the middle point, F<sub>2</sub>, the potential of the anode is

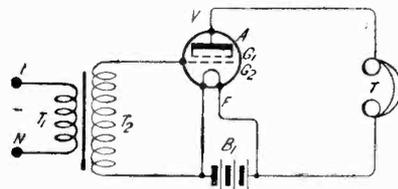


Fig. 7.—A circuit using a special valve used by the author.

+three volts. The result of this is that electrons will flow from the negative end of the filament, *i.e.*, the end nearest F<sub>1</sub>, through the grid G to the anode A, and round through the milliammeter M. This steady anode current may be controlled by varying the potential applied to the grid G of the valve, with the result that the valve will act as an amplifier, but it must be realised that the anode current, being very small, will not give much in the way of output currents.

Fig. 2 shows the exact equivalent of the Fig. 1 circuit, but this time, it will be noticed, there is an obvious high-tension battery  $B_2$ . It will be noticed that  $B_1$  is now a four-volt accumulator, and the extra two-volt cell is outside the filament circuit; the anode is now at a positive potential of +six volts with respect to the end  $F_1$  of the

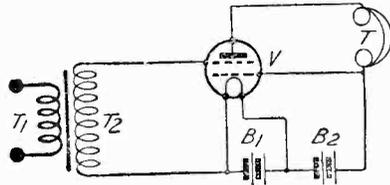


Fig. 8.—A year-old circuit of French origin.

filament, and at a potential of + two volts with respect to the end  $F_3$ . If the filament of the valve, in both cases, will operate effectively off four volts, the insertion of a rheostat in the positive lead in Fig. 1 will turn that circuit into the exact equivalent of Fig. 2, and the results will be identical. It matters little, therefore, whether the high-tension battery is included in the filament circuit as well, a rheostat being provided, or whether a portion of it is included outside the circuit.

Fig. 3 shows an actual low-frequency amplifier circuit which might be said to dispense with a high-tension battery. It will be seen that an accumulator  $B_1$ , having a number of cells, is used to supply both the anode voltage and the filament current. In some sets the accumulator  $B_1$  gives as much as 24 volts, and this kind of circuit has actually been used by large commercial wireless companies, but few would dare to suggest that Fig. 3 was a high-tensionless circuit. It is, however, only a question of degree which separates the Fig. 3 circuit from the circuit of Fig. 1. To speak about a high-tensionless receiver is really, therefore, technically incorrect, and

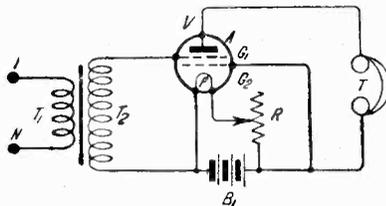


Fig. 9.—A modification of the above.

what we really mean is a receiver which uses only a small anode voltage, which voltage is derived from the accumulator.

Having decided to use our accumulator as the high-tension battery, the next problem is to use it in the most effective way.

In the case of an ordinary valve the most effective way is that illustrated in Fig. 4. It will be seen that the filament rheostat  $R$  is included in the positive lead, and this is a very important point in all so-called high-tensionless receivers. If the valve filament operates off  $3\frac{1}{2}$  volts effectively, a rheostat  $R$  will obviously be necessary, not only to obtain the best adjustment, but also to cut down the six volts from the accumulator  $B_1$ . The six volts from  $B_1$  is distributed over the filament itself to the extent of  $3\frac{1}{2}$  volts, the left-hand side of the filament being negative and the right-hand side positive, and the other  $2\frac{1}{2}$  volts appears across the used portion of the rheostat  $R$ , the slider being negative and the foot of the rheostat positive. The result is that the  $2\frac{1}{2}$  volts across

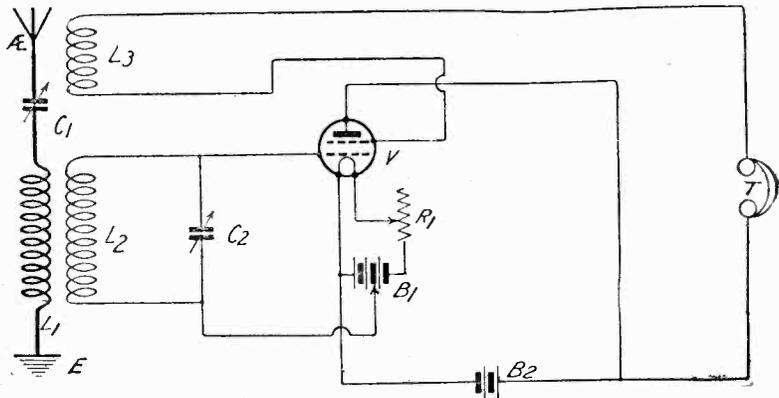


Fig. 10.—A further French circuit in which one grid is used for reaction.

the rheostat  $R$  acts in series with the  $3\frac{1}{2}$  volts across the filament to give the anode a positive potential of +six volts with respect to the negative end of the filament. If the rheostat  $R$  were included in the negative lead to the filament, the anode voltage would be only  $+3\frac{1}{2}$  volts.

The experiments of Messrs. G. V. Dowding and K. D. Rogers have focussed attention on the problem of reducing the high-tension voltage necessary to operate a valve, but some really startling statements have been made which require friendly correction.

The quite pleasing results which are obtainable by using the filament accumulator as a high-tension battery have stimulated their enthusiasm for "an amazing invention" which is to result in "No more H.T." They state: "The point we wish again to stress is that, although innumerable attempts have been made to reduce H.T. to a minimum, no one, previously to ourselves, seems to have endeavoured to eliminate the H.T. battery altogether."

Owing to the very wide publicity which has been given in the general Press to opinions of this nature, it is, perhaps, desirable to throw a little light on the subject for the benefit of those who have, perhaps, neither the opportunity nor the inclination to examine what has been done in the past.

In the beginning of 1918 the trench sets supplied to the British Expeditionary Force were of the crystal type, and, desiring to improve the range and constancy of these sets, I converted a considerable number in the 1st Army area to a circuit illustrated in Fig. 5. This arrangement eliminated the high-tension battery, to use the present popular expression, and so did away with the disadvantages of a piece of apparatus particularly inconvenient on active service. It is interesting to note that no grid

condenser or leak is employed in this arrangement, which proved so effective that Lt.-Col. Trew, who was the officer in charge of wireless in the British Expeditionary Force, informed me that, just before the conclusion of the armistice, he had arranged to convert the whole of the trench sets in the British Expeditionary Force so that they could employ this circuit. The sets proved particularly effective during the battles of Festubert and Givenchy, when the Germans opened their offensive on April 9th, 1918. It will be recalled that on this occasion the 55th Division was, according to official records, the only one on the whole Allied front which held its front intact, and was personally thanked by Sir Douglas Haig and the President of France. Almost the whole of the communications on the first, and critical, day were carried out between front and rear by the wireless sets fitted with this arrangement, owing to the fact that a very heavy bombardment had cut all the ordinary lines of communication.

The interest of this occasion lies simply, as far as this article is concerned, in the fact that high-tensionless receivers were being extensively used for vital communication work. No particular merit is claimed for the idea, which was subsequently published in my book "Thermionic Tubes in Radio Telegraphy and Telephony," the first edition of which appeared in July, 1921. The circuit is reproduced on page 114, and the following passages appear:—

"The anode circuit includes the telephones T, but there is no anode battery," and "Very loud signals have been obtained with this arrangement."

Fig. 6 shows a subsequent arrangement introduced by the General Electric Company of America, and this is really an ordinary receiving circuit in which the accumulator serves as the high-tension battery.

I could refer to a number of other cases, but I think I have indicated clearly that any novelty that may exist must be confined to particular circuit arrangements. The problem of eliminating the high-tension battery, and also its solution, are both old, and there is nothing amazing in regard to the matter to those in possession of the facts.

Coming now to specific arrangements, the most successful for general purposes is probably that which employs a valve using a grid kept at a positive potential for the purpose of lessening the space-charge in the valve.

The new Cowper single-valve circuit, using an ordinary valve, is, however, excellent and better than any arrangement we have yet tried: details were given recently in *Wireless Weekly*, and some particulars are in this issue; a double-grid valve amplifier may be added to the circuit.

A particular form of valve in which the space-charge is reduced is described in my British Patent 154,364, of September 8th, 1918. In this case a grid electrode, connected to the anode so as to form one structure, surrounds the filament, and this arrangement may be used as a rectifier, or an additional grid may be introduced so as to obtain a three-electrode valve effect, at the same time reducing the space-charge in the valve by the extra grid. A suitable circuit for such a valve is shown in Fig. 7. Long before this, however, a grid electrode at fixed positive potential was used to reduce the space-charge in a valve, and the most interesting

facts in connection with the whole matter are concerned with arrangements in quite common use in France and Holland, which have not attained any popularity in this country for the very simple reason that suitable British valves have not been available. Double-grid valves have certainly been made, but their price has been

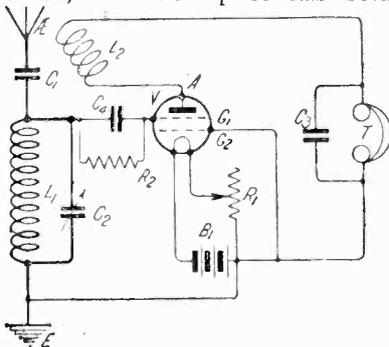


Fig. 11.—A simple circuit for four electrode valves.

prohibitive to the ordinary experimenter. The French and Dutch have a considerable number of circuits using double-grid valves in which the high-tension battery is either altogether missing or else consists of two or three dry cells.

Fig. 8 shows a circuit which is taken out of a French valve manufacturer's catalogue of a year ago. It will be seen that the inner grid of the valve, V, is given a positive potential by means of a battery B<sub>2</sub>, consisting of two or three volts, and the accumulator B<sub>1</sub>. The two batteries may, of course, be connected together and constitute the filament battery of the valve, a rheostat being used in the positive lead. The actual valves have been on sale for a long period for the very purpose we are concerned with.

Fig. 9 shows the arrangement in which the very small high-tension

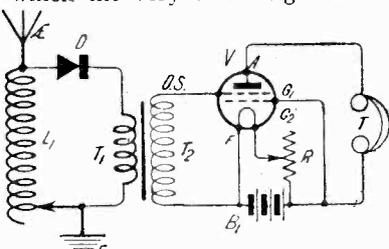


Fig. 12.—An H.T.-less amplifier with crystal receiver.

battery and accumulator are joined into one, a six-volt accumulator B<sub>1</sub> being now employed, and also a rheostat R in the positive lead.

Fig. 10 is another circuit published in the catalogue, and it will be seen that one of the grids

is now used as an anode for the purpose of producing reaction. This circuit does not appeal to me particularly, but it indicates the line on which experiments have been carried out.

The Dutch experimenter has also been working on very similar lines, and in the experiments which we have carried out ourselves we have employed Dutch double-grid valves made by Phillips and supplied by Leslie Dixon and Co.

Fig. 11 shows a circuit which the average experimenter will want to try out with one of these double-grid valves. The condenser C<sub>1</sub> is a 0.0001 μF fixed condenser, for constant aerial tuning, while the inductance L<sub>1</sub> is, say, a No. 50 Lissen plug-in coil shunted by a variable condenser C<sub>2</sub> of .0005 μF capacity. This will enable any of the British broadcast wavelengths to be received, although for wavelengths over about 430 metres the coil L<sub>1</sub> may be a No. 75. The usual grid condenser and leak is provided, while in the anode circuit is a reaction coil L<sub>2</sub>, which is a No. 75. The telephones are shunted by a condenser C<sub>3</sub> of 0.002 μF, while the inner grid G<sub>2</sub> is connected to the positive terminal of the six-volt accumulator B<sub>1</sub>, and the rheostat R, which is of the Lissenstat minor type (an ordinary rheostat has not sufficient resistance), is included in the positive lead; particular care should be taken to see that this is done.

The circuit will give surprising results, and will enable audible signals to be obtained on a loud-speaker at 10 miles from a broadcasting station, although the results will be weak. With 'phones, however, excellent signals are obtainable even on a 5 ft. aerial.

Fig. 12 shows the use of a crystal detector and a high-tensionless low-frequency amplifying valve, while Fig. 13 is simply Fig. 11 with a stage of low-frequency amplification added. With this circuit good loud-speaker results are obtainable up to about 20 miles from a broadcasting station, but results are not equal to those obtained with a set using a high-tension battery. This raises a point which will be discussed subsequently.

If any difficulty is met with in any H.T.-less circuit as regards reaction, try tuning the reaction coil (e.g., a No. 50 shunted by a 0.0005 μF variable condenser).

I have worked an S.T. 100 receiver without a high-tension battery by connecting the rheostats in the positive leads of a six-volt accumulator and, using double-grid valves, connecting the inner grids to the

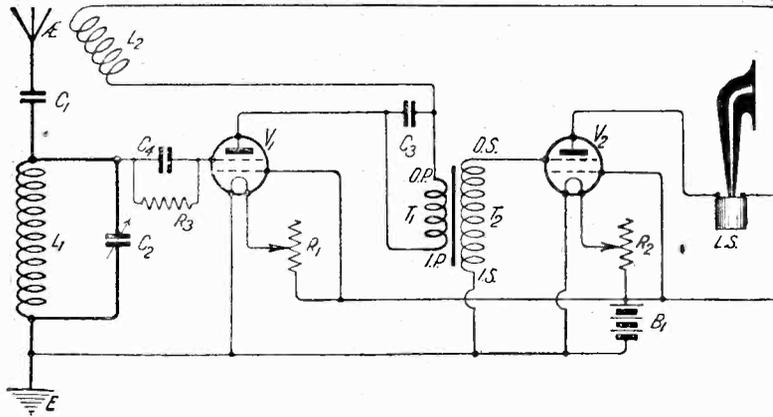


Fig. 13.—A two-valve H.T.-less Receiver.

positive terminal of the accumulator.

It is, in fact, possible to convert any set using ordinary valves into a high-tensionless receiver by connecting the rheostats in the positive leads using double-grid valves, and connecting the inner grids to the positive terminal of the filament accumulator.

It is only fair, however, to state that, while surprisingly good results are obtainable, yet they are not comparable with the results obtained with a properly designed receiver using a high-tension battery. Particularly is this the case where volume is required. The single valve experimenter will be better pleased than the multi-valve man who wishes to cut out his high-tension battery. The latter, and even the former to a large extent, are up against hard, cold, incontrovertible facts.

The difference between the new Cowper circuit and the ordinary non-reflex set is not so marked as when comparing two- or three-valve sets.

The H.T. battery is a great improvement on two valves, so that one might as well use H.T. on both valves.

To state that the results obtainable without a high-tension battery are inferior to those obtained with

such a battery does not mean that high-tensionless receivers are uninteresting. There are, no doubt, many who are ready to sacrifice signal strength for convenience.

It is quite possible, moreover, that the general interest aroused by the discussion may lead to the design of valves using lower anode

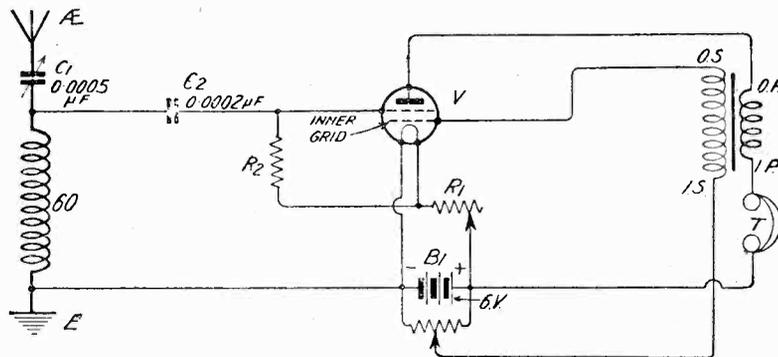


Fig. 14.—A circuit of experimental interest.

voltages. The Dutch and French valves using double-grids seem to work best when an additional six volts is used as high-tension battery, although they work perfectly well with simply the six volts of the accumulator. Any voltage over the extra six volts will not result in an increase in signal strength, but the ordinary valve using proper

high-tension voltage has it every time when actual comparison is made. It may, however, be that in time a very low impedance valve will be produced giving the full amount of amplification, but even if this is so, we shall still use high-tension batteries, or their equivalent, even if they are smaller, and we will still be able to use, and probably will use, all the circuits now employed.

An interesting effect of the discussion will be to draw attention to double-grid valves, and if these can be turned out at, say, 15s. each by British manufacturers, a host of new circuits will be available to experimenters both with ordinary, or medium, high-tension voltages and with very small anode voltages. Many such circuits have already been published, but owing to the expense of the valves, few have been able to try them.

Commencing with the issue of June 3rd, *Wireless Weekly* will be giving a series of articles dealing with high-tensionless circuits of

special design and also special double-grid circuits.

A few further circuits are given here to illustrate the article, which have been extracted from issues of *Wireless Weekly*, in which numerous details have already been published, including a full description of the first high-tensionless loud-speaker set. *Wireless Weekly*, incidentally, was the first periodical to publish high-tensionless receiver circuits.

I can only say, in conclusion, that it is hoped that readers of MODERN WIRELESS will calm the rather hysterical anxiety of their non-technical friends, who, I am told, are holding off buying sets, in many cases, because high-tension batteries have been abolished, and any set using them must be out of date. We have had the aerial-less set, the high-tensionless set, the accumulator-less set, and I have even used a receiver in which there was neither a loud-speaker nor telephone receivers. I forget the last-named arrangement because it was

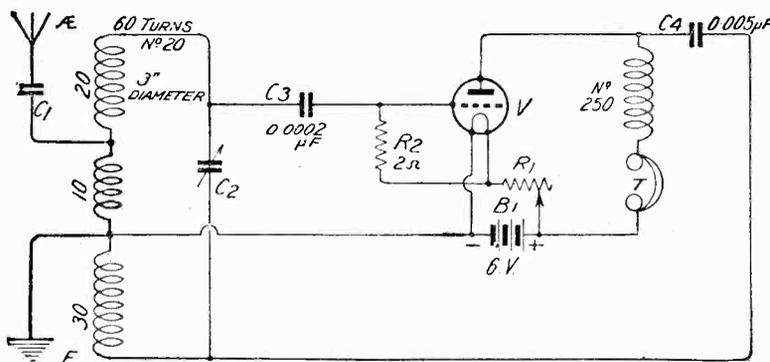


Fig. 15.—Another circuit given by Mr. Cowper.

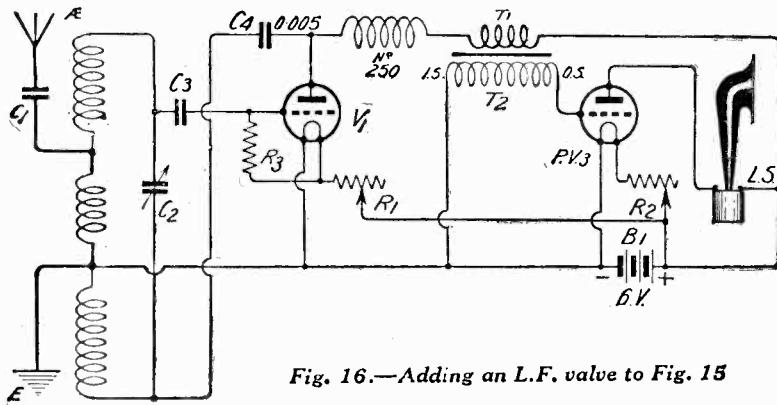


Fig. 16.—Adding an L.F. valve to Fig. 15

some time ago, but I believe that electro-magnetic vibrations were caused to vibrate the teeth. Nevertheless, at the risk of being considered behind the times, I continue to use these inconvenient accessories to wireless reception.

Do you find the interval between issues of "M.W." too long? Buy "Wireless Weekly" in the interval.

## More Readers' Views

### M.W. Modifications of the Grebe C.R. 13

To the Editor of MODERN WIRELESS.

SIR,—The following experiences of the above may be of interest to your readers. They are the results of a month's working on the circuit which is used with a transformer coupled audio-frequency amplifier of 2 L.S.5 valves. The set has been used here and in the north-east corner of Wales.

The amplification per valve is very high. The set is very stable when tuned, and while the initial tuning was difficult it is now possible to go round all the broadcasting stations by using known condenser readings.

Here I have received at loud-speaker strength both the Sheffield and Plymouth relay stations.

The set is equally good for wavelengths down to 300 as for wavelengths up to 2,800. I have not tried above or below these limits.

The selectivity is extraordinary. Here no difficulty is experienced between London, Cardiff and Manchester. Cardiff can be obtained without a trace of London and vice versa.

The background is very silent and absence from distortion is very marked. Broadcasting stations up to 50 miles come in strongly without much loss of strength, with either the earth wire fastened to the aerial terminal and no aerial or with an aerial and no earth.

After many trials I have found that it is best to use a much larger

coil in the first anode coupling than in the second.

For wavelengths from 350 to 600 I use for the couplings the following coils:—

1st coupling	Anode.	Rimar 7.
	Grid	Lissen 75.
2nd coupling	Anode	Lissen 100.
	Grid	Lissen 75.

The No. 7 Rimar is, I believe, about a 200 coil.

Were I building the set again I should have a Vernier condenser for the first tuning grid condenser. The other condensers do not require it.

Adding reaction increases signal strength slightly but makes the potentiometer control very critical.

The set has been used very successfully with a loosely coupled double circuit tuner with tuned aerial and tuned secondary circuits, but owing to the sets selectivity with the single tuned aerial circuit I do not think there is much advantage.

The set has been used very successfully as the second half of the supersonic heterodyne method of reception. In N.E. Wales 2LO, which is very troublesome to find when 2ZY is at work, was easily got by this method, the 2LO wave being heterodyned up to 2,000 metres and received on the M.W. Grebe C.R.13 on 2,000; a loosely coupled dual circuit tuner was of course used for the M.W. Grebe C.R.13.

Yours faithfully,  
C. R. BATES.

Market Harborough.

### Choke Circuits

DEAR SIR,—Your article in a recent issue of MODERN WIRELESS re choke circuits is very interesting. I thought you would like to hear I have been using a similar circuit for over two years, I consider I get very good results, as I have no difficulty in getting any of the B.B.C. stations, Paris, Brussels, Berlin, Airways, North Goodwin, and I have also had "W.G.Y." on 3 valves.

I am not using leaks on grids as I found these made no difference. The chokes are taken from "Ford" coils, also the last condenser. The first two condensers are home made. I usually listen to 2 LO using 4 valves and I get full strength compared with several transformer coupled sets I have heard. The set is very quiet and free from the noises usually heard when using transformers. It operates the loud speaker quite well on 3 valves when tuned to 2 LO and I can get fairly good results when using only 2 valves and speaker.

I use French "R" valves, 4 volts on filament, 60 volts H.T. and 120 ohms 'phones.

Yours faithfully,  
S. W. HULL.


Audley Road,  
Colchester.

Buy your copy of next month's "Modern Wireless" early.

# A Two-Valve Cabinet Receiver

By **STANLEY G. RATTEE**, Member  
I.R.E. Staff Editor.

*A Broadcast receiver which, in addition to being of easy construction, permits tuning over a multiplicity of wavelengths.*

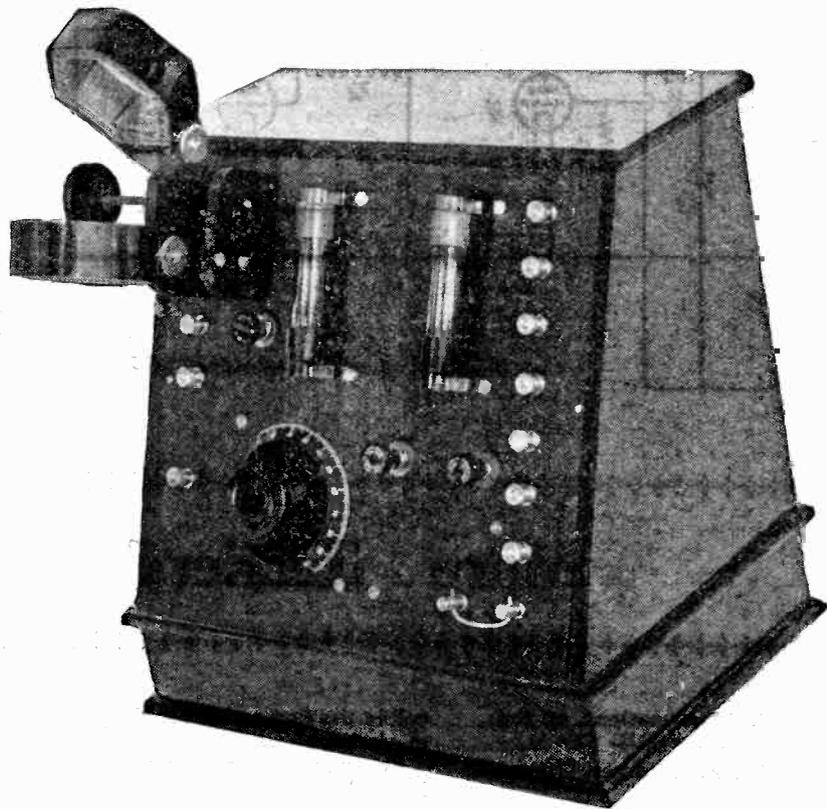

*Fig. 1.—The general appearance of the receiver may be gathered from this photograph. Note that the two terminals for grid cells are short-circuited; when used they should be connected positive on the right, with negative on the left, the short-circuiting wire being removed.*

**T**HOUGH the circuit employed in the receiver about to be described is a well-known straight two-valve arrangement, the results obtained go to show that with careful construction and thoughtful disposition of components in relation to each other, the reception of most, if not all, of the British Broadcasting stations is possible upon the simplest two-valve circuit.

With the receiver as illustrated in the photographs, 2LO at a distance of ten miles is easily audible on a loud-speaker, using an indoor aerial. On the same aerial, Cardiff, Bournemouth and Birmingham can also be heard at good telephony strength on telephones. With a moderately good outside aerial all the B.B.C. stations, in addition to Radiola, are easily tuned.

### General Considerations

In designing this two-valve receiver, it was intended to make the operation of tuning as simple as possible, and for that reason, a single-valve reaction circuit, coupled to a single stage of low-frequency amplification, was chosen in preference to one stage of high-frequency,

followed by the detector with the concomitant tuning of two condensers instead of one. It was further desired to arrange the set in such a manner so as to permit the use of either one or two valves, and also to allow of either bright or dull emitter valves being used.

In order to obtain the maximum efficiency from the combination of a detector and a single stage of low-frequency amplification, an arrangement was decided upon whereupon a higher plate voltage could be applied to the low-frequency valve than in the case of the detector valve. Such an arrangement affords two distinct advantages over the usual method of applying a common H.T. voltage to all valves, in that, by keeping the detector plate voltage as low as possible, the set is less liable to oscillate unintentionally; and, secondly, applying the maximum voltage to the low-frequency valve for loud signals, in the usual manner of a common battery often makes the plate voltage of the detector valve too high for clear detection.

### Components

For the guidance of those readers

who intend constructing this receiver, the names of the manufacturers are given in addition to the components incorporated in the set, and though there is actually no obligation in the choice of components, to obtain results similar to those possible with the receiver illustrated, the values given must be adhered to:—

- One ebonite panel measuring 10 in. by 9 $\frac{1}{8}$  in. by  $\frac{1}{4}$  in.
- One variable condenser of 0.0005 $\mu$ F. capacity (Radio Instruments, Ltd.).
- One two-coil holder (Radio Communication Co., Ltd.).
- One Lissen "push-pull" switch (Lissen, Ltd.).
- Two Lissenstat minors (Lissen, Ltd.).
- One grid condenser 0.0002 $\mu$ F. capacity (Dubilier).
- One fixed condenser of 0.0001 $\mu$ F. capacity (Dubilier).
- One grid-leak, 2 megohms (Dubilier).
- One fixed condenser 0.001 $\mu$ F. capacity (Dubilier).
- One similar condenser, 0.002 $\mu$ F. capacity (Dubilier).
- One low-frequency transformer (Woodhall).
- Twelve brass terminals.

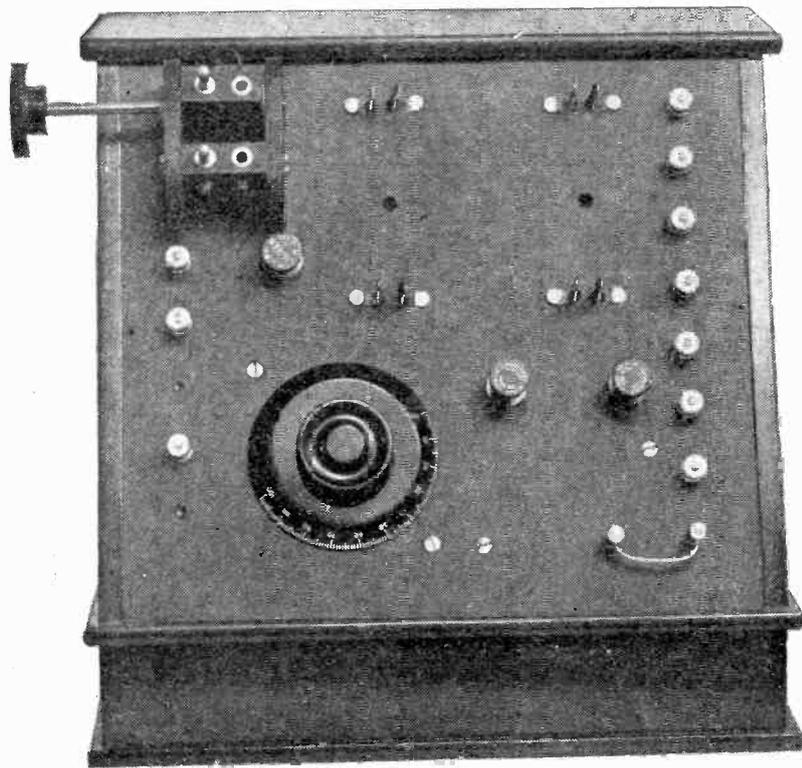


Fig. 2.—The front of the panel with valves and coils removed. Fig. 4 indicates the purpose served by the various terminals.

- Two Myers' valves (bright or dull emitter type).
- Set of plug-in coils for the wave-lengths desired.
- One fixed condenser of  $0.05\mu\text{F}$ . capacity (Dubilier).
- One accumulator (for bright emitter valves 6 volts 40 amperes actual, for dull-emitter valves 4 volts 40 amperes actual).
- One H.T. battery up to 70 or 100 volts.
- One pair of 2,000 or 4,000 ohm. telephones.
- Quantity of No. 16 tinned-copper or "square" wire for connecting purposes.

**The Circuit**

A simple theoretical arrangement of the circuit is shown in Fig. 6, in which  $L_1$  is the aerial inductance tuned by the condenser  $C_2$ .  $L_2$  is the reaction coil,  $C_3$   $R_3$  the grid condenser and leak;  $R_1$  and  $R_2$  the filament resistances;  $V_1$  the detector valve; IP. OP., IS.OS the low-frequency transformer with the condenser  $C_4$  shunted across the primary winding, and T the telephones.  $C_5$  and  $C_6$  are fixed condensers shunted across the telephones and H.T. respectively. The circuit actually employed in the receiver is shown in the next figure, which introduces the switch S for cutting out the second valve,

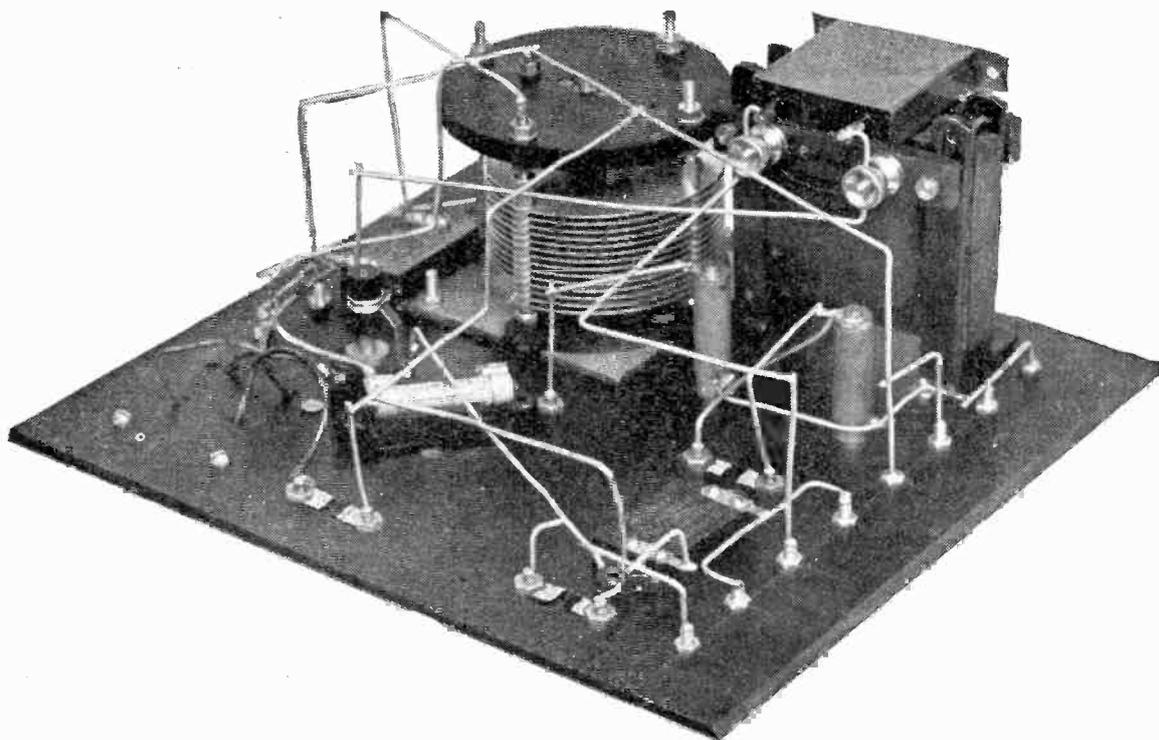


Fig. 3.—A view of the underside of the panel showing the wiring and disposition of the components; the terminals seen to the right of this photograph correspond with those seen to the right of the previous illustrations.

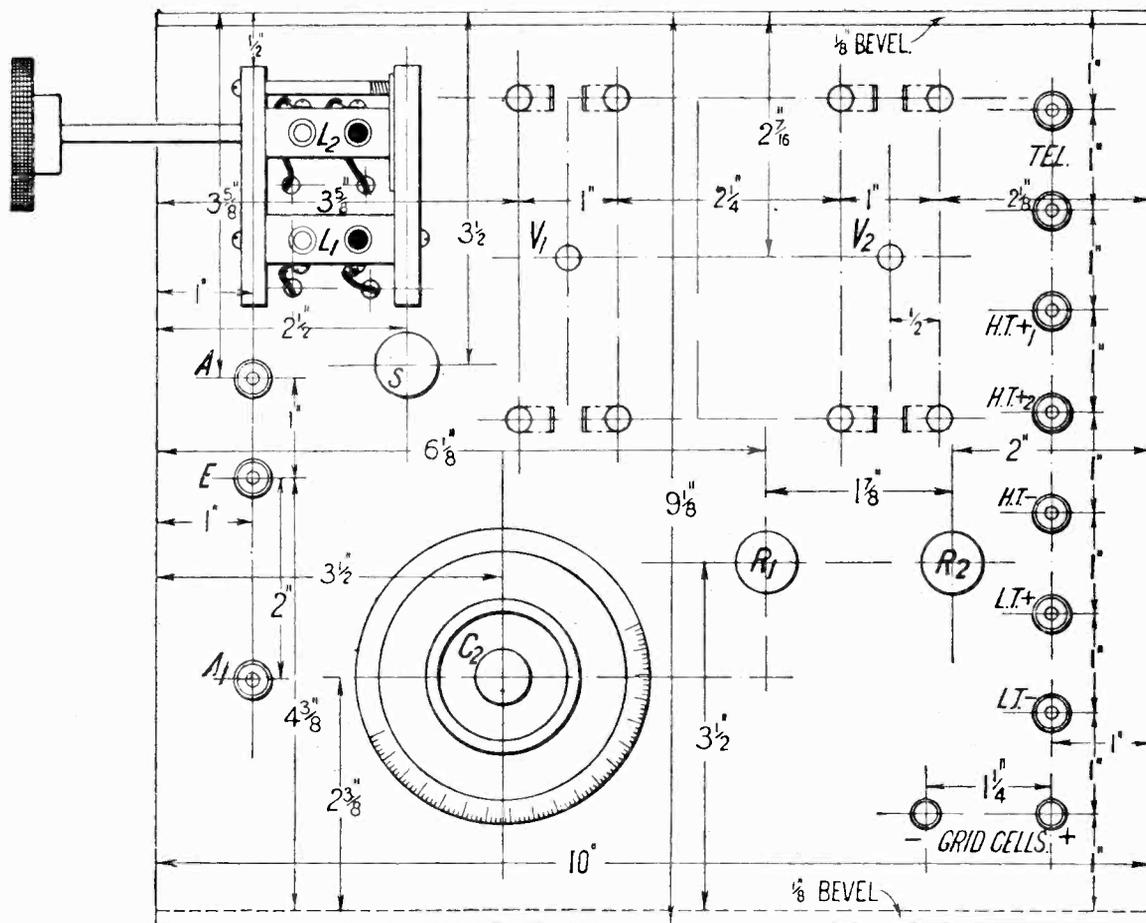


Fig. 4.—The layout of the panel, blueprint No. 44a.

and also shows the arrangement of H.T. battery connections. It will also be seen that constant aerial tuning is employed.

**The Panel**

This is drilled in accordance with the dimensions given in the figure illustrating the lay-out, after which the panel should be treated on both sides with a careful rubbing of fine emery paper in order to remove all traces of the glossy surface. Certain manufacturers are now marketing a specially finished ebonite, which has a highly-polished surface, guaranteed to be non-conductive, and in cases where readers are assured that the material purchased is of this type, the removing of the surface skin is not in any way necessary.

**Wiring the Receiver**

The method of wiring can be gathered from the photograph showing the underneath of the panel, whilst the actual work of wiring the components may be followed by a careful study of the

wiring diagram. All connections must be soldered, and leads must be kept as short as possible, particularly so in the grid circuits.

**Grid Cells**

Should the reader decide to use dull-emitter valves with this receiver, then the incorporation of a grid biasing battery is advocated, and in order that such an addition may be made, two separate terminals are provided. A battery of about 4 1/2 volts made up from flash-lamp cells is sufficient for grid bias, the inclusion of which will eliminate the gruff woolly speech which is sometimes experienced when using dull-emitter valves for low-frequency amplification. Should the battery not be used, or should the cells become exhausted, then the two terminals across which the battery would normally be connected should be short-circuited as shown in the photographs.

**The H.T. Connections**

The two terminals shown in the wiring diagram, H.T. +1 and

H.T. +2, provide the plates of the two valves with the separate voltages referred to in an earlier paragraph. The terminal H.T. +1 should be connected to the socket of the H.T. battery labelled 50 or about that figure, according to the valves in use, whilst the terminal H.T. +2 should be connected to the 70 or 75 socket or higher, according to the results obtained; the H.T. negative of the battery is connected in the normal way to the H.T. negative terminal of the set.

This arrangement permits an adjustable voltage of 50 volts or more to be applied to the plate of the detector valve, and 75 to 100 volts upon the plate of the note-magnifier. By switching over to the single-valve circuit the higher voltage is applied to the plate of the detector automatically.

**Constant Aerial Tuning**

In order to simplify the tuning arrangements, the receiver is fitted with constant aerial tuning, the virtues of which were fully described

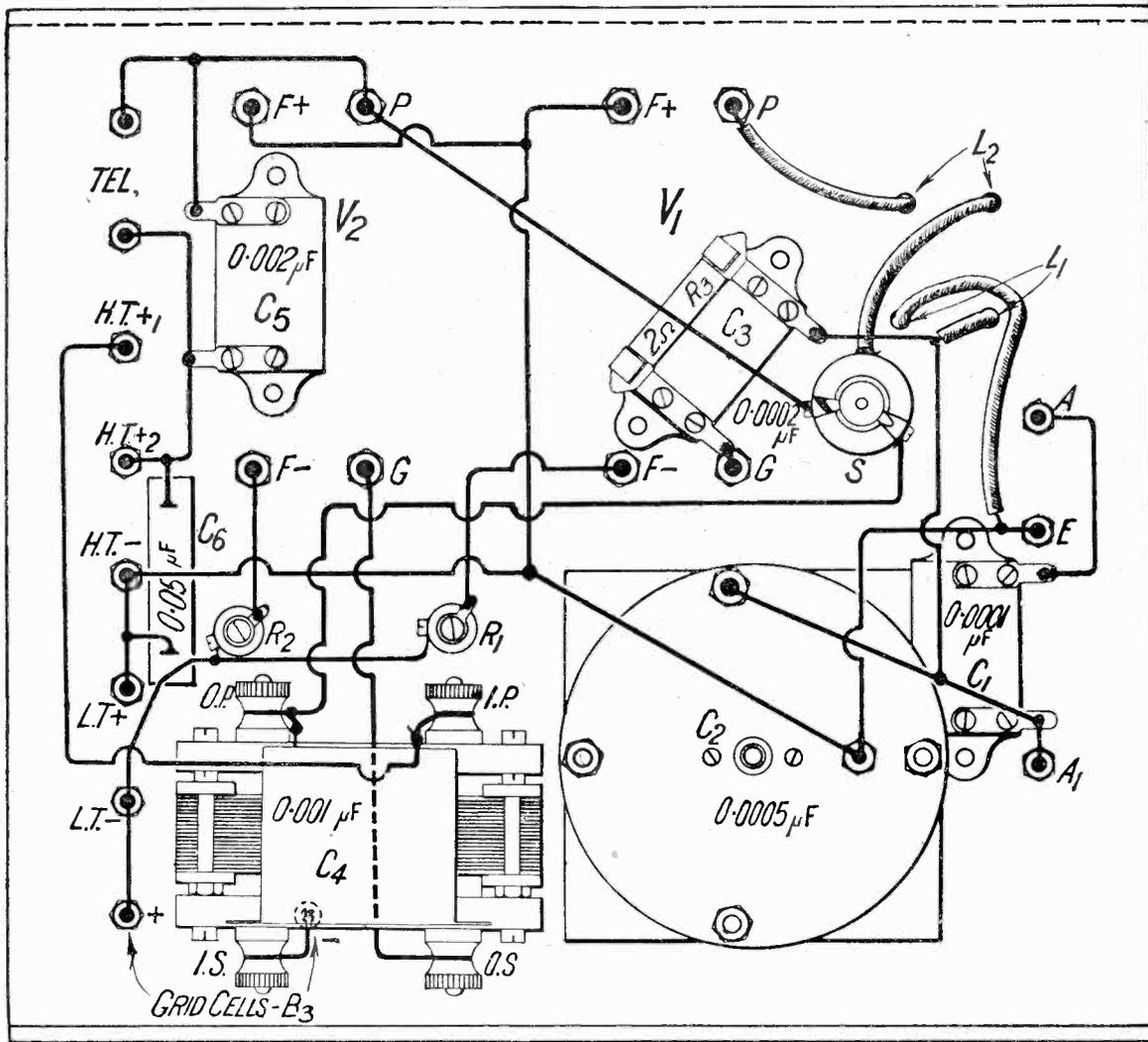


Fig. 5.—Practical wiring diagram, blueprint No. 44b.

in the columns of this journal in the February and March issues of this year.

By means of this arrangement it is possible to cover the whole of the B.B.C. wavelengths with two coils for aerial tuning—namely a No. 50 for the lower waveband and a No. 75 for the higher.

When tuning to the longer wavelengths, say 600 metres and upwards, the aerial should be disconnected from the C.A.T. terminal A (see Fig. 7) and connected to the top of the inductance L<sub>1</sub>—namely, terminal A<sub>1</sub>, the terminal A being left free; the earth connection remaining as hitherto.

**Switching**

The purpose served by the switch S is to permit the use of either one or two valves. With the switch "in," the detector valve only is in circuit when the filament resistance R<sub>1</sub> should be used for filament lighting, the resistance R<sub>2</sub> being in the "off" position.

With the switch "out" both valves are in circuit, when both the filament resistances R<sub>1</sub> and R<sub>2</sub> should be used for filament lighting.

It should be noted by readers that this switching in or out of the last valve changes the position of the telephones in the circuit, at the same time increasing the plate voltage applied to the detector valve in the case of single-valve reception, and decreasing it in the case of the two-valve circuit; the higher voltage then being applied to the low-frequency valve.

When switching over from one valve to two, it may be found necessary to readjust the position of the reaction coil and condenser C<sub>2</sub> on account of the smaller H.T. voltage, which is then applied to the detector valve. Similarly when changing over from two valves to the single-valve arrangement, the reaction coil and aerial condenser may again need readjustment.

**Operating the Receiver**

For the reception of the B.B.C. stations with wavelengths between 300 and 400 metres, connect the aerial to the C.A.T. terminal A, leaving the A<sub>1</sub> terminal free, and the earth to E, when a plug-in coil No. 50 should be inserted in the aerial socket and a No. 50 or 75 in the reaction coil socket. The two coils should be turned at right-angles to each other, the H.T. connections made and the filament current applied. Turn the condenser very slowly, at the same time bringing the reaction coil nearer the aerial coil, taking extreme care whilst so doing that the set is not made to oscillate. When the desired signal has been picked up, leave the reaction coil in position and obtain the best results by varying the condenser slightly. With the best possible results obtained by this means again adjust the reaction coil, making further slight alterations to the condenser.

(Continued on page 37.)



# Above & below the Broadcast Wavelengths

## Give a Dog a Bad Name.

FOR high-frequency amplification for the shorter waves there is, I suppose, no method of coupling to equal for efficiency the tuned anode. Unfortunately this circuit has obtained rather a bad reputation for instability and for proneness to causing self-oscillation in the receiving set. Most amateurs can and do use one tuned anode, but if you suggest the addition of a second high-frequency valve coupled in the same way they are as likely as not to hold up their hands in horror and to tell you that to do such a thing is next door to impossible with any kind of comfort. Now this attitude I believe is due chiefly to the way we have of accepting as gospel everything that is said three times. Various writers have condemned any circuit containing more than one tuned anode as unpractical, and the world of wireless men seems to have accepted their verdict without question. It is a case of "give a dog a bad name and hang

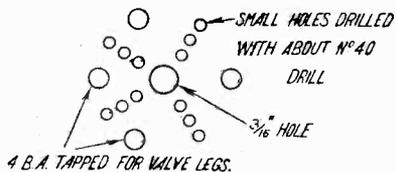


Fig. 1.—A useful method of reducing capacity in valve sockets.

him." As a matter of fact, a pair of tuned anodes can be used for quite short wave reception—certainly down to 300 metres—with no more trouble than any other kind of high-frequency coupling, provided that pains are taken in the design and construction of the set. Put together carelessly a circuit of this kind and you will find that you cannot go near it without its howling at you, and besides being a nuisance to yourself it will also interfere with all your neighbours, for it is capable of causing the aerial to radiate

strongly. But take a little trouble over the details and you can have an exceedingly efficient high-frequency amplifier.

## Unwanted Capacity.

The first thing to do in designing a receiver containing a pair of tuned plates is to take every possible step for the elimination of unwanted capacity. The way in which wiring is done is of the utmost importance, for any capacity between the leads on the high-frequency side of the set will lead to instability. The bare wiring method should always be employed. When wiring is done in this way all leads which must cross should do so at right angles. Wires should be separated from one another by at least  $\frac{1}{2}$  in., and this distance should be doubled if they run parallel for any length. Heavy wire or square rod should be used throughout so as to offer the smallest high-frequency resistance by providing a large surface area.

The most efficient valves for high-frequency work are those of anti-capacity type, such as the Mullard Ora B, S<sub>3</sub> and S<sub>7</sub>, the M.O. V<sub>24</sub> and QX, with their dull emitter counterparts DEV and DEQ, or the Myers's Universal. If these are mounted directly on to the panel by means of clips inter-electrode capacity is very small indeed; but their good qualities are to a great extent neutralised by placing them, as so many of us do, in adapters made to fit ordinary four-socket valve holders. But it is not absolutely necessary to use special valves of this type, for stability can be obtained with any valve of good design if care is taken over the mounting. I have, for example, used the Mullard Ora with complete success in a double tuned anode set for all broadcast reception. For 4-pin valves never use a moulded holder with sockets embedded for their whole length in ebonite. By far the better method is to employ separate valve sockets

and to shorten them as much as possible; they can be cut down to about one-third of an inch in length without in any way impairing their grip upon the valve pins. Valve legs should always be tapped in, for then there is no need to use nuts on their shanks. If nuts are used they must of necessity lie very close together on the underside of the panel with a consequent increase in capacity. A useful tip for reducing the capacity of valve holders is shown in Fig. 1. When the tapped holes for the legs have been made, drill at the centre of the circle upon which they lie a  $\frac{3}{16}$  in. hole; then make three or four small holes very close together between each pair of valve legs, as shown. A drill of about No. 40 gauge is suitable for the purpose. If a small, fine file is available, or if a fretsaw blade can reach the position, still better results will be obtained in the way shown in Fig. 2. Here cuts are made between the pairs of valve legs so that there

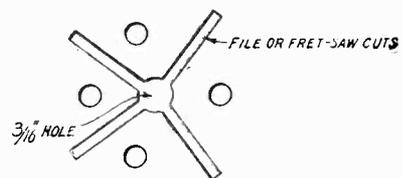


Fig. 2.—An alternative method.

is a considerable air space between them. Ebonite has a higher dielectric co-efficient than air, and therefore produces a greater capacity when it separates current-carrying conductors. On the other hand, its dielectric efficiency is lower than that of air, hence it causes larger hysteresis losses. By drilling holes or making cuts between the legs we decrease the capacity and improve the insulation of the holder without unduly weakening the ebonite. If a Morris template is used there

will be no difficulty about finding the place at which the 3-16 in. hole should be drilled, for it is provided with a central hole.

**Inductances.**

The question of inductances for tuned anode circuits is one that has not received sufficient attention. The instability of most double tuned anode circuits can be traced very largely to cross coupling between the coils in the tuned circuits. Where this occurs oscillation is bound to take place when sharp tuning is approached in both circuits. Now, when you come to think of it, we do not require in the tuned anode inductances quite the same qualities that we want in

are those of wide, shallow form, such as the Igranic or the Lissen inductances. When these are placed at right angles 4 in. apart, there appears to be practically no coupling at all between them on the short wavelengths. It will not as a rule be found desirable to use a double circuit tuner with a pair of tuned anodes. Complete selectivity can be obtained by means of the anode circuits, and the use of a secondary coil in the tuner greatly increases the tendency to oscillate. Nor will it be found possible in most cases to use reaction coupled to the A.T.I. If reaction is required it should be coupled to the second high frequency valve inductance. As a

coupling may be used for the second valve whilst searching is in progress. This can be done very simply by setting its condenser at zero, removing its inductance from its holder and replacing it with a 50,000 ohm non-inductive resistance provided with plug and socket mounting.

**Plate and Filament Potentials.**

Perfect stability with two tuned anodes can be obtained only if the plate and filament potentials of the high-frequency valves are properly adjusted. It is a mistake, really, to attempt to use the same anode potential for all the valves of the set. It is very little more trouble to design the set in the way shown in Fig. 3, so that the potentials of high-frequency valves, rectifier and note-magnifiers may be adjusted independently. If the battery is equipped with sockets giving six volt steps, all that is necessary is to fit three high tension positive terminals to the set, marking them HF, R, and LF. Differently-coloured wander plugs should be used for each. The plugs may be marked very easily by making a hollow with a suitable drill at the top of each and filling with paint. The battery should be one with a maximum voltage of about 120. Eminently suitable for the purpose is the No. 924, made by Messrs. Siemens, which consists of very large cells and is capable of a big output without becoming noisy. A set made up on the lines shown in Fig. 3 will give very much better results than one in which a single high tension plus busbar is used, since all valves can be worked on the proper portion of their characteristic curves. The correct adjustment of filament and plate potentials for tuned anode valves is found in the following way: The filaments are set at about normal brightness and the anode potential is adjusted to the maker's figure. A strong signal is then tuned in as sharply as possible. The set will probably oscillate or even howl loudly. Use the potentiometer to check this to some extent, but do not introduce heavy damping by throwing a large positive potential on the grid of the first valve. Try the effect of varying the anode potential. If this does not stabilise the set, turn to the rheostats. Move them first in one direction and then in the other until the silent point is found. The valves will oscillate if they are receiving either too much or too little filament current. Once the correct setting for a given anode potential has been found the set will as a rule become per-

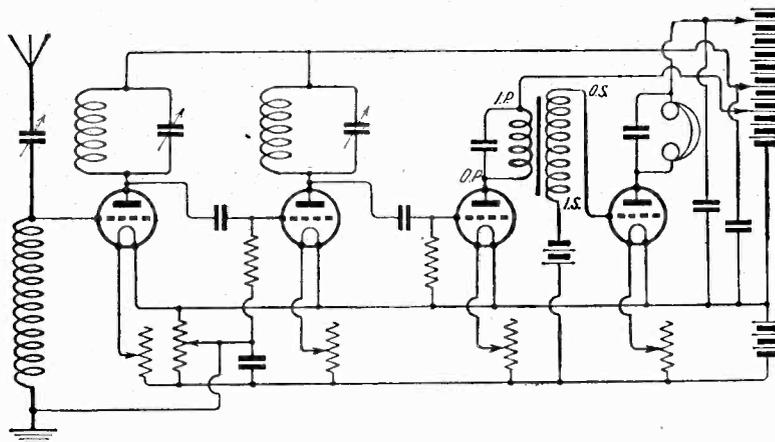


Fig. 3.—A set with multiple H.T. tapings.

the A.T.I., the C.C.I. or the reaction coil. Part of the business of these last coils is to provide a strong coupling when it is needed. The tuned anode inductance, however, we require to behave in exactly the opposite way; we want it to be a coil which will not cause interaction with others or be affected by them. The type of inductance which gives the strongest coupling is the pancake or flat basket design. If these are wound with heavy wire, and so made of large diameter, the distance at which interaction between two of them placed face to face can take place is really amazing. Some time ago I wound a pair with flex wire for broadcast reception, using them as primary and secondary of the tuner. I work them as a rule from 5 in. to 8 in. apart, obtaining very strong signals. With coils of this kind cross coupling may occur at very much greater distances, even up to several feet. Nor can zero coupling be obtained by placing them at right angles to one another unless they are a long way apart. The most suitable coils for the purpose

matter of fact, the signal strength with a pair of tuned anodes is so great that no direct reaction is usually required.

**Tuning.**

It might be thought that with two sharply tuned high frequency circuits searching would be rather a difficult business. As a matter of fact, it is not really, if the secondary circuit is eliminated, for then the only tuning controls are the three condensers, the A.T.C. and those of the anode circuits. These may be reduced to two if a double condenser such as the Fallon "Duanode" is used, but when this is done perfectly sharp tuning of both circuits is not obtainable unless the inductances have been very carefully matched. When searching for transmissions it is only necessary to set the second tuned anode condenser approximately and to work with the A.T.C. and the first. As soon as the sharpest tuning has been obtained with these two the second anode condenser may be finally adjusted. Alternatively, resistance capacity

fectly stable. Do these experiments, if possible, outside broadcasting hours, such as when the station is testing.

**A Stabiliser.**

Should there still be signs of oscillation it is due to cross coupling either between the anode inductances themselves or between one of them and the A.T.I.—that is, supposing that care has been exercised to eliminate unwanted capacity. If the set cannot be tamed in any other way we must introduce a form of stabiliser which was referred to some months ago in MODERN WIRELESS. This consists simply of a 400-ohm potentiometer wired as a rheostat which is placed between the anode inductances and the HT plus lead, as shown in Fig. 4. This method, which I have now had in use for more than a year, is extremely effective, but I cannot pretend to say definitely exactly how or why it works. Certainly, even if the full resistance were thrown into circuit, which is very seldom the case, its effect upon the anode voltage would be negligible. Probably the potentiometer which is inductively wound acts as an adjustable radio frequency choke, and it may be that the extra resistance thrown into the circuit just suffices to prevent the valves from being tuned sharply enough to oscillate. I can, however, state emphatically that it is most effective. I have used the stabiliser now in four different sets, so there can be no question of a freak result obtained, only in one special set of circumstances. In every case it acts equally well. The following experiment will give convincing proof of its powers of soothing even the wildest combination of tuned anodes. Place the slider of the potentiometer so that there is no resistance in the circuit, then tune the set sharply to a strong transmission and get it into violent oscillation. Now move the slider slowly so that the resistance is gradually added. Up to a point nothing will happen, then oscillation will show signs of decreasing, and as the movement is continued it will disappear altogether. As more resistance is added after this point is reached the set begins to oscillate again and finally howls as badly as before. The adjustment of the resistance is not particularly critical, for once the silent point has been found the slider can be moved for some distance before oscillation begins again. When the resistance has been properly set it can be left alone for all wave-

lengths for a wide band on either side of that upon which the original adjustment was made. Small movements may be necessary on wavelengths very much above or below it.

**Quiet, Efficient Working.**

I have at the present time two double tuned anode sets in use, one with a single stage of note magnification and the other with two stages. Both are as stable as sets fitted with aperiodic high frequency transformers. Neither of them can be made to oscillate upon broadcast wavelengths unless the rheostats, the high tension wander plugs, the grid potentiometer or the stabilising resistance are interfered with. All of these may be described as permanent settings which do not require to be touched. Should either set show signs of oscillation it is a pretty certain indication that the

**Arrangement of Inductances.**

The arrangement of the coil-holders on these sets is the result of a considerable amount of experimenting with them in different positions. Fig. 5 shows how they are placed. It will be seen that all three are at right angles to one another. The A.T.I. is mounted upon the side of the cabinet in a horizontal position. The first tuned anode inductance stands upon the panel and is parallel with its short edge, whilst the second is parallel with its long edge. The distance separating each coil from its next door neighbour is 4 in. With this arrangement no interaction of any kind seems to take place, and it is one that may be adopted by experimenters with every confidence for circuits of all kinds.

**Frame Aerial Efficiency.**

I have often wondered if any

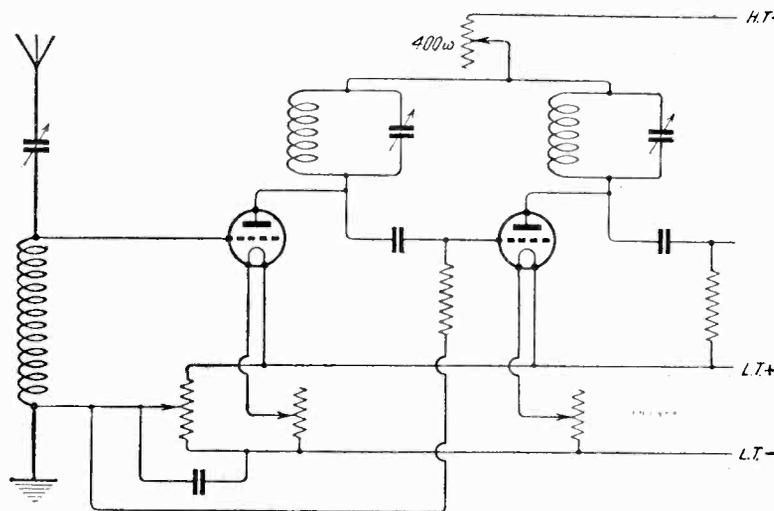


Fig. 4.—The use of a potentiometer in series with the H.T. lead is novel and interesting.

accumulator requires to visit the charging station. The selectivity obtainable is extraordinarily good. At twenty-five miles north-west of London either Cardiff or Manchester can be tuned in without interference from 2LO. 5IT again can be separated from 6 BM, and every British, French and Belgian broadcasting station comes in at good loud-speaker strength, even on the smaller set. I have not so far tried either of these sets on the very short waves, because I have not had the time to make up a suitable set of inductances. But I have very little doubt that they will do quite well, for both are perfectly stable on 300 metres, which is as low as I can tune them with the present set of coils.

definite figure could be given for the efficiency of a frame aerial as compared with an outdoor one in the same locality, but it seems to be a very complicated question. In my own case the outdoor aerial is infinitely superior to any two-foot frame—in fact, with the latter a five-valve set is no more efficient than a crystal and note-magnifier on an outdoor aerial. This I imagine is due to some curious local condition, for quite a short indoor aerial consisting of a suspended wire gives very satisfactory results and is infinitely better than the frame. Mr. Harris puts the frame down at two high-frequency stages worse than the outdoor aerial, whilst another friend who uses both finds that there is

only one high-frequency stage between the two. There is little doubt that when it is used out of doors the frame works much better than it does within doors. If I take my frame down to the bottom of the garden, where it is away from all buildings, the results are quite passable. Another curious point is that the frame is in some cases strongly directional, whilst in others it is not so at all. At my station 2LO comes in best when the frame is pointing about 15 to 20 degrees off its true bearing. This must, I suppose, be due to the presence of gas or water pipes or some other metal objects in the walls. Those who rely upon their frame aerials for detection of howling fiends should be careful before making definite accusations, for bearings taken in this way are frequently most misleading. Not long ago two of us endeavoured

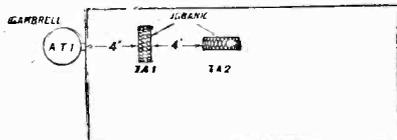


Fig. 5.—Showing how the coils in the author's set are arranged.

to locate a certain bad offender by taking cross bearings from our stations, which are a mile apart. Working very carefully each of us got a definite bearing, and these were plotted out upon a large scale map. You may imagine our surprise when we found that the point of intersection of the straight lines which we had drawn came in the middle of a ploughed field more than half a mile from any house and with no aerial at all anywhere in the neighbourhood. Thinking that we must have made a mistake we did all the work over again on another evening, taking even more trouble over it. The results were exactly the same!

LAMBDA.

### A WARNING

Do not search for stations by making your reaction coupling very tight and then swinging the condenser backwards and forwards in the hope of picking up a carrier wave. If you do this you will be an intolerable nuisance to your neighbours and will completely ruin their enjoyment of signals. If you *must* oscillate use as little reaction as possible and *do not* search near the wavelength of the station which is near to you.

### A Two-Valve Cabinet Receiver—(Continued from page 33).

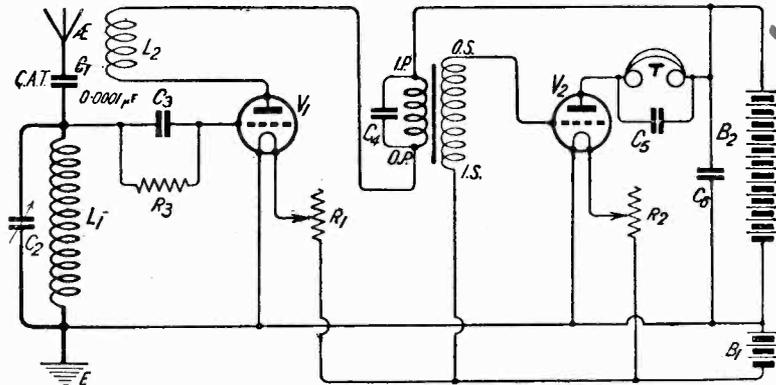


Fig. 6.—The theoretical circuit.

Should the set fail to show any tendency to oscillate, then the absence is indicative of the fact that the connections to the reaction coil should be reversed.

For the reception of the B.B.C. stations working on wavelengths between 400 and 500 metres, the same operations should be gone through, bearing in mind the same precautionary remarks relative to oscillating, using in the aerial socket coil No. 75 and No. 100 in the reaction coil socket.

These operations are precisely the same using either one or two valves.

#### Wavelengths other than B.B.C.

Those readers whose ambition takes them beyond the B.B.C. wavelengths, should, in the case of shipping and wavelengths above, connect the aerial to the terminal A<sub>1</sub>, leaving the A terminal free and with the earth in its normal position, use a No. 50 or 75 in the aerial and a No. 100 for reaction; for aircraft telephony a No. 75 or 100 coil in the aerial with a No. 150 or 200 for reaction; for Radiola a No. 150 in the aerial and a No. 250 or 300 for reaction; for the Eiffel Tower a No. 250 in the aerial and a No. 400 or 500 for reaction, the

operation of the receiver being the same for either one or two valves.

#### Valves.

It will be observed from the photographs that Myers' valves are used, though readers may, of course, use the ordinary four-pin valves

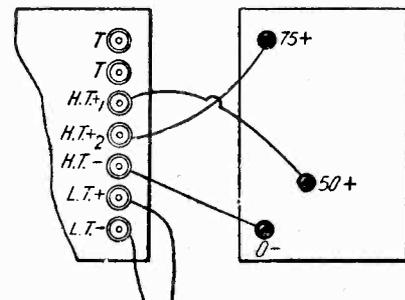


Fig. 8.—Illustrating the H.T. connections. The positions of H.T. + 1 and H.T. + 2 should be found by experiment according to the valves in use.

should their preference lie in that direction.

Whilst testing the set after its completion one of the valves shown was dropped on a tiled hearth without ill effect. This method of treating valves is, however, not to be recommended.

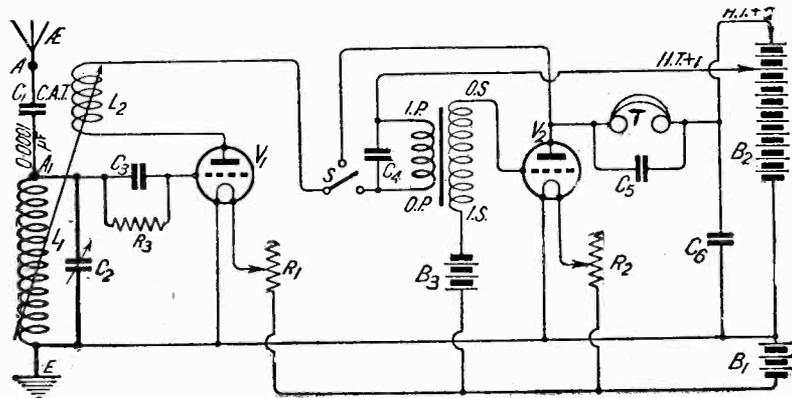


Fig. 7.—The circuit employed in the receiver.

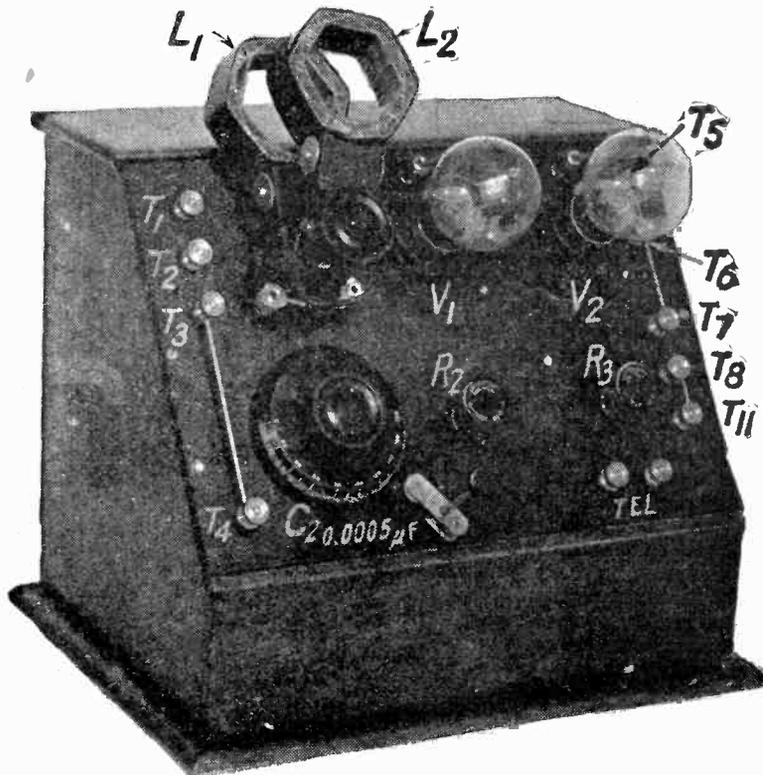


Fig. 1.—The appearance of the completed receiver.

# The “Modern Wireless” High- Tensionless Receiver

By Herbert K. Simpson

*A description of a two-valve set which will give good loud speaker signals without the use of a high-tension battery. The set has the additional advantage that it may also be used with ordinary valves and high-tension battery.*

MUCH attention has been focussed of late upon the problem of eliminating the high-tension battery, and several designs have been put forward with this aim in view. A measure of success has been achieved in some cases, but when one considers the question of working a loud-speaker without the use of an anode battery, the problem assumes greater proportions.

By the use of valves of the four-electrode type, however, quite good loud-speaker signals are obtainable up to about 15 miles on two valves, the first acting as a rectifier, with reaction, and the second being a note magnifier. Apart from the valves, all the components used are of quite standard design, no special parts being required. The valves are obtainable from Messrs. Leslie Dixon, of 9, Colonial Avenue, Minories, London, E.1, and, to ensure the correct type being obtained, reference may conveniently be made to this article.

The appearance of the finished set is seen in the photograph, Fig. 1.  $L_1$  is the aerial coil, being that plugged into the lower socket of the two-coil holder. The upper socket is that holding the reaction coil  $L_2$ , from which two rubber-covered flexible leads terminating in Clix plugs are led to two Clix sockets upon the panel. By this

means the reaction coil may be easily reversed when required.  $C_2$  is the aerial tuning condenser of  $0.0005\mu F$ . capacity.

On the left of the set are seen four terminals, by means of which the three chief forms of aerial tuning, namely, constant aerial, series, or parallel tuning may be employed. On the right of the set are seen five terminals, which enable high-tension to be applied when desired.

acting as a rectifier, reaction being provided by means of the coil  $L_2$  being coupled to the aerial coil  $L_1$ , while the second valve,  $V_2$ , is purely a note magnifier. A terminal  $T_{11}$ , for grid bias, is provided in order that the experimenter may be sure that the valve,  $V_2$ , is acting properly as an amplifier. When no grid bias is used, this terminal must be shorted to the terminal  $T_8$  immediately above it.

### Circuit Diagram

A circuit diagram is given in Fig. 2, and it will be seen that two valves are employed, the first,  $V_1$ ,

### Constant Aerial Tuning

The constant aerial tuning system may be applied to this receiver by joining the aerial lead to  $T_1$ , leaving  $T_2$  free, and connecting  $T_3$  to  $T_4$

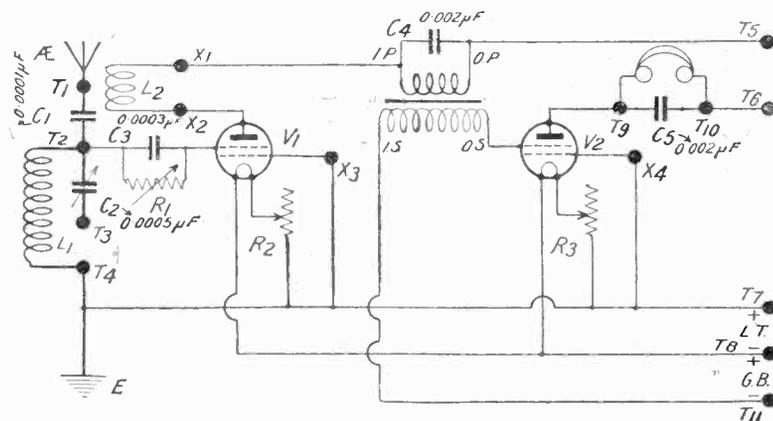


Fig. 2.—The arrangement of the circuit.



and to earth. Tuning is carried out on the variable condenser  $C_2$ , which is in parallel with the coil  $L_1$ . Parallel tuning, with no constant aerial tuning, may be used by joining the aerial lead to  $T_2$ , leaving  $T_1$  free, and joining  $T_3$  to  $T_4$ , and to earth. Tuning is carried out, as before, on  $C_2$ .

**Series Tuning**

The aerial tuning condenser  $C_2$  may be placed in series with the aerial tuning coil by joining the aerial lead to  $T_3$ , leaving  $T_1$  and  $T_2$  free, and the earth to  $T_4$ .

The inner grids of the valves, which are connected to a terminal on the cap of the valve, in the case of the valves mentioned, are joined to L.T. positive, by means of flexible leads from the terminals mentioned to Clix plugs, which plug in to Clix sockets  $X_3$  and  $X_4$  on the panel. The valves plug in to the usual four-pin socket.

**Components and Cost**

As has been mentioned, no specially made components, apart from the valves, are employed, and those used are easily obtainable. The constructor may use such parts as he may already possess, but it is always desirable to adhere as closely as possible to the specification given:—

<i>Components.</i>		£	s.	d.
Cabinet (Wright and Palmer, Type W.1)	.. .. .	16	0	0
Panel, 12 in. by 8 in. by $\frac{1}{4}$ in. (Paragon Rubber Co.)	.. .. .	6	0	0
2-coil holder (Goswell Engineering Co., Type V)	.. .. .	7	6	0
11 Terminals, 4 B.A., at 2d.	.. .. .	1	10	0
1 0.0005 $\mu$ F. variable condenser (K. Raymond, new type, with dial)	.. .. .	5	7	0
2 Lissenstat filament resistances (Lissen, Ltd.)	.. .. .	15	0	0
1 Lissen variable grid leak (Lissen, Ltd.)	.. .. .	2	6	0
1 0.0001 $\mu$ F. fixed condenser (Lissen, Ltd.)	.. .. .	2	0	0
1 0.0003 $\mu$ F. fixed condenser (Lissen, Ltd.)	.. .. .	2	0	0
2 0.002 $\mu$ F. fixed condensers (Lissen, Ltd.)	.. .. .	5	0	0
1 Fynetune Vernier Adjuster (Sparks Radio Supplies)	.. .. .	2	6	0
2 H.T.C. valve holders, Type A (H.T.C. Electrical Co.)	.. .. .	3	6	0
4 Clix, with insulator and locknut, at 4d. (Autoveyors)	.. .. .	1	4	0
4 Clix, with locknut only, at 3 $\frac{1}{2}$ d. (Autoveyors)	.. .. .	1	2	0
1 Powquip L.F. transformer (Power Equipment Co.)	.. .. .	14	6	0
10 ft. tinned bus-bar wire (Sparks Radio Supplies)	.. .. .		10	0
Screws, etc.	.. .. .		4	0
Total	.. .. .	£4	7	7

The valve holders are of a good type, combining safety with low capacity; no metal parts are exposed, thus it is practically impossible to short the filament of the valve across the high-tension supply, when one is used. The metal parts are as far as possible apart, thus ensuring minimum capacity in the socket.

**The Panel**

A half-size drawing showing the

not constant for any given make of transformer. The positions of all holes should be marked out with a sharp-pointed instrument, and all holes of one size drilled first. A template is supplied with each valve holder, ensuring correct drilling. A close-up photograph of the panel is seen in Fig. 5, which makes the layout quite clear.

**Mounting the Parts**

All holes being drilled; the

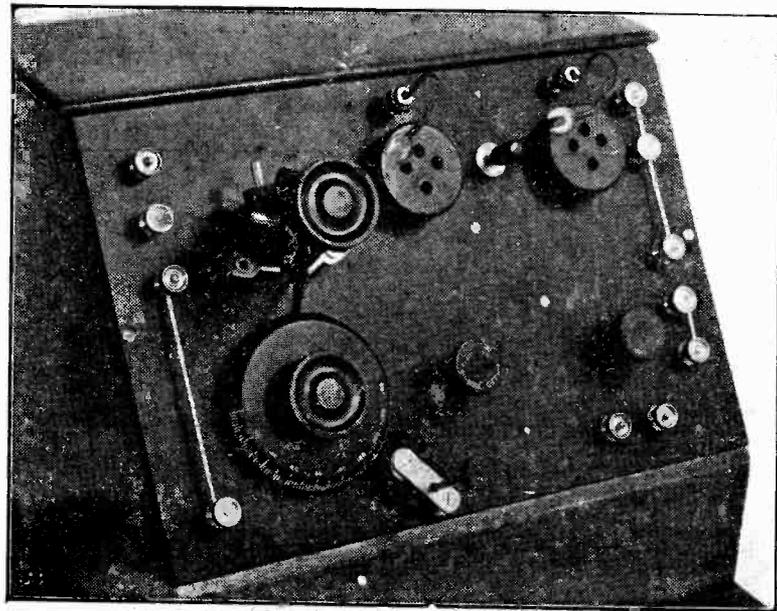


Fig. 5.—The lay-out of parts on the panel. Note the fine adjustment for the tuning condenser.

smallest parts should be mounted up first, leaving such heavy parts as the variable condenser and transformer until the last. When all parts are mounted up, give an extra turn to all the nuts holding parts in position, to ensure that they are all tight. The fixed condensers are not secured to the panel, being held in position by the wiring. The "Fynetune" vernier adjuster on the variable condenser should be laid on the panel and a hole drilled in such a position that the rubber ring bears fairly hard against the dial of the condenser.


**Wiring**

Wiring is carried out with square bus-bar wire, obtained from Sparks Radio Supplies, and presents a very neat and workmanlike appearance. It is also possible to space the wiring out to a better degree than is possible when using systotex covered wire. All points, such as terminal shanks, to which a wire has to be joined, should be well tinned before wiring is commenced, as this makes the process much simpler. Bend the wire to the exact shape before commencing to solder, as the stiffness of the wire will make it difficult to bend without fracturing the joint once it is soldered to any point. A wiring diagram is seen in Fig. 7, and will make the wiring perfectly clear. Figs. 3 and 6 are photographs of the back of the panel.

**The Cabinet**

The cabinet is of the sloping front type, and was obtained from

(Continued on p. 43).

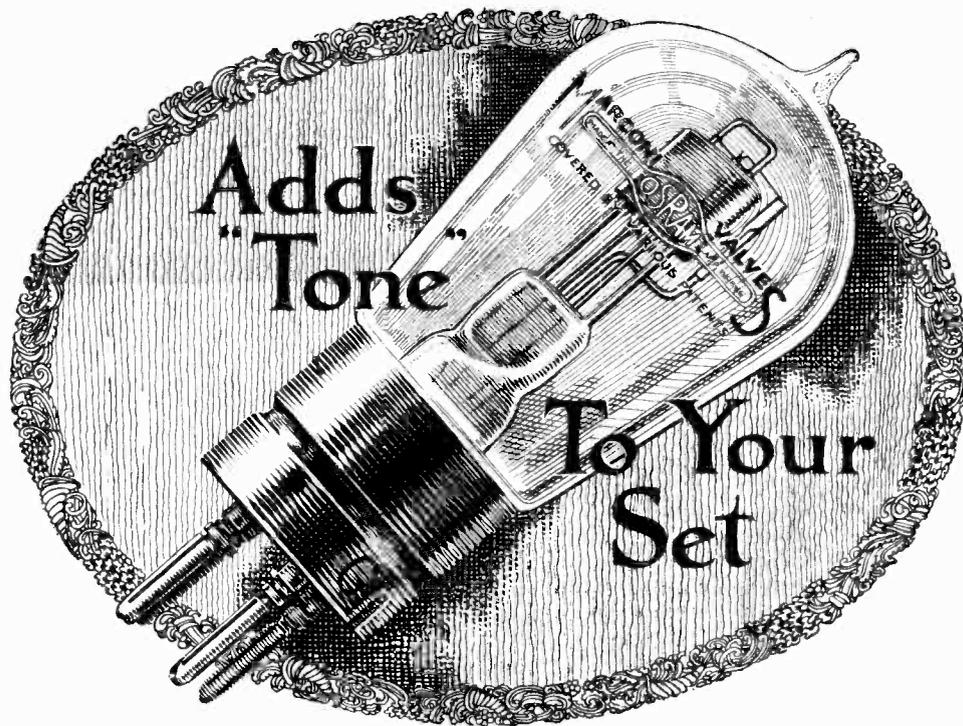

If you have not already tried

# MARCONI VALVES

MADE AT THE OSRAM LAMP WORKS

in your receiver, take the earliest opportunity of doing so, you will be both amazed and delighted with the results.

For both sending and receiving **MARCONI VALVES** have achieved an enviable reputation for

**MAXIMUM RESULTS — RELIABILITY  
LONG LIFE AND ECONOMY.**

You cannot do better than follow the lead given by the largest wireless users to-day and specify



*Sold by all leading Wireless Dealers, Contractors, Stores, etc.*

**BUY BRITISH GOODS ONLY.**

*Visit the  
G.E.C.  
PAVILION  
British Empire  
Exhibition.  
(Palace of  
Engineering.)*



Advt. of THE GENERAL ELECTRIC CO., LTD., Magnet House, Kingsway, London, W.C. 2.

*In replying to advertisers, use COUPON on last page*

# Brandes

*The Name to Know in Radio*



*Result of  
15 years'  
experience*

## **Grandpa a defaulter.**

A running fire of comment on Grandpa's continued absence from the Club. Truth to tell, he is finding that a variation of his habitual custom provides a welcome diversion--he is finding that there are other things besides being lost in a fierce argument. Brandes are convincing him that his appreciation of good music has not deteriorated and that the "Matched Tone" brings perfect reproduction of the broadcast programme. His smoke-room friends deplore this backsliding, but Grandpa knows he's "on" a good thing. Try Brandes--your Dealer has them.

**PRICE**  
**25/-**

*British manufacture  
(B.B.C. Stamped) and  
conform to all new  
licensing regulations.*

*Manufactured at Slough, Bucks, by*

**Brandes Limited, Walmar House, 296, Regent St., London, W.1.**  
Glasgow--47, Waterloo Street. Newcastle--5/6, Post Office Chambers.

# *Matched Tone*

TRADE MARK

## **Radio Headphones**

*Telephone :-- Mayfair  
4208-----4209  
Trade Inquiries Invited*



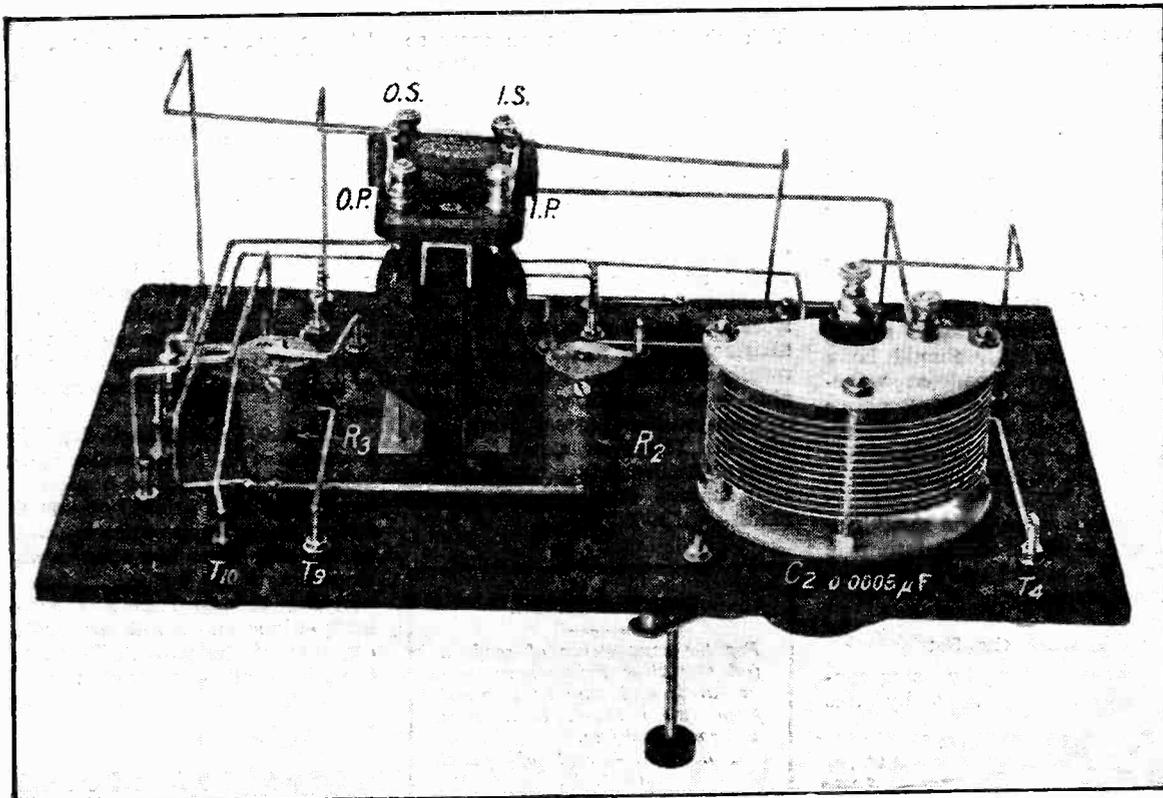


Fig. 6.—A view of the underside of the panel, showing the filament resistances,

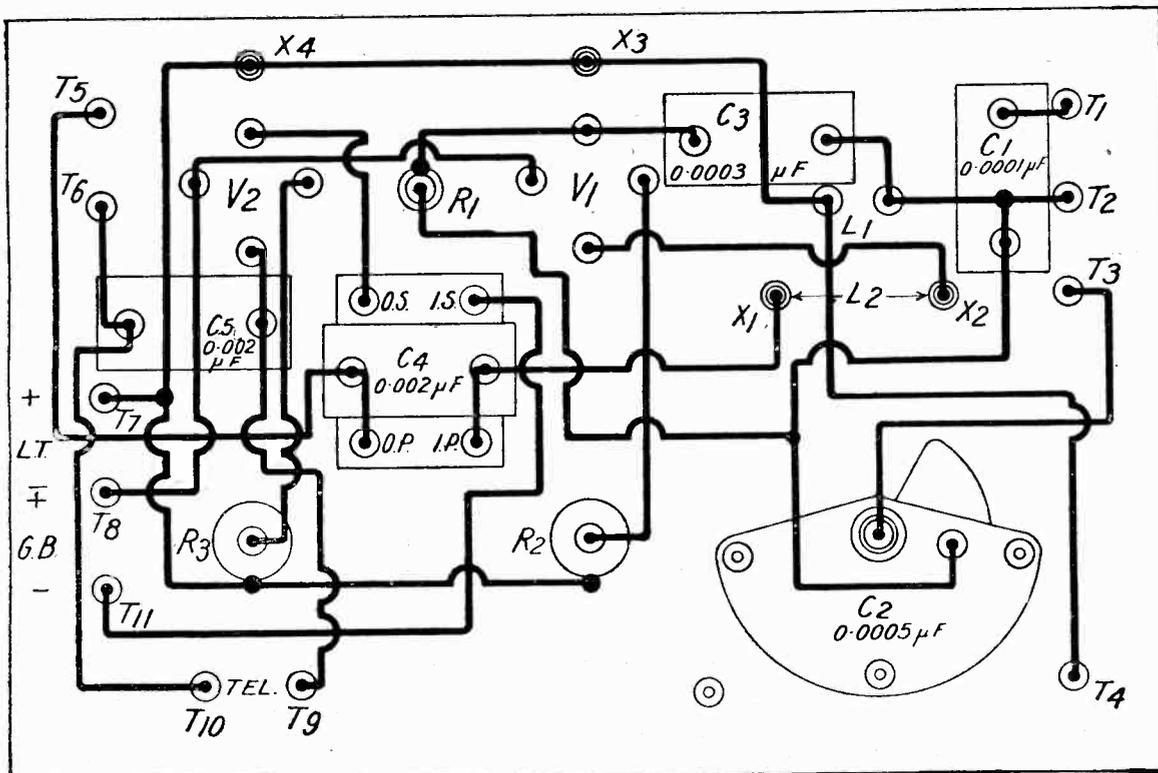


Fig. 7.—The wiring of the receiver. The lettering conforms with that of Fig. 2.

Messrs. Wright and Palmer, of Forest Gate. It is known as the type W1 cabinet, and may be obtained, at short notice, from this firm. For those who propose to make their own cabinet, a dimensioned drawing is given in Fig. 8, and no difficulty should be experienced in the construction. The panel is secured to the cabinet by means of two wood screws, one in the middle of each of the shorter sides.

**Coils to Use**

Using the constant aerial tuning system, the coil L<sub>1</sub> should be a number 50 for broadcast wavelengths up to 420 metres, above which a 75 may be used. The reaction coil L<sub>2</sub>, the movable one in the two-coil holder, should be a No. 75.

A 6-volt accumulator should be used, and is joined to the terminals T<sub>7</sub> and T<sub>8</sub>, in the order positive-negative respectively.

**Testing the Set**

Commence testing by using constant aerial tuning, as by this

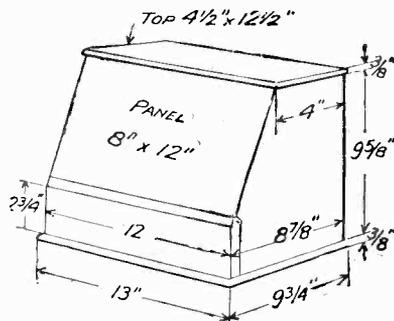


Fig. 8.—A dimensioned view of the cabinet.

means the local station will be easily picked up. Connect the aerial to T<sub>1</sub>, earth to T<sub>4</sub>, and join T<sub>3</sub> to T<sub>4</sub> by means of a piece of wire. Join T<sub>5</sub>, T<sub>6</sub> and T<sub>7</sub> together, and also join T<sub>8</sub> to T<sub>11</sub>, thus using no extra grid bias.

Insert a 50 coil in the lower socket of the coil holder, and a 75 coil in the upper, provided that the wave-length of the station to be received is under 420 metres. If the wave-length is over 420 metres, the aerial coil L<sub>1</sub> may be a 75, and the reaction a 100. Insert the valves and join the fourth electrodes to the Clix sockets upon the panel behind each valve-holder.

Connect the telephones to the terminals marked in Fig. 1, and turn on the filaments of the valves, keeping the moving coil L<sub>2</sub> well away from the fixed coil L<sub>1</sub>. Tune on the condenser C<sub>2</sub>, and when the

local station is heard, bring L<sub>2</sub> closer to L<sub>1</sub>, re-tuning on C<sub>2</sub>. This should result in an increase of signal strength, and if this is not the case, the leads from the reaction coil L<sub>2</sub> to the Clix sockets X<sub>1</sub> and X<sub>2</sub> should be reversed.

**Test Report**

This set was tested out on a standard aerial at 10 miles from 2LO, and results were quite pleasing. A loud-speaker was worked at medium strength—quite satisfactory for many people, but results did not equal those obtainable when ordinary valves and a high-tension battery were employed. The alternative arrangements which may be tried on the set enable comparisons to be made.—J. S.-T.

**BLUE PRINTS.**

For the convenience of readers, full size Blue Prints have been prepared, and may be obtained from Radio Press, Ltd., price 1/6 each, post free.

- No. 47A.—Front of panel (Fig. 4).
- No. 47B.—Back of panel (Fig. 7).

**"A Simple Reflex Set"**

To the Editor of MODERN WIRELESS

SIR,—I feel I must write and thank you for giving the details of Simple Reflex Circuit in January MODERN WIRELESS. I built up the set last Saturday and have since got the following results (all telephony) with two pairs of 'phones: Saturday night, Birmingham too loud for phones; Sunday morning, amateurs as far away as Banbury and also 2 HS. After Birmingham had closed down, I got Aberdeen (over 400 miles), Bournemouth, London and another station, but did not wait for his call sign. Then to my surprise a Continental station quite readable, but as I did not understand the language I could not say if it was Brussels or P and T, Paris. Last night I found, to my surprise, I could get Bournemouth, London or Cardiff whilst Birmingham was carrying on as usual, although I am only three miles distant.

I am, etc.,  
F. J. NOON.

Birmingham.

**A New Idea for the Constructor**

"The next best thing to having the set in front of you."


RADIO PRESS are about to publish No. 1 of a new series of constructor's guides which should prove of immense help to the experimenter who likes to get a very clear idea of his proposed set before he starts work.

"Radio Press Panel Card No. 1 consists of an envelope containing a flat cardboard model of the panel itself, printed on one side with a photograph of the top of the panel, and upon the other with a drawing of the wiring. Accompanying the card is a sheet of instructions and a full size drilling diagram of the panel. The Panel Card will sell at 1s., and the date of publication is announced elsewhere.

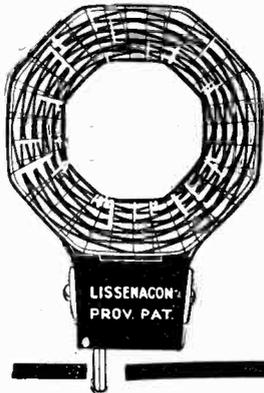**New Radio Press Envelopes**

AS announced in detail in the advertisement pages of this issue, two additions are about to be made to the series of Radio Press Envelopes. These two sets will be of great interest to the constructor, representing as they do the product of two designers working upon widely divergent lines. Envelope No. 3 concerns a three-valve set which has been christened the "Simplicity" receiver, which was designed on the assumption that the average user will obtain actually better results with a very simple set than with one of more elaborate design and difficult operation, while Envelope No. 4 gives instructions for making a "de Luxe" model of the well-known "All-Concert" three-valve receiver, with totally enclosed valves, switching devices, square-law condensers, and other refinements.

The author of Envelope No. 3 is G. P. Kendall, B.Sc., Staff Editor, MODERN WIRELESS, and No. 4 is the work of Percy W. HARRIS, Assistant Editor, MODERN WIRELESS. The price of each is 2s. 6d., post free 2s. 9d., and the date of publication is given in the detailed announcements.



# A GOOD INDUCTANCE

—what it means to your receiver.

**Y**OU may have noticed how a small fragment of cork floating on water is sensitive to every movement of the surface. A large piece of cork would not be so sensitive. This is due, among other things, to the phenomenon of inertia, which is common to all physical bodies.

Inertia and friction losses, for instance, which, in a physical body, make that body more or less difficult to move, can be likened to losses in coils which uselessly absorb the vital energy which ought to be fully transferred and applied.

LISSENAGON coils are to other coils what a fine mirror spot-light galvanometer, for instance, is to a linesman's galvanometer. Both are galvanometers, both are the same in so far as they are used to detect electrical currents, but the former will detect currents in circuits where no deflection of the needle at all could be obtained with the linesman's instrument.

Users of coils should submit them to the test of distant telephony. LISSENAGON coils are splendidly responsive to faint signals in the same way as the fine mirror galvanometer is to minute electrical currents.

The analogy between LISSENAGON coils and the mirror galvanometer can be strikingly proved by alternatively plugging in LISSENAGON coils on distant signals and then plugging in other coils. Distant stations that will be distinct on LISSENAGON coils often cannot be heard at all as soon as the other coils have been substituted.

In the design and making of LISSENAGON coils provision has been made for the fact that low wavelength coils have to deal with enormously higher frequencies than high wavelength coils. Each LISSENAGON coil has been designed to be strongly resonant to a certain pre-determined band of frequencies. The appropriate LISSENAGON coil for a given wavelength is more resonant to the frequency corresponding to that wavelength than any other make of coil, and will also more effectively bar out all frequencies except that to which it is definitely tuned—in other words, LISSENAGON coils are highly selective, and the circuits in which they are used can be much more sharply tuned than the same circuits when other coils are used. This gives LISSENAGON coils an immense advantage on distant telephony. LISSENAGON coils are interchangeable with any other coils.

**LISSENAGON COILS TUNE SO SHARPLY & STRONGLY BECAUSE THEY TUNE WITHOUT ENERGY LOSS. HOLD A LISSENAGON COIL UP TO THE LIGHT.**

**WHY USE MIXED PARTS?** There is a LISSEN part for every vital place of your receiver. We guarantee every LISSEN part to satisfy you perfectly—we EXPECT TO HEAR FROM YOU IF YOU ARE NOT SATISFIED.

If you use mixed parts your finished instrument will never give you the same results as a receiver BUILT WITH ALL LISSEN PARTS.

LISSENAGON TUNING CHART. Note the Intermediate Coils, 30, 40 and 60.

TABLE 1. Wavelength range when used as Primary Coils with Standard P.M.G. Aerial and .001 mfd. condenser in parallel.			TABLE 2. Wavelength range when used as Secondary Coils with .001 mfd. condenser in parallel.		
No. of coil	Minimum Wavelength	Maximum Wavelength	Minimum Wavelength	Maximum Wavelength	PRICE
25	185	350	100	325	4/10
30	235	440	130	425	4/10
35	285	530	160	490	4/10
40	360	675	200	635	4/10
50	480	850	250	800	5/-
60	600	950	295	900	5/4
75	600	1,300	360	1,100	5/4
100	820	1,700	500	1,550	6/9
150	965	2,300	700	2,150	7/7
200	1,885	3,200	925	3,000	8/5
250	2,300	3,800	1,100	3,600	8/9
300	2,500	4,600	1,400	4,300	9/2

A good deal of useful information is given in the Text Book of LISSEN PARTS.  
Post free, 8d. Free to the Trade.

**LISSEN LIMITED,** 20-24, Woodger Road, Goldhawk Road, Shepherd's Bush,  
LONDON, W.12.


Telephones: Hammersmith 3380, 3381, 3382 & 1072.  
Telegrams (Inland): "Lissenium, Shepherds, London,"  
" (Foreign): "Lissenium, London."

**BUILD—WITH LISSEN MASTER PARTS.**

# Reasons why EDISWAN VALVES Are Better
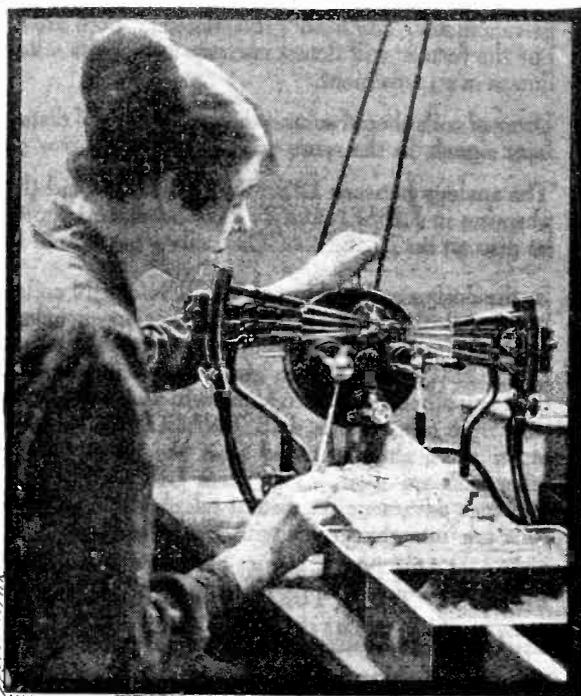
## Funnelling the Stem

The second stage consists of "reaming out" the glass stem to give the required funnel shape—a process necessitating extreme care to ensure exact registration with the bulb. By means of an ingenious arrangement of burners, the glass, rotated on a disc, is subjected to gradually intensified heat and when the required temperature is reached, the actual "funnelling" is performed by hand. In this process the high degree of skill attained, combined with adequate supervision, serves to maintain the essentially exacting standard of "Ediswan" reliability.



**PRICES.**

"R" - - 12/6

"A.R." - 12/6

"A.R.D.E." 21/-

Dull Emitter.

"A.R.05." 30/-

Latest Dull Emitter.


Current consumption  
at 25 volts, '06 of an  
ampere.

*Note the safety cap (Pro-  
Pat.) which is now fitted  
to all Ediswan Valves.  
The filament pins are  
shorter in length than the  
plate and grid  
pins, thus avoid-  
ing any chance of  
making surface  
contacts with the  
wrong sockets.*

Have you had your **FREE** copy of illustrated  
Booklet, "The Thermionic Valve?" If not,  
send a postcard to-day.

Also Manufacturers of the "Toovee"  
"Televox" Loud Speaker, Headphones,  
Batteries, etc. Write to-day for leaflets.

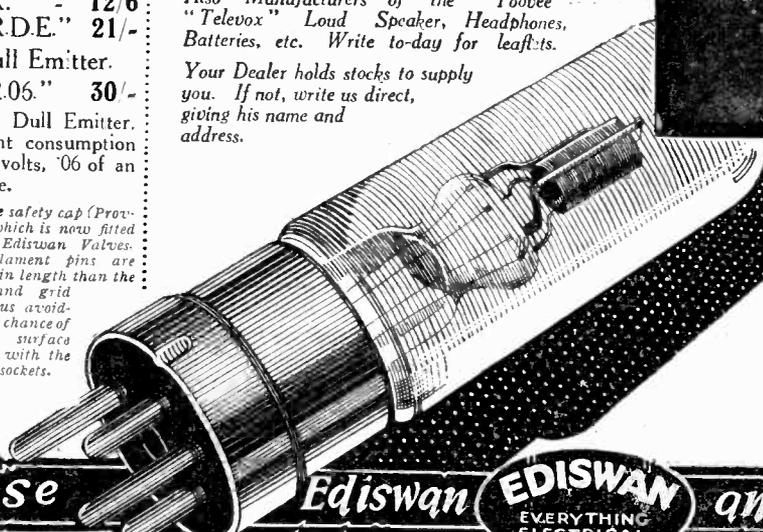Your Dealer holds stocks to supply  
you. If not, write us direct,  
giving his name and  
address.



**THE EDISON SWAN  
ELECTRIC CO., LTD.,**

Contractors to H.M. Admiralty,  
War Office, Royal Air Force.

123/5, Queen Victoria Street, E.C.4  
and 71, Victoria Street, S.W.1.

Branches in all Principal Towns.  
Works: Ponders End, Middlesex.

Use

Ediswan



and hear Everything

Buy British Goods Only.

In replying to advertisers, use **COUPON** on last page

# The Cowper High-Tensionless Circuit

## A Remarkable New Receiver for any Valve

MR. A. D. COWPER, whose remarkable work in evolving new circuits is a feature in both *Wireless Weekly* and MODERN WIRELESS, has now produced a most interesting form of single-valve circuit which will operate without any separate high-tension battery and has the particular advantage of being usable with any types of bright or dull emitter. For example, it has been used quite successfully with the .06 ampere type of dull emitter, the sole battery supply for the whole set being a 4½ volts flash-lamp battery.

The new Cowper circuit, which was first described in *Wireless Weekly* for May 28th, has aroused so much interest that we are reproducing it below. The following technical particulars will enable those of our readers who so desire to build up the set in practical form.


Constant aerial tuning is used in

this set and is necessary in order to obtain oscillation when required. A .0001 mfd. fixed condenser of good make should be used here, and for tuning a No. 50 or 75 coil shunted by a suitable variable condenser of, say, .0003 or .0005 mfd. A grid condenser of .0003  $\mu$ F is used without a gridleak, connection being made to the grid as shown. The plate circuit is taken from the plate of the valve to a reaction coil (a No. 75, 100 or 150 will do here), through the telephones, the primary of a good intervalve transformer to the positive end of the filament battery. The secondary of this transformer is connected at one end to the slider of a standard potentiometer, the other end being connected to a radio-frequency choke coil (a 250 plug-in coil suits here) and thence to the grid.

The operation of the set is quite simple. Tuning is carried out in

the ordinary way, and the reaction coil is brought up against the aerial tuning coil until the maximum amplitude is obtained. It will be found that at one position of the potentiometer the set will give a violent audio-frequency howl, and by bringing the slider of the potentiometer towards the other end the howl will be lessened until a point is reached where it ceases. This is the best point of adjustment. Actually, the circuit operates in a peculiar manner, and audio-frequency reaction, controlled by the potentiometer, is used.

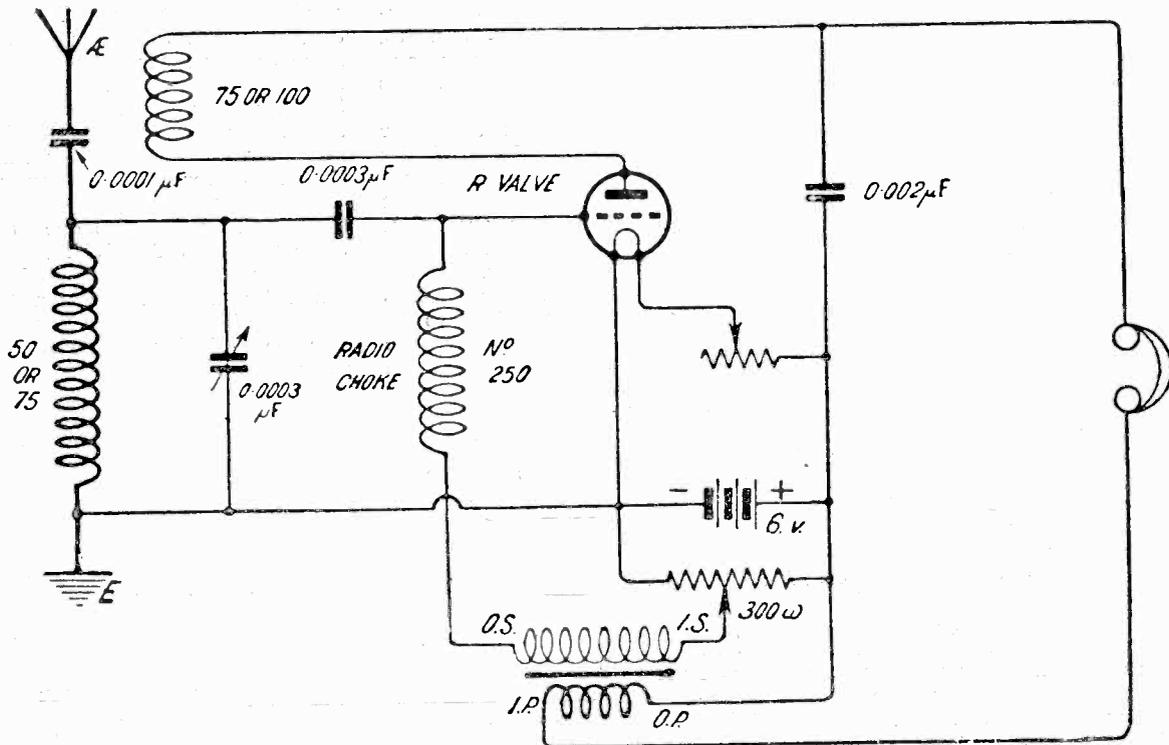Full practical details of how to build a receiver on these lines will be given by Mr. Percy W. Harris in the issue for *Wireless Weekly* dated June 4th. Readers should place their orders in advance. On this date a special series of articles on the whole question of high-tensionless receivers will begin.



The new Cowper circuit.

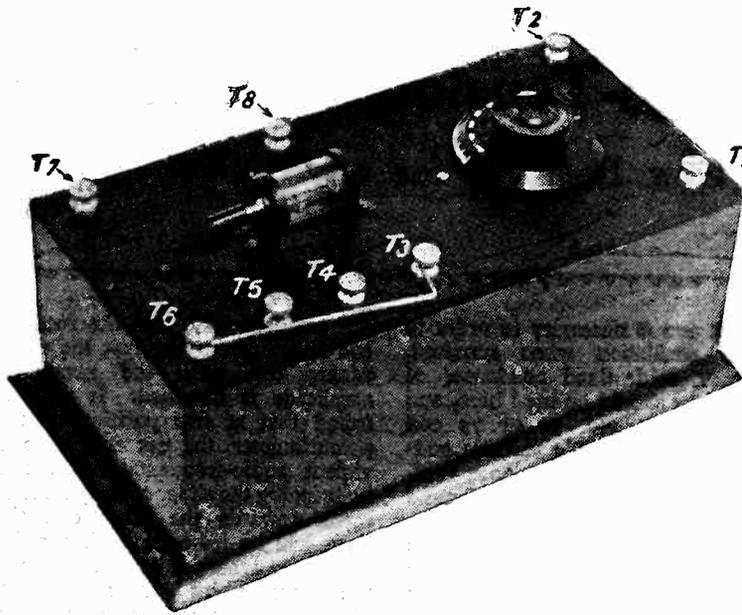


Fig. 1.—Many original ideas are incorporated in this instrument.

# A Crystal Receiver

## With Special Coupling.

Special "Modern Wireless" Design

*In this set special arrangements are made for giving high selectivity. The instrument may also be used as a separate tuner.*

MANY users of crystal receivers, who dwell in regions near the coast, are troubled with interference from ships, and often spark signals from land stations; in most cases it is found impossible to tune out these signals with the tuning arrangements provided in the receiver. Some form of coupled circuit is essential in these cases, and possibly the simplest is that in which the aerial coil consists of a few turns of wire wound immediately on top of the tuning coil, the aerial coil itself being untuned. A set on these lines was described by Mr. Percy W. Harris in *Wireless Weekly* for September 19, 1923. The present set follows the same general form, but provision is made whereby the crystal detector and telephones may be tapped across a part of the closed circuit inductance, thereby reducing the damping in that circuit and so increasing its selectivity. There is the additional advantage of the coupling arrangement that the receiver may be used on any aerial without affecting the tuning of the closed circuit. Great selectivity is obtained by this coupling, but a greater effect is obtained by tapping the crystal detector across only a part of the coil, thereby allowing the closed circuit to oscillate more freely, owing to the reduced damping. Apart from selectivity, the circuit design is a highly efficient one from the point of view of signal strength.

The "aperiodic" method of aerial coupling has been incorporated in the present set, and

this, together with the tapped detector and the use of thick (No. 18) wire, accounts for the good results obtainable. A photograph of the finished set will be seen in Fig. 1, and the terminals on the right of the receiver are those to which the aerial and earth connections are made, the former to T<sub>1</sub> and the latter to T<sub>2</sub>.

The telephone receivers are connected to terminals T<sub>7</sub> and T<sub>8</sub>, while the crystal detector and telephones may be tapped across part of the coil by joining the terminal T<sub>3</sub> to one of the other three terminals T<sub>3</sub>, T<sub>4</sub> or T<sub>5</sub>, by means of the link, which latter is a piece of square-section wire bent so as to have two arms, one 4½ in. long and the other 1 in. long, at right angles to each other. At the end of the shorter arm a hook is formed to enable the link to be easily and quickly secured to the two terminals required to be joined.

### Circuit Diagram.

The circuit arrangement of the receiver is shown in Fig. 2. T<sub>1</sub> is the aerial terminal, the earth lead being joined to T<sub>2</sub>. L<sub>2</sub> is the main inductance, and consists of 80 turns of No. 18 s.w.g. double cotton-covered wire, wound on a cardboard tube 3 in. in diameter, 6½ in. long, tapped at the 26th, 52nd and 80th turns. The aerial coil, L<sub>1</sub>, consists of 10 turns of the same size wire, wound on top of the first coil, between the 52nd and 80th windings. In this diagram a wandering lead is shown with an arrow-head pointing to terminal T<sub>4</sub>. This represents the external link previously mentioned, by means of which T<sub>4</sub> is joined to one of the three terminals T<sub>3</sub>, T<sub>4</sub>, T<sub>5</sub>. The closed circuit inductance L<sub>2</sub> is tuned by the variable condenser C<sub>1</sub>, which has a maximum capacity of 0.0003 μF, this condenser being permanently connected across the


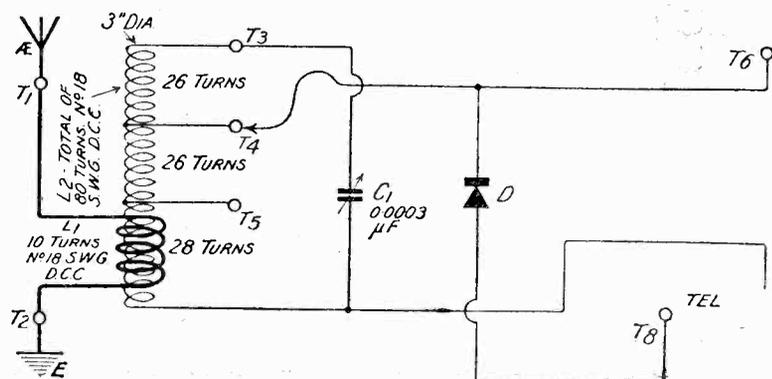


Fig. 2.—The circuit arrangement.
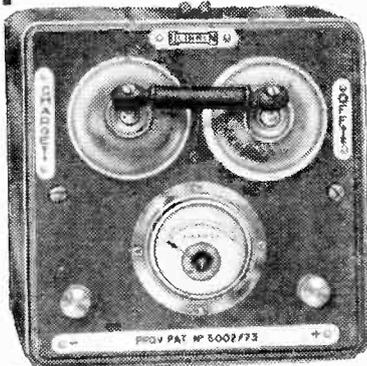
# ULINKIN

(Prov. Pat. No. 5002/23)

**THE D.C. HOME BATTERY CHARGER**  
**Charges Accumulators at Home**  
*Free of all Cost!*



If you have a Direct Current lighting or power circuit of any voltage, the ULINKIN is all you need to charge your own accumulators at home.

The ULINKIN is easily and simply fixed, within a few minutes to your existing circuit, and is then ready for immediate use at all times.

To charge, you simply connect the accumulator to the two terminals on the ULINKIN and switch on. Then, whenever you are using electricity for lighting or heating purposes in any part of your house, the ULINKIN charges your accumulators without consuming any extra current, and therefore free of all cost.

**AUTOMATIC IN ACTION.**  
**NO LAMPS — NO NOISE.**

*Requires no attention and cannot go wrong.*

Price **£2 : 2 : 0** Carriage Free.


Complete with simple instructions for fixing.

**Cut out your present cost and inconvenience by installing a ULINKIN To-day.**  
*Illustrated Pamphlet and full particulars post free on request.*

Sole Distributing Agents:

*Trade Enquiries Invited.*

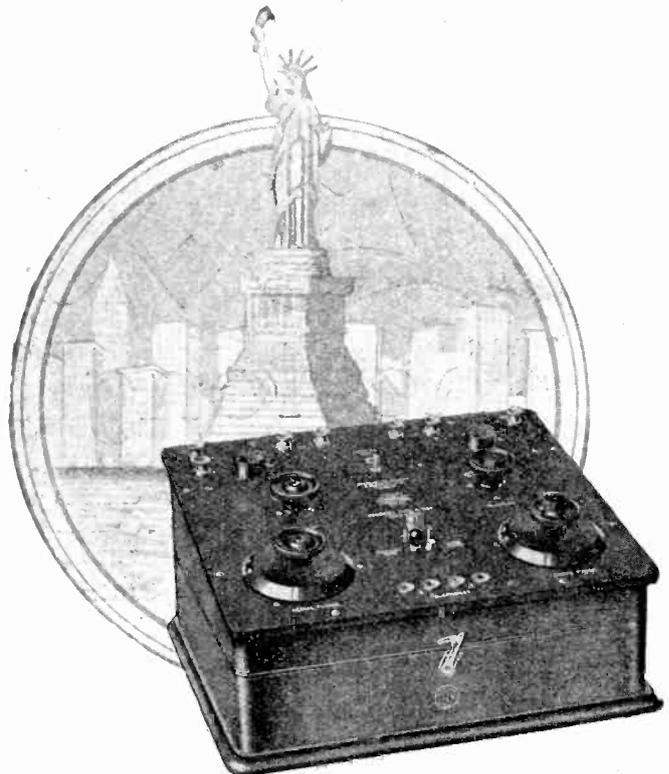**The GRAN-GOLDMAN SERVICE,**  
 (Dept. M9), 71, Fleet Street, London, E.C.4.



## The Sterling "Anodion"

Long Range Two-Valve Receiver

*Best for Long Distance Results*

This Sterling two-valve set has achieved some wonderful long-distance results under favourable conditions and is consistently perfect in performance for all ordinary reception. There is the "Sterling" touch in its workmanship and finish. It is an instrument the experimenter will approve of — compact, efficient and moderately priced.

The "Anodion" is adaptable for reception on all wave-lengths up to 3,000 metres. As supplied it is fitted for British broadcast reception only. The Set as shown, in highly-finished half-hinged walnut case, with sloping panel. B.B.C. Tariff, extra 15/- net. **£9:9:0**

Valves, batteries, head telephones, coils and additional reaction units supplied at extra cost, full particulars of which may be obtained by writing for

**STERLING PUBLICATION M.W. 364B.**

*Obtain from your dealer!*

Advt. of **STERLING TELEPHONE & ELECTRIC Co. Ltd.**  
 210-212, Tottenham Court Rd., London, W.1 Works: Dagenham, Essex.

## Diamond Sunflower


INDUCTANCE

COILS

**THE MOST EFFICIENT COILS**

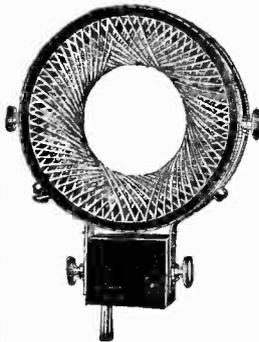**THAT HAVE EVER BEEN PRODUCED**

Give sharpest tuning and maximum signal strength by reason of their revolutionary design.



They are a network of interwoven squares suspended on an ebonite former; the windings are so separated by air passages that self-capacity is practically nil. Their H.F. resistance is the lowest yet obtained. A wider range of position is afforded owing to the special mounting of the coil plug.

No.	20	30	50	70	90	110
..	4/6	4/9	5/0	5/3	5/6	5/9

etc.  
 Standard Plugs to fit all sizes, 1/- each.

The "Diamond Sunflower" Coils are made in all sizes from 20 upwards. Coil against coil "Diamond Sunflower" give the best results. You have only to try them once, then you will use them always. Crystal users are especially recommended the "Diamond Sunflower" coil for receiving the new long wave London Station. If your dealer is out of stock send direct. Table of approximate wavelengths and full list of prices may be had from

**DIAMOND WIRELESS LTD.,**  
 184a, OXFORD STREET, LONDON, W.1  
 Near Oxford Circus. Phone: Museum 1380

# Exide

## The long life battery.

The superiority of EXIDE Batteries for every class of Radio work is unchallenged.

Battery buyers may need some guidance as to the best type of battery for a particular purpose.

We therefore publish the following

*Cut this out for reference.*

### TABLE OF RECOMMENDATIONS

AND BURNING HOURS BETWEEN CHARGES.

Type of Valve.	1 Valve	2 Valves	3 Valves	4 Valves	5 Valves	Battery Type.	Burning Hours.	Price.
Ordinary Bright Emitter ..	3 CZ 2-1 28 33/6	3 CZ 4-1 28 48/-	3 CZ 6-1 28 63/-	3 CX 5-1 26 78/6	3 CX 6-1 25 89/-	Battery Type.	Burning Hours.	Price.
Type "R" Dull Emitter ..	1 HZ 2 100 17/6	1 HZ 2 40 17/6	1 HZ 3 40 21/-	1 HZ 4 40 24/6	1 IJZ 4 30 24/6	Battery Type.	Burning Hours.	Price.
Pea-nut Dull Emitter ..	1 DTG 36 5/-	1 HZ 2 75 17/6	1 HZ 2 43 17/6	1 HZ 3 50 21/-	1 HZ 3 37 21/-	Battery Type.	Burning Hours.	Price.
'06 Amp. Dull Emitter ..	2 DTG 200 10/-	2 DTG 106 10/-	2 DTG 60 10/-	2 DTG 38 10/-	2 DTG 27 10/-	Battery Type.	Burning Hours.	Price.

Prices are uncharged, without acid, except the DTG type, which is supplied fully charged and needs only acid adding to be ready for service.

High Tension Batteries and other types of LT Batteries are listed in Catalogue W.M.—ASK FOR COPY.

Order now from Dealers or Exide Service Agents.

THE **Chloride** ELECTRICAL STORAGE COMPANY LIMITED.




CLIFTON JUNCTION,  
Nr. Manchester.



LONDON:  
219/229, Shaftesbury  
Avenue, W.C.2.

BIRMINGHAM: 57/58, Dale End.

MANCHESTER: 1, Bridge Street.

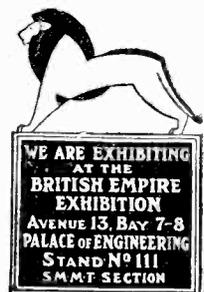

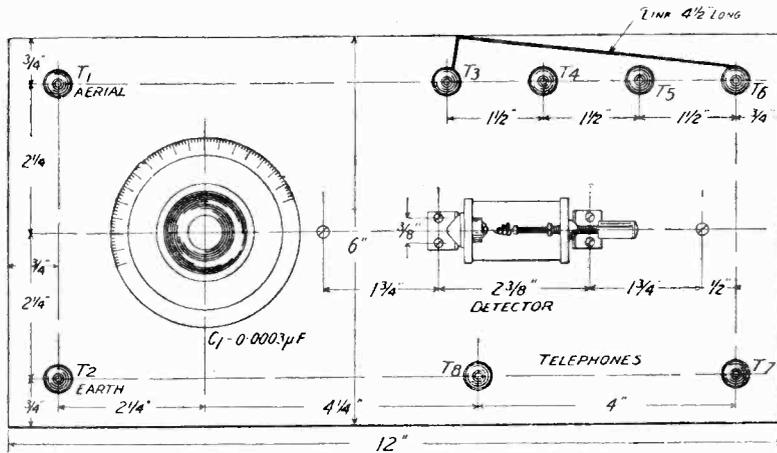


Fig. 3.—The top of the panel, with all dimensions for drilling.

whole of the coil  $L_2$ . D is the crystal detector, and the telephones are joined to  $T_7$  and  $T_8$ . If more than one pair of telephones are used, the receivers may be connected in series by joining one tag of the first pair of telephones to  $T_7$ , the other tag to one of the second pair, and the remaining free tag to  $T_8$ ; to join the 'phones in parallel, one tag of each pair is joined to  $T_7$ , the other of each pair being joined to  $T_8$ .

**As a Separate Tuner.**

The receiver may be used, without alteration, as a selective tuner, for a valve, by joining  $T_6$  and  $T_7$  to the grid and filament respectively of the valve, when the latter is functioning as a high-frequency amplifier. If the valve is acting as a detector, the terminal  $T_6$  of the tuner is joined to one side of the usual grid condenser and leak, the other side of the condenser and leak being connected to the grid of the valve.  $T_7$  is, in this case, connected to the filament positive. The telephones are not joined to  $T_7$  and  $T_8$  when the set is used in this manner, but are normally connected in the anode circuit of the last valve, if more than one valve is used. The crystal detector D in this case is not included in the circuit.

**Components and Cost.**

Very few parts are required for constructing this set, and a list will be found below. The constructor may already possess such component parts as crystal detector, cardboard tube, and so on, and these may be used, and will no doubt be found satisfactory.

**The Tuning Coil.**

The coils are wound upon a cardboard tube 3 in. in diameter, and 6 1/2 in. long. The coil  $L_2$  is wound

first with No. 18 s.w.g. double-cotton-covered wire; 80 turns are put on, and the ends are secured by passing through holes in the

**COMPONENTS.**

COMPONENTS.	£	s.	d.	
Cabinet, 12 in. by 6 in. by 4 in. deep (Wright & Palmer)	..	0	10	0
Panel, 12 in. by 6 in. by 1/4 in. (Paragon Rubber Co.)	..	0	5	0
0.0003 Variable condenser (K. Raymond, New Type)	..	0	5	3
Burndept Crystal Detector	..	0	5	0
8 4 B.A. W.O. Type Terminals	..	0	1	4
Cardboard Tube, 3 in. diameter, 6 1/2 in. long	..	0	0	6
1/2 lb. 18 s.w.g. D.C.C. Wire	..	0	2	0
4 ft. Square Bus-Bar Wire (Sparks Radio Supplies)	..	0	0	4
<b>Total</b>	..	<b>£1</b>	<b>9</b>	<b>5</b>

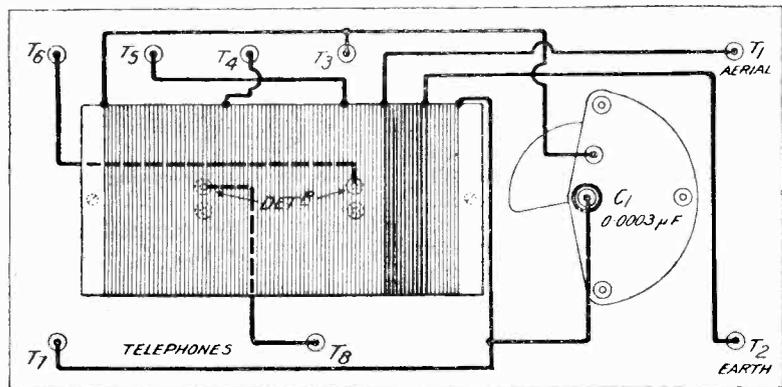


Fig. 4.—The wiring of the set.

cardboard tube. At about ten turns from one end, ten turns are wound on over the first layer, to form the aerial coil. The ends of this coil may be secured by means of string, looped round the wire, passed round the tube, and tied tightly. Tappings to the coil  $L_2$  are made by scraping the insulation off the wire at the point where the tapping is to be taken, and soldering a wire on here. Further particulars as to tappings will be discussed later, when wiring up the set, as it is not necessary to

make the tappings until that stage is reached. The coil is mounted upon the panel by means of two pieces of wood, 2 1/2 in. long, 3/8 in. thick and 3/4 in. high, cut out so that the cardboard tube fits in, the latter being fixed to the wood by small screws.

**The Panel.**

The panel, which is of ebonite, measures 12 in. long by 6 in. wide by 1/4 in. thick, and needs very few holes to be drilled in it, the positions of those necessary being found in Fig. 3. Having located all the holes, make a mark at the centre of the place where a hole is to be made, and make a small indentation with a hammer and a nail. A woodworker's counter-sinking tool may be used, if at hand. The drill point is thus prevented from "wandering," and it is ensured that the hole will be drilled in the correct place.

**Mounting the Parts.**

When all the holes have been drilled, the terminals and clips for the crystal detector should be mounted up, one of the latter being then connected to  $T_6$  and the other to  $T_8$ . These wires must be put on before the coil is mounted, as otherwise the latter would render it impossible to solder the wires to the detector clips.

The coil is then mounted up, so that the end upon which the ten-turn coil is wound is in the middle of the panel, toward the variable

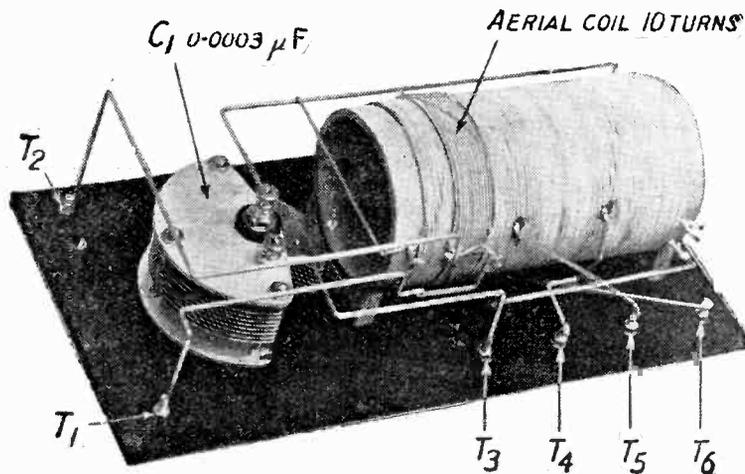


Fig. 5.—A photograph showing how the tappings are made.

condenser, which latter should then be secured in position.

**Wiring.**

Wiring is carried out with square-section "bus-bar" wire, obtainable from Sparks Radio Supplies, and gives a very neat and workmanlike appearance to the set. The ends of the ten-turn coil are connected to aerial and earth respectively, and the end of the larger coil nearest this coil is joined to the moving plates of the condenser and to T<sub>7</sub>. Turn now to the end of the large coil remote from the smaller one, and count 26 turns from this end. Scrape the insulation off here, and join this point to terminal T<sub>4</sub>. Count another 26 turns along, in a direction toward the variable condenser, and, having scraped the wire clear, solder a wire on to this point, carrying the wire on to T<sub>5</sub>. The end of the large coil from which the turns were counted, as above, is now joined to T<sub>3</sub> and to the fixed plates of the variable condenser, thus completing the wiring of the receiver. No difficulty should be experienced in this operation, if the wiring diagram, Fig. 4, is carefully studied, while a glance at the photograph of the back of the panel, Fig. 5, will clear up the whole question.

**Testing the Set.**

When complete, the set may be connected up to an aerial and tested. Connect the aerial to T<sub>1</sub>, earth to T<sub>2</sub>, and telephones to T<sub>7</sub> and T<sub>8</sub>. By means of the link already described connect T<sub>6</sub> to T<sub>3</sub>, and adjust the condenser, with the cat-whisker touching the crystal, until signals from the local station are heard. The crystal may then be adjusted to its most sensitive point, readjusting the condenser C<sub>1</sub> for the loudest signals.

The link between T<sub>6</sub> and T<sub>3</sub> may be taken out, and instead, T<sub>6</sub> may be joined to T<sub>4</sub> or T<sub>5</sub>, whichever gives the best results with least interference. At each alteration the condenser should be readjusted to the best point.

When the set is used as a tuner for a valve, T<sub>6</sub> is connected to the grid (or grid condenser if the valve is working as a detector), and T<sub>7</sub> to the filament. Tuning is carried out on the variable condenser C<sub>1</sub>, which must be adjusted after each

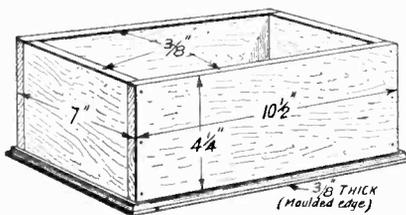


Fig. 6.—The containing box.

alteration of the connection from T<sub>6</sub> to T<sub>3</sub>, T<sub>4</sub> or T<sub>5</sub>.


**Results Obtainable.**

The set will easily cover the band of wavelengths used by the British broadcasting stations, with the coil provided, and good signals should be obtained, on a reasonably efficient aerial up to 15-20 miles from a station. On a 90 ft. aerial some 12 miles from 2LO, very good signals were received, and, owing to sharpness of tuning, the receiver was found to be very selective.

**TEST REPORT**

This receiver is remarkably efficient and has been tried on various sizes of aerials, the tuning remaining substantially constant for all aerials. The efficiency is high and the selectivity is remarkable, the best results being obtained when the crystal detector is connected across the smallest portion of the inductance. For a one control set it should prove ideal for general use, and particularly for those troubled by interference. The set covered the whole broadcast waveband on any aerial.

J. S. T.

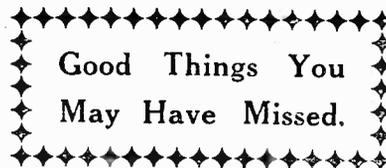

APERUSAL of the recent issues of *Wireless Weekly* will show to those readers of MODERN WIRELESS who do not read the sister journal, that it is possible to miss a number of good things appearing exclusively in *Wireless Weekly*.

There have been, for instance, during the last month a brilliant series of articles by Professor J. H. Morecroft, dealing with the "Wireless Valve and How It Works." Again there has appeared a series of simple back of panel wiring diagrams whereby the veriest amateur may construct his own crystal or valve receiver. This feature is continued week by week.

With so much interest being shown in circuits designed for use without H.T., *Wireless Weekly* again leads the way in that no less than a dozen circuits have been published, including full theoretical and practical details of the new three-electrode valve high-tensionless circuit discovered by Mr. A. D. Cowper, M.Sc.

Some two months ago readers of MODERN WIRELESS were made acquainted with the merits of the Reinartz circuit. In *Wireless Weekly* recently, Mr. John L. Reinartz, the inventor, contributed a most instructive article, describing a new design of All-Wave Tuner, with many novel points.


Aperiodic Aerial Coils is another interesting topic recently dealt with in *Wireless Weekly*, results of actual tests upon given coils being published. The experiments in question have been carried out by Dr. E. H. Chapman, M.A., D.Sc.

The increasing circulation and the demand for back numbers of *Wireless Weekly* (a demand which we can rarely satisfy) is a plain indication of its value. Any reader of MODERN WIRELESS who do not read *Wireless Weekly* should leave an order with his newsagent to supply the paper for a week or two for a trial run. Start on Wednesday next and begin the remarkable new series of articles on high-tensionless circuits.

*Wireless Weekly* was the first periodical to publish high-tensionless circuits and was the first to give a constructional article dealing with a two-valve high-tensionless loud-speaker receiver.

# LISSENIUM

## Lighting the Valve Filament

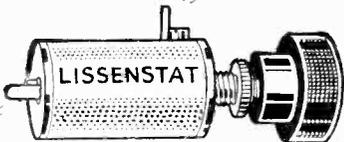

The days are gone when mere lighting of the valve filament was called filament control. The successful tuning of the detector and H.F. valves is a critical thing which largely depends upon the proper regulation of electron emission. Filament temperature

must be exactly right for each station tuned in—especially is this important on long distance work. The introduction of LISSENIUM control has shown what unique filament control can do to improve fine detection of long distance telephony. The difference it makes to tuning is a revelation. There are three types to choose from. Each is suitable for dull emitter and all valves:—

**LISSENIUM** (prov. pat.)—This is the super filament control—brings in stations which have previously eluded every other control of the receiver. **7/6**

**LISSENIUM MINOR** (prov. pat.)—There must be hundreds of thousands of inefficient rheostats in use. The LISSENIUM MINOR has been introduced to provide something of the beautiful LISSENIUM control at a popular price. It is well worth while discarding any existing rheostat and replacing it with this perfect little control. **3/6**


**LISSENIUM UNIVERSAL** (prov. pat.)—Gives full LISSENIUM control, and by means of an ingenious arrangement a minimum resistance can be left in circuit to protect expensive valves, while zero resistance can also be obtained when full battery pressure is required. **10/6**

## Stronger Light—and Fading Signals. The Need for Radio Frequency Amplification.

Have you yet noticed how signals which used to come in strongly are now more difficult to tune in while daylight lasts? No sooner has darkness set in, however, than signals seem to come in strongly again. Summer shows up any weakness in your set if it is without proved radio frequency amplification. Build up wave energy with the aid of LISSENIUM radio frequency amplification. Then see how strongly your signals are received, and with what certainty they come in. There are three well-known types of LISSENIUM radio frequency parts:—When to use the LISSENIUM Selective H.F. Transformer. In some dual and reflex circuits transformer coupling of H.F. valves is essential, and even where it is not indispensable many still like to use transformer coupling. The advantage the LISSENIUM H.F. Transformer has over all others is that it makes a receiver exceedingly sensitive—it is also very stable and as many stages of H.F. as desired can be introduced into a receiver. 150-4,000 metres **19/6**

Blue print with each shows easy connections.
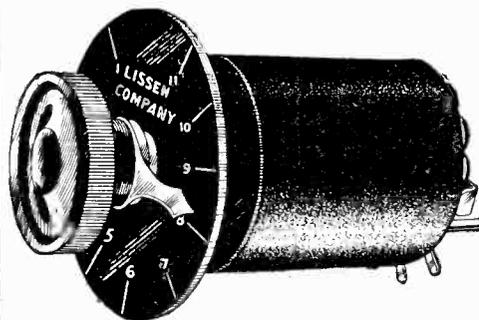
## When to use Lissen Reactance (prov. pat.)



If you desire great purity of reception, a high degree of amplification, and extreme sensitivity, the LISSENIUM REACTANCE should be introduced into the anode circuit of the H.F. valve. Diagram with each shows how. It gives greater amplification than any other H.F. coupling, and it will amplify even the faintest of signals almost as much as a


good audio frequency transformer. Recommended for one or two stages H.F., for which it is easy to control. Beyond two stages some little skill is required. It is widely used, and has done much to popularise radio frequency work. Gives its best results with aerial reaction.

150-10,000 metres **19/6** 150-600 metres **17/6**  
The LISSENIUM REACTANCE AND LISSENIUM H.F. TRANSFORMER have the same outward appearance—latter has four connections instead of two, however.
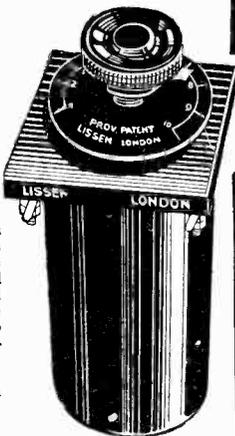
## Successfully Used in the Reception of American Telephony.

No aerial reaction need be used for the LISSENIUM REGENERATIVE REACTANCE (prov. pat.) will take its place. It is non-radiating—replaces plug-in coils—at its lower in cost than a set of coils to cover the same wide range; it is easier to handle, one knob controls tuning and reaction; reception is often possible with both aerial and earth connections dispensed with; cuts out the local station and tunes in the others with full built up strength. Continental stations come in easily. Introduced into the anode circuit it forms an unequalled first stage of radio frequency. Blue print with each shows easy connections—unbroken regeneration possible over the whole range—**£2/12/6**  
150-4,000 metres

Tune always with a vernier—preferably the LISSENIUM Vernier, which is specially designed for fine tuning in H.F. circuits, **12/6**.  
NOTE.—LISSENIUM H.F. Transformer and LISSENIUM REACTANCE are self-tuned and no separate condenser is essential, but the aid of a vernier will oftentimes be an advantage, and the LISSENIUM VERNIER is recommended. All these parts have LISSENIUM ONE HOLE FIXING, OF COURSE. And the radio frequency parts are complete with internally connected switch, so that drilling and soldering are avoided.



## The Loud Speaker's Voice

You have no doubt heard that blurred, woolly reproduction which is more jarring than beautiful. More often than not such reproduction comes from a badly designed transformer. Not all high priced transformers are well designed. If you would have beautiful tone quality, crystal clear music, perfect in every detail of light and shade, song and speech that come through with absolute fidelity of tone, you will fit LISSENIUM Audio Frequency Transformers, at the price you choose. **MAKES A WHISPER LOUD.**—The LISSENIUM T1 has a coil with over 8 ozs. of copper in the coil—the coil will amplify by itself without any iron core at all—for immediately after the detector valve always, throughout when superlative amplification is desired, and especially **30/-** for POWER WORK also.



**AUDIO FREQUENCY IN REFLEX CIRCUITS.**—An all purpose transformer is the LISSENIUM T2, and it has been found an excellent transformer in dual and reflex circuits, where it will yield pure and powerful amplification. May be used for all stages, and recommended to follow the LISSENIUM T1 where multiple stages of audio frequency are used. **25/-**

**SKILFULLY BALANCED DESIGN.**—Many expensive transformers are not so good as the LISSENIUM T3—it is one of the best light transformers made. **16/6**

## Cutting Out Station after Station



Start with any station you please, and you can go right round them all if you use the LISSENCEPTOR and a separate tuning condenser. In turn you can cut out any of the stations you do not want—Morse interference also. Users on the coast say they can now enjoy broadcasting in a way impossible before. Some type of Morse interference calls for somewhat more skill, but 95 per cent. of Morse is cut out easily. Even the more difficult Morse, however, can be sufficiently subdued so that it ceases to be troublesome.

**LISSENCEPTOR Mark 1 type**, for broadcasting .. **7/6**  
**LISSENCEPTOR Mark 1 type**, for 600 metres .. **7/6**

**LISSENCEPTOR Mark 2 type** for broadcasting and 600 metres combined (with switch for more selective tuning) .. **15/6**

THE LISSENCEPTOR ACTS AS A SENTINEL BESIDE YOUR RECEIVER.

## Switching that is Helpful to Regeneration

When working on the lower wavelengths perhaps the set will just oscillate with the condenser in parallel. If the LISSENIUM Series Parallel switch were fitted you could immediately try the effect of putting the condenser in series, and so seeing whether the increased regeneration obtained would more than compensate for the slight damping of signals consequent upon the changing over of the condenser. The LISSENIUM Series-Parallel switch is easy to fit—takes up little room—**3/9**  
LISSENIUM ONE HOLE FIXING, OF COURSE.



## Make Your Batteries Last Longer

In the case of dull emitters, the current taken per valve is small, but there is a drain on the batteries all the same. If the dry cells used are given the opportunity to recuperate the voltage which has dropped when the cells are in use will rise again. Two cells, for instance, which are worked alternately throughout will last a great deal longer than twice as long as one cell which is worked continuously. Apart from the economy of introducing a switch to change over to alternate batteries, the voltage will be steadier and the efficiency of the set improved. The best switch to use is the LISSENIUM two-way switch—easy to fit—hardly any room is taken up—**2/9**  
LISSENIUM ONE HOLE FIXING, OF COURSE.



## What would Happen to the Negative Charge?

If you had an unreliable grid leak in your receiver, the negative charge left on the grid of the valve by each radio frequency oscillation of a radio wave would leak away too quickly, with the result that it would be impossible to regulate the charge that should accumulate on the grid. When the LISSENIUM Variable Grid Leak (prov. pat.) is used it is possible to select the exact value of leak resistance, and to obtain correct grid potential under all conditions of valve and circuit. An interesting alternative use is across the secondary of a transformer or across the loud speaker itself, when it will suppress any tendency for the high notes of the musical scale to be amplified disproportionately to the lower notes.



**LISSENIUM Variable Grid Leak** has positive stops both ways—continuously variable to 6 megohms—LISSENIUM ONE HOLE FIXING, OF COURSE **2/6**

**LISSENIUM Variable Anode Resistance**, 20,000 to 250,000 ohms continuously variable, same outward appearance as the LISSENIUM Variable Grid Leak **2/6**

**WHY USE MIXED PARTS?**—You can be sure that your receiver built with all LISSENIUM Parts will give results which would never be possible with a receiver built with mixed parts.

# LISSENIUM LIMITED

20-24, WOODGER Rd., GOLDHAWK Rd., SHEPHERD'S BUSH, LONDON, W.12.

Telephones—Hammersmith 3380, 3381, 3382, and 1072.  
Telegrams (Inland) "Lissenium, Shepherds, London."  
(Foreign) "Lissenium, London."

BUILD—WITH LISSENIUM MASTER PARTS.



# Released!

*the biggest thing  
of the year.*

THE Genie of the Arabian Nights made a considerable stir on emerging from his brass bottle;—he was a big thing in his way.

The release of the new GENERAL RADIOPHONES is another event destined to create great interest, because—GENERAL RADIOPHONES are different. Their ready response to signal intensity of .0000000011 of an ampere is an achievement which places them far above all competitors for efficiency.

A new method of matching the earpieces by means of specially invented visual gauges, and the incorporation of a carefully designed sound box, ensures singular clarity and natural reproduction.

GENERAL RADIOPHONES are unrivalled for strength and finish, and they weigh only 7 ozs.

Ask your dealer for a demonstration.

*If you have any difficulty in obtaining GENERAL RADIOPHONES send direct to us. Please give name and address of your wireless dealer.*

*Our Technical Service Dept. answers queries free of charge. Address letters to Dept. M.*

**20/-**  
per pair.

**Every pair carries a full guarantee.**

**GENERAL RADIOPHONES**



FAMOUS FOR EFFICIENCY

**GENERAL RADIO COMPANY LIMITED,  
Radio House, 235, Regent St., London, W.1.**

Telephone:  
Mayfair 7152.

Telegrams:  
"Algenrad, London."





To the Editor of MODERN WIRELESS.

SIR,—Having read in your columns various articles on crystals, home made and otherwise, I would like to draw your attention to the specimens enclosed, together with a brief description of how they came into my possession.

A few friends and myself are in the habit of taking small portable crystal sets with us on cycles for experiments of varying distances from the near stations.

On Saturday, December 8, we were at a place near Chesterfield (Derbyshire).

We, as usual, rigged up our aerial (using Electron wire, page 369 MODERN WIRELESS, No. 5, Vol. II.) earth and set, then imagine my discomfiture to find the tube in which I carry my crystal was in none of my pockets.

At this, of course, all thoughts of reception had to be put aside. So feeling rather disconsolate I set off to inspect a nearby quarry, and it was in this quarry that the enclosed specimens attracted my eye; it was lying about in tons.

Curiosity prompted me, and I clipped a piece off and carried it to my set, not without some misgivings as to the stability of my reason. Needless to say, after a few fine adjustments I was able to receive Sheffield relay quite well.

My friends and I were quite jubilant and we left that spot with a goodly collection of these crystals to be had merely by bending one's back.

Of course I am not thinking I have made a great discovery, but one wonders at the price of a good specimen of treated crystal in comparison.

Wishing MODERN WIRELESS every success, I remain, sir,

Yours truly,  
T. PAYNE.

Editor's Note.—The crystals submitted by our correspondent worked quite well in comparison with the commercial types.

To the Editor of MODERN WIRELESS.

SIR,—I wanted to make a receiving set for my parents who live at Maidstone. As they are both getting on for 80 years old I wanted something as simple as possible and yet which would give fairly loud reception as they are both rather deaf. I therefore, made up the "Old Folks" set from the October, 1923, MODERN WIRELESS, and I am pleased to say that it is a great success. They heard the Bishop of London on Easter Sunday and the King at Wembley very clearly, and they are enjoying the programme every evening. I used 3 Ediswan A.R.D.E. valves and 2 R.I. transformers.—Yours truly,

A. T. GRANT.

To the Editor of MODERN WIRELESS.

SIR,—I have wired up the Reinartz circuit with your improvements according to your very lucid directions in the March MODERN WIRELESS and I am taking the liberty of writing to you. I have used loose parts on a walnut board with English apparatus, e.g., R. I. Ltd. transformers and 3-valve panels fitted with Burndept coil-holders and rheostats and M.O. "R" valves.

It all works splendidly and the surprising thing is that I get well such distant stations as Minneapolis, Chicago and Davenport, about 900 to 1,000 miles distant with L.F. amplifiers. The building up of the reaction is very satisfying.

My aerial is 50 feet high, T type from exact centre, and I use Brown's low-resistance telephones with a Burndept tel. transformer in a box.

I have used No. 21 wire B. and S. This is nearly the equivalent of No. 22 S.W.G. In Canada we use the American wire standards. Almost everyone in Canada uses American wireless apparatus, or if made in Canada, instruments of American type.—Yours faithfully,

F. A. MAGEE.

Sparks Street,  
Ottawa, Canada.

To the Editor of MODERN WIRELESS.

SIR,—As regards your latest 3-valve dual, I have converted your ST. 100 Star to that circuit, and find it very good for long distance stations. On Saturday the 12th, after listening on your one-valve reflex, by Kendall B.Sc., to the S.O.S. calls going on, etc.; at about 3 a.m. I turned on the three-valve dual, and tuned in W.G.Y. which was quite strong and clear, and very steady.

The orchestra was playing the Savoy type of music. At about 3.15 I left it at that, and went to bed. The next night, Sunday 13th, at about 12.25, I tuned in the Spanish Station, Radio Elevar, Madrid, and heard that station quite London crystal strength, with practically no fading.

The orchestra was composed of mandolines, etc. G.B.L. had a lot to say, and practically drowned it out, so went to bed again.


The three-valve dual is much too powerful to use here (Earl's Court), even on loud speaker, and I find it is not very pure for the local station. Admittedly my second transformer is not a first-class make, but it worked your All-Concert type satisfactorily. Your ST. 100 was very pure, but not selective. The first night I used it I got Aberdeen on L.S. I must add, that my aerial has walls on three sides of it, as I am in a lower maisonette, and also there are tall houses fifty yards off on the fourth side, so it is not quite ideal! I think MODERN WIRELESS the finest radio magazine, as all your circuits are laid out so clearly. The only fault I find is, that as soon as we get settled down to our circuit, out comes another, and we must try it!

I remain,

Yours truly,

V. KEBBELL.

Earl's Court, W.

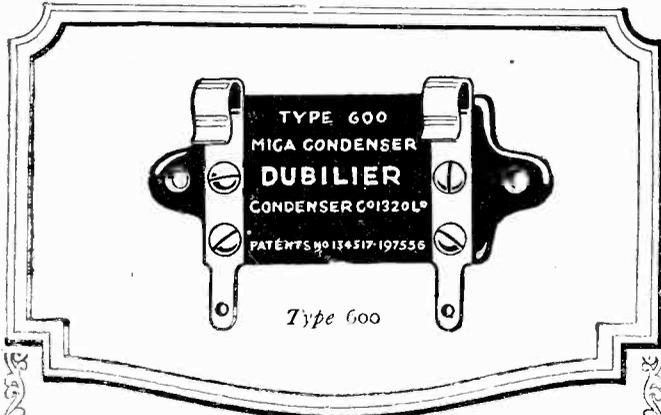

**Confidence.**

When you buy a fixed condenser of any unknown make for your set, you buy on trust.

You hope that it really will be of the capacity stated; you hope that it will remain constant and not produce mysterious faults by leaking or altering its capacity.


Not having an electrical laboratory at your disposal, you cannot prove the matter either way. So you hope for the best.

How much wiser to buy a condenser in which you can have confidence.

There may be an extra outlay of a few pence, but the soundest possible insurance against condenser faults in your receiver is to

*Specify Dubilier.*

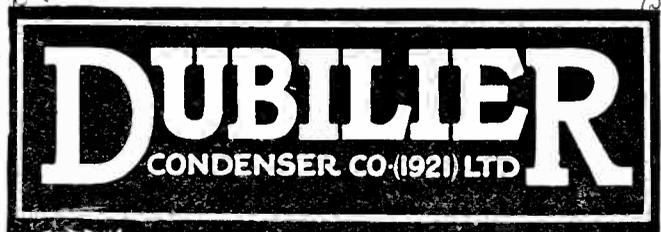*Advt. of the Dubilier Condenser Co. (1921), Ltd., Ducon Works, Goldhawk Road, London, W.12*




E.P.S.59.

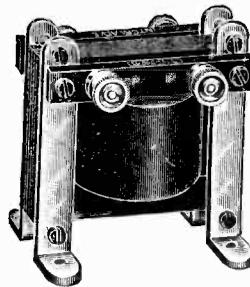**The inimitable "L.F." — Woodhall Number One.**


You cannot get a better Transformer at any price. You cannot obtain "S.T.100" results with an inferior transformer.

The formula used in this famous transformer is a unique one: it combines the best enamelled wire with simultaneous turns of fine silk, giving a spacing to turns and a cushioning effect that eliminate "parasitic noise," and yield pure, full-toned amplification, equally mellow on the top notes of a soprano vocalist, the bass notes of the bassoon, and the octaves between. Behind all formulae and purely mechanical detail, however, is the "human element"—experience, skill, and thoroughness—that individualises Woodhall-Wireless Components and makes them **inimitable.** PRICE **23/6**



**The WOODHALL Variable Condenser**

Type 3 — Light-weight — Metal Ends.

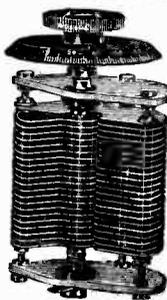

A lighter-weight condenser of similar construction to type 1—with ALUMINIUM END-PLATES and BEST EBONITE BUSHES. The vanes are 24-gauge aluminium and the spacers are 3/32nd in.

Accurate bearings giving smooth movement and adjustable tension. The adjustment of vanes is a point to which very careful attention is paid. Terminals are provided—no soldering required. Mounted on panel by drilling one hole only.

.001	...	...	8/-	.0002	...	...	5/-
.0015	...	...	6/-	.0001	...	...	4/9
.0003	...	...	5/6	.00005	...	...	4/6

Above prices include Knob and Anticapacity Dial.

**The WOODHALL Special Resistances for S.T.100 and other Reflex Circuits**




Constructed by a new method, sealed against the effect of damp or heat, and guaranteed exact and constant. Mounted on best ebonite base with terminals. Standard resistance 100,000 ohms or can be supplied in any value from 20,000 ohms to 5 megohms

**2/9**

**The WOODHALL Panel-Mounting Coil Plug**

For addition of loading coil to existing sets, or for many other purposes. Attached through panel from back, giving neat surface appearance; supplied with drilling template

**1/6**

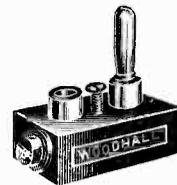

See the name WOODHALL on Variable Condensers, Fixed Condensers, Rheostats, etc., etc. and be sure of the best.

**WOODHALL**

**Guaranteed Components**

Ask your Wireless Dealer for them. In case of difficulty send P.O. direct, giving name of your Dealer. We pay postage. Dealers should specify "Woodhall-Wireless" in ordering from their usual Factors or Wholesalers.

**The Woodhall-Wireless Mfg. Co.**  
55, Cardington Street, Euston, N.W.1  
Telephone: Museum 8566. Wholesale on 7.



From a popular viewpoint, probably the best-known of Wagner's operas is Tannhauser, while his most stupendous work is Der Ring—really consisting of four operas to be performed on successive nights. All these and many others, including Lohengrin and Der Meistersinger, are invariably broadcast during the Covent Garden Season.

Master Musician No. 2.

Richard Wagner

NO one reading the story of Wagner can fail to be impressed with the tremendous difficulties the great composer had to overcome, not only in his early years—when often he was almost reduced to starvation—but right up to his death in 1883.

Wagner was a reformer, and for many years he ploughed a lonely furrow. In his hands the Opera was changed from a disjointed affair of separate airs, duets and finales and developed into a magnificent dramatic spectacle, co-ordinated by one master mind.

Such innovations naturally created intense controversies in musical circles, and although the great composer reached the allotted span of three score years and ten he did not live to see a single one of his operas attain any real degree of international fame.

The Loud Speaker reception of Wagner's operas brings forth this peculiar point: since augmented orchestras are

required to obtain such majestic effects, there is a danger of the Loud Speaker being over-loaded and the music being confused.

The user of the **Brown**, however, is safe from this defect because its cone-shaped aluminium diaphragm is anchored to a tuned reed and therefore attracted in one central position only.

The largest users of **Brown** Loud Speakers are staunch opera-lovers, obviously they choose the **Brown** because its unique construction permits it to give a more truthful rendering.

S. G. BROWN, LTD.  
Victoria Road,  
N. Acton, W.3.

Retail:  
19, Mortimer St., W.1.  
15, Moorfields, Liver-  
pool.



PRICES:

Type H.1, 21 in. high:	
120 ohms ..	£5 5 0
2,000 ohms ..	£5 8 0
4,000 ohms ..	£5 10 0
Type H.2, 12 in. high:	
120 ohms ..	£2 5 0
2,000 ohms ..	£2 8 0
4,000 ohms ..	£2 10 0

**Brown**

Loud  
Speakers

G.A. 866.



The easiest way  
to build a good Set.

THERE are still plenty of Wireless enthusiasts who have still to build their first Valve Set. If they are afraid that they lack skill, here is a new method which will certainly smooth out difficulties.

Radio Press have inaugurated a simplified Envelope System. Each Envelope deals with one Receiving Set in the fullest possible manner. The instrument is shown in large illustrations taken from various angles, and lower views of the panel are also included.

The instructions for making are lucid and comprehensive and cover every possible detail. They are written by an expert in such a way that even a man who has never built up a Set before can go ahead with every feeling of confidence. Enclosed in the Envelope is a full-sized blue print of the rear of the panel to show the actual wiring diagram.

This Envelope scheme—which is an entirely new departure—is proving to be a method whereby anyone can build up a first-class Receiver, professionally designed, at a most moderate cost.

Select the Set you propose building and order your Envelope from your Book-seller to-day.

The Series:

- No. 1. How to build up the S.T. 100 ... 1/6
- No. 2. How to build a "Family" Four-Valve Receiver ... 2/6
- No. 3. How to build the "Simplicity" Three-Valve Receiver 2/6 Ready Shortly
- No. 4. How to build the "All Concert De Luxe" Receiver 2/6 Ready Shortly

**Radio Press's**  
simplified  
**Envelope System**

G.A. 866.

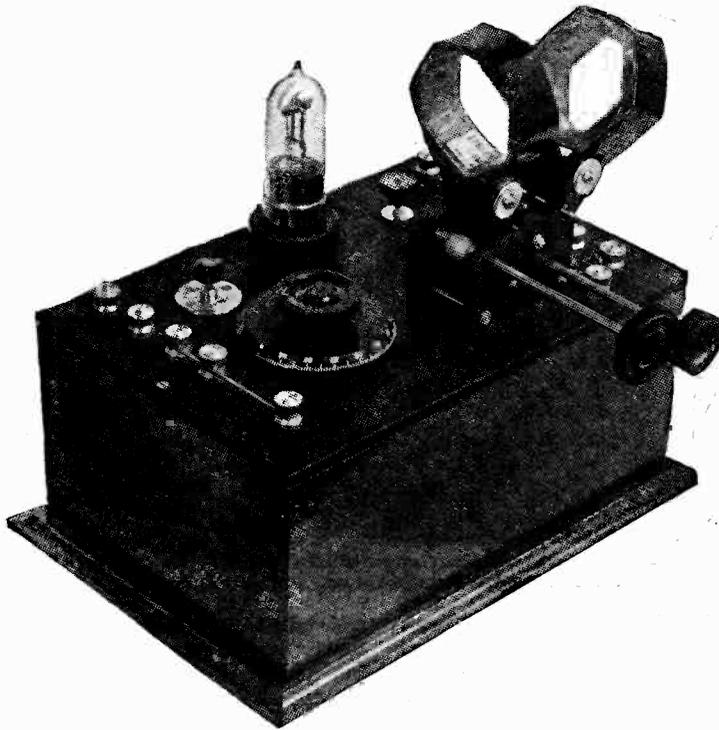


Fig. 1.—The appearance of the finished set.

# An Efficient Single-Valve Receiver

By

HERBERT K. SIMPSON

VALVE sets of many types are continually making their appearance in the technical journals, but the modest single-valve set, in which the valve acts as a rectifier, receives very little attention. This is hardly as it should be, considering the good results which are obtainable from such a set with a minimum of trouble and experience.

The set seen in Fig. 1 is of the single-valve type, reaction being provided on to the aerial coil by means of the two-coil holder, on the left of which is seen the aerial tuning condenser. The valve-holder is seen at the back of the set, with the variable grid leak on the left and the filament control on the right. The terminals on the left-hand side of the set are those in the aerial circuit, by means of which we may use the three chief forms of tuning—namely, constant aerial tuning, series tuning, or parallel tuning. On the right are six terminals. Reading from the top, these are high-tension positive and negative, low-tension positive and negative, and telephones. Two terminals are provided close to the reaction coil socket of the two-coil holder (the right-hand socket), by means of which the reaction coil may be reversed. The two-coil holder used is of a good type, as shown in the illustrations, and can be obtained with a special device, incorporated on one of

the sockets, for reversing the connections to that socket. If this type of coil-holder is used, the necessity for the reaction terminals on the panel will be obviated, the leads going direct to the coil-holder. If in doubt, construct the set exactly as shown.

### Circuit Diagram

A diagram of the circuit arrangement is given in Fig. 3, and from this the various aerial circuit connections may be followed. Constant aerial tuning may be applied by joining the aerial lead to terminal T<sub>1</sub>, leaving T<sub>2</sub> free, and joining T<sub>3</sub>, T<sub>4</sub> and T<sub>5</sub> together. The earth

is connected to T<sub>5</sub> in all cases. If it is not desired to use constant aerial tuning, but to have the aerial tuning condenser in parallel with the aerial tuning coil, the aerial lead is joined to T<sub>2</sub>, leaving T<sub>1</sub> free, and T<sub>3</sub>, T<sub>4</sub> and T<sub>5</sub> are connected together and to earth. Tuning is carried out on the variable condenser C<sub>1</sub>, the coil L<sub>2</sub> being coupled to L<sub>1</sub> to obtain reaction.

### Series Tuning

The aerial tuning condenser may be used in series with the coil by joining the aerial lead to T<sub>1</sub>, earth to T<sub>5</sub>, leaving T<sub>2</sub> free, and connecting T<sub>3</sub> to T<sub>5</sub> with a piece of wire.

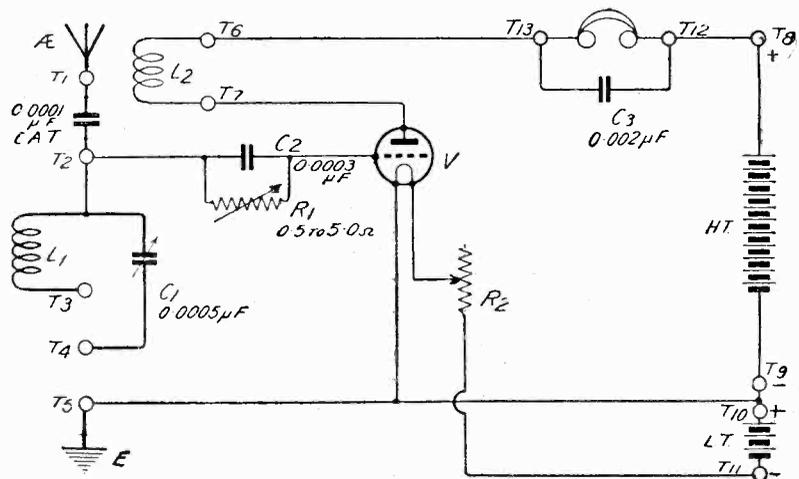


Fig. 3.—The circuit arrangement of the receiver.

Although there is a considerable interest in two, three and multi-valve sets, the single-valve receiver still appeals to a very wide circle. This article gives full constructional details for a thoroughly efficient set.

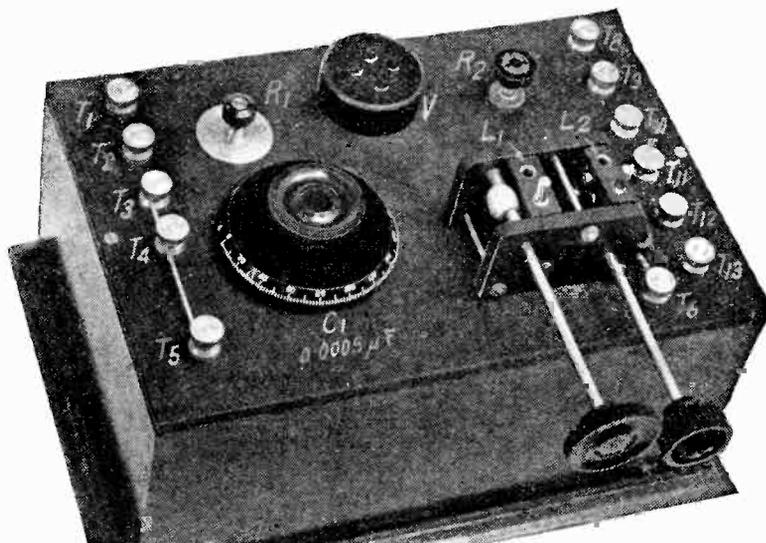


Fig. 2.—A close up view of the top of the panel. Note the vernier adjustment on the coil holder.

**Components and Cost**

The parts required for this set are listed below, and will be found simple and inexpensive. If the constructor has any parts already in his possession, such as a variable condenser, valve-holder, and so on, he may use his own components, but at the same time he is advised to adhere as closely as possible to the specification, as good parts are necessary to ensure efficient working of the receiver.

the socket; but when using Ediswan valves care must be taken that proper contact is made, as the pins on this type of valve are shortened for the sake of protecting the filament.

Dubilier fixed condensers have been used in this set, and a Raymond new type variable condenser. Wiring is carried out with square bus-bar wire, obtained from Messrs. Sparks Radio Supplies.

wise too large a hole may inadvertently be drilled. Make a small indentation with a hammer and a nail at the point where the hole is to be, taking care not to hit too hard, or the panel may be cracked. This prevents the point of the drill from "wandering" when drilling is commenced. A 3/8-in. hole is drilled in the panel, in a position in between the two sockets of the coil-holder, in order to allow the leads to the aerial coil to pass through the panel.

**COMPONENTS.**

	£	s.	d.
Cabinet (Wright & Palmer), 10 1/2 in. by 7 in. by 4 1/4 in. deep ..	9	3	
Panel, 10 1/2 in. by 7 in. by 1/4 in. (Paragon Rubber Co.) ..	5	0	
0.0005 Variable Condenser (K. Raymond; new type) ..	5	11	
Two-Coil Holder (without reaction reversing switch) (Goswell Eng. Co., Ltd.) ..	9	0	
Valve-Holder (H.T.C. Electrical Co., Ltd.) Type A ..	1	9	
Grid Leak (0.5 to 5 megohm) (Watmel) ..	2	6	
Lissenstat Minor Filament Resistance ..	3	6	
13 4 B.A. W.O. type Terminals (K. Raymond) ..	2	2	
Fixed Condensers (Dubilier)—			
One 0.0001 ..	2	6	
One 0.0003 ..	2	6	
One 0.002 ..	3	0	
6 (2 ft.) Lengths Square-section Wire (Sparks Radio Supplies) ..	1	0	
Screws, Rubber Leads, etc. ..			6
<b>Total ..</b>	<b>£2</b>	<b>8</b>	<b>7</b>

**Mounting the Components**

When all holes are drilled, the various parts may be mounted up, commencing with the terminals, valve-holder, and such small parts, leaving the variable condenser and coil-holder until last. In this way the panel does not become so awkward to handle at first. The fixed condensers are held in position on the panel by the wiring, there being no need for securing bolts.

**Wiring**

Wiring is carried out with square-section bus-bar wire, and should present no difficulty to the careful worker. It is advisable to tin all the points to which a wire has to be soldered, for example, terminal shanks, condenser lugs, and so on, before wiring up is actually commenced. A wire is then bent to the exact shape to fit between two, or three, points, as the case may be, and carefully soldered to each point in turn. Rubber-covered flexible leads join the ends of the aerial coil to terminal T3 and the fixed plates of the variable condenser respectively. Flexible leads also join the reaction coil socket to the two terminals on the


**Notes on Components**

The two-coil holder is of a very neat design, incorporating fine adjustment of the coupling between the coils, by means of a cam operated by the usual knob; it is made by the Goswell Eng. Co., Ltd.

The valve-holder, made by the H.T.C. Electrical Co., is made with no metal parts visible, thus rendering it almost impossible to short the filament legs of the valve across high tension when inserting the valve. There is the added advantage of extremely low capacity in

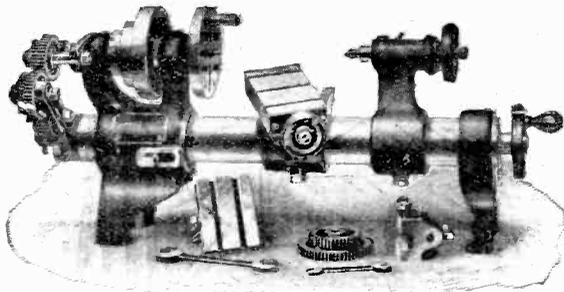**The Panel**

The Panel, which is of ebonite, measures 10 1/2-in. by 7 in., and may be either 3/8-in. or 1/4-in. thick. The ebonite used was obtained from the Paragon Rubber Company, and is of very good quality, there being no need for "matting" (i.e. rubbing with emery paper). A drilling diagram is seen in Fig. 4, with the dimensions necessary for locating the holes. Have all the components to hand before drilling, and ensure that the size of hole is correct before drilling same, other-



The DRUMMOND 4-in. Multi-purpose Lathe.

## Make it yourself!

—half the fun in Wireless is gone if you buy everything complete

Winding coil's, turning up formers, plugs, knobs—a hundred and one jobs, drilling, slotting, boring, screw-cutting—all may be done well and cheaply on the Drummmond. A contact stud—or a bush for your car—make it yourself, and pay for the lathe with the money you save.

**DRUMMOND Bros. Ltd.,** REID HILL, GUILDFORD.

—Post this Coupon—


Please send me, post free, lists of your small lathes, with details of deferred payment system.

Name .....  
 Address .....  
 (Send in unsealed envelope for 1/3.)

The success with which a Valve Receiver will reproduce
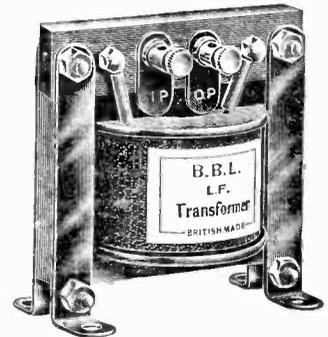
### SPEECH & MUSIC without distortion

depends upon the effectiveness of the L.F. Transformer included in the circuit.



## The "B.B.L."

### Low Frequency TRANSFORMER

An excellent type of light transformer giving maximum amplification in all stages of Audio Frequency. The laminations are built up of Swedish soft iron (stalloy), the receiving bolts being kept clear and so conforming to the best present-day practice. Tested 500 volts between windings. Ratio 4 to 1. No. 17185. Price 13/6.

TRADE ONLY SUPPLIED. KINDLY ORDER FROM YOUR WIRELESS DEALER.

# Brown Brothers Limited

(With which is amalgamated THOMSON & BROWN BROTHERS LIMITED.)

Wholesale only.

HEAD OFFICES AND WAREHOUSES:

GREAT EASTERN STREET, LONDON, E.C.2. 118, GEORGE STREET, EDINBURGH, and branches.

## POINTS of SUPREMACY


Exactly how vital the bearing of correct valve design upon perfect reception the MYERS demonstrates to a remarkable degree.

Valve efficiency is, primarily, the result of a large internal capacity due to bunched leads. This capacity produces valve distortion.

But in the MYERS valve the grid and anode leads are brought out at opposite ends. Thus the electrodes of the MYERS are free at this sterile capacity and perform perfectly.

The deficiency of any valve as an amplifier may be directed to an imperfect vacuum. The presence of gas inside the valve functions as an impermeable wall from which electrons rebound back to the filament.

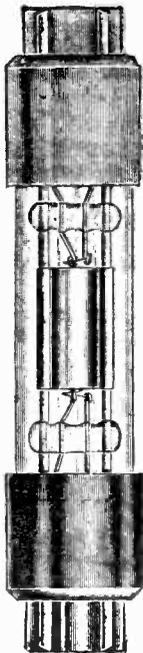The maximum amplification (10) given by the MYERS is the product of a perfectly vacuumed valve. It is pumped free of all gas. The entire electron stream—essential for good amplification—therefore reaches the anode.



Exact Size.

# Myers Valves

### PRACTICALLY UNBREAKABLE

In addition to its other remarkable features the MYERS is ruggedly constructed. It may be roughly handled—even dropped upon a cement floor; but no alarm need be felt for the safety of the glass or filament.

Candidly, there is every reason why you should decide to use MYERS from to-day; and, moreover, to insist upon MYERS at your dealer's. If he cannot supply, send to the nearest selling agent or direct to the Sole Distributors and be supplied post free.

## Cunningham & Morrison

49, Warwick Road, Earl's Court,  
 LONDON : : : : S.W.5

### MADE IN TWO TYPES:

- UNIVERSAL  
4 volts '6 amps 12/6
- DRY BATTERY  
2½ volts '25 amps 21/-
- PLATE VOLTAGE  
2 volts—300 volts

Remember that mounting clips are supplied free. Drilling template with each valve.

### AGENTS:

- LONDON.—The Dull Emitter Valve Co., 83, Pelham Street, South Kensington, S.W.7. Phone: Kensington 3337.
- MANCHESTER.—R. Davies & Sons, Victoria Bolt and Nut Works, Bilberry Street, Manchester.
- NEWCASTLE.—Gordon Bailey & Co., Conset Chambers, Pilgrim Street, Newcastle.
- LIVERPOOL.—Apex Electrical Supply Co., 59, Oldhall Street, Liverpool.
- GLASGOW.—Milligan's Wireless Co., 23-25, Renfrew Street, Glasgow.
- YORKSHIRE.—H. Wadsworth Sellers, Standard Buildings, Leeds.
- SOUTHERN COUNTIES.—D. E. D. A., 4, Tennis Road, Hove.

# Clarke's "ATLAS" SPECIALITIES



**Dealer :** " Oh, yes ; besides CLARKE'S "ATLAS " PATENT PLUG-IN COILS, we stock all other "ATLAS " SPECIALITIES, such as, for instance, the "ATLAS " VARIOMETER, which comprises an ebonite ball-type rotor, swivelling inside an ebonite tube stator. This Variometer, which is of the one-hole fixing type, covers all the British Broadcasting, and is an extremely efficient apparatus.

Further, the "ATLAS " FIXED CONDENSER possesses special features, one of which is that the casings and inserts are made of Bakelite—well known as one of the finest of Insulating Materials, and the copper-foils and sheets of mica forming the dielectric are held under pressure. The value, therefore, of the Condenser is kept constant all the time.

Again, CLARKE'S "ATLAS " VARIABLE CONDENSERS are built not simply for sale but for use in the positions for which the Condensers, of their respective capacities, are destined. They are supplied with full-round or semi ebonite end plaques, the fixed and moving Aluminium Vanes being correctly spaced and beautifully balanced."

**Customer :** " And do Clarke's make Coil Stands, Rheostats, etc. ? "

**Dealer :** " Yes ; their latest type of "ATLAS " 2-WAY AND 3-WAY HORIZONTAL AND VERTICAL COIL STANDS is second to none. They are fitted with plugs and sockets set at standard centres, and the Stands are provided with a neat Tension Adjustment, all fittings being nickel-plated.

Respecting Rheostats, CLARKE'S "ATLAS " 'VELVET TOUCH ' RHEOSTAT is the acme of perfection, and, as its name implies, the action of the contact arm passing over the coils of the resistance spring produces just that 'Velvet Touch ' which, in the cheaper types of Rheostat, is so conspicuous by its absence.

The large ohmic value of this 'Velvet Touch ' Rheostat—viz., 6 ohms—makes it impossible for the full voltage to be put on to the Filaments straight away ; consequently the life of your Valves is increased."

See our Exhibits in the Palace of Engineering,  
British Empire Exhibition, Wembley.

For the American Concerts, try a Set (4) of  
Clarke's "ATLAS " Short-Wave Coils.

Sole Manufacturers :

**H. CLARKE & CO. (MANCHESTER), LTD.,**

RADIO ENGINEERS,

**"ATLAS" WORKS,  
OLD TRAFFORD,  
MANCHESTER.**

'Phones :  
683 & 793 Trafford Park.

'Grams :  
"Pirtoid" Manchester.

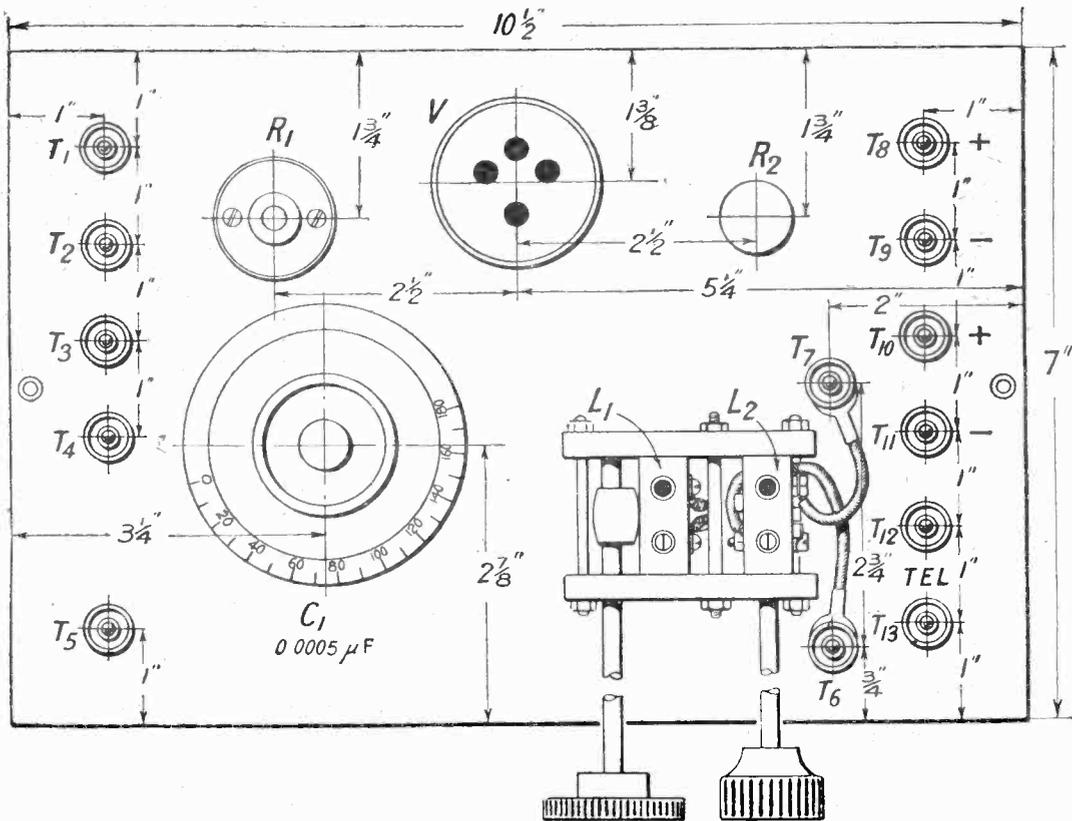


Fig. 4.—A scale drawing of the top of the panel, showing the layout of the parts, and all necessary dimensions for drilling the holes.

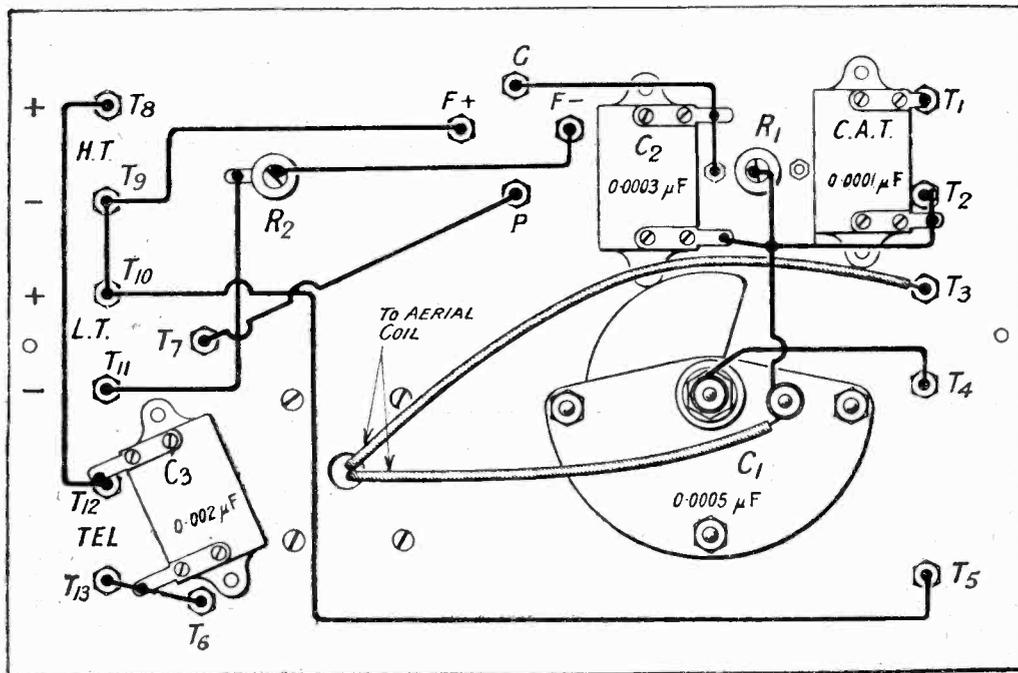


Fig. 5.—The back-of-panel wiring diagram of the receiver. Flexible leads go from T<sub>3</sub> and C<sub>1</sub> to the aerial tuning-coil.

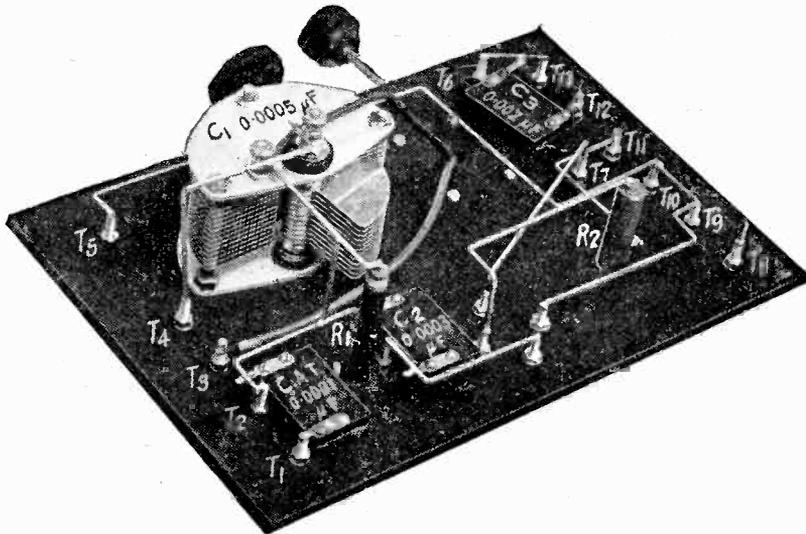


Fig. 6.—A photograph of the back of the panel.

panel. If the special type of coil-holder which incorporates the reversing device, previously referred to, is used these terminals may be dispensed with, and the flexible leads from the coil-socket will then be taken respectively to  $T_{13}$  and the anode of the valve. A wiring diagram is given in Fig. 5, and a photograph of the back of the panel is seen in Fig. 6.

**Coils and Valves**

When using constant aerial tuning a No. 50 coil should be used in the aerial socket, when the wave length of the broadcasting station listened to is below 420 metres, above which a 75 coil may be used. When using parallel tuning a 35 or 50 coil may be required in the aerial socket, according to the size of the aerial, while, when series tuning is employed, a number 75 coil will be necessary. The reaction coil may be a 50 or a 75. Any good make of valve may be used, and no alteration to the set will be necessary if a dull emitter valve is used, as the Lissenstat Minor filament control is equally suitable for either type of valve.

**Testing the Set**

The constructor should now commence testing by using the constant aerial tuning system, in which case the aerial lead is joined to terminal  $T_1$ ,  $T_2$  is left free,  $T_3$ ,  $T_4$ , and  $T_5$  are connected together by a piece of wire, and the earth is joined to  $T_5$ . The batteries are connected to the terminals on the right hand side of the set, indicated in Fig. 4, and the telephones are joined to the bottom two terminals in this row.

Having inserted the valve and coils as mentioned above, turn on

the filament supply by rotating the knob of the filament resistance in a clockwise direction until the filament of the valve is sufficiently bright. Keeping the reaction coil well away from the aerial coil, tune on the variable condenser  $C_1$ , when the local station should be heard at once. Bring the reaction coil up closer to the aerial coil, retuning on the condenser, and note whether the signal strength increases. If this does not happen, the leads from the reaction coil to the two terminals  $T_6$  and  $T_7$  should be reversed. Bringing the coils closer together and retuning on the condenser will now result in an increase of signal strength, up to a point, at which the set will commence to oscillate, and distortion of the speech will take place. Care must be taken not to couple the two coils up sufficiently closely to cause the set to oscillate, as when this takes place, interference will be caused to nearby listeners, thereby upsetting their reception.

The Blue Print of the wiring is No. 46.

**TEST REPORT.**

**The One-Valve Set.**

**T**HIS set was tested on a 75 ft. single wire aerial about 15 ft. high, and also on a 5 ft. indoor aerial.

At 10 miles from 2LO signals came in on a loud-speaker sufficiently clearly for the News Bulletin, etc., to be plainly heard at any part of the room. Constant aerial tuning was used and a No. 50 Lissen coil was in the aerial circuit, while a No. 75 coil was used as reaction. The London station came in on 56 degrees of the condenser.

The 5 ft. aerial was next tried and London came in plainly on the phones, using a 50 coil in the aerial, a 75 in the reaction and using constant aerial tuning. Owing to the very small size of this aerial more condenser was required, and 2LO came in at 74 degrees.

The earth connection was now taken off the earth terminal and the lead was connected to the aerial terminal, no aerial being attached to it. The earth terminal was left free. 2LO came in just as well, if not rather better, on the phones at 65 degrees on the condenser.

Birmingham was next tried for and was received on the 75 ft. aerial with a No. 50 coil in the aerial circuit and a No. 75 as reaction.

The wavelength range on the 75 ft. aerial, using a No. 50 in the aerial circuit and a No. 75 as reaction and using constant aerial tuning, was 250 to 530 metres.

Brussels came in very clearly using the above coils on the 75 ft. aerial using C.A.T. The adjustment of the variable condenser was 12 degrees and the wavelength appeared to be about 265 metres.

For wavelengths over 430 metres, a No. 75 coil in the aerial circuit is recommended, the same size coil for reaction being used. J. S.-T.

**Radio Press Information Department**

Owing to the tremendous increase in the number of queries, and the policy of the Radio Press to give expert advice and not merely "paper circuits," it has been found necessary to enlarge our staff dealing with such matters. In view of the expense incurred, we are reluctantly compelled to make a charge for replies of 2s. 6d., according to the rules below.

All queries are replied to by post, and therefore the following regulations must be complied with:—

- (1) A postal order to the value of 2s. 6d. for each question must be enclosed, together with the coupon from the current issue and a stamped addressed envelope.
- (2) Not more than three questions will be answered at once.
- (3) Complete designs for sets and complicated wiring diagrams are outside the scope of the department and cannot be supplied.
- (4) Queries should be addressed to Information Department, Radio Press, Ltd., Devereux Court, Strand, London, W.C.2, marking the envelope "Query."




## When most you need CONDENSER EFFICIENCY

With a wide spread interest in high-tensionless receivers, it will be known that the H.T. battery conceals numerous inefficiencies. Condensers are by no means guiltless. In such receivers the H.T. cannot be employed to "boost-up" the weak signals—often the product of faulty condensers.

Where great ingenuity has been displayed to remove any resistance to H.F. currents—the condenser, strangely, has been overlooked as one of the greatest offenders. Some well-known makes are known to offer a very high resistance. Think! What an impermeable wall to H.F. currents.

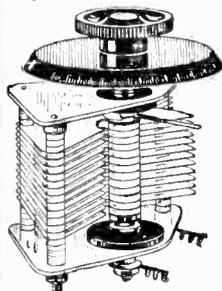When "J.B." Condensers offer a resistance as negligible as 0.05 ohms, the effect upon signal strength is truly amazing. Tuning becomes bright. In fact, if you are building high-tensionless receivers, the only condensers which will bring success to every builder are "J.B."



### SUPER ALL-METAL CONDENSER.

This model has set the standard of modern condenser efficiency. Brass End Plates give it the finish of the scientific instrument which it is. Incorporating all the proven "J.B." mechanical features and generously guaranteed against manufacturing fault for six months. One hole fixing, large top and bottom bush of Grade A, Post Office Ebonite. Spade terminal connections. A distinctive "J.B." condenser costing no more than the many unnamed. The maximum capacity of the "J.B." is up to specification while the minimum is extremely low—essential for capacity reaction circuits and maximum wavelength range.

Twin Model (Brass End Plates) for Dual H.F. tuning. Each half .00025 mfd. ... 19/6 each.

When buying condensers remember that good condensers are the key to perfect reception. Incoming signal energy is lost even in the most efficient tuners. If your condensers are poor further energy is wasted. Therefore use the "J.B." Precision Condenser. They are pre-eminent.

"J.B." Condensers are obtainable from your dealer. If he cannot supply you we strongly advise you to write direct.

Post: One, 6d.; Two, 9d.; Three 1/-.

## JACKSON BROS.

(First Floor) THE Condenser Experts.  
8, Poland St., Oxford St., London, W.1.  
Phone: Gerrard 7414. Trade Inquiries Invited.



A VERNIER BUILT IN!



### MICRO-DENSER


Movement to 1/20° possible with readings on one dial. Crude attachments are superseded. Recommended Complete with for long-distance work Knob and Dial where extremely accurate tuning is indispensable. .001 ... 11/6  
Its H.F. resistance is negligible. This vernier is not an attachment; but is sound engineering practice. .0005 ... 10/-  
.0003 ... 8/9  
.00025 ... 8/9  
.0002 ... 8/-  
.0001 ... 7/9

Twin Model Microdenser for the simultaneous tuning of dual H.F. Stages. Vernier tunings applied to both halves at the same time. Each half .00025 mfd. £1 2 6


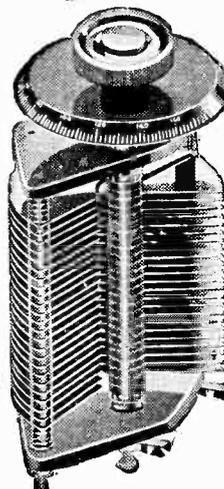
### STANDARD MODEL.

End plates made by special process, ensuring low dielectric losses. Owing to close accurate spacing (dielectric .026), "J.B." take up much less room under panel; silent, metal plain bearings, which do not work slack, are a few of the distinctions obtainable only in the "J.B." Complete with the "J.B." Knob and Dial One hole fixing. .001 ... 8/6  
Spade Terminal .00075 ... 8/-  
Connections provided. .0005 ... 7/-  
.0003 ... 5/9  
This model is a real precision instrument at a minimum cost. .00025 ... 5/9  
.0002 ... 5/-  
.0001 ... 4/9  
Vernier ... 4/-



# AN AMAZING WORK

FOR THE AMATEUR AND THE EXPERT.

The most complete and comprehensive work on Wireless ever published, and of the utmost value to every broadcasting enthusiast.

## WIRELESS TELEPHONY AND BROADCASTING

By H. M. DOWSETT.

For nearly 30 years the author of this wonderful work has been intimately associated with every aspect and development of Wireless Telegraphy and Telephony. He has "demonstrated" in all parts of the world and, apart from his services to various Governments and to the Marconi Company, since 1915 he has been editor of the *Handbook of Technical Instruction for Wireless Telegraphists*, the standard handbook for training ships' operators. Mr. Dowsett is thus thoroughly equipped, not only because of his scientific training as an electrical engineer, but also by reason of his extraordinary practical experience, to produce a work of the highest authority. A glance at the contents of these volumes will show their wide scope, but even a cursory examination of the books themselves would prove they contain a mass of information, of photographs and of diagrams, unequalled in any other work yet produced.

Every page is clearly and fascinatingly written. Every part of each subject is carefully and convincingly explained so that the merest amateur can follow the most intricate description with the ease of an expert. As for the expert himself, he will find hundreds of practical suggestions for improving his own apparatus. Photographs and working drawings abound to elucidate difficult combinations and the most complicated wiring systems are easily unravelled by means of superb coloured diagrams. Mr. Dowsett has produced the *Wireless Vade Mecum*.

SEND THIS COUPON TO-DAY

The GRESHAM PUBLISHING COMPANY, LTD.,  
66, Chandos Street, Covent Garden, London, W.C.2.


Please forward me a copy of the Prospectus of your work, "Wireless Telephony and Broadcasting." It is understood I am under no obligation to purchase.

Name.....

Address.....

M.W. 1.6.24.

(Please write clearly.)

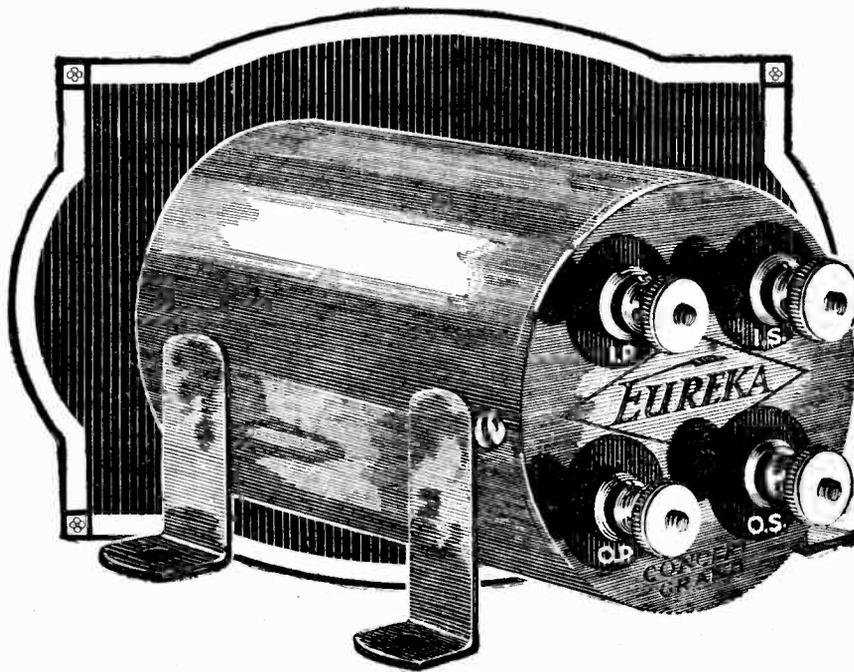

## 2 1/4 miles of wire on a Eureka Concert Grand

INSTEAD of being built to a price, the Eureka Transformer is built to an ideal. As manufacturers of Broadcast Receiving Sets from the commencement, we have had the opportunity of comparing practically every worthwhile Transformer on the market. In our expert opinion, they all failed in one point—purity of tone. Volume they had—for volume is merely the result of mathematical calculation of ratio between windings. A step-up ratio of five to one will produce any amount of noise—it will give volume, but at the expense of purity of tone. The Eureka has been designed regardless of mere cost entirely for those who appreciate the folly of


**Electric Appliances Ltd.**  
7 & 8, Fisher Street, London, W.C.1.  
Scottish Agents: FULLER, BLACKIE & RUSSELL, Ltd., 30, Gordon St., Glasgow.

spending £8 or so on the parts for a three-valve Set and economizing! on the most vital item—the L.F. Transformer.

While other makers, for instance, are so parsimonious as to cut down the amount of wire necessary and use a higher step up ratio to make up for the deficiency, our policy is to use the largest number of turns possible.

Frankly, we would use even more than 2 1/4 miles if the results justified it. That our efforts to produce a Transformer which would set a definite standard of its own—both in appearance, workmanship and performance—are appreciated, is proved by the immense demand for the Eureka.

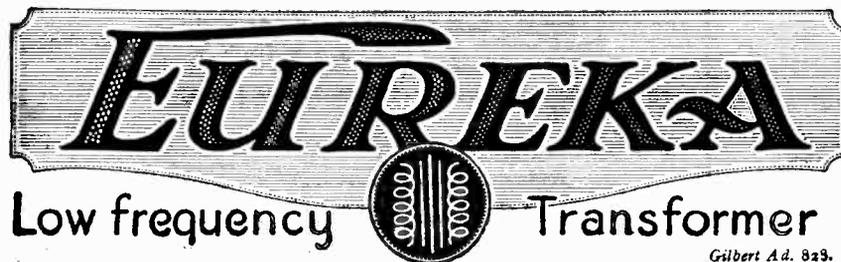In two types from all Dealers:  
**Concert Grand . . . 30/-**  
**No. 2 (for second stage) 22/6**



Gilbert A. d. 829.

Date of Publication: 7th June.

# An Innovation

By  
**RADIO PRESS LTD**

EVER on the watch for new methods of helping readers of MODERN WIRELESS to build up good Receiving Sets that will really work, Radio Press, Ltd., believe that they have hit upon a method that will be extremely popular. The idea is to supply a large cardboard model of the panel of the Receiving Set showing both the back and the front.

## Panel Card No. 1.

### How to make the W 1 3-Valve Set.

Enclosed in the Envelope with the cardboard model of the Panel is a full size drilling plan which can be used as a drilling template for the Ebonite panel. The holes to be drilled are plainly marked and no mistake is possible.

The Cardboard model on one side makes the disposition of each component perfectly plain while the other side clearly shows how every part is wired up.

Full instructions for every step are included together with the theoretical circuit diagram. The total components for this Receiver — even generously priced — do not amount to more than £5 12s. 6d., surely a low figure for a really high-grade 3-Valve Set.

As to operation, this Receiver will easily pick up all B.B.C. stations—the nearest on the Loud Speaker—while 12 miles away it has successfully received 2 L.O. with no aerial at all.

This panel card system is certainly appealing very strongly to those home constructors who want to get a very clear idea of the lay-out and arrangement of the Set before they start work. It undoubtedly permits a very good conception of the ultimate result being obtained before the expenditure of a penny piece on components.

Sold by all Booksellers  
and Published by  
**RADIO PRESS Ltd.**  
Devereux Court,  
**STRAND, W.C.2**  
1/3 Post free.

# 1/-

G.A. 889

# Why Constructors Sometimes Fail

## A Short Chat on an Ever-Topical Subject

By the EDITOR

**N**O matter how efficient a set is described, no matter how simple the construction, no matter how detailed and lucid the instructions, there are always a certain number who do not get the full results, and some who do not get any results at all.

We have, as an organization which depends almost entirely on the confidence which the public places in our designs and circuits, made a special study of the constructor's troubles and tried in every possible way to produce constructional articles which would ensure success.

### The Constructive Ability

The constructor, before he makes his set, must not over-estimate his own ability. He must, moreover, have regard to the simplicity of design of the set. The simpler the design, the greater will be the proportion of constructors who achieve success with the set. For example, a set in which the first valve acts as a detector and the second as a low-frequency amplifier, if built up by one hundred readers would probably result in 90 per cent. getting the correct results. Add reaction to the set and probably 80 per cent. would get the desired results; the others would probably use the wrong sizes of coils, would not tune correctly, would have the reaction coil connected the wrong way round, or something of the sort.

### H.F. Troubles

If, now, a set containing a stage of high-frequency amplification is made, the chances are that the number of successful sets will be lower; while if a dual receiver using two or more valves is described, perhaps only 60 per cent. would get good results.

The fault is either in the article or in the constructor, or just as likely in the apparatus he uses.

As regards the effectiveness of the sets described in MODERN WIRELESS and *Wireless Weekly*, there can be no question. Every

single set which is now published in MODERN WIRELESS and *Wireless Weekly* has been personally tested by a member of the Radio Press staff fully qualified to carry out the work, and I myself, as a matter of personal interest, have tried out many of the sets.

Readers will also be interested to know that sets constructed for MODERN WIRELESS and *Wireless Weekly* are frequently exchanged between different members of the staff to try out. From this it will be seen that every precaution is taken to see that the actual set gives really good results.

We could easily arrange for any one having any doubts as to the capabilities of a set to have a demonstration, provided the application was made early enough and before the set was dismantled.

As regards the description of sets, the numerous letters which we receive make it clear that even absolute beginners frequently get excellent results the first time. Very rarely some slight error in the description occurs, and a correction, in such cases, invariably appears in the next issue of the paper concerned.

### "Improvements"

The reason for lack of success, in some cases, must therefore be looked for elsewhere. It is astounding the extent to which designs published in these papers are improved upon by constructors. A straightforward panel set is converted into a most elaborate cabinet set looking like a piece of furniture, with great long leads between different parts of the set, and innumerable switches introduced to enable different combinations to be obtained. When the set does not work the constructor writes plaintively to us and expects to receive our sympathy and advice.

Some other constructor, even if he adheres to the described arrangement, alters the components and perhaps connects in the set some shabby, nameless transformer.

While we do not expect every constructor to buy a complete set of new components for every set he makes, yet if he departs from the description he does so entirely at his own risk. In some kind of circuits the substitution of different transformers, for example, causes entirely different results to be obtained.

### Transformer Troubles

Where only one note magnifier is employed, the chances are that different transformers may be tried without very much difference, but when two transformers are employed, a low-frequency howl may be set up, or bad distortion may arise. These disadvantages may be corrected to some extent by the man who has a good grounding in the general technics of valve circuits, and problems of this nature are dealt with very frequently in my weekly "Valve Notes" published in *Wireless Weekly*. The constructor, however, without much technical knowledge of the subject meets with difficulties. This is particularly the case when dual circuits are being arranged. I do not for a moment suggest that any particular type of transformer is best for dual circuits; I do, however, suggest that if a constructor departs from the instructions given in the article dealing with a dual circuit, he may find that the results he gets are very different from those which the author of the article originally got.

For example, with a certain pair of transformers, a certain condenser connected in a certain position might be found desirable by the author of the article. The arrangement may be perfectly stable, but if some other kind of transformer is used, the reaction may be increased, or some other effect may be varied, and the circuit may be unstable and give inferior results.

### Dual Circuits

In dual circuits, particularly, is it desirable to adhere strictly to

the specification if at all possible. Often the specification may be varied by the substitution of different components, but, as stated before, the risk is the constructor's. In order to ensure that the set may be exactly reproduced, we are making a practice of specifying the actual names of all the components. This has been done as a result of the answers on question papers which we recently issued. Not only are these lists of components valuable to those who desire to reproduce the set exactly as described, but they also give the constructor some idea of reliable component parts. An unsatisfactory component would naturally not find its way into one of our sets.

While writing about components, it might be as well to suggest to readers that the practice of going into a shop and buying a variometer, or condenser, or even small components such as valve holders, of nameless brand, is a very dangerous practice. The great interest in radio has resulted in a large number of nonentities producing inferior stuff which is sold at large discount to shop-keepers. Many of these, even with the best intentions, may sell these components without knowing their inherent faults. For example, in the case of a valve holder, the effect of a perfectly constructed set may be completely spoiled by leakage in the valve holder due to the use of inferior composition or ebonite.

**An Ebonite Warning**

The same warning may be issued in connection with ebonite, which is sold in many grades, including very poor quality material quite unsuitable for wireless reception. Unfortunately, the selling of branded ebonite is all but unknown in this country, and the lack of enterprise amongst ebonite manufacturers is such that I cannot recall one particular brand which is sold for wireless purposes under a branded name. The result is that the constructor may have very inferior ebonite sold to him, and the only real way to make sure of the quality of the ebonite is to buy a guaranteed branded manufacture, and I would urge readers to support those who are prepared to give a name for their ebonite and guarantee that it is made to a standard.

**Nameless Goods**

We cannot emphasize sufficiently the dangers of buying nameless goods. Frequently such goods are a trifle cheaper; their origin is always doubtful; and if the apparatus is faulty you have nobody

to blame. In the case of named goods, you know the manufacturer, and if there is anything faulty he will replace it.

Readers of our papers who order apparatus from advertisers are particularly secure. If they have any complaint regarding either the quality of the goods supplied or delay in delivery, and they fail to get satisfaction, they have the whole weight of Radio Press, Limited, behind them to have their wrongs set right. In no single case have we been appealed to and failed to obtain full satisfaction for our reader. As a matter of fact, such cases are exceedingly rare because we exercise particular care when accepting advertisements.

The manufacturer of a product which he knows is not of high standing never attempts to advertise it in a reputable journal. Nevertheless, his products very frequently get into the shops, and the foolish purchaser can get no redress.

**Minor Faults**

The experience of individual members of our staff, and of our Information Department, indicates that frequently the source of trouble is in some minor component which is, perhaps, of faulty insulation. A valve holder, for example, is a frequent source of trouble, in spite of the fact that special valve holders are now marketed with widely spaced connections, so that not only is the capacity effect greatly reduced, but also the chance of leakage. The ordinary valve holder with nuts is a very frequent source of trouble; the nuts come very close to each other, and not only is there a greater capacity between the pins, but a very serious chance of leakage. A little dirt, and a few filings, and the set will either not work at all or work in a very inferior manner. A few more pence on a special valve holder will insure you against this trouble.

**Tuning**


Tuning is also a very common source of trouble to beginners, although to the experienced man it will seem very simple. There are still an extraordinary number of constructors who do not realise that when tuning a set it should be possible to tune out both above and below the incoming wavelength. The question of different aerials is an extremely important one and a set which may be stable on one aerial may oscillate furiously on another. For this reason I am encouraging the fitting of sets with a constant aerial tuning con-

denser, consisting of a series condenser of 0.0001  $\mu$ F capacity in series with the aerial, parallel tuning being used. The use of this fixed condenser virtually places practically all aerials on the same plane, by reducing their capacity to a minimum, enabling similar coils to be used in all cases.

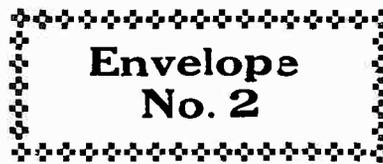**Valves**

As regards valves, I do not attach very much importance to specifying valves in constructional articles. The valves at present on the market are all very much of a muchness, although some manufacturers seem to ensure a uniform standard for their valves, an extremely important matter for the enterprising valve manufacturer.

As regards distortionless reception, this is a matter in which technical knowledge plays more part than anything else; it is a question of the proper operation of the set, the avoidance of excessive reaction, the introduction of grid bias on the low-frequency amplifying valves, the use of good quality transformers, and the ability to introduce various correctives, such as resistances and condensers, to ensure perfect reproduction. Only by reading notes of the character outlined above will the home constructor be able to get the best results. There is far more in radio than merely joining together a number of different components and mounting them on a panel. The best results will always be obtained by those who have some theoretical knowledge of the subject.




To the Editor of MODERN WIRELESS.

SIR,—I have just built "The Family Four-Valve Receiver, No. 2 Envelope," the components being exactly as description, except that I have used "Silvertown" transformers and ebonite panel. I get all B.B.C. stations on G.E.C. loud-speaker with wonderful clearness and volume. Our local station and Manchester I have to tune down when using four valves; the latter station comes in practically as loud as Sheffield and with exceptional clearness. I thought it well to make known my result as this is my first attempt at building a set.

Yours faithfully,  
J. W. MORTON.

Sheffield.

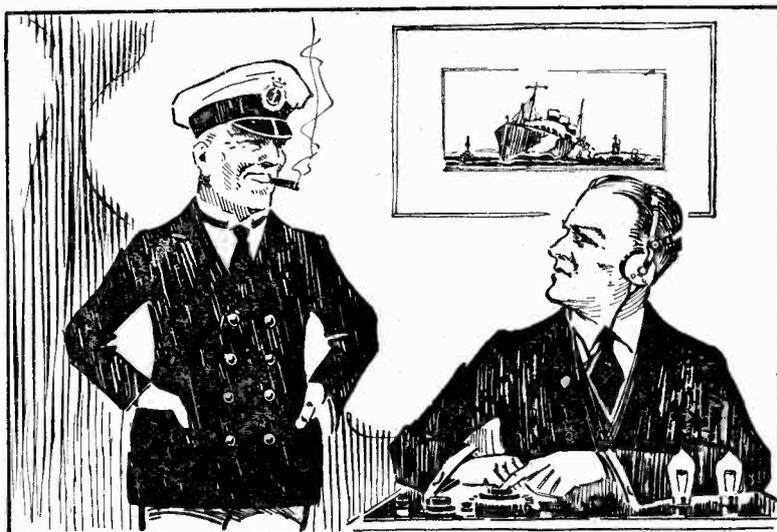

## “If it’s good enough for the biggest ships afloat . .

where Wireless is, of necessity, a matter demanding the R.C.C. Standard of accuracy and efficiency, then the Polar Condenser has certain advantages which you wireless landmen would do well to note:

- 1.—Wide capacity limits.
- 2.—Insulation tested to 1,000 volts.
- 3.—Complete metallic screening.
- 4.—A conveniently divided tuning scale.

*This is an ideal arrangement from all points of view, as the scale is marked in wavelengths (metres) and the capacity is graded so as to give uniform change of WAVE-FREQUENCY for a given movement at any part of the scale.*

- 5.—Robust construction.
- 6.—Compactness.
- 7.—Ease of panel mounting.
- 8.—Low price.

You can buy the POLAR CONDENSER in the following capacities:—  
.001; .0002; .0003; .0005.

#### USES FOR “POLAR” CONDENSERS.

“Polar” Condensers are eminently suitable for the following purposes:—

- (a) Aerial tuning—either series or parallel arrangements—.001 recommended.
- (b) Secondary tuning any capacity may be used, but .001 recommended.
- (c) Tuning of High Frequency Transformers .0005 or .0003 recommended.
- (d) Tuning of High Frequency Reactances .0003 recommended.
- (e) Tuning of separate heterodyne or wavemeter circuits .001 recommended.
- (f) For other general purposes .001 should be used.

Prices: Unmounted, 10/6; Mounted, 20/-; from all Polar Stockists.

Any of the above capacities can be changed to an alternative Maximum Capacity by forwarding the Condenser, with covering remittance of 2/6, to:—




Fleet Ad. Co.

In replying to advertisers, use COUPON on last page



*I've something to show you  
at Wembley!  
Yours  
Stella.*

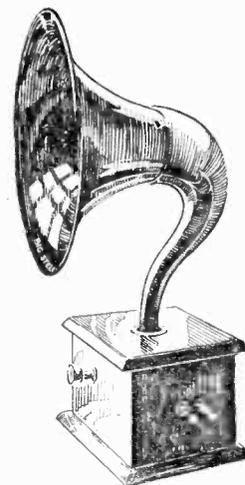PALACE OF ENGINEERING,  
Avenue 11, Bays 8 & 9.  
BRITISH EMPIRE EXHIBITION.



**The WEMBLEY PHONE** (as illustrated).

THE greatest triumph of British Wireless Manufacturing skill, a phone which not only completely outclasses any higher priced headsets by its perfect reception, but is made to sell at a price which at last competes with the inferior imported models—neither of British origin nor backed by responsible Guarantees. The Wembley Phone is BRITISH MADE and GUARANTEED at 14/6 a pair.

**The STELLA PHONE.**

A Super model of the perfect lightweight headset. Like the Wembley Phone, this is entirely British owned and fully guaranteed to give perfect reception. It fits comfortably and lightly yet firmly to the ears, and every pair is most carefully tuned before your dealer gets them. You may pay more, but the extra money will not give you any advantage over the wonderfully clear reproduction you get from the Stella Phone at 17/6 a pair.



14/6

Buy at Wembley, or from any good Wireless Dealer. If unable to obtain from your local store, write direct to:—

**STELLA WORKS,**  
31-37, Wybert Street, LONDON, N.W.1.

Telephone : Museum 8390.

**STELLA  
Loudspeakers.**

Big Stella Mounted in polished Mahogany Cabinet. Guaranteed perfect in every way, 70/-.  
Little Stella, 35/-.  
BEE. N. S. 700022

**“ POWQUIP ”**

**NOTICE TO OUR PRESENT AND PROSPECTIVE CUSTOMERS.**

In order to deal satisfactorily with the enormous demand for “Powquip” intervalve transformers we have found it necessary to take over much larger premises and install extra plant.

We are now in a position to supply “Powquip” transformers in any quantity, large or small, and our up-to-date methods of manufacture and careful inspection ensure that the standard of our products shall be fully maintained.



**“THE TONE IS BRILLIANT.”**

NEW ADDRESS :

**KINGSBURY WORKS, KINGSBURY LANE, THE HYDE,  
HENDON, N.W.9.**



Std. type. Ratio 4 : 1 for 1st stage  
Ratio 2 : 1 subsequent stages.  
**PRICE 14/6**  
either ratio.

Telephone : Kingsbury, 196 and 197.  
Telegrams : “Powquip,” Hyde, London.

Shrouded type. Ratio 4 : 1 1st stage.  
Ratio 2 : 1 subsequent stages.  
**PRICE 18/-**  
either ratio.

**SPECIAL TRANSFORMER RATIO 14 : 1 FOR HIGH TENSIONLESS CIRCUITS, PRICE 16/-**



#### Accumulator Terminal Clips

Messrs. The Runbaken Magneto Co., Ltd., have sent for report a sample of their Radio Accumulator Terminal Clips, for making connections to the accumulator. These are easily removed and non-corrosive. They take the form of a strong spring jaw, with teeth, opening about  $\frac{3}{8}$  in., which can grip the nut or screw of an accumulator terminal, and cut through a superficial layer of corrosion so as to make good electrical contact. The hold was found to be extremely firm, and on trial, even on a badly corroded terminal, where the terminal nut could not be moved without endangering the lead plates, a low-resistance connection was possible.

The connecting wire is made fast to a small screw in the other end of the clip, small tags being bent down on the insulated covering to hold it the more securely.

It might be suggested that the clips would be somewhat easier to connect up if the screw to hold the lead-wire were a little longer. Except for this small point, the clips can certainly be recommended as a substitute on accumulators for ordinary terminals, where sooner or later the latter always corrode and give trouble.

#### Harmotone Crystal

Messrs. The Sclerine Crystal Co. have sent for test a sample of their "Harmotone" crystal, in boxed form, and with a special cat's-whisker. This is a coarsely granular galena type of crystal. The number of sensitive points was found on trial to be very great, and a freshly broken surface showed similar results. Tested

quantitatively and qualitatively in aural tests, in comparison with the customary standard of galena crystals, it showed up well as a good all-round crystal for general use and in reflex circuits.

#### A Short-Wave Plug-in H.F. Transformer

Messrs. Leslie McMichael & Co., Ltd., have handed us for trial a plug-in H.F. transformer to cover the range from 80 to 150 metres, with a .0003  $\mu$ F parallel tuning condenser. This is a highly



A McMichael H.F. short-wave transformer.

finished unit, with the windings in slots on a  $1\frac{1}{2}$  in. diameter ebonite cylinder, and having the usual four-pin fitting at the lower end.

On test it proved to cover exactly the stated range with a condenser of the specified size, and operated successfully in a two-valve short-wave receiver, short-wave amateur Morse and telephony being received with fair selectivity. The amplification was, as is usually observed on these extremely short waves, not of a very high order.

#### Inductance Formers

Messrs. London Hydroid Products, Ltd., have submitted for test samples of their water-proof tubes for inductance formers, which they make in various sizes in demand. The samples were of the 4 in., 4 $\frac{1}{4}$  in., and 5 in. diameter types.

These tubes were of a stout cardboard, treated in a manner to render them less susceptible to moisture. This was confirmed by actual trial by immersing it in water. Tested practically as a former for a receiving tuning-inductance, the signal-strength, sharpness of tuning, and small reaction-demands for steady oscillation gave evidence of small dielectric losses. The insulation-resistance between brass screws inserted an inch apart was the satisfactory figure of nearly 30 megohms.

The tubes were mechanically strong, standing up to a cutting-tool and not tearing readily where wires were brought through for tappings and ends of coils.

#### A Steel Accumulator

Many of the troubles associated with the ordinary lead accumulator appear to be eliminated in the Ni-Fe cell supplied by Messrs. Batteries, Ltd., of Redditch. These are of the type usually known as the Edison cell; they are made under the Swedish Jungner patents. Both of the plates, and the container as well in some models, are made of steel, whilst the electrolyte is an alkaline solution. The voltage per cell falls from about 1.5 to 1.1 during discharge, the greater part of the effective discharge being

**DIAMOND WIRELESS LTD.**

**Filament Rheostats** 5 ohm turned ebonite former .. 1/6

**L.E.S. micro control** 50 ohm for all types of valve .. 3/6

**Harney Crystal Detector** Micrometer adjustment .. 3/6

**Coil holders**, all ebonite, smooth action and beautiful finish, 2 way 3/6, 3 way 4/6

**Variometer**, solid ebonite, internally wound, ball rotor and former 300-700m. With knob and dial. Wonderful value. .. 10/6

**Dr. Nesper Phones.** World famous 4,000 ohm. We guarantee each pair .. 15/6

**Basket coils.** Set of 300-3,000 metres .. 1/11

**H.T. Batteries.** 60 v. excellent, with plugs .. 8/6

**Spearpoint Catswhiskers** Phosverum alloy .. each -/3

**"Diamic" Crystals.** Type A. Exceptional results, per tube 1/3

**Diamond Loudspeakers.** Wonderful tone and strength From .. 18/6 to £3

*We guarantee everything we sell.*

Large assortment of sets and all types of accessories. Visit our showrooms or write for catalogue.

**DIAMOND WIRELESS, LTD.**  
184, Oxford Street, London, W.1.

around 1.2 volts. A very large range of sizes is listed by the manufacturers, up to the largest for power purposes; those recommended for radio are rated at 5 volts (for 4-volt valves), and from 22 to 90 ampere-hours (actual) capacity. These have four cells. Some three-cell types are also listed which would be suitable for the .06 type of valve. The makers claim that these cells are immune from self-discharge; e.g., a small cell they make for bell-ringing and similar domestic uses can be charged once a year, and will last almost indefinitely.

A small two-cell unit, type dAr, of 10 ampere-hours capacity, and rated voltage of 2.5, was submitted for test by the makers, and was put through an ordeal that very few batteries of any type would have any chance of surviving, without apparently suffering the least damage, giving the full capacity and unimpaired voltage after the ill-treatment.

The battery was in a strong steel container, 3 by 2½ by 4 in., and weighed just under 3 lb. Substantial nut terminals, insulated by rubber sleeves, were provided in the top, and screw vent-plugs. The cell was wrapped up in a paper parcel, with no attempt to keep it right side up: only a very slight seepage had taken place, and this of relatively harmless alkali.

The accumulator gave about 2.5 volts on open circuit; with 10 amperes current the voltage was 2. On steady discharge at about 1 ampere, the voltage was, for the better part of the time, around 2.4 volts, and full capacity was shown. After running down completely overnight, and short-circuiting with a short copper wire for half an hour, the cell was rolled down a short flight of stairs, and then thrown out of a first-storey window on to a grass lawn. It was then inverted over a clean sheet of paper; after some time only a very slight seepage of alkali took place.

After standing discharged for a day the voltage had recovered to 2 volts. It was then charged at a rate of approximately 7 amperes, for four hours. Discharged at a 1-ampere rate, it gave approximately 11 ampere-hours, the voltage falling meanwhile from 3. (when freshly charged) to 2.4 and 2.2. It was then short-circuited for half an hour, and placed on charge reversed (a thing that has been known to happen at charging stations) at a 10-ampere rate for two hours. It showed a reversed

voltage of 3 volts, rapidly falling to zero. On giving a charge in the right direction, now at a 5-ampere rate for some four hours, it was gassing freely, and showed full voltage; discharging through a valve which took .4 ampere, it gave practically full capacity, and in actual reception was silent and quite satisfactory in every way.

Several subsequent charges and discharges confirmed that the accumulator was in no way injured by this drastic treatment.

It is an accepted fact that the Edison type of accumulator has a rather smaller current efficiency than the lead type; this fact is of small moment in connection with the accumulators used in a radio set. But the matter of voltage-drop during discharge must be taken into account; for this reason the 5-volt (four-cell) type is recommended for 4-volt valves, and the three-cell for valves requiring 2.5-3 volts.

Whilst the initial cost of these Ni-Fe accumulators is heavy, being twice to three times that of the ordinary lead accumulator, the makers rightly point out that the immunity from sulphating, buckling of plates, etc., and the life, measured in years, which can be expected from a steel accumulator in a steel container, must be set off against first cost.

**Plug-in Basket-Coils and H.F. Transformers**

Messrs. Reynolds & Bradwell have sent for test types of their plug-mounted basket-coils on rigid formers, and basket-coil transformers of the plug-in variety.

The coils are wound on small wooden spokes fixed firmly into an ebonite centre-piece, and fastened securely into the standard type of plug-and-socket fitting for use in ordinary coil-holders. The lower members are wound of a reasonably stout gauge of wire. The construction is neat and substantial, the coils, unlike most basket-coils, appear to be capable of withstanding hard wear and rough treatment.

On actual test, on a double 40 ft. P.M.G. aerial, the range covered with a .0005 μF (actual—not "nominal") variable condenser in parallel was: No. 2, 375-510 metres; No. 3, 460-680 metres; No. 4, 700-1,000 metres; No. 5, 1,000 to 1,450 metres; No. A, 1,300-2,320 metres; No. B, 1,700-3,000 metres; No. C, 2,400 to over 4,000 metres (the last three with .001 condenser). The figures given by the maker differ somewhat from these, and were evidently

**YOUR CABINETS.**

The original House for hand-polished Mahogany, Oak and Teak Cabinets made to customer's own design. Ebonite Panels cut to size, drilled and engraved.

**SPECIAL**

2 M.F. MANSBRIDGE CONDENSERS to H.T. etc. 2/6 each. Post Free.

**W. H. AGAR,**  
MANUFACTURER OF TELEPHONE and RADIO APPARATUS.

Tel. L. Wall 3305. 19, WHITECROSS PLACE, WILSON STREET, E.C.2.

**Leadership**

**I**N every sphere of life or field of business, one man or one firm leaps to the front.

**L**EADERSHIP, however, creates responsibilities. We realise our duty, and appreciate that our duty to the ever increasing number of readers of *Modern Wireless* and *Wireless Weekly* lies in maintaining the high standard of quality prevailing at their inception.

**RADIO PRESS LTD.**  
Devereux Court, Strand, W.C.2.

determined on an aerial of lower capacity. It will be noticed that the No. 2 is not available for the lower wavelength stations, except on an aerial of small electrical capacity or by the use of a series condenser of unusually large size. The No. 3 is also of rather awkward size, as when used with a series condenser (the most efficient manner for valve-reception) one of ordinary size is not very convenient. It is possible that the makers, who are located in Birmingham, were chiefly concerned with a design most suitable for 475 metre reception.

The matter of overlap to cover the whole range might receive attention also. With a series condenser there was no difficulty in choosing a suitable reaction-coil.

In actual reception very satisfactory results were obtained with these coils, tuning being sharp and selectivity higher than is usually observed with plug-in coils. The No. 2 coil, with a .0001  $\mu$ F parallel tuning-condenser at its minimum, when it just tuned to 365 metres on the large aerial, gave a signal-strength, measured by rectification of whole carrier wave of the local station, at least as high as any commercial tuning-device we have tested, being actually 90 per cent. of the standard.

In valve reception, with critical reaction, an unprecedentedly high figure for the signal-voltage was also recorded. The effect of the generous wire-size and small dielectric losses and distributed capacity were noticeable here. With the Nos. 3 and 4, and series condenser, Cardiff, Manchester, Newcastle, Glasgow, Birmingham, Postes et Télégraphes, and Brussels came in well with a detector-valve alone. Aberdeen happened to be badly jammed by Morse.

The plug-in H.F. transformers were of similar general design, but with the customary 4-pin fitting for plugging into a valve-socket holder. The two windings were apparently wound on together on the same former. On test with the "Meg" tester, the mutual insulation-resistance proved to be adequate.

The T2 covered from below 300 to 530 metres with a .0002  $\mu$ F parallel tuning condenser, and with efficient tuning device and L.F. stage, on an I—V—I receiver all the broadcast stations came in well on the loud-speaker, with this as H.F. coupling. The T4 covered from 600 to 1,250 metres; T6 from 1,100 to 2,200; and T7

from 1,800 to 3,200 metres. With three valves Radiola came in extraordinarily well with the T6 on the loud-speaker; Eiffel and Königswusterhausen on the T7—Eiffel being readable on two valves on the loud-speaker.

With a reservation as to the precise numbers of turns on the lower members, these coils and H.F. transformers can be heartily recommended for experiment and regular use, showing an efficiency which compares favourably with that of any of the commercial types of plug-in inductances available.

#### Terminal Tags

Samples of terminal tags have been sent for inspection by S. H. Collett from a wide range of different types manufactured. These are made of the spade and eyelet variety, in brass and copper, and bright, tinned, or nickelled finish, of various sizes. The samples submitted proved to be of the right kind of material, being sufficiently malleable to endure opening up of the jaws to remove an old wire and to replace a fresh one—a severe test. The soldering-tags tinned easily and stood sharp bending.

**A Reader's results  
with the  
Auto - Transformer  
Crystal Set**

To the Editor of MODERN WIRELESS.

SIR,—It may interest you to know that I made up the auto-transformer crystal set described in your spring number. I used 22 and 26 S.W.G. wire instead of the thick wire recommended, and obtained wonderfully good results for a crystal set. Aerial is a standard P.M.G. one, with ordinary water-pipe earth.

Signals are quite loud, and when things are quiet in the vicinity every word from 2LO can be easily heard and distinguished.

The set is made up quite roughly and nothing whatever is soldered.

Perhaps you may describe in an early issue of MODERN WIRELESS how to make a set of this description to receive signals from the proposed 1,600 metre station.

Wishing your paper every success, I am, yours truly,

D. A. TROWBRIDGE.


Staines, Middlesex.

# Quality

## RADIO

### COMPONENTS.

ASK YOUR DEALER FOR THEM

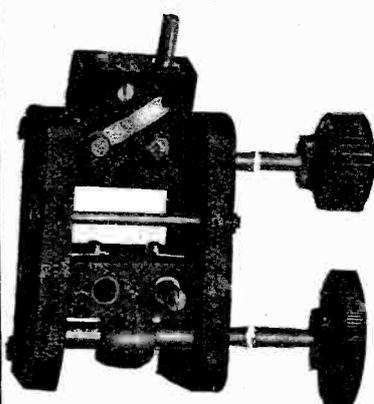

(Prov. Protected.)

### CAM-VERNIER COIL HOLDER


With Reaction Reverse and Shorting Switch.

Price 12/6. Without Switch, 9/-  
Postage 4d.



### CONDENSER & SET CLEANER

Price 9d each. Postage 2d.

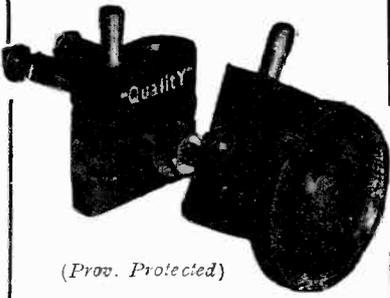

(Prov. Protected.)

### VERTICAL COIL HOLDER

New type for use on vertical panels and inside cabinet doors.

Price 7/6. Postage 3d.

LIST POST FREE.

## GOSWELL


### ENGINEERING CO., LTD.,

12a, PENTONVILLE RD., LONDON, N.1.  
Liberal Trade Terms. Phone: North 3051.

(Continued from page 22.)

the broadcasting station (say 10 or 15 miles) you will hear signals in excellent strength and will not need to use reaction. If, however, you are some distance away turn your potentiometer knob slowly clockwise until you find the best reaction effect produced. For every small movement of the potentiometer readjust your condensers so that you do not suddenly hit oscillation point and cause howling. When you have practised this and obtained the best signals from your local station (I am assuming that you connected the telephones to their right terminals and also a loud-speaker to the specified position) turn the change-over switch to the 5-valve position and light your last two valves by turning on the filament resistances. You should now get excellent signals in the loud-speaker and a little practice with the switch will show you that it is a simple matter to tune in on three valves and then, when everything is right, to turn on to 5-valves for the loud-speaker. You will be astonished at the purity and quality of signals obtained. Note that the change-over switches turn the last filaments on and off.

If you are very close to a broadcasting station you will find that you can turn off the high-frequency filaments leaving the detecting valve alone alight and still hear excellently either on telephones or using the change-over switch on the loud-speaker. For distant stations you will find that the reaction is controlled by the potentiometer without the use of any reaction coil, and on my own aerial I find it is easy to obtain all the reaction necessary to bring the set up to oscillation point with this potentiometer, even on the longer wave such as that used for the Eiffel Tower telephony. However, on some aerials which do not oscillate easily, it may be necessary on the longer wavelengths to use a small reaction coil. If this is so then withdraw the short-circuiting plug and plug-in, say, a 35 or similar coil, and use it carefully to obtain the reaction effects.

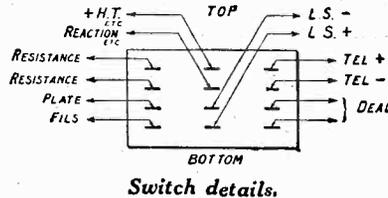


**Valves to Use**

The reader has a very wide choice in the valves he can use, and it would be invidious to make comparisons. I would recommend, however, if it is possible to do so and if you have large enough accumulators, to use bright emitters throughout. For the two high-frequency sockets choose valves which are good for this work. Most of the general-purpose valves will do here, and there are one or two valves sold specially for high-frequency amplification. For detecting any good general-purpose valve will do, or a special detecting valve such as the R.4.B. made by the Marconi Osram Company. "R" type valves serve excellently for the note magnifying stages, and I would recommend you to use on them not less than 100 volts. For the very best results, of course, you should use a power valve in the last socket with the correct grid bias. Readers who construct this set are invited to write to us stating the results they obtain, and in particular the valves they use. Comparisons of readers' results are very helpful.

# BEST BY TEST.

## "ELLA" BATTERY CHARGERS.

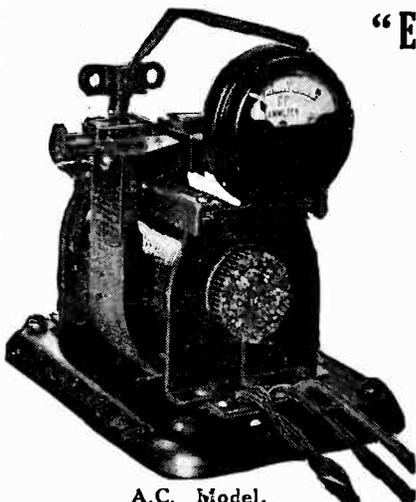


A.C. Model.

Output 5/10 amps. 9 volts. Complete with Pole Indicating Ammeter and all connecting leads and adapter - - \$6 8 0

Wherever electric light is installed wireless accumulators can be charged CHEAPLY and EFFICIENTLY by means of the "ELLA" Battery Charger.

No need to pay exorbitant prices for recharging. Install an "ELLA" and be independent. At the same time charge the batteries of your friends who are not so fortunate as to have electricity supply. Save the price of the Battery Charger and reduce the maintenance cost of your wireless set.

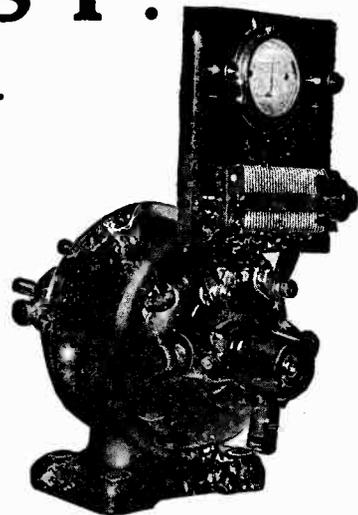Send for Descriptive Leaflet.  
Trade also supplied.




D.C. Model.

Output 5 amps. 9 volts. Machine only \$5 12 6. With Switchboard and Pole Indicating Ammeter and Regulating Resistance as illustrated - - \$6 15 0

**LIONEL ROBINSON & CO.** 3, Staple Inn, London, W.C.2.

'Phone: Holborn 6323 (Two Lines).

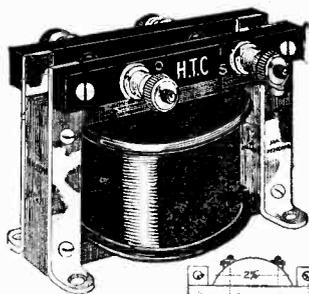


By reason of imperfect design many transformers perform satisfactorily only under certain conditions. This inefficiency has been overcome by the H.T.C. Its design is such that all conditions are favourable. The H.T.C. operates over the extremely wide range of frequencies contained in Broadcast without accentuating any one note or its harmonics. The design also allows for the varying strength of signals so that there is no possibility of any distortion due to overloading. In fact, the H.T.C. is an excellent all-round transformer. You may purchase with more than trust; you may buy them with confidence, although the price is low. The H.T.C. Telephone Transformer is equally perfect, and similar in appearance and finish.

Price 15/- each.

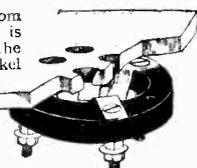**H.T.C. PRODUCTS ARE SCIENTIFICALLY DESIGNED AND THEIR ELECTRICAL PERFORMANCE IS UNRIVALLED**

Again we have successfully made a departure from conventional design in the H.T.C. Valve Holder. It is compact and allows the valve to fit flush to the panel. Contact is made by means of tongues of nickel silver springing against the valve legs. The great advantage of the H.T.C. Valve Holder is a very low capacity and high insulation, which gives a vastly increased efficiency. As no metal parts are exposed it is impossible to short the H.T. across the filament. Type C, as used in constructional articles elsewhere in this issue. (Template supplied.) 1/6 each. Type A. (above Panel Model), 1/9 each.



Patent Pending. Type C

If your local dealer cannot supply write direct to:

**H.T.C. ELECTRICAL CO., LTD.,**  
2 & 2a, BOUNDARIES ROAD, BALHAM, S.W.12.  
Trade Enquiries Invited. TELEPHONE: Battersea 374

**PARAGON**

Is more than a name—it is the recognised **STANDARD OF PERFECT EBONITE QUALITY.**

Exclusive in specification and manufactured to meet the most exacting Radio requirements.

**25** / 0 increased machining speed, without chipping, and double life for cutting tools, are but other exclusive features of

**PARAGON EBONITE**

(Guaranteed to Admiralty "B" Specification)

**Sheets, Rods, Tubes and MOULDINGS FOR ALL PURPOSES.**

Telephone ear caps, transformer and magneto bobbins, magneto parts, rough or machined mouldings of all descriptions.

**WHOLESALE ONLY.**

**The PARAGON Rubber Manufacturing Co., Ltd., HULL.**

**LONDON STORES DEPOT,**  
34-36, Whitfield Street, W.1.  
Telephone, Museum 8489.

**TESTED and RECOMMENDED BY**

**MODERN WIRELESS**

**PARAGON**

Guaranteed Radio Quality Admiralty "B"

*"The Best Made."* **EBONITE PANELS**

Fine grain, dry matt finish, ground edges.

**EACH PANEL in SEALED CARTON**  
Stamped "PARAGON."

**STANDARD SIZES.**

6 1/2 x 5 1/2 x 3/16	1/9d	14 x 12 x 1/4	10/6
6 1/2 x 5 1/2 x 1/4	2/3d	16 x 12 x 1/4	12/-
8 x 6 x 3/16	2/6d	24 x 10 x 1/4	15/-
8 x 6 x 1/4	3/3d	10 1/2 x 7 x 1/4	4/7d
10 1/2 x 8 1/2 x 1/4	5/6d	12 x 6 x 1/4	4/6d
12 x 10 x 1/4	7/6d		

**SPECIAL PANELS**, similar quality and finish, CUT, EDGES SQUARED and despatched same day. 3d. per square inch—postage 6d. extra.

**Stocked by all reputable Stores.**  
But it must be "Paragon."

**PETER CURTIS, LTD.,**

34-36, Whitfield Street, London, W.1.  
Telegrams: "Paracurtex." Phone: Museum 8489.

In Conjunction with  
**The PARAGON Rubber Manufacturing Co., Ltd.**

**Manufacture of Broadcasting Apparatus.**

**USE OF PATENTS**

**T**HE pioneer work of the Marconi Company in connection with wireless telegraphy and telephony is well known, and as the result of many years of research work and considerable expenditure, the Company controls numerous patents relating to the manufacture or use of wireless telegraph and telephone apparatus.

The Company is prepared to grant a licence for the use of its patents in connection with the manufacture of broadcasting apparatus to any member of the British Broadcasting Company, Limited.

A large number of firms (including the principal manufacturers) are already so licensed and pay royalty for the use of these patents, and all apparatus manufactured under licence is so marked.

Any persons or firms manufacturing or offering for sale valve apparatus embodying patents controlled by Marconi's Wireless Telegraph Company, Ltd., without its permission render themselves liable to legal proceedings for infringement.

Whilst hoping that it will not be forced to take legal proceedings the Marconi Company wishes to give notice of its intention to protect its own interests and those of its licensees, and in cases of infringement the Company will be reluctantly compelled to take such steps as may be necessary to defend its patent rights.

**Marconi's Wireless Telegraph Co., Ltd.,**  
Marconi House, Strand, London, W.C.2.

**THE SUPER GADGET!! (Patents Pending)**

Why waste time and money on "Onani" or other special Change-circuit sets when you can do all, and more, on any good standard set by using the

**HUMPHRYS Valve Adaptor? Post Free 3s. 3d.**

e.g.: A certain man had a Burndepth Ultra IV. and 4 Valves (a D.E. 3, 2 D.E.R.'s, and a B.4). The one requires a dry battery, and the D.E.R.'s a 2 volt accumulator, but the B.4 requires a 6 volt accumulator. He wanted to convert his set so as to use each valve with its appropriate battery. Moreover, he wanted a **Tuned Anode and Potentiometer** for the first Valve and an **additional H.T. battery** for the last with a **Grid Bias** upon the last 2 Valves.

The job took under 2 minutes, using four HUMPHRYS Adaptors! In no standard set in the world could this be done except by use of the HUMPHRYS Adaptor. It is uncanny in its possibilities and its powers. Everything converted, yet nothing altered!

S.T. 100 and Reflex circuits strung up on B.B.C. sets while you watch.

**CAN YOU BEAT IT?**

By another device (Patents pending) I eliminate all H.T. from the Detector Valve, obtaining thereby incomparable clarity of reception. *Come and see it.* New and second-hand High Grade Burndepth, Marconi, Elwell and other B.B.C. and experimenters' sets always in stock at cheapest prices.

Buy from me and you get **Expert Service Day and Night.**  
**W. E. H. HUMPHRYS, 14, CLIFFORD STREET, BOND STREET, LONDON, W. 1.**

**USEFUL ADVICE!**

Unless a Leak of the proper resistance is placed across the grid condenser the valve will either choke or the effect of the condenser be destroyed. The value depends on both the characteristics of the valve and the circuit, and can only be obtained through using the **"BRETWOOD" the only accurate variable grid leak** of watch-like precision and scientific design.

**PRICE 3/-**

The only Grid Leak with which it is possible to supply a reliable Chart giving 25 different readings covering from 100,000 ohms to 10 megohms. This Chart is supplied for use with the "Bretwood" Grid Leak only, at a cost of 1/3. Send yours to be calibrated and Chart supplied.

The "BRETWOOD" Valve Holder makes it impossible to short-circuit valve. It acts as its own jig and valve fits flush to panel. Valve legs are held yielding by ball bearing spring device, thus always assuring perfect contact. One screw fixing only. **PRICE 1/9.**

**RADIO IMPROVEMENTS LTD.**

95, Great Portland Street, W 1.



(Prov. Pat.)

Liberal Trade Discounts



**PORTABLE RECEIVER**

ALL B.B.C. STATIONS.  
 FULLY GUARANTEED.

**Complete for 6 Gns.**

Including Batteries and Headphones, One Valve Reflex and Crystal.  
 Extras: Royalties...18/6 Dull Emitter Valve...21/- or 30/-

**3-Valve Portable—Complete, 13 guineas.**

Marconi Royalty, £1 17s. 6d. B.B.C., £1.

**DEFERRED PAYMENTS ARRANGED.**

**Coil-Holders, "Maxone" Special Pattern**

New feature—interchangeable plugs, allowing coils to be reversed without altering connections. Made from best quality ebonite with ebonite anti-capacity handles. Nickelled fittings.


2-way...5/6 3-way...7/6 Single...1/6

**The Wonderful Scott-Taggart 3-Valve Dual**

Complete set of parts with full instructions for assembling. **£6 6 0**

Marconi Royalty .. £1 17s. 6d. extra.

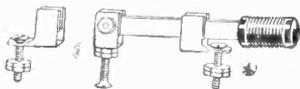Finished instrument in handsome cabinet, tested **£9 17 6** Extra: Royalty, Valves and Coils.



"Maxone" miniature nickel-plated switches, improved type, with drilling template—

S.P.D.T., complete, 1/6 each D.P.D.T., complete 2/- each

Very attractive terms to trade and factors. Send for full lists. A few areas open for Sole Agencies for "Maxone" Receivers.

**J. MACDONALD & CO.,** Sole Manufacturers of "MAXONE" Guaranteed Components.

2, HIGH STREET, CAMDEN TOWN, N.W.1.

'Phone: North 4386. 'Grams: Fraocha, Norwest, London.

**ECONOMIC ELECTRIC LTD.**




Size as illustration.  
 6d. each.



Plug and Socket Terminal, highly finished in Brass, with RED or BLACK INSULATED SLEEVES.

**DEAL WITH "EEC" IT PAYS!**

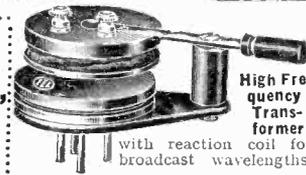

High Frequency Transformer with reaction coil for broadcast wavelengths. Price 10/-

R/26V



T56 Pin Terminal in brass. Size as illustration. 2d. ea. 1/6 doz.




T57 Spade Terminal in Brass. Size as illustration. 2d. ea. 1/6 doz.



R/45G  
**DOUBLE POLE, DOUBLE THROW KNIFE SWITCHES** for panel mounting, solid nickel arms and clips. 1 1/4 in. throw. Price 2/-

R/45H Do., solid copper, 1/6

**NEW 40 page RADIO LIST Post free 4d.**

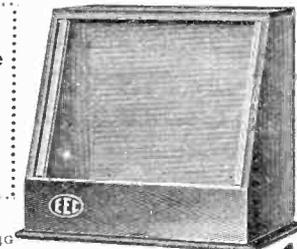

R/74G  
**POLISHED MAHOGANY CABINET.** 10 in. by 8 1/2 in. by 5 1/2 in. 10/9. 12 in. by 10 in. by 7 1/2 in. 12/9.

Head Office: 10, FITZROY SQUARE, LONDON, W.1.

Showrooms:

303, EUSTON RD., N.W.1.

Branch and Works:

TWICKENHAM.

**VALVES repaired Quick!**



Send your "burnt-out" valves to a proper valve manufacturers for repair. You will get them back same as new—and perfectly "hard," i.e., with thorough vacuum. We guarantee our repaired valves:

- (1) Not to consume more current;
- (2) To have same amplification;
- (3) To have same radiation.

If cap is broken new nickel-plated cap supplied FREE. If glass is broken—new glass supplied free, but in no case can new grids or plates be supplied.

Our files are packed with testimonials from users who regularly receive American Broadcasting on our repaired valves.

We cannot be equalled for good work, low price and QUICKNESS.

**RADIONS, LTD., Bollington, Nr. Macclesfield.**



G99D  
 TRADE  
 TERMS

We make the new Radion Low Consumption Valve, price 10s. Uses only a third of usual current. See our advert. elsewhere in this issue.

# The Use of Taps in Wireless Work

By R. W. HALLOWS, M.A., Staff Editor.

*Tapping ebonite and brass is often thought to be a difficult job. This article shows how simple the task can be made*

THE average constructor of home-made wireless apparatus soon attains a certain amount of dexterity in the use of quite a number of tools. He has not been long at the game before he learns to drill straight, to measure carefully, to mark out accurately and to file cleanly; but there is one tool at which for some reason or another he is apt to shy, regarding it apparently as something too advanced for him to tackle. This tool is the tap which is used for threading holes. It is the rarest thing to find any tapped holes at all made in the home-made set. Clearance holes are used everywhere for terminals, valve legs and so on. Now for these things the tapped hole is better, since it makes for a much firmer job. Further, if they are screwed into the panel it is not usually necessary to place nuts upon their shanks, which is a very great advantage in the case of valve legs in particular. If nuts are used upon the shanks of valve legs, they must necessarily come very close together on the underside of the panel with a consequent increase in capacity. A further point about tapping is that it very much simplifies the process of soldering on leads, for terminals and valve legs so treated have not nearly the same tendency



Fig. 2.—Second cut tap.

to loosen under the heat of the soldering iron.

Again there are many jobs of quite a simple kind which cannot be done unless tapping can be undertaken. You wish, for example, to make up a plug and socket coil holder. You drive the plug and socket into  $\frac{1}{4}$  in. holes in the ebonite, and to fix them in place it is necessary to insert screws from the edges as shown in Fig. 1. The holes for them must, of

course, be tapped. If you cannot use the tap you must needs purchase the coil holder, though it can be made at home for about a quarter of what you pay for them.

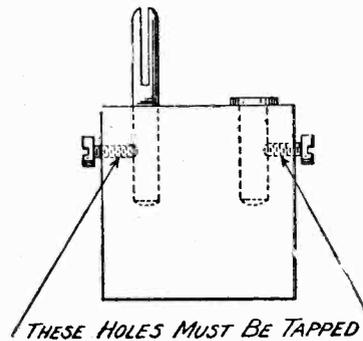


Fig. 1.—A simple job which cannot be done without tapping.

And there are very many other useful jobs which are outside the scope of the home workshop, unless screwed holes can be made.

Why constructors should be unwilling to tackle tapping I do not know, for in the case of ebonite especially, it is one of the easiest of workshop jobs. If you provide yourself with the right tools for the purpose, you will have absolutely no difficulty whatever in turning out thoroughly good work. Beginners at tapping do not know as a rule what kind of tap to buy. They go to the tool shop and ask simply for a 4 B.A. tap. "First, second or third cut?" asks the salesman promptly, and the beginner, not wanting to show a lack of knowledge, frequently makes a shot, selecting either a first or a third without in the least knowing what is the difference between them. In the case of very hard metals, screwed holes have to be made with two or three taps. The first, which is very finely tapered, and has hardly any thread at all upon it, is put through to clear the way for the second, which is tapered only at its point. The job is finished off with the third cut, or plug tap, which has no taper at all. First cut taps are not required for ebonite, which is a soft material,

and plug taps are needed only when we have to thread a hole which does not go right through the panel. As this can be done successfully only with material at least  $\frac{1}{16}$  in. thick, we shall not find much use for the plug or bottoming tap in wireless work. What we need is a second cut tap such as that shown in Fig. 2. Always buy taps of good make—the "saving" on those of inferior quality is only about a penny apiece for B.A. sizes, and with them good work is problematical. Do not be put off with long-shanked taps, for these are always liable to break if any strain is put upon them. The best type are those made by Card's, which in the B.A. sizes measure  $2\frac{1}{8}$  in. over all. The wireless constructor can confine himself entirely to the 4 B.A. tap, though it will be useful if he provides himself also with second cut taps for No. 2 and No. 6 B.A. To use these he will require a tap wrench, such as that shown in Fig. 3. He will also need drills for making holes of appropriate sizes. The tapping sizes laid down in the tables are No. 26 for 2 B.A., No. 34 for 4 B.A., and No. 43 for 6 B.A. These are, as a matter of fact, rather a tight fit and it is a distinct advantage to use drills of slightly larger gauge. One gets quite a full thread by doing so, and



Fig. 3.—A good and inexpensive type of tap wrench.

the tap is very much easier to start and to keep straight in the larger hole. I would recommend those who contemplate taking up tapping to use No. 23 drill for 2 B.A. and No. 32 for 4 B.A., and No. 42 for 6 B.A.

Do not start your activities by tapping upon the panel of the set under construction. Take a few odd pieces of ebonite from the scrap box and use them for practice until you have acquired the art of

keeping straight and putting on a good clean thread. In one of these pieces drill half-a-dozen holes with a No. 32 drill. Then place your 4 B.A. tap in the wrench, fixing it tightly, so that it will not be able to move. Put the point of the tap into one of the holes, see that it is upright and then give half a turn to the right, at the same time applying a certain amount of pressure—just how much pressure should be applied is a thing that one learns by practice. As soon as the tap has started to cut, lift the work up and look at the shank of the tap to see whether you are going straight. If you can start the tap straight it will keep

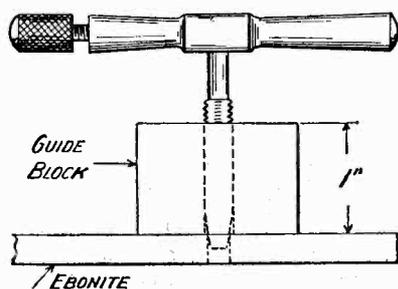


Fig. 4.—Method of using a guide block.

itself straight for the rest of its passage through the ebonite. If, as will probably be the case, you find it slopes a little in one direction, remove it and try again. After one or two attempts you will most likely find that you are getting the knack, and that you are now able to start the tap straight. There are, however, people who can never acquire the art of keeping taps straight. Should it happen that you are one of these, you had better use a guide block to help you. Fig. 4 shows how this is done. The guide block is simply a piece of oak or any hard wood about 1 in. in thickness, through which is drilled a hole just large enough to allow the tap to pass freely. The tap is inserted into it with its point protruding, and the point is pressed into the hole in the ebonite. You may now turn down the tap with a certain amount of confidence for the block will help it to start straight.

Once your tap is started, whether you are using a guide block or not, the rest of the process is easy. Put it through quite quickly by a series of full turns forward and quarter turns backward. Should it feel to be binding a little in the hole remove it and wipe off the ebonite dust with which it will be covered. Then continue as before. Taps will last longer if they are lubricated with a drop of turpentine

at each hole; ebonite, though soft material, has an extraordinary blunting effect upon steel tools unless a little lubrication of this kind is used. When you have succeeded in making half-a-dozen well-threaded holes in your odd piece of ebonite, you can then tackle a real constructional job, feeling pretty sure that you will not make a mess of it. If the instructions given are carried out anyone can learn to tap ebonite in half-an-hour.

As your skill in the use of taps grows, you will find that you can save a good deal of time over the work when numbers of tapped holes have to be made by discarding the wrench and placing the tap in the chuck of the breast drill. Do not begin by doing this, for you will not be successful until you have got the feel of things and know the right amount of pressure to apply. Once, however, you have reached this stage you will find that you can run your taps through as easily and as quickly as drills.

If the constructor's outfit is limited to the 4 B.A. tap alone, he will still be able to tackle the job of making screwed holes of other sizes, for quite satisfactory taps for ebonite work can be made at home with the greatest ease. They are a little more difficult to use perhaps than the correctly made bought tools, and one should not attempt to do so until one has had a little experience. Let us suppose that an occasion arises which calls for a 2 B.A. screwed hole and that you have no tap of this size. Cut off a piece of 2 B.A. studding about 2 in. long. Then with a file make a flat upon it, tapering off a little towards the end. Turn the studding over and make a second flat opposite the first. Then make two more at right angles to the first pair. The end of the studding will now be square and the thread will

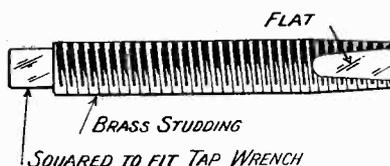


Fig. 5.—A makeshift tap made out of brass studding.

remain only at the corners. These are the cutting edges of the home-made tap. Square off the other end so that it will fit into the wrench, and your 2 B.A. tap is ready for use. Though they are intended for emergencies, brass taps of this kind give very good service, and they will last for quite a long

time if a little turpentine is used to lubricate them. They are extremely useful sometimes, as for example when you find that you have purchased a batch of B.A. screws which are not true to size—this does, unfortunately, happen sometimes as many of us know to our cost. With such screws the standard tap is either too large or too small, and the only thing to do is to convert one of them into a tap in the way described.

We may sum up the golden rules of tapping as follows:

- (1) Make all holes large enough to allow the tapered portion of a second cut tap to enter.
- (2) Start straight. Examine your work as soon as the tap has "bitten" to see that it is going straight.
- (3) Do not use too much force.
- (4) Do not turn it too quickly.
- (5) Lubricate with a little turpentine.
- (6) Do not tackle a big job until you have had some practice on some old scraps of ebonite.

### Results with the Trans-atlantic Receiver Abroad.

To the Editor of MODERN WIRELESS.

SIR,—I promised to let you know what results I got with your trans-atlantic set. I am using the set here and getting excellent results. I only use a single valve amplifier after it and am able to pick up twenty-three broadcasting stations; this I have done in two weeks.

KDKA comes in stronger than 2LO when I was in Edmonton. I will mention a few of the stations I receive, showing distances and location, and bar a little statics, every note of a piano and every word of speech is perfect:—WGAM, WGY, WQAM, WLW, WSAI, 6KW (Cuba), WKY, WCAD (New York). My reception on your set is far better than many of the big sets here costing as much as £150. My only trouble is static, and if you could give me any suggestion *re* this trouble, I shall be much obliged. I am only using a 100 ft. single aerial, about 25 ft. from earth and badly sheltered by trees.

Yours truly,  
ARTHUR VERLEY.

Kingston, Jamaica,  
B.W.I.

# What Beautiful Coils !


*So symmetrically wound !  
So superbly finished !*

*Yes ? but neither of these is the chief merit of*



## Honeycomb Duolateral Coils

(De Forest Patent No. 141344)

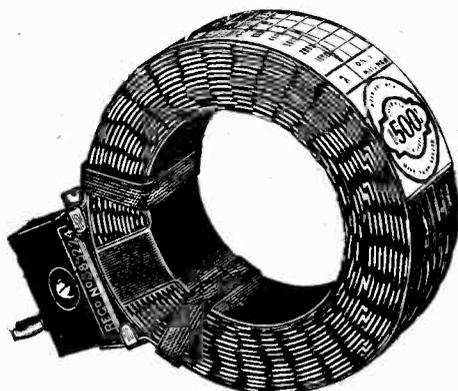

Plug Mounted Coil.



Gimbal Mounted Coil

The real cause of their overwhelming popularity is that they always perform their intended function perfectly. There is nothing haphazard about them no "rule of thumb."

**SCIENTIFICALLY DESIGNED, PRECISELY AND ACCURATELY WOUND, CRITICALLY TESTED.**

### Every coil is a certainty

... and the buyer always gets what he pays for. To enquirers for low priced coils some dealers will offer substitutes, but, even then, they generally say—"of course,

## If you want the best, buy "IGRANIC"

*and every dealer stocks them  
Write for Lists Z. 188.*

Manchester : 30, Cross Street.  
Birmingham : 73-4, Exchange Buildings, New Street.  
Glasgow : 50, Wellington Street.  
Cardiff : Western Mail Chambers.  
Bradford : 18, Woodview Terrace, Manningham.  
**149, Queen Victoria Street,  
LONDON.**



Newcastle : 90, Pilgrim Street.  
Concessionaire for France and Belgium :  
**L. MESSINESI,**  
125, Avenue des Champs, Elysees, PARIS.  
94, Chaussee d'Ixelles, BRUSSELS.

**Works :  
Elstow Road, BEDFORD.**



## Sweeter Music and POUNDS in POCKET

FROM the minute you fit Radion Valves your pleasure goes up and your expenses go down. Your accumulator lasts three times as long, for Radion Valves

Use only .25 amp. at 3.5 to 4 volts. Anode Volts 30 to 90.

On all normal plate voltages no grid bias is needed.

Two Types : A2 for amplifying. D4 for detecting.

Same price for each. Same filament and anode current also. If your dealer does not stock this efficient and economical valve, write direct to us and we will see that you are immediately supplied.

Sole Manufacturers :  
RADIONS, LTD., Bollington, Macclesfield.

### VALVE REPAIRS



(Most makes)

Valves repaired by us are guaranteed:—

- (1) Not to consume more current.
- (2) To have the same amplification.
- (3) To give the same radiation.

Ordinary Bright Emitter Types

Price 6/6 Post extra.

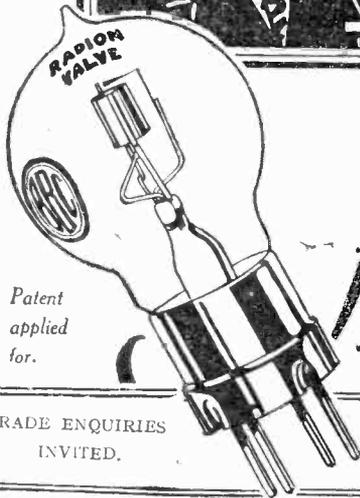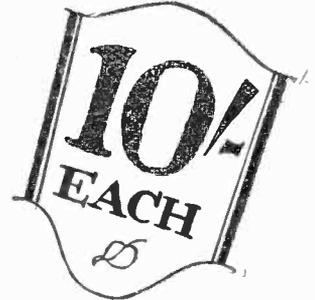


Patent applied for.

# fit the New RADION VALVES

LOW CONSUMPTION

TRADE ENQUIRIES INVITED.

— and amplify enjoyment! n & d.

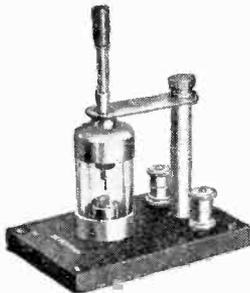

## CRYSTAL HOLDERS

A valuable feature of this crystal holder is that it can be easily taken to pieces and set up again. It is mounted on an ebonite base (3 in. by 2 in.), with glass which protects the crystal from dust.

Price 4/6 each.



## TESTING BUZZERS

Neat and compact. Mounted on ebonite base with terminals and shunt, or mounted with terminals, shunt and switch. Also supplied unmounted.

Price 3/6, 7/- & 8/- each.

MAKERS : The Silvertown Company, 106, Cannon Street, London, E.C. 4. Works : Silvertown, E. 16.

# Silvertown

WIRELESS ACCESSORIES

Quality guaranteed by over 50 years' electrical manufacturing experience.

# Further Notes on the 10-Valve Armstrong Supersonic Heterodyne

By KENNETH ALFORD.

*This article has been written to answer a large number of letters addressed to Mr. Alford concerning his previous contribution.*

A VERY considerable interest has been aroused in this instrument, judging from the voluminous correspondence I have received on the subject, and it appears that certain points of the design cause difficulty. It is, therefore, attempted in this addendum to clear up the more general queries raised.

It must be realised by all that an instrument such as the superheterodyne is not like the common

well in many cases, but to give a constructional description of this instrument "wire for wire" and "hole for hole" would fill at least one whole copy of MODERN WIRELESS. To proceed with the more general points raised: The first appears to be an abject horror of the enormous size of the instrument and the large number of valves used.

Now the superheterodyne can be investigated by anyone possess-

ing a long wave receiver may consist of 3-5 H.F. stages coupled in any conventional way. Resistance cap. or transformer having an optimum preferably between 4,000-8,000 metres.

### The Heterodyne Coils

It was stated in the article that the higher range heterodyne coils were wound "hankwise," a term which has caused some embarrassment. The method was to wind the necessary turns on a circular former to form a "bundle," which is removed from the former and taped or bound into a firm coil. There is no particular virtue in this method, and doubtless readers of MODERN WIRELESS may prefer to try some other method, but in any case the heterodyne coils should be connected to the oscillator valve and their range checked by wave-meter.

### Switching

The instrument is capable of conversion into a 2-, 3- or 4-valve instrument of conventional type, embodying 1 H.F. amplifier, and 1 or 2 note magnifiers. The connections are as shown in Fig. 2.

The operation is fairly obvious and shows the long wave side bridged and allowing the note magnifiers to be added to the short wave side.

The same arrangement may be adopted for cutting out the short wave receiver and using the long wave side only.

The small coil in series with the rectifier valve of the short wave side in the sketch of the technical

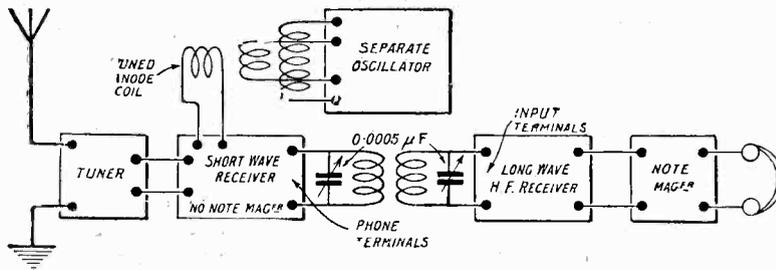


Fig. 1.—How existing sets can be arranged to make a supersonic receiver.

or garden 2-, 3- or 4-valve set, which can be put together with heavy odds on its working well on its first test. The manipulation of the superheterodyne is so essentially different that even although the instrument is perfectly in order, in the hands of some it is considered quite useless. It must, therefore, be clearly understood that in an instrument which represents the higher order of radio technique the operator must be prepared to use patience and endeavour to reason out his apparent difficulties.

In certain quarters the multiplicity of controls has raised comment, but in the design of the instrument practically every "variable" was provided with a variable control. To the uninitiated the advantage of this is obvious, and it must not be supposed that each and every control is brought into operation each time the instrument is used.

Simplicity of operation is all very

ing a good short wave and long wave receiver in separate cases by simply coupling these two instruments together by means of the "transfer coils," and arranging for a separate oscillator or heterodyne covering the required wavelengths to be coupled to the tuned anode circuit of the first H.F. valve on the short wave set. This may be illustrated by a simple diagram, Fig. 1.

Any telephone condenser on the short wave receiver must be removed and also any note magnifier which may be incorporated. The

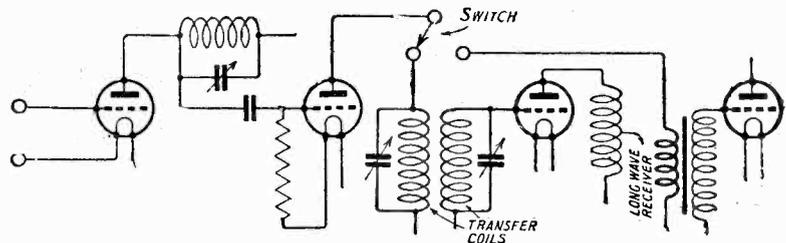


Fig. 2.—Details of switching.

arrangement was a "reaction" coil, which ought to have been labelled, although it is not necessary to use it when the instrument is operating as a superheterodyne. When the instrument is being used as a short wave receiver this reaction coil may be coupled to the tuned anode coil or closed circuit coil in the ordinary way to obtain regeneration.

With regard to the plugs and sockets used in connection with the small electrostatic - reaction condenser, it is necessary to change the position of the plug when the number of H.F. valves in the long wave side is changed. This is due to the fact that the sign of reaction changes, and if the wrong number of valves is bridged by the condenser there can be no regeneration, and the condition of oscillation cannot be reached.

Finally, to those whose ambition is to possess the most wonderful of radio receivers, I would suggest that the construction be undertaken in a painstaking and careful manner, and that the immediate successful operation of the receiver should not be altogether looked for, and that this should only serve as showing those factors which play the most important part in its efficiency.

The wiring should, if possible, be carried out with stiff wire, especially grid and anode wiring, which should be well spaced to avoid capacity effects. The universal adoption of "Spaghetti" or other forms of "hay wiring" is deprecated in the extreme.

It is of considerable assistance, if the short and long wave sides of the receiver are tested independently on signals before the super-sonic arrangements are brought into play. This will eliminate a great deal of uncertainty.

When the instrument is completed and tested on an aerial and found apparently satisfactory it should be connected to a "loop" aerial of dimensions to cover, say, the range of B B C stations, and, as stated in the former article, all these stations should come in at good strength.

The fact which will strike one extremely forcibly when the above achievement has been reached is the extraordinarily small difference in strength of signals received on the frame to the same signals on the outside aerial.

Through the courtesy of Messrs. Cunningham and Morrison, who represent the "Myers" valve in this country, I am replacing the present valves in the instrument

with high  $\mu$  Myers valves, which have a voltage or amplification factor of 20 against 6 or 8 of the ordinary R valve. The results should prove very interesting.

## The Four-valve Family Receiver

To the Editor of MODERN WIRELESS.

SIR,—In accordance with the desire expressed in your instructions, I have great pleasure in informing you that I have successfully constructed your four-valve family receiving set.

I have followed your instructions in every detail, and the results have been magnificent, having had the majority of British broadcasting stations on a loud-speaker.

I am using three "Cossor" valves and a "Marconi" as a detector.

Thanking you, I remain, yours faithfully,

RAYMOND TODD.  
West Hartlepool.

Please your home  
with the Tone

Now is the call of the open; the river, the garden and the picnic, with all their attendant pleasures. But what of Broadcast Music's merry accompaniment? And remember summer conditions compel you to employ apparatus of proven pre-eminence. For instance, truthful reproduction limits your choice of a loud-speaker to the—

**BARNES**  
**MINORPHONE**  
MODEL NO 2

The BARNES is the remarkable reward of patient and scientific research. Mark the volume, purity and richness of tone, free from all inherent resonance

The BARNES MINORPHONE No. 2 merits your distinction—and your ultimate choice—by virtue of its reasonable price. It is an instrument with a strong, distortionless output obtainable at the minimum expense.

Price £2 5s.

Arrange a demonstration at your dealer's. If he cannot supply write us, when we will direct you to the nearest selling agent.

The BARNES MODELS may be seen on Stand V. 907 Palace of Industries, Wembley.

**L. B. TICKLE & CO.**  
61, Borough Road, London, S.E.1  
'Phone: Hop 6880-1. 'Grams: Elveditch, Selist.



For large rooms and all that Summer Radio demands, its power is equally as noteworthy as its acoustic properties—ample for universal use.

Of robust construction with large adjustable diaphragm and detachable horn dull black in finish. The well-designed base is also dull black with polished aluminium top. Resistance 2,000 ohms.

The



## ANODE CONVERTER

BANISHES one of the most troublesome components of the set, namely, the High Tension Battery.

It is worked from the ordinary 6 volt accumulator used for your filaments at a consumption of only 1.15 amperes.

The M-L Anode Converter completely smooths out the ripple that is so noticeable with direct current machines, and the current supply is as perfectly continuous as that from a battery.


"AMATEUR WIRELESS" says:—"... one of the most remarkable appliances yet brought out for the benefit of the amateur Wireless enthusiast." The machine is supplied for the following standard voltage ranges, but special machines can be made to order.

Type A 6-70 volts. For general reception.

Type B 6-120 volts } For two stage power amplification.

Type C 12-300 volts }

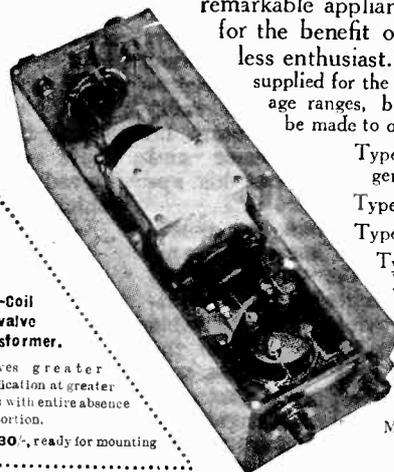Type D 12-500 volts. For low power transmission.



The

M-L  
Twin-Coil  
Intervalve  
Transformer.

Gives greater amplification at greater ranges with entire absence of distortion.


Price 30/-, ready for mounting

Write to-day for full particulars.

The  
M-L Magneto Synd. Ltd.,  
Wireless Department,  
COVENTRY.



# RAYMOND VARIABLE CONDENSERS

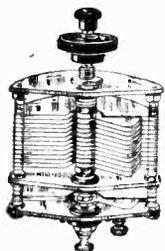

## OUR NEW MODEL CONDENSER

•0005.

WITH VERNIER AT BOTTOM.

COMPLETE WITH DIAL AND TWO KNOBS


6/11 Post 3d. each.

**SUPER CONDENSER**  
WITH THREE PLATE VERNIER "IT" FOR VERY FINE TUNING. Note Important Feature. Vernier regulated from side of dial.  
Reg. Post 6d. set.



.001 .. 12/8  
.0005 .. 10/6  
.0003 .. 8/6

## DUPLEX CONDENSERS

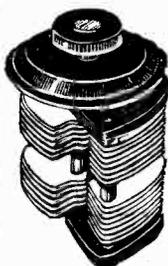

This Condenser is composed of two equal units, of .0005 mfd. operated by one Knob and Dial, thereby enabling you to tune two circuits by one turn of the dial. Can be used in series or parallel. Complete, as shown with aluminium end. Knob and dial.

For Tuned Anode Circuits.

10/-

Post 6d.

Our Air Dielectric Condensers are the simplest and MOST efficient on the market. Lowest in price, Highest in quality. Made for panel mounting and are the most suitable condensers for Broadcasting or Amateur work.

ACCURATE CONSTANT CAPACITY.

RIGID CONSTRUCTION THROUGHOUT.

ELECTRICALLY AND MECHANICALLY PERFECT.

NARROWEST POSSIBLE SPACING AND ALUMINIUM END PLATES.

NEW MODEL, .073 in SPACERS.

POST 3d. Set. 3 sets post free.

Capacity.	Plates.	Price.	Height without connections.
.001	49	6/11	3 1/8"
.00075	37	5/11	2 5/8"
.0005	25	4/11	2"
.0003	15	4/6	1 3/8"
.0002	11	4/-	1 1/2"
.0001	5	3/6	1"
.00005 (Vernier)		2/6	

Prices DO NOT include Dial. This is 9d. extra with Condenser.

Trade dis. on Condensers 20 p.c. plus Postage. Good terms for quantities.



POST 3d. Set. 3 sets post free.


Owing to the thousands of testimonials received for our New Model Variable Condenser we are discontinuing "A" type and selling New Model only.

Specially Recommended by Modern Wireless and Wireless Weekly.

**BUY RAYMOND GOODS.**
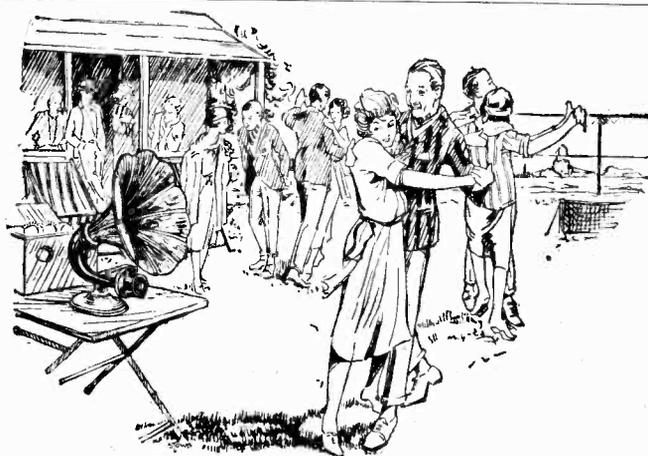
## National Laboratory Certificate

Above new model specially adapted for taking up min. amount of space. All parts nickelled. PASSED NATIONAL LABORATORY TEST. One hole fixing.



## Summer Radio

A most entertaining and enlightening Season is offered by Radio Broadcast this summer, but whether in the Home or Garden, at the Country Club or elsewhere, the pleasures of listening-in are only to be fully enjoyed by associating an AMPLION with the Receiving Set.

The AMPLION, recognised as the World's Standard Wireless Loud Speaker, reproduces Speech as well as Vocal and Instrumental Music in full volume with extreme clarity, and in a delightfully Natural Tone.

# AMPLION LOUD SPEAKERS


afford "Better Radio Reproduction."

Prices range from £2 2s. and all models are obtainable from Wireless Dealers of repute. The leading producers of Radio Apparatus standardise the Amplion.

Write for Illustrated Folder W.H.

**ALFRED GRAHAM & COMPANY**  
(E. A. GRAHAM)

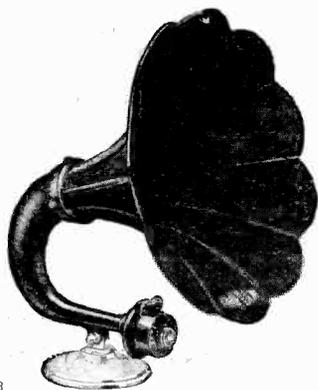ST. ANDREW'S WORKS, CROFTON PARK, LONDON, S.E.4  
Phone: Sydenham 2820-1-2. Grams: 'Navalhada, Catgreen, London.'  
West End Showrooms: 25-28, SAVILE ROW, W.1.  
Suburban Showrooms and Service Station: 82, High St., Clapham, S.W.4.



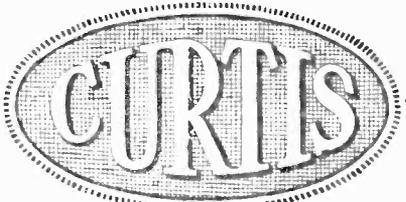
## Visit the BRITISH EMPIRE EXHIBITION

and inspect the full range of GRAHAM PRODUCTS

The GRAHAM Stand is AVENUE 11, BAYS 11-13, PALACE OF ENGINEERING





# RADIO INSTRUMENTS.

Exclusive in Design, Construction,  
and in

**QUALITY of REPRODUCTION.**

PRICES RANGE FROM 20—200 GUINEAS

N.B.—We are open to appoint exclusive Territorial Agents for the distribution of Curtis Radio Instruments on attractive terms, to those in a position to handle instruments of the highest quality.

For Terms and Particulars apply—

Avenue 14. Bay 12.

The Palace of Engineering.  
The British Empire Exhibition

## WEMBLEY.

Which affords a unique opportunity of viewing a most complete and comprehensive range of wireless exhibits of quality and distinction.

There is  
**50 YEARS' EXPERIENCE**  
and the most perfect manufacturing conditions behind the

**CURTIS - SILVERTOWN  
INTERVALVE TRANSFORMER**  
INCOMPARABLE for POWER and PURITY.

PRICE 21/- EACH.

Used exclusively in all Curtis Radio Instruments.

## The "NU-GRAVING" PROCESS

of PANEL MARKING. Neater, cleaner, cheaper than any other known method.

Series 1. 63 words and letterings for wireless. 7 1/2 D. each.  
Series 2. 1/4-circle 0-180; 1/2 circle 0-10; Full-circle 0-100 and 4 valve templates. Postage 1 1/2 d. extra.

Write NOW for our revised list of 16 illustrated pages of Curtis and Paragon accessories and components of quality. It will interest you.

## BIRMINGHAM

A full and complete range of all accessories components and complete instruments NOW AVAILABLE AT OUR NEW BRANCH.

76, NEWHALL STREET, BIRMINGHAM.  
Telephone: Central 5444.

Continuous daily demonstrations.


Also at 312, DEANSGATE, MANCHESTER.  
Telephone: Central 5095.

## PETER CURTIS, LTD.,

34-36, Whitfield Street, London, W.1.


Telegrams: "Paracurtext." Telephone: Museum 8489.

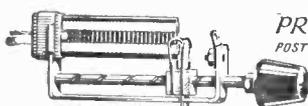In Conjunction with  
The PARAGON Rubber Manufacturing Co., Ltd.



PRICE POST FREE 5/6

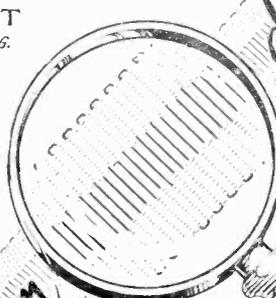**ELLA "ANYVALV" RHEOSTAT**  
FOR PANEL MOUNTING.  
To control the filament voltage of 1 "R" valve; 1 or 2 dull-emitter valves—1, 2, 3 or 4 low consumption valves.



**ELLA "DULVALV" RHEOSTAT**  
FOR PANEL MOUNTING.  
To control the filament voltage of dull-emitter valves.

PRICE POST FREE 3/6

**LIONEL ROBINSON & Co.**  
TRADE ENQUIRIES INVITED. 3, STAPLE INN LONDON, W.C.1.

*The Ribbon does it!*

## ACCUMULATORS GUARANTEED

Direct from Maker to User. Thousands in use.

PRICE.					
2 volt 40 ..	10/-	4 volt 20 ..	12/6	6 volt 20 ..	18/3
2 " 60 ..	12/6	4 " 40 ..	17/3	6 " 40 ..	24/8
2 " 80 ..	15/-	4 " 60 ..	22/3	6 " 60 ..	32/-
2 " 100 ..	18/-	4 " 80 ..	27/-	6 " 80 ..	38/6
		4 " 100 ..	32/6	6 " 100 ..	45/8

Post and Packing 1/- each.

## ADAMS BROS. (Longton), Ltd.

(Members of B.B.C.)  
Sutherland Road, Longton, Staffs


**BWARE OF WORTHLESS IMITATIONS, SEE THE TRADE MARK *Watmel* ON EVERY GRID LEAK.**

## WATMEL VARIABLE GRID LEAK

(Patent No. 206098).

Continuously Variable. Silent in operation. Constant in any temperature. Dust and Damp proof. Each tested and guaranteed. Neat and well made.

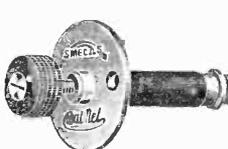GRID LEAK .5 to 5 megohms 2/6.  
ANODE RESISTANCE 50,000 to 100,000 ohms 3/6.  
Suitable any Circuit.



SEND P.C. FOR DESCRIPTIVE FOLDER.

**WATMEL WIRELESS CO.,** Connaught House, 1a, Edgware Road, Marble Arch, W.2. Tel. 4575 Paddington.

Another point to notice is that, the detector having a different impedance at different adjustments will alter the tuning of the circuit  $L_4 C_5$ , principally by altering the unintentional reaction introduced into the circuit  $L_4 C_5$ . Any variation of reaction, whether intentional or otherwise, should always be accompanied by retuning of associated circuits, and, consequently, it is desirable, when operating the Fig. 11 circuit, to retune the condensers  $C_1$ ,  $C_2$  and  $C_5$  after adjusting the crystal detector.

It will be noticed that a condenser  $C_4$  is shown in dotted lines across the primary of the step-up intervalve transformer  $T_1 T_2$ . The writer's experience indicates that this condenser may always be left out without any loss in signal strength, owing to the self-capacity of the primary  $T_1$ . If a condenser

secondary winding  $T_2$ , and for general purposes the writer would recommend a condenser of  $0.001 \mu F$ . A grid battery could be inserted in the point X in the Fig. 11 circuit for the purpose of giving the grid a negative bias.

A few additional connections may be tried by the experimenter. It is usually desirable, in all cases, where a loose-coupled input high-frequency transformer is used, such as  $L_1 L_2$ , to connect the negative terminal of the accumulator to earth.

Another arrangement worth trying when a transformer  $L_3 L_4$  is used in the output circuit of the valve, is to connect one side of the primary  $T_1$  to the negative terminal of the filament accumulator; adhering to the note regarding the I and O terminals of primary and secondary, the right-hand side of  $T_1$  may be connected to the

grid circuit having no effect on the operation of the circuit. As a matter of fact, it is rather a good test to see whether signals may be heard with the crystal off in order to ensure that the valve is functioning properly as a low-frequency amplifier. If good signals are heard in the telephones it is an indication that the valve  $V_1$  is acting as a detector, and will consequently probably distort the low-frequency currents which are fed into its grid circuit by means of the transformer  $T_1 T_2$ . The rectification effect may be eliminated, or practically eliminated, by giving the anode a suitably high anode voltage and giving the grid a negative potential to bring the operating point about the half-way point along the characteristic curve. Under these conditions signals will not be received in the telephones T when the crystal D is raised, or if there are signals, they will be very weak. If, however, no grid battery is connected in the grid circuit signals will usually be stronger, indicating that distortion will occur on the low-frequency side.

Sometimes the signals obtained by raising the contact from the crystal in dual circuits are as loud, or sometimes even louder, than when the crystal is employed, and this is a sure indication that something is wrong with the circuit. One of the probabilities is that an inferior crystal detector is employed.

In the Fig. 11 circuit, the raising of the crystal by relieving the circuit  $L_4 C_5$  of a considerable amount of damping, may result in more capacity reaction in the valve, and this reaction will strengthen the oscillations in the circuit  $L_3 C_2$ . The result is that the valve  $V_1$  is now acting as a detector with reaction, and the results may be quite good compared to the normal arrangement of Fig. 11 with the contact on the crystal, the reaction effect being probably very small. This brings us to the question of how we may improve the signal strength of a circuit of the Fig. 11 type by means of reaction.

#### Adding Reaction to a Dual Receiver.

The desire for obtaining the maximum output from a minimum number of valves will prompt every experimenter to try and obtain better results by the application of reaction to his reflex receiver. The application of reaction to a reflex receiver introduces innumerable problems which require solution and the application of reaction is usually accompanied by the setting up of loud buzzing noises of audible frequency which are

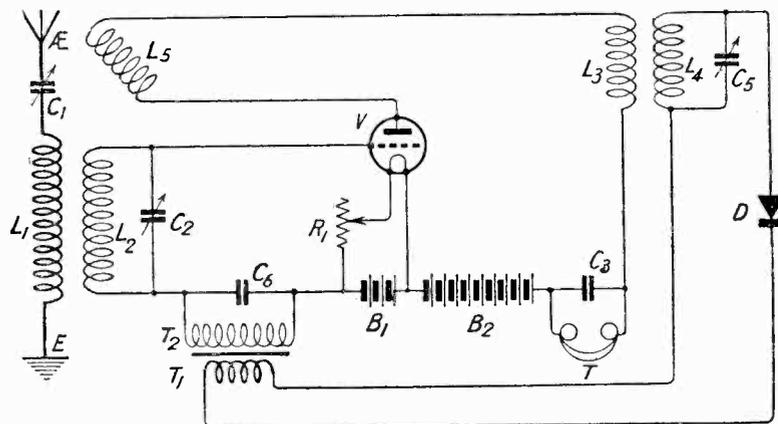


Fig. 12.—A similar circuit with reaction introduced.

is used, its value should not exceed  $0.002 \mu F$ .

As regards the connections to the primary and secondary, it is desirable that the left-hand side of  $T_2$  should be the O.S. terminal, and the right-hand side the I.S. terminal. As regards the primary, the connections are not so important as the experimenter will usually care to try reversing the connections. If a rule is desired, it might be suggested that the right-hand side of  $T_1$  should be the O.P. terminal, while the left-hand side, which is connected to one side of the crystal detector D, is the I.P.

As regards the fixed condenser  $C_4$  across the secondary  $T_2$ , the value of this condenser may be quite low, say,  $0.0003 \mu F$ , and in any case should not be greater than  $0.002 \mu F$ . Even when a  $0.002 \mu F$  condenser is used, there is a certain reduction in the low-frequency potentials established across the

negative terminal of the accumulator  $B_1$ .

#### Signals with the Crystal Off

Many experimenters will have found that when the catwhisker, or upper crystal, is removed from the lower crystal, signals very frequently come in quite well, and this may prompt some to imagine that dual amplification is not effective. What really is happening, of course, is that the valve is acting purely and simply as a detector. It is, in fact, almost impossible to prevent a valve acting as a detector, whatever the conditions may be under which it is operating.

In Fig. 11 the telephones T are included directly in the anode circuit of the valve, and consequently, if there is any rectification, signals will be heard in the telephones. There will, however, be no dual amplification effect whatsoever, the secondary  $T_2$  in the

extremely unpleasant to the operator of the set. Ordinary reaction may cause self-oscillation of an ordinary receiver, but this generally troubles the receiving operator very little; on the other hand, those who have sets in the neighbourhood have very good cause to complain owing to the heterodyning of the radiated oscillations with the incoming signals. The average user of a reflex circuit, however, finds that on tightening the reaction his own set produces an extremely unpleasant noise, and he consequently has to make an immediate adjustment to prevent it. He is, therefore, generally far less troublesome to his neighbours than he who employs an ordinary straight circuit.

Fig. 12 shows a reaction reflex circuit which only differs from Fig. 11 in that a reaction coil  $L_5$  is coupled to the inductance  $L_2$ . The coil  $L_5$  is connected in series with the primary  $L_3$  of the transformer  $L_3 L_1$ . The warning that should be given here is that if the reaction coil  $L_5$  is made of a certain size, the natural wavelength of the anode circuit, due to the inductances  $L_5$  and  $L_3$  in series and the capacity between filament and anode and the self-capacity of the two coils, is near to the wavelength being

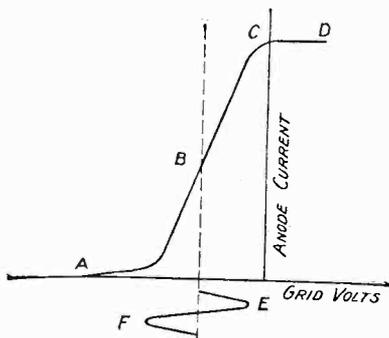


Fig. 13.—Characteristic curve of valve adjusted for reflex amplification.

received, and the valve will oscillate too readily. It is therefore desirable that the coil  $L_5$  should be kept as small as possible, and since a separate aerial circuit is employed a small reaction coil is all that should be necessary owing to the natural damping of the circuit  $L_2 C_2$ . The reaction coil  $L_5$  should, of course, be connected the right way round.

The circuit is not recommended as a particularly good one to start with, but most of the troubles experienced with reflex circuits are absent in a simple arrangement such as shown in Fig. 11 and Fig. 12.

Fig. 11, particularly, is calculated to avoid any tendency towards the low-frequency buzzing which is so prevalent in reflex circuits generally. In Fig. 11 we are more likely to get the buzzing because reaction is employed, and it will usually be

portion of its straight part is used. In this case the high-frequency currents are amplified by the valve without any distortion or rectification, assuming, of course, that a negative potential is applied to the grid to prevent the establishment of

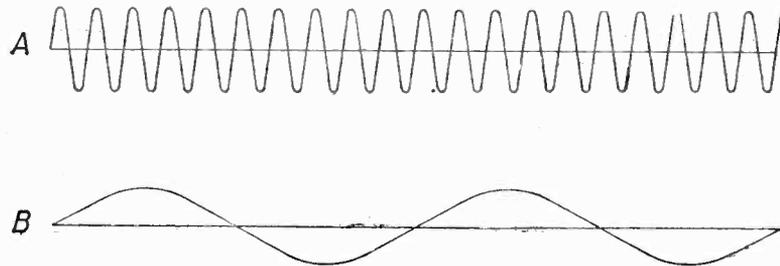


Fig. 14.—The high and low-frequency currents separated out.

found that as the reaction is increased a certain point is reached when buzzing takes place. This buzzing is due to low-frequency reaction, amplified low-frequency currents produced in the output circuit of the valve being conveyed back to the input side, the degree of low-frequency reaction being sufficiently great to cause low-frequency oscillation. If the low-frequency reaction is not sufficiently great to produce low-frequency oscillation, a big build up of signal strength is often obtained, but nearly always at the sacrifice of purity of reproduction.

All reflex circuits tend to oscillate, whatever precautions may be taken. The reason is that, although no low-frequency reaction is produced through the low-frequency output currents of the valve being directly coupled to the input circuit of the valve, there is, in between, a stage of high-frequency amplification, the high-frequency oscillations being modulated by the low-frequency input currents.

We may consider this matter best by considering that the valve in Fig. 12 was oscillating and producing high-frequency oscillations of a frequency determined by the values in the circuit  $L_2 C_2$ . If, when the valve is oscillating we feed low-frequency currents into the grid circuit by means of the transformer  $T_1 T_2$ , we will vary the grid potential at low-frequency, and these variations of grid potential are liable to vary the amplitude of the high-frequency oscillations generated by the valve. This, in fact, is a common method of modulating the high-frequency oscillations of a valve for telephony transmission; but certain conditions are necessary. The modulation effect is not present if the characteristic curve of the valve is absolutely straight, and only a small

grid current. If, however, the representative point on the characteristic curve, *i.e.*, the point representing general conditions at any given moment, moves along a curved portion of the characteristic curve, modulation will occur. For example, if the whole of the characteristic curve is being traversed up and down due to the oscillating of a valve, and we apply a positive potential to the grid, it will be fairly obvious that the tops of the high-frequency current half-cycles will be clipped and distorted. Owing to the valve becoming saturated, the positive half-cycles will not be fully developed because the base line potential for the high-frequency oscillations has been raised by the application of a positive potential to the grid. If a negative effect may be obtained at the bottom bend of the anode current characteristic curve.

Fig. 13 shows a characteristic curve of a valve adjusted correctly for reflex amplification. It will be seen that the anode current curve, A B C D lies to the left of the ordinate passing through zero grid volts; this means that no grid currents will be established. A complete cycle of oscillating current is shown varying the grid potential above and below an average value which results in the middle point of the anode current curve being employed. If a low-frequency potential is now applied to the grid, either in a positive or negative direction, high-frequency currents will travel beyond the bends, and the high-frequency currents will consequently be modulated.

This is probably best explained by Fig. 14. The top line A shows the high-frequency currents generated by the valve, and the line B shows a low-frequency alternating current which is applied to the grid.

Fig. 15 shows, on the top line C,

# Sparta LOUD SPEAKER

*I wonder what's  
inside the base?*

You might well ask that question when you hear the clear, full richness of "Sparta" reproduction. Actually inside the base of type "B," in addition to the perfectly-designed magnets and diaphragm, there is an ingenious arrangement of blocking condensers which has the effect of "smoothing away" all trace of harshness, resulting in remarkably pure distinctness of tone. A visit to a demonstration will quickly convince you that for all classes of vocal, instrumental and orchestral entertainment nothing equals the "Sparta"—the Speaker of combined excellence.

Type "A" 120 ohms .. £4 : 15 : 0  
 Type "H.A." 2,000 ohms .. £4 : 15 : 0  
 Type "H.H.A." 4,000 ohms .. £4 : 15 : 0  
 Type "B" 120 ohms. The first Loud Speaker to provide for additional control through a 6-position tone selector  
 £5 : 15 : 0


Write to-day for List No. 315a, fully describing the complete "Fuller" range.

**FULLER'S UNITED ELECTRIC WORKS, Ltd.**  
 Woodland Works, Chadwell Heath, Essex.

Telephone :  
 11ford 1200 (6 lines).

Telegrams :  
 "Fuller, Chadwell Heath."

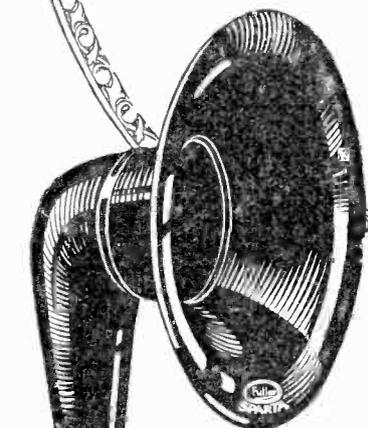London  
 Depot :  
 58, High St.,  
 W.C.2.



Demonstrations of the "Sparta" Loud Speaker are given during broadcasting hours at Gamage's, Harrods, Selfridges, The Service Trading Co., 289-292, High Holborn; City Accumulator Co., Ltd., 79, Mark Lane, E.C.; G. Salmon, 33, Grafton St., Tottenham Court Road; Peto-Scott, Ltd., 64 & 99, High Holborn; Messrs. Piggott Bros., Bishops-gate, E.C.; and at our own depots.

Perfect reproduction of the excellent d nce music regularly broadcast demands a perfect Loud Speaker—the "SPARTA."



**Buy British Goods Only.**

## A Valve for Every Wireless Circuit



### HALT! who goes there

UNPLEASANT reality is mostly forced upon us unexpectedly. Strange how easily we drift . . . an opinion here and a word there mark out our varied paths through life till "HALT!" comes—mostly the HALT OF EXPERIENCE.

Thousands of us have drifted into wireless more or less interested but indifferent to our choice of the components of that wonderful pleasure till the halt of experience has pulled us up sharply. Valves are worthy of choice. There is no unpleasant "HALT" for those who stipulate MULLARD Valves.

The pass word to wireless success—the Master Word is

# Mullard

**THE · MASTER · VALVE**


Advertisement of The Mullard Radio Valve Co., Ltd. (M.W.),  
 Nightingale Works, Nightingale Lane, Balham, S.W. 12.

The British Empire Exhibition, Palace of  
 Engineering, Avenue 14, Bay 13.

In replying to advertisers, use COUPON on last page
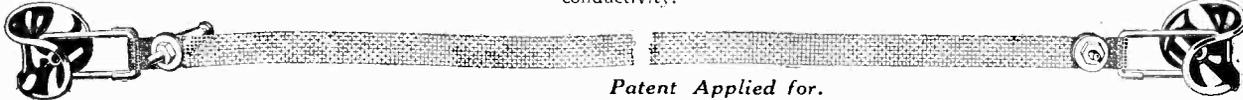
# MAGNIPLEX "REMEMBER" A GOOD AERIAL AND A GOOD EARTH MEAN MAXIMUM EFFICIENCY FROM YOUR SET.

The Range, Strength and Clearness are increased up to 40% by installing a MAGNIPLEX AERIAL as tested by experts. This applies to both Valve and Crystal Sets, either in or out of doors. MAGNIPLEX is made of Special Woven Wire Gauze of high tensile strength and conductivity.



Patent Applied for.

Our claim is backed by a guarantee that we refund your cash if results are not better than your present Aerial, and more than justify the extra cost of the MAGNIPLEX. Any user of MAGNIPLEX will give you a testimonial.

If your dealer does not stock them, send direct to us.

Prices:— $\frac{3}{4}$  in. wide 3d. per ft.;  $\frac{1}{2}$  in. wide 2d. per ft. Supplied in lengths of 50, 75 and 100 feet, including fittings, viz.—End Terminal for Down Lead and Insulators ready for erecting. For lengths under 50 ft. fittings charged 1s. 3d. extra. Postage and packing 1s. extra.

**HELIXO LTD.,** HENRY BUILDINGS,  
GRESSE STREET,  
RATHBONE PLACE, LONDON, W.1.  
Phone: Museum 6039.

## A REVOLUTION IN H.T. EFFICIENCY

H. T. Batteries made up of units are recognised as the ideal. The HOVIMO screw connection solves the problem of joining units without soldering.



The HOVIMO assures perfect "silent" working—is everlasting—allows easy replacement of units—will take the ordinary wander plug—makes it possible to keep your H.T. at an equal voltage. Is British made.

**H. MOLBACK**  
27, Cannon St.,  
E.C.4  
Tele: City 8299.

Ask your dealer for them.


1/6

Per Doz.  
From dealers or direct from me


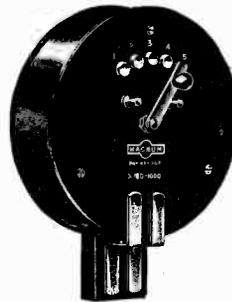
## MAGNUM TAPPED COILS IMPROVED TYPE NOW AVAILABLE.

At the request of many thousands of satisfied users of these wonderful Coils we have simplified the marking of the studs and increased the wavelength range of the Two Coils as follows:—



No. 1 COIL.	
Stud No. 1 equivalent to No. 25 Coil.	
" 2 " " " 35 "	
" 3 " " " 50 "	
" 4 " " " 75 "	
Price 12/6.	Replaces 4 ordinary Coils.

No. 2 COIL.	
Stud No. 1 equivalent to No. 100 Coil.	
" 2 " " " 150 "	
" 3 " " " 200 "	
" 4 " " " 250 "	
Price 15/-.	Replaces 4 ordinary Coils.


Construct your own set and spend the difference. For an outlay of a few pounds you can build a set equal in all respects to a bought set costing several times the amount, to say nothing of the valuable experience and joy of "making it all yourself." We supply all components recommended for every set described in this issue and past issues of MODERN WIRELESS and "Wireless Weekly," including the H.F.S.T.100 and 2-Valve H.T.'less Set. Buy a Radio Press Envelope and build one of the following simply-constructed Sets.

Radio Press Envelope, No. 1	S.T. 100..	1/6	post 2d.
" " " No. 2	Family 4-Valve	2/6	" 2d.
" " " No. 3	Simplicity 3-Valve	2/6	" 3d.
" " " No. 4	All Concert de Luxe	2/6	" 3d.
Magnum Improved 2 Coil Holder	..	each	9/6 "
Magnum Improved 3 Coil Holder	..	..	12/6 "
Magnum Choke for S.T. 100 Star	..	..	7/6 "
Omni Connecting Links, per set of 50	..	..	8/0 "
Magnum H.F. Transformers (matched) from	..	..	4/6 "
4 Electrode R Valve for H.T.'less Circuits	..	..	17/6 "
Myers' Valves, practically unbreakable	..	..	12/6 "
Recommended components for constructing the TRANSATLANTIC V., as described by Mr. Percy W. Harris:		£ s. d.	
Polished Mahogany Sloping Cabinet, with sliding back	..	..	1 10 0
Ebonite Panel, squared and matted, 22 ins. by 11 ins. by $\frac{1}{2}$ in.	..	..	0 15 0
Do. Do. Do. Do. drilled and engraved	..	..	1 4 0
Burndep Dual Rheostats	..	..	0 7 6
Dual Condenser, Square Law, .0002 complete	..	..	1 7 0
Variable Condenser, .. .0005, with Vernier	..	..	1 0 0
Valve Sockets, complete and lacquered	..	..	0 0 1
Igranic Potentiometer	..	..	0 7 0
Fixed Condenser, 2 mfd.	..	..	0 6 0
" " " 1 " "	..	..	0 4 0
" " " .25 " "	..	..	0 3 6
" " " .0003 " "	..	..	0 1 3
Leakand Clips, 2 Meg.	..	..	0 1 2
4-Pol Change-Over Utility Switch	..	..	0 6 0
Dubiler Resistance, 80,000 ohms	..	..	0 5 6
Terminals, complete and lacquered	..	..	0 0 2
Miniature Tumbler Switch	..	..	0 2 3
Magnum 2-Coil Holder	..	..	0 9 6
Magnum Concert Coils, per set of 4	..	..	1 5 0
Hot Pad Transfers, per set	..	..	0 0 6
No. 16 Sq. Section Tinned Copper Wire, per yard	..	..	0 0 1 $\frac{1}{2}$

Carriage paid on Retail Orders value £2 or over. Always Specify Magnum. Send stamp for illustrated list and set of leaflets dealing with K.P. Circuits.

**BURNE-JONES & Company, Limited.** Experimental Stations—  
2 FP New Cross.  
2 PB Kennington.  
2 CT Lambeth.  
6 CW Streatham.  
Manufacturing Radio Engineers,  
MONTFORD PLACE, KENNINGTON, LONDON, S.E.11.  
Phone: Hop 6257.

## S.A.C. DETECTOR "THE FIRESIDE PLUG"

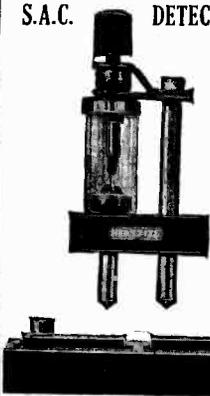

Listen in Luxury. Don't leave your comfortable chair or bed. COSTS ONLY 3/- ASK FOR NEW LIST, or send P.O. 1/- for New Electrical Game and List. Credited against first purchase. All Types of Headphones and Transformers Wound.

Panels Drilled and Engraved. Prompt Delivery. "S. A. CUTTERS," 15, Red Lion Sq. CHANCERY 8042. LONDON, W.C.1

**FOR SECURING YOUR AERIALS**  
And a thousand purposes where great strength and strain is needed. FLEXIBLE STEEL WIRE ROPE, Aeroplane Cable made to Govt. specification to specified breaking strains. PRICES BELOW COST. Orders of 10/- and over carriage paid, otherwise, please add 1/- for postage.

No.	Dia.	Strain, 100 ft.	No.	Dia.	Strain, 100 ft.
0	1/16	5 cwt.	12	7/32	45 cwt.
1	1/8	20 cwt.	13	1/4	70 cwt.
2	3/16	40 cwt.	14	5/16	110 cwt.
3	1/4	60 cwt.	15	3/8	150 cwt.
4	5/16	80 cwt.	16	1/2	200 cwt.
5	3/8	100 cwt.	17	5/8	250 cwt.
6	7/16	120 cwt.	18	3/4	300 cwt.
7	1/2	140 cwt.	19	7/8	350 cwt.
8	5/8	160 cwt.	20	1	400 cwt.
9	3/4	180 cwt.	21	1 1/8	450 cwt.
10	7/8	200 cwt.	22	1 1/4	500 cwt.
11	1	220 cwt.	23	1 1/2	550 cwt.
12	1 1/8	240 cwt.	24	1 3/8	600 cwt.
13	1 1/4	260 cwt.	25	1 1/2	650 cwt.
14	1 3/8	280 cwt.	26	1 5/8	700 cwt.
15	1 1/2	300 cwt.	27	1 3/4	750 cwt.
16	1 5/8	320 cwt.	28	1 7/8	800 cwt.
17	1 3/4	340 cwt.	29	1 7/8	850 cwt.
18	1 7/8	360 cwt.	30	2	900 cwt.
19	1 7/8	380 cwt.	31	2 1/8	950 cwt.
20	2	400 cwt.	32	2 1/4	1000 cwt.

Strainers for use with above, right and left-hand threads. 9d. each or 8/6 per doz.  
**SMITH & ELLIS, Ltd.** (Dept. 85), 11, Little Britain, E.C.1. Tel. City 8994.

**YES, WE MAIL CABINETS!**  
And you receive them by return. Solid Mahogany and Hand Finished. S.T. 100 3-VALVE CRYSTAL, 25/-  
OMNI, 25/-; 3-VALVE DUAL, 25/-; ST PORTABLE, 32/6; W2 & W3, 16 by 9 Panel, 17/6; ST 100, enclosed, 27/6; ST 100, standard, 15/6; 4-Valve FAMILY and Panel, 18/6; W1, 12 by 8 Panel, 16/-; ALL CONCERT and Panel, 18/-; ST 100 16/-.  
All Types of Cabinets kept in Stock. Special Cabinets at 48 hours. Carriage and Packing Free.  
**WRIGHT & PALMER, Cabinet Makers, 335, Katherine Rd., Forest Gate, E.7.** Trade enquiries invited. Phone: East Ham 1151.

the sort of modulated high-frequency currents produced by the valve as a result of the alternating potentials on the grid. These high-frequency currents generated by the valve are rectified by the crystal detector in Fig. 12, or by any other detector used in a dual ampli-

quency potential applied to the grid of the oscillating valve. This will modulate the high-frequency currents generated by the valve; these high-frequency currents are rectified by the crystal detector, and the original impulse is reproduced again on a larger scale which

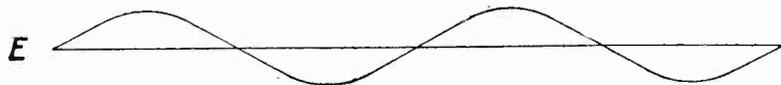


Fig. 16.—Alternating currents produced by the transformer.

cation circuit, because the remarks made here apply equally to all dual amplification receivers. The high-frequency currents shown in line C of Fig. 15 are rectified and produce uni-directional currents as shown in line D, and these produce an average current in the form of uni-directional pulses which pass through the primary of the transformer  $T_1$ ,  $T_2$  in Fig. 12. The transformer converts these uni-directional impulses to alternating currents of the kind illustrated in line E, Fig. 16. These currents are now fed into the grid circuit and reinforce those which we have already assumed are already being introduced into the grid circuit by  $T_2$ .

We thus have a chain of low-frequency reaction which, while quite different from the ordinary kind of chain of low-frequency reaction, yet possesses the same

reinforces it and a process of low-frequency oscillation is set up.

This presumes that the valve V has oscillated, and it will always be found that the effect of low-frequency buzzing is always more likely to occur when the valve is on the verge, or is actually oscillating, due to using too tight a reaction coupling. The same effect, however, may be started even though the reaction is not sufficiently tight to produce self-oscillation. In this case the incoming currents of the carrier wave are modulated by the low-frequency currents in the grid circuit. When the carrier wave is very strong this effect may be obtained, and the introduction of reaction, of course, increases the strength of the carrier wave.

Another thing which starts the circuit buzzing is the actual incom-

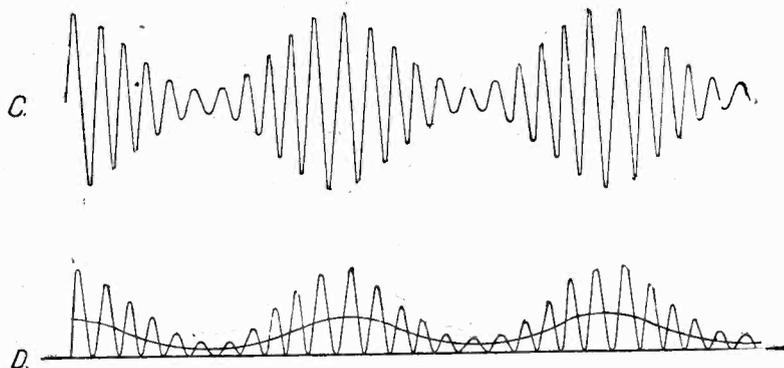


Fig. 15.—High-frequency, rectified, and uni-directional currents shown graphically.


properties of enabling low-frequency oscillation to take place. The low-frequency currents are, in fact, carried by the high-frequency currents generated by the valve, and only appear again after rectification by the crystal detector D.

When considering the generating action of an oscillating valve, we always presume that something has set up a momentary oscillation which is rapidly built up and maintained by the valve. So, in the same way, we may assume, in a circuit of the Fig. 12 kind, that there is some momentary low-fre-

ing signal when receiving telephony. The modulated incoming signals are rectified by the detector and produce a low-frequency current which modulates the carrier wave and so perpetuates the low-frequency oscillation.

Very often a valve may have the reaction so tight that an incoming strong signal will set the valve oscillating, and once the valve oscillates at high-frequency it is very liable to start oscillating on low-frequency, due to the effect which has just been described.

To be continued.

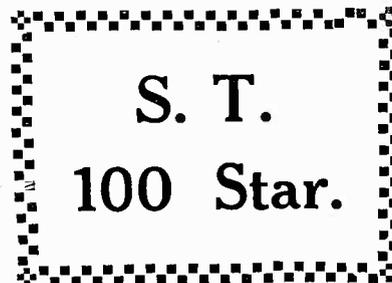

To the Editor of MODERN WIRELESS.

SIR,—I have recently constructed the "S.T. 100 Star," as described in the March number, and am delighted with the results. The following remarks may be of interest. My station is ten miles from 5IT, and I can get all B.B.C. Stations and Ecole Supérieure, Paris, very clearly on ear phones. With the exception of Paris, Aberdeen and Glasgow, all stations came through at the same strength during 5IT's transmission. However, I can get the above three all right, but cannot cut 5IT right out. 5IT is very loud on G.E. Co. loud speaker, and 2LO can be heard faintly. After the B.B.C. Stations closed down last Thursday night, I heard a dance band playing loudly. They finished up with the Austrian National Anthem, followed by the announcer speaking clearly in German. The station turned out to be "Leipzig Mitteldeutsche Rundfunk A.G."—some 600 odd miles away. Last Sunday night I got Petit Parisien, Paris, very clearly on earphones. Recently I tried an indoor aerial of 15 ft. of 28 gauge tinned copper fuse wire. 5IT was loud on phones and was audible on loud speaker at 12 ft. 2LO was faint on earphones. My tuning is rather fine, and unless I move my condenser very slowly I pass over stations.

The following components were used:—G.E. Co. variable condensers and fixed condensers; Burne-dept enclosed crystal; Silvertown transformer; home made choke coil; Igranic 2-coil holder, coil's 35-50-75, valve-holders; Igranic filament rheostats; Watmel variable resistance; Marconi Osram 'R' type valves; G.E.Co. H. T. battery 60 volts and 6 volt accumulator; single aerial 7/22: 90 ft by 30 ft high. I have not soldered any connections.

Wishing MODERN WIRELESS every success.

Yours faithfully,

W. PERCY MCGEOCH.

Knowle, Warwickshire.

# Trouble Corner

Conducted by "ADSUM"

**Adventures with Valves**  
**A** GOOD many things may happen to a receiving valve, some of which may rather puzzle the user if he does not know what symptoms to look for. A comparatively rare occurrence with valves of good quality is a considerable softening of the vacuum within the bulb after a period of use. This happens, as a rule, because the plate and grid, as well as their supports, have not been properly cleaned up in the process of manufacture. All metals contain certain quantities of occluded gases which are given out under the influence of heat. In a well-made valve the processes of bombardment and of cleaning up are so thoroughly carried out that the occluded gases are driven off, with the exception of the minutest

traces, which are not sufficient to make any marked difference to the vacuum. But if you examine a cheap foreign valve carefully you will see that the inner metal parts are dirty-looking. This means that the cleaning up process has not been very thoroughly carried out, and there is a distinct possibility that when the valve is under use the occluded gases will gradually be given out. A new valve

should always be tested for hardness by the application of a high anode voltage. If the valve shows no signs of blue-glow with 100 volts on the plate, it may be taken as being hard enough for practical receiving purposes. Some of the foreign valves are purposely made rather soft, for which reason they make excellent rectifiers. In testing these out in the first instance the blue-glowing point should be noted, and if the valve is suspected of softening it should be tested again. Should softening have taken place, it will now blue-glow with a smaller voltage upon the plate. Very soft valves, by the way, work excellently as rectifiers when there is not more than one stage of H.F. amplification in front of them, but they are of little use when two stages are used. An English valve which

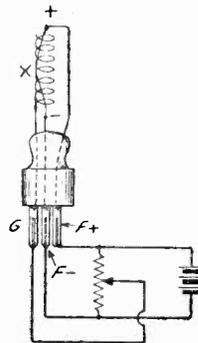



Fig. 1.—Test for displaced filament. The anode is not shown for the sake of clearness.

GO TO

# WATES


ASTOUNDING VALUE

FOR

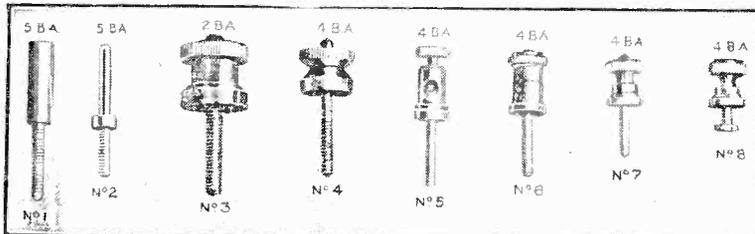

Prices in dozens fitted with nut and washer.

No. 1 8d.	No. 2 8d.	No. 3 2/2	No. 4 1/2	No. 5 1/-	No. 6 1/-	No. 7 10/-	No. 8 10/-
--------------	--------------	--------------	--------------	--------------	--------------	---------------	---------------

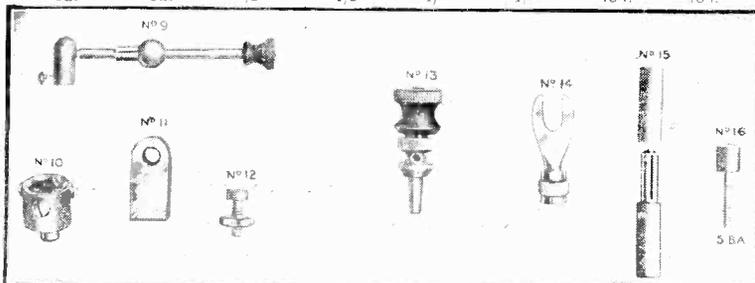


Price each unless otherwise stated.

No. 9 2 1/2 d.	No. 10 2d.	No. 11 1d.	No. 12 6d.	No. 13 3d.	No. 14 1 1/2 d.	No. 14a Pin Type 1 1/2 d.	No. 15 1d.	No. 16 4d. doz.
-------------------	---------------	---------------	---------------	---------------	--------------------	------------------------------	---------------	--------------------

## "DOMINOE CONNECTOR"

KWIKPINS  
3d.  
EACH.

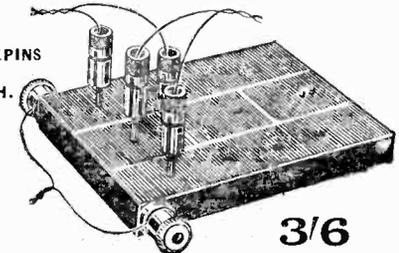

Connect up your headphones in the most efficient manner. You may find series best, or perhaps parallel. The Dominoe connector and kwikpins give you any combination of either up to four pairs of headphones and ensure a clean, firm connection in a moment.

Send for our other interesting lists.

**WATES BROS., LTD.,**  
 12-14, GT. QUEEN STREET,  
 KINGSWAY, W.C.2.

Phone: Gerrard 575/6 Grams: Zvwateseng, Westcent.  
 Bournemouth (wholesale), 101, Old Christchurch Road.  
 Plymouth (wholesale), Central Mill, Raleigh Street.

shows slight traces of softening—that is, one which just begins to blue-glow when the anode voltage is raised to 100 or more with the filament potential at its normal working point—should not be employed as an amplifier, though it will probably give quite good services as a rectifier. In no case should a valve be worked at the blue-glowing point, for if this is done distorted reception will result. Dutch valves will give best results when the plate or filament potentials are adjusted so that they are just short of blue-glowing.

**Displaced Filaments**

Another mishap which may occur to a valve is that the filament may become so strained that it comes into contact with the spiral coil of the grid at some point. With the "R" type of valve it is usually quite easy to detect this by examination if the valve is held between one's eye and the light; but with many other types, and particularly those whose bulbs are covered upon the inside with a metallic layer, it is not at all easy to see whether the filament is out of place. A simple test when a valve is suspected of not being up to the mark will show whether the trouble

is to be found in a displaced filament. Place the valve in a holder on the high-frequency side of the set where the grid potential is controlled by a potentiometer. Move the slider of the potentiometer backwards and forwards and notice whether anything happens to the brightness of the filament. If it is

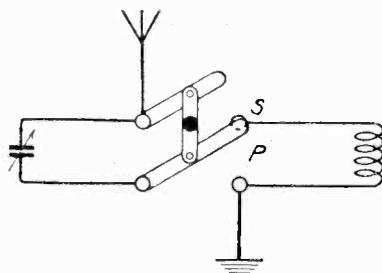



Fig. 2.—Series-parallel connections with parallel arm switch and three studs.

touching the grid, first one portion of it and then the other will glow with unusual brilliance as the slider is moved. Fig. 1 shows the reason why. In the drawing the top end of the filament is the positive one, and the lower the negative. The filament is touching the grid at the point X. If the potentiometer slider is moved right over to the

negative side, the full voltage of the battery passes from the top end of the filament to the point X. When it travels to the positive end the full voltage is again applied to a portion of the filament, this time between the point X and the lower end. If then the movement of the potentiometer makes any difference to the glowing of the filament, it is certain that it is in contact with the grid at some point. As a rule a valve so affected is a hopeless case, but one can sometimes bring about a cure in the following way. Fit up a special holder for the valve, arranging it so that the valve can be placed in such a position that the force of gravity will act upon the distorted filament; that is to say, fix up the valve so that the bowed portion is concave to the horizontal. Then let the filament run rather brightly for some time and give the bulb an occasional tap. This may have the effect of forcing the filament to straighten out a little, but the process is not always successful. The only radical cure is to send the valve to a firm of repairers for a new filament to be fitted.

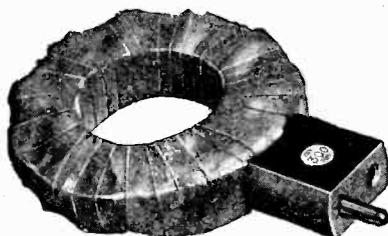**Broken Leads**

A filament that is actually broken is usually easy enough to spot,



	£	s.	d.
Set of 4 Extra Short Wave Coils	0	16	0
Set of 4 Concert Coils	0	16	0
Set of 9 Coils, 75 to 1,000	3	16	6
Prices of single coils and other details on application.			
Holder for three coils for box or panel mounting	1	5	0
Same, mounted on ebonite on special walnut cabinet, complete with tuning chart	2	5	0



## Better Results with BURNDEPT Coils

BURNDEPT Coils give better results because they have lower distributed capacity and less high-frequency resistance than other coils.

They were the first British-made plug-in coils, and that they are still the best is proved by the constant demand for them. This demand recently made possible reductions in their prices. The socket fittings of Burndept Coils are non-reversible and are provided with patent spring contact pins. Perfect and correct electrical contact is assured, however quickly the coils are inserted. Burndept Coils cover all wave-lengths, from 80 to 25,000 metres. They are sold separately or in sets: The Extra Short Wave Coils (80-150 metres), the Concert Coils (for broadcast reception), and Coils 75 to 1,000 (750-20,000 metres).

Very fine adjustment of coils can be made with Burndept Coil Holders. The 5 to 1 gear makes the action particularly smooth and easy to control. Notice the new Burndept Coil Holder Mounting.



BURNDEPT LTD., Aldine House, Bedford St., Strand, W.C.2.

Phone: Gerrard 9072.


Visit our Stand at the British Empire Exhibition in the Palace of Engineering, Avenue 13, Bay 13.

though there are occasions when a valve is unjustly condemned as useless. If the filament will not light up in its own holder always try the valve in another, for the reason may be that there is a disconnection in its own low-tension circuit. See that the pins are properly splayed so that they fit tightly into the legs. A puzzling symptom is occasionally met with: the valve lights up when the rheostat is moved but suddenly goes out and then comes on again if the bulb is tapped. Sometimes the symptoms are not quite so marked; there may be no actual extinction of the filament, but it will glow more brightly if a hand is placed on the top of the bulb so as to push it hard down. In either case the cause is the same; one of the filament leads inside the cap is broken. The ends may be held so closely together that the disconnection is only partial, in which case the valve will be extremely noisy and will, as has been said, brighten up when the bulb is pressed down. Or there may be actual disconnection when the bulb is pressed a little to one side or jarred. When this is the case the filament will light up and go out altogether at intervals when the bulb is moved. The only cure for this

is to have the valve recapped, and this will be possible only if the break has occurred at a point some way from the surface of the glass. Should the break be in the grid and filament leads within the cap tapping or pressing the bulb will produce loud crackling noises in the receivers.

**A Condenser Problem**

A correspondent sends a problem

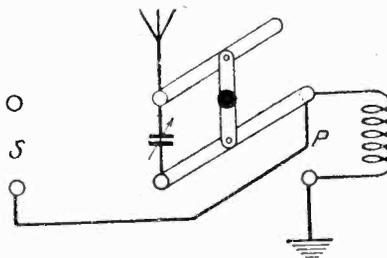

**Fig. 3.—Series-parallel connections with double-pole change-over switch.**

which has very much puzzled him. A new set had been made up which included a series-parallel switch for the aerial tuning condenser. When it was tested out with the condenser parallel, excellent results were obtained, but as soon as the switch was thrown into the series position, nothing at all came through. Coils of various sizes were


tried but the result was the same in every case. The wiring was carefully examined, but no disconnection or faulty connection could be found. It seems probable that the cause of the trouble is to be found in incorrect wiring of the switch. There are several ways of wiring up a series-parallel switch, one of the most convenient of which is given in Fig. 2. This is for a parallel-arm switch with three studs. If a double-pole change-over switch is used, connections may be as shown in Fig. 3. It is possible, of course, that the wiring in the case under review was correctly done, but that the switch arm did not make proper contact when its studs were in the series position. The only other thing that could possibly account for such a failure would be the use of a very small condenser indeed for the A.T.C. If this were done the impedance offered to oscillations in the aerial circuit would be so great that the set would be practically disconnected when the condenser was thrown into series. One would expect, however, that even if the condenser were too small, signals of some kind would come through, though their strength would be very small. It is a safe general rule when working with the (Continued on page 97).

**THE MARK OF MERIT** on any Wireless Set or Component is a guarantee of efficiency, reasonable price, and sound British Manufacture.

**BUY BRITISH GOODS ONLY**

# CONDENSERS

The **MH** Flat Type

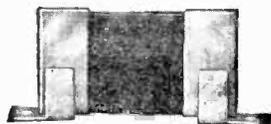

This type of Condenser was introduced by us and is our standard. It is efficient, reliable, easy to fix, and valves can be rapidly interchanged. The price is the cheapest for a good Condenser on the market.

0.001  $\mu$ F to 0.0001  $\mu$ F. 1/4 each.  
0.01  $\mu$ F to 0.002  $\mu$ F. 2/- each.

Two clips supplied with each condenser.

Write for List of Shop-soiled Bargains.

**L.M. MICHAEL LTD**  
IN CONJUNCTION WITH **B. HESKETH LTD**

Showrooms: **RADIO CORNER 179, STRAND, LONDON, W.6.2.**

All correspondence to Head Office:

**HASTINGS HOUSE, NORFOLK STREET, STRAND, LONDON, W.6.2.**

When you assemble your set, ask for—and fit

## GENTS' "TANGENT" TRANSFORMERS.

The "Tangent" L.F. Transformer

Fitted with or without terminals. Insulation perfect and guaranteed for silence and efficiency. Connections clearly marked for identification.

In three types—  
Prices Reduced—Now 12/6, 14/6 and 25/-

ALL TRANSFORMERS ARE TESTED ON ACTUAL BROADCASTING BEFORE DESPATCH.



"TANGENT" L.F. TRANSFORMER.



"DISCOL" H.F. TRANSFORMER.

The "Discol" H.F. Transformer.

Fitted with strong real ebonite checks—unbreakable. All wavelengths from 275 to 4,000 metres. Is recognised as a standard fitment.

PRICE 5/6 each.

Send for Leaflet "Q."

**GENT & CO., LTD.**


London: 25, Victoria St., S.W.1.  
Newcastle-on-Tyne: Tangent House, Blackett St.

Manufacturing Electrical Engineers,

**FARADAY WORKS, LEICESTER.**

Est'd. 1872.
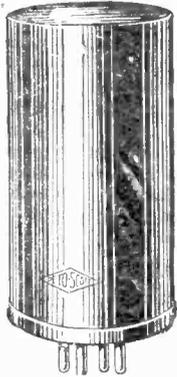
# Will you be ready for Chelmsford? The "Multi-wave" Amplifier.





For H.F. Amplification on all wave lengths above 1,000 metres. Simply plug in—no tuning with variable condenser required. Made in two types. No. 1 for coupling between H.F. and Detector and No. 2 for use where more than one stage of H.F. Amplification is used. In this case No. 2 is used as coupling between the two H.F. Valves. Fully guaranteed. No. 1, 8/6; No. 2, 12/6.

Large Illustrated Folder in colour giving full particulars of the Peto-Scott Unit System containing many diagrams sent free of charge. 48 page Catalogue of all components and instruments, 3d., post free.
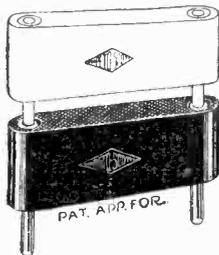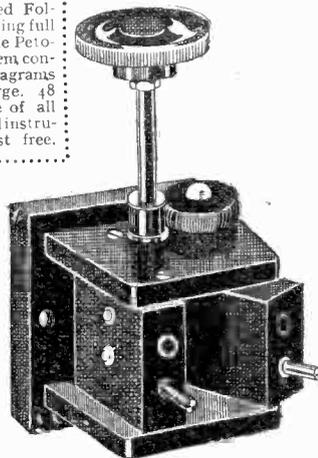
## Friction Drive Coil Holder.

The latest improvement for obtaining very fine tuning. Essential for long distance work and for use with critical reaction. Superior construction made entirely from solid ebonite and hand polished throughout 10/6.



## Plug-in Condensers.

An entirely new system for building up condensers of various capacities. Each condenser is fitted with plugs and also sockets—thus two or more can be plugged into each other until the desired capacity is reached. This method also enables condensers in the Set being rapidly changed without making a single alteration in the wiring. In all values from .0001 mfd. to .0009 mfd. 2/6. From .001 to .004 mfd. 3/- Sockets per pair 2d.



## Double H.F. Condenser


When two stages of high frequency are used both transformers must be tuned simultaneously—here is a Condenser that will do it by turning one Dial only. Each half of the Condenser (value .00025 mfd.) is insulated but can be connected together, when required, to make one to the value of .0005 mfd. One-hole fixing to panel. 14/-

## Long-distance H.F. Transformer

An improved pattern with air core. Wave-length range, 300 to 500 metres. Highly polished, best quality ebonite,

6/6

Also in other sizes up to 2,000 metres.

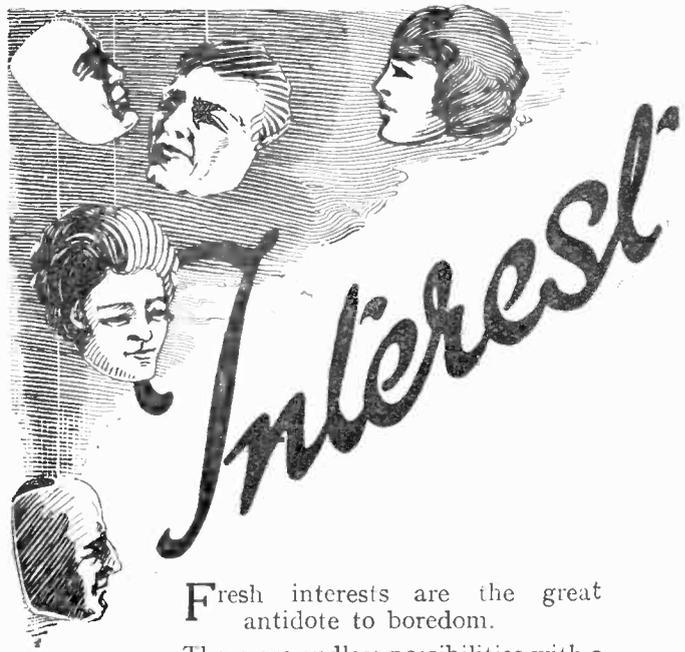

Fresh interests are the great antidote to boredom.

There are endless possibilities with a really efficient portable set that can be carried about like a week-end suitcase. Such a set can be used indoors, on the river, when motoring, or equally well to while away the time on a long train journey.

The new **FELLOPHONE PORTABLE THREE** is shown below. It requires no aerial or earth wires whatever; all being included in the case. Dry cells are also fitted inside so that there are no accumulators to require constant re-charging. It will give excellent results on several pairs of headphones and a Loud Speaker may be used when close to a Transmitting Station.

The compactness and high-class finish will be seen at once on inspection.

Complete with headphones:

**£14-0-0**

(In real cowhide 15 guineas).

Extras: B.B.C. tax £1 0 0, Marconi tax £1 17 6, and 3 Marconi D.E.3 Valves.

**FELLOWS MAGNETO CO., LTD.**

PARK ROYAL, N.W.10.

Phone: Willesden 1560.

## Special offer of complete Parts for the 5-valve Receiver described in this issue.

In accordance with our policy of assisting the experimenter by supplying complete sets of parts for any Receiving Set described in this Magazine we are making a special offer for the very fine 5-Valve Set described by Mr. Percy W. Harris. Complete Instrument in sets of parts for home assembly, including panel, drilled, tapped and engraved, every component necessary including rheostats, resistances,

condensers, coil holders, valve and transformer sockets (absolutely everything excluding valves, coils and H.F. Transformers) £6 10 6. Marconi Royalties £3 2 6 extra. Polished Cabinet with sliding door at rear, extra, 15/6. Finished Instrument (aerial tested) £10 10 0. Marconi Royalties £3 12 6 extra. Panel only, drilled, tapped and engraved, £1 4 6.

**PETO-SCOTT Co., Ltd.**, Head Office & Showrooms: 64, High Holborn, W.C.1

Demonstration Lounge: 99, High Holborn, W.C.1

Branches: London: 77, City Road, E.C.


Plymouth: 4, Bank of England Place (Near Derry's Clock.)

Liverpool: 4, Manchester Street.

Cardiff: 94, Queen Street.

Walthamstow: 230, Wood Street.

G. A. Ltd., 844

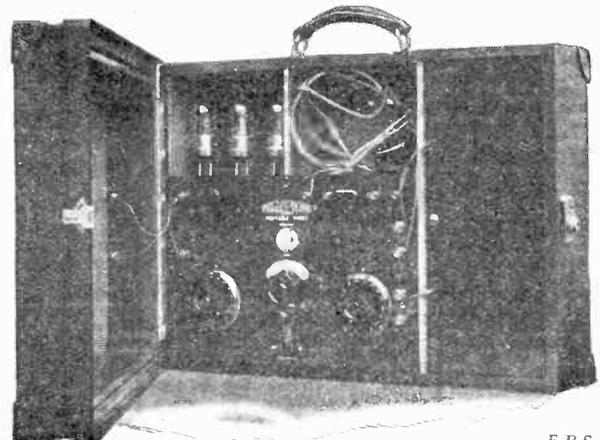

In replying to advertisers, use **COUPON** on last page

E.P.S. 65.

# ANOTHER TESTIMONIAL TO GAMAGES

FAMOUS CRYSTAL

Read this Copy of a Letter from  
**ARTHUR O. MILNE, 'Homeleet,' Northdown Way, Margate**  
'Tis but one of many in praise of this wonderful crystal.

## PERMANITE

Regd. No. 43341.  
Highly sensitive.  
Clear, powerful  
results. Remains  
in adjustment  
longest. Get a  
piece to-day and  
notice the im-  
provements in  
your results.  
**PER LARGE  
PIECE**


**1/6**



"Homeleet,"  
Northdown Way,  
Margate.


It may be of interest to you to know that I am receiving 2 LO regularly on a crystal set, with single slider tuning and a piece of your crystal "Permantite." The name could not have been more aptly chosen, as this piece of crystal was purchased at the exhibition and has been lying idle until about a month ago. My "Cat's-whisker" is a piece of electric main fuse wire, and my 'phones a pair of Brown's "A" type of 4,000 ohms resistance. I am more than delighted with this excellent performance and you are at liberty to use this letter in any way you may wish.  
Yours faithfully,  
**ARTHUR O. MILNE.**

Post Free.

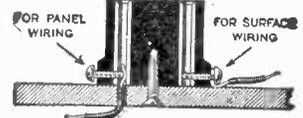

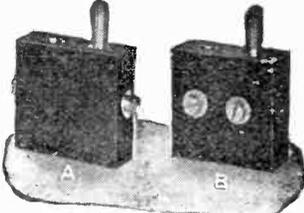
### LEGLESS VALVE HOLDER

This is the easiest valve-holder to fit on the market and, being its own template, can be done by the mere novice. No soldering required. Excellent finish. In best ebonite. Post 3d. Price **1/6**



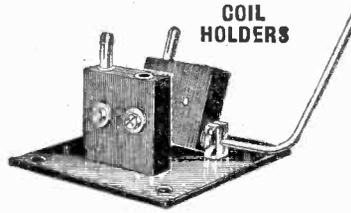
### COIL PLUGS

Handy Coil Plugs. Very useful for Home-made Coils. Made in best quality ebonite. Either type. Price **9d.**


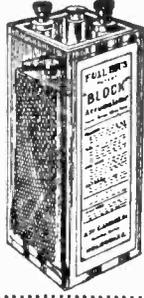
### FULLER'S BLOCK ACCUMULATORS

Special offer of ex-Government Stock but absolutely unused.  
2 volt, **10/6**  
40 amp. Post 1/-.  
4 volt, **21/-**  
40 amp. Post 1/-.  
6 volt, **31/6**  
40 amp. Post 1/6.  
Six accumulators and box sent post free.



This is the ideal Coil-Holder for Honeycomb and Burndep't Coils. Made in best ebonite, with all brass parts finished dull nickel. Perfect movement, which can be tightened when using large Coils.  
For two Coils **6/6** For three Coils **8/6**  
Post 6d. Price Post 6d. Price

### Wireless on EASY TERMS

You may now secure on payment of first deposit, Wireless Sets from £10 upwards, balance being payable in monthly instalments. Write for details to Wireless Department.




### Handy Basket Coil Holder.

This basket coil-holder is beautifully made, and finished in best ebonite. Price **1/3**. Send right away for these. Post Orders may be sent with every confidence of satisfaction.

### Write for WIRELESS Catalogue

Just published, this splendid book should be in the home of every wireless enthusiast. It contains everything from a complete set to the smallest accessory. We will send you a copy post free on request.

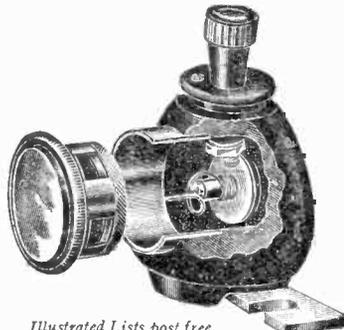**A. W. GAMAGE, Ltd., HOLBORN, LONDON, E.C.1.**




## THE ECCENTRO DETECTOR.

(Patented)  
This Detector is undoubtedly THE BEST ON THE MARKET. It reduces crystal adjustment to the foolproof operation of turning a knob. It is a real piece of mechanism. Dust-proof and Shockproof. Post **8/-** free.

Illustrated Lists post free.

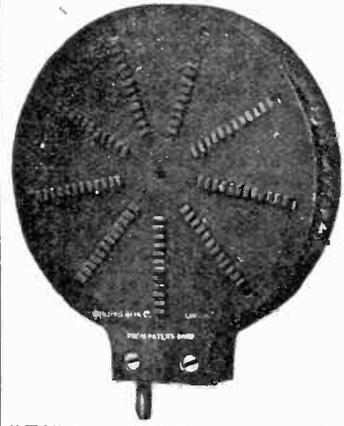**W. JOANES, 42, JENNER ROAD, STOKE NEWINGTON, N. 16.**



## IF you want


to receive long distance stations it is not necessary to add to the number of your high frequency valves. This method only adds to your tuning difficulties and runs down your batteries. It is just as effective and much cheaper to fit

"Efficiency" Inductances and cut out your high frequency losses. The amount of signal strength gained by a high frequency valve can be easily lost again in an inefficient coil. There is nothing mysterious about the action of "Efficiency" Inductances. The greatly improved results obtained with them are entirely due to their scientific design, which incorporates the following points:—  
Low Self Capacity. Maximum Inductance.  
Low Effective Resistance. Uniform Distribution of Current.  
Uniform Size for all Wave-lengths. Great Mechanical Strength.  
Larger Tuning Range. A Backing of 30 years' Coil Winding Experience.

A Postcard will bring copy of our leaflet on inductances.
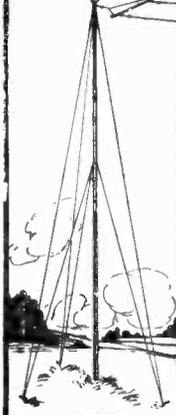
## GAMBRELL Bros., Ltd. 76, Victoria St., S.W.1.

West End Agent: J. V. MULHOLLAND, 4, Blenheim Street, W.1. Works: Southfields, S.W.18. Phone: Victoria 9938.




### 'TURRET' Columbian Pine Masts

**1,000 IN USE.**  
Designed by Naval Experts.

27 ft. Turret Two Complete	37/8
28 ft. Turret Super Mast	53/8
36 ft. in 3 sections	71/8
42 ft. Telescopic Mast	79/8
45 ft. Super Telescopic	84/8
55 ft. Doubly Telescopic	85/19/8
56 ft. Super Mast	86/9/8
Turret Poles, 13ft.	5/9
16 ft. 2 1/2 in. base	7/9
28 ft. 2 pairs clamps	17/9
42 ft. 4 pairs clamps	29/9

Send for List or phone Gerrard 2657

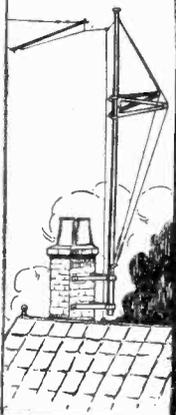

**SIMPSON & BLYTHE, 8-9, Sherwood St., Piccadilly, W.1**

(Continued from page 94).

A.T.C. in series always to use inductances of such a size that the capacity is never below .0003  $\mu$ F. That is to say, if you have a .001  $\mu$ F condenser in series the A.T.I. should always be such that the condenser pointer is not below the 60 degree mark on a 180-degree scale. With parallel condensers the rule is exactly reversed. Here one should strive to use as little capacity as possible.

**When Crystal Detectors Work Badly.**

It happens sometimes that a crystal detector which has been doing excellent work for a long period begins to show signs of a marked falling off in the strength of its signals. Even the most painstaking search for sensitive spots and the most careful adjustment of the pressure between the contact point and the crystal fail to give the results that we formerly obtained. As a rule the inductances, the condensers and the telephones are suspected by turn of being at the root of the trouble, but it is nearly always the detector itself which is at fault in such cases. The reduction in signal strength may be due to one of several causes, but in every case save one it is a matter

of bad contact. It should be remembered that the crystal has to make two contacts: the first with its cup and the second with the catwhisker. Many people take infinite pains over the second without bothering much about the first of these. Things are most likely to go wrong where the crystal is held between the points


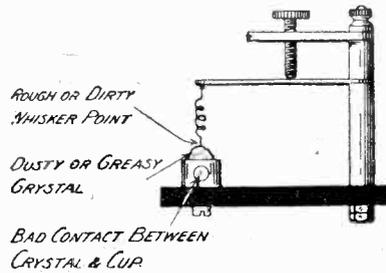


Fig. 4 — Points to inspect in a faulty detector.

of three setscrews. It is always difficult to insert an awkwardly shaped piece of crystal so that it is properly held, and as time goes on a loosening may easily occur. If the detector seems to be working unsatisfactorily always begin by prodding the crystal, using a bodkin or something of that kind for the purpose and not the fingers. Should it show any signs of loosening you have probably found the cause

of its misbehaviour at the first shot. It is rather a good tip to wrap the crystal in bright clean copper foil before inserting it into its cup, when screw contacts are used. By pressing copper foil tightly round the crystal you ensure that a good contact will take place. The foil is scraped away with a knife from the upper surface of the crystal after it is in position. Better still is to dispense with the screws altogether and to embed the crystal in Wood's metal, which has a very low melting point. Never use solder for the purpose, for its melting point is high enough to injure certain delicate types of crystal. Suppose that the crystal is found to be quite firm in its cup, it is possible that its surface is greasy or dusty, either of which is sufficient to impair its working to a very great extent. Never handle crystals, for even the cleanest fingers have a slight film of grease which is transferred to the crystal. For this reason it should always be picked up with a pair of tweezers. To remove dust and grease give the crystal a bath in absolute alcohol and replace it in the holder without touching it. Do not use petrol or methylated spirits, both of which leave solid deposits after evaporation. Should neither of

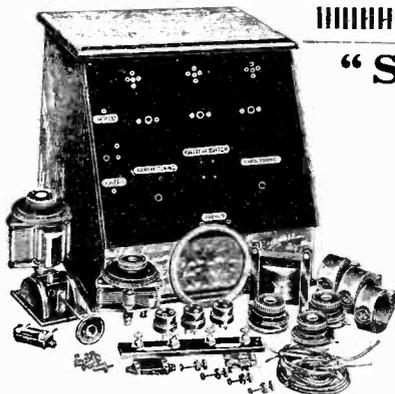

See Catalogue No. M/105 for full particulars.


**"SONOLA" REGD. CONSTRUCTIONAL RECEIVING SETS.**

These Sets are despatched with ready drilled Panels, Assembled Condensers, wound Transformers, and can be easily put together with the aid of a pair of pliers only. Full instructions supplied.


- 2 VALVE PANEL** £5 7 0  
Plus Marconi Royalties 25/-
- 3 VALVE PANEL** £8 15 0  
Plus Marconi Royalties 37/6
- 4 VALVE PANEL** £9 0 0  
Plus Marconi Royalties 50/-

**VARIOMETERS**

**WAVE LENGTH 300 to 560 Metres.**

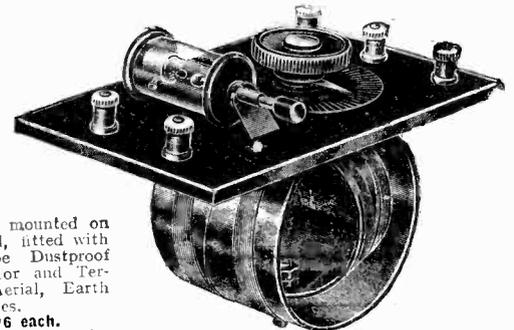


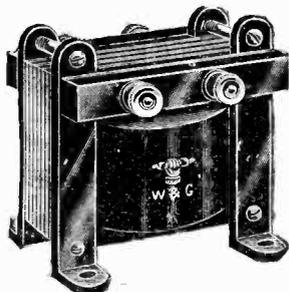As illustrated, mounted on Ebonite Panel, fitted with improved type Dustproof Crystal Detector and Terminals for Aerial, Earth and Telephones. Price 10/6 each. See Catalogue M/105 for wide range from 2/6 each.



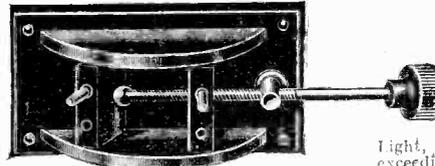**"SONOLA" Regd. LOW FREQUENCY TRANSFORMER.**

Size 3 1/2 x 2 1/2 x 3 1/2 in. Unsurpassed for Silence, Efficiency and Reliability. Provides remarkable amplification with freedom from noise and distortion. Equally suitable with every type of valve. Terminal Type 17/6 No make of transformer gives better results.




**"SONOLA" Regd. MICROMETER REGULATING TWO-COIL HOLDER. P. PATENT.** Enables the finest possible tuning and adds considerably to the efficiency and selectivity of the Receiving Set. Price 10/-

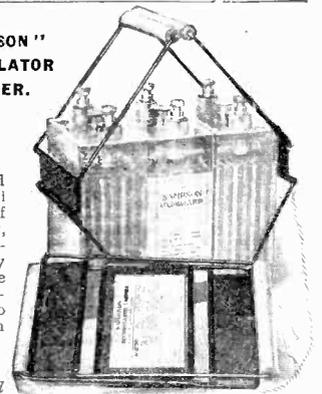**"SAMPSON" ACCUMULATOR CARRIER.**

Patent.

Light, Strong and exceedingly useful. The inconvenience of handling weighty, cumbersome accumulators is entirely obviated. Suitable for any size accumulator. Folds flat to fit the pocket when not required. 3/- each.



From all Radio and Electrical Stores. Refuse substitutes. Write direct if unobtainable.



Stocks also held at GLASGOW DEPOT, 95, PITT STREET.

Fully illustrated Catalogue M/105 contains a wide range of complete sets, Constructional Sets and Component Parts of every description, free on request. Enclose Business Card or Memo for Special Trade Terms. Address all communications to PENDLETON, MANCHESTER.

In replying to advertisers, use COUPON on last page

**WILLESFORD'S WIRELESS SPECIALITIES AND PATENTS ARE ESSENTIAL TO THE UP-TO-DATE LISTENER-IN.**

**PATENT TELEPHONE EXTENSION FLEX.** 12-ft. long. A speciality for the summer. Fitted with plugs and sockets to join up to the ordinary telephone flex, enables listeners-in to sit at any distance from their receiving sets, even out in their gardens if they like.

All Retailers, 2/6, or P.O. 2/8.  
**CRYSTAL AMPLIFYING AND CLEANING POWDER.** A marvellous discovery to greatly increase sensitivity of crystals. Acts like an amplifier.

All Retailers, 1/-, or P.O. 1/2.  
**PATENT MULTI-POINTED CATWHISKER.** The marvel of the age. No trouble finding points. It gets many. Thousands of testimonials.

All Retailers, 1/-, or P.O. 1/2.  
**"SPECIAL" CRYSTAL.** Testimonials say: "I consider your 'Special' Crystal and Multi-pointed Catwhisker a splendid combination. I get marvellous results."

All Retailers, 1/6, or P.O. 1/8.  
**TELEPHONE STAND.** For hanging up headphones when not in use. Made with coloured mahogany wood base, and having an upright with four arms resembling red ivory. Base can be detached and upright screwed into set if desired. No capacity effects.

All Retailers, 10/6, or P.O. 10/9.  
Buying Agents Wanted.  
**WILLESFORD'S, 20/1, Buckingham Street, Strand, W.C. 2.**

*Fix your crystal in*

**GOLD SEAL PLASTIC METAL** the best contact possible, and get louder and clearer signals. Contains no mercury. Of all Wireless Stores Enough for 6d. per packet. 3 cups. Wholesale enquiries (or sample packet 6d.) to: B. LEVY, 53, Ben Jonson Rd. London, E.1

**WIRELESS CRYSTAL DETECTOR PATENT.**

—The Proprietor of British Patent No. 183,104 is desirous of entering into negotiations for the grant of licences thereunder on reasonable terms, or for the sale of the Patent outright. It relates to the type of Crystal Detector in which the Crystal is adjusted between two Electrodes.—Communications please address to DICKER & POLLAK, 20-22, Holborn, London, E.C. 1.

**Max-amp**

High-Grade Intervalve Transformers

18/6

The Editor of "Amateur Wireless" says: "It may interest readers to know that Peto-Scott Transformers are used in the Editorial Set." What better recommendation could there be! Sold only by


**PETO-SCOTT CO., LTD.,**  
64, HIGH HOLBORN, W.C.1  
and Branches.

**L.F. Transformer**

these expedients effect a cure attend to the point of the catwhisker which may be rough or dirty. Smooth it off with a fine file and try the detector again. If no sensitive spot can be found it may be taken that the crystal has "gone off." Some of them do deteriorate with use, especially if the set has been subjected to the effects of powerful atmospherics. It will sometimes be found that fresh sensitive points will be disclosed if the surface of the crystal is chipped with the point of a penknife, but often it is advisable to discard the crystal and to fit a new one.

**Coil Holders.**

It happens occasionally when coil holders are purchased, especially those of the cheaper makes, that the set refuses to function when they are used. The symptoms may be rather mystifying. Place a coil in the holder before it is mounted in the set and touch the screws intended to secure the connecting wires with the ends of two leads coming from a battery and a pair of telephones in series. A reassuring click will take place in the phones, which shows that all is well. Now mount the coil holder on the panel, secure wires to the screw connections and insert an inductance.

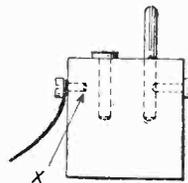

**Fig. 5.—How a coil holder may play up after being connected. Owing to the thickness of the wire the screw does not reach plug at X.**

You switch on and nothing at all happens. The last thing that you suspect is naturally the coil holder, which has already been tested out, but actually the fault is there. Fig. 5 shows how it occurs. In these coil holders the contact screws run through the ebonite into a plug or socket. Sometimes the screw is not long enough to allow for the insertion of a fairly thick wire and a washer below its head. Hence when the wire is connected the tip of the screw does not reach the shank of either plug or socket as the case may be. The remedy is quite obvious—substitute a longer screw. But unless one knows what to suspect, trouble due to a faulty coilholder may take quite an amount of running to earth. Before mounting any coil holder always remove the contact screws entirely and measure them to see that they are long enough to do their job properly.

**Results on the 3-Valve Dual Receiver.**

To the Editor of MODERN WIRELESS.

SIR,—I thought that you might be interested to hear what results have been obtained on your 3-valve Dual Receiver, described in your April issue.

I have had it in use about a week. I am 13 miles from Birmingham, and it comes in on the loud-speaker really too strong for the average-size room. I have also succeeded on several evenings in getting London, Bournemouth, Manchester, Newcastle and Glasgow on the loud-speaker easily. Cardiff is just off the range of my H.F. transformer. Aberdeen I have not yet been able to separate out from Birmingham. All these were obtained without a reaction coil in. I really think the results and the quality of reception is excellent, and so far as I am concerned better than the usual four-valve combination.

I find results are best all round when using constant aerial tuning, and the .0004 series condenser with the H.F. variable condenser.

I have not had time really to do much experimenting with the circuit. By the way, I can tune all the stations in on the loud-speaker without using telephones. With regard to H.T. I am using 120 on 1st, 40 on 2nd, and 120 on 3rd, with 3½ volts negative bias on 1st and 4½ on the L.F. valve.

I should really like to congratulate you on adding yet another circuit to your famous collection, which does all and more than you indicate.

Yours sincerely,

A. J. DAVIES.

Birmingham.


P.S.—Paris comes in almost as loud as Birmingham.

Order your  
**'Modern Wireless'**  
beforehand and  
avoid  
disappointment.

# FORMO SERVICE
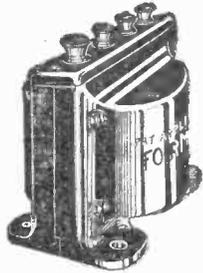
## THE FORMO-DENSOR

CAN BE SEEN ON OUR STAND, AVENUE 11, BAY 8.  
BRITISH EMPIRE EXHIBITION



Shrouded Transformer.

Ratios.  
A-1-2 }  
B-1-3 } 18/-  
C-1-4 }  
D-1-5 }  
1-10 21/-  
For Special  
Circuits :  
C-1st Stage.  
A-2nd Stage

This Condenser is a Perfect Instrument, of ORIGINAL and EXCLUSIVE DESIGN and FINE WORKMANSHIP.  
SINGLE KNOB OPERATING MAIN VANES and VERNIER  
The greatest advance yet made in condenser design.


DEMAND FORMO PRODUCTS,  
**THE FORMO COMPANY,**  
(Arthur Preen & Co., Ltd.)

Offices and Works—  
22, Cricklewood Lane, N.W.2. \*Phone, Hamp. 1787

Complete with  
Knob, Dial and  
Vernier.

.001 .. 10 6  
.0005 .. 9 6  
.0003 .. 8 6

One hole fixing

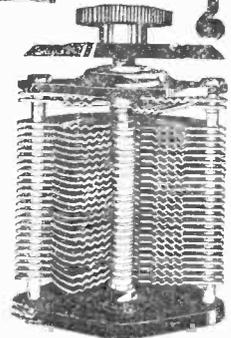

Manufactured  
Entirely by  
British Labour  
in our own works.

## BOUGHT with BONTONE

The moderate price of BONTONE in conjunction with a very generous guarantee and constructional superiority make them a distinctive type.

BONTONE will respond to the weakest signals, and reproduce clearly the most intricate orchestral music. They are entirely the product of our own works. The working mechanism is highly creditable to our telephonic engineers.

That they are comfortable, easily adjusted and may be bought with complete security is your guide.

**GUARANTEE.** We agree to replace or return cash if Phones do not give complete satisfaction subject to Phone being returned to us within 7 days of purchase undamaged.

If you prefer light weight, but still require maximum signal strength, then

**BONTONE LIGHTWEIGHT:**  
will admirably fill the bill.  
**15/6** post free.

These Headphones are similar in construction to the standard BONTONE, and purchaser is guaranteed



4,000  
OHMS  
PER PAIR

**14/6**

Post free

**B. D. & Co. (Edward A. Boynton)**

Offices: 167-173 GOSWELL RD., LONDON, E.C.1  
Works: GOSWELL RD. & CITY RD., LONDON, E.C.1

Admiralty, War Office and India Office Contractors.

Sole Distributing Agent for Scotland: J. W. Gordon, of 98, Sanchiehall Street, Glasgow.

BONTONE are Sensitive, Durable and Comfortable and are obtainable from your dealer. If he cannot supply send direct to the manufacturers.


## B.B.C. WIRELESS DRY BATTERIES For B.B.C. Sets

### No. 1 W.

Standard Pocket Lamp Size—4½ volt with patent spiral wire terminals and plug sockets to take Wander Plugs.

Note — 1 doz. = 54 volts

Used units replaced easily.

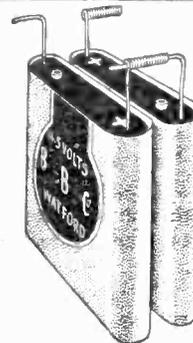

To connect in Series insert straight terminal in spiral of next battery. Bend spiral and thus ensure permanent electrical connection without soldering.

BRITISH MADE.

Connect as illustrated.

Patent applied for.

PRICE CARRIAGE PAID, 7/- PER DOZEN, WITH PLUG.

Standard Sizes :

No. 2 W. Slab, 16½ volts, 3-volt tappings. Size approx. 9 x 1 x 3 ins. ...	Price 3/- each
No. 4 W. Slab, 36 volts, 3-volt tappings. Size approx. 10 x 1½ x 3 ins. ...	6/6 "
No. 5 W. Block, 60 volts, 3-volt tappings. Size approx. 9½ x 3¼ x 3¼ ins. ...	12/- "

Prices include Wander Plug. Carriage Paid.

Manufactured by

Telephone: Watford 617.

**The BRITISH BATTERY CO. LTD.**  
CLARENDON RD., WATFORD, HERTS.

## THE LONDON TELEGRAPH TRAINING COLLEGE Ltd.

Telephone: Western 2696. Morse House, Earl's Court, S.W. Established 28 Years.  
OFFICIALLY RECOGNISED BY THE WAR OFFICE, THE ROYAL AIR FORCE AND POST OFFICE AUTHORITIES,  
**CABLE AND WIRELESS TELEGRAPHY.**

PARENTS DESIROUS of placing their sons in either of the above Services and of affording them the best training facilities should apply for particulars of Courses and the methods of instruction which place this Institution in the first rank. Cable Telegraphy offers at the present time excellent prospects to youths from 16 years of age and upwards, and the College has exclusive facilities for obtaining posts for qualified students in the leading Cable Companies at commencing salaries of from £200 to £300 per annum, with yearly increments of £12 to £25, and with ultimate possibilities of obtaining The College has never given "Guarantees" to obtain appointments and parents are warned against persons who do so as it is manifest that any such "Guarantee" must be of a fraudulent character.



positions as Supervisors, Assistant Superintendents, Managers, etc.

In the Wireless Telegraph Service the commencing salary at the present time is about £90 per annum, plus free maintenance on board Ship, which makes the total remuneration approximately £150 per annum, and Operators when qualified by holding the Postmaster-General's Certificate of Proficiency are nominated by the College for appointments, of which there are a considerable number available at the present time. Positions are also obtainable in the Royal Air Force.

No Correspondence Classes or Branches.

Apply for Prospectus to THE SECRETARY (Dept. M.W.), 262, Earl's Court Road, Earl's Court, London. S.W.5

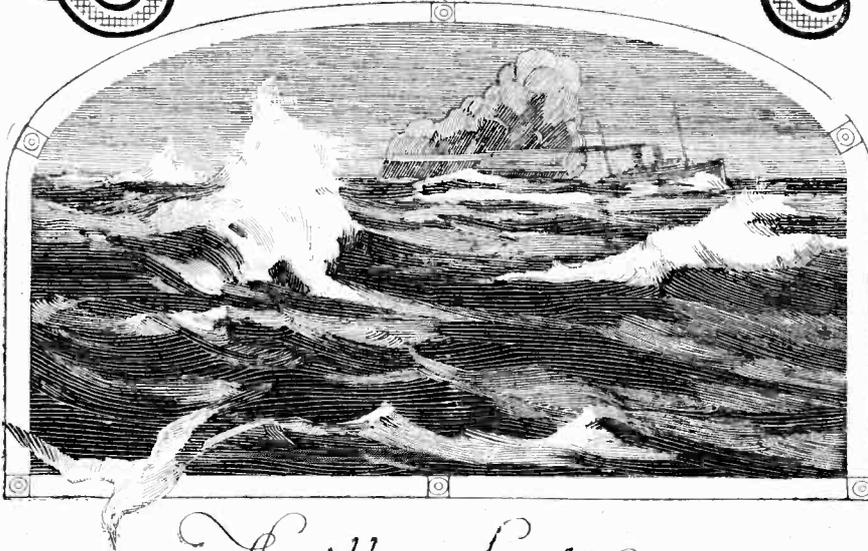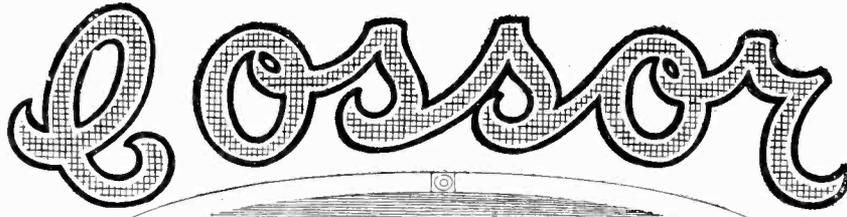In replying to advertisers, use COUPON on last page



## Thrills of distance

**I**F Radio has done nothing else, it most certainly has made us realise that we are no longer an island. Such is the rapid progress of international Broadcasting that anyone can—in one evening—hear French, Dutch, German, Italian, and Spanish spoken by natives in their own language.

A tour of Europe in one hour! Such thrills of distance are available for anyone with a good Valve Set and a knowledge of its use.

But long-distance work demands a careful selection of apparatus. Just as prismatic binoculars have rendered the telescope old-fashioned, so the Cossor P.2—the valve with the red top designed specifically for long-distance work—has superseded the ordinary Valve with long straight filament and open-ended Anode.

There is a reason for this. When a Valve glows it emits a stream of negative particles—electrons—which travel from the filament towards the Grid and the Anode.

This electron stream is the whole basis of valve amplification and rectification—turn your filament current off,

If you are dealing with the almost infinitesimal currents generated by a Broadcasting Station in, say, Madrid, you can't afford to take chances with inefficient valves. Be wise, therefore, and see that every Valve in your Set is a Cossor—and your results will be consistently good.

electrons cease to flow and your Set becomes dead.

Obviously, therefore, the greater the percentage of these electrons we can capture and put to a useful purpose the more efficient will be our Valve. Compare the construction of the Cossor and the ordinary Valve.


In the one case the filament is almost totally enclosed by the hood-shaped Grid and Anode—what chance has the electron stream to leak away here? On the other hand where the Anode is in the shape of a tube quite a considerable percentage of electrons travel direct to the glass without touching either Grid or Anode—a typical case of wasted energy.

Manufactured in two types:

**P.1.** (For Detector and L.F. use) - - - 12/6

**P.2.** (with Red Top) for H.F. use - - - 12/6

From all Dealers.

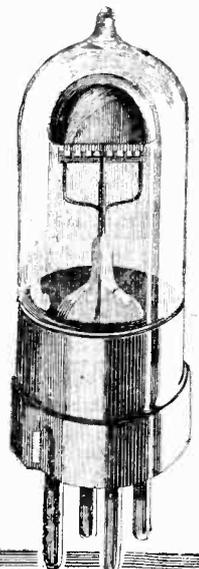

Advertisement of A. C. Cossor, Ltd., Highbury Grove, N.5.

Gilbert Ad. 887.

# 3

## good R.P. Books you should read

### Twelve Tested Wireless Sets

Series No. 14. By Percy W. Harris.

A first-class Book for the home Constructor. Embraces a wide range of Sets from a Crystal Receiver costing but half-a-crown to an S.T.100, an All-Concert Receiver and an improved Reinartz. In addition, a new Set using two stages of high frequency which can be relied upon to pick up American Broadcasting with the greatest ease when conditions are favourable. A special chapter is devoted to wave-traps and devices to enable interference from the local B.B.C. Station and ships to be eliminated. **2/6**

### How to Make a Unit Receiver

Series No. 7. By E. Redpath.

The idea of expanding Bookcases as applied to Wireless. The particular Receiver described in this Book consists of four Units which, when coupled together, will receive every B.B.C. Station and will work a Loud Speaker from the nearest one. Yet the first Unit by itself will enable Broadcasting to be enjoyed if you are within 30-40 miles from a B.B.C. Station. The other Units can be added at your leisure. This economical system will commend itself to the man of moderate means. **2/6**

### Tuning Coils and How to Wind Them

Series No. 18. By G. P. Kendall, B.Sc.

There is probably no single Component in any Receiving set able to exert so much influence as an Inductance Coil. A highly efficient Coil (or Coils) will often make all the difference between mediocre results and really clear and loud reception.

Even if you feel that your present set is giving tolerably good results, the chances are that it will be worth your while—presuming that you are using plug-in coils—for short wave-lengths to use a set of home-made basket coils. Such coils as these have particularly low self-capacity.

This new Book by G. P. Kendall, B.Sc. (staff editor), contains concise details for making every type of Coil used in Wireless to-day. All necessary data, such as diameter of tubes, gauge of wire, number of turns, etc., are given—the results of the author's own experiments. **1/6**

Obtainable from all Booksellers, or post free 2d. extra direct from Publishers

**RADIO PRESS Ltd.**  
Devereux Court, Strand, W.C.2.

# Radio Valves & how to use them

By John Scott-Taggart,  
F.Ins.P., A.M.I.E.E.



By the  
Editor  
of this  
Magazine

**T**O make real progress in Wireless you must be able to understand the principles of the Radio Valve. The importance of this cannot be emphasised too strongly.

While there are several Books on the Valve by the same author, none of them covers quite the same field as "Radio Valves and How to Use Them."

Its explanations are most lucid and graphically illustrated by a very large number of diagrams. It is a book which, although dealing with a difficult subject, is most fascinating and intriguing in its appeal. A book which ought, in fact, to be on every wireless enthusiasts' book-shelf.

It is written from the point of view of the man who is going to use valves.

The following chapter headings will give some idea of its wonderful comprehensiveness:—

- Two-electrode Valves and Their Uses.*
- Three-electrode Valves and how They Work.*
- The use of the Valve as a High- and Low-frequency Amplifier.*
- Using the Valve as a Detector.*
- Multi-valve Receivers in Theory and Practice.*
- Receivers using Reaction and Their Operation.*
- Recent Circuits and Their Application.*

The whole subject of Valves is treated in such an absorbingly interesting manner that the first edition was bought up within a few weeks by those who had read other books by the same author.

Sold by all Booksellers  
and published by  
**RADIO PRESS, Ltd.,**  
Devereux Court, Strand, W.C. 2.

# 2/6

Post free 2/8

RADIO PRESS Series No. 12

G.A. 867

## H.A.H. VARIABLE GRID LEAK.

An invaluable accessory for tuning in long distance calls. It is suitable for all wavelengths. The usual resistance employed for wireless reception is 1½ megohms, and with the H.A.H. instrument a variation down to ½ megohm and up to 5 megohms can be immediately made by turning the switch during operation. Any special calibration can be supplied, and a special model is made for use on the S.T. 100 circuit. **The Resistance Values can always be repeated.**

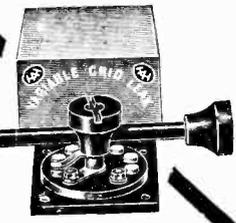


Fig. 1100.  
**"VARLEAK"**  
Price 4/6 each.  
Extension handle,  
Fig. 1110.  
Price 9d. extra.

## H.A.H. COMBINED VALVE PROTECTOR FUSE, BATTERY TESTER, AND SAFETY WANDER PLUG.

**"IT WILL SAVE YOU POUNDS."**

This device is for use as a fuse in the H.T. Circuit, and should this high voltage be accidentally connected to the wireless valve filament, a cheap flashlight bulb worth 7d. only is wasted, instead of one or more expensive valves costing 15/- or 20/- each being burnt out. **Write for Free Catalogue no. 52.**



Fig. 828.  
**"SAVE IT" PLUG.**  
Price 2/- each.  
as illustrated.

Manufactured by  
**A. H. HUNT, Ltd.**  
Department 5,  
H. A. H. WORKS,  
TUNSTALL RD., CROYDON.  
"Keyage, Croydon."  
Croydon 2225.


## SENSITIVE DRILLS

FOR ALL PURPOSES.

- Type F.B. 201 for Flat Bed Lathes .. .. . £3 10 0
- Type D.R. 201 for Drummond Round Bed Lathe .. .. . £3 10 0
- Type B.D. 201 for Power Drive .. .. . £4 15 0
- Type T.D. 201 for Treadle Drive .. .. . £7 5 0

Full specification on application.

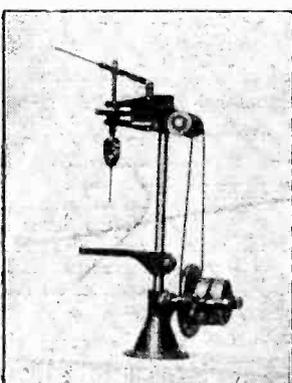**MOORES and GRIFFITHS, LTD.**  
(C. Dale, Receiver),  
Broadway, Bexley Heath, Kent.



B.D. 201


## YOU SAVE 33 1/3% ON ALL WE ADVERTISE

<b>FILOSTAT for D.E. VALVES</b> 2/6 0 to 30 ohms.	<b>BASKET COIL HOLDERS</b> 1/3
<b>CABINET AND EBONITE PANEL</b> , 6 in. by 6 in., each	<b>VARIOMETER BALL ROTOR</b> .. .. . 3/6
<b>VARIABLE CONDENSERS</b> .001 8/6; .0003 5/6; .0005 6/-; .00075 7/6	<b>DIAL &amp; KNOBS</b> , 7d., 10d., 1/-
<b>FILAMENT RESISTANCE</b> 7 ohms .. .. . 1/6	<b>SWITCH ARM</b> , 1st quality .. .. . 9d.
'Phones, 4,000 ohms .. .. . 12/6	<b>TRANSFORMERS H.F. PLUG-IN TYPE</b> . Ranges from 150 to 5,000.
<b>L. F. TRANSFORMER</b> Energo .. .. . 12/6	<b>COIL HOLDERS</b> . 3/8, 4/8, 5/- & 6/- each.
<b>VARIOMETER</b> .. .. . 2/6	1 way .. .. . 1/-
	2 " .. .. . 4/-
	3 " .. .. . 5/6

Ask for our price list C. of British Made Components and you will save money.

Mail Orders Only. Postage 1d. in the 1/-. Special Terms to the Trade.

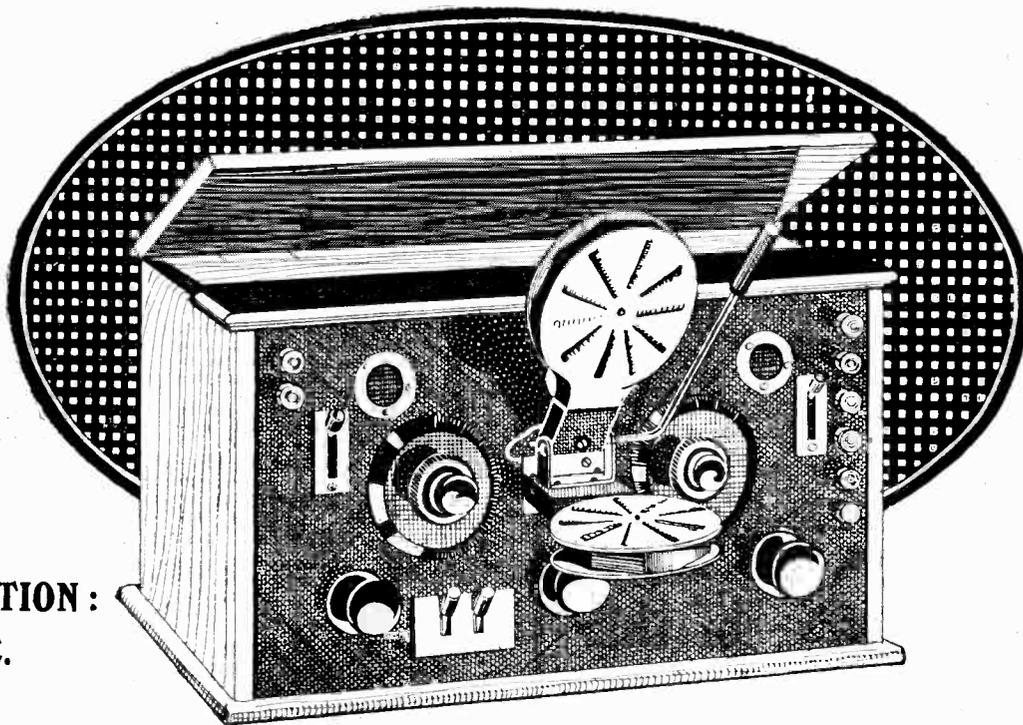**RADIO MAIL ORDER CO.,**  
5, UPPER CHARLES STREET, LONDON, E.C.



DATE OF  
PUBLICATION:  
7th JUNE.

# The Famous All-Concert Receiver

—designed by Percy W. Harris (Assistant Editor of this Magazine)

THE All-Concert Receiver was described in one of the first Constructional Articles ever written for MODERN WIRELESS by Mr. Percy W. Harris.

From the very beginning its undoubted merits—it was one of the earliest 3-Valve Sets—gripped the imagination of wireless enthusiasts and a very large number built it up and got excellent results.

Here, however, is the first opportunity of seeing it in its new guise—that of a superlative Receiving Set, beautifully designed and made up with plated fittings into a polished mahogany cabinet—truly an aristocrat among Sets and fit for any drawing-room.

This Receiver is astonishingly sensitive yet very simple to handle—to its credit stands a formidable list of Stations heard in North London on an average aerial—commencing with all the B.B.C. Stations (London, of course, in immense volume on a Loud Speaker) and continuing with all the better known Continental Stations and also KDKA—the well-known American Broadcasting Station, which operates on 100 metres.

The secrets of its construction are now available to all who purchase the Envelope containing full details, wiring diagrams, blue prints, etc.

If you are contemplating building a good all-round Set you can't beat the All-Concert de-luxe.

Published by Radio Press, Ltd., and sold by all Booksellers

# 2/6


or post free direct, 2/9.

## How to build the All-Concert de-luxe Receiver

RADIO PRESS  
Envelope  
Series No. 4.



G.A. 583

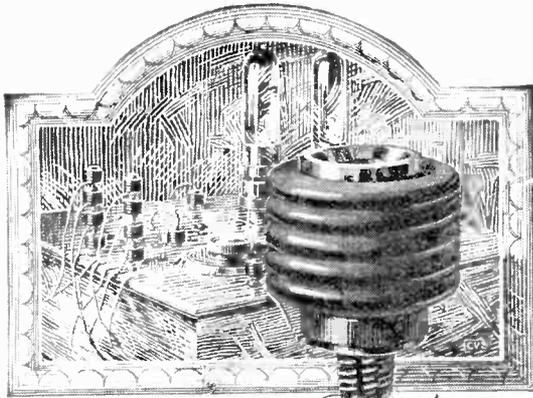

# CLIX

The Electro-link with 159 USES

The introduction of this ingenious combination wonder-plug and socket marks the advent of a standardised system of instantaneous wiring.

These inexpensive universal contacts embrace every utility of terminals, plugs and switches, which they entirely supersede.

Obtainable from all high-class Wireless Dealers or direct from the Patentees and Manufacturers:

**AUTOVEYORS, LTD**  
Radio Engineers and Contractors  
84, VICTORIA STREET, LONDON, S.W.1.

- RETAIL PRICES**
- CLIX... 3d. each.
  - Bushes (six colours) ... 1½d. pair.
  - Insulators (six colours) 1d. each.
  - Locknuts... ½d. each.
  - CLIX with bushes and locknut 4½d. each.
  - CLIX with insulator and locknut ... 4d. each.
  - CLIX is patented all over the world.



## YOU CAN earn more money

Don't allow hesitation or doubt to keep you back from the bigger pay and the better things that will be yours when you have qualified for them. You CAN—you WILL—earn more money when you know more about your calling.

All the world now agrees that a specialised vocational training is necessary to success. The question for the ambitious man who is desirous of something much better in life than he now enjoys is, How can I obtain the training that will raise me above the crowd? Here's the answer: From the International Correspondence Schools.

This institution originated spare time training by post. It is by far the largest organisation of its kind in the world. It has teaching centres in eleven countries and students in fifty. 1,000 British I.C.S. Instruction Papers—specially prepared for correspondence tuition—are marvels of clearness, accuracy and practical helpfulness.

Make up your mind now that you will find out at once what I.C.S. salary-raising training can do for you. As a first step—

**USE THIS COUPON.**

**INTERNATIONAL CORRESPONDENCE SCHOOLS, LTD.,**  
94, International Building, Kingsway, London, W.C.2.

Please send me your booklet containing full particulars of the Course of Correspondence Training before which I have marked X. I assume no obligation.

- |   |  |  |
|---|--|--|
| <input type="checkbox"/> Accountancy    | <input type="checkbox"/> Draughtsmanship           | <input type="checkbox"/> Shorthand Typewriting |
| <input type="checkbox"/> Advertising    | <input type="checkbox"/> Engineering, all Branches | <input type="checkbox"/> Showcard Writing      |
| <input type="checkbox"/> Architecture   | <input type="checkbox"/> French and Spanish        | <input type="checkbox"/> Textiles              |
| <input type="checkbox"/> Book-keeping   | <input type="checkbox"/> Plumbing                  | <input type="checkbox"/> Wireless Telegraphy   |
| <input type="checkbox"/> Building       | <input type="checkbox"/> Professional Exams.       | <input type="checkbox"/> Woodworking           |
| <input type="checkbox"/> Commercial Art | <input type="checkbox"/> Salesmanship              |  |

State which .....

The I.C.S. teach wherever the post reaches, and have over 300 Courses of Study. If, therefore, your subject is not in the above list write it here.


Name ..... Age.....  
Address .....

Perfectly simple and simply perfect
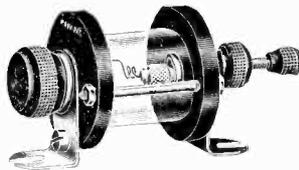
## THE MIC-MET SUPER CRYSTAL DETECTOR

(PROV. PATENT 22153).

This instrument is micrometrical in principle and ensures a perfectly adjusted and rigid contact between crystal and contactor. By a combination of movements between the three knobs, any portion of the exposed part of the crystal may be contacted. For S.T. 100 and other circuits employing crystal rectification, the most efficient detector to use is the MIC-MET. Can be obtained from your local wireless dealer or direct from the manufacturers on receipt of 6s. P.O. Trade enquiries solicited.




British Make

C. & J. ARRIGONI & CO., LTD., COMPTON PASSAGE, CLERKENWELL, LONDON, E.C.1
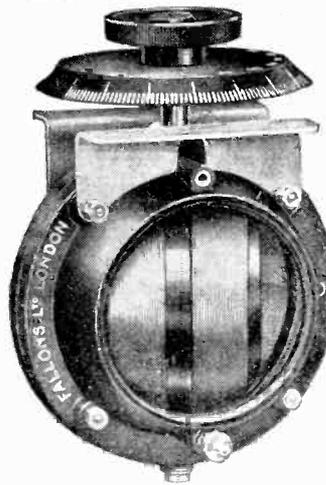
### CABINETS YOU WANT

PICKETT'S Cabinets—they're good value, from 1/6 each, highly polished. Cabinet Works, Albion Rd., Bexley Heath, S.E.1. Write for Lists M.W.



## FALLON'S VARIOMETER

ONLY 10/- Originally sold at 15/- Now sold at only 10/-

You benefit by the Enormous Demand for Fallon Products.

On this line alone you are saved 33 1/3 per cent. Quality exactly as fine as before.

The finest Variometer on the market at ANY price. Inside winding. Suitable for broadcast reception on any P.M.G. Aerial, extraordinary close coupling, ensuring large tuning range. On a 30 ft. indoor aerial the max. wavelength exceeds 420 metres and the min. on a 100 ft. aerial is below 350 metres. The max. on a full size outdoor aerial is 700 metres and the min. on a 30 ft. is 200 metres. Inductance, the highest possible—9.5 to 1. Metal feet can be adjusted to four different positions. Reduced Price Now 10/-.

For particulars of our Condensers we refer you to our advertisement in the May issue of MODERN WIRELESS.

### NEW FALLON CONDENSER with combined Vernier.

This condenser can be had in both styles of our A.II. model, with either moulded or Aluminium ends. Prices:—001, 10/6, 00075, 9/6, 0005, 8/6, 0003, 8/-, 00025, 7/6, 0002, 7/-.

#### FOREIGN AND COLONIAL AGENCIES.

- Australia: The Westralian Farmers, Ltd., PERTH, W.A.
- South Africa: G. D. Henderson & Co., 75, Timber Street, MARITZBURG, Natal; Stuttaford & Co., Ltd., JOHANNESBURG and CAPE TOWN.
- Sweden: Graham Bros., Stockholm
- Holland: De Witt Sidee & Co., 182, De Carpenter St., The Hague
- SCOTTISH DEPOT, 120, WELLINGTON STREET, GLASGOW.

Write direct for trade terms.

## FALLON CONDENSER CO., LTD.

"The Condenser People,"  
Phone: Tottenham 1932.

WHITE RIBBON WORKS,  
Broad Lane, N.15.

### Fynetune VERNIER ADJUSTER

The latest and most efficient device for giving finest possible adjustment to any Condenser or Variometer.


ONE HOLE FIX. **26** POST FREE GETS THE DISTANT STATIONS

**SPARKS RADIO SUPPLIES**  
43 Gt PORTLAND ST LONDON W

STOCKED BY MOST LIVE WIRELESS DEALERS

In replying to advertisers, use COUPON on last page

Date of Publication: 7th June.

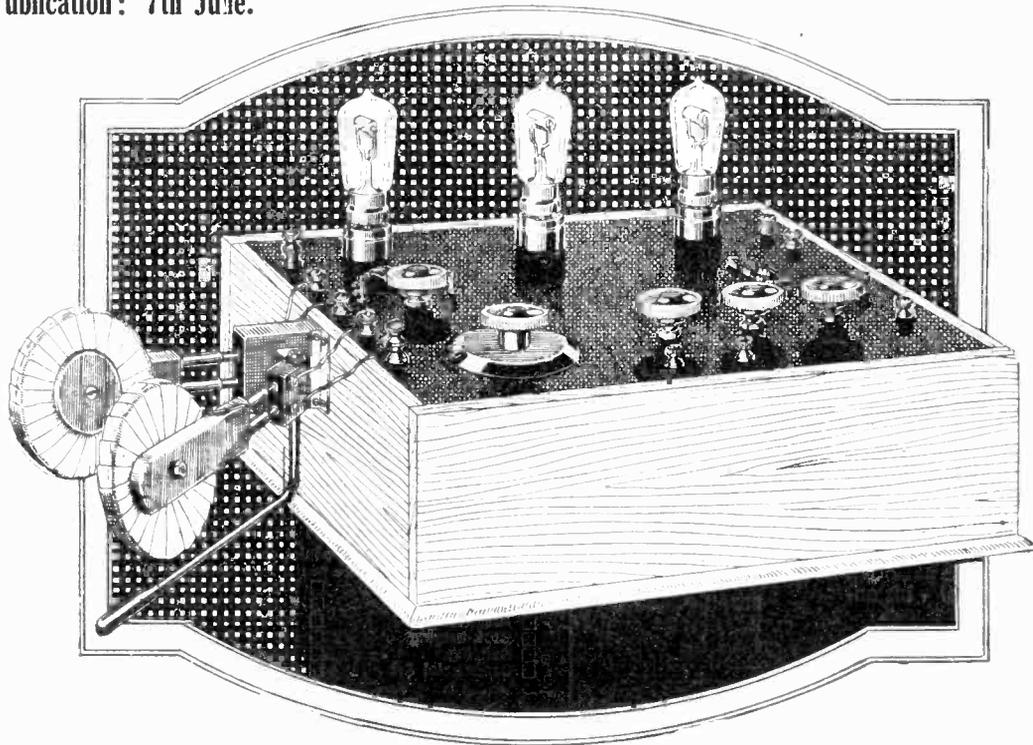

## All the B.B.C. Stations on one knob—

THE usual three-valve Receiver presents rather a difficult problem in tuning (to obtain the best results) to the beginner. Almost invariably there are two condenser dials to be rotated simultaneously and coils to be adjusted. The 'old hand,' of course, makes light of such difficulties, but to the novice, undoubtedly they are certainly quite formidable.

The Set shown above, although using one stage of H.F., is tuned entirely by one variable condenser and one switch and has been designed throughout to give the best results with the greatest possible ease. At the same time, however, simplification in design has also resulted in marked economy in outlay. Any experimenter can now build this splendid 3-Valve set under the new Radio Press Envelope

System at a total cost of but £3 to £4 (excluding Valves and accessories, of course) using the best components. This Receiver covers all wavelengths—for 1,000 metres and under it uses a tapped anode coil and for above 1,000 metres it uses resistance coupling—and any Station is immediately found by setting the switch and tuning on one variable condenser.

If required the L.F. Valve can be cut out instantly by means of a switch. Why not make up this efficient Set, designed by a member of our own Editorial Staff, and which has received all B.B.C. Stations in London—three of them on an indoor aerial. If you have hitherto been afraid to build up a multi-valve Set here is just the Receiver you should build—order a copy from your Bookseller to-day.


RADIO PRESS LTD., DEVEREUX COURT, STRAND, W.C.2.

Envelope No. 3 contains blue prints showing panel lay-out (front and back) and full wiring diagram together with the most explicit instructions for assembly. It is practically impossible for even the most complete novice to go wrong in building up this Set. Photographs showing finished instrument in different positions also included.

2/9, post free.

# How to build the "Simplicity" 3 Valve Set

## Radio Press Envelope No. 3.

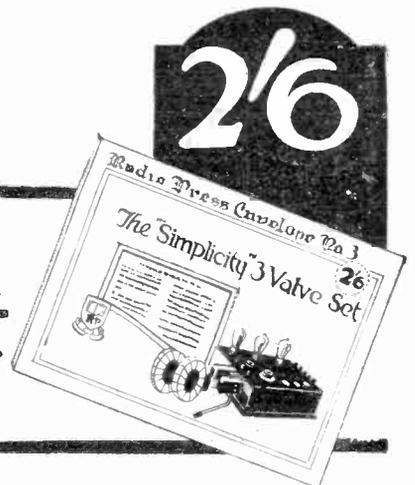



Don't worry  
it out yourself  
—let an expert  
help you

PERHAPS you have built a Set and you cannot get it to work—don't worry, let a Radio Press expert help you. Probably you have made some little slip in the Circuit—maybe you have misread the wiring instructions. All you need is a copy of

## Pictorial Wireless Circuits

By Oswald J. Rankin.  
(Radio Press Series No. 8.)

This Book contains scores of different Circuits, each one of which is shown in pictorial form instead of the more technical diagrammatic manner.


Thousands of beginners have bought it and have been able to appreciate for the first time how easy it is to wire up a Set when the Circuit diagram is understood.

No matter which type of Set you are building, whether Crystal or multi-valve, and whichever type of tuning you will use, variometer or plug-in coils, you will find a wide variety of practical circuits shown in a manner even the veriest novice can readily understand.

From all Booksellers or sent post free 2d. extra direct from Publishers. **1/6**

**Radio Press Ltd**  
PUBLISHERS OF AUTHORITATIVE WIRELESS LITERATURE  
DEVEREUX COURT, STRAND, W.C.2

G. A. 865

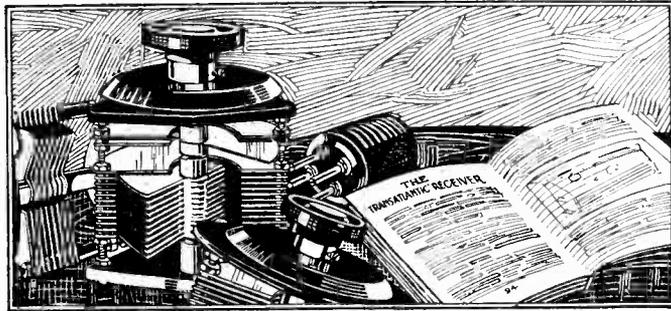

# The Aristocrats

TYPES FOR EVERY  
PURPOSE.

There is a Bowyer-Lowe Square Law Condenser for every wireless occasion. Standard, Double and Vernier types are in stock in the usual capacities. Special capacities can be made to order. In the double type, the two halves are guaranteed accurately matched. In the vernier type accurate setting of both vernier and main portion is always a simple matter because the main portion is always engaged in the same position relatively to the vernier.

POINTS ABOUT  
THEIR QUALITY.

Dials of Blackened Brass to obviate hand capacity effects. Soldering lugs on all models. Positive rubbing contact to moving plates adjustable for pressure, resulting in very low resistance.

FOR PORTABLE SETS.


Where weight is a consideration Bowyer-Lowe Square Law Condensers are a big help. A smaller condenser will yield a given wavelength range equal to that of a larger condenser of the ordinary type.

OBTAINABLE from all good dealers. In case of difficulty write direct.

# Bowyer-Lowe SQUARE LAW CONDENSERS

Write now for our Brochure which explains exactly why these Condensers will add greatly to the efficiency of any Wireless Set to which they are fitted.

BOWYER-LOWE CO. Ltd., LETCHWORTH

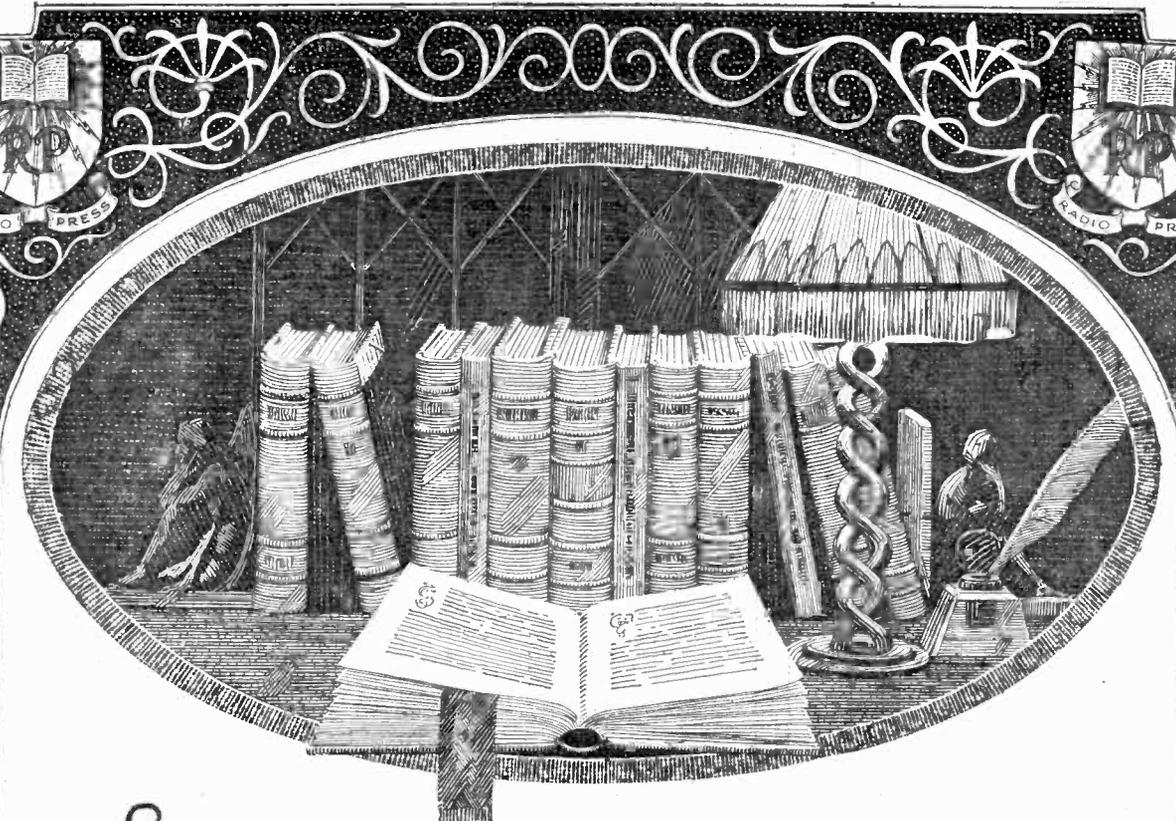

## Stepping stones to success

THE wonderful popularity of Radio is due in no small measure to the wide variety of its appeal.


To some it offers exceptional facilities for enjoying the world's best music—to others it permits the development of latent manual skill—while not a few are intrigued by its unexplained mysteries.

All classes of Radio enthusiasts find in the Radio Press Library an unequalled opportunity for satisfying their desires for high-grade informative Books on every branch of the Science.

	Price		Price
1 Wireless for All ... ..	9d.	14 12 Tested Wireless Sets... ..	2/6
By John Scott-Taggart, F.Inst.P.		By P. W. Harris.	
2 Simplified Wireless ... ..	1/-	15 More Practical Valve Circuits... ..	3/6
By John Scott-Taggart, F.Inst.P.		By John Scott-Taggart, F.Inst.P.	
3 How to Make your own Broadcast Receiver	1/6	16 Home-Built Wireless Components ...	2/6
By John Scott-Taggart, F.Inst.P.		17 Wireless Sets for Home Constructor ...	2/6
4 How to Erect Your Wireless Aerial ...	1/-	By E. Redpath.	
By B. Mitchell, A.M.I.E.E.		18 Tuning Coils and How to Wind Them... 1/6	
5 The Construction of Wireless Receiving Apparatus ... ..	1/6	By G. P. Kendall.	
By P. D. Tyers.		RADIO PRESS ENVELOPES.	
6 The Construction of Crystal Receivers... 1/6		No. 1. How to Build an S.T. 100 Receiver	1/6
By Alan L. M. Douglas.		By John Scott-Taggart, F.Inst.P.	
7 How to Make a "Unit" Wireless Receiver ... ..	2/6	No. 2. How to Build a 4-Valve Receiver... 2/6	
By E. Redpath.		By P. W. Harris. Ready 7th June.	
8 Pictorial Wireless Circuits ... ..	1/6	No. 3. How to Build a "Simplicity" 3-Valve Set ... ..	2/6
By Oswald J. Rankin.		By G. P. Kendall, B.Sc.	
9 Wireless Valves Simply Explained ... 2/6		No. 4. How to Build the All-Concert De Luxe Receiver ... ..	2/6
By John Scott-Taggart, F.Inst.P.		By P. W. Harris.	
10 Practical Wireless Valve Circuits ... 2/6		SIMPLEX WIRING CHARTS.	
By John Scott-Taggart, F.Inst.P.		No. 1. For 2-Valve Set ... ..	1/-
12 Radio Valves and How to Use Them... 2/6		No. 2. For 3-Valve Set ... ..	1/-
By John Scott-Taggart, F.Inst.P.		No. 3. For 4-Valve Set ... ..	1/-
13 500 Wireless Questions Answered ... 2/6			
By G. P. Kendall & E. Redpath.			

From all Booksellers, or post paid 2d. per book extra direct from Publishers.

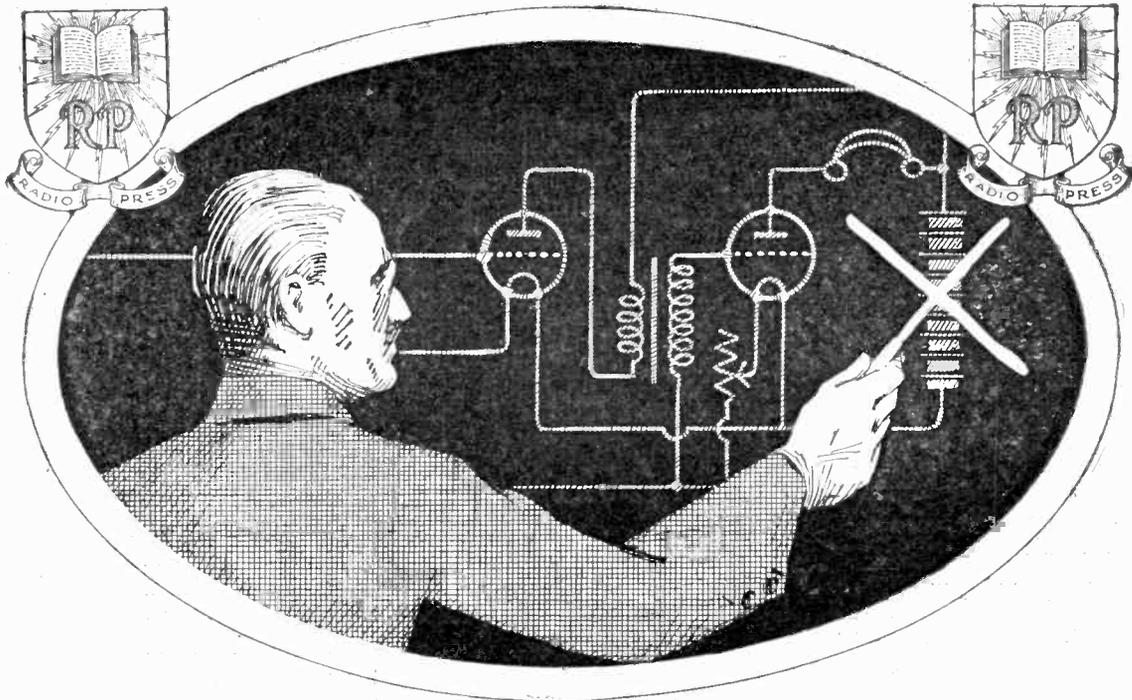RADIO PRESS Ltd.—the Largest Wireless Publishers in the World—  
Devereux Ct., Strand, W.C.2.



# High-tensionless Receiving Sets.

— read "Wireless Weekly" for fullest constructional details of Sets using ordinary Valves without H.T. Batteries

IF you are interested in sound technical research you must not fail to read the next few issues of WIRELESS WEEKLY which will deal specially with the question of the H.T. Battery and the possibility of its elimination. Commencing June 4th Mr. Percy W. Harris (assistant Editor) will describe the construction of a Receiving Set which permits remarkable results (employing a new Circuit) with the ordinary 3-electrode Valve which every one has. Obviously these articles will arouse great interest because it will be the first time that any enthusiast will be given the opportunity of experimenting with the ordinary apparatus he already possesses, instead of having to purchase more expensive 4-electrode Valves. On no account should you miss these

issues and in view of the anticipated heavy demand you will be well advised to place an order with your Newsagent at once. Remember WIRELESS WEEKLY is published by the largest technical wireless staff in the country, and its views are accepted as being dependable and accurate. If you are not yet a regular reader you will be surprised at its generous size, clear cut illustrations and intelligent far-seeing articles. Certainly no other publication in the country can approach it either in appearance or its remarkable value for money. In the adjacent column is given a selection of the constructional articles which have appeared in the last few issues—those in preparation will be quite as attractive.

Radio Press Ltd., Devereux Court, Strand, W.C.2.

## Some exceptional Constructional Articles.

Wireless Weekly has always been famed for its thoroughly practicable Constructional Articles—here are a few taken at random from recent issues. Copies are available on application to Radio Press Ltd., and will be sent post free for 7½d. each.

- "A Simple Short-Wave Receiver." By G. P. KENDALL, B.Sc. (Feb. 6th, 1924.)
- "A Practical Neutrodyne Receiver." By ALLAN T. HANSCOM. (Feb. 13th, 1924.)
- "A Wavemeter on the Buzzer Principle." By G. P. KENDALL, B.Sc. (Feb. 27th, 1924.)
- "A Cabinet Three-Valve Receiver." By HERBERT SIMPSON. (Feb. 27th, 1924.)
- "The Omni-Circuit Receiver." By JOHN SCOTT-TAGGART, F.INST.P. (Issues of Feb. 20th and 27th and March 5th.)
- "A Power Amplifier." By G. P. KENDALL, B.Sc. (March 12th, 1924.)
- "The W.2 Receiver (a Selective Two-Valve Set)." By HERBERT SIMPSON. (March 12th and 19th, 1924.)
- "A Capacity-Reaction Three-Valve Receiver." By STANLEY G. RATTEE. (March 26th, 1924.)
- "A Double Reaction Receiver." By STANLEY G. RATTEE. (April 16th, 1924.)
- "An Improved S.T. 100 Receiver." By JOHN SCOTT-TAGGART, F.INST.P. (April 23rd, 1924.)
- "The Reinartz All-Wave Tuner." By JOHN L. REINARTZ. (May 21st, 1924.)

All these articles are complete with photographs, wiring diagrams, and the fullest details to enable anyone to build exact replicas of the sets described.

Every Wednesday  
From all Newsagents.

6d.

# Wireless Weekly

## Index to Advertisers

PAGE		PAGE		PAGE
86	Adams Bros. (Longton) Ltd. ...	99	Formo Co. ...	90
72	Agar (W. H.) ...	89	Fuller's United Elec. Works, Ltd. ...	101
103	Arrigoni, C. & J. ...	96	Gamage, A. W. ...	89
103	Autoveyors, Ltd. ...	96	Gambrell Bros., Ltd. ...	95, 98
99	B. D. & Co. ...	41	General Electric Co., Ltd. ...	103
105	Bowyer-Lowe Co. ...	54	General Radio Co. ...	70
42	Brandes, Ltd. ...	94	Gent & Co. ...	69
99	British Battery Co., Ltd. (The)...	73	Goswell Engineering Co. ...	76
61	Brown Brothers Ltd. ...	84	Graham (A.) & Co. ...	Cover iv.
58	Brown (S. G.), Ltd. ...	49	Gran-Goldman Service ...	101
93	Burndept, Ltd. ...	65	Gresham Publishing Co. ...	76, 80
90	Burne-Jones, Ltd. ...	90	Helixo, Ltd. ...	84, 85
50	Chloride Elec. Storage Co. Ltd. ...	75	H. T. C. Electrical Co. ...	74, 86
62	Clarke (H.) & Co. (Manchester), Ltd. ...	76	Humphrys, W. E. H. ...	90
100	Cossor Valve Co. ...	101	Hunt (A. H.), Ltd., ...	90
61	Cunningham & Morrison ...	79	Igranic Electric Co., Ltd. ...	80
75, 86	Curtis (Peter), Ltd. ...		International Correspondence	96
49, 72	Diamond Wireless, Ltd. ...	103	Schools ...	103
98	Dicker & Pollak ...	65	Jackson Bros. ...	65
61	Drummond Bros. ...	96	Joanes (W.) ...	96
57	Dubilier Condenser Co. (1921), Ltd. ...	98	Levy, S. ...	98
76	Economic Electric, Ltd. ...	45, 53	Lissen Co. ...	45, 53
46	Edison Swan Electric Co. Ltd. ...	99	London Telegraph Training College ...	99
66	Electric Appliances, Ltd. ...	75	Marconi Wireless Telegraph Co., Ltd. ...	75
103	Fallon Condenser Co. ...	76	Macdonald (J.) & Co. ...	76
95	Fellows Magneto Co., Ltd. ...	94	McMichael (L.), Ltd. ...	94
108	Finchett (C. A.)... ...	82	M. L. Magneto Syndicate ...	82
			Molback (H.) ...	90
			Moore & Griffiths ...	101
			Mullard Radio Valve Co., Ltd. ...	89
			Peto-Scott Co. ...	95, 98
			Pickett Bros. ...	103
			Power Equipment Co. ...	70
			Radio Communication Co., Ltd. ...	69
			Radio Improvements ...	76
			Radio Instruments, Ltd. ...	Cover iv.
			Radio Mail Order Co. ...	101
			Radions, Ltd. ...	76, 80
			Raymond (K.) ...	84, 85
			Robinson (Lionel) & Co. ...	74, 86
			"S. A. Cutters" ...	90
			Silvertown Co. ...	80
			Simpson & Blythe ...	96
			Smith & Ellis ...	90
			Sparks Radio Co. ...	103
			Stella-Works Co. ...	70
			Sterling Telephone Co., Ltd. ...	49
			Tickle (L. B.) & Co. ...	82
			Ward & Goldstone, Ltd. ...	97
			Watmel Wireless Co. ...	86
			Wates Bros. ...	92
			Willesford ...	98
			Woodhall Wireless Co. ...	57
			Wright & Palmer ...	90



**100% EFFICIENCY H.T. BATTERY**

See editorial report, April issue, page 640, also page 657. Giant Unit Dry Cells, Wt. 3 ozs. Compare standard cells on photo. 4/- doz. 60 o/t (vps) in polished Oak B.x. 19/6. Carriage 1/9. Direct from maker, saving 50 per cent.; full details free. Sample cell 6d. Orders in rotation.

Sole Maker:  
**FINCHETT (C. A.), OLD ARMOURY, OSWESTRY.**

**EBONITE PANELS**

Any size cut, 1/4" thick, 1d. for a sq. in.; 3/16" thick 1d. for a sq. in.; 1/2" thick, 1d. for 1 sq. in. Panels drilled any circuit, 6d. Post and packing, 6d.  
**WORMALD & SON, MANCHESTER STREET,**  
Bradford Rd. Manchester. Phone, Central 2868

**WIRELESS PROFESSION.** — Immediate vacancies for number of students from 14 years of age upwards; those just leaving school preferred; appointments guaranteed when qualified; commencing salary £150 per annum plus all found, rising to £500 per annum, according to number of years' service. Prospectus free.—Wireless College, Lansdowne, Bournemouth.

# COUPON

## Questions and Answers

In future this coupon must be accompanied with 2s. 6d. P.O.

"MODERN WIRELESS" June, 1924

## USE THIS COUPON

in writing to advertisers in "Modern Wireless."

CUT HERE

In connection with your announcement in MODERN WIRELESS, please supply me with:


Enclosed please find remittance of.....  
(Leave blank if not an order)

If an open envelope is used in applying for catalogues a half-penny stamp will cover postage.

Name.....

Address.....

Date.....

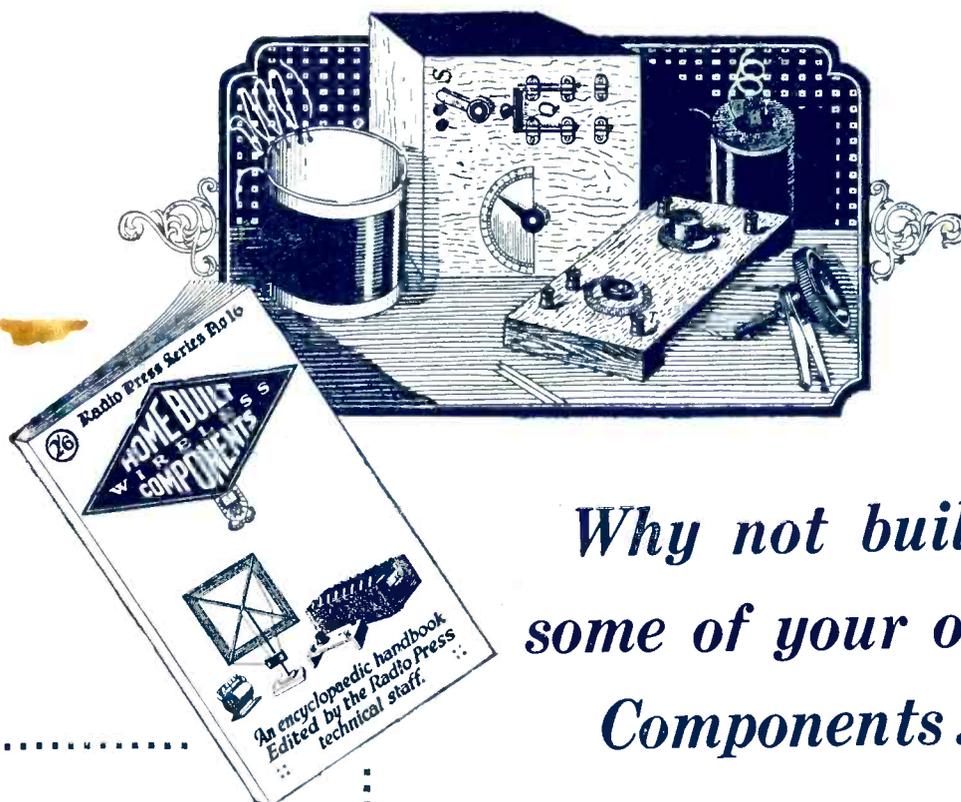

## Why not build some of your own Components?

**This Book  
shows you how to build:**

Frame Aerials of different types.  
Various types of Coils.  
Coil Holders and Tuners.  
Crystal Detectors.  
Grid Leaks.  
Fixed and Variable Condensers.  
High Frequency and Low Frequency Transformers.  
Switches of various types and sizes.  
Valve Panels.  
Resistances.  
Potentiometers and Rheostats.  
Wave Meters, etc.

THE man who takes pleasure in building every component in his Set will obtain a lot of information from this Radio Press Book, *Homebuilt Wireless Components*. It gives a vast amount of information on how to make such components as those shown on the accompanying list. And every article, if made according to the directions, has been actually made up and tested. Most of them are illustrated where necessary with working drawings, so that there should be no difficulty in building them up.

Considering the immense scope of the Book and the fact that more than 130 illustrations are given, its cost is most moderate and will be saved by the first component made up.

**RADIO PRESS, LTD.,**  
Devereux Court, Strand, W.C.2.

2/6

# Homebuilt Wireless Components

## Radio Press Series No. 16.

# Breakdown!



Our 50 page Catalogue  
free on request.

25/-

**I**NFERIOR workmanship makes itself evident sooner or later—usually accompanied by disaster. In every field of production the value of discrimination when purchasing is becoming a vital consideration. Safeguard yourself against breakdown or burning out by purchasing the highest standard in materials, design and finish. The **R.I.** Transformer fulfils these requirements to such a degree that its use has become standard all over the world. Wireless Engineers and Experimenters *know and obtain the best*—that is why they stipulate **R.I.** Transformers.

## RADIO INSTRUMENTS LTD.

Managing Director: J. JOSEPH, M.I.E.E.  
Chief Designer: W. A. APPLETON, M.B.E., M.I.R.E. (late Admiralty Technical Research Officer).  
Works, Offices and Showrooms:

**12, Hyde Street, New Oxford Street, W.C.1.**  
Telephone: Legent 6214-6215-6216. Telegrams: "Instradio London."

### PROVINCIAL DEPOSITS.

- Manchester: 19, Hopwood Avenue.
- Dundee: Caird Hall, Dock Street.
- Dublin: Brown Bros. (Ireland) Ltd., 18, William Street.
- Leeds: Trinity House, Commercial Street.
- Brussels: Trent Livres & Zuaab, 24, Rue de Malines.
- Belfast: Campbell, Cardner & Co., 44, Upper Arthur Street.
- Birmingham: Britannia Works, Gt. Charles Street.
- Glasgow: 47, Waterloo Street.



Printed by ODHAMS PRESS LTD., Long Acre, London, W.C. 2, and published on the 1st of every month at 3, Bolt Court, Fleet Street, London, E.C. 4, by the Proprietors, RADIO PRESS LIMITED, Devereux Court, Strand, W.C. 2. Subscriptions and editorial communications to go to latter address. Advertisement Offices: Scheff Publicity Organisation, Ltd., 125, Pall Mall, London, S.W. 1. Registered as a Magazine for transmission by Canadian Magazine Post. Sole Agents for Australasia: Gordon & Gotch (Australasia), Ltd. Sole Agents for South Africa: Central News Agency, Ltd.—June, 1924.