PRACTICAL

Australia 85c New Zealand 85c

South Africa 80c Malaysia \$2.75

# ELECTRONICS

DECEMBER 1978

50p


# GUITAR SOUND MILLTIPROCESSOR

SPECIAL OFFER!
10+10
AMPLIFIER
KIT £12-50
INCLUSIVE



FREE

CHROMOSONICS 24 CATALOGUE WORTH 40 PENCE

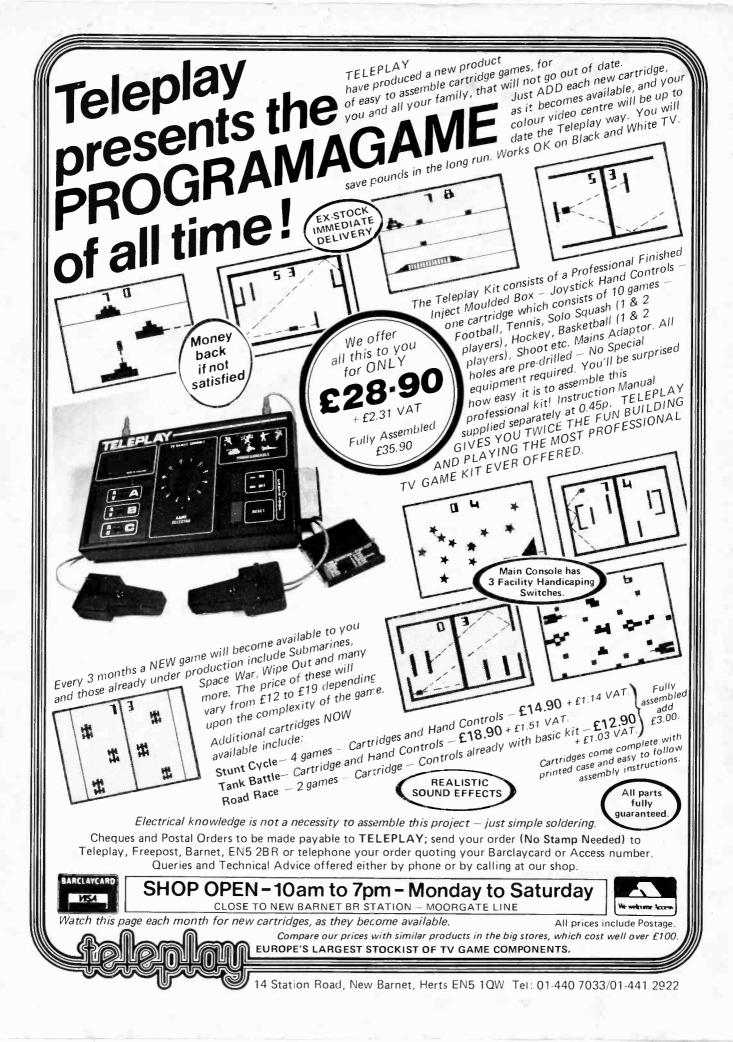

# ELECTRONICS

VOLUME 14 No. 16 DECEMBER 1978

CONSTRUCTIONAL PROJECTS P.E. V.D.U. SYSTEM—2 by A. A. Berk, B.Sc., Ph.D.	
g, orporang the second research	228
ANALOGUE COMPUTER—4 by P. J. Kronis, B.Sc. Programming and special circuits (conclusion of series)  12	236
SAFETY PLUG by T. Sutherns	
	240
GUITAR SOUND MULTIPROCESSOR—1 by M. A. Sawicki M.Sc.(Eng.) and A. Kowalewski Pre-amp, delay block and summers 12	246
RADIO CONTROL FAILSAFE by A. Jenkins	
the real or demogration	260
R.C. MOTOR CONTROL by P. A. Dakin Full Power solid state controller	262
GENERAL FEATURES	
FARNBOROUGH '78 by P. Preston Avionics' latest gear 12	234
MICROBUS by D.J.D.	
A bi-monthly focus on micro's for the home constructor  IMPEDANCE—2 by Toby Bailey and Bob Whitaker	252
	257
INGENUITY UNLIMITED	
Binary to 7-Segment Decoder—Sub-Octave Generator—Combination Lock—One Arm Bandit Mod—Coincidence/Error Detector—CMOS Burglar Alarm	266
SEMICONDUCTOR UPDATE by R. W. Coles	
A look at some recently released devices	270
NEWS AND COMMENT	
EDITORIAL 12	227
MARKET PLACE New products 1:	231
NEWS BRIEFS	
Wildloof Wildlo Olds Late Hight Flowing	239
Hey! 64K! POINTS ARISING	265
	241
SPACEWATCH by Frank W. Hyde	
USSR and Venus, Meteorites, New Planetoid, 100 Days in Orbit, Communications Satellites, Landsats Survey the Sea, Space Facts, Design for a Man-Made City in Space 1.	242
	245
READOUT	
	254
INDUSTRY NOTEBOOK by Nexus What's happening inside industry 12	271
PATENTS REVIEW	
	272
	278 278
Our January issue will be on sale Friday, 8 December 1978	

Our January issue will be on sale Friday, 8 December 1978 (for details of contents see page 1259)

© IPC Magazines Limited 1978. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

# 1-The Connoisseur's Budget Choice





The Connoisseur BD1 transcription turntable is a precision engineered product designed to provide top grade performance at a moderate cost. Simplicity is the main feature of this unit giving excellent performance and reliability.

A slow speed synchronous motor is used and because of its construction the hum field is very low, so that even the most sensitive of pickups can be used, including the Connoisseur SAU2 or the SME 3009 Series II.

Speed change is achieved by a press button unit at the rear of the platform which automatically moves the drive belt from one pulley groove to the other whilst the turntable is turning. The BD1 turntable kit can be assembled by the home constructor within the hour and when completed will give top quality performance. No soldering is required. Complete the unit with a modern BD1 plinth and cover. The plinth is finished in walnut veneer and fitted with spherical, anti-vibration feet. Add to this a strong Acrylic, bronze cover, hinged with 2-position lid stay and you have a first class turntable at a budget price!



Write for further details to: A. R. Sugden & Co. (Engineers) Ltd. Manufacturers of Connoisseur Sound Equipment, Connoisseur Works, Atlas Mill Road, Brighouse, West Yorkshire HD6 1ES Telephone: Brighouse (0484) 712 142, Telex: 517144 Sugden Crighouse, Telegrams & Cables: Connoisseur Brighouse.

# We can help you See and Solve your problems



# HONELIGHT

Universal Portable Inspection Light The shadowless Honelight utilises the principle of optical fibres, in a tube of virtually unbreakable material, insulated, transparent and resistant to alcohol.

It gives all-round illumination to otherwise inaccessible confined spaces and corners. Simple, lightweight and practical (weight with batteries 40 grammes approx.). Suitable for all professions—Electronics, Radio/TV-machines of all types.

Also useful in the realm of Medicine: general and specialised, Dentistry, Veterinary etc. (Operates from 2-1-5 volt batteries).

# Desoldering Tool "SPECIPROD"

High precision manufacture de-soldering pump. Available three sizes for all de-soldering requirements.

Chromed interior, nickel pump, teflon nozzle.

Three Sizes.

"Maxi Super" length 37cm, nozzle diameter 2mm.

"Maxi Mini" length 22cm, nozzle diameter 1.5 mm.

"Maxi Micro" length 16cm (diameter body 12mm, nozzle diameter 1.5mm). (The smallest de-soldering pump available)

Literature and general catalogue available on request from

Special Products Distributors Limited, 81 Piccadilly, London W1V 0HL

# E SUSTAIN UNIT (P.E. OCTOBER 1977)



BUILD A SUSTAIN UNIT EQUAL TO THE **BEST COMMERCIAL MODELS** 

COMPLETE KIT - £7.95\* ALL HIGH QUALITY COMPONENTS AS SPECIFIED.

DESIGNER APPROVED.



ORION

Complete set of semiconductors LP1186 Tuner Head

£4.99 £9.60

Glass fibre PCB, printed with component

£2.45

amplifier

Complete set of semiconductors Glass fibre PCB, printed with component locations

£9.40 £3.50

FERRANTI Semiconductors

# **BUY FROM THE SPECIALISTS!**

We can supply any Ferranti semicanductor device at very competitive prices. Send SAE for our data sheet & price list.

ONE BOOSTER (Everyday Electronics Sept. 1978)

The Tone Booster cuts out that dead, muddy sound and brings your guitar to life! Emphasises harmonics without reducing the low notes to give your guitar a clean penetrating tone

Complete kit of all parts as specified...

....£3.30\*

PE TV SOUND SEPARATOR

Complete set af semiconductars £2.30. High quality glass fibre p.c.b. £1.00. Murata filters: SFE6.0MA 35p. CDA6.0MC 35p. P & P 15p per order. Orders over £5 post free. All devices are top grade, brand new and to full monufacturer's spec. We do not sell seconds or rejects. Send S.A.E. for our data sheet and price list. Prices do not include VAT—add 8% to items marked\*, and 12½% to all others.

DAVIAN ELECTRONICS (Mail order, callers by appointment only).

13 Deepdale Avenue, Royton, Oldham OL2 6XD

Everyone who works with electricity needs to know at some time or other what's going on inside the cable he's handling. What voltage. What current. What resistance. Not knowing the answers, or worse still having inaccurate answers, can make life difficult, even terminal.

# **Eagle Test Equipment gives the right answers**

The range covers general multimeters, high voltage probes, clamp meters, insulation testers. Here are just four. Send the coupon for details of all the rest.



**KEW 7 Multimeter** 1000 OPV. DC volts up to 1000, DC amps up to 100 mA. AC volts up to 1000. Resistance up to 150 Kohms. Pocket size. "Off" damping. Complete with leads & battery. R.R.P. £6.95 ex. VAT.



EM 1200 Multimeter 100,000 OPV. Taut band movement. Overload protection. Reversible DC polarity. AC amps: 15, AC volts to 1500. DC amps up to 15, DC volts to 1500. Resistance up to 200 megohms. R.R.P. £49.95 ex. VAT.



K1400 Multimeter 20,000 OPV. DC and AC volts up to 5000. DC and AC amps up to 10. Resistance up to 20 megohms. "Off" damping. Overload protection. R.R.P. £68.00 ex. VAT.



EM10, 20 & 30 Multimeters 10, 20 & 30,000 OPV. All with antiparallax mirror scale. DC volts to 1000 (1200 for EM30). DC amps to 250 mA (600 for EM30). AC volts to 1000 (1200 for EM30). Resistance up to 6,5 and 60 megohms respectively. R.R.P.'s EM10 £12.40 EM20 £16.40 EM30 £18.95 ex. VAT.

# Test Equipment: EAGLE



Please send	l me de	etails of	your	compl	lete r	range of	Test Ec	Juipment	

Name Company

Address

EAGLE INTERNATIONAL Precision Centre, Heather Park Drive, Wembley, Middlesex HA0 1SU.

PE1

# REENWE

443 Millbrook Road Southampton Tel:(0703) 772501 SO1 OHX

All prices quoted include VAT. Add 25p UK/BFPO Postage. Most orders despatched on day of receipt. SAE with enquiries please. MINIMUM ORDER VALUE £1. Official orders accepted

from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

## **EXPERIMENTERS** CALCULATOR

Based on the C500 chip, this pack of parts enables the more experienced constructor to make an 8 digit 4 function calculator. The comprehensive data supplied includes ful size layout of PCB required, types of suitable display and keyboard that can be used etc. Components included in the pack are C500 calculator chip, driver IC, all components for inverter/clock circuits, R's C's etc. All for only £3-50.

# **RELAYS**

RELAYS
W847 Low profile PC mntg 10×33×20mm
6V coil, SPCO 3A contacts. 93p
W832 Sub. min type, 10×19×10mm 12V
coil DPCO 2A contacts £1-15
W701 6V SPCO 1A contacts 20×30×25mm Only 56p
W817 11 pin plug in relay, rated 24V ac, but works well on 6V DC. Contacts 3 pole c/o rated 10A. 95p
W819 12V 1250R DPCO 1A contacts. Size 29×22×18mm. min plug-in type 72p
W839 50V ac (24V DCI coil. 11 pin plug in type. 3 pole c/o 10A contacts Only 85p
W846 Open construction mains relay. 3 sets 10A c/o contacts. £1-20
Send SAE for our relay list – 84 types listed and illustrated.

## AMPLIFIER KIT £1.75

Mono gen, purpose amp with tone and Vol/on-off controls. Utilizes sim. circuitry to above amp. Output 2W into 8 ohms. Input matched for crystal cartridge. 4 transistor circuit. Simple to build on PCB provided. Can be either battery or mains operated. (For mains powered version add £2.20 for suit-able transformer.) Blue vinyl covera aluminium case to suit (W372) £1.30

## STEREO AMPLIFIER CHASSIS £5.50

Complete and ready built. Controls: bass, treble, volume/on-off, balance, 8 transistor circuit gives 2 watts per channel output. Just needs transformer and speakers for low cost stereo amp. Suitable metal cabinet (W374) £2.00 – or buy the amp, case and transformer for £10-00 and get DIN speaker sockets and knobs free!!

# **TMS4030 RAM**

4096 bit dynamic RAM with 300ns access time; 470ns cycle time; single low capacitance high level clock i/p; Fully TTL compatible; Low power dissipation. Supplied with data £2:75

# MISCELLANEOUS IC's

Supplied with data if requested, MC3302 quad comp. 120p; 710 diff comp. (T099) 40p; ZN1034E precision timer £2.25; LM711 Dual diff comp 65p; LM1303 dual stereo pre-amp 75p; MC1469R voltage reg £1.50; UPC1025H audio £3.50; 575C2 audio £2.48; TDA2640 audio £2.92; SN75110 dual line driver 70p; MC8500 CRCC gen POA

# **EDGE CONNECTORS**

Special purchase of these 0.1" pitch double-sided gold-plated connectors enables us to offer them at less than one-third of their original list price!

18 way 41p; 32 way 72p; 40 way 90p.

# **HEAT SINK OFFER**

Copper TO5 sink 17mm dia x 20mm. 10 for 40p; 100 for £3; 1000 for £25

# 74 SERIES PACK

Selection of boards containing many different 74 series IC's. 20 for £1; 50 for £2.20; 100 for £4.

# THE NEW 1978-9 GREENWELD CATALOGUE

# **FEATURES INCLUDE:**

- 50p Discount Vouchers
- Quantity prices for bulk buvers
- Bargain List Supplement
- Reply Paid Envelope
- Priority Order Form
- VAT inclusive prices

PRICE 30p + 15p POST

## AIR FRESHENER KIT

As featured in Nov EE. Complete kit inc. case and instructions. Only £7.95 + 55p p & p.

## **BC182B OFFER**

Special Offer for quantity users 1k .035 VAT; 5k .032 VAT. Price negotiable on 10k Approx 70k available.

# DIODE SCOOP!!!

We have been fortunate to obtain a large quantity of untested, mostly unmarked glass silicon diodes. Testing a sample batterevealed about 70% useable devices – signal diodes, high voltage rects and zeners may all be included. These are being offered at the incredibly low price of £1-25/1000 – or a bag of 2500 for £2-25. Box of 100,000 £8. Box of 25,000 £17-50. Box of 100,000 £60.

## **POLYTHENE SHEET**

Size  $36 \times 18''$  200g. Hundreds of uses around the home. 100 sheets for £1.50. Box of 1500 for £19.

# PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4-25

# BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL **HELP YOU**

- \* SAVE ON TIME-No delays in waiting for parts to come or shops to open!
- \* SAVE ON MONEY—Bulk buying means lowest prices-just compare with others!
- \* HAVE THE RIGHT PARTguesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC, BRAND NEW, MARKED DEVICES— SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors, 5%. 10 of each value 22pF to 1000pF. Total 210.

PRICES.

K001 50V ceramic plate capacitors, 5%. 10 of each value 22pF to 1000pF. Total 210. £3.35

K002 Extended range, 22pF to 0.1µF. 330 values £4.90

K003 Polyester capacitors, 10 each of these values: 0.01, 0.15, 0.22, 0.33, 0.47p. 110 altogether for £4.75

K004 Mylar capacitors, min 100V type, 10 each all values from 1000pF to 10,000pF. Total 130 for £3.75

K005 Polystyrene capacitors, 10 each of the form 10pf to 10,000pF. E12 series 5% 160V. Total 370 for £12.30

K006 Tantalum bead capacitors, 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, all 35V; 10/25 15/16 22/16 33/10 47/6 100/3. Total 170 trans for £14.20

K007 Telectrolytic capacitors 25V working, small physical size. 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for £3.50

K008 Extended range, as above, also including 220, 470 and 1000µF. Total 100 for £5.90

K022 Extended range, as above, also including 220, 470 and 1000µF. Total 100 for £5.90


K022 Extended range, total 850 resistors, £6.00

K024 Za sabove but 5 of each value £8.70

TRANSFORMERS
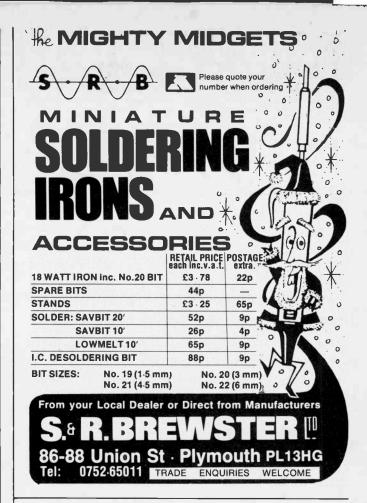
# **TRANSFORMERS**

I HAINS TO HIMER'S
All mains primary: 12-0-12V 50mA 85p; 100mA 95p; 1A £2.50. 6-0-6V 100mA 85p; 1Å £2.40. 9-0-9V 75mA 85p; 1Å £2.10. Mulitapped type 0-12-15-20-24-30V, 1A £3.95; 2A £5.35; 3A £6.90. 20V 2Å £3.90; 25V 1Å £2.25; 12V 8A £4; 24V 5A £7.50; 0-22-34-41V 4A £7.50; 20V @ 300mA twice £2.50; 12V @ 250mA twice £2.00.





# **ELECT**

35 CARDIFF RCAD, WATFORD, HERTS., ENGLAND MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P ADD 30p° TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE.

SEND 45p FOR OUR CATALOGUE.

SEND 45p FOR OUR CATALOGUE.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked \*. To the rest add 12.1%.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday 9.00 am - 6.00 pm. Ample Free Car Parking space evailable.

POLYESTER CAPACITORS: Axial lead type. (Values are in µF) 400V: 0.001. 0.0015, 0.0022, 0.0033 7p; 0.0047, 0.0068, 0.01, 0.015, 0.018 9p; 0.022, 0.033, 10p; 0.047, 0.068 14p; 0.10 15p; 0.15, 0.22 22p; 0.33, 0.47 39p; 0.68 45p. 160V: 0.039, 0.15, 0.22 21 1p; 0.33, 0.47 19p; 0.68 1.0 29p; 1.5 29p; 2.2 32p; DUBILIER: 1000V: 0.01, 0.015 20p; 0.022 22p; 0.047 26p; 0.1 38p; 0.47 48p.

POLYESTER RADIAL LEAD (Values are in µF) 250V: 0-01, 0-015, 0-022, 0-027 5p; 0-033, 0-047, 0-068, 0-1 7p; 0-15 12p; 0-22, 0-33 13p; 0-47 15p; 0-68 18p; 1-0 24p; 1-5 27p; 2-2 31p.

FEED THROUGH CAPACITORS 100µF 350V 8p

2N5777
7 Seg Displays
7 Seg Displays
7 IL312 C An 3" 105
7 IL313 C Cth 3"105
7 IL312 C An 5" 115
7 IL322 C Cth 5" 115
7 IL322 C Cth 5" 115
7 IL707 C A. 3" 99
7 ND357
7 MAN3640
175
LCD 3½ digit 925

SWITCHES\*
TOGGLE 2A 250V
SPST 28p
DPDT 38p
4 pole or/off 54p
SUB-MIN TOGGLE

SUB-MIN TOGGLE
SP changeover
SPST on/off
DPDT 6 tags
DPDT Centre off
DPDT dissed
115p
SLIDE 250V:

52p

41p 45p

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in µF) 500V: 10 40p; 47 68p; 250V: 100 65p; 63V: 0.47, 1.0, 1.5, 2.2, 2.5, 3.3, 4.7, 6.8, 8, 10, 15, 22 8p; 47, 32, 50 11p; 63, 100 27p; 50V: 1.0 7p; 50, 100, 220 25p; 470 50p; 1000, 220 68p; 40V: 22, 33 7p; 330, 470 32p; 1000 49p; 25V: 10, 33 7p; 330, 470 32p; 1000 49p; 25V: 10, 22, 47 6p; 80, 100, 160 8p; 220, 250 13p; 470, 640 25p; 1000 27p; 1500 30p; 2200 41p; 3300 52p; 4700 54p; 16V: 10, 40, 47, 68 7p; 100, 125 8p; 330, 470 16p; 1000, 1500 20p; 2200 34p; 10V: 4, 100 6p; 640 10p; 1000 14p.

TAG-END TYPE: 70V: 2000 98p; 4700 121p; 50V: 3000 75p; 40V: 4000 70p; 2500 65p; 25V: 4700 48p; 2000 37p; 40V: 2000 + 2000 95p; 325V: 200 + 100+50 + 100 190p. OPTO ELECTRONICS\*
LEDs plus clip
TIL209 Red 13TIL211 Grn 18TIL212 Yellow 222" Red 152" Yellow Green19
Spare Clips 2
LS400 255
TIL307 695
ORP12 63
2N5777 45
7 Seg Displays

TANTALUM BEAO CAPACITORS 35V: 01µF 022. 033. 047. 0.68 35V: 01μF 0 22, 0 33 0 47, 0.68 10 2 2μF 3 3 4 7 68 25V: 1 5 10 20V: 1.5 16V: 10μF 13μ each 47,100 40μ. 10V: 22μF, 33, 47 6V: 47,68,100,3V: 68,100μF. 20μ each

MYLAR FILM CAPACITORS MYLAR FILM CAPACITORS 100V: 0 001 0.002, 0.005, 0 01μF 0 015 0 02, 0 04 0 05, 0 056μF 7 p 0 1μF 0 15 0 219p 50V: 0 47μF 11p

CERAMIC CAPACITORS: 50V 0 5pF to 10nF 15nF, 22nF 33nF, 47nF 6р

POLYSTYRENE CAPACITORS 10pF to 1nF 8p; 1.5nF to 47nF 10p

SILVER MICA (Values in pF) 3-3, 4-7, 6-8 10 12 18, 22, 33 47, 50, 68, 75, 82, 85 100, 120, 150, 220 9p each 250, 300, 330, 360, 390, 600, 820 16p each 1000, 1800, 2000, 2200 20p each

CERAMIC TRIMMER CAPACITORS 2. 7pF 4 15pF 6-25pF, 8-30pF 20 MINIATURE TYPE TRIMMERS 2 5-6pF 3 10pF 10-40pF 5 25pF 5 45pF 60pF 88pF

COMPRESSION TRIMMERS

3 40pF, 10 80pF, 25-100-500pF 38.

POTENTIOMETERS (AB or EGEN) Carbon Track, ‡W Log & ‡W Linear valu 15000, 1K & 2K (fin only). Single 5KΩ-2MΩ single gang SKΩ-2MΩ single gang 0/P switch 5KΩ-2MΩ dual gang stereo

SLIDER POTENTIOMETERS 0-25W log and linear values 60mm 5KΩ-500KΩ single gang 10KΩ-500KΩ dual gang Sell Stick Graduated Bezels

PRESET POTENTIOMETERS Vertical & Horizontal
0 1W 50Ω – 5MΩ Miniature
0 25W 100Ω – 3-3MΩ Horiz
0 25W 200Ω – 4-7MΩ Vert

RESISTORS - Erie make 5% Miniature High Stability, Low noise Miniature High Stability Low

ARANGE VAL 1 99

½W 2-2Q-4 7M €24 1.5p

½W 2-2Q-10 M €12 2p

½W 2-2Q-10M €12 5p

½W 2-2Q-10M €12 5p

2% Metal Film 10Q-1MQ 6p

1% Metal Film 51Q-1M 10p

100 - price applies to Resistors of rifot mixed values. 100 1 5 p 4 p 4 p 8 p

Carbon

DiL SOCKETS ★ (Low Profile – Texas) 8 pin 10p; 14 pin 12p; 16 pin 13p; 18 pin 20p; 20 pin 27p; 24 pin 30p; 28 pin 42p; 40 pin 55p.

ROCKER (white) 10A 250V SP changeover centre of TOA 250V ROCKER: (black) on/off 10A 250V ROCKER: (black) on/off 10A 250V ROCKER: 10B 250V Lights when on: 38 240V ROTARY: (ADJUSTABLE STOP) 1 pole/2-12 way 2p.2-6W 3p/2-4W 4p/2-3W ROTARY: Mains 250V AC, 4 Amp

PE DIGITAL THERMOMETER All parts available.

00pF 38.			230	All parts available. Send SAE for list.			DPDT Centre off 79p DPDT 8iased 115p	
	JACK PL	UGS			SOCKET	S	SLIDE 250V: 1A DPDT 14p	A
0	Screened chrome 12p 15p 23p 31p	Plast body 8p 10 <sub>f</sub> 15p 18p		open netal 8p 8p 13p 15p	moulded with break contacts 20p 24p	in line couplers 11p 12p 18p 22p	A DP C/over 15p 13p 4 pole c/over 24p PUSH BUTTON Spring loaded SPST on/off 60p SPDT c/over DPDT 6 Fap 05p 15p 15p 15p 15p 15p 15p 15p 15p 15p 1	4 4 4 4 4
	speaker Audio	PLUGS 11p 13p	SOCKET 7p 8p	S in Line 18p 20p	Push to M	IES * Miniature Take 15p I (white) 10A 25	Non-Locking Push to Break 25p	AI AI AI

3-5mm MQNQ STEREC SOCKETS PLUGS In Line 11p 13p 18p 20p 3. 4. 5 Pin Audio CO-AXIAL (TV) 14p 14p 14p PHONO
PHONO
Pried colours 15p 9p 12p Metal Screened 10p 3-way 20p

BANANA 4mm 2mm 1mm WANOER 3mm 11p 10p 7p 12p 10p 7p 8p 8p

PE VDU SYSTEMS

parts now available (send SAE for list)

Convert your TV into a VDU by using the new Thomson-CSF, TV-CRT controller chip SF.F 96364. 16 lines by 64 characters, text refreshment, cursor management on TV screen, line erasing. line end erasing. Compatible with.

any computing system. any computing sys SFF 96364E AY-5-1013UART 71301 ROM ST SFS80102 RAM 1K 74LS163 RAM MC1488 MC1488 SN75450 SN75451 SN75451 SN75452 SN75454 £11.75° £4.50° £8.20° £2.05° £0.95° £0.85° £0.90° £1.20° £0.70°

£1.60° £5.95° £0.95° £1.09° £3.23° £2.70° 2102 LF 2513 74LS132 81LS97 MHz crystal 14.31B18IMHz

7486 7489 7490

7491 7492 7493

TTL 74★

BD131\*
BD133\*
BD133\*
BD133\*
BD136\*
BD136\*
BD137\*
BD138\*
BD140\*
BD150\*
BF156\*
BF173\*
BF173\*
BF178\*
BF178\*
BF180\*
BF180\*
BF180\*
BF180\*
BF180\*
BF180\*
BF180\* 

BC158 BC159 BC160 BC167A BC16BC BC169C

CMOS\*

MC12496
MC13401
MC13401
MC13401
MC3340P\*
MC340112\*
MM2112\*
MM5038\*
MK50362\*
MM2112\*
MC5160\*
M 85 752 1150 452 30 240 110 195 79 80 95 145 248 125 750 70 125 750 755 755

MC1303 MC1304P MC1310 MC1312P MC1488\*

MC1489★ MC1495★

145 195 385

20

2N3563 **TRANSISTORS** N3614\*
2N3614\*
2N36163\*
2N36163\*
2N36363\*
2N3702
2N3703
2N3705
2N3705
2N3707
2N3707
2N3707
2N3711\*
2N3772\*
2N3712\*
2N3712\*
2N3712\*
2N3712\*
2N371372\*
2N3820
2N3723\*
2N3820
2N3820
2N3821\*
2N3820
2N3821\*
2N382 169 135 24 10 11 10 10 10 16 10 250 170 288 AC117★ AC125★ AC126★ AC127★ AC128★ 351 BC170 201 BC1772 201 BC1778 202 BC1778 203 BC1789 204 BC1789 204 BC1789 204 BC1831 204 BC1831 205 BC1841 205 BC1841 207 BC1841 207 BC1841 207 BC1841 208 BC1841 207 BC1841 208 BC1841 209 BC1 

## ZTX311 173

32 ZTX314 24

32 ZTX314 24

35 ZTX326 40

31 ZTX3326 40

31 ZTX334 20

27 ZTX500 13

28 ZTX501 14

19 ZTX502 19

25 ZTX503 15

36 ZTX553 15

36 ZTX553 15

36 ZTX553 15

36 ZTX550 42

28 ZN898\*\* 35

45 ZN898\*\* 39

44 ZN898\*\* 39

45 ZN708\*\* 19

85 ZN918\*\* 39

46 ZN708\*\* 19

85 ZN918\*\* 39

47 ZN308\*\* 46

2N18930\*\* 18

85 ZN1304\*\* 50

60 ZN180\*\* 22

80 ZN221\*\* 48

40 ZN160\*\* 15

61 ZN1308\*\* 46

2N180\*\* 28

62 ZN2198\*\* 22

80 ZN221\*\* 48

52 ZN2188\*\* 39

46 ZN221\*\* 48

53 ZN2368\*\* 21

100 ZN2221\*\* 28

66 ZN2368\*\* 21

100 ZN2221\*\* 28

67 ZN2368\*\* 21

110 ZN2368\*\* 11

110 ZN2368\*\* 15

20 ZN2218A\*\* 31

85 ZN2308\*\* 45

110 ZN2368\*\* 15

20 ZN2488\*\* 30

20 ZN2220\*\* 20

88 ZN2297\* 45

85 ZN2308\*\* 45

110 ZN2368\*\* 15

20 ZN2488\*\* 32

20 ZN256\*\* 28

20 ZN256\*\* 29

20 ZN305\*\* 55

11 ZN3133 33

16 ZN2505\*\* 30

18 ZN35250 30

21 ZN3302 35

22 ZN3302 35

22 ZN3305 35

23 ZN3868 31

24 ZN3442 36

24 ZN3442 36

24 ZN3442 36

24 ZN3442 36

24 ZN34442 36

24 ZN34442 36

2 | OC42+ | OC42+ | OC42+ | OC42+ | OC43+ | OC44+ | OC70+ | OC71+ | OC72+ | OC72 

2N5777\*
2N6027\*
40311\*
40316\*
40316\*
40327\*
40327\*
40348\*
40361\*
40407\*
40412\*
40467\*
40595\*
40636\*
40636\*
40636\* **Diodes** IN4148 4 CRO33\* 148 Zeners 400mw 2.7-33v 9

# **DIGITAL MULTIMETER**

Announcing DM900 — The Digital Multimeter with a difference — It measures Capacitance too. (as published in E.T.I. August 1978)

Throw away your analogue meters, here's digital accuracy at only half the price of an equivalent commercial Multimeter.

The DM900 is a 3½ digit multimeter with an 0.5in L.C.D. display incorporating:

5 AC & DC Voltage ranges; 6 Resistance ranges. 5 AC & DC Current ranges; 4 Capacitance ranges.

The prototype accuracy is better than 1%.

This is a unique design using the latest MOS ICs and due to the minimal current drain, is powered by only one PP3 battery. There is also a battery check facility. check facility.

DM900 is an attractive hand-held lightweight device, built into a high impact case with carrying handle and has been ingeniously designed to simplify assembly.

Never before have all these features been offered to the electronics enthusiast in a single unit. Price: £54.50° only (p&p insured add |80p)

Send SAE for leaflet. Ready Built and tested units £78.50° including probes and carrying case (P&P insured 80p)

(Demonstration on at our shop)

# YOUR COMPLETE RANGE OF ELECTRONIC HARDWARE....

# BIMENCLOSURES



ALL METAL BIMCASES Red, Grey or Orange 14swg Aluminium removable top and bottom covers. 18 swg black mild steel chassis with fixing support brackets.

> RIM 3000 (250x 167 5x68 5mm)

## MINI DESK RIMCONSOLES

Orange, Blue, Black or Grey ABS body incorporates 1.8mm pcb guides, stand-off bosses in base with 4 BIMFEET supplied 1mm Grey Aluminium

panel sits recessed with fixing screws into integral brass bushes, BIM 1005 (161 x 96 x 58mm) BIM 1006 (215 x 130 x 75mm) £3.05

Orange, Blue, Black or Grey ABS with 1mm Grey Aluminium recessed front cover held by screws into integral brass bushes

MULTI PURPOSE BIMBOXES


1.8mm pcb guides incorporated and 4 BIMFEET supplied.

BIM 4003 (85x56x28.5r	nm) £1,18
BIM 4004 (111x71x41,5	imm) £1.62
BIM 4005 (161x96x52 5	mm) £2 19

# ALL METAL BIMCONSOLES

E ME I AE BIMCOMOCES			
All aluminium, 2 piece desk consoles with	Colour Code	Top Panel	Base
either 15° or 30° sloping fronts, sit on	A	Off White	Blue
4 self-adhesive non-slip rubber feet.	В	Sand	Green
Ventilation slots in base and rear panel for excellent cooling.	С	Satin Black	Gold
pondition on containing.			

15 <sup>O</sup> Sloping Panel	30° Sloping Panel	
BIM7151 (102×140×51[28] mm)	BIM7301 (102×140×76[28] mm)	£10.67
BIM7152 (165×140×51[28] mm)	BIM 7302 (165×140×76[28] mm)	£11.44
BIM 7153 (165×216×51[28] mm)	BIM 7303 (165 x 183 x 102 [28] mm)	£12.61
	BIM 7304 (254x 140x 76[28] mm)	£13.82
BIM7155 (254x211x76[33] mm)	BIM7305 (254x 183x 102 [28] mm)	£15.36
	BIM7306 (254x259x102[28] mm)	
BIM7157 (356x211x76[33] mm)	BIM7307 (356x 183x 102 [28] mm)	£17.58
BIM7158 (356x287x76[33] mm)	BIM7308 (356x259x102[28] mm)	£18.55

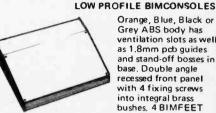

Orange, Blue, Black or Grey ABS body has ventilation slots as well as 1.8mm pcb guides and stand-off bosses in base. Double angle recessed front panel with 4 fixing screws into integral brass bushes, 4 BIMFEET supplied.

BIM 6005 (143 x 105 x 55.5 [31.5] mm) £2.37 BIM 6006 (143 x 170 x 55.5 [31.5] mm) £3.08 BIM 6007 (214 x 170 x 82.0 [31.5] mm) £4.12

# ABS & DIFCAST BIMBOXES

6 sizes in ABS or Diecast Aluminium. ABS moulded in Orange, Blue. Black or Grey, Diecast Aluminium in Grey Hammertone or Natural, All boxes incorporate 1.8mm pcb guides, stand-off supports in base and have close fitting flanged lids held by screws into integral brass bushes (ABS) or tapped holes (Diecast).

ABS		Diecast	Hammertone	Natural
N/A	6	BIM5001/11	TBA	TBA
BIM2002/12	£0.96	BIM5002/12	£1.46	£1.19
BIM 2003/13	£1.13	BIM5003/13	£1.78	£1.46
BIM2004/14	£1.35	BIM5004/14	£2.24	£1.82
BIM2005/15	£1.52	BIM5005/15	£2.84	£2.28
B1M2006/16	£2.37	BIM5006/16	£3.94	£3.33
	BIM2002/12 BIM2003/13 BIM2004/14 BIM2005/15	N/A BIM2002/12 £0.96 BIM2003/13 £1.13 BIM2004/14 £1.35 BIM2005/15 £1.52	N/A BIM2002/12 £0.96 BIM5002/12 BIM2003/13 £1.13 BIM5003/13 BIM2004/14 £1.35 BIM5005/15 £1.52 BIM5005/15	N/A BIM5001/11 TBA BIM2002/12 £0.96 BIM5002/12 £1.46 BIM2003/13 £1.13 BIM5003/13 £1.78 BIM2004/14 £1.35 BIM5004/14 £2.24 BIM2005/15 £1.52 BIM5005/15 £2.84

Also available in Grey Polystyrene with no slots and self-tapping screws BIM 2007/17 (112x61x31mm) £1.00

## **EUROCARD BIMCONSOLES**

Orange, Blue, Black or Grey ABS body accepts full or 1/2 size Eurocards, with bosses in the base for direct fixing, 1.8mm wide pcb guides incorporated and 4 BIMFEET supplied, 1mm

Grey aluminium lid sits flush with body top and held by 4 screws into integral brass bushes.

> BIM 8005 (169x127x70[45] mm) BIM 8007 (to be announced shortly)

# BIMTOOLS



# MAINS BIMDRILLS

Small, powerful 240V hand drill complete with 2 metres of cable and 2 pin DIN plug. Accepts all tools with 1mm, 2mm or .125" dia. shanks. Drills brass, steel, aluminium and pcb's, Under 250g, off load speed 7500 rpm. Orange ABS, high impact, fully insulated body with spring return on/off switch £10.53

Mains Accessory Kit 1 includes 1mm, 2mm, .125" twist drills, 5 burrs and 2.4mm collet £2.48

Mains Kit 2 includes Mains BIMDRILL as above, 20 assorted drills, mops, burrs, grinding wheels and mounted points, 1mm, 2mm, 2.4mm and .125" collets. Complete in transparent case measuring 230x130x58mm £22.14

# 12 VOLT BIMDRILLS

2 small, powerful drills easily hand held or used with lathe/stand adaptor. Integral on/off switch and 1 metre cable.

Mini BIMDRILL with 3 collets up to 2.4mm dia £ 8.10 Major BIMDRILL with 4 collets up to 3mm dia

Accessory Kits 1 have appropriate drills and collets as above plus 20 assorted tools. Mini Kit 1 - £15.12, Major Kit 1 - £19.44 Accessory Kits 2 have appropriate drills, collets plus 40 tools and mains 12V dc adaptor. Mini Kit 2 - £34.02, Major Kit 2 - £39.42.


Accessory Kits 3 as appropriate Kits 2 plus stand/lathe unit. Mini Kit 3 - £45.36, Major Kit 3 - £50.76.

# BIMDIPS



Rapidly inserts and withdraws any 4-18 pin, .3" pitch DIL package without beding the legs. Adjustable metal jaws for MOS type devices grip the bottom of the leg for minimum strain. Will pick up IC's from a bench, a carrier or a


# D. B. BIMSNIPS

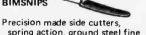

spring action, ground steel fine pointed blades for intricate work


5%" tong £3.34

# **BIMIRONS**

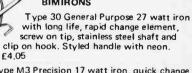


Type M3 Precision 17 watt iron, quick change tip, long life element, styled handle with clip £4.43

# BIMPUMPS

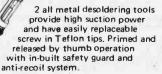

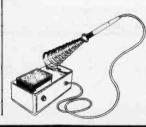BIMPUMP Major (180mm long) £7.99 BIMPUMP Minor (150mm long) £6.80



# RIMSTATION

Type PSU6 Soldering Iron Station complete with 6V, 6 Watt miniature iron having stainless steel shaft, quick change slide on tip and long life element.

Station contains 240V/6V transformer, neon, coiled iron support and sponge iron tip cleaning pad.

New product available shortly

on hook

BIMENCLOSURES (Bimboxes, Bimconsoles and Bimcases) BIMTOOLS (Bimirons, Bimdrills, Bimsnips, Bimpumps, Bimdips) BIMACCESSORIES (Bimfeet, Bimdaptors) BIMDICATORS BIMBOARDS

# BIMDICATORS



2" dia. lens

ECONOMY QUALITY LED'S

Mixed bags of ,125" and ,2" dia, lens in various colours 50 for £5.67, 100 for £10.00

# **FULL SPECIFICATION LED's**

125" or .2" with mounting clips and data Red - £1.67/pack of 5, Green - £2.48/pack of 5, Yellow/Amber - £3.18/pack of 5



# 33 and 34 SERIES

Front viewing (30° angle) LED indicators

BIM 33 is nickel plated, uses 3.2mm dia LED and needs 6.5mm dia, fixing hole

BIM 34 is chromium plated, uses 5mm dia, LED and needs 8mm dia, fixing hole

Red - £2.80/pack of 5, Green/Yellow - £3.24/pack of 5



AH AG

# **A SERIES**

240V Neon with integral resistor. held in 8mm hole by plastic bezel.

Red, Amber, Clear or Opal lens £2/pack of 5, Green lens £3/pack of 5 Low Voltage equivalent of above with Red, Amber, Clear, Opal or Green Lens.

State Voltage, lens style, colour and whether tags or flying leads.





6V £0.54 each, 14V £0.58 each, 28V £0.65 each

LES and Midget Flanged lampholder with 13mm dia. (A) and 18mm dia (B) lens. Solder tags. 1/2" dia. hole fixing (lamps not supplied) plus chrome bezel with A lens

Red, Amber, Clear, Green, Opal £0.66 each



TI Midget Flanged lampholder. Lamps are available on request 8mm fixing hole, solder tags. Front replaceable, 7.25mm dia.


lens. Red, Amber, Clear, Green, Opal £0.43


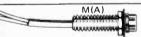
# 05 SERIES

240V Neon with integral resistor. Self retaining in 13mm hole, on blades. 13mm dia, lens with 19mm dia, chrome bezel.

Red and Amber £0.61 each, Green £0.78 each.





# M & MP SERIES

Low voltage nickel plated brass

(M) and Polycarbonate (MP) indicators, 150mm leads, 6.4mm fixing hole Red, Amber, Clear, Green, Opal


6.9mm dia. lens (M) 6V £0.65 each, 14V £0.68 each, 28V £0.79 each 7.5mm dia. lens (MP) 6V £0.55 each, 14V £0.59 each, 28V £0.68 each


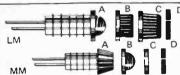
# **BIM M LED SERIES**

Nickel plated brass bodied LES indicator, 21mm wire wrappable leads, 6.5mm fixing hole, 2 styles, 6,8mm dia

Red £0.67 each, Green £0.83 each, Amber £1.00 each



# BIM LM & MM LED SERIES

Subminiature nylon bodied LED indicators with 12mm wire wrappable leads

LM & MM push fit into 4.75mm & 4mm holes respectively. Each series has 4 lens styles in Red £0.67, Green £0.83, Yellow £1,00 each.

Both lenses 'D' are square



# BIM 23, 26 & 56 LED SERIES

Black nylon bodied LED indicators, BIM 23 has 7mm flat face, BIM 26 & 56 utilise 4 & 5mm dia LED's. Push

fit in 8mm hole. Red £0.46 each, Green £0.62 each, Yellow £0.77 each

# BIMACCESSORIES



## RIMDAPTORS

Allows pcb's to be flat mounted sandwich fashion in BIMBOXES RIMCONSOLES, and all

other enclosures having 1.5mm wide vertical guide slots. One plastic BIMDAPTOR on each corner of pcb(s) enables assembly to be simply slid into place. 54mm long, 10 slots on 5mm spacing and can be simply snipped off to length.

Packs of 25 £1.08 per pack

# BIMFEET



11mm dia, 3mm high, grey rubber self adhesive enclosure feet.

Packs of 24 £0.77 per pack

# BIMBOARDS



DIL COMPATIBLE BIMBOARDS



Accept all sizes (4-50 pin) of DIL IC packages as well as resistors, diodes, capacitors and LEDs. Integral Bus Strips up each side for power lines and Component Support Bracket for holding lamps, switches and fuses etc. Available as single or multiple

units, the latter mounted on 1.5mm thick black aluminium back plate which stand on non slip rubber feet and have 4 screw terminals for incoming power.

BIMBOARD 1 has 550 sockets, multiple units utilising 2, 3 and 4 BIMBOARDS incorporate 1100, 1650 and 2200 sockets, all on 2.5mm (0.1") matrix.

BIMBOARD 1 £ 8.83

BIMBOARD 2 f21 01

BIMBOARD 3 £29.84

BIMBOARD 4 £38.79

# DESIGNER PROTOTYPING SYSTEM

2, or 3 BIMBOARDS mounted on BIM 6007 BIMCONSOLE with Integral Power Supply (±5 to ± 15Vdc @ 100mA and fixed +5Vdc @ 1A) All O/P's fully isolated. Short circuit and fast fold back protection. Power rails brought out to cable clamps that accept stripped wire or 4mm plug.

> DESIGNER 1 £55.62 DESIGNER 2 £61.02 DESIGNER 3 £66.42

EBOM

INDUSTRIAL MOULDINGS LIMITED

All quoted prices are 1 off and include Postage, Packing and VAT. Terms are strictly cash with order unless you have authorised BOSS account. For individual data sheets on all BOSS products send stamped, self addressed envelope.

2 Herne Hill Road, London SE24 0AU

Telephone: 01-737 2383

Telex: 919693 Answer Back 'LITZEN G' Cables & Telegrams: 'LITZEN LONDON SE24'

# SAXON ENTERTAINMENTS

THE PIONEERS OF MODULAR DISCO/P.A. EQUIPMENT NOW OFFER PACKAGE DEALS AT INCOMPARABLE PRICES

# CENTAUR STEREO DISCOS

C/W LIGHT SHOW & DISPLAY, **TWIN SPEAKERS & LEADS** 

# Standard 100W

£249 or Deposit £57.12 12 Months @ £21.94 or 24 Months @£12.54

# Super 200W

£299 or Deposit £68.12 ns @ £26.19 or 24 Months @ £14.90

GXL 200W (with twin 200 watt cabinets)

£389 or Deposit £87.32

12 Months @ £33.64 or 24 Months @ £19.19

COMPLETE STEREO **ROADSHOWS – BUILT IN** SOUND TO LIGHT/SEQUENCER & DISPLAY

# TWO YEAR GUARANTEE

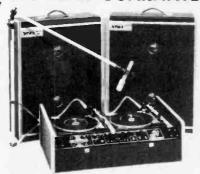


illustration shows GXL Centaur System

These systems feature full mixing for two decks tape & mic with monitoring facilities - override and are supplied complete with sound to light + sequencer, display, speaker leads etc.

# **JUST PLUG IN AND GO!**

BSR Decks - 17,000 Line Loudspeakers - Rugged Aluminium Trimmed Cabinets - Cue Light And Phones Output - Slave Output - Deck Lights/Motor Starts (GXL)

SUPPLY FOR

# MINI DISCO **100 WATT MONO SYSTEM**

£179.50 + carr. £15 + VAT Deposit £42.06

12 Months @ £16.21 or 24 Months @£9.24

Similar in appearance to the Centaur and complete with loudspeakers and leads.

Headphones to suit any system	£7.50
EM507 Electret Mic	£15.00
D1501 Electret Mic	£18.50
Boom Stand	£15.50
Carriage on all disco and PA systems	£10.00
(Included in H.P. Prices)	

20% Deposit Terms On All Orders Over £150 - 12 or 24 Months - Low Interest

# D.I.Y. MODULES FOR ALL DISCO/P.A. AMPLIFIERS

£9.95\* TWO MODULES SUPPLY FOR SA604 60W 4 ohms 50V £13.25 TWO MODULES SHPPLY FOR £13.50 SA608 60W 8 chms 65V £14.25 TWO MODULES SUPPLY FOR ONE MODULE SUPPLY FOR SA1204 120W 4 ohms 75V £15.95 SA1208 120W 8 ohms 95V £21.00 TWO MODULES SUPPLY FOR ONE MODULE £22.50 SA2404 240W 4 ohms 95V £29.50 0-2% Distortion, 30Hz-20, KHz ± 2d8, Fully Short/Open Circuit proof input sensitivity 240 mV to suit most mixers – D.C. & Output Fuses fitted.

# TOP QUALITY COMPONENTS THROUGHOUT

# **COMPLETE LIGHTING CONTROL AT YOUR FINGERTIPS!**



SA308 30W 8 ohms 45V

Lighting Control Unit Mk II 4kW Sequencer + Sound Light + Dimmers Automatic Level Integrated Logic Module £32.50 Panel £2.95 Three Channel Sound to Light

£10.90\*

3kW 1-240W input - master Module £19.75 Plus channel controls Panel £2 95

1 x 18" £29.50

SPARES & ACCESSORIES – LOUDSPEAKERS & CABINETS

Rope Lights - Red or Multicolour £39.50 Melos Echo Chamber per 30ft. Headphones Rope Light Controller for up to 120 ft £30.00 Fuzz Lights-Red/Blue/Yellow/Green £22.80 Magnetic Cartridge Equalisers £3.50\*

100 Watt Chassis Loudspeakers 12" £23.50

Sirens: English Police, USA Police, Destroyer, Alien Voice Simulator Bulgin 8 way lighting plug/socket

£1.90 18" £47.50 (Add £1.50 corr.) Large 12" £21.50 Small 2 x 12" £22.50

£59.00

£7.50\*

£7.50

Empty Loudspeaker Cabinets: Small 12" £15.50, Large 2 x 12" £28 Projector lamps: A1167 £2.90. M6 £5.65.

100W Spot lamps Red/Blue/Yellow/Green £1.50 ea £13.50 for 10 MD Spot Banks: 3-way 300W £19.50,

4-way 400W £22.50. Bubble machines (optikinetics) £41.50

Strobe tubes 80W £8.50 ICI Vynide 50" wide £3.50 Metre Kickproof Grille 24" wide £3.25 Metre Kick Resistant Grill 50" wide £3.25 Metre **FULL RANGE OF RE-AN PRODUCTS IN STOCK** SEND FOR OUR BROCHURE NOW!!

# DISCO MIXERS - COMPLETE OR MODULAR

00000000000

WITH AUTOFADE MODULES Mono module

Stereo module

Available complete and ready to plug in or as an easy to connect module with all controls except monitor switch already fitted – full instructions

FEATURES INCLUDE: Twin Deck - Mic & Tape Inputs - Wide range bass & treble controls – Full headphone monitoring Crossfade – Professional standard performance.

COMPLETE MIXERS (with case) Mono 18V £39.50 £57.50 Stereo 18V Mono mains Stereo mains £63.75

MONO OR STEREO

£33.50

# STROBE UNITS

Pro-Strobe 4-6 Joules £37.50 Super Strobe 2-3 Joules £22.50 (Pro-Strobe has external trigger

# PROJECTORS — PLUTO — NEW LOW PRICES!!! CHOICE OF WHEEL/CASSETTE

P150 150W Tungsten P500 100W Q.I. P500 250W Q.I.

£37 50 £84.95

Liquid wheels Cassettes Picture wheels from (Wide choice available)

£8.00 £4.75

# PIEZO HORNS only £7.50 YES! - only £7.50

(As fitted to our package PA system)

Direct from Motorola Inc., USA at an UNBEATABLE PRICE

No crossover required 4kHz - 30kHz rated 75W/8 ohms 150W/4 ohms use two per 100W amplifier - Full instructions supplied.





# PACKAGE P.A. SYSTEMS (2 Year Guarantee)

Complete with PIEZO horn columns fitted with 100 watt units (100 watt system illustrated)

100 Watt £159.90 + carr Deposit £37.89

12 Months @ £14.58 or 24 Months @ £8.30 Includes 4 Channel 100 Watt Amplifier with Treble, Bass and Master Controls plus Leads and Twin Piezo Horn Columns (shown on right).


# 200 Watt £249.00 + carr. Deposit £57.12

12 Months @ £21.94 or 24 Months @ £12.54 zsix Mixed Inputs plus Three Sets of Bass and Treble Controls plus Slave Output and Master Control.
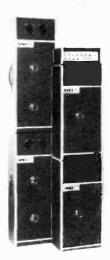
# **ACCESSORIES** Melos Echo Unit £59.00

A high quality Cassette Tape Echo Unit giving long tape life, infinitely variable echo depth and speed control. Suitable for all mics. and

instruments. High quality Boom Stand £15.50. Floor Stand £9.90 DI501 Condenser Mic. Removable Lead - Good Anti-Feedback £18.50. \* EM507 Condenser Mic. - Good Value £15.00. Phasers £19.80.



# D.I.Y. MODULES FOR P.A. SYSTEMS Mono or | Stered

Make your own mixer - Mono/Stereo - up to 20 channels with these, easy to wire modules - Available as PCB's or assembled on panels.





£8.95	Mano C/W panel etc.	£5.95	Mono PCB	Input Stoges Up to 20
£12.50	Stereo C/W panel etc.	£9.50	Stereo PCB.	
£8.95	Mano C/W panel etc.	£5.95	Mono PCB	Mixer/Monitor (One only per system)
£12.50	Stereo C/W panel etc.	£9.50	Stereo PCB	het skatem)

£9.50

Send for free brochure for complete specification

# Saxon AP100 Amplifier £45

Four mixing inputs - 100W into 4 ohms Wide range bass & treble controls + master – Twin outputs

Power supply for

up to 20 channels

# Saxon 150 Amplifier £59

Four mixing inputs - 100W into 8 ohms 150W into 4 ohms - wide range bass & treble controls + master



£1.00

Blank

panel

All prices subject to 8% VAT except where osterisked ( $12\frac{1}{2}\%$ ) Shop premises open Tues to Sat 9 am - 5 pm Lunch 12.30 - 1.30 pm Mail order dept open Mon to Fri 10 am - 4 pm Ring 01-684 6385

# TO ORDER

Send your requirements with cheque crossed P.O. or 60p COD charge to address below or just send your Access or Barclay Card Number NOT THE CARD.

By Phone You may order COD, Access or Barclay Card Post & Packing 50p on all orders except where stated.

SAXON ENTERTAINMENTS 327 Whitehorse Road, Croydon, Surrey. All Enquiries Large SAE Please Brochures on request.



# Wilmslow **Audio**

# THE firm for speakers!

SEND 15p STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS, ETC. AND **DISCOUNT PRICE LIST** 

ACT ● AUDAX ● BAKER BOWERS & WILKINS ● CASTLE ● CELESTION CHARTWELL • COLES • DALESFORD DECCA ● EMI ● EAGLE ● ELAC ● FANE GAUSS . GOODMANS . HELME . I.M.F. ISOPHON . JR . JORDON WATTS KEF & LEAK . LOWTHER . McKENZIE MONITOR AUDIO • PEERLESS • RADFORD RAM . RICHARD ALLAN . SEAS TANNOY • VIDEOTONE • WHARFEDALE

# WILMSLOW AUDIO (Dept. P.E.) SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF

Discount Hi-Fi, etc. at 5 Swan Street and 10 Swan Street

Tel.: Wilmslow 29599 for Speakers

Tel.: Wilmslow 26213 for Hi-Fl

# PROGRESSIVE RADIO

93 DALE STREET, LIVERPOOL L2 2JD. Tel: 051-236-0982

93 DALE STREET, LIVERPOOL L2 2JD. Tel: 051-236-0982

SEMICONDUCTORS ALL FULL SPEC. BC212, BC182, BC237, BF197, BC159 all 8p each. LM380 80p, LM381 95p, 741 8 Pln 23p, 7415 (wide bandwidth) 8 pin 35p. TiL305 Alpha numerical display (with data) £2:50p. BX504 opto isolators infar red led to photo cell, 4 lead 25p, BFY50 plastic 14p, STC 3 volt 1 watt zener diodes 7p each, BD533 33p, MRD3051 photo transistors 35p, FETS similar to 2N3819 18p, MOSFET similar 40673 35p, Intel C1103 1024 bit mos rams 95p, CD4051 45p, 723 14 pin I.C.5. 35p.
DIODES, BY127 9p, IN4002 4p, IN4005 7p, 600v 3 amp 17p, Lucas bridge recs, 400v 1-5 amp 30p. SPECIAL OFFER TBA800 10 for £50.0 NE555 10 for £3:00.

MAN3A 3mm led displays 50p, Min. Nixie 587 0ST 75p.
Pot core unit, has six pot cores including one FX2243 (45mm) and two FX2242 (35mm) 3 TO3 sit, power transistors on heat sink, 3-20mm panel fuseholders and panel with various transistors, diodes and a 5 amp plastic SCR, £1-75p plus 75p postage.

MOTORS, Model type 1-5-6 volts 20p, 'BIG INCH' sub min motor 115 vac, 3 r.p.m. 25p. 24

diodes and a 5 amp piestic 542., E173pp juis 74p posteys 6 MOTORS, Model type 1.5-6 volts 20p, 'BIG INCH' sub min motor 115 vac, 3 r.p.m. 25p. 24 OVAC SYNCH. MOTORS WITH GEARBOX, 1/5 r.p.m. 75p, 1/24th r.p.m. 75p, Crouzet 115 VAC 4 r.p.m. 95p, 12v dc 5 pole 35p, 12v 8 Track Carridge Motors New £1-25p. HI-SPEED MORSE KEY, ALL METAL £2-25p. PLASTIC MORSE KEYS, 95p.

PLESSEY WINKLER SWITCHES, 1 pole 30 way, 2 bank adj. stop 75p.

Crystal microphone inserts 37mm 45p, Grundig electret condenser inserts with built in FET preamp £1-50p, ELECTRET PENCIL HAND MICROPHONES 1K IMP WITH STANDARD JACK PLUG £2-8bp, TIE CLIP CONDENSER MIKES OMNI, 1K IMP, (uses deaf aid battery, supplied)

.14-95p. SOLDER SUCKER, high suction, eye protection shield £4-95p. PROJECT BOXES, BLACK ABS PLASTIC WITH BRASS INSERTS AND LID, 75 x 56 x 35 44p.

SIS x 71 x 35 52p, 115 x 95 x 36 60p.

BUZZERS, GPO open type 3-6v 30p. Large plastic domed type loud note 6 or 12 volts 50p. Solid State buzzers, miniature, 6-9-12-24 volt 15ma 75p each.

TAPE HEADS, Mono Cassette £1:30p. Stereo cassette £3:00, BSR MNI330 half track dual impact of the control of the cont

TAPE HEADS, Mono Cassette £1-30p. Stereo cassette £3-00, BSN mixtas3 nain track dual lin-ped. heads £1-75p, TD 10 Dual head assemblies 2 heads both ½ track R/P with built in erase mounted on bracket, £1-20p. Relays, Min 24v dc 2 pole c/o 3 amp contacts 55p, Min sealed 220v ac 2 pole c/o 40p, Open type 12v dc 4 pole c/o 50p, 4 pole reed relays N/O 20p, 240v 25LB pull 2" travel, large solenoid new £3-95 + 54p. P.P.

CRYSTALS, 300khz 40p. Aerosol Touch up paint one colour yellow/grey, 6oz can 35p. 50v ac cam units, motor switching ten c/o micro switches, supplied with capacitor for 240v ac use

Enlarg pres say postage.

Belling Lee L4305 masthead amplifiers and mains power unit, new but only for group A UHF 67-50p.

E7-50p.

TRANSFORMERS, 6-0-6v 100ms, 9-09 75ms, 12-012 50ms 75p each, 12-012 100ms 95p, 12v 500ms 95p, 1:1 triac/xenon pulse transformers 30p, CHOKES 6MH 3 amp 20p, U.H.FTV Tuners, push button (not varicap) new and boxed 62-50p. Miniature toggle switches, SPST 8 x 5 x 7 45p, DPDT 8 x 7 x 7 50p, DPDT c/o 12 x 11 x 9 75p, Min. push to make-or push to bfeak 16 x 16mm 15p each type. Slider switches, DPDT standard 15p, Min. 12p, Std. c/o 20p, Roller action micro switches 15p.

action micro switches 15p.

TOOLS Small side cutters 5" insulated handles £1.35p. Snub nosed pilers 5" insulated handles £1.35p. Snub nosed pilers 5" insulated handles £1.35p. Board with 14 12 volt reed relays £1.95p. Large mains tester screwdrivers, fully insulated 8" 44p. Test lead jumper sets, 10 leads with insulated croc clips each end, different colours 80p. Telephone pick up coil, suction type with 3.5 mm jack plug 50p. 9 volt battery eliminators, 240v ac input 9v dc out at 120 mA, stabilised replaced PP3, PP6, PP7, PP9 £2.45p. Edge connectors, 0.1 64 way 65p, 34 way 40p, 0.2 18 way 15p, Murata MA401, 40KH2, Transducers Rec/Sender, 23.25p pair, Tape head demagnetisers, 240v ac with on/off switch, straight probe £2.00, curved probe (cassette) £2.35p.

TERMS: cash with order, (of official orders from colleges etc). Postage 30p unless otherw shown, overseas post at cost. VAT inclusive prices S.A.E. for new illustrated lists.

Progressive Radio, 31 Cheapside, Liverpool L2 2DY. Tel: 051-236-0982.

# Get kitted out for winter.

Heathkit electronics kits are perfect for the winter evenings. There are hundreds of things you can make yourself, with easy-to-follow instructions to guide you.

There are kits for the home or car, and there's a whole range of computers and

peripherals too.
And for a thorough and
practical understanding
of the principles of electronics,

there's a complete range of educational courses and experimenter-trainers.
Full details are in the Heathkit catalogues.
Send the coupon now.



Soldering iron worth £4.50. Full details when you send the coupon.


There are Heathkit Electronies Centres at 253 Tottenham Gourt Hoad London (Ol-636 7349)

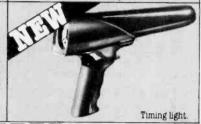253 Tottenham Court Hoad, London (Ol-636 7349) d at Bristol Road, Cloucester (Gloucester 29451)









To: Heath (Gloucester) Ltd., Dept. PE12/78, Bristol Road, Gloucester, GL2 6EE. Please tick the literature you want and include the appropriate amount in postage stamps. 

Heathkit Catalogue only (enclose 20p).

Nama

Address

Registered in England, number 606177



# THIS is the Catalogue you need to solve your

to solve your component buying problems!



- The finest components catalogue yet published.
- 128 A-4-size pages.
- About 2,500 items clearly listed and indexed.
- Profusely illustrated.
- Bargain List sent free.
- At £1.25, incl. p. & p., the catalogue is a bargain.

Send the coupon below now.

912966 London

HOME RADIO (Components) LTD , 234-240 London Road, Mitcham, Surrey CR4 3HD

Please write your Name and Address in block capitals

NAME

ADDRESS

HOME RADIO (Components) LTD Dept PE

Rend No.

234-240 London Road, Mitcham, Surrey CR4 3HD

# ASTRA-PAK

92 GODSTONE ROAD WHYTELEAFE SURREY CR3 0 All prices include V.A.T. Add 25p for P&P (Extra for overseas). Discounts over £10 less 5%, over £20 less 10%, over £20 less 20%. Send SAE for complete list of components.

WHYTEL	EAFE SURF		B components.	ior comple	re nat or
74N 74LSN	74N 74LSN 7486 0.26	1414 145314	LINEARS	24 pin	0.30
7400 0.12 0.21		74167 2.70	CA3045 -14 0.45	28 pin	0.44
7401 0.12 0.21 7402 0.12 0.21	74\$86 1.50	74169 2.10	CA3046 -14 0.70	40 pin	0.55
7402 0.12 0.21 7403 0.12 0.21	7489 200	74170 1.68 1.94	LM380N -14 0.82		
7404 0.13 0.21	7490 0.35 0.95	74172 4.00	LM381N -14 1.20	CM	
7405 0.13 0.21	7491 0.65 7492 0.44 0.82	74173 1.18 1.12	LM710N -14 0.32	4000 0.14	4067 3.50
7406 0.28	7492 0.44 0.82 7493 0.40 0.95	74174 0.89 1.12	LM711N -14 0.32	4001 0.15	4068 0.24
7407 0.28		74175 0.68 1.12	MC1310P -14 1.50	4002 0.16	4069 0.17
7408 0.14 0.21	7494 0,80 7495 0.54 1.05	74\$1753.25	NE555N -8 0.30	4006 0.92	4070 0.17
74508 0.40	7496 0.60 1.30	74176 0,80	NE556N -14 0.65	4007 0.16	4071 0.17
7409 0.14 0.21	7497 2.00	74177 0.82	NE25018 -14 2.00	4008 0.92	4072 0.17
7410 0.13 0.22	74100 0.94	74178 1.20 74179 1.10	SN72702N 0.50	4009 0.45	4073 0.17
7411 0.18 0.21	74104 0.40	74180 090	SN75110N 0.50	4010 0.48	4075 0.17
7412 0.21 0.21	74105 0.40	74181 1.75 3.38	SN76003N 1.95	4011 0.15	4078 1.05
7413 0.25 0.46	74107 0.28 0.40	74182 0.75	SN76013N 1.35	4012 0.16	4077 0.46
7414 0.54 1.05	74109 0.45 0.40	7451822.30	SN76023N 1.35	4013 0.42	4078 0.22
7415 0.21	74110 0.46	74H1830 99	SN76033N 1.95	4014 0.80	4081 0.17
7416 0.27	74111 0.70	74184 1.20	TAA550R 0.35	4015 0.77	4082 0.20
7417 0.27	74112 0.40	74185A1.20	TAA8818 1.40	4016 0.42	4085 0.72
7420 0.13 0.21	74113 0.30 0.40	74186 7.20	TBA120S 0.64	4017 0.77	4086 0.76
7421 0.28 0.21	74114 0.40	74188 2.70	TBA641A 1.88	4018 0.87	4089 1.55
7422 0.17 0.21	74116 1.60	74189 3.60	TBA800 0.75	4019 0.42	4093 0.65
7423 0.25	74118 0.82	74190 1.05 0.96	TBA810S 1.04	4020 0.92	4094 1.80
7425 0.20 7426 0.25 0.28	74119 1.25	74191 0.99 0.96	TCA270S0 2.00	4021 0.82	4095 1.10
	74120 0.82	74192 0.99 1.50	TDA2020 3.20	4022 0.B2	4096 1.10
7427 0.25 0.30 7428 0.34 0.34	74121 025	74193 1.05 1.50	ZN414 1.00	4023 0.15	4097 3.50
	74122 0.40	74194 0.90 2.00		4024 0.66	4098 1.12
7430 0.13 0.21 ( 74\$30 0.30	74123 0.50 0.59	74195 0.84 1.40	OP AMPS	4025 0.15	4099 1.90
7432 0.24 0.31	74124 1.25 74125 0.40 10.46	74196 0,90 1.15	CA3130 -T099 1.00	4026 1.28	4404 1.00
7437 0.24 0.31	74125 0.40 0.46	74197 0.90 1.15	LM301A -8 0.30	4027 0.50	4412 0.30
7438 024 026	74128 0.62	74198 148	LM301A T099 0.46	4028 0.67	4428 0.80
7440 0.13 0.22	74132 0.68 0.82	74199 148 74221 150 1.05	LM348N -14 1.00	4029 D.B6	4445 1.50
7441 0.52	74134 0.36		LM709 -8 0.40	4030 0.48	4449 0.30
7442 0.55 0.70	74135 0.68	74247 0.80 74248 0.95	LM709 -14 0.42	4031 2.34	4501 0.17
7443 0.90	74136 0.55 0.40	74248 0.95	LM709 -T099 0.50	4033 1.25	4502 0.88
7444 0 90	74137 0.94	74251 1.00 0.95	LM741 -8 0.22	4034 2.00	4507 0.50
7445 0.70	74138 0.62	74253 1.10	LM741 -14 0.20	4035 1.00	4508 2.25
7446 0.70	74139 0.62	74257 1.12	LM741 -T099 0:45	4036 2.40	4510 1.05
7447A 0.60 0.94	74141 0.58	74258 1.15	LM747 -14 0.70	4037 0.99	4511 0.98
7448 0.60 0.94	74142 2.00	74260 0.28	LM3900N 0.50	4038 1.00	4512 0.92
7449 0.94	74143 2.00	74281 3.25	MC1458P -8 0.42	4039 2.80	4514 2.85
7450 0.13	74144 2.00	74266 0.43	VOLTATE REG	4040 0.88	4515 2.80
7451 0.13 0.21 7453 0.13	74145 0.64 1.20	74273 2.15 1.80	LM300 -T099 1.00	4041 0.77	4516 1.02
	74147 1.30	74279 1.25 0.55	LM309K -T03 1.30	4042 0.72	4518 0.99
7454 0.13 0.21 7455 0.26	74148 1.15	74283 1.70 1.06	UA723 -14 0.40	4043 0.82	4519 0.50
7460 0.13	74150 0.99	74284 685	7805 T0220 0.85	4044 0.82	4520 1.05
7470 0.28	74151 0.60 0.90 74153 0.60 0.56	74289 3.92	7812 T0220 0.85	4045 1.40	4521 2.00
7472 0.22		74290 0.95	7815 T0220 0.85	4046 1.32	4522 1.35
7473 0.26 0.38	74154 1.00 1.32 74155 0.63 0.98	74293 1.35 1.00	7824 T0220 0.85	4047 0.96	4527 1.60
7474 0.26 0.38	74156 0.62 0.98	74298 1.92 1.40	7905 T0220 1.10	4048 0.60	4528 0.92
73574 0.50	74157 0.63 0.60	74352 1.00	7912 T0220 1.10	4049 0.42	4529 1.10
7475 0.30 0.42	74158 0.58 0.62	74353 1.05 74365 0.52	7915 T0220 1.10	4050 0.42	4536 3.56
7478 0.26 0.39	74159 1.70		OIL SOCKETS	4051 0.84	4553 4.20
7478 0.39	74160 0.80 1.30		8 pin 0.11	4052 0.84	4555 0.85
7480 0.45	74181 0.80 0.80	74367 0.48 74368 0.52	14 pin 0.12	4053 0.84	4556 0.85
7481 0.90	74162 0.60 1.30	74386 0.58	16 pin 0.13	4054 1.10	4558 1.25
7482 0.75	74183 0.80 0.82	74390 1.92	18 pin 0.23	4055 1.00	4566 1.40
7483 0.72 0.97	74164 0.89 1.20	74393 2.00	20 pin 0.27	4060 0.98	4583 0.75
7484 0.90	74165 0.89	73670 2.30	22 pin 0.29	4066 0.48	4585 1.03
7485 0.88 0.97	74186 0.99	7.5070 2.30	0.23	.000 0.40	

O. for £1.25

cheque or P.

POST THIS COUPON

# ELECTROVALUE Buying Guide

HERE IS OUR NEXT SELECTION TO ADD TO THE PAGES YOU ALREADY HAVE SAVED. HERE IS OUR NEXT SELECTION TO ADD TO THE PAGES TOU ALREADY HAVE SAVED If you have bought before from us, you know just how large and varied our stocks are and how good our service is. For those who have yet to know us, we are publishing a series of Ads. month by month to give up-to-date information and prices on much of the stocks we carry. These ads. are appearing in Practical Electronics, E.T.I., Elektor, Practical Wireless and Everyday Electronics so that a complete series will appear each month. So no matter which journals you read, BY DETACHING AND SAVING THESE PAGES YOU WILL ACQUIRE A VALUABLE AND COMPREHENSIVE MONEY SAVING CATALOGUE.

MEET US AT BREADBOARD 78, STAND D.8

# Resistors

Туре	1+	10+	100+
CR25	THE TO S	Ω 9 5% Ε12	1.76N
.33W	3p	2p	1.7014
UPMO33	m4(1 \ 10	1M 5% E24	1.43N
.33W	2р	1.0	
CR25	MZ to	10M 10% E1	1.76N
.33W	3p	2p 300K 2% <i>E2</i>	
MR25	SEZ I TO	4p	3.60N
.4W	5p	4M75% E12	
UPM050	₩471 / 10	1.6	1 43N
.5W	2p	Ω95% <i>E12</i>	1 4314
CR37	● IU 10 3	2p	1 87N
.5W UPM075	3p	10M 5% <i>E2</i> 4	
.75W	30,10	1.6	1 43N
UPM 100	MO 7 to	4M7 5% E12	
1W	50	4p	3.27N
UPM100	<b>●</b> 5M6 to	10M 10% E	
114/	50	4p	3.27N
TRE	100 10	4p 1M 2% <i>E24</i> 4p 1o 0.47Ω ± 0 13p 10 389 10%	
5W	50	40	3.20N
TW1	0.220	to 0.47Q ± 0	.05Ω E12
1W	15p	13p	11.8N
TW1	0.56Ω	to 3R9 10%	
1W	15p	13p	11.BN
GW83	0.47Ω	, 1Ω to 10Ω 1	0% E12
3W	18p	14p	11.0N
GW\$3	12Ω to	10K 5% E12	?
3W	18p	14p	11.0N
GWS7		10Ω 10% ET.	?
7W	18p	14p	11.0N
GWS7	12Ω to	o 10K 5% <i>E12</i>	?

7W 18p 14p 11.0N Net prices apply for complete 100s only. Bulk prices available. E17 values: 1.0, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2. E24 values: as £12 plus 1.1, 1.3, 1.6, 2.0, 2.4, 3.0, 3.6, 4.3, 5.1, 6.2, 7.5, 9.1, and their decades.

# **NEW - ERG DUAL IN-LINE SWITCHES**

42p 78p £1.08 One-pole change-over Two-pole change-over SDC.2 Three-pole change-over SDC.3

(These types colour coded) Multi-type one-pole 8-way Type DS16A-8 SP Multi-type two-pole 4-way Type DS16A2-4 E1.08 For fuller range of switches, see section 5 in our current ads.

CARBON TRACK, ROTARYO, Long spindle, without flat, 0.25 0.375 B.S. bush, nut and washer 0.375 B.S. bush P20 lin 1-gang P20 log 1-gang P20 log 1-gang P20 log + switch P20 log 2-gang JP20 lin 2-gang JP20 lin 2-gang JP20 log 2-gang JP20 log + switch JP20 log - switch DP20 2-gang (separate spindles) DP20 +switch £1.67

Resistance values stocked

100Ω to 4M7 220Ω to 2M2 1K, 4K7 to 2M2 4K7 to 2M2 P20 lin 1002/10 4M/ P20 log 2202 to 2M2 JP20 lin 1K, 4K7 to 2M2 JP20 log. 4K7 to 2M2 DP20 made to order in any values avail able in P20. State front (near bush) and rear tracks clearly.

CARBON TRACK, SLIDER (58mm travel) For knobs, see JV-slider

PG58 mono C1PG58 mono C1PG58ST stereo

Resistance values stocked 4K7 to 1M 10K to 1M 4k7 to 1M 4K7 to 1M 4K7 to 1M 4K7 to 1M PC SR lie PG58 lin PG58 log C1PG58 lin C1PG58 log C1PG58ST lin

C1PG5BST log ± 2dB @ 10%R ± 3dB @ 3.2%F Log stereo matching

MINIATURE PRE-SETS Type PR.10 Horizontal or Vertical – all values 100Ω to 4M7 – **9p** each



Pan pot assembly comprising two carbon track pots mounted at right angles on rigid plastic box and operated individually by joystick control. 100K or 220K per section

£2.25

BOXES

AB7 133 x 70 x 38 AB8 101 x 101 x 38 AB9 101 x 70 x 38 AB10 133 x 101 x 38 AB11 101 x 64 x 51 AB12 76 x 51 x 25 AB13 152 x 101 x 51 AB14/2 127 x 89 x 64 DIECAST 992

89 x 114 x 114 x 114 x 171 x 171 x

35 x 30 64 x 30 64 x 55

89 x 55 121 x 55 121 x 106

67



60p 60p 60p 62p 60p 50p 77p 74p

1.24 1.32 1.62 2.10 3.07 4.39

# We are appointed National Distributors for

# NASCO

# **MICROCOMPUTER KITS**

We give delivery

£197.50 + VAT

Discounts for quantity buyers

# MOTOROLA

Microprocessor Evaluation Kit Net £175.87 +VAT

(PB301 is "double U" type and has vent and various holes)

PLASTIC 116 x PB1 122 x PB601

No discount allowable on items marked Net or N.

999 974

- TEAR OUT AND TAKE GOOD CARE OF THIS PAGE. LOOK OUT FOR THE FOLLOWING ADS. AND
- OUR COMPUTER SERVICE TAKES GOOD CARE OF YOUR ORDER NO MATTER HOW LARGE OR SMALL.

# Knobs

EV18A 18mm EV22A 22mm EV32A 32mm

EV38A 35mm BULGIN K107 pointer 32mm black or K108 pointer 57mm black of



(Caps must be ordered separately)
15mm diameter S1508 short 27p



Types available
D151, D211 0-11
D152, D212, 1-12
D158, D218 wedge
D159, D219 white arrow
Caps in black, red, yellow. green, blue and grey All other items black only

JV SERIES JV SERIES
Plastic cylindrical — black, red, yellow, green, blue, light or dark grey, white
JV18 18mm 27p
JV23 23mm 27p

The following pair are designed for DP20 pots, and have 4mm JV18/4 JV23/6T JV Slider knobs for Rad ight

TA SHOEL KHOOP IOL I	1001011111
mono and stereo pots	In eight
colours as above	
JVS + colour	8p
BLACK PLASTIC	
K1 25mm S	13p
CK1 25mm SM	18p
K2 35mm S	15p
CK2 35mm SM	20p
K3 27mm P	12p
K4 32mm P	12p
K5 19mm	20p
K6 25mm	25p
NK 36mm SK	37p
PK 36mm SP	37p
SK6 41mm SK	36p
K7 19mm B/W	20p
K8 25mm S	20p
S skirted	ZOP
M metal insert	
P pointer	
r pointer	

P pointer Sk skirt, 0-10 B/W black or white



Section 4





Type K/CK














All communications to Dept. PE.12 please

28, ST. JUDES ROAD, ENGLEFIELD GREEN. EGHAM, SURREY TW20 OHB Telephone Egham 3603 Telex 264475

 Northern Branch - 680, BURNAGE LANE. BURNAGE, MANCHESTER M19 1NA(061) 432 4945



- ATTRACTIVE DISCOUNTS ON CASH WITH ORDER (C.W.O.) ORDERS 5% where list value is over £10; 10% where list value is over £25.
- TOP QUALITY MERCHANDISE—— ALL BRAND NEW AND GUARANTEED.
- ACCESS or BARCLAYCARD ORDERS just phone or write your number
- V.A.T. Add 8% to value of order, For items marked ●, add 12½%.
- COLLECT THEM TOO

# SEMICONDUCTORS POTS

## 8 pin DIL £0:13 £0-14 £0-15 1612 14 pin DIL 16 pin DIL 24 pin DIL 1614 £0:40 1815 28 pln DH £0-45 £0-12 TO18 Transistor TU3 Transistor 16117 TO5 Transistor £0 · 12

# VOLTAGE REGULATORS

WEGGEN LOK	_
Positive	
MVR7805 v.a. 7805 TO220	£1-00
MVR7812 v.a. 7812 TO220	£1-00
MVR7815 v.a. 7815 TO220	£1:00
MVR7824 v.a. 7824 TO220	£1:00
Negative	
MVR7905 v.a. 7905 TO220	£1-40
MVR7912 v.a. 7912 TO220	£1-40
MVR7915 v.a. 7915 TO220	£1-40
MVR7924 v.a. 7924 TO220	£1-40
v.a. 723C TO99	45p
72723 14 pin DN	45p
LM309K TO3	£1 · 50

## ZENER DIODES

400mw (Bzy88) DOT Glass encap-sulated range of voltages avail-able 1. 3v, 2. 2v, 2. 7v, 3. 3v, 3. 9v, 4. 3v, 4. 7v, 5. 1v, 5. 6v, 6. 2v, 6. 8v, 7. 5v, 8. 2v, 9. 1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v, 8v. Z4 8p ea.

1w-1 -\$w Plastic and metal encap-sulated Range of voltages available. 1-3v, 2-2v, 2-7v, 3-3v, 3-9v, 4-3v, 4-7v, 5-1v, 5-6v, 6-2v, 6-8v, 7-5v, 8-2v, 9-1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 43v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 10ov No. Z13 15p ea.

19w Metal stud type SO10 case. Range of voltages available, 1-3v, 2-2v, 2-7v, 3-3v, 3-9v, 4-3v, 4-7v, 5-1v, 5-6v, 6-2v, 6-8v, 7-5v, 8-2v, 9-1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 43v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 10v, 10v, 12v, 75v, 82v,

No. Z16 35p ea.

# SILICON

RECTIFIERS				
200m A 15920 50v 15921 100v 15922 150v 15923 200v 15924 300v 1 Amp	£0.06 £0.07 £0.08 £0.09 £0.10			
N4001 50v N4002 100v N4003 200v N4004 400v N4005 600v N4006 800v N4007 1000v	£0.04 £0.05 £0.06 £0.07 £0.08 £0.09 £0.10			
1-5 Amp  S015 50v  S020 100v  S021 200v  S023 400v  S025 600v  S027 800v  S029 1000v  S029 1000v  S031 1200v	£0 08 £0 10 £0 11 £0 13 £0 14 £0 16 £0 20 £0 25			
3 A mp IN5400 50v IN5401 100v IN5402 200v IN5404 400v IN5406 600v IN5407 800v IN5408 1000v	£0·14 £0·15 £0·16 £0·17 £0·21 £0·25 £0·30			
10 Amp IS10/50 50v IS10/100 100v IS10/200 200v IS10/400 400v IS10/600 600v IS10/800 800v IS10/1000 1900v IS10/1200 1200v	£0·19 £0·21 £0·23 £0·35 £0·42 £0·51 £0·60 £0·69			
30 Amp IS30/50 50v IS30/100 100v IS30/200 200v IS30/400 400v IS30/600 600v IS30/800 800v IS30/1000 1000v IS30/1200 1280v	£0 · 56 £0 · 69 £0 · 93 £1 · 25 £1 · 76 £1 · 94 £2 · 31 £2 · 88			
69 Amp 1S 70/50 50v 1S 70/100 100v 1S 70/200 200v 1S 70/200 200v 1S 70/800 400v 1S 70/800 800v 1S 70 1000 1000v SY X38/300 6A 300v SY X38/300 6A 600v SY X38/300 Rev 6A 500v SY X38/300 Rev 6A 600v SY X38/300 Rev 6A 600v	£0 · 75 £0 · 84 £1 · 20 £1 · 75 £2 · 25 £2 · 50 £3 · 90 £0 · 45 £0 · 45 £0 · 45			

CARBON POTS (Linear Track) Single gang with wire end terminations, 8mm × 50mm plastic shaft 10mm bushes supplied with shake proof washer & nut. Tolerance ± 20% of resistance.

		/8			
				47kohms	
1832	2k2ohms	£0.26 *	1837	100kohms	£0-26
1833	4k7ohms	£0.26*	1838	220kohms	£0.26
1834	10kohms	£0-26*	1839	470kohma	£0-26"
1835	22kohms	£0.26°	1840	1Mea	£0-26"
		841 2M			

CARBON POTS (Log Track)
1842 4470hms £0-28\* 1846 100kohms £0-28\*
1843 10kohms £0-28\* 1847 120kohms £0-28\*
1844 22kohms £0-28\*
1845 47kohms £0-28\*
1845 47kohms £0-28\*
1845 47kohms £0-28\*

# **DUAL CARBON POTS (Lin Track)** These high quality dual gang pots are fitted with wire end terminations and 6mm × 50mm plastic shaft 10mm, bush rind supplied with shake proof washer & nut track tolerance ± 20% but matched to within 2db of each other. VC3

1851 4k7 £8.78° 1855 100kohms £8.78° 1.52 10kohms £8.78° 1856 220kohms £8.78° 1853 22kohms £8.78° 1857 470kohms £8.78° 1854 100kohms £8.78° 1858 1Meg £8.78° 1859 2M2 £8.78°

# DUAL CARBON POTS (Log Law)

1860 4k7ohms	£0.78° 186	4 100kohms	£0.78°
1861 10kohms	£0.78° 186	5 220kohms	£0.78*
1862 22kohme	£0.78° 186	8 470kohms	£0.78*
1863 47kohms	£0.78° 186	7 Mea	£0.78*
•	1868 2M2 €	0.78*	

SINGLE GANG SWITCHED (Lin Law) These potentiometers are fitted with double pole on-off switches. The switch is incorporated within the rotary action of the pot. Specification of pot is as VC1.
Switch rating 1-5amps at 250v AC.

1870 4K7ohms £0-60° 1874 100kohms £0-60° 1871 10kohms £0-60° 1875 220kohms £0-60° 1872 22kohms £0-60° 1875 470kohms £0-60° 1873 47kohms £0-60° 1873 47kohms £0-60° 1878 2M2 £0-60°

# SWITCHED POT (Log Track) Specification as VC2 but rack having (log)

law. 1879. 4k7ohms £0-80\* 1833 100kohms £0-80\* 1880 10kohms £0-60\* 1884 220kohms £0-60\* 1881 22kohms £0-60\* 1885 470kohms £0-60\* 1882 47kohms £0-60\* 1886 1Meg £0-60\* 1887 2M2 £0-60\*

DUAL GANG LOG-ANTI-LOG POT 1888 Track specification as dual gang pots VC3 as above, but tracks mounted to log-anti log action. £0.75°

SPECIAL VOLUME CONTROLS
A miniature 18mm type replacement volume control incorporating single pole on-off switch. Resistance value 5kohms. Tolerance ± 20% 18watt rating. 1889 £0-27° VC8

# MINIATURE ROTARY VOL

CONTROL
Skohms log law with on/off switch. 20mm
grooved spindle. Tag connections 17mm
dia. Supplied with fixing nut. Used mainly for replacement. 1890 £0-54° VC9 1890

WIRE WOUND POTS
A range of wire wound single gang pots with linear tracks of 1 watt rating, fitted with 10mm bush and supplied with shake-proof washer and nut.

V C6					
1891	10ohms	£0.80	1895	220ohms	£0.80
1892	22ohms	£0.80	1896	470ohms	£0-80
1893	47ohms	£0-80	1897	1kohms	£0-80
1894				2k2ohms	£0.80
	1899	4k7o	hms	£0-80	

PRE-SET POTS
HORIZONTAL MOUNTING
Miniature type for transistor circuits. The
wiper of the preset is provided with a slot
for screw driver adjustment. The tags of
the preset will fit printed wiring boards
with a pitch of 2:54 mm. All tracks are linear
law.

VC	7				
	1 100ohma	£0.08*	1808	22kohms	£0.08
180	2 220ohms	£0.08*	1809	47kohms	£0.08
180	3 470ohms	£0.08*	1810	100kohms	£0.08
180	4 1kohms	£0.08°	1811	220kohms	£0.08
180	5 2k2ohms	£0.08*	1812	470kohms	£0.08
	6 4k7ohms				
180	7 10kohms				£0-08
	1819	5 4M7	hma	£0.08°	

PRE-SET POTS
VERTICAL MOUNTING
Miniature type for transistor circuits.
Wiper adjustment is made by a screw
driver slot. Designed to fit 2-54mm pitch
board. All tracks are linear law.

VC7					
		£0.08°	1823	22kohms	£0.08
				47kohms	
1818	470ohms	£0.08°	1825	100kohms	£0.08
				220kohms	
1820	2k2ohms	£0.08°	1827	470kohms	£0 08
1821	4k7ohms	£0.08*	1828	1Megohm	86.03s
1822	10kohms	£0.08*	1829	2M2ohms	£0.08
	1830	4M7o	hms	£0.08°	

# **ANTEX IRONS**

O/No. 1943. 15 watt high quality soldering fron totally enclosed element in a ceramic shaft fitted with 3/32" bit. £3.65
O/No. 1947. Replacement element for 1943 iron. £1.90
O/No. 1944. Iron coated bit 3/32" for 1943 iron. £0-46
O/No. 1945. Iron coated bit 1/8" for 1943 iron. £0-48
O/No. 1946. Iron coated bit 3/16" for 1943 iron. £8:46
O/No. 1948. General purpose 18 watt iron fitted with iron coated bit. £3-40
O/No. 1952. Replacement element for 1948 iron. £1.90
O/No. 1949. Iron coated bit 3/32" for 1948 iron. £9-46
O/No. 1950. Iron coated bit 1/8" for 1948 iron £0-48
O/No. 1951. Iron coated bit 3/16" for 1948 iron. £8:46

O/No. 1931. Highly popular ¥25 25 watt quality soldering fron ceramic shafts to provide near perfect insulation break-down voltage of 1500 volts AC and a leakage current of only 3-5uA and another shaft of stainless steel to ensure strength. £3.46 O/No. 1935. Replacement element for 1931 iron. £1 60 O/No. 1932. Iron coated bit 1/8" for 1931 iron. O/No. 1933. Iron coated bit 3/16" for 193t £0-50 O/No. 1934. Iron coated bit 3/32" for 1931 iron. £0.56 O/No. 1953. SK1 soldering kit—this kit contains 15 watt soldering iron fitted with a 3/16" bit plus two spare bits, a reel of solder, heat-sink and a booklet 'how to solder'. In presentation display box. £5:30

O/No. 1939. ST3 soldering iron stand. Stand made from high grade bakelite material chromium plated strong stee spring, suitable for all models, includes accommodation for six spare bits and two sponges which serve to keep the soldering iron bits clean.

FR120 £1 10	TR101 £1 10	TR053		TR205 £1 10
•	•	•	0	0
TR310 <b>€1 50</b>	TR £1	106 65	TR/31 £1 75	
0000	0000			•

Draw your own boards with the new BI PAK etch-resist transfers. Lay the symbols on the board, rub over with a soft pencil. The transfer will adhere to the board. Then complete the circuit with your BI-PAK

0000000 0000000

# PCB TRANSFERS TR £1

65	TR312 £1 10	
		0000





# TR315 £1:95 00000000000000

etch-resist pen. 11 different paks available each containing 10 sheets of transfers as illustration-approx. 1 size-Special Introductory Set, 1 pak each of above £12.00.

# LEDs DISPLAYS & OPTOS

O/no. 1501 1502 1503 1504 1505 1506 1510 1511 1512	Type TiL209 led TiL211 led TiL213 led FLV115 led FLV310 led FLV470 led BDL707 displi BDL727 displi BDL727 displi GRP12 Light resistor	ay ay dependent	Size 125 125 125 22 2 3 3	Colour RED GREEN YELLOW RED GREEN YELLOW RED RED RED	Price £0-10 £0-19 £0-19 £0-10 £0-19 £0-19 £0-19 £1-50 £1-80
1520	OCP71 Photo	transsisto	r		£0.35
1508/12 1508/2	LED CLIPS 5 pack of 5 pack of 5	125 clips 2 clips			£0:15 £0:18

2nd GRADE LEDs

A pack of 10 standard sizes and colours which fail to perform to their very rigid specification, but which are ideal for amateurs who do not require the full spec.

O/NO 107 £1.50

NUMERICAL INDICATORS
Cold cathode ITT 5087ST Side viewing indicator tubes. Displays 019 and decimal points. Wide viewing angle. Operates from 180v with 16Kohms series anode resistor. Character height 16-5mm. Pin connectors and supply details

5 per pack O/NO 1513 60p per pack

# **BRIDGE RECTIFIERS**

SILICON 1 amp Type 50V RMS 100V RMS 200V RMS 400V RMS	Order No. BR1/50 BR1/100 BR1/200 BR1/400	Price £0·20 £0·22 £0·25 £0·36
SILICON 2 amp 50V RMS 100V RMS 200V RMS 400V RMS 1000V RMS	BR2/50 BR2/100 BR2/200 BR2/400 BR2/1000	£0 -45 £0 -48 £0 -52 £0 -58 £0 -68
2 AR No. KBS005 No. KBS01 No. KBS02	MP METAL STUD MOUNT 50 voit 100 voit 200 voit	E0:30 £0:35 £0:40

## THYPICTORS

INTRIBIURS									
S00ma   TO 18 Case	7 Amp TO 48 Case Volts No. Price 50 THY7A/50 100 THY7A/100 £0-51 200 THY7A/200 £0-57 400 THY7A/400 £0-62 600 THY7A/800 £0-82 800 THY7A/800 £0-82								
1 amp TO 5 Case Volts No. Price 50 THY1A/50 66-28 100 THY1A/100 66-22 200 THY1A/200 66-32 400 THY1A/400 66-32	10 Amp TO 48 Case Volts No. Price S0 THY10A/50 £0: 51 100 THY10A/100 £0: 57 200 THY10A/200 £0: 62 400 THY10A/400 £0: 78 600 THY10A/800 £0: 88 800 THY10A/800 £0: 82 81: 22								

16 Amp

1 an		TO 5 Case
Volt	s No.	Price
50	THY1A/50	£0 · 26
100	THY1A/100	£0·28
200	THY1A/200	£0.32
400	THY1A/400	£0-38
600	THY1A/600	£0-45
800	THY1A/800	£0-50

3 an	np TO	66 Case
Volt	s No.	Price
50	THY3A/50	£0-28
100	THY3A/100	£0·30
200	THY3A/200	£0·33
400	THY3A/400	£0·42
600	THY3A/600	£0-50
800	THY3A/800	£0-65

5 Amp Voits No. 50 THY5A/50 100 THY5A/10 200 THY5A/40 600 THY5A/80 800 THY5A/80 5 Amp Voits No.	000000000000000000000000000000000000000	Price £0·36 £0·45 £0·50 £0·57 £0·69 £0·81	
Volt 400	s No. THY5A/40 THY5A/60	00P	Case Price £0:57 £0:69 £0:81

50 100 200	s No. THY16A THY16A THY16A	/50 /100 /200	Price £0-54 £0-58 £0-62
600 800		600	£0:77 £0:90 £1:39
50 100 200	S No. THY30A THY30A THY30A THY30A	/50 /100 /200 /400	Case Price £1:18 £1:43 £1:63 £1:79 £3:50
BT1 BT1 BT1 BT1 2N32	07 08 228		Price £0-80 £0-90 £1-25 £0-93 £0-68 £0-70 £0-77 £0-33

TO 48 Case

/600P /800P	£0·69 £0 81	C106/4	£0 · 60
		orget to state	order num

ORDERIE ber and your name and address,

V.A.T. Add 121% to prices marked\*. 8% to those unmarked. Items marked are zero rated.

P&P 35p unless otherwise shown.

# 930 SERIES DTL

0000

BP930	£0 · 30	BP948 £0-50
BP932	£0.30	BP951 £0-65
BP933	£0 · 30	BP962 £0.30
BP935	£0.30	BP9093 £0 · 42
BP936	£0.55	BP9094 £0 · 42
BP944	£0.30	BP9067 £0 · 42
BP945	£0.50	BP9099 £0-42
BP946	£0:30	

## D.I.Y. P.C.B. **ACCESSORIES**

1609. Etch resistant pen	65p
1608. Paks of etchant, complete with	80 p
instructions	,
C26. 4 pieces 8 × 3½" (approx.) boards	
Single-sided fibre glass	80p
C27. 3 pieces 7 × 3½" (approx.) boards.	
Double-sided fibre glass	60 p



DEPT. PE12, P.O. BOX 6, WARE, HERTS.

SHOP AT

18 BALDOCK ST., WARE, HERTS. OPEN 9 to 5.30 MON—SAT.

# **SEMICONDUCTORS**

# **TRANSISTORS**

Type Price AC107 £0·22 AC113 £0·20	Type Price BC119 £0·25 BC120 £0·40	Type Price BD183 £0.95	Type BSX20	Price	Type TIP41B	Price £0.51	Type 2N2712 2N2714	£0.22
AC115 £0 20	BC125 £0 17*	BD184 £1 · 10 BD185 £0 · 68	BSY25 BSY26	£0.16	TIP41C TIP42A	£0 · 53	2N2904	£0 22 £0 18
AC117 £0:30 AC117K £0:34	BC126 £0 22* BC132 £0 18* BC134 £0 18*	BD186 £0 68 BD187 £0 75	BSY27 BSY28	£0-16	TIP42B TIP42C	£0.55	2N2904A 2N2905 2N2905A	£0 21 £0 18 £0 20
AC121 £0 20 AC122 £0 14	BC135 £0 ·15*	BD188 £0 75 BD189 £0 78	BSY29 BSY38	£0-16 £0-19 £0-19	TIP2955 TIP3055	£0.65	2N2906A 2N2906A	£0 16
AC125 £0.18 AC126 £0.18	BC136 £0 18° BC137 £0 18°	BD190 £0.78 BD195 £0.90 BD196 £0.90	BSY39 BSY40	£0 29	TIS43 TIS90	£0.24	2N2907A	£0 · 20
AC127 £0·18 AC128 £0·18 AC128K £0·26	BC139 £0·32 BC140 £0·30 BC141 £0·28	BD197 £0.95	BSY41 BSY51	£0 · 29 £0 · 25 £0 · 13	UT46	£0·22	2N2923 2N2924	£0 22 £0 15° £0 15°
AC132 £0 20	BC142 £0 22	BD198 £0.95 BD199 £0.99	BSY95 BSY95A BRY39	£0·13	U146	E,0 · 22	2N2925 2N2926G	£0.15° £0.09°
AC134 £0 20 AC137 £0 20	BC143 £0 22 BC145 £0 46	BD200 £0.99 BD201 £0.80 BD202 £0.80	BU105 BU105/02	£0:45 £1:40 £1:95	ZTX107 ZTX108	£0.10*	2N2926Y 2N2926O	£0 08*
AC141 £0 22 AC141K £0 30 AC142 £0 20	BC147 £0.08° BC148 £0.08°	BD202 £0.80 BD201/202 £1.70 BD203 £0.80	BU204 BU205	£1 70	ZTX109	£0 10*	2N2926R 2N2926B	£0.08°
AC142 £0 20 AC142K £0 30 AC151 £0 20	BC149 £0.08° BC150 £0.20° BC151 £0.22°	BD204 £0.80 BD203/204 £1.70	BU208 BU208/02	£2·25	ZTX300 ZTX301 ZTX302	£0 12*	2N3010 2N3011	£0-65 £0-15
AC153 £0 22 AC153K £0 30	BC152 £0·20° BC153 £0·25°	BD205 £0 80 BD206 £0 80			ZTX303 ZTX304	£0 16*	2N3053 2N3054	£0-16 £0-40
AC154 £0 20 AC155 £0 20	BC154 £0-19*	BD207 £1.00 BD208 £1.00	E1222	£0 38	ZTX330 ZTX500	£0.15° £0.14°	2N3055 2N3391	£0 40
AC156 £0 20 AC157 £0 25	BC157 £0·10 BC158 £0·10* BC159 £0·10*	BD222 £0-47 BD225 £0-47			ZTX501 ZTX502	£0 12"	2N3391 A 2N3392	£0 20°
AC165 £0 20 AC166 £0 20	BC160 £0 32 BC161 £0 38	BD232 £0.55 BD233 £0.48	MAT100	£0:19	ZTX503 ZTX504	£0-12*	2N3393 2N3394	£0 20°
AC167 £0 20 AC168 £0 25 AC169 £0 20	BC167 £0·12* BC168 £0·12*	BD234 £0.55 BD235 £0.55 BD236 £0.58	MAT101 MAT120 MAT121	£0 19	ZT X531 ZT X550	£0 · 26 ° £0 · 16 °	2N3395 2N3402	£0 22°
AC169 £0 20 AC171 £0 25 AC176 £0 18	BC169 £0-12* BC169C £0-14* BC170 £0-10*	BD237 £0.55 BD238 £0.60	MJ480 MJ481	£0.95			2N3403 2N3404	£0 21 ° £0 29 ° £0 42 °
AC176K £0 26 AC178 £0 25	BC170 £0·10° BC171 £0·10° BC172 £0·10°	BDX32 £2-20 BDY11 £1-30	MJ490 MJ491	£0-95 £1-15	2G301 2G302 2G303	£0 22 £0 22 £0 22	2N3405 2N3414 2N3415	£0 16°
AC179 £0 25 AC180 £0 20	BC173 £0.12°	BDY17 £1 80 BDY20 £0 80	MJE340 MJE370	£0 45	2G304 2G306	£0 30	2N3416 2N3417	£0 29*
AC180K £0 28 AC181 £0 20	BC175 £0·35* BC177 £0·16	BDX77 £0.90 BF115 £0.22	MJE371 MJE520	£0.80	2G308 2G309	£0 · 36	2N3614 2N3615	£1:00 £1:05
AC181K £0 28 AC187 £0 18	BC178 £0 · 16 BC179 £0 · 16	BF117 £0.50 BF118 £0.75	MJE521 MJE2955	£0.72 £0.98	2G339 2G339A	£0 20	2N3616 2N3646	£1 · 05 £0 · 09*
AC187K £0 28 AC188 £0 18	BC180 £0 25 BC181 £0 25°	BF119 £0 75 BF121 £0 50° BF123 £0 60°	MJE3055 MJE3440 MP8113	£0.60 £0.52 £0.52	2G344 2G345	£0 · 20 £0 · 18	2N3702 2N3703	£0.08*
AC188K £0 28 ACY17 £0 32 ACY18 £0 26	BC182 £0 10° BC182L £0 10°	BF125 £0 50° BF127 £0 60°	MPF102 MPF104	£0.35	2G371 2G371B	£0 18	2N3704 2N3705	£0 07°
ACY18 £0·26 ACY19 £0·25 ACY20 £0·24	BC183 £0 10° BC183L £0 10° BC184 £0 10°	BF152 £0.25° BF153 £0.25°	MPF105 MPSA05	£0.38	2G373 2G374	£0.18	2N3706 2N3707	£0 08*
ACY21 £0.28 ACY22 £0.26	BC184L £0-10*	BF154 £0 22° BF155 £0 35	MPSA06 MPSA55	£0.28°	2G377 2G378	£0 32	2N3708 2N3708A	£0 07°
ACY27 £0 24 ACY28 £0 21 ACY29 £0 35	BC186 £0-22 BC187 £0-22 BC207 £0-11*	BF156 £0 · 28 BF157 £0 · 28	MPSA56 ND120	£0.28* £0.18	2G381 2G382	£0 18	2N3709 2N3710	£0.07°
ACY30 £0.25	BC208 £0 11° BC209 £0 12°	BF158 £0 35° BF159 £0 35° BF160 £0 30°			2G401 2G414	£0 32	2N3711 2N3772 2N3773	£0.07° £1.60 £2.50
ACY31 £0 25 ACY34 £0 25	BC212 £0.11° BC212L £0.11°	BF160 £0 30° BF162 £0 30° BF163 £0 30°	OC19	£0 85	2G417	£0 · 26	2N3819 2N3820	£0 · 20 £0 · 35
ACY35 £0.25 ACY36 £0.35	BC213 £0 11* BC213L £0 11*	BF164 £0 50° BF165 £0 50°	OC20 OC22 OC23	£1 -50	2N388	£0 36	2N3821 2N3823	£0-60
ACY40 £0 22 ACY41 £0 25 ACY44 £0 28	BC214 £0 12* BC214L £0 12*	BF167 £0 24 BF173 £0 20	OC24 OC25	£1 -35 £1 -00	2N388 A 2N404	£0 · 56 £0 · 20	2N3903 2N3904	£0-15** £0-15*
AD130 £0.70 AD140 £0.60	BC225 £0 26* BC226 £0 36*	BF176 £0.38* BF177 £0.26	OC26 OC28 OC29	£1.00	2N524 2N527	£0 40 £0 50	2N3905 2N3906	£0-15*
AD142 £0.85 AD143 £0.75	BC227 £0 16° BC238 £0 16° BC251 £0 15°	BF178 £0 · 28 BF179 £0 · 30	OC35	£0.95	2N598 2N599	£0 40 £0 46	2N4058 2N4059	£0-12*
AD149 £0-60 AD161 £0-42	BC251A £0.16*	BF180 £0 30 BF181 £0 30 BF182 £0 30	OC36 OC41	£0 90 £0 20 £0 22	2N696 2N697	£0 13	2N4060 2N4061	£0 14*
AD162 £0 42 AD161/162 £0 85	BC301 £0 28 BC302 £0 28 BC303 £0 28	BF182 £0 30 BF183 £0 30 BF184 £0 20	OC42 OC44 OC45	£0 24 £0 20	2N698 2N699	£0 12 £0 32	2N4062 2N4284	£0 12*
ADT140 £0.55 AF114 £0.21	BC304 £0 38 BC327 £0 16*	BF185 £0 20 BF186 £0 26*	OC70 OC71	£0 24	2N706 2N706A	£0 10	2N4285 2N4286	£0.18*
AF115 £0 21 AF116 £0 21 AF117 £0 21	BC328 £0:15" BC337 £0:15"	BF187 £0 26 BF188 £0 40	OC72 OC74	£0 · 24 £0 · 26	2N707 2N708	£0 48 £0 14	2N4287 2N4288 2N4289	£0 18" £0 18" £0 18"
AF118 £0 40 AF124 £0 30	BC338 £0 15" BC440 £0 30	BF194 £0.10° BF195 £0.10°	OC75 OC76	£0 · 30	2N711 2N717 2N718	£0 30 £0 30 £0 25	2N4290 2N4291	£0 18"
AF125 £0:30 AF126 £0:30	BC441 £0·30 BC460 £0·38	BF196 £0 10° BF197 £0 12°	OC77 OC81 OC81D	£0.50 £0.22 £0.24	2N718A 2N726	£0 50	2N4292 2N4292	£0:18*
AF127 £0 32 AF139 £0 35	BC461 £0 38 BC477 £0 20 BC478 £0 20	BF198 £0 14* BF199 £0 14* BF200 £0 30	OC82 OC82D	£0 24 £0 30	2N727 2N743	£0 · 29	2N4921 2N4923	£0 55*
AF178 £0 60 AF179 £0 60	BC478 £0 20 BC479 £0 20 BC547 £0 12*	BF202 £0 90° BF222 £0 90	OC83 OC84	£0 · 26 £0 · 38	2N744 2N914	£0.20	2N5135 2N5136	£0 10*
AF180 £0.60 AF181 £0.58	BC548 £0 12*	BF224 £0:17 BF240 £0:17*	OC139 OC140	£1 20	2N918 2N929	£0 30	2N5138 2N5172 2N5194	£0-10* £0-14* £0-56
AF186 £0·50 AF239 £0·38 AL102 £1·20	BC550 £0.14* BC556 £0.14*	BF241 £0 17° BF244 £0 30°	OC169 OC170	£0:35	2N930 2N946	£0-18 £0-40	2N5245 2N5294	£0 40 £0 34
AL103 £1 18 ASY26 £0 38	BC557 £0 13* BC558 £0 12*	BF257 £0 30 BF258 £0 30	OC171 OC200	£0 35 £0 38 £0 95	2N1131 2N1132	£0:18	2N5296 2N5257	£0 36 £0 32
ASY27 £0.40 ASY28 £0.38	BC559 £0.14* BCY30 £0.55	BF259 £0 42 BF262 £0 60* BF263 £0 60*	OC200 OC201 OC202 OC203 OC204	£1 · 20 £0 · 85	2N1302 2N1303 2N1304	£0:15 £0:18 £0:18	2N5458 2N5459	£0 32 £0 35 £0 36*
ASY29 £0.38 ASY50 £0.30	BCY31 £0 55 BCY32 £0 60	BF270 £0.36 BF271 £0.31	OC204 OC205	£0.90 £1.15	2N1305 2N1306	£0 18	2N5551 2N6027	£0 · 34
ASY51 £0 30 ASY52 £0 30	BCY33 £0 55 BCY34 £0 60 BCY70 £0 15 BCY71 £0 15	BF272 £0 80 BF273 £0 36° BF274 £0 38°			2N1307 2N1306	£0 25 £0 30	2N6121 2N6122	£0 70
ASY54 £0:30 ASY55 £0:30	BCY71 £0 15 BCY72 £0 14	BF324 £0 35°	P346A	£0·35	2N1309 2N1599	£0:30		
ASY56 £0:30 ASY57 £0:30 ASY58 £0:30	BCZ10 £0-60 BCZ11 £0-60 BCZ12 £0-60	BF336 £0 35 BF337 £0 30*	P397	£0·45	2N1613 2N1711	£0 20	2S 301 2S 302	£0 · 50 £0 · 43
ASY73 £0 30 AU104 £1 40	BCZ12 £0 60 BD115 £0 50	BF338 £0 38 BF457 £0 37 BF458 £0 37	R20008B	£2·50	2N1889 2N1890	£0:45 £0:45	25 302 A 25 303	£0 43 £0 56
AU110 £1 40 AU113 £1 40	BD116 £0 80 BD121 £0 65	BF459 £0 38	R2010B	£2 · 60	2N1893 2N2147 2N2148	£0 30 £0 75 £0 70	2S 304 2S 305	£0 71
	BD123 £0 65 BD124 £0 70	BF596 £0 28* BFR39 £0 24			2N2160 2N2192	£1.00	2S 306 2S 307	£0 80
BC107 £0.08	BD131 £0 38 BD132 £0 40	BFR40 £0.25° BFR79 £0.28°	ST140 ST141	£0 · 15	2N2192 2N2193 2N2194	£0.38	2S 321 2S 322	£0 57
BC107A £0 08 BC107B £0 09 BC107C £0 10	BD131/132 £0 ·85 BD133 £0 ·40	BFR80 £0 28* BFX29 £0 22			2N2217 2N2218	£0 22	2S 322 A 2S 323	£0:43 £0:57
BC107C £0·10 BC108 £0·08 BC108A £0·08	BD135 £0 38 BD136 £0 35	BFX30 £0 30 BFX84 £0 22	TIC44	£0 29° £0 35°	2N2218A 2N2219	£0 20 £0 20	2S 324 2S 325 2S 326	£0 71 £0 71 £0 71
BC108B £0 09	BD137 £0·35 BD138 £0·40 BD139 £0·36	BFX84 £0·22 BFX85 £0·24 BFX86 £0·25 BFX87 £0·22	TIC45 TIP29 A TIP29 B	£0 · 40 £0 · 52	2N2219A 2N2220	£0 24 £0 20	25 327	£0.71
BC109 £0 08 BC109A £0 08	BD140 £0.36 BD139/140 £0.80	BFX88 £0 22 BFX90 £0 55*	TIP29C TIP30A	£0.50	2N2221 2N2221 A	£0 20		
BC109B £0 09 BC109C £0 40	BD155 £0.80 BD175 £0.60	BFY50 £0-16 BFY51 £0-16	TIP30B TIP30C	£0-60	2N2222 2N2222A	£0 20	40360 40361	£0 · 36
BC113 £0.16*	BD176 £0 · 60 BD177 £0 · 68	BFY52 £0-16 BFY53 £0-16	TIP31A TIP31B	£0 45	2N2368 2N2369	£0:18 £0:14	40362 40406	£0 · 38
BC115 £0·19* BC116 £0·19*	BD178 £0 68 BD179 £0 75	BIP19 £0.38 BIP20 £0.38	TIP31C TIP32A	£0:49 £0:49	2N2369 A 2N2411	£0:14 £0:25	40407 40408	£0 35 £0 52
BC116A £0·19° BC117 £0·20° BC118 £0·14°	BD180 £0.75 BD181 £0.85	BIP19/20 £0-80 BPX25 £1-45	TIP32B TIP32C TIP41A	£0 51 £0 53	2N2412 2N2646 2N2711	£0.25 £0.47 £0.22	40409 40410 40411	£0 75 £0 75 £2 70
DC118 £0.14*	BD182 £0 90	BSX19 £0-18	IIP41A	£0·49	ZIAZ1]]	E0.72	40411	-2 10

# 74 SERIES TTL IC'S

Туре	Price	Туре	Price	Туре	Price	Туре	Price	Туре	Price
7400	£0 10	7427	£0 24	7472	£0.20	74105	£0 38	74163	£0 78
7401	£0.11	7428	£0.33	7473	£0.25	74107	£0·27	74164	£0.85
7402	£0 11	7430	£0 12	7474	€0 . 25	74110	£0 · 45	741€5	£0.85
7403	£0-11	7432	€0.22	7475	€0.29	74111	£0.67	74166	£0.95
7404	£0-11	7433	£0 30	7476	£0 · 25	74118	£0.80	74174	£0.86
7405	£0.11	7437	£0 · 23	7480	£0:44	74119	£1-18	74175	£0.66
7406	£0 · 26	7438	£0 · 23	7481	£0.85	74121	£0 · 24	74176	£0.74
7407	£0.26	7440	£0.12	7482	£0 · 68	74122	€0 39	74177	£0.75
7408	£0:13	7441	€0.50	7483	€0.70	74123	£0-46	74180	£0.84
7409	£0-13	7442	£0.54	7484	£0.88	74136	£0.74	74181	£1 · 60
7410	£0·12	7443	€0.88	7485	£0 88	74141	£0 .55	74182	£0.74
7411	£0·17	7444	£0.88	7486	£0 25	74145	£0-62	74184	£1-18
7412	£0 · 20	7445	£0.65		£1 . 95	74150	£0 95	74190	£1.00
7413	£0 24	7446	£0.65	7489		74151	£0 58	74190	£1.00
7414	£0 · 50			7490	£0:32		£0.58	74192	£0 95
7416	£0 · 26	7447	£0 60	7491		74153	£0.95	74193	£1 00
7417	£0.26	7448	£0-56	7492	£0.37	74154			£0 89
7420	£0 12	7450	£0 12	7493	£0 30	74155	£0.60	74194	
7421	£0·20	7451	£0-12	7494	£0.75	74156	£0 60	74195	£0 82
7422	£0 · 16	7453	£0-12	7495	£0 · 50	74157	€0 60	74196	£0.88
7423	£0 23	7454	£0·12	7496	£0 62	74160	£0.78	74197	£0 · 85
7425	£0·19	7460	£0 12	74100	£0 92	74161	£0.78	74198	£1 45
7426	£0 · 23	7470	£0 25	74104	£0 · 39	74162	£0 · 78	74199	£1:45

# **CMOS ICs**

Type Price CD4000 £0 15 CD4001 £0 18 CD4002 £0 18 CD4006 £0 98 CD4008 £0 98 CD4008 £0 58 CD4010 £0 58 CD4010 £0 58 CD4011 £0 25	Type Price CD4015 £0 98 CD4016 £0 50 CD4017 £0 98 CD4018 £1 00 CD4019 £0 55 CD4020 £1 10 CD4021 £0 98 CD4022 £0 90 CD4023 £0 20	Type CD4026 £1 70 CD4026 £1 70 CD4027 £0 60 CD4028 £0 98 CD4029 £1 15 CD4030 £0 55 CD4031 £2 20 CD4035 £1 30 CD4037 £0 95 CD4040 £0 95	Type Price CD4043 £0 98 CD4044 £0 99 CD4045 £1 40 CD4046 £1 30 CD4047 £1 10 CD4049 £0 55 CD4050 £0 55 CD4050 £0 55 CD4055 £1 40	Type Price CD4070 £0-43 CD4071 £0-23 CD4081 £0-23 CD4082 £0-23 CD4510 £1-30 CD4511 £1-40 CD4518 £1-25
CD4011 £0-20 CD4012 £0-20 CD4013 £0-52	CD4023 £0 20 CD4024 £0 80 CD4025 £0 20	CD4040 £0-95 CD4041 £0-82 CD4042 £0-82	CD4055 £1 40 CC4056 £1 35 CD4069 £0 40	CD4518 £1·25 CD4520 £1·25

# LINEAR ICs

1	Type	Price	Type	Price	Туре	Price	Type	Price	Type P	rice
ı			CA3130	£0 93	MC1350	£1 - 20°	UA710C	£0.40°	SN76115£1	90*
ı	CA3014	£1 .70°	CA3140	£0.90	MC1352	£1 -40*			SN76660£0	·75°
ı	CA3018	£0.75°		F0.39.	MC1460	£2.05	UA711C	£0 32	SL414A £1	95°
ı	CA3020	£1:70*	LM304	£1 60	MC1496	£0.98°			TAA550B	
ı	CA3028	£1 · 02*		E1 · 40*	NE536		11A793C	£0.45	£ £	0.35
ı	CA3035	£1.70°	LM309	£1 · 50	NE550	£0.95	72723	£0.45	TA A621 A	
ı	CA3036	£1 35°	LM320-5v	£1 · 50	NE555		UA/41C	E.U . 24 "	£2	.00
ı	CA3042	£1 · 50°	LM320-12	£1.50	NESSS	£0.82	12141	E0.54		
١	CA3043	£1 85"	LM320-15	£1 50	NE565	£1 .75°	741P UA747C	£0.20*	TAA661 £1	·65°
1	CA3046	£0.80°	LM320-24	#1 50	NE566	£1.50*	72747	£0.79*	TAD100 £1	· 30*
ı	CA3052	£1 60°	LIVISOU I	C4 EE*	NE567	£1 80°	114749		TBA540 £2	
ı	CA3054	£1 .35"	I M3000	C1 33	UA702C	£0-46*	70749	£0.35*	TBA800 £0	
١	CA3075	£1.50°	MC1303L	C1 . 48*	72702	£0.46°	748P SN76013	€0.35*	TBA810 £1	-05*
ı	CA3081	£1.50*	MC1304		UA703	£0 25*	SN76013	N	TBA820 £0	
ı	CA3089	£2-10"	MC1310 4		UA709	£0 25"		£1 · 75*	TBA9200£3	
ı	CA3090	£4 . 25"	MC1312 #	E1 -90*	72709	£0.46*	SN76023	£1.75*	TCA270S	
ı	CA3123	£1 90°	MC1330 4	E1 · 20 *	709P	£0.25°	SN76110	£1.50°	£2	20*
ı	CASIZS	21 90	10101000	.,	1031	20 23	_			

# DIODES

		TRI	ACS		
2 amp Volts 100 200 400	TO5 Case No. TR12a/100 TR12a/200 TR12a/400	Price £0:31 £0:51 £0:71	10 Amp Volts 100 200 400	TO48 Case No. TR110a/100 TR100a/200 TR100a/400	Price £0:77 £0:92 £1:12
6 Amp Volts 100 200 400	TO66 Case No. TR16a/100 TR16a/200 TR16a/400	Price £0 51 £0 61 £0 77	10 Amp Volts 400 BR100	TO220 Plastic No. TR110a/400p DIACS £0-20 D32	Case Price £1:12

# VISIT US AT BREADBOARD SEYMOUR HALL, LONDON, W.I

NOV. 21st—25th

10 a.m. to 7 p.m.

STANDS E2.E3.F2.F3.E10.E11




DEPT. PE12, P.O. BOX 6, WARE, HERTS.

SHOP

18 BALDOCK ST., WARE, HERTS. OPEN 9 to 5.30 MON—SAT.

# KITS FOR SYNTHESISERS, SOUND EFFECTS

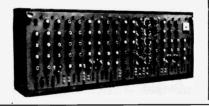

COMPONENTS SETS include all necessary resistor's capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits, PCBs and parts are shown in our lists.

CIRCUIT AND LAYOUT DIAGRAMS are supplied free with all PCBs unless "as published".

PHOTOCOPIES of P.E. texts for most of the kits are available--prices in our lists.

# PHONOSONI

PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.

P.E. MINISONIC Mk. 2 SYNTHESISER
A portable mains-operated Miniature Sound Synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser the function offered by this design give it great scope and versatility. Consists of 2 log VCOs. VCF. 2 envelope shapers, 2 voltage controlled amps, keyboard hold and control circuits. HF oscillator and detector, ring modulator, noise generator, mixer coversupply.

ixer, power supply.
Set of basic component kits
Set of printed circuit boards

from £61-00

P.E. SYNTHESISER (P.E. Feb. 73 to Feb. 74)
The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits. Other circuits in our lists may be used with the Synthesiser to good advantage.

The Main Synthesiser: PSU, 2 linear VCOs, 2 ramp generators, 2 input amps, sample hold, noise generator, reverb amp, ring modulator, peak level circuit, envelope shaper, voltage controlled amp.

Set of basic component kits

Set of printed circuit boards

The Synthesiser Keyboard Circuits (can be used without the Main Synthesiser to make an independent musical instrument): 2 logarithmic VCOs, divider, 2 hold circuits, 2 modulation amps, xer, 2 envelope shapers and PSU. Set of basic component kits

Set of printed circuit boards

GUITAR EFFECTS PEDAL (P.E. July 75)
Modulates the attack, decay and filter characteristics of an audio signal not only from a guitar but from any audio source. Producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range. Circuit does not duplicate effects from the Guitar Overdrive Unit.

Component set with special foot operated switches Alternative component set with panel switches Printed circuit board

£7-69 £5-05

SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice-operated fader, automatic fader and frequency-doubler.

Component set for above functions (excl. SWs)

Printed circuit board

Chippels extra sadditional Audio Mediators, the use

Component set (incl. PCB)

£1.81

Optional extra—additional Audio Modulator, the use of which, in conjunction with the above component set, can produce 'jungle-drum' rhythms.

£2.88

PHASING UNIT (P.E. Sept. 73)
A simple but effective manually controlled unit for introducing the phasing sound into live or recorded

Component set (incl. PCB)

# PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing.

Component set (incl. PCB) £4.74

SOPHISTICATED PHASING AND VIBRATO UNIT
A slightly modified version of the circuit published in
"Elektor". December 1976, and includes manual and
automatic control over the rate of phasing and vibrato. Component set £17-38 Printed circuit board

WAH-WAH UNIT (P.E. Apr. 76)
The Wah-Wah effect produced by this unit can be controlled manually or by the integral automatic controller.
Component set (incl. PCB) £3-63

# AUTOWAH UNIT (P.E. Mar. 77)

Automatically produces Wah-pedal and Swell-pedal sounds each time a new note is played.

Component set, PCB, special foot switches £7-67

Component set and PCB, with panel switches £4-83

## P.E. JOANNA PLUS ORGAN VUICING

The basic five octave electronic piano (P.E. May/Sept 75 and Sound Design) has switchable alternative voicings for Honky-Sound Design) has switchable alternative volcings for Honky-Tonk, ordinary piano, and Harpsichord or a mixture of any of these three, together with facilities including fast and slow tremolo, loud and soft pedal switching, and sustain pedal switching. The modification retains all the circuitry associated with the piano but in addition provides an organ-voice envelope facility with 5 switchable pitches, variable attack and sustain, phasing and

Set of components (excl switches) for PSU. Frequency generator, Pitch and Note Divider, Envelope Shapers, Voicings, and Control circuitries. (Order as KIT 71-5) £99-25 Set of PCBs (Order as PCB SET 71-6)

SYNTHESISER TUNING INDICATOR (P.E. July 77)
A simple 4-octave frequency comparator for use with synthesisers and other instruments where the full versatility of the P.E. Tuning Fork is not required.

Component and PCB (but excl sw.)

## **GUITAR FREQUENCY DOUBLER (P.E. Aug. 77)**

A modified and extended version of the circuit published Component set and PCB £4-52

## **GUITAR SUSTAIN (P.E. Oct 77)**

Maintains the natural attack whilst extending note duration.

Component set, PCB and foot switches £5.13

Component set, PCB and panel switches £3.71

A manually controlled unit for producing the above-named

Component set (incl. PCB)

GUITAR OVERDRIVE UNIT (P.E. Aug. 76)
Sophisticated, versatile Fuzz unit, including variable and switchable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Does not duplicate the effects from the Guitar Effects Pedal and can be used with it and with other electronic instruments.
Component set using dual silder pot Component set using dual silder pot Component set using dual rotary pot E6-89

Printed circuit board

# FUZZ UNIT

Simple Fuzz unit based upon P.E. "Sound Design" circult Component set (incl. PCB) £2.05 £2-05

TREMOLO UNIT
Based upon P.E. "Sound Design" circuit.
Component set (incl. PCB) £2.94

TREBLE BOOST UNIT (P.E. Apr. 76)
Gives a much shriller quality to audio signals fed through it.
The depth of boost is manually adjustable.
Component set (incl. PCB)
£2.51

# P.E. TUNING FORK (P.E. Nov. 75)

Produces 84 switch-selected frequency-accurate tones. A LED monitor clearly displays all beat note adjustments, Ideal for tuning acoustic or electronic musical instruments. Main component set (incl. PCB) £14-93

Power supply set (incl. PCB)

New Electronic Piano. Elektor Aug. 1978 Details in our list.

# **CONSTANT DISPLAY FREQUENCY METER (PE AUG 78)**

A 5-digit frequency counter for 1Hz to 99999Hz with a 1Hz sampling rate. Readout does not count visibly or flicker due to display blanking.

Component set Printed circuit board

£3-034 This kit & PCB are at B% VAT (all others are 12 1%)

## TAPE NOISE LIMITER

IAPE NUISE LIMITER
Very effective circuit for reducing the hiss found in most tape
recordings. All kits include PCBs
Standard tolerance set of components
Superior tolerance set of components
Regulated power supply (will drive 2 sets)
£4-69

# **ENVELOPE SHAPER WITHOUT VCA (P.E. Oct. 75)**

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing voltage controlled amplifier.

Component set (incl. PCB)

ENVELOPE SHAPER WITH VCA (P.E. Apr. 76)
This unit has its own voltage controlled amplifier and has full manual control over attack, decay, sustain and release functions. Component set (incl. PCB)

TRANSIENT GENERATOR (P.E. Apr. 77)

An envelope shaper, without VCA: having the usual attack, decay, sustain and release functions, and in addition it also provides a "Repeat Effect" enabling a synthesiser to be programmed to imitate such instruments as a mandolin or banjo.

Component set
Printed circuit board

Table 1.82

# WAVEFORM CONVERTER

Slightly modified from a circuit published in "Elektor". Converts a saw-tooth waveform into four different waveforms: sine-wave, mark-space saw-tooth, regular triangle form, and squarewave with an externally variable mark-space ratio. Component set (incl. PCB but excl. sw/s) £8-40

# **VOLTAGE CONTROLLED FILTER (P.E. Dec. 74)**

Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.

Component set (incl. PCB) (Order as Kit 65-1) £7.17

RING MODULATOR (P.E. Jan. 75)
Part of the P.E. Minisonic now released as an independent kit for use with other synthesisers.
Component set (incl. PCB) (Order as Kit 59-1) £5-50

NOISE GENERATOR (P.E. Jan. 75)
Part of the P.E. Minisonic now released as an independent kit for use with other synthesises.
Component set (incl. PCB ) (Order as Kit 60-1) £3-84

# SOPHISTICATED POWER SUPPLIES

A wide range of highly stabilised low noise power supply kits is available—details in our lists.

MICROPHONE PRE-AMP (P.E. Apr. 77)
Component set (incl. PCB)

# VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during talk-over'—particularly useful for Disco work or for home-movie shows.

Component set (incl. PCB) £3.97

DYNAMIC RANGE LIMITER (P.E. Apr. 77)
Automatically controls sound output to within a preset level.
Component set (incl. PCB)
£4-58

# POST AND HANDLING

POST AND HANDLING
U.K. orders—under £15 add 25p plus VAT, over £15 add 50p
plus VAT. Keyboards £2.00 plus VAT.
Optional Insurance for compensation against loss or damage
in post, add extra 50p for cover up to £50, £1.00 for £100 cover, £2-00 for £200 cover.
Eire, C.I., B.F.P.O., and other countries are subject to Export postage rates.

# DON'T FORGET VAT!

Add 123% (or current rate if changed) to full total of goods, post and handling. (Does not apply to export orders).

EXPORT ORDERS are welcome, though we advise that a current copy of our list should be obtained before ordering as it also shows Export postage rates. All payments must be cash-with-order, in Sterling and preferably by International Money Order or through an English Bank. To obtain list send 50p.

PHONOSONICS · DEPT. PEGN · 22 HIGH STREET · SIDCUP · KENT DA14 GEH SORRY BUT NO CALLERS PLEASE

# AND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P E projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

OVERSEAS enquiries for list Europesend 20p: other countries-—send 50p.



# KIMBER-ALLEN KEYBOARDS AND CONTACTS

Kimber-Allen Keyboards as required for many published circuits. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust alluminium frame.

\$10.5 pring-loader. Ittes with actuality, and mounted on a load shall be \$25.50
\$1.0 Cetave (137 notes)
\$1.2 Cetave (149 notes)
\$1.2 Cetave (161 notes)
\$1.2 Cetave (161 notes)

Contact Assemblies (gold-clad wire) for use with the above keyboards (1 required for each

iote):	
Type GJ: Single-pole change-over	each <b>25</b> }p
Type GB: 2 pairs of contacts, each pair normally open	each 28∮p
Type GC: 3 pairs of contacts, each pair normally open	each 37∳p
Type GE: 4 pairs of contacts, each pair normally open	each <b>46‡p</b>
Type GH: 5 pairs of contacts, each pair normally open	each <b>58</b> 1/p
Type 4PS: 3 pairs of contacts plus single-pole changeover	each 57p

Printed Circuit Boards for use with GJ, GB and 4PS contacts (thus eliminating much interwiring) are available. Details in our lists.

## RHYTHM GENERATOR

15-Rhythm Tempo, Timing and Logic control unit	(excl. sw's
but incl. PCB)	£9.75
10-Instrument Effects circuits	£14-23
PCB for Effects circuits	£4-25
Power Supply incl. PCB	£8.75

## 128-NOTE TUNE-PROGRAMMABLE SEQUENCER

## (P.E. Nov/Dec 77)

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable. (Please use order codes quoted in brackets.)

Main Circuit (Nov) excl. sw's (KIT 76-1)	£18-03
Power Supply (KIT 76-3)	£4.72
Trigger Inverter and Alt. Output (KIT 76-2)	£1-15
LED Counter (KIT 76-4)	£2-10
PCB (as published) for KITS 76-1 & 3 (PCB 76A)	£2-61
PCB for KITS 76-2 & 4 (PCB 76B)	£2.54

# P.E. STRING ENSEMBLE (PE Mar-July 78)

The new keyboard string-instrument synthesiser.	
Basic component sets:	
Power Supply (KIT 77-1)	£8.77
Tone Generator (KIT 77-2)	£14-66
Diode Gates (KIT 77-3)	£18-81
Chorus Generator (KIT 77-4)	£19-08
Voicing System (KIT 77-5)	£7.38
Printed Circuit Boards:	
Double-sided PCB for Power Supply, Tone Generator	& Diode

Printed Circuit Boards:
Double-sided PCB for Power Supply, Tone Generator & Diode
Gates with most of the Matrix wiring as printed tracking
(PCB 77L/R)
PCB for Chorus Generator (PCB 77C)
FCB for Voicing System (PCB 77D)
Fuller details of kits & PCBs are in our lists.

# FORMANT SYNTHESISER (Elektor 1977/78)

Very sophisticated music synthesiser for the advanced constructor who puts performance before price. Details in our lists.

# DISCOSTROBE (P.E. Nov. 76)

4-channel light-show controller giving a choice of sequential, random, or full strobe mode of operation.

Basic component set Printed circuit board £18.19

# BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie-detector, alphaphone, cardiophone etc.

£3.95
set
ency
£6.59
£7.75

# 10% DISCOUNT VOUCHER (PE6N)

TERMS: Correctly costed, C.W.O., U.K. orders over £50 goods value. Valid until end of month on cover of P.E. This voucher must accompany order.

# TRANSISTORS

AC12B	32p
AC176	28p
BC107	
BC108	13р
BC109	
BC109C	
BC177	
BC184	
BC187	18p
BC204 BC209C	10p
BC209C	13p
BC262	
BC47B	
BD131	
BD132	440
BF244A	
8F245A	
BSY95A	22p
MD8001	210p
OC71	200
OC72	30p
RPY58A	62p
TIS43	50p
ZTX108	71p
ZTX301	71p
ZTX384	12p
ZTX501	13p
2N2219	28p
2N2646	
2N2905	
2N2905A	29p
2N2906	22p
2N2907	
2N3054	
2N3055	
2N3702	
2N3704	
2N3819	
2N3820 2N3B23E	
2N3D23E	45p
2N5459	70p

# INTEGRATED CIRCUITS

301 8-pin DIL	48p
31B 8-pin DIL	220p
320-15	195p
324 14-pin DIL	87p
341-15	87p
709 8-pin DIL	48p
723 T05	87p
723 14-pin DIL	51p
726 TO5	1005p
741 8-pin DIL	24p
748 8-pin DIL	57p
4007 14-pin DIL	17‡p
4011 14 pin DIL	17 p
4024 14-pin DIL	46 p
4024 14-pin Dit	18p
4069 14-pin DIL	126p
4136 14-pin DIL	
AM2833 B-pin DIL	360p
AY10212 16-pin DI	LO1/P
AY16721/6	188p
CA3046 14-pin DI	L /ip
CA3080 8-pin DIL	63p
CA3084 14-pin DI	L209p
FX209 16-pin DI	L729p
LM323	562p
M252 16-pin DI	L680p
MC3340 B-pin DIL	150p
MCM6810 24-pin DI	L670p
SG3402N 14-pin Di	L262p
STK025	595p
TDA1022 16-pin Di	L582p
XR2207 14-pin Di	L420p
ZN425E 16-pin Di	L375p

PRICES ARE CORRECT AT TIME OF PRESS.
E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.

**PHONOSONICS** 

# **ELECTRONI·KIT**

# "EDUCATIONAL KITS OF EXCEPTIONAL QUALITY"

(AUDIO magazine)



# THIS IS A POWERFUL RADIO RECEIVER!

# The same kit is also 150 other different actual working projects e.g.:

Computer & Logic Circuits, Electronic Organ, Timer, Light Control, Agility Tester, Lie Detector, Siren, Horn, Buzzer, Bird, Metronome. Cds cell light & sound control, Photogun, Light Oscillator, Light Switch, Light and Sound Morse Code. Field Strength Meter, Hygrometer, Sphygometer, Etc., Etc. Radio Receiver, Transmitter, Amplifier, Audio Generator, Signal Tracer & Injector, Continuity Tester, Telegraph, Photoradio Receiver, Radio Receiver/Microphone Mixer. Illuminometer, Voltmeter, Ammeter, Sound Level Meter, Ohmmeter, Diode & Transistor Tester, Transparency Indicator, Etc., Etc.

The above is just a *selection* of the circuits available—you can also design your own circuits with these superb new Denshi-Gakken "EX" construction kits.

No previous experience of electronics is required but you learn as you construct and have a great deal of fun too. The kits are completely safe for *anyone* to use.

Kits are complete with very extensive construction manuals PLUS Hamlyn's "All-Colour" 160 page book "Electronics" (free of charge whilst stocks last).

ALL KITS ARE FULLY GUARANTEED. Addon sets (to increase the scope of each kit) are available, plus spares and accessories as required. 150 PROJECT KIT £39.75 60 PROJECT KIT £25.75 120 PROJECT KIT £33.75 30 PROJECT KIT £18.95 100 PROJECT KIT £29.25 15 PROJECT KIT £16.75

Prices include educational manuals, free book, VAT, p & p (in the U.K.), free introduction to the British Amateur Electronics Club.

Callers at 20 Bride Lane will be very welcome. Trade and Educational enquiries invited.

Cheque/P.O./Barclaycard/Access No. (or 14p for illustrated literature) to DEPT. PE.

ELECTRONI-KIT

20 BRIDE LANE, LUDGATE CIRCUS,
LONDON, EC4Y 8DX (01-353 6430)

# GODDARD'S COMPONENTS MAIL ORDER

110 LONDON ROAD, ST. ALBANS. HERTS. AL1 1NX

Callers Welcome MON-SAT: 9.30-5.30

THURS: Closed all day


SHOCK-PROOF

POLYSTYROL IN GREY 4mm thick walls

Lunch: MON-FRI: 1.30-2.30, SAT: 1.00-2.00

ALL PRICES INCLUDE VAT

# STFRFO

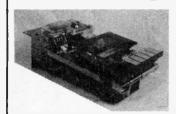

£25.75 + £1.25 p&p

CASSETTE RECORDER DECK **AND PRE AMPLIFIERS** 

with + solenoid auto-ston

- + Cr02 switch
- + piano key operation
- + twin level meters

+ mic. sockets

Tech. Spec.: Bias and erase freq. 88 kHz 8 Transistors 1 SCR 10 Diodes

Power supply extra Circuits, Diagrams and top panel template supplied Top Plate £3.50 + 50p P&P

# T-BOX



1001 -90p 1004 - £2.001002 - £1.60 1005 - £3.00 1003 - £1.80 50p each p&p. £1.00 for 3 p&p

Larger sizes are pillar fixing Smaller sizes are slotted Inside Measurements: Box No. | Breadth Height ' Weight 1001 60 an 50

100 1002 75 130 61 175 1003 90 160 71 2B5 1004 193 340 93 95 1005 125 220 110

TRADE ENQUIRIES WELCOME!

# DIGITAL CLOCK

**BATTERY DROP LEAF** CLOCK MOVEMENT

Hrs. Mins. Date Easy-to-set regulator screw Size: 140mm x 85mm x 60mm Window size: 63mm x 28mm No. height: 19mm Date height: 10mm Weight: 270gm



£4.95 + 50p p&p

# CD WATCHES

**TOUCH GENTS** CTG

**UNISEX C551** 6 Colours

£11.95

LADIES S/S C652 £16.95

LARGE GENTS C165




ALL WATCHES 5 FUNCTION ... 1 YEAR GUARANTEE P&P 50p per watch, Inc. Insurance

# AT LAST! AVAILABLE IN KIT FOR

THE FAMOUS POCKETSIZE **METAL DETECTOR** 

Seemet readily detects concealed ferrous and non-ferrous metals within range of its detector field. Ideal for finding concealed pipes, wires, nails etc. One-handed operation, uses standard PP3 Battery (not supplied).

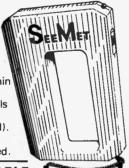ONLY £3.25 plus p. & p. 25p. (inc. VAT), full instructions supplied.



**BLOCK CAPS PLEASE** 



I enclose cheque/P.O.

# **UNBEATABLE DIMMER OFFER**

from Britain's largest Dimmer Makers.

Complete Kit of Parts for our VCL 500M, 500W Dimmer Switch. Only £2.00, plus p. & p. 25p. (inc. VAT) full instructions supplied.

Send coupon below with your remittance.

Please supply: SEEMET KITS PE3 NAME at £3.50 incl. of p. & p. ADDRESS DIMMER KITS at £2.25 inc. of p. & p

Fotherby, Willis Electronics Ltd.

**POSTCODE** 

GLADSTONE TERRACE, STANNINGLEY, LEEDS, LS28 6NE. Telephone: Leeds (STD 0532) 563373 Telex: 557111 GLYNWED 100 MINIATURE SILICON DIODES CV 9637 with preformed leads for 50p,

£4 per 1000. UNIJUNCTION TRANSISTORS 2N 4871, @ 22p, 2N 6028 @ 25p, 2N 6029 @ 25p,

UNIJUNCTION TRANSISTORS 2N 49/1, @ 22p, 2N 6029 @ 25p, 2N 6029 @ MEV 21 @ 22p, MV 4894 @ 22p, AJDSE29 @ 22p, Similar to TIS 43 @ 20p. SILICON PNP TO 3 POWER TRANSISTORS 2N 3792 @ 55p, BDX 94 @ 75p. CMOS RCA or NATIONAL CD 4001 @ 10p, CD 407 @ 10p, CD 4011 @ 10p, CD 4020 @ 60p, CD 4029 @ 60p, CD 4042 @ 60p. MULLARD TAA 320 MOST PRE-AMPLIFIER I.C. with circuits for Level Sensor

at 35p.
50 BC 107-8-9 TRANSISTORS Assorted Untested @ 57p.
50 BC 107-8-9 TRANSISTORS Branded but untested @ 57p.
TANTALUM BEAD CAPACITORS. 1uf 35v.w., 33uf 35v.w., 47uf 35v.w., 1uf 35v.w., 2.2uf 35v.w., 33uf 16v.w., 47uf 35v.w., 10uf 10v.w., 10uf 25v.w., 20uf 6v.w., 22uf 16v.w., 133uf 10v.w., 47uf 6v.w., All at 9p each. 100uf 3v.w., @ 15p.
100uf 10v.w., @ 25p, 330uf 3v.w. @ 15p.
SIGNETICS FM 1.C. ULN 2111A @ 50p.
TRANSFORMERS 240 volt AC Input Type 1. 22-0-22 volt 500mA @ £1.60 (P&P 25p). Type 2. 24 volt Tapped at 14 volt 1 amp @ £1.30 (P&P 25p). Type 3. 45 volt & Amp £5 @ (P&P 95p), Type 4. 50 volt 2 Amp, 45 volt 500mA @ £3.50 (P&P 85p), Type 5. 20 volt 1 amp Twice, 10 volt 1 Amp Twice @£4.50 (P&P 95).
MEDIUM POWER TRANSISTORS MP 8112 @ 15p. MP 8512 @ 16p.

MEDIUM POWER TRANSISTORS MP 81 12 @ 15p, MP 85 12 @ 15p.
MINIATURE ROTARY SWITCHES 2P 4W @ 20p, 3P 3W @ 40p, 1P 10W 2 Bank

@ 40p.
5 WATT NPN DARLINGTON TRANSISTORS @ 20p. 3 for 50p.

100 C280 CAPACITORS Assorted for 57p.
20 PHOTO TRANSISTORS AND DARLINGTONS Assorted Untested @ £1.
McMURDO 8 Pin Plugs @ 20p, 8 Pin Sockets @ 20p, Covers @ 15p.
10 ASSORTED MULTI TURN TRIM POTENTIOMETERS @ 60p.
S.C.R's 10 Amp Type 100 PIV @ 25p, 400 PIV @ 50p, 800 PIV @ 60p.
3 PIN PLUG AND SOCKETS like R.S. European type with two metres of Cable

@ 75p pair.

1uf 25v.w., ELECTROLYTIC CAPACITORS @ 6 for 25p.

400mW GOOD ZENERS Unmarked. 3.6v, 6.8v, 10v, 11v, 12v, 13v, 16v, 18v, 24v, 30v 33v. 36v all at 10 for 40p.

339, 36v all at 10 for 40p.

5 TURN POTENTIOMETERS 5K @ £1, Ten Turn 1K, 5K, 100K @ £1.50.

50 TWO WATT ZENERS Assorted Untested @ 57p.

AUDIO I.C.'s SN 76001N @ 50p. TAA 820 @ 50p. TBA 800 @ 80p. TBA 810 @ £1,

SL 414 @ £1.50, SN 76013ND @ £1.

DISC CERAMICS .01uf 50v.w. @ 20p doz ..1uf 18v.w. @ 25p doz.

26 ASSORTED PRE-SET POTENTIOMETERS for 57p.

CLOCK P.C. BOARDS with Suzzer, Mercury Switch, Sridge Rectifiers, Transistors etc.

Please add 20p for post and packing, unless otherwise stated, on U.K. orders under £2.

Overseas orders at cost.

# J. BIRKETT **RADIO COMPONENT SUPPLIES** 25 The Strait, Lincoln LN2 1JF Tel. 20767

for £

7400	001 17p 002 17p 006 95p 007 18p 008 80p	93 SERIES 9301 1 9302 1	VEROBOARD	FRANSISTORS AC126 25p BFX86/7 30p		DIODES ZENEERS
74172 720P 1/4LS298 249P 1 81LS	009 40p 100 50p 1010 50p 1011 17p 1012 18p 1013 50p 1011 18p 1013 50p 1014 84p 1015 84p 1016 45p 1016 45p 1017 100p 1018 89p 1018 89p 1019 45p 1019 100p 1019 110p 1021 110p 1021 110p 1023 22p 1028 100p 1021 100p 1023 100p 1024 80p 1031 200p 1033 180p 1033 180p 1034 200p 1031 200p 1033 100p 1041 80p 1043 100p 1044 90p 1044 90p 1044 90p 1044 90p 1044 90p 1044 90p 1045 110p 1046 110p 1047 100p 1048 55p 1050 49p 1051 80p 1	9308 9319 9310 2 8311 2 9314 1 9314 1 9316 2 9321 2 9322 1 9324 2 9322 2 93268 2 9370 2 9374 2  BUCKED BRIGADE* SAD1024 11  LINEAR I.Cs **Ay1-021 2 *Ay1-1313 6 *Ay1-1313 7 *A	Comper class   Comp	AC127/8 25p BFX88 30p- AC127/8 25p BFW10 90p- AC187/8 25p BFW10 90p- AC187/8 25p BFW10 90p- AC187/8 25p BFW50 22p- AF116/7 30p BFY51/2 22p- AF16/7 30p BFY51/2 22p- AF16/7 30p BFY51/2 22p- AF16/7 30p BFY51/2 22p- BFW50 30p BFW50 200p- BFW50 30p MU2955 10p- BFW50 30p MPF103/4 APP-BFW50 30p MPF103/	PEVDU	**BY127**
RESISTORS High Stab Carbon in the stab of	ch valve <b>0p</b> /100 each v orz/Vert	valve	VEROBOARDS IC BREADBOARD (20 × 14 pin DIL ICs or 16 × 16 pin DIL ICs) 4.15" × 6.15" 270p  VQ BOARD Specially designed for DIL ICs - No track	ANTEX SOLDERING IRONS  Model C 15W 360p CX 17W 360p X25 360p CCN 380p  Spare Bits C/CX/CCN 46p	and a free Power S Trouble-shooting s kits or modules pur	ude VAT and P&P upply circuit design) ervices available for

**VAT RATE:** All items at 8% except where marked\* where  $12\frac{1}{2}\%$  applies.

Please add 25p p&p & VAT at appropriate rates.

Government, Colleges, etc. Orders accepted.

CALLERS WELCOME

Mon.-Fri. 9.30-5.30 Saturday 10.30-4.30

# TECHNOMATIC LTD.

17 Burnley Road, London NW10 (2 minutes Dollis Hill tube station) (ample street parking)
Tel: 01-452 1500 Telex: 922800

PLEASE SEND SAE FOR LIST.

1

# 

ACE MAILTRONIX LTD Dept. PE, Tootal Street

You must try our fabulous new range of 'ELEKITS' for an easy build introduction to electronics. All kits, and there are many to choose from, come complete with case, to follow instructions and COMPONENTS. Battery powered (not supplied) | for , safety and economy ELEKITS will give hours of enjoyment learning as you build. A small selection from the 'ELEKIT' range is shown below.

Wakefield W. Yorkshire WFI SJR Watch this space for future kits!







# PRICES INCLUDE V.A

# COMPONENTS

The ACE 2nd edition illustrated catalogue shows a considerably enlarged range of components, modules, 'Elekits'. Many PRICE REDUCTIONS from edition one. Component range includes—CAPACITORS, HARDWARE, CASES, LED'S, VERO PRODUCTS, RESISTORS, RS COMPONENTS, TRANSISTORS, DIODES, SCR'S, IC'S (Linear, TTL, CMOS, Audio), SWITCHES, PLUG/SOCKETS, BOOKS, TRANSFORMERS, TOOLS, SPEAKERS AND TEST EQUIPMENT. Typical VAT inclusive prices:—

	LED's RED 15p	2N3702/3/4/5 11p
	LED's GREEN 25p	2N3819 24p
	8-pin 1C SKT 15p	OA90/91
i	AC126 20p	IN41484p
	AC128 27p	IN4001
	BC107/8/913p	WO4 25p
	BC177/8/919p	Zener BZY88 12p
	BC182/3/4L11p	741 8-pin 22p
	BC212/3/4L11p	555 35p
	BC547/8/9 13p	4001 . , 20p
	BC557/8/9	7400 15p
I	BCY70/71 20p	7490 , 6 <b>2</b> p
	BFY50/1/2 23p	Push sw 16p
	OC71	Slide toggle 19p
	TIS43 35p	W/C switches 54p
	ZTX107/8/914p	O.25 CF Res 6p per 3
	2N2926G 13p	
	2N3055 54p	

MODULES Ready built.

Power supplies 1, 2 and 3 rail, Fixed and variable.

DPM's 31/2 digit. LED and LCD Count/display 4 and 6 digit.



SEND 30p FOR THE ACE ILLUSTRATED CATALOGUE WHICH INCLUDES FULL LIST OF COMPONENTS, KITS AND READY-MADE MODULES. 30p REFUNDED WITH FIRST ORDER OF £5 OR MORE.

	_		_	
N	А	M	H	

ADDRESS

BRING YOU THE NEW CHINAGLIA



MULTIMETER

THE **PROFESSIONAL** SOLUTION T<sub>0</sub> **GENERAL MEASUREMENT PROBLEMS** 

£32-50 inc. VAT.

The best instrument for the workshop, school, toolbox, T.V. shop and anywhere accurate information is needed quickly and simply.

- Single-knob range selection

  110° Full-view mirror scale and fine line pointer

  (Clear unambiguous scales

  A well-damped cylindrical magnet movement with resilient bearings

  31 ranges providing coverage from 150mV to 1-5kV d.c.; 7-5V to 1-5kV a.c.;

  50μA to 2-5A d.c.; 25mA to 12-5A a.c.; 10kΩ and 10MΩ resistance and six circular level ranges.
- signal level ranges. Accuracy ±2.5% d.c., ±3% a.c. and 2% resistance

For details of this and other exciting Alcon instruments please write or phone:-



19 MULBERRY WALK, LONDON SW3 6DZ TEL: 01-352 1897

# **BAD NEWS FOR KNOB TWIDDLERS**

A 300W Lightdimmer with NO knob. Dimming and on/off functions are controlled by touch. Features include

- ★ No mains rewiring.★ Easy to build uses one MOS 1C.
- \* Switches on to preset brightness. \* Can be switched and dimmed from many locations using TDE/K kit making 2-way switching easy.

\*\* PRICE TD300K £9.67 TDE/K TDE/K £1.62

LIGHTING CONTROL KITS (300W) TSD300K TOUCH-SWITCH & DIMMER combined. One touchplate for on/off. Small knob controls brightness. £5.62

TS300K TOUCHSWITCH, Two touchplates, ON/OFF £4.32. TS300K TOUCHSWITCH, two touchplates, ON/OFF 124-32.
TSA300K AUTOMATIC. One touchplate. Preset time delay off.

£4.32 LD300K LIGHTDIMMER £3.02

# SCR (C106D) 5A/400V Diag COMPONENTS

12A

16A

20A

# 0.2" L.E.D.: Red 13

0.2" LE.D.s
Red 13p (£1.08/10)
Green 23p yellow 27p
DL/27.5" display £1.62
ECD.5" 4 dight 45p
NE555 31p (4 tor £1.08)
741 27p (5 for £1.08)
M3911 temperature control/thermometer IC £1.08
AY-5-1224 £3.51
AY-5-1230 £5.23
XY-5-1230 £5.23
XY-5-1230 £5.23
XY-5-1230 £5.23
XY-5-1230 £5.24
XY-5-1230 £5.25
XY-

TRIAC BARGAINS

86p

80p

90p

113n

54p

400V Plastic Case

6.5A with trigger

# DIGITAL VOLTMETER/THERMOMETER KIT



Based on the 7106 single IC  $3\frac{1}{2}$  digit D.V.M. the Kit contains a PCB, resistors, capacitors, pre-sets, I.C. and 0.5" liquid crystal display. Com-ponents are also included to enable the basic D.V.M. kit to be modified to a Digital Thermometer using a single transistor as the

ONLY £23.75

# MINI MAINS **TRANSFORMERS**

Standard 240V mains primary 6-0-6V 92p 9-0-9V 97p 12-0-12V 102p

# 24HR CLOCK/APPLIANCE TIMER KIT



Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains: AY-5–1230 Clock/Appliance Timer IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, complete with PCBs and full instructions. £14.85 White box (56 x 131 x 71mm) – drilled £2.70 – undrilled £2.38

ABOVE PRICES INCLUDE V.A.T.

Quantity discounts on request. Add 25p postage and packing. Mail order only to:

T.K. ELECTRONICS (PE) 106 Studley Grange Road, London, W7 2LX.



# **VOLUME 14 No. 16 DECEMBER 1978**

# INVENTIVE

ELSEWHERE in this issue you will find the brief results of our inventors' competition. This competition which carried £490 worth of Scopex 'scopes as prizes was run in the June and July issues of P.E. and attracted a large range of entries, from simple applications for flashing l.e.d.s to complex systems for aircraft guidance. We were amazed by the sheer range of ideas and by the incredible ingenuity of a number of readers.

Apart from simply giving the results, some comments may prove interesting and helpful to other readers: The entries which have been awarded prizes have been partly selected because they had been built and proven; it was surprising to find the number of excellent ideas which were put forward by people without either the time or ability to develop that idea. These suggestions have not been overlooked, although we did not feel we could award any of them a prize, they were considered none-the-less and, in fact, it is likely that a fair amount of money will be spent on the development and testing of one of these ideas as the first step in its ultimate production.

Another large group of entries received described the design of a new

component or mechanical assembly for use in consumer equipment already on the market. Unfortunately there is little we can do with such ideas except advise the inventor to patent his system or component and then sell it to one of the manufacturers.

A third group of ideas were for equipment which could be produced and marketed on a small scale but which were not considered to be economically viable to put into quantity production. A number of these ideas were for use in schools and colleges and their designers might do well to approach local authorities to assess a demand and then try to interest a small equipment manufacturer in the idea as a side line.

# **EXHIBITIONISM**

P.E. is not renowned for its exhibitionism—nor are any members of staff we are glad to say. However from November 21 to 25 we will have a stand at the Breadboard Exhibition in London (see page 1278 for further details) and will be exhibiting and demonstrating a number of projects.

One project we are sure will be of interest is the *P.E. Microprinter* which will form our cover feature next month. We believe this will be the first time a

d.i.y. printer has been published in the U.K. and this design will enable the computer fanatics to make a 40 column printer for approximately £100. So don't miss us at Breadboard—we will also be giving out free gifts; £3,000's worth of them!

# **PRICES**

The price of many componentsparticularly in MPU related areascontinue to fall almost weekly. Because of these reductions readers are advised to check with suppliers before buying. The Chromasonics catalogue given away inside this issue contains a page of memories. The catalogue was printed before this page was written and in the meantime Chromasonics have been able to reduce the price of many memories. For instance the 2112A-2 quoted at £3.24 was available at the time of going to press for £2.14. The 2111A-1 has been reduced from £3.51 to £2 46 and the more expensive 2114 from £16.20 to £8.10.

These are not the only reductions and, as suggested above, a phone call or two before any purchase could save a few pence or even pounds.

Mike Kenward

# **EDITOR**

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

Alan Turpin PRODUCTION EDITOR

David Shortland TECH. SUB EDITOR

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Judith Kerley SECRETARY

Editorial Offices: Westover House, West Quay Road, Poole, Dorset BH15 1JG Phone: Editorial Poole 71191

We regret that lengthy technical enquiries cannot be answered over the telephone.

Advertising Offices: King's Reach Tower, King's Reach, Stamford Street, SE1 9LS Phone: Advertisements 01-261 6676 Telex: 915748 MAGDIV-G

Make Up/Copy Dept.: 01-261 6601 Classified: 01-261 5762

# ADVERTISEMENT MANAGER D. W. B. Tilleard

# Technical Queries Back Numbers

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in Practical Electronics.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to one published project only.

Components are usually available from advertisers; where we anticipate supply difficulties a source will be suggested.

Copies of most of our recent issues are available from: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 OPF, at 75p each including Inland/Overseas p & p.

C. R. Brown CLASSIFIED MANAGER

P. J. Mew REPRESENTATIVE

# Binders


Binders for PE are available from the same address as back numbers at £2.85 each to UK addresses, £3.45 overseas, including postage and packing, and VAT where ap-

propriate. Orders should state the year and volume required.

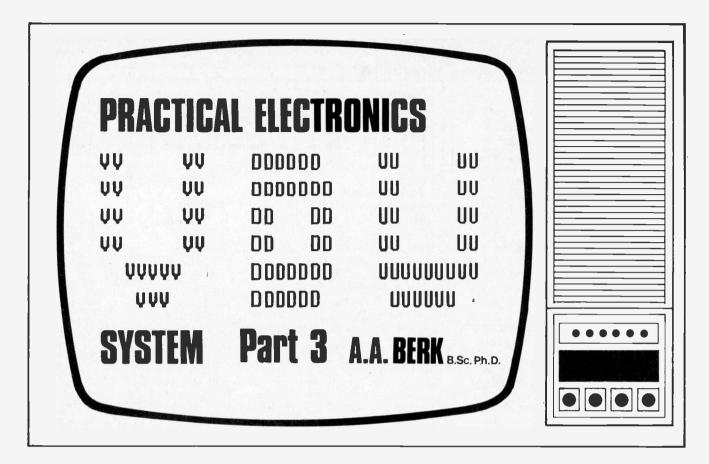
# Subscriptions

Copies of PE are available by post, inland or overseas, for £10.60 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

Cheques and postal orders should be made payable to IPC Magazines Limited.



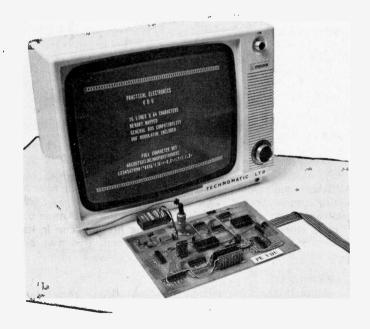- ★ Interfacing the VDU to an MPU system
  - ★ Some cursor management suggestions
    - ★ Simple keyboard interface
      - ★ Addition of lower case characters
        - ★ Further advice on the use of the UHF modulator.



THE "PE VDU" is a complete output peripheral for MPU systems, and will interface easily to any data bus and address bus, including the 6800, Z80, 8080, and SC/MP systems such as the Science of Cambridge MK14.

However, an appreciation of address decoding is necessary for successful interfacing.

# **ADDRESS DECODING**

When an MPU places an address upon the address bus, it is usually either looking for a *reply* from that address location (to appear on the data bus) or is in the process of *sending* a word of data to change that location. It is thus of utmost importance that any address location be uniquely identifiable. In order to ensure this, each memory device has, in addition to a minimal number of address lines, one or more chip selects (CS) lines (or more usually  $\overline{\text{CS}}$  lines). It is up to the designer to ensure that a given memory device receives a  $\overline{\text{CS}}$  pulse only when it is supposed to be selected. For example, the 1K memory in the VDU has ten address lines AO to A9 because  $2^{10} = 1024$  (or 1K for short). These are to be connected to the address bus of the MPU.

To select this block of memory when required, the upper six address lines (A10 to A15) must be decoded to send a  $\overline{\text{CS}}$  pulse to the memory for exactly the right bit pattern on these address lines. The 74154 is an excellent device for this type of function and a possible arrangement for connections is shown in the diagram of Fig. 1.

Operation of the device is as follows. Any bit pattern on A12 to A15 selects one of the outputs (normally high) and forces a zero to appear there. The zero outputs on  $\rm O_0$  to  $\rm O_{15}$  occur as D, C, B and A take up the binary numbers as shown in the right-hand table. Thus the binary number 0010, for instance, forces  $\rm O_2$  low. This may be connected to the  $\overline{\rm CS}$  input of a memory device which will then be selected.

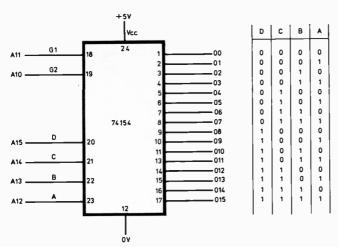


Fig. 1. Using a 74154 to decode the address lines thus generating the necessary  $\overline{\text{CS}}$  signals

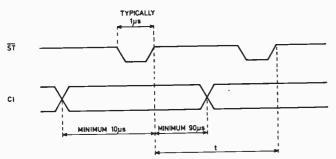



Fig. 2. Timing diagram for CO, C1, C2 and ST lines


Time "t" is a minimum of 132ms for  $\rm C_0$   $\rm C_1$   $\rm C_2=0$  0 0 (Cursor home and page erase command); and 8.3ms for any other command word. A method of generating these times in software has been discussed. Another approach is to use monostables to generate them directly. A UART or PIA (MC6820) may be used to interface to the control lines in either method. For the monostable generation of the timing pulses, a ready line from the mono's must also be fed to the UART or PIA, to signal when they have finished timing and are ready for the next command. A suggested diagram for this is shown in Fig. 3.

The 8.3 ms and 132 ms mono's are set to give a "high" for the required time on a negative excursion input. The 74123 is fitted to provide all the monostable functions required. The  $1 \mu \text{s}$  mono is set to give a zero pulse on the  $\overline{\text{ST}}$  line when it receives a rising edge from the appropriate mono at the end of its timing pulse. In Fig. 3, the MPU sets up a control word on  $C_0$   $C_1$   $C_2$  and then sends a start pulse to the monostables. The correct mono is automatically selected by the logic shown. While one of the mono's is timing, the ready line is low. The MPU detects a ready signal (high) at the end of this period for the next command. The PIA or UART used to access this piece of hardware will have  $\overline{\text{CS}}$  lines, or their equivalent, and may thus be treated as a memory location as described above in address decoding.

If software cursor delays are used, the author has found that the UART or PIA may be conveniently replaced by a simple TTL latch such as the 74174.  $C_0$   $C_1$   $C_2$  and  $\overline{ST}$  are connected to the outputs of this device and the inputs con-

Fig. 3 (below). Using monostables to generate the timing pulses, instead of software. A suggested circuit.

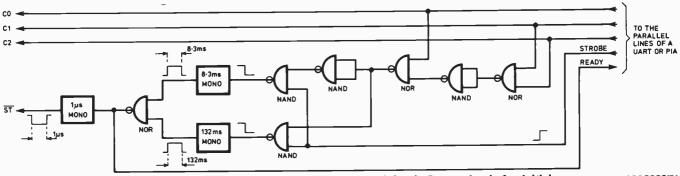

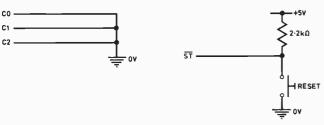

All this depends upon G1 and G2 being low. Thus only for zeros on A11 and A10 will the 74154 select any of its outputs. This causes  $0_0$  to  $0_{15}$  to select sixteen 1K pages, one of which could be the VDU.

In order to simplify address decoding two  $\overline{CS}$  inputs are included on the VDU; these are labelled  $\overline{VDU}$  select and enable. Both must be low for the VDU RAM to be selected.

# **CURSOR CONTROL**

Part One explained how to use the cursor control lines  $C_0$ ,  $C_1$ ,  $C_2$  and  $\overline{ST}$ . Fig. 2 illustrates the timing diagram to be followed when using these lines.

Fig. 4 (left). Reset circuit for initial page erase, necessary when the cursor is generated by software

nected directly to the data bus. This is a purely 'output' device and does not affect the information on the Bus. To prevent Bus loading, the LS version is recommended. The Clock input to the latch is to be treated as the Chip Select line. Hence the C $_0$  C $_1$  C $_2$  word should be set up first followed by the pulsing of the  $\overline{\rm ST}$  line and a suitable delay before any repetition.

# OTHER CURSOR GENERATION METHODS

There are several monitor programs for memory mapped VDUs on the market—these should all work admirably with the PE VDU. Most of them, however, generate the cursor in software, and under these circumstances the VDU must be "page erased" at the start so that the first location in its memory appears at top left of the screen. This may be assured by a reset button on the ST line as shown in Fig. 4.

# **KEYBOARD**

As this VDU is not a videowriter, a keyboard is not interfaced to it directly. There are many ways to add a keyboard

to a MPU system. One of the simplest, and fastest, is illustrated in Fig. 5.

DO to D6 are the seven lines of character information given out by the keyboard. These must be latched before entering the buffer. Most keyboards perform this function automatically. This information is only allowed through and onto the data bus if the CS line is low. The keyboard may thus be thought of as a memory location and accessed via memory decoding. The strobe pulse from the keyboard informs the MPU when a new piece of information is available. This line may be connected up in several ways.


The strobe may simply be connected to D7 of the data bus through the buffer. A service routine in the monitor checks D7 continually for a strobe and D0 to D6 are then read and acted upon. Alternatively, the strobe may be connected to an interrupt line of the MPU. The monitor program must then contain an interrupt service routine to accept data from the keyboard, act upon it and return to the program which was interrupted.

A more sophisticated method is to latch the strobe pulse and clear the latch when the data is read. This allows the MPU to use the keyboard information at its leisure.
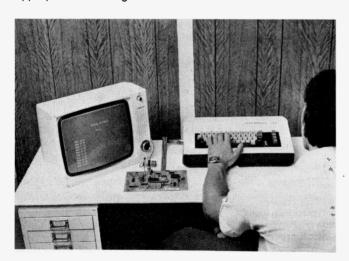
# **ADDING LOWER CASE CHARACTERS**

Adding other characters to the VDU is very simple indeed. The easiest method is to use the lower case version of the 2513. This may be wired in parallel with the upper case 2513 (except for their  $\overline{CS}$  lines). These character generators are simply Read Only Memories (ROMs). They have  $\overline{CS}$  inputs which are used to enable them (pin 11). In order to address either ROM, its pin 11 must be low. The data in the ROM is accessed by six address lines fed from RAM through IC11 (six bit latch). Two lines from the RAM (DO6 and DO7) are unused as six bits are enough for 64 characters. Lower case characters occur when DO5 and DO6 are both ones. This may be seen from the ASCII code. A little logic decoding is necessary to turn the upper case 2513 off ( $\overline{CS}$  high) and the lower case on ( $\overline{CS}$  low) for this occurrence.

This only uses half the lower case ROM and a little more logic decoding will access the other half which contains a varied collection of special symbols. By this method, most other character generators may also be added with the appropriate decoding.



The photographs in Part 1 showed the VDU displaying reverse field characters. In this part the position of switch S1 is set so that the more common white characters on a dark background ere generated

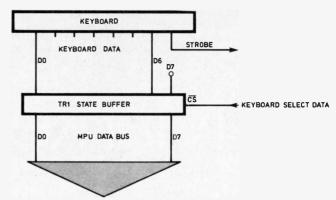



Fig. 5. Simple method of interfacing a keyboard το an ινιτυ system

# **FURTHER HINTS ON UHF MODULATOR**

The stripline modulator, mounted on the p.c.b., has given good results by following the suggestions given below.

The value of VR1 should be changed to  $1k\Omega$ . This matches impedances more accurately for the UHF modulator, though may be found a little low for straight video. The p.c.b. track taking the +9V from the battery to the modulator should be cut, and about 5mm removed from it. This gap should then be bridged by a  $2 \cdot 2k\Omega$  resistor. C6 is at one end of this resistor, and a further 10nF capacitor can be placed between the other end and the 0V track nearby. It will also be found that the 33pF tuning capacitor, C4, may be ommitted to tune to most TV sets. Finally, a 12pF capacitor may be placed in the UHF feed line. Printed circuit track should be removed to accommodate this component, and care must be taken to remove tracking as near to the output end as possible—to prevent damage to that part of the p.c.b. track which forms L3.

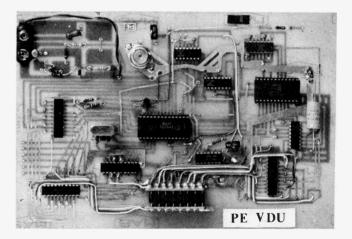The kits and boards available from Technomatic include the above modifications.



# **LIGHT-PEN?**

As a final note, the CRTC chip data sheet informs the reader that a light-pen facility is available. Unfortunately, this is not really so at present. It is still possible to add a light-pen to the PE VDU and its addition conjures up all sorts of dazzling features. Instant editing of the screen's contents would be a most elegant process. Games would be beautifully interactive. Even the demise of the keyboard can be envisaged, with the top right-hand corner of the screen containing a full ASCII character set which may be "typed" in to the MPU system simply by holding a light-pen up to the appropriate character.

Ah well, perhaps next Christmas!





# LET THERE BE FLUORESCENT

Christmas is coming and the nights are getting dark. Use fluorescent lanterns and give batteries more spark.

These Sterling lanterns from Dixons have a built-in carrying handle and a spring clip for wall fixing. A ribbed tube cover maximises illumination although the diffusion of fluorescents makes them no good for burglars.



The XP500 costs £5.95 and runs off eight 1.5V HP2's or equivalent. The XP1000 at £7.95 is similar but can also be used off a 12V car battery (a 15ft lead for use with a cigar lighter socket is supplied).

# **CATALOGUES**

Home Radio's new catalogue has an interesting Barbara Hepworth design on the cover. The index mentions several hundred items. Home Radio say they have over 3,000 components. Price is £1 plus 25p p&p. Home Radio Ltd., 240 London Road, Mitcham, Surrey, CR4 3HD. (01-648 8422)

A stamped, self addressed envelope,  $9 \times 6\frac{1}{2}$ , is all you need to send for the latest TUAC catalogue—30 pages of technical specs. on their pre-amps, power supplies, disco mixers, sound to light sequencers, trannies, high power loud speakers, musician and p.a. combination amps, slave amps, components and hardware.

Transistor Universal Amplification Co. Ltd., 119 Charlmont Road, London, SW17 9AB.

Magenta Electronics have a 31 page catalogue with everything for the hobbyist.

Send a 12 × 9 SAE to Magenta Electronics Ltd., Newton Leys, Burton-on-Trent, Staffs., DE15 0DW. (0283 65435)

# **PRODUCT GUIDES**

A new guide to Mullard "preferred" power transistors is available. Categories included are complementary power transistors, complementary Darlingtons, npn high-voltage transistors, npn switching power transistors and transistors for switched-mode power supplies. Also included in the guide are recommended power transistor line-ups and an equivalents list.

Central Enquiry Handling Unit, Mullard Ltd., New Road, Mitcham, Surrey. (01-580 6633)

General Instrument Microelectronics product guide has information on their devices under the headings—Microprocessor, Microcomputer, Memory, Telecommunications, Home Information Centre, Entertainment, TV Games, Consumer, Industrial/Mosfet.


General Instrument Microelectronics Ltd., Regency House, 1-4 Warwick Street, London, W1R 5WB. (01-439 1891)

# **PLUG-IN TIMERS**

Superswitch have extended their TIMAC Range of timers by introducing three new models with automatic controls.

The new 24-hour TIMAC (Cat No. T1301) has 96 built-in quarter hour time selectors for easy setting. "ON" sequences are clearly indicated by red segments which are exposed when the time selectors are operated.

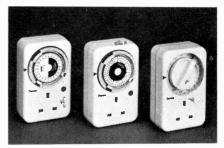The new 7-day TIMAC (Cat No. T1307) uses a similar built-in time selector system. In this model the 84 time selectors give 12 two-hour "ON" sequences per day. These sequences are indicated by blue segments



which are exposed when the time selectors are operated.

The new 2 hour TIMAC (Cat No. T1300) incorporates a mechanical timer to give control when shorter periods are required. The large dial allows very accurate settings for both domestic and industrial use.

All three units plug into standard 13 amp outlet sockets and have 3,000W ratings.

The recommended prices of the three units are: T1301, £13.50; T1307, £15.75; T1300, £12.50.


# **ANTI-CLOCK**

More of a conversation piece than a device to get you to work on time, this clock does tell the time—eight minutes past ten in the photograph. It has a black face, white hands and numerals, and a high frequency, 400 day, battery operated, electronic, torsional pendulum movement.



The face does not show real time going backwards but at least makes for more awareness of the fact that time passes relentlessly on, however it is displayed.

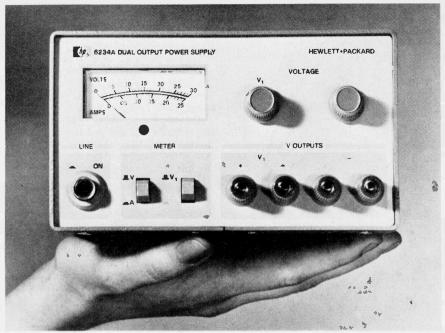The "Backward" clock is available at £13.95 (inc. VAT and p&p) from designers and manufacturers Accutec Designs Ltd., 121a Strathville Road, London, SW18. (01-874 4641)



**DUAL POWER SUPPLY UNIT** 

The dual-output bench power supply from Hewlett-Packard offers two independently adjustable and isolated power sources in one compact unit. Both of the d.c. power sources are of the constant voltage/current limit type with each output voltage being adjustable continuously over a 0 to 25V range. The maximum current available per output is 0-2A and is limited to prevent overloading.

The HP-6234A offers considerable flexibility to the user with output voltages that can be arranged to provide identical or different voltages in any polarity combination with respect to zero or other common positive or negative voltage points. The outputs can also be connected in series to provide up to 50V at 0.2A. Both sources are fully isolated to permit either of the output terminals to be grounded.


With pushbutton switches users can select either voltage or current for each output to be monitored on the unit's meter. Other features include two multiple-turn controls for precise voltage setting, regulation to 0.01 per cent and ripple and noise of less than  $200 \, \mu V$  rms.

The 6234A is priced at £112. For further information contact Hewlett Packard Limited, King Street Lane, Winnersh, Wokingham, Berkshire.
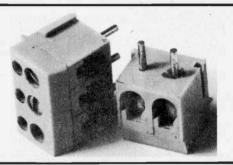
# TIDY TERMINATIONS

Flying leads to circuit boards can be a nuisance to terminate neatly. Also, to enable future access to the underside of the board, several inches of lead may have to be left spare.

These Verospeed terminal blocks fit across two pitches of 0.1 inch matrix board. They come in 2-way or 3-way units and the mouldings are designed to mechanically interlock, allowing any number of terminations to be built up. Each termination



incorporates a test socket for 2mm plugs. A captive screw contact takes up to 1.5mm<sup>2</sup> wire. The contact is made from tin plated brass and has a phosphor bronze leaf wire protector. Nominal voltage, 380V. Nominal current, 16A.

2-way, pack of three, 78p. 3-way, pack of three, 98p. Verospeed catalogue free. Prices include p & p but add VAT at eight per cent.

Verospeed, Barton Park Industrial Estate, Eastleigh, Hants SO5 5RR. Telephone: 0703 618525/6.

# **CHOOSE A CARD**

There are now two other versions of the Casio Mini Card calculator mentioned in the June Market Place, a Scientific Card, fx-48, and a Timer Card, ST-24. Full details of all three are available from suppliers Tempus.

If you ever found the old Westminster chiming clocks a useful aid to slumber breaking then the Timer Card may be of interest. As well as the usual sports timing functions there is a repeater timing function. This enables any period of time up to 24 hours (minus one second) to be repeatedly alarmed.

Thus by setting to a repeat of, say, one hour or 30 minutes, one can have a gentle Westminster system sounding out all night (if too loud put it in a drawer). When you have slumbered enough, one of these signals will lightly pull you out at the top of one of your alternating deep/light sleep cycles. Far more civilised than a nerve jarring, sudden awakening from a deep sleep trough by a sergeant-major type of alarm clock.

Prices (batteries supplied) from Tempus are: Mini Card, LC-78, £16.95; Scientific Card, fx-48, £19.95; Timer Card, ST-24,

All prices include VAT and p&p, and each  $91 \times 55 \times 6$ mm calculator is complete with a leatherette case and 30 booklet pages of user information

Tempus, Talk of the Town, 19-21 Fitzroy Street, Cambridge CB1 1EH.

# **NEW MUSIC CENTRE**

For £139·50 (inc. VAT and p&p) you get—Amps. 2 × 14W r.m.s. into 4Ω, t.h.d. 0·5 per cent typical, push buttons for all functions; Deck—BSR P182 semi-automatic single player, 3 speeds, SC12M cartridge, sapphire stylus, 10·5in turntable; Speakers—8 × 5in rated 15W r.m.s.; Radio—VHF, MW, LW, AFC, Stereo Beacon; Cassette—Auto CRO2 (chrome), 6 piano keys inc. pause, automatic record level, auto stop on play, digital turns counter, cassette storage rack; Two mikes; Cabinet—teak, walnut or black veneers, hinged tinted dust cover; 12 month guarantee.




Will it fit—width 610, depth 460, height 108mm; Speakers— $206 \times 152 \times 352$ mm.

For a colour illustration send SAE.

Delivery ex-stock from Readers' PCB Services Ltd., Fleet House, Welbeck Street, Whitwell, Worksop, Notts. (0909 720695)
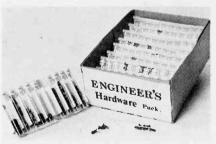
# **NUTS FOR CHRISTMAS**

The next time the wife tells you a nut or bolt has dropped out of the hairdryer, food mixer, kids' toy, etc., get this hint in for a Christmas present. Spend a quarter of an hour digging around your cake tin of mixed nuts, screws, washers and bolts, and then in exasperation say, "If only I had an Engineer's Hardware Pack". "A what?," she'll say. Then you can explain Home Radio's kit of 2 to 8BA nuts—brass and nylon; screws—brass, self tapping, chrome, nylon, grub; washers—brass,



shakeproof and nylon; solder tags; and metric screws and nuts. Finally dig once more into your tin of allsorts and sit her down with a large glass of cheap sherry in case she moans at the price.

£21 plus 8 per cent VAT from Home Radio (Components) Ltd., 240 London Road, Mitcham, Surrey, CR4 3HD. (01-648 8422)

# **JOANNAS**

The latest six and  $7\frac{1}{4}$  octave touch sensitive electronic piano kits from Clef Products will be demonstrated for the first time at the Breadboard '78 Exhibition.



The Joanna 72 and 88 have been developed from the P.E. Joanna and are designed by A. J. Boothman. The Joanna 88 is a full size 88 note piano. The new design has a greater degree of precision in the damper action, and adopts layout techniques to eliminate beehive breakthrough, which has been a problem in pianos due to the requirement of maximum system gain to cope with the instant wide dynamic range.

For further information contact Clef Products, 16 Mayfield Road, Bramhall, Cheshire.

## **NICE MEDICINE**


One of the world's smallest relays, the G2E, is available with coil ratings from 1.5V to 24V at currents of 18.8mA to 300mA.

Relay contacts are rated at 0.5A (100V a.c. PF = 1) or 1A (24V d.c.), while the carry current is 2A for both versions.

This subminiature component measures only  $16 \times 11 \times 10.5$ mm and weighs just 3.5gm. Termination pins are arranged on 2.5mm pitch.

Life is in excess of  $5 \times 10^6$  operations, and switching frequency is 1,800/hr max. Coil resistances range from  $5\Omega$  to  $1,280\Omega$  and only 290mW of pull-in power is needed.

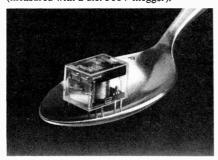Both operate and release times are  $\gg 5 \text{ms}$ , and insulation resistance is  $\ll 100 \text{M}\Omega$  (measured with a d.c. 500V megger).



A transparent case protects the component from dust. Operating ambient temperature range is -25 °C to +55 °C.

Available at £1·15 each from outlets in major cities. Contact IMO for distributors. Further distribution enquiries welcome.

IMO Precision Controls Limited, 349 Edgware Road, London W2 1BS. Telephone 01-723 2231/4.



# PLAY, PLAY, PLAY

If you are a player of pub video games machines and would like one of your own, no not a pub but a programmable video games centre, then this system may be for you.

In the beginning, Atari, in Sunnyvale, California, invented a coin-operated game called Pong. This was popular so they invented more games, like Breakout and Indy 500.

These games were introduced into pubs in Great Britain by a Swedish video and vending machine group. Now the games are available on cartridges, 192 games on nine cartridges so far.

The progammable system consists of a control panel, mains unit, aerial switch box, a pair of paddle controllers and a pair of joystick controllers, plus a 27 game Combat cartridge.

A further eight cartridges are available with from four to fifty games variations on each. Other titles are Air-Sea Battle (27 variations), Star Ship (17), Street Racer (27), Video Olympics (50), Surround (14), Black Jack, and Basic Maths (8). Breakout has 48 variations and Indy 500 (14).

Other titles in progress are: Space War (17), Home Run (Baseball), Outlaw (16), Hunt and Score (8), Codebreaker (20), Hangman (9), Football (American) and Basketball.

The distributors, Cherry Leisure, also announce that cartridges which encompass junior and middle school spelling and vocabulary are being prepared, with over 10,000 words in the program.

System complete, plus Combat, £169.95 (inc. VAT). Additional games cartridges, £14.95. Should be available in all major cities. Trade enquiries to Cherry Leisure, 387 High Road, Willesden, London NW10 2JR. Telephone 01-459 2236.

# **GRAND MASTER TRAINER**

The basic and three level models of the very popular microprocessor controlled Chess Challenger range have now been joined by their very latest and most sophisticated version, the Chess Challenger 10.



This latest addition to the range is capable of playing at ten levels: beginner, intermediate, experienced, advanced, superior, expert and excellent. The three other levels cover: two move puzzles, tournament practice and postal chess (with a response time of up to 24 hours). The level of play is changeable at any time during the game and an override switch enables you to make multiple moves before the computer responds or *even* add or subtract pieces from the board!

The problem mode allows you to establish your own chess problems and see how the computer reacts. Each time you press a key the Challenger emits a single tone and when it has responded it gives a double tone. The Challenger 10 is priced at £199.95 including VAT and delivery. It is available by mail order from Gemini Electronics, Newton Buildings, 50 Newton Street, Manchester. (061-236 3083)

# **ANTEX**

The latest shortform catalogue from Antex includes three of their very popular models:

The model C (15W), which is available in six voltage ranges and has seven suitable bits.

The model CX (17W), which is only slightly larger than the model C, but has a greatly improved breakdown voltage rating and is available in two voltage ranges (220, 240V-100, 120V).

The model X25 (25W) is no longer a miniature iron but is more suited for general purpose work around the home or garage. Of the five different types of bit available, two are dual in line blocks for desoldering i.c.s.

The MLX is a 25W iron, ideal for car, boat and caravan owners because it is fitted with a 12V element

Antex Ltd., Mayflower House, Armada Way, Plymouth, Devon.

# Farnborough

A review of some of the latest developments in civil and tactical avionics by Peter Preston

THE 1978 Farnborough International Air Fair afforded the opportunity to view some of the latest developments in civil and tactical avionics from 450 companies, representing 16 participating nations. Crawley-based MEL announced that, following a contract from Mobil North Sea Ltd., trials with MADGE (Microwave Aircraft Digital Guidance Equipment) (1) were planned within the next six months on the Beryl "A" platform.

This marks the first commercial order of a British MLS (microwave landing system), and MEL are set for an all-out assault on the North Sea market, said to be worth £10M between now and 1986. Particular emphasis is placed on the portability and cost-effectiveness of the system, which was originally developed for military use. It can be transported in a Land Rover, rigged by two men in less than 20 minutes (11 mins is the record!) and handle up to 240 aircraft simultaneously.

Clear accurate glideslope, localiser and distance-to-go information over a range of some 20 nautical miles enables day or night operations to be maintained in conditions which would otherwise inhibit offshore supply services. The estimated cost of closing down a platform such as Beryl "A" is put in excess of £1M per day, and as the quest for black gold extends even further from coastal bases, the requirement for a high-integrity helicopter guidance system will become even more pressing. MEL must be considered to be in an enviable position with regard to their offshore MLS experience; MADGE should receive C.A.A. certification within the next 12 months.

Marconi showed their new Lynx A.D.F. which enables pilots to obtain bearings from a ground beacon by merely pressing a button. The version designated AD 380S also



incorporates the 2182kHz maritime radiotelephone distress frequency. Search-and-rescue helicopters can home on a vessel transmitting on this frequency without having prior information relating to its position.

# SATELLITE COMMUNICATIONS

Satellite communications equipment from many sources was in abundance at the show and amongst the more interesting systems was Marconi's Compack miniature ground terminal. This self-contained unit weighing 50kg can be carried by three men and assembled in about 10 minutes. The system can be erected in mountains or jungle to provide





# 9178

reliable, fade-free communication over thousands of miles, and is constructed to withstand severe climatical conditions.

As always, radar was in great prominence at Farnborough, and Plessey used the opportunity to give their new GF75 (2) multi-role defence radar an airing. Designed to meet the tactical warfare needs of the 1980's this highly-mobile helicopter transportable unit incorporates the most sophisticated ECCM (Electronic-Counter-Counter-Measures) and data-processing facilities. Pulse compression and an advanced DMTI (Digital Moving Target Indicator) provide a degree of clutter rejection comparable with pulse doppler systems.

The GF75 has applications in gap-filling, low cover, forward area alert, coastal defence and missile acquisition sector control and reporting.

Yet another British airport has chosen the Cossor Compass 9000 system (4) for their Secondary Surveillance Radar display and processing requirements. The order, from East Midlands Airport near Derby, follows similar announcements from Newcastle, Gatwick and RAE Farnborough.

Compass 9000 is a complete ATC radar display system, including refresh and controller units. Character/Vector generators will provide a raw/synthetic or mixed display, and code/callsign correlation may be added. Up to 24 display units can be accommodated and training simulation, self-generated map and a "hand over" facility are made available. Another important development from the same stable is a new monopulse technique for processing aircraft transponder signals, which dramatically improves the integrity of SSR (Secondary Surveillance Radar) information received by air traffic controllers.

Although available independently, this technique is an essential part of the ASDEL system (3), the first to be able to interrogate and identify selectively each aircraft within its range—bringing major benefits to aircraft operation and safety.

# **TRANSCEIVERS**

Some VHF and UHF multi-facility transceivers were shown by the French T.R.T. company alongside a digital radio altimeter (6) and an interesting portable MF radio beacon (5). Aimed at the military and oil field markets the beacon, designated the RBM 200 series, is available with the option of 8, 15 or 8 (selectable) and 100W outputs. It is lightweight and can be rapidly tuned to an assigned frequency by means of a synthesiser.


The Farnborough show was the largest and most important exhibition of its kind to be presented anywhere in the world in 1978. A biennial event, it is the podium from which the world's aviation industry shows its capabilities and can be relied upon to provide a vast array of state-of-the-art technology.

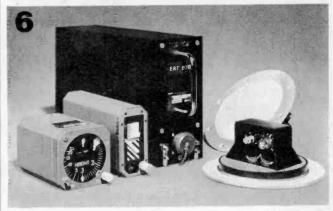
Readers are encouraged to give their support to future venues, which reflect strongly our own expertise in the highly-competitive aerospace industry.










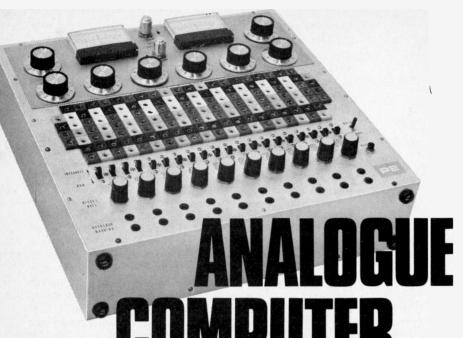

- ★ Lissajous Figures
- Flight Simulation
- **★** Special Circuits

T was mentioned last month that damping is caused by air resistance or electrical resistance. This form of damping is called "viscous damping" in mechanical vibrations and is proportional to the velocity. Viscous damping is something that in many cases we wish did not exist. For example, it forces us to burn fuel continuously to propel an aeroplane through the air. Spaceships travelling in vacuum do not have to do this, although they have to burn fuel to decelerate. In other cases we find damping very useful. Mechanical vibration is one of these cases, where damping helps to reduce unwanted and dangerous vibrations. Without it motor cars would provide a very rough ride. The mechanical and electrical damped systems are shown in Fig. 4.1.

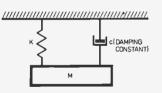

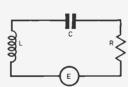


Fig. 4.1. The mechanical and electrical equivalent circuits for damping.

In the mechanical system damping is provided by a dashpot which is full of viscous oil. This system very closely resembles the suspension unit of a motor car.

The equations describing the response of these systems are:

> Mechanical  $M\ddot{x} + c\dot{x} + Kx = F$ Electrical  $L\ddot{q} + R\dot{q} + 1/Cq = E$

c = damping constant

q = charge,

F = a forcing function

therefore q = current E = voltage (function of time)


Table 1 shows the equivalent mechanical and electrical quantities.

Mechanical		Electrical	
Mass	M	Inductance	L
Spring stiffness	K	1/Capacitance	1/C
Force	F	Voltage	E
Velocity	ż	Current	iorq
Displacement	X	Charge	q
Viscous Damping	С	Resistance	R
	TAB	LE,1	

Rearranging the mechanical equation we obtain:

$$\ddot{x} = -\frac{c}{M}\dot{x} - \frac{K}{M}x + F$$

The flow diagram and the patch panel connections are shown in Fig. 4.2.

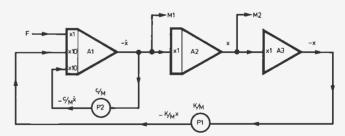

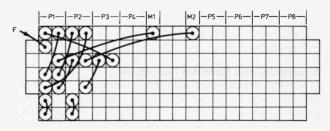


Fig. 4.2. Flow diagram and patch panel layout for investigating a damping system.

To run the program:

- (1) Check A1 and A2 are integrating, and A3 adding.
- (2) Switch power on and set potentiometer values.
- (3) Computer mode: Hold.
- (4) Press "reset" for a few seconds and release. Switch to compute.
- (5) Apply a forcing function to A1 input.

Several functions can be tried, for example "step", "ramp", "impulse", "sinusoidal", or "random".

# Impulse Function

An impulse function is a force of a relatively large value and short duration. It can be simulated by momentarily applying a voltage to the input of A1. The application of this function produces the results shown in Fig. 4.3. Repeat this experiment with several settings of P2.

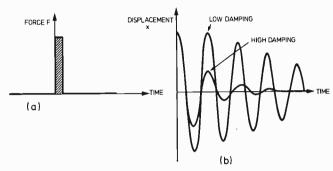


Fig. 4.3. The graphic representation of an impulse function is shown in (a). Graph (b) shows its effect on the circuit in Fig. 4.2.

# Step Function

A step function of about 10V should be applied and a similar procedure followed as with the impulse function. At low damping settings the needle will overshoot the 10V level and oscillate about this value. As more damping is applied the overshoot will become less until at a certain value there will be no overshoot and the needle will take the shortest time to settle at the value of 10V. This is called critical damping. If more damping is applied the needle will take longer to reach the value of 10V. These results are shown in Fig. 4.4.

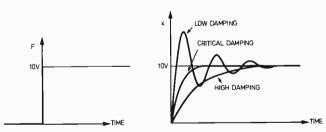


Fig. 4.4. Graph showing the effects of damping after a step function has been applied to Fig. 4.2.

One application of the above is in analogue measuring instruments, like moving coil meters. The input is usually a step function and the needle is damped to a value very near the critical damping value so that the meter can be read with the minimum of delay.

# Sinusoidal and Random Functions

Similar experiments can be carried out by applying sinusoidal and random excitation. We have seen how a sinusoidal function is obtained. A random function is difficult to produce but it can be simulated by adding together two sinusoidal functions of different frequency and amplitude. Three amplifiers are required per sinusoidal function and

therefore nine amplifiers will be needed to experiment with random excitation. One application of this is the problem of the suspension unit of a motor car. Here we have a mass sitting on springs and dampers with the wheels following the uneven contour of the road. The requirement is that as little vibration as possible is transmitted through the suspension unit to the car body. In this case a perfectly satisfactory solution is impossible to obtain and the values of spring stiffness and damping constant are compromises. The best possible values can, however, be worked out using the analogue computer and this saves the designer the expensive and time consuming task of testing many different models of the unit.

# Lissajous Figures

These figures are produced by the combination of two curves, applied at right angles to each other. For example, two sinusoidal functions applied to the X and Y inputs of an X-Y plotter will produce a circle, if they are in phase with each other and have the same frequency. Where the curves are out of phase and differing in frequency, intricate meshing figures are formed, similar to the one shown in Fig. 1.1, at the beginning of this article. In these figures damping was used to vary the amplitude of the oscillation. In real life damping can only be positive, i.e. it can only act to suppress oscillation. However, mathematics, and therefore computers also, allow us to apply negative damping. To do this the flow diagram of Fig. 4.2 is altered by adding an inverting amplifier in the feedback loop containing P2, to change the sign of the damping term in the equation. In this case there is no need to apply a forcing function F. When compute is selected, the oscillation will begin with the amplitude growing progressively until the amplifiers saturate. To produce good figures, very little damping should be applied and the difference in frequency between the X and Y functions should be small.

# Flight simulation

The flight of a rocket can be described by simple mathematical equations involving no more than Newton's law of motion. We can start with a program to simulate the flight of a lunar craft. The diagram with all the forces acting on the spacecraft is shown in Fig. 4.5. The equation of

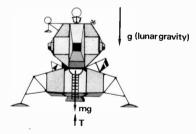


Fig. 4.5. Forces acting on the spacecraft.

motion according to Newton is:

$$T - mg = m\ddot{x}$$

To practice lunar landings, we need to have a thrust control and information about the speed and the altitude of the craft. The flow diagram shown in Fig. 4.6 satisfies these requirements, with potentiometer P1 providing the thrust control and M1 and M2 displaying velocity and altitude respectively. Notice the use of A3 as a sign inverter.

These experiments are of course very simple and the limitations will become very obvious to the programmer. To start with, the equation above assumes that motion can only take place vertically up or down. In reality, movement is in three dimensions and although we can still describe this

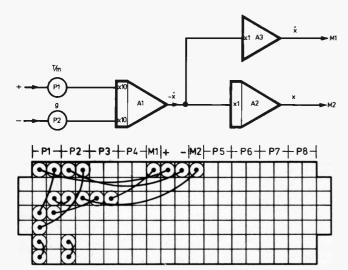


Fig. 4.6. Flow diagram and patch panel layout for amplitude scaling example.

motion mathematically, the equations become more complicated and require more computing elements if it is to be solved.

The other limitation which becomes very apparent when trying to run these programs, is the problem of the limited voltage range over which results can be obtained.

With the equations as they stand, one volt represents 1 unit of the relevant dimension. For example if SI units are used, one volt will represent 1 metre (distance), or 1m/sec (velocity), or 1m/sec² (acceleration), or 1 Newton (force). Therefore our flight will be limited to a height of about 26m (if -13m is taken as ground level) and the velocity to  $\pm 13$  m/sec. Suppose that the following data apply to the lunar craft.

mass m = 1,000kg. max. engine thrust T = 10,000N

lunar gravity = 1.6m/sec.


Using these values, it will be found that all three amplifiers will saturate very quickly. In fact, with full thrust applied, A1 will saturate in seconds. This is obviously unsatisfactory. Fortunately, we can get round this problem by scaling the various quantities.

# **Amplitude scaling**

To do this we have to estimate the maximum likely values of the variables and their derivatives. Let us assume for convenience that we may work in the range  $\pm 10V$  and that, in the lunar lander example, we wanted to investigate the flight up to a height of 100m. Hence we may represent 100m by 10V. We therefore apply a scale factor of 10/100 = 0.1. We also estimate that the speed will not exceed 50m/sec. Hence we apply a factor for the velocity of 10/50 = 0.2. So the velocity will be represented by the computer variable 0.2  $\mathring{x}$  and the height by 0.1 x both measured in volts. We are also going to scale the acceleration by 0.2 to give a computer variable of 0.2  $\mathring{x}$ . We can now rewrite the equation as:

$$0.2 \ \ddot{x} = 0.2 \ (T/m - g)$$

The modified flow diagram in Fig. 4.7 shows the new machine variables in square brackets.

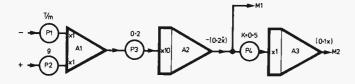

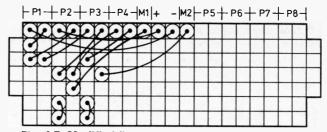


Fig. 4.7. Modified flow diagram and patchpanel layout.

To find the value of P4, we have to examine the process of integration carried out by A3.

$$K ? (0.2 x) dt = 0.1 x$$

From this we can see that  $K=0\cdot1/0\cdot2=0\cdot5$ . Now if the sensitivity of M1 is adjusted so that it shows 10V at full scale deflection (f.s.d.) then 1 volt will represent  $1/0\cdot2=5$ m/sec, and f.s.d. will represent 50m/sec. Similarly 1V on M2 will represent  $1/0\cdot1=1$ 0m. By using P1 as a thrust control, take offs and landings can be practised. To carry out a gentle landing the velocity should be very near zero when the altitude is zero. You should practice doing this with the minimum of hovering, since this is fuel consuming!

The lunar lander can be converted to a vertical take-off aeroplane by the addition of air resistance or drag. The equation and flow diagram is shown in Fig. 4.8.

$$T - mg - D = m\ddot{x}$$
  
or  $T - mg - Cd \dot{x}^2 = m\ddot{x}$   
if D is proportional to  $\dot{x}^2$ 

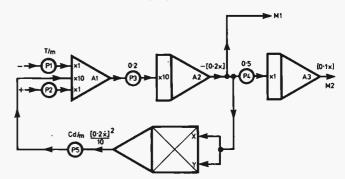


Fig. 4.8. Modified flow diagram to convert the lunar lander to a vertical take-off aeroplane.

# Time Scaling

The solutions to different problems may extend over periods of time ranging from microseconds to many hours. It is not convenient to record results that occur within a split second or results that take many hours to produce. This is not the only reason, however, that we want to avoid both high speed and low speed computer operation. At high speed (e.g. at high frequencies) phase shifts in computing elements and recording instruments produce time lags and therefore errors in the results. At slow speed error voltages tend to build up when integrated. Fortunately we can use time scaling to get round these problems. This we can do by simply reducing or increasing the gain of integrators only. Time is not involved in the operation of adders. Forcing functions should also have their frequencies adjusted by the same factors as the integrators.

To summarize, voltages must be neither too big, nor too small, and the time scale must be neither too fast nor too slow.

# **Special Circuits**

Many special circuits and techniques are used with analogue computers. Some of these involve the use of diode

shaping circuits to produce non-linear functions. In physical systems we often find such effects as backlash, Coulomb or dry friction, dead space, and we may need to simulate these effects on the analogue computer.

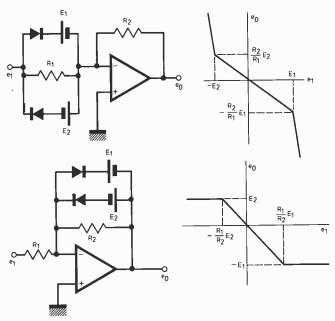


Fig. 4.9. Diode Limiter Circuit.

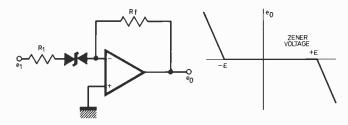


Fig. 4.10. Dead Zone Circuit.

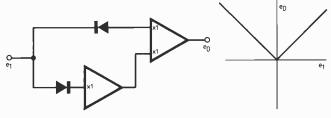


Fig. 4.11. Absolute Value Circuit.

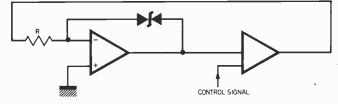


Fig. 4.12. Flip-Flop Circuit.

In this relatively short article, it has not been possible to touch on every subject in the field of analogue computation. Nevertheless it is hoped that the reader has been given a good introduction to the subject and that the constructor will be able to write his own programs and run them on the computer.

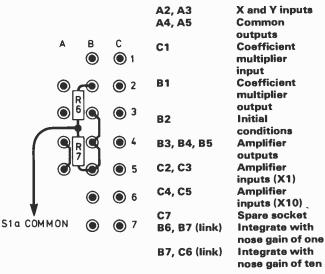


Fig. 3.2. This figure was incorrectly printed in Part 3 of the series.

# **News Briefs**

# MERSEY MICRO CLUB

A NEW group, called the Merseyside Mini/Micro Computer Club, has got off the ground under the guidance of Science and Technology Education on Merseyside (STEM). Local distributors have promised to help, in giving talks and demonstrating their products, as well as offering publicity.

Anyone who is interested in microprocessors and small computer systems are very welcome to join, whether new to the world of computing or with many years' experience.

A varied programme is expected to include such subjects as kit building, system configuration, games programs, programming in high level language, business and operating systems.

For further details, contact: Martin Beer (Chairman), Merseyside Mini/Micro Computer Club, 19 Abercromby Square, P.O. Box 147, Liverpool University, Liverpool L69 3BX.

# LATE NIGHT VIEWING

Avionics Limited (a GEC-Marconi Electronics company) has won an important contract from the Ministry of Defence Procurement Executive for the development of a Visual Augmentation System for RAF Tornado aircraft. The system, which is to be fitted to the Tornado Air Defence Variant, will enable the crew to see a television picture of the scene ahead, taken with a highly-sensitive low light camera system.

The Visual Augmentation System is being developed by the company's Electro-Optical Surveillance Division at Basildon, England. It will show details, to both the pilot and the navigator, of targets at ranges well in excess of those which can be achieved with the unaided human eye and at ambient light levels ranging from daylight to starlight.


The new airborne system is an extension of the company's highly successful low light television systems which are widely used for industrial, commercial and naval applications including surveillance, target tracking and weapon aiming.



T is a regrettable fact that in these days of high labour costs more and more people with no electrical knowledge consider themselves competent enough to wire up plugs, extension leads and the like. Many are incorrectly wired and are, or may become, potentially lethal. Consequently, people who use these sockets, e.g. anybody running a disco or mending a friend's TV are placed at risk. There is little point in carefully "earthing" all the exposed metal if the socket has no earth wire.

To check connections before touching anything is obviously desirable but usually not possible as it is time consuming and not very polite. One can quite easily check a plug's wiring by pretence of checking the fuse, but eyebrows would be raised if you started removing the wall socket!

In disco work the problem is even more serious since most discos contain much exposed metal. This will be connected to the earth pin of the mains plug and hopefully to a true earth. Any insulation breakdown or broken wire in the equipment arising from vibration, damp or misuse—all very likely—that connects a high voltage to a part of a chassis will make the whole disco "live". The first person to touch a

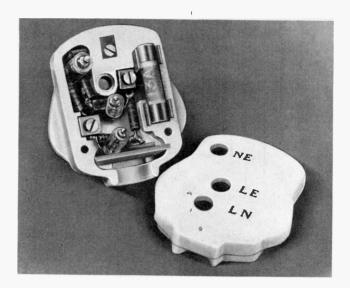

metal part will thus receive a considerable shock. Since his hands are likely to be sweaty and hence conductive the shock may well be fatal. However, despite the importance of correct earthing there is rarely time to remove sockets and even if time is available the results may be misleading. Just because a socket is connected to an earth wire does not mean that the earth wire is connected to earth!

In a recent case brought to the author's attention a professionally wired school science laboratory lacked an earth connection. Had a piece of equipment with a live to chassis short been plugged in, then every metal case in the laboratory would have become live. Fortunately the fault was discovered before this happened and it was speedily corrected. Furthermore, earths are subject to corrosion and a socket known to be safe may become dangerous after a few years.

Faced with this problem it was decided to design a tester that would be small, simple, robust and above all quick to use. The unit devised has been in constant use ever since.

# THE CIRCUIT

As can be seen from Fig. 1 the circuit contains three identical neon indicators. Each is designed to draw about 3.5mA from the mains, which ensures that floating earths will be identified as such providing the live/earth cable capacitance is less than about 50nF, which corresponds to several kilometres of cable.


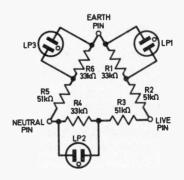


Fig. 1. Circuit diagram
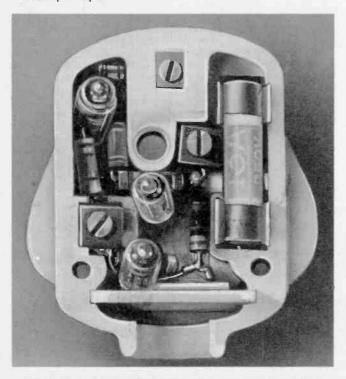
## CONSTRUCTION

The unit is built into a standard 13A mains plug as shown below. This requires careful construction and removal of some of the internal partitioning. When built and checked a thin smear of epoxy resin should be applied to prevent components moving.

It is necessary to shield LP3 from light generated by the other neons. This may be achieved by paint or a small piece of black pvc tape.



# COMPONENTS ...

R1, R4, R6 R2, R3, R5 33kΩ (3 off) 51kΩ (3 off)

R2, R3, R5  $5 \text{ R}\Omega (3 \text{ off})$  LP1-3 90V neon (3 off)All resistors  $\frac{1}{4}\text{W}$  5% carbon

13A mains plug

# USE

The plug is inserted into a socket for a few seconds and the pattern of neons noted. The plug should then be removed since it is not considered good practice to pass a current between live and earth. It is permissible in this case because of the short duration of the current and the safety orientated use. A number of neon patterns may be obtained and they are explained in Fig. 2. It should be emphasised, however, that only one pattern is safe and that any glow whatsoever in LP3 means the socket is dangerous.

The tester's simplicity makes it an aid that no DJ or constructor could safely do without.

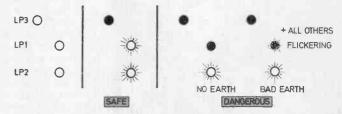


Fig. 2. Neon patterns and indications



# POINTS ARISING

# CHROMASONICS CATALOGUE (this issue)

Under regulators on page 5 the pin connections of the TO220 devices should be altered to the following:

Positive—1 in, 2 out, 3 common. Negative—1 common, 2 out, 3 in.

# **SOUND TRACK MONITOR (September 1978)**

In Fig. 2 there should be a break between C2 negative and TR1 emitter.

# TV GAME CENTRE (July-August 1978)

In Fig. 2.1, S5 is shown incorrectly wired. It should connect between Boundaries O/P and SEL B, and S1 between SEL A and Boundaries O/P. D11 is 7.5V. Resistor R33 is  $B\cdot 2k\Omega$ .

In Fig. 2.2, the lower pad on the p.c.b. for R36 is missing, and so the component lead will have to be carefully soldered directly to the track.

In Fig. 1, IC4(a) should be input—pin 6, and output—pin 7. Also S18 connects to IC1 pin 21, S17 connects to pin 20, and S9 connects to pin 18. IC1 pin 1 goes to QV.



FRANK W. HYDE

# THE USSR AND VENUS

In December there will be two nations in operation at the same time on the planet Venus. Under the Soviet programme for the study of the planets and outer space, the first vehicle of the new mission, Venus-11, an automatic station, was launched on September 9th to continue the programme of exploration of Venus. In the course of its journey it will make studies of the solar wind, cosmic rays, ultra-violet and X-rays from outer space. Gamma-rays are also part of the programme. The instrumentation of the vehicle is a joint Soviet-French project.

Venus-11 was put into the inter-planetary flight path from an intermediate orbit of an artifical earth satellite. The spacecraft will reach the vicinity of Venus in December. The deputy director of the Academy of Sciences Space Research Institute, said that "The first flight of this kind was made in 1961, when Venus-1 was launched from a heavy earth satellite. Venus-4 made the first controlled descent into the Venusian atmosphere."

This mission was recognised as a suitable basic structure and has since been adopted for other flights. The present United States programme follows this pattern. Previous flights of both American and Russian spacecraft have resulted in extensive data about the atmosphere and the surface structure of Venus. Along with the discovery of the nature of the atmosphere was the fact that Venus has no measurable magnetic field. Later Venus vehicles, Venus-5 and Venus-6, made simultaneous measurements at different points. In 1975 Venus-9 made a soft landing and sent back details of the Venusian surface. The landing craft from Venus-10 landed on the surface, sending back a picture of another part of the planetary terrain.

The American programme already under way as described in previous Spacewatch issues has now reached its decisive stages. With the Russian Venus-12 launched on September 14th, four vehicles are due in the

vicinity of Venus in December. The United States will in fact have six operative vehicles, four of which will enter the Venusian atmosphere and descend to various levels including the surface. The programmes so far undertaken by both the Soviet Union and the United States have followed similar patterns. Such a spectacular event as the one to take place in December this year is indeed a milestone of the greatest technical skills applied to extra-terrestrial exploration.

## **METEORITES**

At a Conference in Sudbury, Ontario, Dr John Wood of the Harvard-Smithsonian Center for Astrophysics at Cambridge, Massachussetts, stated that his findings indicated that the most probable origins of meteorites was asteroidal bodies. Dr Wood finds that the bodies that most nearly fit the facts are asteroids of the order of tens of kilometres in diameter. He suggests that certain asteroids acquired molten cores from aluminium-26 decay, differentiated into iron core and stony shell and cooled quickly through the upper temperature levels. All this violently overturns the traditional theories.

# **NEW PLANETOID**

The Soviet Institute of Theoretical Astronomy has registered a new asteroid which has been named "Constitution".

# A HUNDRED DAYS IN ORBIT

A new record for a stay in space was made when Vladimir Kovalyonok and Alexander Ivanchenkov celebrated their hundredth day in space. September the 21st is a fitting date for that to have been accomplished. They have suffered no serious discomfort and together with other long term astronauts show no long term adverse effects of the long residence in the weightless condition. This is the general view of all those engaged in the medical and biological studies of such effects. However, one Soviet doctor has declared 120 days as the limit of human endurance. There does not appear to be much support for the idea. No doubt confirmation or otherwise will be provided in the near future.

The two record breakers did not use the first aid kit much during the period of 100 days, preferring to "buck themselves up" with a tonic drink made from eleuthera bark.

# COMMUNICATIONS SATELLITES

On the 14th September Britain became one of the 16 countries committed to establish the European communications satellite system by the middle of the next decade. New wave lengths will be used and the method will be digital. The result of this will be to ensure not only a greater number of channels of operation but also better quality of long distance transmissions. Use will be made of the higher operational frequencies, 11 to 14 Gigahertz band, a little used band at the present time. Up till now the 4-6GHz band has been the most popular. Each year has, however, seen an almost regular doubling of traffic. The higher band and digital transmission will enable narrower bandwidths as well as improved levels of distortion.

# LANDSATS SURVEY THE SEA

The multispectral scanners of the Landsats 1 and 2 have been turned onto the Indian Ocean. In a collaboration effort the Cousteau Society and the Mapping Agency of the United States have investigated the possibility of using satellite imagery for shallow water surveys. Present charts of the Chagos Archipelago are based on an 1837 survey by ship.

The Landsat surveys show a number of discrepancies. Some very dangerous reefs were shown to be up to 15 kilometres from the positions shown on those charts. In one area a new reef was discovered. It was more than eight kilometres long and in an area shown by the charts to be safe and deep water. This discovery was instantly radioed to all shipping centres and new charts quickly prepared.

This highlights the importance of the system and provides a quick method of checking charts and changes that have taken place. It also has the advantage of freeing small survey ships for other work such as the location of small navigation hazards.

# **SOME SPACE FACTS**

At the end of August this year the total number of successful launches of spacecraft reached a total of 2,300 since the first Sputnik which heralded the space age. Of these vehicles 40 per cent came from the United States, 55 per cent from the Soviet Union and 5 per cent from other States. Of the 1,275 spacecraft launched by the USSR, 83 per cent were research satellites, three per cent were manned flights and two per cent were launched in co-operation with other States.


# A DESIGN FOR A MAN-MADE CITY IN SPACE

Stanford University and Ames Research Centre (controlled by NASA) are both becoming more and more occupied with the idea of designing a protective environment. This would be large enough to support about 10,000 people. One of the main difficulties is the adaptation of the human body, the mind too, in a cosmic environment. The tendency in all such speculative design is to model on the known existence and build the new in a similar shape to the old. The predisposition to introduce artificial gravity is one of the common additives to such designs.

The shape that has been considered viable is a doughnut design which optimises the surface area/space ratio. It is claimed that an artificial community with simulated conditions akin to those on earth could be a viable creation. This scarcely seems like progress or a desirable substitute. To build in the stresses and strains of existing life style is surely the prostitution of technology. Rather would it not be reasonable to develop genetically the body or carrier for a new age and environment. Adaptation so far has not been difficult for astronauts. What can be achieved with one or two people together surely can be done with communities. In the size of space environment envisaged, only mental adaptation would be imperative, all else would follow. If no real desire exists to reach out, it is better to leave well alone and stagnate instead of progress.

The Sinclair PDM35.

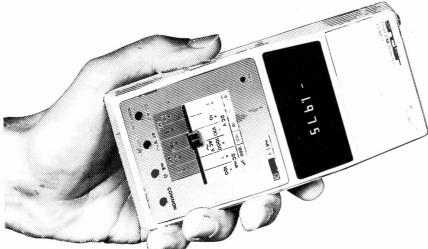A personal <u>digital</u> multimeter for only £29.95



#### Now everyone can afford to own a digital multimeter

A digital multimeter used to mean an expensive, bulky piece of equipment.

The Sinclair PDM35 changes that. It's got all the functions and features you want in a digital multimeter, yet they're neatly packaged in a rugged but light pocket-size case, ready to go anywhere.

The Sinclair PDM35 gives you all the benefits of an ordinary digital multimeter – quick clear readings, high accuracy and resolution, high input impedence. Yet at £29.95 (+8% VAT), it costs less than you'd expect to pay for an analogue meter!

The Sinclair PDM35 is tailormade for anyone who needs to make rapid measurements. Development engineers, field service engineers, lab technicians, computer specialists, radio and electronic hobbyists will find it ideal.

With its rugged construction and battery operation, the PDM35 is perfectly suited for hand work in the field, while its angled display and optional AC power facility make it just as useful on the bench.

#### What you get with a PDM35

 $3\frac{1}{2}$  digit resolution. Sharp, bright, easily read LED display, reading to  $\pm 1.999$ . Automatic polarity selection. Resolution of 1 mV and 0.1 nA  $(0.0001 \, \text{L} \, \text{A})$ .

(0.0001 u A).
Direct reading of semiconductor forward voltages at 5 different currents.
Resistance measured up to 20 M 11.
1% of reading accuracy.

Operation from replaceable battery or AC adaptor. Industry standard 10 M  $\Omega$  input impedance.

#### Compare it with an analogue meter!

The PDM 35's 1% of reading compares with 3% of full scale for a comparable analogue meter. That makes it around 5 times more accurate on average.

The PDM35 will resolve 1 mV against around 10 mV for a comparable analogue meter – and resolution on current is over 1000 times greater.

The PDM35's DC input impedance of 10 M 11 is 50 times higher than a 20 k11/volt analogue meter on the 10 V range.

The PDM35 gives precise digital readings. So there's no need to interpret ambiguous scales, no parallax errors. There's no need to reverse leads for negative readings. There's no delicate meter movement to damage. And you can resolve current as low as 0.1 nA and measure transistor and diode junctions over 5 decades of current.

#### Technical specification

DC Volts (4 ranges)

Range: 1 mV to 1000 V. Accuracy of reading 1.0% ± 1 count. Note: 10 M minput impedance.

AC Volts (40 Hz-5 kHz)

Range: 1 V to 500 V.

Accuracy of reading:  $1.0\% \pm 2$  counts.

DC Current (6 ranges)

Range: 1 nA to 200 mA.

Accuracy of reading:  $1.0\% \pm 1$  count.

Note: Max. resolution 0.1 nA.

#### Resistance (5 ranges)

Range: 111 to 20 Min.

Accuracy of reading:  $1.5\% \pm 1$  count. Also provides 5 junction-test ranges.

**Dimensions:**  $6 \text{ in } x \text{ } 3 \text{ in } x \text{ } 1 \frac{1}{2} \text{ in.}$ 

Weight: 61/2 oz.

Power supply: 9 V battery or

Sinclair AC adaptor.

Sockets: Standard 4 mm for

resilient plugs.

**Options:** AC adaptor for 240 V 50 Hz power. De-luxe padded carrying wallet. 30 kV probe.

#### The Sinclair credentials

Sinclair have pioneered a whole range of electronic world-firsts – from programmable pocket calculators to miniature TVs. The PDM35 embodies six years' experience in digital multimeter design, in which time Sinclair have become one of the world's largest producers.

#### Tried, tested, ready to go!

The Sinclair PDM35 comes to you fully built, tested, calibrated and guaranteed. It comes complete with leads and test prods, operating instructions and a carrying wallet. And getting one couldn't be easier. Just fill in the coupon, enclose a cheque/ PO for the correct amount (usual 10-day money-back undertaking, of course), and send it to us.

Sinclair Radionics Ltd, London Road, St Ives, Huntingdon, Cambs., PE17 4HJ, England. Regd No: 699483.

To: Sinclair Radionics Ltd, London Road, St Ives, Hun	tingdon, Cambs., PE17 4HJ. PE/12
Please send me(qty) PDM 35(s) @ £32.35 (incl. VAT) each£	Name
(qty) De-Luxe carrying cases  @ £3.24 (incl. VAT) each	Address
power @£3.24 (incl. VAT) each£ Post and packing (please add)£0.65	
I enclose cheque/PO made payable to Sinclair Radionics Ltd for (indicate total amount)	
I understand that if I am not completely satisfied with my PDM 35. I may return	World leaders in fingertip electronics

#### VALVE MAIL ORDER CO.

**Climax House** Fallsbrook Road, London SW16 6ED

> SPECIAL EXPRESS MAIL ORDER SERVICE

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m. Valves, Tubes and Transistors · Closed Saturday Terms C.W.O. only · Tel. 01-677 2424-7 Quotations for any types not listed S.A.E. Post and Packing 25p per order +8% V.A.T. Items marked \* 121%

Prices correct when going to press

Price when new £39.00 OUR PRICE ONLY £16.20

(P&P £1.00 each) Please note rope kits are available only by Mail Order ropelight

PIEZO HORNS
FANTASTIC SPECIAL OFFER
TO READERS OF PRACTICAL ELECTRONICS

Tweeters for your disco. PA
system or Hi-Fi. Frequency range 5K-20K
No X over required. They can be used in
any PA system up to 100W. Why pay more? OUR PRICE ONLY £4.99 each (P&P 35p each)

ROPELIGHTS Ropelight kits now available fro Roger Squire's — 22 feet long, 4 channel, including Tube, Bulbs and Multipin connectors. These ropelights are ex-demonstration stock and will require some bulb ex-demonstration stock and will require some bulb replacement — we will supply 20 spare bulbs free with your kit. Additional sets of 20 bulbs cost £4 86 each

#### BULGIN OCTAL PLUGS **AND SOCKETS**

0 There's always hundreds of Bulgin
Octal multiway plugs and sockets in stock at
Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System. P552 SOCKET £0.65 (P&P 35p) P551 PLUG £1.84 (P&P 35p) Carriage on 10 or more nominal £1 00 Also available 6-way multicore cable (6 Amps per core) ex stock. £0.65 per metre. Please phone for carriage quote.

**PROJECTORS** SQUIRE MULTIFECT 150
— including ratator and effects
wheel A truly versatile projector
which uses a powerful 150W
Tungsten bulb, all effects
attachments simply slot in ready for use

A BARGAIN AT £40.50 (P&P £1.00)

#### **PLUS MANY DISCO ACCESSORIES**

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES. For example fane and H. H. Disco Speakers 12" and 15" DSR and Garrard decks at discount prices.

SOLAR 250 Utilising a 250W Quartz-lodine bulb giving brilliant light output, this

projector is fan-cooled and can be used free standing or ceiling mounted Dual effect system for stunning versatility. Rotators are extra. Huge choice of special effects and attachments! NOW ONLY £70.20

Plus sockets. Fuses

Send Mail Orders to: Roger Squire's Mail Orders, Barnet Trading Estate, Park Road, Barnet, Herts EN5 5SA 01-441 3527 (Hotline) 01-441 1919 (Switchboard) Open: Mon-Fri, 9-5, 30

Personal callers: ROGER SOUIRE'S DISCO CENTRES LONDON: 176 Junction Road, Tufnell Park, N19 500, 01-272 7474 BRISTOL: 125 Church Road, Redfield, Bristol 855 9JR. 0272 550550 MANCHESTER: 251 Deansgate, Manchester M3 4EN. D61-831 7676

Open from 10-5 Tues-Sat 10-8 Weds. Closed Mondays.

#### CRESCENT RADIO LTD.

1 ST. MICHAELS TERRACE, WOOD GREEN, LONDON N22 4SJ (MAIL ORDER DEPT.)

01-888 4474

#### TELESCOPIC AERIAL

B Section Telescopic Aerial Length, extended: 96 cm. (37¾") Length, closed: 16 cm. (6¼") Nut and bott fixing at base of aerial. Only 70p each + 12½% VAT

"FLIP"!

AN ELECTRONIC VERSION OF TWO-UP OR ODDS AND EVENS.
We supply a complete kit of parts which includes a strong case and attractive front panel to give the finished game a long life and professional appearance.
Full assembly instructions are supplied. If you can solder you can make this great game.
An ideal first project to introduce you to electronics.

electronics.

Not only will 'FLIP' start you on a great hobby but you will own a game which will amuse you and your friends for hours.

Complete Kit: £5.25 + 8% VAT Post Free!

#### **BARGAIN LOUDSPEAKER**

heavy duty Mounting plate is integral with L/S chassis and has fixing holes with centres spaced at 5½" (diagonally)
Only £5.00 + 12½% VAT.

#### 2 WAY 8 OHM

HEAVY DUTY XOVER.

A 2 way 8 ohm H/D Xover suitable for L/S systems up to 100W. Input via screw terminals. Fitted with a 3 position 'HF LEVEL' switch which selects either Flat, —3d8 or —6d8.

Buy now while stocks last! Only £3.00 + 8% VAT.

#### **3 KILOWATT PSYCHEDELIC**

LIGHT CONTROL UNIT
1000W lighting per channel, max.
A 3 channel sound to light unit housed in a robust metal case, with a sensitivity control for each channel i.e. Bass, middle and treble.
Full instructions make this unit easy to connect to your present amplifier.
S A F for space sheet S.A.E. for spec. sheet. Still only £20.00 + 8% VAT.

#### POWER SUPPLY UNIT

PP1 – switched 3,  $4\frac{1}{2}$ , 6,  $7\frac{1}{2}$ , 9 and 12 volts at 500mA, with on/off switch and pilot light. Size: 130 × 55 × 75mm approx. Our Price: £6.00 + 8% VAT

#### SIX-PIECE **MINIATURE SCREWDRIVER** SET

Six precision screwdrivers in a hinged plastic box. Blade sizes: 0-8mm, 1-4mm, 2mm, 2-4mm, 2-9mm, 3-8mm. Our Price: £1.75 + 8% VAT



#### PIEZO ELECTRIC HORN UNITS

High Quality, High Power Tweeter. No Xover read. Freq. Response: 3.8kHz-28kHz. Spec. sheet sent on receipt of S.A.E. Our Price: £6.50 + 8% VAT.

#### **BARGAIN TRANSFORMER**

240V Primary 12—0—12V 500mA sec. Approx. size: 60 × 40 × 50mm. Fixing centres: 75mm. Price: £1.50 + 8% VAT.



'P&P' orders up to £5, Add 30p. Orders £5-£10, Add 50p. All orders over £10 post free! Please add V.A.T. as shown. S.A.E. with all enquiries please.



1

Personal callers welcome at: 21 GREEN LANES, PALMERS GREEN, N.13.



## 10+10 IMPLIFIER KIT

# £12-50


**INCLUSIVE** 

The Complete Stereo Amplifier Kit is £10.95 plus £1.55 post and packing.

This exclusive offer to P.E. readers, is an opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price.

The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a 24V 2A power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, sockets, wire, and an easily assembled wrap around cabinet to house the finished unit.



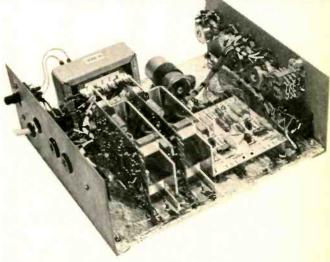

VLS	To: RTVC (P.E. Offer) 21D High Street, Acton, London W3 6NG <b>Mail order only</b>
of the coupon in BLOCK CAPITALS	Please send mekit/s at £12·50 (£10·95 plus £1·55 for p&p)
CK	I enclose P.O./Cheque NoValue
BLO	Name
n i	Address
odno	<u></u>
he co	
oft	Tel. No. (Home or Work)
Please complete both parts	Please allow 28 days for delivery OFFER CLOSES WEDNESDAY JANUARY 10th
ete bo	Name
ig F	Address
30 00	<u></u>
Pleas	
	From: RTVC (P.E. Offer) 21D High Street, Acton, London W3 6NG

# GITAR SOUND MULTI-PROCESSOR

PARTI

#### Mark A. Sawicki M. Sc. (Eng.) Alex. Kowalewski

NTIL now there has been no device which fills in the space between foot pedal effects and the incredibly expensive guitar synthesisers such as Roland, Arp and the Synthi Hi-Fli. Consequently the Guitar Sound Multiprocessor was designed to fill in the gap.

Some of the effects available are indicated opposite. These are of course variable and are only representative of what can be commonly achieved using the processor. By simple control manipulation it is possible to augment these, for example, to produce repeating echoes, rotary sounds, adding a metallic quality to the phaser effect or even computer voice sounds. To aid in achieving these a table of panel control settings is given in the final part.

To simulate the effects available with this unit one would have to rig up about six or seven separate effects units in a complex spaghetti network. The whole processor is based around a charge transfer device which processes incoming signals by varying delay times. Fig. 1 shows a fragment of a charge transfer unit such as the one used in this project. The device used is the Reticon SAD-1024 which is a dual analogue delay line, comprising two chains of 512 MOS transistors and storage capacitors arranged in a bucket

brigade configuration.

#### THE CHARGE TRANSFER DEVICE

Charge Transfer Devices form a fairly new family of integrated circuits which have only recently become cheap enough and available enough for the amateur to use. Charge transfer is the key to their operation, as the device samples an analog signal and shunts the samples along from cell to cell, just like a bucket brigade moving water. Indeed this analogy is so popular that the two types of CTDs are called Bucket Brigade Devices (BBDs) and Charge Coupled Devices (CCDs) respectively. Their relative merits lead to slightly different applications on the basis of price and complexity.

\*Cover shows Mike Rutherford from Genesis



#### Fuzz

This is a particularly simple and well-known effect implemented by symmetrical clipping of the signal. The result is to harden the sound by introducing very large odd-harmonic distortion.

#### Tremolo

Periodic modulation of the amplitude of a signal produces the well-known effect which, once implemented using a lamp and photo resistor is now achieved by variable gain amplifiers.

#### Vibrato

This effect is produced by a periodic variation in the pitch of a signal at a fairly slow rate (about 4Hz to 16Hz). In the past unreliable mechanical devices had to be used but the variable delay produced by a bucket brigade device provides an ideal solid-state solution.

The change in pitch occurs since the rate at which the signal exits is different from that at which it enters the device.

#### Flanging

Flanging gives a spacey sound as though the sound had travelled down a long tunnel. This is caused by passing the signal through a comb-filter, that is regularly spaced minima in the response.

In flanging, the minima are harmonically related while in a "phaser", which produces a similar but less profound effect, they are not. To obtain the full effect the notch spacing is varied periodically with time by using a variable delay circuit.

In the past, tape recorders had to be used to obtain the delay so that the effect was impractical when playing live.

#### Reverberation

This is the decaying multiple echo audible in concert halls and large rooms. Before the advent of solid state delay, the effect could only be produced by use of tape recorders or delicate and accoustic feedback-prone spring lines. The delayed signal is attenuated and fed back additively to obtain "reverb" which as opposed to "echo" only utilises short delays.

Let's look at the BBDs since this is the device used in this project. Going back to our analogy, in Fig. 1 the buckets are capacitors, the firemen are MOSFETs and the fire-chief is a two phase clock oscillator.

The two clocks ( $\emptyset_1$  and  $\emptyset_2$ ) are simply in antiphase and are non critical in terms of mark-space ratio and rise time as long as they do not overlap. Each time  $\emptyset_1$  is high, the first MOSFET turns on, and capacitor  $C_s$  is charged to the input voltage.  $\emptyset_1$  then goes low, freezing the voltage on  $C_s$  and  $\emptyset_2$  goes high turning on the third device. This combined with the second in the so-called tetrode configuration, discharges  $C_s$  into  $C_1$  so that the voltage which was on  $C_s$  is now on  $C_1$ —the action is like a switch buffered by a unity gain amplifier. On the next transition,  $\emptyset_1$  his high, taking a new sample and putting the previous one on  $C_2$ —there are thus two "buckets" per sample cell.

With the clock instructions, and pursuing the analogy, the bucket filling continues down the line (n cells) until the last bucket contains the same charge quantity as was present in the first bucket at the commencement of the sequence.

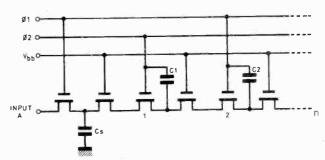


Fig. 1. Section of SAD 1024 equivalent

#### SCHEMATIC

Fig. 2 shows a complete block diagram of the sound processor. Block 1, the pre-amp, is required to maintain the output from the processor at a suitable level to drive any popular type of ancillary equipment, Block 2, the input low pass filter, is required to limit the input bandwidth with a sharp professional roll off. Delays are matched such that the cut off frequency is approximately 0.3 times the clock frequency giving a band below the Nyquist frequency of 0.5 times the clock frequency.



Prototype Sound Multiprocessor. Note the easy accessibility of all controls to the performer

1247

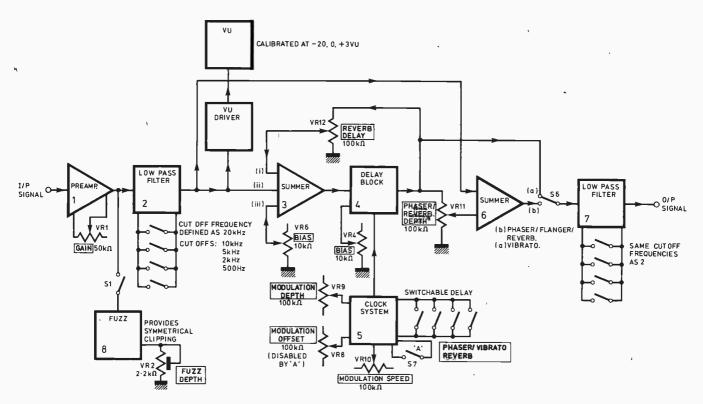


Fig. 2. Block diagram of the Sound Processor

Table 1 shows the frequency to delay time configurations. Roll off is 36dB/octave giving approximately 20dB rejection at the Nyquist frequency.

Table 1.		
Filter Frequencies	<b>Clock Frequencies</b>	<b>Delay Times</b>
20kHz	60kHz	4-27ms
10kHz	30kHz	8.53ms
5kHz	15kHz	17.07ms
2kHz	6kHz	42.67ms
500Hz	1.5kHz	170-67ms

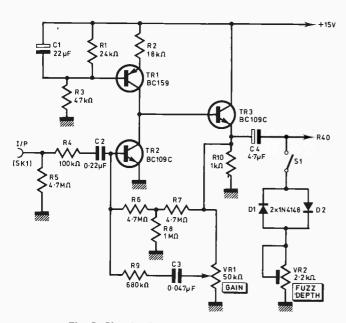


Fig. 3. Circuit of preamplifiers and fuzz

Block 3, the input summer, derives a proportion of the delayed signal for reverberation and phaser (flanger) reinforcement.

Block 4, the delay block based on the SAD1024 bucket brigade, provides a clock controlled delay where:

Time delay = 
$$\frac{256}{\text{f(clock)}}$$
 seconds

Block 5, the clock system, provides the delay block with suitable clock frequencies for controlling the amount of delay. The clock system has a frequency range of 1.5kHz to 60kHz.

The frequency modulation is produced by a triangle oscillator built on a pair of popular 741 op-amps, with variable frequency and modulation depth, individually adjustable to suit your requirements.

Block 6 is the output summer which determines phaser depth and controls the amount of reverberation fed through with the original signal.

Block 7 is an output low pass filter similar to block 2, giving a low impedance output and smooths the output by removing the sampling steps. Its cut-offs can be selected to match the input filter and delay settings.

Block 8 is an optional fuzz effect employing a pair of low cost silicon diodes providing standard symmetrical clipping.

#### PRE-AMPLIFIER AND FUZZ

Fig. 3 shows the complete circuit diagram of the preamplifier. It is comprised of a constant current section, with a BC109C and BC159 in a common emitter configuration, and another BC109C as an emitter follower. The gain of the pre-amp is determined by VR1, the minimum gain being about 7 and the frequency response being approximately 7Hz to 20kHz. The optional fuzz effect is produced by two diodes connected back to back for symmetrical clipping of the incoming signal waveform, and its level is adjusted by means of VR2. The whole pre-amplifier is mounted on the main board as can be seen in Fig. 5.

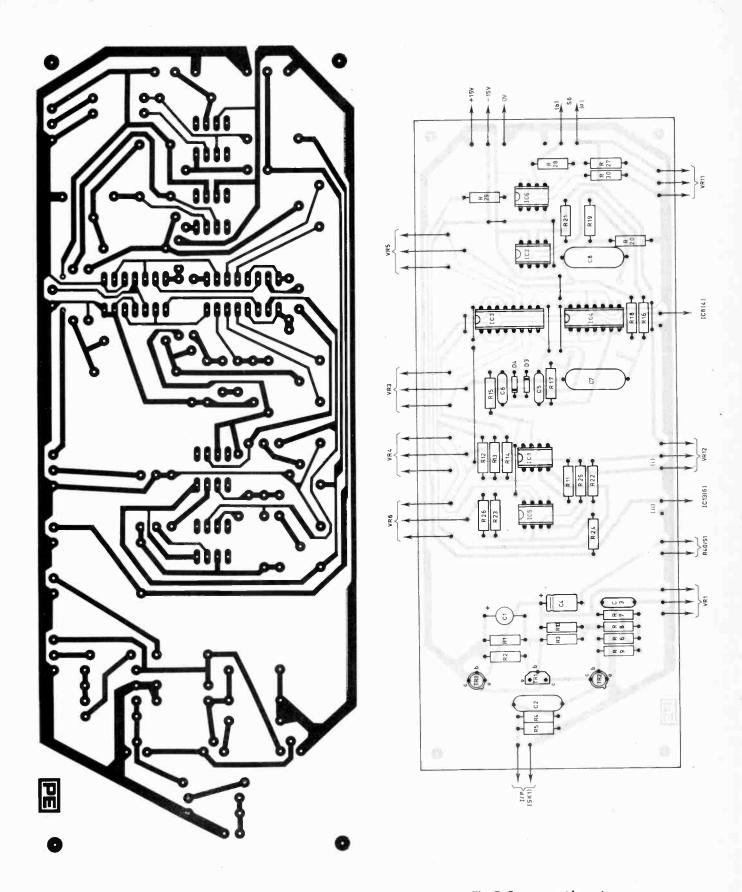


Fig. 4. Printed circuit of main board

Fig. 5. Component layout

#### COMPONENTS ...

D		ist		
n	uз	11.10	OF:	

resistors	
R1	24kΩ
R2	18kΩ
R3	47kΩ
R4	100kΩ
R5-R7	4-7MΩ (3 off)
R8	1ΜΩ
R9	680kΩ
R10	1kΩ
R11	47kΩ
R12	100kΩ
R13	47kΩ
R14	100kΩ
R15	10Ω
R16	33kΩ
R17-R18	1kΩ (2 off)
R19	33kΩ
R20-R24	100kΩ (4 off)
R25	33kΩ
R26-R29	100kΩ (4 off)
R30-R32	33kΩ (3 off)
R33	72kΩ
R34	25kΩ
R35-R37	100kΩ
R38	270kΩ
R39	100kΩ
R40-R41	8-2kΩ
R42-R43	100kΩ
R44-R45	100kΩ
R46-R47	8-2kΩ
R48-R51	100kΩ
R52	47kΩ
R53	100kΩ
R54-R55	1kΩ
R56-R57	6⋅8kΩ
All 5% carbon	n thin film
R46-R47 R48-R51 R52 R53 R54-R55 R56-R57	8-2kΩ 100kΩ 47kΩ 100kΩ 1kΩ 6-8kΩ

#### Capacitors

C49-C50

C1	22μF bead tantalum 16V
C2	0·22μF polyester 250V
C3	0-047μF polyester 250V
C4	4-7μF elect. 16V
C5-C6	0-1μF polyester 250V
C7-C8	0.68µF polyester 250V
C9	8-2nF polystyrene ±2½%
C10	2.2nF polystyrene ±2½%
C11	680pF polystyrene ±2½%
C12-C13	220pF polystyrene
C14	0·22μF polyester 250V
C15-C16	1nF polystyrene ±5%
C17-C18	1nF polystyrene ±5%
C19-C20	3-3nF polystyrene +5%
C21-C22	8-2nF silver mica 1%
C23-C24	39nF (3 x 10nF ceramic + 6.8nF poly-
	styrene + 2.2nF polystyrene)
C25-C26	56pF polystyrene ±5%
C27-C28	2·2nF polystyrene ±5%
C29-C30	470pF polystyrene ±5%
C31-C32	150pF polystyrene ±5%
C33-C34	56pF polystyrene ±5%
C35-C36	4.7nF polystyrene ±5%
C37-C38	820pF siver mica 1%
C39-C40	330pF polystyrene ±5%
C41-C42	100pF polystyrene ±5%
C43-C44	100pF polystyrene ±5%
C45-C46	1nF polystyrene ±5%
C47-C48	1nF polystyrene ±5%
C40 0F0	2.2.5.1

3-3nF polystyrene ±5%

C51-C52	8-2nF silver mica 1%
C53-C54	39nF (made up before)
C55-C56	4.7nF polystyrene ±5%
C57-C58	820pF silver mica 1%
C59-C60	330pF polystyrene ±5%
C61-C62	100pF polystyrene ±5%
C63-C64	56pF polystyrene ±5%
C65-C66	56pF polystyrene ±5%
C67-C68	150pF polystyrene ±5%
C69-C70	470pF polystyrene +5%
C71-C72	2.2nF polystyrene ±5%
C73	100pF polystyrene ±5%
C74	82pF silver mica 1%
C75	1,000µF elect. 16V
C76-C77	1,000µF elect. 25V
C78	0-1μF polyester
C79	0.1μF polyester
C80-C81	10µF elect. 25V

#### **Transistors**

TR1	BC159
TR2-TR3	BC109C (2 off)

#### **Integrated Circuits**

IC1-2	741N (2 off)
IC3	SAD1024
IC4	CD4013B
IC5-IC7	741N (2 off)
IC8	CD4046
IC9-IC13	741N
IC14	Dual (±15V) voltage regulator (RC4195D)

#### Diodes

D1-D2	1N4148
D3-D4	1N914
D5-D6	1N4001
D7/D9	TIL209 Green (2 off)
D8/D10	TIL209 Red (2 off)
D11	TIL209 Yellow
D12-D15	1A silicon bridge rectifier

#### **Switches**

S1	On/off slide type
S2-S5	Two pole push button change-over (4 off)
S6	Single pole change-over
S7	Single pole change-over
8-\$15	Six pole push button change-over

#### Miscellaneous

LP1—Mains neon, T1—15V, 0·2A. 15V, 0·2A 6VA low voltage transformer with two secondaries (R.S. 207–217) FS1–200mA fuse, fuseholder, Euroconnector mains socket, ME1–100µA f.s.d. VU meter

#### **Potentiometers**

VR1	50kΩ
VR2	2·2kΩ
VR3	1kΩ
VR4	10kΩ 3. 00.
VR5	1kΩ 3in. 20 turn cermet trimmers
VR6	10kΩ
VR7	25kΩ preset
VR8-VR1	2100kΩ lin. (5 off)


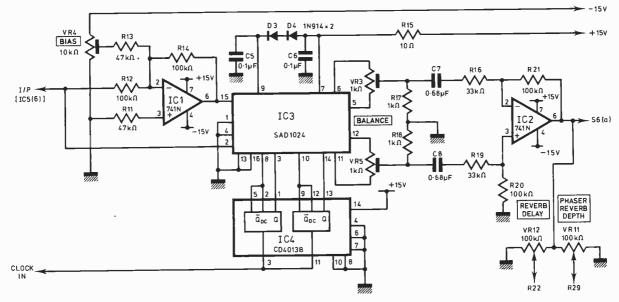


Fig. 6. Circuit of delay block

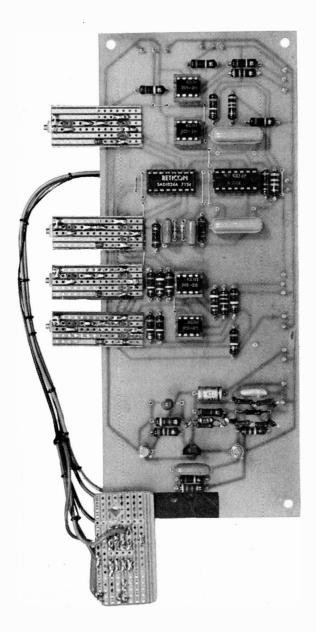

(Left) Main board. Here the cermet multiturn trimmers are mounted on small strips of Veroboard. The small Veroboard at the base is the meter driver circuit

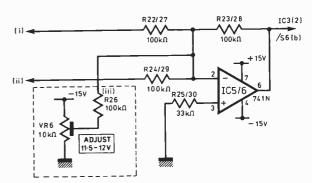


Fig. 7. Circuit of Summer 3. Summer 6 is identical apart from the exclusion of the boxed circuit

Due to the small amount of components required for the fuzz effect unit, it can easily be mounted on switch S1 situated on the far right-hand side of the control panel.

#### **DELAY BLOCK**

Fig. 6 shows the complete circuit diagram of the delay block which is centred on the SAD1024 dual-in-line bucket brigade on either side of which there is a buffer of a 741 opamp (Summers 3 and 6 respectively). The first being inverting and the second of differential configuration. The SAD 1024 requires a dual clock drive, one for each path, hence a dual D-type flip flop is used to split the signal from the clock. The logic level present at the D input is transferred to the Q output during the positive going transition of the clock pulse. Setting or resetting is independent of the clock and is accomplished by a high level on the set or reset line respectively. The SAD1024 is trimmed for symmetrical clipping. The bias on summer 3 is used for channel A, providing approximately 6V d.c. at pin 2, and channel B is at the same level at pin 15.

**Next Month: Filters and board construction** 

### MICRO-BUS

#### Compiled by DJD

Appearing every two months, Micro-Bus will present ideas, applications, and programs for the most popular microprocessors; ones that you are unlikely to find in the manufacturers' data books. The most original ideas will probably come from readers working on their own microcomputer systems, and payment will be made for any contribution featured here. This is also the place to air your views, in general, on this new technology, so let's be hearing from you!

#### PROGRAMMING PROMS

ICROPROCESSORS are now so cheap that it is feasible for the amateur to consider designing equipment based on a dedicated micro, but this is not possible without some way of programming memories so that this equipment will retain its "operating system" even when it is switched off. The most satisfactory type of non-volatile memory to emerge so far is the UVEPROM (Ultra-Violet Erasable Programmable Read-Only Memory), and the most economical of these, the 2708, provides 1K bytes of storage for as little as £7.

There are, however, two disadvantages of the 2708 which have been avoided in the next generation device from Intel—the 2716. The first is that the 2708 needs two supply rails of -5V and +12V in addition to the regular +5V supply; this can be overcome by deriving these supplies from the primary of the transformer supplying the +5V by using voltage doubler circuits as shown in Fig. 1.

The second drawback is that the 2708 is rather tricky to program; the memory locations must be programmed in sequence in several passes, and a 27V pulse is needed to program each byte. Nevertheless these difficulties are worth surmounting until the 2716 becomes available at a reasonable cost, and what follows is a description of a simple system of programming 2708s received from Tony Marshall of London.

"This PROM programmer is being used with an M6800-based microprocessor system, but could easily be adapted for others. The hardware was kept as simple as possible by



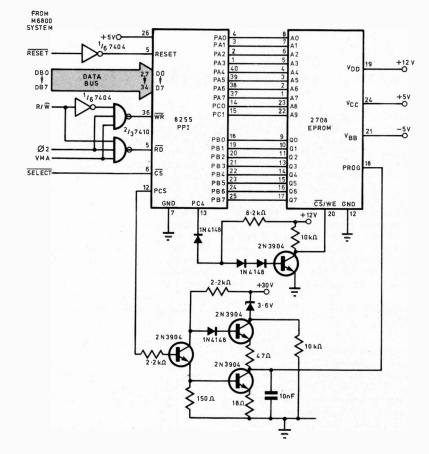


Fig. 2. Programmer for 2708-type ultra-violet arasable programmable read-only memories.

 

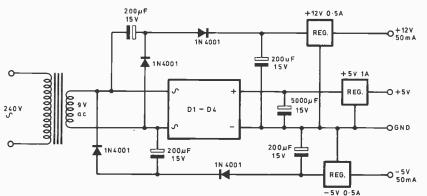

doing as much work as possible in the software, and it is based on a design described by D. W. Hoare and K. H. Yap at the 1977 SERT symposium "Microprocessor Systems and Software". The complete software for an M6800 to program and check a 2708 will be given here.

"To program a 2708 the  $\overline{\text{CS}}/\text{WE}$  input is first taken to +12V to put the chip in Write Enable mode. The address and data for a particular byte to be programmed are latched and a delay of 20 microseconds allowed for these to stabilise, and then a 27V 500 microsecond program pulse is applied to the PROG input. This is repeated for the 1024 bytes in the ROM, and the whole chip is

			NAM	PROM		9638				ORA		#\$20 PPIC	C.E.M.O.	ur por	OGRAM F	ou ce
		* PROM	PROGRA	MMER USIN	3 PPI	993A				STA		ROM+1			ADDRESS	
		*				003D				INC		NOC	MEV.	KDH .	-DUNE G	-
	2000	START	EGU	\$2000	DATA IN MEMORY	6040						ROM				
	9499	SIZE	EQU	1024	ROM SIZE	0042		0001		INC		KUM				
	8100	PPIA	EGU	\$8100	PPI SELECT ADDRESS	0045			ИОС	INX		#START+	CTTE			
	8101	PPIB	EQU	PPIA+1		9946				BNE		LOOP2	3122			
		PPIC		PPIA+2		0049				DEC		COUNT	FINT	SHED?		
	8103	PPICNT	EBU	PPIA+3				0000		BNE		LOOF1	NO			
		*	ADV 55			004E 0050				LDA		<b>*</b> \$30				
		* VARI	ABLES					8102		STA		PPIC	PUI	IN RE	AD MOD	E
		COUNT	RME	1		9955		0102		SWI	-		FINI	SHED		
	0001	ROM	RME	2		6677	J.		*	U#1						
	0002 0002	XTEMP		2					* READ	/ co	MPA	ARE PROG	RAM			
8883	0002	X I EMF	KME	-					*							
			OUTTNE	TO PROVID	F DELAY	0056	86	82	CHECK	LDA	Α	<b>*</b> \$82				
		# DELA	Y = A #	A + 15 U	SEC (1 MHZ CLOCK)			8103		STA	Α	PPICNT	₽ =	INFU		
		*	,					0000		LDX		<b>*</b> 0				
0005	44	DELAY	DEC A			005E	DF	01		STX		ROM				
	26 FD		ENE	DELAY				2000		LDX		#START				
9998			RTS			0063			LOOP3			ROM+1				
	•	*						8100		STA		PPIA				
		* PR06	RAM PRO	M : BEGIN	HERE	0068				LDA		ROM	5.54			
		*				896A				ORA		*\$36	KEAL	MODE		
0009	86 80	SET	LDA A					8102		STA		PPIC	CET	DATA		
	E7 8103			PFICHT				8191		LDA		PPIB	SAM			
989E	86 DB		LDA A	<b>\$216</b>		0072			TEST	BED.	A	Ø,X ERUAL	SHILL			
9919	97 00		STA A			9974	27	0.3	* NOT:		o Di Ci					
	CE 9000	LOOP 1	LDX	<b>#</b> 0					* NU1.							
	DF 01		STX	ROM								DATA IN	PROM			
	CE 2000		LDX	#START								SHOULD				
	96 92	L00P2	LDA A	ROM+1 PPIA	LOW 8 ADDRESS BITS	0076	E 4	98	* -	LDA						
0010	87 8100		STA A	ROM	EUM 6 HDDRESS CT15	0078				SWI						
	D6 01		DRA B	#\$2Ø	SELECT				EQUAL	INC		ROM+1				
	CA 20		STA B	PPIC	SELECT	0070				BNE		NOC2				
	F7 8102 A6 00		LDA A	9, X	DATA			0001	L	INC		ROM				
	B7 B101		STA A			9981			NDC2	INX						
	86 01			#21-15/6				2400	)	CPX		#START	+SIZE			
	8D D6		ESR	DELAY	21 USECS	9985				BNE	,	L00P3				
	C4 03		AND B			0087	3F			SWI			F1N	ISHED	OK	
	F7 8102		STA B	PPIC	PROGRAM PULSE				*							
	86 50		LDA A	<b>#500-15</b>						END						
	BD CD		BSR	DELAY	500 USECS											

Fig. 3. Complete program for the M6800 to program and verify a 2708.

programmed a total of 216 times so that each location receives a total program-pulse width in excess of 100ms. The total time needed is about 2 minutes.

To latch the address and data lines for the duration of the program pulse some sort of interface circuit is needed. The Motorola M6820 PIA does not provide enough output lines, but there is no reason why, with care, parts from one microprocessor family should not be used with a system based on another; the Intel "Programmable Peripheral Interface" or PPI provides three 8-bit ports and so is ideal, and its control signals WR and RD can be generated from the M6800's 02, R/W, and VMA using two TTL gate packages.

#### PROGRAMMABLE PERIPHERAL INTERFACE

Intel's 8255 PPI contains four 8-bit registers; three of these control the three read/write I/O ports, A, B, and C, and the fourth is a write-only control buffer used for programming the mode of operation. Ports A and B can be defined for either input or output, and port C is divided into two 4-bit halves each of which can be defined for input or output. Two of the three modes of operation use port C to provide special purpose control signals; mode 1 allows ports A and B to be either input or output with port C providing handshake control signals, and mode 2 allows port A to act as a bidirectional data port, again with control signals provided by port C.

There is also a facility for setting or clearing individual bits in port C by writing an appropriate word to the control buffer. The PROM programmer uses the PPI in mode O in which all three ports provide simple I/O; this is selected by writing \$80 or \$82 to the control buffer, the former defining port B for output and the latter defining it for input.

#### PROGRAMMER CIRCUIT

The complete circuit of the PROM programmer is shown in Fig. 2. The 12V Write Enable signal is switched from a PPI

output using a transistor, and the 27V programming pulse is switched with a three-transistor circuit; the rise-time of the program pulse must lie between 0.5 and 2.0 microseconds, and the 10nF capacitor at the output ensures this.

The program shown in Fig. 3 will program a 2708 using this interface circuit, and then verify that the data is correct. It assumes that the data is stored in a 1K block of memory starting at \$2000, and the PPI is addressed as locations \$8100 to \$8103. Subroutine DELAY uses a software timing loop to provide a delay proportional to the value in accumulator A; in systems with clock rates of other than 1MHz the delay constants should be recalculated.

To program the PROM the program is entered at SET, and if all is well it will return

to the monitor in under two minutes. To then verify the data the program is entered at CHECK and if all is well it will return at \$0087; any errors will be reported with a return at \$0078. In fact the system has programmed 2708s from several sources without ever giving any errors.

To erase a 2708 for re-use an ultra-violet lamp unit similar to the CHAMP-U.V. described in the June 1978 PRACTICAL ELECTRONICS was used, and it takes about 30 minutes. Complete erasure can be checked using the CHECK part of the program in Fig. 3 by first modifying the instruction at \$0072 to 'CMP A £\$FF'."

#### ONE-LINE CHARACTER DISPLAY


The following ingenious circuit displays a line of ASCII characters on a standard oscilloscope; it was received from *Dr. S. C. Craddock of Consett*, and what follows is based on his description.

"This simple one-line VDU fills the gap between 7-segment displays and T.V. based full-sized VDUs. The oscilloscope needs no modification provided that it has a flat response from 10Hz to 500kHz, a time-base setting of 50Hz or thereabouts, and negative pulse synchronisation. Few oscilloscopes would fail to meet these specifications."

The circuit is shown in Fig. 4. It uses a mixture of 74 series TTL devices and 40/45 series CMOS devices. The 2513 is a character generator with a 64-character set. The microprocessor has only to output one of the 16-20 characters every millisecond. The subroutine listing in Fig. 5 shows how to do this.

The particular keyboard used clears a status bit, D7, when a key is pressed to indicate that data is ready in the keyboard buffer; the subroutine therefore first sets this bit by writing to the keyboard address. It then outputs a set of 16 characters one at a time at 1 millisecond intervals until the keyboard

Fig. 4. Dr. S. C. Craddock's one-line V.D.U. circuit.

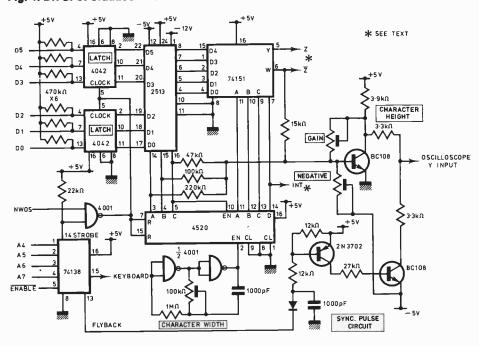

status bit is cleared, and then returns with the key value in the accumulator.

As it stands the circuit deflects the spot up away from the undeflected raster to form the characters; there is therefore a negative image of the line of characters below the actual line, as shown in the photograph of Fig. 6. This avoids the need for a z-modulation input on the oscilloscope, but if one is available one of the outputs Z or  $\overline{Z}$  can be used to blank the spot instead, and the  $15k\Omega$  resistor from  $\overline{Z}$  should then be omitted. A negative-going sync. pulse is generated at the end of the line of characters to trigger the oscilloscope.

The display could be interrupt-driven by taking the point marked INT (pin 14 of the 4520) to the interrupt input on the microprocessor; a character could then be output at each interrupt, generated when the previous character had been displayed, and between interrupts the micro would be free to do something else. In Dr. Craddock's system

		OT STAIC		RS TO BE DISPLAYED
	, P2 PC	INTS TO	DISPLAY CIR	CUIT ADDRESS
	3			
0000	KYBD	•	x,00	KEYBOARD ENABLE
0020	STROBE		X.50	DISPLAY STROBE
0030			X'30	; FOR SYNC/FLYBACK
0000	,	- 0220		
0000		.=OF20		
OF20 03	BEGIN:	SCL		
OF21 CAOO	BEGIN:	ST	WWDD (3)	
OF21 CAGO	Cı	LDI	KYBD(2) -17	SET KYBD STATUS BIT
OF25 O1	A:	XAE	-17	; FOR COUNT
0F26 C501	A:		41.411	
		LD	01(1)	;LOAD CHARACTER
OF28 CA2O		ST	STROBE(2)	STORE TO VOU
OF2A C400		LDI	9	
OF2C BF01		DLY	1	DELAY 1 MS.
OF2E OI		XAE		
OF2F F401		ADI	1	; INCREMENT AND
OF31 9CF2		JNZ	A	; TEST COUNTER.
OF33 C230		LD	FLYBK(2)	*
OF35 C5FO		LD	@-16(1)	; RESET Pl
OF37 C200		LD	KYBD(2)	; KEY PRESSED?
OF39 9402		JP	В	; YES
OF3B 90E6		JMP	C	NO - DISPLAY AGAIN
OF3D 3F	B:	XPPC	3	; RETURN
OF3E 90E0		JMP	BEGIN	
	3			
0000		. END		

Fig. 5. Subroutine for SC/MP to read then write 16 characters from memory.

the oscilloscope input is switched automatically between the VDU circuit and the output of a digital-to-analogue converter

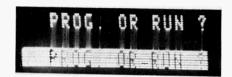




Fig. 6. Typical display generated by the one-line V.D.U. To avoid the need for Z-modulation the spot is deflected clear of the raster to generate a character.

by the strobe pulses for the relevant latch, so that text and waveforms are displayed together on the same oscilloscope.

# readout

#### ... a selection from our postbag

Readers requiring a reply to any letter must include a stamped addressed envelope. Opinions expressed in Readout are not necessarily endorsed by the publishers of Practical Electronics.

#### Patently Obvious?

Sir—I read with great interest the details of the patent application by Tokyo Shibaura Electric Company on improving musicality. (P.E. Oct. p. 1100).

It must be easily realised that no electrical component can be a perfect realisation of its electrical value. Components are manufactured according to manufacturing tolerances using various materials. An electrical component such as a resistor or capacitor will give harmonic distortion to a sine wave due to its non linearity. This will be usually very low and negligible for most practical applications.

Aluminium electrolytic capacitors are usually the worst commonly used component in this respect. Listeners have claimed to detect audible differences due to the inclusion of a large capacitor between amplifier and loudspeaker. Indeed, one writer to a hi-fi magazine claimed that the published distortion figures of the PE Gemini amplifier featured some years ago could only be obtained if the amplifier was measured before the electrolytic capacitor.

In the circuits of Fig 1 and Fig 3 of your review of the patent, the capacitors are used in smoothing the DC supplies. In fact this is a very common practice in amplifier design. A small non-polarised capacitor  $(0.1 \text{ to } 2.2 \mu\text{F})$  is placed on the circuit board of the power amplifier. Its purpose is to prevent amplifier instability at high frequencies. Hence it is not placed with the main electrolytics as its effect will be negated by the inductance of the power leads to the power amp.

The amount of improvement will depend on how susceptible the power amplifier is to supply variations. Owing to the nature of transistors, fluctuations on the power supply can be present at the output. This is one of the causes of dynamic crosstalk between amplifier channels. In practice, feedback will reduce this to low proportions. Other techniques of reducing dynamic crosstalk are additional smoothing of low current circuits and cascade circuitry.

In the circuit of Fig 4 the aluminium electrolytic is used in the signal path. Here additional components are added to present as low an impedance as possible at all audio frequencies. Ideally because of the non linearity of the aluminium electrolytic, an alternative capacitor should be of high enough value to present a low impedance at audio frequencies with the aluminium capacitor being used to maintain the phase response at low frequencies. If the second capacitor is a tantalum-as occurs in some parts of moving coil head amps-a third non polarised capacitor is used to maintain the low impedance at very high frequencies. It may be of course that the very high frequencies are removed by the designers, bandwidth limits, but in audio terms, it is better to remove extreme high frequencies by a linear filter than a non linear.

I find it hard to believe that the patent exists as described in your magazine. The ideas behind it have been applied many times in the past by audio engineers, including myself, who would appear to have a far greater understanding of the problem than the author of the patent would appear to have as read from your article.

I trust that this information is of help to your readers.

Graham Nalty, Borrowash, Derby.

To obtain a patent is often surprisingly easy—if the Patent Office Examiner doesn't know of, or can't find, any prior publication of what is claimed, then he will accept the application. It is thus quite conceivable that the patent in question is a re-hash of old ideas, even though those ideas are new to the inventor. But, and it is a big but, sometimes an inventor stumbles on an idea that, although simple in hindsight, has been overlooked or forgotten by others over the years. One object of reporting new patents in PE is to give readers an opportunity to make up their own minds on just such issues.

Adrian Hope

#### Communications -

Reader D. N. Townsend, interested in electronics and computers, would be pleased to know if there are any amateur computer clubs or associations in the Leeds area.

124 Main Street, Leeds, Yorks., LS17 8JB. Reader M. V. Ramesh would like to establish a few pen friends in England (preferably students undergoing graduate study in electronics).

F-76, Students Hostel, Indian Institute of Science, Bangalore-560 012, India.



£14.95 Per stereo pair + £3.40 p&p.

simulated teak veneer, with instructions.



#### EASY BUILD RECORD PLAYER KIT



for the D-I-Y man who requires a stereo unit at a budget price comprising ready assembled stereo amp, module. Garrard auto/ manual deck with cueing device, pre-cut and finished cabinet work Output 4 watts per channel, phones socket and record/replay socket including 2 SPHERICAL HIFI speakers. £19.95 p&p £4.05

#### **BARGAINS FOR PERSONAL SHOPPERS**

PORTABLE STEREO RADIO CASSETTE RECORDER UNREPEATABLE



150 16 VOLT MAINS TRANSFORMER, 21/2 amp £2.50 BSR Record auto deck on plinth with £11.95 tereo cartridge ready wired LED 5 function men's digital watch £5.95 stainless steel finish LCD 5 function men's digital watch stainless steel finish £6.95

LCD 8 Function CHRONOGRAPH men's digital £13.95 watch, stainless steel finish POCKET CALCULATOR, With LED display, memory £2.95 and percentage key

AM/FM DIGITAL CLOCK RADIO Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer

weeter inc. crossovers



£13.95 125 Watt Power Amp Module Mains power supply for above unit. £3.50 MUSIC CENTRE CABINET with hinged smoke acrylic top, finished in natural teak veneers, size 30%" x 14½" x 7%" approx. £5.95

MULLARD Built power supply £1.50 DECCA DC 1000 Stereo Cassette P.C.8 complete with switch oscillator coils and £2.95 tape-heads. DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 31/2" approx £20.00

VIDEOMASTER' Super Score TV Game £14.95 vith pistol mains operation PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock

.W. MW, SW, VHF mains/battery operation £41.95 " TAPE TRANSPORT Mechanism—a selection £8.95 of models from

SANYO Nic/cad, battery, with mains charger equivalent size and replaces 4 SP11 type batts. Size 3¾"x 1¼ x 2" approx. £7.50 £1.50p

7777 TUNER AMPLIFIER CHASSIS COMPLETE

Ready built. Designed in a slim form for compact, modern installation Rotary Controls Vol Dn/Dff, Bass, Treble, Balance.

Push Buttons for Gram, Tape, VHF, MW, LW and 5 button rotary

selection switch.

Power Output 5 watts per channel Sine at 2% THD into 15 Dhm
7 watts speech and music.
Tape Sensitivity Playback 400mV/30K OHM for max output Record

Tapes as maturity riaprack south 750 km in that output weeds 200m/550k output available from 255kHz. (150m//100k) deviation FM signal Frequency Range (Audio) 50Hz to 17kHz within ± 1dB Radio FM sensitivity for 3dB below limiting better than 10 uV AM sensitivity for 20dB S/M MW 350 uV/Metre LW 1mV/Metre AM sensitivity for 20dB S/N MW 350 uv/ments
Size approx length 16" x height 23" x depth 43" **£19.95** p&p £2.25 240 Volts AC Complete with Circuit diagram.

ullard

**AUDIO MODULES IN BARGAIN PACKS** 

**CURRENT CATALOGUE** 

#### SEE OUR PRICES

PACK 1. 2 x LP1173 10w. RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input.

OUR PRICE £4.95

PACK 2. 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2. Stereo pre amp for magnetic, ceramic and auxiliary inputs.

illus. OUR PRICE p+p £1.00

£7.45

**ACCESSORIES** 

Suitable power supply parts including mains transformer, rectifier, smoothing and output capacitors. £1.95 £1.00 p+p

Recommended set of rotary stereo controls comprising BASS, TREBLE, **VOLUME and BALANCE.** 

p+p 50p 95p

PACK 3. 1 x LP1179/2 FM Tuning head with AM gang, 1 x LP1165/1 AM/FM IF module, 2 x LP1173/10w. RMS output power audio amp modules + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input.

> OUR PRICE p+p £1.00

THIS MONTHS OFFER
added to our bargain packs.
When you buy Pack 3 at £9 95, together with a mains transformer at £1,95 and a set of controls for 95p you receive FREE a Mullard LP1400 Decoder to match Listed at £11.90



#### 20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak finished cabinet. Silver fascia with alumin rotary controls / pushbuttons, red mains indicator and stereo jack socket. Functions switch for mic. magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm face. £29.90

SPECIAL OFFER FOR PERSONAL SHOPPERS ONLY

FREE. 4 dimensional stereo sound adaptor, when purchasing the 20x20 Viscount amplifier

#### 30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output. 60x60 watts peak. For use with 4-15 ohms speakers. £23.00 without cabinet. £29.00 complete with cabinet. p&p £2.50 in each case.

**f23.00** + £2.50 (NOTE Cabinet not **f29.00** £2.50

without cabinet paper available separately.)

SPECIAL OFFER Complete with 30x30 WATT AMPLIFIER IN KIT

Cabinet WITH SPEAKERS 2 Goodnan compact 12" bass woofers with cropped size 14,000 Gauss magnet. 30 watt RMS handling + 3\%" approx. £49.00

BUILT AND READY TO PLAY

30x30 Viscount. Available fully built and tested

BARGAIN **PORTABLE** DISCO CONSOLE with built-in nre-amp

tweeters and crossovers.

Here's the big-value portable disco console from RT-VC! It features t BSR MP 60 type auto-return, single play professional series record decks. Plus all the controls and features you need to give fabulous disco performances Simple connects into your existing slave or external amplifies

£64.00 pap £6.50

+ p&p £4.00

39.00

+ p&p £2.50

50 WATT MOND DISCO AMP £29.95 &P £2.50 Size approx

13%" x 5%" x 6%" \

50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and trible controls and master volume.

SPECIAL OFFER. The above 50 watt amp plus 4 Goodmans Type 8P. 8"
speakers. Package price £45.00 + £4.00 P&P.

70 & 100 WATI MONO DISCO AMP
Size approx.

14" × 4" × 10\fmathref{1}".

Brushed aluminum

Brushed aluminium fascia and rotary controls

Five vertical slide coptrols master volume tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to (PFL) lets YOU hear next disc before fading 140 watt peak it in. VU meter monitors output £57 p & p [4.00 100 watt £65 Output 100 watts RMS 200 watts peak

BDS 95 TYPE Belt drive chassis turntable less cartridge. £2.55 p & p £24.95 £2.55 p & p CARTRIDGES to suit above £4.95 Tenorel magnetic stereo.

GARRARD DECK CC10A. Record changer with cue and stereo ceramic cartridge. Size 12" x 81/2" approx. £7.95

BARGAINS FOR PERSONAL SHOPPERS

GARRARD 86SB Deck £26.95 | GARRARD SP25 MKIV Deck

GARRARD35SB Deck. £24.95 with Shure head. £25.95

Plinth and cover for BSR decks £6.00



210 HIGH STREET, ACTON W3 6NG ALL PRICES INCLUDE VAT AT 121/2% All items subject to availability. Price correct at 1.11.78 and subject to change without notice.

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Half day Thursday. ACTON: Mail Order only. No callers GOODS NOT DESPATCHED OUTSIDE UK



Why pay more when you can enjoy the advantages of true capacitor discharge ignition (CDI) at virtually pre-inflation prices? The benefits to your car and your pocket are enormous - easy starting in the coldest of cold weather, an end to burnt contacts and arcing problems, better engine wear and petrol consumption and, of course, easy and secure fitting to your vehicle. ORDER NOW WHILE WE CAN HOLD TO THESE PRICES -

State if for pos. or neg. earth.

INC. V.A.T. AND POST FREE IN U.K.

> DIY KIT COMPLETE

**READY BUILT** ONLY

£14·95

Why be without?

- MADE IN OUR DWN U.K. FACTORY
- SWITCH FOR INSTANT RETURN TO ORDINARY IGNITION
- NEG OR POS EARTH MODELS
- **M** HEAVY GAUGE ENCLOSED METAL CASE
- BUILT FOR YEARS OF DEPENDABLE SERVICE
- FULL 12
  GUARANTEE MONTHS

Pay by Access or Barclaycard if you wish

#### STIRLING SOUND

37 VANGUARD WAY, SHOEBURYNESS, ESSEX. Tel: (03708) 5543 Shop – 222/224 West Rd., Westcliff-on-Sea.

	To Stirling Sound, 37 Vanguard Way, Shoeburyness, Essex.	
	Please send	@ £14.95 @ £12.75
Í	NAME	
i	ADDRESS	
:	DE 12	

BREADBOARD'78 Stand

#### THE CHEAP **VIDEO** COOKBOOK

by D. Lancaster Price: £6.95

110 WAVEFORM GENERATOR PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston Price: £3.15

YOUR OWN COMPUTER by M. Waite

Price: £1.70 UNDERSTANDING DIGITAL ELECTRONICS by G. McWhorter Price: £3.95

**BEGINNER'S GUIDE TO TAPE RECORDING** by I. R. Sinclair Price: £3.15

**BEGINNING BASIC** by P. E. Gosling

Price: £3.15

THE CATHODE-RAY OSCILLOSCOPE & ITS

by G. N. Patchett

Price: £4.00

RAPID SERVICING OF TRANSISTOR EQUIPMENT Price: £2.75

by G. J. Kina

Price: £3.20

COLOUR T.V. WITH PART, REF. TO THE PAL SYSTEM by G. N. Patchett Price: £6.00

ELECTRONICS & RADIO AN INTRO. by M. Nelkon

INTEGRATED CIRCUITS & SEMICONDUCTOR **DEVICES THEORY & APPLICATION** 

Price: £6.80

\* ALL PRICES INCLUDE POSTAGE \*

#### THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

> 19-21 PRAED STREET LONDON W2 INP

> > Phone 01-723 4185 Closed Saturday I p.m.

ELTA istribution

75 Willowtree Avenue Gilesgate Moor Durham DH11DZ (0385) 62760 or 61765 Company

#### ALL GOODS TOP QUALITY, NEW AND BRANDED AT TREMENDOUS PRICES BC170

AC126 0.44 BC184 AC127 0.40 BC262 AC128 0.40 BC478 BC107 0.10 BD131 BC108 0.10 BD132 BC109 0.10 BF245A BC109C 0.15 BFY51	0.15 0.10 0.25 0.29 0.34 0.38 0.24 0.20	2N2219 2N3055 2N3702 2N3704 2N3706 2N3819 2N5459	0.25 0.50 0.11 0.12 0.12 0.25 0.32
BC177 0.15 8SY95A  TRANSFORMERS {P/P 0.35} 240V 12V or 6-0-6V @ 200m 220V 12V or 6-0-6V @ 200m 240V 12V & 12V both @ 250m 240V 12V & 2	A 0.98	C/MOS 4000 4001 4002 4006 4007 4009	0.15 0.15 0.15 0.78 0.17 0.45
LINEAR 348 Quad 741 14 dil 342 Volt. Reg TO-202 200mA +5V, +12V, +24V please sta 317 Adj. Volt Reg. @ 500mA 741 Op Amp. 8 dil 555 Timer 8 dil	1.13 ate 0.79 1.48 0.27 0.28	4011 4012 4013 4015 4016 4017 4018 4020	0.15 0.15 0.45 0.78 0.40 0.78 0.85 0.95
RESISTORS JW 100R to 10M (10, 47, 68 et VEROBOX		4022 4023 4024 4025	0.90 0.18 0.65 0.18
71 x 49 x 19 mm Black ABS  C.S.C. BREADBOARD & TEST EQUIPMENT Experimentor 300 Logic monitor LM1 Logic monitor LM2 Logic Probe LP1 Logic Probe LP2 Protoboard 100 Protoboard 60 Protoboard 203 Protoboard 203A D.F.M.MAX 100	6.20 6.55 28.40 66.55 30.55 18.10 11.95 9.45 53.65 72.77 74.95	4026 4027 4028 4029 4030 4032 4033 4047 4049 4050 4054 4056 4066	1.60 0.50 0.78 0.95 0.50 0.90 1.20 0.40 0.40 0.90 1.35 1.35 1.10 0.53
Sloping front boxes; 6.75 × 7.5 × 3.25" DMC1 3.00 × 5.63 × 6.0" DMC2	4.25 3.85	4093 4510 4511	0.70 1.10 1.15

OPTOELECTRONICS. 7 Seg. display Red 0.6": c.a. 1.30; c.c. 1.30. 9 Seg. Alphanumeric display Red 0.6": c.a. 1.80; c.c. 1.80. L.e.d.s.: 3 mm red 0.10; 3 mm green 0.18; 3 mm yellow 0.18; clips 0.08.

CASH / POs / DRAFTS / CHEQUES / IMOs / ACCESS NO. ACCEPTED. Telephone us with your ACCESS No. for really fast service.
TERMS P/P 25p (unless otherwise stated) plus VAT @ 8%. TRADE / EXPORT / EDUCATION AUTHORITY ORDERS WELCOME.

#### MAINS TRANSFORMERS (TM)

All have 230/240v 50Hz Primary

Voltage 1v 2.4v 4v 6v 6.5v 6.5v 6.5v-0-6.5v 6.3v-0-6.3v 6.3v 8.5v 8.5v + 8.5v	2 amp 5 amp 7 amp 3 amp 3 amp 200 mA 100 mA 750 mA 100 mA 2 amp 1 amp	Our Ref. TM 1 TM 2 TM 32 TM 3 TM 37 TM 21 TM 21 TM 7 TM 33 TM 4 TM 12	Price £1.94 £1.62 £2.70 .85 .85 £1.62 £1.62 £1.62 £1.89 £1.62	Post .40 .45 .60 .40 .40 .40 .45 .40 .50
sep. winding 9v	1 amp 1 amp 21 amp 23 amp 5 amp 4 amp 12 amp 100 mA 3 amp 100 mA 1 amp 2 amp 2 amp 1 amp 2 amp 3 amp 1 amp	TM 12 TM 5 TM 6 TM 11 TM 38 TM 15 TM 50 TM 21 TM 21 TM 7 TM 10 TM 19 TM 41 TM 11 TM 12 TM 12 TM 13 TM 14	£1.62 £1.62 £1.89 £2.70 £3.24 £4.86 £1.05 £1.62 £2.16 £1.89 £1.62 £3.24 £2.70 £1.62 £1.90 £1.62	40 45 45 .80 £1.25 £1.25 £1.25 .50 .50 .50 .50
1 amp) 20v 20v 20v-0-20v 24v 24v 24v +	2 amp 6 amp 12½ amp 6 amp 1½ amp 2 amp	TM 50 TM 46 TM 15 TM 15 TM 16 TM 17	£3.78 £4.32 £4.86 £4.86 £2.12 £2.70	£1.25 £1.25 £1.25 £1.25 .60
2v 7 amp 24v 25v 26v 30v 37v 40v 40v 40v 40v tapped @ 30v, 20v &	2 amp 4 amp 1 1 amp 2 amp 8 amp 37 amp 3 amp 5 amp	TM 39 TM 40 TM 18 TM 39 TM 15 TM 34 TM 46 TM 48	£2.97 £3.78 £2.43 £2.98 £4.86 £31.86 £4.32 £5.02	.70 .80 .60 .60 £1.25 Enquire £1.25 £1.25
10v 40v-0-40v	6 amp 2 ½ amp	TM 15 TM 48	£4.86 £5.02	£1.25 £1.25

#### **FREE GIFT**

To all customers this month we will send a free copy of our unique booklet

"TEST EQUIPMENT"

50v – 2 amp with 6.3v shrouded 50v		TM 22	£4.86	
60v tapped 40v	8 amp	TM 29	£11.65	£1.75
& 20v 70v	2 amp 4.5 amp	TM 46 TM 24	£4.32 £7.02	
75v – 3 amp with 6.3v	4.5 атр	INI 24	17.02	£2.50
shrouded	<del></del>	TM 23	£8.10	£2.00
75v 80v tapped 70v	4½ amp	TM 24	£7.02	£2.50
& 75v 80v centre	4 amp	TM 24	£7.02	£2.50
tapped	21 amp	TM 48	£5.02	£1.25
100v	1 amp	TM 25	£7.02	
100v-0-100v 200v	amp amp	TM 25 TM 25	£7.02 £7.02	£1.75 £1.75
250v-0-250v	• '		27.02.	21.75
with 6.3v 2A		TM 36	£3.78	
250v 500v	100 mA 50 mA	TM 36 TM 36	£3.78 £3.78	£1.00
260v	60 mA	TM 26	£3.76	£1.00
1000v (and				
other secs) 4 Kv	60 mA 5 mA	TM 43 TM 49	£6.50	£2.00
5 Kv	5 mA	TM 30	£4.05 £7.02	.70 £1.00
8 Kv	5 mA	TM 45	£4.05	£1.00
8.5 Kv	10 mA	TM 31	£10.26	£2.00

Full range of Mains to 120v Auto-transformers available

**SOUTHERN TRANSFORMERS 103 TAMWORTH ROAD CROYDON CR9 1SG** 

# impedance

#### BY TOBY BAILEY & BOB WHITAKER

PART 2

F you examine the specification of, say, a tuner or a tape deck output it will generally be stated in the form of the output level and the output impedance. For example, if the output impedance is  $10k\Omega$  and the output is connected to an input with an impedance of  $5k\Omega$  then only a third of the open-circuit output voltage will appear at the input.

Once you know the open-circuit output voltage and the impedance of an output you can predict how it will behave when faced with any load.

Thevenin's theorem states that any chunk of linear circuitry connected to two terminals can be represented as a perfect voltage source in series with an impedance. It also says how to find the output of the voltage generator and the value of the impedance. By a perfect voltage generator is meant a voltage source which is capable of supporting its full output into arbitrarily small load impedances, i.e. the voltage doesn't drop when heavy currents are supplied. By a linear network is meant circuits made up of a mixture of some or all of resistances, capacitances and inductances.

The output voltage of the voltage generator can be measured as the open circuit voltage across the terminals of the network, the series impedance can be measured across the same terminals if we first turn off all internal generators in the circuit and replace them with their internal impedances; which will be zero in the case of a perfect voltage generator.

#### **EXAMPLES**

Look at the circuit shown in Fig. 9(a). A 1kHz source with an unloaded output of 1V and an internal impedance of  $100\Omega$  is connected to a T-network. We will now use Thevenin's theorem to simplify it to an equivalent circuit consisting of a perfect voltage generator and a single impedance. First, however, we will redraw the circuit with complex impedances—R1 has been lumped together with C1 to make one impedance.

You should have no trouble with the calculations if you follow the first article in this series (October '78). The result is shown in Fig. 9(b). Now we can calculate the open-circuit output voltage which is:

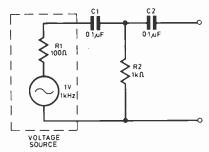


Fig. 9(a). Circuit to which Thevenin's theorem can be applied to get a simpler equivalent

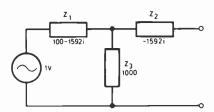


Fig. 9(b). The same circuit with complex impedances

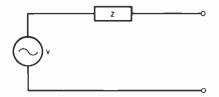


Fig. 9(c). Abstract equivalent of previous

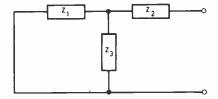


Fig. 9(d). Translating the complex impedance Z into its components

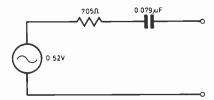


Fig. 9(e). Thevenin equivalent

$$V \times \frac{Z_3}{Z_1 + Z_3} = \frac{1 \times 1000}{1100 - 1592i} = \frac{1 \times 1000 \times (1100 + 1592i)}{3.74 \times 10^6} = \frac{1 \times 1000 \times (1100 + 1592i)}{0.294 + 0.425i} = \frac{1 \times 1000}{1100 + 1592i} = \frac{1 \times 1000}{1100 + 1592i}$$

This complex number has a magnitude of 0.52 and a phase angle of 55 degrees. This means that the voltage generator in our equivalent circuit of Fig. 9(c) has an output of 0.52V and is 55 degrees out of phase with the original one—the latter piece of information isn't often of much interest.

The impedance Z which must be put in series with the generator is the impedance across the terminals if we switch off the voltage generator and replace it with its internal impedance of  $100\Omega$ ; see Fig. 9(d). Readers who have followed the examples in Part 1 should have little difficulty in arriving at a value of:

$$Z = 705 - 2017i$$

We can now translate this complex impedance back into its components. The real part of Z corresponds to a  $705\Omega$  resistor and using the formula for the impedance of a capacitor on the remaining imaginary part we get:

2017= 
$$\frac{1}{2\pi f C}$$
  
C=  $\frac{1}{2\pi 1000 \times 2017}$   
=0.079  $\mu F$ 

So we see the equivalent circuit of Fig. 9(a) in Fig. 9(e). From this circuit we can deduce the effect of any sort of load.

#### **BIAS NETWORK**

Another example of the use of Thevenin's theorem is shown. In Fig. 10(a) a typical biasing stage where the values of the base biasing resistors have been found by assuming a base current of  $10\mu A$  and employing the rule of thumb that the current through them should be ten times the base current. But what effect does the loading actually have? If we assume that the 10V supply has negligible internal resistance then we can produce the Thevenin equivalent of the bias network, as shown in Fig. 10(b). The open-circuit output of the bias networks is:

$$\frac{39}{56 + 39} \times 10V = 4 \cdot 1V$$

and the series resistance is simply the

parallel impedance of the bias resistors  $(22k\Omega)$ . We can now see that if the base of the transistor draws  $10\mu A$  then the voltage will drop by

 $22 \times 10^3 \times 10 \times 10^{-6} = 0.22V$ 

On the basis of this calculation we could well decide this was far within the necessary tolerances and increase the bias resistor values to save current and increase the input impedance of the stage.

#### **NORTON'S THEOREM**

There is another very similar theorem which allows all sources to be converted into a perfect current generator (one with infinite internal impedance) and an impedance connected in parallel. The output of the current generator is the current produced when you short the output of the network. The impedance is calculated in exactly the same way as for the Thevenin impedance (Fig. 11).

The two theorems are essentially very similar because any Thevenin equivalent can be turned into a Norton equivalent very easily and vice-versa.

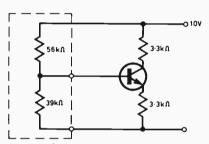


Fig. 10(a). Typical biasing stage


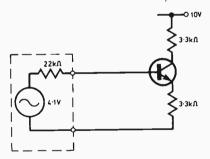


Fig. 10(b). Thevenin equivalent

As an example, suppose we have a transistor connected as a common emitter amplifier with an output impedance of  $20k\Omega$  and a signal current of 0.5mA. We then have two possible equivalent circuits, Figs. 12(a) and 12(b), often one will be more useful than the other for a particular calculation.
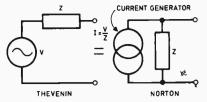
#### MAXIMUM POWER TRANSFER THEOREM

Another theorem relating to the loading of sources deals with the way to extract the maximum power from any given one. Good engineering design requires loading a source with a resistance that will permit



THEVENIN AND NORTON CIRCUITS ARE INTERCHANGEABLE

Fig. 11. Equivalent voltage and current generators

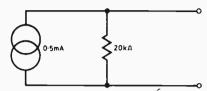


Fig 12(a). Norton equivalent of common emitter amplifier

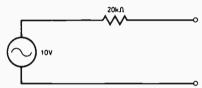


Fig. 12(b). Thevenin equivalent of same

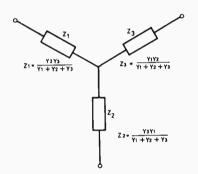


Fig. 13. Star network with delta to star conversion formula


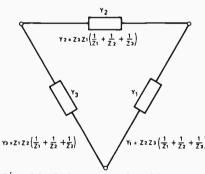


Fig. 14. Delta network with star to delta conversion formula

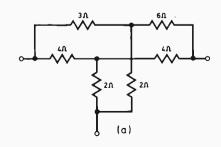

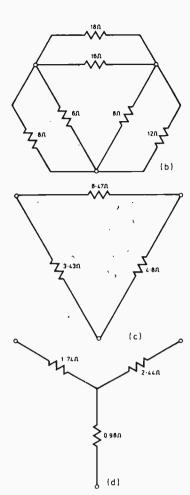


Fig. 15(a-d). All of these circuits are equivalent

maximum power transfer. Let us first take the purely resistive case, where we put a load R2 across a source with open-circuit voltage V and internal resistance R1. The power dissipated in R2 changes as R2 is varied—it reaches a maximum when R1 = R2.

The general case of this is when we have a complex internal impedance and a complex load impedance is  $R+X_{\rm i}$ , the maximum power is dissipated into the load when the load impedance is  $R-X_{\rm i}$ 


#### STAR-DELTA TRANSFORM


The last of this selection of useful impedance theorems for this article states that the networks shown in Figs. 13 and 14 are interchangeable, if the component values are changed according to the formulae shown with each circuit.

Using the circuit in Fig. 15(a) as an example of the use of these formulae for simplification of networks, first we transform each of the "stars" in Fig. 15(a) to a delta in Fig. 15(b). Note that we can reduce the two "deltas" to one delta since there are now three pairs of parallel resistors—this was not the case with the two "stars". We now have a single delta, Fig. 15(c), from which we can return to a single star form if we wish as in Fig. 15(d).

# NEXT NONTH

# Electronic NOUGHTS and CROSSES

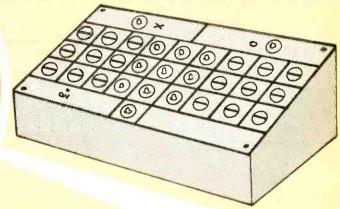

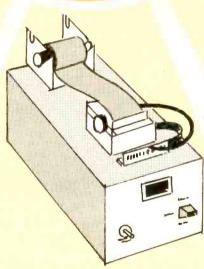

### Etectric VEHICLES

Why is it taking so long for electric traction to take over from the conventional internal combustion engine (i.c.e.) powered vehicle?

A look at what's going on in the UK has revealed some interesting facts.

This issue sees the completion of the P.E. V.D.U. and next month we bring you another first in the microcomputer field; the first d.i.y. printer. Suitable for most systems the P.E. Microprinter slashes the cost of this invaluable peripheral.


MICROPRINTER



PRACTICAL

ELECTRONICS

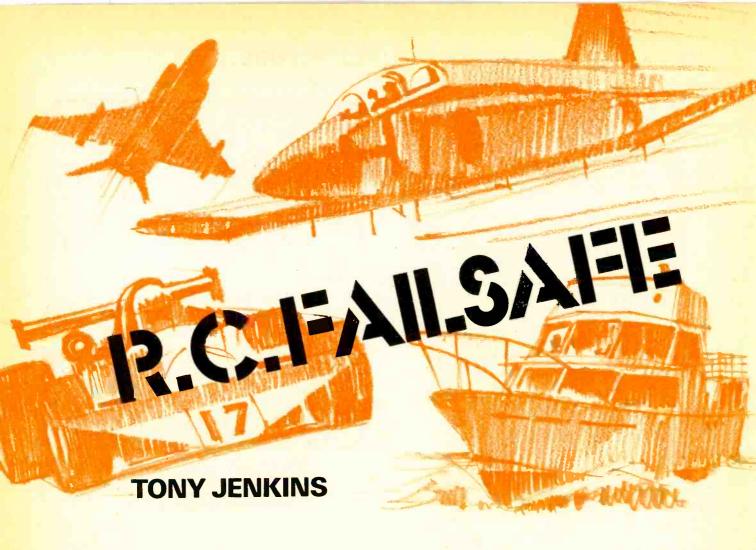OUR JANUARY ISSUE WILL BE ON SALE FRIDAY, 12 JANUARY 1979



If your radio controlled model out-ranges the transmitter, pre-program it to avoid a crash, with this simple circuit

MODERN digital radio control equipment is normally very reliable, but there is always a danger of loss of signal, due to faulty transmitter, dead transmitter battery, or the model even going out of range.

The normal result of this is total loss of control, and probable loss of the model as well!

The unit to be described can eliminate this problem, because when it is connected in line with a servo, if the signal is lost, after a short time (approx. half a second) the unit feeds a signal to the servo, which causes it to take up a preset position (which can be adjusted throughout the servo's normal range of movement), where it will remain until signal is regained, when control will revert to the transmitter as normal.

A typical installation may require two to four units, normally one for each servo in use, set so that if signal is lost, a model aircraft for example, may go into a shallow dive, circling slowly, with engine at idle.

It is also possible to use them on a glider, so the transmitter may be switched off, and the model left circling, thereby conserving battery life, as receiver consumption is minimal with no servo movement.

#### CIRCUIT DESCRIPTION

Referring to Fig. 1, IC1 is a CMOS quad 2 input NAND gate connected to function as a data selector. When pins 2 and 12 are "high" the pulses on pin 13 appear at the output, pin 8. When pins 2 and 12 are "low", pulses from the 555 oscillator (connected to pin 5 of IC1), are fed to pin 8.


Control of pins 2 and 12 is via the rectifier circuit consisting of C3, D1, D2, R1, and C1. When there is a signal from the receiver coming into pin 13 on IC1 (and also C3), the voltage on the positive end of C1 will be around 4.5 volts, well above the threshold of the CMOS logic i.c., so the pulses from the receiver will be fed through to pin 8, and from there to the servo.

When the signal is lost, there will be a d.c. level on the input to the unit, no signal will pass through C3, capacitor C1 ( $1\mu F$ ) will discharge via R1 ( $680k\Omega$ ), and the voltage on C1 will fall below the switching threshold of IC1, and so approximately half a second after loss of signal, control of the servo will be transferred to IC2. When the signal is recovered, C1 will again charge, and control of the servo will be transferred back to the receiver.

The oscillator formed by IC2 is slightly unusual, in that instead of the usual near square wave output, the output consists of short 1–2ms (variable by VR1) positive pulses,

with a gap of approximately 20ms between, thus simulating the output of the receiver decoder.

The operation of the oscillator is as follows: C2 charges via VR1, R3, and D3, until the voltage across it equals two thirds of the supply voltage, at which point pins 3 and 7 of the i.c. go "low", as the internal comparator (I/P at pin 6) switches. C2 then discharges at a much slower rate, via R2 (D3 now being reversed biased) until the voltage on it is reduced to one third of the supply voltage, when the other comparator (I/P at pin 6) in IC2 switches, pin 7 is then effectively open circuit, pin 3 goes "high", and the cycle commences again.

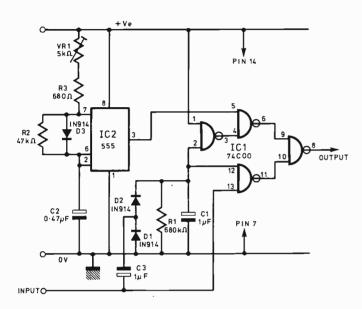

#### CONSTRUCTION

This unit is *only suitable for positive pulse systems,* which the majority of modern R.C. equipments use.

Construction is fairly straightforward, if normal care is taken. Figs. 2 and 3 show the p.c.b. layout.

Insert and solder all components (taking care to observe correct polarity, etc.), leaving IC1 to the last. This is a CMOS device, and may be damaged by careless handling, unless precautions are taken.

A servo extension lead to suit the equipment is required. To connect the unit, the positive and negative wires in the extension lead should be cut, a short length of insulation should be removed, both positive leads connected to the positive pad on the board, and both negative leads to the negative pad. Now trace the control lead from the receiver (in three wire systems the remaining wire), normally if the receiver connecting block is checked, it will be the only wire not common to all servos.

This should be cut and the insulation removed from the ends. The end that will connect to the receiver should be connected to the "in" pad on the unit, and the other end to the "out" pad. The unit is now ready for testing.

#### TESTING .

Set the preset to mid travel, connect up the R.C. equipment with the unit in line, with the servo. Switch on the transmitter, then the receiver, and check that control is as normal. Switch off the transmitter, the servo should jerk towards one end of its travel, as normal. After a short delay, the servo should move back towards the centre of its travel, and the position may now be varied by means of the preset.

#### COMPONENTS ...

#### Resistors 680kΩ R1 47kΩ 6800 R3 All & watt 5% **Potentiometers** VR1 5kΩ Sub min hor'preset (4.7kΩ will do) Capacitors 1µF Tantalum bead (2 off) C1, C3 0.47µF Tantalum bead C2 **Integrated Circuits** 74000 IC2 LM/NE 555 Diodes D1, D2, D3 1N914/1N4148 Miscellaneous Printed circuit board (available from W.K.F. Electronics. Worksop 720695) Servo extension lead—to suit equipment in use.

Fig. 1. (left). Circuit diagram of Failsafe

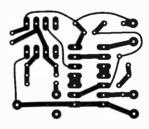


Fig. 2. Printed circuit layout (actual size)

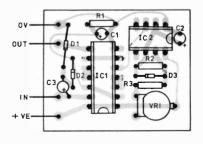


Fig. 3. Component layout

#### WARNING

To cope with the different pulse lengths used by different manufacturers, the pulse range available from the unit is wider than required by most servos. Do not exceed the servos normal range of movement, as it is possible (although most types will withstand a certain amount of mistreatment), that damage may occur. Adjust the preset slowly.


#### **INSTALLATION**

If all is well, the unit(s) may now be installed in the model. This is simply a matter of sticking them in a suitable position with "servo-tape", and adjusting them for a suitable trajectory with no signal.

If the unit does not work in one mode, but is okay in the other, check the area around the rectifier (C3, D1, D2, R1 C1). If the unit does not work at all, carefully inspect the board for solder bridges or wrongly placed components.

If nothing is visibly wrong, temporarily transfer the lead from the output to pin 3 of IC2, if control by the preset is now possible, it is probable that IC1 is faulty. If still no output, it is probably IC2 (or associated components).

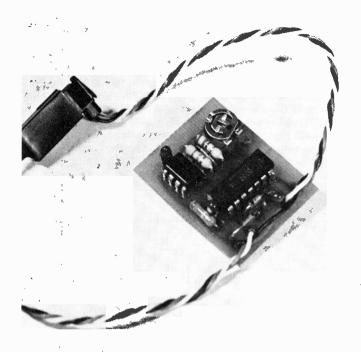The unit may also be built as a servo tester, in which case only R2, R3, C2, D3, IC2, and VR1 are then required. VR1 should now be a calibrated potentiometer, and the output is taken from IC2 pin 3. It can be built into a suitable box with 6V battery and on/off switch, and a socket for the servo.



One R.C. Failsafe board. As many can be used as required to preset the various servos

# R.C.MCTCR CCNTRCL PA.DAKIN

#### Transistor proportional control with no junction losses at full power

OST motor controls for R.C. systems use a servo to operate switches and resistors or wipers on a resistance board, etc. This causes heat, reduces the torque available from the motor and is susceptible to dirt and wear.

This circuit will overcome these problems and unlike most solid state controllers will have *full power* output, as well as proportional control forwards and reverse.

It is suitable for cars and boats, and with modifications can be used in aircraft. The receiver must give a positive pulse output of 1 to 2ms every 20ms.

#### **CIRCUIT DESCRIPTION**

The full circuit diagram is shown in Fig. 1. The controller uses two 3140 operational amplifiers connected in the voltage comparitor mode, one inverting and the other non-inverting. The positive incoming pulses from the decoder produce a ramping voltage across' R2 C1 which is used to trigger the i.c.s. VR1 and VR2 are adjusted so that a 1.5ms pulse is "neutral" (sticks centre) and no voltage appears at point A.

As the pulse lengthens to 2ms (full forward) IC1 produces an output of varying duty cycle between 0–100 per cent which turns on TR4, and supplies drive current to the Darlington output pair TR5 and TR6. Transistor TR6 has an inherent volt drop of approximately 0.65V. Therefore to supply full voltage to the motor, VR4 is adjusted so that at maximum voltage at point A, relay RLB operates and short-circuits TR5 and TR6.

As the decoder pulses shorten to 1ms (full reverse) IC2 will produce an output of varying duty cycle. When an output appears at point B relay RLA is operated reversing the motor connections. The motor drive is exactly as before except in the opposite direction. Again RLB operates at full reverse to give maximum power.

TR3, R9 and D7 form a simple series regulator to supply a constant voltage to the relays. This is essential since the motor battery volts may vary by up to  $\pm 16$  per cent of nominal voltage, which would affect the relays, pull-in point.

Diodes D2 and D3 prevent the i.c. with a low output, sinking the output of the other i.c. when it is high. D5 and D6 are protection diodes across the relay coils to prevent high voltage transients affecting the circuit.

Capacitors C2 and C3 prevent relay chatter. C4 is motor suppression. D9 and D10 give visual indication of output from the i.c. These may be left as permanent fixtures or temporarily wired for setting up only.

It should be stated at this point that the relay confacts are rated at 5A. It has been found that the contacts will handle up to 15A when not *switching* at these high currents. RLA operates when little or no current is flowing, and RLB provides a low resistance path across TR5 and TR6. If a single-pole-make is not available a d.p.d.t. may be used, and the contacts paralleled up to handle up to 10 amps. Although the 3140 is specified, several units have successfully been built using the standard 741, and it must be emphasised that the minimum specified voltage for this i.c. is  $\pm 3V$  (6V supply). However, with careful selection some can be found to work well with a single 4V supply.

#### COMPONENTS

#### Resistors

 $10k\Omega$ R1 R2 180kΩ R3, R4 2.2kΩ (2 off) R5. R6 150Ω (2 off) R7-R9 1kΩ (3 off) R10  $10k\Omega$ (See Table 1) R11 R12  $1k\Omega$ 

R13 27k $\Omega^*$  All  $\frac{1}{4}$ W 5% except where stated. \* required for smooth changeover if 3140 op-amps are used

#### **Potentiometers**

VR1-VR4 10kΩ min cermet.

#### Capacitors

C1 1μF C2 47μF C3 100μF

C4 1µF non polarised

All tantalum bead types (12V minimum) except where stated

#### **Integrated Circuits**

IC1, IC2 3140 or 741 (2 off)

#### Diodes

D1-D6 1N4148 or similar (6 off) D7 (See Table 1)

D7 (See Table 1N4148

D9, D10 Any 20mA i.e.d. red and green (1 off each)

D11, D12 BZX61 (2 off)

#### **Transistors**

TR1-TR4 BC182L or BC184L (TR3 - BD131 if relay

currents exceed 100mA each)

TR5 BD131 or TIP31A TR6 2N3055 or TIP3055

#### Miscellaneous

Stripboard or p.c.b. (approx 35 x 75mm)

Metal box 63 x 76 x 25mm approx.

6BA or M3 nuts and screws as required

Solder tags, heatsink compound, plug to suit receiver

Wire suitable for 10A minimum

2 relays p.c.b. mounting 5A contacts d.p.d.t. 100mA operating current max. (RS 349–642)

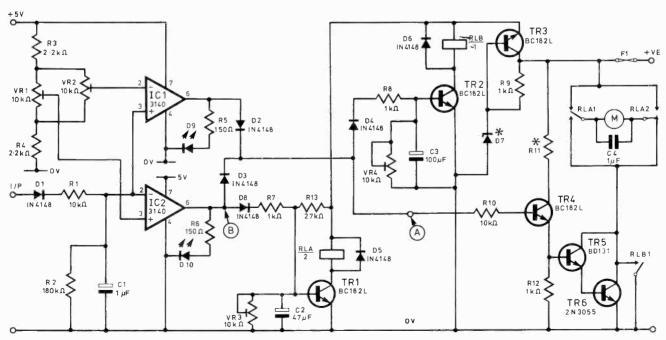


Fig. 1. Circuit diagram

#### **CIRCUIT CONSTRUCTION**

For use in aircraft, only part of the circuit need be constructed. Omit IC2, D3, D8, D5, D7, TR3-TR6, R5, R7, R8-R10, R13, VR3, C2, and RLA. This will give an "all or nothing" control which is all that is required for electric flight.

The circuit can be constructed on a p.c.b. (or stripboard), of approximate dimensions  $35 \times 75$ mm (smaller for aircraft). See Figs. 2 and 3.

Resistor R11 and diode D7 must be chosen to suit motor supply voltage. See Table 1. Pay particular attention to polarites of diodes, capacitors, and pin connection of i.c.s and transistors. TR5 and TR6 must be mounted on the case which acts as a heatsink. If 12–15V supplies are used, and the motor is drawing more than about 8A, an extra heatsink may need to be added to the top of the case. For the lower power controller (6–9V supplies), RS type Extra Flex may be used for the heavy current wires. If the average current consumption is greater than 8A a higher rated wire should be used. See Fig. 4 for relay wiring.

#### **SETTING UP PROCEDURE**

First check again the position, value and pin connections of all components. Having done this, connect the unit to the receiver only, ignore centre taps on 4-wire systems. Switch on transmitter and receiver with transmitter throttle control in the centre (neutral position) and the l.e.d.s may glow. Adjust VR1 and VR2 until both I.e.d.s are just extinguished (The l.e.d.s may have to be shaded so that an accurate setting can be made.) Slowly move the stick to the forward position; D9 should gently glow and increase to full brightness. The same should happen to D10 when the stick is moved in the reverse direction. This has set the neutral position. Leave the transmitter controls in Neutral. Connect the motor supply but not the motor. It would be advisable to substitute a low value fuse of about 0.5A or 1A for F1, to protect TR5 and TR6 against shorts whilst setting up. Set VR3 to its earth end, and VR4 to its "base" end. Neither relay should be energised. Gently give reverse until D10 just starts to glow, and adjust VR3 to pull in relay RLA. Return sticks to neutral and relay RLA should drop out. If not. readjust VR3. Now move sticks to full forward position and adjust VR4 to operate Relay RLB. Return sticks to neutral and check that no l.e.d.s glow and no relays are energised.

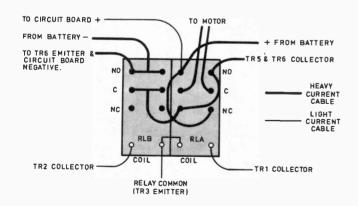


Fig. 4. Relay wiring arrangement for the standard configuration of two-pole change-over type relays.

	Та	ble 1.	
Nominal Motor Voltage	R11 Value	e & Rating	D7 Voltage
6	<b>33</b> Ω	2W	5-6
9	47Ω	2W	6-2
12	62Ω	2.5W	6-8
15	75Ω	3.0W	6-8 or 12V if 12V relays are used

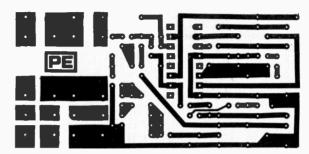


Fig. 2. Printed circuit layout shown at full size

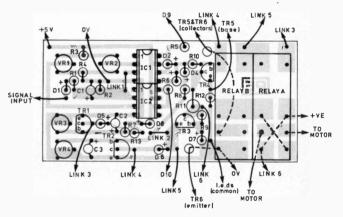


Fig. 3(a). Component layout. IC1 and IC2 may be plugged into a single d.i.l. socket

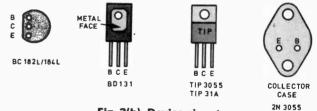


Fig. 3(b). Device pinouts


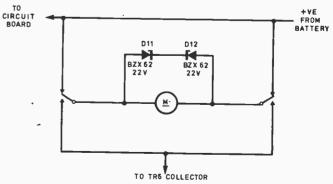


Fig. 5. Clamping diode circuit to suppress motor interference.

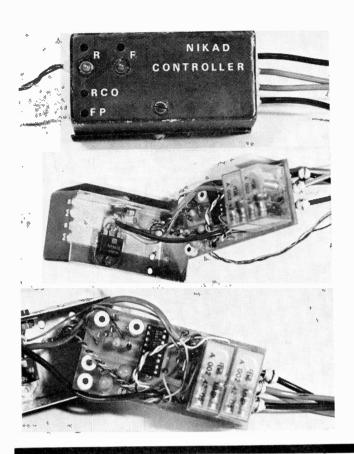

Increase to full reverse and again check that RLB operates. If not, adjust VR4 slightly until it operates at full forward and reverse.

When all is satisfactory remove the low value fuse and connect the controller output to the motor and check for full proportional control in both directions. If the motor is run with no load, the full effect of the controller will not be seen, since the motor will run up to full revs at approximately half throttle. Having set up the controller and fitted it in its box the unit can now be mounted in the model.

#### **FURTHER NOTES AND SUGGESTIONS**

For relays that require a pull-in current greater than 100mA, TR3 should be a BD131 or TIP31A. This may be soldered directly into the board and will handle approximately 500mA without a heatsink. R11 is a high wattage type because when a TIP 3055 and TIP 31A are used for the Darlington output pair, should both have low gain, 200mA or so will flow as base current in TR5. This current is limited by R11. However if TR5 and TR6 are fairly high gain, the wattage may be reduced to 0.5W.

Fig. 3(b) shows semiconductor connections for specified types. If interference is suspected from the motor, try earthing one side of the motor connections to its case but ensure the batteries are left floating or damage to the control unit may occur.


If motor interference still persists, remove C4 and add clamping diodes as shown in Fig. 5. These are BZX61 22V. These should limit any r.f. spikes to approximately 22V.

### News Briefs

by Mike Abbott
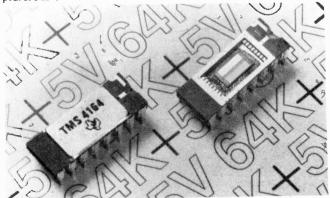
#### HEY! 64K!

Anyone who read October's Industry Notebook might puzzle over the plan being debated whereby a mass production unit would be created using government money, to produce a 64K RAMin the UK. There was a time when one would have heralded an attempt at a single supply 64K RAM with a blast of trumpets, but the drum roll has stopped. It's all over bar the shouting. The 64K RAM is here!



Sample quantities of a new dynamic RAM became available in the fourth quarter of 1978, from Texas Instruments. Volume production is scheduled for the first quarter of 1979.

Organised as  $64K \times 1$ , the TMS 4164 was expected to be the first

available 5V 64K dynamic RAM on the market. It comes in a 16-pin, 300-mil standard dual-in-line package, complying with Jedec standardized pin-out requirements and allowing upward compatibility with the 16K Dynamic RAM.

The TMS 4164 single 5V power supply design is TTL compatible, offers considerably lower power dissipation and is more immune to system noise. Five-volt operation also reduces the effective electric field across gate oxide offering higher system reliability. In addition, a compact layout and optimized design/process combination for 5V-only operation results in improved performance.


Access times range from 100 to 150 nanoseconds maximum, with minimum cycle times of 200 to 250 ns. Power dissipation is 200 mW maximum or three µW maximum per bit. Comparing the 462 mW power dissipation of the 16K RAM at 375 ns cycle time, total maximum power dissipation of the new 64K RAM is reduced by 60 per cent with improved cycle times while bit density is quadrupled. This advancement allows practically an order of magnitude power per bit improvement.

The TMS 4164 features a 256 cycle refresh with a 4 ms maximum refresh period, as a result of the lower power dissipation. This refresh period is a 100 per cent improvement over the 2-ms refresh period of current 4K and 16K RAMs. The small chip size of 34,000 square mils is a significant contributing factor to lower production costs and improved reliability.

Due to TMS 4164 refresh compatibility with the 16K RAM, the basic refresh controller timing does not require major changes. The only provision required is for an 8-bit refresh counter/multiplexer when upgrading to 64K from a 16K system. Also contributing to higher system operating efficiency is a 1.3 to 1.6 per cent refresh overhead time, compared to 2.4 per cent on the 16K RAM.

Two clocks, RAS/ROW address select and CAS column address select control the gating of the 8-bit addresses so that timing characteristics are essentially identical to the TMS 4116 16K RAM. Row address set-up time is zero nanoseconds; hold time, 15ns. Column address set-up is 5ns and RAS/CAS spacing is 15 and 50ns. This allows the system designer a full 35ns interval to change addresses and bring CAS low, without extending access time beyond 150ns.

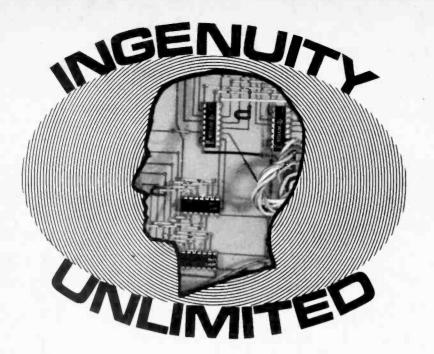More details from Texas Instruments Ltd., Memory Products Group, Manton Lane, Bedford, MK41 7PA.



A selection of readers' A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Why not submit your idea? Any idea published will be awarded nayment

idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g., with regard to abbreviations and circuit probable. with regard to abbrevia-tions and circuit symbols. Diagrams should be on separate sheets, not in-serted in the text. Each idea submitted must be accompanied by

a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.

WITH the addition of just two i.c.s a 7447 BCD to 7-segment decoder can be made to decode any four bit binary number to display zero to fifteen on a one and a half or two digit common anode 7segment display.

Gates ICla-c detect any binary number with a decimal value greater than nine with the output of IC1c going high. IC2a inverts this output so that its output goes low turning on segments b and c of the ten


From Table 1 it can be seen that for numbers with a decimal value greater than nine inputs B and D must be inverted and input C must be inverted when input B is low. These functions are carried out by IC1d and IC2a-c.

The circuit was devised to give an easily read indication of the binary address on a 7489 RAM but can be used in any application where a four bit binary number has to be monitored.


> W. McIvor, Accrington, Lancs.

Decimal	Binary	Input to 7447
	DCBA	DCBA
10	1 0 1 0	0 0 0 0
1 1	1 0 1 1	0 0 0 1
1 2	1 1 0 0	0010
1 3	1 1 0 1	0011
1 4	1 1 1 0	0 1 0 0
1 5	1 1 1 1	0 1 0 1

#### **BINARY TO 7-SEGMENT DECODER**

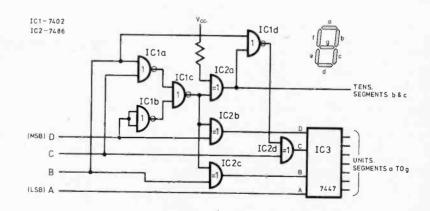

#### SUB-OCTAVE GENERATOR

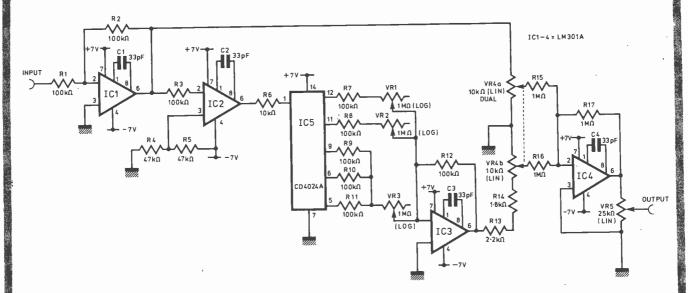

S HOWN is a circuit for a sub-octave generator, developed for use with a synthesiser. It functions as follows.

IC1 is an inverting unity gain buffer which drives the comparator IC2. The trigger level of this comparator is set for convenience at half the negative supply level (it could, of course, be set at almost any other negative value if desired). The output from this ic then feeds the clock input of a CMOS CD4024 binary divider. Only five of the seven outputs are used in this version although the others could be added quite easily.

Each output from 12 down is an octave below the other and these divided versions of the original frequency input are then fed through individual level controlling pots (VR1-3) to the buffer IC3. The ratio of "original" to "treated" sound is varied with the dual pot VR4, the original content being siphoned off from the output of IC1. The signals are then mixed into IC4 and fed via the level control VR5 to the output.

Although the supply lines quoted are  $\pm 7V$  there is no reason why  $\pm 9V$  should not suffice. Since the maximum level of input signal must exceed the comparator

threshold without going higher than about 75 per cent of the positive line, some adjustment of input signal level might then become necessary. In its present use the unit is used with a 5V signal level.

P. L. Watson, Bromham, Bedford.


SHOWN is an electronic combination lock. It uses four thyristors that latch on when the correct push-buttons are operated. TR1 and associated circuitry form a timer circuit that closes RLA1 for a pre-set period of time; about 5-7 seconds. This means that anyone who is uncertain of the combination, even if he is lucky enough to find S1, would not have enough time to find the rest. S6-S10 are connected so if depressed during or at the end of a combination, any number sequence already set up, would be destroyed. In the same way the timer destroys a sequence at the thyristors, when the time runs out, by releasing the thyristor current.

Any 9-12 volt relays will do to switch the thyristors, but to be on the safe side, the solenoid or lock must not draw more than 1-2 amps.

The combination can be changed by moving the position of the switches and it will be found that it is almost impossible to operate the solenoid unless the combination is known.

A. J. Bexley, Woking, Surrey.

#### **COMBINATION LOCK**

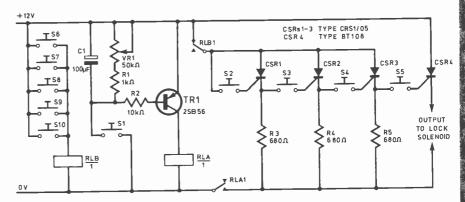

#### ONE ARM BANDIT MOD

AVING built the one-armed bandit featured in Practical Electronics May 1977, the author was very pleased with its performance except for the operation of the "Hold" switches. In the original design these were s.p.d.t. switches which had to be made to obtain a hold and cancelled after operating the handle, otherwise one was left with a hold on the next operation. In the heat of a hectic battle against five children, it was quite easy to forget to cancel the "Hold" switch which would lead to considerable argument as to whether one would have scored a win if one had remembered to cancel the hold!

For the sake of peace and quiet it was therefore decided to modify the circuit to:

- (a) replace the switches with pushbuttons (to give a more realistic effect)
- (b) to give a HOLD SELECTED indication, and
- (c) to incorporate circuitry that would automatically cancel any selected hold after each operation.

The circuit is shown in block form in Fig. 1. ICs 1, 2 and 3 are components from the original circuit. Normally the Q outputs from the latches are high thereby enabling the displays. When a hold becomes available, pin 8 of IC1 goes low. When a hold button is pressed (S2, 3 or 4), the Q output of the latch will go low disabling the display. The Q outputs of the latches are wired to the decimal points of the displays to indicate a hold has been selected.

The start handle is now operated causing the output of IC2 to go high for approximately 5 seconds. At the end of this time IC2 output goes low and the negative going transition will trigger the latch reset one shot.


This will give a negative pulse which will reset the latches ready for the next operation.

An optional extra is the "Cancel Hold" switch which allows one to cancel a selected hold if one should so desire. This. is simply an RC circuit which gives a negative-going pulse to the latch reset oneshot when the button is pressed. The diode prevents the RC circuit from incrementing the hold available counter IC1.

As in the block diagram, ICs 1, 2 and 3 are from the original circuit whilst ICs 20, 21 and 22 form the new circuitry together with R37-41, C7, C8 and D5.

Each latch is constructed from two cross coupled NAND gates, the latch reset and one-shot from two more NAND gates and three NAND gates are used as inverters for driving the decimal points in the displays.

> K. Longley, Heywood, Lancs.

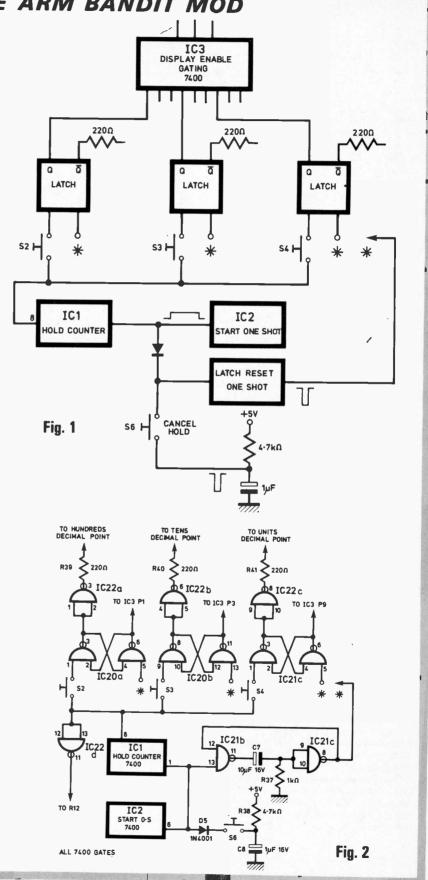

#### COINCIDENCE/ERROR DETECTOR

This circuit will detect whether two inputs occur simultaneously or one before the other. It is basically a modified half-adder. With no inputs applied, the output from ICla is at zero, disabling all output gates. The outputs from inverters IC3c and IC3d set the inputs of IClb and IClc ready to accept signals.

If A and B are set to 1 simultaneously no change will occur on the output of IC4a. As this is high and the output of IC1a is high,  $Q_2$  is enabled. IC2a, 1d, 3a, 3d and 4a make up an EXCLUSIVE OR which performs the "no-change" function.

Suppose A occurs before B. The outputs of IC1b and IC2a go high. The output of IC3c goes low, disabling IC1c. When the B input occurs, this is prevented from entering into the EXCLUSIVE OR and the state of A and "not B" only is recognised. IC2b combines this information with the output of IC1b and gives the "A before B" condition at Q<sub>1</sub>. If B occurs before A, this time IC1b is disabled, and the "B before A" condition is decoded as above.

P. Landau, Southend-on-Sea, Essex.


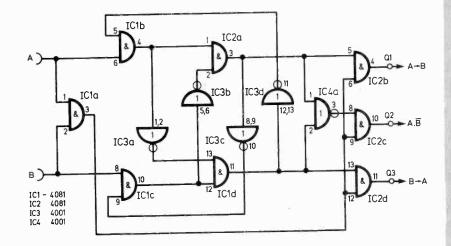


			Table	1		
t <sub>n</sub>		t <sub>n</sub>	+1	Q <sub>1</sub>	$Q_2$	Q,
Α	В	A	B	1		
0	0	0	0	0	0	0
0	1	1	1	0	0	1
1	0	1	1	1	0	0
1	1	1	1	0	1	0

No output
B operated before A
A operated before B
A & B operated simultaneously

#### CMOS BURGLAR ALARM

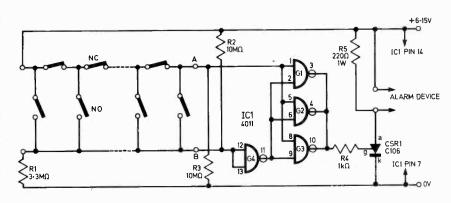

This circuit features high sensitivity with an extremely low current consumption—under 3µA at 12V. The circuit is so sensitive that a finger placed on each guard line will set the alarm off.

Normally, both of the inputs to gates G1/2/3 are high, so the output is low. If, however, either of these inputs go low (by breaking line A or shorting lines A and B together), the outputs of gates G1/2/3 will go high and trigger the thyristor. The gates G1/2/3 are in parallel to provide ample gate current for the thyristor. This should be a sensitive type such as the C106.

Any battery voltage from 6V to 15V can be used, to suit the alarm device. The sensitivity of the circuit can be increased by increasing resistors R1, R2 and R3.

R. C. Hoare, Leeds.

# Semiconductor UPDATE...

FEATURING: SN76477N SH1705 H11F1, 2, 3

R.W. Coles

#### **NOISES OFF?**

Electronic games and novelties are always popular, and thanks to advances in Large Scale Integration, they are now reaching a level of sophistication which will make them more than a passing fad. The well-known "Tele-Tennis" and its derivatives are already with us, but soon we can expect to be deluged with crafty microprocessor-based games which will pose a challenge not only to our manual dexterity, but also to our intellect! Those fortunate enough to own home computers such as the PET, can already enjoy the delights of "Lunar Lander", "Star Trek" and "Klingon Capture", but in the near future I feel sure that many lower cost, dedicated, microprocessor games will also appear.


To give these future games an air of realism, Texas Instruments have designed a complex, programmable, sound generator chip which provides an excellent complement to the video displays on which most games will be based. And of course, a device like the SN76477N sound generator is ideal for use with all of those simple electronic party games you have had buzzing around in your head for weeks, whether they involve your pet micro or not!

"What sort of sounds?" you may ask. Well, the data sheet shows examples of the SN76477N connected up to pretend it's a train, propeller 'plane, gun shot, explosion, siren, phasor gun, musical organ and a "space war" (whatever that is!). Not that that's all it can do. The nicest thing about this new chip is that it's up to you to program the noise of your dreams. A dragon snoring, a bull bellowing, a bandersnatch snatching, all may be simulated with a handful of resistors and capacitors, a little trial and error, and an SN76477N.

Within the portals of its plastic 28 pin package the new chip contains a bewildering array of programmable sound generator building blocks. A super low frequency oscillator which generates square and triangular ramp waveforms, a voltage controlled audio oscillator, a noise generator and filter, a mixer, a monostable, an output amplifier and even facilities for adjusting the attack/decay of the output waveform, are all included.

The chip will drive a speaker with the aid of a single external transistor and will run from either an existing regulated 5V supply or from an internal regulator fed from an

#### **Typical SN76477N Application**

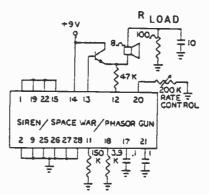

Notes. The value of resistor R<sub>load</sub> may be varied to produce the desired sound loudness. Pins that are not shown in the application schematic are not connected (open). All capacitors in microfarads.

external unregulated 7.5 to 9.0V supply. Bipolar I<sup>2</sup>L technology is employed, rather than MOS, to facilitate the combination of logic and linear circuitry on the same chip.

To produce a single type of noise, the SN76477N can be used alone, but if you want to switch from gun-shots to choochoo trains, an external switching array, either mechanical or electronic, will be necessary.

At last! The electronic "Whoopee-cushion" has arrived!

#### **BRIDGE THAT GAP**

In the past, if you needed a 3 to 5A power supply for 5V TTL systems or microprocessors, you had to wire up three or more LM309 regulator devices, a smoothing capacitor, a bridge rectifier and a transformer. The three or more LM 309's and the bridge rectifier needed to go on a heatsink of course, and the resultant assembly was both complex and bulky.

For future designs, the heat sink assembly can be very much simplified by the use of the **SH1705** regulator from Fairchild. First, the SH1705 reduces the number of TO3 packages required from a possible *five* to just *one*, because it boasts a 5A regulator current rating. Second, the new device gets rid of the big bridge rectifier package altogether, because Fairchild have crammed a diode bridge into the SH1705 as *well* as the regulator chip!

To make a 5V 5A supply, then, all you now need is a single SH1705, a capacitor, and a transformer. (You will still need a heatsink of course!)

The new device has all the usual features you have come to expect from fixed voltage regulators, such as internal over-current and over-temperature protection, excellent line and load regulation and more than 40dB of ripple rejection (even at 5A). The TO3 package used has four pins, with the case acting as the ground or OV connection. Pins 2 and 3 are a.c. input pins, pin 4 is the output from the bridge/input to the regulator, and pin 1 is the regulated 5V output.

Quite an improvement!


#### PHOTON F.E.T.

I have mentioned optical-isolators before in this column, but in the past the devices I referred to were really logic isolators, where a logic input applied to a light emitting diode was coupled within the package to a phototransistor to produce a logic level change at the output. The consequent  $G\Omega$  insulation resistance between inputs and outputs has made these devices very useful in some applications, but equivalent devices for isolating analogue signals have been rather more difficult to produce due to the need for a linear transfer function.

A new device family from General Electric, comprising the **H11F1, 2 and 3**, are ready to put this right, and may reduce the status of the analogue optical isolator to that of a "Jelly bean" part like their digital precursors. The new devices are described as Photon Coupled Bilateral Analogue FETs and they use the combination of a gallium arsenide infra-red emitting diode and a symmetrical bilateral silicon photo detector which behaves as an ideal isolated FET.

Because the output device is an FET, you can use it as a linear variable resistance which is controllable over a  $100\Omega$  to  $300\,M\Omega$  range, in isolated attenuators or a.g.c. systems for example. You can also use it as an analogue switch. A logic level applied to the input diode can be used to switch a 60V peak to peak sine wave in less than  $15\mu_{\text{S}}$ , a useful facility in solid state audio switches and instrumentation systems.

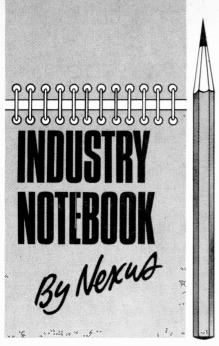The new devices come in low cost 8 pin mini-d.i.p. packages and boast a linearity of 99.9 per cent. (Well, nobody's perfect!)



#### Man v Machine

I am sometimes accused of enthusiasm for technology to the extent of being insensitive to its impact on society and the dignity of man. I recall from my earliest student days being warned that electricity could kill people. A very good servant, it was explained, but a very bad master. So, with all forms of technology. It needs to be kept in its place as a servant, a useful tool, no more, no less.

Yet who has not experienced a trembling fear that one day 'artificial intelligence' would get the better of us? I was pleased to see, therefore, that David Levy, a former chess champion of Scotland, easily defeated the most advanced machine in a match of six games, Levy scoring three wins, a draw and only one lost game, the sixth game being redundant as Levy had already won.

The match, held in Canada, was played against a CDC Cyber 176 computer programmed to examine up to three million positions and analyse up to a dozen moves ahead.

Now for the bad news. The program used. Chess 4.7, is reckoned to be stronger than 99.5 per cent of all chess players in the world. Levy thinks that a machine of even greater analytic power with superprogramming could be outright world champion by the year 2001, defeating even the best human player. Would this be a reason for putting a hatchet through the machine? Or would it just prove that the best human computer programmers, aided by the machine, are better than the best human chess players? The machine itself is still but a machine, just as an intelligently applied block and tackle enables a physically puny man to lift great weights.

#### Muddle

Computer programming again but in a different context, that of defence. I have often written of startling falls in electronic hardware costs. But while hardware costs continue to tumble, software costs of

computer-based systems continue to rise because programming is labour intensive and good programmers in short supply. In the United States the defence forces between them are currently using 200 different computer architectures which use 450 programming languages. This has come about because engineers have been optimising hardware and then specifying tailor-made computer systems to suit.

Now an attempt is being made to rationalise computer usage so that all purposes can be met from half a dozen user architectures and seven programming languages.

A similar, though less acute, problem exists in the UK forces and there is now an attempt at similar rationalisation, one of the new contenders for a "standard" computer being the established Ferranti Argus 700 now being developed in a military version.

I like the quote, attributed to a US Air Force General, "More and more our radios and radars tend to look like computers which, just coincidentally, happen to radiate and receive".

How true this is can be seen from the initial announcements on the new WG34 anti-submarine helicopters being built by Westland and scheduled for service by the mid 1980's. Prime contractor for the avionics systems is Marconi and by extensive use of distributed microprocessors, the WG34, it is said, will do the work of the 13 men in to-day's Nimrod, with a crew of only three

#### The Little Marvel

Well over a million 6500 type 8-bit MPUs were delivered in the first six months of the year according to market analysts.

But as well as MPUs there are dozens of other exciting single-chip devices coming to the market place. RCA, for example, now has a smoke detector on a single chip. GIM has an appliance timer for cookers, central heating and similar domestic functions and, amazingly, TI has compressed into a single chip a complete speech synthesizer which is used as the heart of their Speak & Spell teaching aid. I have heard Speak & Spell in action. It has an all-American drawl but I understand an English-accent version will be available for the UK.

The single-chip 64K random access memory (RAM) has arrived. First off the mark appears to be TI with trade samples available, according to latest reports, this month (November). So far as I know, no official book has been opened on runners and riders in the great 64K hurdle, but if there were it might look something like this. Top favourite to be first past the post, TI at odds-on. Second and third favourites Mostek and National Semiconductor. A dark horse who may yet be a surprise, Motorola. Among the also-rans, Inmos, lagging by about two years but likely to improve.

#### Ferranti

The National Enterprise Board has done handsomely, profiting from participation in Ferranti. In turn, Ferranti has done well with NEB support. But I seem to remember that

Ferranti, some years ago, was clobbered heavily by the government of the day for doing rather too well on a fixed-price missile contract and had to cough up millions which could have been held in reserve against a rainy day. And that part, at least, of Ferranti's misfortunes came about because of cut-backs in CEGB ordering from Ferranti's heavy electrical division, still suffering from depression.

A new venture for Ferranti is entry into the CCTV market, with accent on large security surveillance projects. It seems Ferranti will be systems engineers, bringing in CCTV equipment from outside, although some equipment may be developed inhouse eventually. This new area of diversification is within the newly formed Ferranti Instrumentation Ltd., a re-vamp of the old Instrumentation Division which is also getting involved in building containerisation equipment in the old heavy transformer plant.

#### Calculator Market

In a recent survey the world calculator market shows only a modest increase this year. But no need to get worried because total sales are forecast at nearly 24 million units as compared with 22 million in 1977. There is, however, a small drop in the cheapest hand-held models from 6.8 million to 6.7 million, indicating perhaps the beginning of market saturation for those costing less than 15 US dollars. The more expensive hand-held, including programmable, units all show an increase in sales.

#### Automation


At the recent Internepcon Show of electronic production equipment one of the star exhibits was the Dynapert automatic component insertion machine. Computer-controlled, it mounts components in bandoliers (testing them at the same time is an option) and in correct sequence at the rate of 19,000 components an hour. It then inserts them in p.c.b.s at the rate of 9,000 components an hour per operating head. Another Dynapert machine, destined for ICL, can stuff d.i.p. components into p.c.b.s at 4,000 an hour.


#### Iran Goes Solid State


Iran is getting ready for when the oil runs out. Latest move in industrialisation is a brand new semiconductor plant located at Shiraz. Some £11-12 million has been invested and the plan is to produce 30 million transistors and up to 20 million i.c.s a year. Output will be marketed through Iran's state-owned Electronic Component Industries and most of it is expected to be absorbed within Iran. If so, then Iran's electronics industry must be growing faster than most of us had imagined. The new plant will start with finished imported wafers but plans to move to diffusing its own within a few months. Among equipment suppliers are Teradyne with some £1.5 million of automatic test equipment installed, placed on Teradyne's UK base at Weybridge, Surrey.
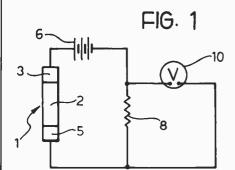
# PATENTS REVIEW...

Copies of Patents can be obtained from :
the Patent Office Sales, St. Mary Cray, Orpington, Kent
Price 95p each



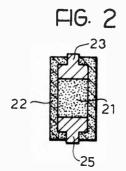

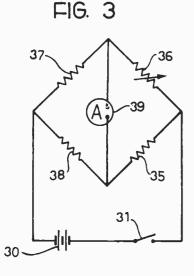

#### **FUEL/AIR RATIO**

Fiat in BP 1 496 265 refers to new electronic devices for analysing the percentage of carbon monoxide and oxygen in the exhaust gases of a motor vehicle. Such analysis is necessary to optimise engine performance and fuel-air ratios.

In a known system (Fig. 1) a sensor 1 is formed from a bar of semi-conductor metallic oxide, such as chromic oxide or titanium dioxide, which is sandwiched between two metallic electrodes 3 and 5.

The sensor is fixed in the vehicle exhaust, fed with current from battery 6 and the voltage drop across resistor 8 read by meter 10.

The conductivity of the metallic oxide can be directly related to the composition of the engine exhaust gases, particularly the relative amounts of carbon monoxide and oxygen, when raised to a temperature of between 500°C and 900°C.

The voltage drop across resistor 8 can thus provide either a direct reading of the air/fuel ratio or direct control on the engine. But Fiat have found such systems unreliable in practice due to temperature fluctuations and now use a new type of sensor reminiscent of primitive, pre-war semi-conductor devices.

Fig. 2 shows such a Fiat sensor, with a sleeve 22 of ceramic material containing metallic oxide powder 21 compressed between electrodes 23, 25.

Fig. 3 shows the improved method of connection. Two similar sensors of the new type are incorporated as arms 37, 38 in a Wheatstone Bridge with fixed resistance 35 and variable, nulling resistance 36. The sensor in arms 37, 38 are both located in the exhaust system and thus both rise to the same exhaust temperature while bathed in the same exhaust gas flow.


The ceramic wall of one sensor is porous and the wall of the other is impermeable to exhaust gas. It follows that changes in the sensors due to exhaust gas temperature fluctuations and other irrelevant factors will cancel out.

The bridge will be unbalanced by, and give a reading on, only those variations which are due to the parameter it is desired, to measure, namely the physical composition of the exhaust gases. Thus bridge ammeter A will give a correct and accurate reading representative only of airfuel ratio, independent of exhaust gas temperature.

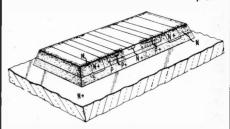
#### **BIPOLAR TRANSISTOR**

In BP 1 494 151 RCA of the U.S.A. explains how it is practically impossible to make a satisfactory bipolar transistor by conventional methods of diffusing impurities into a thin, epitaxial layer of silicon on an insulating substrate.

To produce accurate diffusion of impurities using silicon on sapphire (SOS) is impractical because silicon as deposited epitaxially on sapphire is inferior in crystalline structure to bulk silicon, and short circuits result. The patent seeks to avoid such problems. Although lengthy in content details, the basic ideas are simple.



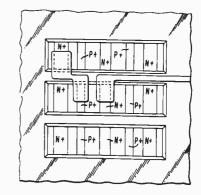The RCA bipolar transistor is formed from a silicon layer of "n" type which consists of two separate strata which are both epitaxially deposited but differently doped. Using conventional photo, resist techniques the base region is formed by a double ion implantation of "p" type impurity, such as boron.



The emitter region is formed by "n"-type ion implanting. This implantation is through an elongated opening in the previously formed silicon dioxide layer. According to RCA this ion implantation technique and multi-strata foundation provides the missing link to reliability.

# LOOK! Here's how you master electronics. ... the practical way.

This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.

#### 1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

### 2. Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

### 3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

#### 4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

Post now, without obligation, to:-


### BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

P.O. Box 156, Jersey, Channel Islands.


ADDRESS \_\_\_\_\_\_\_PEB 12/78

Block caps please



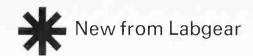

#### TV GAMES COMBINER CM 7042

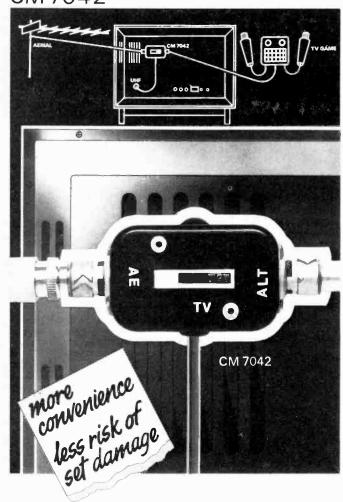

To avoid the inconvenience and risk of set damage inherent in continually plugging-in and unplugging aerials and TV games, Labgear have developed the CM 7042 TV Games Combiner.

With this simple device both the aerial and the game can be left permanently connected to the receiver and selected at will via the two-way switch.

The CM 7042 can also be used for other dual-input applications such as combining normal aerial and VCR; combining two aerials; or – in reverse – to switch a single input between two receivers.



Available from Radio & Television Retailers LABGEAR LIMITED, CAMBRIDGE, ENGLAND




#### 'ATARI' VIDEO COMPUTER

CARTRIDGE SYSTEM(ROM)

Designed and built by Atari (part of Warner Bros.) in the USA this unit is the most advanced games centre available

Just look at a few of the cartridges (up to 50 games each) available in full glorious multi-colour and very realistic on TV Sounds.

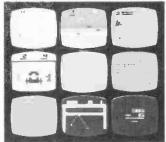
Examples of some of the many cartridges available. Combat, Air Sea Battles. Space War, Outlaw, Video Olympics, Surround, Black-jack, Breakout, Basic Math.



The Video Computer (based on Signetics 2650) comes complete with 27 Game Combat Cartridge kinks, bi-planes, bombers, jetsl, 2 joysticks, 2 rotational controllers, mains adaptor and aerial switching unit. Fully guaranteed for 12 months. £169.95\*

Additional Cartridges (over 21 due) by agrky 759 months.

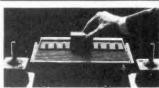due by early '79) mostly priced at £14,95★



Full Colour Brochure available on request

★ Prices include VAT, packing & delivery charges and money back guarantee Send cheque or P.O. to:



#### **VIDEOTIME PRODUCTS**

56 Queens Road, Basingstoke, Hants RG21 1REB Tel: (0256) 56417. Telex 858747 (Trade & Export Enquiries welcome)




#### AITKEN BROS.

#### 35, High Bridge, Newcastle upon Tyne Tel: 0632 26729


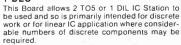
#### S/DEC

This, the most popular Board is designed solely for the use of discrete components and is particularly useful for basic educational purposes. (No. of Contacts: 70) Complete with matching ZB5D Blob Board + 9 Project Booklet. PRICE £3.75 inc. VAT.



required.
(No. of Contacts: 208) Complete with matching ZB1 IC Blob Board + 4 Project Booklet.
PRICE £4.85 inc. VAT.

#### μ-DEC 'A'

The µ-Dec 'A' is specially designed for ease of use with IC's and allows 2 DIL or 4 TO5 stations to be used but will accommodate discrete components with equal facility.

(No. of Contacts: 208) Complete with matching ZB2 IC Blob Board + 4 Project Booklet.

PRICE £4.98 inc. VAT.

#### µ-DEC 'B



The  $\mu\text{-DEC}$  'B' is for similar uses as  $\mu\text{-DEC}$  'A'. but has two 16 lead IC sockets as part of the


Board.
(No. of Contacts: 208) Complete with matching ZB2 IC Blob Board + 4 Project Booklet.
PRICE £7.75 inc. VAT.
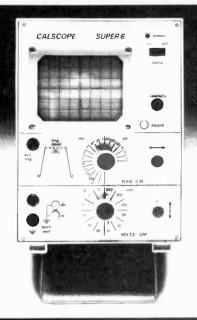
#### PANEL METERS


Dims: 60mm x 45mm.
50μ amp. 100μ amp. 500μ amp. 1MA, 5MA,
10MA, 50MA. 100MA. 500MA. 1 amp. 2 amp.
25ν dc. 30ν dc. 50ν ac. 300ν ac. "S", "VU".
50-0-50μa, 100-0-100μa, 500-0-500μa. PRICE £4.46 Inc. VAT.

POTS\* CAPACITORS, BOXES, INST. CASES, DIN PLUGS, RESISTORS, ETC., ALWAYS IN STOCK. POSTAGE AND PACKING 20p EXTRA. CATALOGUE AVAILABLE. PLEASE SEND 75p.





Super 6 £162.00 plus VAT

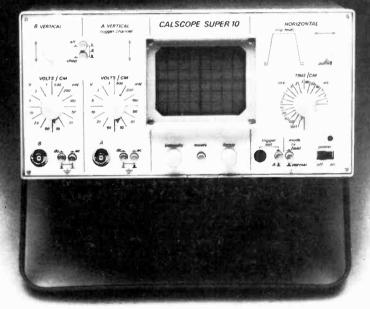

Super 10 £219.00 plus VAT

# The professional scope you've always needed.

When it comes to oscilloscopes, you'll have to go a long way to equal the reliability and performance of Calscope

Calscope set new standards in their products, as you'll discover when you compare specification and price against the competition.

The Calscope Super 10, dual trace 10 MHz has probably the highest standard anywhere for a low cost general purpose oscilloscope. A 3% accuracy is obtained by the use of stabilised power supplies which cope with mains fluctuations. The price £ 219 plus VAT.

The Super 6 is a portable 6MHz single beam model with easy to use controls

and has a time base range of 1µs to 100ms/cm with 10mV sensitivity. Price £162 plus VAT.

#### Calscopes are available from:

Audio Electronics 301 Edgware Road London W.2. Tel.: 01-724 3564 Access and Barclaycard facilities (Personal Shoppers)

Maplin Electronics Supplies Ltd. P.O. Box 3 Rayleigh, Essex Tel.: 0702 715 155 (Mail Order)

CALSCOPE



#### WIRE WRAPPING CENTRE






For .025" (0,63mm) sq. post "MODIFIED" wrap, positive indexing, anti-overwrapping device.

A For AWG 30 BW-630 B For AWG 26-28 BW-2628

C Bit for AWG 30 BT-30 BT-2628

3 IN 1 WIRE DISPENSER

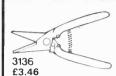New wire dispenser cuts and strips three different colours of wire. Quick and easy to use pocket size. £4.07



UNIVERSAL CUTTER Cuts everything. Leather, wire, plastic, tin-plate, cardboard. Stainless steel blades.

blades. Just one of the range of high quality pliers, cutters, tweezers and screwdrivers.

DIP/IC EXTRACTUR
TOOL £1.19
The EX-1 Extractor is
foreally suited propose enthusiast or lab engineer.
Featuring one piece spring steel construction. It will extract all LSI, MSI and SSI devices of from 8 to 24 pins.
Extractor Tool EX-1.

STRAIGHTENER

£2 79



#### WIRE-WRAPPING KIT

Contains: Hobby Wrap Tool WSU-30 M, Wire Dispenser WD-30-B, (2) 14 DIP's, (2) 16 DIP's, Hobby Board H-PCB-1, DIP/IC Insertion Tool INS-1416 and DIP/IC Extractor Tool EX-1.

Wire-Wrapping WK-4B Kit (Blue)

£19.22




- Solve probe attachment problems.
- Simplify prototype and production testing, field service work, and quality service control

IC TEST CLIPS £2.77 FOR DUAL-IN-LINE

- PACKAGES

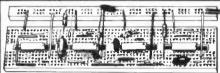  Provide full access to Integrated circuit DIP leads.
- Remove DIP's damage free.
- Available in sizes to accommodate all DIP's; TC-14 fits 14-pin DIP's etc.



#### FROM 80p TERMINAL AND DISTRIBUTION STRIPS

Bread boarding building blocks with universal matrices of solderless plug-in tiepoints.

- Facilitate quick, solderless circuit build-up and check-out on universal .1" x .1" matrix.
- Accept all components with leads up to .032" diameter.
- Require no special patch
- Includes integral non-shorting instant mounting



HOBBY WRAP TOOL

Wire-wrapping, stripping, unwrapping tool for AWG 30 on .025 (0.63mr Square Post. A£4.74 B£5.07

m)	Wrap A	WSU-30
	Modified B	WSU-30M



DIP SOCKET

Dual-in-line package, 3
level wire-wrapping, phosphor bronze contact, gold plated pins. 025

(0.63mm) sq., 100

(2.54mm) centre specing

2,54mm) centre spacing.				
14 Pin Dip Socket	14 Dip			
16 Pin Dip Socket	16 Dip			

DIBDON CARLE ACCENT	14.14	
RIBBON CABLE ASSEME		ì
With 14 Pin Dip Plug - 2" Long	DE 14-2	
With 14 Pin Dip Plug - 4" Long	DE 14-4	
With 14 Pin Dip Plug 8 Long	DE 14-8	
With 16 Pin Dip Plug 2" Long	DE 16-2	
With 16 Pin Dip Plug -4" Long	DE 16-4	
With 16 Pin Dip Plug -8" Long	DE 16-8	



DISTRIBUTORS WANTED\*\*\*

### OK Machine&ToolU.K.

48a The Avenue Southampton SO12SY

Telephone Southampton (0703) 38966/7 Telex 477222 Cablegram OKMAC

#### **DISTRIBUTORS** WANTED\*\*\*



Learn how to become a radioamateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

WAA Brachure, without obligation to: BRITISH NATIONAL RADIO PEK 12/78 & ELECTRONICS SCHOOL, P.O.Box 156, Jersey, Channel Islands. ADDRESS. (Block caps please)

#### STORAGE CABINETS



Metal cabinets with transparent plastic drawers. Ideal for components, small parts, nuts, bolts etc. Many other uses in the home, workshop, laboratory

Type 1118

Choose from the following range to suit your own needs:

Type	Height	No. of Drawers				Price
	(ins.)	Total	Small	Medium	Large	
1118	11	18	15	2	1	£8.65
1838	18	38	35	2	1	£12.95
1633	16	33	30	2	1	£10.95
2236	22	36	30	4	2	£14.75
2260	22	60	60		_	£14.95

All cabinets are finished Blue, 12" wide x  $5\frac{3}{4}$ " deep. Prices include VAT and Post. Satisfaction or money refunded. Cheque/P.O. to:

#### MILLHILL SUPPLIES (TOOLS)

35 PRESTON CROWMARSH. BENSON, OXON. OX9 6SL



PHONE 01-672 3137/672 9080
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING
CONTROL SYSTEMS TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.

#### PRICES INCLUDE VAT. P & P FREE correct at 1.10.78 TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD. (PE128) or quote Access/Barciaycard No. and post to TUAC LTD. (PE128) 119 Charimont Road, London SW17 9AB. We accept phone orders from Access/Barciaycard Holders. Phone 01-672 9080.

# 7" x 9" x 13"

#### **NEW FROM TUAC** ULTRA QUALITY HIGH POWER New D.C. Coupled Design AMPLIFIERS

Featuring Electronic Short Open & Thermal Overload Protection

Brief Spec

Input Sensitivity 0.775.v. R.M.S. (O.D.B.) at 25 K Ohms Frequency Response 20 Hz-20 KHz
Hum & Noise – 100 dB Relative full output

£45.00

£30.00


£26.25 £18.50

T.H.D. at full power 0.1% T.D. 500 300W into 2 Ohms 220W into 4 Ohms

220W into 4 0 mms
140W into 8 0 mms
Power supply P.S. 300
T.D. 150 150W into 4 0 hms
100W into 0 0 hms
Power supply P.S. 150
T.D. 150. 60 Version 60W into 8 0 hms
40W into 15 0 hms.

Power supply P.S.60

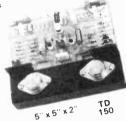Note P.S. 300 will drive 2 T.D. 150 amplifiers



All output ratings are R.M.S. continuous sine wave output

#### AMPLIFIER MODULES



SPEC. INPUT SENSITIVITY 60 mV for full output Frequency response 20 Hz-20 KHz HUM & NOISE - 70 dB

TL30 5" x 5" x 2"
\* 35 watt 10 amp output transistors

TL60 5" x 5" x 3"

60 watt R.M.S. continuous sine wave output
2 R.C.A. 110 watt 15 amp outpout transistors

TL100 5" x 5" x 3"

100 watt R.M.S. continuous sine wave output
2 R.C.A. 150 watt 15 amp output transistors

TP125 7" x 6½" x 3"
125 watt R.M.S. continuous sine wave output
4 R.C.A. 150 watt 15 amp output transistors

£21.50

£13.25

£18.50

£27.50

#### 4 CHANNEL SOUND **TO LIGHT** SEQUENCE CHASER

#### - 4LSMI

- Full wave control
- **RCA 8A Triacs**
- 1000W per channel Fully supressed and fused
- Switched master control for sound
- operation from ½W to 125W Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection

£21.50

Model 501 500W per channel as

£14.00

## 2.

#### STEREO DISCO MIXER

With touch sensitive switching and auto fade

INPUTS: Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume, treble and bass controls for each pair of sliders. Sensitivity mag. 3mV (R I A A. comp.) Flat 50mV at 1kHz. Bass controls ± 18dB at 60Hz. Treble controls ±18dB at 15kHz.

15kHz.

OUTPUT: Up to 3 volts (+ 12dB) available. Attenuated output for TUAC Power Modules. Rotary master and balance controls. Band width 15Hz – 25kHz ± dB.

P.F.L.: Output 250mV into 8 ohms. Rotary volume control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator. Miscellaneous Facilities: Two illuminated deck on/off switches. Mains illuminated on/off switches. Auto fade illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instructions.

Size: 25in long × 6in high × 3in deep. £149.00

Mono Disco Mixer with autofade £49.00

#### **3 CHANNEL** LIGHT MODULATOR SILMB

- RCA 8A Triacs
- 1000W per channe
- Each channel fully suppressed and fused
- Master control to operate from 1W to 125W

£20.75

Single Channel Version 1500 Watts

£9.75



#### FRONT PANEL FOR LIGHTING **EFFECT MODULES**

(complete with switches, neons and knobs) as illustrated



For SILMB £7.25





**FUZZ LIGHTS** Red, Green, Blue Amber. £24.50



£8.25 S1LMB Combined with 3SDM1 Size  $9'' \times 4\frac{1}{2}$ 

#### **POWER** SUPPLIES



Vacuum varnish impregnated. Transformers with supply board incorporating pre-amp supply

PS250 for supplying 2 TP125s	£30.00
PS200 for supplying to TL100s	£30.00
PS60/60 for supplying 2 TL60s	£30.00
PS125 + 45 volts for TP125	£18.50
PS100 + 43 volts for TL100	£17.00
PS60 + 38 volts for TL60	£15.50
PS30 + 25 volts for TL30	£11.75
PSU 2 for supplying disco mixer	£7.50
· · · · · · · · · · · · · · · · · · ·	

#### STOCKISTS - CALLERS ONLY

A1 Music, 88, Oxford Street, Manchester (Tel 061-236 0340) Geo Mathews, 85/87, Hurst Street, Birmingham (Tel 021-622 1941) Soccodi, 9, The Friars (Tel Canterbury 60948) Cookies Disco Centre, 126/128, West Street (Tel Crewe 4739) Garland Bros. Ltd., Deptford Broadway, London 01-692 4412 Luton Disco Centre, 88, Wellington Street, Luton (Tel Luton 411733) Session Music, 163, Mitcham Road, Tooting (Tel 01-672 3413) Mon-Sat 10am to 6pm. Closed Wed. Electra Centre, 58, Lancaster Road, Preston (Tel Preston 58488)

TRADE & EXPORT ENQUIRIES 01-672 3137



ADD SEQUENCE CHASING + **DIMMING EFFECTS FOR TUAC 3 CHANNEL LIGHT** MODULATOR



- Speed Control 3 per min. to 10 per sec.
   Full logic integrated circuitry
   Dimmer control to each channel

3SDMI

£15.25

SUPPLIERS TO H.M. GOVT. DEPTS. MANUFACTURED AND ASSEMBLED IN GT. BRITAIN FULLY TESTED AND GUARANTEED SEND NOW FOR OUR FREE 28 PAGE ILLUSTRATED CATALOGUE. SEND STAMP PLEASE



# ORDER TO SENTINEL SUPPLY, DEPT PE, 149A BROOKMILL RD., DEPTFORD SE8 Address Phone your order with Access or Barclaycard

Send SAE if brochure only required.

I enclose cheque/P0's for

£

Cheque No

Motorola, I WATT A 9-16V 8-16Ω, 10-400MV sensitivity, S.C. proof, n 90p. Data and circuits alone, 20p + SAE	AUDIO AMPLIFIER I.C. o heat sink required. Supplied with data and circuits
	NI DACKE
Don't let your environment dehydrate you.	N PACKS
Buy o Honeywell <b>Humidity Controller</b> membrane operated with $\frac{1}{8}$ shaft, ideal for greenhouses, centrally heated homes, etc. Build your own humidity alarm, 3-75A. Contacts at 250V £1.50 each. 3 for £4.00	VERNITRON FM4 10-7mHz miniature ceramic filters 50p each. 3 for £1.00. Miniature mains transformers, fully shrauded. 240V in 60-6V at 100MA out. Ex. New equipment, complete with mains lead and plug an input and short leads on output. 95p.
4 aluminium baxes 128 x 44 x 38 mm ideal for	Semiconductor Borgains
signal injectors, etc. £1.00. 100 miniature reed switches ideal for	TH3 Thermistors 10 for £1.00.
ourgior alarms, model railways, etc. £3.30.  5 × 6-pale 12 valt reed relays on board	100 new and marked transistars. Lots of types including BC148, BC154, BF274, BC212L, BF200 etc. £4.95.
£2.45.	200 new and marked transistors, including all
High quality computer panels smothered in top grade components: 5 lbs £4.75; 10 lbs £8.95.	above plus 2N3055, AC128, BFY50, BD131etc. £9.95.
Miniature edgewise panel mounting level	100 mixed diodes including zener, power and
meters 200 ua.fsd <b>90p.</b> Miniature transistorised f.m. front end with	bridge types Marked and Unmarked £2.95.
integral tuning gang 88-108MHz <b>£2.50</b> .  New U.H.F. transistor TV tuners	Bridge rectifier 100V 2.5 amp. 4 for £1.00. Brand new ITT 25kV T.V. triplers for Decca Bradford chassis £2.50, 5 for £10.00.
Rotary type with slow drive and AE. socket 22.50,	50 Germanium diodes ideal for crystal sets' etc. £1.00.
Numinium TV coax plugs. 10 for £1.00. Hardware Packs each containing 100's af items ncluding: BA nuts and bolts, Nylon, Self- opping, Posidrive, "P" clips, Cable clamps, Fuse holders, Spire nuts etc, etc. £1.00 per	Full spec. I.R. diodes, 200V 1A. 20 for £1.00. 100 for £4.50. SN76115N £1.00. BF200, 6 for £1. BC212L, 10 for £1. BC154, 12 for £1. BF274, 12 for £1. BC148, 12 for £1.
pound. Heavily insulated E.H.T. Discharging	Varicap diodes, 10 for £1.
rabe with lead and earth connector 60p each.	Companent Bargains 300 mixed resistors \( \frac{1}{4} \) & \( \frac{1}{2} \) watt \( \frac{\tau1.50}{2} \). 300
Ultrosonic transducers, transmitter and re-	madern mixed caps, most types, £3.30. 200
terver 14mm diam. 40kcs £4,25 per pair.  Mogrietic earpieces with plug and lead 25p	mixed resistors, mostly 1 & 2 wait, £1.50, 100
each, 5 for £1.00.	mixed polyester caps £2,20, 100 mixed modern
Crystal earpieces with lead 40p each. 3 for	miniature and ceramic plate caps £1.20, 100 mixed electrolytics £2.20, 300 printed circuit
0.00	resistors £1.00. 25 mixed pots and presets
0 assorted canvergence pats £1 2 quil, low profile I.C. sackets, 14 pin £1	£1.50. 100 mixed carbon film and metal film
	resistors mostly miniature lots of values £1.20
DE LUXE-FIBRE GLASS	500 for £4,90, 100 mixed high wattage
PRINTED CIRCUIT ETCHING KITS Includes 150 sq. ins. copper clad f/g board,	resistors, wirewaund, etc. £2.20. 20 assorted VDRs and Thermistars £1.20. 25 assorted
1 lb ferric chlaride, 1 dola etch resist pen,	preset pots, skeleton, etc. £1.20.
abrasive cleaner, 2 mini drill bits, etch tray and	Bargain Parcels Save Pounds
instructions – only £5.30.	Huge quantities of electronic components must
150 sq. in. fibre glass board	be cleared as space required. 1000's of
Data pen         90p           1 b ferric chlaride to mil spec         £1.25           5 bs ferric chlaride to mil spec         £5.00           nstruction sheet         20p	capacitars, resistars, transistars. Ex equipment panels etc. covered in valuable components. No time to sort. Must sell by weight 7 lbs = £4.95; 14 lbs = £7.95.
	ID CHECKE OF POSTAL ORDER WITH

#### New from Mantec

A comprehensive Home Study Course in Electronics

Suitable for Beginners and Students The Course which gives you "Right from the Start" the practical experience as well as the all important back-up theory.

Suitable preparation for C and G examinations Ensure your future in tomorrow's technology

The home study course that tells not onl<u>y how</u> but why The Course includes:- 1 The Manual, Easy to read and understand, set out in a clear and concise way, includes numerous

experiments and diagrams. 2 The Kit. All components necessary for the experiments

and projects covered. Mantec also provides a tutorial support service for students requiring further advice.

Special offer: The complete study course only £25.00 inc. V.A.T. Also available in "The Right From The Start" manual. Only £5.99 inc P&P.

Mantec the leaders in Manufacturing Technology Mantec, 7 Dellsome Larre, Welham Green, Hatfield, Herts.

To: Mantec, 7 Delisome Lane, Welham Green, Patfield, Herts.
wase send me"Right from the Start" home study course(s).
I enclose Cheque/Postal Order for £
Name;
Address:

Inc. V.A.T. and P.P.

X4 KIT £14 . 95

TACHS PULSE SLAVE UNIT £3.35

lease state polarity pos or neg earth ccess or Barclaycard No.

## Complete the Circuit at Breadboard'78

Lektrokit have made sure that, no matter how often you go'round the exhibits at Breadboard '78, you'll keep coming back to Stands D8 and D9. "Completing the circuit" every time.

Because Lektrokit—as only Lektrokit could—have combined their vast array of components with those of AP Products Inc to bring you the most comprehensive range of breadboarding and testing devices on earth.

Nowhere else at Breadboard '78 will you see everything you're likely to need all in one place, all in one go, and at the right price.

If you can't get to Breadboard '78 contact us for more details and the name of your nearest Lektrokit dealer and take a look at how much you can get for how little.

Lektrokit Breadboards FROM £3.25, inc p & p and VAT

Hole for hole, top value! Lektrokit Breadboards are modular, so they can be linked together to form any size. With a pitch of 0.1", even the smallest breadboard—217L—can accept 8, 14, 16 or 18 pin Dil devices. You just take a


riporierit, cri	COSC a HOIC	, and paoniti
Model No.	Contacts	Price, each
217L	170	£3.25
234L	340	£5.75
248L	480	€6.65
264R	512	£6.65
264L	640	£8.32

(All prices include packing, postage and VAT)



Eleven models, from TC-8 to TC-40 to fit all DIP sizes. Prices from £3.08 for the TC-14, £3.25 for the TC-16, etc.

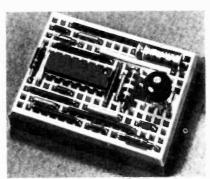
Test clip grips IC's without slipping or shorting between pins—makes testing IC's on boards easier, aids removing and inserting DIP's without damage. Each IC pin can be brought up to a convenient contact post for test leads or probe connections.



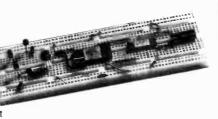
## Lektrokit Super Strip SS2

ONLY £11.05 inc p & p and VAT Super Strip accepts ALL DIP's—as many as nine 14-pin at a time and/or TO-5's and discrete components. With interconnections of any solid wire up to 20 AWG.

Super Strip has 840 contact points, combining a power/signal distribution system with a matrix of 640 contacts in groups of 5. Distribution system has eight bus-bars, each with 25 contact points



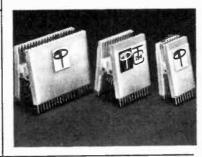

#### Lektrokit All-Circuit Evaluator FROM £12.53 inc p & p and VAT


ACE" in the hole for home constructors and project builders who do things faster and easier! No laying out circuit diagrams, printed circuit boards, soldering everything together, trouble-shooting, making mods, then chucking it and starting the whole time-consuming business all over again!

With ACE, you just plug in components and make connections with ordinary 22-gauge solid wire. No soldering. You can build any working project complete, as fast as you could lay out a circuit diagram before.

Seven ACE models altogether—with from 728 to 3,648 contacts. IC capacity (all 14-pin DIP's) from 9 to 36. Buses from 2 to 36. Posts from 2 to 4. Prices from £12.53 including packing and postage and VAT


Lektrokit's policy is the right product, whatever the project, at the right price. And it's backed by a nationwide network of retailers.

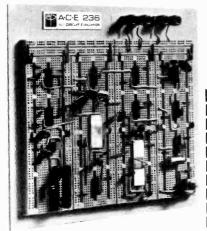Send for the name of the dealer nearest you—plus a FREE full-colour catalogue. And, if you can, see and try out the great Lektrokit range at Breadboard '78—from Nov. 21 to Nov. 25 at Seymour Hall, Seymour Place, London.



I enclose P.O./cheque for £  (Allow 28 days for delivery, All prices above include packing, postage and VAT).
To Lektrokit Limited, London Road, Reading, Berks, RG6 1AZ. Tel. Reading (0734) 669116/7 Please send me the name of my nearest Lektrokit dealer—plus FREE catalogue. Please supply the following (list items required)
Write to: Lektrokit Ltd, London Road, Berks, RG6 1AZ or send coupon.
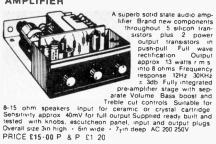
#### SUPERSOUND 13 HI-FI MONO **AMPLIFIER**



PRICE £15.00 P & P £1 20

#### HARVERSONIC MODEL P.A. **TWO ZERO**



Special introductory price £28.00 + £2 50 carriage and packing

Mullard LP1159 RF-IF module 470 kHz £2:25 + P & P 20p. Full specification and connection details supplied. Pe VHF FM Tuner Head covering 88-108 MHz 10-7 MHz I.F. output. 7-8V + earth. Supplied pre-aligned, with full circuit diagram with precision-geared F.M. gang and 323PF + 323PF A.M. Tuning gang only £3:15 + P. & P. 35p.

STILL AVAILABLE

HA34 3 Valve Audio Amp. 4½w o/p. Reacy built and tested £8.50
£1.40 P & OP.
Also HSL "Four" Amp. Similar to above but in kit form. £8.00
£1.40 P & P.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday Closed Wednesday.

Prices and specifications correct at time of press. Subject to alteration without notice

#### MAINS OPERATED SOLID STATE **AM/FM STEREO TUNER**



200 240V Mains operated Solid State F.M. A.M. Stereo Tuner Covering M.W. A.M. 540-1605KHz V.H.F. F.M.

540-1605KHz VHF FM 88-108MHz Built-in Ferrite rod aerial for MW Full AFC and AGC on AM and FM Stereo Beacon Lamp Indicator Built in Prewith variable

control Max o p Voltage 600mV R M S into 20K Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 in wide 4 in high. 9 in deep approx

Limited number only at £28 00 + £1 50 P & P

MAINS TRANSFORMER. PRI. 0·110 and 240. SEC. 28V at 1.8 amps. Also tapped at 12V  $\cdot$ 3 amp. Overall size  $2\frac{1}{4}$ "h x  $3\frac{1}{4}$ "w x  $2\frac{3}{4}$ "d. £2·50 + P&P £1·00.

#### 10/14 WATT HI-FI AMPLIFIER KIT

10/14 WAIT HI-FI AMPLIFIER KII
A stylishly finished monaval amplifier with an output of 14 watts
from 2 EL84s in push-pull. Super reproduction of both music
and speech, with negligible hum. Separate inputs for mike and
gram allow records and announcements to follow each other.
5-15Ω speaker and 2 independent volume controls, and separate
bass and treble controls are provided giving good lift and cut.
Valve line-up. 2 EL84s, ECC83\_EF86 and E260 rectifier. Simple
instruction booklet 25p + S.A.E. (Free with parts). All parts sold
separately. ONLY £14-50 P. & P. £1-40. Also available ready
built and tested £19-00 P. & P. £1-40.

## "POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11% - 14 Hin x 14 Hin deep. Weight 19oz. Power handling 20W R.M.S. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Send S.A.E. for full details. Only £8-40 each + P. & P. (one 90p, two £1-10). Now available in either 8in round version or 4½ × 8in rectangular, 10 watts R.M.S. 60Hz-20KHz £5-25 + P. & P. (one 65p, two 75p.).

STEREO MAGNETIC PRE-AMP Sens. 3mV in for 100mV out. 15 to 35V neg. earth. Equ.  $\pm 1$ dB from 20Hz to 20KHz. Input impedance 47K. Size 1in  $\times$  2in  $\times$  5in H. £2-60 + 20p. P & P.

2in PLASTIC CONE HF TWEETER 4 ohm. £3.50 per matched pair + 50p P. & P.

HIGH POWER HI-FI 8 ohm Dome Tweeter. 1in voice coil. Magnet size 3in dia. Suitable for use in up to 50 watt systems. £4.50 each 60p P. & P.

#### HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in, even lower noise level with improved ensitivity integral pre-amp with Bass. Trebbe and two Volume controls Suitable for use with Ceramic or Crystal cartridges Very simple to modify to suit magnetic cartridge—instructions included Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality-ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extructor to build an april of the product of Brief specification. Prower output 14 waits and size of the product of Brief specification. Prower output 14 waits and are the product of Brief specification. Prower output 14 waits and are the product of Brief specification. Prower output 14 waits and 12-30.00Hz. Sensitivity, better than 80mV erox response. 308 12-30.00Hz. Sensitivity, better than 80mV erox product 17 rebb cut approx to -18dB. Negative feedback 18dB over main amp. Power requirements 35V at 14.

Overall size 12 in wide x 8 in deep x 2 gin high.

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S A E

AMPLIFIER KIT (Magnetic input components 33p extra)

£13-50 P & P 80p

POWER PACK KIT

CABINET

£5.50 P & P 95p £5.50 P & P 95p

SPECIAL OFFER—only £23-75 if all 3 items ordered at one time plus £1-25 P. & P.

Full after sales service Also available ready built and tested £31-25 P & P £1 50

#### **HARVERSONIC STEREO 44**

HARVERSUNIC STEREO 44
A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control volume controls 2 pin din speaker sockets and 5 pin din tape rec play socket are mounted on the printed circuit panel. Size approx 9<sub>1</sub> in - 2½ in - 1 in max depth supplied brand new and tested with knobs brushed anodised alumnium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only 51-00 - 50p P & P. Mains transformer with an output of 17V a.c. at 500m A.can be supplied at £1-50 - 40p P & P. it required. Full connection details supplied.

STEREO DECODER

SIZE 2" . 3" . 3" ready built. Pre-aligned and tested for 9-16V neg, earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6 00 plus 20p P. & P. Stereo beacon light if required 40p extra.


#### HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 MERTON HIGH ST., MERTON, LONDON, S.W.19 Tel: 01-540 3985

A few minutes from South Wimbledon Tube Station

(Please write clearly)

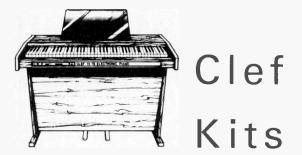PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY P. & P. ON OVERSEAS ORDERS CHARGED EXTRA



Only Suppliers of Kits approved for designs by A.J. Boothman.

## **JOANNA 88 JOANNA 72**

The author of the P. E. JOANNA Touch Sensitive Electronic Piano has extended the design to cover 88 or 72 note instruments.

The considerable increase in flexibility of Six or 71 Octave Keyboards is coupled with the unique touch sensitive configuration of the P.E. design, simplified construction, and a number of circuit design improvements.

#### P.E. STRING **ENSEMBLE**

The very versatile String Machine, with rich Chorus, as published in Practical Electronics for Group or home entertainment.

The P.E. Design now makes this newly popular Keyboard Instrument available for home construction. (Australian readers contact John Carr & Co. Sydney.)

Send S.A.E. for details to - Clef Products 16 Mayfield Road, Bramhall, Cheshire SK71JU

## Codespeed THE LOW COST ANSWER IN MAIL ORDER ELECTRONICS

**Full Spec. Devices** 

PACK C1 10 x 12 pin Hybrid circuits each containing 16 resistors/capacitors, Useful values. Ideal for semiconductor circuits and pcb miniaturisation. With data. 10 hybrid circuits for 50 PACK DM1 5 " 14 pin dual in line chips, each containing 23 quality matrixed switching didden With data 500.

values. Ideal for semiconductor circuits and pco miniaturisation. While services from the control of the part of t

**Untested Devices** 

PACK E1 (80% Guaranteed good) 5 x MAN3, 7 segment 0.127" common cathode LED displays Excellent value £1,00 PACK MU1 (Untested – so no guarantees) Another bargain! 2 x Upper half of a calculator case with built in keyboards. Most are ex-equipment, but believed to be o.k. A srip at only 60p the pair PACK R2 2 miniature plug in relays. One DC relay (15.5k coil) and one AC relay (3.5k coil). Both 4 pole change-over contacts. 2 relays for 25p

Your satisfaction is guaranteed or raturn the complete pack for replacement or a refund. For free catalogue send S.A.E.

MAIL ORDER ONLY – NO CALLERS PLEASE.
Postage and packing please add 25p (Overseas orders add 60p)

CODESPEED, P.O. Box 23, 34 Seafield Road,

Copnor, Portsmouth, Hants, PO3 5BJ

Come and get a great deal

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat Tel. orders on credit cards £10 min. Trade and export enquiries welcome

A. Marshall (London) Ltd. Dept. PE. Head Office mail order: Kingsgate House, Kingsgate Place, NW6 4TA. Tel: 01-624 0805. Retail Sales London: 40-42 Cricklewood Bdwy, NW2 3ET. Tel: 01-452 0161/2. Telex: 21492. London: 325 Edgware Rd. W2. Tel: 01-723 4242. Glasgow: 85 West Regent St, G2 2QD. Tel: 041-332 4133. Bristol: 1 Straits Pde, Fishponds Rd, BS16 2LX. Tel: 0272 654201.

Regent	ot, GZ ZUD.	Tel: 04	1-33	12 41.	33. E	STISTOL:	13	traits r	ue, i	ishpoi	ius r	iu, us i	0 21												0.50
2N696 0.39	2N2219 0.38	2N3397 (	0.19	2N4062	0.20	2N5247	N 44	40410	0.82					BC214B	0.17			BD244A			0.37.	BFXB9	1.37	MJE520	0.30
	2N2219A 0.39	2N3438			1.35		0.44	40411	3.10					BC214C				BD244C		BF183	0.44	BFY50	0.27	MJE521	0.70
	2N2220 0.39	2N3440			2.65		0.44	40594	0.87	BC147	0.13	BC1828	0.13	BC214L	0.18	BC557	0.14	BD245A	0.69	BF184	0.41	BFY51	0.27	MJE2955	1.65
		2N3440 (			0.27	2N5295		40595	0.98		0.13	BC182L	0.15	BC214LB	0.18	BC558	0.13	BD245C	0.85	BF185	0.37	BFY52	0.27	MPF3055	
2N699 0.58						2N5296		40673	0.80	BC148	0.13	BC182LA		BC214LC	N 18	BC559	0.15	RD246A	0.72	BF194	0.16	BFY90	1.35	MPF1 02	0.33
2N706 0.30		2N3442 1						40669	1.30	BC148B	0.13	BC182LB		BC237B		BCY70	0.21	BD246C	0.93	BF195	0.16	BR101	0.55	MPF103	0.44
2N706A 0.30	2N2222 0.25	2N3638 (		2N4123		2N5298			0.48	BC148C	0.13	BC 183	0.12		0.13	BCY71	0.26	BD433	0.44	BF196	0.16	BRY39	0.55	MPF104	0.44
2 N 7 0 8 0.30	2N2222A 0.25	2N3638A I		2N4124		2N5447						BC183A			0.13	BCY72	0.18	BD434	0.46	BF197	0.18	BSX19	0.35	MPS105	0.44
2N718 0.20		2N3702 (				2N5448			0.4B	BC149	0.15				0.13	BD115	0.88	BD435	0.46	BF198	0.19	BSX20	0.35	MPSA05	
2N718A 0.54		2N3703 (						AC128	0.48	BC149C		BC183B			0.16	BD131	0.55	BD435	0.46	BF199	0.13	BSX21	0.35	MPSA06	
2N720A 0.85	2N2646 0.80	2N3704 (						AC151	0.43	BC157A		BC183C		BC239B		BD132	0.75				0.13	BU104	1.80	MPSA12	
2N722 0.45	2N2647 1.55	2N3705 [	0.14		0.22			AC152	0.54			BC183L			0.17			BD437	0.55	BF224J		BU105	1.55	MPSA14	
2N727 0.50	2N2903 1.60	2N3706 (	0.14	2N4287	0.22	2N5459		AC153	0.59			BC183LA			0.18	BD135	0.40	BD438	0.55	BF225J	0.27			MPSA55	
2N914 0.3B	2N2904 0.31	2N3707 (	0.14	2N4288	0.22	2N546D	0.65	AC153K	0.59	BC159A	0.17	BC183LB		BC258B	0.19	BD136	0.40	BD529	0.49	BF244A	0.38	BU126	1.08		
	2N2904A 0.31	2N3708 (	0.12	2N42B9	0.22	2N5484	0.37	AC176K	0.70	BC159B	0.17	BC183LC		BC259B	0.19	BD137	0.41	BD530	0.55		0.33	BU204	2.20		
2N917 0.38		2N3709 (		2N4347	2.20	2N5485	0.40	AC176	0.54	BC160	0.38	BC184	0.12	BC300	0.43	BD138	0.41	BD535	0.70	BF245A	0.44	BU205	2.40		2.45
2N918 0.45		2N3771		2N4348		2N5486			0.59	BC161	0.38	BC184B	0.13	BC301	0.43	BD139	0.43	BD536	0.70	BF245B	0.44	BU2D6	2.70		2.15
2N929 0.37		2N3772		2N4918		2N5490			0.65	BC167	0.13	BC184C	0.13	BC302	0.37	BD140	0.43	BD537	0.74	BF257	0.35	BU208	2.70		0.49
2N929A 0.37		2N3773				2N5492		AC188	0.54		0.13	BC184L	0.15	BC3D3	0.54	BD181	1.90	B0538	0.77	BF258	0.35	ME0401	0.22	TIP29C	0.65
	2N2907 0.25	2N3819		2N4920		2N5494			0.65	BC168A		BC184LB	0.15	BC307	0.16	BD182	2.20	8D539	0.60	8F259	0.35	ME 0402	0.22		0.54
		2N3820 I		2N4921		2N5496			1.00		0.13			BC307A	0.16	BD183	2.35	80540	0.60	BF336	0.42	ME0404	0.17	TIP30C	0.70
2N930A 0.95								AD162	1.00		0.13	BC212	0.15	BC307B	0.16	BD187	0.95	BDX 14	1.32	BF337	0.49	ME0412	0.22	TIP31A	0.54
2N1711 .0.30									0.60		0.13		0.15	BC308	0.16	BD235	0.46	BDX1B	1.90	BF338	0.52	ME0414	0.22	TIP31C	0.72
2N1889 0.30		2N3900 (			0.75	2N6107				BC169C			0.15	BC308B	0.16	80236	0.44	BDY20	1.10	BFR39	0.30		0.16	TIP32A	0.59
	2N2925 0.19			2N4924	1.15	2N6108		AF109	0.52			BC2126	0.15	BC309A	0.16	B0237	0.44	BDY55	1.90	BFR40	0.29		0.16	TIP32C	0.82
2N1893 0.30					0.30	2N61D9			0.16	BC177	0.22			BC3098	0.16	B0238	0.44	BDY56	2.10	BFR41	0.30	ME4003	0.16		0.76
	2N3053 0.25			2N5087	0.30			BC107A	0.16	BC177A		BC212LA					0.44	BF115	0.39	BFR79	0.30	ME4101	0.11		0.97
2N2192 0.58	2N3O54 0.72			2N5D88	0.30				0.16	BC177B	0.25	BC212LB		8C309C	0.16						0.30	ME4102			0.86
2N2193 0.50	2N3055 0.75	2N3906	0.18	2N5089	0.30	2N6122			0.16	BC178	0.22	BC213	0.15	BC327	0.22	BD239C		BF160	0.33	BFR80		ME4102		TIP42C	1.08
2N2193A 0.52	2N3390 0.50	2N4031	0.55	2N5190	0.65	2N6123			0.16		0.25	BC213A	0.15	BC328	0.20	BD240A		BF161	0.65	BFR81	0.30	ME4103			0.70
2N2194 0.42	2N3391 0.40	2N4032	0.65	2N5191	0.75	2N6124			0.16	BC178B	0.35	BC213B	0.15	BC337	0.20		0.59	BF167	0.37	BFX29	0.34				0.59
2N2194A 0.45	2N3391A 0.45	2N4036	0.72	2N5192	0.80	2N6125	0.47	BC108C	0.17	BC179	0.25	BC213C	0.15	BC338	0.23	BD241A		BF173	0.37	BFX30	0.34	ME6101			
	2N3392 0.17		0.60	2N5193	0.75	40361	0.55	BC109	0.16	BC179A	0.25	BC213L	0.17	BC547	0.13	BD241C		BF177	0.27	BFX84	0.30	ME6102		TIS34	1.05
	2N3393 0.17			2N5194	0.80	40362	0.55	BC109B	0.17	BC179B	0.25	BC213LA	0.17	BC547A	0.13		0.55	BF178	0.27	8FX85	0.38	MJ2955			0.50
2N2217 0.55					0.97	40363	1.45	BC109C	0.18	BC179C	0.26	BC213LB	0.17	BC547B	0.13	BD242C		BF179	0.33	BFX86	0.30	MJE340		TIS43	0.47
2N2217 0.35				2N5245		40408		BC140	0.30	BC182	0.12	BC213LC	0.17	BC548	0.13	BD243A		BF180	0.37	8FX87	0.35	MJE370	0.62	TIS90	0.22
											0.12	BC214	0.17	BC549	0.14	BD243C	0.87	BF181	0.37	BFX88	0.30	MJE371	0.86	TIS91	0.27
2N2218A 0.38					0.38	40409		BC141	0.32	BC182A	0.12	BC214	0.17	BC549	0.14	BD243C	0.87	BF181	0.37	BFX88	0.30	MJE371	0.86	11591	0.27

#### LINEAR CIRCUITS

		ĻΙ	NEAL	H L	IKCL	ווע	5	
	CA3018	0.75	LM379S	4.25	LM7815K	1.75	TAD100	2.00
	CA3018A	1.10	LM380N8	0.96	LM7824K	1.75	TBA120	0.80
	CA3020	2.20	LM380N14		LM78L05C		TBA500	2.24
	CA3020A	2.50	Lindouiti	1.08		0.30	TBA5000	2.34
	CA3028A	0.90	LM381AN	2.70	LM78L12C	?	TBA51D	2.35
	CA3028B	1.25	LM381N	1.69		0.30	TBA5100	2.48
	CA3030	1.50	LM382N	1.32	LM78L15C	?	T8A520	2.60
	CA3030A	2.20	LM384N	1.55		0.30	TBA5200	2.70
	CA3038	2.90	LM386N	0.88	MM5314	4.60	TBA530	2.35
	CA3038A	4.10	LM387N	1,10	MM5316	4.60	TBA5300	2.45
	CA3045	1.55	LM388N	1.00	NE555	0.33	TBA540	2.60
	CA3046	0.77	LM389N	1.00	NE556	0.85	TBA5400	2.70
	CA3048	2.45	LM702C	0.81	NE558N	1.98	TBA550	3.60
	CA3052	1.78	LM709	0.70	NE560	4.50	TBA5500	3.80
	CA3080	0.85	LM7098	0.50	NE561	4.50	TBA56000	3.00
	CA3080A	2.10	LM70914	0.49	NE562	4.50	TBA570	2.10
	CA3086	0.50	LM710	0.67	NE565	1.39	TBA5700	2.20
	CA3088B	1.87	LM71014	0.64	NE566	1.75	TBA7000	2.20
	CA3089B	2.90	LM711CN	0.72	NE567	1.90	TBA720A0	2.06
	CA30900	4 40	LM723C	0.75	NE571N	4.95	TBA750	2.36
	CA3130	1.06	LM723C14		SAS560	2.70	TBA7500	2.45
	CA3140	1.04	LM741C	0.70	SAS570	2.70	TBA800	1.30
	LM301	0.30	LM741C8	0.30	SAJ110	2.10	TBA810S	1.30
	LM307N	0.50	LM741C14		S041P	1.35	TBA820	0.80
1	LM308N	0.95	LM747CN	0.99	S042P	1.35	TBA920	2.99
	LM309KC	1.95	LM7488	0.50	SN76001N	1 20	TCA160C	2.55
	LM317K LM318N	2.45	LM74814	0.90	SN76003N	1.30	TCA1608 TCA270	2.99
	LM318N	2.45	LM1303N LM1304N	1.15	2M / DUU 3 M	2.38	TCA730	4.50
	LM320T12		LM1304N	1.52	SN76013N	2.30	TCA740	4.50
	LM320T15		LM1303N	1.22	3117001311	1.50	TCA750	3.00
	LM320T24		LM1310N	2.10	SN76023N	1.00	TCA760	2.00
	LM320P5	1.15	LM1351N	1.30	5117002311	1.50	TCA105	1.49
	LM320P12		LM1458N	0.45	SN76033N		TCA44D	1.65
	LM320P15	1.15	LM1496N	0.97		2.35	T0A1022	7.50
	LM320P24		LM1808N	2.10	TAA263	1.35	T0A1024	1.24
	LM323K	6.95	LM1812N	6.20	TAA300	3.70	TDA1034	4.75
	LM339N	0.60	LM1820N	1.16	TAA320A	1.15	TDA2020A	D
	LM340T5	88.0	LM1828N	1.90	TAA350A	3.00		4.50
	LM340T15		LM1830N	1,90	TAA521	1.10	UAA170	2.15
	LM340T24		LM1841N	1.90	TAA522	2.10	UAA 180	2.15
	LM341P5	0.80	LM1845N	1.50	TAA550	0.48	TL080CP	1.25
	LM341P12		LM1848N	1.98	TAA560	2.10	TL081CP	0.90
	LM341P15		LM1859N	1.90	TAA570	2.20	TL082CP	1.10
	LM341P24		LM1889N	4.90	TAA370A	5.45	TL083CN	1.40
	LM348N	0.95	LM3301N	0.60	TAA630	2.40 3.90	TL084CN	1.45
	LM358N	0.60	LM3302N	0.55	TAA960	4.20	LF355N	0.80
	LM360N	3.00	LM3401N	0.55	TAA970	2.50	LF356N LF357N	0.80
	LM370N LM371H	3.30 2.35	LM3900N	0.68	TAA611B TAA621	2.50	LF13201N	0.80 3.00
	LM371H LM350K	6.45	LM3905N	1,15	TAA661A	1.65	LF13201N	3.00
	LM373N	3.35	LM3909N	0.7B 1.10	TAA661B	1.45	LF13741H	0.80
	LM374N	3.36	LM3911N LM7805K	1.75	TAA700	4.50	LF13741N	0.60
	LM377N	1.80	LM7812K	1.75	TAA930A	1.45	C13741N	0.00
	LM378N	2.40	LM324	0.75	TAA930B	1.45		
	CHIO/ DIE	2.70	LIVIJZ4	0.73	177300			

## EXPAND AND KIM

NOT A KIT BUT A READY TO USE MICROCOMPUTER

#### **AMERICA'S FASTEST SELLING MOST POPULAR 6502** BASED SYSTEM - EASILY EXPANDED INTO A PERSONAL HOME COMPUTER

The basic KIM 2 includes Hex keyboard and display, audio cassette interface. VDU interface. Superb documentation. 2K monitor software in ROM. Powerful instruction set. The beauty of this system is the ease of instruction set. The beauty of this system is the ease of extension and versatility with all the possible future requirements catered for. Up and running in minutes. Any future benefits from Commodores PET computer will be software compatible with their KIM system and in fact your KIM system has the design flexibility to suit any requirements.

KIM IS EXPANDABLE—Expand as you learn up to 65K

KIM 1 = Basic board with above features assembled

KIM 3 = 8K static RAM card plugs into motherboard

KIM 3 = 8K static RAM card plugs into motherboard

KIM 4 = Motherboard (takes 6 x KIM 3) + power supply

KIM 6 = Prototype board for user designation

The Commodore PET and KIM are both based on the 6502 micro

VDU INTERFACE = VDU card — takes control

Fully assembled TTY Card - ASC II keyboard in - converts TV set to cheap computer terminal via aerial socket. Also standard RS232 connector for micro computer or modem = 16 lines x 64 characters

SEND SAE NOW FOR FULL DETAILS.

4000 400 4010 050	CMOS	4068 0.27	4086 0.89
4000 <b>0.22</b> 4016 0.52			
4001B 0.22 4017B 1.05	403D 0.84 4050B 0.85	4069B 0.24	4089B 2.10
4002 0.22 40188 1.05	4031R 2.25 4051B 0.85	4070B 0.85	4093B 1.00
4006 1.25 40198 0.52	4035B 1.30 4052B 0.86	40718 0.24	4094 2.30
4007 0.22 4020B 1.15	4037 1.20 4053B 0.98	4072 0.27	4095 1.30
4008B 0.99 4021 1.05	4041B 0.85 4054 1.48	4073B 0.24	4096 1.30
4009 0.58 40228 1.00	4042B 0.86 4055 1.65	4075B 0.24	4097 4.65
4010 0.58 4023B 0.22	4043 1.05 4056 1.65	4076B 0.99	4098 1.00
4011B 0.22 4024B 0.76	4044 1.00 4059 6.00	4077 0.70	45108 1.20
4012 0.22 4025B 0.22	4045 1.76 4060B 1.15	4078 0.27	4511 1.75
40138 0.52 4027B 0.55	4046B 1.50 4063 1.35	4081B 0.24	4516 2.10
4014 1.00 40288 0.92	4047B 0.96 4066B 0.75	4082 0.27	4518B 1.20
4015 1.05 4029B 1.10	4049 0.96 4067 4.85	4085 0.89	40100 1.20

#### TTI

			П	L			
74LS00N	0.26	74LS162N	1.43	7400N	0.17	7490AN	0.45
74LS01N	0.26		1.43	7401N	0.17	7491AN	0.85
74LS02N	0.26	74LS168N	2.43	7402N	0.17	7492N	0.45
74LS03N	0.26	74LS169N	2.43	7403N	0.17	7493N	0.45
74LS04N	0.29		1.33	7404N	0.17	7494N	0.90
74LS10N	0.26	74LS175N	1.26	7405N	0.22	7495N	0.76
74LS12N	0.26	74LS181N	3.95	7406N	0.56	7496N	0.70
74LS13N	0.58	74LS189N	3.74	7407N	0.55	7497N	1.95
74LS14N	1.43	74LS190N	1.00	7408N	0.22	74100N	1.40
74L\$20N	0.26	74LS191N	1.00	7409N	0.22	74107N	0.35
74LS26N	0.39	74LS192N	1.98	7410N	0.20	74118N	0.95
74LS27N	0.50	74LS193N	1.98	7411N	0.26	74119N	1.40
74LS28N	0.42	74LS196N	1.28	7412N	0.20	74121N	0.28
74LS30N	0.26	74C00N	0.24	7413N	0.36	74122N	0.55
74LS37N	0.32	74C02N	0.24	7414N	0.80	74123N 74125N	0.55
74LS38N	0.32	74C04N	0.24	7416N	0.36	74125N 74141N	0.45
74LS40N	0.29	74C08N	0.24	7417N	0.36	74141N	1.35
74LS42N	1.07	74C10N	0.24	7420N 7423N	0.22	74148N 74145N	0.86
74LS47N	1.09	74C14N			0.32	74145N 74150N	1.20
74LS48N	1.09	74C20N 74C30N	0.24	7425N 7427N	0.32	74150N	0.76
74LS49N	1.09	74C32N	0.24	7427N	0.22	74153N	0.76
74LS51N	0.26	74C42N	0.92	7430N 7432N	0.30	74154N	1.20
74LS54N 74LS73N	0.42	74C48N	1.38	7432N 7437N	0.35	74155N	0.70
74LS75N	0.42	74C73N	0.54	7437N	0.33	74157N	0.78
74LS78N	0.42	74C74N	0.56	7440N	0.20	74160AN	1.10
74LS83AN		74C76N	0.54	7441AN	0.84	74161AN	1.10
74LS85N	1.10	74C83N	1.30	7442N	0.76	74162AN	1.10
74LS90N	1.10	74C85N	1.30	7445N	1.40	74163AN	1.10
74LS91N	1.20	74C86N	0.64	7446AN	0.90	74164N	1.36
74LS92N	0.86	74C89N	4.39	7447AN	0.80	74165N	1.36
74LS93N	1.10	74C90N	0.85	7448N	0.80	74167N	2.50
74LS95AN	1.10	74C93N	0.85	7450N	0.22	74174N	1.60
74LS96N	1.35	74C95N	1.04	7451N	0.22	74175N	1 00
74LS107N		74C1D7N	1.22	7453N	0.22	74176N	0.90
74LS109N		74C150N	4.14	7454N	0.22	74177N	0.90
74LS122N		74C151N	2.47	7460N	0.22	74180N	1.00
74LS123N		74C154N	3.68	7470N	0.46	74181N	2.00
74LS124N		74C157N	2.21	7472N	0.30	74182N	0.80 1.50
74LS125N		74C160N	1.11	7473N	0.44	74184N	1.50
74LS126N		74C161N	1.11	7474N 7475N	0.32	74185AN 74188AN	3.25
74LS136N		74C162N	1.11	7475N 7476N	0.45	74189N	2.60
74LS145N		74C163N	1.04	7470N 7480N	0.60	74199N	1.40
74LS151N 74LS153N		74C164N 74C165N	1.04	748UN 7481N	1.00	74191N	1.20
74LS153N		74C173N	0.90	7482N	0.90	74192N	1.20
74LS154N		74C174N	0.90	7483N	1.05	74193N	1.20
74LS156N		74C175N	0.90	7484N	1.20	74196N	1.20
74LS158N		74C192N	1.11	7485N	1,36	74197N	1.00
74LS160N		74C193N	1.11	7486N	0.36	74198N	2.00
74LS161N		74C195N	1.04	7489N	2.45	74199N	2.00

#### SIEMENS LEDS + OPTO



#### VDII CONVERT TV SET TO VDU

CONVERT TV SET TO VDU

The new CRT control chip from Thomson CSF
SFF96364. Convert your TV set into an electronic

VDU – 16 lines x 64 characters – requires RAM.
character generator and little else for a basic VDU.
Available as chip or full display control. 5 voits TIL compatible, line
erase, full card includes UART.
Modem, char, gen etc., comp video
out from encoded keybd in.

Send S.A.E. for data.



#### 1978 CATALOGUE

40 PAGE CATALOGUE
New enlarged micro section —
largest range of quality components
from franchised suppliers available
in UK. All VAT inclusive prices.
Over 8,000 line items plus lots
more. 45p post paid, 35p to callers
at any of our four branches.

#### DILSKTS

ow profile IC skts

8 pin 15p 22 pin 30p

14 pin 16p 24 pin 35p

16 pin 18p 28 pin 45p

18 pin 27p 40 pin 55p

**FULL RANGE OF** Capacitors Resistors Plugs/skts Meters Clocks

catalogue 31 DIGIT PANEL METER KIT

## **NEW LOW PRICES**



## THYRISTORS plastic powe

4 amps 8 amps 100v o 38 100v o 47 200v o 44 200v o 54 400v o 54 400v o 68 8randed Texas quality product



#### WE STOCK MORE

Stocking distributors officially appointed

NATIONAL **TEXAS** MULLARD SIEMENS SESCOSEM

**VERO ANTEX ELECTROLUBE** SIFAM ARROW HART MAKES COMPONENTS BUYING EASY

MAIL **ORDER** 

Quick service on all orders – please add 40p for P&P to all orders. Tel. orders on credit cards £10 minimum.









**ELECTRONIC COMPONENT CENTRE** 58-60 GROVE ROAD, WINDSOR, BERKS SL9 1HS TELEPHONE CREDIT CARD ORDERS WINDSOR (07535) 54525 TRADE EDUCATIONAL & EXPORT WELCOME.



VOLTAGE

## **ORIES & MICRO**

PLUS LOWER PRICES AND USUAL NEW FULL SPEC DEVICES. NOW POST FREE ORDERS OVER £3 - CASH OR CHEQUE OVER £10 5% OFF

CREDIT CARD ORDERS WELCOME BY POST OR PHONE. CASH OR CHEQUE OVER £3.POST & PACKING FREE. OTHER ORDERS ADD 25p P & P. NORMALLY 24 HOUR TURNAROUND ON EX STOCK PRODUCTS. U.K. ADD 8% V.A.T. TO PRICES MARKED \* ALL OTHER PRICES ADD 121% V.A.T. ALL PRICE EACH. NEW PRICE LIST WITH ECONOMY MICRO GEAR FREE. SEND S.A.E. (DATA COSTS EXTRA) PLEASE DUTTE MARGENTE CALLES WELCOME AT OUR ENLACED STORE THE CAST MARGEN.

(0	ATA COSTS EXTRA).	PLEASE QUOTE MAGAZII	NE, CALLERS WELCOME A	T OUR ENLAR	GED STORE	E. TUE	S-SAT (LUN'	CH 1 - 2)					01.11
DI FA	P TO All grade 1 707CA/704CC f1.20 x 0500 CA or CC f1.20 x 1.747 CA or CC f1.89 x	each 22pf to 0.1 ut £5 SET 2: TANTULUMS 1ut to 200 ut 20v to 35v Total 50 CAPACITORS £5 SET 3: ELECTROLYTIC 25 VOLT TOTAL 80. 10 each 1/2/5/10/47/100/220. 5 each	PAK A: 12 x RED LEOS £1★ PAK B: 6 x 741 DlL 6 £1★ PAF C: 4 x 2N3055 £1★ PAK D: 12 x BC1 09 £1★ PAK E: 13 x BC1 82 £1	TRANSISTORS MATCHING 20px AC127 17px AC127 10px AC187 20px AC188 20px AC188 40px AD161 40px AD162 40px AF239 42px BE107 8px BC108 8px	BD131 37 B0132 37 80695 69 BD696 69 BFY50 16 BFY51 16 BFX29 28 BSX20 18	0p * * 777p * * 80p *	CMDS Full Range in Lis 4000 14p: 4001 14p: 4002 14p: 4007 14p: 4008 65p: 4009 35p: 4010 15p: 4011 14p: 4013 35e:	★ 7401 ★ 7402 ★ 7404 ★ 7405 ★ 7408 ★ 7409 ★ 7410 ★ 7413	7p★ 8p★ 10p★ 15p★ 8p★ 10p★ 12p★ 25p★ 10p★	74LS02 18pm 74LS08 19pm 74LS10 20pm 74LS13 40pm 74LS14 11m 74LS20 19pm 74LS22 26pm 74LS22 26pm	74LS153 55p ± 74LS157 55p ± 74LS158 £1.15 ± 74LS160 £1.20 ± 74LS162 £1.30 ± 74LS163 £1.20 ± 74LS164 £1.28 ± 74LS165 75p ± 74LS165 75p ± 75	THE PARTY OF THE P	7
RE Ser Till GF 3 CCC	OS BIG & Bright. O 3mm/]" DIA 9p* O 5mm/]" DIA 9p* om CLIP & LOCK RING 3p* om CLIP & LOCK RING 3p* EEN OR YELLOW WITH CLIP DI 5mm DIA 19p* EMORIES: 10% off 8 up.	500/1000 £5 SET 4: 4WATT RESISTORS 5% C.F. 10 each 10 ohms to 10 meg ohm. 1014 500. £5 SET 5: 2ENERS 400mW TOTAL 100. 3-33 VOLT EST 6: 100 PRESETS £5 PASSIVE GEAR. RESISTORS 4v 5% C.F. 2p	PAK F: 13 x 2N3704	8C109 9pm 8C109C 15pm 8C147 12pm 8C148 12pm 8C149 12pm 8C157 15pm 8C158 15pm 8C159 15pm 8C167 10pm 8C188 11pm	MJE340 44 MJE2955 75 MJE3055 75 MPU131 3 0RP12(P) 49 TIP41A 60 TIP42A 65 TIP2955 60 TIP3055 50 TIS43 3	1 μ ± i	4015 60p1 4016 35p1 4017 55p1 4018 65p1 4020 60p1 4023 15p1 4024 45p1 4025 15p1 4027 35p1 4028 52p1	↑ 7425 ↑ 7430 ↑ 7440 ↑ 7442 ↑ 7445 ↑ 7447 ↑ 7470 ↑ 7474 ↑ 7474	20p* 8p* 14p* 50p* 69p* 32p* 25p* 25p*	74LS30 28pm 74LS47 35pm 74LS55 30pm 74LS73 45pm 74LS74 45pm 74LS74 74LS83 £1m 74LS85 £1m	74LS173 £1 ★ 74LS174 £1 ★ 74LS181 £3 ★ 74LS191 95p★ 74LS191 £1.30 ★ 74LS195 £1.30 ★ 74LS195 £1.30 ★ 74LS196 £1.30 ★ 74LS198 £1.30 ★ 74LS198 £1.30 ★	IC SUPERMARKET. 301 OP AMP 555 TIMER (NE555) 556 DUAL TIMER 709 DIL 14 710 COMPARATOR 723 REGULATOR 741C 8 PIN DIL OPA 741 T099 OR DIL 14	30p± 27p± 60p± 25p± 40p± 18p± 13p±
21 21 21 21 EA (4 27	02 RAM 450ns £8px 102 RAM 350ns £1.20x 102 RAM 250ns £1.35x 14 STATIC 4k RAM. SY USE. NO ELOCK, 5 x 1k) 18 PIN £6-60 eech 08 EPROM £7x 15 iN7EL £29x 32 5v. EPROM POAx	PRESETS PREVERT Type 45 POTS 106 /J/N 26 p  CAPACITORS TANTS 12 p CRAMIC 50v 5% HI STAB 22pl to 0.1ul 22 47 5p  ELECTROLYTICS 25 VOLTS 1/10/47/100ul ALL 10p 160v 20a) 220/470ul 30p	PAK M: 4 x PAIRS NPN/PNP 2 AMP 60 VOLT E1 PAK N: 50 x OA81/9 PAK P: 20 x SMALL SIGNAL NPN. SIMILAR TO 109 PAK 0: 50 x 0.2 20u/ 6.3 VOLT ELECTROLYTIC PAK R: 14 x 8C107 E1 PAK S: 14 x 8C106 E1 E1	BC189 12p BC177 18p ± BC177 18p ± BC179 18p ± BC182 10p BC182 10p BC183 10p BC183 10p BC183 10p BC184 10p	2N3053 18 2N3055 45 2N3614 £ 2N3702 2N3704 2N3706	9p 10p 10p 10p 10p 10p 10p 10p 10p 10p 10	4029 60p1 4030 35p1 4042 54p1 4043 55p1 4049 28p1 4050 28p1 4066 40p1 4067 £41	* 7476 * 7480 * 7482 * 7483 * 7486 * 7490 * 7491 * 7492	35p± 29p± 39p± 75p± 75p± 29p± 30p± 70p± 40p± 29p±	74LS93 85px 74LS107 42px 74LS112 £1x 74LS122 75px 74LS123 63px 74LS124 £1.58x 74LS132 £1x 74LS133 55px 74LS138 55px	74LS240 £2.30 ± 74LS241 £2.30 ± 74LS242 £2.30 ± 74LS245 £3 ± 74LS251 £2 ± 74LS257 £1.60 ± 74LS259 £1.60 ± 74LS298 £2.25 ±	747 DUAL 741 748C 0P AMP 3900 DUAD 0P AMP 7905 1 AMP 5 VOLT 7805 (703) LM309K 7808, 7812, 7815 8038 SIG GEN 7900 SERIES 78013 & 76023 CA 3130	60p± 33p± 45p± 60p± £1± 60p± £3.55± £1± £1.35±
80 68 68 68 + 68 68	ICRO BUSS STOP  80 CPU 1 MHZ £5* 00 CPU 1 MHZ £7* 09 CPU POA* 09 CPU POA* 46 PIA + MIK BUG ROM TIMER £26* 20 & 6821 PIA £65* 50 ACIA 1 MHZ £85*	1000ul 25v 35p KNOBS 1" DIA & TRIM 15p HEATSINKS To 3 25px To 3 LARGE 50px TV4 25p To 5 or To 18 VERD ALL 0.1" & MOST PRODUCTS AT NORMAL PRICES S A 0VERTISED i.e.	PAK X: 4 x 555 TIMER £1# PAK Y: 5 x DUAL TRANSISTORS MD7021. 6 LEAD TO5 £1# PAK 7: 20 x PMP SMALL	BC212 12p BC212L 12p BC213L 12p BC213L 12p BC214L 12p BC214L 12p BCY71 20p*	2N3820 3 2N3904 1 2N3906 1 2N5457 3 2N5777 44 TIL31 IR £2	38p 15p 15p 32p p★ 2★	4073 18pv 4081 16pv 4082 21pv 4510 70pv 4511 70pv 4518 85pv 4520 65pv 4543 £1.75v 4553 £44	# 7494 # 7495 # 7498 # 74100 # 74107 # 74121 # 74123 # 74141 # 74154	75p ± 65p ± 65p ± £1 ± 28p ± 25p ± 40p ± 70p ± 95p ±	74LS151 £1 ★ DIL SOCKETS 8 PIN, 14 PIN or 16 PIN 12g ★ 18 PIN 20g ★ 24 & 28 PIN 50g ★ 40 PIN 75g ★	TRIACS DISCO 10A 400V £1± BR10D DIAC 25p SCR 1A 400V 50p C1060 4A	CA 3140 CA 3046 CA 3054 L200 – 21 AMP 3-38 L2005 – 214 5 VDI LM300 REGULATOR LM38B 1 WATT AMP LM38B 1 UAL PREAMP LM38F QUAL PREAMP	70p* 49p* £1 lv £3* £3* £1* 75p. P£1.05*
AY SF 83 1N MI MI	5 1013 VART 64* 51 014 5V, UART 65* 98364 VDU IC 1CHIP POA* TERFACE: RS232 & 3: 1488 & 1489 90p* 1C8880 & 6889 £2* LS95 & 96 £1.40* AL 1 MHZ £3*	3	JACKSONS TUNING CAPACITOR 0.390 PF 0.881 DIDOES x 1000 £10 KEYBOARD DECODED ALPHANIM, ASCI1 £55* BUBBLE MEMORY COMMING, INTEL 3085 + SUPPORT POA	10% di DIDDES & BRIDI 1 AMP 50 VOLT B IN4148 or IN914 DAB1 or CA91 OA202 or DA202 IN4001 1 AMP 50 IN4004 7p* IN40	10gE 20g	p★ 4p 5p p★	555 timer 100	* 74157 74164 74190 74193 leds 100 fo 0 for £20.	75jr★ or £7.74	All LO Profile.  PCB DRILL  †* CHUCK £10 ±  18 pin 100 for £1  100 for £6, BC10			£10* £4* £1

					_		
РН	OF	=	_		-	OLENT)	
		_   4	46	Osborne	Rd., South	sea, Hants	
	-	a new Such as	catalog	jue –	with a	lot of	new
4000 4001 4002 4008 4011 4012 4013 4014 4015 4016	0.18 0.18 0.79 0.18 0.18 0.45 0.99 0.79 0.39	4017 4018 4020 4023 4015 4017 4028 4042 4046 4049		4050 4052 4070 4081 4093 4402 4412 4445 4502 4510	0.49 0.95 0.28 • 0.18 0.79 0.38 0.38 1.75 0.99	4511 4514 4516 4518 4528 4531 4543 4543 4581 4582 4584	1.20 2.40 0.99 0.99 0.99 0.99 1.85 1.25 0.69
Cermet 1 Type 94			Гуре 90Н	I/∨ <b>0.36</b>		Туре Е	0.59
Transfor 1VA 1.2VA	1.10	6VA pcb 6VA enc		6VA ope 20VA m		20VA . 50VA	3.30 5.48
LED'S Red	0.17		Green	0.25		Yellow	0.25
		and hund	reds of o	ther com	ponents.		
Send n	ne you	r 1978 d	catalog	ue – fr	ee.		
Name							
Audres	>	*******	•••••	• • • • • • • • • • • • • • • • • • • •	•••••	• • • • • • • • • • • • • • • • • • • •	
	*******		•••••	•••••		• • • • • • • • • • • • • • • • • • • •	

#### PRIMARY 220–240 50HZ. ALTERNATIVE SECONDARY VOLTAGE AND CURRENT AVAILABLE BY SERIES OR PARALLEL CONNECTION Curent £ p/p Type Voltage Voltage Current £ p/p 0.5A EACH 0.6A EACH 1A EACH 1.6A EACH 3A EACH 4A EACH 06FE06 08FE06 12FE06 20FE06 50FE06 6+6 6+6 6+6 6+6 6+6 1.50 1.80 2.00 2.60 3.10 3.60 20FE24 24+24 50FE24 24+24 60FE24 24+24 80FE24 24+24 0.4A EACH 2.60 0.8A EACH 3.10 1.2A EACH 3.60 1.5A EACH 4.50 70p 70p 85p 100p 50FE28 28+28 60FE28 28+28 80FE28 28+28 0.75A EACH 1.1A EACH 1.4A EACH 3.10 3.60 4.50 70p 85p 100p 60FE06 06FE09 08FE09 12FE09 20FE09 50FE09 0.3A EACH 0.5A EACH 0.75A EACH 1A EACH 2.5A EACH 3A EACH 9+9 9+9 9+9 9+9 9+9 9+9 50p 50p 60p 70p 70p 85p 1.50 1.80 2.00 2.60 20FE30 30+30 50FE30 30+30 60FE30 30+30 60FE30 30+30 0.35A EACH 0.75A EACH 1A EACH 1.2A EACH 2.60 3.10 3.60 4.50 MULTI-TAP RANGE, VOLTAGE AVAILABLE 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 12-0-12 OR 15,0-15 30FE30 | 0.12-15 | 24-30 | 1A | 3.40 | 70p 60FE30 | 0.12-15 | 2A | 3.70 | 85p 80FE30 | 0.12-15 | 3A | 4.50 | 100p 100FE30 | 0.12-15 | 4A | 5.80 | 115p 12+12 12+12 12+12 12+12 12+12 12+12 12+12 0.25A EACH 0.3A EACH 0.5A EACH 0.8A EACH 2A EACH 2.5A EACH 3A EACH 50p 50p 60p 70p 70p 85p 100p 60FE12 80FE12 OGFE15 15+15 OBFE15 15+15 12FE15 15+15 20FE15 15+15 50FE15 15+15 60FE15 15+15 80FE15 15+15 0.2A EACH 0.25A EACH 0.4A EACH 0.6A EACH 1.6A EACH 2A EACH 3A EACH 50p 50p 60p 70p 70p 85p 100p CENTRE TAP SECONDARY 06 6-0-6 1A EACH 2.00 19 9-0-9 1A EACH 2.00 12 12-0-12 1A EACH 2.00 15 15-0-15 1A EACH 3.10 10 20-0-20 1A EACH 3.10 12 22-0-26 1A EACH 3.10 12 26-0-26 1A EACH 3.00 13 03-0-30 1A EACH 3.60 18 28-0-28 1A EACH 3.60 18 28-0-26 2A EACH 5.15 18 36-0-36 2A EACH 5.15 FE06 6-FE09 8-FE12 12-FE15 15-FE20 20-60FE52 26-60FE52 26-80FE30 30-100FE36 36-100FE36 36-06FE20 20+20 08FE20 20+20 12FE20 20+20 20FE20 20+20 50FE20 20+20 60FE20 20+20 80FE20 20+20 0.15A EACH 1.50 0.2A EACH 1.80 0.25A EACH 2.00 0.5A EACH 2.60 1.2A EACH 3.10 1.5A EACH 3.60 2A EACH 4.50 50p 50p 60p 70p 70p 85p 100p

CHARGER 48FE12 | 0-6-12 66FE12 | 0-6-12 70FE12 | 0-6-12

FLADAR ELECTRIC P.O. BOX 19 WESTCLIFF-ON-SEA

ESSEX, 0702-613314

TRANSFORMER

4A 3.10
5A 3.80
6A 4.86

08FE24 24+24 0.15A EACH 1.80 12FE24 24+24 0.2A EACH 2.00

70p 85p 100p

50p 60p TRADE ENQUIRIES

PLEASE ENQUIRE FOR OTHER TYPES NOT SHOWN

PAYMENT TERMS:

Please Add 8% VAT

C.W.O. Cheques, Postal Orders

0.26 | 20p 0.26 | 20p 0.30 | 20p 0.60 | 25p 0.75 | 30p

## SEIKO-20% OFF!

#### FX 003 MEMORY BANK (£130) £104

Star" of the 1979 Seikos available from us today! Full time and calendar display. Displays past and future calendars with flashing reminder for important dates, set yearly

#### CITIZEN — LARGE REDUCTIONS

on most quartz analogue digital models

#### FROM CASIO – OF COURSE



PQ-7

#### TRAVEL ALARM CLOCK

Battery powered quartz alarm clock with repeat feature Countdown alarm/timer. 1/10 second stopwatch. Constant LC Display. Nightlight. 1 year batteries.  $4\frac{3}{4} \times 1\frac{1}{4} \times \frac{1}{2}$  inch. 1.6 oz. For car, caravan or boat. (£24.95.) £19.95

NEW



#### QL-10. CIGARETTE LIGHTER/ CALCULATING ALARM CLOCK

Soft piezoelectric system gas lighter. 6 digit LCD clock ± 15 seconds/month. Permanently prog. calendar (1901-2099). Two alarm functions plus countdown alarm. Time memory. Calculator with time/date calculations, K, %. ½ × 2¾ × 4 inches. 3.6 oz 18 months £39.95 battery, Pouch, Prov. price

#### **AO-1000 CALCULATING ALARM CLOCK PLUS** 3-WAY STOPWATCH

Hours, minutes, seconds, am/pm. 24 hour Alarm with sign. Stopwatch: Net times, lap times. 1st & 2nd place times from  $\frac{1}{10}$  sec. to 10 hrs. with ST & LAP from  $\frac{1}{10}$  sec. to 10 hrs. with ST & LAP signs. Calculator: 4 key memory, %,  $\sqrt{\phantom{a}}$ x 23 x 45 ins

RRP £26.95

Our price £21.95

**CQ-81** Calculating alarm clock plus two alarm/timers LCD 1 year batteries.  $1\frac{5}{8} \times 2\frac{3}{4} \times 5$  ins.

£17.95

CQ-2 Special Offer. Clock, calendar, 4 alarms stopwatch, Time/Date calculator (RRP £39.95) P.O.A.

The incredible FX-8000. LCD 41 sc. functions 1/100 sec. stopwatch, 2 x 5 alarm/timers (£35.95) £29.95

#### MINI CARD CALCULATORS

LC-78 Mini Card. Full Memory. %, J, K.£16.95 FX-48 Math Card. Full scientific with SD.£19.95

**ST-24 Card Time.** 24 hour stopwatch (or clock) 2 alarm/timers. Calculator as LC-78. £19.95

ST-1 four way stopwatch. Calculator

£24.95

All Casio scientifics. Lowest prices

**OPTIM Coronet 600** Cartridges from £9.95

£48.50

#### FAIRCHILD TIMEBAND Grandstand

Cartridges from £12.50

£119.95

ATARI Video Computer System Probably the very best available to date! Cartridges from £14.95

#### BORIS. Communicating chess computer.

One of the world's most advanced portable chess games. No T/V required. c100

## THIS MONTH'S





second to 13 hours. Stainless steel, mineral glass Water resistant to 100 feet.

£29.95

## LOW COST WATCHES

From National or similar high quality.

PH-G1 FOUR DIGIT (Left)





4 digits 5 functions Backlight £9.95 PH-G2 As above

topwatch £14.95

PH-G3 ULTRA SLIM (Right) 6.5mm approx 5 functions, light, case, battery hatch.

£18.95



6 digits, up to 23 functions. Net. lap & 1st & 2nd place times to 1/100 £18.95



PH-ALARM CHRONO. Same chrono functions 24 hr. alarm Hours, mins, sec or date, day, am/pm Day, date, month, year. S/S case, Mineral glass £39.95

CBM Giant 4 digit. 5 functions. Light



£9.95 (Right) 18 × 3 ALARM

95 × 3

(£15.95) Chrome

Bracelet


95 × 2

Gilt, Strap

6 digits, 6 functions plus backlight and alarm setting 5 minute snooze facility, (£28.95) £22. £22.95
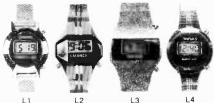
#### **LADIES LCD WATCHES**

5 functions, Backlight, Gold or silver finish. (specify) Dress Watch, Round Milanese bracelet, L1 £14.95 Cocktail Watches. 3 styles, integral bracelet. £18.95



WATCH BATTERIES 65p each. DIY KIT 35p.

## CASIO QUALITY

All CASIO watches have a calendar display, night illumination, mineral glass and stainless steel cases, water resistant to 100 ft (except sports watches - 66 ft).

**SPORTS WATCHES** 

F-100 £24.95

52QS-14B Right 8 mm (£44-95) £34.95





Up to 25 functions. Net lap and first and second place times to 1/100th sec, F-100. Resin case, strap. 52QS-14B. S/S encased version and bracelet.

4 DIGIT WATCHES (except World Time)
Hours, minutes, ten seconds, seconds by flash, am/p
Day, date, month. Stopwatch. Dual time (except 31QR-20B).



31QR-20B (£35.95)

£29.95

51QR-19B

(£44.95) £34.95

6 DIGIT WATCHES (except Sports and Alarm) Hours, minutes, seconds, day, OR Hours, minutes, date, day, ten seconds, seconds by flash. Day date, month, year Selectable 12 hour (with am/pm) or 24 hour clock.

54QS-16B

Lett. 6 digit. (£49.95)

£39.95

54QS-15B

6 digit (£54.95)

£44.95

CHRONOGRAPH. 6 digits as above, with stopwatch measuring net, lap and 1st & 2nd place times from 1/100 sec to 6 hrs. Dual time facility.



45CS-22B (£69.95)

£54.95 29CS-11B

(FR4 95)

£69.95

WORLD TIME WATCH. The time in ten capitals plus one optional time. Instant summertime correction. Hrs., mins, 10 secs, secs by flash. Perpetual calendar, day, date, month. Running digital seconds display.

#### ALARM WATCHES 25CR-16B

(£74.95)

£54.95



£69 95





Hours, mins, seconds (or hrs. mins, date) day, am/pm Day, date, month, year. 24 hr alarm, on/off indicator.

ULTRA SLIM DRESS WATCHES Five models from £59.95 CASIO LADIES' LCD WATCHES

Backlight 27CL-15B £29.95

27CL-17B £39.95

Three other models available

Send 25p for our litus, catalogue, Casio, Citizen, Seiko, etc. Prices include VAT P.&P. Send cheque, P.O. or phone your credit card No. to:

Dept.P.E., Talk Of The Town, 19/21 Fitzroy Street Cambridge CB1 1EH, Tel 0223 312866

#### TOTAL AMPLIFICATION FROM

## CRIMSON ELEKTRIK

#### – WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS -

#### STEREO PRE-AMPLIFIERS



#### **CPR 1 – THE ADVANCED PRE-AMPLIFIER**

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion < .005% at 30dB overload 20kHz. Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp. signal levels. Signal to noise ratio 86dB; slew-rate 3V/uS; T.H.D. 20Hz – 20kHz < .008% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 130 × 80 × 20mm. Supply to be ±15 volts.

#### MC 1 - PRE-PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Sensitivity 70/170uV switchable on the p.c.b. This module brings signals from the now popular low output moving-coil cartridges up to 3.5mV (typical signal required by most pre-amp disc inputs). Can be powered from a 9V battery or from our REG 1 regulator board.

#### **REG 1 – POWER SUPPLY**

The regulator module, REG 1 provides 15-0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

#### **POWER AMPLIFIERS**

It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification: T.H.D. typically, 0.1% any power 1kHz 8 ohms; T.I.D. insignificant, slew rate limit 25V/uS; signal to noise ratio 110dB; frequency response 10Hz-35kHz, 2dB; stability unconditional; protection drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 x 80 x 25mm.


#### **POWER SUPPLIES**

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).
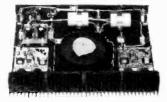
#### POWER AMPLIFIER KIT

The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.





POWER AMPLIFIER MODULES	
CE 608 60W/8 ohms 35-035v CE 1004 100W/4 ohms 35-0-35v	£16-30 £19-22
CE 1008 100W/8 ohms 45-0-45v	
CE 1704 170W/4 ohms 45-0-45v	£29-12
CE 1708 170W/8 ohms 60-0-60v	£31.90
TOROIDAL POWER SUPPLIES	
CPS1 for 2 x CE 608 or 1 x CE 1004 . CPS2 for 2 x CE 1004 or 2/4 x CE 608	£14-47 £16-82
CPS3 for 2 x CE 1008 or 1 x CE 1704	£17.66
CPS4 for 1 x CE 1008	£15-31
CPS5 for 1 x CE 1708 CPS6 for 2 x CE 1704 or 2 x CE 1708	£22-68 £23-98
	123.30
HEATSINKS Light duty, 50mm, 2°C/W	£1-30
Medium power, 100mm, 1-4°C/W	£2:20
Disco/group, 150mm, 1-1°C/W	£2.85
Fan. 80mm, state 120 or 240v	£18-50
Fan mounted on two drilled 100mm heatsinks, 2 x 4°C/W, 65°C max:	
with two 170W modules.	£29-16
THERMAL CUT-OUT, 70°C	£1.90

POWER AMP KIT £32-40
PRE-AMPS: These are available in two versions— one uses standard components, and the other (the S) uses MO resistorts where necessary and tentalum capacitors. CPRI £29.49 CPRIS £39.98 MCI £18.50 MCIS £29.49 POWER SUPPLY: REGI £6.75.TR6 £1.75
BRIDGE DRIVER, BDI Obtain up to 340W using 2 x 170W amps and this module. BDI £5.40

CRIMSON ELEKTRIK 1A STAMFORD STREET, LEICESTER LE1 6NLL Tel. (0533) 537722

All prices shown are UK only and include VAT and post. COD 90p extra, £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 international Reply Coupons for detailed information.

Distributor: Miric Teleproduckter, Box 12035, S-750 12 Uppsala 12, Sweden.

# COMPONENTS

Low Imp Dynamic Mic's Brand new in packs £1.62 Triecs 10 amp 400v brand new AEI full spec. all with fitted heavy duty heat sink £2.55

Motorola tweeters. Only £16.50 each. Ideal for P.A. work or discos.
SPECIAL CAPS OFFER LECTROFLASH Photoflash caps, ideal for strobes or the serious photographer. All brand new. 200uf at 500vdc each £1.60 400uf at 500vdc each £1.60 2500ul at 70vdc each £2.00 100 + 500uf at 250vdc each £3.00 IMCO AC working cap 16uf ± 5% at 500 only £3.00 each P61sic Computer grade caps for your power amp 3900uf at 100v each £2.20 Caps by G.E. 1400uf at 200vdc. Screw terminals each £1.85 Smooth out granny with 83,500uf at 45vdc 60v surge computer grade each £3.50 cm year production with \$150 per 10 per terminal seach £1.85 per 10 per terminal seach

£3.50 Somputer grade each Connecting wire 15p per 10 metres or mixed at £3.00 per kilo approx. Tagstrips 30 way new. 15p Group Board 17 or 34 way brand new 12p and 24p Meters 1 ma meters ex-equipt but in terrific condition £3.20

Transformers All with 110-240v ac

primarys. 24vac @ 10 amps. £7.50 inc (open const) 9vac @ 3 amps. £3.80 inc (clamp const) 240v in. 15-0-15 @ 2 amps. £3.55 inc (clamp const) 13vac @ 3amp 15vac @ 1 amp £6.80 inc

(C core const) Toroid 240vac in 35v @ 4 amps £12.00

Toroid 240vac in 35v & 4 amps £12.00 inc (potted toroid) 240vac in 12v-12v-40v & .5a .5a 4 amps only £7.50 each 240vac in 12v-40v at .5a and 2.5 amps only £6.50 each 240vac in 35·0-35 at 4 amps only £7.04 each 240vac in 6.3v at 10 amps £6.50 each 240vac in 6.3v at 10 amps £6.50 each

## DIAL-A-BOX

As featured in "P.E. MARKET PLACE" a comprehensive stars As featured in "P.E. MARKET PLACE" a comprehensive stan-dard range of boxes for the con-structor, or custom built to your specification. Send your require-ments with S.A.E. or phone for

Linears and Transistors We hold comprehensive stocks of most popular types at realistic prices eg.— LM 380 complete 2.5 watt amplifier. 85p each. Suitable etched timed pcb £1.00. Components for same £1.20 set 10.00 components for same £1.20 set 10.00 components for same £1.20 set 10.00 complete \$1.00 complete \$1.00 complete \$1.00 complete semi-conductor lists to follow. Solenoids 12 Volt DC operation, ideal for door locking-lock release. Mainly executions for the same set 10.00 conclusions for some semi-conductor lists to follow. Solenoids 12 Volt DC operation, ideal for door locking-lock release. Mainly executions for some semi-conductor lists to follow over single semi-conductor lists to follow of sole for door locking-lock release. Mainly executions of the semi-conductor lists to follow over single semi-conductor lists to follow of the semi-conductor li Linears and Transistors We hold com-

Magnetic Disc Recorders Few only left of these units which provide an ideal basis for magnetic disc echo or multiple recording. Only £5.50

magnetic disc echo or multiple recording. Only £5.50
Wooden Cases Size approx 14" x 5" x 9" inished in dark oak colour ideal for use as amplifier case, small loudspeaker case, baby alarm amp Only 75p
I/C socket panels with over 60 ic sockets fitted, mainly 14 pin easily removed with a blowtorch from rear. Only £2.50
Lamp panels with over thirty lampholders fitted ideal for light displays or moving light shows. Only 85p
Power Supply Unit Complete ready to go. Ex-equipment but guaranteed in working order. Delivers 5v and 7.5v at up to 10 amps total 240 v primary Only £5.50
Relay TV converters ex relay service so o guarantee but ideal break-down units containing a host of RF components including a TV modulator if's caps etc; Only £2.75

Only £2.75
ISKRA 3 speed record decks. Single players with specially wound motor for 240v and separate winding giving 14v for deck amplifier. Only £6.85
Plenty of spares for ISKRA decks. Arms £1.00. Turntables £1.00 atc.
Barrier Strips 3 way 10p each or 10 for 60n

£1.00. Turntables £1.00 etc.
Barrier Strips 3 way 10p each or 10 for 60p
Solda-tag packs Approx 50 assorted single, double, rivet type, all sizes. 25p per pack
ALI-Facks All sizes of off-cuts ideal for that odd job 25p
Self Adhesive cabinet feet 4 for 15p
PSU Hearts twin heatsink with rectifier two caps, two high wattage resistors and other components. Only 35p
Terminal strips 16 way similar to barrier strips 38p each.
Triac operated mains timer in perspex box all in original wrapping £1.05 each was all to original wrapping £1.05 each cable Ties long re-usable 6° plus. 3p each.
Double sided sticky tane in 6° strips with

each. Double sided sticky tape in 6" strips with

easy tear ends 5p each
"P' Clip packs 30p each
1.C. packs all types, many with original markings very cheap £1.20

All prices include VAT - Please add 35p Post & Packing to total cost of order. Open daily 9.30am-6pm - Access or Barclaycard accepted + S.A.E. for lists.

## 322-324 WHITEHORSE ROAD, CROYDON, SURREY CRO 2LF TEL 01-584 9872



Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together invertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top. ALL INTERLOCK

As supplied to Post Office, Industry and Government Depts.

SINGLE UNITS (1D) (5in x 2½in x 2½in) £3.50 DOZEN. DOUBLE UNITS (2D) (5in x 4½in x 2½in) £5.50 DOZEN. TREBLE (3D) £5.50 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2),

£7.90 for 8. EXTRA LARGE SIZE (6D1) £6.90 for 8.

#### PLUS QUANTITY DISCOUNTS

Orders over £20, less 5%, Orders over £60, less 7½%. PACK-ING/POSTAGE/CARRIAGE: Add £1.00 to all orders under £10. Orders £10 and over, please add 10% carriage. QUOTATIONS FOR LARGER CUANTITIES. Please add 8% V.A.T. to total remittance. All prices correct at time of going to press.




Modern, slim-line power panel, countless uses in nome, office factory, showrooms. Perfectly safe, unbeatable, Can be mounted on wall or trailed anywhere in room. Nest rubber base. Smart PVC outer cover. Black £3.10, White £3.30, P&P 60p each.

## FLAIRLINE SUPPLIES (PE12)

124 Cricklewood Broadway, London N.W.2 Telephone 01-450 4844
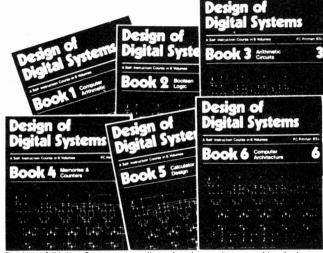
# **Understanding Digital Electronics New teach-yourself courses**



<u>Design of Digital Systems</u> is written for the engineer seeking to learn more about digital electronics. Its six volumes – each A4 size are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers.

#### The contents of Design of Digital Systems include:

**Book** 1 Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.

**Book 2** OR and AND functions; logic gates; NOT, exclusive-OR, NAND. NOR and exclusive-NOR functions: multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.

**Book 3** Half adders and full adders; subtractors; serial and parallel adders; processors and artithmetic logic units (ALUs); multiplication and division systems.

Book 4 Flip flops; shift registers; asynchronous and sychronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).

Book 5 Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control program structure.

**Book 6** Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.









<u>Digital Computer Logic and Electronics</u> is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes – each A4 size – and serves as an introduction to the subject of digital electronics. Everyone can learn from it – designer, execxutive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems; AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops; binary counters, shift registers and half adders.

CAMBRIDGE LEARNING ENTERPRISES. Unit 23, Rivermill Site, FREEPOST, ST. IVES, HUNTINGDON, CAMBS. PE22 4BR, ENGLAND. TELEPHONE ST. IVES (0480) 67446. PROPRIETORS: DRAYRIDGE LTD. REG. OFFICE: RIVERMILL LODGE, ST. IVES. REGD. IN ENGLAND NO. 1328762

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and fuel consumption; you could be calling people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

The six volumes of Design of Digital Systems cost only:

£8.10 +90p post & packing

And the four volumes of Digital Computer Logic and Electronics cost only:

£4.60 +90p post & packing

But if you buy both courses, the total cost is only:

E12 +£1 post & packing

Price includes surface mail anywhere in the world: Airmail extra.

## Flow Charts & Algorithms

HELP YOU PRESENT:

safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

THE ALGORITHM WRITER'S GUIDE explains how to: define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size: A5, 130 pages. This book is a MUST for those with things to say.

£2.95

 $\pm$  45p post and packing by surface mail anywhere in the world. Airmail extra.

#### GUARANTEE

If you are not entirely satisfied your money will be refunded.

Please allow 21 days for delivery.

<del></del>
Cambridge Learning Enterprises, Unit 22, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs. PE17 4BR, England.
Please send me the following books:sets Digital Computer Logic & Electronics @ £5.50, p & p included
sets Design of Digital Systems @ £9.00, p & p includedCombined sets @ £13.00, p & p includedThe Algorithm Writer's guide @ £3.40, p & p included
Name
Address
l enclose a *cheque/PO payable to Cambridge Learning Enterprises for £
Please charge my *Access/Barclaycard/Visa/Eurocard/Mastercharge/ Interbank account number
Signature*delete as appropriate.
Telephone orders from credit card holders accepted on 0480-67446
(Ansafone). Overseas customers should send a bank draft in sterling drawn on a London Bank, or quote credit card number.  PE23
on a conduit pain, or quote credit card number. FE23

## For a merry musical Christmas an electronic musical door chime which can play 24 different tunes!



Plays Greensleeves God Save the Queer Rule Britannia Land of Hope and Glory Oh Come All Ye Faithful Oranges and Lemons Westminster Chimes Sailor's Hornpipe Beethoven's "Fate Knocking The Marseillaise Mozart Wedding March Cook House Door The Stars & Stripes Beethoven's Ode to Joy William Tell Overture Soldier's Chorus

Twinkle, Twinkle Little Star Great Gate of Kiev

Maryland Deutschland über Alles

Bach Colonel Bogie The Lorallie


CCHROMATRONICS, River Way, Harlow, Essex, U.K. £1595 Please send Chroma Chime Kits at £18-90 each including VAT and post and packing PLEASE USE BLOCK CAPITALS l enclose cheque/PO value £\_\_\_\_\_\_or debit my ACCESS/BARCLAYCARD account No PE

'These tunes play longer if the push button is kept pressed

wonderboard

SOLDERLESS CIRCUIT BOARDS

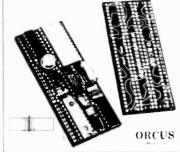Build **Your Circuits Just Once** In Minutes...



Please allow 7 - 21 days for delivery

It's crazy to build, unbuild, construct and destruct your circuits on expensive "Breadboards". Now very economically on WONDERBOARD, you plug your components into one side of the board, the wires into the other, and you install the finished circuit in your equipment. They're like PC boards, but no soldering (which is enemy No. 1 of prototypes). Change any wire or component any time without disturbing others. Up to six interconnecting wires and one component lead into one multicontact. WONDERBOARDS accept all IC's from 4 to 60 pins and discrete components too

Reliable? They conform to applicable sections of USA Military Standard MIL-A-46 146 and are used by the US Navy. You can't ask for better. WONDERBOARDS the universal board for equivalents of single-sided, double-sided, plated-thro' hole, and multilayer printed circuits.

"Small Wonder" 12 IC DIL-14 capacity (Equiv. No. tie-points 1302)

"Big Wonder" 48 IC DIL-14 capacity (Equiv. No. tie-points 5208)

£2.80

£11.20

All prices include VAT and P&P. Send cheque or postal order to:-

CHARCROFT ELECTRONICS LIMITED Charcroft House, Sturmer, Haverhill, Suffolk CB9 7XR Telephone Haverhill (0440) 5700 Telex. 817574

See us at BREADBOARD '78 21st-25th November '78 Seymour Hall, London W1. Stand F10



## WAR ON OUR **EXCESS STOCKS!!!**

FANTASTIC BARGAIN PACK OFFERS TO CLEAR OUR MASSIVE INVENTORY.

Cut	out and post whole coupon
	Insert No: of Packs required in box
1.	Twenty Transistors T018 / T05 / plastic silicon / germanium £1·00
2.	Twenty Rectifier diodes 500MA/1A/6A axials & studs £1 00
3.	Resistors 400 yes 400-mixed $\frac{1}{8} \cdot \frac{1}{4} \cdot \frac{1}{2}$ carbon films £1 ·00 (Count by weight)
4.	Zener diode pack 15 zeners 250/400MW $1$ W/5W £1 00
5.	Ten Potentiometers log lin with & without switch £1.00
6.	2 miniature transformers 3 VA assorted voltages £1 · 00
7.	100 assorted capacitors including electrolytic/disc/mylar £1·00
8.	Precision (1%) resistors metal films 100 for $\pounds 1 \cdot 00$
9.	Linear amplifier IC's including 741's 709's 710's etc. 9 for £1·00
10.	JUMBO JUNK BOX FILLER! All sorts of semiconductors & IC's resistors, caps, pots, presets, wire, fuses, etc. etc. Kilo gross weight for £2·20
**	One free pack (1-9) if you buy all 10 packs.
_	(your name & address)
To:	
This	is your label—please print clearly.

## ARROW ELECTRONICS LTD LEADER HOUSE COPTFOLD **BRENTWOOD**

ESSEX. MAIL ORDER OR COLLECT AT OUR SHOP.
ALL INCLUSIVE PRICES — NO VAT OR P & P.TO ADD

## HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropiate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: complete pre-amplifier in single pack, multi-function equalisation, low noise, low distortion, high overload, two simply combined for stereo.

APPLICATIONS: hi-fi, mixers, disco; guitar and organ, public address

SPECIFICATION: Inputs-magnetic pick-up 3mV, ceramic pick-up 3mV, tuner 100mV, microphone 10mV, auxiliary 3-100mV, input impedance 47kN at 1kHz. Outputs—tape 100mV, main output 500mV R.M.S. Active Tone Controls—treble ± 12dB at 10kHz, bass ± 12dB at 100Hz. Distortion—0.1% at 1kHz, signal/noise ratio 68dB. Overload—38dB on magnetic pick-up. Supply Voltage— ± 16-50V Price £6.27 + 78p VAT. P. & P. free

HY5 mounting board B.1. 48p + 6p VAT. P. & P. free



The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of, I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up to date technology available. FEATURES: complete kit, low distortion, short, open and thermal protection, easy to build

APPLICATIONS: updating audio equipment, guitar practice amplifier, test amplifier, audio oscillator SPECIFICATION: Output Power—15W R.M.S. into 80 Distortion—0.1% at 15W Input Sensitivity—500mV. Frequency Response—10Hz-16kHz - 3dB

Price £6-27 + 78p VAT. P. & P. free

**HY50** 25W into  $8\Omega$  The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World. FEATURES: low distortion, integral heatsink only five connections, 7 amp output transistors, no

external components.

APPLICATIONS: medium power hi-fi systems, low power disco, guitar amplifier

SPECIFICATIONS: medium power hi-fi systems, low power disco, guitar amplifier

SPECIFICATION: Input Sensitivity—500mV Output Power—25W R.M.S. into 8Ω Load Impedance—4-16Ω, Distortion—0-04% at 25W at 1kHz Signal Noise Ratio—75dB Frequency Response—10Hz-45kHz – 3dB. Supply Voltage— ± 25V. Size—105 × 50 × 25mm

Price £8.18 + £1.02 VAT. P. & P. free



The HY120 is the baby of I.L.P. s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: very low distortion, integral heatsink load line protection, thermal protection, five connections, no external components.

APPLICATIONS: hi-fi high quality disco public address, monitor amplifier guitar and organ

SPECIFICATION: Input Sensitivity—500mV Output Power—60W R.M.S. into 8Ω Load Impedance—4–16Ω. Distortion—0.04% at 60W at 1kHz. Signal Noise Ratio—90dB. Frequency Response—10Hz-45kHz. –3dB. Supply Voltage— ±35V. Size—114 × 50 × 85mm

Price £19.01 + £1.52 VAT. P. & P. free

**HY200** 120W into 8Ω The HY200 (now improved to give an output of 120 watts) has been designed to stand the most rugged conditions such as disco or group while still retaining true hi-fi performance.

FEATURES: thermal shutdown very low distortion, load line protection, integral heatsink, no external

components.

APPLICATIONS: hi-fi disco, monitor power slave, industrial, public address SPECIFICATION: Input Sensitivity—500mV Output Power—120W R M S into 8Ω Load Impedance—4–16Ω. Distortion—0 05% at 100W at 1kHz Signal Noise Ratio—96dB Frequency Response—10Hz-45kHz – 3dB. Supply Voltage— ± 45V. Size—114 × 50 × 85mm

Price £27.99 + £2.24 VAT. P. & P. free

**HY400** 240W into  $4\Omega$ 

The HY400 is I.L.P. s  $\,$  Big Daddy  $\,$  of the range producing 240W into  $4\Omega^{+}It$  has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: thermal shutdown very low distortion, load line protection, no external components APPLICATIONS: public address, disco, power slave, industrial SPECIFICATION: Output Power—240W R M.S. into 4Ω. Load Impedance—4-16Ω Distortion—0.1% at 240W at 14Hz Signal Noise Ratio—94dB Frequency Response—10Hz-45kHz - 3dB Supply Voltage —±45V Input Sensitivity—500mV Size—114 × 100 × 85mm


Price £38.61 + £3.09 VAT. P. & P. free


POWER SUPPLIES: PSU38—suitable for two HY30s £6.44 + 81p VAT. P. & P. free. PSU50—suitable for two HY50s £8.18 + £1.02 VAT. P. & P. free. PSU70—suitable for two HY120s £14.58 + £1.17 VAT. P. & P. free. PSU90—suitable for one HY200 £15.19 + £1.21 VAT. P. & P. free. PSU180—suitable for two HY200s or one HY400 £25.42 + £2.03. VAT. P. & P. free.

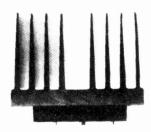Free post + packing applicable to U.K. only







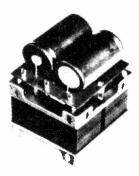

## TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd. Crossland House. Nackington, Canterbury Kent CT4 7AD Tel (0227) 64723

Please supply	
Total Purchase price	
Account number	
Name and Address	

Registered office No. 1032630

Signature..............



#### **RECEIVERS AND COMPONENTS**

VALVES, Radio - T.V. - Industrial - Transmitting and VAIVES. Radio – T.V. – Industrial – Transmitting and Projector Lamps. We dispatch Valves to all parts of the world by return of post, Air or Sea mail, 4000 Types in stock, 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves, Projector Lamps and Semiconductors. COX RADIO (SUSSEX) LTD., Dept. P.W. The Parade, East Wittering, Sussex, PO20 8BN, West Wittering 2023 (STD Code) 024366.

POWER AMP MODULES. 75 watts RMS with less than 0.017 distortion. Ready built or kit, from £10.50. Details free. I. G. Bowman (Dept. PE1). 59 Fowey Avenue, Torquay.

P.C.8s PAXOLIN  $10\frac{1}{2}$ " x  $4\frac{1}{2}$ " 4 - £1.25. 12" x 9" 70p.  $17\frac{1}{2}$ " x  $9\frac{1}{2}$ " £1.15. D.S. 10" x  $8\frac{1}{2}$ " 80p. Fibre Glass D.S. 13" x 6" £1.30.  $11\frac{1}{2}$  x  $7\frac{1}{2}$ " £1.60. Panel with 42 assorted 74 series ICs £1.50. 20 wire ended neons £1. 300 small components. trans, diodes £1.50. 7 lbs assorted components £3.60.  $3\frac{1}{2}$  lbs £1.95. List 15p. Refundable. Post 20p under £1. Insurance add 15p.

J.W.B. RADIO 2 Barnfield Crescent, Sale, Cheshire M33 1NL

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., 103 South Brink, Wishech, Cambs, 0945-4188. Immediate settlement.

TUNBRIDGE WELLS COMPONENTS, Ballard's, 108 Camden Road, Tunbridge Wells, Phone 31803, No Lists, Enquiries S.A.E.

BRAND NEW COMPONENTS BY RETURN BIGHAND NEW COMPONENTS BY RELOWN
Electrolytic Capacitors 16V, 25V, 50V, 0.47, 1.0, 2.2, 4.7, & 10 mfds. — 5p. 22, 47—5‡p. (50V—6p). 100—7p. (50V—8p). 220—8p. (50V—10p). 470—11p. (50V—16p). 1000/15V—15p. 1000/25V—18p. 1000/40V—35p. 
 Subministure
 bead
 tantalum
 electrolytics

 0·1
 0·22
 0·47
 1·0
 @ 35V
 4·7
 @ 6.3V—8p

 2·2/35V
 8·4·7/2·5V—9p
 10/25V
 15/16V—12p

 22/16V
 33/10V
 47/6V
 68
 8·100
 @ 3V—14p
 Mullard Miniature Ceramic E12 Series 63V 2% 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p. Vertical Mounting Ceramic Plate Caps. 50V. E12 22 pf.—1000 pf. E6 1500 pf.—47000 pf.—2p. Polystyrene E12 Series 63V. Hor. Mounting. 10 pl. to 1000 pf.—3p. 1200 pf. to 10000 pf.—4p. 

NICAD RECHARGEABLE CELLS, replacement sizes for penlite (AA size) ¥1.20, U11 (1.8AH) £1.85, U2 (4AH) £2.25, P&P 16p per cell, CWO to A. FRIDAY, 27 Batteries Close, Lynstead, Sittingbourne, Kent. (Postal Only).

127, Chesterfield Road, Sheffield S8 ORN

NEW COMPONENTS, C.MOS, TTL, Transistors, regulators etc. At give away prices,  $16K \times 1$  Dynamic Ram, \$10,00,741 10p, 7805 50p, Send 25p + SAE for comprehensive list, I. F. Soler, 34 Portland Road, Ashford, Middlesex, TW15 3BT.

## SMALL A

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.60 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

#### CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertise-ment rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.

2. The publishers reserve the right to refuse or withdraw any advertisement.

3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

#### **SERVICE SHEETS**

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo etc. With free Fault-finding guide, from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc. 75p plus S.A.E. Colour TV Service Manuals on request, S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

#### FOR SALE

M.E.: \$53, Organ, Built P.C.B's, Pedals, Pair 49 Note Keyboards, Stops, Case, etc. Also P.W. Rhythm Generator, Telephone: Christchurch 78339.

6800 D2 256 RAM. Full bus buffering, with PSU and extras, £235. Tel, Oakley 2867. Mr. P. WATSON.

#### COLOUR MODULATOR

FOR ALL TV GAMES!

• Red., Green & Blue inputs • Switchable background colours • FREE Interface details for Tank battles – Uffelike effects

WILLIAM STUART SYSTEMS

137. Billericay Road Herongate Brentwood Essex (M13 3SD

Tel: 0277 810244 Barclay Card Access Accepted

"RUN YOUR OWN BUSINESS AS AN EXTRA HOME ACTIVITY. LARGE PROFITS. A GENUINE OPPORTUNITY TO SUCCESS." Full details on receipt of s.a.e. Industrial Supplies. 102 Parrswood Road, Withing-

NEW BACK ISSUES of "PRACTICAL ELECTRONICS" available 65p each Post Free, Open P.O./Cheque returned if not in stock – Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks, Tel. (0423) 55885.

FOR SALE: Lavoie 265A Oscilloscope. Offer to Box No. 77.

PET 2001 Personal computer with 8K Ram, little used and for sale because Company must expand to a much bigger system. Offers over £100. Tel: (0291) 690484.

SEEN MY CAT? 5000 Odds and ends. Mechanical Electrical. Cat free, Whiston, Dept. PRE, New Mills, Stockport.

#### SPECIAL OFFER HATFIELD INSTRUMENTS LABORATORY POWER SUPPLY **UNITS TYPE 6130**

0-30V 0-1A

Continuously Variable and Metered

ONLY **£38.00** PLUS VAT (£3.04)

#### HATFIELD INSTRUMENTS **LIMITED**

**BURRINGTON WAY PLYMOUTH PL5 3LZ** TEL: (0752) 772773

MOTOROLA 6800 D2. Assembled. As mint. Extra memory and 5u. P.S.U. £120.00. Phone: 021-559 4554.

**ELECTRONIC KITS-SAE** for new catalogue, and clearance list of obsolete kits. AMTRON U.K. 7 Hughenden Road, Hastings, Sx.

#### **LADDERS**

LADDERS. Varnished 254ft. Extd. £34.56, Carr. £2.70. Leaflet. Callers welcome. Open Sat. Ladder Centre, (PEE4) Halesfield (1) Telford, Salop. Tel: 586644.

#### **EDUCATIONAL**

#### COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Foll details from:

> ICS SCHOOL OF ELECTRONICS Dept. B272 Intertext House, London SW841 J Tel. 01-622 9911 (all hours) State if under 18

#### **TECHNICAL TRAINING**

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing. Electronics, Computers: also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS Dept. B272 Intertext House, London SW84LJ Tel. 01-622 9911 (all hours) State if under 18

#### CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS Dept. B272 Intertext Flouse, London SW8 4U J Tel. 01-622 9911 (all hours) State if under 18

#### **BOOKS AND PUBLICATIONS**

COMPREHENSIVE TV REPAIR INSTRUCTIONS for your set T.V./other publications AUSE (PE) 76, Church Street, Larkhall, Lanarkshire ML9 1 HE.

#### RECORD ACCESSORIES

STYLI for Hi-Fi, Music Centres, 111, List free for s.a.e, Also cartridges, leads, accessories details, Felstead Electronics (PE) Longley Lane, Gatley, Cheadle, Ches. SK8 4EE.

#### **MISCELLANEOUS**

#### 100 WATT GUITAR/PA/MUSIC **AMPLIFIER**

With superb treble, bass. Overdrive, slimline, 12 months guarantee. Unbeatable offer at £39. Also twin channel with separate treble/bass per channel £48. Money returned if not absolutely delighted within 7 days. Also fuzz boxes great sound robust construction £6.80. Also 100 watt 12 in. speakers £22.50.

All inclusive of P.P. Send cheque or P.O. to: WILLIAMSON AMPLIFICATION 62, THORNCLIFFE AVENUE, DUKINFIELD, CHESHIRE. TEL: 061-344 5007

SUPERB INSTRUMENT CASES BY BAZELLI, manufactured from P.V.C. faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 50p, chassis punching facilities at very competitive prices, 400 models to choose from, free literature (stamp would be appreciated). BAZELLI, Dept. No. 23, St. Wilfred's, Foundry Lang Haltun Langster, LA2 6LT. Lane. Halton. Lancaster. LA2 6LT.

PRINTED CIRCUIT BOARDS made to your requirements, write for details and price list. Western Circuit Designs, 31 Great Hinton, Trowbridge, Wilts. BA14 6BY.



#### **RADIO** CONTROL **SPECIALISTS**

Kits for multi channel systems. Special parts and accessories.

S.A.E. FOR LEAFLETS Tel: 0602 395418

MICRON R/C, Hayworth Road, Sandiacre, Nottingham.

#### THE FABULOUS **D2 MICROPROCESSOR EVALUATION KIT** FROM MOTOROLA.

Featuring \*24 key keyboard \*Seven segment display \*Cassette interface \*Erom & Ram Expandable \*Interface Capability \*Full Documentation \*5 Volt power supply Required \*One years FREE membership of The Amateur Computer Club with every purchase\*. £176 + £1,50 P & P + 8% VAT.

#### **ENAMELLED COPPER WIRE**

SWG	l lb	8 oz	4 oz	2 oz
10-19	2.60	1.40	.66	.55
20-29	2.80	1.60	.85	.65
30-34	3,00	1,70	.95	.70
35-40	3,35	1,90	1.10	.79
40-43	4.50	2.50	1.90	1.25
44-46	5,00	3.00	2.10	1.65
47	8.00	5.00	3.00	1.76
48	15.00	9.00	6.00	3.30

Tinned Copper, Even Gauges 14-30 £3 per lb. Multicore 60/40 Solder 18SWG £3.24 per lb. Prices include P & P and VAT. SAE brings list of copper and resistance Wires.

## THE SCIENTIFIC

## WIRE COMPANY

PO Box 30 London E.4. Reg. Office, 22 Coningsby Gdns

#### **LOSING RADIO 4?**

NEW! 200 KHz to Med. Wave Converter, inductive (place near receiver) and coax outputs, £9-70.

TIME? MSF 60 KHz Receiver, built-in antenna, £13-70 or with parts (no case or pcb) for sequential YEAR, MONTH, DATE, DAY, HOURS, MINUTES, SECONDS display £24-40.

PROGRAM YOUR OWN tunes on a MUSICAL DOORBELL, change it each day, just needs bell transformer and speaker, only £19-50.

Each easy-assembly kit includes all parts, printed circuit.

case, postage etc, instructions and money back assurance so SEND off NOW.

#### **CAMBRIDGE KITS**

45 (FM) Old School Lane, Milton, Cambridge.

COMPUTER HOBBIST. Components at lowest prices. Write for free price list, stating your specific interests. PACS, 12 Alma Road, Monkstown, Co. Dublin, Ireland.

#### NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £9.75 plus 25p P & P

P. & P.

'Brain-Freeze' 'em with a MINI-STROBE
Kit, pocket-sized 'lightning flashes', vari-speed,
for discos and parties. A mere £4:30 plus 20p
P. & P. Experiment with a psychedelic
DREAM LAB, or pick up faint speech/sounds
with the BIG EAR sound-catcher; ready-made
multi-function modules. £5 each plus 20p
P. & P. P. & P

LOTS MORE! Send 20p for lists. Prices include VAT. (Mail order U.K. only).

#### **BOFFIN PROJECTS**

Cunliffe Road, Stoneleigh Ewell, Surrey (P.E.)

GLASS FIBBE P.C.B's Drilled Tinned 15p square 20p postage.\* Send your master to H.T.E., 50 M field Avenue, Elgin, Morayshire. \*Same Day Service.

#### **PRINTED CIRCUITS** and HARDWARE

Readily available supplies of Constructors' hardware. Printed circuit boards, top quality for individual designs. Prompt service. Send 25p for catalogue. From:

#### RAMAR CONSTRUCTOR SERVICES,

Masons Road, Stratford upon Avon, Warwicks. Tel. 4879.

#### PRACTICAL ELECTRONICS P.C.B.'s in glass fibre tinned and drilled

in glass fibre tinned and drilled
Dec. 77 Car Burglar Alarm 1412-1 88p,
May 78 Moving Light Display £2.96.
May 78 Chorus Generator £2.55.
July 78 Dimwit £1.78.
Aug 78 Touch Switch 85p,
Aug 78 Dight Performance Power Supply £2.38.
Oct. 78 High Performance Power Supply £2.38.
Oct. 78 Haple Performance Power Supply £2.38.
For full list and current boards please send S.A.E.
P.C.B.'s also produced from customer's own master –
please send for quote. C.W.O. Please.

METAL DETECTOR. INDUCTION BALANCE £29.50
Please send S.A.E for descriptive leaflet.

#### PRDTO DESIGN

14 Downham Road, Ramsden Heath, Billericay, Essex CM11 1PU

MORSE CODE TUITION AIDS
Cassette A: 1–12 w.p.m. for amateur radio examination.
Cassette B: 12–24 w.p.m. for professional examination pre-

paration.
Morse by light system available. Morse Key and Buzzer unit for sending practice.
Prices each cassette (including booklets) £4.50. Morse Key and Buzzer £4.50.
Prices include postage etc., Overseas Airmail £1.50 extra.

MHEL ELECTRONICS (Dept. PE) 12 Langshore Way, Milton, Portsmouth P04 8LS.



Videograph II links to the aerial socket of your tv and provides a full colour oscilloscope display! A must for hi-fi, home entertainment, discos, organs etc.

New - signal invert control, integral square wave generator. Plus - full details for testing your audio system for transient distortion, crosstalk etc.

Complete **619.95** Luxury cabinet and Kit only controls. £9-95

NC. POST, PACKING, VAT. READY BUILT VIDEOGRAPH £59.95

VILLIAN
STUART
SYSTEMS Ltd

Dower House, Billericay Road.
Herongate, Brentwood,
Essex CM13 3SD
Telephone. Brentwood (0277) 810244

#### TRANSISTORISED IGNITION KIT

\*£4.86 incl. carr & VAT\*

Complete pock of parts with p.c.b. to build our transistorised ignition system based on Dartington Power Transistors specially developed for auto ignition.

Send S.A.E. for FREE CIRCUIT diagram

All components with p.c.b. (less cose) £4.86 SOLEC PRODUCTS, 68 Dale Street, Monchester, M1 2HS

FIFTEEN CMOS PROJECTS -Electronic Maze; 70 m.p.h. Alarm, etc. FIFTEEN detailed circuits PLUS 14-pin socket, kits VOUCHERS, - all just £1 from DAVID IAN DESIGNS, 47 Hampton Court Parade, East Molesey, Surrey.

#### CABINET FITTINGS

FOR Stage Loudspeakers and Amplifier Cabs Fretcloths, Coverings, Strop & Recess Hondles, Feet, Costors, Jacks & Sockets, Connons, Bulgin B woys, Reverb Trays, Locks & Hinges, Corners, Trim, Specker Bolts etc. Send 2 × 9p Stamps for samples and illustrated catalogue.

ADAM HALL (P.E. SUPPLIES)
Unit 3, Carlton Court, Grainger Road
Southend-on-Sea, Essex.

#### SINTEL FOR BOOKS, CMOS AND COMPONENTS

6800 Booklet 1.80, MOT CMOS Databk 3.50, 6800 Appl Mon 12.95, 6800 Prog Man 5.35, SC/MP Introkit Man 0.75 NS TTL Databk 2.10, RCA CMOS Databk 5.45, 8085 User's Man 5.15, 280 Ass Long Prog Mon 7.50, 280 CPU Man 5.60, 280 CTC Spec 0.80, 280 PIO Mon 3.30, Also of full range of CMOS send for free catalogue MPUs: MEK6800D2 205.20, MC6820 7.50, 280 18.14, 280A 24.19, 280CTC 10.96, 280PIO 10.96, Memories 2102-A 2.00, 2112A 4 3.13, Displays: Type FND500 CC 1.40, Type TIL321 CA 1.40, 51COT 5.29, Crystolis: 32768KHz 3.19, Clack ICs: AY51202 3.35, AY51224 3.73, MK50253 5.83, Soldercon Pins: 100 0.54, 1000 4.32, 3000 11.34. Free catalogue by return. All dems CWO Prices inclusive of VAT, Add 35p p&p SINTEL, P.O. Box 75B, Chopel Street, Oxford, Tel. (0865) 49791.

ELECTRONIC KITS MOTOROLA POSITIVE VOLTAGE REGULATORS - 1 amp MC 7805 ... 95p MC 7812 ... 95p MC 7806 ... 95p MC 7815 ... 95p MC 7808 ... 95p MC 7818 ... 95p NOTE ALL PRICES INCLUDE V.A.T.
TERMS – C.W.O. Cheques and P.O. payable Furama Electronics P&P 25p. Callers welcome. FURAMA ELECTRONICS
PORCESTOR Yorkshire DN1 1ES

## RECHARGEABLE BATTERIES

#### TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. SAE FOR LISTS. £1.00 for Booklet "Nickel Cadmium Power". Write or call: 2 Union Drive. BOLDMERE. SUTTON COLDFIELD. WEST MIDLANDS. 021 354 9764, or see them at TLC. 32 Craven Street, Charing Cross, London WC2.

#### NICKEL CADMIUM BATTERIES

RIUKEL CADMIUM BATTERIES

Rechargeable and suitable for 'fast charge' HP 7 (AA)

Ret.1.13, SUB C £1.47, HP 11 (C) £2.15, HP 2 (D)

£3.27, PP3 £4.09, PP3 charger £5.81. All above

Nickel Cadmium batteries are guaranteed 'EVER READY'

full spec, and are supplied complete with solder tags (except

PP3). Just in stock — New rechargeable sealed lead acid

maintenance free batteries suitable for burglar alarms etc.

1,2 amp hr. 6v £4.40, 2.6 amp hr. 6v £5.65.

Quantity prices available on request. Data and charging

circuits free on request with orders over £10 otherwise 30p

post and handling (specify battery type), all prices include

VAT. Please add 10% P&P on orders under £10. 5% over

£10.

Cheques, postal orders, mail order to.

SOLID STATE SECURITY
DEPT PE, 10 BRADSHAW LANE,
PARBOLD, WIGAN, LANCS. 02575-4726.




#### MAKE YOUR OWN PRINTED CIRCUITS

Etch Resist Transfers – Starter pack [5 sheets, lines, pads, I.C. pads] £1.40. Large range of single sheets in stock at 29 pper sheet.

Ferric Chloride – Ilb bags 80p (P&P 50p)\*

Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. Full instructions supplied. 2 sheets [20 x 25cm] negative paper and 2 sheets [18 x 24cm) positive film £1.20. S.A.E. lists and information. P&P 20p/order except\*

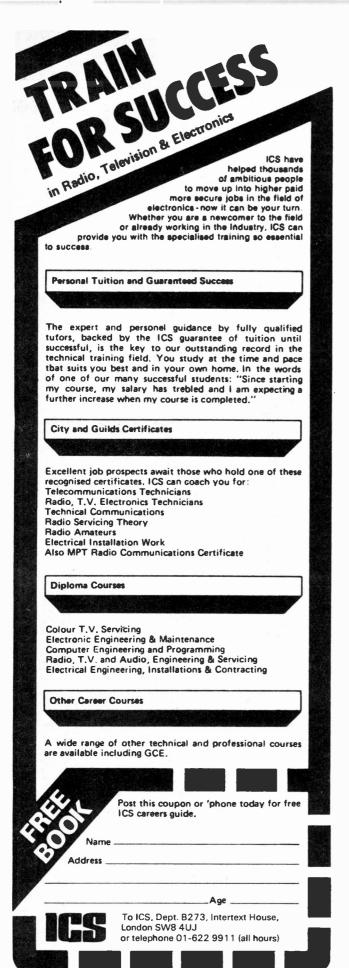P.K.G. ELECTRONICS OAK LODGE, TANSLEY, DERBYSHIRE



# GLOUCESTER INDUSTRIAL SALES AND AUCTIONS LIMITED

Eastington Trading Estate, Nr. Stonehouse, Glos.
Tel: Stonehouse 4118

(M.5 Motorway - Exit No. 13)

We hold regular monthly auction sales of mostly new electronic and electrical goods consisting of transistors, triacs, integrated circuits, diodes, capacitors and resistors, together with fractional motors, transformers, power packs, etc., etc.

Phone or write to be put on our auction mailing list.

Why not get in touch with our Mr. Jack Bailey and enquire about our terms for the disposal of your surplus stocks, etc., through our auctions.

SINCLAIR PRODUCTS\*
Microvision TV £172. PDM35 £27-25.
Misrovision TV £172. PDM35 £27-25.
Mains adaptor £3-24. Case £3-25. DM235 £47-50. Rechargeable battery units £7-95.
Adaptor/charger £3-70. Case £8-50. Cambridge prog calculator £13-15. Prog library £2-95. Mains adaptor £3-20. Enterprise programmable calculator £20-95.

S-DEC\$ AND T-DECS\*
S-DeC £3-39. T-DeC £4-44. u-DeCA £4-52. u-DeCB £6-73. 16 dil adaptors £2-14.

TV GAMES
Send sae for data. AY-3-8500 + kit £8-95.
Tank battles:- chip £6-90, kit £7-05. Stunt cycle:- chip £6-90, kit £7-60. AY-3-8600 + kit £12-50. Rifle kit £4-95.

kit £12-50. Rifle kit £4-95.

MAINS TRANSFORMERS
6-0-6V 100ma 79p, 1\(\frac{1}{2}\) a £2-35. 6.3V 1\(\frac{1}{2}\) a £1-89. 9-0-9V 75ma 79p, 1a £1-99. 2a £2-60. 12-0-12V 50ma 79p, 100ma 90p, 1a £2-49. 13V \(\frac{1}{2}\) a 95p.

BATTERY ELIMINATORS
3-way model 6/7½/9V 300ma £2-95.
100ma radio models with press-stud connectors 9V £3-35, 6V £3-35, 9 + 9V £4-50.

SWANLEY ELECTRONICS
Dept. PE, 32 Goldsel Road, Swanley, Kent.
Postage 30p extra. Prices include VAT.

CONTINENTAL SPECIALITIES\*
EXP300 £6-21. EXP350 £3-40. EXP650
£3-89. EXP84 £2-48. P86 £9-94.
JC12, JC20 AND JC40 AMPLIFIERS
A range of integrated circuit audio amplifiers with free date and printed circuits. JC12 £6
watts £1-60. JC20 10 watts £2-95. JC40
20 watts £3-95. Send sae for data.

PRINTED CIRCUIT MATERIALS
50 sq ins pcb 40p. 1 lb FeCl £1-05. Dalo pen
73p. taminate cutter 75p. Small drill 20p.

73p. Laminate cutter 7 bp. Small drill 20p. BATTERY ELIMINATOR KITS
Send sae for data. 100ma radio types with press stud connectors 44 V £1-80, 64 £1-80.
94 £1-80. 44 + 44 V £2-50. 6 + 64 €2-50.
9 + 94 £2-50. Stabilized 8-way types 3/44/6/74/9/12/15/18V 100ma £3-20.
Amp £6-40. Stabilized power kits 2-18V 100ma £3-60. 2-30V 1A £6-95. 2-30V 2A £10-95. Car convertor input 12V dc output 6-7½/9V 1A stabilized £1-95.

6-7½/9V 1A stabilized £1-95.

COMPONENTS (send for full list)
1N4148 1.4p. 741 15p. Plastic equivs
BC107, BC109, BCY22 47p, BCY21 4.9p.

W resistors £12 10R to 10M 0.9p. 16V
electrobytics 47, 1.25, 10,22mf 5p. 100mf
6p. 1000mf 10p. Polyesters 250V, 015,
068, 1mf 1pb. Ceramics 50V £6 22pf to
33n 1.7p. Polystyrenes 63V £12 15pf to 10n
2.5p. Zeners 400mw £24 2V7 to 33V 6.1p.
Presets 0.1W 100 to 4M7 6.8p.

# FOR YOUR GUIDANCE VALUE ADDED TAX

Unless otherwise shown, all prices in advertisements are inclusive of VAT. Where prices are exclusive, readers should ensure that they have added the correct amount of VAT before ordering.

Export orders are not subject to the addition of Value Added Tax.

#### U.K. RETURN OF POST MAIL ORDER SERVICE also WORLDWIDE EXPORT SERVICE



This kit is suitable for record players, tape play back, guitars, electronic instruments or small P.A. systems. Two versions are available. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors. Both kits have printed front panel and volume, bass and treble controls Spec. 10M output into 8 ohms. 7M into 15 ohms. Response 20c/s to 30kc/s, input 100M.V. high imp. Size  $9\frac{1}{2} \times 3 \times 2$  in, A/C mains operated.

••• £12.50

Stereo £20 post

Easy to build. Full instructions supplied



#### **ELAC SPEAKER** 10 inch

Large ceramic magnet 50-16,000 c/s. Bass resonance 55 c/s. 10W. 16 or 8 ohm impedance.


RCS STEREO PRE-AMP KIT. All parts to build this pre-amp. Inputs for high, medium or low imp. per channel, with volume Inputs for high, medium or low imp. po control and P.C. Board. Can be ganged to make multi-way mixers

MAINS TRANSFORMERS ALL POST	75p each
250-0-250V 70mA, 6 3, 2A	€3 - 45
250-0-250 80mA, 6 3V 3 5A, 6 3V 1A or 5V 2A	£4-60
350-0-350 80mA, 6 3V 3 5A, 6 3V 1A or 5V 2A	£5 · 80
300-0-300 120mA 2 × 6 3V 2A C.T. 6 3V 2A	£8 ⋅ 50
220V 45mA, 6 3V 2A	£1 · 75
HEATER TRANS, 6 3V 3A, £1-45. ; amp.	£1 · 00
GENERAL PURPOSE LOW VOLTAGE Tapped outputs	at
2A 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V	£5 ⋅ 30
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£5 · 30
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£8 ⋅ 50
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£11-00
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£14·50
5, 8, 10, 16V JA £2, 12V 100mA £1, 12V 300mA £1.	

12V 750mA £1.30. 40V 2A tapped 10V or 30V £2.95. 10-0-10V. 2A £2.50. 40V 2A £2.95. 30V 5A 34V 2A ct. £3.75. 2× 18V 6A £9.12-0-12V 2 amp £9.95. 25-0-25V 2 amp £4. 20-0-20V 1A £2.95. 30V 14 £2.75. 20V 1A £2.20. 9V 3 amp £2.75. 60V 40V. 20V or 20-0-20V, 1A £3.50. 30-30 2A £7. 9V 250mA £1.30. 30V 2 amp £3. AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £5.25W £6. 400W £7.500W £5.25W £6.400W £7.500W £6.25W FÜLL WAVE BRIDGE CHARGER RECTIFIERS. 6 or 12V outputs 11/2 55p; 4A £1-25. HALF WAVE 12V 11/2 25p.
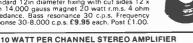
#### GOODMAN'S COMPACT RUBBER **SURROUND BASS WOOFER**

Standard 12in diameter fixing with cut sides 12 x 10in 14,000 gauss magnet 20 watt r.m.s. 4 ohm impedance. Bass resonance 30 c.p.s. Frequency response 30-8,000 c.p.s. £9.95 each. Post £1.00.



Ready made in chassis form. Mains operated. Volume balance, treble and bass slider controls Pick up and tape inputs. Recording output. Socket.

Front panel size: 16½ x 1½in.
Chassis size: 13 x 15in.
Bargain **£18.50** Post 50p Made by Rank.

## HEATING ELEMENTS WAFER THIN Size 10; +8; +4in Operating voltage 200 250v a c 250w approx Suitable for Heating Pads Food Warmers. Convector Heaters etc. Must be clamped between two sheets of metal or asbestos ONLY 40D FACH (FOLIR FOR CL.SA)

ONLY 40p EACH (FOUR FOR £1-50) ALL POST PAID—Discounts for quantity

#### **E.M.I.** $13\frac{1}{2} \times 8in$ SPEAKER SALE!

10W Model £7.95 15W model £10·50 Post 65p

20W model £11.50 Post 75p State 8 or 15 ohms

TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A" 20 x 13 x 12in. For 12in. dia. or 10in. speaker. Illustrated £14.50 Post £1.60 Illustrated £14.50 roots MODEL "B" BOOKSHELF For 13 × 8in. EMI £8.50 Post £1

R.C.S. BOOKSHELF complete with speakers. Size 14 x 9 x 6in. approx.

Response 50 to 14,000 cps
12 watt rms 8 ohms £19 pair Post £1.50
ACOUSTIC WADDING 18in. wide, 20p ft.

#### MONO PRE-AMPLIFIER

A mains operated solid state pre-amplifier unit designed A mains operated solid state pre-amplifier unit designed to compliment amplifiers without low level phono and tape input stages. This free standing cabinet incorporates circuitry for automatic R.I.A.A. equalisation on magnetic phono input and N.A.B. equalisation for tape heads. Power ON/OFF, PHONO/TAPE switches and pilot lamp are on the front panel; phono socket

input and output are rear post and output are 10a. ocated. AC mains 240V. fize 6 x 31 x 2in. Post 50p. Size 6 x 31 x 2in.

£4 50 ea. - 2 for £8.



#### BAKER MAJOR 12 INCH £16.88

Post £1 00



30-14,500 c/s 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 25W NOTE 4 or 8 or 16 ohms available

£12.96

£15.12

£22.68

baker,...

0

Module kit, 30–17,000 c/s with tweeter, crossover, baffle, 19  $\times$  12 in, instructions. As illustrated. £20.52 Please state 4 or 6 or 16 ohms Post £1 60

#### "BIG SOUND" **BAKER SPEAKERS**

Robustly constructed to stand up to long periods of electronic power. As used by leading groups and discos. Useful response. 30–13,000 c.s. Bass Resonance 55 c/s.

**GROUP "25"** 

12in 30W 4, 8 or 16 ohms

**GROUP "35"** 12in 40W 4, 8 or 16 ohms

GROUP 50/12in

2in 60W or 8 or 16 ohms with luminium presence dome

GROUP 50/15in

15in 75W 8 or 16 ohms £36.72 With aluminium presence dome. Post £1:60 Disco, Group - PA Cabinets in stock. Send for Leaflet. Cabinet Fittings, Handles. Corners, Feet, Covering Material all in stock.

**BAKER 150 WATT ALL PURPOSE TRANSISTOR AMPLIFIER** 

Ideal for Groups Disco P.A and Musical Instruments 4 inputs speech and music 4 way mixing. Output 4/8/16 ohm. ac. (Mains 240V. Separate treble and bass controls. \$150 of £150 Ovolt line model £14 extra.

#### **BAKER 50 WATT AMPLIFIER**

Two inputs with volume controls. Master treble, bass and volume controls. Takes all impedance loudspeakers

£59 Post £1. £59 Post £1.

R.C.S. SOUND TO LIGHT DISPLAY MK II Complete kit of parts with R.C.S. printed circuit. Three 1000W channels. Will operate from 200mV signal source. CABINET extra £4.

**GOODMANS CONE TWEETER** Price £3.25

3 WAY CROSSOVER WITH TREBLE & MID RANGE CONTROLS. 50 WATT. £5 POST £1.

#### R.C.S. 100 WATT VALVE **AMPLIFIER CHASSIS**



Professional model Four inputs Treble, Bass, Master Volume Controls Ideal disco. P.A. or groups S.A.E. for £99 details 5 speaker outputs. 3 or 8 or 15 ohm order Suitable carrying case £16-50.

LOW VOLTAGE ELECTROLYTICS
1 2 4 5 8 16 25 30 50 100 200mF 15V 10p. 500mF 12V 15p.
25V 20p; 50V 30p. 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p. 2500mF 50V 62p; 3000mF 25V 47p;
50V 65p. 3800mF 100V 11-60. 4700mF 63V £1-20. 5000mF 6V 25p;
12V 42p; 25V 75p; 35V 85p; 5600mF 76V £1.60; 1200/76V 80p.

#### HIGH VOLTAGE ELECTROLYTICS

	nun	VOLIAGE	E C	HOLTIICS	
		8+8/450V	50p	50+50/300V	50p
		8+16/450V	50p	32+32/450V	75
		16+16/450V	50p	100+100/275V	65p
50/350V	50p	32+32/350V	50p		
	8/350V 16/350V 32/500V	8/350V 22p 16/350V 30p 32/500V 75p 50/350V 50p	8/350V 22p 8+8/450V 16/350V 30p 8+16/450V 32/500V 75p 16+16/450V	8/350V 22p 8+8/450V 50p 16/350V 30p 8+16/450V 50p 32/500V 75p 16+16/450V 50p	16/350V <b>30</b> p 8+16/450V <b>50</b> p 32+32/450V 32/500V <b>75</b> p 16+16/450V <b>50</b> p 100+100/275V

**ROBUST BLACK PLASTIC BOX** 

Size 6½ x 3¾ x 2½n with brushed aluminium facia. Ideal for constructional projects.

#### R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS

All parts and instructions with Zener diode, printed circuit rectifiers and double wound mains transformer Input 200/240V ac Output voltages available 6 or 7 5 or 9 or 12V dc up to 100mA or less Size 3 < 2 y - 4 Jan Please state voltage required

£2.95

#### **ELECTRO MAGNETIC** PENDULUM MECHANISM

95p Post 30p

1 5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed ideal displays, teaching electromagnetism or for metronome, strobe etc.

#### **BSR AUTOCHANGER**

Plays 12in, 10in or 7in records Auto or Manual: A high quality unit backed by BSR reliability with 12 months guarantee a c 200/250V Size 13½ × 11<sub>7</sub>in Above motor board 3½in Below motor board 2½in

With STEREO/MONO CARTRIDGE £12.95 All Post 75p BSR P182 SINGLE PLAYER.
Snake Arm Flared Turntable (Ceramic Cartridge GARRARD AUTOCHANGER plays all records BSR P163 BELT DRIVE DECK, less cartridge GARRARD AP76 Single Player less cartridge

BSR DE LUXE AUTOCHANGER BSH DE LUXE AUTOCHANGER Features balanced arm. Cueing device, stylus pressure gauge, 3 speed – plays all size records. Fitted with stereo ceramic cartridge. Size: 13 - 12 ins. Post \$1.

with Sonotone V100 £21.50 magnetic cartridge



#### R.C.S. DISCO DECK SINGLE RECORD PLAYER

fitted with auto stop, stereo compatible cartridge. Baseplate. Size 1 × 8‡in. Turntable. Size 7in diameter a c. mains. 220.250V speeds plays all size records. £7.95 Two for £15, Post 75p.

## **HEAVY METAL PLINTHS**

With PVC Cover Cut out for most BSR or Garrard decks Silver grey finish Model A Size 12½ × 14½ × 7½ in Model B' Size 16 × 13½ × 7 in \$7.50.

Pust £1-50

Extra Large Plinth and Cover. For transcription decks. Size  $20 \times 17\frac{1}{2} \times 9$  in. uncut board. Shop callers only £18-50.

TINTED PLASTIC COVERS ONLY
Sizes: 14½ x 12½ x 4½ n. £3. 17½ x 14 x 4in. £4.50.
16½ x 14 x 4in. £4. 15½ x 13½ x 4in. £3.75.
15 x 13½ x 3in, £3.50. 17½ x 9½ x 3½in, £3.
14½ x 14½ x 2½in Rosewood sides £4.
Ideal for record decks, tape decks, etc. Post £1.

#### BAKER HI-FI SPEAKERS

HIGH QUALITY-BRITISH MADE "SUPERB"

12in 25 watt

Ouality loudspeaker low cone resonance ensures clear reproduction of the deepest bass. Special copper drive and concentric tweeter cone. Full range reproduction with remarkable efficiency in the upper register. Bass Resonance. 25 c.s. Flux Density. 16 500 gauss. Useful response. 20–17 000 c.s. 8 or 16 ohms models.

"AUDITORIUM" £22.68

12in 35 watt

A full range reproducer for high power Electric Guitars, public address, multi-speaker systems, electric organs ideal for Hi-Fi and Discotheques Bass Resonance 35 c/s Flux Density 15,000 gauss Useful response 25–16,000 c/s 8 or 16 ohms models

"AUDITORIUM" £34.50

15in 45 watt Post £1 60

BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 j.in. sides, 6 x 4in. 95p; 8 x 6in. £1.40; 10 x 7in. £1.55; 14 x 9in. £1.90; 16 x 6in. £1.85; 12 x 3in. £1.20; 16 x 10in. £2.20; 12 x 8in. £1.70. ALUMINIUM PANELS, 18 s.w.g. 6 x 4in. 24p; 8 x 6in. 38p; 10 x 7in. 54p; 12 x 5in. 50p; 12 x 8in. 70p; 16 x 6in. 70p; 14 x 9in. 94p; 12 x 12in. £1; 16 x 10in. £1.16. ALUMINIUM ANGLE BRACKET, 6 x 3 x 3in. 15p. ALUMINIUM BOXES, WAMY SIZES IN \$TOCK 4 x 2 x 2 x 2 in. 86p; 3 x 2 x 1in. 65p; 6 x 4 x 2 in. 95p; 8 x 6 x 3in. £1.50; 9 x 4 x 10 f. 170; 6 x 4 x 4 in £1.70; 6 x 4 x 6 f. 30

£1.50; 9 x 4 x 4in. £1.70; 6 x 4 x 4in. £1.30. THE "INSTANT" BULK TAPE ERASER £4.95

Suitable for cassettes, and all sizes of tape reels a c mains 200/240V Post Leaflet S A E 500 Head demagnetiser £4,75





TRANSFO ALL EX-STOCK—SAME D 12 OR 24 VOLT OR 12-0-12V PRIMARY 220-240 VOLTS Amps 111 05 025 2:20 0 45 111 0 5 0:25 6:40 0.78 111 0 5 0:25 6:40 0.78 111 0 5 0:25 6:40 0.78 112 1 3:51 0.78 113 4 2 4:03 0.96 114 1 2 4:03 0.96 115 1 3:51 0.96 116 8 4 7:42 1.14	ORMERS  AY DESPATCH. VAT 8%  30 VOLT RANGE  Prim 220/2/40V Sec 0-12-15-20-24-30V. Voltages available   3, 4'5, 6, 8   39, 10,  12. 15, 18, 20, 24, 30V or 12V-0-12V, 15V-0-15V. Ref. Amps £ P & P 112 0 5 2-64 0-78 79 1 0 3-57 0-96 20 3 0 6-20 1 14 21 4 0 7.99	238 200 3-0-3 2.57 0.55 212 1A, 1A 0-5, 0-6 2.85 0.78 13 100 9-0-9 2.14 0.38 235 330, 330 0-9, 0-9 1.99 0.38 207 500, 500 0-8-9-0-8-9 3.53 0.78 236 200, 200 0-15, 0-15 1.99 0.38 214 300, 300 0-26, 0-20 2.80 0.78 221 700 (DC) 20-12-0-12-20 3.41 0.78 205 1A, 1A 0-15-20-0-15-27 399 0.96 204 1A, 1A 0-15-27-0-15-27 3.99 0.96 239 50 12-0-12 2.57 0.38	2.5% Iw Resistors. 25W (AL	30) £3-75 60) £4-57 80) £7-15 50) £17-28 2 £1-30 80 £4-25 £6-70 £13-88 & P 35p res inset brass PC cards, flush 40 63p 40 63p 50 50 50 50 50 50 50 50 50 50 50 50 50 5
72 10 5 8.12 1 14 116 12 6 8.99 1 32 17 16 8 10.72 1 32 115 20 10 13.98 2 08 187 30 15 17.05 2 08 226 60 30 36.14 OA	51 50 9.87 1 32 117 6 0 11.17 1 45 88 8 0 14.95 1 64 89 10.0 17.25 1 84 Prim 220/240V Sec 0-24-30-40-48-60V.	DC-1000V AC-1000V DC-100mARes-150KD 1 1000Ω/V Bargain £614*P & P62p VAT 8% 120,000 ohm/V Multimeter, mirror scale. Range AC/DC to 1000V, DC currents to 250m, Resistance to 3 Megs. 5° x 3⅓° x 1⅓ £14.38 P5 £1.05 VAT 8%.	Resistance 0-6K-60K-60M-60M auto o/load protection £23-30	amic. Cartridge ng voltages 20-
50 VOLT RANGE   Prim 220/240V Sec 0-20-25-33-40-50V   Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V, 25V-0-25V   Ref	Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V or 24V-0-24V, or 30V-0-30V.  **Ref   Amps	TEST METERS U4315 Budget Meter 20KD/V DC 2K/V A 1000V AC/DC 2-5A AC/DC 500K res, in robus steel case and leads £15-85. AV08 £81-70 T7 169 incircuit transistic 4234-7 AV071 £33-50 tester £34-7 AV073 £44-20 DA116 digital £102-0 EM272 £53-70 Megger 8M7 Battery. Vec Megger P&P £1-15 VAT 8%. Full range of AVO's, Megger's and Cases.	20-240V). Spe C Sec. 0-36-48 twice. To give 36-0-36 48-0-48 72V or 92V. Special 36-0-36 50V. Special 36-0-36	00V line to 10W £2-95 66p 0-120V x 2 pr 240} Screen 0-0-9V 1 A
PRIM 120/240V SEC 120/240V CTTAPPED Ref VA (Walts) £ P & P & P 07* 20 4-40 0 79 149 60 6.70 0 96 150 100 7.61 1 14 151 200 11.16 1 50 152 250 13.28 1 84 153 350 16.43 1.84 154 500 20.47 2 15 155 750 29.06 OA 156 1000 37.20 OA	Ref VA (Wat(s)	ISOLATOR - Special Price 0-200-220-240V, 0-240V Centre Tap, 250V, Ref. 62 ELECTROSIL Metal oxide low noise resistors.  ELECTRONIC CONSTRUCTION KIT 10 projects (including electronic organ). N soldering needed £7 29. VAT 8% P & P 70p.	A S-DECS Solderless bread boarding S Dec 70 contacts £3:10 T Dec 208 contacts £4:50 U Dec 14 for I.C.s etc £4:50 Dec 18 for I.C.s etc £6:50 VAT 8% P A P 40P ANTEX SOLDERING IRONS 15W £3:75 Stand £1:52	0-110-120 Pri 240V
157 1500 51.38 OA 158 2000 61.81 OA 159 3000 86.86 OA *Please specify 115 or 240V required HIGH VOLTAGE ISOLATORS Prim 200/220V or 400/440V Sec 110/120V CT or 200/240 CT	57S 5000 0-10-115-200-220-240 88-50 0A  CASED AUTO TRANSFORMERS 240V cable in & 115V USA 2 pin outlet VA £ P & P Ref 15 4-96 0 96 113V 75 7-73 1-14 64W 150 10-01 1 14 4W 200 9-92 1-45 65W	PANEL METERS 2" 0-50µA 5-50 4" 0-50µA 6-70" 0-500µA 5-50 0-500µA 8-70 Carriat 0-1mA 5-50 0-1mA 8-40 65p 0-30V 8-50 0-30V 8-40 VAT 8" VU Ind Panel 90mm 250µa £3-36	25W £3.95 + 12½% VAT P A P A P P A P P A P P A P P A P P A P P P A P P P A P P P A P P P A P P A P P A P P A P P A P P A P P A P P A P P A P P A P P P	0-240 15- 2A £1-50 .70p. 80 240-240 er 200VA
Va         Ref         £         P & P           60         243         6.70         1.32           350         247         16.43         1.84           1000         250         37.10         OA           2000         252         61.81         OA	250 10.49 1.45 69W 500 19.17 1.64 67W 750 23.41 1.76 83W 1000 27.88 0A 84W 11500 26.02 0A 33W 2000 49.97 0A 95W Torous to list. Please call (open 9am-5pm Mon-	C60 30p P. & P. 15p C90 42p P. & P. 15p VAT 8%.	Barrie Electronics  TELEPHONE: 01-488 3316/7/  AREST TUBE STATIONS: ALDGATE & LIVE	N 1BJ 8

IND	EX	TO	AD	VER	TISE	ERS
-----	----	----	----	-----	------	-----

ce Mailtronix Ltd1226	Fladar1286	Radio Component Specialists129
dam Hall (P.E. Supplies)1293	Flairline Supplies1288	Ramar Constructor Service129
hitken Bros1274	Fotherby Willis1224	R.S.T. Valve Mail Order124
Alben Engineering1212	Furama Electronics1292	Radio & T.V. Components125
Alcon Instruments Ltd1226		,
Arrow Fasteners1290	G.I.S.A.L. (Gloucester Industrial Sales &	
Astra-Pak1218	Auctions Ltd)1294	Saxon Entertainments 1216, 121
(3(10-) 0K	Goddards Components1224	Scientific Wire Co129
	Greenweld Electronics1212	Sentinel Supply128
arrie Electronics1296	Greenweid Liectronics	Service Tradingcover
li-Pak 1220, 1221	Harversons1284	Sinclair124
lirkett J	Hatfield Instruments Ltd1292	Sintel Ltd
offin Projects1293	Heathkit Ltd1218	Solec Products
loss Industrial Mouldings 1214, 1215	Heathkit Ltd1216	Solid State Security129
rewster S & R1212	1001111	Southern Transformers125
Pritish National Radio &	I.C.S. Intertext	Special Products121
Electronics School1273, 1280	I.L.P. Electronics1291	Squire, Roger124
Electronics School 1273, 1280		Stirling Sound125
	J.W.B. Radio1292	
Cambridge Kits1293		Sugden A. R. & Co
Cambridge Learning1289	Labgear Ltd1274	Swanley Electronics129
Calscope (Scopex)1279	Lektrokit1283	
Canon Components1288		
harcroft1290	Mantec Ltd1282	T.L.C129
hromatronics1290	Maplin Electronic Supplies cover iv	Technomatic Ltd122
lef Products1284	Marshall A. (London) Ltd1285	Teleplay (Logic Leisure) cover
odespeed1284	MHEL Electronics1293	Tempus128
rescent Radio Ltd1244	Micron R/C1293	T.K. Electronics122
rimson Elektrik1288	Mill Hill Supplies1280	Trampus Electronics128
.R. Supply Co1292	Minikits Electronics1293	T.U.A.C128
Оприу объементи и дога	Modern Book Co1256	
avian Electronics1210	O.K. Machine & Tool (UK) Ltd1280	Videotime Products127
elta Distributors1256		
	P.K.G. Electronics1293	
.D.A1282	Phoenix1286	Watford Electronics121
agle International1211	Phonosonics	William Stuart Systems 1292, 129
lectroni-Kit Ltd1223	Progressive Radio1217	Williamson Amplification129
lectrovalue Ltd1219	Proto Design1293	Wilmslow Audio121

## RELAYS SIEMENS, PLESSEY, etc.

RELAYS, WIDE RANGE OF A.C. and D.C. RELAYS AVAILABLE from stock, phone or write in your enquiries

#### FT3 NEON FLASH TUBE

High intensity multi turn high voltage, neon glow discharge flash tube. Design for gnition timing, etc. 11-50. P. & P. 25p. (t1-89 inc. VAT.) 3 for £3. P. & P. 50p. (£3.78 inc. VAT. & P.)

#### RODENE UNISET TYPE 71 TIMER

0-60 sec. 230V a.c. operation. Incorporating a lapsed time indicator and repeat facilities. A precision motorised timer ideal for process timing, photography, welding, mixing, etc. Price £6 P. & P. 60P.



N.M.S

WHY PAY MORE?
MULTI RANGE METER Type MF15A a.c. d.c. volts 10 - 50 - 250 - 500 - 1000 Ma 0 - 5 0 - 10 0 - 100 Sensitivity 2000V - 24 range, diameter 133 by 93 by 46mm including test leads. Price £7-00 plus 50p P. & P. (£8-10 inc. VAT & P.)



#### METERS (New) - 90 mm DIAMETER

A.C. Amp., Type 6272, 0-1A, 0-5A, 0-15A, 0-20A, A.C. Volt. 0-15V, 0-300V, D.C. Amp., Type 65C5, 0-2A, 0-10A, 0-20A, D.C. Volt. 0-15V, 0-30V, All Types 63.50 ea. + P. & P. 50p. (£4.32 incl VAT), except 0-100A, D.C. price £500 - 50p. P. & P. (£5.94 incl. VAT)





#### MINIATURE UNISELECTOR

12 volt. 11-way, 4 bank (3 non-bridging, 1 homing), £2:50. P. & P. 35p (£3:08 inc. VAT & P.), N.M.S.

#### 600 WATT DIMMER SWITCH



Easily fitted. Fully guaranteed by makers. Will control up to 600W of lighting except fluorescent at mains voltage. Complete, with simple instructions £3.95, post 25p (£4.53 inc. VAT & P. 1.000 wait model £5.60, post 25p (£6.32 inc. VAT & P.). 2.000 wait model £7.5, post 40p (£10.96 inc. VAT & P.).

#### MICRO SWITCHES

Sub min Honeywell roller m/s type 3115m 906t.

10 for £2.50 post paid LEVER OPERATED 20 amp. C/O. Mfg. by Unimax USA 10 for £4, P. & P. 50p (min. order 10) (£4.86 mc. VATI D P. C/O lever m/switch mfg. by Cherry Co. USA. Precious metal low resistance contacts. 10 for £2.25 P. & P. 30p. Total inc. VAT £3.02 (min. 10) Sub min lever m/switch type MML 46.10 for £2.50. N.M.S.

Post Paid £2.70 inclusive

#### MERCURY SWITCH

Size 27mm × 5mm, 10 for £5.00 (inc VAT £5.72) min quantity 10.



#### VORTEX BLOWER AND VACUUM UNIT

VORTEX BLOWER AND VACUUM UNIT

Dynamically balanced totally enclosed 9in rotor with max air
delivery of 1.5 cubic metres per
min Max static pressure 600mm

W.G. Suction or blow from 2 side
byside 37mm I.D. circular aperlures fitted to base of unit Powerful continuously rated 115V ac
motor mounted on alloy base with
fixing facilities Dimensions
length 22cm - width 25cm height 25cm These units are ex equipment but have hi
minimum use Fully tested prior to despatch Price 112
11 50 P. & P. (£1.458 inc. VAT. & P.)
Suitable transformer for 230 240V ac. £6 - £1.2 & P. & P. (£7.4)



Suitable transformer for 230 240V a.c. £6 - £1 P. & P. j£7 56 inc. VAT & P. j

#### CENTRIFUGAL BLOWER Smith type FFB

1606 022 220/240V A.C. Aperture 10 x 4⅓cm overall size 16 x 14cm. Price £3 75 P. & P. 75p. (inc. VAT £4.86). Other types available. S.A.E. for details



240 volt. D.C. BLOWER UNIT MFR

Precision 24 volt. D.C. -8 amp Blower Heat that works well on 12V -4 amp D.C. Producing 30 cu.st. min at normal air pressure. £4-50 P. & P. 75p (inc. VAT £5-61), N.M.S.

## INSULATION TESTERS NEW!

Test to I.E. Spec. Rugged metal construction is suitable for bench or field aurk constant speed dutch Sire. L. 8in With H 6in weight 6ib. 500V 500 megohms. £48. Post 80p. (£53-78 inc. VAT & P.). 1,000V 1,000MQ, £55. Post 80p. (£60-26 inc. VAT & P.). SAE for leaflet



All Mail Orders-Callers-Ample Parking

Dept. PE, 57 BRIDGMAN ROAD CHISWICK, LONDON W4 5BB Phone 01-995 1560

#### **VARIABLE VOLTAGE TRANSFORMERS**

#### INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V All Types SHROUDED TYPE

200 wat (1 amp inc. a.c. voltmeter 0.5 KVA (2) amp (MAX) 1 KVA (5 amp MAX) 2 KVA (10 amp MAX) 3 KVA (15 amp MAX) 5 KVA (25 amp MAX) 10 KVA (25 amp MAX) 15 KVA (75 amp MAX)

£168.00 £260.00 CARRIAGE AND PACKING EXTRA

#### LT TRANSFORMERS 0-10-15V at 3 amp (ex new equip) £2-50 P. & P. 50p (£3-24

mc, val) 13-0-13V at 1 amp £2:50 P. & P. 50p (£3:24 inc VAT) 25-0-25V at 2 \( \frac{1}{2} \) amp £4:50 P. & P. 75p (£5:67 inc VAT & P.) 0-4V/6V/24V/32V at 12 amp £15:00 P. & P. £1 50 (£17:82 inc

VAT & P.) 0-6V/12V at 20 amp £13.50 P. & P. £1.50 (inc VAT £16.20) 0-12V at 20 amp or 0-24V at 10 amp £12:00 P. & P. £1 50 (£14:58 inc VAT & P.)

0-6V/12V at 10 amp £8:25 P. & P. f 1:25 (inc VAT £10:26) 0-6V/12V/17V/18V/20V at 20 amp £16·50 P & P (£19·44 inc VAT & P.)

0-10V/17V/18V at 10 amp £10:00 P. & P. £1:40 (inc VAT £12.31

types in stock, phone for enquiries or send sae for leaflet

#### HY-LIGHT STROBE KIT MK IV

Latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/240V a.c. operation. Designed for larger rooms, halls, etc. Speed adjustable 1–20 f.p.s. Light output greater than many (so called 4 Joulel strobes. Price £1900. Post £1 (£21-60 incl. VAT & P.). Specially designed case and reflector for Hy-Light £8-80. Post £1 (£10-58 inc. VAT & P.).

#### XENON FLASHGUN **TUBES**

Range available from stock S.A.E. for details



**ULTRA VIOLET BLACK LIGHT** 

#### SQUAD LIGHT

A new conception in light control. Four channels each capable of handling 750 watts of spotlights, floodlights or dozens of small mains lamps. Seven programs all speed controlled plus flash modulation, effectively giving 14 different displays. Makes sound-to-light obsolete. Completely electrically and mechanically noise free. Post 75p S.A.E. (Foolscap) for further details.

## WIDE BANGE OF DISCO LIGHTING

## Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding heavy duty brish assembly, continuously rated 25 WATT 10/25/50/100/150/250/500/1kg/ 1-5k0, £2-40. Post 20 pt (£2.81 inc. VAT.8. P.) 50 WATT 100/2500 £2.90. Post 25p (£3.40 inc.

100 WATT 1/5/10 25/50/100/250/500/1kΩ/1-5kΩ/2 5kΩ (3.5kΩ 25-90 p. 8.p. 35p. (£6.75 nc VAT) Black, Silver, Skirded knob calibrated in Nos. 1-9 1\frac{1}{2} in. dia brass bush Ideal for above Rheostats **24p** each.

## RELAYS

230/240V A.C. Relays: Arrow 2 c/o. 15 amp £1.50 (£1.84 inc

VAT & P). T.E.C. open type 3 c/o. 10 amp **£1.10** (**£1.40** inc. VAT & P). Omoron or Keyswitch 1 c/o. 7 amp **£1.00** (**£1.30** inc. VAT & P).

Ondron or Reywitch 1 c/o. / amp £1.00 £1.30 inc. VAT & P1.

D.C. Relays: Open type 9/12V 3 c/o 7 amp £1.00 £1.30 inc.

VAT & P1. Sealed 12V 1 c/o 7 amp octal base. £1.00 £1.30 inc.

VAT & P1. Sealed 12V 2 c/o 7 amp ottal base. £1.25 £1.56 inc.

VAT & P1. Sealed 12V 3 c/o 7 amp 11-pin. £1.35 £1.67 inc.

VAT & P2. 24V. Sealed 3 c/o 7 amp 11-pin £1.35 £1.67 inc.

VAT & P1. (amps = contact rating). P& P on any Relay 20p.

Other types available — phone for details.

Diamond H heavy duty A.C. relay 230/240V a.c., two C/O contacts 25 amps res at 250 a.c. £2.50 p&p 50p. (£3 24 inc VAT + p&p) Special base 50p.

AT CURRENT RATE MUST BE ADDED TO ALL ORDERS FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED.

## SERVICE TRADING CO. ACCOUNT CUSTOMERS MIN. ORDER £10-00

#### PARVALUX MOTOR TYPE SD2

12 volt. D.C. shunt  $\frac{1}{30}$  H. P. Motor. Continuously rated 4,000 r.p.m. £10 P. & P. 75p (inc. VAT £11-61). N.M.S.

#### GEARED MOTORS

100 r.p.m. 115lb.in. 110V 50Hz 2 8A single phase split capacitor motor immense power Continuously rated Totally enclosed Fan cooled in-line gearbox Length 250mm Dia 135mm Spindle dia 15 5mm Length 145mm Ex-equipment tested £12. Post £1 50 (£14-58 inc. VAT & P.) Suitable transformer 230/240V operation £8. Post 75p £9-45 inc. VAT & P.)

#### GEARED MOTORS

28 r.p.m. 20 lbs inch 115v a.c. Reversible motor. 71 r.p.m. 10 lbs inch 115v. a.c. Reversible motor



Both types similar to above drawing. Price either type  $\bf £4.75$  p8p 75p (£5.94 inc VAT +p8p) Supplied complete with transformer for 240v a.c. operation  $\bf £7.25$  p8p £1.00 (£8.91 inc VAT +p8p)

Crouzet 230/240V. AC 2RPM synchronous geared motor. Brand new £2:90 p&p 30p. {£3:45 incl VAT} (quantity discount available)

#### FRACMO GEARED MOTOR

56 r.p.m. 50lb.in. 240V a.c. 50Hz. 0.7 amp. sharplength 35mm. dia. 16mm. weight 6 kilos 600 grammes. Price £15 00 P. & P. £1. 50 (£17.82) N.M.S.



#### PARVALUX GEARED MOTOR

230/240V A.C. 30 rpm 50lbs inch. Price £15-00 P & P. £1-00 (£17-82 inc. VAT)



#### PARVALUX GEARED MOTOR

230/250V a.c. 500 rpm, 31bs inch. 2 right angled spindles £11.00 P & P £1.00 (£12.96 inc VAT & P.).

#### **CITENCO 19 RPM**

FHP mutor type C 7333-15 220/240V a.c. 19 p.m. reversible motor torque 14 5 kg gear ratio 144-1. Brand new incl. capacitors our price £14-25, P. 8-P. £1.25 (£16-20 inc. VAT & P.)



PROGRAMME TIMERS
12 cam model £7 50. Post 60p (£8.75 inc. VAT & P.). Also available for 50V operation Price as above



Venner Type ERD Time switch 200/250V a.c. 30 amp contact 2 on/2 off every 24 hrs at any manually pre-set time. 36 hour Spring Reserve and day omitting device Built to highest Electricity

Board specification Price £7.75.
P & P 750 (£9.18) RRT



#### SANGAMO WESTON TIME SWITCH

Type S251 200/250V a.c. 2 on/2 off every 24 hours. 20 amps contacts with override switch dia. 4 x 3 price £6.50 F. & P. 50p inc. VAT £7.56. Also available with Solar dial

#### FRACMO MOTOR

1400 rpm H.P. 1/30 continuously rated 115V a.c. supplied complete with transformer for 230/240V a.c. op. Complete with anti-vibration cradle mounting £10-00 P. & P. £1-00 (£11-88 inc. VAT & P.).

#### **ROTARY VACUUM** AIR COMPRESSOR

& PUMP
Carbon vana oil free vacuum pump
and compressor. Approx 20 inch
vacuum 10 PSI at .79 CFM
Powered by 110V a.c. 1.8 amp
Parvalux motor fitted with additional shaft at rear, suitable
light loads. Inc. capacitor £14.00 p&p £1.50 (£16.74 inc. VAT
+ n&p) Suitable transformer for 230/240V a.c. operation p&p) Suitable transformer for 230
 £5.00 p&p £1.00 (£6.48 inc VAT + p&p)


#### Yet another outstanding offer.

IMFD 600V Dubilier wire ended capacitors

£1-50 p&p 50p. (£2-16 inc VAT + p&p) (Min 10) 230V a.c. FAN ASSEMBLY



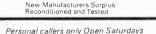Powerful continuously rated a.c. motor complete with 5 blade 6 in Aluminium fan. Price £3-00. P. & P. 65p (£3-94), N.M.S



**9 LITTLE NEWPORT STREET LONDON WC2H 7JJ** Phone 01-437 0576

Published approximately on the 15th of each month by IPC Magazines Ltd.. Westover House, West Quay Road. Poole, Dorset BH15 LJG. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia, and New Zealand—Gordon & Gotch (A/sia) Ltd.: South Africa—Central News Agency Ltd.
Subscriptions INLAND and OVERSEAS £10.60 payable to IPC Services. Oakfield House, Perrymount Road, Haywards Heath, Sussex.
Practical Electronics is sold subject to the following conditions, namely, that it shall not the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold or hired out or otherwise disposed of in a multiply described in a price production of the publishers and the production of the publishers are substrained agreement of the publishers and the production of the publishers are substrained agreement. mutilated condition of in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# MARPLIN

everything for the modern D.I.Y. electronics enthusiast and more.



#### 100W RMS STEREO DISCO A genuine 100W RMS per channel (both channels driven) stereo disco with auto fade on microphone, VU

driven) stereo dis meters full monitoring and cueing facilities and a very high quality light show. Complete construction booklet MES41, price 25p. Cabincomes complete with lid and carrying handles.



#### VERY LOW-DISTORTION **AUDIO OSCILLATOR**

ne wave (<0.01%) out igh quality hi-fi audio

equipment. Also includes square wave output. Range 20Hz to 26kHz. Output 0V to 1V in three continuously variable steps. Total cost around £21. Full construction details in our catalogue. Send the coupon below, now (All prices include V.A.T. and p & p)





#### **PEDAL UNIT**

A completely self-contained pedal unit. 13-note. 2-Octave range. 4 organ stops. It can be added to any organ. A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass quitar sound. A must for the solo quitarist. Full construction details in our catalogue - post the coupon below. now!



#### 'PE' STRING ENSEMBLE

Come and see all our projects

on display at the Electronics hobby show

new improved Disco and Hi-fi Stereo Amp.

Unbeatable prices and finest quality components only when you buy from Maplin. All parts available to build this fascinating project. Component schedule available shortly (s.a.e. appreciated). Demonstration model in our shop soon Phone now and compare our prices



#### SYNTHESISER

The International 4600 Synthesiser, A very comprehensive unit. Over 400 sold. We stock all the parts costing less than £500 including fully punched and printed metalwork and a smart teak cabinet. Far less than half what you'd pay for a ready made synthesiser of equal quality. Specification on request. Full construction details in our construction book £1.50. (All prices include V.A.T. and p & p)



#### 10 CHANNEL STEREO GRAPHIC EQUALISER

A new design with no difficult coils to wind, but a specification that puts it in the top-flight hi-fi class. All this for around £70 including fully punched and printed metalwork and woodwork. Send for our

> component schedule now. Full construction details price 25p. (All prices include V.A.T. and p & p)



#### INTEGRATED CIRCUITS


Over 35 pages in our catalogue devoted to hundreds of useful I.C.s. All with data, pin connections and many with applications circuits and projects to build Post the coupon now!


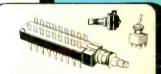
#### TOUCH-SENSITIVE PIANO

The revolutionary new IC AY-1-1320 first seen on 'Tomorrow's World' is now available. Complete kit of IC's to build a 60-note piano (18 x 1C's) order as HQ53H price £36.86. Preliminary circuit details in our October newsletter. Complete design, pcb's attractive veneered wooden cabinet

available soon. It's the most realistic-sounding electronic piano we've ever heard and includes simulated damping, loud and soft pedals. Full details in our newsletters. (All prices include V.A.T. and p & p)



#### SWITCHES

We stock a wide range of switches including a really low-priced high quality interlocking push-button switch system which is extremely versatile. We've got toggle switches, slide switches, push switches, rotary switches there are dozens to choose from, but it's only a tiny part of our fantastic range.



bi-monthly newsletter keeps you up to date with guaranteed prices – our latest special offers details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy)



as soon as it is published (8th January, 1979). I enclose 75p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately.

1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1				
NAME				
ADDDESS				

## MAPLIN ELECTRONIC SUPPLIES P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR

Breadboard at Seymour Hall, London W1.stands E7-E9

On Saturday 25th Nov, there will be a continuous demon-

stration of our Organ MES55, 5600 Synthesiser, new Piano,

Telephone: Southend (0702) 715155 Shop. 284, London Road, Westcliff-on-Sea. Essex

PE12