



THE BETAMAX VIDEO SYSTEM SERVICING THE PHILIPS TX CHASSIS SAFETY IN SERVICING VINTAGE TV - VCR CLINIC CTV DATENY OPERATION

Interested in Television Servicing? ZED Pack. Effect Repairs at Min switches including:

5Ω, 10Ω, 20Ω, 30Ω, 50Ω, 100Ω, 200Ω, 1K, 8 of one type £1.00, 8 of


21 300 mixed ½ and 4 watt and minia- ture resistors 220 10 Assorted switches including: Miniature etc. Fantastic Value 61.20 23 300 mixed 0 apactors motypes 210 100 mixed 1 apactors 11.20 24 100 mixed Printed Circuit resistors 11.45 225 100 Assorted Styme Loade Block St. 11.00 210 200 General Purpose Certranium 11.00 27 300 mixed Printed Circuit resistors 11.50 227 210 Assorted Sync Diode Block St. 11.00 210 100 mixed Miniature Ceramic and 11.50 200 General Purpose Certranium 11.00 211 200 Assorted Sync Diode Block St. 11.00 210 200 Miniature Terry Printed St. 11.00 211 210 Assorted VDR Xano 210		Try	a ZED Pa	ck. E	ffe	ct Repairs a	at Min
22 150 mixed 1 and 2 wattresistors £1.95 Miniature ct. Pantastic Value £1.20 23 100 mixed capacitors types £1.95 221 100 Mixed 2 wastresistors £1.00 24 100 mixed lextraytirenc Capacitors £1.20 223 20 Assorted 3 Work holes caps £1.00 25 100 mixed Printed Circuit £1.95 224 100 Assorted 1 Ware bases £1.00 26 100 mixed High Wattage Resistors. 226 227 120 Assorted 1 Ware bases £1.00 27 100 mixed High Wattage Resistors. 226 227 120 Assorted 1 Ware bases £1.00 210 100 mixed High Wattage Resistors. 226 220 Assorted Wine Humpse Germanium Diodes £1.00 210 25 Assorted Posters. Skelton et L. 230 20 Assorted Wine Humpse Germanium Diodes £1.00 211 25 Assorted Posters. Skelton et L. 233 20 Assorted Wine Humpse Germanium Diodes £1.00 212 20 Assorted Work humpse Germanium Diodes £1.00 Capse Germanium Diodesis fillion Capsered Fillion Cap	ZI				10 As	sorted switches including:	
23 300 mixed capacitors, most types manzing value 1.00 Assorted Silver Mice a caps 12.00 24 100 mixed Polystyrenc Parsitors, 12.20 223 20 Assorted TV Knobs including; 1.00 25 100 mixed Polystyrenc Parsitors, 12.20 224 100 Assorted Value bases 1.100 26 300 mixed Printed Circuit 1.195 224 100 Assorted Value bases 1.100 27 300 mixed Printed Circuit 1.145 225 120 Assorted Value bases 1.100 28 100 mixed Miniature Caraniand 228 200 Assorted Proce Germanium, 100 100 210 25 Assorted Proce Germanium 1.100 Capaciors, Superb Buy at 1.120 211 10 Mixed Hardware, Nuts, Bolts, 12.30 231 10 Winder Hardware, Press Kale 1.100 211 10 Kinde Hardware, Nuts, Bolts, 12.30 231 120 VT Tube Bases 11.00 211 100 Mixed Dirace, Nuts, Bolts, 12.30 231 100 Winaure Teary Press Kale 11.00 211 100 Mixed Dirace, Nuts, Bolts, 12.30 231 100 Winaure, Press, Malex, 100 100 Mixed Press, 100							
21 100 mixed Points (Pice 12, 30 223 100 Mixed Pice TV convergence Pots £1.00 25 100 mixed Points (Pice 12, 30 223 224 100 Mixed Pice TV convergence Pots £1.20 26 100 mixed Points (Pice 12, 30 223 224 100 Assorted Via Verbass £1.20 27 300 mixed Points (Pice 12, 31, 325 224 10 Assorted Via Verbass £1.00 28 20 General Purpose Germanium £1.50 220 223 Sorted Pice Sockes £1.00 210 25 Assorted Pice Sockes £1.00 224 20 Assorted Via Verbass £1.00 211 25 Assorted Pice Sockes £1.00 23 Assorted Pice Sockes £1.00 212 25 Assorted Pice Sockes £1.00 20 Assorted Verb Buy at Capacions Supports Buy at Capacions Sup				721			
24 100 mixed Polystyres (papetors 1:2.30 22.33 20 Assorted TV Knobs including: Control types (1:2.30) 25 100 mixed Polystyres (papetors 1:1.50) 2.23 100 mixed Ninitad Circuit creations (1:1.60) 2.24 100 bystrk Gaps 11.00 28 100 mixed Minitad Circuit creations (1:1.60) 2.24 100 bystrk Gaps 11.00 29 100 mixed Minitader Caramic and Plate caps 11.50 2.29 20 Assorted Symc Diode Blocks (1:1.00) 210 23 Assorted Presets, Steleton etc. £1.00 2.30 40 minitader Tantalitation Capacitors, Superb Buy at £1.20 2.30 40 minitator Tantalitation Capacitors, Superb Buy at £1.00 2.30 2.30 40 minitator Tantalitation Capacitors, Superb Buy at £1.00 2.30 2.30 2.30 2.30 2.30 2.30 2.30 2.30	23						
26 300 mixed Printed Circuit E1.20 Components E1.20 27 300 mixed Printed Circuit F1.95 Z.44 ID Sansted Valve bases B9A, EITT, etc. E1.00 28 100 mixed High Wattage Resistors, wirewoundsetc. Z.25 Z27 Z20 Assorted Valve bases E1.00 29 100 mixed Miniature Caramiuan Plate caps E1.50 Z.27 Z20 Assorted Virols Statularus E1.00 E1.00 210 25 Assorted Prests, Steleon etc. E1.00 Z.23 200 deserted Similarus Terry clips, E1.00 E1.00 213 Thermistors, Billingpers, "Picips etc. E1.00 Z.23 200 Assorted Virols, Steleon etc. E1.00 214 100 mixed Miniarus Terry clips, BC100, BC148, BC154, BE724, Switches, Red Kohob E1.00 Z.24 CV PriD Battry Connectors E1.00 214 100 mixed Miniarus Pressto Make" Switches, Red Kohob E1.00 Z.24 Switches, Red Kohob E1.00 213 100 Miniarus Pressto Make" Switches E1.00 Z.24 Switches E1.00 214 200 Assortel Virols B Sowitches E1.00 Z.2	Z4						
Components £1.95 224 100 Assorted Valve bases 7 300 misced Printed Circuit £1.45 225 105 park Gaps £1.00 8 100 misced High Wattage Resistors. £26 20 Assorted Sync Diode Blocks £1.00 9 100 misced High Wattage Resistors. £27 21 Assorted IC Sockets £1.00 210 25 Assorted Presets, Skelston etc. £1.00 Zagacions. Superb Buy at £1.20 211 20 Assorted VDR Yan marked £1.20 Z30 Odminiature Tantalum Capacitors. Superb Buy at £1.00 Capacitors. Superb Buy at £1.00 12 20 Assorted VDR Yan marked £1.20 Z31 10 Miniature Tantalum Capacitors. Superb Buy at £1.00 Z30 Odminiature Tantalum Capacitors. Superb Buy at £1.00 210 ID DR Coll Bucket £1.00 Z31 ID Miniature Tantalum Capacitors. Superb Buy at £1.00 211 ID Miniature Tantalum Capacitors. Superb Buy at £1.00 £1.00 £1.00 212 ID Miniature Reset Superb Budge Signal, Z30 Superb Budge Signal, Z30	-						
27 300 mixed Printed Circuit B9A, EIT, etc. £1.00 28 100 mixed High Wattage Resistors, 22.5 22.7 10.5 Spark Gaps £1.00 29 100 mixed High Wattage Resistors, 22.8 22.8 20 Assorted Sync Diode Blocks £1.00 210 25 Assorted Potentiometers £1.50 22.9 22.0 22.8 22.7 20 Assorted Winkature Terry clips, £1.20 211 25 Assorted Potentiometers £1.00 22.9 20 Assorted Works Buy at El.20 £1.00 21.20 20.5 CTV Tube Base £1.00 212 20 Assorted Potentiometers £1.00 22.3 20.5 CTV Tube Base £1.00 213 10 Mixed Hardware, Nuts, Bolt, 22.3 23.5 CTV Tube Base £1.00 214 10 Mixed Hardware, Nuts, Bolt, 23.5 23.5 CTV Tube Base £1.00 214 10 Mixed Hardware, Nuts, Bolt, 23.5 23.5 CTV Tube Base £1.00 214 10 Mixed Hardware, Nuts, Bolt, 23.5 23.5 Storted Poets, 55.0 CTV, Tube Base £1.00 214.10 21.00 Storted Hardware, Nuts, B	Z6			774			£1.20
resistors £1.45 £2.5 105 park Gaps £1.00 28 100 mixed High Watter Cramic and Plate caps £2.9 27 12 Assorted Sync Diode Blocks £1.00 210 25 Assorted Presets, Skeleton etc. £1.50 729 20 Assorted VDR Sync Diode Blocks £1.00 210 25 Assorted Presets, Skeleton etc. £1.00 Capacitors. Superb Buy at Capacitors. Supe	Z7			227			£1.00
29 100 100 12.95 22.7 12 Assorted IC Sockets # 1.00 210 25 Assorted Miniature Caramic and Plate caps # 1.50 23 00 General Purpose Germanium # 1.00 211 25 Assorted Miniature Caratalum Capacitors. Superb Buy at # 1.20 # 1.20 212 20 Assorted Viniature Terry clips. # 1.00 # 1.00 213 116 Mixed Hardware, Nuts, Bolts, Zait 210 10 Sorted VDR3 Pert Bases # 1.00 214 100 mixed Ne and marked Zait 100 Kiniature Terry clips. # 1.00 214 100 mixed Ne and marked Zait Situating Construct Construct Process of Malker's Sorted Mal							
29 100 mixed Miniature Ceramian Z28 20 General Purpose Germanium Fl.00 Z10 25 Assorted Pressts, Skelson etc. 11.50 Z39 20 Assorted Miniature Tantalum Capacitors, Super Buy at IL.20 Z11 25 Assorted Pressts, Skelson etc. 11.00 Zapacitors, Super Buy at IL.20 Capacitors, Super Buy at IL.20 Z13 20 Assorted Pressts, Skelson etc. 21.00 Zapacitors, Super Buy at IL.20 Z14 100 mixed New and marked Z33 20 XPP3 Battery Connectors 11.00 Z14 100 mixed New and marked Z33 20 XPP3 Battery Connectors 11.00 Z15 100 Mixed Diodes including: Z34 21 Sub MinS P.C.O. Slide Switches 11.00 Z14 200 Transistors as above but including power types like BD 31, Zapacitors, Alf II Bypes (Sapacitor) Z36 Simulater Kocksts, witches 11.00 Z16 201 Mixed Diodes including: Z40 100 Miniature Red Switches 12.00 Z16 201 Mixed Diodes including: Z41 100 Miniature Red Switches 12.00 Z16 201 Mixed Diodes including: Z41 100 Miniature Red Switches 12.	Z8						
Piate caps f1.50 Diodes f1.00 210 25 Assorted Miniature Tatalum Capacitors. Superb Ruy at 12 f1.00 f1.00 211 20 Assorted Viniature Tatulum Capacitors. Superb Ruy at 12 f1.00 f1.00 213 116 Mixed Hardware, Nuts. Bolts, Selftappers, "P" clipsetc. f1.20 f1.20 f1.20 214 100 Mixed Hardware, Nuts. Bolts, Selftappers, "P" clipsetc. f1.20 f1.20 f1.20 214 100 Mixed Hardware, Nuts. Bolts, PBC 1054, BE 724, BC 2121, BC 238, BC 184, BE 724, BC 2121, BC 238, BC 184, BE 744, Capacitors as above but f2.30 f1.00 f1.00 214 200 Transistors at float spec- including power types like BD 131, Carene, Power, Bridge, Signal, Germanium, Silicon etc. All full spec. f2.39 f2.40 f1.00 f1.00 215 100 Mixed Diodes including: Carene, Power, Bridge, Signal, Carene, Power, Bridge, Signal, 200 f1.00 f1.00 </td <td>7.9</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>11.00</td>	7.9						11.00
211 23 Assorted Presets. Skeletonetc. £1.00 Capacitors. Superb Ruy at £1.20 212 20 Assorted VDRS and the standard stand	27						£1.00
212 20 Assorted VDR's and Thermistors 230 40 Miniature Terry clips, ideal for small Tools etc. £1.00 213 11b Mixed Hardware, Nuts, Bots, Selfapper, "P" clips, etc. 231 5CTV Tube Bases £1.00 214 100 mixed New and marked 233 20x PP3 Battery Connectors £1.00 214 100 mixed New and marked 233 20x PP3 Battery Connectors £1.00 215 Lots of similar types ONLY £4.95 Switches, Red K nob £1.00 214 100 mixed New and marked 235 Switches, Red K nob £1.00 215 Lots of similar types ONLY £4.95 Z34 Switches, Red K nob £1.00 214 200 Soldes including: 239 35mm Jack Sockets, switches £1.00 210 Mixed Diodes including: 239 3.5mm Jack Sockets, switched, enclosed Type 8 for £1.00 216 201 M148 Gen Purpose Diodes £1.00 241 100 Miniature Reed Switches £1.00 217 201 M4003 / 1002 £1.00 242 20 Miniature Reed Switches £1.00 218 20 A Mi403 100 for £1				Z 29			
Thermistors £1.20 ideal for small Tools efc. £1.00 213 Ib Wiscel Hardware, Nuts, Bots, ZJ 5 CTV Tube Bases £1.00 214 100 mired New and marked 233 20x PP3 Battery Connectors £1.00 214 100 mired New and marked 233 20x PP3 Battery Connectors £1.00 BC212L, BC248, BC154, BE774, Switches, Red K nob £1.00 BC212L, BC238, BC154, Land/or Z36 12 Min D.P.C.O. Slide Switches £1.00 including power types Ike BD131, Z37 8 Standard 2 Pols 3 Pos Switches £1.00 Z15 100 Mirade Diodes including: (2x.2 Flat type) 4 for £1.00 Z16 20 IN4148 Gen Purpose Diodes £1.00 Z43 100 Miniature Reed Switches £1.00 Z18 20 A sorred 2-per sorred £4.95 Z40 100 Miniature Reed Switches £1.00 Z18 20 IN403/1002 £1.00 Z43 12 Subminiature Reed Switches £1.00 Z18 20 for £1.00 FE1.00 Z42 20 Miniature Reed Switches £1.00 Z16 20 IN403/1002 £1.00			eton etc. £1.00	7.20			£1.20
	212		£1.20	2.30			£1.00
214100 mixed laws and marked23320x PP3 Battery Connectors \pounds 1.00transistors all full gets including: BC12L BC238, BC184L and/or Lots of similar types23320x PP3 Battery Connectors \pounds 1.00(Z14A)20X Instance and show but including power types like BD 131, 2X1510X Mac D'odes instanced and the Dodes including: 2X1510X Mac D'odes including: 2X162X178 Standard 2 Pole 3 Pos Switches \pounds 1.00(Z14A)20X Instance and show but including power types like BD 131, Care, Power, Bridge, Signal, Germanium, Silicon etc. All full spec.238 $4x$ HP1 HB att Holders 4 x1P1 HB att Holders 4 x1P2 HB attery Pole 2201 H148 Gen Purpose Diodes 5 11.0023123 Dot Hinders 4 x1P1 HB att Holders 4 x1P1 HB at	Z13			Z31			
Transistors alfull spec: includes:Z346 * Miniature "Presto Make"PBC108, BC148, BC154, BE724, BC1212, BC238, BC154, LandorSwitches, Red Knob£1.00Lots of similar typeONLY £4.95Switches£1.00(Z14A) 200 Transistors as above but including power types like BD131, 2005 AC128, BPT S0 etc.23612 Min D.P.C.O. Slide Switches£1.00Z15100 Mixed Diodes including: 2 Zeners.2384 xh P11 B att Holders $4 for £1.00$ Z16100 Mixed Diodes including: 2 Zeners.2384 xh P11 B att Holders $2 for £1.00$ Z17201 Mixed Diodes including: 2 Zeners.24.95Z 40100 Miniature Reed Switches£1.30Z1820 Assorted Zeners. 1 watt and 400 mw£1.60Z 41100 Subminiature Reed Switches£1.30T1820 Assorted Zeners. 1 watt and 400 mw£1.50ZENERS for £1.0020 × 1N4003 / 100 × 10.00High quality COAX PLUGS Silver plated pin, grub scient Signer 1 and 400 mw£1.50ZENERS for £1.00100 for £1.200Lid 5320 for £1.2010 for £1.20010 for £1.20020 × 1N4003100 for £1.501004 25v20 for £1.00100 for £1.200100 for £1.20020 × 1N4003100 for £1.501004 25v20 for £1.00100 for £2.50100 for £2.50100 for £5.001004 25v20 for £1.0050 for £1.00100 for £2.50100 for £2.501004 25v20 for £1.00100 for £2.50100 for £2.50100 for £2.501004 25v20 for £1.0010 for £2.501							
PEC108, EC148, EC148, EBC154, EPC74, BC124, EC238, EC184, and/or Switches, Red K.nob £1.00 Lots of similar types ONLY £4.95 Z35 I 2 Sub Min S.P.C.O. Slide Evitches £1.00 (Z14A) 200 Transistors as above but incluing power types like BD 131, ZN3055, AC128, BFY S0 etc. Z37 8 Standard 2 Pole 3 Pos Switches £1.00 215 100 Miniature Reed Switches £1.00 (2x2 Flattype) 4 for £1.00 216 201N418 Gen Purpose Diodes £1.00 Z42 20 Miniature Reed Switches £1.00 218 20 Assorted Zneers. Z43 12 Sub Miniature Reed Switches £1.00 218 20 Assorted Zneers. Z43 12 Sub Miniature Reed Switches £1.00 218 20 Assorted Zneers. Z43 12 Sub Miniature Reed Switches £1.00 218 20 Assorted Zneers. Z43 12 Sub Miniature Reed Switches £1.00 218 20 Fr £1.00 FL £100DES Yers small. 20k Y 2 5ma.30ma park Yers 27mb.31, 20k Y 2 5ma.30ma park 104 350 * 10 for £1.00 FL £100DES Yers 27mb.31, 20k Y 2 5ma.30ma park Yers 27mb.31, 20k Y 2 5ma.30ma park 214 350 * 10 for £	Z 14			-			£1.00
BC212L, BC238, BC184L and/or Z35 12 Sub Min.S.P.C.O. Slide C14A) 200 Transistors as above but Z36 12 Min.D.P.C.O. Slide Switches £1.00 Market State 236 12 Min.D.P.C.O. Slide Switches £1.00 Z15 100 Mixed Diodes including: Z36 4×HP11 Batt Holders 4 for £1.00 Z15 100 Mixed Diodes including: C2.2 Flat type) 4 for £1.00 22.31 Z16 201N4148 Gen Purpose Diodes £1.00 Z41 100 Subminiature Reed Switches £1.30 Z17 201N4148 Gen Purpose Diodes £1.00 Z41 100 Subminiature Reed Switches £1.00 Z18 20 Assorted Zeners. L.00 Z41 12 Subininiature Reed Switches £1.00 S0cKET 3 for £1.00 CAN COUPLERS \$6 re £1.00 COAX COUPLERS 5 for £1.00 No more messy soldering. 24 pin 1.0 Sostet Capseitors. Nulf af 350* 10 for £1.00 DAssorted Polyseter Capacitors. 10 of or above 42.00 10 of or above 42.00 1004 c2s 20 for £1.00 PECIAL OFFERS. 20 or N14000 100 for £2.50				234			£1.00
		BC212L, BC238, BC184	4L and/or	Z35			
Including power types like BD 131, 2N305, AC 128, BFY50 etc.237 49, 958 Standard 2 Pole 3 Pos Switches $f.1.00$ 2N305, AC 128, BFY50 etc. $f.9.95$ 2N38 $d x H P11 B att Holders(2 × 2 F1 at type)d for f1.00(2 × 2 10 Miniature Reed Switchesf f.2.30(2 × 2 10 Miniature Reed Switchesf f.2.30(2 × 2 10 Miniature Reed Switchesf f.2.30(2 × 2 10 Miniature Reed Switchesf f f f f f f f f f f f f f f f f f f $	(7144)			736			
2130355, AC 128, BFY50 etc. £9,95 Z38 $4 \times HP1 I$ Batt Holders Z15 100 Mixed Diodes including: Z38 $4 \times HP1 I$ Batt Holders Z15 100 Mixed Diodes including: Z39 3.5mm Jack Sockets, switched, enclosed Type 8 for £1.00 germanium, Silicon etc. All full enclosed Type 8 for £1.00 Z41 100 Subminiature Reed Switches £2.30 Z16 201N4148 Gen Purpose Diodes £1.00 Z41 100 Subminiature Reed Switches £1.00 Z17 201N4148 Gen Purpose Diodes £1.00 Z41 100 Subminiature Reed Switches £1.00 Z18 20 Assorted Polysen Soft £1.00 FHT DIODES Very small. 20k V 2.5m. 30m a pask 50 re a.5 of £1.00 Silver plated pin, grub screw firmer, grub screw firmer, grup memory firmer, grup memory firmer, grup memory firmer, grup memory screw firmer, grup memory screw firmer, grup memory screw firmer,	(Z14A)						
Zener, Power, Bridge, Signal, Germanium, Silicon etc. All full spec. Z39 3.5mm Jack Sockets, switched, enclosed Type Z16 201N4148 Gen Purpose Diodes £1.00 Z41 100 Subminiature Reed Switches £2.30 Z17 201N4003/1002 £1.00 Z42 20 Miniature Reed Switches £1.00 Z18 20 Assorted Zeners. Z43 12 Subminiature Reed Switches £1.00 High quality COAX PLUGS, Silver plated pin, grub sercev file quality to 0 for £1.00 £1.50 Z43 12 Subminiature Reed Switches £1.00 COAX COUPLERS SOCKET 3 for £1.00 Special Cook (COUPLES) Very small. 20k V 2.5m. 30m peak Socket (Strong 1, 20k V 2.5m. 30m peak Socket (Strong							
Germanium, Silicon etc. All full enclosed Type 8 for £1.00 zpc 2.30 3.30 2.30 3.3	Z15						for £1.00
spec. £4.95 Z40 100 Miniature Reed Switches £2.30 Z17 201N4003/10D2 £1.00 Z41 100 Subminiature Reed Switches £1.00 Z18 20 Assorted Zeners. Z33 12 Subminiature Reed Switches £1.00 I watt and 400 mw £1.50 Z42 20 Miniature Reed Switches £1.00 High quality COAX PLUGS. 5 for £1 CAX COAX FLYING 5 for £1 COAX FLYING 3 for £1.00 Store FL80 Store FL80 Store FL80 SOCKET 3 for £1.00 No more messy soldering. 24 pin LC sockets for \$1.00 tor 61.20 10 of nor value 80p CoAX FLYING 20 for £1.00 No more messy soldering. 24 pin LC sockets for \$1.00 tor 61.20 10 of nor value 80p 10 of nor £1.20 No more messy soldering. 24 pin LC sockets for \$1.00 tor 61.20 10 of nor value 80p 10 of nor £1.00 No sonted Polytester Capacitors. Multard C20's and other 20 or Nt4000 10 of for £2.50 10 of nor £1.00 No sonted Polytester Capacitors. 10 of nor £2.50 20 × 1N400S 10 of for £2.50				Z39			for £1.00
$ \begin{array}{c c c c c c c c c c c c c c c c c c c $				Z40			
Z1820 Assorted Zeners. I watt and 400 mwZ4312 Subminiature Reed Switches£1.00High quality COAX FUUGS, Silver plated pin, grub screw, COAX FUYING SOCKET5 for £1 Sor £1 COAX FUYING $2.2 \mu f 33$ 20 KV 2.5ma. 30ma peak Sopea. 3 for £1.00CENERDIODES Sor £1.00ELECTROLYTIC $1 \mu f 33v$ 10 for £1.00 $1 \mu f 35v$ 10 for £1.00 ft.100COAK I.1.400mw. 100 for £1.00 $2.2 \mu f 33$ 20 for £1.00 $10 \mu f 25v$ 10 for £1.00 ft.100Nom cre messy soldering. 24 pin $1.5 \text{ spec1AL OFFERS}$ 100 for £1.250.20 km k1.20 km k2 mm 1.00 100 for £2.50 1.00 for £1.00 $100 for £1.30$ 100 for £2.50 $100 \mu f 25v$ 10 for £1.00 $100 for £1.00$ 100 $40v^2$ 3 for £1.00 $100 a Assorted Polyester Capacitors.Mulard C296's and others1000 \mu 430v^*100 for £1.00100 a Assorted Polyester Capacitors.Mulard C296's and others100 a Assorted Polyester Capacitors.Mulard C296's and others100 a Assorted Polyester Capacitors.100 a Assorted Polyester Capacitors.Mulard C296's and others100 a Assorted Polyester Capacitors.100 a Assorted Polyester Capac$	Z16						£4.20
I watt and $400 mw$ I watt and $400 mw$ High quality COAX PLUGS, Silver plated pin, grub screw, fixing			£1.00				
High quality COAX PLUGS, silver plated pin, grub screw fixing.EHTDIODES $C.27, 43, 34, 756, 692, 698, 72, 27, 43, 34, 756, 692, 698, 7527, 309, ALL 400mw,100 for slame100 for flame100 for f$	Z18		£1.50	Z43	12 Sut		
Silver Plated pin. Struct Struct <td>High</td> <td></td> <td></td> <td>IODES</td> <td></td> <td></td> <td></td>	High			IODES			
$ \begin{array}{ c c c c c c c c c c c c c c c c c c c$	silver	plated pin, grub screw	Very small. 20kV	2.5ma. 30ma	peak	7v5c27v, 30v. ALL 400mv	v.
$ \begin{array}{ c c c c c c c c c c c c c c c c c c c$	fixing.			50p ea. 3 for	£1.00		
	COAX	FLYING	RRM	LISERS		1.3 watt, 12v, 13v, 18v, 47	v
LELC LINULY IIC. No more messy soldering. 24 pin DIODES Laf 63v 20 for f1.00 LC. sockets for S1.00 letc. $59EC1AL OFFER: 5$ for f1.00 $50 = 1.00$ 100 for f2.20 10µ 25v 20 for f1.00 $59EC1AL OFFERS$ $50 = 1.00$ 100 for f2.20 10µ 25v 20 for f1.00 SPEC1AL OFFERS 100 for f2.20 100 for f2.50 10µ 25v 20 for f1.00 SPEC1AL OFFERS 100 for f2.50 100 for f2.50 10µ 25v 20 for f1.00 SPEC1AL OFFERS 100 for f2.50 100 for f2.50 30µ f 25v 10 for f1.00 SPEC1AL OFFERS 100 for f2.50 100 for f2.50 30µ f 25v 10 for f1.00 50 for f1.00 100 Assorted Polyester Capacitors. 100 for f2.50 1000µ f 35v 8 for f1.00 50 for f1.00 100 for f2.50 100 for f2.50 1000µ f 35v 6 for f1.00 50 for f1.00 100 for f2.50 100 for f2.50 20µ f 40v 5 for f1.00 50 for f1.00 100 for f2.50 100 for f2.50 20µ ot 100v f1.00 50 f100 <							
$ \begin{array}{llllllllllllllllllllllllllllllllllll$					4 pin		20.00
$\begin{array}{c c c c c c c c c c c c c c c c c c c $	1µf 350	v ' 10 for £1.00			0		
10µ/2 25v 20 for £1.00 SPECIAL OFFERS 100 for £3.00 22µf 16v 20 for £1.20 100 Assorted Polyester C apacitors. 100 for £3.00 160µf 25v 20 for £1.90 160v-400v only £2.00 20 × 1N4005 101 for £3.00 330µf 25v 10 for £1.00 160v-400v only £2.00 20 × 1N4148 100 for £2.50 470µf 25v 10 for £1.00 100 Assorted Mullard C280's 20 × 1N4148 £1.00 1000µf 35v 8 for £1.00 Cosmetic imperfects tetc. £2.00 10 × SK E 4F2/06 470µf 35v 8 for £1.00 Electrolytics Cosmetic imperfects £2.00 10 × SK E 4F2/06 100 v S £1.00 1000µf 40v* 5 for £1.00 Electrolytics Cosmetic imperfects £2.00 10 × SK E 4F2/06 10 × SK E 4F2/0			100 for £12.50.				
$\begin{array}{c c c c c c c c c c c c c c c c c c c $	10µf 25	v 20 for £1.00	SPECIA				
$ \begin{array}{c c c c c c c c c c c c c c c c c c c $			100 Assorted Pol	yester Capaci			
$ \begin{array}{c c c c c c c c c c c c c c c c c c c $	160µf 2	5v* 20 for £1.50		nd others	62.00	20 × 1N4 148	£1.00
$ \begin{array}{c c c c c c c c c c c c c c c c c c c $			100 Assorted Mu			10	10 for £2.50
$ \begin{array}{c c c c c c c c c c c c c c c c c c c $	470µf 2	5v 10 for £1.00			£2.00		
1000 μ f 40v* 5 for £1 etc. 12.00 8 × BY255 (3A 1,300V) £1.00 *Axial. All others are Radial. PACK OF EACH £5.00 8 × BY255 (3A 1,300V) £1.00 CAN TYPES 22 μ f 375v (3 pin) 50p 12V BULBS on leads. Suitable for most VIDEO RECORDERS. 100 + 100 + 80 pea. 3 for £2.00 100 + 200 350v £1.00 100 ex to 1000 at 350 + 100 200 at 350 + 100 80p 200 at 350 + 100 80p 200 at 60 + 100 6 for £2.00 2000 μ f 100v £1.00 60p 70p each 4 for £2 CA270AE £1.00 6 for £5.00 MC 1327P £1.00 6 for £5.00 TBA 810P £1.00 6 for £5.00 TBA 810P £1.00 6 for £5.00 TBA 810P £1.00 6 for £5.00 S5 Timer 30p 4 for £1.00 55 Timer 30p 51.50 500 * 50.00 500 * 50.00 500 * 50.00 500 * 50.00 500 * 50.00 500 * 50.00 500 * 50.00 500 * 50.00 500 * 50.00 500 * 50.0					cts		
* Axial. All others are Radial. CAN TYPES 22 μf 375v (3 pin) 50 p 50 μf 250v (3 pin) 50 p 12V BULBS on leads. Suitable for most VIDEO RECORDERS. 70 p each 4 for £2 12V BULBS on leads. Suitable for most VIDEO RECORDERS. 70 p each 4 for £2 12V BULBS on leads. Suitable for most VIDEO RECORDERS. 70 p each 4 for £2 12V BULBS on leads. Suitable for most VIDEO RECORDERS. 70 p each 4 for £2 12V BULBS on leads. Suitable for most VIDEO RECORDERS. 70 p each 4 for £2 12V BULBS on leads. Suitable for most VIDEO RECORDERS. 70 p each 4 for £2 12V BULBS on leads. Suitable for most VIDEO RECORDERS. 700 # for £1.00 100 # for £1.00 100 # for £1.00 700 # for £1.00				н		8 × BY255 (3A 1,300V)	£1.00
CAN TYPES $22\mu f$ 375v (3 pin) 50p $50\mu f$ 250v (3 pin) 50p $12V$ BULBS on leads. Suitable for most VIDEO RECORDERS. 80p ea. 3 for £2.00 $100 + 200$ 350v £1.00 $100\mu f$ 350v 80p $2000\mu f$ 100v £1.00 $100\mu f$ 100v £1.00 $2000\mu f$ 100v 60p $2.200\mu f$ 40v 60p $2.200\mu f$ 40v 70p $3.500\mu f$ 35v 50p $2.20\mu f$ 40v 70p $3.500\mu f$ 70v £1.00 0.1μ 1000v Flameproof 5 for £1.00 SPECIAL OFFER 100 $2000\mu f$ 40v £1.00 SPECIAL OFFER £1.20 $2000\mu f$ Colour £2.50 $1000 of DK colour £2.50 100 of OK colour £1.20 100 of EACH colour £1.00 100 of CK colour £1.00 100 of OK colour £1.00 100 of OK colour £1.00 100 of OK colour £1.00 100 of EACH colour $	•Axial.	All others are Radial.	TACK OF LACE		23.00		
$ \begin{array}{c ccccccccccccccccccccccccccccccccccc$						6A. 100V. Bridge Rectifie	r.
$ \begin{array}{c c c c c c c c c c c c c c c c c c c $					ble for	· ·	3 for £2.00
100 μf 350v 80p MC 1327P £1.00 6 for £5.00 2000 μf 100v 60p TBA 820 £1 each, 6 for £5.00 2.200 μf 40v 60p TBA 820 £1 each, 6 for £5.00 2.200 μf 40v 70p Soup at 35v 50p 2.200 μf 40v F1.00 6 for £5.00 2.200 μf 40v TT/RBM £1.00 6 for £5.00 2.200 μf 40v F1.00 6 for £5.00 55 Timer 30p 4 for £1.00 2.200 μf 40v F1.00 0·1 μ 1000v Flameproof 5 for £1.00 55 Timer 30p 4 for £1.00 3.500 μf 40v £1.00 0·1 μ 1000v Flameproof 5 for £1.00 SN76660N 50p 5 for £1.00 10.000 μf 40v £1.00 For £1.00 S00" Focus Assembly. Rotary type £1.50.3 for £1.00 100 of ONE colour £1 £2,50 4 *3500" Focus Assembly. Rotary type £1.50.3 for £1.00 100 of ONE colour £1 £1 £1.00 *1.50 *350" focus Assembly. Rotary type £1.50.3 for £1.00 100 of EACH colour £10 *100 *100 *1000	100+20	0 350v £1.00					6 for £5.00
$ \begin{array}{c c c c c c c c c c c c c c c c c c c $						MC1327P£1.00	6 for £5.00
2.200 μf 40v 60p 2.200 μf 40v 70p 3.500 μf 35v 50p 2.20 μf 40v 70p 3.500 μf 35v 50p 2.20 μf 40v £1.00 6.700 μf 70v £1.00 6.700 μf 40v £1.00 6.700 μf 40v £1.00 5.700 μf 40v £1.00 6.700 μf 40v £1.00 SPECIAL OFFER \$1.00 20 of ONE colour £1.50 20 of EACH colour £2.50 100 of ONE colour £4 120 of EACH colour £1.20 100 of ONE colour £4 1500 "Biox Assembly. Rotary type £1.50.3 for £1.00 "3500" Focus Assembly. Rotary type £1.50.3 for £1.00 "3500" Focus Assembly. Rotary type £1.50.3 for £1.00 "3500" Biox Assembly. Rotary type £1.50.3 for £1.00 "3500" Biox Saps Edpi/25v 200 for £1.00 "300" Biox Saps Edpi/25v 200 for £1.00 "350" Sour Saps Edpi/25v 200 for £1.00 "350" Sour Saps Edpi/25v 2000 for £1.00 <td< td=""><td></td><td>100v 60p</td><td></td><td></td><td></td><td></td><td></td></td<>		100v 60p					
$\begin{array}{c c c c c c c c c c c c c c c c c c c $						TBA810P£1.00	6 for £5.00
220µf 400v [TT/RBM £1.00 [0-1µ 1000v Flameproof 5 for £1.00 SN76660N 50p 5 for £2.00 6,700µf 70v £1.00 £1.00 SN76660N 50p 5 for £2.00 THORN SPARES 3500° Transductor £1.20,3 for £3.00 3500° Transductor £1.50,3 for £1.00 3500° Transductor £1.50,3 for £1.00 3500° Transductor £1.50,3 for £1.00 100 of ONE colour £4 *500° Focus Assembly. Rotary type £1.50,3 for £1.00 100 of EACH colour £4 *1500° 360° .0022 2000v Line Capacitor 10 for £1.00 100 of EACH colour £10 *150° 260° .0022 2000v Line Capacitor 10 for £1.00 1500° Bick zapi t60µf 25v 2000r Line Spice Capacitor 10 for £1.00 1500° Bick zapi t60µf 25v 2000r Line Spice Capacitor £3.50° 900/950° 3 stick triplers £1.00,3 for £3.50 £3.50° "900/950° 3 stick triplers £1.00,3 for £3.50 *950° Can. 10 + 300 + 100 + 16µf THORT CONVERGENCE POTS 3.50m stereo jack plug, £2.95 each, £25 for 10. Further discout \$510 (BT 106) 75 peach \$500, 2002, 3002, 5002, 100 S						TAA661BCIOO	
THORN SPARES THORN SPARES SPECIAL OFFER 20 of ONE colour £1.20 20 of ONE colour £1.20 20 of CNE colour £1.20 100 of EACH colour £1.00			0.1μ 1000v Flame	eproot 5 fe	or £1.00		
SPECIAL OFFER "3500" Transductor £1.20, 3 for £3.00 PHONO PLUGS, metal with plastic tops. Red, grey or black. £1 "3500" Focus Assembly with VDR £1.30, 3 for £4.00 20 of EACH colour £2.50 #8500" Focus Assembly with VDR £1.50, 3 for £1.30 100 of ONE colour £1 "8500" Focus Assembly with VDR £1.50, 3 for £1.30 100 of ONE colour £1 "8500" Focus Assembly with VDR £1.50, 3 for £1.30 100 of ONE colour £1 "8500" Focus Assembly Rotary type £1.50, 3 for £1.00 100 of EACH colour £1 "1500" Finats Econdour Line Capacitor 10 for £1.00 100 of EACH colour £1 "1500" Finats Caps Edopt 25x 20 for £1.50 1500" Finat Stemere and the provide the provid	10,000µ	f 40v £1.00				THODICO DOC	
PHONO PLUGS, metal with plastic tops. Red, grey or black. 20 6 3500° Focus Assembly. Rotary type £1.50.3 for £4.00 20 of CACH colour £2.50 8500° Focus Assembly. Rotary type £1.50.3 for £4.00 100 of ONE colour £2.50 8500° Focus Assembly. Rotary type £1.50.3 for £4.00 100 of ONE colour £4 7500° Focus Assembly. Rotary type £1.50.3 for £1.50 100 of ONE colour £4 7500° Focus Assembly. Rotary type £1.50.3 for £1.50 100 of EACH colour £10 500° Focus Assembly. Rotary type £1.50.3 for £1.50 100 of EACH colour £10 500° Focus Assembly. Rotary type £1.50.3 for £1.50 100 of EACH colour £10 500° Focus Assembly. Rotary type £1.50.3 for £1.50 1500° Terable metal boost Diode (W11) 5 for £1.50 500° Focus Assembly. Rotary type £1.50.3 for £1.50 1500° Terable metal boost Diode (W11) 5 for £1.50 100 of £1.50 1500° 161.90 1500° 161.90 1500° Terable metal boost Diode (W11) 5 for £1.50 500° Can. 100 + 300 + 100 + 16µf £1.00.3 for £2.50 1500° Terable metal boost Diode (W11) 500° Can. 100 + 300 + 100 + 16µf 501. 100.3 for £2.50 502. 100.2 for £3.50 <t< td=""><td></td><td></td><td></td><td></td><td></td><td></td><td></td></t<>							
20 of ONE colour £1 20 of CNE colour £2.50 100 of CNE colour £2.50 100 of CNE colour £4 100 of CNE colour £4 100 of EACH colour £4 100 of EACH colour £10 100 of EACH colour £100	PHONO			"3500" Fo	cus Assen	nbly with VDR	£1.50
100 of ONE colour 100 of CNE colour 100 of CNE colour 100 of CNE colour 100 of EACH colour 100 of Bas Caps (50µ/25v 20 for £1.50 SPECIAL OFFER LIGHTWEIGHT STEREO HEADPHONES. Good quality with available on large quantities. 100 of CNE colour 100 of CAL 100 of EACH colour 100 of	20 of ON	NE colour	12				
Special OFFER £1.00 500° jellypot L.O.P.T. Pinkspot £3.50 LIGHTWEIGHT STEREO HEADPHONES. Good quality with available on large quantities. *1500° islup of L.O.P.T. Pinkspot £1.00, 3 for £2.50 *1500° jellypot L.O.P.T. Pinkspot £1.00, 3 for £2.50 *160, 3 for £2.50 *1500° islup of L.O.P.T. Pinkspot £1.00, 3 for £2.50 *160, 3 for £2.50 *1500° islup of L.O.P.T. Pinkspot £1.00, 3 for £2.50 *160, 3 for £2.50 *1500° islup of L.O.P.T. Pinkspot £1.00, 3 for £2.50 *100 + 100 + 10µf *1500° islup of L.O.P.T. Pinkspot £1.00, 3 for £2.50 £1.00, 3 for £2.50 *1500° islup of L.O.P.T. Pinkspot £1.00, 3 for £2.50 \$502, 100, 300, 5002, 100 SS 106 (BT 106) 75p each \$502, 100, 3002, 5002, 100 \$502, 100, 2002, 150, 8 \$600, 2002, 150, 8 *2.000, 10 for £5.50 ************************************	100 of O	NE colour	£4	1 "1590/91"	'Portable	metal boost Diode (W11)	5 for £ 1.00
Special OFFER \$100,950" 3 sick triplers \$100,350" £2.00 LIGHTWEIGHT STEREO HEADPHONES. Good quality with available on large quantities. \$100,100 + 300 + 1	100 of E	ACH colour	£10	"1500" Jel	lypot. L.O).P.T. Pinkspot	£3.50
SPECIAL OFFER LIGHTWEIGHT STEREO HEADPHONES. Good quality with 3.5mm stereo jack plug. £2.95 each, £25 for 10. Further discount available on large quantities. THYRISTOR CONVERGENCE POTS 512. 102. 2020. 3020. 5020. 1000 SS 106 (BT 106) 75p each 3 for £2.00, 10 for £5.50					3 stick tri	plers	
3.5mm stereo jack plug, £2.95 each, £25 for 10. Further discount available on large quantities. 50. 100. 200. 100. 200. 100. <		SPECIAL OF	FER				
available on large quantities. SS 106 (BT 106) 75p each 3 for £2.00, 10 for £5.50 2000. 1K. 8 of one type £1.00, 8 each type £6.00.	3.5mm s	tereo jack plug. £2.95 each, £2			1131		
	available	on large quantities.				5peach 2000, 1K, 8 of on	

im	um Cost.	
Z44	0	
Z45		
Z46 Z47	φ	
2.11	include insulators and wash	
Z48		
Z49		
	Knobs, 15mm long × 11mi Fit standard 34mm square	
	The standard 5 2 min square	10 for £1.00
Z50		
Z51	as above I Aluminium Finish. Standa	10 for £1.00
LJI	Slider Knobs. (Decca)	10 for £1.00
Z52		
763	Black and Chrome. ¹ / ₄ " Shal Tuner P/B K nobs, Black and	
Z53	Fit most small Diam Shafts	
	ITT, THORN, GEC etc.	8 for £1.00
Z54	•	
	$\frac{1}{3}$ " Shaft, suitable for most s with recessed spindles	8 for £1.00
Z55	5 14 Pin DIL I.C. Sockets	12 for £1.00
Z56		12 for £1.00
Z57	7 16 Pin DIL TO QUIL I.C. Sockets	10 for £1.00
Z58		10 for £1.00
Z59		
Z60	0 0.47 $\Omega \frac{1}{2}$ Watt Emitter Resi	stors 40 for £ 1.00
	VCD DATEDVD	
В	V.C.R. BATTERY P HITACHI PORTABLE V.C.R.	Nicad pack
	Type VTBP60E	£20 each.
B	Brand New and Boxed	3 for £50
		25/26 Nicad
p e	back. Type VA214. Also suitable tc. Brand new and boxed. £20 es	ch, 3 for £50.
	THORN "VIDEOSTAR" Nicad	
	s above but secondhand, unteste	
		d. Contain 10
	'C" size Nicads (HP11) which ca	d. Contain 10
	"C" size Nicads (HP11) which ca f necessary. £10 ea	d. Contain 10 in be replaced ch, 3 for £25.
,	C'' size Nicads (HP11) which ca f necessary. £10 ea MISCELLANEOUS tripler for CVC45 etc.	d. Contain 10 in be replaced ch, 3 for £25.
BG100	C'' size Nicads (HP11) which ca f necessary. £10 em MISCELLANEOUS tripler for CVC45 etc. uput transformer for	d. Contain 10 n be replaced ch, 3 for £25. only £3.50
BG100	C'' size Nicads (HP11) which ca f necessary. £10 em MISCELLANEOUS tripler for CVC45 etc. uput transformer for	d. Contain 10 n be replaced ch, 3 for £25. only £3.50
BG100 Line ou RBM82 ITT VC and Phi Decca I	C'' size Nicads (HP11) which ca f necessary. £10 ea MISCELLANEOUS tripler for CVC45 etc. uput transformer for 23A £4.25 200 4P/B Transistor Tuner. Suitab ilips sets. 3 hole fixing Bradford Tuner.	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 buttol UHF M	C'' size Nicads (HP11) which ca f necessary. £10 ea MISCELLANEOUS tripler for CVC45 etc. atput transformer for 23A £4.25 200 4P/B Transistor Tuner. Suitab ilips sets. 3 hole fixing Bradford Tuner. £4.00 hodulator UHF out Video in. Ch. 3	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6.
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 butto UHF M 2 ¹ / ₄ "×2">	C'' size Nicads (HP11) which ca f necessary. £10 ear MISCELLANEOUS tripler for CVC45 etc. uput transformer for 23A £4.25 2000 4P/B Transistor Tuner. Suitab litps sets. 3 hole fixing Bradford Tuner. £4.00 hotype with 9 foot coaxial lea	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. di and plug.
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 buttoo UHF M 2½"×2"5 With cc GEC H	*C** size Nicads (HP11) which ca f necessary. £10 ear MISCELLANEOUS tripler for CVC45 etc. uput transformer for 23A £4.25 200 4P/B Transistor Tuner. Suitab lips sets. 3 hole fixing Bradford Tuner. £4.00 fodulator UHF out Video in. Ch. 3 x4* complete with 9 foot coaxial lea onnection data £3.00 Vibrid 2040 series Focus Assembly	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. di and plug. 9 each, 2 for £5.00 with lead and
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 buttoo UHF M 24"×2" With cc GEC H VDR rc Conver, cod office	*C'' size Nicads (HP11) which car f necessary. £10 ear f necessary. £10 ear MISCELLANEOUS tripler for CVC45 etc. triplet for CVC45 etc. triplet transformer for 23A £4.25 2200 4P/B Transistor Tuner. Suitabilitys sets. 3 hole fixing Bradford Tuner. Bradford Tuner. £4.00 todulator UHF out Video in. Ch. 3/ \$2.00 vg/t complete with 9 foot coaxial lear £3.00 typoid 2040 series Focus Assembly od gence Panel for above. Brand new 8rand new	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each cach, 4 for £12.00 6. di and plug. 0 each, 3 for £5.00 with lead and 0 each, 3 for £5.00
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 butto UHF M 24"×2"> With cc GEC H VDR rc Conver, and plu GEC 20	*C'' size Nicads (HP11) which ca f necessary. £10 ea MISCELLANEOUS tripler for CVC45 etc. uput transformer for 23A £4.25 2200 4P/B Transistor Tuner. Suitabilitys sets. 3 hole fixing Bradford Tuner. n type £4.00 fodulator UHF out Video in. Ch. 3/ x4" complete with 9 foot coaxial lee sonnection data £3.00 typid 2040 series Focus Assembly ogence Panel for above. Brand new 10 Transistor Rotary Tuner with /	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. d and plug. 0 each, 2 for £5.00 with lead and 0 each, 3 for £5.00 leads £3.00 each
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 buttoo 5 buttoo GEC H VDR rc Converg and plu GEC 20 leads Bush C	*C*' size Nicads (HP11) which ca f necessary. £10 ear MISCELLANEOUS tripler for CVC45 etc. uput transformer for 23A £4.25 200 4P/B Transistor Tuner. Suitab lips sets. 3 hole fixing Bradford Tuner. n type £4.00 fodulator UHF out Video in. Ch. 34 x f' complete with 9 foot coaxial leas sonnection data £3.00 tybrid 2040 series Focus Assembly od £2.00 gence Panel for above. Brand new ug. 010 Transistor Rotary Tuner with / £1.9 TV 25 Quadrupler type Q25B equiva	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. d and plug. 0 each, 2 for £5.00 with lead and 0 each, 3 for £5.00 leads £3.00 each A: 500
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 butto UHF M 24"×2"> With cc GEC H VDR rc Conver, and plu GEC 21 leads Bush C TU25 3	*C** size Nicads (HP11) which ca f necessary. £10 ear MISCELLANEOUS tripler for CVC45 etc. tuput transformer for 23A £4.25 2000 4P/B Transistor Tuner. Suitab lips sets. 3 hole fixing Bradford Tuner. 4' complete with 9 foot coaxial lear onnection data £3.00 (ybrid 2040 series Focus Assembly od £2.00 gence Panel for above. Brand new 9.010 Transistor Rotary Tuner with / 21.97 TV 25 Quadrupler type Q25B equiva State State	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each de and plug. 0 each, 2 for £5.00 with lead and 0 each, 3 for £5.00 leads £3.00 each K. SKT, and 5 each, 3 for £5.00 eleats £3.00 each 5 each, 3 for £5.00 eleats £3.00 each 5 each, 3 for £5.00 eleats 5 each, 5 each, 5 each 5 each 5 each 5 each 5 each, 5 each 5 each
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 butto UHF M 24" x2" With cc GEC H VDR rc Conver, and plu GEC 21 leads Bush C TU25 3 Focus V Decca C	*C'' size Nicads (HP11) which ca f necessary. £10 ea MISCELLANEOUS tripler for CVC45 etc. uput transformer for 23A £4.25 2200 4P/B Transistor Tuner. Suitabilitys sets. 3 hole fixing Bradford Tuner. ntype £4.00 Modulator UHF out Video in. Ch. 30 x4' complete with 9 foot coaxial lee nenection data £3.00 gence Panel for above. Brand new ug 010 Transistor Rotary Tuner with / 1017 Transistor Rotary Tuner with / 51.00 VDR Rods 2¾" x4". Suitable for GEE	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each d and plug. 0 each, 2 for £5.00 with lead and 0 each, 3 for £5.00 with lead and 0 each, 3 for £5.00 leads £3.00 each 5 each, 3 for £5.00 leads 5 each, 3 for £5.00 2 each, 3 for £5.00 5 each, 5 for £5.00 5
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 butto UHF M VDR rc Conver and phi VDR rc Conver and phi UHF M VDR rc Conver and phi Sush C TU25 3 Focus V Decca c Grundij	*C*' size Nicads (HP11) which ca f necessary. £10 ea MISCELLANEOUS tripler for CVC45 etc. uput transformer for 23A £4.25 200 4P/B Transistor Tuner. Suitab lips sets. 3 hole fixing Bradford Tuner. n type £4.00 fodulator UHF out Video in. Ch. 3 vaf complete with 9 foot coaxia les ponection data £3.0 tybrid 2040 series Focus Assembly od £2.00 gence Panel for above. Brand new ug. 010 Transistor Rotary Tuner with / £1.09 TV 25 Quadrupler type Q25B equiva QK £3.00 VDR Rods 23"×4". Suitable for GFE etc. 75 g UHF/VHF Varicap Tuner for 150 £12.50	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 be ach, 2 for £5.00 with lead and 0 each, 2 for £5.00 leads £3.00 each XE, SKT, and S each, 3 for £5.00 leads £3.00 each XE, SKT, and S each, 3 for £5.00 C, each, 3 for £2.00 NGB, 3010GB.
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 buttoo UHF M 24" x 2"5 With cc GEC H VDR r Conver, and plu Ieads Bush C TU25 3 Focus V Decca C Grundij EHT L	*C*' size Nicads (HP11) which ca f necessary. £10 ear MISCELLANEOUS tripler for CVC45 etc. uput transformer for 23A £4.25 200 4P/B Transistor Tuner. Suitabilitys sets. 3 hole fixing Bradford Tuner. In type £4.00 fodulator UHF out Video in. Ch. 3 val complete with 9 foot coaxial lear sonnection data £3.00 tybrid 2040 series Focus Assembly od £2.00 gence Panel for above. Brand new ug. 010 Transistor Rotary Tuner with / £1.09 TV 25 Quadrupler type Q25B equiva QK £3.00 VDR Rods 23"×4". Suitable for GFE etc. 75 g UHF/VHF Varicap Tuner for 150 £12.50 ead with Anode cap (CTV) suitable	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. d and plug. 0 each, 2 for £5.00 with lead and 0 each, 2 for £5.00 leads £3.00 each A 50 £5.00 leads £3.00 each £3.00 each £3.0
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 buttoo UHF M 24"×2"> With cc GEC H VDR r Conver and plu GEC 21 leads Bush C TU25 3 Focus V Decca c Grundij EHT L sets Im EHT C	*C** size Nicads (HP11) which ca f necessary. £10 ear MISCELLANEOUS tripler for CVC45 etc. tuput transformer for 23A £4.25 2300 4P/B Transistor Tuner. Suitab Bradford Tuner. n type £4.00 fodulator UHF out Video in. Ch. 3' *Complete with 9 foot coaxial les onnection data £3.00 (ybrid 2040 series Focus Assembly od £2.00 gence Panel for above. Brand new gence Panel for above. Brand new 10 Transistor Rotary Tuner with / £1.9 TV 25 Quadrupler type Q25B equiva VK £3.00 VDR Rods 21" ×1". Suitable for GE g UHF/VHF Varicap Tuner for 15(£12.50 ead with Anode cap (CTV) suitable long 60 30p per metri	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. d and plug. 9 each, 2 for £5.00 leads £3.00 each AE. SKT, and 5 each, 3 for £5.00 leads £3.00 each AE. SKT, and for £5.00 leads £3.00 each AG. 5 for £5.00 leads £3.00 each AG. 5 for £5.00 chan 10 for £5.00 leads £3.00 each AG. 5 for £5.00 chan 3 for £5.00 c
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 butto UHF M 24"×2" With cc GEC H VDR r Conver, and plu GEC 21 leads Bush C TU25 3 Focus V Decca c Grundij EHT L sets Im EHT C Anti C 4.433 N	*C** size Nicads (HP11) which ca f necessary. £10 ear MISCELLANEOUS tripler for CVC45 etc. triplet ransformer for 23A £4.25 200 4P/B Transistor Tuner. Suitab lips sets. 3 hole fixing Bradford Tuner. n type £4.00 fodulator UHF out Video in. Ch. 3 ×4" complete with 9 foot coaxial les onnection data £3.00 tybrid 2040 series Focus Assembly od £2.00 gence Panel for above. Brand new us. 010 Transistor Rotary Tuner with / £1.9; TV 25 Quadrupler type Q25B equiva OVER Rods 21"×1". Suitable for GEt etc. 75 g UHF/VHF Varicap Tuner for 15(gi UHF/VHF Varicap Tuner for 15(sit2.50 ead with Anode cap (CTV) suitable holong 30p per metro orona Caps	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. d and plug. 0 each, 2 for £5.00 with lead and 0 each, 3 for £5.00 C. p each, 3 for £5.00 C. p each, 3 for £5.00 C. p each, 3 for £3.00 Deach, 2 for £5.00 C. p each, 3 for £3.00 C. p each, 3 for £3.00 Deach, 3 for £3.00 Deach, 3 for £3.00 Deach, 3 for £1.50 c, 10 metres £2.50 3 for £1.50 Deach, 3 for £2.50 Deach,
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 buttoo UHF M 24"×2" With cc GEC H VDR K Conver, and plu GEC 2 leads Bush C TU25 3 Focus V Decca G Grundij EHT L Sets Im EHT C Anti C 4.433 N 750 24 6 MHZ	*C'' size Nicads (HP11) which ca f necessary. £10 ea MISCELLANEOUS tripler for CVC45 etc. uput transformer for 23A £4.25 200 4P/B Transistor Tuner. £4.00 folduator UHF out Video in. Ch. 3i £4.00 folduator UHF out Video in. Ch. 3i £3.00 y'' complete with 9 foot coaxial les £3.00 yod £2.00 gence Panel for above. Brand new £1.9 VDR Rods 21'×1''. Suitable for GE4 £1.50 ead with Anode cap (CTV) suitable 600 'able 30p per metro orona Caps \$1.0 'able 30p per metro for there, ceramic 3 pin \$1.0	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. d and plug. 0 each, 2 for £5.00 with lead and 0 each, 2 for £5.00 leads £3.00 each X 5.00 each X 5.00 each X 5.00 each X 6 for £5.00 leads 5 each, 3 for £5.00 cach, 3 for £5.00 Deach, 3 for £5.00 Deach, 3 for £5.00 Deach, 3 for £5.00 Do Each, 3 for £5.00 Deach, 4
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 buttoo UHF M 24" × 2" With cc GEC H VDR rc Conver, and plu GEC 21 leads Bush C TU25 3 Focus V Decca G Grundig EHT L EHT L EHT L EHT C Anti C 4.433 N 750 24 6 MHZ C 1.437 (TAIYC)	*C'' size Nicads (HP11) which ca f necessary. £10 ea MISCELLANEOUS tripler for CVC45 etc. tiput transformer for 23A £4.25 2300 4P/B Transistor Tuner. £4.25 200 4P/B Transistor Tuner. £4.00 folduator UHF out Video in. Ch. 3i £4.00 ver complete with 9 foot coaxial lea £3.00 yord coatal case £3.00 tybrid 2040 series Focus Assembly £2.00 gence Panel for above. Brand new £2.00 gence Panel for above. Brand new £3.00 VDR Rods 23" × 1". Suitable for GE4 £1.90 ead with Anode cap (CTV) suitable 600 'able 30p per metric orona Caps £1.00 Loudspeaker \$00 per metric sound filters, ceramic 3 pin 0" type 0'' type 50 7200 Control Knobs 50	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 5. d and plug. 0 each, 2 for £5.00 with lead and 0 each, 2 for £5.00 leads £3.00 each A 5.00
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 butto UHF M 24"×2" With cc GEC H VDR r Conver, and plu GEC 21 leads Bush C TU25 3 Focus V Decca C Grundli EHT L Sets Im EHT C Anti C 4,433 N 750 24 6 GHZ "TAIYO PYE C Degaus	*C** size Nicads (HP11) which ca f necessary. £10 ear MISCELLANEOUS tripler for CVC45 etc. triplet ransformer for 23A £4.25 200 4P/B Transistor Tuner. Suitab lips sets. 3 hole fixing Bradford Tuner. n type £4.00 fodulator UHF out Video in. Ch. 3 ×4' complete with 9 foot coaxial les onnection data £3.00 tybrid 2040 series Focus Assembly od £2.00 gence Panel for above. Brand new g. 010 Transistor Rotary Tuner with / £1.9; TV 25 Quadrupler type Q25B equiva OVR Rods 21"×1". Suitable for GEt etc. 75 g UHF/VHF Varicap Tuner for 150 (able 30p per metro orona Caps Mic CTV Crystals £1.0 Loudspeaker : sound filters, ceramic 3 pin 0" type 50 T200 Control Knobs ·VDRs. 14' diam, for RBM etc.	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. di and plug. 0 each, 2 for £5.00 with lead and 0 each, 3 for £5.00 leads £3.00 each KE, SKT, and 5 each, 3 for £5.00 leads 10 each, 2 for £5.00 leads 10 each, 2 for £5.00 leads 10 each, 2 for £5.00 0 each, 3 for £2.00 0 GB, 3010GB. each, 3 for £1.50 0 each, 3 for £1.50 0 each, 4 for £2 p each, 3 for £1.00
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 butto UHF M 24"×2" With cc GEC H VDR r Conver, and plu GEC 21 leads Bush C TU25 3 Focus V Decca C Grundij EHT L sets Im EHT C Annti C Annti C G 4,433 N 750 24 6 MHZ "TAIYA" PYE C Degaus Mains N 242 Sets Sets Sets Sets Sets Sets Convertioner Sets Sets Sets Sets Sets Sets Sets Sets Sets Sets Sets Sets Sets Sets Sets	*C** size Nicads (HP11) which ca f necessary. £10 ear MISCELLANEOUS tripler for CVC45 etc. triplet fransformer for 23A £4.25 200 4P/B Transistor Tuner. Suitab lips sets. 3 hole fixing Bradford Tuner. for todulator UHF out Video in. Ch. 3 ×4' complete with 9 foot coaxial les onnection data £3.00 tybrid 2040 series Focus Assembly od £2.00 gence Panel for above. Brand new us. 010 Transistor Rotary Tuner with / £1.97 TV 25 Quadrupler type Q25B equivi OK & 63.00 VDR Rods 21"×1". Suitable for GEt etc. 75 g UHF/VHF Varicap Tuner for 150 212.05 ead with Anode cap (CTV) suitable orona Caps Mhz CTV Crystals £1.00 Loudspeaker sound filters, ceramic 3 pin O" type 50 T200 Control Knobs ·VDRs. 14' diam, for RBM etc. Neons reenfeed Resistors.	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. d and plug. 0 each, 2 for £5.00 with lead and 0 each, 2 for £5.00 leads £3.00 each NE, SKT, and 5 each, 3 for £5.00 C. 0 each, 3 for £5.00 C. 0 each, 3 for £5.00 C. 0 each, 3 for £3.00 0 beach, 3 beach, 3 beach 0 beach, 3 beach 0 beach
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 butto UHF M 24"×2" With cc GEC H VDR r Conver, and plu GEC 21 leads Bush C TU25 3 Focus V Decca C Grundij EHT L sets Im EHT C Annti C Annti C G 4,433 N 750 24 6 MHZ "TAIYA" PYE C Degaus Mains N 242 Starset Sta	*C'' size Nicads (HP11) which ca f necessary. £10 ea MISCELLANEOUS tripler for CVC45 etc. tiput transformer for 23A £4.25 200 4P/B Transistor Tuner. £4.25 200 4P/B Transistor Tuner. £4.00 fodulator UHF out Video in. Ch. 3i £4.01 fodulator UHF out Video in. Ch. 3i £4.00 fodulator UHF out Video in. Ch. 3i £3.00 gence Panel for above. Brand new £3.00 god £2.00 gence Panel for above. Brand new £1.07 VDR Rods 2!* ×!*. Suitable for GEE equividable 010 Transistor Rotary Tuner with / £1.25 gudf-VHF Varicap Tuner for 150 £1.20 ead with Anode cap (CTV) suitable for GEE orona Caps Mhz CTV Crystals £1.00 Loudspeaker 500 sound filters, ceramic 3 pin 0" 0"type 50 7200 Control Knobs *VDRs. 1" diam, for RBM etc. Nords resistors. seramic, 9 watt, with fusible link. 68.7anoelwaro	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. d and plug. 0 each, 2 for £5.00 with lead and 0 each, 2 for £5.00 leads £3.00 each X 5, 507 £5.00 0 each, 3 for £5.00 C. 0 each, 3 for £5.00 0 each, 3 for £5.00 C. 0 each, 3 for £3.00 0 each, 3 for £3.00 0 each, 3 for £1.50 0 each, 3 for £1.50 0 each, 3 for £1.50 0 each, 3 for £1.50 0 each, 3 for £1.00 8 for £1.00 10 for £1.00 8 for £1.00 10 for £1.00
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 buttoo UHF M VDR π GEC H VDR π GEC 2 leads Bush C TU25 3 Focus V Decca C Grundit EHT L sets Im EHT C Anti C 4.433 N TSΩ 24 6 MHZ "TAIYC PYE C Degaus Mains N 2k2 Ser White c Philips (2k2 Ser White c Philips (*C'' size Nicads (HP11) which ca f necessary. £10 ea MISCELLANEOUS tripler for CVC45 etc. tiput transformer for 23A £4.25 2300 4P/B Transistor Tuner. Suitabilitys sets. 3 hole fixing Bradford Tuner. £4.00 Iduator UHF out Video in. Ch. 3: 4 .00 Iduator UHF out Video in. Ch. 3: 4 .00 Variation of the set of the	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. d and plug. 0 each, 2 for £5.00 leads £3.00 each X 5.00 fill00 X 5.00 f
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 buttoo UHF M VDR π GEC H VDR π GEC 2 leads Bush C TU25 3 Focus V Decca C Grundit EHT L sets Im EHT C Anti C 4.433 N TSΩ 24 6 MHZ "TAIYC PYE C Degaus Mains N 2k2 Ser White c Philips (2k2 Ser White c Philips (*C** size Nicads (HP11) which cases for necessary. £10 eastern for necessary. £10 eastern WISCELLANEOUS tripler for CVC45 etc. tiput transformer for 23A 23A £4.25 2300 4P/B Transistor Tuner. £4.25 2300 4P/B Transistor Tuner. £4.25 2300 4P/B Transistor Tuner. £4.25 200 4P/B Transistor Tuner. £4.00 fodulator UHF out Video in. Ch. 3: £4.00 fodulator UHF out Video in. Ch. 3: £4.00 fodulator UHF out Video in. Ch. 3: £2.00 gence Panel for above. Brand new £2.00 gence Panel for above. Brand new £1.9 TV 25 Quadrupler type Q25B equivalog £3.00 VDR Rods 2!* ×!*. Suitable for GE £1.2 sound filters, ceramic 3 pin 0* £1.0 long 60 lable 30p per metricorona Caps of' type 50 T200 Control Knobs £1.0 VDRs. I! diam, for RBM etc. Neons voto Control Knobs £1.2 Discharge probe, with heavible link. £1.2 Diong probe, with heavible link. <td< th=""><th>d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. d and plug. 0 each, 2 for £5.00 with lead and 0 each, 2 for £5.00 with lead and 0 each, 3 for £5.00 each 3 for £5.00 each 3 for £5.00 each 3 for £5.00 each 3 for £5.00 casch, 3 for £5.00 casch, 3 for £5.00 0 each, 3 for £3.00 0 each, 3 for £1.00 0 each, 3 for £1.00 0 each, 3 for £1.00 0 each, 3 for £1.00 0 for £1.00 0 each, 3 for £1.00 8 for £1.00 0 each, 3 for £1.00 8 for £1.00 0 each, 3 for £1.00 8 for £1.00 0 each, 3 for £3.00 0 each, 3 for £1.00 8 for £1.00 0 each, 3 for £1.00 0 each, 3 for £1.00 10 for £1.00 10 for £1.00 10 each, 3 for £3.00</th></td<>	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. d and plug. 0 each, 2 for £5.00 with lead and 0 each, 2 for £5.00 with lead and 0 each, 3 for £5.00 each 3 for £5.00 each 3 for £5.00 each 3 for £5.00 each 3 for £5.00 casch, 3 for £5.00 casch, 3 for £5.00 0 each, 3 for £3.00 0 each, 3 for £1.00 0 each, 3 for £1.00 0 each, 3 for £1.00 0 each, 3 for £1.00 0 for £1.00 0 each, 3 for £1.00 8 for £1.00 0 each, 3 for £1.00 8 for £1.00 0 each, 3 for £1.00 8 for £1.00 0 each, 3 for £3.00 0 each, 3 for £1.00 8 for £1.00 0 each, 3 for £1.00 0 each, 3 for £1.00 10 for £1.00 10 for £1.00 10 each, 3 for £3.00
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 buttoo UHF M VDR π GEC H VDR π GEC 2 leads Bush C TU25 3 Focus V Decca C Grundit EHT L sets Im EHT C Anti C 4.433 N TSΩ 24 6 MHZ "TAIYC PYE C Degaus Mains N 2k2 Ser White c Philips (2k2 Ser White c Philips (*C** size Nicads (HP11) which ca f necessary. £10 ear MISCELLANEOUS tripler for CVC45 etc. tiput transformer for 23A £4.25 230 4P/B Transistor Tuner. Suitabilitys sets. 3 hole fixing Bradford Tuner. £4.20 foldulator UHF out Video in. Ch. 3i *Complete with 9 foot coaxial lear onnection data £3.00 (ybrid 2040 series Focus Assembly od gence Panel for above. Brand new gence Panel for above. Brand new fg. 010 Transistor Rotary Tuner with / £1.9 TV 25 Quadrupler type Q25B equiva VDR Rods 23"×3". Suitable for GF etc. 75 g UHF/VHF Varicap Tuner for 150 able 30p per metro orona Caps Mhz CTV Crystals £1.0 Loudspeaker sound filters, ceramic 3 pin 0" type 50 T200 Control Knobs vDRs. 11" diam, for RBM etc. Neons reenfeed Resistors. seramic, 9 watt, with fusible link. G8 Transductor. £1.2 Discharge probe, with heavily insulat ad and chassis connector. 60	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. d and plug. 0 each, 2 for £5.00 with lead and 0 each, 2 for £5.00 with lead and 0 each, 3 for £5.00 C. 0 each, 3 for £5.00 C. 0 each, 3 for £5.00 C. 0 each, 3 for £3.00 0 each, 3 for £3.00 0 each, 3 for £3.00 0 each, 3 for £3.00 0 each, 3 for £1.00 0 each, 3 for £1.00 0 each, 3 for £1.00 0 for £1.00 0 each, 3 for £1.00 8 for £1.00 0 each, 3 for £1.00 8 for £1.00 0 each, 3 for £1.00 8 for £1.00 0 each, 3 for £1.00 10
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 buttoo UHF M VDR π GEC H VDR π GEC 2 leads Bush C TU25 3 Focus V Decca C Grundit EHT L sets Im EHT C Anti C 4.433 N TSΩ 24 6 MHZ "TAIYC PYE C Degaus Mains N 2k2 Ser White c Philips (2k2 Ser White c Philips (*C** size Nicads (HP11) which cases for necessary. £10 easonal filters, caramic 3 provide a size and for the size size and for the size size and for the size size size size size size size siz	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 6. d and plug. 0 each, 2 for £5.00 with lead and 0 each, 2 for £5.00 with lead and 0 each, 3 for £5.00 leads £3.00 each N. 5 for £5.00 0 each, 3 for £5.00 0 each, 3 for £5.00 0 or split Diodes p each, 3 for £1.00 0 each, 3 for £1.50 5 for £1.00 0 each, 3 for £1.50 0 for £1.00 0 each, 3 for £1.00 8 for £1.00 0 each, 3 for £1.00 10 for £1.0
BG100 Line ou RBM82 ITT VC and Phi Decca I 5 buttoo UHF M VDR π GEC H VDR π GEC 2 leads Bush C TU25 3 Focus V Decca C Grundit EHT L sets Im EHT C Anti C 4.433 N TSΩ 24 6 MHZ "TAIYC PYE C Degaus Mains N 2k2 Ser White c Philips (2k2 Ser White c Philips (*C** size Nicads (HP11) which ca f necessary. £10 ear MISCELLANEOUS tripler for CVC45 etc. triplet ransformer for 23A £4.25 2300 4P/B Transistor Tuner. Suitabilitips sets. 3 hole fixing Bradford Tuner. 54.25 2000 4P/B Transistor Tuner. Suitabilitips sets. 3 hole fixing Bradford Tuner. 64.00 fodulator UHF out Video in. Ch. 3 Ver complete with 9 foot coaxial lear onnection data £3.00 (lybrid 2040 series Focus Assembly od £2.00 gence Panel for above. Brand new gence Panel for Brand for Brand for the panel for the set panel for t	d. Contain 10 n be replaced ch, 3 for £25. only £3.50 each, 3 for £10.00 le for some Pye £2.75 each each, 4 for £12.00 5. d and plug. 0 each, 2 for £5.00 with lead and 0 each, 2 for £5.00 leads £3.00 each A 5.00

threads. **ONLY £2.50** ſ

each type £6.00. **GEMINI ELECTRONIC COMPONENTS**

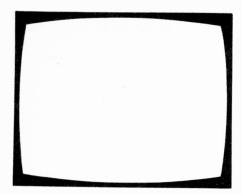Dept. TV, The Warehouse, Speedwell Street, London S.E.8. Please quote ZED code where shown. Send cheque* or Postal Order. Add 60p P&P and 15% VAT. *Schools etc. SEND OFFICIAL ORDER. Allow up to 28 days for delivery. Most orders despatched same day. ZED PACKS now available for CALLERS at 50 Deptford Broadway, London, S.E.8. Send large S.A.E. for list of Quantity, Prices and Clearance Lines etc.



TELEVISION

August 1983

Vol. 33, No. 10 Issue 394

COPYRIGHT

[©]IPC Magazines Limited, 1983, Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

SUBSCRIPTIONS

An annual subscription costs £11 in the UK, £12 overseas (by surface mail). Send orders with payment to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex.

BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at £110p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in Television, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope. Requests for advice in dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

TELEVISION AUGUST 1983


this month

513	Leader	

Teletopics 514 News, comment and developments. 516 VCR Clinic Features of some recent machines plus fault notes from Derek Snelling, Mike Sarre, T. L. Bingham, Les Harris and Michael J. Cousins, T.Eng. (C.E.I.). 520 The Betamax Video System, Part 1 by Eugene Trundle Most of our previous articles on VCRs have concentrated on VHS or V2000 machines. This new series sets out to redress the balance. Basic features of the Betamax system plus notes on various models from Sony, Sanyo and Toshiba. 524 CTV Battery Operation by George R. Wilding Monochrome portables work happily enough with a 12V battery connected directly. Colour portables, which require higher voltage supply lines, call for something more. A look at some of the techniques in use and an account of the operation of the Thorn TA126 converter unit. 526 Dotty Daydreams by Les Lawry-Johns Les's sister-in-law may be o.k., but her son seems to be a source of concern. Plus various visitations to this well known high street emporium. 527 Servicing the Philips TX Chassis by John Coombes Large numbers of Pye and Philips monochrome portables are fitted with this chassis. There are various circuit features and fault finding procedures worth knowing about, also one or two modifications. 530 Vintage TV: The Pilot Model VS9 by Chas E. Miller Pilot's radio sets before and just after the war were distinctive, and their first telly continued the tradition: It used American valve types and featured a well designed video circuit and an r.f. oscillator e.h.t. system. **Next Month in Television** 531 **TV Fault Finding** 532 Notes on TV faults from George R. Wilding, John Coombes, T. L. Bingham, Peter H. Dolman and Mick Dutton. VCR Servicing, Part 20 533 by Mike Phelan This time the 3V23's signal circuits, including the frequency halving and cue features on the audio panel. A Matter of Safety 537 by Tony Thompson TV servicing is a dangerous and potentially lethal business, so it pays to be aware of possible hazards and the precautions required. 539 Letters 541 Long-distance Television by Roger Bunney Reports on DX reception and conditions and news from abroad. Details of a simple braid break filter suggested by the Home Office. 543 Service Briefs: Thorn Modification notes and servicing hints from recent issues of Ferguson Feedback. 544 **Service Bureau** 545 Test Case 248

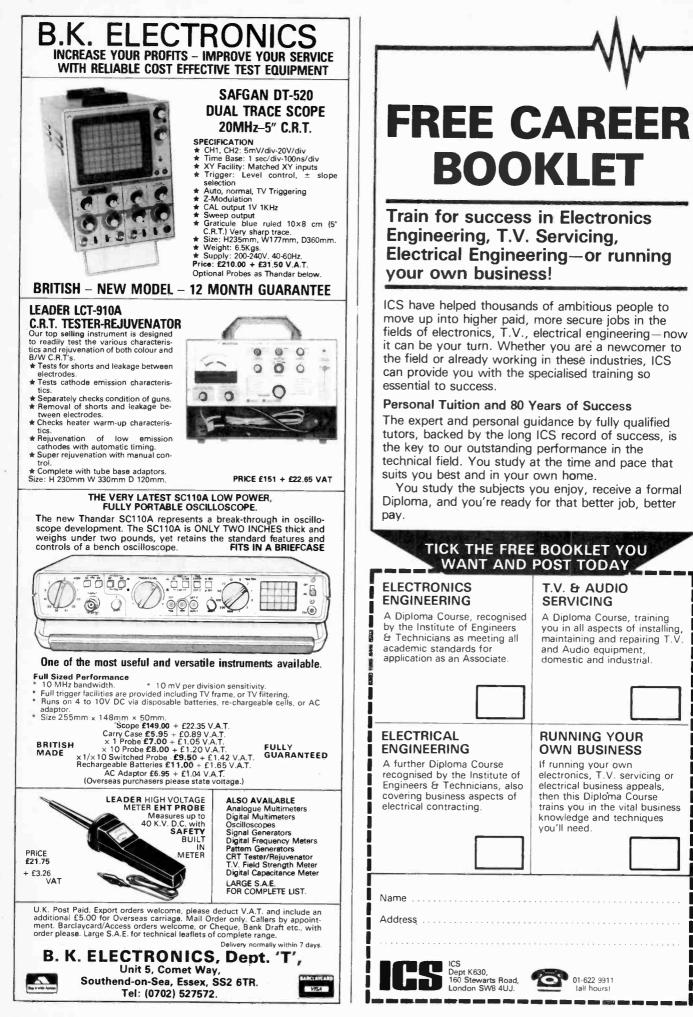OUR NEXT ISSUE DATED SEPTEMBER WILL BE PUBLISHED ON AUGUST 17





P. V. TL 38A WATER STREET, AC TRADE COUNTER OPE	CRINGTON, LANCS	hrough, we lo the rest. SBB5 6PX.	OF T	hone: Accringto Accringto SUPPLIEF ELEVISION COM	on (0254) 32611 RS
INTEGRATED CIRCUITS TA: AN240 3.84 MSN5807 7.87 AN240 3.91 MS1513L 2.00 TA: AN240 3.91 MS1513L 2.00 TA: AN2140 3.91 MS1513L 2.00 TA: CA555 46 SA5560S 1.89 TA: CA741 25 SA550S 1.89 TA: CA748 45 SA5580 2.90 TA: CA3055 1.80 SA5580 2.90 TA: CA3055 1.80 SA5580 2.90 TA: CA3055 1.80 SA5580 2.90 TA: LA4021 3.27 SL301B 5.50 TA: LA423 3.57 SL1310 1.80 TA: LA4402 3.28 SL76544 2.05 TA: LC7120 5.81 SN76023N 2.00 TA: LC7120 5.81 SN76115N 2.27 TA:	7202P 4.27 TBA700 2 7204P 4.27 TBA750 2 7204P 3.77 TBA750 2 7205AP 3.72 TBA800 2 7205P 3.40 TBA800 2 7204P 3.40 TBA800 2 7204P 3.40 TBA800 2 7202P 5.98 TBA900 2 7222 2.42 TBA900 2 7223P 5.98 TBA950(2X) 2 7230P 5.98 TBA950(2X) 2 7230P 5.98 TBA950(2X) 2 7230P 5.98 TBA950(2X) 2 7230P 5.98 TBA950(2X) 2 72050 7.16 7 10.490 6009P 4.39 TCA900 2 A300 58 TCA900 2 A300 58 TCA900 2 A350A 60 TDA440 <	212 TDA2581 3.30 7906 254 TDA2590 3.25 7908 281 TDA2591 2.95 7915 1.62 TDA2593 2.95 7915 1.10 TDA2593 2.95 7915 1.10 TDA2593 2.95 7915 3.04 TDA2581 3.07 7918 3.94 TDA2580 3.40 7912 3.05 TDA2580 3.40 79115 3.05 TDA2580 1.35 791.15 3.05 TDA2580 1.35 791.15 3.06 TDA2580 2.90 791.24 2.00 TDA3580 2.50 792.4 2.10 TDA3580 2.50 791.15 3.05 TDA3580 2.50 791.24 2.10 TDA3580 2.50 792.4 2.20 UPC1182H 2.95 2.95 2.90 UPC1182H 2.95 2.95 2.50 UPC1186H<	98 T.T.L. 74LS 98 74L500 19 98 74L502 19 98 74L504 21 98 74L504 21 98 74L504 21 98 74L504 21 72 74L509 19 72 74L504 19 72 74L514 14 74L514 45 74 74L514 45 74 74L522 19 74 74L526 19 74 74L527 19 74 74L532 19 74 74L532 19 74 74L532 19 74 74L532 19 74	174(S33) 19 14(S42) 33 74(S38) 20 74(S42) 35 74(S42) 20 74(S107) 46 74(S42) 36 74(S107) 46 74(S42) 36 74(S107) 46 74(S42) 36 74(S112) 27 74(S44) 80 74(S112) 27 74(S44) 80 74(S112) 27 74(S45) 19 74(S112) 27 74(S54) 19 74(S123) 52 74(S57) 28 74(S124) 46 74(S75) 26 74(S138) 48 74(S76) 22 74(S153) 44 74(S86) 60 74(S155) 44 74(S86) 62 74(S155) 44 74(S86) 62 74(S155) 44	74LS160 60 74LS251 54 74LS161 60 74LS253 1.00 74LS162 85 74LS275 53 74LS163 60 74LS258 67 74LS164 65 74LS273 80 74LS164 65 74LS273 80 74LS174 57 74LS283 70 74LS191 66 74LS233 70 74LS192 65 74LS323 1.10 74LS194 66 74LS335 1.10 74LS192 65 74LS335 1.10 74LS193 66 74LS366 36 74LS194 80 74LS367 36 74LS197 80 74LS368 36 74LS241 80 74LS373 99 74LS243 76 74LS373 90 74LS245 1.18 74LS245 1.18
MC1330P 90 SN76533N 1.70 TB MC1349 1.99 SN76533N 2.49 1 MC1349 1.99 SN76033N 2.49 1 MC1350 1.50 SN76544N 2.35 TB MC1352 1.75 SN76650N 1.05 TB MC13491 1.50 SN76660N 80 TB MC1495L 3.00 SN76660N 80 TB MC140401BCP 66 SN76530A 1.47 TB MC1404UB 43 SV153 2.14 TB ML231/ETTR8016 TA7051P 95 TB ML232 2.20 TA7051P 3.43 TB ML236 5.35 TA7108P 3.46 TB ML236 2.50 TA7130P 2.43 TB ML238 6.00 TA7132P 3.76 TB ML232 2.92 TA714P 95 TB ML236 2.18 TA7130P	A120A 80 1DA1170 (A),(S),(AS),(SA). TDA1170 A120B 1.30 TDA1170 A120B 1.30 TDA1200 A120SB 1.37 TDA1270 A120U 1.10 TDA1327 A395 1.20 TDA1352B TDA1412 A440N (TBA1441) TDA202 A440N (TBA1441) TDA202 (A440P 2.50 TDA2190 TDA2190 TDA2190 TDA2200 (A480(Q) 1.50 TDA2220 A450(Q) 1.38 TDA2521 TDA2522 A450(Q) 1.38 TDA2522	A.D UPC1212C 1.34 YE 3.50 UPC123DH 3.95 I.C. SI 3.50 UPC135DC 4.15 DLL to 3.50 UPC135DC 4.15 Buto 3.55 UPC1367H 4.49 8 way 1.70 UPC137H 4.49 16 way 5.95 VOLTAGE REG. 78 16 way 2.80 VOLTAGE REG. 78 22 way 2.80 YOLTAGE REG. 78 24 way 2.80 Y017 7812 78 14 way 2.80 YOLTAGE REG. 78 14 way 2.80 YBL 57 78 14 way 2.40 7818 78 16 way 2.40 7818 78 18 way <t< td=""><td>22 00000 23 40018 21 40028 22 40028 21 32 40018 21 32 32 40118 22 32 332 40128 23 40138 33 40148 7 40168 37 4018 7 40178 66 34 40188 7 40218 7 40228 7 40228 7 40228 7 40228 7 36 40258 2 2</td><td>4028B 64 40708 22 4029B 90 40718 22 4032B 1.04 40728 22 4035B 104 40738 22 4035B 99 40738 22 40408 72 40768 80 4042B 56 40778 22 40408 71 40768 80 4042B 56 40778 22 40408 71 40788 24 4043B 71 40948 1.56 40494B 24 40948 1.56 40494B 24 40948 1.56 40494B 72 41618 72 40505B 72 41618 72 0 40538 72 41638 72 0 40558 72 41638 72 0 40568 43<45058</td> 1.88 1 40668 43<45058</t<>	22 00000 23 40018 21 40028 22 40028 21 32 40018 21 32 32 40118 22 32 332 40128 23 40138 33 40148 7 40168 37 4018 7 40178 66 34 40188 7 40218 7 40228 7 40228 7 40228 7 40228 7 36 40258 2 2	4028B 64 40708 22 4029B 90 40718 22 4032B 1.04 40728 22 4035B 104 40738 22 4035B 99 40738 22 40408 72 40768 80 4042B 56 40778 22 40408 71 40768 80 4042B 56 40778 22 40408 71 40788 24 4043B 71 40948 1.56 40494B 24 40948 1.56 40494B 24 40948 1.56 40494B 72 41618 72 40505B 72 41618 72 0 40538 72 41638 72 0 40558 72 41638 72 0 40568 43<45058	45188 76 45568 48 45198 64 45608 1.76 45208 76 45618 74 45218 1.68 45668 1.20 45228 88 45808 3.60 45228 88 45818 1.84 45278 1.20 45828 800 45288 88 45818 1.00 45298 1.04 45298 1.00 45298 1.4 45298 1.00
SEMICONDUCTORS BC212 9 BC1 AC107 35 (A),(B),(C) 20 BC212L 13 BD1 AC126 30 BC114 12 BC213 13 BD1 AC127 32 BC115 17 BC213B 10 BD1 AC128 32 BC115 17 BC213B 10 BD1 AC128 40 BC117 30 BC214 9 BD1 AC142K 40 BC117 30 BC214 9 BD1 AC144K 39 BC118 24 BC214 9 BD1 AC142K 48 BC117 30 BC214 9 DD1 AC176 35 BC139 29 BC237 14 BD1 AC176 35 BC142 30 BC251A 18 DD1 AC186 48 BC147 13 BC252A 12 BD1 AC188 35 <	336 388 DB955 1.39 BF310 3 337 38 BD696 1.50 BF311 3 337 38 BD696 1.50 BF331 3 33 35 BD707 55 BF331 3 339 35 BD707 55 BF337 4 144 1.70 BF115 38 BF337 4 144 1.70 BF117 36 BF335 5 159 65 BF127 47 BF337 3 160 1.90 BF127 47 BF353 1 179 70 BF158 18 BF457 3 182 1.20 BF160 27 BF489 4 133 75 BF167 24 BF459 1 201 85 BF173 22 BF380 1.3 202 91 BF179 28 BF743 3 <td>Hat BT102/500 R2540 2.80 28C643 120 120 RCA1633 90 2SC1095 16 BT106 1.60 RCA1633 90 2SC11095 16 BT107 1.68 IP293C 43 2SC1173 11 BT108 1.68 IP293C 43 2SC1307 11 BT101 1.68 IP193C 43 2SC1307 11 BT101 1.68 IP193C 43 2SC1307 11 BT101 3.66 TIP31C 55 2SC1472 11 BT103 3.66 TIP32C 42 2SC1527 11 BT103 3.66 TIP32C 42 2SC1527 13 BU105 1.25 TIP44C 47 2SC1202 13 BU105 1.25 TIP44C 47 2SC2027 13 BU106 1.80 TIP47 70 2SC2027 14 BU126 1.75 TIP47<!--</td--><td>5 1.72 5mm 1779E 17 2.20 11 2 TYPE 17 2.20 11 2 TYPE 17 2.30 74 6 14 2.73 Green 14 2.73 Green 14 3.00 74 10 w 14 1.57 Amber 22 2.67 2.90 71 TYPE 3.142 Amm 12 2.60 Green 14 3.250 Green 14 3.250 Green 14 3.250 Vellow 14 1.34 2.20 COLOUR Red Dnly B COLOUR B COLOUR</td><td>DY802 98 EF184 1.09 DY867,7 66 EH90 1.02 ECC81 1.08 EL34 3.50 ECC82 98 EL94 1.05 ECC82 98 EL94 1.05 ECC83 1.07 EL90 82 ECC84 80 EY86,7 68 ECC84 80 EY86,7 68 ECC84 80 EY86,7 68 EC780 80 GY36,1 50 EC780 80 GY36,1 56 EC780 80 GY36,1 56 EC781 1.50 K176 8.50 EC181 1.60 K176 8.50 EC184 1.65 K178 12.00 EC182 1.30 PC37 1.65 EC182 1.30 PC37 1.65 EC184 1.99 PCC85 85 EC182 1.36 PCF80 1.00</td><td>PCF200 1.35 PL95 1.00 PCF800 1.38 PL504 1.65 PCF801 1.13 PL508 2.90 PCF802 1.2 PL509/19 5.30 PCF805 1.80 PY88 81 PCF806 1.30 PY500 2.30 PCF808 1.63 PY800/1 69 PCH200 1.45 UCH81 2.25 PCL82 1.20 UCL83 1.82 PCL80 2.UY85 1.35 PCL805 1.09 PL802T 4.00 PD500 2.33 40KD6 5.30 PC180 1.09 PL802T 4.00 PJ36 1.87 170.44A 1.60 PL30 1.43 12BY7A 3.75 PL81 94 3A728 2.25 PL83 1.43 12BY7A 3.75 PL84 84 WIREWOUND <u>RESISTORS *</u> 4W IR-100 22X 229</td></td>	Hat BT102/500 R2540 2.80 28C643 120 120 RCA1633 90 2SC1095 16 BT106 1.60 RCA1633 90 2SC11095 16 BT107 1.68 IP293C 43 2SC1173 11 BT108 1.68 IP293C 43 2SC1307 11 BT101 1.68 IP193C 43 2SC1307 11 BT101 1.68 IP193C 43 2SC1307 11 BT101 3.66 TIP31C 55 2SC1472 11 BT103 3.66 TIP32C 42 2SC1527 11 BT103 3.66 TIP32C 42 2SC1527 13 BU105 1.25 TIP44C 47 2SC1202 13 BU105 1.25 TIP44C 47 2SC2027 13 BU106 1.80 TIP47 70 2SC2027 14 BU126 1.75 TIP47 </td <td>5 1.72 5mm 1779E 17 2.20 11 2 TYPE 17 2.20 11 2 TYPE 17 2.30 74 6 14 2.73 Green 14 2.73 Green 14 3.00 74 10 w 14 1.57 Amber 22 2.67 2.90 71 TYPE 3.142 Amm 12 2.60 Green 14 3.250 Green 14 3.250 Green 14 3.250 Vellow 14 1.34 2.20 COLOUR Red Dnly B COLOUR B COLOUR</td> <td>DY802 98 EF184 1.09 DY867,7 66 EH90 1.02 ECC81 1.08 EL34 3.50 ECC82 98 EL94 1.05 ECC82 98 EL94 1.05 ECC83 1.07 EL90 82 ECC84 80 EY86,7 68 ECC84 80 EY86,7 68 ECC84 80 EY86,7 68 EC780 80 GY36,1 50 EC780 80 GY36,1 56 EC780 80 GY36,1 56 EC781 1.50 K176 8.50 EC181 1.60 K176 8.50 EC184 1.65 K178 12.00 EC182 1.30 PC37 1.65 EC182 1.30 PC37 1.65 EC184 1.99 PCC85 85 EC182 1.36 PCF80 1.00</td> <td>PCF200 1.35 PL95 1.00 PCF800 1.38 PL504 1.65 PCF801 1.13 PL508 2.90 PCF802 1.2 PL509/19 5.30 PCF805 1.80 PY88 81 PCF806 1.30 PY500 2.30 PCF808 1.63 PY800/1 69 PCH200 1.45 UCH81 2.25 PCL82 1.20 UCL83 1.82 PCL80 2.UY85 1.35 PCL805 1.09 PL802T 4.00 PD500 2.33 40KD6 5.30 PC180 1.09 PL802T 4.00 PJ36 1.87 170.44A 1.60 PL30 1.43 12BY7A 3.75 PL81 94 3A728 2.25 PL83 1.43 12BY7A 3.75 PL84 84 WIREWOUND <u>RESISTORS *</u> 4W IR-100 22X 229</td>	5 1.72 5mm 1779E 17 2.20 11 2 TYPE 17 2.20 11 2 TYPE 17 2.30 74 6 14 2.73 Green 14 2.73 Green 14 3.00 74 10 w 14 1.57 Amber 22 2.67 2.90 71 TYPE 3.142 Amm 12 2.60 Green 14 3.250 Green 14 3.250 Green 14 3.250 Vellow 14 1.34 2.20 COLOUR Red Dnly B COLOUR B COLOUR	DY802 98 EF184 1.09 DY867,7 66 EH90 1.02 ECC81 1.08 EL34 3.50 ECC82 98 EL94 1.05 ECC82 98 EL94 1.05 ECC83 1.07 EL90 82 ECC84 80 EY86,7 68 ECC84 80 EY86,7 68 ECC84 80 EY86,7 68 EC780 80 GY36,1 50 EC780 80 GY36,1 56 EC780 80 GY36,1 56 EC781 1.50 K176 8.50 EC181 1.60 K176 8.50 EC184 1.65 K178 12.00 EC182 1.30 PC37 1.65 EC182 1.30 PC37 1.65 EC184 1.99 PCC85 85 EC182 1.36 PCF80 1.00	PCF200 1.35 PL95 1.00 PCF800 1.38 PL504 1.65 PCF801 1.13 PL508 2.90 PCF802 1.2 PL509/19 5.30 PCF805 1.80 PY88 81 PCF806 1.30 PY500 2.30 PCF808 1.63 PY800/1 69 PCH200 1.45 UCH81 2.25 PCL82 1.20 UCL83 1.82 PCL80 2.UY85 1.35 PCL805 1.09 PL802T 4.00 PD500 2.33 40KD6 5.30 PC180 1.09 PL802T 4.00 PJ36 1.87 170.44A 1.60 PL30 1.43 12BY7A 3.75 PL81 94 3A728 2.25 PL83 1.43 12BY7A 3.75 PL84 84 WIREWOUND <u>RESISTORS *</u> 4W IR-100 22X 229
AF124 48 BC172 15 BCA61 30 BD AF125 46 BC172A 10 BC547 13 BD AF126 46 BC172A 10 BC547 13 BD AF127 38 BC172C 10 BC548 13 BD AF127 38 BC172C 10 BC542 27 BD AF139 55 BC173C 12 BC342 27 BD AF178 1.54 BC174A/B BC559 7 BD AL102 2.00 BC177 27 BC559 7 BD AU107 2.00 BC182 12 BU116 45 BD BC108 <td>227 57 BF196 16 BFY51 238 65 BF197 16 BFY52 243 85 BF198 18 BFY90 244 85 BF198 18 BFY90 244 85 BF198 18 BFY90 244 85 BF198 21 BR100 34 410 79 BF2200 35 BR1010 34 437 96 BF225 20 BRC4443 50 438 94 BF241 25 BRC4444 507 52 BF257 28 BRY56 505 55 BRX46 5050 55 BF258 25 BRY56 5510 60 BF259 35 BSV57B 520 35 BSV57B 520 58 BF271 24 BT00 1 1 1 1566 BF273 24 BT00 1 1 1 1 15656 35 BF273 <</td> <td>24 BU500 2.30 2X8/3702 11 24 BU526 2.46 2X8/3703 10 36 BU507 2.94 2X8/3705 10 34 BU/X81A 2X8/3706 10 34 BU/X81A 2X8/3706 10 34 BU/X81A 2X8/3706 10 34 BU/X8246 48 MIST 36 M2010 19 2X8/326 48 VA1104 35 OT121 131<2X8236</td> 69 VA1040 51 VA1053 36 R2010B 1.92 2X8107 7 5 52 X41035 36 R2010B 1.92 2X8107 5 9 <t< td=""><td>V518P 76 PANEL CLIPS 3mm 4 ORS 75 55 6. FALTERS 40 75 55 6. FALTERS 40 75 55 6. FALTERS 40 1.50 1.30 1.39 10.632/Mhz 6.00 75 6. FALTERS 4. 00 8. Mhz 74 1.30 1.39 10.632/Mhz 6.00 75 75 75 75 75 75 75 75 75 75</td><td>PHILIPS 210/300 Mono 10.00 PHILIPS G8 8.75 PHILIPS G9 7.75 PHILIPS G1 13.50 PYE 691/3 17.75 PYE 691/3 17.75 PYE 697 (Printed) 14.50 PYE 713/731 10.00 PYE 725 90° 10.50 PYE 725 90° 10.50 DECCA 1700 9.00 DECCA 1700 9.00 DECCA 1700 9.00 DECCA 1700 9.00 DECCA 2230 8.58 DECCA 1700 9.50 GEC 2110 9.45 GEC 2200 6.65 ITT CVC 25/30/32 8.65</td><td>11 // 1R-22K 25p 17 // 1R-22K 28p (Preferred values)* CARBON RESISTORS * 1// 3R3-8M2 20 1// 10R-10M 30 Sold in packs of 10 per type SOLDERING EQUIPMENT WELLER Iron 15// 4.31 WELLER Iron 25// 4.31</td></t<>	227 57 BF196 16 BFY51 238 65 BF197 16 BFY52 243 85 BF198 18 BFY90 244 85 BF198 18 BFY90 244 85 BF198 18 BFY90 244 85 BF198 21 BR100 34 410 79 BF2200 35 BR1010 34 437 96 BF225 20 BRC4443 50 438 94 BF241 25 BRC4444 507 52 BF257 28 BRY56 505 55 BRX46 5050 55 BF258 25 BRY56 5510 60 BF259 35 BSV57B 520 35 BSV57B 520 58 BF271 24 BT00 1 1 1 1566 BF273 24 BT00 1 1 1 1 15656 35 BF273 <	24 BU500 2.30 2X8/3702 11 24 BU526 2.46 2X8/3703 10 36 BU507 2.94 2X8/3705 10 34 BU/X81A 2X8/3706 10 34 BU/X81A 2X8/3706 10 34 BU/X81A 2X8/3706 10 34 BU/X8246 48 MIST 36 M2010 19 2X8/326 48 VA1104 35 OT121 131<2X8236	V518P 76 PANEL CLIPS 3mm 4 ORS 75 55 6. FALTERS 40 75 55 6. FALTERS 40 75 55 6. FALTERS 40 1.50 1.30 1.39 10.632/Mhz 6.00 75 6. FALTERS 4. 00 8. Mhz 74 1.30 1.39 10.632/Mhz 6.00 75 75 75 75 75 75 75 75 75 75	PHILIPS 210/300 Mono 10.00 PHILIPS G8 8.75 PHILIPS G9 7.75 PHILIPS G1 13.50 PYE 691/3 17.75 PYE 691/3 17.75 PYE 697 (Printed) 14.50 PYE 713/731 10.00 PYE 725 90° 10.50 PYE 725 90° 10.50 DECCA 1700 9.00 DECCA 1700 9.00 DECCA 1700 9.00 DECCA 1700 9.00 DECCA 2230 8.58 DECCA 1700 9.50 GEC 2110 9.45 GEC 2200 6.65 ITT CVC 25/30/32 8.65	11 // 1R-22K 25p 17 // 1R-22K 28p (Preferred values)* CARBON RESISTORS * 1// 3R3-8M2 20 1// 10R-10M 30 Sold in packs of 10 per type SOLDERING EQUIPMENT WELLER Iron 15// 4.31 WELLER Iron 25// 4.31
26" A66/120X 34.00 26" A67/120X 34.00 22" A56/140X (410X) 110° 36.00 26" A66/140X (410X) 110° 36.00 26" A66/140X (410X) 110° 36.00 20" A51/161X 55.00	MULL A31/510 110° 12″ 18.50 MULL A31/510 110° 14″ 20.00 A50/120 V/R 110° 20″ 15.00 A50/120 V/R 110° 24″ 17.50 VEGA 12″ 30° (Jap Types) 15.00 CMELS20 (15″ Mono) 1500 MULL A320 (200 COLOUREX) 18″ A47/343X 19″ A49/120X 20″ A51/110X 20″ A51/110X 25″ A63/200X 26″ A66/120X 27″ A56/120X 28″ A67/120X 28″ A65/120X 53.00 1 year warranty Option on 4 years Quetes on delivery and glass	PHILIPS //idt G8 Knobs Sm/Lg 0 389 h G8 Knobs Sm/Lg 0 389 h G8 Knobs Sm/Lg 0 389 h E.W. Correction Coll 1.95 Transductor 90° 2.40 RGB 10G Diodes 50 Switch K30 2.60 Focus Unit G11 5.90 T93 3W resist. 60 T91 Speakers Sm 4.10 1500 Controls 70K Contrast RK5 excl 32 Focus Control Unit 1.33 VK5 excl 32 Focus Control Unit 1.33 Thorn/GEC Vide 8500 Mains Fitter Choke 6.50 6500 Mains Fitter Choke 6.50 6500 Mains Fitter Choke 6.50	Control(30) 50 Modulohm 60 Height Control 25 Focus Control 2.20 Aains Filter Choke 6.50 <u>NEW PRODUCTS</u> Foletext Adaptor 127.00	THORN 3000 SCAN 7.95 THORN 8000 11.33 THORN 8000 10.65 THORN 8000 10.65 THORN 9000 10.65 THORN 1591 8.68 THORN 1591 8.68 THORN 1691 9.68 THORN 1691 9.68 THORN 1691 9.75 PHURN 1615 9.75 PHURN 1615 9.75 RANK BUSHRANGER 10.00 NEW PRODUCTS Fluorescent Torch Fluorescent Torch 6.50 Travel Plugs 3.50 Philips Clock Radio 21.39	WELLER Gun 12.00 Pair Tips Gun 42 3/16" Tips iron 51 ANTEX 15-W Iron 520 ANTEX 15-W Iron 520 Iron Stands 2.20 ANTEX bits 65 ANTEX elements 2.20 Solder Sucker 6.50 Solda Mop 72 DIY Solder 50 Solder Copy of 7.00

					_				
Þ			/ TI	JBES			ty	er Pack pe of 10	CM7061 Power Unit 12V 10.7
				JDE		11/2" QUICK 100ma		73	
RE	PLACE	IENT	ELECTROLYTICS	ELECTRONIC TUNERS	AND ASSEMBLIES	250ma-500m 1.5A-2A-2.5/		60 60	CM7067 UHF 12V MHA (Specify A-B or C/D) 9.7
PHILIP	9 (200/20 S 320 (40	0/400/	200V) 2.07	Mullard ELC1043/05 Mullard ELC1043/06	8.40 8.40	11" ANTISL		14 1 764	CM7068 UHF 12V MHA High Gain (Specify A-B c C/D) 14.4
DECCA	30 (400/ 80 (400/	350V)	3.00	4 P/B DECCA/GEC/ITT 6 P/B DECCA/GEC/ITT	6.88 7.50	1.5A, 2A	1a, 600ma, 630ma, 750ma, 850ma,	1.70	CM7053 Behind Set UHF Amp. (Mains) 11.8 CM7054 Behind Set UHF Amp. (Battery e.g
DECCA	100 (800	/250V) 0/200/	3.97 400/350V) 4.83	4 P/B PYE 6 P/B PYE	9.00 16.00	2.5A, 3A, 5A 20mm ANT		2.70	Caravans) 9.4 CM7043 Second Set Amp. UHF 10.9
PHILIP	S G8 (600 S G9 (600	1/300V)	2.30	PHILIPS G8 Tuner PHILIPS G8 Ass. (Square /E	10.50 arly) 13,50	80ma 100ma		4.80 2.50	CM7093 Behind Set UHF Amp. 3 Sets 13.8 CM7063 Dist. Amp. VHF/UHF 17db/output 12V-20.1
PHILIP	S G11 (47	0/250	/) 2.90	PHILIPS G8 Ass. (Sloping/L PHILIPS G9 Tuner	ate) 13.90 10.50	160ma, 200n	18 1a, 630ma, 800ma, 1A, 1.25A, 1.6/	2.20	
PYE 73	1 (600/30	0V)	2.31	PHILIPS G11 Tuner ITT/PYE/GEC 7 Button P/B	9.00	2.5A, 3.15A		A, 2A 1.30 1.90	CM6011 Outdoor Splitter (2 way) N/B 7.1
RBM A	823 (600/ 145 (300/	(300V)	2.83	GEC 2110 6 way P/B U321 UHF Tuner	7.98	20mm QUI0 100ma, 250m	X BLOW na, 500ma, 630ma, 800ma	90	CM9003 Flush Single Outlet 1.3 CM9010 Flush Twin Outlet 1.6
RR1 T2	0A (220/4 C5/9 (200	(V00I	2.00	THORN 8800 SELECTOR (HMV Model 2725/6 way		1A, 1.25A, 1 1" MAINS	6Å, 2Å, 2.5Å, 3.15Å, 5Å	60	CM9034 UHF Group Filters with DC Through Pass (state A/B/CD) 6.9
ITT CV	C 20 (220) 10 (600/2	/400V)	2.00 1.94	THORN 9000 SELECTOR	11.40 7.20	2A, 3A, 5A,	10A, 13A	1,00	CM6006 6 Way Passive Splitter 10.9 CM7042 TV Games Combin. 2.55
GEC 20	40 (1000/ 40 (300/3	2000/3	5V) 1.19	HITACHI 4 way Chan, Selec		AERIAL Surface Mou	ACCESS. Int. SB11 Indoor Spl		CM9009 Flush TV/FM Outlet 2.70 CM7069 Tri Star Amplified Set Top Aerial V/B 17.50
THORN	1 3500 (40	0/40V)		RR1 T20A 6 way Chan. Sela	ctor 9.75	Splitter	1.70 COB11 Single Ou Int. Outlets 80 TRR /VSP	utlet 80	CM7090 Amplified Carevan Aerial 12V DC V/B 15.5 CM6038 UHF/VHF 625 Pattern Gen. * 50.0
THORN	1 1400 (15	50/100.	/100/100/150/320V) 2.79	RR1 T20/22/26 PHILIPS 8 way TIP Switch U			per 100 1.18 Transformer per 10 1.80 CS200/SP Comb.	2.83 /Solitter	CM6052 UHF/VHF PAL Colour Bar Gen.* 190.00 * While stocks last
THORN	1500 (12	/300V)		ITT CVC8 (5 wheel modified		P.V.C. Tape F.M. Plugs	35 25 CS1000 Comb/Sp	3.03	RECTIFIER TRAYS AA119
THORN	3500 (10	00/63\	100/400/350V) 2.78 () 86	ITT 6 way with VCR PHILIPS KT3	8.90 14.50	PL259 Plugs Line Connec	40	6.15	THORN 1400 3 Stick 4.25 BA102 1. THORN 1500 3 Stick 4.55 BA115 1.
THORN		00 (250	0/2500/63V) 3.38	PHILIPS KT30 PYE 697 Repair Kits	10.30 6.97	Reducers for	PL259 16 UP1300 M.H.A.	UHF/VHF	THORN 1500 5 Stick 5.29 BA145 1. THORN 1600 2.00 BA148 1.
THORN	8000/850	30 (400	/350V) 2.56	ELC 2003	£16.50 HES	27mhz	0db Rejection 2.10 XTRABOOST XS 6db, 12db, 4 Nay Amp UHF	20 11.63	THORN 3000 /3500 7.98 BA154 I THORN 9000 5.99 BA155 14
GEC (2)	9000 (40 00/200/15	0/50)	2.64	4A Double Pole On/Off Sw General Purpose Push/P	tch	Attenuators 18db	1.80	33.75	THORN 8500/8800 6.15 BA156 19 THORN 8500 8800 7.00 BA317 20
THORN	S 69 2200 4700 P/0	C 25V	1.25	Philips G8 Push On/Off Swi 4A Double Pole Rotary On/	tch 1.38	Olympic II Aerial	2.30	42.00	DECCA 1730/1830 4.48 BAX13
	S 320 400 1591/169			A1 Beam Switch (THORN 3 A1 Controls 5m (THORN 35	500) 70	Aerial Isolate	the pair 18.00 Super Set Top or Kit 2.08 XG8 High Gain A	erial	DECCA 30 6.76 BB105B 30
CAP	ACITOR	IS	DISC	GEC 2110 A1 Control IM5 (I GEC 2110 A1 Control IM5 (I GEC 2040 On/Off Switch	30) 89 Red, Blue, Green) 58 88	4m Fly Lead 2m Fly Lead	1.20 A,B,ČD or W/ 90	o 17.90	DECCA 100 6.14 BY126 12
	AXIAL	Price	CERAMIC CAPACITORS	On/Off Switch G11/G12	1.58		SUNDRY TUNER ACCI RANK Tuner P.B.		GEC 2100 7.40 BY133 15
6V3 10V	33	9	8kV (12kV - Mag)	On/Off Switch GEC/TCE TX	9/10 1.06		13" × 3"-2" × 3"-2" × 3"	35	GEC 2040/2028 5.60 BY176 85
1.01	22 47 100	10	39pF 200pF each 150pF 220pF 30p	SLIDER POTENT Lin or Log	CONVERGENCE 3 N/5R-6RB-10R-15R-20R	POTS	RANK Drive Cams GEC 2110 Tuner Neons	14	GEC 2110 Post Jan '77 7.00 BY182 87
	220 470	15 20	180pF 250pF	470R-1K-2K2-44- 10K-47K-470K 65	50R-100R-200R-500R	60	SUNDRIES Delay Lines DL60, DL700, DL50		PHILIPS G8 Long Focus 550 6.75 BY199 28
16V	33 68	11	CERAMIC	SKELETON	METRIC CONVERGENCE	DOTE	CRT Tube Base EHT Final Anode Cap	70	Pye/Philips K3 Tripler 6.65 BY210/600 28
	220 1000	16 27	<u>CAPACITORS</u> 63V A range of pref.	PRE-SET POTS Standard or miniature	PHILIPS G8			25p mbr.	PYE 713/4 Lead 7.00 BY223 90
3300 25V	53 10	11	values each 22pF-4700pF 6p	Horizontal or Vertical 100R-2M2 16p	5R-10R-20R-50R	60		10 4.80	Philips/Pye KT3 6.67 BY298 22
2.54	22 47	13 15	PANELS	+ UNITS	RECHARGEABLE BA		Moulded Plastic Hex. 6mm	n Trim	R.B.M. A823 (plug in) AV 7.60 BYX10 20
	100 220	15 29	AFC UNIT PHILIPS G8 IF GAIN MODULE (Pye/	(Philips) 9.00	CH1/22 For PP3/NN1604 1 battery (RX22)	6.40	Double End 4mm/8mm Trim T Focus Rod		KORTING (similar to Siemens TVK1) BYX36/600 35
	470 1000	30 55	CDA PANEL (Pye/Invict REAR CONVERGENCE P	a/Ecko/Dynatron) 20.00 ANEL (Philips G8) 23.00	CH4/50 For HP7/NN1500 1-4 batteries (RX6)) 5.55	Focus Holder Keynector Safe Block (mains)	2.00	ITT KB CVC5/9 6.90 BYX71/600 90
4700	2200 98	51		CONTROLS	CH3/RX6 For SP2/HP2/I SP11/HP11/NN1400/HP7	NN1300/	Cassette Drive Belts price eac 35mm		RRI T20 6.80 0A90 10
40V	10 22	10 10	Log or Lin Without Swit	idle Length 44mm Ich	NN1500	14.00	46mm 57mm	22	TV11 74 TV19 on 0A95 6
63V	400	48 12	5K-10K-25K-50K-100K-250 With D.P.S.T, Switch	•	2-4-6 batteries in pairs. (RX6-RX14-RX20)	10112007	66mm	39 41	1V13 79 1 1V20 1.20 (N914 4
	22	12	Log: 5K-10K-25K-50K-100 250K, 500K, 1M, 2N	K 81p A	CH3/RX4 For SP2/HP2/I SP11/HP11/NN1400/HP7	7	71mm 76mm	43	DECCA 20 2.48 IN4002 4
	4.7	12 11	Dual gang Controls 16mm Rotary Controls 1	1.25 0K, 22K, 100K, 1M, 10K 39p	NN1500 2-4 batteries in pairs.	9.55 (RX6-RX14-	90mm 110mm	59	OECCA 27R/47R 1.40 IN4004 5
	15 22 47	12 13			RX20) BATTERIES		Torch (handy for tool box) I.C. Inserter	1.18	DECCA 56R/688 1.40 IN4005 5 R.B.M. A823 56R/68R 94 IN4006 5
	100 220	19 23 37	THERMAL CUT OU THORN 3000 2A Metal 1	L60 POTS	RX6 - HP7/NN1500 RX14 - SP11/HP11/NN14	1.39 100 2.17	SM Neon Screwdriver DIN Plugs 3 pin	22	R.B.M. 161 82 IN4007 6 GEC 2000/2018 70 IN4148 2
	470	40	THORN 8500 2.5 Plastic 1 GEC 2040 Metal 2	1.60 GEC TCE 55	RX20 - SP2/HP2/NN130 RX22 - PP3/NN1604	2.34 4.69	4 pin 180° 5 pin	20	GEC 27840 64 IN4448 10 PYE 713/15 385/15/458 1.80 IN5401 12
100V	1000 2200	58 94 13		DECCA, RANK 55	VIDEO/AUDI	<u>0</u> 3.06	Stnd. 5 pin Phono Plugs	12	PYE 725/31 3R0/56R/27R 1.84 IN5402 14 PYE 725 56R/27R 1.04 IN5403 12
1007	10 22 47	13 15 20	THICK FILM RE THORN 3500 (5 pin conn	SISTOR NETWORK nection) 1.98	VHS E60 Scotch E120 Video Tape	3.66 5.00	Car Aerial Plug 2.5mm Jack Plug	14	PHILIPS 210/5050 30R/125R/2k85 IN5404 12 1.75 IN5405 13 PHILIPS 210/5050 30R/125R/2k85 IN5405 13
1	100 220	20 36 70	PYE 731 (6 pin connection THORN 9000 (Circuit Res	on) 2.20	Scotch E180 Video Tape BETA L500	5.13 4.90	3.5mm Jack Plug Stnd. Jack Plug	20	PHILIPS 210/5051 -/118R/148R 93 IN5406 16 PHILIPS G8/5081 47R Section 50 IN5407 16 PHILIPS G8/5083 2R2/68R 95 IN5408 16
450	1 4.7	33 30			BETA L750 PHILIPS VCC 240	5.80 5.93	Stereo Jack Plug SA Connector Block (12)	40	THORN 1400 1.20 ITT44 4
	10	30 30 65	Please send large S.A. DF615 Full Range Speak	PRODUCTS E. for full EAGLE Catalogue	PHILIPS VCC 360 PHILIPS VCC 480	8.30 10.21	Fuse Wire 5A-15A-30A Battery Plug Thom TV's Can Purpose Power Supply	28 1	THORN 1500 1.38 ITT2002 11 THORN 1600 1.77 Y969 (30V) THORN 3500 94 Thorn 3500) 89
500	22 33	50 75 32	Multimetres KE/V 7N	er 6½" 8.95 2,000 5.25	VIDEO CASSETTE Red/Blue/Green/Brown	CASES 80	Gen. Purpose Power Supply 9V 200ma Mains Connector 4 www. 134	1	THORN 8000 1.24 BZY15-24R 1.18
600	10	32 32 41	KE/V 20 EM5	2,000 5.25 14.50 5,000 opv 9.95	Book Type – Any Format Scotch Audio Tape		Mains Connector 4 way 13A TEST EQUIPMENT	3.00	ZENER DIODES
SPECI	AL DIO	DES	EM10 EM50	10,000 opv 9.99 10,000 opv 11.50 50,000 opv 19.95	C90 Ferric C90 Super Ferric	65 96	Portable Oscilloscope Probes x10	150.00	
SKE 49 SKE 5F	£	1.09 1.19	EMC321 Carrying Case f Digital Meter TS1000		Video Recorder Heads		CRT Tester/Rejuvenator	172.00	75V. BZY9390, 18V 1.18
Y723 Y827	£	1,30 1.42	MM20 MM50	44.50 20,000 0.P.V. 21.95 50,000 0.P.V. 25.95	VHS (Universal) Philips V2000	38.00 52.00	KHP30 Measuring Probe () EHT T120 RE Signal Injector	29.95	BZY88 (400M W) 10 2V7-3V-3V3-3V6-3V9-4V3-4V7-5V etc. up to 24V.
	MIXED	c	MM100 MMT20	100,000 0.P.V. 25.95 100,000 0.P.V. 36.50 16.95	ELECTROLUE		T120 RF Signal Injector Test Lead Set	4.00 4.20	HOW TO ORDER ADD 65p per order for Post and Packing (UK).
	CAPS	~	Case for MM100	15.95	PRODUCTS Electrolube Adhesive	62	Degaussing Coil (stick type) Oegaussing Coil (disc type)	17.00 24.00	(Export orders will be charged at cost.) THEN ADD 15% VAT TO TOTAL COST.
Volts C).91 mF	84	T1206 2 Station Intercor		Electro-Mech lubricant Elect. cleaning solvent	1.49 1.62	SERVICE AIDS		Orders which contain aerosols or degaussing coils are very heavy — please add extra 30p per can/coil.
400V (600V ().1mF	20 38	Transistor Equivalent	DKS (No VAT)	Freezer Foam cleanser	1.49 1.12	SERVISOL Freeze-It SUPER SERVISOL	96 88	First Class Mail is used whenever possible. All enquiries S.A.E. please.
	0.047mF	24 46	TVT 80 A-Z only TVT 80 2N/2S series on	3.75 ly 4.00	Heat transfer compound Silicone compound	1.94	SERVISOL Foam Cleanser SERVISOL Plastics Seal	84 88	VAT invoice on request.
).033mF).1mF	33 35	TVT 80/80 A-Z and 2N/2 LIN IC Books LIN 1	5.95	Special contact fluid (Si Permagerd	1.52	SERVISOL Flastics Seal SERVISOL Silicone Grease SERVISOL Tubes Silicone Grea	1.00	Goods are despatched on the day we receive your order. If for any reason we are out of stock we will
0).22mF).47mF	66 98	LIN 2	5.95 P.V. MICROCOMPUTER	Elec. mech. lubricant pe CENTRE	an 74	SERVISOL Aero Klene SERVISOL Aero Duster	78 94	try to inform you as quickly as possible. We try our best to give a speedy, fair and efficient
).91mF	59 1.15	Why not pay us a visit a	nd see our range of Micros, S ring for prices.		erals. Please	SERVISOL Excel Polish SERVISOL Video Head Cleaner	76	service. As our regular customers know, orders telephoned in before 4 p.m. will be despatched the
).0022mF).0047mF	28 32	Spectrum 16K	Vic 20		ire aiso ed dealers	Super 40 Fire Extinguisher 640G	1.50 2.80	same day. Give us a ring — we'll give you service.
0	0.022mF	30 62	48K Jupitea Ace	Commodore 64	Oric for	the Micro	Heat Sink Compound 25G Silicone Rubber Tube 110G	1.08 2.98	Please ask if what you need is not listed — we will try to help.
	.005mF 1.0052mF	65 1.20	Texas	Lynx		cessories	Solda Mop standard reel	72	Prices are subject to change without notice.

÷



G.G.LCOMPO 108 SCOTLAND ROAD, CARLIS PHONE (0228) 20358/39693	NENTS SLE, CUMBRIA CA3 9EY	ACCESS NOW AVAILABLE	Hitachi	OP PRESS) and Sony tubes ow rebuilt.
INTEGRATED CIFCUITS TYPE PRICE (£) TYPE PRI	5.00 AC128K 30 BC212L 10 E 1.50 AC128K 30 BC212L 10 E 1.50 AC128K 30 BC212L 10 E 1.80 AC142K 30 BC212L 10 E 1.80 AC176L 28 BC237B 11 E 2.95 AC176K 30 BC303 26 E AC187K 30 BC303 26 E AC188K 33 BC337 11 E SAD161 42 BC543 10 E AD161 42 BC549 10 E AD161 42 BC543 10 E 25 AU110 210 BD14 BD131 33 B 10 B 10 BC142 23 BB23 33 B 13 B B 10 BC108 14 BD201 33 B 10 BC178 BC108 10	PYPE PRICE TYPE PRICE 35115 .30 BU205 1.42 35115 .20 BU206A 1.35 3784 .28 BU208A 1.48 35185 .29 BU208A 1.48 37185 .29 BU208A 1.48 37185 .29 BU208A 1.48 37137 28 BU208A 1.48 37137 13 BU407 1.12 37196 .11 BU506 .80 37197 11 BU502 .200 37198 .48 BUW81A .20 3728 R2500 .26 R2000B 1.78 3725 .26 R2000B 1.78 .37 3728 R2540 .235 .35 .337 .38 .30 11P29C .45 3737 .28 R2540 .235 .35 .30 11P31C .48 17438 .30 11P29C	PHILIPS G8 7.90 PHILIPS G9 8.75 PHILIPS G9 8.75 PHILIPS G11 13.50 THORN 1590/1 8.68 THORN 1590/1 9.68 THORN 1590/1 9.68 THORN 1515 9.75 THORN 1710 10.20 PYE 725(90) 10.20 DECCA 2230 8.30 DECCA 400 8.58 GEC 2110 9.46 ITT CVC 20 7.75 RBM 720/22A 7.35 RBM 4823 7.20 PHILIPS G8-550 6.65 THORN 1500-3S 4.25 THORN 1500-3S 4.25 THORN 1500-3S 4.55 THORN 1500-3S 4.55 THORN 1500-3S 4.55 THORN 1500-3S 4.55 THORN 3000/3500 7.75 THORN8000 4.00 THORN8000 5.90	PCL82
EXAMPLE PRICES: can rebuild over 700 A55 120X£38.00* types of PIL tubes — A66/57 120X£45.00* List on Request. A61 120VR£23.00* Available. Please ask for A65 510X63.00* available. Please ask for	DECCA 30(400/400)350V2.55 DECCA 80/100(400)350V2.90 PHILIPS G8(600)300V .2.90 PHILIPS G8(600)300V .2.00 PHILIPS G11(470)250V .2.20 PYE 691/7(200-300)350V .2.10 RBMA823(2500/2500)30V .1.10 THORN1400(150/100/100/100/ 150)320V 2.40 THORN3500(175/100/100/	DECCA/ITT 6W PYE201 6W PHILIPS G85/L PHILIPS G85/Q HITACHI 4W ITT CVC5 7W ITT CVC5/9 PHILIPS G11 (TIP SW.) 1043/05TFK	6.45 LARGE RANGE OF LATTA 7.40 I/Cs NOW AVAILBLE 15.80 TYPE PRICE (£) TYPE 13.90 LAY240 3.00 LA443 12.00 AN7140 2.40 LC713 18.50 AN7140 2.40 LC713 18.50 AN7140 2.40 LC713 18.50 AN7150 3.30 TA722 19.40 HA1322 2.10 TA722 12.80 HA13366 2.30 UPC1 17.55 HA1337 3.80 UPC1 7.56 HA1388 4.20 UPC1	VUPC/STK SMALL PART OF OUR RANGE, WE WILL BE DELIGHTED TO SEND DELIGHTED TO SEND DELIGHTED TO SEND DELIGHTED TO SEND WHOLE RANGE PRICE (É) 22 2.76 74 4.50 ORDERING Please Add Sop For P/P U.K. Add 15% To This Totel. 22 4.50 Fors P/P U.K. Add 15% To This Totel. 25H 3.20 ELIVERY BY RETURN ON ALL 185 3.20 RETURN ON ALL

Switch to the biggest wholesaler of quality late model used TV's

- Thousands of Quality Sets always in stock
- Colour/Mono/VCR's and Audios available
- Murphy/Pye/Philips/Sony/National Panasonic and other big names
- \bullet We are big we buy in bulk we offer you the keenest prices
- Cash and Carry or we will deliver
- New and used stands always in stock



TELEVISION AUGUST 1983

JUST OUT!

OUR GREAT NEW CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices.

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.



We hold vast Stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock.


The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/ Access credit cards, which we accept over the telephone.

To receive your NEW 1983 BI-PAK Catalogue, send 75p PLUS 25p p&p to:-

TRANSISTORS, ETC.				
Type Price (E) Type Price (L) Type Price (L) Type AC107 0.48 AU103 2.40 BC AC117 0.38 AU107 2.75 BC AC126 0.36 AU1107 2.75 BC AC128 0.46 BC107* 0.16 BC AC128 0.46 BC107* 0.16 BC AC124 0.60 BC113 0.22 BC AC141 0.65 BC107* 0.16 BC AC142 0.60 BC114 0.22 BC AC153 0.42 BC118 0.34 BC AC154 0.41 BC126 0.30 BC AC178 0.52 BC137 0.30 BC AC178 0.	Price (£) Type Price 1192 0.56 BC377 1204* 0.39 BC394 1205* 0.39 BC440 1206* 0.37 BC441 1207* 0 BC471 1208* 0.37 BC471 1208* 0.37 BC471 1208* 0.37 BC471 1208* 0.37 BC472 121* 0.36 BC479 121* 0.36 BC548* 121* 0.16 BC550* 121* 0.16 BC550* 121* 0.16 BC550* 122* 0.17 BC441 0.18 BC557* 122* 0.22 BC30* 123* 0.16 BC550* 123* 0.16 BC550* 123* 0.16 BC550* 123* 0.22 BC30* 124* 0.18 BD123 1255* 0.28 B	0.29 BD235 0.68 0.39 BD235 0.63 0.52 BD235 0.63 0.52 BD235 0.63 0.58 BD253 0.68 0.30 BD253 0.68 0.30 BD253 0.68 0.31 BD435 0.70 0.33 BD435 0.70 0.33 BD435 0.74 0.44 BD436 0.71 0.43 BD435 0.74 0.44 BD438 0.75 0.33 BD435 0.74 0.44 BD437 0.74 0.45 BD519 0.88 0.16 BD520 0.88 0.16 BD529 0.87 0.17 8D603B 1.23 0.30 BD663BR 1.38 1.50 BDY18 1.55 1.50 BDY20 2.295 1.50 BDY38 1.38 1.56 BF117	bf222 0.51 BPX29 1.62 bf224 0.22 BR101 0.53 bf240 0.22 BR101 0.53 bf241 0.31 BR303 1.06 bf241 0.31 BR303 1.06 bf244 0.51 BRC443 1.76 bf254 0.43 BRY39 0.60 bf254 0.48 BRY56 0.42 bf255 0.58 BS527 0.47 bf255 0.54 BT106 1.50 bf255 0.54 BT116 1.45 bf255 0.54 BT116 1.45 bf255 0.54 BT116 1.45 bf262 0.38 BU105 1.80 bf262 0.38 BU105 1.80 bf270 0.47 BU120 2.98 bf271 0.47 BU120 2.98 bf373 0.65 BU204 2.50 bf385 0.72 C106F	Type Price (f.) Type Price (f.) Type Price (f.) <
LINEAR IC* Type Price(E) T Type Price(C) SN7603N 2.20 T CA8100M 2.50 SN76110N 1.20 T CA3005 1.85 SN76115N 1.20 T CA3012 1.45 SN76131N 2.10 T CA3012 1.45 SN76131N 2.10 T CA3012 1.45 SN76131N 2.10 T CA3012 1.45 SN76131N 2.10 T CA3020 1.88 SN76520N 1.92 T CA3028A 0.60 SN76520N 1.92 T CA3028B 1.09 SN76530N 0.97 II CA3028B 1.09 SN76530N 0.97 II CA3028B 1.09 SN76530N 1.98 T CA3065 1.74 SN76534N 1.88 T CA3065 1.74 SN76544N 1.85 T CA3065 1.74 SN76550N 1.81 T CA3065 1.90 SN76650N 1.48 T CA3065 1.91 TA3250 2.20 M MC1307P 1.82 TA300 3.8F MC135P 2.92 TAA521 1.10 M MC135P 2.92 TAA521 1.10 M MC135P 2.92 TAA521 1.10 M MC135P 2.92 TAA550 0.35 M MC135P 2.92 TAA520 3.39 M MC135P 2.92 TAA500 3.51 M MIC19 0.58 TAA500 3.59 M MC135P 2.92 TAA500 3.51 M MC135P 2.92 TAA500 3.59 M MC135P 2.92 TAA50 3.39 M MC135P 2.90 M M	Price (£) DIODES BA4800 1.84 Type BA500° 2.21 AA113 BA510° 2.21 AA113 BA510° 2.21 AA113 BA520° 2.24 AA133 BA540° 2.88 AA123 BA550° 3.13 AA213 BA551 2.42 BA104 BA651 2.42 BA104 BA651 2.42 BA104 BA651 2.42 BA104 BA651 2.42 BA104 BA700 2.50 BA111 BA701 BA702 BA154 BA703 2.06 BA121 BA703 2.06 BA121 BA703 2.06 BA121 BA703 2.06 BA121 BA704 55 <td>Type Price [£] Price [£] BY114 0.60 0.17 BY118 1.10 0.21 BY126 0.20 0.28 BY133 0.35 0.28 BY140 1.40 0.42 BY133 0.35 0.28 BY140 1.40 0.42 BY179 0.83 3.85 BY182 1.14 0.26 BY179 0.83 3.85 BY182 1.44 0.36 BY180 0.490 0.37 BY180 0.490 0.38 BY190 0.490 0.39 BY238 0.25 0.41 BY180 0.30 0.58 BYX38/600 0.70 BY38 0.25 0.45 0.417 MR854 1.10 0.12 0.45 0.474 0.40 0.481 0.19 0.12 0.45 0.420 0.40 0.481 0.19<!--</td--><td>VDR's, etc. VALVES Type Price (E) Type (Price (E)) C295ZZ DY80/3 0.75 /02 0.28 ECC81 0.78 Z295CD ECC81 0.78 0.75 /02 0.28 ECC81 0.78 Z296CD ECC82 0.95 ECC82 0.95 /A258 0.22 EC80 0.83 A258 0.22 EC80 0.60 /A265 0.22 EF80 0.60 A265 0.22 EF80 0.60 /A265 0.22 EF80 0.67 PC86/30 0.67 E299DD C134 a10.23 PCC85 0.79 PC500 0.72 PCC80 0.74 VA1026 0.79 PCF80 3.80 VA1035 0.29 PCF80 3.80 VA1036 0.29 PCF80 3.80 VA103 0.29 PCF80 3.80 VA103 0.29 PCF80 3.80<!--</td--><td>C Voltage: 0.6, 1.2, 3, 12, 30, 60, 120 600, 1200. AC Voltage: 3, 6, 15, 60, 150, 300, 600, 900. DC Intensity M/A: 0.6, 0, 6, 6, 60, 600, 3000. AC Intensity M/A: 0.3, 3, 30, 300, 3000. DC Resistance: 0.2, 5, 50, 500, 500DX. geleveldB: - 10 to + 12. Price £15 including p/p and VAT. P. & P. UK: £0.30 per order. Overseas: At cost. Please add VAT at 15%. Delivery by return of mail on all stock items. It is only possible to show part of our range here. Our catalogue [30p reflundable] shows Service Aids, 7400</td></td></td>	Type Price [£] Price [£] BY114 0.60 0.17 BY118 1.10 0.21 BY126 0.20 0.28 BY133 0.35 0.28 BY140 1.40 0.42 BY133 0.35 0.28 BY140 1.40 0.42 BY179 0.83 3.85 BY182 1.14 0.26 BY179 0.83 3.85 BY182 1.44 0.36 BY180 0.490 0.37 BY180 0.490 0.38 BY190 0.490 0.39 BY238 0.25 0.41 BY180 0.30 0.58 BYX38/600 0.70 BY38 0.25 0.45 0.417 MR854 1.10 0.12 0.45 0.474 0.40 0.481 0.19 0.12 0.45 0.420 0.40 0.481 0.19 </td <td>VDR's, etc. VALVES Type Price (E) Type (Price (E)) C295ZZ DY80/3 0.75 /02 0.28 ECC81 0.78 Z295CD ECC81 0.78 0.75 /02 0.28 ECC81 0.78 Z296CD ECC82 0.95 ECC82 0.95 /A258 0.22 EC80 0.83 A258 0.22 EC80 0.60 /A265 0.22 EF80 0.60 A265 0.22 EF80 0.60 /A265 0.22 EF80 0.67 PC86/30 0.67 E299DD C134 a10.23 PCC85 0.79 PC500 0.72 PCC80 0.74 VA1026 0.79 PCF80 3.80 VA1035 0.29 PCF80 3.80 VA1036 0.29 PCF80 3.80 VA103 0.29 PCF80 3.80 VA103 0.29 PCF80 3.80<!--</td--><td>C Voltage: 0.6, 1.2, 3, 12, 30, 60, 120 600, 1200. AC Voltage: 3, 6, 15, 60, 150, 300, 600, 900. DC Intensity M/A: 0.6, 0, 6, 6, 60, 600, 3000. AC Intensity M/A: 0.3, 3, 30, 300, 3000. DC Resistance: 0.2, 5, 50, 500, 500DX. geleveldB: - 10 to + 12. Price £15 including p/p and VAT. P. & P. UK: £0.30 per order. Overseas: At cost. Please add VAT at 15%. Delivery by return of mail on all stock items. It is only possible to show part of our range here. Our catalogue [30p reflundable] shows Service Aids, 7400</td></td>	VDR's, etc. VALVES Type Price (E) Type (Price (E)) C295ZZ DY80/3 0.75 /02 0.28 ECC81 0.78 Z295CD ECC81 0.78 0.75 /02 0.28 ECC81 0.78 Z296CD ECC82 0.95 ECC82 0.95 /A258 0.22 EC80 0.83 A258 0.22 EC80 0.60 /A265 0.22 EF80 0.60 A265 0.22 EF80 0.60 /A265 0.22 EF80 0.67 PC86/30 0.67 E299DD C134 a10.23 PCC85 0.79 PC500 0.72 PCC80 0.74 VA1026 0.79 PCF80 3.80 VA1035 0.29 PCF80 3.80 VA1036 0.29 PCF80 3.80 VA103 0.29 PCF80 3.80 VA103 0.29 PCF80 3.80 </td <td>C Voltage: 0.6, 1.2, 3, 12, 30, 60, 120 600, 1200. AC Voltage: 3, 6, 15, 60, 150, 300, 600, 900. DC Intensity M/A: 0.6, 0, 6, 6, 60, 600, 3000. AC Intensity M/A: 0.3, 3, 30, 300, 3000. DC Resistance: 0.2, 5, 50, 500, 500DX. geleveldB: - 10 to + 12. Price £15 including p/p and VAT. P. & P. UK: £0.30 per order. Overseas: At cost. Please add VAT at 15%. Delivery by return of mail on all stock items. It is only possible to show part of our range here. Our catalogue [30p reflundable] shows Service Aids, 7400</td>	C Voltage: 0.6, 1.2, 3, 12, 30, 60, 120 600, 1200. AC Voltage: 3, 6, 15, 60, 150, 300, 600, 900. DC Intensity M/A: 0.6, 0, 6, 6, 60, 600, 3000. AC Intensity M/A: 0.3, 3, 30, 300, 3000. DC Resistance: 0.2, 5, 50, 500, 500DX. geleveldB: - 10 to + 12. Price £15 including p/p and VAT. P. & P. UK: £0.30 per order. Overseas: At cost. Please add VAT at 15%. Delivery by return of mail on all stock items. It is only possible to show part of our range here. Our catalogue [30p reflundable] shows Service Aids, 7400
CAPACITORS Metallised Paper 2n2F 1500V DC 2n2F 600V AC 24p 15nF 3n6F 1700V DC 4n7F 1500V DC 10nF 1000V DC 4n7F 1500V DC 40p 22p 10nF 1000V VHF 100 UHF CONVERTER CM6022 CM6022	VAC 30p 82,10 VAC 32p 150,1 VDC 46p 200,2 VDC 60p 270,3	18p 20p Phone y order thro We do the We do the 0,120, 80, 20pF 30p 000pF 39p	rest. SPECIAL OFFER 30, 120, 270, 470, all at 20p each	EAST CORNWALL COMPONENTS 119. HIGH STREET. WEM. SHROPSHIRE. SY4 5TT TEL:WEM (0939) 32689 UFFICE DPR: 9.00 AM-5.00 PM MON-FRI. NEW PROPRIETORS: CAPTIME LTD.

TELEVISION AUGUST 1983

•

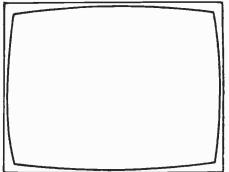

EDITOR

John A. Reddihough

ASSISTANT EDITOR Luke Theodossiou

ART EDITOR Roy Palmer

ADVERTISEMENT MANAGER Roy Smith

01-261 6671

CLASSIFIED ADVERTISEMENTS

Barbara Blake 01-261 5897

FRONT COVER

This month's front cover photograph was taken at the factory of c.r.t. rebuilding specialists TSR Vacuonics Ltd. It shows an operator spot welding the cathodes on the stem supports of a colour c.r.t. gun.

CHANGE OF ADDRESS

The editorial office location has changed. Please note the new address which is: King's Reach Tower, Stamford Street, London SE1 9LS.

PCB SERVICE

Send orders to Readers' PCB Services Ltd. (TV), Fleet House, Welbeck Street, Whitwell, Worksop, Notts – see note on page 457 last month. A revised list of boards available will be published next month.

TELEVISION AUGUST 1983

TELEVISION

A Loss of Confidence

At one time it was fashionable for editors of technical magazines or their contributors to write occasional pieces that gave a glowing view of the prospects ahead. In the early thirties it was easy enough to write that in ten years' time high-definition TV would be established, maybe with colour, that cars would be better and faster and so on. Twenty years later, in the early fifties, there were still grounds for optimism. Nuclear power could provide cheap and plentiful energy, the jet engine was revolutionising travel, and the transistor had begun to revolutionise electronics. Automation was a buzz word and people were becoming design conscious, which would in turn revolutionise our homes, products and the environment.

The boom of the sixties seemed to confirm that all was on course for a better standard of living with more options and facilities at everyone's disposal. Since then, everything seems to have gone sour. Nuclear power has turned out to be expensive and of questionable need, for the time being at any rate. All that flowering of design ended up in a mass of shoddy goods and a shoddy environment, with buildings twenty or less years old being demolished because they simply didn't work. In this sort of situation it's not so easy to be confident about the prospects that lie ahead.

Another factor that makes prophecy less enlightening is that we nowadays very often know years ahead what to expect. Developing something may take ten or twenty years. We've known that satellite TV is coming for several years already, and by the time it does come we may well greet it with a great big yawn. The problems seem increasingly to be not so much what can be achieved and how to go about it, but how to fund development work and what to do with its results when they eventually turn up. Cable TV is a classic example, It'll be expensive, especially if it's to be of the all singing, all dancing interactive variety, and the great question is whether people will actually want it. Channel 4 does not seem to have unleashed a flood of innovative programme material, and there's little reason to feel that cable or satellite TV will. More can mean worse! It's not an exactly confidence building prospect.

When one looks at the wider scene one detects a general loss of confidence in future prospects. The sort of article I keep coming across runs along the following lines – I've not made it up either. "Large sections of industry are facing a painful process of readjustment with substantial job losses. The aim must be to support future orientated industry. Major surgery is expected in the iron and steel industry and shipbuilding, the plans being to promote the creation of more jobs in modern industries such as electronics, industrial design and (yes, here it comes!) information technology." That sort of thing can be written about almost any industrial country today. This time it was Spain of all places.

There's a small problem here that seems to go largely unnoticed. If everyone stops building ships and goes in for information technology instead, it won't be all that long before it's the information technology industry that will be facing a painful process of readjustment. Assuming, that is, that such industries really do get going. Information technology is the current buzz phrase but is inherently vague. One could perhaps define it as the use of computer technology to increase the availability of information generally. But this brings us to the same problems that cable/satellite TV pose. Will there be a need for all this extra information? And who will be willing to pay for it? I'm not suggesting that there are no worthwhile developments being introduced or in

I'm not suggesting that there are no worthwhile developments being introduced or in prospect. The compact disc for example seems to be genuinely worthwhile. It stores more, better quality wanted information than its predecessor and in the long run should be as cheap. That is progress, and should surely be cause for its inventor Philips to feel full of confidence. It's strange therefore to find Philips pressing for an increased (19 per cent) EEC tariff on the players, as mentioned in the May Teletopics. Philips have since gone to some trouble to explain their view of the matter The hope is that the compact disc will lead to "the complete regeneration of the European audio industry", though "a breathing space" is required while volume production is being built up. This is puzzling. Surely the last people who should need a "breathing space" are those who developed the system and got there first. The problem seems to be that Japanese firms can move to the mass production stage at a much faster rate.

This doesn't say much for European production technology or for European methods of funding industry, a point that was emphasized by speakers at the recent *Financial Times* Electronics Conference. During his introduction Peter Benson, formerly deputy chairman of British Telecom, put the question "are our existing (European) institutions able to cope with the growth of the industry?". The consensus seeemd to be definitely not, and that the European electronics industry was not in good shape at all in comparision with the USA and Japan. Meanwhile there are mutterings in Japan that the boom years have come to an end and that life is going to be more difficult from now on.

Returning to Philips' views on the compact disc, the suggestion is that if it's unsuccessful there could be "a domino effect, hitting first the audio industry, then TV manufacturing, component suppliers and so on". It would be nice to sit down and pen a piece on the good times ahead, but the general view now that we've arrived in the mid eighties seems to be one of a distinct lack of confidence.

Teletopics

MINI CTVs

Details of two mini colour sets have been released. Matsushita's set (National Panasonic) is called the Travelvision and uses a conventional though newly developed 30° deflection miniature colour tube that gives a 1.5in. picture (22×28 mm). It measures 38mm high, 110mm wide and 180mm deep and weighs only 600g (1.34lb) excluding batteries. The set was on show at this summer's Chicago Consumer Electronics Show and is due for release in the USA in the near future. Plans for a PAL version for the UK market have not been finalised.

The Travelvision is equipped with video input terminals, making it convenient for use as a video monitor as well as a portable TV set. There's also an audio input socket and an earphone/headphone jack. The set can be operated from an a.c. mains supply, 12V d.c. car battery, nickelcadmium rechargeable battery or eight AA dry batteries. Power consumption is 2.9W with a d.c. supply and 5W when fed from the mains. The audio output is 0:12W from a 32mm round speaker. There's continuous variable tuning with an illuminating bar that scans the screen.

The second set has been developed by the Epson Corporation and Suwa Seikosha Co. Ltd. (Seika) and is quite different. It measures $160 \times 80 \times 28$ mm and uses a liquid crystal colour display system. This flat display is certainly something of a breakthrough and one wonders what larger versions will look like – it's illuminated for maximum visibility under dark or light viewing conditions. John Patterson, national sales and marketing manager of Epson (UK) Ltd., commented that "there are no plans to make the new receiver available in the UK, but it does reflect the continuous research and development being undertaken in Japan".

LARGE LCD CTV

At the other extreme, Mitsubishi have developed a very large, flat, full-colour liquid crystal display system which was also on show at the Chicago exhibition and is already being marketed. The version shown at Chicago gave a display of 1.2×1.8 m though there are five standard sizes ranging from 0.9×1.4 m to 2.9×4.6 m. The depth is only 40cm.

Mitsubishi hope to receive orders for 200 units in the first year, priced at ten to thirty million yen per square metre. The LCD system is said to give a full colour display of animation, patterns and characters and is designed for use with inputs from a VCR, camera or computer. It's intended for applications such as advertising, displaying information at stations, airports and conference halls, plant monitoring, etc.

The display uses specially developed light sources, featuring high and uniform brightness, behind liquid crystals with red, green and blue colour filters arranged in a grid. The light emitted from the sources is controlled by the action of the liquid crystals.

UNUSUAL TVs

Tektronic have developed a field-sequential colour display system consisting of a monochrome c.r.t. combined with a liquid crystal colour switch. The fast LCD switch provides alternate red/green/blue fields and since there's no shadowmask or phosphor matrix high resolution can be achieved. Intended uses are for instrument and control process displays and computer readouts where high resolution is important.

Philips have introduced a slow-rate TV system that enables single frame pictures to be transmitted via normal speech circuits. There are three units, a transmitter to convert the signal from the camera into slow-rate data that can be handled by a telephone circuit, a receiver to convert the slow-rate data into a video signal for monitor display, and a control unit to enable any of four pictures to be selected or alternatively displayed simultaneously. The system is intended for use in security and surveillance applications. The transmitter stores a single frame and uses a sampling system to release picture elements at a rate compatible with the bandwidth of the cable link: the slow-rate pictures can be recorded on an audio cassette for future use.

MULLARD SOLID-STATE IMAGE SENSOR

Mullard have introduced a solid-state image sensor, development type number RGS-4, which is intended to sell in the same price range as a monochrome TV camera tube. Suggested applications include measuring equipment, industrial robots. CCTV in hazardous environments, videophones, bar-code readers, military photographic and sensing devices, etc. The RGS-4 needs only simple peripheral electronics, gives a consistently good picture quality and has good sensitivity to both blue and infra-red light. It has an imaging diagonal of 7mm, which corresponds to the format of Super-8 film, a resolution of 200 horizontal by 300 vertical elements, and can be used with low-cost, commercially available lenses. The standard illumination is 15μ W per square cm but the device can operate at down to less than 0.5μ W per square cm, giving pictures under poor lighting conditions. A 30V supply is required and the total power consumption of a camera using the sensor can be less than 3W.

The RGS-4 is a resistive-gate sensor made up of photosensitive elements which are connected via chargecoupled device channels to a buffer and output register, i.e. the charge carriers generated by the incident light are periodically transferred to potential wells below the control electrodes and are then moved into and out of the shift register as a video signal.

RELIABILITY

The NEDO consumer electronics sector working party is due to publish a report on the considerable improvements that have been achieved in component and TV set reliability in the UK. The on-line component failure rate has been reduced from 200 parts per million to 40 p.p.m. since 1977/8, with receiver fault rates during the first year falling from 5 per cent to 0.6 per cent.

Though the reduced component count per set has contributed to this improvement, the main factor has been improved component quality – such that the difference between UK and Far Eastern component reject levels is now insignificant. The aim has been to achieve a "zero defect approach", with the reason for every failure found rather than simply sticking to a contractual quality specification. This has required close collaboration between setmakers and component manufacturers, with liaison at several levels. The long-term aim is to be able to eliminate

goods inward testing by setmakers, also on-line fault finding and the amount of soak testing necessary.

Plastic mouldings now account for over a third of online rejects, and accordingly the working party has started a programme of co-operation with the Plastics Processing sector working party to improve the quality of the mouldings used in TV sets. Although full analysis of the problems has not yet been completed, close liaison between setmakers and suppliers has been established.

At the end of last year a joint union-management delegation from Thorn's Gosport and Enfield plants paid a return visit to six major Japanese CTV plants. The earlier visit took place in 1978, "when the UK consumer electronics industry was wilting under pressure from Japan." The conclusion this time was that Thorn have now caught up with and in some cases overtaken the use of advanced manufacturing processes by leading Japanese CTV manufacturers, though Matsushita would not permit a visit to the "almost completely automated" TV assembly line being developed at Ibaraki.

One thing we may come to see in TV sets is increasing use of surface mounted components, again a field in which Japan has established a lead. In mass production there seems to be a cost advantage in surface mounting as opposed to the automatic component insertion techniques now being used.

VCR NEWS

The new Mitsubishi VCR plant in the UK is to be at Livingston near Edinburgh. The plant involves an investment of some $\pounds 2$ million and is expected to be in full production by the end of next year.

Considerable efforts are being made to get VCR kits excluded from the EEC-Japanese quota agreement, which could have severe consequences for the operation of European VCR assembly lines unless amended. One of the points being made is that the local content of European manufactured VCRs is being steadily increased – the local component content of J2T machines is expected to reach 35 per cent by the end of this year for example. The quota agreement has also led to a shortage of c.r.t.s – Thorn for example expect to be short of some 20,000 90° 22in. tubes, which are not produced in Europe and are normally obtained from Hitachi and Toshiba.

Philips have added a front-loading V2000 format machine, Model VR2350, to their new range. Features include stereo sound, high-speed picture search and multiple slow-speed options. Further front-loading Betamax machines are due from Toshiba shortly – Models V31B and V33B. Features include high-speed picture search, slow motion and still picture, the V33B having a 14 day/ eight programme timer and remote control.

Research workers at NHK, Japan, have demonstrated that the use of recently developed (by Fuji) metal-powder coated tape and a domestic VCR modified for digital recording can give a much increased recording information density, with good picture quality, compared with the conventional analogue machine. Improved head sensitivity and tracking accuracy would be required for successful operation of the system.

LATEST FROM ITT

The latest version of the ITT CVC1200 chassis is the CVC1202, which is intended to drive 20in., 90° mini-neck (22.5) tubes. Since these tubes use a pincushion distortion free yoke, the EW diode modulator circuit is omitted. An

TELEVISION AUGUST 1983

associated change is the use of a BU208D line output transistor with integral efficiency diode.

A retrofit kit (VRFK02) has been introduced by ITT to enable various current ITT TV sets and VCRs to be connected at video/audio frequency. The direct video/ audio input unit is fitted as standard in the 26in. remote control Model CT2712/1, and VCRs TR3913 and TR3943 have the necessary output sockets.

NEW BOOKS

The 1983/4 Video Yearbook, now in its seventh edition, is available at $\pounds 25/\$44$ from specialist bookshops or $\pounds 27/\$48$ direct by mail order from Specialist Publications Group, Link House Magazines plc, Link House, Dingwall Avenue, Croydon CR9 2TA, UK. The 800-page reference book covers all aspects of the video industry in over 80 countries around the world and is a valuable source of information for all those involved in the industrial, professional or broadcast video fields.

The latest book in the "IBA Technical Review" series is entitled "Developments in Teletext". The 69-page book is profusely illustrated and includes seven papers by engineers working in the teletext field. It covers ten years of teletext development including the enhancements of additional levels, with the possibility of using alpha-geometric coding, networking, i.c. decoders and the NEWFOR system of teletext subtiling. The book is intended for engineers and students directly involved in this field of broadcasting and is also available to technical libraries and educational centres. Enquiries to IBA Engineering Information Service, Crawley Court, Winchester, Hants, SO21 2QA.

ADDRESSES

Please note that the magazine's editorial office has been moved to the firm's headquarters building. The new address is given on page 513.

South West Aerial Systems have moved to 11 Kent Road, Parkstone, Poole, Dorset BH12 2EH (telephone 0202-738232).

We omitted to give the address of Heron Electronics Ltd. last month. This is Heron House, 19 Marylebone Road, London NW1 5JL.

SERVICE EQUIPMENT

A new analogue multimeter, Model 1001, has been introduced by Avo. It's housed in a tough ABS plastic case and is priced at £28.50. The meter provides a.c. or d.c. voltage measurements up to 1kV, d.c. measurements up to 1A and resistance measurements up to $2M\Omega$. There's also a continuity buzzer for resistances up to 20Ω . The sensitivity is $10k\Omega/V$ d.c. and $1k\Omega/V$ a.c.

Alcon Instruments Ltd., 19 Mulberry Walk, London SW3 6DZ have introduced a small, pocket-sized signal injector in the form of a pen-shaped signal probe – the Chinaglia USIJET. The main signal generator is a 500kHz blocking oscillator whose output is modulated at 1kHz for identification and demodulation check purposes. Because of the waveform, the equipment produces detectable harmonics at up to 500MHz, which is useful in many servicing applications. The power consumption is 25mA from an internal 1.5V battery to give a 20V peak-to-peak output at the probe tip. A fly-lead connects the case to the earth line and the probe can cope with circuit voltages up to 500V d.c. The price, complete with earthing lead and instructions, is £11.55 including VAT.

VCR Clinic

New Machines

The Mitsubishi range of VCRs has recently been added to the list of machines we handle. There are three models at present, the HS700, HS320 and HS303. The latter is the standard machine with wired remote control, pause and visual search, while the HS700 is a portable --- it's really a normal VCR made to work in the vertical position and given a handle. The power pack can be removed and replaced with an optional extra rechargeable battery, and a camera can be plugged in directly. Being based on a standard VCR, it's not particularly light. So I'd not recommend it for someone who wants to do a lot of outdoor camera work. For someone who wants a machine for occasional portable use or for moving around from room to room however it's ideal, and has the advantage over many portables that the tuner and power supply/ charger are built in. It's also only about £50 more than the standard machine.

The HS320 is the up-market model, with infra-red remote control and Dolby sound. The handset tucks away into a compartment at the bottom right front corner. There are a couple of features that could confuse the user. First a switch called "panel lock", behind the front flap. When this is switched to on in the record mode all the machine's front controls are disabled. The idea is to stop the children messing up a recording. But you're bound to get a customer who switches it on, forgets it and then phones to say he can't get the machine out of record. The other point is that with the timer flap open to set the timer the channel change buttons are inoperative. This raises two potential problems - the customer who doesn't shut the flap properly and can't change channels, and the fact that with the front off for servicing the microswitch must be taped down if you want to change channels.

The HS320 has "stepped" slow motion, as used in Ferguson machines, and can be slowed down or speeded up using two buttons on the remote control unit. As well as an electronic counter it has an elapsed time indicator which tells you, in hours, minutes and seconds, how much tape has been used during the current recording or playback. This doesn't work in fast forward or rewind: if these are selected the display flashes to indicate that the elapsed time is no longer correct. In slow motion it goes to one tenth normal time irrespective of the slow speed selected, and in visual search it goes to seven times normal forwards or backwards as appropriate.

Whilst on the subject of displays, when the machine is first plugged in the clock display will flash if left, indicating that the clock has not been set to the correct time. This flashing should stop after two-three hours — the point when it stops flashing indicates that the timer back-up battery is fully charged. Finally the machine incorporates "fine edit", i.e. when record is selected the tape backs up for a few seconds then locks on to the control pulses of the previous recording before going into record, so that the transitions between "takes" are noise free.

Two other new models have recently come in, the Hitachi VT14 and VT17. The VT14 is a top loading stereo machine with Dolby, similar to the VT11. The features include I.R.T. (instant record timer), which enables the machine to be set to record for up to four hours in thirty minute steps without setting the timer. The VT17 is a front-loading two-speed machine with four heads two extra ones for the long-play facility. On playback the machine automatically selects long or standard play as required. The slow motion is at half speed, not stepped as in the Mitsubishi machine, and the comprehensive range of features includes picture sharp/soft control. A small improvement is that the infra-red receiver has been moved up to near the top of the machine instead of being tucked away virtually underneath as in previous models. **D.S.**

Hitachi VT9300

A niggling fault with the Hitachi VT9300: I've had three of these machines now with dirty channel change switches as they approach one year old. It's simple enough to cure, just take the front off and spray with Servisol, but shouldn't really be necessary and is the first time I've had trouble with channel change switches. **D.S.**

Panasonic NV2000

The complaint we had with a Panasonic NV2000 was warble on the sound, and certainly the speed seemed to be fluctuating every half second or so. I tried the easy way first, but a new capstan motor did not provide a cure (incidentally this comes as a unit complete with a loading motor). On scoping the waveform at pin 12 of IC2005, part of the capstan set-up procedure, I found that instead of a regular trapezoid the waveform went from a small sawtooth to a large one over a period of four cycles, followed by two cycles of the correct waveform, then back again. This waveform is generated in IC2005, but an output goes to IC2001 and on spraying this with freezer the correct waveform would return. Changing IC2001 alone didn't completely cure the fault however: both i.c.s D.S. had eventually to be replaced.

Mitsubishi HS320

We've had a couple of faults on Mitsubishi HS320s. The first was clearly playing at the wrong speed, and the drum speed was also off. Waveform 25, which is derived from a crystal oscillator on the chroma panel, was found to be missing, due to the crystal (X6A0) being faulty. The second machine occasionally laced up only half way before going into play. This was soon traced to the microswitch that tells the machine when lace-up is complete — it's position needed altering slightly. The switch is located in the far left corner of the machine, by the end of travel of the left loading arm.

Apparently both these faults are to be expected. Mitsubishi mentioned another fault, though we've not had it yet. This is the tape-end phototransistor going shortcircuit, giving the symptom that the tape will travel in one direction only as the machine thinks it's at one end of the tape. An unusual point is that one of the phototransistors is mounted directly on one of the panels. This means that care is required if this panel is removed during servicing as

TRANSISTORS AD161 32p BCX34 11p NKT453 1.65 AD162 32p BD131 30p PN107 7p	MIXED	DAOVO	BRC/ D/200 1.00 TA7109AP 2.80
10100		PACKS	BRC/M/300 1.00 TAA611 1.40
AD162 32p BD131 30p PN107 7p AC131 40p BF137 20p R1038 80p	300 Mixed Resistors 1.50	10 Spark Gaps 1.00 10–16 pin Quil IC Socket 90p	ML237B 2.00 TBA120C0 70p MC1327AP 1.25 TBA395 1.00
AC138 40p BF197 15p R1039 80p AC153 32p BF199 15p R20088 1.80	300 Mixed Capacitors1.50150 Mixed Electrolytics2.00	20 Assorted TV Knobs 1.00	MC1358P 1.30 TBA4800 1.40 SAA5010 6.00 TBA641 2.05
AC141K 39p BF238 20p R2010B 1.10	100 W/W Resistors 1.00	10-16 pin Quil to Dil IC Socket 90p	SL432A 1.80 TCA270SA 1.05
AF239 41p BF255 10p R2265 1.30	20 Mixed Conv Pots 1.00	100 Mixed Diodes 1.00	SL1430 2.50 TCA270C 1.05 SAS590 2.60 TCA270CQ 1.05
BC108A 15p BF257 28p RCA16446 30p	40 Mixed Pots 1.50	50 Mixed Mica Washers 65p 300 Mixed Resistors & Capacitors	SN15846N 60p TDA1035T 3.50 SN74123N 65p TDA1170S 1.50
BC109B 15p BF259 28p RCA16599 1.25 BC109C 15p BF274 11p RCA16600 1.40		1.50	SN74154N 1.40 TDA1200 2.42 SN76013ND/HS 1.80 TDA2540 3.50
BC117 21p BF435 41p 2N3703 20p BC142 30p BF450 43p 2SA473 10p	40 Mixed Presets 60p 20 Mixed VDR & Thermistors 1.00	10-16 pin Dil to Dil IC Socket 1.00	SN76023N 1.80 TDA2690A 1.50
BC153 16p BF459 40p 2SC346 8p BC154 16p BF460 58p 2SC1162 48p	20 Mixed Von & mermisters 1.00	50 Electrolytics & 50 Capacitors 1.00	SN76033N 2.00 TDA3560 6.00 SN76115 2.00 TDA9503 2.90
BC159 15p BFR87 25p 2SC785R 12p BC171 9p BFT42 30p 2SC3020 15p	100 Mixed Ceramic Discs 1.00	50 Mixed Poly Capacitors 1.00	SN76226N 1.25 TEA1009 1.95 SN76227N 1.00 MC14426P 4.80
BC172 9p BFT43 30p 2SC388A 20p BC174B 23p BFY51 34p B2322 50p	20 Mixed Valve Bases 1.00	30 Mixed Neons & Bulbs 1.00	SN76544N 1.20 MC14429P 4.50 SN76660N 80p MC14514 5.00
BC182LB 12p BFY52 34p R2323 50p BC184LC 12p BU105 1.00 TIP31 35p			SN76666N 75p UA758PC 2.50
BC208 9p BU126 1.10 TIP32 35p BC237 12p BU207 1.05 TIP110 80p	AERIAL SOCKETS	Thom Mains TX 3000/3500 7.50 Thom Mains TX 8000/8500 10.00	TA71MP 1.00 UPC1365C 5.75 SW153 2.50
BC238 8p BU208A 1.15 T9010V 1.45 BC251 8p BU326A 1.30 T9016V 1.20	AE Socket & Lead. Pye, ITT, Thom 25p AE Socket & Lead. GEC 25p	Thorn S.O.P.T 8000/8500 3.50 Thorn Scan TX 3000/3500 6.00	DIODES AA112 8p IN4007 6p
BC307 10p C1172B 9p T9017V 1.20 BC308 8p C1129 9p T9050V 1.50	AE. Socket & Lead. (long) GEC 25p AE. Socket & Lead. Pye 691/693 25p	Thom HT TX 3000/3500 6.00 Thom LOPT 9600 12.00 Thom LOPT 1615 7.25 Thom LOPT 1615 7.25	AA119 8p IN4742A 8p
8C347 8p E9005 14p T9051V 1.00 BC394 8p E5386 14p T9052V 1.30	AE. Socket & Lead. Philips KT3 25p AE. Socket & Lead. Thorn col. portable 25p	Thom LOPT 1615 7.25 Thom LOPT 1590/91 7.25	AA143 8p IN52548 8p BA115 8p IN5349 14p
BC454 8p ME0404 8p T9053V 1,30 BC455 8p ME0412 8p T9054V 98p	AE Socket & Lead. (long) Pye 725/731 25p	Thom LOPT 1690/91 725	BA154 8p IS025 8p BB103 8p IS131 8p
BC460-6 40p ME6002 8p T6059V 1.00 BC549 8p MJE182 47p \$2800B 90p		Thorn LOPT 9600 17.00 ITT LOPT CVC1-9 9.60	BR303 46p IS1658 8p BT106 1.50 MR854 35p
BC556 8p MJE340 50p S2800C 1.00	UHF TV Aerial for portable 50p Indoor Aerial Parabolic Type Reflector	Pye LOPT 713 10.00 Pye LOPT 725 9.85	BT116 1.00 SKE1/02 20p
BC595 8p NKT241 8p S2800E 1.40	to Help Combet Ghosting Problems 2.50 Line Connectors 38p	Pye LOPT 169 9.70 GEC LOPT 3133 7.40	BY127 12p MCR406 35p BY204 26p TIC106C 40p
	Coax Plugs 10 for 1.65 Band Change Switch Assy, Pye 725 40p	Diode Split OPT AT2076/35 14.75	BY298 22p TIC45X 50p BYX22/400 30p 2N4444 1.50
$\begin{array}{llllllllllllllllllllllllllllllllllll$	Flush Mounting TV/FM Diplexer 1.00	Sanyo LOPT AM-WM-21 6.75 Sanyo LOPT AM-WM-21 6.75 Sanyo LOPT AM-WM-4 7.30 Philips LOPT G8 7.80	IN60 8p Y827 80p IN2070 8p ZX150 12p
with Focus Silder & Leads 2,75	Switched Flush Fitting Aerial Outlet 1.00		IN4001 4p 0A91 5p IN4002 4p MCR106/7 1.00
Pye 713 Control Knobs 4 for 50p Tube Base Socket ITT CVC32 45p	CAN TYPES	MULTISECTION CAPACITORS 100+150+150 16+16 450V 45p	IN4003 4p MCR106/8 1.50
Tube Base Socket Thom 3000/8000 etc 50p IC Inserter 16 Pin 50p	0.2MF 250V 50p 1250MF 40V 50p 2MF 250V 50p 1250MF 50V 50p 22MF 275V 50p 1500MF 70V Thorn 3K	350V 50p 200+100+100+50 220+47 350V 65p 350V 60p	IN4004 5p TD3F800H 2.80 IN4005 5p TD3F800R 3,00
Large IC Extractor 50p Crystal 4.43MHz 65p	50MF 275V 50p 1.00	200 + 150 + 50 350V 60p 200 + 200 + 100 200 + 200 + 100 350V 55p	1N4006 59 BY255 30p
EHT Lead & Cap for Split Oiode Lopt 90p Anode Cap 47p	100MF 150V 65p 1500MF 100V 1.05 100MF 250V 70p 2000MF 30V 50p	325V 54p 200 +200 +75 +25 32 +32 +16 275V 52p 350V 60p	ZENER DIODES TOSHIBA 200MV 10p each
Sanyo Anode Cap Assy + Lead. 12TCD-CT-1665p Degause Thermistors. PT37P. ITT/GEC 35p	100MF 450V 75p 2200MF 40V Thorn 4K 220MF 400V Thorn 9K 95p	200+200+100+32 16+16 500V 45p 350V 70p 50+50+8 300V 55p	6.2v, 12v.
Degause VDR E299D /HP230 3000 /8000 25p Casters Set of 4 1.90	1.3.0 2500MF 35V 65p 220MF 450V Thorn 4K 2500MF 40V 65p	100 + 50 + 150 350V 58p 100 + 50 + 100 350V 55p 400 + 400 200V 72p 16 + 16 350V 45p	BZY88 10p each 3.9v, 5.6v, 12v, 16v, 20v, 30v, 33v.
Double Fuse Holder on Small Pax Board 20mm type 10p	1.30 3000MF 30V 65p 400MF 350V Thom 8K 3300MF 16V 50p	32 + 32 + 16 350V 52p 100 + 150 + 50 350V 55p	TOSHIBA 500MV 10p each
Single Fuse Holder on Small Pax Board 20mm type 5p	1.00 3300MF 25V 60p 800MF 250V Print 4700MF 16V 72p	350V 70p 63V 1.20	5.6v, 6.8v, 7.5v, 8.2v, 11v, 15v. BZX61 16p each
Direct Panel Mounting 20mm Fuse Clips (pair) 15p	type 80p 4700MF 40V 75p 800MF 250V 70p	200+200+100 300V 1.80	9.5v, 10v, 11v, 15v, 27v, 72v.
Single Fuse Holder on Small Pax Board. As per early 3000 mains input 6p		200 +100 325V 65p 500 +500 175V	MAINS DROPPERS
EHT Cable Metre 25p 13A Plugs 12 for 4.80	CAPACITORS	Thorn TX9 1.00	Pye 78 + 161 50p ENT TRAYS
TX9 Tube Base and Panel 65n	3.3PF 350V 3000PF 2KV 6.8PF 63V 3300PF 250V	ELECTROLYTICS 1MF.63V 20/£1 100MF 25V 10/£1	Pye 147 + 260 50p Thom 56 + 1K + 47 + 12 Thom 3000 5.50
3K PSU PL22 edge connector. 40p + Lum to PSU (New)	8.2PF 350V 4700PF 400V 10PF 350V .0047MF 500V	1.5MF 63V 20/£1 100MF 160V 10/£1 2MF 350V 10/£1 150MF 25V 20/£1	1.00 Thom 8000 3.50 Thom 50 +40 +1K5 60p Thom 8500 5.00
3K5 Complete Lum with all Plugs (New) 2.00 LM340 T12 on Heatsink 25p	12PF 1000V 0075MF 2KV 22PF 63V 01MF 250V	2.2MF 25V 20/£1 160MF 25V 20/£1 4MF 64V 20/£1 160MF 40V 10/£1	Thorn 128 +16 +1K7 + 11011 6500 5.00
T9051V on Heatsink 60p BF259 with Heatsink 14p	30PF 63V .01MF 600V	4 MF 350V 10 /£1 250 MF 16V 10 /£1 6.8 MF 40V 20 /£1 250 MF 25V 10 /£1	Thorn 120 + 72 + 300 Thorn 9600 6.00
TIP110 with Heatsink 40p L129/130/131 Coil 10p	47PF 350V .015MF 400V 182PF 63V .02MF 200V	10MF 40V 207E1 330MF 10V 207E1 10MF 160V 107E1 330MF 35V 107E1	50p RBM 250+14+58 Thorn 900/950 3.00
6MHz Ceramic Filter 25p DL700 (Philips) Chroma Delay Line 1.00	250PF 2000V .02MF 250V 330PF 63V .022MF 250V	15MF 16V 207E1 330MF 63V 107E1 15MF 63V 207E1 470MF 63V 207E1	(TV161) 63p Thom 1500 3 stick 3.40 Pye 3R5+15+45 (713) CFC 2000
DL50 Chroma Delay Line 1.00 T9006A Lum Delay Line 1.00	330PF 160V 047MF 400V 330PF 8KV 1MF 250V	22MF 10V 20 /E1 470MF 10V 10 /E1 22MF 63V 20 /E1 470MF 25V 10 /E1	90p GEC 2100 5.39 Pye 713 4 lead 5.83
8K5/9K Lum. Delay Line 65p Plastic Cover for 3K5 SP8385 5p	470PF 250V 1MF 600V 560PF 63V 22MF 400V	22MF 160V 10/E1 470MF 40V 10/E1 32MF 275V 10/E1 680MF 40V 10/E1	CUT OUT Pye 713 5 lead 5.97
TX9 Back Ground Control 10K 15p TX9 Gain Control 100R 15p	1000PF 250V .33MF 250V	33MF 40V 207E1 1000MF 10V 107E1 33MF 50V 207E1 1000MF 18V 107E1	Thorn 3000 Metal 1.45 Pye 725 6.35
1500 Metal Chassis Supports Pair 40p Thorn 8K5 Focus Pot 2.40	1500PF 250V 39MF 250V 1800PF 160V 47MF 250V	33MF 250V 107E1 1500MF 16V 107E1 33MF 350V 107E1 1500MF 35V 107E1	Thorn 8/8500 Plastic 1.45
Thorn 4000 Focus Pot 2.75 Thorn 18Ω 9W (3K5) R752 30p	2700PF 63V Any 10 @ £1.00	50MF 25V 20/£1 2200MF 25V 6/£1 100MF 18V 10/£1 2200MF 40V 6/£1	FUSES
			20mm 11/ 50MA 10 for 70p 250MA 10 for 65p
THICK FILM RESISTOR UNITS 3500 Thom (5 Pin Connection) video 1.70	2R 5W Thorn 3K 30p 36R 17W 23p	330R 7W 16p 4K7 7W Fus. 25p	315MA A/S 10 for 50p 750MA 10 for 65p 500MA 10 for 50p 7A 10 for 50p
4000 Thorn (4 Pin Connection) 1.90	2.2R 4W 16p 235R 9W Fus. 25p 3.3R 9W 30p 220Ω 7W Fus. (Korting)	370R 17W 23p 5K1 7W 16p 1K2 10W Fus 25p 8K2 7W 15p	1A 10 for 50p 10A 10 for 50p 2.5A 10 for 1.00 20A 10 for 50p
TANTALUM CAPACITORS	10R 9W 18p 30p 10R 9W TX9 20p 270R 5W 15p	2K2 5W Fus. 25p 8K2 9W 8K Thom 20p 10K 7W 15p	3.15A 10 for 1.00 50A 10 for 50p
0.1MFD to 470MF 6.3v/10v/16v/35v £6 per 100	15R 17W 23p 270R 7W 16p 22R 9W Eus. 25p 280R 17W 23p	2K2 /W Fus. 25p 10K 9W 16p 2K7 9W Fus. 25p 12K 9W TX9 20p	AM-LS-200 Mono Scancoils Sanyo 1.00 M-LS 145 Mono Scancoils Sanyo 1.00
MINIATURE CERAMIC DISC	27R 7W Fus. 25p 330R 5W 15p	3K9 4.5W Fus. 25p 39K 4W 15p	4–2761–44570 Scancoils Sanyo 1.00 Thom 4000 Coil L401 40p
1PF to 10NF 50v/250v/500v £2 per 100 or £15 per 1000	Thorn 8/8K5 ex equip panels Thorn 3/3K5 ex untested untested	morn would rou panel ex-	Thom 4000 Coil L701/2/3 12p
HIGH VOLTAGE DISC	PSU 2.88 PSU	3.75 factory 2.50	Pye 713 Coil L831/832 65p Philips G8 Coil L482 Late Type 65p
Most Values Available 2KV to 12KV £5 per 100 or from £40 per 1000	FTB 3.75 LTB Decoder 4.00 Video	2.50 boxed 4.75	Philips G9 Luma Delay Line 90p Pye 713 Luma Delay Line 90p
With these items No Mixed Values in Lots of 100	Thom 9K ex equip panels Chroma	2.00 new 1.75	Convergence Yoke Assy AT1023/05 5.90
SERVICE AIDS	PSU 12.00 IF	1.75 PC206 new 2.75	SWITCHES ETC Rank A823 4 P/B Assy 5.80
Ambersil MS4 Silicone Grease 12oz 2.15 Ambersil Freezer 12oz 1.99	Thorn OKE an again name	3.75 Thom 3/3K5. EHT & scan TX +	Telpro 4 P/B Assy 5.80
Ambersil Amberlube 6oz 1.89 Ambersil Ambertron 16oz 1.95	Thorn 9K6 ex equip panel Autovox Decode boxed	er FG/01 new R2008B on alum chessis ex- 5.00 equip 1.80	Thorn 3500 6 P/B Assy + Leads 1.75
Ambersil Anti-Static Screen Cleener 7oz 1.95 Ambersil 40 + Protective Lubricant 14.1oz 2.15	Decoder 5.75 Autovox IF & tur Thorn TX9 main panel new boxed	ner penel A/01 Thom 8/8K5 damaged FTB for	ITT CVC9 On/Off Switch + Relay 90p Philips G8 On/Off Switch 65p
Ambersil Amberclens Foaming Cleaner 13oz 1.26	Complete (no tuner) ex- Thom 4000 Conv		Thorn 3/3500 A1 Switch 50p
Ambersil Circuit Lacquer 14oz 2.15	factory 11.00 ex-factory	3.75 for spares 2.25	Thorn 4000 A1 Switch 50p Korting Shift Pot 50Ω 65p
POST A PART	ELECTRONICS		2-5A Push to make on/off switch 15p
236 FURTHER		TRADE COUNTER	NOW OPEN
CANVEY ISLA	ND. ESSEX	ORDERS DESPATCHE	
		ADD 60p P&P, THE	N 15% VAT.
Telephone 0	200 090000		
Telephone 0 Telex 99305	DOCCED C	ADD POSTAGE FOR OVE	RSEAS ORDERS.
Telephone 0 Telex 99305	DOCCED C	ADD POSTAGE FOR OVE DERS WITH AEROSOLS, PLE	RSEAS ORDERS.


HUSSAIN CENTRAL TV

Clearance deal to the trade

10,000, yes, 10,000 sets to be cleared at ridiculous prices in ones or hundreds, i.e. Pye 205 £3, GEC Hybrid £3, Philips G8 £5, and mono's £1.50.

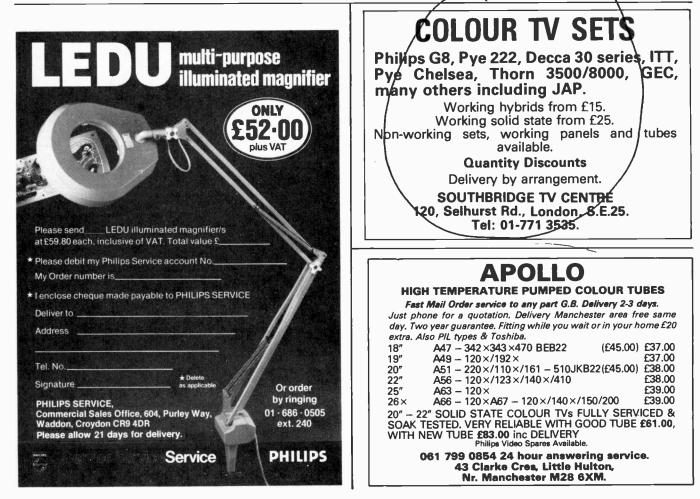Hundreds of modern sets at giveaway prices, i.e. Philips G11, G9, Grundig, Bush T20, Thorn 9800, Solid State ITT, Decca 100 and 80, etc.





that end sensor will then be inoperative. Likewise care should be taken to ensure that the panel is refitted correctly so that the sensor lines up with the hole in the cassette housing. **D.S.**

Ferguson 3V29

Here's one that nearly had me swinging from the trees every 10-60 seconds the tape speed appeared to slow for a fraction of a second, giving the symptom of intermittent sound slurring. All the pulses seemed to be rock solid except, after close scrutiny, the capstan trapezoid waveform which altered just slightly. After changing the main servo chip IC3 (HA11711) without success I decided to speed things up a bit by changing the servo panel complete. Again no joy. Neither did changing the motor drive amplifier panel make any difference. So it seemed that the capstan motor was suspect.

This is where things got really bad. A new motor was ordered and fitted, but the problem remained. There was another machine close by, so clutching at straws I changed the capstan. Again no difference. To cut a long story short, a motor from another machine was tried. A certain amount of swapping about was then done in order to check the motors, which were eventually cleared of suspicion. The only other item in the faulty machine was the electrolytic capacitor across the motor, C001. This final remaining item turned out to be the culprit. M.S.

Grundig 2 × 4 Super

No vision on playback, except for several diagonal lines, was traced to L723 (a 4.7μ H choke) in the drop-out compensation circuit on the Y module being opencircuit. T.L.B.

Ferguson 3V29/3V30

In the event of erratic, unstable picture and sound, possibly intermittent, check the stability and accuracy of the 12.5V regulated line at TP1 on the power supply panel. If the voltage is high or unstable, suspect the preset R5 (1k Ω) which can go high in value or become erratic in operation. T.L.B.

Hitachi VT11E

The fault on this machine was no output from the r.f. modulator. Although it's not shown in the Hitachi service manual, the 9V rail to the modulator is fed via what appears to be a 6.8μ H choke just inside the can, near the edge connector. It seems to go open-circuit for no apparent reason – it's one of those chokes that look like a capacitor that looks like a resistor! T.L.B.

Toshiba V8600

The fault with a Toshiba V8600 seemed to be slight tuner drift, as a result of which the colour would go off. I found that by pressing down on the tuner can any selected channel would go completely off tune. When the tuning pin voltage was measured whilst pressing the tuner can down it was found to rise to about 30V. Checks around the channel selector chip (μ PC1363C) in the fault condition then showed that channel 1 (pin 11) was rising from 0V to 31V while supply pin 14 dropped to 0.5V. The trouble was due to a crack in the 12V supply line print

TELEVISION AUGUST 1983

close to the tuner's earthing lugs. I assume that the crack had been "resistive", lowering the voltage at pin 14 and causing pin 11 to rise off ground to give slight detuning. L.H.

ITT VHS VCR

This was a strange fault with an even stranger cause. The machine was an ITT one, similar to the Ferguson 3V29. The customer's complaint was that if the third channel button was selected and the machine set to make a timer recording the channel selector would reset to channel one. On trying the machine in the E-E mode we found that the channel reset to number one and in addition the clock display disappeared when the power supply panel was prodded. So we measured the 12.5V regulated supply and prodded the panel. The voltage dropped to 10V. On investigation we found that a diode had been dropped on to the panel during production. It had got trapped under the set 12.5V preset and was intermittently shorting the wiper to one end of the track!

JVC HR7700/Ferguson 3V23

Perhaps the most obscure and difficult faults to locate on these machines are those on the mechacon panel. The problems are aggravated by the use of double-sided print, and it's not uncommon for the panel to act as a catchment for liquid spilt into the machine.

A recent illustration of this was a machine fitted with the original mechacon panel. The initial fault was no tape loading (not no cassette loading). This turned out to be due to transistor X7 (2SA1020) in the loading motor control circuit being open-circuit. Further checks revealed that there was no fast forward control or rewind in the cue memory mode. The counter memory mode worked perfectly, so it appeared that in the cue mode the microcomputer control i.c. (ICI) was receiving a permanent cue signal. Tracing back, we found that pin 12 of IC26 (data selector cue signal input pin) was low, indicating that a cue signal was present. Investigation in this area brought us to R223 (10k Ω) which had gone open-circuit due to corrosion. It's the collector load resistor for the cue signal switch transistor X49, which is directly coupled to pin 12 of IC26. M.J.C.

Ferguson 3V23

The fault on a 3V23 fitted with the early mechacon board was no reel motor functions, and it was immediately evident that the reel motor switching transistors X24, X23 and X18 had all suffered badly. These were replaced and the other five transistors in the reel motor switching network checked and found to be in order. We next checked transistor X2, which controls the voltage applied to the reel motor and hence its speed, and X2's driver transistor X46. Both were o.k.

On applying power smoke came from X18 even though no reel motor function was selected. So X18 was replaced and X2 removed. On applying power once more we found that X46 was hard on. It's controlled by the microcomputer IC1, via various items including IC9 which is connected to pin 11 of IC1. The voltage at this pin was high, but in my experience of these machines I've never known the microcomputer i.c. to be faulty. Fortunately it turned out that IC9 was at fault with an internal short – it's a CMOS gate i.c., type TC4025. M.J.C.

The Betamax Video System

Part 1

There are currently three competing formats on the domestic VCR market—Betamax, VHS and V2000, which were developed by Sony, Matsushita/JVC and Philips/ Grundig respectively. It's likely that all three will be with us for many years to come, if only because of the huge investments these systems represent for the manufacturers on the one hand and the purchasers/rental organisations on the other. It's true to say that there's very little difference in the performance of the three systems, and that it's very difficult to tell them apart simply by viewing a replayed picture, providing we are comparing like with like in terms of screen size, software quality, signal coupling to the TV set (video or u.h.f.) and so on.

Format Comparison

The main features of the three formats are shown in Table 1. It can be seen that the Betamax system uses the highest writing speed at 5.83m/sec — the head drum is relatively large and the peripheral speed is thus high. This offers the best conditions for a wide luminance frequency response. The linear tape speed is low: whilst this is a disadvantage in terms of audio quality with conventional longitudinal sound recording, it combines with the narrow video track width (approximately 33 microns) to give a high recording density figure, approaching that of the V2000 system. Hence the Betamax cassette is significantly smaller than those of the other systems and is the only one that fits easily into a jacket pocket. In other respects there's little to choose between the specifications of the three systems in terms of performance.

The early machines produced by all manufacturers in the Betamax camp tended to have a battleship air about them — they were large, heavy, and often finished in grey and black! They are rugged and robust however, and built to last. Second generation machines such as the Sony C5 and C7 are also bulky, but this image has finally been shaken off by current machines such as the Sanyo VTC5300 and the Sony F1 and C9.

Most Betamax machines (the Sanyo VTC5000 is an exception) perform fast transport operations with the tape fully laced up — there is little evidence that this leads to undue head wear, as was originally feared. Initially this feature saved frustrating seconds when searching for a particular point on the tape, but the advent of picture search and "counter go to" facilities on later machines of all formats have overcome this problem.

The Tape Deck

One reason for the ponderous look of early Betamax machines is the deck layout, with the large video drum and the characteristic long, U-shaped tape threading path. Betamax threading is a little reminiscent of the Philips N1500 and N1700 series machines, in that a loop of tape is drawn out of the cassette and wrapped around the drum by means of a single post on a loading ring. In Betamax machines the loading ring completely surrounds the drum and the stationary heads as shown in Fig. 1. In the rest

Eugene Trundle

position, the threading post protrudes into the cassette holder, insertion of a cassette initiating the threading process. The loading ring then moves anti-clockwise through almost 270° while the tension regulator arm simultaneously moves out to define the tape exit path from the supply reel. This U-wrap system was developed from Sony's very successful semi-professional U-matic system: Sony maintain that tape friction and strain are less than with the alternative M-wrap system. It also has the advantage that the critical head entry and exit guides are kept separate from the threading mechanism, offering better alignment and long-term stability. It's certainly been my experience that tape interchange problems seem to be less common with Betamax VCRs. The total angle of the tape around the drum and guides is less than the 540° of the M-wrap system: it's claimed that this results in more reliable operation and reduced tape stress, as well as facilitating very high-speed picture search and the latest feature, swing search - this allows forward and backward running of the tape at normal speed without noise bars.

Because of the helical scanning and the fact that the cassette is parallel to the machine's plane, a change in the tape path angle is required — so that the tape starts its path around the head at a higher level than the exit point. The long return path A-B accommodates this feature easily and means that the drum and loading ring can be mounted parallel to the deck surface. The latter is at the required angle to the machine and the cassette. All this is in great contrast to the VHS system, where the deck, the machine and the cassette are all parallel but the head drum is tilted.

Fig. 2 shows a "linear" diagram of the tape path across the deck, drawn from the point of view of the tape — in practice tape guides A and B are at a higher level than guides C and D. After emerging from the supply reel the tape first encounters the tension regulator, which is a simple mechanical negative feedback arrangement operating on a brake band wrapped around the supply reel turntable. Next comes the adjustable guide A, which aligns the tape with the full-width erase head. This is

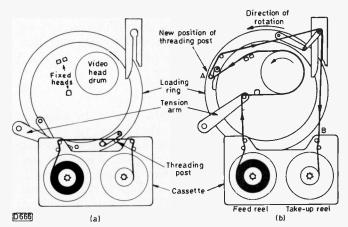


Fig. 1: The Betamax threading cycle, (a) at start, (b) at the completion of threading.

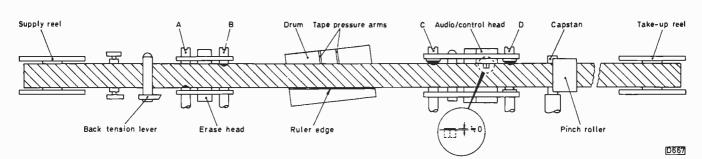


Fig. 2: "Linear" diagram of the tape path around the deck, drawn from the point of view of the tape. In practice tape guides A and B are at a higher level than guides C and D and their associated audio/control head. B is the head entry guide and C the head exit guide.

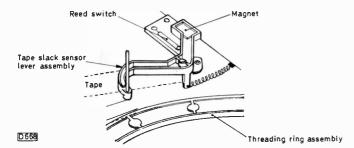


Fig. 3: Mechanical slack sensor used in Sony machines. When slack tape results in the sensing pole being deflected sufficiently, the magnet moves round to close the reed switch. This signals the syscon to enter the stop mode.

followed by the height adjustable guide B which also forms the head wrap entry guide. The tape now travels along a helical path around half the periphery of the head drum, guided by and sitting upon a ruler edge which is at exactly 5° to the plane of the path of the rotary heads. This sets the video tape track angle, which due to the linear movement of the tape during record and replay is slightly more than 5°.

The tape runs off the drum on to exit guide C, which is height adjustable, and then passes the audio/sync head and its associated, adjustable guide. The capstan comes next: it's deck mounted of course, but the pressure roller is fixed to the threading ring and is brought into engagement during record and play by a neighbouring solenoid. This completes the operational part of the tape path: from here the tape climbs up the gradient, around the spacing poles or rollers on the threading ring, and back into the take-up reel. In some machines it deflects a slack-detector arm on the way (see Fig. 3).

The different levels and sometimes slight inaccessibility of the stationary heads and guides can make thorough cleaning difficult in some models — I recommend the use of cotton buds on sticks (the sort intended for babies' ears)

Table	1:	Characteristics	of	current	formats.
-------	----	------------------------	----	---------	----------

Characteristic	Betamax	VHS	V2000
Video writing speed (m/sec)	5.83	4.85	5.08
Longitudinal tape speed (cm/sec)	1.87	2.34	2.44
Video track width (μm)	32.8	49	22.6
Slant azimuth offset	±7°	±6°	±15°
Information density (hrs/m²)	1.63	0.926	1.786
Cassette volume (cc)	368	489	523

TELEVISION AUGUST 1983

and a dental mirror for this. If the mirror is of the illuminated type, so much the better: it's also useful for examining the tape path when adjusting guides.

The method of driving the loading ring depends very much on the vintage of the machine. In later types a loading motor does the job, whereas early machines have an ingenious mechanical linkage from a single motor which is the prime mover of everything in the machine capstan, drum and all.

Video Head Drum

The head drum brings us to another fundamental difference between the Betamax and other formats. The Betamax head assembly is in the form of a three-layer "sandwich" with only the centre portion rotating. This has given rise to the term head disc rather than drum. A typical head disc is shown in Fig. 4, which also shows the tacho magnets. This form of head construction usually means that head cleaning must be done by holding the cleaning pad stationary on the disc's periphery, then rotating the heads via the drive belt. Where appropriate, this can be done by hand rotation of the motor fan. As with any video head cleaning operation, this must be done with great care — the 33 micron heads are no less fragile than those of any other format!

With all Sony machines and some Toshiba ones, eccentricity adjustment of the head disc is necessary when this has been replaced. It requires the use of a sensitive dial gauge which must be rigidly mounted on the disc's surface. Although the same dial gauge can be used on all models, the mounting kit varies — it's essential to have the correct type. Eccentricity setting is necessary to establish the exact centring of the video head disc before tightening

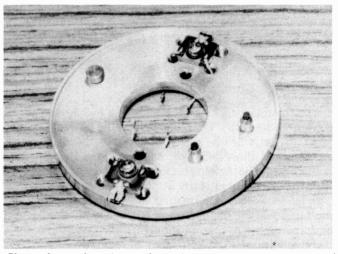


Fig. 4: Sony video head disc – the mounting screws, central to each head assembly, should be left severely alone!

its mounting screws, and is checked by rotating the head with the dial gauge sensing arm trailing on the disc's periphery. Great care is necessary here to ensure that the gauge sensor tip does not foul the video heads.

Sony mention dihedral adjustment in their manuals. This is a procedure whereby each video head can be "nudged" sideways via its mounting on the head disc by means of tapered screws on each side. The threaded holes for this can be seen at each side of the head mounting plate at the edge of the disc in Fig. 4. Although a setting-up procedure is given in the manual (using the monoscope portion of the alignment tape), I've never found it necessary to carry out this adjustment during many head replacements. The alignment of the heads on the drum is accurately set with a microscope at the factory, and there's no reason to doubt its accuracy — perhaps only if the machine was being precision adjusted as a master copier would dihedral adjustment be required.

As with all current formats, each head has an azimuth offset to avoid the need for guard bands between video tracks (slant-azimuth technique). For the Betamax system, head A is skewed 7° clockwise and head B 7° anticlockwise. In current machines the video head gap width is 0.4μ m, which with a head writing speed of 5.8m/ sec provides a minimum recording wavelength of 1.3μ m.

Test Cassettes and Jigs

A range of special cassettes and jigs is available for use during the repair and alignment of Betamax machines. They devolve into two categories: expensive ones that will be useful with any make or model of Betamax VCR, and cheap ones, such as eccentric screwdrivers and metal gauge blocks, which are designed for one model. Into the first category come the alignment tape, eccentricity dial gauge, forward/rewind cassette torque meter and handheld torque meter. They need careful handling, especially the dial gauge and hand-held torque meter, neither of which would survive a fall to the floor ... Along with the necessary colour bars and r.f. sweep, the alignment cassette has a monochrome (monoscope) test pattern that seems to make even a half-dead machine perform beautifully! All these items are essential if serious work on Betamax machines is envisaged, and it would be folly to attempt major deck servicing or component replacement without them.

A word of advice here. The major jigs and test tapes are common to machines made by different manufacturers, and it pays to shop around. A few minutes spent getting quotes on the phone will be amply repayed, as prices seem to vary widely — and as far as I can see the products are exactly the same!

Tape Track Configuration

The Betamax track layout is shown in Fig. 5. As with all current domestic VCR formats, the heads rotate anticlockwise and the tape is pulled past the drum in an anticlockwise direction. The diagram shows the tracks as viewed from the head therefore, on to the oxide side of the tape. Each head starts at the lower edge and writes one field of video information during its journey across the tape, leaving the top edge 20msec later. During this time the drum has rotated through 180°. The tape wrap is slightly more than this to give a small overlap period during which head changeover switching is done. The control and audio tracks are recorded longitudinally in the

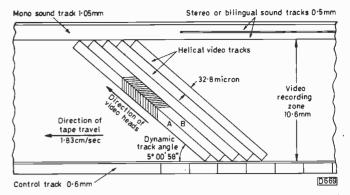


Fig. 5: Betamax tape track layout. The tape is 12 7mm $(\frac{1}{2}$ in.) wide. One control pulse is recorded for every two video tracks.

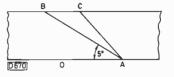


Fig. 6: The difference in track angle between moving and stationary tape.

conventional manner — the upper (audio) track is split into two for stereo sound etc.

The difference in the effective video track angle between tape which is moving and tape which is not has already been mentioned in passing. It arises from the fact that when the tape is moving the tape position advances during each head sweep — see Fig. 6. The static angle, OAB, is 5° as set by the drum ruler edge. If the tape advances by the distance BC during the 20msec field period however the head's path will be AC and the track angle OAC. In practice the difference is less than one degree, but with a 33 micron video track width it's quite sufficient to cause a grave tracking error, giving rise to the "torn" picture shown in Fig. 7 — this was taken during pause on a basic Betamax machine.

The position of the noise bar on the TV set's screen depends on the chance position of the tape track relative to the head path at the instant the tape stops, but in no position can it be eliminated. This problem, which is common to the VHS format, led to special arrangements being devised to get good still frame reproduction. These usually take the form of extra wide heads and shunting the bar out of the way at the top or bottom. Toshiba, in their

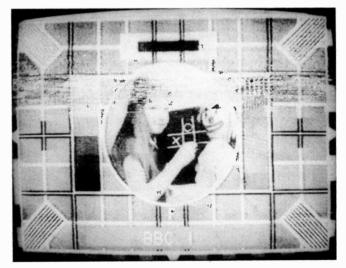



Fig. 7: Still frame noise bar produced by a "basic" VCR. The severe mistracking is due to the heads following path AB in Fig. 6 instead of path AC.

Model V8600, pioneered a more radical approach however.

Toshiba Four-head Drum

The four-head drum approach used in this Toshiba machine is depicted in Fig. 8. Heads A and B are conventional 33 micron Betamax heads and are used in the normal record and play modes. During still-frame reproduction, playback is via the special heads B1 and B2

Fig. 8: Toshiba four-head arrangement. The two auxiliary heads B1 and B2 both read B tracks.

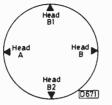

which are switched in for this mode of operation. Both have the correct azimuth slant for the B channel tracks, and they are extra wide to enable them to "see" enough of a B video track (provided the tape is stopped in a suitable position) to ensure noise-free reproduction along the whole length of the recorded TV field in spite of the difference in angle between the tape track and the head path.

The wide-head technique is now in common use – it's employed in many VHS machines to secure noise-free, still-frame pictures with two-head drums. For still frame in the V8600, the tape is inched along to a suitable position by the capstan servo: the resultant picture is in fact a repeated still field because both auxiliary heads are reading a channel B track. Subjectively, the results are very good. In conventional freeze-frame arrangements (with a two-head machine) an annoying judder effect is present when the televised subject is a fast moving one. This is because image movement takes place between field scans, so that the two-field still frame contains two different pictures! The Toshiba four-head machine is immune to this effect.

The Toshiba machine's auxiliary heads are used on trick-speeds too. Slow motion is in effect an advancing series of still-frame pictures with the capstan servo pulsing under the influence of individual control track pulses and a special slow-motion tracking control. The disturbance due to the effective angular displacement of the video tracks during double-speed replay is minimised by the extra width of the auxiliary B1 and B2 heads.

Deck Mechanics

The first generation machines in all formats were pianokey operated. Rather like an audio tape deck, much of the safety interlocking, and some of the function movements, were carried out mechanically by levers and slide bars operated directly by the keys. Great ingenuity went into the mechanics of these machines, and it's worth noting that Betamax machines were the only ones in common use with a single motor. Examples are the Sony SL8000UB and the Sanyo VTC9300, in which the single motor, necessarily a large a.c. type, drives all deck functions, the capstan, the drum, the take-up reel, fast forward and reverse, threading and all! The servo (there's only one) operates an eddy-current braking system, working on a disc mounted on the motor shaft. This latter arrangement will be familiar to many engineers as the basis of the servo systems used in the early Philips machines.

TELEVISION AUGUST 1983

When piano keys went out of fashion their place was taken by soft-touch controls. This idea makes great demands on the system control (syscon) department. The syscon acts as a policing system as it were, to forestall user abuse and prevent damage to the tape under normal (and most abnormal) operating conditions. Early leveroperated machines lent themselves to mode interlocking by means of a slide bar, and such chores as reel braking were carried out directly from the operating keys. Such a machine required only a relatively simple syscon, and simple logic chips, either a purpose designed one or a handful of general purpose TTL devices, sufficed.

A much more comprehensive syscon is necessary in a touch-button operated machine, and its functions need to include: mode interlocking; operation of solenoids for the pinch roller, reel brakes and, in some machines, cassette ejection (Toshiba hit the heights with the V8600, which has seven solenoids); control of up to five motors; generation of switching signals for various other parts of the machine; and so on. Thus our policeman has now become a very busy housekeeper as well! This role is ideally suited to a microcomputer i.c., at least one of which will be found in all domestic VCRs offering soft-touch control of the deck functions. Such machines as the Sony C5 and C7 are of this type. All this costs money, and a low-cost alternative has been engineered by Sanyo, a machine designed to provide picture search, electronic deck control and slim, light design, but still retail at under £300 in the UK.

Look – No Solenoids!

By clever adaptation of the tape threading system, the Sanyo VTC5000 manages without any solenoids at all. To achieve this it breaks new ground in the Betamax deck system by unthreading during the stop and fast transport modes, just like VHS. There are three stages of operation as follows.

In the stop mode the tape remains unthreaded, with the reel brakes on and the cassette eject lever free to operate. In fast forward and rewind the loading ring rotates to an intermediate position, with but a small loop of tape drawn out of the cassette. This first phase locks the cassette cradle down mechanically to prevent ejection and also takes off the reel brakes, these operations being carried out by a boss and cam respectively on the loading ring. Fast transport in either direction can now take place safely, driven by a single central reel motor with a swinging idler wheel which snaps to the left or right automatically (under the influence of the motor shaft) to drive the appropriate reel.

During play, record, pause and picture search the loading ring completes the full 270° or so of the Betamax threading path, and at the completion of the threading cycle a "loading-end" roller slips into a cam on the periphery of the loading ring. This operates a lever to engage the pinch roller and start normal tape movement, which continues (provided the capstan motor continues to rotate) until the loading ring once again returns to the stop or fast transport positions.

The reel drive motor in this machine also turns the reels during normal forward motion and for picture search in either direction. In these modes the reel drive is via a slip mechanism of course, and the engagement of this is also invoked by a mechanical link from the loading ring, on the basis that slip drive is required when the tape is fully threaded, direct drive being required when the ring is in the intermediate position. The back tension arm is swung

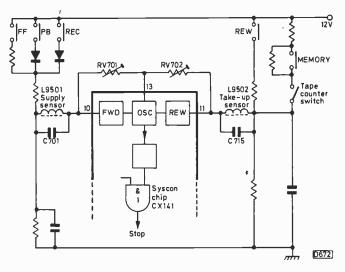


Fig. 9: Sony tape-end sensor circuit.

into position, during modes other than stop, by a further cam on the loading ring.

The new Toshiba V9600 uses a similar mechanism in a front-loading machine. This unusual deck system requires two extra syscon features. When the tape-end sensor is activated during rewind there may not be enough tape left on the take-up reel to provide the full threading loop, so the machine performs a short fast forward operation for tape safety's sake before entering stop. Secondly, to avoid the short wait for the machine to thread up each time the operator goes from stop to record or play (or vice versa) a so-called stop-pause mode is provided. In this condition the machine remains threaded ready for the next operation if required, thus maintaining the convenience of previous Betamax machines.

Automatic Programme Search

One interesting aspect of the syscon in current top of the range Betamax machines is the APS (automatic programme search) facility, which enables the user to find the beginning of each recorded sequence or programme on a tape without having to memorise the corresponding tape counter number. The idea is to "mark" the control track with a special signal that indicates each start point.

The basic format specification calls for control track pulses at 25Hz rate – a digital (on/off) signal with a 1:1 mark-space ratio. In APS machines the mark-space ratio of the control track signal is changed to almost 2:1 during the first nine seconds or so of each new recording. During rewind or forward APS the syscon examines the control track, recognizing the short-lived change in pulse width. Each time it happens, a one is clocked into a counter, and when the counted store equals the user's request the APS ends and play commences. This control track pulse width modification has no effect on the operation of the servos, since these are concerned only with the timing of the leading edges of the control track pulses.

Tape-end Sensors

The method of detecting tape end on Betamax machines is quite different to that employed with other formats. The idea is that a short piece of metallic leader tape is included at each end of the tape: this is magnetically detected by inductive end-sensor coils.

A typical circuit is shown in Fig. 9. The CX141 chip contains an oscillator that operates at 200kHz, the frequency being determined by the LC circuit L9502 and C715 - the coil forms the end-sensor. It's a small ferritecored coil mounted on the deck close to the take-up reel and held in contact with the tape. The oscillator runs normally during rewind, its output holding off the syscon's auto-stop circuit. When the leader tape appears, the end sensor coil L9502 becomes saturated magnetically as a result of which oscillation stops. The detector within the i.c. senses this and signals stop to the syscon. The same thing happens in the forward modes using the supply reel sensor L9501 which resonates with C701. The threshold of operation is set by RV702 and RV701 respectively. This seems as good a system as any for tape-end detection - there are no bulbs to burn out or contacts to keep clean, and the system is quite unaffected by the bench lamp during servicing!



George R. Wilding

Whilst mains-battery monochrome portables operate very successfully from a stabilised l.t. rail of around 11V, such a voltage is inadequate for use with a colour portable. Depending on requirements, quite a variety of design approaches are to be found in mains-battery colour portables.

Alternative Approaches

The Sony 9in. Model KV9000UB for example operates with a 22V rail obtained from a series regulator. For 12V battery operation a sort of miniature line timebase is used to produce the 23V required at the collector of the series regulator transistor. This "miniature line timebase" is driven from the collector of the line driver transistor and consists of an inverting amplifier, a driver stage and an output stage which produces a pulse output for rectification. Switching between 12V and 24V operation is automatic.

The National Panasonic 13in. Model TC333G (chassis M6A) operates with a 110V rail obtained from a chopper of the blocking oscillator type. This requires a 275V input which is provided by a simple rectifier when connected to the mains. For operation with a 12V battery, a conventional converter is used to produce the required 275V. It consists of an astable multivibrator which drives a pushpull power amplifier: the output transformer's secondary winding steps up the output which, after full-wave rectification by a bridge circuit, gives 275V d.c.

A rather different approach is used in the 11in. Sanyo Model CTP1101 and the 13in. Hitachi Model CWP130 (NP6C-3; chassis). These both use chopper circuits driven from the line timebase. In the case of the Sanyo set, 120V and 80V h.t. lines are produced from the secondary

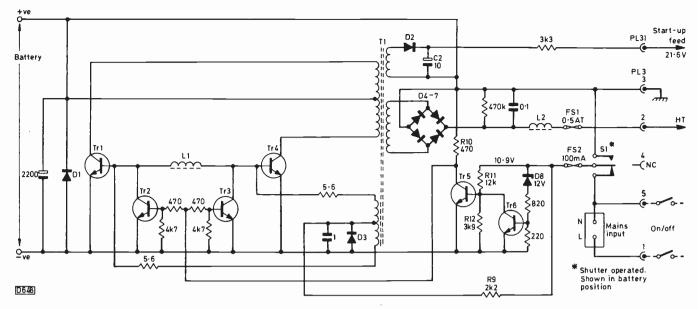


Fig. 1: Circuit diagram of the Thorn TA126 converter for use with later versions of the TX9 chassis, simplified by omitting the links for 12/24V operation. The converter will provide an average five hours' operation from a typical car battery.

winding on the chopper transformer. The main supply line produced across the transformer's secondary winding in the Hitachi set is 108V. In both chassis separate primary windings and chopper transistors are used for mains and 12V battery operation.

Thorn Colour Portables

Until the advent of the TX90, the only UK produced mains-battery colour portable was the 14in. version of the Thorn TX9 chassis. With both these chassis the converter is a separate, optional extra unit. There are two quite different converters for use with the TX9 chassis, due to the two very different power supply arrangements used in earlier and later versions of the chassis. In the earlier version the 115V stabilised h.t. line is produced by a regulating thyristor. Since a thyristor requires an a.c. input, on battery operation the converter (type TA92) has to produce a regulated output which is fed to the main chassis at the output of the thyristor circuit. The converter consists of a blocking oscillator arrangement with extra windings for 24V operation. An internal trip operates when the nominal 12V battery input falls to about 11V or alternatively if the current demand rises above 500mA.

In the later version of the TX9 chassis a self-oscillating chopper power supply is used – a Siemens type circuit controlled by a TDA4600 i.c. So the converter (type TA126), which again works with either a 12V or 24V battery, simply steps up the voltage to provide the 300V or so required by the chopper. It will not drive versions of the set with teletext or full-feature remote control, but can be used with the simple remote control systems U718 and U725, though in the latter case the standby facility will not be available.

The TA126 Converter

The complete circuit, simplified by omitting the links for 12/24V operation, is shown in Fig. 1. Transistors Tr1 and Tr4 form a push-pull oscillator with feedback via transformer T1 to their bases. R9 provides a start-up supply. The natural frequency of oscillation is 5kHz, but the addition of the saturation choke L1 raises this to 15kHz.

TELEVISION AUGUST 1983

In operation a 550V peak-to-peak waveform is produced across the winding that feeds bridge rectifier D4-7. As a result an unstabilised output of between 260V and 370V, depending on the input, is delivered via the interference suppressor choke L2 and fuse FS1 to the main chassis. D2 produces a chopper start-up supply of about 65V across C2. The main board chopper system with automatic overload protection is thus in operation with either a mains or battery input. An additional trip in the converter comes into operation if the battery voltage is excessive.

The receiver's normal on/off switch operates in both modes, there being no separate switch on the converter. As with the TA92 converter, the positive side of the battery is connected to chassis via pin 3 of plug 3. Thus one side of the receiver's on/off switch can be used to supply l.t. to fuse FS2. With the set switched off and the battery connected, the two transistors Tr2 and Tr3 will be forward biased via R10, shorting out the base-emitter junctions of Tr1 and Tr4 so that the oscillator is inoperative. With the set switched on, Tr5 is forward biased via FS2, R11 and R12. The bias to Tr2 and Tr3 is thus removed and the oscillator comes into operation.

Tr6 provides the trip action. It's normally non-conductive since there's insufficient voltage for the zener diode D8 to conduct. If the battery voltage exceeds 16V, as could happen under heavy charge or at charge completion, D8 conducts and Tr6 switches on. Tr5 is thus switched off and the oscillator is stopped via Tr2 and Tr3 as when the set is switched off. Note that D8 must be changed to a 27V type when the unit is used with a 24V battery. With a low battery voltage the under-voltage trip in the chopper circuit will come into operation, the receiver cycling on and off.

Fitting the TA126 converter is simplicity itself. The original plug-in mains lead is removed, since the converter is supplied with a separate mains lead with two-pin connector for inserting into the rear shutter socket. PL3 is then plugged into the socket previously used by the original mains lead and PL31 connected. With no internal or external adjustments, the converter provides a neat solution to battery operation. There's an in-line fuse in the battery lead (negative side): this must be rated at 8A with a 12V battery and 4A with a 24V battery.

Dotty Daydreams

Les Lawry-Johns

Before I tell you about Dotty, I must first tell you about the visit we had from a well known contributor to *Television*. During a quiet moment one morning the door opened and in walked this tall, handsome fellow, a sort of cross between Howard Keel and Humphrey Bogart.

"Is this Tiny Tim's shop?" he asked.

"Yes sir" I replied, thinking it was the inspector of taxes.

"Keith Cummins, glad to meet you" he announced.

"Well bugger me sideways" I stammered. "What a nice surprise. Come and meet Keith, Honey Bunch."

So we exchanged pleasantries before getting down to the serious business of running down the editor. After a while we agreed that maybe he wasn't quite such a bad bloke really, and after all someone had to think of the readers sometime or another.

During the conversation an assortment of characters wandered in and out, giving us their views on life and death, talking as though their affairs were of great importance and not realising how important were the people to whom they were addressing their trivialities. One was the author Alex Granger, who had just written a book about himself and signed a copy for us. Another was Johnny Moon who is, er, Johnny Moon.

The morning passed pleasantly enough, and in due course Keith had to go, collect his wife, and wend his way back to Southampton. Cheers Keith! Nice to have met you.

Brown Eyes

My dream girl true has eyes of blue,

but I think I could go for brown.

A picture of love, was this turtle dove,

from her head to her feet right down.

H.B. had been to visit her sister, and on her return reported that the HMV radiogram had at last broken down. It had been agreed that I would pay a visit to repair it. Which is how I came to be ringing her door bell that morning.

Dorothy answered and gave me a welcoming smile. When Dorothy smiles you know you're being smiled at. I've never really got used to those enormous brown eyes, those generous lips and perfect white teeth. She always seems to have a look of surprise on her face, and very nice it is too, except that is when she's addressing her son Fraser. A state of war has existed between them for several years, and there seems little likelihood of a truce at this late stage.

"Come in Les. Try not to tread on Tiny (the small dog) and steer clear of Gillie – she's been playing with the hedgehogs again and is full of fleas." Gillie is another small dog, though not as tiny as Tiny. "Keep away from Fraser too. He's smothered his face with his father's after shave again and stinks of the muck. Can't think why the girls keep phoning up for him. Queer taste some people have. Can't think what they see or smell in him."

"Henry Cooper says it works" growled Fraser.

Sensing that a battle was about to begin, I decided it was time to start on the radiogram. Switching on produced

a click and an audio hum, so the trouble was probably in the i.f. stages and with a bit of luck it would have AF117s in it. Easy to deal with – with a bit of luck. I removed the long rear cover.

"What do you think it is Les?" asked Fraser. "A bit of AF117 trouble?"

I looked at him amazed. "What makes you think that?"

"It said it was likely in that daft little book you wrote called questions and answers. You've probably forgotten and I don't blame you. I just looked in the back and saw some transistors that looked like them."

I couldn't agree with him of course. "No Fraser, it's probably the double diode triode's load resistor that's gone high in value."

Fraser looked at me for a long time. He's got a nice line in repartee. "Bullshit" he said.

The battle between Dorothy and Fraser then flared up briefly before Fraser got the message and went off on his bike. Meanwhile I'd crept behind the radiogram and carefully snipped the screen leads of the AF117s. The radio them boomed to life. In case you're wondering about this, the screen connection tends to short internally to the collector.

"I do apologise for Fraser" said Dorothy. "Don't know where he gets it from. Even his dad's a gentleman compared to that horror. He argues with his father about motor bikes. It never seems to stop. I can't bear it much longer. I've asked the doctor for some drop dead pills, but I'll probably end up by taking them myself..."

I packed my bag as quickly as I could. "I'll be off now Dot. Just in case Fraser comes back."

I told Honey Bunch about Fraser when I got back. She cheered me up no end. "Fraser starts work next week. At the builders on the corner." Fraser working, thirty yards away...

Another Disaster

Another Wally. When Walter came in carrying his Thorn 9600 I knew I was in for trouble. Not from the set I hoped. It's his way of rambling on about the old days. At the outbreak of war, before we both joined the Fleet Air Arm (that answers a few questions, doesn't it?). Wally said that the sides of the picture were bowed in, so naturally I thought of the BY298 in the EW modulator circuit. It does lead a hard life. So I turned the set on its side, slapped a BYX71 across it on the print side, and snipped the supect from the top.

I turned the set upright and switched on. There was still slight bowing, but this was easily corrected by the presets on the small correction panel. The upsetting thing was that everything on the left side of the screen appeared in the wrong colours. People on the left-hand side had blue faces and didn't become normal until they moved to the centre of the screen. I questioned Wally about this, but he maintained that everything had been fine until I'd upended the set. I was not inclined to suspect the decoder, but did have fears about the shadowmask. If it had slipped, would it go back or did it need help? I turned the set up on the opposite end and gave it a sharp slap.

"Oh charming" said Wally. "I bring my set in for repair and you bash it to bits."

On the level the picture remained the same. With blue faces on the left. I didn't know what to do. So I muttered something about leaving it to bed itself in for a while.

This gave Wally the opportunity to tell H.B. about the time when we were both operators (projectionists) at the Majestic cinema (now ABC 1, 2 and 3) at the beginning of 1940. I'd been there only a couple of days and hadn't had a chance to get to know where everything was. It was the chief's day off, and as the second was having his tea break I was in charge. It was the organ interlude. Up came the mighty Crompton, with Tom Linn playing it. Wally showed the slides so that people could sing, and I kept Tom in the spotlight. The final slide was shown and it was time for the organ to descend again into the depths from which it has sprung some ten minutes before. Nothing happened and Tom looked around and up at us. People began to laugh as they realised that the organ was there to stay. It was up to me to do something however. After all I was in charge. "Close the tabs Wally" I bawled, "I'll nip down and see what's wrong." Or words to that effect.

So I rushed down the ten thousand stairs, knocking over the ice cream girl (complete with tray) on the way. Down into the stalls, through to back stage, down into the organ room. Still strangely empty. I looked around at all the fuse boxes and my heart sank. Too many. But something had to be done and done quickly. I pressed the buttons near the motor, but nothing happened. No juice to the motor. Then I saw a handle on a clip at the rear of the motor. There was a clip to engage a gear for manual operation.

Quick as a flash I inserted the handle and engaged the gear. I turned as fast as I could but it was a pretty low gear. I turned and turned and the organ came down an inch or so. Couldn't turn any faster and all of a sudden my hand slipped. The handle whizzed round and the organ gathered speed on its descent. Faster and faster it came. What if? The organ was by now out of sight of the audience, and again I had to do something. Stupidly I tried to grab the spinning handle. Incredibly it stopped – it must have been a very low gear. And so I was able to wind Tom down the last few inches, while Wally'd got the news on the screen. By this time I was flaked out across the motor.

The next day the chief informed me that it was only a fuse that had failed, and that I should have checked them first. Willy Stagg was his name.

When Wally had completed the tale the blue faces on the left of the screen didn't look so blue, so with a certain amount of trepidation I told him to take it away as it would find its own level. It did.

Servicing the Philips TX Chassis

The Philips TX monochrome portable chassis has been in production for several years and large numbers have been sold in the Philips and Pye model ranges. There have been several versions, with 12 and 14in. tubes, and with/without remote control. There have also been a number of modifications – most of these are of little significance from the servicing point of view, though it's worth noting that a simplified field generator stage is used in later production.

Power Supply Circuit

As with any set, the power supply is the key to what goes on. The circuit of the TX's power supply, which consists basically of a transformer-fed mains bridge rectifier followed by a series regulator, is shown in Fig. 5. This is conventional though there are one or two points worth noting. First, one of the diodes in the bridge rectifier circuit, D110, also serves as the reverse polarity protection diode on battery operation. Switch SK2 is part of the battery input socket. This can cause problems, as we shall see. Secondly the error detector/amplifier transistor TS112 is operated from the line output stage derived 26V boost rail. This provides protection against excessive voltages in the line output stage, since excessive boost voltage will cut off TS112 and in turn TS111 and TS110.

In the event of line output stage failure, TS112, TS111 and TS110 will again be cut off. The result could be excess voltage on the 10.8V line which will also be unstabilised, i.e. fed via R110 only. This would damage the tube, whose heater is connected across the 10.8V rail. To avoid this situation, diodes D115 and D116 conduct when the line output stage is not working, thus reducing the voltage on the 10.8V line. These diodes were not fitted in early production sets.

The fourth transistor TS113 provides the tuner with a

John Coombes

stabilized 11.3V supply. The tuning voltage is stabilized by a TAA550 in the usual way.

Line Timebase

The line generator circuit (Fig. 6) is rather unusual. The first transistor TS380 provides the flywheel sync action: a line-frequency sawtooth is applied to its emitter while the line sync pulses are applied to its base. Following the flywheel sync filter, TS392 sets the voltage conditions in the line hold control network. The oscillator itself consists of TS390 and TS391 which are connected in an emitter-coupled astable multivibrator configuration.

The driver and output stages (Fig. 7) follow normal practice. D450 is the efficiency diode, D451 the boost diode, C451 the boost reservoir capacitor and C450 the flyback tuning capacitor. The output stage provides 9.5kV e.h.t. for the tube, a 350V supply for the tube's first anode, a 95V supply for the video output stage and the tuning system, and the 26V boost line.

No Sound or Raster

If there's no sound or raster, check the voltage at the emitter of TS110. If there's no voltage here, check the fuses – VL100 (on the mains transformer), VL110 and VL111. If VL100 or VL110 is open-circuit, check the bridge rectifier diodes D110/111/113/114 and the protection capacitors C116-9 for shorts and if necessary the mains transformer T110 for shorted turns. If VL111 is open-circuit, the l.t. reservoir capacitor C112 could be leaky. Alternatively there could be a short-circuit in the line or sound output stage. Check the output transistor TS450, then D450, C450 and the scan coupling capacitor C455 in the line output stage. Check the smoothing

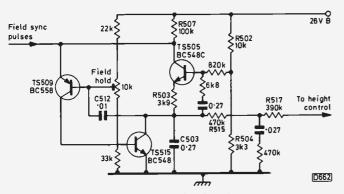


Fig. 1: Early field generator circuit with constant-current transistor TS505.

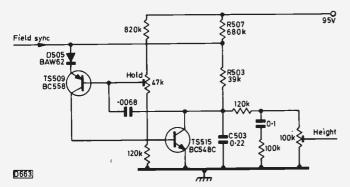


Fig. 2: Later field generator circuit.

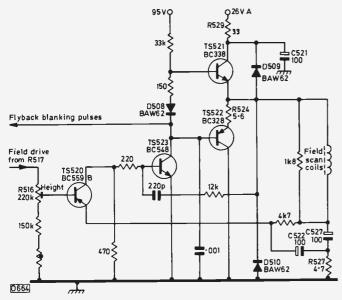


Fig. 3: Field driver and output stage circuit.

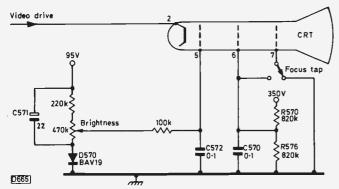


Fig. 4: C.R.T. biasing arrangements. D570/C571 provide switch-off spot suppression.

capacitor C314 (47 μ F) and the output coupling capacitor C311 (100 μ F) in the audio output stage.

If the fuses are o.k., check the voltage at the collector of TS110. If this is low at 2-8V, check TS110, TS111 and TS112 as necessary. If the voltage at the collector of TS110 is more than 8V, check the boost voltage - at pin 6 of the line output transformer. If the voltage here is less than 15V, check the line output transistor, check whether C455 is leaky, then check the line output transformer by substitution. If the voltage at pin 6 is in excess of 15V, check whether R451 is open-circuit, thus removing the supply to the line oscillator. In the event of R451 being open-circuit, check for shorts in the field generator circuit. If R451 is o.k., check the voltage at the base of the line driver transistor TS410. The reading should be about -0.1V. If this is present, check TS410 and TS450. If the reading is absent, check whether R401 is open-circuit, thus removing the supply to the line oscillator stage. Finally check TS390, TS391 and TS410 by replacement.

Normal Sound, No Raster

For the sound normal, no raster condition, first check whether the tube's heater is alight. If not, check the continuity of the heater winding. Next remove the aerial plug. If there's insufficient brightness, check the a.g.c. amplifier transistor TS351 (BC548) by replacement. If there's still no brightness, turn the contrast to minimum, the brightness to maximum, and make voltage checks at the c.r.t. base. The cathode voltage (pin 2) should be 67V. If this is incorrect, check the video output transistor TS560 (BF422) and if necessary the field flyback blanking transistor TS565 (BC548C). If the voltage at pin 2 is correct, check the grid voltage (pin 5) which should be about 57V. If this voltage is missing, check whether the grid decoupling capacitor C572 (0.1μ F) is short-circuit, then check whether the 95V supply is being developed across C452. If not, check R450 and D453 for being open-circuit. Next check the first anode voltage (pin 6) which should be 160V. If not, check R570 ($820k\Omega$), R452 and D455. Finally check the e.h.t. circuit if necessary from pin 8 of the line output transformer through the rectifier to the final anode of the c.r.t.

Normal Sound, Weak or No Picture

In the event of normal sound with a weak picture or no picture, check the voltage at the emitter of the video output transistor TS560. This should be 3.3V. If incorrect, check TS560; if correct, check the video driver transistor TS350 (BC558).

Field Collapse

In the event of field collapse, check whether the field output stage feed resistor R529 (33 Ω) is open-circuit. If so replace it and check the output transistors TS521/2 (BC338/BC328). Next check the field output stage midpoint voltage – 10·1V at the emitter of TS521. If this is incorrect, check the output transistors, the field driver transistor TS523 (BC548) and the preamplifier transistor TS520 (BC559B). If necessary check the scan coupling capacitor C527 (100 μ F) and the earth return resistor R527 (4·7 Ω), then suspect the field generator circuit. Check the transistors TS505/TS509/TS515 and the values of resistors R515 (470k Ω), R517 (390k Ω) and R516 (height control – 220k Ω).

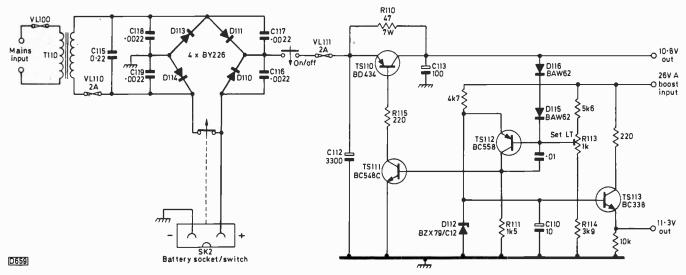


Fig. 5: Power supply circuit. In some sets TS110 is a BD202, with R115 150 Ω , R110 22 Ω and R111 5.6k Ω

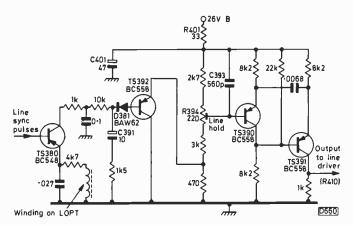


Fig. 6: Line generator circuit.

The original field generator circuit is shown in Fig. 1. The charging capacitor C503 charges from the 26V rail via R503, R507 and the constant-current transistor TS505. When the ramp at the emitter of TS505 reaches the voltage at its base, set by R502/4, TS505 switches off. The positive-going voltage at its collector then switches TS509 on, and in turn TS515 to discharge C503. The later simplified circuit is shown in Fig. 2. This time C503 charges from the 95V line via R503 and R507. When the voltage at the junction of R503/7 exceeds the voltage at the base of TS509, both transistors switch on as before. In normal operation the positive-going field sync pulses fed to the emitter of TS509 drive this transistor on just ahead of the free-running switch-on-point.

Loss of Line Sync

In the event of loss of line sync, first remove the aerial input and check that the l.t. line is correctly set for 10.8V. If the correct voltage cannot be obtained by adjusting R113, check TS110, TS111, TS112 and make sure that R114 is $3.9 k\Omega$ (in some sets it's $4.7 k\Omega$). If the supplies are correct, check the voltage at the positive side of the a.g.c. smoothing capacitor C351 (47μ F). With the aerial disconnected the reading should be 4.3V. With the aerial connected a reading of 6-8V should be obtained. If the voltage conditions are incorrect, suspect the a.g.c. amplifier transistor TS351 (BC548).

If necessary, try adjusting the line hold control R394 TELEVISION AUGUST 1983

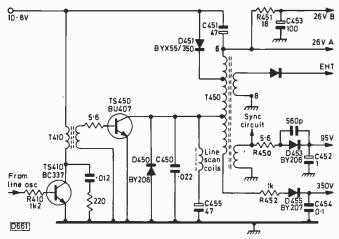


Fig. 7: Line driver and output stages. In 14in. sets C455 is C465, $3 \cdot 3 \mu F$.

with the emitter of the flywheel sync transistor TS380 shorted to chassis and the aerial connected. If line lock cannot be obtained, replace the line oscillator transistors TS390 and TS391. If line lock can be obtained but the sync floats on removing the shorting link, suspect TS380 and TS392.

Miscellaneous Faults and Modifications

Sound buzz with unstable picture, possibly intermittent: Suspect the battery socket – the switch can become tarnished. Replacement cures.

Uncontrollable sound: Suspect the d.c. volume control R302 ($4.7k\Omega$) or the TBA120AS intercarrier sound chip (IC310).

Intermittent line collapse, with vertical line: Change C393 to 0.0015μ F. Philips advise that the value of C393 in all sets bearing factory code HU on the chassis or serial plate is checked and changed to 0.0015μ F if necessary.

Bright vertical line at left-hand side: If a replacement line output transformer does not cure this, change C412 to 0.0068μ F and TS410 to a BC637 (note that the base connections differ).

Distortion at low volume: Change R300 to $18k\Omega$, R311 to 56Ω , R312 to $3.3k\Omega$ and R315 to $120k\Omega$.

Brightness range: Where the tube is type 12VCUP4, R576 should be $470k\Omega$. Where the tube is type 12BJP4 it should be $820k\Omega$.

Vintage TV: The Pilot Model VS9

Chas E. Miller

Now just a forgotten name recalled only when one browses through old service sheets, Pilot was at one time a leading radio manufacturer. They were perhaps best known for their series of "Little Maestro" receivers, small mains table sets which obviously derived from US "midget" models though they were considerably more refined. The firm also produced some of the first portable sets able to work on a.c./d.c. mains supplies or self-contained batteries. This was the "Twin Miracle" range, introduced just prior to World War 2.

At that time Pilot catered for the upper section of the market with some large table models of frankly American appearance (and very similar to some contemporary Ferguson sets). They featured high-quality push-pull output stages. After the war came some more fine sets, such as Model BS648 which had seven wavebands, an r.f. amplifier and bandspread tuning on the short waves. With this sort of pedigree, it was predictable that Pilot's first TV receiver would be of individual design, using mainly American type valves.

The Pilot VS9 was a 9in. console model for use in the London area only, having a t.r.f. receiver unit. It was for a.c. mains operation only, and was built on three separate chassis, i.e. vision and sound, timebases plus audio output, and h.t. plus e.h.t. power supplies. These chassis were interconnected by means of colour-coded octal plugs and sockets, making dismantling easy.

The TRF Stages

On the r.f. side, there was one common stage followed by three vision only and two sound only stages. These all used 8D3 valves, which were miniature r.f. pentodes similar to the Mullard EF91 and with the miniature allglass B7G base. The contrast was controlled by varying the screen grid voltage applied to the common vision/ sound stage and the first vision only stage, a curious method since contrast adjustment would alter the sound level as well.

The vision strip was aligned to the upper sideband. The

significance of this was the fact that the Alexandra Palace transmitter used double-sideband transmission. It continued in operation until March 1956, when Crystal Palace came on air. Crystal Palace used vestigial sideband transmission, in common with the other transmitters, and the vestige was the upper sideband. So the Pilot VS9 and other sets that were similarly tuned had to be realigned for Crystal Palace reception.

Video Circuit

The video department was quite elaborate (see Fig. 1). For vision demodulation one half of a 6AL5 double diode was used – the other section was not used. Another 8D3 was employed as the video amplifier, and this was followed by a further 6AL5, one section of which provided d.c. restoration while the second section acted as an interference limiter. The following valve acted as a cathode-follower for the video output, which was used to modulate the c.r.t.'s grid. The feed to the sync separator was taken from its anode. The valve chosen for this job was the 6SH7, an r.f. pentode that had been used in vast quantities during the war in American radar equipment. Here however it was strapped as a triode.

This valve and most of the rest had the octal base of blessed memory. Since the last valves featuring this base – line output types such as the PL36 – disappeared from UK TV sets some twenty years ago, few young engineers will have had the pleasure of their company. There were eight strong pins spaced equally around a central spigot which had a key to ensure correct insertion into the holder – even at arm's length in a darkened room! Anyone who has struggled to fit a PFL200 and bent the pins umpteen times would appreciate the octal base no end!

Timebases

A 6J7 was used as the sync separator. This type of valve was usually associated with tasks such as grid-leak detection in cheap t.r.f. midget radios! The line sync pulses were

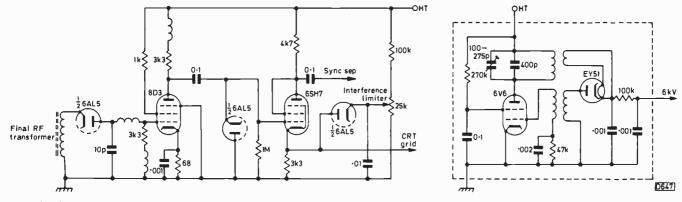


Fig. 1 (left): The video circuitry used in the Pilot Model VS9. The video drive was applied to the c.r.t.'s grid, the brightness control setting the cathode voltage. The interference limiter is a simple peak clipper circuit. Fig. 2 (right): The e.h.t. generator circuit, consisting of an r.f. oscillator and rectifier. The resonant circuit employed air-cored coils and was tuned for maximum power output. Screening was required to avoid interference.

taken directly from the anode of this valve, but the field sync pulses were passed to an 8D3 that acted as a pulse clipper. The anode of this valve was tied to that of the 6J5 triode field blocking oscillator. For field output a 6V6 was used, in a rather unusual manner. It was not uncommon in the early days for the output valve to be *RC* coupled to high-impedance scan coils, but Pilot went a stage further – with *RC* coupling to a conventional transformer that drove low-impedance scan coils. The declared intention of this arrangement was to prevent d.c. passing through the transformer, but to what end was not stated. Height control was effected by varying the 6V6's cathode voltage by means of a 1k Ω variable resistor.

A similar arrangement was used for width control in the line output stage. Another similarity was the use of a 6J5 line blocking oscillator. How oddly simple these early timebases look to modern eyes! The line output stage had only a plain two-winding transformer, with no boost line or flyback e.h.t. system. Linearity was controlled by means of a series connected RC network across the transformer's secondary winding. The output valve was an 807, another veteran of war and peace in its more familiar role as a transmitter power amplifier. It was capable of giving 50W of r.f., whilst a pair could easily provide 120W of audio. It should have had little trouble in scanning a 9in. c.r.t. with a modest 55° deflection angle.

Audio Circuit

A third 6AL5 was used as the audio detector and interference limiter. This was followed by a 6J5, here fulfilling its intended role as an audio amplifier. The audio output valve was an EL33, and it's a minor mystery why Pilot should have chosen a continental type valve for this purpose rather than the to be expected US type such as a 6V6.

Power Supplies

There was a second 6V6 in the set however. It was employed as an r.f. oscillator in the e.h.t. generator section (see Fig. 2). The voltage developed across the transformer's overwinding was rectified by an EY51 to provide approximately 6kV for the tube's final anode.

The h.t. supply came from a power pack of almost unbelievable complexity. Two 5V4G rectifiers were used in a full-wave circuit to provide 410V which was then dropped to around 290V by a smoothing network comprising no fewer than four iron-cored chokes, the c.r.t.'s focus coil, and nine electrolytic capacitors. This was a true a.c.-only design, with a double-wound mains transformer. Thus the chassis was "dead" irrespective of how the mains plug was inserted (we've come a long way, haven't we!). Despite its monstrosity, this power pack needed only a 2A mains fuse, demonstrating its modest appetite for current and inherent resistance to surges.

Later Models

Pilot went on to build further interesting radio and TV sets during the 50s, but by the end of the decade the firm had been taken over by Ultra Electric Ltd. Ultra sets appeared thinly veiled as Pilots for a while, in the all too familiar manner of the early 60s badge engineering explosion, but before long Ultra shed their domestic electronics interests and in the process yet another two marques were added to the ranks of Thorn products. T'was so often thus!

TELEVISION AUGUST 1983

next month in

TELEVISION

• SERVICING THE DECCA 70/90 CHASSIS The Decca 70 chassis and its derivatives were introduced in 1979. Although they've proved to be very reliable, those who've dealt with them in large numbers will notice various fault patterns. Neil Dobson has had extensive experience of these sets and describes the fault conditions he's encountered.

4GHz LNA

A low-noise head amplifier is essential for satellite TV reception at 4GHz. Hugh Cocks described a simple 4GHz converter recently and there've been requests for an LNA to go with it. The price of gallium arsenide f.e.t.s is now such that it's feasible to build a DIY LNA. The design presented by Hugh Cocks features a gain of 43dB with a noise figure of less than 2dB.

• THE ULTIMATE PATTERN GENERATOR? The Grundig VG1000 provides a wide range of patterns and test signals, with facilities such as variable video output. Steve Beeching has been using one for some time and finds it ideal for VCR work and almost too good for TV receivers! With VCRs becoming more sophisticated, more accurate alignment is essential for optimum performance. Those seeking to operate an effective VCR workshop will need equipment of this standard.

COMMON FAULTS KNOW-HOW

Do you or don't you know how to deal quickly with the most common TV fault conditions? S. Simon presents a simple question and answer guide that tests your knowledge and provides practical hints on effective test procedures.

THE AYR TELETEXT ADAPTOR

Owners of non-teletext sets can fit an adaptor to receive the teletext services. Adaptors have come down in price and with the latest models installations are less critical. Vivian Capel reports on the Ayr adaptor, which costs less than some kits.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

ΤΟ

(Name of Newsagent)

Please reserve/deliver the September issue of TELEVISION (90p), on sale August 17th, and continue every month until further notice.

TV Fault Finding

Some symptoms can be caused by several defects rather than a single faulty component – this is particularly so in cases of low gain, poor definition or poor field linearity. A rather rare complaint came our way recently when the owner of an old Hitachi colour set (Model CSP680) phoned to say that the "red colouring was all grainy". Inspection showed that all the colouring was in fact grainy, and that there was still too much noise on the picture when the colour was removed by turning the control to minimum.

The first step was to check the aerial input connections – about the only weakness of these older Hitachi colour sets is a tendency for the outer ring of the coaxial socket to break away from the base, leaving the aerial's braid connection "floating". The plug and socket were both o.k. in this case, but we found that the short aerial input lead came from a splitter. It transpired that the owner was using a single downlead from his TV and f.m. radio loft aerials, with another splitter in the loft. The cable itself was of the 405-line variety, and followed a circuitous route inside the house: the trouble was further compounded by the fact that after heavy rain the roof and nearby trees acted as signal screens.

Running the set directly from the loft aerial instead of via the splitters produced a big improvement, but there was still a bit of grain noticeable in highly coloured areas of the picture. There's an a.g.c. preset (R267) on the signals panel in these Hitachi sets, and on adjusting this virtually all picture noise disappeared. **G.R.W.**

Fidelity CTV14R

The symptoms were very unusual – noise on the screen and hiss from the speaker when tuning between channels, both ceasing at the optimum tuning point though the picture and sound failed to appear. The culprit was the TDA440 i.f. chip. **G.R.W.**

Sanyo 80P Chassis

This colour portable (Model CTP3106) uses a self-oscillating chopper circuit with the chopper transformer T301 providing mains isolation. In the event of no results, first check whether the 110V line is present. If not, check the mains fuse F1001 (2A). If this is open-circuit, check for shorts in the mains filter capacitor C1001 (0.1μ F), the chopper supply rectifier D301 (ERC04-10) and its reservoir capacitor C308 (100 μ F).

If the mains fuse is o.k., check the chopper supply fuse F301 (0.8A). If this is open-circuit, check the chopper transistor Q304 (2SD841 or 2SC3047) and C315 (1,500pF) in the snubber network across the chopper transistor Q301 (2SC536) and the drivers Q302 (2SB774) and Q303 (2SC536) for being open-circuit; diodes D305 (EQA01-08RG zener) and D307 (1S2095A) for being open-circuit instead); the chopper coupling capacitor C314 (47 μ F) for being short- or open-circuit; and the 110V rectifier D320 (UF3N) for being short-circuit. If necessary check the

chopper transformer T301 which could have short-circuit turns.

If the chopper supply fuse F301 is o.k., check the voltage across the chopper supply reservoir capacitor C308. If absent, check whether any of the following items is open-circuit: filter choke L1001, the on/off switch SW1001, the surge limiter resistor R301 (6.8Ω) and filter choke L302.

If there is 300V across C308, check the waveform at the collector of the chopper transistor Q304. If this is present and correct (520V peak-to-peak), check whether Q303 or D306 (ERB28-04) is short-circuit or D320 open-circuit (no 110V line). Then check C460 (33μ F h.t. decoupler) and C461 (1.5μ F scar coil coupling) in the line output stage for being short-circuit. Alternatively the chopper transformer T301 could be open-circuit.

If there's no waveform at the collector of Q304, check the voltage between its collector and emitter. If there is no voltage, check R318 (0.33Ω) and R313 (2.7Ω) in its emitter circuit. Either could be open-circuit, as could T301. If the voltage is 300V or more, Q304 or its base bias resistor R302 (390k Ω) could be open-circuit, as could either R314 (27 Ω) or C313 (0.1μ F), hence no chopper drive. If not, suspect the chopper transformer T301 for open or shorted turns. J.C.

Rank T26A Chassis

Loss of sound and raster, maybe intermittently, should lead to a check on the BU208A line output transistor and if necessary diode 5D12 (BY228) which can go open- or short-circuit. J.C.

Decca 70 Series Chassis

Set tripping with no fuses blown presents something of a problem. The usual cause is that C633 (680pF) is shortcircuit. This capacitor is part of a snubber network across one of the chopper transformer's secondary windings. J.C.

Grundig CUC95 Chassis

Failure of the chopper transistor TR634 (BU208A) at switch on was traced to R646 (270k Ω) in the start-up circuit going high in value. T.L.B.

Fidelity CTV14R

The problem of striations over the screen was traced to the 180V video h.t. line reservoir capacitor C903 $(4.7\mu F)$ being open-circuit. T.L.B.

ITT CVC40 Chassis

This solid-state receiver gave the symptoms of a set with lazy timebase valves! Both the width and height were initially insufficient, resulting in approximately twenty per cent underscan. Over a period of some ten minutes the picture gradually expanded to fill the screen. Checks made during this time revealed that the regulated 127V rail was low to start with, at about 108V, slowly rising to the correct level some minutes later.

The effect was found to be insensitive to temperature variations, and the cause was eventually traced to the

Reports from George R. Wilding, John Coombes, T. L. Bingham, Peter H. Dolman and Mick Dutton

chopper output smoothing capacitor C11 (22μ F, 375V). At switch on its capacitance was low, resulting in a line frequency ripple variation on the 127V rail. Only the most positive excursions were being sensed by the control circuit, so the average rail potential remained low. After some minutes the capacitor reformed, as a result of which the 127V rail's level and ripple content became normal. **P.H.D.**

Mitsubishi Colour Portable

A Mitsubishi colour portable had given excellent service for about seven years, until the owner had stored it for a while. When he came to use it again there was no raster. When we switched on there was a healthy e.h.t. rustle and we could see that the tube heaters were alight. The sound was normal, so we started to make checks on the tube base voltages. The first anode voltages were low.

When we tried to advance the settings of the red and blue controls the voltages dropped. With these controls



Part 20

Mike Phelan

This month we'll look at the signals section of the 3V23. This consists of the pre-rec board, the YC board and the audio board. With the exception of the latter, the circuitry is much simpler than that used in the machines we've described previously, due mainly to the elimination of many discrete components through the use of larger scale integration. The audio board is quite complicated, because we now have Dolby noise reduction and frequency shift on double-speed playback, but more on this later.

The pre-rec board (see Fig. 89) is very straightforward and simpler than in previous models in the JVC/Ferguson range. Improvements on the YC board and the inclusion off, there was a faint green picture. The tube base is of the enclosed type, similar to that used in the Rank Z718 chassis, and had developed leakage between the metal earth ring and both the red and blue first anode pins. The leakage could be measured on an Avo, with the tube base removed. Stripping the base down and cleaning it resolved the problem. M.D.

Hitachi NP6C Chassis

The problem with an Hitachi CWP132 colour portable (NP6C chassis) was that the power supply would intermittently fail to start – the switch-mode transformer in the power supply would also make some most peculiar screeching noises. We removed the main panel from the set and checked around the power supply for poor joints. There were some very bad connections to module CP901, which provides the reference voltage and h.t. sensing, and when these were resoldered the problems were completely cured. M.D.

of f.m. a.g.c. have enabled the playback f.m. level and balance controls to be eliminated. The drop-out compensation circuit is now on this board. The circuit doesn't warrant much description, as it's simpler than the one already discussed. Transistors X6 and X7 are incorporated to mute the input while the machine is in the "record start" mode, i.e. ten seconds before the start of a timed recording, to allow the tape to lace up. When the exact record time arrives the record start 12V line from the mechacon panel goes to zero – by this time the servos are locked, so the recording starts without a lot of noise on the picture.

Luminance Record Path

The YC board is mounted above the tape deck on a hinge, so that it's screened by the metal cabinet. There are six main i.c.s and several smaller devices. We'll look at the luminance record path first (see Fig. 90). The input is

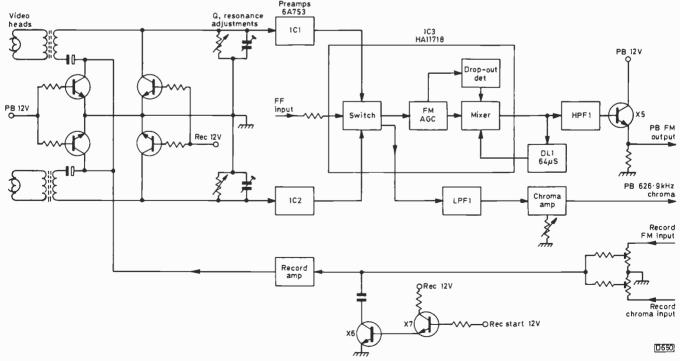


Fig. 89: Block diagram of the pre-rec board.

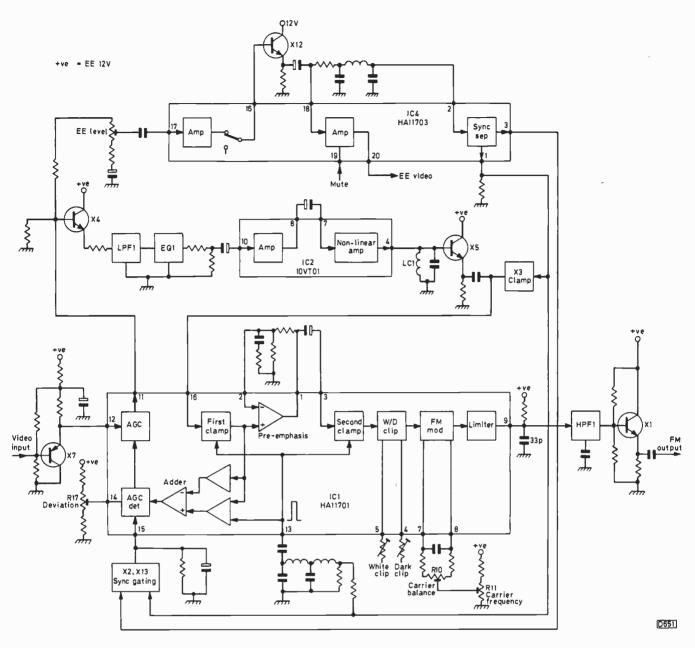


Fig. 90: The luminance signal path (YC board) on record.

applied to the base of X7 and then passes to the gaincontrolled amplifier in IC1. This stage sets the signal at a level controlled by the deviation preset R17, which determines the highest frequency obtained from the f.m. modulator on peak whites. A delayed sync pulse, coincident with the signal's back porch, enters the i.c. at pin 13: this, together with the video signal, goes to an adder – we'll return to this bit later. The a.g.c. time-constant components hang on pin 15. X2 and X13 provide sync gating for the a.g.c.

The luminance output at pin 11 is split two ways. The E-E signal goes to pin 17 of IC4 for amplification, then via the emitter-follower X12 to the mute circuit between pins 18 and 20. The mute action is operated by a voltage from the junction board when the test signal is selected. IC4 also contains a sync separator which provides clamping/gating pulses.

The record signal proper passes via X4 to low-pass filter 1 (LPF1), which provides a roll-off at 3.5MHz to remove the chroma. Equaliser EQ1 compensates for the loss of h.f. caused by this. The following non-linear amplifier in IC2, together with the tuned circuit LC1 and X5, act as a

compressor so that low-amplitude signals are boosted. We'll see why this is necessary shortly. X3 clamps the signal at the sync level, the following first clamp in ICI clamping the back porch (black level). Thus the black level of the signal at this point is fixed, though the sync pulse amplitude is variable.

We can now see how the a.g.c. detector works, and why the clamp pulses to it are delayed. The video signal goes to both inputs of the adder (it's a subtractor actually), but one signal has a pulse on its back porch. The video signal cancells out, leaving a pulse whose amplitude is determined by the difference between the sync and black levels.

Pre-emphasis comes next: because of the compression previously applied, the net effect is of greater preemphasis with low-level signals. This improves the signalto-noise ratio. The signal is then clamped again before passing through dark and white clip circuits which remove the pre-emphasis spikes. Next comes the f.m. modulator, which in this machine is integrated: though an i.c. is now used, the circuit configuration is similar to that in the 3V00. Pins 7 and 8 are connected to the emitters of the two oscillator transistors, so that R11 sets the frequency

TELEVISION AUGUST 1983

534

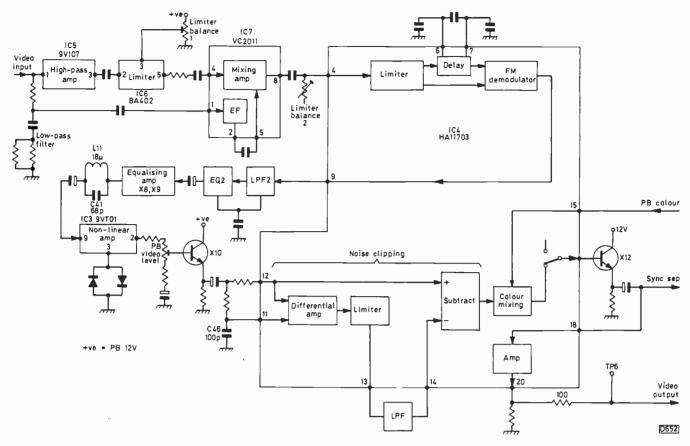


Fig. 91: The luminance signal path (YC board) on playback.

and R10 the mark-space ratio (for 50:50). The limited f.m. signal emerges at pin 9 and then passes via HPF1, which provides a roll-off below about 1MHz, and X1 to the pre-rec board, where it's mixed with the 626.9kHz chroma.

Luminance Playback Path

On playback (see Fig. 91) the f.m. from X5 on the prerec board goes first to pin 1 of the high-pass amplifier IC5. The lower frequencies are separated and go to pin 1 of IC7 while the higher frequencies are limited by IC6 and then go to pin 4 of IC7, which mixes the limited h.f. and unlimited l.f. components of the signal. The resulting output passes to another limiter in IC4. This double limiting idea was used in the 3V00, the purpose being to prevent loss of the l.f. components. The f.m. demodulator in IC4 works on the pulse width, but unlike the one in the 3V00 uses a pi-network of capacitors connected to pins 6 and 7 instead of a delay line.

LPF2 and EQ2 remove remnants of the f.m. carrier while the equalizing amplifier X8/9 artificially enhances the signal's h.f. response. The non-linear amplifier in IC3 compensates for the signal compression on record by giving a corresponding expansion. C41/L11 provide the main de-emphasis, but a small amount of this occurs in the equalising stages X8/9.

After X10 the signal is split into two paths which go to the two inputs of the differential amplifer in IC4. C46 removes the h.f. component of the signal applied to pin 11. Thus the output from the differential amplifier contains only the h.f. signal component, including noise. The noise is of generally greater amplitude than the signal and is removed by the limiter. The network between pins 13 and 14 removes all but the highest frequencies: these, mainly noise, are then subtracted from the original input at pin 12.

Finally the colour is added, entering via pin 15, and after further amplification the composite video signal is ready to go to the junction board on its way to the r.f. modulator.

Chroma Circuits

The chroma signal circuit (see Figs. 92 and 93) does not require detailed description since it works in precisely the same way as that in the 3V00 (see Parts 5 and 6). Most of

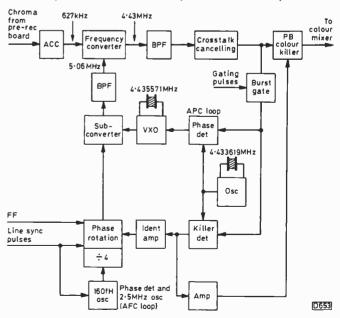


Fig. 92: Block diagram of the playback colour system.

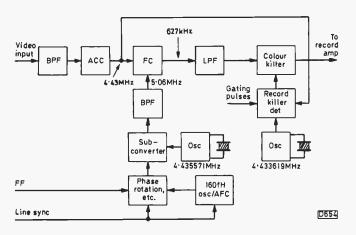


Fig. 93: Block diagram of the record colour system.

the important bits are in four i.c.s, IC201 (HA11710), IC202 (HA11717), IC203 and IC206 (both HA11706).

The Audio Panel

The audio circuit contains several interesting features. First, there's provision for Dolby noise reduction. This can be switched off at the front panel. There is also a system to record a cue signal on the tape for one second at the beginning of every new recording. Finally there's a feature which is probably unique – on double-speed playback the sound is halved in frequency to make it more intelligible.

The basic audio circuit centres around an HA12005 i.c. which carries out the same functions as the AN262 in the 3V00. There is auto level control and muting (for still, slow and fast search).

The double-speed frequency shifting circuit brings us to a bucket-brigade device or BBD (see Fig. 94). The MN3010 contains two 512-stage BBDs. These can be considered as a sort of shift register or delay line which can handle an analogue (e.g. audio) signal. Two clock signals, in opposite phase to each other, are required. Each clock pulse transfers the signal along from one stage to the next, so that it arrives at the output 513 clock pulses later. A glance at Fig. 94 shows how this happens.

When inverted Q is low, non-inverted Q is high. Thus T1, T3 etc. conduct. C1 is charged by the signal. When the clock pulses change polarity, T2 etc. conduct. The charge on C1 is thus transferred to C2 and so on. The signal is in this way stepped through all 512 stages, giving us a sort of delay line. We can do one thing with it we cannot do with a delay line however – we can alter the delay time by changing the clock frequency.

Say we run the clock for 512 cycles with a signal input, thus filling up the BBD. If we then halve the clock frequency for the next 512 cycles, the signal will emerge at half frequency, i.e. shifted down one octave, which is exactly what we want for double-speed playback. While this is happening however the signal is being clocked in at half speed, which is of no use to us. So we need two BBDs to run alternately (see Fig. 95). The MN3010 contains the required BBDs. For 512 clock cycles S1, S4 and S6 are closed so that the signal enters BBD1 at normal speed (clock Q1) but is read out of BBD2 at half speed (clock Q2). As S5 is open, the signal coming out of BBD1 at normal speed is not used. After 512 cycles the Q11 output changes state, S2, S3 and S5 close, and the signal comes out of BBD1 at half speed. And so on.

The two balance potentiometers are adjusted to null out any residual clock frequency signal and the low-pass filter

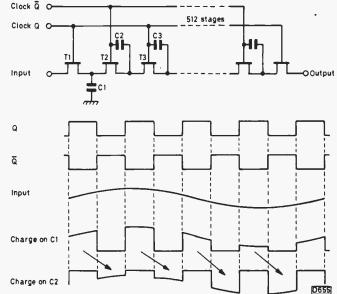


Fig. 94: Operation of the BBD sound frequency halving system for double-speed playback operation. The output is the same as the input, though delayed, after filtering to remove the switching waveform component.

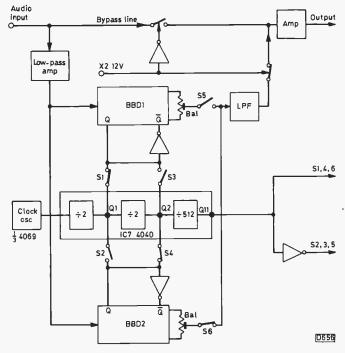


Fig. 95: Block diagram of the BBD frequency halving system.

converts the squarewave back into an analogue signal. During normal playback the bypass path is closed. All the switches are 4066 quad bilateral switch i.c.s.

Finally the cue facility (see Fig. 96). For one second at the start of each recording the cue set line from the mechacon panel goes low, starting the oscillator by turning on X20 and also energising the relay so that the 30Hz output is fed to the full erase head and recorded on the tape. After one second the cue set line goes high, X20 turns off and the erase head is reconnected to the bias oscillator. This happens on every recording regardless of the setting of the cue switch.

On playback the 30Hz signal has no effect, but on rewind or fast forward the cue head is still in contact with the tape although the latter is not laced up. Due to the tape speed, the cue signal is replayed at something like 400Hz. X48 and the first half of IC40 amplify it, while

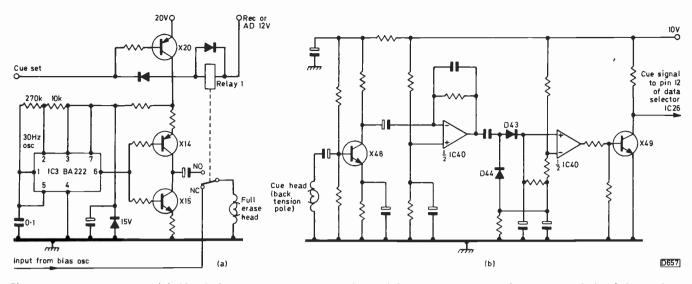


Fig. 96: The cue system. (a) Circuit for recording the cue signal. (b) Cue playback circuit. The record circuit is on the audio board, the playback circuit on the mechacon panel.

D43 and D44 form a diode pump which takes the noninverting input of the second operational amplifier high after a few cycles. The base of X49 thus goes high, while its collector voltage falls from 10V to zero, i.e. logic zero. This is conveyed to the microcomputer via one of the four data selectors in IC26.

That's all for now. Next time we'll look at the tuner/ timer board (another two microcomputer i.c.s!).

A Matter of Safety

It's hoped that as responsible engineers most of you give every consideration to the safety of TV viewers by checking, as a matter of course, the sets you are servicing. Likewise when replacing components you probably fit correctly rated and type fuses, capacitors, resistors and so on, and follow makers' instructions regarding safety components. And so you should. But on the personal level there's an unfortunate tendency to plough on regardless of what could happen, even though it's inevitable that our work, involving as it does journeys to customers' homes where we deal on a daily basis with an invisible, instant and potentially lethal source of power, places us all at some risk some of the time. It's a classic case of familiarity breeding contempt!

In this article I've endeavoured to identify the main danger areas and make suggestions on how to minimize accidents or rather the likelihood of them happening. It's possible that you may be unable to recall when you last felt the effects of a sharp stab of electricity. If so you might be forgiven for thinking that these comments don't apply to you. But think of this. Accidents are not all electrical, while there's always a first time for a severe shock. You never know when, you're never expecting it, and the first shock could be the last.

Test Equipment

We all have pet ideas on safe practice. Some time ago I was taken to task by a reader for stating that test equipment should not be earthed. Now this was a simplification and requires qualification. It's my opinion that any piece of workshop test equipment that might conceivably be used at any time for field servicing should have its earthing disconnected. This is all the more important with

Tony Thompson

metal-cased items such as mains-powered soldering irons, signal generators, oscilloscopes and such like. The fact that scopes are likely to have earthed-screen probes makes them especially hazardous in use.

The workshop itself should of course be equipped with an adequately rated isolation transformer for each bench, though I'm sure that many of us will be aware of workshops that are not so equipped. It goes without saying that both the sets being serviced and the equipment used to service them should be powered from an isolated mains supply. It's an unfortunate fact however that few isolating transformers could be considered even remotely suitable for the hard-pressed field service engineer to lug around on his calls. Every outside call exposes the service engineer to the danger of raw mains.

Most TV sets have a live chassis, i.e. the metalwork, screening cans and structural members are used as a convenient return to one side of the mains, intended to be the neutral side, isolated by the receiver's on-off switch. Unfortunately the connections to the mains plug or socket can be incorrectly polarised, as a result of which the metalwork becomes truly live. It should also be remembered that the neutral lead could be open-circuit, due to a faulty switch for example. The chassis will again be at full mains potential. For reasons of impedance, the danger of a fatal shock from this latter state of affairs is slight, though some receivers have a very low input impedance, so low that a possibly dangerous current could under certain circumstances flow.

More directly dangerous under such fault conditions is the use of earthed servicing equipment. One hand on the earthed casing, another on the exposed, live metalwork, and you've got the right conditions for experiencing something rather nasty.

Most sets produced in recent years incorporate a bridge rectifier in the mains input circuit, as a result of which the chassis is always at half mains potential. Care is needed but shocks due to this are likely to be slight unless earthed test equipment is used. With such chassis however another hazard is with us. Get your earthed iron or scope lead in contact with the metalwork and you'll blow a fuse. Accidentally touch other more sensitive areas and away will go that expensive output transistor or hard to replace thyristor etc. The use of an unearthed soldering iron on half-mains potential chassis is not to be recommended either, due to the possibility of leakage within the insulation system of the iron presenting the chassis with an opposed polarity, again blowing fuses or offering a shock hazard. The answer here is to use a low-voltage, transformer-fed tool: one of the quick-heat variety gun-style irons might be your preference, or a "soldering station" type with its transformer within an insulated casing that doubles as an iron rest. It's a good idea that iron rest: we've all burnt customers' carpets, and ourselves, by balancing the hot iron on the edge of the toolbox!

Basic Precautions

In case you're not aware of the fact, it can take only a few milliamperes across the heart muscles to make you feel very sick, sometimes for several days. If you're really unlucky, such an apparently innocuous current when delivered at high potential can be terminal, especially if informed help is not at hand to provide resuscitation.

It's essential to take precautions against all elements of chance or luck. First, periodic checks should be made on test equipment. Inspect the condition of mains leads and the tightness and correct wiring of plugs and connectors. This task should be carried out as routine, preferably by a senior engineer specifically charged with this duty and allowed time to carry it out effectively. This is likely to be wishful thinking for many of us of course: so it's up to you, the front line man, to protect yourself and carry out such checks.

A point here about the correct wiring of plugs. No, not polarity: surely that's obvious? What's not so obvious, at least it wasn't to me until recently, is the following tip which I pass on as good advice. When wiring the plug, arrange things so that the live connecting wire is the shortest within the plug body. That way if the wire gets wrenched free of the clamp the connection to break first will be the live one. The other connection(s) should have a little slack left. Simple, isn't it?

You should go about your day-to-day business wearing a wet suit and thick rubber gloves. Though probably effective, that wouldn't be very practical however. So what can we do to provide ourselves with a measure of protection without inconveniencing ourselves unduly? First, the outside engineer should wear insulating footwear, with plastic or rubber soles. As most shoes are made like this nowadays, this shouldn't be much of a problem. Leather soles are not too good for insulation, especially when wet.

Secondly, put only one hand at a time inside a set – unless it's essential to use two, say when adjusting the convergence. This way you'll minimise the risk of forming a circuit with your arms as conductors. Your free hand should be well away from the chassis metalwork, or any other metalwork for that matter. If you must, keep your free hand behind your back or in your pocket.

It's not a good idea to wear loose neck or wrist chains

that can dangle down into an open chassis just when you've got your mind on some difficult bit of fault diagnosis. If you do, you may find the missing voltage without recourse to your meter!

Whenever possible stand on a carpet, never a stone floor. If you are in doubt, a wad of old newspapers makes a good insulator.

I've been emphasizing electrical dangers, but in practice deaths from or as a direct result of electrical shocks form a very low proportion of the range of injuries suffered in our trade. One death is too many of course, so we must be on our guard at all times. There are other dangers however. Here are a few points to help guard against these.

The Tube

First, the e.h.t. cavity should always be discharged before changing a tube. You knew that one of course. When a set is having its tube changed, it should be completely disconnected from the mains supply. Ignore these two elementary precautions, put your thumb in the e.h.t. cavity or catch your knuckles on the set's mains switch whilst carrying the tube, and the results could be most instructive. Follow recommended safety procedures when tube changing. These involve protecting the eyes against possible implosion (rare these days thank goodness), holding tubes correctly (i.e. not by the neck), plus safe storage and packing of new and used tubes that have been manufactured or rebuilt to proper standards. Many regunning firms nowadays have their products BSI certified.

Physical Injuries

Physically, the sheer weight and awkwardness of TV sets can be a problem, as letters in this magazine have pointed out in the past. Backache, slipped discs, lumbar trouble, and damage – sometimes permanent – to the arm and neck muscles, wrists and fingers, are very real hazards. It must be emphasized, especially to the young and eager, that such injuries can permanently affect one's livelihood and career prospects. It's only too obvious that to eliminate the possibility of all such injuries completely is impractical, but with thought one can limit their occurrence and minimise their extent.

Whenever possible avoid single-handed carrying of large, awkward to handle sets – say the older 26in. or consolette types of sets. Always carry sets with the tube face towards you to keep the weight close to your own centre of gravity. This places much less strain on your arms and back. It's sometimes easier to carry a set "on end": this can lead to problems with displaced shadowmasks however, so it's best to keep the set horizontal whenever you can. When picking up a set from the floor, keep you knees together and bend from the knee and not the back. This way you can avoid getting a slipped disc or being ruptured.

Radiation

Due to the e.h.t. colour sets produce X-ray radiation. For this reason screening cans around the line output stage should always be replaced, even though it's a fact that modern sets are less efficient X-ray generators than earlier types that used thermionic valves in the e.h.t. circuit. The c.r.t. itself radiates X-rays, the thick glass minimizing but not eliminating the problem. Manufacturers claim that the dose rate is so low that it's acceptable. The problem is that a fault resulting in excessive e.h.t. will produce a correspondingly higher radiation level, something that's clearly undesirable for engineer and viewer alike.

If you are in doubt as to symptoms, a good generalisation might be that a correctly sized and linear (especially linear horizontally) picture is probably an indication that the e.h.t. is at a satisfactory level. Conversely a small or horizontally narrow picture that doesn't "bloom" when the brightness level is altered, and seems pin sharp and "hard" in detail, possibly accompanied by spitting or arcing from the cavity connector or from points around the line output transformer and the c.r.t. spark gaps, tells a very different story. Experience tells here – so does an e.h.t. meter!

In Conclusion

There are acts of Parliament (Health and Safety at Work, Factories Act, Consumer Safety, etc.) that deal with some of the points I've raised, especially with working conditions. Anyone with grounds for suspecting that his or her situation is such that an unacceptable degree of discomfort or danger is present is urged to read up on these – local libraries can help.

By their very nature accidents are avoidable. Yet we all suffer them at one time or another. If you think ahead, consider the problems carefully, avoid being unduly rushed, and work defensively in the ways outlined here, you should survive any minor problems. These may then become a matter to joke about rather than a painfully permanent reminder of one's carelessness.

Letters

SONY KV1810UB

I read with interest the excellent article by David Botto in the March issue on servicing the Sony Model KV1810UB. However the waveforms shown in Fig. 3 (a) and (b) refer I think to the collector of the chopper driver transistor Q604 rather than, as stated, the collector of the predriver transistor Q605. The waveform at the collector of this latter transistor should be a ramp of about 2V peak-topeak.

Also, I find it prudent to check the start-up circuit comprising the GCS Q602 and associated components. It's not uncommon to find Q602 defective in some way. If it's short-circuit, R608 and D605 may have suffered as well. If this start-up supply is not present and the 19V rail is externally powered, a great deal of time could be spent checking other things. I trust this will be of some value to other readers.

P. Hardy, Reading, Berks.

David Botto comments: When the Sony KV1810UB is operating with a 240V a.c. mains input the waveform at the collector of Q605 will be as shown in Fig. 1 (a). If the receiver is not connected to the a.c. mains however, and tests are made — as recommended in my article — using an 18V d.c. supply connected to pin 17 of the power regulator board, negative to chassis, then a different waveform will be observed at the collector of Q605. On

TELEVISION AUGUST 1983

DILLI			LVLJ	
Specia	list valve and	l vintage s	service	
		-		
INEWV, D	OXED, GUAP	ANTEED	VALVES	
3AT2B £4.16 ECF80		£0.50 PCF800	£1.75 PL504.Mul	£3.50
6/30L2 £0.70 ECF8		£1.50 PCF801	£1.15 PL509 +	£4,80
6F23 £0.50 ECF88 10F18 £0.58 ECH8		£0.56 PCF802 + £0.54 PCF805	£0.83 PL519+ £2.00 PL508+	£4.90 £2.25
12BY7A £2.91 ECH8		£1.25 PCF806	£1.00 PL802T	£5.00
	3.Mul £2.00 GZ32	£1.60 PCF806 +	£1.20 PL802	2.3.00
21LU8 £5.00 ECH8		£1.55 PCH200	£1.40 Philips	£7.10
30FL1 £1.08 ECH8	4.Maz £1.25 KT66.UK	£8.95 PCL82 +	£0.90 PY33.Maz	£1.10
30FL2 £1.08 ECL80		£8.50 PCL83.Mul		£0.70
30FL12 £1.70 ECL82		£0.74 PCL84 +	£0,86 PY500A +	£1.55
30FL14 £3.00 ECL86 30L15 £0.60 EF80	6 £0.75 PC88 £0.56 PC92	£0.80 PCL85 + £0.85 PCL86 +	£0.90 PY800.Maz £0,89 PY801.Maz	£1.20 £1.30
30L15 £0.60 EF80 30P12 £1.00 EF85	£0.50 PC97		£0.99 U26	£0.87
30PL14 £2.25 EF86		£1.14 PD500	£2.86 U52	£4.00
40KD6 £6.85 EF86.1			£2.30 U191	£0,70
DY86/7 Maz £0.75 EF89	£0,85 PCC85	£1.00 PFL200.Maz	£1.30 UCF80	£1.15
DY802 Maz £0.71 EF183			£1.15 UCH42	£3.00
EABC80 £0.68 EF184		£0.80 PL81	£0.70 UCH81	£0.65
ECC81 £0.59 EH90	£0.90 PCC189	£0.75 PL82	£0.58 UCL82	£1.50
ECC82 £0.90 EL40	£3.00 PCC189.Mul	£2.50 PL83 £0.70 PL84	£0.48 UCL83 £0.75 UL41	£1.74 £3.05
ECC83 £0.58 EL84 ECC84 £0.78 EL509	£1.00 PCC805 £5.95 PCF80.Maz		£2.00 UL44	£3.05
ECC85 £0.98 ELL80		£1.75 PL95	£2.00 UL84	£0.95
ECC88 £0.63 EY51	£0.80 PCF200	£1.30 PL504 +	£1.46 UY85	£0.67
+ Imported brand, Mi INCLUSIVE If order	ui, Mullard, Maz, Mazo totals under £10, add 5 – NO VAT, POST I	5p handling char		
Our valves are genuin clean condition. Mulla types deno	ely new and unused, o rd or Mazda valves are tted 'Mul' 'Maz' are as	supplied wherev	er availablity pe	ested, rmits,
Please enquire for any Our full valve listing li etc 3	ists 1,000 types TV, au Send 35p (pp) for your	dio, transmitting, copy inc. 50p vo	oscilloscope, vir ucher.	ntage,
15p e	TED. (Clean and Boxed ach: DY86/7, EF80, PC 20p each: PCL85, 21-2-3, ECL80, PCC84,	F808, PLC86, PY8 PL36, PFL200	300/1	atch.
LAST CHANCE:	g reels of high qualit UPPLY MULLARD CTV	y TV Solder (16a	wg) £7 post pa	id.
ORDERING INF				55p
Mail order only. Same	e day despatch. SAE antee on new valves, 2	enquiries. 35p for	r valve listing. 9	0 day
	Meiling Address On			
		·		
Irw	BILLINGTON in Drive, Horsham, W		NL.	

RILLINGTON VALVES

our workshop oscilloscope, using an 18V d.c. supply only, it appears as shown in Fig. 1 (b). As Mr. Hardy says, the waveforms shown in Fig. 3 (a) and (b) in my article were not correct, and I apologise to readers for this.

The important thing about this waveform when making tests is not so much its exact shape as that it must be "clean", not with ragged edges as shown in Fig. 1 (c). If the waveform is ragged in this way, C624 (47μ F, 25V electrolytic) must be replaced. Once the external 18V d.c. supply has been removed and the 240V a.c. mains supply connected, the waveform at the collector of Q605 must of course be as shown in Fig. 1 (a). Note that the waveforms shown in Fig. 1 (b) and (c) may vary a little as the line oscillator is running free.

BUSH T20/T22 CHASSIS

A couple of Bush T20/T22 receivers have caused me some problems recently. A report may help others confronted with the same symptoms.

The first set, a T20, produced no results other than some arcing noises. I soon discovered that the tripler was responsible for this — there was a pinhole fracture in the

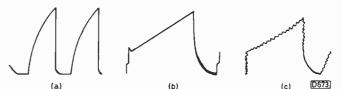


Fig. 1: Sony KV1810UB waveforms – see comments on letter from P. Hardy.

casing. A new one produced a picture and sound, but turning up either the brightness or contrast controls resulted in severe arcing at the e.h.t. cap. The surround was cleaned and treated with silicone grease, but this had no effect on the fault. Assuming that the e.h.t. was high I replaced the line flyback tuning capacitor 5C14, the h.t. being correct at 200V. This again made no difference, so I decided to replace the line output transformer, whose notoriety is well documented. As luck would have it, a T22 had just come in for repair, so panel swapping was tried. Fitting the line output panel didn't change the fault however. In desperation the whole chassis were interchanged. Still the same! It was the tube of course.

This was by no means the end of the story unfortunately. On a soak test arcing sounds were heard from the set accompanied by tracking effects on the screen, along with focus variations. I quickly turned down the lighting and peered at the e.h.t. cap. Not from there this time but from the focus pin. The white surround was blackened and badly burnt, and nice flashes could be seen in the dark. A new base was fitted together with a new focus unit — there were signs that it had been running warm, and anyway I was nervous.

On looking at the screen yet another fault had put in an appearance. There were four regular dark and light vertical bands an inch wide and and inch apart, starting at the left and gradually diminishing in intensity towards the right. Many components were bridged or tested while trying to trace the cause of this one. The culprit was eventually discovered to be 5C17 (0.47μ F) which forms a reservoir for the clipper diode in the tripler, i.e. the feed to the beam limiting circuit. Bridging it was not sufficient to clear the fault.

On a soak test the set was fine apart from a tendency to show very quick changes in contrast level on a "contrasty" scene. The cause of this fluttering effect also took a while to find, due to its intermittent nature – it wouldn't show up on a test card display. It was eventually traced to the a.g.c. preset on the i.f. subpanel.

The set was now fit to be returned to its owner — and I wasn't sorry to see it go!

The second problem set was a T22 which came in for replacement of the tripler and line output transformer. After refitting the panel all was thought to be well. When the set was switched on however there was a normal picture but no sound. Thinking I'd disconnected the speaker leads, I checked these first. But no! The i.f. subpanel is prone to causing intermittent sound in these sets, so a disturbance test was carried out. Again no luck. Turning the volume up produced some audio noise, so I tried the effect of tuning. This gave very edgy sound but no picture/sound sync.

I decided to check the 12V supply to the TDA2190 sound chip and found this to be 22V. Switch off quickly and ponder about the possible damage done — and the cause! Cold checks on the 12V regulator failed to reveal anything amiss, so I had to switch on again. A check at the input to the regulator gave a reading of zero volts. What! With no 36V line (input to the 12V regulator etc.) there should be no 12V line and as this feeds the signals circuits and the line oscillator there should be no results! The 36V line is produced by the EW diode modulator, across the reservoir capacitor 5C8 (1,500 μ F), and the line output transistor sits on this line. A check directly at the emitter of the BU208A produced a reading of 0V, but a check directly across 5C8 gave the correct reading of 36V. It was now apparent what had happened — a slight turn of the

line output panel earthing screw produced a normal 36V line and normal 12V regulator action. Still no sound however as the TDA2190 had been killed.

That was an interesting one indeed. This T22 lived happily ever after, once I'd replaced the on/off switch (intermittent) and the seven-segment channel display unit (one segment unlit, another dim), plus the TDA2190 (expensive!) of course. I suppose you're wondering where that 22V came from if not from the 12V regulator? Well so am I, and after this collection of nightmares I don't feel particularly inclined to speculate on the matter! Any ideas?

Stephen Leatherbarrow, Middleton, Manchester.

PLUGS, SOCKETS AND SAFETY

I fail to understand why Victor Rizzo (letters, June) goes to such lengths to devise his 13A to 5A plug adaptor when one could be made more quickly from a 13A trailing outlet wired to a 5A plug. This would also be much safer.

I am also worried by P. Richard's letter (same issue) in connection with Victor Rizzo's portable light unit. He's concerned about the earthed metal box used in the construction of the unit, but unless the mains powered transformer unit is constructed to IEC Class II standard ("all insulated" or "double insulated" — see BS2754) the exposed metalwork must be earthed (IEC Class I). Class 0 equipment, in which no earth is provided and protection against shock relies upon basic insulation only, is not permitted in the UK under the Electrical Equipment (Safety) Regulations, 1975.

Thus earthing the light unit is necessary to ensure its safe operation. In the example quoted of the light unit being used next to a live TV chassis, the TV set should of course be run via a mains isolation transformer. The hazard is not in the use of the earthed light unit but in the TV set with its exposed live chassis not being used with an isolating transformer.

Andrew Longbottom, Glasgow.

Your June issue carried a letter from Victor Rizzo outlining a method he'd devised to overcome the problem of installations with 5A socket outlets and equipment fitted with 13A plugs. With all due respect, I sincerely trust that no one ever decides to follow his example and make the sort of ad hoc arrangements suggested and illustrated. It's absolutely contrary to the principle which the electrical industry has been advocating for so long, i.e. the need for continued and increased safety levels for electrical equipment of all types.

5A socket outlets are made for accepting 5A plugs, likewise with 13A sockets and plugs. To carry out the sort of lash-up suggested is to invite the risk of danger and possible injury to the individual no matter how experienced he may be in electrical matters. It's far better to spend a little time changing the plug to the correct rating of the socket than to encourage the use of unorthodox and potentially dangerous methods. Better to be a live service engineer who does occasionally have to take the time to change a plug than a dead one who has hastened his departure from this life by trying to be just a little too clever.

J.J. Fallon,

Director — External Relations, MK Electric Ltd.

Long-distance Television

Roger Bunney

The 1983 SpE season has had one of the latest and slowest starts of any I can recall, and I've been TV-DXing for over twenty years! Following the excellent opening on May 2nd, reported last month, there were two weeks of relatively quiet conditions punctuated by small openings and it wasn't until the 25th that the first really good opening occurred. Since then there's been some sort of activity on most days, indicating that the season has at last got under way. The SpE log for the period is as follows.

- 6/5/83 SR (Sweden) chs. E2 and 4; Swiss SRG E2; TSS (USSR) R1; CST (Czechoslovakia) R1; RTVE (Spain) E2.
- 12/5/83 TSS R1, 2; TVP (Poland) R1; MTV-1 (Hungary) R1.
- 13/5/83 TSS R1, 2; TVP R1, 2.
- 16/5/83 A good opening. RAI (Italy) IA, B; RTVE E3, 4; JRT (Yugoslavia) E3; CST R1; TVP R1, 2; TSS R1, 2; Swiss SRG E2.
- 17/5/83 TSS R1; MTV-1 R1; RTVE E2; NRK (Norway) E2; SR E2. The USSR 0249 monochrome test pattern was seen on ch. R1 with reduced width/height!
- 20/5/83 WG (W. Germany) BR-1 E2; TSS R1; RTVE E2.
- 21/5/83 RTVE E2.
- 22/5/83 Buster Keaton film on ch. R1 (unidentified) during the afternoon.
- 23/5/83 RTVE E2, 3.
- 24/5/83 TSS R1, 2; RTP (Portugal) E3; RTVE E2.
- 25/5/83 A very good opening from late afternoon onwards. TSS R1-4; TVP R1-3; MTV-1 R1, 2; ORF (Austria) E2a; RAI IA, B; JRT E4; CST R1; RTP E2, 3; RTVE E2-4; Swiss SRG E2; unidentified signals and JTV (Jordan) E3.
- 26/5/83 NRK E2.
- 27-28/5/83 RTVE E2.
- 31/5/83 RAI IA, B; RTP E3.
- 2/6/83 TSS R1; unidentified ch. R1 colour bars at 0910.
- 3/6/83 TSS R1-3 (noted by C. Willis at 0500); CST R1, 2; RTVE E2-4; TVR (Rumania) R2; ORF E2a; TVP R1, 2; RTP E2, 3; NRK E2-4; SR E2-4; RTVE Canary Islands E3 blockboard test card with Izana identification at the bottom received by H. Cocks.
- 4/6/83 TSS R1, 2; TVP R1; RTVE E2-4; RTP E3.
- 6/6/83 TSS R1, 2; TVP R1; CST R1; NTV (Nigeria) Sokoto E3 received by H. Cocks at 1600-1730 (coloured dancers).

On May 12th Ryn Muntjewerff (Holland) noted the TSS electronic "Leningrad" pattern with the identification KHEE. The JTV reception on May 25 was by Ian Johnson in Bromsgrove and lasted for an hour starting at 1900. At the time I was receiving at Romsey a ch. E4 news announcer with "Groucho" moustache and captions with French wording – thoughts are that this could be CLT (Lebanon).

bland) R1; MTV-1 (Hun-2. (Italy) IA, B; RTVE E3, (Italy) IA, B; RTVE E3, (Italy) IA, B; RTVE E3,

loggings.

The results obtained with this new u.h.f. installation have been startling. Crystal Palace ch. 23 at 65 miles previously provided some 520μ V on average via an amplifier with similar gain. This is now up to 1.05mV average! In group C/D the gain is perhaps an odd dB or so down, but the polar response is much smoother with a lack of side lobes.

On May 31st Cyril Willis received Gwelo ZTV (Zimbabwe) ch. E2 very strongly from 1840-1910 with "Flintstones" cartoons. This signal was via TE skip. A scratchy aurora was noted in Aberdeen on May 17th from 2000-2300. Following severe thunderstorms on June 5th, an unusual "fluttery" tropospheric lift was noted on semi-

My thanks to Ian Johnson (Bromsgrove), Hugh Cocks

(E. Sussex), Tim Anderson (Stroud), Mel James (Anglesey), Cyril Willis (Ely), Arthur Milliken (Wigan), Ian Menzies (Aberdeen), Gosta van der Linden and Ryn

Muntjewerff (Holland) whose reports supplement my own

I was very busy during May changing all the aerials on

the main lattice mast and renewing the coaxial feeders.

After seven years of faithful service, the Antiference

XG21W was scrapped and replaced with a twin Triax

panel grid stack - the system was described in my article

on wideband u.h.f. aerials in the August issue last year. A

distant signals - most unusual!

New Aerial Arrangements

The Band I array consists of a modified type WB2 with a widely spaced, three-element reflector: the aerial is mounted so that it apparently points straight up into the sky. The spacing was chosen to obtain a response slightly above the horizontal level, with the aim of reducing interference pick up from below. With such a wideband system it's impossible to achieve optimum spacing throughout the spectrum for the required polar response. The ideal spacing is 0.25λ , but I chose 0.27λ at 55MHz. At 61.5MHz this provides only a 3.9dB interference reduction, but at 49.5MHz the reduction is 16dB (measured as signal voltage).

A 13-element Triax wideband array is used for Band III – it's a really heavy aerial, due to the use of half inch elements. An active aerial has been installed below the Band III array. This is mainly for experimental use and for Band II (TV). The Band I system is mounted at 67ft, the u.h.f. aerials at 60ft and the Band III array at 55ft. The indoor amplifier/filter arrangements are now due for replacement – the new system will incorporate braid break filters in all input feeders.


The new u.h.f. system has proved very useful for assessing ATV reception at 435MHz during the past month – some eight signals have been logged. Picture material varies from a BATC test card with identification to views of an operator, his equipment etc., obtained via a camera, or computer originated information from a ZX81, Spectrum, etc.

News Items

Medium wave a.m. stereo: Sansui have developed a stereo decoder chip that will decode any of the four a.m. stereo systems at present being introduced in the USA. The chip



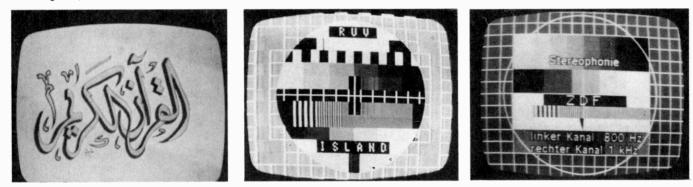Left: U.H.F. DX. ZDF (W. Germany) ch. E21 received in Helsinki by Seppo Pirhonen. Centre: ATV reception at Romsey, showing a Spectrum microcomputer derived identification. Right: French news caption via RTM (Morocco), ch. E4.



Left: The Koran, via RTM ch. E4 (photo taken in Morocco). Centre: The PM5544 pattern, received from Iceland on ch. E4 via SpE – photo from Keith Harmer, Derby. Right: The FUBK pattern with stereo sound test transmission received by Garry Smith (Derby) via tropospheric propagation.

switches automatically between standards. Sansui have also developed a PLL synchronous detector that would increase the price of a standard a.m. radio receiver by only 20 per cent.

France: It seems that the new fourth service, 4-Canal Plus, which is due to come into operation around May 1984, will be scrambled. The viewer will require a magnetic card to insert into his descrambler, the scrambling being a random system.

Satellites: Some 48 prime programme channels are expected to be available in the USA by the end of this year – these are channels for cable operators or domestic reception via 6ft dishes plus terminals. When more specialised channels (religious etc.) are taken into account the total will be something like 70. There's talk of 150 channels being available by 1987. Just what the programme standards will be like is anybody's guess.

Hungary is planning a DBS service to come into operation in late 1986 or early 1987. The programmes will differ from the MTV-1 and -2 services.

AFN: An American Forces Network TV station is to be installed at Svesterberg (Holland) and may use system M chs. A5 and 6 or A80 and 83.

From our Correspondents . . .

John Abbot (South Africa) has replaced the dish he's been using for reception of the Russian Stat-T satellite transmissions at 714MHz, 99°E with a broadside array of Wolsey Colour Kings. The signals are amplified by a 38dB gain preamplifier with a 1.8dB noise figure and, having retuned the sound i.f. in his Philips monochrome receiver to 6.5MHz, he can now watch TSS-1 in comfort.

Anthony Mann, previously at Perth, Western Australia and now at Baton Rouge, USA, has identified a spurious 26·19MHz emission from KABC Los Angeles, ch. A7. This was received in New Zealand recently but another distantly received spurious TV signal at 26MHz has yet to be identified. The SpE season in the USA opened up on May 5th, with signals virtually daily.

Tim Anderson (Stroud, Gloucestershire) has been DXing for some two years but recently moved to premises that have restricted his installation. Even so a Plustron TVR5D with its whip aerial is giving excellent results. A WB3 Band I aerial, Vorta 14-element Band III array and Vorta VPX22W were previously used, with RTE to the west received daily at fair to good quality. He has a ch. E3 dipole in the roof space and this has given good SpE signals, proof that even minimal equipment can be used to good effect. Tim occasionally goes mobile with his VPX22W.

Transmitters Local and Exotic

The latest edition of the IBA's "Transmitting Stations – a Pocket Guide", dated May 1983, has now been published. Copies are available from Engineering Information, IBA, Crawley Court, Winchester, Hants SO21 2QA.

A list of exotic Band I stations that could be received in NW Europe via multiple-hop SpE, TE or F2 has been produced by the BDXC (Holland). These, plus a couple of additions, are as follows, arranged in channel order.

Channel E2: Dubai (UAE), Fih (Lebanon), Freetown (Sierra Leone), Gwelo (Zimbabwe), Jounieh (Lebanon),

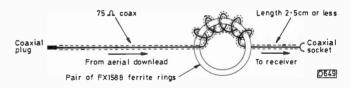


Fig. 1: Braid break filter suggested by the Home Office. Use five turns on a pair of FX1588 rings for 40-220MHz (13 turns on FX1587 or FX1588 rings for 3-40MHz).

Kabwe (Zambia), Kissi (Ghana), Kisumi (Kenya), Malabo (Equatorial Guinea).

Channel E3: Abafon/Ibadan (Nigeria), Bulajewo (Zimbabwe), Dharan (Saudi Arabia), Jamasi (Ghana), Jaradi/Sokoto (Nigeria), Lusaka (Zambia), Mougu (Zambia), Nabi-Saleh (Syria), Suweilih (Jordan).

Channel E4: Ajancote (Ghana), Al-Aineh (Yemen), Big Bend (Swaziland), Harare (Zimbabwe), Hassake (Syria), Ibadan (Nigeria), Isa Town (Bahrain), Jaji/Kaduna (Nigeria), Kitwe (Zambia), Laayoune (Morocco), Maaser el Chouf (Lebanon), Malherbes (Mozambique), Nairobi (Kenya), Scaba (Swaziland).

Quite a few of these transmitters have been received in the UK in recent years, some fairly regularly.

Developments in Band I

By now most enthusiasts will probably have noticed signals from cordless phones, 50MHz amateur stations and other sources spreading across the European Band I TV spectrum. Recently at Romsey I noticed a form of personal mobile radio operating at 64-19MHz and two other discrete frequencies under 100kHz away. The signals consisted of varying tone sequences. Contacting two main PMR companies revealed nothing - they didn't operate below 72MHz. There are however many smaller companies operating in this field. One was contacted about the 64 19MHz signals. Denials were made, along with suggestions of "continental interference". The firm was known to have installed a certain make of equipment however, and this is advertised as going into the 60MHz region. They were told that the Home Office was being informed about the intrusion. That same night the transmissions ceased!

Cordless phones are an increasing problem. I recently heard that a London company is installing a 49MHz system with a range of thirty miles! Apart from phone harassment and informing British Telecom there's little one can do until the new Telecomms bill comes into force.

Amateur radio operators had a chunk of Band I until the forties, losing it when the 405-line service spread across the UK. They are now getting part of it back. In the meantime however the use of Band I has changed both locally and internationally. Amateur operators could cause serious interference to TV services in those countries still using (and likely to go on using) Band I, especially via SpE in the summer months.

The interests of DXers carry little weight of course, but I still feel that we could make representations to the Home Office and would be interested to hear others' views. Interference to other services would be the thing to emphasize – for example the proposed 50-52MHz alloca-

SERVICE BRIEFS - THORN

The following items have appeared in recent editions of *Ferguson Feedback*. **1696/7 monochrome chassis:** In later production a 100μ F, 25V electrolytic capacitor was added between the supply and chassis pins 1/16 of the TDA1180 sync/line oscillator i.c. to provide extra smoothing and thus prevent hum on the line scan causing distorted verticals.

1790 monochrome chassis: In the event of slight field cramp, check that C51 in the field driver stage is 82pF and not 150pF.

TX9 chassis: The sync separator bias resistor R203 (main panels PC1040/PC1044) has been increased in value from $1M\Omega$ to $1.5M\Omega$ to improve the sync performance when a set

SOUTH WEST AERIAL Systems



The 'VEGA 402DE' is a VHF/UHF 6" screen mono TV for System B/G operation (5.5MHz sound) and is ideal for basic TV/DXing (or Continental travel) use. Operation is from a removable heavy duty mains PSU or an external 12 volt source (all plugs etc supplied). The receiver has rugged construction and contained within a metal cabinet, the carrying handle doubling as a receiver stand.

doubling as a receiver stand. The 402DE features very good sensitivity and sharp selectivity with its 4 individually tuned IF stages (5 stage at UHF). Aerial input is via separate VHF/UHF 75 ohm coaxial sockets, in addition a strong integral whip (40" extended) is provided to rear. The VHF tuner is an 11 position 'click stop' turret covering all Band 1/3 'E' channels — we adjust the ch.E2 coil to include ch.1A allowing **ALL** Band 1 TV/DX channels to be received — the fine tuning range in Band 3 is sufficient to cover virtually all European channels without adjustment. UHF coverage uses a small rotary tuner control (with varicap fine tune) covering the ch.21—68 range.

The 'VEGA 402DE' (USSR manufacture) is a very solid, basic but reliable receiver and intended for African export. South West Aerial Systems are the sole UK distributor for this model. (Delivery ex-stock). VEGA 402DE 6" mono TV (5.5MHz sound, VHF/UHF) — inclusive of VAT, delivery — £58.95.

Send 54p for our extensive 1983 catalogue detailing aerials (DXing and domestic), amplifiers, filters, etc. Customer consultancy to solve difficult reception problems, TV/FMDXing a speciality. Include SAE ALL enquiries please. Access/Barclaycard welcome.

NOTE OUR NEW ADDRESS ... South West Aerial Systems, 11 Kent Road, Parkstone, Poole, Dorset BH12 2EH. Tel: 0202-738232.

tion could be shifted to 50.5-52.5MHz to slot in between the ch. R1 and IA carriers.

A simple notch filter can be used by those experiencing high-level amateur interference – suitable designs have been featured in this column in the past and are also shown in my DX-TV book (Babani Press). A very simple but effective 25dB notch filter can be made by winding ten turns of 26g enamelled wire on a T50-12 Ambit ferrite ring, with a 2-22pF trimmer across the winding to tune the circuit. Connect the aerial to the centre of the winding and take the output from one end or the other. A suitable braid break filter (see Fig. 1) is described in a leaflet available from the Radio Regulatory Dept., Home Office, Waterloo Bridge House, Waterloo Road, London SE1 8UA (called "Ferrite Ring Filters FS64/1A and FS64/2A"). Many CB/ amateur radio shops sell ferrite rings - Bredhurst Electronics sell them at 80p a pair, though CB shops often charge up to £1 each.

is used in conjunction with poor quality video signals, e.g. from home computers, TV games, etc.

To eliminate the possibility of random dot patterning in versions using a chopper power supply (PC1044 panel), a 470pF capacitor has been added across the 12 5V rectifier D67 and its series choke L101, which should be of the aircored type (part no. 06D0-244-001). In addition the inductance of L66 has been reduced to 2.2μ H to optimise the drive to the base of the chopper transistor.

TX10 chassis: A rare fault that could cause some difficulty with diagnosis: distorted verticals followed by loss of width and eventual tripping has been traced to the line output transistor's base-emitter junction protection diode D831 going open-circuit.

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1 00 postal order (made out to IPC Magazines Ltd.), the query coupon from page 545 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

THORN 3500 CHASSIS

The trouble with this set is that the sync separator transistor VT203 keeps going short-circuit collector to emitter at switch on. A replacement lasts anything from a few days to a few months. All the components in the sync separator circuit have been checked and found to be in order.

The position of VT203 on the chassis is such that it's vulnerable to e.h.t. spark-overs from either the e.h.t. cable or the degaussing shield. Dress the cable well away from the video and decoder panels and make sure that the earthing leads from the tripler, the c.r.t. base and the line output stage are all firmly connected to the shield. If these points are in order and the c.r.t. spark gaps are o.k., a higher rated transistor such as a BC142 could be tried.

SONY KV2000UB

The trouble is irregular start-up. The set normally starts up at switch on and works all right until switched off. Occasionally however the set fails to start, with the indicator neon pulsing weakly at about one second intervals and an accompanying plop from the loudspeaker. If left for a day or two the set is once more o.k.

We suggest you replace the start-up diode D507 on the timebase panel, then C612 $(3.3\mu F)$ and Q604 on the power supply panel – the former is the 21V reservoir capacitor and the latter is one of the two transistors in the pulse width modulator circuit. The CX158 line generator chip IC508 occasionally causes this trouble – check that it's being supplied at pin 8 (7V or more) when the fault is present.

THORN 1400 CHASSIS

There's no raster on either system and the boost line reads just over 200V. Whilst investigating the fault the line scan coils became open-circuit with the result that the boost voltage returned to normal and a vertical white line appeared on both systems.

The problem appears to be shorting turns in the line section of the yoke, as a result of which the line timebase is being loaded down.

TANDBERG CTV2-2 CHASSIS

There have been several faults on this set – mostly in connection with the line output transformer derived 12V supply and the transformer's 60V tap off, due mainly to a dry-joint on the transformer. Everything is now in order apart from the horizontal convergence. The relevant controls have no effect, but no component faults can be found in this area.

The problem is fairly common on this chassis and is almost always due to a dry or open-circuit joint at the EW modulator transformer T752 on the timebase panel. Any discontinuity between the secondary on T752 and the convergence coil L902 will have the same effect.

THORN 3500 CHASSIS

Squiggly lines start at the top and bottom left-hand corners of the picture and continue for about four inches towards the centre of the screen. These lines are still present when the signal path is disconnected. The picture is otherwise good.

This sort of thing is usually caused by the tube's Aquadag coating not being earthed. There should be three leads from the degaussing shield, to the tripler, the line output stage and the c.r.t. base. If all these are in order, check the h.t. smoothing capacitor C619 (replace with one of 220μ F, 100V), the line linearity coil damping resistor R521 (1.2k Ω), capacitors C631 and C616 (0.01 μ F) in the power supply and that the core of L502 is present.

KÖRTING HYBRID COLOUR CHASSIS

There are two faults on this set. First the picture pulls to the right, almost going into a circle. I suspect the AA133 flywheel sync discriminator diodes but can't obtain replacements. Any suggestions for alternatives? Secondly there's an ident fault, the faces turning from red to green.

The flywheel sync discriminator diodes could be the cause of the first fault and almost any pair of diodes can be used – BA155s are commonly used for this purpose. Other things worth checking are the PCF802 line oscillator valve and the 25μ F decoupling capacitor C417 in this stage. The PAL switch (red/green faces) is in the TAA630 i.c., but before condemning this check the settings of the ident amplitude and frequency controls R883 and R887, especially the former (if it has little effect, check the electrolytic C819 – 1μ F – which is in series with it). Also check for dry joints around the ident transistor T748. The manufacturers suggest using a scope to adjust R883 and R887, but if necessary try adjusting each in turn, restoring them to their initial settings if no improvement is obtained.

PHILIPS N1502

The problem is with the two-minute delay circuit which doesn't switch off automatically. The release relay is activated by the monostable multivibrator TS115/6, and shorting out TS115 produces correct operation. Checks on the preceding transistors TS110, TS111 and TS112 have failed to reveal the cause of the trouble however.

The first transistor in the circuit, TS110, is turned on by various function switches. To eliminate switching problems, short-circuit the base and emitter of TS110 and monitor its collector voltage to check that it rises. It's difficult to check the following f.e.t. TS111's action since there will be little change in its drain voltage if it switches on. TS112 can be checked by putting a resistor of approximately 10k Ω between its base and chassis. TS112 should then switch TS116 on. D121 which is between these stages could be open-circuit, or TS115 could be failing to turn on. These checks should enable the circuit's operation to be evaluated, thereby tracing the source of the fault.



248

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

The Thorn 1600 chassis has always seemed to us to be a strange one – unable to make up its mind whether or not it's a portable, a bit wasteful on power consumption with 400 Ω in its dropper section and a shunt stabiliser, also precarious to work on with its hinged chassis and "peek-aboo" through-board arrangement for the c.r.t. neck and base. Electrically it's fairly conventional however, and most of the faults that occur are easy enough to diagnose. Our most recent encounter with one took us rather longer than it should have done, as you will see as the story unfolds.

The reported symptom was that the set took a very long time to "warm up" and come on. This in itself is unusual in a solid-state chassis. We switched on and found that we had sound (not very good) immediately, but there was no discernible picture of any sort for three-four minutes. Finally a small, distorted and blurred image appeared, indicating that all was not well in the line output stage. The tube's heater is fed from the line output transformer, which would explain the delay before any image became visible. After a minute or two more the picture slowly expanded to fill the screen - the e.h.t. regulation was poor however, and upon changing channels we were again confronted with a small "wiggly" image broken into lines and accompanied by a rough squeal from the area of the line output transformer - ugh! We switched off and felt the temperature of the BU205 line output transistor - you could have fried an egg on it!

In view of the loss of line lock we started our investigation in the line oscillator stage, which is of the usual sinewave type with two npn transistors VT13 and VT14 and feedback via the coil L19. The coil's centre tap is grounded from the a.c. point of view by C113 (100μ F), and as we've had trouble in this area in other sets we fitted a new electolytic. There was no change in the symptom, and the low voltage readings we found around the two transistors were probably due to the main problem, which we decided must lay elsewhere, especially as the line oscillator's output waveform P, at the emitter of VT14, looked reasonably like that shown in the manual. Time to shift one place right (in the computer parlance we're also currently struggling with) and look at the line driver stage, VT15 and its associated components.

The voltage at the collector of VT15 should read 140V, but what we found was 180V, virtually the same as the

heavily-loaded h.t. line. This suggested that VT15 was drawing very little current and, in contrast to the throbbing line output transistor VT16, both VT15 and its collector feed resistor R142 ($2.2k\Omega$, fusible) were very cool. VT15's collector waveform Q was around 40V peakto-peak instead of 210V p-p, and very far from the square shape it should have had. The key to the problem was perhaps revealed when we switched the scope to d.c. coupling and found that the transistor was not bottoming on the "negative" half-cycles of its output waveform they reached down to only about 130V. Had we thought about this more deeply, we would probably have gone straight to the faulty component. As it was, we changed the BF337 line driver transistor, using the recommended BF259, and tested the two perfectly good diodes in its emitter circuit before we got wise. So what was the culprit? We'll confirm your diagnosis next month!

ANSWER TO TEST CASE 247 – page 488 last month –

Last month's case involved an ITT CVC40 chassis which was completely dead so far as sound and picture were concerned, though you'll remember that the 300V line (output from the mains bridge rectifier) was found to be present and that the line oscillator was working (from its start-up feed via R4 and R3). The problem appeared to be in the CMP40 switch-mode control module, but a new one had made no difference to the symptoms.

The clue to the problem was the low voltage reading at the emitter of T801. The supply here comes from the set's 12V line, via D7, when the set is running normally, though there's a start-up feed via R806 since the 12V supply is derived from the line output transformer. This start-up feed has a high source impedance – R806 is $470k\Omega$ – and during start-up is isolated from the rest of the set by D7 which is then reverse biased. D7 is mounted on the mother board, and what had happened was that it was leaky and was thus allowing the i.f. strip, the tuner, the decoder and various other circuits to hang on the end of R806, thus mopping up most of the available energy with the result that the switch-mode power supply, and in particular T801, couldn't get started.

If we'd hooked up an independent 12V supply the set would have worked perfectly, but that would not necessarily have made the diagnosis any easier!

QUERY COUPON Available until 17th August 1983. One coupon, plus a £1.00 (inc. VAT) postal order, must accompany EACH **PROBLEM** sent in accordance with the Ĩ notice on page 544.

TELEVISION AUGUST 1983

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £11, overseas (surface mail) £12 per annum, payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

			ITEL	
	Manch	ester's No.	1 in Ex-Rer	ntal TVs
	Ονε	er 2,000 ⁻	FVs in s t	tock
	Specia	al Offer on W	orking Color	ur TV's
All sets are		with repolished		oles of UNTESTED TVs
	inets ready f			available
Philips G8	3 550s	22/26 £45	Thorn	10 for £125
Philips 18		£40	Philips	6 for £90
Philips G8 GEC S/St	o 520s ate	22/26 £35 from £35	Bush GEC	6 for £80 6 for £60
Thorn 17"		£30	Decca	6 for £60
Decca 30		20/22/26 £30	Mono TVs a	
Japanese Many oth		from £30 vailable from	New TV tro All sizes	lly stands. £4.95
Ivially Oth	£25			ubject to V.A.T.
Dis	scount on qu	uantity		, .
	Ex Equ	uipment Panel	s & Tubes Av	vailable
	Deliverie	es may be arranged		Scotland.
440 D		Ring for quote. (
419 Ba	arlowmo	oor Road, Cho	oriton, Manc	chester 21 2ER.
		Tel: 061	861 8501	
****	\sim \sim \sim \sim \sim \sim		(XXXXXXXX	
TV TUB		POLISHING		
WORKING	TV's WOR FREE DELIVE	POLISHING KING PANELS RY*	UNIVERSAL	PROGRAMME SELECTOR VARICAP TUNING
WORKING Quality, Hig	TV's WOR FREE DELIVEI gh Temperatur	POLISHING KING PANELS RY* re Reprocessing	UNIVERSAL FOR	PROGRAMME SELECTOR
WORKING	TV's WOR FREE DELIVE	POLISHING KING PANELS RY* re Reprocessing Two year guarantee (optional extension	UNIVERSAL FOR 6 way interlocked d.p. switch 100 K tuning potentiometers	PROGRAMME SELECTOR VARICAP TUNING
WORKING Quality, Hig Colour Tubes Oelta up to 20"	TV'S WOR FREE DELIVE The temperatur One year guarantee (optional extension up to three years) £26 £30	POLISHING KING PANELS RY* re Reprocessing Two year guarantee (optional extension up to four years) £29 £33	UNIVERSAL FOR Way interlocked d.p. switch 100 K tuning potentiometers Top quality through hole plated pcb	PROGRAMME SELECTOR VARICAP TUNING
WORKING Quality, Hig Colour Tubes Oelta up to 20" up to 22" up to 22" oup to 26"	TV'S WOR FREE DELIVE gh Temperatur One year guarantee (optional extension up to three years) £26	POLIS'HING KING PANELS RY* re Reprocessing Two year guarantee (optional extension up to four years) £29	UNIVERSAL FOR Kor 6 way interlocked d.p. switch 100 K tuning potentiometers Top quality through hole	PROGRAMME SELECTOR VARICAP TUNING
WORKING Quality, Hig Colour Tubes Oelta ⁹ up to 20" ⁹ up to 22" ⁹ up to 22" ⁹ up to 26" ¹⁰ 26" ¹⁰ 26" ¹⁰ 26" ¹⁰ 26"	TV'S WOR FREE DELIVEI on ever guarantee (optional extension up to three years) £26 £30 £32	POLISHING KING PANELS RY* re Reprocessing Two year guarantee (optional extension up to four years) £29 £33 £35	UNIVERSAL FOR Way interlocked d.p. switch 100 K tuning potentiometers Top quality through hole plated pcb Dimensions: 5" by 2 <u>1</u> " by 1" Ideal for replacement when original parts are obsolete or unobtainable Template guide supplied for	PROGRAMME SELECTOR VARICAP TUNING
WORKING Quality, Hig Colour Tubes Oelta Oup to 22" Oup to 22" Or 26" St heat, narrow neck) Line & PIL To 20"	TV'S WOR FREE DELIVEI on ever guarantee (optional extension up to three years) £26 £30 £32	POLISHING KING PANELS RY* re Reprocessing Two year guarantee (optional extension up to four years) £29 £33 £35	UNIVERSAL FOR UK 6 way interlocked d.p. switch 100 K tuning potentiometers Top quality through hole plated pcb Dimensions: 5" by 24" by 1" Ideal for replacement when original parts are obsolete or unobtainable Template guide supplied for drilling of your own fascia design	PROGRAMME SELECTOR VARICAP TUNING
WORKING Quality, Hig Colour Tubes Oelta ⁹ up to 20" ⁹ up to 22" ⁹ up to 22" ⁹ up to 26" ⁰⁷ 26" st heat, narrow neck) Line & PIL to 20"	TV'S WOR FREE DELIVE The per guarantee (optional extension up to three years) £26 £30 £32 £33	POLISHING KING PANELS RY* e Reprocessing Two year guarantee (optional extension up to four years) £29 £33 £35 £36 £42	UNIVERSAL FOR Way interlocked d.p. switch 100 K tuning potentiometers Top quality through hole plated pcb Dimensions: 5" by 3!" by 1" Ideal for replacement when original parts are obsolete or unobtainable Template guide supplied for drilling of your own fascia design Range of pre-cut and drilled fascia/mounting kits for selected TV chassis enabling	PROGRAMME SELECTOR VARICAP TUNING
WORKING Quality, Hig Colour Tubes Oelta ⁰ up to 20" ⁰ up to 22" ⁰ up to 26" ⁰ st heat, narrow neck) Line & PIL to 20" to 22" to 22" to 22"	TV'S WOR FREE DELIVEI on eyear guarantee (optional extension up to three years) £26 £30 £32 £33 £36 £38 £40	POLISHING KING PANELS RY* re Reprocessing Two year guarantee (optional extension up to four years) £23 £33 £35 £35 £36	UNIVERSAL FOR Way interlocked d.p. switch 100 K tuning potentiometers Top quality through hole plated pcb Dimensions: 5" by 23" by 1" Ideal for replacement when original parts are obsolete or unobtainable Template guide supplied for drilling of your own fascia design Range of pre-cut and drilled fascio/mounting kits for	PROGRAMME SELECTOR VARICAP TUNING
WORKING Quality, Hig Colour Tubes Oelta Oelta Oup to 20" Oup to 22" Oup to 26" Of 26" St heat, narrow neck) Line & PIL Oto 20" Oto 22" Oto 22" St heat, narrow neck) Line & PIL Oto 20" St heat, narrow neck) Line & St heat MON A50-120W/R E	TV'S WOR FREE DELIVEI on eyear guarantee (optional extension up to three years) £26 £30 £32 £33 £36 £38 £40 //AT for optional guar tube. IO TUBES (One Year	POLISHING KING PANELS RY* ce Reprocessing Two year guarantee (optional extension up to four years) £29 £33 £35 £36 £42 £44 £44 £46 rantee on any type of colour Guarantee) Monc Portables £16	UNIVERSAL FOR Way interlocked d.p. switch 100 K tuning potentiometers Top quality through hole plated pcb Dimensions: 5° by 24° by t° Ideal for replacement when original parts are obsolete or unobtainable Template guide supplied for drilling of your own fascia design Range of pre-cut and drilled fascia/mounting kits for selected TV chassis enabling our unit to be fitted without further cutting drilling or modification All orders despatched same day	PROGRAMME SELECTOR VARICAP TUNING Regd. Design No. 1006611
WORKING Quality, Hig Colour Tubes Delta Up to 20" Up to 20" Up to 26" 2 2 2 2	TV'S WOR FREE DELIVEI gh Temperatur One year guarantee (optional extension) up to three years) £26 £30 £32 £33 £36 £38 £40 //AT for optional guar tube. IO TUBES (One Year 12, A61-120W/R £13, tubes exchange glass DWING ITEMS CALL Solour TV's, with we	POLISHING KING PANELS RY* re Reprocessing Two year guarantee (optional extension up to four years) £29 £33 £35 £36 £42 £44 £44 £46 rantee on any type of colour Guarantee) Mono Portables £16 s required. ERS ONLY Il view tubes fitted (1 year	UNIVERSAL FOR Way interlocked d.p. switch 100 K tuning potentiometers Top quality through hole plated pcb Dimensions: 5" by 2 <u>4</u> " by 1" Ideal for replacement when original parts are obsolete or unobtainable Template guide supplied for drilling of your own fascia design Range of pre-cut and drilled fascia/mounting kits for selected TV chassis enabling our unit to be fitted without further cutting drilling or modification All orders despatched same day DIRECT REPLACEMENT FA Type 30-80 Replaces 7 pian	PROGRAMME SELECTOR VARICAP TUNING Regd. Design No. 1006611
WORKING Quality, Hig Colour Tubes Oelta ⁹ up to 20" ⁹ up to 22" ⁹ up to 26" ⁹ z6" st heat, narrow neck) Line & PIL to 20" to 26" ease add £12 plus V MON A50-120W/R £ All 1 FOLC blid state working c guar Workin	TV'S WOR FREE DELIVEI on ever guarantee (optional extension up to three years) £26 £30 £32 £33 £36 £38 £40 /AT for optional guar tube. IO TUBES (One Year 12, A61-120W/R £13, tubes exchange glass DWING ITEMS CALL colour TV's, with we rantee on tubes) from g TV Panels at Reasc	POLISHING KING PANELS RY* re Reprocessing Two year guarantee (optional extension up to four years) £23 £33 £35 £36 £42 £44 £44 £46 rantee on any type of colour Guarantee) Mono Portables £16 s required. ERS ONLY HI view tubes fitted (1 year onable Prices	UNIVERSAL FOR UK 6 way interlocked d.p. switch 100 K tuning potentiometers Top quality through hole plated pcb Dimensions: 5" by 2!" by 1" Ideal for replacement when original parts are obsolete or unobtainable Template guide supplied for drilling of your own fascia design Range of pre-cut and drilled fascis/mounting kits for selected TV chassis enabling our unit to be fitted without further cutting drilling or modification All orders despatched same day DIRECT REPLACEMENT FA Type 30-C Replaces 7 pian chassis	PROGRAMME SELECTOR VARICAP TUNING Regd. Design No. 1006611
WORKING Quality, Hig Colour Tubes Oelta ⁹ up to 20" ⁹ up to 22" ⁹ up to 26" ⁹ z6" st heat, narrow neck) Line & PIL to 20" to 20" to 26" ease add £12 plus W A50-120W/R £ All the FOLC Did state working of guar Working Durished with our points	TV'S WOR FREE DELIVEI on ever guarantee (optional extension up to three years) £26 £30 £32 £33 £36 £38 £40 /AT for optional guar tube. IO TUBES (One Year 12, A61-120W/R £13, tubes exchange glass DWING ITEMS CALL colour TV's, with we rantee on tubes) from rg TV Panels at Reaso tubes with scratch pourpose built polishi tube.	POLISHING KING PANELS RY* re Reprocessing Two year guarantee (optional extension up to four years) £23 £33 £35 £36 £42 £44 £44 £46 rantee on any type of colour Guarantee) Mono Portables £16 s required. ERS ONLY Ill view tubes fitted (1 year onable Prices es or small chips, can be ng equipment. Only £7 per	UNIVERSAL FOR UK 6 way interlocked d.p. switch 100 K tuning potentiometers Top quality through hole plated pcb Dimensions: 5" by 2" by 1" Ideal for replacement when original parts are obsolete or unobtainable Template guide supplied for drilling of your own fascia design Range of pre-cut and drilled fascia/mounting kits for selected IV chassis enabling our unit to be fitted without further cutting drilling or modification All orders despatched same day DERECT REPLACEMENT FA Type 30-80 Replaces 7 pian chassis Type 30-C Replaces 7 pian perspex illumin Type 100 Replaces 8 posi	PROGRAMME SELECTOR VARICAP TUNING Regd. Design No. 1006611
WORKING Quality, Hig Colour Tubes Delta up to 20" up to 22" up to 26" or 26" st heat, narrow nack) Line & PIL to 20" to 26" line & PIL to 20" to 26" line & PIL to 20" to 26" line & PIL to 20" to 26" MON A50-120W/R £ All FOLC blid state working co guar Workin but good, working DLISHED with our peliver	TV'S WOR FREE DELIVEI on ever guarantee (optional extension up to three years) £26 £30 £32 £33 £33 £36 £38 £40 /AT for optional guar tube. IO TUBES (One Year 12, A61-120W/R £13, tubes exchange glass DWING ITEMS CALL colour TV's, with we rantee on tubes) from ng TV Panels at Reasc tubes with scratch purpose built polishin tubes from Lut y for tube orders over	POLISHING KING PANELS RY* re Reprocessing Two year guarantee (optional extension up to four years) £29 £33 £35 £36 £42 £44 £44 £46 rantee on any type of colour Guarantee) Mono Portables £16 s required. ERS ONLY Il view tubes fitted (1 year only £45 onable Prices es or small chips, can be ng equipment. Only £7 per ton. Fixed Charge £3. *Free er £50 + VAT.	UNIVERSAL FOR Way interlocked d.p. switch 100 K tuning potentiometers Top quality through hole plated pcb Dimensions: 5" by 3!" by 1" Ideal for replacement when original parts are obsolete or unobtainable Template guide supplied for drilling of your own fascia design Range of pre-cut and drilled fascia/mounting kits for selected TV chassis enabling our unit to be fitted without further cutting drilling or modification All orders despatched same day DIRECT REPLACEMENT FA Type 30-80 Replaces 7 pian chassis Type 30-0C Replaces 7 pian perspex illumin Type 100 Replaces 8 posi- Type CVC8-9 Replaces 5 rect	PROGRAMME SELECTOR VARICAP TUNING Regd. Design No. 1006611
WORKING Ouality, Hig Colour Tubes Oelta Oup to 20" Oup to 22" Oup to 26" Of 26" St heat, narrow neck) Line & PIL O to 20" D t	TV'S WOR FREE DELIVEI gh Temperatur One year guarantee (optional extension up to three years) £26 £30 £32 £33 £33 £36 £38 £40 /AT for optional guar tube. (O TUBES (One Year 12, A61-120W/R £13, tubes exchange glass DWING ITEMS CALL colour TV's, with we rantee on tubes) from 10 Panels at Reasc tubes with scratch purpose built polishin tube. 0 40 miles from Lut y for tube orders ove o all prices. Callers w	POLISHING KING PANELS RY* re Reprocessing Two year guarantee (optional extension up to four years) £29 £33 £35 £36 £42 £44 £44 £46 rantee on any type of colour Guarantee) Mono Portables £16 s required. ERS ONLY II view tubes fitted (1 year n Only £45 onable Prices es or small chips, can be ng equipment. Only £7 per ton. Fixed Charge £3. *Free er £50 + VAT.	UNIVERSAL FOR Way interlocked d.p. witch 100 K tuning potentiometers Top quality through hole plated pcb Dimensions: 5' by 3'' by 1'' Ideal for replacement when orginal parts are obsolete or unobtainable Toplate guide supplied for drilling of your own fascia design Range of pre-cut and drilled fascia/mounting kits for solution to be fitted without further cuting drilling or modification All orders despatched same dey DIMENTED ALL ALL ALL ALL Type 30-20 Replaces 7 plan Chassi Type 100 Replaces 8 posi used in Deccar/ Type CVC8-9 Replaces 5 rect	PROGRAMME SELECTOR VARICAP TUNING Regd. Design No. 1006611
WORKING Quality, Hig Colour Tubes Oelta Oelta Out 20" Out 20	TV'S WOR FREE DELIVEI on evear guarantee (optional extension up to three years) £26 £30 £32 £33 £36 £38 £40 /AT for optional guar tube. IO TUBES (One Year 12, A61-120W/R £13, tubes exchange glass DWING ITEMS CALL colour TV's, with we rantee on tubes) from ng TV Panels at Reas tubes with scratche purpose built polishin tube. o 40 miles from Lut y for tube orders over o all prices. Callers w prehensive price list fube Types that can 1	POLISHING KING PANELS RY* re Reprocessing Two year guarantee (optional extension up to four years) £29 £33 £35 £36 £42 £44 £44 £46 rantee on any type of colour Guarantee) Mone Portables £16 s required. ERS ONLY II view tubes fitted (1 year only £45 onable Prices es or small chips, can be ng equipment. Only £7 per ton. Fixed Charge £3. *Free ar £50 + VAT. velcome. Please phone first. and a wall chart of approx be processed by us. 14-134 Midland Rd. uton, Beds.	UNIVERSAL FOR Way interlocked d.p. witch 100 K tuning potentiometers Top quality through hole plated pcb Dimensions: 5' by 3'' by 1'' Ideal for replacement when orginal parts are obsolete or unobtainable Toplate guide supplied for drilling of your own fascia design Range of pre-cut and drilled fascia/mounting kits for solution to be fitted without further cuting drilling or modification All orders despatched same dey DIMENTED ALL ALL ALL ALL Type 30-20 Replaces 7 plan Chassi Type 100 Replaces 8 posi used in Deccar/ Type CVC8-9 Replaces 5 rect	PROGRAMME SELECTOR VARICAP TUNING Regd. Design No. 1006611
WORKING Quality, Hig Colour Tubes Oelta Oelta Out 20" Out 20	TV'S WOR FREE DELIVEI gh Temperatur One year guarantee (optional extension up to three years) £26 £30 £32 £33 £36 £38 £40 /AT for optional guar tube. IO TUBES (One Year 12, A61-120W/R £13, tubes exchange glass DWING ITEMS CALL Solour TV's, with we rantee on tubes) from ng TV Panels at Reasc tubes with scratche purpose built polishin tube. o 40 miles from Lut y for tube orders ove o all prices. Callers w prehensive price list fube Types that can 1 L Sat 9am-5pm. Tel. 0582-	POLISHING KING PANELS RY* re Reprocessing Two year guarantee (optional extension up to four years) £29 £33 £35 £36 £42 £44 £44 £46 rantee on any type of colour Guarantee) Mone Portables £16 s required. ERS ONLY II view tubes fitted (1 year only £45 onable Prices es or small chips, can be ng equipment. Only £7 per ton. Fixed Charge £3. *Free ar £50 + VAT. velcome. Please phone first. and a wall chart of approx be processed by us. 14-134 Midland Rd. uton, Beds. -410787	UNIVERSAL FOR Way interlocked d.p. switch 100 K tuning potentiometers Top quality through hole plated pcb Dimensions: 5' by 3'' by 1'' Ideal for replacement when original parts are obsolete or unobtainable Tenglate guide supplied for drilling of your own fascia design Range of pre-cut and drilled fascia/mounting kits for selected TV chassis enabling our unit to be fitted without further cutting drilling or modification All orders despatched same day DIRECT REPLACEMENT FA Type 30-20 Replaces 7 plan chassis Type 30-20 Replaces 7 plan chassis Used in Deccar/I Type CVC8-9 Replaces 5 rectu SELECT	PROGRAMME SELECTOR VARICAP TUNING Regd. Design No. 1006611
WORKING Quality, Hig Colour Tubes Oelta P up to 20" P up to 22" P up to 22" P up to 22" P up to 26" O' 26" ast heat, narrow neck) Line & PIL p to 20" p to 26" Mease add £12 plus W A50-120W/R £ All th FOLC olid state working of guar Workin our good, working of guar Workin our guar Workin our good, working of guar Workin our good, working of guar Workin our good, working of guar Workin our good, working of guar Workin our good, working of Workin our good, working of Workin our guar Workin our guar Workin Work	TV'S WOR FREE DELIVEI on eyear guarantee (optional extension up to three years) £26 £30 £32 £33 £36 £38 £40 /AT for optional guar tube. IO TUBES (One Year 12, A61-120W/R £13, tubes exchange glass DWING ITEMS CALL colour TV's, with we rantee on tubes) from ng TV Panels at Reasc tubes with scratche purpose built polishin tubes with scratche purpose built polishin tubes from Lut y for tube orders ove o all prices. Callers w prehensive price list fube Types that can 1 £ Sat 9am-5pm. Tel. 0582- Widdx. Tel. 9684-27019 L, Chesham, Buckingham	POLISHING KING PANELS RY* re Reprocessing Two year guarantee (optional extension up to four years) £29 £33 £35 £36 £42 £44 £44 £46 rantee on any type of colour Guarantee) Mono Portables £16 s required. ERS ONLY Il view tubes fitted (1 year only £45 onable Prices es or small chips, can be ng equipment. Only £7 per ton. Fixed Charge £3. *Free er £50 + VAT. velcome. Please phone first. and a wall chart of approx be processed by us. 114-134 Midland Rd. uton, Beds, 410787	UNIVERSAL FOR UK Switch 100K tuning potentiometers Top quality through hole plated pcb Dimensions: 5" by 2%" by 1" Ideal for replacement when original parts are obsolete or unobtainable Template guide supplied for drilling of your own fascia design Range of pre-cut and drilled fascia/mounting kits for selected TV chassis enabling our unit to be fitted without further cutting drilling or modification All orders despatched same day DIFECT REPLACEMENT FA Type 30-60 Replaces 7 pian chassis Type 30-C Replaces 7 pian perspex illumin Type 100 Replaces 7 pian chassis Type CVC8-9 Replaces 5 rectu SELECE FASCIA/MOUNT	PROGRAMME SELECTOR VARICAP TUNING Regd. Design No. 1006611
WORKING Quality, Hig Colour Tubes Oelta Oelta Out 20" Out 0	TV'S WOR FREE DELIVEI on eyear guarantee (optional extension up to three years) £26 £30 £32 £33 £33 £36 £38 £40 (AT for optional guar tube. IO TUBES (One Year 12, A61-120W/R £13, tubes exchange glass DWING ITEMS CALL colour TV's, with we rantee on tubes) from rg TV Panels at Reasc tubes with scratch pourpose built polishin our pose built polishin tube. o 40 miles from Lut y for tube orders ove o all prices. Callers w prehensive price list Tube Types that can l 1 Sat 9am-5pm. Tel. 0582- Widdx. Tel. 9684-27019 (, Chesham, Buckingharr shden, Northants. Tel. 03272 (), Northants. Tel. 03272	POLISHING KING PANELS RY* re Reprocessing Two year guarantee (optional extension up to four years) £29 £33 £35 £36 f42 £44 £44 £46 rantee on any type of colour Guarantee) Mono Portables £16 s required. ERS ONLY Il view tubes fitted (1 year only £45 onable Prices es or small chips, can be ng equipment. Only £7 per ton. Fixed Charge £3. *Free er £50 + VAT. velcome. Please phone first. and a wall chart of approx be processed by us. 114-134 Midland Rd. uton, Beds, -10787	UNIVERSAL FOR Way interlocked d.p. switch 100 K tuning potentiometers Top quality through hole plated pcb Dimensions: 5' by 3'' by 1'' Ideal for replacement when original parts are obsolete or unobtainable Template guide supplied for drilling of your own fascia design Range of pre-cut and drilled fascia/mounting kits for selected TV chassis enabling our unit to be fitted without further cutting drilling or modification All orders despatched same day DIRECT REPLACEMENT FA Type 30-80 Replaces 7 plan chassis Type 30-02 Replaces 7 plan chassis Type 20-02 Replaces 7 plan chassis Type CVC8-9 Replaces 5 rectu SELECT FASCIA/MOUNT	PROGRAMME SELECTOR VARICAP TUNING Regd. Design No. 1006611

TELEVISION AUGUST 1983

-



C

				Plus stock to			
AC127	0.150	B FX88	0,150	2N3771	0.900	741C8	0.150
AC128	0.150	BFY50	0.140	2N3772	0.950	NE555	0.180
AC187	0.150	BFY51	0.140	2N3773	1.000	LM3900	0.250
AD149	0.480	BT106	0.900	LM309K	1.000	7400	0.110
AD161	0.220	BT116	0.900	7805	0.350	7401	0.110
AD162 AF139	0.220	BT119	1.100 1.100	7812 7818	0.380	7402 7405	0.120
AF239	0.220	BT120 BU126	0.700	7824	0.380	7405	0.200
AU106	1.000	BU205	0.750	7905	0.350	7413	0.190
AU110	1,100	BU208	0.800	78L05	0.300	7414	0.260
BC107	0.070	BU208A	0.850	78L12	0.300	7425	0.110
BC108	0.070	BU326	0.850	78L18	0.300	7441	0.300
BC109	0.070	BU407	0.750	78L24	0.300	7442	0.300
BC147	0.055	BU526	0.800	2SC495	0.700	7447	0.400
BC148	0.055	BY127	0.080	2SC1306	1.000	7473	0.190
BC149 BC157	0.055 0.055	BY133 BY164	0.080	2SC1969 2SC2029	1.300 1.200	7474 7475	0.180 0.150
BC157	0.055	0A47	0.060	2SC2078	1,200	7485	0.300
BD131	0.250	0C28	1.000	MB3712	1.500	7486	0.160
BD132	0.250	ŎČ29	0.800	TA7205	1.500	7489	1,100
BD135	0.200	0C35	1.000	UPC575	1.000	7490	0.220
BD136	0.200	R2008B	0.800	LM380	0.500	7493	0.250
BD137	0.200	R2010B	0.800	LM381A	0.600	74123	0.160
BD138 BD139	0.200	TBA520 TBA530	0,750 0,750			74141 74393	0.250 0.500
BD140	0.200	TBA550	0.750			74LS09	0.120
BD144	1.100	TBA550	0.750	VALVE	s	74LS164	0.300
BD150	0.300	TBA560	0.700	DY802	0.450	741 \$107	0.350
BD157	0.380	TBA800	0.350	ECC82	0.400	74LS221	0.420
BD158	0.380	TBA810S	0.600	ECC83	0.430	/4LSZ40	0.580
BD159	0.400	TBA820	0.750	ECC84	0.400	74LS244	0.580
BD166 BD175	0.300 0.300	TBA920 TBA950	0.800 0.800	ECC85	0.400	SOCKET	e
BD177	0.300	TBA990	0.800	ECH81 ECH84	0.520	8 PIN	0.070
BD179	0.320	TCA800	0.800	ECL80	0.570	14 PIN	0.080
BD181	0.450	TCA940	0.850	ECL82	0.590	16 PIN	0.090
BD433	0.320	TDA1170	0.900	FCL84	0.570	18 PIN	0.120
BD535	0.400	TDA2522	0.800	ECL85	0.570	20 PIN	0.140
BD536	0.400	TDA2530	0.800	ECL86	0.490	22 PIN	0.160
BD537 BD538	0.420 0.420	TDA2532 TDA2540	0.750	EF80 EF85	0.310 0.340	24 PIN 28 PIN	0.180 0.200
BDX65	0.800	TDA2540	0.700	EF89	0.430	40 PIN	0.250
BF180	0.160	TDA2593	0.800	EY86	0.310	10 1111	012.00
BF181	0.180	TDA2640	0.800	EY87	0.310	LED	
BF194	0.050	TIP29	0.150	PC97	1.000	3mm Red	0.050
BF195	0.050	TIP41A	0.220	PCF802	0.570	3mm Yellow	0.100
BF196	0.060 0.060	TIP42A TIP2955	0.220 0.340	PCL81 PCL82	0.540 0.700	3mm Green 5mm Red	0.100 0.050
BF199 BF200	0.060	TIP2955	0.340	PCL84	0.500	5mm Yellow	0.050
BF258	0.180	2N3053	0.180	PCL85	0.550	5mm Green	0.100
BE337	0.200	2N3054	0.400	PCL86	0.550	Shin Green	0.100
BF338	0.200	2N3055	0.320	PFL200	0.850	ELECTROL	TIC
BF362	0.300	2N3440	0.580	PL504	0.950	4700UF-	0.000
BFX87	0.150	2N3442	0.850	PY500A	1.600	16V CAN	0.200
	Please add	40p. P&P and	VAT at 159	6. Govt. College	s, etc. ord	ers accepted.	
	Quotation	ns given for La	arge Quantit	ies. Please allov	v 7 days f	or delivery.	
	All	brand-new Co	mponents.	All valves are n	ew and be	oxed.	
		12	INMIT F	ECTRONICS	:		
	9 THE BRO	ADWAY PRE	STON ROAD	, WEMBLEY, N	IDDLESE	. ENGLAND	
	5 5/10		Telephone	01-904 2093			

TELEVISION AUGUST 1983

TV LINE OUTPUT TRANSFORMERS

- TASTRETONN	
RANK BUSH MURPHY	PHILIPS
Z146 A640 dual std mono 7.0 Bush A792, A793	00 170 series dual std mono 7.00 210 300 series mono 7.00
single std mono 7.0	00 G8 & G9 series colour 8.00
A774 single std mono 7.0 A816 solid state mono 9.0	
	EKCO RV305-769-725-741 8.00
DECCA MS1700 2001 2020 2401mono 7.0	
MS2404 2420 2424 mono 7.0 CS1730 1733 colour 8 0	
CS1830 1835 colour 8.0	
'30'series Bradford colour 8.0 80 series colour 8.0	Kuba, Luxor, Korting, Tyne, Berry
100 series colour 8.0	
FERGUSON HMV MARCON	
1600 9.5	RANK BUSH MURPHY
G.E.C.	
2047 to 2105 7.0 2000 to 2064dual std mono 7.0	0 Z7i8 series primary 6.00
DUAL STD hybrid colour 11.0 SINGLE STD hybrid colour 10.0	Z718 series EHT overwind 7.00
-	ULTRA THORN
Indesit 20EGB 24EGB mono 9.0	0 1690 1691 EHT overwind 7.00 1590 overwind 5.00
KB-ITT	1615 winding 7.50
VC200 VC205 VC207 mono 7.0	
CVC5CVC7CVC8CVC9 col. 8.0 CVC20 series colour 8.0	6 G6EHT 8.00
CVC30 CVC32 series colour 8.0	G6 primary 6.00
PRICES INCLUD	E PYE
P. & P. & 15% VA	
All lopts and windings	are new and guaranteed
Open MonFri. 9 to 5.30 pm	
Delivery normally by return.	S.A.E. all enquiries Barclaycard and For orders
PAPWORTH	Access welcome at the
TRANSFORME	VICA Trans
80 Merton High Street	cash
London SW191BE	01-540 3955

VIDEO CASSETTE RECORDER SERVICING COURSE

3 WEEKS

(25th JULY TO 12th AUGUST)

Intensive course intended for qualified TV Service Engineers who have a sound knowledge of Colour TV principles — some previous background of VCR principles would be advantageous.

Training includes theoretical concepts together with practical project and fault diagnosis work on state of the art VCR's using electronic test and mechanical alignment equipment.

On successful completion of the course a Technician Education Council 'Record of Success' will be awarded.

(Also courses of between 6 months and 15 months in Electronic Equipment Servicing — TV/Video, Computers, Microprocessors and Robotics leading to Technician Education Council Certificate and/or Higher Certificate awards.

Further details from:

LONDON ELECTRONICS COLLEGE (Dept T3/4)

20 Penywern Road, Earls Court, London SW5 9SU Tel: 01-373 8721

N.J. ELECTRONICS, ^{82 – 84} STORFORTH LANE TRADING ESTATE, HASLAND, CHESTERFIELD, DERBYSHIRE S41 OSN Tel. CHESTERFIELD (0246) 209079

TELEVISIONS: We have over 600 Televisions is stock with prices from £10.00, Please ring for price and availability on various models VIDEO PANELS: Ferguson 3V23 Panels (NEW) Price on application.

PUSH BUTTONS	_	LINE TRANSFORMERS		PHILIPS 570	£9.50 £9.50
DECCA 30 4 way	£6.00	AUTOVOX 90° AUTOVOX 110°	£9.75 £9.75	PHILIPS 210 PYE 691 P.C. PYE 725	
DECCA 30 6 way GEC 2110 6 way	£7.96 £8.40	DECCA 1700	£9.80	PYE 731	£9.50
GEC 2112 7 way	£13.10	DECCA 1830	£9.50	PYE 169 mono RRI A640/793	£9.30 £9.90
GEC 2136 6 way ITT CVC5 7 way		DECCA 2230 DECCA 80	£8.30 £7.20	RRI Z774	£11.50
ITT CVC8/9	£14.00	DECCA 100	£7.50	RRI T20 SABA	£11.95
ITT CVC20/30 ITT CVC25	£7.96 £8.05	GEC 2110 GEC diode split	£9.65 £12.00	SKANTIC	£14.00 £13.98
PHILIPS 520	£12.50	GRUNDIG 1500	£13.70	THORN 1590/1	£9.70
PHILIPS 550	£13.55	GRUNDIG 6011	£11.50	THORN 1615 THORN 1690/1	£9.20 £8.45
PHILIPS G11 TIP SWITCH	£23.00	ITT CVC5/8 ITT CVC20	£10.00 £8.50	THORN 1500 20"	£7.00
PYE 713 4 way	£9.15	ITT CVC30/32	£8.50	THORN 1500 24" THORN 9600	£7.00 £12.00
PYE 715 6 way PYE 725 6 way	£12.98 £12.98	ITT CVC40 ITT CVC45	£12.50 £8.50	THORN 9800	£19.10
RRI 823 4 way	£8.75	INDESIT mono	£10.60	EHT TRAYS	
RRI 823 6 way RRI T20 6 way	£9.45 £9.35	KORTING 90° KORTING 110°	£11.00 £9.95	DECCA 1830	£4.30
RRI Z718 6 way	£9.90	PHILIPS G8	£8.50	DECCA 2230	£6.50
TELPRO 4 way THORN 3500	£7.90 £3.50	PHILIPS G9 PHILIPS G11	£9.00 £12.75	DECCA 80 DECCA 100	£5.95 £6.00
THORN 9000	£4.00	PHILIPS K30	£12.75	THORN 9000	£7.80
THORN 1615	£9.15	КТЗ	£6.60	SIEMENS Universal	£6.16

This is only a fraction of our stock, please send large SAE for our FREE Comprehensive Catalogue. Please add 65 pence post/packing plus 15% VAT to all orders. Goods are despatched on the same day that we receive your order by first class post and should be received within four days.

COLOUR TELEVISION & MUSIC CENTRE

WE HAVE MOVED TO A NEW WAREHOUSE

35 Stafford Road, Weston Super Mare, Avon.

(15 mins. past Bristol on M5)

NOT EX-RENTAL

COLOUR TELEVISIONS SOLID STATE

★ FANTASTIC OFFER ★

All in perfect running order

PYE CHELSEA 18", 6 Button, Sliding Controls, Brilliant Condition

£39.50

THE ABOVE ARE WORKS MODIFIED FOR MOST PARTS OF THE WORLD VHF - UHF

PYE 721 20"-26", could be mistaken for new

£57.00 each

PYE 725 20" as new

£69 each

Minimum 5 sets

★ ★ ★ BIG REDUCTIONS FOR EXPORT ORDERS OVER 100 SETS ALL OTHER MAKES IN STOCK OFF THE PILE

* * *

(G.E.C., SOLID STATE, FERG 9000 & 8500, G's, DECCAS etc.)

Ring Now: W.S.M. 413537

TOP TWENTY T.V. SPARES STOCK NO. 001 Philips G8 Loptx (Genuine Philips) 002 Decca 30 series Loptx (Genuine Decca) 003 Decca 100 series Loptx (Genuine Decca) 004 ITT CVC 25/30/32 Loptx (Genuine ITT) 070 10 × BU208A 050 ITT CVC 5/9 EHT Tray 051 Decca 1730/1830 Doubler 053 GEC 2040 Hybrid EHT Tray 054 Thorn 1500 (5 Stick) EHT Tray 055 Thorn 8000 Doubler 056 HTT ITay 057 Philips G9 EHT Tray 058 ITT Universal EHT Tray 059 ITT CVC 5/9 CHT Tray 050 TTT CVC 5/9 EHT Tray 051 Decca 1730/1830 Doubler 055 Thorn 8000 Doubler 056 Thorn 1500 (5 Stick) EHT Tray 057 Philips G9 EHT Tray 058 ITT Universal EHT Tray 059 A00 FD 250V Philips G11 051 S00 X BY127 Diodes 052 3.00 053 50 × BY127 Diodes 050 25 × 2N3055	001 Philips G8 7.50 066 P 002 Deccs 30 Series 7.00 067 K 006 PK 003 Deccs 100 Series 5.00 066 D 066 E 004 ITC CVC 25/30/32 7.00 007 RRI C20 087 K 005 Philips G9 7.50 086 C 006 RRI 120 11.62 000 RRI 2718 18" 18.95 007 RRI A823 7.00 081 2 083 3 008 RRI 2718 18" 18.95 083 3 084 2 008 RRI 2718 109/31 7.00 300 084 2 084 2 084 2 011 Thorn 1690/31 7.00 3000 084 2 087 088 087 3 012 Thorn 1615 6.50 085 013 1TT CVC 5/9 6.50 087 3 087 4 013 Phorn 9500/9002 8.50 092 103 088 0900 011 Thorn 3500 28.00 084 094 5 0900 013 7 horn 3500 208 4.50 085 092 022 17 horn 8500 11.00 033 02.00 097 1 033 598 1004 EHT T350 0850 098 5 086 5 021 Thorn 3500 520 11.004 EHT T350 085 00 084 099 5 096 5 097 5 098 5 051 Decca 1730/1830 2.00 097 11 051 095 11T CVC 5/9 3.00 054 THT T350 150 00 051 055 Thorm 8000 100 055 00 055 00 055 050 00 055 050 00 0	ye C1200 5 Lead 4.50 12: ording Hybrid 5.00 12: ording Hybrid 5.00 12: Ording Albrid 5.00 12: CAPACITORS 12: 220/400 CVC 32- W: 200 + 300 Pye 681/ 12: 200 + 100 Poilions 68 1.99 IN 175 + 100 + 100 Thorn 14 470 / 250 Philips 14 400 + 400 Poil 20: 200 + 150 14 470 / 250 Philips 14 400 + 400 Poil 20: 200 + 150 14 400 + 400 Poil 20: 200 + 150 14 400 + 400 Poil 20: 200 + 150 14 10 × 220 AF 16V 15 5 × 91NF Philips 10 5 × 91NF Philips 10 5 × 91NF Philips 10 5 × 1/250 Suppres- 5 × 1/250 Suppres- 5 × 1/250 Suppres- 5 × 1/250 Suppres- 5 × 1/250 Suppres- 7 713 4 Way 7.87 17 797 7156 Way 11.95 11 Philips G8 13	$ \begin{array}{cccccccccccccccccccccccccccccccccccc$	TRANSISTORS - DIODES 235 50 × BC213L 2.50 250 10 × BD124 9.00 270 10 × BU208A 9.00 271 10 × BU208 9.00 271 10 × BU208 9.00 271 10 × BU208 7.50 273 5 × BU205 7.50 281 10 × 2N2905 (Fexus) 281 10 × 2N2905 (Fexus) 281 10 × 2N2905 (Fexus) 350 Thorm 1590/1 41×22 2.00 352 Thorm 1590/1 41×22 2.00 352 Thorm 1500/1 42×22 2.00 352 Thorm 1500 363 5 × Thorm 350 370 Pye 731 Thick Film 1.00 370 Pye 731 73/731 Vis. Gain 6.50 372 Pye 731 3R3 50W Medule 373 Thord 1.02 374 For Pye 713/731 Vis. Gain 1.03 375 Forundig 5010/6010 Video Module 9378 Grundig 5010/76010 1.04 384 5 × Philips 63 1.02 385 5 × Philips 6	$\begin{array}{cccccccccccccccccccccccccccccccccccc$
All components are A1 quality from prime manufacturers, and are dispatched by post same day as order received together with any refund due. All goods should be deliv- ered within 4 working days. <i>Please add 15% VAT and 90p P & P</i>	058 ITT Universal 5.00 113 059 5 XV11 For (Slop PTV's 1.00 114 100 114 060 3 XTV45 Z718 115 REC 1.00 114 116 106 061 TKC2 5.00 117 100 062 TVK52 Continental 2.50 118 117	Philips G8 11 ving) 12.98 10 Thorn 9000 6 Way2.50 11 Inorn 1615 4 Way5.75 1 Decca 6 Way 6.95 11 Decca 4 Way 6.95 11 Decca 4 Way 6.95 12 Decca 4 Way 6.95 12 Decca 2 Way 7.95 2 Decca 106 // Tapered (6 2	183 TDA2571 2.15 184 TDA2591 0.98 185 TDA2593 2.23 190 TDA2600 4.00 191 TDA2611 1.24 192 TDA2640 2.35 210 ETTRB016 2.26 211 ETTR016 2.26 211 ETTR018 2.34	Log. Color 2.50 388 5 × Philips G8 47k Log. Vol. 2.50 389 Philips G8 Plastic Mains Sw. 0.75 390 Philips G8 Metal Mains Sw. 1.23 391 Philips G8 Line Eql/ Stor. Coil 2.25	Skt. 5.50 483 10 × Metal Coax Plug 1.70 1.70 484 Focus Unit T20 Type 1.25 485 Focus Unit Thom 485 Focus Unit Thom 8500 Type 1.25
3400 EHT 19.50 GEC 2110 6 B +0 3100 +3300 GEC 2136/1 GEC 2136/1 3400 12.00 GEC 2136/1 B +0 3500 +3800 GEC Convert 4000 +5000 4000 +5000 2113 +2 6000 Decca 30 9.50 Hitachi 190 4 Decca 100 8.00 ITT CVC 5 7 Decca 1700 9.00 ITT CVC 20 - Dymetron TV202 +203 11.00 ITT CVC 25	DN HOUSE, MU ERS STRICTLY BY VAY' Dy return TONS +20 Mono 4 way -30 +80 +100 6 way -30 +30 +30 +30 +321 +2144 119 +2121 +2144 119 +2121 +2144 119 +2121 +2144 119 +2121 +2144 119 +2121 +2144 119 +2121 +2144 119 +2121 +2144 119 +2121 +2144 119 +2121 +2144 119 +2121 +2144 148 way 8.50 6 way 10.50 6 way 10.50 6 way 12.50 +30 +32 6 way 7.40 VCR 6 way 8.50	APPOINTM	FORD, SAL ENT. PLEASE ON'S LARGEST with over "TEL ACONDON E LONDON E TEL IAKES IN S OVER 22" CI S 22" G8 (Tea	OP. QUOTE STOC TELEVISION WI 4 ¹ / ₂ thousand sq. EMAAN HODA STREET Bethnal Green Road) .2. FREE CAR : 01-739 2707 TOCK AND G COMPLETE DLOUR FROM	AND. HOLESALER feet. Y'' PARK GUARANTEED ET.50 EEL OF TEN £12
Grundig 5010UE Philips 68 53 6010UE + 2222 12.00 Philips 68 53 Grundig 5010 12.00 Pye 713 + 711 Grundig 1500 15.00 Pye 713 + 711 Grundig 5010 EHT 19.50 Pye 725 6 w ITT CVC 5 9.60 Rank A823 4 ITT CVC 45 8.50 Rank A823 6 Philips G8 8.50 Rank Z718 6 Philips 210 Mono 10.75 Salora 5 was Philips 570 9.50 Skartic/Luxc Pye 189 + 569 + 769 10.00 Teipro 4 was Pye 891 + 697 PCB 14.25 Torn 9000 5 Pye 913 + 151 + 717 9.50 Storn 9 was	20 Square 10.50 50 Stoping 16.50 54 way 8.00 7 Chelses 6 way 12.50 way 9.00 way 9.00 way 9.00 way 9.00 way 9.00 way 12.50 way 9.50 way 12.50 y 10.00 y 10.00		- SINGI EEE DELIVERY TELEPHONE DEO HI QUALITY UNIVER	E STANDARD TO THE LONE 01-739 2707	
Pye 725 10.20 TUNER Pye 731 +735 +737 +741 10.50 ELC 1043/06 Rank 720A 11.50 ELC 1043/06 Rank 774 11.00 CAPACITOR Rank 7718 23.00 G11 470mfd/ Rank 7718 20 +22 +26" 23.00 G11 470mfd/ Rank 7718 20 +22 +26" 23.00 G11 470mfd/ Rank Mono Portable 14" 9.50 INTEGRATE Tandberg 110° 11.25 TA7607AP Thorn 1590 +1591 10.90 TAA550 Thorn 1615 9.00 TDA2540 Thorn 1690 +1691 8.50 TDA5513	1.60 /250v Elco	VHS F VHS F BETA REPL	Part No. 3HSS (Part No. 4HSS (1 MAX Part No. P ACEMENT KIT SE ADD 15% V.A FULL CATALOGI	5mm Centre Hole) 5mm Centre Hole) S3B (14 Pieces Boxed) .T. PLUS P. & P. £1 JE AVAILABLE ON ADS - MOTORS -	£29.95 EACH £38.95 EX. £ 8.25 V.A.T. .50 PER ORDER REQUEST.

NORTHERN T.V. DISTRIBUTORS

NEW TRADE WAREHOUSE NOW OPEN!! GOOD QUALITY SETS AT GOOD PRICES

OFF THE PILE	WORKING
£25.00	£35.00
£23.00	£30.00
£14.00	£22.00
£13.00	£20.00
£18.00	£28.00
£40.00	£60.00
£25.00	£35.00
£25.00	£35.00
i. etc	
£10.00	
£2.00	
	£25.00 £23.00 £14.00 £13.00 £18.00 £40.00 £25.00 £25.00 £25.00 £25.00

UNIT 2. PERTH COURT TEAM VALLY IND. ESTATE GATESHEAD, TYNE & WEAR Tel. Newcastle 875389

CENTREVISION

NO. 1 IN WALES

2000 + CTV

9000 Sq Ft

★ DECCA 18" £20 + VAT

★ KORTING 22-26 CTV £15 + VAT ★ HITACHI CTV FROM £32 + VAT ★ THORN 9000 20" £48 + VAT

★ RANK Z719-Z718-T20 VARIOUS PRICES ★ PHILIPS 550 22" REMOTE £35 + VAT ★ GEC SOLID STATE FROM £32 + VAT ★ THE TRADE SAY THE BEST QUALITY SETS ON THE MARKET TODAY

★ BULK TERMS TO OTHER WHOLESALERS ★ ALSO PANEL'S-STANDS AND TUBES

DECCA 30 SERIES 22" IN 10'S £18 SELECTION OF WORKING SETS DONT DELAY PHONE TODAY 0222-44754 **CENTREVISION HOUSE** SLOPER ROAD. CARDIFF CF1 8AB.

Some Inline sets also available

I.E. -ITT, C.V.C. 25 & 30 Bush T20 & T22 Thorn 9000 etc

> All prices subject to availability of stock

Sets also available at our **Birmingham Branch:**

811 WASHWOOD HEATH ROAD WARD END **BIRMINGHAM 8 2NP** Tel: 021-784 2561

If the Transformer you	ı requ	Allow up to 28 days for ire is not listed please p	hone.
RANK BUSH MURPHY		DECCA	C
Z146 A640 dual std mono	8.51	MS1700 2001 2020 2401 mono	8.00
Bush A792, A793 single std mono		MS2404 2420 2424 mono	8.00
A774 single std mono	8.50	1210 1211 1511 portable	11.50
A816 solid state mono	9.00	GYPSY portable	11.50
Z712 T16a T16b mono portable	9.00	CS1730 1733 colour	8,00
A823 A823b A823av colour	10.00	CS1830 1835 colour	8.00
ZITS ZIZZ Series colour	10.00	'30' series BRADFORD colour	8.00
T20a T22 series colour	10.00	80 series colour	8,00
		100 series colour	8.00
WINDING		PHILIPS	
T20A T22	5.51	210 300 series mono	8.00
	_	320 series solid state mono	8.50
G.E.C.		G8 series colour	8.00
2047 to 2105 3112 to 3135	8.00	G9 series colour	8.50
"GAIETY" FINELINE	8,00	G11 series colour	14.98
2114 portable mono	8.00	KT2 Lopt	9.00
3133 3135 M1501H portable mono	8.00	KT3 Lopt	10.60
DUAL STD hybrid colour	11.00	KB-ITT	
SINGLE STD hybrid colour	10.00	VC200 VC205 VC207 mono	8.00
	8.50	VC300 VC301 VC302 portable	8.00
or 110°		CVC1 CVC2 colour	9.00
		CVC5 CVC7 CVC8 CVC9 colour	9.00
FERGUSON HMV MARCONI		CVC20 series colour	9.00
1590 1591 1592 1593 mono	8.00	CVC30 CVC32 series colour	8.00
1612 1613 1712 mono	8.00	CVC40 series	14.56
1690 1691 mono	8.50		
1600 1615 series mono	9.74	L.O.P.T TESTER	
	8.58	Total Price Including VAT,	£16.79
8000 8500 8800	11.70	Tidman Mail Order	l td
	11.52		
9500 9600 9650	9.56	236 Sandycombe Ro	
9800 TX9 TX10	P.0.A.	Richmond, Surrey	
		Approx. 1 mile from Kew B	
INDESIT, GRUNDIG, TANDBU	JRG,	Phone: 01-948 370	
Best will be strong to the str			
TELEFUNKEN, FIDELITY,		Mon-Fri 9 am to 12.30 pm	1.
TELEFUNKEN, FIDELITY, KORTING, TYNE, B+O. Price on application.		Mon-Fri9 am to 12.30 pm 1.30 to 4.30 pm. Sat 10 am to 12 pm.	1.

TELEVISION AUGUST 1983

IN STOCK

VISIONTEL BEST QUALITY EX RENTAL SETS FR £10 HERE IN CENTRAL LONDON Hundreds of sets always in stock AT VERY COMPETITIVE PRICE ! JUST ARRIVED	S					
VHS VIDEO RECORDERS						
We also have PYE, DECCA, GEC, ITT, GRUNDIG, JVC, PHILIPS G9 + G11, THORN 9000 and MANY MORE						
	7					
FOR FURTHER DETAILS TELEPHONE 328 378 OR COME ALONG TO						
55 KILBURN HIGH ROAD, NW6						
	I					
TELEVISION TUBE SHOP LTD						
BRAND NEW TUBES AT CUT PRICES	ORE					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W19.95 230DB4CT46831.00 A31-120W/200W1795 240DB4/240AB4A 22.00 From £20. Guaranteed Com	plete.					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W19.95 230DB4CT46831.00 A31-120W/300W17.95 240DB4/240AB4A22.00 A31-410/510W17.95 CT507 equiv21.95	plete. from £3.					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W 19.95 230DB4CT468 31.00 A31-120W/300W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 CT507 equiv 21.95 A34-100W/510W 310DGB4/DMB4 23.00 Mono's and non-complete sets A34-514W 310EUB4 19.95 QUALITY COLOUR TUBE	plete. from £3. E S					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W 19.95 230DB4CT468 31.00 A31-120W/300W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 CT507 equiv 21.95 A34-100W/510W 18.50 310DGB4/DMB4 23.00 A34-514W 24.25 310EUB4 19.95 A38-160W/170W 310EUB4A 18.50 310EYB4 A14 120W//P 25 00 310EYB4 18.75	plete. from £3. E S ibes.					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W 19.95 230DB4CT468 31.00 A31-120W/300W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 CT507 equiv 21.95 A34-100W/510W 18.50 310DGB4/DMB4 23.00 A34-514W 24.25 310EUB4 19.95 A38-160W/170W 17.50 310EUB4 18.50 A44-120W/R 25.00 310FXB4 17.50 A50-120W/R 19.00 310FXB4 17.50	plete. from £3. ES ibes.					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W 19.95 230DB4CT468 31.00 A31-120W/300W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 240DB4/240AB4A 22.00 A34-100W/510W 18.50 310DGB4/DMB4 23.00 A34-514W 24.25 310DCB4/DMB4 23.00 A34-514W 24.25 310EUB4A 19.95 A38-160W/170W 17.50 310EUB4A 18.50 A44-120W/R 25.00 310FXB4 17.50 A50-120W/R 100GNB4A 31.00 310HCB4 A61-120W/R 21.00 310HCB4 31.00	plete. from £3. E S ubes.					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W 19.95 230DB4CT468 31.00 A31-120W/300W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 240DB4/240AB4A 22.00 A34-100W/510W 18.50 310DGB4/DMB4 23.00 A34-514W 24.25 310DCB4/DMB4 23.00 A34-514W 24.25 310EUB4A 19.95 A38-160W/170W 17.50 310EUB4A 18.50 A44-120W/R 25.00 310FXB4 17.50 A50-120W/R 100GNB4A 31.00 310GNB4A A61-120W/R 21.00 310HCB4 31.00 A61-120W/R 21.00 340A YB4 30.00 A40A YB4	plete. from £3. ES ubes.					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W 19.95 230DB4CT468 31.00 A31-120W/300W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 CT507 equiv 21.95 A34-100W/510W 18.50 310DGB4/DMB4 23.00 A34-514W 24.25 310EUB4 19.95 A38-160W/170W 17.50 310EUB4 18.50 A30EVJAW/R 25.00 310EUB4A 18.50 A44-120W/R 25.00 310FXB4 17.50 A50-120W/R 19.00 310GNB4A 31.00 A61-120W/R 21.00 340AB4 22.50 190AB4/C4 340AYB4 30.00 340AYB4 30.00 Some Rebuilt Japanese 340RB4/CB4 26.00 340RB4/CB4 26.00	plete. from £3. ES ubes.					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W 19.95 230DB4CT468 31.00 A31-120W/300W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 CT507 equiv 21.95 A34-100W/510W 18.50 310DGB4/DMB4 23.00 A34-514W 24.25 310EUB4 19.95 A38-160W/170W 17.50 310EUB4A 18.50 310EUB4A 18.50 310FXB4 17.50 A44-120W/R 21.00 310FXB4 17.50 A50-120W/R 100 310GNB4A 31.00 A61-120W/R 21.00 310GNB4A 31.00 A61-120W/R 23.00 340A XB4 30.00 340A XB4 30.00 340A XB4 26.00 340A HB4 26.00<	plete. from £3. ES ubes.					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W 19.95 230DB4CT468 31.00 A31-120W/300W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 CT507 equiv 21.95 A34-100W/510W 18.50 310DGB4/DMB4 23.00 A34-514W 24.25 310EUB4A 18.50 A38-160W/170W 17.50 310EUB4A 18.50 A38-160W/170W 17.50 310EVB4 18.75 A44-120W/R 25.00 310FXB4 17.50 A10FXB4 17.50 310FXB4 17.50 A10FXB4 100 310HCB4 30.00 A61-120W/R 21.00 340AB4 22.50 190AB4/C4 23.00 340AB4 22.50 Available from £14.00 + VAT £2.10 340AB4 26.00 Available from £14.00 + VAT £2.10 AVAT £2.10	plete. from £3. ES ubes.					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W 19.95 230DB4CT468 31.00 A31-120W/300W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 CT507 equiv 21.95 A34-100W/510W 18.50 310DGB4/DMB4 23.00 A34-514W 24.25 310EUB4A 18.50 A38-160W/170W 17.50 310EUB4A 18.50 A38-160W/170W 17.50 310EUB4A 18.50 A34-120W/R 25.00 310FXB4 17.50 A10FXB4 17.50 310GBB4A 31.00 A50-120W/R 19.00 310GRB4A 31.00 A61-120W/R 21.00 340AB4 22.50 190AB4/C4 340AB4 26.00 340AXB4 30.00 340AB4/CB4 26.00 340AHB4 26.00 340AB4 26.00 Recorditioned and VB4/CB4 26.00 340AHB4 26.00 TRADE	plete. from £3. ES ubes. (ABLE) ble.					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W 19.95 230DB4CT468 31.00 A31-120W/300W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 CT507 equiv 21.95 A34-100W/510W 18.50 310DGB4/DMB4 23.00 A34-514W 24.25 310EUB4A 19.95 A38-160W/170W 17.50 310EUB4A 18.75 A38-160W/170W 17.50 310EVB4A 18.75 A50-120W/R 1000 310FXB4 17.50 A50-120W/R 1000 310FXB4 22.50 190AB4/C4 21.82 340AB4 22.50 190AB4/C4 23.00 340AYB4 30.00 340AXB4 26.00 340AYB4 26.00 Recorditioned and used ture From £10 Guaranteed. Don't delay, ring today. 340AXB4 26.00 Atom Papese Available from 24.00 A 6" £14.00 + VAT £2.10 COLOUR TUBES	plete. from £3. ES ubes. ABLE) ble.					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W 19.95 230DB4CT468 31.00 A31-120W/300W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 CT507 equiv 21.95 A34-100W/510W 18.50 310DGB4/DMB4 23.00 A34-514W 24.25 310EUB4A 19.95 A38-160W/170W 17.50 310EUB4A 18.50 A38-160W/170W 17.50 310EYB4 17.50 A10GB4/DB4A 17.50 310EYB4 18.75 A50-120W/R 21.00 310FXB4 17.50 A10GB4/C4 23.00 340AYB4 22.50 190AB4/C4 23.00 340AYB4 26.00 A40AXB4 26.00 340AXB4 26.00 Available from £14.00 + VAT £2.10 A56-120X £54.00 COLOUR TUBES A56-120X £54.00 A30AB22 73.50 A56-410X 64.00 A44-271X 60.00	plete. from £3. ES ubes. (ABLE) ble.					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W 19.95 230DB4CT468 31.00 A31-120W/300W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 CT507 equiv 21.95 A34-100W/510W 18.50 310DGB4/DMB4 23.00 A34-514W 24.25 310EUB4A 19.95 A38-160W/170W 17.05 310EUB4A 18.50 A50-120W/R 19.00 310FXB4 17.50 A50-120W/R 19.00 310GBB4A 31.00 9AGP4 £21.82 340AB4 22.50 190AB4/C4 23.00 340AYB4 30.00 340AYB4 30.00 340AYB4 30.00 Some Rebuilt Japanese & European Types Available from 14.00 £14.00 + VAT £2.10 COLOUR TUBES COLOUR TUBES (NEW & MULLARD/THORN COLOREX)* 12VARP22 £62.50 A56-120X £54.00 330AB22 73.50 A56-410X	plete. from £3. ES ubes. (ABLE) ble.					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W 19.95 230DB4CT468 31.00 A31-120W/300W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 C507 equiv 21.95 A34-100W/510W 18.50 310DGB4/DMB4 23.00 A34-10W/70W 17.50 310EUB4 19.95 A34-10W/R 24.00 310EUB4 19.95 A34-10W/R 25.00 310EUB4 18.50 A34-120W/R 25.00 310FXB4 17.50 A50-120W/R 19.00 310FCB4 31.00 A61-120W/R 21.82 340A B4 22.50 190AB4/C4 23.00 340A YB4 30.00 340A AB4 26.00 REuropean Types Available from Available from 21.400 + VAT £2.10 340A AB4 26.00 Some Rebuilt Japanese A56-120X £54.00 A56-120X A44-271X 60.00 A56-120X £54.00 A47-342X 61.00 A56-120X £54.00	plete. from £3. ES ubes. (ABLE) ble. (ABLE) ble. (FABLE) ble. (Sar TVs. kes and tube (Sare refur-					
BRAND NEW TUBES AT CUT PRICES A31-19W/20W 19.95 230DB4CT468 31.00 A31-120W/300W 17.95 240DB4/240AB4A 22.00 A31-410/510W 17.95 CT507 equiv 21.95 A34-100W/510W 18.50 310EUB4A 23.00 A34-514W 24.25 310EUB4A 19.95 A38-160W/170W 17.50 310EUB4A 18.50 310EUB4A 106XB4 17.50 A50-120W/R 100GB4A 31.00 A61-120W/R 21.00 310GRB4A 31.00 A61-120W/R 21.00 310HCB4 22.50 190AB4/C4 23.00 340AXB4 22.50 190AB4/C4 23.00 340AXB4 26.00 Available from £14.00 + VAT £2.10 340AXB4 26.00 NEGONDA 6" 14.00 Tel. (0582) 68934 Tel. (0582) 68934 Tel. (0582) 68934 Tel. (0582) 68934 Tel. (0582) 68934 330AB22 73.50 A56-120X £54.00 330AB22 73.50 <th>plete. from £3. ES ubes. (ABLE) ble. V LTD. r TVs. kes and tube /s are refur- standard.</th>	plete. from £3. ES ubes. (ABLE) ble. V LTD. r TVs. kes and tube /s are refur- standard.					

Old Bulb Required for 110° Colorex ADD 15% VAT TO ALL THE ABOVE PRICES.

ALL TUBES TESTED BEFORE SALE & FULLY GUARANTEED TELEVISION TUBE SHOP LTD 52 BATTERSEA BRIDGE RD., LONDON, SW11. Tel. 228 6859/223 5088 CARRIAGE: Mono £3, Colour £10.

TELEVISION AUGUST 1983

ALL IN GOOD WORKING ORDER.

PRECISION VISION LTD

67 London Road, Headington, Oxford

Phone: 0865 750212

,

THE NO. 1 SOURCE IN THE SOUTH GOOD STOCKS OF MODERN COLOUR UNBEATABLE PRICE AND QUALITY DON'T DELAY RING TODAY TELETRADERS ST. LEONARDS WAREHOUSE ST. LEONARDS ROAD, NEWTON ABBOT, DEVON Telephone: (0626) 60154	1983 PRICE LIST DISPLAY ELECTRONICS GOLD LABEL COLOUR TUBES 2 YEAR GUARANTEE 90° up to 19″
	The above prices are for standard 38mm Delta Gun Types.
A.B.C. TRADE SALES COLOUR T.V.'s Philips G8, Pye, Decca 30's, Thorn's 3000's, 3500's, 8000's Prices start from £12 - Working sets from £20 Hundreds of Mono T.V.'s from £2.00 Jap. sets from £30.00 Special prices for quantity 9,000 sq. feet Warehouse 83 SHOWELL ROAD, BUSHBURY, WOLVERHAMPTON, STAFFS. Tel. Wolverhampton 722637	38mm Delta Gun Types. Add £5 Gun surcharge for 20AX Types. Other in-line & P.I.L. Types, prices on application. GOLD LABEL MONO TUBES 2 YEAR GUARANTEE 19"/20"£12 23"/24"£14 GREEN LABEL COLOUR TUBES 12 MONTHS GUARANTEE 90° up to 19°£28 90° up to 22"£31 90° up to 26"£34
M W ELECTRICAL BROOK PARK AVE. (OFF MARINE RD.) PRESTATYN	Green Label Prices apply only to stan- dard 38mm Delta Gun Types. They will be of particular interest to customers refurbishing ex-rental sets.
"WE DO NOT BOOST TUBES"	
COLOUR TV'S COMPLETE FROM £10.00 TRADE WORKERS FROM £25.00 MINIMUM OF TEN G8, DECCA, BUSH, THORN. ALSO MONOS ETC. NEW & GRADED TVS ALSO AVAILABLE OPEN SAT MORN, LATE NIGHT THURS 8pm TEL: PRESTATYN (07456) 89849/89970	BUDGET CORNER Buy any 5 mixed types take 20% discount. Buy any 3 mixed types take 10% discount. Budget prices apply only to colour tubes. The mix can include Gold & Green Label Types if required.
	CALLERS WELCOME
EMCO – EUROSONIC – GRUNDIG – TELETON + ALL BRITISH MAKES	Late night Thursdays until 8 p.m.
ETC., ETC. ● ALL SPARES READILY AVAILABLE ● IMMEDIATE CREDIT AVAILABLE — TRADE ONLY If you are a trader simply phone for the part you require and we will send it – no quibble – no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf ". e.g. LOPTX – EHT trays – droppers – OSC coils – switches – cans – smoothers – I.C.'s, etc. etc. YOU CAN BE 95% SURE WE CAN SUPPLY ANY TV COMPONENT BY RETURN IF YOU NEED SPARES FAST – RING NOW! ACCESS AND BARCLAYCARD ACCEPTED. Applies to U.K. only.	Saturdays until Midday N.B. Customers intending to collect orders are requested to telephone in advance:- even popular types may be out of stock for short periods. UNIT 1 SWAN WHARF WATERLOO ROAD UXBRIDGE MIDDLESEX
TELEWROW (W'TON) THE TELECENTRE, WORCESTER ST., WOLVERHAMPTON (0902) 773122	Telephone: UXBRIDGE 55800

TELEVISION AUGUST 1983

+-----

+

SETS & COMPONENTS

PHILIPS 550s (Mark 5/Twin Panel/VCR Button) excellent cabinets. Regular supply of working sets. Box T.V. 181

SCRATCHED TELEVISION TUBES, Don't despair, send for repair, 20 years experience. Phone 0507 85300.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs: 0945 384188. Immediate settlement.

A56-120

services.



No other consumer magazine in the country can reach so effectively

those readers who are wholly engaged in the television and affiliated

electronic industries. They have a need to know of your products and





GOOD WORKING COLOUR £25.00, Mono £10.00 No V.A.T! (070682) 7166. Cleaned, polished.

SECOND HAND Colour TV spares and tubes. Most makes. Telephone Southport (0704) 74411. Anytime.

NEW SUSSEX WAREHOUSE, Trade Televisions. Colour from £10, mono £3. Tel. Brighton 673482

JAPANESE COLOUR TVs, Hitachi, Sony, Panasonic, Mitsubishi, Toshiba, Sharp. Colourland TV. Trade Only. 0484 863489.





(No. 1 for s/hand T.V.s)

- 1. 400 sets to choose from.
- 2. Most leading makes sold.
- 3. Fresh stocks weekly.
- Delivery to any part of Ireland.
 All sets with VHF/UHF tuners.
- 6. Colour from only £70 mono from £15.

Visit our new spacious warehouse:

TELE SPARES LTD. Unit 113 Elm Road, Western Ind. Estate, Dublin 12. Tel: 01 521756/521211.

VII(CE PA)

AERIALS

AERIALS & ACCESSORIES

ALTIALS & AUGESSUMIES OUALITY components at competitive prices. UHF 10 element from £1.18. 18 element from £2.20. FM2 from £2.40. FM4 from £4.95. Lashing Kits from £1.20. Wall Bits. from \$5p. Masts available 2' to 20' Aluminium coax plugs from 10p. Coax cable from £9.30. Full range of Accessories and Amplification Equipment available. Comprehensive price list on request. (Trade Only).

S.C.S. AERIALS (Aerial Distributors) 14 Tanners Crescent, Hertford, Herts. SG13 8DS Tel: 0992 50478.

AERIAL BOOSTERS

Next to the set fitting B45H/G-UHF TV, gain about 20dbs, Tunable over the complete UHF TV band, Price £3.70. BII-VHF/FM RADIO, gain about 14dbs, when on the off position connects the senial direct to the radio. Price £7.70. All boosters we make work off a PP3/005p/6F22 type battery or &V-18V DC. P&P 30p per order. ELECTRONIC MAIL ORDER LTD, 62 Bridge St, Remsbottom, Lance BLD 9AG, Tel (070682) 3036 Access/Visa Cards Welcome SAE Leaflets

BOOKS & PUBLICATIONS

IDENTIFY DX-TV SIGNALS IDENTIFY DX-TV SIGNALS The 2nd Edition of "Guide to World-Wide Television Test Cards" by Keith Hamer and Garry Smith is now available. Over 100 countries are featured with 240 photo's of Test Cards, Clock and Identification cap-tions etc., plus additional information on transmis-sion standards, colour systems and Services. Available price £2.35 fully inclusive World-wide (Air Mail: Europe £3.35; Rest £3.70) from:-**HS PUBLICATIONS**

Dept. T(G), 7 Epping Close, Derby DE3 4HR.

COMPLETE FULL-SIZE SETS any published service sheets £2 + LSAE except CTVs/Music Centres from £3 + LSAE. Manuals from 1930 to latest. Quotations, free 50p magazine, price lists, unique technical publications for sale. Repair data/circs almost any named TV/ VCR £8.50 by return. TIST, 76 Church Street, Larkhall, Lanarks ML9 1HE. Phone (0698 883334).

"RADIO AND TELEVISION SERVICING" books, new editions for the last 6 years always in stock. Prices on request. Bells Television Services, 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.

SERVICE SHEETS

COURSES

CONQUER THE CHIP ... Master modern electronics the PRACTICAL way by SEEING and DOING in your own home. Write for your free colour brochure now to British National Radio & Electronics School, Dept. C4. Reading. Berks RG1 1BR.

FULL-TIME COURSES IN Microprocessor Computers **Video Cassette Recorders** Colour TV. Diploma - High Diploma or City and Guilds Qualifications. Apply: Registrar, **Reeswood College**, 299A Edgware Road, London W2 1BB. 01-402 9985. Courses commence 21st September 1983 and 18th January 1984.

MISCELLANEOUS

BURGLAR ALARM EQUIPMENT. Latest discount atalogue out now. Phone C.W.A.S. ALARM 0274 682674.

SANDHURST PUBLICATIONS **Television Service Sheet Specialists** Workshop Manuals, large selection of Japanese and European TV Sheets. Callers 5.30-7.00 pm. Upper Floor. Send S.A.E. for Catalogue and Enquiries:

49C Yorktown Road,

Sandhurst, Camberley, Surrey GU17 7AG.

TECHNICAL INFORMATION SERVICE SERVICE SHEETS: full size by return - radio, mono, etc. £2 + large sae. CTVs & Music Centres from £3.

SERVICE MANUALS: Sole suppliers most obsolete equipment. Everything stocked to latest releases. Fantastic stocks CTVs/Videos. E.g. A823 £6.50; Autovox (early) £6.50. Tyne 5000/6000 Series £7.50. COMPREHENSIVE TV REPAIR COURSE – Complete data almost every fault. – Huge beginners section. – Only £8.50.

TV REPAIR MANUALS - All 12 for £75. - Mono portables (new) £6.50. - Early VCR, £10.50.

CIRCUIT DIAGRAM COLLECTIONS IN HUGE BINDERS: British CTV (3) £42.50; Foreign CTV (2) £27; Early VHS/Phillips video £15; Mono TV standard + portables £29.

REPAIR SYSTEMS (REPAIR DATA, CIRCUITS, ETC): Video 1, £24.50; Foreign CTV, £40; Mono TV, £31.50.

SAVE £12 - BRITISH CTV ONLY £60 - LIMITED TIME; Complete integrated TV Repair System £160.

Quotations/free 50p magazine/price lists/etc for large sae.

£2 plus 8" \times 10" S.A.E. for service sheet and manual catalogues with £4 vouchers. PHONE 0698 883334 FOR FAST QUOTES - Open 4-6 daily, 11-1 weekends. T.I.S., 76 CHURCH ST., LARKHALL, LANARKSHIRE ML9 1HE.

30,000 SERVICE SHEETS IN STOCK. COLOUR MANUALS ALSO AVAILABLE

TV Monos, Radios, £3.00. Tuners £3.00. Tape Recorders, Record Players £3.00. Transistors £3.00. Car Radios £3.00 + SAE. Stereograms & Music Centres £3.00. Radiograms £3.00. Also Colour available. State if circuit will do if sheets are not in stock. Circuits £3 – colour. All TV Sheets are full length 24 × 12 not in Bits and Pieces. All other Data full lengths. All Sheets £3 except colour. SAE please. Old Valve Radios £3 + SAE 9 × 3.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX.

(MAIL ORDER)

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. £1.25 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

T.V. VIDEO, AUDIO SERVICING available in Beds, Bucks and Northants. Trade contracts sought, RAVEN ELECTRONICS office hours, Milton Keynes 567789.

	PLEASE WRITE IN BLOCK CA sement below in the next avail	PITALS able issue of Television for
nsertions. I enclose Che	eque/P.O. for £	
		Send to: Classified Advertisement Dept.
VAME		
		London SE1 9LS. Telephone 01-261 5846.
Company registered in Er	ngland. Registered No. 53626. Registered Office: K	ing's Reach Tower, Stamford Street, London SE1 9LS.

FOR SALE TUBE REBUILDING PLANT for sale. Fire salvage in **SPECIAL OFFER** good restorable condition. Offers. Phone 0706

(1) L.E.D. Miniature/3mm/5mm - 7 colours available. (II) Single and dual digits display in lots of 1,000 and 5,000.

Ring 688 0977 - Limited Stock

SITS VACANT

NEWARK VIDEO CENTRE is looking for a **VIDEO ENGINEER**

Aged 20-30

With some Video recorder repair experience. Who is willing to work in highly equipped surroundings for next to nothing. The right person will become a video engineering superstar and have the opportunity to be involved in Some exciting technical projects. For details: Ring Newark 71475 or write to: NEWARK VIDEO CENTRE 108 London Road, Balderton, Newark, Notts NG24 3AQ.

WANTED

MACDONALD Radio Television Servicing Books, Volumes 1968/1982 Wanted. Evenings (96) 24551 Sittingbourne.

WANTED FOR CASH. Video, TV's, spares, electronic components. Tel: 965 1230. Box No. TV 175.

WANTED CONTINUED

PHILLIPS, G8, G11 REQUIRED, working or not, must be good cabinets. Regular supply required. Notts/ Derby. Ripley 811124.

SURPLUS, DAMAGED AND BANKRUPT ITEMS. TV's, VIDEO, WASHERS ETC ... Anything considered. UP TO £500,000 CASH available

Phone in strictest confidence: Mr. R. Walker Bradford (0274) 688458

WANTED PHILIPS/PYE G11 Colour TVs, any quantities, Hornchurch 58513, Mr. Morris,

WANTED, ITT CD751 Remote Handset. Good price, any condition. John, 01-597 1443.

SELLING OR BUYING

A classified advertisement could solve your problem at very little cost

> RING MANDI 01-261 5846

N.G.T. COLOUR TUBES

First Independent Rebuilder with

B.S.I. CERTIFICATION (Certificate No. 004)

All Colour Tubes are debanded, high temperature pumped and rebanded using new adhesives and new tension band.

19" £30, 20" £32, 22" £33, and 26" £38. No exchange tube required on delta types. Delivery U.K. mainland: £7.50.

N.G.T. ELECTRONICS LTD.,

120, SELHURST ROAD, LONDON S.E.25 Phone: 01-771 3535.

20 years experience in television tube rebuilding.

add VAT at 15%

A.B.C. ELECTRONICS

Rear of 20, HANKINSON ROAD. WINTON, BOURNEMOUTH. TEL: 519542

TRADE TV's BEST PRICES Colour From £12.00 + VAT B&W From £2.00 + VAT

DISCOUNT ON QUANTITIES

ALL MAKES - ALL SIZES - ALL COMPLETE CALL IN OR RING FOR COMPETITIVE QUOTE FULLY REFURBISHED SETS AVAILABLE + DELIVERY SERVICE

TELEVISION AUGUST 1983



523415

01-570-6976.

Mako

Thom

3500 Thom 8500 Philips G8 GEC

515

Bush

£4.00 £4.00 £4.00

£4.00

£9.00

£6.00 £6.00

COMPLETE OR PART Television tube rebuilding

plant. Training installation and delivery arranged if

CHANNEL MASTER 9502A ROTOR. Excellent con-

dition, Supplied with 20M cable. £25.00. Telephone

TELEVISION 1972 Project complete in cabinet, wiring

T.V. PANELS - T.V. PANELS

SPECIAL CLEARANCE

De-coder

£4.00 £4.00 £3.00 £3.00 £4.00

£9.00

Tripler IF

£3.00

£3.00 £6.00

£3.00 £3.00

£5.00

Video

-

required. For details ring 0265 4951.

nearly finished. Offers. Tel. 01-363 8857.

T/Base panel Line

£4.00

£5.00 £6.00 £8.00 £8.00

☆ Parts also available for other makes
 ☆ Add 15% VAT on all above prices.
 ☆ Add £1.50, postage & packing.

Colour TV's in 10's ea. £25. Mono £2.50

Please refer back to June & July issue of Television Magazine.

M S ELECTRONICS

Unit 1, Warwick Street,

Earlsdon, Coventry. Tel. (0203) 714213.

M S VISION

72 Robertson Street, Glasgow. Tel. (041) 221 2146.

£10.00 £4.00 68.00

£9.00

Telepart **Pattern Generator**

WV2 4LJ Tel: (0902) 773122

Telex: 336810

13 WORCESTER ST., WOLVERHAMPTON,

Conve

dence

£4.00

£5.00

£5.00 £4.00

* Exceptionally light and durable * Pocket size for outside service * PP3 battery power source ive different test patterns for colour no TV * Cross hatch grid * Dot matrix * White raster * Horizontals * Verticles * Five di and mono TV

A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customers home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10x7.5x4 cm and weighs only 190 grams.

PRICE £14.95 (Subject to V.A.T.)

POST & PACKING £1.15

Telepart **Colour Bar Generator**

- -Exceptionally light & durable * Compact 13×17.5×5.5 cms powered for mobility * Cross hatch * Battery powered for mobility

grid 9 White raster * Grey scale * Colour bars * Sound

A Versatile Generator for Servicing or aligning mono or colour TV receivers. Lightweight and very compact for outside service. Features sound facility often not found on more costly generators.

PRICE £49.95 (Subject to V.A.T.) POST & PACKING £1.15

Power Supply

A Power Supply can be supplied for the Telepart COLOUR BAR GENERATOR. This compact unit mounts by 2 screws into the Battery compartment and converts the unit to a bench instrument.

PRICE £5.50 (Subject to V.A.T.)

Supplied by return, off the shelf

DIODES	BZX 83c20 1	On Voltage Bassilater	
OA 47 8 OA 90 8	BZX 83c27 BZX 83c33	Op Voltage Regulators 0p 5V/UA78PO5SC 60p 0p 5V/LM79MO5CP 25p	PHILIPS DIY HOME SECURITY ALARMS KITS Send for details. Prices £54 to £112.
OA 91 8 IN 60 5 IN 541 5 IN 914 5	p BZX 84c6v8×10 3 p BZX 85c8v2 1 p BZX 87c5v1 1	Op 8V/79M08c 30p Op LM 342/12 30p Op L3V/MC 7012 30p	21
IN 914 -3 IN 2069a 10 IN 2070 10	a BZY 88c0v7	0p 12V/MC 7912 20p 0p 12V/LM 340T12 25p 0p 15V/78M15 15p	attention attention and attention
IN 4001 3 IN 4002 3	p BZY 88 6.8v 1 p BZY 88 6v2 1 p BZY 88 6v2 1 p BZY 88612 1 p CV 8617 1	0p 18V/MC78M18 20p 0p 24V/78M24 30p	And the second s
IN 4005 4 IN 4006 4	p CV 8617 1 p Y 716 2	0p 7p TIS 90 15p 7p TIS 91 30p	
IN 4004 4 IN 4005 4 IN 4006 4 IN 4007 5 IN 4148 3 IN 4448 3	p Y 730 2 p Y 827 3 p Y 860 3	0p TIS 92 30p	Many -
IN 4742 10 IN 4722 10	p Y 933 p Y 997 3	P CB Radio transistor P 16119 2A/40v.50Meg p 5 for £1.	
IN 5235 10 IN 5254 10	All diodes at 10p or less in this	U 14727 15p	
IN 5392 10 IN 5928B 10	P list 20 of one type £1.		and and a second s
IAV 30 10 IM 72Z55 10 IR 106a 20 IR 3051 10	R 1039 5	p MR 856 10p MR 508 10p	RADIO CONTROL CAR KITSMINI £30PORSCHE £25MIRAGE £25
	R 2009	1 MR 501 10p 1 MR 502 20p	Various Tools and Accessories
IS 921 10 IS 3011a 10 IS 3072a 10 IS 5024a 50	R 2029 50 R 2210 60	p MR 854 10p BYF 1202 10p	Sellotape PVC Black 50p 50mm × 20M 70p
IS 5030 50 ITT 921 10 ITT 923 10	R 2257 66 R 2265 56	p BYF 1204 10p p BYF 3123 40p	Telescopic aerials (radio) £1 Xcelite pliers £3.90
ITT 1075 10 ITT 2001 10 ITT 2002 10	R 2306 50 R 2322/2323 pair 80	p BYF 3214 40p BYX 10 6p	Xcelite snips£5Xcelite cutters£3.90
TTT 4150 10	R 2396 50	p BYX 38/300 35p p BYX 38/300 25p	GKN Supascrew kits £2.50
ZE 1.5 10p ZF 3.0 10p ZF 3.3 10p ZF 4.3 10p	R 2030 f R 2443=BD124 40	1 BYX 55/350 10p BYX 55/600 (Bead) 10p	Pull up large aerial 75p
ZF 10 10p	R2737=TIP31A 40 R2738=TIP41 30	p BYX 71/350 20p BYX 71/600 50p	Portable TV aerial 75p
ZF 15 10p ZF 33 10p	R2928=BU 208 60 R 2813 60	p BYV 95 8p	Neon screwdriver50pPhillips snips£2
ZF 43 10p ZF 47 10p ZF 82 10p	R3129=TIP47 40 R 3018 60	P BYZ 106 10p BPW 41 15p	2 way baby alarm/intercom with long leads £5 Phillips universal battery tester/charger, fuse/bulb tester £5
ZPD 3.9 10p ZPD 4.7 10n	K 3019 00	BYW 56 2A/1000v 8 p BZY 93 50 p BZV 15/12 30 p	Volt/ohm test meters 1000 ohm/volt
ZPD 5.6 10p ZPD 10 10p ZPD 47 10p	BU 195 75	BZV 15/18 30p	2 hour 13A/240V Timer (plug in socket)
ZPY 8v2 10p ZPY 12 10n	B/U 108 £	p	+ 2A/8.4V Sealed Nicad " "AA"/1.25V Nicad £1
ZPY 24 10p ZPY 43 10n	BU 137 £	ITT computer bookset 2020 £4	Duracell PP3 $60p$ $\frac{3''}{2''} \times \frac{1}{2''}$ microphone/speaker $50p$
ZPY 47 10p ZPY 56 10n	BU 204 70	Transformer 240v/20v-	Continental 2 pin plug with 5 ¹ / ₂ ft mains lead (black & blue) 5 for £1
ZTK 22 10p ZTK 33 10p	BU 206 £	Viewdata torroidals £5 + £2 postage	Xcekute 5" bent nose plier £3 50
ZTK 33a 10p ZTX 102c 10p ZTX 107 10p	BU 208/02 £1.2) Sankyo tape motor 75p	De-solder pump + 2 nozzels $f_{2,2}$
ZTX 108c 10p ZTX 109k 5p	BU 222 £ BU 326 £	Swiss made 250rpm/240V	Quantity Reductions 20 Slider Knobs 70p BY204/4 25 for £1.00 6 Mixed UHF Aerial Isolating
ZTX 213 5p ZTX 341 10p ZTX 342 10p		Sharp tape motor 400-040 £1.50	BD132/676a 20 for £2 Sockets, some with long leads £1.00
ZTX 384 10p ZTX 450 10p	BU 526	neck £1.50	W005 bridge 20 for £2 G11 touch button red 5 for £1 Mixed Packs 6Meg filter 10 for £2.60 15 Panel mount rocker switch
ZTX 550 10p	DINION	LD57CA 15p	BY210/600 25 for £1.00 250V/10A £1.50 BY298 3 amp/fast/R 20 for £1.50 Pack of mixed coloured wire £1.00
ZW 13 12p ZW 27 10p ZW 43 10p ZW 310 10p	TIC 106a 30r	Mono scan coil £3 G 8 transductor £1 Thorn 4000 tube base £4	BD239 20 for £2.00 1 dick of mick of onour drawner 21.00 MR856 25 for £1.50 25 LED red/yellow/green £1.50 BU126 10 for £6.00 201/C Holders £1.20
ZX 68 50p ZY 47 10p ZY 72 10p	TIC /16d 300 TIC /16n 350	A1 pots Thorn 3500 50p	BU208 10 for £5.00 20 Large LED Red £1.00 BU205 10 for £8.00 20 Small LED Red £1.00
AA 112 10p AA 113 10p	TIC 206m 30p		BU105 10 for £6.00 10×20 Turn 100K Pots £1.00 2SC2122A 10 for £8.00 100 Mixed Transistor £2.50
AA 119 8p AA 143 10p	TIC 226m 30r TIC 236m 30r TICV 106D	BRIDGES KBL 005 30p KBL 02 30p	BF38 10 for £1.00 20 Convergence Pots 80p BD136 10 for £1.25 20 Convergence Pots 80p BF224 20 for £1.40 100 Mixed Sticks £1.00
BA 102c 10p	(T092 case 2A/400V) 10p	KBP 04 30p W02 15p	OA90 40 for £1.00 10 Thermistors 50p IN4148 40 for £1.00 20 Slider Pots £1.00
BA 157 Bp BA 159 Bp BA 173 Bp BA 182 Bp BA 201 Bp BA 202 Bp	TIP 29A 20p TIP 30 30p TIP 30A 35p	W005 20p	IN4448 40 for £1.00 30 Presets 50p BYX10 100 for £4.00 15 VDB + thermistors decauseing
BA 201 Sp BA 201 Sp BA 202 Sp BA 243 Sp BA 248 Sp	TIP 30A 35p TIP 31 30p TIP 31B 40p		KT3 multicaps 10 for £7.50 50 High voltage ceramic condensers £1.50 40 glass reed switch £1
BA 310 8p	TIP 32 25 F TIP 33 50 p	AT 2076/55 GEC split diode transformer £10	Mixed Mounting Kit for Power 10 press to make switch £1 Transistors 50p 40 Pots £1,50
BAV 10 10p BAV 21 10p BAW 21 10p	TIP 34 50p TIP 35 50p TIP 36 50p	AT 2048/11 LOPTI Mullard £2.50 75R/25 Watt 25p	300 Condensers £1.50 10 Gun Switches 50p 300 Resistors £1.50 5 Tube Bases £1.00 150 Electrolytics £2.00 10 Output Content
BB 103 10p BB 105A 10p	TIP 41A 30p TIP 41B 40p	18R/11 Watt 25p 3.3M/3 Watt 10p	15 Bulbs 40p 1,000 Diodes, Condensers, 100 Diodes £1.50 Resistors on Bandolier £3.00
BB 105B 10p BB 105G 10p BB 121a 10p BZX 46c22 15p	TIP 41c 40p TIP 42 30p TIP 42B 40p	TV Sound Tuner Kit, ideal for TV sound on	100 Fuses £2.00 Lucky Dip 600 gram £1.00 100 W/W Res. £1.50 25 mixed High voltage pulse
BZX 46c22 15p BZX 61c110 6p BZX 61c115 6p	TIP 47 TIP 48 40p	your Hi-Fi £9.50 Front End Music Center. VHF/	consdenser £1.00 Jungle Bag 5Kg £5.00
BZX 61c110 6p BZX 61c15 6p BZX 61c20 10p BZX 61c30 10p	TIP 49 30p TIP 100 30p	MW/LW 13"×3½" £5	SENDZ COMPONENTS
BZX 61c220 10p BZX 70c33 8p BZX 79c2v4 10p BZX 79c4v7 8p	TIP 112 30p TIP 117 50p TIP 120 35p	Output Stage for music centerf5 Both items £9	
BZX 79c5v6 8p	TIP 125 35p TIP 130 30p	circuit supplied (as previous ad)	63 Bishopsteignton, Shoeburyness, ESSEX SS3 8AF
BZX 79c6v2 8p	TIP 131 30p TIP 136 30p TIP 640 75p	SONY 1400KV Chroma Panel £6 SONY 1400KV Tuner unit£3.50	SAME DAY SERVICE
BZX 79c11 10p BZX 79c12 8p	TIP 040 75p TIP 2955 35p TIP 3055 35p	SONY 1400KV Touch button unit	All items subject to availability. No Accounts : No Credit Cards
BZX 79c30 8p BZX 79c43 8p		Panel VDP 12/80 D2N 720 Issue 3. Complete with All	Postal Order/Cheque with order
BZX 79c47 8p BZX 83c4v3 10p BZX 83c5v6 10p	MJ 2253 60p MJ 3040 60p MJE 1300S 30p	I.C.'s. Usually £100. ONLY £10.	Add 15% VAT, then 50p P+P Add Postage for overseas
BZX 83c8v2 10p BZX 83b12 10p	MJE 2955C3 30p MV 2209 10p	VIEWDATE DECODER	Callers: To shop at 212 London Rd., Southend, Tel, 0702-332992
BRC 83c13 10p	SP 8385 25p	PANEL TEXAS	
TELEVISION AUC	JUST 1983	12 m	559
		yo de	

Shoeburyness, SAME DA All items subjec No Accounts : Postal Order/Ch Add 15% VAT, Add Postage Callers: To shop a	COMPONENTS steignton, ESSEX SS3 8AF Y SERVICE t to availability. No Credit Cards seque with order then 50p P+P for overseas at 212 London Rd., . 0702-332992	Mains in 110-120-220-240V A.C. and white camera. Power consump voltage: 14V D.C. Dimensions 150 120mm (d). Accessories: Mains lead and video/audio remote cable (2 metres)	otion: 12V A. Output	12/300 10p 4.7M/350v 10p 16/350 25p 50/350 10p 220/350 30p 300/350 40p 700/350 50p 22/375 15p 30/385 CVC 820HT 60p 0.1/400 15p 56K/400v 20p 220/400 50p 220/400 50p 220/400 40p 2×10,000Pf/400 in box 40p 2210/450 40p 0.1/600 15p 0.4/600 15p 0.1/600 15p 0.1/800 15p
Transducer Hand Set insert. Crystal. tranducer, 11C SAA 1124 & lead Crystal. tranducer, 11C SAA 1124 & lead Chen Ward Construction OOSI 012 E002 £1.00 OOSI 012 E002 £1.00 OOSI 012 E002 £1.00 Rank/Toshiba preh unit 0354 4 Push button unit preh £1.00 6 Push button Unit Thorm £1.00 6 Push button Unit Torm £1.00 6 Push button Unit for CEC 2040 and ELC 1043/05 6 Augh button Unit for CEC 2040 and ELC 1043/05 6 Augh button Unit for CEC 2040 270/10/6 for Thorm 4000 70/17/1KS £1.00 72/07/07/39 £1.01 72/07/07/07/07/07/07 £1.00 72/07/07/07/07/07/07 £1.00 72/07/07/07/07/07 £1.00 72/07/07/07 £1.00 72/07/07/07 £1.00 72/07/07/07 £1.00 72/07/07/07 £1.00 72/07/07/07 £1.00 72/07/07/07 £1.00 72/2	CVC3 ITT £7.50 EHT Spit Diode Leads £1.00 Triplers Universal Tripler £3.50 11 TEZ Rank £3.60 9000 Thorn £5.60 9000 Thorn £5.60 9000 Thorn £4.00 GEC 2110 £4.00 GEC 2110 £4.00 GEC 2110 £4.00 Decca 80 100 £4.50 LP1194 Pye 731 £3.50 Grandig TVK 52 £2.50 11TBO £3.00 LP1194 Pye 731 £3.50 Decca 80 100 £4.50 LP1194 Pye 731 £3.50 Grandig TVK 52 £2.50 11TBO £3.60 LP1193/63 £4.00 BC 100/41 £3.25 BG 100/61 £3.25 BG 100/61 £3.25 BG 100/61 £3.25 BG 100/61 £3.25 New Philips Infra Red Transmitter 9ch & Vol. & brightness Change 27.00 THORN Tuner Panel. 6 Slider ports. Knobs, touch button. Ultrasonic transductor, ICS, components & mains switch £3.75 GEC Portable Line Trans. £3.00 THORN stouch button. Ultrasonic transductor, ICS, components & mains switch £3.75 GEC Portable Line Trans. £3.00 THORN 9000 Frame Panel £5.00 GHORN 8800/9000 Remote Unit U705 £6.00 THORN 8800/9000 Remote Unit U705 12.00 THORN 8800/9000 Remote Unit U705 12.00 THORN 8800/9000 Remote Lint U705 13.00 GB Convergence Panel £12.00 THORN 8800 remote control unit U705 13.00 GB Convergence Panel £3.00 GB CONTHORN 8800 remote control unit U705 13.00 GB CONTER Panel £3.00 GB CB SO CONTER PANEL £3.00 GB CB S	Tube base + base unit for 820 Euro chasis 54.00 CVC 9 IF panel and decoder £7.00 GEC Linc O/P Trans. & Rec Sick for Portable £3.00 CVC 20/25/30/35/40 decoder panel (untosted) £5 CVC 20/25/30/35/40 decoder panel (untosted) £5 CVC 20/25/30/35/40 decoder fanel (untosted) £5 CVC 40/45 IF panel £5 Mains Panel with switch and lead £1.50 Thom 3500 6 push button unit & cable form £1.50 Rec & Trans G11 Ultrasonic t/text transmitter G22 C66/02 £19 Handset Rank Infra Red £10.00 Infra Red full ramote transmitter Dynatron TV CIV 62-63-64 £19 40K Transducer Y0K Transducer 50p PHTILIPS NES1 IN E1.20 Lmb 37M Reg 30p Phorn T603 TV MPN T066 80V 6A A 10p 20 GEC Black Spark Gaps £1.00 G11 Line Driver Transformer 35p 2 SD350A BU208A £1.00 Complete CVC 825 Chassis (both panels) £40.00 GH Teletext Transmitter £19.00 BG200/43 Tripler £3.00 DECCA IF 80-100 £3.50 G11 Time Base Panel £12	1 S00/16 20 3300/16 20 3300/16 20 3300/16 20 10000/16 25 1500/16 56 3300/18 20 470/25 55 10000/16 11 1250/25 10 1250/25 10 1300/25 20 4700/25 22 5000/25 22 1000/35 22 500/30 20 3300/30 33 3300/30 33 3300/30 33 3300/30 33 3300/30 33 3300/30 33 3300/30 23 3300/30 24 200/40 22 200/40 22 200/40 22 200/40 22 200/40 22 200/40 22 200/35 22 3000/40 22	p 0.647/1000 10p 0.01/1000 10p 0.01/1000 10p 1.5/1000 20p 0.01K/1250 10p 0.005/1500 10p 0.005/1500 10p 0.005/1500 10p 0.005/1500 10p 0.005/1500 15p 0.118/1500 15p 0.118/1500 15p 0.12KV 15p 0.12KV 10p 0.12KV 10p 0.12KV 10p 10n/2KV 15p 9 51.8200/2KV 10p 9 50.2/2KV 10p 9 100/014KV 10p 9 100/014KV 10p 1000/100/XV 10p 120/12KV 10p 120/12KV 10p <t< th=""></t<>

SAVE () NOW ONLY 12pEACH COLOUR PR

with the Television **Colour Print Service**

While prices go up elsewhere, Television makes a bargain offer in its Colour Print Service. Now you can have as many films printed as you like, including Giant Superprints, at only 12p a print. There is no developing charge and just 25p towards postage and packing.

At this new price, the magazine Colour Print Service, already used by hundreds of thousands of readers, is as fast and efficient as ever. Here's all you have to do to enjoy its advantages.

Send any make of colour print film, including disc film, inside the envelope enclosed with this issue. Or fill in the coupon below and send with your colour print film in a strong envelope to: **Television Colour Print Service**, FREEPOST,

READING RG1 1BR. No stamp is required.

SEND NO MONEY

We are so confident in the reliability of our service and the quality of our prints (each one date-stamped with the month and year of developing) that you don't pay until you've seen them. LUXURY COLOUR PRINTS

You will be amazed at the beautiful colours and sheen finish of these prints. They have elegant rounded corners and are borderless to give you maximum picture area. And with the Giant Superprints, you get 30 per cent more picture area than the standard enprints at no extra cost!

UNBEATABLE VALUE

All you pay for the Colour Print Service is 12p for each good print received plus 25p towards postage and packing. The most you would pay us for processing and printing a 24-exposure film for example is £3.13. Compare that with the price you would pay in the shops.

FREE ALBUM PAGES

With each film we process, you receive an album page voucher. Collect and return three vouchers, and you receive a set of FREE album pages to fit into our specially designed album for any size of print up to 4in. by 6in. HOW YOU BENEFIT

You benefit in three ways Firstly, you pay nothing for the actual processing-only for prints and postage and packing. Secondly, you enjoy a personal service with every care taken over each individual order. And thirdly, you pay only for what you get-with no credit vouchers as with many other companies. An invoice comes with your prints, so it is a straight business transaction.

48 HOURS IN-LAB SERVICE Your films will be processed within 48 hours* of receipt, but

please allow for postal delays. The price of this offer is limited to the U.K.

*C41 Process cassette and cartridge film only.

Offer excludes Black & White, transparency, sub-miniature, C22 & Agfa CNS film uperprints can only be produced from Kodacolour II, C41 cassette, cartridge and disc film not half frame. Prices correct at time of going to press.

this label if you have no envelope, or pass it to a friend. It is used to pack your prints.

To: Television Colour Print Service FREEPOST, Reading RG1 1BR							
Please print my film Superprint size Standard Enprint size							
f film is being ordered Please send me							
of 110/24 of 126/24 of 35/24							

Tick box(es) as required.

FILMS AT REDUCED PRICES Always keep your camera actionready. Order replacement films

discount).

of disc/15

FILM THE REPORTED A at our specially reduced prices: 110/24, 126/24 or 35/24 at £1.20 a roll, or three for £3; disc/15. £1.30 each (no quantity

PRIN

If you have any queries, contact our Customer Service on Reading (0734) 597332.

	Colour Print Service ADING RG1 IBR	
Mr/Ms		
Address		
	Postcode	

Tuner Units ELC1043/05 Mullard £6.00 ELC1043 (Ex Panel) £3.75 ELC1042 , £5.00 ELC2000 , £7.00 ELC2004 £10.00 £10.00 ELC2060 , £7.00 ELC2060 , £7.00 ELC2060 on panel NEW £5.00 U321 (UHF) Mullard £6.00 U322 (UHF) , £4.00 V314 (VHF) , £5.00 Small V/Cap Mitsumi UHF , UHF , £4.00	SENDZ COMPONENTS 63 Bishopsteignton, Shoeburyness, ESSEX SS3 8AF SAME DAY SERVICE All items subject to availability. No Accounts : No Credit Cards Postal Order/Cheque with order Add 15% VAT, then 50p P+P Add Postage for overseas Callers: To shop at 212 London Rd., Southend. Tel. 0702-332992		TBA120SQ £1 TBA120U 4 TBA120C 4 TBA120C 4 TBA140 £1 TBA395 5 TBA395 5 TBA396 5 TBA396 5 TBA440 £1 TBA440C £1 TBA510 £1 TBA520 £1 TBA530 £1 TBA530 £1 TBA540 £1 TBA540 £1 TBA540 £1 TBA540 £1 TBA550Q £1 TBA570 £1	A0p BT119 .00 BT120 BT109 BT109 40p BT138/10A BD BT146 TCA270 TCA270 75p TCA270Q 75p TCA4500A 1.00 TCA650 1.00 TCA660 1.00 TCA740 1.00 TCA740 1.00 TCA740 1.00 TCA740 1.00 TCA940 1.00 TCA740 1.00 TCA940 1.00 TCA740 1.00 TCA940 1.00 TCA940 1.00 TCA940 1.00 TCA940 1.00 TCA940 1.00 TDA4003A 1.00 TDA1003A	£1.00 BD437/438 on heat sink 60p 60p £1.00 BD507 50p 90p BD509 30p 30p BD510 30p 21.00 BD517 30p 21.00 BD519 30p 21.00 BD513 30p 21.00 BD534 30p 21.00 BD544D 30p 21.00 BD595 35p 21.00 BD678 50p 21.00 BD678 50p 21.00 BD678 30p 21.00 BD678 30p 21.00 BF115 20p 21.00 BF115 20p 21.00 BF137 20p
VHF , £3.00 VHF Rotary Mitsumi £1.00 Portable & rotary Tuners Sanyo & Mitsumi UHF £5.00 Mossfit UHF VHF NSF. ET021 DX £8.00 Sylvania UHF VHF F6013 (Fits Rank) £4.50 Sylvania UHF £6.00 Sylvania UHF £6.00 Decca Bradford Tuner 5 Button £4.00 NSF AEG UHF/VHF £6.00 Small Tuner DX 175- 220MHz Auto Changeover £5.00 9000 Thorn Tuner on Panel £7.00 D.P.D.T. switch Black knob: Chassis or PCB mount 4p each or 40 for £1.00 THORN 1400 4P.B. Mechanical Tuner THORN 1500 4P.B. Mechanical Tuner THORN 3500 4P.B. Mechanical Tuner THORN 8000 4P.B.	Diodes 1 Amp 1600v 7p 3 Amp 100v 7p 3 Amp 1200v 10p 7 Seg Display, Led Red-50p Delay Lines TAU80 £1.00 DL11 50p DL50 £1.00 DL70 £1.00 DL70 £1.00 DL70 £1.00 DL700 £1.00 MDL-CBL Min. 50p 3.15 Fuses 4p Co-Ax Joint 12p Co-Ax Belling Lee Plug 12p UHF Modulator CCIR. 43.00 Infra Red Emitting Diode. 20p NE286H Small Neon Lamps GEC GEC 5p Mullard 5 Watt Amps. £12 LP1162 New 75p T.V. Tubes A31/300 Hitachi £12 A34/170W Hitachi £8	CA1310 50p CBF16848 50p DM7492 50p MEF4001 10p HEF4016 15p HEF4016 15p HEF4016 15p HEF4016 15p MC1307 75p MC1330 75p MC1349 50p MC14016 £1.00 MC14001 £1.00 MC14016 £1.00 MC14069 £1.00 MC143514 50p MC14314 50p MC14314 50p MC14314 S0p MC14314 S0p MC14314 S0p MC14314 S0p MC14314 S0p MC14314 S0p MC14314 S0p MC14314 S0p MC14314 S0p MM5840 S0p MM5840 <td>TBA641 BX1 £2 TBA651 £1 TBA653 £1 TBA720A £1 TBA750Q £1 TBA800 £1 TBA810S £1 TBA820 £1 TBA920Q £1 TBA920Q £1 TBA920Q £1 TBA920Q £1 TBA920Q £1 TMS950 £1 TMS990Q £1 TMS9930 £12 TMS9940 £12 TMS9930 £12 TMS9940 £12 TMS9940 £12 TMS9940 £12 TMS9901 £6 TMS9902 £6 TMS9902 £6 TMS9902 £6 TMS9902 £6 TMS9902 £6 TMS9902 £6 TMS9903 £1 SN76014 £2 SN76015 £1 SN76016 £1 SN76023N £1 SN76023N £1<td>1.00 TDA1010 2.00 TDA1170 1.00 TDA1170 1.00 TDA1127A 1.00 TDA1327A 1.00 TDA12140 TDA2140 TDA2140 70p TDA2532 1.00 TDA2532 1.00 TDA2540 1.00 TDA2540 1.00 TDA2540 1.00 TDA2540 1.00 TDA2540 1.00 TDA2560 2.00 TDA2660 5.00 TDA2660 5.00 TDA2680 5.00 TDA2680 5.00 TDA2680 5.00 TDA2680 5.00 TDA2680 5.00 TDA2680 5.00 TDA3500 75p TDA3500 75p TDA3590 1.00 SN16862AN 1.00 SN16864AN 50p MIE505 1.00 MIE5340 MIE661 MIE660</td><td>£1.00 BF157 20p £1.00 BF161 20p 30p BF164 60p 30p BF164 60p £1.00 BF167 20p £1.00 BF173 10p £1.00 BF178 25p £1.00 BF178 25p £1.00 BF181 20p £1.00 BF184 20p £1.00 BF184 20p £1.00 BF194 20p £1.00 BF198 10p £1.00 BF198 10p £1.00 BF198 10p £1.00 BF222 10p £1.00 BF245 20p £1.00 BF264 15p 50p BF261 15p 50p BF261 15p</td></td>	TBA641 BX1 £2 TBA651 £1 TBA653 £1 TBA720A £1 TBA750Q £1 TBA800 £1 TBA810S £1 TBA820 £1 TBA920Q £1 TBA920Q £1 TBA920Q £1 TBA920Q £1 TBA920Q £1 TMS950 £1 TMS990Q £1 TMS9930 £12 TMS9940 £12 TMS9930 £12 TMS9940 £12 TMS9940 £12 TMS9940 £12 TMS9901 £6 TMS9902 £6 TMS9902 £6 TMS9902 £6 TMS9902 £6 TMS9902 £6 TMS9902 £6 TMS9903 £1 SN76014 £2 SN76015 £1 SN76016 £1 SN76023N £1 SN76023N £1 <td>1.00 TDA1010 2.00 TDA1170 1.00 TDA1170 1.00 TDA1127A 1.00 TDA1327A 1.00 TDA12140 TDA2140 TDA2140 70p TDA2532 1.00 TDA2532 1.00 TDA2540 1.00 TDA2540 1.00 TDA2540 1.00 TDA2540 1.00 TDA2540 1.00 TDA2560 2.00 TDA2660 5.00 TDA2660 5.00 TDA2680 5.00 TDA2680 5.00 TDA2680 5.00 TDA2680 5.00 TDA2680 5.00 TDA2680 5.00 TDA3500 75p TDA3500 75p TDA3590 1.00 SN16862AN 1.00 SN16864AN 50p MIE505 1.00 MIE5340 MIE661 MIE660</td> <td>£1.00 BF157 20p £1.00 BF161 20p 30p BF164 60p 30p BF164 60p £1.00 BF167 20p £1.00 BF173 10p £1.00 BF178 25p £1.00 BF178 25p £1.00 BF181 20p £1.00 BF184 20p £1.00 BF184 20p £1.00 BF194 20p £1.00 BF198 10p £1.00 BF198 10p £1.00 BF198 10p £1.00 BF222 10p £1.00 BF245 20p £1.00 BF264 15p 50p BF261 15p 50p BF261 15p</td>	1.00 TDA1010 2.00 TDA1170 1.00 TDA1170 1.00 TDA1127A 1.00 TDA1327A 1.00 TDA12140 TDA2140 TDA2140 70p TDA2532 1.00 TDA2532 1.00 TDA2540 1.00 TDA2540 1.00 TDA2540 1.00 TDA2540 1.00 TDA2540 1.00 TDA2560 2.00 TDA2660 5.00 TDA2660 5.00 TDA2680 5.00 TDA2680 5.00 TDA2680 5.00 TDA2680 5.00 TDA2680 5.00 TDA2680 5.00 TDA3500 75p TDA3500 75p TDA3590 1.00 SN16862AN 1.00 SN16864AN 50p MIE505 1.00 MIE5340 MIE661 MIE660	£1.00 BF157 20p £1.00 BF161 20p 30p BF164 60p 30p BF164 60p £1.00 BF167 20p £1.00 BF173 10p £1.00 BF178 25p £1.00 BF178 25p £1.00 BF181 20p £1.00 BF184 20p £1.00 BF184 20p £1.00 BF194 20p £1.00 BF198 10p £1.00 BF198 10p £1.00 BF198 10p £1.00 BF222 10p £1.00 BF245 20p £1.00 BF264 15p 50p BF261 15p 50p BF261 15p
Filter State Mullard Surface Wave. Eilter RW 154_Cotour TV Filter 40p Crystal T/V T/V 4.433-G19KHz T/V 4.433-G19KHz 50p 6 MHX Crystal 50p 8.8867-238KHz Min 50p Biniature.ITI Gauge 75p Filters B 5-5MHz 15p 6MHZ 35p BT19 £1.00 B BT120 £1.00 B BT24435K 5p G11 Thyristor 60p BG11 Thyristor 60p BG11 Teletext Decoder Panel B Philips £1.00 BT119 £1.00 BT119 £1.00 BT19 £1.00 BT19 £1.00 BT19 £1.00 BT19 £1.00 BT19 £1.00 BT19 £1.00 BT10 £1.00 BT10 £1.00 BT10 £1.00 BT119 £1.00 BT110	$\begin{tabular}{ c c c c c c c c c c c c c c c c c c c$	2SB566 10p F 2SC381 10p B 2SC458 50p B 2SC515 10p B 2SC732 10p B 2SC733 10p B 2SC732 10p B 2SC733 10p B 2SC128 10p B 2SC1172 £1,00 B 2SC1173 10p B 2SC1311 20p B 2SC144 20p B 2SC1546 20p B 2SC1647 £1,00 B 2SC1073 8p B 2SC2073 8p B 2SC2222 15p B 2SC1230 15p B 2SC100 £2,00 B	B/T6016 £1 ML236E £1 ML2378 £1 ML238B £2 BTT822 £1 BTT6018- £1 BTT822 £1 BTT822 £1 BTT822 £1 BTT822 £1 BTT822 £1 BTT822 £1 BTT824 £1 BT7824 £1 BT78250 200 Line Transistor Semiconductors BT106 BT100A BT106 BT106 £1 BT106 £1 BT108 BC1 C107 10p C113 10p C114 10p C115 10p C116 10p C117 20p C125 10p C125 10p BC2 C139 D0p BC2 C139 10p BC2 10p	AFI 39 AFE 39 30p AFE39 AF567 AL102 50p AU113 73 10p BC307 74 10p BC307 83 10p BC31 84 10p BC331 94 BC331 94 BC331 96 BC341 107 BC381 87 10p BC342 107 10p BC342 107 10p BC342 107 10p BC342 138 38 30 138 38 30 139 10p BC411 139 BC412 139 BC412 139 BC421 139 BC421 139 BC421 139 BC421 149 BC430 151	9 10p BC547 10p BC547 10p BC548 10p BC556 10p 7 10p BC556 10p 7 10p BC557 10p BC558 10p BC558 10p BC538 10p BC33 10p BC33 10p BC33 10p BC33 10p C359 10p BC33 10p BD124 25p 10p BD124 25p 10p BD124 25p 10p BD124 10p BD133 10p BD133 10p BD133 10p BD133 10p BD134 10p BD135 25p BD182 10p BD140 25p BD182 10p BD140 25p BD182 10p BD140 25p BD182 10p BD140 25p BD182 10p BD140 25p BD182 10p BD140 10p BD174 10p BD135 10p BD174 10p BD135 10p BD176 10p BD

pp. 518 Condor st25

iv