MARCH 1984

Australia \$1.80, New Zealand \$2,10; Malaysia \$5.50;

£1.00

£1.00

£1.00

£1.00

THE CED VIDEO BISC SYSTEM

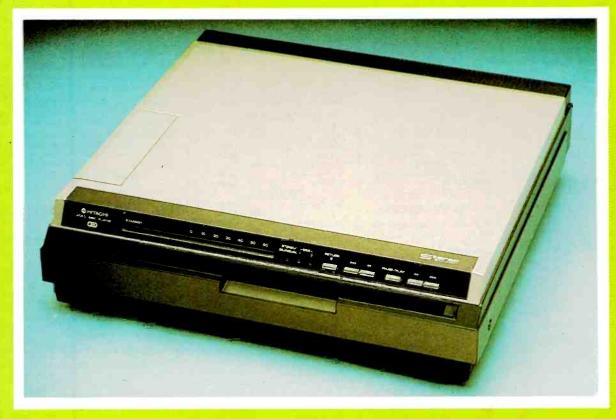

DX SIGNAL DETECTOR/ALARM
VCR CLINIC

Interested in Television Servicing? Tru a ZED Pack. Effect Repairs at Minimum Cost.

	IIy u ZZ	- L U	C12.	sirect irepairs a	re r.war		iii Oost.	
Z1	300 mixed \frac{1}{2} and \frac{1}{4} watt and minia-		Z 20	10 Assorted switches including:		Z44	TO3 Mounting kits (BU208)	8 for 60p
1	ture resistors	£1.95		Pushbutton, Slide, Multipole,		Z45	TO 220 Mounting kits (TIP 33) 10 for 60p
Z2	150 mixed 1 and 2 watt resistors	£1.95		Miniature etc. Fantastic Value	£1.20	Z46	TO 126 Mounting kits (BD13)	
Z3	300 mixed capacitors, most types	21.,,	Z21	100 Assorted Silver Mica caps	£2.20	Z47	Pack of each Mounting kit. Al	
	amazing value	£3.95	Z22	10 Mixed TV convergence Pots	£1.00		include insulators and washer	
Z4	100 mixed electrolytics	£2.20	Z23	20 Assorted TV Knobs including:	21100	Z48	3a 1000v Diodes (IN5408 typ	
Z5	100 mixed Polystyrene Capacitors			Push Button, Aluminium and		Z49	Brushed Aluminium Push But	
Z6	300 mixed Printed Circuit	22.20		Control types	£1.20	247	Knobs, 15mm long × 11mm I	
	Components	£1.95	Z24	10 Assorted Valve bases	21.20		Fit standard 3 mm square sha	
Z7	300 mixed Printed Circuit	21.75		B9A.EHT.etc.	£1.00		1 it standard 5 2 min square sin	10 for £1.00
~·	resistors	£1.45	Z25	10 Spark Gaps	£1.00	Z50	Chrome finish 10mm × 10mn	
Z8	100 mixed High Wattage Resistors.		Z26	20 Assorted Sync Diode Blocks	£1.00	250	as above	10 for £1.00
20	wirewounds etc.	£2.95	Z27	12 Assorted IC Sockets	£1.00	Z 51	Aluminium Finish. Standard	
Z9	100 mixed Miniature Ceramic and	22.75	Z28	20 General Purpose Germanium	21.00	LJI	Slider Knobs. (Decca)	10 for £1.00
1 ~	Plate caps	£1.50	220	Diodes	£1.00	Z52	Decca "Bradford" Control K	
Z19	25 Assorted Potentiometers	£1.50	Z29	20 Assorted Miniature Tantalum	21.00	LJL		
Z13	25 Assorted Presets, Skeleton etc.		LLY	Capacitors. Superb Buy at	£1.20	Z53	Black and Chrome. 4" Shaft	
Z11 Z12	20 Assorted VDR's and	£1.00	Z30	40 Miniature Terry clips,	11.20	Z33	Tuner P/B Knobs, Black and	Chrome.
212	Thermistors	61.30	230	ideal for small Tools etc.	61.00		Fit most small Diam Shafts,	0.6 61.00
7.13		£1.20	Z31	5 CTV Tube Bases	£1.00	764	ITT, THORN, GEC etc.	8 for £1.00
Z13	1 lb Mixed Hardware, Nuts, Bolts,	61.20	Z31 Z32	10 EY87/DY87 EHT bases	£1.00 £1.00	Z54	Spun Aluminium Control Kn	
	Selftappers, "P" clips etc.	£1.20					1" Shaft, suitable for most sets	
Z14	100 mixed New and marked		Z33 Z34	20×PP3 Battery Connectors	£1.00		with recessed spindles	8 for £1.00
1	transistors, all full spec. includes:		Z34	6×Miniature "Press to Make"		Z55	14 Pin DIL I.C. Sockets	12 for £1.00
1	PBC108, BC148, BC154, BF274, BC212L, BC238, BC184L and/or		77.20	Switches, Red Knob	£1.00	Z56	16 Pin Quil I.C. Sockets	12 for £1.00
1			Z35	12 Sub Min S.P.C.O. Slide	C1 00	Z 57	16 Pin DIL TO QUIL I.C.	100 0100
(714)	Lots of similar types ONLY	£4.95	7.27	Switches	£1.00	7.00	Sockets	10 for £1.00
(Z14A)			Z 36	12 Min D.P.C.O. Slide Switches	£1.00	Z58	22 Pin DIL I.C. Sockets	10 for £1.00
l	including power types like BD131,		Z37	8 Standard 2 Pole 3 Pos Switches	£1.00	Z59	B9A Valve Bases P.C. Type	20 for £1.00
	2N3055, AC128, BFY50etc.	£9.95	Z38	4×HP11 Batt Holders				
Z15	100 Mixed Diodes including:				or £1.00			
	Zener, Power, Bridge, Signal,		Z39	3.5mm Jack Sockets, switched,		1	C.R. BATTERY PA	CKS.
	Germanium, Silicon etc. All full		77.40		or £1.00		ACHI PORTABLE V.C.R. N	
	spec.	£4.95	Z40	100 Miniature Reed Switches	£2.30		VTBP60E	£20 each.
Z16	20 IN4148 Gen Purpose Diodes	£1.00	Z41	100 Subminiature Reed Switches	£4.20		nd New and Boxed	3 for £50
Z17	20 IN4003/10D2	£1.00	Z42	20 Miniature Reed Switches	£1.00	Diai	id 1.0 and Doxed	J 101 4,50

1 watt and 400 mw
High quality COAX PLUGS,
silver plated pin, grub screw
fixing. 5 for £1 COAX COUPLERS 5 for £1
COAX COUPLERS 5 for £1
COAX FLYING
SOCKET 3 for £1

20 Assorted Zeners.

Z18

ELECTROL	YTIC
1μf 63v	20 for £1.00
1μf 350v	10 for £1.00
2.2μf 63v	20 for £1.00
4μf 350v* .	10 for £1.00
10μf 25v	20 for £1.00
22μf 16v	20 for £1.00
100μf 25v	20 for £1.20
160µf 25v*	20 for £1.50
330µf 25v	10 for £1.00
400μf 40v*	8 for £1.00
470µf 25v	10 for £1.00
470µf 35v	8 for £1.00
1000μf 35v	6 for £1.00
1000μf 40v*	5 for £1
*Axial. All others are	Radial.

CAN TYPES	
22µf 375v (3 pin)	50p
50μf 250v (3 pin)	50p
100μf 350v	80p
2000μf 100v	£1,00
1000µf 100v	60p
2,200µf 40v	60p
2,200µf 63v	70p
3,500µf 35v	50p
220µf 400v ITT/RBM	£1.00
6,800µf 70v	£1.00
10,000µf 40v	£1.00

20 of ONE colour 20 of EACH colour 100 of ONE colour 100 of EACH colour

R.B.M. USERS LOOK!

Z43

£1.50

No more messy soldering. 24 pin I.C. sockets for SL901 etc. SPECIAL OFFER: 5 for £1.00 100 for £12,50.

SPECIAL OFFERS

100 Assorted Polyester Capac Mullard C296's and others	itors.
160v-400v only	£2.00
100 Assorted Mullard C280's	
Cosmetic imperfects etc.	£2.00
200 Mullard Miniature	
Electrolytics Cosmetic imperfe	ects
etc.	£2.00
PACK OF EACH	£5.00

12V BULBS on leads. Suitable for most VIDEO RECORDERS.

70p each 4 for £2

CAR RADIO SUPPRESSOR KIT

Comprises: in line aerial suppressor, power lead suppressor and clock/accessory suppressor. With leaflet. £1.95 each, 10 for £12 Further Discount on large quantities

£3,95

£1 £2,50 £4 £10

SN76660N 50p THODNEDADEC

12 Subminiature Reed Switches

10 of one value

10 of one value

1.3 watt, 12v, 13v, 18v, 47v

10 of each

10 of each

25 × IN4002

20 × IN4003

20 × IN4005

20 × IN4148

10 × BYX10 12 × BY127

Very small.

TRA 820

CA270AE£1.00

MC1327P£1.00 TBA120SB 5

TBA810P£1.00

TAA 661B £1.00

555 Timer 30p

8 × BY255 (3A 1,300V)

10 × BA 158 (600v 400ma) IN5402 3a 200v 466A. 100V. Bridge Rectifier.

I.C.'s

ZENER DIODES 0v7. 2v7.4v3.4v7.5v6.6v2.6v8. 7v5. 27v. 30v. ALL 400mw.

DIODES

ITIONNES)
"3500" Transductor	£1.20, 3 for £3.00
"3500" Focus Assembly with VDR	£1.50
"8500" Focus Assembly. Rotary type	£1.50, 3 for £4.00
"8500" .0022 2000v Line Capacitor	10 for £1.00
"1590/91" Portable metal boost Diode (W11)	5 for £1.00
"1500" Bias Caps 160µf 25v	20 for £1.50
"1500" Jellypot, L.O.P.T. Pinkspot	£3.50
"900/950" 3 stick triplers	£1.00, 3 for £2.50
"950" Can. 100 + 300 + 100 + 16µf	£1.00

"MITSUMI" MINIATURE ROTARY

SPECIAL OFFER PHONO PLUGS, metal with plastic tops. Red, grey or black

UHF TUNERS
Single nut fixing as used in various JAP portables
"Mitsumi" varicap tuner "AM-UF-125".

SPECIAL OFFER
LIGHTWEIGHT STEREO HEADPHONES, Good quality with
3.5mm stereo jack plug. £2.95 each, £25 for 10. Further discount available on large quantities.

IHUKNSPAKES		
"3500" Transductor	£1.20, 3 for £3.00	
"3500" Focus Assembly with VDR	£1.50	
"8500" Focus Assembly. Rotary type	£1.50, 3 for £4.00	
"8500" .0022 2000v Line Capacitor	10 for £1.00	
1590/91" Portable metal boost Diode (W11)	5 for £1.00	
"1500" Bias Caps 160µf 25v	20 for £1.50	
"1500" Jellypot, L.O.P.T. Pinkspot	£3.50	
"900/950" 3 stick triplers	£1.00, 3 for £2.50	
"950" Can. 100 + 300 + 100 + 16μf	£1.00	

THYRISTOR CONVERGENCE POTS

5(1), 10(1), 20(1), 30(1), 50(1), 100 Ω , 200(1), 1K, 8 of one type £1.00, 8 of each type £6.00. SS106 (BT106) 75p each 3 for £2.00, 10 for £5.50

PACKS.

£6.60

£1.00

£1.00

£1.00 100 for £3.00

£1.50 100 for £5.00

£1.00 100 for £2.50

£1.00

8 for £1.00

6 for £5.00

6 for £5.00

4 for £1.00

6 for £5.00

5 for £2.00

80p ea. 3 for £2.00

50p each, 5 for £2.00

£1 each, 6 for £5.00

100 for £2.50

£1.00

THORN "VIDEOSTAR" 3V25/26 Nicad pack. Type VA214. Also suitable for J.V.C. etc. Brand new and boxed. £20 each, 3 for £50.

THORN "VIDEOSTAR" Nicad packs. Same as above but secondhand, untested. Contain 10 "C" size Nicads (HP11) which can be replaced if necessary. £10 each, 3 for £25.

MISCELLANEOUS

BG100 tripler for CVC45 etc.	only £3.50
Line output transformer for	4.35 b. 3.5 610.00
RBM823A ITT VC200 4P/B Transistor Tuner. Su	1.25 each, 3 for £10.00
and Philips sets. 3 hole fixing	£2.75 each
Decca Bradford Tuner.	12,/3 (acii
	1.00 each, 4 for £12.00
5 button type £4 UHF Modulator UHF out Video in. C	
2½"×2"×½" complete with 9 foot coaxia	
	3.00 each, 2 for £5.00
GEC Hybrid 2040 series Focus Assem	
	22.00 each, 3 for £5.00
Convergence Panel for above. Brand n	
and plug.	£3.00 each
GEC 2010 Transistor Rotary Tuner wi	
leads	£1.95 each, 3 for £5.00
Bush CTV 25 Quadrupler type Q25B ed	
TU25 3OK	£3.00 each, 2 for £5.00
Focus VDR Rods 23"×1". Suitable for	
Decca etc.	75p each, 3 for £2.00
Grundig UHF/VHF Varicap Tuner for	
fil	2.50 each, 3 for £30.00
EHT Lead with Anode cap (CTV) suit	
sets 1m long	60p each, 3 for £1.50
EHT Cable 30p per m	etre, 10 metres £2.50
4.433 Mhz CTV Crystals	70p each, 3 for £2
75Ω 2½ Loudspeaker	60p each, 4 for £2
6 MHz sound filters, ceramic 3 pin	00p cacii, 4 101 22
"TAIYO" type	50p each, 3 for £1.00
PYE CT200 Control Knobs	8 for £1.00
Degaus VDRs. 11" diam, for RBM etc.	5 for £1.00
Mains Neons	10 for £1.00
2k2 Screened Resistors.	20101 21100
White ceramic, 9 watt, with tusible link,	8 for £1.00
E.H.T. Discharge probe, with heavily ins	
with lead and chassis connector.	60p each, 3 for £1.50
TINITETION O LT TOTAL	

UNIVERSAL TEST LEAD KIT

Comprises: Red and black meter leads with 14 inter-changeable probes, clips, points, plugs etc with screw threads.

ONLY £2.50 ONLY £2.50

I.C. EXTRACTING TOOLS


Small 90p Large £1.20

SMART ALUMINIUM FINISHED **4" SHAFT KNOBS** i'' diam. Ideal for TV or Hi-Fi. 10 for £1 100 for £8

GEMINI ELECTRONIC COMPONENTS

Dept. TV, The Warehouse, Speedwell Street, London S.E.8.

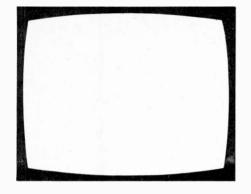Please quote ZED code where shown. Send cheque* or Postal Order. Add 60p P&P and 15% VAT.
*Schools etc. SEND OFFICIAL ORDER. Allow up to 28 days for delivery. Most orders despatched same day.
ZED PACKS now available for CALLERS at 50 Deptford Broadway, London, S.E.8. Send large S.A.E. for list of Quantity, Prices and Clearance Lines etc.



TELEVISION

March 1984 Vol. 34, No. 5 Issue 401

COPYRIGHT

PPC Magazines Limited, 1984, Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

SUBSCRIPTIONS

An annual subscription costs £11 in the UK, £12 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at £1-20p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month

241 Leader

242 Long-distance Television Roger Bunney
Reports on DX reception and conditions and news from

247 The CED Video Disc System

The RCA CED video disc system was the outcome of heavy research and development expenditure over many years. It's an elegant solution to the problem of how to store video signals on a disc, doing so by means of frequency modulated capacitance variations. A look at the techniques involved and the players released in the

UK late last year

250 Teletopics News, comment and developments.

252 Vintage TV: The Ferguson 841T

The UK's leading setmaker didn't enter the TV field at the very start. When they did, shortly after the war, this is what they came up with.

253 VCR Clinic

Notes on VCR faults and servicing techniques contributed by Steve Beeching, T.Eng. (C.E.I.), Derek Snelling, Mike Phelan, Les Harris and Mick Dutton.

256 Letters

257 Next Month in Television

258 Servicing the Sony KV1400UB

Another popular small-screen Sony colour set. The interrelationships between the switch-mode power supply and the line timebase mean that a systematic approach is called for in dealing with the dead set symptom. This and other fault conditions you may come up against.

260 TV Fault Finding
Notes on TV faults from Mick Dutton, P. Hardy, M. S. Barakat and John Coombes.

262 VCR Servicing, Part 26
The Ferguson 3V24's drum servo system.

265 The Card Game is Over

Monthly report from that famed servicing centre.

Les Lawry-Johns

266 DX Signal Detector/Alarm

Two PLL i.c.s are used as a narrow-band filter to detect the presence of the signal's line sync component, producing an output to gate the video signal through to a simple audio amplifier to provide an audible indication.

A Question of Black Level

A black-level signal is useful for servicing, for editing video programmes and other purposes. A simple black-level generator is described.

270 Service Bureau271 Test Case 255

OUR NEXT ISSUE DATED APRIL WILL BE PUBLISHED ON MARCH 21

233

Mike Phelan

MANOR SUPPLIES

NEW MKV CHEQUERBOARD & PAL COLOUR TEST GENERATOR FOR TV & VCR.

TEST **DEMONSTRATIONS** AT 172 WEST END LANE





- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial
- ★ Additional video output for CCTV & VCR.
- Facilities for sound output.
- ★ Easy to build kit. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- Also available with VHF Modulato

Also available with vith Modulator.	
Price of Kit	£80.50
De Luxe Case $(10'' \times 6'' \times 2\frac{1}{4}'')$	£8.50
Optional Sound Module (6MHz or 5.5MHz)	£4.50
Built & Tested in De Luxe Case including Sound	Module
	£120.75

SPECIAL TEST Post/Packing £2.50 Post/Packing £2.50
Post/Packing £2.50
Post/Packing £2.50
All above prices include VAT 15%

PAL COLOUR BAR GENERATOR (Mk4)



- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT £34.50. DELUXE CASE £8.50. BATT HOLDERS £3.20. MAINS SUPPLY KIT £4.80 (Combined P&P £1.80).

MK 4 DE LUXE (BATTERY) BUILT & TESTED £66.70 + £1.80 P & P. MK 4 DE LUXE (MAINS) BUILT & TESTED £78.20 + £1.80 P & P. VHF MODULATOR (CHI to 4) FOR OVERSEAS £6.60. EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V. (ALL PRICES INCLUDE 15% VAT)

MANOR SUPPLIES TELETEXT ADAPTOR KITS

MK 1 (Texas XMII) Cable remote control £158.70 p.p. £2.80.
MK 2 (Philips/Mullard) Infra-red remote control £198.40 p.p. £2.80.

Further details on request. Tel 01-794 8751/7346

Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order).

TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF TECHNICAL EXPERTS

TELEVISION MAGAZINE PROJECT PARTS

COLOUR PORTABLE TV MONO PORTABLE TV, SMALL SCREEN MONITOR LISTS AVAILABLE, PANEL TEST SERVICE

PHILIPS UHF MODULATOR (AUDIO & VIDEO INPUT) £17.25 p.p. £1.00.
MULLARD TELETEXT DECODER + INTERFACE suitable for Thorn,
TX10 £69.00 p.p. £1.80. (Decoder only £57.50 p.p. £1.80).
SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND tested
for T.V. SOUND & VISION £2.80 p.p. £1.20.
THORN TX9, TX10 SAW FILTER IF PANEL £9.80 p.p. 80p.
PAL DECODER KIT FOR RGB MONITORS £31.00 p.p. £1.00.
SPECIAL OFFER TEXAS XMII TELETEXT DECODER NEW & TESTED, AT REDUCED PRICE £46.00 p.p. £1.60.
TELETEXT 23 BUTTON DE-LUXE HANDSET WITH 5 YDS. CABLE
£7.80 p.p. £1.20. XMII STAB. POWER SUPPLY £4.40 p.p. £1.20.
CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC
AND UHF MODULATOR, BATTERY OPERATED. ALSO GIVES
PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET
£12.65 p.p. 60p. (ALUM CASE £2.90 DE LUXE CASE £5.50 p.p. £1.20.)
ADDITIONAL GREY SCALE KIT £3.35 p.p. 45p.
UHF SIGNAL STRENGTH METER KIT £3.30 (VHF version also available). ALUM CASE £2.90 DE LUXE CASE £8.50 p.p. £1.80.
CRT TESTER & REACTIVATOR PROJECT KIT FOR COLOUR &
MONO £32.20 p.p. £2.80.
BUSH 2718 BC6100 SERIES IF PANEL £5.75 p.p. 90p.
BUSH A816 IF PANEL (SURPLUS) £1.90 p.p. 90p.
DECCA 80, SERIES, IF, FRAME T.B. £5.75 each p.p. £1.40.
DECCA 80, LINE SCAN UNIT Salvaged £11.50 each p.p. £2.00.
GEC 2040 Convergence panels, Decoder panels £2.88 each p.p. £1.80.
THORN TX9 PANELS ex factory solvaged complete cond £23.00 p.p. £2.80.
THORN TX9 PANELS salvaged ex factory £17.25 p.p. £2.00.
THORN TX9 PANELS salvaged ex factory £17.25 p.p. £2.00.
THORN TX9 PANELS ex factory salvaged complete cond £23.00 p.p. £2.80.
THORN TX10 T.B. PANELS salvaged ex factory £17.25 p.p. £2.00.
THORN TX10 T.B. PANELS ex factory salvaged ex factory £17.25 p.p. £2.00.
THORN TX10 T.B. PANELS ex factory salvaged ex factory £17.25 p.p. £2.00.
THORN TX10 T.B. PANELS ex factory salvaged ex factory £17.25 p.p. £2.00.
THORN TX10 T.B. PANELS ex factory salvaged ex factory £17.25 p.p. £2.00.
THORN TX10 T.B. PANELS ex factory salvaged ex factory £17.25 p.p. £1.40.
OPHILIPS G8/G9 IF/DECODER PANELS salvaged ex factory £1 SPECIAL OFFER ELEVEN POSITION VARICAP CONTROL ON UHF/VHF £2.10 p.p. £1.00.

BUSH "Touch Tune" Varicap Control Z179, Z718 types £4.40 p.p. 95p.

VARICAP UHF-VHF ELC 2000S, ELC2060 £11.30 p.p. 90p.

VARICAP VHF MULLARD ELC 1042, PHILIPS, BUSH £7.95 p.p. 80p.

UHF/625 Tuners, many different types in stock. DECCA Bradford 5 position VARICAP VHF MULLARD 22 UHF/625 Tuners, many different types in stock. DECUMENT 1.80 etc.

T.V. SOUND IF Panels £7.82 p.p. £1.00.

LOPT TESTER Serivice Dept approved £17.82 p.p. £1.20.

LOPTS NEW & GUAR. P/P Mono £1.35p, Colour £1.45p, Bobbins 80p.

BUSH 161 to 186 (twin panel) £6.80 R.B.M. A823 £5.60

BUSH, MURPHY 774 series £9.80 R.B.M. 2179 £11.30

BUSH, MURPHY 774 series £9.80 R.B.M. 2179 £11.30

FERG. HMV, MARCONI, ULTRA R.B.M. T20, T22 Bobbins £6.44

950, 1400, 1500, 1580, 1590, 1591 £6.80 DECCA 80, 100 £10.15

THORN 1600, 1615, 1690, 1691 £10.50

GEC 2000 to 2038 series £7.80 GEC 2028, 2040, 2100 £6.70

GEC series 1 & 2 £9.20 GEC 2110 Series £12.20

INDESTI 20/24EGB £8.80 ITT CVC2 to 9, CVC20 £11.30

ITT/KB VC 200, 300 ... £8.80 ITT CVC2 5 to 9, CVC20 £11.30

ITT/KB VC 200, 300 SERIES £8.80 PYE 713, 715 £7.85

PYE, INVICTA, EKCO, FERR 974 731 to 741 £10.60

SPECIAL OFFER PYE 725 (907) 731 to 741 £10.60

BECCA 20/24, 1700, 2000, 2401 £4.40

PHILIPS GB £10.15

PHILIPS GB £11.30

BECCA 20/24, 1700, 2000, 2401 £4.40

PHILIPS GB £11.30

E7.85

PYE 40, 67 £2.00

THORN 3000/3500 SCAN, EHT £7.85

PYE 40, 67 £2.00

THORN 3000/3500 SCAN, EHT £7.85

PYE 40, 67 £2.00

THORN 9000 to 9600 £14.80

KB VC1 £3.25 THORN 9800 £21.90

MANOR SUPPLIES 172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door W. Hampstead British Rail Stns. (Richmond, Broad St.) (St. Pancras, Bedford) W. Hampstead (Brit. Rail) access from all over Greater London. Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11. ALL PRICES INCLUDE VAT AT 15%



TOP WINTER VALUE FROM BTC-THE TV SPECIALISTS



You won't better these BTC bargains!

Top quality sets to set you up for the winter televiewing boom. Brighten your winter profits with better sets from BTC.

COLOUR

DECCA BFD 30 TELPRO KORTING PYE 697, GEC 2040

UNTESTED
ONE TO TEN \$20.00
ONE TO TEN \$20.00
OVER TEN \$18.00
SOLID STATES

HYBRIDS

 WORKING

 ONE TO TEN
 £28.00

 ONE TO TEN
 £28.00

 OVER TEN
 £25.00

1COLOUR

PHILIPS G8's 2-CHIP BUSH/MURPHY GEC 2110, 8500 3500 VARICAPS P/BUTTON HITACHI's 18" PHILIPS
 UNTESTED

 ONE TO TEN
 £28.00

 ONE TO TEN
 £28.00

 OVER TEN
 £25.00

 OVER TEN
 £25.00

 ONE TO TEN
 £28.00

WORKING
ONE TO TEN £45.00
ONE TO TEN £45.00
OVER TEN £40.00
OVER TEN £40.00
OVER TEN £40.00

COLOUR

1-CHIP BUSH/MURPHY THORN 3000, THORN 8000 18" PYE's ROTARY JAPS
 UNTESTED

 ONE TO TEN
 £22.00

 ONE TO TEN
 £22.00

 OVER TENS
 £30.00

WORKING
ONE TO TEN £35.00
ONE TO TEN £35.00
OVER TENS £40.00

COLOUR

LATER SETS
ie. THORN 9000
TOUCH TUNE SETS
etc.

£30.00 **OVER TENS** £40.00 WORKING UNTESTED ONE TO TEN ONE TO TEN £55.00 £45.00 ONE TO TEN £45.00 £55.00 **OVER TENS** £50.00 **OVER TENS** £40.00




SINGLE STANDARD MONO TV's IN BATCHES OF 20 @£4.00 EACH

SPARES PANELS, TUNERS, LOPTS, TUBES, STANDS, INDOOR AERIALS.
ALWAYS IN STOCK — NEW OR S/HAND ABOVE SPARES INCLUDE BRITISH & CONTINENTAL TV'S. PLEASE RING OR WRITE FOR QUOTES.

0274~306018

CASH & CARRY SPECIAL SERVICE TO THE TRADE OR ASK ABOUT SPECIAL DELIVERIES ON LARGE QUANTITIES. OPENING TIMES MON-FRI 9.00-12.00/1.00-5.45 (CLOSE 4.30 SAT)

BRIARWOOD TRADING COMPANY

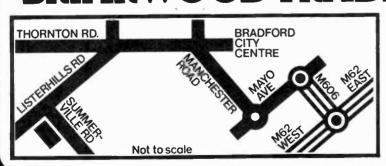



BRIARWOOD TRADING COMPANY LEGRAMS MILL, SUMMERVILLE ROAD, BRADFORD BD7 1NH

P. V. TUBES

Just phone vour prder through, we do the rest



BARCLAYCARD VISA

Telephone: Accrington (0254) 36521 Accrington (0254) 32611

SUPPLIERS

38A WATER STREET, ACCRINGTON, LANCS BB5 6PX.

OF TELEVISION COMPONENTS TRADE COUNTER OPEN MON-FRI 9 a.m.-5 p.m. SAT 9.30 a.m.-5 p.m. TBA720 TDA2581 3.30 7905 INTEGRATED CIRCUITS 98 98 T.T.L. 74LS SERIES TA7202P 4 27 TBA750 TBA800 MSN5807 MS1513L MS1515L SAS560S TDA2590 3 25 7908 7908 58 74LS37 58 74LS38 58 74LS40 58 74LS42 58 74LS47 74LS48 TA7204P TA7205AP TA7208P TA7210P 54 1.00 53 67 74 19 741 592 35 74 5160 741 5251 TDA2591 2 95 98 98 98 98 72 72 72 72 74LS00 74LS02 74LS03 74LS04 74LS05 74LS08 7908 7912 7915 7918 7924 794,05 74L S93 74L S181 74LS253 TBA810AS TBA820 TBA890 TDA2593 TDA2600 TDA2611A TDA2680 TDA2690 TDA3566 TDA3566 TDA3950 TDA9503 UPC1185H UPC566H UPC566C UPC1025H 1 10 20 74LS93 20 74LS107 36 74LS109 80 74LS112 80 74LS113 80 74LS114 74LS162 74LS163 74LS163 74LS164 74LS165 74LS253 74LS257 74LS258 74LS259 74LS273 3.40 6.60 2.42 3.74 1.95 2.92 TBA920(Q) TBA950(2X) TBA970 TBA990 CA741 CA748 SAS570S SAS580 1.89 A7222 TA7223P TA7227P 89 50 70 1.54 1.10 36 36 36 36 99 99 80 1.20 CARORS SASSON 2.90 5.50 741 500 74LS49 74LS283 58 58 58 58 37 CA3065 LA4031P LA4102 LA4250 LA4400 LA4422 4.09 1 35 79L12 74LS49 74LS51 74LS54 74LS55 74LS73 74LS74 74LS75 SL901B SL917B SL1310 TA7228P TA7310P TA7609P TA7611AP 74LS09 74LS10 74LS11 74LS13 74LS175 19 74LS123 19 74LS125 74LS293 794 15 74LS353 74LS353 74LS365 74LS366 74L S191 TCA160 1.20 74LS125 74LS126 74LS132 74LS138 74LS139 74LS151 74LS191 74LS192 74LS193 74LS194 74LS197 TCA760 TCA760 TCA270SQ TCA800 TCA940 TDA440 TDA1002 SL13270 2.92 2.50 4.00 74LS14 74LS15 TAA300 TAA310 TAA320 TAA350A TAA550 TAA570 TAA630 TAA661B SOFTWARE FOR 19 YOUR COMPUTER LC7130 5.93 SN78003N 2.83 46 22 80 80 LC7120 -SN76013N 74L S76 74LS240 74LS241 74LS368 74LS373 We have a vast 3.40 SN78023N SN76110N SN76115N 2.00 1.15 2.27 74L S78 74LS153 range of software 74LS83A 74LS86 74LS85 74LS85 74LS90 74LS155 74LS156 74LS157 74LS158 74LS374 74LS393 74LS670 LM1303N HA1151 UPC1025H UPC1181H UPC554 UPC1182H UPC1186 UPC1156H 74LS242 1.62 1.34 2.95 19 TDA1003A TDA1004A 74LS26 for most home 74LS27 19 74LS244 74LS245 computers. We will 1.99 1.60 1.70 MC1307 SN76131 N 3.90 1.96 TDA1006A 741 530 19 gladly supply mail order. Please ask for MC1310F MC1327 SN76226(DN) 741 532 4.00 4.70 4.37 TDA1011A TDA1035 SN76227N SN76532N SN76533N SN76533N SN76544N SN76650N 1.18 1 20 4.26 UPC1156H UPC1158H UPC1163-H UPC1212C UPC1230H UPC1350C UPC1367 UPC1378H STK445 MC1351P 2.93 TRA1204 TDA1044 78 98 your favourite title. 90 1.99 1.50 1,75 1.70 2.49 2.35 1.05 (A),(S),(AS), TBA1208 TBA120SB TBA120U MC1330F TDA1044 TDA1170 TDA1190 TDA1200 TDA1270 TDA1327 '4000 R' 76 45398 72 45418 1.68 45438 1.88 45518 1.88 45538 22 45118 22 45128 22 45138 22 45148 22 45158 4027B 4028B 4029B MC1349 MC1350 39 64 90 1,04 ANGGE 1,34 3,95 4,15 I.C. SOCKETS SERIES 4070B 4071B 4072B 96 1.12 96 2.40 DIL to DIL 8 way 14 way CMOS 4001B 4002B MC1352 MC1358F 1.10 22 SN76660N SN76666N TRA395 4032E 1.70 3.45 4.49 29 32 32 32 32 34 16 way 18 way 20 way 22 way 24 way MC1495L TRA396 4035E 4073B SN 76660N SN 76530A SW 153 TA 7050P TA 7051P TA 7074P TBA440N (TBA1441)
2.75
TBA440P 2.50
TBA480(Q) 1.50
TBA510 3.00 TDA1352B 1 60 TDA1352 TDA1412 TDA2002 TDA2140 TDA2190 TDA2020 TDA2030 TDA2030 TDA2632 MC14011BCP MC14049UB 66 43 400RB ANSRE 99 72 4075B 22 4516B 76 4554B 76 4556B 1.20 1.20 2.80 5.95 4.70 9.06 8.10 4516B 4518B 4519B 4520B 4521B 4522B 4526B 4011B 4040F 4076R 76 45568 64 45608 76 45618 88 45608 88 4568 88 45818 1.20 45828 88 45838 62 45858 72 45978 1.00 45988 2.64 45988 1.04 45988 STK441 4040B 4042B 4043B 4044B 4046B 4047B 4049UB 4012B 4013B 4014B 4015B ML231/ETTR8016 1.76 74 1.20 3.60 1.84 80 1.00 40 88 1.84 2.40 2.00 **VOLTAGE REG.** 4081B 4093B 4094B 4099B M C232 1.00 3,43 4.66 2.80 4.17 7806 7806 7808 7812 MI 236 TA7108P TRA5200 1.68 1.68 1.58 1.59 1.79 1.50 3.50 2.45 DIL to QUIL 14 way 16 way 18 way 1.56 1.20 72 31 70 MI 237 TA7120 TBA530(0) 4016B TA7120P TA7129AP TA7130P TA7141P TA7193P TA7171P TBA530(Q) TBA540 TBA550(Q) TBA560Q TBA570 TBA641BX1 45268 45278 45288 45298 45308 45318 45328 MI 238 4017B 4018B ML239 ML920 ML922 ML926 ML928 TDA2522 TDA2523 4050B 4051B 4052B 4053B 4060B 4066B 1.93 95 5.67 1.85 1.85 34 72 4160B 7815 4020B 4020B 4021B 4022B 4023B 4024B 4025B 4161R 72 72 72 72 72 1.88 76 76 70 70 21 50 21 TDA2524 TDA2530 TDA2540 TDA2541 7818 78 78 72 41618 72 41628 72 41638 96 45028 43 45058 22 45108 7824 78L05 78L08 QUIL to QUIL 14 way 32 16 way 36 TA7172F 4536B MRF475 MRF477 TRA673 40688 TA7176F 2.50 TBA700 2.12 TDA2571 500 R2540 2.00 2SC643A 1.50 1.20 RCA16334 90 2SC1096 1.72 1.60 RCA16335 90 2SC1172Y2.20 1.69 TIP30C 43 2SC113Y1.69 1.69 TIP30A 47 2SC1305 2.73 1.21 TIP30C 42 2SC1307 3.00 3.66 TIP31C 52 2SC149 1.67 3.66 TIP31C 42 2SC1320 68 24 BT102/500 24 12 30 BT106 1.6 30 BT107 1.6 36 BT108 1.6 41 BT116 1.2 BC213 BC213B BC213L BC214 BC214 NEW VALVES 30FL2 1.70 EF183 13 BD137 10 BD138 9 BD139 9 BD140 SEMICONDUCTORS 9F27: 1.24 BF274 1.39 BF310 1.50 BF311 95 BF322 L.E.D.s BD696A 1.49 BF273 BD138 BD139 BD140 BD144 BD150 BD697 BD695 BD698 BD707 PCF200 1 35 PI 504 165 DY802 DY86/7 ECC81 ECC82 ECC83 .70 EF183 98 EF184 66 EH90 .08 EL34 98 EL84 .07 EL90 80 EY86/7 BC115 BC116A BC117 1.38 1.13 1.12 PCF800 PCF801 PCF802 PCF806 PCF808 PCF808 PCL800 PCL82 PCL805 PCL805 PD500 PFL200 PL36 PL81 T11 TYPE Red PL508 2.30 81 2.30 69 2.25 PL509/19 PY88 PY500A PY800/1 Green Yellow BC118 BC214L BDX32 2.10 BF337 14 22 1.07 AC141K 39 BC119 BC237 14 BD159 14 BD160 BF115 BF117 38 36 BF338 Amber AC142K BC139 28 32 BC238 1.90 52 BF365 BT120 3.0 BT151/800 UCH81 42 2SC1520 68 75 2SC1678 2.67 1.06 2SC1909 2.90 47 2SC1953 1.44 50 2SC2028 1.82 70 2SC2029 2.60 65 2SC2078 2.90 BC140 BC141 BC142 BC143 BC147 (A),(B),(C) BC251A BC252A BF362 BF363 BF371 BF457 BF458 BF459 BFR39 35 BD 166 BF125 TIP33B ECC85 ECC88 EY500A EZ80/1 UCL83 1.82 26 47 23 18 27 24 22 52 46 BD179 BD182 BD163 BD201 1.20 TIP34B 2.00 TIP41C T1 TYPE 1.35 IJY85 1.35 PL802T 40KD6 21LU8 17D A4A BU104 200 GY501 FCF80 1.45 1.20 92 1.09 2.93 1.86 1.87 4.00 5.30 3.00 1.60 5.00 3.75 ECF82 ECH81 ECH84 ECL80 GZ34 KT66 KT88 PC92 AC187 AC187K 12 14 14 BC2528 BC261A/B18 AC188 AC188K **BC148** BC262A/B 18 BC300 50 BD202 Yellow 1.75 TIP2955 1.50 TIP3055 1.42 TIS91 1.80 TV106/02 2SC2091 1.34 BD203 3AT2B 12BY7A BFR39 BFR90 BFT42 BFT43 BF.W10 BFX29 BFX84 BFX85 BFX86 1.74 39 39 B (301 BD204 BU204 2SC2166 2.73 ECL82 ECL86 1.30 1.99 PC97 PCC85 1.65 AD149 BC158 BC303 33 BD222 BF178 46 BF179 28 BF180 39 BF181 39 BF182 36 BF183 29 BF184 36 BF185 36 BF194/394 16 BF195 16 BF178 BU205 94 1.43 BC158 BC159 BC160 BC161 BC170B BC171 BC171A THV FLASHING COX21 COX22 Red Only BC307 20 BC308A /B 25 BC327 18 BC328 18 AD161 BD223 BU206 EF80 EF86 PCC805 1.40 PL83 15/80 THY 15/85 2.20 BD225 BD232 BD233 BD234 BU208 1 BU208A 1 BU208/02 A0161/2 1.15 1.60 1.80 1.96 PCF80 PL84 54 49 89 1.20 1.65 2N696 12 2N918 2.10 2N2904 1.75 2N2905 LINE OUTPUT TRANS. WIREWOUND (General Purpose Thyristors) DEC 1 BC337 BC338 ose (vristors)
J (DEC 1
11 Multipurpos.
10 Thyristor
10 DEC 2
10 Multir
17 Th RESISTORS * BU326A 1.75 2N2905 BU407 1.70 2N3054 BU500 2.30 2N3055 BU526 2.46 2N3702 R.B.M. T20A **AF118** BD235 3 COLOUR Red/Green Yellow V518P R.B.M. A774 Mond BC461 BC547 BC548 407

JUS00

BUS26 1

24 BUS06 1.4

95 BUS07 2.94

34 BUWR1A

15 E1222 40 2N

MJE340 68 2NS

VJ3000 1.98 2NS2

T112 1.91 2SB33

121 1.91 2SB33

121 1.91 2SB37

18 1.92 2NS107

150 2SCA715 1.96

67 2SCA95

50 2SCA95 11.74 AW 1R-10K BC171B 65 57 75 30 BD236 BFX88 R.B.M. A774 Mono R.B.M. Z179 R.B.M. Z718 22" PHILIPS 320 PHILIPS 320 Mono PHILIPS G8 BFY50 BFY51 BFY51 BFY52 BFY90 BR100 **AF124** BC172 13 BD237 13 30 27 AF125 BC172A BD238 65 85 85 79 74 86 94 52 55 60 60 75 62 AF126 AF127 AF139 AF178 AF239 AL102 BC548 BCX32 BCX34 BC549 BC550 BC557 BC558 BD243 BD244 BD244 BD410 BD434 BD437 BC172B BC172C BC173C BC174A/ BF197 BF198 BF199 BF200 16 BFY51 16 BFY52 18 BFY90 21 BR100 35 BR101 25 BR103 20 BRC4443 25 BR24444 BUVvo.. 3.8 E1222 3.8 AUE340 4.9 AUE340 4.0 DT112 1.9 56 R2008 8.8 R2008 8.8 R2255 72 R2323 1.20 R2461 Thyristor £2.26 PHILIPS G9 PANEL CLIPS PHILIPS G11 BC177 BC178 27 26 MISTORS VA1104 75 PYE 697 (Printed)
PYE 713/731
PYE 725 90°
PYE 169
DECCA 80′ 100
DECCA 1700 CARBON RESISTORS *
W 3R3-8M2 2
W 3R3-8M2 2
W 10R-10M 3 14.50 **BD438** BF224 10.00 20 20 BC182 BC182L BC183L BC184L BCY72 BD507 BF225 VA1040 AU107 2.00 BD115 BD508 BF241 BD115 BD116A BD124P BD131 BD132 BD133 BD509 BD510 BD517 BD520 BD526 25 BRX46 28 BRY39 25 BRY56 35 BSV67 84 BSV57B 75 BT100 24 BT101 1 86 VAR650 **AU113** 2.00 **BF256** CRYSTALS 36 62 BF257 BF258 BF259 BF262 53 75 VA1039 W 10R-10M (A),(B),(C) 20 BC108 20 (A),(B),(C) 20 Sold in packs of 10 per type B C204 B C208 10 13 10 9 1.68 DECCA 1730 DECCA 2230 8.58 81 Posistor 1. 1.98 GEC Duel 1.10 2 0 4 1.31 (CK1) 1 BC209 GEC 2110 SOLDERING BC109 20 (A),(B),(C) 20 BC212 BD 135 38 38 BD535 82 | BF263 91 | BF271 GEC 2110 GEC 2040 GEC 2200 ITT CVC 1-9 ITT CVC 25/30/32 ITT CVC 20 1.98 10.692Mhz 6.00 BC212L 13 BD136 BD536 EQUIPMENT REBUILT COLOUR TUBES
ALL AVAILABLE EX-STOCK ON GLASS FOR
GLASS EXCHANGE FROM TRADE COUNTER.
SOME TYPES AVAILABLE WITHOUT EXCHANGE FOR SMALL GLASS CHARGE
17" A44/271X 30.00 WELLER Iron 15W 4.31 NEW MONO TUBES MULL A31/510 110° 12″ 18.50 MULL A34/510 110° 14″ 20.00 A50/120 WR 110° 20″ 15.00 Bridge Trans. Midth Control(30) COMPONENTS WELLER Iron 25W 4.31 PHILIPS G8 Knobs Sm/Lg G11 Final Anode Lea E.W. Correction Coil WELLER Gun 12.00 THORN 3000 EHT THORN 3000 SCAN doluboM PR 2M2 Height Control Pair Tips Gun 3/16" Tips iron 42 A61/120 V/R 110° 24' VEGA 12" 90° (Jap Types) CME1520 (15" Mono) 51 18" A47/342X (Low Focus) 18" A47/343X (Stnd. Focus) 20" A51/110X 30.00 Transductor 90° RGB 10G Diodes 2.60 50 <u>RR1</u> T.20 Focus Control ANTEX 15/V Iron 5.20 THORN 9000 THORN 9000 3500 Mains ANTEX 25W Iron MULLARD COLOUREX 18" A47/343X 5.20 Switch K30 Focus Unit G11 or 39 3 W resist. 19" A49/120X 30.00 59.00 PYE 731 Mains Filter Choke THORN 1591 Iron Stands 2.20 19" A49/12UX 22" A56/12UX 22" A56/14X 25" A68/20UX 26" A66/12UX 26" A67/20UX 22" A56/14UX (410X) 110° 26" A66/40X (410X) 110° 19" A49/120X 20" A51/110X 22" A56/120X 60 6.50 THORN 1691 9 68 THORN 1591 Speakers Sm Lg ANTEX bits 65 THORN TX10 12.50 9.75 34.00 34.00 34.00 36.00 36.00 THORN 1615 PHILIPS KT3 RANK BUSHRANGER 4.10 4.50 ANTEX elements 2.20 Solder Sucker 6.50 25" A63/200X 26" A66/120X 1500 Controls NEW PRODUCTS Philips KT3 Posistor KT3 Elect. 225/25 380V 57.00 Frame 390K/line 470K Contrast 1K5 Solda Mop 72 26" A67/120) 58.00 1.50 2.50 PYE 741 7.95 DIY Solder 50 22" A56/500) 58.00 NEW PRODUCTS scent Torch 63.00 58.00 92.00 Focus Control Unit 20" A51/161X 22" A56/510X Sitter A51 570X A56 510 1.83 Video Leads 4.25
(Direct Recording)
Electrical Circuit Testers
Battery Chargers Universal6.75
L5 7" × 3§" Speaker 15R 4.25
5 pin-5 pin Audio leads 95 500G Solder 7.00 Fluorescent Torch Travel Plugs Philips Clock Radio Fluore 50.00 A56 510 A66 510 Thom/GFC 22" A56/5 A56 540X A66 540X 3.50 21,39 Thorn 9000 Focus Unit 3.25
Thorn 9000 Focus Control 3.25
8500 Focus Unit 4.75
TX10 Focus Controls 9.00 year warrant stion on 4 year delivery s charges Please order from latest copy Television magazine to avoid missis price increases. A66 500X P.I.L. TUBES — we can rebuild your own glass — please ring for quotes. Quotes

Video Lamps with holder

3.30

				Ī		-	LANGEAR
D 1	/ TI	JBES		11" QUICK E	type	Pack of 10	CM7061 Power Unit 12V 10.70 CM7062 Reg. Power Unit 12V 11.67
				100ma 250ma-500ma	i-750ma-1A	73 60	CM7060 MHA 10db 12V W/B 9.38 CM7065 VHF/UHF MHA W/B 12V 13.86 CM7067 UHF 12V MHA (Specify A-B or C/D) 10.21
PYE 169 (200/200/100/		ELECTRONIC TUNERS Mullard ELC1043/05	8.40	1.5A-2A-2.5A 11/ ANTISU		60	CM7088 UHF 12V MHA High Gain (Specify A-B or C/D) 15.19
PHILIPS 320 (400/400/35) DECCA 30 (400/400/35) DECCA 80 (400/350V)	200V) 2.07 0V) 3.40 3.00	Mullard ELC1043/08 4 P/B DECCA/GEC/ITT 6 P/B DECCA/GEC/ITT	8.40 6.80 7.50	250ma, 500m 1.5A, 2A	a, 600ma, 630ma, 750ma, 850ma, 1,	1.70	CM7053 Behind Set UHF Amp. (Mains) 12:13 CM7054 Behind Set UHF Amp. (Bettery e.g. Ceravans) 9.92
DECCA 100 (800/250V) DECCA 1700 (200/200/	3.97	4 P/B PYE 6 P/B PYE	9.00 16.00	2.5A, 3A, 5A 20mm ANTI	SURGE	2.70	CM7043 Second Set Amp. UHF 11.54
PHILIPS G8 (800/300V) PHILIPS G9 (800/300V)	2.30 2.21	PHILIPS G8 Tuner PHILIPS G8 Ass. (Square/E	10.50 arly) 13.50	80ma 100ma		4.80 2.50	CM7083 Behind Set UHF Amp, 3 Sets 14.54 CM7083 Dist. Amp. VHF/UHF 17db/output 12V 20.10 CM7108 VHF/UHF 8+1 Dist. Amp. 41.20
PHILIPS G11 (470/250) PYE 691/7 (200/300/35 PYE 731 (600/300V)	/) 2.90 0V) 2.70 2.31	PHILIPS G8 Ass. (Sloping/L PHILIPS G9 Tuner	10.50		e le, 630me, 800me, 1A, 1.25A, 1.6A,	2.20 2A 1.30 1.90	CM9700 27mhz CB Suppress. 3.86 CM8011 Outdoor Splitter (2 way) W/B 7.46
RBM A823 (2500/2500) RBM A823 (600/300V)		PHILIPS G11 Tuner ITT/PYE/GEC 7 Button P/B GEC 2110 6 way P/B	9.00 13.95 7.98	2.5A, 3.15A 20mm QUIC			CM9003 Rush Single Outlet
RBM Z146 (300/300/35 RR1 T20A (220/400V)	2.00	U321 UHF Tuner THORN 8800 SELECTOR	7.50	1A, 1.25A, 1.	a, 500ma, 630ma, 800ma 6A, 2A, 2.5A, 3.15A, 5A	90 60	CM9034 UHF Group Filters with DC Through Pass (state A/B/CD) 6.97 CM6006 6 Way Passive Splitter 10.97
ITT CVC5/9 (200/200/7 ITT CVC 20 (220/400V) GEC 2110 (600/250V)		(HMV Model 2725/6 way THORN 9000 SELECTOR	13.40	1" MAINS 2A, 3A, 5A,		1.00	CM7042 TV Games Combin. 2.88 : CM9009 Rush TV/FM Outlet 2.90
GEC 2040 (1000/2000/3 GEC 2040 (300/300/150	ISV) 1.19	U322 HITACHI 4 way Chan, Selec	7.20 tor (Also Rank A823) 10.75	Surface Mou	ACCESS. SB11 Indoor Splitt	er 1.91	CM7069 Tri Star Amplified Set Top Aeriel W/B 17.50 CM7090 Amplified Ceravan Aeriel 12V DC W/B 15.52
THORN 3500 (400/40V) THORN 950 (100/300/1	30 00/16/275V) 1.83	RR1 T20A 6 wey Chan. Sele RR1 T20/22/26	ctor 9.75 11.00		1.70 COB11 Single Out int. Outlets80 TRR/VSP per 100 1.18 Transformer	2.83	CM6038 UHF/VHF 625 Pattern Gen.* 50.00 CM6052 UHF/VHF PAL Colour Bar Gen.* 190.00 • While stocks last
THORN 1400 (150/100 THORN 1500 (150/150/ THORN 1500 (12/300V)		PHILIPS 8 way TIP Switch L	23.00	Coax Plugs P.V.C. Tape	per 10 1.80 CS200/SP Comb/S	plitter 3.03	RECTIFIER TRAYS DIODES
THORN 3500 (175/100/ THORN 3500 (1000/63)	/100/400/350V) 2.78	ITT CVC8 (5 wheel modified ITT 6 way with VCR (Also S PHILIPS KT3		F.M. Plugs PL259 Plugs	25 CS1000 Comb/Spli 40	6.15	THORN 1400 3 Stick 5.20 BA102 17 THORN 1500 3 Stick 5.20 BA115 13
THORN 3500 (1000/70\ THORN 8000/8500 (250	/) 86 10/2500/63V) 3.38	PHILIPS KT30 PYE 697 Repeir Kits	10.30 6.97	Reducers for	tors 35 PU1240 Power Uni r PL259 16 UP1300 M.H.A. U Odb Rejection	HF/VHF	THORN 1500 5 Stick 5.29 BA145 17
THORN 8000/8500 (700 THORN 8000/8500 (400 THORN 9000 (400/400)	1/350V) 2.56	ELC 2003	£16.50	27mhz	2.10 XTRABOOST XS2U 6db, · 12db, 4 //ay Amp UHF/	11.63 /HF	THDRN 3000/3500 7.98 BA155 14 THORN 8000 5.28 BA155 14
GEC (200/200/150/50) PHILIPS 69 2200/63V	7) 3.28 2.64 1.25	4A Double Pole On/Off Swit	tch ish 75	18db Top Tenna	1.80 Set Top 6 Nay Amp UHF /	33.75 /HF	THORN 9000 7.93 BA317 26
THORN 4700 P/C 25V PHILIPS 320 400/400/2	1.20 200V 2.74	Philips G8 Push On/Off Swit 4A Double Pole Rotary On/(tch 1.38 Off 66	Aerial M.H.A/P.U. Aerial Isolata	2.30 the pair 18.00 Super Set Top or Kit 2.06 XG8 High Gain As	5.50	DECCA 1/30/ 1830 4.48 BAX16 8 DECCA 1910/2213 Bradford 5.92 BB105B 30
THORN 1591/1691 470	0/25V 1.20	A1 Beam Switch (THORN 35 GEC 2110 A1 Control IM5 (R GEC 2040 On/ Off Switch	500) 70 led, Blue, Green) 58 88	4m Fly Lead 2m Fly Lead	1.20° A,B,CO or N/B	17.90	DECCA 80 6.60 BY 105G 30 DECCA 100 7.50 BY 105G 12
AXIAL	CERAMIC CAPACITORS	Dr/ Off Switch G11/ G12 Or/ Off Switch GEC/ TCE TX9	1.58		SUNDRY TUNER ACCES		GEC 2100 7.40 BY133 15 GEC 2200 (20AY) 6.50 BY164 45
Volts Mfd Price 6V3 33 9 10V 22 10	8kV (12kV vNag) 39pF 200pF each	SLIDER POTENT			1½" × ½"-2" × ½"-2" × ¾" RANK Drive Cams	35	GEC 2040/2028 6.60 BY176 85 GEC 2110 Pro Jan 77 7 90 BY179 63
47 10 100 10	150pF 220pF 40p 180pF 250pF	Lin or Log 470R-1K-2K2-44-	3 W/5R-6RB-10R-15R-20R 50R-100R-200R-500R	PUIS 60	GEC 2110 Tuner Neons SUNDRIES		GEC 2110 Post Jan '77 7.00 BY182 87 PHILIPS G8 Short Focus Lead 6.75 BY184 55
220 15 470 20	CERAMIC	10K-47K-470K 65 SKELETON	METRIC		Delay Lines DL60, DL700, DL50 CRT Tube Base		PHILIPS G8 Long Focus 550 6.75 BY206 14 PHILIPS G9 6.37 BY210/600 28 Pye/Philips K3 Tripler 6.65 BY210/600 28
16V 33 11 68 11 220 16	CAPACITORS 63V A range of pref.	PRE-SET POTS Standard or miniature	CONVERGENCE PHILIPS G8	POTS	EHT Final Anode Cap EHT Cable 25	53	PYE 691/3 6.58 BY210/800 33
1000 27 3300 53	values each 22pF-4700pF 6p	Horizontal or Vertical 100R-2M2 16p	5R-10R-20R-50R	60	6.3V CRT Boost Trans. 13A Plug Top box 1 Quick Set Adhesive	0 4.80	Philips/Pye KT3 6.67 BY298 22
25V 10 11 22 13	AFC UNIT PHILIPS G8	S + UNITS	SINCLAI	R	Moulded Plastic Hex. 6mm Tools	Trim	R.B.M. A823 (plug in) AV 7.60 BYX10 20 BYX36/10 30 KORTING (similar to Sigmont 1/41)
47 15 100 15 220 29	IF GAIN MODULE (Pye/ COA PANEL (Pye/Invict	/Philips) 9.00 ta/Ecko/Dynatron) 20.00	COMPUTE		Double End 4mm/8mm Trim To Focus Rod	oks 20 1.25	7.32 BYX36/000 35 ITT KB CVC5/9 6.90 BYX55/000 30
470 30 1000 55	REAR CONVERGENCE F		SPARÈS	;	Focus Holder Keynector Safe Block (mains) Cassette Drive Belts price each	7.00	ITT KB CVC20/25/30 (Mullard) 5.95 BYX/1/800 90 10 10 10 10 10 10 10 10 10 10 10 10 10
2200 51 4700 98 40V 10 10		CONTROLS ndle Length 44mm	We have a full range of for Sinclair comp		35mm 46mm	35	TV11 74 TV18 90 0A91 10
40V 10 10 22 10 400 48	5K-10K-25K-50K-100K-250 With D.P.S.T. Switch	0K-500K-1M 39p	Please ring and ask		57mm 66mm	37 39	TVI3 79 TV20 1.20 OA202 11 IN914 4 IN4001 4
63V 1 12 22 12	Log: 5K-10K-25K-50K-100 250K, 500K, 1M, 2N	Ж 81р <i>А</i> 1,25			71mm 76mm 90mm	41 43 43	MAINS DROPPERS IN4002 4 DECCA 20 2.48 IN4003 4
4.7 12 10 11 15 12	Dual gang Controls 16mm Rotary Controls	10K, 22K, 100K, 1M, 10K 39p	BATTERIES RECHARGE RX6 - HP7/NN1500	ABLE 1.39	110mm Torch (handy for tool box)	59 42	DECCA 27R/47R 1.40 IN4004 5 DECCA 56R/6R8 1.40 IN4005 5 R.B.M. A823 56R/68R 94 IN4006 5
22 13 47 19	THERMAL CUT OU		RX14 - SP11/HP11/NN RX20 - SP2/HP2/NN130	00 2.34	SM Neon Screwdriver	40	R.B.M. 161 82 IN4007 6 GEC 2000 /2018 70 IN4148 2
100 23 220 37	THORN 3000 2A Metal GEC 2040 Metal	1.60 TOOK 55 2.50 GEC TCE 55	RX22 PP3/ NN1604 VIDEO/AUD		4 pin 180° 5 pin	22 20	GEC 27840 64 IN4448 10 PYE 713/15 3R5/15/45R 1.80 IN5401 12
470 49 1000 58 2200 94	THORN 8000 Plastic	2.35 PHILIPS G8 DECCA, RANK 55	VHS E30 VHS E60 Scotch E120 Video Tape	3.06 4.00 5.00	Stnd. 5 pin Phono Plugs	20 12	PYE 725/31 3R0/56R/27R 1.84 IN5402 14 PYE 725 56R/27R 1.04 IN5403 12 PHILIPS 210/5050 30R/125R/2k85 IN5404 12
100V 10 13 22 15	THORN 3500 (5 pin con	SISTOR NETWORK nection) 1.98	Scotch E180 Video Tape BETA L500	5.13 4.90	Car Aerial Plug 2.5mm Jack Plug 3.5mm Jack Plug	14	1.75 IN5405 13 PHILIPS 210/5051 -/118R/148R 93 IN5406 16
47 20 100 36 220 70	PYE 731 (6 pin connecti THORN 9000 (Circuit Re	of, R704/7) 1.98	BETA L750 PHILIPS VCC 240	5.80 6.20	Stnd. Jack Plug Stereo Jack Plug	20 36	PHILIPS G8/5081 47R Section 50 IN5407 16 PHILIPS G8/5083 2R2/68R 95 IN5408 16 THORN 1400 1.20 ITT44 4
450 1 33 4.7 30	Please send large S.A.	PRODUCTS .E. for full EAGLE Catalogue	PHILIPS VCC 360 PHILIPS VCC 480 PHILIPS LVC 1700	8.30 10.21 15.70	5A Connector Block (12) Fuse Wire 5A-15A-30A Battery Plug Thorn TV's	5 28	THORN 1500 1.38 ITT2002 11 THORN 1600 1.77 Y969 (30V
10 30 22 65 33 75	DF615 Full Range Speal Multimetres KEW 7N	xer 6½" 8.95 2.000 5.25	VIDEO CASSETTE	CASES	Mains Connector 4 way 13A	5.00	THORN 3500 94 Thorn 3500) 89 THORN 8000 1.24 BZY15-24R 1.18 THORN 8500 1.36 BZY15-12R 1.18
500 10 32 600 1 41	KE /V 20 EM5	14.50 5,000 opv 9.95	Red/Blue/Green/Brown Book Type - Any Forms video Heads		TEST EQUIPMENT		BZX61/85 (1.3 W) 20 6/2-7/5-8/2-9/1-10/-11/-12/-13/-15/- etc. up. to
SPECIAL DIODES SKE 49 £1.09	EM10 EM50 EMC321 Carrying Case	10,000 opv 11.50 ; 50,000 opv 19.95 for above 2.25	3HSS 4HSS	38.00 38.00	Portable Oscilloscope Probes x10	155.00 10.90	75V.
SKE 5F £1.19 Y723 £1.30	Digital Meter TS1000 MM20	20,000 O.P.V. 21.95	PS3B Video Recorder Heads Philips V2000	42.00 52.00	KHP30 Measuring Probe (3	172.00 okv) 29.95	BZY9390, 18V 1.18 BZY88 (400MW) 10 2V7-3V-3V3-3V6-3V9-4V3-4V7-5V etc. up to 24V.
Y827 £1.42	MM50 MM100	50,000 O.P.V. 25.95 100,000 O.P.V. 36.50	ELECTROLU	BE	T120 RF Signal Injector Test Lead Set	4.00 4.20	HOW TO ORDER ADD 65p per order for Post and Packing (UK).
OIELECTRIC CAPS	MMT20 Case for MM100 T1206 2 Station Interco	16.95 15.95 m 6.95	PRODUCT Electrolube Adhesive	62	Degaussing Coil (stick type) Degaussing Coil (disc type)	17.00 24.00	(Export orders will be charged at cost.) THEN ADD 15% VAT TO TOTAL COST.
Valts D.C. 250V 0.91mF 84 400V 0.22mF 29	While	stocks last OKS (No VAT)	Electro-Mech lubricant Elect. cleaning solvent Freezer		SERVICE AIDS		Orders which contain aerosols or degaussing coils are very heavy — please add extra 30p per can/coil. First Class Mail is used whenever possible.
600V 0.1mF 38	Transistor Equivalent TVT 80 A-Z only	3.75	Foam cleanser Heat transfer compour	1.12 nd 1.14	SERVISOL Freeze-It SUPER SERVISOL	1.02	First Class Mail is used whenever possible. All enquiries S.A.E. please. VAT invoice on request.
0.047mF 46 0.033mF 33	TVT 80 2N/2S series of TVT 80/80 A-Z and 2N/	2S together 7.50	Silicone compound Special contact fluid (S	1.94 Snorkel) 3.20	SERVISOL Foam Cleanser SERVISOL Plastics Seal SERVISOL Silicone Grease	1.00 1.08	Goods are despatched on the day we receive your
0.1mF 35 0.22mF 66 0.47mF 98	LIN IC Books LIN 1 LIN 2	5.95 5.95	Permagard Elec. mech. lubricant p	1.52 pen 74	SERVISOL Tubes Silicone Gras SERVISOL Aero Klene	se 1.64 84	order. If for any reason we are out of stock we will try to inform you as quickly as possible.
1250V 0.1mF 59 0.91mF 1.15	Why not pay us a visit a	P.V. MICROCOMPUTER and see our range of Micros, ring for prices.	Software Books and Perip		SERVISOL Aero Duster SERVISOL Excel Polish SERVISOL Video Head Cleanser	1.10 88 82	We try our best to give a speedy, fair and efficient service. As our regular customers know, orders telephoned in before 4 p.m. will be despatched the
1500V 0.0022mF 28 0.0047mF 32 0.022mF 30	Spectrum 16K 48K	Vic 20 Commodore 64	Sharp authoris	are also sed dealers or the	Super 40 Fire Extinguisher 640G	1.50 2.50	same day. Give us a ring — we'll give you service.
0.033mF 62 0.005mF 65	Texas	Atari 800 Lynx	Dragon BB(and ac	C Micro ccessories	Heat Sink Compound 25G Silicone Rubber Tube 110G	1.08 2.98	Please ask if what you need is not listed — we will try to help. Prices are subject to change without notice.
2000V 0.0052mF 1.20	Quantity discounts on	application (Trade Only). Minim	niim of 5.		Solda Mop standard reel	74	

INCREASE YOUR PROFITS IMPROVE YOUR SERVICE WITH RELIABLE COST EFFECTIVE TEST EQUIPMENT

LEADER LCT-910A C.R.T. TESTER-REJUVENATOR

Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W C.R.T's.

- * Tests for shorts and leakage between
- * Tests cathode emission characteris-
- Separately checks condition of guns.
 Removal of shorts and leakage be-
- tween electrodes.

 Checks heater warm-up characteris-
- tics.

 ★ Rējuvenation of low emission cathodes with automatic timing.

 ★ Super rejuvenation with manual con-
- ★ Complete with tube base adaptors.
 Size: H 230mm W 330mm D 120mm.





CLOPT TESTER
Revolutionary L.O.P.T. tester. Operates in dynamic mode which actually tests the LO.P.T. under high voltage conditions without de-soldering or removal.

Size 75 ×100 ×40 mm. Supply 240V AC

PRICE £25,99 +£3,VAT

CRT TESTER-REJUVENATOR

BK's C.R.T. TESTER-REJUVENATOR Tests and rejuvenates blue, green & red guns separately. Fitted with delta and P.I.L. sockets. Compact size $120 \times 65 \times 60$ mm. Supply 240V AC

PRICE £32.00 + £4.80 VAT





PRICE £175 + £26.25 VAT

LOPT TESTER

BK's REVOLUTIONARY DYNAMIC 'LOPT' TESTER



HAMEG HM 203-4 20MHz **DUAL TRACE OSCILLOSCOPE**

*CALIBRATION OUTPUT

*CH1 ADD AND INVERT FACILITY

*ALT/CHOP SWITCH

*ALICATOR SWITCH
*LARGE RECTANGULAR SCREEN 8 x 10 gmm.
*PUILT IN SEMICONDUCTOR COMP. TESTER
*SIZE 285mm x 145mm x 380mm.
*SUPPLY 110-125-220-240V AC 50-60Mz

2 YEAR WARRANTY

Analogue Multimeters
Digital Multimeters
Oscilloscopes Oscilloscopes
Signal Generators
Digital Frequency Meters
Pattern Generators CRT Tester/Rejuvenator T.V. Field Strength Meter Digital Capacitance Meter LARGE S.A.E. FOR COMPLETE LIST.

ALSO AVAILABLE

The new Thandar SC110A represents a break-through in oscillo-scope development. The SC110A is ONLY TWO INCHES thick and

Full Sized Performance

10 mV per division sensitivity.

10 mV per division sensitivity.

Full trigger facilities are provided including TV frame, or TV filtering.

Runs on 4 to 10V DC via disposable batterias, re-chargeable cells, or AC adaptor.
Size 255mm x 148mm x 50mm.

weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope. FITS IN A BRIEFCASE

PRICE £165.00 + £24.75 VAT

SPECIFICATION:

*BANDWIDTH DC-20MHz *SENSITIVITY CH1,CH2 2mv-50V/DIV *TIMEBASE 40mS to 0.25 CM TRIGGER DC-40MHs Auto-Normal-TV

WITH COMPONENT TESTER

PRICE

£264.00 + £39.60 VAT Optional probes as above

U.K. Post Paid, Export orders welcome, please deduct V.A.T. and enquire for Overseas carriage cost. Barclaycard/Access orders welcome, or Cheque, Bank Draft, etc., with order please. Large S.A.E. for technical leaflets of complete range. Delivery normally within 7 days.



+ £3.45

* FULLY GUARANTEED

Dept. 'T',

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572



SPECIAL PROMOTIONAL OFFER

BUY 3 OR MORE

A56-120X

ONE YEAR GUARANTEE UP TO THREE YEARS)

ONLY **£23.80** + VAT

OFFER ENDS 31st MARCH

Callers only. To Luton or any of the stockists – Please phone first. - Send for a fully comprehensive price list and a wall chart of approx. 1800 colour tube types (including Base Connection Diagrams) that can be reprocessed

WELL VIEW

114-134 Midland Rd. Luton, Beds.

Open Mon-Fri 8am-6pm, Sat 9am-5pm. Tel. 0582-410787

Your Local Tube Stockist:

Well View, Southampton. Tel. 0703 331837. Retach Ltd., Northwood, Middx. Tel. 09274-27019 West One Distributors Ltd., Chesham, Buckinghamshire. Tel. 0494-778197

Rushden Rentals Ltd., Rushden, Northants. Tel. 0933-314901 Daventry Rentals, Daventry, Northants. Tel. 03272 77436

Please note that we have no connections whatsoever with any other business having similar name to ours.

20AX APOLLO **30AX**

HIGH TEMPERATURE PUMPED COLOUR TUBES

Fast Mail Order service to any part G.B. Delivery 2-3 days. Just phone for a quotation. Delivery Manchester area free same day. Two year guarantee. Fitting while you wait or in your home £20.

18" A47 - 342 ×343 470 BEB22 (£45.00) £37.00 19" A49 - 120 ×/192 × £37.00 20" A51 - 220 ×/110 ×/161 - 510JKB22 (£45.00) £38.00 A56 - 120 ×/123 ×/140 ×/410 22" £38.00 25" A63 - 120 × £39.00 26× A66 - 120 × A67 - 120 × /140 × /150/200 £39.00 20AX 56-510 £48.00 30AX 56/66-540 £48.50 20" - 22" SOLID STATE COLOUR TVs FULLY SERVICED & SOAK TESTED, VERY RELIABLE WITH GOOD TUBE £61.00,

WITH NEW TUBE £83.00 inc DELIVERY 061 799 0854 24 hour answering service. 43 Clarke Cres, Little Hulton, Nr. Manchester M28 6XM.

CENTREVISION

For Video, Television, Audio MANUFACTURERS SECONDS

Plus selection of modern TV's: T20 9000 etc.

Hybrids at give-away prices.

Also:

Tubes, Parts, Stands etc, plus working sets.

Sloper Road, Cardiff. Telephone: 0222 44754

Switch to the biggest wholesaler of quality late model used TV's

- Thousands of Quality Sets always in stock
- Colour/Mono/VCR's and Audios available
- Murphy/Pye/Philips/Sony/National Panasonic and other big names
- We are big we buy in bulk we offer you the keenest prices
- Cash and Carry or we will deliver
- New and used stands always in stock



SCOTTS THE TELEVISION CENTRE

8-10 RHODA STREET, (Off Bethnal Green Road) LONDON E2 Telephone: 01-739 3123

Working/Serviced Philips 22"-26" G8 520	£35.00
Working/Serviced Philips 550's	£45.00
Working/Serviced Bush 22" s/state	£30.00
Working/Serviced Pye 18" Chelsea	£49.00

TV STANDS £2.50



AND MANY MORE MAKES IN STOCK!

LONDON'S LARGEST SUPPLIER OF GOOD WORKING TV'S

★ FREE DELIVERY TO THE GREATER LONDON AREA ★

TELEPHONE NOW 01-739 3123



13 WORCESTER ST., WOLVERHAMPTON, WV2 4LJ Tel: (0902) 773122 Telex: 336810



Telepart Pattern Generator

* Exceptionally light and durable
* Pocket size for outside service
* PP3 battery power source
* Five different test patterns for colour
and mono TV * Cross hatch grid * Dot matrix
* White raster
* Horizontals * Verticles

**Porizontals * Verticles*

A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customers home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10x7.5x4 cm and weighs only 190 grams.

PRICE £14.95 (Subject to V.A.T.) POST & PACKING £1.15



FREE CAREER BOOKLET

Train for success in Electronics Engineering, T.V. Servicing, Electrical Engineering—or running your own business!

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the fields of electronics, T.V., electrical engineering—now it can be your turn. Whether you are a newcomer to the field or already working in these industries, ICS can provide you with the specialised training so essential to success.

Personal Tuition and 80 Years of Success

The expert and personal guidance by fully qualified tutors, backed by the long ICS record of success, is the key to our outstanding performance in the technical field. You study at the time and pace that suits you best and in your own home.

You study the subjects you enjoy, receive a formal Diploma, and you're ready for that better job, better pay.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY

ELECTRONICS ENGINEERING

A Diploma Course, recognised by the Institute of Engineers & Technicians as meeting all academic standards for application as an Associate.

T.V. & AUDIO SERVICING

A Diploma Course, training you in all aspects of installing, maintaining and repairing T.V. and Audio equipment, domestic and industrial.

ELECTRICAL ENGINEERING

Address

A further Diploma Course recognised by the Institute of Engineers & Technicians, also covering business aspects of electrical contracting.

RUNNING YOUR OWN BUSINESS

If running your own electronics, T.V. servicing or electrical business appeals, then this Diploma Course trains you in the vital business knowledge and techniques you'll need.

															_	_			_	_	_	_		Ī	_					
			2	18									á				٠,	."	-											
,	1				è		,	6	•		4			í	í,	1	ſ	1						4						





EAST CORNWALL COMPONENTS


NEW 1984 CATALOGUE NOW AVAILABLE - Many prices reduced - range increased - fully illustrated. Price 65p, per copy + p&p (free upon request

with orders over £5) - inclu	ides 30p. Credit Note, special of	offer sheets, order form and pre-paid envelope. SEND NOW FOR YOUR COPY.	
400mW Plestic 3V-75V 8p each. 10/75p 1.3W Plastic 3V-200V 15p sech. 10/ 1.5W Flange 47-47V 21.40 2.5W Plastic 7.5-75V 21.26 each 20W Stud 7.5-75V 87p each Elistegrated Circuits. (El EACH	TBAA61BX1 4.50 UPC1181H 1.60 TBAA700 2.85 UPC1212C 1.30 TBAA700 2.85 UPC1212C 1.30 TBAA800 1.60 UPC123DK 3.80 TBAA810 1.00 UPC135DC 4.25 TBAA810S 1.20 UPC137BH 4.40 TBAA810 1.60 UPC2002H 2.80 TBAA890 3.88 TBAA890 3.00 TERMINIAL	W 1RO to 10M (E12 Range)	600, 2.82. mA, 125, .6, 2,
AN214Q 3.88 SN76533N 1.60 AN715Q 2.90 SN76650N 1.05 CA3065 1.75 SN76660N 0.75 CA4031P 2.88 SN76666N 0.80 CA4102 3.30 STK015 6.50 CA4250 3.50 TA7105P 3.20 CA4400 2.98 TA7120P 2.20 CA4402 3.07 TA7129P 2.30	TBA950/ZA 3.05 BLOCKS TBA990 1.88 5 amp. 12 way 0.19 TCA450C 3.90 TCA270S 4.00 TCA270S 4.02 TCA2800 3.10 Antex 15W (for 5.00	Wy pack 1 0 sech value E12 - 2R2 to 2M2 730 pieces 52	for
LC7120 5.33 TA7130P 1.65 LC7130 5.26 TA7172 1.80 LC7137 5.16 TA7173 5.50 LM380N 0.80 TA7172P 1.80 LM1303N 2.52 TA7176 2.50 HA1151P 3.12 TA7202P 4.18 MC1310P 1.85 TA7204P 1.86 MC1310P 1.85 TA7204P 1.50 MC1312P 2.25 TA7208P 3.27 MC1327P 1.26 TA7208P 3.27 MC1330P 0.83 TA7222P 1.88 MC1340P 1.86 TA7222P 1.88 MC1340P 1.86 TA7223P 3.68	TDA4400 3.80 Antex 25W iron 8.20 TDA1003A 5.50 Antex elements 2.00 Antex bits 0.95 TDA1006A 4.50 Spare nozzles for TDA1100 3.50 Antex Soldering Antex Soldering TDA1200 2.98 antex Soldering TDA12700 3.70 Antex Soldering TDA1327A 3.66 Antex Soldering TDA1327A 3.66 Antex Soldering Antex Soldering TDA1327A 3.66 Antex Soldering Antex	10	0.95 1.15 0.80 0.68 0.85 1.08 1.05 0.78 1.34 0.93 0.95 1.28
MC1352P 1.80 TA7609P 4.28 MC1358P 1.30 TA7611AP 2.88 MC1496L 1.15 TAA2163 2.48 MC1496L 1.15 TAA2163 2.48 ML2318 2.10 TAA550 0.60 ML2328 2.10 TAA550 0.60 ML2328 2.30 TAA511A12 3.50 NE655 0.25 TAA630S 3.90 C-mos 555 0.88 TAA661B 1.70 NE556 0.80 TAA700 2.80 SAA1024 5.35 TAA840 3.38 SAA1024 8.40 TAD100 2.80	TDA2002 2.80 ALL SERVISOL TDA2030 4.60 PRODUCTS TDA2030 2.78 Switch Cleaner 0.88 TDA2140 5.90 Circuit Freezer 0.96 TDA2521 4.10 Foam Cleaner 0.84 TDA2530 2.70 Silicone Gresse TDA2540 3.80 (Agrosol) 1.00 TDA2541 3.80 Altistatic Spray 0.82 TDA2550 3.50 Plastic Seal 0.88 TDA2551 3.20 Fire Extinguisher TDA2551 3.20 Fire Extinguisher TDA2551 3.20 620 2.80	MULTIMETER SPECIAL MULTIME	00. 0.
SAS560S 1.85 TBA120 AS, SAS560S 1.85 S.S.A.SB 1.30 SAS550 2.85 0.T.U UQ 1.32 SAS590 2.82 TBA120B 1.30 SC9503P 1.10 TBA231 1.45 SL432A 4.00 TBA281 2.66 SL901B 5.20 TBA395 1.20 SL917B 6.25 TBA480Q 1.50 SL1327Q 1.10 TBA40Q 2.30 SN76003N 2.44 TBA510 2.80 SN76013N 1.90 TBA510Q 2.80 SN76013N 1.90 TBA510Q 2.80 SN76013N 1.90 TBA510Q 2.80	TDA2591 2.98 Video Head TDA2593 2.98 Cleaner 0.88 TDA2510 3.20 Silicone Grease TDA2511A 2.90 Solida Mop (Std) 0.72 TDA2680 3.50 (L/Gauge) 0.72 TDA3950A/8 2.60 Additional P&P on UPC5574 2.95 NIEGAD UPC56684 2.95 NIEGAD	VA1033/34/38/ VA1033/34/38/ VA1033/34/38/ VA1033/34/38/ VA1033/34/38/ VA1033/34/38/ VA1033/34/38/ VA1033/34/38/ VA1077 O.31 VA1077 O.31 VA1079 VA1	0/10 5/10 0/10 0/10 5/10 5/10 5/10 0/10
\$N76110N 1.12 IBA540/Q 1.40 \$N76115N 2.00 IBA550/Q 1.82 \$N76131N 1.65 IBA550/Q 1.82 \$N76121N 1.65 IBA550Q 1.80 \$N76227N 1.10 IBA550 1.50 THANSISTORS + DIODES	UPC1025H 2.90 Charges (narges UPC1025H 0.90 PP3, AA, C, D UPC1156H 4.20 Price £5.00 UPC1163H 0.98 10 for £5.00	Value Valu	0/10 0/10 5/10 0/10
Type	Price Price Type	Cl. Type Price	e (C) 88 80 0.76 10.00 1

EAST CORNWALL COMPONENTS
119 HIGH STREET
WEM
SHROPSHIRE SY4 5TT TEL: 0939 32689

ORDERING: All components are brand new and to full specification. Please add 45p postage/packing (unless otherwise specified) to all orders and then add 15% VAT to the total. Either send cheque/cash/postal order or send/telephone your Access or Visa number. Official orders from schools, universities, colleges etc most welcome.

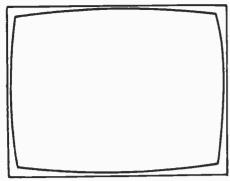(Do not forget to send for our latest catalogue – details at top of advertisement.)



EDITOR

John A. Reddihough

ASSISTANT EDITOR

Luke Theodossiou

ART EDITOR

Roy Palmer

ADVERTISEMENT MANAGER

Roy Smith 01-261 6671

CLASSIFIED ADVERTISEMENTS

Barbara Blake 01-261 5897

PETER GRAVES

Please drop us a line to let us know your new address.

FRONT COVER

Our thanks to Hitachi Sales (UK) Ltd. who provided this month's cover photograph showing the Hitachi Model VIP101P CED video disc player.

Investment decisions

The Tele-Jector story is an intriguing one. It seems that the directors of a firm called London and Liverpool Trust, whose main operation is the distribution of business equipment (photocopiers, computers, etc.), got this bright idea for making money. A subsidiary, Tele-Jector, would instal projection TV equipment in pubs and clubs and would generate a substantial revenue from hire agreements. The clever bit is that it wouldn't cost anyone anything. The publican would be able to recover the cost of his Tele-Jector through the advertising revenue it would produce, and with enough Tele-Jectors out on lease the whole exercise would soon pay for itself so far as London and

Liverpool Trust were concerned. Only it didn't work out like that.

The height of its fame came when Tele-Jector made an £8m bid, just over a year ago, to obtain exclusive rights to show Football League matches on its screens. London and Liverpool shares shot up to a high of 350p. Unfortunately for Tele-Jector the bid fell through – the broadcasting authorities made a successful counterbid, and it transpired that not all League clubs would be prepared to participate. Even if they had, it would have taken some effort to recover the £8m and the cost of the other programme material provided in cassette form and the Tele-Jectors themselves. Looked at in this light the scheme looks rather less clever. It seems even less clever when you consider the underlying assumption – that pubs and clubs would be filled with avid Tele-Jector viewers. One wonders whether the directors of London and Liverpool Trust ever set foot in their local. If they had, they might have discovered that the box, when present, is seldom given much serious attention. At least the publicans appreciated that, and far

fewer than were estimated to be necessary to make the venture pay decided to take it on.

At the end of the day London and Liverpool Trust were faced with the cost of providing programme material for an uneconomically small number of Tele-Jectors, and those publicans who had taken it on found that there was negligible advertising revenue. There was also some criticism of the leasing terms. London and Liverpool Trust's shares dropped to a low of 11p, and liabilities of £18m incurred by the project threatened the

company's existence. A sad case of things going badly awry.

Is there a lesson to be learnt from this? Well, it could be an example of one of Parkinson's laws at work – that a group of people, in this case the directors, will often take a collective decision that each individually considers to be highly doubtful. It could also be an example of making an investment with a view to generating a quick profit. Of more relevance to television, doesn't it seem analogous to some of the headier notions of bonanzas to be made from developments such as cable and satellite TV? There was indeed a time when ITV was "a licence to print money", but it looks increasingly as if that was a once only state of affairs. The more TV there is, of one sort or another, the greater the competition and the harder the economic climate.

There has been much criticism that those responsible for investment in the UK seek too quick a return on their money. I'm not at all convinced that this is fair. In a highly uncertain world, is it reasonable to lock up funds in long-term projects whose outcome is difficult to foresee? We need industrial investment for sure, but investment in projects

that don't turn out is worse than no investment at all.

In an interesting article in Electrical and Radio Trading, Erik Arnold argues that, amongst other things, the UK TV industry has reached its present sorry state due to lack of investment in new product technology. Those of us with fairly long memories might question this. For a start, successive governments through the fifties to the mid-seventies engaged in stop-go economic policies. Consumer taxes and credit control product of TV simple means of putting such policies into effect, but meant that industries such as TV bore the brunt of the accelerator/brake business. This sort of thing hardly encouraged long-term planning – you can't be expected to undertake expensive investment when wondering how to finance a warehouse full of unsold TV sets awaiting the next "go". Firms nevertheless did invest in research and development, but if I read him right Erik Arnold argues that they didn't go about this in the right way. They left much of the technical research to component suppliers whilst concentrating on assembly. So we don't have integrated firms that can develop and produce their own tubes, i.c.s and systems through to the end product offered to the consumer.

This is largely due to the structure of the industry and is not necessarily a bad thing. It would hardly be sensible for every TV firm to produce its own types of tube - a case of reinventing the wheel time and again – while i.c. development is best left to those with semiconductor technology know-how. This doesn't mean that setmakers simply sit back and make use of whatever's on offer. That way does lead to disaster, in terms of unreliable consumer products. Developing reliable components that will survive in the stressful conditions of a TV set and the knock about home environment is a two way business between the component manufacturer and his customer, while UK setmakers have often taken the initiative in going to component manufacturers with their requirements and jointly working on the solution. Whether it would be better for component manufacturers and setmakers to be part of the same company is something that could be argued about endlessly. Provided they both have technical compentence it

shouldn't really matter.

This does leave unanswered the criticism that the UK's industry has failed to come up with new product technology such as the VCR. For this you need a certain vision and confidence that perhaps we lack today. But really successful new products are not everyday occurrences. There is probably no harm in manufacturing under licence rather than undertaking the original research.

Long-distance Television

Roger Bunney

Now that we're into the new year it's possible to summarise the conditions during 1983. They were pretty good! Sporadic E signal propagation continued after its usual ending in late August, and there was a little F2/TE reception as the sunspot cycle dwindled. More encouraging were the good tropospheric openings towards the end of the year – indeed December both started and ended with spells of enhanced tropospheric propagation. There were good tropospheric openings during all months from late August – my own most interesting catch was ORF-1 (Austria) ch. E9 on September 26th, a 20kW transmitter at Bruck near the Hungarian border.

Reports from our Australian friends suggest that they are enjoying a good SpE season, and one must hope that this heralds a good season ahead for us in the UK. With the 405-line transmitter closures, many will be able to enjoy Band I/III relatively clear of local transmissions. This could be the last year of Band I being free from interference, so make the most of it!

What with other activities during December, reports of reception normally slacken off. From the letters received however it seems that the main event was the good tropospheric opening on December 27-29th. Reception was mainly from the E./S.E., with signals from W./E. Germany, the Benelux countries and France. The prevailing high-pressure system first gave a signal lift on the 27th, with strong French u.h.f. signals and W. Germany (just). There was further improvement in Band III and at u.h.f. on the 28th, with a peak on the 29th when signals extended from W. Germany across the UK as far as Wales. Unusually, the emphasis was on W. German Band V signals, reaching as high as ch. E60. The in-vision teletext/scrambled information from Paris ch. 8 was present, but not the mystery ch. 5. RTL (Luxembourg) was widely seen, the PM5534 test pattern carrying the identification "RTL PLUS". We've a report that RTL have been using both PAL and SECAM at their ch. E7 outlet. ATV activity was high during the period. F3YX, to the S.W. of Paris, was seen here at Romsey - a new station for me and a most welcome bonus to see out 1983!

Meteor shower/scatter reception has been remarkably

good, with two prime showers during the period. The Geminids produced active conditions over the 10-14th, the peak on the 13th producing signal pings and more sustained bursts throughout Band I, reaching into the lower end of Band III (chs. E5, E6 and R5) on occasions. In early January the Quadrantids again produced MS reception – the peak appeared to be on the evening of the 3rd.

There was little SpE reception over the period. The log is as follows:

23/12/83 NRK (Norway) ch. E3.

30/12/83 Unidentified signals on chs. R1 and R2. 3/1/84 RAI (Italy) IA; unidentified signals on E3, 4. 4/1/84 RTVE (Spain) E2, 3, 4; RTP (Portugal) E2.


My thanks to Simon Hamer (Powys), Hugh Cocks (E. Sussex), Graeme Wilson (Cleveland), John Tellick (Surrey) and Ryn Muntjewerff (Holland) for reception reports.


Robert Copeman reports that December started off quietly in Australia so far as SpE reception is concerned, though conditions had opened up by the end of the month – with little evidence of double-hop propagation unfortunately. He mentions that the increasing number of Band II f.m. radio stations in operation there is giving greater scope for v.h.f. DXing. The Network 0/28 (cultural service) is to loose most of its ch. 0 outlets with a move to u.h.f. operation only. This should ease DX reception by 1985.


Jim Maden reports a "lousy" season in S. Africa, with no sign of ZTV Gwelo ch. E2. This is most unusual and he wonders whether the transmitter is now off the air. Bulawayo ch. E3 has moved to Band III - due to interference from Europe! Jim views TSS-1 via the Ekran 714MHz downlink, and comments on the flashing diamond caption previously mentioned - at TSS programme closedown. The translation of the Ekran caption reads "don't forget to switch off the television", with the words in red on a white diamond with a blue background. The centre words that flash are "switch off", and there's also an 800Hz tone. During various October/November TE openings Jim received RTVE, RAI and RTP, the highest frequency signal being ch. E3/IA vision. Finally Jim mentions that TSS now use an African lady who speaks fluent Russian for the discussion of African affairs - so watch out for her on ch. R1 during the next SpE season . . .

Radio Receivers

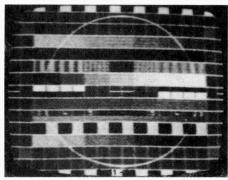In the January column I mentioned the Lowe Electronics AR2001 scanner, which covers 25-550MHz. Revco Electronics have since told us that the professional version of their SX200n will shortly be available at some £400. It



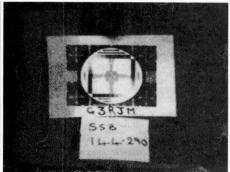

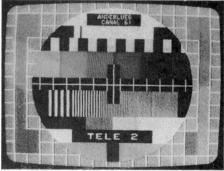

Left: The new Rumanian test pattern (similar to DFF/GDR), received by Ryn Muntjewerff from Bucharest on ch. R2. Centre: ATV reception in Holland by Ryn Muntjewerff, at 435MHz. G3RJM card (Newcastle) with G8PZF background. Right: Tropospheric reception by John Tellick (Surbiton) from Anderlues, Belgium, during the September opening.

covers 26-520MHz, with the only gap being 88-108MHz. A.M. and f.m. signals are catered for: the sensitivity is $0.5/1\mu V$ (f.m./a.m.) at v.h.f., $0.5/2\mu V$ (f.m./a.m.) at u.h.f. The image rejection is 50dB at v.h.f., 40dB at u.h.f., with sharp selectivity. The unit will interface with certain NEC computers for outboard control, for example to increase the channel memory and for high-speed reprogramming. Perhaps more interesting is the availability of a prescaler that gives operation at up to 3GHz! More details can be obtained from Garex Electronics, 7 Norvic Road, Marsworth, Tring, Herts HP23 4LS (0296 668684).

Perhaps more down to earth is a range of Tandy (USA) portables for TV sound. Their 1984 catalogue features four receivers, one hand held, with full system M v.h.f. channel coverage – one receiver has full u.h.f. coverage as well. The Portavision 55 covers low and high bands (Bands I/III) and has a 70 channel u.h.f. tuner (click stops plus fine tuning). The price is \$79.95. The Portavision 5 has similar v.h.f. TV coverage plus air/PMR at 108-175MHz and is perhaps the best for general v.h.f. coverage at \$59.95. The Personal Portavision covers just the low/high TV bands at \$44.95. All three models include MW and 88-108MHz, give good sound reproduction and are sensitive (there's a tuned r.f. stage for each band).

I'm using the Portavision 5, which I've realigned from ch. A2 sound to ch. E2, i.e. from 59.75MHz to 53.75MHz. By shifting the coverage in this way a gap has appeared at the top end of the low band, but ch. R3 (83.75MHz) can still be received. Apart from this gap there's full coverage over 53-220MHz. The radio has proved to be very useful during SpE openings since it will resolve both f.m. sound and the a.m. vision buzz. In addition to the integral whip aerial, there's a Motorola (car radio) socket for an external aerial. You can't obtain these sets from Tandy UK (in part due to the battery/ 115V a.c. operation) but you can obtain them by mail order from Tandy Corporation, Export Sales, Fort Worth, Texas 76102, USA. Note that you may get involved with import duty/VAT - it may be easier to obtain sets secondhand via a friend.


News Items

Belgium: The French language ECS downlink channel "TV5" (uplink at a French station near Troyes) came into operation on January 2nd, with programmes from 1900-2200 nightly. TDF-A2 is used on Monday and Thursday, SSR on Tuesday, TDF-TF1 on Wednesday and Sunday, TDF-FR3 on Friday and RTBF on Saturday. TV5 will not be scrambled until mid/late summer. The channel is for feeding via 12GHz terminals to cable networks and is also available on ch. E56 (Brussels). There are rumours that BFBS propose to instal transmitters in Belgium.

UK: Mention was made of a pirate station, "Second City Vision", in the June 1983 column, operating in the Birmingham area on ch. 40 after the closedown of the local BBC-2 station. There have been press reports recently of activity over a five mile area, using the name Telstar Television. The authorities have been trying to close down the aspiring broadcaster, whose output includes current feature films etc. No reader has reported reception of the station, whose location appears to be the Edgbaston area. If it's still around, a good time to try would be at Easter – Bank holidays seem to be favourite times for this activity.

Luxembourg: The RTL-Plus channel came into operation on January 2nd. It's intended for W. Germany but is being carried on Belgian cable systems. Start of programmes is

SOUTH WEST AERIALS

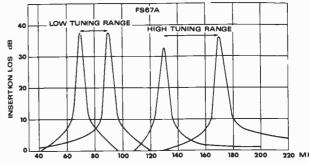

This is the specification for the Post Office FS67A twin stop filter — just one of the expanded filter range carried by South West Aerials. Additional filters now supplied (to PO standard) are single notch (Bands 1 or 3); Low Pass; High Pass; Low/High Pass and the twin stop filter as above. The FS67A has an adjustable Low Band and similar High Band stop, ideal for preventing TV and breakthrough from adjacent PMR/mobile transmitters. Housed in a bright aluminium housing with i/p skt, o/p flying lead. Our range of filters covers channel pass/stop; Band pass/stop; single/double notches for all bands, di/triplexers; UHF/UHF combiners; all band aerial stackers; Group pass UHFs — to name a few!

Our catalogue at 54p covers these and more — aerials, amplifiers, Das, hardware. Extensive ranges of TV/FM DXing equipment (Band 1 DXing arrays), TVDX multi-standard mono/colour TVs and books.

TVDX multi-standard mono/colour TVs and books.

Your one-stop mail order source for local fringe and TVDXing equipment.

FS67A Twin stop (Low/High band PMR) filter @ 35dB stop depth Polytron Single channel 'in line' notch (Band 3, UHF Grp A or E)

Triax MTH13 wideband Band 3 13 el. 11.9Bd gain. Very high quality
Hirschmann/Stolle R0250 aerial rotor/control consul (uses 3 core

cable) £47.85
BATC Publications — 'Amateur Television Handbook', Vol 1 £2.40; Vol 2 £2.75,
'TV for Amateurs' £2.40

The above prices include VAT, postage/large items Securicor. Access/Barclay-card accepted. Include SAE please with ALL enquiries and customer consultancy service. Delivery 10-14 working days for stock items.

South West Aerials, 11 Kent Road, Parkstone, Poole, Dorset BH12 2EH. Tel. 0202 738232

LINE OUTDUT TRANSFORMEDS

IV LINE OUTP	UI	IKANSFUKIVIEI	42	
ADD 15% VAT to ALL prices.		Delivery by return of post		
If the Transformer you	requi	re is not listed please pho	ne.	
Bush A792, A793 single std mono A774 single std mono A816 solid state mono Z712 T16a T16b mono portable A823 A823b A823ev colour Z179 Z722 series colour T20a T22 series colour	8.50 9.00	DECCA MS1700 2001 2020 2401 mono MS2404 2420 2424 mono 1210 1211 1511 portable GYPSY portable CS1730 1733 colour CS1830 1835 colour '30' series BRADFORD colour 70, 80, 100 series 110, 130 series	8.00	
WINDING T20A T22 Z179 T26 FERGUSON HMV MARCONI	5.51	PHILIPS 210 300 series mono 320 series solid state mono	8.00 8.50	
1590 1591 1592 1593 mono 1612 1613 1712 mono 1690 1691 mono 1600 1615 series mono 3000 3500 EHT or SCAN	8.00 8.00 8.50 9.74 P.O.A.	G8 series colour G9 series colour G11 series colour KT2 Lopt KT3 Lopt	8.00 8.50 14.98 9.00 10.60	
9500 9600 9650	11.70 11.52 9.56 P.O.A.	KB-ITT VC200 VC205 VC207 mono VC300 VC301 VC302 portable CVC1 CVC2 colour CVC5 CVC7 CVC8 CVC9 colour	8.00 8.00 9.00 9.00	

8.00

8.00

8.00

11.00

10.00

8.50

INDESIT, GRUNDIG, TANDBURG,
TELEFUNKEN, FIDELITY,
KORTING, TYNE, B+O.
Price on application.
HAMOND COMPONENTS
(Midland) Ltd.
416, Moseley Road,
Birmingham B12 9AX.
Phone 021-440-6144

3133 3135 M1501H portable mono 8.00

2047 to 2105 3112 to 3135

2114 portable mono 1201H

DUAL STD hybrid colour

SINGLE STD hybrid colour

SINGLE STD solid state 90°

'GAIETY" FINELINE

Tidman Mail Order Ltd., 236 Sandycombe Road, Richmond, Surrey. Approx. 1 mile from Kew Bridge.

CVC20 series colour

L.O.P.T TESTER

CVC40 series

CVC30 CVC32 series colour


Total Price Including VAT.


Phone: 01-948 3702 Mon-Fri 9 am to 12.30 pm. 1.30 to 4.30 pm. Sat 10 am to 12 pm.


9.00

8.00

£6.30

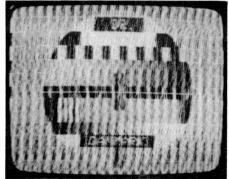

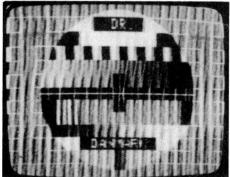

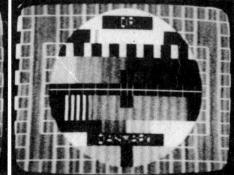

Tropospheric reception from Denmark ch. E8 on December 4th, showing progressive reduction of the bandwidth from 6 to 3 to 2MHz to reduce interference, using the equipment described in the February-April 1982 issues of Television.

1727 local time (1657 Sunday) with closedown at 2230/2300 (2400 Friday/Saturday). The system B PAL transmissions are on ch. E7, the test pattern carrying the identification "KANAL 7" at the top and "RTL PLUS" at the bottom. It's expected that ch. E24 will also shortly be used

Denmark: The experimental South Jutland service TV Syd will continue until next year. If successful, this could lead to full regional Danish TV. The main transmitter is at Sonderjylland on ch. E7 with 60kW e.r.p.

Satellite News

Luxembourg has applied to the ITU for permission to use four channels at 10·7, 10·95, 12·5 and 12·75GHz. The satellite would be privately funded and able to provide reception using 1m dishes. Norway, Sweden and Finland have reached agreement on the Tele-X satellite project. Ireland is inviting organisations to tender to provide the proposed Irish satellite TV service. It's hoped that this will be on air in 1987, with five channels.

The Indian Insat 1b satellite is apparently giving good results. There will eventually be two TV channels, with direct to community receivers as with the 1975-6 SITE experiment via ATS-6.

The North American conference on satellite services has confirmed eight slots for US DBS use in the 12GHz band, between 61.5° and 175°W. These include spot beam coverage of Alaska and Hawaii. The conference decided on a service area signal strength of $-107 dBW/m^2$ - the USA had sought -105dBW/m². The USA had also hoped for more slots to cater for time zone variations. STC in the USA plans to commence a five-channel 12GHz service this autumn covering the N.E., and hopes that domestic reception via 2ft dishes will be possible. Due to congestion, domestic 4GHz craft are to use a reduced orbital spacing of 2°. As a result, receiving dish specifications will need to be tightened. Domestic dishes in the USA range from 6-12ft and are usually of the prime focus type, with a comparatively wide beamwidth. Whereas an 8ft dish will work well with the present 4° spacing, with minimal adjacent satellite/channel interference, a 2° spacing could lead to problems, particularly with dishes of less than 8ft diameter.

The US government has approved funds for the VOA-TV service to Europe from the TDRS-1 satellite at 41°W. Transmissions are expected to start this May/June. The Home Box Office company has apparently acquired the use of an ex-US DOMSAT which is being moved to approximately 40°W, with test transmissions expected to be in progress by the time you read this and a service starting in March. The Television Entertainment Group, a

consortium consisting of Goldcrest (UK) and four US firms (including HBO), hopes to use this satellite to provide a 24-hour programme of films, sport, pop music etc. The HBO/VOA services would be in the 4GHz band, intended for cable distribution.

From our Correspondents . . .

Bud Lloyd Bennett, now in Bahrain, is using two stacked long Yagi aerials – Dutch Kamco type assembled in Kuwait – and a 40dB head amplifier to receive the 714MHz signals from the Ekran satellite at 99°E. He says that reception is weak, though improvements are being worked on – including a notch filter to remove Bahrain ch. 55 which causes interference.

Nick Harrold has built a 12GHz unit, to the basic Chris Wilson/Grahame Harding design featured in the September 1982 issue, and has received OTS using an 8ft. petal dish (who said a petal wouldn't work at 12GHz?). The Satellite plc programmes are scrambled, but with sync reinsertion a viewable picture can be received. The coded sound is impossible to decipher however. Some days after this reception the channel was transferred to the ECS-1 satellite. TDF-FR3 is still present via OTS, with the cogwheel type scrambling illustrated in the January 1984 issue (page 126) and noisy SECAM. For 4GHz reception Nick is now using a commercial 110° LNA. He reports that AFRTS is received with good colour from the 1°W Intelsat. RTM (Morocco) has moved to the 31°W Intelsat (from 27.5°W) and is much weaker.

We've received another letter from Mel Thurlbourne in the Falklands. He reports that TV signals are now being received, generally from 1800-2100 local time, with the aerial system pointed to the north. They are on chs. A2 and 3, most likely via SpE. Charlie's Angels and Kung Fu have both been seen – in colour and dubbed in Spanish! An Argentinian news programme has also been seen. The reference oscillator in the decoder needed a tweak to obtain correct colour lock, and since then things have been going well. Stanley residents use VCRs, to the UK system I. The Cable and Wireless Intelsat link is now in operation, but for communications only.

Bill Cotterill (Tipton, W. Midlands) received most of Europe, plus Jordan ch. E3, via SpE during the summer months, using the TV-DX system described in the February-April 1982 issues, a Hugh Cocks upconverter/preamplifier, and a wideband Band I aerial (Ian Beckett's design, see June 1976 issue). For u.h.f. he uses a Jaybeam JBX21 array, also a system L-I converter (see February 1983 issue). The early December tropospheric opening produced excellent signals from France, Holland and Belgium.

POST A PART ELECTRONICS 236 FURTHERWICK ROAD, CANVEY ISLAND, ESSEX Telephone 0268 690868 Telex 99305 ROSSER G.

TRADE COUNTER NOW OPEN

ORDERS DESPATCHED SAME DAY
ADD 60p P&P, THEN 15% VAT.
ADD POSTAGE FOR OVERSEAS ORDERS.
ORDERS WITH AEROSOLS, PLEASE ADD 25p PER CAN.

1				
	Pye 713 Speaker 5" × 3" 70Ω 1.00 Pye 713 Complete Tube Base Panel with Focus Silder & Leads 2.75 Pye 713 Complete Tube Base Panel with Focus Silder & Leads 2.75 Pye 713 Control Knobs 4 for 50p Tube Base Socket TTC CVC32 45p Tube Base Socket Thorn 3000/8000 etc 50p C Inserter 16 Pin 50p Large IC Extractor 50p Crystal 4.43MHz 65p EHT Lead & Cap For Spiit Diode Lopt 40p Anode Cap Assy + Lead 12TCD-CT-1665p Degause VDR Ez990 /HP230 3000/8000 25p Casters Set of 4 1.90 Double Fuse Holder on Small Pax Board 10p 20mm type 5p Direct Panel Mounting 20mm Fuse 6p Clips (pair) 15p Single Fuse Holder on Small Pax Board 4p As per early 3000 mains input 4p FHT Cable 12 for 48p 13A Plugs 16 for 5p IX9 Tube Base and Panel 4p 3K PSU PL22 edge connector. + Lum to PSU INew) HUM340 T12 on Heatsink<	10 10 10 10 10 10 10 10	1,00 1,00 1,00 1,00 1,65 1,92 2,08 80 80 1,40 1,10 70 1,30 80 1,10 1,10 1,10 1,10 1,10 1,10 1,10	200+200+100 325V 65p Thom 3K5 2.25
	TXS Back Ground Control 10K 15p	BC107	1.30 1.30 1.25 1.45 1.30 1.00 1.10 48 40 42 42 45 61 2.5 30 2.10 1.35 3.50 3.50 3.50 3.50 3.50 2.00 1.96 2.00 2.00 2.00 2.00 2.00 2.00 2.00 2.0	200+100 325V 65p Thorn 3K5 2.25
	Thorn Mains TX 3000/3500 7.50 Thorn Mains TX 8000/8500 10.00 Thorn S.D.P.T 8000/8500 3.50 Thorn S.D.P.T 8000/8500 3.50 Thorn S.D.P.T 8000/8500 6.00 Thorn C.D.P.T 8000/3500 6.00 Thorn LOPT 1615 7.25 Thorn LOPT 1615 7.25 Thorn LOPT 1800/91 7.25 Thorn LOPT 1800 9.80 Thorn LOPT 1800 9.80 Thorn LOPT TAY 9.85 Pye LOPT 713 10.00 Thorn LOPT TAY 9.85 Pye LOPT 713 10.00 Thorn LOPT TAY 9.85 Saryo LOPT AM—WM—4 7.30 Diode Split LOPT AM—WM—4 7.30 Philips LOPT 68 7.80 Saryo LOPT AM—WM—4 7.30 Philips LOPT 68 7.80 Saryo LOPT (CVC1) 4-2751 4-4700 171 LOPT CVC5-9 Bard 8752 10.25 Bard 8752 10.25 Bard 8752 10.25 Korting AZ1010 10.25 Korting AZ1010 10.25 Korting AZ1010 10.25 Korting AZ1010 10.25 Siemens V1155 11.75 Salora FR0029 10.25	MIZ37B 2.00 SN76530P 1.30 TBA720A 2.49 TDA2690A MIZ39B 2.86 SN76545 1.40 TBA2600 1.62 TDA3560 MIZ39AP 1.25 SN76562N 1.00 TBA2600 2.08 TDA3560 MIZ39AP 1.25 SN76666N 80p TBA1440 1.92 TEA1009 MIZ455P 1.80 SN76666N 75p TBA1440 1.92 TEA1009 MIZ455P 1.95 TCA270C 1.05 MIZ4426P 1.92 TEA270SA 1.05 MIZ4426P 1.92 TEA270SA 1.05 MIZ4426P 1.05 MIZ4426P	1.50 6.00 2.99 3.48 1.95 5.00 2.50 2.50 2.50 2.50 2.50 2.75 3.00 1.75 2.75 3.00 1.75 1.80 1.80 1.80 1.80 1.80 1.80 1.80 1.80	Pye 713 Luma Deley Line 90p 9

UNIVERSAL PROGRAMME SELECTOR FOR VARICAP TUNING

UK Read, Design No. 1006611

6 way interlocked d.p. switch 100 K tuning potentiometers


Top quality through hole plated pcb

Dimensions: 5" by 2½" by 1" Ideal for replacement when original parts are obsolete or unobtainable

Template guide supplied for drilling of your own fascia design

Range of pre-cut and drilled fascia/mounting kits for selected TV chassis enabling our unit to be fitted without further cutting drilling or modification

All orders despatched same

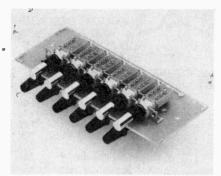

SEND LARGE S.A.E. FOR FREE CATALOGUE

We supply the following:

Programme Selectors, Tuners, Triplers, Transistors, Resistors, Capacitors, Integrated Circuits including European and Japanese types, Plugs, Sockets, Motors, Drive Belts, Audio and Video Connectors and MUCH, MUCH MORE,

> ALL ORDERS DISPATCHED WITHIN 24 HOURS

DIRECT REPLACEMENT FASCIA/MOUNTING KITS

Type 30-80 Replace 7 piano-key unit as fitted to Decca/Telefunken 30 and 80 chassis

Type 30-C Replaces 7 piano-key unit as fitted to Decca console using long

perspex illuminated control panel

Type 100 Replaces 8 position touch tune selector (AEG SAS 660 SAS 670) as

used in Decca/Telefunken 100 chassis

Type CVC8-9 Replaces 5 rectangular push button plus thumbwheel as used in

SELECTOR £11 + VAT - FASCIA/MOUNTING KITS (each) £2 + VAT

ALDERSON-JAMES LTD.

168 KINGS ROAD, HARROGATE, NORTH YORKS, HG1 5JG, TEL, 0423-60058

ELETRADERS

Forde Road, Brunel Industrial Estate, **Newton Abbot, Devon** Telephone: (0626) 60154

The Best Quality Sets Available **Anywhere**

Philips G8 550 £35 GEC & Pve Hybrid £5 **Grundig Solid State** £20 Decca Bradford £10 ITT CVC 5,8,9 £25

Also Philips G9, G11, ITT CVC 35, 45, 50, Thorn 9000, 9600, 9800, Bush T20.

All sets complete with excellent cabinets Full spares back-up of tubes and panels send for list e.g. PL509 £1, PY500 £1 Bulk terms to other wholesalers

☆ ☆ ☆

THE NO. 1 WHOLESALER IN THE SOUTH

VIDEO HEADS

BETAMAX Part No. P\$3B

MONOLITH

HIGH QUALITY UNIVERSAL VIDEO HEAD REPLACEMENTS FOR ALL VHS AND BETAMAX VCR MACHINES

VHS Part No. 3HSS (5mm Centre Hole) £29.95 PRICE VHS Part No. 4HSS (15mm Centre Hole) £29.95 EACH

£38.95 EX.

REPLACEMENT KIT (14 Pieces Boxed) £ 8.25 V.A.T. PLEASE ADD 15% V.A.T. PLUS P. & P. £1.50 PER ORDER OUR FULL CATALOGUE AVAILABLE ON REQUEST.
Please allow between 14 and 28 days for delivery.

AUDIO + VIDEO HEADS - MOTORS - PARTS

Suppliers to most U.K. Distributor/Service Organizations

THE MONOLITH ELECTRONICS CO. LTD. 5-7 Church Street, Crewkerne, Somerset TA18 7HR, England Telephone Crewkerne (0460) 74321 Telex 46306 MONLTH G

MAIL ORDER ADVERTISING

British Code of Advertising Practice

British Gode of Advertising Practice Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfill orders within 2B days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

Mail Order Protection Scheme
If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

become insolvent or bankrupt, provided:

(1) You have not received the goods or bad your money returned; and

(2) You write to the Publisher of Television summarising the situation not earlier than 28 days
from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you
how to make your claim and what evidence of paymont is required.

We guarantee to meet claims from readers made in accordance with the above procedure
as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement
in this magazine not, for example, payment made in response to catalogues etc., received as a
result of answering such advertisements. Classified advertisements are excluded."

The CED Video Disc System

Derek Snelling

The RCA CED (capacitance electronic disc) video disc system was launched on the US market on March 22nd, 1981. It was said to have been the biggest product launch in business history, and was the outcome of substantial research and development expenditure by RCA over a period of many years – RCA are reputed to have invested more in their video disc system than in the development of the NTSC colour system (shadowmask tube and all). RCA's work on video disc systems started in the early sixties, and the decision to go ahead with the capacitance system was made in 1978.

Acceptance of video discs in the USA was slow to start with, though greater success has been achieved more recently following price reductions. The CED system was launched on the UK market last October, with discs manufactured by RCA and players produced by Hitachi.

Basic Principles

The information on the CED disc is carried in a V-shaped spiral groove and consists of frequency-modulated capacitance variations. These variations take the form of vertical undulations along the track. Fig. 1 shows the principle. The disc is 12in. in diameter and is housed in a protective plastic caddy. It's removed from the caddy by the player and is never touched or removed from the caddy outside the machine. The caddy contains brushes that clean the record automatically upon insertion and removal.

The disc is conductive and is tracked by a diamond stylus (for durability) to which a metal electrode is attached. Thus the disc forms one capacitive plate and the metal electrode the other, the groove undulations producing capacitance variations of the order of 10⁴ pF. These undulations are approximately 850Å deep (it's their frequency that varies). The electrode tip is typically 2,500Å thick and the diamond tip straddles several undulations at once – it's important to appreciate that the diamond tip is merely a carrier for the electrode and doesn't "play" the disc in the way that an audio stylus does. The plastic disc is made conductive by adding carbon to the compound from which it's pressed.

The stylus tip electrode is connected to a tuned line resonant at 890MHz. This forms part of what is called the resonator assembly, which also includes an 896MHz oscillator whose output is coupled to the stylus driven line. The circuit is shown in Fig. 2 and the action in Fig. 3. Q101/C105/C106/L105/C108 form the 896MHz oscillator whose output is coupled by L103/4 to L102, the stylus driven line. The capacitance variations at the stylus tip alter the resonant frequency of this line slightly, as a result of which the position of the 896MHz oscillator's signal shifts up and down the trailing slope of the 890MHz response curve. The result of this is amplitude modulation of the 896MHz carrier. Since the depth of the undulations in the groove is constant, the amplitude modulation is constant. But the rate of the amplitude modulation varies, thus producing an f.m. output.

L101 couples this amplitude modulated carrier to the peak detector diodes D101/D102. C103 filters out the

carrier and the result, at the base of the buffer transistor Q102, is an f.m. output carrying the information stored in the disc's groove.

This is fed to a preamplifier before being sent for splitting into audio, chroma, luminance and DAXI information – all the signals are f.m. An automatic fine tuning signal is taken from the preamplifier circuit to varicap diode D103 to maintain the average centre frequency, i.e. to ensure that the 896MHz signal remains at the centre of the falling slope of the basic 890MHz response. The detected output from the arm must now be processed.

Processing the Sound Signals

Two subcarriers, 711kHz and 898kHz, are used for the sound signals. A block diagram of the sound processing system is shown in Fig. 4. Filters separate the two signals, the first of which carries mono sound with a mono disc or L+R (the same thing really) with a stereo disc and the second L-R with a stereo disc. On bilingual discs or discs

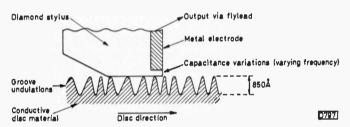


Fig. 1: Cross-section showing the stylus resting on the base of the V-shaped groove. The groove undulations, which cause capacitance variations, vary in frequency.

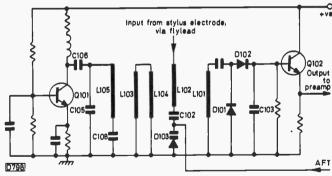


Fig. 2: The resonant circuits and detector used to retrieve the f.m. signal from the disc.

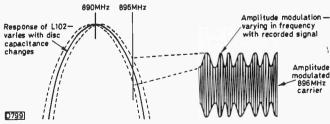


Fig. 3: Principle of signal retrieval. The frequency of the 890MHz resonant circuit varies with the disc capacitance variations, giving rise to an amplitude modulated carrier. The amplitude modulation varies in frequency.

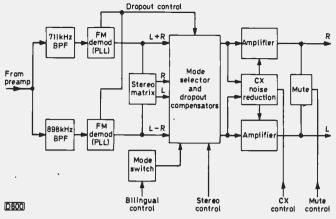


Fig. 4: Block diagram of the sound processing system.

with two sound tracks the main track is at 711kHz and the subsidiary one at 898kHz. The bandwidth is 30-15,000Hz, and the signal-to-noise ratio can be improved by 20dB by the use of CX noise reduction, which is a feature of some discs.

Video Signal Processing

The video signal processing system is shown in block diagram form in Fig. 5. A 1.5-9MHz bandpass filter passes the composite chroma/luminance signal to the video f.m. detector. The bandwidth of the demodulated luminance signal is approximately 3MHz, with the interleaved chroma signal on a 1.52MHz subcarrier – near the centre of the luminance bandwidth. The non-linear aperture correction system is used to eliminate phase modulation of the video signal by the 711kHz sound carrier. The technique used is to filter out the 711kHz component, invert it and then add it back to the video signal to provide cancellation.

The dropout compensation can replace up to three lines before signal degradation becomes noticeable.

A CCD (charge-coupled device) comb filter is used to

separate the luminance and chrominance signals – this is the standard PAL delay line technique, though in solid-state form. Because of the wide bandwidth of the CCD filter the chrominance output contains low-frequency luminance information. This is separated by a 1MHz low-pass filter and added to the luminance signal.

The 1.52MHz chroma signal obtained from the 3MHz low-pass filter is mixed with the output from a 5.95MHz voltage-controlled crystal oscillator to obtain a 4.43MHz chroma signal which is then phase altered to the PAL standard and added to the luminance signal for sending to the u.h.f. modulator. This produces an output for feeding to the TV set's aerial input socket.

A 4.43MHz crystal oscillator and phase detector are used to control the 5.95MHz oscillator. The phase detector's output is also used to operate the jitter servo circuit, whose purpose is to maintain a constant stylus-to-groove velocity in order to compensate for such things as warped or eccentric discs or an off centre hole. The result of such defects would otherwise be varying colour or horizontal instability of the picture. In addition, the outputs from the 4.43MHz and 5.95MHz oscillators are mixed to produce a 1.52MHz clock signal for the CCD comb filter i.c.

Another output from the 3MHz chroma low-pass filter, is the DAXI (digital auxiliary information) signal, which is recorded on lines 20 and 333 during the field blanking period. This information is used to tell the machine if the stylus is tracking correctly, whether a mono/stereo or bilingual disc is being played and also, by checking the field number, whether the stylus has kicked back one or more grooves or, in visual search, whether the stylus is kicking forwards or backwards correctly.

The Mechanics

The arm is a lateral tracking one driven by a d.c. motor. To ensure that the stylus remains centred in the groove, the position of the output signal coupling flylead is detected: if this moves off centre from the arm, due to the arm being ahead of or behind the stylus, an error signal to

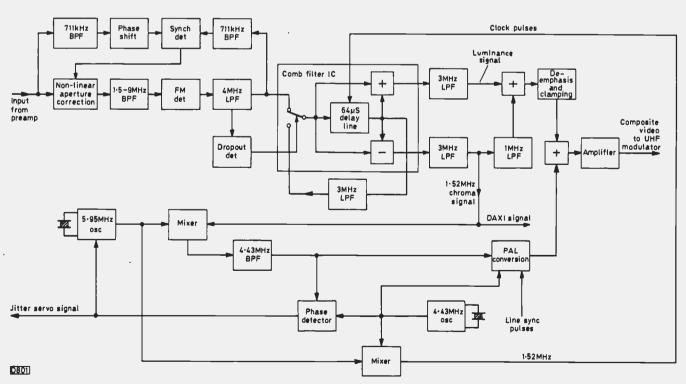


Fig. 5: Block diagram of the video signal processing system.

correct the arm position is generated. Fig. 6 shows the arm servo system.

The disc rotates at 375 r.p.m. on a turntable driven by a three-phase direct-drive d.c. motor containing an eight-pole rotor. The motor does not need to be locked to the mains frequency. Motor rotation is detected by a printed coil which generates a frequency proportional to the motor speed. This is used to control the motor speed – three Hall elements generate the three-phase drive current.

The arm assembly with the cartridge and stylus is interesting. It contains the stylus position sensors and three coils - the kicker, lifter and jitter coils. The kicker coil makes the stylus jump one or more grooves either forwards or backwards. It works by pushing (electromagnetically) on a small permanent magnet mounted near the stylus. It's used during search, pause and to nudge the stylus if it sticks in the groove. The lifter coil is used to lower the stylus on to the disc – only the stylus is lowered on to the record, not the arm assembly, unlike an audio record player. The stylus is also lowered on to a cleaning pad each time a disc is removed from the player. Power is required to lower the stylus: in the event of power failure the stylus rises automatically to prevent possible damage to the stylus or disc. The jitter coil moves the stylus forwards or backwards slightly in the direction of the groove, momentarily altering the relative stylus-to-disc speed to compensate for wow and flutter.

Practical Points

So much for the basic player. Now for a few practical points on the Hitachi range of models. There are three machines, the VIP101P, VIP201P and VIP202P. The VIP101P provides mono sound reproduction only. Features include pause (without picture) and ×16 forward search. The VIP201P and VIP202P provide mono, stereo or bilingual sound reproduction (depending on the disc) with ×120, ×16 and ×4 forwards and backwards search, pause (without picture) and step (a sort of freeze frame). The VIP201P has eleven-function remote control while the VIP202P has an optional wired eleven-function remote control system.

The $\times 120$ visual search is not visual search in the same sense as with a VCR. In this mode the arm travels across the disc rapidly, the stylus being lowered at intervals to sample the picture for a few fields – a sort of peep search.

The position of the arm on the disc is indicated by an LED fitted to the end of the arm. It's viewed through a window along the front of the machine. There's a rough scale in minutes along the window, to give an idea of how much playing time has gone – the maximum playing time is 75 minutes per side. Whether side one or side two of the disc is being played is also shown on the front: this is detected by a microswitch at the rear of the machine and is necessary because the disc can be inserted in the caddy either way up.

Once the machine detects that a disc has been inserted and the caddy removed – by correct sequential operation

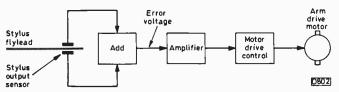


Fig. 6: The arm servo system.

Photo-interruptor
Arm motor beneath
Photo-interruptor plate

Arm assembly

Stylus

Cover

LED

Turntable

Loading motor

Caddy rail

(raises and lowers disc)

Fig. 7: Some of the mechanical aspects of the player discussed in the text.

of the door flap microswitch and a microswitch at the rear of the machine – the disc is lowered to the playing position and the arm moves across to the start of the disc. A metal plate attached to the arm passes between the two halves of a photo-interruptor: the plate has a hole in it, the position of the hole determining the set-down point. This plate can be adjusted using a test disc.

The cartridge/stylus can easily be changed by removing a small plastic cover on the top left of the machine, unclipping the stylus cover, pulling out the old assembly and dropping in the replacement. Also housed beneath this cover is a transit screw and spacer. These must be fitted whenever the player is transported, and removed prior to its use. The arm assembly complete with coils, tuned line, oscillator and preamplifier is considered by Hitachi to be a non-serviceable item that should be replaced complete.

Apart from these components the rest of the electronics are mounted on a single large panel in the top of the machine – the top can be hinged up and locked in the vertical position for servicing. A word of caution here. If the machine is operated in this position with a disc in place, you could well drop something on the disc, ruining the disc and possibly the stylus. If it's necessary to operate the machine with the top off, remove the cartridge/stylus assembly and trick the machine into loading by operating the two microswitches and the photo-interruptor in the correct sequence.

When you press reset, the arm returns to the rest position and the disc unloads ready for removal. If the disc is not removed, it will be lowered back into the play position and rotated after a few minutes. This is done to prevent the disc warping due to heat in the machine. The disc can be unloaded by pressing reset again.

Sound and Picture Quality

What does all this technology give us by way of picture and sound? Well, the quoted bandwidth is not significantly different from that of a VCR, and having seen the picture quality I'd put it at about equal to the better VHS machines, no sharper but with perhaps slightly better noise performance. The sound is of course vastly superior, though I've not yet heard the new Panasonic machine with hi-fi, helically-recorded sound. Although the price is half that of a VCR, it doesn't of course record. Neither does it have the improvement in picture quality and the extra features available with LaserVision, though you have to pay extra for all that.

Teletopics

8mm VIDEO

The 8mm video system, which has been developed for use in light-weight camcorders, is to be introduced by a number of firms later this year. Several firms have released details of their plans following Kodak's worldwide announcement of its intention to enter the field with the Kodavision series 2000 video system. Kodak have also gone into the video tape market, with a comprehensive range of open-reel and cassette tapes. Kodak's tape is being produced by TDK while the camcorder and its associated equipment will be manufactured by Matsushita.

Matsushita camcorders will also be sold by General Electric (GE) in the USA, where RCA will be selling Hitachi manufactured camcorders. Sanyo have also announced their intention to enter the 8mm camcorder market in the USA and have already exhibited prototypes. In Europe, Philips have brought forward plans to launch their VKR8500 8mm camcorder, with a possible launch date as early as June.

The Kodavision camcorders weigh about 5lb each (there are two models), are easy to carry and use, and share several features including a fast f/1.2 6:1 power zoom lens, a in. Newvicon pickup tube, and automatic white balance to adjust for colour temperature variations. The two camcorders also feature fast forward and reverse. five times visual search, and an electronic viewfinder - the latter provides a miniature monochrome TV display. The review feature enables the user to replay the last four seconds of the previous recording, and both camcorders incorporate automatic exposure control. Model 2200 features manual focus, two record/playback heads and a stillframe capability. Model 2400 features an autofocus lens with manual override, three heads for jitter-free still frame and frame advance, and provision to "write" the date on the tape as it's being recorded. The 2400 also has pushbutton fade in/out control and backlight control.

A key item in the Kodavision system is the cradle, which turns the camcorder into an easy to use playback device. To play an 8mm tape, the camcorder is inserted in the cradle which provides standard video and audio outputs. The cradle also serves the function of camcorder storage, and will charge the battery while the camcorder is in situ – the cradle can also be used to charge a separate battery to extend the equipment's recording time. In addition, the cradle is designed to include the optional



The Kodavision camcorder Model 2200.

Kodavision tuner/timer, which has 105 channel capability and offers twelve preset channel positions. The cradle is compatible with existing ½in. VCRs so that the material recorded on 8mm tape can be transferred to ½in. tape and vice versa. Most cradle functions can be controlled by a remote control unit that comes with each cradle.

The Kodavision system is due for release in the USA this summer and in the UK this autumn. UK prices have not been decided, but on a rough conversion of the US prices announced you could expect to pay some £850 for the basic 2200 camcorder, £1,000 for the 2400, £120 for the cradle and £190 for the tuner/timer.

JVC, who have also developed 8mm equipment, maintain that the goal of compactness is easier to achieve using standard ½in. VHS tape. JVC's Video Movie VHS camcorder (not Victor Movie as we called it last December) is now in production and has been launched in Japan. Shipments to the USA are due to start this spring and to Europe during the summer. It uses a VHS-C E30 cassette, an ultra small drum and a new parallel loading system. The pickup tube is a ½in. Saticon.

It seems therefore that home video movie enthusiasts will soon have on offer at least two competing systems – there's also Betamovie, which was first to appear. As regards price and weight, there will probably be little to choose between them.

DBS CO-OPERATION

Last month's leader discussed some of the problems of starting a UK satellite TV service for direct domestic reception. Since then, high level talks have been held at the Department of Trade with representatives from the BBC, the IBA, the Independent Television Companies Association and United Satellites with a view to saving the project from collapse. Senior government officials from both the Home Office and the DTI were present. The BBC has proposed a compromise plan under which the two broadcasting authorities would share the costs of a four-satellite system providing three TV channels. There are both legal and practical problems, which are being discussed by a tripartite working party headed by the managing director of the BBC's DBS operation Bill Cotton, the IBA's director general John Whitney and London Weekend Television's chairman Brian Tesler.

STEREO TV SOUND

The BBC's experimental stereo TV sound transmissions from the Crystal Palace transmitter have been mentioned before in this column. The outcome was that whilst a second f.m. sound carrier, as used in W. Germany, could provide a largely satisfactory stereo sound service with terrestrial TV a digitally modulated second sound carrier might prove to be a more attractive solution. The advantages of the digital approach have since been confirmed by tests carried out at the Wenvoe transmitter – this area was chosen because the nearby mountains can cause severe multipath propagation (ghosting) and it was considered important to establish that digital sound signals can be received satisfactorily under such conditions.

These tests have given very encouraging results. The effect of multipath reflections was found to be very small, the digital signal providing excellent stereo quality even in areas of extremely low signal strength where the picture was badly impaired by noise. It was also found that the additional signal passed satisfactorily through the five-station relay chain used to feed one of the remote valleys. The conclusion is that the BBC's digital system is fully

viable. It uses a bit rate of about 700 kbit/s (sufficient for two high-quality sound signals), the phase modulated carrier being set at about -20dB with a sound-vision carrier separation of about 6.55MHz.

A further full scale trial from Crystal Palace on BBC-2 is planned to ensure that the system will not give rise to compatibility problems with the very wide range of monophonic TV sets in use. Discussions are being held with industry, the IBA and the Home Office to achieve an agreed UK standard, but it seems that regular stereo TV sound transmissions in the UK could be some four years away.

SKY CHANNEL

Subscribers to Radio Rentals' cable TV network at Swindon are now able to receive five hours a night of programmes from Satellite Television plc broadcast via the ECS satellite. The transmissions can be received on a 10ft dish and the cable network operators pay Satellite Television ten pence a month per subscriber. It's expected that the service, which at present consists of mainly American programmes, will shortly be available via other pay-TV cable networks. Satellite Television's main source of income comes from advertisements carried on the transmissions, which are also taken by cable networks in Norway, Finland, Switzerland and Malta. The uplink is from the PO tower in London.

NAMES

Morphy-Richards is a well enough known brand name that's never before appeared on a TV set. There are now two Morphy-Richards 12in. monochrome portables however, the T730 and T739. The latter in addition incorporates an LED clock with 59-minute sleep feature. Some more brand names that might turn up on the service bench in the future. Saisho, sold by Dixons, uses Panasonic chassis; Triumph, sold by Currys, uses Toshiba chassis; Solarvox, sold by Comet, uses ITT chassis.

TRADE RESULTS

Figures for the third quarter of 1983 show CTV deliveries ahead of 1982 by 6.5 per cent. For the first time there was a fall in VCR deliveries, of 5.2 per cent, possibly reflecting the effects of the Japanese-EEC import limitation agreement. Monochrome portable deliveries increased by 23 per cent and an even greater increase in deliveries of teletext equipped sets occurred.

During the first nine months of 1983 CTV deliveries increased by 20 per cent, with imports increasing from 31 to 35 per cent. It appears that there was a surge in imports towards the end of the year, consisting mainly of Grundig and ITT sets from W. Germany. There's been a change in the market, with imports accounting for a greater proportion of large-screen CTV deliveries than previously.

VCR NEWS

The VHS system has been given a significant boost with the announcement that leading US TV manufacturer Zenith Radio will in future be marketing VHS instead of Beta machines. Until now the VHS system has held 75 per cent of the US market.

Two keenly priced V2000 system VCRs have been released by Grundig. The 1600 is a basic, simple to operate top-loader with a suggested price of £369. The two-speed Model 2080 is able to provide up to 16 hours' recording/playback time in the half-speed mode. Features include instant record (single button operation), a go-to

facility, freeze frame with manual or auto advance, and an eight-programme capacity which can be set up to a year in advance. The suggested price is £479.

Heron Electronics have introduced a playback only VHS machine. It's manufactured by Funai and will be sold under the Ingersoll brand name at a suggested retail price of just under £300. Heron's managing director Ron Sulkin comments that with the large amount of prerecorded material now available there's a need for an inexpensive player-only machine.

The latest addition to the Ferguson range is the 3V38, a slim front-loader with a suggested price of £429. The specification is similar to the 3V35 (£489) but without remote control. ITT's latest Model VR3605 also retails at £429. Panasonic's latest models are the NV370 (£516.50) and the two-speed NV688 (£633.50).

SCOPEX BACK IN PRODUCTION

Production of the Scopex Model 14D15 double-beam oscilloscope and the 14D10 model with TV delay system for line selection is now in full swing again, only a few weeks after the acquisition of Scopex assets by Bridage Scientific Instruments and the formation of the new company Scopex Electronics Ltd. Enquiries should be sent to Scopex Electronics Ltd., 63-65 High Street, Skipton, North Yorkshire BD23 1EF (0756 69511).

EXPANSION IN WALES

Matsushita (Panasonic) have announced a £1m investment plan for their Cardiff TV factory, where CTV production is being increased from 600 to 1,000 sets a day. About twenty per cent of the plant's output, which includes radio tuners marketed under the Technics brand name, is exported.

GEC-Hitachi are to start production of 14 and 16in. colour sets at their Hirwaun plant. Two new production lines will be installed to produce the small-screen models. At present about a third of the UK CTV market of 3·1 million sets a year consists of the smaller screen models, a high proportion of which are imported.

EAST CORNWALL CATALOGUE

A new mail order/trade catalogue is available from East Cornwall Components. In addition to the usual items there's a comprehensive listing of i.c.s, multisection capacitors, test equipment and tools. A retail shop is also in operation at the mail order address – 119 High Street, Wem, Shropshire SY4 5TT (0939 32689).

HEAD CLEANING

A new head cleaning cassette for use with VHS machines has been introduced by Bib. It can be used wet or dry and incorporates a new non-abrasive spun-bonded polyester cleaning tape made to Bib's specification. The cleaning time is ten seconds and the cassette provides 35 cleanings, i.e. about four years' average use. Bib recommend regular head cleaning after 40-50 hours' playing time to remove dust and oxide particules. The new cleaner has a recommended retail price of £9.98 including VAT.

Issue 9 (December 1983) of Ferguson Feedback contains a detailed article on head cleaning. Thorn recommend cleaning by hand, using chamois leather and either isopropyl alcohol (IPA) or Isceon (MMV3601). The chamois leather should be wrapped tightly around a finger and moistened with the cleaning fluid. Then clean the heads and surrounding area by rubbing backwards and forwards across each head six or seven times (don't clean

in the vertical direction or with the heads in motion). Apply sufficient pressure for the head profile to be felt through the leather. Finally rub backwards and forwards six or seven times with dry chamois leather. Thorn comment that the main cause of poor head cleaning is the application of insufficient pressure to the head face.

MOVE TO REAR PROJECTION TV

Mitsubishi have added a 40in., rear-projection set, Model VS400R, to their range of projection sets on sale in the USA. The set features a wide viewing angle (120°), high picture brightness (180 foot lamberts) and a 139-channel frequency-synthesis tuning system. A six-element glass lens is used instead of the conventional three-element plastic one. Mitsubishi officials are convinced that there will be a significant move from front-projection TV sets to rear-projection types.

Sanyo have launched a 46in. rear projection set, Model CVP9110T, in the UK. The set features a stereo sound system delivering up to 10W per channel and uses three 7in. tubes each with its own lens. A suggested price of £2,700 is quoted.

ITT RECEIVER-MONITORS

ITT have launched two new 14in. colour receiver-monitors to meet the increasing demand from microcomputer

users. The basic RL2301/1 has RGBS inputs while the RL2301/M also has provision for a PAL composite video input and loop-through facilities. Both sets are equipped for off-air reception. ITT comment that the use of RGBS (RGB plus sync) inputs provides superior colour graphic displays since the video input does not have to be decoded.

DIGITAL TV TRANSMISSION

The BBC's Engineering Research Department has been carrying out tests on methods of reducing the information rate required for digital television. It is generally assumed that a basic information rate of 216 million bits per second (216 Mbit/s) is required for a TV signal consisting of separate brightness and colour components. The BBC has recently carried out a field trial using a system that reduces this rate to less 140 Mbit/s - the component signals were passed through the British Telecom 140 Mbit/s digital circuit between London and Birmingham. Two high quality stereo sound signals, using the BBC's NICAM-3 digital coding system, were also transmitted over the circuit. There was negligible loss of picture quality. During earlier experiments composite PAL signals were passed through a digital London to Birmingham circuit. The BBC's next target is a further bit rate reduction to 53 Mbit/s, the eventual target being a bit rate less than 34 Mbit/s.

Vintage TV: The Ferguson 841T

Vivian Capel

Thorn have for many years been the UK's leading indigenous TV manufacturer. The firm did not enter the TV field at the outset however, and the earliest model appears to have been the post-war Ferguson 841T. There were two versions, with 9in. (MW22-7) and 12in. (MW31-7) tubes – the e.h.t.s were 5 and 6kV respectively. They were single-channel, t.r.f. sets for reception of the Alexandra Palace transmissions. The design seems to have owed something to radar practice, with lots of EF50 valves (eleven) and a transitron oscillator as the field generator.

This was one of those models that had to be treated with respect by the service engineer, the e.h.t. being mains derived. Though the voltage was low by modern standards, it packed a hefty punch and could be lethal because of the high current that could be passed. The chassis was mains isolated however, by a single transformer that supplied all the chassis' power requirements. This had a centre-tapped h.t. secondary winding (see Fig. 1) which fed an FW4-500 full-wave rectifier. There was a 4V filament winding for this and a separate 6V winding for

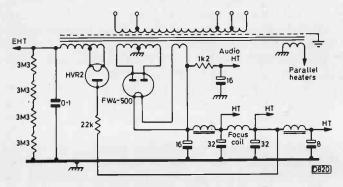


Fig. 1: The Ferguson 841T's power supply circuit.

the parallel connected valve (plus c.r.t.) heaters. Then there was the e.h.t. winding, plus a bit for the HVR2 rectifier's filament. The arrangement of the e.h.t. rectifier circuit was a bit unusual. The rectifier was connected to the low-voltage end of the winding, with its anode returned to the h.t. line. Thus the h.t. voltage was added to that obtained from the e.h.t. winding. A string of $3.3 \text{M}\Omega$ resistors was connected across the e.h.t. supply, providing a constant load to improve the e.h.t. regulation and also serving to discharge the $0.1 \mu\text{F}$ e.h.t. reservoir capacitor.

One of the reasons for the comparatively large valve complement (twenty plus c.r.t.) was the use of EF50s in the r.f. sections. These all-metal envelope valves did not have as much gain as the later r.f. pentodes that took their place. No fewer than five were used in the vision r.f. stages, the first two being common to the sound channel. A further two were used in the sound only r.f. circuits. In cases of low gain it was often necessary to replace most if not all the EF50s. They tended to suffer from loss of emission, and replacing one or two would make only marginal improvement. Another problem often encountered with this type of valve was noisy and intermittent pin contact. Fortunately in the 841T the five vision r.f. pentodes were mounted in a row along the rear edge of the chassis, and were thus easily replaced.

An EA50 was used for vision demodulation, driving another EF50 that acted as the video amplifier (see Fig. 2). Since the c.r.t. was grid modulated, the video output at the anode of V11 was positive-going. The vision interference limiter circuit operated on a time-constant basis: large positive-going spikes caused the diode across R74 to conduct, thus short-circuiting the output. The diode used was part of an EBC33 whose triode section served as the line blocking oscillator.

An unusual feature was the use of d.c. restoration in both the video feeds, to the tube and to the sync separator. D.C. restoration in the latter path was required because the sync separator had to operate with negative-going sync pulses. This complicated the design of the sync separator quite a bit – it had to be saturated during the video part of the signal, then driven to cut-off by the sync pulses, thus producing positive-going pulses at its anode.

A.C. coupling without d.c. restoration means that the signal's d.c. conditions vary with the content of the video signal – a line with a predominantly white content will have a different mean level than one that's mainly dark, due to the different proportions of the negative- and positive-going portions of the waveform. Hence the brightness level will float and the sync pulses will move up and down. Another problem is the fact that the video amplifier must be able to accommodate larger signal excursions and be able to deliver about twice the output required with a stable d.c. level. With an EF50 used as the video amplifier, there was little gain to spare.

The use of a.c. coupling to the c.r.t.'s grid avoids the problem of tube damage in the event of failure of the video output pentode, and the inclusion of a d.c. restorer maintains the correct d.c. conditions at the grid. Many devotees in the early days maintained that grid rather than cathode modulation gave superior results, but the complications, both in the tube drive and sync separator circuits, led to the general adoption of cathode drive.

The sync separator stage used an EF50 and this was followed by a further EF50 which was used to amplify, invert and integrate the field sync pulses. Yet another EF50 was employed as the field oscillator. This was

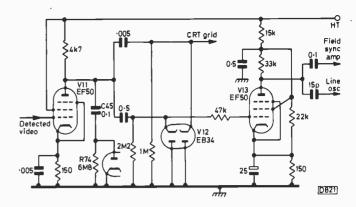


Fig. 2: The video amplifier and sync separator circuits, with d.c. restoration in both feeds.

arranged as a transitron, with feedback between the anode and control grid and also between the screen and suppressor grids. The operation has been described before in this series. The EL33 field output valve was RC coupled to a transformer driving the scan coils.

The line timebase was simple indeed in those preflyback e.h.t. days. The blocking oscillator's output drove an EL38 output pentode that operated as an amplifier rather than a switch, with simple transformer coupling to the scan coils.

The audio circuit was conventional, using an EBC33 and EL33 output pentode, but the negative feedback loop incorporated a tone control. Sound was considered important in those days!

One wonders whether there's anyone left at Thorn who can recall the 841T. It's a far cry from the TX series!

VCR Clinic

JVC HR7700/Ferguson 3V23

The problem was no clock display. If the clock crystals on the tuner/timer board are red ones, the first step is to change them to blue ones. Other minor capacitor changes have been suggested but are not essential. In this case however these changes did no good despite the fact that the timer microcomputer i.c. was deprived of clock oscillations. The culprit was in fact the microcomputer i.c. itself.

S.B.

Sharp VC8300

It's not often that we get bounce backs, to adopt a phrase from the world of TV repair. A certain Sharp machine (VC8300) with a servo fault caused some concern however. The initial report was of a tracking fault after the machine had been in operation for a couple of hours. So it was soak tested, with the scope tied to the capstan servo. A small servo adjustment seemed to cure the problem, a fact that seemed to be confirmed by making a double check from cold the following day.

Some days later it was back with us again, this time with the complaint that the fault occurred just after switching on. Again we gave it a lengthy soak test, with the scope monitoring the capstan servo ramp and sample pulses at TP711 and TP712. This proved that long-term drift was present. The sample pulses started off high up the ramp,

Reports from Steve Beeching, T.Eng. (C.E.I.), Derek Snelling, Mike Phelan, Les Harris and Mick Dutton

then slowly moved down over a period of three-four hours. Further checks for capacitor or other component value drift proved inconclusive, so we came to the conclusion that the trouble was due to the capstan motor. A month or two later, when the customer was getting really upset, a replacement motor arrived. A further soak test confirmed that our diagnosis was correct.

S.B.

JVC HR7200/Ferguson 3V29

I'm not sure whether this one has been covered before, but to avid VCR fault collectors, here's a beaut! This JVC HR7200 (Ferguson 3V29) machine had a replay colour fault: the colours were in horizontal bands, so they were obviously not phase locked. I did puzzle initially why the colour-killer didn't operate, then discovered that there isn't one fitted – pin 10 of IC403 is left open-circuit. The colour phase-locked loop is in IC403, which was soon eliminated. So was the 4·435571MHz crystal as it measured correctly in the record mode. With the scope connected to certain points the colours would lock, giving normal playback colour bars. This proved that the a.p.c. loop could be locked. The question remained as to why it wouldn't do so.

There are two phase detectors in IC403, the a.p.c. and ident detectors. Both are fed with gated burst, at pins 14

and 13 respectively. The only difference is that the input to pin 14 goes via a 90° phase shift network. A scope comparison showed that the phase shift was correct, and the only discrepancy we could detect was in certain voltage readings. Pin 1 was at 5.9V instead of 5.6V while pin 14 was at 6.04V instead of 6.4V. These could be put down to tolerances. We eventually found that C462 (15pF), part of the 90° phase shift network in the feed to pin 14, was resistive, though of the correct capacitance value – it measured a few hundred $k\Omega$ on the AVO.

Note that the circuitry around pins 13 and 14 of IC403 is high-impedance. Thus readings here will be valid only if $a \times 10$ scope probe or a high-impedance digital voltmeter is used.

JVC HR2650

The complaint was that when editing by either insert or audio dub the original sound was erased. Before starting on any repair work we had to make sure that the customer was doing the right thing. On this machine the camera records sound on ch. 1 or if stereo chs. 1 and 2. The tuner records on both channels. Now when audio dubbing or insert editing it's possible to select to over record both channels or ch. 2 only. The customer complained that with the switch in the ch. 2 dub only position and then insert editing a title on to his tape all the original sound was erased, whereas the original sound on ch. 1 should have been left alone. A cross check with a stock machine confirmed that this should be so, the ch. 1 sound remaining untouched. In the customer's machine it was erased.

A tuner recording was made and a further check carried out using the audio dub facility. Ch. 2 was over recorded and ch. 1 fully erased – but a small amount of the original sound could still be heard on ch. 2! The fault? Well, the ch. 1 and ch. 2 audio erase heads had been reverse wired in production! As a result, when an audio dub was performed ch. 2 erase went to the ch. 1 erase head, thus wiping ch. 1, and the ch. 2 record head erased and over recorded, thus explaining the residual sound that was left on ch. 2.

Defeat!

There are occasions when circumstances dictate a course other than investigative repair. Such an occasion arose just before Christmas. A local dealer sent around a Sony SLF1 portable which wouldn't thread up after inserting a cassette. Three microcomputer i.c.s control this function. One in particular scans the cassette detector switch and has an output for threading drive. Whilst it scanned the switch input, it didn't activate the threading output. Sony technical agreed that a replacement for this i.c. and/or one of the other two was in order, and after replacing two of them to no avail it became obvious that without any technical information on the starting routines a great deal of time would be required to sort the fault out. The dealer was not prepared to pay for this and I believe the machine went back to Sony. If any Sony engineer has sorted it out, I'd be glad to hear from him ... S.B.

Toshiba V8600 with a Hangover

Being Christmas, I suppose it had to happen. Andy did say the customer suspected that someone had spilt white wine into the machine. The whole area around IC604 and IC602 was badly corroded. Most components had to be removed for cleaning and the wire links had to be replaced. After a good clean up the machine was tried. The pinch solenoid didn't operate. This was traced to Q642 not providing IC602 with clock pulses (derived from the PG circuits). I wonder whether Andy reordered the foaming cleanser?

VCR Supply Lines

The fault with a Mitsubishi HS700 (the portable machine with the built-in tuner) was that it wouldn't record. A check showed that it was working correctly so far as the E-to-E mode was concerned, but attempting a recording produced no results – not even erasure of the previous sound or picture. A point here – when dealing with a no record fault, always use a tape with a previous recording on it in order to check whether the erase circuits are working or not. This can aid diagnosis.

The fact that so much was defective, i.e. no recording, no erasure and both the sound and vision affected, led me to suspect that a voltage rail was missing - in this case the REC 9V rail. A check showed that it started off at 9V but over a few seconds fell to 7.8V. Shorting across to the permanent 9V rail brought the voltage up to the correct level but didn't affect the problem in the slightest. The manual is not very well set out, as a result of which we had to spend some time trying to find the record voltage rail to the erase oscillator. Eventually a line labelled DREC 9V was found. This was at 0.2V instead of 9V. The problem was traced to IC2H1, which processes the sound, a replacement curing the fault. A DREC 9V line is not found in many machines – it stands for delayed record 9V, the purpose being to allow noise-free transitions between recordings. The sequence after record is selected is as follows:

- (1) The machine laces up and REC 9V appears.
- (2) The machine winds tape back for a short period.
- (3) The machine goes into the combined record/playback mode. During this time the E-to-E mode is maintained, i.e. the machine doesn't playback the tape, the idea being to use the previously recorded control pulses while synchronising the motor speed to the incoming sync signals.
- (4) The DREC 9V line appears and the machine goes into the full record mode. With the heads synchronised to the previous picture, a noise-free transition occurs.

This fault prompted me to make a list of the various voltages found in VCRs and their purposes to help with fault diagnosis. I've used 9V as the nominal voltage, but the rails may be at 12V – the principle remains the same.

The basic lines are usually 18V, 15V, 12V and 9V. These are present all the time once the machine has been plugged in and the operate switch is on. They power such things as the clock, timer, microcomputer (usually a 5V feed derived from one of the other rails), aerial amplifier and, in some models, the infra-red remote control receiver.

The not-PB 9V line is present all the time during operation except during playback. It powers the tuner and i.f. strip plus associated changes to provide the E-to-E mode.

The PB 9V line is present only during playback. It switches the signal processing circuits and the servos to the playback mode.

The REC 9V line is present only during record. In

addition to switching the signal processing and servo circuits to the record mode it switches on the bias oscillator/erase circuits.

The DREC 9V line is present on record only, after a few seconds delay. Used for noise-free transitions between recordings.

Thus failure of the not-PB 9V line would give normal playback but no sound or picture in the E-to-E mode, and record via the video and audio input sockets only. Failure of the PB 9V line would give normal operation except for no playback. This assumes that the relevant voltage disappears, but as regular readers will know this seldom happens. What usually occurs is that the voltage drops sufficiently to affect some parts of the circuit but not others, or enough to cause intermittent operation. Worst of all is a switching transistor that leaks, causing part of the voltage to be present all the time. This can give rise to some very obscure faults – as the machine tries to record and playback at the same time for example.

Grundig 2×4 Super

A Grundig 2×4 Super arrived with the complaint that it chewed tapes. The machine worked all right on rewind and fast forward, though it was a bit sluggish. On record and playback however the take-up reel failed to rotate. This created a loop of tape, as a result of which the machine entered the alarm mode. We investigated without a tape in and discovered that the reel motors were deprived of power – there was only about 4V at the emitters of the drive transistors instead of 12V. A check back to the power supply revealed that the 2V zener diode at the top centre was dry-jointed!

The power supply in this machine is liberally sprinkled with small safety resistors that tend to go open-circuit at the drop of a hat – R443, R453 and R485 are the favourites. With R443 (390 Ω) open-circuit the machine will not switch on – the clock displays 8s and the relay doesn't energise. This resistor is in the base circuit of transistor T443 that bypasses the relay contacts to power up the microcomputer i.c. so that the latter can give a "relay on" signal. R435 and R485 (both 100Ω) are in the 150V and -150V dynamic track following output stage supplies respectively – R435 will also remove the 33V tuning supply when open-circuit. Lack of dynamic track following shows up as noise bars in fast search (like a VHS machine). Also the voltage at the brushes above the head will be ± 60 -80V instead of approximately zero volts $\pm 15V$.

M.P

Akai VS2

Failure to load was the problem. The tape would half load then retract, with the "breakdown" signal showing. We found that the brakes were not being released from either the take-up or the supply reel. The brakes are operated by a pin which is engaged in a fork on the underside of the mechanism, but the pin had disappeared – when the bottom cover was removed it dropped out of the bottom PCB. We had no further trouble after glueing it back in place.

M.D.

Sony SLC6

A customer phoned to say that his new VCR had already chewed up three tapes. We called and found a tape jammed inside the machine. After removing this we

inserted our own tape and found that the machine laced up correctly. When play was selected however the tape went slack and the slack sensor operated. Also the machine wouldn't go into fast forward, and in rewind the tape became very taught.

This suggested a problem with the take-up spool brake, so the machine was taken to the workshop for further examination. With the machine on the bench we inserted our dummy cassette so that we could see what was happening to the take-up wheel. There was plenty of take-up torque in play, and the brake was released correctly in rewind. Removing the cassette carriage enabled us to see what the problem was. There's a "cassette in" microswitch at the base of the cassette tray, and the wiring to this should be routed via plastic clips around the edge of the metalwork. This wire was not properly in place, and was getting trapped between the take-up wheel and the reel inside the cassette when the latter was in position. The problem didn't show with our dummy cassette because this doesn't contain tape reels.

M.D.

Ferguson 3V23

The problem was intermittent failure to eject the cassette. When the button was pressed you could hear the motor running, but there was no movement. We found that the middle cog wheel on the side of the cassette housing was quite sloppy. On removing the cassette housing we noticed that the screw which holds the spindle on which this cog wheel is mounted had worked loose: tightening the screw removed the cog wheel play and cured the eject problem.

M.D

Sharp VC7300

The complaint was that the machine was stuck in play. Removal of the top cover revealed that the tape was loaded. When the machine was powered the tape unloaded. Play was selected, then stop: the machine remained loaded and the loading motor made a complaining noise – it was turning the wrong way, i.e. to load. I next noticed that the main solenoid did not release when the stop button was pressed. Pulling out the plunger enabled the machine to unload.

A switch which is activated by the main solenoid via a lever changes the polarity of the supply across the loading motor. Because the solenoid plunger had stuck, the switch was applying the wrong polarity supply to the loading motor. Lubricating the plunger solved the problem. This also solves the mystery about the VC8300H (VCR Clinic, November) with its thermal fuse open-circuit. Because the solenoid wouldn't pull in, the loading switch would be in the wrong position with the loading motor running in reverse.

Bulbs

When checking ex-rental Ferguson 3V29/30 series machines in the workshop we've noticed that the cassette lamp seems to fail rather a lot. We eventually realised that it seems to happen if the machine is switched on at the mains with the operate switch in the on position. With the operate switch kept in the off position, the bulb failure rate was cut dramatically. A similar thing happens with the clock bulbs in the Toshiba V5470B. If the machine is unplugged for the first time in a couple of years to go into the workshop, the clock bulbs almost always fail: unfortunately there's no way to prevent this.

Letters

THORN TX9 CHASSIS

In the January issue TV Fault Finding feature there was mention (page 145) of chopper transistor (TR62) failure in the latest version of the Thorn TX9 chassis. My experience has been that when TR62 goes short-circuit the reason is that R165 (300k Ω) has gone high in value. This resistor forms part of a sawtooth generating network connected to pin 4 of the TDA4600 chopper control i.c., the sawtooth in turn affecting the drive to the chopper transistor. The result of R165 going high in value can also be intermittent blowing of TR62.

Brian Francis, Tech. (C.E.I.), Plympton, Plymouth.

POOR AERIAL DESIGN

It's a sad fact that the majority of u.h.f. TV aerials installed are of the cheap (some would say cheap and nasty) variety. The average customer does not seem to be prepared to pay for the good quality aerials produced by the better known manufacturers, and I doubt whether this situation will change in the foreseeable future. There's one little thing that could be changed however, at very little cost to anyone. It would enormously improve the performance of many of these cheap aerials.

For some reason the smaller aerial manufacturers tend to make their group A arrays with a reflector that's too short and too close to the dipole. The length tends to be 260-270mm when it should be 345mm: the reflector-dipole spacing is usually 70-80mm when it should be 100mm. A reflector of this sort is literally worse than useless, as it acts as a director on the lower channels.

The performance of some of these aerials at the bottom end of the channel group is disastrous. On channel 21 the polar diagram looks like a starfish: the gain drops to about 4dB and the front-to-back ratio is 1:1! For vertical polarisation some aerial riggers throw the reflector away and mount the array about 200mm from the top of the mast, thus using the mast itself as a reflector.

This situation is becoming acute as so many Channel Four transmitters use channel 21. Surely the offending manufacturers would find it in their own interests to make a small and cheap modification that would greatly diminish the quality gap between themselves and the "big boys"?

W. Wright, Wright's Aerials, Micklebring, Nr. Rotherham.

TV FAULT REPORT

The following recent fault experiences may help some other readers. The first concerns an Hitachi P27FM 12in. monochrome portable – the one with the f.m. radio – the complaint being field roll when the set was first switched on. This could be corrected by adjusting the rear mounted hold control, but further drift would occur some minutes later. Eventually the end of the control's range would be reached. Well, field oscillator circuits are usually simple and easy to repair, so I gave the owner a ridiculously reasonable quote. On removing the set's case however I discovered that the entire field timebase is contained within a KC531C i.c. A spray with the freezer confirmed

that it was at fault, replacement curing the trouble. Unfortunately the repair was more expensive than originally envisaged. Ouch!

The Philips G8 chassis has been around for many years and rarely do I find anything that surprises me. This particular one came in for tube replacement plus a general service and set up. After carrying out the work, the h.t. control was set to minimum and the set was switched on. To my surprise the h.t. voltage at the two fuses on the power supply panel was 210V. Increasing the control's setting increased the voltage, its stability indicating that the circuit was regulating – but at the wrong point. This sort of thing is usually caused by R1368 (470k Ω), which is in series with the h.t. preset, or the feedback resistor R1372 (390k Ω), but both were perfect.

The panel was removed and appeared to be an early version (the set itself was the later 550 series/BEAB/VCR compatible version), but not quite. The panel contained aspects of both versions - the panel went through several modifications. I decided to bring it up to the later standard. The h.t. preset was changed to $22k\Omega$, with $5.6k\Omega$ in parallel, and the chassis return resistor was changed to $10k\Omega$. R1384 was changed to $4.7k\Omega$ and a diode was added in parallel with the charging capacitor C1376 - I used a BY207, with the anode to chassis. Some components were of the later values while others had the original values, and it seemed that the combination wouldn't do the job. Switching on with the later values fitted and the preset at minimum produced a regulated 150V supply, with the correct 205V when the control had been advanced to approximately mid-way.

Intermittently changing colours was the fault reported on an old GEC hybrid colour set. These receivers are now nearing the end of their useful life, but I occasionally still come across a good example. This was one such, in excellent condition throughout, with a crisp tube and polished, unmarked cabinet. The purity was appalling, but resetting this along with the convergence and grey-scale tracking produced a good picture. I switched off and on to check the operation of the degaussing circuit, and as everything appeared to be all right I left it at that. The owner had moved before the fault appeared, so I put the fault down to this.

A week later I was back. This time I switched off the blue and green guns and watched in red. This showed that the purity was continuously varying, drifting out and then back in. I've never seen a set do this before, but the circuit is simple enough, with a couple of thermistors – the usual VA8650 and a strange three-legged one with two sections. The VA8650 fell to pieces when I touched it, so I replaced it with confidence that the fault was now cured. All connections were checked, and the double thermistor had been replaced recently. Purity and convergence adjustment produced a good picture, and the red raster no longer varied.

After another week I was back again and, on removing the rear cover, saw it immediately. The double thermistor had a tiny hairline crack through the small end section. Replacing it put an end to my visits. Apparently the crack had been too small to see on previous visits, repeated thermal cycling eventually widening it.

A Philips TX 12in. monochrome portable (Model 12B711) gave croaky sound, reminiscent of crossover distortion, at low levels. At normal listening and high volume levels the output was normal and undistorted. Speaker replacement made no difference, and no transistor leakage could be measured. The TBA120AS was replaced

to make sure, but this didn't seem to have much effect. There's a modification to cure the condition, which is present with some of these portables. Change R300 from $27k\Omega$ to $18k\Omega$, R311 from 33Ω to 56Ω , R312 from $2.7k\Omega$ to $3.3k\Omega$ and R315 from $180k\Omega$ to $120k\Omega$. The modification increases the output stage quiescent current and provided a complete cure. My thanks to Philips Service for their advice.

Another common trouble with these sets is cracks in the print around the brightness/volume/contrast control potentiometers. They are usually very hard to see, but are easily found with an ohmmeter.

Stephen Leatherbarrow, Middleton, Manchester.

KEEP AN EYE ON THE ROOF

Some four years ago I reported in these columns on some of the unexpected things that can happen during the course of servicing. One case I mentioned concerned a customer who'd installed his own u.h.f./v.h.f. aerial on the roof of the block of flats in which he lived. His reception gradually deteriorated over a period of time, and when he eventually went up on to the roof to try to discover why he found that no less than six other aerials had been fitted to his mast, all in extremely close proximity. They'd all been installed by bona fide aerial companies, but not one of them had asked for permission to install an aerial on his property. He had them all removed a bit sharpish!

The saga of this gentleman and his aerials is by no means over however. Some three months ago he decided that some streamlining of his array was due. Since the old v.h.f. aerials were no longer in use they were to be scrapped and, at the same time, it was decided to replace the existing mast with a sturdier one (a scaffold pole to be exact). Suitable reinforcement was carried out and the single u.h.f. array was mounted at the top of the pole, the space below being left clear for the future installation of a CB aerial and a v.h.f. stereo radio aerial. He then painted the complete pole with red and white stripes (barber shop style) to deter (he said) anyone from fitting anything to it in the interim period.

Eventually he gets his other aerials and up he goes to fit them. What does he see? Two lovely u.h.f. arrays smack in the middle of his mast! He traced one to a particular flat and, after speaking to the tenants, got the name of the firm who'd installed it. A fitter from the firm came round and said he'd resite it. That was on a Friday. On the following Monday our customer went up to trace the owner of the remaining aerial. He managed this and found it had been installed by the same firm. He also found that the first aerial had been resited on a lightning conductor, complete with a large lump of baton in the U of the clamp bolt to act as a spacer!

Now I'd expect this sort of thing from a cowboy outfit, but the firm concerned is a prominent member of the National Federation of Aerial Contractors... If a customer is given a quote for an aerial installation this will include all the fittings. If the aerial is then attached to someone else's mast this means that the bracket, pole, lashing wire etc. which have been paid for have not been used. In my previous communication I suggested that managers should take a greater interest in the way their firm's work is carried out. It seems that this suggestion has not been heeded.

Steve Knowles, London N4.

next month in

TELEVISION

• ALL ABOUT FIELD STRENGTH

A set's performance depends on the strength of the signal it receives, but how do you go about measuring this and assessing the results? There's much cause for confusion in this subject, with field strength being quoted in various ways and meters calibrated quite differently. Harold Peters explains what it's all about and how to relate and interpret the various figures — including satellite TV field strengths.

• THE RIGONDA VL100

Large numbers of these 6in. monochrome portables were sold in the UK. Many repairers are reluctant to handle them because of the Russian markings and lack of information. Malcolm Burrell took a detailed look at the innards and tried out various transistor substitutions: notes to help others deal with these interesting sets.

• WIDEBAND UHF PREAMPLIFIER

At many sites a lift in the signal fed to the set will help – the problem has become more widespread with Ch. 4 now being generally available. The important thing in most cases is low noise rather than high gain. This preamplifier, presented by Roger Bunney, uses a BFR91 transistor which is intended as a low-noise wideband device.

• MORE THAN MEETS THE EYE

Full use of the senses rather than the meter can be a great help in speedy fault diagnosis. Robert Thompson tells you how to read the signs.

• TEST REPORT

In reviewing the B and K 467 c.r.t. tester/ reactivator Eugene Trundle takes a look at c.r.t. failure mechanisms and the effects on these of c.r.t. design changes in recent years.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO(Name of Newsagent)
Please reserve/deliver the April issue of TELEVISION (£1), on sale March 21st, and continue every month until further notice.
NAME
ADDRESS

Servicing the Sony Model KV1400UB

David Botto

We've handled quite a few of these receivers, which are reliable, well designed and give excellent picture and sound. Just the same, you can get puzzling faults.

As with many modern sets, failure in either the power supply or the line timebase results in the dead set symptom. As the first logical step in this event is to determine in which section of the receiver the fault lies, we'll start by considering the operation of the power supply. We'll use the Sony board lettering identification system to identify sections of the chassis.

The Power Supply

The switch-mode power supply consists of a series chopper arrangement – though Sony choose to call it a choke-coupled flyback converter. The circuit is shown in Fig. 1. It's on board D, along with the line and field timebases.

The a.c. mains input is fed via the on/off switch S901, fuse F601 (3.15AT), choke T601 and the surge limiting resistor R601 (3.9Ω , 10W) to a bridge rectifier consisting of two ERC04-06SU2 double diodes. The fuse sometimes goes open-circuit for no apparent reason, a new one restoring picture and sound. Before fitting a replacement, check whether the old one is blackened. If so, then the bridge rectifier is suspect. Note that D602's two anodes are returned to the h.t. line rather than chassis:

Q605 (2SC1942) is the chopper transistor and Q604 (2SC2230A) the driver. Q602/3 (both 2SC633A) form an astable multivibrator circuit which if left to run on its own operates at about 10kHz. When the set is running normally, the multivibrator is triggered by pulses from the line output transformer. The frequency is thus 15·625kHz. L603 is the reservoir inductor and C621 the h.t. filter capacitor. When Q605 switches off, the efficiency diode D606 (ERC25-06) conducts to maintain the current flow.

The control action is provided by transistor Q601 (2SA733) which senses the h.t. voltage at its base – D603 provides a stable reference at its emitter. If the h.t. voltage rises, Q601's base voltage will rise and its collector current will fall. Since the collector of Q601 is connected to the junction of R611/2 in the multivibrator circuit, the effect is to shorten the on period of Q602 and thus the on time of Q605 to compensate. The reverse occurs when the h.t. voltage falls.

Excess current protection is provided by transistors Q651/2 (2SA733 and 2SC633A respectively) which are connected together to act as a thyristor. The emitter of Q652 senses the voltage developed across R651. Excessive h.t. current will increase the negative voltage developed at this point with the result that Q651/2 will switch on, removing the drive to Q604. The circuit also provides over-voltage protection. In this event the output from D652, developed across C653, will be sufficient for D653 to conduct. Q651/2 will then switch on as before.

Dealing with a Dead Set

So there's a dead set sitting on your bench. Is the fault due to the power supply or an overload elsewhere? To

find out you'll need an 18V d.c. supply – we always use two PP9 batteries in series, guaranteed absolutely ripple free! It's also vital – as with all Sony sets – to have a means of controlling the mains input voltage, i.e. a variac or tapped mains transformer. In addition, a 100W, 240V bulb is required.

Removing the link (see Fig. 2) right next to Q605's heatsink isolates the power supply. Connect the negative end of your 18V supply to chassis and the positive end to the positive side of C609. Don't connect the mains supply at this stage. Connect a meter in series with the 18V supply to measure the current drain – start on a high current range. The reading should be around 25mA. A digital multimeter is best for all tests on the power supply.

With an oscilloscope connected via a 10:1 probe to the collector of Q602, a waveform similar to that shown in Fig. 3(a) should be seen – of about 12V peak-to-peak. This tells you that the multivibrator is working. If the waveform is missing, disconnect the collector of Q651. If the waveform now appears, the fault is in the overload protection circuit. Check Q651/2 and capacitor C654 – examine it for corrosion. Diode D651 (1S1555) can also fail.

If there's still no waveform with the collector of Q651 disconnected, it's possible that there's a fault in the error detector circuit. Check Q601, the zener diodes D607 (RD3·9E) and D603 (RD12E-B2) and capacitors C608 and C622 (also make sure they're not corroded). This leaves only the multivibrator circuit itself. We've found this to be reliable, but if necessary check Q602/3 and diode D604 (1S1555).

If the waveform at the collector of Q651 is correct, connect the scope – still via the 10:1 probe – to the collector of Q604 and the emitter of Q605. The waveforms shown in Fig. 3 (b) and (c) should be seen.

To avoid damage, two quick checks should be made before connecting the mains a.c. supply. First check the waveform at the collector of Q602 again, then momentarily short the anode of D653 to chassis. The waveform should disappear and won't come back until the 18V supply has been disconnected for a minute or so. The second check is to connect the junction of R605/6 to the 18V d.c. supply. As RV601 is adjusted the waveform will vary – in fact at one end of the control the multivibrator will stop. These checks confirm that the overload protection circuit is working and that the error detector circuit is in order.

Note that if Q605 fails, D606, Q651 and Q652 are likely to be faulty. Knowing how this power supply works is useful since similar circuits are used in other Sony sets.

Disconnect the batteries and remove the link from resistors R605/6, then connect the mains supply via the variac or tapped transformer. Monitor the waveform at the emitter of Q605 with the scope, via the 10:1 probe. Increase the a.c. input slowly, watching for smoke or signs of overheating. At about 40V a.c. the scope should show a waveform of some 170-180V peak to peak and the h.t. across C621 should be about 100V. If all is well, switch off the mains input – without altering the a.c. voltage setting – and connect the 100W bulb between the h.t. line and

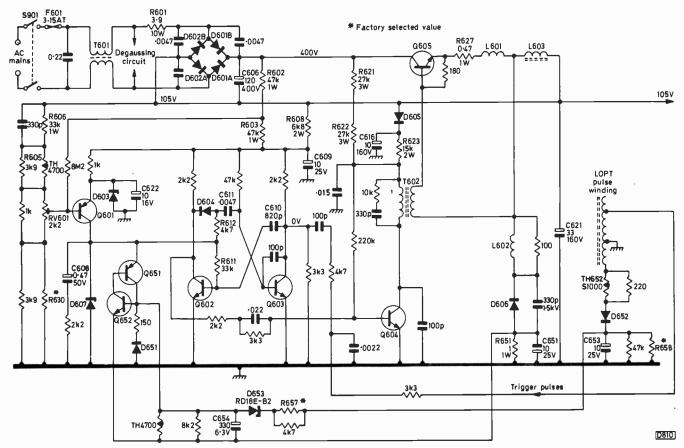


Fig. 1: Circuit diagram of the switch-mode power supply. The multivibrator's main time-constant network comprises R611/C610, the control transistor Q601 adjusting C610's charging time.

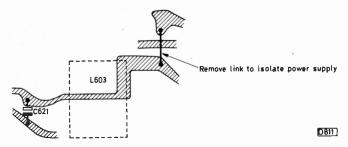


Fig. 2: Location of the power supply isolating link.

chassis.

Restore the a.c. input and check the waveform at the emitter of Q605 – see Fig. 3(d). As the a.c. input is increased to 150V the h.t. line should reach 95-110V depending on the setting of RV601. Slowly increase the input to the full 240V. The h.t. voltage should remain at 105V. If during these tests any of the waveforms don't seem to be clean, having a lot of "fuzz", replace C609 and check C606. On rare occasions C616 dries out and causes problems.

Switch off, remove the 100W bulb and reconnect the link (Fig. 2). Switch on with the a.c. input at a low setting and gradually increase the input. At 40V a.c. there should be a squarewave at the emitter of Q605 and at 60V a.c. the frequency of this squarewave should increase because pulses should arrive from the line output transformer to trigger the multivibrator. If there's no change in the frequency of the waveform, find out why before increasing the a.c. input further.

Picture and sound should begin to appear when the a.c. input is about 80-90V. With the full 240V a.c. mains input, an 18V peak-to-peak line-frequency waveform

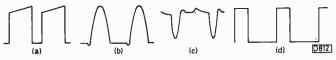


Fig. 3: Power supply check waveforms.

should be present at thermistor TH652 and at the anode of D652.

Timebase Troubles

If the line timebase is dead, check the output transistor Q503 (2SC1875) and the efficiency diode D503 (GH1F). If necessary, check the 12V regulator transistor Q811 (2SD471) and the three rectifier diodes fed by the line output transformer T801. These are D811 (V09C), D802 (GH1F) and D801 (HF1), for the 12V, first anode and 170V supplies respectively. If all is well, apply a very low a.c. mains input and monitor the waveform at the collector of the line driver transistor Q502 (2SC2230A) to see whether line drive is present. Check that it's reaching the base of Q503. Switch off as soon as line drive waveforms are seen.

Lack of line drive can be caused by failure of the line oscillator transistor Q501 (2SA677) or Q502, also the feed resistors R514 ($4.7k\Omega$, 2W) and R513 ($47k\Omega$, 1W).

In earlier Sony receivers it was almost unknown for the line output transformer to fail. T801 in the KV1400UB does sometimes fail however. The only reliable test is by substitution. Note that the e.h.t. rectifier is encapsulated within the transformer. First make sure that R811 (1.2Ω , 4W flammable) and the two diodes (D504/5, type SIB01-02) in the centring circuit are o.k. Also examine all the small electrolytics in the line timebase for excessive leak-

age or signs of corrosion.

We've not had many problems with the field timebase. If diode D511 (1S1555) fails, field sync is lost. The output transistors are Q553 (2SD669A) and Q554 (2SB649A). They rarely fail. If the sides of the picture are bowed, suspect leakage or failure of the pincushion correction transistor Q581 (2SD571) and/or its emitter resistor R584 (82 Ω).

The Signals Side

The audio circuit (board A) also rarely needs attention. If the sound does fail, the first thing to do is to measure the voltage at pin 6 of the intercarrier sound i.c. (IC251, type CX095C). It should be 5.4V. If way off, check the sound mute stages on board M2 – test transistors Q182 (2SC634A) and Q181 (2SC733) for leakage, also diode D181 (1S1555). If the 5.4V reading is correct, check the audio circuit. The output transistors Q252 (2SD669A) and Q253 (2SB649A) can fail. In this event check the emitter resistors R260/1 (both 33Ω , $\frac{1}{2}$ W) and the driver transistor Q251 (2SC926A).

There are five i.c.s on the signals panel (board A). In addition to IC251 these are IC281 (M5135P) for a.f.c., the i.f. chip IC201 (CX177B) and the two decoder chips IC301 (CX108) and IC302 (CX109). IC301 contains the luminance amplifier, chrominance processing and reference oscillator stages (there's also an external transistor, Q305, in the oscillator circuit) while IC302 is mainly concerned with colour demodulation and matrixing. IC201 also feeds the intercarrier sound chip of course. These i.c.s are all very reliable.

A difficult fault to trace is intermittent loss of sound and picture with a peak white raster. A number of $0.0047\mu F$

capacitors will be seen in the vicinity of IC201-C207, C208, C211, C213 and C216. Replace the lot!

In the event of colour problems, start by connecting the 10:1 scope probe to the junction of C310 (100pF) and R313 (1k Ω). With a colour bar input, chroma bars should be seen. It's handy to know how to disable the colour killer: this is done by applying 4V (use one of your PP9 batteries and a $5k\Omega$ preset) to pin 24 of IC302. If there is still no colour, go straight to the oscillator transistor Q305 (2SC403C) – there should be a 4.43MHz sinewave at its collector. If there isn't, check the transistor and the components in this area.

The colour-difference and luminance outputs from board A can be easily checked with the scope at plug A5. The luminance signal should be present at pin 1, with R - Y, G - Y and B - Y at pins 3, 4 and 5 respectively.

The RGB output transistors Q701-3 (2SC2278) are on c.r.t. base panel C. Predominance or absence of one colour can be caused by leakage or failure of one of these transistors.

If the set is stuck on one channel, first clean the touch contacts then suspect the two i.c.s (IC151/2, both type M51231P) on touch sensor panel M1. This doesn't happen often.

We've not had problems with panel S (18V regulator, a.g.c. amplifier plus i.f. preamplifiers). If the tuner should fail it's best to obtain a new one from Sony rather than trying to repair the old one. If the tuning drifts off after the set has been on for some time, change D172 (μ PC574J), the 33V regulator on panel M2.

It's best to obtain all replacement parts from Sony. After carrying out any soldering on the printed boards, spray on a very thin coat of circuit varnish in order to prevent future corrosion.

TV Fault Finding

Grundig 3402

The customer complained that the set would sometimes not switch on from cold. He mentioned that a faint hum could be heard from the back. This model is fitted with the CUC220 chassis, with full remote control. We made the set go into the fault condition by turning it on and off over a period of hours. The customer was correct in saying that a humming noise could be heard from the back - it was coming from the chopper transformer TR651. Voltage measurements showed that all the outputs derived from this transformer were present and correct, but we noticed that the standby relay hadn't operated. Pin 13 on the tuning panel was shorted to chassis to prove that the fault was not in the remote control circuitry. This still produced no results, so we removed the relay's cover. The problem was now clear - the relay contacts were jammed open. Careful cleaning provided a cure, but to be on the safe side we decided to fit a new relay.

Thorn TX9 Chassis

The problem was that the picture would intermittently flicker. This seemed to be due to a fault in the tuner unit, but was difficult to prove since it was so intermittent. A new tuner unit was fitted and the set given a long soak test. After several days the fault reappeared, but once again it was hard to decide upon a specific cause. Luckily

Reports from Mick Dutton, P. Hardy, M.S. Barakat and John Coombes

we had another set with the same chassis in the workshop, so we tried swapping over the i.f. modules. This cured the fault on the first set, and after a time it put in an appearance on the second set. Careful examination revealed that one leg of the a.g.c. reservoir capacitor C35 $(1\mu F)$ was loose. A replacement cleared the fault. M.D.

Philips K30 Chassis

The complaint with this K30 series set was that the background colour would change intermittently. On soak test we found that the red level was varying: with the blue and green guns switched off, it was possible to watch the red level gradually drifting up and down. With the use of freezer and a hairdryer the problem was traced to D4255 (BAV21) on the RGB output panel. The diode was going leaky when warm – it's in the red channel d.c. stabilising circuit.

Grundig CUC720 Chassis

Picture jitter was the complaint with this set: a few minutes after switching on, the picture would become very unstable both vertically and horizontally. We suspected the switch-mode power supply, but the output voltages remained stable during the fault condition. We nevertheless tried reducing the output voltage (R647), which made

the jitter less prominent. We also noted that the control didn't seem to have much range. When we removed the plastic cover from the print side of the power supply the reason for the fault was obvious. The BU208A chopper transistor's base connection had a white deposit around it, causing a dry-joint. Someone had been very generous with the heatsink compound during manufacture, and this had pushed right through the base pin connection. We had to remove the transistor and file its pins clean before a satisfactory connection could be made.

M.D.

Rank T22 Chassis

The initial problem with this set was no results. This was soon traced to the 1Ω feed resistor in the BU208 line output transistor's base circuit being open-circuit. A few days later the customer complained that the set had once again gone dead. This time the $1.8k\Omega$ feed resistor 5R3 in the line driver transistor's collector circuit had sprung open. We thought we might have disturbed the soldering on this resistor during the previous repair, and after resoldering it the set seemed to work all right. A few days passed, then the same thing happened again.

This time we resoldered the resistor and left the set running. After several hours the picture went unstable horizontally, giving an effect similar to that produced by tripler breakdown. The problem was traced to pin two of plug 4Z2 having a bad connection. This pin makes the chassis connection between the line output and the scan drive panels.

M.D.

ITT 1611

This set, fitted with the ITT80 (90°) chassis, would intermittently go dead or fail to switch on from cold. We found that in the fault condition the mains supply was not present at the mains panel. After removing the remote control receiver assembly we found that the mains input was present at the relay-operated on/off switch but one side of this was open-circuit. Stripping the unit down and cleaning the contacts provided a complete cure. M.D.

Tatung 120 Series Chassis

Loss of one colour is quite a common fault on these sets. Swapping over the RGB leads at the tube base will eliminate the decoder of suspicion. The RGB output stage transistors on the tube base panel may then need to be checked as appropriate, but the cause of the trouble is more often the feedback resistors R226 (red channel), R244 (green) and R251 (blue). They are $100 k\Omega$ metal film resistors with a 2% tolerance rating, but tend to increase in value to something like $2M\Omega$.

In the event of field collapse, check the supply to the TDA1170 field timebase chip – there should be 23V at pin 2. If this is missing, check rectifier diode D404 (BA159) and the surge limiting resistor R434 (10Ω) in the line output stage. One or other is likely to be open-circuit. If there's a short-circuit in the i.c., R434 will burn and go open-circuit. This resistor is a metal film safety component (fusible) and must be replaced with the same type. J.C.

Thorn 1690 Chassis

The complaint with this set was a common enough one – a severe hum bar which also upset the field sync. The l.t. rail

was slightly low at 10.5V, and adjustment to 11.3V only made matters worse. The mains rectifier diodes W8/9 were changed, then the reservoir capacitor C70 and the series regulator transistor VT10, but the fault persisted. The error amplifier transistor VT13 appeared to be sensitive to freezer spray so a replacement was fitted. Still no difference. The zener diode W5 was then changed, apparently clearing the fault. The l.t. rail was low at 10V however, and when reset to 11V the hum bar reappeared.

A scope was then used to check the ripple at the emitter of the series regulator transistor. It was higher than expected at about 4V peak-to-peak, and of 20msec duration instead of 10msec. This revealed that the rectifier circuit was operating in the half-wave mode, and a quick check at the anodes of the two rectifier diodes confirmed that one of them was receiving no current from the transformer. A meter then showed that one half of the secondary winding was open-circuit – it had been poorly soldered at a tag. A clean up and some fresh solder restored normal operation.

Bush TV350

This set came in with a faulty picture – going negative. On checking we found that the fault was in the a.g.c. circuit. The set worked o.k. with a weak signal, but with a strong signal overloading was seen. Checks on the transistors, diodes and capacitors in the a.g.c. circuit showed that they were all in order, but there was no gating pulse from the line output transformer. A resistance check showed that the pulse winding was open-circuit. Apparently the transformer is no longer available - from Mastercare anyway - so we decided to add a few turns to the existing transformer. About seven-eight turns of "3000" line oscillator coil wire were used, connected to terminals 2 and 3 of the transformer. As a safety measure, insulating tape was used before and after the winding. When the set was switched on it was found to be working normally. Note that if the winding is in antiphase the field locking is difficult - in this case reverse the connections of the new winding to pins 2 and 3. M.S.B.

ITT CVC20 Chassis

In the event of excessive width, check whether C72 $(4.7\mu\text{F})$ is short-circuit then if necessary check the EW modulator diodes D23 (MR854) and D24 (BYX71-350) by substitution. J.C.

Amstrad CTV2000

This set uses a chopper power supply with the control circuit and the chopper transistor in a single chip, IC502 (type STR451). In the event of no sound or picture, check for 103V output at pin 2. If this voltage is present, check the voltage at the collector of the line output transistor Q705 (2SD904). If correct at 102V, check back to the collector of the driver transistor Q704 (2SC1756) where a reading of about 75V should be obtained. If this voltage is absent the feed resistor R726 (1k Ω , 1W) is probably opencircuit.

Thorn 9000 Chassis

In the event of tripping with a loud hum, check for dryjoints or open-circuit print at the mains rectifier's reservoir capacitor C702 (400μ F). J.C.

VCR Servicing

Part 26

Mike Phelan

The 3V24 uses dual-loop servos, like the 3V23, but in this case the phase control loops are both contained in an HA11711 i.c., as in the 3V16 mechanically controlled machine which we discussed earlier in this series. The drum motor is a direct drive, Hall effect type, also as in the 3V23.

Servo System on Record

Fig. 117 shows the basic drum and capstan servo arrangements in the record mode. Briefly, the drum servo is locked to the off-air field sync pulses after division by two. This is done by comparing the phase of the 25Hz pulses with that of a trapezium waveform derived from pulses obtained from a pick-up head associated with the drum motor. The divided-by-two field sync output also provides the feed to the control head. The 1,500Hz FG (frequency gear) signal produced by the drum motor assembly is converted to a control voltage for the speed control loop. The capstan servo is controlled by a 32.768kHz crystal oscillator whose output is divided down to 21Hz and then converted to a trapezium. This is compared to the 126Hz FG signal after division by six. The FG signal also operates the capstan speed control loop.

Servo System on Playback

On playback (see Fig. 118) the crystal oscillator provides a reference signal for the phase-control loops in both servos. It's divided down to 25Hz (not 21Hz this time). In the drum servo it's used to gate the sample trapezoid obtained from the feedback pulses provided by the pick-up head. In the capstan servo the divided-down output from the oscillator is converted to a trapezoid which is gated by the pulse output from the control head. There are also shuttle search, still frame and (by remote control only) slow-motion facilities. The speed control loops operate in the same way in both the playback and the record modes.

The Drum Servo

Fig. 119 shows the drum servo in greater detail. We'll look at the drum motor drive amplifier later. Suffice it to say for now that it has a forward and a reverse input (the latter is used for braking – the head never goes backwards!), also a control input, switched by transistor X6, so that the motor is stopped in fast forward/rewind/stop. As in the 3V23, the forward and reverse inputs are driven by two operational amplifiers so that the phase and speed control voltages can be added. When X6 is on, the two control lines are grounded via the isolating diodes D8 and D9 and the motor stops. Transistor X5 is included to ensure that only one control line goes high at one time – otherwise the motor drive amplifier would be damaged. A similar arrangement was used in the 3V23.

The speed control loop is mostly contained in IC3 (type VC1029). The 1,500Hz FG input is amplified to approximately 1V peak-to-peak. It emerges at pin 3 and is fed

back in at pin 4. It's then squared and converted to a sawtooth whose slope is constant, determined by the setting of the drum free-running speed control R13. If the drum speed decreases, the average ramp voltage falls. This is integrated within the i.c. to provide a d.c. voltage, and is also inverted to produce a rising output to speed up the motor. Note that with this type of system if a decrease in speed is called for the forward output to the motor drive amplifier goes low and the reverse output goes high, braking the motor until the correct speed is reached.

The phase control loop is the same as that in the 3V16, so we'll not go into detail. The network connected to pin 10 of IC1 should by now be familiar. R1 is the customer's tracking control which gives ±10msec phase shift (equivalent to a quarter revolution of the head drum) each side of the mean point set by R2 and the linear position of the control head. The latter is adjusted with an alignment tape while R2 is adjusted on the machine's own recording. D1 conducts on record, shorting out R1 and R2. This reduces the monostable multivibrator's time-constant, which is still adjustable by R4 to set the record head switching point. IC1 also contains the capstan servo, which is why the oscillator's output is divided down to 21Hz on record.

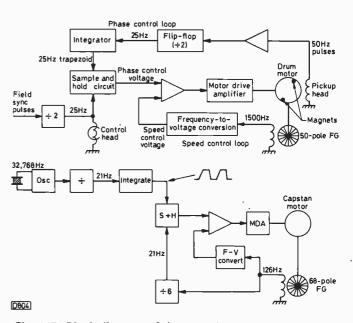


Fig. 117: Block diagram of the record servo system.

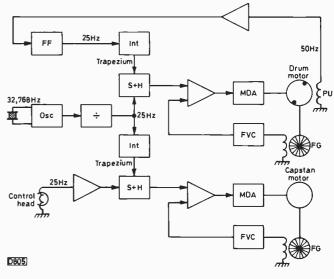


Fig. 118: Block diagram of the playback servo system.

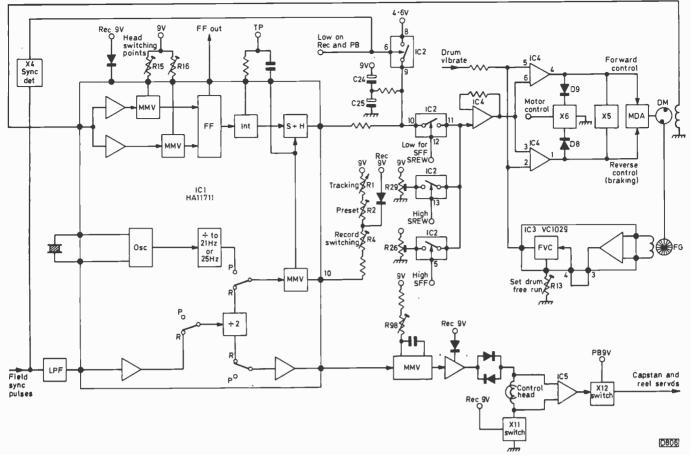



Fig. 119: Main features of the drum servo.

Pin 8 of IC2 is fed with a 4.6V reference voltage, this being approximately the correct value for the drum to free run at the correct speed. C24 and C25 form a timeconstant to maintain this voltage against short-term variations. Pin 6 of IC2 is low in record and playback (switch open) while pin 12 is high (switch closed), thus enabling the phase control loop. If the sync pulses are lost during record, sync detector X4 drives pin 6 high to maintain the drum speed and prevent hunting. Pin 12 goes low in shuttle search (search fast forward and search rewind), opening the phase control loop: either pin 5 or pin 13 goes high, connecting the appropriate presets R26/R29. These are set to give the correct drum speeds (1,560 or 1,425 r.p.m.) to maintain the correct number of lines per field in the shuttle search modes. In stop, fast forward and rewind pin 6 goes high so that C24/5 are charged to the reference voltage to give the minimum lock-up time when record or playback is selected.

As in the 3V23, a "drum vibration" signal is fed to pin 5 of IC4 in slow motion to correct the sideways motion of the picture. This is necessary because the different writing speeds when the tape is alternately moving and still would cause a variation which has to be corrected. For this purpose a waveform obtained from the flip-flop in the slow-still i.c. is added to the loop error voltage.

Drum Motor Drive

Fig. 120 shows the drum motor drive amplifier circuit. As mentioned in Part 24, the resistors on this panel are of the chip type to conserve space. The motor has two sets of stator coils and a permanently magnetized rotor. Each coil is driven by a six-transistor bridge circuit. There are two Hall effect sensors (HG1 and HG2) which are switched on

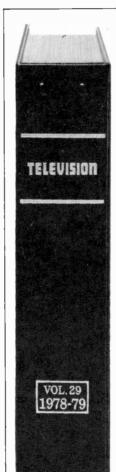

Bind it

It's so easy and tidy to file your copies away using the Easibind binder. Each binder is designed to hold twelve issues and is attractively bound and blocked with the TELEVISION logo.

UK price £4-50 including postage, packing and VAT. For overseas orders add 60p. Please allow three-four weeks for delivery. Why not place your order now? Send the completed form below with the remittance payable to: IPC Magazines Ltd., Post Sales Dept., Lavington House, 25 Lavington Street, London SE1 0PF.

it's easy

Order Form
l enclose p.o./cheque value
forbinders
Years required(BLOCK LETTERS PLEASE)
Name Address
Address
Date

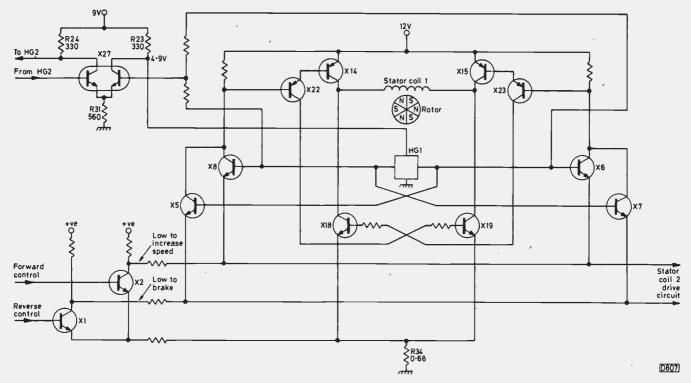


Fig. 120: The drum motor drive amplifier circuit.

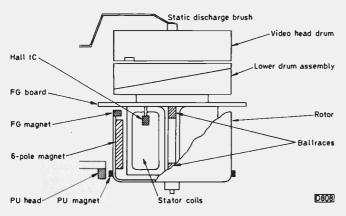


Fig. 121: Basic construction of the drum motor.

by the rotor magnets, also two control amplifiers (X1 and X2) and a balance circuit (X27). Only one bridge circuit is shown in Fig. 120 – the bridge circuit for stator coil 2 is identical.

As the motor rotates, HG1 produces two antiphase sinewave outputs that switch X6 and X8 on alternately. When X8 is on, X14, X19 and X22 are on: when X6 is on X15, X18 and X23 are on. Thus the current through stator coil 1 is reversed smoothly as the motor rotates.

To increase the motor speed, X2's base current is increased. Its collector voltage falls, thus increasing the conduction of X6 and X8 (and the corresponding transistors in the stator coil 2 circuit). The output transistors X14/15/18/19 in turn conduct more heavily and the motor speeds up. To provide braking, X1 turns on and X2 off. X5 and X7 then turn on. These are connected in the same way as X6 and X8 but with reversed base connections to the Hall effect i.c. As a result, the rotating stator field reverses, and so would the motor if the process continued, but the servo action prevents this – "reverse" is just used to slow the motor.

The 0.68Ω resistor R34 provides a convenient test point for scoping the motor current and also a slight amount of negative feedback as the earth return current for both

bridges passes through it.

This leaves the dual transistor X27 with its common emitter connection - it's a long-tailed pair. The Hall effect i.c.s are fed with approximately 5V via R23 and R24, the output sinewaves sitting on about 4V. Because the rotor pole fluxes are not necessarily equal, the two Hall effect i.c.s can give markedly different outputs. This would produce a rhythmic speeding up and slowing down of the head during each rotation – and bent verticals on the picture. To prevent this, the outputs from each Hall i.c. are fed to the bases of X27. As the outputs are in antiphase they cancel, leaving an average d.c. level which is what we need to monitor. If the d.c. tends to rise, the relevant half of X27 will turn on harder, reducing the supply to the i.c. Because of the common emitter resistor R31, an increase in the current flowing through one half of X27 will reduce the current flowing through the other half. This reduces the supply to the other i.c. and increases the output level from it. This balancing system ensures that the outputs remain the same. In practice the correction voltages are in the form of 25Hz sinewaves, most of the errors coming from magnetic imbalance of the rotors.

Before we leave the drum servo, a few words on the construction of the motor (see Fig. 121). The lower drum assembly, including the motor centre, is a finely machined alloy casting containing the two ballraces for the spindle. Under this is the printed FG coil on a printed board which also carries the Hall effect i.c.s, disposed at 90°. The plastic encapsulated stator coils are mounted vertically on this. The assembly is covered by the cylindrical rotor, which is a steel pressing and also acts as a flywheel. The six-pole permanent magnet, of cyclindrical form, is inside the rotor, with the 60-pole annular FG magnet on its upper end. The pick-up magnets (one N pole, one S pole) are mounted externally on the rotor, the pick-up head being mounted on the chassis. A word of warning – the ballraces are preloaded on assembly: don't dismantle the unit, as this preload is difficult to achieve on reassembly.

Next month we'll look at the capstan and reel servos.

The Card Game is Over

Les Lawry-Johns

Some time back I mentioned the card game we played at the Call Girl at lunchtime on Sunday. Honey Bunch's partner was Sean (John). For a long time Sean suffered from a bad heart and a damaged leg. Recently his leg got much worse and he was taken to hospital. He was found to have lung trouble and didn't survive long after an operation. H.B. took it upon herself to arrange the burial and all the other things that have to be done when there are no relatives to handle them. It's now over and done with, but we are left puzzled by the vacuum that Sean left behind him. No papers, no letters, nothing. He didn't talk much, and when he did he talked so softly that few heard all he said. We know that he had been resident in the Waterford or Wexford area and that he had served in the police force there for some ten years. We also know that the magazine has a number of readers in that area. He spoke of his father, brother and dog. Perhaps someone there knows a little more about John Joseph O'Leary? If so, we should like to hear from them. He was well known and liked here.

Testing Ultrasonic Handsets

Someone brought in a remote control handset that wasn't working. I checked it over, resoldered several suspect joints and fitted a new battery. I then realised that I didn't have a suitable set to check it on. All our new sets have infra-red remote control. The cat (Spock) was asleep on top of one of these sets. I pointed the unit at her and pushed the button. Her ears flicked. I waited a while then tried again, with the same result. This world shaking scientific test was carried out several times. We wrote: handset repaired and subjected to repeated tests on suitable receiver.

The Philips G11

The G11 can be a bit of a pain at times. One pained me the other day. A white line across the screen testified that all was not well with the field timebase circuit or the supply to it. Normally the TDA2600 field timebase chip goes short-circuit internally and blows the 800mA fuse on the line output panel. So, finding the fuse blown, I removed the heatsink on the TDA2600 and fitted a new chip. I then checked for shorts and fitted a new fuse. Switch on and pop goes the fuse.

I checked again for shorts. None. So I removed the chip, replaced the fuse and tried again without fitting a TDA2600. The fuse held. Fit another TDA2600. Pop. Conclusion: the i.c. was in order, the short occurring only when it came into operation. I looked at the circuit diagram and tried this, that and the other. It took this idiot some time to find that one of the two parallel-connected $1,000\mu F$ output coupling electrolytics was dead short. I should have found it in the first place.

Miss Spray

Miss Spray came in to tell me that her Pye 725 was playing up – the colours were constantly changing. We immediately diagnosed a faulty RGB output stage thick-

film resistor unit, and this proved to be correct. However... She had these two little dogs with her and they immediately caught the smell of Ben. They then tried to cover every vestige of such smell as best they could. After telling me her tale of woe she noticed what was going on. "You naughty boys" she snapped, "sorry Lorry".

I smiled weakly. Thank heavens they were small dogs. It took me about an hour to remove all traces of their visit.

Mrs Plunky's G8

Mrs Plunky phoned to say that her Philips TV (G8) had suddenly lost height. As she was on her own she couldn't bring it in. Not wishing to be away too long, I grabbed a G8 timebase panel and the rest of the boxes and sped to her house. I took in only the toolbox and the panel. She showed me the picture, and although the height was indeed lacking there was also a nasty curve inwards at the right-hand side. I decided against the panel and nipped out for the spares box. Removing the rear cover, I held a mirror to the front of the h.t. reservoir capacitor: there was severe deterioration, so out it came. Unfortunately I'd forgotten to put a 600 µF, 300 V electrolytic in the box. I'd several of the 470μ F type for the G11 and one $200+300\mu$ F 350V electrolytic can (Pye hybrid type). The latter was too long to fit in the original position, but it stood up nicely and the clip could be fitted to keep it there. The two positive tags were moved together, soldered to the red lead, then black to the negative tag and all was well. A nice picture with full height and width.

"Who's a clever boy then?" I squawked. "Who's the best boy in the world?" Unknown to me however Mrs Plunky had returned and was standing behind me. She was giving me an odd look.

"Do you always sound like a parrot?" she queried.

"Er, well. It't not so much a matter of parrots. My wife is trying to teach this young cockatiel to speak and it's sort of catching."

"She seems to be teaching it to be rather conceited" sniffed Mrs Plunky. "Do I owe you anything for this quick little job?"

Oh dear. No one seems to appreciate me any longer.

Round the Room Four Times

We get our share of strange tales. This young couple struggled in with their Ferguson 9600. The young man started the tale, which was eagerly taken up by the girl.

"The set goes all right for some time and then the picture goes funny" said he. "And we have to unplug it, wheel it round the room four times, then it's all right for the rest of the evening" said she. I looked at the set for some time, then asked the key question. "Clockwise or anticlockwise?"

She was struck dumb for once. "Clockwise" said he after a pause.

I turned the set up and, with the rear cover off, looked for a dry-joint under the centre section. "It curves in at the sides" he said helpfully. So I concentrated on the EW correction circuit and found one of the modulator diodes loose in its solder at one end. A quick dab of the iron with

the help of some fresh solder completed the job. When the set was turned the right way up the picture was slightly impure at one side – well, would you like being stood on end?

"Now listen" I said, with as straight a face as I could manage. "When you get back, wheel the set around the room four times anticlockwise. To unwind it, see?"

The girl nodded. The young man got the message but went along with the leg-pull. "Magnetism of the earth" he said.

"Exactly, and good luck to you both."

"When are you going to repair the set?" asked the girl.

"Already done dear. It had a cold and needed warming

DX Signal Detector/Alarm

G.R. Exeter

The circuit described in this article is capable of detecting very weak TV signals and providing an audible indication that a signal is present. It was developed primarily for use with rapidly changing sporadic E propagation. The basic idea is shown in Fig. 1. The video signal itself is used to provide the sound, giving an immediate indication of signal-to-noise ratio and interference. The filter section detects the 15,625Hz line frequency component of the signal, producing a switching voltage to control the video feed to the audio amplifier. In use, the channel being monitored must initially be clear of 625-line signals - the presence of some 405-line information will not upset the circuit's operation. Two phase-locked loops are arranged as a narrow-band filter to generate the switching voltage. System M, 525-line signals (line frequency 15,750Hz) are also detected.

Circuit Description

Fig. 2 shows the circuit. For the phase-locked loops, two TDA2591 (alternatives TDA2590 or TDA2593) i.c.s are used. These are fairly complex i.c.s intended for use as the sync separator and line generator sections of a TV receiver. Not all the internal circuitry is used. The sections that are used are shown in block diagram form in Fig. 3. These are the sync separator, oscillator and phase detector, i.e. the phase-locked loop, the coincidence detector whose output varies the gating of one input to the phase detector, and the pulse generator and output stages. Use is also made of the fact that the voltage at pin 4 can be employed to switch off the output at pin 3, while the burst gating/blanking pulse output at pin 7 is used for setting up.

It might at first sight appear that the output from the coincidence detector, at pin 11, could be used to indicate the presence of a signal without any further complication. The output here is similar whether the input consists of noise or a strong locked signal however. Instead, the two TDA2591s are run with slight frequency offsets: when a signal is present, an output is obtained once both circuits have locked in. The principle is shown in Fig. 4.

A negative-going video input should be used, though reduced performance will still be obtained with a positive-going input. The video input is first filtered by R1 and C1 to reduce the noise bandwidth. As there's no need to worry about picture cogging, more filtering than usual is

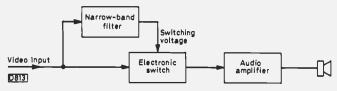


Fig. 1: Principle of the DX signal detector/alarm.

employed. This filtering also means that there's no need to make use of the noise-cancelling circuits within the i.c.s. The video signal is then buffered by Tr1 and fed via C2 and C8 to the sync separators in the i.c.s and via R23 and C16 to a convenient input for the TBA120S i.c.

The external oscillator capacitors are connected to pin 14 of the two TDA2591 i.c.s while pin 15 is used to set the frequency. High quality components should be used here in the interests of long-term frequency stability. The phase detector output at pin 13 is filtered and fed back to pin 15.

The output obtained at pin 3 of IC1 is applied to pin 4 of IC2 so that the latter produces an output only when pin

Components List

Resistors:		Capa	Capacitors:				
R2 R3 R4 R5	4k7 1M8 1k2 82k	C1 C2 C3 C4 C5	1n5 0.47 0.1 4.7 10n	ceramic polyester polyester 63V axial electro. polyester			
R6 R7 R8 R9 R10	12k 100k 2k7 2k7 10Ω	C6 C7 C8 C9 C10	4n7 47 0.47 0.1 4.7	polystyrene 25V axial electro. polyester polyester 63V axial electro.			
R11 R12 R13 R14	1M8 1k2 82k 12k	C11 C12 C13 C14	10n 4n7 47 47	polyester polystyrene 25V axial electro. 10V axial electro.			
R15 R16 R17 R18 R19	100k 10Ω 1k 10k 2k2	C15 C16 C17 C18 C19	47 0·1 1 0·1 1n	25V axial electro. polyester 63V axial electro. polyester ceramic			
R20 R21 R22 R23	100Ω 1k2 820Ω 100k	C20 C21 C22	100 0·1 47	25V axial electro. polyester 25V axial electro.			
R24 R25 R26 R27 All ¼W	10k 100k 10Ω 10Ω , 5%						

Miscellaneous:

D1	1N4148
Tr1, 2	BC252B or equivalent
IC1, 2	TDA2591
IC3	TBA120S
IC4	LM380
RV1, 2	47k sub. min. horizontal preset
RV3	10k 15mm min. PCB mounting

Small speaker

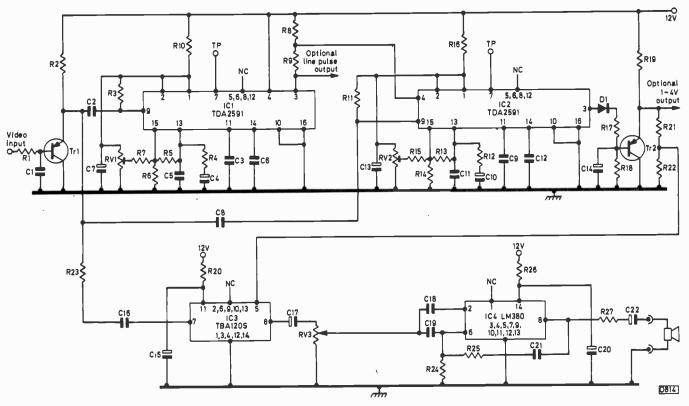


Fig. 2: Circuit diagram.

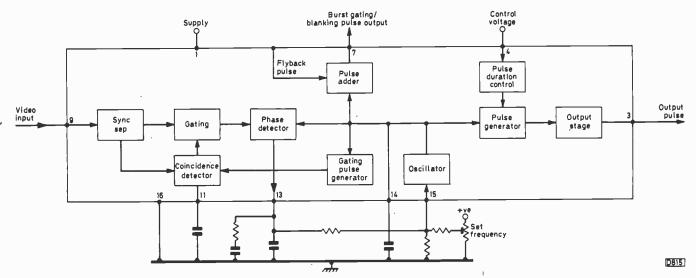


Fig. 3: Block diagram of the sections of the i.c.s used.

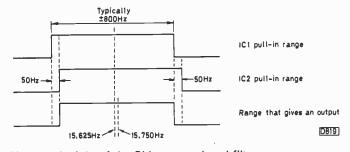


Fig. 4: Principle of the PLL narrow-band filter.

3 of each i.c. is high (with pin 4 at half the supply voltage, there's no output at pin 3). This output is integrated and buffered by Tr2, producing a control voltage which is typically less than 2V with no signal and 3-5V when a signal is present. This is an on/off output, though noise and phase jitter make the control voltage appear to

change more linearly.

The TBA120S is used to provide the switching action, the output from Tr2 being fed to pin 5 – in normal use, the d.c. volume control is connected to this pin. The i.c. smooths out the on/off transitions and avoids a jarring crash when a signal is detected. Another advantage of the TBA120S is the 70dB attenuation possible, ensuring that there is no stray low-level output from the speaker.

The switched video output appears at pin 8 of the TBA120S and is then fed via a volume control potentiometer to pin 2 of a simple audio amplifier i.c. This in turn drives the speaker.

Construction

The prototype was constructed on a PCB (see Figs. 5 and 6) and has given satisfactory operation for many months. The following points should be noted however.

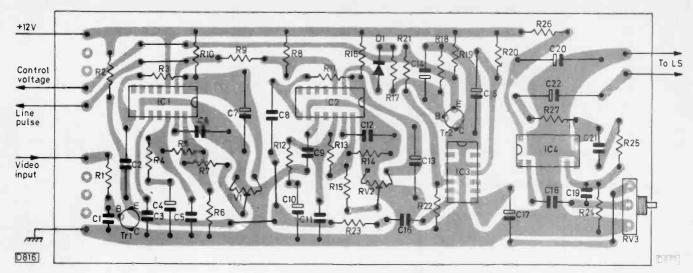


Fig. 5: Component layout.

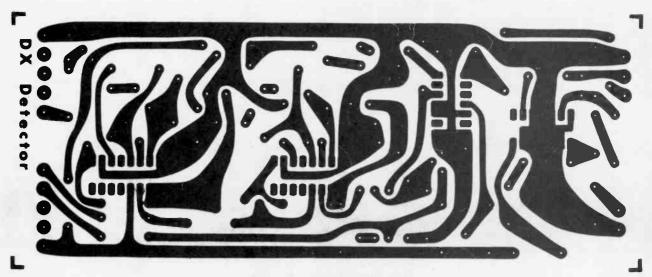


Fig. 6: Track pattern, scale 1:1.

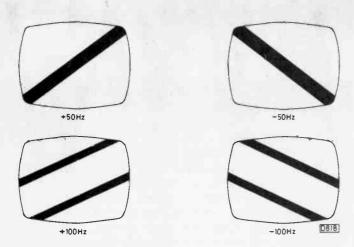


Fig. 7. Adjustment displays.

First, in all systems using two oscillators at the same frequency there's a tendency for them to lock together if the earthing and supply decoupling are inadequate. A small amount of coupling was present with the prototype when the input was grounded, but this was sufficient for only a few Hz of common lock-in range and didn't upset the setting-up procedure.

Secondly the input is very sensitive to 15kHz signals. If

it's not connected directly to a low-impedance source of video in the i.f. strip, it should be screened from any nearby timebase radiation. Timebase currents should be kept separate from the receiving system.

Thirdly the TBA120S's volume control characteristic has a fairly wide spread. The values of the pot-down resistors linked to pin 5 may require optimisation therefore. The device used should have internal bias resistors connected to pins 7 and 9. All devices examined, other than ITT ones, appeared to have these: the ITT i.c.s rely on the presence of a quadrature coil to provide d.c. bias at pin 9, a difference that doesn't show when the i.c. is used as an f.m. detector.

A miniature 8Ω speaker was used, with R27 included to restrict the maximum power. Any small speaker can be used. A 12V regulated supply capable of supplying 140mA is required. If not already available in the set, one can be built using any of the popular i.c. regulator circuits.

Alignment, Testing and Use

To set up the system, ground the input and loosely couple pin 7 of IC1 (11V peak-to-peak burst gating/blanking pulse output) via suitable attenuating resistors to the video channel of a system locked to a standard broadcast signal. Adjust RV1 for an offset of approxi-

mately 50Hz (see Fig. 7). This, as shown, can be judged by the slope of the pulse output displayed on the screen. Repeat this step for IC2, setting the offset in the opposite direction. If available, a frequency counter can be used, adjusting for $15,625 \pm 50$ Hz. If the frequency difference is too large, IC1 and/or IC2 may not be able to pull in: if too small there may be false locking problems. The prototype worked well with 50Hz and 100Hz offsets. Pin 7 is used as the setting-up monitoring point rather than pin 3 as there will always be an output at pin 7 of IC2.

The unit should now be working. If there are problems, a further test can be made at the emitter of Tr2 as video signals are applied and removed. The voltage here should vary from below 2V to greater than 3V. The audio control stages can be tested by varying the voltage at the base of Tr2 between 0V and 4V (volume control midway) with an input signal present. The audio output should be present at 4V.

The total supply current with no audio output should be

about 100mA, and without IC1 and IC2 about 35mA.

When two strong signals are received simultaneously, it's possible that IC1 may lock to one and IC2 to the other, giving a lock-out condition. Usually however a warning of improving conditions will already have been given, so the condition should not be troublesome.

As it stands the unit is capable of monitoring one channel continuously. To cover more channels, either more receiver systems and detectors are required or alternatively the tuner could be stepped through several preset channels at a rate slow enough for the detector to respond, say three-four seconds per channel. A method of doing this was described in the January issue. The system response time is set by the filtering at pin 3 of IC2, and is sufficiently fast to give a response with the stronger meteor-scatter signals.

Finally, a word of warning. Some Russian transmissions start at 4 a.m. our time. I can testify that SpE reception does occur at this time!

A Question of Black Level

Malcolm Burrell

Black level is quite a useful test signal: it's also useful for video purposes. When making a programme, presentation comes a close second to the actual content. Adding a little black level between programme segments improves the editing, and a minute of black at the start of the tape, where most of the wear occurs, removes picture dropouts here. Thus when the cassette is inserted dropout effects should clear before the programme begins. In addition, rolling noise bars at the start are not seen. Tape noise and dropouts tend to be more easily seen on a plain blank raster, enabling the tape quality to be more easily assessed.

Black level can be obtained in several ways. One source is a camera with the lens capped. Another is a broadcast transmission, though you will be lucky to find a transmitter broadcasting black when you want it – the days are passed when transmitter line-up consisted of perhaps an hour of black-level and tone signal. Yet another source is a workshop pattern generator. Some don't give true black level without modification, so you might have to make do with a red or blue raster with the colour removed – some VCRs have a monochrome/colour switch.

Black Level Generator

In the interests of convenience however I decided to make use of a Ferranti ZNA234 chip mounted in a compact case. This is basically a pattern generator i.c. that also provides fully interlaced sync pulses. It might seem a little wasteful, but only the mixed sync output is used. The 5V supply required is obtained from a battery via a 78M05UC stabilizer – the chip likes about 135mA, which is more than mini-regulators can handle. The prototype uses a 2.5MHz crystal, though this can be replaced with a single fixed capacitor of about 15pF if you're not too concerned about stability.

The mixed sync output from the ZNA234 drives a couple of gates in a TTL chip. The gate outputs are linked together via 27Ω resistors to give a 75Ω output. Connect the signal to the VCR via a short screened lead terminated

with a u.h.f., BNC or phono plug as required. You can thus record black level at any desired point by connecting the output to the video input socket and switching the machine to "aux" or "camera".

The unit can be easily constructed on Veroboard and accommodated in a small Vero box near the machine. Battery life will not be very long, but for short periods of use this is not very important. An LED indicator is useful next to the on/off switch.

You can't fade to black of course when using this black-level generator – it's much more of a cut to black level. Suppose however that you wanted to keep a selection of news items. You could judge the point at which the first is faded down, then add your black level for anything from three to ten seconds. You then edit in the next item as it is faded up.

This black-level facility is particularly useful with a VCR that doesn't have back-wind or insert-edit facilities, since most of the disturbance that arises will occur during black and thus be much less objectionable. It also makes a much cleaner distinction between the different items on the tape. The ZNA234 costs about £8.50, so the total cost of construction need not be more than £12 or so. If you want to use the chip's other patterns, refer to the TV pattern generator article in the October 1981 issue.

Overseas readers with 525-line signals can use this chip by connecting pin 2 to chassis instead of to 5V and employing a 2.52MHz crystal.

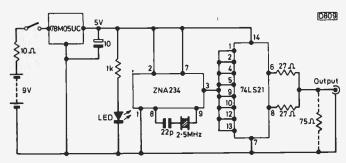


Fig. 1: Black level generator circuit.

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1-00 postal order (made out to IPC Magazines Ltd.), the query coupon on page 271 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

FERGUSON 3V00

When playing back a recording the picture continuously moves from left to right by about three eights of an inch. The fault is more noticeable when the picture subject is stationary, and doesn't occur with prerecorded tapes.

It seems that the head speed is varying on record only. If the variation is erratic and random, suspect a dirty record/playback switch. This is the longer one of the two slide switches on the left-hand audio/servo board. Try cleaning it first. If the hunting is rhythmic and regular, the two head servo presets (discriminator and drum sample) probably need adjustment. Failing this the drum motor may be defective – check the ripple as described in the manual.

SABA F CHASSIS

There is slight cramping, about a quarter of an inch deep, across the centre of the picture. It's only apparent when the camera shot is moving up or down and when the credits roll.

This can be an awkward problem and is due to non-linearity in the field oscillator circuit. Check by substitution capacitors C691 $(0.1\mu\text{F})$, C692 $(0.0022\mu\text{F})$ and C693 $(0.022\mu\text{F})$. They go slightly leaky and for some reason cause distortion at the centre of the field sawtooth waveform at pin 1 (triode anode) of the PCL805.

GEC HYBRID COLOUR CHASSIS

The flywheel sync diodes used in this chassis share a common encapsulation, but the FSY41A doesn't seem to be available any more. Any ideas for substitutes?

We've successfully used a pair of 1N914 or ITT2002 diodes in this position. A pair of 1N4148 or BY206 diodes should work just as well.

RANK A823A CHASSIS

The line output transistors have been replaced and I now want to balance the line output stage (6L4/5). It seems however that the balancing network has been removed. How do I monitor the adjustment?

6R6 and 6C5 were omitted in later production. To balance the stage, adjust the coils for minimum picture width: a "null" should be found, and this corresponds with correct balance.

ITT CVC25 CHASSIS

The problem with this set is vision interference – it takes the form of streaking horizontal lines on all channels. Removing the aerial input leaves a snowy raster with mushy sound: the interference remains but is not as bad. The cause could be in the field timebase as there has been lack of height with top foldover on one or two occasions, though it lasted for only two-three seconds.

First check the connections between the printed panel and the mains switch – dry-joints can occur here. Then check the mains filter capacitor: replace this if it's of the cylindrical yellow type, as these are given to internal arcing. If the fault persists and no bad joints can be found around the power supply panel, in particular around the surge limiter resistors R76/7 and the BY133 h.t. rectifiers, concentrate on the field timebase. If the problem lies here it's more likely to be with the output transistor pair T8/9 than in the pluggable module.

THORN 3000 CHASSIS

There's a good, clean monochrome picture but this becomes increasingly noisy as the colour is turned up. At the correct colour control setting the noise gives the impression of a poor level signal from the aerial, but the signal strength here is first class.

If the colour is locked, check transistor VT110 and the a.c.c. smoothing capacitor C173 ($2.5\mu\text{F}$) on the i.f. panel. If necessary, check the chroma amplifier transistor VT309 and the blanking diodes W316/7 on the decoder panel.

PHILIPS G11 CHASSIS

No sound or raster led to a check on the h.t. fuse which had blown. Tests in the line timebase failed to reveal anything amiss, but the only way of preventing fuse failure is to disconnect the h.t. supply to the line timebase. The h.t. is 180V instead of 153V.

The excessive h.t. is the cause of the problem and is likely to be due to failure of the BD201 active smoothing transistor. The 27V zener diode D4021 usually fails as well. A common cause of this situation is the h.t. reservoir capacitor C4029 which develops loose internal connections at the rivets. Try gentle mains application via a 110V transformer at first to save fuse blowing – a 100W lamp will do if you don't have a transformer.

RANK T22 CHASSIS

There's no colour on this set except when the colour-killer override link is connected. With the set slightly off tune there are colour patches on the screen. Replacing the three decoder i.c.s has made no difference.

We've known electrolytic capacitors cause this sort of thing in the T130A decoder. Check C83 ($3.3\mu F$) and C85 ($1\mu F$) by substitution and C84 ($0.22\mu F$) by replacing it with a polyester type if you find it's a tantalum electrolytic. If necessary check C87 ($4.7\mu F$) as well.

THORN 8500 CHASSIS

The problem is vertical black lines, about one eighth to a quarter of an inch wide, at roughly quarter inch intervals right across the screen: they are not straight but curve with the edge lines of objects on the screen. Neither changing channels nor cleaning the tuner contacts improves matters.

Check the condition and adjustment of the set tuner gain control R102. If this is o.k., suspect the tuner – we've known this effect to be caused by a form of tuner instability.

GEC C2110 SERIES

There's poor field linearity, with bottom cramping and a white line that moves rapidly up and down the bottom half of the screen. Field collapse sometimes occurs for a few seconds, then a full, normal picture appears for a while before the linearity faults return.

These sets are prone to problems due to poor earthing of the field timebase panel (at PL28/1). You can check this by using a screwdriver to link the panel's earth print to the metal chassis. If all's well here and capacitors C457/8 (field charging) and C462 (bootstrap) are o.k., the field output transistors are probably faulty.



Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults

Good service costs money in the TV trade - the cost of service attention by a reputable and well organised firm can be considerable. In our part of the world (and most, we suspect) there are several rather shady operators who offer their services at very low rates and whose attention can be inexpert to say the least. From time to time we encounter the results of their efforts when a set owner, in desperation, brings us a set to sort out. Similar situations have been described in these pages by other contributors: here's one of our botch stories.

The set's owner, a rather shady character himself, brought in a dog-eared and frayed Tandberg 22in. TV set. He then went back to his van and brought out the back cover - always a bad sign. Without removing his handrolled cigarette from his mouth, he hissed in a conspiratorial whisper "give us an estimate mate, colour's all wrong". We switched the set on there and then so that if the tube was flat he could take it back with him. A quick check showed that all three colours were present, but the picture looked like a colour snapshot negative! We promised to contact him when we'd got to the bottom of the

On the bench we started by turning the colour right down to check the grey scale tracking. It was reasonable, though marred by a degree of impurity on one side. We made a mental note to deal with that later. The set was then tuned to the local Channel 4 test pattern, and on advancing the colour control setting a strange sight met our eyes! In order, from left to right, the colour bars were magenta, yellow, red, cyan, blue and green. Someone had swapped the drive leads to the tube - but inspection proved otherwise. The leads were correctly positioned on the tube base panel and at the RGB output stages.

Tongue in cheek we interchanged the leads - R drive to the green cathode, G drive to blue and B drive to red. This produced reasonably good colour within the tracking and purity constraints previously mentioned. Suspecting some diabolical trickery in the decoder or RGB output stages we carefully examined the panel, but could see nothing amiss on either side.

With full colour bars still displayed, we made an oscilloscope check on the RGB drives. They were correct, with the right R, G and B primary colour waveforms coming from the right amplifiers! Back to the c.r.t. base panel. We could see no modifications or wiring alterations, and to confirm that we were not becoming unhinged we checked at the appropriate tube pins themselves - nos. 2, 6 and 11 for R, G and B respectively with this A56-120X tube. The waveforms were correct.

When the man returned for his set he had a considerable bill to pay, mostly down to time rather than components. It had taken us half an hour to find a means of refitting the set's back cover, and rather longer to sus out the cause of the colour problem. You needn't concern yourselves with the back screws, just the wrong colour effect: answer next month!

ANSWER TO TEST CASE 254 - page 217 last month -

The problem described last month was no field scan in a Doric colour portable fitted with the Rediffusion Mk. 5 chassis and our attempts at diagnosis, having twice convinced ourselves that the field oscillator/driver chip was faulty. The virtually zero d.c. voltage at pin 3 of the chip should have pointed us in the right direction, for if Q502 was not switching on - and it wasn't, without any drive there should have been a fairly high voltage at its collector and thus at pin 3 of the i.c., due to the conduction of

Q501 was not conducting however, for the very good reason that its base bias resistor (Q502's load resistor) was open-circuit. It looked all right, but there was 73V at one end and nothing at the other. The design of the field timebase chip is such that with zero feedback at pin 3 it shuts down, which is what was happening. We must confess that we were happier with PCL805s and the like sometimes you got a dud spot on the height control, or the valve got broken . . .

QUERY COUPON

Available until 21st March 1984. One coupon, plus a £1.00 (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice on page 270.

TELEVISION MARCH 1984

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 OPF. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £11, overseas (surface mail) £12 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

						UPC 1366C UPC 1367C	3.00 3.00	BC108 BC109	0.11 0.10	BF274 BF337	0.11 0. 32	REGULA	rors	THICK FILI	
RI I		ECT	DC	AHIC	2	UPC 1368H	4.00	BC116	0.13	BF338	0.32	78 Series 1			
IN J		.ECT	ηL	JIRIC	-2	UPC 1370C2	4.00	BC140 BC141	0.30 0.30	BF355 BF458	0.56 0.48	15V 18V 24			0.60
82 - 84 ST	ORFO	ORTH LANE	TRA	DING ES	TATE	UPC 1373H UPC 1377C	1.11 4.50	BC142	0.30	BF459	0.51	79 Series 1 Voltages as		33MΩ t 47MΩ	0.60 0.60
HASLAND						UPC 1378H	4.00	BC143	0.27	BFR79 BFY50	0.26	negative ou			0.00
CHESTER		1				UPC 1382C	1.97	BC147	0.09	BFY51	0.24	78L Series 1			KC
S41 OSN	ILLU	•	TEI	(0246) 2	100070	UPC 1384C UPC 1447W	5.70 0.98	BC148 BC149	0.10 0.09	BFY52	0.23	12V 15V 24V 79L Series		*	
341 USN			IEL	. (0246) 2	203079	UPC 1470H	0.90	BC154	0.11	BU 105 BU 108	1.40 1.60	Voltages as		T018	0.06
						UPC 2002V	2.80	BC157	0.10	BU124	0.98	negative ou			0. 09 0.15
INTEGRATE	ED CI	RCUITS		UPC 41C	3.50	DIODES		BC158 BC159	0.11 0.11	BU126	1.60			T05 25mm	0.19
BTT 822	1.90	TA 7609P	4.00	UPC 393C UPC 554C	2.90 1.34			BC170	0.13	BU137 BU204	1.40 1.40			T03	0.17
CA 3089	1.20	TA 7611AP	2.90	UPC 555H	0.80	BA148 BA159	0.18	BC171	0.10	BU205	1.40	MODILLE	•	T03 FINNED	0.60
ETT 6016	1.95	TA 75902P		UPC 556H3	1.70	BB103	0.10 0.20	BC172 BC173	0.13 0.12	BU208 BU208A	1.55 1.90	MODULE	3	T0220	0.34
ETTR 6016	1.95	TAA 320A	1.30	UPC 557H	0.92	BB105B	0.20	BC174	0.12	BU208D	2.30	PYE IF GAI	N 7.1	BO TO126	0.34
MC 1307P MC 1310P	1.70 1.20	TAA 470 TAA 550	2.30 0.39	UPC 566H3	3.50 0.55	BY127	0.11	BC182L	0.09	BU326 BU407	1.80 i 1.40			WOUND	
MC 1327P	1.10	TAA 691	1.95	UPC 575C2	1.49	BY133 BY176	0.11 1.35	BC183L BC184L	0.09 0.09	BU426V	1.70	SWITCH		COMPONEN	STI
MC 1330P	1.50	TAA 700	1.65	UPC 577H	3.50	BY184	0.40	BC207	0.03	BU526 BUW81A	1.62 2.55	Thorn 3000/		G11 E.W. Coil	1.32
MC 1349P MC 1351P	1.10	TBA 120A	0.75	UPC 585C UPC 741G	1.49 0.95	BY187	0.69	BC212L	0.09	E1222	0.35	Gen Purpos Pull	0.80	G11 E.W. Trans	
MC 1352P	1.20 1.50	TBA 120AS TBA 120B	0.75 0.78	UPC 1009H	2.41	BY190 BY210-800	0.60 0.29	BC213L	0.11	FT3055 MJE340	0.65 0.50	G11 Non Re		Decca 100 E.W.	
MC 1358P	1.20	TBA 120C	0.75	UPC 1017G	2.50	BY223	0.25	BC237 BC238	0.10 0.10	MJE520	0.45	Round Shaf		Coil Linearity Coil	1.32
ML 236E	3.00	TBA 120SA	0.75	UPC 1018C	1.19	BY226	0.27	BC250	0.11	R2008B R2009	1.70 1.90	G12 G8 Plastic	0.85 0.85	AT4042/02	1.15
ML 237B SAA 1021	1.80 3.80	TBA 120U TBA 231	0.75 1.65	UPC 1023H UPC 1024H	0.63 0.63	BY227 BY295	0.31 0.25	BC251 BC252	0.11 0.10	R2010B	1.90	G8 Metal	1.30	Transductor	4.05
SAA 1024	2.40	TBA 396	1.70	UPC 1025H	3.70	BY296	0.25	BC253	0.11	R2028 R2029	1.90 1.90	ITT Petrick	0.95	90° 110°	1.65 1.85
SAA 1025	4.40	TBA 395	1.70	UPC 1026C	1.60	BY298	0.25	BC301	0.31	R2030	1.90	1500 Rotary 3 Pole Sing		110	1.93
SAA 1124 SAA 1130	2.40 4.30	TBA 480 TBA 510	0.99 1.20	UPC 1028H UPC 1031H2	2.40 2.40	BY299 BYX10	0.25 0.21	BC302 BC303	0.31 0.33	R2265 R2305	1.90 0.65	Rank TCE,		CRYSTALS	
SAA 5040	7.50	TBA 520	1.50	UPC 1032H	0.98	BYX36-600	0.21	BC307	0.13	R2306	0.70	2 Pole +No	om Make		
SAS 560	1.80	TBA 530	1.45	UPC 1035C	2.50	BYX71-350	0.50	BC308 BC327	0.13 0.11	R2322 R2354B	0.70 0.78	Philips G11/ Remote	/G12 1.30	4.43MHz	1.80
SAS 570 SAS 660	1.80 2.30	TBA 540 TBA 550	1.70 1.80	UPC 1037H UPC 1041H	1.62 1.28	BYX71-600	0.99	BC328	0.13	R2396	0.80	Thorn 1615		8.86MHz 8.86MHz	1.80
SAS 670	2.30	TBA 560C	1.90	UPC 1042C	2.60	BYX55-600 BR100	0.33 0.35	BC337	0.11	R2441 R2461	0. 83 2. 00	Control	3.50	Miniature	1.75
SL 901B	4.50	TBA 570	1.10	UPC 1043C	2.60	0A47	0.10	BC338 BC350	0.13 0.12	R2477	0.78	3000 A1	0.55		
SL 917B	6.20	TBA 750	1.50	UPC 1156H	2.40	0A90	0.08	BC365	0.30	R2501 R2540	2.00 2.10	3500 A1 Vert Gun S	0.55 witch	VIDEO THIC	:K
SN 16862AN SN 16964AN	2.50 2.50	TBA 800 TBA 810S	1.10 0.90	UPC 1158H UPC 1161C3	0.7 8 1.5 8	OA91 SKE5F	0.08 1.40	BC413 BC460	0.11 0.48	SP8385	2.10	(A1)	0.25	FILMS	
SN 29848	2.25	TBA 820	1.20	UPC 1163H	0.98	IN60	0.08	BC461	0.52	T9011V T9016V	0.80	Horiz Gun S		3500	1.45
SN 57108AN	1.95	TBA 890	3.50	UPC 1167C2	1.58	IN4001	0.05	BC462	0.53	T9035V	0.82	(A1)	0.25	Pye 713	1.90
SN 76001AN SN 76003	1.60 2.20	TBA 920 TBA 950	2.00	UPC 1168C	2.75 1.75	IN4002 IN4003	0.05 0.05	BC463 BC527	0.53 0.13	T9038V T1P29	3.50 0.38			Pye 731	1.90
SN 76013N	2.50	TBA 990	1.60	UPC 1171C	1.62	IN4004	0.06	BC528	0.13	TIP30A	0.34	DELAY L	INES		
SN 76013ND	2.50	TBA 1440	2.70	UPC 1173C	2.14	IN4005	0.07	BC546 BC547	0.10 0. 09	TIP31A TIP31C	0.34 0.48	DL50	1.00	FILTERS	
SN 76023N SN 76131N	2.20 1.35	TBA 1441 TCA 270S	2.70 1.90	UPC 1176C UPC 1177H	2.43 2.60	IN4006 IN4007	0.07 0.07	BC548	0.09	TIP32A	0.34	DL700	1. 8 0 1.70	6MHz	0.78
SN 76226DN	1.60	TCA 270SQ	1.90	UPC 1178C	2.14	IN4148	0.03	BC557	0.10	TIP32C TIP33B	0. 48 0.75	TAD80	1.70	SW150	2.20
SN 76227N	1.20	TCA 640	2.60	UPC 1180C	3.00	IN5402	0.13	BC558 BD131	0.10 0. 30	TIP41A	0.46	Luminance		SW154	2.20
SN 76532 SN 76550	2.00 0.29	TCA 650 TCA 660	2.40 2.80	UPC 1181H3 UPC 1182H	1.62 2.70	IN5404 IN5406	0.15 0.17	BD132	0.36	TIP41C TIP42A	0.58 0.45	TBA560)	2.00		
SN 76546	1.80	TCA 740		UPC 1183H	2.30	IN5408	0.17	BD135 BD136	0.30 0.30	TIP42C	0.68			SUNDRIES	
SN 76660	0.90			UPC 1185H2	3.50	Y969	0.87	BD139	0.33	TIP30A TIP31A	0.34 0.34	TUNER	i	12 Way Termin	al
SN 76666N SN 76707	1.10 1.70	TCA 830S TCA 940		UPC 1186H UPC 1187V	0, 98 1,70	ZENERS		BD140	0.60	TIP31C	0.48	PRESETS	;	Block 2A	0.20
TA 7061AP	3.60	TCA 4500A		UPC 1188H	3.60			BD150A BD207	0.70 0.90	TIP32A TIP32C	0.34 0.48	G8/G9	0.48	5A	0.22
TA 7063AP	3.50	TDA 1003	2.00	UPC 1190C	2.00	400MW 2V4 to 75V	0.10	BD221	0.40	TIP33B	0.75	Thorn/GEC	0.48	Min Insulated (Clip Red or	PLOC
TA 7066P TA 7072P	3.90 2.90	TDA 1004A TDA 1044	2.20 2.50	UPC 1191V UPC 1197C	1.70 1.70	1.3W	0.10	BD228 BD233	0.35 0.53	TIP41A TIP41C	0.46 0.58	G11	0.48	Black	0.07
TA 7073AP	3.20	TDA 1170	2.80	UPC 1198H	1.41	2V7 to 91V	0.18	BD234	0.38	TIP42A	0.45			Standard Croc	0.00
TA 7074P	3.30	TDA 1180	2.10	UPC 1200V	1.97	100V to 200V	0.19	BD238 BD239	0.38 0.42	TIP42C TIP100	0.68 0.70	EHT LEA	ns	Clip GEC Neon	0. 08 0.15
TA 7076P TA 7089P	3.30 2.40	TDA 1190 TDA 1327	2.00 1.70	UPC 1204C UPC 1208C	1.63 2.00	BZV15C12R	1.18	BD253B	0.65	TIP130	0.70			3500 Cut out	2.00
TA 7093P	2.90	TDA 1412		UPC 1211C	4.00	BZV15C24R	1.18	BD416	0.42	TIP2955 TIP3055	0.74 0.55	Diode Split		Focus Spark	0.45
TA 7108P	2.44	TDA 2002	1.90	UPC 1212C	1.34	BZV15C30R	1.18	BD534 BD595	0.33 0.55	TIS90	0.90	lead EHT Cap	1.60 0.75	Gaps Rank Tuner	0.15
TA 7117P TA 7120P	3.20 1.61	TDA 2010 TDA 2522	1.80 2.40	UPC 1213C UPC 1215V	1.53 2.70	BRIDGE RI	ECT.	BD596	0.55	TIS91 2N3055	0.24 0.73	10M Pack of	of EHT	Cams	0.08
TA 7129AP	3.20	TDA 2522		UPC 1216V	1.99	B40	0.80	BD681 BD807	0.58 0.50	2SB350A	1.90	Cable	1.50	5yds PVC Tape	
TA 7130P	1.38	TDA 2530	2.20	UPC 1217G	3.59	BY164	0.50	BDX32	1.70						
TA 7137P	2.00	TDA 2532		UPC 1218H UPC 1222	3.00	BY179	0.70	BF127	0.30	THYRISTO	RS		DIS	COUNTS	5
TA 7139P TA 7146P	2.75 2.00	TDA 2540 TDA 1365	2.20 5.75	UPC 1223	2.00 3.70	W005	0.25	BF137 BF180	0.30 0.29	KONIG 15/80	Univers	al 2.47			=
TA 7157P	3.20	TDA 2541	2.30	UPC 1225	3.00	TRANSIST	ORS	BF181	0.27	KONIG 15/85		al 2.47		ERS OVER	
TA 7171P	3.20	TDA 2560	2.05	UPC 1226 UPC 1227	2.49 2.00	AC127	0.30	BF182 BF185	0.28 0.32	BR101 BR103		0.37 0.62	£50	IN VALUE	
TA 7172P TA 7176AP	3.30 3.00	TDA 2571 TDA 2581	2.10 1.30	UPC 1228H	0.90	AC127 AC128	0.30	BF194	0.10	BRY39		0.56		5%	
TA 7193P	5.20	TDA 2582	1.80	UPC 1230H	3.60	AC153K	0.36	BF195 BF196	0.11	BRY49		0.65			
TA 7202P	3.30	TDA 2593		UPC 1238V	1.90	AC176	0.30 0.30	BF196	0.13 0.13	BRY55 BRY56		0.60 0.37		ERS OVER	
TA 7203P TA 7204P	3.30 2.16	TDA 2600 TDA 2611A	5.00 1.15	UPC 1245 UPC 1250	2.20 2.40	AC186 AC187	0.30	BF198	0.16	BT100		0.37	£120	IN VALU	E
TA 7205P	1.40	TDA 2640	1.80	UPC 1350C	4.50	AC188	0.30	BF199 BF200	0.18 0.34	BT106		1.55		10%	
TA 7208P	2.70	TDA 2653	2.10	UPC 1353C	2.80	AD149	0.88	BF240	0.16	BT116 BT119		1.60			
TA 7210P TA 7222P	5.60 1.70	TDA 2680 TDA 2690		UPC 1356C2 UPC 1358H	3.00 3.00	AD161 AD162	0.45 0.45	BF245 BF256L	0.30 0.40	BT119 BT120		2.00 2.00		r Value no	
TA 7223P	3.50	TDA 3560	5.10	UPC 1360C	3.50	AF139	0.48	BF258	0.40	DEC1		1.70	ınclu	iding VAT)
TA 7227P	5.10	TDA 3561		UPC 1361C	3.70	AF239	0.60	BF259	0.32	OT112		1.85	VIDEO	HEADS	R,
TA 7310P TA 7313P	1.70 2.80	TDA 3950 TDA 4600	2.40 2.10	UPC 1363C UPC 1365C	3.50 5.00	AU113 BC107	2.60 0.10	BF264 BF273	0.40 0.13	0T121 2N4444		1.55 1.55		EXCLUDE	
70101	2.50	. 57. 1000	2.10	15.5 ,0000	5.00	30.3"	0.10	1	3.10			,,,,,	Ortio		

N. J. ELECT	RONICS	FOCUS UNITS	SMOOTHING CAPACITORS	RESISTORS (CARBON)	EHT TRAYS Decca 1830 5.90
SERVISOL	PLUGS-SOCKETS	RRI T20 1.80 1.90 1.90 Focus Rods 1.10	Decca 200/200/400 350V2.70 Decca 400/400 350V 2.90	½ Watt IRO to 10M (10 Pack) 0.18	Decca 2230 6.25 Decca 80 6.25
Super Servisol 0.88 Freezer 1.04 Aero Kleen 0.86 Silicone Grease	Phono Plug Plastic (red or black) Phono Plug Metal Phono Line Skt 0.18	CAPACITORS MIN PLATE CERAMIC 63V	Decca 400/800 350V250V 2.90 Philips 600 300V 2.50 Philips 2200 63V 1.55	1 Watt 2R2 to 10M (10 Pack) 0.39 2 Watt 4R7 to 10M (10 Pack) 0.60	Decca 100 6.25 GEC 1028 6.25 GEC 2040 6.25 GEC 2110 6.25
(serosol) 1.10 Silicone Grease (tubes) 1.70 Foam Cleaner 0.92 Plastic Seal 0.96	Phono Chassis Skt 0.19 DC Plug 2.1mm 0.19 DC Plug 2.5mm 0.19 OC Chassis Skt 2.1mm &	1.8PF to 12,000PF 0.05 10,000PF to 12,000PF 0.06 POLYSTYRENE 160V	Philips 470 250V 2.00 Philips (69) 600 300V 2.80 PYE 200/200/100/32 2.85 PYE 600 300V 2.90 RRI 2500/2500 30V 1.20	RESISTORS (WIREWOUND)	GEC 2200 6.25 Grundig 5011 6.25 HTT CVC 5/8 6.25 HTT CVC 20 6.25
Heatsink Compound 1.20 Solda Mop 0.75 Video 40 0.93 Super 40 1.60 Add 30p per can additional post	2.5mm 0.19 Coex Plug 0.15 Coex Coupler /* Mono Jack Plug 0.15 /* Stereo Jack Plug 0.27 3.5 St Jack Plug 0.25	10PF to 820PF 10,000PF to 15,000PF TANTALUM BEAD .1MF 35V .15MF 35V 0.16	RRI 2500/2500 30V 1.20 RRI 220 400V 2.90 Thorn 150/160/100 300V 1.90 Thorn 4700 25V 0.85 Thorn 1000 70V 0.70 Thorn 200/100/100 350V 2.85 Thorn 175/100/100 400V 2.40 Thorn 400 400V 2.40 Thorn 400 400V 2.55	2½W 0R22 to 10R 5W 0R47 to 6K8 0.15 7W 0R47 to 12K 0.15 11W 0R1 to 18K 0.18 17W IR0 to 6K8 0.24	1TT CVC 45 6.25 Korting 90° 6.95 Philips 520 6.50 Philips 550 6.50 Philips G9 6.25 Philips 570 6.50
SOLDER	1" Jack Line Coupler Mono 0.22 1" Jack Line Coupler	.22MF 35V 0.16 .33MF 35V 0.16 .47MF 35V 0.16		PRESETS	Philips KT3 8.95 PYE 691/697 6.30 PYE 713 5 lead 6.50
Mini Pack 0.35 }Kilo 18\$WG 7.00 }Kilo 22\$WG 7.95	3 Stereo O.25 3" Mono Jack Chassis Socket O.24 3" Stereo Jack Chassis Socket O.24	.68MF 35V 0.16 1MF 35V 0.16 1.5MF 35V 0.16 2.2MF 35V 0.17 3.3MF 35V 0.18	PUSH BUTTON UNITS Decca 30 4 way 6.80	Horizontal and Vertical Standard and sub mid sizes 100R to 4M7 0.12	PYE 713 4 lead 7.60 PYE 725/731 6.25 RRI 823 7.75 RRI T20 6.50
SOLDERING AIDS	3.5mm Socket 0.10 2.5mm Socket 0.10	4.7MF 35V 0.18 6.8MF 35V 0.20 10MF 35V 0.20	Decca 30 6 way	Decca 20 mono 1.35	Tandberg TV2-2 6.50 Thorn 1500 3 stick 4.95 Thorn 1500 5 stick 5.50
Antex 15W Iron 6.25 Antex 25W Iron 6.60 Antex 15W Bit 0.70 Antex 25W Bit 0.75 Desolder Pump 6.00 Nozzle 0.85 Antex Elements 15W & 2.50	D.I.N PLUGS 2 Pin 0.10 3 Pin 0.10 4 Pin 0.14 5 Pin 180° 0.19 5 Pin 240° 0.19 5 Pin 360° 0.19 6 Pin 0.23 7 Pin 0.23	22 MF 16V 0.24 MIXED DIELECTRIC .01 1000V 0.24 .01 1500V 0.25 .022 1000V 0.28 .1 1000V 0.30 .1 1250V 0.46 .1 1250V 0.46 .2 1000V 0.78	GEC 2136/7 GEC 2112 Conversion 13.00 Hitachi 190 4 way 8.95 ITT CVC5 7 way 10.00 ITT CVC8/9 12.85 ITT CVC20/30 6 way 8.00 ITT CVC 25 6 way 8.50 Philips 520 11.00 Philips 550 13.55 Philips G11 22.50 PYE 713 4 way 8.70	Decca 30 3R9 0.60 Philips G8 2R2 + 68R 0.84 Philips 210 (no link) 1.10 Philips 210 (with link) 0.95 PYE 725 3R3 1.79 LWC B69 BB L + 56R 1.40 PYE 725 + 56R + 3R 1.55 RRI 823 56R + 68R 0.85 Thorn 1500 1.55 Thorn 1500 1.45	
MIXED PACKS	D.I.N. LINE SDCKETS	.22 1250V 0.60 .47 1000V 0.79	PYE 715 6 way 13.50 PYE 725 (UHF-VHF) 13.50 RRI 823 4 way 8.75	Thorn 3500 0.97 Thorn 8000 1.20 Thorn 8500 0.97	LINE OUTPUT TRANSFORMERS
Mixed Dust Cores 0.70 Transistor Mount Kit 0.70 10 yds Assorted Wire 0.50 100 Capacitors 1.00 300 Carbon Res 1.00 100 2½ Watt Wirebounds 2.00	2 Pin 0.11 3 Pin 0.22 5 Pin 180° 0.22 5 Pin 240° 0.22 6 Pin 0.23 7 Pin 0.23	8KV DISCS 180PF, 210PF, 270PF, 330PF, 500PF 0.30 POLYESTER 250V .01MF .0.06 .022MF .033MF .0.06 .047MF .0.06 .068MF .0.06 .1MF .0.07	RRI 823 6 way 9.50 RRI 720 6 way 9.50 RRI 718 6 way 9.50 Thorn 3500 6 way 2.75 Thorn 8500 6 way 2.75 Thorn 9000 6 way 2.75 Thorn 1615 4 way 8.70 Telpro 4 way 8.50	Thorn 8800 0.97 Thorn 9800 0.90 GEC 2110 0.85 CONVERGENCE	Autovox 90° 9.75 Autovox 110° 9.75 Decca 1700 Mono 9.80 Decca 1830 9.80 Decca 2230 8.30 GEC 2110 9.50
REGUN C.R.T.s (2 year warranty)	SOCKETS 0.10 2 Pin Switched 0.12 2 Pin Unswitched 0.12 3 Pin 180° 0.22	.22MF 0.08 .33MF 0.08 .47MF 0.13 .68MF 0.13 1MF 0.16 MYLAR FILM 100V	FUSES	5R 7R 10R 12R 15R 20R 50R 100R 200R 500R 0.38 G8 Metric 10R 15R 20R 0.50 Thorn 50R 200R 0.50	Grundig 5010 11.50
A44-271X 32.00 A47-342X 32.00	5 Pin 180° 0.22 5 Pin 240° 0.23 6 Pin 0.23	.001MF 0.06 .0022MF 0.06 .0047MF 0.07 .01MF 0.07 .022MF 0.07 .033MF 0.08	20mm A/S (10 Pack) 100mA, 160mA, 250mA 1.50		ITT CVC20
A47-343X 32.00 A49-192X 32.00 A51-110X 32.00 A56-120X 32.00 A56-140X 33.00 A56-500X 45.00 A66-120X 37.00 A66-140X 38.00 A67-120X 38.00	7 Pin 0.25 D.I.M. PCB SOCKET\$ 2 Pin Unswitched 0.25 5 Pin 180° 0.24 FM Plug 0.20 FM Socket 0.19	0.08 .068MF 0.09 .1MF 0.09 .22MF 0.13 .47MF 0.22 DISC CERAMIC 50V .01MF, .022MF, .047MF, .1MF 0.04 S CORRECTION	315mA 1.20 500mA, 630mA, 800mA 0.95 1A, 1.25A, 1.6A, 2A 0.95 2.5A, 3.15A, 4A, 6.3A 0.95 20mm 0/B (10 Pack) 160mA, 250mA, 315mA, 500mA, 630mA, 800mA, 1A, 1.6A, 2A, 3.15A 0.45 1½" A/S (10 Pack)	P134P 0.35 PT37P 0.85 PTH451A 0.75 VA1026 0.50 VA104 0.60 GEC Dual 1.60 G11Transient VDR 0.42	Korting 110° 12.50 Philips 210 9.90 Philips GB 8.90 Philips G9 8.50
A50-120WR 14.00 A61-120WR 15.00 Carriage £8.00 per tube +	AM Plug 0.20 AM Socket 0.19	.91MF G11 0.55	250mA, 500mA, 630mA 1.50 800mA, 1A, 1.25A, 2A 1.50 2.5A, 3A, 5A 2.30	VALVES	Philips 570 9.50 PYE 691 P.C. 13.00
AERIAL ISOLATORS	BATTERY HOLDERS HP7 2 per side, end to end 0.28	10MF 0.08 22MF 0.08 47MF 0.09 100MF 0.09 220MF 0.15 470MF 0.22 1000MF 0.33 2200MF 0.50	1½" O/B (10 Pack) 250mA, 1A, 1.5A 2A, 3A, 5A Mains Fuse (10 Pack)	DY86 0.75 DY802 0.75	PYE 731 8.95 PYE 169 10.75 RRI 640/793 11.75
40mm×40mm with 500mm Lead 0.60 67mm×65mm with 430mm Lead 0.60 Philips Plestic Moulded	HP7 2 per side, side by side 0.28 HP11 4 end to end 0.37 HP11 2 rows single sided 0.37 PP9 Press Stud 0.10	ELECTROLYTIC 40V 470MF 0.30 2200MF 0.70 ELECTROLYTIC 63V 1MF 0.08 2.2MF 0.08	2A, 3A, 5A, 13A 0.90 LOUDSPEAKERS	PCF802 0.95 PCL82 0.85 PCL84 0.85 PCL85 0.95 PCL86 0.95 PFL200 1.20	RRI 823 11.90 RRI T20 12.90 SABA 12.50 Skantic 12.50 Thorn 1500 20" 7.00
Type for KT3 Chassis 0.80	PP3 Press Stud 0.10	4.7MF 0.08 10MF 0.08 22MF 0.11 47MF 0.12 100MF 0.19 220MF 0.30	8 × 5 16 ohm 2.98 6 × 4 16 ohm 2.60 6 × 4 25 ohm 4.30	PL504 1.60 PL508 2.30	Thorn 1591 10.50 Thorn 1615 10.00
VIDEO HEADS	T20 CRT Base 1.35	470MF 0.42 1000MF 0.65 ELECTROLYTIC 100V	8 × 3 70 ohm 3.40 5 × 3 50 ohm 3.00 7 × 3½ 16 ohm 3.00	PY800 0.89 PY500A 2.30	Thorn 9000 10.90
3HSS Ferg-JVC-Akai 34.00 4HSS Nat Pan 34.00 PS3B Sony-NEC- Toshiba 39.00	Toshiba CRT Base 1.40	0.47MF 0.10 1MF 0.10 2.2MF 0.10 4.7MF 0.10 10MF 0.12 22MF 0.16 47MF 0.17 100MF 0.26 220MF 0.45 330MF 0.55	5½ × 3 80 ohm 2.90 Thorn 1590 large 4.00	PLEASE ADD 6	55 PENCE POST/ UR ORDER TOTAL
BOOKS	TRIM TOOLS	ELECTROLYTIC 250V		AND THEN 15%	VAT. GOODS ARE
A-Z Equivalent Book (Two Parts) 7.50 NB: Zero VAT on Books	Twin Bladed Bronze- Phosphor 0.25 Long Plastic, Hex at one end 0.11	10MF 0.28 22MF 0.31 ELECTROLYTIC 450V	1043/05 7.95 1043/06 7.95 U321 7.25 U322 7.25 G8 11.75	SHOULD BE RE	BY RETURN AND CEIVED WITHIN 4 NG DAYS.

					_																		
AA117	0.090	BC157	0.055	BD222	0.310	BU108	1.000	0C72	0.500	TIP29C	0.250	3N.128	0.550	2SA473	0.370	28 pin	0.200	PCL82	0.630	LM723	0.320	LED 5mm	
AA119	0.090	BC159	0.055	BD225	0.310	BU110	1.100	OC200	1,800	TIP30	0.160	3N.143	0.650	2SB54	0.250	40 pin	0.250	PCL84	0.500	LM741 D	ii 0.150	YELLOW	0.100
AAY32	0.090	BC182	0.060	B0232	0.310	BU111	1,400	OCP71	1.000	TIP31A	0.240	101.004		2SB77	0.320			PCL85	0.550	LM741		LED 5mm	
AC107	0.280	BC182L	0.060	BD237	0.210	BU126	0.700	ORP12	1.000	TIP32	0.240	IN.914	0.020	2SB337	1.200	VALVES		PCL86	0.550	Met	0.450	GREEN	0.100
AC126	0.170	BC183	0.060	BD238	0.240	BU204	0.750	ORP60	1.000	TIP32A	0.240	IN.4001	0.040				0.000					GNEEN	0.100
AC127	0.150	BC183L	0.060	BD433	0.280	BU205	0.700	ORP61	1.000	TIP33	0.500	IN.4002	0.040	2SB405	0.220	DY87	0.530	PCL805	0.550	LM3900	0.250		1
AC128	0.150	BC184	0.060	BD437	0.280	BU208	0.750	R2008B	0.800	TIP34	0.500	IN.4003	0.040	2SC460	0.210	DY802	0.450	PFL200	0.850	NE555	0.150	BRIDGE	- 1
AC128K	0.230	BC184L	0.060	BD535	0.380	BU206A	0.800	R2010B	0.800	TIP41A	0.220	IN.4004	0.040	2SC495	0.600	ECC82	0.400	PL36	0.800	NE556	0.400	RECTIFIE	RS
AC141K	0.230	BC212	0.060	BD536	0.380	BU208D	1,200	RZUIUD	0,000	TIP41C	0.250	IN.4005	0.040	2SC733	0.400	ECC83	0.430	PL504	0.950	BYX55/		1A/50V	0.180
AC142K	0.220	BC212L	0.060	BD537	0.400	B U326	0.850	SAS560	1.100	TIP42A	0.220	IN.4006	0.040	2SC1161	1.100	ECC84	0.400	PL508	1.900	350	0.300	1A/ 100V	0.180
AC153K	0.230	BC213	0.060	BD538	0.400	BU406	0.850	SAS570	1,100	TIP42C	0.250	IN.4007	0.050			ECC85	0,400	PY81			0.000		
AC176	0.180	BC213L	0.060	BDX32	1.000	BU407	0.750	SN76003N	11,400	TIP47	0.400	IN.4148	0.020						0.700	BYX55/		1A/200V	0.190
AC176K	0.200	BC214	0.060	BDX65	0.800	BU408	1.000	SN76013N	1.400	TIP48	0.400	IN.5400	0.090	2SC1279	0.240	ECH81	0.490	PY88	0.480	600	0.300	1A/400V	0.210
AC187	0.150	BC214L	0.060	BF180	0.160	BU500	1,100	SN76023N	1.400	TIP49	0.400	IN,5401	0.100	2SC1306	1.000	ECH84	0.520	PY500A	1.600	BYX55/		1A/600V	0.230
AC187K	0.200	BC237	0.070	BF181	0.180	BU526	0.800	SN76033N		TIP110	0.470	IN.5402	0.100	2SC1307	1.000	ECL80	0.570			600	0.300	1A/800V	0.280
AC188	0,170	B C238	0.070	BF183	0.200	BY126	0.060	SN76110N	0.700	TIP112	0.540	IN.5403	0.110	2SC1520	0.250	ECL82	0.590			BYX55/		2A/100V	0.350
AC188K	0.230	BC300	0.160	BF184	0.200	BY127	0.080	SN76115	0.700	TIP115	0.450	IN.5404	0.110	2SC1969	1,300	ECL84	0.570	ZENERS		800	0.320	2A/200V	0.360
ACY18	0.480	BC301	0.180	BF185	0.200	BY133	0.080		0.900	TIP117	0.560	IN.5405	0.120 0.130	2SC2029	1,200	ECL85	0.570	400MV		BYX70	U.DEO	2A/400V	0.420
ACY19	0.480	BC302	0.180	BF194	0.050	BY164	0.220	SN76227	0.800	TIP120	0.430	IN.5406 IN.5407	0.130		1.200	ECL86	0.570	BZY88 R	lange		0.000	2A/600V	0.540
AD142	0.600	BC303	0.180	BF195	0.050	BY176	0.850	TOOOGO		TIP121	0.460							2V7 to 3	9V0.060	500	0.290		
AD149	0.450	BC327 BC382	0.060	BF196	0.060	BY179	0.350	T2800D	0.520	TIP122	0.470	IN.5408	0,130	2SC2122A		EF80	0,310	1.3W Ze	Dare	BYX70/		2A/800V	0.580
AD161 AD162	0.220 0.220	BC337	0.060	BF199 BF200	0.060 0.160	BY182 BY184	0.320 0.320	TAG06-60 TAG521-	0.420	TIP125	0,470	VOLTAGE		2SC2952	0.270	EF85	0.340	BZX61 F		500	0.310	3A/ 200V	0.660
AF124	0.250	BC328	0.060	BF257	0.180	BY187	0.320		0.720	TIP126	0.560	REGULAT		2\$D234	0.370	EF89	0.430	2V7 to 3		BYX70/		3A/400V	0.680
AF125	0.250	BC557	0.060	BF258	0.180	BY196	0.200	200 TAC4442		TIP127 TIP2955	0.560	7805	0.350	2SK135	4.000	EF183	0.450	24/ (0.3	970.120	800	0.360	3A/600V	0.700
AF125	0.250	BCY32	1.500	BF259	0.180	BY206	0.110	TAG4443 TAG4444	0.760 0.760	TIP2955	0.380	7812	0.350	MB3712	1.500	EF184	0.530			BYX71/		6A/ 200V	1.000
AF127	0.250	BCY33	1.500	BF336	0.180	BY207	0.110	TAA550	0.760	TIP3054	0.340	7815	0.350	TA7205	1.500	EL34	1.900	MEMOR	IFS	600	0.800	6A/400V	0,800
AF139	0.220	BCY34	1.500	BF337	0.200	BY223	0.720	TBA120S	0.150	TIS61	0.150	7818	0.350	UPC575	1.000	EY86		2114	0.750	000	0,500		
AF239	0.220	BCY42	0.200	BF338	0.200	BYX10	0.150	TBA395	0.600	TI\$90	0,150	7824	0.350	UP C5/5	1.000		0,310			ľ		25A/ 100V	1,500
AL112	0.700	BCY56	0.160	BF362	0.300		0.130	TBA396	0.600	TIS91	0.180	1				EY87	0.310	2716	2,200	LED			\neg
AL113	0.800	BCY70	0.160	BF422	0.210	CA270	0.400	TBA520	0.750	11001	0,100	7905	0.350	ICS	- 1	PC97	1.000	2532	2.900	LED 3mm	.	ELECTROL	LYTIC
ASZ15	1.000	BCY71	0.160	BF458	0.190	CA3086	0.250	TBA530	0.750			7912	0.400	SOCKETS	- 1	PCC85	0.420	2732	2.900	RED	0.050	4700UF-16	v I
ASZ17	1.000	BCY72	0.160	BF459	0.190	CA3089	1.500	TBA540	0.750	2N.2904	0.200	7915	0.400	8 pin	0.060	PCF80	0.580	2764	5.000			CAN	0.200
AU106	1.000	BD115	0.250	BFX29	0.200	CA3240	0.900	TBA560	0.700	2N.2905	0.200	7918	0.400	14 pin	0.080	P CF200	1.350	4116	0.750	LED 3mm			
AU110	1.100	BD124P	0.500	BFX84	0.200	C106D	0.230	TBA800	0.350	2N.2906	0.180	7924	0.400	16 pin	0.090	P CF801	1.100	6116	3,000	YELLOW.		TRIPLERS	
AY102	1,800	BD124	1.100	BFX85	0.200	MC1327	0.700	TBA810S	0.600	2N.2907	0.180	701.00	0.000	18 pin	0.120	P CF802	0.570	LM324	0.300	LED 3mm	1		1
AY106	1,800	BD128	0.350	BFX87	0.150	MJ2500	1.000	TBA820	0.750	2N.2926	0.080	78L05 78L12	0.280 0.280					LM380	0.600	GREEN	0.100	LP1195	
		BD131	0.250	BFX88	0.150	MJ2501	1.100	TBA920	0.800	2N.3019	0.280	78L12	0,290	20 pin	0.140	PCF806	1.150			l		(4000Ser)	2.250
BA145	0.100	BD132	0.250	BFY50	0.140	MJ2955	0.550	TBA950	0.800	2N.3053	0.180	74L18	0.280	22 pin	0.150	PCH200	1.000	LM381	1.000	LED 5mm			
BA148	0.100	BD135	0.200	BFY51	0.140	MJ3000	1.150	TBA990	0.800	2N.3054	0.350	74L18	0.280	24 pin	0.180	PCL81	0.540	LM709 [0.300 liC	RED	0.050		
BA154	0.060	BD136	0.200	BFY52	0.140	MJ3001	1.150	TCA800	0.800	2N.3055	0,320	74024	0.200							ľ			
BA157	0.120	BD137	0.200	BFY56	0.250	MJE28A	0.300	TCA940	0.850	2N.3055H	0.380	LM309K	1.000	Di		-1 40 · E	00.0				<u> </u>		
BB101	0.130	BD138	0.200	BYF57	0.250	MJE30A	0.300	TDA1170	0.900	2N3440	0.580	LM317K	2.200	Pleas	se ad	d 40p. F					. Colle	eges, etc	:
BB103	0,160	BD139	0.200	BFY84	0.250	MJE340	0.250		0.600	2N.3442	0.850	LM317T	1,800				01	ders ac	cepted	1.			- 1
BB105B	0.180	BD140	0.200	BR100	0.140		0.000		0.800	2N.3771	0.850	LM323K	4.200			Ouoteti				Quant	tioe		- 1
BB205B	0.240	BD144	0.900	BSX19	0.150	MJE520	0.300		1.500	2N.3772	0.900	LM723	0.320										- 1
BC107	0.070	BD150	0.300	BSX20	0.150	MJE2955k			1.400	2N.3773	1.000	78HGKC	5.700							deliven			- 1
BC108	0.070	BD157	0.380	BSX21	0.180				1.400	2N.4031	0.250	78HQ5KC	5.200	All br	rand-r	new Col	mpon	ents. Al	i vaive	es are n	ew ar	nd boxed	d. I
BC109	0.070	BD158	0.380	BSX26	0.160	0A47	0.080		0.800	2N.4036	0.250	78GU1C	1.900				<u> </u>						
BC115	0.100	BD166	0.300	BSX29	0.190	0A90	0.040		0.800	2N.4037	0.250	79GU1C	2.150			0.0		100.4	-				- !
BC118	0.110	BD175	0.300	BZX76	0.100	A091	0.040		0.750	2N.4443	0.760	79HGKC	6.700			- (GH	$\Delta \Gamma$	ACIL	IA	LT).		
BC140 BC141	0.190 0.190	BD177 BD179	0.300	BT106	0.900	0A200	0.070		0.700	2N.4444	0.760	IADANITA).F			-					- •		
BC142	0.190		0.450	BT109 BT116	0.900	0A202	0.070		0.700	2N.5061	0.200	JAPANES			9	THE B	ROAL	YAWC	PRE!	STON	ROAL) .	
BC143	0.190	BD181 BD201	0.330	BT119	1.000	0C28 0C29	1.000 0.800		0.800	2N.6294 2N.5296	0.300	TRANSIS 2SA73	0.300										
BC147	0.055	BD202	0.380	BT120	1,000	0C35	1,000		0.700	2N.6106	0.400	2SA73 2SA104	0.320							, ENGL			
BC148	0.065	BD203	0.420	BU104	1,000	0C45	0.500	TIP29	0.750	2N.6100	0.400	2SA104 2SA198	0.220		Te	lephor	ne: 0	1-904 2	2093 8	ኔ 904-1	115/	6.	
BC149	0.055	8D204	0.420	BU105	0.800	0C71	0.300	TIP28A	0.220	2N.8109	0.400	2\$A203	0.300										
1 -5.70	0.000		3,723	_0.00			3.500	111 600	J.22.V	21410100	3,700	-0	3200			1016	X No	. 932	505	Sunmit)		

GRANDATA LTD.

Manchester's No. Over 2,000 TVs in stock Special Offer on Working Colour TV's

All sets are Servi	ced with repolished	Some Examples of	UNTESTED TVS
cabinets ro	eady for sale	availabl	е
Philips G8 550s	22/26 £45	Thorn	10 for £125
Philips 18"	£40	Philips	6 for £90
Philips G8 520s	22/26 £35	Bush	6 for £80
GEC S/State	from £35	GEC	6 for £60
Thorn 17" 8000	£30	Decca	6 for £60
Decca 30	18/20/22/26 £30	Mono TVs avail. s/s	£4 each
Japanese	from £30	New TV trolly stands	
Many other mal	kes available from	All sizes	£4.95
f	25	All Prices subject to \	√.A.T.
Discount	on quantity	•	

Ex Equipment Panels & Tubes Available Deliveries may be arranged to the North and Scotland. Ring for quote. Callers welcome.

419 Barlowmoor Road, Chorlton, Manchester 21 2ER. Tel: 061 861 8501

ALL SETS HAVE BEEN ENGINEERED AND ARE IN PERFECT WORKING ORDER

PRICES AVAILABLE ON THESE SETS NOW!!!

PYE CHELSEA's
PYE 721s, 731s, 725s
PHILIPS 520s, 550s
BUSH T20, T22, T24s
(Remote Control)

THORN 8000 & 8800s
THORN 9000, 9200, 9600
(Remote Control)

HITACHI & NAT/PANASONIC

Minimum 5 Sets

Big reductions for export orders over 100 sets

COLOUR TELEVISION & MUSIC CENTRE

35 Stafford Road, Weston Super Mare Opening hours: 9-6 Mon-Sat, 9-1 Sundays

(W-S-M 413537)

Avon

(W-S-M 413537)

275

(Note new address)

(15 minutes past Bristol Southward on M5)

TELEVISION MARCH 1984

TOP TWENTY T.V. SPAI	RES
STOCK NO.	
001 Philips G8 Loptx (Genuine Philips)	7.50
002 Decca 30 series Loptx (Genuine Decca)	7.00
003 Decca 100 series Loptx (Genuine Decca)	
004 ITT CVC 25/30/32 Loptx (Genuine ITT)	7.00
371 Pye 713/731 Vision Gain Module	6.50
(replaces expensive 212-27327) 270 10 × BU208A	8.50
050 ITT CVC 5/9 EHT Tray	3.00
051 Decca 1730/1830 Doubler	2.00
053 GEC 2040 Hybrid EHT Tray	3.00
054 Thorn 1500 (5 Stick) EHT Tray	3.50
056 Thorn 1400 EHT Tray	2.00
057 Philips G9 EHT Tray	3.50
058 ITT Universal EHT Tray	5.00
011 Thorn 1690/91 Loptx	7.00
012 Thorn 1615 Loptx	6.50
085 470 MFD 250V Philips G11 335 50 × BY127 Diodes	1.50 3.00
270 10 × BU326	10.00
280 25 × 2N3055	7.50

All components are A1 quality from prime manufacturers, and are dispatched by post same day as order received together with any refund due. All goods should be delivered within 4 working days.

Please add 15% VAT and 90p P & P

BEOTICIES	TRAVO
RECTIFIER	
050 ITT CVC 5	
051 Decca 1730	
052 Decca 80 S	eries 4.50
053 GEC 2040 H	lvbrid 3.00
054 Thorn	1500 (5
Stick)	3.00
055 Thorn	1 8000
Doubler	2.00
056 Thorn 1400	2.00
057 Philips G9	3.50
058 ITT Univer	
059 5 ×	
PTV's	1.00
060 3 × 1	
REC X	
	1.00
061 ITT CVC 45	
062 TVK52 Cont	inental 2.50
063 RRI Z179	3.00
064 Pye 691 /69	7 3.50
065 Pye CT200	4 Lead 3.50

	068 Pye CT200 5 Leed 4.50 067 Korting Hybrid 5.00 068 Grundig3010/1500 3.00
	CAPACITORS 080 220/400 CVC 32- T20 1.20 081 200 + 300 Pye 691/ 697 2.00 082 600/300 Philips G8 1.90 083 175+100+100 Thorn 3500 085 470/250 Philips G1 1.90 086 400+400 Decca 30 2.50 087 200+200+75+25 1TT5/9 1.50 087 200+200+75+25 1TT5/9 1.50 088 400/400V Thorn 9000 1.50 089 10 × 220MF 16V Elect 0.50
	094 5 × 4·7MF/100V C514 T3500 1.25
_	096 5 × 91NF Philips
	G11 2.25 097 10 × 1/2000V 2.00 098 5 × 1/250 Suppression ITT 2.75

111 Pye 715 6 Way 11.9! 113 Philips G8 (Sloping) 12.98 114 Thorn 9000 6 Way2.50 115 Thorn 1615 4 Way 5.7!	7
(Sloping) 12.98 114 Thorn 9000 6 Way 2.50	5
114 Thorn 9000 6 Way 2.50	3
114 Thorn 9000 6 Way 2.50	9
)
116 Decca 6 Way 6.9!	
117 Decca 4 Way 6.56	
118 GEC 2110 6 Way 7,9!	
119 GEC 2136/7 Tapered (6	
(Vav) 7.95	
120 ITT CVC5 9.2	
121 ITT CVC8 11.49	
122 ITT 6 Way with	
V.C.R. 7.99	

PUSH BUTTON UNITS

123 R.R.I. A823 etc. 4 Way 7.95 124 Hitechi 4 Way 7.95 125 R.R.I. T20 6 Way 8.95	270 10 × BU208A 271 10 × BU208 272 10 × BU328 1 273 5 × BU205 280 25 × 2N3055 (Te) 281 10 × 2N2905

	}
INTEGRATED CIRC 140 5 × TBA440	UITS 3.00
141 5 × TBA120AS	1.80
142 5 × TBA540	4.00
143 5 × TBA540Q	4.00
145 5 × TBA560	3.50
146 5 × TBA810S	3.00
147 5 × TBA9200	4.50
148 5 × TBA990Q	3,25
149 5 × TBA520Q	4.00
150 5 × TBA530Q	4.25
151 5 × TRA950	4.50

THE O A TOMOLOG	7.40
148 5 × TBA990Q	3.25
149 5 × TBA520Q	4.00
150 5 × TBA530Q	4.25
151 5 × TBA950	4.50
155 5 × MC1327Q	
160 TDA1170 161 TDA1190	1.35
161 TDA1190	1.90
162 TDA1006A	1.45
164 TDA 1035	1.83
165 TDA1044	2.23
166 TDA1190	1.90
167 TDA1412	0.90
172 TDA2002	1.80
173 TDA2020	2.50
	2.15
178 TDA2523	2.35
179 TDA2532	2.40
180 TDA2540	1.65
181 TDA2541	2.67
182 TDA2560	3.28
183 TDA2571	2.15
184 TDA2591	0.98
185 TDA2593	2.23
190 TDA2600	4.00
191 TDA2611	1.24
192 TDA2640	2.35
210 ETTR6016	2.28
211 ETT0016	2.28
212 BTT6018	2.28

	167 TDA1412	0
Ì	172 TDA2002	1
	173 TDA2020	2
	174 TDA2030	2
	178 TDA2523	2
ļ	179 TDA2532	2
1	180 TDA2540	1
	181 TDA2541	2
l	182 TDA2560	3
ı	183 TDA2571	2
	184 TDA2591	0
ļ	185 TDA2593	2
i	190 TDA2600	4
Ì	191 TDA2611	- 1
	192 TDA2640	2
	210 ETTR6016	2
١	211 ETT6016	2
	212 BTT6018	2

			DIODES
235 5	$0 \times B$	C213L	2.50
250	10	×	BD124
Meta	d)		9.00

٦	270 10 × BU208A	8,50
- 1	271 10 × BU208	7.50
	272 10 × BU326	
	273 5 × BU205	
	280 25 × 2N3055	Texas)
		7.50
4	281 10 × 2N2905	
1	(Equiv. BC161/303)	0.50
ı	335 50 V RV127	3.00

	SPECIFIC SPARES
	350 Thom 1590/1
1	41×21 2.00
	357 Thom 1590/1
1	5×21 2.00
	352 Thorn 1600
	Dropper 0.50
	358 5 × Thorn 3500 200R
	Conv. Pot. 1.00
ı	359 5 × Thom 3500 50R
1	Conv. Pot. 1.00
	370 Pye 731 Thick Film 1.50 371 Pye 713/731 Vis. Gain
	Module 6.50
	372 Pve 731 3R3 50W
ı	Metal clad 1.29
ı	378 Grundig 5010/6010
ı	Video Module 4.00
1	384 5 × Philips G8/10R
1	Conv. Pot. 2.40
1	385 5 × Philips G8 2.40
ı	386 5 × Philips G8 2k2 Lin.
1	Bright. 2.50
1	387 5 × Philips G8 10k
	Log. Color 2.50
1	388 5 × Philips G8 47k
1	
	389 Philips G8 Plastic Mains Sw. 0.75
ł	390 Philips G8 Metal
1	Mains Sw. 1.23
1	391 Philips G8 Line Ed/
4	Stor. Coil 2.25
	403 5 RRI T20 C.R.T.
1	Base 4.35
	435 10 × Decca 30 10R
I	Fusible 0.50
-	

437 Decca 30	47k
Vol. +Switch	1.25
453 5 x 5R Universal (Conv.
Pot.	1.00
454 5 ×20R Universal (Conv.
Pot.	1.00
455 5×100R Univ	ersel
Conv. Pot.	1.00
456 5×470R Univ	
Conv. Pot.	1,00
457 10 ×100k Tuner Pr	eset
TCE etc.	3.00
458 10 ×100k Tuner Pr	eset
Philips G8	3.00
459 ELC1043/05 Rep	
Tuner	6.00
460 ELC1043/06 Rep	aired
Tuner	6.00
461 U321 New Tuner	7,95
462 U322 New Tuner	7.95
469 Cut Out Metal 2100	1.00
470 5×GEC2100 3	
Thermistor	1.00
479 5×Gen. Purpose	
tary Switch	3.60
460 5 ×Gen. Purpose	
Push SW.	3.75
	GEC
etc.	2.25
482 5 × Universal A	
Skt.	5.50
	Совх
Plug	1.70
484 Focus Unit	T20
Туре	1.25
485 Focus Unit Thorn	8500
Туре	1.25

436 5×Decca 30 3R9 Modulohm 1,75

NEW PRODUCTS			
023	Thor	n 1	590/91
LOP1	ľΧ		8.50
024	Thorn	1500	15K\
LOP1	TX .		4.00
220 5	L901B Ir	nt. Circu	uit 4.00
230	10	×	AC128
Trans	sistor		1.50
290	10	×	BT108
Thyri	stor		9.00
291 5	$5 \times BT1$	09	4.50
293 5	5 × BT1	20	4.50
496	TX10 (Chass	Focus
Unit			7.00
089 1	0 × Ar	nti Trac	k EHT
Cap			2.00

V. SPA

MUXTON HOUSE, MUXTON, TELFORD, SALOP, REG. OFFICE ONLY. CALLERS STRICTLY BY APPOINTMENT. PLEASE QUOTE STOCK NO.

FREEWAY COMPONENTS

TEL: 0934 - 419147

TRANSISTORS	BC32716
AC11730	BC33710
AC11730	
AC12730	BC33810
AC12830	BC47725
AC14126	BC47930
AC14227	BD12460
	BD13132
AC18128	
AC18730	BD139
AC18828	BD140
AD14096	BD144 1.40
AD14296	BD160 1.45
AD14390	BD20185
AD140	
AD14988	
AD16145	BD235
AD162	BD243
AF11740	BD244
AF12450	BD37960
AF12640	BD38060
AF13948	BD442
AL102 1,80	BD535
AL113 1.80	BD536 .50
AU106 2.00	BD53750
AU110 2.00	BD53850
AU1132.00	BDX321.60
BC10812	BF17832
BC10912	BF179
BC14035	BF19611
BC14135	BF19712
BC14225	BF19817
BC14325	BF19915
BC14710	BF25828
BC14810	BF25928
BC14910	BF337
BC15710	BF338
BC15810	BF458
BC15910	BF459
BC16130	BFY5027
BC17110	BU108 1.78
BC17210	BU126 1.75
	BU204 1.55
BC17818	BU204 1.55
BC17918	BU205 1.40
BC18210	BU206 1.65
BC18720	BU208A 1.80
BC21210	(Pack of 10) 12.00
BC23710	BU326A 1.40
	BU407D 2.49
BC303 30	BU806D 2.00

	_
600500220005	BU807 2.00 MJE340 50 R2068 1.80 R2010B 1.80 R2540 2.40 TIP29C 46 TIP30C 45 TIP31C 50 TIP31C 50 TIP41C 50 TIP42C 50
5	INTEGRATED
Ō	CIRCUITS
2	ETT6016 1.80
Ö	ETTR6016 1.80
0	HA1156W 1.25 HA1166 3.50
Ö	HA1166 3.50 HA1366W 1.70
ŏ	LM1303P 4.95
0	MC1327P 1.20
Ö	MC1330P 1.00
0	MC1351P 1.35 MC1358P 1.35
Ö	MC1358P 1.35 NE545B 2.90
ŏ	NE55545
0	SAA5000 3.50
2	SAA5010 4.80
2	SAS560S 1.96 SAS570S 1.96
2	SAS570S 1.96 SL901B 6.20
7	SL901B 6.20 SL917/918B 4.95
5	SN78023D 1.99
B	SN76033N 2.45
8	SN76110N95
5	SN76131N 1.40 SN76226N 1.65
2	SN76227N 1.10
6	SN76510N90
7	SN76533N 1.80
5	SN76660N 60 SN76666N 75
2	SN76666N75 TA7176P 1.00
Ś	TA7205P 1.30
5	TA7217AP 1.80
5	TA7611AP 3.45
!	TAA350A 1.90
	TAA621AY1 3 E0
27588222578555	TAA550 .25 TAA621AX1 .3.50 TBA120A .95 TBA120AS .75
5	TBA120AS75
	· · · -

TBA120S75	LINE OUTPUT
TBA120T 1.10	TRANSFORMERS
TBA120U 1.10	Autovox 90°10.45
TBA395 1.75	Autovox 110° 10 45
TBA396 1.00	Baird 26" 90°11.20 Baird 26" 110°11.20
TBA48095	
TBA510 3.20	B&O 3100, 3300,
TBA520 1.30	3400 EHT 19.50
TBA530 1.45	B&O 3100, 3300,
TBA540 1.35	340011.50 B&O 3000, 3200
TBA550 1.50	B&U 3000, 3200
TBA560 1.50	EHT16.90 B&O 3500, 3600,
TBA570 1.40	4000, 5000,
TBA720A 2.60	6000, 5000,
TBA750 1.50	600011.25 Decca 30, 22309.75
TBA800 1.05	Decca 80 8.93
TBA810AS 1.35	Decca 100 9.38
TBA810S 1.35	Decca 1730,
	1630 10.43
TBA820 1.20	Decre 1700 9.75
TBA820M 1.95	l Dynatron 731 735
TBA920 1.70	737, 741 10.50 Dynatron TV 202/
TBA950 1.80	Dynatron TV 202/
TBA990 1.60	310.25 Ekco CT 262, 862,
TCA270Q 1.50	Ekco CT 262, 862,
TCA270SQ 1.30	226, 82710.50
TCA800 2.10	GEC Solid State 9.00
TCA940 1.80	Grundig 5010/UE, 6010 UE, 2222 .12.00
TDA1002 1.15	Grundig 501012.00
TDA1003A 1.50	Grundig 1500 15.00
TDA1004A 2.50	Grandia 5010
TDA1035T 3.50	Grundig 5010 EHT19.50
TDA1170S 2.70	Indesit 24" Mono 11.50
TDA141280	ITT CVC510.70
TDA2020 2.55	ITT CVC25, 30,
TDA2030H 2.95	32
TDA2190 3.50	ITT CVC20 9.00
TDA2522 2.00	ITT CVC45 9.00
TDA2523 4.30	Korting 90°11.20
TDA2530 2.20	Korting 110° 11.20
TDA2532 2.50	Luxor 222114.00
TDA254095	Luxor 26' 90° 11.20
TDA2541 2.50	Nordmende11.25
TDA2560 2.00	Philips G8 7.50
TDA2571A 2.50	Phillips K7021.75
TDA2581 1.50 TDA2590/91 2.50	Philips G9 8.80
TDA2590/91 2.50 TDA2593 2.50	Philips Mono 10.88
IDA2080 2.50	Philips 570 9.38

TDA2600 5.80

Baird 26" 90°11.20 Baird 26" 110°11.20
Baird 26" 110° 11.20
B&O 3100, 3300,
3400 EHT 19.50 B&O 3100, 3300,
3400 11 50
3400
FHT 16 90
EHT16.90 B&O 3500, 3600,
4000. 5000.
4000, 5000, 6000
Decca 30, 22309.75
Decca 80 8.93 Decca 100 9.38 Decca 1730,
Decca 100 9.38
Decca 1730,
1630 10.43
Decca 1700 9.75
Dynatron 731, 735,
1630
310.25
310.25 Ekco CT 262, 862,
226 827 10 50
226, 827 10.50 GEC Solid State 9.00
Grundia 5010/HF
Grundig 5010/UE, 6010 ÜE, 2222 .12.00 Grundig 501012.00 Grundig 150015.00
Grundia 501012.00
Grundia 1500 15.00
Grundia 5010
EHT
Indesit 24" Mono11.50
TT CVC510.70
ITT CVC25, 30,
ITT CVC20 9.00
ITT CVC45 9.00
Korting 90° 11.20
Korting 110° 11.20
Luxor 2221 14.00 Luxor 26' 90° 11.20
Nordmende11.25
Philips G8 7 50
Philips G8 7.50 Philips K70 21.75
Philips G9 8.80
Philips G9 8.80 Philips Mono 10.88
Philips 570 9.38
Phillips K912.25

Pye 691, 697 . 14.25 Pye 731 10.45 Pye 713	Decca 1730, 30, 80, 100, 6 way. 7.65 Decca 1730, 20, Mono 4 way. 6.60 Salora 5 way. 10.50 Luxor 6 way. 13.75 Skantic 6 way. 13.75
Rank T20A	TUNERS AEG 05 (1043/05)8.00 AEG 06 (1043/06)8.00 AEG 202 (U321) 8.00 AEG 204 (U322) 9.00 Mitsumi Rotary (Portables)8.00
TFK 711 & 711A 10.50 Thorn 1615 9.00 Thorn 1690 8.20 Thorn 1590/91.10.90 Thorn 8000A .10.15 Thorn 8000 .11.50 Thorn 8000 11.50 Thorn 8000 .11.00 Zanussi 26' .10.70	VALVES PCF80 1.05 PCF82 1.65 PCL82 1.10 PCL84 1.10 PCL86 1.05 PFL200 1.65 PL508 2.80 PL508 2.80 PL509 3.45
PRESS BUTTONS Pye 715, 207 Chelsea	PUSUS 3.45 PY500A 1.80 FUSES (Packs of 10) MAINS 2A, 3A, 5A, 13A 1.00

F YO 1 13. 201	
Chelsea 11.90	FUSES (Packs of 10)
Pye 713, 715 8,00	MAINS
Pye 691, 697 repair	2A, 3A, 5A, 13A 1.00
kit 6.30	20mm ANTI-SURGE
Philips G8 550	80mA, 100mA,
sloping15.50	160mA, 250mA,
Telpro 4 way 9.50	315mA, 400mA,
GEC 2110 BBC/	500mA, 630mA
ITA 8.50	600mA, 1A, 1.25A,
GEC 211213.00	1.6A, 2A, 2.5A,
GEC 2136/7 8.40	3.15A, 4A, 5A 1.40
Hitachi 190 Nat. Pan.	20mm QUICK-BLOW
4 way 7.90	100mA, 150mA,
ITT CVC8/9 11.90	250mA, 315mA,
ITT CVC510.50	400mA, 500mA,
ITT CVC20, 30,	630mA, 1A, 1.5A,
327.70	1.6A, 2A, 2.5A, 3A,
Rank T20A 8.90	4A, 5A 0.60

MULTI-SECTION ELECTROL	
Rank 823 800/300v	2.05
Rank 823 2500+2500/30v	1.30
Rank 823 300+300/300v	2.20
Rank T20 220/400v	1.50
PHG8/GEC 600/250v	1.80
PHG8/GEC 600/300v	2.20
PHG9 2200/63v	1.25
PHG11 470/250v	1.60
Pye 691 200+300/350v	2.40
Pye 691 1000+1000/40v	80
Pye 731 800/250v	2.10
GEC 2000 200+200+150+50/	
350v	2.50
GEC 2010 1000+2000/35v	95
Thorn 3500 1000/70v	1.00
PHG9/Pye 731 600/300v P.C.B	

LHI IKAY
ITT Universal 5.50
To fit most sets including: Decca, GEC.
ITT, Pye, Philips, Rank, Telpro, Saba.
Autovox, Bang & Olufsen, Grundig,
Doric, Skantic etc.

VIDEO HEADS
VHS (3HSS 5mm centre hole)32.45
VHS (4HSS 15mm centre hole)32.45
Reta (PS3B Sony Toshiha etc.) 41.75
Beta (PS3B Sony, Toshiba etc.)41.75 Any doubts which you need please ring
our sales office.
Our Sales Office.

SPECIAL OFFER

Thorn 9000 6-way switchbank 1.50 each. 2 for 2.50. Take one for 750 when you order other goods totalling 15.00 excl. VAT.

Add 60p carriage & 15% VAT and send cheque or P.O. to: FREEWAY COMPONENTS THE AIRPORT WESTON-SUPER-MARE **AVON BS24 8RA**

"Colour Televisions

FIRST COME! FIRST SERVED!

Not ex-rental . . .

All in excellent cabinet condition. Many working.

Largest selection of makes and models. Fresh stocks weekly

Available in singles or in quantity.

Many late models eg: G11, 9600, Decca 100 etc.

Clearance sale of old models:

Philips G8

£10.00

Bush A823

£10.00

Hybrid mixed

£5.00

Panels, Spares, Tubes etc. available.



RING US NOW!!!

COLOURTRADE

Tel: 021-359 0449 221, Bridge Street West, Newtown, Birmingham, B7.

PUBLICATIONS

INDEX TO THE TELEVISION MAGAZINE

MOST USEFUL TO THE T.V. / VIDEO SERVICE ENGINEER

In the form:-

(Chassis type/Model no. Page no. mnth./yr.) As advertised in Nov. 83 issue Jan. 74 to Jan. 84 (10 years) Prices:-

- 1. T.V.'s 1st Edition (Jan. 74 to Sept. 83) £4.65
- 2. T.V.'s 2nd Edition (Jan. 74 to Jan. 84) £6.65
- (Jan. 74 to Jan. 84) £5.65 3. VCR's
- 4. Chassis Guide

£1.50

Mr. M. Saiepour B.Sc., M.Sc., AMIEE 2 The Paddocks, Widmerpool Notts. NG12 5PY

BI-PAK SOLDER DESOLDER KIT

DESOLDER KIT
Kit comprises: ORDER NO. VP80
1 High Quality 25 watt General
Purpose Lightweight Soldering Iron
240v mains ind 316" (4.7mm) bit
1 Quality Desoldering Pump High
Suction with automatic ejection with automatic ejection with automatic ejection with submatic ejection for anti-corrosive casing and Teflon nozzle
1.5 metres of De-Soldering braid on plastic dispenser.

dispenser 2 yds (1.83m) Resin Cored Solder on Card 1 Heat Shunt tool tweezer Type

Total Retail Value over £12 00

OUR SPECIAL KIT PRICE £9.95

DIGITAL VOLT METER MODULE

3 × 7 segment displays Basic Circuit 0-2v± instructions provided to extend voltage & current ranges Operating voltage 9/12v. Typ. Power Con-sumption 50mA

Q/No. VP99 Once only price

SINGLE SIDED FIBREGLASS

Order	NoPieces	Size	Sq. Ins	
FB1	4		29,100	£1.50
FB2	3		3" 100	£1.50
FB3	4	13 × 3	3" 156	€2.00
	BLE SID	ED FIE	REGLA	SS
BOA	RD			
FB4	2	14 x	4" 110	£2.00

"BCSBB"

SEMICONDUCTOR BARGAIN BOX

This collection of Components & Semiconductors for the hobbytst is probably the most value packed selection ever offered, it consists of Resistors; carbon & wirewound of various values. Capacitors; All types sorts & sizes including electrolytics. Potentiometers; single, dual, slider & preset. Switches, Fuses, Heatsinks, Wire, P.C. Board, Plugs, Sockets, etc. PLUS a selection of Semiconductors for everyday use in popular Hobby Projects, these include: SCR's, Diodes, Rectifiers, Triecs & Bridges as well as a first class mix of Transistors & IC's.

In all we astimate the value of this BCSBB – in current retail catalogues to be over £25.

So help yourself to a great surprise and order a Box today for just £6,50 ONLY at BI-PAK. You can cell us on 0920 3182/3412 and order it with your Barclaycard or Access Card – 24hr. Answerphone Service NOW, Order No. V.P. 85.

TRIACS - PLASTIC

HIACS - PLASTIC 4 AMP - 400v - T0202 - TAG 136G 1 OFF 10 OFF 50 OFF 40p £3.75 £17.50 8 AMP - 400v - T0220 - TAG 425 60p £5.75 £27.50 650 NO

MINIATURE FM TRANSMITTER
Freq: 95–106MHz. Range: 1 mile
Size: 45 × 20mm Add: 9v batt.
Not licenced in U.K.
ideal for: 007–M15–FBI–CIA–KGB etc. ONLY

PROGRAMMABLE UNIJUNCTION TRANSISTOR

PUT case T0106 plastic MEU22 Similar to 2N6027/ 6028 PNPN Sificon Price: 1–9 10–49 50–99 100+

6028 PNPN Silicon Price: 1-9 10-49 50-99 Each 20p 18p 15p Normal Retail Price £0.35 each.

BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises
1 Expo Mini Drill 10,000RPM 12v DC incl 3
collets & 3 × Twist Bits
1 Sheet PCB Transfers 210mm × 1 Etch Resist Pen 1 Jlb pack FERRIC CHLORIDE

crystals
3 sheets copper clad board
2 sheets Fibreglass copper clad board Full instructions for making your own PCB boards

Retail Value over £15.00

OUR BI-PAK SPECIAL KIT PRICE £9.95 ORDER NO. VP81

Silicon NPN'L' Type Transistors
T0-92 Plastic Centre Collector Like
BC182L - 183L - 184L
VCB0 45 VCE0 30 ICZ00mA H/e 100-400
All perfect devices – uncoded. OROER AS
SX183L 100 off

£1.50 £2.50 £10.00 Silicon General Purpose NPN Transistors
T0-18 Case. Lock fit leads – coded CV7644
similar to BC147 – BC107 – ZT89 ALL NEW VCE
70v ICS0mA. ORDER AS CV7644
50 off 100 off 500 off 1000 off
PRICE £2.00 £3.80 £17.50 £30.00

Silicon General Purpose PNP Transistors
T0-5 Case. Lock fit leads coded CV9507 similar
2N2905A to BPX30 VC60 IC600mA Min HFE 50.
ALL NEW. ORDER AS CV9507.
50 off 100 off 500 off 1000 off
PRICE £2.50 £4.00 £19.00 £26.00

OPTO 7-Segment Displays Brand new 1st Quality LITRONIX DL 707R 14-pin

Red 0.3" Common Anode Display 0-9 with right hand decimal point TTL compatible 5v DC Supply. Data supplied

5 pieces £3 10 pieces £5 S 50 pieces £20 100 pieces £35 1,000 pieces £300 (60p each) (50p each) (40p each) (35p each) (30p each) PACKS

THE MORE YOU BUY -THE LESS YOU PAY

SEMICONDUCTORS FROM AROUND THE WORLD

100 A collection of Transistors, Diodes, Rectifiers &

Bridges SCR's, Triacs, I.C.'s & Opto's all of which are current every-day useable devices.

Guaranteed Value Over £10 Normal Retail Price. Data etc in every pack. Order No. VP56

Our Price £4.00



OUR GREAT NEW 1984 CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices. These are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality componens at competitive prices and THAT WE STILL DO.

We hold vast stocks "n stock" for fast immediate delivery, all items in our Catalogue are available ex stock. The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the

To receive your NEW 1984 BI-PAK Catalogue, send 75p PLUS 25p p&p to:-



st add VAT at 19% to your

HUSSAIN CENTRAL TV SALE

No. 1 in Midlands

Special Clearance to trade

G8, Philips from £8, Pye 205 from £5, GEC Hybrid from £5, Decca 1800 Series, G9, G11, Pye 223, Pye Chelsea, ITT CVC5, CVC9, CVC25 and 30, Thorn 8500, 9000, GEC, National, Hitachi, Mitsubishi, Toshiba, and black and white, 75p. Most makes and sizes available. Buy T.V., tubes and spares free.

Ring us today 021-622 1023 or 021-622 1517 48/52 Pershore St., Birmingham City Centre.

TELEVISION TUBE SHOP LTD

BRAND NEW TUBES AT CUT PRICES

A31-19W/20W19.95		
A31-120W/300W17.95		
A31-410/510W 17.95	CT507 equiv	21.95
A34-100W/510W18.50	310DGB4/DMB4	23.00
A34-514W24.25	310EUB4	19.95
A38-160W/170W17.50	210011044	18.50
A44-120W/R25.00	210EVD4	18.75
•	310FYR4	
A50-120W/R19.00	310GNB4A	
A61-120W/R 21.00	310HCB4	
9AGP4 £21.82	340AB4	
190AB4/C4 23.00	340AYB4	
	340AXB4	
Some Rebuilt Japanese	340RB4/CB4	
& European Types	340AHB4	26.00
Available from	RIGONDA 6"	

COLOUR TUBES

(NEW	& MULLARD/	THORN COLOR	EX)*
12VARP22	£62.50	A56-120X	£54.00
330AB22	73.50	A56-410X	64.00
A44-271X	60.00	A56-500X/510X	K63.00
A47-342X	61.00	A63-120X	63.00
A47-343X	61.00	A66-120X	65.00
A49-191X	53.00	A66-140X/410X	X70.50
A51-161X	70.00	A66-500X/510X	K65.00
A51-220X	55.00	A67-120X	65.00
A51-500X/5	10X64.50	A67-140X/2002	K69.50
A51-570X	73.00	A67-150X	75.00

*Old Bulb Required for 110° Colorex *
ADD 15% VAT TO ALL THE ABOVE PRICES.
Please allow 7 days for delivery

ALL TUBES TESTED BEFORE SALE & FULLY GUARANTEED
TELEVISION TUBE SHOP LTD

52 BATTERSEA BRIDGE RD., LONDON, SW11. Tel. 228 6859/223 5088 CARRIAGE: Mono £3, Colour £10.

TUNERS + TUNERS

- ★ If you repair sets regularly phone us today and we will dispatch immediately – no need to send cash 'up front'.
- ★ All tuners dispatched by first class post for receipt by you the next day.
- ★ All popular tuners/tuner repairs supplied 'off the shelf'.
- Unusual types repaired same day as received (subject to spares availability).



13 Worcester Street, Wolverhampton, WV2 4CJ. Phone: (0902) 773122.

PRECISION VISION LTD.

67 LONDON ROAD, HEADINGTON, OXFORD

SPECIAL OFFER THIS MONTH:-

- ☆ Large quantity of 18" Decca PIL Tube 80 Series, all in good working order.
- ★ Used VHS, Beta, 2000 System Videos in excellent working order.

PLEASE PHONE FOR CURRENT STOCK POSITION (0865) Oxford 750212

G.G.L.COMPONENTS 108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY PHONE (0228) 20358/39693

Buy it with Access

ACCESS NOW AVAILABLE Trade Counter Now Open at Unit 7 South John Street. Carlisle.

(STOP PRESS) Hitachi and Sony tubes now rebuilt.

INTEGRATED CIRCUIT	Te	TRANSISTORS		LINE O/D TO	NIEW MANAGE
TYPE PRICE (£) TYPE PRICE (£) T	TYPE PRICE (E) TYPE PRICE	TTVDE PRICEITVDE PRI	PETTOE BOICE DOL	LINE O/P TR.	NEW VALVES DY80272
LC7120 4.30 TBA4800 1.40 T	DA25912.70 AC12722	DC1041 44 DE115	A PLIANE 4 42 PPA	M 7719 19/20/22	DCEO02
	DA25932.30 AC12822	BC20812 BF167	6 BU2061.35 PHII	ILIDE CO 7.00	PCL82
MC1327A 1.00 TBA520Q 1.30 T	DA2600 E 20 AC128K 26		0 DU200 . 1.35 FRII	LIPS CO	PCL84
			BU200A , 1,40 FRII	LIPS C11 42 FA	PCL80590
MC1330P90 TBA540Q1.27 T			13 BU206/02 1.70 FRII	OBN 4500/1	PCL86
ML231B1.95 TBA550Q1.40 T			2 BU320A . 1.48 THC	ORN 1090/18.68	PFL200
		BC300 25 BF196	13 BU407 1.12 THC	ORN 1690/19,68	Pr 504
	AC187K30			ORN 7040	PL5041.50
SAS560S1.83 TBA80080			1 BUSZO Z.00 ITIC	ORN IX 1012.50	PL508
SAS570S1.90 TBA810AS1.15	AD14970	BC3711 BF 1981	E MA IFOAD AD DVE	731//13(110)10.20	PL509/5195.65
SAS5802.40 TBA8201.40	DIODES AD145/0		5 MJE34040 PTE	725(90) 10.20	PY8869
SAS5902.40 TBA8902.95 B	AD16142	BC547IU BF256LC	5 MJE3000 1.50 III	CVC 1-9 9.60	PY500A1.90
SL901B4.80 TBA920Q1.50 B.	Δ115 14 AF126 20	BC548 10 BF258	5 N2008B 1.45 DEC	CCA 22308,30	PY81/800
	BA154	BC557 10 BF259	6 R2010B 1.45 DEC	CCA 808.58	
	A1134	BC558 10 BF337	8 R2540 2.35 DEC	CCA 1008.58	ANTI CHICA CHICAG
	B105B25 AU1102.10	BD124P55 BF3383	0 TIP29C45 GEC	C 21109.45	ANTI-SURGE FUSES
SN76003N 2.05 TCA270SQ 1.30 Bi	B105G25 AU1132.20	BD131 33 BF355 3	2 TIP30C45 ITT	CVC 207.75	AV SZUMINI BUMA
Chimococki a on Torras			8 TIP31C46 ITT	CVC 25/30/328.00	100, 160, 200MA1.7
SN76023N 1.80 TCA940 1.55 B SN76110N 90 TDA1002A 1.50 B	1V420 4= DC100D14		0 TIP32C47	E.H.T. TRAYS	315, 400, 500, 630, 800MA,
CNITCORON 4 45 TO A LOOPA . 1.50 P	V164	BD202 70 BF459 3	6 TIP33B80 RBN	M T20/22A	1A, 1.25, 1.6, 2A 1.2
SN76226DN 1.45 TDA1003A 2.80 B		BD203 70 BFR90 1.6			2, 3.15, 4, 5A 1.3
\$N76227N 1.00 TDA1004A 2.70 B \$N76660N 65 TDA1035 3.20 B	Y17960 BC14026			ILIPS G8-5506.90	A /O 4
SN76660N65 TDA10353.20 B	Y210/800 30 BC141 26	BD222 50 BFT43 3	0 TIP295570 PHII	ILIPS G96.45	A/S 1.25"
SN76666N83 TDA10443.10 B	Y22386 BC14223	BD232 50 BFX85 3	0 TIP305555 THO	ORN 950 MK2 4.35	250, 500, 630, 750, 1A, 1.25,
TN7120P2.05 TDA11701.80 BY	Y227M	BD233 37 BFY51 2	2 TV106/02 1.60 THC		1.5, 2A
TA7130P2.00 TDA141290 B		BD234 40 BR100 1	8 2N3054 55 THC		2.5, 3, 5A
TA7193P4.20 TDA21903.20 B	VVEE (600 36 BC148	BD235 32 BR101 3		ORN3000/35007.75	(PRICES PER PACK)
TA7205AP 2.80 TDA2020 2.95 B			5 2N3703 12 THC	ORN8000 4.00	
	YX71/60078 BC15811	BD237 40 BT106 1.1	5 2N5496 50 THC	ORN8500/88005.90	SUNDRIES
TBA120A 62 TDA2523 2.25 O	A9007 BC15911	BD238 39 BT116 1.3	0 2SC1172Y THO	ORN90008.40	PYE IF GAIN MOD7.85
TBA120AS 70 TDA2530 2.10 1N	N4001-707 BC16022	BD410 50 BT106/2 . 1.5	81.85 PYE	E 731 6.55	E/W COIL G111.65
TBA120B 90 TDA2532 2.20	N5401-8 12 BC172 10	BD434 50 BT119 , 2.3	0 2SC2029 .2.00 DEC	CCA 2230	VA1104 70
TBA120\$B90 TDA25401.95	non == DU1//	DD437 / U D I IZU Z.3	0 ZSCZU/8 .Z.00 IIDEC	CCA 80 6.301	GRIBANSDUCTOR 2.25
TBA120U 1.00 TDA2560 1.80 Y					
TBA3951.25 TDA25811.70 BZ	ZAO1-14119814 BC182LB11	BD/07 1.05 BU126 1.7	8 25C2078 .2.20 GEC	C 2001H6.95	B/L COAX PL
TBA39685 TDA25902.25 B2	ZX61-range18 BC182LB11 ZY88-range11 BC183LB11	BDX321.65 BU2041.5	0 25C1969 .2.45 ITT	CVC 20/306.85	LINE CONNZ
			<u>Uni</u>	iversal	
VE WILL ONLY SUPPLY			BUTTONS/TUNERS		SMALL PART OF OU
UALITY, BRANDED COMPO	NENTS. DECCA 30(400/400):	350V2.55 DECCA/ITT	4W6.4	45 LARGE RANGE OF LA/TA	UPC/STK RANGE, WE WILL B

2.90

QUALITY, BRANDED COMPONENTS. DEC REPUTATION COUNTS WITH US

REBUILT TUBES

Fuli range of tubes available. Range includes Deltas, PIL, 20AX/30AX inc. Hitachi and Sony tubes also. Prices and delivery on application.

Quantity discounts available on request.

BLICH MIIDDHY

IV ELECTRICE!	_	•	•	
CCA 30(400/400)350V CCA 80/100(400)350V				
0)250V				,
LIPS G8(600)300V				

PHILIPS G9(200)63V PHILIPS G9(2200)63V PHILIPS G11(470)250V PYE 691/7(200-300)350V RBMA823(2500/2500)30V THORN1400(150/100/100/100/ 1.15 150)320V 2.40 THORN3500(175/100/100/ 400)350V THORN3500(1000)70V THORN9000(400)400V 2.25

DECCA/ITT 4W6.45	LARGE
DECCA/ITT 6W7.40	
PYE201 6W15.80	TVDE
PYE201 6W	AN240
PHILIPS G8S/Q12.00	AN7140
HITACHI 4W8.50	
ITT CVC5 7W9.40	HA132
ITT CVC8/912.80	HA1366
PHILIPS G11 (TIP SW.) 23.80	HA1377
1043/05TFK	HA1388
U321 TFK	LA4102
U322 TFK	LA4400

E RANGE OF LA/TA/UPC/STK /Cs NOW AVAILBLE SAE PRICE (£) | TYPE PRICE (£) 3.00 2.40 3.30 2.10 2.30 2.80 I A4422 2.75 LA4422 LC7137 TA7222 TA7227 UPC575 UPC1025H UPC1181 UPC1182 UPC1185 UPC2002 3.20 2.30 2.50 3.80

RANGE, WE WILL BE DELIGHTED TO SEND DETAILS OF OUR WHOLE RANGE

ORDERING ORDERING
Please Add 50p
For P/P U.K. Add
15% VAT To
This Total.
Export Orders —
Cost.
DELIVERY BY
RETURN ON ALL
STOCK ITEMS.

TV LINE OUTPUT TRANSFORMERS

FAST RETURN OF POST SERVICE

KANK BUSH MURPHT	
Z146 A640 dual std mono	7.00
Bush A792, A793	
single std mono	7.00
A774 single std mono	7.00
A816 solid state mono	9.00
DECCA	
DECCA	7.00
MS1700 2001 2020 2401 mono	7.00
MS2404 2420 2424 mono	7.00
CS1730 1733 colour	8.00
CS1830 1835 colour	8.00
'30' series Bradford colour	8.00
80 series colour	8.00
100 series colour	8.00
FERGUSON HMV MARCON	VI

8.00 1600

G.E.C 2047 to 2105 7.00 2000 to 2064 dual std mono 7.00 DUAL STD hybrid colour 8.00 SINGLE STD hybrid colour 10.00 Indesit 20EGB 24EGB mono 9.00 VC200 VC205 VC207 mono 7.00 CVC5 CVC7 CVC8 CVC9 col. 8.00 CVC20 series colour 8.00 CVC30 CVC32 series colour 8.00

PHILIPS 170 series dual std mono 7.00 210 300 series mono G8 & G9 series colour 8:00 PVF 169-173-569-368 7.00 EKCO RV305-769-725-741 8 00 WALTHAM 125 9.00

REWIND SERVICE - available for most continental types, i.e. Kuba, Luxor, Korting, Tyne, Berry Skantic, K80 £15.00 inc pp, VAT. Old lopt

WINDINGS

RANK BUSH MURPHY

T20a T22 Pry & Sec

Z718 series primary Z718 series EHT overwind	6.00 7.00
ULTRA THORN 1690 1691 EHT overwind	7.00
PYE 691 to 697 EHT overwind 691 to 697 primary	4.00 5.00

PRICES INCLUDE **15% VAT**

Add 65 pence postage to all lopts and windings All lopts and windings are new and guaranteed

8.00

Open Mon.-Fri. 9 to 5.30 pm Delivery normally by return.

CVC45

PAPWORTH TRANSFORMERS

80 Merton High Street, London SW19 1BE

S.A.E. all enquiries Barclaycard and Access welcome

For orders

placed at the post office Trans

01-540 3955

USING YOUR SPARE TIME PROFITABLY?

If not, you're losing money. Money that you could be making by selling used colour televisions from home in the evenings. In fact, provided you start correctly and know exactly how to operate, you can easily earn a substantial CASH INCOME with a starting capital of less than £20. Our new unique publication "How to Deal Successfully in Used Colour Televisions" enables you to follow in the footsteps of many experts who have a great deal of combined experience in this lucrative home business, and who have 'pooled' their knowledge to help you. After all, to follow the advice of someone who has travelled the ground before you, is to be given the best possible start. And the hundreds of valuable trade secrets, hints, tips and suggestions in the guide show exactly how anyone of average intelligence can succeed immediately.

Every aspect, from securing the first television right through to rapid expansion of sales, is covered with the detailed knowledge of experts to ensure certain success. Indexed Information on almost all makes of television is presented in clear tabular form, describing performance, reliability, price and service. In particular, the tips on expanding the business are very practical, and are almost automatic when put into practice. Pages of unique advice on advertising ensure that maximum sales are secured, and sources of supply are described in detail – for both televisions and new/used spares. Monochrome sets are also covered, as are 'invisible" cabinet repairs. Plus FREE on-going advice and FREE regular updating service.

You can start tomorrow - but you'll need our guide. The latest big illustrated edition is out now, and costs just £4.95 - a small price to pay for financial

ORDER TODAY FROM:

GLOBUS INDUSTRIES LTD., UNIT 18, DARLEY ABBEY MILLS, DERBY.

Please allow up to 28 days for delivery

To: Globus Industries Ltd., Unit 18, Darley Abbey Mills, Darby.
Please send by return post "How to Deal Successfully in Used Colour Televisions
Lenclose cheque/n o for £4 95

NAME
ADDRESS

ELECTRONIC EQUIPMENT SERVICING

(TELEVISION/VIDEO full-time College courses)

- College Diploma or BTEC awards -

TRAINING INVOLVES A HIGH PERCENTAGE OF WORKSHOP FAULT DIAGNOSIS ON TELEVISION & VIDEO CASSETTE RECORDERS

- 15 MONTHS COURSE for beginners to include Electronic Fundamentals
- 6 MONTHS COURSE for BSc, HND, CGLI, TEC and similar applicants
- 3 WEEKS INTENSIVE VCR COURSE for applicants with Colour
 TV trade experience

The above courses commence on April 24th and September 19th Also courses in Computers/Microprocessors, and Robotics leading to BTEC awards.

LONDON ELECTRONICS COLLEGE (Dept T3/4)

Prospectus from: 20 Penywern Road,

Earls Court, London SW5 9SU

Tel: 01-373 8721

HOW DARE THEY!

If you see an advertisement in the press, in print, on posters or a cinema commercial which makes you angry, write to us at the address below. (TV and radio commercials are dealt with by the I.B.A.)

The Advertising Standards Authority. If an advertisement is wrong, we're here to put it right.

ASA Ltd., Brook House, Torrington Place, London WC1E 7HN.

SATELLITE RECEIVING EQUIPMENT

1.9M, 2.5M and 5M Harrison Dishes Sat-Tec R5000 4GHz Receivers Avcom COM-2B 4GHz Receivers California Amplifier 4GHz LNAs Chaparral Feed Horns

Demonstrations by appointment only

Dealers wanted

HARRISON ELECTRONICS

22 Milton Road,

Westcliff-on-Sea, Essex SS0 7JX. Telephone: Southend (0702) 332338

A.B.C. TRADE SALES

COLOUR T.V.'s

Philips G8, Pye, Decca 30's,
Thorn's 3000's, 3500's, 8000's

Prices start from £12 - Working sets from £20

Hundreds of Mono T.V.'s from £2.00

Jap. sets from £30.00

Special prices for quantity

9,000 sq. feet Warehouse 83 SHOWELL ROAD, BUSHBURY, WOLVERHAMPTON, STAFFS.

Tel. Wolverhampton 722637

SOUTH LONDON TELEVISION ANNOUNCE

NEW LARGE WAREHOUSE NOW OPEN

100's COLOUR TV's IN STOCK

		•		
Philips G8 - 520		£15	ITT Hybrid	£15
Philips G8 - 550		£18	ITT S/State	£18
G9's £20	G11's	£35	Pye 205's	£6
Thorn 8500		£15	Mono (single standard)	£2
GEC S/State		£15	Secondhand Tested Tubes	
Pye 725 series		£18	Agents for Sussex Regunned	Tubes
Pye Chelsea		£18	Stands and Panels	
Japanese		£18	Philips 1700 VCR's	£20
Delivery in London Area			All prices subject to V.A	.T.

South London Television, Elim Hall, Southey Road, London SW19
Tel: 01-543 5437

"NORTH LONDON WHOLESALER'S"

 \star

*

TV SALES

Constantly changing stock of most popular colour sets,

Plus:-

Large selection of working mono's from just £4 each.

Re-gunned tubes available. 5 mins. M.1.

Please telephone us for details on:-

WATFORD 45590

LONDON'S LARGEST TELEVISION WHOLESALER . with over 4½ thousand sq. feet.

"TELEMANN"

8-10 RHODA STREET,
(Off Bethnel Green Road)
LONDON E.2. FREE CAR PARK
TEL: 01-739 2707
ALL MAKES IN STOCK AND GUARANTEED

PYE 22" COLOUR FROM £7.50
PHILIPS 22" (Teak cabinet) PARCEL OF TEN £15
MONO DUAL STANDARD PARCEL OF 20 £1
— SINGLE STANDARD £3

COMPLETE

FREE DELIVERY TO THE LONDON AREA! TELEPHONE 01-739 2707 - NOW!

VISIONTEL

BEST QUALITY EX-RENTAL SETS FROM £10 HERE IN CENTRAL LONDON!

100's OF SETS ALWAYS IN STOCK – COMPETITIVE PRICES

VIDEO RECORDERS

(SUBJECT TO AVAILABILITY)

We also have PYE - DECCA - GEC - ITT - GRUNDIG - JVC - PHILIPS G9 - THORN 9000 and MANY - MANY - MORE!

FOR CURRENT STOCK DETAILS TELEPHONE 01 328 3787

OR VISIT US AT 55 KILBURN HIGH ROAD NW6

TELEVISION TUNER REPAIRS ALL TYPES

BRITISH, EUROPEAN JAPANESE ETC.

MEN-TU ELECTRONICS LTD. SALTERNS LANE, FAREHAM, HANTS.

Tel: 0329-235116

WIZARD DISTRIBUTORS

MANCHESTER

SPECIALIST DISTRIBUTORS TO THE TRADE OF T.V. & VIDEO SPARES.
WE STOCK A FULL RANGE OF PARTS &

COMPONENTS INCLUDING C.R.T.'s

RANK - THORN - PHILIPS - ITT
DECCA - GEC ETC.

THANDER & LEADER STOCKIST TRADE COUNTER OPEN: 9-4.30 CATALOGUE ON REQUEST. Mail Order Enquiries Welcomed

EMPRESS STREET WORKS, EMPRESS STREET, MANCHESTER M16 9EN. TEL: 061-848 0060.

TV VALVES

COLOUR VALVES PY500/A-65p, PL509/519-£1.50.
MONO VALVES ECC82, EF85, EF183, EF184, DY87,
DY802, PCF80, PCF802, PCL82, PCL83, PCL84, PCL85/
805, PCL86, PCC84, PCC89, PC92, PC97, PC86, PC88.
PFL200, PL36, PL504, PY800, PY88 ETC.
MONOCHROME VALVES ALL 35p EACH.
ALL VALVES EX-EQUIPMENT & TESTED.
P&P 50p Per order, Access/Visa Cards welcome.
ELECTRONIC MAIL ORDER, 62 Bridge St.,
Ramsbottom, Lancs, BL0 9AG. Tel. (070682) 3036.

TELEVISION

Trade Supplies of Good Quality Colour & Mono TV's. Most Makes available, suitable for Sale or Re-Rent.

GENERAL **FACTORS**

UNION STREET, DONCASTER (0302) 49583-68416)

GOOD MOTORWAY ACCESS

REBUILT COLOUR TUBES **DELTA TYPES**

Example Prices

All sizes up to 22'' - £28.00All sizes up to 26'' - £32.00

All In Line P.I.L. Mono Gaming Machine C.R.T.s

Fast U.K. Delivery

Call or Phone:

RE-LIFE T.V. TUBES PLANE STREET, OLDHAM, LANCS. 061-665 2668

Big reductions on Contract Orders Home or Overseas. Wholesalers Required in certain parts of the U.K.

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and

The prepaid rate for semi display setting £6.00 per single column centimetre (minimum 2.5 cms). Classified advertisements 35p per word

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement

TELEVISION

Trade & Retail supplies of s/h colour & mono TVs. Most makes available. workers or non-workers

SOUTHPARK DISTRIBUTORS

Unit 4 Rubastic Road, Brentpark Industrial Estate, Southall, Middx. UB2 5LL. 01-574 4631, Ext 28

EX RENTAL C.T.V.'s & REGUN TUBES

RBM, THORN, DECCA, PYE GEC, GRUNDIG, ITT, PHILIPS G8, G9, G11, **JAPANESE** From £10

Also all modules from £4 untested.

STARLITE ELECTRONICS. 80 Como St., Romford, Essex. **Telephone Romford 752537** London Code 3.

SCHRADER TUNABLE UHF Masthead Amplifier RB45 A.S. MV 30DB gain, 1.6DB noise. CH. 17-65. P.S. inclusive £39.50 P&P £1.50. R. VAN REYSEN, 28 Pemberton Road, East Molesey, Surrey.

N.W.ELECTRONIC

Sale of the Year!

Open 6 days

2,000 Colour T.v.'s to Choose from

BUSH 1 CHIP £10 BUSH 2 CHIP £15 (Excellent Cab condition. Change over sets - high percentage workers)

GEC 2010 PLASTIC AND WOOD CAB	£25
PHILIPS G8	£15
PYE 223	£35
BUSH 718 TIL TUBE	
BUSH T22P.O.A. (dependent on quantity red	quired)
Other makes in stock include G11, HITACHI, SANYO	ETC.


White Goods

FRIDGES, FRIDGE/FREEZERS, HOOVER TWINS, HOTPOINT TWINS, AUTOS etc.

SPECIAL OFFER - We need the room 100 HOOVERMATICS MIXED 3174, 3334, 3301L £500 - DELIVERY ARRANGED. LARGE QUANTITY FRIDGES, FRIDGE/FREEZERS FROM £10 HOOVER AUTO'S FROM £14

Don't forget we are open all day Saturday 9-5.30

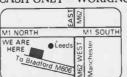CASH ONLY - WORKING TV'S FROM £29 - ASK FOR DETAILS.



UNIT 1, WHARFEDALE ROAD, M606, EUROWAY ESTATE, BRADFORD. [0274] 688458

OPEN MON - SAT 9 - 5.30

(minimum 12 words), box number 70p extra. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2612, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5846).

•

.

•

.

BARRY TV SERVICES

(EAST ANGLIA)

Your friendly wholesalers. We cater for the smaller dealer who requires regular small supplies of quality used colour TV's. From £25 + VAT. Fully working with good tubes and cabinets, straight from our retail shelves, ready to sell or rent.

Delivery available

Contact John, Dave or Steve on Ely 61462 or Cambridge 69215

COLOUR BAR GENERATOR

Pal Colour Generator with 11 patterns plus sound. Grey scale, Colour Bars, Red, Green & Blue Raster, Crosshatch, Dots, Chequer Board, Black Raster, White Raster, Half Black & White 275.90.



BLACK AND WHITE GENERATOR BLACK AND WHITE GENERATOR
Crosshatch, Peak White, Dots, Half Black & White and
Grey Scale
In Circuit Translator Testar
Capacitance Meter measures 10pFto 1µFcomplete with
English and Impairs.

moving coil meter

Prices include P&P & VAT.

C.M.J. ELECTRONICS Unit 8, 16 Union Mill Street, Horseley Fields, Wolverhampton WV1 3DW. Tel: (0902) 871568.

TRADE COLOUR TV's ALWAYS 200 IN STOCK Phillips 68 from £10 Bush Twin Chip from £8 Pye Chelsea from £15

Avo repairs prompt service scopes etc. Colour TV's in good working order from £35. E.G. Phillips G8's 22" £35. Ring us for spares and type availability

anytime.

Also Videos. V2020 and V2023's etc.

ALL STOCK CHANGES WEEKLY

(0934) 514047/512792/27560 P&R SUPPLIES, Unit 5, Worle Industrial Estate,

Weston-Super-Mare. Exit 21 M5.

★ TELEBEST ★

.

We specialise in working sets.

BUSH · DECCA · G.E.C. GRUNDIG · PYE · PHILIPS THORN Etc.

From £25 plus VAT.

Non workers available

Mono £1.00 plus VAT

Call Ronnie on: 01-514 1333 for stock availability 841 Romford Road, Manor Park, London E12.

SCRATCHED TELEVISION TUBES. Don't despair. send for repair, 20 years experience. Retube Limited, North Somercotes, Louth, Lincolnshire. Phone 0507

GREYFIELD ROAD, HIGH LITTLETON, **NEAR BRISTOL**

(A. H. GORE LTD. EST)

TELESCENE" BRISTOL

TRADE SALE OF T.V.s

COLOUR MONO

£18.00 to £30.00 INC. VAT £4.50 EACH INC. VAT

ALL COMPLETE MOST WORKING

ALL SIZES

All Enquiries Welcome

Tel TIMSBURY 72228 After 6pm BRISTOL 834548

TUBES £29.00 INCLUSIVE, REGUNS ONE YEAR GUARANTEE, **TUBES £14.50**

QUANTITY DISCOUNTS SIX MONTH GUARANTEE SLIGHTLY USED

A56-120 A51-110 A49-191 A47-342 or 343 A44-270-1 A66-120 A67-120 (All 26" add £5) IN-LINE 51-161 From £35 plus 100's more

Professional Stick DE-GAUSING COILS £19.50 inclusive of delivery. One year

guarantee.

Delivery £5 per tube. British Isles. No need to spend £5 returning old tube if you buy from us. U-VIEW TUBES, 29 WARMSWORTH ROAD, DONCASTER, YORKSHIRE DN4 0RP.

Tel: 0302-855017 Callers ring first, Open every day including Sunday Local stockists. Cash & Carry only at the above prices. Ring first. Please bring old tube if possible. K. M. ELECTRONICS, 8 Hillfield Place, Aberporth, DYFED EQUIRED 0239 810963

DELTA TVs, Unit 5A, Union Mill, Union Mill Street,
WOLVERHAMPTON
0902 870757 OTHER ST OTHER STOCKIST REQUIRED

SATELLITE TV RECEIVER

Receives 3.65-4.2GHz band. Ideal for demonstration terminal in UK. 100 degree KELVIN LNA. £385 + Carriage.

SAE DATA, TVDX lists.

H. Cocks, Cripps Corner, Robertsbridge, Sussex. Tel: 058083 317.

GLOBETEL

Tel: 807 6992

Les & Phil - Ex. S.T.S. Colindale Rear of Globestone Ltd., 1-7 CHURCH ST., EDMONTON.

We have now opened our own warehouse for used T.V.'s at very fair prices.

All popular makes in stock, eg: Philips, Pye, Grundig, Jap. sets, etc.

Look forward to seeing both old and new cust.

We also stock & buy used videos - VHS only.

GRUNDIG. We sell complete working sets from £40. Reconditioning panels from £4. We buy remote control handsets. OCHREMILL 0785-814643.

Thorn 3000/3500

UNIVERSAL

i year guarantee

TRIPLERS

The UNIVERSAL TRIPLERcan be used in most G.E.C., I.T.T., Pye. Rank, Decca & Continental

WING ELECTRONICS

15 Waylands, off Tudor Rd, Hayes End, Middlesex

SPARES, PANELS AND MANUALS **PHILIPS · GRUNDIG**

TELEVIEW 01-994 5537 194, Acton Lane, London W.4.

WOODSDALE COMPONENTS RANK BUSH MURPHY **TRANSFORMERS**

Line Ouput Z718 (T703A, T706A) New (Complete)

£20.50

Less Focus Module and Rectifier

£10.50 £9.00

T20, T22 (T705A) T26 (T705B) Switch Mode T114A/B

£9.50 £8.00

Genuine RBM Units.

AERIALS

UHF Aerials P & C Wideband 4 Bay Bowtie (12.5 dB) £20.00 Above with built-in Broadband amp. (27dB) plus stabilised power £45.00 supply

Prompt Postal Service. Add 15% VAT to all prices. DISCOUNT for QUANTITIES.

34 Field End Road, Eastcote, Pinner, Middlesex. HA5-2QT. Tel: 01-868 5580.

N. Skehan

Agents Office. Callers by appointment only.

SETS & COMPONENTS - CONT

GRUNDIG MILLIVOLTMETERS 100 μ V/300V. Working order £15 + £3.00 p&p. Also P.S.U.s, isolating transformers, etc. S.A.E. Lists, S.H.E., 5 St Josephs Park, Ballycruttle, Downpatrick BT30 7EN.

TELEVISIOM

CANVEY COLOUR TUBES

Unit 3, Charfleets House, Charfleets Industrial Estate, Canvey Island, Essex. Tel: Canvey Island (0268) 690577

CURRENT PRICE LIST

DELTA TUBE TYPE FROM £27.50 to £31.50 INLINE TUBE TYPE FROM £35.00 MONO TYPES P.O.A.

ALL PRICES EXCLUSIVE OF VAT.

All Tubes Guaranteed for 2 YEARS and Reprocessed to Original Manufacturers Specifications.

COLOUR T.V.s

THE BEST IN LONDON 200 + TVs WEEKLY

LOADS SMALL SCREEN WORKING SETS TO ORDER — ALL MAKES

WINDSOR WHOLESALE TEL: 01-968 8771.

WETSTED UBES PRESENTS AN UNBEATABLE OFFER

£26 ALL DELTAS ONE PRICE £40 ALL P.I.L. ONE PRICE

- SPECIAL CRT POLISHING SERVICE
 WHILE U WAIT Only £5
- * ALL DELTA SIZES FROM STOCK
- * DISCOUNT FOR ORDERS OF 5 CRTs OR OVER
 - * FREE DELIVERY WITHIN 20 MILE RADIUS OF MAIDSTONE

Ring Now

Ring Now

Maidstone 872400

or visit our factory.

Unit 32, Branbridges Ind Est.

East Peckham, Kent.

* Agents required in South
Prices do not include VAT

KWW.

- * Britains most reliable source of quality TVs.
- * Hundreds of working polished TVs.
- * New adjustable TV stands.
- * Pye 18" Chelsea's working & polished £35.00 in quantity.

Krystal Marketing Ltd., Breedon Cross Storage, Dale Road, Selly Oak, Birmingham B29 6AQ.

Phone 021-471 3023 Telex 335540-G Ask for Les

TVs WANTED FOR CASH IN EIRE

UHF/VHF colour and black and white, any quantity. Working or non working. Will collect any part of Eire.

BOX NO TV 185.

SECOND HAND Colour TV spares and tubes. Most makes. Telephone Southport (0704) 74411. Anytime.

JABCO LOPT TESTER

Used by Mullard, Plessey, Ministry of Defence, BBC, IBA, and worldwide etc. etc. £16.50 inclusive. C.W.O. delivery 3 days. £18 overseas post by sea. £21 airmail.

J. BAKER & CO.

1 Old Shoreham Road, Southwick, Sussex BN4 4RD. Tel: Brighton 593315

COLOUR TV PANELS Fully Tested & Working

					Line	rrame	
	1F	CDA	Decoder	LTB	Board	Board	Power
DECCA 13/30	3.00	_	7.00	5.00	-	_	4.00
BUSH 'A'	2.00	_	5.00	5.00	2.50	_	2.00
THORN 8-81"	_	_	10.00	5	_	_	5.00
PYE 205	3.00	3.50	5.00	8.00	_	2.00	_
THORN 3+34K	3.00	-	5.00	8.00	_	-	10.00
G8	6.00	_	8.00	5.00	15.00	_	5.00
BUSH twin chip dec	oder 10.00						
					fitted wit	h	
					brand ne	w	

Post & packing: 1 panel £1.50; 2 panels £2.25; 3 panels £3.00 etc.
Hybrid panels do not include valves.

Terms cash with order.

26° CRT's:

£3.00 etc. transformer 26" CRT's fully tested £10

LAVITE LTD.,

Golcar C of E School, Church St., Golcar, Huddersfield. Tel.: 0484-643273

Callers by appointment only.



We have moved into additional warehousing and are now offering MORE CHOICE AND BETTER VALUE

Guaranteed - Complete Sets from £10.00
Trade Workers from £25.00
Panels By Post from £3.00
Mono's from £1.00
Stands — Aerials — Accessories Etc.

Make 84 your most Profitable year with SCREENPLAY'S unbeatable Stocks and Prices

OPEN 5 DAYS -

Phone: Hitchin 31644

SECTION THREE, UNIT FOUR, SERL COMPLEX, LONDON ROAD, BALDOCK, HERTS.



SERVICE PAG

CAPITAL REGUN TUBES! 19 Goulton Road. London E5

YOUR NORTH EAST LONDON C.R.T. DEALER

Deltas from £25 Philips G11 Tubes f37-£40

2 YEAR GUARANTEE

Phone ANGUS 01-986 0702

WANTED

WANTED - WANTED - WANTED TV's - TV's TV's Colour & Mono. Also Videos (regular supplies if possible). Any quantity, any make. Telephone Bradford 0274 480281. Manchester 061-798 0037.

WANTED. Telequipment Oscilloscope Type S54 for parts. Telephone 0222 797469 anytime.

WANTED PHILIPS PM5334 Television Sweep Generator. Telephone 01-328 7641.

WANTED, ET 021 Tuner, VHF-UHF. Phone Rob, (01) 341 2642 mornings.

COMPLETE TUBE RE-GUNNING plant. Electric ovens also Lopt winding machine. KELLEHER BROS, TV House, Kanturk, Cork, Ireland. Tel. 029 50046.

WANTED. We will clear any amount of colour sets from small Rental Companies, Hotels, etc. Please phone P & R Domestic Electrical Clearance Supplies, Weston Super Mare (0934) 514047.

WANTED, OUANTITY G11's or other late colour T.V.s. No rubbish. Can collect Sussex/Kent. (0424)

WANTED FOR CASH any videos, TV's, televertas, test equipment or tube plants. Ring Scott on 01-299

WANTED HITACHI CTV's, Model CTP210 & CBP220. Phone Littlehampton 4717 anytime.

AERIALS

2 METRE PARABOLIC DISHES

Glassfibre Construction. Suitable for 4 And 12 GHz £290 Polar Mounts And Feed Supports Available.

Send S.A.E. for Details SP ANTENNA SYSTEMS, 3 Woolpack Corner, Biddenden, Ashford, Kent TN27 8BU Tel: 0580 291090

AERIALS AND ACCESSORIES

North Londons Specialist Aerial Supplier Wholesale and Mail Order.

VHF/UHF antennas, masts, brackets, cable, amplifica-tion and distribution equipment etc. All types of serial hardware and software supplied. Single and multipoint systems planned and installed. Send 50p for our new 1983 catalogue and price list.

S.C.S. AERIALS (Aerial Distributors) 26-28 Port Vale, Hertford, Herts. SG14 3AB. Tel: 0992 50478.

AERIAL BOOSTERS

Next to the set fitting

B45H/G-UHF TV, gain about 20dbs, Tunable over the complete

UHF TV band, Price 28.70.

BIL-VHF/FM RADIO, gain about 14dbs, when on the off position
connects the serial direct to the radio. Price £7.70.

All boosters we make work off a PP3/005p/6F22 type battery or
8Y-18V DC, P&P 30p per order.

ELECTRONIC MAIL ORDER, 62 Bridge St, Ramsbottom,
Lancs Blu 9AG, Tel. (070582) 3036

Access/Jiss Cards Welgame

SAE Leaflets

SAE Leaflets

Access/Visa Cards Welcome SAF Leaflets

SERVICE SHEETS

SERVICE MANUALS. Covering any radio, T.V., Audio, etc. from only £1.95 plus L.S.A.E. - S.a.e. for details. DATATECH, P.O. Box No. 66, Gloucester GL1 3LZ.

TECHNICAL INFO SERVICES 76 Church St – Larkhall – Lanarks **Giant TV & VCR DIAGRAM MANUALS**

Brit CTVs 3 vols £45 Vol. 1 Decca G.E.C. ITT Vol. 2 Philips Pye Redif. £17 £17 Vol. 3 Rank Bush Thorn £17 Foreign CTVs 2 vols £32 Mono (Stand + Port) Early VCR (VHS/Philips) 2 vols £32 £17

£7.50 each New T.V. Rep. Manuals 1983 Brit. CTV or Foreign CTV 4 £105 Complete set of 15 for

VCR later models + Betamax

Comprehensive practical T.V. Repair course in manual £8.50

Large SAE brings FREE 50p magazine inc. service sheet/details of unique T.V. publications. Any quotation plus price lists, etc.

Full size service sheets £2 + l.s.a.e. £3 + l.s.a.e. CTVs/Mus. C.

Worlds largest collection of service manuals 1930 to date. From £4.50 to £35 each.

e.g. Autovox/G8/A823

£17

FOR FAST QUOTES RING 0698 883334

SANDHURST PUBLICATIONS

Television Service Sheet Specialists Workshop Manuals, large selection of Japanese and European TV Sheets. Callers 5.30-7.00 pm. Upper Floor. Send S.A.E. for

Catalogue and Enquiries:
49C Yorktown Road, Sandhurst, Camberley, Surrey GU17 7AG.

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. £1.50 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

30,000 SERVICE SHEETS IN STOCK. COLOUR MANUALS ALSO AVAILABLE

TV Monos, Radios, £3.00. Tuners £3.00. Tape Recorders, Record Players £3.00. Transistors £3.00. Car Radios £3.00 + SAE. Stereograms & Music Centres £3.00. Radiograms £3.00. Also Colour available. State if circuit will do if sheets are not in stock. Circuits £3 - colour. All TV Sheets are full length 24 × 12 not in Bits and Pieces. All other Data full lengths. All Sheets £3 except colour. SAE please. Old Valve Radios £3 + SAE 9 × 3. Ensure payment with order.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX.

(MAIL ORDER)

ORDER FORM	PLEASE WRITE IN BLO	CK CAPITALS	
Please insert the advertis	sement below in the nex	t available issue of Televi	sion for
insertions. I enclose Che (Cheques and Postal Ord		 Lloyds Bank Ltd and mad	e payable to Television)

Send to: Classified Advertisement Dept
--

NAME	• • • •
ADDRESS	••••

TELEVISION Classified Advertisement Dept., Room 2612, King's Reach Tower, Stamford Street, London SE1 9LS. Telephone 01-261 5846. Rate 35p per word, minimum 12 words. Box No. 70p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

3/84

TOP QUALITY	SPECIAL CLEAR	RANCE	TOP QUALITY
Makes		Non-Workers	Working
Philips G8S,	2 chip Bush/Murphy	£16	£30
Thorn 3000,	3500, 8000, 8500	£18	£30
Thorn 8800, 9	000, 9800, Touch Tune Sets etc.	£30	£45
Bush T20's, I	Philips G11's	£50	£70
GEC Solid St	ate, all types	£25	£45
ITT CVC 5/8/	9	£14	£30
_			

MONO IN BATCHES OF 20 at £2.00 EACH. Discount for quantity. Other makes available on request.

Spare TV parts and panels available for the ove sets mentioned at competitive prices. ease refer to last month's issue of Television for price list.

ELECTRONICS

ase refer to last month's issue of Television
for price list.

N.B. Note to give prompt service, telephone to order in advance to avoid disappointment.

ONE METRE DISH for satellite T.V. Slight damage, hence £60 o.n.o. Peter 01-452-3292.

RADIO AND T.V. SERVICING 1965/66 - 1977/78. (Less 1967/68), 12 volumes £55. Tel, 0222 372930.

JAPANESE COLOUR TVs, Panasonic, Hitachi, Mitsubishi, Toshiba, Sharp. Fully refurbished - to trade only. J. M. PEARSON TELEVISION 0484 863489.

JVC CX610GB VHF/UHF. PAL/SECAM. Colour TV/ Monitor. 5.5/6.0/6.5mhz, sound I.F. as new £135. Telephone 01-577 5355.

VINTAGE TELEVISIONS FOR SALE, (Pre-War sets wanted). For details Tel. 088 94 78416.

SECONDHAND HEATHKIT signal tracer for sale, fully assembled model IT-5283. Tel. 01-289 0598.

COURSES

CONQUER THE CHIP . . . Master modern electronics the PRACTICAL way by SEEING and DOING in your own home. Write for your free colour brochure now to British National Radio & Electronics School, Dept. C4, Reading, Berks RG1 1BR.

VIDEO

EUROLEC VIDEO SERVICES

Tel: 01-669 2611 Telex: 893819 Eurlec

Address for correspondence only: 35 Sandy Lane South, Wallington, Surrey SM6 9RF

We still have a number of new LVC 60 and LVC 90 for 1700 format machines, Price £5.50 & £7.50 inc. p&p and 1700 format machines, Price £5.50 & £7.50 inc. p&p and VAT. We also hold stocks of high and low density ½" tape on 7" spools, suitable for Sony and similar machines. Due to our increases sales of VHS tapes we can now offer the following lengths, E10, 15, 20, 30, 45, 90, 120 & 180 (shorter lengths on reasonable quantity orders). We also import a good grade of VHS cassette at £3.50 + VAT for E120, £3.90 for E180, (minimum quantity either type or mixed, 10 off. Allow 7 days for delivery and add 25p for postage per cassette). delivery and add 25p for postage per cassette).

The more professional user may be interested to learn that as a result of the change by many companies and authorities to front loading machines, we are normally in a position to offer a range of second user Umatic edit suites, prices start at £1,900 for a complete suite, checked and overhauled where necessary, Sony, JVC and National generally available. We can also offer used colour studios and portable cameras.

Finally, due to the transfer to colour systems by various major users, we also have two complete monochrome TV studios on offer for export of UK use.

For current stock availability, please telephone or telex numbers above.

STOP PRESS! Trade in units currently available!

JVC 2200 VHS portable recorder, charger and carrying case £250 + VAT. Sony SLC 2000 camera in travelling case, SL 3000 UB portable Beta recorder with two batteries, car power adaptor, TT3000 tuner timer £700 + VAT. Current Philips projection TV, 60CP 2605 integral tuner, no screen £750.

NTSC -- PAL Transfers, ring for quote. VAT Reg. No. 335 7096 45

SITUATIONS VACANT

MASTERCARE is Europe's No. 1 in servicing Consumer Electronics for the Trade

ORKSHOP SUPERVISOR

Are you an experienced Service Engineer with a recognised trade qualification, proved field experience and a talent for motivating people?

Check out these advantages of joining Mastercare:-

- Active participation in a wide variety of assignments
- Responsibility to lead a small team of Engineers
- Full parts and admin back-up by Mastercare professionals.
- Regular up-date training on new products
- Plus naturally, staff status, a competitive earnings package and all the benefit's you would expect from a large and successful Company



JOIN THE MASTERCARE TEAM WE START WHEN IT STOPS!

Contact me Alan French, CGS Limited, Arkwright Road, Basingstoke Road, READING RG2 9LX Tel: Reading (0734) 863186-8

Growth ● Prospects ● Satisfaction ● Security ●

BUSINESS/PROPERTY FOR SALE

FOR SALE

A small television repair business in East Devon seaside town. Considerable number of T/V, Radio

Service Sheets 1934 to date. Elderly Test, P.A. and similar gear.

TELEPHONE (0297) 20201

SETS & COMPONENTS

RANK BUSH MURPHY TV PANFLS

Repair, exchange, sales service, prompt efficient service. All chassis covered. New PCB available to replace burnt T20 line Panel. We charge only £16 to repair switch mode power supply. Ring Monday to Saturday and ask for Mr. Kheli.

T. K. Panels Service, 31 Bronte Paths, Stevenage, SG2 0PG. Tel. (0438) 61567.

BOOKS AND PUBLICATIONS

"RADIO AND TELEVISION SERVICING" books, new editions for the last 6 years always in stock. Prices on request. BELLS TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.

COMPLETE FULL-SIZE SETS any published service sheets £2 + LSAE except CTVs/Music Centres from £3 + LSAE, Manuals from 1930 to latest. Quotations, free 50p magazine, price lists, unique technical publications for sale. Repair data/circs almost any named TV/ VCR £8.50 by return. TIST, 76 Church Street, Larkhall, Lanarks ML9 1HE. Phone (0698 883334).

EARN CASH NOW With New Published Manuals

Domestic appliance reconditioning and repair. Two volumes only £12.50 post free. Also, a professional guide to sewing machine repair for profit. Two volumes only £8.50 post free. Both with full repair and fault guides. Leaflets available.

MARCHANT (Dept TVT), 30 Chester Road East, Shotton, Clv/yd, N. Wales.

MISCELLANEOUS

BURGLAR ALARM EQUIPMENT. Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 682674.

TOOL KITS

Impress your customers with our smart executive type case. can be purchased with or without

tools. Size: 43×32×9cm

(Money refund if dissatisfied)

(Aluminium frame). Tools: Seven nut spinners (B.A. and metric), soldering iron, crosspoint and screwdrivers, neon tester, inspection mirror, 5" cutters and pliers. Price with tools £40.00 (includes a component box). Price without tools £25.00 (includes a component box). Price of tools alone, no case £20.00. Please add £2.50 p&p.

KITONICS

7 The Meadows, Berwick Upon Tweed


COLOUR TV SETS

Philips G8, Pye 222, Decca 30 series, ITT, Pye Chelsea, Thorn 3500/8000, GEC, many others including JAP.

Working hybrids from £15.
Working solid state from £25.
Non-working sets from £5.
Working panels and tubes available.

REBUILT TUBES

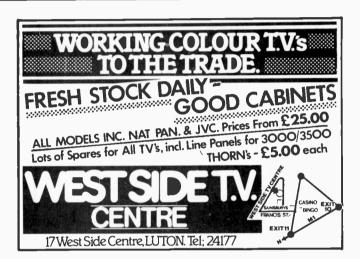Delta – In Line – PIL. SOUTHBRIDGE TV CENTRE 120, Selhurst Rd., London, S.E.25. Tel; 01-771 3535.



IRISH T.V. DEALERS

Large quantity of working Colour & B/W T.V. sets UHF-VHF. Nordmende, Bush, Philips, Ferguson, Pye, etc. at very competitive prices.

Working colour sets at £70

Fresh stocks weekly, quantity discount, delivery arranged. (SPECIALISTS IN OVERSEAS ORDERS)

For further details ring:
J. HYDE at 01-264139 Extn. 11.

T.V. TRADE SALES, E.D.I. House, Kylemore Pk. West, Dublin 10. (Open 10 to 5.30 pm) Prices exclude VAT.

EMCO – EUROSONIC – GRUNDIG – TELETON + ALL BRITISH MAKES ETC., ETC. ● ALL SPARES READILY AVAILABLE ●

IMMEDIATE CREDIT AVAILABLE — TRADE ONLY

If you are a trader simply phone for the part you require and we will send it – no quibble – no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf". e.g. LOPTX – EHT trays – droppers – OSC coils – switches – cans – smoothers – I.C.'s, etc. etc.

YOU CAN BE 95% SURE WE CAN SUPPLY ANY TV COMPONENT BY RETURN IF YOU NEED SPARES FAST — RING NOW!

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.


TELE#PART (W'TON)

THE TELECENTRE, WORCESTER ST., WOLVERHAMPTON (0902) 773122

DISPLAY ELECTRONICS

UNIT 4, SWAN WHARF, WATERLOO ROAD, UXBRIDGE, MIDDLESEX. UXBRIDGE 55800

Your Accessible CRT Rebuilders

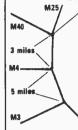

UXBRIDGE

Constructional Work on the Poyle /Uxbridge section of the M25 is now in progress and when completed we shall be less than 10 minutes from: M3 /M25 junction 2 /12 M4 /M25 junction 4 /14 M40 /M25 junction 1 /15

WATFORD STOCKIST TV SALES WATFORD 45590 SOUTH LONDON STOCKIST N & R ELECTRONICS 01-672 0802

1984 PRICE LIST Delta types

• •				
90° up to 19″	. £33			
90° up to 22"	. £36			
90° up to 26"	. £39			
110° up to 22"	. £42			
110° up to 26"	. £45			
. In-Line types				
Up to 22"	. £46*			
Up to 26"	. £49*			
*Multipole 30AX ADD				

QUALITY CHECK LIST

- **☆ BRAND NEW GUNS**
- ☆ HOT PUMPED
- ☆ RF BOMBED
- ☆ PULSE FLASHED
- ☆ EMISSION STABILISED

BUDGET DISCOUNTS AVAILABLE

Ask for Green Label Prices

28mm Monotubes available

CALLERS WELCOME

Please phone first to reserve your requirements.

LATE NIGHT THURSDAYS UNTIL 8 PM SATURDAY UNTIL MIDDAY

CRT REBUILDERS SINCE THE '60s TO MAJOR AIRLINES, M.O.D., UNIVERSITIES, INDUSTRY AND OF COURSE TO THE TV TRADE IN GENERAL

All diodes at 10p or less in this list 20 of	Min 12 volt Relays 75p Y 716 10p	— МЈ 3040	60p 60p	PHILI		Y HOME SEC		
one type £1.00 OA 47 8p OA 90 8p OA 91 8p	Y 730 10p Y 827 30p Y 860 30p	MV 2209 SP 8385	10p 25p	8Ω 4" speakers	£1	Philips GP	422.4CH	10 Mixed
OA 47 8p OA 90 OA 91 8p OA 91 8p OA 91 8p OA 91 8p IN 60 5p IN 541 3p IN 914 3p IN 2069a 10p IN 2070 10p IN 4001 3p IN 4002 3p IN 4004 4p IN 4006 4p IN 4006 4p IN 4006 4p IN 4006 4p IN 4148 3p IN 4448 3p IN 4448 3p IN 4742 10p IN 4751 10p IN 4751 10p IN 5254 10p IN 5255 10p IN 5393 10p IN 5393 10p IN 5392 10p	Y 933 5p Y 969 50p Y 997 30p R 1038 40p	Voltage Regulators +5V/UA78POSSC -5V/LM79MOSCP	30p 25p	4700/10v × 10 68/16 × 10	50p 50p	(£40 co		TV & radio speakers £5 + £2 post
IN 2069a 10p IN 2070 10p IN 4001 3p	R 1039 40p R 2009 80p R 2010b £1	-8V/79M08c +6V/78M06c LM 337	30p 30p 30p	150/16 × 10 47/25 × 10 220/25 × 10	50p 50p 50p	Stereo D Cartri		Mullard
IN 4002 3p IN 4004 4p IN 4005 4p	D 2257 60m	+12V/LM 340112	30p 20p 25p	1/250 × 10 8000/30v	50p 50p	12 Volt Aeri	al Changer	Broadband R.F. power modules
IN 4006 4p IN 4007 5p IN 4148 3p	R 2265 Sop R 2305 Sop R 2306 Sop R 2306 Sop R 2322/2323 pair 80p R 2323 15p	+13V//8M13 +18V/MC78M18 +24V/78M24	15p 20p 30p	470/40v × 10 22/100v × 10 100/350v	£1 £1 70p	over Relays	<u>£1</u>	K.I'. power modules
IN 4448 3p IN 4742 10p IN 4722 10p	[K 2390 30 0	MC 7724cp	40p 10p	400/350v .47/500v 1/600v	70p 25p 25p	GEC H V/Cap tuner, a Series		VHF. BGY33 £15
IN 4751 10p IN 5235 10p IN 5254 10p IN 5392 10p	R 2030	TIS 91 TIS 92 TIS 93	20p 20p 20p	.022/1kv 200/150/150/300v 150/150/100/300v	10p 70p 75p	6 Push Button GEC 2100 Ser Replacement for	ies	UHF. BGY22E £5 PT4236C
IN 5393 10p IN 5928B 10p IAV 30 10p	R2737 40p R2738=TIP41 30p R2775=TIP41c 40p R3129=TIP47 40p	CB Radio transistor	j	130/130/100/3000	/5 _{P.}	Button Unit Various Tools as	€12	£5 PT9783
IM 72Z55 10p	S 2008b 80p BU 105/04 80p	U 14727	15p	G11 Neon Switch GPO 5 way plug			in Accessor Ra	£1 25p 25p to socket £3
IS 164 10p IS 921 10p IS 3011a 10p	BU 108 £1 BU 124 50p BU 126 80p BU 180a 65p	11 10005	40p 15p 15p	12v screwdriver teste Mains timer. 13 amp Sellotape PVC Electi	- up tric Insul	o 2 hours: easy to ation	o use, plugs in	
IS 3072a 10p IS 5024a 50p IS 5030 50p	BU 204 70p BU 205 £1	MR 508 MR 501 MR 502	10p 10p 10p	25mm × 20M Telescopic aerials (ra UHF Radio Aerial	dio)	50p	50mm × 20M	1 70p £1 50p £3.90
TTT 921 10p TTT 923 10p TTT 1075 10p TTT 2001 10p	BU 208 60m	BYF 1204	10p 10p 40p	Xcelite pliers Xcelite snips Xcelite cutters				£5 £3.90
TTT 2001 10p TTT 2002 10p TTT 4150 10p	BU 208 on heat sink 70 BU 208 A £1.20 BU 208 D 90p BU 222 £1 BU 326 £1 BU 407 60p	BYF 3126 BYF 3214 BYX 10	40p 40p	GKN Supascrew kits VU meter			J	£2.50 45p 75p
IR 106a 20p IR 3051 10p IR 3051 10p IS 164 10p IS 921 10p IS 3011a 10p IS 3072a 10p IS 5024a 50p IS 5030 50p ITT 921 10p ITT 921 10p ITT 2001 10p ITT 2002 10p ITT 2002 10p ITT 4150 10p ITE 33 2F 33 10p IF 33 2F 33 10p IF 343 10p IF 10 10p IF 11 10p IF 12 10p IF 12 10p IF 12 10p IF 13 10p IF 14 150 10p IF 15 10p IF 16 10p IF 17 20p IF 18 10p IF 18 10p IF 19 10p IF	BU 426V 60 p	BYX 36/600 BYX 38/300 BYX 55/350	6p 35p 25p 10p	Pull up large aerial "V" TV aerial Soldering iron 6v/23v Portable TV aerial	v			£1 £2.50 75p £2
ZF 10 10p ZF 11 10p ZF 12 10p ZF 15 10p	BU 526 75p BUX 84 50p	BYX 55/600 (Bead) BYX 71/350	10p 20p	Phillips snips 2 way baby alarm/int Phillips universal batt	ercom v	vith long leads	ulb tester	£5
ZF 15 10p ZF 33 10p ZF 43 10p ZF 47 10p ZF 82 10p	I E 1579 25n	I RVV 05	50p 20p 8p	Volt/ohm test meters Eisenmann NICAD	1000 o	hm/volt SER 5.5V/150 ma		£5 £5 £2 £2,50
ZF 47 10p ZF 82 10p ZPD 3.9 10p	E 1611	BYV 96D BYZ 106 BPW 41	10p 10p 15p	12V Nicad pack. "A. Hitachi TP 007 Batte "AA"/1.25V Nicad "C" Nicad	ry pack	7.2v/1.6A		£7 £1
ZPD 4.7 10p ZPD 5.6 10p ZPD 10 10p	E 5444 10p E 5577 10p E 8018 25p E 9004 10p	DEV 13/12	8p 50p 30p 30p	"D" Nicad Duracell PP3 ** ** microphone/s	neaker			£2 £3 60p 50p
ZPD 47 10p ZPY 8v2 10p ZPY 12 10p	E 9005 10p	D73/ 15/20	30p 30p 10p	Continental 2 pin plug with 5th mains lead (black & blue) 5 for £				
ZPY 8v2 10p ZPY 12 10p ZPY 16 10p ZPY 24 10p ZPY 43 10p ZPY 47 10p ZPY 56 10p	TIC 106a 30p TIC 116n/Y 1003 35p TIC 126N 40p TIC 226m 30p TIC 225S 40p TIC 226E 40p TIC 226E 30p TIC 236E 30p	Bush thyristor RCA 76122 ITT computer bookset 2020 G8 20 turn 100K pot	£1 £2 35p	1 De-solder pump + 2 nozzels 2 Plastic box for i.c.s with anti-static pad 6"×3"×\ \frac{1}{2} \] 2 Plastic box for i.c.s with anti-static pad 6"×3"×\ \frac{1}{2} \]				
ZTE 2 10p	TIC 226E 40p TIC 226m 30p TIC 236E 30p TICV 106D (T092 case 2A/400V) 10p	Transformer 240v/20v- 500Ma Viewdata torroidals	75p £6	Flat Red LED 500gm 60/40 solder i Clearweld glue pack	reel			12p £7 30p £1
ZTK 33 10p ZTK 33a 10p ZW 13 12p	(T092 case 2A/400V) 10p TIP 29 20p TIP 29C 25p	CVC 20 tube hase	£2 75p 75p	Dual v/u meter-20-1 15 service manuals, 7 3 × C90 Cassettes	+10db Thorn 3:	504 & 3448, etc		£2,50 70p
ZTK 22 10p ZTK 33 10p ZTK 33a 10p ZW 13 12p ZW 27 10p ZW 43 10p ZW 310 10p ZY 47 10p ZY 47 10p	TIP 29 20p TIP 29C 25p TIP 30 35p TIP 30A 35p TIP 30B 40p TIP 30C 45p	Swiss made 250rpm/240V motor very small	75p	Can Freezer 75R/25 Watt 18R/11 Watt		25p 25p	15 Bulbs Video lamps Antistatic D	£1.75 40p 20 for £5 200 for £25
AA 112 10p	TIP 30 45p TIP 31 30p TIP 31 A/RCA 16334 35p TIP 32 25p	Sharp tape motor 400-040 £ Mono scan coil 110° small		120R/17 Watt Front End Music Cer MW/LW 13"×3½"	nter. VI	20p	100 Diodes 100 Fuses	£1.50 £2.00
AA 119 8p AA 143 10p AA 144 10p	TIP 33B 50p TIP 33C 70p TIP 34A 50p	neck £	1,50	Output Stage for must Both items circuit supplied (as pr		er £5 £9	100 W/W R BF 199 BC 547	.es. £1.50 20 for £1 100 for £4 rn 100k pots. Rank £2
BA 102c 10p BA 157 8p BA 159 8p BA 173 8p	TTP 34C 50p TTP 35B 50p TTP 35C 50p	LD57CA Mono scan coil G 8 transductor	15p £3 £1	SONY 1400KV Chro SONY 1400KV Tune SONY 1400KV Tou	ma Pan er unit	tel £6 £3.50	Thorn 9 volt BF 470 Metal BD 1	: power supply regulated £3.00 20 for £2 24 10 for £8
BA 173 8p BA 182 8p BA 201 8p	TIP 33B 50p TIP 33C 70p TIP 34A 50p TIP 34C 50p TIP 35B 50p TIP 35D 70p TIP 36 50p TIP 36 70p TIP 41B 40p TIP 41B 70p	AT 4041/41 transductor 2K5 Lin pot with 40mm spindle	£1 20p	3 books, Electronic S Print Circuits/1st Step	ystems/ s in TV	Guide to £1.40	20 Slider Kr 6 Mixed UI- some with k	70p IF Aerial Isolating Sockets, ong leads. Fit ITT, GEC,
BA 102c 10p BA 157 8p BA 157 8p BA 159 8p BA 173 8p BA 182 8p BA 201 8p BA 202 8p BA 248 8p BA 248 8p BA 248 8p	TIP 41B 40p TIP 41D 70p TIP 42/BRC 6109 30p TIP 47 40p	1982 Hitachi Ae isolator Mullard FM decoder 1401 Philips service pack, flat film	50p £1 15,	Texas Viewdata Deco Issue 3 with all IC's Quantity F		£10.00	Philips, Pye	Mixed Packs C Transistors £4.50
BAV 10 10p BAV 21 10p BAW 21 10p	TIP 48 40p TIP 49 30p TIP 57 30p	57 condensers 56nf-2.2uf VHF 3 Transistor rotary tun DX-TV	£1	BY204/4 BY206 BD132/676a		25 for £1.00 25 for £1.00 20 for £2	15 Thorn se	rvice manuals £3 ount rocker switch 250V/ £1.50
BB 103 10p BB 105A×12 £1 BB 105B×12 £1	TIP 42/BRC 6109 TIP 47 TIP 48 TIP 48 TIP 48 TIP 49 TIP 49 TIP 49 TIP 57 TIP 100 TIP 115 TIP 115 TIP 117 TIP 120 TIP 125 TIP 130 TIP 130 TIP 131 TIP 136 TIP 130 TIP 130 TIP 140 TIP 147 TIP 640 TIP 147 TIP 14	15K-20 turn pots Thorn panel 6×100 pot + changeover switch (Irish) Battery converter TA 75 for	20p 50p	W005 bridge G11 touch button red 6Meg filter	1	20 for £2 6 for £1 10 for £2.60	Pack of mix 25 LED red 20I/C Holde	ed coloured wire £1.00 //yellow/green £1.50 :rs £1.20
BB 105G×12 £1 BB 121a 10p BRC 83c13 10p	TIP 120 35p TIP 125 35p TIP 130 30p	colour TV. 12/24v Thorn 3787 Thorn 3500 2A cut out	£12 75p	BY210/600 BY298 3 amp/fast/R BD239		25 for £1.00 20 for £1.50 20 for £2.00	20 Large LI 20 Small LE 10×20 Turn	ED Red £1.00 ED Red £1.00
BZX 46c22 15p BZX 61 9-1 6p BZX 61c110 6p BZX 61c15 6p	TTP 131 30p TTP 136 30p TTP 140 50p	Stereo GEC amp 20 watt + pamp with 4 pots + mains por	pre-	MR856 BU126 BU205		25 for £1.50 10 for £6.00 10 for £8.00	100 Transist 20 Converge 100 Sticks	ence Pots 80p £1.00
BZX 61c20 10p BZX 61c30 10p BZX 61c220 10p	TIP 147 50p TIP 640 50p TIP 2955 35p	special offer	£6	BU105 2SC2122A BF458		10 for £6.00 10 for £8.00 10 for £1.00	10 Thermist 20 Slider Po 30 Presets	ors 50p
BZX 70c33 8p BZX 79c3v9, 4v7.	T 6032 30p T 6036 40p T 6040 40p	Decca-TTT etc. FEO4/1/250AC/4 Mains filters		BD136 BF224 OA90		10 for £1.25 20 for £1.40 40 for £1.00	15 VDR + etc. 40 glass ree	thermistors, degaussing, HT, £1.00 d switch
7v5, 11, 12, 30, 47 10p each	T 6052 .40n	(grey type) × 4		IN4148 IN4448 BYX10	1	40 for £1.00 40 for £1.00 00 for £4.00	10 press to 40 Pots 10 Gun Swi	make switch 70p £1.50 tches 50p
BZX 83c4v3 10p BZX 83c5v6 10p BZX 83c8v2 10p BZX 83b12 10p	T 9004 40p T 9005 40p	BRIDGES SKB 2/08 L5A KBL 005	30p 30p	KT3 multicaps 50 High voltage cera condensers	mic	10 for £7.50 £1.50	5 Tube Base 1,000 Diode Bandolier	s, Condensers, Resistors on £3.00
BZX 83b12 10p BZX 83c20 10p BZX 83c27 10p BZX 83c33 10p BZX 84c6v8×10 30p BZX 85c8v2 10p	ZTX 107 10p ZTX 108c 10p ZTX 109k 5p ZTX 213	KBL 02 KBP 04 W02	30p 30p 15p	Mixed Mounting Kit Transistors 300 Condensers	for Pow	50p £1.50	Lucky Dip 6 Jungle Bag 20 Knobs	5Kg £5.00 £1.00
BZY 88c0v7 10p	ŽTX 102c 10p ZTX 107 10p ZTX 108c 10p ZTX 109k 5p ZTX 213 5p ZTX 241 10p ZTX 342 10p ZTX 384 10p ZTX 384 10p ZTX 385 10p	W004 W005 GEC remote panel. Main	15p 20p	300 Resistors 150 Electrolytics	<u> </u>	£1.50 £2.00		6mm spindles for audio/TV\$3
BZY 8863V9 10p BZY 884V3 10p BZY 88 6V2 10p	ZTX 451 10p ZTX 550 10p VERY SPECIAL OFFER		£6		SE	NDZ		ONENTS
BZY 88c12 10p CV 8617 10p Wire 3300/50 Ends 25p	CVC 25/3 chassis with P.S. Lorit + Tripler (no modules) £15	transformer AT 2048/11 LOPTI	£10 2.50			TO O	RDER CK PAG	E

SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

10 011221		- DAORTAGE	
Thorn Spares		BY 223 BY 224/600 BY 226 BY 227 BY 227 BY 228 BY 229/400 BY 234 BY 237 BY 254	80p
9000 tube base and panel 9000 Front Panel	£1.50 £5	BY 224/600 BY 226	50p 15p
9000 Front Panel (remote)	£8	BY 227	15p
8800/9000 remote unit U705		BY 228 BY 229/400	20p 30p
receiver	£6	BY 234	10p
9000 Frame panel 9000 Cyclops panel	£8 £1.50	BY 237 BY 254	5p 10p
8000/8500 timebase panel	£8	BY 255	10p
8000/8500/9000 chroma pane		BY 298 BY 299	10p 10p
8500 convergence panel	£6	BY 406	8p
4000 Frame panel	£5	BY 527 BY 407a	20p 10p
4000 Power supply 1600 Mains lead, switch	£3	BY 602	10p
3500 6 push button + cable		F 247 XK 3102	10p 50p
form	£1.50	XK 3123	50p
T605 1vNPN T066 80v/6A 9000 Sound output panel	10p £1	Hitachi 2A/1500V metal case end	wire 20p
3500 Focus unit	£1.50	 	p
4000 thick film.		Line Transformers G8 Trans. Philips	£7.50
00\$1-012-E002	£1	G11 Split Diode	E12.00
00S1-012-0108 00S1-018D	£1 £1		E10.00 E10.00
3500 2amp thermal cutout	75p	Thorn B/W AD5308F + Stik	+
3500 IF panel	£2	Lead GEC 2040	£1.50 £5.00
3500 Frame panel	£4	GEC 2110	£7.00
3500 Video panel	£5 £5	Mullard AT 2036 Pye mono	£1.50 £3.00
3500 Line panel 3500 A1 Diode	20p	Rank mono T704A	£3.50
Export 3500 IF panel	£2	GEC Portable Line Trans.	£7.50 £3.00
Remote unit, 11ic, transforme relay + 5 volt unit		EHT Split Diode Leads	£1.00
IC board with set of SN74LS	£2 £1	EHT Cable/Metre	
4000 Tube base	£4	Triplers	03.00
3500 A1 pots 9000 Frame panel	50p £7	11 TEZ Rank G9 Philips	£3.00 £4.00
3 Way regulated adaptor 240\		GEC 2110	£4.00
6V/7.5/9V/300mA	£3.50	9000 Thorn	£6
Rank/Toshiba preh unit 0354	£9.50	9500 Thorn	£4.50
2 banks of 3 PB unit. Pye 731	£2	2040 GEC	£3.50
	£1.00	· ·	£2,00
6 Push button VHF/UHF for v/cap. GEC-Decca type	£7,00	•	£4.50
7 Push button for CVC5 ITT			£4.50
	£2.00		£3.50 £2.50
KT3 (Export) 12 P.B.u 6 Push button Unit Thoru	£2 £1,00	_	£3.00
6 Push button unit for GEC 20		_	£4.00
and ELC 1043/05 6 Push button unit PYE 713	£6.00	D22 for Pye 18" colour	
7 Lamps for P.B./Unit	10p	•	£4.00
Mains Droppers			£4.00 £3.25
Pye 731 3+56+27R	50p		£3,25
3500 Thorn 6/1/100 Thorn 50/17/1K5	60p £1.00	'	£3.00
120/20/20/48/117	£1.00	T/text ultrasonic rec'r panel £	
270/10/6 for Thorn 4000 18/320/70/39	50p £1,10	Video cassette lamps on lead.	
Thorn 50-40R-1K5	50p	12-14V. 50p or 3 for GEC 8 touch unit assy comple	£1,00 te
Ae Socket & Lead GEC, ITT, Philips, Pye	25p	with all I.C.'s + pots	£6.00
	each		£1.00
Rank Toshiba Tube Bases	30p		£2.00
Speakers 6×4G11 25 ohm	£1.00	G11 Transient Suppressors 245V 10 for	£1.00
5½×2½ 3 ohm 4	E1.00	G11 Scan Coils	£5.00
5×3 80 ohm 5×3 50 ohm	70р 50р	•	or £1
5×3 35 ohm	70p	•	£6.00
	80p [1.00	KT3 AE Sockets	25p
7×3 70 ohm	E1.00	NPN PNP 80V 6 Amp TO66 C Trans. pai	O.P. r 25p –
5×3 8 ohm 7×3 16 ohm	70p E1.00	5 button touch tuner BBC1/2	-
5" dia 16 ohm 1	E1.00	ITV1/2 video with ic SAS 560 570T	Γ/ £7.00
5" dia 8 ohm 1 6½" dia 4 ohm 1	E1.50 E1.50	Control panel 5 sliders + main	S
6 <u>≹</u> ″ dia 3 ohm £	£1.50		E1.50
2}" dia 8 ohm 3" dia 8 ohm 3" dia 15 ohm	75p 75p	G11 8 touch button unit replace old 6 P.B.U.	£20
3" dia 15 ohm	60p	Tube base + base unit for 820	
Diodes Diodes	10-	Euro chassis GEC Line O/P Trans. & Rec S	E4.00
BY 127 BY 133 BY 134 BY 176 BY 179	10p 10p		E3.00
BY 134 BY 176	10p	CVC 20/25/30/35/40 decoder	
BY 179	25p 40p	panel CVC 20/25/30/35/40 decoder	£10
BV 184	25p 10p	panel (untested)	£5
BY 187 BY 190 BY 196	40p	CVC 40/45 IF panel	£5
BY 196 BY 198	30p 10p	40K Transducer	50p
BY 198 BY 204/4 BY 206	8p	PHILIPS NE511N I LM337M Reg.	E1.20 30p
BY 206 BY 210/400 BY 210/600 BY 210/800	8p 5p		30p 11.00
BY 210/600	8р	G11 Line Driver Transformer	35p
BY 210/800	10p		
International Rectifier EHT Di			or 8p
6A/600V Stud Diodes 6A/1000V Stud Diodes	20p 20p	BTW 92/800R EHT Rectifier	£3
BTW 30/50	-2P		
	50p	wire ends 16Kv	10p
	50p	wire ends 16Kv 25A473 PNP C/P	10p 10p

Thorn 1613/1713 chassis	£9	.75	180/8KV 210/8KV
Hills 520 multimeter + case. 20, protected + logic test facility. 10:		50	1000/10KV 210/12KV
NEW MULLARD TELETEX	DISPLAYS		1000/12KV 1200/12KV
Decoder Panel (VM6230) £15.00 Panel 6101 £15.00	4040 Clock 7seg Red LED	£1 50p	
Panel 6330 £15,00	4 digit LCD 88:88	£1.00	Thorn 3500
G8 T/Unit Panel £12,00 G8 IF Panel £12,00	2 digit LED 8.8 2 digit LED ÷1.8 with panel	50p	175/100/100/3 KT3/200/25/2:
G8 Convergence Panel	MC14511	£1.00	47/220/350v
(late type) £12.00 G8 Line O/P Panel £12.00	4700/63 250/64	£1.50	150/150/100/1 2500/2500/63v
G8 Power Supply £12.00	3300/70	50p	470/470/250v 150/200/200/3
G8 IF & Chroma £15	.1/100	5p	400/400/200v 300/100/100/1
G11 IF Detector £3.00 Complete CVC 825 Chassis (both	1/100 × 10 4.7M/100	30p 5p	100/200/325v
panels) £40.00 AEC V/Cap Resistor Unit UHF	140/100 470/100	25p	150/150/100/3 300/300/100/3
with IC SA\$660 SA\$670 £3.00	2000/100	20p 70p	1500/2000/30v 400/200/200/3
Z714 RANK IF Panels 6MHz 1 I.C. SL437F £3.00	800/160 .1/250 Pulse	50p 5p	150/150/100/1 100/350 + 300
Z909B RANK 1F Panels Export 5.5MHz 2 I.C.'s	G11 0.47/250	10p	275v 300+300/300
TBA1205B TCA2705Q £2.50	2,2 250v 3n3/250 A.C.	10p 10p	225+25/380
Z743 RANK IF Panel Export 5.5MHz 3 I.C.'s	.39/250V	15p	200/100/100/3
TBA750+SC9504P+ SC9503P £1.50	4n7/250 tested 5KV 22/250	25p 15p	CMA 10
Pye G11 Front panel with transducer, pots, tuner pots, 6 pb	47/250	10p	CMA 11
switch+lead £5.00 GEC V/cap VHF/UHF tuner and	100/250 G11 470/250V	20p £1.75	CMA 30 CMA 40
IF+ sound O/P PC 706B3	500/250 GEC600/250	50p	CMC 10/2
(Export) £12.00 GEC Line O/P PC 659B3 £10.00	700/250	60p £1	CMC 16 CMC 38
GEC Power Supply (Export) £10.00	800/250 32/300	40p 20p	CMC 45 CMC 47
G11 dynamic correction panel £6	4/350	20р 5р	CMC 52 CMC 57
CVC 20 Front panel with sliders + mains input panel £4	8/350 12/300	8р 10р	CMC 10/2 CMC 16 CMC 38 CMC 45 CMC 47 CMC 52 CMC 57 CMC 58 CMC 59
CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp	600/300V	£1.50	CITICOI
assy + pots £14	4.7M/350v 16/350	10p 25p	CMC 67/2 CMC 68
CVC 5 Mains on/off + 5 pots £2 GEC Convergence panel £1	33/350	20p	CMD 12 CMD 32
Universal Focus. Fits Pye, Thorn and Decca Units.	50/350 220/350	10р 30р	CMD 33
Large Type 75p Decca Small 75p	300/350 22/375	40p 15p	CMD 40 CMD 41
KT3 Focus Unit 75p	220/385	75p	CMF 25 CMF 26
CVC 32 Focus Unit Focus Rod 25p	330/385 CVC 820HT 0.1/400	60p 15p	CMF 31
G11 focus £2.00 ITT Small for use with Split	KT3 E/W .39/400 .56K/400v	20p 20p	CMF 40 CMH 10
Diode 50p	8/400 33/400	15p 20p	CMH 31
TV11 50p Remo TV12SP 50p	400/400	40p	CMK 12 (untes CMK 30 (untes
TV13 50p TV14 50p	394K/400V 220/450	20p 40p	CMN 20
TV18 60p TV20 £1.00	0.1/600 .047/600	15p 15p	CMN 21 CMN 40
TV45 50p Thorn 14/1500 rec stick 5p	0.047/1000	10p	CMN 45 CMP 10
16 Button Key Pad 1 to 0 + * +	0.01/1000 0.1/1000	10p 10p	CMP 11
#+ 4 blank (Cherry) £3.00 Condensers	.15/1000 .47/250V A.C.	20p 10p	CMP 30 CMP 40
470/16 6p 1500/16 20p	.47/1000 .001K/1250	50p	CMS 11 CMS 40
3300/16 20p 10000/16 25p	0.0047/1500	10p	CMU 12
15000/16 50p	.005/1500 .0105/1500	10p 10p	CMU 14 CMU 30
47/25 5p	1n8/1500 2n0/1500	15p 10p	CMU 40 CMU 45
470/25 5p 680/25 5p	2n2/1500	15p	CMZ 30
1500/25 Radiai 10p 1500/25 10p	G11.11000/1500 .01/1600	15p 15p	GMA 90
3300/25 20p 4700/25 25p	G11.8200/2KV 0.1/2KV	15p 20p	GMC 120 GMR 64
5000/25 25p 470/35 6p	10n/2KV	15p	TMN 2 VCA 20
2200/35 25p	3n9/2KV 0.0015/2KV	15p 10p	VCA 21 VMC 26
220/40 5p	5n2/2KV 6n2/2KV	10p 15p	VMC 34
400/40 20p 1250/40 20p	20n/2KV 2n0/2KV	15p	VMC 44 + 45 VMC 51
1500/40 20p 2500/40 25p	2n2/2KV	15p 15p	Hai
1000/50 20p 1250/50 25p	7500pf/2KV 4n7/2KV	10p 15p	Transducer Han crystal, transduc
2000/50 20p 3000/50 25p	8n2/2KV 20n/2KV	15p 15p	lead
3300/50 25p 2.2/63 5p	0.0082/2500	15p	Thorn 4000 inse
15/63 5p	150/3500 1800/4KV	10p 5p	Decca RC 11 Decca RC 12
100/63 6p	4.7nf/5KV	10p	G11 Infra-red fu C11 Ultrasonic f
2200/63 50p Infra Red and Ultrasonic G11 Teletext	Decoder Panel	£30	G26c 674/02 an 66/02
RANK & ITT Mains Remote On-Off RANK & ITT Mains Remote Switch 2	Switch (720R) 865 ohm	£1.50 £1.50	Philips, 2 button Rank, Infra-red
RANK & ITT Remote Switch 2800 of G11 Mains Switch	ım	£1.50	Dynatron-Full re
4 amp Mains Switch GEC Mains Switch 4 amp		40p 25p	63, 64 Philips full remo 20C934; 7228/7
THORN Rotary Mains Switch		50p	797/IST 66K 18
G8 Mains Switch Mains Dropper PYE 3R5+15R+45R		75p 50p	G11, Full remot assy.
Thyristor 600/4 amp C106/2 G11 Preh Red LED P/Button for C.H.	Change	24p 20p	G11, Full remot (exchange unit)
RANK TOSHIBA Transductors TPC-2 CVC 5 Mains on/off	2011	50p	Philips infra red channel for 60 C
+250K+100K+500K+50K+500K Po Thorn 12 or 24 volt battery	ot on Panel convertor for portable c	£2.00 olour	Philips infra red channel for 60 C
T/V	£12.00 Pc		KT 3

170/8KV 180/8KV GEC portable chassis + LOPT 2114 New £4 Thorn 1613/1713 chassis £0.75 lulti-Caps /350v 25/385v £1.75 £1.00 60p £2,00 50p 70p £1.70 £1.50 40p £1.50 2,00 50p /100/100/320v 3v 300v 16/275v 375v 32/32/300v)v /350v /100/320v 00/200/100/16/ £2.00 £2.00 £1.00 70p £1.50 350v T Panels £2.00 £2.00 £2.00 £1.50 £5,00 £4,00 £8,00 £1,50 £1,50 £1,5 £6,00 £8,00 £3,75 £4,00 £4,00 £5,00 £5,00 £5,00 £2.00 £2.00 £1.50 £2.00 £1.50 £1.00 £4.00 £4.00 ested) ested) £1.50 £1.50 £1.00 25p £2.00 £2.00 £2.00 £2.00 £2.00 £10.00 £8.00 £7.00 £7.00 £5.00 £5.00 £5.00 £2.50 £5.00 £2.00 £10 £10,00 £3,00 £5,00 £4,00 £5,00 and Sets and Set Insert, ucer, SAA 1124 & £3,50 £5.00 £14.00 £14.00 I full teletext £19.00 c full teletext for and G22c c full reletext for and G22c and G22c and G22c and G26. The full relevant for a full relevant full remote fu

				SN76013ND £1.50	—
Tuner Units GEC or Hitachi 6 push button	CENID7	S. S.	AA1272 £3,00 AA1276 £3.00	SN76023N £1.50 SN76023N £1.50	Transistors A1222 15p A1223 15p
unit £12 ELC 1043/06 (AEG) £6	SENDZ COMPON		AA5000 £1.50 AA5000A £1.50	SN76115 50p SN76131 50p	AC121 15p
ELC1043/05 Mullard £6.00 ELC1043 (Ex Panel) £3.75	63 Bishopsteignton	, S.	AA5012 £3.50 AA5012A £4.00	SN76226 £1.00 SN76227 60p	AC151 15p
ELC1042 ,, £5.00	Shoeburyness, ESSEX SS SAME DAY SERVICE	S.	AA5020 £3.50	SN76228N £1.00	AC131 15p AC138 15p
ELC2000 ,, £7.00 ELC2004 £10.00	All items subject to availa	ability. Š	AA5030 £5.00 AA5040 £3.50	SN76270 £1.00 SN76532N 50p	AC152 15p AC153K 15p
ELC2006 £10.00 ELC2060 , £7.00	No Accounts : No Credit	Carus c	AA5040A £4.40 AA5050 £3.50	SN76544N £2.00 SN76545 £3.50	AC142K 15p AC169 15p
Mullard 1043/05 on panel £5.00 U322 (UHF) , £4.00	Postal Order/Cheque with Add 15% VAT, then £1 I	i oraer S	AF1039 £2.00 AS560 £1.00	SN76546 £1.00 SN76550 30p	AC176 15p
V314 (VHF) ,, £5.00	Add Postage for overs	BAS S	AS570 £1.00	SN76552 30p	AC176K 15p AC178K 15p
U341 UHF £7.00 ELC1043/05 Thorn £5.90	Callers: To shop at 212 Lon Southend. Tel. 0702-332		A5660 £1.00 AS670 £1.00	SN76570 £1.00 SN76620 50p	AC179 15p AC186 15p
Small V/Cap Mitsumi UHF , £4.00	Southend. Tel. 0702-332		AF1032P £2 L901B £4.40	SN76650 50p SN76660 40p	AC187K 15p AC188 15p
VHF " £3.00	THORN 1400 4P.B. Mech. Tuner BRC-M-2	00 40p <u>T</u>	A7122 £1.15 AA320A 50p	SN76620AN 50p SN76666 £1.00	AC188K 15n
Portable & rotary Tuners Sanyo & Mitsumi UHF £5.00	THORN 1500 4P.B. Mech. Tuner BRC-M-3 THORN 1590 4P.B. Mech. Tuner BRC 1330	75p T	`AA470 £1.50	SN76707N 75p	ACY18 20p ACY21 25p
NSF-UHF/VHF Varicap (old type) £10.00	THORN 3500 4P.B. Mech. Tuner BTT822 THORN 8000 4P.B. Mech. Tuner BTT6016	£1.20 T.	AA550 25 p AA570 75 p	SN76708AN 75p SN76720 £1.00	AD143 50p AD149 50p
Mosfit UHF/VHF (new type) £10.00	THORN 8500 4P.B. Mech. Tuner BTT6018/	ML237B £1.50	AA611 £1.50 AA621 £2.00	UA783P3C 40p BT100A/02 40p	AD161/162 pair 40p AF139 25p
SONY 1400KV Tuner unit £3.50 TV Sound tuner kit for sound on	postage each BTT6218	£1.50 T	AA661 £1.75 AA641 £1.50	BT109 £1.00 BT138/10A 70p	AF181 £1.00
your Hi Fi £9.50	Diodes BTT8224 1 Amp 1600v 7n CA270AB	£1.00 T.	`A7117 50 p	BT146 30p	AF239 25p AF367 25p
Thorn Tuner PANEL with 6×100K pots + cursors NO	3 Amp 100v 7p CA270CV	V 50p T	A7315AP 50p A7607AP 40p	TBA540Q £1.50 TCA270 £1.00	AL102 £1.75 BC161 30p
TUNER £1.00 U321 on panel ITT 40 £6.00	Delay Lines		A7609P 50p BA120A 40p	TCA270Q £1.00 TCA640 £1.00	BD138 30p BD229 20p
Tuner unit VHS Sylvania GTR Videon MTS 900 £2.50	DL20A 80p CA1310 DL600 £1.00 CA3065Q	50p T	BA120AS 50p BA120SA 40p	TCA660 £1.00 TCA270S £1.00	BD437/438 on
Thorn 3500 tuner panel with ELC	DL700 £1.00 CA3089Q	50p T	BA120B 40p	TCA270SQ £1.00 TCA740 £1.00	heat sink 60p BD507 50p
1043/05+pots £7.00 Mullard Video Modulator.	UDL11 30p CA3094A KT 3 Luminence 75p CA3146	1 1 1 T	BA120SB 40p BA120SQ £1.00	TCA800 £1.00	BD509 30p BD510 30p
Application, video tape recorders, TV cameras, video games, closed	MDL-CBL Min. 50p CD4510	50p T	BA120U 50p BA120C 40p	TCA830 £1.00 TCEP100 £2.25	BD517 30p BD519 30p
circuit T/V, C.C.I.R. system. Data	3.15 Fuses 4p CD4510 Co-Ax Joint 12n DM7492	50p T	BA1441 £1.00 BA231 75p	TCE120CQ £1.00 TDA440Q £1.00	BD534 30p BD535 30p
supplied. £10.00 VT 100 Sound Tuner Kit. TV.	Co-Ax Belling Lee Plug 12p HEF4001	10p T	BA395Q 50p BA396Q £1.00	TDA1003A £1.00 TDA1010 £1.00	BD544D 30p
Viosound. The latest design in low noise fitted with DNR, RF output	UHF Modulator CCIR £3.00 HEF4016	15p T	BA396 75p	TDA1060A £1.50	BD562 30p BD610 40p
and audio £30.00	Infra Red Emitting Diode 20p HEF40533 NE286H Small Neon Lamps M913	£2.00 T	BA440P £1.00 BA1440C £1.00	TDA1151 30p TDA1170 £1.00	BD646 50p BD676A 30p
Sylvania UHF VHF F6013 (Fits Rank) £6.00	GEC 5p M1024=S Mullard 5 Watt Amps. LP1162 M1025=S		BA480Q £1.00 BA510 £1.00	TDA1190 £1.00 TDA1327A £1.00	BD678 50 p
Sylvania F6003 £6.00 Sylvania UHF F4720B £6.00	New 75p MC476p MC1307	£1.00 T	BA510Q £1.00 BA520 £1.00	TDA1412 30p TDA2010 £1.00	BD807 20p
Sylvania VHF 900 £6.00	T.V. Tubes MC1330	75p T	BA530 £1.00	TDA2140 £3,50	BD948 30p BDX75 20p
Decca Bradford Tuner 5 Button £4.00	12" A31/300 Hitachi £12 MC1349 15" A38/170W Hitachi £8 MC1352	£1.0Ò T	BA540 £1.00 BA550Q £2.50	TDA2522 £1.00 TDA2532 £1.00	BDX32 £1.25 BF115 20p
Small Tuner DX 175-220MHz Auto Changeover £5.00	18" Hitachi Peal Tube £25 MC1358 MC14001		BA560CQ £1.00 BA570 £1.00	TDA2540 80p TDA2541 £1.00	BF121 20p BF127 20p
9000 Thorn Tuner on Panel £7.00 D.P.D.T. switch Black knob:	Integrated Circuits		BA625 50p BA641 £2.00	TDA2575A £1.00 TDA2581 £4.00	BF137 20p BF157 20p
Chassis or PCB mount 4p each or 40 for £1.00	AM25LS23PC 10p MC14016	25p T	BA651 £1.00 BA673 £1.00	TDA2590 £1.00 TDA2593 £1.00	BF160 20p
	MC14069	15p T	BA720A £1.00	TDA2560 50p	BF161 20p BF164 60p
BFT84	8p BC347 10p MC14514 MC1748 BC349b 10p MC14514	80p T	BA750Q £1.20 BA780 £1.50	TDA2600 £5.00 TDA2611 £1.00	BF179 30p BF180 20p
BFW11 20p 2SC2229 BFX29 30p 2SC7350	15p BC350 20p MCM2114 15p BC365 10p MEM4956		BA800 40 p BA810S 70 p	TDA2653 £1.00 TDA2002 £1.00	BF181 20p BF182 20p
BFX84 25p 2SD180 T BFY50 15p 6A	O3 80v/ BC384 10p ML231 15p BC394 10p ML232		BA820 70p BA890 £1.00	TDA2640 £2.00 TDA2680 £1.00	BF184 20p BF194 10p
BFY52 20p 2SD200	£2.00 BC413 10p ML236E	£1.50 T7	BA900 £1.20 BA920 £1.50	TDA2690 £1.00 TDA2593 £1.00	BF195 10p
BPW41 25p BC107	10p BC416 10p ML238B	£3.50 T	BA920Q £1.50	TDA3190 £1.00	BF196 10p BF197 12p
BRC116 40p BC108 BRX43 15p BC109	10p BC440 30p ML239 5p BC454 10p MM5387	£1.00 T	BA950 £1.00 BA990Q £1.00	TDA3500 £2.00 TDA3560 £3.50	BF198 10p BF199 10p
BRX48X 10p BC113 BRY56 30p BC114	10p BC455 10p MM5611 10p BC456 10p MM5840	96 70	MS1000NL £4.00 MS1943NL £2.00	TDA3571Q £1.50 TDA3950 £1.50	BF200 20p BF222 10p
BSS68 10p BC115 BSY79 10p BC116	10p BC462 23p N64100	£1.00 T	MS9980 £4.00 MS9901 £2.00	TDA9403 £3.00 SN74LS 125AN 30p	BF224 15p
BSY95a 10p BC117	20n BC478 10n NE555P	′′ 60p T	MS2716JL £2.00 MS3529 £2.00	SN74LS132 15p	BF238 20p BF240 16p
BSX19 17p BC125	10n BC532 10n IL-1	30p T?	MS4014 £1.50	SN16861 50p	BF244 40p BF245b 20p
BSX20 17p BC139 FT3055 30p BC141	10p BC546 10p OPT600 25p BC547 10p OPT601 25p BC548 10p SAA611	30p T?	X012 £5.00 MS9902 £3.00	SN16862AN £1.00 SN16964AN 50p	BF256 10p BF257 20p
TCE82 30p BC142 2N930 5p BC143	25n BC556 10p SAA661		PD2114C 4K RAM 00ns 75p	SN29764 £1.00 RGP30G 10p	BF257 20p BF258 25p BF259 25p
2N2221 8p BC147 2N2222 8p BC148	10p BC557 10p SAA1020	£4.00 U	ILN2216 75p N29848 50p	MPSA14 10p MPSA43 10p	BF262 15p
2N2906 10p BC149	10p BC559 10p SAA1024	£2.50 SN	N29770BN £1.00	MJ13005 30m l	BF263p 25p BF264 15p
2N3566 10p BC154	10p BCX31 25p SAA1025 10p BCX32 25p SAA1073	£3.00 SN	N29772BN £1.00	MJE51T 25p MJE340 28p	BF271 10p BF273 10p
2N3702 10p BC157a 2N3703 10p BC159	10p BCX32/36 pair 50p SAA1074 10p BD116 25p SAA1075	£3.00 SN	N74107 £1.00 N74167 70 p	MJE660 25p MJE661 25p	BF274 10p BF324 25p
2N3705 10p RC160	10n BD124 (metal) 600 SAA1130		N7472N 20° p N75108AN £1.00	МJE3055 £1.00 МJE2801 30р	BF355 30p BF362 20p
2N3583 2N3904 50p BC172 15p BC173	10p BD130Y 25p SAA1174 10p BD131 30p SAA1176	£3.00 SN	N76001 £1.00 N76003 £1.00	MJE2955 50p MJE13005 30p	BF363 15p
12N3906 15p DC124	10p BD132/238 30p SAA11/0 BD135 25p SAA1250	£3.00 SN	N76018 £1.00	Sanikron Diode	BF391 15p
2N4442 £1.00 BC182L 2N4444 £1.00 BC183	10p BD136 30p BD138 30p	 	N76008 £1.00	SKE2G2/04 30p	BF394 10p BF419 30p
2N5983 30p BC187	10p BD140 30p 10p BD175 30p 5-5MHz	15p	3 Pin Blue Thermistor (fits most sets) 20p	TV Crystals 4MHz	BF423 15p BF448 30p
1 2N6099 40p BC204	10p BD176 25p 6MHz 10p BD182 £1.00 BFU455K		BLY49 50p I.C. Heat Sink 20 for £1	4.433-619	BF450 20p BF458 30p
2N6130 500 PC212	10n BD183 70n	-	20×TO5 Heat Sink £1.00 CVC 9 power supply	6MHz 8.867238	BF459 30p
2N6348 20p BC214	10p BD204 60p 7	hyristors	board £1.50	Large or small	BF468 30p BF469 30p
2X 2N6099 on DC220	e_ BD222 300 RT106 Me	tal £1.20	CVC 20/2 mains panel £2.00	50p each GEC Power Panel	BF470 20p BF480 50p
2SA437 20p BC239 2SB407 Sanyo BC250	10p BD223 BD228 30p BT120 BD226 20p BPC4443	£1.00	FED4/1220/4 3 pin ITT 1. MFD 4 Amp Mains	TV106 Thermistor PT34 New £1,00	BF594 10p BF597 10p
1 TO3 10m (BC25)	10p BD233 30p BRC4443 10p BD235 30p G11 Thyris	75p stor 60p	Filters 50p ITT Mains Filter .1/250v/	1.07 INCH \$1.00	BF694 10p BF758 30p
2SB566 100 BC262	10p BD238 30p Decca 80-1 20p BD239 15p 2N4444	.00 60 p	CVC 20 to 45 chassis 50p Pots 10 k with Switch 25p		BF760 30p
2SC381 10p BC263b 2SC458 50p BC294 2SC515 10p BC298	30n BD243c 30n		Pots 47 k with Switch 25p		BFT34 15p
2SC515		hermistors	Mullard Surface Wave Filter RW 153P Colour	DIL – DIL	DIL – QIL
2SC828 10p BC303	30p BD252 20p VA1104 30p BD253B 50p ITTP72665 7p BD331 20p PTH451 A	312 15 p	TV Filter 40p Mullard Surface Wave	40 Pin × 4 42 Pin × 5 £1.00	16 Pin × 10 £1.00 18 Pin × 10 £1.00
2SC1172A 10p BC308	7p BD331 20p PTH451 A 7p BD332 20p PT37P Fits		Filter RW 154 Colour TV Filter 40p	28 Pin × 5 80p 16 Pin × 10 70p	28 Pin × 4 £1.00 8 Pin × 10 50p
2SC1311 200 BC327	10p BD373b 20p Degausing 10p BD416 25p most sets)	Thermistor (fits	G11 Line Scan P.C.B. £1.00	24 Pin × 5 75p 14 Pin × 10 70p	QUIL - QUIL
2SC1419 20p BC328 2SC1546 20p BC328/33/2 2SC1725 20p BC337	Pair 15p BD437 25p GEC Doul	ole Thermistor 75p	ELC 1042 P.C.B. 30p	18 Pin × 10 80p	16 Pin × 10 £1.00
2SC1725 2SC2068 20p BC337 BC338	10p BD439 50p BD501 30p				
	<u> </u>			_	