

Servicing Panasonic U3 Chassis Compact Disc Signal Decoding CCTV Fault Conditions • DX-TV Salora's Astra Receiver System VCR Clinic • TV Fault Finding Universal Response Curve A COMPLETELY NEW DIMENSION IN SOUND QUALITY!

728 DECODER **PROJECT KIT**

The Maplin NICAM 728 Decoder converts the additional digital code present* in the TV signal to a high quality stereo soundtrack with a quality similar to that of Compact Disc.

This fully working system is based upon the Toshiba NICAM chip set which has only just become available. For full introduction, text and illustrations plus an introductory article by the IBA, see the first part of our 3-part series in the October 1989 edition of Electronics - The Maplin Magazine (XA34M price £1.00). It's on sale from September 8th, so order your copy TODAY!

*Currently being transmitted from Crystal Palace and Emley Moor See the Maplin Magazine for IBA launch schedule. Upgrades almost any modern colour TV set no need to purchase a new TV set or VCR!

Features

★ Single +12V power requirement

switching (Mono-

★ British Design

XA00A at £6.00.

NICAM is not present ★ High Quality Optimum * Automatic audio Performance without

★ Reverts to FM audio if

- any additional ICs * NICAM mode
- Stereo-Bilingual) indicators



★ Kit available from November 1989 ★ Features IBA introductory article

British Digital Stereo Sound for **Television**

The World's most advanced high quality stereo system for landbased television!

TELEVISION ENGINEERS




This price available to trade only, ring 0702 552961 and quote LP02C special 5 off deal reference: Television.

Normal Price £99.95 (Inc. VAT) each (Order Code LP02C)

Initial availability limited - book your orders now!



All items subject to availability, all items will be on sale in our shops in Birmingham, Bristol, Leeds, Hammersmith, Edgware, Manchester, Nottingham, Southampton and Southend-on-Sea

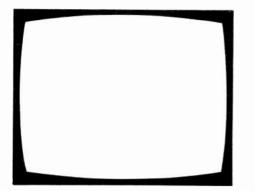



October 1989

Vol. 39, No. 12 Issue 468

Nick Beer

On sale September 20th

COPYRIGHT

© IPC Magazines Limited, 1989. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

INDEXES

Indexes to Vols. 36 and 37 are available at 80p each from the Editorial Office (address above).

SUBSCRIPTIONS

An annual subscription costs £20 in the UK, £24 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

BACK NUMBERS

Subject to availability, copies of issues published during the last 12 months are available at £1.80 each from Television, Vouchcheck Services, Unit 13, Thornham Grove, Stratford, London E15 1DN. Please make cheques/postal orders payable to IPC Magazines Ltd.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in Television, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. Correspondents should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to address the given above (see "correspondence").

this month

909 Leader

- **910** Servicing the Panasonic U3/U3W Chassis These sets were used in a wide range of popular models and have an established fault history. A thorough run-down on what you can expect.
- 915 Teletopics News, comment and developments.
- 916 VCR Clinic Reports from Philip Blundell, Eng., Tech., Ian Bowden, Eugene Trundle, Nick Beer, E. Shirt and Jeff Herbert.
- 918 Letters
- 919 Next Month in Television
- **921** Review: Salora's Astra Package Ian Bowden Details of Salora's latest satellite TV receiver package with notes on installation and performance.
- **923** The SEME-Panasonic Spares Operation Why major setmakers find it best to contract out the supply of spares and the system now in operation at SEME.
- 924 Servicing Compact Disc Players, Part 8 Joe Cieszynski How the off-disc digital signals are decoded, with specific reference to the Sony CX23035 chip, up to DA conversion. Including notes on fault diagnosis.
- 928 CCTV Faults Peter Graves Closed-circuit TV installations produce their own types of faults. An account of some unusual problems that have been experienced.
- **930** Servicing Salora Colour Receivers, Part 3 Nick Beer and Ian Bowden Operation of the Ipsalo-2 circuit with hints on fault tracing. Fault lists for the G and H chassis.
- 936 Long-distance Television Roger Bunney Reports on reception and conditions and news from abroad.
- 938 TV Fault Finding Reports from Philip Blundell, Eng. Tech., Alfred Damp, Ray MacDonald, J.S. Ruwala, J.K. Potts, Steve Leatherbarrow and J.R. Armagh.
- 942 The Universal Frequency Response Curve Stan Amos, B.Sc., C.Eng., M.I.E.E.

A universal frequency response curve that enables the effects of *RC* networks to be determined can be drawn. With a modifying factor it also applies where inductance is included.

- **944** A Day in the Life of ... Les Lawry-Johns A visit from SEME Stan and some more set difficulties.
- 945 Test Case 322

OUR NEXT ISSUE DATED NOVEMBER WILL BE PUBLISHED ON OCTOBER 18


TELEVISION OCTOBER 1989

			ي مد الحج									and the second sec
LINEAR IC'S — Cont. TEA.1002 6509 TLO-614 409 TLO-614 409 TLO-71 389 TLO-72 559 TLO-74 929 TLO-82 469 TLO-83 679 ULN-2003 699 ULN-2003 699 ULN-2003 699 ULN-2004 1709 ULN-2804 1709 ULN-2804 1709 ULN-2804 1709 ULN-2804 1709	25A.979 85p 25A.939 50p 25A.932 30p 25A.1006 120p 25A.1008 125p 25A.1008 125p 25A.1008 125p 25A.1011 1400p 25A.1015 30p 25A.1015 30p 25A.1016 40p 25A.1016 150p 25A.1018 150p 25A.105 150p	25C-1114 415p 25C-1116 280p 25C-1116 290p 25C-1116 10p 25C-1161 10p 25C-1162 35p 25C-1164 600p 25C-1217 360p 25C-1217 360p 25C-1217 360p 25C-1216 300p 25C-1216 300p 25C-1216 200p 25C-1216 200p 25C-1216 300p 25C-1216 300p 25C-1	25C-2228A 60p 25C-2229 25p 25C-2220 80p 25C-2223 80p 25C-2226 60p 25C-2227 600p 25C-2228 760p 25C-2228 120p 25C-2228 120p 25C-2227 80p 25C-2227 90p 25C-2227 90p 25C-2227 90p 25C-2227 120p 25C-2229 180p 25C-2229 180p 25C-2232 125p 25C-2234 125p 25C-2235 60p 25C-2235 60p 25C-2236 125p	2SC-3179 164 2SC-318 244 2SC-3209 12 2SC-3209 12 2SC-3212 510 2SC-3224 88 2SC-3264 58 2SC-3266 400 2SC-3266 400 2SC-3266 400 2SC-3266 30 2SC-3268 30 2SC-327 280 2SC-3298 122 2SC-3298 122 2SC-3298 122 2SC-3303 172	jp 2SD.792 zsD.741 2SD.754 zsD.741 2SD.755A zsD.741 2SD.755A zsD.741 2SD.755A zsD.741 2SD.755A zsD.741 2SD.755A zsD.741 2SD.811 zsD.742 2SD.811 zsD.742 2SD.822 zsD.742 2SD.836A zsD.822 2SD.836A zsD.836A 2SD.836A zsD.836A 2SD.836A zsD.836A 2SD.836A zsD.836A 2SD.836A zsD.836A 2SD.836A zsD.836A 2SD.841 zsD.836A 2SD.841 zsD.836A 2SD.841 zsD.8450 2SD.8450	80p 400p 100p 140p 450p 450p 450p 400p 100p 150p 200p 80p 200p 250p 260p 80p 80p	2SD-1609 2SD-1639 2SD-1649 2SD-1651 2SD-1666 2SD-1666 2SD-1666 2SD-1667 2SD-1668 2SD-1677 2SD-1783 2SD-1783 2SD-1815 2SD-1825 2SD-1846	210p 100p 260p 270p 120p 120p 120p 120p 120p 120p 100p 10	25D-1941 25D-1984 25J-49 25J-50 25J-77 25K-49 25K-55 25K-55 25K-134 25K-135 25K-135 25K-135 25K-135 25K-137 25K-312 25K-312 25K-313 25K-315 25K-35K-35K-35K-35K-35K-35K-35K-35K-35K-3	500 150 425 350 45 50 100 100 415 415 415 160 150 150 150 150 150 150 130 750 130 70 70 200	VIDEO HEADS JVC/AKAI/FERGUSON 3HSS (For all Models) NATIONAL PANASONIC 4HSS = 3HSSN (NV322, NV332, NV340, NV2000, NV201 NV8170, NV8200, NV8400, NV8600, NV8610, NV8620). AKAI VS-109/201/202/301/303	£14.00 £14.00 0. NV7000. £24.00
UPC-554 130p UPC-555 60p UPC-556H 80p UPC-566 60p	2SA-1103 200p 2SA-1104 200p 2SA-1105 250p 2SA-1106 250p	2SC-1312 40p 2SC-1317 25p 2SC-1318 25p	2SC-2307 500p 2SC-2308 40p 2SC-2312 300p	2SC-3316 280 2SC-3327 60 2SC-3331 40	p 2SD-858 p 2SD-863 p 2SD-864	250p 60p 200p	BRIDGE	RECTIFIERS	6		AMSTRAD	
UPC-571 220p UPC-574 60p UPC-575C2 90p UPC-576 200p	2SA-1111 120p 2SA-1112 150p 2SA-1123 70p	2SC-1325 400p 2SC-1327 20p 2SC-1328 40p 2SC-1342 120p	2SC-2314 70p 2SC-2320 40p 2SC-2324 120p 2SC-2329 480p	2SC-3333 120 2SC-3355 90 2SC-3356 120	p 2SD-866A 2SD-868	120p 140p 450p	W005 W01 W02	1A/50V 1A/100V		16p 18p	VCR 4500, 5200, 9000 VCR 7000	£19.50
UPC-577 64p UPC-580 300p UPC-595 95p UPC-595 190p UPC-596 190p UPC-1001 220p UPC-1018 170p UPC-1023 60p	2SA-1124 80p 2SA-1127 50p 2SA-1133 200p 2SA-1141 350p 2SA-1142 150p 2SA-1152 150p 2SA-1156 150p 2SA-1170 500p 2SA-1186 500p	25C-1342 120p 25C-1345 60p 25C-1358 350p 25C-1359 60p 25C-1383 35p 25C-1384 35p 25C-1393 35p 25C-1393 80p 25C-1398 70p	25C-233 150p 25C-233 200p 25C-2333 200p 25C-2335 120p 25C-2351 120p 25C-2351 120p 25C-2353 120p 25C-2353 120p 25C-2350 120p 25C-2361 150p	2SC-3358 80 2SC-3378 120 2SC-3393 80 2SC-3400 40 2SC-3402 500 2SC-3416 80 2SC-3417 90 2SC-3419 120 2SC-3410 120	p 2SD-871 p 2SD-879 p 2SD-880 p 2SD-882 p 2SD-882 p 2SD-882 p 2SD-892A p 2SD-894 p 2SD-894	400p 450p 60p 40p 80p 100p 120p 200p 200p	WO2 WO4 WO6 WO8 BR81D BR82D BR84D BR86D BR86D BR88D	1A/200V 1A/400V 1A/600V 2A/100V 2A/200V 2A/200V 2A/400V 2A/600V 2A/600V		19p 21p 23p 28p 33p 33p 37p 43p	FERGUSON 3V32/JVC HR7655 3V42/44/45/46/47	£38.00 £21.00
UPC-1025 230p UPC-1026 95p UPC-1028 90p UPC- 1031H2 180p UPC-1032 60p UPC-1158H2 70p UPC- 1152C1 130c	2SA-1198 70p 2SA-1206 100p 2SA-1208 70p 2SA-1208 100p 2SA-1210 120p 2SA-1210 120p 2SA-1202 120p 2SA-1202 120p 2SA-1262 160p 2SA-1263 280p 2SA-1264 280p	25C-1403 500p 25C-1403 500p 25C-1407 550p 25C-1413 240p 25C-1413 240p 25C-1414 150p 25C-1424 450p 25C-1448 100p 25C-1448 100p 25C-1449 120p 25C-1450 200p	2SC-2362 50p 2SC-2369 100p 2SC-2371 45p 2SC-2373 210p 2SC-2373 210p 2SC-2407 110p 2SC-2408 120p 2SC-2412K 50p 2SC-2412K 50p 2SC-2413 50p 2SC-2458 40p	2SC-3422 110 2SC-3457 200 2SC-3457 200 2SC-3457 250 2SC-3457 250 2SC-3459 250 2SC-3461 400 2SC-3466 350 2SC-3467 70 2SC-3482 300	P 2SD-900 P 2SD-905 P 2SD-916 P 2SD-917 P 2SD-921 P 2SD-923 P 2SD-946 P 2SD-947 P 2SD-950	400p 600p 130p 300p 320p 360p 120p 100p 300p 350p	BR32 BR34 BR36 BR62 BR64 BR251 BR252 BR254 BR256	3A/200V 3A/400V 3A/600V 6A/200V 6A/400V 25A/100V 25A/200V 25A/200V		43p 43c 43c 44c 80p 72p 150c 165c 185c	FISHER FVHP510/520/530/615/620/622/710/715/ 722910 FISHER VBS 7100/VBS 7500	£20.75 £29.00
UPC-1182 110p UPC-1183 200p UPC- 1185H2 230p UPC-1186 80p UPC-1186 80p UPC-1187 150p UPC-1188H 400p	2SA-1265 280p 2SA-1290 150p 2SA-1294 450p 2SA-1295 500p 2SA-1301 350p 2SA-1301 350p 2SA-1307 160p 2SA-1317 30p	2SC-1450 200p 2SC-1454 320p 2SC-1472 40p 2SC-1473 70p 2SC-1474 125p 2SC-1475 60p 2SC-1505 80p. 2SC-1507 140p	2SC-2459 50p 2SC-2459 50p 2SC-2470 65p 2SC-2481 120p 2SC-2482 40p 2SC-2483 120p 2SC-2483 4240p 2SC-2509 80p 2SC-2519 80p	2SC-3502 120 2SC-3503 90 2SC-3504 120 2SC-3504 100 2SC-3568 200 2SC-3583 170 2SC-3595 220 2SC-3605 60	P 2SD-967A P 2SD-958 P 2SD-965 P 2SD-970 P 2SD-973 P 2SD-973A P 2SD-985	350p 520p 60p 100p 170p 60p 70p 120p 120p	BR256 BR258 BR351 BR352 BR354 BR356 BR356 BR358 BY164	25A/600V 25A/800V 35A/100V 35A/200V 35A/400V 35A/600V 35A/600V 1.5A/100V		200p 240p 185p 200p 225p 230p 260p 40p	FISHER VBS 9000/VBS 9900 FISHER VBS 7000	£29.00 £30.00
UPC:1200 325p UPC:1222 130p UPC:1230 210p UPC:1238 120p UPC:1253 120p UPC:1277 240p UPC:1377 240p UPC:1350 115p UPC:1350 115p UPC:1353 180p UPC:1363 190p	2SA-1318 30p 2SA-1329 200p 2SA-1346 30p 2SA-1352 100p 2SA-1355 100p 2SA-1356 100p 2SA-1370 100p 2SA-1371 100p 2SA-1380 100p 2SA-1371 100p 2SA-1380 100p 2SA-1380 100p 2SA-1386 400p 2SA-1386 400p	2SC-1509 45p 2SC-1514 65p 2SC-1515 60p 2SC-1520 120p 2SC-1541 110p 2SC-1545 120p 2SC-1545 140p 2SC-1569 140p 2SC-1570 30p 2SC-1583 30p	25C-2527 300p 25C-2545 55p 25C-2547 65p 25C-2550 70p 25C-2551 70p 25C-2552 150p 25C-2553 150p 25C-2555 150p 25C-2562 90p 25C-2564 260p	2SC-3631 130 2SC-3636 280 2SC-3657 400 2SC-3675 160 2SC-3678 280 2SC-3679 200 2SC-3679 200 2SC-3679 200 2SC-3679 200 2SC-3715 480 2SC-3717 120 2SC-3719 150 2SC-3746 120	P 2SD-1012 P 2SD-1021 P 2SD-1022 P 2SD-1024 P 2SD-1031 P 2SD-1051 P 2SD-1061 P 2SD-1061 P 2SD-1061 P 2SD-1061 P 2SD-1071 P 2SD-1073	120p 120p 400p 130p 200p 130p 200p 130p 250p 450p 350p	BY179 TRIACS TIC206D TIC225D TIC226D TIC226D TIC236D	- 4A/400V - 6A/400V - 6A/400V - 8A/400V		40μ 40μ 60p 69p 68μ 85μ	VT11/14/33/61/63 HITACHI VT19 HITACHI VT19 HITACHI VT120, VT 220 HITACHI VT3000 HITACHI VT3000 HITACHI VT5000, VT 5500 HITACHI VT500, 8000, 8300, 8500, 8 VT9500, 9700	£20.00 £38.00 £38.00 £31.50 £14.00 £20.00 700, 9300, £20.00
UPC-1368H 425p UPC-1373 85p UPC-1378 210p		2SC-1586 540p	2SC-2568 120p 2SC-2570 60p 2SC-2577 125p 2SC-2578 220p 2SC-2579 130p 2SC-2579 240p	2SC-3747 120 2SC-3789 75 2SC-3790 120 2SC-3795 200	2SD 1111 2SD 1128 2SD 1128 2SD 1135	520p 60p 200p 150p	TIC246D TIC253D TIC263D T2800D			105p; 190p; 205p;	NATIONAL	
UPC-1334 1700 UPC-1334 1700 UPC-1337 4500 UPC-1403CA 7500 UPC-1403C 5000 UPC-1403C 4000 UPC-1500C 4000 UPC-1500C 4000 UPC-1500C 4000 UPC-1525C 4000 UPC-1525	258.324 55p 258.370 45p 258.546 70p 258.560 35p 258.560 35p 258.561 50p 258.562 35p 258.566 110p 258.595 80p 258.595 60p 258.647 30p 258.648 55p 258.649 40p 258.649 40p 258.649 20p 258.703 259 258.703 20p	23C-1027 50p 2SC-1675 200p 2SC-1675 200p 2SC-1684 45p 2SC-1684 45p 2SC-1885 60p 2SC-1730 40p 2SC-1730 40p 2SC-1734 45p 2SC-1741 45p 2SC-1741 45p 2SC-1755 90p 2SC-1755 90p 2SC-1756 40p 2SC-1758 30p	2SC-2579 130p 2SC-2580 240p 2SC-2580 240p 2SC-2581 140p 2SC-2581 140p 2SC-2681 40p 2SC-2681 40p 2SC-2681 45p 2SC-2681 45p 2SC-2681 45p 2SC-2681 45p 2SC-2685 450p 2SC-2685 450p 2SC-2685 550p 2SC-2685 550p 2SC-2686 150p	2SC 3798 220 2SC 3811 80, 2SC 3813 200 2SC 3855 280, 2SC 3855 280, 2SC 3823 280, 2SC 3823 280, 2SC 3823 280, 2SC 4222 260, 2SD 422 260, 2SD 425 280, 2SD 425 280, 2SD 425 280, 2SD 425 280, 2SD 425 480, 2SD 48	 250-1159 250-1160 250-1160 250-11634 250-1164 250-1168 250-1188 250-1188 250-1188 250-1188 250-1189 250-1189 250-1189 250-1196 250-120 250-1211 250-1221 250-1229 250-1229 250-1239 250-1248 	80p 90p 150p	THYRIST (SCR's) 2N:5061 2N:5062 2N:5064 C106D TIC116C TIC116C TIC116D TIC126M ZN:4444 BR103 BR303			52μ 20μ 28μ 29μ 28μ 59μ 70μ 75μ 75μ 75μ 75μ 75μ 37μ	NV 777/NV 330 NV 430/NV 460 NV 730 4 HEAD NV 366 4 HEAD NV 360 PORTABLE 4 HEAD NV 370/NV 380 NV 782/NV 810 NV 650/NV 810 NVG 50 NVG 30 NVG 33, NVG 45, NVG 46 NVG 400	£26.50 £21.00 £30.50 £41.00 £43.50 £43.50 £43.50 £41.50 £41.50 £41.00 £41.00 £42.00
2N.427 560p 2N.428 425p 2N.428 425p 2N.428 425p 2N.435 340p 2N.448 510p 2N.448 510p 2N.448 510p 2N.448 510p 2N.434 9100 2N.434 920p 2N.434 920p 2N.434 920p 2N.434 920p 2N.433 35p 2S.450 120p 2S.450 120p 2S.450 120p 2S.450 150p	25B-718 70p 25B-727 200p 25B-754 80p 25B-754 80p 25B-757 45p 25B-775 160p 25B-775 160p 25B-775 160p 25B-775 160p 25B-785 60p 25B-825 135p 25B-825 135p 25B-826 180p 25B-826 180p 25B-826 190p 25B-1077 190p	25C-1819 140p 25C-1826 60p 25C-1826 20p 25C-1846 100p 25C-1846 100p 25C-1846 100p 25C-1846 100p 25C-1846 100p 25C-1847 20p 25C-1870 700p 25C-1804 125p 25C-1904 125p 25C-1904 30p 25C-1907 75p 25C-1907 250p 25C-1913 190p 25C-1913 190p	25C-2681 2705 25C-2682 1205 25C-2680 1205 25C-2690 1205 25C-2705 705 25C-2705 705 25C-2719 805 25C-2719 805 25C-2721 1205 25C-2740 4505 25C-2740 4505 25C-2740 4505 25C-2741 4005 25C-2745 4005 25C-2745 605 25C-2745 605 25C-2745 5505 25C-2742 5505	25D-356 400 25D-356 400 25D-371 2400 25D-380 6500 25D-388 800 25D-388 1700 25D-388 900 25D-388 900 25D-380 900 25D-400 200 25D-415 1200 25D-426 1500 25D-427 3500 25D-428 450 25D-427 3500 25D-438 250 25D-437 3500 25D-447 4000 25D-428 250 25D-437 3500 25D-437 350 25D-437 350 25D-437 350 25D-437 350 25D-525 700	 25D-1266 25D-1272 25D-1273 25D-1273 25D-1275 25D-1276 25D-1276 25D-1277 25D-1279 25D-1281 25D-1282 25D-1292 25D-1309 25D-1310 25D-1310 25D-13128 25D-1328 25D-1328 25D-1328 25D-1328 25D-1348 	180p 200p 100p 160p 200p 190p 600p 300p 400p 425p 140p 140p 140p 70p 85p 150p	BT106 BT116 BT117 BT119 OT121 TIC44 TIC45 TIC47 T7088 17089 17127 15/80H 15/858 SG613	*		85p 180p 80p 100p 22p 27p 32p 200p 200p 200p 230p 850p * * *	SANYO VTC 5000, VTC 5400, VTC 6000, VTC 6500 VTCM10/11/20/21/25/30/31/35/40/50 VTC 5100, VTC 5150, VTC 5300 VTC 5550 VTC 5550 VTC 5500, VTC 9150, VTC 5300 VTC 9100/3300/9455/9500 VTC 930/9355 VTC 9500	£28.00 £28.00 £28.00 £28.00 £30.50 £30.50 £30.50
2SA-606 300p 2SA-608 15p 2SA-634 50p	2SC-382 120p 2SC-388A 60p 2SC-454 45p	2SC-1944 350b	2SC-2812 40p 2SC-2814 40p 2SC-2834 400p 2SC-2834 400p 2SC-2837 360p	2SD-526 70p 2SD-545 60p 2SO-549 120p 2SD-551 400p	2SD 1376 2SD 1379 2SD-1380 2SD-1383	125p 100p 100p 100p	* U322LO * U341 * U342 * * * *			600p * 500p * 500p *	SHARP	-
25A-640 60p 1 25A-673 20p 1 25A-684 60p 2 25A-699 100p 2 25A-708 300p 2 25A-715 80p 2 25A-720 20p 2 25A-726 80p 2 25A-726 25p 2 25A-733 30p 2	2SC 460 10p 2SC-461 30p 2SC-515A 100p 2SC-535 50p 2SC-563 20p 2SC-563 120p 2SC-664 25p 2SC-663 120p 2SC-663 120p 2SC-664 25p 2SC-684 300p 2SC-684 340p	2SC-1946 1500p 2SC-1947 450p 2SC-1957 70p 2SC-1959 20p 2SC-1969 160p 2SC-1969 160p 2SC-1970 200p 2SC-1971 400p 2SC-1972 600p 2SC-1973 150p 2SC-1983 130p	2SC-2853 70p 2SC-2876 120p 2SC-2877 120p 2SC-2878 40p 2SC-2878 40p 2SC-2878 40p 2SC-2879 120p 2SC-2817 120p 2SC-2911 120p 2SC-2912 120p 2SC-2928 550p	2SD-555 500p 2SD-560 150p 2SD-571 80p 2SD-575 530p 2SD-600 80p 2SD-601 40p 2SD-601 40p 2SD-602 60p 2SD-612 100p 2SD-613 70p 2SD-636 30p 2SD-637 40p	2SD-1390 2SD-1391 2SD-1391 2SD-1395 2SD-1395 2SD-1396 2SD-1398 2SD-1398 2SD-1400 2SD-1400 2SD-1406	350p 450p 150p 240p 250p 210p 300p 280p 280p 280p	VIDEO LA UNIVERSAL V 12V 60 mA (3) RED OR BLUE	(IDEO LAMPS 00mm WIRES)			VC 381, VC 383, VC 386, VC 387, VC 388, VC 483 VC 483, VC 3300, VC 8381, VC 9100, VC 9300, VC 9500, VC 9700, VC 582, VC 583, VC 651, VC 681, VC 781	£19.00
2SA-798 55p 2 2SA-748 90p 2 2SA-769 130p 2	2SC-710 20p 2 SC-711 40p 2 SC-730 450p 2	2SC-1985 120p 2SC-1986 160p 2SC-2001 60p	2SC-2944 620p 2SC-2979 320p 2SC-2988 280p	2SD-638 60p 2SD-639 60p 2SD-640 350p 2SD-642 50p	2SD-1409 2SD-1415 2SD-1425	160р 190р 190р 430р	CASSETT	E DC MOTO	ORS	1	SONY	
2SA-771 130p 2 2SA-781 150p 2 2SA-798 55p 2 2SA-814 170p 2 2SA-814 30p 2 2SA-872 40p 2 2SA-872 40p 2	ISC-733 25p 2 ISC-761 150p 2 ISC-762 150p 2 ISC-783 105p 2 ISC-790 80p 2 ISC-792 380p 2 ISC-828 25p 2	25C-2003 25p 25C-2004 60p 25C-2021 40p 25C-2022 200p 25C-2023 180p 25C-2026 60p 25C-2027 450p	2SC-3012 300p 2SC-3019 320p 2SC-3025 550p 2SC-3039 140p 2SC-3040 260p 2SC-3042 300p	2SD-655 60 p 2SD-661 60 p 2SD-666 70 p 2SD-667 70 p 2SD-668 120 p 2SD-668 40 p 2SD-669 40 p 2SD-673 350 p 2SD-676 250 p	2SD-1427 2SO-1428 2SD-1429 2SD-1430 2SD-1431 2SD-1431 2SD-1432 2SD 1433	350p 380p 450p 410p 280p 400p 600p 750p	6V 9V 12V CW 12V CCW 13.2V CW 13.2V CCW			240p 240p 240p 240p 240p 290p -	DSR-335R (FOR C20, 30, 40 SLF1, SLF1E) DSR-43R (FOR SLC7 RANGE SL 5000, SL 5100, SL 3000)	SLF1UB, £19.00 £16.50
2SA-899 60p 2 2SA-907 650p 2 2SA-907 700p 2 2SA-913 200p 2 2SA-916 30p 2 2SA-921 50p 2 2SA-921 50p 2 2SA-933 40p 2	SC-839 25p 2 SC-867A 150p 2 SC-930 20p 2 SC-941 25p 2 SC-943 160p 2 SC-943 160p 2 SC-945 20p 2	2SC-2029 120p 2SC-2053 120p 2SC-2055 150p 2SC-2056 450p 2SC-2058 40p 2SC-2060 60p 2SC-2071 140p	2SC-3057 150p 2SC-3068 60p 2SC-3070 120p 2SC-3077 120p 2SC-3114 40p 2SC-3117 120p 2SC-3118 100p 2SC-3148 410p	2SD-716 115p 2SD-717 180p 2SD-718 100p 2SD-722 240p 2SD-725 400p 2SD-734 60p 2SD-741 120p 2SD-743 130p 2SD-756 100p	2SD-1439 2SD-1441 2SD-1448 2SD-1450 2SD-1450 2SD-1451 2SD-1453 2SD-1455 2SD-1457	140p 320p 440p 140p 260p 260p 170p 320p 220p	* * * * MONO HEAD			* * * *	705HIBA /21/V9600	£22.00
25A-935 40p 2 25A-939 40p 2 25A-939 140p 2 25A-940 50p 2 25A-940 50p 2 25A-940 50p 2 25A-940 50p 2 25A-950 60p 2 25A-954 75p 2 25A-954 70p 2 25A-956 60p 2 25A-956 70p 2 25A-956 70p 2 25A-956 70p 2 25A-956 70p 2 25A-966 70p 2 25A-968 70p 2	SC 982 60 m 2 SC 983 120 p 2 SC-1000 60 p 2 SC-1012 75 p 2 SC-1013 140 p 2 SC-1014 140 p 2 SC-1030 190 p 2 SC-1046 60 p 2 SC-1050 280 p 2 SC-1060 90 p 2 SC-1061 85 p 2 SC-1070 65 p 2 SC-1070 65 p 2 SC-1070 65 p 2	SC-2073 70p SSC-2075 80p SSC-2078 95p SSC-2078 95p SSC-2081 950p SSC-2085 100p SSC-2086 60p SSC-2131 50p SSC-2131 50p SSC-2131 50p SSC-2131 50p SSC-2136 80p SSC-2168 175p SSC-2186 600p	25C-3149 180p 25C-3150 200p 25C-3151 230p 25C-3152 250p 25C-3153 320p 25C-3154 400p 25C-3155 200p 25C-3156 400p 25C-3157 200p 25C-3158 200p 25C-3159 200p 25C-3159 200p 25C-3173 180p 25C-3173 340p	325736 100 3250-757 120p 3250-758 140p 3250-763 140p 3250-763 140p 3250-763 140p 3250-763 140p 3250-763 140p 3250-763 140p 3250-773 40p 3250-777 40p 3250-777 40p 3250-786 100p 3250-786 100p 320-788 100p	2SD-1459 2SD-1468 2SD-1468 2SD-1496 2SD-1505 2SD-1554 2SD-1555 2SD-1576 2SD-1577 2SD-1577 2SD-1579 2SD-1591 2SD-1595	220p 60p 150p 150p 120p 500p 150p 150p 150p 150p 150p 150p 160p 200p	STEREO HEAD MINI HEAD AUTO REVERS * * * * UNIVERSAL T SONY ON/OFF PHILIPS SWIT K30, K35, K4 * * *	SE HEAD * * * * RIPLERS = SWITCHES CHES	* * * *	50p 230p 260p 260p 200p 150p * * *	GRANDATA LT For Address & Ph Please turn over	ONE

÷,

VCR	FERGUSON	VIDEO MOTORS	4000B SERIES CMOS IC's	7400 280 7	4HC251 25p 74LS114 28p 4HC253 35p 74LS122 35p	8255 200p 75188 55p 8256 1200p 75189 55p
PINCHROLLERS		AMSTRAD	4000 13p 4001 13p	7401 16p 7. 7402 180 7.	4HC257 40p 74LS123 35p 4HC258 50p 74LS124 85p	8257 220p 75195 185p 8259 280p 75451 40p
AKAI	3292, 3V00, 3V01150 3V16, 3V22, 3V2365	VCR-7000 REEL MOTOR1700	4002 13p 4006 34p	7403 20p 7	V4HC259 52p 74LS125 30p V4HC273 42p 74LS126 30p	8271 3400p 75454 65p 8272 1200p 75492 55p
V\$9300, V\$9500, V\$9700, V\$9800 280p	3V29/30120 3V31/3285	FERGUSON & JVC	4007 13p	7405 10p 7	4HC279 35p 74LS132 30p 4HC280 61p 74LS133 30p	8279 270p 8T26 95p 8282 300p 8T28 110p
VS1, VS2, VS3, VS4, VS5, VS6,	3V35/3680 3V38-3980	CAPSTAN MOTOR2100 PU-45979	4008 38p 4009 20p	7407 36p 7	4HC283 61p 74LS136 30p 4HC298 50p 74LS138 28p 4HC299 105p 74LS139 28p	8283 400p
VS9, VS10 360p AMSTRAD	3V42/4365	CAPSTAN MOTOR1950 PU-55371V	4010 21p 4011 13p	7409 20 7	4HC354 38p 74LS145 65p 4HC356 48p 74LS147 90p	8284 440p 8287 360p OPTO
VCR4500, VCR4600, VCR4600	3V44/4565 3V45/5465	DRUM MOTOR1950 PU-46414	4012 13p 4013 19p	7414 45p 7	74HC365 34p 74LS148 75p 74HC366 36p 74LS151 27p	8288 650p COUPLERS 8748 1100p
Mk2, VCR4700 280p VCR5200 360p	3V5565	REEL MOTOR2650 PU-51381V2650	4014 32p 4016 18p	7417 32p 7	74HC367 36p 74LS153 31p 74HC368 36p 74LS154 78p 74HC373 46p 74LS155 36p	8755 1400p AY3-1015 290p
VCR7000 360p	FISHER	NATIONAL	4017 29p 4018 30p	7421 250 7	74HC374 48p 74LS156 36p 74HC375 52p 74LS157 22p	SP0256AL2 500p 4N25 50p Z80ACPU 150p 4N26 50p
FERGUSON	rionea	REEL MOTOR1350	4019 28p 4020 33p	7430 25 p 7	74HC377 52p 74LS158 27p 74HC386 20p 74LS160 38p	Z80BCPU 400p 4N27 50p Z80ADMA 500p 4N28 50p
3V00, 3V16, 3V22, 3V23 280p 3V29-30, 3V31-32 280p	VBS-7000245	MYN-135V5L FOR NV333, NV366	4021 36p 4022 36p	7438 32p 7	74HC390 50p 74LS161 38p 74HC393 47p 74LS162 38p 74HC423 65p 74LS163 36p	Z80AP10 220p 4N29 50p Z80BP10 340p 4N30 90p
3V35-36, 3V38-39, 3V42-43, 3V44-45, 3V48, 280p	VBS-9000120	SANYO	4023 13p	7447 600p 7	74HC533 65p 74LS164 36p	Z80ACTC 200p 4N31 90p
3V53, 3V54-55, 3V56-57, 3V58-59,		REEL MOTOR700 4-529V-10800	4024 25p 4025 13p	7451 10p 7	74HC540 70p 74LS166 55p 74HC541 70p 74LS168 60p	Z80AS10 460p 4N33 100p
3V64-65, FV10-11, FV12-14 HITACHI	HITACHI	SHARP	4026 60p 4027 18p	7470 300 7 7473 250 7	74HC563 60p 74LS169 55p 74HC564 60p 74LS170 68p	Z80AS10-1 580p 4N36 58p Z80BP10-2 580p 4N37 58p
VT11, VT33 280p	VT-11, VT-33100	REEL MOTOR1500	4028 29p 4029 34p	7474 35p 7	74HC573 68p 74LS174 30p 74HC574 65p 74LS175 32p 74HC574 65p 74LS175 32p	Z80ADART 500p 4N38 58p 74S289 180p
VT61-62, VT63-64, VT65,	VT-5000120 VT-5500130	RMTOV 1008 GEZZ	4030 17p 4031 90p	7481 900p 7	74HC583 90p 74LS190 47p 74HC595 85p 74LS191 43p 74HC597 80p 74LS192 41p	74S387 200p 75107 65p http picture avec
VT110-122, VT120-128, VT130-135,	VT-800060 VT-850060	CAPSTAN MOTOR700	4032 52p 4033 60p	7485 23p 7 7486 28p 7	74HC620 110p 74LS193 41p 74HC623 110p 74LS194 41p	75110 75p 75113 100p
VT138-150, VT168,-220 VT5000, VT8000, VT9300,	VT-930050 VT-950050	A-6751131A FOR SLC6 CAPSTAN MOTOR2500	4034 76p 4035 42p	7490 35p 2	74HC640 90p 74LS195 44p 74HC643 90p 74LS196 45p	75122 110p 75150 95p MAN.72 115p
VT9500 280p	VT-950050 VT-970060	BHF 1100D FOR SLC7	4036 180p 4037 75p	7492 45p 7493 35p 7	74HC646 120p 74LS197 42p 74HC648 120p 74LS221 45p 74HC651 100p 74LS240 45p	75154 100p MAN.74 115p 75162 700p MAN.4640 180p
JVC HR3300, HR3330, HR3360,			4038 46p 4039 180p 4040 30p	7495 400 7 7497 800 7	74HC652 100p 74LS241 42p 74HC670 75p 74LS242 43p	75182 95p MAN.8910 230p 75183 95p DL.747 160p
HR3660, HR4100, HR7700 280p	JVC	VIDEO LAMPS UNIVERSAL30 12V60mA (300mm WIRES)	4040 30p 4041 36p 4042 30p	74107 340p 7 74111 52p 7	74HC688 80p 74LS243 50p 74HC690 110p 74LS244 40p	
HR7200, HR7330, HR7660, HR7610, HR7650, HR7655 280p	HR-3300, HR-3330,150	PANASONIC VIDEO LAMPS60	4042 30p 4043 36p 4044 36p	74119 85p	74HC691 110p 74LS245 40p 74HC4002 25p 74LS247 40p 74HC4015 85p 74LS248 40p	
HRD110, HRD111, HRD120, HRD121, HRD140, HRD150 280p	HR-3360, HR-3660, HR-4100180	IDLERS & PULLEYS REPLACEMENTS	4044 36p 4045 72p 4046 42p	74123 200p	74HC4016 75p 74LS249 70p 74HC4017 48p 74LS251 24p	
HRD160, HRD225, HRD455, HRD565, HRD725	HR-720070	HITACHI	4046 42p 4047 45p 4048 27p	74125 446p 74126 45p	74HC4020 50p 74LS253 36p 74HC4022 40p 74LS256 52p	SOLDERING IRON
MITSUBISHI	HR-760080 HR-761095	FF REW IDLER	4046 27p 4049 18p 4050 20p	74141 55p	74HC4024 34p 74LS257 32p 74HC4028 40p 74LS258 35p 74HC4040 34p 74LS259 50p	ANTEX XS25W 240V Soldering Iron 240Vac 540p
HS200, HS300, HS301, HS302,	HR-765075 HR-765590	6886971 190p PLAY IDLER	4050 20p 4051 38p 4052 35p	74153 450	74HC4040 34p 74LS259 50p 74HC4049 38p 74LS260 30p 74HC4050 38p 74LS266 22p	Spare Element for XS25W 240V 260p ANTEX C15W 240V Soldering Iron
HS303, HS304, HS310, 280p HS320, HS700	HR-770077 HRD-110, HRD-111,100	V-6861482 320p	4053 35p 4054 53p	74157 45p	74HC4051 85p 74LS273 44p 74HC4052 85p 74LS279 33p	240Vcm 540p
NATIONAL	HRD-120, HRD-225 HRD-250, HRD-455,100	JVC IDLER ASSEMBLY	4055 52p 4056 52p	74164 50p	74HC4053 85p 74LS280 88p 74HC4059 85p 74LS283 51p	Spare Element for C15W 240V 260p
NV100, NV180, NV300, NV333,	HRD-565, HRD-566, HRD-725, HRD-755	PU-47752 450p	4060 40p 4063 52p	74173 549p	74HC4060 33p 74LS290 26p 74HC4066 33p 74LS293 26p 74HC4072 31p 74LS293 26p	
NV340, NV366, NV600, 280p NV777, NV788		PU-51402A 145p	4066 20p 4067 120p	74175 65p	74HC4075 26p 74LS366 31p 74HC4078 32p 74LS367 28p	
NV230, NV370, NV430, NV460, NV730, NV810, NV830, 280 p	MITSHUBISHI	PU-55373 225p	4068 13p 4069 13p	74180 5#p	74HC4094 50p 74LS368 30p 74HC4316 100p 74LS373 45p	DESOLDERING PUMP
NV850, NV870, NV890, NV2000, NV2010, NV3000, NV7000,		IDLER ARM PU-55373-3-8 285p	4070 13p 4071 13p	74192 40p	74HC4351 110p 74LS374 45p 74HC4352 160p 74LS375 46p 74HC4510 120p 74LS390 42p	SOLDERING IRON
NV7200, NV7800, NV8600,	HS-200200	FAST FORWARD IDLER PU 45896C 210p	4072 13p 4073 13p	74197 46p	74HC4510 120p 74LS390 42p 74HC4511 70p 74LS393 37p 74HC4514 120p 74LS399 68p	ANTEX XS25W 240V Soldering Iron
NV8610, NV8620, NVG14 NVG7, NVG10, NVG12,	NATIONAL	NATIONAL	4075 13p 4076 42p	74HC SERIES	74HC4515 120p 74LS629 95p 74HC4516 125p 74LS641 88p	240Vac 540p Spare Element for XS25W 240V 260p
NVG18 360p NVG21, NVG25, NVH65 360p	NATIONAL	IDLER 200p	4077 13p 4078 13p	CMOS	74HC4518 55p 74LS642 105p 74HC4520 60p 74LS644 105p	ANTEX C15W 240V Soldering Iron 240Vcm 540p
PHILIPS	NV-300160	SANYO	4081 13p 4082 13p	74HC02 14p	74HC4538 75p 74LS645 105p 74HC4543 75p 74LS670 62p 74HC7266 75p 74LS674 310p	Spare Element for C15W 240V 260p
VR6460 280p	NV-333135 NV-777100	REEL PULLEY 143-0-662T-01201 520p	4085 36p 4086 30p 4089 75p	74HC04 15p	74HC22106 580p 74LS687 250p 74HC40104 190p	
SANYO	NV-2000150 NV-3000160	SHARP	4089 75p 4093 18p 4094 44p	74HC10 200p	74HC40105 250p IC'S 74LS SERIES 2114 200p	
VHR1100, VHR1300, VHR1500, VHR2300 360p	NV-700095 NV-720090	IDLER NIDL0005 GEEZ 195p	4095 58p 4098 50p	74HC14 250	LOW POWER 2532 330p SCHOTTKY 2716 200p	DESOLDERING PUMP
VTC5000, VTC5150, VTC5500, VTC9300, VTCM10, VTCM20 280p	NV-8600160	IDLER NIDL0006 GEEZ 195p	4099 42p 4501 27p	74HC21 20p 74HC27 20p	T.T.L 2732 280p 74LS00 12p 2732A 300p	Desolder Pump 290p
SHARP		SONY	4502 36p 4503 30p	74HC30 2000	74LS01 12p 2764 240p 74LS02 12p 27C64 550p 74LS03 12p 27128 350p	Spare Nozzle 60p
VC381, VC386, VC2300, VC3300,	PHILIPS	REW. PULLEY A 6706-348-B 400p	4504 55p	74HC42 300	74LS03 12p 27128 350p 74LS04 12p 26256-25 400p 74LS05 12p 41256-12 450p	
VC7300, VC7700, VC8300 360p VC9100, VC9300, VC9500, VC9700	VR-6460170	REW. PULLEY	4506 58p 4507 30n	74HC73 24p 74HC74 24p	74LS08 12p 256DRAM 450p 74LS09 14p 4116 75p	2
VC387, VC481, VC482, VC483, VC486, VC496, VC581 360p		A-6706-391-A/B 300p	4508 67p 4510 32p	74HC75 23p 74HC76 23p	74LS10 12p 4164 150p 74LS11 12p 6116 180p	SOLDER MOP 65p
VC582, VC583, VC585 VC651, VC681, VC685, VC750,	SANYO	SERVICE AIDS	4511 30p 4512 38p	74HC85 33p	74LS12 12p 6264 400p 74LS13 20p 6502 300p 74LS14 24p 6502A 400p	
VC780, VC781, VC785,		SERVISOL PRODUCTS	4513 80p 4514 65p	74HC93 50p	74LS15 14p 65C02 930p 74LS20 14p 6503 570p	-
VC787 360p VC793, VCT72	VTC-500075 VTC-5300100	V. HEAD CLEANER 100p SWITCH CLEANER 115p		74HC107 23p 74HC109 23p	74LS21 14p 6520 170p 74LS22 14p 6522 330p	SOLDER
SONY	VTC-550095 VTC-9300220	SILICONE GREASE 135p	4518 36p	74HC113 28p	74LS24 35p 6530 1050p 74LS26 14p 6532 460p 74LS27 14p 6545 880p	18 SWG 500g 500p
SLC5, SLC6, SLC7 360p SLC9, SLC20, SLC24, SLC30,		FOAM CLEANER 120p	4520 36 p	74HC125 3.2p	74LS28 14p 6551 530p 74LS30 14p 6800 210p	20 SWG 500g , 650p
SLC33, SLC44, SLHF100 360p SLF1, SLF11, SLF25, SLF30,	SHARP	ANTI-STATIC 120p AEROKLEANE 100p	4522 43p	74HC131 33p	74LS32 15p 6802 220p 74LS33 15p 6803 800p	
SLF1, SLF11, SLF25, SLF30, SLF60, SLF100		AERO DUSTER 125 PLASTIC SEAL 115	4527 41p 4528 38p	74HC133 33p	74LS38 15p 6809 600p	
**********	VC-381/383/386125 VC-6300150	If you purchase more	4529 65p 4532 48p	74HC138 33p	74LS42 25p 6818 380p 74LS47 52p 6820 140p	SOLDERING IRON
* 75 OHM COX CABLE WITH * * SOCKETS FOR TV TO VIDEO *	VC-7300/7700/7750150 VC-8300150	than one Servisol product postage will	4551 75p 4553 140p		74LS48 48p 6821 140p 74LS51 13p 6840 310p	STAND
* BLACK COLOUR 2 METRES * * LONG, ONLY £1 EACH + VAT *	VC-8381, VC-9100125 VC-9300, VC-9500135	be £2.00	4555 29 4556 36	74HC151 32p 74HC153 32p	74LS54 13p 6845 620p 74LS55 15p 6850 110p 74LS73 24p 8080A 400p	Soldering Stand 200p Spare Sponge 40p
		******	4557 140p 4583 60p	74HC155 4-3p	74LS74 18p 8085A 300p 74LS75 24p 8086 500p	
	SONY	* UNIVERSAL *	4584 30 4585 40	74HC158 34p	74LS76 24p 8088 500p 74LS78 24p 8155 360p	
AKAI VP-7100 160p		* TRIPLERS *	40101 78	74HC161 44p	74LS83 37p 8156 360p 74LS85 37p 81LS95 120p 74LS86 25p 81LS96 130p	
VS-1 150p	SL-C5, SL-C6140 SC-C7140	* 450p *	40103 120p	74HC163 4-4p	74LS90 26p 81LS97 130p 74LS91 55p 81LS98 130p	FLOPPY DISCS
VS-2EG 100p VS-4 120p	SC-C9165 SL-8000-8080200	*******	40104 80g 40105 140g 40106 25g	74HC165 5-5p	74LS92 32p 8224 240p 74LS93 26p 8226 240p	5 ¹ /4 inch DSDD (10 in box) Branded Name £7.50
VS-5EG 100p VS-9300 160p		*******	40106 35 40107 50 40108 260	74HC173 52p	74LS95 41p 8228 270p 74LS96 52p 8243 250p 74LS107 28p 8250 850p	5 ¹ /4 inch DSDD (bulk pack) 25 £10.00 3 ¹ /2 inch DSDD (10 in box) Branded
VS-9500 155p VS-9700 160p	TOSHIBA	* SONY ON/OFF *	40109 74	74HC175 33p	74LS109 28p 8087 11000p 74LS112 28p 8251 270p	Name £13.00 3 inch CF2 Branded Name £2.40
VS-9800 155p		* SWITCHES *	40114 180	74HC182 6-0p	74LS113 28p 8253 230p	
AMSTRAD	V-55/5785 V-5250/5280230	* 200p *	40147 240	74HC191 55p	5000 ITEMS AND QUOTATIONS A	T LISTED HERE AS WE ARE HOLDING IRE GIVEN FOR LARGE QUANTITIES.
TVR-1-2-3 210p VCR-4600 & Mk 2 210p	V-5480210 V-5475160		40161 55 40162 55	74HC193 41p 74HC194 48p	Quotations given for large guaritities. Ple	 Govt, Colleges, etc. Orders accepted. ase allow 7 days for delivery. All brand new boxed. Prices quoted are subject to stock
VCR-4700 210p VCR-5200 210p	V-7540160		40163 55 40174 48	74HC195 4-8p 74HC221 80p	availability and may be changed without	notice.
VCR-7000 80p	V-960085	* PHILIPS *	40175 60 40181 170	о 74HC237 50р 74HC238 55р	GRAND	
SEE PREVIOUS	PAGES FOR MORE	* 150p *	40182 70 40192 48	o 74HC240 48p o 74HC241 47p	K.P. HOUSE, UNIT 15, PO	P IN COMMERCIAL CENTRE, , MIDDLESEX, ENGLAND
		★K30, K35, K40, KT3, KT4	40193 48 40194 58	74HC243 60p	Telephone: 01-900 2329	Telex No: 932 885 (Sunmit) -903 6126
GKAND	ATA BARGAINS	*******	40208 240		Fax: 01 Access & Visa Card accept	-903 6126 ed. Open Monday to Saturday

1.1.1

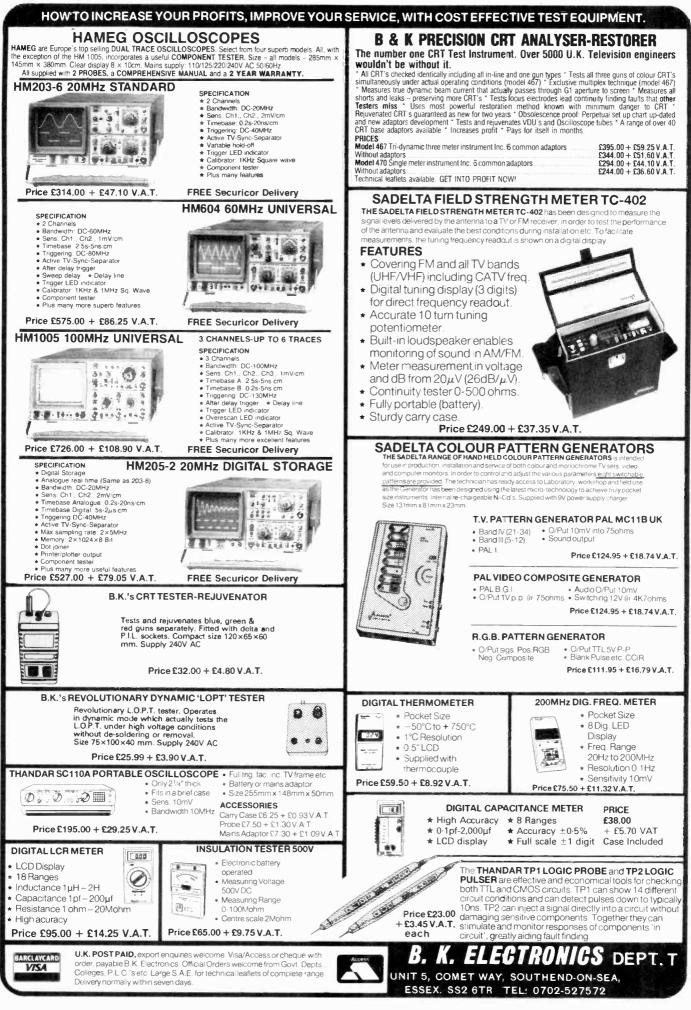

ABBEY STREET, 4 ABBEY STREET, 91: 0254 36521/32611/3 91ex: 635562 Griffin G 91ex: 635562 Griffin G	ACCRINGTON, LANC 390936 BB5 1EE (For P.V.) ell Fax No.	COL O S MO E. 9an	RADE UNTER PPEN IN-FRI n-5pm SAT n-4pm	Up to 1K ADD P+P (U.K.). He cable, service colls please all (U.K.). Export cost. Frst Cla whenever possit to total except w rate. Bulkier iter carrier £8.50 + (except tubes).	D ORDER £1.00 per order avier parcels e.g. aids, degausing low £3.25 P+P profers charged at ss Mail is used pie. Add 15% VAT here it states zero ms will be sent by - VAT up to 25K the on Saturdays.	BOOKS AN Goods are If for any n you as qu speedy, fa request. G ask if wha Prices are cases we i We need e MINIMUM	VAT ON P+P. D MANUALS ARE ZERO V.A.T. despatched on the day we receive your orde asson we are out of stock we will try to, infor ickly as possible. We try our best to give ir and efficient service. V.A.T. invoice ve us a ring – we'll give you service. Pleas you need is not listed – we will try to hely subject to change without notice. In som nay have to supply an equivalent. Supr dates for credit card orders. ORDER 55.
DEO HEADS ICES DDWN AGAIN 16.50 SSV FERQAKALIEC 16.50 SSN NATPAN 16.50 DEK FOR MOST MAKES JUST ASK. 16.50	REMOTE CONTROLS THORN/FERG TV 13.00 THORN/FERG VIDEO 3V23 3V31 IR8945 14.95	WE	AVAILABLE AT THE NOW HAVE A CONTINUOUS SUP				WE HAVE TRIPLERS, LDPTX, PUSH BUTTON ASSY ORTS, CAPACITORS, RESISTORS, POTS, RISES, DROMPERS, STVLI, LEAUS, CABLES, etc. ASK US INTEGRATED CIRCUITS We have in stock all listed Commodore IC's.
W TYPES ADDED RECENTLY BA 3H\$\$DB 26.00 LDSTAR 3H\$\$0B	3V35 IR8946 14.95 3V43 IR8947 19.12 GRANADA UNIVERSAL 16.50 PHILIPS 16.50	ALI	READY FOR	PLETE WITH REMO		5	COMPUTER IC'S/TRANS LMG121R0P 7. LMI889 1. MARRING 3.
L2 3HSSR 25.00 L4 3HSSR 25.00 L5 PSF1 25.00 L6 PSF2 25.00 L35 3HSSR .25.00 MSUNG UMIVERSAL 24.45	G11 TXT IR8435		VIDEDS HAVE DPERATING INSTRUC PLoader £36	DEOS	t Loader with Remote	£128 £128	MC1488 D. MC1493AP D. MC1493AP D. ZK81 4. SPEC.48K RDM 5. QL RDM 256K 12. QL RDM 125K 7. TC724H024 0.
AKE UP IDLERS/CLUTCH SSY AMM32773 5.63	K13/30 TXT IR8420 16.50 RC5 REPLACEMENT 13.95 PLUS MANY MANY MORE!!! SATELLITE EQUIPMENT	14" Portable Pye. Standar Fidelity. Star Ferguson. Sl	s. Standard From £65 rd £69 ndard £87 tandard £79	22". Standard. Decca, Remot	ote. Text . Toshiba e 160 Series	. £65 £108	TMRS1000 8 TMMRS3128P-1951 10 ULAGC001E (SPEC) 6 ULA1305T 2 Z80A CPU 1 ZN7400E 11
AI BV327815 4.87 ISTRAD 7000 2.20	SAKURA ASTRA SYSTEM	Ferguson, Ri Philips, Stan 20'' Decca M	ndard £90	Ferguson TX1 Philips. Remo		£139 Text £113 £117	SN7438N 22 74LS00 11 74LS32 0 74LS157 0 74LS157 0
(G 3/2977/F	4 CORE POLAR CABLE	WE HAVE I	Please Ring				74LS260 0 251641-02 P.1 2732 2 2754 2 27128 2 27256 2
S gen THORNU/VC 4.95 HER 490400000 3.95 HER 490400000 4.50 AG 3292 F/F 1.46 AG 3000 TAKEUP 4.85 AG 3000 TAKEUP 4.85 AG 3000 TAKEUP 4.95 AG 3000 TAKEUP 4.95 AG 3000 TAKEUP 4.95 AG 3016 TAKEUP late 5.85 AG 3016 TAKEUP late 5.85 AG 3016 TAKEUP late 5.85 AG 3020 TAKEUP late 5.85 <td>F LINE CONN 0.45 CRIMP TOOL 29.95 COMPASS 6.00 SAKURA STEREO SYSTEM 229.00 SIGNAL STRENGTH METER 53.92 AND A COMPLETE RANGE OF AERIALS</td> <td>eg STK548 STK7300 STK5333 STR5010 STR580 TRANSISTO</td> <td>1 . 6. 8 . 7. 2. 4. 03A. 5. 41 9.</td> <td>16 30FL2 . 20 DY802 00 DY86/87</td> <td>S 1.70 PC97 0.98 PC805 .0.66 PCF80 1.50 PCF200 0.98 PCF800 1.23 PCF801</td> <td>1.65 1.40 1.00 1.35 1.38</td> <td>RAM 4118 2 RAM 4116-4 RAM 4116-2 8249 2 8247 6 B8247 6 B8CUID ULA 1</td>	F LINE CONN 0.45 CRIMP TOOL 29.95 COMPASS 6.00 SAKURA STEREO SYSTEM 229.00 SIGNAL STRENGTH METER 53.92 AND A COMPLETE RANGE OF AERIALS	eg STK548 STK7300 STK5333 STR5010 STR580 TRANSISTO	1 . 6. 8 . 7. 2. 4. 03A. 5. 41 9.	16 30FL2 . 20 DY802 00 DY86/87	S 1.70 PC97 0.98 PC805 .0.66 PCF80 1.50 PCF200 0.98 PCF800 1.23 PCF801	1.65 1.40 1.00 1.35 1.38	RAM 4118 2 RAM 4116-4 RAM 4116-2 8249 2 8247 6 B8247 6 B8CUID ULA 1
IACHI 6413663 2.68 IACHI 6414221 5.04 IACHI 6343531 0.70 IACHI 6383531 0.70 IACHI 63462 5.02 IACHI 6345173 0.40 IACHI 636571 2.90	AND ACCESSORIES ON PAGE 23 IN CATALOGUE ANTIFERENCE UNIVERSAL NO. 1 CLAMP	BU208A BU326A TIP41C 2SC233	. 0. . 0. 0.	95 ECC84 85 ECC85 25 ECC88	0.80 PCF802 0.98 PCF805 1.35 PCL82 1.30 PCL84 1.25 PCL805 1.60 PCL86	1.12 1.80 1.20 1.20 1.09 0.92	4 164/4564-15 41256-15 6522 COMMODDRE 6264 COMMODDRE 6510 COMMODDRE 6500 COMMODDRE 6562 COMMODDRE
TACHI 6886971 2.90 TACHI WIND RDLLER 0.78 TPAN VXP0463 3.20 IT PAN VXP0433 1.10 TPAN VXP0401 1.08 V PAN VXP0344 1.22 TP PAN VXP0331	SB11 SPLITTER 2.50 CS200 COMBINER/SPLITTER 3.94 COB11 OUTLET 0.96 PU1240 POWER UNIT 11.65 PU1300 MHA 9.09 72 Mut-5 LITER 2.10	1	T PROTECTORS	ECL82 98 ECL84 98 ECL86 98 EF30 98 EF36	0.95 PL504 2.20 PL508	1.65	6556 COMMODDRE 6561 COMMODORE 6561 COMMODORE 6582 COMMODORE 2 6581 COMMODORE 3800 COMMODORE 1 8501 COMMODORE 8701 COMMODORE 905114 PLA.COMM
TPAN VXP0433 5.50 NYD RELL DRIVE PUL 5.10 NYO SOOR ILA ASSY 1.85 MSUNG	27 MHZ FUTER 2.10 DIPLEXERS 0.68 MATCHED TRANSFORMER 2.83 XS2 XTRASET 14.46 XS04 4 WAY DA 22.50 XS 4/6. 43.13		0. 5, Diodes, Zeners, Volt Regs, Leds, Filament Lamps,	98 ' EH90 EL90	0.99 PL509/19 0.72 PY88 1.75 PY500A 3.50 PY800/1 1.26 UCH81 0.68 UCL83 2.25 UY85	0.81 1.75 0.69 2.25 1.82 1.35	901225 CHA ROM. COMM 901226 BAS ROM. COMM
E HAVE A FULL RANGE OF MDTORS, TYRES. LT KITS, LAMPS eIC IN STOCK . EASE SAK FOR CATALOGUE	SUPER SET TOP AERIAL 6.50 CARATENNA AERIAL 7.20 TRAVELLER AERIAL 11.50 SILVER SENSOR AERIAL 7.40 XG8 HIGH GAIN AERIAL 21.00	AND HAVE REPAIR SP SPECTRUM	PECIALISTS IN COMPUTER PARTS LOTS OF GOODIES NEEDED TO PECTRUMS AND COMMODORES 4 48K MEMBRANES	GZ34 KT66 KT77	0.56 PL802T 1.45 40KD6 3.50 21LUB 9.75 17DWB 8.50 3AT2A hyp. 12.00 12BY7A	4.00 5.93 3.00 4.50 5.00 3.75	ZTX510 ZTX551 ZTX5501 ZTX750 IS 2472 901227
PECIAL OFFERS IS E180 TAPE (10) .22.90 a LACO PL/UGS (10) .3.75 IDIOLINE PHONE 201 15.00 IDIOLINE PHONE TEL1 .9.50	POWER SENSOR AERIAL WITH AMP	ULA	LY 1.35 6.50 5.00 S MEMBRANES LY 4.50	PC92 PCH200 PCF808	. 4.50 6L6GC . 1.45 6L6GT 1.63 12BG7 . 12BH7A	3.68 2.81 3.20 5.25	NEW PRODUCTS MAINS SMOKE ALARM ADAPTORS TO ALLOW BATTERY SMOKE ALARMS TO RUN OFF MAINS
ABGEAR 17261 P.U. 12.39 17262 P.U. 13.50 17065 UHF/VHF H6 15.18 17065 UHF/HB 14.7	SECURITY EQUIPMENT CONTROL PANELS SHORROCK ACORN PANEL		TELEVISION WALL B PS245 TELETWIST TWIN Articulated TV Wall Bracket 12"-20" White (Loadbearing Cap. 36Kg)	RACKETS	-00	<u>)</u> -	PHILIPS BACK UP BATTERIES 9 2.4V 4 WAY TRAIL SOCKET WITH PLUG & CABLE RED MK4 REMOTE
Y7268 VHF H. GAIN A/B/C0 17.57 17253 BEHNID SET (MAINS) 15.81 17243 SECOND SET AMP 14.73 17093 THREE SET AMP 18.55 17063 DIST.AMP VHF/UHF 25.77	817S SHORROCK	g/PIR is	P6045 DESIGNER TWISTER 12"-20" White (Loadbearing Cap. 36Kg)	27.00	->>	<	SOCKET KIT FOR TDA2600 . 3V38/39 LOWER DOOR FLAP 3V38/39 UPPER DOOR FLAP
17108/7298 8+1 DIST_AMP 49.96 19700 27MHz 08 SUPPRESSOR 4.90 16011 OUTDOR SPLITTER 8.63 1900300 FLUSH SING.OUTLET 1.95 1900301 FLUSH SING.OUTLET 1.95 19010 FLUSH SING.OUTLET 2.47	now in stock. PHANTOM 240 PIR (Mains) PHANTOM SC Self Contained 240 PIR/Ligt watt PL9 tube PHANTOM PC 240V Self Contained Cour	nt with low 34.50	P6041 LITTLE TWISTER Small, ideal for Bedroom/Kitch 14" White (Loadbearing Cap. 16Kg)	en 14.08	DISKS GOLDSTAR 5.25" 20D OS/QD (80X 10 GOLOSTAR 3 ¹ /2" HF 20D OS/DD (80) UNBRANDEO 3 ¹ /2)) . Diskettes (10)	5.66 651, 682, 684, 685, 693, 783
19034 UHF FILTERS AG/CD 8.89 19033 6 WAY PASS SPLIT 11.72 17042 TV CAMES COMBINER 3.24 19005 FLUSH TV/FM EMULATOR 3.88 19006 VH/FUHF DIPLEXER 4.17 17122 TELEVERTA UP VHF TO UHF 41.90	which operates during hours of darkness ORION 5 PIR with built in halogen flood 1 EXCELLENT VALUE	22.50	TEST METERS HT700 METER 20,000 R/v PHILIPS METER	10.99 . 25.90	DS/DD (BOX 10) . AMSTRAD 3" DISK	S	7.70 H/GOS High quality spaker 29.50 cable 100m 000 senes by Popular Request!
ATOS TELEVERTA DOWN UHF VHF 43,73 AT234 DIST AMP UHF VHF 24,96 AT234 DIST AMP UHF VHF 24,96 AT274 4 war DIST,AMP 26,16 AT082 UHF VHF DIST,AMP 26,16 AT082 UHF VHF DIST,AMP 74,13 AT080-10 UHF WHA 16,89 AT271 UHF WIDEBAND 15 db 9.09 A5004 4way VIDED DIST AMP 60,20	5Zone/Keypad operated CASTLE OMEGA 5E 5Zone/Keypad operated	66.00	STATIONERY SERVICE CALL PAD (100) REPAIR TICKET (100) JOB CARD (100) RENTAL PAYMENT CARD (50) MAINTENANCE AGREEMENTS (10	1.99 3.90 . 2.50 3.50 0) . 3.50	SPECIA ALTA C90 AUDI	0	We are the mail order specialists and v try hard to stock all that we advertis its not our policy to print lists in catalogues of goods that we do not ho in stock. Please ring us should you have any spe
ABGEAR SATELLITE RANGE MS188 IF Interim Dist Pump 57.00 MS110 IF Line Pump	WE STOCK CABLE, CLIPS, BELLS, BOXE BATTERIES, SOUNDERS, BUZZERS, XEN CONTACTS, SMOKE ALARMS, TRUNKING	IONS,	WE WELCOME OROERS FRI Colleges and government on official requisition.	OM SCHOOLS, Institutions	TAPE (BOX 10 1.99 ON)) Y	Please ring us should you have any she requirements or if you need quantity discounts. We will always try to give you person, and friendly service.



BUY WITH WE WILL ONLY SUPPLY TOP G.G.L.COMPONENTS QUALITY, BRANDED COMPONENTS. PO BOX 72, UNIT 7, SOUTH JOHN STREET, CARLISLE, CUMBRIA CA2 5AL PHONE (0228) 39693/20358 FAX (0228) 515127 **REPUTATION COUNTS WITH US** TYPE PRICE (E) PRICE (E) INTEGRATED LINE O/P TRANS TRANSISTORS TYPE BU807 PRICE (E) CAPACITORS TYPE 1UF at 250V.. 4.7UF at 250V LK 542 TYPE PRICE CIRCUITS DECCA 100 8.30 STK5421 STK5481 STK7308 STR4090 . 8.95 . 8.95 . 8.95 TDA2 ĩõ BU8264 25 **TYPE** AN303 AN305 PRICE (£) .25 FERGUSON 1690/1 BC107 9.95 15 10 TDA2540 BU907 2 95 10UF at 250V BC14 3.75 TDA254 FERGUSON 1790/1 .7.95 BU908 1.95 8.95 22UF at 250V ăŇ 3.50 6.95 FERGUSON TX9 23.50 BC148 10 2.95 33UF at 250V 55 STR4009 7.95 **AN318** DA2576/ RC307 12 BUW81A 47UF at 250V. 100UF at 250V STR501034 6 50 FERGUSON TX90 (14") 1975 AN562 4 95 DA2577 BC327 BC328 BUX84 STR4211 3.95 FERGUSON TX90 (20") 19.75 AN71458 DA2578A 2.35 4.95 TRAA1 (All Single Ended PCB Type) HA1339A HA1366W FERGUSON TX100.90 20.95 R4050 2.95 8.95 R45 BC337 .11 DA2581 SG61 FERGUSON TX 100 110 20.95 BC338 .12 TR454 4.95 DA2582 SG26 5.95 5.75 3.50 3.50 1.95 DIODES HA1366WR 1.85 FIDELITY ZX2000 14"/20" BC360 T6071V(KIT) STR5412 6.95 DA2591/3 TYPE PRICE HA1374 2.45 (Inc. Mod.) RC546 10 10 10 STR58041 6.95 TDA2594 T9053\ BC546 BC547 BC548 BC557 BY127 BY133 HA1377 2.95 STR6020(KIT) 5 75 TDA2595 FIDELITY 7X3000 14"/ T9054\ TDA2595... TDA2600... TDA2611A TDA2653A TDA2655B TDA3190... TDA3330... TDA3540... TDA3540... TDA3540... HA1393 2 95 20 TA7193P 4 50 T9064V 11.50 TA7205AF TA7222P. BY17965 .1.25 1.50 3.50 10 TIP29E TIP310 FIDELITY 7X 22"/26" 22.95 1300 BY223 BC558 10 HINARI CT4/5 21.95 **BY227** 20 HA13008 12.95 BC639 25 TIP320 TIP410 TA7227 2.95 BY229/800 95 LA1201 1.25 ITT CVC20 850 RC640 7 TA7270 BD 131 BD 132 BY299 BYX55/600 1N4007..... LA1230 2 95 50 50 TIP42C.. TIP112H ITT CVC25/30/32 TA7609 3.35 8.50 LA136 2 45 295 295 TBA120AS TBA120U ... TBA800P ... TBA810S ... ITT Compact 80. PHILIPS G8..... 11P112H 15/80H... 15/85R... 2SC867A 2SC1034 2SC1034 2SC1114 2SC1413 2SC1942 2SC3156 2SD725. 2SD870. 1 00 21.05 A3541 A3560 A3561A A3562A A3562A A3565 IA3571 B/Q JA3650 JA3651 A3651AQ A3652 A3652 .07 1.00 BD222 .50 .50 LA4445 LA4460 .. 9.95 1N5408 BD225 PHILIPS G11 19 95 SKF5F3/10 1 50 B0237 40 PHILIPS KT3. 12.95 RD23 40 70 40 ZENER DIODES TBA820 LA7800 1 95 PHILIPS K30 19.95 BD278A BD437... 114. BZX61C (1.3 Watt) 3V3, 4V7, 5V1, 5V6, 6V2, 6V8, 7V5, 8V2, 9V1, 10V, 11V, 12V, 13V, 15V, 18V, 20V, 24V, 27V, 30V, 33V, TBA820M Δ7801 2 90 PHILIPS CTX 14"/16" ... TRA920S 195 .17.95 M293B1. MC13002 MC14497 6 95 TBA920S ... TBA950/2X TBA1440G TDA440.... TDA1020 ... TDA1035T .225 .295 .295 BD438 PHILIPS CTX 20" 17.95 BD677 65 RBM T20/22A .9.95 BD701 95 TDA3653AQ TDA3653AQ TDA3654AQ TDA4500.... TDA4503.... 36V, 47V, 56V, 62V, 75V, 100V, 110V, 120V, 130V. Pkts SHARP C1410 23.95 SAA1250 3.85 BD707 95 2.75 2SD1350 4.75 SAA1251 4.95 RD907 95 28 30 7805 7812 7815 2.40 1.00 **ON/OFF SWITCHES** BF337 BF338 SAA3027 3.95 TDA 1037 1.95 A A 5000 3 05 Decca 80/100 . TDA1044. TDA1044. TDA1151. TDA11705 2.95 1.25 1.80 TDA4600/2 ... TDA4600/2D 70 SAA5000/ SAA5010. SAA5012. SAA5030. E.H.T. TRAYS Ferguson TX9/10 (Rem) . 1.75 11 BF422 35 7824 Continental 20AX Focus 8.95 Continental 30AX Focus 8.95 DECCA 80 7.20 TDA7270 3.35 Ferguson TX90 (Rem) 1.75 BF423 35 5.95 TDA8180 BF458 35 TDA1180F 2.65 Fidelity AVS Series 1.50 .95 .50 .70 2.3C SAA5050 6.95 **RF460** TUNERS TDA1190Z 2.85 Fidelity CTV140. .2.95 .3.95 .3.95 .2.60 DECCA 100 DECCA 120/130 ITT CVC20/25/30/32 7.35 SAF1039F 2.75 TDA9503 TDA9513 1.50 BF400 BF470 BF757 TDA1470 3 25 ELC 1043/05 SL470/1DP 2 95 Fidelity CTV14R 2 95 75 TDA1506 4 35 ELC 1043/06 TFA1012 TDA1508 TDA1510 TDA1512 TDA1515 .4.39 .3.80 .3.50 .4.50 Fidelity CTV14S 2.95 6.95 BF871 .80 .490. .490. 14:30 UPC1031H ITT CVC45 7.50 Grundia CUC731 3.50 BR103 75 U321 .8.75 1.70 1.70 1.70 2.50 .95 .95 .75 65 PHILIPS 68 550 7 90 BR303 1 95 Hitachi CPT2650. UPC1182H 1.95 ..7.95 .14.95 16.95 PHILIPS KT3 7 95 BT151/800 15 U341 1400 TDA16704 4 20 UPC1185F Philips G8 1 35 RBM T20/22A THORN 9000 ... UNIVERSAL ... BU126 BU205 BU208 .3.70 .6.95 .1.95 230 4.35 4.20 3.70 4.35 U343(coax skt) TDA1770A UPC1230H UPC1365C Philips G11. 1.35 U343 (phono). .8.00 AA71 6.95 6.95 TDA1870. TDA1908A Philips G11 (Rem) 1 75 UPC UPC 378H Philips KT3. 1.50 3.95 1.50 1.55 12120 11 95 TDA1950A TDA2002 382 BU208[UE5-B31F. UPC13940 Z80ACPU FUSES 2.95 Philins KT/CTX (Rem) 175 BU326A 1.45 20mm A/S: (Pkts of 10) 250MA, 315MA, 400MA, 500MA, 630MA, 800MA, TK4332 TK435 TDA2002 TDA2003 TDA2004 Pye G11 (Rem).. 5.95 5.95 BU401 1.25 1.75 TV ELECTROLYTICS DECCA 80 (400/800) 450 FIDELITY ZX(220/385) 3.9 PHILIPS G1600/300) 2.50 PHILIPS G11(470/250) 2.20 RBM T20A(220/400) 2.50 THORN 1690 (4700/25) 1.3 .50 BU407D 2.90 RBM T20/22A 3K3 Vol ... 2.45 TK437 BU426A .35 TDA2005 2.55 Sony KV1612 (Rem)... 500mm, 325 1A, 1.25A, 1.6A, 2A, 235, 3.15A, 4A, 5A, 6.3A,8A.....**1.20** 20mm 0/8: (Pkts of 10) 500MA, 630MA, 800MA, 1A, 60 .4.50 .3.95 .2.20 .2.50 .1.35 .2.90 BU500 1.95 TDA2020 3 20 STK459... STK461... STK463... STK465... STK5332 I C SOCKETS BU508A BU508D BU526A Sony KV2022 (Rem) 3 95 .75 TDA2030 1 80 18 Pin Dil-Dil 24 Pin Dil-Dil 28 Pin Dil-Dil 40 Pin Dil-Dil 9.95 9.95 1.75 Tatung 160/161 TDA2170 2 05 2.50 25 30 40 295 Tatung 165 1.75 BU536. BU705. 2.75 TDA2525 2.95 Thorn Universal 1.00 THORN 9000(400/400 SANYO/FISHER SHARP VIDEO SPARES VIDEO PILOT LAMPS FERGUSON TV SPARES **GEC/HITACHI SPARES** NV2000/2010 Ferguson 3V23 (Plug) Ferguson 3V29 (Plug) Panasonic NV2000/7200 ก HM3232 Complete Maintenance **VIDEO SPARES** TX9/10 5.95 VC8300 Focus Unit TX10 Kit (Genuine). VTC5000/5300 HM6251 .21.50 Cassette Lamo 70 70 Line O/P Trans TX9 23.50 HM9032 .5.95 Cassette Lamp.. .70 Loading Roller. Pinch Roller 1.25 Channel Bank 7.95 Sharp VC8300 ... 70 8.50 Line O/P Trans TV10 20.95 Pinch Roller 3.95 VIDEO SPARES Pinch Rolle Sharp VC9300. 1 95 Play Idler (Genuine). 1 95 1.25 On/Off Switch (Remote) V4000/VT8000 Capstan Motor Reel Idler (Genuine) ..5.70 Rewind Idler 3.50 Universal .50 Push Button TX9. 16.95 Reel Idler (Genuine) . Reel Motor (Genuine) 7.95 31.95 Push Button TX10. 16.95 Video Head 17.95 Video Head VC9300/381 **VIDEO HEADS** 35.00 EE/Rew Idler 2 65 Capstan Motor . Cassette Lamp... Pinch Roller RFI Choke TX9..... Alba 4000 Amstrad VCR4500 FVHP615 29.95 FF/Rew Pulley NV7000/7290 Tuner... 14.95 Gear Idler Assembly 5.95 22.95 23.50 Pinch Roller ... 3.95 Complete Maintenance Pinch Roller 4 50 Amstrad VCR4600 TX90/100 Play Idler. 4.50 17.50 Reel Idler (Genuine) Kit (Genuine) ... 3.95 Amstrad VCR7000 24 95 Reel idler. Line O/P Trans TX90 14" Line O/P Trans TX90 20" 19 75 Video Head 22.95 Cassette Lamp 17.50 70 Reel Motor (Genuine). Amstrad VCR9000 24 95 Video Head .24.95 Pinch Roller Ferguson 3V00/22/29/39 Ferguson 3V32 Ferguson 3V42/44/45/55 Fisher FVH520/615/720 24.50 16.95 47.50 26.95 24.95 V4001/VT9300/9500 3.95 Unlock Assembly Line D/P Trans TX100 90' 19.95 Play Clutch (Genuine). Video Head . 23.95 31.95 Capstan Motor 4.95 SERVICE MANUALS line D/P Trans TX100 110 20.95 FF/Rew Idler 1.95 Reel Idler (Genuine) 1.25 VC481 ins Trans. (TX90) 17.95 FF/Rew Pulley 95 17.95 (All Genuine) Video Head Capstan Motor Reel Idler (Genuine) 22.95 On/Off Switch (Remote) . Push Button TX90 .1.75 Ferguson TX9 Complete Hinari VXL2/4. 24.95 27 95 Pinch Roller3.95 3.95 Hitachi 8000/9300/9500 12.95 22.95 Ferguson TX10 Complete Play Idler. 3.95 38.95 Reel Motor (Genuine). 18 50 Hitachi VT11/33E 22.95 **REMOTE CONTROLS** Tuner.. Video Head . 22.95 Ferguson TX85 .9.95 Video Head 23.95 Mitsubishi 303/310 27.95 Ferguson TX90. Ferguson TX100 Ferguson TX9 U/S Basic 14.50 27.95 29.95 16.95 34.95 21.95 24.95 14 95 Panasonic NV230 Panasonic NV230 Panasonic NV333 Panasonic NV366 Panasonic NV370/380 V4100/VT11E/VT33E FERGUSON Ferguson TX9/10 N/Text 12 95 Capstan Motor (VT11E) Capstan Motor (VT33E) 18.95 SONY SPARES VIDEO SPARES Ferguson TX9/10 Text.. Ferguson 1790/1 .1.95 3V00/16/22 29.95 Ferguson TX Stereo Text 12.95 Fidelity AVS1600 5 95 27.95 Capstan Motor C7 Clutch Assy..... FF/Rew Idler (Genuine) 7 95 Ferguson TX100 Text Capstan Motor 24.95 15 95 Fidelity AVS2000 Pinch Roller C5/6/7 . .3.95 Panasonic NV430 Drum Motor 24 95 Ferguson 3V23 Video. Fidelity CTV14R 5.95 Rewind Kit C5/7 4.65 Panasonic NV688 44.95 Pinch Roller Pinch Roller 3.95 Ferguson 3V31 Video 16.95 Fidelity CTV20B 5 95 Rewind Kit C6 3 45 Panasonic NV730 34.95 Video Head 22.95 Take-Up Clutch (Small). Ferguson 3V35 Video Panasonic NV730 Panasonic NV777 Panasonic NV2000/7000 Panasonic NVG7/9 Panasonic NVG10/11/15 .5.65 16 95 Video Head C5/6/7 19.50 29.95 Fidelity CTV201 5.95 29.95 16.95 24.95 29.95 44.95 Take-Up Clutch (Large) 5 95 V4005/VT63E Fidelity CTV14R/S . 12.95 Philips CF1.. 6.95 Video Head Capstan Motor End Sensors (Pair). 15 95 16.95 Grundig TP200. 12.95 Philips CTX-F 2.50 VIDEO BELT KITS .1.95 .4.95 Grundin TP400TT 12.95 3V29/30 Philips CTX-S. Akai VS1/2/3/5..... Amstrad VCR4500 1.95 Pinch Roller . ITT FS9/FS10 Text ... ITT RG301/305 Text . Panasonic NVG18 Capstan Motor 37 95 Philips KT34.50 1 95 Panasonic NVG20/21/25 Video Head 49.95 39.95 Loading Motor .8.70 14.50 Philips K35 3.50 Amstrad VCR700 1.50 Philips VCR6460/6520 21.95 Ferguson 3V00/16/22 Ferguson 3V23...... Ferguson 3V29/30.... Philips KT4/40 Pinch Roller 4.50 PANASONIC VIDEO (TT RG306 Text 14.50 5 95 2 50 Philips VCR6460/6520. Philips VCR6462/6560. Samsung VX510/616... Sanyo VHR1100/1300. Sanyo VHR1500....... Sanyo VTC5000/5500... 37.50 Panasonic NV7200 Video Philips G11 U/S Full Rem. Pilot Lamp ... 15.95 ..80 Philips 2A .. 6.95 27 9 SPARES 29.95 42.95 35.00 24.95 23.95 15.95 Reel Idler .2.85 Philips 2B 6.95 NV333/366 Take-Un Clutch 2 45 Philips G11 U/S Text. 15.95 Ferguson 3V35/39 1.95 Complete Maintenance Kit (Genuine)..... VIDEO RECORDERS Philips G11 I/R Full Rem. 12 95 Ferguson 3V44/45 1.95 Fake-Up Idler..... Ferguson 3V35/36 13 75 28.95 Sanyo VI (2500/5500 Sentra 8000 Sharp VC5300/381/481 Sharp VC581/583/682 Solavox 1000 Sony C5/6/7 Sony C20/30 Toshiba V9600/V31B Toshiba V55/57 Philips G11 I/R Text... Fisher FVH520/615 1.95 16.95 Video Head .. Cassette LED .1.95 Ferguson 3V44/45 11.95 11.95 Hitachi 8000 1.95 Philips KT3/30 N/Text 12.95 3V35/36 Pinch Roller 3.95 Ferguson 3V46/47/52 Hitachi 9300 1 95 Philins KT3/30 Text 12.95 27.50 24.95 Play Idler (Genuine) Capstan Motor 22.95 Ferguson 3V54/55 11 95 Hitachi VT11F 95 4.95 12 50 Philips RC5 (Genuine) Cassette Housing. 25.95 Panasonic NV333 Panasonic NV370 05 Ferguson 3V59 Reel Idler (Genuine) 1.25 19.50 22.95 Mains Trans.... Philips AV5600 Video. 15.95 21.95 Reel Motor (Genuine). 14.95 Ferguson 3V65 11.95 **Bedifusion Mk 4 Text** 13.95 Ferguson FV11 Panasonic NV730 Panasonic NV777 24.95 16.95 Reel Idler. .2.85 Video Head 17.95 9.95 1.95 Sony RM604/605/606 14.50 9.95 Take-Un Clutch 2.45 Ferguson FV12 1.95 NV370/380 Sony RM613/615. Take-Up Idler... Panasonic NV2000/2010 1.95 Complete Maintenance Philips VR6460 .6.50 Sony RM630/632/635 14.50 Panasonic NV7000/7200 1.95 ORDERING Video Head .. 16.95 Kit (Genuine) Pinch Roller Philins VB6462 6 50 Panasonic NV70 Sanyo VTC5000. Sanyo VTC5300... Sharp VC7300... Sharp VC8300... Sharp VC9300... Sany CC9300... 12.95 Tatung RTP40/43/45. 1 00 15.95 Philips VR6467 Please add 75p for p/p U.K. Add 15% VAT to this total. 3V44/45 6.50 1 04 Philips VR6520 37.95 2.50 Capstan Motor Reel Idler (Genuine)2.95 . 6.50 Manuals £1.00 p/p each Service Cassette Housing Loading Motor Video Head Philins VR6542 6 50 29.95 21.95 **REPAIR KITS** Export Orders p/p Philips VR6560 6.50 NV730/770 Philips KT3/30 N/Text ... 6.50 2.45 charged at cost Delivery by return on stock Take-Up Clutch. .1.95 Complete Maintenance Philips KT3/30 Text 6.50 Philips VR6660 6.50 Sonv C5/7 ... 2.50

Philips VR6760

.8.95

Sony C6

Video Head

26.95

Kit (Genuine)

12.95



_	EA 3000 TV's	FCI & VIDEO'S	LEA S IN STOCK	lesale RAN AT UNBEATA	ICE S BLE PRICES – HU OF SPECIAL OFFERS WHIL	ALE JRRY NOW.		
W PHILIPS G11 KT3/K30 BUSH T20 GRUNDIG TOSHIBA TX9 TX TEXT STEREO TEX	ORKIN	G CTV' £18 £30 £18 £35 £30 £30 £55 £75 OWN SE	S WO SETS SPARES AV MOST TV (CALLER		VORKING VI FERGUSON 3V2 JVC 7200 PANASONIC SHARP AMSTRAD 7000 3V31/3V35 HITACHI VT11	DEO'S 9/3V30 £65 £75 £75 £80		
NEW INFR VHS BLOCKS ★ DELIV	ra red han Video hea S of 10 S Ery can i	D SETS FRO DS FROM £1 ETS FROM BE ARRANG	M £10 5 £40 ED ★	TRADE SHOWROOM ARGE QUANTITY OF READY TO SELL VIDEO'S & TV'S Call in – you will be delighted	WAREHOUSE OFF LITTL CALDMORE TEL. 0922 72 MOBILE OF	IN PASSAGE E LONDON , WALSALL 24542/722208 360 749202 m Sunday by appointment		
SCOTLAND'S INDEPENDENT		EX * F	TV & VIDEO HOLESALER		MMA U. /1754 Pershore R Birmingham, B Telephone 021-4	d., Cotteridge, 30 3BH		
	colour tvs from £5	DIRECT Loads Available	working text from £35	Fully serv	iced video recorders	IDEOS! with bulbs, belt &		
	Delivery Service	WORKING TVs FROM	DISCOUNTS FOR QUANTITY	idlers changed and cabinets resprayed ready for retail. Example 3V29 £70. 3V30 £70. 3V40 £75 3V35s £100 + many more P.O.A.				
WORKING A G11s	ALL OUR PRICES NCLUDE VAT	PHONE FOR OUR PRICE LIST	VIDEOS ALWAYS AVAILABLE		enquiries welcome es nly a phone call a and place your	way so ring today		
UNIT D/B, PROJECT 9 INDUSTRIAL ESTATE, McPHAIL STREET, GLASGOW G40 1ND 041-554 7637 (Gerry) All prices plus VAT.								

No. 3 LIST BAKERS DOZEN PACKS All packs are £1 each, if you order 12 then you are entitled to another free. Please state which one you want. Note the figure on the extreme left is the pack ref number and the next figures is the quantity of items in the pack, finally a short description

- BD152 Gas or liquid shut off valve, clockwork dial, setting can be on for up to 12 hours. Same as BD152 but thermostatically operated 12v operated drip proof relay, ideal for outdoor or increa operations. BD153 BD154 12v operated drip proot relay, rulear for outdoor, or, in-car operation. 12 way Samp screw down polythene bodied connector strips. Used to be called choc blocks when made of Bakelite 12 way 25amp connector blocks. Plug together 12 way connector blocks, ideal for nuick inins in leads. BD158 4 BD159 BD160 10 quick joins in leads. Component mounting tag strips each with 50 BD168 2 stand up tags. Short wave air spaced trimmers 3-30pf. Screw BD169 4 Short Short wave air spaced trimmers 3-30pf. Screw driver operated Assorted neon type numicator tubes made by BD170 4 HIVAC BD175 1 2watt mains motor driving gearbox, final speed 200rpm 12v Lilliput bulbs Panel mounting BD177 5 3 Panel mounting slim line indicator lights with amber lens. These take Lilliput bulbs. Oblong mains neon indicator lights, approx 1in. × BD178 BD179 3 PVC grommets for insulation through 3/s hole BD181 BD182 100 25pf air spaced tuning capacitor, small hole fixing 20am plate to the space of the second state of the second state of the space of the second state of the se BD189 1
- BD190 1 BD191 Lamp holder adaptors which take two pin plugs, 6
- also supplied BD200 BD205
- also supplied. 10 digit switch pad, telephone type. Very small 12v operated relay with one pair change-over contacts Mains transformer 230v primary and two 8v
- BD212 1 /zamp secondaries.
- 5 core curly leads, tinsel wire for phones, etc. Sub-min toggle switches double pole double BD213 BD214
- throw BD215 4
- Mini dpdt slide switches with chrome dolly instead of the usual plastic toggle. Standard wire ending push-ons for standard 1/4in. BD217 100
- tags. Ditto, but right angled. Soldercon tags. With these you can make your own sockets for ICs etc. 100 100 BD218 BD219
- 200 watt fire spirals, bright nickle chrome wire Battery operated motor made for 9v cassette players but speed controllable by lowering voltage. 50k quad pots. Standard 1/4in spindle single hole BD223 BD224 4
- BD227 4
- fixing Ice stat thermostat. Ideal for controlling water pipe BD228 1 antifreeze coils.
- antifreeze coils. Instrument buzzer, variable low, medium or soft. Eagle educational kits. One makes chemical bal-ance with weights and the other has electricals for experiments. 500uf + 500uf 50v electrolytics. Mains transformer with 9v 750mA secondary. Computer grade electrolytic 3150uf at 40v. 8×4 f6ohm loud speakers permanent magnet, 5 watte BD229 BD233 2
- BD234 4
- 2
- watts. Standard size ½meg pot with ¼in spindle and dp BD246 4
- BD247 1
- Standard size Vameg pot with Vain spindle and dp switch. The medium wave permeability tuner, couple this to a ZN414 and you have a radio. A noise suppressor/mains filter 13A socket on plate with spur, fits normal oldedical become BD248 BD249
- electrical box.
- BD253 Oven thermometer - bimetal type, reads 200-500°F 1

There are over 1,000 items in our Bakers Dozen List. If you want a complete copy please request this when ordering.

CAMERAS. Three cameras, all by famous makers. Kodak, etc. One disc, one 35mm and one instamatic. All in first class condition, believed to be in perfect working order, but sold as untested. You can have the three for £10 including VAT, which must be a bargam – if only for the lenses, flash gear, etc. Our ref 10PS8

EQUIPMENT WALL MOUNT: It is a multi-adjustable metal bracket that could be used for mounting flood light, bud speaker. TV camera, even a fan and on almost any sort of wall or ceiling even between wall and ceiling. The main fixing brackets rotate such that an inward or an outward comer can be accommodated front panel also lifts upwards or downwards to a reasonable angle and can be easily removed separately for wring A very useful bracket Regular proc would be around £6 each. Our price only £3. Our ref 3P72 or 2 tor £5. Our ref 5P152

MICROPHONE LEADS. 6m twin screened wire terminating one end with a standard ¹/4in mono jack plug and the other end with the usual screwed on microphone connector. With colled spring for lead protection. Price £1 Our ret 87214

EXTRA SPECIAL CROC CLIPS. Medium size, just right for most hook-ups Normally sell for around 10p to 15p each. These are insulated and have a length of wire connected to them but this is very easy to snip off if you do not need it. 20 for \$1. Our ref BD117A

DON'T MISS THAT IMPORTANT CALL. Fit an extension lead and take your phone in the other room with you 5m long, one end has the standard flat BT socket and the other the standard flat BT plug so you don't have to interfere with the house phone winng, you simply plug it in Proce £3. Our ret 3P70.

COPPER CLAD PANEL for making PCB. Size approx 12in long \times 8¹/₂in wide Double-sided on fibreglass middle which is guite thick (about 1/16in) so this would support guite heavy components and could even form a chassis to hold a mains transformer, etc. Proc £1 each Our rel BD683

POWERFUL IONISER

Generates approx. 10 times more IONS than the ETI and similar circuits. Will refresh your home, office, shop workroom etc. Makes you feel better and work harder – a complete mains operated kit, case included £12.50 + £2 PAP. Our ref 12P5/1.

LINEAR RECORD PLAYER. Made by BSR, their ref VL315. Hailed as the most sophisticated of record players, is completely electronically controlled. Due to cancelled export order we are now able to other these brand new, complete with carridge and diamond stylus at only £15 plus 52 post. This is a 12v DC operated unit. Our ref 15P25 Two or more post free.

VIDEO TAPES. These are three hour tapes of superior quality, made under licence from the famous JVC Company. Offered at only £3 each. Our rel 3P63. Or 5 for £11. Our rel 11P3. Or for the really big user 10 for £20 Our rel 20P20

ELECTRONIC SPACESHIP



ELECTRONIC SPACESHIP. Sound and impact controlled, responds to claps and shouts and reverses when it hits anything. Kil with really detailed instructions I cleal present for budding young electrician A youngster should be able to assemble but you may have to help with the soldering of the compo-nents on the pob Complete kit £8 Our rel 8730.

THERE IS GOING TO BE A BURIAL! For several years now we have been offering mains operated clocks at only £1 each. These are cooker clocks which in addition to telling you the time would also switch tings on and off at pre-set times. However, despite this sully proce these have been very slow sellers and as we have still almost 10,000 of them in a strea which we have in dear use nor maintenance. store which we have to clear we are making one even siller final offer before burying them. You can have 16 brand new clocks still in onginal packing for only 25. Our ref 5P151 Add 23 post if not collecting. BUSH RADIO MIDI SPEAKEDS

BUSH RADIO MIDI SPEAKERS. Stereo pair BASS reflex system, using a full range 4in criver of 4ohms impedance. Mounted in very nicely made black fronted wainut finish cabinets. Cabinet size approx 81/2in wdg. 14in hgh and 31/2in dege. Fitted with a good length of speaker filex and terminating with a normal audio plug. Price £5 the pair plus £1 post. Our ref 5P141

31/2in FLOPPY DRIVES. We still have two models in stock. Single sided, 80 track, by Chinon This is n the manufactures in slock single leads and ICD connectors. Price 1240, reference 40P1, Also a double sided, 80 track, by NEC. This is uncased. Price 159,50, reference 60P2. Both are brand new Insured delivery £3 on each or both.

ATARI 65XE COMPUTER



At 64K this is most powerful and suit-able for home and business. Brand new, complete with PSU, TV lead, own-er's manual and six games Can be er's manual and six games Can be yours for only £45 plus £3 insured delivery.

REMOTE CONTROL FOR YOUR 65XE COMPUTER. with This outil you can be as much as 20 feat ways as you will have a pystock that can transmit and a receiver to plug into and operate your computer and TV. This is also just right you want to use it with a big screen TV. The youth that can be also just right you want to use it with a big screen TV. The such or use for additional control and one handed play. Price £15 for the rado controlled pair. Our ref 15P27.

65XE COMPENDIUM. Containts: 65XE Computer, its data recorder XC12 and its joystick, with ten games, for £62 50 plus £4 insured delivery.

AGAIN AVAILABLE: ASTEC PSU. Mains operated switch mode, so very compact Outputs: +12v 2.5A, +5v 6A, ±5v 5A, ±12v 5A Size: 71/4in long × 43/8in wide × 23/4in high. Cased ready for use Brand new. Normal price £30+, our price only £10, add £1 post. Our ref 10/P34.

VERY POWERFUL 12 VOLT MOTOR. Vard Horsepower Made to drive the Sinclair C5 electric car but adaptable to power a go-kart, a mower, a rail car, model railway, etc. Brand new. Price £20 plus £2 postage. Our ref 20P22

PHILIPS LASER

PHILIP'S LASEH This is helium-neon and has a power rating of 2mW. Completely safe so long as you do not look directly into the beam when eye damage could result. Brand new full spec, 230 plus 25 insured delivery. Maina operated power supply for this tube gives 8kv striking and 1.25kv at 5m Å running. Complete kit with case £15, ditto for 12v battery. Also £15, Our net 15x2

ORGAN MASTER, Is a three octave musical keyboard. It is beautifully made, has full size (gano size) keys, has gold plated contacts and is complete with nbbon cable and edge connector. Can be used with many computers, request information sheet. Brand new, only £15 plus £3 postage Our ref 15P15 compu... postage

FULL RANGE OF COMPONENTS at very keen prices are available from our associate company SCS COMPONENTS. You may already have their catalogue, if not request one and we will send it FOC with your goods

A REAL AIR MOVER. Circular axial fan. It moves 205cu ft per minute which is about twice as much as our standard 4 /2m square fans. Low noise, mains operated, 61/2m diameter. Ex computers. Regular price over 230 but yours for £10 if you order quickly. Our ref 10P71 A

HIGH RESOLUTION MONITOR. 9in black and white, uses Philips http://http://www.made.pu.pu.al.acquered frame and has open sides. Made for use with OPD computer but suitable for most others. Brand new, £16 plus £5 post. Our reference 16P1

12 VOLT BRUSHLESS FAN. Japanese made. The popular square shape (4¹/₂in × 4¹/₂in × 1³/₄in). The electronically run fans not only consume very little current but also they do not cause interference as the brush type motors do. Ideal for cooling computers, etc., or for a caravan. £8 each. Our ref 8P26



FUD DARTGARM 31/2n made by Chnon of Japan. Single sided. 80 track, Shugar, compatible interface, interchangeable with most other 31/2n and 51/4in drives. Completely cased with 4 pn power lead and 34 pn computer lead £40 plus £3 ins det. Our ref 40P1.

MINI MONO AMP, on p c.b. size 4" × 2" (app.) Fitted volume control and ahole for a tone control should you require it. The amplifier has three transistors and we estim-ate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low proce of £1.15 each of 13 for £12.00



BRIGHTON, SUSSEX BN3 50T. MAIL ORDER TETMS: Cash, P.O. or cheque with order. Orders under 520 add 51 50 service charge. Monthly account orders accept from schools and public companies Access & Bivard orders are accepted – minimum 55 Phone (0273) 734648 or 203500

NEW THIS MONTH

POPULAR ITEM AGAIN AVAILABLE. Twin 0005 tuning capacitor with normal Vain spindle now listed by many firms at over £10 each. We have them brand new and in perfect condition at £2 each. Dur ref 2P40

 $\begin{array}{cccc} \textbf{SUB-MIN} & \textbf{PUSH} & \textbf{SWITCHES.} & \textbf{Not much bigger than a plastic transistor but double pole ~ \ensuremath{\mathbb{PCB}}\xspace$ Three for $\ensuremath{\mathbb{E}}\xspace$ Our ref BD688.

CARTRIDGES for the Double Microdrive Price 4 for £5. Our ref 5P146.

NICAD CHARGER UNIT. Metal pronged, plastic case contains mains transformer and rectrifiers with output lead and plug – made to charge two cells but no doubt adaptable or wonderful spares value. Only 50p each, two for £1. Dur ref 0B385.

EDGEWISE PANEL METER. If you are short of panel space then this may be the answer II has a FSD of 100µA and a rice full vision scale. It fits through a hole approx 134in \times 12/in Another feature is that it has an indicator lamb behind the scale which you could light up, it would then serve as an on/off indicator. Price Ω 1 our ref B070

AA CELLS. Probably the most popular of the rechargeable NICAD types 4 for £4. Our ref 4P44

COMPUTER SPECIAL. The Perex 16meg Byte tape streamer. These are brand new and really an exceptional bargain. A few only so hurry. Only Ω 15 Dur ref 15P29

20WATT 40CHM SPEAKER. With built-in tweeter Really well made unit which has the power and the quality for h-fi reproduction 6/2m dameter Proce S Dur rel 5P155 It is heavy so please add £1 to cover postage if not collecting.

MINI RADIO MODULE. Only about 2in square with ferrite aenal and solid data tuner with its own knob it is a superhet and it operates from PPD battery and would drive a crystal headphone direct but be better with our mini mono amp. Price £1. Our ref B0716

BULGIN MAINS PLUG AND SOCKET. The old faithful 3 pin with screw terminals. The socket mounts through a 1½ in hole and the mains is brought in by the insulated plug. Used to be quite expensive but you can have 2 pairs for £1 or 4 of either plug is socket for £1 you could make yourself a neat and compact bench panel with these. Our ref 80715, 807155 or 80715P.

MICROPHOME. If you want a low cost microphone then just arrived we have a very small hand-held dynamic mic with on/off switch in the handle, its lead terminates with one 3.5 plug and the other a 2.5 plug for remote control. Price only S1 Our rel BY11

EXTENSION CABLE WITH A DIFFERENCE. It is flat on one side making it easy to fix and to leok tidy. It is 4 core so suitable for telephone, bell, burglar alarms, etc. 50 yard coil for £5 Dur ref 5P153

MOSFETS FOR POWER AMPLIFIERS AND HIGH CURRENT DEVICES. 140v 100w pair made by the famous Hitach Company Reference 25K413 and its compliment 25J118 Dnly £4 the pair Our ref 4P42.

BATTERY OPERATED TRAVEL MECHANISM. On a plastic panel measuring approx $9n \times 3^{1}/2n$ is driven by a reversible 12v battery motor, littled with pulley and belt which rotates a threaded rod and causes a platform to travel backwards and forwards through a distance of approx 5n Price 25. Our ref 5P140.

MAINS OPERATED WATER VALVE with hose connection for inlet and outlet suitable for low pressure Auto plant watering, etc. Only £1 each. Our ref BD370. 20 VOLT 4AMP MAINS TRANSFORMER. Upright mounting with fixing feet. Price £3 Our ref 3P59

16 OHM PM SPEAKERS. Approx 7in × 4in. 5 watts Offered at a very low pro so you can use two in parallel to give you 10 watts at 8 ohms £1 for the two 0 ref BD684

EHT TRANSFORMER. 4kv 2mA Ex-unused equipment £5 Our ref 5P139

4 CORE TINSEL COPPER LEAD. As fitted to telephones, terminating with flat BT plug 2 for £1 Our ref BD639.

EHT TRANSFORMER, 8kv 3mA £10 Our ref 10P56

VERY USEFUL MAGNETS. Flat, about 1in long, 1/2in wide and 1/4in thick. Very powerful 6 fcr £1 Our ref BD274(a)

ACORN COMPUTER DATA RECORDER. Ref ALFO3 Made for the Electron of BBC computers but suitable for most others. Complete with mains adaptor, le and handboo⊨ £10.00. Ref 10P44. Add £2 special packing.

SOLAR CELLS. Will give a good current (depending on size) from sunlight or bright daylight: Module A gives 100mA. Price 11 Our ref BD631 Model C gives 400mA. Price 52. Our ref 2P199. Module D gives 700mA. Price 53. Our ref 3P42.

SOLAR POWERED NI-CAD CHARGER 4 NI-CAD batteries AA (HP7) charged in eight hours or two in only 4 hours. If is complete, boxed ready to use unit. Price 26 Our Ref. 4P3

METAL PROJECT BOX. Ideal size for battery charger, power supply etc. sprayed grey, size 8" $\times 4^{1}$ /4" \times 4" high, ends are lowered for ventilation other sides are flat and undrilled. Price S3 Order Ref. 3P75

13A PLUGS. Sleeved and complete with fuse, parcel of 5 for £2 Order Ref.

13A ADAPTERS - Takes 2 13A plugs, packet of 3 for £2. Order Ref 2P187 $\label{eq:20v-0-20v-Mains transformers 2^{1/2} amp (100 watt) loading, tapped primary 200-245 upright mountings £4. Order Ref. 4P24$

CAPACITOR BARGAIN – axial ended – 4700uf (// 25v Jap made Normally 50p each, but your will get 4 for £1 Ref 613

SINGLE SCRIEENED FLEX 7.02 copper conductors, pvc insulated then copper screene finally outer insulation. In fact quite normal screened flex 10 £1. Our rel Bi#668

3 CORE FLEX BARGAIN No. 1 – Core size 5mm so ideal for long extension leads carrying up to 5 amps or short leads up to 10 amps 15mm Ω 2 Ref 2P189

3 CORE FLEX BARGAIN No. 2 - Core size 1 25mm so suitable for long extension leads carrying up to 13 amps - or short leads up to 25A, 10m for £2 Order Ref 2P190

Other field of the criste ALPHA-NUMERRIC KEYBOARO – this keyboard has 73 keys with contactless capacitance switches giving long trouble free life and no contact bounce. The keys are arranged in two groups, the main area fields a GWERTV array and on the right is 15 key number pad, board size is approx. 13 × 4 – brand new but offered at only a fraction of its cost namely [3, plus £1 post. Ref. 3P27.

ATH HORSEPOWER 12 VOLT MOTOR. Made by Smiths, the body length of this is approximately 3in, the diameter 3in and the spinel & 1/6th of an inch diameter it has a centre flange for fixing or can be fixed from the end by means of 2 must. A very sowerful little motor which revs at 3,000 rpm. We have a large quantity of them so if you have any projects in mind then you could rely on supplies for at least two years. Price 16 Dur ref 6P1, discount for quantities of 10 or more

3 VOLT MOTOR Very low current so should be very suitable for working with solar cells £% each Our ref 80681


PET CAPACITOR MICROPHONE EAGLE CI.200. Output equivalent to a high rease informatic microphone while retaining the characteristics of a capacitor class dynamik. microphone while retaining the characterist microphone Price £1. Our ref BD646.


 $\mbox{SUB-MIN TOGGLE SWITCH.}$ Body size 8mm \times 4mm \times 7mm SBOT with chrome dolly fixing nuts. 3 for $\epsilon 1.00$ Order ref BD649

SUB-MIN PUSH SWITCH OPDT. Single hole fixing by hexagonal nut 3 for £1 Our ref BD650

CORNWALL COMPON 31

BARCLAYCARD

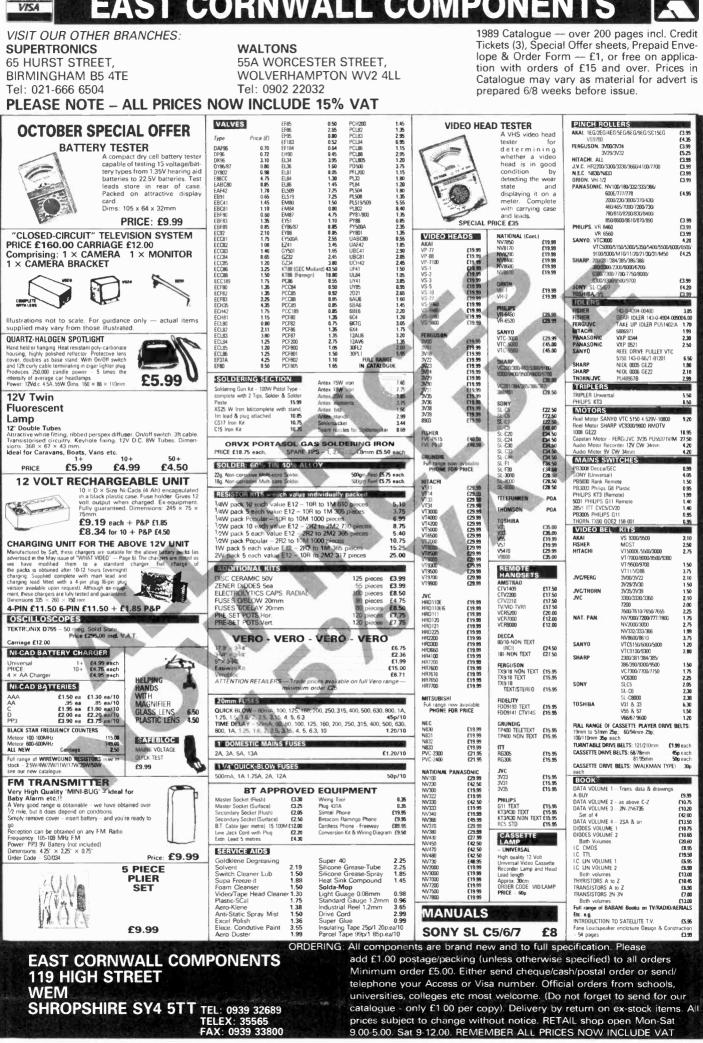

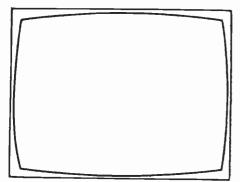

EDITOR

John A. Reddihough

Please note that the telephone numbers below are for contact with the advertisement departments only. Editorial enquiries should be sent to the editor at the address given on page 897.

ADVERTISEMENT MANAGER

David W.B. Tilleard 01-261 6671

SECRETARY

Janet Reeve 01-261 6671

CLASSIFIED ADVERTISEMENTS

Pat Bunce 01-261 5942

ADVERTISEMENT COPY AND MAKE-UP

Ron Scorey 01-261 6035

SUBSCRIPTION ENQUIRIES

0444 440 421

CORRECTIONS

The satellite TV servicing aid (see August issue) should not in its present form be used with the Grundig head unit. See letter on page 919.

A pin connection is omitted in Fig. 2, page 925. Pin 57 RAOV is an output from the RAM address generator.

HELD OVER

Due to shortage of space in this issue several items we had planned to include have had to be held over. This includes the Service Bureau page.

COVER PHOTO

This month's cover photograph shows a Panasonic Model TC2000. See U3/ U3W chassis servicing article on pages 910-912.

TELEVISION OCTOBER 1989

TELEVISION

Sky's Take-off?

Sky Television has made an astute move in offering viewers an "all-in" package for reception of its programmes. For $\pounds4.49$ a week the viewer gets the receiving equipment installed, with maintenance, and access to Sky's four-channel service. The company is backing its move into the rental field with a $\pounds21m$ advertising campaign. Between September 2nd and the end of the year $\pounds10m$ will be spent on TV and press advertising. A further $\pounds11m$ has been earmarked for the first half of 1990. Sky Movies is to start scrambling on February 1st 1990 when a $\pounds2.29$ weekly charge will be made to receive the channel: there will however be no extra charge for those who take up Sky's $\pounds4.49$ a week offer. Subscribers also have to pay a deposit of $\pounds35$. The minimum contract period is one year, after which anyone who decides to terminate the contract will get the $\pounds35$ deposit refunded.

Installation is being handled by a 1,200 strong network of engineers able to carry out around 75,000 installations a month. The firms involved are Cranleigh Aerials, Satellite Aerials of Watford, StarTrak and Tele Aerial Satellite. Amstrad and Cambridge Computers are providing the basic receiving equipment, with Philips and Thomson contracted to supply decoders for the scrambled transmissions when these start. Apparently the initial agreement with Amstrad and Cambridge Computers is for the supply of over half a million receivers – Amstrad has orders for 460,000. There should be no problems here in view of the present excess production capacity in the industry. Sky is holding discussions with other suppliers.

Sky's move to supply the public directly is likely to upset the trade no end – its terms are certainly competitive and the move could represent a massive bypassing of the established trading system. Applications are being handled by Sky staff at Livingston and Peterborough, the aim being to arrange for installation anywhere in the UK within ten working days of the initial enquiry. During the next year Sky expects 55 per cent of its viewers to be direct subscribers, with 30 per cent buying their own equipment from High Street outlets and 15 per cent renting from the usual organisations. Those who already have equipment have not been overlooked: anyone who buys a dish before September 30th will be provided with a decoder for just a £15 refundable deposit and will be exempted from the $\pounds 2 \cdot 29$ a week charge for the first six months after scrambling starts.

This looks like a make-or-break effort on Sky's part. It represents a huge potential investment, but the modest looking \pounds 4·49 a week could well prompt many waverers to equip themselves for Sky reception. With the deposit, the first year's charge comes to \pounds 268·48, which is perhaps not quite so cheap looking. The final outcome will depend of course on viewer satisfaction with the programmes provided. In this connection research commissioned by Sky shows that 81 per cent of present satellite TV viewers have expressed satisfaction with the services, with 60 per cent using satellite TV to complement their viewing of ITV/BBC programmes and 40 per cent viewing mainly the satellite TV transmissions.

Sky's aim in committing itself to this major investment and the extensive promotion is clearly to get its services accepted by the public prior to BSB's delayed launch. Sky hopes to get back on target of having its services available in 1-15m households by the end of January 1990. This would of course bring with it substantially increased advertising revenue. And in the long run Sky will benefit from subscribers paying their £4-49 a week indefinitely.

Meanwhile Rupert Murdoch made quite a stir with his James MacTaggart Memorial Lecture at the Edinburgh International Television Festival. This was a strange effusion – though such occasions are not known for down-to-earth contributions. There was reference to a "wide variety of channels" and mention of the possibilities of cable – apparently he sees fibre optic cable as being able to make available to all "a global cornucopia of programming and nearly infinite libraries of data, education and entertainment". If he feels too strongly about cable why is he playing about with Sky's satellite channels? Well of course Astra is giving him enough to worry about for the present. But haven't we heard all that about the potential of cable before? It's a matter of cost and whether there's a real need. Rupert the visionary doesn't seem to pay sufficient regard to the finite conditions in which every economic activity has to operate. One suspects that in practice he's far more concerned with the day-to-day nitty gritty than his lecture suggests.

Why did he feel it necessary to make such heavy-handed criticism of the existing TV arrangements in the UK? They have their shortcomings, but it's hard to envisage a greatly improved system, and the "private" services in parts of Europe hardly instil confidence. Television, our Rupert tells us, is "in transition to a future offering consumers new choice". Lack of competition can certainly lead to poor programming, but his suggestions of a great new TV world seem to be something of a mirage. But by all means let's see what Rupert can make of the opportunities he has siezed.

Binders

New arrangements have been made to enable readers to obtain binders for their copies of *Television* Each binder holds twelve issues and costs £4.50. Orders should be sent to Television Binders, 78 Whalley Road, Wilpshire, Blackburn BB1 9LF. Make cheques out to Television Binders.

Servicing the Panasonic U3/U3W Chassis

The Panasonic U3 and U3W chassis are virtually identical. They succeeded the U2 chassis which was covered in the February 1985 issue of *Television*. Models fitted with the U3 and U3W chassis include the TC208, TC221, TC225, TC2000, TC2011, TC2024, TC2211, TC2213, TC2216, TC2221, TC2223, TC2226, TC2622 and TX2284. The range ran from 20 to 26in. tubes and from standard through to remote control with teletext. A large number of these sets are still in service but the life of some of them has been cut short by premature failure of the c.r.t.

Purple Electrolytics

Those who have worked on the U2 chassis will have noticed the number of faults caused by defective electrolytic capacitors. This was a problem with Panasonic sets of this era. As a rule only the dark purple capacitors are affected. When servicing these sets a check on all these capacitors should be the first job. There are two reasons for this. First the symptoms that occur when one of these capacitors is faulty can be very strange and misleading. Secondly you won't miss any that are beginning to show signs of deterioration, thus preventing call-backs. The troublesome capacitors are on the main horizontal section of the chassis and the c.r.t. base panel.

Your first check should be to wiggle and pull each of these capacitors. This will usually result in at least one of them coming away in your hand. What happens is that electrolyte begins to exude in a brown, powdery form around the positive leg. This highly corrosive material rots the leg away and begins to eat into the Paxolin panel. In really bad cases the powder can be found on the print side of the panel, having eaten its way through the PCB hole where the capacitor's positive leg once resided. The next step is to remove each capacitor in turn and inspect it for signs of leakage. This may sound like a lengthy job, but in practice it's soon done and definitely pays dividends.

Any leaky capacitors should of course be replaced, but make sure that all electrolyte on the panel has been thoroughly washed away with alcohol or something similar before you carry out any soldering in the affected area. The electrolyte spits when heated and if left will corrode the PCB. Use capacitors from Panasonic as replacements for the purple ones. Circuit references of the suspect capacitors include C572 (10μ F, 250V), C551 (100μ F, 35V). C558 (1,000µF, 25V), C356 (1µF, 350V),C854 (47µF, 250V), C856 (47µF, 35V), C809 (1µF, 250V) and C853 (100 μ F, 250V). Some of the symptoms that arise when these capacitors fail are: varying sound level; purity errors; one side of the screen dark while the other is progressively lighter; varying brightness level; a high pitched whistle from the power supply; ringing on the picture; and corrugated verticals on the picture.

Tuning System Faults

Failure of the tuning system has been a problem in recent years. These sets employ a search and store arrangement and the symptoms vary from not searching and/or storing to no front panel operation (remote channel change etc.) due to heavy loading on the 12V supply.

910

The cause of the trouble is the tuning/memory chip which is IC1101 (TMS3452N2L) in some sets, IC1103 (TMS3453N2L) in others. If the supply is excessively loaded, lift pin 40 of this device as a check. On board TNP66035ZA this condition will usually be accompanied by overheating of R1214 (330Ω , 1W). These problems seem to occur when a set comes in for the first time since it was new, for example when being overhauled for rerenting. Note that these chips are static-sensitive devices, so the proper precautions should be taken when fitting a replacement. Also the auto-search must be operated immediately after the replacement in order to initialise the chip.

There are occasions when the 12V rail is low or missing and this is not due to excessive loading. On board TNP66035ZA a check around the 12V regulator circuit should reveal the cause of the trouble – suspect items are R1151 (22Ω , 0.5W), Q1124 (2SD762) and zener diode D1117 (QA116R2). Note that R1151 is a critical safety component. Board TNP66048ZA has a simple zener diode 12V regulator circuit. On one occasion I've had an open-circuit secondary winding on transformer T1101 (TLP15275).

No Go

The no go condition is usually accompanied by a scream from the power supply, indicating the presence of an overload. My approach to this is to check the following items. This will usually bring the culprit(s) to light. First the two diodes D552 and D553 in the EW modulator circuit. D552 is type TVSC27-15M and D553 type TVSC2406M. Check these as a pair - when one goes the other usually follows. If you have to replace them you may find that with the set working there's no EW correction as the driver transistor Q753 (2SD762) has been adversely affected by failure of the diodes. This sequence of events is also experienced with the earlier U2 chassis. Use genuine replacements. Many engineers are tempted to use a BYX71-600 or the heftier BY223. These will work, but their long-term reliability in this circuit is poor. As is often the case, European semiconductor devices don't last in Japanese line output or power supply circuits.

If the EW modulator diodes are o.k., check the following: the BU208A line output transistor Q551; the 2SC2653 line driver transistor Q501; the RH15 195V supply rectifier D555; the ERC24-06M 26V supply rectifier D554; the ERC24-06M 18V supply rectifier D556; the TVSC2408M h.t. supply (160V with 22 and 26in. sets, 128V with 20in. models) rectifier D851; and the RU3N 27V supply rectifier D852. Also check the ERZC10ZK241U protection diac D854 – very often it has a hole blown in its side. This item is connected across the h.t. supply. Measure the h.t. at TPS1 or the positive leg of the reservoir capacitor C853.

If you still have a non-working set, try lifting one end of the h.t. smoothing choke L851 and connecting a bulb as a dummy load across C853 (TPS1 is on the output side of the choke). If the h.t. comes up, you've got an overload. In this situation I'd be tempted to suspect the line output transformer. While Panasonic line output transformers are exceptionally reliable, I have had the odd one fail. If

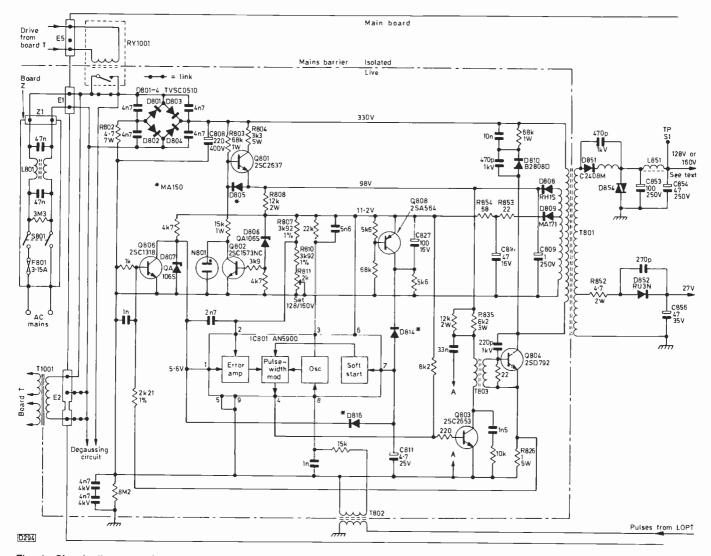


Fig. 1: Circuit diagram of the chopper power supply used in the Panasonic U3 and U3W chassis. The e.h.t., 195V, 26V and 18V supplies are derived from the line output transformer. The 18V supply feeds the 12V regulator.

possible check it out of circuit with a Megger. Check every other possibility before condemning the transformer – it rarely fails.

If the h.t. doesn't come up with the dummy load, the fault will be in the power supply. A check on the following items should reveal the cause of the fault. First check the 4.7Ω , 7W surge limiter resistor R802 – note that it's on the negative side of the mains bridge rectifier. It often goes open-circuit. We've also had cases where the 220μ F, 400V reservoir capacitor C808 has become leaky. This is a silver can electrolytic, not one of the purple ones. If there's no voltage at the base of Q801 you'll find that R803 (68k Ω , 1W) is open-circuit.

No output from the power supply is very often caused by one of the transistors having gone short-circuit. The chopper transistor Q804 (2SD792) is an obvious suspect. If it's o.k., go on to check Q801 (2SC2637), Q802 (2SC1573NC), Q803 (2SC2653), Q806 (2SC1318) and Q808 (2SA564). Also suspect the QA1-06SB reference zener diode D807 and R835 ($8.2k\Omega$, 3W). The resistors in series with the h.t. adjustment potentiometer R811 should be checked carefully - R807 and R810 have a tolerance of one per cent. It's rare for the AN5900 chopper control chip IC801 to be faulty but this can happen. And all the electrolytics should checked. A loud, high-pitched whistle from the chopper transformer, sometimes coupled with a line running down the screen and

TELEVISION OCTOBER 1989

ρ

line tearing, can be caused by C809 (1 μ F, 250V), C853 (100 μ F, 250V) or C854 (47 μ F, 250V).

If the mains fuse F801 has blown you'll probably find that two of the TVSC0510 mains bridge rectifiers D801-4 have gone short-circuit. An alternative cause is an intermittent short-circuit in the degaussing posistor D812.

If the set intermittently goes into the standby mode when switched on, the contacts on the relay are probably carbonised – they can be cleaned.

A final point about the power supply: Panasonic mains switches are exceptionally reliable.

If the power supply is in order but the line output stage is dead check whether the h.t. feed resistor R559 (22 Ω , 20W) is open-circuit. Failure of the line timebase has on occasion been traced to the AN5435 sync/timebase generator chip IC501.

Bowed Sides

If the sides of the picture are bowed in, check the EW modulator driver transistor Q753 (2SD762).

Intermittent Shutdown

Intermittent shutdown is not a common fault. When it does occur, try replacing the 11V zener diode D501. This usually clears the trouble. If not it will be necessary to provide the power supply with a dummy load bulb and

carry out detailed checks - the trouble is usually due to thermal failure of one of the previously mentioned transistors in the power supply. The "heavier" components in the line output stage don't usually fail intermittently.

Field Faults

The most common field faults are lack of height and field collapse. They are often intermittent. Resoldering the connections to the field output transistors Q402 (2SD856) and Q403 (2SD837) used to cure this fault in nine out of ten cases. They are mounted, along with the EW modulator driver transistor Q753, on a large heatsink that runs across the depth of the bottom panel, about a third of the way in from the left as you look in at the back of the set. More recently we've tended to find that the transistors themselves are faulty - usually both leaky or one or the other short-circuit. Also check R430 (0.82Ω, 0.5W). The electrolytic to watch here is C414 (2,200 μ F, 35V).

Fault Guide

For no sound or vision with the raster present check whether there is 12V at the emitter of the 12V stabiliser transistor Q552 (2SD762). Check O552, D558 (MA26WO) and zener diode D559 (QB111ZB) if this voltage is absent.

As previously mentioned, problems due to the tuning/ memory chip are common. A not so common cause of no signals is the 33V regulator IC70 (μ PC574J) having gone short-circuit. In this event you might well find that its feed resistor R71 (22k Ω , 1W) is open-circuit. A faulty tuner usually results in a snowy picture rather than no signals. Fit the improved type TNV87510F2T. For low gain in poor-signal areas fit modification kit XFMK83-1.

For no sound, first check that the 27V supply is present at pin 10 of the STK4019 audio output chip IC251. If not, suspect that R852 (4.7 Ω , 2W) or R257 (3.3 Ω , 1W) is open-circuit. If R257 is open-circuit suspect that IC251 is also faulty.

Varying sound is not as common a problem with this chassis as with the U2 - thank the Lord! The first thing to do - you guessed it - is to check the electrolytics associated with the sound circuitry. Next favourite is the RD12 zener diode D251.

There are no stock faults in the i.f. and colour decoder sections of the receiver. No colour has on occasion been traced to the crystal X601 (TSS116M1).

For no picture with the c.r.t. cut off check R323 (10 Ω). For an overbright raster check the surge limiter R556 (22 Ω) in the 190V supply. For varying brightness or one side of the picture being brighter than the other check C572 (10µF, 250V) and C356 (1µF, 350V).

For lack of either red, green or blue check D604/5/6 (MA1130), R313/4/5 (270Ω) or Q351/2/3 (2SC2923).

If the c.r.t.'s heaters are out check R558 (0.56Ω , 0.5W).

Tube Life

As with the U2 chassis, these sets use the A51-570X, A56-540X and A66-540X range of tubes, which tend to fail before their time - or are we expecting too much in comparing them with the tubes used in older chassis such as the CVC5 series? Economically, to us replacement seems to be a dubious proposition. Some engineers prolong tube life by shorting out R558. This is not

usual Panasor there's a pocl The problem pocket when The simplest very little - t new case top the screw will available fron the complete the rubber c functions - ma stock electrc





Remote Co

incorporated On the whole (TF0A420K03



The magazine for all those interested in a technology that will not stand still-satellites, cable, video, equipment interfacing and high definition. Each monthly issue carries indepth servicing articles on TVs and VCRs with regular test reports and coverage of vintage and DX TV.

Ple

Na

(PL

Ac

...

Ti

• inc

available for All I've had t

Modifications

A number of production modifications were made. It's not really practical to check each set to see whether they've been incorporated. The following are worth noting where relevant to a particular complaint.

To improve the focus and peak white capability, change C351 from 180pF to 220pF, C352 from 120pF to 220pF, C353 from 180pF to 330pF, R351/2/3 from 10k Ω to 8.2k Ω (2W), R354 from 80Ω to 82Ω , R355 from 270Ω to 180Ω , R356 from 180 Ω to 82 Ω and R370/1/2 from 2.7k Ω to $1.5k\Omega$ (0.5W). These components are all on the c.r.t. base panel. On colour decoder panel B change R303 from $2.2k\Omega$ to $4.7k\Omega$, R309 from $68k\Omega$ to $270k\Omega$ and R325 from $22k\Omega$ to $27k\Omega$.

To prevent ringing/ghosting change C303 from 120pF to 82pF and R305 from $1k\Omega$ to 560 Ω .

To improve the red chroma replace R619 with a wire link, fit a $1.2k\Omega$ resistor (R631) in place of link J28 and add C629 (20pF). Additionally in Models TC2221/3 remove J14 and add R630 ($6.8k\Omega$).

Manual Errors

A couple of errors in the manual are worth noting. The sub-contrast control should be adjusted for a drive of 2.4V, not 3V. The sub-colour control should be adjusted for a 1.8V peak-to-peak waveform, not 2.3V p-p.


In Conclusion

In conclusion, the vital thing with these sets is to check the electrolytics. Apart from the odd rogue set the experienced engineer will have no problems with these chassis. The usual precautions should of course be taken. Remove flux after soldering and varnish joints. Clean up electrolyte and muck around the e.h.t. cavity.

The successor U4 and U4W chassis will be covered in a future article.

. . .

HIGH GRADE COMPONENT PARCELS

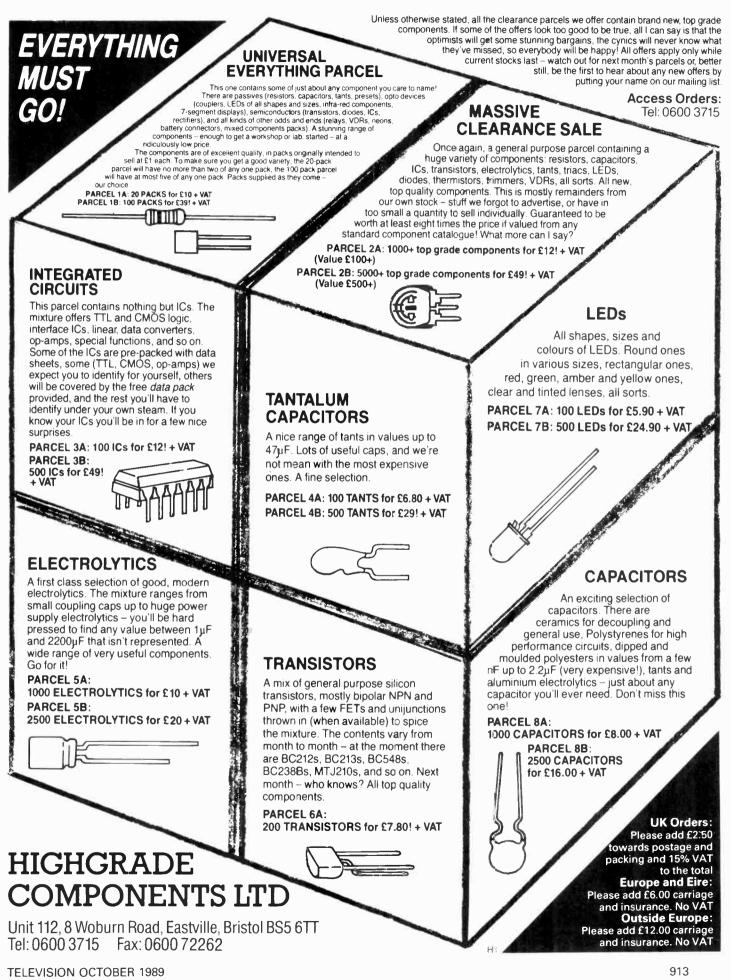

				<u> </u>		
SPECIAI		R	THI	S MO	NTH	
UNIVERSAL TRIPLER. NEW TYPE VIDEO LEADS		£4.00	4-6 Volts Relays		2	
AMSTRAD Line O.P. Transistors with Diode BU208A	£1.00	Send for list of video spare	THORN PANEL	£15.00 to £40. S		
VIDEO LAMPS, Long Lead			Thorn Panel with SAA501 515/753 509/12 515/357 564	2 IC /03 508 161 515/353 515/173 515/357	£2. £3.	
FIDELITY SPLIT DIODE FCC2215/ K30 FRONT PANEL TEL-TEX TYPE	AE£20 FCC2015BE£10 FCC2215B	E£10		TX9 TX90 NEW TX9 TX10 TX100		
NEW G11 LINE OP PANEL PHILIPS YEARS AHEAD		£9.00		THORN MAIN CHA	SSIS	
THE CREDIT CARD CALCULATOR Solar Powered NEW PHILIPS SBC 1833 Solar & Battery Powered Ca	lculator	£8.00	TX9, TX90, TX100, TX92	25 E15.00 TX10 An	ode Cap and Lead £1	
THORN PANEL TX9 REC & REMOTE PANELS with Mains Trans TX10 REC & REMOTE PANELS with Mains Trans				TEXT DECODER TX10	£8.00	
TX10 TUBE BASE ON PANEL		£3.00	TEXT DECODER VM610 PANELS VM6103/2 TRX	102 TRA	013 63	
THORN PANEL No. 515-353, 548.02, 564.01, 509/102, THORN TX STEREO SOUND O.P. PANEL (I.C. TA	. 515/173,508/161	£5.00 £1.00	DC and AC and Resistant		£12	
THORN VIDEO AERIAL AMP 01 M4-597-001 KT3-K30-K4-K40 CTX ETC Mains Switch	75p each	£6.00	GII 8 Touch Button with	£10.00	£18 TV AERIAL/VIDEO	
G8 LOPTS PHILIPS	£6.00	NEW IN -		Post £5.00	Combiner Switch and Sockets	
G11 LOPTS PHILIPS DESK TYPE Dual Power Calculator SBC1704	£3.00 £7.00	WANDER P	HONES Key Pad and Har	nd Set. No Case £1.00	Lead 50p	
K40 FOCUS POT 4.7μ KT3 W/W	£1.00 10 for £1.00		IVERSAL BATTERY TE CALCULATOR SBC 170		THORN RECEIVER	
FOCUS POT HDK TPA6006	£2.00	THORN 850		£2.00	564/314 564/323	
KT3 Triples K3 Tex Front Panels with LC's (SAA3027P/SAB3013/HO44 G8 100K Pots on Panel & Lead for 6 Push Button Unit	\$328) £6.00 £5.00 £2.00	NEW GEC 2 DX-TUNER	2110 LOPT VHF-UHF SEND FOR I	£2.00 DATA 50p	M293B1 SAA5012 £6	
K30 Mains Switch remote K35 Mains Switch remote K35 Aerusl Switch and Plug in Lead to Tuner	£1.00 75p £1,50	TUNER	POWER SUPPLY Mark 2	75p	HCF4556BE MC14493P	
LARGE Foacs Pots Tts Pye. GEC, 171, Decca	20p each 75p	THORN 900	0 4 7m 400V	-40p		
8 PUSH BUTTON UNIT for CTX Chassis £1.50 G8 Power Supply Panel £4.00		G8 TUNER G8 SPEAKI	V/CAP on Panel	£3.50 	THORN RECEIVER 564/314	
EX DECCA %(-10) Decoder £5.00 EX DECCA %(-10) Frame £5.00 THORN 8000-8500-5800 Decoder £6.00		9,000 SPEA	KER	£1.00	544/301 544/321	
GLASS BEADS Diodes 200v/1.2A	50 for £1.00	ONE LC K3	0 Sound OP Panel 35 Decoder	£30p £7.00	544/341 SAA1060	
G11 IF Panel £8.00 G11 Decoder Panel £8.00		K30 IF/K35 THORN Log		£2.00 £4.00	MAB8440P SAB3035	
JVC HEADS 31455 £20 G11 Condenser 470/250V 1TT £2.00 G9 Power Panel £3.50 G8 Transductor £1.25		THORN Lopt 8503-8803 £4.00 £6.00 TX9 THORN Tuner Panel with ICS Pots & mains trans. £3.00				
G8 Push Button Unit £2.00 G8 Con/Panel New Back Type £4.00		THORN 1600 Rec- & Anode Cap 50p KT3-K30 Slider Pots 4.7k £1.00 for 10 BRIDGES RECTIFIER				
KT4-KT3-K30 Handset Replacement HT520 METER 20,000 Fuse Diode Protector Logic Test Fac	£12.00 £15.90 £12.00	K35 20 Túrn Pots 6p each BR-31 50V 2Amp HITACHI & GEC 20k Pots and 100K and 69K Philips 20 for £1.00 8 for £1.00				
9000 SERIES Decoder 01 929 014 080 Thorn	£5.00	100K POT 8	k 20K v/cap type with band	l switch 5p		
LATEST VIDEO For Latest Philips, GEC, Pye and Hitachi, Front panel with LED's.	memory chip and push button and pots and £6.00 NEW	KT3 K30 Sp K30 Push B	weaker utton Switch 6 Way		TX90 MOD 37141B The Sweep Tuning System	
20AX GEC LOPT Panel with Split Diode RANK T20 Fouces Pot RANK 718 Fouces Pot	£4.00 75p £1.00	-	O/P Panel Plug in and KT	3 sound o/p £3.00 £1.50	TX9 139/001 £5.00	
16" LOPT Split Diode 2433481	£6.00	K35 L.O.P.T. Split Diode £6.00 T6070V TX9 Transi				
T703A LOPT Transformer Rank with Focus Pots and Diode		RANK 120 Front Fanel 20.00 C8.6 Button Unit, New Type \$2.00 C8.6 Button Unit, New Type \$2.00				
HITACHI Mains Switch	50p 	6 off LED D	DISPLAYS, Mixed	£1.00 £3.00	TX9 90D4-093-001-01G £1.00	
-I CONDENSER Axail Leads 450 A/C 1200 D/C MAINS TRANSFORMER 240v in/20v/8v	<u>15p</u>	AERIAL SP	TESTER, Infra Red	£1.00		
GREEN FLAT, NEC, LED's 15V015V 1 Amp Print Type £1	3p each 100 for £2		TIONAL Dynamic Micro OTS with Band Switch	bhone £2.00 10p	20MM 1Amp A5 Fuse £3.00 per 100	
12+12V 2.8VA Print 1"×1" 75p 8+8V 1 Amp Print 75p		PUSH BUT	TON Mains Switch with So	crew Holes Fixing 4 for £1		
ET596 UHF V/CAP Tuner, small £2.50 FIDELITY Panels with I.C. £1.00 FIDELITY LOPT Split Diode AT2076/80 £3.00		PYE 731 Li PYE 731 No	ne Trans ew Power Supply	£3.50 £4.00	TX90 TX925 TX100	
FIDELITY Panels with I.C. £1.00 FIDELITY LOPT Split Diode AT2076/80 £3.00 AT 2076/80 £5.00 ITT CVC20 to 45 PANELS Send for list 5.00		800s DIODES at 3 amps. Glass Beads 6p each. 20 for £1.00 Mains Switch with Standard Lead KT3 Line Output Transformer £5.00 3 for £1 or £				
MULLARD TEL-TEX DECODER Type VM6103 WE HAVE OVER 1,000 6 DIODE TRIPLER AT £1 EACH	£7.00	THORN 8500 Time Base £3.00				
THORN main T/V chassis complete TX9-TX10-TX90-TX92	5-TX 100 £15.00	7 SEG DISPLAYS 4 Bank Displays Z-4042T 25p 00 SPLIT DIODE FBS1245AR £5.00				
TX10 8 way button unit £8.00 TX900 with PRR-SR7 £6.00 PHILIPS VHS Tape 180 £2.25			PANEL PC895A7 LIST OF VIDEO SPARE	£10 S £13 to £46 HEADS	Mono 11 Piece Kit £8.00 Stereo 14 Piece Kit £8.00	
2431851 2433952	CTK Lopt 36212		RANSFORMERS	AT2036/00 AT2076/55 AT2048/11 AT2076/71T	SHARP MSHIFCF09	
2432211 2432984 2432301 K4 L.O.P.T. 2432491 K40 2432871 2434274 SPLIT-DI			2-338-30942 £1.00	AT2055 AT2080/15 AT2076/35 RCO ST CT33	TX9 LOPT	
2432871 2434274 OF LO P T 2432981 TX9 L.O P T 2432984 2432101-2 £10 EA			2-338-30633 £1.00 1-268-30050 £1.00	AT2076/38 OT2041 AT2076/51 FB165KA Oric CVC 820 2076/51		
2433212 TX100 Green Spot 2433481 Split Diode 1100 £15.00	36761 36831 PHILIPS	311 311	2-138-98094 £1.00 2-338-30634 £2.00	CVC 800 2432461 243345	ii EAUN 002-01	
2433581 2433751	36833	312 312	2-138-96044 £1,00 2-138-53861 £1,00	REGULATED POWER SUPPLY. Size 6"×5"×21/2" 0-3v = 0-4 5v = 0-6v Lamp Pre-set 3v-to-12 volts, 1	AMP TUNER IF for VT568 Hitachi	
ITT TUNER CAN I C Holders	T. 36921/79 E10 EACI SEND FOR LIST BRITISH MADE V.H.S.		<u>2-138-98094</u> <u>£1.75</u> DS from £15 to £20. \$	amp £5.00 Post £2_00	& GEC £9.00	
CMR 800/3 £20.00	SEND FOR DATA 20 AMP COST OVER \$4	100. 30 VOL		ELL POWER SUPPLY 19" RACK		
and Frame £5.00 DIL - DIL PIN DATA 40 Pin × 4 £1.00		IT. NEW. NO	ON/OFF SWITCH, NO	HANDLE WITH CORD. BLACK		
Min with co-ax socket UHF v/cap 42 Pin × 5 £1.00 tuner 40dB gain £1.50 or 10 for 28 Pin × 5 80p £10 16 Pin × 10 70p	1 DFF - NEW ROHDE & SCHWAR			A T.V./RF 25-1000MHz T.V. TES IONITORING RECEIVER £1,200	T TRANSMITTER £8,000	
£10 16 Pin × 10 70p Can be adapted for video 24 Pin × 5 75p TTTT PANEL 14 Pin × 10 70p		_				
CMC 301 CMC 113 CMC 302 18 Pin × 10 80p CMC 115 CMC 303 CMC 964 80 </td <td>SENDZ COMPONENTS</td> <td>S, 63 BI</td> <td>SHOPSTEIGN</td> <td>TON, SHOEBURYNE</td> <td>SS, ESSEX SS3 8AP</td>	SENDZ COMPONENTS	S, 63 BI	SHOPSTEIGN	TON, SHOEBURYNE	SS, ESSEX SS3 8AP	
£5.00 DIL - QIL		:	SAME DAY SE	RVICE		
UMLR 800 16 Pin × 10 £1.00 Power Supply Switch Mode 18 Pin × 10 £1.00 £5.00 28 Pin × 4 £1.00	•	ailability. N	o Accounts: No Cre	dit Cards. Postal Order/Che	que with order.	
SEL ITT AB Mains Switch IFB254F/2 Front Panel u/v 30p	Add	15% VAT, 1	-	Id Postage for Overseas.		
	212 LONDON RO	AD. SO	Callers: To shop at AD, SOUTHEND. Tel. 0702-332992. Fax. 0702 338805			
DECCA - GEC - III Philips Electrodynamic 6 push button - £5.00 Stereo Headphones 100 BC-BF Transistor £1.00 N6315 £10	Open 9-1/2.30-6. GVMT + s	,				
100/ DC DF (148550) 11.00 (1001.) 110	· · · · · · · · · · · · · · · · · · ·					

.

Teletopics

SATELLITE TV LATEST

BSB's first satellite, Marcopolo 1, has been successfully launched into orbit from Cape Canaveral, by a Delta II rocket. It's nearly 24ft in length and will spin at 50 r.p.m. for stability. The satellite's design life is ten years. It will undergo tests for about a month before being handed over to BSB by its builder Hughes Aircraft Company. A second satellite is due up later this year. The two satellites are costing BSB \$300m to build and launch.

During its first five months Sky Television lost £75m. Losses are at present running at about £2m a week and profitability is expected to take at least two years to achieve. According to figures from Astra and consultants McKinsey, some 79,000 receivers had been sold or rented up to mid-July. The forecast is for some 500,000 installations by the end of the year. Manufacturing capacity is estimated to be around 1.2m a year. McKinsey's figures also show that Amstrad has more than 63 per cent of the market, Grundig has 12 per cent and Alba just over 10.5 per cent.

Tandy has introduced a satellite TV system which is being stocked in the company's 300 stores nationwide. The SR100 satellite system includes a remote controlled, preprogrammable, 16-channel receiver that's simple to operate and connects easily to an existing TV set. The system sells at £369.95 fully installed with a 12-month onsite maintenance contract or £299.95 for DIY installation.

The Grundig range of satellite TV equipment has been extended to include a 75cm offset steel dish to give extra signal pick-up. Like other Grundig dishes, the new one is a distinctive grey colour. It's compatible with existing Grundig systems and can be motorised.

TranSat Ltd (Berrycroft House, Ashbury, Nr Swindon, Wilts SN6 8LX) has introduced two new satellite TV products of particular interest to installers, the SAM and the Snapper. The SAM is a compact satellite/aerial alignment meter which gives very accurate signal measurement. It has both a visual display and an audio alarm and can be operated from the mains or via the company's portable, rechargeable power supply. There are two versions, analogue or digital. The meter can be conveniently combined with TranSat's u.h.f. converter and can be used for aligning conventional TV aerials as well as satellite dishes. The Snapper is a hand-tool that snaps and seals TranSat's unique range of waterproof connectors, effectively replacing traditional crimping tools and F connectors. An optional security lock that prevents tampering is also available. TranSat can be contacted on 079 371 353.

VIDEO NEWS

Sony has introduced a range of metal high-grade cassettes for use with 8mm equipment. According to Sony the tape gives a 12 per cent increase in picture sharpness and colour vividness and a 2dB improvement in video and colour signal-to-noise ratio. The P5-90HG cassette has a three hour recording time in the long play mode and costs $\pounds 10.99$, a premium of $\pounds 2$ over standard grade tape.

Sony is to launch what's claimed to be the world's smallest and lightest full-function camcorder this autumn. The CCD-TR55 measures just $106 \times 107 \times 176$ mm and weighs 790g. It features a $\times 6$ zoom, 1/4,000 sec fast shutter, digital superimposer, fader, various editing fea-

tures and a multi-angle viewfinder. There's single-speed recording/dual-speed playback and the machine has a 270,000 pixel CCD. The compact design has been made possible by using advanced PCB technology, a miniature video head drum and the new FL Mecha drive mechanism. The price is expected to be around £999.

Mitsubishi is setting up a third VCR factory at Livingston, Scotland. This will enable the company to increase production of both VCRs and components and will create 550 jobs during the next year.

CHANGES AT RUMBELOWS

Thorn EMI is reorganising its loss-making Rumbelows retail chain. There have been redundancies at head office and thirty shops have closed. A further 30-50 "marginal" stores are being closely monitored. The firm's servicing company Solutions has been closed down: servicing is now run on a regional basis and will gradually be contracted out to other companies. The product range has been reduced by forty per cent and new lines have been introduced. Thorn EMI blames depressed trading conditions, price cutting and increases in rents and rates. Under the restructuring scheme four regional boards are being set up. Some of the shops operate under other names, such as Atlantis, Hometech and Ketts. A rumour that the DER rental chain is to be closed down and the Radio Rentals and Multibroadcast chains merged has been denied by Thorn EMI.

COMPONENT SOURCES

Proops Distributors Ltd. of Heybridge Estate, Castle Road, Camden Town, London has opened its warehouse to the public. The 10,000ft warehouse stocks a wide range of new and surplus items from solar panels to back magnets and from PCBs to valves. It's open for six days a week, offering professionals and enthusiasts alike surplus high- and low-tech components at bargain prices. Proops originally traded in the Tottenham Court Road, where it was active for thirty years from the early Fifties. The shop closed down some ten months ago.

Double D has opened a new warehouse at Ringwood Road, Bournemouth. The firm is part of Willow Vale Electronics.

Cirkit has published a new catalogue for constructors, featuring over 3,000 products. The 184-page catalogue is now arranged in alphabetical sections for quick reference and all prices include VAT. It's available for £1.50 from Cirkit Distribution Ltd., Park Lane, Broxbourne, Herts EN10 7NQ.

Seleco (UK) Ltd. has moved its sales and servicing departments to 51-52 Heming Road, Washford, Redditch B98 0EA. The spares and service telephone number is 0527 510 785.

IN BRIEF

The government has decided to allocate the 40GHz band (40.5-40.5GHz) to microwave TV services . . . The Cable Authority has warned five franchisees that they would lose their licences if they fail to start building their networks by the end of the year . . . Bourns Electronics Ltd. (90 Park Street, Camberley, Surrey GU15 3NY) has developed a new, rugged high-voltage potentiometer for use as a focus control in monochrome and colour receivers. The cermet element used in the 3386-HV1 has a temperature stability of ± 150 parts in 10⁶ per °C. Standard resistance values are 2.5M Ω and 5M Ω , the contact resistance variation being one per cent maximum.

VCR Clinic

Salora SV6600/Sanyo VHR1300

The complaint was of intermittently stopping in play or record, then being difficult to get going again. We ran the machine in the workshop for four days and it never stopped once. When it was returned the fault immediately occurred - isn't that always the way? - so back it came. This time we were able to see the fault. When play was selected the machine would lace up and would then straight away unlace and stop. Take-up was present, the capstan turned, so did the drum. As the machine started to unlace just after the capstan and take-up started, leaving insufficient time for a cutout operation from either of these functions, I checked the head switching waveform at pin 28 of IC4002 on the top PCB. It was absent. As it's fed to the system control chip to provide an indication of drum rotation (or lack of it) this was the reason for the machine stopping.

The pulses from the PG coil enter IC4002 at pin 25. There were no pulses here either, because the pick-up coil was open-circuit – the slightest pressure would correct the problem. To restore correct operation we had to order and replace the complete stator assembly. I.B.

Panasonic NV-G10

If the channel display comes on when the VTR switch is operated but there's no on-LED light, play or E-E, check the voltages around IC1001. If 13.5V is present at pin 6 there's a good chance that this i.c. is faulty. **P.B.**

Philips VR6180

This machine had severe colour crosstalk on playback and I hit a major snag when I looked at the manual – it had the 5V signal panel and I didn't have the supplement for this. Anyway I decided to start by changing the delay line 5102, which turned out to be the cause of the trouble. Rock on! **P.B.**

Grundig VS300

This machine wouldn't accept a cassette. If an attempt was made nothing happened except that F1 flashed on the display. On the basis of past experience with older models I homed in on the brake solenoid switch. This had dirty contacts, but when a new one was fitted it still didn't pull in. Its driver transistor T2141 (BC876) was open-circuit. For anyone not familiar with these machines, when the on/off switch is operated with no cassette inserted the brake solenoid should pull in for a moment. Sometimes the driver transistor goes short-circuit as a result of which the solenoid's thermal fuse blows. This is available as a spare part from Grundig. **P.B.**

Philips VR6660

This machine worked correctly in the playback and E-E modes. When record was selected however the monitor's screen went blank and nothing was recorded on the tape. When checks were made on the power supplies I found that the +12b line dropped in the record mode due to excessive current. Checks on the i.f. board led to the head

Reports from Philip Blundell, Eng. Tech., lan Bowden, Eugene Trundle, Nick Beer, E. Shirt and Jeff Herbert

amplifier can P400 where C2013 was found to be shortcircuit. Along the way I had a wild goose chase around the P604 system control board which was fitted with a small subpanel. This isn't shown on the circuit diagram but is included in the manual for the VR6862. **P.B.**

JVC HRS10/Ferguson 3V33

Failure of the fast forward and rewind functions, with the motor whirring followed by shutdown, might be taken for slippage in the reel drive unit. First however check that the pin on relay lever assembly 10 in not slipping out of the toe of the L-shaped slot in slide plate 9 as the control cam approaches its fast forward/rewind position. If it is, check for wear in plate 9, the lubrication of assembly 10 and the operation of the spring in assembly 10. The numbers refer to those in the exploded view of the deck mechanics shown in the service manual.

Tatung VRH8495/Philips Equivalents

These machines use the deck with clockwise ring loading and the "road-runner" pinch wheel. If, especially after work on the deck, you get a fixed pattern of dropout blips spread all over the screen of the monitor, check the earthing of the lower drum block. It's linked to the deck by a metal retaining finger at the right of the drum. This finger clamps the lower drum to its plastic mounting and has a long "tail" that's bolted to the deck metalwork. E.T.

Hitachi VT530E

The symptom with this new machine was no playback picture, sound o.k. Close examination of the monitor's screen showed that there was a bit of unlocked chroma signal scudding about. An open-circuit low-pass filter, CP202, in the post-demodulator luminance circuit was the cause of the fault. Sometimes these *LC* assemblies have to be replaced. On this occasion however we were able to dismantle the filter and resolder the termination of the very fine wire from a tiny ferrite-cored coil. **E.T.**

Sony HVC4000P

These early and rather bulky cameras were excellent in good light and many of them are still about, as often as not working with VHS equipment via plug-in adaptors. This one had no picture, but slight noise was perceptible on the monitor's screen, changing as the sensitivity switch was operated. In addition the tint changed as the white balance was altered manually. All these things pointed to a stuck-closed iris, and sure enough the iris drive motor had seized up. A microscopic drop of oil at each end of the spindle restored pictures.

Ferguson 3V53

Play-only machines were never very popular but we've had two examples of this model in for repair recently. Both had the same fault – no go, power supply not operating. There's no write-up on this power supply's operating principle. Its in the form of a module and most problems seem to stem from failure of the i.c.-based oscillator to start up. If you encounter this, try replacing C23 (47μ F, 25V) and zener diode D20. We've found that more reliable operation is obtained by using a 16V, 400mW zener diode in this position. E.T.

Panasonic NV333

There were several problems with this machine. First, there was considerable flutter on sound. This was quickly remedied by replacing the capstan motor. All belts, the idler and the reel clutch were then changed. When the machine was tried it went into a state of confusion: the record LED was on all the time, the machine wouldn't switch off and the clock and timer couldn't be set. After a bit of checking we found that the 2.5A fuse associated with the mains transformer's 17V a.c. winding was open-circuit due to overloading on the 5V rail. The cause of this was internal shorts in the MN1405VKK microcomputer control chip. N.B.

Salora SV8500/Mitsubishi HS304

This machine was being checked after coming back off rental. The customer had pointed out to the engineer who collected it that the sound was intermittent in E-E and playback. While thinking about getting to the heads to clean them I spotted the cause of the trouble – the r.f. modulator's audio pin had never been soldered. **N.B.**

Panasonic NV-F70

This machine was virtually dead, the characteristic squeal at switch-on being rather muted. We found that rectifier D1111 in the power suppy was short-circuit. This surprised us as it's a very large device that looks as if it's capable of carrying several amps. **N.B.**

Panasonic NV-M3

Diagnosis was not particularly difficult but the conditions may be of interest to those not familiar with camcorder servicing. The machine came in from a local factory, owned by a multinational electronics firm, for a routine service. Twaddle I thought, but it genuinely did need attention. Both the power zoom and the auto-focus motors were noisy, mechanically and electrically. As a result there was pick-up by the microphone. The belts and the pinch roller were worn, and the eyepiece rubber surround was, as so often, pretty distressed. On top of this the S4161P pick-up tube was in poor condition. The estimate was thus a high one, and to our surprise was accepted within a week. Excellent results were obtained after carrying out the repairs and setting up the unit. **N.B.**

Akai VS1/2/4

If the problem is poor sync with a single line on the tape about a quarter of an inch (six millimeters to the youngsters) from the bottom edge, look closely at the first tape guide. You'll find that the centre pin has pulled out of the plastic subdeck moulding and that the spring used is reminiscent of that used on the good old pogo stick. The waste bin is the only place for it (the spring). Replace it with something a lot lighter – old retractable pen springs work wonders. Glue the shaft back in place, pressing it well home, then reassemble using the new spring. I've

TELEVISION OCTOBER 1989

N.W. LONDON'S LEADING VIDEO SPARES DISTRIBUTOR

AKAI VS109/201/202/203/301/303	£23.50
ALBA 4000/GOLDSTAR	£23.50
AMSTRAD VCR4500/5200/9000	£18.95
AMSTRAD VCR4600/7000	£20.65
FERGUSON/JVC UNIVERSAL 3HSSV	£12.97
FERGUSON 3V32/JVC HR7655	4 Head £36.54
FERGUSON 3V42/44/45/46/47/50/JVC HRD140/141/143/150/157	£20.45
FERGUSON 3V43/JVC HRD725/755	6 Head £45.95
FERGUSON 3/32/JVC HR7555 FERGUSON 3/42/44/45/46/47/50/JVC HRD140/141/143/150/157 FERGUSON 3/43/JVC HR0725/755 FERGUSON 3/43/JVC HR07565 FERGUSON 3/43/JVC HR07656 FISHER UNIVERSAL FVHP520/72C ETC	4 11680 144.25
HITACHI VT5000/6500/7000/8000/8500/8700/9000 ETC	£20.65
HITACHI V 15000/6500/7000/8000/8500/8700/9000 ETC	C18 05
HITACHI VT11/14/33/34 ETC HITACHI VT7/17/19/35/38/39	4 Head £37.50
HITACHI VT8/56/65/120/130/135/220	P.O.A.
MITSUBISHI HS301/202/303/304/310/320/700	£29.95
	4 Head £40.59
PANASONIC NV333/2000/7000/8600 UNIVERSAL 3HSSN	£12.97
PANASONIC NV366 PANASONIC NV370NV380/PHILIPS VR6460/6520/6920/64VR60 PANASONIC NV320/NV460 PANASONIC NV689/789	4 Head £29.95
PANASONIC NV370/NV380/PHILIPS VR6460/6520/6920/64VR60	£17.10
PANASONIC NV430/NV460	£21.95
PANASONIC NV688/788	1 Hand C20 05
PANASONIC NVS81/788 PANASONIC NV730 PANASONIC NV770/NV30 PANASONIC NV771/NV30	3 Head £26 00
PANASONIC NV810	£39 75
PANASONIC NV810 GENUINE	£45.87
PANASONIC NV968/788 PANASONIC NV777/NV330 PANASONIC NV777/NV330 PANASONIC NV777/NV330 PANASONIC NV810 GENUINE PANASONIC NV810 GENUINE PANASONIC NV810 GENUINE PANASONIC NV810 GENUINE PANASONIC NV96-79/0 GENUINE PANASONIC NVG-79/10/11/12 PANASONIC NVG-79/10/11/12 PANASONIC NVG-79/10/11/12 PANASONIC NVG-79/10/11/12 PANASONIC NVG-18/00/GENUINE PANASONIC NVG-30/21/22/25/28 PANASONIC NVG-30/45/130 PANASONIC NVG-33/45/145 PANASONIC NVG-33/45/145 PANASONIC NVG-30/21/22/25/28 PANASONIC NVG-30/45/145 PANASONIC NVG-33/45/145 PANASONIC NVG-33/45/145	£49.50
PANASONIC NVG-7/9/10/11/12	£28.45
PANASONIC NVG-15/400 GENUINE	£40.75
PANASONIC NVG-18	£42.45
PANASONIC NVG-20/21/22/25/28	£40.59 627.50
PANASONIC NVG-33/45/46	£40.50
PANASONIC NVG-33/45/46 GENUINE	P.O.A.
ANNO VTC5000/5100/5160/5100/5300/5350/5370/5400 ETC SANYO VTC5000/5100/51500/5350/5370/5400 ETC SANYO VHR1100	£27.50
SANYO VTC5500/9300/9350/9355/9455/9500	£29.90
SANYO VHR1100	P.O.A.
SANYO VHR1110/1150/1300/2300 SANYO VHR1500	£26.95
SANYO VHR1500 SANYO VHR1500/3200/3400/3500 SAMSUNO VR0000100/2510/500 F16 FTC UNIVED SAM	£42.50
SAMSUNG VB900/910/VX510/520/816 ETC UNIVERSAL	2 Maad C22 50
SAISHO/HINARI UNIVERSAI	2 Head \$20.95
SHARP VC105/108/205/208/400/405/408/500/582/583/651 SHARP VC200/220/300/381/383/386/387/388/481/482 ETC SHARP VC483/486	£19.00
SHARP VC200/220/300/381/383/386/387/388/481/482 ETC	£19.00
SHARP VC483/486	£34.50
SHARP VC6000/6300/7300/7700/7750/8300	£38.00
SONY UNIVERSAL 1 PIN DSR36	£15.50
SONY SLF1/30/60/C20/30/40 DSR35R	£18.95
SONY SLC8/9/60/80/SLF200 ETC TOSHIBA V21/31/33/50/51/53/9600	£32.45 £20.95
WE CARRY HUNDREDS OF VIDEO SPARES INC. IDLERS CLUTCHES MOTO	RS. BELT KITS. PINCH-
ROLLERS, ORIGINAL SONY SWITCHES ETC.	
WE CARRY HUNDREDS OF VIDEO SPARES INC. IDLERS, CLUTCHES, MOTO ROLLERS, ORIGINAL SONY SWITCHES ETC. NEW CATALOGUE OUT NOW AVAILABLE FREE OF CHARGE TO THE TE WELCOME (Subject to Status) All Ex-Stock thems despatched same dup, No minimum order value, Non acc Visa or Access credii cards. Please add 90p plus VAT to sil al	ADE. NEW ACCOUNTS
All Ex-Stock nems despatched same day. No minimum order value. Non acc	ount holders can pay by
Prices are subject to change without notice.	nuro prices.
RING JS FOR THE BEST QUOTE	
	NICO
ON HAND PORTABLE & MOBILE CELLULAR PHO	
O	ASK 7
OMEGA ELECTRONICS	
UNIEGA ELECTRONICS	FOR
NEW ADDRESS:	
OMEGA ELECTRONICS	OUR
	UUN
304 CROWN HOUSE, NORTH CIRCULAR ROAD	CATALOGUE
LONDON NW10 7PN	GATALOGUE
Tel: 01-965 5748 Fax: 01-963 0351	
	dans callesting
Personal Callers are advised to telephone their orders be	etore collecting.

done lots of these repairs – when you've seen the spring for yourself you'll see why the fault occurs. E.S.

Akai VS1 and VS4

These machines have an on-screen display. A fault that can only be described as the space invaders syndrome occurs – a screen full of As that flicker at clock rate. The culprit is the character generator chip IC2 on the operation PCB (front panel). It's an MB88303. I've had this fault on several occasions. **E.S.**

Samsung V7 Series

No erase and no new sound track – yes, it's the bias oscillator. If you dismantle the erase block carefully you can replace the transistor. It's nothing special and usually goes open-circuit emitter-to-collector. E.S.

Samsung VI611

Tape left out when the cassette is ejected looks at first sight like a case of poor rewind torque. Usually however it's that biggest blight of our lives the mechanism state switch. You'll find it hidden between the subdeck and case moulding webs. E.S.

Sanyo VHR3100

The complaint with this machine was no record sound, playback sound o.k. A prerecorded tape produced a good picture and sound but, as the tape loading and front loading mechanism operated, the verticals in the E-E picture bent and hum bars appeared on the screen. The E-E picture returned to normal as soon as the mechanism drive motors stopped. With the machine in the record mode, once the tape was fully loaded and the hum bars had gone the E-E sound was lost (muted). Hence the no sound on record problem. As we've had power supply faults with these machines we checked all the regulated rails carefully with a digital meter. They were all within 0.2V of the readings specified in the manual, and no detectable drop occurred in the loading and unloading modes when the hum bars appeared on the screen.

As a working machine was available and the boards can all be removed easily we decided to isolate the cause of the fault by panel swapping. The top signals board seemed to be the most likely source of the problem as most of the

Letters

CD-GRAPHICS

I think I can solve the mystery of the extra subcode words mentioned in Part 7 of Joe Cieszynski's excellent series on servicing compact disc players. The R-W words, which account for approximately three per cent of the bits on the disc, have been set aside for a graphics display system called CD-Graphics (CD-G) or Back Ground Video (BGV). CD-G is part of the original CD digital audio Red Book specification and is thus an internationally agreed standard.

The idea behind CD-G is to allow simple graphics and text (e.g. song lyrics, artists' biographies, pictures etc.) to be displayed on a TV screen while a CD disc is being played. I first saw the system in Japan last year. The display looks very similar to a teletext picture, each CD-G display consisting of 288×192 pixels. Up to 16 colours can be selected from a palette of 4,096. A CD disc can store up to 1,500 graphic images, and up to 1,500 languages can be written on to it. The images and text can be scrolled on and off the screen.

The system is very popular in Japan, where many discs are encoded with graphics. I understand that several UK CD discs also have them. The graphics can be seen only when a special decoder is used however. It's attached to either the digital or subcode socket on a standard CD player and the TV set. Future CD players will incorporate the decoder. Rumour has it that JVC may launch a CD-G decoder in Europe later this year. A more detailed description of CD graphics will appear in an article currently being prepared for *Television*. *George Cole*,

Peterborough.

SATELLITE TV SERVICING AID

I would like to make a couple of points regarding D.J. Stephenson's novel satellite TV servicing aid (August) to prevent potential builders from coming to grief.

First, the choice of mains transformer. The author states that "any transformer whose secondary winding is in the range 15-30V can be used". In view of the calculations the author provides this clearly isn't so. Ironcored transformers typically have a load regulation of 10-15 per cent. Some small transformers are considerably worse than this. Taking the best case at the upper end of sound processing is carried out here. But changing this then the system control panel and the front function and tuning boards made no difference. We finally swapped the power supply panel. This cured the no sound on record and the hum bars with the motors running problems.

A scope check soon revealed the source of the fault. There was ripple on the 12V and 13V rails. We then found that there was a dry-joint on the reservoir capacitor C5001 (2,200 μ F, 50V) at the input to the STR7226 regulator chip. As a result the chip could cope under low-load conditions, i.e. in the E-E and playback modes, but on record the extra load produced by the bias oscillator drive to the sound and erase heads caused excessive ripple on the switched 12V line. This upset the sound mute control in IC2001. J.H.

the range, a transformer with a nominal secondary voltage of 30V r.m.s. will produce an off-load terminal voltage of at least 33V. With a rectifier and reservoir capacitor added the output will be $33 \times 1.414 = 46.67V$, which is clearly well in excess of the maximum input voltage of 78 series regulators. A 15V r.m.s. transformer is about ideal and should be recommended for the project. If any reader wishes to use a transformer from a junk box, the maximum off-load terminal voltage of the one chosen must not exceed 20V r.m.s.

Secondly a word on upping the nominal output voltage of 78 series regulators. While adding a resistor in series with the earthy leg is in order, the load regulation does suffer quite badly as the author points out. A better way of producing a small increase in the output voltage without upsetting the load regulation is to take advantage of the constant 0-6V forward drop across a silicon diode. Two 1N400X type diodes in the earth return (see Fig. 1) will bring the output up to 16-2V which is very close to the originally specified 16-5V.

Thirdly an r.f. choke should be added to isolate the d.c. supply from the r.f. throughput. A few turns of enamelled copper wire wound around a small ferrite bead should be sufficient. Depending on the exact method of construction this could reduce the unit's through loss significantly. It may be particularly helpful where the signals are marginal.

I would also like to suggest a couple of inexpensive modifications to improve the unit's safety and possibly its operation.

78 series regulators are generally reliable devices and usually fail safe, i.e. with no output. Over the years however I've had several where the earth return has apparently failed internally. In this case the device fails with the output equalling the input. The same problem

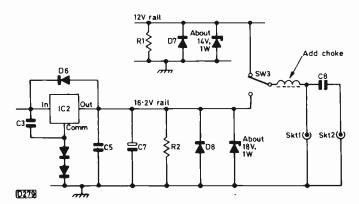


Fig. 1: Modifications to D.J. Stephenson's satellite TV servicing aid. See letter from G.R. Darby. The diodes in series with IC2's earthy lead are in the 1N400X series.

would arise in the event of failure of a component in the earthy connection to the 16V regulator. This condition could spell instant death to the LNB/polariser. Protection can be provided by adding across the regulator outputs zener diodes rated at a volt or so above the rail voltage. In the event of a voltage-rise failure the relevant diode will conduct heavily, probably going permantly short-circuit. This will shut down the regulator and the fuse will probably blow soon after.

Finally a few comments on decoupling. As suggested in the article, 78 series regulators are notoriously noisy and have a tendency to instability. In the circuit diagram the 0.1μ F capacitors are correctly shown connected directly across the regulator terminals. This must also be the case physically – the capacitors should be mounted not more than a few millimeters from the regulator terminals. If the regulators are mounted off the board via flying leads the decouplers must be soldered directly to the i.c. pins. *G.R. Darby, Proprietor Monitech*,

Earls Barton, Northampton.

The satellite TV servicing aid should include a u.h.f. choke between SW3 and the junction of Sktl and C8 otherwise the power supply will shunt the signal. A few turns of ½in. diameter will do. I would also suggest that two or three diodes in series would be better than RV1. Mixed germanium and silicon devices could be used if necessary to obtain 16V, anodes towards the regulator of course. Regulation will be better than with RV1 but a resistor between the output and the common connection of the regulator will be necessary with large diodes. *Ralph Taylor, MIEE, GW2HCJ, Penrhyndeudraeth, Gwynedd.*

IMPORTANT CORRECTION

A correction is required to my article on the design of a satellite TV servicing aid (August issue). The unit as described must under no circumstances be connected to the Grundig head unit without modification. No more than 5V should be connected across the magnetic polariser used in the Grundig unit and this should be 40-80mA from a constant-current source. The unit works perfectly well with any outdoor unit incorporating the popular V/H switched Marconi LNB.

D.J. Stephenson, B.A., I.Eng., Wirral, Merseyside.

REPAIRING CARBON CONTACT KEYS

In connection with Nick Beer's very informative article on remote control units (September) I'd like to add a hint on the repair of carbon contact keys. A much more permanent repair can be carried out by glueing a small disc of aluminium kitchen foil over the worn out carbon layer. I learnt this trick when I discovered a number of small clock-radios that had been discarded because it had become impossible to program the clock circuit. Nearly all of them responded to this treatment, each repair taking less than fifteen minutes.

Geoff Lewis,

Canterbury, Kent.

PLAYING 525-LINE TAPES

I am writing to describe the method I've used to play 525line tapes with a 625-line VHS machine – the VCR used

next month in

TELEVISION

SERVICING THE PANASONIC NV730B

Despite the relatively high price, these dual-standard SP/HP machines sold in large numbers. There is a very distinctive fault pattern, and once you are familiar with this servicing should present few problems. Nick Beer provides a thorough rundown on this machine's habits.

• THE HI-BAND 8mm SYSTEM

This autumn sees the European launch of the Hiband 8mm video format, Video-8's answer to the Super-VHS format. In a special article George Cole butlines the basic 8mm system and then describes the developments that have led to the Hi-band version in which the luminance deviation is raised to 5.7-7.7MHz, increasing the horizontal resolution to over 400 lines and improving the signal-to-noise ratio by 4.4c B. Hi-3 is the first format to use metal evaporated (ME) tape.

SERVICING THE PHILIPS KT3 CHASSIS

The KT3 was the basic chassis used in a wide range of Ph lips and Pye models fitted with 90° tubes. It was available for a number of years and sold in large quantities. John Coombes provides a detailed guice to fault finding.

• THE FERGUSON SRA1 SATELLITE TV RECEIVER The SRA1 satellite TV receiver was introduced by Ferguson for reception of the Astra transmissions. In addition to an evaluation and notes on installation J. LeJeune describes the internal arrangements, with a block diagram to clarify the operation.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

was an old Panasonic piano-key Model NV8600. The procedure is simple. First replace the 50Hz reference signal fed to pin 25 of IC201 on the servo board with a 60Hz reference. This can be generated by a 555 timer i.c. Then, with a 525-line tape inserted and the machine in the play mode, adjust R2116 (capstan free run) until the capstan servo locks and similarly R223 (drum free run) to obtain drum servo lock. Both of these adjustments can be carried out by looking at the playback picture.

The result should be a locked monochrome display. Most domestic TV sets should be able to display these pictures without any problems, though some may require a tweak of the field hold control.

Keith Hunter, Ealing, London.

Laung, London.

MORE ON PVC LEADS

As mentioned in a letter last month, PVC leads attack plastic because the plasticiser in the PVC can't wait to get out. The old TV and radio sets of the Fifties generally used brown-sheathed mains leads with red and black cores inside. Being thrifty, I often used to think that this was good stuff to salvage – until I found that it was far too tough and too brittle to reuse.

When PVC is in direct contact with other plastics the plasticiser has a direct migration path. I foolishly coiled a mains lead around a power supply that I'd built into a Verobox made of ABS plastic: the mains lead cut deep grooves into the case.

Things start to get dangerous when people mistakenly use large chunks of expanded polystyrene as a cheap form of loft insulation. This is invariably laid directly over PVCsheathed mains wiring, and the insulation of the latter deteriorates. I understand that house fires have been caused in this way.

So this is a serious warning: keep PVC-covered cables away from other plastic. Incidentally this is why manufacturers use plastic bags to wrap cables separately inside those niches in styrofoam packing material.

By the way, our revitalised 405 Alive group for 405-line equipment enthusiasts is now going great guns, with 40-page newsletters. For details readers should send me an SAE.

Andy Emmerson, 71 Falcutt Way, Northampton NN2 8PH.

The loss of solvent in the PVC covering of mains leads that are stored for long periods in contact with other plastic surfaces will make the PVC covering brittle and hence present a safety hazard. This problem also occurs when cable is supplied in boxes of polystyrene chips.

Don Trower, Engineering Operations Radio, Broadcasting House, London.

VCR TIPS

In the June Service Bureau a Ferguson 3V23 suffering from intermittent switch off and eject was mentioned. This was a fault with the mechacon circuit and the modification for early boards PU49564A-D is to add a $68k\Omega$ resistor in parallel with R86. With later boards PU10458A-M you add a $68k\Omega$ resistor in parallel with R37 and a $10k\Omega$ resistor across pin/socket connections 74 and 76. This modification effectively clips noise generated in the remote control receiver circuit.

With reference to John de Rivaz's letter (June) and

Brian Renforth's subsequent letter (August) – my compliments to his memory! – I did indeed succeed in converting a Ferguson 3292 and a 3V23 to play NTSC tapes. The 3V23 conversion was very successful because both the drum and capstan reference signals are obtained by counting down from 4·43MHz to 50Hz in IC1 (servo-2 circuit). If the 4·43MHz crystal is replaced with an NTSC 3·58MHz chroma crystal and pin 6 of IC1 is disconnected this chip will count down to 60Hz. Slight modification to the drum and capstan speed potentiometers will enable NTSC tapes to be locked, unfortunately only in monochrome – I never did succeed in obtaining colour.

Possibly an easier solution would be to search through the piles of old mechanical ex-rental 8902 machines for an 8928 (JVC HR3330TR). This looks the same as the 8902 and was indeed installed as the 8902, the difference being that the 8928 is a triple-standard PAL/SECAM/NTSC machine. The little changeover switches are under the clock display but were blacked out by a piece of black tape. This machine will play (but not record) NTSC with 4.43MHz chroma. The only problem is to convert a TV set. I found that the easiest one to adapt is the old Ferguson TX9 with the PC1001 main board. The line speed takes care of itself. The field timebase needs only slight modification for speed and height. Chroma can be obtained by disconnecting pin 23 of IC52 to disable the PAL switch, short-circuiting TP2 to TP3 to disable the killer and shifting the U and V references to I and Q by adjusting L57/R75 (otherwise pictures are all blue/green).

Finally may I just say to all old colleagues from the old firm around the country that I'm still going strong! Dave Plummer, I. Eng., FSERT, Bexhill on Sea.

POTENTIOMETER TIP

Here's a tip I've used for years but have never seen in print. Noisy volume controls and dirty potentiometers, whatever their use, can be cured by putting a spot of fine oil on the track and then moving the wiper from end to end several times. This may not seem to be the right thing to do but I can assure you that it works – television and radio sets, even computers, respond to this treatment. The oil can be applied in situ, making the repair easy. *F. Gregory*,

Walton-on-Thames, Surrey.

HELP WANTED

Could any reader supply a circuit diagram for the Matsui SX5260T double tape deck?

B.C. Harper, The Post House, Giffordtown, Nr. Ladybank, Cupar, Fife KY7 7UW. Telephone 0337 30 435.

A Grundig infra-red 13-function remote control unit, type VIF-KI, has been advertised in this magazine. Does anyone have any information on decoding the thirteen outputs from the receiver?

R. Hadfield, 45 Erica Way, Copthorne, Crawley, W. Sussex RH10 3XG. Telephone 0342 715 333.

Could anyone supply a circuit diagram for the Soverign Model C140 colour portable? I'm prepared to cover any expenses. The set requires slight attention before I can use it for DXing.

G. Adams, 64 West Grove, Gipsyville, Hull HU4 6RQ.

Review: Salora's Astra Package

Being a Salora dealer the firm for which I work handles the recently introduced Salora Astra satellite TV receiving system. We have thus gained experience of its operation under various conditions. In addition I've had from Salora one of these systems to try out and experiment with.

Outdoor Units

The 55cm offset dish is manufactured by Fuba in West Germany and is made of glass-fibre reinforced plastic with a flame deposited aluminium coating beneath the surface. It's beige in colour and elliptical in shape, the stated size refering to the minor axis (width). Rigidity is ensured by eight ribs on the rear side. There are two large vertical ribs fitted with a spring-loaded pivot shaft which clips into the mast clamp assembly. This together with four wing-nuts and their associated jamming plates clamps the dish securely once the correct elevation has been set with the plastic fine adjustment knob. The mast clamp is designed to fit on to any pole size from 40 to 66mm in diameter. The dish's half-power beam width is quoted as being less than 3°.

The LNB support arm consists of a 40cm length of inverted U-section extruded aluminium which slots neatly into a moulded socket at the base of the dish. A wing bolt clamps the arm in place. Two plastic clips on the underside of the arm retain the cables. The business end of the arm is fitted with a cast aluminium holder which clamps around the neck of the flared feedhorn.

The feedhorn is fitted with a sealing cap of the same colour as the dish (no garish red or blue!). Four small bolts and an O ring clamp the feedhorn and the magnetic polariser together. The latter is able to provide over 100° of rotation with a through loss of less than 0.25dB. This may sound relatively high for a magnetic type, but the loss varies with frequency and the quoted figure is the highest across the band 10.95-11.7GHz.

Another four bolts and an O ring clamp the LNB to the other end of the polariser. This is of the same type as used on some of Salora's earlier satellite TV systems and has a noise figure of better than 1.5dB. An F socket is used for the output connection. The unit comes with a plug, some adhesive tape and an eleven-stage pictorial fitting guide.

Mast

The dish assembly must be fitted to a mast. Salora provides a wall bracket that consists of a 39cm length of galvanised pipe (of 48mm diameter), two U-bolts, four stand-off legs and a strengthening strut. When assembled this gives a 35cm stand-off which provides a wide enough azimuth adjustment range for most purposes. The wall fixing holes are well spaced, unlike some mounts I've seen where all four bolts could almost be secured into the same block. Alternatively Salora can supply a patio mount (this arrangement was used with the test installation). It consists of an 80cm length of galvanised pipe with two threesection clamps. The bottom one attaches the three 50cm long angle section legs, the other one clamping the three struts from the legs almost half-way up the mast. All the components are galvanised and when bolted together the structure is very solid. There's a hole in each leg for bolting to the ground. With the dish fitted the complete assembly is around 100cm high.

The 5902 Tuner

The 5902 indoor tuner unit is compact and neat looking: it measures 38cm wide, 7cm high (including the feet) and 27cm deep (including the projecting sockets). A label on the front states "Stereo Satellite Receiver ASTRA". I'll come back to the significance of this later. The only button on the front is the red on/standby switch which operates on the secondary side of the mains transformer. It's to the right of the multi-function two-digit LED display. Everything else is done by remote control – the unit has the same case design as with 15L portable TV receivers.

The rear of the unit has provision for connecting two aerials, via male and female IEC connectors (the tuner comes with a screw connection female plug). A 6mm diameter hole in the back panel provides access to the a.g.c. test point, a through pin in the main PCB. Connection to this is a bit tricky as the pin is some 6mm inside. I'd have preferred the screw terminals or push-in connectors used with some other units but found that a miniature, insulated crocodile clip could be used. A standard IEC male/female connector is provided for r.f. loopthrough, a male to female coaxial lead being provided for connection to a VCR or TV set. The r.f. output is adjustable over chs. 30-39, and a test pattern facility is incorporated.

There's a group of four phono sockets. The top two are labelled for use with a Sky decoder. They enable a baseband output and a composite video input to be connected. The lower two provide a second baseband output and a 0/12V switching signal for use with an external aerial swithing box which enables two dishes to be connected to one of the tuner's inputs. Thus a total of three dishes can be connected. Next to this there's a scart connector which provides composite video and stereo audio outputs to a VCR or TV set - there's no status switching d.c. Finally a 2.1mm barrel socket provides the current drive (0-150mA) for the magnetic polariser. A 2.1mm barrel plug is included. I'm sure that most installers would be much happier with something like screw terminals instead of having to solder the twin lead to the small plug. Apparently this connector is a design stipulation for use of the tuner in West Germany (the tuner is sold elsewhere in Europe). To make installation easier and quicker, I understand that Salora is to supply an adaptor lead with a barrel plug at one end and connectors such as Scotchlocks at the other end.

The 5902 tuner has 48 programme locations and a tuning range of 10.9635-11.74525GHz. This is sufficient to cater for the two projected Astra satellites as well as the current 1A. Frequency synthesis tuning is employed, the user simply calling up the required channel via the remote control unit which also provides for polarisation adjustment. For the latter you enter a number from zero (no current to the polariser) to nine (maximum current). This gives coarse adjustment, which is followed by fine tuning

for best results. The final setting is then stored in the memory with the relevant programme.

The unit can be used with ten different sound systems. Four, designated A0-A3, have stereo sound on separate carriers, with narrow bandwidth (150kHz) and Panda 1 de-emphasis. Three, designated A4-A6, have narrow bandwidth (150kHz) mono sound with Panda 1 de-emphasis. The final three, designated A7-A9, have wide bandwidth (230kHz) mono sound with 50µsec de-emphasis. With any of these systems you can tune through the range 5.5-8.5MHz and store the required frequency. You can't change the preset bandwidth and de-emphasis. The factory preset frequencies cover the three main systems in use: A0 has 7.02 and 7.20MHz stereo carriers as used by MTV; A1 has 7.38 and 7.56MHz stereo carriers as used by Sky Radio; A7 has a 6.5MHz mono carrier as used by Screensport, Eurosport, Sky News etc.

Now back to the Astra label. The 5902 tuner can be used to receive MAC transmissions via the Astra satellite(s). An extra, external unit connected to the baseband output is required for this. It seems however that it will not be possible to use this tuner, or any other similar arrangement, to receive the BSB's MAC transmissions since BSB will supply the decoding/access chips required only for fitting in dedicated BSB tuner units or a panel for use inside a TV set or tuner. In addition you would need to use a DBS band LNB and the polarisation system is different.

Construction

A look inside the tuner reveals a main panel plus two small sound detector panels, a regulator board, a display panel and an infra-red remote control amplifier panel. From the top the main panel looks rather bare, with mainly i.c.s, links and the power supply components being visible. This is because extensive use is made of surfacemounted components on the underside of the board. The mains input is directly connected to the primary winding of the mains transformer, with the on/standby switch controlling three d.c. supply lines. This leaves the 5V supply to the modulator block for r.f. loop through. When you switch to standby via the remote control unit only the 12V video and audio supplies are removed. As a result you get a blank raster on a monitor/TV set tuned to the unit's output.

A look through the manual suggests that there's a version of the tuner capable of providing 13/18V polariser switching for use with the Marconi type head unit.

Installation

I'll describe how I got the loan system, with patio mount, working. After unpacking, the dish only required the mast clamp to be clipped on to its back and the fine adjustment knob located in its slot. The feedhorn holder was then fitted to the support arm by means of two screws and the arm was slotted into the dish and secured with the wing bolt. The feedhorn, polariser and LNB were next assembled, making sure that the polariser was the correct way round. This is the only fiddly bit: the spacing between the polariser body and its flange at the LNB end is very close, making it difficult to get the bolts started in their threads. The complete assembly was then clamped by the feedhorn holder. After unfolding the patio mount and tightening all the bolts the mount was placed in a suitable position, with a concrete block across each leg as this was

The tuner was connected to the mains supply and a length of speaker cable was soldered to the barrel plug, connection at the other end being made with a couple of block connectors to the short leads from the polariser. I used about 12m of CT125 coaxial cable, which only just fits into an F plug if you trim down the insulator and file down the centre conductor so that it fits the LNB's F socket. With everything connected, the tuner was powered up and a preprogrammed channel was selected. Using a long coaxial lead, I positioned a TV set where I could just about see it but more importantly hear the sound whilst adjusting the dish.

to be only a temporary installation (unfortunately!).

I knew that the wall of the house faced approximately south but, without an inclinometer or an accurate compass, I had only a rough idea as to the direction and elevation. So the method I used was to hold the dish with a hand at each side and rock it up and down whilst turning slowly from a nearly south direction towards the east. In a matter of twenty seconds I heard the hiss from the TV set. It was then just a matter of slowing down the rocking motion to find the correct elevation, whereupon a relatively steady signal was received. The dish elevation, almost vertical, and the direction in which the LNB support arm was pointing were noted - the arm lined up with a large stone in the garden wall. The dish assembly was then fitted to the patio mount, lined up and clamped just tightly enough to hold it in position.

Polarity was adjusted via the tuner for best results, then a second length of speaker cable was connected to the a.g.c. test point and chassis via crocodile clips and run to a digital meter at the dish - the minimum meter resistance that can be connected between the test point and chassis is $100k\Omega$. The idea is to get the voltage level reading down to a minimum. Dish azimuth adjustment is done by loosening the two wing nuts on the mast clamp and turning the whole assembly. A slight problem here is that a piece of perforated sheet best described as a small cheese grater is fitted to the mast clamp surface to bite into the mast. Because of this the clamp nuts have to be undone until the dish is completely free before it will swing round, making fine azimuth adjustment more difficult. I did however find that a small azimuth movement can be made by tightening just one of the wing nuts to pull the clamp around very slightly. The fine elevation adjustment provides a very accurate setting, and when clamped by the jamming plates is firmly held. There's some flexing of the mast clamp itself, allowing the dish to move slightly from side to side, but even in windy conditions during the test there were no signs of signal degradation because of this.

Local installers tell me they prefer systems that use the Marconi front end as only a single cable run is required, making installation easier, neater and most importantly quicker. The separate polariser feed used with this system could be considered a slight drawback, but I understand that a special cable is available from Raydex to simplify matters. It's referred to as type SAT1002 and consists of a coaxial cable of CT100 type with two extra insulated conductors on the outside for connection to the polariser.

Performance

The system's performance was excellent. During the test period there were two heavy rain storms which produced a noticeable increase in sparklies on the reduced power test transmissions. Only a very few sparklies were visible intermittently on the programme channels however. Eurosport seemed to be the most susceptible to this. Thus the performance is comparable with both the 65cm offset dish systems I've seen in use.

Construction of the dish and mount assembly is the best I've come across with an Astra system, providing secure fixing whether on the wall or a patio mount. In particular the use of galvanised steel components secured by plated nuts and bolts is far better than the other systems I've seen. The tuner is very impressive. Being designed specifically for Astra use it provides all the necessary facilities, i.e. audio de-emphasis characteristics and tuning range together with provision for future developments in transmission standards and encryption. The frequencysynthesised tuning and "dial-in" polarity settings make setting up easy and quick. Operation is straightforward and the unit is well designed and finished. Even the instruction book is well laid out and easy to understand – when you find the English section. Overall I'd say that this is the best Astra package I've seen. The only real disappointment was having to send it back.

Sales

Sales of Astra systems have so far been slow in this area (North Devon). It seems to me that there was greater interest back in February when the services started. This is a pity, since better receiving systems have become available in recent months. The public seems to be waiting for the situation to settle down before investing in satellite TV receiving equipment.

Acknowledgement

My thanks to Salora (UK) Ltd., and in particular John Breeds, for making available for test their Astra system.

The SEME-Panasonic Spares Operation

Fast, hassle-free provision of spares is vital to the efficient service department. It's important to the service engineer, the customer and, not least, the manufacturer's reputation. Realising this, more and more setmakers are appointing specialist components companies to handle the provision of spares to non-account dealers and service engineers.

The latest major company to have adopted this policy is Panasonic, which has appointed leading components distributor SEME Ltd. to handle, from August 1st, all orders from those outside the company's franchised dealership network. This arrangement will ensure that non-account dealers and service engineers have speedy access to all original Panasonic spares.

Commenting on this, SEME's managing director Colin Richardson makes the point that "service spares turnover probably accounts for a very small percentage of a manufacturer's sales but a large proportion of his invoice queries, bad debts, returns and other problems: by allowing SEME to deal with the trade's need for low unit price spares required with a fast turn-round a manufacturer can limit his sales invoicing, delivery and accounting volumes to his major dealers." SEME's extensive coverage of around 10,000 delivery points throughout the UK will ensure that the public has to travel no farther than a local High Street outlet for service help. In addition, SEME's computer tracks orders and invoices to give an accurate split between FOC warranty supply and chargeable repair work. Tailor-made reports can also be easily prepared to assist management and inventory control.

SEME has established a new sales office at Buckingham specifically to deal with orders for Panasonic spares. It's staffed by three new sales people and a technical liaison engineer, all of whom have been jointly trained by SEME and by Panasonic at the latter's Bracknell head office. The Buckingham office is linked by computer with SEME's warehouse at Melton Mowbray to ensure a fast and efficient response.

SEME was founded by Colin and a former colleague at Radio Spares, Basil Johnson, more than seventeen years ago. When Radio Spares decided to move away from the domestic electronics market and concentrate on industrial customers Colin and Basil saw that there was a business opportunity. Operating very modestly from two small vans, they started to supply spares to the domestic market, Colin as South Midlands Electronics and Basil as East Midlands Electronics. Apart from meeting every Wednesday to purchase spares they ran completely separate operations. It was not long however before they decided to join forces in order to buy in bulk at discount prices. The next step was joint warehousing and finally, on August 17th, 1972, SEME came into being.

And this is where the famous elephants, which are the company's trade mark, came on the scene. The company couldn't be registered as South East Midlands Electronics because this conflicted with an existing trading name. Instead it was decided to use just the initials SEME. When the registrar asked Colin what the initials stood for he replied, quick as a flash, "small elephants, medium elephants".

SEME grew very quickly from the two-van operation and soon took on a small sales team. Colin had family support in the form of his wife Jeanette, now company secretary, his brother-in-law Ken Cheesman who is now technical director and his brother Malcolm who is sales director. Today the company employs some 90 people and has 25,000 sq. ft of warehousing at Melton Mowbray, about 2,500 of it devoted to Panasonic spares. The sales team of sixteen visits customers on a two, four or sixweekly basis to collect orders which can also be placed by phone of fax. Orders are dealt with on a same-day basis and are despatched either by first class post or Securicor delivery. SEME also employs a team of technical assistants who check all pattern parts against original spares.

In addition to stocking spares for many other manufacturers, SEME is the sole source of under-guarantee parts for NEC and Fidelity.

The new SEME telephone number exclusively for Panasonic spares is Buckingham (0280) 823 523. The fax number is (0280) 814 916. Orders by post should be sent to SEME Ltd., Chandos House, School Lane, Buckingham MK18 1HD. When ordering, dealers should ideally have the part number. In the absence of this, the product type (e.g. TV, VCR etc.) and model number should be quoted along with a description of the part required.

Servicing Compact Disc Players

Part 8: Signal Decoding

Over the past three months we've outlined how the audio signal is converted into digital words which are then encoded and stamped on the disc. This month we'll consider the decoding process in the player.

The decoder receives from the r.f. amplifier a signal in eight-to-fourteen modulated form. We've already discussed the r.f. section but will recap briefly to avoid the need for too much referring back. The r.f. signal provided by the laser unit's pick-up detectors contains information representing the transitions from land to pit and pit to land on the surface of the disc. These transitions produce a sinusoidal rather than a squarewave voltage signal however. The off-disc signal is thus unsuitable for digital decoding in its initial form. Remember also that the transitions represent only the ones in the data stream: you can argue that the zeros are not stamped on the disc and must therefore be reinserted by the decoder.

To convert the sinusoidal r.f. signal into a squared, digital waveform it's amplified and sliced by an operational amplifier. This circuit, see Fig. 1, incorporates auto-asymmetry control which compares the output from the slicing amplifier with a fixed d.c. level. The purpose of this circuit is to smooth out any amplitude variations introduced by disc eccentricity. Such variations would result in a phase shift in the sliced data – this would cause problems in the decoder.

The following decoder description is based on the Sony CX23035 chip, see Fig. 2. This particular chip has been chosen for two reasons. First, it's widely used by CD player manufacturers other than Sony. Secondly, when we looked at the r.f. amplifier section in Part 4 (June) we referred to the circuit used in the Sony CX20109 chip which is designed to work with the CX23035 decoder chip. By using the same chip set throughout the series the descriptions should follow each other more clearly.

The Phase Locked Loop

The e.f.m. signal from the slicing amplifier shown in Fig. 1 is applied to a phase locked loop via pin 5 of the CX23035. The oscillator in this loop is varicap controlled and has a free-running frequency of 8.6436MHz. The two inputs to the phase comparator are the 4.3218MHz e.f.m. and the divided-by-two output from the 8.6436MHz oscillator. Its output appears at pin 11. When this d.c. control voltage is applied to the varicap diodes, the oscillator becomes locked to the incoming e.f.m.

The phase-locked oscillator controls much of the de-

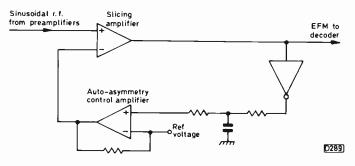


Fig. 1: The signal squaring system.

Joe Cieszynski

coder operation and also the disc servo. Thus before making any other checks in the decoder or performing any other adjustments it's important to ensure that the oscillator is correctly set up. In their service data manufacturers give various ways of carrying out this adjustment. In most cases it's a matter of setting the d.c. control voltage applied to the varicap diodes to a specific figure. If you don't have the service data available you may decide to set the oscillator with the aid of a frequency counter. Be warned however that in some cases the frequency counter will not give a correct readout, probably due to harmonic distortion in the oscillator's output. Also note that in some players the oscillator operates at 4·3218MHz.

I've emphasised the importance of this adjustment because the timing of all the data in the decoder will be incorrect if the oscillator is not running at the correct frequency. The result will be no sound output. In addition because data in the e.f.m. signal is used as a sample by the disc speed servo, problems may well occur in this area. In this case the disc will rotate at some incredible velocity until the central control microcomputer shuts down all operations. In some cases the disc may even run backwards at high speed. If these symptoms are intermittent, it's likely that the oscillator is working at the edge of the control range because someone hasn't set it up as per the manual. The importance of this adjustment is highlighted by the fact that in most manuals it's the first one given. In other words there's no point in attempting any other adjustments until this one is correct.

The squared e.f.m. data contains the logic one information. Thus the zeros still have to be reinserted. This is in effect done by the phase-locked loop. Because the oscillator is locked to the data, the spaces between the ones can be counted at the oscillator's rate of 4.3218MHz. The decoder can thus clock in the missing zeros. This is illustrated in Fig. 3: where a transition coincides with a phase-locked loop (PLL) clock pulse a one is inserted; where there's no coincidence between a clock pulse and a transition a zero is inserted. This makes it clear why the PLL clock must be set up correctly: any error will result in a phase shift between the clock and the incoming data as a result of which the one transitions will be missed.

Following this operation the e.f.m. data is latched into the decoder by the PLL signal. The system ensures that the PLL remains synchronised with the off-disc signal. An edge detector ensures that the correct data is then passed to the 23-bit shift register.

EFM Demodulation

It's now time for the 14-bit words to be converted to the original 8-bit audio data symbols. This is done by the e.f.m. demodulator, which contains a look-up table in its ROM. Those interested will find this in many manufacturers' training manuals. It's not really of any practical use to the service engineer however. A random selection of three lines from this table is shown below:

14-bit word		8-bit symbol
01001000100000	=	00000000
00100001000000	=	00001111
0010000010010	==	11111111

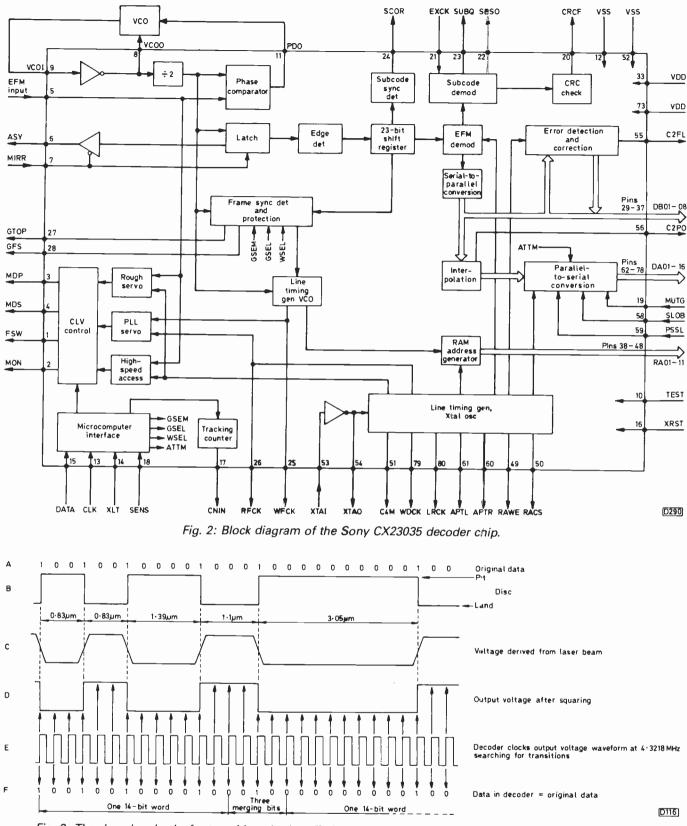


Fig. 3: The decoder checks for transitions in the off-disc signal then generates the appropriate ones and zeros.

In case you're trying to recall how the 8-bit symbols came to be in the form of 14-bit words, let me remind you of the relevant points made in Part 5 (July). In that instalment we considered in some detail the problems that would arise if data words containing either consecutive ones or more than ten consecutive zeros were to be stamped on the disc. Because the original 16-bit audio samples inevitably contain such binary combinations they are first split into 8-bit symbols which are then converted into 14-bit words that obey the e.f.m. rule – not more than

ten consecutive zeros and not less than two consecutive zeros.

Error Correction

The 8-bit symbols are next converted to parallel form and are then put through the error detection and correction processes discussed in Part 6 (August). Error correction relies heavily on the additional data added in the Q and P parity blocks (see Fig. 11, Part 5, July).

TELEVISION OCTOBER 1989

A more detailed view of the error detection and correction (ERCO) and interpolation blocks is shown in Fig. 4. After serial-to-parallel conversion the data from the e.f.m. demodulator is stored in an external RAM (the connection is via pins 29-37 of the decoder chip). The RAM first makes the data, in the form of 24 8-bit audio symbols, four 8-bit P parity symbols and four 8-bit Q parity symbols (32 symbols in all), available to the C1 decoder where the P parity bits are used to detect and correct any single error per block of 32 symbols. If more than one error is detected the C1 decoder will be unable to carry out correction. Instead it places a flag on the remaining 28 symbols (the four P parity symbols are now redundant), marking them all as unreliable, and passes them on.

The symbols are next de-interleaved by introducing different delay times for different symbols. Any symbols that were given error flags by the C1 decoder will now be scattered and interleaved between a number of correct symbols. The C2 decoder thus receives a combination of correct and unreliable symbols. If there are no more than four errors over 16 frames it will use the Q parity bits to correct the errors. If there's a larger error the C2 decoder will pass the remaining 24 8-bit audio symbols in uncorrected form to the following descrambling and interpolation circuits.

The interpolation block converts the 8-bit symbols back into the original 16-bit word (L/R audio samples). It also looks for any words that carry a flag inserted by the C1 decoder, replacing such words with an interpolated one. This completes the decoding process.

The Sony CX23035 decoder chip provides the 16-bit audio data output in either serial or parallel form. Pin 59 (PSSL) is for serial/parallel selection – a low for serial and a high for parallel output. Most manufacturers including Sony seem to opt for a serial output which, being slower, greatly simplifies CD player design. Pin 78 is used for the serial data output. The other output pins 62-77 can be used for various read/write data: with many players that use this chip in the serial output mode these pins are left disconnected. When used in the parallel output mode pin 62 carries the least significant bit while pin 78 carries the most significant bit. In this mode the read/write data is not required.

The RAM

The RAM used in the decoding system has three main functions as follows: (1) It's used for for de-interleaving the 8-bit symbols which were scattered amongst the frames during the recording process. (2) It serves as a buffer between the error correction processes. (3) It absorbs jitter, i.e. wow and flutter.

The RAM's capacity is of the order of $8 \times 2K$ bits (in other words it can store up to 2,000 symbols) but it's not allowed to fill up completely. A detailed description of the movement of data into and out of the RAM would be tedious and probably send readers to sleep before the end. In view of this I've devised a simplified description that should satisfy all but the most probing minds.

The data comes off the disc in serial form but the 8-bit symbols fed to the error correction stages are in parallel form. This is necessary because the 8-bit symbols are still scrambled within each frame and are interleaved across several frames: in order to de-interleave and unscramble the symbols (or, to put it simply, to reshuffle them) they must be handled as complete units rather than one bit at a

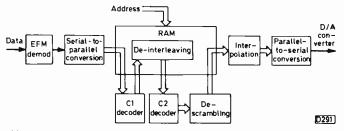


Fig. 4: How the signal is handled during the error correction processes: the RAM makes it available to the various decoders and carries out de-interleaving.

time. As we've seen (Fig. 4) the symbols move from the e.f.m. demodulator to the RAM, from the RAM to the C1 decoder and back again, from the RAM to the C2 decoder and back again after descrambling, and finally from the RAM to the interpolation block. After parallel/ series conversion (if required) the data is fed to a digital-to-analogue converter.

In practice the movement of data is not as straightforward as Fig. 4 might suggest. There are several reasons for this. First, as we saw in Fig. 9, Part 6 (August), after Cl decoding the symbols pass through a series of unequal delay lines in order to carry out the de-interleaving process. This delay is performed by extracting the symbols from the RAM in a different order from that in which they were fed in. Secondly you can't write into and read out of a RAM at the same time. Thus the symbol shuffling that occurs during the ERCO processes has to be done in a particular order – in reality not more than three symbols are moved at any one time. Finally, don't forget that fresh data from the disc continuously enters the e.f.m. demodulator and has to be stored in the RAM fairly quickly.

Movement of the symbols through the decoder is clocked at a rate of 2.16MHz by the crystal oscillator connected to pins 53-54 of the CX23035 chip.

Correction Capability

The ERCO section of the decoder can correct an error up to 448 symbols long, which is equivalent to fourteen frames. Thus an error burst of up to 1.9msec duration will go unnoticed, this duration being equivalent to a 2.5mm flaw in the disc. After interpolation a dropout to an extent of 48 frames can be concealed, representing an area of 8.7mm on the disc – which is how the idea of drilling a half-inch hole in the disc and hearing no dropout arose. Bear in mind however that a minute scratch travelling along the track could cause an error of greater than 48 frames. This will result in audio mute and probably track jumping.

Jitter Absorption

We mentioned earlier that the RAM absorbs wow and flutter. CD player specifications usually quote the wow and flutter as being unmeasurable: Sony try to be a little more precise in stating that its players have "quartz precision". Having read this, the uninformed person may conclude that the disc rotates at a very precise speed. Nothing could be farther from the truth! The disc servo is designed to ensure that the disc rotates at a velocity that results in a data rate of approximately 4·3MHz. If this velocity fluctuates slightly however it won't affect the rate at which the RAM is read, it will alter only the rate at which the data from the e.f.m. demodulator is written into the RAM. Thus the wow and flutter are literally determined by the precision of the crystal clock oscillator.

One possibility had to be considered by the designers. What would happen if the RAM became full because the disc was rotating a little too fast? The answer is that some of the music data would be lost. To prevent this, the disc servo is linked to the RAM. If the RAM begins to overfill, the servo slows the disc for a moment, reducing the data input rate. Conversely if the RAM starts to look empty the servo speeds up the disc a little. With the CX23035 decoder the margin of correction is ± 4 frames.

Subcode Decoding

We must not forget the 8-bit subcode symbol at the start of each frame. Each 96-bit subcode word starts with a distinct subcode sync pattern. This sync symbol is detected by the chip which also diverts the 8-bit subcode into its own decoder. The sync signal is fed out at pin 24. It goes to the central control microcomputer chip which contains enough RAM to store 96 8-bit symbols. On receiving a sync signal the microcomputer clears part of its RAM and prepares to write in the latest subcode data. Once 96 8-bit symbols have been arrayed in this RAM the subcode word can be read and the mute and front display activated as required.

The Q subcode containing the display data appears at pin 23 of the CX23035 chip. The output pin for all the other data (P, R, S, T, U, V, W) is pin 22. Only the P and Q data is used at present. In the event of the other words being brought into use in the future existing players would simply ignore the additional data as the central control microcomputer chip would not be programmed to interpret and act on it. If there's an error in the subcode, the CRC output at pin 20 goes low to inform the microcomputer chip that the subcode is erroeous. The microcomputer will then perform the CRCC operation mentioned in Part 7.

Frame Sync Detection

Each frame of data starts with a 24-bit frame sync signal. When the disc speed is correct this will have a repetition rate of 7.35kHz. Since disc speed variation will alter the frame sync frequency the sync signal serves as a disc servo sample.

As you can see from Fig. 2, the frame sync signal is extracted from the data stream before the e.f.m. demodulator. This is because the frame sync signal is the only data on the disc – apart from the merging bits – that's not eight bits in length and has not been converted into a 14-bit word.

The sync passed to the disc servo is known as guard frame sync (GFS) because the detector is designed to protect against errors. These errors will be present not only when there's a dropout. They also occur during the disc run-up period when the disc is being brought up to normal speed and the data rate is thus slow. You may recall that the detector is designed to look for the very only time that so many consecutive zeros are present. The detector operates on a "window" principle, i.e. it not only looks for the distinctive double burst of ten zeros but also expects them within a certain time period, the window. During the run-up period when the data rate is slow the detector would miss the sync signal. As this would cause disc servo problems the window is ignored during the disc run-up. In Fig. 2 you'll see that there are inputs WSEL

TELEVISION OCTOBER 1989

(window select), GSEL and GSEM. These come from the microcomputer and are used to switch the sync detector's action.

A signal generator is incorporated in the frame sync section to provide protection: it supplies pulses that act as substitutes for any missing ones. In addition the phase of this internally generated signal is compared with that of the off-disc frame sync signal. When the two are locked, the window width is set for "normal speed" operation. When the two are not locked (during the run-up) the GSEL and GSEM inputs alter the action of the detector to enable it to pick out the lower frequency frame sync signal.

Fault Diagnosis

Any fault in the decoder will result in loss of sound. This is not very helpful however since almost every fault in a CD player will remove the sound. Furthermore because of the complex links between the decoder chip and the central control microcomputer chip it's very difficult to prove that the decoder i.e. has failed – unless it's approaching melting point. So where can you begin?

Let's first consider the possibilities when the disc is rotating but there's no sound output. If the disc speed is correct, the servo must be receiving the frame sync signal. This means that the early stages of the decoder are working. My first checks would be on the supply lines, the PLL oscillator and the clock oscillator (pins 53/4 of the CX23035 chip). I would then check the focus and tracking servo adjustments, but as we've not covered these areas I'll not go into any detail for the present.

The next step would be to scope significant data lines, such as the serial audio data (pin 78), RAM address (pins 38-48), GFS (pin 28) and the microcomputer clock (pin 13). In some cases it might be helpful to check for P and Q subcode outputs (pins 22 and 23). The presence of these outputs would lead me to doubt whether the decoder chip has failed – large chips such as the CX23035 rarely fail in just one section, which would be the case since only the ERCO blocks remain after the subcode take-off point.

Let's now consider the situation when the disc either fails to rotate or takes off uncontrollably. There are once again many possible causes of these symptoms, and to isolate the cause to the decoder chip can be difficult. With the CX23035 you may find yourself arriving at this chip quite quickly because it contains the disc servo. This is not the case with some other chip sets. In addition if the disc won't run at approximately the correct speed it will be impossible to scope any relevant signals. The only advice I can offer here is that in most cases these symptoms are produced by faults in the focus or tracking servos and that you should therefore start by ruling these out. If these servos appear to be operational and you've carried out the other basic checks such as supply lines, oscillators, etc. there's little choice but to check the decoder chip by substitution. This step is not to be taken likely with the CX23035 since it's an 80-pin surface-mounted device.

Finally there's one decoder fault that doesn't result in total loss of sound. This is when a single RAM address line fails. In this case the result is a very coarse "rushing water" sound on both channels. The same effect may be produced when the RAM chip fails.

Next month we'll consider the final stages of audio signal processing – the digital-to-analogue converter, L/R signal separation and filtering.

CCTV Faults

Peter Graves

As with all complicated electronic equipment, closedcircuit television presents its own particular problems. You think you've seen it all, then something unexpected occurs. Here are some of the more uncommon problems we've encountered in the field.

Misting Windows

Camera housings designed for outdoor use have a heater under the front window to keep it clear of condensation. In modern housings the heater consists of one or more high-wattage, aluminium-clad resistors connected across the mains supply. A thermostat inside the housing brings the resistor(s) into circuit when the temperature drops to a point where condensation is likely to form. A small metal shield above the resistor(s) guides the warm air flow.

Several cameras in housings were installed around the edge of a large site. After a short period of operation we received a complaint that the windows were misting up. This is not unusual in a new installation, particularly if moisture has been trapped inside the housings when installed. A visit to the site during the day showed nothing out of the ordinary.

The complaints persisted and a second visit was made. Visual inspection of the pictures showed some apparent misting so we decided to clean the housings. When the first camera was swung down on its pole we realised that the weather was too warm for condensation to form – then the cleaning cloth showed a black deposit! The housing manufacturer had used ordinary mains cable to wire the heaters and black rubber sleeves to insulate the connections to the resistors. The heat produced by the resistors had been enough to melt the sleeves and the cable insulation, the fumes produced being responsible for the "misting" problem.

A heat-resistant type of cable was fitted, with silicone rubber sleeves – and the manufacturer was made aware of his mistake.

Sticky Iris

On several occasions a customer complained about a "no picture" fault. It would sometimes clear itself, but at other times was still there when an engineer called. You could see from the picture and the video waveform that the iris appeared to be sticking open.

The camera is used to supervise an outside area and is mounted in a weatherproof housing with an infra-red lamp for night-time illumination. It's fitted with a low-light tube and a zoom lens. The lens iris is motorised, being driven by an auto-iris circuit within the camera. When the scene illumination drops, the output video level falls. The voltage change is detected by the auto-iris circuit, which responds by opening the iris to restore the original video level. Conversely when the scene illumination rises the iris is driven towards the closed position. Fig. 1 shows the arrangement. The circuit tries to keep the video waveform at a constant level. Access to the camera is poor – it's some twenty feet up a vertical pole and is difficult to get at from a ladder. As soon as the camera was disturbed by removing the cover of the weatherproof housing the lens iris would come unstuck and operate correctly. It then couldn't be made to stick. Several days later the customer would be on the phone again. In the end we had to remove the camera and lens from the housing and take it back to the workshop for a closer look.

To prevent the drive motor stalling and possibly damaging the lens when the iris reaches the end of its physical travel microswitches are incorporated in the auto-iris circuit – see Fig. 2. Suppose that the iris has been driven far enough for the cam on the lens to operate microswitch S1. This will bring diode D1 into circuit. Its polarity is such that it is reverse biased, thus preventing further movement of the motor in the direction concerned. Should the motor voltage reverse, D1 will be forward biased and the motor can run, moving the lens towards the other end of its travel. The arrangement is such that the motor can be driven in either direction provided it doesn't reach one end. D2 operates at the other end of travel.

Both switches appeared to be working correctly – they make a distinct click when they operate, and the motor would stop – but we decided to check them with an ohmmeter. As a result we discovered that one of them had developed a high-resistance path internally. This meant that when it operated it effectively added a resistor in parallel with the diode.

When the light dropped at night the iris would open until the microswitch operated. The diode should then have stopped the motor from turning any farther, but the resistance allowed current to flow. As a result the motor continued to turn until it stalled. Sometimes it turned far enough to jam the lens iris which would stick until physically disturbed. There was no obvious cause of the microswitch failure and a replacement provided a complete cure.

Auto-pan Problem

Maintenance at this site, with elderly equipment installed, had previously been carried out by other companies. It was a very large site and the cameras were controlled from a central point via a telemetry system. As the camera controls were operated, digital signals were sent to a receiver at the selected camera. They were then decoded and used to operate the relays that activate the camera functions – Fig. 3 provides an outline of the system.

The faulty camera was used to watch a large open area and had an auto-pan facility. When auto-pan was selected, the pan-and-tilt head continuously moved the camera from side to side. No problem here but the camera would sometimes, without auto-pan being selected or any of the other camera controls being operated, move across from right to left until it reached the end-stop at the far lefthand side. It would then stop.

The previous maintenance company had blamed noise on the phone lines carrying the telemetry signals and had done nothing about the problem. Telemetry systems are not normally troubled by noise however since error detection is built into the system. In addition, noise would be unlikely to initiate just one of the control functions.

Since the other cameras worked correctly it was unlikely that the fault was at the control room end. A quick

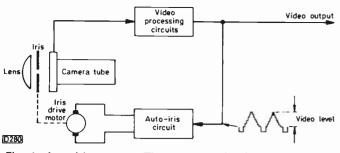


Fig. 1: Auto-iris system. The auto-iris circuit drives the iris so that it opens or closes to maintain a constant average video level.

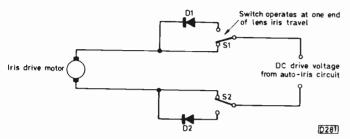


Fig. 2: The microswitch arrangement.

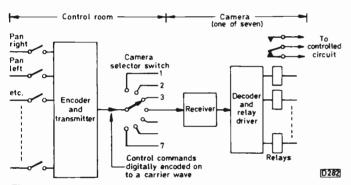


Fig. 3: Outline of the telemetry control system.

check on the receiving unit revealed that the smoothing capacitor in its power supply had partially failed, as a result of which there was some 2V of hum on the 12V rail. Presumably this was upsetting the decoder and relay driver as fitting a replacement cleared the problem.

Vandalism

Running the connecting cables to a camera on a panand-tilt head that can be moved over a wide range always presents problems. There must be enough slack to allow it to move freely, but if there's too much slack the cables can get caught in the mountings. Pan-and-tilt head motors are powerful enough to rip the cables off. In modern installations the cables are run up the inside of a length of flexible conduit to provide protection. The conduit is less likely to get caught and gives the job a neat, professional appearance.

The pan-and-tilt camera concerned was one of two used for surveillance at a car park. They were in continuous use and were fitted with infra-red lamps for night-time operation. As the light level changed the lamps were automatically switched on and off by photoelectric cells at the rear of the lamp housings.

The first hint of trouble came when one of our engineers was called out because "both cameras were dead". On arrival a rather apologetic security officer told him that the problem was due to the earth leakage circuit breaker coming out and that it had been reset. Both pictures were present and as the security staff were satisified with them our engineer returned to base. On the following day we received another call because one on the pan-and-tilt units had apparently stopped tilting. The camera was on a pole, and visual inspection from the ground showed that the flexible conduit had kinked into a tight loop, preventing the tilt axis operating. While making preparation to winch the camera's mounting pole down we noticed that the photoelectric cell from one of the lamps was lying on the ground next to the pole – an unusual occurrence as they have a tigh bayonet fitting and don't usually fall out by themselves.

Closer inspection showed that the camera had been severly stoned from a nearby bridge. The stones had knocked out the photoelectric cell and we guessed that the ingress of rain into the open socket had been responsible for the earth leakage breaker trip operating on the previous day. The stones had also distorted the camera housing and damaged the nut that held the flexible conduit, allowing it to rotate. This had in turn made the conduit kink, locking the tilt axes. Fortunately the camera had been pointing away from the direction of attack, so that the glass camera housing faceplate and the lenses and filters of the infra-red lamps had escaped damage.

Our experience is that deliberate vandalism like this is rare but it brought to mind several other cases, like the poor picture fault with an indoor camera looking at an exit door. It was mounted without a housing some seven feet from the floor and the lens had been sprayed with some oily liquid. Another indoor camera had to be put into a housing to prevent persistent fiddling with the lens settings by persons unknown.

Camera Development Problem

Vidicon cameras were built by a small company. To start with each camera was hand-built in the development department by a technician, using rat's nest point-to-point wiring. The cameras worked but tended to be unreliable, could be built on only a one-off basis, and looked extremely untidy. As demand increased it was realised that a more professional approach was needed, and that construction would have to be turned over to nontechnical wiremen. The plans were redrawn in the production department, with the interconnecting cables redesigned as cable looms. This took place against dire warnings from the development department that the cameras would never work with looms because of the extra cable lengths and interaction between them.

The first camera to come off the production line was put on the test bench. It set up well on a test chart, except for the fact that the top of the picture appeared to be pulled over slightly. Consternation in production, cries of "we told you so" in development!

The test engineer started his investigation. He progressively replace the loomed wires with a point-to-point rat's nest. Eventually the looms had been removed completely and the wiring was back to the development department's standard. Unfortunately the fault was still present!

Further investigation was carried out by the production department. It was eventually found that the distortion was caused by an incorrectly specified capacitor in the line output stage. It was an original design fault, not an assembly error. In fact all the cameras had the fault. It was just that no one had looked at them as critically as they had looked at that first one off the production line!

Servicing Salora Colour Receivers

Part 3: G and H Chassis continued

Nick Beer and Ian Bowden

Last month we described the operation of the Ipsalo-1 circuit used in earier versions of the G and H chassis. The Ipsalo-2 circuit is totally different. Fig. 1 shows the overall Ipsalo-2 circuit as used in the H chassis while Fig. 2 shows the circuitry within the LF0034A hybrid chip that provides the drive for the chopper transistors TB700 and TB701. The G chassis uses an LF0034 hybrid chip which is slightly different from the LF0034A and there are several other differences in the implementation of the Ipsalo circuit, with a completely different set of component reference numbers as well. The following description applies to the H chassis version of the Ipsalo-2 arrangement.

The mains input is rectified by the diode bridge DB708-711 which develops about 320V across its reservoir capacitor CB721. Note that CB721 and the smoothing capacitor CB722 are two sections of a double unit.

Start-up Action

As these sets and subsequent models have no transformer derived start-up/standby supply, a simple start-up pulse generator circuit is used to get the chopper transistors going initially. Once the circuit is operating normally, the hybrid chip HB1 takes over the supply of drive to the chopper transistors. The start-up pulse generator consists of resistors RB734/716/715, capacitor CB715 and diac DB725. CB715 charges via the three resistors from the 320V supply. When the voltage across it reaches approximately 35V the diac fires, discharging CB715 via RB705 and CB712 to provide a short base drive pulse for TB701, the "lower" chopper transistor. As the diac is also connected to one of the two secondary windings on the driver transformer MB700, a drive pulse will also be induced in the other secondary winding. This is coupled to the base of the "upper" chopper transistor TB700. Thus both transistors receive drive pulses and the full 320V is switched on and off across the primary winding (pins 2-1) of the combi transformer MB500. As the voltage across CB715 falls, the diac will cut-off. CB715 will then start to charge again and the cycle will repeat.

This repeated switching of the chopper transistors results in a voltage being developed across the close-coupled secondary winding (pins 17-18) on the combi transformer. DB504 rectifies the output from this winding, producing a d.c. supply that's fed back to pin 19 of the hybrid chip. An emitter-follower (Q1) within the chip produces, in conjunction with the 9.1V zener diode connected to pin 20, a regulated 8.5V start-up supply which appears at pin 18. It's used to supply the bistable circuit (pulse-width modulator) within the chip and provides a start-up voltage for the TDA2593 sync/line generator chip ICB501, the chopper driver transformer MB700, the line driver transistor TB500 and the line pulse lengthening circuit TB508/9 etc. The line generator will then produce pulses to drive the line output stage and the bistable in the chopper control hybrid chip – the input to the chip is at pin 15. Thus normal drive to the chopper transistors will be established, but with a very short switch-on time. As the line output stage comes into operation a supply of 142V (125V in 16 and 20in. models) will be developed across CB513. This is fed to pin 12 of the hybrid chip, and as a result the ramp charging circuit comes into operation, increasing the on time of the chopper transistors. In this way a soft start is achieved. As the chopper transistors come under the control of the hybrid chip their on-to-off time will be far greater than that provided by the start-up pulse generator, which is overridden by connecting the junction of CB715/DB725/RB715 to the collector of TB701 via DB714 and RB708.

The set has now reached its normal operating state. What can be a problem when fault finding is that this start-up sequence takes very little time – from switch-on to normal running takes about one second.

Regulation

Regulation of all the supply lines is based on feedback of the voltage developed across CB513. This voltage is connected directly to pin 12 of the hybrid chip. A resistor within the chip provides a link to pin 13, which is connected to the smoothing capacitor CB719. The voltage at pin 13 depends on the conduction of Q6. It's fed via RB718 to a charging capacitor within the chip, connected between pins 6 and 8. This capacitor charges, producing a ramp waveform which is applied to the base of Q3. When the ramp voltage reaches a certain level Q3 switches on and the bistable circuit changes state. When the next pulse from the line generator chip arrives at pin 15 it switches on Q5 to discharge the ramp capacitor. Since Q5 shorts the base of Q3 to chassis the state of the bistable changes back again.

Should the charging voltage at pin 13 of the hybrid chip rise above the normal level - in this case the voltage across CB513 will have fallen - the ramp developed by the charging capacitor will reach the triggering point earlier. Thus the mark-space ratio of the bistable will increase, Q3 remaining on for a longer time before the next line pulse switches it off again. The chopper driver transistor Q4 is held conductive by the d.c. voltage, derived from the combi transformer, fed in at pin 3. Q4 switches off when Q3 switches on. So with Q3 remaining on for a longer period Q4 will be switched off for a longer period. When Q4 switches from on to off the energy built up in the primary winding of the driver transformer MB700 is released into the secondary windings, producing drive pulses for the chopper transistors. Under the conditions so far outlined the length of the drive pulses will increase, keeping the chopper transistors on for a longer time. Thus more energy will be built up in the combi transformer before the chopper transistors switch off again. The result is more energy being transferred from the mains to the secondary windings on the combi transformer, bringing the output voltages back up to the correct level.

Note that a fall in the voltage across CB513 leads to an increase in the voltage at pin 13 of the hybrid chip. This is because of the inverting action of the regulating transistor Q6: when the voltage across CB513 falls, Q6's base voltage is reduced and its collector voltage rises. The



TV SERVICE SPARES PHILIPS SPARES PHILIPS SPARES G8 VARICAP CONTROL £2.50 p.p. £1.00. G8 PANELS (Tested) Power £12.50, Scan £15.00, Signals £15.00 p.p. £2.50. KT3, K30 PANELS, tested, exchange, sound, power, bridge rect, frame, RGB £7.50 each. Decoder (Non-text) £10.00 p.p. £1.50. G11 TDA2600 IC HOLDER 70p p.p. 30p. G11 PANELS (tested), frame, IF, decoder £12.50 each. p.p. £2.00. Scan £15.00 p.p. £2.80. Power tested exchange £18.00 p.p. £2.80. G11 PANELS EX-RENTAL (unitested) Scan, Frame, Decoder £2.50 p.p. £2.00. G11 FPANEL (new) less Tuner £2.50 p.p. £1.30. G11 8POS Touch Tune Channel Selector (replaces old type) incl. instructions £25.00 p.p. £1.80 £25.00 p.p. £1.80 G9 POWER SUPPLY UNIT £5.00 p.p. £2.30. HANDSETS EX-RENTAL, TEXT UNTESTED. KT, TEXT/VIDEO TYPE £3.50 ματολικό μα **THORN/FERGUSON SPARES** 8000, 8500, 8800, 9800 PANELS tested, exchange. £8.80, Frame. Decoder £10.00 p.p. £2.30. 9000 Series 1F/Decoder tested £10.00, Line/Power £20.00, Frame £18.00 p.p. £2.80. 9500/9600 Line Scan £25.00, Power £20.00 p.p. £2.80. TX9 Panels complete & tested £28.00 exchange (shop only) TX9 TX1 Exclamation of the second seco

 TX9 Panels complete & tested 228.00 exchange (shop only)

 TX9/TX10 Facia, control panel mcl, infra-red receiver £5.00 p.p. £2.00

 TX16 Focus control £8.50 p.p. £1.00,

 TX9/TX10 Saw filter IF panel £5.00 p.p. 80p.

 TX9/TX10 Saw filter IF panel £5.00 p.p. 80p.

 TX9/TX10 Remote & tuning control panel 1515 (incl. SAA5012) £7.50 p.p. £1.80.

 TX9/10 Remote & tuning 1508A (incl. SAA5012) £2.50 p.p. £1.80.

 TX10 Stere Tune 1509G (incl. UAA1008 + BATT.) £3.50 p.p. £1.80.

 TX10 Stere Audio Board £3.50 p.p. £1.80.

 TX10 Stere Audio Board £3.50 p.p. £2.80.

 TX10/TX90/TX100 Chassis complete & boxed (untested) £20.00 p.p. £2.80.

 IC
 SELECTION

 £1.80
 TDA1170
 £2.20
 TDA2594

 £1.20
 TDA180
 £2.20
 TDA2595

 £1.80
 TDA11902
 £2.20
 TDA2595

 £1.80
 TDA11902
 £2.20
 TDA2595

 £1.80
 TDA11902
 £2.20
 TDA2640

 £6.80
 TDA1701
 £3.20
 TDA2640

 £6.80
 TDA1701
 £3.20
 TDA2641

 £6.80
 TDA1701
 £3.20
 TDA2641

 £6.80
 TDA1871
 £6.80
 TDA2651

 £1.80
 TDA1840
 £2.80
 TDA2651

 £1.80
 TDA1840
 £3.20
 TDA2651

 £6.80
 TDA2651
 £3.20
 TDA2640

 £6.80
 TDA1840
 £3.20
 TDA2650

 £6.80
 TDA2651
 £3.20
 TDA2640

 £6.80
 TDA2640
 £3.20
 TDA2640

 £6.80
 TDA2640
 £3.20
 TDA2640

 £6.80
 TDA2640
 £3.20
 TDA2640

 IC SELECTION £1.80 SL1430 £3.50 SL1432 £5.80 SN762260N £3.80 SN767015 £3.80 STK5481 £4.80 STK5481 £5.80 STK5481 £5.80 STK5481 £5.80 STK5481 £5.80 STR451 £2.80 STR451 £2.80 STR451 £2.80 STR451 LA7800 £3,80 TDA3571 TDA 3571 TDA 3576 TDA 3656 TDA 3651 TDA 3652 FDA 3653A TDA 3653B TDA 3653B TDA 3654 TDA 3654 TDA 4420 TDA 4421 IDA 4421 IDA 4422 FDA 4500 TDA 4503 £4.80 LA7800 LA7801 M293B1 MC13002P ML237 ML238 ML238 £4.80 £7.50 £1.90 £3.20 £5,80 £5,80 £4,20 £3,20 £3.20 £5.90 ML923 £5.70 £3.20 SAA1024 £6.80 £3.20 SAA1024 SAA1025 SAA1124 SAA1251 SAA3027 SAA5000 SAA5010 £5.80 £5.80 £3.50 £6.80 £5.80 £2.80 £5.80 £3.20 £3.80 £3.80 £3.50 £4.20 £0,80 £10,80 £7,80 £6,80 £5,80 £6,80 £8,80 £5,80 £1,20 £2,20 £2,20 £2,20 £2.20 £3.21 £6.80 £5.80 £6.80 £5,80 STR50103 £6.80 TDA4503
 \$5,80
 \$TR\$003

 \$5,80
 \$TR\$020

 \$5,80
 \$TR\$020

 \$5,80
 \$TR\$120

 \$5,90
 \$TA\$105

 \$5,20
 \$TD\$1040

 \$5,20
 \$TD\$1040

 \$5,20
 \$TD\$106

 68.80
 TDA2510
 66.80

 £5,80
 TDA2522
 £3.80

 £1,20
 TDA2534
 £5.80

 £2,20
 TDA2571
 £3.80

 £2,20
 TDA2577
 £4.80

 £3,30
 TDA2577
 £3.80

 £2,20
 TDA2577
 £3.80

 £3,30
 TDA2577
 £3.80

 £3,40
 TDA2574
 £3.80

 £2,20
 TDA2577
 £3.80

 £2,30
 TDA2578
 £3.80

 £1,40
 TDA2578
 £3.80

 £1,90
 TDA2578
 £3.80

 £1,90
 TDA2578
 £2.90

 £2,90
 TDA2582
 £2.80

 £3,80
 TDA2593
 £2.80
 SAA5010 SAA5012 SAA5020 SAA5030 SAA5030 SAB3035 SAB3035 £6.80 £3.50 £6.80 £9.80 £2.50 £3.50 1DA4505 1DA4600 1DA4600 1DA4610 1DA8180 1DA8190 1DA9403 £2.80 £2.80 £3.80 £6.89 £3.80 LDA3541 £3.80 1DA3541 TDA3560 1DA3561A 1DA3562A 1DA3565 TDA3566 SAF1032 \$4.80 1DA9503 £3.80 SAF 1032 SAF 1039 SL470:471 SL486 SL490 £5.80 £5.80 £3.80 £5.80 TDA9505 TDA9513 TEA1009 TFA1014 TEA2018A £1 80 £4.80 £2.20 £3.50 £2.20 IC p.p 50p VARICAP TUNERS: Grundig 8630 series £5.00 p.p. £1.00. U321, U322/ U341/NSF204, ELCI043 (equiv), SC4, VHF NSF203 £7.80 p.p. £1.80. UHF/VHF UV411 £10.80, U343 £10.80 p.p. £1.00. LINE OUTPUT TRANSFORMERS
 CALVSP ORVHERS
 \$5.60

 R.B.M. T20, T22 Bobbin
 \$5.60

 DECCA Bradtord (state Mod No)
 \$8.80

 FIDELITY ZX2001, 3000 (Not 22') £15.50
 \$68.80

 ITT CVC 5109, CVC20
 \$9.80

 ITT CVC 5109, CVC20
 \$9.80

 ITT CVC 5109, CVC20
 \$9.80

 ITT CVC 51, CVC30 series
 \$8.80

 ITT CVC 52, CVC30 series
 \$9.80

 ITT CVC 1200/1200
 \$12,50

 PYE 725 (90') 731 to 741
 \$9.20

 PHILIPS G8
 \$6.80
 SONY KV1882 SONY KV2092/2096 .. £34.50 .. £34.50 £9.80 £12.50 THORN TX9 £3.20 ...£8.80 ...£7.80 ...£9.80 £22.50 £22.50 £22.90 SPECIAL OFFER THORN TX10 £16.50 PHILIPS G8 PHILIPS G9 РИПЛРS (5) РИПЛРS (KT3, ..., РИПЛРS (K30, K35, РИПЛРS (TX-E, S, РИПЛРS (TX-E, S, РИПЛРS (T4/K40,... РИПЛРS (Т4, ..., РИПЛРS (СТ1, ..., £4.80 £2.80 £5.00 TTT V C300 PHILIPS 320 PHILIPS G11 GEC 2028, 2040, 2100 PYE 691-7 chassis type only R.B.M. T20, T22 £1.00 £5.00 £26.80 £32.80 £9.80

172 WEST END LANE, LONDON, NW6 1SD PLEASE ADD VAT 15% TO ALL PRICES INCL P+P

 TRIPLERS: THORN 9000 £8.80 p.p. £1.50.

 UNIVERSAL (best quality) £7.80 p.p. £1.50.

 CONTINENTAL TVK & BG RANGE (quote exact no.) replacements £13.80

 DECCA/TATUNG £7.80 p.p. £1.50.

 6.3V CRT Boost Transformers for Colour & Mono £5.90 p.p. £1.40.

 655 CONTENTS & State of the last of the \$51 mm.

CALLERS WELCOME AT SHOP PREMISES THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS Telephone 01-794 8751, 794 7346

MANOR SUPPLIES

455 CRVSTALS for Remote Control Handsets. 4 for £1.00 p.p. 50p. **VHF to UHF** Converters £26.50 p.p. £2.50.

LOPT's p.p. £1.50

1/54

opposite occurs when the voltage across CB513 rises.

Circuit Protection

In the event of very heavy loading across CB513, for example the line output transistor being short-circuit, the voltage at pin 12 of the hybrid chip will be very low. As a result there will be virtually no charging voltage at pin 13 and the bistable will be switched only by the line pulses fed in at pin 15. As these are of short duration (8 μ sec), the drive pulses used to switch on the chopper transistors will also be of short duration and the minimum amount of energy – just enough to produce the 28V supply – will be transferred from the mains to the secondary side of the combi transformer, preventing damage to the power supply.

Should the regulating section of the hybrid chip try to increase the energy supplied to the set above a safe level (this would mean an increase in the voltage at pin 13) zener diode DB720 will conduct, switching on Q5 to short out the charging capacitor. The bistable will then be driven by the line pulses alone, giving power supply protection. In this state enough energy should be supplied to the close-coupled secondary winding on the combi transformer to keep the line oscillator and Ipsalo circuit going. To unlatch Q5 the set must be switched off for a few seconds.

If for any reason the voltage across CB513 rises, the action of the regulation circuit will cut back the charging voltage, shorten the conduction time of the chopper transistors and thus provide over-voltage protection.

Standby Operation

When an 18V standby signal is produced by the remote control panel it has two effects. First, it's coupled to the base of the regulating transistor Q6 via DB721 and RB719, as a result of which Q6's collector voltage falls to a low level. As we've seen, the effect of this is to reduce the energy supplied to the secondary side of the combi transformer to a minimum level, all that's needed being the 28V supply to keep the line oscillator, Ipsalo and remote control circuits going. The second action is to bring transistor TB507 into action to invert the lengthened line drive pulses applied to the line output transistor. As a result the line output stage removes energy from the secondary side of the combi transformer instead of adding to it as it does via the action of the flyback pulses during normal operation. This stops any build-up of unwanted energy.

Fault Finding

Now for some hints when fault finding in this circuit.

First remember what's required to get the set into the normal running condition: (1) a mains input, (2) a rectified supply across CB722, (3) operation of the start-up pulse generator so that the 28V supply is produced, (4) development of an 8-5V start-up supply at pin 18 of the hybrid chip and (5) a line pulse output at pin 3 of the TDA2593 chip ICB501, with the pulses reaching pin 15 of the hybrid chip. We'll consider each of these in turn.

No mains supply to the rectifiers probably means a blown mains fuse or an open-circuit mains switch contact. We had one case where pressing the mains switch in produced a burst of mains energy that was just enough to get the set started before the switch went open-circuit and the set died. No 320V supply across CB722 usually means that the filter resistor RB713 (22 Ω , 5W) is open-circuit. The usual reason for this is that one or both of the chopper transistors has gone short-circuit. Replace them as a pair and check by lifting one end of each that all the rectifier diodes on the primary winding side of the combi transformer are o.k. A common cause of this condition is a dry-joint at or a defective line scan coupling capacitor. This is CB532 (330nF, 250V) which should always be checked when you look at one of these sets.

No 28V supply could mean that the start-up pulse generator circuit isn't working. This is usually due to the diac being open-circuit or a dry-jointed or open-circuit $33k\Omega$ resistor (RB734/715/716). If there's a continuous whine at approximately 5kHz from the combi transformer the start-up circuit is working. If the voltage at the cathode of the 28V supply rectifier DB504 is very low, look for a short across the supply. The usual cause is a faulty audio output chip (ICB100, TDA2030) or a short-circuit 18V regulator chip (ICB502, MC78M18BT).

For no 8.5V start-up supply at pin 18 of the hybrid chip, check the voltage at pin 19. If this is less than 15V, check at pin 20. Zero voltage here indicates that zener diode DB722 is short-circuit, something that does happen from time to time. If approximately 9.1V is present at pin 20 the internal transistor is open-circuit, so the hybrid chip will have to be replaced. On one occasion the decoupling capacitor CB717 was short-circuit, as a result of which the voltages at pins 18, 19 and 20 were at nearly zero.

If there are no line-frequency pulses at pin 3 of the TDA2593 chip ICB501, check that approximately 8.5V is present at pins 1, 2 and 4. If so, try another i.c. On the only occasion when we had a fault in this area the chip was defective.

If there are line pulses at pin 15 of the hybrid chip the set should be able to start up. If the set is dead, it's likely that there's an overload condition. In this case proceed as follows.

Overload Checks

Check the voltage at pin 7 of the hybrid chip. If it's around 0.6-0.7V, zener diode DB720 is conducting. So there's either excessive loading on the secondary side of the combi transformer or DB720 is faulty.

Also check the voltage across CB513, i.e. at pin 14 of the combi transformer. If it's zero or very low there's likely to be a short in the line output stage. If the voltage is between 40V and its correct level of 125/142V (depending on tube size, see earlier) look for loading on one of the other combi transformer outputs, e.g. a faulty tripler (check by disconnecting the input lead). One of the secondary winding rectifier diodes might be short-circuit or there might be a short across one of the supplies make resistance checks to find out which one is shorted. Another possibility is a leaky diode (DB510/DB511) in the EW modulator circuit. If the line output stage is suspect, a simple check is to unplug the scan coils and connect two suitable diodes in series between pin 13 of the combi transformer and chassis - cathode to pin 13, anode to chassis. When the set is switched on the 125/142V and all the secondary supplies should be present. Don't leave the set in this condition for longer than you have to.

The same symptoms, i.e. no results with a high voltage at pin 13 of the hybrid chip and some 0.6-0.7V at pin 7, will be present when DB717 or DB718 is open-circuit, cutting off Q6. Alternatively Q6 could be open-circuit.

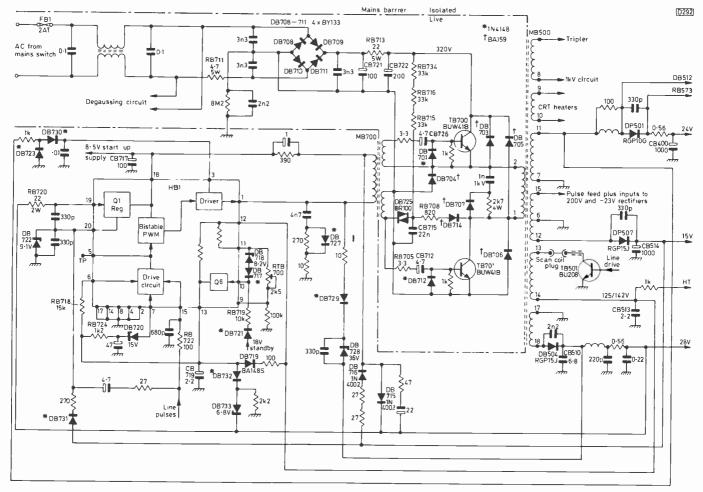


Fig. 1: The Ipsalo-2 circuit as used in the H chassis.

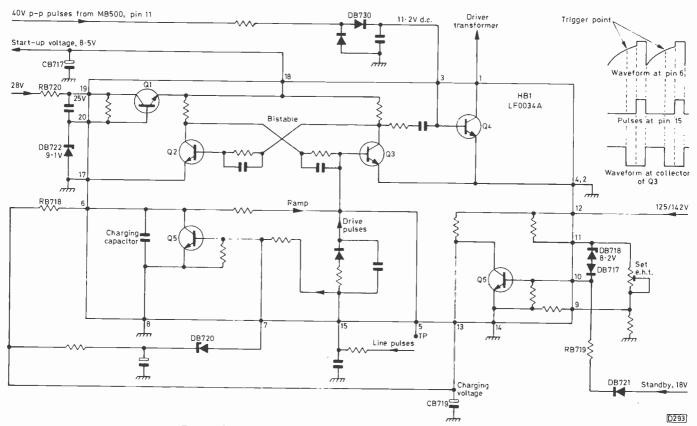


Fig. 2: Circuitry in and around the LF0034A hybrid chip HB1.

We once found that DB732 was leaky, producing around 21V at pin 13.

If the voltage at pin 7 is at the correct level (0.12V) or less, the overload should be along the lines of a complete

TELEVISION OCTOBER 1989

short-circuit across the 125/142V supply, e.g. a short-circuit line output transistor.

G Chassis Fault Guide

We will finish this instalment with fault lists for the G and H chassis, starting with the G chassis. Where a fault depends on whether the Ipsalo-1 or -2 circuit is used this will be specified.

(1) Patterning on high chroma levels. Realign the sound trap LA1 on the tuner/i.f. motherboard.

(2) Field collapse. The usual cause is the TDA1170S field timebase chip ICB1.

(3) Low brightness, contrast and colour levels, Ipsalo-1 sets. Check the BC307 transistor TA6 in the beam limiting system.

(4) Intermittent tripping, Ipsalo-1 sets. Try replacing the 18022 regulation thyristor THB1. Also ensure that a heatsink has been fitted to it. If not, fit one – part no. SCX077 (this part no. includes the thyristor).

(5) Set will not switch to standby from remote control, Ipsalo-1 versions. The 9.1V zener diode DB5 is probably faulty.

(6) Set carries out search tuning but will not store a channel. Check that the -23V supply is present at pin 2 of ICC8 (ER1400). If it is, suspect the chip.

(7) Set searches but will not stop when a channel is found. TC11 (BC237A) open-circuit base-to-emitter.

(8) No sound or picture, intermittent raster, Ipsalo-1 sets. TB17 (BFR80) on timebase motherboard faulty. A BD136 can be used.

(9) Low brightness. RH7 (1M Ω) on c.r.t. base panel open-circuit.

(10) Intermittent random channel change. Suspect ICS1 (MC74C922) on front panel, also the remote control decoder chip if fitted.

(11) Tuning drift. Usually a faulty AY-3-8203 microcomputer chip (ICC7). See (16).

(12) Reluctant to change channels or sticks on one channel. Suspect ICC7. See (16).

(13) Noise through speaker at switch on. Check CA55 $(47\mu F)$ in the audio output stage by substitution.

(14) Set will not start from standby but starts from cold, Ipsalo-1 version. TB15 (BFR80) intermittently opencircuit.

(15) Width and height variation, Ipsalo-1 sets. DB11 (8-2V zener diode) faulty, causing h.t. variation.

(16) The AY-3-8203 chip has been replaced with a type suffixed A. For compatibility the following modifications (boards STC0072-75) need to be made: add a 330 Ω resistor in series with DC25; change RC47 from 10k Ω to 27k Ω ; add a 220 Ω resistor in series with the store line; change CC38 from 68nF to 100nF.

(17) Excessive crackle on audio at switch on. Connect a 100k Ω resistor (RA97) between pin 5 of EJ1 and chassis. (18) The Toshiba tubes used in some sets magnetise and are difficult to degauss. Change CH1 from 1.5μ F to 3μ F and RH30 from 10 Ω to 22 Ω . These components are on the c.r.t. base panel.

(19) For tuning drift caused by a varying varicap voltage, particularly with 8-button models, reduce RCP1 from 470k Ω to 100k Ω and increase RCP2 from 12k Ω to 15k Ω . (20) For poor degaussing, try the following remedies. Reverse plug H2/1 on the c.r.t. base panel, add a 10nF capacitor between the gate and cathode of THH1 and a 1.5 μ F capacitor in parallel with CH1.

(21) Intermittent tripping with high beam current, Ipsalo-1

sets. Check that RA28 and RA29 are 33 Ω . Add a 3-3k Ω resistor between the base and emitter of TA6 and a 12k Ω resistor from the base of TA6 to pin 7 of connector A1 – cut the existing print to pin 7. On the tuning/memory panel, remove RC75 and DC9 and fit a 1N4148 diode with its anode to pin 13 of connector C2 and its cathode connected via a 12k Ω resistor to pin 22 of ICC1 and via a 1k Ω resistor to pin 20.

(22) Difficulty in starting sets with battery kit via the remote control unit. Add a $2 \cdot 2\Omega$ resistor and an RGP10G diode connected in series between pin 19 (resistor) and pin 15 (cathode of diode) of transformer MB1. Also add a $6 \cdot 8k\Omega$ resistor between pin 5 and chassis.

(23) Incorrect tuning potentiometer selected for number displayed. Poor plug and socket conection (S2) on front top control PCB or a dry-joint on one of the three data bus leads on the tuning potentiometer PCB.

(24) Cannot select correct tuning potentiometer. ICCP1 or ICCP2 on tuning potentiometer panel faulty.

H Chassis Fault Guide

The H chassis list is as follows.

(1) Peak white raster with flyback lines. RH7 ($680k\Omega$, 0.5W) on the c.r.t. base panel open-circuit. This removes the beam current limiting feedback.

(2) Width and height variation, Ipsalo-2 sets. DB718 (8·2V zener diode) leaky, causing variation in the 125V/ 142V supply.

(3) Excessive width, Ipsalo-2 sets. Width control RTB502 open-circuit.

(4) Set dead, Ipsalo-2 versions. 15V supply rectifier DB507 open-circuit or dry-jointed. This seems to be more common with Models 1H4/8.

(5) Slight width quiver, Ipsalo-2 sets. 142V supply slightly low. HB1 faulty.

(6) Crackling or shriek on sound. Audio output chip ICB100 (TDA2030) or, with Ipsalo-2 sets, intercarrier sound chip ICD2 (TDA1236) faulty.

(7) No sound, low contrast. ICC7 (AY-3-8203A) on the remote control panel faulty.

(8) No or intermittent failure to start at switch-on, Ipsalo-2 sets. DB722 (9.1V zener diode) faulty, causing loss of the start-up supply.

(9) Mains fuse and RB711 open-circuit, chopper transistors o.k., Ipsalo-2 sets. Reservoir/smoothing block CB721/ 2 faulty.

(10) Field distortion at top of screen with reduced width. ICB400 (TDA1170S) faulty.

(11) Set running with very low 142V supply (around 50V), Ipsalo-2 version. DB732 (1N4148) short-circuit.

(12) Top of picture stretched with a white line across the middle of the screen DB400 (1N4002) faulty.

(13) Set won't go to standby via remote control. Switch on back in wrong position – should be in position 2 (opencircuit). Alternatively TC102 (BC307) on remote control panel open-circuit base-to-emitter. With Ipsalo-2 sets TB100 (BC307) short-circuit will cause this fault – it's on the main panel.

(14) Field roll. ICB501 (TDA2593) faulty.

(15) Chopper transistors blowing, Ipsalo-2 sets. This can be caused by cracks or chips in driver transformer MB700 or a faulty hybrid chip (HB1).

(16) Tuning range too low, also drifting. CB105 (2.2nF) leaky.

(17) Sound muted and contrast low. ICC4 (4049 on remote control panel) faulty with permanent high at pin 6

- same effect as holding in the store button. Models 1H1 and 1H6.

(18) Slow to start and when running hum on vision causes flaring, Ipsalo-2 sets. CB712 and CB726 (both 4.7μ F) in chopper transistors' base circuits faulty.

(19) Twitching or varying width. EW amplitude control RTB503 ($10k\Omega$) noisy.

(20) When teletext is fitted with early production sets poor reception and data corruption may well occur. If so ensure that improved tuner/i.f. pair (types SK4743 and STD0063AM) have been fitted and that a 330 Ω resistor is connected between pin 1 of the tuner and chassis.

The following two faults relate to 1HC and 1HG sets. (21) Chroma displaced to right of luminance. Change RB291 and RB292 from $1k\Omega$ to 470Ω . After doing this, RTB203 may well have to be adjusted to remove Hanover blinds.

(22) Poor definition coupled with tendency for the tuning not to lock at the optimum point. Particularly with early versions of these sets this is sometimes due to incorrect adjustment of the a.f.c. coil LD6. One eighth to a quarter turn is usually enough.

The following four faults apply to Models 1H4 and 1H8.

(23) No sound or picture, noisy raster on screen. ICC1 (MC7805) on remote control panel faulty, causing loss of supply to the tuner prescaler circuit.

(24) Only snow on screen. Faulty prescaler circuit inside tuner.

(25) No on-screen channel number display. ICC101 (SAA1075) on remote control panel faulty.

(26) Set comes on at number 17 instead of number 1 and cannot be switched back to numbers 1-16. TS1 (BC307) on front panel short-circuit.

TV LINE OUTPUT TRANSFORMERS PRICES INCLUDE VAT & CARRIAGE

VIDEO HEADS, TRANSISTORS, IC's, ALSO STOCKED.

BAIRD: 8290, 8752, 8773, 8180	12.00	ITT: VC200 to VC402 CVC1, CVC2 (FORGESTONE) CVC5, CVC7, CVC8, CVC9, CVC20 CVC25, CVC30, CVC32, CVC45	9.20
A774 with stick rectifier A816, T16, T18, Z712, Z715 T20, T22, T26, Z179, A823	9.78 10.35 11.50	CVC800, 1100, 1150, CVC40 CVC1200, 1204, 1210, 1215, 2600 PYE: 169, 173, 569, 368	P.O.A. P.O.A. 9.20
DECCA: 1210, 1211, 1511 1700, 2001, 2020, 2401, 2404	11.50 9.20	CT200, CŤ200/1, CŤ213 725-731, 735, 737, 741	10.35 9.78
CS1730, 1733, 1733, 1830, 1835 30, 70, 80, 90, 100 120, 130, 140, 160	9.20 9.20 9.20 P.O.A.	PHILIPS: 170, 210, 300 320 series 320 series TX, T8, TX2, TX3 mono 38 and G9 Series KT2, KT3, series 58 and G9 Series	9.20 9.78 P.O.A 9.20 9.20
FERGUSON, THORN: 1590, 1591 1690, 1691. built in rect	9.20 9.78	CTX G11. K30. K4. K40. split diode K12, CF1, 2A, 2B, 3A, NC3	P.O.A. P.O.A.
1600, 1615, 1700, 1790 3000, 3500, 8000, 8500, 8800 9000, 9200, 9300 series 9500, 9600, 9650 series TX9, TX10,TX90, TX100, TXP5 MOVIESTAR 3781, 3787, 8180 TX10 focus unit	P.O.A. P.O.A. 12.00 12.00 P.O.A. 12.00 10.87	REDIFUSION Mk1 to 5 DORIC Mk3, Mk1 SONY KV 1400, 1612, 2000 GRUNDIG, G.E.C. NORDMENDE: 8290, 8180, Z306 SANYO: 5101, 5103, 7118, 7130 SHARP: C1851H, C2051H, 1405 HINARI: C14, C15 TANDBURG: 190, CTV2, CTV3	P.O.A. 11.50 P.O.A. P.O.A. P.O.A. P.O.A. P.O.A. P.O.A. P.O.A.
FIDELITY: FTV12 mono ZX2000 ZX3000 14", 16", 20" ZX3000 22"	10.35 16.43 27.28	TELEFUNKEN: most models in s HITACHI: 1471, CPB260, 2501 SAISHO MATSUI SENTRA Delivery by return of post	P.O.A. P.O.A.
CASED AUTO TRANSFORMERS 240V to 115V USA 2 PIN SOCKE Size 1000 watt 500 watt 300 watt	T Price 48.30 28.75 25.30	Tidman Mail Order L 236 Sandycombe Roa Richmond, Surrey TW9 Approx. 1 mile from Kew Bri Phone: 01-948 3702 Mon-Fri 9 am to 12:30 pm	td., ad, 2EQ. ^{dge.}
TOROIDAL TRANSFORMERS W	OUND	Sat 10 am to 12 noon.	

U.H.F. TELEVISION DISTRIBUTION AMPLIFIERS T.S. 2008 8-Way U.H.F. Distribution Amplifier 000 Price 110(1) £19.95 each + Carriage & VAT (Total £24.68) 10 +£17.22 + Carriage & VAT 20+ £15.84 + Carriage & VAT Frequency: 470 - 860 MHz Specification: Minimum Gain per outlet: 2dB Mains: 240V A.C. T.S. 2004 4-Way U.H.F. Distribution Amplifier Price £14.95 each + Carriage & VAT (Total £18.93) 10+ £13.23 + Carriage & VAT 20+ £12.17 + Carriage & VAT Frequency: 470 - 860 MHz Specification: 00 Minimum Gain per outlet: 2dB Mains: 240V A.C. TAYLOR BROS. (OLDHAM) LIMITED Telephone: 061-652 3221 Bisley Street Works, Lee Street, Fax: 061-626 1736 VISA

Oldham, Lancs., England. OL8 1EE

669911 Taylor G

Telex

Long-distance Television

Roger Bunney

The general view amongst DX-TV enthusiasts seems to be that the present Sporadic E season has not been a particularly good one. I tend to agree. There were openings throughout the month and the log (below) suggests that July was very active. Those who could spend much of the day with the receivers switched on were able to log many signals, but those who had to rely on random on/off operation missed many of the small openings. During a good year random viewing will catch many more signals. Over the years I've noticed that SpE tends to be less fruitful during periods of high sunspot activity. As the peak of cycle 22 approaches this winter, so we have once again experienced reduced SpE reception. Any comments on this?

The SpE log for July in the UK follows. It was compiled a little earlier than usual because of August holidays.

- 5/7/89 TVE (Spain) ch. E2; DR (Denmark) E3, 4; CST (Czechoslovakia) R2.
- 6/7/89 TVE E2, 3, 4; TVE-2 E2; RTP (Portugal) E3; RAI (Italy) IA, B; TDF C+ (France, Canal Plus) L2, 3; JRT (Yugoslavia) E3, 4; CST R1; MTV (Hungary) R1; TVR (Rumania) R1, 2, 3; TVP (Poland) R1, 2; TSS (USSR) R1, 2.
- 7/7/89 TVE E2, 4; RAI IA; TSS R1, 2; NRK (Norway) E2.
- 8/7/89 TVE E2, 3, 4; RAI IA; NRK E2, 3, 4; SVT (Sweden) E2, 3.
- 9/7/89 TVE E2; RAI IA; JRT E3; +PTT (Switzerland) E2, 3.
- 10/7/89 TVE E2, 3, 4; RAI IA, B; C+ L2; ZTV Gwelo E2 (Zimbabwe via TE).
- 11/7/89 SVT E2; TVE E2, 3, 4; RAI IA.
- 12/7/89 TVE E2, 3, 4; C+ L2; RAI IA, B.
- 13/7/89 EPT (Greece) E3; JRT E3, 4; RAI IA, B; Ekalano (Italian private) E2; TVE E2, 3, 4; TVE-2 E2; C+ L2, 3, 4; MTV R1, 2; TVR R4, 5; ORF (Austria) E2a, E4; +PTT E2; RTP E2; TSS R1, 2.
- 14/7/89 TVE E2, 3, 4; RTP E2, 3; RAI 1A; JRT E3; SVT E2, 3; YLE (Finland) E3; DR E3,4.
- 15/7/89 RAI IA, B; Ekalano E2; C+ L2; TVE E2, 3, 4; RTP E3; TVE-2 E2; RTBF (Belgium) E3 (short skip into Midlands); RTM (Morocco) E4, M4; Arabic signals noted on E3, E4 (likely JTV-Jordan E3, Syria E4).
- 16/7/89 TVE E2, 3, 4; TVE-2 E2.
- 17/7/89 TVE E2, 3, 4; RTP E2, 3; RAI IA.
- 18/7/89 TVE E2, 3, 4; RTP E2, 3; TVP R2.
- 19/7/89 TVE E2, 3, 4. 20/7/89 RAI IA, TVR R2.
- 21/7/89 RAI E2, IA, B; JRT E3, 4; RTSH (Albania) IC; EPT E3; TVR R2; MTV R1, 2; ORF E2a, E4; C+ L2, 3, 4; TVE E2, 3, 4; +PTT E2; TVP R1, 2, 3; ARD (West Germany) E2; NRK E2, 3, 4; TSS R1, 2, 3, 4, 5.
- 22/7/89 TVE E2, 3, 4; RAI IA, B; JRT E3, 4; C+ L2, 4; EPT E3; ORF E2a; MTV R1, 2, 3;RTSH IC; TVR R2, 3; + PTT E2, 3, 4; CST R1, 2; TVP R1, 2, 3; TVR R2, 3; ARD E2; SVT E2, 3, 4; NRK E2, 3, 4; TSS R1, 2, 3; YLE E4; Tele Uno (Italian private) E3.
- 23/7/89 TVE E2, 3, 4; RTP E3; RAI IA; C+ L2; TVE-2 E2; TVP R1, 2; RUV (Iceland) E3, 4.

- 25/7/89 TSS R1, 2; JRT E3; ARD E2; RAI IA, B; Ekalano E2; +PTT E2, 3; C+ L2, 4; RTP E3;TVE E2, 3, 4; ch.E2 Dubai or Iran – Arabic programming at 1205BST.
- 26/7/90 TVE E2, 3, 4; RTP E3.
- 27/7/89 TSS R1, 2; CST R1, 2; RAI IA, B; Ekalano E2; Radio Tele Uno IA; JRT E3, 4;TVE E2, 3, 4; TVE-2 E2; ORF E2a, E4; C+ L2; ARD Grunten E2; AFRTS A2 Iraklion, Crete.

28/7/89 C+ L2; RAI IA, B.

29/7/89 TVE E3.

I'll briefly highlight the more important reception noted in the above log. The AFRTS (American Forces) reception from Iraklion, Crete on the 27th was by Bill Cotterill (Tipton) who logged programmes from 1034 onwards on ch. A2/E3. This was a 525-line transmission of course: the vision locked with reduced height and adjustment of the field hold control enabled the picture to be held steady without rolling. Bill noted Arabic signals in ch. E4 on the 21st, from 1430-1500, and on the 15th in chs. E3/4. Also on the 15th Simon Hamer (Powys) received Moroccan signals at 1925 BST in chs. E4 and M4 (the latter Band III). On the 10th Cyril Willis (King's Lynn) noted a rugby match at 1800 BST from Gwelo (ch. E2) Zimbabwe. This was via transequatorial skip.

Tropospheric Conditions

There was improved tropospheric reception on several days – the weather in the UK was mainly hot, sunny and settled during the month, producing a general enhancement on all Band III/u.h.f. channels. The first period around the 5-6th produced signals from Denmark, Norway and the Benelux countries. Simon Hamer was very active – he motors to a site on a nearby mountain, giving him a clear take-off to the horizon! Simon logged Danish signals in chs. E5, 6, 7, 8, 10 with TV2 signals in chs. E22, 26, 30, 35, 40, 53 and 56. In addition ARD (W. Germany) was present on several channels.

A second period with enhanced signals occurred on the 17-20th. The 17th was better towards the west, with RTE-1/2 signals throughout Band III/u.h.f. A peak on the 20th extended reception into the Midlands, again with signals from France, Denmark, E/W. Germany and the Benelux countries. As a result of ducting, the E. German signals were stronger than those from W. Germany. A further improvement came on the 23rd.

Matters Arising

Some points arising. Dalibor Frkovich (Yugoslavia) reports reception of the Egyptian low-power (900W) ch. E2/4 transmitters at Dumyat, also a signal on ch. E3. There used to be a ch. E3 transmitter at Port Said: could this have reopened? A mystery Belgian signal has been received on ch. E58, a PM5544 pattern with the identification "Andurlues, channel 58" but no BRT or RTBF. Could this be a new Canal Plus venture?

Tim Anderson (2 Burry Road, St. Leonards on Sea, East Sussex TN37 6QX) has for sale a 22in. Finlux receiver with stereo sound and SECAM/PAL/NTSC colour capability – in fact all standards except System D sound. Coverage includes chs. IC and R3/4/5. The set has a scart socket, remote control, etc. Asking price is £425 or near offer. To be collected/inspected, contact Tim directly.

My thanks to the following for sending in reception

936

^{24/7/89} TSS R1, 2.

reports: Cyril Willis (King's Lynn), Roger Fussell (Torpoint), Simon Hamer (Powys), Brian Renforth (Newcastle), Peter Schubert (Rainham), Bill Cotterill (Tipton), Tim Anderson (St. Leonards) and Iain Menzies (Aberdeen).

News Items

UK: Nicam stereo sound transmissions are to start this September in the London and Yorkshire ITV areas. During 1991 coverage should extend to 75 per cent of the country. The BBC's transmissions will include Nicam stereo sound over 70 per cent of the country by mid-1992. **France:** A new European pop video service called MCM (Monte-Carlo Musique) is to be broadcast by Tele Monte Carlo for 18 hours daily. It will replace the French M6 programme currently being relayed. RCL-TV has requested channel allocations in thirteen French cities for a non-stop news service to be called "Infos Cites 8". The La Cinq network lost £84m in 1988.

Denmark: The TV2 network is to be financed entirely by advertising starting some time in 1990. Most regional stations want to opt out of the network and become independent. A new TV2 transmitter is in operation at Nakskov, using ch. E52 with 100kW e.r.p.

Hungary: The town of Siofok 110km south west of Budapest made history when Hungary's first commercial station TV-S started broadcasting.

Gibraltar: A new test pattern with the identification "TV Algeciras" has been seen at low power, in ch. E48 with horizontal polarisation.

Satellite TV

BSB's first satellite has been successfully launched into orbit. Three of the Astra 1A satellite's transponders switched off recently: it's not certain whether an electrical fault or solar storm was responsible for the automatic power close down. Sky's entertainment and news channels may adopt scrambling next year. Advertising limited to three minutes between films may be introduced on the Movie channel.

Ian Waller (Lincoln) reports that the West German Kopernikus (DFS) satellite at 23.5° E is at present transmitting on three channels as follows: ARD-1 Plus and RTL+ share an 11.65GHz transponder with horizontal polarisation; Pro-7 is at 12.558GHz horizontal; colour bars are on test using half the 11.575GHz transponder with vertical polarisation. There's a suggestion that the aerial for the Intelsat 63°E craft has been repositioned to cover W. Germany. Tests are being carried out at 10.95GHz.

The La5 and M6 services are to be transmitted via the TDF-1 satellite. Early plans are being formulated by France/W. Germany for two high-powered, 12-transponder satellites to be launched in the mid-Nineties.

On a personal note, during the summer my reception to the east has been limited to (just) $10^{\circ}E$ by trees in leaf. Matters should improve in the autumn! I understand that the ECS craft at $16^{\circ}E$ is very active with up to five downlinks on test.

Books

I've been sent a copy of the 1990 World Satellite Annual for review. It's a supplement to the World Satellite Almanac published in 1988 and is of much the same size. These are upmarket publications from the USA, covering



the international scene including Western and Eastern eraft, their technical characteristics, programme/communication operations, history, footprints etc. Having used the Almanac I can vouch that it's an invaluable work of reference: the 1990 Annual goes a step further in presenting the latest information. The Annual costs £31 inclusive and the Almanac £32 inclusive from Swift Satellite TV Services, 17 Pittsfield, Cricklade, Swindon, Wilts SN6 6AN. Despite the cost these books are well worthwhile for anyone seriously interested in satellite work.

The MFT Company Ltd. (164 Station Road, Lower Standon, Henlow, Beds SG16 6JH) has recently published the *Fixed Dish Installation Guide* by M. Turff. It's an A4 format publication and is packed with information presented in a way that's easy to understand. Good value at £3.50 inclusive – the book comes free if you purchase a complete TVRO package from the company!

New EBU Listings

The following "private" W. German transmitters are now listed: Aachen ch. E27 100W; Bremen E29 63kW; Salzgitter E30 95W; Regensburg E34/38 5kW; Dortmund E47 200W; Bremen E49 63kW. Salzgitter with vertical polarisation, all others horizontal.

Help Wanted

Ian Uden (21 Crosbie Road, Harborne, Birmingham B17 9BG) intends to use a v.h.f./u.h.f. Pye model 99 for DXing. The set has four switched v.h.f. positions labelled A-B, C, D-H2. Can anyone provide frequency details?

TV Fault Finding

Philips CP90 Chassis

A number of these sets are coming in for repair now. These two were typical. The first one had low h.t. with a noise coming from the power supply. The line output transformer had shorted turns. A dry-joint at the earth connection to the combined focus/first anode control module was the problem with the second set – the symptom was an intermittent full-white raster. **P.B.**

Bush Model BC6004

If you have one of these sets that's tripping, don't leave it for long in this condition if you can help it. If D687 (SKE4F1) is faulty the 122V supply can go high. The result of this is that C836 and C835 explode, spraying the set – and your hair – with foil and wadding. R835 ($3.9k\Omega$) flashes over to the TBA530 chip which also dies. Over the years I've had this state of affairs in the workshop on two occasions. In neither case did I cause the problem, but I had to clear up the mess both times! **P.B.**

Hitachi CPT2596 (G8Q Chassis)

When this set was switched on the h.t. would come up then trip out. We disconnected the outputs from the chopper transformer one by one but the fault persisted. Checks on IC901 revealed that some of the voltages were incorrect. In particular there was zero voltage at pin 2, which is the input to an error amplifier. There should be $2 \cdot 3V$ here, supplied by R917 and D908 which is fed from a feedback winding on the chopper transformer. This winding read open-circuit to chassis. The transformer's chassis connection is pin 3: there was a hairline crack at the solder connection pad here. A.D.

Toshiba 210T6B

This set was dead and appeared to trip when switched on. We disconnected the 112V supply to the line output stage but this made no difference – in fact the 112V supply was missing, but the standby and remote control supplies were present. Transistor Q803 is used to kill the oscillator section of the chopper chip IC801 for standby or for the electronic trip action. In standby it's driven by QR01 which is in turn driven by the optocoupler DR10. QR01 was leaky collector-to-emitter but replacing it made no difference. The basic cause of the trouble was that the optotransistor in DR10 was faulty. Replacing DR10 restored normal results.

Ferguson TX10 Chassis

This set defied all logical attempts at repair. It would intermittently go to standby or either the volume, colour or brightness would increase or decrease. All the usual things were tried, i.e. a check for dry-joints around the chopper/e.h.t. transformer, changing the focus control, checking for a poorly earthed c.r.t. Aquadag coating etc. The only effective cure was to unplug the infra-red preamplifier – the set then behaved itself. A replacement preamplifier was tried, but if anything this made matters worse. Someone suggested extra earthing to the pream-

Reports from Philip Blundell, Eng. Tech., Alfred Damp, Ray MacDonald, J.S. Ruwala, J.K. Potts, Steve Leatherbarrow and J.R. Armagh

plifier's screening can, but that didn't help either. Another thought was c.r.t. flashovers. A second set was backed on to the faulty one, but within minutes it was back in standby.

As we were staring defeat in the face, memories from the very back of the mind were recalling the ITT80 chassis that changed channels if the house had an overhead mains supply. The majority were cured by fitting a ferrite ring in the mains lead. So a ferrite ring was fitted in the wiring loom to the infra-red preamplifier assembly. After a few anxious hours while the set behaved itself we began to sigh with relief. We've had no further trouble. **A.D.**

Panasonic TC2204 (U1 Chassis)

We all need experience, but sometimes it can be a hinderance. This old set suffered from very intermittent line jitter, affecting only the top half of the picture. I've not dealt with many of these sets, but having had similar trouble with later Panasonic receivers due to capacitor problems in the power supply this is where I started. After wasting much time in this way the cause of the trouble turned out to be the rather obvious C510 $(100\mu F, 16V)$ which decouples the feed to the TDA2591 sync/line generator chip. These capacitors often show signs of strain, but this one was like new and read perfectly on my component tester. **R.M.**

Some Quickies

ITT CVC1175/Solarvox 20809: After five minutes the picture brightness went low, with lack of width and field foldover. C716 (10μ F, 350V) on the chopper module was leaky – it gets hot.

Sony KV2216U (YE2 chassis): For pincushion distortion replace Q802 (SG264A).

ITT CVC1120 chassis: With the dead set symptom check whether the line driver transistor's $1.2k\Omega$ feed resistor R744 is open-circuit. J.K.P.

Sony 21XRTU

The complaint with this set was field collapse. We found that R802 (1-2 Ω) was open-circuit. After replacing it we switched on. There was an e.h.t. arc from the line output transformer and R802 burnt out instantly. Another resistor was fitted and the line output transformer was replaced. This time there was an EW fault because D808 was short-circuit.

The arcing had also destroyed the chips on the teletext panel. So if you get one of these sets with a field fault make sure that the line output transformer is o.k. before you give an estimate -I understand that this is a stock fault. J.S.R.

Sony KV2704

The customer complained that the set would work for five-ten minutes and would then go to standby. When I switched it on I noticed that the width was excessive - in

fact there was an EW fault. As soon as I tapped the line panel the set went to standby. I suspected a dry-joint but decided to deal with the EW fault first. A check on the SG264A gate-controlled switch which drives the EW modulator diodes revealed that it was leaky. When it was replaced the set worked perfectly and no longer went into the standby mode.

During the same week I had a call from another customer who reported a similar fault on one of these sets. This time the SG264A GCS was o.k., the problem being due to one of the EW modulator diodes. I fitted a BYW96E and it worked very well. J.S.R.

Hitachi CPT2260/2660/Salora Ipsalo-2

These sets use the Salora Ipsalo-2 circuit. This one was dead. The fuse was intact and the supply at the collector of TB700 was present. We changed the two 4.7μ F chopper drive coupling capacitors CB712 and CB726, which are very often faulty in these sets, and checked whether the BR100 start-up diac DB725 was short-circuit. When the set was switched on the e.h.t. built up but the set started to trip. The h.t. supply across CB513 was correct at 142V but the 15V rail was at only 3.5V. Diode DB507 had gone high-resistance. When a replacement was fitted the set came to life. J.S.R.

Sanyo CTP7132 (80P Chassis)

For a dead set with 320V present at the collector of the choper transistor Q304 first check its $470k\Omega$ base bias resistor R302. If this is o.k., check or better replace the 10μ F drive coupling capacitor C312. It's just below Q304's heatsink. J.S.R.

Ferguson TX100 Chassis

There was sound but no raster (black screen). The e.h.t. and first anode supplies were o.k. but the c.r.t.'s cathodes were at 200V. The outputs from the TDA3562A colour decoder chip were low at only about 1V, so the chip was as usual changed. No good. Perhaps the field timebase/ c.r.t. protection circuit had come into operation? A check revealed that there was no drive from the field output chip though its supply was present. So this chip was replaced, again as usual. Again no good! Then I found that there was no input from pin 1 of IC4. I followed the same routine: supply o.k. so fit new chip, but still no raster. As I was pressed for time I phoned our ever helpful Ferguson distributor. He said he hadn't had this one, but shouldn't I try the field feedback circuit? Well there are quite a few components here. I decided to follow the old principle of checking high-value resistors and low-value electrolytics first. My initial check on C101 hit the nail on the head (it's exact value depends on the type of tube).

Nowadays a lost raster is often caused by field collapse. It's a good idea to read and note the first anode voltage, then turn the first anode control hard up in case a tell-tale white line appears. In this particular case switching off and on again inside a second or so produced a clean, bright line which stayed on. J.R.A.

Toshiba 145R7B

There were no results with no output from the LED and the 5V supply was missing. Ra25 was found to be opencircuit, a replacement putting matters right. Don't try to make the chassis tracks correspond to the circuit diagram

TELEVISION OCTOBER 1989



however! There's an error on the diagram: Ra25 is not connected to the h.t. line as shown, in fact it obtains its supply from the bridge rectifier end of R801. I suggest amending the diagram in case this causes trouble. J.R.A.

Hitachi CPT1455

"Faulty on/off switch" it said on the label. It never is of course, but how do you explain this to the paying customer? The set was dead, as these usually are when they come in. The STR4211 chip in the power supply had failed. A replacement was fitted along with the precautionary bits (see Hitachi data and sheets) and the set was switched on.

The sound was poor, as if the loudspeaker was off centre with coil rubbing. It was also extremely weak. The 56Ω resistor that feeds the two output transistors was open-circuit and one of the transistors was short-circuit. Nothing unusual so far. The faulty items were replaced along with the 1N4148 diode. This produced clean sound, in a way, until the volume control was at about midsetting. At higher settings there was no increase in volume and back came the distortion. The driver transistor was o.k. and all the voltages were about right. In despair we hooked up the scope and fed a sinewave into the TDA4503 chip. At above the half-way setting of the volume control the output became distorted. A new chip cured the fault. It didn't cure the customer when he read his bill for "a switch". J.R.A.

Ferguson TX85 Chassis

These sets employ a rather unusual line driver stage with three transistors. Two dead sets recently had problems here. The first simply had a dry-joint on one of the 100Ω , 12V supply resistors. With the second set we had to replace all three transistors: two were short- and one was open-circuit. S.L.

Ferguson TX90 Chassis

This set produced no results though the h.t. and 12V supplies were both present and correct. A scope check on the line drive waveform came next and I was rewarded. It was missing at the secondary of the driver transformer but was present at the primary. A base-emitter short in the line output transistor perhaps? No, simply an open-circuit wire on the driver transformer where it joins the print connection. We were able to remove and repair the transformer. S.L.

15/80H 15/85R 17052 17053 17074 17089	2.72 25 3.28 25 5.61 25 5.61 25 9.30 25	EXAMPLE SC1678 1.99 SC1741 1.22 SC1810 1.77 SC1815 0.22 SC1826 0.65 SC1826 0.65 SC1829 2.22	2 AN2140 5 AN234 0 AN236 0 AN236 0 AN240P 7 AN241	2.40 BC 5.09 BC 3.33 BC 0.99 BC 1.71 BC	CES 2207 0.14 22128 0.25 22131 0.10 2214 0.10 2225 0.40 2237 0.10	BOX54B BDX62A BDX63A BDX83 BDY81 BF115	0.21 1.96 1.21 1.18 0.29	BU126 BU137 BU205 BU206 BU206 BU207 BU208	1.10 6.53 1.15 1.27 1.65	HA1196 HA13001 HA1306 HA13402 HA13342	7.43 1.73 2.26 7.87 2.65 4.02	MC1330P MC1350P MC1351P MC1352P MC1357P MC1358P	1.98 0.90 1.32 1.40 2.15 1.48	SAS560T SAS570T SAS570S SAS580 SAS5600	5.42 5.42 2.61 2.15 1.33	STR1096 STR4090 STR440 STR451 STR453	4.98 9.52 5.37 4.93 8.16	TBA970 TBA990 TCA270S TCA270SQ TCA290A	3.06 T 1.90 T 2.15 T 1.05 T 2.39 T	4440 DA4442 DA4500 DA4600-2 DA4610	326 4.15 4.75 2.10 6.88
17127 17376 1N4001 1N4002 1N4003 1N4004 1N4005 1N4005 1N4006 1N4007 1N4148	2.50 29 1.58 25 0.04 25 0.06 25 0.05 25 0.05 25 0.05 25 0.05 25 0.06 25 0.05 25 0.07 25 0.08 25 0.07 25	SC1875 4.54 SC1893 3.02 SC1906 0.91 SC1921 1.32 SC1923 0.33 SC1924 1.91 SC1929 2.22 SC1942 1.91 SC1959 0.23 SC1957 0.29 SC1957 1.93 SC1953 1.93	AN253 AN260 AN272 AN295 AN301 AN302 AN305 AN315 AN316	1.80 80 3.85 80 7.92 80 5.52 80 3.09 80 8.88 80 2.46 80 5.53 80	2238 0.10 2238 0.08 2238 0.25 2239 0.25 2251A 0.31 2234 0.50 1200 0.35 1201 0.23 1202 0.33 1203 0.30 1203 0.30 1203 0.30 1207A 0.06	BF117 BF118 BF121 BF123 BF123 BF123 BF127 BF153 BF154 BF154 BF156	0.06 0.07 0.25 0.13 0.13 0.29 0.59 0.59 0.59 0.25 0.25 0.25 0.23 0.18	BU208/02 BU208A BU208D BU209 BU226 BU326A BU406 BU406 BU400 BU407	1.12 1.88 1.12 1.43 1.93 2.45 0.99 1.49 1.53 0.82	HA13365 HA1366WR HA1367 HA1368 HA1368 HA1370 HA1370 HA1374 AA117 HA1377 HA1389R	1.38 2.75 2.45 2.07 3.71 1.80 9 1.75 2.05	MC14493P MC14494P MC14497 MC14510BAL MC14511BCP MC14528BCP MC1712 MC5192 MC7724CP	4.20 2.15 3.46 3.75 1.10 2.15 3.88 19.50 3.49	SAS660 SAS6700 SAS6710 SAS6710 SBA750 SC84203 SC9504P SDA2006 SDA2112/2 SG264A	1.33 1.33 2.21 1.61 19.35 1.95 10.28 5.25	STR454 STR6020 T6029V T6035V T6036 T6037 T6044V T6045 T6049	4.95 5.85 7.98 0.73 0.67 2.11 0.97 1.20 1.45	TCA420A TCA440 TCA530 TCA640 TCA650 TCA650 TCA730 TCA750 TCA8000 TCA830S	2.25 T 2.24 T 2.25 T 3.05 T 2.60 T 3.81 T 2.25 T 5.95 T 2.38 T	DA4620 DA5500 DA5700 DA7270S DA8190 DA9403 DA9403 DA9503 DA9513 DB1033 DE1081	6.73 7.45 2.75 2.25 3.96 1.50 2.92 3.15 2.68 7.05
1N4448 1N5401 1N5402 1N5403 1N5404 1N5408 1N914 1S1555 1S44	0.05 25 0.11 25 0.13 25 0.18 25 0.15 25 0.14 25 0.04 25 0.31 25 0.10 25	SC1962 1.92 SC1969 1.71 SC1983 3.21 SC1985 1.55 SC2009 0.34 SC2029 2.31 SC2028 2.11 SC2063 0.95 SC2078 3.38	AN320 AN321 AN321 AN322 AN337 AN340P AN355 AN362 AN370	5.47 80 2.25 60 6.78 80 1.53 80 5.98 80 1.50 80 3.95 80 3.43 80	C306A 0.11 C309 0.17 C317A 0.13 C327 0.33 C328 0.11 C337 0.09 C338 0.12 C368 0.18 C340 0.69	BF159 BF160 BF167 BF173 BF177 BF178 BF179 BF179 BF180 BF181	0.18 0.31 0.38 0.34 0.55 0.40 0.36 0.36 0.36 0.35	BU412 BU426A BU500 BU508A BU536 BU608 BU705 BU806 BU806 BU807 BU826A	5.29 1.67 1.45 1.89 1.65 1.65 2.50 0.85 1.40 1.95	HA1389 HA1392 HA1394 HA1394 HA1397 HA1398 HA1406 HA1452 HD14538 HD38702-A2 HD38750A53	2.39 1.36 2.37 3.76 2.95 2.07 0.85 2.07 7.95 5.77	MCR106-5/6 MCR220/7 ME0411 ME6002 ME6102 ME8001 ME0411 MJ2501 MJ3001 MJ3001	123 228 0.75 026 0.28 0.34 0.75 3.30 1.43 1.53	SG613 SG629 SG6533 SI1125H SI1630HD SKE263/04 SKE263/04 SKE471/06 SKE4F2/08 SKE4F2/06	8.75 8.27 10.31 7.50 20.50 1.39 0.85 0.35 1.07 0.80	T6052V T6058 T6059 T9003V T9005V T9011V T9013V T9014V T9016 T9019W	0.87 3.08 2.77 1.25 2.38 1.40 4.95 2.42 1.02 1.98	TCA890 TCA900 TCA910 TCA940 TCA940E TD3F800R TD3F900H TDA1001B TDA1003A TDA1005A	2.04 T 1.65 T 0.82 T 2.93 T 3.67 1 5.36 1 2.31 1 1.79 1	EA1002 EA1009 EA1014 EA1020SP IIC106C EC106M EIC44 EIC44 EIC45 EIC47 EIP120	2.30 0.90 1.50 4.93 0.61 0.77 0.72 0.56 0.77 1.55
1S921 2N2219A 2N3053 2N3054 2N3055 2N3442 2N3702 2N3702 2N3705 2N3706	0.37 29 0.35 29 0.99 29 0.79 29 1.16 29 0.14 29 0.18 29 0.16 25 0.14 29	SC2073 1.54 SC2085-0 1.65 SC2091 1.30 SC2161 2.44 SC2166 0.87 SC2216 0.68 SC2233 1.24 SC2236 1.85 SC2237 1.24 SC2236 1.85 SC2374 1.43	AN5132 AN5250 AN5610 AN5612 AN5613 AN5630 AN5630 AN5701N AN6250 AN6300	4.42 BC 4.40 BC 7.43 BC 2.07 BC 4.20 BC 3.95 BC 1.66 BC 2.95 BC 4.40 BC	2441 0.46 2454 0.36 2460 0.42 2461 0.47 2462 0.51 2463 0.30 2478 0.32 2479 0.41 2532 0.28 2546 0.17	BF182 BF183 BF184 BF185 BF194 BF195 BF195 BF196 BF197 BF198 BF199	0.34 0.39 0.43 0.39 0.14 0.17 0.16 0.17 0.15	BUW84 BUX84 BUX85 BY126 BY127 BY133 BY164 BY176 BY179 BY182	1.39 0.50 0.69 0.13 0.13 0.05 0.44 0.52 1.42 1.05	HD38750A-7 HD38800A50 HD44801A05 HISH1010 HISH1004 BISH1002 HM6231 HM6231 HM6232 HM6251 HM7103	7.25 14.09 12.50 8.59 6.00 9.50 9.01 10.95 5.25 4.85	MJE2955 MJE3055 MJE340 MJE320 ML231 ML232B ML237B ML238 ML238 ML923 ML926	1.89 1.25 0.49 0.99 3.01 2.51 5.77 3.10 3.58	SKE4F2/10 SKE4G2/02 SKE5F3/10 SK51/10 SL1310 SL1430T SL414 SL432A SL439 SL471	1.33 0.96 1.60 2.15 3.14 2.31 3.69 3.44 2.48 2.38	19034V 19035V 19051 19054V 19057V 19062V 19064 1A7027 1A7050 1A7051	1.45 1.40 7.14 5.46 2.77 0.49 3.90 4.80 1.74 1.74	TDA 1006A TDA 1010AF TDA 1011 TDA 1010 TDA 1010 TDA 1010 TDA 1028 TDA 1035S TDA 1035S TDA 1035T TDA 1037	4.25 2.40 1.02 1.51 2.45 2.42 2.95 2.55	FIP110 FIP112 FIP117 FIP126 FIP132 FIP132 FIP299 FIP2955 FIP29A	0.53 0.34 0.95 0.40 0.38 0.99 0.96 0.84 0.86 0.86
2N3707 2N3711 2N3771 2N3772 2N3773 2N3819 2N3823 2N3904 2N3908 2N3908 2N4301	0.11 29 2.04 29 1.55 29 2.20 29 0.40 29 1.17 29 0.15 29 0.15 29 0.62 29	SC2335+Kit 7.00 SC2551 125 SC2565 3.14 SC2570 0.00 SC2577 1.60 SC2578 6.75 SC2571 0.91 SC2671 0.91 SC2671 0.91 SC268A 1.05 SC3153 6.50	AN6340 AN6341 AN6363 AN6531 AN6551 AN6552 AN6610 AN7111	6.46 BC 1.42 BC 16.00 BC 1.95 BC 0.50 BC 0.68 BC 1.65 BC 1.25 BC	2547 0.10 2548 0.10 2549 0.10 2550 0.10 2556 0.16 2557 0.10 2558 0.10 2559 0.10 2559 0.10 2559 0.10 2559 0.10 2560C 0.14 2635 0.34	BF200 BF218 BF224 BF237 BF240 BF241 BF245 BF2458 BF2458 BF246A BF255	0.37 0.35 0.17 0.65 0.19 0.17 0.59 0.49 2.52 0.20	BY187 BY189 BY198 BY207 BY208 BY210-400 BY210-600 BY210-600 BY223 BY224-600	0.77 1.76 1.62 0.22 1.11 0.18 0.27 0.19 1.43 1.88	HM9032 HM9012 HM9015 HT4207 HT4208 KA2101 KC581C KC582C L200CV LA1201	4.00 3.22 3.24 13.25 20.65 1.00 7.68 4.85 1.69 0.75	MM5314N MM5316N MM538N MM5369N MM5387AA/N MM5841N MN1400VL MN1405 MN1435VX MP1192	8.99 9.16 3.11 2.01 6.20 6.64 13.65 7.92 9.50 5.07	SL480 SL490 SL901B SL918A SN16861AN0 SN16862AN SN16966N SN29717N SN29715N	3.14 2.37 9.07 0.82 2.98 10.25 7.19 3.66 6.04	TA7054 TA7060AP TA7061AP TA7069 TA7070P TA7072P TA7074P TA7076P TA7076P TA7089P TA7092P	2.55 0.71 1.27 3.13 1.83 2.57 1.98 7.50 3.10 9.94	TDA1037D TDA1044 TDA1047 TDA1059B TDA1059B TDA1054M TDA1060 TDA1082 TDA1151 TDA1190 TDA11907	2.05 1.95 3.25 1.21 1.21 2.60 3.25 1.22 2.11	11P298 11P29C 11P29D 11P3055 11P30A 11P30C 11P30C 11P31A 11P31B 11P31C 11P32A	0.63 0.40 0.75 0.66 0.41 0.40 0.34 0.34 0.30 0.30
2N4240 2N4444 2N5293 2N5294 2N5296 2N5297 2N5298 2N6109 2N6109 2N6130	2.00 25 0.90 25 0.50 25 0.50 25 0.61 25 0.61 25 0.61 25 0.61 25 0.65 25	3C373 1.16 SC383 1.33 SC384 1.27 SC394V 0.81 SC403C 0.66 SC403C 0.64 SC495 0.34 SC555 0.18 SC535 0.16	AN7145 AN7146 AN7151 AN7156 AN7158 AN7218 AN7223 AU107 AU10	9.90 BC 2.37 BC 2.85 BC 2.34 BC 0.80 BC 4.55 BT 5.87 BC 5.69 BC	D536 0.20 D537 0.24 D539 0.36 D540 0.24 D034 0.40 D115 0.36 D116 0.70 D124 1.31 D131 0.42	BF256 BF257 BF258 BF259 BF263 BF263 BF271 BF273 BF274 BF324	0.28 0.34 0.33 0.34 0.57 0.57 0.34 0.57 0.34 0.23 0.23	BY226 BY227 BY229-1000 BY229-600 BY229-600 BY229-600 BY295-600 BY298 BY299 BY407	0.25 0.20 0.60 1.12 0.92 0.13 1.03 0.20 0.60 0.90	LA1210 LA1230 LA1320 LA1357N LA1363 LA1364 LA1365J LA1365 LA1387 LA3850	1.56 1.44 2.87 9.00 1.05 3.02 1.15 1.53 5.95 1.43	MP2794 MP2812 MP8512 MPC596 MP5256C MPS6570 MPSA42 MPSA56 MPSA92 MPSA92 MPSU05	4.00 5.07 1.57 2.13 0.60 0.48 0.35 0.08 0.45 0.86	SN29722 SN29723AN SN29764AN SN29767 SN297708N SN297718N SN297718N SN29791 SN29798N SN2709	11.95 8.77 2.38 3.90 3.69 5.60 4.15 1.67 5.56 0.44	TA7033P TA7102P TA7108P TA7109 TA71228/P TA7124P TA7124P TA7129P TA7130P TA7136AP TA7137P	3.99 5.88 1.61 3.71 0.87 2.34 1.50 1.27 1.89 0.98	TDA1200 TDA1235 TDA1236 TDA1236 TDA1270 TDA1327A TDA1412 TDA1420 TDA1420 TDA1440 TDA1470	1.51 3.88 3.30 3.74 1.50 1.08 1.52 3.45 2.90	TIP328 TIP32C TIP33 TIP33A TIP33C TIP34 TIP41A TIP418 TIP41C	0.46 0.28 0.85 1.02 0.80 0.75 0.49 0.31 0.68
2N6180 2N6292 2SA1006 2SA1011 2SA1015 2SA1012 2SA1020Y 2SA1020Y 2SA10278 2SA473 2SA766S	0,73 29 1,65 29 1,50 29 1,65 29 1,65 29 0,49 29 1,25 29 0,80 2	50550 0 05 50537 0 55 50605L 1.16 50643A 1.54 506468 0.67 50668 0.67 50668 1.66 50682 1.88 50684 1.66 50693 0.63 50694 1.65	AY105K AY105 BA524 BA310 BA1310 BA1320 BA1322 BA1330 BA145	2.08 60 1.09 80 8.94 80 0.14 80 1.98 80 1.98 80 3.95 80 2.75 80 0.19 80	0133 0.53 D135 0.36 D136 0.36 D137 0.26 D138 0.28 D139 0.34 D140 0.32 D144 1.43 D150 0.75 D157 0.67	6F336 BF337 BF338 BF355 BF362 BF362 BF363 BF371 BF391 BF418 BF418	0.33 0.45 0.49 0.49 0.49 0.49 0.49 0.49 0.59 0.59 0.59 0.59 0.59 0.59 0.59 0.5	BY409 BY448 BY713 BYW56 BYX55-600 BYX71-600 BYX71-600 BYX71-350 BYY56 BZY93C30 C106D	1.49 1.35 0.65 0.14 0.23 0.85 0.62 1.20 \$.86	LA330 LA3361 LA3390 LA4032P LA4100 LA4101 LA4102 LA4112 LA4112 LA4125 LA4138 LA4140	1.45 1.60 5.52 2.35 1.25 1.30 0.75 0.56 2.25 4.98 0.70	MP SU10 MP SU56 MP SU56 MP SU50 MR 818 MR 854 MR 914 MS 958 16 RS MS M5840H MV S460-02 NE 542	1.56 0.60 1.33 0.50 1.20 17.35 13.95 0.34 2.65	SN7400N SN7401N SN7402N SN7404N SN7408N SN7410N SN74121 SN74121 SN7413N SN74141N	0.61 0.36 0.65 0.52 0.27 0.27 1.60 0.37 2.65	TA7137F TA7141AP TA7146P TA7146P TA7148P TA7152P TA7152P TA7152P TA7162P TA7172P TA7176P TA7176P TA7173P	0.586 3.87 4.23 1.67 3.26 2.72 4.50 3.61 1.41 1.75 4.80	TDA1470P TDA1506 TDA1510 TDA1512 TDA1515 TDA1559 TDA1559 TDA1670 TDA1770 TDA1906 TDA1906	6.58 4.60 2.89 3.15 4.48 2.75 1.27 2.98	TIP42A TIP42B TIP42C TIP47 TIS43 TIS90 TL011CP TL011CP TL494CN FL072CP TMP4320	0.50 0.79 0.82 0.65 1.43 0.21 1.56 8.95 1.45 15.00
2SC1173Y 2SC1474 2SC1509 2SA1095 2SA1095 2SA103 2SA329 2SA489 2SA490 2SA490 2SA493 2SA562	1.25 25 1.25 29 1.35 25 3.00 25 6.00 25 0.40 29 1.17 25 1.32 25 2.25 25	C711A 0.50 SC717 1.28 SC734 1.43 SC780 3.96 SC790Y 1.85 SC828 0.28 SC687A 3.04 SC8876 0.96 SC930 0.54	BA154 BA155 BA156 BA159 BA182 BA222 BA302 BA302 BA311 BA312	0.40 BC 0.12 BC 0.05 BC 0.09 BC 1.96 BC 1.96 BC 1.24 BC 0.65 BC 1.45 BC	D160 1.60 D163 0.71 D166 0.42 D175 0.20 D179 0.30 D181 0.99 D182 0.99 D183 0.99 D184 1.21	BF418 BF422 BF423 BF450 BF450 BF457 BF459 BF459 BF460 BF469 BF469 BF470	0.33 0.35 0.40 0.40 0.40 0.40 0.40 0.40 0.40 0.4	C106M CA3046 CA3089 CA3090AQ CA3094 CA3094 CA3094 CA3131EM CD4001 CD4002 CD4008	0.37 0.76 1.55 0.83 3.25 2.20 2.95 0.34 0.27 1.35	LA4192 LA4220 LA4220 LA4420 LA4422 LA4430 LA4440 LA4460 LA4460 LA4461	1.50 1.25 1.72 1.00 1.29 1.95 1.90 1.75 1.70	NE555 NE556 NP1106 DA202 DA47 DA91 OA95 OC28 DC29	0.19 0.65 11.51 0.11 0.16 0.14 0.09 2.52 2.15	SN74151AN SN74154N SN74190 SN7420N SN7430 SN7430 SN7430 SN7472 SN7474N SN7474N SN7490AN SN741S26N	1.51 1.27 1.35 0.34 0.49 0.27 1.54 0.44 0.93 1.45	TA7204P TA7206P TA7207P TA7207P TA7208P TA7210P TA7214P TA7215P TA7217AP TA7222	2.16 12.49 1.48 2.15 1.45 3.63 2.58 1.45 1.95	TDA1940 TDA1950 TDA2005 TDA2006 TDA2006 TDA2004 TDA2002 TDA2003 TDA2030 TDA2030 TDA2140 TDA2150	2.50 1.45 1.55 1.48 0.90 1.00 1.35 2.14 6.20	TMS1024NIL TMS1025N TMS3720ANS TMS3755 TMS3894NL TMS5102NLL TUA2000 TY6010B ULN2204	14.95 13.65 19.25 6.25 8.98 2.97 8.50
2SA564 2SA614 2SA628 2SA639S 2SA659 2SA673 2SA684 2SA697 2SA699	0.652 25 4.88 25 0.37 25 1.75 25 0.49 25 1.50 25 1.20 25 0.80 25 1.25 25	CG355 4.13 CG340 4.68 SD1128 2.96 SD1128 2.96 SD1128 0.94 SD1128 0.94 SD11273 1.30 SD152K 2.66 SD152K 2.64 SD159B 3.83 SD234 0.47 SD235 0.66	BA317 BA318 BA328 BA333 BA335 BA5102A BA511 BA514 BA521	0.04 80 0.09 80 1.65 80 1.37 80 2.50 80 1.95 80 1.00 80 1.20 80	D189 0.69 D190 0.69 D201 0.49 D202 0.60 D203 0.46 D204 0.41 D207 1.79 D208 0.208 D209 1.23 D202 0.50	BF471 BF472 BF479 BF480 BF491 BF506 BF532 BF596 BF596 BF597	0.25 0.33 0.49 0.49 0.49 0.20 0.20 0.20 0.20	CD4011 CD4012 CD4013 CD4016 CD4017 CD4020 CD4020 CD4021 CD4023 CD4025 CD4028	0.29 0.24 0.33 0.36 0.40 1.23 0.39 0.28 0.54 0.64	LA5112N LA7020 LA7025 LA7027 LA7040 LA7040 LA7042 LA7800 LA7801 LB1274 LC7800	1.18 13.06 11.97 10.92 9.20 3.90 1.03 0.90 3.61 9.20	DC36 DC44 DC45 DC72 DC75 ON236 DN782 DT121 PT6042 PT8504	7.53 0.35 0.18 0.44 0.44 1.06 1.98 1.45 2.45 4.98	SN76001N SN76013ND SN76023ND SN76023ND SN76033N SN76110N SN76115AN SN76115AN SN76131 SN76227N SN76226DN	1.65 3.50 2.97 3.91 5.54 0.90 1.61 0.82 0.85 2.00	TA7226 TA7230P TA7230P TA7230P TA7240AP TA7245P TA7310P TA7310P TA7313AP TA7314 TA7323P	3.57 4.22 1.35 3.46 2.55 5.92 2.15 0.65 5.94 3.15	TDA2151 TDA2160 TDA2161 TDA2170 TDA2270 TDA2520 TDA2522 TDA2522 TDA2524 TDA2525 TDA2532	4.01 2.40 4.50 3.96 2.25 2.50 4.50 3.90 2.50	UPA53C UPC1003 UPC1009C UPC1025H UPC1028H UPC1032H UPC1042C UPC1165H UPC1161C UPC1182H	4.94 5.95 6.32 2.90 2.00 0.82 8.95 3.94 4.98 1.50
2SA715 2SA748 2SA817 2SA835 2SA836 2SA836 2SA844 2SA872 2SA884 2SA937R 2SA940	1.95 25 0.18 25 2.50 25 0.89 25 0.59 25 2.15 25 0.97 25 2.23 25	SD24 2.28 SD257 1.91 SD292 4.08 SD313 2.65 SD325D 2.26 SD350 3.05 SD353 7.56 SD401 1.40 SD401 1.40 SD414 1.98	BA526 BA527 BA532 BA536 BA536 BA536 BA556 BA7100 BA841A BA843	7.98 80 2.99 80 1.50 80 1.70 80 1.70 80 1.00 80 11.35 80 28.98 80 3.96 80	D225 0.46 D228 0.63 D229 1.05 D232 0.49 D233 0.42 D238 0.23 D239 0.45 D238 0.20 D239 0.45 D240 0.57 D241 0.39 D242 0.50	8F694 8F757 8F759 8F761 8F762 8F869 8F870 8F959 8F959 8F959 8F950 8F970	0.22 0.59 0.47 1.05 0.38 0.49 0.30 0.49 0.30 0.49 0.49 0.49	CD4040B CD4047 CD4049 CD4052 CD4066 CD4069 CD4070 CD4070 CD4081 CD4093 CD4093	0.60 1.06 0.24 0.54 0.29 0.25 0.14 0.40 1.10	LD3120 LD3150 LM1017N LM1877 LM2808 LM2877 LM317CKC LM324N LM329N LM339N LM340K	1.13 2.75 3.81 3.50 5.94 7.45 1.08 0.98 0.41 11.85	R1038 R1039 R2008B R2009 R2010B R2029 R2030 R2030 R2257 R2255 R2265 R22305	2.19 2.19 1.33 1.98 2.96 1.33 1.33 2.35 1.49 1.18	SN 76228N SN 76242 SN 76243 SN 76396 SN 76533N SN 76532N SN 76545 SN 76546N SN 76546 SN 76549 SN 76570	3.27 5.23 5.23 2.90 2.47 0.91 4.87 3.47 2.45 3.08	TA7325P TA7339P TA7340P TA7607AP TA7609 TA7611AP TA7616P TA7622AP TA7622P TA7629P	1.15 1.85 5.95 2.10 2.65 2.32 5.25 8.94 2.50 7.50	TDA2530 TDA2541 TDA2540 TDA2540 TDA25450 TDA2575A TDA2575A TDA2576A+1 TDA2581 TDA2581	1.88 2.15 5.94 2.17 0.50 2.73 Kit 12.35 1.60	UPC1186H UPC1185H UPC1185H UPC1188 UPC1212C UPC1225H UPC1230 UPC1238 UPC1238 UPC1278H UPC1351C	1.05 2.10 8.77 0.80 4.83 1.48 2.10 5.95 1.81
2SA940-2 2SA950 2SA951 2SA966 Y 2SA999 2SB774 2SB185 2SB375 2SB400 2SB405	0.72 25 1.75 25 0.85 25 0.75 25 0.65 25 1.13 25 3.87 25 0.40 25 1.03 25	SD471 2.13 SD560 2.95 SD600 2.91 SD611 0.65 SD635 0.40 SD636 0.40 SD655 0.35 SD655 2.065 SD657 2.00 SD651A 0.95	BAV18 BAV19 BAV20 BAV21 BAV21 BAV62 BAX12 BAX13 BAX16 BC107B	0.06 Br 0.11 BC 0.35 BC 0.12 BC 0.11 BC 0.11 BC 0.11 BC 0.11 BC 0.08 BC 0.01 BC	D243A 0.37 D243C 0.50 D244C 0.31 D244C 0.72 D245C 0.70 D246C 0.80 D253 1.05 D278A 0.70 D317 1.20 D318 2.72 D375 0.42	BFR39 BFR61 BFR62 BFR79 BFR81 BFR86 BFR89 BFR89 BFR80A BFR29 BFR84	0.41 0.52 0.23 0.25 1.08 1.63 0.85 0.37	CD4528 CD4556 CR02AM-8 CV12E CX095D CX104 CX108 CX109 CX109 CX130 CX130	2.04 1.47 1.70 3.14 8.77 12.48 7.86 8.75 11.10	LM348N LM380N LM567CN LM6402/011 LM6402A093 LM748 LM8360 LM8361 LR3419 LR3471	2.15 2.80 1.71 10.23 10.15 0.69 3.87 3.57 9.37 9.37	R2322 R2323 R2354A R2354B R2443 R2461 R2540 R2540 R2540X R2515 R2540X R2515	0.67 0.76 0.64 2.01 1.36 1.50 1.91 3.30 0.67 2.00	SN 76611 SN 76620 SN 76660N SN 76666N SN 76708 SN 76709N SN 76707N SN 76705N SN 76705N SN 76730 SN 76810N	2.59 2.59 2.48 1.41 4.86 5.94 1.23 6.60 5.54 0.60	TA7630P TA7640AP TA7676P TA7676P TA7726P TA7726P TAA320A TAA350A TAA570 TAA621AX1 TAA661B	0.95 2.40 2.55 2.81 10.25 1.27 0.90 1.85 4.85 1.00	TDA2591 TDA2594 TDA2593 TDA2595 TDA2600 TDA2611A0 TDA26120 TDA2611A TDA2610 TDA2620	3.40 3.40 5.52 7.60 1.25 4.68 1.25 2.79	UPC1350C UPC1353 UPC1355C UPC1365 UPC1365 UPC1365C UPC1366 UPC1360C UPC1378H UPC141C	1.40 1.58 2.13 4.20 4.10 2.50 1.65 4.51 2.44 4.95
2SB511 2SB54 2SB54 2SB56 2SB618A 2SB631 2SB643 2SB669 2SB681 2SB695	1.39 29 0.56 29 2.00 29 2.00 29 2.00 29 0.50 29 3.67 29 3.96 29	SD 731 2.11 SD 731 0.80 SD811 7.63 SD823 1.88 SD837 1.48 SD841 2.00 SD856 1.00 SD8570 1.88 SD8571 1.93 SD852 1.15 SD882 1.15 SD884 1.75	BC109B BC113 BC119 BC126 BC132 BC135 BC135 BC137 BC138	0.14 BC 0.14 BC 0.36 BC 0.20 BC 0.14 BC 0.14 BC 0.18 BC 0.18 BC 0.34 BC	0.380 0.76 0.410 0.49 0.433 0.44 0.434 0.45 0.435 0.48 0.436 0.60 0.437 0.41 0.438 0.52 0.441 0.59 0.442 0.66 0.509 1.42	BFX85 BFX86 BFX87 BFX88 BFX50 BFY50 BFY51 BFY52 BFY79 BFY90 BLY49	0.41 0.35 0.55 0.38 0.45 0.30 0.30 0.33 0.27 0.40 0.42 0.42 0.42	CX136 CX139 CX157 CX158 CX177 CX187 CX755 CX885A E1222 E5024	11 49 11.83 5.52 5.50 8.75 5.26 12.95 6.85 0.40 8.28	LU1141 LU52012 LU52011 LU03112 M193 M21C M293 M51102L M5115P	7.27 5.95 14.95 12.37 6.83 1.30 1.98 6.71 1.69 5.24	RGP01-15 RGP10 RGP30M RT402 RT905A S1299 S2800D S2802 S2802 S2818 S3702S S40W	0.70 0.30 1.58 2.30 5.34 1.84 2.90 4.05 5.21 13.10	SN 76832N SN 94041 SN 94042 SP 55384 ST 1702L ST A401 ST A401 ST A441C ST A471C ST K0029 ST K0050	1.35 5.54 4.35 1.98 0.99 2.50 3.10 7.95 5.54 7.72	TAA691 TAA700 TAA970 TAG26-600 TBA120AS TBA120SB TBA120T TBA120U TBA120A	8.58 2.37 4.87 2.83 1.20 0.70 1.05 0.97 2.50 1.05	TDA2630 TDA2631 TDA2640 TDA2652 TDA2653 TDA2654 TDA2670 TDA2680 TDA2680 TDA2740 TDA2780AQ	2,50 2,73 3,61 8,25 6,18 4,73 2,48 3,20 6,00	UPC1458 UPC151C UPC2002 UPC30C UPC32C UPC32C UPC339C UPC47C UPC4558C UPC474	2.00 2.95 1.48 2.51 4.70 4.95 4.35 4.10 2.15
2SB774 2SB819 2SC1096 2SC1104 2SC1106 2SC1114 2SC1116 2SC1124 2SC1129 2SC1131 2SC1158	0.65 29 1.13 29 1.16 78 3.99 78 4.54 78 3.25 78 4.95 78 1.26 79 1.65 A(0.64 A(SDS38 D.42 SK105H 2.15 S05-0022 0.63 S08 0.42 S12-T022 0.36 S15 0.64 S05 0.80 D140 1.06 D143 1.05 D145 1.60	8C140 8C141 8C142 8C143 8C143 8C1480 8C1480 8C1480 8C1498 8C153	0.45 80 0.34 80 0.23 80 0.34 80 0.11 80 0.13 80 0.13 80 0.11 80 0.13 80 0.13 80 0.14 80	D510 0.75 D519 0.88 D529 0.60 D530 0.80 D533 0.67 D534 0.52 D535 0.46 D536 0.50 D536 0.50 D537 0.50 D538 0.50 D537 0.50	BR100 BR101 BR103 BR303 BRC84 BRX49 BRX49 BRX49 BRX39 BST8D140G BSTC0246	0.22 0.75 0.66 1.15 2.04 0.60 0.34 0.60 0.57 4.98 8.64	ES386 GD243 GF758 HA11215 HA11215 HA11225 HA11225 HA11229 HA11235 HA1125 HA1125 HA1125	0.25 4.34 0.84 1.75 2.53 4.29 3.46 1.75 5.25 4.79	M51203L M51203L M51231P M5134-9341 M51353P M51393AP M51393AP M51393AP M51394P M5142P M5142P M5143L	3.15 3.07 4.13 5.25 5.98 9.48 12.50 6.85 3.77 2.55	SA000 SA008 SA41006 SAA1020 SAA1020 SAA1025 SAA1024 SAA1025 SAA1024 SAA1121 SAA1124 SAA1130 SAA1130	9.98 5.17 1.85 4.76 4.40 2.81 4.25 7.44 2.45 4.99 7.77	STK016 STK022 STK031 STK040 STK054 STK058 STK077 STK1039 STK2110 STK2110	6.91 5.25 12.95 13.34 3.95 27.50 7.67 5.75 7.33 16.95	TBA1440 TBA1441 TBA395 TBA396 TBA400 TBA440C TBA440C TBA4800 TBA510 TBA520 TBA530	1.03 1.94 1.95 1.10 1.20 2.39 2.34 1.30 1.37 1.84 1.30	TDA2795 TDA2791 TDA2910 TDA3300B TDA3300 TDA3506 TDA3500 TDA3500 TDA3500	2.78 1.81 13.25 6.98 2.88 4.40 12.09 4.25 5.95	UPC554C UPC575C2 UPC580C UPC587C2 UPC592H UPC595 UPC596 UPC596 UPO1514C UPO2819C UPD553-164	5.11 1.85 2.40 6.60 1.34 2.15 2.95 1.98 4.76 4.90 19.52 11.50
2SC1162 2SC1172 2SC1213 2SC1226 2SC1226 2SC1293 2SC1306 2SC1317 2SC1364 2SC1383	0.55 AL 2.22 AL 6.09 AL 0.89 AL 1.46 AL 1.90 AL 1.90 AL 0.50 AL 0.50 AL 0.49 AL 0.49 AL	D161 0.30 D162 0.45 F114 2.47 F115 1.24 F118 1.20 F127 0.65 F139 0.40 F178 1.46 F178 1.45 F179 0.55	BC159 BC160 BC161 BC158 BC169C BC170 BC171 BC172B BC173 BC174B	0.16 80 0.40 80 0.28 81 0.36 80 0.16 80 0.16 80 0.11 80 0.17 80 0.27 81 0.27 81	D677 0.40 D679 0.57 D680 0.52 D681 1.48 D696 2.47 D699 1.85 D700 3.70 D707 0.60 D709 0.50 D710 0.80	BSTC0233 BSTC0143 BST01043 BSV578 BSW68 BSX19 BSX20 BSY52 BSY52 BSY79 BT108	6.12 3.07 2.85 3.94 0.60 0.34 0.19 0.50 0.51 1.45	HA1138 HA11414 HA1156 HA1160 HA1166X HA1167 HA11706 HA11705 HA11703 HA11701	1 38 5 03 5 65 1.16 4.79 6.60 6.45 3.61 8.00 4.22 4.56	M51515BL M51517L M5192 M5194AP M5231L M53274P M54532P M54544L M58478P	2.75 2.90 2.20 5.74 4.80 1.33 1.50 1.22 6.75	SAA 1250 SAA 1251 SAA 1251 SAA 3027P SAA 5000 SAA 5010 SAA 5012 SAA 5020 SAA 5020 SAA 5020	3.95 3.20 8.11 2.55 3.25 4.40 5.50 5.78 6.33 7.74	STK2240 STK2250 STK3042 STK3044 STK4019 STK403 STK4032 STK405 STK4055 STK4055 STK4055	16,65 18,95 4,95 4,50 4,78 4,78 4,78 4,78 4,95 1,95 7,21	TBA540 TBA560C TBA5700 TBA570A TBA570A TBA770 TBA720 TBA720 TBA730 TBA7500	1.15 1.40 1.60 1.71 2.45 1.85 2.30 3.55 2.90	TDA3510 TDA3520 TDA3540 TDA3541 TDA3560 TDA3576 TDA3576 TDA3590 TDA3591 TDA3650 TDA3650 TDA3652 TDA3651A0	9.71 6.99 2.22 4.25 2.83 7.48 6.79 6.45 5.90 2.60 3.95	UPD8049C-1 X0022CE X0029CE X0031CE X0035TA X0040TA X0040TA X0040CE X0040CE X005CE X0055CE X0055CE	11.50 5.75 7.09 6.32 6.18 4.50 4.35 6.25 6.25 6.00 5.77
2SC1391 2SC1398 2SC1413A 2SC1446 2SC1447 2SC1447 2SC1505 2SC1505 2SC1514 2SC15730 2SC1583 2SC1617	0.75 AF 5.00 AF 1.25 AF 2.07 AF 0.60 A1 1.00 AF 1.37 AF 1.63 AJ 0.34 AF 3.89 AF	F180 0.55 F181 0.53 F186 0.53 F239 0.53 F279 0.88 N115 3.91 N155 1.88 N206 2.51 N208 3.55 N210 2.211 N211 3.251	BC176 BC179 BC182 BC182LB BC183LB BC183LB BC184 BC184 BC186 BC186 BC187 BC204	0.26 B 0.26 B 0.09 B 0.14 B 0.25 B 0.13 B 0.25 B 0.	DB09 DB00 DB10 0.69 DB79 0.74 DB95 2.18 DS01 0.99 D902 0.65 DW83C 0.99 DW84C 0.99 DX53A 1.88 DX53B 3.35	BT119 BT120 BT121 BT123 BT151-800R BT16018 BU106 BU106 BU109 BU110 BU110 BU125	1.75 2.17 2.48 1.98 1.00 2.42 2.48 1.50 2.25 5.69 2.48	HA11710 HA11713 HA11711 HA11715 HA11715 HA11716 HA11725 HA11725MP HA117555P HA117555P HA11781 HA1180	3.45 2.90 2.00 9.90 7.76 13.10 18.26 16.00 6.23 21.15 5.15	M58485P MA8001 MA8003 MB3705 MB3712 MB3730 MC13002 MC13002 MC1327P	12.75 1.07 0.82 1.16 1.98 1.85 1.69 2.09 3.90 2.25 1.33	SAB 1009B SAB3011 SAB3013 SAB3021 SAB3024 SAB3209 SAB3210 SAF1032P SAF1039 SAF1039 SAS5010 SAS500S	5.98 7.34 2.47 7.90 6.35 5.82 3.10 3.58 1.95 8.39 1.86	STK437 STK4372 STK460 STK466 STK4803 STK501 STK502 STK502 STK5314 STK5730 STK7216 STK72	7.50 13.13 7.02 11.77 9.52 6.32 7.25 12.40 3.20 13.10 3.71	TBA760 TBA800 TBA8105 TBA8105 TBA810T TBA820 TBA820 TBA890 TBA920 TBA940 TBA940 TBA950	1.71 1.08 1.61 1.75 0.66 0.82 3.30 1.65 1.87 1.55	TDA3650 TDA3651AQ TDA3651AQ TDA3651A TDA3651A TDA3651A TDA3651A TDA4050B TDA4050B TDA4050B TDA4290 TDA4420 TDA4420 TDA4422 TDA4427S TDA4421	1.95 2.50 4.50 3.40 7.20 1.95 4.90 2.30 8.32 9.00 2.27	X0074GE X0079GE X0079CE X0099CE X0096CE X0109CE X0109CE X0113CE X0195CE X0195CE X0204CE X0204CE X0206 CE ZPY120	5,75 7,09 6,328 6,500 4,305 6,275 6,275 6,275 6,275 10,000 15,965 4,965 5,955 11,257 7,508 4,965 5,955 11,257 7,509 4,968 3,255 4,968 4,969 4,975 4,99

	VID	ACCESS (E	ADS	*	FRO	£ mo	1	3.9) 5 ₌	ACH
		- PLUS + P	UUS VHS A	NATIONAL PANAS Head Part Nos.: VEHO Machine Nos.: NV300	CONIC 099 0103 0115 0 NV322 NV332 NV	121 0131 333 NV340 NV	390 NV2000		HEADS Head Part No.	UNIS	Prie 1 +
Machine Nos	.: VCR4500 VCR5200 VC	R9000	VHST VHSR	NV3000 NV7000 NV NV8200 NV8400 NV86 Head Part Nos.: VEH0 Machine No.: NV370 N	00 NV8610 NV86 171 VEH0218 IV3708		50 NV8170	VHSB VHSM	BETA A BETA B BETA D BETA E BETA T		£16.9 £16.9 £27.9 £34.4 £21.0
VCR4600 FERGUSOI Machine Nos	N/JVC : 3292 8903 3V00 3V01	3V06 3V16 3V22 3V23 3V24	9VH4600	Head Part Nos.: VEHO Machine No.: NV330 N Head Part Nos.: VEHO Machine No.: NV430	W7 77			VHS N VHS W	BETA W BETA X VHS VIDI	EO	E19.9 E31.9
3v29 3v30 3 Fisher	V31 3V35 3V36 3V38 3V	39 3V49 1620 D720 P420 P510 P520	VHS A	Head Part Nos.: VEHO Machine No.: NV366 SHARP				VHS X	VHS A VHS B VHS C VHS D		213. 213. 218. 281.
P530 P615 P GEC	2620 P622 P710 P720 P7	21 P722	VHS U	Head Part Nos.: DDRN Machine No.: VC581/2 Head Part Nos.: DDRN Machine No.: 2C9 VI	/3 651 681/2/3/5 AU 0001 HED0 00	659 699 102 HE02 04 05		VHS S	VHS E VHS F VHS H VHS I		£75. £81. £21. £21. £21.
Machine Nos Iead Part No	os.: 5458161 5458165 5.: 4000H 4001H 4002H os.: 5458282 5458413 54 5.: 4001H 4004H	58415 5458992	VHS I VHS K	VC386 VC387 VC388 V VC9100 VC9300 VC940 Head Part Nos.: DDRN Machine No.: VC7300	/C477 VC481 VC 00 VC9500 VC960 1U 0001 HE09	482 VC930 VC		VHS C VHS D	VHSK VHSL VHSM VHSN		£81. £14. £26.
HITACHI Machine Nos Head Part No	s.: VT3000 os.: 5458104		VHS A	Head Part Nos.: DDRN Machine No.: VC6300 Head Part Nos.: DDRN	IU 0001 HE10			VHS E	VHS R VHS S VHS T VHS U		£21. £18. £19. £20.
Aachine Nos Jead Part No Aachine Nos	.: VT4000 VT4200 VT500 os.: 5458161 5458165	00 VT8040 VT8100 VT8500	VHS H VHS I	Machine No.: VC8300 Head Part Nos.: DDRM Machine No.: VC2300 SANYD	NU 0001 HE14			VHS L VHS F	VHS V VHS W VHS X VHS Z		£29.1 £21.1 £35.1 £14.1
lead Part No	os.: 5458282 5458413 54			Head Part Nos.: 14302 Machine No.: VTC5000 Head Part Nos.: 14302	0 VTC5150 VTC53 242 T02200			BETA D	ORIĜINA 01X0 003 01X0 027 01X0 033	085	£31.3 £46.1 £47.1
	s.: VR3605 VR3033 VR39 963 VR3993 VR3975 VR3	05 VR3913 VR3914 VR3935 3985 VR3986 VR3833	VHS A	Machine No.: VTC5350 Head Part Nos.: 14307 Machine No.: VTC9300 Head Part Nos.: 14307	762 T02000 0 VTC9455 VTC95 72 T02100	500		BETA D BETA X	01X0 040 01X0 056 01X0 057 01X0 082	002 013 002	£48.3 £61.5 £31.3 £46.1
Machine Nos HR3360 HR	3660 HR3750 HR3860	00 HR3320 HR3330 HR3350 HR4100 HR7200 HR7600 HRD121 HRD140 HRD150		Machine No.: VTC9300 SONY Head Part Nos.: A6760 Machine No.: SL3000,	2 044A, 044B, 05		7MF	BETA X BETA A	01X0 083 PHILIPS 310 274 4 691 200 5	063 14	£66. P(£49.)
HRD220 HRE MITSUBIS Machine No.	0225 HI : HS200		VHSA VHSA VHSO	Head Part Nos.: A676/ Machine No.: SL5W, 5 Head Part Nos.: A676/ Machine No.: SLC20, SLF1, F30, HF72, T20,	2 012A, 038Å, 05 5000 5100 SLC5, 2 072A, 122A, 13 C30, C33, C40, 0	5A, 129A C6, C7 I6A, 139A, 213		BETA B	691 200 3 691 200 9 691 201 1 691 201 6 691 201 7 691 202 8	98 2 6 8	£62.1 £61.1 £61.1 £61.2 £49.2 £55.2
	SON/JVC			SEFT, F30, HF72, 120,	2.55		DRI		BEL		
VID1 VID2 VID3 VID4	01X0-003-381 01X0-018-024 01X0-018-025 01X0-018-729	Tension band T3292/PU545 Take up idler T3292/PU477 Rewind idler assembly T3V Take up idler T3V00/PU492	52 16/PU49282 80	2	5.00 6.20 6.95	VP 77 VP 68	AKAI DBK135 DBK135	£0.86 £0.86	HR 2200 HR 3300 HR 3330	JVC DBK137 DBK107	ន ព ព
/ID5 /ID6 /ID7 /ID8	01X0-040-006 01X0-033-454 01X0-040-007 01X0-040-017	Loading belt T3V29/30/PU4 Roller Assy. (cass. Housing Take up idler 3V29/30/PU4 Reel motor assembly 3V29/) T3V23/PU 3967B		0.26 4.50 2.90 27.95	VP 7100 VS 1 VS 2 EG VS 3 VS 5 EG VS 10	DBK103 DBK134 DBK101 DBK134 DBK101 DBK136	£1.42 £1.76 £1.08 £1.76 £0.68 £1.65	HR 3360 HR 3600 HR 3660 HR 3660 HR 4100 HR 7200	DBK 126 DBK 103 DBK 107 DBK 103 DBK 127 DBK 139	ដ្ឋា
/ID9 /ID10	01X0-065-009 01X0-065-016	Capston motor 3V35/36/38/ Cass. housing Assy. 3V35/	39/PU55371	1V	22.10 22.00	VS 9300 VS 9500 VS 9700 VS 9800	DBK103 DBK103 DBK102 DBK103	£1.65 £1.42 £1.42 £1.96 £1.42	HR 7600 HR 7650 HR 7700	DBK138 DBK132 DBK108	ຄື ຄື ຄື
GEC/HI [®] VID11 VID12 VID13	TACHI V5577355 V6413663 V6861471	GEC 4100/Hitachi VT11E c GEC 4000/Hitachi VT33 f/f GEC 4001/2/Hitachi 93/950	rewind arm		23.50 2.75 1.95	3292 3 V 01/16 3 V 22 3 V 23	FERGUSON DBK103 DBK103 DBK103 DBK108	E1.42 E1.42 E1.42 E0.83	NV 300 NV 330 NV 332/333 NV 336	DBK110 DBK110 VID7521 VID7521	ព ព
/ID14 /ID15 /ID16	V6861482 V6886971 V2423461	GEC 4001/2/Hitachi 93/950 GEC 4004/Hitachi VT33 t/f ET541 Tuner Unit		assy.	4.20 1.80 6.00	3 V 24 3 V 31/32 3 V 35/36 3 V 38/39 3 V 42/43/44 3 V 45/48/54	DBK137 VID7806 DBK150 DBK150 VID7540 VID7540	£0.68 £0.94 £0.88 £0.88 £0.70 £0.70	NV 450 NV 777 NV 2000 NV 3000 NV 7000 NV 7200	DBK133 DBK131 DBK109 DBK113 DBK111 DBK111 DBK140	ជ ជ ជ ជ ជ ជ ជ ជ ជ ជ ជ ជ ជ ជ ជ ជ ជ ជ ជ
VID17 VID18	IAL PANASONI VXP0329 VXP0344 VX70078	Fast forward idler NV2000 Idler NV7000/7200		PLEASE NOTE	0.85 0.85 3.50	3 V 55/57 VBS 7000 VBS 7600	VID7540 VID7540 FISHER DBK146 DBK105 DBK105	£0.70 £2.66 £2.34	NV 8600 VC 381/383 VC 385/386	DBK112 SHARP DBK116 DBK116	
VID19 VID20 VID21 VID22	VXZ0078 VXP0521 VXP0463 VXP0432	Tension Band NV7000 Idler NV370 Reel Idler NV777 Pinch Roller NV333	ALL	L VIDEO SPARES HANDLING	2.65 3.40 3.30	VBS 7000 VBS 9000 FVHP 420 V 4000 H	DBK105 DBK10 VID7532 GEC DBK129	£2.34 £1.76 £1.62	VC 2300 VC 6000/6300 VC 6500 VC 7300	VID7545 DBK117 DBK117 DBK118	ជជជជជជ
	VXP0401 /FISHER	Idler wheel NV333	1	E1.25 + VAT	9.50	V 4001 H V 4002 H V 4100 H	DBK129 DBK129 DBK128 HITACMI	£0.68 £0.68 £1.95	VC 8300 VC 9300/9500 VC 9700	SONY	ដ
(1D24 (1D25 (1D26 (1D27 (1D28	4529V10800 1430662T01201 PR2758 1430490400900 1430420400300	Reel motor VTC5000/5150 Reel drive pulley VTC 5000 Pinch roller VTC5000/5150 Gear idler Fisher FVH-P61 Heart idler Fisher FVH-P61	ò		9.50 4.95 3.85 4.50 2.95	VT 11-VT 88 VT 3000 VT 5000 VT 6500 VT 6500 VT 7000 VT 8000	DBK128 DBK103 DBK125 DBK142 DBK142 DBK143 OBK129	£1.95 £1.42 £1.46 £0.77 £0.68 £0.68	SL 8000 SL 8080 SL 8500 SL 8600 SLC 5 SLC 6 SLC 6	DBK115 DBK115 DBK115 DBK115 DBK100 VID7519 DBK100	อออออออออออออออออออออออออออออออออออออออ
SHARP /ID29 /ID30	RMOTP1029 RMOTV1008	Capston motor 73/9300 Reel motor VC9700			33.55 17.95	VT 8500 VT 9300 VT 9500 VT 5000,5150	DBK144 DBK129 DBK129 SANYO VID7807	20.68 20.68 20.50 20.50 21.19	SLC 0 SLC 7 SLC 9 SLJ 7 SLT 7 ME SLT 7 MER	DBK100 DBK130 DBK100 DBK100 DBK100	ជជជជជ
(ID31 (ID32 (ID33	NIDL0006 NIDL0005 NIDL0004	Idler VC387H etc Reel idler VC9300 etc Idler wheel VC2300			1.75 1.85 2.15	VTC 6000 VTC 5300 VTC 5400 VTC 5500 VTC 6500	VID7807 DBK105 DBK105 DBK106 VID7533	£1.19 £1.19 £0.70 £0.70 £1.76 £0.78	V 55/57 V 66/67 V 7540	TOSHIBA VID7543 VID7540 DBK123	ដ ដ ដ
/ID34 /ID35	LAMPS/BULBS LA9295 LA9210S	Universal tamp without soci Universal tamp with socket	ket 290mm 310mm		0.45 0.50 0.50	VTC 9300 VTC 9350 VTC M10/11/20 VTC M21/30/31 VTC M50	DBK104 DBK145 VID7809 VID7809 VID7809	£2.66 £2.66 £0.61 £0.61 £0.61	V 8600 V 9600 V 5250 V 5280 V 5475	DBK124 VID7830 DBK148 DBK148 DBK122	ជួយពួក
JUST	SUPPLY MAKE.	P.C. MTG. leadless lamp Etc. lamp plus plastic shrou RGE RANGE OF SLIM MODEL & PART No QUOTE. AVERAGE	Line re . If pos	SSIBLE NUM	2.53 / FAX MBER •29052	or SAE Telepho (24hr.	available wit please 9" > ne 0902 - 7 answering mai & Barclaycan	× 4″ 712083 ^{chine}	alte Stock For quantit a Orders fro Nationals et	Prices subject to ration without no c queries by post ies of 100+ per line isk for special quote m Goyt. Institutions, c., accepted with of goods should be de	tice only e – Please , Schools, ficial orde

REGISTERED OFFICE. THE COACH HOUSE MUXTON LANE, TELFORD * MAIL ORDER - CALLERS STRICTLY BY APPOINTMENT


The Universal Frequency Response Curve

We are all familiar with the RC coupling arrangement shown in Fig. 1 and know that the value of the capacitor must be large enough to maintain the response down to the lowest frequencies required. Below this, the increasing capacitive reactance introduces a loss.

If the frequency response of this series capacitance/ shunt resistance combination is plotted the curve shown in Fig. 2 will be obtained. In this both the horizontal and the vertical calibrations are logarithmic, frequency is in octaves and amplitude in dB. This being so, the curve becomes a straight line at the higher and lower frequencies. At high frequencies the line is horizontal, representing the level response required of most amplifiers. At low frequencies the line has a slope of 6dB per octave.

If these two straight lines are continued towards the centre of the diagram they will meet at a frequency where the curve has a 3dB loss: this is usually known as the cut-off frequency. At one octave above this cut-off frequency the loss is only 1dB and at higher frequencies the loss becomes zero. At one octave below the cut-off point the loss is 7dB, but note that this is 1dB relative to the straight low-frequency roll-off line. At still lower frequencies the curve merges with the straight line, the response falling at the rate of 6dB per octave.

At the cut-off frequency the capacitor's reactance is equal to its resistance. Thus $1/(2\pi fc) = R$, from which the cut-off frequency is given by $f = 1/(2\pi RC)$. Now RC is the time-constant t of the coupling circuit, so we can say that $f = 1/(2\pi t)$, i.e. approximately 1/(6t). This is interesting because it shows that the low-frequency response does not depend on the individual values of the coupling capacitor and the shunt resistor but on their product, the time-constant. So there's an infinite number of combinations of R and C that will produce the same frequency response. If the capacitor's value is doubled, the resistor's value can be halved without any effect on the response curve. If the capacitor's value is doubled

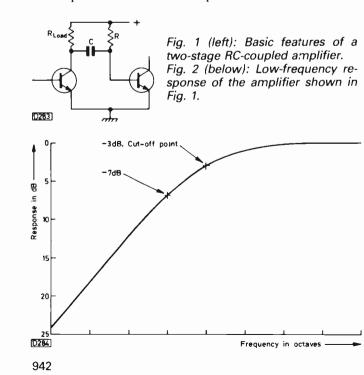

Stan Amos, B.Sc., C.Eng., MIEE

while retaining the same resistance value, the cut-off frequency is halved, i.e. the amplifier's frequency response is extended downwards by one octave.

As a numerical example, suppose we decide that an a.f. amplifier should have a loss of less than 1dB at 50Hz. This means that the cut-off frequency is 25Hz and, from the above relationship, the time-constant is $1/(6 \times 25)$, i.e. approximately 0.007sec. Any combination of R and C with a product of 0.007sec will do. A bipolar transistor stage of the type shown in Fig. 1 has an input resistance that's largely determined by the active device itself. This might be say $1k\Omega$. Thus the coupling capacitor should have a capacitance of 7μ F.

If the second transistor had been a field-effect type with a very high input resistance, the resistor after the coupling capacitor might be a biasing component with a value of say $1M\Omega$. To obtain the l.f. response just described, the value of the coupling capacitor would have to be reduced to 0.007μ F.

The relationship between cut-off frequency and timeconstant given above applies to an *RC* circuit but has universal application and can thus be used for inductive circuits as well.

The curved portion of the response shown in Fig. 2 sits symmetrically in the angle formed by the two straight lines. The curved part has a -3dB loss at the cut-off frequency, the loss (relative to the appropriate straight line) being 1dB one octave away, 0.5dB two octaves away. Beyond these points the curve merges with the straight lines.

Universatility

Why is this curve so important? Because it applies not only to a circuit (e.g. Fig. 1) with low-frequency attenuation but to any combination of reactance and resistance, whether series- or parallel-connected. It's truly the universal frequency response curve, applicable to all the simple response shapes commonly encountered in electronics. The most familiar ones are the l.f. attenuation already considered, l.f. boost, h.f. attenuation and h.f. boost. These are all shown in Fig. 3.

For the frequency response characteristic shown in Fig. 2 to apply to all of these the horizontal scale must remain the same whether movement to the right indicates increasing or decreasing frequency. Similarly the vertical scale must represent gain as well as loss. Fig. 4 shows the universal frequency-response curve.

Bass Boost

As a second numerical example, suppose that we need to provide a rising low-frequency response as part of the tone control system of a hi-fi amplifier, say a lift of approximately 12.5dB at 50Hz. From the universal curve we can see that a 12dB lift at 50Hz corresponds to a lift of 7.5dB at 100Hz and 3dB at 200Hz. So 200Hz corresponds with the "cut-off" frequency, and this gives us a time-constant t of 1/(6f) = 1/1,200.

We could obtain the required frequency response shape from an *RC* circuit in the forward amplifying chain


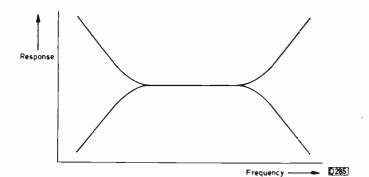


Fig. 3: Basic frequency-response characteristics.

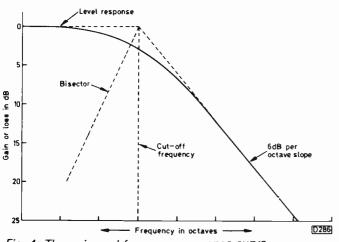



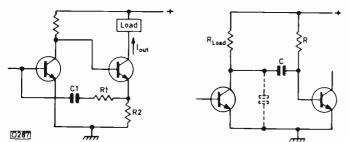


Fig. 5 (left): Two-stage current amplifier using frequencydiscriminating negative feedback for l.f. boost.

Fig. 6 (right): The shunt capacitance that causes h.f. loss in a two-stage RC-coupled amplifier.

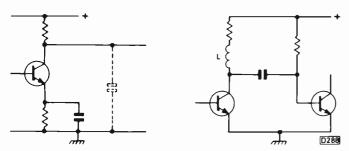


Fig. 7 (left): Use of negative feedback to compensate for h.f. loss caused by shunt capacitance.

Fig. 8 (right): Use of an inductor to maintain the h.f. response of a video amplifier.

of the amplifier, but an alternative method is to use frequency-selective negative feedback. Fig. 5 shows one possible way of applying feedback to a current amplifier. If considerable feedback is used, the gain and frequency response of the amplifier are dictated by the series connected components R1, R2 and C1. In fact the h.f. current gain (where the reactance of C1 is small) is given

TELEVISION OCTOBER 1989

by R1/R2. The increasing reactance of C1 as the frequency progressively falls removes the feedback, giving the required lift. The time-constant controlling the frequency response is thus R1 × C1. So we have R1 × C1 = 1/1,200. If R1 is 50k Ω , C1 must have a value of 1/ (1,200 × R1), i.e. 1/(1.200 × 50 × 10³)F, which comes out at 0.017 μ F.

Parallel Networks

The two numerical examples considered so far have both involved series-connected RC circuits. Our next example involves a parallel-connected network and applies to the upper end of the passband. A simple RCcoupled amplifier of the type shown in Fig. 1 has an h.f. loss whose amplitude can be estimated by using the universal frequency-response curve. This loss is introduced by the capacitance that shunts the load resistor, effectively reducing its value as the frequency rises. There are three main components of this capacitance: the transistor's output capacitance, the following transistor's input capacitance and the inevitable stray capacitance. The total capacitance lumped together is represented by the single dashed-line capacitor in Fig. 6.

Because a transistor's input capacitance depends on the Miller effect and is not simply the physical capacitance between its base and emitter (or gate and source), it's not easy to estimate the value of this total capacitance. Let's assume however a total shunt capacitance of 30pF with a load resistor of $4k\Omega$. This results in a timeconstant of $t = 4 \times 10^3 \times 30 \times 10^{-12}$ sec, i.e. 0.12μ sec. The corresponding cut-off frequency is $f = 1/(6t) = 1/(6t) \times 0.12 \times 10^{-6})$, i.e. 1.4MHz. At this frequency therefore the amplifier has a loss of 3dB and, from the universal response curve, the loss is 1dB at 700kHz, 7.5dB at 2.8MHz and 12.5dB at 5.6MHz. We are assuming that the gain of the transistors themselves remains constant at frequencies of this order – a fair assumption with modern devices.

The h.f. attenuation caused by the parallel *RC* network in Fig. 6 (from the a.c. point of view the noncollector ends of the load resistor and shunt capacitance are both earthed) can be compensated by using a parallel *RC* network in the emitter circuit to introduce negative feedback – see Fig. 7. It should be fairly obvious that for precise compensation the cut-off frequencies and timeconstants of the two networks must be equal. Thus using the figures from the previous example the time-constant of the emitter network must be 0.12μ sec. Suppose that the emitter resistor has a value of 500Ω . The value of the capacitor required in the emitter circuit is $t/R = (0.12 \times 10^{-6})/500F = 240$ pF.

Inductance

The method of calculating capacitance used so far applies equally to inductance. We'll conclude this article with an example. Inductors are not very often used to adjust the frequency response because they are fiddly to wind and respond to magnetic fields. Moreover the same effect can usually be achieved using capacitors, which are available in a wide range of values. Inductors are sometimes used in video amplifiers however to maintain the h.f. response. This forms the basis of our final example.

Fig. 8 shows an inductor L connected in series with a transistor's load resistor. We'll assume that the aim is to maintain a good frequency response over the video

bandwidth despite the effects of shunt capacitance which, as we've just seen, produces a cut-off at 1.4MHz. To offset the effect of the capacitance, the *LR* circuit must similarly have a "cut-off" at 1.4MHz and the inductive time-constant must be equal to the capacitive time-constant, i.e. 0.12μ sec. Now the time-constant of an inductive circuit is given by *L/R*. Thus the inductance required is $L = tR = 0.12 \times 10^{-6} \times 4 \times 10^{3}$ H = 480 μ H.

If this value was used in our video amplifier the results obtained would be disappointing – a check on the frequency response would show it to be far from level over the passband. This is because two important factors have been overlooked. The first is that we've not allowed for resonance. Since the inductance and the capacitance form a tuned circuit, by making both timeconstants 0.12sec we've ensured that the resonant frequency is 1.4MHz – right in the middle of the video bandwidth. True, the $4k\Omega$ load resistor in series with the inductor provides a high degree of damping, but the response curve will nevertheless have a significant hump centred at 1.4MHz.

To keep the boost to an acceptable level and ensure a reasonably level response the value of the inductance should be significantly less than the value worked out above. The mathematical concept of maximal flatness gives some idea of the inductance value to use. A maximally flat curve is one without maxima and minima, falling away from the ideal level response very gently as the frequency rises. This response can be obtained by using an inductance with a value of 0.41 of that previously calculated, i.e. 196μ H.

The second factor overlooked so far is that with an amplifier designed to handle pulse-type signals the shape of the frequency-response curve is not the best criterion of performance. Phase response also matters, and to secure a good response with pulse signals it's useful to aim at securing a maximally-flat group-delay/frequency curve. This is attained by using an inductance value 0.32 times that initially calculated, i.e. 154μ H. So an inductance value between $154-196\mu$ H would be suitable, suggesting a value of around 175μ H. If inductive compensation is to be used a medium-wave tuning inductor could, if available, be used, saving a lot of work.

This final example of inductance calculation has led us into the further subjects of resonance and maximal flatness. It was worth including in order to illustrate the problems that inductors can introduce. The capacitive examples were straightforward and illustrated the simple method of calculating the component values required to obtain the desired response. The shape of the curve can be sketched once the cut-off frequency is known, the only figures required being the 3dB point (gain or loss at cut-off) and the 1dB gain or loss an octave away.

A Day in the Life of . . .

Les Lawry-Johns

I'd been at the shop on the previous day and decided to pay another visit after lunch to make sure that everything was all right and to attend to any customers. As there weren't many I thought I'd pop into the Coach and Horses next door to have a word with the landlord Dave. Perhaps he might know about the surveyor who'd called at the shop yesterday? I knew that he was looking it over on behalf of a building society, but didn't know who had initiated the interest. Dave's son had been looking around lately, and I felt he might know something. He didn't, so I sat back and started on my half of bitter, which is all I drink when driving.

A magician friend of mine sat nearby, with his daughter and her husband. I showed them the August issue which contained those lovely letters about my retirement. I've said thanks before for all your good wishes, but must do so again. I really didn't know you cared so much.

After finishing our drinks we went our various ways. Shortly after I'd returned to the shop Bob appeared. He looks after the radio bits and pieces at the local hospital and entertains the patients with music etc. With him was the hospital's ITT TV set which had given up the ghost. He plonked it on the bench and after removing the rear cover I switched it on. Apart from the degaussing buzz there was no response. It was an ex-rental set and I'd not seen one like it before, so I can't tell you the model number.

H.T. was present at the collector of the line output transistor, and when I went on to check the components in its base circuit the set started up. So I switched off and checked carefully for dry-joints. There were a few around the coil in the base circuit. After resoldering these and some more in the vicinity the set started up each time I

switched on. I replaced the back and asked Bob for a couple of quid. He insisted on making it a fiver. So I wrote him out a bill and he carted the set off happily. That was about all the servicing required. A few friends popped in to pass the time of day, and shortly afterwards I locked up and drove back to the bungalow.

That was yesterday. I was up early this morning. Slide out of bed and step carefully over the dogs. Then start to dress, making a point of pulling my socks on whilst standing up. I'm determined to keep this up because when I have to sit down to do it I'll know I'm really getting old. Dressing complete, I walked up the road to collect the morning paper. We don't have it delivered to ensure that I keep active first thing. Back for breakfast and to feed the cat who won't live in the house but spends her time out on the roof of the shed. I hope she'll change her mind about this when winter comes. Spock's over sixteen now and won't last much longer.

After H.B. had departed on her morning's run around I looked out and saw someone familiar coming towards the front door. It couldn't be, but it was. Stan from SEME. He looked over the bungalow and the dogs didn't bark once. They know him well. After a few pleasantries Stan departed, without an order. H.B. returned shortly after and announced that one of her daughters wanted a remote control unit for her Philips TV set. So having seen Stan off I had to phone SEME for the unit.

Later another of H.B.'s daughters called, bringing with her an Alba PTV10 portable radio/TV set. I couldn't get a reading across the mains input, so I checked the transformer. It said there was a thermal fuse in series with the winding but I couldn't find it. In fact I destroyed the winding while trying to do so. Another order to make.



322

Each month we provide an interesting case of TV/video servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

Reg runs a bed-and-breakfast guest house in a large coastal town nearby. It seems that his guests are becoming more and more demanding, especially those who book in advance. By all accounts, hot-and-cold in every room, sea views and lunches packed to order are no longer good enough. There must, for some guests anyway, be an en suite colour telly.

To meet the demand in the first floor front, Reg dug out an old TV which had been lying amongst the cots, teamakers and extra blankets in the lumber room. He'd had it mended a year or two ago but it had then developed a colour problem and hadn't been used since. Now here he was with the set, on our doorstep. Leaving a quick description of the fault, and a Bay View Guest House business card, he zoomed off in the direction of the sea.

The set was a Mitsubishi Model CT2023B, about six years old. It's problem was a bad colour "stain" in the picture, on the right-hand side about a third of the way up. Our first suspect was of course the degaussing system. A quick finger test was made on the degaussing circuit posistor R901. The fact that it was warm exonerated the degaussing system, which was indeed working correctly.

External degaussing was tried next. A mains-powered degaussing coil produced vivid and pretty patterns on the screen, but when it was withdrawn and switched off the colour stain remained as before. With a plain coloured raster you could see that the error was large but was confined to a small area, in which each electron beam spilled badly on to the phosphor of the others.

In this set the neck rings and yoke can be adjusted for optimum colour purity. We went through the procedure with little conviction – small but intense areas of bad purity are seldom affected by the setting of the tube neck's ring magnets. This was no exception. Setting up the purity worked in every respect apart from the problem area. After a couple more goes with the degaussing coil we decided that the problem was either in the deflection yoke or the tube itself, with the odds heavily on the latter possibility. A second-hand scan yoke was tried, not an identical one to the original but one that was sufficiently similar to prove the point. This it did: the yoke was blameless. By now it seemed almost certain that the cause of the problem was a localised defect in the tube's shadowmask. A phone call conveyed the unhappy news to Reg. How and when did the fault arise we asked him? Apparently all had been well until the set had developed a sound problem, the details of which he couldn't recall. When the set was returned, the sound was fine but the picture problem had appeared. We came to the conclusion that the previous repairer had dropped the set when delivering it and had wrecked the shadowmask.

Thinking about this while he was driving home, the technician had a sudden thought – of such intensity that he turned around and returned to the workshop! Ten minutes later he emerged with a big smile. Well? See next month's *Television*!

ANSWER TO TEST CASE 321 – page 863 last month –

Last month's test case had John deeply involved with a Sharp VCR whose fault was intermittent shutdown during play or record. When it happened the tape and the spools stopped completely, as they would in the pause mode, with the head drum rotating. This VCR was not slyly entering the pause mode however: the cessation of reel sensor pulses sent the syscon into the emergency shutdown mode.


The initial theory of low take-up torque was wrong – if this had been the cause of the problem the capstan would have continued to operate, spilling tape into the machine. The ideas of excessive back tension or drum friction were nearer the mark, but tests proved that these were both normal. When he came to check the pinch roller pressure, a sensible move under the circumstances, John did what he should have done at the outset – he took a close look at the capstan and pinch roller. The cause of the problem was then immediately apparent. There was a great build-up of black gunge on the capstan shaft, thickest at points corresponding to the top and bottom edges of the tape. It was sufficient to hold off the roller from the tape's surface, so that the tape was not gripped tightly as it passed through.


In these circumstances traction depended on tape type, temperature, the time of day and Murphy. Loss of tape drive via the pinch roller stopped the reels, the syscon then instigating shutdown. A new pinch roller and a thorough clean of the capstan shaft, along with the rest of the tape path, restored normal working.



Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by the The Riverside Press Ltd., Thanet Way Whitstable, Kent. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £20, overseas (surface mail) £24 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.



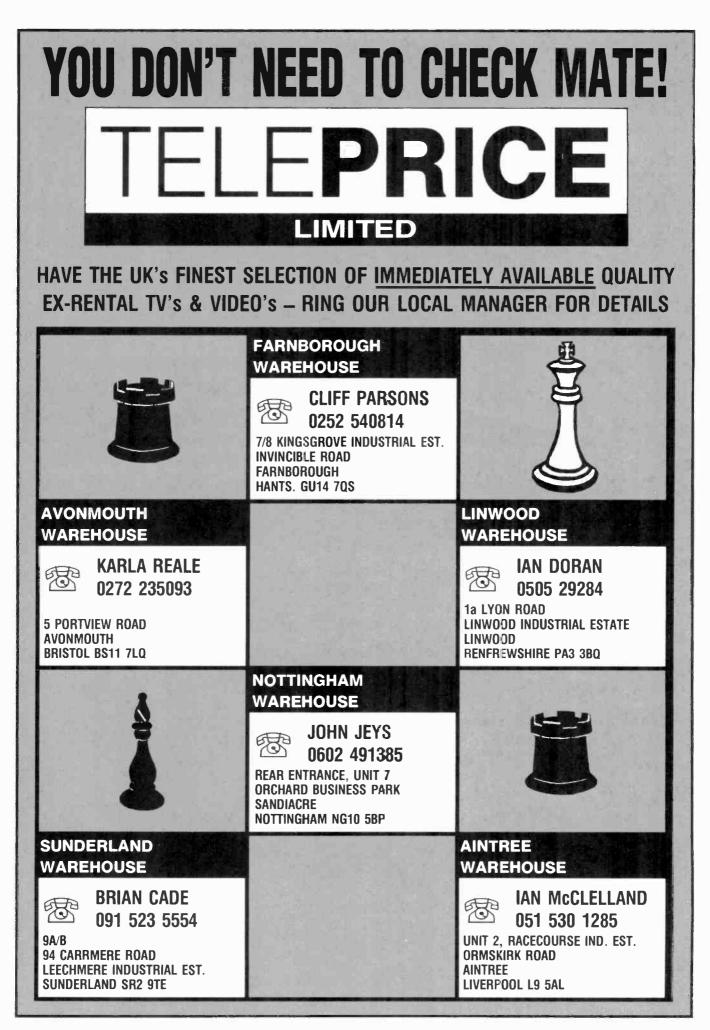


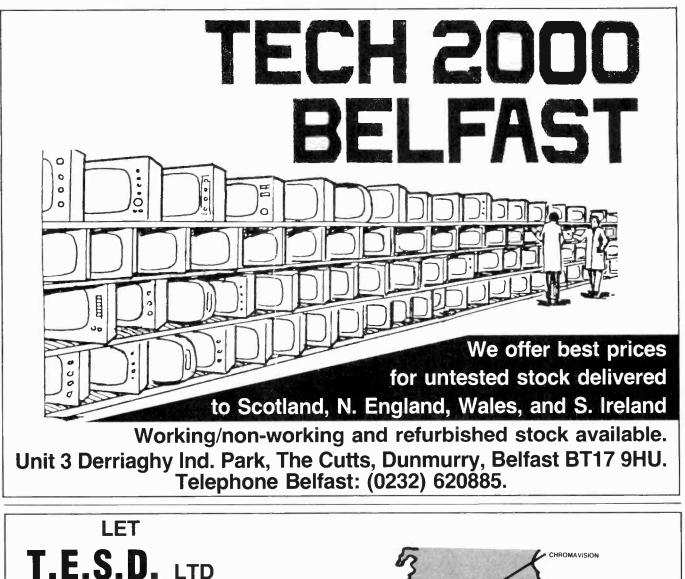



TELEVISION OCTOBER 1989

JOHN TODD TELEVISION & VIDEO WHOLESALERS	
4,000 sq ft OF TV & VIDEO	

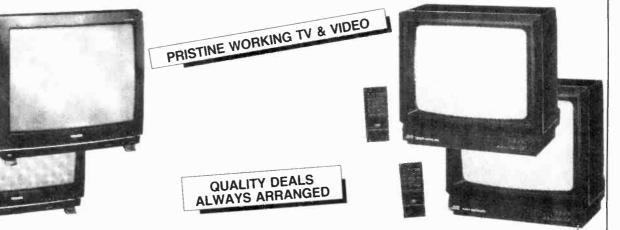

Thorn 3V29/30 Working

All 9000 Series Televisions, Working/Non-Working, Untouched, as since disconnected, from rental user Thorn/No Thorn Portable Televisions, all makes,	£10
working from	£40
working, from Thorn TX9 Off the Pile	£26
Thorn TX9 Working and Tested	635
Thorn TX10 Non Text Off the Pile	£30
Thorn TX10 Non Text Working and Tested	£40
Thorn TX9 & 10 Text Off the Pile.	£45
Thorn TX9 & 10 Text Working and Tested	
ITT Digivision Off the Pile Working/Non Working	£80
USUAL BARGAIN CORNER COLOUR SETS FROM 25	
PHILIPS G8, DECCA, BRADFORDS ETC.	

CAMERA EQUIPMENT,
BATTERIES AND ACC.,
CAMCORDERS, PORTABLE
UNITS, FULL SIZE, C
FORMAT VHS, TUNER
TIMERS, CHARGERS
ETC. ETC.
ALL STOCKED IN QUANTITY
— PHONE FOR DETAILS.

11101110125/00 1101Killg	,5
Thorn 3V29/30 Non-Working£5	55
Thorn 3V35 Working£9	95
Thorn 3V35 Non-Working£7	′5
Thorn 3V31/32 Working£10	0
Thern 3V31/32 Non-Warking£6	i5
Various Front Loading VHS Videos from Sharp, Philips, Hinari etc, etc£7	'5

OTHER LINES IN STOCK IN QUANTITY INCLUDE DATATEXT 90 PORTABLES, TEXT PORTABLES, **GRAPHIC PRINTERS, THERMAL** PRINTERS, VIDEO PRINTERS, **KEYBOARDS, VIEWDATA** TERMINALS.

TX9 CATHODE RAY TUBES. **TESTED AND PERFECT AT £15.00.** AND MANY, MANY MORE.

STOP PRESS! FERGUSON FREE STANDING STEREO TELEVISION SPEAKERS BLACK ASH FINISH. WILL SUIT ALL STEREO TELEVISIONS INCLUDING FERGUSON 22BS, 51AS, 59BS, 66BS PLUS MANY MORE — IN FACT ANY TV. WITH AN EXTENSION SPEAKER SÓCKET. THESE UNITS CAN BE USED IN CLOSE PROXIMITY WITH **BRAND NEW & BOXED £15** THE TV WITHOUT CAUSING PROBLEMS. Per Pair Plus VAT

> PRICES. ALL PRICES EXCLUDE VAT. NEW HANDSETS CHARGED EXTRA. **ORIGINAL HANDSETS FREE.**

TRADE ONLY

£65

JOHN TODD TELEVISION & VIDEO WHOLESALERS Units 15/16, Stone Business Park, Stone, Staffs

BARCLAYCARD PHONE 0785 817695 and talk to Harry or Paul Roman

TELEVISION OCTOBER 1989

VISA



GLASGOW SCOTLAND'S LARGEST WHOLESALER **75 ROBERTSON STREET, GLASGOW** (EX SABACO'S PREMISES) Junction 19 off M8 LARGE SELECTION OF GRANADA AND THORN WORKING AND OFF THE PILE **AT UNBEATABLE PRICES! DUE TO TREMENDOUS SUCCESS OF LAST MONTH'S OFFER** WE ARE REPEATING OUR SENSATIONAL OFFER FINLANDIA REMOTE CONTROL SETS (WORKING) from $\pounds 25 + VAT$ including hand unit Spares available and diagram Deliveries can be arranged **RING STUART** 041-221 2146 for latest prices

THE RIC MONITOR II 100 WATT SPEAKER KIT £60.00 + £3.50 P&P (pair)

RESPONSE: 55Hz - 20kHz BASS POLYMER CONE D: 22cm DOME TWEETER: 14mm OVERALL SIZE (HWD): 382,252,204mm RECOMMENDED AMP POWER: 10-100 watts per channel The performance stan-dard achieved in this this compact design is distinc-tively superior to anything else available at the price. The drive units used are of sophisticated design and have been carefully integrated with a Complex Crossover.



Stereo performance is exceptionally good with a well focussed sound stage and sharp resolution of detail. Distortion throughout the frequency range is low even at quite high power input and this gives a great sense of dynamic range and openness especially when used in bi-wired mode

Supplied with:--- 2 READY CUT BAFFLES, ALL CROSSOVER COMPONENTS, 2 BASS MID-RANGE, 2 DOME TWEETERS, HOOK UP WIRE, GRILLE CLOTH, SCREW TERMINALS AND SCREWS

CROSSOVER KIT. To build 2 sets of crossovers **£11+£1.75** post. (Featured in *Everyday Electronics*—May 1989 issue). Reprint Free with Kits

AMPHONIC 125 + 125 POWER AMPLIFIER




8in SOUND LAB 60W £12.95 Res freq. 38Hz full range 12in DANTEX 100W £21.75 Res freq. 23Hz bass unit Postage £3.20 each order

★ SPECIAL PURCHASE Batteries C size NiCad 2.2 Ah EVERY-READY AN220 £1.98 each

BARGAIN PACKS BUY 10 GET 1 FREE Please state pack(s) required

No=	•0	rder No. Qty = Quantity per pack	
No BP010		ty	1
BP012	- 1	2 6 ¹ /2" Speaker 4Ω 10 watt	
BP013 BP0154		V AS Speaker 411 O Wall made by E.M.I.	
		grill. For small p.a. or in car use.	
BP015E	3 1	J 30 watt, dome tweeter. Size 90×66mil JAPAN made	
BP016	6	2200µf can type Electrolytic 25V d.c computer	
BP017	3	grade <i>made in UK by PHILIPS</i> 33000µf 16V d.c. electrolytic high quality	
BP018	3	computer grade <i>UK made</i> 2000μf 50V d.c. electrolytic high quality	
		computer grade made in USA	
BP019 BP020	20 4	20 ceramic trimmers Tuning capacitors, 2 gang dielectric a.m. type	
BP021	10	3 position, 8 tag slide switch 3 amp rated 125V a.c. made in USA	1
BP022	5	Push-button switches, push on push off, 2 pole	ł
BP023	6	change over. PC mount <i>JAPAN made</i> 2 pole 2 way rotary switch	ł
BP024	2	Right angle, PCB mounting rotary switch, 4 pole, 3 way rotary switch <i>UK made by LORLIN</i>	1
BP025	4	3 pole, 3 way miniature rotary switch with one	ļ
BP026	4	extra position off (open frame YAXLEY type) 4 pole, 2 way rotary switch UK made by LORLIN	I
BP027 BP028	30 10	Mixed control knobs	
BP029	6	Slide potentiometers (popular values) Stereo rotary potentiometers	1
BP030	2	100k wire wound double precision potentiometers UK made	
BP031	6	Single 100k multitune pots, ideal for varicap	
BP032	4	tuners <i>UK made by PHILIPS</i> UHF varicap tuner heads, unboxed and	
BP033	2	untested <i>UK made by PHILIPS</i> FM stereo decoder modules with diagram	1
BP034	3	UK made by PHILIPS	1
		AM IF modules with diagram UK made by PHILIPS	l
BP034A	2	AM-FM tuner head modules. UK made by MULLARD	I
BP034B	1	Hi-Fistereo pre-amp module inputs for CD, tuner	
		tape, magnetic cartridge with diagram. UK made by MULLARD	Į
BP035 BP036	6 6	All metal co-axial aerial plugs Fuse holders, panel mounting 20mm type	I
		JAPAN made	1
BP037	6	In line fuse holders 20mm type UK made by BULGIN	l
BP038 BP039	20 6	5 pin din, 180° chassis socket Double phono sockets, Paxolin mounted	L
BP041	3	2.8m lengths of 3 core 5 amp mains flex	l
BP042 BP043	2 30	Large VU meters JAPAN made 4V miniature bulbs, wire ended, new untested	l
BP044	2	Sonotone stereo crystal cartridge with 78 and LP styli JAPAN made	l
BP045	2	Stereo cassette record and play heads	l
BP046	4	JAPAN made 6-0-6 4VA mains transformers, P.C. mount	
BP047	1	UK made 24V 750mA mains power supply. Brand new	
		boxed UK made by MULLARD	
BP049	10	OC44 transistors. Remove paint from top and it becomes a photo-electric cell (or P12)	
BP050	30	UK made by MULLARD Low signal transistors n.p.n., p.n.p. types	
BP051	6	14 watt output transistors. 3	l
		complimentary pairs in T066 case	Ļ
BP052A	1	(Ideal replacement for AD161 and 162s) Tape deck pre-amp IC with record/replay	
PD052	E	switching No LM1818 with diagram	
	5 10	5 watt audio ICs. No TBA800 (ATEZ) Motor speed control ICs, as used with most	
		cassette and record player motors	L
BP055	1	Digital DVM meter I.C. <i>made by PLESSEY</i> as used by <i>THANDAR</i> with diagram	ŀ
BP056	4	7 segment 0.3 LED display (R.E.D.)	
BP057 BP058 2	8 00	Bridge rectifiers, 1 amp, 24V Assorted carbon resistors	
BP059	1	Power supply PCB with 30V 4V/A transformer.	
BP060	1	MC7818CT IC & bridge rectifier: Size 4"×2¾" Transcription record player motor 1500rpm	
		240V a.c.	
BP061 BP063		6.35mm Mono jack plugs	
		6.35mm stereo switched jack sockets Coax chassis mount sockets	
BP065	1	3mtr Euro-mains lead with a matching	
	_	chassis socket	
		MULTIBAND RADIO	
		VHF 54-176 MHz + AM CB BANDS 1-80 Listen to: AIR TRAFFIC CONTROL,	
Sparth		AIRCRAFT, RADAR	
N.		PUBLIC UTILITIES	
STRA:		LI5.95 MANY MANY MORE	
13 × 1	I	POSTAGE £2.85 SQUELCH CONTROL	
		"RUBBER DUCK AERIAL"	
RADI	0	and TV COMPONENTS ACTON LTD	
		STREET, ACTON LONDON W36NG	
MAIL OI	RDE	R TERMS. POSTAL ORDERS and or CHEQUES	ī
with ord	ers.	Orders under £20 add £3.00 service charge. Nett	1
1000		ounders and r.c.o. only.	10

 ACCESS + VISA. Phone orders between 9.30 & 12pm please Phone: 01-723 8432 or 01-992 8430 Callers 323 Edgware Road, London W2





An easy to build amplifier with a good specifica-tion. All the components are mounted on the single P.C.B. which is already punched and backprinted.

- 30W×2 (DIN 4 ohm)
- CD-Aux, tape I, tape II, tuner and phono inputs
- Separate treble and bass

 Separate treble and bass
 Headphone jack
 Size (H.W.D.) 75×400×195mm
 Kit enclosed: case, P.C.B., all components, scale and knobs £36.80. post £3.50
 (Featured project in *Everyday Electronics* April 1999 jacua Poprint Econ with kits 1989 issue). Reprint Free with kit



In the cut-throat world of consumer electronics one of the questions designers apparently pon-der over is "Will anyone notice if we save money by chapping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are quite common and that really is quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a com-pact independent TV tuner that connects direct to your Hi-Fl is a must for quality reproduction. The unit is mains operated. This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. £29.50 +£2,50 p&p

As above but with built-in stereo headphone amplifier for the hard of hearing

You can tune into the TV channel you want while still receiving the picture on your TV set. In fact it is rather like a second television, but without the screen. So that the ordinary TV can be placed for everyone to see, and the volume on it can be comfortable for others, while the sound tuner can be placed where you can control it. You will need to plug in one of your own listening aids such as headphones or an induction loop to hear the sound. The tuner is mains operated, has 5 pre-selected tuning controls and can be used in conjunction with a video recorder.

Size: 270×192×65mm. £35.90 +£2.50 p&p



£6.20 +£1.50 P&P 2 for £10 +£2.50 P&P EXTRACTABLE HOUSING FOR YOUR CAR STEREO * SIZE DIN E HANCLE INCLUDED * SPACE FOR MEMORY BATTERY 2 SPEAKER SYSTEM

2 SPEARER 3TS IEM. ENABLES YOU TO REMOVE YOUR VALUED STEREO FROM YOUR CAR (WITHOUT THE AID OF A HAMMER AND CHISEL, CHAINSAW ETC). £9.95 postage £2.50



All Idlers	are Ma	nufacturers	s Origin	al. V	IDE	O "RE	FU	RB" K	ITS
FERGUSON	3V29/30	FERGUSON	3V35/39	FISHER	FVH-P615	HITACHI VT8	000 Series	НІТАСНІ	VT9000
Take Up Idler Reel Idler Take Up Clutch Belt Kit Pinch Roller	1.85 2.75 2.75 1.95 3.95	Take Up Idler Reel Idler Take Up Clutch Belt Kit Pinch Roller	1.85 3.25 2.80 1.75 3.95	ldler Belt Kit Pinch Roller	4.95 1.95 3.95	F/F Rewind Idl. Wind Roller Reel Table Belt Kit Pinch Roller	3.95 0.80 2.45 1.50 3.95	Play Idler Play Pulley Belt Kit Pinch Roller	Series 4.35 0.90 1.50 3.95
KIT 1	£10.75	KIT 2	£10.85	KIT 3	£10.65 £8.95	KIT 4	£10.85	KIT 5	£10.70 £9.45
HITACHI	VT11/17/ 19/33	PANASONIC	NV300/333	PANASONIC	NV370/830/	PANASONIC	NV2000	PANASONIC	NV7000
F/F Rewind Idl. Belt Kit Pinch Roller	2.75 2.95 3.95	VXP 0433 Idler VXP 0401 Idler Belt Kit Pinch Roller	4.95 1.05 2.95 3.95	VXP 0521 Idler Belt Kit Pinch Roller	850 3.95 1.95 3.95	VXP 0329 Idler VXP 0331 Idler Belt Kit Pinch Roller	2010 0.95 2.25 3.95	VXP 0343 Idler VXP 0344 Idler Belt Kit Pinch Roller	Series 4.95 0.95 1.95 3.95
KIT 6A	£7.95	KIT 7	<u>£12.90</u> £10.75	KIT 8	£9.85 £7.95	KIT 9	£6.95	KIT 10	£9.15
As above includi Clutc Mechan	ng h	SANYO Reel Drive Reel Motor Belt Kit	VTC5000 5.95 6.95 0.95 £1 3.85	SHARP Idler 0005 Belt Kit Pinch Roller	VC9300/ 9500 3.50 2.50 3.95 <u>.29.95</u>	SHARP Idler 0005 Belt Kit Pinch Roller	VC381- 390 3.50 2.50 3.95 <u>£9.95</u>	ORDERI Please add Post & Pac Then add 15% C.W.O ON Sorry	50p king % VAT LY
KIT 6B	£17.50	KIT 11	£11.95	KIT 12	£8.50	KIT 17	£8.50	Trade O	nly
VOLTA REGULAT		VIDE	:0 H	IEAD	S	VII	DEC	HEA	DS
STK 772B STK 5332 STK 5361 STK 5421 STK 5481 STK 5482 STK 7348 STR 441 STR 451	Each 5.95 3.95 6.95 5.95 5.95 4.95 5.95 5.95	AKAI VP 7100/7200/970 VP 77-88 VSI-2.5 ALDA 4000	Each 00 14.50 14.50 14.50 24.25	HINARI VXL2 VXL4 VXL5 VXL6 VXL35 V20H	Each 23.00 23.00 22.00 23.75 23.00 22.00	PHILIPS VR6420/6460 VR6462/3/4 SAISHO VR705-805-905 VR1000-1600 VR1000-1600	Each 21.50 35.00 23.00 23.00	SOLAVOX 1000 SONY C5/6/7 SLC 20/24/30/33/4	Each 24.25 18.95 4 21.50
STR 454 STR 4211 STR 5412 STR 6020 (kit) STR 50103 * STR 58041 * R2M AVAL		AMSTRAD 4500/5200 4600/4700 7000 90 00	22.00 23.75 23.00 23.75	MATSUI VX500-773 inc MITSUBISHI	22.00	SAMSUNG VB900-910 VX510/20 VX616/626/627 VX717	24.00 24.00 24.00 24.00	TOSHIBA V31/33 9600 V55-57 V71-87 V93	22.50 14.50 23.00 23.00
GENUINE SH GEZZIOUS REE MOT	L DR	FERGUSON 3V00-3V22 3V29 (P.C.B. or " 3V23/35-39 3V32 3V48 3V44/45/54/55	14.50 14.50 14.50 38.00 38.00 24.50	HS303/304 HS320 HS700 HS300/1/2 ORION VH 2500-2948 inc VR 2949-821 inc.	28.00 28.00 28.00 32.50 23.00 23.00	SHARP VC200/VC300/330 381/4/5/7/VC388 477/481 VC220 VC581/3/5 VC9300/9500/9700 DDR MU 0001	21.50 21.50 21.50 21.50 21.50	TRIUMPH VR9500 VR9501 VR9592	
Suitable AMSTRAD	e for	FIDELITY	24.00	PANASONIC		SANYO VTC9100/9300 VTC5000/6500	35.00 29.50	3 HEA	
VR7000 Saisho VR705-805-9 Sharp	905	FISHER FVHP 420-910 (in GEC/HITACHI 5000	23.50	NV2000/3000/7000 8000 NV300/32/33 NV230/260/270/28 NV470/480/NV100 NV370 NV380 NV330 NV366	14.50 14.50 0 31.50	VTCM10/11/20/21 HR 1100/1300 SENTRA 8000	29.50 39.95 24.25	LES3 5%	
VC381/3/6 VC2300/3300 9300/9500/95 £13.95 6	700	VT6500/8000/9300 VT11/33 VT17/19 VT35/38/39 GOLDSTAR	0 22.50 22.50 39.00 39.00	NV430/460 NV730 NV777 NV788 NVG10/12/14 NVG18 NVG21	31.50 31.50 27.95 46.00 23.50 41.75 46.00	UNIT 2 BURTO	00, J.C. AI N RD., SH	BYN COMPLE EFFIELD S3 8E	Х,
210.50 0		4000 Series 8000	24. 2 5 24.25	NVG30 NVG40	30.00 30.00	V.A.T. Reg. No.			Est. 1973)

TELEVISION OCTOBER 1989



Microwaves

B Stock

£69.00

R/C Handsets are Extra All prices are exclusive of VAT

ASK ABOUT OUR

FREE

DELIVERY

Panasonic NV333

Panasonic NV366

Panasonic NV7000

Panasonic NV 7200

Panasonic NU370

£65.00

£75.00

£75.00

£85.00

£95.00

IMPORTANT ANNOUNCEMENT BY THE DISPLAY ELECTRONICS GROUP

The Directors of the Display Electronics Group are pleased to announce that we have acquired the business and assets of the CRT manufacturing unit of Centronic Ltd. Centronic Ltd. have been established as CRT manufacturers for more than 40 years and the business will be continued by a new company New Century Electronics Ltd.

Display Electronics Ltd. have been established as CRT Regunners/Remanufacturers for more than 20 years.

As a result of the experience thus consolidated into the one group we are able to offer, uniquely, a total CRT engineering capability. Although the two companies' activities are complimentary they will be run as separate enterprises. Manufacturing/ product development will be undertaken by New Century Electronics at our Uxbridge (near London Airport) head office. Regunning/remanufacturing will be continued at our lver (Bucks.) factory.



る

0270 582924 (2 lines)

Williams Street Warehouse.


Crewe, Cheshire.

FROM M6 J16

CREWE TOWN

MACON WAY

FIRE

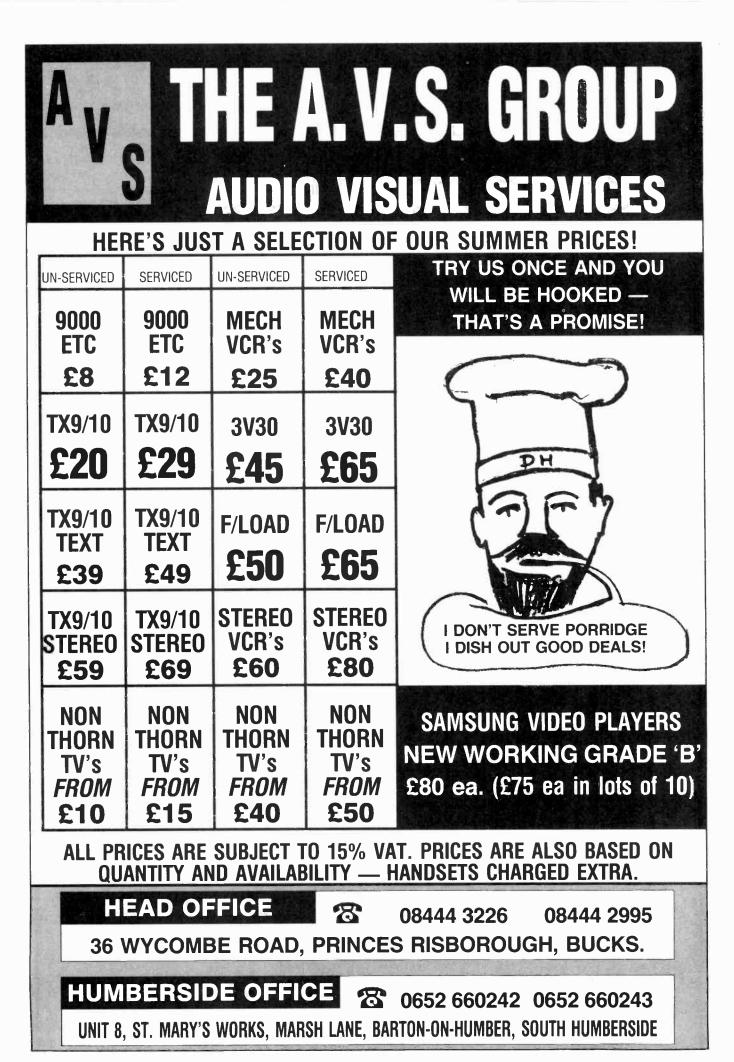



UNIT 18, TILE CROSS TRADING EST. TILE CROSS ROAD, MARSTON GREEN, BIRMINGHAM B33 0NW.

THORN EX-RENTAL SETS FULLY RECONDITIONED & GUARANTEED GOOD RANGE HELD AT KEEN PRICES — PHONE FOR DETAILS

!!! TRADE SERVICE AVAILABLE !!! UNRANTEED LIDEOS O on all makes ^{4UDIO} MIDI SYSTER ATELLITE IN STOCH **EXPORT ENQUIRIES WELCOME RING: NORMAN, GLORIA OR PAUL** 021 779 5734 021 779 5465 **TRADE ONLY** 021 779 5466 021 779 4701 FAX: LA4440 LA4445 LA4460 LA4461 LA4500 LA4505 LA4507
 C3.80
 T. POWE

 C3.80
 T. POWE

 C4.50
 16 PADDINGTON G

 C4.50
 16 PADDINGTON G

 C3.30
 CONDON W2 11

 C3.31
 W2/CFRERGUSON 3HSS

 C3.31
 HTACHI VIS000

 C4.32
 HTACHI VIS0000

 C4.35
 SUV DEO SPARES

 C3.31
 V/C Pinch Roller

 C3.31
 V/C Pinch Roller

 C3.31
 V/C Pinch Roller F/Rew.

 C1.32
 UNC Pinch Roller F/Rew.

 C1.33
 UNC Pinch Roller S000.5300

 C3.34
 CHACH ANGE 10 ANGE 1 AN103 £1.95 £2.20 £1.75 £2.30 £2.90 £2.50 £1.50 £1.50 £1.50 £1.50 £1.75 HA11749 HA11753 HA11753 HA11758 HA17758 HA17758 HA17788 HA17788 HA17788 HA171788 HA12002 HA12003 HA12003 HA12002 HA12038 HA12403 HA12403 HA12413 HA12402 HA12413 HA12402 HA12413 HA13007 HA13402 HA134 TDA3540 TDA3541 TDA3560 TDA3560 TDA3561A TDA3562A TDA3562A TDA3652 TDA4500 TDA4600/20 TDA4600/20 TDA4600/20 TDA4500 TDA7270 UPC575C UPC1001H UPC1018C UPC1025H 17.503 55.253 2503 557.75 557.75 557.50 757.75 557.50 757.75 557.75 57 57.75 57 57.75 57 57.75
 111211
 111211
 111211
 111211
 1112111
 1112111
 1112111
 1112 B41320 B41320 B41330 B413602A B43502A S J HEDUZU TA 7063P TA 7065P TA 7005P TA 7007AP TA 7073P TA 7073P TA 7073P TA 7073P TA 7074P TA 7123P TA 7136P TA 7217AP TA 7207P TA 7227TAP TA 7207P TA 7222AP TA 7222AP TA 7222AP TA 7222P TA 7222P TA 7222P TA 7222P TA 7222P TA 7223P TA 7223P TA 72240AP TA 72240AP TA 72240AP TA 7223P TA 7223P TA 7223P TA 7223P TA 7223P TA 7232P TA 7232P TA 7235P TA 723 POWELL AN1270 AN203 STK430 AN210 AN211A 16 PADDINGTON GREEN, LONDON W2 1LG Tel: 01-723 9246 STK433 STK433 STK436 STK436 STK437 STK439 STK439 STK443 STK443 STK443 AN2178 AN228W AN236 AN240P AN241P AN259 AN260P 1.44508 LA4520 LA4570 LA5112 LA5212 LA5224 LA62324 LA62527 LA62527 LA62520 LA7016 LA7031 LA7032 LA7215 LA7250 LA7507 LA7520 LA7507 LA7520 LA7507 LA7520 LA7507 LA7520 LA7507 LA7520 LA7507 LA7520 LA7507 LA7507 LA7500 LA7520 LA7500 LA7520 LA7500 LA7520 LA7500 LA7520 LA7500 LA7520 LA7500 LA7520 LA7500 LA7507 LA750 STK426 STK469 STK469 STK463 STK463 STK463 STK463 STK463 STK463 STK463 STK4029 STK0029 STR000 STR000 STR000 STR000 STR000 STR00 $\begin{array}{c} \mathbf{22.00}\\ \mathbf{21.00}\\ \mathbf{22.05}\\ \mathbf{22.05}\\ \mathbf{22.05}\\ \mathbf{22.05}\\ \mathbf{22.05}\\ \mathbf{22.05}\\ \mathbf{22.05}\\ \mathbf{22.05}\\ \mathbf{22.05}\\ \mathbf{22.03}\\ \mathbf{22.05}\\ \mathbf{22.03}\\ \mathbf{22.03}\\$ £15.00 £15.00 £21.00 £22.00 £21.00 AN262 AN264 AN271 AN271 AN271 AN271 AN295 AN301 AN305 AN301 AN305 AN305 AN316 AN316 AN316 AN316 AN316 AN340P AN360 AN3640 AN3640 AN3640 AN377 AN6102 AN51511 AN5265 AN5410 AN5410 AN5410 UPC1031H UPC1032H £38.00 £22.00 £36.00 £22.00 UPC1158H UPC1185H UPC1188H UPC1225H UPC1230H UPC1263C UPC1277H UPC1363C UPC1364C UPC1364C UPC1384C UPC1384C UPC1384C UPC1384C UPC1394C UPC1394C UPC2002 UPC4558C £20.00 £23.00 £4.95 £2.95 £1.75 £2.75 £1.85 £2.95 £1.95 £2.250 £29.50 £3.00 £5.95 £4.95 £28.75 BC639 BC640 BFR90 BFR90 BFY90 BR303 BRY56 B1106 B1208A BU208A BU208A BU208A BU208A BU208A SU500 BU508A 2N3055 2N3773 2SA733 2SA1104 2SA1106 LC7800 M51534P M5155P M51102L M51104L M51514 M515168L M515168L M515168L M515168L M515168L M515168L M515168L M51574 M53730 M83714 M83773 M83774 M83775 M83775 M83775 M83776 M8776 M87 AN5510 AN5512 AN5612 AN5612 AN5620X AN5730 AN5730 AN5733 AN5750 AN5750 AN5753 AN6250 AN6326N AN6326N AN6326N AN6328N AN6336N AN6336N AN6336N AN6356N AN6356N AN6356N AN6356N AN6356N AN63571 AN6352 **ENQUIRIES OTHER ITEMS** £5.50 IDA1074A TDA1074A TDA1151 TDA1170S TDA1170S TDA1510 TDA1515 TDA15155 TDA15155 TDA15155 TDA2002 TDA2004 TDA2004 TDA2006 TDA2006 TDA2006 TDA2006 TDA2020 TDA2020 TDA2020 TDA2020 TDA2026 TDA200 CASSETTE MOTORS £3.45 £3.45
 CASSETTE HEADS

 £1,50
 Auto Rev.

 £2,50
 Auto Rev.
 2SB546A £2.75 2SC461 2SC1364 Enquines invited for any Japanese I.Cs. As we have imported for over 10 years ITEMS DESPATCHED WITHIN 48 HOURS 2SC1942 2SC1969 STK014 STK015 STK016 STK025 STK043 STK077 STK078 STK080 2SC2166 2SC2580 2SC2581 2SC3156 2SD401A 2SD1398 2SD1453 Please add 70p post and packing and then add 15% VAT to total Callers by appointment: opening times 10am-5pm, Mon-Fn, 9-12 Sats. VISA/ACCESS ACCEPTED MIN. TELEPHONE ORDER \$5.00

TELEVISION OCTOBER 1989



TELEVISIONS - VIDEOS - TELEVISIONS



A NEW NAME IN

TRADE SURPLUS TVs

Large selection mainly THORN — GRANADA STOCK

Discount ten or over

ALL SIZES AVAILABLE Thousands in stock. Good quality. Fresh stock every week.

Portables, Teletext, VHS Videos, STD 20", 22", 26"

Complete loads at discount prices

All stock collected from source by our transport and handled with care.

(0388) VIEW-TEL TELEVISIONS SWAN STREET, EVENWOOD, 832832 Nr. BISHOP AUCKLAND, CO. DURHAM.





ALL STOCK ITEMS ARE DESPATC

£4.95 £4.95 £4.95 £4.95 £4.95 £4.95

£5.95 £4.95 £4.95 £4.95

65.95

£6.95 £6.95 £4.95

VIDEO HEADS REPLACEMENTS GENUINE HEADS All our replacement heads are brand new precision Japanese heads not refurbished. Panasonic Panasonic NV2000, NV2010 NV7000, NV7200 NV333, NV370 NV366. NV688, NV777, NV788 £44.00 £44.00 £44.00 £64.50 £64.50 Panasonic Panasonic £16.00 3HSS(N) £16.00 Fils model numbers: NV7000. NV2000, NV7000. NV333, NV8600. SHSS(N) £19.90 Fits model numbers: NV370 & Philips VR6460. 3HSS(4N) £38.50 Fits model number: NV366 538.50 Fits model number: NV366 538.50 Fits model number: NV366 538.50 NV730. £67.50 All others available P.O.A. Ferguson 3V00, 3V16, 3V22 3V29, 3V30 £59.90 £59.90 £66.90 £59.90 3V32 3V35, 3V36, 3V38, 3V39 Fils model number: NV730 E16.00 SHSS(V) £16.00 Fils model numbers: 3V00, 3V16, 3V22, 3V28, 3V36, 3V38, 3V38, 1V32, 3V36, 3V38, 3V38, 1H2200 HR3300, HR3300, HR3330, HR3300, HR3200, HR3200, HR300, HR300, HR3300, HR3300, HR3300, HR3300, HR3300, FIR54VB SHS54VB £14.50 Fits model numbers: 3V32. £44.50 Sharp VC7300, VC7700, VC7750 £69 90 VC8300 F69 90 VC9300, VC9500, VC9700. VC381, VC383, VC386. VC482. All others available P.O.A. £62.00 £62.00 £62.00 Sharp £26.50 SHSSISP £26.50 Fils model numbers: VC9100 VC9500, VC9700, VC381, VC3831, VC383, VC388, VC482 Sanyo VTC5000, VTC5150 VTC5300, VTC5400 £39.90 £39.90 £39.90 Toshiba VTC9300 PS3B(T) £26.50 Fits model numbers: V9600, V31B, V33B. SLC5, SLC6, SLC7 £49.50 £49.50 £54.50 £54.50 SLC3, SLC3, SLC3, SLC SL8000, SL8080. SLC20, SLC30 ... SLC9. Hitachi 3HSS(H) £26.50 Fits model numbers: VT8000, VT9300 etc. Fits model numbers: VT8000, VT9300 etc. Sony £19,95 Fits model numbers: SLC5, SLC6, SLC7, SL300 also various NEC models £26,50 P848(25) £26,50 Fits model numbers: SLC20, SLC30, SLC40, SLC50, SLC50, SLC50, SLC50, SLC50, SLC50, SLC50, SLC50, SLC60, SLF60, Toshiba £59.90 £69.90 V9600. V8600. V31, V33 V55, V56 £59.90 £59.90 Hitachi PITACOL VT5000, VT5500 VT6500, VT8000, VT8300 VT6500, VT8700 VT9300, VT9500, VT9700 VT11E, VT14E VT17E, VT19E VT33E £49.50 £49.50 £49.50 £49.50 £49.50 £45.50 £54.60 Amstrad/Saisho Amstradyzatsh0 £28,50 SHSS(R) £28,50 Fits model numbers: VCR7000 and all models using Oron chassis. £28,50 Fits model numbers: VCR4500, VCR5200, VCR5200, £49.50 Philips VR6460 £44 nn Fisher/Fidelity VR6462, VR6467 3HSS(SF) <u>529.90</u> VR6462, VR6467 Fits model numbers: FVHP615, FVHP710, Please call if your model is not listed. V1000. £42.90

		GENUINE	BELT	KITS	REPLACEMEN
S	Panasonic			Panaso	nic
044.00	NV2000, NV201	0	£6.50	NV2000,	NV2010
£44.00 £44.00	NV7000, NV720 NV333, NV366				NV7200 IV366
£44.00	NV333, NV366 NV370, NV830, NV688	NV850	£2.80	NV8600.	NV8610
£64.50	NV688		£6.50	Ferguso	n
£64.50	NV777, NV788 . NV8600, NV861	0	£4.70		16, 3V22
£67.50				3V23	30
	NV230, NV430,	NV870	£3.20	3V35,3V	36, 3V38, 3V39
£59.90	NV870, NV810.		£2.80	Sanyo	
£59.90	Ferguson	20	00.00	VTC5000	VTC5150
£66.90	3V00,3V16,3V2 3V23	2	£6.50 £3.90	VTC9300	, VTC5400
£59.90	3V29 3V30		£4.90	Sony	
	3V35, 3V36, 3V3	38, 3V39	£2.90	SLC5, SL	C7
£69.90	Sanyo			SLC6	
£69.90 £62.00	VTC5000, VTC5 VTC5300, VTC5			SL8000, 9	SL8080
£62.00	VTC9300	400	£4.50	Sharp VC7300	VC7700, VC7780
£62.00	Sonv				•07700, •07780
	SLC5, SLC7		£6.50	VC9100, 1	VC9300, VC9500
	SLC6		£7.50		C383, VC386
£39.90	SL8000, SL8080 Sharp		£6.50	Hitachi	/75500
£39.90 £39.90	VC7300, VC770	0 VC7750	\$6.50	VT8000, V	/T5500 /T8300, VT8500
135.50	VC8300		P6 50	VT9300, \	/T9500, VT9700
£49.50	VC9100, VC930 VC381, VC383, V	0, VC9500	£6.50	VT11E, V	T14E, VT17E, VT19.
£49.50	VC381, VC383, V Hitachi	VC386	£6.50		
£49.50 £54.50 £54.50	VT5000 VT5500		06.50	Akai VS9700	
£54.50	VT5000, VT5500 VT8000, VT8300), VT8500	£2.90	VS2, VS3	, VS4, VS5
	VT9300, VT9500 VT11E, VT14E, V VT33E), VT9700	£3.30	V\$9300, V	/S9500, VS9800
£59.90 £69.90	VT11E, VT14E, V	VT17E, VT19	£6.50	Many othe	ers available
£59.90	Akai				SENSOR LAMP
£59.90	V\$9700 V\$2, V\$3, V\$4, V V\$9300, V\$9500		26.50	All Panaso	onic
	VS2, VS3, VS4, V	√S5	£4.90	All Fergus	on/JVC
£49.50	V\$9300, V\$9500), VS9700	££.50	Sharp VC	9300 etc
£49.50	Many others ava	liadie		Amstrad 7	'000
£49.50 £49.50				All Hitachi	
£45.50	CREDIT CA				SENSOR L.E.D.
£54.60	ORDERS BY		Acces	All Ferrus	onic. on/JVC
£49.50	TELEPHONE			All Hitachi	
	RECEIVED E	37			END SENSORS
£44.00 £42.90	4 PM. ARE DESPATCHI		BARCLAYCARD	Hitachi VT	64E
ted.	SAME DAY		VISA		REEL MOTORS
1000.	UNITE DAT	î		Sham VC	9300, VC381 etc
				Amstrad/5	Saisho etc.
				Panasonio	NV333, NV366
				Sanyo V II	C5000, 5300, 5400 NV7000, 7200
					: NV7000, 7200
	HUNDREDS OF V			1 anasonia	
INC. PLAY	DLERS, CLUTCH	ES, MOTORS			DRUM MOTOR
INC. PLAY		ES, MOTORS		Ferguson/	JVC 3V00, 3V22, etc.
INC. PLAY Service	DLERS, CLUTCH	ES, MOTORS ION BANDS,		Ferguson/ Sharp VC	JVC 3V00, 3V22, etc. 7300, VC7700 3300.
INC. PLAY SERVICE BELTS	DLERS, CLUTCH MANUALS, TENSI AUDIO/CONTROL	ES, MOTORS ION BANDS, HEADS,		Ferguson/ Sharp VC	JVC 3V00, 3V22, etc. 7300, VC7700 3300.
INC. PLAY SERVICE BELTS ALIGNME	IDLERS, CLUTCH MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T	ES, MOTORS ION BANDS, HEADS, APES ETC.		Ferguson/ Sharp VC: Sharp VC8 Hitachi VT	JVC 3V00, 3V22, etc. 7300, VC7700 3300 5000 CAPSTAN MOTO
INC. PLAY SERVICE BELTS ALIGNME **SPEC	IDLERS, CLUTCH MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T HAL ORDER FACI	ES, MOTORS ION BANDS, HEADS, APES ETC. ILITIES**		Ferguson/ Sharp VC: Sharp VC: Hitachi VT Sharp VC:	JVC 3V00, 3V22, etc. 7300, VC7700 3300 5000 CAPSTAN MOTO 3300
INC. PLAY SERVICE BELTS ALIGNME **SPEC	IDLERS, CLUTCH MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T	ES, MOTORS ION BANDS, HEADS, APES ETC. ILITIES** EMS**	S,	Ferguson/ Sharp VC: Sharp VC: Hitachi VT Sharp VC: Sharp VC: Sharp VC:	JVC 3V00, 3V22, etc. 7300, VC7700 3300 5000 CAPSTAN MOTO 3300 7300 VC7700
INC. PLAY SERVICE BELTS ALIGNME **SPEC **FO	IDLERS, CLUTCH MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T HAL ORDER FACI	ES, MOTORS ION BANDS, HEADS, APES ETC. ILITIES** EMS**	LARGE RANGE	Ferguson/ Sharp VC: Sharp VC: Hitachi VT Sharp VC: Sharp VC: Sharp VC:	JVC 3V00, 3V22, etc. 7300, VC7700 3300 5000 CAPSTAN MOTO 3300 7300 VC7700
INC. PLAY SERVICE BELTS ALIGNME **SPEC **FO PINC	IDLERS, CLUTCH MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T CIAL ORDER FACI R NON-STOCK IT	ES, MOTORS ION BANDS, HEADS, APES ETC. ILITIES** EMS**	LARGE RANGE	Ferguson/ Sharp VC Sharp VC4 Hitachi VT Sharp VC2 Sharp VC2 Sharp VC7 Ferguson/ Ferguson/	JVC 3V00, 3V22, etc. 7300, VC7700 5000 CAPSTAN MOTO 3300, VC7700 JVC 3V00, 3V16, 3V2 JVC 3V29, 3V30 JVC 3V29, 3V30
INC. PLAY SERVICE I BELTS ALIGNME **SPEC **FO PINCI 2000, NV2010	IDLERS, CLUTCHI MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T IAL ORDER FACI R NON-STOCK IT H ROLLERS	ES, MOTORS ION BANDS, HEADS, APES ETC. ILITIES** EMS**	LARGE RANGE OF IC'S & SCMI-	Ferguson/ Sharp VC2 Sharp VC2 Hitachi VT Sharp VC2 Sharp VC2 Sharp VC2 Ferguson/ Ferguson/ Ferguson/ Hitachi VT	JVC 3V00, 3V22, etc. 7300, VC7700 5000 CAPSTAN MOTO 3300, 7300, VC7700 JVC 3V00, 3V16, 3V2 JVC 3V03, 3V16, 3V2 JVC 3V35, 3V36, etc. 5000
INC. PLAY SERVICE BELTS ALIGNME **SPEC **FO PINC 2000, NV2010 333, NV366, N	IDLERS, CLUTCH MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T IAL ORDER FACI R NON-STOCK IT H ROLLERS 0, NV7000, NV7200 V370, NV430.	ES, MOTORS ION BANDS, HEADS, APES ETC. ILITIES** EMS**	LARGE RANGE	Ferguson/ Sharp VC2 Sharp VC2 Hitachi VT Sharp VC2 Sharp VC2 Sharp VC2 Ferguson/ Ferguson/ Ferguson/ Hitachi VT	JVC 3V00, 3V22, etc. 7300, VC7700 5000 CAPSTAN MOTO 3300, 7300, VC7700 JVC 3V00, 3V16, 3V2 JVC 3V03, 3V16, 3V2 JVC 3V35, 3V36, etc. 5000
INC. PLAY SERVICE BELTS ALIGNME **SPE(**FO <i>PINCI</i> 730, NV2010 730,	IDLERS, CLUTCHI WANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T IAL ORDER FACI R NON-STOCK IT H ROLLERS), NV7000, NV7200 V370, NV430.	ES, MOTORS ION BANDS, HEADS, APES ETC. ILITIES** EMS**	LARGE RANGE OF IC's & SEMI- CONDUCTORS	Ferguson/ Sharp VC2 Sharp VC2 Hitachi VT Sharp VC2 Sharp VC2 Ferguson/ Ferguson/ Ferguson/ Hitachi VT Hitachi VT	JVC 3V00, 3V22, etc. 7000, VC7700 3300 CAPSTAN MOTO 3300 7300, VC7700 JVC 3V00, 3V16, 3V2 JVC 3V03, 3V36, etc. 5000 8000, 6500, etc. 3300, 9500, etc.
INC. PLAY SERVICE I BELTS ALIGNME **SPE(**FO PINCI 7300, NV2010 (333, NV366, N 730. rauson/JV	IDLERS, CLUTCHI MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T IAL ORDER FACI R NON-STOCK IT H ROLLERS 0, NV7000, NV7200 V370, NV430 C	ES, MOTOR: ION BANDS, HEADS, APES ETC. LLITIES** EMS** £4.95 £4.95 £4.95 £7.95	LARGE RANGE OF IC'S & SEMI- CONDUCTORS AVAILABLE FOR TV. AUDIO &	Ferguson/ Sharp VC: Sharp VC: Hitachi VT Sharp VC: Ferguson/ Ferguson/ Ferguson/ Hitachi VT Hitachi VT Hitachi VT	JVC 3V00, 3V22, etc. 7300, VC7700 5000 CAPSTAN MOTO 3300, 7300, VC7700 JVC 3V00, 3V16, 3V2 JVC 3V35, 3V36, etc. 5000 8000, 8500, etc. 3300, 9500, etc. 11, VT14, VT17.
INC. PLAY SERVICE I BELTS ALIGNME **SPE(**FO PINCI 7300, NV2010 (333, NV366, N 730. rauson/JV	IDLERS, CLUTCHI MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T IAL ORDER FACI R NON-STOCK IT H ROLLERS 0, NV7000, NV7200 V370, NV430 C	ES, MOTOR: ION BANDS, HEADS, APES ETC. LLITIES** EMS** £4.95 £4.95 £4.95 £7.95	LARGE RANGE OF IC's & SEMI- CONDUCTORS AVAILABLE FOR TV.	Ferguson/ Sharp VC: Sharp VC: Hitachi VT Sharp VC: Ferguson/ Ferguson/ Hitachi VT Hitachi VT Hitachi VT Hitachi VT Akai VS1- ¹	8000, 8500, etc. 9300, 9500, etc. 11, VT14, VT17 27
INC. PLAY SERVICE I BELTS ALIGNME **SPE(**FO <i>PINC</i> '2000, NV2010 '333, NV266, N '730 rguson/JV 00, 3V16, 3V22 rguson/JV	IDLERS, CLUTCHI MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T IAL ORDER FACI R NON-STOCK IT H ROLLERS D, NV7000, NV7200 V370, NV430. C 3V233V24 D HB3660, HB2200	ES, MOTOR: ION BANDS, HEADS, APES ETC. LITIES** EMS** EMS** £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95	LARGE RANGE OF IC'S & SEMI- CONDUCTORS AVAILABLE FOR TV. AUDIO &	Ferguson/ Sharp VC: Sharp VC: Hitachi VT Sharp VC: Sharp VC: Ferguson/ Ferguson/ Ferguson/ Hitachi VT Hitachi VT Hitachi VT Sony C5, (JVC 3V00, 3V22, etc. 7300, VC7700 5000 CAPSTAN MOTO 3300, 7300, VC7700 JVC 3V00, 3V16, 3V2 JVC 3V29, 3V30, etc. 5000 8000, 8500, etc. 11, VT14, VT17 7. V55
INC. PLAY SERVICE I BELTS ALIGNME **SPE(**FO <i>PINC</i> '2000, NV2010 '333, NV266, N '730 rguson/JV 00, 3V16, 3V22 rguson/JV	IDLERS, CLUTCHI MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T IAL ORDER FACI R NON-STOCK IT H ROLLERS D, NV7000, NV7200 V370, NV430. C 3V233V24 UHB3660, HB2200	ES, MOTOR: ION BANDS, HEADS, APES ETC. LITIES** EMS** EMS** £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95	LARGE RANGE OF IC'S & SEMI- CONDUCTORS AVAILABLE FOR TV. AUDIO &	Ferguson/ Sharp VC3 Sharp VC4 Hitachi VT Sharp VC2 Sharp VC2 Sharp VC2 Ferguson/ Ferguson/ Ferguson/ Hitachi VT Hitachi VT Hitachi VT Sony C5.(Akai VS1-1 Many, mar	JVC 3V00, 3V22, etc. 7300, VC7700 5000 CAPSTAN MOTO 3300, 7300, VC7700 JVC 3V00, 3V16, 3V2 JVC 3V29, 3V30, etc. 5000 8000, 8500, etc. 11, VT14, VT17 7. V55
INC. PLAY SERVICE (BELTS ALIGNME **SPEC PINCI 7330, NV366, N 730, 3V16, 3V22 3330, HR336, 3V36	IDLERS, CLUTCHI MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T IAL ORDER FACI R NON-STOCK IT H ROLLERS 0, NV7000, NV7200 V370, NV430 C	ES, MOTOR: ION BANDS, HEADS, APES ETC. LITIES** EMS** EMS** EMS** E4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95	LARGE RANGE OF IC'S & SEMI- CONDUCTORS AVAILABLE FOR TV. AUDIO & VIOEO Panasonic	Ferguson/ Sharp VC: Sharp VC: Sharp VC: Sharp VC: Ferguson/ Ferguson/ Ferguson/ Hitachi VT Hitachi VT Hitachi VT Many, mar IDLE	JVC 3V00, 3V22, etc. 7300, VC7700 CAPSTAN MOTO 3300. CAPSTAN MOTO 3300, VC7700 JVC 3V00, 3V16, 3V2 JVC 3V29, 3V30, JVC 3V29, JVC
INC. PLAY SERVICE I BELTS ALIGNME **SPEC **FO PINCI 7300, NV2011 (333, NV366, N 730, 3V16, 3V22 (3300, HR336, N 730, 3V16, 3V22 (3300, HR336, SV36 735, 3V36, 3V36 (59100, VTC93	IDLERS, CLUTCHI MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T IAL ORDER FACI R NON-STOCK IT H ROLLERS 0, NV7000, NV7200 V370, NV430 C 2, 3V23 3V24 0, HR3660, HR2200 0, HR7300 1, 3V39 HRD 120 00	ES, MOTOR: ION BANDS, HEADS, APES ETC. ILITIES** EMS** EMS** EA95 E4.95 E4.95 E4.95 E4.95 E4.95 E4.95	CARGE RANGE OF IC'S & SEMI- CONDUCTORS AVAILABLE FOR TV. AUDIO & VIOEO Panasonic NV22000, NV220	Ferguson/ Sharp VC: Sharp VC: Hilachi VT Gharp VC: Ferguson/ Ferguson/ Hitachi VT Hitachi VT Hitachi VS1-1 Many, mar IDLEI	JVC 3V00, 3V22, etc. 7300, VC7700 5000 CAPSTAN MOTO 3300, 7300, VC7700 JVC 3V00, 3V16, 3V2 JVC 3V30, 3V36, etc. 5000 8000, 8500, etc. 3300, 9500, etc. 3300, 9500, etc. 11, VT14, VT17 77 75 75 77 77 77 77 77 77 7
INC. PLAY SERVICE I BELTS ALIGNME **SPEC PINCI 730. rguson/JV2 03, 3V16, 3V22 3300, HR336 29, 3V30, HR336 29, 3V30, HR336 35, 3V36, 3V38 ryyo C9100, VTC93 C5000, VTC93	IDLERS, CLUTCHI MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T CIAL ORDER FACI R NON-STOCK IT H ROLLERS), NV7000, NV7200 V370, NV430. C 2, 3V23 3V24 , 1H3660, HR2200 200, HR7300 2, 3V39 HRD120 00 50, VTCS300,	ES, MOTOR: ION BANDS, HEADS, APES ETC. LITIES** EMS** EMS** EA.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95	LARGE RANGE OF IC'S & SEMI- CONDUCTORS AVAILABLE FOR TV. AUDIO & VIOEO Panasonic NV2000, NV270	Ferguson/ Sharp VC: Sharp VC: Sharp VC: Sharp VC: Ferguson/ Ferguson/ Ferguson/ Hitachi VT Hitachi VT Hitachi VT Many, mar IDLE 10	JVC 3V00, 3V22, etc. 7300, VC7700 CAPSTAN MOTO 3300. CAPSTAN MOTO 3300, VC7700 JVC 3V00, 3V16, 3V2 JVC 3V29, 3V30, etc. 3000, 9500, etc. 11, VT14, VT17 7. 7. 7. 7. 7. 7. 87 WHEELS (Genuine) (Genuine)
INC. PLAY SERVICE I BELTS ALIGNME **SPEC **FO PINCC 00, NV2010 (333, NV366, N 730, NV366, N 730, NV36, SV36 (29, 3V30, HR7, 35, 3V36, 3V36 (29, 3V30, HR7, 35, 3V36, 3V36 (20, 3V36, NC2, 35, 3V36, NC2, 35, 3V36, 3V36 (20, 3V36, NC2, 35, 3V36, 3V36 (20, 3V36, NC2, 35, 30, 30, NC2, 35, 30, 30, 30, NC2, 35	IDLERS, CLUTCHI MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T IAL ORDER FACI R NON-STOCK IT H ROLLERS 0, NV7000, NV7200 V370, NV430 C 2, 3V23 3V24 0, HR3660, HR2200 0, HR7300 1, 3V39 HRD 120 00	ES, MOTOR: ION BANDS, HEADS, APES ETC. ILITIES** EMS** EMS** £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95	CLARGE RANGE OF IC's & SEMI- CONDUCTORS AVAILABLE FOR TV. AUDIO & VIOEO Panasonic NV22000, NV22C NV22000, NV22C	Ferguson/ Sharp VC: Sharp VC: Hilachi VT Gharp VC: Ferguson/ Ferguson/ Ferguson/ Hitachi VT Hitachi VT Hitachi VS1-1 Many, mar IDLEI	JVC 3V00, 3V22, etc. 7300, VC7700 5000 CAPSTAN MOTO 3300, 7300, VC7700 JVC 3V00, 3V16, 3V2 JVC 3V30, 3V36, etc. 5000 8000, 6500, etc. 9300, 9500, etc. 11, VT14, VT17 7, 75 10, VT14, VT17 77 75 87 WHEELS (Genuine) (Genuine) (Genuine)
INC. PLAY SERVICE BELTS ALIGNME *SPEC PINCC (2000, NV2010 (333, NV366, N 730, NV366, N 740, N 740, N 740, N 740, N 740, N 740, N	IDLERS, CLUTCHI MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T IDL ORDER FACI R NON-STOCK IT H ROLLERS), NV7000, NV7200 V370, NV430. C 2, 3V233V24 2, HR3660, HR2200 200, HR7300 200, HR7300 200, HR7300 200, VTCS300,	ES, MOTOR: ION BANDS, HEADS, APES ETC. ILITIES** EMS** EMS** E4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95 £4.95	LARGE RANGE OF IC'S & SEMI- CONDUCTORS AVAILABLE FOR TV. AUDIO & VIOEO Panasonic NV2000, NV22 NV330, NV230	Ferguson/ Sharp VC: Sharp VC: Sharp VC: Sharp VC: Ferguson/ Ferguson/ Ferguson/ Hitachi VT Hitachi VT Hitachi VT Many, mar IDLE 10	JVC 3V00, 3V22, etc. 7000, VC7700
INC. PLAY SERVICE BELTS ALIGNME **SPEC **FO PINCI (2000, NV2010 (333, NV366, N 730, NV366, N 740, NV366, N 740, NV366, N 750, N	IDLERS, CLUTCHI MANUALS, TENSI AUDIO/CONTROL NT TOOLS AND T CIAL ORDER FACI R NON-STOCK IT H ROLLERS), NV7000, NV7200 V370, NV430. C 2, 3V23 3V24 , 1H3660, HR2200 200, HR7300 2, 3V39 HRD120 00 50, VTCS300,	ES, MOTOR: ION BANDS, HEADS, APES ETC. ILITIES** EMS** EMS** E4.95 £4.95	LARGE RANGE OF IC'S & SEMI- CONDUCTORS AVAILABLE FOR TV. AUDIO & VIOEO Panasonic NV2000, NV22 NV330, NV230	Ferguson/ Sharp VC: Sharp VC: Hitachi VT Gharp VC: Ferguson/ Ferguson/ Ferguson/ Hitachi VT Hitachi VT Hitachi VT Hitachi VS1-1 Many, mar IDLEI 10.000.	JVC 3V00, 3V22, etc. 7300, VC7700 5000 CAPSTAN MOTO 3300, 7300, VC7700 JVC 3V00, 3V16, 3V2 JVC 3V30, 3V36, etc. 5000 8000, 6500, etc. 9300, 9500, etc. 11, VT14, VT17 7, 75 10, VT14, VT17 77 75 87 WHEELS (Genuine) (Genuine) (Genuine)

IDLER WREELS	
Panasonic	
NV2000, NV2010	
NV7000, NV7200	£2.90
NV333, N∀366	£2.90
NV370, NV230, NV430 (Genuine)	£4.50
NV777, NV788	£4.50
NV730	£4.50
Ferguson/JVC	
3V00, 3V16, 3V22 (Large clutch)	£5.95
3V00, 3V16, 3V22 (Small clutch)	£6.95
3V29, 3V30, HR7200, HR7300	
3V35, 3V36, 3V38, 3V39, HRD120	£3.90
Sanyo	
VTC9100, VTC9300	£1.90
VTC5000 Reel drive pulley	£6.50
VTCM10 Feel drive pulley	09.93
Sony	
SLC5, SLC7 Rewind kit	£4.95
SLC6	£4.95
Sharp	
VC9100, VC9300, VC9500 (Genuine)	£3.90
VC381, VC383, VC386 (Genuine)	£3.90
VC482, VC483, VC581 (also Saisho) (Genuine)	£3.90
VC482 etc. (Equivalent)	£2.98
VC9300, 381 etc. (Equivalent)	£2.98
Hitachi	
VT8000, VT8300, VT8500	£4.72
VT9300, VT9500, VT9700	£4.75
VT11E, VT14E, VT17E, VT19	£3.96
VT33, VT63, VT64, VT65	£3.96
Akai	
VS2, VS3, VS4, VS5	£4.50
Fisher	
FVHP615, FVHP710, FVHP725, etc.	£6.90
We also carry all play idlers and clutches etc. for r	nodels
listed plus many more.	

FOR TV AND VIDEO	
THIS MONTH'S SPECIALS	WE CARRY HUNDREDS OF INC. PLAY IDLERS, CLUTC SERVICE MANUALS, TEN BELTS AUDIO/CONTRO ALIGNMENT TOOLS AND **SPECIAL ORDER FAI **FOR NON-STOCK
STK 5481 CHIP £5.22 PLUS VAT	PINCH ROLLERS Panasonic NV2000, NV2010, NV7000, NV7200 NV333, NV366, NV370, NV430 NV730
HEADS 3HSS(V) FERGUSON & JVC	Ferguson/JVC 3V03, 3V16, 3V22, 3V23 3V24 HR3300, HR3560, HR3660, HR220 3V29, 3V30, HR7200, HR7300 3V35, 3V36, 3V38, 3V39 HRD120
$ \frac{3}{3} \frac{3}{29} - \frac{3}{29} \frac{3}{29} \frac{3}{29} \frac{3}{29} - \frac{3}{29} \frac{3}{2$	Sanyo VTC\$100, VTC9300 VTC5000, VTC5150, VTC5300, VTC5400 SLC5, SLC7 SLC6
3HSS (N) PANASONIC NV2000 – NV2010 – NV3000	SL8000, SL8080
NV7000 - NV7200 - NV333 BOTH AT £14.50 + VAT	Hitachi V15000, V15500 V18000, V1300, V18500 V19300, V19500, V19700 V111E, V114E, V117E, V119 V133E
ADD 70p POST & PACKING	Akai VS9700 VS2, VS3, VS4, VS5 VS9300, VS9500, VS9700
24HR ANSWERING SERVICE FOR ORDERS PLACE Please add 70p post & packing and then add 15	ESTON, NOTTINGHAM NG9 2ND 602-431097 D AFTER 5.30 p.m. % VAT to total
OFFICIAL ORDERS ACCEPTED FROM SCHOOLS, COLLEGES, ETC ALL PRICE ENQUIRIES SHOULD BE ACCOMPANIED BY STAM	E EXPORT ENQUIRIES WELCOME. PED ADDRESSED ENVELOPE

LARGE RANGE OF REMOTE CONTROL'S

£3.50 £3.00 £3.00 £3.95

£3.50 £2.90 £3.50 £2.90

£1.00 £2.50 £4.25

£3.60 £4.95 £4.25

£3.50 £3.90 £3.90 £3.90 £3.90

£4.50 £1.50 £1.50 £3.90 £3.90

£3.90 £3.95 £3.50

£1.80 £0.65 £2.90 £1.80 £2.30 £1.80

£2.90 £2.90

£5.75

£18.20 £18.20 £16.80 £9.90 £19.80


£29.90 £26.40 £26.40 £24.80

£39.90 £29.30 £24.75 £34.50 £25.80 £25.80 £34.50

£34.50 £34.50 £28.80 £42.90 £29.90

£1.20 each



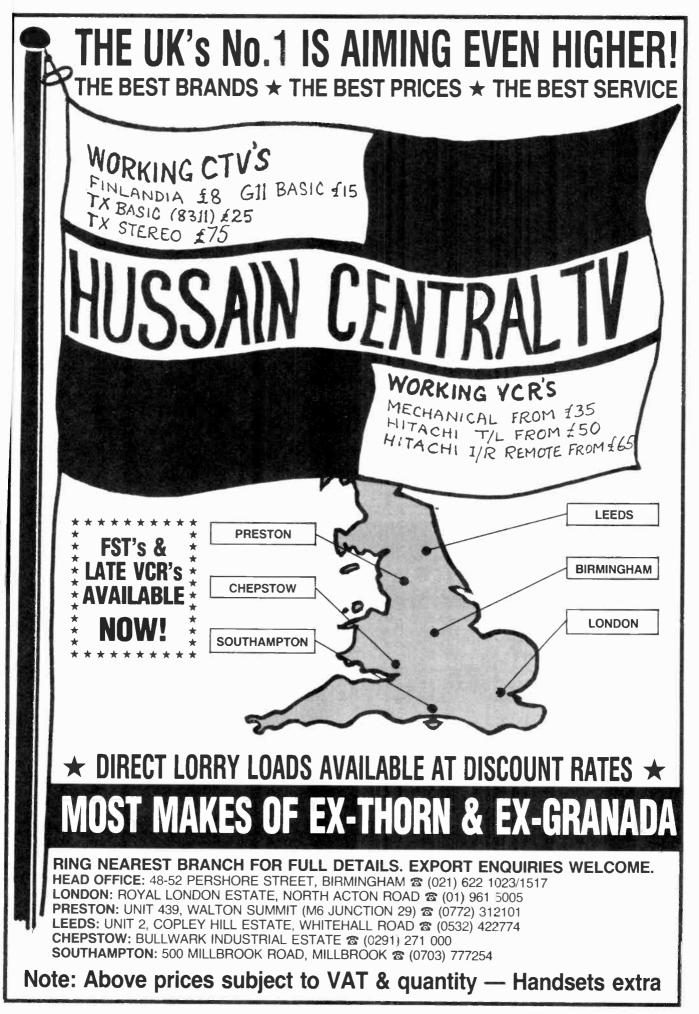

★ TRADE WAREHOUSE ★



TV'S AND VIDEOS

FULLY RE-CONDITIONED EX-RENTAL READY FOR RETAIL OUTLETS



GOOD VARIANTS; BASIC; TX9s; TX10s; NON-TEXT; TEXT; STEREO SUPERSOUND; PORTABLES; ETC.

VIDEOS

UNBEATABLE

PRICES

3V23s; 3V30s; 8941/8944; 3V32/8942; NON-THORN; THORN; REMOTE CONTROL; MECHANICAL; ETC.

***** GOOD DISCOUNT FOR QUANTITIES *****

CONTACT

YORKSHIRE KEN COXON TVS

UNIT 10, SHAW LANE INDUSTRIAL ESTATE, DONCASTER DN2 4SE Telephone: (0302) 342932

PAGERS

ENGINEERS DON'T

LOSE YOUR MESSAGES

WHILE ON THE MOVE

WE SUPPLY ACTIVATED

PAGERS FROM

TO BUY =£99 + VAT TO LEASE = £10 + VAT

p. month

Air service charge: £4.95 +

VAT p. month

NATIONWIDE COVERAGE

SIEMENS FAX

FROM £650 + VAT

(16 Grey Levels, Portable,

and Fotocopy facility)

If interested, please write to:

458A WEST GREEN ROAD,

LONDON N15 3PT.

- 0

TONE

PAGER

-0-

NUMBER

PAGER

VIEWVISION

WORD

PAGER

0-

VOICE

MESSAGING

EX-RENTAL

TVs & VIDEOS

Competitive

Prices

TX10, TX9, STEREO

TEXT, 3V29, 3V30, 3V31, etc

-0-

WE CAN SUPPLY

YOU TRADE PRICED

COMPUTERS &

ACCESSORIES

ALTAI AERIAL AMPs

SINGLE OUTPUT

£5.50+VAT

TWO OUTPUTS

£6.80+VAT

(With mains on/off

switch, 7dB Gain

470-860 MHz UHF)

TEL:

01-365 1620

Mobile:

0836 329886

NORTH EAST DONNELLY'S TVs

THE CHAPEL FRONT STREET, TANTOBIE COUNTY DURHAM DH9 9RE Telephone: (0207) 282435


CENTREVISION SLOPER RD, LECKWITH, CARDIFF PHONE 0222 344754

If you buy new televisions & Video's, **SAVE UP TO £70** and buy boxed, guaranteed seconds.


Quality ex-rental TV & video at GREAT DISCOUNTS, try before you buy.

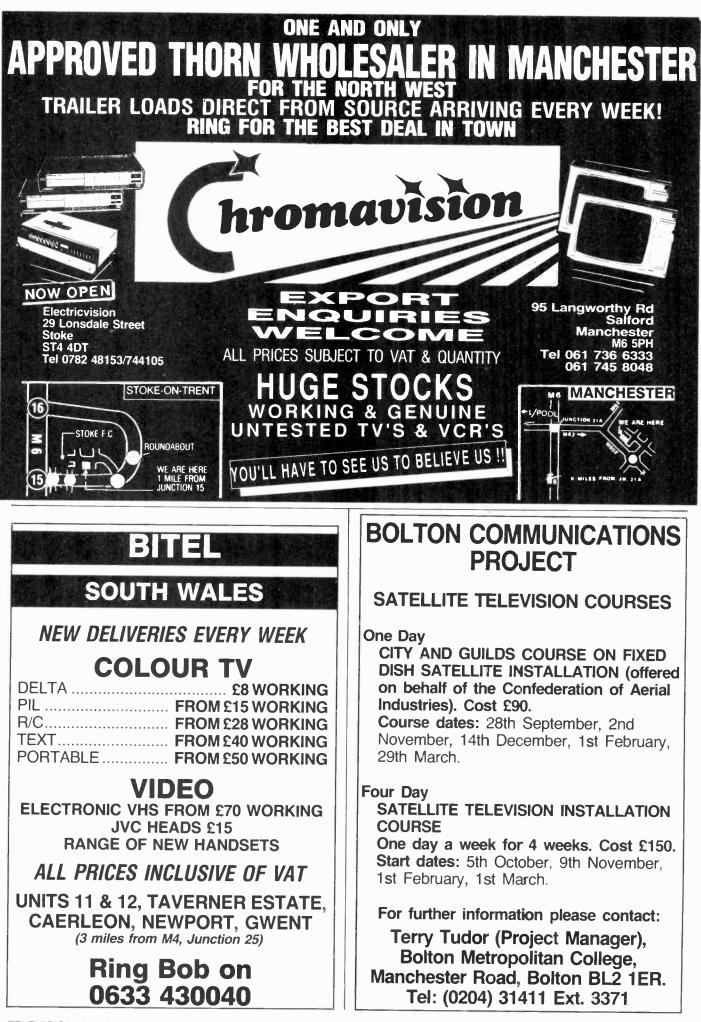Phone for our latest price list with all our monthly up to the date bargains.





TELEVISION OCTOBER 1989

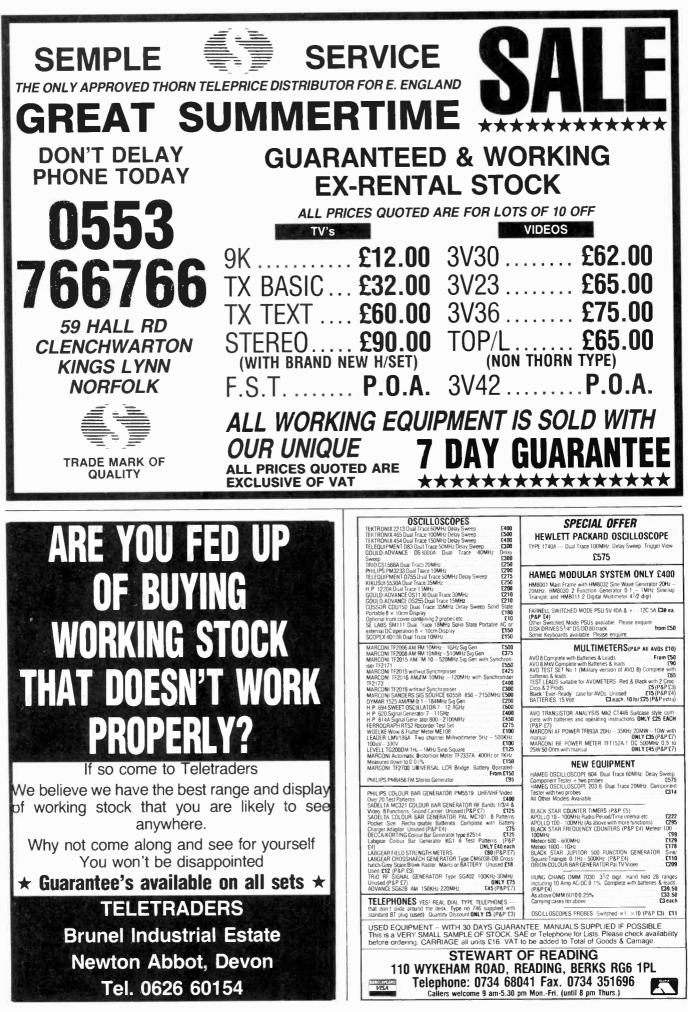

Start a subscription to	
TELEV	SION
The most convenient way regular copy of <i>Television</i> i Just complete the order for No postage stamp is require enclosed in an o Annual subscription rates: Uk surface ma	s to order on subscription. m below, detach and post. d if posted in the UK unless outer envelope. K and Eire, £20; overseas
enter my subscription to Television as dicated below.	 Charge my Access/Visa/American Express/ Diners Club card. (Please delete as appropriate).
EASE USE BLOCK CAPITALS) Idress	
	Signature
Postcode	Card valid from to
ck one:	Name and address of cardholder
My cheque for f is enclosed made payable to Television . (Please enclose this card with your cheque in an outer envelope which you have stamped and addressed as overleaf.)	Name
	(PLEASE USE BLOCK CAPITALS)
	Address
] Invoice me later for £	Destendo
ode: 08	Postcode

No stamp required if posted in th U.K.

TELEVISION

FREEPOST 1061 Haywards Heath RH16 3ZA





TELEVISION OCTOBER 1989





ELIMITED ELECTRONICS of their new premises at **TRADING ESTATE,** (JUST OFF A6) (050) 981-6580

VHS videos from £25

Knock out prices on colour TVs: Ferguson, Phi ips, Pye, from £8. Mono £1.

G11 text working £30, Ferguson TX Text only £55 with Text £65 with hand set


Videos available

UIPMENT PANELS

Line	Power	Frame
scan 18 20 20	17 17 3	14 X 14.00
20 But +	20 VAT (Panels Only)	11.50

MANCHESTER

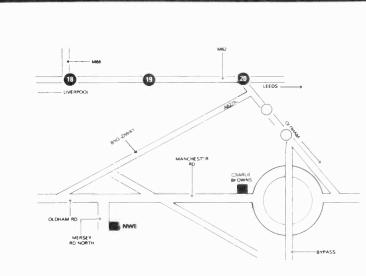MERSEY ROAD NORTH, INDUSTRIAL ESTATE, FAILSWORTH



Tel

(061-683) 4612

NOW FOR PRICES OR WILL BE DELIGHTED

OPEN 6 DAYS

SAT 9-5.30

Sonic TV Distributors

WE HAVE THE BIGGEST GENUINE UNTESTED RANGE OF THE SET AT VERY, VERY LOW PRICES

THOUSANDS OF WORKING SETS READY FOR SHOWROOM

WORKING VIDEOS AT UNBEATABLE PRICES

ELECTRONICS, WORKING VIDEOS FROM £50

COME DOWN — THE PRICE IS RIGHT

BIRMINGHAM Tel: 021-565-1727 Fax: 021-555-5367 SONIC HOUSE ABBERLEY STREET SMETHWICK, BIRMINGHAM B66 2QU

5 MINUTES DRIVE FROM J1 & 2 ON M5

PRESTON Tel: 0772-655011 Telex: 0902-333199 UNIT 34 ROMAN WAY LONGRIDE ROAD, PRESTON PR2 5BB

10 MINUTES DRIVE FROM J31 ON M6

EXPORT ENQUIRIES WELCOME BULK ORDERS ONLY ALL PRICES ARE SUBJECT TO 15% VAT

& BASED ON QUANTITY







FINEST QUALITY LOWEST PRICES SPECIAL DISCOUNTS FOR BULK BUYERS

2 YEAR GUARANTEE, 4 YEAR OPTIONAL

ALL MAKES INC. SONY

NATIONWIDE DELIVERY

PHONE NOW FOR FREE LISTS SHERWOOD TUBES LTD 60A PEVERIL STREET, NOTTINGHAM NG7 4AH. Tel. 0602 786896

NEW PRODUCT !!!

HOW MANY WASTED HOURS HAVE YOU SPENT ON SERVICING?

E.C.S. OFFERS YOU A COMPLETE INDEX OF EVERY TV AND VIDEO FAULT LISTED IN TEN YEARS OF TELEVISION MAGAZINE.

INDEX'S ARE ALPHABETICALLY LISTED BY MAKE, MODEL, FAULT AND REFERENCE AND ARE NOW AVAILABLE FOR JUST

£7.50 FOR TELEVISION FAULTS £7.50 FOR VIDEO FAULTS OR £15.00 FOR BOTH SETS COMPLETE WITH PROTECTIVE RING BINDER

REGULAR UPDATES ARE ALSO AVAILABLE, BUT ONE OF THE ABOVE INDEX'S MUST BE PURCHASED IN ORDER TO QUALIFY FOR THIS SERVICE.

To secure your order please make Cheques/Postal Orders payable to:



and send to:

UNITS 3-4 KINGSLAND BUILDINGS, BOROUGH ROAD, BIRKENHEAD, MERSEYSIDE L42 9NB.

PLEASE ADD £1.50 PER ORDER FOR P+P.

GENERAL FACTORS

Working colour TV's from Basic to Text, all on working display with good **Cabinets – Ready** for sale or rent.

PYE – PHILIPS G11, KT-3, K-30 – REDIFFUSION Mark 3-4, GRUNDIG, TOSHIBA, ITT, etc.

Direct loads, various sizes, mixed types. You collect. Ask for details.

USED VIDEO & TV SPARES

Spares for Video and TV available

Phone for details of current stock, if we don't have it, we can probably get it for you. **SPECIAL** spares for Philips VHS.

All new stock as used spares prices, phone us.

VIDEOS VIDEOS VIDEOS

VHS Beta 2000 System from £15.00

New B, grade faulty stock VHS VCR's. Ask for details and prices. All prices plus VAT,

Union St., off Sepulchre Gate West. Doncaster South Yorks DN1 3AE

10 am-5 pm MON-FRI. Tel 0302-349583 24hr Ansaphone Fax 0302-349510 Mobile 0836-368878

21/2 miles from A1M for M18 - M1

NEWCASTLE upon **TYNE** Solid State 2110 PHILIPS GEC G11 PHILIPS GEC Starline KT3 K30 Basic DECCA 80 or 100 series PHILIPS FINLANDIA PHILIPS K30 Remote Basic **FINLANDIA** Remote PHILIPS K30 Text Trade workers always available Loads direct from source **Trimline Basic** ERGUSON TX Basic ITT FERGUSON TX9 ITT CVC30 Text FERGUSON TX10 Text GRUNDIG Basic DORIC Mkiv DORIC Mkiii FINLANDIA Basic Text Basic Text **Delivery and Discount on Quantity** VIDEOS FERGUSON 3V29 FERGUSON 3V30 NV333 PANASONIC HITACHI VT8300 COLOUR PORTABLES P.V.S. ALWAYS AVAILABLE 35 Nunsmoor Road, Fenham, Newcastle upon Tyne Phone (091) 272 2303





MIDLAND TELEVISION

WORKING C.T.V.

Philips KT3 & K30	£15
Philips KT3 & K30 Text	£56
Bush T20 & T26	£15
Grundig 7400 from	£25
Toshiba	
Sanyo	

WORKING C.T.V. **FERGUSON**

3V23	£65
3V30-8940	
3V31	
3V32 L/P	
3V35	£78
3V43 L/P Hi/Fi	
3V65	£100
DUILIDO	
PHILIPS	

THORN

8800	26
9000	£15
9600 R/C	£15
9900 R/C	£20
TX9&TX10Basic	£27
TX9&TX10 R/C	£33
TX9&TX10Text	£56
Stereo Text	£95
FST Text	£95
FST Stereo Text £	105

3V65	
PHILIPS	
VR6462	£78
VR6560	
VR6740	
VR6760	£100

ALL PRICES

SUBJECT TO

VAT AT 15%

BARCLAYCARD

VISA

TOSHIBA

£33	
£56	V65
£95	V72 £100
£95	V75£100
£105	GRUNDIG VHS £78

0.65

2.00 2.65 2.38 2.65 2.65 2.65

0.48 0.75 0.65 0.95

2.16 3.31-5.71 3.44-3.75 3.75

4.44-4.86 3.00

9.50 2.50

Trunk Mounting Socket

Carrier Up to 50kg P+P for small light parcels

All prices Ouoted are plus VAT Carrier Up to 25kg 6.5t

12.95 POA

We specialise in working and guaranteed Thorn & Co-op stock. No customer too large or small. Our collection days are Wednesday, Thursday & Friday. Call Steve or Keith for stock availability. SPECIAL OFFER, free delivery in Leicestershire, Warwickshire, Cambridgeshire, Lincolnshire, Northamptonshire and London areas

> 4 MINS J22 M1 Nationwide Delivery Service Available

MARKET STREET, COALVILLE, LEICS

ALL R/C & TEXT SETS SUPPLIED WITH

J.W

U.H

Grou 10 Elemen 18 Elemen 18 Ele wit

Diamone Diamone Diamone Antiferer

Antiferen Set Top A

V.H

FM Omr FM Dipd FM 2 Ele FM 3 Ele FM 4 Ele FM 6 Ele

Loft S 12" x 1" 24" x 1"

16' x 2" 16g 20' x 2" 14g

Standard Repair Kit Smeter wire Coil Corner Plates 4/4" J Bolt & Nut 1/4" V Bolt & Nuts 2/2" V Bolt & Nuts

Must to Mast 1" to 2" Cross Clamp 142" to 2" Universal

HANDSETS	TEL: (0530) 8	310836 or 810837
	Station Road, Stechford Birmingham B33 8BB	021-784 8478
.F. Aerials	Coaxial Cable	Amplifiers
Dups A, B, CD & W nt Aerial 2.25 nt End Mount 3.47 ith Support Arm 4.38 IDC10 Boxed 6.95 IDC10B Roxed 9.95 IColour Grid 16.95 IColour Grid 16.95 tox XGR 20.50 tex XGR 20.50 tex XGR 20.50	Priced in 100 Metre Lengths all Cables can be supplied in 100 or 250 Metre Lengths Attenuation figers are Approx at 900 M1iz/100M. Volex Raydex CS5B 21dB Brown 13.50 CS6B 72dB Brown 13.95	Antilerence OX4 29.95 Wolsey Electronics The Full Range of Domestic & Professional Equipment is Available from Suck. The following List are the Most Popular Lines Set Back 12(1B) 9.99 Two Set 2 x 7(1B) 9.99
.F. Aerials Heavy Duty 7.95 le Heavy Duty 3.64 Heavy Duty 4.80 Heavy Duty 6.95 Heavy Duty 7.95 Heavy Duty 12.95 Stowed	CT125PE15dBDS 52.95	1w0.5et 2.100 7.50 Three Set 12.94x1B 7.50 Four Set 12.94x1B 16.90 O260/F2020B 16.90 Amerhysi VoldBmV 120.45 Amerhysi VoldBmV 124.45 J W Hardy communications 4 Way Amplifier 2dB 19.95 Silver 2xBB 4xdBmV 32.56 Silver 2xBB 4xdBmV 38.95 Booster 2xBB 54dBmV 39.50 19.50 19.50
Stand & Bracket	Cable Accessories	Splitters & T Units
Masts Alloy 16g 6.95 g 16.95 g 26.50	Cable Clips 5,6 & 7mm per 100 0.78 9mm Black per 100 0.95 11mm Black pet 100 1.05 Adhesive Tupe 2001 3/47 Black 0.32 10M Self Amalgamating 2.99 2.99	Wolsey Electronics Die-Cast T Unis 3.75-8.82 Die-Cast Splitters 7.14-10.08 Die-Cast Outdoor I.d 0.99 Indoor Lid 0.55 Line Terminator JSohn 0.40 Mun Splitters POA Mun Splitters 2.450

Altai In Door 2 Way 'Y' 3 to 6 Way Cable Connecto Coax Plug Alloy per 100 Coax Plug Alloy each Coax Cuppler per 50 Coax Cuppler each F Screw On Imm 12.95 0.17 5.95 **Chimney Lashing** 2 Way Resistive 2 Way Inductive 1.28 0.80 SAC Splitters 0.17 2 way 2 Way Inductive 3 Way Resistive Diplexer UHF/VHF Diplexer A/E Diplexer K/CD 0.06 0.14 0.12 0.22 Attenuator 3.6.12.18&24dB 1.00 2¹/2" V Bolt & Nuts. Chimney Brackets 6" x6" Pressed 6" x6" Welded 6" x9" Welded 7.9" Welded 7.9" ZWelded 13¹/2" Cradle Welded Double Lashing Pair Fly Leuds 0,68 0.98 1.48 2M Plug to Plug 2M Plug to Socket 9.60 9.66 **Coax** Outlet Plates Wall Fixings Altai Surface Socket Welded Wall Brackets ai Surface Twin ai Flush Wall Socket ai Flush Twin Alt Clamps Painted Galvanised Altai Flush Wall Socket Altai Flush Twin POIU Single Isolated POIU 12 to 38dB PO2U TV/FM Iso PO2U RSI Show Room PO2U RSI Show Room 6° Galvanised 6° Galvanised 6° Painted 7° Painted 7° K Painted 7° K Painted 7° K Galvanised 6" x 6" Garanie 6" x 9" Painted 9" x 9" Painted 12" T&K Painted 18" T&K Galvanised 14" T&K Galvanised 24" 1, &K Galvanised 16" Tripod Galvanised Drills, Plugs, Screws 1.48 2.26 3.75 4.75 7.45 5.35 Aerial to Mast Clamps 15mm to 2" Cross Clamp V Bolt & Nuts fl Must to Mast Clamps

LINEAGE 60p PER WORD (MINIMUM INSERTION £10). 5% DISCOUNT 6 INSERTIONS. 10% DISCOUNT 12 INSERTIONS. SEMI-DISPLAY £9.00 PER S.C. CM. (MINIMUM 2.5 CMS) £8.60 PER S.C. CM. 6 INSERTIONS, £8.10 PER S.C. CM. 12 INSERTIONS. ALL PRICES PLUS 15%. BOX NUMBER £2.00 EXTRA HEADING ADDRESS SIGNATURE

PLEASE DEBIT MY ACCESS/BARCLAYCARD NO.

MARCEANCARD VISA FOR INSERTIONS £ SEND TO: CLASSIFIED ADVERTISEMENT, TELEVISION ROOM 2331. IPC MAGAZINES LTD., KING'S REACH TOWER, STAMFORD STREET, LONDON SEI 9LS. Company registered in England. Registered No. 5326. **Registered Office: King's Reach Tower,** Stamford Street, London SE1 9LS. 10/89

SKILLED TECHNICIAN WANTED. Good pay rates apply. Jomill Enterprises, 173 Dalston Lane, E8. Tel. 01-533 2229

TWO PART TIME TV AND VIDEO experienced engineers required to work on all makes, suitable for recently retired or working engineers, hours to suit, excellent pay, London East area. AER VISION Tel. 01-539 5513

TV/AUDIO/VIDEO

FIELD & BENCH ENGINEERS We are a fast expanding electrical retailer. We need



TELEVISION OCTOBER 1989

Mast Clamps

0.30 0.65 0.12

0.75

1.60

Amstrad Satellite Now in Stock SRX100 £154.50 SRX200 £199.00



TRIPPING

Price £35.00





INDEX TO	
ADVERTISERS	
Admin Televisions	974 937 974 939 974
Asjaa meenauuta Audio Electronics Audio Visual Services A.Z. Electrics	905 956 965
Bell Radio Bi-Tel B.K. Electronics Bolton Metropolitan College Budget TV Bull, J & N Electrical Business Credit Limited	979 963 901 963 967 907 958
Campion Wholesale Ltd. Carter, John (Electrica) Ltd. Central TV & Video Wholesalers Ltd. Centrevision Chromavac Ltd. Chromavision Cleavision Celebourn Electronics Coxon, Ken, T.V 's Crewe Wholesale T V. C.T.V.	979 958 978 962 905 963 960 977 962 955 966
Display Electronics Ltd Donberg Electronics D.S. Distributors	955 977 971
Display Electronics Ltd. Donberg Electronics D.S. Distributors East Comwall Components East London Components. Economic Devices Electronic Components. Electronic Components. Electronic Mappiles.	
Flintdown Garma U.K. Ltd General Factors G. G. L. Components Glasgow Wholesale TV Grandata Ltd	977 906 973 904 950 900
FintGown Gamma U.K. Ltd General Factors G. G. L. Components Glasgow Wholesale TV Grandata Ltd	966 977 913 952 966 976 961
ICS	906 903 953 972
Jomill Enterprises	967
Kesh Electronics	- 1
Light Soldering Developments Ltd.	903 931
Manor Supplies	978 976 975 977
N.G.T. Electronics Ltd	957 978 969 917
PC TV Services Powell, T. P.V.S.	957 973
Radio Component Specialist	951 974 978 967
Renze CRT Ltd Rep TV Semple Service Sendz Components Sendz Components Southoride TV Southside TV Southside TV Stewart of Reading Sutfok TV & Video Supervision Supervision Swift Television Publications Taylor Bros (Oldham) Ltd Technical Advisory Systems	964 973 970 962 965 964 974
Supervision	952 903 976 935 976
Swift relevision Publications	976 948 947 964 959 960 975 948 935 949 935 949 950
View-Tel Viewvision Visions London	958 962 946
West Midlands TV & Video Williams, Dave. Willow Vale Electronics Witsgrove Ltd. Wizard Distributors.	906 974 977 954 966
Zoneport	960

SERVICE MANUAL	C
VIDEO RECORDERS	
BOOK 1 NAT PAN 200C + 2010 + 333 + 370 BOOK 2 SONY C5 + 6 + 7 + 9 BOOK 3 SHARP VC9500 BOOK 4 FERGLVC 3VC1 BOOK 5 NAT PAN 200C	£17.00 £17.00
BOOK 3 SHARP VC9000 BOOK 4 FERG/JVC 3V21 BOOK 5 NAT PAN 2000	£10.00 £10.00
BOOK 6 NAT PAN 370 BOOK 7 FERG 3V23	£10.00 £10.00
BOOK 8 PHILIPS 6462 BOOK 9 ADJUSTMENTS FISHER FVH-P716 HITACHI MANUALS IN STOCK PLEASE RING	£10.00 50p £10.00
TELEVISION MANUALS	£5.00
CTX-S	£5.00 £5.00
CTX-E CP90 ITT CP9350	£5.00
TASHIKO 140971	£5.00
C16WK1 CTV C20XK5	
C20TA5 C16TK1	C5 00
C22XZ1/26 C20DZ2 C20BZ5 COMPOSITE C22Y77/26	£5.00 £5.00
	£5.00
GRANADA VIDED REC VHSAS1 FISHER VHSCC1 AMSTRAD	£10.00
VHSWH HITACHI VHSDH1 HITACHI VHSYH2 HITACHI	£10.00 £10.00
TECS AUTHORISED EQUIPMENT MODIFICATION BOOK	
ALL MANUALS ADD £1.80 PP NO VAT	
NEW VIDEO FRONT PANELS SONY C5/C7/C9 NAT PAN 2000/2010	£5.00 £5.00
FERG 3V22 3V22 TOPS	
3V33 CASS LIDS MANY VIDEO/TV PARTS IN STOCK	£2.00
LARGE SAE FOR LIST ALL GOODS TRAI	DE ONLY
BELL RADIO 322 HUNGERFORD ROAD, CREWE CW1 1H	IC I
TEL: 0270 582849	
QUALITY USED T	D.
& VIDEO	••
COMPLETE RANGE	OF
T.V's AND VIDEOS	
MOST MAKES AND	
MODELS AVAILABL	.E
STOCK ARRIVING DA	
T.V's from £3.00	
Videos from £30.00	ן כ
Free Delivery Service	
UNIT 80, BARRACKS ROA SANDY LANE INDUSTRIAL ES	
STOURPORT-ON-SEVERN	
WORCESTERSHIRE DY13 9	UR
Just 10 Mins from M5 Junct. 6 Worc's Nort	h
02993-79642 0	-
ULJJJJ-/JUHL U	
79643	



Micro Switches mixed 15 for £2	CV 8617 Y 716 Y 729	10p 10p	T 6054	40р 40р	Varta Batteries 2.4V 100M/A 50p		lours Battery battery test £6	Regulated Power S 3-12 volts 1 an	10
Philips small stereo	Y 730 Y 827: 6A/IKV	.30р 10р 20р	T 6070V £1	50p 1.00	TV Battery 50p 1.2V NC. 2.4V NC. each	Hill Deluxe Cad Charger	Universal Ni-	in box with switch mains lead &	<u>ا</u>
Rank UHF 4 push	Y 860 Y 933 Y 969	30p 5p 50p	T 9005	40p 40p 1.00	4 amp-1.2V Nickel Cadmium Battery D	Nickel Cadn	nium Battery	Philips' Video Cleanin SBC461 Philips' Headpho	
GRC power supply	Y 997 Min 12 volt Relays	.30р 75р	ZTX 107	10p 10p	Cell £1.00 3.25V Battery 50p 12V Video Pattern D 50p	<u> </u>	C-D-PP9 £4.50 Changer over	Compact Disc Stereo T ITT Display Tube 5870	ypc £10
Rank front panel	R 1038 R 1039 R 2009	40p 40p 80p £1	ZTX 109k ZTX 213	5p 5p	12V Video Battery Packs 4Amp U2 Cells £10 24V 4Amp (100VA)		/s 45 watts 50p	8 Seg Display FND500	
Z950 £5 GEC IF tuner panel	R 2010b R 2029 R 2710	£1 50p 60p	ZTX 342	10p 10p	Z4V 4Amp (100VA) Trans £4.00 Mains 240V (100VA) to	2100 Series Re	Unit for GEC eplacement for	Model 3000 Pocket Personal D. Volts range AC, DC 2	.M.M. 2001/V to
PC786B £12.50 Rank IF 742 £3	R 2210 R 2257 R 2265	60p 50p	ZTX 451	10p 10p	240V out fully shrouded £5.00	Touch Button 8 SEG LED	Unit £8 Display with	400V R 2000Km Export PYE73	£20
TX10 8 Button Unit £10	R 2305 R 2306 R 2322/2323	50p 30p pair 80p	MJ 2253	10р 60р 60р	ITT CVC45 8 way resistor unit for v/cap £3	driver I.C.	LM1017 50p	6 Push Button unit wi VHF) band switch	£4
6 Button Unit Rediffusion Mark 3 £5	R 2323 R 2396 R 2461	15p 50p	MJE 2209	оор 10р 50р	CVC40.8 button unit with mains lead & slider pots		LIPS' D PHONES	TTT Micro Phone M5 switch	·
Rediffusion Mark 4 & 7 Push Button unit £10	R 2030 R 2443=BD124 R 2540	80p 50p 30p £2	SAB 3205 £1	1.00	with sockets £10.00 Book on An Introduction	Electron	ic Buzzer	11/2 Volt Sub Min Rela Philips Solar Scien SBC1730 Calculate	ntitic
Tuner IF Cans ITT	R 2540 R 2737 R 2738=T1P41	£2 40p 30p	$200 \pm 100 \pm 100 \pm 50.300V$		to Satellite TV £5.95 No VAT	6 Volt, 12	2 volt 40p	15v-0-15v 1 An Transformers 1	10
CMR200 £10 TTT SEL HF Modul 2	R 2775=TIP41c R 3129=TIP47	40p 40p	150 + 200 + 250M 300V ; Computer Transformer	50p	Book TV DX Handbook by R. Bunney £5.95 No VAT	Print Type Tr.		RGP30K RGP30G	10p 8p
UK IF Tuner £8	R 4050 S 2008b 2SD898B	£1.00 80p £1	20v/2.25A; 20v/1.5A; 17/.5A; 19/.5A; 28/.05A	£3	Electronics Hobbyists Handbook £4.95 No VAT	print type 1 Changeover	iy 1½×1½×2 0 amp D.P. £1	RGP10B RGP15 RGP15G	5p 10p 6p
4 types of front panels Fidelity 2000/3000 types £5	2SC1942 Hitachi sets etc. STR454	£1	PHILIPS METERS 4T5003-SBC 851 Analogue		·			T6024WG1 GP10 GP15Q	10p 5p 5p
CVC20, CVC32 1.F.	STR6020 S 2000AF line o.p.	£2 £2 £1	Multimeter £22	2.00	Philips Digital Multimeter with 5BC812 PHILIPS	n memory and	auto ranging £63.00	1HORN RGP80G DUBLE 7 SEG Displa	30m
CVC40 Cans £5 CMR800/3 NEW £20	2SC940 BU 105/04 BU 108	£1 80p £1	GEC 20AX MkI Power Supply PC818	£10	25 Watt Solder Iron	Various Tools a	£4.00	I N5 26RA or	10 for £1
CMR800/3 £20 CMR803/2 £20	BU 124 BU 126	50p 80p 65p	Voltage Regulators		Self adjusting cutter stripper 10 mixed tube bars				£5.00 £4.00
20AX Line lin coil 50p	- BU 180a BU 204 BU 205	65р 60р 75р £1	-8V/79M08c	30p 30p 30p	5000 Diodes-Resistors T/V V/Aerial 300Ω or 75Ω * D/P such mains switch				£3 pack £1.50
GEC switch mode trans 20AX ITT mains CVC9 to	BU 206 BU 207 BU 208	£1	+10v/78LA10	зор 20р 30р	* D/P push mains switch Mains lead & two pin socket T/V loop aerial	for radio cassett	e	:	20p each 35p 75p
CVC33 print type 60p ITT 2,800 mains	BU 208A BU 208D	80р 75р 90р £1	LM 337	30p 30p	Radio Telescopic Aerial Philips Neon Lamps for TV s	ets			£1.00 5p
remote switch 50p	BU 222 BU 326 BU 407	£1 £1 60p	+12V/LM 340T12 5	50p 50p	Freeze Philips Foam Cleaner Philips Contact Cleaner Philips				£1.20 £1.20
2110 GEC Sound O/P	BU 426A BU 426V	45p 60p	+24V/78M24	20p 30p	Cans of Anti Static, Degrease Lorlin Full Remote Relay Sw	itch fit most T/	V sets, mains 4	tag. 2 tag. 12 volt	£1.20 at £1.40 £1.00
Panel £1 2110 GEC L.O.P.T. Panel £6	BU 500 BU 500D BU 508A	£t.10 £1 90m	MC 7824	40р 40р	Mains timer. 13 amp — up to Screen locking agent, large ca	a 2 hours: easy in	to use, plugs in	to socket	£3.00 £1.50
2110 GEC Power Panel £5	BU 508V BU 705	90p £1 £1	TIS 92 2	10р 20р	Red E.H.T. LEAD and Ano Weller solder iron 25 watt Hitachi Silver Oxide Battery		C \$044.1.5V		£1.00 £4.00
Line o/p frame panels GEC 20AX £10.00	BU 806A BU 807 BU 824	£1 £1 £1 50p	U 19885 4	20р 40р	100 Coax Plugs De-solder pump + 2 nozzles		X 3K44 1,3V		60p £12.00 £4.00
ITT CVC40 Push Button Unit & Mains	BUT 11 BUT13 600V-28A BUW 11	50p £1 50p	U 3845	15p 15p	Flat Red LED and Green 500gm 60/40 solder reel	·			5p £6
Switch £12 Tuner & IF Panel.	BUW 84 BYW 20-08-9	60p £1	MR 501	10p 10p	Solder 1 kilo reel Dual v/u meter -20 – +10db K30 thermistor 232266298009				£5.50 £1 75p
Complete 6 button and preset IF with s/wave	BYW 95 BUX39 25A-150V BUX84	10p £1 50p	BCW 71R 3	10р 30р 10р	De-solder Pump Portasol Flameless Gas Solder	ing Iron			£2.50 £16.00
filter and tuner. Mullard M342 5"×6½" £6.00	BUX85 BUY49 TIC 106a	50p 20p	BYF 1204 1	юр 10р 40р	Green & Red, LED pack mix Hill Meter Leads, S/Rubber a			100 f	or £1.00 £4.00
POTS	TIC 116m TIC 116n/Y 1003	30p 30p 30p	BYX 10 1	40р 10р	Miniature Linesman Pliers	HII £2.	20 Miniatur	e Pliers	£2.20
BA 301 £1 TA 4127 £1 HD 3884 2A23 £3 TA 4184 £1	TIC 126N TIC 225S TIC 226E	30p 30p 30p	BYX 38/300 2	35p 25p	Miniature Side Cutters KT3 PANELS	£2.20	Miniature Enc		£2.20
IA 2125 £1	TIC 226E TIC 226m TIC 236m TIC 236m TAG 226/600 TICV 106D	30p 30p	BYX 55/350 1	75p 10p 10p	Sound Output RGB Output C Panel, I.F. Panel and Line O	SC		HILIPS VHS VCR /R6760 and derived t	ypes £19.50
TA 4190 £1 TA 4138 £1 TA 4196 £1	[(1092 case 2A/400V)	30p 10p	BYX 71/350 2	20p 50p	PYE 6 Key Switch & Panel	£7.00 each		Mixed Packs	219.50
TA 4174 £1	TIP 29 TIP 30 TIP 30A	25p 25p 25p	BYX 72/300 2 BYX 36/600 5	20p 50p	G11 Front Panel	£10		wer Trans RCA 1618 for BD124 and Mou	
TA 4167 £1 TA 4199 £1	TIP 30B TIP 30C	25p 25p	BVY 95C 1	10р I 2р	SONY 1400KV Chroma Pane SONY 1400KV Touch button		Kits 25 Panel Mo	unt Bulbs & Neons	£1.00 £1.50
BA 546 £1 BA 328 £1 TA 4176 £1	TIP 31 TIP 32 TIP 33B	25p 25p 25p 25p 25p 25p 25p 50p	BYZ 106 1	10p 10p 15p	GEC Decoder Panel PC772A. PC446A		10A 25 LED red/ 20I/C Holder	yellow/green	£1.50 £1.50 £1.20
TA 4145 £1 TA 4191 £1 HA 11710 £1	TIP 33C TIP 34A TIP 34B	70p 50p 60p	BYW 56 2A/1000v G11	15p 8p 15p	12 Volt Mains Trans 500M/A	£1.00	20 Large 1.E 20 Small LEI	D Red D Red	£1.00 £1.00
TA 4188 £1	TIP 34C TIP 35B	оор 70р 50р 70р	BYW 95C 1 BZU 15/24 5	10p 54p	NEW TX9 CHASSIS New Ty	pe Thorn	10×20 Turn		£1.00
TA 4197 £1 TA 4183 £1 TA 4197 £1 TA 4183 £1 TA 4183 £1 TA 4195 £1	TIP 35C TIP 35D TIP 36	70p 80p 50p	BZY 93c75 5 BZV 15/18 3	50p 10p		£15.00			tp each
TA 4195 £1 TA 4175 £1 TA 4175 £1 TA 4177 £1	TIP 36C TIP 41 TIP 41B	80p 50p 70p 15p 40p	BZW 70c6v2 1	80р 0р 0р		25 for £1.00	Mixed 100 T PET	ransistor B.F. and B. £1.50 1000 for	C. and r £10,00
TA 4192 £1 TA 4146 £1	TIP 41D TIP 42	70p 10p	Bush thyristor RCA 76122	0p £1	KT3 touch button black G11 touch button red	25 for £1.00 6 for £1 6 for £1	12 Volt 4 An Type D Cells	np Video Battery Pac	k 10 of £8.50
TA 7265 £3 TA 7699P £3	TTP 42/BRC 6109 TTP 48 TTP 49	10p 40m	Transformer 240v/20v-500Ma7 Chassis type Transformer 240v/12 Volts 500m/a 7	/5p /5p	K30 full remote Dawer Ass w I.C.	ith 3 €7.00	40 glass reed		£8.50
The Service Engineers Guide to Teletex £2	TIP 57 TIP 110 TIP 100	30p 30p 20p 30n		£Ż		£6.00 20 for £1.50 10 for £6.00	40 Pots	nake switch	±1 70p £1.50
4 Types Fedility front panels with i.c. & pats	TIP 102 TIP 115	30p 30p 50p	Infra red led		BU205 BU105	0 for £8.00 0 for £6.00	mixed	Pin, 10 Tube Bases,	£2.00
#2 each BB 103 10p	TTP 117 TTP 125 TTP 126	50p 35p 40p	15K-20 turn pots 2	5р Юр Юр	BF458 BF224	0 for £1,00 20 for £1,40	Bandolier 20mm Fuse 1	. Condensers, Resiste Jolders	ers on £1.00
BB 105A×12 £1 BB 105B×12 £1 BB 105G×12 £1	TTP 126 TTP 127 TTP 130 TTP 131	40p 30p	BRIDGES		50 Ceramic Condensers Mixed Mounting Kit for Powe	0 for £1.00 £1.50 r	Chassis Mour EHT Diodes	nt 20) for £1) for £1
BB 121a 10p 47 10p each	TIP 131 TIP 136 TIP 140	бр 30р 50р	KBL 02 3	0p 0p	Transistors 300 Condensers	50p £1.50	300 Mixed D	iodes	£2
1A/1600V 10p DG3P EQV-BY228 10	TIP 142 TIP 640 TIP 2955	80p 50p 35p	W02 E	0р 5р 5р	300 Resistors 150 Electrolytics 15 Bulbs Philips	£1.50 £2.00 40p	100_500M/A	Fuse	£I
for £1 2 amp bridge rec. wire	TIP L761A-1000V/4Am T 6032	p 75p 30p	W005 2	эр ∣ Юр Юр Ґ	GEC-Hitachi Thick Film Fram	ie £5	Philips etc.	Pots IT1-GEC-Hita 20 witch with Remont	chi-) for £1
end 15p SKE4G2/02 15p	T 6036 T 6040 T 6047	40р 40р 40р	MAINS	-	SENDZ COM		CMC113	Kellkan	£I
Eqv. BYX71/600 500ns.	Ť 6049 T 6051	40p 40p	MICRO SWITCH GEC & Double etc.	£1	TO ORDER SEE BAG	CK PAGE	12v DC relay amp D.P. ch	11/2×11/2×2 print typ ange over	e 10 £1

SENDZ	COMPONENTS	Thorn TX90 Chassis with Line Linearity		£20.00	Philips Handset 1C £3.0 SAA3010P £ MABS461/WO63 £
TO ORDER SE		\$4471 £1.00 2SD1878 £1.00 TDA8443/C3 £1.00		£50p. £1.00	MAB 8420P C031 £3.0 MAB 8400B 6 £3.0
	K35 Decoder £8.00	TDA3506 £1.00 SAA5241 P/A £5.00	220/4005	£1.00 £1.00	MAB 8440P-D070 €3.0 MAB 8440P-D033 €3.0
LA11440 £1	K35 Sound OP £4.00 Thick Film Daughter KT3 3122-127-43891 £3	SAA7020_04 €3.00 11D614080SA90 €4.00	1200PE 15KN 01.2KV	10p 10p	MAB 8440P 10056 €3.0 MAB 8441P 1001 €3.0
TAA7750 50p 11A 411485 €1	12 C.H. K30 Tex Ree Front Panel with 1 C. £5		150m-385y 1000m-160y TX90	50p £1.00	M58484P £2.0 Hand Sets
UPC1373 50p M58657P £1 M491BB1 £3	K35 IF £5.00	225m + 25m 380v £1.00 220m 385v £1.00 240m 400v £1.00	1+1 MED Mans Filter 1 100 × 10	30p	Fidelity £15.00 to £35.00
M491BB1 £3 M50441/550 £1 M58658P £1	Plug In K4 Focus Pot £1,00	G11 470m 250x £2.00 400m 400v £1.00	22/100 4 7M 100 6800pt-1000s	10p 5p	111 8 and 6 Push Burton €1.0 Pse 725 LOP1s €6.0 Pse 731 LOP1s €6.0
Receiver TX100 Panel	Endebity Tube Base with transitor & focus pot £1.50	175m/100m 100m 350s £1.00 TX9 500m + 500m 175s £1.00	470/100	20p 75p	Pye 7314 OP4x 66.0 Thorn 8500-88004 OP1x 65.0
LC: No. SAB3035 	Bush Tube Base on panel £1.00		47/160 300/300/300V in 1.6KV	10p 80p	CMC 30E front panel £5.0 CMC 303 front panel £5.0
SAA1060 PCT8571P	TX10 Tube Base on Panel £3.00	C7 Hand Set £6,00	800/160 	50p- 5p	CMC 302 Panel with TC mains switch etc £5.0
New Model Philips Meter £25.00	11001 O.P.1. Green Spot	G8 LOPT Panel £7.00 G8 Tuner Unit + Panel £4.00	2.2.250v 7N5 1500V	10p 15p	CMD 800 Decoder £8.0
C. Cam Decoder with TDA3591 E5	EX100 Thorn	G8 IF & Chroma £6.00 G8 Chroma £3.00	3n3/250 A C 33/250V	10p 20p	GTI €1.5
Toshiba VHF/UHF EG522F £6	Line Transformers G8 Lopt £5.00	G11 Chroma Panel £4.00	- 39/250V 4n7/250 tested - KV	15p 25p	3.1.C. Power Supply G11 Full Remote Receiver Panel £3.0
Mitsum MECI-F51 £5	G9 Lopt £4.00 6 Diode Tripler, Multard 75p	G11 LOP1 Panel £6.00 G11 IF Panel £5.00	22/250 47/250	15p 10p	PHILIPS SBC 469 Stereo Microphone
Thorn Spares New 9000 Decoder £8.50	Line O.P. Trans. Mono. E.X. 12"-14" Philips G8		100/250 GI-C600 250	20p 60p	€23.0 Meters Hills 520 €17.0 Meters Hills 420 €10.0
9000 Frame panel £8 9000 Cyclops panel £1.50	27482 €10 4822 €10 10273 €10	G11 IF Detector £3.00 G11 Selector gain module £3	700/250 2-200PE-2Kv	£1 10p	Hills HD5000 Digital Meter 1000V DC 750AC 10 Amp 20 MRG Rangers £2
8800 convergence panel 66 8500 convergence panel 66	Ehorn 1690 I OP1 £7,50 2 I Pois 3,500 L off each type £3,00	Pye G11 Front panel with transducer. pots, timer pots, 6 pb switch+lead £5.00	300+300 MED 350s 800/250	£1.00 40p	IfI 100 Multimeter £6.7 111 300 Multimeter £7.7
4000 Power supply £3 1600 Mains lead, switch 1605 INNPN 1066 805/6A 10p	G8 Trans Philips £7,00 G11 Split Diode £12,00	Pye 6 button switch portable £1.00 GEC V cap VHF/UHF tuner and IF + sound O/P PC 706B3 (Export) £12.00	32/300 4 350	20p 5p	F11500 Multimeter €9.0 F17700 €15.0 F1D1000 Digital £20.0
9000 Sound output panel £1 3500 Focus unit £1.50	CVC820 Split Diode 11'1 £10,00 Thorn B/W AD5308F + Stik + Lead £1,50	GEC Line O/P PC 659B3 66.00 2110 GEC Power Panel 68.00	8.350 4.7M 350k	8p 10p	HD3000 Digital £25.0 HD5000 Digital £25.0
3500 Mains Trans £4 3500 cut outs 10 for £4	GEC 2040 £3.00 GEC 2110 £7.00	CVC 20 Front panel with sliders + mains input panel £4	33 350 220/350	20p 30p	HD5500 €29.0 HD6000 Digital €32.0 HD8000 Digital €37.0
3500 IF panel £2 3500 Frame panel £3	Nullard A.1.2036 £1.50 Pye 169 Lune Trans £3.00		- 300/350 - 400/350	.50p 40p 50p	HD9500 Digital with capacity Temp Trans Volts Ohms and Amps tanges - £6
3500 A1 Diode 20p 4000 Tube base £4	Pice mono £3.00 Rank mono 1704A £3.50 Split Diode Trans £7.00	CVC 40 PUSH BUTTON ASSY with sliders complete with lamp assy + pots	22/375 220/385 (TTT)	50p 15p 75p	Infra Red Hanset Tester
3500 A1 pots 50p Beam limiter panel £1.50 3500 Power panel with Y969 £1	GE C 20 AX Rank Z522 £3.00 Rank L O P T Z970 £3.00	8 button units £9.00 Universal Focus Fits Pye, Thorn and	330/385 CVC 820HT	60p	Works at 24 feet – Sound repeater Works off 9 volt battery £8.0 Fits in top pocket
3 Way regulated adaptor 240V 6V / 7,5/9V/300mA £3.50	CVC800 Line Trans £6,00 CVC825 Split Diode £10,00	Decca Units T147 Rank tube base on panel £1.00 Z718 Focus Unit £1.50	0-1/400 K13-E/W-39/400	15p 15p	Handset Tester with LED £4.5
Rank Toshiba preh unit 0354 £9.50 4 Push button unit preh £1.00	CVC 45 £5,00 GEC Portable GEO [2041 £3,00 GEC Portable GEO [2046 £3,00	120 Focus Unit £1.00 Large Type 75p	56K-400K 4700pt/400	20p 10p	Repaired Handsets Philips K4-K35, RC5350-RC5300, RC5370, RC5375, repaired same day
6 Push button VHF/UHF for v/can_GEC-Decca type £7.00	GEC Portable G107F2046 £3.00 E111 Spin Diode Leads ITT £1.00 3500 L O P 1 & HT Frans each £2.00	Decca Small 75p KT3 Focus Unit 75p	8/400	10p 15p	\$10.0
7 Push button for CVC5 111 £8.00 KT3 12 Push button unit £2.00	LOPT Rank Z763 £5.00 K35 Split Diode 3122/13835930 £10.00	K30 Focus Pot 75p K30 Tube base on panel £1.00	3 3/400 -400/400	20p -40p	RC4001 Full Remote K13 K30 Teletext Handsets exchanged £15.0
KT3 (Export) 12 P.B.u £2 6 Push button Unit Thorn £1.00 6 Push button GRC £6.00	Universal Tripler	TX10 Focus Units £8,50 CVC 32 Focus Unit 75p	394K-400V 1000ms160k	20p £1.00	NEW Type RC4001.9 CH not 12 66.0 GFC Full Remote Infra-red, 1983 model
6 Push button PYE 731 £6.00 Hearing aid unit £3.00	with small focus pot. Green type £7.00	Fidelity Focus Unit 14R–14S 30p 3500 Thorn Focus Unit £1.00	220/450 47/500	40p 25p	£15.0
Rank Z718 4 P/B/Unit MECH £4.00 7 Button Unit GEC with Lamps £7.00	Black 1riplers KT3 Tuplers £6.00 STC_Universal Tripler £6.00	TT1 Small for use with Split Z718 Bush Focus £2.00	0-1/600 0-1/1200V wire end	15p 20p	FOSHIBA HAND SETS CT9185 £7.0 C19176 £7.0
697 Push Button Unit £6.00 Z916B panel £5.00 T513AP panel £5.00	11 [J] £2.50 [1] [GA £2.60	Diode 50p Remo IV12SP 50p	0 450 A/C wire end 22/1000	20p 20p	CT9133 £7.0 Rediffusion MK3 £5.0
	ITLCVC 5-8-9 £3.50 Rank T25LF Tripler £2.00 Rank ITTCP A823 £3.50	1600 Thorn EFIT Rec and Lead 50p 1∨14 50p 1∨20 €1.00	047.600 0.047.1000	15p 10p	TOSHIBA HAND SETS
Video Funer V 6100/05 E/V and Tel/Text unit and	TU 25 30K Rank £3,00 11 11 Z Rank £3,00	TV20 €1.00 TV45 50p	0.01.1000	10p	11/AND SETS 24 Button CT938 Fuliremote £5.0 32 Button CT983 Videotext £6.0
hand set £90,00 Send for data	G9 Philips £4.00 GEC 2110 £4.00	TX9.8 Button Unit £6,00	150m 385v 47/10008	£1.00 65p	THORN VCR Front Display Panel £7,0
TT14 GEC TEX-DECODER 13 IC Panel with cable form £9,50	3500 Thorn £3.00 8500 Thorn £4.00 9000 Thorn £7.00	LX90.8 Button Unit £6.00	- 47/250V A.C 001K 1250	10p	Large type HT TV and V C R
	9500 Thorn £4.50 9600 Thorn £4.00	TAM 8 BUILOB CHIL 60.00	0,0047 1500 005 1500	10p 10p	Handset £15.0 GFC Ultrasome 8CH Full Remote £10.0
PHILIPS K40 Text Panel £8.00	2040 GEC £3.50 GEC EV M25 Tripler £2.00	FX90-1X925 8 Button	0105 1500 In8/1500	10p	G11 Full Remote Ultrasonic £32.0 G11 Ultrasonic Teletext Handset £20.0
KT3-K30 OI-425	Universal Fripler £5.00 G8 Tripler £5.00 CVC20-32 £5.00	FX100.8 Button Unit £6.00	2n2 1500	15p 15p	8 C H. Ultrasonic GEC Full Remote C2014H/C2219H €15.0
OF-550 E.W 10p OF-513 correction 10p	Decca 80 100 £4.50 Grandie INK 52 £2.50	FX10.8 Button Unit £10.00	G11.8200/2KV	15p 15p	New Replacement for G11 Ultrasonic Fall Remote €12.0 Thorn 4000 insert with 7 buttons €5.0
OF-557 50p	111BO Pvc 731 £3.00 11111Y £4.00	IX107TX100-16 Button €10.00	0.1 2KV 3n9/2KN 0.0015 2KV	20p 15p	Decca RC 11 €14.0 Decca RC 12 €14.0
DIODES 10p	D22 for Pye 18" colour portable = £4.00 LP 1193.63 £4.00 BG 100.41 £3.25	UHF-VHF BAND S W	6n2 2KV	10p 15p	Dynation-Full remote CTX 62 63 64 £19,0
BY 127 10p BY 133 10p	1 RO Tupler print type with foacs PO7 BG2087 £5	GIT drawer ASS 3 pots Mains switch	2n2/2KV 470pt 4KV	15p 10p	Hitachi infra red handset £18.0 Philips full remote K 13, 16C928/20C934 7228 7324, K12 26C 797 151 66K
BY 134 10p BY 176 25p BY 179 40p	I text ultrasonic rec'r panel €14,00 12-14V 20 for €5,00 200 for €25,00 CU C S tauch unit asy complete with dl	and lead £2.00	7500pt/2KV 3000PE 3000X 467 2KA	10p 10p	1826 £12.0 G11, Full remote top button assy £12.0 G11, Full romote repair service (exchang
BY 184 25p BY 187 10p	GEC 8 touch unit assy complete with all EC 8 + pots £4.00 G11 E.W. Transformet 50p	K30 Drawer Ass with pots cable forme £1.00	4n7 2KN 6n2.2KN 7n1 1500N	15p 10p 10p	Unit} £18.0 GLC intra red full remote 8 channel
Bት 190	G11 F.W. coils £1.00 G11 Transient Suppressors 245V 20p	TX10 Drawer with 8 way pots, ass £2.50	- 8n2/1500V 9n4/2000	10p 10p	(ECSAA1250) £14.0 Philips infra red full remote 9 channel to 60 CP2605 £6.0
BY 198 10p BY 204/4 8p BY 206 – BY 407 Fqv. 8p	G11 Scan Coils £5.00 G11 100K tuner pols 12 for £1 KT3 II: panel £6.00		8n2/2KA 0.0082/2500	15p 15p	Philips mfra red full remote 12 channel for 60 CP2605 £12.0 K35
BY 206 = BY 407 Eqs. 8p BY 208-800 8p BY 210/400 5p	K13 line OSC transformer £1 K13 K30 mtra-red receiver	TX10 Fx port with band switch (drawer) £2.50	150/3500 1800/4KN	10p 5p	K13/K30171ext £12.5 K13/K301a01remote £15.0
BY 210/800 10m	head £1 K30 drawer unit with IC's	Hills Meter for the car man, volts, amp.	4.7nf/5KV 170/8KV	10p 10p	K13 Power supply £4.0 GEC intra-red 2236-2026 £4.4 GEC 8 button full remote £14.0
BY 224/600: 4 8A/600v bridge 50p BY 226 15p	(home) £10 K30 drawer unit with IC's (export) £10	ohm with dwell and r.p.m. £35.00	180/8KV 210/8KV	10p 10p	 GEC push pad handset button blobs 10 each
BY 227 15p BY 228 1500v 20p	K13 AE Sockets 50p K13 receiver panel £8	Hills 9 piece tool kit in case £5,00	 1000/10KV 47/100V Fubs: Thermosth 167 	10p 80p £1.00	Pve & Philips handset K13 K30 classis No RC5150-RC5176-RC5171-RC5177 Special Price £13.0
Flat BY 229 black 15p BY 299 Red 20p BY 229/400 30p	K13 line driver transformer 50p Pye K30, GEC etc. Pre-mains stand-by	Abbey Security Smoke Alarm Model	L Fube Thermpath 167 Rank Secam Decoder Pa VHI 1115Δ	£1.00 mel UEIF & £13,00	RC4001 K13 and Felerex £14.0 H CVC 32 handset repaired £15.0 CVC 32 Handset £15.0 CVC 45 3 and 2 Pin £15.0
BY 299/60p Tag 30p . BY 237 5p	switch €1 Decca 80 100 IF panel €5 NPN PNP 80V-6 Amp TO(66 O P	101 £5.00	10 off 91 CAP G11 Philips K4 CAP 150M 38	£2.00	A X10 Hand Set Lexi 12.2
BY 254 10p BY 255 30p	Trans pair 25p 5 button touch tuner BBC1 2 TTV1 2	Philips Coaxial Cable Stripper SBC325	Philips Coaxial Cable St SBC325		1X9 with Text £12.5 1X9 & TX10 button point £2.0 TX10 bocus Pots £5.5
BY 298 10p BY 299 10p	video with ic SAS 5601 570 ° £7.00 Control panel 5 sliders + mains lead £1.50	£7.50 CVC 20-25-30 Mains Switches	660	•	IFI I V & Video Processor 1200 Evpe £10.0
BY 406 8p BY 527 20p BX 107: 10p	G11 8 Jouch button unit replaces old 6 P B U €24 Tube base + base unit for 820 I uro	Infra Red and Ultrasonic G11 Feletext E RANK & 11T Mains Remote On-Off Sw	Decoder Panel Exi	S	PHILIPS
BY 407a 10p BY 448 10p BY 527 10p	chassis £4.00 GFC Line O P Trans & Rec Stick for	RANK & ITT Remote Switch 2800 ohm G11 Mains Switch	£1.50 50p	ř	UNIVERSAL HAND SET £12.00 RC5 KT3 = K45
BY 602 10p BY 602 10p BY V 26C 10p	Portable £3.00 CVC 2025 30 35.40 decoder panel £10	4 amp Mains Switch GFC Mains Switch 4 amp	25p 30p	L	We have all parts for Philips Handsets RC 5353 £15.0
F 247 10p GP20G 5p	CVC 20/25 30/35 40 decoder panel (untested) £5 CVC 40/45 II panel £5	KT3 Mainswitch G8 Mains Switch	£1.(4) 75p		RC 5353 615.1 RC 5300 612.0 Philips RC 5 615.0
	CVC 40/45 IF panel £5 40K Transducer 50p PHILIPS NE511N £1.20	G11 Preh Red LED P/Button for C.H. C RANK TOSHIBA Transductors TPC 20	hange 20p 11 50p	Ν	TEXT-TYPE Replace Hand Sector
GRP80G (TX10) 30p XK 3102 50p		Munie Suntab [17] Lana Leon Dunt	75p		Philips K13-K30_K4 etc £12.3
GRP80G (TX10) 30p XK 3102 50p BYV 28/200 20p Brdge 1 X10 800/3 amps 30p	LM337NEReg 30p 20 GEC Black Spark Gaps £1.00	Mains Switch HTLLong Type Print Mains Switch Philip Long Type TAG	75p		THORN HAND ST 19
GRP80G (TX10) 30p XK 3102 50p BYV 28/200 20p	L M337Nt Reg 30p 20 GF C Black Spark Gaps £1.00 K L3 Front Panel Control Assy £2.50	Mains Switch Philip Long Type TAG Mains Switch GEC Long Type TAG 2000 Chassis Fidelity Mains Switch (4-1-4	75p 75p (G) 60p	D	HIORN HAND SE1S 9000 = 9600 [N9] [N10] [N100 Text and Non-Text £10.0
GRP80G (TX10) 30p XK 3102 50p BYD 38/200 20p Bridge TX10 800/3 amps 30p Bridge TX10 800/3 amps 40p Bridge Rec D35B10 40p International Rectifier EHT Dodes G7 50p	1 M337M Reg 30p 20 G1 C Black Spark Gaps €1.00 K134 ront Panel Control Assv Assv €2.50 B1W 30 50 \$0p	Mains Switch Philip Long Type TAG Mains Switch GEC Long Type TAG	75p 75p (G) 60p 60p	D	9000 - 9600 TX9 TX10 TX100

r.