

THE

2 metre f.m. transmitter



World Radio History

Т	.T.L. 74 I.Cs by	TEXAS, NATIONAL,	I.T.T., FAIRCHILD Etc	
7400 14p 7413 7401 14p 7414 7402 14p 7416 7403 14p 7416 7404 14p 7416 7405 14p 7420 7405 14p 7420 7405 20p 7423 7406 20p 7425 7407 40p 7425 7408 20p 7427 7410 15p 7428 7411 20p 7432	30 p 7437 25 p 746 60 p 7438 25 p 747 30 p 7440 5 p 747 30 p 7441 65 p 747 30 p 7441 65 p 747 30 p 7442 65 p 747 25 p 7446 60 p 747 25 p 7446 70 p 748 25 p 7446 15 p 748 40 p 7451 15 p 748 40 p 7451 15 p 748 35 p 7453 15 p 748 25 p 7453 15 p 748	0 30p 7492 45p 74122 40p 2 25p 7493 40p 74123 60p 3 30p 7495 60p 74125 50p 4 30p 7495 70p 74125 50p 5 30p 7496 70p 74125 50p 6 30p 74104 40p 74130 130p 6 30p 74104 40p 74130 130p 7 74105 40p 74130 130p 74130 130p 6 30p 74104 40p 74131 100p 74132 651 5 100p 74107 30p 74132 651 65 9 74105 30p 74135 100p 630p 74136 60p 74136 60p 74137 100p 630p 74137 100p 74137 100p 74137 100p 74136 60p 74136 <	b 74141 60p 74156 70p 74174 100p 0 74142 270p 74157 70p 74175 75p 0 74143 270p 74150 90p 74176 100p 0 74143 270p 74160 90p 74176 100p 0 74144 270p 74161 90p 74177 100p 0 74144 270p 74162 90p 74178 140p 0 74147 230p 74163 90p 74178 140p 0 74148 160p 74164 125p 74180 100p 0 74150 120p 74165 125p 74181 200p 0 74150 120p 74165 125p 74181 200p 0 74151 65p 74166 125p 74182 75p 0 74153 65p 74166 125p 74184	74188 350p 74189 350p 74190 140p 74190 140p 74191 140p 74192 120p 74193 120p 74194 100p 74195 100p 74196 100p 74196 100p 74198 185p 74199 185p
	by MULLARD, T	SEMICONDUCTO EXAS, MOTOROLA, S	RS SIEMENS, I.T.T., R.C.A.	
10 for 10 for 10 for AD161 350p BC184 AD162 350p BC184 BC107 30p BC184 BC108 90p BC212 BC109 90p BC212 BC147 90p BC2141 BC148 90p BC2141 BC149 90p BC2141 BC153 90p BC237 BC153 90p BC338 BC182 90p BC388 BC182 100p BC317 BC183 90p BC317 BC183 90p BC317	90p 8C548 90p 8D1 100p 8C548C 120p 8D1 90p 8C5498 100p 8D1 100p 8C549C 120p 8D1 100p 8C556 100p 8F1 90p 8C557 120p 8F1	35 350p BF199 220p E430 1150p 36 350p BF202 210p MPSA05 250p 37 350p BF224 150p MPSA06 250p 39 350p BF225 150p MPSA65 250p 40 350p BF225 150p MPSA65 250p 80 280p BF225 150p MPSA65 250p 81 280p BF225 250p TH254 350p 82 280p BF252 280p TH254 350p 82 280p BF252 280p TH254 350p 82 280p BF259 280p TH254 750p 83 280p E100 400p ARE FDR NN 95 90p E204 430p TYPE DR NND 97 90p E310 430p TYPE DR NND 97 90p E300 450p	b TIP29C 465p TIP34B 800p 1N4006 50p 0 TIP30A 350p TIP35C 2000p 1N4007 60p 0 TIP30A 380p TIP31C 2000p 1N4007 60p 0 TIP30A 380p TIP41A 560p BYX94 70p 0 TIP31B 435p TIP42A 700p 2N930 150p 1 TIP31B 435p TIP42A 700p 2N2907 150p 1 TIP32A 550p TIP23C 700p 2N2907 150p 1 TIP32A 550p TIP23C 700p 2N303 200p 1 TIP32A 550p TIP32S 550p 2N3053 200p 1 TIP32C 850p TIP3055 550p 2N3053 200p 1 TIP32C 80p 1N4002 40p 2N3072 90p	10 for 2N3705 90p 2N3706 90p SCR PUTS ETC. 2N2646 450p 2N6072 450p BRV39 300p BRY39 300p BTY55 3220 BT106 1250p BT106 1250p TIS88A 230p
LINEAR I.Cs CA3130 100p CA3140 100p CA3076 200p CA3076 200p CA3076 200p CA3076 200p CA3076 200p CA3089 210p CA3089 210p CA3089 210p CA3089 210p CA3089 210p CA3089 210p LM300TO5 130p LM309K 100p LM311TO5 260p LM311TO5 260p LM324 150p LM3250N 110p LM326N 200p LM326N 200p LM3270T 75p LM723TO5 75p LM7248 45p LM733 180p LM748 550p MC310P 155p MC3110P 155p MC312P 200p MK555S 28p MM33	DECODER BDARD CONTAINS 18 × 74156 TO CLEAR 2 × 7409 3 50 1 × 74150 Obtails 1 × 74150 Dechnical 2 × 60 way E E CONNECTORS E PESEISTORS E 12 SERIES 2 watt 100 100 OFF ANY ONE VALUE £1:00 WIRE WOUND RESISTORS BY V.T.M. SK SK 9 Watts 50 1000 for £50 00 1000 for £50 00 D000 for £50 00 DOUE LP1152 200p LP1153 400p LP1154 400p LP1155 400p LP1165 400p <td>01/10 01/10 01/10 01/10 18p 7410 17/25 7p 330/50 20p 7412 17/25 7p 470/10 14p 7420 17/25 7p 470/15 14p 7420 17/25 7p 470/15 20p 7430 2 2/25 7p 470/15 22p 7432 2 2/25 7p 470/15 22p 7432 3 3/25 7p 100/16 27p 7476 4 77/25 7p 2200/16 32p 7442 4 77/25 7p 2200/16 35p 74131 10/16 7p 3300/16 59p 74131 10/16 7p 3300/16 59p 74181 10/16 7p 4700/40 65p 74181 10/16 7p 700/40 55p 74181 10/16 7p 700/40 5p 74181 10/25 8p 001</td> <td>ERS 4000 14p 4030 55p POT 10 for 100p 4001 14p 4033 55p CORES 10 for 100p 4006 90p 4041 100p LA3 100-S 10 for 100p 4007 15p 4008 35p LA3 100-S 10 for 200p 4007 15p 4008 12p LA3 100-S 10 for 200p 4013 35p 4004 405 14p LA3 100-S 10 for 200p 4015 39p 4055 14p LA3 100-S LA3 100-S 10 for 200p 4015 39p 4055 140p LA3 100-S LA3 100-S 10 for 200p 4015 39p 4055 135p D.LA3 500 LA3 500-S 10 for 200p 4015 39p 4005 135p D.L707 CO 7 SEGMER 10 for 200p 4022 19p 4012 15p 4022 15p 4022 15p 4022 15p 4025 15p 4022 15p 4022 15p 4022 15p 15p 15p 4022<</td> <td>S S S S S S S S S S S S S S S S S S S</td>	01/10 01/10 01/10 01/10 18p 7410 17/25 7p 330/50 20p 7412 17/25 7p 470/10 14p 7420 17/25 7p 470/15 14p 7420 17/25 7p 470/15 20p 7430 2 2/25 7p 470/15 22p 7432 2 2/25 7p 470/15 22p 7432 3 3/25 7p 100/16 27p 7476 4 77/25 7p 2200/16 32p 7442 4 77/25 7p 2200/16 35p 74131 10/16 7p 3300/16 59p 74131 10/16 7p 3300/16 59p 74181 10/16 7p 4700/40 65p 74181 10/16 7p 700/40 55p 74181 10/16 7p 700/40 5p 74181 10/25 8p 001	ERS 4000 14p 4030 55p POT 10 for 100p 4001 14p 4033 55p CORES 10 for 100p 4006 90p 4041 100p LA3 100-S 10 for 100p 4007 15p 4008 35p LA3 100-S 10 for 200p 4007 15p 4008 12p LA3 100-S 10 for 200p 4013 35p 4004 405 14p LA3 100-S 10 for 200p 4015 39p 4055 14p LA3 100-S LA3 100-S 10 for 200p 4015 39p 4055 140p LA3 100-S LA3 100-S 10 for 200p 4015 39p 4055 135p D.LA3 500 LA3 500-S 10 for 200p 4015 39p 4005 135p D.L707 CO 7 SEGMER 10 for 200p 4022 19p 4012 15p 4022 15p 4022 15p 4022 15p 4025 15p 4022 15p 4022 15p 4022 15p 15p 15p 4022<	S S S S S S S S S S S S S S S S S S S

World Radio History

ISSUE 857

JULY 1978 · VOLUME 54 · NUMBER 3

BRITAIN'S LEADING JOURNAL FOR THE RADIO & ELECTRONIC CONSTRUCTOR

Published by IPC Magazines Ltd., Westover House, West Quay Rd., POOLE, Dorset BH151JG

	News and Views
20	EDITORIALStandards
21	NEWSNEWS
24	SPECIAL PRODUCT REPORT—SES Electronic Ignition Kit
27	PW READER'S PCB SERVICE—Prices and details of the PCBs available
28	STRAY SIGNALS
38	SHOW ROUND-UP-IEA/Electrex; Wireless Show; Energy Show
43	PRACTICAL WIRELESS—Preview of our next issue
52	NEW BOOKS —Comments on the latest books in the electronics field
53	HOTLINES—Recent developments in electronics
54	PRODUCTION LINES —Information on the latest products
60	KINDLY NOTE—"Bovington" Tank Game, June 1978
65	ON THE AIR—Amateur Bands
00	SW Broadcast Bands
	MW Broadcast Bands
	VHF BandsRon Ham BRS15744
	VHF Personality—John BraneganRon Ham BR \$15744
	For our Constructors
22	PHASE-LOCKED CALIBRATOR
22	An off-air frequency standard receiver
32	PW "PURBECK" OSCILLOSCOPE-4lan Hickman
	The Y-amplifier
44	PW "AVON" 2m TRANSMITTER1B. L. Phillips G8FWM
	Beginning the circuit description and constructional details
52	FOLLOW-UP TO THE MORSE TUTOR
	Extra information on our project of August, 1977
55	IDEAS DEPARTMENT
50	Stereo headphone blender. Electronic switch DIGITAL LOCK
56	A multi-combination, multi-purpose lock
59	FOLLOW-UP TO THE "JUBILEE" ORGAN
55	Extra information on this popular project
61	μDECNOLOGY Project No. 4
0.	Fuzz box
	Comonal Internet
	General Interest
25	THE START OF EMPIRE BROADCASTINGRon Ham
	How our overseas broadcasting system started
29	INTRODUCTION TO LOGIC-1
	What can electronic logic do for us? Gates
41	IC OF THE MONTHBrian Dance M.Sc.
	The ESM532 audio amplifier
50	MAKING IT WORK
	A step-by-step approach to fault finding
_	

COPYRIGHT

© IPC Magazines Limited 1978. Copyright in all drawings, photographs and articles published in 'Practical Wireless' is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by 'Practical Wireless' to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

RECEIVER UNIT small personnel type made for use by Army covers 500Kc to 18Mc/s by means of a 4 way plug in coil unit, uses 5 min valves inc BFO in superhet circ reqs 67·5v HT & 1·5 L.T. as o/p for 4K phones supplied tested with circ £13. HT batteries if req £1·30 ea or 2 or more £1 ea.

AERIAL DRIVE UNIT suitable 2mt beam & up, 24v DC motors max speed 6 RPM supplied with remote 360' Ind again 24v DC & connections, ex aircraft radio compass two items £13.

HANDSETS rubber covered m.c. type nom 100 ohm with press to talke swt suit 19 or 62 sets store soiled elec okay $\pounds 2.50$.

VALVE TESTER ADAPTOR type MX849 for use with American I-177 valve tester extends range, in case with data £5-40.

V.H.F. TEST SET type 210 contains sig gen covering 20 to 88Mc/s in 4 bands good second harmonic o/p, int 2Mc/s xtal check, int pulse mod or CW o/p, noise generator with 50 Ma meter, all in case with cal charts & circ, note these req 200v DC & 6-3v £13.

DYNAMOTOR UNIT 27.5v DC 1/P o/p 200 or 400v DC 280 Ma intrating, these can be used as motor only by removing ext fan ass, will run on 6 to 24v DC very powerful as $1 \times \frac{1}{4}$ shaft approx motor size $6\frac{1}{4} \times 3\frac{1}{4}$ dia new American surplus £6.50.

CRYSTAL OVEN small type takes 2x Hcl8 size 2 \times 14 \times 2" 12/24v new £1-20.

CABLE min 25 core non scr colour coded new 10 mts for £3.

METERS panel mt type i Ma fed special scale 2" £1.30 also 100 Ua F5D scale 0 to 100 2" £3 both new.

CRYSTAL UNIT dual 100Kc & I Mc/s in 10X case with suggested circ $\pounds 2.80$.

TRANSISTOR VHF pwr type 2N3375 stud mt 7.5w at 100Mc/s 3w at 400Mc/s new £1.80 ea.

BATTERIES sealed lead acid type 6v rechargeable 1.8 A/Hr size 22 \times 2 $^{\prime\prime}$ new £5.40.

RECEIVER UNIT single channel crystal controlled for use in range 225 to 400Mc/s double superhet 21 min valves 230v 50c/s I/P 19" rack mt wich circ 430.

FREQ METERS type BC221 125Kc to 20Mc/s req 135v HT & 6.3v with handbook & charts few only $\pounds 27$.

DIODES power types 100 PIV 10 amps 4 for £1.60. 1000 PIV 10 amps 4 for £2.50 both new full spec. C.R.T.s

CV1746 6 $\frac{1}{2}$ " P.I trace CRDF tube £6, 5CP1 5" P.I trace £7. 5ADP1 5" P.I trace £8.50 all electrostatic types new.

C.R.T. VISOR complete with magnifier & padded eye piece approx size 5 \times 4 \times 7" okay for colour slide viewer new £3.

TRANSFORMERS HT type Pria 230v sec 1125-0-1125v at 565Ma new £12-50, Isolating type pria 240 sec 120v at 60 watts enclosed new £3. Auto type 230/115v at 1 Kva £13.

RECTIFIER UNIT general purpose unit made for operation of Army telephone & teleprinter units 1/P 200/250v o/p dual 12v DC at 3 amps ea circ. connected for 24v ct complete in case very conservative rating will do 8 amps okay for battery charger with circ £8-50.

TEST SET special purpose complete in case size $14 \times 16 \times 10''$ contains large number of good quality parts as follows, HD rotary swts, plugs & sks, trips, power filters, relays, ind lamps, posts, small 400c/s variat cet cf 16.

TEST SET special purpose contains 4 panel meters as follows, 0 to 500Ma x2, 0 to 1 amp DC mirror scale, 0 to 40v DC, plus lamps, tog swts, fuse holders etc in case size $17 \times 12 \times 7^{\prime\prime}$. 69.

TEST SET M.7C used for testing telephone circs contains mains p.u. meter 200 Ua $3\frac{1}{4}$ ", 3x AF atten swt 10, 40 & 60Db, valve amp, filters etc in neat case with front cover & circ size 19 \times 9 \times 9" £10-80.

TEST SET I.F. used to check 30Mc/s head amps, contains mains p.u. with trans 225-0-225v at 70 Ma 6-3v etc, also high grade 100 Ua meter scale 0 to 100 4" dia, 30 Mc/s amp, misc coax fittings etc in case size 19 \times 7 \times 10" f10-80.

CRYSTALS mixed type 10X & 10X] in range 5 to 8Mc/s 20 for £2-20.

BLOWER MOTORS single ended 50 cfm outlet 2 \times 1²/₂" 240v new £6.60.

Above prices include post & V.A.T. good ex equipment unless stoted new, SAE for list 19 or enquire. Shop open Tues to Sat.

A. H. SUPPLIES 122 Handsworth Road Sheffield S9 4AE

Phone 444278 (0742)



Practical Wireless, July 1978

RADIO EXCHANGE LT



NEW ELECTRONIC MASTER KIT

NEW ELECTRONIC MASTER KIT WITH SPECIAL V.H.F. TUNER MODULE TO CONSTRUCT. A completely Solderless Electronic Construction Kit, with ready drilled Bakelite Panels, Nuts, Bolts, Wood Screws etc. Also in the kit: Transistors, Capacitors, Resistors, Pots, Switches, Wire, Sleeving, Knobs, Dials, S" × 3" Loudspeaker and Speaker Case, Crystal Earpiece, etc. Also ready wound Goils and Ferrite Rod Aerial. These are the Projects you can build with the components supplied with the kit, together, with comprehensive Instruction Manual Pictorial and Circuit Diagrams. PROJECTS: V.H.F. Tuner. Module ★ A.M. Tuner Module ★ M.W. L.W. Diode Radio ★ Six Transistor V.H.F. Earpiece Radio ★ One Transistor M.W. L.W., Radio ★ Two Transistor Push Pull Amplifier ★ Eight Transistor V.H.F. Loudspeaker Receiver ★ Variable A.F. Oscillator ★ Jiffy MultTester ★ Four Transistor and Diode M.W. L.W. Radio & A.F. R.F. Signal Injector ★ Five Transistor Push Pull Amplifier ★ Sensitive Hearing Aid Amplifier ★ Three Transistor and Diode Short Wave Radio ★ Signal Tracer ★ Three Tran-sistor Push Pull Amplifier ★ One Transistor Class A Output Stage to drive Loudspeaker ★ Sensitive Tran-sistor Push Pull Amplifier ★ Three Transistor Code Practice Oscillator ★ Jive Transistor Regenerative Radio ★ Five Transistor V.H.F. Tuner ★ Three Transistor Code Practice Oscillator ★ Five Transistor Regenerative Radio ★ Five Transistor M.W. L.W. and Diode Tuner ★ Five Transistor Code Practice Oscillator ★ Five Transistor Regenerative Radio ★ Five Transistor A.H.F. Tuner ★ Three Transistor Code Practice Oscillator ★ Five Transistor Regenerative Radio ★ Five Transistor M.W. L.W. Radio with Loudspeaker Push Pull Output £14.99 + P&P £1-10 ★ One Transistor Home Broadcaster.



SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio ampli-fier. Brand new components throughout. 5 silicon tran-

fer. Brand new components throughout. 5 silicon tran-throughout. 5 silicon tran-throughout. 5 silicon tran-transistors pius 2 power output ransistors pius 2 power output ransistors pius 2 power output full wave rectification. Output approx. 13 watts r.ms. into 8 ohms. Frequency re-sponse 12Hz 30KHz ± 3db. Fully integrated pre-amplifier stage with suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output pluss. Overall scutcheon panel, input and output plugs. Overall size 3^* high $\times 6^*$ wide $\times 7\frac{1}{2}^*$ deep. AC 200/250V. PRICE £15.00. P. & P. £1.20.

HARVERSONIC MODEL P.A. TWO 7FRO



TWO ZERO An advanced solid state general purpose mono amplifier suitable for Public Address system. Disco, Guitar, Gram, etc. Features 3 individually con-trolled inputs (each input has a separate 2 stage pre-amp). Input 1, 15mv into 47k. Input 2, 15mv into 47k. (suitable for use with mic, or guitar etc.). Input 3 200mv into 1 mer. suitable for gram. tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240v. Size approx. 124" w. x5" h. 71#"d. Special introductory Price 228:00–22: 50 cart. & pkg. Mullard LP1159 RF-IF Module 470 kHz £2: 25 -Special introductory Price $\pm 28^{-00} - 22^{-30}$ carr. & pkg. Mullard LP1159 RF-1F Module 470 kHz $\pm 22^{-25}$ P,&P, 20p. Full spec, and connection details supplied. Pye VHF/FM Tuner Head covering 88-108 M/Hz. 10 -7 M/Hz 1.F, output, 7-8 Volt + earth. Supplied pre-aligned, with full circuit diagram with precision-geared FM gang and 323PF + 323Pf A.M. Tuning gang only $\pm 3^{-15} + P$, & P, 35p.

£3:15 + P. & P. 35P. STEREO DECODER SIZE 2' \times 3' \star 1' ready built. Pre-aligned and tested for 9:16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (in-clusive of hints and tips) supplied. £6:00 plus 20p. P. & P. Stereo beacon light if required 40p extra.

All prices and specifications correct at time of press and subject to alteration without notice.

MAINS OPERATED SOLID STATE **AM/FM STEREO TUNER**



AM/FM STEREO TUNER 200/240V Mains oper-ated Solid State FM AM Stereo Tuner. Covering W.W. A.M. 540-1605 KHz VHF/FM 88-108 MHz. Built-in Ferrite rod aerial or M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp voltage adjustable by pre-set control. Max o'p Voltage 600m/v RMS into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8½ w × 4th × 9½ d approx.

91"d approx. LIMITED NUMBER ONLY at £28.00 + £1.50 P. & P.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in, wide, Our price £2.00 yd, length, P. & P. 50p per yd. (min. 1 yd.). S.A.E. for samples. 10/14 WATT HI-FI AMPLIFIER KIT

10/14 WATT HI-FI AMPLIFIER KIT A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super repro-duction of both music and speech with negligible hum. separate inputs for mike and gram allow records and announcements to follow each other. Fully shroudd section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 25p + SAE (Free with parts). All parts sold separately. ONLY £13-50 P. & P. £1-40. Also available ready built and tested £18-00P. & P. £1-40.

built and tested £18.00 P. & P. £1.40. "POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER Size 114" × 14 $\frac{1}{16}$ · 1 $\frac{1}{16}$ deep. Weight 1902. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20kHz. Can be mounted on ceilings, walls. doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £8.40 each + p. & p. (one 90p, two £1.10). Now available in either 8" round version or 41" < 81" rectangular. 10 watts RMS 60Hz-20KHZ £5.25 + P. & P. (one 65p, two 75p). ERECIAL OFFER

SPECIAL OFFER, 61° long throw, roll surround, ceramic magnet 8 ohm 10 watt speaker chassis. Specially suitable for Hi Fi. £3. 95 - 75p P. & P. 2" PLASTIC CONE HF TWEEFER 4 ohm, £3.50 per matched pair + 50p P. & P. HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridges. Very simple to modify to suit magnetic cartridges. Very simple to ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts-no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response: $\pm 3dB 12-15,0000$ Hz. Sensitivity: better than 80mV into IM Ω : Full power bandwidth: $\pm 3dB$ 12-15,000 Hz. Bass boost approx. to $\pm 12dB$. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v, at 1 0 amp. Overall Size 12^w, $\times 8'd. < 21^{w}$, Polly detailed 7 page construction manual and parts list free with kit or send 25p plus large 5.A.E. AMPLIFIER KIT ... £13:50 P. & P. 80p (Magnetic input components 33p extra) POWER PACK KIT ... £5:50 P. & P. 95p SPECIAL OFFER—only £23:75 if all 3 items ordered at one time plus £1:25 p. & p.

 $\begin{array}{c} CABINE1 & \ldots & \pounds 5 \cdot 50 \ P, \& P, 95p \\ SPECIAL OFFER—only \pounds 23 \cdot 75 \ if all 3 \ items \\ ordered at one time plus \pounds 1 \cdot 25 \ p, \& p, \\ Full after sales service \\ Also avail, ready built and tested \pounds 31 \cdot 25, P, \& P, \pounds 1 \cdot 50, \\ \end{array}$

Also avail. ready built and tested £31 · 25, P. & P. £1 · 50. HARVERSONIC STEREO 44 A solid state stcreo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets & 5 pin din tape rec./play socket are mounted on the printed circuit panel, size approx, 91 · 21 · 1 max, depth. Supplied brand new & tested. with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £9 · 00 plus 50p . & P. Mains transformer with an output of 17v a/c at 500m a can be supplied at £1 · 50 + 40p P & P if required. Full connection details supplied. HA34 3 Valve Audio Amp. 41 w. output ready built and

 $\begin{array}{l} \hline HA34 \ 3 \ Valve \ Audio \ Amp. \ 4 \ w. \ output \ ready \ built \ and \ tested \ \$8 \cdot \$0 + \$1 \cdot 40 \ P. \ \& P. \ Also \ HSL \ 'FOUR' \ amplifier \ kit. \ \$8 \cdot 00 \ + \ \$1 \cdot 40 \ P. \ \& P. \end{array}$

ALL ENOURIES.

PLEASE NOTE: P. & P.

CHARGES OUOTED APPLY TO

U.K. ONLY, SEND SAE WITH

HARVERSON SURPLUS CO. LTD. (Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19. Tel.: 01-540 3985 A few minules from South Wisneledon I use Station. Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday. Closed Wednesday.

J. BIRKETT Radio Component Suppliers 25 The Strait, Lincoln LN2 1JF TEL: 20767 14/ 125v.w. 1% CAPACITORS at 10p each. 6 TO 1 FRICTION SLOW MOTION DRIVES @ 60p ea. 10-7 MHz CRYSTAL FILTERS B.W. ± 15 KHz @ 61 80. 10-7 MHz CRYSTAL FILTERS B.W. ± 7-5 KHz @ 63. MOS PRE AMPLIFIER I.C. TAA 330 with data @ 33p. LARGE FLANGE 1000pf SOLDER.IN FEED THRU's 6 for 18p. 20 PHOTO TRANSISTORS AND DARLINGTONS Assorted untested for fi

MOS PRE AMPLIFIER I.C. TAA 330 with data @ 33p. LARGE FLANGE 1000pf SOLDER.IN FEED THRU's 6 for 18p. 20 PHOTO TRANSISTORS AND DARLINGTONS Assorted untested for £1. 30 VARI-CAP DIODES similar to BA 102 etc Untested for 57p. ERIE RED CAP. 010/ 100v.w. CAPACITORS for 35p each. 10000/ 40v.w. ELECTROLYTICS at 3 for 33p. 6 WATT WIRE WOUND VARIABLE RESISTORS 1-2K @ 22p. 100 C 280 CAPACITORS Assorted for 57p. 101 LINE FUSEHOLDERS for 13⁵ fuses at 22p. 102 C 280 CAPACITORS Assorted for 57p. 103 LINE FUSEHOLDERS for 13⁵ fuses at 22p. 104 C 280 CAPACITORS Assorted for 57p. 104 LINE FUSEHOLDERS for 13⁵ fuses at 22p. 105 C 280 CAPACITORS Assorted for 57p. 105 LINE FUSEHOLDERS for 13⁵ fuses at 22p. 106 C 280 CAPACITORS Assorted for 57p. 107 C 280 CAPACITORS Assorted for 57p. 108 LINEED URE STALS 28 KHz. 28 5 KHz. Both at 50p each. 108 LINEED URE STALS 28 KHz. 28 5 KHz. Both at 50p each. 108 LINEED URE STALS 28 5 KHz. 20 for 300 with data © 50p. 108 LINEED URE BAND AMPLIFIER © 30p. 109 WITH ANSISTORS at 7 for 50p. 100 C 71 at 100 for 50p. 100 LINE TANNSISTORS at 7 for 50p. 100 LINE TANNSISTORS at 7 for 50p. 100 LINED DATE DATE TO 100 for 100, 1 to 3 for 00 p. 100 MW UNMARKED GOOD ZENERS 3 for 6 for 30p. 100 ASSORTED TANALUM BEAD CAPACITORS for £1 s0. 107 ASSORTED BANDED WHF FETS at 12 for £1. 100 ASSORTED TANALUM BEAD CAPACITORS for £1 s0. 107 LAPACITORS PMT-2P I I I 100 v.w. at 20p doz. 14" COLL FORMERS ASSORTED TANSISTORS at 50p. 100 LL LM 380 with circuits at 80p. 101 LLFORMERS ASSORTED TANSISTORS wITH COVER at 35p per set. 101 LAPA PRE-SIMILIER AT 27p. 102 WATT ZENERS ASSORTED TANSISTORS at 20p doz. 14" COLL FORMERS ASSORTED TANSISTORS at 20p doz. 14" COLL FORMERS ASSORTED TANSISTORS WITH COVER at 35p per set. 101 LLAPA PRE-AMPLIFIER I.C. TAA 433 with data @ 40p. 11T - 13U 400v.w. POLYESTER CAPACITORS at 20p doz. 14 AINS TRANSFORMER 240v input 55 volt 10 amp out @ 55 .50. 150 AC 124 FRANSISTORS R 27 per set. 101 LLAPA PRE-AMPLIFIER I.C. TAA 433 with data@ 40p. 11T - 13U 4000 w.W. POLYESTER CAPACITORS at 20p doz. 1 MAINS TRANSFORMER 240v input 24 volt Tapped at 14 volt 1 amp @ £1.25 (25p post and packing). JACKSON TYPE 3pf AIR SPACED VARIABLE CAPACITOR @ 75p. ITT 1uf 100v.w. MINATURE POLYESTER CAPACITORS 20p doz. MULLARD 455 KHz PLUS 10.7MHz I.F. MODULE with data @ £4. 100uf 100v.w. ELECTROLYTICS at 60p each. Please add 20p for post and packing on UK orders under £2 unless otherwise stated. Overseas orders at cost.

SINCLAIR PRODUCTS* PDM35 digital multimeter £25-95. Mains adaptor £3-24. Deluxe padded carry case £3-25. 30kV probe £18-38. New DM235 digital meter P.O.A. Cambridge scientific programmable calculator £13-15. Prog. library £4-65. Microvision tv £200.

CUT PRICE TELETEXT Texas instruments XM11 tilax module £126. Labgear 7026 ready to use, attrac-tively cased, complete unit. Plugs into tv aerial socket. Full colour. Remote control page select £355.

Control page select 2333. TV GAMES KITS Send see for free data. Tank Battle chip AV-3-8710 plus economy kit £17-95. Stunt Motor Cycle chip AY-3-8760-1 plus economy kit £17-95. 10 game paddle 2 chip AY-3-8600 plus economy kit £14-70. AY-3-8500 chip plus economy kit £14-75. Modified Shoot kit £4-95. Rifle kit £4-95. Colour generator kit £1-50. Joystick controls £1-90. 4-43Mhz pal crystals 90p.

ASSEMBLED TV GAMES All attractively cased. 4 game black and white model (tennis, fotball, squash and pelola) £11 •5. 6 game colour model with pistol attachment £21 •5. Tank Battle game £39 •55. Stunt Motor Cycle game £33 •55. Stabilized mains adaptor for all games £3 •10.

MAINS TRANSFORMERS 6-0-6V 100ma 78p. 1{a £2·35. 6·3V 1}a £1 89. 6-0-6V 75ma 78p. 1]a £1 99. 2a £2:40. 12-0-12V 50ma 78p. 100ma 90p. 1a £2·49. 13V 1a 95p. 15-0-15V 1a £2·79. 30-0-30V 1a £3·59.

JG12, JC22 AND JC40 AMPLIFIERS A range of integrated circuit audio ampli-fiers supplied with free data and printec circuits. JC12 6 watts £1:60. JC20 10 watts £2:95. JC40 20 watts £4:20. Send sae for free data on our range of matching power and preamp kits.


FERRANTI ZN414 IC radio chip £1.05. Extra parts and pcb for radio £3.85. Case £1. Send sae for free data.

PRINTED CIRCUIT MATERIALS PC Etching kits: Economy £1-70, Standard 53-12. 50 ag ins pcb 40p. 1 lb FeCi £1-65. Etch resist pens: Economy 45p, Dalo 73p. Small drill bit 20p. Etching dish 68p. Laminate cutter 75p.

SWANLEY ELECTRONICS


DEPT, PW, PO Box. 68, 32 Goldsel Rd., Swanley, Kent BRs STQ Mail order only. Please add 30p to the total cost of order for postage. Prices include VAT. Overseas customers deduct 7% on items marked * and 11% on others. Official credit orders welcome.

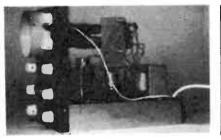LOCK! Here's how you master electronics.the practical way.




Build an oscilloscope.

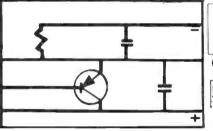As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



2 Read, draw and understand circuit diagrams.

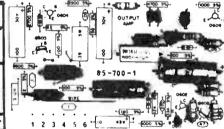In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computors and countless other electronic devices and their servicing procedures.



This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of

an absolute minimum of theory.

employed electronics engineer.

every course.

3 Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v etc.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.



To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

British National Radio & Electronic School


P.O. Box 156, Jersey, Channel Islands.

NAME ADDRESS

WB7 Block caps please

Practical Wireless, July 1978

World Radio History

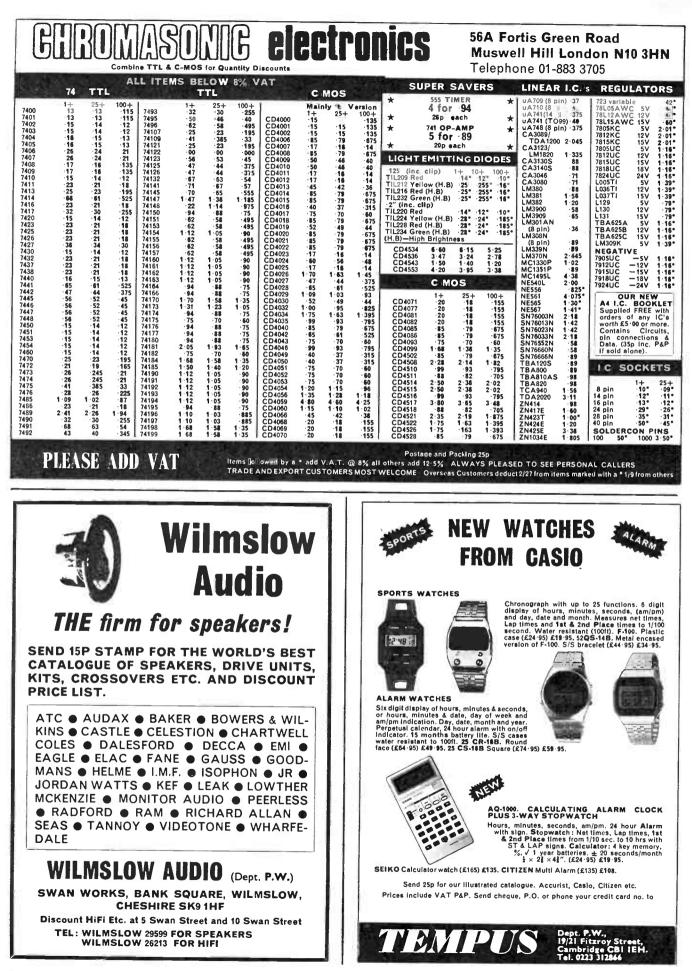

15—240 Watts! The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all i.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier. HY5 **Preamplifier** FEATURES: Complete pre-amplifier in single pack-Multi-function equalization-Low noise -Low distortion-High overload-Two simply combined for stereo. APPLICATIONS : HI-Fi-Mixers-Disco-Guitar and Organ-Public address APPLICATIONS: HI-Fi-Mixers-Disco-Guitar and Organ-Public address SPECIFICATIONS: INPUTS. Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxillary 3-100mV; Input Impedance 4 7%Q at 14Hz. OUTPUTS. Tape 100mV; Main output 500mV R.M.S. ACTIVE TONE CONTROLS. Trebie ± 12dB at 10kHz; Bass ± at 100Hz. DISTORTION. 0-1% at 11kHz. Signal/Noise Ratio 68dB. OVERLOAD. 38dB on Magnetic Fick-up. SUPPLY VOLTAGE ± 16-50V. Price £5-22 + 65p VAT P&P free. The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board. 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date **HY30** technology available 15 Watts FEATURES: Complete Kit-Low Distortion-Short, Open and Thermal Protection-Easy to Build. APPLICATIONS: Updating audio equipment—Guitar practice amplifier—Test amplifier— audio oscillator. SPECIFICATIONS: OUTPUT POWER ISW R.M.S. into 8Ω: DISTORTION 0-1% at 1-5W. INPUT SENSITIVITY 500mV. FREQUENCY RESPONSE 10Hz-16kHz-3dB. SUPPLY VOLTAGE ± 18V. Price £5-22 + 65p VAT P&P free. into 8Ω HY50 The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World. **HY50** remains and robust High Floetity modules in the World. FEATURES: Low Distortion—Integrat Heatsink—Only five connections—7 amp output tran-sistors—No external components APPLICATIONS: Medium Power Hi-FI systems—Low power disco—Guitar amplifier SPECIFICATIONS: INPUT SENSITIVITY SOMW OUTPUT POWER 25W RMS Into 8Ω LOAD IMPEDANCE 4-16Ω DISTORTION 0-04% at 25W at 16H 25 Watts into 8Ω at 14Hz SIGNAL/NOISE RATIO 75dB FREQUENCY RESPONSE 10Hz-45kHz-3dB. SUPPLY VOLTAGE ± 25V SIZE 105 50 25mm Price £6·82 + 85p VAT P&P free The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in HY120 modular design. FEATURES: Very low distortion—Integral heatsink—Load line protection—Thermal protec-tion—Five connections—No external components APPLICATIONS: HI-Fi—High quality disco—Public address—Monitor amplifier—Guitar and 60 Watts into 8Ω organ SPECIFICATIONS INPUT SENSITIVITY 500mV. OUTPUT POWER 60W RMS into 8Ω LOAD IMPEDANCE 4-16Ω DISTORTION 0-04% at 60W at 14Hz SIGNAL/NOISE RATIO 90dB FREQUENCY RESPONSE 10Hz-45kHz- 3dB SUPPLY VOLTAGE ±25V SIZE 114 50 85mm Price £15-84 + £1 27 VAT P&P free. The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true HI-Fi performance. **HY200** FEATURES : Thermal shutdown-Very low distortion-Load line protection-Integral heatsink No external components APPLICATIONS: Hi-Fi-Disco-Monitor-Power slave-Industrial-Public Address הר העשמים אוירו שווגנס Monitor Power slave-Industrial Public Address SPECIFICATIONS INPUT SENSITIVITY 500mV OUTPUT POWER 120W RMS Into 8 גע LOAD IMPEDANCE 4-16 גע DISTORTION 0 05% at 100W at 114L2. 120 Watts into 8Ω at 1kHz. SIGNAL/NOISE RATIO 96dB FREQUENCY RESPONSE 10Hz-45kHz-3dB SUPPLY VOLTAGE ±45 v SIZE 114 50 85mm Price £23-32 + £1-87 VAT P&P free. The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4111 it has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to tead the market as a true high power hi-fidelity power module. **FEATURES:** Thermal shutdown—Very low distortion—Load line protection—No external **HY400** 240 Watts APPLICATIONS: Public address—Disco—Power slave—Industrial into 4Ω SPECIFICATIONS - Public autors = Disco = Power stave=industrial SPECIFICATIONS OUTPUT POWER 240W RMS into 4 Ω LOAD IMPEDANCE 4-16 Ω DISTORTION 0 1% at 240W at 1kHz SIGNAL NOISE RATIO 94dB FREQUENCY RESPONSE 10Hz-45kHz – 3dB SUPPLY VOLTAGE ±45 V INPUT SENSITIVITY 500mV SIZE 114 100 85mm Price £32 17 + £2 57 VAT P&P free. PSU36 suitable for two HY30's £5 22 plus 65p VAT. P/P free. PSU50 suitable for two HY50's £6 82 plus 85p VAT. P/P free. PSU70 suitable for two HY120's £13'75 plus £1'10 VAT. P/P free. PSU30 suitable for one HY200 £12'65 plus £1'01 VAT. P/P free. PSU3180 £23'10 + £1'85 VAT. B1 £0 44 + £0'06 VAT. POWER SUPPLIES TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS I.L.P. ELECTRONICS LTD., CROSSLAND HOUSE, NACKINGTON, CANTERBURY, KENT, CT4 7AD. Please Supply I.L.P. ELECTRONICS LTD.. Total Purchase Price I Enclose Cheque 🔲 Postal Orders 📋 Money Order []

CROSSLAND HOUSE, NACKINGTON, CANTERBURY, KENT, CT4 7AD.

 Total Purchase Price

 I Enclose Cheque

 Please debit my Access account

 Barclaycard account

 Account number

 Name and Address

 Signature

Regd No. 1032630.

GREENWELD 443 Millbrook Road Southamoton SO1 OHX Tel:(0703) 772501

All prices quoted include VAT. Add 25p UK/BFPO postage. Most orders des-patched on day of receipt. SAE with enquiries please. MINIMUM ORDER VALUE £1. Official orders accepted

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL **HELP YOU**

- ★ SAVE ON TIME—No deloys in waising for parts to come or shops to open!
- * SAVE ON MONEY-Bulk buying means lowest prices-just combare with others!
- * HAVE THE RIGHT PART-No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC, BRAND NEW, MARKED DEVICES-SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

SENT BY RETURN OF DOST. VAT INCLUSIVE PRICES. Not solve the provided and the second s

£6:00 K022 Extended range, total 850 resistors from 1R to 10M £8:30 K041 Zener diodes, 400mW 5% BZY88, etc. 10 of each value from 27V to 36V, E24 series. Total 280 for £15:30 K042 As above but 5 of each value £8:70

EDGE CONNECTORS

EDGE CONNECTORS Special purchase of these 0.1° pitch double-sided gold-plated connectors enables us to offer them at less than one-third their original list price! 18 way 41p; 21 way 47p; 32 way 72p; 40 way 90p.

SOLAR CELLS

As used on space labs. etc., these tiny cells give 50uA (au 0.5V in sunlight, Ideal for powering small C-MOS pro-jects, etc. Can be banked together for greater power output. Size 19 × 6-5mm. 3 for £1; 10 for £3; 25 for £7; 100 for £25.

POWER PACK

Wood grained metal case 90 × 80 × 75mm containing mains transformer giving 6V & 200mA, 2 co-ax. sockets, PC board with 11²⁷ fuseholder R's C's, etc. Only 75p.

S-DECS & T-DECS

S-DEC Breadboard T-DEC Breadboard

£3-25 £4-20

SIRENS

Work off 4 \times HP7 batteries, emit very loud noise. Overall size 110 \times 75 \times 60mm. Use as Burglar Alarm in car, house, workshop, etc. ONLY £1.95.

PC ETCHING KIT MK III Now contains 200 sq. Ins. copper clad board, 1lb. Ferric Chioride, DALO etch-resist pen, abrasive cleaner, two mini-ature drill bits, etching dish and instruc-tions. £3.4) tions. £3-9)

SEND 455 FOR OUR 1977/8 CATA-LOGUE. CONTAINS 500 DISCOUNT VOUCHERS. AMENDMENT SHEET No. 2 GIVES DETAILS OF OVER 100 ITEMS SLASHED 539(III (Send SAE If you've stready got cat.)

Our latest Bargain Sheet is FREE, send SAE for your copy. DARLINGTON COMP PAIR

BD695A and BD696A-45V 8A 70W plastic powerll gain 750 @ 4A. PNP-NPN pair £1-50.

from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale ilst now available for bona-fide traders. Surplus com-ponents always wanted.

	VEROCAS	ES
Plastic	top and bottom al	ly panels front
and ba		
1237	154 × 85 × 40	£2-53
1238	154 × 85 × 60	£2.79
1239	154 × 85 × 80	£3-32
3007	180 × 120 × 40	£3-30
3008	180 × 120 × 65	£3-50
3009	180 × 120 × 90	£3-74
410	205 × 140 × 40	£3-51
411	205 × 140 × 75	£4-05
412	205 × 140 × 110	£5-12
VE		DOVEO
	RO PLASTIC	
Profess	sional quality two to	one arey noty-
tivrene	with threaded leas	ste les porte
Profess Styrene	sional quality two t with threaded inse	one grey poly- erts for mount-

 Styrene with threaded in PC boards

 Ing PC boards

 2518
 120 × 65 × 40

 2520
 150 × 80 × 50

 2522
 188 × 110 × 60
 £2-17 £2-45 £3-23 SLOPING FRONT BOXES 1798 2528 Pottir 171 × 121 × 75/37 · 5 £4 · 19 220 × 174 × 100/53 £8 · 90 box. 71 × 49 × 24mm black or

Potting box. 71 × 49 × 24mm black or white 40p Hand controller box 94 × 61 × 23mm White 64p

We keep a very large range of VERO products, including their recently introduced G range of cases and Series II boxes. SAE for their catalogue.

VEROBOARD VEROBOARD Our packs of vero oficuls are one of our biggest sellers—and no wonder, they are amazing valuel! Each pack contains 7 or 6 pieces to make up a total area of 100 sc. ins. All packs are the same price. £1:30 each and are available as follows:

Pack A all 0-1" pitch Pack B all 0-15" pitch Pack C mixed 0-1 & 0-15" Pack D all 0-1" plain

Also available by weight 11b £3-95 10lbs £32-50

Regular size vero 17×33×0-17 £2:00, 10 strips £15 17×33×0-157 £1:76; 0-17 plain £1:63 DIP Breadboard size 6, 15×4-5", can accommodate 20×14 pin ICs £2-35 VQ Board, size 148 × 75mm 0.1" pitch. Copper strips in rows of 4 to facilitate construction with IC's. Layout sheet provided \$5p

VERO PINS AND TOOL

Spot face cutter for 0.1 or 0.15 pitch 75p 0.1" pins single sided 30p/100 0.1" pins double sided 35p/100 0.15" pins single sided 30p/100 0.15" pins double sheets 35p/100

 Algorithm
 Algorithm

 LOW COST PLASTIC BOXES

 Made of high impact ABS. The lids are r(lained by 4 screws into brass inserts. [rterior of box has PCB guide slots (except V219)

 V210
 83 × 62 × 40mm black

 V213
 100 × 15 × 40mm black

 V216
 120 × 100 × 45mm white

 V218
 120 × 100 × 45mm black

CALCULATOR CHIP

Type C500 by GL 4 function + constant. 8 digit. Multiplexed output for simple keyboard Interfacing 24 pin DIL. With comprehensive data + socket £1 50. With

comprehensive data + socket £1-50. **RESISTOR OFFER.** Miniature 1W 5% carbon film, but the leads, although full length have been preformed for vertical mounting. Now in the following values only: 68R, 150R, 330R, 390R, 470R, 1k, 1k, 2 k7, 3k9, 5K6, 15K, 22K, 27K, 3K, 68k, 100K, 470K, 820K, 1M—19 velues altogether. 100 off each value, total 1300 resistors for £6. Or 1000 off each value, total 13000 resistors for £45 (this works out at 0-2368p per resistor!!)

SPECIAL TRANSISTOR **OFFERS**

Plastic versions of these popular types. BC108-9. BCY10-71-72 at very low prices. PN108 (BC108) 18 for £1 PN107 (BCY70) 14 for £1 PN172 (BCY72) 15 for £1 PN179 (BCY71) 14 for £1	
Complementary Power Pair. BD525 & BD526. Motorola plastic power, 60V 2A devices, normally 94p pair. Special cfler price 50p pair.	
Small signal PNP transistors, like 2N3702 (Marked MSPS1218) 20 for £1.	
TANT BEAD CAPS-4-7µF 50V, nor- mally 14p each. Our special offer price 12 for £1.	

The Antenna that Hertz missed out on!

We suppose it was quite an achievement to predict radio-wave transmission and then devise a shockexcited VHF dipole in those far off days, but what a time the Grand Old Man could have had on the range -5-30 MHz. if only he'd had a Joystick VFA (Variable Frequency Antenna) to play with. And what's more, whilst his original experiment was transmission across a room, with the Joystick many delighted users have found an indoor installation (it's only 7' 6" long) has got them better DX (receiving and transmitting) than experienced on previous antennae.

In use by Amateur Transmitting and SWL Stations world-wide and in government communication.

SYSTEM "A"

£36.00

250 w. p.e.p. OR for the SWL.

SYSTEM "J"

£42.60

500 w. p.e.p. (improved 'Q' on receive).

PARTRIDGE SUPER PACKAGES

COMPLETE RADIO STATIONS FOR ANY LOCATION All Packages feature the World Record Joystick Aerial (System 'A'), with 8ft, feeder, all necessary cables, matching communication headphones. Deliv. Securicor our risk. ASSEMBLED IN SECONDS! BIG CASH SAVINGS

PACKAGE No. I As above with R.300 RX. SAVE £17-28!

£195.00

 $\pounds 210.55$

PACKAGE No. 2 Is offered with the FRG7 RX. SAVE £12-211

PACKAGE No. 3

Here is a lower-price, high-quality package featuring the LOWE SRX30., with all the Partridge extras. SAVE 612-21!

£177.00

RECEIVERS ONLY, inclusive delivery, etc. R.300 £184-50 FRG7 £162-00 SRX30 £146-25

> All prices are correct at time of going to press and include VAT at 121% and carriage.



Just telephone your card number Phone 0843 62535(ext.5) (or 62839 after office hours)



or write for details, send 9p stamp



MAINS TRANSFORMERS

MAINS TRANSFORMERS					
All these have 230/240v	50Hz Primary				
VOLTAGE	CURRENT	REF.	PRICE £1-94		
1v 2·4v	2 amp 5 amp	TM 1 TM 2	£1-62		
4v	7 amp	TM 32	£2.70		
6v	amp 3	TM 3	85		
6-5v	1 amp	TM 37	85		
6·5v	200 ma	TM 21	£1-62		
6 · 5v-0-6 · 5v	100m A	TM 21	£1 ·62		
6-5v-0-6-5v	750m A	TM 7 TM 33	£2-16 £1-62		
6-3v-0-6-3v 6-3v	100mA 2 amp	TM 33	£1-89		
8-5v	1 amp	TM 12	£1-62		
8.5v + 8.5v sep winding	amp 1	TM 12	£1-62		
9v	1 amp	TM 5	£1-62		
9v	1 amp 'c' core	TM 6	£1-80		
9v	31 amp	TM 11	£2·70		
9v	5 amp	TM 38	£3-24		
10v	25 amp	TM 15 TM 15	£4-86 £4-86		
10v-0-10v 12v-0-12v	12¦amp 4 amp	TM 27	£4-32		
12v	amp 1	TM 9	£1-05		
13v	amp	TM 7	£2-16		
12v	1 amp	TM 10	£1-89		
12v-0-12v	50m Á	TM 19	£1-62		
12v-0-12v	1 amp	TM 41	£3·24		
15v tapped 9v	2 amp	TM 11	£2.70		
15v 15v–0–15v	7 amp	TM 27 TM 27	£4·32 £4·32		
15v-0-15v	31 amp 31 amp	TM 35	£4-86		
17v		TM 12	£1-62		
18v	amp	TM 13	£1-90		
20v	amp	TM 14	£1-62		
20v	5 amp	TM 27	£4·32		
20v	121 amp	TM 15	£4-86		
20v-0-20v 13v	6 amp	TM 15 TM 21	£4-86 £1-62		
24v	100mA 1‡ amp	TM 16	£2·12		
24v	2 amp	TM 17	£2.70		
24v + 2v 7 amp	2 amp	TM 39	£2 .97		
24v	4 amp	TM 40	£3-78		
25v	11 amp	TM 18	£2·43		
26v	2 amp	TM 39	£2-98		
30v tapped 24, 20, 15 & 12	31 amp	TM 27 TM 15	£4-32 £4-86		
30v 37v	8 amp 37 amp	TM 34	£31-86		
40v tapped at 30v, 20v & 10		TM 15	£4-86		
50v-2 amp with 6-3v shrou		TM 22	£4-86		
50v	8 amp	TM 29	£11-65		
60v	5 amp	TM 24	£7·02		
75v-3 amp with 6.3v shrou		TM 23	£8-10		
75v	41 amp	TM 24	£7·02		
80v tapped 60v & 75v 100v	4 amp 1 amp	TM 24 TM 25	£7.02 £7.02		
100v-0-100v	1 amp	TM 25	£7.02		
130v tapped 120v	amo	TM 28	£3-78		
200v	amp amp amp	TM 25	£7.02		
250v-0-250v with 6-3v 2A	50mA	TM 36	£3-78		
250v	100mA	TM 36	£3·78		
500v	50mA	TM 36	£3-78		
260v 1 Kv	60mA	TM 26 TM 44	£3·24 P.O.A.		
2Kv		TM 44	P.O.A.		
5Kv	5m A	TM 30	£7.02		
8-5Kv	10m A	TM 31	£10-26		
Quality prices evailable	Plases unlose you		hhe hal		

8°5Kv IMM 1 E10 25 Quality prices available. Please, unless you are calling, add 25% to your order to cover the cost of carriage, Also it you want to collect, telephone the day before. Quick Cuppa. Mini immersion heater, ideal for taking on holiday, for making a "quick cuppa" tea, or for having by the bedside for baby's feed etc. 250w heater @ 230 volts or ap-proximately 90 watts @ 110 volts. Price £2:95. Meson Screwdrivers. Two useful models: - 74" price 78p and

proximately 90 waits (g) 110 voits. Price 22 vs. Neon Screwdrivers. Two useful models: - 74 price 78p and 54° fmA Moving Coll Panel Meter. A large instrument, size approximately 4° square at the front and 4° deep. Intended for panel mounting, its scale is callbrated 0-7 and it was intended to be used as rev. counter. £14 each. Pressure Switch. Adjustable through a range of pressures from where it can be operated by sucking or lowing to approx. 50 psi-10 amp changeover microswitch, metal body with threaded inlet. Price £2:80. Push-Push Switch. Fixed through panel this is a ratchet action, double pole changeover switch, the contacts we understand are hard gold plated. Spindle is j' diameter so that a standard radio knob can be fitted. Price 32p + 3p. Good quantity available at usual discounts. C.R.T. Display Unit. We feel this would be easy to convert to an oscilloscope, it has all the necessary ingredients. It is in a case size 15" × 10" × 11" approx. with a carrying handle and a front protection flap. Plenty of controls and is mains operated through step down transformer. Size of the tube is 3". Price £16"5. VU Meter Edgewise mounting, through hole size 14" × 4" approx: these are 100 micro amp isd and fitted with internal 6 volt bub for scale illumination, also have zero reset. The scale is not calibrated but has very modern appearance. Price £1:45. Casasette Mechanism. Jab. made to rigid specification.

Price 51*85. Cassette Mechanism. Jap. made to rigid specification. These will fit many music centres and cassette players. Chassis size approx. 4⁴ wide by 5¹/₂" deep. 6¹ worder and tape position counter at the rear. The six levers for "play" "last forward". "rewind". "stop", record and eject are all at the front, as is the auto mechanism to stop the motor when tape end is reached. These are new and unused and have record playback and erase heads. Limited quantity. Price

£15-50 ETS:30. Shortened 3kw Tangential Heater. This is in fact near enough the same size as the normal 2kw tangential. Motor runs a bit faster to compensate for the increased heating and the fan impeliers are metal to save any possi-bility of extra heat distorting them. The heater element is tapped so that 1, 2 or 3kw's of heating can be used or of course this will blow cold. Price £8:95, post £1:50p + 12p.

course this will blow cold. Price £8.95, post £1-50p + 12p. Omron 410 Relay. Built like a contactor, this has a clear plastic cover over the working parts but the terminais are all brought out of the front so that connection may be made without removing the cover also the relay may be fitted into position and the wires brought to it afterwards, generously rated at 10 amps the contacts are really more like 15 amps, they are changeover and there are 4 sets of them. A really robust relay which looks as though it will give a lifetime of service. Size $3\frac{1}{2} \times 3^{-} \times 3\frac{1}{2}^{-}$ high. Price £4-50. 8 Track Cartridge Players. In car units with amplifiers but this amplifier may need attention, mechanism guaranteed O.K. £9:00 + 19p.

Low rpm Crouzet Meters. Two more types have just come in; these are 2 rpm and 15 rpm, both 115v motors but as these consume only two to three watts it is a simple matter to divide the mains voltage using a mains working condenser, resistor auto transformer or of course use them in pairs. Price £2.25, £2.00 + 16p each.

12 volt Minlature Relay. Gold plated contacts with plastic dust covers 4 sets of changeover contacts, 90p, bases 45p.

MULLARD UNILEX



postage.

SPIT MOTOR WITH CARTER G/BOX

Probably one of the best spit motors made. Originally intended to be used in very high priced cookers, however tor instance your garden barbeque or to tumbler for stone pollshing; in fact there are no ends ses. Normal mains operation. £4-32. G V التجا

PP3/PP9 REPLACEMENT MAINS UNIT

Japanese made in plastic container with leads size $2^{\prime\prime\prime} \times 14^{\prime\prime\prime} \times 14^{\prime\prime\prime}$, this is ideal to power a calculator or radio, it has a full wave rectified and smoothed output of 9 volts suitable for a loading of up to 100mA. £2:53.

SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will re-ceive an amazing assortment of stations over the 19, 25, 29, 31 metre bands. Kit contains chassis front panel and all the parts £1.94 -crystal earphone 55p including VAT and nostage.

RADIO STETHOSCOPE

Easiest way to fault find, traces signal from aerial to speaker when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Kit comprises transistors and parts including probe tube. twin stetho-set. £3.95.

$\overline{\mathbf{\tau}}$ **BREAKDOWN PARCEL**



BREAKDOWN PARCEL Four unused, made for computer units and these components, unlike those wire ends of usable length. The transis-the diodes have approx. If leads. List of the major components is as follows:-17 assorted transistors-38 assorted diodes-60 assorted resistors and condensers-4 gold plated plugs in units which can serve as multipin plugs or as hook up boards for experiments or quickly changed circuits (note we can supply the socket boards which were made to receive these units). The price of this four unit parcel is £1 including VAT and post (con-bles than value of the transistors or diodes alone). DON'T MISS THIS SPLENDID OFFER.

INFRA RED BINOCULARS

Made for military purposes during and immediately after the last war to enable snipers, vehicle drivers, etc. to see in the dark. The binoculars have to see in the dark. The binoculars have to be fed from a high voltage source (5KV approx.) and providing the objects are in the rays of an infra red beam then the binoculars will enable these objects to be seen. Each binocular eye tube contains a complete optical lens system as well as the infra red cell, technical data on which is available. The binoculars are unused, believed to be in good order. Sold without guarantee.

Price £17:50 per set. Post & VAT £2:50.

SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W). Unit in box all ready to work. £9:95.

-

MINI-MULTI TESTER

10

MINI-MULTI LESTER Amazing, deluxe pocket size pre-cision moving coli instrument-jewelied bearings-1000 opv-mir-rored scale. 11 instant ranges measure:-DC volts 10, 50, 250, 1000 AC volts 10, 50, 250, 1000 DC amps 0-1 mA and 0-100 mA Continuity and resistance 0-150K ohms.

Continuity and resistance or sort coms. Complete with insulated probes. Complete with insulate

FREE Amps ranges kit enable you to read AC current from 0-10 amps, directly on the 0-10 scale. It's free if you purchase quickly, but if you already own a mini tester and would like one send £1:50p.

Terms: Prices include Post & VAT. But orders under £6.00 please add 50p to offset packing. Bulk enquiries-Please Phone for Generous Discounts 688 1833.



IT'S FREE!

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains sell out before our advertisement can appear-It's an interesting list and it's free-just send S.A.E. Below are a few of the Bargains still available from previous lists.

Mains Transformer. Small 2 secondaries, 115 volts at 10 mA and 6·3 volt @ ‡A, a useful transformer for many instruments.

£2.78, 25 Watt Audio Systems in Cabinets. Comprising 8" woofer and terminal connection panel. and 3" tweeter with crossover and terminal connection panel, mounted in simulated teak finish cabinet with fabric front. mounted in simulated teak finish cabinet with fabric front. These are extremely good quality units comparable with those selling at twice the price. Cabinet size approx. 20° high 104° wide and 84° deep, heavy cabinet made of thick block-board. Price £25:00 the pair, well worth your coming in to collect them but if you cannot collect them, then still worth adding £5:00 the pair for carriage. Another Special item, for callers this month is a pen re-corder. Mains operated this is biggish instrument which probably cost originally several hundreds of pounds. We are having a reverse auction on this. The starting price is £50 but the price will come down £5:00 per week until it is sold.

£50 but the price will come down £5.00 per week until It is sold. Opto Electronics. Two special bargains in this field, the OPCP 70, price 75p and the ORP 12, price 85p. Tilt Switch 15 amp. Meant to switch off heater should It be knocked over; this pendulum operated switch is on only when it is in the upright position. It could be incorporated in burglar alarm, car alarms etc. Contacts look quite able to cope with 15 amp loads at mains voltage. Price 50p + 4p. Neon Indicator Lamp. Two features about this particular one are—it has screw down terminal connectors for wiring and is fixed by a single threaded screw. The lens is clear so you could colour to suit your needs. Price 35p. Indicator Lamp Holders. For low voltage lamps (Liliput) type, we have these in five different colours—red, yellow, blue, green and white. Price 35p. Heating Pade. These measure 11' long x §j" wide and are flat. Look rather like pleces of thick blotting oaper. Wire ended 250 watt or joined in series they would be approximately 60 watt each. Dozens ol use. Price 35p. This is control to suit your needs. Price 35p.

Rod Thermostat. For high temperatures up to 550°F. This is adjustable either at the head or remotely by a length of flexible

adjustable either at the head or remotely by a length of flexible drive. Price £2:95. Interval Timer. As used in schools and similar establish-ments to trigger off the bell which sounds the end of lessons, lunch breaks etc. This is another one off item we feel for callers only. It is in polish hardwood case, glass fronted, comprises a 24 hour switch, a large brass disc and other smaller discs on which the time is set out in relatively small intervals and a pair of contacts to switch a bell or something similar at precise times during the week. Price £35:06. Two More Mullard Modules. Pre amp module ref. 1181/1183, stereo or mono. It is on a printed circuit board with wire connections. Supplied complete with connection diagram. Price 39p. Mullard IF Module Type 1181. In a metal case 24" long ×


steres or mono. It is on a printed circuit board with wire connections. Supplied complete with connection diagram. Price 99p. Mullard IF Module Type 1181. In a metal case 2§" long x 1§" wide x [" thick. Can be mounted on a printed circuit board connection to wire lead outs. Price £1:25. Silicon Diodes. Two special bargains this month. 400 volt 1 amp, 10 for £1:25. So volt 1 amp, 20 for £1:25. Large quan-tities available at very much discounted prices. Flax Cable Bargains. Core size Sam 2 white pvc outer, pvc covered cores. Concured coded with the usual blue, brown and green/yellewiPrice too mat voit for £19:25. Electrical thus fulling the training the second stocks of all the mains items fould forring mains and light installations, for example 1181 of the installation tiems we have in time for our next newsletter but if there is anything you are wanting by all means give us a ring. Plastic Case Sections. Small very tough plastic cases at very reasonable prices, always repeatable. The case is 2-11/16" long. Section A is 1° deep and section A 25p. 28p. Computor Caspacitors. Made by famous American com-panies for 15" thick. Price, section A 25p. 30p. Computor Caspacitors. Made by famous American com-panies in omker a large storage bank 15,500 uil 0 volts work-ing, 15 volts surge, 10 for 8£. Alarm Beils. Holiday time contents, at work ing, ideal if you want to make a large storage bank 15,500 uil 0 volts work-ing, 15 volts surge, 10 for 8£. Alarm Beils. Holiday time contents, at windows and doorways. Join them all in scries through al atching circuit os out of a really loud bel or hooter, prices of these various pats are as louse triget mats under carets, at windows and doorways. Join them all in scries through al atching incuiting sound of a really loud bel or hooter, prices of these various pate are as lools.

as ally is to define the set of t

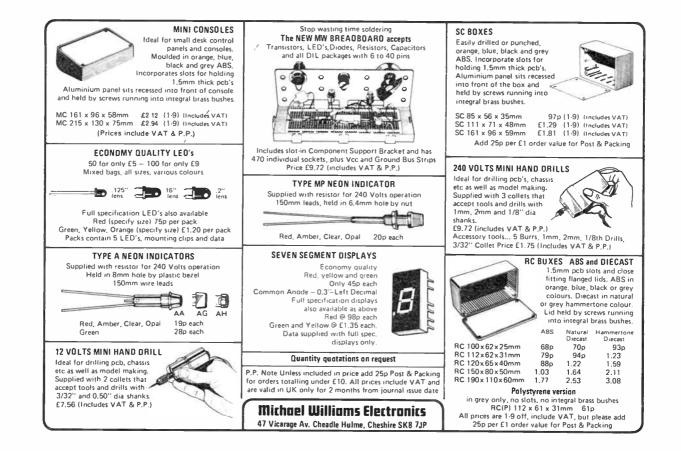Can any reader help We urgently need some reasonably priced decoders to go with the F.M. tuner we have. If you can help us to find a supply we will be very much obliged and will try to do you a good turn some day—thank you.







TTL		CMOS	
0-16 7472 0-19 7473 0-36 7474 0-36 7475 0-19 7476 0-14 7485 0-36 7479 0-36 7479 0-74 7493 0-36 7496 0-36 7496 0-36 7496 0-16 74107	- 0.28 - 0.30 - 0.30 - 0.40 - 0.35 - 0.35	$\begin{array}{cccccccccccccccccccccccccccccccccccc$	
		MISCELLANEOUS	
		U ₂ size N CAD BAT.	£1 · 95
			0.18
50mA	£1-15		
100mA	£1-40	BNC Socket	0.90
1 Amp Sh.	£2 44	Signal Injector	£5-20
1 Amp ,,	£3·12	Multimeter 1,000 OPV.	11
1 Amp "	£3 · 60	ranges (p & p 50p)	£6 · 25
1 Amp ,,	£4 24	Telephone pick-up co	il 0 .92
2 Amp Unsh.	£5·75	- 3″8Ω Spkr. (20p p & p	o) 0·99
2 Amp Unsh.	£7·00	4″8Ω Spkr (30p p & p)	
		0-1mA panel meter	£4·20
). imp. 8Ω. 34v. d	l.c.	240v AC/9v 120mA	£3·78
	6 13 7447 6 13 7451 6 16 7470 6 16 7472 6 18 7472 7472 6 18 7473 7475 755 7475 7475 7475 7475 7475 7475 7475 7475 7475 7475 7475 7475 7475 7475 7475 7475 7475 7477 7	$\begin{array}{cccccccccccccccccccccccccccccccccccc$	0.13 7447 -0.80 4001 -0.17 4047 0.13 7451 -0.16 4002 -0.17 4049 0.16 7470 -0.30 4011 -0.19 4039 0.16 7472 -0.30 4011 -0.19 4039 0.18 7472 -0.30 4014 -0.19 4059 0.38 7474 -0.30 4015 -0.15 4502 0.38 7474 -0.30 4015 -0.15 4502 0.38 7474 -0.30 4015 -0.15 4502 0.38 7474 -0.30 4016 -0.52 4511 0.38 7474 -0.33 4016 -0.52 4516 0.38 7477 -0.45 4022 -0.15 4516 0.35 7417 -0.73 4042 -0.57 4528 0.35 7414 -0.73 4042 -0.57 4528 0.35 7411 0.76 8 pin 741 50mA

Jones Supplies

588, Ashton Rd., Hathershaw, Oldham, Lancs. 061-652-9879



Practical Wireless, July 1978

World Radio History

a tremendous range from Mainline, a division of one of

the largest industrial electronic component distribution groups in the business.

The enormous resources, buying power and organisation guarantees fast reliable service and top quality components at the right price.

Diodes Transistors Integrated circuits Resistors Capacitors Switches Relays Diecast Boxes Potentiometers

Fill in coupon below for the Mainline Components Catalogue.

Mainline

380 Bath Road, Slough, Berks. Tel: 06286 (Burnham) 63616

Manufacturers and trade enquiries invited for larger quantities.

Learn all about **MICROPROCESSORS** with the MOTOROLA Microprocessor Evaluation Design Kit M6800.

featuring:-

- 24 Key Keyboard
- 7 Segment Display
- Cassette Interface
- EROM Expandable
- RAM Expandable
- Wire Wrap Capability
- Parallel and Serial
 Interface Capability
- Single 5 Volt Supply Required
- Layout on Boards
- Documentation

Please send for detailed descriptive leaflet & prices.

Motorola Semiconductors.

We are pleased to announce that in conjunction with our parent company we can offer the complete range of Motorola semiconductors including zener diodes, diodes, transistors, SCR's, Triacs, digital and linear integrated circuits etc. As the available range is far too large to be listed please ask for your specific requirements.

TO: MAINLINE, 380 BATH ROAD, SL Tel: 06286 (Burnham) 63616	DUGH, BERKS.	8
Please send me your latest FREE catalogue	I enclose cheque/P.O. f	
Please send me the following devices		
	Name	
	Address	

The following are the more popular types of 2N TRANSISTORS by well known manufacturers such as Motorola, SGS, RCA, Fairchild. They are brand new and should not be confused with surplus offers often being advertised ! Also we stock, or can obtain, other 2N transistor types not listed below. So please write and let us know what you are looking for.

Please add 8% VAT to your 2N transistor orders, plus 25p per order for postage and packing.

Туре	price	Type	price
2N697 f	E 0.3 6	2N3442	£1.63
2N706	0.37	2N3766	0.86
2N706A	0.24	2N3866	1.05
2N708	0.30	2N4033	0.60
2N718	0.41	2N4123	1.94
2N914	0.32	2N4125	0.20
2N916	0.96	2N4400	0.15
2N918	0.38	2N4401	0.18
2N929	0.24	2N4402	0.21
2N930	0.24	2N4403	0.23
2N930A	0.25	2N4441	1.06
2N1132	0.85	2N4442	1.30
2N1613	1.27	2N4443	1.43
2N1711	0.32	2N4444	1.88
2N1890	0.77	2N4870	0.78
2N1893	0.30	2N4871	0.74
2N2102	0.93	2N4918	0.67
2N2218	0.29	2N4919	0.70
2N2218A	0.32	2N4920	0.74
2N2219	0.30	2N4921	0.63
2N2219A	0.31	2N4922	0.67
2N2221	0.23	2N4923	0.70
2N2221A	0.26	2N5060	0.42
2N2222	0.18	2N5061	0.43
2N2222A	0.21	2N5062	0.49
2N2369	0.21	2N5063	0.52
2N2369A	0.23	2N5064	0.55
2N2646	0.56	2N5088	0.21
2N2904	0.30	2N5108	4.03
2N2904A	0.31	2N5190	0.69
2N2905	0.38	2N5191	0.74
2N2905A	0.32	2N5192	0.80
2N2906	0.23	2N5193	0.75
2N2906A	0.23	2N5194	0.80
2N2907	0.23	2N5195	0.85
2N2907A	0.23	2N5400	0.27
2N3053	0.35	2N5401	0,28
2N3054A	0.84	2N5415	0.81
2N3055	0.89	2N5416	1.11
2N3055H	1.08	2N6027	0.62
2N3439	1.09	2N6028	0.79
2N3440	0.83		

Special quotations for quantities of 25 or more of one type.

Mainline

B. BAMBER ELECTRONICS

Dept. P.W.5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

OSMOR 10V REED RELAY COILS (two 1k ohm coils) to fit 1" reeds (not supplied)

HF CHOKES wound on 1" × 1" long ferrites. 4 for 50p. VHF CHOKES wound on 6-hole tubular

ferrites. 5 for 40p. DUAL TO18 HEATSINKS 1" × 1" × 1"

screw-in clamps, 3 for 50p.

MAINS TESTER SCREWDRIVERS 100 to 500V. Standard size 50p. Large 70p. RADIO PLIERS 5² £1 · 80. 6³ £2 · 00. RADIO PLIERS 54" £1 30. 64" £2:00. DIAGONAL SIDE CUTTERS 64" £2:20. SMALL SIDE CUTTERS LJ2. Standard £4:00. LJ7 (with wire holding device) £4:50. MINIATURE FILE SETS. Set of 6 £2:20. Set of 10 £3:60 (Round, flat, etc.)

TAP AND DIE SETEN (18, etc.) TAP AND DIE SETEN (18, piece) contain 1 each of 0, 2, 4, 6, 8, BA SIZES in Dies, Plug Taps, Taper Taps + American type tap wrench, Ttype tap wr'ch, Die Holder, £12:58. LARGE ELECTROLYTIC PACKS. Con-tain range of large electrolytic capacitors, low and high voltage types, over 40 pleces, 5:00 per pack (+ 121 % VAT). Silder Switches. 2 pole make and break (or can be used as 1 pole change-over by linking the two centre pina), 4 for 50p.

NEW RANGE OF QUALITY BOXES &

AB10 AB13	$5\frac{1}{2} \times 4 \times 1\frac{1}{2}$ 6 × 4 × 2	75p £1·00
AB14	7 × 5 × 21	£1 25
AB15	6 × 6 × 3	£1 · 50
AB16	$10 \times 7 \times 3$	£1.75
AB17	$10 \times 4\frac{1}{4} \times 3$	£1 50
A825	$6 \times 4 \times 3$	£1-2
Very smail		
WB1	5 × 2 ± × 2 ±	75p
WB2	$6 \times 4\frac{1}{2} \times 1\frac{1}{2}$	£1 35
WB3	8 × 5 × 2	£1 80
WB4	$9 \times 5 \pm \times 2 \pm$	£2 00
WB5	$11 \times 6_{\pm} \times 3$	£2 25
WB6	$11 \times 7\frac{1}{2} \times 3\frac{1}{2}$	£2 50
WB7 WB853	$12 \times 6_2 \times 5_2$	£2 85
	8 × 5+ × 3+	£2 2

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED RANGE OF SPEAKERS & MEW CABINETS. BRAND NEW & BOXED

AT BARGAIN PRICES.

A I BARGAIN PRICES. TYPE L2 TRIANGULAR CORNER CABI-NETS. Smart woodgrain Formica type finish with nyton grille. Overall height 23" × 12" wide. Contain three 15 ohm 64" × 4" Full range speakers in parallel + 100V line transformer (easily disconnected for 5 ohm operation). £7:50 each (or 2 for £14:00) + 124% VAT. TYPE MTAC CELLING SERVICE

operation). £7:50 each (or 2 for £14:00) + 121% VAT. TYPE M744 CELLING SPEAKERS. White piastic facia 10" square, for recess mounting into celling, with 8" dia. 15 ohm full range speaker. £4:00 each + 121% VAT. TYPE L4 PORTABLE SPEAKER CABI-NET. Smart woodgrein Formica type finish with nylon grille, 15" high × 14" wide × 7" deep (tapering). Containing 10" round, 15 ohm full range speaker + 100V line trans-former, £7:00 each + 121 VAT. TYPE HT4 HOTEL SPEAKER CABINET, Wood veneered, 121" wide × 51" high × 31" deep, with aluminium grille + volume control and 4 way + off switch panels on front. Very smart. Contains 3 ohm 5" × 3" ellopical speaker + 100V line transformer. £5:00 each + 121% VAT. TYPE 8079 FULL RANGE SPEAKER, 10" dia, 15 ohm, £5:00 each (or 2 for £9:00) + 121% VAT.

SEMICONDUCTORS

SEMICONDUCTORS BSX20 (VHF Osc/Mult). 3 for 50p. BC108 (metal can). 4 for 50p. PBC108 (plastic BC108). 5 for 50p. BCY31 Transistors. 4 for 50p. BCY22 Transistors. 4 for 50p. BCY22 Transistors. 4 for 50p. BCY32 (UHF amp/mixer). 3 for 50p. 2N3819 Fet., 3 for 60p. BC138 DNP SiLICON. 4 for 50p. BC138 DNP SiLICON. 4 for 50p. BC148 NFN SILICON. 4 for 50p. BC148 NFN SILICON. 4 for 50p. BC197 (Metal can) 4 for 50p. BC107 (Metal can) 4 for 50p. BC107 (Metal can) 4 for 50p. GERMANIUM DIODES, approx 30 for 53p.

741CG op amps by RCA, 4 for £1.

RED LEDs (Min type) 5 for 70p.

SPEAKER CABINET TYPE M321, White matt finish wood cabinet with white sprayed cloth grille, 9" × 9" × 4j" deep, containing 6j" dia, 15 ohm full range speaker, with 100V line transformer. £4:50 each or 2 for £8:00 + 1016 V VAT

Ine transformer. £4:30 eacn or 2 tor as yet + 121% VAT. 8-TRACK CARTRIDGE PLAYER UNITS, with internal mains psu and 25 walt mono amplifier (100V line). To play standard 8-track cartridges. All contained in a smart veneered wood cabinet, size approx. 14" wide x 51" high x 11" deep. Supplied with circuits. Brand new and boxed. SPECIAL OFFER £33:00 each. + 121% VAT.

VIDICON SCAN COILS (Transistor type, but no data) complete with vidicon base £6-50 each. Brand New.

12V CONTINENTAL TYPE PLUG-IN RELAYS, 2 pole change-over, 60p each, Bases for above (only supplied with relays)

GLASS BEAD FEEDTHROUGH INSU-LATORS. Solder-In type, overall dia. approx. 5mm, Pack of approx. 50 for 59p. DIE-CAST ALUMINIUM BOXES Send for Latest Price List.

PLASTIC PROJECT BOXES with screw on lids (in black ABS) with brass inserts. Type NB1 approx 3 in x 2 ± in x 1 ± in 45p each Type NB2 approx 3 ± in x 2 ± in x 1 ± in 55p each Type NB3 approx 4 ± in x 3 ± in x 1 ± in 55p each TO3 transistor insulator sets, 10 for 50p

Tost anasistor insulator sets, to for sep PLUGS AND SOCKETS N-Type Plugs 50 ahm, 60p each, 3 for £1:50, PL259 Plugs (PTFE) brand new, packed with reducers, 75p each, SO239 Sockets (PTFE), brand new (4-hole fixing type), 60p each.

SOLDER SUCKERS (Plunger type). Stan-dard Model £5:50. Skirted Model £6. Spare Nozzles 60p each.

Nozzles 60p each. NEW MARKSMAN RANGE OF SOLDER-ING IRONS. S125D 25W 240V £4·00. S125D 25W 240V ±4·50. S125DK 25W 240V + bits etc., KIT £5·30. BENCH STAND with spring and sponge for Marksman Irons £2·70. Spare bits MT9 (for 15W) 60p, MT5 (for 25W) 50p, MT10 (for 40W) 55p. All BD(CS ± 8° VAT

ALL PRICES + 1" VAT.

MULLARD \$5A2 \$5V STABILISER VALVES (Brand New) 78p each or 2 for £1-20 TCP2 TEMPERATURE CONTROLLED

RON

IRON. Temperature controlled iron and PSU. £30+ VAT (£2-40). SPARE TIPS Type CC single flat. Type K double flat fine tip, Type P, very fine tip. £1 each + VAT (8p). MOST SPARES AVAILABLE.

MULTICORE SOLDER + Kg. (1-11b) 60 × 40, 20 s.w.g. on plastic reel £3 + VAT (24p).

WELLER SOLDERING IRONS EXPERT. Bull-in-spotlight Illuminates work. Pistol grip with fingerth trigger. High efficiency copper soldering tip. EXPERT SOLDER GUN \$100D £12-00. EXPERT SOLDER GUN KIT (spare bits, case, etc.) £15-00. Spare bits 40p pair.

MIXED COMPONENT PACKS, contain-ing resistors, capacitors, pots, etc. All new. Hundreds of items, £2 per pack, while stocks last

PUSH BUTTON TELEPHONES A Ten Digit push button intercom telephone with handset, finished in smart grey plastic. Ex-equipment. but good condition only £2-6quipme £2-50 each.

FULL RANGE OF BERNARDS/BABANI ELECTRONICS BOOKS IN STOCK. S.A.E. FOR LIST.

VARICAP TUNERS Mullard type ELC1043/ 05. Brand New, £5:00 + 12+% VAT.

BARGAIN PACK OF LOW VOLTAGE ELECTROLYTIC CAPACITORS. Up to 50V working. Seatronic Manufacture. Approx 100. £1:50 per pack + 121% VAT.


Dublier Electrolytics, 50µF, 450V, 2 for 50p. Dublier Electrolytics, 50µF, 450V, 2 for 50p. Dublier Electrolytics, 100µF, 275V, 2 for 50p. TCC Electrolytics, 100µF, 33V, 3 for 50p. Dublier Electrolytics, 5000µF, 30V, 30r 60p. Dublier Electrolytics, 5000µF, 30V, 60p each. ITT Electrolytics, 6800µF, 35V, 60p each. ITT Electrolytics, 6800µF, 25V, high grade screw terminals, with mounting clips, 50p each.

PLEASE ADD 121% VAT TO ALL CAPACITORS

Terms of Business: CASH WITH ORDER. MINIMUM ORDER 12. ALL PRICES INCLUDE POST & PACKING (UK ONLY) SAE with ALL ENQUIRIES Please PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN CALLERS WELCOME BY APPOINTMENT ONLY



World Radio

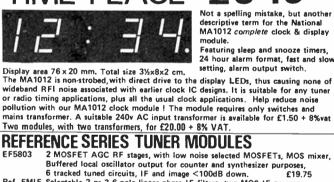

6 tracked tuned circuits, IF and image < 100dB down. £19.75 Ref. FMIF Selectable 2 or 3.6 pole linear phase IF filters, two MOS IF preamps, twin detector coil for 0.07% THD △f 22.5kHz. Noise mute, adjustable range AFC, meter output. £16.25 Ref. MPX With the incomparable HA1196 PLL low noise, wide range decoder IC,

preamp and LC low pass filter on input, twin LC pilot and base-bandpass filters on the output. With 2 x LM380N ICs for monitor amp purposes available on the board. £16.45

Our other	r ranges of	FM and Al	<i>I tuner</i>	modules	available	as before.
EF5801	17,45	EF5600	12.95	7252	26.50	7122 13.22
7030	10.95	EC3302U	7.50	7253	26.50	Most also available in kits:
91196	12.99	8319	11.45	91197	11.35	details in catalogue & price list
COULC	COD LIN	B.4187 (0184	4.0	1.0		

ILS FOR LW, MW, SW 1,2, and 3 now listed in catalogue 30 & 33p ea TOKO 10k series coils now for 1.5 to 30MHz, giving a total coverage in osc and rf coils Low cost meters: Internally illuminated edgewise meters 200uA, and back lit flat face meters 200UA. A wide choice of scales - or material to DIY. Equipment boxes: These must be the best value in ABS (black) equipment boxes with close fitting (flanged) lids. 8x6x4 (cms) 54p ea*, 10x7.5x4 (cms) 66p ea*, and 12x10x4.5 (cms) 76p ea*. Also new stackable component storage boxes and trays. DETECKNOWLEDGEY: theory and practise of metal locator principles including BFO IB, phase angle, pulse induction. A unique reference for users and constructors. £1.00 Our usual unique range of coils, filters etc for radio: from TOKO; 350,000 in stock. The best in linear ICs for RF, HA1137:£2.20; HA1196:£4.20; HA1197:£1.40, plus all common radio and multiplex devices, audio ICs (TBA810AS £1.09), MOSFETs, a unique line in varicap diodes for AM tuning :: see the latest catalogue for details, 45p


Postage 25p per order, VAT 12.5% except where otherwise indicated (*8%). Send to: 2 Gresham Road, Brentwood, Essex. tel (0277) 216029. Only 200m from station !

 $(\mathbf{0})$







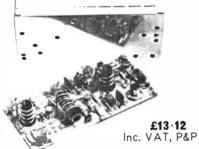


TECHNICAL CHARACTERISTICS: Output terminal for digital frequency meter;

Antenna impedance—75 to 300 Ohms; Frequency ranges 87-5 to 104MHz or to 108MHz; Sensitivity—0.9u V 26dB signal to noise ratio ±75kHz deviation; Intermodulation 80dB Image rejection-60dB; Tuning voltage—1V to 11V; Total gain—33dB; Intermediate frequency—10-7MHz; Power supply voltage + 15V; Power consumption 15mA; Dimensions 104 × 50mm.

TECHNOLOGY:

Double sided epoxy printed circuit board with plated through holes; Dual gate effect transistors; Silvered coils.

OPTOELECTRONIC OPTIONS

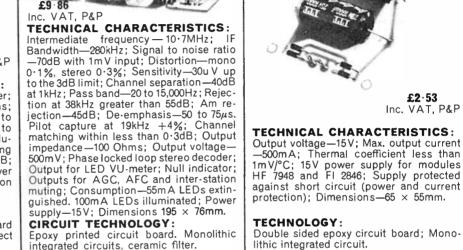

IF AMP AND DECODER

THE MOST

COMPREHENSIVE RANGE

STABILISED POWER SUPPLY

£2·53

Inc. VAT, P&P

OF TUNER MODULES

EVER DISPLAYED

ALS 1500

£8.06 Inc. VAT, P&P £22.74 Inc. VAT, P&P £13.50 Inc. VAT, P&P FREQUENCY METER ILLUMINATED POINTER Digital display of received Station finder LED VU-METER station frequency Station strength indicator £8.77 £4.35 Inc. VAT, P&P Inc. VAT, P&P TOUCH CONTROL NUMERICAL DISPLAY PRE-SELECTION UNIT Pre-selected channel number LED channel indication

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT Telex 965780 Telephone (0227) 63218





CLIP ON capacitive discharge electronic ignition in KIT FORM

Smoother running Instant all-weather starting Continual peak performance Longer coil/battery/plug life Improved acceleration/top speeds Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic spontion system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins Because of the superb design of the Sparkrite circuit it completely eliminates

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders. coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg, or pos. earth and fully illustrated nstallation instructions

NOTE – Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.35 inc. VAT. post & packing Electronic Design Associates, 82 Bath Street, Walsall, WSI 30E

.

Electronics Design As 82 Bath Street, Walsall, V		
Name		
Address		
Phone your order with Access or Inc. V.A.T. and P.P	Barclaycard QUANTITY REQ'D.	Send SAE if brochure only required.
X4 KIT £14.95		I enclose cheque PO's for
		£
TACHS PULSE SLAVE UNIT £3.35	1 1	Cheque No.

BARGAIN PARCELS SAVE POUNDS

Huge quantities of electronic components must be cleared as space required. 1000's of capacitors, resistors, transistors. Ex equipment panels etc. covered in valuable com-ponents. No time to sort. Must sell by weight 7 lbs-£4-95; 14lbs-£7-95; 28lbs-£12-06; 58lbs-£29-06; 112 lbs-£36-09. luminium TV coax plugs 10 for £1-09 tandard wire ended neons 12 for £1-09 Iniature 5K log pots with s/p switch 4 for

Miniature 5k 15g pots with sp switch 4 lof f1. CON'T LET YOUR ENVIRONMENT OEHYORATE YOU OR YOUR POS-SESSIONS. Buy a Honeywell Humidity controller. Compact (34' × 14'' × 17'), wide range of control, adjustable by 1" spindle with flat. Contact Rating 3: 75A @ 240VAC, 7:5A@ 120VAC. Ideal for Greenhouses, Centrally Hested Homes, Offices, etc. Build your own Humidiflers or Dehydration Alarma. £1:50 ea.4 for £5. New Miniature FM Frontends 88-103MHz, 10:7MHz. 1.F. or with Integral Tuning-gang £2:50. TBA 120A 50p each SN 76115N £1 each.

20 mm anti-surga fuses your selection 800MA to 3:15A, 12 for £1:09

800 MA to 3 15 A. 12 for £1 100 Component Bargains 300 mixed resistors ± & ‡ watt £1 158 300 mixed resistors mostly 1 & 2 watt. £1 50. 100 mixed resistors mostly 1 & 2 watt. £1 50. 100 mixed modern miniature and ceramic

100 mixed polyester caps £2:20. 100 mixed modern miniature and ceramic plate caps £1:00. 100 mixed wirewounds £2:20. 300 printed circuit resistors £1:00. 125 mixed film resistors, mostly miniature £1:00, 500 for £3:50.

25 mixed pots & presets £1:59. 100 High wattage resistors, wirewound etc. £2:20. Modern Vertical Presets with slotted knobs, 2200, 470K, 500K, 1 MEG, 25 for £1, 4 Packs £3:50. Small 50 wirewound Horiz. Convergence Preset with Knob. 10 for £1.

, reset with Knob. 10 for £1. Mctorola 1 watt Audio 1.C. MFC 8010 9-16y, 8-16Ω, 10-400MV. Sensitivity S.C. proof, complete with circuits and data £t-19 each, 5 for £4.

25 mixed pots & presets £1-58

SN 76115N £1 each


20

Selba-£29-09; 112 /bs-£30-09. Handy Packs 4 aluminium boxes 128 x 44 x 38 mm ideal for signal injectors, etc. 51-09. Miniature Edgewise Panel Meters 200 AFSD 201 AFSD 202 AFSD 203 AFSD 204 AFSD 20

top grade components 5 lbs L4 / 5. 10 lbs 28-95. OE LUXE FIBRE GLASS PRINTEO CIRCUIT ETCHING KITS Includes 150 aq. ins. copper clad //g board, 1b ferric chioride, 1 Dalo etch resist pen, abrasive cleaner, 2 mini drill bits, etch tray and instructions/only 25-30. 150 sq. in. fibre glass board £2-00 Dalo pen. 90p. 150 sq. instruction steri 250 Miniature mains transformers, fully shrouded. 240V. in 6-0-8V at 100ms out. Exa new equipment. Complete with mains lead and plug on input and short leads on output 90p.

lead and plug on input and short leads on output 90p. Semiconductor Bargains TH3 Thermistors 10 lor £1. 100 new 4. marked sillcon and germanium transistors including BC148, BF194, BC183, etc. £3:95 200 new 4. marked transistors including 2N3055, AC128, BFY50, BD131, etc. £4:95 100 mixed diodes NAtl48, atc. £1:50. 100 mixed diodes Including zener, power and bridge rectlifter 100v 2:5 amp 4 for £1. S0 Germanium diodes, Ideal for crystai sets, etc. £1. Miniature Vernitron FM4 10:7 MHz Cera-mic Filters 50p each 3 for £1. New U.H.F. transistor TV tuners 4 push-button type £3:56 Hardware Packs each containing 100's of Items including BA nuts and bolts, Nyion, Self-tapping, Posidrive, "P'' clips, Cable clamps, Fuse holders. Spire nuts etc., £1 per pound, 40p P & P ON ALL ABOVE ITE

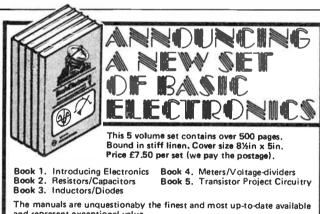each, 5 tor £4. 100K Stereo Slider Pots. Modern, slim type. 50p each, 3 for £1. Double Gang A.M. Tuning Condensors with integral 100K pot. For varicap tuning on VHF as used in modern Thorn music centres. £1. 40p P & P ON ALL ABOVE ITEMS. SEND CHEQUE OR POSTAL ORDER WITH ORDER TO SENTINEL SUPPLY, DEPT PW 149A BROOKMILL ROAD, DEPTFORD, SE8 CALLERS BY APPOINTMENT ONLY



and represent exceptional value. This series has been written in a fascinating, absorbing and exciting

way, providing an approach to acquiring knowledge that is a very enjoyable experience. Suitable for industrial trainees, City and Guilds students, DIY enthusiasts and readers of electronic journals.

Each part explains electronics in an easy-to-follow way, and contains numerous diagrams and half tone blocks with construction details and circuit diagrams for making the following transistor projects: Lamp Flasher, Metronome, Wailer, Photographic/Monostable Timer, Metal Locator, Geiger Counter, Radio Receiver, Intercom., Intruder Alarm, Electronic Organ, Battery Eliminator, Anemometer, Sound Switch, Light and Water-operated Switches, Pressure-operated Switches, Light meter, Radio Thermometer, Ice Alarm,

Order now: Selray Book Company 60 Hayes Hill Bromley BR2 7HP	DUR 100% GUARANTEE Should you decide to return the set after 10 days exam- ination, your money will be refunded by return of post.
Amount enclosed: £	
Name:	
Address:	
	PWI



HOME MICROCOMPUTER



NORTHERN SEMINAR MANCHESTER

£5.50 APRIL 1

After the enormous success of the Wembley Seminar, Lynx have been persuaded that there are sufficient Northerners waiting to attend their own show. All day. Microprocessor Lectures and presentation of the Nascom 1. Only 350 seats.

Z80 2K R.A.M. P.C.B.

OWERTY KEYBOARD MONITOR PROGRAM VDU INTERFACE (TV) **CASSETTE INTERFACE** TELETYPE INTERFACE

EXPANDABLE SYSTEM

NASCOMI £197.50 + VAT

LYNX ELECTRONICS (LONDON) LTD., 92 BROAD STREET, CHESHAM, BUCKS. 02405 75151

VA	VE	0	£		0.044	£		£	e 13	£	DELACT	£
VA		.		1-25 0-45	SP61 TT21	0-85	58/255N	6-50	6J7 6J7G	0.75	25L6GT 30C15	1-00
		-	PCC89	0-55	U25	1.00	5B/258N		6K7		30C17	1.10
£	5 EF83	£	PCC189	0.65	U26	0-85			6K7G		30C18 s	iee
A1065 1-2 AR8 0-6		1-50		0 · 50 0 · 40	U27	1.00	5R4G Y 5U4G		6K8GT 6L6M	0-55	PCF805	1.00
ARP3 0.6		0.55		0.65	U191	0.75	5V4G		6L6GT		30F12	1 20
ATP4 0-5	0 EF91	0.65	PCF86	0-65	U801 UABC8	0.80	5Y3GT	0.65	6L7G	0.65	30FL12	1.20
812H 3-0 DAF96 0-6		0-75	PCF200	0.90		0.60	5Z3		6SA7		30FL14	1.00
DET22 19-5		0.22	PCF201 PCF801		U8F80	0.55	5Z4G 5Z4GT	0.70	6SG7 6SJ7		30L15 30L17	1-00
DF96 0-6	0 EF184	1-60	PCF802	0-65	UBF89	0.50	6A87	0.60	65 J7G		30P12	1.00
DK96 0-8		2.00	PCF805	1-80	U8L1 U8L21	1.00	6AC7	0 - 60	6SK7	0.60	30PL1	1.00
DL92 0-5 DY86/870-5		0-75	PCF806 PCF808		UCC85	0.50	6AH6 6AK5	0-70	6SL7G		30PL13 30PL14	1-10
DY802 0.5		0-60	PCH200		UCF80	0-80	6AK8	0-40	6SN7G 6SQ7	0.75	35L6GT	
E55L 7.5		2.20	PCL81	0-60	UCH81	0.60	6AL5	0-40	6V6GT	0.75	35W4	0.60
E88 CC/01 1-3	EL37 EL41	3-00		0-65	UCL82 UF41	0-75	6AL5D	0.65	6X4		35Z4GT	0.70 0.70
E180CC 1-3		0.70		0 · 70 0 · 70	ŬL41	0.75	6AM5 6AM6	1-60	6X5GT 6Y6G	0.55	50C5 50CD60	
E180E 6-0	0 EL82	0.60	PCL805/	85	UL84	0.75	6AN8	0-85	6Z4	0.85		1.20
E182CC 3-5 EA76 2-0	0 EL84	0.60		0.75	UM80	0.60	6AQ5	1.30	6-30L2	0.90	75	1.00
EA8C800-5		0-70	PD500 PFL200	2.25	UY82 UY85	0.55	6AQ5W 6AS6	0-85 0-80	787	0.80	75C1 76	0-80
EB91 0-4	0 EL91	1-90		0 20	VR105/3		6AT6	0.75	7V4 9D2	0-80	78	0.75
	0 EL95		PL81	0-75			6AU6	0-48	9D2	0.75	80	0.75
	0 EL504	0-80					6AV6	0.20		11.00	85A2	2-20
	0 EL822	1.50	Add 12	4%	for V.	A.T.	6AX4G	0.80	12A6	0.60	723A/B 803	6-00
EC52 0.4	0 EM31	0.75L		_			6AX5G		12AT6	0.42		18-00
ECC81 0-5				0 - 50	VR150/3			1.00	12AT7 12AU7	0.55	807	1.00
ECC82 0 5 EBC83 0 5		0-60		0-50 0-65	X66	1.25	687 68A6	0.75	40.01/0	0.70	813 8298	8-50
ECC84 0-4		1.00		1-10	X61 M	1.50	68E6	0-50	12AX7	0 - 50	832 A	4-50
ECC85 0-5		0.45	PL508	1 . 30	Z800U	3-00	68G6G	1.00	128A6 12BE6	0.50	866A	2.80
ECC86 1 2 ECC88 0	25 EY81 10 EY86/87	0-45		2 · 40 2 · 80	Z801U	3.50	68J6	1-10	128M7	0.60	931A	6-00
ECC189 0-1		0.55		0-60	Z900T 1A3	1-50	68Q7A 68R7	0 · 60 2 · 30	1200	0.55	954 955	0.50
ECF80 0-5	60 EZ80	0.45	PY80	0-60	163	0-30	68W6		1261	4 25	956	0.50
ECF82 0-4 ECF801 0-7		0-60	PY81/80	0 0-55	1R5	0.55	68W7	1.00	1215GT 12K7GT		957	6 90
ECH34 0-1		0-65	PY82	0.45	154	0.40	6C4	0-40	12K8G1		1625 1629	0.70
ECH35 1-5	50 GZ33	3-50	PY83	0-50	1S5 1T4	0-40	6C6 6CH6	0.55	1207G	г	2051	1.00
ECH42 0-1		2.00	PY88	0.65	1X28	1-10	6CL6	0.75	125C7	0-50	5763	2.00
ECH81 0-4 ECH84 0-1		2.50	PY500 PY859	1-35 5-75	2D21	0.55	6D6	0.50	125U7	0 55 0 70	5842	6-50
ECL80 0		5.75	PY801	0-66	2K25	9.00	6EA8	0.80	125J7	0.55	6057	0.85
	55 MH4	1.00	QQ V03-		2X2	0.80	6F8G 6F12	0.75	12507	0.55	6060	0.85
ECL83 1-2 ECL85 0-1		1.00	00103-	2.50	3A4 3D6	0-60	6F17	1-00	12Y4		6064	0.85
ECL85 0-1		0-55	QQ V03-	2.50		20.00	6F33	4-20		1.00	6065 6067	1.00
EF37A 1-9	50 PABCE		QQ V06-	40A	3E29	5-50	6M6	4.20	19G3		6080	3-50
EF39 2.1		0.40		4-00	354	0.50	6J4WA		19G6	6.00		3-80
EF40 0		0.50	Q V03-12 S C1/400		3V4 58/2548	0·85	6J5 6J5GT	0-75			6146B 6360	4 20
EF80 0		0.12	SC1/600		30/2348		616		20P3 20P4		8020	5-50
POSTAG					£5 400-						10000	
£5-£10 60p	; over £10	free,	minimun	n ord	er £1.		C	:01	LON	101	R	
A lot of the	se valves i	116	VALV	ES A	ND		-	_	RONIC			
Imported	and pric		TRANS	IST	DRS	170	Goldh		Rd	lon	don V	V.12
vary for ea			Felephon			1.10						
so we rese		en 1	or valve						1-743			
	prices	IOF 🗼	ors, e	lc.:	retail		Open	Mo	ndav	to F	riday	
	when -	10 A -			1 U Cult							
new stock avoidable.		/n• 7	49 3934, xport 74	trad	e and				1.30-			

TECHNICAL TRAINING IN ELECTRONICS TELEVISION AND RADIO SERVICING


ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained person. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until vou are successful.

City & Guilds Certificates: **Telecommunications Technicians Radio, TV, Electronics Technicians Technical Communications Radio Servicing Theory Radio Amateurs Electrical Installation Work MPT Radio Communications Certificate Diploma Courses**:

Colour TV Servicing Electronic Engineering and Maintenance Computer Engineering and Programming Radio, TV, Audio Engineering and Servicing **Electrical Engineering, Installation** and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET. **15** To: International Correspondence Schools Dept. No. 276W, Intertext House, LONDON SW8 4UJ or telephone 622 9911 Subject of Interest Name Address Tel:

	-	TEXAS	1	74L's		4001	200	OP. AMPS.	1			1			-				-		-	-	
7400	14p 14p	7497 2	290p	74LS00 74LS02 74LS04	30p 30p 30p	4006 4007 4008	95p 20p 115p	CA3130 1080 CA3140 750	p	RC4136 709	140p 130p 40p	MEMOR 1702A 2102-2	EPR	ом Л	700p 160p	MPSA12 MPSA56 MPSU05	62p 40p 72p	2N2926R	B 9p	DIODES BY127 OA47	12p 9p	OA202 IN914 IN916	4p 7p
7402	16p	74104	75p	74LS08	30p	4009	50p	CA3160 120p LM301A 40p		733	150p 25p	2107	RAN		700p	MPSU06 MPSU55	78p	2N3053	22p 65p	0A81 0A85	15p	IN4001/2	6p
7404	20p	74107	36p	74LS10 74LS13	32p 55p	4010	60p	LM318N 175	p	747	75p	8080 A	C.P.	.u.	750p	MPSU56	98p	2N3055	48p	OA90	15p 9p	IN4003/4 IN4005/7	7p 8p
7405	25p 40p		60 p	74LS20	32p	4012	20p	LM324N 85p LM348N 140p		748	40p 216p	AY5-1013 RO3-2513			600p	OC28 OC35/6	140p	2N3442 2N3643	151 p 54 p	0 A 91 0 A 95	9p	IN4148 IN5401/3	4p
7407	40p	74111	75p	74LS22 74LS27	34p 45p	4013 4014	55p 115p	MC1458P 60		3900	70p		_		0300	OC71	32p	2N3644	54p	0 A 200	9p 9p	1N5401/3	15p 20p
7408	22p 22p		716p	74LS30	30p	4015	90p	LINEAR I.C.			_	LOW P		E DIL Y TEXAS	3	R20088 R2010B	225p 225p	2N3702/3 2N2704/5		BRIDGE	REC	TIFIERS	
7410	18p	74119 2	25p	74LS47 74LS55	150p 45p	4016 4017	50p	AY-1-0212 65 AY-1-1313 71	50p	NE543K NE555	225p 30p	8 pin	12p	22 pin	36p	T1P29A	50p	2N3706/7	14p	1A 50V	25p	4A 400V	96 p
7411	26p 25p	74120 1		74L\$73	60p	4018	110p	AY-1-5050 2	50p N	E556	85p	14 pin 16 pin	13p 14p	24 pin 28 pin	40p	TIP29C TIP30A	62p		14p 320p	1A 100V 1A 400V	27p 31p	6A 50V 6A 100V	96 p
7413	40p	74122	52p	74LS74 74LS75	60 p 75 p	4019 4020	52p 120p	AY-3-8500 71 AY-5-1315 75	75p	E561B	450p	18 pin	30p	40 pin	60p	TIP30C	72p	2N3819	27p	2A 50V	40p	8A 400V	120p
7414	85p 40p		75p	74LS83	120p	4021	115p	AY-5-1317A	- N	1E565	140p	TRANS	STO	RS		TIP31A TIP31C	56p 68p		50p	2A 100V 3A 200V	45p 70p	10A 400V 25A 400V	
7417	40p	74126	65p	74LS85 74LS86	144p 85p	4022 4023	100p 22p			E566	160p	AC125/6	20p	BF194	13p	TIP32A	63p	2N3866	97p	3A 600V	80p	VM18	
7420	18p 43p		82p	74LS90 74LS93	80p 80p	4024	80p	CA3046 1	15p R	RC4151	432p	AC127/8 AC176	20p 20p	BF195 BF196	11p 17p	T1P32C T1P33A	85p 97p	2N3903/4 2N3905/6		4A 100V	90 p	1A100V	48p
7422	28p	74136	\$1p	74LS107	55p	4025 4026	22p	CA3048 25 CA3053 7		G3402N	275p 54p	AC187/8	20p	BF200	40p	TIP33C	120p	2N4058	19p	TRIACS			
7423	36p 33p			74LS112 74LS123	120p	4027 4028	65p 68p	CA3065 20	00p 5	N76003N	275p	AD149 AD161	60p 45p	BF244B BF256B	34p 60p	TIP34A TIP34C	124p	2N4060 2N4123/4	19p 22p	3A 400V 6A 400V		15A 400V	
7426	43p 40p	74145	OF-	74LS138	140p	4029	120p				280p 175p	AD162	48p	BF257	34p	TIP35A	243p	2N4125/6	22 p	6A 500V		40430 T	066
7428	40p		60p	74LS139 74LS151	150p	4030	55p 250p	CA3090AQ 42	25p S	N76013ND	160p	AF114/5 AF116/7	22p 22p	BF258 BF259	39p	TIP35C TIP36A	290p 297p	2N4401/3 2N4427	34p \$7p	10A 400V	140p	40669 T	130p 0220
7430 7432	18p 37p		30p	74LS153	200p	4034	240p				280p	AF127	40p	BF339	32p	TIP36C TIP41A	360p	2N4871	60p	10A 500V	160 p		130p
7433	43p	74153	\$1p	74LS157 74LS158	130p 150p	4035 4040	130p	LM377N 20	Np 3	N76023ND P8515		AF139 AF239	40p 48p	BFR39 BFR40/1	34p 34p	TIP41C	70p 84p	2N5179 2N5245	75p 40p	SCR-TH	YRIS	TORS	
7437 7438	37p 37p		40p	74LS160	180p	4042	90p				800p	BC107/B	10p	BFR79 BFR80/1	34p 34p	TIP42A	76p 96p	2N5296	58p	BT106	5	itud	150p
7440	18p	74156	97p	74LS161 74LS162	180p	4043	100p	LM381AN 10	60p 斗	AA661A BA120	150p 97p	BC108/B BC109	10p	BFR88	34p 37p	TIP2955	78p	2N5401 2N5457/8	62p 40p	C106D MCR101		lastic 092	70p 30p
7441	85p 75p		97p	74LS163	180p	4046	140p		200 1	BA641B	300p	BC109C	11p	BFW10 BFX29	90p 30p	TIP3055 TIS43	60p 40p	2N5459	40p	2N4444	F	lastic	140p
7443	120p	74160 1	08p	74LS164	120p 225p	4047 4049	100p 55p	MC1310P 11	Юр 🕴		225p 112p	BC147 BC148	9p 8p	BFX30	34p	2N696/7	25p	2N5460 2N5485	65p 45p	2N5060/2 2N5064		092	40p 45p
7444	120p 97p		08p	74LS173	230p	4050	57p		P T	BA810	125p	BC157	11p	BFX64/5 BFX86/7	30p 30p	2N698 2N706/8	43p 22p	2N6107 2N6027	70p			0.0000	
7446	108p	74183 1	00p	74LS174 74LS175	160p	4051 4054	110p	MC1496L 11	12p 1		100p	BC158/9 BC169C	13p 15p	BFY50	22p	2N918	43p	2N6247	60 p 200 p	ОРТО-Е ОСР 71			
7447 7448	75p 85p			74LS181 74LS190	375p 250p	4055	140p 135p		10р т	DA2020	360p	BC172	11p	-BFY51 BFY52	22p 22p	2N930 2N1131/2	19p 25p	2N6254 2N6292	140p 70p	ORP 12	130p 97p	ORP 61 2N5777	90 p 48 p
7450 7451	18p 18p		60p	74LS191	200p	4060	130p				140p	BC173C BC177	11p 20p	BFY56	48p	2N1304/5	75p	3N128	108p	ORP 60	90p	TIL116	90p
7453	18p	74170 2	60p	74C 74C00	25p	4066	65p 425p	MFC4000B 12		N425E	420p	BC178 BC179	17p	BFY90 BLY83	90p 756p	2N1306/7 2N1613	75p 22p	3N140 3N141	108p	LEDs			
7454 7460	18p 18p		50p	74C02	25p	4068	24p	VOLTAGE REC				BC182/3	20p 12p	BRY39	48p	2N1711	22p	3N187	200p	TIL209 Re TIL211 Gr	ed 14p	0.2"Red 0.2"Gree	16p
7470	38p	74174 1	20p	74C04 74C08	27p 27p	4069 4070	27p 65p	1A +ve T02 5V 7805 10			0220 130 p	BC184 BC187	14p 32p	BSX19/20 MJE340	20p 70p	2N1893 2N2102	32p	40380 40361/2	43p 43p		18p	0.2"Amb	
7472	32p 36p	74175 1	97 P	74C10	27p	4071	27p	6V 7806 10	0p 1	2V 7912	130p	BC212	14p		175p 216p	2N2160 2N2218A	120p	40409/10	75p	TIL32	81p		360
7474	37p	74177 1:	20p	74C14 74C42	90p	4072 4073	27p 30p		2	4V 7924	130p	BC213 BC214	12p 16p	MJ2501	250p	2N2219	25p 22p	40594	325p 100p		200p	TIL312 TIL313	120p 120p
7475 7476	43p 37p		ZOD	74C48 74C73	230p	4076 4081	170p		ui III	leat Sink 17°/W	25p	BC461	40p	MJ2955 MJE2955	108p	2N2222 2N2389	22p	40595 40635	110p 60p	FND357	130p	TIL321	130P 130P
7480	54p	74182 1	50p	74C74	70p	4082	21p 24p	18V 7818 10	HOp s	ultable for	r i l	BC478 BCY70	32p 20p	MJ3001	250p	2N2484	32p	40636	140p	FND507	120p	DRIVE	
7482	108p 90p	74185 1	90 p	74C85 74C86	200p	4093 4098	120.0		10p	т	0220	BCY71	24p	MJE3055 MPF102/3		2N2648 2N2904/A	52p 22p	40673 40841	90p 85p	DL704 DL707	160p	75491 75492	84p 96p
7483	99p		90 p	74C90	90p	14502	180p		992 0	1A -ve 5V 79L05	T092	BD131/2 BD135/8	85p 54p	MPF104/5	40p	2N2905/A	22p	40872	85p	DL747	250p	9368	200p
7485	120p	74191 1:	20p -	74C93 74C107	90p	14503 14507	90p 55p	6-25V 78L62 4	Hap			BD139	56p	MPSA06	37p	2N2906/A	22p	40872	97p	TIL311	700p	9374	200p
7486	36p 340p		00p	74C151	260 p	14508	300p			2V 79L12 5V 79L15	80p	BD140 BDY56	60p 225p			VATUR		SIVE POID		dd 25p P&		ather a	1
7490	38p	74194 10	60 p 🔤		250p	14510	130p				160p	BF115	24p		der son	100	2.1	1.1.1		1	1.1.1.2		
7491 7492	90p 58p		10p	4C161	155p	14516	120p	LM323K 70	10 p 1	BA625B	120p	BF167 BF173	25p 27p		BY	5				NAT	In		
7493	36p	74197 13	30p	4C162 4C183	155p	14515	160p				150p	BF178	30p	APPO	INTM	ENT			UI		116		
7494 7495	90p 75p		50 P 7	4C164	140p	1 4520	110p	VARIABLE 723 DIL 4	150	M317 T02	20 325 p	BF179 BF180/1	35p 35p		DNLY								
7496	90p	74221 11		1000	20 p	14528 14560	130p 270p	78MGT2C 14	15p L			BF184/5	24p		54 S	andhurst P	toad,	London N	W9	Tel. 01-20	04 433	3 TIX 92	2800
-		-		-		-		and the Residence of	-	-		-	-	1000				1.163.07		and the second			

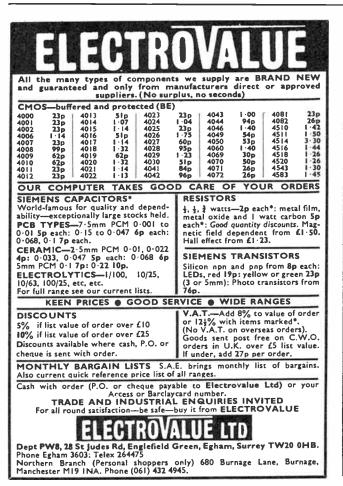

Your career in Electronics?

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any •bligation.

BRITISH NATIONAL F SCHOOL, P.O. Box 156, Jersey, Chann	ADIO & ELECTRONICS
NAME	
ADDRESS	(Block caps please)

TRANSISTOR/IC PRICE AC107 \$\$0 BC 31 1:00 \$\$73 TIP34C AC107 \$\$0 BC 31 1:00 \$\$73 TIP34C		HARDWARE, KNOBS, CHASSIS RADIOS/AMPLIFIERS, WIRE AND CABLES, TEST METERS, PANEL
120 33 1.00 k5Pi174 70 35C 128 40 38 2.00 i175 70 36A 176 45 39 2.00 i175 70 36A 187 45 55 3.00 2373 1.80 36E 187 45 55 3.00 2373 1.80 36C 188 45 Y70 19 MEC337 15 41A ACY19 50 71 23 HD2369 1.40 41B 20 45 72 16 H60210 20 41C 44 75 8D115 80 0401 20 42A 414 70 121 2.00 0411 20 42C 42B 161 95 123 2.00 0411 20 42C 42B 162 95 127 2.00 0411 20 42C 42B <tr< td=""><td>2.30 2.368 2.3 1.43 80 7400 17 74.180 3.20 3.00 2369 2.3 15.3 80 7401 17 74.180 3.20 3.00 2398 15.4 90 7402 17 74.180 3.20 3.00 2398 15.4 90 7402 17 74.180 1.20 3.00 2412 72 201 1.20 7404 17 74.193 1.20 3.00 2412 72 201 1.20 7404 17 74.193 1.20 3.20 24477 1.00 RCA40347 35 7405 52 74.193 1.20 65 2498 1.80 RCA40347 50 7407 52 74.195 75 75 2646 72 40352 50 7408 52 74.197 1.00 80 2697 404341 1.50 74.09 22 74</td><td>METERS, PLUGS, SOCKETS, CONNECTORS, SLEEVING, ALUMINIUM BOXES, PCB, VERO PRODUCTS, GROMMETS, STABILISED POWER SUPPLIES, SMALL SPEAKERS. IN OTHER WORDS ALMOST EVERYTHING FOR THE ENTERPRISING CONSTRUCTOR.</td></tr<>	2.30 2.368 2.3 1.43 80 7400 17 74.180 3.20 3.00 2369 2.3 15.3 80 7401 17 74.180 3.20 3.00 2398 15.4 90 7402 17 74.180 3.20 3.00 2398 15.4 90 7402 17 74.180 1.20 3.00 2412 72 201 1.20 7404 17 74.193 1.20 3.00 2412 72 201 1.20 7404 17 74.193 1.20 3.20 24477 1.00 RCA40347 35 7405 52 74.193 1.20 65 2498 1.80 RCA40347 50 7407 52 74.195 75 75 2646 72 40352 50 7408 52 74.197 1.00 80 2697 404341 1.50 74.09 22 74	METERS, PLUGS, SOCKETS, CONNECTORS, SLEEVING, ALUMINIUM BOXES, PCB, VERO PRODUCTS, GROMMETS, STABILISED POWER SUPPLIES, SMALL SPEAKERS. IN OTHER WORDS ALMOST EVERYTHING FOR THE ENTERPRISING CONSTRUCTOR.
$\begin{array}{c ccccccccccccccccccccccccccccccccccc$	70 2907 22 40486 85 7419 25 74+100 50 20 2924 14 40543 1:35 7420 20 74+11 60 30 2926 14 40554 80 7422 20 74+14 55 3014 40559 90 7423 30 74L0 32 3053 22 40650 60 7426 30 74504 3054 65 40636 1:0 7426 30 74506 3054 65 40636 1:0 7428 30 74506 14 3055 70 40669 1:0 7432 30 74510 14 3252 2:0 40679 1:0 7432 30 74510 14 3252 74 40642 1:0 7437 40 76630 16 3810 122 3794 18 16093 122	★ SPECIAL OFFER ★ BIGITRON stereo cassette deck complete mechanism, inc, heads, motor keys etc. Brand new in manufacturer's packing, £7.50 each + 12½ VAT.
$\begin{array}{cccccccccccccccccccccccccccccccccccc$	35 3905 15 3A 600V 24 7448 85 3036 1.50 3906 15 3A 600V 30 7450 20 3046 65 3926 15 3A 600V 30 7450 20 3046 65 4014 *75A 100V 7451 20 3075 1-50 4036 65 1A 40V 30 7460 20 3089 2-60 4037 55 1A 100V 40 7470 30 3089 3-90 7 4058 20 3A 200V 50 7472 25 MC724 1-85 4059 15 4A 50V 40 7472 30 1216 1-46 4059 15 4A 50V 40 7475 48 1307 1-85 6 4061 15 4A 50V 775 48 1307 1-85	SWITCHES PUSH BANKS TOGGLE STD. TOGGLE STD. TOGGLE MIN SUDE ROTARY SUDE
$ \begin{array}{c ccccccccccccccccccccccccccccccccccc$	$ \begin{array}{c c c c c c c c c c c c c c c c c c c $	ALUMINIUM BOXES AB7 $2 \times 54 \times 14$ 66p AB8 4×4 14 66p AB9 4×4 14 66p AB9 4×2 14 66p AB9 4×2 $77p$ 8114 $66p$ AB10 4×2 2 $93p$ AB13 $6 \times 4 \times 2$ $93p$ 8114 4×2 AB14 $7 \times 5 \times 24$ 610 61×30 61×30 AB15 $8 \times 6 \times 3$ 61×30 61×30 61×30 AB16 $12 \times 5 \times 3$ 61×30 61×30 61×30 AB19 $12 \times 5 \times 3$ 61×30 61×30 61×30 AB19 $12 \times 8 \times 3$ 61×20 Prices subject to change + 8% VAT. 72×20
184 12 00 30 205 2.50 697 186 21 87 30 SDT1062 698 187 25 88 30 I064 699 204 15 BF10 1.00 1152 706 205 15 30 24 1159 706 207 15 44 5503 929 208 15 50 24 5553 930 209 15 51 24 7603 1050 212 15 52 24 7604 1132 213 12 53 34 9200 1302 214 15 72 90 9801 1303 237 12 890 1:20 9803 1304 238 12 18101 50 TIC44 30 1305	$ \begin{array}{cccccccccccccccccccccccccccccccccccc$	TRANSFORMERS 50-64 250Ma 0.45 50-64 1.5A 2.10 50-37 1.5A 2.10 70 250Ma 1.20 70 250Ma 1.20 70 2450Ma 1.20 70-93 1.00Ma 1.00 122 1.00Ma 600 123 1.4MP 1.60
239 15 BRY39 50 TIP29A 45 1306 257 16 BSY45 29C 60 1307 259 16 66 29C 60 1308 251 12 BSX19 32 30A 60 1309 261 21 BS24 10A 60 1309 263 26 21 32A 30A 60 1309 267 25 81 30C 65 1479 300 40 BSY38 30 31A 50 1602 301 40 39 30 31A 50 1602 303 45 52 30 31C 65 1613 303 45 52 30 31C 65 1613 318 12 BY101 23 32A 63 1860 1493 3128 16 11430 332A 33A	34%0 37 4076 1.00 74165 1.20 810 1.10 555 60 4077 70 74166 1.20 820 1.05 5717 4078 25 7717 4078 25 717 74078 25 717 74078 25 717 74078 25 7177 74078 25 707 74167 2.60 7051.50 1.50 1.50 1.52 735 4082 2.87 74174 1.12 78051.50 1.60 7.73 1.40 81 3.10 1.51 1.74168 2.50 7.73 1.40 83 2.00 4512 7.74168 2.30 747	$\begin{array}{cccccccccccccccccccccccccccccccccccc$
C.T. ELECI	rronics (Act	'ON) LTD.
		Registered in England 1179820
.	TON LANE, LONDON, W4 5DG. Teleph	

Warehouse Trade counter: 270 ACTON LANE, LONDON W4 5DG

CALLERS ONLY, NO MAIL ORDER, OTHER THAN TRADE. OPEN 9.30 A.M.-6.00 P.M. MONDAY TO SATURDAY. ALL THE ABOVE GOODS ARE SUBJECT TO VAT +.

SWITCHES .

BOOKS BY BABANI

	ase books to the value of £5.00 from the list	below
	hoose any 60p pak from this page FREE.	
BP2	Handbook of Radio, TV & Industrial &	
	Transmitting Tube & Valve Equivalents	60pt
BP3	Handbook of Tested Transistor Circuits	40p1
8P6	Engineers and Machinists Reference Tables	40p1
BP7	Radio & Electronic Colour Codes and Data	15pt
BP10		
	beginners	95pt
8P16	Constructors Manual of Electronic Circuits for	
0.010	the Home	50p†
8P16	Handbook of Electronic Circuits for the Amateur	
0010	Photographer	60p1
8P18	Boys and Beginners Book of Practical Radio	
0022	and Electronics	60pt
8P22 8P23	79 Electronic Novelty Circuits	75p1
8P24	First book of Practical Electronic Projects 52 Projects Using IC741 (or equivalents)	75pt
8P26	Radio Antenna Handbook for Long Distance	75pt
0120	Reception and Transmission	85pt
8P27	Giant Chart of Radio Electronic Semiconductor	ophi
0121	and Logic Symbols	60pt
8P29	Major Solid State Audio Hi-Fi Construction	oopi
0123	Projects	85pt
8P32	How to Build Your Own Metal & Treasure	ospi
01.52	Locators	85pt
8P34	Practical Repair & Renovation of Colour TVs	95pt
8P35	Handbook of IC Audio Preamplifier & Power	oop.
	Amplifier Construction	95pt
8P36	50 Circuits Using Germanium, Silicon & Zener	
	Diodes	75pt
8P37	50 Projects Using Relays, SCR's and TRIACS	£1-101
8P39	50 (FET) Field Effect Transistor Projects	£1-251
129	Universal Gram-motor Speed Indicator	8pt
160	Coil Design and Construction Manual	75pt
161	Radio, TV and Electronics Data Book	60pt
196	AF-RF Reactance—Frequency Chart for	
	Constructors	15pt
202	Handbook of Integrated Circuits (ICs) Equivalents	
	and Substitutes	75p†
205	First Book of Hi-Fi Loudspeaker Enclosures	75p†
213	Electronic Circuits for Model Railways	85p1
214	Audio Enthusiasts Handbook	85p†
216	Electronic Gadgets and Games	85p1
217	Solid State Power Supply Handbook	85p1
219	Solid State Novelty Projects	85p1
220	Build Your Own Solid State Hi-Fi and Audio	95
222	Accessories	85pt
223	Solid State Short Wave Receivers for Beginners 50 Projects Using IC CA3130	95pt 95pt
223	50 Projects Using IC CA3 130 50 CMOS IC Projects	95p1 95p1
225	A Practical Introduction to Digital IC's	95p1
225	How to Build Advanced Short Wave Receivers	£1-201
RCC	Resistor Colour Code Disc Calculator	10p1
		· op /

BOOKS BY NEWNES

No. 229 Beginners Guide to Electronics	Price £2-251
No. 230 Beginners Guide to Television	Price £2-251
No. 231 Beginners Guide to Transistors	Price £2-251
No. 233 Beginners Guide to Radio	Price £2-751
No. 234 Beginners Guide to Colour Television	Price £2-251
No. 235 Electronic Diagrams	Price £1-801
No. 236 Electronic Components	Price £1-081
No. 237 Printed Circuit Assembly	Price £1 081
No. 238 Transistor Pocket Book	Price £3-901
No. 225 110 Thyristor Projects Using SCRs & Triacs	Price £2-501
No. 227 110 COS/MOS Digital IC Projects For the Home Constructor	Price £2-251
No. 226 110 Operational Amplifier Projects for the Home Constructor	Price £2-501
No. 242 Electronics Pocket Book	Price £3.901
No. 239 30 Photoelectric Circuits &	FIGE 13.901
Systems	Price £1 801

NUTS AND BOLTS

8A BOLTS slotted chee	 packs se head. 	of BA thre	aded cadmiu	im plated	l screws	
Supplied in	multiples o	of 50.				
Type 1in OBA 1in OBA 1in 2BA 1in 2BA 1in 2BA 1in 4BA	No. 839 840 842 843 844 845	Price £1 20 £0 75 £0 85 £0 45 £0 52 £0 44	Type In 4BA in 4BA in 6BA in 6BA	No. 846 847 848 849 850	Price £0-32 £0-25 £0-40 £0-21 £0-25	
BA NUTS - 50.	- packs of	cadmium p	lated full nu	its in mu	Itiples of	
Type OBA 28A	No. 855 856	Price £0-72 £0-48	Type 4BA 6BA	No. 857 858	Price £0-30 £0-24	
BA WASHE supplied in r	RS – flat nultiples of	cadmium (f 50.	plated plain	stamped	washers	
Type 08A 2BA	No. 859 860	Price £0-14 £0-12	Түре 48А 68А	No. 861 862	Price £0-12 £0-12	
SOLDER TA	GS – hot ti	inned suppli	ed in multiple	es of 50.		
Туре 08А 28А	No. 851 852	Price £0.40 £0-28	Т _{үре} 48А 68А	No. 853 854	Price £0-22 £0-22	
10	0.0			-		-

Push button DPDT, 2 amp 250V a.c. MIDGET WAFER SWITCHE	1964		£0.98* £0.98*
			£0.83°
Push button SPST, 2 amp 250V a.c.	1963		
off, 2 amp 250V a.c. Push button SPST, 2 amp 250V a.c.	1961 1962		£0.85* £0.78*
250V a.c. Miniature DPDT toggle, centre	1960		£0·70*
Miniature SPST toggle, 2 amp 250V a.c. Miniature DPDT toggle, 2 amp	1959		£0-55•
Description Miniature SPST toggle, 2 amp 250V a.c.	No. 1958		Price £0-50*
RDCKER SWITCH A range of rocker switches SPST – moulded in high insulation. Material available in a choice of colours ideal for small apparatus.	Colour RED BLACK WHITE BLUE YELLOW LUMINOUS	No. 1980 1981 1982 1983 1984 1985	£0.26* £0.26* £0.26*
Tamp 250V a.c. Rotary on-off mains switch Push switch – Push to make Push switch – Push to break	1976 1977 1978 1979		£042* £050* £013* £018*
DPDT standard slide Toggle switch SPST 1 amp 250V a.c. Toggle switch DPDT	1974 1975		£0 14• £0 33•
DPDT miniature slide	No. 1973		Price £0-11*

AND FUSES

				-	
Descriptio 20mm x 5n 1 in x in c 1 in car inl Panel mour Panel mour	nm chassis chassis mou ine type nting 20mm	Inting		Drder No. 506 507 508 509 510	Price £0.07• £0.12• £0.15• £0.20 £0.30
QUICK BL	DW 20mr	n			
Type 150mA 250mA 550mA 800mA	No. 611 612 613 614	Type 1A 1-5A 2A 2-5A	No. 615 616 617 618	Туре ЗА 4А 5А	No. 619 620 621
ANTI-SUF	CE 20		each exce	epting 616 whi	ch is 7p.
Type 100mA 250mA 500mA	No. 622 623 624	Type 1A 2A 1-6A All 7p	No. 625 626 627 each	Type 2-5A 3-15A 5A	No. 628 629 630
QUICK BL	DW 11in				
Type 250mA	No. 631	Type 500mA All 7p	No. 632 each	Type 800m/	No. 634
Түре 1А 1-6А	No. 635 636	Type 2·5A 3A	No. 638 639	1 _{уре} 4А 5А	No. 641 642
2A	637	All 6p	each		

CASES AND BOXES

and sid No. 155 156 157 158 ALUMI	es, aluminium Langth Bin 11 in 6 in 9 in NIUM BDXE ction each be	bottom, front Width 5jin 6in 4jin 5jin 5jin	ctions vinyl cc and back. Height 2in 3in 1≩in 2∛in 2∛in om bright al with half inct	Price £1-52* £2-12* £1-30* £1-76*
No. 159 160 161 162 163 164 165 166 167	Langth 5∦in 4in 5∦in 5∦in 3in 7in 8in 6in	Width 2≱in 4in 2¥in 2∛in 2∛in 2in 5in 6in 4in	Height 1 tin 1 tin 1 tin 2 in 2 in 2 tin 2 in 2 in	Price 82p* 62p* 62p* 74p* 64p* 44p* £1.04* £1.32* B6p*
	1 pole 12 way 2 pole 6 way 3 pole 4 way	VAFER	SWITCH	48p* 48p* 48p* 48p* 48p*

		S
No. Seconda 2021 6V-0-6 2022 9V-0-9		Price 90p* 90p* 95p*
MINIATURE MAINS Priman with two independent secondar No. Type 2024 MT280-0-6V, 0 2025 MT150-0-12V.	-6V RMS	Price £1.50* £1.50*
1 AMP MAINS Primary 240V No Secondary 2026 6V-0-6V 1 amp 2027 9V-0-9V 1 amp 2028 12V-0-12V 1 amp 2029 15V-0-15V 1 amp 2030 30V-0-30V 1 amp	Price £2:50* £2:00* £2:60* £2:75* £3:45*	P. & P. 45p P. & P. 45p P. & P. 55p P. & P. 66p P. & P. 86p
STANDARD MAINS Primary Multi-tapped secondary main amp, 1 amp and 2 amp cui 0 19 25-33-40-50V. Voltages available by use of tap 4, 7, 8, 10, 14, 15, 17, 19, 25.	ns transformers rrent rating. Seco is:	ondary taps are

P. & P. 86p P. & P. 86p P. & P. £1-10

AUDIO LEADS

Price £5-50* £6-60* £8-40*

Rating 1 amp 2 amp

FM Indoor Ribbon Aerial	£0-60°
Length 1.5m	£0-75*
to pins 3&5. Length 1.5m	£0.85*
to pins 1&4. Length 1.5m	£0.85*
	£1-10*
AC mains connecting lead for cassette	£0.68*
5 pin DIN phono plug to stereo	£1.05*
2+2 pin DIN plugs to stereo jack socket	£1.05-
headphones. Length 0.2m Car stereo connector. Variable geometry plug to fit most car cassette, 8 track	£0-90*
with inline fused power lead and instructions. 6 6m Coiled Guitar Lead Mono Jack Plug	£0-60*
to Mono Jack Plug BLACK 3 pin DIN plug to 3 pin DIN plug.	£1-50*
Length 1.5m	£0.75*
Length 1.5m	£0.75*
Length 1 5m	£0.75°
All colour coded, Length 1.5m	£1-30*
Length 1.5m	£0.80°
5 pin OIN plug to 5 pin OIN plug mirror image, Length 1.5m	£1-05*
2 pin DIN plug to 2 pin DIN inline socket.	£0-68*
5 pin DIN plug to 3 pin DIN plug, 1&4	£0-83*
2 pin DIN plug to 2 pin DIN socket.	£0.98*
5 pin DIN plug to 2 phono plugs.	
5 pin DIN plug to 2 phono sockets.	£0.75*
5 pin DIN socket to 2 phono plugs.	£0-68*
Connected pins 3&5. Length 23cm Coiled stereo headphone extension lead.	£0-68*
Black. Length 6m AC mains lead for calculators etc.	£1.75* £0.68*
	 3.5mm Jack plug to 3.5mm jack plug. Length 1.5m 5 pin DIN plug to 3.5mm, Jack connected to pins 38.5 Length 1.5m 5 pin DIN plug to 3.5mm, Jack connected to pins 18.4 Length 1.5m Car aerial extension. Screened insulated lead. Fitted plug & skt. AC mains connecting lead for cassette recorders 8 radios. 2 metres 5 pin DIN plugs to stereo headphone jack socket 2 + 2 pin DIN plugs to stereo headphones. Length 0.2m Car stereo connector. Variable geometry plug to fit most car cassette. 8 frack cartridge & combination units. Supplied with inline fused power lead and instructions. 6 con Colied Guitar Lead Mono Jack Plug to Mono Jack Plug BLACK Length 1.5m 2 pin DIN plug to 5 pin DIN plug. Length 1.5m 5 pin DIN plug to 5 pin DIN plug. Length 1.5m 5 pin DIN plug to 5 pin DIN plug. Length 1.5m 5 pin DIN plug to 5 pin DIN plug. Length 1.5m 5 pin DIN plug to 5 pin DIN plug. Length 1.5m 5 pin DIN plug to 5 pin DIN plug. Length 1.5m 5 pin DIN plug to 5 pin DIN plug. Length 1.5m 5 pin DIN plug to 2 pin DIN socket. Length 1.5m 5 pin DIN plug to 2 pin DIN socket. Length 1.5m 5 pin DIN plug to 2 pin DIN socket. Length 1.5m 5 pin DIN plug to 2 pin DIN socket. Length 1.5m 5 pin DIN plug to 2 pin DIN socket. Length 1.5m 5 pin DIN plug to 2 pin DIN socket. Length 1.5m 5 pin DIN plug to 2 pin DIN socket. Length 1.5m 5 pin DIN plug to 2 pin DIN socket. Length 1.5m 5 pin DIN plug to 2 pin DIN socket. Length 1.5m 5 pin DIN plug to 2 pin DIN socket. Length 1.5m 5 pin DIN plug to 2 pin DIN socket. Length 1.5m 5 pin DIN socket 10 2 phono sockets. Connected pins 38.5. Length 2.5m 5 pin DIN socket 10 2 phono sockets.

AVDEL BOND CYANOACRYLATE G2

The wonder adhesive which works in seconds. Bonds plastic, rubber, transistors, components, permanently – immediately¹ O(D143, ONLY **70p**• for a 2gm phial

BI-PAK CATALOGUE NEW EDITION NOW AVAILABLE

Send for your copy of our revised catalogue and price list NOW1 It contains 127 pages packed with literally hundreds of semiconductors, components and our famous range of BI-KITS audio modules. DALY 65- DOST BEEF DNLY 65p PDST FREE

DRDERING Do not forget to state order number and your name and address. V.A.T. Add 12 $\frac{1}{2}\%$ to prices marked*, 8% to those unmarked. Items marked are zero rated.

P&P. 35p unless otherwise shown.



DEPT. PW7, P.O. Box 6, Ware, Herts COMPONENTS SHOP: 18 BALDOCK STREET, WARE, HERTS.

SEMIC		7110	TO	D (co		
CERAMIC PAK				ISTORS			MIDGET WAFER
Containing a range of first quality miniature ceramic capa- citors.				ULLY GUARANTEE	b		SWITCHES 1965 - 1 pole 12 way 48p* 1966 - 2 pole 6 way 48p*
16160 - 24 - 3 of each value:- 22pf. 27pf, 33pf, 39pf, 47pf, 68pf. 82pf 16161 - 24 - 3 of each value:- 100pf.	Type Price AC126 £0.18 AC127 £0.18 AC128 £0.18	Type Price BC109C £0-08 BC147 •£0-08 BC148 •£0-08	8C550 •£014 8C556 •£014	Type Price BFY52 £0.16 BIP19 £0.38 BIP20 £0.38	Type Price TiP3055 £050 TIS43 £0-24 TIS90 •£0-22	Type Price 2N3708A 2N3709 •£0.07	1967 3 pole 4 way 48p 1968 4 pole 3 way 48p IC PAKS
120pf, 150pf, 180pf, 220pf, 270pf, 330pf, 390pf 16162 - 24 - 3 of each value:- 470pf, 560pf, 680pf, 820pf, 1000pf, 15000pf,	AC128K £0.26 AC132 £0.20 AC134 £0.20 AC137 £0.20	8C149 *£006 8C157 *£010 8C158 *£010 8C158 *£010	BC558 •£0 12 BC559 •£0 14 BD115 £0 50	BIP19/ 20MP £0 B0 8RY39 £0 45 BU105 £1-40	UT46 •£0-22 ZTX107 •£0-10 ZTX108 £0-10 ZTX109 •£0-10	2N3710 •£007 2N3711 •£007 2N3819 £020 2N3820 £035	Manufacturers "Fall-outs" which include functional and part
2200pf, 2200pf, 3300pf 60p* 16163 - 21 - 3 of each value:- 4700pf, 6800pf, -01uf, -015uf, -022uf, -033uf, -047uf 60p*	AC141 £0.22 AC141K £0.30 AC142 £0.20 AC176 £0.18	BC167 •£0 12 BC168 •£0 12 BC169 •£0 12 BC169 •£0 12 BC169C •£0 12	8D121 £065 8D124 £070 8D131 £038 8D132 £040	BU105/02 £1-95 BU204 £1-70 BU205 £1-40 BU208/02 £2-95	ZTX300 •£0-12 ZTX500 •£0-14 2N1613 £0-20 2N1711 £0-20	2N3B21 £0.60 2N3B23 £0.60 2N4058 •£0.12 2N4059 •£0.14	functional Units. These are classed as 'out-of-spec' from the maker's very rigid specifications, but are ideal for learning about I.C's and experimental work.
ELECTROLYTIC	AC176K £0-26 AC178 £0-25 AC179 £0-25 AC180 £0-20	BC171 •£0-10 BC172 •£0-10 BC173 •£0-12	BD131/ 132MP £0.85 BD133 £0.40 BD135 £0.38	E1222 £0-38 MJE2955 £0-98 MJE3055 £0-60 MJE3440 £0-52	2N1889 £0.45 2N1890 £0.45 2N1893 £0.30 2N2147 £0.75	2N4060 •£0-14 2N4061 •£0-12 2N4062 •£0-12 2N4284 •£0-18	16224 100 Gates assorted 7400-01- 04-10 50-60 etc £1-20 16226 30 MXI Assorted types 7441-
PAKS A range of paks each containing 1B first quality, mixed value miniature electrolytics.	AC180K £0-28 AC181 £0-20 AC181K £0-28 AC187 £0-18	BC177 £016 BC178 £016 BC179 £016 BC180 £025	BD137 £035 BD138 £040 BD139 £036	MPB113 £0-52 MPF102 £0-35 MPF104 £0-38 MPF105 £0-38	2N2148 £070 2N2160 £100 2N2192 £038 2N2193 £038	2N42B5 •£0 1B 2N42B6 •£0 1B 2N4287 •£0 1B 2N42BB •£0 1B	47-90-154 etc £1-20 16227 - 30 Assorted Linear Types 709-741-747-748-710-588 etc £1-50 16228 - 8 Assorted types 51403-76012
16201 - values from 47mFD - 10mFD 60p* 16202 - values from 10mFD -	AC187K £0.20 AC188 £0.18 AC188K £0.20 AD140 £0.60 AD142 £0.85	BC181 •£0.25 BC182L •£0.10 BC183 •£0.10 BC183L •£0.10	BD139/ 140MP £0.80 BD155 £0-80	MPSA05 *£0-30 MPSA06 *£0-30 MPSA55 *£0-28 MPSA56 *£0-28	2N2194 £0.38 2N2217 £0.22 2N2218 £0.22 2N2218A £0.20	2N4289 •£0 1B 2N4290 •£0 1B 2N4291 •£0 1B 2N4292 •£0 1B	16228 - 8 Assorted types SL403 76013 76003 etc 16229 - 5 I.C's 76110 Eqv. to MC1310P-MA767 £1-50*
100mFD 60p* 16203 - values from 100mFD - 680mFD 60p*	AD143 £0 75 AD149 £0 60 AD161 £0 42 AD162 £0 42	BC1B4L £0.60 BC207 £0.11 BC208 £0.11 BC209 £0.12 BC212 £0.11	BD176 £060 BD177 £068 BD178 £068	0C22 £1-50 0C23 £1-50 0C24 £1.35 0C25 £1-00	2N2219 £0-20 2N2219A £0-24 2N2904 £01B 2N2904A £0-21	2N4293 *£0-18 2N4921 *£0-55 2N4923 *£0-65 2N5135 *£0-10	JUMBO PAK SEMI CONDUCTOR
CARBON RESISTOR PAKS	AD161/ 161MP £0.35 AF114 £0.21 AF115 £0.21	8C212L •£0 11 8C213 •£0 11 8C213L •£0 11 8C213L •£0 11 8C214 •£0 12	8D201/ 202MP £1.70 BD203 £0.80	0C26 £1.00 0C28 £0.80 0C29 £0.95 0C35 £0.90 0C36 £0.90	2N2905 £0 18 2N2905A £0 20 2N2906 £0 16 2N2906A £0 19 2N2907 £0 20	2N5136 *£0.10 2N5138 *£0.10 2N5194 £0.56 2N5245 £0.40 2N5294 £0.34	16222 Transistors Germ and Silicon Rectifiers-Diodes-Triacs Thyristors I.C's and Zeners ALL NEW & CODED.
These paks contain a range of Carbon Resistors assorted into the following groups.	AF116 £021 AF117 £0:21 AF118 £0:40 AF124 £0:30	BC214L •£0 12 BC237 •£0 16 BC23B •£0 16 BC23B •£0 16 BC251 •£0 15	8D203/ 204MP £1.70 8DY20 £0.80	0C36 £090 0C70 £024 0C71 £015 TIC44 •£029 TIC45 •£035	2N2907A £0-22 2N296G *0.09 2N2926Y £0-08 2N29260 £0-08	2N5296 £0-56 2N5457 £032 2N5458 £0-32 2N5459 £0-35	Approx 100 pieces Offering the amateur a fantastic bargain PAK and an eriormous saving £225
16213 - 60 mixed w 1000hms - 820 ohms 60p* 16214 60 mixed w 1K ohms - 8-2K ohms 60p* 16215 - 60 mixed w 10K ohms -	AF125 £0.30 AF126 £0.30 AF127 £0.32 AF139 £0.35	BC251A •£016 BC301 £028 BC302 £028 BC303 £028	BF457 £0.37 BF458 £0.37 BF459 £0.38	TIP29A £0.40 TIP29B £0.52 TIP29C £0.50 TIP30A £0.50	2N2926R CO 08 2N2926B CO 08 2N3053 CO 16 2N3054 CO 40	2N5551 •£0.36 2N6027 £0.39 2N6121 £0.70 2N6122 £0.70	MAMMOTH I.C. PAK
83K ohms 66p [•] 16216 - 60 mixed iv 100K ohms 820K ohms 60p [•] 16217 - 40 mixed iv 100 ohms -	AF1B0 £040 AF1B1 £060 AF186 £058 AF239 £035	BC304 £038 BC327 £016 BC328 £015 BC337 £015	BF596 •£0 28 BFR39 £0 24 BFR40 •£0 25 BFR79 •£0 28	TIP308 £0.60 TIP30C £0.60 TIP31A £0.45 TIP318 £0.47	2N3055 £040 2N3414 •£016 2N3415 •£016 2N3415 •£029	40311 £0.38 40313 £0.95 40316 £0.95 40317 £0.40	16223 - Approx 200 pieces assorted fail-out integrated circuits, including: Logic, 74 series, Linear, Audio, and D.T.L. Many coded devices, but some
820 ohms 600 mixed 3 W 1K ohms - 8-2K ohms 600 16219 40 mixed 3 W 10K ohms -	AL102 £0.38 AL103 £1.20 AU104 £1.18 AU110 £1.00 AU113 £1.00	BC33B £015 BC440 £030 BC441 £030 BC460 £03B	BFX29 £0-22 BFX30 £0-30 BFX84 £0-22	TIP31C £049 TIP32A £049 TIP32B £051 TIP32C £053	2N3417 •£0-29 2N3614 £100 2N3615 £1•05 2N3616 £1•05	40326 £040 40327 £045 40346 £045 40347 £065	UNTESTED SEMI-
B2K ohms 60p* 16220 - 40 mixed 1 w 100K ohms - 820K ohms 60p* 16230 60 mixed 1 w 1 Meg -	BC107A £0.08 BC107B £0.08 BC107C £0.08 BC108A £0.08	BC461 £0.38 BC477 £0.20 BC478 £0.20 BC479 £0.20 BC547 £0.12	BFX86 £0.25 BFX87 £0.22 BFX88 £0.22	TIP41A £049 TIP41B £051 TIP41C £053 TIP42A £053 TIP42B £055	2N3646 •£0.09 2N3702 •£0.08 2N3703 •£0.08 2N3704 •0.07	40348 £080 40360 £036 40361 £036 40362 £038	CONDUCTOR PAKS 16130 - 100 Germ. gold bonded OA47 diodes 60p
10 Meg ohms 16231 40 mixed w 1 Meg 10 Meg ohms 60p*	BC108B £00B BC109C £00B BC1098 £00B	BC54B •£0 12 BC549 •£0 12	BFY50 £016	TIP428 £0-55 TIP42C £0-57 TIP2955 £0.65	2N3705 *£0.07 2N3706 *£0.08 2N3707 *£0.08 2N3708 *£0.07	40406 £0.45 40407 £0.35 40408 £0.52 40409 £0.75	16131 - 150 Germ. point contact 100mA.0A70/81.diode 60p 16132 100 Silicon diodes 200mA 0A200
COMPONENT PAKS		74	SERIE		'S		16133 150 Silicon fast switch diode 75mA IN4148 60p 16134 50 Silicon rectifiers top hat 750mA 60p
16164 - 200 Resistor mixed value approx (Count by weight) 60p° 16165 150 Capacitors mixed value approx (Count by weight) 60p°	Type Price	Type Prico	BI-PAK STILL LC FULL SPECIFICATI	Type Price	Type Price	Type Price	16135 20 Silicon rectifiers stud type 3 amp 60p 16136 50 400mW zeners D07 case 60p
16166 50 Precision resistors Mixed values 60p 16167 w resistors mixed values 80	7400 014 7401 014 7402 015 7403 015	7409 015 7410 014 7411 023 7412 023	7441 064 7442 064 7445 090	7482 0.85 7483 0.85 7484 0.98 7485 1.00	7493 040 7494 088 7495 0.70 7496 080	74122 0.50 74123 0.70 74141 0.75 74154 1.20	16137 30 NPN transistors BC107/8 plastic 60p* 16138 30 PNP transistors BC177/178 plastic 60p*
16168 5 pieces assorted ferrite rods 600° 16169 2 Tuning gangs MW/LW VHF 600° 16170 - 1 Pack wire 50 meters	7404 0.15 7405 0.15 7406 0.30 7407 0.30	7413 0-27 7414 0-58 7416 0-28 7417 0-28	7447 078 7448 080 7475 048 7480 050	7486 0.30 7489 2.50 7490 0.42 7491 0.75	74100 1-00 74110 0-50 74118 0-90 74119 1-85	74180 1.00 74181 2.00 74190 1.40 74198 1.85	16139 25 NPN T039 2N697/2N1711 silicon 60p 16140 25 PNP T039 2N2905 silicon 60p 16141 30 NPN To18 2N706 silicon.
assorted colours single strand 60p 16171 10 Reed switches 60p* 16172 3 Micro switches 60p* 16173 15 Assorted pots 60p*	7408 015	7440 0.15		7492 045	74121 0 30	74199 1.85	switching 60p 16142 25 NPN BFY50/51 60p 16143 30 NPN plastic 2N3906 silicon 60p*
16174 – 5 Metal jack sockets 3 x 3-5 mm 2 x standard switch types 60p° 16175 – 30 Paper condensers – mixed values 60p°	Type Price	Type Price	Type Price	SIC'S	Type Price	Type Price CD4071 0-23	16144 30 PNP plastic 2N3905 silicon 60p* 16145 30 Germ OC71 PNP 60p 16146 15 plastic power 2N3055 NPN
16176 - 20 Electrolytics trans. types 60p° 16177 - 1 Pack assorted hardware Nuts/bolts, gromets etc 60p	CD4000 015 CD4001 018 CD4002 018 CD4006 098 CD4007 018	CD4012 0 20 CD4013 0 52 CD4015 0 98 CD4016 0.50 CD4016 0.50 CD4017 0 98	CD4023 0 20 CD4024 0 80 CD4025 0-20	CD4031 2-20 CD4035 1-30 CD4037 0-95 CD4040 0-95	CD4046 1-30 CD4047 1-10 CD4049 955 CD4050 055	CD4072 0-23 CD4081 0-20 CD4082 0-23	TO220 case: £1.20 16147 10 TO3 metal 2N3055 NPN £1.20 16148 20 Unijunction transistors
16178 - 5 Mains slide switches assorted 60p* 16179 - 20 Assorted tag strips and panels 60p	CD4007 0.18 CD4008 0.98 CD4009 0.58 CD4010 0.58 CD4011 0.20	CD4017 098 CD4018 100 CD4019 055 CD4020 110 CD4021 098	CD4027 0 60 CD4028 0 98 CD4029 1 15	CD4041 0 B2 CD4042 0 B2 CD4043 0 9B CD4044 0 94 CD4045 1 40	CD4054 1-10 CD4055 140 CD4056 135 CD4069 040 CD4070 040	CD4510 1-30 CD4511 1-60 CD4516 140 CD4518 1-25 CD4520 1-25	1Is43 60p 16149 101 amp SCR T039 £1.20 16150 8 3 amp SCR T066 case £1.20
16180–15 Assorted control knobs 60p° 16181 – 3 Rotary wave change switches 60p° 16182 – 2 Relays 6-24v operating 60p° 16183 – 1 Pak, copper laminate approx			LINEAF		CD4070 040		G.P. SWITCHING TRANSISTORS
200 sq inches 16184 - 15 Assorted fuses 100mA- 5 amp 16185 50 metres PVC sleeving	Туре Price САЗО11• £1:05	Type Price MC1456G	Type Price	Type Price uA710C• £0.40	Type Price SN76013N*	Type Price	T018 sim to 2N706/B BSY27/ 2B/95A ALL usuable devices No open & shorts ALSO available in PNP similar to 2N2906, BCY70
assorted size and colours 60p METAL FOIL	CA3014* £1.70 CA2018* £0.75 CA3020* £1.70 CA3028* £1.02	£140 MC1466L £450 MC1469R £295 MC1496G	£1.50 LM320-24v £1.50 LM380-14P	72710* £0.30 uA711C* £0.32 72711* £0.32 uA723C £0.45	£1.75 SN76023N* £1.75 SN76110*	£1.65 TAD 100* £1.30 TBA5400* £2.20	20 for 50p, 50 for £1, 100 for £1.80, 500 for £8, 1000 for £14 - When ordering please state NPN/PNP
CAPACITOR PAK	CA3035* £1.70 CA3036* £1.35 CA3042* £1.50 CA3043* £1.85	£0.98 NE536*£3.50 NE515A*£3.50 NE540*£1.50	£0.85 LM381 £1.55 LM3900N £0.65	72723 £045 uA741C £024 72741 £024 741P £020	£1-50 SN76115 £1-90 SN76660*	TBA6418* £2.25 TBAB00* £0.80 TBA8105*	SILICON DIODES G.P.
- like williard C280 series. Mixed values ranging from O1uf - 2-2uf. Complete with identification sheet. O/N.16204 £1-20*	CA3046* £0.80 CA3052* £1.60 CA3054* £1.35 CA3075* £1.50 CA3081* £1.50	NE550 £095 NE550D NLA NE555 £032 NE556 £082 NE561 £395	MC724P £1.50 MC1303L* £148 MC1304P* £1.90	uA747C* £070 72747* £079 uA748* £035 72748* £035	£0.75 SL414A* £1.95 TAA550B £0.35 TAA621A*	TBAB20* £0.80 TBA9200* £3.40 TCA2705* £2.20	300mW 40PIV (min) sum-min FULLY TESTED. Idea) for Organ builders. 30 for 50p, 100 for £1.50, 500
SLIDER PAKS 16190 - 6 Slider potentiometers mixed values 60p*	CA3081 £1 50 CA3089 £2 10 CA3090 £4 25 CA3123 £1 90 LM301 £0 39	NE5628 £3 95 NE565A £1 75 NE566 £1 50 NE567 £1 80	MC1310P* £0.95 MC1312PQ* £1.90	Send	£2.00		for £5, 1,000 for £9.
16191 - 6 Slider potentiometers all 470 ohm 60p ^e 16192 - 6 Slider potentiometers all 10k fin 60p ^e	LM304 £2.00 LM308* £1.60 LM309K £1.50 LM320-5v £1.50	uA702C* £046 72702* £046 uA703A* £025 uA709C* £025	MC1330P* £1-20 MC1350* £1-20	your orders			
16193 6 Silder potentiometers all 22K 1in 60p* 16194 6 Silder potentiometers all 47K 1in 60p*	LM320-12v £1.50	72709* £046 709P* £025	£1-20	to De	pt. PW7,	P.O. B	ox 6, Ware, Herts
16195 – 6 Slider potentiometers all 47K log 60p*	1000				SHOP 18 AT:		STREET, WARE, HERTS EN 9 to 5.30 Mon./Sat.
					AL	U 1	



EDITOR

Geoffrey C. Arnold

ASSISTANT EDITOR Dick Ganderton, C. Eng., MIERE

ART EDITOR

Peter Metaili

TECHNICAL EDITOR

Ted Parratt, BA

NEWS & PRODUCTION EDITOR Alan Martin

TECHNICAL SUB-EDITOR

Peter Preston

TECHNICAL ARTIST

Rob Mackie

SECRETARIAL Sylvia Barrett Debbie Chapman

EDITORIAL OFFICES

Westover House, West Quay Road, POOLE, Dorset BH15 1JG Telephone: Poole 71191

ADVERTISEMENT MANAGER 01-261 6671 Roy Smith

CLASSIFIED ADVERTISEMENTS 01-261 5762 Colin R. Brown

ADVERTISEMENT OFFICES King's Reach Tower, Stamford Street, London SE1 9LS

BINDERS

Binders, for either the old or the new format, are ± 2.85 and Indexes are 45p (Inc VAT) and can be obtained from the Post Sales Department, IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 OPF. Remittances with overseas orders for binders should include 60p to cover despatch and postage.

BACK NUMBERS

We are very glad to announce the re-establishment of a PW Back Numbers Service for our readers. In future back numbers dated from June 1977 only will be available from our Post Sales Department for 65p, which includes postage and packing. Cheques and Postal Orders should be made payable to IPC Magazines Ltd.

Send your orders to:- Post Sales Department, IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF.

<u>Standards</u>

FROM time to time, *Practical Wireless* receives letters decrying the fact that we continue to publish circuit diagrams in which symbols other than those laid down in BS:3939 are used. We are by no means the only "offender", and in fact a letter published in the latest issue of *Electronic Technology*, the journal of the Society of Radio and Electronic Technicians, slates the whole of the UK technical press, with the exception of the text-book publishers.

The writer of that letter, a lecturer in Radio and TV studies at a south coast technical college, complains that his students have to learn not only the BS:3939 symbols for their examinations, but also a variety of other symbols in order to understand circuits published in technical journals. He sees this as a waste of time, and exhorts those responsible to get into line.

While I am, in general, in favour of standardisation, it is as well to realise that we live in a real world. Even if all UK technical journals and magazines used BS:3939 symbols exclusively from now on, there is a wealth of material, both existing and still coming in from abroad, which uses other symbols. If we are not to dismiss that material completely, we must accept that there is this variety and learn to interpret the various forms encountered.


It is, in any case, arguable whether some of the BS:3939 symbols are the best. Taking the humble resistor as an example, while the rectangular box may be simple for a computer or other mechanical draughting machine to draw, the zigzag is much easier to draw freehand with a little practice. Since many draughtsmen now use rubdown transfers to produce finished drawings, it makes little difference to them anyway, so why not make life a little easier for the student and development engineer trying to produce a neat sketch, by sticking with the zigzag? Again, with logic symbols, it has always struck me that the familiar shapes of MIL-STD-806B make a diagram much easier to understand than do the featureless outlines of their BS:3939 counterparts.

It has been said that the prime reason for the adoption of some of the BS:3939 symbols was that they were easier for machines to draw. Since the vast majority of circuit diagrams must surely still be produced by human means, the justification for those symbols is therefore highly questionable. It makes one wonder whether, at some time in the future, the standard which will replace BS:3939 will consist merely of rectangular boxes containing numbers from 1 to n, each indicating a different type of circuit element!

Geoffrey C. Arnold

PLEASE NOTE—CORRESPONDENCE

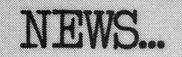We do not operate a Technical Query Service except on matters concerning constructional articles published in PW. We do not supply service sheets or information on commercial radios, TV's or electronic equipment. All queries must be accompanied by a stamped self-addressed envelope otherwise a reply cannot be guaranteed.



NEWS ...

Aid for R & D

The Dept. of Industry has set up an Electrical Technology Requirements Board (ETRB) to fund research and development in the electrical engineering industry. The Board will be composed of eminen't British engineers and chaired by Mr. T. W. B. Sallitt, Director, Hawker Sidderly Group Ltd.

The Board will cover such products as motors and generators, transformers, switchgear, cables and accessories, domestic appliances, and miscellaneous electrical equipment including lamps and batteries.

Major objectives of The Board will be to identify those areas which will most benefit from additional research and development, so as to promote technological innovation and to increase the application of known technology.

The Board welcomes applications from private companies as well as research organisations, for financial support on research and development projects, usually on a co-operative basis, in any of the fields mentioned above.

Enquiries should be addressed to: Dr. L. Goldstone, Executive Officer/ Secretary ETRB, Abell House, John Islip Street, London SW1. Tel: 01-211 3450.

Look in

Five new promotional films, to be shown by Independent Television programme companies, have been made by the IBA to promote 'better viewing'.

- The five films are:
- (1) The importance of the receiving aerial (30 seconds).
- (2) The importance of correct receiver adjustment (60 seconds).
- (3) The expanding coverage of the IBA transmitter networks (60 seconds).
- (4) New technical developments in television broadcasting (60 seconds).
- (5) Controlling the day-to-day quality of ITV broadcasts (30 seconds).

Film (2) on receiver adjustment is to be backed by a special leaflet which dealers and rental companies will be encouraged to distribute to viewers.

The films include shots of many IBA engineering installations and

developments, including the unique Emley Moor concrete aerial tower, low-power solid-state transmitters for local relay stations, the special SABRE adaptive receiving aerial that brings ITV colour to the Channel Islands, DICE—the IBA's pioneering digital standards converter used for intercontinental relays, optional subtitling for the deaf which may become possible by using ORACLE teletext techniques, etc.

New source

Amtest Radio and Electronic Equipment, is a new company set up to specialise in equipment and aerials for s.w. listeners.

They hope in the near future to provide a similar service for long, medium and v.h.f. listeners with the emphasis on DXing.

The company will answer any enquiry, provided it is accompanied by a SAE.

Amtest Radio and Electronic Equipment, 55 Vauxhall Hill, Worcester WR3 8PA. Tel: 0905 22704.

The Wireless?

A foreign spy, an astronaut in deep space, a man in the street ... what have they in common? A radio receiver!

The cost and sophistication varies enormously over the range of available equipment, from a few pounds for the portable 'transistor' to thousands for radar and satellite communications. No matter what the application the advances since the days of the cat's whisker crystal detector have been considerable and it is proposed to survey the subject at a conference on 'Radio Receivers and Associated Systems' organised by the I.E.R.E. to be held at the University of Southampton from 11-14 July, 1978.

Thirty-seven papers will be delivered formally and a further twenty will be presented in poster-booth sessions. An exhibition of relevant equipment is to be organised by the Electrical Research Association. Further details from:

Conference Secretariat, I.E.R.E., 99 Gower Street, London WC1E 6AZ. Tel: 01-388 3071.

Mobile Rally

The Nunsfield House Community Association Amateur Radio Group are holding a mobile radio rally on Sunday 11 June 1978 at Elvaston Castle Country Park, which is located 5 miles south-east of Derby on the B5010.

NEWS ...

Talk-in stations will be available from 10.00am; G3EEO/P on 160m, G3ZBI/P on 2m f.m. ch. S22, and on 70cm G8KGC/P on f.m. chs. SU8 and SU20. All the usual rally attractions will be present; over 40 trade stands housed in two marguees, bring and buy sale, RSGB bookstall, childrens rides and entertainments, sideshows and a full catering service at competitive prices. The I.B.A. will also be present demonstrating their ORACLE teletext service. The rally will be open from 11.00am and should provide an ideal day out for all the family. Further details are available from: Ian Cage G4CTZ, 25 Petersham Drive, Alvaston, Derby DE2 0JU.

Summer School

The Dept. of Electrical Engineering Science at the University of Essex will be holding its annual electronics summer school for teachers during the week 10–14th July, 1978. This year, as well as running two established courses in linear and digital circuit design, a third course in Electronics Systems is being introduced. The object of the course being to cover some of the more difficult material of the AEB Electronics Systems syllabus as well as discussing the teaching aspects of the 'A' level.

The linear design course is concerned with the use of transistors and operational amplifiers in analogue applications; particular emphasis being placed upon design related to basic circuits in a hi-fi amplifier. The digital design course concentrates on the use of the transistor as a switch and develops design using integrated logic circuits. A programme of laboratory work is included on each course. Teachers who require further information contact: R. J. Mack, Dept. of Electrical Engineering Science, University of Essex, Wivenhoe Park, Colchester. Tel: 0206 44144 Ext. 2408/ 2299.



MMM (

200000

phase-locked calibrator

The purpose of this project is to provide an accurate calibration source for digital frequency meters. The 200kHz Long Wave BBC signal is the standard frequency employed, and by regeneration is formed into a 4 volt peak to peak square wave output. It is emphasised that the calibrator requires moderate signal strength for reliable operation, but should function in most areas of the British Isles.

Circuit Description

The aerial coil is tuned by a trimmer in addition to a fixed capacitor. The signal is fed direct to the gate of Tr1, an f.e.t., which is used purely as a high impedance buffer and works in the source follower mode. This feeds its output through C2 to the base of Tr2 which forms a direct coupled amplifier with Tr3. Tr4 is another buffer used to feed the digital frequency meter without influencing circuit performance.

Regeneration is effected principally by capacitive coupling between the can of Tr3 and the aerial circuit. The overall gain of Tr2-Tr3 is sufficient to clip what would otherwise be a sine wave into a sloping square wave at the collector of Tr3. Transistors 2-4 are not run at the full 9 volt supply but are fed via a decoupled resistor, R7, at about 4.5 volts. This, in conjunction with aerial damping resistor R1, serves to restrict the degree of feedback. This technique was adopted when trying to lock on to a French transmission at 180kHz, a rather weaker signal than the 200kHz transmission.

Phase Locking

The circuit as a whole constitutes a free-running multivibrator which happens to use a tuned aerial as part of its feedback loop. Now, as with any multivibrator, it can be triggered by a suitably strong impulse, and the closer the triggering frequency is to that of the multivibrator, the more readily will phase locking occur. By adjusting the aerial close to 200kHz we allow the received signal to trigger the circuit.

However, we have a problem with triggering in that the received signal strength will vary by vast amounts, depending mainly on the distance from the transmitter. One way to overcome this problem is to devise a multivibrator with minimal feedback level, thereby reducing the trigger level required: hence the technique described here.

Construction

The m.w. winding supplied with the ferrite rod is discarded. Only leads 3 and 5 on the l.w. winding are used; lead 4 may be cut short, the ends carefully cleaned, and the two wires resoldered. If "P" clips are not available for mounting the rod it can be glued with Araldite direct to the top of the board.

The board is drilled to take four 4 BA mounting bolts, two of which secure the "P" clips, and also, as appropriate, for the type of trimmer used. These bolts may also be used to mount the unit in a suitable case if desired.

The components are back-wired on 0.15in matrix plain Veroboard and the layout shown should be adhered to, as spurious feedback plays such an important role.

The leads of R8 are formed into loops close to the resistor body before they pass through the board; these loops form the earth and output terminals. A PP3 type connector is fitted enabling either a PP3 or PP6 to be used.

***** components

R2 4.7kΩ
R4 47kΩ
R6 1kΩ
R8 1kΩ
n trimmer
and the second second second second second
v. with ferrite rod, or similar, "P", plain Veroboard 64mm × 95mm case (optional), PP3 connector

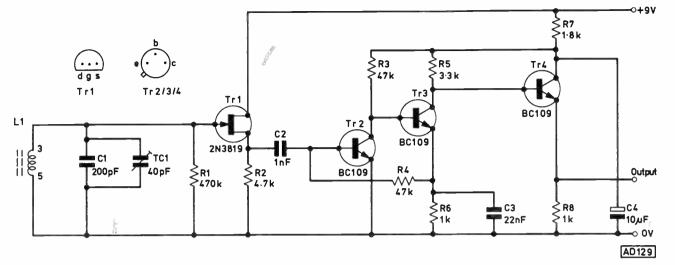


Fig. 1: (above) The complete circuit diagram of the Phase-Locked Calibrator


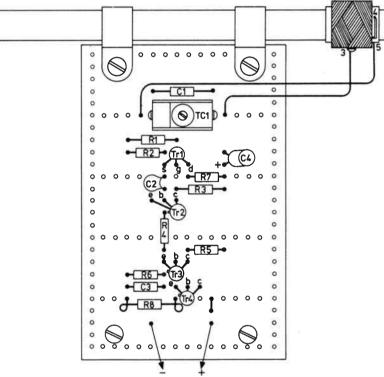


Fig. 2: (below) Component layout and wiring of the perforated board

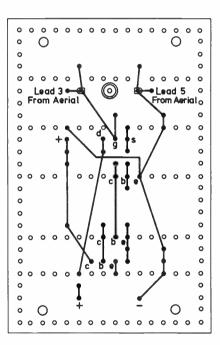

AD130

Alignment

The equipment required for setting up is no more than a Long Wave receiver and an insulated trimming tool (a plastic knitting needle filed to shape will serve). Proceed as follows.

1. Screw down TC1, then unscrew 1_2 to 3_4 of a turn.

2. Connect the frequency meter earth to the 0V side of R8 and the probe to the output loop. Ensure that the unshielded section of the probe runs directly away from the aerial.

3. Connect a battery to the calibrator and then tune in 200kHz on the receiver which is placed nearby with both aligned for best reception.

4. Adjust the coil former on the ferrite rod until a heterodyne whistle is heard from the receiver; continue until the note is fairly low.

5. Using the trimming tool adjust TCl until the beat disappears altogether. At this point the calibrator is phase locked to 200kHz.

6. Switch on the frequency meter, and after a suitable warming-up period make any adjustment necessary.

The coil former may be fixed in place with a few drops of candle wax melted with a soldering iron.

Final Notes


Remember that any digital frequency meter will have a last digit error of plus or minus one, so don't expect the readout to be rock steady. Static or manmade interference, including radiations from the meter itself, if too close, can cause a momentary spurious reading. The circuit, which consumes about 4mA, is quite tolerant of falling battery voltage.

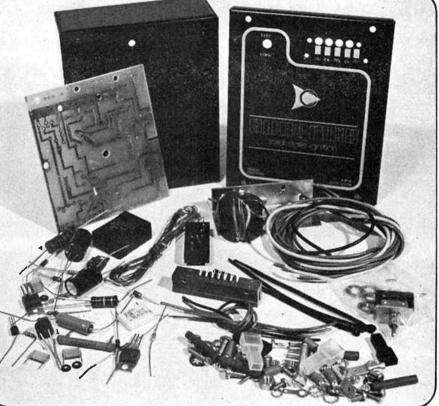The prototype was used some 90 miles from the transmitter at which range locking occurs without difficulty, but at appreciably greater ranges it could be more of a problem.









The S.E.S. Capacitive Discharge Electronic Ignition System has been available for some time in readybuilt form. It is now offered in kit form for the electronics constructor at $\pounds 15.75$ including post, packing and VAT, which represents a considerable saving in cost. Switched selection of electronic or conventional ignition is provided, plus an "isolated" position as an anti-theft device. All the electronics are mounted on a plug-in printed circuit board. This board can be returned to Surefire should service be required, leaving the case fitted to the vehicle, which can continue to run on conventional ignition. The board and edge-connector contacts are all gold plated for reliability.

Assembly

Putting the kit together is quite straightforward, following the clear instructions provided. Total assembly time for the review model was three hours. All the parts required are included—even down to the solder and heatsink compound. The components list allows each item to be easily identified, and also serves as a price list should any replacements be needed, though all components are guaranteed for twelve months. Besides the assembly drawings, a system block diagram, a circuit diagram with typical oscilloscope waveforms, and a full circuit description are provided. There is also a "family tree" fault analysis and testing diagram.

For constructors running into problems with their kits, Surefire offer a repair and fault diagnosis service. To diagnose and repair the printed circuit plug-in module, there is a standard charge of £3, while for the complete kit the charge is £5. In both cases this covers the cost of any parts used in the repair, and includes carriage, insurance and VAT.

Installation

Comprehensive fitting instructions are provided, which are claimed to cover most types of ignition systems likely to be encountered, including those with tachometers. In the case of the review kit, it was found necessary to transpose the male and female "Lucar" connectors on two of the leads connecting into the vehicle ignition system, compared with the assembly instructions given. It is probably best to check against your car before the leads are assembled.

The kits are available direct from Surefire Electronic Systems, Piccadilly Place, London Road, Bath BA1 6PW.



On September 1st; 1927, a British radio amateur, Gerald Marcuse, G2NM, began Empire Broadcasting by transmitting a variety of home-made and recorded programmes on $32 \cdot 5$ metres, using a Zeppelin aerial, from a 100ft mast at his home, 700ft a.s.l., in Caterham, Surrey.


Wireless World, a weekly journal in those days, campaigned vigorously from about 1923 for the BBC to start a regular broadcasting service to the British Empire similar to that given by two Dutch stations (PCGG and PCJJ) to their colonies. Although at first, the BBC were cautious both technically and financially, they did commence tests from Chelmsford, (5SW), in November 1927 and inaugurated a regular Empire service, from Daventry, in December 1932. This has grown into the BBC World Service which dominates international broadcasting today.

Gerald Marcuse, who was born in 1886 and died in 1961, devoted the major part of his life to amateur radio establishing many "firsts" in global communications. He was President of the RSGB during the years 1929 and 1930 and made an Honorary Member of the Society in 1946, the highest award the RSGB can bestow, joining a list of famous names which includes Sir Oliver Lodge, Rene Klein, and Senatore Guglielmo Marconi. In 1922, Gerry held the first amateur licence for wavelengths below 200 metres and in 1923/24 he contacted Canada and the USA on 40 occasions as well as QSOs with the Canadian Steamer Arctic off Canadian Islands and the American Fleet voyaging from Honolulu to Australia. He broadcast concerts from the Savoy Hotel, London, to American amateurs in 1925 and in the same year he made the first phone contact with the US Carrier Seattle, 600 miles east of Australia.

South American Contact

G2NM's achievements were widely reported in the technical press and in January 1925, *Wireless Weekly* published a half page picture of his station and under the heading, British Amateur Works Brazil, are the words . . . "Perhaps the most fascinating of all wireless romances occurred recently when Mr Gerald Marcuse established communication with the Rice Expedition in Brazil, a distance of approximately 7000 miles"... This was a first between the UK and South America.

An interesting item appeared in the Current Topics section of Wireless World (7.9.27) entitled, Reciprocal Empire Broadcasting, which read . . . "Amateur broadcasting to the Empire was inaugurated on Thursday last by Gerald Marcuse (2NM), of Caterham, who transmitted a programme of musical items on a wavelength of $32 \cdot 5$ metres. Mr Marcuse informed Wireless World that the delay in the hour of starting was due to the excellence of reception from Australia,

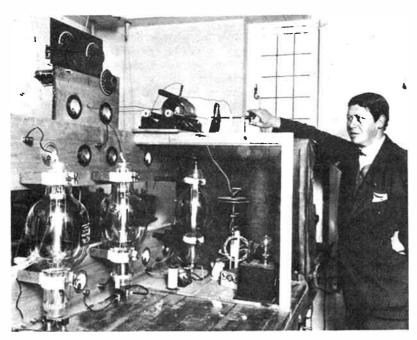

Practical Wireless, July 1978

A photograph of Gerald Marcuse standing alongside his transmitter at 2NM. Reproduced from the November 30th, 1927 Wireless World the broadcasting station 2FC at Sydney sending out an excellent programme on 29.8 metres. Rather than upset reception 2NM delayed transmissions."

This was typical of Gerry's whole attitude to radio, the true amateur spirit prevailed at all times, he was one of the first British amateurs to use telephony and his voice was heard in many parts of the world by radio amateurs and short wave listeners using commercially-built receivers.

The RSGB's history book, World at Their Finger Tips, says that Gerry first got the idea of providing a broadcast service to the British Empire when an amateur, (BER) in Bermuda rebroadcast his transmissions to other amateurs in neighbouring islands.

After much correspondence and a great deal of pressure from G2NM the Postmaster General decided, on August 9th, 1927, to authorise him to transmit speech and music, for two hours daily, except Sundays, for a limited period commencing September 1st, 1927, with a power not exceeding 1kW and wavelengths of 23 and 33 metres. In fact transmissions from 2NM continued almost daily until the end of August 1928.

Among his programmes were the sounds of Big Ben, the songs of the blackbird and thrush from his garden, piano playing of a local friend, voices from his nearby church choir, gramophone records, rebroadcasts of 2LO transmissions and several concerts. Naturally, *Wireless World* followed Gerry's work and in the caption below a picture of his transmitter (*WW* 30.11. 27) they proudly announced, "Mr Marcuse scored a new success on November 11th when his relay of the Albert Hall Armistice Concert was heard in Bombay".

The Wireless World Editorial (27.4.27) pointed out that British amateurs were accustomed to listening to the Dutch broadcast station at The Hague, PCGG, which sent out regular Sunday afternoon concerts for the benefit of UK listeners. Furthermore, Holland had again set an example by leading the way in shortwave broadcasting, because, on March 15th the station, PCJJ, established at the Philips Lamp Laboratories at Eindhoven communicated by wireless telephony with the Dutch station at Bandoeng, in the Dutch East Indies, on a wavelength of 30 metres. The Editorial continued "Since that initial success fairly regular broadcasting has been conducted. Now, as we go to press, comes the announcement that the Sydney station, 2BL, has successfully rebroadcast one of the programmes".

A reader, Arnold J. I. Bradley, writing to the Editor of Wireless World (12.10.27) said "My congratulations upon the splendid stand you have made in the interests of Empire broadcasting and to Gerald Marcuse for the excellent transmissions, restricted though they may be. I sincerely hope that as a result of this the British public will give credit, which is admittedly due to the splendid band of amateurs who, in spite of bureaucratic red tape, are doing their bit to keep alive that fine British pioneering spirit". Arnold Bradley's remarks were typical of many letters on this subject in the late twenties, and he continued "Let the BBC highbrows and "nobrows" listen to PCJJ's radio acknowledgements of regular reception by Britishers in the Antipodes-that should convince them that Empire broadcasting is possible". In another letter, reader J. D. Cumming, Cape Town, (WW 14.9.27) aimed at Captain P. P. Eckersley, then Chief Engineer of the BBC, said, "It is a pity that Mr Marcuse and Captain Eckersley cannot exchange enthusiasm for a few months".

BBC Experiments

The first experimental transmissions by the BBC to the British Empire took place on November 5th, 1927 from their experimental short-wave station at Chelmsford, 5SW, and as World at Their Finger Tips points out; "Marcuse had shown the advantages to be gained by using wavelengths around 32 metres for Empire broadcasting. The BBC began their overseas service on 20 metres with the result that for a long time signals from 2NM were received more consistently and more strongly in Australasia and other distant places than were those from the BBC shortwave station at Chelmsford".

Reader, J. W. Riddiough, Menston, Yorks, writes $(WW \ 21.9.27)$, "Bravo, 2NM. If the BBC cannot or will not do it, there are amateurs who can and will".

To find the most suitable times for broadcasting to Australia the BBC engineers at Chelmsford conducted a 36-hour continuous transmission test which was monitored by Amalgamated Wireless (Australasia) Ltd from 12 noon GMT on November 5th, 1927, to midnight on the 6th. Questions were asked; What proportion of listener's money is being spent on Empire transmissions? and the answer, given to Wireless World by an official at Savoy Hill, "Not a penny, the BBC is collaborating with the Marconi Company in these tests, but we are not spending more money than the ordinary programmes demand. Our part in the experiments is to provide the Marconi Company with broadcast material. As on Armistice day, transmission of this material is also suitable for the British public; the Dominions merely have the opportunity to share it". Gramophone records were broadcast throughout the 36-hour tests.

Wireless World, (21.12.27) suggested that shortwave enthusiasts should make a point of listening for the transmissions from 5SW, Chelmsford, on a wavelength of 24 metres at 12.30 to 1.30pm and 7pm to midnight GMT. The programmes were relayed by line from London and consisted of the ordinary transmissions from 5XX. One valuable and possibly unique report came from H. A. Hankey, representative of the Wireless League, who, in the spring of 1928, made a voyage to the Antipodes, via South Africa, on the steamer Demosthenes of the Aberdeen Line. Hankey was permitted to install an Eddystone 3-valve (Det. and 2 l.f.) short-wave receiver, fed by a 50ft wire aerial, in the ship's navigation room just below the bridge. During the voyage he checked the Chelmsford signal at 35 different points en route and the results were published, along with a map indicating the check points, and a log of the respective signal strengths, in Wireless World (27.6.28). While off Loanda he heard a strength 9 signal of a special broadcast from the Albert Hall at which the Prince of Wales was present.

Along with international broadcasting came a demand for new short wave receivers and Wireless World (29.6.27) devoted 6^{1}_{2} pages to the detailed construction of a 2-valve receiver, by H. F. Smith, covering 20 to 70 metres, for Empire Broadcasting. Some 18 months later, the same author took another 6 pages to promote The New Empire Receiver, which had 3 valves, (Det. and 2 l.f.) and 3 plug-in coils for ranges 23-45 metres, 38-90 metres and an "ultra short-wave" band 16-28 metres. The approximate cost of the components, including cabinet, but without valves and accessories was £7.2s.6d. Early in 1929, Burndept produced their Empire Screened Four, "A Short-Wave


Receiver with Screened-grid H.F. Amplification" covering 20-48 metres. The circuit consisted of a screened grid h.f. stage followed by a leaky grid detector with reaction and two l.f. stages; the price, £25, exclusive of royalty, valves and batteries.

Receiver Designs

Somewhat different to the Short-Wave 2 described by H. B. Dent, *Wireless World* (4.11.32) covering from 15 to 80 metres with 5 plug-in coils. The blueprint was obtainable from *WW* for 1s.6d, post free, the receiver was available for inspection at their Editorial Offices in Fleet Street and the approximate cost of the parts, excluding valves, was £4.12s.0d.

For some years, up until the end of 1924, Wireless World was the official organ of the Radio Society of Great Britain, and in July 1925 the first issue of the T and R Bulletin, forerunner of today's Radio Communication, was published at the instigation of Henry Bevan Swift, G2TI, and Gerald Marcuse.

In later years the Marcuse family moved to the picturesque seaside village of Bosham, Sussex, where today, outside the church stands a teak seat on which is a bronze plaque inscribed:-"In Memory of Gerald Marcuse, G2NM, Pioneer of Empire Broadcasting, President RSGB 1929-30", accompanied by the badges of both the RSGB and RAOTA. This memorial seat was handed over to the Chairman of Bosham Parish Council (Mr Frank Parham) by representatives of the Radio Amateur Old Timers' Association at a short ceremony outside the church on July 21st, 1962. In the same year RAOTA also arranged for a commemoration plaque to be installed at Gerry's former home in Caterham which reads:-"From this house Gerald Marcuse, G2NM, inaugurated Empire Broadcasting in September 1927".

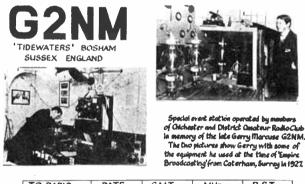

TO RADIO	DATE	GMT	MHz	RST
			Į.	
		l		

The QSL card of special event station G2NM, operating from Bosham, West Sussex, on 24/25th June, 1978

To commemorate the 50 years of Empire Broadcasting, the Chichester and District Amateur Radio Club are operating a station from Bosham on June 24th and 25th, and have a special QSL card to mark the occasion. Although they will be active on 2m, G8NMF, they intend to concentrate their efforts on the DX bands, as Gerry did. Owing to the limited space available, people wishing to visit the station **must** first contact Terry Allen, G4ETU, QTHR, to make arrangements.



To:- READERS PCB SERVICES LTD, PO BOX 11, WORKSOP, NOTTS

Please supply PCB/s as indicated by tick/s in box/es.....

lssue	Project	Ref	Price P/I	P
Dec 75	Sound-To-Light Display	DN0798	1 · 15+12	
Dec 75	Disco System, Amp. (2 req	'd) each AM0421	4-40+22	
Dec 75	Disco System, Light Modu	lator AM0423	3.50+22	
Mar 76	CMOS Crystal Calibrator	A M0438	1.19+12	
July 76	Disco Preamplifier	A003	0.65+12	
Oct 76	Digital Car Clock (set)	A011/012/013	2 · 58 + 12	
Oct 76	Interwipe	DN8JM	0.80+12	
Oct 76	Video-Writer (set)	D002/3/4/6 A007	21 - 44 + 50	
Nov 76	Cirtest Probe	A018	0.48+12	
Nov 76	Burglar Alarm	A019	0.20+12	
Dec 76	Chromachase	A021	5.70+22	
Jan 77	Oscilloscope Calibrator	A023	1 • 25 + 12	
Apr 77	Gas/Smoke Sensor Alarm	A028	0.65+12	
May 77	2-Way Intercom	D019	1.28+12	
May 77	Protected Battery Charger		2.38+12	
May 77	Seekit Metal Locator	A031	3.38+12	
June 77	Versatile AF Generator	A033		
	Tele-Games	D029		
July 77	20W IC Amplifier	A034		
July 77	Radio 2 Tuner	A035	1.68+12	
July 77	Digital Clock Timer	A036	3.58+15	
Aug 77	Shoot (Telegames)	D035	-	
Aug 77	Atomic Time Receiver	D036	2.65+15	
Aug 77	Morse Code Tutor Cards (4.75+15	
Sept 77	Jubilee Electronic Organ		19.00+75	
Sept 77	Electronic Car Voltage Re	•	1.25+12	
Oct 77	Audio Level Indicator	D039		
Oct 77	Sine-Square Wave Genera		-	
Nov 77	Laboratory Power Supply	A039	3.50+12	
Jan 78	Direct Conversion Receive		· · · ·	
Jan 78	Proportional Power Contro	oller DN9JM R001	0·78+12 1·40+15	
Mar 78	Audio/Visual Logic Probe Europa Stereo Amplifier	R002	9.55+45	
Apr 78	DX'ers Audio Filter	D001	2.35 + 15	П
May 78	Bovington Tank Game	R006		
	Audio Distortion Meter (se		-	
	Darkroom Timer	R011	1.55+15	
July 78	Avon Transmitter	R015/16/19/20		П
July 78	Digital Lock	D002	1.25+15	
July 78	Morse Tutor	R014	2.35+15	ň
Post and VAT. Re	d packing is for one board o mittances with overseas or h by sea or air mall as requ	ders must be suf		
	e Postal Order/Cheque	ACCESS welc Send card num		
				T 0
	made payable to Ri			
ADDRE	i\$\$	•••••		•••
	rrespondence concerning to DERS PCB SERVICES and			sed



by **POINT CONTACT**


Constructors of electronic kits come in all varieties, as well as all shapes and sizes. What I mean is, for some the actual job of constructing a project and getting it going is what provides interest and gives them satisfaction. For others, this is only a means to an end, what they want is a finished disco or a 2 metre transceiver at less cost than the readymade commercial equivalent. For these, things are very much easier than they used to be, with printed circuit boards and all components available by return of post. Gone is most of the sweat of "chassis bashing", often undertaken with woefully inadequate tools. (Have you ever made holes for five octal valve holders in a 16s.w.g. aluminium chassis with no more than a 4BA clear twist drill and a penknife?).

Of course, the two categories of constructor mentioned are opposite extremes of a spectrum. For example, hams and SWLs who make their own gear are usually equally absorbed in its design, construction, and mode of functioning on the one hand and in its operation and the contacts made with it on the other.

Whichever category you fall into, we all have to get interested in "how it works" when it doesn't, if you see what I mean. It can be very disappointing to make something up-a radio for example-only to be greeted by a sullen obstinate silence when it is switched on! Sometimes, visually checking everything over carefully again will reveal the fault, but regrettably this is rare. In this predicament, test equipment is the answer and of course the most basic item is a good multimeter, with a sensitivity of at least 10,000 ohms per volt. This enables all the d.c. conditions in a circuit to be checked out and it is surprising how often when they are put right it all works perfectly.

Even more powerful as a troubleshooting tool than a multimeter is an oscilloscope, especially if it has calibrated Y-sensitivity and time-base ranges. A stabilised power supply, a signal generator etc., each is a godsend if at hand when needed. With designs for such things being published from time to time in *PW*, the enthusiastic electronics constructor nowadays has the opportunity to build up a first-class set of test equipment for the home laboratory.

Talking of test equipment, when walking through the lab the other day, Point Contact noticed a knot of curious engineers crowded round a bench. They were trying to guess the purpose of an object rescued from the scrap heap by one of the younger engineers. The cover had been removed exposing a few components and a mains transformer. This had the primary and secondary mounted side by side, separated by an extra limb of core laminations. On the front panel was a knob labelled ADJUST SPARK GAP and lower down there were two leads coming out. One was a threecore mains lead, the other terminated in the handle of what might have been a short stubby poker or a science

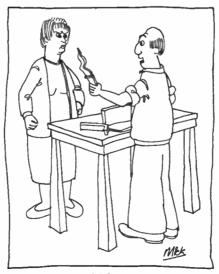

IT'LL NEED SHARPENING, BUT IT CUT THE ALUMINIUM ALRIGHT !"

fiction death-ray gun. The only other item on the front panel was a toggle switch, prosaically labelled MAINS ON-OFF.

No one could think what the object was until the word TESVAC on the front panel prodded my memory. Many years ago, Point Contact used to use something similar for TESting VACuum systems. The fat insulated body of the poker contained an aircored transformer or Tesla coil, the well-insulated high potential output lead of which projected three inches beyond the end of the SRBP body and terminated in a metal tip. We stuffed the end of the mains lead (the plug had disappeared) into the nearest 3-pin 5-amp socket-and nothing happened. Turning the knob, however, produced a fine fierce spark sizzling away continuously and a high-voltage mica capacitor picked off the h.f. components of this and fed them through the screened lead to the Tesla coil. Here the voltage was stepped up further to, I suppose. hundreds of kilovolts resulting in a continuous mauve corona discharge from the metal tip, while the lab rapidly filled with the pungent smell of ozone.

Oh yes-how does it test a vacuum? Well, lab vacuum systems are usually made of glassware and the inevitable leak is at a greased flange joint or through a sub-microscopic pin-hole. When your vacuum system won't pump down to as hard a vacuum as you'd like, you wave the metal end of the vacuum tester all over the glass surfaces. The air in the vicinity of the leak is ionised and as its pressure falls on passing through the leak into the near vacuum, it ionises much more readily. Great mauve streamers appear inside the glass, sprouting from the otherwise invisible leak.

Owing to the high source impedance the tester is quite safe; one can draw a three inch long spark to one's fingertip with no worse result than a sensation like a pin prick!



During the past few years something of a revolution has taken place in the field of amateur electronics. The valves and transistors of the past have been overtaken by a wide range of integrated circuits (i.c.s) or "chips" as they are often called. These new devices make possible amateur electronic projects which, only a few years ago, would have been just science fiction dreams. The integrated circuits available range from simple two- or three-stage audio amplifiers up to microprocessors with some 20,000 or more transistors packed on to a tiny chip of silicon.

Some integrated circuits, such as those for audio, radio or television applications, are linear types and they work in much the same way as their discrete component counterparts. It will be noticed however, that the great majority of i.c.s advertised have type numbers in the 74 and 4000 series. These are logic devices originally developed for use in digital computers and industrial control systems.

What can Logic do for us?

So all of these digital logic chips are available but how can they be used in amateur projects? Let us consider radio communication. Amateur radio operators and keen short wave listeners often need to measure frequencies accurately. The old methods of using heterodyne wavemeters, calibration charts or even crystal markers work quite well but they are rather inconvenient. Modern communications receivers often indicate the frequency, to perhaps the nearest 100 hertz, as a number on a digital display. This facility is achieved by using logic circuits.

Basically all we need do to measure frequency is to count the number of cycles of the signal that occur in an accurate time period. If the time period is a millisecond then the answer will be the frequency in kilohertz. Logic devices are very good at counting things and measuring time periods.

To measure time we simply count down from an accurate crystal-controlled oscillator. The count can be arranged to provide the answer in hours, minutes and seconds. In fact this is precisely how a digital watch or clock works.

Many amateur radio stations use the radioteletype (RTTY) mode of communication where signals from a typewriter-style keyboard are converted into coded patterns of pulses and then transmitted. At the receiving end, the pulse patterns are decoded and the message is printed out as text on a sheet of paper. Because printers are rather expensive some stations display the messages as text on a modified television receiver. Extensive use is made of digital logic for coding, decoding and displaying the RTTY messages. Morse code, still used by many radio amateurs, can be dealt with in the same way. Messages, typed on a keyboard, are converted by logic to perfect Morse code and at the receiver the signals are decoded and displayed as text on a TV screen.

Logic is very good at sequential control tasks such as running a model railway, controlling a machine, or even switching the lights on a Christmas tree. There are many ways we can use this capability for amateur projects.

Recently logic has crept into television in the form of TV games and Ceefax/Oracle decoders. There are some TV sets which can display the time or channel number on the screen by using logic. In other cases, digital techniques may be used for tuning and for remote control. Even those touch switches on the front of some sets use digital logic.

Some large scale integrated (l.s.i.) digital circuits have been specially developed for use in electronic organs, digital multimeters, digital clocks and calculators. By far the most complex of the logic devices are microprocessors which, unlike the more specialised circuits, can easily be programmed to perform an almost infinite variety of tasks perhaps only limited by the imagination of the user.

People sometimes regard digital circuits as rather mysterious. It is true that when we enter the digital world we shall meet some new concepts, new devices, new circuit symbols and a whole new vocabulary of technical terms. In fact, however, digital systems are not too difficult to understand, and in this series we shall explore the way in which they work and some of the ways in which they can be used.

Digital Signals

First, let us take a look at the signals involved in a digital logic system. Readers will already have met analogue signals, such as those in an audio amplifier, where the level of the voltage or current in the circuit varies in proportion to the signal level. Thus the amplitude can vary continuously over the whole range of signal levels, to give a virtually infinite number of discrete voltage or current levels.

In contrast to the analogue case the signals in a digital logic system can have only two possible levels. One of these is called the "zero" or 0 level, and this corresponds to the signal being turned off. The second level is called the "one" or 1 level and is equivalent to the signal being turned on.

Sometimes in the literature and in data sheets for logic circuits, other names may be used to describe these two signal levels. As an example the 0 level may be referred to as the "low" or "false" level, but it will still have the same value as the 0 level. Alternative names for the 1 level are "high" and "true" respectively. In this series we shall use the 0 and 1 terminology since it seems to be the most popular.

Since logic devices first appeared a whole series of different families of logic, each with their own special characteristics, has been developed. As a result actual voltage or current levels representing the 0 and 1 signals can have a wide variety of values according to the particular family of logic being considered. Over the years some families of devices have become obsolete and others have never become available to the amateur user.

The two commonly met ranges of logic as far as the amateur is concerned are the 74-series TTL (transistor transistor logic) and the 4000-series CMOS (complementary metal oxide semiconductor) types. Sometimes 900-series DTL (diode transistor logic) may be met, but its signal levels are virtually the same as those for TTL.


In the case of TTL, where the devices run from a +5V supply, the 0 level is usually around 0 to 0.3V whilst the *I* level is normally about +4V to +5V. In the case of CMOS logic, the circuits will operate quite reliably over a range of supply voltages from +5V up to +15V. Here the 0 level is effectively 0V and the *I* level is virtually the supply voltage level. Later in the series we shall examine the logic levels rather more closely to see the effects of noise and loading on the performance but for the moment, assuming that we use either TTL or CMOS devices with a +5V supply, we can say that the 0 level will be 0V and that the *I* level will be +5V for all logic signals.


In a typical logic system there may be many input signals, each of which may be at either 0 or 1, and these are combined together and operated upon in various ways to produce a series of digital output signals which will also be at either 0 or 1.

Let us relate this to a simple real-life situation. Suppose we have a hot drinks vending machine and we want to produce a cup of coffee. First of all we shall need a "coffee" input which we shall call signal C. When C is at 1 it will cause a valve to open and pour a measured amount of coffee into the cup. Now some people like their coffee white whilst others prefer it black, so we need a second signal M to control the "milk" input to the cup. For black coffee M will be 0 (no milk) and for white coffee M will go to 1 to allow a shot of milk to be added to the coffee in the cup.

The third constituent of our cup of coffee may be sugar so we might have a third input labelled S which adds sugar to the coffee when S is set at 1. Here we may run into a problem because some people prefer to have more sugar than others and at present we can only cater for no sugar at all or some sugar. We need some arrangement that will allow us to produce, say, one, two or three spoonsful of sugar as desired.

Suppose we have two inputs for sugar which we shall call S1 and S2. We can arrange that when S1 is at 1 it will cause one spoonful of sugar to be added. The valve controlled by S2 however is arranged to add two spoonsful when it is opened. Now if we set both S1 and S2 to 1 there will be three spoonsful of sugar added to the cup. Other combinations of the states of S1 and S2 will allow us to have two, one or no spoonsful of sugar in the coffee. This principle of

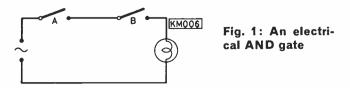

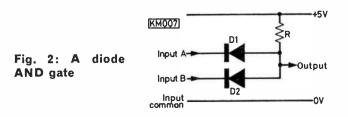

having several "weighted" logic inputs to represent one input signal could be extended to give a finer control of the quantity of sugar selected. We shall see later that in this way analogue signals can be represented as a combination of several "weighted" digital signals.

Now by choosing various combinations of these four input signals C, M, S1 and S2 our drinks machine can be made to produce a wide variety of different combinations. Suppose we want to have a moderately sweet black coffee. The states of the four input signals might be set as follows:

C = 1
M = 0
S1=0
S2 = 1

Readers can work out the other possible combinations for themselves and will find that some are not very palatable. Will it work? Some of the latest drinks vending machines in the USA do in fact use logic, and microprocessors, to control their operation.

The "AND" Gate

Having seen how the digital signals themselves can be arranged, let us now examine some of the actual logic elements and see how they work. A large part of any logic system is likely to be made up from elements called "gates" so let's start with them. A gate is basically a logic unit whose output state is directly related in some way to the combination of logic signals applied to its inputs.

Suppose we have an electrical circuit consisting of a switched table lamp which is plugged into a switched wall socket. The circuit will be as shown in Fig. 1. It is obvious that the lamp can light only when both of the switches are closed to complete the circuit.

This electrical circuit is in fact performing the same function as a logic gate. Here the output signal is the light from the lamp so that the output is at 1 when the lamp is lit. The inputs to the gate are represented by the two switches. When a switch is closed that input is at 1 whilst an open switch gives a 0 input. With this arrangement we can get a 1 output (lamp lit) only when switches A AND B are both at 1(closed). A gate performing this particular function is called an AND gate for obvious reasons.

We can produce an all-electronic AND gate by using diodes arranged as shown in Fig. 2. This is a 2-input AND gate of the type used in digital computers before the advent of digital integrated circuits.

Suppose both inputs A AND B in Fig. 2 are set at 0 (0V). Both diodes D1 and D2 will conduct and draw current through the load resistor R. Assuming that the resistor R has a much higher resistance than the forward resistance of the diodes, the voltage at the output point will fall to virtually zero giving a 0 output state. If we now set input A at 1 (+5V), diode D1 will cut off but provided input B is still at 0 diode D2 will now take up the current originally drawn by D1 and the output level will remain at 0.

When both A AND B inputs are set at 1 both of the diodes will cut off and no current will flow in R. Now the output level will rise to +5V to give a 1 output state. Thus the diode circuit produces the same logical results as the electrical lamp and switch circuit.

If we needed to have more input signals these could be provided by merely adding more diodes. With more inputs the 1 at the output should only occur when all of the input lines are at the 1 level.

Truth Table

A convenient way of setting down the various logic conditions in a gate circuit is by means of a Truth Table. In this table all of the possible combinations of input states are listed, together with their corresponding output states.

For a two-input AND gate such as that shown in Fig. 2 the truth table would be as shown in Table 1. In the case of an AND gate which has three inputs the truth table will have eight possible states as shown in Table 2.

TABLE 1

Inj	Output	
А	В	Y
0	0	0
1	0	0
0	1	0
1	1	1
	_	

TABLE 2	TA	BL	Е	2	
---------	----	----	---	---	--


	Output		
Α	В	C	Y
0	0	0	0
1	0	0	0
0	1	0	0
1	1	0	0
0	0	1	0
1	0	1	0
0	1	1	0
1	1	1	1

Try working out the truth table for a four-input AND gate and you should end up with 16 combinations but the output will be at 1 only when all of the inputs are at 1.

Integrated Gate Circuits

In an actual TTL 2-input AND gate the circuit is roughly as shown in Fig. 3 and is much more complex than our simple diode gate.

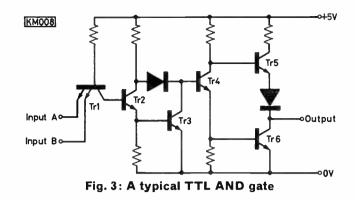The gate action proper occurs in transistor Trl which has two emitters. This stage acts in much the same way as the diode gate so that the transistor




stops conducting if both emitter inputs are at 1. Transistors Tr5 and Tr6 form a "totem pole" output stage which gives a low output impedance and fast switching. For a 1 output Tr5 is "on" and Tr6 is "off" and vice versa for the 0 state. Thus the output is clamped to either 0V or +5V through one or other of the output transistors. The other transistors in the circuit provide the required drive signals for the output stage.

In the 4000-series CMOS circuit a 2-input AND gate would be made up roughly as shown in Fig. 4. In this circuit the series *n*-channel transistors provide the AND gate action operating in much the same way as the series switches in our electrical circuit. The pchannel f.e.t.s Tr1 and Tr2 are used to pull the point X up to the supply rail if either of the inputs is at 0. When both inputs are at 1 Tr3 and Tr4 will both conduct to bring point X down to 0V. The output stage in this case is a push-pull complementary pair. If X is at 0, Tr6 will be "off" and Tr5 will be "on" so the output terminal will be clamped to the positive supply rail to give a 1 output. If X is at 1 the output level will be clamped to 0 via Tr6. In some cases there may be several other stages to provide full drive for the output stage but the operation is much the same.

For more inputs a TTL gate would have more emitters on Tr1, whilst a CMOS gate will have more transistors in series.

Symbol for an AND Gate

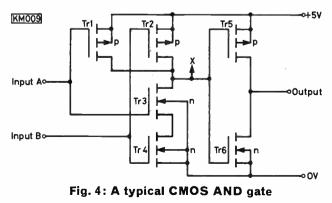Obviously we cannot draw out the complete circuit for every gate so a special symbol is used to indicate an AND gate. This is shown in Fig. 5(a) for a 3-input gate. Where there are a lot of inputs the gate symbol may be modified as in Fig. 5(b) for drawing convenience.



continued on page 60



This month's instalment deals with the construction of Board 3, the Y amplifier. This board uses a ground plane, in view of the high gain and wide bandwidth. With a ground plane, a low impedance earth return is available everywhere, ensuring that decoupling capacitors are fully effective.

As double sided boards were ruled out on the grounds of excessive cost, the component interconnections use conventional wiring. It may well be possible to produce a successful single sided printed wiring layout, but the author lost a considerable amount of time trying to do just this and therefore returned to the ground plane construction used in a previous oscilloscope design. Figs. 3 and 5 show the component layout and wiring, which should be followed closely to avoid instability. Note that i.c. sockets must not be used.

Up to this point, the components mentioned have all been fairly conventional, apart from the special mains transformer and the tube itself, of course. On this board we encounter some more out of the way components, but their use is more than justified by the performance which is obtained.

Take the dual junction gate f.e.t. type E421 (Siliconix) used in the input stage for example. The low temperature coefficient of input offset results in no drift of the trace level from switch on, even on the most sensitive setting of about 2.5 mV per division.

This dual f.e.t. acts as a source follower, providing the necessary high input impedance for use with the frequency compensated input attenuator S3 and a low output impedance to drive the 733 video amplifier IC301. Network R301, R302 and C301 protects Tr301a from excessive input voltages without causing deterioration of high frequency response. R303, R304 and R306, R307 provide d.c. level shifting of Tr301's outputs to bring them within the input range of IC301. They result in a small degree of attenuation of the input signal at d.c. and are therefore not bypassed, to keep the a.c. and d.c. gains equal.

The purpose and adjustment of VR301 is covered in the last article, and at this stage it should simply be set to mid-travel.

The 733 video amplifier IC301 forms the main gain block, and its gain is switched by S301 to provide an overall sensitivity for the complete instrument of 5, 10 and 20 mV/division. A fourth position of S301 brings VR302 into circuit, providing a continuously variable gain facility and incidentally providing a maximum sensitivity of approximately 2.5 mV per division.

The bandwidth of the 733 varies with gain, but even at maximum gain it is 40 MHz, so that in practice the bandwidth of the complete instrument is determined entirely by the Y deflection amplifier Tr303 to 308.

Note that owing to its common mode rejection (typically 60 dB even at 5 MHz) the output of IC301 is balanced, even though an unbalanced input is applied at pin 1.

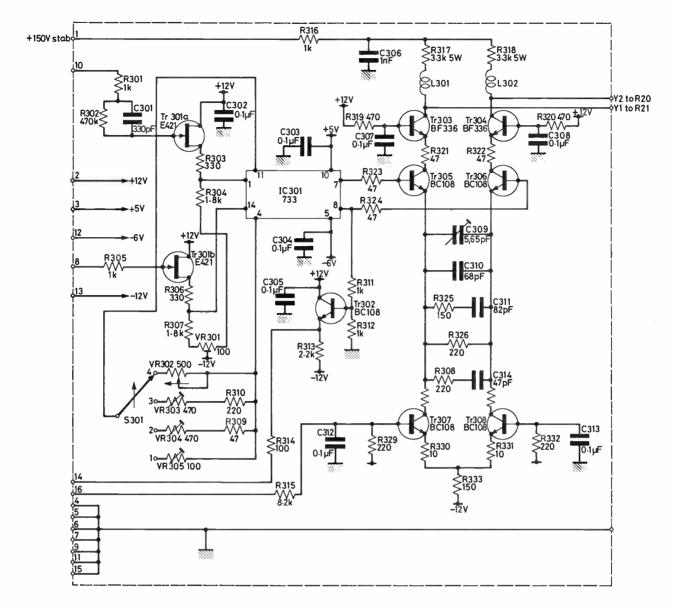


Fig. 1: The circuit diagram of the Y amplifier, clearly showing how the essential bandwidth is achieved; gain block IC301 couples to the Y deflection amplifier, and the R326 by-passing C/R network maintains upper frequency response. Note that R329 and R332 are connected to the -6V supply and that the unmarked resistors in the collector circuits of Tr307 and Tr308 are both 47Ω (R327, 328)

Tr302 is the trigger pick off amplifier. This is by no means a trivial function, as the action of an oscilloscope's trigger slicer circuit can easily reflect back a small disturbance into the Y amplifier. This results in slight notches in each cycle of the displayed waveform, which move up and down as the Trigger Level control is varied. Here, R311, R312 attenuate the signal by a factor of 2 and emitter follower Tr302 acts as a buffer.

An emitter follower provides only limited reverse isolation at high frequencies, but disturbances emanating from the trigger circuit, before they can reach the Y deflection amplifier input, are also attenuated by the ratio of R311 to the output impedance of IC301. This ratio is very much greater than 2:1, as IC301's output stages are emitter followers.

Further buffering is provided by another emitter follower and 2:1 attenuator on Board 4, described next month. R314, like the 47Ω resistors in the Y deflection amplifier, is an anti-parasitic stopper resistance.

The bandwidth of an oscilloscope is usually limited by the Y deflection amplifier. Certain steps can be taken to maximise the bandwidth and a fairly obvious one is to use symmetrical deflection, i.e. to drive the deflection plates in antiphase. For if only one of the two plates were driven, twice the voltage swing would be required, so needing twice as high a collector supply voltage.

For a given deflection transistor dissipation, we would then have to halve the standing current through the output transistor. Twice the voltage at half the current means four times the collector load resistance and this would result in a quarter of the bandwidth!

The Y output transistors Tr303 and Tr304 are used in the grounded base mode. The low input impedance at their emitters results in virtually no signal voltage swing at the collectors of Tr305 and Tr306. There is therefore no Miller multiplication of their internal collector/base capacitance, minimising capacitive loading on IC301's outputs.

The collector/base capacitance of a BF336 is approximately $3 \cdot 5$ pF and this, together with the Y plate capacitance of the 3BP1 c.r.t. and wiring strays, results in a total capacitive loading at the output of Tr303 (and Tr304) of around 10 pF. A peak to peak voltage swing of around 90V is required to provide a reasonable degree of overscan and choosing a conservative value of dissipation for Tr303 and 304 leads us to a standing current for each of just over 15 mA, with $3 \cdot 3k\Omega$ collector loads. Allowing a minimum Vce of 10V to maintain a good high frequency response leaves us with an h.t. requirement of 120V—the excess 30V is dropped by R316.

\star components

Resistors		
₩ 5% ci	arbon	
10Ω	2	R330, 331
47Ω	7	R309, 321, 322, 323, 324, 327, 328
100Ω	1	R314
150Ω	2	R325, 333
220 Ω	5	R308, 310, 326, 329, 332
330 Ω	2	R303, 306
470 Ω	2	R319, 320
1kΩ	4	R301, 305, 311, 312
1 · 8kΩ	2	R304, 307
2 · 2k Ω	1	R313
8 ∙2kΩ	1	R315
470 kΩ	1	R302
5W w.w.		
1kΩ	1	R316
3·3kΩ	2	R317, 318
Potentiom	eters	5
Miniature	vert.	skeleton preset
100Ω	2	VR301, 305
470Ω	2	VR303, 304
‡inch diar	neter	,
500Ω	1	VR302
		•
Inductors		
See text	L30	1, 302
Capacitor		
Ceramic	-	
47pF	1	C314
68pF	1	C310
82pF	1	C311
330pF	1	C301
Disc cera	•	
1nF	1	C306
0·1µF	8	C302, 303, 304, 305, 307, 308, 312, 313
Trimmer		
565pF	1	C309
•		
Semicond	ucto	'8
Transisto		
BC108	5	Tr302, 305, 306, 307, 308
BF336	2	Tr303, 304
E421	1	Tr301 (Siliconix)
Integrated	circu	
LM733	1	1C301
	•	
Switches		
1p 4w rot	arv	1 S301
	J	
Miscellane		
Printed ci	rcuit	board (1) (Watford Electronics)
		board test pins and matching sockets (3)

Now $3 \cdot 3k\Omega$ and 10pF gives a time constant of $3 \cdot 3 \times 10^{-8}$ sec corresponding to a -3dB point of 5MHz and this is in fact the measured -3dB frequency of the oscilloscope for full screen Y deflection. With suitable inductive peaking in the collector circuits, this could be extended by about 20 per cent to 6MHz or a shade more if overshoot were accepted on fast edges. This bandwidth would be independent of the amplitude of the Y deflection. However, in this design a different approach has been adopted. The voltage gain of the Y deflection amplifier from the bases of Tr305, 306 to the collectors of Tr303, 304 is the ratio of the collector to collector load resistance ($3 \cdot 3k\Omega +$ $3 \cdot 3k\Omega$) to the emitter to emitter resistance (R326, 220 Ω).

A gain of 30 for a cascade stage is quite modest, considerably more gain could be obtained by using a lower value for R326.


Advantage has been taken of this extra available gain by partially bypassing R326 at high frequencies with capacitors C309, 310, 311 and 314. This provides increased output current swing at Tr303, Tr304 collectors at high frequencies to charge the capacitance of the Y plates, so maintaining the frequency response level.


This substantially reduces the rise time when displaying pulses or square waves, but there is a limit.

After all, the available current through Tr303 and Tr304 together is set by the tail resistor R333. All the input signal can do is alter its distribution between them.

If due to the large size and fast risetime of an input square-wave, the current needed to charge the deflection plate capacitance quickly enough exceeds the tailcurrent, then we cannot faithfully display the waveform.

The "in" phrase for this is to say that the output voltage of the Y deflection amplifier is "slew-ratelimited". If either the amplitude of the input were

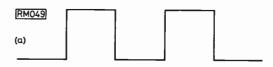

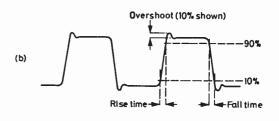

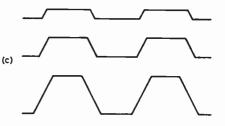


Fig. 2: An ideal square wave is shown in (a) with typical degradations which occur in practice shown in (b). At (c) are the output waveforms from a slew-rate-limited amplifier for three increasing values of input

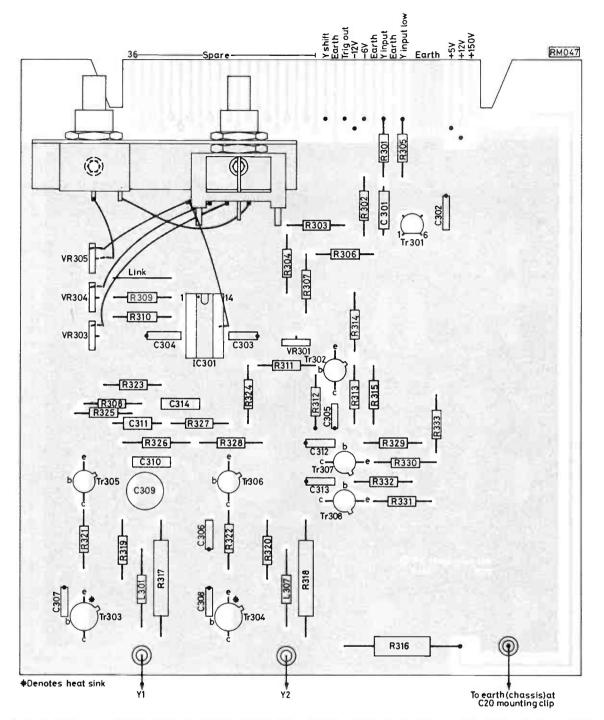


Fig. 3: The component layout of the Y amplifier board. Note that the components are mounted on the copper ground plain side of the board

reduced or its risetime were longer, the output voltage would be able to follow fast enough and the c.r.t. would display the waveform accurately. This is demonstrated in Fig. 2(c) and in fact for four divisions of vertical deflection $({}^{1}_{2}$ screen) the -3dB point is 11 MHz, for two divisions 17 MHz and for one division a remarkable 21 MHz. In other words, the smaller the amplitude of the signal, the higher the frequency which can be displayed. Now many readers will know that a square wave consists of sine waves, i.e. a fundamental and its third, fifth, seventh, etc., harmonics, the amplitude of the harmonics being

Several readers have enquired about the possibilities of using alternative tubes for Purbeck. We cannot advise anyone as to the suitability of components other than those specified. Not only will the mechanical construction need alteration, but revised amplifiers and e.h.t. supplies will also be required.

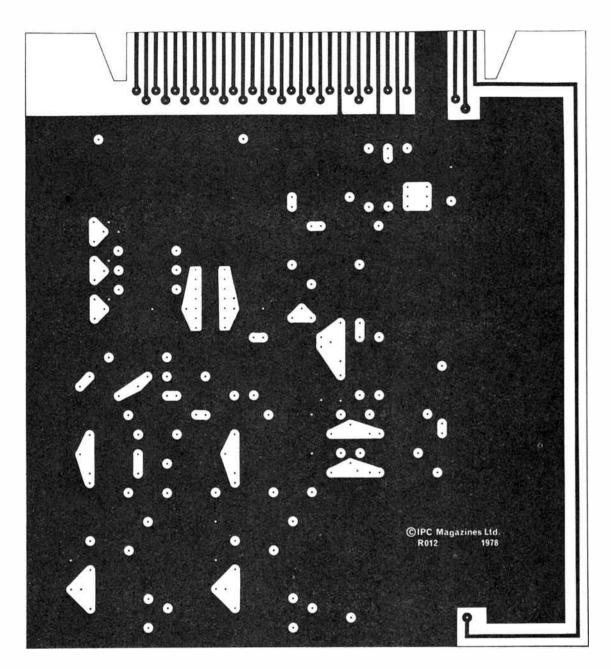


Fig. 4: The copper ground plain pattern of the Y amplifier board

smaller, the higher their frequency.

In other words, the amplitude/frequency characteristic of the amplifier matches the requirements for displaying square waves and pulses. For a vertical deflection of 1 division, the rise time of the oscilloscope is 20 ns, so the display of a 5MHz square wave looks commendably square, whilst even a 10 MHz square wave looks as if it is obviously meant to be

WARNING

Extra care must be taken when working on any part of this instrument while power is switched on. 1100 volts can kill. When delving into the insides of the scope for any reason with power on keep one hand in your pocket square! L301, 302 provide a modest degree of peaking, as do L1 and L2, but are not in any way critical. L301, 302 are 35 turns of 38 s.w.g. wire on $100k\Omega$ carbon composition resistors. L1, 2 (see Part 3) are similarly constructed with 15 turns of 38 s.w.g. wire. R308 and R325 shape the peaking provided by C311, 314 to give a flat frequency response and minimise overshoot and ringing on fast edges.

The emitter current of Tr305, 306 is provided by a long tailed pair TR307, 308. These provide a convenient means of injecting the Y shift voltage via R315. If the Y shift were injected ahead of IC301, the position of the trace would change when the Y gain selected by S301 was changed.

The author has not seen six transistors used in this configuration before: readers might like to think up a name for it—a long-tailed cas-cascode perhaps.

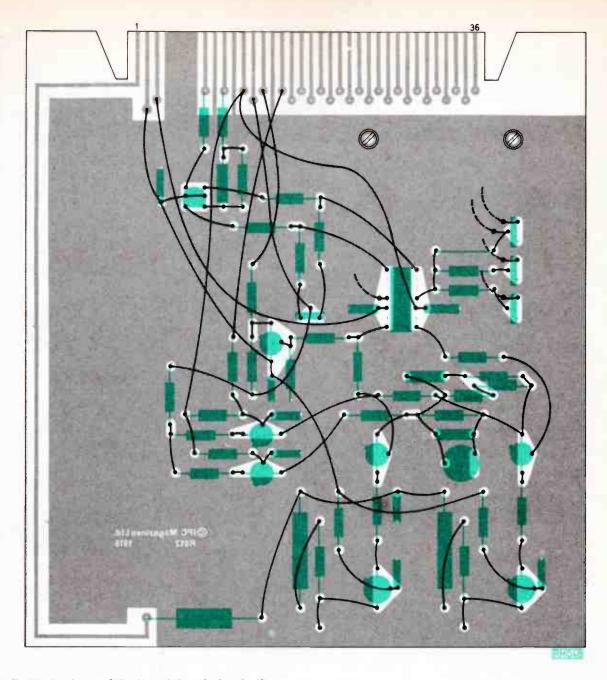


Fig. 5: Back wiring of the board, in relation to the components. This layout of the wiring should be followed to avoid any possibility of instability occurring

When Board 3 has been assembled, check each power supply pin to 0V with an ohmmeter to make sure none is short circuit and centre all pre-set pots and C309. Then plug it into the main frame, disconnect the Y plates from the temporary $47k\Omega$ and $100k\Omega$ resistor chain across the $\pm 150V$ STAB supply (see last month) and connect them via R21, L1 and R20, L2 sockets to pins Y1 and Y2 of the board.

Don't forget the ground link at the rear of the board either. You can also put up a crude timebase of sorts by disconnecting one of the X plates from the $47k\Omega$ and $100k\Omega$ resistors and reconnecting it via a $47k\Omega$ resistor. A 0.1μ F capacitor from the Y plate to pin 2 of Board 1 will give a small 50Hz sinusoidal X deflection. So, plug in briefly and check that all stabilised supply voltages are normal, indicating no short circuits anywhere.

It should be possible to centre the trace vertically with the Y shift control. If not, adjust VR301 as necessary. With a suitable range selected at S3, feed in a sine wave from an audio oscillator. When its frequency is carefully adjusted to exactly 50Hz, 100Hz, 150Hz, etc, a stationary pattern known as a Lissajous figure should be obtained. At 50Hz, this will vary from a line to an ellipse and more complicated figures will be obtained at higher frequencies.

This simple test will enable you to check that the Y amplifier is basically operational and to test that the Y shift works, also that the gain can be varied in steps by S301 and in position 1, by VR302.

Next month we will look at the construction of Board 4, which carries the timebase circuits.

SHOW ROUND-UP

The Twelfth Instruments, Electronics and Automation Exhibition (IEA/ Electrex) was held at the National Exhibition Centre, Birmingham, from 13-17 March, and about 300 companies demonstrated devices and components dedicated to improved efficiency in a variety of electronic applications.

This was an international event, but dominated by British manufacturers, and if the exhibition can be said to have suggested one particular theme, if would probably have been process control in its widest sense. Consequently, although there was little of direct relevance to the home constructor, individual elements and new component applications showed some of the latest developments of interest to anyone involved in electronics.



Graham and White's microprocessor-controlled tachometer.

Connectors are of course a perennial necessity, and Souriou displayed their latest range of high quality connectors for printed circuit and rack mounted applications, these being manufactured to BS, DIN, and VG specifications. Less basic in interest, except perhaps for the housewife eventually, was the display of advanced digital weighing systems with microprocessor control by W. and T. Avery, who have been in the field for many years. Amongst the units available were recording systems fo. load-cell weighers with options such as gross, net, and tare ticket printing, remote cut-off, data outputs, and axle-weighing facilities.

Elsewhere in technical processes, Graham and White showed their new tachometer with memory hold. This is an optical (hand) instrument with microprocessor control, which can be held up to 600mm from the shaft being checked. Reflected light pulses are converted to a meter reading, and the measured level can be "held" for 30 seconds.

Solid State Controls were justly proud of their 5kW direct temperature controller, which features proportional control in the -100 °C-+1600 °C range, and is expected to replace more complex controllers in industrial situations.

Of more direct interest to us. Semiconductor Specialists featured a range of V-MOS power transistors by Siliconix which utilise the MOS process in power transistors for the first time. These devices can be fully driven by the output of a logic gate or microprocessor to deliver up to 2 amps from a 90V rail, making them suitable for audio and r.f. power amplifier applications. Broadly in the same field, Eagle International presented current extensions to their already large range, including the new K1400 high accuracy multimeter (20,000 ohms per volt) along with a new selection of public address amplifiers and associated items.

Although the exhibition was undoubtedly effective in bringing many new developments to the public eye, and was well organised in terms of balance, the same could not be said



The Eagle K1400 multimeter.

of the more human facilities provided by the Exhibition Centre itself. Food and drink was expensive and uninteresting for the captive thousands (eight miles from the city centre!), while the stereotyped snack and drinks bar—identical in each hall—provided little that could be considered conducive to productive conversation or inter-stand relaxation.

At least Pye-Ether provided some relief, however. By means of the lucky ticket system, it was possible to win a bottle of champagne once an hour. The method of selection was not revealed, and although the random pin is the approved traditional method, experience of the show might indicate a suitable ERNIE type microprocessor at the centre of this important operation. Technology rules—OK?

Ted Parratt



If this magazine has maintained one central aim in the forty-odd years of its existence, it has been that of covering the needs and interests of those involved in constructing their own "wireless" equipment. Its identity and direction as a constructor's journal is not now so unswerving as it was in the heyday of sound broadcasting, and a diversity of technical innovations and developments have occasionally deflected it into other channels of activity.

Its current direction may be seen as a result of expansion to cover the interests of constructors in the domestic aids, home entertainment, test gear, and musical instrument fields, but at the root of its long-term personality there is still a deep involvement in the world of the radio amateur and the enthusiastic broadcast band listener. The "Wireless Show", held at the Victoria and Albert Museum from October to December 1977 and organised by Carol Hogben, Assistant Keeper of Regional Services, in association with the Vintage Wireless Society, must surely have been worthy of its attention.

Neither Oersted in 1820, Maxwell in 1864, nor even Hertz, sometimes regarded as the real "father" of radio experimentation, as late as 1888, could conceivably have imagined the dynamic reaction of manufacturers and designers to the stimulus they had created, nor could they have foreseen the almost architectural excellence represented by cabinet designs of the thirties.

The programme covering the range

of exhibits described the show as "130 Classic Radio Receivers—1920s to 1950s," and gave an initial photographic glimpse of some of the stylish, yet functional designs which dominated the British radio receiver field.

It would take a great deal of space to give details of all the models shown, but some of the more unusual items were noted. The first one in the show was a Butler Crystal receiver (1922) which featured Vernier capacitor tuning, and was priced at £2/10/0 $(\pounds 2.50)$. In the same year, Burndept produced their Mark IV Tuner and Ultra IV receiver, which was a valve model, battery operated, driving a Primax pleated cone loudspeaker. One of the first kits, the Cossor Melody Maker receiver, was produced in 1928. This was a 3 valve battery set with horn loudspeaker and cost £7/8/6d. (£7·42+).

Moving up into the "quality" class, the Philips 2511 (5 valve) a.c. mains receiver in "Philite" (Philips bakelite) case with cone speaker in heptagonal enclosure, was reputed to offer good value for money at £37/10/0 (£37.50), a considerable amount in 1930.

More mature readers may remember the Ekco Consolette SH25 of 1932, costing 24 guineas (\pounds 25.20). This was a 5 valve a.c./d.c. mains superhet designed by J.K. White, and was the first to feature a tuning scale with station names.


Another interesting model was the Ekco "Radiotime" receiver of 1947, which retailed at $\pounds 24/3/0$ ($\pounds 24.15$), an a.c. mains superhet featuring

built-in clock and alarm, and this had a strikingly modern appearance. Further unusual receivers included the famous Murphy "Baffle Board" sets of 1946-50, designed originally by A.F. Thwaites. These were console receivers of much improved audio performance, featuring a six valve circuit for a.c. mains in a veneered wooden case.

In a world which has largely been taken over by an enormous quantity of trivia, dominated by scenes (some good, some bad) from the "box", it is refreshing to consider a period when the restriction to sound alone stimulated a powerful reaction of the imagination. While radio still possesses this potential force, it seems unlikely that its exploitation will reach such an exciting pitch as that displayed by the variety of designs evident at the show. Modern receivers are light, efficient, and economical in operation, providing in most cases excellent value for money and a high degree of fidelity. and it is not necessarily a disadvantage that a certain uniformity of shape and function has taken over. Nevertheless, anyone who visited the "Wireless Show" can hardly have failed to experience a sensation of mixed admiration and affection for the designs which represented the parents of high fidelity, a firm base built upon by future generations of engineer and designer in the quest for technical perfection and aesthetic appeal.

Ted Parratt



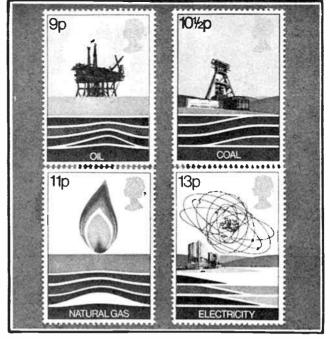

It has become almost commonplace in the last two or three years to allow the term "alternative energy" to slip into conversation about the broad base of human technology. As time passes, the vitality of the term will expand, for energy is the life-blood of an industrial society, and the need for a continuously expanding source of this commodity will surely become more deeply felt as production of consumer items expands, and the demand for warm and comfortable dwellings continues.

The coherent reactions of scientists and engineers to these needs found their fruition in the "Energy Show" held at Olympia last autumn, where many companies demonstrated a variety of answers to both the domestic and the industrial thirst for energy.

Although there were one or two somewhat bizarre contributions, such as the converter to produce natural gas from chicken excrement, which is then fed to a compressor and used to fuel a Land Rover, in the main the responses were related to the production of electricity, and the conservation of heat and power generally.

Lanchester Polytechnic demonstrated its wave power system, based upon the "duck" generators pioneered by Stephen Salter of Edinburgh University. Testing of strings of "ducks" is continuing under a twoyear contract with Sea Energy Associates, and plans to test a 10 kilowatt system were well under way in October. The system appears highly viable, and measurements based upon annual averages indicate that the potential energy available from the British coastline should be within the range of 40 to 70 kilowatts per metre of wave front. Extrapolation of the essential figures (making a conservative assumption of a conversion level of 50% efficiency in the generator devices) shows that it is reasonable to expect that 1 kilometre of Scottish coastline will yield about 35 megawatts of power, sufficient to satisfy the electrical needs of a town of about 80,000 people.

Predictably, a large slice of the proceedings was taken up by stands dealing with solar power. While Lucas provided examples of secondary-cell charging systems utilising solar power, (and wind driven alternators), much the most dynamic illustrations were provided by the non-commercial contributors. The silicon solar cell found more public exploitation via the Royal Aircraft Establishment, Farnborough. One of their experimental solar cell batteries, used in an artificial satellite, was arranged so as to provide power directly to a model railway, access to the Sun's rays being at the mercy of the visitor to the stand. In this way, a direct relationship between Sun, cell and train, showing the link with the environment, was imaginatively established.

Another project, of similar value but only shown in model form, was the solar double-glazed panel installed at Wallasey School, Cheshire, used to augment the school heating system.

Perhaps the most controversial aspect of the entire show, however, and this is a personal opinion, was that dealing with the production of electrical power by nuclear means. The efficiency of the system can hardly be doubted since the cost, as quoted by the UKAEA, is 40% less than from comparable oil-fired stations, and 30% less than coal-fired. However, developments in fast-breeder reactors, and the vital problem of risks from their radioactive waste for future generations, were barely touched upon.

One rather novel exhibit was the National Coal Board's nitrogen operated go-kart. Heat is taken from the air by liquid nitrogen, which then boils, providing pressure for a pneumatic motor. It is hoped that the system can be adapted to power hand tools in mines and on building sites.

In addition to those companies interested in the production of energy, there were also those concerned with saving it. The techniques involved ranged from extensive air curtains for the conservation of heat in offices and factories, and for the maintenance of refrigerated conditions. These included improved insulation methods for domestic applications such as lofts and ceilings, and this section led eventually into a gastronomically interesting stand dealing with economical cooking methods.

Overall the show demonstrated a developing interest in the central problem of energy supply in an expanding community, and also the commercial dynamic which will clearly rise to meet it; most of all though, it displayed the increasingly sophisticated reaction of the inventive minds of engineers to the stimulus of shortage, and if current answers are anything to go by, this challenge will be effectively met.

Ted Parratt.



The ESM 532 20W Power Amplifier

During the past few years integrated circuits which can provide fairly high audio output power levels have become available and one can now obtain up to 20W from suitable monolithic devices. This article describes the new ESM 532 integrated circuit produced by Thompson-CSF Ltd. which can deliver up to 20W at 1% total harmonic distortion into a 4 ohm loudspeaker.

Characteristics

The ESM 532 is basically an operational amplifier which can deliver output currents of up to $\pm 3.5A$. The power supply voltage to the device can be a single supply of not more than 36V or balanced supplies of not more than $\pm 18V$; higher voltages are likely to damage the device even if the higher voltage is only applied as a 'spike' of very short duration. The minimum operating voltage is 9V (or $\pm 4.5V$ with balanced supplies), but obviously the output power available is quite low at such voltages.

The ESM 532 is a quad-in-line device with the connections shown in Fig. 1. Alternate pins are bent so that their tips are at different distances from the body of the device. It can be seen that the normal inverting input (marked -) and non-inverting input (marked +) of an operational amplifier are provided. External frequency compensating components must be connected to pin 3 to ensure stability, whilst the bootstrap connection to pin 1 enables maximum power to be obtained.

A metal insert is fixed along the back of the device and must be clamped to a suitable heat sink. A layer of silicone grease should be placed between the metal insert and the heat sink to ensure good thermal contact; even better is one of the special heat conducting greases available. The thermal resistance between the silicon chip and the metal insert is about 5° C per watt; the heat sink should have a thermal resistance not much greater than 5° C/W.

The ESM 532 is not likely to be damaged by overheating if the heat sink is too small, since the device incorporates protective circuitry which will greatly reduce the output current if the temperature of the silicon chip exceeds the danger point of about 150°C. Nevertheless, it is bad practice to allow any integrated circuit to work at its maximum temperature for a long time.

An additional circuit in the ESM 532 prevents it from being damaged by high currents flowing when the output is accidentally shorted either to ground or to the positive supply line. When such shorting occurs, the internal circuit limits the maximum output current to $\pm 3.5A$ at chip temperatures of up to 100°C or about 1A at a temperature of 150°C.

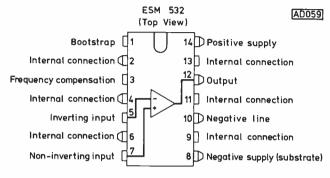


Fig. 1. The connections to the ESM 532

Circuits

Two circuits using the ESM 532 as an audio amplifier will be discussed. One of these employs balanced power supplies and the other a single power supply. The ESM 532 can also be used in television vertical sweep circuits, but these will not be covered here.

Balanced supplies

An ESM 532 20W amplifier circuit using balanced power supplies is shown in Fig. 2. The gain of the circuit is equal to (1+R5/R2) or about 32 (30db) with the values shown, but reasonable variations in the values of R5 and R2 can be made to achieve a fairly wide range of gain values.

The capacitor C1 prevents R5 and R2 from acting as a potential divider at zero frequency. Thus one obtains full negative feedback at this frequency with a circuit gain of unity. Any input offset voltage is

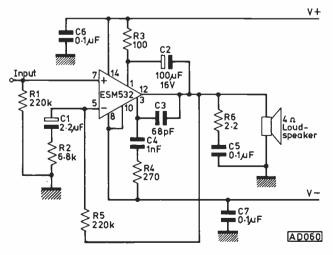


Fig. 2. A 20W amplifier circuit using balanced power supplies

therefore not multiplied by the audio frequency gain of the circuit and the quiescent output voltage is very close to the ground potential; the steady quiescent current passing through the loudspeaker can therefore be kept very small.

The bandwidth (or rather the high frequency response) of the circuit is controlled by the value of C3, the compensation capacitor. The bandwidth is approximately equal to $2.7 \times 10^{-4} \text{ R2/R5C3}$; thus with the values shown, the response extends to about 160kHz, but can be reduced by increasing C3.

The capacitors C6 and C7 are required for good high frequency decoupling to ensure stability; they should be soldered close to the ESM 532. Although these capacitors are connected in parallel with very much larger capacitors in the power supply, the latter capacitors are electrolytics with a fairly large effective series inductance and may be some distance from the device. C6 and C7 have a far smaller series inductance than electrolytics.

Power Supply

A simple power supply for feeding the circuit of Fig. 2 is shown in Fig. 3. D1 to D4 may be four separate diodes (e.g. 1N4002) or a single bridge rectifier containing four diodes (e.g. type REC 63 from Doram). Full wave rectification occurs in this circuit, the output voltage being nearly 1^{1}_{2} times the transformer secondary voltage.

The use of the light emitting diode and its series resistor R1 to indicate when the power supply is switched on is, of course, optional.

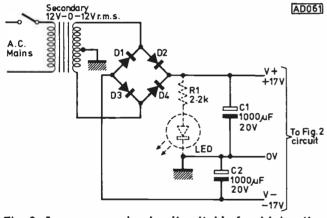


Fig. 3. A power supply circuit suitable for driving the Fig. 2 circuit

Single Supply

The circuit of Fig. 4 has a similar performance to that of Fig. 2, but a single power supply is used. A positive bias must be applied to the non-inverting input in this circuit otherwise the output would be at a low voltage and would not be able to swing lower in voltage to amplify negative going peaks. The positive bias brings the output potential to a positive quiescent value and therefore a large electrolytic capacitor C4 must be included in series with the loudspeaker to prevent a constant quiescent current from flowing through the loudspeaker.

The gain of the circuit is approximately equal to R7/R5 + 1 or about 28 (29db) with the circuit values shown. The bandwidth is about 12Hz to 140kHz with the value of C5 shown. At high values of gain a capacitor in series with a resistor should be connected from the junction of R7 and R5 to ground, the

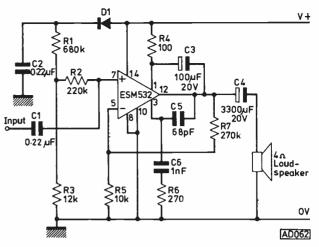


Fig. 4. A 20W amplifier using a single power supply

product of the values of this capacitor and resistor being appreciably less than the product of the value of C4 and the loudspeaker impedance.

Comparison

In general readers will find the circuit of Fig. 2 more convenient than that of Fig. 4, since no large output capacitor is needed in series with the loudspeaker. Thus the high switch-on transient currents are eliminated together with the switch-on 'plop' noise and one obtains optimum response at low frequencies. On the other hand, the power supply used with the Fig. 2 circuit does require a tapped secondary winding on the mains transformer.

Heat sinks suitable for use with the ESM 532 are available from Staver Thermal Products Ltd., Heron Trading Estate, Bruce Grove, Wickford, Essex SS11 8BS under the type numbers V3-3-2020 and V3-5-2020, the latter having the lower thermal resistance of $4 \cdot 5^{\circ}$ C/W. When the ESM 532 has been connected on its circuit board, silicone grease should be placed on it and the heat sink bolted to the board so that it is held in good contact with the ESM 532. Readers can make their own heat sinks using a sheet of metal of area not less than about 70 sq. cm. and bending it as required, leaving the part in contact with the device quite flat.


Other devices

One may well ask how the ESM 532 compares with other 20W devices? It has the same maximum current rating as the SGS-ATES TDA2020, but has a somewhat lower voltage rating than the latter. At present the ESM 532 appears to be somewhat cheaper than the TDA2020 and has the advantage that its typical quiescent current is only 25mA at 28V. The TDA2020 has the lower thermal resistance of 3°C/W (junction to case). The other characteristics of the two devices are quite similar, but the connections are different.

A lower voltage version of the ESM 532 is produced with a maximum rating of 30V under the type number ESM 432. The ESM 532N is similar to the ESM 532, but has a bracket for the connection of a heat sink.

Availability

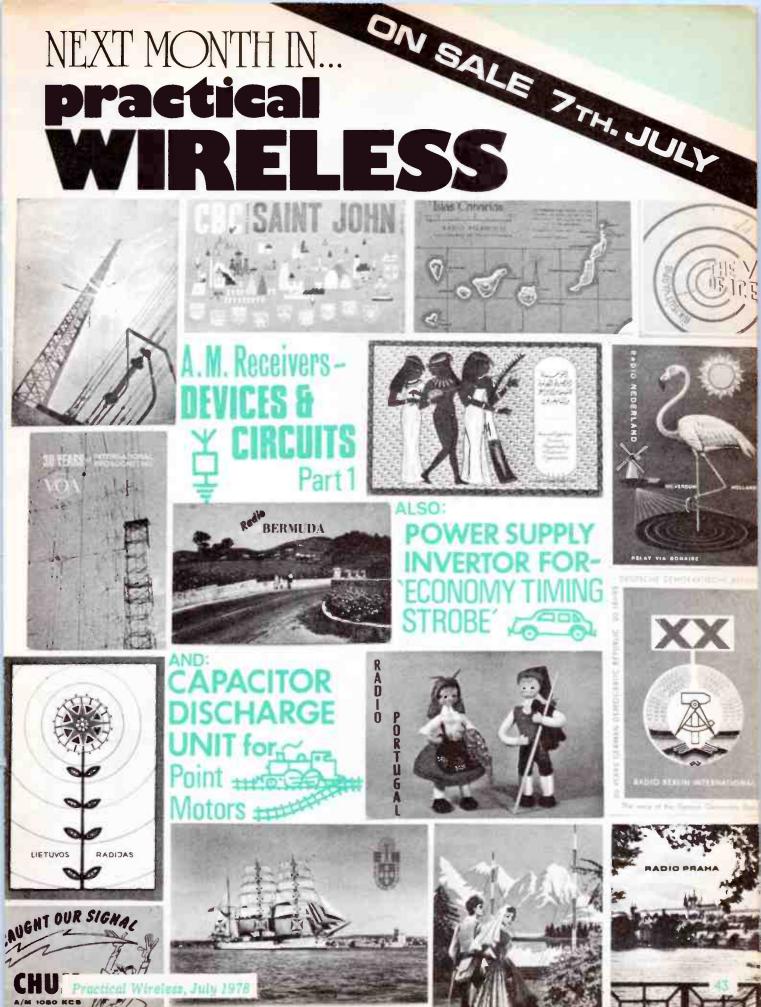The ESM 532 is available from Phoenix Electronics Ltd., 46 Osborne Road, Southsea, Hants at $\pounds 2.95$ including VAT and packing and postage.



World Radio History



With the increased activity on 2 metres, some who may have contemplated working this band, have possibly been deterred by the cost of a "black box" and the uncertainty of modifying commercial equipment. With this situation in mind, the Author has designed a simple, easily-built 2m f.m. transmitter, that can be assembled by anyone who can use a soldering iron and small tools whilst possessing a reasonable amount of patience. The completed unit will perform well, being as versatile as the constructor ultimately wishes to make it. An r.f. output of around 10 watts can be expected if the unit is constructed as described but power far in excess of this may be achieved if the design is regarded as a working basis and the p.a. stage is developed.

Construction

A simple printed circuit technique is employed, with most components fixed directly to the print side of the board. There are very few holes to be drilled and the units may be secured in a suitable housing by straightforward fixing screws. For continued ease of assembly, the transmitter is made on three separate boards; one contains the audio modulator and crystal oscillator, the others the frequency multipliers and the final the power output stage. For low power working (QRP) only the first two boards need to be made, as the output of the second is on 2m, although at only a few tens of milliwatts.

Constructors who have not yet etched a printed board will now find how easy it really is and full instructions are given with details of the board layouts. As with all projects of this nature, it is strongly recommended that the components used are of the kinds specified. Resistor wattages are not critical, but as their ultimate size is governed by their powerhandling capacity, space may determine type.


The Crystal Oscillator and Audio Stages: Board 1

The theoretical circuit is given in Fig. 1 and consists of a Colpitt's oscillator using 8MHz crystals. Six channels are shown in the schematics—three, in fact, were used for the prototype—but there is no reason why many crystals cannot be included by using a suitable multiway switch and increasing the number of islands on the board; using the smaller HC25 series crystals would permit more channels to be fitted in the space allotted. The trimmers in series with each crystal allow easy netting to the assigned frequency.

The f.m. is applied to the oscillator by a reactance stage, fed by two audio pre-amps. Deviation is controlled by a $10k\Omega$ potentiometer and the maximum attained on the prototype was 8kHz. Notice the inclusion of decoupling in the audio stages to prevent r.f. pickup—so often a cause of poor audio quality in home-constructed equipment. The printed board layout is shown in Fig. 2.

Preparing Board 1 (Fig. 2)

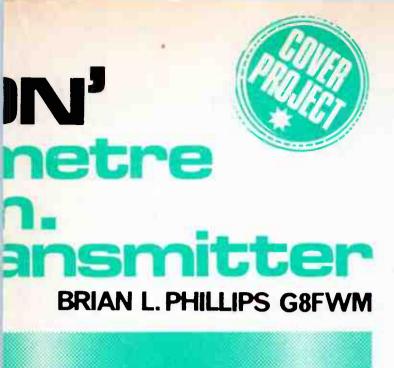Cut a piece of single-sided copper board to the size shown and with some fine abrasive paper, clean the copper surface to remove any oxide or tarnish.



Using a soft, lead pencil, draw out the islands on the board, and then draw around these and the interconnections of the earth plane edge. The small islands and fine connections are then filled in by means of an etch-resist pen or fine paint brush, using quick drying paint, such as car touch-up paint, thinned down if necessary. The larger areas are then put in careReaders who intend to operate the Avon Transmitter should be in possession of the appropriate licence issued by the Home Office to those who have passed the City and Guilds Radio Amateurs' Examination. Details may be obtained from: The Home Office, Radio Regulatory Department, Amateur Licensing Section, Waterloo Bridge House, Waterloo Road, London SE1 8UA.

fully and when the board is dry, each island and connection examined to make sure no copper bridges exist between them. One should also ensure adequate clearances.

Place the board in a suitable plastic or earthenware container and pour on just sufficient ferric chloride solution as is necessary to cover it. The solution can be purchased ready-mixed from most radio component stores, or can be made up by a chemist. It is however a corrosive, albeit a mild one, so handle carefully and wash off any of the solution that comes into contact with the skin *immediately*.

Initially, leave the board submerged for about twenty minutes, agitating occasionally. You will see the chemical action taking place quite clearly and when all the unwanted copper has been eroded, take out the p.c.b., wash in clean water and then dry.

Using a wet abrasive pad—such as a Brillo pad the paint is now removed and a final wash and dry will leave the copper gleaming. After a final check of the work, drill the mounting holes for fixing to the metal chassis.

Each board in the transmitter is etched in this way and provided the simple instructions are followed you should easily be able to provide good examples.



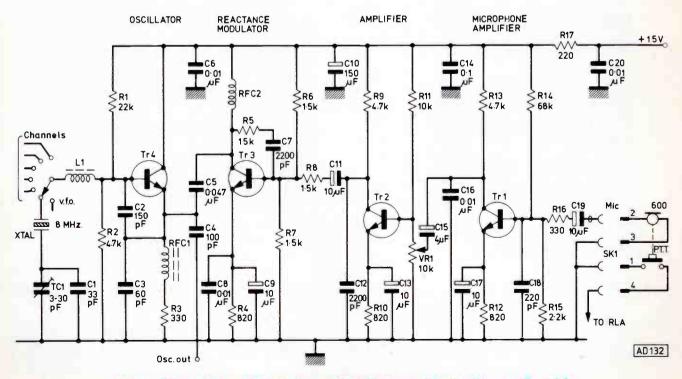


Fig. 1: Circuit diagram for the Crystal Oscillator and Audio Stages-Board 1

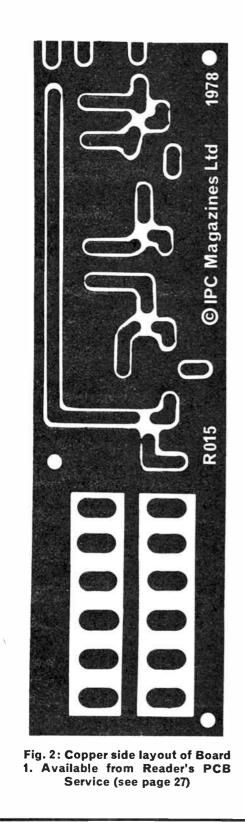

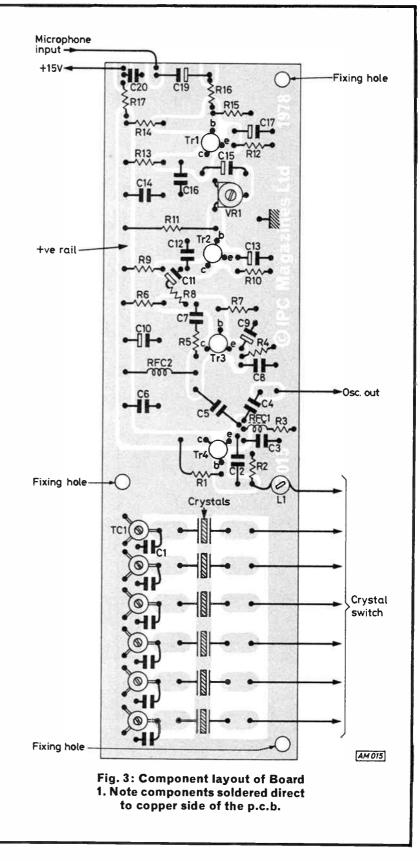

Mounting Components (Fig. 3)

There is no hard-and-fast rule about fixing the components to the board, but the Author favours soldering the resistors first, followed by the capacitors, the coils and finally the transistors. Keep lead lengths short—typically 6-12mm for transistors—and solder neatly, holding the iron in place just long enough for the solder to flow to the joint. An iron of 15W rating with a bit size of 3mm or so is to be preferred for work of this nature.

★ components

		BOA	RD 1				
Resistors						Trimmers	
+ watt 20%		1.1.1.1				3-30pF cer	amic * TC1
220Ω	1	R17	4·7kΩ	3	R2, 9, 13		
330Ω	2	R3, 16	5·6kΩ	1	R6	Semicondu	ictors
8200	3	R4, 10, 12	2 22kΩ	1	R1	BC173	4 Tr1, 2, 3, 4
1·5kΩ	2	R7, 8	33kΩ	1	R11	8C 109C	4 111; 2; 0; 4
2 · 2kΩ	1	R15	68kΩ	2	R5, 14		
					1 P.M. 19	Inductors	
Potention	eter					RFC1	10 turns 32 s.w.g. enamelled copper or
10kΩ log.	pre-set	t 1 VF	1				ferrite bead
						RFC2	As many turns as possible of 32 s.w.g
Capacitor	5						enamelled copper pile-wound onto a 1/2-wat
Ceramic 50							1MΩ carbon resistor
33pF	*	C1	220pF	1	C18	L1	10 turns 24 s.w.g. enamelled copper close-
60pF	1	C3	2200pF	2			wound on 6mm former with iron-dust core
100pF	1	C4	0.01µF	4			
150pF	1	C2	0.047#F	1	C5	Miscellaneo	ous
	1.5					Crystal(s)	within the 8MHz range.
Polycarbona	ate						$quency = crystal frequency \times 18$
0.1µF	1	C14					r type of crystal(s) selected
							BNC socket-v.f.o. input. RS type 455-703
Electrolytic	25V axi	al leads					Tuchel socket, chassis mounting. (Microphone
4μF	1	C15				input)	
10µF	5	C9, 11, 13, 17, 19					
150µF	1	C10	,,			* 1 require	d for each crystal


Testing Board 1

Connect a 15 volt supply to the board—having first established that the polarity is correct—and check the voltages shown: a 15 per cent error is quite acceptable, due to component tolerances. With a 600Ω microphone and a pair of earphones across C11 to the earth line, check for clean audio and the operation of the deviation control.

The oscillator can be tested by connecting a suitable 8MHz crystal in position (i.e. 8.08333MHz for S20-145.5MHz) and listening for the 8MHz signal on a tunable h.f. receiver, coupled loosely to the vicinity of the oscillator stage.

For the moment no audio will be apparent on the signal, because the amount of deviation available at the oscillator is small; it requires the multiplication of subsequent stages to raise this to the required level of 5-6kHz.

Fig. 4: Circuit diagram for the Multiplier Stages - Board 2

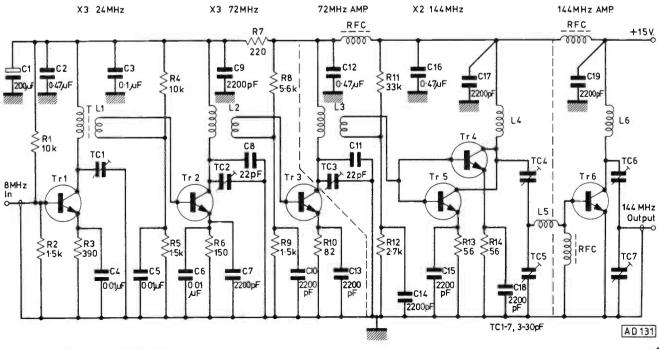


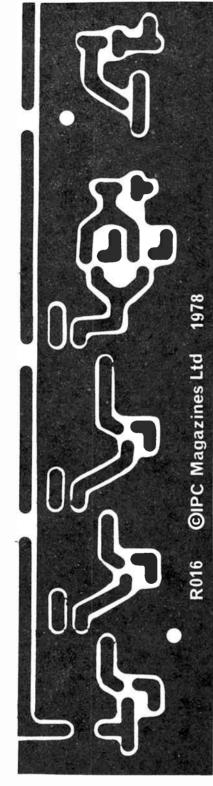


Fig. 5: Copper side layout of Board 2. Available from Reader's PCB Service (see page 27)

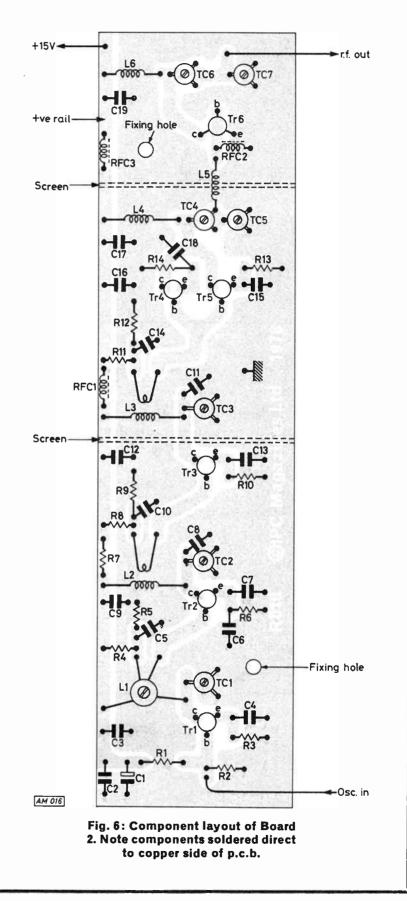

World Radio History

★ components

		BOA	ARD 2						
Resistors						Semicond	uctors		
+ watt 20%						BC173	5	Tr1, 2, 3, 4, 5	
56Ω	1	R14	2.7kΩ	1	R12	2N4427	1	Tr6	
82Ω	1	R10	5.6kΩ	1	R8				
150Ω	1	R6	10kΩ	1	R1	Inductors			
220Ω	1	R7	18kΩ	1	R4	RFC1		urns 32 s.w.g. enamelled copper on fer	
390Ω	1	R3	33kΩ	1	R11			bead	
1·5kΩ	3	R2, 5, 9	56kΩ	1	R13	RFC2	3 turns 24 s.w.g. enamelled copper on ferrit bead		
Capacitors Ceramic 50V						RFC3		turns 32 s.w.g. enamelled copper o ite bead	
22pF	2	C8, 11				L1	18 t	urns 24 s.w.g. enamelled copper, close	
2200pF	9		13, 14, 15	47	10 10		wound on 6mm former with iron-dust core Coupling coil: 4 turns insulated, single-cor wire at lower end of former. Fix with cyano acrylate adhesive.		
0.01µF	3	C4, 5, 6	10, 14, 15	110	10, 19				
	3	64, 5, 6							
Paper						L2, L3		urns 18 s.w.g. enamelled copper 6-3mn	
0∙47µF	1	C3					dia.	, spaced one wire apart. Coupling coil turns insulated, single-core wire ove	
Polycarbona	te							tre of winding. Fix with cyanoacrylat	
0.47µF	3	C2, 12, 16	1912-11-4					esive.	
	051/					L4, L6	3½ tu dia.	urns 18 s.w.g. enamelled copper 6-3mn	
Electrolytic 2 200µF	1	C1				L5	1 tur	rn 18 s.w.g. enamelled copper on 6·3mn ndrel	
Trimmers						Miscellane	ous		
3-30pF cerai	nic					Heat Sinl	k. Pust	h-on type 85° c/w for 2N4427. RS typ	
	7	TC1, 2, 3	4, 5, 6, 7			401 - 419			


The Multiplier Stages: Board 2

The circuit of the Multiplier is given in Fig. 4 and consists of a stage of tripling to 24MHz followed by a further tripler to 72MHz and an amplifier into a doubler for 144MHz.

Transistor Tr1 accepts the crystal oscillator input in its base circuit, and the collector is tuned to 24MHz. This output is link-coupled to Tr2 and its collector is tuned to 72MHz by L2 which in turn is link-coupled to Tr3, also tuned to 72MHz. This brings the signal to a suitable level, sufficient to drive Tr4 and Tr5 in parallel to double to 144MHz in the collector circuit, via L4. Separate current-limiting resistors are used in each emitter circuit to ensure both transistors contribute equally to the output signal. Tests using a common-emitter resistor proved that invariably one transistor tends to be "lazy" and its partner does all the work. This is, of course, due to differences between transistor characteristics. Drive to Tr6 is fed via a low impedance network through TC4 (tune), TC5 (load) and L5. This stage is tuned at its collector to 144MHz and again a capacitance/resistance arrangement is used to feed either the aerial (low power), or the following stage on Board 3. The r.f. output available at this point is about 80-100mW. The board etching layout is given in Fig. 5.

Board 2—Component Layout (Fig. 6)

A plan view of the board for etching purposes is given in **Fig. 5** and **Fig. 6** shows the component locations. There are two screens 25mm high on this p.c.b. to prevent feedback and instability. These are made from brass, tinplate or Radiometal, cut to size and soldered vertically across the board to the earth plane. Care is necessary when crossing "live" tracks: undercut the screen with a small file before fixing, to ensure adequate clearance.

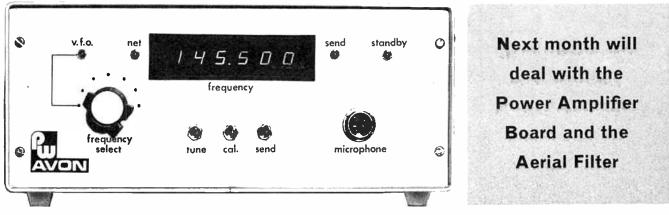


Nothing is more frustrating than getting all the bits to build a PW project, spending time putting it all together and then switching on only to find it doesn't work! Unfortunately, however much care one takes in the constructional stage, this is always a possibility and when it happens, many readers are at a loss to know how to proceed.

From time to time articles have appeared purporting to give the answer to this problem, but people still get stuck, as my postbag shows. Yet really, with a methodical approach one can steadily and reliably progress through a circuit and finish up with it all working. So how? Instead of abstract generalisations, readers may get a much better insight into how to go about it if I give a specific example-a "case study" if you like. And since it has proved such a popular constructional project, I've chosen my "Handy-Mini Power Supply" published in the August 1977 issue, page 260, as the example.

Systematic Approach

With so many readers building this design, one or two were bound to hit some snag or other, e.g. "... have completed the Mini Power Supply... cannot adjust it at all with VR3...please can you help?", from J. D. of Huddersfield. This is where a systematic approach comes into its own, resulting in "... After following your instructions ... Another Tr4 and everything is working correctly ... Thanking you once again for your help" from-you've guessed it-our old friend J. D. again.

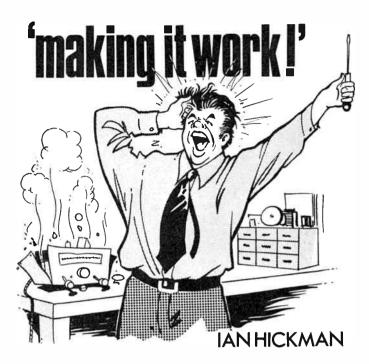So how do we go about it? Well, let's assume you've made up a Handy-Mini Power Supply, tried it and found that it doesn't work. First of all, you may have noticed a slip-up in the editing (mea culpa!). Fig. 3 incorrectly labels the capacitor between base and emitter of Tr3 as C5, actually it's C4, 5µF, as shown in the circuit of Fig. 1 reproduced here, and the



component list. (A correction has, in fact, since been published, but never mind, either value in either place would actually work.)

Multimeter

The technique is to get the circuit working bit by bit. First of all, check that all the circuitry is completely insulated from the metal box, heatsink, etc. Use the highest ohm range on your multimeter for this purpose. If you haven't got a multimeter yet, you really should. It's not necessary to pay an enormous

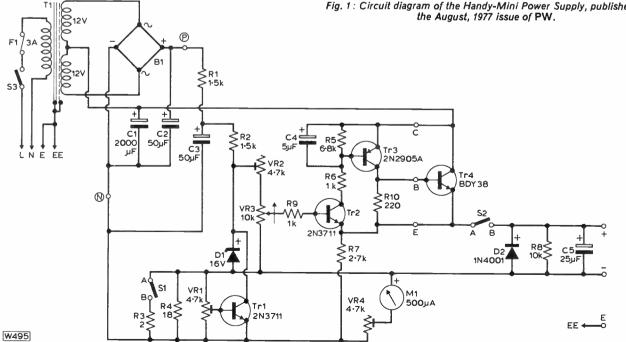


Fig. 1 : Circuit diagram of the Handy-Mini Power Supply, published in

price, but it is worth getting one with a sensitivity of at least 10,000 ohms per volt. Very good value for money is the U4324, advertised in this magazine at $\pounds 14.50$ upwards, but adequate multimeters can be found at a few pounds less than this. They usually use 3V internal batteries for the ohms range and are not likely to damage any common diodes or transistors on any of the ohms ranges.

Stage by Stage

Next, set all preset pots to mid travel, put a short circuit across R4 and disconnect: Tr1 collector, Tr2 base and collector, Tr3 collector, Tr4 base and emitter and the point *P*. Switch S2 to OFF. These moves have isolated the current limit circuit (Tr1, etc.) and divided the rest of the circuit up into sections so we can bring it into operation in stages. With experience you will get into the habit of *building* a circuit in stages and testing it again and again as each stage is added. Now switch on and check that there is approximately 18V across C1 and 36V across C2. (All voltages measured with the negative lead of the voltmeter on the negative lead of C5).

If only one of the voltages is correct, most likely the wiring or B1 is faulty. Before replacing the latter, remember it may have been damaged by a shortcircuited C1 or C2, so check these as well. If neither voltage is there, the trouble may be the wiring, the fuse or T1. From now on, I won't keep saying "the wiring" every time when pointing out possible faults, but remember that if you are using good quality components from a reliable supplier, the wiring is always the most likely cause of trouble. If you are using salvaged components or gems from the junk box—well, good luck! Apart from costing you a lot of time, dud components can cost you money by burning out other good components.

Safety

So now you've checked your "raw supplies" are present and correct, reconnect point P and check that there is approximately 26V across C3 and 16V across D1. ALWAYS PULL OUT THE MAINS PLUG AND DISCHARGE C1 AND C2 THROUGH A 470Ω RESIS-TOR BEFORE WORKING ON THE UNIT. Faults should be fairly obvious, e.g. 30V or so across D1-it's open circuit; just under 1V-it's in back to front! Having checked that the voltages are now right, measure the voltage across the track of VR3 and set it to 12.7V by adjusting VR2. Check that the voltage at the slider of VR3 can be adjusted from 0 to 12.7V. Reconnect the base of Tr2 and temporarily link its collector to point "c"-i.e. top end of R5. We have thus connected Tr2 as a straightforward emitter follower and adjusting VR3 should swing the voltage at Tr2 emitter from 0 to 12V. If it doesn't, it can only be wiring or components and our bit-by-bit approach has only added R9, Tr2 and R7 since the last stage.

Progressing

So assuming you've surmounted that hurdle, remove the temporary connection from Tr2 collector and connect the collector to R6 as in Fig. 1. Also reconnect Tr3 collector to R10. You should now be able to vary Tr2 emitter voltage from 0 to 12V with VR3 as before. Tr2 and Tr3 are now acting as a "complementary compound emitter follower". Sounds technical doesn't it? All it means is that Tr3 does most of the work, with Tr2 turning on just enough to provide sufficient base current to Tr3 to cause it to turn on and pull Tr2 emitter up to about 0.6V below the voltage at the slider of VR3. So Tr3 is supplying most of the current drawn by the load, which in this case consists just of R7 and your voltmeter.

If for any reason you aren't getting this negative feedback from Tr3 via R10—C4 short circuit or Tr3 open circuit for example—Tr2 emitter voltage might not quite make 12V because now all the load current will have to pass through R6. To make quite sure, temporarily put $2.7 k\Omega$ in parallel with R7—you should still be able to make 12V at Tr2 emitter.

Assuming all is well, reconnect Tr4 base and emitter. Now we have two d.c.-coupled complementary stages of amplification (Tr2 and Tr3) driving an emitter follower which provides 100 per cent negative feedback to the emitter of Tr2, and again we should be able to adjust the output from 0 to 12V with VR3. At this stage, we have only added a single component, Tr4, so if something is wrong now the answer is pretty obvious.


Load Testing

Set the voltage at Tr2 emitter to 12V and connect a 100 Ω resistor (at least 1¹₂W rating) in parallel with the voltmeter. The output voltage as measured by the voltmeter should not change by more than the thickness of the pointer. With S1 open, remove the short from across R4 and reconnect Tr1 collector. Check that VR3 can set Tr2 emitter volts to 12V as before. Now on connecting 100Ω in parallel with the meter the output voltage should fall (set VR1 so that it falls to around 5V) but should return to 12V on closing S1. If this is not the case, one of the components in the current limit circuit, R3, S1, R4, VR1 or Tr1, is faulty. For example, output stuck at 0V-Tr1 collector-emitter short circuit. Now close S2 and check that 0 to 12V is available at the output terminals. We have now checked that everything is functional and it only remains to calibrate the unit as in the original article.

The principles of systematically getting a circuit going stage by stage are well illustrated by the above. If you are new to electronics or sometimes have problems getting a circuit to work, it would be well worth while studying the circuit of the original article in conjunction with the systematic approach described above, even if you have no intention of making up a Handy-Mini Power Supply. You will then grasp the principles and be able to apply them to repairing a transistor radio or getting a hi-fi amplifier to work, etc. Although the example given is a simple one, the principles are quite general and the more complex the circuit, the more important it is to divide it up and get it going stage by stage.

Purbeck Oscilloscope

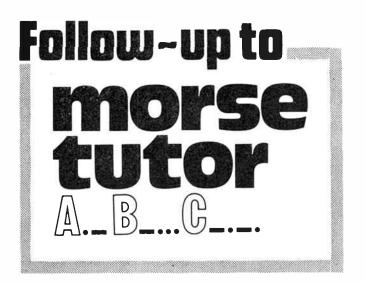
This approach is followed in the PW Purbeck now being published, and should allow any PWreader with an elementary knowledge of how transsistors work and a little constructional experience to build a high-performance oscilloscope for a fraction of the cost of a comparable commercial instrument.




Although we try to take every reasonable precaution to ensure accuracy of presentation and technical efficiency in our constructional projects, it sometimes happens that circuit references turn out to be incorrect or the occasional instance of a reversed diode or capacitor causes universal consternation. When this happens, the editorial department attempts to publish a correction as soon as possible.

In the case of the Morse Tutor, of our August 1977 issue, the details have only just emerged of a divergence between the theoretical and practical instructions. The details are as follows:

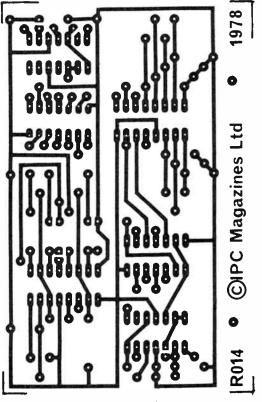The circuit diagram on p. 264 is correct except for the omission of the input B connection to IC2. This should be shown as pin 1. In the "Pin Connections" table on p. 266, "R" and "S" are reversed, i.e. "S" is the 0V terminal.



Copper track layout of the p.c.b.

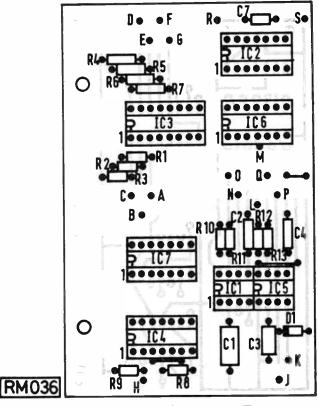

Component layout of the Morse Tutor

The facts concerning the layout on Veroboard are not so simple. It appears that the component overlay relating to a p.c.b. layout was somehow confused with a Veroboard layout, resulting in the essential interconnections being lost. This refers to board A only, and the two remaining boards are correct. How the error arose is not clear, but was probably due to the major changes occurring at the time in the editorial team, with a retiring member handing over the halfformed details to his replacement, the fault probably appearing at the original artwork stage.

Whatever the facts, we have now prepared an accurate p.c.b. layout, complete with component overlay, to assist those who attempted this project. The new p.c.b. and the original code cards are available from Reader's PCB Service.

NEW BOOKS

THE SECRET WAR

by Brian Johnson Published by the British Broadcasting Corporation, 35 Marylebone High Street, London W1M 4AA 352 pages, 243×170 mm. Price £6.50

Those who have been fascinated by the recent BBC Television Series *The Secret War* will be enthralled by this book, which is based upon it, with some additional material. The earliest developments in radar and other radionavigational systems by both the combatants are described in some detail, with a wealth of photographs and drawings. In all, there are over 350 illustrations in the book, many of them previously unpublished.

Apple Scabs beware

An apple a day is said to keep doctors away, and even the old teacher has come in for one of these little green spheres. But have you ever thought how difficult it might be to get you a ripe apple? And did you know that electronics is helping, too?

Apparently, one of the evils of the apple (apart from Adam) is a thing with the endearing title of Apple Scab, a nasty fungus thing which does even nastier things to apples. By making careful measurements of the environment and equating chis with the severity of the attack, growers were able to apply fungicide sprays. But what was the optimum and how could one get away with the minimum amount of spraying thereby saving costs and helping to combat environmental damager?

The answer is electronics. One with-it farmer has installed a complete Apple Scab Bashing system. Electronic sensors in the field (literally!) measure the air temperature, the degree of leaf wetness (hold up your twig I wanna take your temperature!) and relative humidity. All the information is collected and monitored by a predictive computer system complete with microprocessor. The systems gives instant information on how and when to do naslies to the fungus. The entire system electronics employs CMOS and draws only 60mW of power-ideal for battery operation.

Before electronics came on the scene, these figures and measurements took a great deal of time to accumulate, process and then interrogate. The current set up allows all this to be done instantaneously and an operator can be fully trained to handle the system and use it in less than one hour. The result will be, presumably, more happy teachers and fewer overworked doctors.

Smokers beware

Pollution is a current topic which receives much attention in the national press. Eventually, legislation will be brought in to limit the amount of pollution from things like car exhausts, factory chimneys etc. But how do you check if a very tall chimney is polluting or not—except by a long, hard climb?

Some university researchers in the U.S. have come up with a very useful solution based on a laser. It is accompanied by the staggering claim that it can detect and measure---accurately, pollution at a distance of eight miles! The system should be ideal for checking the pollution from those very high smoke stacks. It's even been rumoured that some tall chimney owners keep pollution down during "office" hours and burn all that nasty polluting stuff at night when no one can check.

The system can detect numerous nasties, such as sulphur dioxide and even water vapour. The laser beam is "shone" at the polluting air. Each pollutant absorbs the coherent (i.e. laser) light at different frequencies. So the system receives the reflected laser light and 'tunes' across the band to find out which absorbants/ pollutants are there and how many of them there are. If distance appears to be no object, accuracy certainly isn't. The new laser set up can detect and measure concentrations of, for example, methane of one part per billion over a path of 100 metres.

Doubtless joyous headmasters will use such a device to detect the odd puff of Woodbine pollution generated from the rear of their cricket pavilions!

Solid State Cameras

Some time ago the charge-coupled device appeared on the professional electronics market. It appeared to have a number of applications one of which was to form a photosensitive array for use in solid state TV cameras. The very latest development in this field comes from Japan where a leading manufacturer has revealed some details of its new entirely solid state colour TV camera. This could be a significant breakthrough, and many feel that the vidicon colour cameras for home video just appearing on the market could establish good sales, but only to be ousted by the new solid state versions late in 1979. The camera from Japan uses three c.c. devices, one for each of the primary colours. Each c.c.d. array has some 111,192 separate picture sensitive elements on it-and the surface measures only 10.3mm \times 9.1mm the Japanese have ended up with an effective sensor area of 8.8mm \times 6.6mm which just happens be the size of 0.6 inch vidicons. This clever move allows the same cheap lenses to be used with the new solid state devices.

A REVIEW OF RECENT DEVELOPMENTS

In general, the author does not have any more information on products than appears in the article

CB Linears Out

Have you noticed that the tempestuous uproar about the UK Citizens Band has now practically disappeared? There seems little doubt that it will come and, hopefully, we will have learnt something from the problems in the U.S. and will avoid these (are you listening Westminster?) The latest news from across the pond is that the FCC (they are the American Gods of what you can and cannot do with radio waves over there) has just announced a ruling making it illegal for anyone to produce, import or market linear amplifiers operating in the relevant band. The days when an innocent U.S. youth could purchase a 50mW Citizens Band transceiverand then hook it up to a linear which took up half the garage are over. Apparently nearly 50 per cent of all interference complaints on TVs and radios were traced to linears, hence the ruling.

Fast Pot

Talking components, how about a potentiometer which has manufacturers data for 2,000 revolutions per minute! The design is a contactless one and uses optical means. Construction is quite clever. It consists basically of a resistive film plus an electrode, and sandwiched between them is a photoconductive film. For the technical buffs, the photoconductive material is officially named as cadmium-selenium which has been doped with tellurium-so there! This photoconductive film makes permanent contact between the contact electrode and the resistive film. A disc with a slit in it is attached to the rotary shaft of the potentiometer and a light source provides illumination. As the shaft is rotated, so the slit of light moves along the photoconducting film causing it to "connect" the contact on the side of it, with the part of the resistive element directly opposite on the other side.



PRODUCTION LINES alan martin

New receivers

National Panasonic have recently introduced two new radio receivers designed to appeal particularly to s.w. listeners. They are the RF-2200, an eight-band portable priced at £134.95 and the RF-4800, a ten-band communications receiver costing £319.95.

The RF-2200 is a comprehensive portable radio, built for the enthusiastic DX'er or the traveller who wants to keep in touch with world news, wherever they may be. Frequencies from m.w. to f.m. are covered in eight bands, tuned by a two-speed tuning knob coupled to a band dial that has 10kHz divisions, and a crystal marker calibrated at 500kHz and 125kHz intervals.

Other features include a meter that combines battery check, crystal marker check and optimum tuning indicator. Power output via a 10cm loudspeaker is 3W, with separate bass and treble controls.

Measuring 318 \times 188 \times 100mm, the RF-2200 weighs 3.0kg.

The RF-4800 communications receiver is designed for the amateur's shack or for mobile use.

Keyboard switches

Erg is launching a unique push-button keyboard switch, the Erg-KEY RS5020.

The switches have two main features, first a contact bounce time of only 25µs. Rarely before has this speed been achieved in a mechanical switch.

Secondly, it has a very low profile; only 5 08mm above its mounting plane.

Extremely high reliability is achieved by using a unique, patented torsion bar technique. An operating life of 10 \times 10⁶ operations is expected over an operating temperature range of -40°C to +60°C.

Further information on price and availability from: Erg Industrial Corp. Ltd., Luton Road, Dunstable, Bedfordshire LU5 4LJ. Tel: 0582 62241. Its ten bands range from I.w. (145– 410kHz), m.w. (520–1610kHz) to s.w. split into seven bands including marine band and covering a range from 1.6-27.3MHz.

Tuned frequency is indicated by tuning scale for l.w./m.w. and s.w. up to 3.0MHz, and by a combination of

tuning scale and a large five-digit l.e.d. display for the s.w.2-s.w.7 bands. Independent calibration of these s.w. bands is by separate control, and tuning to optimum signal strength on all bands is indicated by a tuning meter.


A 3W internal amplifier with separate bass and treble controls drive either an internal or external loudspeaker, or can be connected to an external amplifier via the 'rec out' sockets.

Powered by dry batteries, 12V car battery or a.c. mains, the RF-4800 measures $482 \times 200 \times 354$ mm and weighs 8.0kg.

Further information from: National Panasonic (UK) Ltd., Whitby Road, Slough, Berks. Tel: 0753 34522.



The RF-2200 portable radio

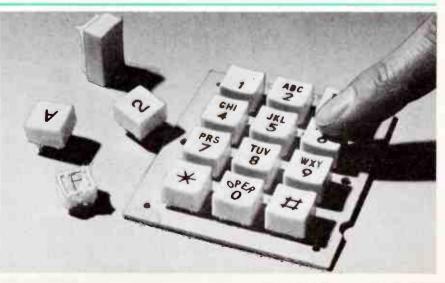

Practical Wireless, July 1978

World Radio History

Some original circuit ideas provided by our readers. These designs have not been proved by us, and we cannot therefore guarantee their effectiveness. They should at least provide a basis for experimentation.

Why not send us your idea? If it is published, you will receive payment according to its merits. Articles submitted should follow the usual style of PW in circuit diagrams and the use of abbreviations. Diagrams should be clearly drawn on separate sheets, not included in the text.

Each idea should be accompanied by a declaration that it is the original work of the person submitting it, and that it has not been accepted for publication elsewhere.

This circuit was developed to improve the stereo effect experienced when listening with stereo headphones. When listening with loudspeakers the stereo effect is produced by the interaction between the two speakers. With headphones, however, there is no such interaction and to obtain a realistic stereo image

The network of capacitors and inductors alters the amount of blend with frequency, the amount increas-

The phones used for the prototype were of an inexpensive type which could be taken apart easily and the components were mounted inside the headphone bodies. The 10mH chokes used were Repanco

ing at those frequencies which provide the main direc-


type CH4 and the capacitors were of the tantalum

variety. An extra wire was threaded through the headband to connect the right- and left-hand parts of the circuit. The original signal wires to the headsets need to be disconnected and the blend circuit

inserted. R1, C1, C2 and L1 are mounted inside the

left headphone and R2, C3 and L2 inside the righthand one. The circuit can be used with all stereo


Stereo Headphone blender

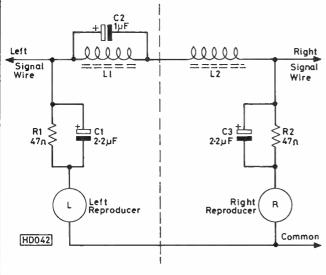

headphones of 4 to 8Ω nominal impedance. *R. N. Soar, Mexborough, S. Yorks.*

some form of blend circuit is needed.

tional information.

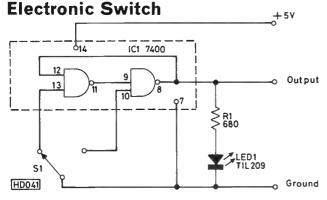

When testing JK flip-flops it is unsatisfactory to use an ordinary switch connected to the clock input. This electronic switch uses a 7400 i.c. in an 'anti-bounce' circuit, with an l.e.d. to indicate a high or low output.

Connect a +5V supply to pin 14 and 0V (Ground) to pin 7. A 6V battery could be used. The unit is a bistable which does not change state when the switch is momentarily open circuit. The circuit can be constructed simply using Veroboard.

> A. P. Cooper, Wimborne St. Giles, Dorset.

OCK P. J. WHEELER

Introduction

This is a design for an electronic lock which can replace the standard mechanical lock in many applications. It is impossible to "pick" as with a mechanical lock, and can have over 250,000 million different combinations, which will take all but the luckiest thief many hours to work through!

The lock can be used to disable a burglar alarm, taking the place of a mechanical key switch. Operation of the lock consists of depressing five keys on a keyboard in the correct sequence, the first key resetting the lock, and the other four keys providing the code.

The circuit can easily be extended with the addition of another i.c. and a few diodes to accept a nine digit code, which provides for extra security, although for most applications it is very tedious keying nine digits once the novelty has worn off, let alone trying to remember them! The operating code is programmed into the lock by the wiring between the keyboard and the p.c.b. and can easily be changed in the future.

The lock uses CMOS logic integrated circuits which have the advantage of negligible power consumption, thus continuous battery operation is quite feasible.

On the prototype, the quiescent current was about $1\mu A$, giving a battery life of well over 6 months. The output can be used to switch almost any solenoid, via a separate relay, if necessary, or can be used to disable a burglar alarm direct.

Operation

The operation of the lock is dependent on a decoded decimal counter type CD4017. From the truth table for this device given in Fig. 1, it can be seen that for each clock pulse, the counter switches to another output in sequence. The circuit for the lock is shown in Fig. 2.

Each time a key is depressed, one of the diodes D1-D5 conducts and C1 charges through R2. When the voltage on C1 reaches the threshold voltage of IC1d, the output will go low, charging C2 through R3 thus producing a pulse of about 50ms duration at the output of IC1c. C1 and R2 delay the production of the pulse to eliminate any effects due to contact bounce in the keyboard switches.

The first key to be depressed can be any one of the keys connected to the "reset keys" input. Irrespective of the position of the counter, none of the keys will be gated to R4, therefore it will be at logic 0. The pulse

produced by depressing the key is therefore gated through IClb to the reset input of IC3, which resets the counter. After a short delay due to R5 and C3, this pulse clocks the counter to output 1, enabling IC2c, which is an analogue switch. This sounds rather complex, but can be considered as an electronic relay.

When the control terminal is low, there is a very high resistance between the input and output (about $10^{10}\Omega$), and is effectively an open switch. However, when the control terminal is high, the resistance between the input and output is about 300 Ω , which is virtually a closed switch. Thus any voltage on pin 8 of IC2 will appear across R4 when the counter is at position 1. This effectively connects the first key of the code to R4, and if this key is depressed, pin 6 of IC1 will be at logic 1, and the pulse will be inhibited from the reset input of the counter by the action of the NOR gate IC1b. The clock pulse will still reach the counter and advance it to output 2. This enables the second key, and the process is repeated.

If the wrong key is depressed at any time, R4 will be at logic 0 and the counter will reset to its initial condition as described above. As the correct keys are

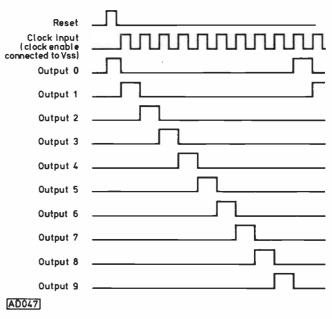


Fig. 1: Truth table for the CD4017 counter

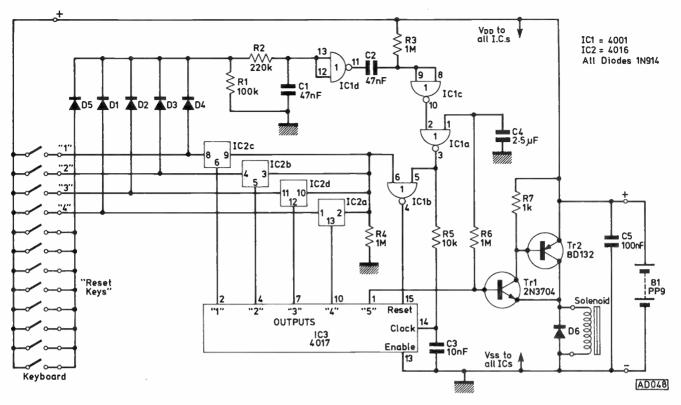


Fig. 2: Circuit diagram for the complete digital lock

depressed, the counter will increment to output 5, which will switch on the complementary output pair, Tr1 and Tr2. This energises the load, D6 providing protection against back e.m.f. from inductive loads. C4 also charges through R6, and after about 2^{1}_{2} seconds, the counter is reset to its initial condition via gate ICla. C5 provides suppression of spikes that can appear on the supply line and interfere with the logic activity.

Component Selection

Probably the most difficult item to obtain will be the calculator keyboard. This consists of 19 switches mounted on a p.c.b., which should be waterproof types, for use outdoors. These are dome type switches, operated by a thin piece of domed metal collapsing and making contact when pressure is applied.

This type of keyboard really needs a mounting frame and buttons, which are not readily available, however, the following method makes a presentable unit from this keyboard.

A small piece of white Fablon may be stuck over the entire front face of the unit, and Letraset numbers (or letters if you are hopeless at remembering numbers—the code can easily consist of an easily memorised word) put over the top of each dome.

The entire keyboard is then covered with a sheet of transparent self-adhesive plastic to protect the Letraset from rubbing off while in use. The keys can still be operated through the layers of plastic, and this makes the keyboard reasonably immune to cups of coffee being spilt over it!


Many types of calculator keyboard have the keys wired in a matrix arrangement, as opposed to one common rail and a lead to each switch. If this is the case, it will be necessary to remove the interconnecting tracks from the board, and rewire the unit. If a keyboard is available, with more than 12 keys, the remainder can be wired to the "reset keys" input on the p.c.b., thus effectively increasing the number of combinations available. Indeed as few as five keys could be used, with only one key connected to the "reset keys" input, the number of different combinations going down to a mere 3,125.

Solenoid selection can also be a problem. The lock will operate on any supply voltage between 4 and 15 volts, and the solenoid should be chosen to suit this.

The other components are non-critical: almost any silicon diodes can be used, and most silicon transistors will suffice for the output stage, although the current rating of Tr2 should be well in excess of the load current of the solenoid.

Construction

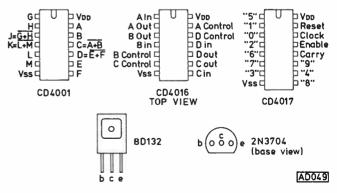Most of the components are mounted on a p.c.b., the track and component layout being shown in Figs. 3 and 4 respectively. There are four links needed on the board, and these should be inserted first, followed



Connections to the integrated circuits and transistors


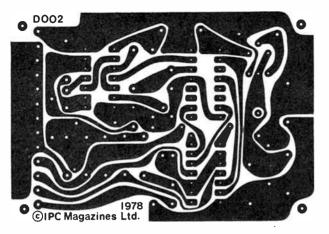


Fig. 3 (above): PCB viewed from the copper side. This board is available from the PW Reader's PCB Service Fig. 4 (above right): Component layout of the digital lock

by the other components, leaving the integrated circuits until last, as they are easily damaged by static. The use of sockets is advised unless you have a properly earthed soldering iron. Tr2 is mounted with its metal face in contact with the board, with a short 6BA nut and bolt securing the transistor to the board. It is a good idea to connect fairly long wires from the keyboard to the p.c.b. as the code, and consequently the wiring, may need to be changed in the future. The load should not be connected yet, but if a spare l.e.d. is available, this can be connected across the load pins on the board with a $1k\Omega$ series resistor for testing purposes.

★ components

Resistors	
R1 100kΩ	
R2 220kΩ	
R3 1MΩ	
R4 1MΩ	
R5 10kΩ	
R6 1MΩ	
R7 1kΩ	
All ‡W 5%	
Capacitors	
C1 47nF Ceramic	
C2 47nF Ceramic	
C3 10nF Ceramic	
C4 2·5µF Electrolytic (16V)	
C5 100nF Ceramic	
Semiconductors	
D1-D6 1N914, 1N4148	
Tr1 2N3704	
Tr2 BD132	
IC1 CD4001AE or MC14001CP	
IC2 CD4016AE or MC14016CP	
IC3 CD4017AE or MC14017CP	
Other Components	
2 off 14 pin DIL sockets	
1 off 16 pin DIL socket	
Keyboard (see text)	
Solenoid (see text)	
PP9 Battery and Connector	
Printed Circuit Board	
59	

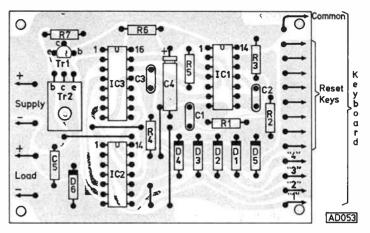

Testing

If the lock does not work, connect a voltmeter between pin 10 and IC1 and earth. Each time a key is pressed, the voltmeter should give a short positive "kick" and then return to zero. This should be checked for all the keys, and they must work every time if the lock is to be reliable.

If that does not identify the problem, connect a voltmeter across R4. The meter should read almost supply volts while the correct keys are pressed. When the lock is working, connect the supply direct to the board, and the load across the output. After further checking, the digital lock can be installed.

Possible Modifications

If a nine digit code is required, an extra CD4016 can be wired to switch 4 more keys to R4, controlled from outputs 5-8 of IC3. The output stage is taken from output 9 of IC3. Remember to include a diode from each extra key to R1, so that these keys produce a clocking pulse to operate the circuit.

If the lock is to be used with a burglar alarm, a relay can be used to disable the alarm, and the output stage can be made to stay on until another key is pressed by removing R6 and replacing C4 with a link.

However, the current drawn when the relay is on for long periods will probably be too high for economical battery operation, therefore the lock could draw its supply from a mains operated power supply, or from the burglar alarm itself.

If the load is to be switched on for other periods the values of R6 and C4 can be altered, the time the load is on being approximately given by $T=R6 \times C4$. R6 can be increased up to about $10M\Omega$, but if an electrolytic capacitor is used for C4, R6 should not be increased above $4 \cdot 7M\Omega$, due to leakage current in the capacitor causing large timing errors. Care should be taken to prevent voltage spikes greater than 15V reaching the CMOS, since they can cause irreparable damage.

PLEASE MENTION PRACTICAL WIRELESS WHEN REPLYING TO ADVERTISEMENTS

Fallow-up to THE fibbles

Notes on the Jubilee Organ project

Although the Jubilee Organ has undoubtedly emerged as very popular, in the time which has elapsed since its final part was published in our January 1978 issue, certain points have arisen which could cause some confusion. In order to dispose of these details, the following notes are provided as a complete list of published corrections, along with suggested modifications.

General Constructional Corrections:

- (1) September 1977, p 353. Transistor BFY71 should read BCY71.
- (2) November 1977, p 509. The circuit diagram of the accompaniment section shows the base of Tr5 connected to the 12V positive rail. This connection should be broken, leaving the base of Tr5 connected to the free end of R44 (1M Ω) only. The p.c.b. provided via Reader's PCB Services is correct.


The end of R45, shown connected to the 12V positive rail, should be connected to the junction of R40 and C17. Again, the recommended p.c.b. is correct.

(3) The collated components list, September 1977 p 353, contains the information "3-off 33nF". This should read "3-off 3 3nF Polystyrene".

Operational and Setting-Up Instructions:

November 1977, p 506—in describing the interim keying tests, a mistake was made in the text. When the flying lead is connected to the +12V point (positive end of C8) the note is inhibited. It is when the lead is removed from this point that the note will sound, and it is under this condition that VR5 should be adjusted. Re-applying the 12V will terminate the tone according to the sustain setting of VR6. When S2 is open the tone burst will occur when the flying lead is removed from the 12V point. The same reversed logic would apply to testing the repeat percussion effect.

Our "Postscript" in the final part of the article (January 1978) gave details of a modification to enable major chords to be memorised, thereby introducing a continuous "vamp" facility. The fact that no drawings accompanied the text seems to have caused considerable confusion, so in order to illuminate the situation, the relevant diagram, showing the necessary switching, is now provided for reference.

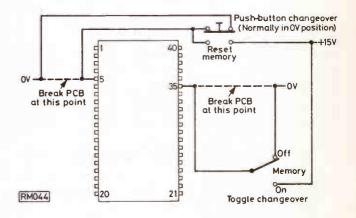

Circuit diagram of the Major Chords Memory modification

As published originally, the text could be misleading, and should have said that to enable the memory, pin 35 of IC13 should be connected to +15V, while pin 5 should normally be at 0V, but momentarily connected to +15V via the push-button changeover when the memory is to be reset. This will cancel any previously selected chord.

Suggested Modifications

Manfred Pfeifer of Bristol suggests in a letter to the author the following swell pedal modification:

"The volume is controlled by a foot operated pedal, linked via a l.d.r. To maintain a suitable range, the l.d.r. (ORP12) is connected in series with a 16μ F capacitor, and then wired in parallel with R92. A small bell transformer supplies 5V a.c. to provide a light source for the l.d.r."

Another constructor, Lorin Knight, of Letchworth, suggests some further improvements. He has included three extra stops (one for future use), with one used for continuous rhythm as already described, and one used as an additional percussion stop for the melody. Cl2 is shunted with a 47k Ω preset and an extra 4 $\cdot 7\mu$ F. The preset is adjusted so that the amplitude only drops 6-10dB after the percussive attack, giving rise to a gradually "flattening" envelope shape, similar to that of a piano.

INTRODUCTION TO LOGIC—continued from page 31

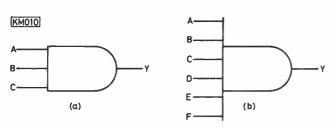


Fig. 5: AND gate symbols

Practical Gate Devices

Let's now take a look at some of the actual AND gates available in integrated circuits.

In 74-series TTL the most commonly met AND gate is likely to be the 7408, which contains four separate 2-input AND gates in one package. Other types are the 7411 which has three 3-input AND gates, and the 7421 which is a dual 4-input AND gate. The function and pin connections for these types are shown in Fig. 6.

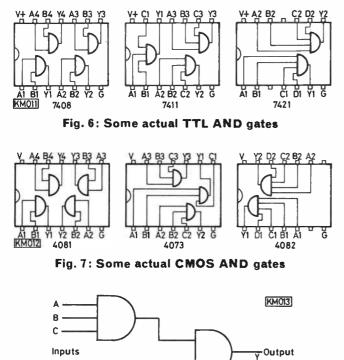



Fig. 8: Cascading AND gates to provide more inputs

The 4081 in the CMOS series provides the same logic functions as a 7408 but the pin layout is different. Other gates in the CMOS series are the 4073 triple 3-input AND gates and the 4082 which contains two 4-input AND gates. Fig. 7 shows the pin connections and functions of these CMOS devices.

If we wanted a 6-input AND gate this could be made up by using two 3-input gates feeding into a 2-input gate to form a cascaded tree of gates as shown in Fig. 8. This principle could be extended to give any number of inputs if desired.

Next month we shall look at some of the other types of gate circuit used in logic systems.

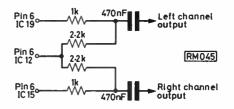He also suggests modification of the DIN output socket, to introduce stereo effect. This gives drums to the left, melody centre, and accompaniment to the right.



Circuit diagram for Stereo Effect modification

Several readers have requested detailed cutting and drilling instructions for alternative keyboard versions. It was felt that in cases where the calculator keyboard was not opted for, general details for other types would necessitate a proliferation of differing instructions. Aside from this confusion, the conventional keyboard, for which we had approximate constructional details, appeared to be in limited supply (very limited supply as it eventually proved), and so we decided to confine our constructional notes to the details for the calculator version in general, and the initial measurements for the front and back panels. This was considered enough to cover the bare essentials, and the majority of constructors seem to have come to terms with this problem.



Bovington Tank Battle Game, June, page 38

The coil winding details for this project were inadvertently omitted from the components list. L1 80 turns 40 s.w.g. enam. copper wire on 6mm dia. former with dust core. L2 3 turns 22 s.w.g. tinned copper wire 6mm dia. x 8mm long air-spaced, tapped ${}^{3}_{4}$ turn from top.

Tr1 should be a BC108.

C24 should be connected to the tap on L2, not as shown in the circuit diagram (the printed circuit board is correct).

A small section of track is missing from the p.c.b. copper track pattern shown in the article. To overcome this a thin wire link should be used to connect together the pads for the +ve ends of C12 and C13. Solder this link onto the copper track side.

D3 to D12 are type 1N4148.

R32 is selected according to type of indicator used. (Shown in Fig. 7.)

D

F

J-DeCnology

£,



In recent years "fuzz boxes" have been rife on the pop scene particularly with regard to guitars. The idea seems to be that one uses a fuzz box to make a guitar not sound like a guitar!

This month's μ DeCnology circuit shows a very simple circuit for obtaining a fuzz effect. It is very sensitive and can be used to fuzz sound direct from a microphone or even a record player.

The commonest approach to fuzzing involves taking a luckless sine wave, chopping the tops or peaks off (known by the purists as "squaring"), and then amplifying the resultant noise with an ordinary audio amplifier.

We are cheating a little with our circuit by simply using the very high gain of the 741 op. amp. with no


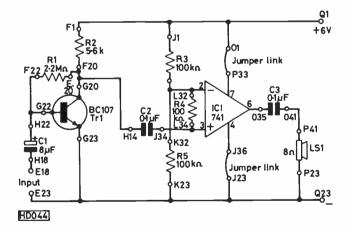



Fig. 1: Main circuit diagram including preamplifier

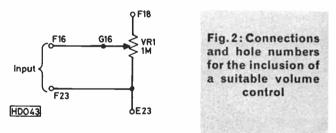negative feedback. To increase the sensitivity still further, an extra stage of preamplification has been added by using a BC107 transistor. This preamp stage is also very simple, being reduced to a bare minimum of components.



When you have "plugged" the components into your μ DeC by their own leads (see Fig. 1) you should connect 6V to holes' Q1(+) Q23(-). The input is connected to holes F22 and E23. On test it was found that almost any microphone would work well and give a horrendously fuzzed voice output. Those tried included a cheap crystal insert, a commercial crystal microphone, a magnetic type (some 300 Ω impedance), and a small loudspeaker. Even small earpieces were tried and found to work.

Six volts proved ample for good sensitivity. Increasing this to 12V made the circuit super sensitive and if this is done there is a good chance of positive feedback which will make the circuit oscillate. In a permanent form, one could transfer the components from μ DeC to Blob Board and then put the Blob Board in a metal case thus screening the circuitry from both the output loudspeaker and the microphone. This should prevent instability and make a useful fuzz box which could be used in many applications. For example, as a party game or at a disco, records could be announced with fuzz in followed by the record. Alternatively, the participants might be

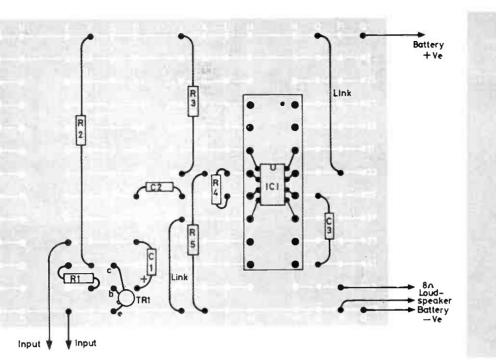

required to guess what was being said (not easy when this unit is set for full fuzz).

The unit could be made completely portable with its own 12V battery. With 12V applied, the total current drawn by the circuit was barely 1mA quiescent. With speech going through this rose to average 2mA max so battery life would be very long.

If 12V is used it would be prudent to use a variable potentiometer, the input would then be connected between the slider of the pot and μ DeC hole E23. (see Fig. 2).

The input and output blocking capacitors gave a degree of control of the sharpness of the sound—one hesitates to use the word "tone". The value of Cl specified gave reasonable results. Increasing it (more microfarads) gave more bass and less treble. Reducing it (down to 0.1μ F) increased the top or treble con-

★ components

Resistors	
R1 2.2M12	
R2 5-6kΩ	
R3 100kΩ	
R4 100kΩ	
R5 100kΩ	
Capacitors	
C1 8µF/12V electrolytic	
C2 0-1/1F	
C3 0-1//F	
Semiconductors	
IC1 741 Op amp	
Tr1 BC107	
Miscellaneous	
LS1 8Ω loudspeaker	
One µDeC A	
One µDeC DIL holder	
µDeC jumper leads	
6V or 12V battery	

siderably. Similarly one can try different values for C3. One could even switch in two or three values at C3 to give a built in control over the "bassiness" of the fuzz.

Fig. 3: The μDeC Layout of the "Super-Sensitive Fuzz"

Just one word of warning before any fuzz fanatics start connecting the circuit up to external equipment. It would be dangerous to connect this circuit to cheap record players which might be live to the mains.

If you do connect it to a tape recorder, or amplifier (or whatever) it would be sensible to include $0 \cdot 1\mu F$ (400V working) capacitors in all leads to and from the equipment.

The circuit has been tried with a battery tape recorder and worked well and with a hi-fi system. A radio signal from a simple diode tuner also gave acceptable results. An amusing exercise is to tune in to Radio 4 and listen to the news with the fuzz circuit connected: and then try to guess what the news was!

The component values are standard and easily available from advertisers in *Practical Wireless*. While most are uncritical it is suggested that they be adhered to until the circuit is made to work. Almost any transistor will work and those tried include the BC108 and BC109, 2N2926—but be careful that the lead connections are correctly identified. The BC107/8/9 are all the same and so no problems should be encountered.

We are pleased to announce the reintroduction of the publishers subscription service for *Practical Wireless*. The annual cost to either UK or overseas addresses is £10.60. Application may be made to: *Practical Wireless*, *Subscriptions Department*, *Oakfield House*, *Perrymount Road*, *Haywards Heath*, *Sussex RH16 3DH*. *Remittances should be made payable to IPC Services*.

				CONTRACTOR AND
BISTORS:BC118 19p BC184L AC107 38p BC119 28p BC184L AC117 32p BC125 18p BC184L AC117 32p BC125 18p BC184L AC126 32p BC125 18p BC184 AC126 32p BC126 19p BC187 AC127 32p BC132 29p BC204 1 AC127 32p BC134 19p BC204 1	14 p* BD137 48p BF338 37 15 p* BD138 48p BF337 35 23 p BD139 44p BF458 58 26 p BD140 58 p BF459 52 16 p* BD145 75p BF596 22 p 16 p* BD163 85p BF597 22 p	5p OC77 88p 7453 21p 10+ 21p 21p <td>100mW + - 5% 3V-33V 10p each: 10/85p 1W 3V3-200V 15p each: 10/£1·75 4</td> <td>RECISION POLY- ARBONATE CAPACITORS Mi High Stability—extremely Low Leakage 40V A.C. RANGE alue Dimen- Price</td>	100mW + - 5% 3V-33V 10p each: 10/85p 1W 3V3-200V 15p each: 10/£1·75 4	RECISION POLY- ARBONATE CAPACITORS Mi High Stability—extremely Low Leakage 40V A.C. RANGE alue Dimen- Price
AC141 22p1BC133 19p1BC212L 1 AC141K 44p1BC137 19p1BC212L A1 AC142 29p1BC138 23p1BC213 L AC142 44p1BC138 23p1BC213L 1 AC153K 34p1BC140 33p1BC214L 1 AC153K 34p1BC140 33p1BC214B 1 AC176 35p1BC143 34p1BC214B 1 AC176 35p1BC143 34p1BC214B 1 AC176 13p1BC143 34p1BC214B 1 AC176 13p1BC143 34p1BC214B 1 AC176 13p1BC143 34p1BC214B 1 AC176 35p1BC143 34p1BC14B 1 AC176 35p1BC143 34p1BC14B 1 AC176 35p1BC14B 1 AC178 34p1BC14B 1 AC178 34p1BC14B 1 AC178 34p1BC14B 1	3p* BD187 59p BFT43 40 4p* BD232 85p* BFW10 65 3p* BD234 58p BFW10 65 4p* BD233 £2:35 BFX11 75 5p* BDX18 £2:35 BFX85 29	DP TIP20 S4p 7475 S2p 18 Pin DIL: 9* TIP31A S5p 7476 43p 1+ 24p 5p TIP32A S7p 7482 84p 10+ 23p 10* TIP32A S7p 7482 84p 10+ 23p 10* TIP32A S1p 7490 64p 50+ 19p 1 10* TIP32A S4p 7490 64p 50+ 19p 1 10* TIP32A S4p 7490 64p 10+ 17p 10* TIP41A 74p 7493 S4p 10+ 17p 10* TIP3055<£1.15	SKELETON PRESETS: (/ (Vertical or Horizontal) 00 000 ohm to 1M—Tp0* each: 50 for 0 0 S3*6*. 100 for £5*69* 0 RESISTORS—High stability. 0 low noise carbon film 5% tW 0	4F) sions (mm) each L D
AC179 44p BC147A 11p ⁺ BC238 1 AC187 32p BC147B 12p ⁺ BC239 1 AC187K 42p BC148 10p ⁺ BC252C 2 AC188 37p BC148 11p ⁺ BC253C 2 AC188K 42p BC149 10p ⁺ BC253A 2 AC183K 42p BC149 11p ⁺ BC258A 2 AC183K 41p BC149E 11p ⁺ BC258A 2 AC194K 41p BC149C 12p ⁺ BC281A 3 AC194K 41p ⁺ BC149C 12p ⁺ BC149C 12p ⁺ BC284A 3 AC194K 41p ⁺ BC149C 12p ⁺	Top BDY11 85p BFx87 311 8p BDY20 g1-85 BFx88 28 10* BF115 42p BFV50 22 20* BF120 75p BFV51 22 20* BF120 75p BFV52 22 25p BF121 34p BFV53 34 25p BF123 34p BFV72 21 25p BF123 34p BFV77 21 30* BF123 34p BFV77 21	P TISBO 25p ⁷ 74141 940 BA145 18p D TISBO 25p ⁷ 74141 940 BA148 18p D TISB1 28p ⁷ 74154 £1.75 BA155 18p D 2N705 48p 74155 £1.16 BA155 18p D 2N2646 75p 74150 £1.76 BAX13 8p D 2N2646 1.28 74190 £1.76 BAX13 8p D 2N2904 A36p 74190 £1.20 BB1108 54p D 2N2005 A36p SN76001N £1.57° BR100 54p D 2N2005 22p SN76001N £1.57° BR100 24p	only—from 2:20 to 2:2M0. All at 2p° each, 15p° for 10 of any one value, 55p° for 100 of any one value, SPECIAL PACK:10 of each value 2:20 & 2:2M0 (730 resistors) & 8-56*.	-47 33 19 £2.48 -5 33 19 £2.24 -88 50.8 22 £2.48 -0 50.8 22 £2.48 -5 50.8 25.4 £3.14 -0 50.8 25.4 £3.74 3V D.C. RANGE
AD142 81 pBC154 15p* aC267 AD143 43pBC157 12p* BC267C AD149 45pBC157A 13p* BC268A AD161 55pBC1558 12p* BC268A AD162 55pBC158B 13p* BC268C AF114 32pBC159 12p* BC301 AF115 32pBC159E 13p* BC301 AF116 32pBC159C 14p* BC304 AF116 32pBC159C 14p* BC304 AF116 32pBC159C 14p* BC304	430 BF152 320 BF153 340 BF054 340 BF054 340 BF054 340 BF158 170 BRV39 401 140 BF158 170 BRV39 401 340 BF158 340 340 340 340 340 340 340 340 340 340 340 340 340 85.76 333 340 BF164 250 BS.X70 233 340 BF165 350 BS165 357 333 B5165 350 BS165 357 333 340 BF165 350 BS173 343 BS165 357 333 340 B5165 350 BS173 343 340 BS165 350 BS173 343 340 BS165 350 BS173 343 340 BS165 350 BS173 343 340 BS173 340 BS173 340 BS173 340 BS173 340 BS173 340 BS173	10 2N2907A 55p 5N75013N £1.70 BV127 16p 10 2N29260 17p* SN75013N £1.70 BV127 16p 44 2N29260 17p* SN75013N £1.55 OA41 35p 10 2N29262 17p* SN75023N £1.55 OA41 15p 10 2N3053 42p SN75023N £1.55 OA81 15p 10 2N3054 57p SN75023N £2.46 OA80 7p 10 2N3054 57p SN75226DN £1.52 OA80 7p 10 2N3054 17p* SN75626 £1.120 OA80 5p 10 2N3052 17p* SN75650 £1.120 OA80 5p 10 2N3052 17p* SN75650 £1.120 OA80 5p 10 2N3052 17p* SN75650 £1.120 OA80 5p 0 A820 5p 10 2N3052 17p* SN75650 £1.120 OA80 5p 0 A820	5% Tol. V 2°5W (0°22R-22R)14p: 5W 0 10R-12K)16p: 10W (0°47R-10K) -18p. TANTALUM BEAD 1	
AF126 400 BC10/B 140 BC3078 13 AF121 330 BC168A 140 BC308A 14 AF124 340 BC168B 140 BC308A 14 AF125 340 BC169B 240 BC309 17 AF126 340 BC169C 230 BC33 4 AF127 390 BC170 140 BC328 1 AF138 450 BC1708 150 BC337 15 AF178 440 BC170C 160 BC337 15 AF178 440 BC170C 160 BC338 1 AF178 450 BC170 140 BC338 1 AF179 450 BC170 140 BC338 1	50° 8F173 27p 85752 55 60° 8F177 34p 8T106 £1.5 70° 8F178 42p 8U105 £1.6 20° 8F179 33p 8U108 £2.2 82p 8F180 33p 8U108 £2.3 82p 8F180 33p 8U204 £1.5 70° 8F181 33p 8U204 £2.3	19 2N3704 17p° TAA253 £1:13° TIL209 22p - 19 2N3705 17p° TAA253 £1:16° (0-125° Led) 3 19 2N3705 17p° TAA5506 55p 10 2N3707 17p° TAA570 £2:02 TIL211 44p 1 20 2N3709 17p° TAA611B £2:75° (0-125° Led) 2 10 2N3319 42p TBA5400 £2:20° Green) 4 12 2S321 75p TBA5400 £2:35° 1N4001 A50V - 19 RCA40530 95p TBA5500 £3:35° 1N4001 A50V - 19 RCA4054 73p — TBA5400 £3:35° 1N4001 A50V - 19 RCA4054 73p — TBA5400 £3:35° 1N4001 A50V - 19 RCA40550 17p TBA5500 £3:35° 1N4001 A50V - 10 RCA40550 17p (10 20 20 20 20 20 20 20 20 20 20 20 20 20	-110*2:2#F(35V-12p*: 3:3#F) 35V-13p*: 4:7#F(35V-15p*; 3:8#F(35V-17p*: 10#F(25V- 10#F(35V-21p*; 15#F(30V) 10#F(35V) 10#F(35V-17p*; 100#F(33V) 11 121p*: 88#F(3V-17p*; 100#F(3V) 221p* 5 ELECTROLYTICS: 5 5 5 5 5 5 5 5 5 5 5 5 5 5	7 £4.00 £2.72 £2.24 8 £4.88 £3.38 £2.06 0 £6.94 £4.68 £3.38 £2.06 5 £9.92 £5.40 £4.66 2 £13.32 £9.08 £8.00 md s.s.e. for free detailed lists
AF181 75 BC1718 15 BC371 2 AF185 35 BC172 12 BC374 18 AF239 45 BC172 12 BC470 BC480 AF239 45 BC172 12 BC48 14 AF239 45 BC172C 16 BC460 1 AF279 86 BC172C 16 BC470 12 AU113 £1-34 BC173 15 BC58A 13 BC107 12 BC177A 19 BC538 13 BC107 14 BC177A 19 BC538 14 BC138 14 BC138 14 BC138 14	21p BF185 22p C1128 9p BP185 B2p GET872 15p 32p BF194 12p GET881 15p 33p BF194 12p GET882 15p 33p BF194 12p GET882 15p 32p BF195 12p ME000 24p 33p BF194 13p GET800 24p 33p BF195 12p ME000 24p 33p BF195 15p ME300 25p 34p BF197 15p MJ2955 £1.40 35p BF193 15p MJ2955 £1.40	TBA641 (B11) TA 100V TA 100V p INTE- TBA641 (B11) TA 100V TA 100V p INTE- TBA720Q £2:60* TN4003 7p (p GRATED TBA750 £1:91* TA 200V Ta 200V p CIRCUITS: TBA810A 5£1:32* TA 400V Ta 400V p 7400 TP TBA810A 5£1:42* TA 600V Ta 600V p 7401 TP TCA270C £2:80* TA 800V Sp 7402 p 7403 TP INES55 61:9* TA 800V Sp 7402 p 7404 TP INES55 61:9* TA 800V Sp 7402	And to flow and the second se	additional stock items, plugs d sockets, lusss, discs, poly- ter capacitors, bridge rectifiers ghvoltage electrolytics. Whole- le price lists available to bona le companies. ADD 8% VAT D ALL ITEMS EXCEPT THOSE ARKED WITH * WHICH ARE §%. PLEASE ADD 25 Post
BC108 12p BC178A 21p BCY70 1 BC108A 14p BC178B 21p BCY71 2 BC108B 14p BC178B 21p BCY71 2 BC108C 14p BC179C 21p BCY71 2 BC108C 14p BC179C 21p BCY72 1 BC109C 14p BC179C 24p BC115 6 BC109C 14p BC1272 12p BD116 6 12p 12p <td< td=""><td>18p BF200 38p ° MJE520 S44 23D BF224J 25p ° MJE521 907 18p BF224J 35p ° MJE205 £14 19 BF244 20p ° MJE3000 £21 10 pl BF241 18p ° MJE3050 £21 10 pl BF241 18p ° MJE3055 £14 10 pl BF241 18p ° MPU131 35p 87p BF255 27p ° OC41 75p 87p BF257 48p ° CC42 75p</td><td>PP 7405 24p 741 (8 pin DIL) 38p° 1 A 1000∨ PP 7409 25p 758 8 5p 1N4009 7p PP 7410 28p 784 £1 05 1N4148 6p PP 7410 28p 784 £1 05 1N4148 6p 10 7413 40p 1N5401 16p 3 1N5402 17p 10 7413 40p 1N5402 17p 1N5406 20p 10 7410 20p SOCKETS: 1N5408 20p 1N5408 20p 10 7430 20p SOCKETS: 1N5408 7p 1N5408 20p</td><td>27p*: 580, 1000-35p*: 1500, an 2200-43p*. at 1500, at 15</td><td>d Packing to all orders. Export d cost of air/sea mail. MARCO TRADING (Dept. W7) The Old School, Edstaston, wem, Shropshire SY4 SRJ</td></td<>	18p BF200 38p ° MJE520 S44 23D BF224J 25p ° MJE521 907 18p BF224J 35p ° MJE205 £14 19 BF244 20p ° MJE3000 £21 10 pl BF241 18p ° MJE3050 £21 10 pl BF241 18p ° MJE3055 £14 10 pl BF241 18p ° MPU131 35p 87p BF255 27p ° OC41 75p 87p BF257 48p ° CC42 75p	PP 7405 24p 741 (8 pin DIL) 38p° 1 A 1000∨ PP 7409 25p 758 8 5p 1N4009 7p PP 7410 28p 784 £1 05 1N4148 6p PP 7410 28p 784 £1 05 1N4148 6p 10 7413 40p 1N5401 16p 3 1N5402 17p 10 7413 40p 1N5402 17p 1N5406 20p 10 7410 20p SOCKETS: 1N5408 20p 1N5408 20p 10 7430 20p SOCKETS: 1N5408 7p 1N5408 20p	27p*: 580, 1000-35p*: 1500, an 2200-43p*. at 1500, at 15	d Packing to all orders. Export d cost of air/sea mail. MARCO TRADING (Dept. W7) The Old School, Edstaston, wem, Shropshire SY4 SRJ
BC114 15p BC183B 13p* BD132 4 BC115 18p BC183L 13p* BD133 5	41p BF259 44p OC45 40p 54p BF262 40p* OC70 40p	p) 7440 200 10+ 190 1544 7p 10 7442 300 50+ 170 15920 7p 10 7445 £1 20 100+ 150 15921 100	68 100-27p* 150 220-35p*	i: Whixall 464 (STD: 094-872) props. Minicost Trading Ltd.)

You'll learn a lot from the free Heathkit catalogue.









by Eric Dowdeswell G4AR

Some readers of this column may have become a little irritated at the frequent mention in the last few months, without explanation, of sunspot activity coupled with the increased action on the 10m (28MHz) band. So, let's try to account for this interesting phenomenon.

Sunspots and flares involve the release of vast quantities of energy from the surface of the sun which, radiating outwards, reach and ionise the outer layers of our atmosphere. Given sufficient ionisation these layers can then act as reflectors for radio signals that reach them from Earth. The principal layer that concerns us is the outer E layer.

With little or no ionisation, signals on the 10 and 15m bands tend to penetrate the E layer and be lost in space. As Solar Event on page 65 of the May issue of PW showed clearly, sunspots are increasing rapidly in number and in activity so that signals at the higher frequencies are now being returned to earth. In many cases the signal is then reflected up to the E layer, bounced down again, to give multi-hop worldwide paths.

Band I TV signals around 45MHz are already being received in southern Africa mainly due to a form of transequatorial propagation (TE). A similar northsouth path can often be noticed on the 10 and 15m bands when ZS and ZE stations can be heard and worked from Europe to the exclusion of signals from other directions.

The effects of the daily, monthly and annual changes in propagation conditions may be fairly well known to the SWL but there is an eleven-year cycle of change that will not have been experienced by those taking up the hobby in fairly recent times. When the number of sunspots occurring is plotted against time, in years, it is found that the peaks repeat at roughly eleven year intervals, although the amplitude of the peaks can vary considerably.

We are now getting out of the sunspot doldrums of the early 1970s, when minimum sunspot activity favoured the lower frequencies, and into a period when working worldwide DX with a bit of wet string for an aerial will be no more difficult than making a local telephone call! With heavy ionisation the F layer can remain an effective reflector long after local sunset,

Remember that a half-wave aerial is only about 16ft or so on 10m, so a simple beam is not impossible in the tightest situation. With electrical loading the "wingspan" can be reduced even further. More importantly, a beam gives discrimination against signals off the back of the beam, which can be very worthwhile in the heavy QRM that is bound to accompany the increased use of the 10m band.

Newcomers

Tom Hillier of Paignton was staggered at the help and information he received from readers following his appeal in this column for info on the B40 receiver. "Real service here and a grand lot of chaps. I replied to each one by return post." So, Tom, I hope that you soon get settled down on the bands and start to send logs in on the rare DX.

From Wilmslow, Cheshire, Steve Turner BRS37620 sends his first letter although he has been reading PW for some time. He has a surplus R208 and inverted "L" aerial but confesses to occasionally listening on his dad's Trio 9R59DS. Bill Land of Cheltenham is a newcomer to this column but not entirely to radio. He is BRS34761 and at 73 can't get around too well nowadays. He has an Eddystone 750 and Trio 9R59DS that he'd like to swap for an S27, with adjustments, so if you can help, write to Bill at 7 Wellbrook Road, Bishop's Cleeve, Cheltenham.

Readers' News

A determined character is our **Brian Smith** of Barry, Glam. as he intends to enrol for an RAE course in September and take the exam in December! With the best will in the world OM I think that this is unwise. As I have said before, the RAE and expenses mean a lot of money and one must be reasonably sure of passing before taking the exams. Next May would be much more realistic. Brian's present project is the DXer's audio filter in the May PW.

Nice to hear from Brian Hughes in Worcester, again. His FRG7 has been patrolling the bands fed from dipoles and a 66ft wire. He found 10 and 15m very good listening all through March. G4GOF conceals the identity of Jess Luxton (Bergheim, Battery Hill, Fairlight Cove, Hastings) who writes to express his gratitude to all those who helped him to pass his Morse test. He'd be glad to QSL any reports on his 80m c.w., enclosing an s.a.e., to his QTH given here. Another FRG7 enthusiast, John Whiting of Fareham, Hants, has a 135ft wire and is now BRS40086. Having told him that ZA is just about the rarest thing going he reports hearing ZA6KB on 14285kHz s.s.b! I hope you're right OM! Bob Bell in Blyth, Northumberland has actually been digging around inside his FRG7 putting one or two things right! Bang goes the guarantee!

David Greenhalgh BRS39965 (Poynton, Cheshire) and John Hodgson (Morpeth, Northumberland) both ask for guidance on the "rare" calls that I am always asking for in logs. Well, I do have a list and I'll publish it next month. In the meantime John seems to be doing pretty well already on all bands from 160 to 10m. He was not caught by AP1RIL however! Chaos! reports Peter Cockerell (Leigh-on-Sea, Essex) and other readers on the Clipperton Island DXpedition. Very rare indeed, so hardly surprising. Once the frequency is known it is a good idea to listen an hour or so before conditions peak for our area and thus avoid some of the QRM.

Club News

Blackwood & District ARS GW6GW is pleased to see the extra pages being allocated to "On the Air". Dates to note:— June 9th Gwent TV Group talk and demo, June 16th TVI by GW3NWS and June 23rd visit to BBC TV Cardiff. RAE class every week with meetings at Oakland Community College, near Blackwood, Gwent, 1930 on Fridays.

Don't forget the Stevenage & District ARS first and third Thursday 2000 at Hawker Siddeley Dynamics staff canteen. Code classes start half an hour earlier, with RAE course at local college. June 15th sees G4DDX talking on DF receivers.

Log Extracts (s.s.b.)

P. Cockerell:— 20m C5ABC (Gambia) CE0AE C02GS FP0BC HC1BU HP1A HL9KL KG6SW PY0FN TR8GM ZL4LR/A (Campbell Is).

J. Hodgson:— 80m EA8ER EP2TY 40m VK7AZ 20m TR8AF VP2LLL VP8PU ZD8RP.

J. Whiting:— 20m HC2HM J3OH (Grenada) M1D TR8ACQ ZK2AT 10m VP8PM ZF1JJ.

B. Hughes:— 20m J3AH VP2KT WD9FCC/VQ9 5U7AG 15m EP2SI JA8GLP ZBC2J 10m A2CBW KZ5JW 5T5KJ.

S. Turner:— 20m JT1BK JY9VK.

B. Smith:— 80m HC1WAS HK3BQM HV3SJ 20m TR8GM.

Reports on the various bands are welcome and should be sent direct, by the 15th of the month, to:-

AMATEUR BANDS Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashtead, Surrey KT21 2TW. Logs by bands, each in alphabetical order.

MEDIUM and SW BANDS Charles Molloy G8BUS, 132 Segars Lane, Southport, PR8 3JG. Reports for both bands **must** be kept separate.

VHF BANDS Ron Ham BRS15744, Faraday, Greyfriars, Storrington, Sussex RH20 4HE.



MEDIUM WAVE DX by Charles Molloy G8BUS

Every now and again a well established Radio Amateur on reading Practical Wireless comes across Medium Wave DXing and he decides to "have a go" on this band as a diversion from his normal activities. The results if reported to this column are invariably interesting and the report from Ken Hurrell G3NBC of Sturminster in Dorset is no exception. Using a Marconi Gannet marine receiver along with an 80ft horizontal wire aerial about 15ft above the ground he pulled in 9 Canadian and 22 US stations between 2300 and 0300GMT during the past winter months. Highlights of the log are WSM Nashville Tennessee on 650kHz, CBF Montreal 690, WLW Cincinnati 700, CBL Toronto 740, WBBM Chicago 780, Schenectady NY 810, KMOX St Louis 1120, WOAI San Antonio Texas on 1200. Ken remarks that in some cases the time of reception depended on the closing down of European stations. There were also a number of stations which could not be identified due to fading, QRM, etc-the real DX! With both WSM and WOAI reception was such that it was possible to listen to a complete programme and both stations verified with a QSL card. During DX conditions CJYQ, WINS, and WABC were listened to as regular programmes.

The interesting feature of this log is the fact that several rather difficult stations were heard using a long-wire aerial, due no doubt to picking the right time and skill in handling the receiver. Medium wave DXers invariably use a loop aerial to take advantage of its directional effect which reduces QRM and static. During DX conditions, i.e. when the path is open, some strong signals can be heard from North America, strong enough occasionally to be heard on a transistor portable using its internal aerial. The following night there may not be a North American to be heard with any type of receiver or aerial. The experienced DXer is aware of this, but the newcomer is often dis-couraged if he cannot hear DX on a first or second attempt. Patience and persistence are the qualities required in a medium wave DXer. Even at this time of year you can hear North America during DX conditions. Try it during the hour before sunrise; you may be surprised.

Loops and Wavetraps

A letter from E. G. Oxtoby refers to the PW Medium Wave Loop Aerial Wavetrap, which confuses two quite different pieces of equipment. A medium wave loop is a directional aerial and is used to pick up DX instead of an ordinary aerial. A wavetrap is not an aerial. It is a device, comprising a parallel tuned circuit, which is inserted between aerial and receiver to suppress or reduce the strength of a local station. Wavetraps are seldom used these days as receivers are now more selective than they used to be, but one could be of Proto-Board Now circuit designing is as easy as pushing a lead into a hole.

No soldering. No de-soldering. No heat-spoilt components. No manual labour. No wasted time.

With a Proto-Board you can hook your circuit together as quickly as you can think.

No. of

And you can have second thoughts, and third thoughts, equally quick and easy, till you've got the whole thing right.

IC Capacity

Then you can solder up if you want to, but most engineers don't because the Proto-Board push-fit connectors are highly reliable.

Postage

And everything is visible; come back next week and you 'read' the circuit immediately.

Contact terminals are arranged in sets of five, each connected across the back, and in the Model 203A illustrated you get 1770 contacts, in six rows of 59 x 5. plus four double power rails, each with 100 contacts connected lengthwise and two horizontal power units with 40 contacts each. Many other models: see chart. Proto-Board breadboards will accept transistors, ICs, LSI packages, resistors, capacitors, LEDs, trimmers. relays etc.; most plug straight in.

Try one. You'll wonder how you ever فالقرب والقادية أواويهم

Solderless Tie-points	(14-pin DIP's)	Unit Price	& Package	VAT	Total Price	Other features
630	6	£ 9.20	£1.00	£0.82	£11.01	Kit–10 minute assembly
760	10	11.80	1.00	1.02		Kit-with larger capacity
940	10	17.20	1.25	1.48		8 distribution buses, higher capacity
1240	12	22.95	1.25	1.94		Large capacity, moderate price
2250	24	34.45	1.50	2.88		Even larger capacity; only 1.73 pence per tie-point
3060	32	45.95	1.50	3.80		Largest capacity; lowest price per tie-point
2250	24	55.15	1.50	4.53		Built-in 1%-regulated 5V, 1 A low ripple power supply
2250	24	74.10	1.50	6.10		As above plus separate ½ Amp + 15V and - 15V internally adjustable regulated supplies
	Tie-points 630 760 940 1240 2250 3060 2250	Soldertess (14-pin DIP's) 630 6 760 10 940 10 1240 12 2250 24 3060 32 2250 24	Solderless Tie-points (14-pin DIP's) Unit Price 630 6 £ 9.20 760 10 11.80 940 10 17.20 1240 12 22.95 2250 24 34.45 3060 32 45.95 2250 24 55.15	Solderless Tie-points (14-pin DIP's) Unit Price & Package 630 6 £ 9.20 £1.00 760 10 11.80 1.00 940 10 17.20 1.25 1240 12 22.95 1.25 2250 24 34.45 1.50 3060 32 45.95 1.50 2250 24 55.15 1.50	Solderiess Tie-points (14-pin DIP's) Unit Price 8 Package VAT 630 6 £ 9.20 £1.00 £0.82 760 10 11.80 1.00 1.02 940 10 17.20 1.25 1.48 1240 12 22.95 1.25 1.94 2250 24 34.45 1.50 2.88 3060 32 45.95 1.50 3.80 2250 24 55.15 1.50 4.53	Solderless Tie-points (14-pin DIP's) Unit Price & Package VAT Total Price 630 6 £ 9.20 £1.00 £0.82 £11.01 760 10 11.80 1.00 1.02 13.82 940 10 17.20 1.25 1.48 19.93 1240 12 22.95 1.25 1.94 26.14 2250 24 34.45 1.50 2.88 38.83 3060 32 45.95 1.50 3.80 51.25 2250 24 55.15 1.50 4.53 61.18

Ine

Proto-Board

How to order. Telephone 01-890 0782 and give us your Access, Barclaycard or American Express number, and your order will be in the post that night. Or, write your order, enclosing cheque, postal order, or stating credit card number and expiry date. (Don't post the card!). Alternatively, ask for our latest catalogue, showing all CSC products for the engineer and the home hobbyist. (Prices are for UK only. For Europe add 10%, outside Europe add 124%) to total prices.)

CONTINENTAL SPECIALTIES CORPORATION (UK) LTD SPUR ROAD NORTH FELTHAM TRADING ESTATE FELTHAM MIDDLESEX TWI 40TJ P TELEPHONE 01-890 0782 TELEX 881 3669



REGISTERED IN LONDON 303780 VAT No. 224470 7471 TRADE MARK APPLIED FOR CSC (UK) LTD 1977 DEALER ENQUIRIES WELCOME

MK14-the only low-cost keyboard-addressable microcomputer!

The new Science of Cambridge MK14 Microcomputer kit

The MK14 National Semiconductor Scamp based Microcomputer Kit gives you the power and performance of a professional keyboard-addressable unit – for less than half the normal price. It has a specification that makes it perfect for the engineer who needs to keep up to date with digital systems or for use in school science departments. It's ideal for hobbyists and amateur electronics enthuslasts, too.

But the MK14 isn't just a training aid. It's been designed for practical performance, so you can use it as a working component of, even the heart of, larger electronic systems and equipment.

MK14 Specification

- * Hexadecimal keyboard
- ★ 8-digit, 7-segment LED display
- 512 x 8 Prom, containing monitor program and interface instructions
- * 256 bytes of RAM
- ★ 4MHz crystal
- ★ 5V stabiliser
- * Single 6V power supply
- * Space available for extra 256 byte RAM and 16 port I/O
- Edge connector access to all data lines and I/O ports

Free Manual

Every MK14 Microcomputer kit includes a free Training Manual. It contains



Regd No. 213817088.

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.

Please send me an MK14 Standard Microcomputer Kit. I enclose cheque/ Money order/PO for £43.55 (£39.95 + 8% VAT and 40p p&p). Allow 21 days for delivery. operational instructions and examples for training applications, and numerous programsincluding math routines (square root, etc) digital alarm clock, single-step music box, mastermind and moon landing games, self-replication, general purpose sequencing, etc.

Designed for fast, easy assembly Each 31-piece kit includes everything you need to make a full-scale working microprocessor, from 14 chips, a 4-part keyboard, display interface components, to PCB, switch and fixings. Further software packages, including serial interface to TTY and cassette, are available, and are regularly supplemented.

The MK14 can be assembled by anyone with a fine-tip soldering iron and a few hours' spare time, using the illustrated step-by-step instructions provided.

Tomorrow's technology – today! "It is not unreasonable to assume that within the next five years... there will be hardly any companies engaged in electronics that are not using microprocessors in one area or another."

Name -

Address (please print)

Phil Pittman, Wireless World, Nov. 1977.

The low-cost computing power of the microprocessor is already being used to replace other forms of digital, analogue, electro-mechanical, eyen purely mechanical forms of control systems.

VAL and

IS

..........

The Science of Cambridge MK14 Standard Microcomputer Kit allows you to learn more about this exciting and rapidly advancing area of technology. It allows you to use your own microcomputer in practical applications of your own design. And it allows you to do it at a fraction of the price you'd have to pay elsewhere.

Getting your MK14 Kit is easy. Just fill in the coupon below, and post it to us today, with a cheque or PO made payable to Science of Cambridge. And, of course, it comes to you with a comprehensive guarantee. If for any reason, you're not completely satisfied with your MK14, return it to us within 14 days for a full cash refund.

Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN. Telephone: Cambridge (0223) 311488

Science of Cambridge

Practical Wireless, July 1978

World Radio History

use if the DXer lives near a broadcasting station. The Aerial Tuning Unit is another device that is sometimes confused with a loop. The a.t.u. matches an aerial to a receiver and a good match means maximum transfer of signal. An a.t.u. is unsuitable for use with a loop.

Ferrite Rod Aerials

"Would it be possible to make up a type of ferrite rod aerial in a box, on a swivel or something for use with the FRG7?" asks Bob Bell of Blyth who continues to say that he does not have a medium wave loop and a ferrite rod would be much handier size-wise. Yes, it is possible, I tried it several years ago using a ${}^{3}\theta$ in diameter ferrite rod, 8in long, with 60 turns closewound as the main winding and six turns for the coupling winding. The tuning capacitor was about 300pF. The results were disappointing as the pick-up was a lot less than from a standard 40in loop, though I did manage to hear WWL New Orleans 770kHz using this aerial and an R1155 receiver. Pick-up depends on the number of turns and the effective cross-sectional area enclosed by the windings, and a marginal improvement will be obtained by spacing the turns on the windings. The reduction in self-capacitance of the windings enables additional turns to be wound on.

At that time a DXer in the United States got hold of a mammoth ferrite rod one inch in diameter and 12in long, and he achieved quite good results with it. The largest rod I could find was ⁵8 in diameter and 8 in long. Two of these rods were used with a 10in length of Paxolin tubing of ⁵₈in internal diameter. A rod was inserted into each end of the tubing so that they met in the centre. The rods were fixed to the ends of the tubing by adhesive so that the two ends inside the tubing were pressed hard against each other. Fortunately they were a tight fit. The main winding comprised 150 turns of plastic covered wire wound on top of the tubing, spaced at approximately one wire diameter and was tuned with a 330pF variable capacitor and slow motion drive. A coupling winding of 10 turns was led off to the receiver. The results were quite encouraging. The main advantage of this aerial was the high Q and consequent good selectivity, but the pick-up was still less than from a loop. The aerial was mounted on a small stand and was very convenient to use but it was rather top heavy and easy to topple over. A small loop would give as good results and would be a lot easier to make though the experimenter may find ferrite rods an interesting diversion.

Receivers

Experimenting of a different kind being done by Derek Taylor who has obtained a second-hand Barlow Wadley XCR30 and is making comparative tests with his FRG7, on the medium waves. He says "The receiver is very good on medium waves, especially when used with a loop, and in fact seems to be far more selective than the FRG7". It is interesting to note that these two receivers are reviewed in the 1978 edition of the World Radio and TV Handbook and the XCR30 is given "Good" for selectivity but "Poor" for overall performance on the medium waves. The corresponding rating for the FRG7 was "Fairly Good" and "Fair". These tests are of course subjective and one man's meat etc seems to apply to receivers in the DX world. Both the XCR30 and the FRG7 yield good logs for reporters to this column but it is interesting to compare results when the opportunity arises. To be of any value though, the two receivers should be checked for proper alignment, as they should be in any event when used for serious DXing.

Logs and News

Derek Taylor's log with FRG7 and loop includes Radio St Lucia 600kHz at 0110, WLW Cincinnati 700 at 0215, Ougadougou 746 at 2355, WJR Detroit 760 at 0216, WGY Schenectady 810, WCFL Chicago 1000 at 0345, Radio Lighthouse Antigua on 1165 at 0119. James Edwards who lives near Wigan, used the PW m.w. loop with his Realistic DX160, and between 0100 and 0300 he pulled in CFRB Toronto on 1010kHz, KDKA Pittsburg 1020 and WCAU Philadelphia 1210. G. Cox of Dudley reports that MEBO 2 is no longer on 773 but has moved to 908kHz. The current situation about this ship-borne radio in Libya is confusing. Sweden Calling DXers reports that this station and the Voice of Peace are both off the air but that MEBO 2 is expected to resume broadcasting before long.



SHORT WAVE BROADCASTS by Charles Molloy G8BUS

Peter Gatehouse of Buckingham mentions that the tree to which his long wire was attached blew down and he is now looking for a more suitable replacement. Bill Stevenson of Swinton had a similar experience though in his case it was the aerial that broke. An outdoor aerial should be anchored to a building or mast if this is possible, and in an exposed situation the mast should have guy wires or ropes to prevent it moving in strong winds. My experience indicates that it is not the effective part of the aerial, i.e. between the insulators, that breaks but the terminating wire between insulator and support. Thin nylon rope, which has a bit of "give" will help here.

It might be possible to put guy ropes onto the branch of a tree but the usual method recommended is to fit a pulley to the tree trunk, pass the terminal wire or rope over the pulley and fix a weight on the end of it. The idea is that as the tree moves in the wind the weight moves up and down taking the strain off the wire/rope. I have not tried it but it would be interesting to hear from any reader who has practical experience of this or any other method of using a tree instead of a mast.

"Does a 75 ohm screened feeder spoil the efficiency of a 300 ohm ribbon feeder dipole?" asks D. R. A. Lowe of Lichfield. Yes, there will be a mismatch loss at the resonant frequency of the dipole, though if the aerial is used at other frequencies it will not matter. Ribbon feeder with a characteristic impedance of 300 ohms is a convenient material with which to construct a folded dipole. A dipole incidentally, is a one-band aerial. Divide 468 by the frequency in MHz to get the length of the aerial in feet. A dipole for the 25m band for example would be 42ft long.

Cut a length of 300 ohm feeder to the correct length, bare the two wires at one end and solder them together and then do the same at the other end. Fit an insulator to each end and you now have the aerial. Find the exact centre of the aerial and cut one of the two wires at this point. The impedance here is 300 ohms. This is the place to join another length of 300 ohm feeder which will be the downlead and there will be a perfect match between downlead and aerial. The feeder is joined to the balanced (A and A1 or dipole) input to the receiver. If you want to use the dipole at other frequencies join together the two wires at the receiver end of the feeder and connect to the normal aerial socket and you will now have a "T" aerial.

11 Metre Band

Activity on the 11 metre band (25605-26095kHz) is stirring as broadcasting authorities realise that solar activity is on the increase. A recent report in Sweden Calling DXers referred to a programme in Afrikaans on 25790kHz at 2000 which was probably a test transmission from Radio RSA. It is worth watching this band during the daytime and reports, even if the exact frequency is uncertain, will be welcome, but watch out for harmonics. Bob Bell (Blyth) mentions hearing Italy on 25285kHz at 1540 and if the frequency is correct then very likely it is a harmonic. Other interesting loggings from the h.f. end of the spectrum in Bob's log are USSR on 23920kHz, 24040, 24120 and 24720 which may be harmonics and Israel on 25605 and the VOA on 26040, all heard during the afternoon. Bob would like to contact anyone in the Blyth area interested in forming a DX club. Write to Bob Bell, 5 Byron Avenue, Blyth, Northumberland NE24 5RN. Bob feels that there may be many people like himself "tucked away in their shacks all over the Blyth area".

DX

World International Broadcasters is the full name of WINB Red Lion in the USA. R. Guest has had difficulty in contacting this station which transmits in English, welcomes reception reports and "verifies" with a QSL card. Write to WINB, PO Box 88, Red Lion, Penna 17356, USA, which is the address given in the Word Radio and TV Handbook. From Selly Oak, Birmingham comes news of R. J. Irvine's DXing activities using an ex-WD R209 receiver and a 30ft long wire. He mentions that this receiver does not have an r.f. gain control. Why not fit an aerial attenuator as described last month? Stations heard included United Nations Radio (relayed by the VOA), Moscow Radio Ping Pong Station on 12160kHz at 1540 (does anyone have any information on this station?) Sri Lanka in English on 17850 at 1900 wedged between Family Radio and the VOA.

"What is a DXer" is the title of an interesting article in RSA Calling, Nov 1977/April 1978 issue. The article traces the progress of the newcomer from being a Novice Radio Listener through being a Radio Country Chaser, Programme Listener, Short Wave Listener, Reception Monitor and finally to being a DXer. Radio RSA is anxious to hear reactions to the article and ask for letters on this subject to go to DX Corner, Radio RSA, PO Box 4559, Johannesburg, RSA. Nick Stewart (Dundee) writes to say that he is now a reception monitor for Radio Budapest and he reports regularly to this station on their nightly transmission on 6110kHz. This type of reporting can be of immense value to a radio station and many international broadcasters have a network of "monitors" across the world, who give a regular picture of the ever-changing reception conditions.

Radio Grenada on 15105 with a good signal at 2000 is reported by **Harold Emblem** from Mirfield in Yorkshire who uses an Eddystone 730 and long wire. This station was also heard by R. Guest who reports that it has a request programme from 2045 to 2200 on a Thursday. Radio Grenada is listed as being on 15105 with a power of 5kW with broadcasts to Europe between 1945 and 2200GMT. Two unusual items from the ISWC are Radio Tahiti on 15170kHz in English at 1900 and Bangkok on 9655kHz in English at 1100.



by Ron Ham BRS15744

The auroral co-ordinator for the British Astronomical Association, **Ron Livesey** writes "Both my own solar observations and information from professional circles indicate that this coming solar cycle is going to be a strong one". I agree Ron, it looks that way. Although the BAA have a good visual auroral detection network, stretching from ships in the north Atlantic, through Britain, across Norway and Finland to the Russian border, their observations are limited to the hours of darkness, and then to clear skies.

We radio enthusiasts can therefore use our equipment, unrestricted by overcast skies, to help gather that wealth of natural information which will undoubtedly come over the next few years. To this end, both Graham Knight, GM8FFX, my opposite number in Radio Communication, and myself are co-operating with Charlie Newton, G2FKZ, RSGB Auroral co-ordinator, and Ron Livesey to ensure that the utmost value is gained from our readers' reports.

The "Active" Sun

Solar radio noise was recorded at 136MHz by Cmdr Henry Hatfield, Sevenoaks, and myself, and at 142MHz by John Smith, Rudgwick, Sussex, on about 15 days between March 23rd and April 18th compared with only one day for the same period in 1977. Large bursts of noise, some lasting several minutes, were received on March 26th and 27th and April 1st, 7th, 8th, 9th, 10th, 11th, 13th, and 18th, of which two were spectacular; at 1200 on the 9th I watched my radio telescope record a six-minute burst at 95 and 136MHz and heard the noise on other equipment working simultaneously on 28 and 50MHz. Alan Baker, G4GNX, Newhaven, heard this burst overpower terrestrial signals on 144 and 1.8MHz. During the early afternoon of the 11th, Henry Hatfield recorded two massive bursts which he associated with a bright ribbon flare, several baby flares and an ugly black filament which he saw on the sun with his spectro-

helioscope. On this sunny April day there was 6 inches of snow in Henry's garden.

At 0730 on the 13th I heard strong bursts of solar noise on 10m with a long wire aerial feeding my FR101 and at 6m with a dipole into my R216. For several days Henry watched the progress of two sunspot groups and was not surprised when a radio noise storm raged from the 14th to the 18th, during which time G4GNX and myself heard this noise on several radio frequencies.

The 10 Metre Band

With solar particles battering the earth's atmosphere it was not surprising that radio blackouts and ionospheric disturbances, affecting the h.f. bands, were reported on April 5th, 11th and 14th by Barry Ainsworth, G4GPW, Sompting, Sussex, Alan Baker, Roy Bannister, G4GPX, Lancing, Sussex, Alan Baker, Roy Bannister, G4GPX, Lancing, Sussex, the BBC world Service, the Daily Telegraph newspaper and Dr Harold Brodribb, St. Leonards-on-Sea. Neil Clarke, BRS 34306, Knottingley, Yorks, listens on 10m with a Yaesu FRDX400, fed by a TA32 beam at 25ft a.g.l., and like many of us he monitors the Cyprus, 5B4CY, and project TESSA, ZE2JV, beacons both of which he received almost daily throughout March.

On the 18th, G4GNX heard AA4AA, the first of the new American call-signs, strong signals from PY, RA, VU, and also worked two Russian stations on s.s.b. Between 1234 and 1858 on the 25th, Alan reported 589 signals from 5B4CY and had s.s.b. contacts with a K2, 2 UA6s, and 3 Ws. Both Gordon Goodyer, BRS 37345, Petworth, Sussex, and myself observed the excellent conditions on the 26th; around 1600, Gordon, using his Eddystone 750, heard strong signals from Africa, Europe, the Middle East and South America. Meanwhile at 1436 stations from North America were pounding in at my QTH and the beacon signals from Bahrain, A9XC, Florida, N4RD, ZE2JV, and 5B4CY were averaging 579. This same group of beacons were heard again at midday on April 9th and in the space of six minutes, from 1005, I heard a VK work OE. OH, PA0 and YU giving them reports of 57 and 59. JAs and VKs were again heard at 1000 on the 31st, and at 0850 on April 7th I received a 59 signal from JA8RUZ calling European stations from northern Japan.

Conditions were good on April 8th, 9th and 10th when strong signals were frequently received from the regular beacon stations, and on the 10th, Nigel Golds, BRS 36910, West Chiltington, Sussex, heard a 488 signal from the German beacon DL0IGI. Around 1830 on the 8th, Gordon Goodyer heard Ws 1, 2, 3, 5, 8, 9, and signals from Tanganyika to South America and Canada. On the 9th, he heard the Mauritius beacon, 3B8MS and signals from British Honduras, Brazil, Cyprus, Portugal and the USSR, while G4GNX, at 1445, worked WD4LBI on c.w.

Auroral Propagation

Between 1719 and 2015 on March 26th, John Branegan, GM80XQ, Saline, Fife, had auroral contacts on 2m with GM8NCW, Fife, G8LVM, Stoke, G8BHH, Wolverhampton, and heard EI6AS on s.s.b., and DL, LA, and SM on c.w. At 1945, the radio aurora eased off and John said "we were treated to one of the finest visual aurora I have ever seen which started as a bright yellow-green band along the northern horizon and by 2000 had added a great stream of bands right up the northern sky and over my head to the south".

During a less intense event between 1656 and 1900 on the 27th he heard signals from DL, EI, GI, GW, and PA. This report fits nicely with the solar activity on the 26th and 27th and the 24-hour ionospheric disturbance reported by the BBC World Service on the 27th. At 1818 on April 4th **Dermot Cronin**, G4GRO/ EI9DC stationed at the *Royal Sovereign* in the English Channel, heard GM8FFX, at 42A on s.s.b. Around midnight on April 11th/12th, **Mr McDonald**, seven miles east of Oban, saw an aurora which was mainly a white glow, with some movement, and indistinct beams.

OSCAR-8

Vic Hartopp, G8COB, Northampton, listened to the first few days of OSCAR-8's life and John Branegan worked out his own orbital parameters after the first three orbits, and has followed the satellite on all modes since. On March 19th, John's first OSCAR-8 QSO with PA0KT was spoilt by rapid fading which he thinks was due mainly to his horizontally polarised aerial. Since changing to a circularly polarised 2m helical he has worked several stations.

John has now built an OSCAR-8 plotter and contributes information to the Scottish AMSAT net, organised by GM8BKE, on Sundays at noon, 144-28MHz. "As yet", says John, "not many stations are using OSCAR-8. Reasons are—continuous high Doppler shift—the receiver must be tuned continuously to hold s.s.b.—the need for circular polarisation on the up-link, and on Mode J, the difficulty of reading the very weak down-link signal".

Readers' Equipment

Neil Clarke uses a 6-element beam at 30ft a.g.l. for 2m DX listening, and for the repeaters, he has a Lowe VHF Monitor receiver, AJV1515, with a ground-plane aerial at 35ft and a ${}^{5}_{8}$ -wave Mag Mount on his car. Harold Brodribb is building a tuner for the 6m band ready for the sporadic-E season and Gordon Goodyer is considering using a m.o.s.f.e.t. pre-amp in front of his CR100. Frank Luman, Glasgow, has added a $5{}^{1}_{2}$ in JVC TV set which tunes through Bands I and III and u.h.f., to his DXTV gear, and for the same reason I have installed a JVC 3060, $2{}^{1}_{2}$ in TV receiver tuneable through the European Channels 2-4, 5-12, and 21-69. Denis Sullivan, Chiswick, now has a new National Panasonic RF-2000 in addition to his Trio QR666.

Overseas DXers Visit BBC

One of our Swedish readers, Moritz Saarmann, on holiday with two friends, Håkan Holmlund and Jan-Olof Karlsson, visited the headquarters of BBC World Service at Bush House, London, on March 21st.

All three are SWL members of Radio Club Tellus, near Mölndal, just south of Gothenburg, which has its own amateur station, SK6IQ, comprising a Swedish receiver, similar to the Hammarlund Super Pro, a much modified R208, and a Heathkit SB102 transmitter. The club, where some twenty members meet weekly, uses all bands and runs courses on DXing for beginners, c.w. and a variety of technical subjects.

At home Moritz uses a Drake SW4 on the h.f. bands, a Hallicrafters SX42 (500kHz to 108MHz), for part of the v.h.f. bands and a Dynaco FM5 stereo for Band II. His aerials are dipoles for both h.f. and v.h.f. and a long wire. Hakan and Jan-Olof use long wire aerials feeding an Eddystone 960 and a Kungs domestic receiver respectively. Hakan, who also has a Hallicrafters SX18 and a Pioneer stereo which he uses on Band II, is Deputy Secretary General of the Swedish DX Federation, whose annual meeting, the traditional DX Parliament, will be held from June 9th to 11th this year.

While at Bush House the three visitors were studio guests for a recording of a World Radio Club letters programme, with Peter Baresby, Mark Deutch, Henry Hatch and the Author.

Tropospheric Openings

At 2110 on April 7th, Frank Luman received a picture from NRK, Oslo, Ch.E-6, and during the following evening he watched RTE, Dublin. Conditions

on v.h.f. fluctuated frequently during early April; on the 3rd, Garry Hibbert, G8HXB, Portslade, Sussex, heard repeaters GB3BC, BM, and PI while static on Devils Dyke, Brighton; at 0142 on the 5th G4GNX heard a GW8/M working through GB3LO and at 1555 on the 9th he had a s.s.b. contact with G8KHD/P who was running 10 watts from a Liner-11 in Buxton. Brian Fenwick, G8BTC, Brighton, heard both GB3BC and FZ1THF on R6 during the evening of the 8th and FZ3THF, R4, on the 9th. On the 17th, Keith Smith, G3TLB, Crowborough, heard ON0OV on R4 and Dermot Cronin heard a GU direct at Royal Sovereign.

Nigel Hewitt, G8JFT, used his Uniden 2m rig and a ¹₄-wave ground plane to work locals and the West Country from his bedside in the Royal Sussex County Hospital, Brighton, while recovering from appendicitis. We all hope that Nigel will be fully fit and that conditions are good for the RSGB VHF National Field Day and SWL contest on July 1st and 2nd.

Thanks again for all your interesting reports; there is a lot happening so let me hear from you soon.





JOHN BRANEGAN

by Ron Ham

One of John Branegan's earliest memories of home is listening to *Chidrens Hour*, on a 3-valve straight set, built by his Father around 1933 from what he thinks was a design by F. J. Camm in *Practical Wireless*. John, born in 1927, moved to Woolston, Southampton, in 1935, where his Father was involved with the building of Spitfires, and in 1938, at the age of 11, he became an SWL when he first heard American short-wave stations on his Father's new Murphy superhet. In 1943, John left the King Edward VI Grammar School, Southampton, and joined the Royal Navy as Electrical Apprentice transferring to Radio Artificer before completing his training.

On his first ship, the aircraft carrier *Illustrious*, John had charge of two v.h.f. radars and rooms full of v.h.f. communications equipment. Later, while serving in the Mediterranean and in particular at a shore wireless station in Malta, he became interested in propagation. Meanwhile he passed the City and Guilds final in telecomms, and in 1953, while serving with submarines, he took the examination for a Commission. In 1954, John became a Sub-Lieutenant and joined a frigate for service in the Far East which was interrupted by a spell at Heriot Watt, Edinburgh, where he obtained graduate qualifications for IERE.

In 1963, he began training for nuclear submarines where he served until he retired in 1977 having been promoted to Commander in 1973. At his present QTH, a bungalow, 360ft a.s.l. in Saline, Fife, he now spends all of his spare time on v.h.f. with a special interest in satellite work and propagation studies. For the h.f. bands he uses an FRG-7 receiver preceded by Microwave Modules converters for 2m and 70cm, in addition, a GEC receiver covers Band II f.m. and a much modified Pye TV is used for video DX. In his aerial farm are crossed dipoles for 10m, OSCAR down-link and CB, an 8-element rotatable Yagi for 2m DX, a 7element fixed Yagi for 2m auroral studies, a homebrew 14-element parabeam for 70cm DX and OSCAR-7 and 2 fixed aerials for the 70cm repeaters GB3ML,, Central Scotland, RB10, and GB3ED, Edinburgh, **RB14**.

Commander John Branegan, now GM8OXQ, is a regular contributor to the auroral sections of the British Astronomical Association and the RSGB, and to my v.h.f. column, and is always pleased to meet any local radio enthusiasts who want help or just to have a natter.

						ENED MINIATU			OMPONENT PAKS	DR	IDGE RECTIFIERS
	TRAN	3F	UKM	-KS	Ref mA 238 200	Volts 3-0-3		PAP 55 50 F	ligh Quality Metal Oxide		2A £
					212 1A, 1A	0-6, 0-6			5% 1 + 1 W resistors.		2A £
	. EX-STOCK—	SAME F	AY DESPAT	CH VAT 8%	13 100	9-0-9		-38 150	Mixed Value Capacitors.		4A £ 4A £
			AT PLOTAT) 0-9, 0-9) 0-8-9-, 0-8-9		0-38 0-71 10 F	teed Switches.		4A £ 6A £'
12 AN	ND 24 VOLT OR 12-	-12V	30 V O	LT RANGE	208 1A.1A				Wire Wound Resistors		10A* Ē
PRI	Amps	rs	Prim 220/240V :	Sec 0-12-15-20-24-30V	236 200, 200	0-15, 0-15		-38 mix		VAT 12	* *VAT 8% P & P
Ref 1	12V 24V £	PAP	nection to approp	-0-15V available by con-		0-20, 0-20		-78 25	Assorted presets.		
	0.5 0 25 2 20	0.45	Ref Amps	É P&P) 20-12-0-12-20		78	tag terminal strips.		
	1-0 0-5 2-64 2 1 3-51	0-78	112 0·5 79 1·0	2·64 0·78 3·57 0·96		0-15-20-0-15-20 0-15-27-0-15-27		0.0		Magneti	c to Ceramic Cartri
18 4	4 2 4.03	0-95	3 2 0	5-27 0-96	204 1A, 1A	0-15-27-0-15-27	5-39 1	-96	dware pack nuts, bolts, hers, insulators		er (MPA 30) opera
	6 3 5-35 8 4 6-98	0.96	20 3.0 21 4.0	6-20 14	239 50	12-0-12		-38			8 20-45 £3 50. VAT 12
72 10	0 5 7-67	1-14	51 5-0	8 37 32	S112 500	12-15-20-24-30	2.64 0	70p	P&P 40p. VAT 121%.	p & p 35	5p.
16 13		1-32	117 6·0 88 8·0	9-92 1-45		MINI-MULTIM			SPECIAL OF	CED	12 way Greico h
15 20	10 13-18	2.08	89 10.0	11 73 1 64 13 33 1 84		AC-1000V DC-10					black plastic term
87 30		2.08			20.000 ohr	rgain £5-68-VA n/V Multimete	mirror	scale.	Avo Meter (107) Mk Ranges DC to 1000V c		
		OA	60 V O	LT RANGE	Ranges AC/	DC to 1000V DC	current to	250mA	1 amp AC to 1000V	3 ohmic	
	50 VOLT RANGE 240V Sec 0-20-25-33-	0.001	Prim 220/240V 5	ec 0-24-30-40-48-60V.	Resistance	io 3 Mohms. I≟″,£11·34. Ρ & Ι	2 £1-85 V	AT 8%	ranges to 10M ohms. 10,0 1000 AC safely cut-out	00/V DC	pull-out type 25p, 15
V-0-20V	or 25V-0-25V availab	e by con-	nection to approp	0-30V available by con-		TEST METE			PP £1.15. VAT 8%.	2.40 .00.	2 × Fuse boards, 2 c 11 fuse holders 21
ection to	appropriate taps.		Ref Amps	£ P&P	AVO 8 MK5	£77-10 AVC	0 MM5	£26-10	Plug In Save Batterier	1	30p + pp 15p, VAT
7ef 02	Amps £ 0.5 3.41	P&P 0·78	124 0·5 126 1·0	3-88 0-96 5-58 0-96	AVO 71 AVO 73	£31-30 Wee £42-50	Megger	£32-50	3300 fits into 13A socket	6-7 5-9V	
03	1 0 4 57	0.96	127 2.0	7 60 1 14		in circuit Transis	tor Tester	£30-00	300mA multiplug outlet Stabilised 3-6-7 5-9V/40	£3·30	
04	2-0 6-98 3-0 8-45	1 14	125 3·0 123 4·0	10-54 1-32 12-23 1-84	U4315 Budge	t Meter 20KΩ/VC	C, 2K/VA	C 1000v	multiplug outlet	£8-81	BE1 Prim 0-12
06	4-0 10-70	1.50	40 5-0	13-95 64	AC/DC, 2-5	A AC/DC, 500 eads £15-95. VA	К 108. in Т 8% Р 4	robust P ¢1-15	VAT 12 % P & P 55p		0-120V (120
18	6-0 14-62 8-0 17-05	1 64	120 6·0 121 8·0	15-66 1-84		ONIC CONSTR			DECS SOLDERLE	SS	240V) Sec 24V 10
19	10-0 21-70	0A	121 8-0 122 10-0	20-15 OA 24-03 OA	10 projects	(including elect	ronic orga	an). No	BREAD-BOARDI	NG	£5-50 P&P£1-0 BE7 0-110-120-220
	SOLATING (SCRE		189 12-0	27-13 OA	soldering ne	eded £7-29. VAT		° 70p	S Dec 70 contacts T Dec 208 contacts	£1 98 £3 63	Pri. 240V. Sec. 20
PRIM	A 120/240 SEC 120/240	CT			HIGH O	NEW RANG		EDC	U Dec "A" for LC.s etc	£3-99	1A. £1 50, 30p på
Ref V	VA (Walls) £	P&P		ANSFORMERS	Sec 45-36-	0–36–45 Sec to	o give	36-0-36.	U Dec "B" for I.C.s etc	£6-99	BE3 100V line 1 4Ω 7/10W £2-0
49	20 4-40 60 6-20	0-79	Ref VA (Walts) 113 15 0-115-2		36-0-36, 45-0	-45V, 72V or 90	v		VAT 8% P & P 40p		P & P 66p
50	100 7.13	1-14	64 75 0-115-2	10-240 3-95 0-96	2A	£9-89		P & P £1-38	ANTEX SOLDERING	IRONS	BE4 Prim 120
51 52	200 11-16 250 12-79	50		00-220-240 5-35 0.96	3A	£11-47		£1-48	15W £3-75 18W 25W £3-95 Stand	£3-75 £1-40	240V 9-0-9 1 £1-88 P & P 0-3
53	350 16-28	1.84	84 1000 0-115-2	00-220-240 18.70 2.08	4A 5A	£13-90 £18-74		£1-84 £2-15	VAT 8% P & P 46p	21.40	BE5 15W matchin
54 55	500 19-15 750 29-06	2 · 15		00-220-240 23-36 OA	6A	£20-77		£2·30			trans. sec 15:
56	1000 37-20	OA		00-220-240 48 00 OA		PANEL METE			Audio kit 25W + 25W. (with instructions £35.)		sult EL89 £1-5 P & P 30p. Ref. 3
57 58	1500 45-60 2000 54-80	0A 0A			2" 0-50µA 0-500µA		0-50µA 0-500µA	£6.70 £6.70	Cab-mounting hardwar	e £14-50.	240-240 isolate
59	3000 79-05	ÖÅ	CASED AUTO	TRANSFORMERS	0-1mA	£5-50	0-1mA	£8-40	P&P £1.73, VAT 121%		200VA £4-20 P &
state Vol	its required 115V or	240V.		5V USA flat pin outlet	0-50V		0-50V	£8-40	PLASTIC BOX	S	BE6 Pri 0-220V se 4500V 10MA £4-
HIG	H VOLTAGE MAI	S	VA £ 15 4-9	P&P Ref 6 0-96 113W	VU Indicator	Panel 48 × 45 2	50µa FSD	£2-60	ABS Slotted Brass	Inserts	P & P £1.00
	1SOLATING n 200/220V or 400/440	-	150 8 4	8 1-14 4W	65p Carriage	Edge 54 × 14 2	ouµa roD	£2.60	PB1 180mm × 62 × 40 PB2 100mm × 75 × 40	56p 63p	Ref. 62 240-24 isolator 250V.
Se	n 200/220V or 400/440 ac 100/120V or 200/240		200 9-9 250 10-4			-1 KVA 240V 1	0 240V A	nciosed	PB3 120mm × 100 × 45	70p	£5.20 P & P 96
'a F	Ref £	Ρ&Ρ	500 15-7	3 1-64 67W	style termin	al connection.	Special		P&P 29p VAT 8%		from second second
	243 5 89 247 14 11	1 32	750 18-5 1000 22-0		£18-70. Carr	iage £2.75. Ref.	BE7.	100	Barrie Elec	tron	aice Itd
000 2	250 41-78	0A	1500 26-6		Prices corre	ct 8-5-78. Ple	ase add				
000 2	252 54 25	OA	2000 37.4	5 OA 95W	VAT after P	& P.		3	, THE MINORIES,		
ur wide r	range of transformer	are too r	umerous to list. p	lease call (open 9am-5p	m Mon-Fri) or	send your require	emente		TELEPHONE	01-48	8 3316/7/8
a strastl	& semiconductor sta	chiete De	and Multi Motors	Audio accessories, sen		Jee. requi		10.000			ATE & LIVERPOOL S



THIS is the Catalogue you need to solve your component buying E APILE problems HOME The finest components catalogue yet published. Over 200 A-4-size pages. About 5,000 items clearly listed and indexed. Nearly 2,000 illustrations. Bargain List sent free. • . At £1.40, incl. p. & p., the catalogue is a bargain. Send the coupon below now. HOME RADIO (Components) LTD., Dept. PW., 234-240 London Road, Mitcham, Surrey CR4 3HD Please write your Name and Address In block capitals NAME ADDRESS

> (Rean No Dept. P.W London 912966) CR4 3HD

BENTLEY ACOUSTIC CORPORATION LTD. 7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX All prices inclusive of V.A.T. at 123% Telephone 6743 042 1:20, 54M8A :70 6F24 :90 7V7 : 5:00 19405 : 65 50 EH5 : 85	DAP91 35 EC54 1.00 EK90 .70 KT41 1.00 PENDL- UL41 .90 AA129 18 BF13 .44 DAF96 1.00 EC66 .84 FL32 1.00 KT44 1.00 4020 1.00 UL41 .90 AA129 18 BF130 .44 DC90 70 EC86 .84 FL32 1.00 KT44 1.00 4020 1.00 UL41 .90 AA213 .21 BF180 .45 DD4 .80 EC63 .64 FL33 .70 FL200 1.35 UL40 .00 AA713 .10 BF181 .47 DD43 .75 EC92 .00 RL41 .00 KT61 .100 PL33 .100 UM41 .40 AC127 .28 BF165 .47 DF91 .30 EC07 .76 EL31 .100 KT61 .40 PL31 .40 UU12 .46
DB2 -60 sANS -70 6F23 1.00 774 -80 19BG6G 50L60T1.00 OC3 -50 8AQS -75 6F26 45 724 -80 19BG6G 50L60T1.00 OC4 -50 6AQS -50 6P26 45 724 -80 19DG 66KU 1.00 66KU 1.00 66KU 1.00 72 -70 IA3 -60 6ARS 1.06 6722 1.00 8DB -52 19H1 400 72 -70 IA3 66 6ARS 1.06 6632 1.00 68K3 -140 6AA3 -140 6AA3 -140 6AA3 -140 6AA3 -140 6AC1 -50 10C1 -70 201 706 6AC2 -120 6AC1 -50 10C2 -100 6AA3 -140 10C1 -60 6AC1 -50 10C2 -20 2021 -20 2021 -20 126	$\begin{array}{c c c c c c c c c c c c c c c c c c c $
1T4 360 0BAA 850 6L1 2:60 10713 -60 352.6 -75 6097 2:00 1U4 -60 6BAA 480 6L1 2:60 10714 2:60 352.6 -75 6097 2:00 1U5 -65 6BQ7,A 10 6L1 2:00 12.46 1:00 23.07 2:00 6463 2:00 2D21 -65 6BR7 1:00 6L1 2:00 12.46 30.04 7:67 7:025 2:00 2GK3 -76 6BR3 1:29 6LD12 -40 12.246 30 30.01 8:00 7:05 2:00 3X4 -65 6BW6 3'76 6LD12 -40 12.46 30 30.015 1:00 7:45 9:00 5:5 3B7 -56 6BX7 -46 6P1:12 -60 12.47 45 9:00 -55 30.16 7:5 12.047 52 9:00 5:5	$ \begin{array}{c c c c c c c c c c c c c c c c c c c $
syngr as 66LBA -96 68K7GT 70 12K8 -75 307L12 -28 ATP4 50 SZ40 6CM7 -00 68Q7 70 1290T 50 307L13 128 AZ1 50 SZ40 -75 0C38 -75 6U4GT 100 128A7 -75 307L13 128 AZ1 50 SZ40T 100 6CU5 90 6U70 55 128C7 50 307L14 180 AZ31 100 6/30L2 90 6D3 -76 6U8 50 128U7 -55 35A3 100 B36 -76 6A3G 140 6D3 -86 6X4 45 128U7 -80 35L63 80 B128 90 6AC7 70 6D3 60 6X64 45 128U7 -80 35L63 80 BL32 90 6AA6 70 6F1 80 6YG 128Y7	Encial 1.60 EF92 .70 International and the state of the state state of the

ETCH RESIST TRANSFER-KIT SIZE 1:1

Complete kit 13 sheets $6in \times 4\frac{1}{4}$ in £2.50 with all symbols for direct application to P.C. Board. Individual sheets 25p each. (1) Mixed symbols (2) Lines 0.05 (3) Pads (4) Fish plates and connectors (5) 4 lead and 3 lead and pads (6) DILs (7) Bends 90° and 130° (8) 8-10-12 T.O.5. cans (9) Edge connectors 0.1S (10) Edge connectors 0.1 (11) Lines 0.02 (12) Bends 0.02 (13) Quad in line.

CIRCUIT LAYOUT TRANS-FERS SIZE 2 : 1

One sheet 12 in \times 9 in giving all transfers as in etch resist from No. 3 to No. 10 inclusive makes circuit layout easy. Black only. Price £1. Also lines and bends. Price £1.

FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex etc. Choice of colours red, blue, black or white. Size of sheet 12 in \times 9 in. Price £1.


GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering. Colours red, blue, black or white. Each sheet 12 in \times 9 in contains capitals, lower case and numerals. Jin kit or Jin £1 complete. State size required.

ALL ORDERS DISPATCHED PROMPTLY. ALL POST AND VAT PAID. Ex. U.K. add 50p for air mail. Shop and trade enquiries welcome.
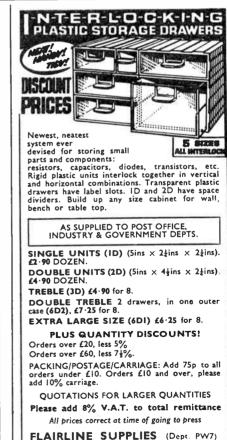
> E. R. NICHOLLS P.C.B. Transfers Dept., PW, 46 Lowfield Road, Stockport, Ches. 061-480 2179

BRAND NEW SURPLUS MODULES AND OTHER ITEMS AND OTHER TIEMS 2 STAGE STEREO PRE-AMP on 6" × 74" P.C.B. 4 push buttons, gram, tape in/out, aux. on/off. 4 slider controls. vol., bal., bass., treble, input approx. 100mV for 300mV out with knobs. Now only £6.00 STEREO POWER AMP to match on 64" × 54" P.C.B. 10W + 10W out for 60mV in. Includes rect., smoothing and supply for pre-amp. Bargain at only £4-90 Build your own music centre SPECIAL OFFER PRE-AMP & POWER AMP Pair only £10.00 TRANSFORMER to suit 240v/22v £2.70 ELAC SPEAKERS 8", 8Ω with tweeter cone. £8.50 POWER TRANSFORMER 240v in, 36v out 21A continuous plus 24v 1A with 18v tap will power suitable 35W + 35W amp. drop through power surable sort of type. Impregnated. Quantity available. Exceptional value at £4.90 weighs nearly 41b—hence £3.90 to callers. **PUSH SWITCHES** with modern square buttons. 8 switches on bar, 4 independent plus 4 inter-dependent latching. As used on music centres etc. £1:50 centres etc 500pF + 500pF twin gang, air spaced capacitor. diecast frame. Ball bearing shaft. Anti backlash. Geared S.M. drive. $2\frac{1}{2}n'' \times 2n'' = 1\frac{1}{2}n''$, plus shaft $1\frac{1}{2}n''$ Rear ext, shaft. only 85p Cash with order, Prices inc. P & P and V.A.T. ELECTRONICAL SUPPLIES CROYDON 40, Lower Addiscombe Rd., Croydon, CRO 6AA. Tel: 01-688-2950.



124 Cricklewood Broadway, London NW2 Tel. 01-450 4844



A. D. E. (SECURITY) CO., 217 WARBRECK MOOR AINTREE, LIVERPOOL TEL: 051-525-3440 STOP PRESS ! Trade Price List Available Applications on Official Stationery only

Practical Wireless, July 1978

Doram Electronics Ltd PO Box TR8

Wellington Road Estate

Reg No. 1155856. Wellington Bridge Leeds LS12 2UF

ΩAM



Come and get a great deal Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat Express Mail Order TeL orders on credit cards £10 min. Trade and export enquiries welcome A. Marshall (London) Ltd, Dept: PW London: 40-42 Cricklewood Broadway, NW2 3ET Tel: 01-452 0161 Telex: 21492 & 325 Edgware Road, W2 Tel: 01-723 4242. Glasgow: 85 West Regent Str, G2 2QD Tel: 041-332 4133. Bristol: 1 Straits Parade, Fishponds Road, BS16 2LX Tel: 0272 654201 2N929 0 37 2N3417 0 25 2N4062 0 20 2N5245 0 37 AF106 0 60 BC182L 0 15 AY-3-8500 CA3062 3 75 LM341P240 80 LM923 0 50 LM78L05CZ SN76018KE 2N330 0 37 2N3439 0 83 2N4121 0 27 2N5248 0 14 AF109 0 82 BC183A 0 12 6 50 CA3084 1 10 LM348N 0 95 LM1303N 1 15 0 30 1 60 2N1131 0 52 2N341 0 52 2N34122 0 27 2N5248 0 14 AF109 0 82 BC183A 0 12 6 50 CA3084 1 10 LM348N 0 95 LM1304N 1 52 LM78L12CZ SN76023N1 50

2N1303	0 80 2N3442 1 45 2N4123 0 19 2N5294 0 44 AF115	0 70 AC184 0 12				LM1304N 1 52	LM78L12CZ	SN76023N1 50
2N1305	0 80 2N3565 0-25 2N4124 0-19 2N5401 0 44 AF118	0 70 BC184L 0 15				LM1305N 1-52	0 30	SN76023ND
2N1501	0-35 2N3566 0 25 2N4125 0-19 2N5416 1-65 AF124	0-70 BC205 0 17				LM1307N 1 22	LM78L15CZ	1 - 30
2N1613	0 30 2N3567 0 25 2N4126 0 19 2N5447 0 16 AF139	0 75 BC212A 0 15				LM1310N 2 10	0 30	SN 16033N2 35
2N1637	0-72 2N3638 0-17 2N4235 1 35 2N5448 0 16 AF200	1 30 BC212LA 0 18				LM1351N 1 30	LM78224CZ	SN76110N1 30
2N1890	0-30 2N3639 0 38 2N4236 1 65 2N5449 0 20 AF201	1-30 BC213B 0 15			LM373N 3 35	LM1458N 0 45	0.30	SN76115N1 65
2N1893	0 30 2N3644 0 40 2N4237 1 65 2N5457 0 35 AF239	0 70 BC213LA 0 17		CA3076 2-12 CA3080 1 85	LM374N 3 35	LM1496N 1-97	MC1035P 1 90	SN76116N1-80
2N1991	1 10 2N3662 0 25 2N4240 1-70 2N5458 0-35 AF240	1 25 BC214 0 17			LM377N 1 80	LM1800N 1 94	MC1327P 1 70	SN76131N1 30
2N2193	0-50 2N3663 0-29 2N4250 0 26 2N5555 0-65 AF279	0-88 BC214L 0 18		CA3080A 2 10 CA3086 0 50	LM378N 2 40	LM1812N 6 20		SN76226N1 68
2N2194		0 95 8C237B 0-15	CA3018 0.75		LM3795 4 25	LM1820N 1-16	MC1352P 1-20	SN76227N1 30
2N2217	A FF 0412300 A 44 2194200 U 32 0410400 A 44 401400	1 30 EC238B 0 13	CA3018A 1-10		LM380N8 0 96	LM1828N 1 90	MC1433G 3 65	SN76228N1 55
2N2218	A 38 0413304 A 44 2194204 U 38	0-70 BC239C 0 17	CA30.0 2 20		LM380N141 08	LM1830N 1 90	MC1435G 2 20	SN76531N0-82
2N2219	2 19 200 U 32 LIVELO U 40 1	0 16 BC256A 0 29			LM381AN2 70	LM1841N 1 90	MC1439G 1-75	SN70532N1-55
2N2221	21428/ 0.22 2140124 0.43 0.00	0 16 BC257A 0-18		CA3130 1-06 CA3140 1 04	LM381N 1 69	LM1845N 1 50		SN76533N1 · 30
2N2222	2144200 0.22 2140125 0.41	0-16 BC258B 0-24		LOBST1 2 25		LM1848N 1 98		SN76514N1 60
2 22270	0410700 4 40 2144292 0 21 210200 0 50 000110	0-22 BC259B 0-19		LM114H 2.75	LM384N 1 55	LM1850N 1 90		SN76515N1 80
2N2368	0 97 2N3709 0.12 2N4302 0.31 00302 3 05 BC114	0 22 BC261A 0 25		LM301AH0 50	LM386N 0-85	LM1889N 4 90	MC1468L 3-85	SN76546N1-58
2N2369	0.07 2N3710 0 19 2N4303 0.33 10020 0 50 BC115	0 22 BC2628 0 26				LM2907N-8	MC1469R 3 10	SN76550-2
2N2483	0 10 2N3711 0 19 2N4342 0 60 10011 0 10 BC116	A 04		LM301-8 0 30	LM388N 1 00	1 80	MC1488L 4 25	0.38
2N2613	0.00 213712 1 20 2N4401 0-20 10346 0 01 BC118	A 00 DC203D V.20		LM304 2 60	LM389N 1-00		MC1495L 5-50	SN76552-2
2N2646	0.00 2N3714 1.55 2N4402 0.20 40363 4 45 BC135	0-22 BC264B 0 65 0-22 BC307B 0 16	CA3029 0 75		LM555CH 0 38	1 80	MC1529G 7-10	0-57
2N2848	1 10 2N3716 1.70 2N4403 0.20 40290 0.70 8C136	0 21 BC308B 0 16		LM308H 1 20		LM3301N 0-60	MC4024P 2 20	SN76570N1 80
2N2904	0 31 2N3794 0 21 2N4822 0-83 40408 0-82 BC137	0-22 BC309C 0 16	CA3030 1 50 CA3030A 2-20		LM7-18 2 99		MM5314 4-60	SN76620AN
2N2905	0 31 2N3819 0 36 2N4870L 0 58 40440 0 70 BC138	0-44 BC327 0-22	CA3030A 2-20 CA3033 3 70	LM317K 3-35		LM3401N 2 55	MM5316 4 60	0.99
2N2906	0-25 2N3820 0 39 2N4871L 0-51 40512 1-70 BC140	0 30 BC328 0 20				LM3900N 0 68	MM5320 4 20	SN76650N1 20
2N2907	6-25 2N3821 0 95 2N4898 1 55 40504 0-87 BC141	0 32 BC337 0-20			LM703LN 1 15	LM3905N 1 15	NE555 0 33	SN76660N0 66
2N2923	0-17 2N3827 0 27 2N4901 1 65 40595 0-98 BC142	0-32 BC414 0 17				LM3909N 0 78	NE556 0-65	SN76666N0-99
2N2924	8 17 2N3854 A 8-36 2N4902 2-20 40673 0.80 BC147	0-13 BC415 0 16		LM320T152 15		LM3911N 1 10	NE560 4-50	SL610C 2-75
2N2325	0-19 2N3855 0-30 2N4903 2-75 AC126 0-48 BC148	0 15 BC416 0 17	CA3038A 4 10	LW3201132 15			NE561 4-50	SL611C 2.75
2N3011	0-37 2N3856A 0-19 2N4904 1-85 AC127 0-48 BC149	0 15 BC547A 0 13	CA3039 0-77	LM320MP5	LM710 0.67	LM4250CN 1.30	NE562 4 50	SL612C 2-75 SLB20C 3-85
2N3020	0-75 2N3858A 0-20 2N4905 2 40 AC128 0 48 BC153	0 30 BC547B 0-13	CA3040 3 75			LM78L05CH	NF565 1 39	SL621C 3.75
2N3053	0 25 2N3859A 0-22 2N4920 0 83 AC151 0-43 BC154	0 30 BC548 0-13			LM711CN 0-72	0 85	NE566 1 75	SL623C 6-25
2N3054	0-72 2N3860 0-18 2N5086 0 30 AC152 0 54 BC157A	0-15 BC5498 0-14	CA3342 1 65		LM723C 0 75		NE567 1 90	SL640C 4-40
2N3055	0-75 2N3866 1-98 2N5087 0 30 AC153 0-59 BC158B	0.15 BC558 0 13		LM320MP15	LM723C-14	0 85	NE558N 1-98	SL641C 4-40
2N3108	0-75 2N3901 0-30 2N5088 0-30 AC153K 0-59 BC159B	0-17 BC559 0-15	CA3045 1 58	1.15		LM78L15CH	NE571N 4-95	SL701C 2.50
2N3133		0 38 BCY54 2.40		LM320MP24	LM726 5-80	0.85	SAS560 2.70	TAA263 1 35
2N3242		0-13 BCY58 0-27	CA3047 2-20		LM741C 0 70		SAS570 2.70	TAA300 3-70
2N3250	0.35 2N3906 0 18 2N5130 0 22 AC187 0.59 BC168B	0 13 BCY70 0 21			LM741C-80 30	0.85		TAA320A
2N3301	0-45 2N3962 0-95 2N5131 0-22 AC187K 0-65 BC1698	0-13 BCY71 0 26			LM741C740 30		SAS590 2.40	1.15
2N3302	0-39 2N4031 0-55 2N5137 0-22 AC188 0 54 BC170B	0-19 BCY72 0 18			LM747CN 0 99	1 75	SN76001N1-30	TAA350A
2N3392	0-17 2N4032 0-65 2N5143 0-22 AC188K 0-65 BC171B	0-17 BCY78 0-43	CA3050 2 66		LM748-8 0 50	LM7812KC	SN76003N2-38	3.00
2N3394	0-17 2N4033 0-65 2N5180 0-58 ACY17 1-00 BC172C	0-15 8D121 2-20		LM340T150 88	LM748-14 0.50		SN76008KE	TAA521 1-10
2N3397	0-19 2N4036 0-72 2N5190 0 65 ACY22 0-65 BC173C	0-17 BD131 0-55			LM716 1.00	LM7815KC		TAA522 2-10
	OUR NEW 1978 CATALOGUE IS AVAILABLE	NOWI			LM900 0 50	1 75		TAA550 0-48
	LOTS OF NEW PRODUCTS AND IDEAS.		CA3054 1 10	LM341P120 80	LM911 0-50	LM7824KC	SN76012ND	TAA560 2-10
1			CA3059 2 10		LM921 0 50	1 75	1-30	TAA570 2-20
	PRICE 45p POST PAID OR 35p TO CALLERS.		Prices correct a	16 May 1978	All prices inclu	de VAT, p&p	40p.	

"CASTLE ELECTRONICS"

7, CASTLE STREET, HASTINGS, SUSSEX Tel: (0424) 437875

2" METERS:-

All new ex WD. Panel 0-40v, 0-25MA, HF Ammeters 0-2A. Thermometer 70-160F Chrome Front Bezel-all £2.25.

POWER SUPPLIES

New ex GPO 250v, 24vo/p ±2v 500 M/A £6.00. VALVES :--

New Mullard & Brimar 6 CH6, 4 for £1. EF83 3 for £1. PC97 + EF 80, 2 for £1.

NICADS :---

All flow	
6 × 1.2v (- 7.2v) 250M/AH	£1-75
5 × 1.2v (6v) 50M/AH	£1-00
2-4v 20AH Vented 8" H 3" Dia.	£6 · 50

Buzzers 12v × 1" × 1" 2 for £1. Min. High Power Motors, 6-12v DC German 11" × 11" £1-25. Ilb new assorted components £1.95.

Vero type boxes $2 \times 4 \times 1''$ 50p $6 \times 3 \times 2''$ £1. Micro Switches 5A 240v c/o Button 10 for £1. Headphones-New ex tank £2-50. New ex Army £2-25. Stereo Slider Controls, 34" long 10K. 50K, 100K, 250K. 3 for £1 20. Bridge Rectifiers 2A 40v 3 for £1 Jackson Slow Motion Drives 6:1 2 for £1-50

Wavechange Switches-New 3 \times IP7W + 2 \times \times IP2W, 4 \times IP10W, Lever Switch IP4W + 2 4P2W-all 75p.

SAE for list new Ex. WD panel meters-all £2-25. Amtron Electronic Kits—Components.

ALL PRICES INCLUDE VAT POST AND PACKING.

'CASTLE <u>ELECTRONICS''</u>

Practical Wireless, July 1978



In case with variable transformer £29.00 pp 86p S2 Drill stand (holds both drills) £18 50 pp 106p S2 DRILL STAND A robust, all metal stand with

ample throat dimensions. Will take both P1 and P2 Drills. £18.50 pp 106p. SUPER 30 KIT 30 tools incl. Drill P1-

without stand. £19.39 pp £1. P1 DRILL £9.67 pp 38p

S1 DRILL STAND £5-13 pp 38p

FLEXIBLE DRIVE SHAFT £5-94 pp 34p

TRANSFORMERS

Continuous a/c 12v. D/C £7 56 pp 81p Variable speed a/c 12v. D/C

£9.50 pp 81p

Drills, Stones, Burrs etc. 40p each. Circular Saw Blades—set of 4 with Arbor $\pounds 3 \cdot 50$ P&P any quantity 25p. Please send 9" \times 4" S.A.E. for leaflet and order form. All prices include VAT

PRECISION

Tel. 01-977 0878

119a HIGH STREET

HAVE YOU TRIED SPADE DRILLS

and other soft materials? No clogging - cooler -cleaner holes - there's a range of sizes, 0-1 to 2-5mm

for printed circuit boards

PETIT

E

TEDDINGTON MIDDLESEX TWIL 8HG

S2

HIGH QUALITY AUDIO AND RF **MODULES FOR MUSIC CENTRES** AND OTHER HI-FI EQUIPMENT

Fully aligned—S meter—tuning meter output—Ceramic filters at 10.7 Mhz and 470 kHz—MPX Decoder. This is a complete and fully tested 3 band receiver module with £21.95 AFC and mute.

FM 050 STEREO FET AM/FM TUNER

Similar circuitry to 020 but has a 6-way selector panel with MW LW/ Mono/FM Stereo plus two spare stereo inputs for tape and phono. £21-95

IF 005 HIFI 10-7 MHZ IF STRIP

Complete FM IF strip with MPX Decoder can be used with any mechanically tuned or varicap front end. Has a complete MW/LW Superhed receiver only requiring a tuning capacitor. Fully aligned, same switch configuration as FM 050.

PA 020 STEREO POWER AMPLIFIER

25 Watts RMS per channel

- £9.50
- ✤ Class AB Operation
- ÷ 16 Transistor Circuit
- * Unstabilised supply required
- Tip 34A + Tip 33A Output



- 30 Hz-18KHz @ -1dB
- ★ Output 8 ohm
- ★ Input 50 Kohm

This power amplifier which features an advanced designed design with complemen-tary pair of transistors in class AB oush pull. Will comfortably deliver 25 watts per channet. And comes complete with heat sink.

PR 020 Hi-Fi Preamplifier

The PR 020 is a low noise preamplifier with full bass and treble cut and boost. It has four rotary controls and four specially selected transistors. It is designed to match most high quality power amplifiers.



SW 020 8 Way Selector Panel £3.95

When used in conjunction with PR 020 provides switching for different inputs. Features Mono/ Stereo switch. Loudness/Filter/ Tape replay playback, Phono, Auxiliary + two other inputs. Has PC Board mounting 5 Way Din socket for tape deck.



in. Image rejection 60 dB. Dual gate MOS FETS. £10-9	Õ
UT01 115—150 MHz covers amateur bands, aircraft etc. £10.9	0
IF 15 Narrow band IF amp. Dual conversion 10.7 MHz 455 KHz AM—FM Detector. £13.95	5
MAG 020 Super low noise magnetic pick up amplifier £2.9	5
TX 020 Power Transformer 41 volts RMS at 2.8 amps. £6.9	9
PSV 020 Power supply board. 18 bolts stabilised + 50 volts D.C output £3.9	
The above items are only a small range of the modules we have in stock We also carry knobs, chassis front and rear extrusions, dials to match the FM 020 meters, front ends, cabinets. In fact everything you need to make place of evulpment that not only meets professions standarts but look	*

LIT02 Low poise varican front end 10:7 MHz JE out 88-108 MHz

piece of equipment that not only meets professional standards but looks professional as well. If you would like to see our range please send a SAE + 15p postal order. Prices include VAT and postage.

REED HAMPTON LTD., 19 CHURCH LANE, WALLINGTON, SURREY

Tel: (01) 661 1825/6



45p

Full Illustrated Catalogue . Send 30p For Post & Packing.

Post and Packaging 15p kits/pads/sockets/coolers. 45p for anodised heat sinks MOULDED ELECTRONIC COMPONENTS INT. LTD., 34D QUARRY HILL ROAD TONBRIDGE, KENT. PHONE: 8732 365810

10p

Larger range of transistor pads and insulating bushes in catalogue. All prices include V.A.T.

From.....

.....

MOULDED ELECTRONIC

COMPONENTS INT. LTD.

34d OUARRY HILL ROAD. TONBRIDGE

TO220 INSULATING KITS 5 Washer 5 Buahes Mellnex 20p/Kit Mica 25

KENT PHONE 0732 365010 5 @ 65p 5 @ 75p

Mica 25p/Kit

DIODE CRADLES

RS		VA CLI LON CIAL E	IDON	SVV16	5 6ED). Roai	D,
SEMICONDUCTO AA119 0 20 A5/26 0 45 AAY30 0 13 A5/27 0 50 AAY32 0 15 A5/215 1 25 AAZ13 0 25 A5/216 1 25 AAZ13 0 25 A5/216 1 25 AAZ17 0 25 A5/216 1 25 AAZ17 0 25 A5/210 1 25 AC107 0 75 A5/22 0 0 75 C107 0 75 A5/22 0 0 75 AC107 0 25 AU13 1 70 AC128 0 25 BA148 0 15 AC141 0 28 BA148 0 15 AC142 0 BA148 0 15 AC142 0 BA148 0 15 AC142 0 BA148 0 15 AC142 0 BA155 0 12 AC142 0 28 BA155 0 12 AC188 0 55 BA15 0 12 AC188 0 55 BA16 0 07 ACY18 0 65 BC109 0 13 ACY20 0 65 BC113 0 15 ACY30 1 25 BC114 0 12 AC149 0 70 BC115 0 19 AD149 0 70 BC115 0 19 AD149 0 70 BC115 0 19 AD149 0 70 BC15 0 19 AD161 0 73 BC15 0 19 AF116 0 25 BC35 0 15 AF116 0 25 BC35 0 19 AF139 0 40 BC47 0 10 AF139 0 40 BC47 0 10 AF130 0 45 BC36 0 13 AF211 2 75 BC36 0 11 AF211 2 75 BC36 0 0 11 AF211 2 75 BC36 0 0 11 AF211 2 75 BC36 0 0 1	RS BC159 013 BC167 013 BC170 016 BC171 014 BC172 013 BC177 013 BC177 013 BC177 013 BC177 013 BC178 01 BC178 01 BC178 01 BC178 01 BC178 01 BC183 011 BC183 011 BC183 011 BC183 014 BC213 014 BC214 011 BC236 012 BC227 012 BC37 012 BC37 012 BC38 014 BC38 014 B	BD123 1 50 BD123 1 50 BD131 0.51 BD135 0.35* BD135 0.35* BD135 0.35* BD135 0.35* BD135 0.35* BD138 0.43* BD138 0.44* BD138 0.44* BD182 1.38 BD182 1.48 BD182 1.48 BD238 0.42* BD182 1.48 BD238 0.42* BD182 1.48 BD237 0.30* BD238 0.42* BD240 0.42* BD250 0.5* BD140 0.43* BD250	BFS61 0.25* BFS98 0.25* BFW11 0.900 BFW11 0.900 BFX84 0.38 BFX85 0.41 BFX85 0.41 BFX87 0.35 BFX88 0.32 BFY50 0.28 BFY51 0.28	BZX61 0.20 Series DZY88 0.13 Series CRS/140 0.60 CRS/140 0.60 CRS/140 0.75 CRS/240 0.75 CRS/240 0.75 GJ3M 0.75 GJ3M 0.75 GJ3M 0.75 GJ3M 0.75 GJ3M 0.75 GJ3M 0.75 GJ3M 0.55 MJE320 0.65 MJE320 0.65 MF102 0.30 MF103 0.30 MF104 0.30 MF5A060 40 MF500 40 MF555 0.47 OA7 0.55 OA7 0.55	$\begin{array}{ccccc} 0 & A70 & 0 & 30 \\ 0 & A79 & 0 & 30 \\ 0 & A81 & 0 & 30 \\ 0 & A85 & 0 & 30 \\ 0 & A85 & 0 & 00 \\ 0 & A91 & 0 & 01 \\ 0 & A90 & 0 & 01 \\ 0 & A200 & 0 & 10 \\ 0 & A200 & 0 & 11 \\ 0 & A200 & 0 & 11 \\ 0 & A200 & 0 & 12 \\ 0 & A2200 & 0 & 85 \\ 0 & A2200 & 0 & 0 \\ 0 & A2200 $	OC82 0.75 OC83 0.55 OC122 1.50 OC139 2.25 OC141 2.25 OC170 75 OC171 0.75 OC171 0.75 OC171 0.75 OC201 1.90 OC202 1.95 OC203 1.75 OC203 1.75 OC203 1.75 OC204 1.25 OC205 1.75 OC206 1.75 OC207 1.25 OC208 1.75 OC209 2.25* R2009 2.25* R2009 2.25* R2009 2.25* T1C246 1.30 T1209 0.25 T1P32A 0.75 T1P33A 0.50* T1P33A 0.30 T1P33A 0.35* T1P33A 0.35* T1P335 0.30 T1P335 0.30<	$\begin{array}{ccccc} 25271 & 0.22*\\ 25278 & 0.56*\\ 25278 & 0.56*\\ 271 \times 107 & 0.11*\\ 271 \times 108 & 0.12*\\ 271 \times 300 & 0.13*\\ 271 \times 501 & 0.14*\\ 271 \times 501 & 0.14*\\ 271 \times 500 & 0.13*\\ 10000 & 0.15\\ 10000$	2N697 0.18 2N698 0.30 2N705 0.80 2N705 0.80 2N706 0.12 2N708 0.21 2N708 0.21 2N708 0.21 2N103 0.26 2N1132 0.26 2N1303 0.37 2N1304 0.45 2N1305 0.50 2N1307 0.50 2N1308 0.40 2N147 1.50 2N147 1.40 2N147 1.40 2N147 1.40 2N147 1.40 2N2218 0.33 2N2219 0.42 2N2222 0.25 2N2222 0.25 2N2226 0.53 2N2906 0.25 2N2907 0.25 2N2906 0.25 2N2926 0.13* 2N2926 0.13* 2N2926 0.13* 2N2926 0.13*	2N3055 0.45 2N3441 0.40 2N3441 0.40 2N3441 0.40 2N3441 0.40 2N3442 0.20 2N3525 0.40 2N3702 0.15 2N3705 0.15 2N3705 0.15 2N3707 0.14 2N3707 0.14 2N3707 0.14 2N3708 0.14 2N3709 0.15 2N3709 0.14 2N3709 0.14 2N3701 0.16 2N3702 0.16 2N3703 0.16 2N3701 0.16 2N3701 0.16 2N3702 0.16 2N3711 1.50 2N3820 0.36 2N3820 0.36 2N3820 0.22 2N3820 0.22 2N4050 0.22 2N4050 0.22 2N4050 0.22 2N4050 </th
VALVES AZ31 110* CBL31 130 ECC814 0.55* CBL31 100* ECC841 0.55* CL33 2.00* ECC841 0.55* CY31 1.00* DAF96 1.00* DAF96 1.00* DF301 0.40* DF301 0.40* DF301 0.40* DF301 0.40* DF301 0.40* DF301 0.40* DK32 2.5* ECH33 2.85* DK96 10* DL92 5.5* DL94 1.20* DL94 1.0* DL95 ECL307	EH90 0.75 EL32 1.50 EL33 3.50 EL41 1.25 EL42 1.75 EL81 1.0 EL84 0.55 EL91 3.52 EL91 3.52 EL95 0.55 EL95 0.55 E	0031 045 0Z4 0.75* PC86+ 045* PC97 1.08* PC97 1.08* PC084+ 045* PC084+ 045* PC284+ 045* PC284+ 045* PC284+ 045* PC780+ 05* PC780+ 05* PC780+ 05* PC780+ 05* PC780+ 05* PC780+ 05* PC7805+ 040* PC7805+ 040* PC7805+ 040* PC7805+ 040* PC7805+ 040* PC183+ 040* PC183+ 040* PC1805+ 040* PL0500 3:00* PL050 3:00* PL050 040* PL050 1:0* PL051 1:2* PL051 1:2* PL051 1:2* PL051 <	PL84† 0 60° PL504/5007 PL504/5007 PL508† 1 60° PL509† 3 60° PK802† 3 60° PY811 0 72° PY82 0 45° PY82 0 45° PY82 0 45° PY83 0 60° PY83 0 60° PY83 0 60° PY831 1 16° PY800/81† PY800/81† PY800/81† 0 92° QV02-6 3 50 QV02-6 3	UCC255 0-50* UCF20 0-75* UCH21 1-20* UCH21 1-20* UCH21 1-20* UCH22 1-20* UCH22 0-50* UCL22 0-50* UCL22 0-50* UC43 1-44* UF41 0-75* UF85 0-50* UF85 0-50* U	6AC7 0-75* 6AG7 0-75* 6AG7 0-73* 6AG7 0-73* 6AK5 0-30 6AK5 0-30 6AK5 0-30 6AM4 2-30* 6AM4 2-30* 6AM5 1-35* 6AM5 2-50* 6AM5 1-55* 6AM5 1-55* 6AU5C 1-55* 6BA7 1-55* 6BA7 1-55* 6BA7 1-55* 6BA7 1-51* 6BA7 1-51* 6BA5 6BA7 1-51* 6BA5 6BA5 1-51* 6BA5 6BA5 1-51* 6BA5 6BA5 1-51* 6BA5 6BA5 1-51* 6BA5 6BA5 1-51* 6BA5 6BA5 1-51* 6BA5 6BA5 1-51* 6BA5 6BA5 1-51* 6BA5 6BA5 1-51* 6BA5 6BA5 1-51* 6BA5 1-51* 6BA5 6BA5 1-51* 6BA	6BR7 4 00" 6BR8† 120" 6BS7 4 00" 6BS7 4 00" 6BW6 3 75" 6BW7 1 12" 6BX76 T 4 96" 6CG7 1 72" 6CG6A 4 05" 6CG6A 4 05" 6CG6A 4 05" 6CG7 1 72" 6CH6 4 42" 6CH6 4 47" 6CH6 4 71" 6CH6 4 71" 6CH6 4 71" 6CH6 4 71" 6CH6 4 71" 6CH6 4 75" 6CH7 1 60" 6F28 1 60"	6L6GC 1.75* 6N2P 0.75 6N2P 0.75 6N2 0.75 6N2 0.75* 6N2 0.80* 6R7 0.80* 6SA7 0.70* 6SA7 0.70* 6SN7GT† 0.70* 6SN7<0.75*	12AU5 0:50* 12AV5 0:60* 12AV7 2:64* 12AY7 0:52* 12AY7 0:52* 12AA77 0:52* 12BA7 1:00* 12BA5 0:50* 12BH71 0:60* 12BF1 4:00* 30C15 1:20* 30C15 1:20* 30C15 1:20* 30C15 1:20* 30C15 1:20* 30C11 1:20* 30C1 1:50* 90AG 7:26* 90AG 7:26	92AV 7.18 15022 1.80 15022 1.80 15022 1.80 15022 1.80 15022 1.80 15022 1.80 15022 1.80 15022 1.80 8074 1.00 812A 7.36 833A 306 833A 306 872A 1.84 92050 2.95 5554 3.87 5651 3.87 5654 5.58 6146B 5.58 6146A 5.58 6146B 5.28 6146B 5.28 6146B 5.28 8068 5.30 8038 5.30 8138 1.54
INTEGRATED CIF 7400 0.20 7412 0.26 7401 0.20 7413 0.45 7402 0.20 7416 0.40 7403 0.20 7417 0.40 7403 0.20 7417 0.40 7404 0.28 7420 0.25 7405 0.23 7423 0.35 7407 0.55 7423 0.35 7409 0.28 7427 0.35 7409 0.28 7427 0.35 7409 0.28 7427 0.35 7409 0.28 7427 0.35 7409 0.28 7427 0.35 7409 0.28 7428 0.50 7410 0.20 7430 0.50	7432 0-31 7433 0-37 7437 0-42 7438 0-37 7439 0-32 7443 0-32 7444 0-72 7441AN 0-92 74450 0-20 7450 0-20 7451 0-20	2 7474 0 40 7475 0 59 2 7476 0 42 7480 0 60 7482 0 85 7483 1 00 7484 1 00 7486 0 40	7491AN 0:85 7492 0:60 7493 0:70 7494 0:80 7495 0:80 7495 0:80 7496 0:80 7497 3:87 74100 1:75 74107 0:45 74110 0:57 74118 1:89 74118 0:95	74119 2.00 74120 1.10 74121 0.45 74122 0.60 74123 1.00 74125 0.80 74126 0.80 74128 0.80 74128 0.80 74128 0.80 74130 0.80 74134 0.85 74143 3.00 74143 3.00	74145 1.00 74147 2.45 74148 2.06 74150 1.75 74151 0.96 74155 0.90 74155 0.90 74156 0.90 74157 0.96 74159 2.50 74170 2.60 74172 5.00 74173 1.75	74175 1 00 74176 1 00 74178 1 65 74179 1 65 74180 1 85 74190 1 48 74191 1 48 74192 1 25 74193 1 25 74195 1 10 74195 1 20 74194 1 25 74195 1 20 74196 1 20 74197 1 00 74198 2 25	74199 2-25 76013N 1-75* LM309K 1-50 TAA570 2-30* TAA6305 3-50* TBA4800 TBA5200 TBA5200 TBA5300 2-30*	TBA550Q TBA560CQ 3 22* TBA673 219 TBA700 152* TBA720Q 2.30* TBA750Q 2.99* TCA760A 1.38*	DIL Sockets ⁸ PIN 0·15 14 PIN 0·15 16 PIN 0·17
BASES CRT'1 B7G skirled 0.15 1CP31 B7G skirled 0.13 2AP1* B9A unskirled 0.13 2BP1* B9A unskirled 0.13 3BP1 Int Octal 0.20 Nuvietor base 0.55 3GP1 Jutotal 0.15 Aprin DIL 0.15 14 pin DIL 0.15 14 pin DIL 0.17 Valve screening 3KP1* Valve screening 3KP1*	31.00 56 8.50 56 9.00 56 5.00 56 7.00 57 7.00 51 8.00 D 8.00 D 8.00 D 10.00 D	P1 25:00 P7 25:00 P11 25:00 P11 25:00 P14 10:00 P14 5:00 P14 5:00 P14 5:00 P15A 5:00 G7-5 25:00 G7-5 25:00 G7-5 25:00 G7-32 36:00 H3-81 31:00 H3-81 31:00 CR97* 5:00 CR97* 5:00 GR30* 10:00	VCR138A* 12: VCR139A* 8- VCR517A* 10 VCR517B* 6- VCR517C* 6- Tube Bases 0 *=Svrplus VAT 8%	00 00 00	SUITA	BLE FO	STOCK		
Terms of business: CWO. post VAT. Others 8%, † Indicates c ruling at time of despatch. Acc packing £1 on credit orders. Or QUOTATIONS FOR ANY TY	age and packi heap quality v ount facilities rer 10,000 types	ng valves and sen ersion or surplus, available to appro of valves, tubes (but also available ved companies w	iby leading UK a ith minimum or	and USA manufa ler charge £10. C	cturers. Price		elephone 01- elex 946708	677 2424 E & O.E.

79



Handy size Reels & Dispensers OF THE WORLD'S FINEST CORED SOLDER TO DO A PROFESSIONAL JOB AT HOME

Ersin Multicore Solder contains 5 cores of non-corrosive flux that instantly cleans heavily oxidised surfaces and makes fast, reliable soldering easy. No extra flux is required.





Practical Wireless, July 1978

Relays, Min. sealed 12v dc type 4 pole changover 55p, Min 24v dc 2 pole c/o 3 amp contacts 55p, Min sealed 220V AC 2 pole c/o 40p, Open type 12v dc 4 pole c/o 50p, 4 pole reed relays N/O 20p.

SSp., Min seeled 220V A C 2 pole c/o 40p. Open type 12v dc 4 pole c/o 50p. 4 pole reed relays N/O 20p. CRYSTALS, 300khz 40p. 4-43 mhz CTV 45p. Aerosol 'Touch up' paint one colour yellow/ grey, 6oz can 35p. 50V A C cam units, motor switching ine c/o micro switches, supplied with capacitor for 240V AC use £1.95p plus 35p postage. Belling Lee L4305 masthead amplifiers and mains power unit, new but only for group A UHF £7.50p. TRANSFORMERS, 6-0-6v 100ma, 9-09 T5ma, 12-012 50ma 75p each, 12-012 100ma 95p. 12-50ma 85p, 1:1 triac/xenon pulse transformers 30p, CHOKES 6MC 3 Amp 20p. U.H.F. TY 50ma 85p, 1:1 triac/xenon pulse transformers 30p, CHOKES 6MC 3 Amp 20p. U.H.F. TY 50ma 85p, 1:1 triac/xenon pulse transformers 30p, CHOKES 6MC 3 Amp 20p. U.H.F. TY 50ma 85p, 1:1 triac/xenon pulse transformers 30p, CHOKES 6MC 3 Amp 20p. U.H.F. TY 50ma 85p, 1:1 triac/xenon set the set of the set of

TERMS: cash with order, (or official orders from colleges etc). Postage 30p unless other wise shown, overseas post at cost. VAT inclusive prices. S.A.E. for lists.

Progressive Radio, 31 Cheapside, Liverpool L2 2DY. Tel: 051 236 0982.

ы

simplify those smaller jobs. PC115 provides 6.4 metres approx. of 0.71 mm solder for fine wires, small components and printed circuits. PC115 69p Or size 19A for kit wiring or radio and TV repairs. 2.1 metres approx. of 1.22 mm solder. Size 19A

SOLDER MIG

97n

r lists

29p* 45p* 16p 60p* 21p* 29p* 75p 69p

15p 39p 8p 25p etc etc.

World Radio History



SMALL ADS

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.80 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846)

Receivers and Components

ELECTRONIC COMPONENTS since 1966. Price list and 50 mixed resistors FREE on request. J. R. Hartley, 78B High Street, Bridgnorth, Salop WV16 4DY.

TRANSISTORS, RESISTORS, CAPS, POTS, Plugs & Sockets, Zeners, TTL, Cable, Boxes, All at very good prices. 65 Railway Road, Leigh, Lancs. Telephone Leigh 679575.

BRAND NEW COMPONENTS BY RETURN.

Electrolytic Capacitors 16V, 25V, 50V.
0-47, 1-0, 2-2, 4-7 & 10 m/ds.—5p. 22, 47—5ip. (50V—6p). 100—7p. (50V—8p).
22, 47—5 p. (50V—6p). 100—7p. (50V—8p). 220—8p. (50V—10p. 470—11p. (50V—16p). 1000/15V—15p. 1000/25V—18p. 1000/50V—22p.
Subminiature bead tantalum electrolytics.
Subminiature bead tantalum electrolytics. 0-1, 0-22, 0-47, 1-0 @ 35V, 4-7 @ 6-3V-8p. 2-2/35V & 4-7/25V-9p. 10/25V, 15/16V-12p. 2-2/35V & 4-7/25V-9p. 10/25V, 15/16V-12p. 14p.
22/16V, 33/10V, 47/6V, 66 at 10V W 31-14P
Mullard Miniature Ceramic E12 Series 63V 2%. 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p.
Vertical Mounting Ceramic Plate Caps. 50V. El2 22 pf.—1000 pf. E6 1500 pf.—47000 pf.—2p
Polystyrene E12 Series 63V. Hor. Mounting. 10 pf. to 1000 pf3p. 1200 pf. to 10000 pf4p.
to the temploreness apply Vante Mary FA Sarias
01 to 1-4p. 15, 22-5p. 3, 47-8p. 68-1p. 10-14p. 15-20p. 2.2-24p.
Mutan (Bolyastar) Film 100V, Vertical Mtg.
001, 002, 005-3p. 01, 02-4p. 04, 05-3p.
Miniature Film Resistors Highstab. El2 5%. 0·125 watt 10Ω to 2M2Ω
0.250 watt Ω to I0MO, (10% over IM)
0.500 watt 10 Ω to 2M7Ω.
IN4148-3p, IN4002-5p, IN4006-7p, IN4007-8p
BC107/8/9, BC147/8/9, BC157/8/9, BF194 & 7-9p.
20mm. fuses -15, -25, -5, 1-0, 2-0, 3-0 & 5A-3p. Printed Circuit Holders for 20mm. fuses-5p.
Post 10p (Free over £4). Prices VAT inclusive.

THE C. R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 ORN

ASSORTED small Japanese L.F. Trans-formers 20 for £1.25. Assorted Nuts, Bolts, Washers, Eyelets, Self Tapping, Self Cut-ting Screws, A real bargain 11b weight £1.75. Assorted Ceramic Capacitors 100 for £1.00. Assorted Polystyrene Capacitors 100 for £1.50. Assorted Polyester Capacitors 100 for £2.00. Assorted Carbon and Carbon Film Resistors 100 for £1.00. Assorted Wire-wound Resistors 100 for £2.00. Assorted Transistors/Zeners, Diodes, all marked, 100 for £2.00. All above prices include VAT and Postage. T. Powell, 306 St Paul's Road, London N.1. Telephone 01-226 1489.

S'CONDUCT'S		CAPACITORS
BC 107 \$p	BU 208 £1 .90	0-1/600v 5p
BC 132 10p	BY 127 10p	25/25v 5p
BC 147 8p	TIP 29 35p	
BC 2048 1p	1N 645 11p	W/W RESIST'S
BC 351 11p	1S 940 4p	2.5W Axial 12p
BD 131 34p	INT'G'D C'C'T	TS 5W Radial 6p
BD 138 37p	LM 741 8P DIL 1	19p 10W Axial 9p
BT 106 £1-10	M252 B1 AA £7	00 15W Radial 11p
BU 205 £1-89	(Rhythm Gen.)	
BRIDGE RECT.	15 B05 (1A /50y)	16p Min Order £2. p&p
25p. Prices Includ	In VAT	SAE FOR LISTS
Export and Whol		elcome
K & A DISTI		BARKBY ROAD,

TIRRO ELECTRONICS the mail order divi-sion of RITRO ELECTRONICS UK offers a wide range of components for the amateur enthusiast. Large SAE or 20p brings list. GRENFELL PLACE, MAIDEN-HEAD, BERKS SL6 1HL.

CONDITIONS OF ACCEPTANCE **OF CLASSIFIED ADVERTISEMENTS**

Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.

7. The publishers reserve the right to refuse or withdraw any advertisement. 3. Although every care is taken, the Publishers shall not be liable for cierical or printers' errors or their consequences.

VALVES

Y ALV ED Radio - T.V. - Industrial - Transmitting Projector Lamps and Semiconductors We Dispatch Valves to all parts of the world by return of post, Air or Sea mail, 2700 Types in stock, 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves, Projector Lamps and Semiconductors.


COX RADIO (SUSSEX) LTD. Dept. P.W. The Parade, East Wittering, Sussex PO20 8BN

West Wittering 2023 (STD Code 024366)

TRANSIST					
I MARINA IA .	ORS	E 1N4004	6p	7410	19p
ACY21 54p	TIS43 43p	IN4006	7p	7411	26 p
ACY21 54p ACY22 64p AFZ12 260p	ZTX300 14p	IN4148	3p	7413	41 p
AFZ12 260p	ZTX450 15p	IC		7420	18p
A SY501200	ZTX500 17p	NE555	28p	7430	18p
BC107 9p	2N3053 24p	709	55p	7432	37p
	2N3055 65p	741	45p	7437	37p
BC109C 11P	Diodes	TTL		7442	75p
BC154 19D	AAZ15 150	7400	15p	7446	108p
BC214 17p	AAZ15 15p BY238 20p	7402	16p	7474	37p
BC413 18p	1 114814 49	1400	16p	7475	43p
BFY51 23p	IN4001 5p	7404	25p	7476	37p
BSX20 24p	IN4002 5p	7407	41p	7490	36p
OC35 150p	IN4003 6p	7408	23p	7493	36p
ELECTROL	TIC CAPA	CITIOR	5 (V/	UF) 6.	3v/470
5p; 1000 13p	; 2200 14p;_33	00 15p;4	700 20	p;10V/	10, 47,
220 6p; 470	9p; 2200 15p;	3300 16); 16V	/100, 21	0 8p ;
330, 470 16p;	1000 15p: 25	V/22, 33 🕻	p; 100	220 80	330.
470 12p; 1000) 18p: 35V/47,	100, 7p,	220, 33	15p:	504/1;
22, 33 7p; 47,	100 8p; 330, 4	70 16p; 10	00 230		
DIAC, D32 2	Sp, THERMIS	STOR, C.	24 20 p	•	
THYRISTO	R TIC106F 25	, BR 139	4 p .		
RESISTOR	S CARBON P	3 L.M.			
0.25W 2.20	-4 7 MO E24	P			
0.5W 2.2N	-4 7 MO E12	1.3 D .	80.		
METAL FILI	TIC CAPA ; 2200 14p; 33 9p; 2200 15p; 25) 18p; 35V/47, 100 8p; 330, 4 5p, THERMI3 R TIC106F 25 8 CARBON 1 -4 7 MO E12 -4 7 MO E12 M CAPACIT 0082 3p. 01,	010 µF/1	60V	0.092	·037.
0055, 0068,	0082 3p. 01.	012, 01	5, 102	z, 1033,	22 50
-047, -056 4p	0082 3p. 01, 068, 082, 56, 68 7p. 82	1.5 18-	5, 18	p, .z, .	22 3 D.
-33, -47 €p.	50, 08 /p. 82	, 1°5 19p.			
Mall order on	ly. P. & P. 25p	Prices in	ciude	VAT.C	.w.o.
STE Ltd., S	ystem Technic k Hill, Edenbri	ues (Elec	tronic	s) Ltd.,	PW2,
Dafield, Stic	k Hill, Edenbri	dge, Ken	t, TN8	SNL.	
				P	
11p. 2N545	Sp. ACI28 14 58 31p. UT4 50 BR100	6 19p. T 12p. D32 . 741P 2	1543 2 22p. 10p. F	OA20 OA20 Postage	0 5p.
OA202 5p.	ists cheques				-
OA202 5p. S.A.E. for 1 to:	ists cheques SELTI	RONIC	s		
OA202 5p. S.A.E. for 1 to:	ists cheques SELTI	RONIC	s		
OA202 5p. S.A.E. for 1 to:	ists cheques	RONIC	s		
OA202 Sp. S.A.E. for I to:	ists cheques SELTI	RONIC	s		
OA202 Sp. S.A.E. for I to:	ists cheques SELTI	RONIC	s		
OA202 Sp. S.A.E. for I to: 9, Rodi	ists cheques SELTI ney Garder	RONI(ns, Brai		, Esse	x.
OA202 Sp. S.A.E. for I to: 9, Rodi	ists cheques SELTI ney Garder	RONI(ns, Brai		, Esse	x.
OA202 Sp. S.A.E. for I to: 9, Rodi	ists cheques SELTI	RONI(ns, Brai		, Esse	x.
OA202 Sp. S.A.E. for I to: 9, Rodi	SELTI SELTI ney Garder	RONIG III, Brai	CS ntree E TI	MER	x. KIT
OA202 Sp. S.A.E. for I to: 9, Rodi	ists cheques SELTI ney Garder LOCK/API Switche	RONIG ns, Brai PLIANG	ET	MER	x. KIT
OA202 Sp. S.A.E. for I to: 9, Rodi	ists cheques SELTI ney Garder LOCK/API Switche on and c	RONIC ns, Brai PLIANC s any app off at pres	ETI	MER	KIT a day.
OA202 Sp. S.A.E. for I to: 9, Rodi	ists cheques SELTI ney Garder LOCK/API Switche on and c Kilt cc	RONIC ns, Brai PLIANC s any app off at pres	ETI	MER of up to 1230	KIT o 1kW a day. Clock/
OA202 Sp. S.A.E. for I to: 9, Rodi	Ists cheques SELTI ney Garder	RONIG s, Brai PLIANG s any app off at press ce Time	ETI liance AY-5- r I.C.	MER of up to 1230	KIT o 1kW a day. Clock/ LED
OA202 Sp. S.A.E. for I to: 9, Rodi	SELTI ney Garden LOCK/API Switche on and c Appilan display.	RONIC s, Brai PLIANC s any app off at pres ontains: ce Time mains	ETI liance et time AY-S- sup	MER of up to 1230	x. KIT o 1kW a day. Clock/ LED isplay
OA202 Sp. S.A.E. for I to: 9, Rodi	SELTI ney Garder LOCK/API Switche Applian display, drivers,	RONIC ns, Brai PLIANC s any app off at pres ontains: ce Time mains switches	liance AY-5- r I.C. sup LEDs	of up to 1230 UNER	KIT o 1kW a day. Clock/ LED isplay PCBs
OA202 Sp. S.A.E. for I to:	SELTI ney Garder LOCK/API Switche on and C Applian display, and fuil	PLIANO sany app off at press matains: ce Time mains switchess instructio	liance et time AY-5- r I.C. sup LEDs	of up to 1230 0 5" ply, d , triac, ONLY 3	X. KIT o 1kW a day. Clock/ LED isplay PCBs E13-75
OA202 Sp. S.A.E. for I to:	SELT SELT SELT LOCK/API Switche on and of Applian display, drivers, and full x 131 x 7 fum	CLIANCE s any app off at pres ontains: ce Time mains switches instructio	liance at time AY-S- r I.C sup LEDs ons. crylic	of up to 1230 0 5" ply, d , triac, ONLY 3	KIT hikW a day. Clock/ LED isplay PCBs £13-75 £2-20
OA202 Sp. S.A.E. for I to:	SELTI ney Garder LOCK/API Switche on and C Applian display, and fuil	CLIANCE s any app off at pres ontains: ce Time mains switches instructio	liance at time AY-S- r I.C sup LEDs ons. crylic	of up to 1230 0 5" ply, d , triac, ONLY 3	X. KIT o 1kW a day. Clock/ LED isplay PCBs E13-75
OA202 Sp. S.A.E. for I to:	SELTI SELTI DOCK/API Switche Switche KIT cc KIT cc KIT cc Applian display, drivers, and full x 131 x 71mm n above drilled	RONIC ns, Brain PLIANC s any app fif at pres mains: ce Time mains: switches instructions witches witches instructions witches	liance at time AY-S- r I.C sup LEDs ons. crylic	of up to 1230 0 5" ply, d , triac, ONLY 3	KIT o 1kW a day. Clock/ LED isplay PCBs £2:20 £2:50
OA202 Sp. S.A.E. for I to:	SELTI SELTI SELTI Switche on and of All aplay, drivers, above drilled 55° 7 sec. LEI	PLIANO s any app off at presonants ce Time mains sinstructic with red A ready for D Display	LEDs ons. crylic KIT	of up to 1230 0 5" ply, d , triac, ONLY 3	x. KIT a day. Clock/ LED isplay PCBs £13-75 £2-20 £2-50 £1-50
OA202 Sp. S.A.E. for I to:	SELTI SELTI SELTI LOCK/API Switche Switche Chi T cc Ki T cc Ki T cc Applian display, drivers, and full a above drilled 55" 7 seg. LEI	PLIANO s any app off at pres intains: ce Time mains switches instruction with red A ready for D Display e Timer 1.	LEDs crylic KIT	MER of up to sonce 1230 , 0 5" ply, d , triac, ONLY s window	x. KIT o 1kW a day. Clock/ LED isplay PCBs £1:50 £4:85
OA202 Sp. S.A.E. for I to:	SELTI mey Garder EOCK/APPI Switche on and of Applianc above drilled of 7 so LEE lock Applianc	PLIANO s any app off at pres intains: ce Time mains switches instruction with red A ready for D Display e Timer 1.	LEDS crylic KIT C. Control	of up to so once 1230 , triac, ONLY a window	x. KIT o 1kW a day. Clock/ LED isplay p2:20 £2:50 £1:00 £4:85 £1:00
OA202 Sp. S.A.E. for I to: 9, Rodu 24 HR. C 24 HR. C U127 Dual 0 Mhile box 58 While box 88 DL727 Dual 0 AY-5-1230 CL LM3911 Ther	SELTI SELTI SELTI SUBJECT Source	PLIANO s any app off at pres intains: ce Time mains switches instruction with red A ready for D Display e Timer 1.	LEDs crylic KIT C. 34	MER of up to sonce 1230 - , triac, ONLY s window	x. KIT o 1kW a day. Clock/ LED isplay PCBs £1:50 £1:50 £1:00
OA202 Sp. S.A.E. for I to:	SELTI SELTI SELTI SUBJECT Source	PLIANO s any app off at pres intains: ce Time mains switches instruction with red A ready for D Display e Timer 1.	LEDs crylic KIT C. 34	of up to so once 1230 , triac, ONLY a window	x. KIT o 1kW a day. Clock/ LED isplay PCBs £1:50 £1:50 £1:00
OA202 Sp. S.A.E. for I to: 9, Rodu 24 HR. C 24 HR. C U127 Dual 0 Mhile box 58 While box 88 DL727 Dual 0 AY-5-1230 CL LM3911 Ther	SELTI SELTI SELTI Seltan Switche Switche Switche Switche Star Site Star Star Star Star Star Star Star Star	PLIANO s any app off at pres intains: ce Time mains switches instruction with red A ready for D Display e Timer 1.	liance et time AY-S- crylic KIT C- control 38 24	MER of up to sonce 1230 - , triac, ONLY s window	x. KIT o 1kW a day. Clock/ LED isplay PCBs £1.30 £2.20 £2.50 £1.50 £1.60 £1.00) £1.00)



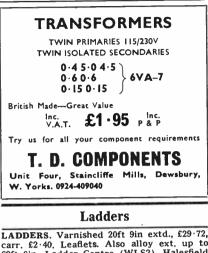COMPONENTS FOR P.W. PROJECTS. Components lists with prices available for P.W. projects from October 1977 onwards. Send SAE stating project and month of publication (maximum four project and month of publica-tion (maximum four projects per SAE). Lists sent by return together with ACE order form/catalogue. ACE MAILTRONIX, Tootal Street, Wakefield, W. Yorks WF1 5JR.



carr. £2.40, Leaflets. Also alloy ext. up to 62ft 6in. Ladder Centre (WLS2), Halesfield (1) Telford. Tel: 586644. Callers welcome.

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

Books and Publications

SIMPLIFIED TV REPAIRS. Full repair instructions individual British sets £4-50, request free circuit diagram. Stamp brings details unique. TV Publications (Ause PW), 76 Church Street, Larkhall, Lanarkshire.

RADIO BOOK SERVICE
WORLO RADIO TV HANOBOOK 1978 Edition £8-25
A Practical Introduction to Orgital IC's
28 Tested Transistor Projects (R. Torrent)
How to build your own Metal & Treasure Locators (F. G. Rayer)
Fun & Games with your Electronic Calculator (J. Vine)
Radio Antenna H'book for Long Olistance Reception
Servicing Transistor Radio Receivers
Solid State Short Wave Receivers for Beginners S.A.E. FOR FULL LIST
4 CHILCHESTER COURT, WICKHAM RD, BECKENHAM KENT BR3 2QW

YOU CAN'T HELP BUT MAKE MONEY. If you follow the planned and detailed in-formation on how to start your own busi-ness rewinding Armatures, set out in the new manual which is profusely illustrated and leads you through easily understood stages of fault diagnosis, taking data, test procedures, laying down new windings, where to obtain work, how to cost jobs etc. NO PREVIOUS ELECTRICAL KNOW-LEDGE REQUIRED, Complete instruction manual £4, plus 30p P&P. CWO. Copper Supplies, 102 Parrswood Road, Withington, Manchester 20. Dept. PWB.

THE DALESFORD SPEAKER BOOK by R. F. C. Stephens.

This book is a must for the keen home constructor. Latest technology DIY speaker dealgns. Contains fuil plans for infnite baffle and reflex dealgns for 10-100 watts, also unusual contre-bass system for those with want Hi-fi be "Heard and not seen". 51 = 51 (52 ° Dhost naid, \$5 Overseas)

VAN KAREN PUBLISHING 5 SWAN STREET WILMSLOW CHESHIRE

Service Sheets

SERVICE SHEETS, Radio, TV etc, 10,000 models. Catalogue 24p, plus SAE with orders, enquiries. Telray, 154 Brook Street, Beneter BP, 719 Preston PR1 7HP.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc., 75p plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S., 190 King's Road, Harrogate, N Yorkshire. Tel: (0423) 55885.

Service Sheets

SERVICE SHEETS - COLOUR TV SERVICE MANUALS Service Sheets for Mono TV, Radios, Record Players and Tape Recorders 75p. Please send large Stamped Addressed Envelope.We can supply manuals for most makes of Colour Television Receivers by return of post. B.R.C. PYE ECKO PHILIPS ITT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVICTA FERGUSON H.M.V. MARCONI AND MANY MORE

Let us quote you. Please send a Stamped Addressed Envelope for a prompt reply. Also comprehensive T.V. repair manuals by J. M. Court, S.A.E. for details. MAIL ORDER ONLY

port.

ings, Sussex.

Miscellaneous

G. T. TECHNICAL INFORMATION SERVICE 10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON WIR 1PA

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo, etc. With free fault-finding guide, from 50p and SAE. Catalogue 25p and SAE. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

Wanted

"RADIO AND TELEVISION SERVICING" books wanted from 1964-65 edition up to date. £3.00 plus postage paid per copy by return of post. Bell's Television Services, 180 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

WANTED. Goodman's Loudspeaker unit type Axiom 80. Whayman, 95 Elizabeth Avenue, Little Chalfont, Amersham, Bucks.

Aerials

ANTI-TVI TRAP DIPOLES

CUT OUT TV1 TX-ing and SWL-ing, MODELS:— SWL, £29.81; 500 Watt or SWL, £41.06. Aerial Matching Unit 500 Watt & SWL 10-160 metres inc. Shipping Band, £16.25. Shipping band, £18.49. Inc. VAT and P & P. Send 10" × 7" 121p s.a.e. and 3 × 9p stamps for details, aerial article, test reports, testimonials G2DYM

LAMBDA, WHITEBALL, WELLINGTON, SOMERSET

Electrical

STYLI-Illustrated equivalents (List 28) also cartridges, leads, etc. Superb quality and service at lowest prices: Fully guaran-teed, free for SAE from FELSTEAD ELEC-TRONICS (PW), Longley Lane, Gatlet, Cheadle, Cheshire SK8 4EE.

KNOBS blue nylon s_8 " long, $\frac{1}{2}$ " dia, fit $\frac{1}{4}$ " D flat shaft. £4.80 100 4% discount per 100 to 40% max. 20p per 100 p&p, 1,000+ post free. Scarle, 23 Hardwicke Road, Reigate, Surrey. Reigate 45004.



ATTENTION SWLs & DXers superior aerial wire 20swg, copper plated, steel core, tough pvc insulation. 4p per metre + 2p per metre carr. AMTEST, 55 Vauxhall Street, Worcester WR3 8PA

LARGE SUPPLIER OF SERVICE SHEETS All models at 75p PO/Cheques plus s.a.e. Except Colour and Car Radios. Free TV fault finding chart or TV list.

C. CARANNA 71 Beaufort Park, London NW11 6BX

01-458 4882

For Sale NEW BACK ISSUES of "PRACTICAL WIRE-

LESS" available 65p each post free. Open P.O./Cheque returned if not in stock-Bell's Television Services, 190 Kings Road,

SEEN WHISTONS CAT? 5000 odds and ends. Mechanical/Electrical Cat free. WHISTON (Dept. PW), New Mills, Stock-

PW VIDEOWRITER. Cased, perfect, £110 ono. Heathkit 1M-102 DVM, £190 ono.

BACK ISSUES. From 1957 PW, PT, RC, 25p.

ELECTRONIC KITS-SAE for new catalogue, and clearance list of obsolete kits. AMTRON UK, 7 Hughenden Road, Hast-

LOGIC PROBE, suitable TTL/CMOS 5-15V indicates Logic states and Trigger Pulses £12 inc. C. Marshall, 22 Oakfield Road, Croydon, Surrey CRO 2UA.

Asthall Leigh 241. Evenings.

Plus postage. Amersham 22434.

Harrogate, N. Yorks, Tel: (0423) 55885.

Strictly by return.

EX MINISTRY EQUIPMENT Aerial Rotation Motor units, complete with Remote Position Indicator connectors and Data. Transistor Curve Tracers. DC Motors. 5V DC Stabilised Power Supplies. Thumb Wheel Switches. Ten Turn Potentiometers. DC Milliampmeters. Lever Switches. Seven Segment Gas Displays. Terminal Blocks. 12 Way Cable. 100 Way Cable. 240V Solenoids. Push Buttons. Odd Items of Test Equipment. Aircraft Instruments and Equip-ment. Lots of Items in Stock. 9" × 3" S.A.E. For List. Mail Order Only. Eldun Electronics, 31 Alexander Drive, Timperley, Cheshire, WAIS6NF.

OUTSTANDING 2200 HI-FI FM TUNER. Latest silicon superhet design, Varicap Tuning, Full Coverage 88-102 MHZ, Ideal for Push button/Manual tuning. Supplied Built & Tested with full instructions only £9.95 (P&P 50p). GREGG ELECTRONICS, 86-88 Parchmore Rd, Thornton Heath, SHIFFRY.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from P.V.C. faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p, chassis punching facilities at very competitive prices. 400 models to choose from, free literature (stamp would be appreciated). BAZELLI, Dept No 25. St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

			/PA/MUSIC
guara with turne boxes watt	superb treble, b ntee. Unbeatab separate treble, d if not obsolute great sound, r 2 In. speakers a	ass. Overdriv le offer at £3 bass per ch ly delighted w obust constru £22:58.	re, slimline, 12 months 39. Also twin channel annel £48. Money re- vithin 7 days. Also fuzz uction £6-60. Also 100
All ir	clusive of P.P	. Send cheq	ue or P.O. to:
	62 THORNCLI	SON AMPLI	DUKINFIELD.
Wev	ould like you t	o know that w	ve make-
* S * P	EC Cabinets pecial cabinets rototype printe strument pane	d circuits	
We	also have a c	Uantity	GB3/AT Cabinet
punc	hing service, a	and undertai	
		ELECTRO	
			field S18 3BD
		el: (0742) 669 (Refundable)	
	LOS	ING I	DX:
wh	istles and cw	with a Tur	DIG it OUT from hable Audio Notch hypassed when off,
NO	LONG WA	-6 MHz rea	0 KHz Converter, ceiver, only £8.80.
WH	ERE's the RA	ARE DXII	MHz, 100, 25 KHz
Cal	ibrator, marke		
Cal MSF	60 KHz T	IME REC	EIVER gives you
Cal MSF SEC	60 KHz T	IME REC	EIVER gives you utput for MONTH.
Cal MSF SEC DA EXP	60 KHz T CONDS, MINU TE and YEAR LORE VLF.	IME REC JTES and or , ferrite rod	EIVER gives you
Cal MSF SEC DA EXP £9 MUS	60 KHz T CONDS, MINU TE and YEAR LORE VLF. 70. SICAL DOO	IME REC JTES and or ferrite rod 10-150 K RBELL?	EIVER gives you utput for MONTH, I, agc, only £13.70. Hz receiver only 19 tunes or PRO-
Cal MSF SEC DA EXP £9 MUS GR	60 KHz T CONDS, MINU TE and YEAR LORE VLF. 70. GICAL DOO AM YOUR (IME REC JTES and ou ferrite rod 10-150 K RBELL? I DWN, just	EIVER gives you utput for MONTH, I, agc, only £13.70. Hz receiver only 19 tunes or PRO- needs bell trans-
Cal MSF SEC DA EXP £9 MUS GR for £17	60 KHz T CONDS, MINU TE and YEAR LORE VLF. 70. CAL DOO AM YOUR (mer and spea 90.	IME RECI JTES and ou , ferrite rod 10–150 K RBELL? I DWN, just ker, surpris	EIVER gives you utput for MONTH, I, agc, only £13-70. Hz receiver only 19 tunes or PRO- needs bell trans- se guests for only
Cal MSF SEC DA EXP 69 MUS GR for £17 SIG. Ecc	60 KHz T CONDS, MINI TE and YEAR ADRE VLF. 70. GEAL DOO AM YOUR (mer and spea 90. GEN. 10-200 h eosy-assemb	IME REC JTES and ou , ferrite rod 10–150 K RBELL? I DWN, just ker, surpris KHz, sine/s ly kit includ	EIVER gives you utput for MONTH, I, agt, only £13-70. Hz receiver only 19 tunes or PRO- needs bell trans- se guests for only square, only £9-80. Is all ports printed
Cal MSF SEC DA EXP 29 MUS GR for £17 SIG. Eoc circ	60 KHz T CONDS, MINI TE and YEAR LORE VLF. 70. ICAL DOO AM YOUR (mer and spea '90. GEN. 10-200 h eosy-assemb uit, case, poi	IME RECI JTES and ou ferrite rod 10-150 K RBELL? 1 DWN, just ker, surpris KHz, sine/s ly kit includ stoge etc.,	EIVER gives you utput for MONTH, , acc, only £13·70. Hz receiver only 19 tunes or PRO- needs bell trans- se guests for only square, only £9·80. les all parts printed instructions money
Cal MSF SEC DA EXP 29 MUS GR for £17 SIG. Eoc circ	60 KHz T CONDS, MINI TE and YEAR LORE VLF. 70. SICAL DOO AM YOUR (mer and spea 90. GEN. 10-200 h eosy-assemb uit, case, poi k assurance so	IME RECI JTES and ou ferrite rod 10-150 K RBELL? 1 DWN, just ker, surpris KHz, sine/s ly kit includ stoge etc.,	EIVER gives you utput for MONTH, , acc, only £13-70. Hz receiver only 19 tunes or PRO- needs bell trans- se guests for only square, only £9-80. les all parts printed instructions money OW.

MARDENBROOK (ELECTRONICS) LTD will construct electronic projects, e.g., wiring of units-p.c.bs assembly, etc. Please write to us at Concept House, 3 Dene Street, Dorking, Surrey.

100 Resistors 75p					
‡₩ 5% c/FiLM 2·2 Ω-2·2M Ω (E12) 10 each of any value					
Send stamped envelope for FREE SAMPLE					
C60 CASSETTES 30p C90 CASSETTES 45p All prices include VAT. Quantity Discounts 10 Units 5%	All Cassettes in Plastic Case with Index and Screwed Assembly. Add postage 10p in £1. SALOP ELECTRONICS 23 WYLE COP,				
50 Units 7% 100 Units 10%	SHREWSBURY. Tel. 53206				

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' Hardware. Printed circuit boards, top quality for individual designs. Prompt service. Send 25p for catalogue from:

RAMAR CONSTRUCTOR SERVICES Masons Road, Stratford-on-Avon, Warwicks Tel: 4879

CRYSTALS brand new 0.002% precision HC18/U wire leads, £2.95 each, UK post paid, no VAT: 4.0, 5.0, 6.0, 7.0, 8.0, 10.0, 10.7, 18.0, 20.0, 48.0, 100.0MHz. Also 100kHz/HC13 and 1.0MHz 0.005%, wires or pins, £3.25. 455kHz/HC6 £3.55. Any freq 2.5.180MHz, made 6 weeks, £3.50. Also AM/CW/SSB Communication Receiver low-cost modules and kits New range being Cost modules and kits. New range being prepared. Send SAE for details when ready. P. R. GOLLEDGE ELECTRONICS, Merriott, Somerset TA16 5NS. Tel: 0460 73718.



83

RECHARGEABLE BATTERIES

*AA' pencell (HP7) £1 32: Sub 'C' £1 64; 'C' (HP11) £2:43; 'D' (HP2) £3 56; PP3 £4.98, Matching chargers £6:98 each except PP3 charger £62. Charging holders, 4 cells only 80p, Prices include VAT. Add 10% post package and insurance orders under £20 5% over £20. SAE for full details plus 75p for 'Nicket Cadmium Power' booklet. 250/12 volt inverters now available. Mail Orders to Dept. PW, SANDWELL PLANT LTD., 201 Monmouth Drive, Sution Coldfield, West Midlands. Tel: 021-354 9764, Callers to T.L.C., 32 Craven Street, Charing Cross, LondowWC2.

ENAM	URE & COIL WINI ELLED COPPER W	IRE
Only top All orders	quality materials sup dispatched within:	plied. 24 hrs.
S.W.G.	1 lb reel	1 lb ree!
10 to 19	£2.05	£1-60
20 to 29	£3-15	£1-80
38 to 34	£3-45	£1-90
35 to 40	£3-65	£2-10
All prices are	e inclusive of P. & P	. in U.K.
COPPER SUP Withington, Ma	PLIES, 102 Parrsw anchester 20. Tel:	ood Road,

GOVERNMENT SURPLUS SUPER SWITCH PACK

10 Reed Switches (Open) 8 Microswitches 5 D.P. Toggle switches 5 instrument knobs with fixing screws Plus free gitts. Send £2:50 + 50 p PP to

B.B. SUPPLIES DEPT P.W. 125 High Street, Deal, Kent.

T inserts 1% × % 20 ohm DC. Ideal for microphone or speaker use. 50p each incl. PP. Quantity discounts available.

Radio Receivers

SHORTWAVE 3.2.12 MHz+M.W. Small Portables (Superhet+INT.Speaker) fl0.95, headphones for use with this set f4.95. VHF/Airband 88-135 MHz+M.W. Pocket Sets (Superhet+Int Spur.) f9.95 available without Air (108-135 MHz) Band at f8.45. Mains-Battery MW+VHF+Air (108-174 MHz) Portables f13.55. Prices include P & P, Accs & VAT, Noble Electronics, 26 Lloyd Street, Altrincham, Cheshire WA14 2DE. Tel: 061.941 4510.

Situations Vacant

Radio Technicians

Government Communications Headquarters has vacancies for Radio Technicians. Applicants should be 19 or over.

STANDARDS required call for a sound knowledge of the principles of electricity and radio, together with appropriate experience of using and maintaining radio and electronic test gear.

DUTIES cover highly skilled telecommunications/electronic work, including the construction, installation, maintenance and testing of radio and radar telecommunications equipment and advanced computer and analytic machinery.

QUALIFICATIONS: Candidates must hold either the City and Guilds Telecommunications Part 1 (Intermediate) Certificate or equivalent HM Forces qualification.

SALARY (inc. supps.) from £2,673 at 19 to £3,379 at 25 (highest pay on entry) rising to £3,883 with opportunity for advancement to higher grades up to £4,297 with a few posts carrying still higher salaries.

Opportunities for service overseas.

Further particulars and application forms available from:

GCHQ

Recruitment Officer, (Ref. PW/7) GCHQ, Oakley, Priors Road, Cheltenham, GL525AJ. Cheltenham (0242)21491 Ext2270

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Wireless for insertions

1 enclose Cheque/P.O. for £.....


(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).

		ļ	
		King's Reach Tower,	SS, tisement Dept., Rm. 2337,
	 	Rate 29p per word, minimum 1	2 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered office: King's Reach Tower, Stamford Street, London SE1 9LS

Distantia di Constanti di Const		
HI-FI DISC	OUNT CEN	TRES
	DISCO	UNT
	SPEAK	ERS
	Guaran TITAN 5	Ω as app. tees: years
	OTHERS	l year
		VAT
HI-FI TYPES		Sonic Price £4-95
S" FANE 501 Mid or Full ran 8" x 5" 15w Various makes 8 8" A.F. Model 80 Dual Cone 8" A.F. Model 83 Dual Cone FANE 8" 808T Dual Cone WH'FEDALE L'TON 3XP ki 10" DENTON 3XP KI 10" DENTON 3XP KI	Ω Sp. Price Sp. Price Sp. Price	£3-35 £5-95 £6-95
FANE 8" 808T Dual Cone WH'FEDALE L'TON 3XP kit 10" DENTON 2XP KIT Pair 10" GLENDALE 3XP KIT	Sp. Price Pr. £60.70 £39.15 £82.44	£3-95 £41-95 £26-95 £56-95
10" ELAC Model IORM	5p. Price Pair Sp. Price	£56-95 £19-99 £3-85
GROUP/DISCO TYPES 12" TITAN T12/45R 12" TITAN T12/60R 12" TITAN T12/100A 100w 12" CELESTION C12M	£15-80 £22-50	£10-95 £12-95
12" TITAN T12/100A 100w 12" CELESTION G12M 12" CELESTION G12H 30w 12" CELESTION G12H 30w 12" CELESTION G12/50 50w	£22 · 50 £36 · 00 £16 · 50 £22 · 00 £25 · 75	£22-95 £12-99 £16-95
12" GOODMANS 12 PD	Sp. Price	£17-50 £21-95 £18-95 £18-95
	0 £29-95 00 £31-95 80L £27-95 100L £28-95	£19.95 £21.95 £18.95
12" GUITAR 12" FANE CRESCENDO 12A	100L £28 95 80B £28 95 £59 95 £69 95	£19-95 £19-95 £41-95
12" FANE 12 BASS 15" TITAN T15/60 60w		£39 95 £39 95 £17 95 £19 95
IS" TITAN TIS/100 100w IS" FANE 'SPECIALIST' BASS IS" BASS 100 IS" GOODMANS ISP	£41.00 85 £39.95 £42.00	£29-95 £29-95 £31-50
IS" CELESTION GISC IS" FANE CRESCENDO/IS IS" FANE CRESCENDO BAS	5p. Price £36-00 £76-89 5 £79-95	£23-95 £26-95 £51-95 £51-95
15"		£51-95 £51-95 £72-95 £72-95
18" TITAN 118/100 100w	£51-00	£38-95 £39-95 £41-95
18" FANE CRESCENDO BASS	£94.75 £120.75	£72-95 £59-95 £75-00
HORN UNITS (Ca CELESTION MH1000 25w	1PEDANCE. rr. 85p) £17-00	£13-75
FANE 910 MK 11 50w 920 100w 144 30 50w 173 50w	£17-75 £62-95 £7-95	£10-99 £44-50 £4-95
: 1104 50 70w HIGH POWER 'CROSS-01	£11-75 £16-95	£7.95 £10.95
FANE HPXIR or HPX2R Carr. ADD-ON HIGH FREQUEN	35p £3-25	£2·25
F.A.L. 'Add-on' Carr. £1 TITAN TIH 70w Carr. £1	£51-84 £33-00 £33-00 £39-00	£35-95 £23-95 £23-95
TITAN TS2H 100w Carr. £1 TITAN T2H Carr. £1 EXTRA SPECIAL MAIL		£26 · 95
TITAN TA/50A 50 W	AMPLIFIER	R Multi
	urpose thre ontrolled inpu	e ind. ts. Treble
a Fresence Nobust, well sty	ractive Black	cabinet (Silver 19.95
PAIR FANE POP 15 12" S Suitable for use with above v	PEAKERS	
SUITABLE TWIN SPEAKER C		9 · 95 411 · 95
Also for personal sho AMPS, T'TABLES, JIN DISCO CONSOLES, LIGH	GLE MACH	and the second sec
CREDIT TERMS AVAILAB	LE orders	£20
Phone orders accepted from card holders. 403 SAUCHIEHALL STREET	Branches	at
Tel: 041 332 0700 24 NEWGATE SHOP	GLASG	
Tel: 0632 25168 NE	WCASTL	E
Mail Orders & Export enquir Branch. Add £1 carr. on Otherwise add £1-25 £1-50 (15") £2-5	ies to NEWC Hi-Fi spkrs. a (12" Spkr).	ASTLE or kits.
£1·50 (15") £2·5	50 (18")	



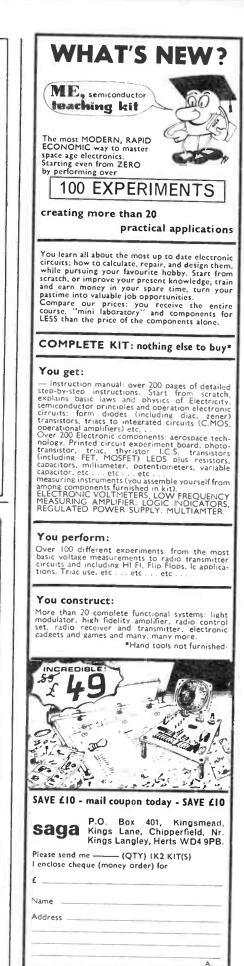

	TRANSIETOR	1	n 1	p 1	
<section-header><section-header> Support Description of the province of the pr</section-header></section-header>	TRANSISTORS P AC107* 23 BC167A 11 AC107* 23 BC167C 12 AC117* 13 BC167C 17 AC12* 19 BC171 11 AC12* 19 BC171 11 AC12* 18 BC171 11 AC12* 18 BC172* 14 AC14* 24 BC177* 14 AC14* 24 BC177* 14 AC14* 28 BC187* 14 AC14* 38 BC187* 14 AC14* 38 BC187* 14 AC14* 38 BC187* 13 AC114* 40 BC187* 27 AC14* 35 BC21	ME4102 10 ME6002 14 MJ400* 90 MJ41* 160 MJ2955* 99 ME370* 55 MJ231* 60 MJE320* 45 MJE320* 45 MJE320* 45 MJE320* 15 MJE320* 15 MJE305*80 MP102 MP103 38 MP104 36 MP105 38 MP105 38 MP105 30 MP107 50 MP33904 00 MP5A05 405	PSA35 24 MPSA350 24 MPSA350 24 MPSA350 24 MPSU02 36 MPSU02 36 MPSU02 36 MPSU02 37 MPSU03 38 MPSU04 39 MPSU05 53 MPSU32 50 OC23* 150 OC28* 150 OC28* 150 OC44* 31 OC44* 32 OC44* 32 OC46* 28 OC46* 28 OC77* 30 OC76* 38 OC77* 30 OC76* 38 OC80* 78 OC80* 78 OC200* 48 OC10* 40 OC200* 48 OC10* 40 OC200* 48 OC200* 48 OC10*	T P3055* 52 T S43 36 T S43 36 T S45 45 T S46 45 T S46 45 T S46 45 T S46 50 T S46 70 T S46 7	P12180* 17 21218.4* 31 212218.4* 31 212218.4* 31 212212.4* 35 212220.4* 35 212222.4* 35 212222.4* 35 212222.4* 35 212222.4* 35 212222.4* 35 2122368 21 2122368 21 2123368 21 2123370 10 2123370 10 213370 10 21
2-71/F; 4-150/F; 6-250/F; T.DEC 3990 ⁺ Crynin 300 - 3000 ⁺ 2000 ⁺ 8-300 ⁻ 200 U-DEC 'A' 4259 ⁺ U-DEC 'B' 6990 ⁺ Crynin Siger C'A' 4259 ⁺ 3-300 ⁻ 10-400 ⁻ 200 U-DEC 'B' 6990 ⁺ Crynin Siger C'A' 4259 ⁺ 3-300 ⁻ 10-400 ⁻ 10-400 ⁻ 10-400 ⁻ Siger C'A' 4259 ⁺ Crynin TopC 8 pin 35 LM301A 3-400 ⁻ 10-400 ⁻ 10-500 ⁻ 10-500 ⁻ 10-500 ⁻ Siger C'A' 4259 ⁺ TopC 8 pin 35 LM301A 25-200 ⁻ 30 ⁻ 37 Receiver and Transmitter 100 ⁻ 700 ⁻ 750 LH 173 B pin 150 LM324A 100-500 ⁻ 1000 ⁻ 30 ⁻ 60 ⁻ 150 ⁻ 10 ⁻ 350 ech A ^{+1-1031A} 400 ⁺ 10 ⁺	170 NE571 450 30 RAW2102-2* 7400 240 RC4136D 120 7401 110 ROW2513* 707 7402 205 SG3402* 295 7403 110 ROW2513* 704 7401 110 ROW2513* 7404 7401 110 ROW2513* 7404 7407 110 ROW7210* 17407 7407 120 SN72710* 17407 7408 317 SN76033N 141 7408 315 SN76033N 100 7411 120 SN76033N 101 7411 125 SN76033N 117 7411 125 SN76033N 117 7411 125 SN76033N 117 7411 125 SN76033N 117 7411 125 SN76023N 140 7421 125 SN76033N 117 7411	24* (TEXAS) 11 7475 38 14 7476 38 14 7476 38 14 7476 38 14 7480 48 14 7481 46 14 7481 46 14 7481 46 14 7481 46 14 7481 46 14 7481 16 15 7483 72 38 7484 921 17 7485 106 17 7485 106 17 7490 33 17 7491 32 30 7492 32 30 7495 57 27 74105 82 33 74101 142 33 74110 143 33 74118 83 33 74112 38 40 </td <td>4001 17 405 4002 17 405 4006 105 405 4007 18 405 4008 87 405 4009 50 405 4010 50 406</td> <td>3 42 4067 48 6 4068 5 89 4069 5 89 4071 7 89 4071 8 9 4071 9 48 4072 9 48 4073 1 91 4075 1 91 4073 20 4078 5 19 4085 7 45 4086 7 45 4086 7 45 4086 7 45 4086 7 45 4086 7 45 4086 9 9 4093 1 205 4096 5 111 4160 100 4162 9 320 4174 1 8 4418 1 8 4418 18 58 44412</td> <td>58 4502 120 380 4503 66 51 22 4506 51 20 20 4506 51 20 20 4507 52 21 21 4518 298 21 4511 150 21 4513 206 85 4514 252 21 4513 206 85 4514 252 21 4515 299 21 4515 299 21 4515 299 105 102 4521 268 85 4521 268 85 4521 268 85 4521 268 103 4527 192 105 4521 268 150 150 1517 105 4521 268 150 103 153 105 4523 180 150 150 150 1054 4533 160</td>	4001 17 405 4002 17 405 4006 105 405 4007 18 405 4008 87 405 4009 50 405 4010 50 406	3 42 4067 48 6 4068 5 89 4069 5 89 4071 7 89 4071 8 9 4071 9 48 4072 9 48 4073 1 91 4075 1 91 4073 20 4078 5 19 4085 7 45 4086 7 45 4086 7 45 4086 7 45 4086 7 45 4086 7 45 4086 9 9 4093 1 205 4096 5 111 4160 100 4162 9 320 4174 1 8 4418 1 8 4418 18 58 44412	58 4502 120 380 4503 66 51 22 4506 51 20 20 4506 51 20 20 4507 52 21 21 4518 298 21 4511 150 21 4513 206 85 4514 252 21 4513 206 85 4514 252 21 4515 299 21 4515 299 21 4515 299 105 102 4521 268 85 4521 268 85 4521 268 85 4521 268 103 4527 192 105 4521 268 150 150 1517 105 4521 268 150 103 153 105 4523 180 150 150 150 1054 4533 160

A Arigo 15 RéCTIFIERS 16 100717 10 100717 10 100717 10 100717 10 100717 10 100717 10 100717 10 100717 10 100717 10 100717 10 100717 10 100717 10 100717 10 100717 10 100717 10 100717 10 100717 10 10 100717 10 100717 10 100717 10 100717 10 100717 10 100717 10 100717 10 10 100717 10 10 10 100717 10 10 10 10 10 </th <th>CA-CHICK-ZO</th> <th>ORD ELECT</th> <th>TIL209 Red 13/5-L TIL211 Grn 23 TIL Osite sïde) 0:2" Red 17 TIL 0:2" Yellow, TIL 10:2" Yellow, TIL</th> <th>Segment Displays TOGGLE 2A 2500 T-01 Futaba 450 312*3" C.An 125 313 *3" C.Cth 125 321 *5" C.An 140 321 *5" C.An 140 321 *5" C.An 140 4 pole on off 5 322 *5" C.Cth 140 4 pole on off 5 SUB-MIN 140</th> <th></th> <th>-</th>	CA-CHICK-ZO	ORD ELECT	TIL209 Red 13/5-L TIL211 Grn 23 TIL Osite sïde) 0:2" Red 17 TIL 0:2" Yellow, TIL 10:2" Yellow, TIL	Segment Displays TOGGLE 2A 2500 T-01 Futaba 450 312*3" C.An 125 313 *3" C.Cth 125 321 *5" C.An 140 321 *5" C.An 140 321 *5" C.An 140 4 pole on off 5 322 *5" C.Cth 140 4 pole on off 5 SUB-MIN 140		-
3A/800V* 27 MVAAM15 105 33 × 5" SEP 60p 65p 33p	A A119 15 A A129 25 A A215 15 A EX15 15 A EX11 160 B X100 24 B Y100 24 B Y126 14 B Y126 14 B Y127 14 D A47 12 D	RECTIFIERS (plastic case) 1A/50V 20 1A/100V 22 1A/200V 25 1A/400V 23 1A/50V 34 2A/100V 34 2A/200V 44 2A/00V 53 2A/400V 73 4A/200V 75 4A/400V 72 4A/400V 72 4A/400V 72 4A/400V 73 4A/600V 78 6A/200V 78 6A/400V 78 6A/200V 78 6A/200V 78 6A/200V 78 6A/200V 78 79 739V 400mW 9 700mW 9 700mW 9 733V 1-3W 1-3W 17	Brit 0:3W ORP6i #4 DL 2":24" 50 ORP12 63 DL 2:5;3" 55 OPT0 XA 40 Ω 2:5" 65 OPT0 XA 8Ω 5W TIL111/2 10A 105 8Ω 5W TIL111/2 10A 34 6" x 4" 190 TIL111/2 144 34 6" x 4" 160 TO3 Can Type 54,500V 35 6.400V 35 15V,18V 145p each 355 6.400V 95 15V,18V 145p each 355 6.400V 155 0.14 1009K 135 10.4500V 125 91 a-ve: 5V, 12V 220 40430 125 104.400V 155 0.14 1009K 135 10.4 102 104.400V 125 0.14 10.220 124 40528 10.4 102 10.4 104.7022) 5V, 12V 20 14/100 LQ 10.15 0.1 0.15 0.15 <td>107 - 3° C.C.II. 391 TOGGLE 107 - 6° An 108 SP changeover 5 D357 149 SP changeover 5 D357 149 SPST on off 5 N825 - 6° Green 120 SPST blased 8: NR25 - 6° Green 250 DPDT 6 tags 7 NR26 - 6° Green 250 DPDT Blased 11 NR26 - 6° Green 250 DPDT Blased 11 OR 4 digit 975p SLIDE 250v IA DPDT 1 Plastic (TO220) case IA DPDT C/0 11 H DPDT C/0 12 Yarable Type Y SPSH BUTTON 723 + 210 + 37V Y SPDT C/over 61 MINIATURE LM330h1 - 12 to 37 300 On/0f 104 250V 23 ROCKER: (white) 5A 250V SP change on/of 104 250V 23 ROCKER: (white) 5A 250V SP change on/of 104 250V 23 ROCKER: (Illuminated, red) Chrome Bezel 5A 250V SP ROCKER: (Illuminated, red) Chrome Bezel 5A 250V SP</td> <td>"PURBECK OSCILLOSCOPE" AUTHOR APPROVED PARTS including PCBs available. Cathode Ray Tube 3PBI £7.75</td> <td>Build this fantastic TV GAME with realistic battle sounds-Steerable Tanks- Controllable Shell Trajec- tory and Minefields to avoid. Complete kit incl. Cases, Controls and Mains Detachable Power Supply. No extras required. Only £24·30° (P&P add 30p). IC AY-3.8710 £9·78° Basic Kit (just add controls) Only £17·98- (p&p 30p) Complete Kit incl. cases & controls</td>	107 - 3° C.C.II. 391 TOGGLE 107 - 6° An 108 SP changeover 5 D357 149 SP changeover 5 D357 149 SPST on off 5 N825 - 6° Green 120 SPST blased 8: NR25 - 6° Green 250 DPDT 6 tags 7 NR26 - 6° Green 250 DPDT Blased 11 NR26 - 6° Green 250 DPDT Blased 11 OR 4 digit 975p SLIDE 250v IA DPDT 1 Plastic (TO220) case IA DPDT C/0 11 H DPDT C/0 12 Yarable Type Y SPSH BUTTON 723 + 210 + 37V Y SPDT C/over 61 MINIATURE LM330h1 - 12 to 37 300 On/0f 104 250V 23 ROCKER: (white) 5A 250V SP change on/of 104 250V 23 ROCKER: (white) 5A 250V SP change on/of 104 250V 23 ROCKER: (Illuminated, red) Chrome Bezel 5A 250V SP ROCKER: (Illuminated, red) Chrome Bezel 5A 250V SP	"PURBECK OSCILLOSCOPE" AUTHOR APPROVED PARTS including PCBs available. Cathode Ray Tube 3PBI £7.75	Build this fantastic TV GAME with realistic battle sounds-Steerable Tanks- Controllable Shell Trajec- tory and Minefields to avoid. Complete kit incl. Cases, Controls and Mains Detachable Power Supply. No extras required. Only £24·30° (P&P add 30p). IC AY-3.8710 £9·78° Basic Kit (just add controls) Only £17·98- (p&p 30p) Complete Kit incl. cases & controls
SCR** ThyristorsBB105B BB105B Thyristors40 DRIA EditionDiversition34 SouthardJACK PLUGSSOCKETS1A50V 1A50V 1A100V 42X5J166 SouthardNoise Diode Spare Wire (Sool) 80; Combs 10p ea. 10 board wire in bady spare Wire (Sool) 80; Combs 10p ea. 10 bag Anhydrous 85p + 30p D. 4; D 10 ba	3A/600V* 27 3A/1000V* 30	MVAM115 105 BA102 25	21 × 17" 152p 121p 78p 32 × 17" 195p 163p 128p 107p	Stop Shafting Assembly, Accommodates up to 6 Wafers 69	Send S.A.E. for leaflet.	Price: Only £24.30* (p&p 30p)
3A50V33OALO ETCH RESIST PEN*750210 k way. 4 pole/210 3 way413A100V1324x5/x17"65(The extra spare line gained is to be used in No. 18)NOTARY: Mains 250V AC, 4 Amp413A400V104x2/x14"66COPPER CLAD BOARDS* stativityFor a fill controlSocketsIn line 2PIN Loudspeaker 3/4 & 5 pin Audio13p8p20p3A400V1204x2/x14"66COPPER CLAD BOARDS* (Table Double SRB)For a fill controlSocketsIn line 2PIN Loudspeaker 3/4 & 5 pin Audio13p8p20p3A400V1204x2/x14"66Glasssided8'x 10.5" PSpEasybuild Organ, General Coverage Receiver, Chromachase, 24hrs. Digital Cock, 'JUBILEE' Electronic Organ, General Purpose SW Receiver, Chromachase, 24hrs. Digital Cock, 'JUBILEE' Electronic Organ, General Purpose SW Receiver, Cast Metal Sciel Colors6p 1-way - 15p 3-way 20pSize 51" x 34" incl. large LCD display. Complete with assembly instructions & IC Data.TIC4425100 rpin 350p:1000 pins 350p: 100 rpin 521000 pins 350p: 1000 pins 350p:1000 pins 350p: 1000 pins 350p:1000 pins 350p: Tank Battle "Bovington" Game, Audio 20010p10p10pTIC4425100 rk3"148160 rk3" 148160 rk3"140 rk1140 rk1140100100 rk3"100 rk3"100 rk1100 rk3" 160 rk3"100 rk3"100 rk3"100 rk3"110425100 rk3"100 rk3"100 rk3"100 rk3"100 rk3"<	SCR's* Thyristors 1A50V 38 1A100V 42 1A200V 47 1A400V 52	BB106 40 Noise Diode Z5J 160 ALUM. BOXES	Pkt of 36 pins Spot face cutter Pln insertion tool Spare Wire (Spool) 80p; Combs 10p ea. FERRIC CHLORIDE	Break Beforc Make Wafers, 1 pole/ 12 way, 2p/5 way, 3p/4 way, 4p/3 way, 5p/2 way Spacer and Screen ROTARY: (Adjustable Stop) 1 pole/2 to 12 way, 2p/2 to 5 way, 3 pole/	Screened Plastic Open Moulded chrome body metal with 2:5mm 12p 8p 8p 8p break 3:5mm 15p 19p 8p contacts MONO 23p 15p 13p 20p	PANEL METER KIT Complete Kit for low current (1mA at 9V) 200mV or 2V F.S.D.
2N444 140 12X83 ²⁷ 118 20p; 20 pin 27p; 22 pin 30p; 24 pin 30p; 2 pin 30p; 24 pin 30p; 1 canonic AdvON' 2m FM time to be provided and the start of	3A50V 38 3A100V 43 3A200V 60 3A400V 100 5A400V 120 5A400V 120 7A400V 120 BA400V 150 BT106 150 C104D 555 TIC44 255 TIC44 25	3x2x1" 45 21x51x11" 68 4x4x11" 68 4x21x11" 68 4x21x11" 60 4x51x11" 78 4x21x2" 64 5x4x2" 82 6x4x2" 88 7x5x21" 114 8x6x3" 148 10x7x3" 172 10x41x3" 142	DALO ETCH RESIST PEN* 75p (The extra spare line gained is to be used in No. 18) COPPER CLAD BOARDS* Fibre Single- Double- Glass sided sided sided 8"x 10.5" 8"x 10.5" 6" x 6" 75p 90p 6" x 12" 130p 175p SOLDERCON PINS* 1000 pins 350p 1000 pins 350p	2 to 4 way, 4 pole/2 to 3 way 4 ROTARY: Mains 250V AC, 4 Amp 45 PW PROJECTS Easybuild Organ, General Coverage Receiver, Chromachase, 24hrs. Digital Clock, 'JUBILE' Electronic Organ, General Purpose SW Receiver, Gas 4 Smoke Sensor Alarm, 'SEEKIT' Metal Locator, 'PURBECK' Oscilloscope,	Din 2PIN Loudspeaker 3,4 & 5 pin Audio Plugs Sockets In line 3,4 & 5 pin Audio 13p 8p 20p CO-AXIAL (TV) 14p 14p 14p PHONO 6p -way 15p assorted colours metal screened 10p 8p 20p BANANA 4mm 10p 10p -	 zero and reference are built in. Only one IC and a few components—Built in half hour— Very high input impodence (1 million Meg A) so works with potential divider for DMM etc Size 5⁴ x 3⁴ incl. large LCD display. Complete with assembly

INDEX TO ADVERTISERS

A.D.E. Security A. H. Supplies Alben Engineerin; Amateur Radio Ambit Internation	· · · ·	· · · · · · ·	···· ····	••••	75 2 2 78 12
Bamber B. Barrie Electronics B. B. Supplies Bentley Acoustic Bib Hi-Fi Limited Bi-Pak Ltd. Birkett, J British National School J. Bull (Electrical)	Corpn Radio	 	 Electro	 18, nics 5,	4
Cambridge Kits Caranna C. Chromasonics Colomor Continental Speci Copper Supplies Cox Radio (Sussee) Crescent Radio C. R. Supply Co. C. T. Electronics C.W.A.S				···· ···· ···· ····	83 83 6 81 15 67 84 82 12 82 17 83
Doram Electronic					75
Eldun Electronics Electronic Design Electronic Supplie Electrovalue	Associ	ates	•••• •••	···· ····	83 14 74 16
Fidelity Fastenings Flairline Supplies			•••		10 74

75 2 2 78	G.C.H.O G.T. Information Greenweld Electr	Service				84 83 8
12 12 73 84 74	H.A.C. Short-Wa Harversons H.M. Electronics Heathkit Home Radio	ve Sup 	plies	···· ····	· · · · · · · · · · · ·	85 4 83 63 73
80 19 4	I.L.P. Electronics Intertext ICS	Ltd.			7, 	13 15
16	Jones Supplies	•••				10
9	K. & A. Distribut Kramer & Co.	ors		••••		82 80
83 83 6	Lambda Lynx Electronics					83 15
81 15 67 84 82 12 82 17 83	Mail Sales Mainline Maplin Electronic Marco Trading Marshall A. (Lond Minikits Electroni Monolith Moulded Electron	Supplie on) Lto cs	 I.	· · · · · · · · · · · · ·	cover	88 11 75 1V 63 77 83 76 78
75	Nicholls E. R.			•••	•••	74
83 14	O.K. Machine & T	ool (U	.K.) Lt	d.		75
74 16	Partridge Electron P.B. Electronics Powell T		• • •		 cover	8 76 II
10 74	Precision Petite Progressive Radio			····		77 80

Radio Book Services		82
Radio Components Speciali	sts cover	
Radio Exchange Ltd.		3
Ramar Constructor Service	· · · · ·	
		83
Reed Hampton		78
[K.S.C. ([]-F])		76
R.S.G.B. R.S.T. Valve Mail Order Co	*** ***	88
R.S.I. Valve Mail Order Co	• • • • • • •	79
Radio & T.V. Components	Ltd •	64
Saga Ltd		85
Salas Elementes		83
Conducate DE and Lot		84
Salaman of Court 14		
Science of Cambridge		68
Scientific Wire Co., The		83
Selray Book Co		14
Seltronics		82
Sentinel Supplies		14
Sonic (Hi-Fi)	1	85
Sonic Sound Audio		2
Southern Valve Co		76
S.T.E. Ltd.		82
Stirling Sound		73
Swanley Electronics		4
	*** ***	
70.0		
T.D. Components		82
Technomatic Ltd		16
Teleradio	8	38
Tempus		6
The Trading Post		77
T.K. Electronics	8	32
Trampus	8	30
Man Kasa Dublistin		
Van Karen Publishing	(32
Watford Electronics	86, 1	
West London Direct Suppli	es 8	35
Williams, Michael		0
Williamson Amplification		33
Wilmslow Audio		6
		•
Z & I Aero Services	,	38
Z & I Aero Services	··· ··· ·	50

Head Office and Warehouse 44A WESTBOURNE GROVE LONDON W2 55E Tel: 727 5641/2/3

Z & I AERO SERVICES LTD. Reg No. 242 1255 03

Retail Shop **85 TOTTENHAM COURT ROAD** LONDON WI Tel: 580 8403 Open all day Saturday

Please send all correspondence and Mail-Orders to Head Office

										AC/DC TAUT SU MULTIMETERS	JSPENSION				
IB3GT	0.65	6AK6	0.75	6CW4	3.75	I2BA6	0.65	ECL80	0.60	EZ80	0.50	PD510	3.35	TYPE U4315	
IR4	0.50	6AK7	0.85	6CY5	1.00	12BE6	0-80	ECL81	0.75	GY50I	0.90	PL36	1.10		
IR5	0.50	6AL5	0.40	6CY7	1.00	12BH7A	0.75	ECL82	0.60	GZ30	0.65	PL81	0 80	COLUMN A	
154	0.40	6AM6	0.70	6DO6B	1-45	128Y7A	0.80	ECL83	1.15	GZ32	0.65	PL82	0.55	and the second se	
155	0.40	6AM8	0.70	6DT6	0.80	35W4	0.70	ECL84	0.70	KT66	4 - 50	PL83	0 - 50	100000	
IT4	0.40	6AN5	2.50	6GH8A	0.80	50C5	1.00	ECL85	0.65	KT88	5 · 80	PL84	0.75		
iùà	0.70	6AN6	0.85	6GK5	0.70	*75C1	0.80	ECL86	0.82	OA2	0 - 55	PL95	0.70	the second s	1
iŭs	0.80	6AO5	0.85	6]4	1.20	*85A2	0.82	EF80	0.40	OA3	0.75	PL504	1.05		
IX2B	1.20	6AR5	0.70	6JSGT	0.80	*90C1	1.20	EF85	0.48	OB2	0.90	PL508	1.30		
2CW4	4-50	6A56	1.00	6]6	0.55	*807	1.00	EF86	0.90	OB3	0.75	PL802	2.80	and the second second	
*2D21	0.80	6A57G	·20	6.7	0.80	*811A	3.80	EF92	0.75	OC2	1.40	PY81	0.70		
*3-500Z	40.00	6AT6	0.75	6K6GT	0.82	*829B	8.80	EF97	0.70	0C3	0.75	PY82	0.55	DOM AND	
*3E29	8 · 50	6AU6	0 - 50	6L6GT		*832A	8·20	EF98	0.90	OD3	0.75	PY83	0·70 0·75	A DECEMBER OF	
3Q4	0.75	6AV6	0.75	6N7GT	0.85	*B66A	3.00	EF1B3	0.70	PABC80	0.45	PY88	1.30	100	1
354	0-50	6AW8A	0.75	6Q7	0.90	*872A	6.00	EF184	0.70	PC86	0·85 0·85	PY500A	7.80		
5AQ5 5AT8	0.75	6AX4GTI		65A7	0.80	•5763	2.85	EFL200	1.20	PC88 PC92		TT21 TT22	7.80	Sensitivity D.C.	20,000 o.p.v.
5AT8	0.80	6AX5GT	1 - 30	65G7	0.80	DAF96	0.60	EH90	0.60	PC92 PC95	0·85 0·70	U25	1.00		
5T4	0.75	6BA6	0-45	65K7	0.80	DF96	0.60	EL34	0.95	PC95 PC96	0.50	U25 U26	1.00	Sensitivity A.C.	2,000 o.p.v.
5U4G	0.90	6BE6	0-48	65L7GT	0.70	DK92	1 · 00 0 · 60	EL36	0.65	PC97	0.95	UABC80	0.58	D.C. Current	50µA-2·5A
5U4GB	0.95	6BF5	0.85	65N7GT	0.70	DL96	0.90	EL81 EL82	0.60	PC900	1.00	UBC81	0.60	A.C. Current	0.5mA-2.5A
5U8	0.75	6BF6	0.75	65Q7	0.80	ECC84	0.48	EL82 EL83	0.00	PCC84	0.50	UBF89	0.60		75mV-1000V
5V4G	0.60	6BH6	0.85	6V6GT	0.92	ECC85 ECC86	1.25	EL84	0.45	PCC85	0.60	UBL21	0.85	D.C. Volts	
5X4G	0.80	6B]6	0.80	6X4	0.90	ECC88	0.75	EL86	0.75	PCC88	0.65	UCC84	0.75	A.C. Volts	IV-1000V
5X8	0.90	6BN6	0.80	6X5GT 12AC6	0.80	ECC89	0.80	EL95	0.70	PCC89	0.75	UCC85	0.55	Resistance	300Ω-500kΩ
5Y3GT 5Z4GT	0.65	6BQ7A 6BR8A	1.20	12AC6	0.80	ECCI89	0.80	EL504	0.80	PCC189	1.00	UCF80	0.75	Capacity	0 · 5 / F
6AB4	0.55	6BU8	0.85	I2AE6	0.85	ECF80	0.60	EM80	0.65	PCF80	0.65	UCH8I	0.65		
6AB7	0.60	6BW7	1.00	12AT6	0.60	ECF86	0.80	EM81	0.60	PCF82	0.45	UCL81	0.70	Accuracy	2·5% D.C.,
6AC7	0.80	6BZ6	0-65	12AT7	0.50	ECF200	0.90	EM84	0.60	PCF84	0.65	UCL82	0.75		4% A.C.
6AF4A	0.80		0.70	12AU6	0.65		0.90	EM87	1.00	PCF201	1.10	UCL83	0.80	Price complete	with pressed
6AG5	0.65		0.55	12AU7	0.47	ECF801	0.95	EY51	0.60	PCF806	1.00	UF85	0.50	Frice complete	with pressed
6AG7	0.85	6CB6	0 - 55	12AV6	0-85		0.95	EY8I	0.20	PCL81	0.65	UL84	0.85	steel carrying o	ase and test
6AH6	0.95	6C57	0.85	12AV7	I - 00	ECH81	0.55	EY87	0.20	PCL82	0.80	UM80	0.60	leads.	£15·85*
6AJ5	0.62		1.00	12AX7	0 · 55	ECH83	0.60	EY88	0.55	PCL84	0.75	UM81	0.75	Packing & postage	£1.50*
6AK5	0.55	6CU6	I · 00	12AY7	0.82	ECH200	0.80	EY500A	1 - 50 -	PCL86	0.85	UM84	0.45	terms a pest-se	
1	_					_									line changes and

VAT is not included. Please add 121% on all items except those marked with asterisk, on which VAT is 8%. Postage and packing charges are $\pounds 0 \cdot 10$ per \pounds subject to a minimum of $\pounds 0 \cdot 30$.

OUR NEW 1977/1978 CATALOGUE IS NOW READY AND WILL BE SENT ON RECEIPT OF REMITTANCE FOR £0-30

YOUR OWN RADIO STATION!

Have you ever wished you could set up your own radio station at home and chat to people in far-off lands? It's really fun, and not half as difficult as it may sound. Over one million people all over the world are now radio amateurs and the number is growing rapidly, for amateur radio is a unique hobby. It offers the newcomer an exciting and fascinating combination of a scientific hobby, a competitive sport, and an entry into a world-wide fellowship which knows no boundaries. It has its own customs and traditions, its own international language, and its "ham spirit".


Sounds great, but how does one get started? Well, you're in luck! We have just published a brand-new adition of A Guide to Amateur Radio by Pat Hawker, G3VA, which provides a complete introduction to the subject. Written in a highly readable way by an acknowledged expert, this book explains just what amateur radio is, and how it came to be. The basic principles of antennas, receivers and transmitters are covered, and the reader is guided in the correct choice of equipment and other points involved in setting up a station, including obtaining a transmitting licence. There is also much useful reference material, including lists of international call sign prefixes. If you are a keen short-wave listener who might like to move up to amateur radio, this is the book for you!

120 pages


Illustrated

Only £1.71 post paid

SGE

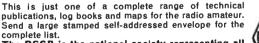

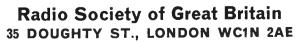The RSGB is the national society representing all UK radio amateurs. Membership is open to all interested in the hobby: write to the membership section and ask for full details.





HIGH OUALITY Very Low Distortion Audio Signal Generator AN IDEAL INSTRUMENT FOR HI-FI TESTING

Based on a Linsley Hood design.



Published on approximately the 7th of each month by IPC Magazines Limited, Westover Honse. West Quay Read, POOLE, Derset BHID 136: Printed in England by Index Printers, Dunstable, Bed-Sok Agents for Australia and New Zealand-Gordon and Gotch (Asia) Ltd.: South Africa-Central New Agency Ltd. Subscriptions INLAND and OVERSEAS 20-60 payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Susex. PRADIAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price above on the cover, excluding Eire where the selling price is subject to V.A.T. and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorized cover by way of Trade or affixed to or as part of any publication or advertising, literary or pic-torial matter whatsoever.

World Radio History

U.K. RETURN OF POST MAIL-ORDER SERVICE ALSO WORLD WIDE EXPORT SERVICE

R.C.S. 100 watt MIXER/AMPLIFIER ALL VALVE





2 x 12" CABINETS for Disco or PA all fitted with carrying handles and corners. Black vynide covered. Other cabinets in stock. SAE for leafiet 60 WATT R.M.S. £52 With one horn £60 With two horns £68 Carr. £3 80 WATT R.M.S. £56 With one horn £64 With two horns £72 Carr. £3 100 WATT R.M.S. £69 With one horn £78 With two horns £86 Carr. 25 SINGLE I2inch CABS COMPLETE 30 WATT R.M.S. £32. WITH HORN £40. 40 WATT R.M.S. £34. WITH HORN £42. 60 WATT R.M.S. £41. WITH HORN £49. CARR £3 EA. **"SUPERB HI-FI"** 12in 25 watts A high quality loudspeaker, its remarkable low come resonance ensures clear reproduction of the despest bass. Fitted with a special copper drive and concentric tweeter come resulting in full range reproduction with remark-able efficiency in the upper register. able efficiency and register. Bass Resonance Flux Density 16 Useful response 20 8 or 16 ohms models. 25cps 16,500 gauss 20-17,000cps £22.00 Post "AUDITORIUM" 12in. 35 watts A full range reproducer for high power, Ideal for Hi-Fi and Discotheques. Electric Unitars, public address, multi-speaker systems, electric organs. Bass Resonance 35cps Flux Density 15,000 gauss Useful response 25-16,000cps 8 or 16 ohms models. £2 .00 Port "AUDITORIUM" 15in. 45 watts ISIN. 42 WALLS A hich waitings loadspeaker of exceptional quality with a lavis response to above 8,000 c.p. Ideal Ior Fublic Address, Discotheques, Electronic instruments and the home Hi-Fi. Bast Resonance 35 cps Flox Density 15,000 gauss Useful response 20-14,000 cps 8 or 16 obms models. £26.00 Post £1.60 Loudspeaker Cabinet Wadding 18in wide, 20p per ft. HI-FI Enclosure Manual containing plans, designs, crossover data and cubic tables, 85p. **E.M.I.** $13\frac{1}{2} \times 8in$ SPEAKER SALE! With tweeter. And crossover. £7.95 Post 45n I5W model £10.50 8 ohms. Post 65p **GOODMANS 20W Woofer** Size 12 × 10in 4 ohms. Rubber cone surround. Hi-Fi base unit.

BAKER DISCO SPEAKERS

HIGH QUALITY-BRITISH MADE

337 WHITEHORSE ROAD, CROYDON

RADIO COMPONENT SPECIALISTS Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30) Minimum post 30p. Components List 20p. Cash price incl. VAT. Access & Barclay cards welcome. H.P. available. Phone your order Tel. 01-684 1665







£9.95 Post 65p

World Radio History

MARPLIN

everything for the modern D.I.Y. electronics enthusiast and more.



World Radio History

Telephone: Southend (0702) 715155 Shop: 284, London Road, Westcliff-on-Sea, Essex (Closed on Monday) Telephone: Southend (0702) 715157