


IMPROVING SHORT-WAVE RECEPTION

MONTHLY  
ONE SHILLING


The  
**Wireless  
World**

*COVERING  
EVERY WIRELESS INTEREST*

JUNE, 1941

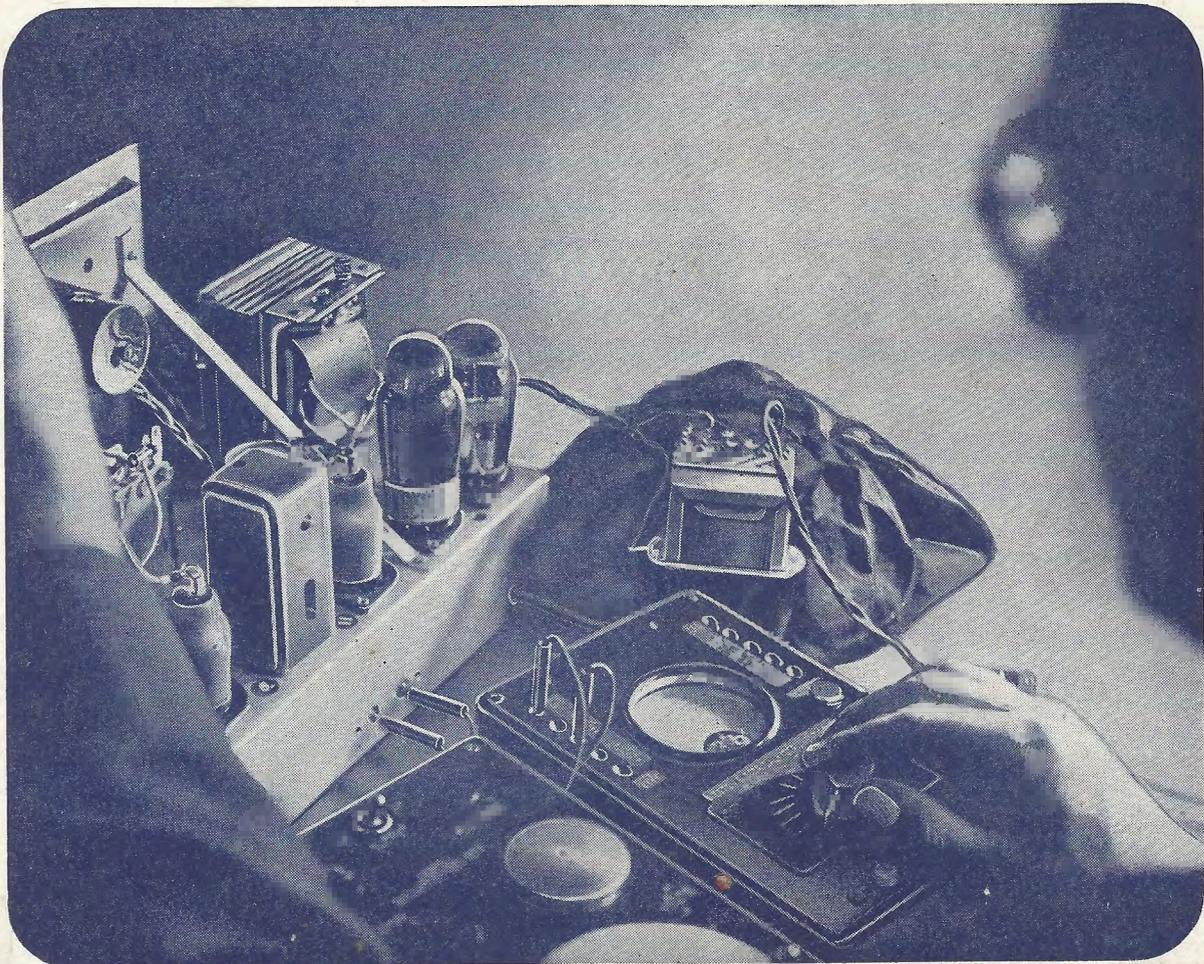

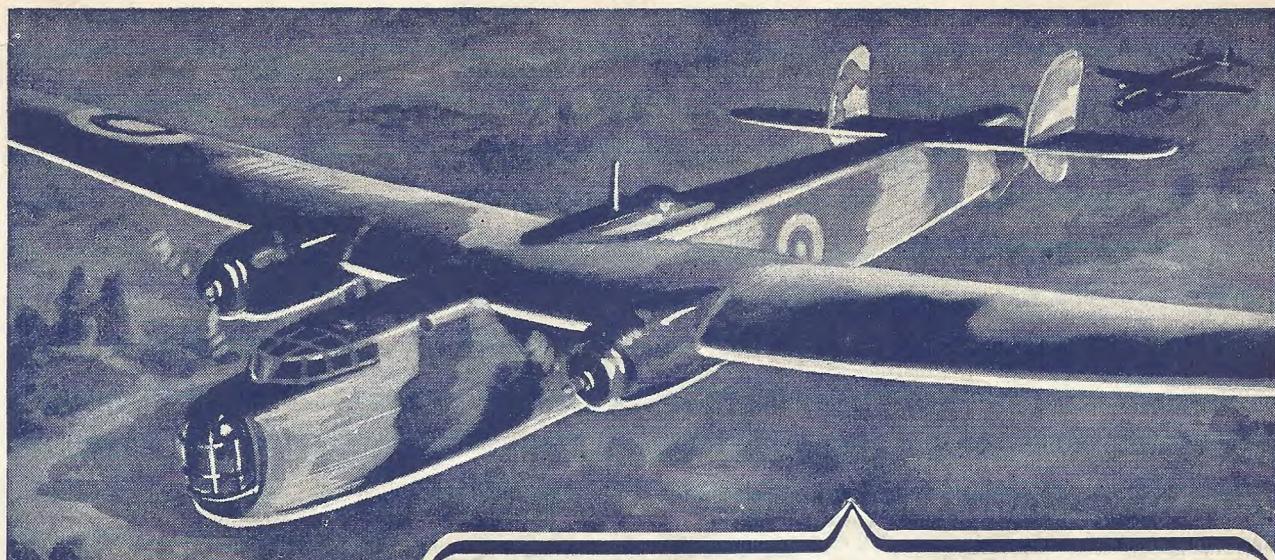BROADCAST RECEIVER MAINTENANCE : WARTIME MAKESHIFTS



# SILVERED MICA CONDENSERS

*for SERVICE and the SERVICES*

Every U.I.C. Condenser is subject to the most thorough mechanical and electrical inspection, and is tested for:—


- CAPACITY : Tolerance can be made as close as  $\pm 0.5\%$
- LOSS FACTOR : Average 0.05% (maximum 0.2%) at 1,000 Kc/s.
- TEST VOLTAGE : As specified, but normally 1,000 v. D.C.

Constant production check measurements are made on the effect of repeated cycles of HEAT & HUMIDITY on DIELECTRIC STRENGTH—INSULATION RESISTANCE — NOISE, etc.

Approved as satisfying all current official specifications.

Send for interesting Technical Brochure.

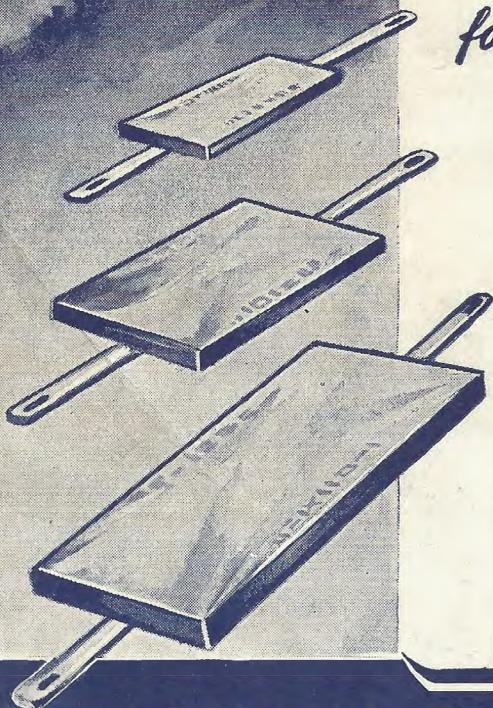CONTRACTORS TO GOVERNMENT DEPTS.  
On A.I.D. APPROVED LIST.




## UNITED INSULATOR CO LTD

*The Pioneers of Low Loss Ceramics*

12-16 LAYSTALL STREET, LONDON, E.C.1

Tel: TERMINUS 4118-9

Grams: CALANEL, SMITH, LONDON

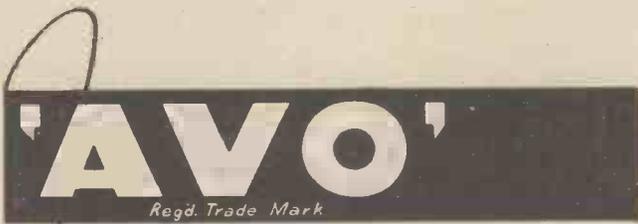

*Meters that Matter*



BRITISH MADE

FROM years of intensive research in the design and manufacture of electrical testing equipment has grown the range of world-famous "AVO" Instruments. To-day, wherever rapid precision testing is demanded, there will be found the meters that matter—"AVO" Meters.

46 range Model 7  
Universal AvoMeter

40-range Model 40  
Universal AvoMeter

"Avo" Valve Tester with Universal Panel

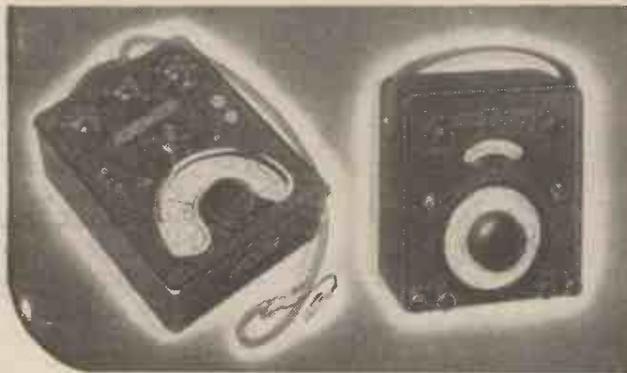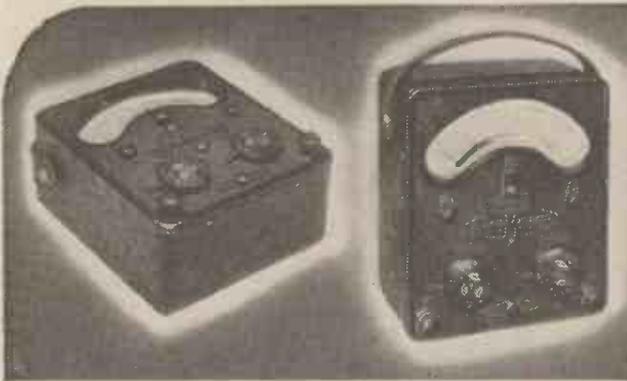

All-Wave "Avo" Oscillator

"Avo" Test Bridge

Universal AvoMinor.

D.C. AvoMinor

**OTHER "AVO" INSTRUMENTS  
(Not Illustrated)**

- "Avo" Bonding Meter.
- "Avo" Milliohmmeter.

Write for literature fully descriptive of any "Avo" Instrument in which you are interested.

In spite of greatly increased production, most of our output of "AVO" Instruments is being taken by the Services. Delay in delivery of Trade orders is consequently inevitable, but we shall continue to do our best to fulfil your requirements as promptly as possible.

Sole Proprietors and Manufacturers:  
**THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT Co. Ltd.**  
Winder House, Douglas Street, London, S.W.1.  
Phone: VICTORIA 3404-7.

# RAF *wants* Radio Enthusiasts

## SKILLED & SEMI-SKILLED TRADESMEN —

the R.A.F. needs your knowledge and ability. You can be enrolled as :—

Wireless Mechanics - (18 to 50)

Radio Mechanics - - (18 to 50)

Electricians - - - - (18 to 38)

## UNTRAINED MEN WHO ARE KEEN ON RADIO—

the R.A.F. will quickly train you and add to your knowledge. Recruits are now wanted for training as :—

Radio/Wireless Mechanics  
(18 to 32)


*(THESE ARE ALL  
GROUND DUTIES)*

Get full details by posting the coupon on the right, or, better still, go to-day to the R.A.F. Section of the nearest Combined Recruiting Centre (address from any employment exchange) and *volunteer* for R.A.F. Wireless Trades.



Men are wanted NOW to maintain and operate the wireless installations without which the grand work of the R.A.F. would not be possible. These jobs are interesting, the pay and conditions are good, and you have the satisfaction of doing work of first-rate importance.

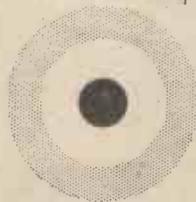-----  
*Please send me details of Wireless Trades in the R.A.F.*




NAME.....

ADDRESS

FT 15/Ap./A

To Air Ministry Information Bureau, Kingsway, London, W.C.2.

# The Highest Degree OF RAPID ASSEMBLY

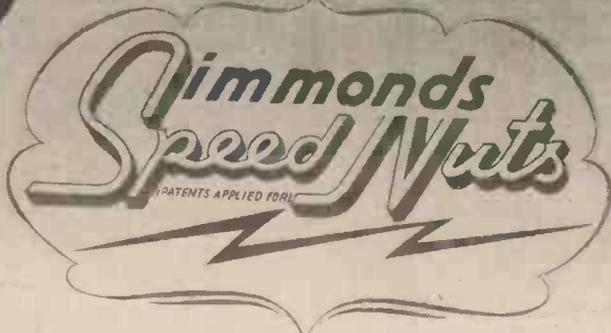

speed up and simplify assembly and cut down costs. They are available in a wide range of standard types, but our Development Department is at the service of Manufacturers whose particular needs call for special designs.



**SIMMONDS AEROCESSORIES LTD**

GREAT WEST ROAD, LONDON.



## New and Improved TAYLOR VALVE TESTERS

The Taylor range of Valve Testers, all of proved performance, now incorporate a circuit which enables accurate measurements of mutual conductance to be made on at least 99% of British and American receiving valves.

By means of the illustrated directions provided with every instrument, it is also possible for the user to work out the correct switch setting for any new type of receiving valve which may be produced.



NOTE THE SCOPE OF THIS—  
**TAYLOR MODEL 45**

**MUTUAL CONDUCTANCE.** Measures mutual conductance of at least 99% of British and American receiving valves.

**17 VALVEHOLDERS.** The 17 different types fitted, include the new American Bantam, Loktal, Mazda Octal and Midget Deaf-Aid types.

**TESTS EVERY VALVE** under correct working condition.

**MULTI-ELECTRODE VALVES.** Each section can be tested independently.

**CATHODE LEAKAGE.** Calibrated scale shows leakage: as high as 10 megohms.

**"GOOD," "?", "REPLACE."** The Taylor 4½-in. square type moving coil meter has a scale for indicating the slope of valves.

**FILAMENT CONTINUITY AND SHORTS.** These are indicated by a lamp mounted on the panel.

**NOTE:** MODEL 47 also includes provision for the measurement of D.C. volts, amps. and ohms.

**MODEL 45 £14-3-6**

Portable Model £14-19-0 (No purchase tax payable on any of these models.)

**MODEL 47 £16-16-0**

Every Taylor Valve Tester is supplied complete with a grid connecting lead—comprehensive book of Instructions and an up-to-date Valve Manual.

Fully descriptive Brochures are available on request.

BRITISH MADE AND GUARANTEED 6 MONTHS.

# TAYLOR

Electrical Instruments Ltd.,  
419-422, Montrose Avenue,  
SLOUGH, Bucks.  
Phone: Slough 21381.

# B.I. RADIO MATERIALS

We have had a long experience in the manufacture of all kinds of Cables and Wires, Aluminium Sheets and Strips, Static Condensers, Insulators and Iron Work, Telephone Cords, and Copper Earthing Rods, for Radio use.



U.K. Regd. Trade Mark.

**BRITISH INSULATED CABLES LTD.**  
CABLE MAKERS AND ELECTRICAL ENGINEERS  
Head Office:  
**PRESCOT, LANCS. Tel. No. PRESCOT 6571**



## ENJOY "MUSIC WHERE YOU WANT IT"



Cabinet  
Models from 21/6

**B**USY days and evenings in your home leave little time for leisurely listening beside the radio set. Yet the need for entertainment is greater than ever. That is why more and more people are adopting W.B. Extension Speaker listening. They are enjoying their favourite programmes in the kitchen, the workroom or the shelter. Thousands are getting the fullest enjoyment from their radio by this means. Why not you? Ask your dealer for a demonstration.



# Stentorian

THE PERFECT EXTRA SPEAKER FOR ANY SET

WHITELEY ELECTRICAL RADIO CO. LTD., MANSFIELD, NOTTS.

# PREMIER RADIO

PLEASE NOTE—ALL KITS ARE NOW SUBJECT TO PURCHASE TAX. THIS IS INCLUDED IN THE PRICE

## PREMIER SMOOTHING CHOKES

Type	Current	Henrys	Res.	Prices
C 40/500	40 MA	20-34 H	500 ohms	6/-
C 60/180	60 MA	8 H	180 ohms	6/-
C 60/400	60 MA	25-34 H	400 ohms	8/8
C 60/500	60 MA	18-30 H	500 ohms	8/8
C 100/400	100 MA	20-34 H	400 ohms	10/8
C 150/185	150 MA	20-34 H	185 ohms	15/4
C 200/145	200 MA	20-34 H	145 ohms	18/-
C 250/120	250 MA	25 H	120 ohms	20/-

## "LEARNING MORSE"

Premier Morse Practice Key on Bakelite Base and Brass Movement	3/3
General Purpose Morse Key	5/10
Bakelite Buzzers	2/-
3 Henry Chokes	7/6
Complete Kit of Parts for Valve Oscillator, as described in W.W. "Learning Morse"	25/-

## PREMIER SHORT-WAVE KITS for OVERSEAS NEWS

Incorporating the Premier 3-Band S.W. Coil, 11-86 Metres without coil changing. Each Kit is complete with all components, diagrams and 2-volt valves. 3-Band S.W. 1-Valve Kit, 18/-; 3-Band S.W. 2-Valve Kit, 27/6.

## DE LUXE S.W. KITS

Complete Kit, including all Valves, coils, wiring diagrams and lucid instructions for building and working. Each Kit supplied with a steel Chassis, Panel and plug-in coils to tune from 13 to 170 metres.

1-V. S.W. Receiver or Adaptor Kit	24/6
1-V. S.W. Superhet Converter Kit	28/-
2-V. S.W. Receiver Kit	35/6

## PREMIER PICK-UPS

Heads (will fit any tone-arm)	8/9
Premier Pick-ups with Volume Control Tone Arm	17/6

**ANOTHER SPECIAL OFFER**  
Rothermel Brush Piezo Crystal Pick-ups. Standard, S.B. Model with arm ... 34/9

## PREMIER 1941 HIGH FIDELITY AMPLIFIER KITS

Each Kit is complete with ready drilled chassis, selected components, specially matched valves and full diagrams and instructions.

	Kit of Completely Parts with Wired and Valves Tested		
4-watt A.C. Amplifier	£2 14 0	£3 11 6	
6-watt A.C.	£6 16 6	£7 13 6	
8-10 watt A.C./D.C.		£7 9 0	
15-watt A.C.	£7 18 9	£9 8 0	
Black Crackle Steel Cabinet			17/6 extra.

## MAINS TRANSFORMERS Wire-ends. All L.T. Windings Centre-Tapped

SP 250	250-0-250 v. 60 ma., 4 v. 1-2 a., 4 v. 2-3 a., 4 v. 2-3 a.	13/4
SP 300	300-0-300 v. 60 ma., 4 v. 2-3 a., 4 v. 2-3 a., 4 v. 2-3 a.	13/4
SP 301	300-300 v. 150 ma., 4 v. 2-3 a., 4 v. 2-3 a., 4 v. 1 a., 4 v. 1 a.	17/4
SP 350A	350-350 v. 100 ma., 5 v. 2a. (not C.T.), 6.3 v. 2-3 a.	16/-
SP 350B	350-350 v. 100 ma., 4 v. 2-3 a., 4 v. 2-3 a., 4 v. 2-3 a.	16/-
SP 351	350-350 v. 150 ma., 4 v. 1-2 a., 4 v. 2-3 a., 4 v. 3-4 a.	17/4
SP 351A	350-350 v. 150 ma., 4 v. 3 a., 4 v. 2-3 a., 4 v. 1 a., 4 v. 1 a.	22/-
SP 352	350-350 v. 150 ma., 5 v. 2 a., 6.3 v. 2 a., 6.3 v. 2 a.	18/-

**Auto Transformers.** Step up or down. 100-125 v. to 200, 230 or 250 v. A.C., 60 watts, 11/4; 125 watts, 15/-; 250 watts, 22/-

**L.T. Transformers, all C.T.**  
4 v. 2-3 a. ... 11/4 6.3 v. 2-3 a. ... 11/4  
2.5 v. 5 a. ... 11/4 7.5 v. 3 a. ... 11/4  
5 v. 2-3 a. ... 11/4 12 v. 3-4 a. ... 18/-

**Push-Pull Driver Transformers, 3:1** ... 6/6

**Universal Output Transformers, 1:1 Ratios.** Single or Push-pull ... 6/6

## MATCHMAKER UNIVERSAL OUTPUT TRANSFORMERS

Will match any output valves to any speaker impedance.

11 ratios from 13:1 to 80:1. 5-7 watts, 16/10. 10-15 watts, 21/10. 20-30 watts, 36/10.

Paxolin Valve Holders, chassis mounting, 4 or 5 pin, 4d. each. 7 pin, 4d. each.

Valve Screens, for American type valves. Small size, 1/2. Medium size, 1/2.

## PREMIER MICROPHONES

Transverse Current Mike, High grade large output unit. Response 45-7,500 cycles. Low hiss level, 23/-.


ALL ENQUIRIES MUST BE ACCOMPANIED BY 2½d. STAMP.

## NEW PREMIER S.W. A.C. RECEIVER

In response to many requests we have now produced an A.C. version of the popular Premier Short Wave SG3 Kit. Circuit: Pentode H.F. Stage, Pentode Detector, Beam Power Output, and F.W. Rectifier. 200-250 v. A.C. Operation. Built-in Power Pack. Hum-free operation. For use with Phones or P.M. Speaker.

Complete Kit of Parts with drilled chassis, all components. Plug-in Coils covering 13-170 metres, 4 valves and full instructions and circuits

£6-14-6

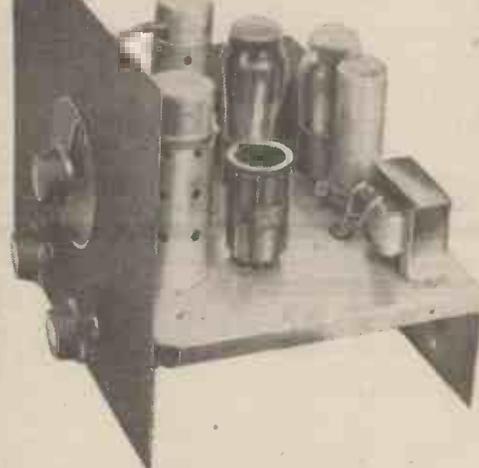

Battery Version Kit also available ... £4 15 4  
Extra Coils 9-15, 200-2000m. also supplied.

"The Wireless World" said they were "very much impressed" ... See full Test Report pp. 492-3 December issue. Send for details.

## PREMIER BATTERY CHARGERS for A.C. MAINS

Westinghouse Rectification complete and ready for use

To Charge:	6 volts at 1 amp.	26/-	
2 volts at ½ amp.	13/4	12 volts at 1 amp.	28/-
6 volts at ½ amp.	22/-	6 volts at 2 amps.	43/6

## MOVING COIL SPEAKERS

All complete with transformer. Rola 6½ in., 15/-; 10 in. P.M.s, 22/6; Goodman 8 in. P.M.s, 20/-.

## ENERGISED MODELS

Plessey 8in., 175 ohm field, 7/6; 10in. B.T.H. 1,600 ohm field, less transformer, 11/6.

Moving Coil Mike. Permanent magnet model requiring no energising. Response 90-5,200 cycles. Output .25 volt average. Excellent reproduction of speech and music, 49/-.

## SHORT-WAVE CONDENSERS

Trolitul insulation. Certified superior to ceramic. All-brass construction. Easily ganged.

15 m.mfd.	2/4	100 m.mfd.	3/-
25 m.mfd.	2/6	160 m.mfd.	3/7
40 m.mfd.	2/6	250 m.mfd.	4/-

## SHORT-WAVE GEAR

Short-Wave Coils, 4- and 6-pin types, 13-26, 22-47, 41-94, 78-170 metres, 2/- each, with circuit.

Premier 3-Band S.W. Coil, 11-25, 19-43, 38-86 metres. Suitable any type circuit, 2/11.

4-pin or 6-pin Coil Formers. Plain or Threaded, 1/2 each.

Bakelite Dielectric Variable Condensers. .0005 mf. Suitable Tuning or Reaction, 1/6 each.

Short-Wave H.F. Chokes. 10-100 m., 10½d. each. High grade Pie-Wound U.S.A. type, 2/- each.

Lissen Dual Range Screened Coils, Medium and Long Waves, 2/9 each.

## PREMIER REPLACEMENT VALVES

4 volt A.C. Types, 5-pin, A.C./H.L., A.C./L., A.C./P., A.C.H.P., A.C.V.H.P., A.C./V.M. All 5/6 each.

Premier I.F. Trans. 450-470 kc. Air cores, 5/- each. With or without top grid connection.

Flexible Couplings, ¼ in. bore, 11d. each. Valve Screens for International and U.S.A. types, 1/2 each.

Jacks, Single circuit, open or closed types, 1/9. Plugs, 1/9.

Electric Soldering Irons. 200-250 volts, 5/10. Super Model, 11/9.

Potentiometers. All resistances, 2/4, with switch, 3/3.

Beehive Stand Offs, 2½ in., 7d. each. Mains Noise Suppressors, comprising double wound Choke and Conds., 6/6 each.

Microphone Cable, weatherproof. Shielded and Rubber covered, 1/- yard.

**ELECTROLYTIC CONDENSERS.** Cardboard cases. 500 v. working, 4 mfd. and 8 mfd., 2/- each, 8+8, 4/-, 4+4 2/11, 4+4+1 3/9, 4+4+4 4/3, 16+8 4/11, 16+16 6/-, 25 mfd. 25 volt, 1/6, 50 mfd. 12 volt, 1/6, 15 mfd. 100 volts, 1/3, 4 mfd. 500 volt, 4/8. 1+1 Mains Buffer, 1/2.

Microphone Transformers. Suitable for all mikes. Centre Tapped Primary A, 20 and 40:1; B, 30 and 60:1; C, 50 and 100:1, 6/6 each. Microphone Stands. Floor Type, 32/6.

# PREMIER RADIO CO.

ALL POST ORDERS to: JUBILEE WORKS, 167, LOWER CLAPTON ROAD, LONDON, E.5 (Amherst 4723).

CALLERS to: Jubilee Works, or 169, Fleet Street, E.C.4 (Central 2833) or 50 High Street, Clapham, S.W.4 (Macaulay 2381).



# Masteradio

VIBRATORPACKS  
BRITISH EQUIVALENTS OF  
AMERICAN TYPES

A SELECTION FROM THE FULL RANGE OF STANDARD VIBRATORPACKS

TYPE	OPERATING VOLTS	CONSUMPTION AMPS.	OUTPUT VOLTS D.C. UNSMOOTHED	OUTPUT M.A.	TYPE OF RECTIFIER
6A300	6	7	300	100	Sync. Vibrator
6B300	6	7	300	100	OZ 4 Valve
12A300	12	3.5	300	100	Sync. Vibrator
12B300	12	3.5	300	100	OZ 4 Valve
VP551	6	6/7	300-275-250-225	100	OZ 4 Valve
VP552	6	6/7	do.	100	Sync. Vibrator
VPG554	12	3/3.5	do.	100	OZ 4 Valve
VPG552	12	3/3.5	do.	100	Sync. Vibrator
VP553	6	4/5	200-175-150-125	100	OZ 4 Valve
VPG553	12	2/2.5	do.	100	OZ 4 Valve

THE PORTABLE POWER SUPPLY FOR RADIO TRANSMITTERS & RECEIVERS.

PUBLIC ADDRESS SYSTEMS.

SCIENTIFIC APPARATUS.

EMERGENCY POWER SUPPLY SYSTEMS.

Used by:  
The WAR OFFICE  
The AIR MINISTRY  
The POST OFFICE  
and POLICE FORCES.

Proven for long life and reliability under war conditions (in all services, on land, sea and in the air).

Size only 5 3/8" x 4 1/2" x 5 3/8" high and weighing only 6 lbs. approx.


Write for details:—

**MASTERADIO LTD.** VIBRANT WORKS, WATFORD, Herts.  
'Grams: MASTIOLA. 'Phone: WATFORD 9885/9890.

Efficiency as high as 70% including rectification.

Outputs of up to 30 watts from 6 or 12 volts Battery. (Special Vibratorpacks up to 60 watts.)

## WHARFEDALE GOLDEN CHASSIS

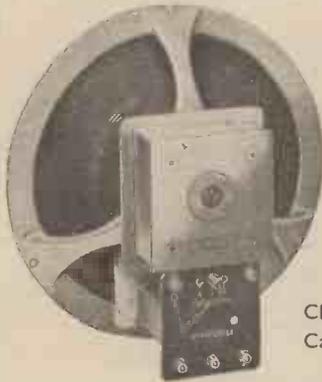

As supplied to the B.B.C.


Supplies of this first-class Loud Speaker are still available.

Delivery 2/3 weeks.

### PRICES:

	Less Trans.	With Trans.
Chassis only - - -	60/-	75/-
Cabinet Model - - -	97/6	112/6

RESPONSE CURVE

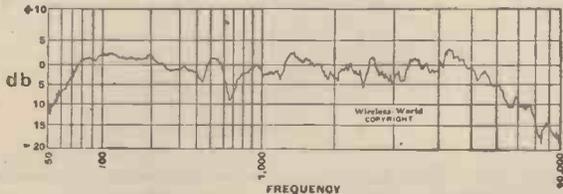

**WHARFEDALE WIRELESS WORKS**  
SOLE PROPRIETOR: D. E. BRIGGS,  
HUTCHINSON LANE, BRIGHOUSE, YORKS.  
'PHONE: BRIGHOUSE 50. 'GRAMS: "WHARFDEL."

## M.R. SUPPLIES

continue to offer from stock the following FIRST-CLASS BARGAINS in RADIO and ELECTRO-TECHNICAL EQUIPMENT. We still maintain our long-standing reputation for prompt despatch and service.

**PHOTO-ELECTRIC CELLS.** Great opportunity which cannot recur. Brand new 25 Cetrion 5W3 Cells ex contraband. For cine and light control, sensitive to infra-red and ultra-violet, 100/400 micro-amps per lumen. Gas-filled, cesium, in tube 2 1/2 in. by 1 in. Supplied with full technical data sheet. Many important applications, only 20/6 each. **PRELIMINARY AMPLIFIERS** for photo-cell. Also suitable for microphone. Fully smoothed and decoupled, high gain. Size 8 in. by 2 1/2 in. by 6 1/2 in. high overall. Require external H.T. and L.T. and one H.F. Pen. and one Det. valve, 15/-. Modern components worth more.

**SPECIAL PRECISION SYNCHRONOUS CLOCK MOVEMENTS** for public or factory clocks or for recording drums, etc., 200/250 v. 50 c. Model "A," fitted auxiliary motor for remotely starting and re-setting, for clocks up to 4 ft. dia., 49/6. Model "B," as above, but for heaviest duty, clocks up to 6 ft. dia., 59/6. Also a few, without remote setting, for dual-faced clocks up to 4 ft. dia. (also suitable for twin recording drums), 39/6. These are all first-class, brand new modern instruments.

**TIME SWITCHES,** breaking up to 10-amps. Providing 2 on-off actions per 24 hours, with vernier setting. For either A.C. or D.C. mains, any voltage and suitable for switching on and off any electrical device, radio, lights, signal, etc. With 8-day movement, 49/6. With 14-day movement, 55/-. **ELECTRO-MAGNETIC COUNTERS.** Coil res. 3 ohms or 500 ohms, counting up to 9999. Many industrial and domestic applications—checking production, phone calls, mechanical actions, etc. Hundreds already sold to large concerns. Ex-Govt. and completely reliable, 5/6.

**GEARED HIGH-TORQUE MOTORS.** Operation 15/30 v. A.C. Spindle 60 r.p.m. Reversible, with auto-2-pole make switch. For radio tuning, recording instruments, contact making, drawing cine curtains, and hundreds of other uses, 8/6. Also 200/250 v. A.C. model, very high torque, final speed 3 or 6 r.p.m. (two models). Precision made 25/-.

**G.E.C. HIGH FIDELITY MICROPHONES.** Linear response Transverse Current, Model 1575, in bronze housing with suspension hooks. (List 27 10s.) A few, brand new, at 52/6 each. Also model 1574 LAPEL type, only 1 1/2 in. sq., complete with cord and connector, marvellously efficient. (List 24 5s.) A few, brand new, at 39/6 each. Great opportunity.

**ROTHERMEL-BRUSH D.104 PIEZO-CRYSTAL MICROPHONE INSETS.** The heart of the famous D.104 5-guinea Microphone, only require housing but can be used exactly as supplied. Only 2 1/2 in. dia. Guaranteed perfect, 25/-. **MINIATURE P.M. M/COIL UNITS.** Only 3 in. dia., 12-ohms imp. For use either as mike or speaker, with excellent response, 13/6. Suitable transformer, 3/6.

**SLIDING RHESOTATS.** Fully enclosed with bushed cable entries. Fine smooth action. 4 ohms 5 amps, 10 ohms 3 amps, 50 ohms 1.4 amp., 100 ohms 1 amp., 200 ohms 7 amp., any one 13/6. Also 375 ohms 1 amp., 24/6.

**LOW TENSION RECTIFIERS.** Perm. metal. D.C. delivery 12/14 v. 1.5 amp., 10/9. D.C. delivery 12/14 v. 6 amps., 33/6. Suitable TRANSFORMERS, 200/250 v. to 7/11/15 v. 2 amps., 11/6. To 22 v. 2 amps., 13/3. Special model for 6-amp. Rectifier, for 8 and 12-rod charging (appexd), 35/-. **CADMIUM STEEL CHASSIS,** 8 in. by 7 in. Drilled for 1 valve. Ideal for power pack or larger units (strapping two together). 6 for 7/6, post free.

**ROTHERMEL PIEZO-CRYSTAL PICKUPS,** Std. model on arm, 39/6. Exact "W.W." HEAVY-DUTY OUTPUT TRANSFORMERS, 11 ratios, 12/1 to 75/1, with G.T. for P.P., high inductance, no loss, weight 7 lbs., 30/6. Also best replacement type 8 ratios, all matching, 5/6. **FERRANTI A.P.5 INTERVALVE TRANSFORMERS.** Brand new, 12/9. **G.E.C. POTENTIOMETERS,** 50,000 and 500,000 ohms only, either 2/6. **L.F. CHOKES,** 20 h. 100 m.a. 100 ohms, 8/6.

Latest supplementary list with each order.

**M.R. SUPPLIES, 68, New Oxford St., London, W.C.1**

Telephone: MUSeum 2958

# RAYMART


CRAFT A CREED

# Condensers and Dials

Owing to heavy Government demand we have considerably increased our range of Micro-Variable Condensers and Precision Dials. All have features not found in competitive makes. In the case of the Condensers—heavy all brass construction, ball-bearing spindle (electrically shorted) Ceramic (RMX) insulation, smooth operation with freedom from end or side play.


The Dials are noted for their fine appearance, accurate workmanship, and non-reflecting satin finish, graduations being deeply engraved and clear and easy to read. In addition a range of Knobs both skirt and otherwise to match these Dials are available. Full description of these instruments are available on receipt of a stamped addressed envelope.

### STANDARD (VCX) SERIES CONDENSERS

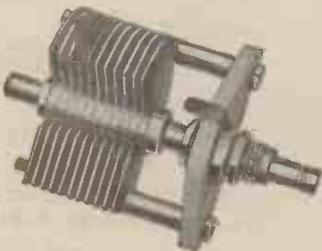


VCX

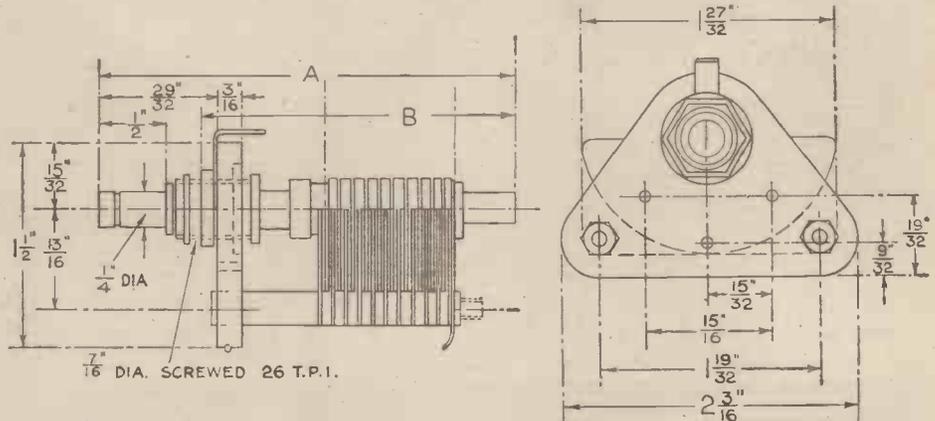
The VCX series condenser can be mounted by means of the three holes where both rotor and stator are required to be insulated from panel.



### MIDGET (MCX) SERIES CONDENSERS

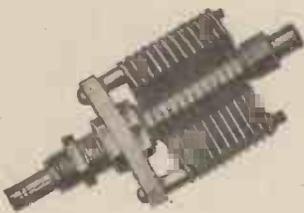


MCX

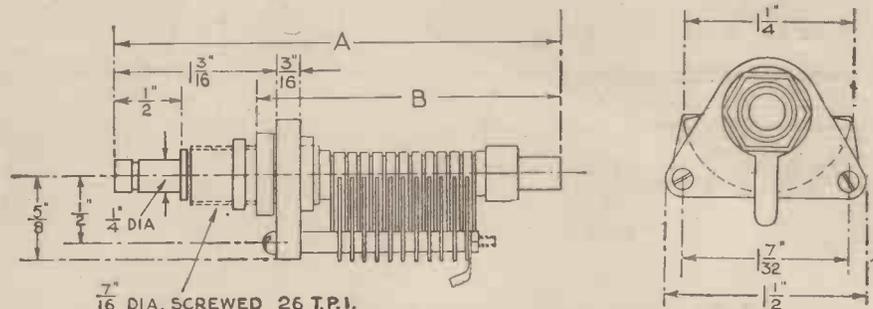

Special condensers can be made with intermediate capacities. The ganging feature may also be omitted with a consequent saving in length. Such alterations, however, can only be considered where the quantity justifies the resetting of machines to make the special parts required.

### PRECISION DIALS AND KNOBS

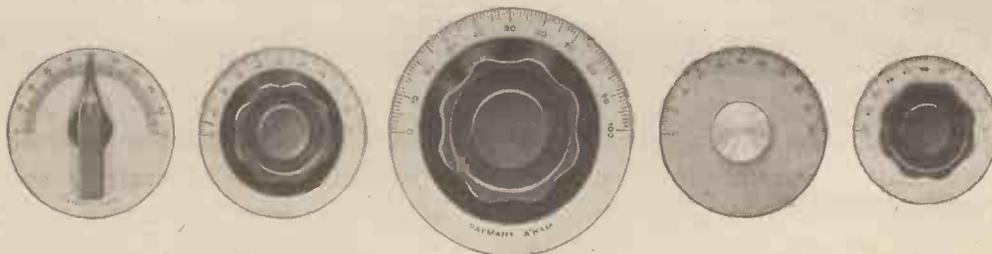

Our range of specialised short wave and communication equipment is the most comprehensive manufactured in this country.

Every necessary component for the construction of short and ultra-short wave Transmitters, Receivers, Oscillators and other scientific instruments are available. Your enquiries are solicited. Where the material is for use on Government Contract, delivery dates can be given if the priority and service is mentioned at the time of writing.

# RAYMART

CRAFT A CREED

44 & 48, HOLLOWAY HEAD, BIRMINGHAM, 1. Phone: MIDLAND 3254



# FREQUENTITE

THE PIONEER BRITISH-MADE LOW LOSS CERAMIC

THE OUTSTANDING properties of Frequentite—Low Loss and High Mechanical Strength—led to a demand which even before the war severely taxed our productive capacity. The needs of the fighting services have inevitably led to restriction in supplies for general industry, *but we can now meet all requirements*

*promptly.* Extensions to our plant, the employment of specialised new equipment, and progressive improvements in our manufacturing technique made during the past seven years, now enable manufacturers to obtain bulk supplies of the most intricate designs. Please write for Catalogue No. SP.10.

## STEATITE & PORCELAIN PRODUCTS LTD.

Head Office and Works: STOURPORT-ON-SEVERN, WORCS. Telephone: Stourport 111. Telegrams: Steatite, Stourport.

# The Wireless World

31st Year of Publication  
 Covering Every Wireless Interest  
 JUNE, 1941

Proprietors :  
 ILIFFE & SONS LTD.

Editor :  
 HUGH S. POCOCK.

Editorial, Advertising  
 and Publishing Offices :  
 DORSET HOUSE,  
 STAMFORD STREET,  
 LONDON, S.E.1.

Telephone :  
 Waterloo 3333 (35 lines).

Telegrams :  
 "Ethaworld, Sedist, London."



**PUBLISHED  
 MONTHLY**

Price: One Shilling

(Publication date 20th  
 of preceding month)

Subscription Rates  
 Home and Abroad  
 14/- per annum

EDITORIAL .. .. .	147
MAKING THE MOST OF SHORT WAVES. By L. A. Moxon, B.Sc., A.C.G.I. .. .. .	148
SHORT-WAVE RECEIVING CONDITIONS .. .. .	151
MAKESHIFTS. By W. H. Cazaly .. .. .	152
NOISE IN FM RECEIVERS .. .. .	156
REDUCING LOADING ON SHORT WAVES .. .. .	159
FREQUENCY MEASUREMENT .. .. .	160
THE PSYCHOLOGICAL PAUSE .. .. .	162
THE WORLD OF WIRELESS .. .. .	163
NEWS IN ENGLISH FROM ABROAD .. .. .	164
LETTERS TO THE EDITOR .. .. .	166
RANDOM RADIATIONS. By "Diallist" .. .. .	168
RECENT INVENTIONS .. .. .	170

Branch Offices :

COVENTRY :  
 8-10, Corporation Street.  
 Telephone : Coventry 5220.  
 Telegrams : "Autocar, Coventry."

BIRMINGHAM :  
 Guildhall Buildings,  
 Navigation Street, 2.  
 Telephone :  
 Midland 2971 (5 lines).  
 Telegrams :  
 "Autopress, Birmingham."

MANCHESTER :  
 260, Deansgate, 3.  
 Telephone :  
 Blackfriars 4412 (4 lines).  
 Telegrams :  
 "Iliffe, Manchester."

GLASGOW :  
 26B, Renfield Street, C.2.  
 Telephone : Central 4857.  
 Telegrams : "Iliffe, Glasgow."



*As many of the circuits and apparatus described in these pages are covered by patents, readers are advised, before making use of them, to satisfy themselves that they would not be infringing patents.*

Address your staff through a

## CELESTION LOUDSPEAKER

—with a volume sufficient to overcome local noise.

The same speaker will carry music to your staff—true music, not just a volume of sound.

The Celestion method of suspension enables the sound to be directed wherever you want it.

6 WATTS INPUT  
 CADMIUM PLATED  
 AND SPRAYED  
 BATTLESHIP GREY

**Celestion Limited, Kingston-upon-Thames, Surrey**  
 Acoustical Engineers

Telephone : KINGSTON 5656-7-8.



# SELECTIVITY



## SIMMONDS DOUBLE CRYSTAL FILTER

The paramount importance of high selectivity has long been recognised by radio engineers, but it is only comparatively recently that bandpass filters employing quartz crystal resonators have been made commercially available. After considerable research work our radio laboratory has evolved a new type of crystal bandpass filter employing a pair of quartz crystals, which will be found invaluable in many branches of radio tele-communication. Standard filters are available for frequencies within the range of 440-480 Kcs., having bandwidths of 300 cycles or 3 Kcs. Filters for other frequencies can be made to order. Simmonds crystal filters have an outstanding performance, including a very sharp cut-off and readily adjustable characteristics which make them very suitable for use in the Intermediate Frequency stages of super-heterodyne receivers.



**SIMMONDS AEROCESSORIES LTD.**

GREAT WEST ROAD, LONDON.



# The Wireless World

COVERING EVERY  
WIRELESS INTEREST

ESTABLISHED  
1911

Vol. XLVII. No. 1068

JUNE, 1941

Price One Shilling

## Presentation of Broadcast News

### *Is a Change of Technique Overdue?*

WHAT most technical wireless people call the "programme side" of broadcasting is little concern of ours. In conformity with the clearly expressed wishes of the vast majority of our readers, we confine ourselves to the other side of wireless—to the means rather than the end. But, although we leave the details of programme organisation and make-up severely alone, it is our duty to keep a watchful eye on the broader and more fundamental issues, especially when it seems that our medium of communication is not being used to best advantage.

Now the dissemination of news is the most important function of broadcasting at the present time, and it has long been our opinion, confirmed by careful observation of the reactions of listeners of different types, that there is room for improvement in the technique of news presentation. In the first month of the war, when the Press of this country showed signs of resenting B.B.C. competition, we urged that there was no real foundation for antagonism, and that Press and broadcasting should be complementary channels of distribution, only needing to find the right techniques for changing conditions. We said "the trouble at present is that broadcasting is too much like the newspapers, and the newspapers are too much like broadcasting."

#### *No Basic Change*

That trouble still persists after nearly two years of war. One often reads long passages in the morning papers that contain not only the substance but very often the exact phrasing of something that has been heard during the previous evening's news bulletin. The make-up and style of the broadcast bulletins has undergone little fundamental change since 1939—or, for that matter, since 1922.

As compared with the Press, broadcasting enjoys the advantages of extreme speed and living actuality. It suffers under the handicaps of being unable (in the present absence of a television service) to employ such graphical aids as pictures, maps and diagrams to explain

and amplify the news; in addition, the listener, unlike the reader of the printed page, cannot absorb information at his own pace. Consequently, news bulletins must be read at a compromise speed—too slow for some listeners and too fast for others.

These inherent advantages and disadvantages should obviously be taken into account in devising an improved technique of news presentation, and as a first step we suggest a sharp line of demarcation should be drawn between real news on the one hand, and commentary, exposition or speculation on the other. News proper might be broadcast in almost telegraphic phrasing, with the utmost economy in words. Change of speed in reading is a dramatic trick that is perhaps not to our national taste, but, skilfully done, it makes for easy assimilation of facts by the listener. The telegraphic trick of repeating numbers and extremely significant words or phrases might be helpful; the time spent in repetition would be more than offset by savings effected elsewhere. The interlarding of bulletins with "geography lessons" and passages from reference books annoys the well-informed listener, and belongs more properly to a commentary. Intuition, skill and a sympathetic outlook are needed for the arrangement of the items of a bulletin in their proper order, and pains should be taken to see that the burning question of the hour (in the estimation of the average intelligent listener) is dealt with first—even if there is "nothing to report."

#### *New-style Newspapers, Too?*

Although there has been little change in the Press so far as the fundamentals of news presentation are concerned, there seems to be a growing realisation of the fact that its function is changing. The newspaper cannot compete with broadcasting in speed of reporting events, but it has advantages in explaining and commenting on the news. This, we think, is now being realised by the Press, and we look forward to the time when the two channels of news distribution will be more nearly complementary.

# Making the Most of Short Waves

## *Improving the All-wave Receiver*

**D**URING recent years, SW broadcasting has made rapid strides. Great improvements have been made on both the transmitting and receiving sides. The number of stations operating has greatly increased; the use of beam aerials and higher powers has made better signals available; and the development of the "all-wave" superhet has extended the circle of SW listeners far beyond the select few.

There remains, however, a long way to go. Short waves still fall far short of the standard of reliability desirable, or even that to which we are accustomed on medium waves. An American station which provides excellent entertainment one evening may the next be submerged by noise, distorted by selective feeding, jammed by morse interference, or perhaps not audible at all. The reasons for this are various. In the first place, of course, we have to rely entirely on the various reflecting layers for long-distance reception, and these layers, though extremely useful, are very capricious servants. They sometimes go more or less completely on strike; at others they pass the signal on to us in a distorted, badly fading or noise-ridden condition.

It is unfortunate that the receiver tends to introduce further elements of unreliability. It adds more noise, which may entirely swamp the signal. Second-channel and other forms of interference are added by the frequency changer. It is possible for the AVC circuits to operate in such a way as to render distortion produced in transit more obtrusive, or even to produce similar distortion in a synthetic manner. In addition, the simpler receivers provide little encouragement to the listener wanting to tune in a short-wave signal, and he may be compelled to exercise great skill and patience.

All these deficiencies in the

By **L. A. MOXON, B.Sc.,  
A.C.G.I.**

receiver present serious problems to the designer, and it is the purpose here to show how they can be overcome or minimised. The value of an RF stage for improving the ratio of signal to noise, and reducing second-channel interference is well known, and some design considerations for making the best use of it will be outlined. Band-spreading will be considered in some detail as it is essential to a solution of the tuning problem; the latter also demands a very high degree of "staying put" on the part of the oscillator circuits, and the very accurate scale calibration that this makes possible. The uses of double frequency changing will be discussed, and finally a number of minor design points which repay attention will be considered.

### **Importance of an RF Stage**

Engineers, yielding to public demand, have evolved what might almost be called a standard receiver; the familiar three waveband, four-valve superhet with frequency changer, an IF stage operating at about 465 kilocycles, double-diode triode for detection, AVC and AF amplification, and a high-slope output pentode. This design can give quite good results, but requires elaboration if a maximum of short-wave reliability is to be approached. Probably the first essential is to increase the signal-to-noise ratio by addition of an RF stage.

There are two main sources of noise in receivers, the tuned circuits and the valves. Assuming adequate gain from the first valve, only this and the preceding circuits need be considered, since other sources of noise will have much less amplification following them. In any con-

ductor a certain amount of noise is generated by thermal agitation of electrons, and the voltage produced is proportional to the square root of the impedance of the conductor. In the case of SW tuned circuits, low impedances are the rule and circuit noise can usually be neglected in comparison with valve noise. The latter can be taken as proportional to the square root of the anode current,  $I$ . Although not strictly true when applied to different types of valve, this has been found a useful guide in practice. As amplification of the signal is proportional to the effective conductance  $G$ , we can state

Signal-to-noise ratio =  $\frac{G}{\sqrt{I}}$  × a constant.

Mains RF pentodes and hexodes all take very roughly the same anode current. The advantage of having, as first valve, a variable- $\mu$  pentode with a  $G$  of 2.4 over a frequency changer with a conversion conductance of 0.8, is obvious, and measurement confirms the expected improvement of 3 to 1. A television type of RF pentode used with a working slope of 7 gives a further reduction of 3 to 1 in valve noise which is then comparable with the circuit noise. This limits the additional improvement to about 2 to 1. If a high-slope RF valve is fitted, its use is best confined to short waves. Such valves are not in general suited to medium wave use on account of their very limited signal-handling capacity and the large signals likely to be applied. They offer no compensating advantage, since thermal noise on medium waves limits signal-noise ratio to that obtainable with a low slope valve.

The gain of the RF stage may be regarded as just adequate if it is equal to the improvement in signal-noise ratio expected from the stage. Under these conditions a quota of noise will be added by the frequency changer equal to that which the

## Making the Most of Short Waves—

signal has collected from the RF valve. The RMS addition of the two components gives an increase of 3 db. in total noise, and this is only just appreciable. It may be possible to get greater gain, but noise level sets a limit to the amount of sensitivity which can be usefully employed. This limit can be achieved in practice (with or without an RF stage) by making the FC, IF, AF and output stages as efficient as possible. Unnecessary RF gain is harmful for the following reason.

Over a range of a few hundred kc/s on either side of the frequency to which the set is turned, little attenuation can be expected from the signal circuits, and all stations within this range will reach the frequency changer. If two signals which happen to be spaced by a frequency equal to the IF of the receiver are present in sufficient strength, they will beat together to produce an appreciable IF component, which may cause interference with all weak stations over quite a wide tuning range. The RF stage amplifies not

of the low slopes, it appears essential to use tuned anode couplings in order to get adequate gain. With mains valves some form of transformer or tapped coil coupling is usually more satisfactory.

The additional tuned circuit that an RF stage brings with it is some help with image rejection. In an

the effective impedance, and therefore gain by the factor

$$\left[ \frac{C_s}{C_s + C_p} \right]^2$$

An average value for  $C_s$  may be about  $25\mu\mu\text{F}$ , and  $C_p$  can be kept down to about  $30\mu\mu\text{F}$ . At 16 metres a coupling impedance of more than

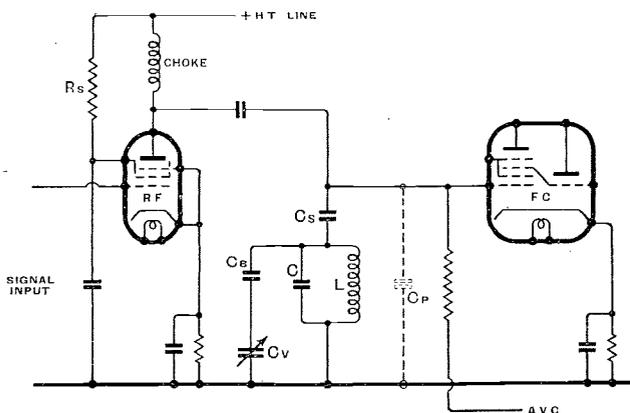


Fig. 2. Showing application of image rejector to a practical design: switching complications omitted.  $C_p$  represents the stray capacities across the coupling impedance. For band-spreading a section  $C_v$  of the gang condenser is connected, in series with a small capacity  $C_b$ , across the circuit LC.

average design, with an IF of 465 kc/s, it contributes some 12 db. to a total of 20 db. rejection at 15 megacycles. This is not a very satisfactory improvement, and in one receiver\* a further 10 db. was obtained by using a band-pass intervalve coupling.

### Image Rejection

In a later receiver a total of 40 or 50 db. rejection was obtained by means of a simple image rejector of which Fig. 1 shows the principle. This circuit, used as an anode coupling impedance, would give maximum gain at the resonance of LC. At some lower frequency the circuit LC, looking like an inductance, with  $C_s$  and produces a very low impedance. This can be utilised for image rejection by suitable choice of  $C_s$ . The practical application of the circuit is illustrated by Fig. 2. Its working is somewhat modified by the capacity  $C_p$  consisting of various strays—the interelectrode capacities of the RF and FC valves, the self-capacity of the HT feed choke, wiring, and possibly switch capacities. These must be kept as low as possible, since their effect is to reduce

1,000 ohms is unlikely, but this is adequate if a high-slope valve is used. From 25 metres upwards the gain may then be excessive unless  $R_s$  or  $C$  is increased.

Fig. 3 shows the measured selectivity of the image rejector at 15 Mc/s compared with the estimated performance of a simple circuit with similar losses. The tapping-down effect of  $C_p$  helps to keep the losses low and improves the suppression of double beats as well as images.

It will be appreciated that the oscillator must be tuned to a lower frequency than the signal. In theory,

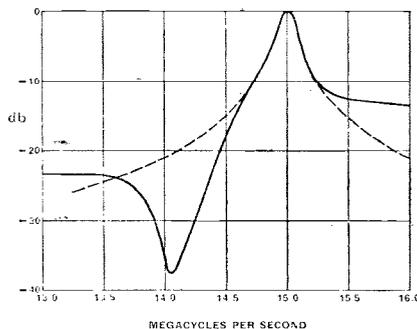


Fig. 3. Measured selectivity of image rejector at 15 Mc/s. The estimated curve for a simple tuned circuit with similar losses is shown in dotted lines. Some additional selectivity is given by the aerial circuit.

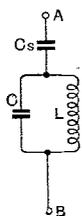


Fig. 1. Basic circuit of the simple image rejector described in the text. In the absence of circuit losses, the impedance between A and B would be infinite for the wanted signal and zero for the image.

only the wanted, but *both* the unwanted stations, and the interference tends to be increased in proportion though some help is afforded by the selectivity of the usual extra circuit. Those who like "gadgets" may find a variable gain control useful. Otherwise slightly more than the "just adequate" gain is quite a good compromise. Some increase in gain may be permitted on the longer SW bands in view of the greater signal selectivity, but it is desirable to avoid extreme variations over the frequency range. This argument does not apply to receivers with double frequency changing and a high value of first intermediate frequency.

Battery valves have much lower values of both  $G$  and  $I$  than mains valves, and are about the same from the noise point of view. On account

\* The Murphy Model A76.

## Making the Most of Short Waves—

Cs could be replaced by an inductance and the oscillator tuned high, but in practice difficulties arise over stray capacities.

This circuit was developed for use with a band-spread receiver using switched inductances pre-set to each of the short-wave broadcast bands (the Murphy A92). The value required for Cs depends on C, Cp and the IF. It was not found to be very critical, but had to be changed for each band, with the exception of 25 and 31 metres, which were able to share one value.

Most short-wave broadcasting stations lie within seven narrow bands, all less than 300 kc/s in width and centred around 6.1, 7.25, 9.6, 11.8, 15.22, 17.8 and 21.6 megacycles respectively. It is standard practice to cover the entire frequency range, or at least up to 18 Mc/s, by capa-

desired frequency. There are many possible means to this end, as illustrated in Fig. 4. Referring to this family tree, the left-hand side requires little discussion; slow-motion drives and mechanical or optical

condenser at specified points. This may consist of a notched disc with a spring-controlled arm locating in the notches and giving a definite "feel" to the correct setting. An auxiliary means of tuning with its


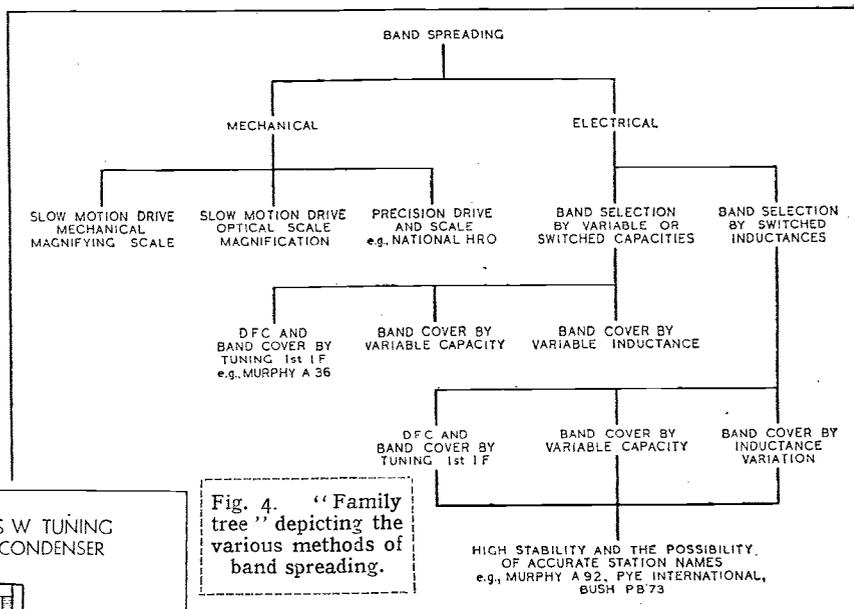


Fig. 4. "Family tree" depicting the various methods of band spreading.

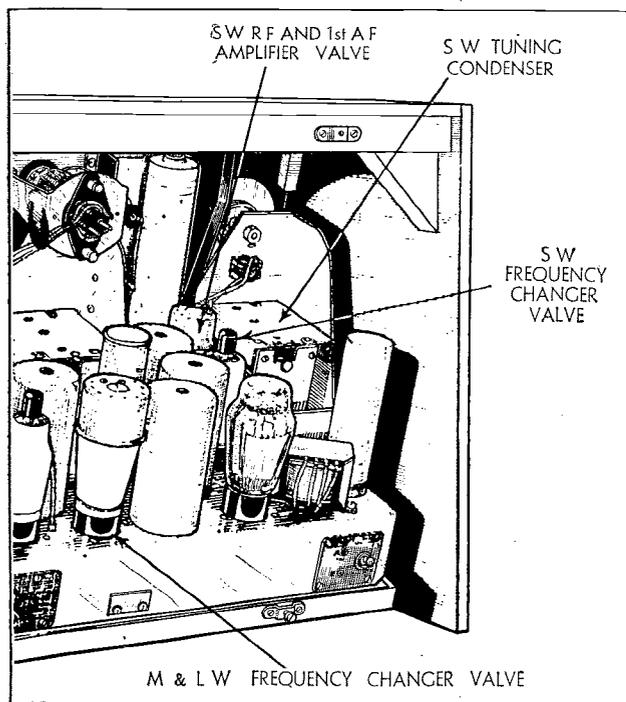

(Left) Components associated with the double frequency-changing system of the Murphy Model A36 receiver.

magnifying scales are very useful devices, but the very high mechanical standard required by the ideal is not readily achieved in mass production. Some American communications receivers employ very successful precision drives and geared-up scales which

enable the receiver to be tuned accurately to any desired frequency within a wide range. For broadcast reception there is some advantage in being able to switch rapidly from one band to the next without tuning through a lot of intervening noises, and this is most readily achieved by electrical band-spreading methods.

One interesting method is to provide means of arresting the tuning

own scale must be employed to cover the bands thus selected. This method was employed some years ago on the Murphy A36 receiver, which employed double-frequency changing. SW signals were converted to an intermediate frequency in the medium-wave band, and tuned-in as medium-wave signals. The medium-wave tuner, therefore, provided the auxiliary means. An alternative would be to vary the oscillator inductance about 8 per cent. by means of an iron dust core or piece of non-ferrous metal moving inside it. A small auxiliary tuning condenser can be used, but is not satisfactory over a wide tuning range. A given spread at 6 Mc/s, compared with 18 Mc/s, would require 27 times as much charge of capacity, so that full cover of the former would severely cramp the latter. The inductance method possesses the same fault, but only to the extent of 3 to 1, which is tolerable. The double-frequency changing method described has the advantage of a constant band-spread scale calibration in terms of frequency differences. That is to say, a difference of 100 kc/s on the band-spread scale remains 100 kc/s whatever the

city variation and a single set of tuning inductances. As each station's share of the tuning scale is less than a thousandth part, it is not surprising that tuning tends to be difficult.

The useful portions of the tuning range constitute only a small proportion of the total. It is the function of band spreading to open out the wanted parts of the scale and make it easy to adjust the receiver to the

band selected by the main tuning control.

All systems which cover a wide frequency range by variable capacity share one disadvantage: that of tuning drift on the higher frequency bands, especially during the warming-up process. This is discussed in the next instalment. No wide-range inductance tuning devices are available, and the only alternative seems to be the use of separate oscillator inductances for each band, selected

by a switch. This is no longer the formidable problem it would have been some years ago, thanks to the development of iron-dust cores which enable compact and easily adjustable coils to be constructed. In this way it is possible to produce really stable circuits, and there are two alternative methods of band-spreading, with a possible third. These will be described and discussed in a concluding instalment.

(To be concluded.)

# Short-wave Receiving Conditions

PROSPECTS FOR JUNE

(COMMUNICATED BY THE ENGINEERING DEPARTMENT OF  
CABLE AND WIRELESS, LTD.)

ALTHOUGH somewhat more settled than during the preceding month, short-wave receiving conditions during April were, nevertheless, not as favourable as those during the corresponding month of 1940.

Ionosphere storms occurred on fifteen days of the month as follows: On four consecutive days commencing April 10th and 18th and, in addition, on the 3rd and 7th (first week) and on the 24th, 25th, 26th, 28th and 29th (last week). In this connection readers of these reports may recall that, in the April issue of this journal, published on March 20th (see page 118), the possibility of a relatively high disturbance factor was suggested for a few days in the vicinity of April 9th and 17th and, in addition, at the beginning and end of the month.

Sudden ionosphere disturbances of the Dellinger type occurred as follows, these and other times given in this report being G.M.T. on the 24-hour clock notation: (A) April 19th at 1019, (B) April 20th at 1040.

The effects of (A) and (B) were in each case confined mainly to easterly and southerly routes, and were in evidence for a period of about fifteen minutes; those on April 19th were, however, the more pronounced.

Particulars of the broadcast bands which, it is considered, should prove most reliable during June under normal conditions of propagation at the times stated for five selected routes are given below; these may serve as a guide when considering the possibilities of reception from places not too remote from those specified.

Attention is drawn to the fact that a number of factors, for example, (a) transmitting power, (b) efficiency of aërials at both the transmitting and receiving end, and (c) ionosphere abnormalities, may often result in

better reception being obtained on wavebands other than those quoted. Moreover, transmission on each of the stated wavebands may not necessarily be available.

**Tokio:** Midt, 19 or 25 m; 0400, 19 m; 0700, 16 or 19 m; 1000, 16 m; 1300 and 1500, 16 or 19 m; 1800, 19 or 25 m; 2000, 19, 25 or 31 m.

Whereas in winter difficulties may be encountered for several hours on this route, in summer, and in particular during the month of June, favourable conditions persist throughout most, if not all, of the 24 hours. Echo effects may be prevalent during the period 1900 to 2100.

**Montreal:** Midt, 25 or 31 m; 0400, 31 m; 0900, 19 or 25 m; 1100, 1500 and 1900, 16 or 19 m; 2200, 19 or 25 m.

Under normal propagation conditions the most favourable period for reception should be between 1200 and midnight. The most difficult period is likely to be for a few hours in the vicinity of 0700.

**Singapore:** 0100, 19, 25 or 31 m; 0500 and 1000, 16 m; 1500, 16 or 19 m; 1900, 19 or 25 m; 2200, 25 or 31 m.

The period from 0100 to 0500 is expected to be a difficult one; in addition, the route may on occasions be subject to echo effects for one or two hours around 0700 due to signals traversing the major arc of the Great Circle (i.e., via Southern Australia and West Indies).

**Salisbury, Rhodesia:** Midt, 25 or 31 m; 0300, 31 or 41 m; 0600, 16 or 19 m; 1000 and 1400, 16 m; 1700, 16 or 19 m; 2000, 19 or 25 m.

Conditions should be favourable for reception throughout most of the 24 hours; signals may, however, be subject to echo effects around 0400 and to weakness for a short period around 1100.

**Rio de Janeiro:** 0100, 25 or 31 m; 0500, 31 m; 1000 and 1500, 16 m; 1800, 16 or 19 m; 2200, 19, 25 or 31 m.

Signals may be subject to weakness between 0500 and 1000 and to echo effects for one or two hours around 2000.

In temperate latitudes in the Northern Hemisphere, the highest values of critical frequency (F layer) usually occur during winter day and the lowest during winter night; the values for summer, both day and night, are normally between these two extremes.

As a result of the smaller range of critical frequencies encountered in summer, the usefulness of a frequency band employed for inter-communication within the Northern Hemisphere at this season may extend over several hours; in fact, under favourable conditions satisfactory long-distance communication (for example, with the Far East) may often be carried out for over 24 consecutive hours without the necessity of a change of frequency.

The E layer, in contrast to the F layer, has its maximum critical frequency in summer at about local noon; in consequence, under certain conditions of layer height it may frequently become the controlling factor in "skip-distance" calculations, particularly during late forenoon and early afternoon.

At the time of writing this report it would seem that conditions during June, and particularly during the latter part thereof, are likely to be more stable than of late.

## Maintaining a Service

ALTHOUGH some journals, especially those from the Western Hemisphere, at times fail to reach this country owing to enemy action, every effort is made to obtain duplicate copies or, if this is not possible, photostat reproductions of the journals, in order that the Abstracts and References section of *The Wireless Engineer* may be a complete bibliography of articles on wireless and allied subjects published in the world's journals.

In this section of our sister journal the space devoted to abstracts from journals published in enemy countries is considerable. This fact has greatly enhanced the value of the section.

In addition to some 280 abstracts and references, the May issue contains articles on the rhombic transmitting aerial and receiver aerial coupling circuits.

Published on the first of the month, *The Wireless Engineer* is obtainable to order through newsagents, or direct from our publishers at Dorset House, Stamford Street, London, S.E.1, at 2s. 6d., including postage.

# Makeshifts — Wartime Measures to Meet a Shortage of Servicing Components

By W. H. CAZALY

IT must be made quite clear at the outset that the advice that follows on alterations to the circuits and components of probably very well designed receivers is necessarily of a generalised nature, and that the results that may follow on such alterations cannot be forecast with certainty. There is far more than meets the eye in even an apparently simple design of commercial broadcast receiver, and improvement seldom accrues from incautious and unintelligent "monkeying" with the products of experienced circuit engineers. On the other hand, we are faced nowadays with exceptional conditions, and if a receiver is put out of commission through a lack of some component that is unobtainable, it is worth while making some attempt to get it going again, even if the attempt is not very successful. After all, the patient can only be killed once! And the maintenance of domestic radio reception in these days is of such importance—it may even be a matter of life or death—that liberties with the circuits may be permitted that would be rightly frowned upon in less unsettled times. It must be borne in mind that many of the factors involved in successful emergency adaptations will be peculiar to the particular cases the reader has to deal with and cannot be foreseen by the author. If some suggested alteration does not work, it may be either because the components involved are unsuitable for change, or because all the factors operating have not been taken into account. The only thing to do is to have a shot at it, anyway. With this warning, one can now proceed

## Valve Types

A shortage of replacement valves is likely to cause the greatest difficulties. Receivers may have to be adapted to work either with valves of characteristics different from the originals or without certain valves. As used in the stages of a typical superheterodyne receiver, valves fall into functional categories that will be dealt with in turn.

If a signal-frequency RF valve breaks down, reception is still possible without further alteration if the aerial is connected directly to the grid of the frequency-changer, via a very small pre-set condenser, which should be ad-

justed to suit the aerial used. A certain all-round reduction of goodness of performance may be noticed; the signal/noise ratio may be higher than previously, especially on short waves, and AVC may not operate quite so efficiently. Local station reception will be hardly affected.

If a spare valve of a different make is available with characteristics similar to those of the original, probably no alteration at all will be necessary. If, however, the replacement valve is not of the variable mu type—it may be an old tetrode—it will be better to use it in the IF stage, and to place

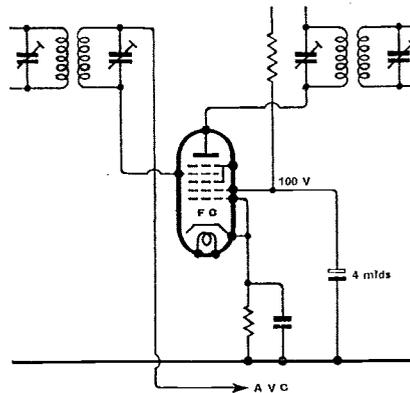


Fig. 1.—A frequency-changer valve may often be used as an IF amplifier if the oscillator grid and anode are given fixed working potentials as shown.

the IF valve thus released in the RF stage. The AVC feed to the new IF valve should be disconnected and the grid returned to the chassis or to some point of negative potential if it is of the type that requires negative bias to keep it stable. If the new valve is not metallised, possible instability from this source may be avoided by covering the glass envelope with "silver" foil (in one continuous piece) and earthing this foil to the chassis.

It is possible to make use of a frequency-changer as an amplifier, employing only the signal amplifying portion and earthing the oscillator grid, while the oscillator anode is taken to a suitable point at HT and earthed by a condenser. This is shown in Fig. 1.

The frequency-changer offers more

serious problems. It cannot be dispensed with, and of whatever type the replacement is, it must make the best use it can of the existing oscillator circuits. The values of inductance and tracking capacities of this circuit will have been taken care of by the designers, and it is inadvisable to attempt any alterations in this direction. All that can be done is to connect the existing oscillator assembly leads to the appropriate pins of the replacement valve. This subject is rather too involved for adequate treatment here, but it is hoped to return to it in a later article.

## Dispensing with the IF Amplifier

Should an IF valve break down, the choice of a replacement—if one is available—should be governed by the considerations outlined for the case of an RF valve. If no RF valve of any kind is available, the IF amplifier must be dispensed with and the output of the frequency-changer fed direct to the diode rectifier. Local station reception at least will still be possible, but considerable loss of volume and selectivity may make the set almost useless for anything more. The arrangement is shown in Fig. 2. If the lack of a suitable IF amplifier is likely to be prolonged or permanent, it may be best to dispense with AVC and replace the diode rectifier with a leaky grid detector—utilising, perhaps, the existing triode portion of the DDT. This is a more sensitive type of detector than is the plain diode. To increase signal strength, it may be worth while to attempt to use fixed reaction on the IF coil. For this, some thirty or forty turns should be wound on the IF coil former about half an inch away from the secondary; if the winding is put on as if it were a continuation of the secondary, reaction will be in the right sense. This reaction winding can be energised from the anode of the leaky grid detector through a pre-set condenser. A little experimenting with the number of turns will be necessary, and when stable reaction—not oscillation—is obtained, it should be left fixed (not too near the point of oscillation, or quality will suffer badly) and the transformer tuned to the IF. Band-pass response will be poor, but this trick may add a little much-needed strength to the signal. The AVC line should be taken direct to

## Wireless World

some earthy point—depending on whether the frequency-changer does or does not require a steady initial bias. It may be worth while, in this connection, to take this AVC line to a potentiometer across some source of considerable bias and use it as a RF manual volume control.

The above outline partly covers, evidently, the procedure possible to adopt if the double-diode-triode breaks down and cannot be replaced. Since the

another value calculated from the formula

$$\frac{\text{Bias voltage required}}{\text{Total anode current taken with new valve}}$$

Current is expressed as a fraction of an ampere.

When changing from triode to pentode output, of course, an extra lead to HT will have to be provided for the pentode screening grid. Quality will be appreciably improved by fit-

sistance, the maker's figures should be consulted to see if the original resistance is approximately correct. If it is not, it will have to be replaced by a calculated value based on the anode current of the valve and its correct bias at that value of anode current. If a pentode is substituted for a triode, the speaker transformer should be replaced by a more suitable one in the interests of quality, but if this cannot be done, quality can be partially preserved at the expense of sound volume by connecting a resistance of the order of anything from 4 to 20 ohms, as determined by experiment, in series with the speech coil.

It is not advisable to try to replace the original output valve by one taking considerably more anode current. If one taking appreciably less anode current is used as a substitute valve, it will be possible to make up for the lower total anode current of the set by connecting a resistance across the HT smoothed power supply, as shown in Fig. 3. If such a "bleeder" resistance is not used, the lower anode current through the speaker will not only insufficiently energise its field, but will raise the anode voltage on all the valves, which is not good for them and may set up instability. Also, the change in anode current and consequent anode voltage caused by the action of AVC on controlled valves will lessen the effect of AVC and may cause a kind of motor-boating. The wattage of the "bleeder" resistance should be

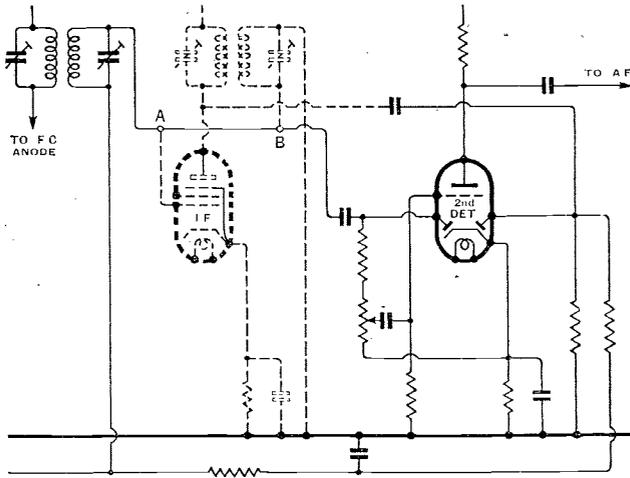


Fig. 2.—An unused IF stage is shown in dotted line. The connection from the first IFT secondary, A-B, should be as short and direct as possible to avoid coupling with other parts of the circuit; it may even have to be of screened wire. Re-adjustment of the first IFT trimmers will probably be necessary.

signal strength in a superhet is normally considerable by the time it reaches the rectifier circuit, it may be well to try anode-bend rectification, since this deals with signals of considerable strength without the distortion—within limits—that might easily arise with leaky grid detection. AVC must be dispensed with. "Power grid detection" may also be utilised, but this is likely to put an excessive load on the HT battery in a battery receiver, since the current taken with the high anode voltage required and no bias may be several mA. This high anode current will preclude the use of resistance-capacity coupling to the output stage and a transformer will have to be used—not more than 1:1.5 step-up—so that it may be inconvenient.

### Replacing Battery Valves

The output stage of a battery receiver presents straightforward problems. A pentode and a triode output valve may be exchanged, if due attention is paid to matters of bias. The comparative inefficiency of the triode may to a certain extent be offset by turning up the volume control. If bias is obtained "automatically" by the potential developed across a resistance in the HT negative lead, this resistance may have to be changed for

ting a correctly wound transformer to match the pentode to the speaker. If one of the pentodes used in a QPP output stage breaks down, the remaining one can be used without more alteration than reducing the bias—which will be obtained from a battery—so that it falls on the midpoint of the straight part of the  $I_a/V_g$  characteristic curve. Output will be considerably reduced and the volume control will have to be turned down. Class B output is not much used nowadays, but if a breakdown occurs in such a stage, it will be best to replace the whole of it by pentode output. For this, a bias battery and a new intervalve transformer will be needed, the latter to replace the original Class B driver transformer, which, having a step-down turns ratio, is quite unsuitable for ordinary use.

The output stage of a mains receiver presents much more serious problems, because it normally accounts for more than half the total anode current, upon which depends the energising of the speaker field coil, the anode voltage applied to the valves (through the voltage drop in the field coil) and, perhaps, automatic bias to valves other than the output. If possible, the replacement valve should take nearly the same anode current as the original valve, and if the bias is obtained by a cathode re-

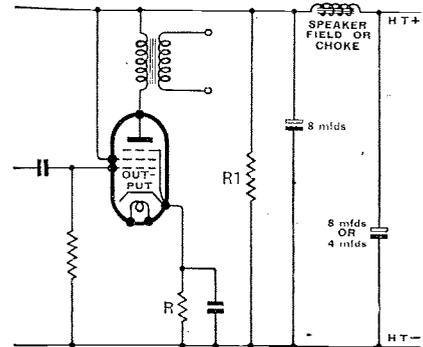


Fig. 3.—Alterations consequent on the fitting of a replacement output valve taking a considerably lower anode current than the original. The value of the bias resistance R will be  $\frac{E \times 1000}{I}$ ,

where E is rated bias voltage and I total anode current in mA. The added "bleeder" resistance R1 will be  $\frac{250 \times 1000}{I_1 \times I_2}$  ohms, where I1 is total anode current of original valve and I2 is that of substitute valve, both in mA.

## Makeshifts—

ample for continuous passing of the current. It should not be forgotten that even a general-purpose triode, passing only about 5 mA with 250 volts on its anode, can give an output that is enough for many domestic purposes. If such a triode replaces a pentode that took 40 mA, the "bleeder" will have to carry 35 mA at 250 volts—i.e., be 7,000 ohms rated at 8 watts minimum.

If one of the pentodes in a mains push-pull output stage goes out of commission, probably it will still be possible to use the remaining valve as a straight output pentode, but a "bleeder" will be necessary to pass current equal to that passed by the defunct valve, and also it will be necessary to examine the bias resistance circuit. If bias was originally obtained through a resistance common to both cathodes, the resistance should be doubled in value (so that the original bias is developed across it with the anode current of only one output valve passing through it). Another trouble may arise from an increase of hum after the change has been made. The only remedy for this lies in an increase of the smoothing in the power supply, preferably by the use of an extra condenser in parallel with the existing smoothing condenser.

The rectifier presents a very awkward problem if it cannot be replaced by the usual diode type. If by a lucky chance the receiver happens to be of the AC/DC variety *and is being used*

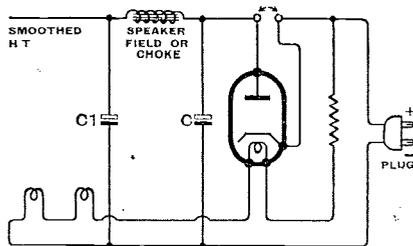


Fig. 4.—The rectifier of an AC/DC set may be dispensed with on DC mains (not AC), by joining the cathode and anode sockets on the valve holder, as shown. As C and C<sub>1</sub> are polarised electrolytics, the mains polarity must be correct.

on DC mains, the rectifier can be cut out altogether, as shown in Fig. 4. But, in this case, certain precautions must be taken. The mains plug *must* be plugged in "the right way round," because the smoothing condensers will be polarised and will blow up if the mains supply connection is reversed.

The best thing to do is to fit a non-reversible plug and socket, so that, in the course of domestic upheavals consequent upon dusting and such-like non-technical interference, the lay person cannot reconnect the set wrongly. Moreover, in case the receiver should be taken to a district supplied from AC mains, connection to which of the altered circuit will have disastrous results, a note about the alterations should be stuck to the back of the set in a conspicuous place.

Mention must be made of the possibility of using valves with different heater voltages and currents. Thus, 4-volt AC valves might be replaced by the 6.3-volt variety or vice versa. The safest and best way of doing this is to provide a separate filament or heater transformer for the new valve or valves, the design of which can be readily worked out from the *Wireless World* Data Charts, based, perhaps, on laminations from a good-sized unwanted choke or AF transformer. In such a case the load provided on the heater windings of the existing mains transformer by the valves that have been replaced must be simulated by a resistance, in order to prevent undue rise of heater voltage which would damage the original valves still remaining. Thus, if two 4-volt AC valves taking 1 A each were taken off the 4-volt heater circuit, their heaters would have to be replaced by a resistance of 2 ohms capable of passing 2 A. Or, if one 6.3-volt valve were taken out, the load its heater represents (at 0.3 A) would have to be replaced by 21 ohms. A small heater transformer is not very difficult to make, and care only has to be taken over insulation and layer-winding of the primary. The connections are shown in Fig. 5.

## Extra L.T. Winding

Another possibility is that of making a small low-voltage auto-transformer fed from the original heater circuit. Yet another way, if room can be found for it on the original transformer, is to put on an extra winding; the extra load will probably not make much difference to the heating of the transformer. It involves finding the number of turns used in the original heater winding, by counting them or by calculating from the ratio of input primary volts to the output volts of this heater winding (ascertained preferably by an AC meter), the turns needed for the new secondary. Results should always be checked up by an AC meter, as incorrect heater cur-

rent will seriously shorten the life of a valve.

The volume control is another component that may be difficult to replace.

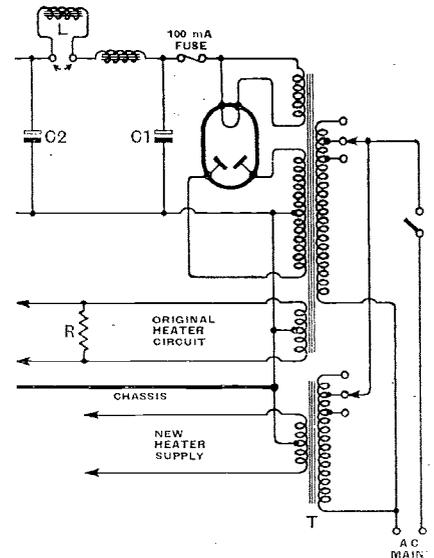


Fig. 5. Connections of an extra heater transformer T. R is a resistance to compensate for reduction of load on the original transformer, L is an extra choke, of 10 to 15 H, that may be inserted when more smoothing is required.

If only one of a lesser resistance value is obtainable, it may be possible to use it in series with a resistance that will make up the total to the value of the original. Control will only be partial and, if the slider of the new component is insulated from chassis, the series resistance may be put either at the "live" end—if loud volume is seldom wanted—or at the earthy end, if the set is normally used at average or considerable volume. If the new component is of higher value, it can be put in parallel with a fixed resistance, so that the combination will make up the original load on the diode, as can be calculated from the

formula  $R_1 = \frac{R \times R_2}{R_2 - R}$  where R is the value of the original volume control. R<sub>1</sub> is that of the fixed resistance, and R<sub>2</sub> that of the new volume control.

If no replacement volume control at all is procurable, it is possible to use a step control, with a stud switch and a string of resistances. Even a 3-way switch will provide a useful measure of control, by providing high, medium and low levels, the medium being fixed at the most favoured level. Another way of controlling sound output if the earlier stages of a receiver are already taken care of by AVC is to provide attenuation in the speech coil circuit, as shown in Fig. 6.



# Noise in FM Receivers

## Further Light on the Behaviour of Discriminator and Limiter Circuits

THE problems of noise in frequency-modulated systems have been carried a stage further towards solution by a very methodical series of investigations with the cathode ray oscillograph on the life history of a noise pulse in its passage through the receiver.<sup>1</sup>

It has been shown that when a noise pulse of very short duration is applied to the input of a receiver, the output is in the form of a train of waves having a frequency the same as that at the centre of the IF passband, and a duration equal to the reciprocal of the cut-off frequency. With the usual FM band width of 200 kc/s the cut-off frequency would be 100 kc/s and the duration of the pulse 10 microseconds. Thus, with an intermediate frequency of 5 Mc/s, there would be 50 cycles in the wave-train.

The shape of the envelope of this wave-train is determined by the shape of the selectivity curve and a double-peaked curve results in the formation

topped, but disappears when the curve is rounded. Lack of symmetry tends to fill in the valley between the two lobes as in Fig. 1D.


The discriminator output resulting from noise wave-trains of different types is a useful indication of errors of alignment in the RF circuits. If the low-frequency peak is higher than the other, the discriminator output has the form shown in Fig. 1E. If the high frequency peak is greater, the output falls below the zero line as shown in Fig. 1F. Similar curves to these are obtained by mistuning the secondary of the discriminator one way or the other.

The usual discriminator output consists of two separate diode circuits connected in series, and these should be balanced from the point of view of frequency response. The output circuit is earthed on one side and not at the centre, so that it often happens that there is more capacity across one

of the wave-train was considerably modified by the signal strength, and this was found to be due to the effect of grid current in altering the tuning of one or more of the RF circuits. The limiter grid circuit was, of course, the worst offender, and some idea of the magnitude of the detuning effect which may be met with is given by the curves in Fig. 2.


The trouble may be minimised in several ways. A larger tuning capacity giving a lower L/C ratio may be used, or the circuit response may be broadened by damping. Another useful expedient is to ensure that both primary and secondary of the RF transformers have circuits of equal Q, and that less than critical coupling is employed.

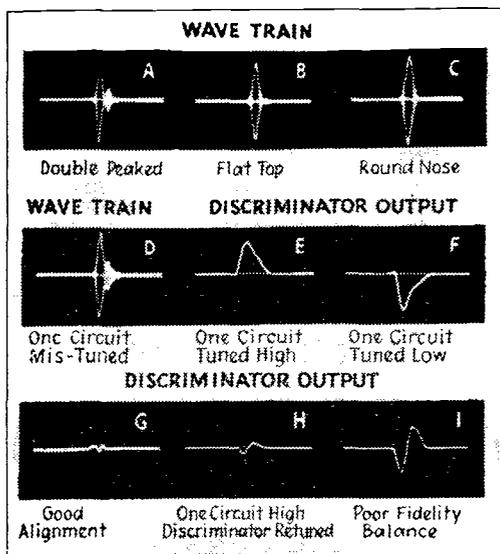The oscillograms shown so far were taken with noise only and they are not valid for signal-to-noise ratios of more than 1/10. For higher signal-to-noise ratios, the noise output is a function of the interaction between the sig-



(Left) Fig. 1. Oscillograms of noise wave-train (A to D) and output from discriminator (E to I). The lack of balance in the last oscillogram is equivalent to 10  $\mu\text{F}$  across 100,000 ohms on one side of the output circuit.

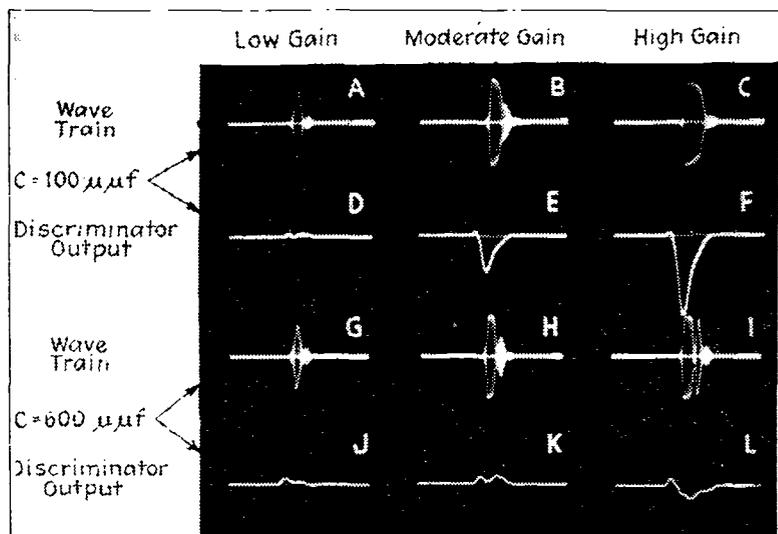(Right) Fig. 2. Illustrating the detuning effect of grid current at high noise amplitudes. The more marked valleys between lobes in G, H and I indicate that mistuning is less with a lower L/C ratio (larger tuning capacity, C).



of a marked secondary lobe as shown in Fig. 1A. The secondary lobe is still discernible when the response is flat

side than the other. The effect of an out-of-balance capacity of 10  $\mu\text{F}$  across 100,000 ohms is shown at I in Fig. 1.

At an early stage in the investigations it was discovered that the shape

of the noise wave-train after passage through the RF circuits. The result may be amplitude or frequency modulation, or a combination of both, depending on the phase of the noise and carrier waves.

<sup>1</sup> "Impulse Noise in FM Reception," by V. D. Landon, *Electronics*, Feb., 1941.

## Noise in FM Receivers—

To investigate the matter more closely, special equipment was built to ensure constant phase relationship between the signal carrier and noise impulse generators. A 10,000 c/s

o deg. and 180 deg., amplitude modulation is at maximum and frequency modulation, as shown by a small discriminator output, is at minimum, while at 90 deg. and 270 deg. the conditions are reversed. At intermediate

these oscillographic records that frequency as well as amplitude modulation may result from noise impulse, and the action of the limiter stage was accordingly further investigated.

In Fig. 4 the wave-trains resulting from the injection of a noise impulse are shown for various signal-noise ratios, and phase relationships. The amplifier gains have been adjusted to show the action both above and below the threshold of the limiter stage. In the plate voltage limiter a low anode voltage is used, and the RF swing at the anode is limited to something less than the DC anode volts. The grid leak limiter depends for its action on the self-biasing action of the valve caused by the flow of grid current in the leak as the signal is increased. Values of 100,000 ohms and 20  $\mu\mu\text{F}$  were used in the limiter grid circuit to give as short a time constant as possible.

It will be seen that from the point of view of amplitude modulation the grid leak limiter is not as good as the plate voltage limiter. The grid condenser does not charge up quickly enough to follow the rising front of the impulse. Also, when the response starts there is a tendency for the valve to over-bias, and the carrier is attenuated for a short time after the pulse has ceased, until the mean grid voltage is restored.

By themselves the oscillograms of Fig. 4 do not tell the whole story. The curves of Fig. 3 show that amplitude

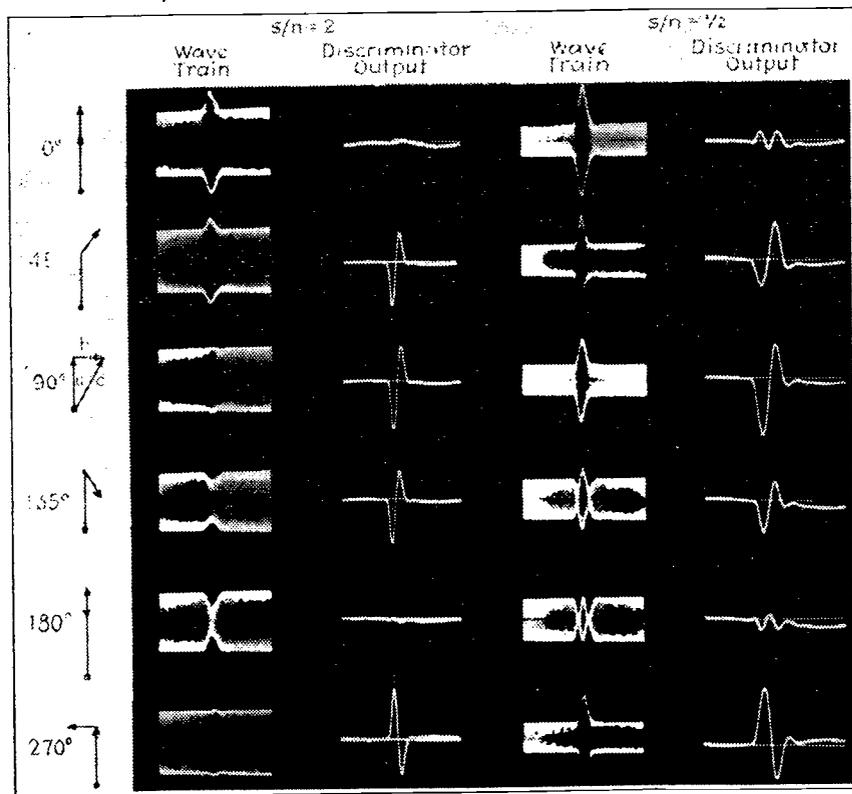


Fig. 3. Oscillograms, in the presence of a signal, of noise wave-trains and discriminator output for different phase angles between the noise impulse and signal carrier. In the right hand set of records the signal-to-noise ratio is less than unit and although the wave-train is considerably modified, the discriminator output preserves the same character. This is probably due to limitation of high frequencies in the audio circuits.

oscillator was used as the master driver, and its output was divided, one section being multiplied to a frequency of 5 Mc/s, and the other passed to a circuit designed to produce narrow uni-directional pulses at 10,000 per second. Finally the output from both branches was brought together and applied to the input of an IF amplifier with 200 kc/s band width and a mean frequency of 5 Mc/s. The phase between the signal and noise impulse was varied by altering the tuning of one circuit in the frequency multiplier.

The results of combining two elements in different phases are shown by the oscillograms of Fig. 3. At

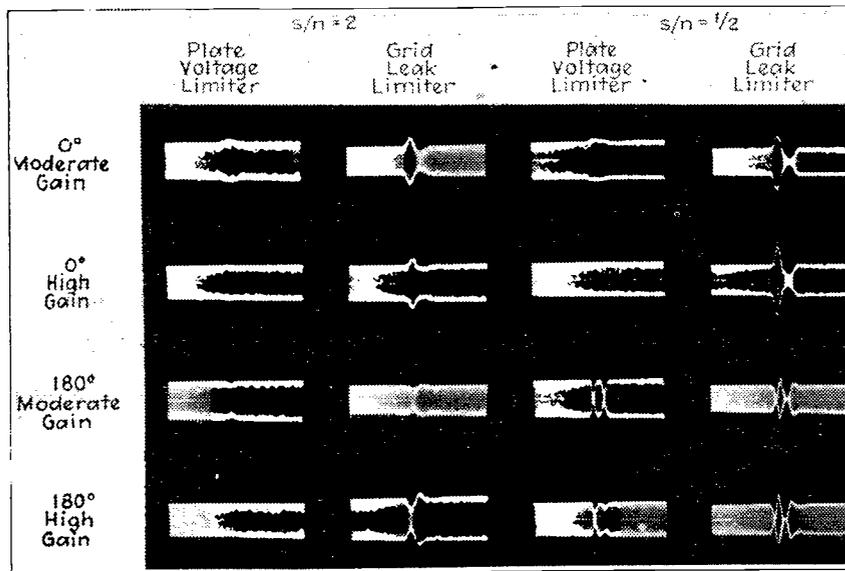


Fig. 4. Waveforms of impulse noise and carrier for different types of limiter.

phases both modulations are present. The effectiveness of amplitude limiting stages as noise suppressors is called into question when it is revealed by

modulation does not come through the discriminator when the noise pulse and the carrier are synchronised, and Fig. 2 proved that grid current in the


## Noise in FM Receivers—

limiter may actually increase the noise by its detuning effect on the preceding RF circuit. Fortunately it is in

That the limiter can be effective in reducing noise when the signal carrier is tuned at the edge of the pass band, is shown by the oscillograms of Fig. 6.

that of simple amplitude limitation. If the curves of Fig. 6 with and without limiter are compared it will be observed that one effect of the limiter is to equalise the area enclosed by the impulse curve above and below zero line; without the limiter the impulse is definitely asymmetrical. Analysis of the frequency distribution and total energy constant of the spectra produced by various types of impulse shows that less noise is likely to result from the symmetrical type of curve. Fig. 3 indicated that a reasonably symmetrical discriminator output was obtained without a limiter stage, when the carrier was accurately tuned to the centre of the pass band, so that the chief function of the limiter is the reduction of noise arriving when the instantaneous frequency of the carrier is off centre, e.g., when peak modulation causes mistuning. The grid leak limiter, in spite of its failure to remove amplitude modulation, provokes the least detuning due to grid current, and in practice is probably the best type to use.

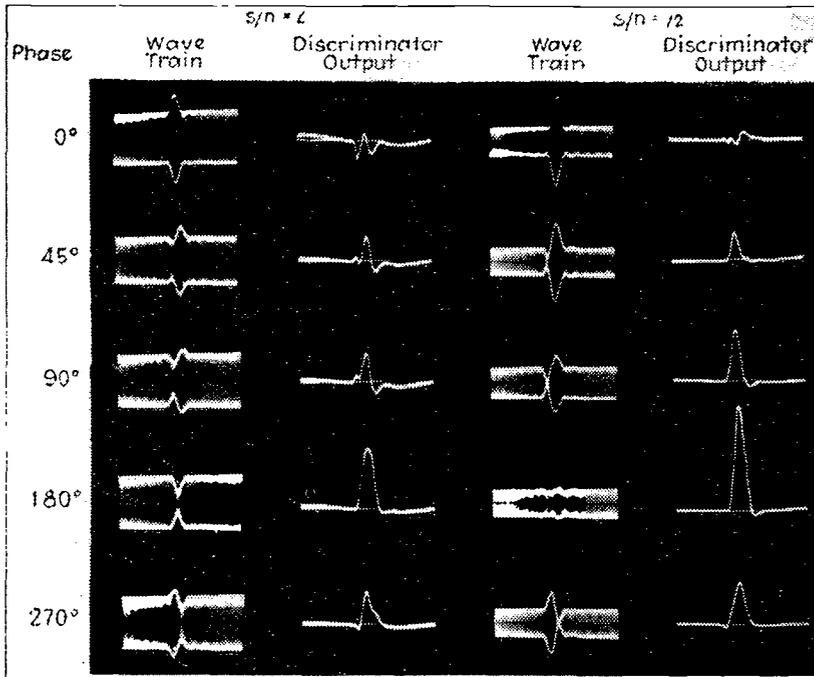The limiter stage is justified by considerations other than that of noise reduction, and its usefulness in limiting distortion due to lack of flatness in the top of the IF amplifier response



just such circumstances that the limiter action is most effective, i.e., when the carrier is not exactly in the centre of the pass band of the amplifier.


If the carrier is tuned to the edge of the pass band, beats are generated between the noise wave-train and the carrier. The frequency of the beat is  $f_c$ , or the cut-off frequency, i.e., half the band-width, and the beat note goes through one cycle in  $1/f_c$  seconds. As was seen earlier in the article, this is the duration of the noise wave-train. In the first oscillogram in Fig. 5 the noise train starts 180 deg. out of phase with the carrier and causes a small valley hardly deep enough to show in the reproduced photograph. As it grows it changes its phase until at the peak it is in phase with the carrier, after which it reaches a phase difference of 180 deg. at the moment of returning to zero amplitude. The phase relations on the left of the figure refer to the peak conditions. As the relative phase changes the valley of the beat note travels progressively across the noise pulse. The corresponding discriminator outputs show that for the off-tune condition greatest noise occurs with 180 deg. phase difference between noise and carrier. Yet in these circumstances there is least evidence of amplitude modulation in the original wave-trains.

(Above) Fig. 5. Noise wave-train and discriminator output with carrier tuned to edge of pass band.

(Right) Fig. 6. Illustrating noise reduction by plate and grid leak limiters with carrier off tune. Carrier tuned to edge of pass band; signal-noise ratio, 2.

The discriminator output is shown for both plate and grid leak limiters, and it will be noticed that the performance of the grid leak limiter is at least as good as that of the plate limiter in spite of the disturbed wave-train which the former type of limiter produces (Fig. 4).

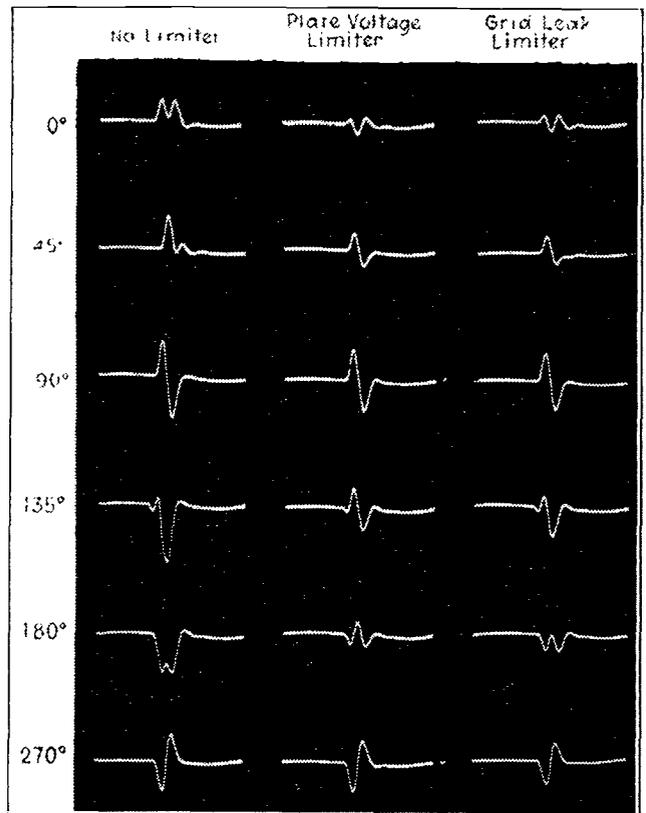It would seem, therefore, that the effectiveness of the limiter is dependent on some factor other than



curve would alone suffice to ensure its retention in FM receiver circuits.

# Reducing Loading

## on Short Waves

### *Offsetting the Effect of Cathode Lead Inductance*

WHEN valves are used at high frequencies the input impedance decreases as the operating frequency increases. This loss in the input circuit of the valve is the result of the increase of the input conductance due largely to the cathode lead inductance, because this cathode lead inductance is common to the anode and control grid return circuits.

It is now generally recognised that the inductance of the cathode lead of an amplifier or converter valve, which is common to both anode and control grid circuits, represents a degenerative coupling between these circuits. This degeneration exhibits itself in ordinary

circuit in which loading effects due to the cathode lead inductance are eliminated or substantially reduced is described below with reference to the diagrams.

In the schematic arrangement of a typical amplifier stage, shown in Fig. 1, the valve is provided with a cathode, preferably indirectly heated, control grid G, screen grid G1, suppressor grid G2, and anode. The input circuit is connected between control grid and the cathode, the cathode being coupled to the secondary of the input circuit by condenser C1. The output circuit is connected between anode and the usual voltage supply source, the by-passing condensers C3 and C2 being used between anode screen and cathode. The common cathode lead inductance is represented by an inductance L and may be either due to the length of the internal cathode tube lead, or to the length of connecting wire, or to both.

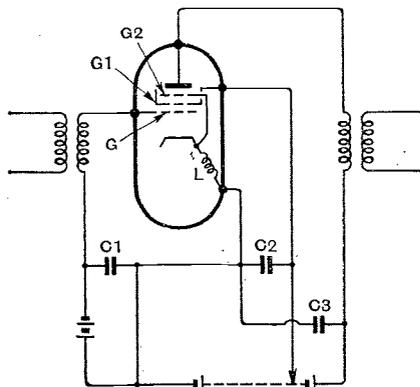


Fig. 1.—Showing how the inductance of the cathode lead, represented by L, is common to the control grid and other return circuits; it thus causes an anti-reaction or degenerative effect, increasing the loading of the input circuit.

valves as a resistance which appears in shunt with the input terminals of the valve and which decreases as the frequency increases. The common cathode lead inductance may be due to the length of the internal cathode lead or to the length of the connecting wire, or to both. The effective input conductance is, as a first approximation, directly proportional to this inductance. It also depends as a first approximation on the square of the operating frequency and on the cathode transconductance of the valve. The cathode transconductance is equal to the sum of the valve transconductance and the product of the valve transconductance divided by the ratio of the screen grid to anode current. This form of input loading probably accounts for a considerable portion, if not actually the major portion, of the input loading in many commercial valves.

A valve construction and associated

### Split Cathode Connection

The degenerative effect due to L may be overcome by means of the circuit arrangement and valve shown in Fig. 2. Here the cathode is provided with two separate leads, the inductances of which are represented by L1 and L2. In this arrangement two leads are provided, one for the anode and screen-grid return, and the other for the control grid return. If the mutual inductance between these two leads is negligible, the common cathode impedance is substantially eliminated, and the input loading due

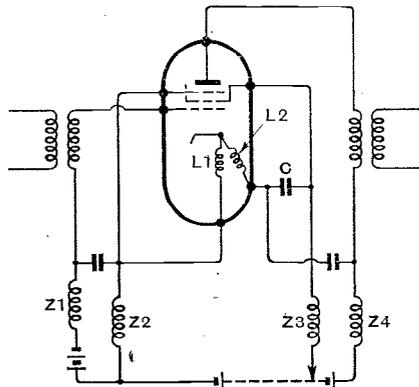


Fig. 2.—Minimising loading effects by provision of two independent leads for the valve cathode.

to this cause will be practically non-existent. However, if valves provided with two cathode leads are used in practical amplifier or converter stages, the input loading would not necessarily be greatly reduced. The reason is that if the impedance of the path through the HT supply is small as compared with the impedance of the path through L2, as it may be in an actual circuit, most of the AC anode and screen grid return current will flow through the supply path, and hence through the grid return lead. If it does so, then the object of having two leads is not fully realised, for the first cathode lead again constitutes a common inductance. However, this difficulty is removed by the insertion of choke coils or resistances as indicated at Z1, Z2, Z3 and Z4. In this way AC anode currents are prevented from flowing through the HT supply path to the cathode lead L1 and are forced to flow through the separate return lead L2. The impedances Z3 and Z4 can be used alone or the impedances Z1 and Z2 used alone. These additional circuit elements present a high impedance to currents of the operating radio frequencies and preferably, though not necessarily, a low impedance to the DC return currents.

The operation of the valve can be still further improved by mounting the by-passing condenser C (Fig. 2) inside the valve and connecting it directly to the cathode.

### Circuit Values

In one successful example, in which the screen grid lead was by-passed to the control grid-cathode return lead, the impedance Z3 was a 60,000 ohm resistance and impedance Z4 a 5,000 ohm resistance; the by-pass condensers were all of 0.0002 mfd. With this arrangement an input conductance of about 130 micromhos at 60 Mc/s was

## Reducing loading on Short Waves—

measured as compared to 500 micromhos in a conventional valve for the same value of anode current. The improvement was, therefore, in the ratio of 4 to 1.

Carrying the above further, the cathode may be provided with as many leads as there are electrodes in addition to the cathode. These leads can then be each separately connected by means of by-pass condensers to one of the other electrodes using suitable chokes or resistances to keep the radio frequency currents out of common paths due to common leads.

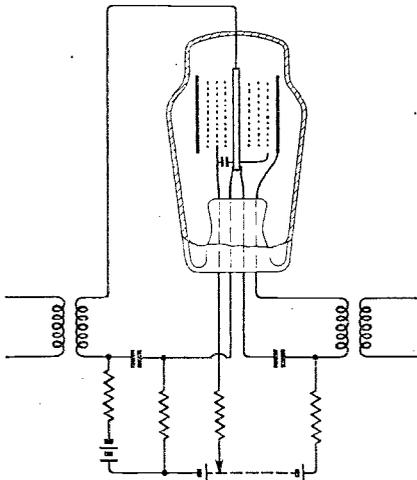


Fig. 3.—Construction of a valve with two cathode leads and a built-in bypass condenser.

The AC screen grid current in the above arrangement still flows through the first or control grid cathode lead, and since the ratio of the screen grid to cathode current was about 1 to 5 in the valve tested, the degenerative effect of the screen grid current gave rise to an input conductance of about 100 micromhos. This would leave roughly 30 micromhos for the input conductance of the valve if the degenerative effect of the screen grid current could be eliminated. The overall improvement might then be of the order of 16 to 1.

## Special Construction

A valve incorporating this improvement is shown in Fig. 3, provided with two cathode leads and a by-pass condenser connected inside the envelope directly between the screen grid and cathode. This by-pass condenser, by obviating the effect of the screen grid impedance, eliminates the degenerative effect of the screen grid current and ensures better shielding at high frequencies. The condensers can be of two types; namely, commercial

condensers mounted on the tube structure, or built-up condensers which make use of mica spacers at each end of the mount.

The degenerative effect of the AC screen grid current can be still further reduced by using valves designed to

have a low screen grid current. It is now generally known that such valves also have the virtues of reduced fluctuation noise and increased efficiency.

This development is reported from the Laboratories of the Radio Corporation of America.

# Frequency Measurement

## THE G.P.O. CHECKING STATION


IT is the responsibility of the General Post Office, as the Department entrusted with the control of all wireless communications in this country, to see that transmitters operating under its licence adhere as closely as the existing state of technical development permits to their allotted frequencies. The matter first became of great importance when the value of short waves for world-wide communication became evident in about 1924. Soon after that date the G.P.O. set up a frequency standard, with the necessary associated apparatus, for the accurate measurement of the frequency of signals received from stations under its control. This apparatus was installed at the Post Office Research Station, Dollis Hill, on the outskirts of London.

Dollis Hill proved to be an inconvenient site for routine measurements and still more for the important subsidiary work of investigating interference, and so the frequency measuring station was transferred to Colney Heath, near St. Albans. The accuracy attained at the new site ultimately

it was decided to equip a new station, transferring operations to a new site in clear open country, where reception conditions are good, particularly from the point of view of freedom from all kinds of interference.

The latest checking station is described by C. F. Booth and G. Gregory in the October, 1939, issue of *The Post Office Electrical Engineers' Journal*. It is pointed out that, in addition to its primary function of measuring the frequency of transmitters under G.P.O. control within the range of 15-30,000 kc/s, a station like this must be laid out for the investigation of jamming, the measurement of incoming signals from overseas, observation on the choice of frequencies for new services, and at the same time to keep a watch on the activities of British amateur transmitters. In addition, it must perform special interception work where required. The station must also be prepared to measure, on request, the frequencies of stations under the control of other administrations.

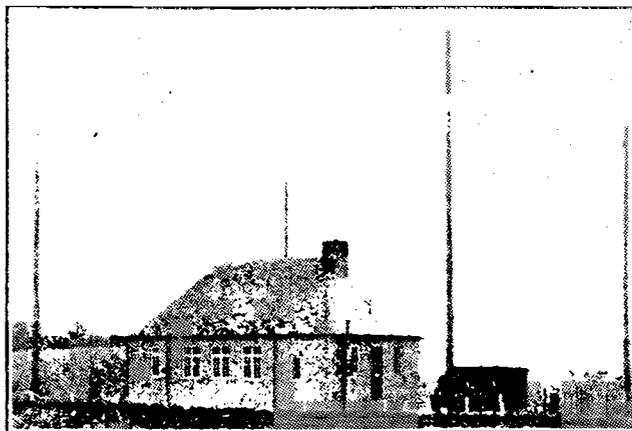The specification for the equipment of the new station was a stringent one. The stability over a period of weeks of the frequency standard was to be within  $\pm 1$



Courtesy "P.O. Elect. Engrs' Journal."

The G.P.O. frequency control station; several types of aerial systems are installed, in order to ensure good reception of the wide range of wavelengths which can be measured.

rose to within 12 parts in a million, but this was not considered good enough when crystal-controlled transmitters became almost universal, and

part in a million, with a short-period stability of  $\pm 1$  part in 10 million. These requirements were satisfied by a Marconi-Ekco type 482-C cry-

## Frequency Measurement—

stal frequency standard, which, in addition to generating the fundamental frequency, provides a number of harmonics and includes two interpolating oscillators, a crystal-controlled clock, and facilities for listening. The complete measuring equipment was built up around this unit, and the arrangement of apparatus for collecting and "presenting" the signals for frequency measurement is shown in the key of the accompanying photograph. The receivers used are a Marconi-Ekco RG37 and an American HRO "communication" set.

Means are available for checking the station's sub-standard frequency unit from the Rugby time signals, and regular checks are also made against the primary standard frequency generator at Dollis Hill.



Three main methods of measuring the frequency of received signals are in use. The first, that of normal interpolation, operates over the range 14.5 to 30,000 ks/s and is used when the highest accuracy is not essential.

The second method, used between 1,000 and 30,000 kc/s, depends on inter-modulation, a harmonic from the 1,000-kc/s multivibrator being modulated by the output of the interpolating oscillator in such a way that the sum or difference frequency produced coincides with the frequency of the signal under observation. The accuracy over the greater part of the range is of a very high order; errors are greatest towards the long-wave end of the range, so this method is mainly used for routine short-wave measurements.
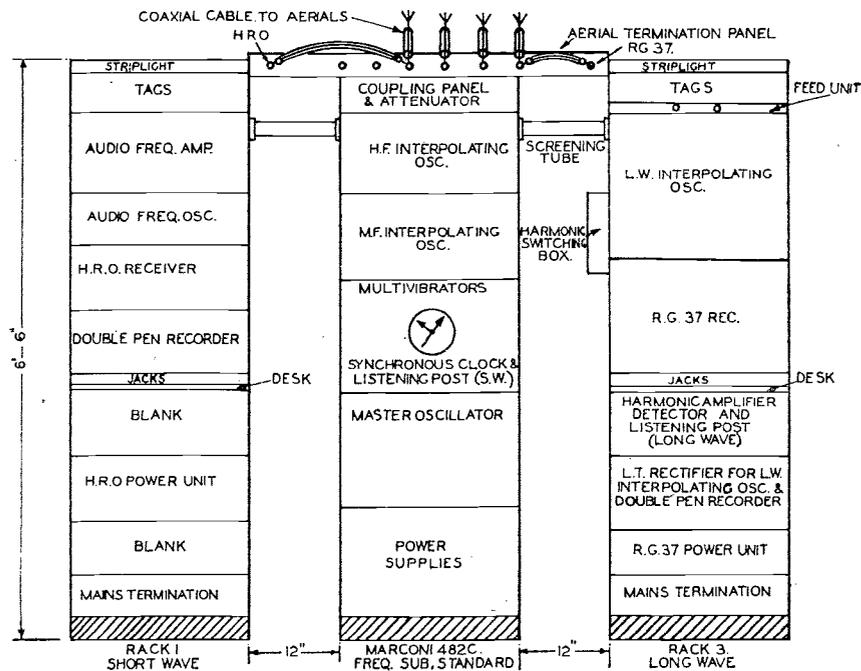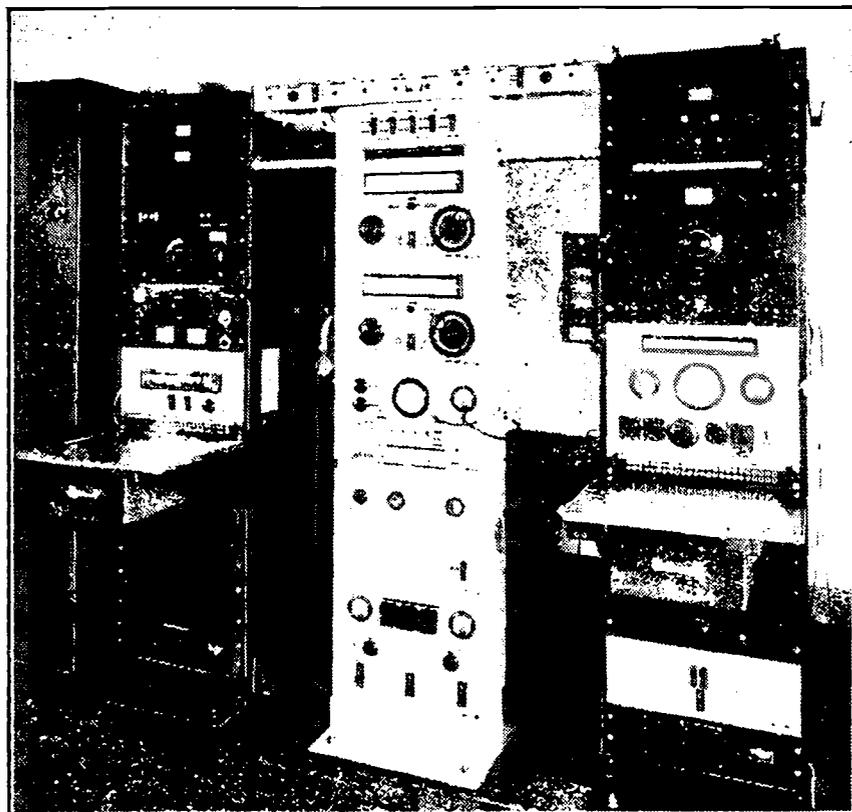
## Graphical Records

To increase the accuracy of measurement on long and medium waves a third method, that of audio-frequency interpolation, is used. In addition, the principle of allowing the signal to beat directly with a harmonic of one of the multivibrators and recording the beats against time as shown by the crystal clock, may also be employed, with the limitation that the signal must be of a frequency within about  $\pm 30$  c/s of a multivibrator harmonic. One pen of the recorder is actuated by the resultant slow beats and the other pen marks an impulse each second from the clock.

One of the many checks made on the accuracy of the station's apparatus consists of carrying out simultaneous comparisons between the sub-standard frequency generator at that station and the standard at Dollis Hill. Simultaneous measurements of the



Courtesy P.O. Elect. Engrs. Journal.

Frequency measurement equipment at the G.P.O. station; the key shows the functions of the various units.

same transmitter are made at the two stations and very good agreement is reached. In the case of observations of the N.P.L. standard frequency

transmissions, it is stated that the frequencies as determined at the two stations seldom differ by more than a few parts in 10 million.

# The Psychological Pause

## A Phase in the Learning of Morse

AS readers of a previous article<sup>1</sup> may remember, it can be taken as a fairly well-established fact that there are two stages in learning Morse, just as in learning to skate or to ride a bicycle, to quote two parallels only. The first stage is the conscious assimilation of the alphabet, so that when dash-dot is heard, N is thought of: the second is the driving of this into the subconscious mind, so that when dash-dot is heard it is impossible *not* to think of N.

Again, it can be accepted that teaching methods should differ from one stage to the other: slowly sent letters with slow dashes and dots during the short first stage; quickly sent ones with long pauses between letter and letter, these slowly decreasing as the learner gains speed, during the second stage. (Incidentally, it may be worth mentioning that my own experience indicates that if anyone feels like learning non-wireless systems of Morse signalling, and if these systems work at low speeds, lamp, for example, it is best for this study to be done either during the first stage or else left until the end of the second stage is neared: i.e., when the learner is at about six words a minute or at about 20, respectively. If he tries to learn lamp with a friend as a relaxation when they are doing about twelve words on buzzer, it will merely tend to delay the progress of the second stage.)

Now during this second stage a "pause" almost invariably occurs, a horrid period that may last for days or even weeks, during which the learner makes no progress, curses the shade of Samuel Morse, bites pieces off the end of his pencil, swears that he will never manage it—even chucks up the whole thing in despair. This "pause" often happens at about 14 words a minute or at about 18: some particularly unfortunate people may get it twice. Some, on the other hand, never meet with it at all: they are usually, but by no means invariably, of the stolid, easy-going type; and if one of such favoured persons wants to learn how really unpopular he can make himself, he need only remark happily to some fellow-learner whom he has caught up and passed that he "really can't

<sup>1</sup> On Learning Morse; *The Wireless World*, August, 1940.

see what all the trouble is about. Why, I just do a bit better every week, and if you chaps would only—." The rest is likely to be a strangled silence.

Despite this scepticism, the pause is a very real one, and there is little doubt that it is due to a quarrel between the conscious and subconscious minds (to put it most unscientifically). The bossy conscious worries: "I can't get it. . . . What *was* that letter? . . . Oh, I *am* making a mess of it. . . . This will never do, it's worse than last time"; and the squashed subconscious cannot make heard its gentle: "Let me alone, I'm getting it all right. . . . Oh, *do* let me alone!"

### Helping the Subconscious Mind

Now there are several dodges that can be tried, all with the object of distracting momentarily the conscious interferer, and it is especially worth noting that if this can be done *once*—if, that is to say, *one* transmission of a goodish length can be taken reasonably well at an "impossible" speed, it is almost certain that the sticking point will be passed, for good and all. Next time that this speed is heard the subconscious will be able to assert itself: "I did it yesterday—I told you I could do it," and the conscious will ungracefully subside with a grumbled: "Well, perhaps you're right, go ahead, but don't worry me" (which is, of course, exactly what is needed).

One such dodge, mentioned with all due reserve, is to get slightly drunk. Another, more generally applicable, is to recite mentally (or better still audibly) some passage of poetry or the Bible or the multiplication table or anything else favoured while a transmission is being taken: in this case, for obvious reasons, it should be a test in code, not in plain English. Another, ridiculously simple and often ridiculously effective, is to do with the left hand something demanding a certain degree of attention while the right hand writes down the text—for example, to balance a pencil across the forefinger or to keep a pencil standing upright on end by checking it as it falls with the circle formed by forefinger and thumb. Such devices have the advantage that the transmission can be in plain language

or code as desired, but may distract the *eye* too much and make writing too difficult. Others which may be tried, and which need no visual attention, are buttoning and unbuttoning one's coat, turning a coin over and over in the left hand, and such like: the trouble is that, as a rule, these do not demand sufficient attention to keep the conscious mind from interfering. What is "sufficient" here, however, obviously varies from one person to another and even for the same person from day to day: sometimes the subconscious has already so nearly asserted itself that very little is needed for it to take full charge, and here very simple devices will suffice. It is a matter for the learner himself to try; and it is amusing to note that the fact that he is thus observing himself may in itself supply the needed extra attention.

Another possibility, often recommended by teachers although as a rule with no idea why desirable, is that of forcing oneself to copy one letter behind in code, or several letters behind in plain language, so that no letter is written down until well after it has been sent. Here the conscious mind is kept busy remembering the letter or letters: it is particularly effective when the transmission is taken on a typewriter (a thing that all beginners should learn to do), and above all if the learner is only a fair typist, something about midway between the "three pecks and a damn" class and the machine-gun expert. Yet another is to form the letters with excessive attention, almost drawing them rather than writing; or to make them extremely small and yet legible—I have as a souvenir of the last war a full-length Army test message taken down, quite legibly, on a scrap of paper the size of a Coronation stamp by a learner whom (he said) this dodge saved from "drink and dependency."

It is a matter for personal experiment. In any case, let it yet again be emphasised that if only the pause-speed can be *once* passed it is extremely rare for any further trouble to recur at this speed, so that a little experimentation may save the learner "weeks of 'orrid doubt" and "faith and 'ope and cursing and despair" (to quote Kipling from memory).

R. R.-H.

# THE WORLD OF WIRELESS

## CENSUS OF SERVICE ENGINEERS

Forces Will Take 87 per Cent.

THE publication of the Revised Schedule of Reserved Occupations and Protected Work, in which it will be remembered service-men continue to be reserved from 35 years of age, was thought an opportune moment to reveal the result of the second Service Questionnaire issued by our contemporary, *The Wireless & Electrical Trader*.

When the first census was undertaken by *The Trader* soon after the war began, it was estimated that with the reservation age at 30, as it then was, 66.5 per cent. of the pre-war service engineers were liable for military service. The latest census, which is based on 416 replies covering 875 engineers, reveals that the percentage of the originally employed service personnel which will be left in the retail side of the wireless industry is 13. The details of the other 87 per cent. are:—

	per cent.
Already called up	44
Already volunteered	31
Liable for call up	12

The census also shows how the remaining engineers are likely to be supplemented. *The Trader* states that this is taking place in two ways—by the employment of "improvers" of all ages and by the return of managers and owners of retail businesses to the service bench.

Unless the Schedule is modified in the very near future the following is an analysis of servicing personnel (based

on the number of pre-war engineers) likely to remain available in the retail side of the industry:—

	per cent.
Fully-trained engineers (reserved)	13
Owners and managers	39.5
Improvers (reserved)	18

It is stressed, however, that this does not mean that the personnel available is equivalent to 70.5 per cent. of the original staffs, for it must be remembered that the majority are not up to the technical standard of the pre-war engineers.

## FREE EUROPEAN AMATEURS

Hospitality from the R.S.G.B.

IN extending greetings and good wishes to the large number of European amateur wireless men at present in this country, the Radio Society of Great Britain, through *The T. & R. Bulletin*, offers to publish notes from any representative group. Poles and Czechs, Free French and Belgians, Norwegians, Danes and Dutch are among those at present in these islands. They no longer have a journal of their own, and the offer of space in the Society's journal will doubtless be much appreciated. It will serve not only as a connecting link between exiled amateurs of the same nationality, but will also give an opportunity for them to get into personal touch with British amateurs with whom they worked in peacetime.

## B.B.C. SHORT-WAVE TRANSMISSIONS

THE latest schedule of the B.B.C.'s short-wave European programmes, which will be current when this issue is in print, shows that there are a number of changes in the wavelengths to be used for the transmissions of news in English in the European and World Services. The times (BST) of transmissions and the wavelengths used are given below.

00.00	... 49.59*	41.49*	30.96*		
00.45	... 31.32,	31.25,	25.53.		
01.30	... 49.59*				
02.00					
02.45	... 31.32,	31.25,	25.53.		
06.30					
08.15	... 31.55,	31.25,	25.53,	19.82,	19.66.
10.00	... 49.59*	41.49*	31.55,	30.96*	25.53,
			19.82,	19.66,	19.60.
13.00	... 31.25,	25.53,	19.82,	16.84,	13.97,
15.00	... 19.82,	16.84,	13.97,	13.93,	13.92.
15.30	... 49.59*	41.49*	25.38*	25.29*	
18.00	... 31.75,	25.53,	19.82,	16.84,	13.93,
20.00	... 31.25,	25.53,	24.92,	19.82,	19.66,
22.45	... 31.25,	25.53,	19.82,	19.66.	

The wavelengths marked with an asterisk are used in the European Service.

## MAINTAINING ELECTROLYTIC CONDENSERS

THE Radio Manufacturers' Association draws attention to the risk of serious deterioration to electrolytic condensers that arises when sets remain out of use for long periods. To prevent "deforming" the Technical Advisory Committee recommend that the receivers should be switched on for 5 or 10 minutes every six months, or at the most every 12 months, and that during this "reforming" period they should be watched to see if any abnormal symptoms manifest themselves.

## "WIRED WIRELESS" INTERFERENCE

IT is reported in *Broadcasting* (U.S.A.) that a Federal Communications Commission investigator has traced interference with broadcast reception at Providence, Rhode Island, to harmonic radiation from a local relay service operating a radio-frequency distribution system.

## CARAVAN RECEIVERS

Interpreting the Regulation

IT is understood that whilst the Home Office regulation of last summer, prohibiting the use of a receiver in road vehicles, has not been altered the police have been given wider discretion regarding the application of the regulation to caravans.

It will be remembered that soon after the announcement banning car radio it was made clear that the order would not apply to caravans off the highway which were habitually used as residences, having no motive power and the wheels removed. The police are now to use their discretion regarding the use of receivers in caravans even if they have motive power. They must, however, be off the highway.

It should be remembered that when on the road the receiver must be rendered unusable by the removal of valves and the disconnection of batteries.

## BONDS OF FRIENDSHIP

AT the present time, when the ties between Great Britain and America are binding the two countries closer together, the following cablegram from Mr. Sarnoff, president of the R.C.A., to Mr. Donisthorpe, at the Tenth Annual General Meeting of the Radio Industries Club, is of special interest.

"Each year, since Marconi's first wireless message from England to America forty years ago, radio has strengthened bonds of friendship between our countries, to-day it carries cordial and affectionate greetings to British Radio Industries Club and best wishes for success of Annual General Meeting this year, next year and many years to come.—David Sarnoff."

## U.S. AMATEURS' TEST

AMATEUR radio operators in the U.S.A. recently took part in what is probably the greatest radio practice drill ever undertaken—the origination and relaying of 3,700 separate messages between as many local chapters of the American Red Cross and the headquarters in Washington, D.C., St. Louis, and San Francisco.

The test, which was sponsored by the American Radio Relay League, was designed to test the ability of radio amateurs to serve the Red Cross in any national emergency. The 3.5 and 7 Mc/s amateur bands, which offer

# Wireless World

## The World of Wireless—

reliable domestic communication day and night, carried most of the traffic which consisted of 15-word messages.

### EXPORT PROHIBITION

UNDER a Board of Trade Order (S.R. & O., 1941, No. 492), which came into force on April 24th, receiving valves and electric insulated (other than paper-insulated) wire and cable, are among articles which may not be exported to any destination without an export licence. The Order also prohibits the exportation without licence to certain specified destinations of paper-insulated electric wire and cable, insulating materials containing mica and certain mica manufactures.

## U.S. TELEVISION

ACCORDING to our American contemporary, *Broadcasting*, it is expected that television stations in the States will very soon be granted facilities by the Federal Communications Commission for "full-time commercial operation." It will be remembered that the F.C.C.'s authorisation of "limited commercial operation" was rescinded in March, 1940, following a dispute between the Commission and the parties concerned.

The standard of transmission favoured is 525 lines, 30 frames interlaced, as recommended by the National Television System Committee. The proposed 30 hours per week operation is likely to be reduced to 15 hours.

## FROM ALL QUARTERS

### New Summer Time

In this and the succeeding two issues of *The Wireless World* the use of the designation BST will denote time two hours ahead of GMT.

### Amateur Radio Conference

ARRANGEMENTS are being made by The North Manchester Radio and Television Society for the holding of a Conference of radio amateurs at which various matters will be discussed, including "The Future of Amateur Radio," "The Shortage of Radio Components," and "The Radio and its Possible Uses in Home Defence." Invitations have been sent to various allied Forces in this country to send representatives. All interested are invited to attend the Conference.

## NEWS IN ENGLISH FROM ABROAD

### REGULAR SHORT-WAVE TRANSMISSIONS

Country : Station	Mc/s	Metres	Daily Bulletins (BST)	Country : Station	Mc/s	Metres	Daily Bulletins (BST)																												
<b>America</b>				<b>Japan</b>																															
WNBI (Bound Brook)	17.780	16.87	4.0‡, 6.0.	JLQ2 (Tokio) .. ..	9.500	31.57	11.30.																												
WBOS (Millis) .. ..	9.570	31.35	11.45.	JZI .. ..	9.535	31.46	7.0.																												
WCAB (Philadelphia) ..	15.270	19.65	12.30 a.m., 7.45.	JZJ .. ..	11.800	25.42	7.0.																												
WCBX (Wayne) .. ..	9.650	31.09	9.55‡, 11.45‡.	<b>Manchukuo</b>																															
WCBX .. ..	11.830	25.36	7.30‡.	MTCY (Hsinking) .. ..	11.775	25.48	9.0 a.m., 11.5.																												
WCBX .. ..	17.830	16.83	2.0‡, 3.0, 4.0‡, 4.15‡, 5.0‡, 5.30‡.	<b>Sweden</b>																															
WGEO (Schenectady) ..	9.530	31.48	8.30‡, 10.55‡.	SBO (Motala) .. ..	6.065	49.46	11.20.																												
WGEA (Schenectady) ..	15.330	19.57	1.0, 2.0‡, 6.0, 7.45.	<b>Thailand</b>																															
WPIT (Pittsburgh) .. ..	15.210	19.72	6.0.	HSP5 (Bangkok) .. ..	11.715	25.61	1.45.																												
WRUL (Boston) .. ..	11.790	25.45	8.15‡, 9.30‡.	HS6PJ .. ..	19.020	15.77	1.45.																												
WRUL .. ..	15.350	19.55	8.15‡, 9.30‡.	<b>Turkey</b>																															
<b>Australia</b>				<b>U.S.S.R. (Moscow)</b>																															
VLQ (Sydney) .. ..	9.615	31.20	9.0 a.m., 9.0.	49-metre band .. ..	—	—	2.0 a.m., 8.30, 10.0, 12.0 midt.																												
VLQ5 .. ..	9.680	30.99	2.30, 5.30, 9.15, 11.30.	41 .. ..	—	—	8.30, 10.0.																												
VLQ2 .. ..	11.870	25.27	9.0 a.m., 3.40, 7.55.	31 .. ..	—	—	6.0, 8.30, 10.0.																												
VLQ7 .. ..	11.880	25.25	3.15, 9.0, 12.0 midt.	25 .. ..	—	—	1.0, 6.0, 8.30.																												
VLQ8 .. ..	17.800	16.85	8.0 a.m.	19 .. ..	—	—	} 8.33 a.m., 1.0.																												
VLQ8 .. ..	17.800	16.85	8.0 a.m.	16 .. ..	—	—	}																												
<b>China</b>				<b>Vatican City</b>																															
XRVC (Chungking) .. ..	7.508	39.96	12.30 1.10, 10.30, 11.30.	HVJ .. ..	6.190	48.47	9.15.																												
<b>Egypt</b>				<b>LONG- AND MEDIUM-WAVE TRANSMISSIONS</b>																															
SUX (Cairo) .. ..	7.860	38.14	7.50, 11.10.	<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="text-align: left;">Country : Station</th> <th style="text-align: center;">kc/s</th> <th style="text-align: center;">Metres</th> <th style="text-align: center;">Daily Bulletins (BST)</th> </tr> </thead> <tbody> <tr> <td colspan="4"><b>Egypt</b></td> </tr> <tr> <td>Cairo .. ..</td> <td style="text-align: center;">1,348</td> <td style="text-align: center;">222.6</td> <td style="text-align: center;">7.50, 11.10.</td> </tr> <tr> <td colspan="4"><b>Ireland</b></td> </tr> <tr> <td>Radio-Eireann .. ..</td> <td style="text-align: center;">565</td> <td style="text-align: center;">531</td> <td style="text-align: center;">2.40, 7.40, 11.5‡, 11.10‡.</td> </tr> <tr> <td colspan="4"><b>U.S.S.R.</b></td> </tr> <tr> <td>Moscow 1 .. ..</td> <td style="text-align: center;">172</td> <td style="text-align: center;">1,744</td> <td style="text-align: center;">12.0 midt.</td> </tr> </tbody> </table>				Country : Station	kc/s	Metres	Daily Bulletins (BST)	<b>Egypt</b>				Cairo .. ..	1,348	222.6	7.50, 11.10.	<b>Ireland</b>				Radio-Eireann .. ..	565	531	2.40, 7.40, 11.5‡, 11.10‡.	<b>U.S.S.R.</b>				Moscow 1 .. ..	172	1,744	12.0 midt.
Country : Station	kc/s	Metres	Daily Bulletins (BST)																																
<b>Egypt</b>																																			
Cairo .. ..	1,348	222.6	7.50, 11.10.																																
<b>Ireland</b>																																			
Radio-Eireann .. ..	565	531	2.40, 7.40, 11.5‡, 11.10‡.																																
<b>U.S.S.R.</b>																																			
Moscow 1 .. ..	172	1,744	12.0 midt.																																
<b>Finland</b>				<b>French Equatorial Africa</b>																															
OFD (Lahti) .. ..	6.120	49.02	8.15, 11.15.	Brazzaville .. ..	11.970	25.06	9.45.																												
OFD .. ..	9.500	31.58	1.15 a.m., 8.15, 11.15.	<b>India</b>																															
OFE .. ..	11.780	25.47	1.15 a.m., 9.40 a.m., 8.15, 11.15.	VUD2/3 (Delhi) .. ..	9.590	31.28	10.0 a.m., 2.30, 5.50.																												
OIE .. ..	15.190	19.75	1.15 a.m., 8.15, 11.15.	VUD .. ..	11.830	25.36	10.0 a.m., 2.30, 5.50, 7.15.																												
<b>Iran</b>				<b>India</b>																															
EQB (Teheran) .. ..	6.155	48.74	8.30.	VUD3 .. ..	15.290	19.62	10.0 a.m.																												

It should be noted that the times are **two hours** ahead of GMT, and are p.m. unless otherwise stated. The times of the transmission of news in English in the B.B.C. Short-wave Service are given on the preceding page.

\* Saturdays only. § Saturdays excepted. † Sundays only. ‡ Sundays excepted.

## Wireless World

which is to be opened at 2.30 p.m. on Sunday, June 8th, at the Cheetham Liberal Club, 433, Cheetham Hill Road, Manchester. Further details can be obtained from the Club Secretary, Mr. R. Lawton, 10, Dalton Avenue, Thatch Leach Lane, Whitefield, Manchester.

### "The Trader" Fortnightly

As a wartime measure our contemporary, *The Wireless & Electrical Trader*, has changed from weekly to fortnightly publication. It is understood the volume of each issue will to some extent be increased and that it is intended to include two of the service sheets which have been a popular feature of *The Trader* for a considerable time. The first fortnightly issue was dated May 10th.

### The R.C.M.F.

At the recently held Annual General Meeting of the Radio Component Manufacturers' Federation, Mr. H. G. Aytoun Key, of Benjamin Electric, was elected chairman for the forthcoming year. Speakers at the meeting paid tribute to the work of the Federation in representing the collective interests of the component section of the wireless manufacturing industry. It is proposed to draw up a complete list of the products of the various member firms in order that outside enquiries as to sources of supply may be dealt with more expeditiously.

### Edinburgh Day Classes for Service Men

SUFFICIENT applications have been received by the Edinburgh branch of the Scottish Radio Retailers' Association for day classes to be started in co-operation with the education authorities for the training of service men to fill the gaps in the industry caused by the demands of the Services. Some of the necessary equipment for the training has been given by wireless firms in the city.

### Hands Across the Sea

BRITISH amateur G5LY has written to the American Radio Relay League stating that of 70 QSL cards sent to American amateur transmitters, only one recipient replied. The Editor of *QST* writes, "How about it, fellows? A card to our friends across the pond means a great deal these days!"

### Cuban Amateur Reserve

As a result of a Presidential decree Cuban amateurs are to be formed into a volunteer emergency reserve to be known as the Auxiliary Corps of Radio Amateurs. Under the guidance of the Ministry of Communications, the corps will be a valuable reserve of trained men with equipment for use in a national emergency.

### Receiver Sales in Canada

DURING 1940 there was an increase of over 20 per cent. on the previous year's sales of receivers in Canada, the total being approximately 438,000. The sales of U.S. receivers in Canada, which have been rising steadily since 1932, are expected to be adversely affected by the recently imposed taxes on sets.

### Dr. G. W. C. Kaye

It is with regret that we record the death of Dr. G. W. C. Kaye, D.Sc., F.R.S., who since 1922 had been superintendent of the physics department of the National Physical Laboratory. Dr. Kaye, who had received many professional honours, died on April 16th, a few days after his 61st birthday.

### R.C.A. Laboratories

It was recently announced by the president of the Radio Corporation of America that a branch of the parent company was to be established for research work. It will be known as R.C.A. Laboratories and will be housed in new premises to be built at Princeton, New Jersey. Mr. Otto S. Schairer will be vice-president in charge of R.C.A. Laboratories, with Dr. C. B. Jolliffe as chief engineer, Mr. E. W. Engstrom as director and Dr. V. K. Zworykin and Mr. B. J. Thompson as associate directors.

### U.S.-Norway Direct Radiotelegraph Circuit

THE reopening of the direct radiotelegraph circuit between the United States and Norway, which had been closed since Germany took over control of the country in April, 1940, was recently announced by R.C.A. Communications. The Norwegian terminal is the Oslo station of the Administration of Posts, Telegraph and Telephone, which has been reconditioned. During the past year, all radiotelegraph traffic from the U.S.A. for Norway has been handled over the Berlin circuit, except for the first few weeks, when it was transmitted via Stockholm, Sweden.

### Australia's Transmitters

AUSTRALIA now has a total of 129 broadcasting stations. Of this number 26 medium-wave and 3 short-wave transmitters are operated by the National Broadcasting Service. The remainder are commercial stations. According to recent figures issued by the U.I.R., the average power of the transmitters is very low, being approximately 1.6 kW.


## The Wireless Industry

A RANGE of new power type loud-speaker units is described in a leaflet (No. 25) recently issued by the General Electric Co., Ltd., Magnet House, Kingsway, London, W.C.2. The types listed include omni-directional diffusion units for halls and factories, weatherproof moving coil driving units for horn loading, including a folded type designed for mounting on car-bumpers, etc.

Mr. G. H. Walton has been appointed works manager of British Insulated Cables, Ltd., on the retirement of Mr. E. A. Bayles, who continues his association with the company in a consultative capacity.

R. A. Rothermel, Ltd., announce that from May 1st the price of the Rothermel New Junior Pick-up has been increased from 23s. 6d. to 26s.

## The "Fluxite Quins" at work

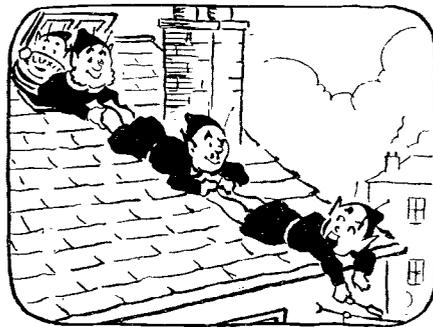

Cried Ol, from the gutter, "Hold tight!  
Till I've soldered this aerial right.

I can see now quite plain

Why it's broken again.

Pass me down, lads, the tin of FLUXITE!"

See that FLUXITE is always by you—  
in the house—garage—workshop—  
wherever speedy soldering is needed.  
Used for 30 years in Government  
works and by leading engineers and  
manufacturers. Of Ironmongers—in  
tins, 4d., 8d., 1/4 and 2/8.

Ask to see the FLUXITE SMALL-  
SPACE SOLDERING SET—compact  
but substantial—complete with full  
instructions, 7/6.

Write for Free Book on the art of  
"soft" soldering and ask for Leaflet  
on CASE-HARDENING STEEL and  
TEMPERING TOOLS with FLUXITE

TO CYCLISTS! Your wheels will  
NOT keep round and true unless the  
spokes are tied with fine wire at the cross-  
ings AND SOLDERED. This makes  
a much stronger wheel. It's simple—with  
FLUXITE—but IMPORTANT.

## THE FLUXITE GUN

is always ready to put Fluxite on the  
soldering job instantly. A little  
pressure places the right quantity on  
the right spot and one charging lasts  
for ages. Price  
1/6, or filled 2/6.

FLUXITE LTD.  
(Dept. W.W.),  
BERMONDSEY  
STREET, S.E.1

ALL MECHANICS WILL HAVE

# FLUXITE

IT SIMPLIFIES ALL SOLDERING

# LETTERS to the EDITOR

## The Editor Does Not Necessarily Endorse the Opinions of His Correspondents

### Post-war Amateur Transmission

IN discussing the outlook for amateur transmitters after the war, all your contributors and correspondents take the gloomy view that the G.P.O. will refuse to restore the privileges (or should it be "rights"?) enjoyed previously by the amateur.

Why should the G.P.O. do any such thing? The frequency bands occupied by amateurs are allotted by international agreement, and presumably can only be diverted to other uses by similar agreement. So long as these bands are occupied by amateurs in other countries, the G.P.O. could not usefully employ them for its own purposes, and so the motive of self-interest would not arise—except, perhaps, with regard to the ultra-short waves. C. T. C.

WHY be almost apologetic for saying that a transmitting amateur without a knowledge of morse "seems all wrong." There is a great deal more than "mere conservatism" (I again quote from your April Editorial) behind that point of view. A "phone only" transmitter would get very poor value from the few watts allowed by his licence and would be quite unable to observe the common courtesies of non-interference with morse transmitters.

### RADIOPHARE.

IT seems that the majority of British amateurs believe that a more difficult code test would be beneficial to the amateur movement. I do not know how the R.S.G.B. feel about this, but it is interesting to note that the Society's American counterpart, the American Radio Relay League, is reported (by *Radio News*, February, 1941, issue) to have approached the Federal Communications Commission with a view to "the lowering of standards of admission to the ranks of the licensed amateur."

*Radio News* continues: "It is said the A.R.R.L. believes there should be more amateurs and accordingly has asked the F.C.C. to make the entrance examinations leading to a licence a little easier. Code restrictions will be lowered instead of raised, and it may become a possibility that amateurs will be licensed with considerably less

than 13 w.p.m. code speed requirements and lighter technical requirements. The exact code speed prerequisite . . . is supposed to be in the neighbourhood of 4 to 5 w.p.m."

E. A. S. JONES,  
(ex 2FOA).

Gibraltar.

[The two cases seem hardly comparable. The U.S.A., in process of re-arming, naturally wishes to have a large body of amateurs from which to draw recruits for the wireless branches of its fighting services. In this country, so far as the present discussion is concerned, we are thinking solely of the post-war position.—Ed.]

### "Mystery" Record Players: G.P.O. Ruling


IT is considered that the publication of the article on "Mystery" Record Players in the April *Wireless World* might encourage some of your readers to construct similar apparatus, and you will appreciate that if such a device were connected to an efficient aerial it would radiate appreciably. Its possession and use would then be regarded by the G.P.O. as infringements of the Defence Regulations

(S.R.O., 1939, Nos. 1687 and/or 1688). The P.M.G. has no objection to the use of this class of apparatus provided signals are of so low a field strength that no radiation can be detected outside the premises in which the device is housed.

E. F. H. GOULD,  
For Engineer-in-Chief, G.P.O.  
(Radio Branch).
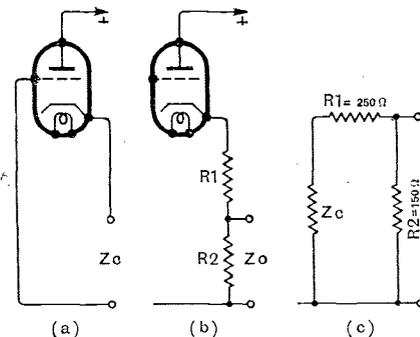
### The Cathode Follower

I SHOULD like to suggest that the formula given for the impedance of a cathode follower in the article "Photographing Transients," by Dr. T. H. Turney, in your issue for April, 1941, page 99, is inaccurate.



The fundamental formula for the output impedance of a cathode follower (diagram (a)) is

$$Z_c = \frac{I}{\frac{I}{R_A} + g} = \frac{I}{g} \cdot \frac{\mu}{\mu + 1}$$

## BOOKS ON WIRELESS

issued in conjunction with "The Wireless World"

	Net Price	By Post
"FOUNDATIONS OF WIRELESS," by A. L. M. Sowerby, M.Sc. Second Edition Revised . . . . .	5/-	5/6
"RADIO LABORATORY HANDBOOK," by M. G. Scroggie, B.Sc., A.M.I.E.E. (Second edition ready shortly) . . . . .	10/6	11/1
"WIRELESS SERVICING MANUAL" by W. T. Cocking, A.M.I.E.E. Sixth Edition revised and enlarged . . . . .	6/-	6/6
"HANDBOOK OF TECHNICAL INSTRUCTION FOR WIRELESS TELEGRAPHISTS," by H. M. Dowsett, M.I.E.E., F.Inst.P., M.Inst.R.E. Sixth Edition Revised . . . . .	21/-	21/9
"WIRELESS DIRECTION FINDING," by R. Keen, B.Eng. Hons. Sheffield, A.M.I.E.E. Third Edition . . . . .	25/-	25/9
"RADIO DATA CHARTS," by R. T. Beatty, M.A., B.E., D.Sc. Second Edition . . . . .	4/6	4/11
"TELEVISION RECEIVING EQUIPMENT," by W. T. Cocking, A.M.I.E.E. . . . .	8/6	9/-
"RADIO INTERFERENCE SUPPRESSION," by Gordon W. Ingram, B.Sc. . . . .	5/-	5/4
"LEARNING MORSE," Sixth Edition . . . . .	6d.	7½d.
"RADIO DESIGNER'S HANDBOOK," Edited by F. Langford Smith, B.Sc., B.E. (Reprint in preparation) . . . . .	8/6	9/1
"THE WIRELESS WORLD" GREAT CIRCLE PROJECTION MAP . . . . .	2/-	Post free

Obtainable from Leading Booksellers and Railway Bookstalls or by post (remittance with order) from

ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1

## Wireless World

i.e.  $Z_c$  is equal to the resistance of  $R_A$  and  $\frac{I}{g}$  in parallel.

Thus in the circuit given (b), the output impedance

$$Z_o = \frac{I}{\frac{I}{R_2} + \frac{I}{R_1} + Z_c},$$

which, in the case under consideration, cannot be less than

$$\frac{I}{\frac{I}{R_2} + \frac{I}{R_1}}$$

or 93.66 ohms,  
even if  $Z_c = 0$ .

Actually  $Z_c$  will be about 100 ohms, so  $Z_o$  will be about 105 ohms, a value considerably different from the 20 ohms given in the article mentioned.

Cardigan. E. F. GOOD.

### Club for South Manchester

WILL any young reader who is interested in the formation of a radio and television club in the South Manchester area please communicate with me? J. ROBERTS.

30, Milton Grove,  
Whalley Range,  
Manchester.

## Vibrator Power Packs

A New Development in Smoothing for Use with Sensitive Receivers

THE standard type of vibrator pack as designed for use with broadcast receivers has proved itself to be not only efficient and reliable but also remarkably silent in operation. When it is used in conjunction with communication receivers of advanced design, the extreme sensitivity and also the extension of the wavelength coverage is apt to disclose traces of contact noise which would pass unnoticed under the conditions of use for which the unit was originally designed.

### Low-frequency Ripple

Masteradio, Ltd., have recently investigated the matter, and have evolved a modified form of smoothing which enables communication sets of the most sensitive type to operate at full gain while drawing their HT supply from a vibratory rectifier. We have recently had an opportunity of trying out the new system, which is

termed the "Silent Surge" circuit, and there can be no doubt that it marks a considerable step forward.

The residual ripple from a standard vibrator pack arises chiefly from contact pulses in the LT battery leads, and is radiated over a wide band of frequencies. Low frequencies are particularly troublesome, and may affect the 50-kc/s band which is included in certain communication sets.

### Balanced Smoothing


In the normal vibrator system the battery circuit, although of low impedance, is not symmetrical to earth, and the small intermittent field which is established is sufficient to cause trouble when the receiver sensitivity is high. The method of overcoming this difficulty which Masteradio have adopted is first to prevent the greater part of the contact pulse from reaching the battery leads by connecting a large reservoir condenser of the order of 1,000 mfd. across the LT supply inside the vibrator screening, and, secondly, to use a balanced smoothing circuit in the external battery leads. With this method the battery may be earthed on either side or left unearthed altogether without evoking any interference. A modified form of this smoothing circuit has been developed in which a part of the unwanted ripple can be used for the balancing out of residual hum in the filament circuits of sets using directly heated valves, and also for reducing the ripple in the rectified HT supply leads, thus enabling less expensive smoothing to be used.

Another improvement has been effected in units of the self-rectifying type by shunting the contacts with a resistance-capacity circuit, the time constant of which bears a definite relationship to the duration of the spark. In this way the transients occurring at the corners of the square waveform are removed and there are fewer high-frequency components to filter in other parts of the circuit. The current rating of the vibrator can be exceeded by a considerable margin without deterioration of the contacts when this circuit is employed.

We were given the opportunity of handling a National H.R.O. receiver deriving its HT supply through the new circuit, and were unable to find any part of the wavelength spectrum where vibrator noise was more than a whisper. Tests with an oscilloscope also demonstrated convincingly the smoothing out of unwanted ripple components.

# VORTEXION

## 50W. AMPLIFIER CHASSIS

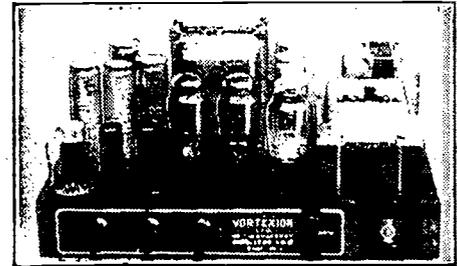


A pair of matched 6L6's with 10 per cent. negative feed-back is fitted in the output stage, and the separate HT supplies to the anode and screen have better than 4 per cent. regulation, while a separate rectifier provides bias.

The 6L6's are driven by a 6F6 triode connected through a driver transformer incorporating feed-back. This is preceded by a 6N7 electronic mixing for pick-up and microphone. The additional 6F5 operating as first stage on microphone only is suitable for any microphone. A tone control is fitted, and the large eight-section output transformer is available in three types:—2-8-15-30 ohms; 4-15-30-60 ohms or 15-60-125-250 ohms. These output lines can be matched using all sections of windings and will deliver the full response (40-15,000 c/s) to the loud speakers with extremely low over-harmonic distortion.

CHASSIS with valves and plugs .....	£17 10 0
Goodmans P.A. Speakers in stock.	
Papier Maché Horn Speakers .....	£6 6 0
Moving Coil Microphones .....	£5 5 0
Chromium Microphone Stands from .....	15 0

**Many hundreds already in use for  
A.R.P. & GOVERNMENT purposes**

### 15w. AC & 12-VOLT DC AMPLIFIER

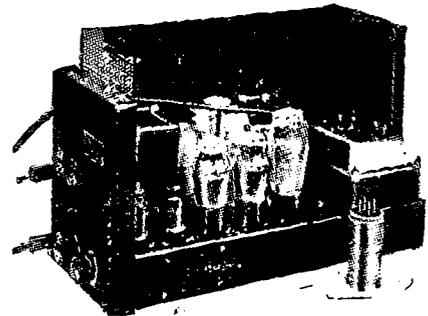

TYPE CP20

This small Portable Amplifier operating either from AC mains or 12-volt battery, was tested by "THE WIRELESS WORLD," October 1st, 1937, and has proved so popular that at customers' demand it remains unaltered except that the output has been increased to 17.2 watts and the battery consumption lowered to 6 amperes. Read what "The Wireless World" said:—

"During tests an output of 14.7 watts was obtained without any trace of distortion so that the rating of 15 watts is quite justified. The measured response shows an upper limit of 18,000 c/s and a lower of 30 c/s. Its performance is exceptionally good. Another outstanding feature is its exceptionally low hum level when AC operated even without an earth connection. In order to obtain the maximum undistorted output, an input to the microphone jack of 0.037 volt was required. The two independent volume controls enable one to adjust the gain of the amplifier for the same power output from both sources, as well as superimpose one on the other, or fade out one and bring the other up to full volume. The secondary of the output transformer is tapped for loud speakers or line impedances of 4, 7.5 and 15 ohms." Prices:

AC and 12-volt CHASSIS with valves, etc. ....	£12 12 0
AC only CHASSIS with valves, etc. ....	£8 18 6

Gauge Case for either chassis, 12/6 extra.

Plus 2C% War Increase.

Delivery: Prompt delivery on "Priority 1A" orders.

**Vortexion Ltd., 257, The Broadway,  
Wimbledon, S.W.19. Phone: LIBerty 2814**

# RANDOM RADIATIONS

## Tell-tale Lamps

HOW many of us have run down accumulators and shortened the lives of H.T.B.'s by leaving battery wireless sets switched on when we imagined that they were off? It's so easy to do it with two designs of receiver. The first is the one whose volume control does not actuate the battery switch when turned counter-clockwise as far as it will go. I have one of that kind: the volume control is just a plain rheostat and the wave-change switch has four positions: SHORT, MEDIUM, LONG and OFF. The set, however, becomes silent when the V.C. is at its minimum position, though both H.T. and L.T. current are still flowing merrily. The other design that may catch you out is the one whose wave-change switch has a GRAM position. You turn the knob absent-mindedly when you've finished listening, and don't notice that its indicator registers GRAM. Again the loudspeaker's voice is stilled; again the load on the batteries continues unchecked and unsuspected. With battery sets of either of these kinds the only safe way is to fit a tell-tale in the shape of a small 0.06 amp. filament lamp placed in a conspicuous position so that it is bound to catch your eye. The lamp is, of course, wired in parallel with the valve filaments. The tiny extra load makes little difference to the life per charge of the L.T.B. and the lamp genuinely earns its keep by acting as a safeguard.

## The Americans, MW and SW

HOW have the medium-wave Americans been coming in during the winter months? I'd like to know, if any readers care to write, for I haven't been able to try for them much myself. For various reasons I can't rig up a decent medium-wave aerial, and the little set I have here needs the best of aerials if it is to be of any use as a distance-spanner on the MW band. Only on rare occasions have I been able to hear anything of "broadcast band" Americans. I imagine, though, that if I heard them at all with this supremely inefficient gear, others with good apparatus may have had fine reception. On the short waves I'm rather luckier, for the set isn't too bad on them, and the rather comic aerial seems to suit its SW circuits fairly well. My best results have been on the 19-metre and 25-metre bands; but

By "DIALLIST"

that may well be because my Heath Robinson outfit isn't happy on other short-wave bands. Perhaps a little later on I'll be able to manage a better set and a less comic aerial.

## Too Difficult!

WHEN you've been used to doing your short-wave DX-ing with a communication receiver and then have to take to an "all-wave" set of the domestic kind in its stead, you realise what a tricky piece of apparatus the latter is to work. To the man used to what is commonly called a broadcast receiver the C-R, with its many knobs, dials and switches, looks rather frightening: he probably feels when he tries one for the first time that it will take him a long while to become familiar with its working. Actually, for all its complicated appearance, the bigger set is by far the easier to use. There is, of course, an art in handling a C-R so as to get the very best results out of it. When, for example, selectivity, RF (or IF) amplification and AF amplification are all variable, the C-R artist can work wonders by giving each control exactly its right setting. But apart from such skilled achievements, the C-R is less difficult to use than the "simple set" for short-wave reception just because of its better tuning arrangements. Bandspreading combined with smooth, backlash-free slow-motion gears and large dials with clear graduations, make it so easy to find exact resonance, or to alter the tuning by the few kilocycles that separate one station from its next door neighbours on either side. But when, say, the entire 19-metre band with its score of stations occupies only a fraction of an inch on the dial and the coarse and rather jerky gears move a pointer half as thick as a poker, I, at any rate, find the tuning-in of all but the noisier short-wave stations a difficult and fiddling business. With a C-R you can always return quickly to a station if you leave it for a while to search elsewhere; with the other kind it is often a very different business.

## The Debate Continues


WHAT is the highest frequency in use on the other side of the Atlantic that is picked up in this country with any kind of regularity? The question arose just before I sat down with this note, when a fellow

enthusiast and I were discussing a problem. Neither of us could remember just what had happened "below ten" in 1938 and 1939. I seemed to recollect reports of reception of U.S.A. police and other transmissions on frequencies as high as 60 megacycles: he maintained stoutly that nothing with a carrier above 40 megacycles had been heard. Neither of us can get hold of his text books or his pre-war records, so there the matter has to rest, unless some reader will kindly help. And here's a further question awaiting an answer: What is the smallest skip-distance recorded for 50-megacycle transmissions? In other words, what is the shortest range outside its normal quasi-visual area at which such an U.S.W. signal has reappeared by means of its sky wave? I maintained that in certain circumstances a 50-megacycle transmission, though unreceivable at 100 miles, might be picked up at seven or eight hundred. My adversary contended that the skip distance would always be far greater; he maintained, in fact, that the signal would in all probability never reappear, that it wouldn't be receivable anywhere outside the limits of its direct-wave area. I seem to remember reading much the same thing about far lower frequencies in the now discredited text books of years ago!

## S.B.S.T.

FOR the radio long-distance enthusiast this time business is getting a bit too complicated. Even before the war countries adopting some kind of summer time didn't all start it or end it on the same date. And countries near the equator didn't as a rule have special summer time at all. When on the night scheduled for its opening here you had wrestled with the problem whether putting the clocks forward an hour or back an hour was the correct thing to do and had acted accordingly, you looked ruefully at that neat world time-chart that had been so useful during the darker months and perhaps tried to work out what hour it then was in Nebraska or Japan. Another time-chart might eventually be compiled as you were able to ferret out information whether this country or that did or did not adopt a summer time and, if it did, when the change was made. In the course of a few days 6 p.m. in London might be noon in New York, then 1 p.m., then noon again. And now comes S.B.S.T. to present the D-Xer with maddening perplexities. To the best of my belief London's 6 p.m. is, at the moment of writing,

## COMMUNICATIONS DEPEND....

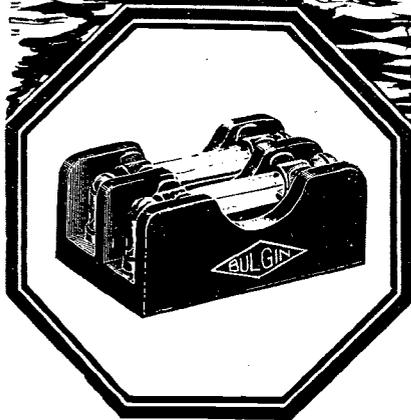

## ON SMALL PARTS....

IN countless instances quite intricate pieces of apparatus are wholly dependent on the proved reputation and reliability of their component parts.

All products from the House of Bulgin are pre-eminent for superior design and workmanship, and every article bearing our Trade Mark has to pass exacting and exhaustive tests during the course of its production.

That is why every manufacture of national importance incorporates Bulgin Components.

*Let us send you*

Our 80 pp. Radio Service Manual :  
Fully illustrated, 280 circuits and diagrams.  
Over 25,000 copies sold.  
1/3 post free.

ALWAYS DEPEND ON

# BULGIN

REGISTERED • TRADE • MARK

A. F. BULGIN & CO. LTD., BY-PASS RD., BARKING, ESSEX.

Telephone: RIPPLEWAY 3474 (4 lines)

### Random Radiations

New York's noon. But what it is now, or will be when this appears in print, in Moscow or Vladivostock, are mysteries too deep for my poor harassed brain to fathom.



### Unfinished Argument

THE other day I ran across an officer who in times of peace is one of our keenest amateur transmitters. We hadn't met before, but when he told me his call sign I realised that he wasn't exactly a stranger, for I recalled many occasions in the days before the war when I'd listened to him working this station or that. Curiously enough, I'd a clear recollection of a Sunday morning argument on the subject of receiving aerials between him and another enthusiast, to which I had listened with the greatest interest. When I reminded him, he also remembered it. The two, who lived many miles apart, had arranged to meet and thrash out the subject at close quarters instead of through the ether. Unfortunately, the outbreak of the war knocked that idea on the head and the argument on which I had eavesdropped so long ago still awaits its continuation.

### Things to Come

Like myself, this erstwhile keen amateur has had very little opportunity for more than a year and a half of indulging in our own particular kind of wireless. As we discussed past adventures on the short waves I could see that his fingers were as eager to get back to the controls of his transmitter as mine are to rest again on the knobs and switches of my big communication receiver. Even when on leave I have not been able to put it into action. All my radio gear had to be stowed away when the war came and brought an influx of evacuees. One of them now sleeps in what was once my wireless den. May it not be long before that room returns to its rightful uses! But I shall have a rare job in unpacking and sorting out the wireless gadgets that now repose in packing cases in a dry cellar. I've forgotten now which case contains what, and though everything was carefully stowed I'm sure that I shall be looking here, there and everywhere for various bits and pieces. And, of course, the thing that one wants most urgently is dead certain to be at the very bottom of the last case in which one rummages. But that unpacking will be a time of such joy that little bothers of that kind won't matter very much.

*The Choice  
of Critics*

### BULGIN FOR FUSES

*The finest Radio and small Electrical glass-enclosed Fuses in the World. The comprehensive range, from 60 mA. to 25 A., covers every requirement. Accurate and uniform in characteristics and made to British Standard Specification No. 646, R.M.A. and R.C.M.F. specification. Absolutely fireproof and safe, sure in action upon 50-75% overload. It is better to be safe than sorry!*

# RECENT INVENTIONS

*A Monthly Selection of the More Interesting Radio Developments*

## RADIO NAVIGATION SYSTEMS

THE pilot of an aeroplane navigates his craft over an area of country in which a number of beacon stations O, Fig. 1, are arranged to radiate a network of beams B. The plane is fitted with a receiver, the tuning of which is continuously and automatically varied over a wide band of frequencies. As a result it

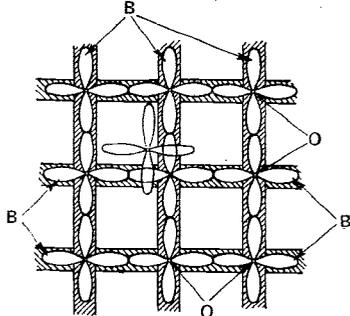


Fig. 1.

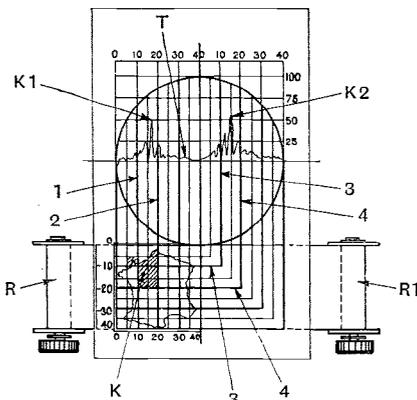


Fig. 2.

Visual system of aircraft position finding.

picks up, simultaneously, the signals from all the beacon stations within range, each being indicated in a manner that distinguishes it from the others.

The received signals, after rectification and amplification, are applied to a cathode-ray receiver, Fig. 2, where they appear as traces T of different amplitudes and positions on a calibrated fluorescent screen. The screen is associated with a chart of the locality, which is mounted on rollers R, R1 and is so arranged that by following the co-ordinate lines 1, 2 enclosing, say, the amplitude peak K1 corresponding to the North-South beam, and the co-ordinate lines 3, 4 enclosing the peak K2 corresponding to the East-West beam, the geographical position of the actual transmitter K can be identified. In the drawing a map of France is shown.

M. Wallace. Convention date (France) 21st February, 1938. No. 525393.

## CATHODE-RAY TUBES

THE object of the invention is to reduce the risk of high-voltage leakage from the anode of a cathode-ray tube to any of the other electrodes such as the grid or cathode, or even to the focusing or deflecting coils, via the glass surface of the bulb. For this purpose the anode is mounted independently at one end of a tubular glass support, the other end of the support being sealed to the glass bulb of the tube at a considerable distance away from any of the other electrodes.

Since the glass support must be sealed to the metal of the anode at one of its ends, and to the glass wall of the tube at its other end, it is most conveniently made for assembly in three sections. The two end sections are each made of the particular type of glass best suited to the kind of seal required, whilst the middle section is of glass capable of being welded to both end-sections.

A. F. Pearce. Application date, 18th April, 1939. No. 527980.

o o o

## SECOND-CHANNEL INTERFERENCE

THE drawing shows an aerial input coupling designed to minimise second-channel interference in a superhet set. The aerial primary coil L is coupled to a secondary coil L1 forming part of the first tuned input stage, both coils being in series with a fixed condenser C. The secondary L1 is also in series with a coil L2; the circuit as a whole is tuned by a variable condenser C1 and is connected across the input terminals T of the first amplifier valve.

If the signal range is 150 to 300 kilocycles, and the intermediate frequency is 450 kc/s, the local oscillator will operate over a range of from 600 to 750 kc/s and second-channel interference is liable to occur between 1050 and 1200 kc/s.

To eliminate such image frequencies, the coupling between the coils L and L1 is adjusted so that, within this range,

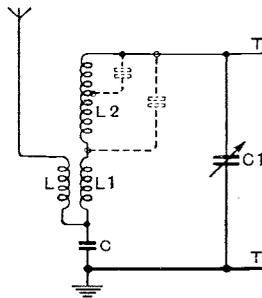


Image-frequency suppression circuit.

the voltages developed across the winding L1 are equal in amplitude but opposite in phase to those developed across the condenser C. They will accordingly balance out, though the desired signal


frequencies will scarcely be affected and will pass through to the amplifier.

Ferranti, Ltd., and G. I. Thomas. Application date March 18th, 1939. No. 526503.

o o o
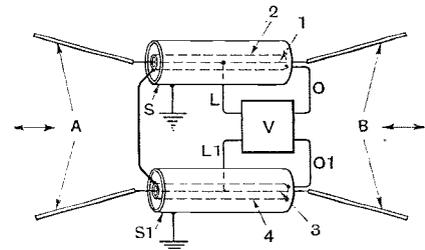
## RADIO RELAY STATIONS

THE Figure shows a short-wave installation for relaying simultaneously in different directions, so that a signal, introduced, for instance, at any one point, can be reproduced throughout a whole chain of such stations. The system is primarily designed for working on a common carrier wave, the signal being preferably superposed as a frequency modulation. It can also be used, among other things, to stabilise the frequency of a network of short-wave radio stations.



Half-wave resonators for S-W relay stations.

Two pairs of V-shaped aerials A, B, of opposite directivity as indicated by the two arrows, are so coupled together that there is little or no reaction between the input and output circuits of the common amplifier V. The coupling circuits comprise two half-wave tubular or coaxial resonators 1, 2 and 3, 4, which are equivalent electrically to a transformer having a single primary winding and a single secondary winding, with uniformly distributed capacity and inductance. Screening is effected by tubes S, S1.

In operation a signal arriving, say, from the left, is collected by the pair of aerials A, and half the energy is fed by the leads L, L1 to the input of the amplifier V. The output from the amplifier is fed by the leads O, O1 to the "primaries" 2, 4. These, in turn, energise the "secondaries" 1, 2 of the two pairs of aerials A, B and so re-radiate the amplified signal simultaneously in opposite directions.

Marconi's Wireless Telegraph Co., Ltd. (assignees of G. W. Hansell). Convention date (U.S.A.) April 1st, 1938. No. 527168.

The British abstracts published here are prepared with the permission of the Controller of H.M. Stationery Office, from specifications obtainable at the Patent Office, 25, Southampton Buildings, London, W.C.2, price 1/- each.

# ELECTRADIX RADIOS

## HEADPHONES

### L.R. Double Headphones



Field Signallers, 120 ohm Phones. All leather headbands with slide adjustment chin strap and 4ft. cord. Comfortable ... **5/-**

L.R. Single Phone & Cord - 2/-

## MORSE INKERS

Captured Contraband, new Tape Strip Recorders; portable or Table. Dot-dash, Cheap. Wheatstone Strip Hand Perforators, 15/- Paper Tape for Morse, green or white. Brass Tape Reels in mahogany case, 4/6.

The ROLLS-ROYCE of BUZZERS is the CAMBRIDGE-TOWNSEND. Tiny and Shrill. 10/-



Perfect for Wavemeters, ideal for signals. High note Model "T" Diaphragm blade. Platinum Contacts. The smallest Buzzer possible ... **10/-**

## VARIABLE CONDENSERS

.0005 mfd. Tekade, 1/6; .00075 Polar Compax, 2/-; S/W. Formo, 2/6; J.B. Midget, .0001, 2/6; 3-gang variable, .0005, 3/6.

## RHEOSTATS

### 10-watt Small Rotary



Back of panel, one hole, front knob, 4 ohms, 2 1/2 amps., 2/6; 6 ohms, 1.7 amps., 2/6; 10 ohms, 1 amp., 2/6; 20 ohms, 1/2 amp., 2/6; 30 ohms, .3 amp., 2/6; 30,000 ohms Volume Controls, 1/6.

RESISTORS, on mica, 8 ohms, 1 1/2 amps., 9d.

## RECORD CUTTER NEEDLES

Real Diamond, 7/6. Rotary Needle Sharpeners, 1/6. Wood Needles, round or triangle, 1/- doz.

## CAMERASCOPES

True Twin Camerascopes, 2 lens viewers, short focus, stereoscopic. 1/6 post free.

## RELAY FOR RADIO WORK

A 2 ma. Table Relay. Compact vertical type, enclosed. Screened 2,000 ohm coils. Platinum contacts. Single pole change-over. 1/2 amp. contacts. Wood base. Metal case. Size 2 1/2 in. diam., 3 1/2 in. high. Price ... **8/6**

No. 6 Telephone Relay. Single pole change over. Double wound for 2 volts or 6 volts, 25 ma. 7/6.

ALUMINIUM FOIL. 12in. by 12in., 9d. sheet.

LOUD SPEAKERS (state wants).

## OZONIZERS

SWEET AIR IN ANY ROOM, with a Lesdix Neron Ozonizer. A.C. mains only. Can be hung on the wall; 10 watts, 1 tube, 20/-; 25 watts, 2 tube, 25/-.

## DYNAMO BARGAINS

110-volt, .8 amp. D.C. ball bearing, semi-enclosed. 1,850 revs., 15 lb. 6in. x 5in. Cheap. Only **15/6** Post Free.



200 volts 1/2 amp. ... **19/6** Post free  
200 volts 1 1/2 amps. ... **27/6** "

## MOTOR DRIVES GEARS

Skew drive Gear Boxes for Cine. or Boat, 1/2 or 1/3 h.p., 10/-. Ditto on C.I Pedestal, with flywheel, 15/-. Small 2 to 1 Gear Boxes, 1/3 h.p., 4/6.

DYNAMOS. Double Current, Govt., cost £15, two commutators, D.C., 6/8 v., 3/5 ams. and H.T. 400/600 v. 100 mm., 5 1/2 in. dia., 12 1/2 in. long, 17 lbs., 4,000 revs., ball bearings, 25/-. We have some surplus soiled sets, 15/-.  
SMALL A.C. MAINS MOTORS. Enclosed, self-start on load. 230 v., 1/80 h.p., Type 40, 1,500 revs., 18/6. Split phase, 1/10 h.p., 2,500 revs., 45/-.  
SMALL D.C. MAINS MOTORS. 1/40 h.p., Type 60, 220 v., K.B. series, 1,750 revs., 15/-. Ditto, 1/40 h.p., G.E.C., 230 v. series, 2,000 revs., 16/-. Ditto, 1/12 h.p., Croydon 110 and 230 v. shunt, 1,700 revs., 30/-. M.G. for A.C., 220 v. to 100 v., 1 amp. D.C., 77/6. 100 v., 15/-. All fully guaranteed.

## MICRO-MOTORS

A.C. split phase synchronous motors, squirrel cage rotor, 3/4 in. dia. Dog clutch drive to reduction gear from 2,000 revs. to 58 r.p.m. Voltage 15 to 20 volt, 50 cycles, reversible, double shaft, enclosed, laminated, new. Suit model drive, remote control switching, tuning drive, etc., 8/-. Post free.

## ALTERNATORS

1-PH. PHASE HIGH CYCLES TEST ALTERNATORS. The famous 52a WATFORD H.F. Alternators, 250 watts at 500 cycles, 20 volts 10 amps. Self-exciting Inductor type, slot wound stator. Small size. Cost £30. Sale, 70/-. WOOLWICH 400 watt 46/W/A 500 cycles 50 volts 3 amps. and D.C. of 70 volts 3 amps., £5/10/-.

VERTICAL MOTOR-ALTERNATORS. 170 cycles, Marconi type, 1/2 kW. and 1/4 kW. Motor off 100 volts D.C., £10. 2 1/2 kW. NEWTON Vertical, 580 cycles 200 volts 25 amps., 1,600 revs. Motors, 220 volts D.C., £20.  
3-PHASE ALTERNATORS. G.E.C. 333 cycles 3 ph. 120 volts 1 amp., fitted reed Tachometer. Self-exciting horizontal, £6/10/-.

A.C. HAND ALTERNATOR. Permanent steel magnets, wound armature driven by gearing and handle. Output of 80 volts 20 ma. A.C. For Medical Treatment, A.C. experiments, etc. Sale, 7/6. Carriage, 1/-.

## VIBRATOR H.T. KITS

### Home-made L.T. Battery-operated

Supersede H.T. Batteries. The Vibrator converts D.C. to A.C. by vibrating uniformly. Any voltage to 100 watts obtained by transformers and rectified for radio H.T.



### WE OFFER


American Vibrators totally enclosed, slightly dented covers. **10/-**  
4-pin non-sync. at the low price of

## SWITCHES, METERS, ETC.

### A Special Design in Auto-Switches

with time-lag tripping on 2 to 3 amps. Safety thermo switch with quick-break auto overload trip, for back of panel with front indicating knob, compact, 4in. x 2in. x 1/2 in. deep. Any voltage up to 1,000 v.

Worth a guinea. **5/6**  
ONLY **5/6**

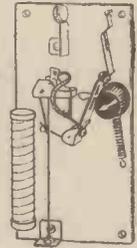

### Magnetically tripped Switches that operate instantaneously

Circuit Breakers of first-class make, in place of fuses. Operate instantly on an overload. Fireproof construction and bakelite or metal cover. Made in single, double, and triple pole. Prices are very low, and type marked with a star have thermal trip delay.

### SINGLE POLE, HEAVY IRON CASE 250/400 volt

Illustration shows S.P. with cover removed.



Rating	Type	Price
6 amps.	S 11/1G	11/6
6 "	S 11/1Z*	13/6
10 "	S 11/1G	16/-
15 "	S 11/1G	18/-

## HOT WIRE METERS

### For Radio or Low-Frequency

1/2 amp., 2 1/2 in. dial, front panel, 100 ma. to 1/2 amp., 10/-  
200 ma. to 1 1/2 amp., 7/6. 500 ma. to 2 amps., 7/6.  
To 2 1/2 amps., 15/-. High voltage model in square ebonite case, 1 1/2 amps., 10/-. Special Sullivan Meters with cut-out switch, 15/-. High-grade magnet damped H.W. Meters. 100 to 500 ma., 4in. dial, Marconi type, 25/-. 200 ma. to 1 1/2 amps., J. & P., brass case, 27/6. 2 amp. and 3 amp. ditto, 32/6. 6in. and 8in. H.W. Meters to 10 amps., 20 amps. and 50 amps., 40/-.

## PM METERS

Genuine Weston Model 354. Central zero 1 to 15 amps., pol. mag. dead beat. Flush panel, 2 1/2 in. dial, nickel or black. Sale price, 7/6. Varied ranges of large Switchboard Meters. M.I. & M.C.

## LAB. GALVANOMETERS

Vertical Ballistic with mirror on coil, quite new, by Tinsley, 60/-. Mirror Galvos. In brass case, 90/-  
Galvos. by Gambrell Paul and Nalder, £3/10/- and £4 each. Universal Multiplying Galvo. Shunts, 35/-  
Silvertown, Siemens and Fuller horizontal 3 1/2 in. Galvos., 7/6. Vertical Telegraph type, Central Zero Scale, 4/6. Multiplex Vibrators, 45/-. Wheatstone Bridges.

## HORIZONTAL BRASS-CASED GALVOS., 7/6.

CELL TESTERS, Megger 3-0-3 mov. v coil, aluminium case, 25/-.

If you have Resistances to measure you will find this Standard RESISTANCE BOX guaranteed to standard. 1,000 ohms, 4,300 ohms, 8,000 ohms, 12,400 ohms. Cheap.



## MEGERS AND OHMMETERS

Evershed Bridge with decade res. box, 10,000 ohms. Meggers: 100 volts, 250 volts and 500 volts, and small MEG. for D.C. mains. N.C.S. Ohmer 500 volts to 20 megs. Ev. Edg. Metrohm, 250 volts, .01 to 20 megs. Silvertown Portable Test Set, Bridge type, .001 ohm to 1 meg.

Add postage for all mail orders.

# ELECTRADIX RADIOS

218, UPPER THAMES STREET, LONDON, E.C.4  
Telephone Central 4611

21d. stamped envelope must be enclosed for post replies.

**CLASSIFIED ADVERTISEMENTS.** The charge is 6/- for each paragraph of 2 lines or less, and 3/- for every additional line or part thereof, average 7 words to a line. Each paragraph is charged separately. ADVERTISEMENTS for the July issue are accepted up to Firs. Post on Tuesday, June 10th, at the Head Office, Dorset House, Stamford Street, London, S.E.1. or one day earlier at provincial Offices.

THE PROPRIETORS retain the right to refuse or withdraw advertisements at their discretion. They are not responsible for clerical or printers' errors, although every care is taken to avoid mistakes. Cheques and postal orders should be made payable to Illiffe & Sons Ltd. and crossed. Notes are legal tender and cannot be traced if lost in transit.

ADVERTISERS may have letters, other than circulars, addressed to numbers at this office. The words Box 000, c/o "WIRELESS WORLD" must be paid for and a further 1/- added for registration and forwarding replies. DEPOSIT SYSTEM. Full particulars upon application to the Deposit Dept., "Wireless World," Dorset House, Stamford Street, London, S.E.1.

**TRANSFORMERS & CHOKES**  
**PARTRIDGE**  
*a guarantee in itself*

If your work is for the Government and you are experiencing difficulty in obtaining transformers from your usual source, please get into touch with us.

We can still give prompt deliveries providing your order quotes the number of the Government contract for which the goods are required. The latter is essential.



King's Bldgs., Dean Stanley St., London, S.W.1.  
Phone: VICTORIA 5035

**BOOKS**

**THE SUPERHETERODYNE RECEIVER**

by Alfred T. Witts. A reliable and comprehensive guide to the superheterodyne receiver, incorporating all recent developments. It provides the essential working knowledge required by every keen amateur, radio student and service engineer. Recognised everywhere as the standard work. "Gives all the information necessary for a complete understanding of the Superheterodyne Receiver," says PRACTICAL WIRELESS. Fourth Edition. 4/6 net.

**INTRODUCING RADIO RECEIVER SERVICING**

by E. M. Squire. One of the best books available on this subject. A concise introduction to the practical operation of a radio receiver which will be especially valuable to students, radio service engineers, testers and dealers, enabling all to attain a working knowledge of receivers and servicing equipment in a minimum of time, and without unnecessary theoretical frills. 6/- net.

★ Write for 4-page illustrated leaflet, of books on Radio and Television.

**PITMAN**  
Parker Street, Kingsway, W.C.2

**CLASSIFIED ADVERTISEMENTS** intended for the JULY issue can be accepted up to Tuesday, June 10th.

**NEW RECEIVERS AND AMPLIFIERS**

**HAVE** Your Amp. or Receiver Built to Your Spec.; high fidelity equip. a speciality. Estimates and advice free.—S.A.R. Supplies, 293, Norwood Rd., S.E.24. [9580]  
**McMURDO** Silver 15-17 Olympic Autoradiogram, new, at pre-war list, 72 guineas; Ekco C511 Console, pre-tax, 17 guineas; Ossor 72, pre-tax, 9½ guineas.—A.C.S. Radio, 44, Widmore Rd., Bromley. [9563]  
**£15/10** Only, usual price £22.—Wireless World 2 R.F. Receiver, with push-pull quality amplifier, chassis, 10 valves, including tone control stage, 8 watts triode output, ideal for quality reproduction from radio and gramophone; limited number.—Bakers Selhurst Radio, 75, Sussex Rd., South Croydon. [9519]

**RECEIVERS & AMPLIFIERS—SECONDHAND, ETC.**

**PARTRIDGE** 30-watt Amplifier, separate mains supply for first stage, diode damping inaudible hum level, 10 hrs. use; £16.—Advertiser, 117, Clayton Rd., Newcastle, Staffs. [9544]

**SCOTT** 15, with Capehart Changer, Operadio Amplifier, in magnificent cabinet, £110; Marconi 345, £8/17/6; Philips, 361a, £13/10/—A. C. S. Radio, 44, Widmore Rd., Bromley. [9564]

**FOR** Sale, Guthman-Silver Comm. set, single span set mounted on single chassis, 2-stage amp., ACHL2 trans., coupled 2 PX25s p.p., all little used; offers.—Box 2581, c/o The Wireless World. [9577]

**Wanted**  
**SKYRIDER** Defiant, also Magnavox 66; full particulars.—2, Cliff Rd. Gardens, Leeds, 6. [9558]

**NATIONAL** Standard HRO, complete, coils, speaker, or SX17, SX23.—Details, price, 2, Church St., Evesham. [9570]

**WANTED**, several HRO receivers, in good condition, also Hallicrafters.—Write Box 2578, c/o The Wireless World. [9566]

**COMMUNICATION** Receiver, A.C. mains; excellent price paid for good make in first class condition.—Details, Chancery Prec. Inst. Service, Middle Claydon, Bletchley. [9573]

**HIGH** Class Chassis or auto change radiograms wanted for spot cash. High price paid. Midwest, Scott, H.M.V., R.G.D., etc.—27, Worcester St., Wolverhampton. [9507]

**PUBLIC ADDRESS**

**LET** Us Estimate for Your P.A. work; wide experience in office, factory, dance-band and air-raid alarm systems, etc.; estimates and advice free. Compet. prices.—S.A.R. Supplies, 293, Norwood Rd., S.E.24. [9581]

**NEW MAINS EQUIPMENT**

**VORTEXION** Mains Transformers, chokes, etc., are supplied to C.P.O., B.B.C., L.P.T.B.; why not you? Limited, but unequalled.  
**VORTEXION**, Ltd., 257, The Broadway, Wimbledon, London, S.W.19. Phone: Lib. 2814. [9571]

**SHORT-WAVE EQUIPMENT**

**RADIOMART**, largest distributors communication equipment. National distributors.—48, Holloway Head, Birmingham. [9555]

**NEW LOUDSPEAKERS**

**BAKERS** Brand New Surplus Speaker Bargains.  
**EVERY** Music Lover Interested in Realistic Reproduction should write for free descriptive leaflet now.

**£5/10**; usual price £10.—Brand new permanent magnet infinite baffle speaker, complete with beautifully finished cabinet in polished walnut.

**£2/10**; usual price £5.—Brand new super quality triple cone speaker, permanent magnet model; exceptional bargain; limited number.

**SECURE** One of These Exceptional Bargains Now.  
**BAKERS** Triple Cone Conversions Will Immensely Improve Reproduction of Your Present Speaker. ("For a few shillings you have converted a speaker scheduled for the scrap heap into one worth pounds.—W. E. Darby, Grad.I.E.E.") Write for details.

**BAKERS SELHURST** RADIO, 75, Sussex Rd., Sth. Croydon [9423]

**SECOND-HAND LOUDSPEAKERS**

**MAGNOVOX** 66 Speaker, perfect; £4.—Advertiser, 117, Clayton Rd., Newcastle, Staffs. [9545]


**CABINETS**

**A** CABINET for Every Radio Purpose.  
**SURPLUS** Cabinets (Undrilled) from Noted Make.

**WE** Have Hundreds in Stock (no Catalogues); send measurements of chassis, etc., and say what kind of cabinet required; stamp for reply. INSPECTION Invited.

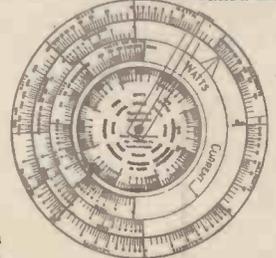**H. L. SMITH** and Co., Ltd., 289, Edgware Rd., W.2 Tel.: Pad. 5891. [9331]

*Answers!*  
**FLIK-O-DISK**  
*Quick!* TRADE MARK



100% British Design

100% British Made

Answers all OHM'S LAW problems—for example:  
**What will be the voltage when current I flows through resistance R?**  
**What will be the voltage with watts value W and I current flowing?**  
**What is the current flowing where watts value is W and voltage is E?**  
**What current will flow through R resistance where voltage is E?**  
**What will be the resistance where current I flows at voltage E?**  
**What will be the resistance where watts W is at voltage E?**  
**What will be the resistance where watts W is at current I?**  
**What is the wattage at voltage E through resistance R?**  
**What is the wattage of current I through resistance R?**  
**What will be the wattage of I current at E voltage?**

The scales read from 1 millivolt to 1,000 volts. From 1 ohm to 1,000,000 ohms. From 1 milliamp to 10 amperes. From one-tenth of a milliwatt to 10,000 watts.

FULL INSTRUCTIONS WITH EACH INSTRUMENT

PRICE 4/6 Postage 3d.

Order at once whilst deliveries are good

**IONIC COMPUTERS**

514, Ipswich Rd., Trading Estate, SLOUGH, BUCKS, ENG.

**WARD** WE MANUFACTURE:  
**ROTARY CONVERTERS** DC/AC for operating P.A. amplifiers, Radio Receivers, etc.  
**DC/DC ROTARY TRANSFORMERS**, SMALL ALTERNATORS, SMALL DC MOTORS, H.T. GENERATORS, MAINS TRANSFORMERS up to 10 k.v.a. PETROL ELECTRIC generator sets up to 50 k.v.a.  
**BATTERY CHARGERS** for private and industrial use  
We can also handle general small engineering work.  
Full details of any of the above upon request  
**CHAS. F. WARD**  
46, FARRINGTON ST., LONDON, E.C.4  
Telephone: Holborn 9703.  
Works:  
37, White Post Lane, Hackney Wick, E.9.

**TRIX** SOUND EQUIPMENT  
RELIABLE AMPLIFICATION  
The TRIX ELECTRICAL COMPANY LTD.  
65, Bolsover St., London, W.1. Euston 5471

# buying sound equipment?

**I**F you are buying Sound Equipment and P.A. Gear you will find an investigation of the R.S. Amplifiers range interesting and well worth your while. We do not claim to build "the best in the world"—perfection, we hope, is unattainable else we should not strive. But we do sincerely believe that what we make is as good as it can be made and perhaps better than most. Below are listed briefly a few items from our standard catalogue which will gladly be sent on request. If you have any special needs tell us and we'll be happy to co-operate.

## AMPLIFIERS

"M.M. Twin."—Double speaker equipment giving 12 watts output. Five valves, AC/DC 190-260 volts. Complete with "mike," stand and cables.

"Universal Fifteen."—15 watts output. Two speakers (Exponential Horns), 11 watts and 13 watts. Complete with "mike," stand and cables.

"Porta Thirty."—30 watts output. Two speakers (this equipment can accommodate up to fifteen speakers!). AC 200-250 volts. Complete with "mike," C.P. stand and cables. The acme of perfection in portable amplification.

## CHASSIS

Five types of chassis are available: 50 watt, 30 watt, 15 watt, 12 watt and a 12-watt Battery Unit.

Crystal Microphone.  
Speaker Units (Exponential Horns), 11 watts and 13 watts.  
"Mike" stands.

# R.S. Amplifiers LIMITED

THREE & FOUR HIGHFIELD ROAD  
SHEPPERTON - MIDDLESEX

'Phone: Walton-on-Thames 1019

**DYNAMUS, MOTORS, ETC.**  
ALL Types of Rotary Converters, electric motors, battery chargers, petrol-electric generator sets, etc., in stock, new and second-hand.  
**WARD, 46, Farringdon St., London, E.C.4.** Tel.: Holborn 9703. [0518]

**GRAMOPHONE MOTORS**  
**CAPEHART** Autochanger, taking 20 mixed, and turns them over, latest, as new. £65; Columbia portable Record Player, new, £6/10.—A.C.S. Radio, 44, Widmore Rd., Bromley. [9565]

**WANTED**  
WANTED, new or second-hand Radiogram motors, A.C. or Universal.—Particulars, etc., to Hadley Bros., 587, Bearwood Rd., Smethwick. [9557]

**RECORD** Changers and Gram Units, 500 wanted for cash, full prices paid; £2/10 paid for H.M.V., etc. record players any condition.—27, Worcester St., Wolverhampton. [9506]

**VALVES**  
**PURCHASED**; service engineers' stocks; new and old types.—Details, Chancery Prec. Inst. Service, Middle Claydon, Bletchley. [9574]

**WANTED**, for Rogers-Majestic 11/9 Radiogram, 6FM valve, Triode-Pentode, Octol base, 6.3 volts.—Box 2579, c/o The Wireless World. [9569]

**TEST EQUIPMENT**  
**WANTED**  
**URGENTLY**; signal generators, analysers, valve testers, etc.—Details, Chancery Prec. Inst. Service, Middle Claydon, Bletchley. [9575]

**MORSE EQUIPMENT**  
**FULL** Range of Transmitting Keys, practice sets and equipment for Morse training.—Webb's Radio, 14, Soho St., London, W.1. 'Phone: Gerard 2089. [9553]

**BUSINESSES FOR SALE OR WANTED**  
"THE Wireless and Electrical Trader" is an essential part of the equipment of every Wireless Trader, its pages reflect the very latest turn of trade events, and it is read by all the leading dealers and manufacturers, for particulars of businesses offered or wanted. By subscription, to the trade only, 17/6 per annum, post free.—Send your trade card for specimen copy to Dorset House, Stamford St., London, S.E.1. [0614]

**REPAIRS AND SERVICE**  
**L.T.P.** Repair All Mains Transformers and Chokes. Prompt delivery.

**LONDON TRANSFORMER PRODUCTS, Ltd.**, Willesden, N.W.10. Wil. 6486 (3 lines). [9552]

**MAINS** Transformers, output transformers rewound.—Davies, 30, Morley Avenue, Manchester, 14. [9578]

**ALL** Types of Receivers and Amp. Serviced; aligning and testing constructor's sets a speciality. Compet. prices.—S.A. Radio, 293, Norwood Rd., S.E.24. [9582]

**MAINS** Transformer Service, repairs, rewinds, or construction to specification of any type, competitive prices and prompt service.—Sturdy Electric Co., Dipton, Newcastle-on-Tyne. [0516]

"SERVICE with a Smile."—Repairers of all types of British and American receivers; coil rewinds; American valves, spare line cords.—F.R.L.; Ltd., 22, Howland St., W.1. Museum 5675. [8934]

**METROPOLITAN RADIO SERVICE**—Guaranteed repairs to American and British receivers; linecord resistances, Majestic I.F. transformers, and rewinds; trade supplied.—1021, Finchley Rd., N.W.11. Speedwell 3000. [0435]

**NEW COMPONENTS**  
**AERIAL** Equipment.—Insulators, Short-wave five ring quartz 3in. long, non-hygroscopic, 3/6 a dozen. Small porcelain shell, 1/- per dozen. 12in. stand off, 4/6 per dozen. Aerial wire, 7/22 copper, 2/6 per 100ft. coil. All carriage paid. Cash with order or c.o.d.—P. and F., 49, John Bright St., Birmingham, 5. [9561]

**COMPONENTS, SECOND-HAND, SURPLUS, ETC. PREMIER RADIO.**

**PLEASE** See Our Displayed Advertisement on page 5.

**SOUTHERN RADIO'S** Wireless Bargains.

**ALL** Goods Previously Advertised Still Available.

**SOUTHERN RADIO**, 46, Lisle St., London, W.C. [Central] 6653 [9239]

**GARRARD** Record Changer, 10in. or 12in.; £7.—Advertiser, 117, Clayton Rd., Newcastle, Staffs. [9546]

**G. A. RYALL**, Arnehurst, Marsh Lane, Taplow, Bucks.—Goods advertised in May issue still available, except Amplifiers, Speakers and Transformers. [9556]

**G. A. RYALL**, Arnehurst, Marsh Lane, Taplow, Bucks.—Goods advertised in April issue still available, except Amplifiers, Speakers and Transformers. [9562]

**COULPHONE** Radio, New Longton, Preston, Tungsram and American valves. Pickups with volume control, 17/6; 10in. Rola P.M. with transformer, 22/6; Goodman's 8in. P.M., 17/6; electrolytics, 500r.; 8 mfd., 2/9; 8+8 mfd., 4 leads, 4/9; 16+8 mfd., 6/3; 50v. 50 mfd., 1/9.—S.A.E. for new list. [9551]

**FERRANTI** Multi-range D.C. Test Instrument with Case and Leads, £6; Collaro A.C. gramophone motor with unit plate, 35/-; Magnavox "Diode" 33 speaker, 2.500 ohm field, 50/-; Ferranti transformers, A.F.5, A.F.6. OPM.6(c), 10/- each; chokes, B.2 10/-, B.3 5/-; Varley choke, 20 h. 140 ma., 10/-; Nicore I transformer, 10/-.—9, Kimberley Gardens, Newcastle-on-Tyne, 2. [9579]

# GALPINS

**ELECTRICAL STORES**  
Owing to War Conditions this business is now transferred to:—  
**21, WILLIAM ST., SLOUGH, BUCKS**  
'Phone: SLOUGH 20855

Terms: Cash with Order

**ELECTRIC LIGHT CHECK METERS**, small, late type, well-known makers, in good condition, electrically guaranteed for 200/250 volts 50 cy. 1 phase A.C. mains. 5 amp. type, 6/-; 10 amp., 7/6; 20 amp., 9/- each. Post 1/- on all types.

**D.C. ELECTRIC LIGHT CHECK METERS**, 200/250 volts 5 and 10 amps., 4/6 each, post 1/- (in new condition).  
**PHILLIPS HIGH VOLTAGE CONDENSERS**. Infid. at 4,000 volt working, 5/6 each, carriage 1/6.  
**EX R.A.F. GLASS ACCUMULATOR TANKS**, 5x5x8in., new and unused, 3/6 each, post 1/-.

**EX R.A.F. SWITCH PANEL**, with case (new), fitted 6 small knife switches, leads, cords and cleats, complete in wood case, 2/6 each, post 6d.

**HIGH-VOLTAGE TRANSFORMERS**, useful for 'all test work or television. Input 200/240 volts, output 5,000 and 7,000 volts, 7/6 each, post 1/-.

**VOLTAGE CHANGING TRANSFORMERS** (Auto Wound), 100/110 to 200/240 v., or vice versa, fully guaranteed, 1,000 watts; 60/-; 2,500 watts, 110/-.

**DUG-OUT LAMPS**, Ex R.A.F., solid brass construction, glass dome, complete with 12-volt bulb (any bulb can be fitted), wall fitting, 3/- each, post 6d.; Ditto, wing type, as new, 2/6, post 6d.

**DUG-OUT LAMPS**, Ex R.A.F., porthole type, or can be bracket fitted, glass dome, three colour fitting, white, red or green, solid brass construction, 6in. dia., complete with bulb; any size bulb can be fitted. Price 5/-, post 6d.

**EX R.A.F. AUTOMATIC CHARGING CUT OUTS AND VOLTAGE REGULATORS**, to suit any dynamo up to 20 volts at 15 amps., fully adjustable, wiring instructions, complete in metal case. Price 3/6, post 9d.

**DYNAMOS**, all shunt wound and fully guaranteed, 50/75 v.-15 a., £6/10/-; All carriage forward.

**25-VOLT D.C. MOTOR**, maker "Crompton," 1/2 h.p., ball bearing, in perfect order, £3, carriage forward.

**110-VOLT D.C. MOTOR**, totally enclosed, rated at 8 amps., ball bearing, in new condition, make good slow-speed dynamo, £2/5/-, carriage forward.

**GUNMETAL PULLEYS**, 7in. diameter, to take 1in. dia. rope, complete with rope guard and hook, 7/6 each, post free

**PHILLIPS TRANSFORMERS**, 220 v. input, output 2,000-0-2,000 volts, 200 m/a and 2 L.T.s., 50/- carriage forward.

**1/2 HP 110 v D.C. MOTOR**, in good working order, 25/-, carriage forward.

**SLIDER RESISTANCE**, 2,500 ohms at 200 m/a, worm and wheel control, 25/-, post free.

**FLOODLIGHTS**, 12in. dia., multi mirror type with 5in. dia. margin spot centre, any bulb can be fitted, 15/- Carriage paid.

**AERO DYNAMOS**, output 12v.-12 amps., new, 15/- each. Carriage 2/6.

**PRESS-BUTTON UNITS**, 8-way, 7 x 6 x 1 1/2 ins., fitted capacitors, condensers, etc. Price 5/6, post free.

**1 kW AUTO TRANSFORMER CORE** for rewinding, complete with clamps and bobbin. Price 12/6, carriage paid.

**CROMPTON DYNAMO**, output 220 volts, 10 amps., 4 pole, shunt wound. Price £8/10/-, carr. forward.

**ROTARY CONVERTOR**, D.C. to A.C., input 220 volts D.C., output 85 volts 2 kW., 50 cycle, 3 or 1 phase Price £5, carr. forward.

**ROTARY CONVERTOR**, D.C. to D.C., 25 volts input, output 350 volts at 50 m/a. D.C. Price 30/-, carr. paid, 20 WATT SPEAKER (American), 110 volt A.C., complete with metal rectifier and speech transformer: in large cabinet. Price £4/10/-, carr. forward.

**LARGE TRANSFORMER**, input 230 volts 50 cycles, output 300-0-300 volts at 6 amps. Price £3/10/-, carr. forward.

**LARGE TRANSFORMER**, input 230 volts 50 cycles, output 300-0-300 volts at 10 amps. Price £5, carr. forward.

**ROTARY CONVERTOR** for charging. Input 220 volts 50 cycles A.C., output 12 volts 10 amps D.C. Price £5/10/-, carr. forward.

**BELL PUSHES**, ex-G.P.O., solid ebonite, two silver contacts, as new, 1/6, post free.

**MILLIAMMETERS**, 2-in. dia., 0-30, 25/-; ditto, 0-150, 25/-; ditto, 2 1/2-in. dia., 0-100, 25/-, post free.

**TUNGSTEN CONTACTS**, new, one fitted screw and one fitted blade, 1/9 the pair, post free.

**HT 8 RECTIFIERS**, second-hand, in perfect order. 7/6 post free.



**You just plug in with Solon Electric Soldering**

With the Solon you can work wherever there's a lamp holder—and do better work! Solon Electric Soldering is easy, neat, strong and clean. No stopping to heat up—constant heat maintained at point. 15 hours soldering uses only 1 unit.



Made for following standard voltages:—200/220, 230/250.



Handyman model supplied complete with Resin-Cored Solder, Flex and Lamp Adaptor **9/4**  
Solon Resin-Cored Solder **6D.** per reel.

**W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.**

(Dept. 23/E), Engineering Sales Dept., Milton Court, Westcott, Dorking, Surrey.



**FOR THE RADIO SERVICE MAN, DEALER AND OWNER**

The man who enrolls for an I. C. S. Radio Course learns radio thoroughly, completely, practically. When he earns his diploma, he will KNOW radio. We are not content merely to teach the principles of radio, we want to show our students how to apply that training in practical, every-day, radio service work. We train them to be successful!

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

Dept. 38, International Buildings, Kingsway, London, W.C.2.  
Please explain fully about your instruction in the subject marked X

Complete Radio Engineering  
Radio Service Engineers

Elementary Radio Television

If you wish to pass a Radio examination, indicate it below.

Inst. of Wireless Technology  
P.M.G. Certificate for Wireless Operators  
Provisional Certificate in Radio Telephony and Telegraphy for Aircraft  
City and Guilds Telecommunications

Name ..... Age.....  
Address .....

(Use penny stamp on unsealed envelope)

**RADIO CLEARANCE, Ltd.**  
**L**ISSEN 2v. Battery Pentodes, 4-pin, side terminals, P.T.2A, 4/11 each.  
**L**OW-LOSS Ceramic Valve Holders Lissen Hi-Q, baseboard and chassis, 7-pin, 1/- each.  
**L**OW-LOSS Short-wave Condensers, variable ceramic insulation brass vanes, Lissen Hi-Q, minimum capacity 5 microfarads, 20 mfd. List, 5/6 each; our price 2/6 each.  
**P**USH-PULL Switch, Lissen 2-point, 4d. each; 3-point, 6d. each.  
**Y**AXLEY Type Switches, 4-pole, 3-way, 9d. each.  
**Y**AXLEY Type Switches, 4-bank, 2-pole, 4-way, 2/6 each.  
**Y**AXLEY Type Switches, 6-bank, 3/- each.  
**Y**AXLEY Type Switches, 9-bank, 3/6 each.  
**R**OLA P.M. Speakers, latest model, 7/8in. cone, with power and pentode transformer, boxed, 17/6 each.  
**S**TRAIGHT Line 3-wave-band Dials, 1/11 each.  
**M**AINS TRANSFORMER. 300-0-300v., 100 m.a. 5v. 2 amps. 6.3 5 amps. Drop-through chassis type, 12/6 each.  
**M**AINS TRANSFORMERS. Wearite 100 watt, auto transformers, 100-110v., 200-250v., reversible, 14/11 each.  
**C**HASSIS Mounting Valve Holders, American Octals, 6d. each.  
**C**HASSIS Mounting Valve Holders, English Clix type, 4-5-7-pin, 3d. each.  
**C**ENTRALAB Volume Controls. Midget type, 2,000, 5,000, 25,000, 50,000, 100,000 ohms. Less switch, 2/9 each; 1,000, 25,000, with switch, 3/6 each.  
**P**RESS Button Units, 6inx6inx2in., complete with 6 press buttons and capacitors, 4/11 each.  
**P**LESSEY Motor Tuning Units, including fractional h.p. A.C. motor for 12v. continual running on 24v., intermittent running and 2-gang 0.0005 condenser, 8/6 each.  
**8**-WAY Push-button Switches, 1/3 each.  
**4**-WAY Push-button Switches, 1/3 each.  
**D**RIPPING Resistances for All Purposes, total resistance 535 ohms, 5 taps in steps of 50 ohms, standard for Pye, Lissen, Ever Ready, etc., 3/6 each.  
**R**ESISTANCES, 100 ohms, 10 watt, 1/- each.  
**10**W.T. Coils Connecting Wire, 4d. each, glazed.  
**P**USH-ON Pilot Lamp Holders, 3d. each.  
**P**LESSEY Single-gang 0.0005 Variable Condensers, 1/1 each. 2-Gang 0.0005 variable condensers with Vernier control, 1/11 each.  
**P**ERMUABILITY Tuned Press Button Units, 2/6 each.  
**B**.I. Wire-end Bias Electrolytics, 50 mfd., 12v., 1/6 each.  
**T**UBULARS, wire-end non-inductive paper condensers, all sizes up to 0.01, 5d. each; 0.1, 7d. each.  
**T**.C.C. 2 mfd. Electrolytic Condensers, 200v. working, 1/3 each.  
**C**ONDENSERS, 0.0005 triple, 1/9 each.  
**W**ESTERN Metres, 0.50 m.a. and 0.300 m.a. moving coil type, 25/- each.  
**I**L.B. Reels, 16 and 20 gauge Tinned Copper Wire, 2/6 each.  
**E**LECTROLYTICS, 12x16 mfd., .525v. peak, with clip fitting, 3/11 each.  
**T**.C.C. 1x1 mfd. Paper Condenser, 250v., A.C. working, 450 D.C. working, 1/11 each.  
**T**.C.C. 1 mfd. Paper Condenser, 350v. working, 1/- each.  
**D**DOUBLE Fuse Holders, complete with two 1in. fuses, 1/6 each.  
**T**.C.C. Bias Condenser, 25 mfd., 25 volt, 1/6 each.  
**W**E Have in Stock a Large Selection of High-voltage Paper Condensers, all capacities, too numerous to advertise. Advise interested clients to call. Also large selection of high-voltage transmitters and chokes.  
**A**LL Orders Must Include Sufficient Postage to Cover. Hours of business: Week-days 9.4.30, Saturdays 9.1 p.m. Please write your name and address in block letters. We cannot undertake to answer enquiries unless full postage is included (2½d.).  
**R**ADIO CLEARANCE, Ltd., 95, High Holborn, London, W.C.1. Telephone: Holborn 4631. [9568]  
**Wanted**  
**E**LIMINATOR Wanted, send us yours: a fair price by return.—Buntons, 12, Yewcroft Av., Newcastle-on-Tyne, 5. [9550]  
**L**IGHTING Accumulators Wanted, lead, acid or Edison type, state quantities, capacity, condition and price.—Wireless College, Colwyn Bay. [9548]  
**TUITION**  
**R**ADIO Training.—P.M.G. exams. and I.E.E. Diploma: prospectus free.—Technical College, Hull. [0611]  
**P**RACTICAL Radio Postal Courses, coaching for I.P.R.E. R.A.F. A.I.D. exams.; booklet free.—Secretary, I.P.R.E., Bush House, Walton Avenue, Henley-on-Thames. [9547]  
**R**ADIO Engineering, Television and Wireless Telegraphy; comprehensive postal courses of instruction.—Apply British School of Telegraphy, Ltd., 179, Clapham Rd., London, S.W.9. (Estd. 1906). Also instruction at school in service for H.M. Merchant Navy and R.A.F. [9249]

**ARMSTRONG**  
Have a limited quantity of replacement parts for various Model Armstrong chassis, including:—  
**ARMSTRONG 465 K.c. I.F. Transformers** wound with Litz wire and incorporating Iron Cores. These transformers are highly efficient. Price 18/6 a pair.  
**ARMSTRONG 110 K.c. I.F. Transformers** designed to increase the efficiency of our older type chassis. Price 17/6 a pair.  
**ARMSTRONG Mains Transformers**, replacement stocks for most models. Price 21/- to £1/15/-  
**SPEAKERS** including High Fidelity models suitable for all Armstrong chassis. Prices from 21/-. Various small parts available. Kindly send stamped addressed envelope for reply.  
**ARMSTRONG MANUFACTURING CO.**  
WARTERS ROAD, HOLLOWAY, LONDON, N.7.  
Phone: NORTH 3213

**METAL CASES**  
FOR RADIO & RADIO INSTRUMENTS also CASES & BOXES IN WOOD & REXINE MANUFACTURERS of FABRICATED PARTS IN WOOD AND METAL TO THE RADIO AND AIRCRAFT INDUSTRY  
Send 2½d. in stamps for details of RADIO CABINETS FOR THE HOME.  
**LOCKWOOD & CO.,** Lowlands Road, Harrow, Middlesex. Phone: BYRON 1818.

**ACOUSTICAL MANFG CO.**  
SPECIALISTS IN Amplifiers, Transformers, and all Sound Equipment  
have (owing to enemy action) removed to:  
**138-140, WARDOUR STREET, LONDON, W.1,**  
where our full services are available.

**RELAYS** for A.C. and D.C.  
**SILENT & RELIABLE**  
2 VA coil consumption, from 2-600 volts, tested to 2,000 volts. Unmounted and in cast iron casing. Also Time Lag Relays. High Sensitive Relays, complete control plants.  
Apply for leaflet SPN/WW  
Multiple contact Relay L F  
**LONDEX LTD.**  
Electrical Remote Control Engineers and Manufacturers  
Anerley Works, 207, Anerley Road, London, S.E.20.  
Tel.: HYDENHAM 6256/6259.

**RADIO RECEIVER SERVICING AND MAINTENANCE**

By E. J. G. Lewis. Everything connected with wireless servicing, maintenance and repair is exhaustively described and is set out for immediate reference. 8s. 6d. net.  
 "The book is so practical, so replete in facts, and so well arranged that the reader will gain the necessary knowledge to work in a logical manner" (Wireless World).

**MODERN RADIO COMMUNICATION**

By J. H. Reyner, B.Sc. (Hons.), A.C.G.I. A comprehensive guide to modern radio theory and practice. A particularly valuable introduction for prospective recruits for Signals branches of the Services. Deals fully with every point and explains fundamentals in the clearest possible manner. There is no more popular or successful book. 2 vols. 7s. 6d. each.  
 "A thoroughly good book" (T. & R. Bulletin). "Among the most important of elementary textbooks" (Wireless World).

**SHORT-WAVE RADIO**

By J. H. Reyner. A comprehensive practical survey of modern developments in the use of short, ultra-short and micro-waves. It provides a great deal of valuable data concerning the practical methods of their use in radio and television transmission. 10s. 6d. net.  
 "One of the finest short-wave treatises available" (Journal of the Institute of Engineers, Students Quarterly Journal).

**THERMIONIC VALVES IN MODERN RADIO RECEIVERS**

By A. T. Wits. This up-to-date handbook is a practical guide to the whole field of modern theory and practice in the application of thermionic valves to radio receivers. For radio mechanics. 8s. 6d. net.

**ELECTRICAL AND WIRELESS EQUIPMENT OF AIRCRAFT**

Including Repair, Overhaul and Testing of Magnetos  
 By S. G. Wybrow. The primary object of this book is to indicate to ground engineers, in broad outline, the basic principles of design, together with notes on the care and maintenance of equipment, fault localisation and repair. A volume in the Aeronautical Engineering Series—Ground Engineers. Fourth Edition. 5s. net.

From Booksellers or from

PITMAN'S, 39, Parker St. Kingsway, W.C.2.



**Joining the R.A.F.?**

ARMY—NAVY—MERCANTILE MARINE OR TAKING UP WORK OF NATIONAL IMPORTANCE in which a thorough knowledge of the Morse Code is essential for becoming a skilled W/T operator? Then investigate the proved Candler method of

**MORSE CODE TRAINING**

There are courses for beginners and operators.

A Candler trained operator now serving in the R.A.F. says—

"... I should like to thank both yourself and the company for the great start which I obtained through taking your Junior Code Course. The experience which I gained from that, has kept me 'miles in front' of others who relied on obsolete means of learning code."

Fill in the Coupon and learn more about this highly efficient Candler method of Code training in your own home.

**JUNIOR Scientific Code Course** for beginners. It teaches all the necessary code fundamentals scientifically.

**ADVANCED and High-Speed Telegraphing Course** for operators who want to increase their w.p.m. speed and improve their technique.

**TELEGRAPH Touch-Typewriting Course** for W/T operators who want to become expert in using a typewriter for recording messages.

Courses supplied on Cash or Monthly Payment terms.

**COUPON**

Please send me a Free Copy of Candler "Book of Facts."

NAME.....

ADDRESS.....

Post Coupon in Id. unsealed envelope to London Manager

**CANDLER SYSTEM CO. (55.W.),**  
 121, Kingsway, London, W.C.2.  
 Candler System Co., Asheville, North Carolina, U.S.A.

641

**SITUATIONS VACANT**  
 WIRELESS Technical Instructors Required in Army Units.

**EMOLUMENTS.**—Pay 8/9 per day (7 days a week); clothing, rations and accommodation, or if this cannot be provided allowances at authorised rates; if married and otherwise eligible, family allowance payable in respect of wife and children, subject to allotment from pay.

**CANDIDATES** Should Preferably be under 35 and over 24, and

(A) Hold one of the following qualifications:—

Graduateship of the Institution of Electrical Engineers.

Final (Grade III) Certificate of City and Guilds of London Institute Examination in Radio Communication.

Higher National Certificate in Electrical Engineering.

Certificate of City and Guilds of London Institute in Radio service work.

(B) Be able to pass an examination on the following syllabus:—

Simple algebra, including quadratic equations; simple trigonometrical ratios and identities; vectors.

Properties of electrical currents; heating of conductors; magnetic fields; unit of current; Ohm's Law; resistance in series and parallel; potentiometers.

Magnetic effect of current fields due to parallel wires; field due to a solenoid; electro-magnets. Meters.

Induction; effect of rotating a coil in a magnetic field.

Mutual and self induction and inductance; effect of inductance on growth and delay of current.

Capacity; charging storage and discharge of condensers; through resistance and inductance.

Alternating currents; vector diagrams; effect of resistance variation; effects of L and C in A.C. circuit; phase difference of currents; resonance in a series circuit; parallel circuit of L and C; Q factor.

Elementary knowledge of valves; simple theory of amplifiers, oscillators and detectors; general principles of radio practice.

**SUITABLE** Candidates will be interviewed at Local Centres, and, if successful, will be enlisted and appointed Acting Sergeant Tradesman. For those who are on the Schedule of Reserved Occupations, special arrangements will be made to enable them to be enlisted. In the event of any applicant found to be reserved under Schedule of Reserved Occupations special application will be made for relaxation of the Schedule. No guarantee can be given that this application will be successful.

**APPLICATION** Forms may be Obtained by Postcard from the Under-Secretary of State, The War Office (A.G.6e), Whitehall, S.W.1. [9520]

**LABORATORY** Assistant Required by Firm in S.W. London, good ground knowledge essential.—Write, stating age, experience, and salary required, Box 2580, c/o The Wireless World. [9572]

**IMMEDIATE** Position Available to Man with Comprehensive Knowledge of 16 mm. Sound on Film Projectors; must be capable of carrying out all repairs to projectors and amplifier speakers; good salary to right man; accommodation provided if necessary.—Write, giving full details of experience to Box 2572, c/o The Wireless World. [9498]

**BROADCAST** Officer Required by the Gold Coast Government for two tours of 12-24 months, with possible permanency; salary £450, rising to £720 a year; free passages and quarters; candidates, age 25-35, must have been properly trained as radio communication engineers and have had at least two years' responsible practical experience, preferably in connection with broadcast transmitters, broadcast studio equipment, or radio relay service; a knowledge of modern superheterodyne short wave receivers is essential.—Write, stating age and full particulars of qualifications and experience, to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting M/9617. [9576]

**TECHNICAL TRAINING**  
 GREAT Possibilities Exist for Technically Qualified Engineers, key men in wartime and afterwards. Through the home-study courses of The T.I.G.B. take a recognised engineering qualification such as A.M.I.Mech.E., A.M.I.E.E., A.M.I.B.E., A.F.R.Ae.S., A.M.I.Chem.E., O. and C., etc., in which examinations. The T.I.G.B. students have gained 25 FIRST PLACES and Hundreds of Passes. Write to-day for "The Engineer's Guide to Success"—Free—containing the world's widest choice of engineering courses covering all branches, including Aeronautical, Mechanical, Electrical Wireless, Chemical, etc.

**THE TECHNOLOGICAL INSTITUTE OF GREAT BRITAIN**, 82, Temple Bar House, London, E.C.4. [9535]

**PRINTING**  
 CARDS, memos, billheads, 1,000 7/6; rubber stamps, samples—"B" Tices, 11, Oaklands Grove, London, W.12. [9410]

**PATENT NOTICE**

**THE** Owner of Patent No. 482835 is desirous of arranging by way of licence or otherwise on reasonable terms for the commercial development in Great Britain of this invention, which concerns Improvements in or Relating to Television Plant.—For particulars, address Elkington and Fife, 20 to 23, Holborn, London, E.C.1. [9567]

**HUGE TELEVISION PURCHASE!**

**CHASSIS, COMPONENTS, CABINETS, C.R. TUBES, etc.**

We have just completed the purchase of the stock of the pioneer Television manufacturer. Chassis, C.R. Tubes, Speakers, Cabinets, Amplifier units, Components and accessories of every description. Enquiries invited from public and trade. To be cleared at ridiculous prices. Inspection invited. Here are only a few items.

**POWER PACK AND AMPLIFIER CHASSIS**

Size 16 1/2 in. x 13 1/2 in. x 4 in. Planned as the main unit for Television receivers costing many pounds. Includes heavy mains transformer 350-0-350, 120 m.a. with 4 4-volt 5 amp. tappings. High voltage transformer for supplying C.R. Tube. Various condensers including 16 x 16 mfd, 550 volt working, 1-16 mfd. 450 volt working, 50 x 50 x 2 mfd. B.I. Electrolytics, etc., etc. Pentode output transformer; chokes; resistors; trimmers; bias electrolytics; mica and tubular condensers; short-wave coils, etc., etc. The quality of the workmanship and components is of the highest class. Also a slightly smaller chassis fulfilling the same functions but made for a different model, 62/6.

67/6

**TIME BASE CHASSIS**

For 8in. Cathode Ray Tube. Well-made cadmium-plated chassis, size 17in. x 14 1/2 in. x 2 1/2 in., containing approximately thirteen fixed resistors ranging from 15,000 ohms to 1 megohm, five variable resistors, 2,000 to 20,000 ohms, approximately 14 various tubular and electrolytic condensers, also sundry focus and scanning coils and chokes. (Complete circuit and service manual available, price 6d. each.)

30/-

**VISION UNITS**

To fit on above Time Base. Consists of 3 Mullard T.S.E.4 and 1 Mazda D1 Valves. Approximately 25 resistors ranging from 75-75,000 ohms, and about 30 condensers of various values, together with Reflector, Grid and various Band Pass Coils, also approximately 10 chokes of various descriptions and W6 Westector. All completely wired and carefully screened in metal box. (Complete circuit and service manual available, price 6d. each.)

40/-

**TUBE SUPPLY UNITS**

For high voltage 16/18in. Tubes. Approx. 6,000 volts output. Includes B.I. 1 x 1 mfd. 7,000 volt d.c. test condensers with porcelain insulators, transformer and rectifying valve, all shielded in metal case. (B.I. condenser supplied separately at 20/- and the transformer at 10/6.)

45/-

**MAINS TRANSFORMERS**

These are one of the best jobs we have seen. Originally made for Television Power Packs where accuracy and robustness are essential. Weight 12 lb., size 5 1/2 in. x 4 1/2 in. overall. 350-0-350 volts, 120 m.a. Four tappings each giving 4 volts 5 amps. Brand new and unused. Each

25/-

**CABINETS**

Cabinets of every description available. Table type, Consoles, and large pedestal lift-up lid. All in first-class condition. Beautiful examples of the cabinet-maker's art. Made to house costly Television receivers. Let us know your needs, or better still, come and inspect.

**C-R: TUBES**

The consignment includes 8in., 10in. and 15in. MAGNETIC type Cathode Ray Tubes, which are not available to-day through ordinary channels. Brand new in original cartons or mounted on new chassis. Send us your requirements and we will quote by return. To be cleared at low prices but must be collected by purchaser.

Most lines advertised last month still available.

**LONDON CENTRAL RADIO STORES**  
 23, LISLE STREET, LONDON, W.G.2  
 GERRARD 2969

# QUICK COURSE IN MORSE

by R.A.F. Signallers

## on COLUMBIA Records

A complete new course of instruction in Morse Code made with the co-operation of R.A.F. Signallers. From the Alphabet to Fast Transmission with varying degrees of typical jamming. Invaluable to those about to join the Fighting Forces, A.T.C., or Merchant Service.

What an advantage to enter, already proficient in this important part of the training! Start now—ask your local dealer about these records—today!

4 Records; DB 1995-98 12/- (+2/8d. Tax)  
Booklet of Instruction included

*This space reserved for*



W. BRYAN SAVAGE LTD.

### BOOKS, INSTRUCTIONS, ETC.

WANTED, Ghiradi Radio Physics Course.—6, Denmark Rd., Southport. [9559]

WEBB'S Radio Map of the World Locates Any Station Heard. Size 40x30in. 4/6, post 6d. On linen, 10/6, post 6d. Webb's Radio Globe, 12in. model. Radio prefixes, zones, etc. 27/6.—Webb's Radio, 14, Soho St., London, W.1. Phone: Gerrard 2089. [9554]

EVERY Radio Dealer Who is Not a Regular Reader of "The Wireless and Electrical Trader" should send his trade card at once for a specimen copy and full details of the "Trader" Services. "The Wireless and Electrical Trader" has the widest influence, and is read by all the leading manufacturers and traders. Trade only, 17/6 per annum, post free. Published at Dorset House, Stamford St., London, S.E.1. [0615]

"LEARNING Morse" (Sixth edition). An easy method of mastering the international signal code, gives method of practising with the key, and also details of an easily constructed morse practice set. Price 6d. net, by post 7½d., from Iliffe and Sons Ltd., Dorset House, Stamford Street, London, S.E.1.

"RADIO Laboratory Handbook." By M. G. Scroggie, B.Sc., A.M.I.E.E. (Second Edition ready shortly). The only practical handbook on the subject. Specially compiled for amateurs and industrial and official laboratory engineers. Complete information about equipment, the necessary instruments, and the correct methods of operating them. Price 10/6 net, by post 11/1, from Iliffe and Sons Ltd., Dorset House, Stamford Street, London, S.E.1.

"FOUNDATIONS of Wireless." By A. L. M. Sowerby, M.Sc. Second Edition. An elementary textbook of receivers. Deals fully with the construction of wireless sets, valves, and the process of detection. Price 5/- net. By post 5/6, from Iliffe and Sons Ltd., Dorset House, Stamford Street, London, S.E.1.

## ENGINEERING OPPORTUNITIES



This unique Handbook shows the easy way to secure A. M. I. C. E., A. M. I. Mech. E., A. M. I. E. E., A. M. I. A. E., A. M. I. W. T., A. M. I. R. E., and similar qualifications. WE GUARANTEE—"NO PASS—NO FEE." Details are given of over 150 Diploma Courses in all branches of Civil, Mech., Elec., Motor, Aero, Radio and Production Engineering, Draughtsmanship, Training, Inspection, Government Employment BUILDING (the great after-war career), R.A.F. MATES, etc. Write for this enlightening Handbook to-day. FREE and post free. Men with Radio knowledge can obtain attractive posts in the Services.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, 387 Shakespeare House, 17, 18, 19 Stratford Place, London, W.1

## FOR SHORT-WAVE COMPONENTS

Communication Receivers for work of National importance; and all accessories for short-wave work and experiments. Call or write to

### WEBB'S RADIO

14 SOHO ST., OXFORD ST., LONDON, W.1

# INVENTORS

We continually seek new inventions and products in all branches of industry for development and production by the manufacturing Companies of the Simmonds Group throughout the world.

SIMMONDS DEVELOPMENT CORPORATION LTD.  
BUSH HOUSE, W.C.2.



## THE SIMMONDS GROUP



## MALLYORY

# VIBRATORS

are always dependable

(BRITISH PATENTS)

ALONG every front Mallyory has pioneered in vibrator design to ensure safety, dependability and long service.

Mallyory offers synchronous and non-synchronous vibrators for 6, 12 and 32 volt input also a new range of accepted "STRATOSPHERE" vibrators for high altitude aircraft service.

Mallyory engineers are at your disposal.

## P. R. MALLYORY & CO. INC.

INDIANAPOLIS, INDIANA, U.S.A.

Represented exclusively in Great Britain by

FRANK HEAVER LTD., Kingsley Rd., Bideford, N. Devon, Eng.

## WHY LEAVE YOUR SPEAKER AT HOME?



Our Compact 2ft. mouth HORN, for use in limited space. Ideal for clear speech. Unbolts for packing into a small space.

Price - - £4 - 16 - 3 (ex works)

UNIT WITH TWIN DIAPHRAGM £15 - 15 - 0

(about 40 watts required for full excitation)

## VOIGT PATENTS LTD.

THE COURTS, SILVERDALE, SYDENHAM, S.E.26

Telephone: SYDenham 6666.

# WIRELESS SERVICING MANUAL

By W. T. COCKING, A.M.I.E.E. (of "The Wireless World")

Sixth Edition, Revised and Enlarged

A complete book of reference. The most reliable practical guide for amateur and professional

It deals fully with Testing Apparatus and explains the methods of locating and curing faults in receiving equipment. Includes an additional chapter on automatic frequency control.

Ganging, Automatic Volume Control, Instability, Distortion, Mains Hum, Whistles, Local Interference and aerials are all separately treated.

PRICE 6/- net

By post 6/6

Issued in conjunction with "THE WIRELESS WORLD" and published by the Proprietors:—

ILIFFE & SONS LTD., DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1

# ROLA

## LOUD SPEAKERS

THE WORLD'S FINEST REPRODUCERS

## TRANSFORMER LAMINATIONS

Core Width  $\frac{9}{16}$ " to  $1\frac{1}{2}$ " (E's & I's)

### EIGHT STOCK SIZES

A Comprehensive Bulletin together with details of Associated Covers and Clamps with design data will be sent to manufacturers on request.

### BRITISH ROLA LIMITED

MINERVA RD., PARK ROYAL, N.W.10. WILlesden 4322



# FREE TO ENGINEERS AND RESEARCH LABORATORIES

Two publications have been issued by Multicore Solders Ltd., which give much useful information about soldering in general, in addition to facts about the advantages of Ersin Multicore Solder, with its three cores of non-corrosive Ersin Flux. Executives are invited to send for copies of these publications and a free sample of this A.I.D. and G.P.O. approved solder.

### MULTICORE SOLDERS LTD.

BUSH HOUSE, LONDON, W.C.2.

Tel: TEMple Bar 5583/4



## Cheerfulness


When cheerfulness is in danger of disturbance, light a 'Player,' and with a few 'puffs' put trouble in its proper place. The friendly Sailor, as always, stands for cheery contentment and a guarantee that quality and purity remain unchanged.

KEEP THAT HAPPY EXPRESSION

*Player's Please*




N.C.C.547F

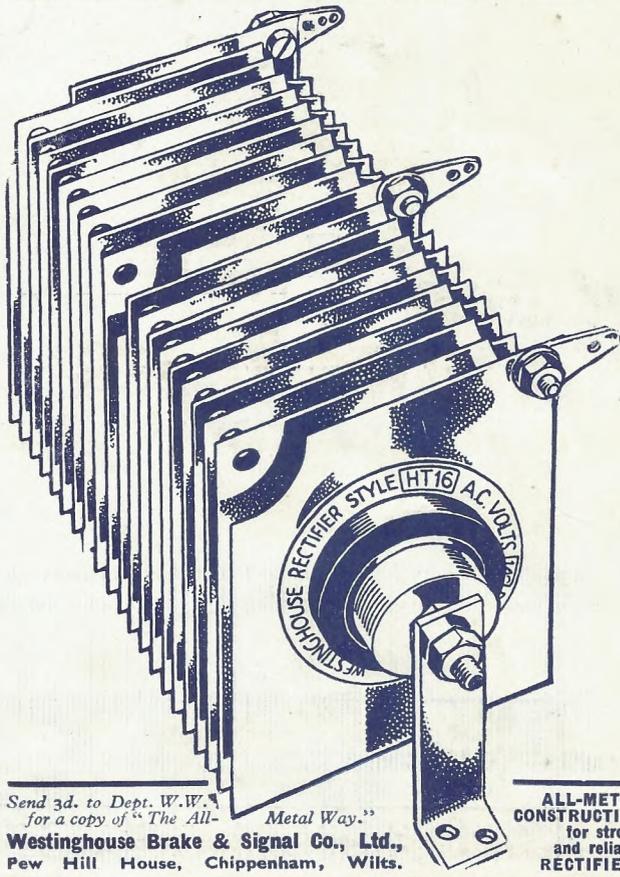

Send 3d. to Dept. W.W. for a copy of "The All-Metal Way."

Westinghouse Brake & Signal Co., Ltd.,  
Pew Hill House, Chippenham, Wilts.

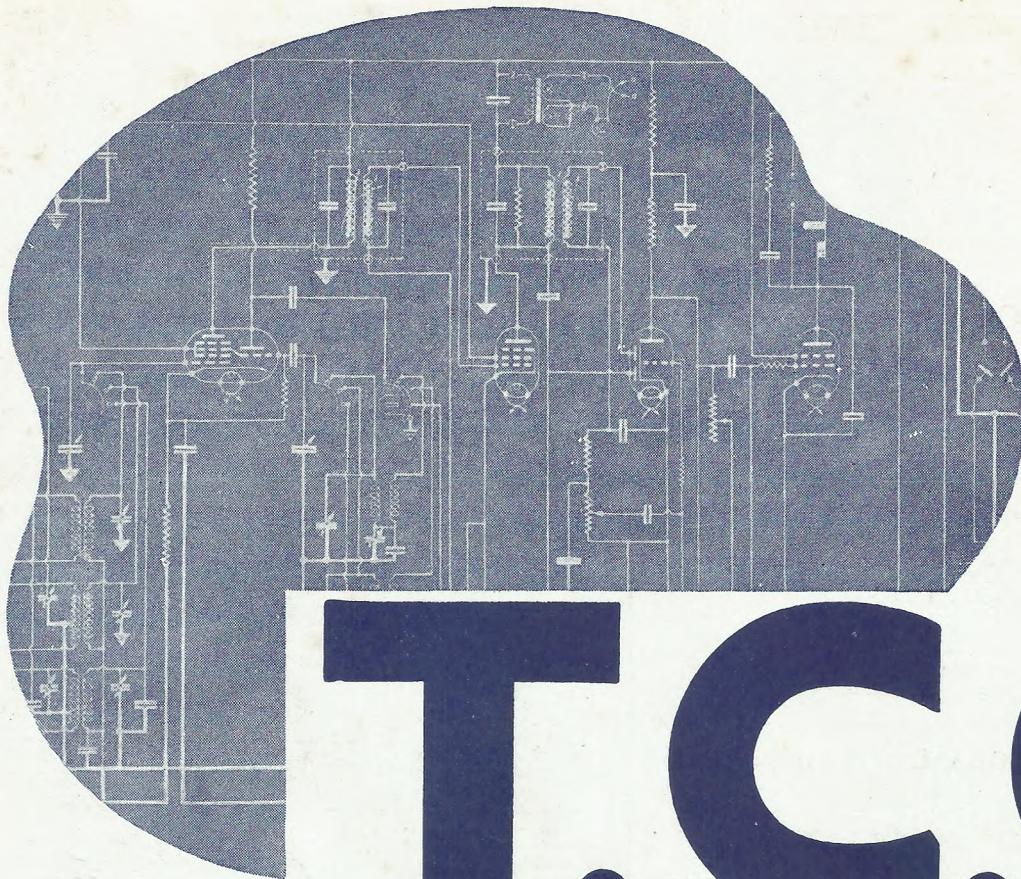**ALL-METAL  
CONSTRUCTION**  
for strong  
and reliable  
RECTIFIERS



# T.C.C.

## PRE-EMINENT IN PEACE INDISPENSABLE IN WAR

Advertisement

of

THE TELEGRAPH CONDENSER CO., LTD.

G.A. 2175