

HAM TIPS



A PUBLICATION OF THE RCA TUBE DIVISION

Vol. XVI, No. 4

© 1956, Radio Corporation of America

December, 1956

VISUALIZING SWR

'SWR Circle' Clarifies Mistaken Theories

By Morton Eisenberg*, W3DYL

Most amateurs have a working knowledge of Standing Wave Ratio (SWR) and are aware that it is preferable to have minimum SWR on feeders so that power lost in the antenna feeder is kept to a minimum. However, this writer has heard numerous remarks on the air which indicate that many theories exist on the subject of how the SWR can be varied, including the erroneous idea that SWR can be varied by changing the length of the feeder.

To help clear the air of such misinformation, this article contains a graphical presentation of the relationship between the SWR on a transmission line and the length of the line. The presentation, usually referred to as the "SWR Circle," shows how the feed-point impedance can be found when the SWR and electrical length of the transmission line are known.

The SWR on the transmission line between the transmitter and the antenna coupler, "A" in Figure 1, can be varied by tuning and adjusting the coupler by inserting a device such as an impedance bridge in the "A" line. In this manner, a "flat" or nonresonant line ($SWR = 1.0$) can easily be realized.

The SWR circle applies to the "B"-line. coupler to antenna or, if no coupler is used, transmitter to antenna. Although optimum tuning of the transmitter and coupler assures that the maximum rf power is being transferred to the feeder terminals, it has no effect on the SWR.


In Figure 2, the SWR circle is plotted for a 52-ohm cable. Similar SWR circles can be drawn for any other cable characteristic impedance and the procedure will be described later in this article.

Referring to Figure 2, suppose an SWR of 2:1 is measured on the "B"-line because a 52-ohm coaxial feeder is terminated by a 26-ohm resistive antenna impedance. Depending on the feeder length, the feed-point impedance could be 26 ohms resistive at Point X, 104 ohms resistive at Point Y, or any one of the infinite number of complex impedances, such as Point Z. Point Z represents a feed-point impedance of 65 ohms resistive in series with a 39-ohm inductive reactance. The convenient way to write this mathematically is: $65 + j39$.

Point X is the feed-point impedance which is found when there is no feeder, or when the feeder length is equal to a half-wavelength or any multiple of a half-wavelength. Point Y is the feed-point impedance when the feeder is equal to a quarter-wavelength or odd multiples of a quarter-wavelength. The feed-point impedance at Point Z is due to the feeder length being equal to one-eighth-wavelength.

It should now be clear that varying the length of the feeder cannot vary the SWR on the "B" line, nor can it vary the feeder losses per foot. When the feeder length is increased, simply "go around the SWR circle" in a clockwise direction. Remember that one full trip around the SWR Circle is equal to a half-wavelength of feeder.

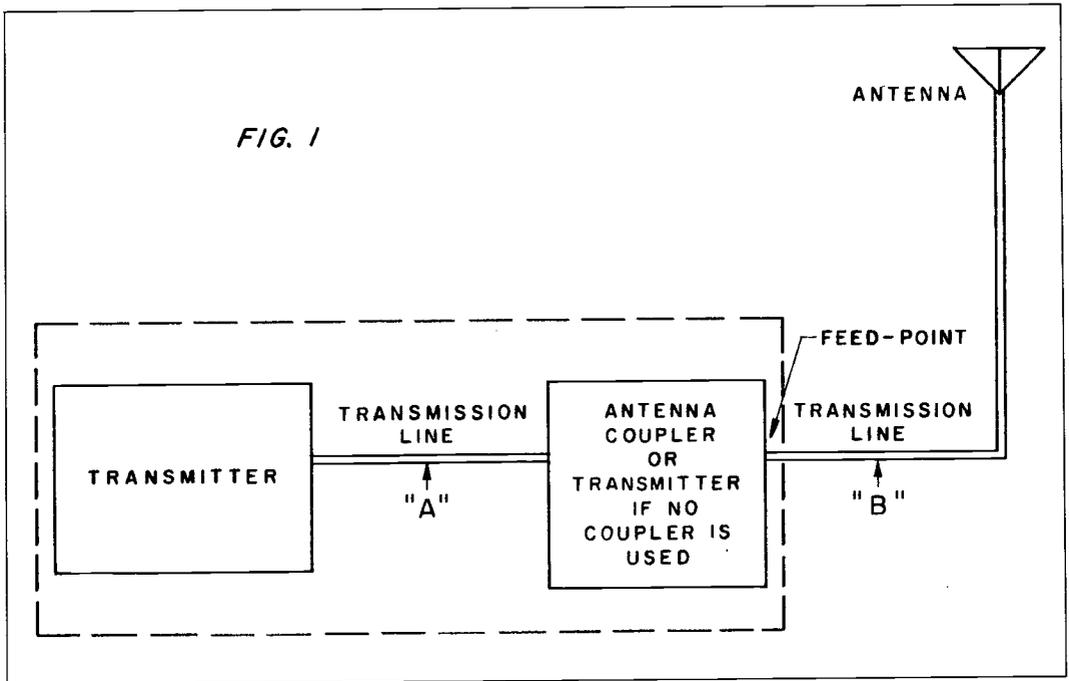* Defense Electronic Products Division, Camden, N. J.



The use of different feeder lengths to obtain variation in feed-point impedance is known to hams as "pruning the feeder to get the antenna to load." "Pruning the feeder" is sometimes necessary because of the limited impedance-matching capabilities of the coupling circuits. In this manner, a feed-point impedance which will more easily match the feeder to the transmitter (or coupler) can be obtained. *It is important to note* that although the feeder length has been changed, the SWR remains constant. You are simply going to another point on the SWR circle.

The SWR on transmission line "B" can be adjusted for minimum only by doing one of the following: (1) changing the transmitter frequency, (2) adjusting the length of the antenna element or elements, or (3) adding or adjusting a matching device at the junction of the antenna and the feeder.

Adjusting SWR for Receiver Feeders

The SWR situation on the receiver feeder is slightly different from the problems arising in transmitter feeders. In this case, the SWR is a result of a mismatch of the input impedance of the receiver and the characteristic impedance of the feeder. Consequently, the SWR can be adjusted to 1.0 by the use of a coupler at the input terminals of the receiver. This coupler is only necessary, of course, if

the input impedance of the receiver is not equal to the characteristic impedance of the feeder.

Other SWR Circles

For various cable characteristic impedances, SWR circles can be drawn by the procedure in the following example:

To draw a circle where the SWR = 3:1, with a 300-ohm line, the circle would cut the 100-ohm point ($\frac{300}{3} = 100$) and

the 900-ohm point ($300 \times 3 = 900$) on the horizontal axis. The center to be used for the compass would be $\frac{900 + 100}{2} = 500$. Setting the com-

pass to a distance equivalent to $\frac{900 - 100}{2} = 400$ units, with 500 as

the center, will complete the job.

The SWR circle is an extremely simple method of visualizing the effect of an antenna-to-line mismatch on the feed-point impedance. It is also an easy, more understandable way of showing that varying the feeder length is a futile way to minimize losses. The SWR (or the loss) remains unchanged. To accomplish a change in SWR (or to eliminate a line loss) for any specific frequency would require a climb up to your "sky-piece."

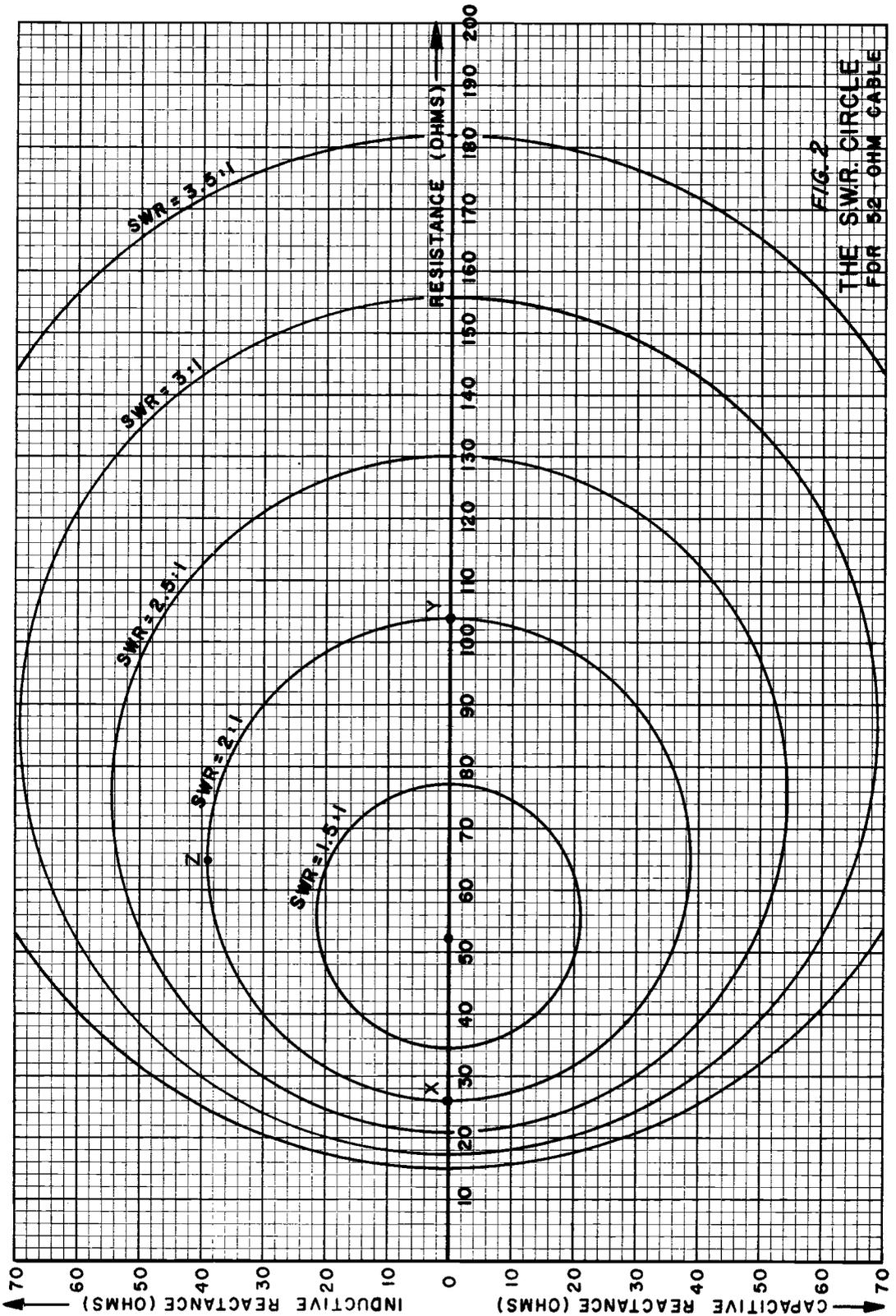


FIG. 2
THE SWR CIRCLE
FOR 52 OHM CABLE



Tmk(s) ®

From your local RCA distributor, headquarters for RCA receiving and power tubes.

RCA HAM TIPS is published by the RCA Tube Division, Harrison, N. J. It is available free of charge from RCA Distributors.

Harvey Slovik, Editor
Robert Leedy,
Technical Editor

FORM 3547 REQUESTED



WHEN MAILING
PLACE POSTAGE HERE

Devices and arrangements shown or described herein may use patents of RCA or others. Information contained herein is furnished without responsibility by RCA for its use and without prejudice to RCA's patent rights.



GONSET COMMUNICATOR
Portable or Fixed 2-Way UHF



MORROW MB 540-A
For Mobile, Portable,
or Fixed Operation



R & W L1000A
Table-Top KW Amplifier



JOHNSON "VALIANT"
For Phone, CW, and SSB

**DESIGNED FOR "100% QSO"
... they use RCA TUBES**

Known by the signals they deliver—and the brand of tubes they use—these remarkable "leading designs" are making amateur-communication history. And their designers know that top-quality equipment requires top-quality tubes in the sockets.

"100% QSO" calls for tubes that can hold up under a wide variety of operating conditions with healthy power in reserve, tubes with electrical uniformity for easy replacement with minimum circuit realignment.

These facts—plus the fact that RCA TUBES are available just about everywhere—are a few of the important reasons why many of the leading designers and manufacturers of amateur radio equipment use RCA TUBES.

73's for '57



RCA TRANSMITTING TUBE MANUAL-114
236 hard-line pages covering 140 types of tubes, including the very code, installation, operation, and maintenance information. RCA Tube Division, Dept. 1000, P.O. Box 1000, Harrison, N. J. 07033

RCA TUBES FOR AMATEURS
RCA Corporation of America • Tube Division • Harrison, N. J.

