

Capacitors in Control Circuits

(Continued)

value. When S_1 and S_2 are subsequently opened, the relay does not drop out immediately but continues to hold through action of capacitor discharge current flowing through the two resistors in series. Dropout occurs at the instant that the discharge current falls below the minimum value required to maintain the holding amperet-turns. This circuit is employed in cases where low pickup requirements permit a low value of relay amperet-turns. A high-resistance, high-turn coil may thus be used, and the capacitance of the control capacitor materially reduced.

The relay shown in Figure 6 has two coils wound upon the same core. One has a large number of turns; the other a small number. The low-turn coil provides the high value of amperet-turns required for picking up the relay armature against strong spring bias or gravity pull. When switch S_1 is opened, the armature is held during the delay interval by discharge current from capacitor C flowing through the high-turn coil and control resistor R .

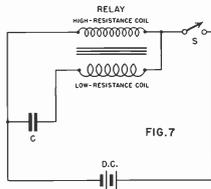



FIG. 7

The circuit of Figure 7 has been designed for rapid pickup and rapid dropout. A special dual relay winding is provided, consisting of high-resistance coil and low-resistance coil, both containing the same number of turns wound upon a common core. The low-resistance coil provides a high-value of amperet-turns for quick pickup. When switch S_1 is closed, current flows through the coil and inductor C , picking up the relay. This charging current is of short duration. When the switch is later opened, capacitor discharge current flows through the two coils in opposite directions, giving rise to bucking fields, and the relay quickly drops out.

REFERENCES

For additional information on the subject of capacitor-type control circuits, the reader is referred to the following:

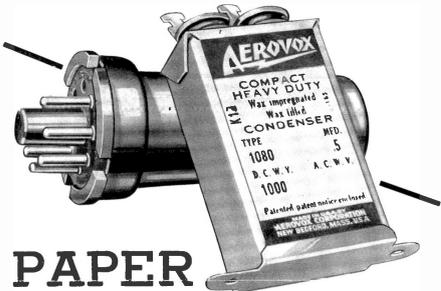- General Electric Review, Vol. 42 No. 11 (November 1939) p. 462
- Electrical Engineering, Vol. 59 No. 2 (February 1940) p. 65 (Transactions)
- Electronics, Vol. 9 No. 8 (August 1936) p. 28; and Vol. 11 No. 2 (February 1938) p. 26



PAPER CONDENSERS

● The Type 80 condenser shown above is intended for heavy-duty service. The wax-impregnated wax-filled section is housed in a sturdy non-rusting metal case. Base mounting lugs. Handy soldering lug terminals. This type is extensively used for replacement in sound equipment, and for initial equipment in quality radio receivers, in electronic assemblies, and in communications equipment generally. Available in .5 to 4.0 mfd., 1000 v. D.C.W.

Non-inductively wound high grade uncased sections neatly shaped and wrapped in black paper with pitch-sealed ends. 8' leads. Popular for condenser block repairs, 200, 400, 600 and 1000 v. D.C.W.



Tubular or cartridge type paper condensers. Non-inductively wound. Thoroughly wax-sealed. Pigtail leads won't work loose. 400, 600, 1000 and 1600 v. D.C.W.



Stamped metal case paper condensers which remain the popular choice for good assemblies, 200 and 400 v. D.C.W. Also the oil-filled "bath tubs".

The Aerovox line includes several other popular types of paper condensers such as listed at the left. Also oil-filled condensers for the most exacting kind of service, particularly in the higher voltages up to 50,000 v. D.C.W.

Ask Our Jobber . . .

Put your condenser requirements up to him and he'll help you solve them under existing conditions. Ask for the new 1942 wartime catalog—or write us direct.

NEW BEDFORD, MASS., U. S. A.
Sales Offices in All Principal Cities

AEROVOX

CORPORATION

In Canada
AEROVOX CANADA LTD.
Montreal
EX-100, 100, 100 St. N. E.
LONDON, ONTARIO

Radio Editors of magazines and newspapers are hereby given permission to reprint in whole or in part, with proper credit to the Aerovox Corporation, the contents of this issue of the Aerovox Research Worker.

The AEROVOX

Research Worker

The Aerovox Research Worker is a monthly house organ of the Aerovox Corporation. It is published to bring to the Radio Experimenter and Engineer authoritative, first-hand information on condensers and resistors for radio work.

VOL. 14, NO. 8

AUGUST 1942

60c per year in U.S.A.
60c per year in Canada

Capacitors in Control Circuits

By the Engineering Department, Aerovox Corporation

THE operation of fixed capacitors in industrial time-delay control circuits is based upon the time constants of resistance-capacitance and resistance-inductance combinations. The phase-shifting property of R-C and L-C circuits is employed to obtain operation of an electrical device or circuit interruption at some instant subsequent to applying the operating voltage. The simple resistance-capacitance circuit is the basis of a number of timing devices in present industrial use.

The time constant of a resistance-capacitance circuit is the time required for a current flowing in the circuit to fall to 1/e or 0.37 of its initial value. Such is the case of capacitor discharge current flowing through fixed resistance, and is given as:

$$(1) \quad \tau = RC \text{ microseconds}$$

R is expressed in ohms and C in microfarads
 $\tau = 2.718$

The time constant of a resistance-inductance circuit is the time required

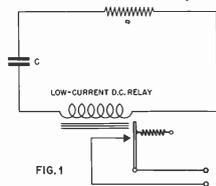


FIG. 1

for a current flowing in the circuit to change to a value of $1 - \frac{1}{e}$ or 0.63 of its original or final value. This is the case of a current forced through a series inductor, and is given as:

$$(2) \quad \tau = \frac{L}{R} \text{ microseconds}$$

R is expressed in ohms and L in microhenries

Equations (1) and (2) may be multiplied by 10⁶ to give the time constant in seconds.

Two rudimentary applications of the time constant of circuits to obtain time-delay operation in a simple manner are illustrated by Figures 1 and 2. In Figure 1 it is assumed that the capacitor C has been fully charged from a direct-current source, that the charging potential has been removed from the circuit and the arrangement shown in the schematic established. The capacitor will then discharge through the circuit containing the resistor and any other series-connected electrical device (such as the relay coil shown) at a rate determined by the C and R values, assuming that the reactance and resistance of the relay coil are negligible.

The progress of current decay in similar circuits of low, medium, and high resistance is shown by the curves of Figure 1-A. It is seen from these curves that a high current may be maintained for short time or a low current for a longer time, depending upon the circuit resistance. The curves are plotted for a given capacitance. From such operation, it is easily understood that the relay contacts in the R-C circuit will be held closed by the capacitor discharge cur-

rent until such instant as the latter falls below the minimum value necessary to maintain closure amperet-turns. From Equation (1) and Figure 1-A, we observe that the interval of closure may be prolonged by increasing the value of C, R, or both.

The circuit of Figure 2 shows a rudimentary arrangement for obtaining a time-delay effect of the opposite kind. Here it is assumed again that the reactance and resistance of the relay coil are negligible and that the useful time lag is supplied by the series inductor L and series resistor R. When the main switch is closed, connecting the direct-current source to the circuit, a current builds up gradually to the level required to close the relay contacts at a rate determined by L/R. Thus, we have Figure 1 a relay which picks up immediately when the main switch is closed and continues to hold for a predetermined time interval after the

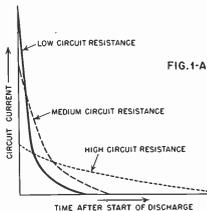


FIG. 1-A

AEROVOX PRODUCTS ARE BUILT BETTER

Printed in U. S. A.

Copyright 1942 by Aerovox Corporation

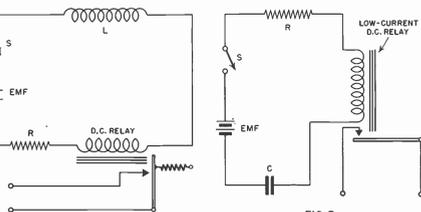


FIG. 2

FIG. 3

(3)

switch is later opened. In Figure 2, on the other hand, we have a relay which picks up at some preset instant after the main switch is closed and drops out immediately upon opening the switch.

Figure 3 shows a simple capacitor circuit in which relay pickup occurs at the instant the main switch is closed and drops out at some later instant determined by the circuit time constant. Operation is based upon charging current which diminishes to the dropout value according to the RC rate. The charging current flowing through the circuit into the capacitor C is equal at any instant to:

$$I = \frac{E}{R} \epsilon^{-\frac{t}{RC}}$$

- I is the instantaneous charging current (amperes)
- E is the inductor potential (volts)
- R is the circuit resistance (ohms)
- t is the time interval measured from the instant of circuit closing (seconds)
- $\epsilon = 2.718$
- C is the capacitance of control capacitor (farads).

The circuits of Figures 1 and 3 are useful for obtaining a delay in dropout, while those of the type illustrated in Figure 2 are employed for delayed pickup. The relay contacts in the capacitive circuits are shown normally open, but reverse performance might be obtained by arranging the contacts in the normally-closed condition. In practical industrial timing circuits where a succession of operations are to be performed at various instants, special relay construction is employed in which several armatures are arranged on a single magnetic structure to be dropped out individually at preset instants.

In any of the simple circuits discussed thus far the size of the relay coil must be such that the required ampere-turns for efficient operation will be obtained with the current value available at the desired instant of operation. Likewise, C in Figure 1 must be large enough to deliver the required discharge current over the selected interval of operation.

In practice, both the resistance and reactance of the relay coil must be taken into account in the design of the circuit. Simple circuits of the capacitive type, such as Figures 1 and 3, would demand low-current d.c. relays for direct application.

REQUIREMENTS FOR CONTROL CAPACITORS

For most industrial timing-circuit applications, large capacitance will be required in order that the maximum amount of energy (expressed in watt-seconds for a given charging voltage) may be stored. The present availability of very high capacitance electrolytic units enables the design of

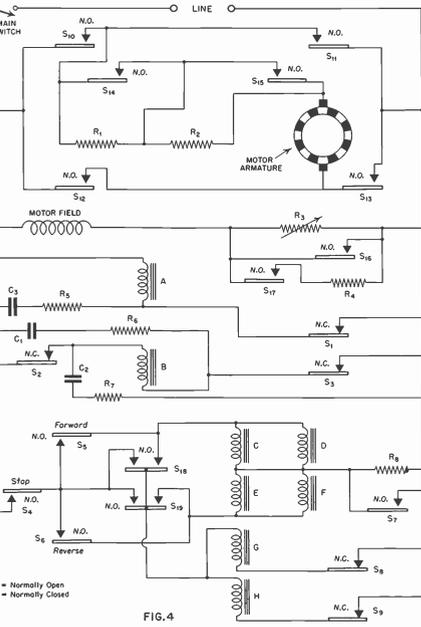


FIG. 4

N.O. = Normally Open
N.C. = Normally Closed



capacitor-control circuits of high energy storage capability affording long time-delay intervals. The actual length of the delay interval may, of course, be governed by the control-circuit series resistance and does not depend largely upon the magnitude of charging voltage. The electrolytic capacitor is not applicable, however, to circuits in which zero current level must be reached, due to the normal leakage of these units. For these circuits, there are available oil capacitors of remarkably high capacitance.

CAPACITOR-CONTROL IN MOTOR ACCELERATION

One of the most important present uses of capacitor control is in the provision of successively-timed operations preceding or following interruption of the operating voltage. Motor acceleration is one such application. In the capacitor-controlled motor-accelerator, successive values of starting resistance are cut out of the circuit automatically after the main power switch has been closed, this operation being performed entirely by capacitor-control circuits. An interesting circuit for a motor controller of this type has been described by Stansbury and Jochem'. Employed in this circuit (see Figure 4) are relays which pick up and drop out at preset times by means of capacitor control, and relays which drop various of their armatures at preset intervals.

The latter type relay is constructed by providing several separate armatures and sets of contacts for a single magnetic structure. The control mechanism (aside from the R-C control) which determines the instant at which these armatures are dropped out is the reluctance of the independent magnetic circuits—the drooping ampere-turns are adjusted by setting the magnetic gaps of the independent armatures when in the closed position.

Capacitor Relay Timing in Industrial Control. Carroll Stansbury & Theo. B. Jochem. *Electrical Engineering*, Feb. 1949 p. 65 (Trans.)

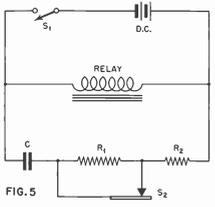


FIG. 5

This is a simple and effective means of adjustment and its direct effect upon the time constant may be understood from examination of the equation:

$$(4) \quad t = CR \log_e \frac{n i_0}{n i}$$

- C is the capacitance of control capacitor (farads)
- R is the resistor value (ohms)
- i_0 is the initial transient current (amperes)
- i is the transient current (amperes)
- t is the time constant (seconds)
- n is the number of relay-coil turns.

The motor controller of Figure 4 is arranged to start up a motor automatically and bring it up to its various safe speeds either in the forward or reverse direction. The arrangement is such that the starting resistors R₁ and R₂ are in series in the starting condition and are automatically cut out successively as the motor gains speed. These operations are performed at the proper safe time intervals.

The capacitor-timed relay A is arranged to start up a motor automatically and bring it up to its various safe speeds either in the forward or reverse direction. The arrangement is such that the starting resistors R₁ and R₂ are in series in the starting condition and are automatically cut out successively as the motor gains speed. These operations are performed at the proper safe time intervals. The capacitor-timed relay A is arranged to start up a motor automatically and bring it up to its various safe speeds either in the forward or reverse direction. The arrangement is such that the starting resistors R₁ and R₂ are in series in the starting condition and are automatically cut out successively as the motor gains speed. These operations are performed at the proper safe time intervals.

Operation of the controller circuit is explained briefly as follows: When the main switch is closed, relay B picks up and its contacts S₁ and S₂ are opened, while its contact S₃ is closed. C₁, C₂, and C₃ are accordingly charged through R₁, R₂, and R₃, respectively. Relay A operates simultaneously, closing its contacts S₄ and S₅. The motor armature is connected to the line through the entire starting resistance R₁ plus R₂ when the forward pushbutton S₆ is closed since contacts S₄ and S₅ are closed at this time by C and C₁. However, as S₇ closes, it opens auxiliary contact S₁, disconnecting relay B through which C₁ now discharges, starting the timing process.

Contacts G and H then short-circuit the starting resistors successively through the contacts S₈ and S₉, the contactor coils having been connected

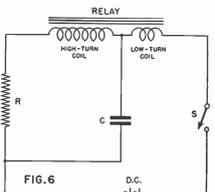


FIG. 6

to the line through the timing action which closed S₄ and S₅ successively. Contact S₆ has opened during this course of events, and not until it has again closed will contactors C and D be picked up. The armature carrying S₁ is mounted on the same magnetic structure as S₄ and S₅, however S₁ has the larger magnetic gap so that S₄ and S₅ are opened before contactors C and D close. This arrangement prevents contactors S₄ and S₅ from closing simultaneously with C and D and thereby connecting the motor armature directly across the line.

An auxiliary contact S₇ is operated by S₆ when the latter closes, disconnecting relay A and allowing C₁ to discharge through A. S₄ and S₅ then open successively at predetermined instants, due to the timing in relay A, inserting R₂ in series with the motor field. When the motor is operating forward, C₁ discharges through the coil of relay B for timing. When the motor operates reverse, the opening of S₆ permits C₁ to discharge through the same relay. Thus one capacitor controls timing, with the motor running in one direction, while the other capacitor (in reserve for timing when direction of rotation is reversed) is being charged to the full line voltage.

ADDITIONAL SPECIAL-PURPOSE CIRCUITS

Figures 5, 6, and 7 show capacitor-control circuits suggested by F. H. Winters' for various particular functions. In Figure 5; when the main switch S₁ is closed, current from the source DC picks up the relay. The auxiliary contacts S₂ are closed at the same time by ganging with S₁, short-circuiting the high resistance R₁ to permit control capacitor C to charge rapidly through the low resistance R₂. The latter has been inserted in the circuit specifically to limit the current through the S₁ contacts to a safe

Some New Uses of Capacitors in Control Circuits. F. H. Winters. *General Electric Review*, Nov. 1939 p. 462.