

75 cents


hcr

focus
on
communications
technology ...

ham radio

magazine

FEBRUARY 1973

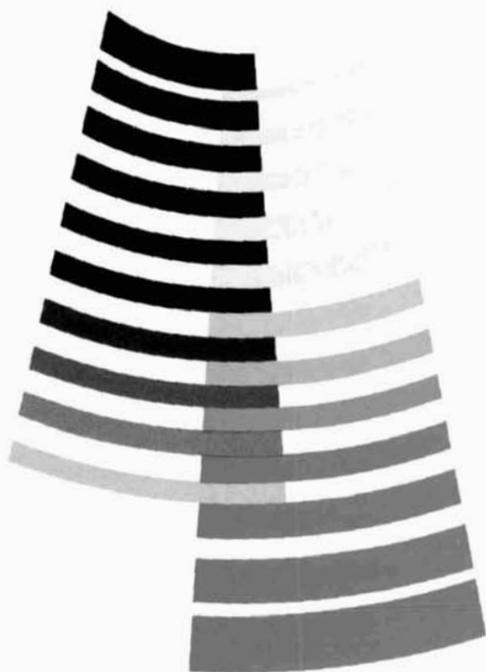

**designing
COMMUNICATIONS
RECEIVERS
for good
strong-signal
performance**

this month

- rf speech clipper 18
- vhf fm receiver scanner 22
- solid-state noise blanker 38
- tunable audio oscillator 50

Savoy

HIGH ACCURACY CRYSTALS
FOR OVER 30 YEARS




\$3.75

Postpaid in U.S.A.

TYPE 900A

TYPE 901

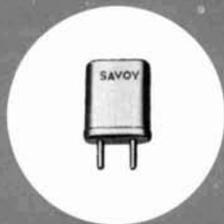

Either type for amateur VHF in Regency, Swan, Standard, Drake, Varitronics, Tempo, Yaesu, Galaxy, Trio, Sonar, Clegg, SBE, transmitter or receiver. GE, Motorola, RCA or Oven use \$4.95. Quotes on others.

Specify crystal type, frequency, make of equipment and whether transmit or receive when ordering.




BASSETT VACUUM TRAP ANTENNA SYSTEM

Complete packaged multi-band antenna systems employing the famous Bassett Sealed Resonators and Balun from which air has been removed and replaced with pure helium at one atmosphere. Operating bands are indicated by model designation.

MODEL DGA-4075 \$59.50
MODEL DGA-204075 . . \$79.50
MODEL DGA-2040 \$59.50
MODEL DGA-152040 . . \$79.50

BASSETT VACUUM BALUN

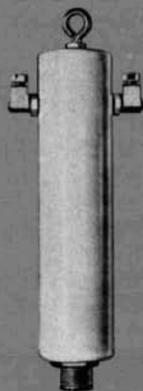

The famous sealed helium filled Balun . . . employed with the DGA Series Antenna Systems. Solderless center insulator and easily handles more than full legal power while reducing unwanted coax radiation. Equipped with a special SO-239 type coax connector and available either 1:1 or 4:1.

MODEL DGA-2000-B . . . \$12.95
Postpaid in U.S.A.

CONTACT YOUR DISTRIBUTOR OR WRITE FOR DATA


Savoy Electronics, Inc.

P.O. Box 7127 - Fort Lauderdale, Florida - 33301

Tel: 305-566-8416 or 305-947-1191



STEP UP TO **ALPHA 77**

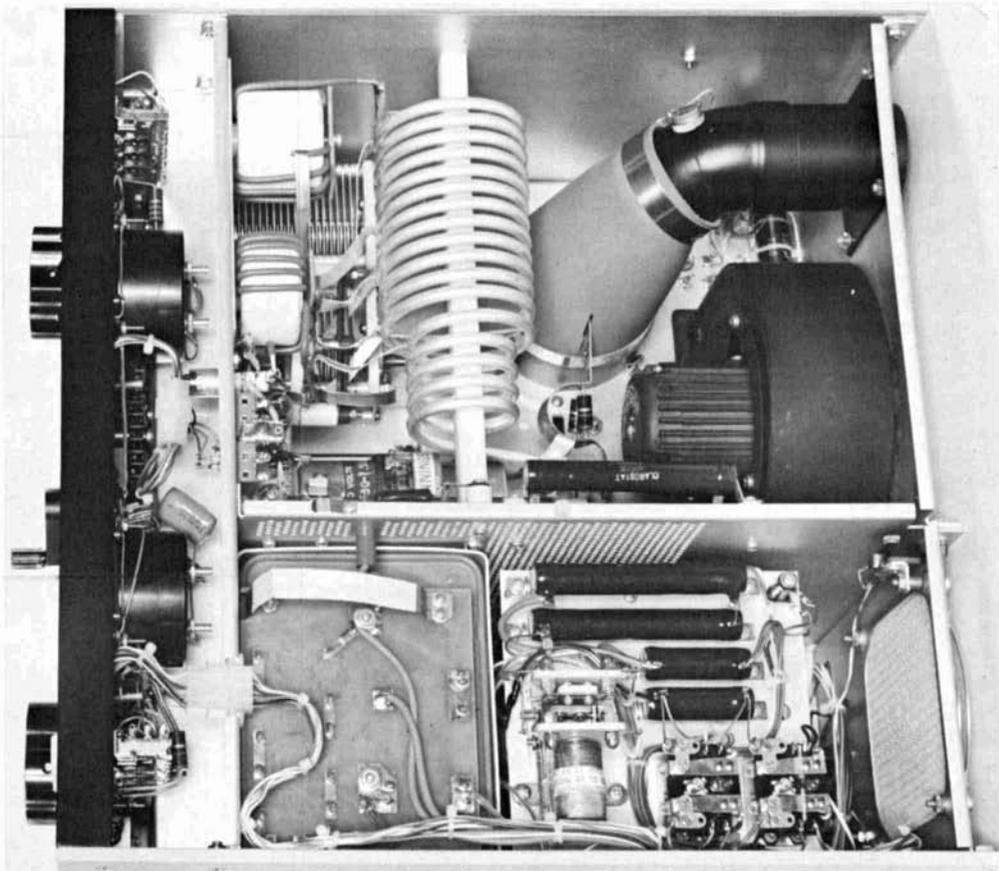

... THE ULTIMATE LINEAR

- **MAXIMUM LEGAL POWER** — IN ANY MODE — CONTINUOUSLY!
- **COOL, WHISPER-QUIET, BATTLESHIP-RUGGED.**
- **UNPRECEDENTED TWO-YEAR WARRANTY** on major power components — the transformer and filter capacitor! And a full year warranty on the entire amplifier!
- **NEW FACTORY-DIRECT PRICE . . . JUST \$1495 COMPLETE!**

Step up to **THE ULTIMATE!** Trade in your old gear on the incomparable **ALPHA 77**, now available at **PAYNE RADIO**, Springfield, Tennessee and a few other selected dealers, as well as factory-direct. Write or phone today for your copy of the fully-illustrated **ALPHA 77** brochure.



EHRHORN TECHNOLOGICAL OPERATIONS, INC.
BROOKSVILLE, FLORIDA 33512
(904) 596-3711



RAYTHEON

**MODEL - 1230
RECEIVER**

THE NEW STANDARD OF RECEIVER EXCELLENCE

- **SYNTHESIZER STABILITY** (Better than 1 Hz/day at any freq.)
- **CONTINUOUS TUNING** (2-30 MHz)
- **TRACKED PRE-SELECTION ON ALL BANDS**
- **DIRECT DIGITAL READOUT TO NEAREST Hz**
- **PHASE LOCKED DETECTORS FOR AM, FM, FSK**
- **INDEPENDENT SIDEBAND AVAILABLE**
- **ALL SOLID STATE including DISPLAYS**

\$3930

FOR COMPLETE DATA WRITE TO:

RAYTHEON COMPANY

MARKETING DEPT. (SP)
6380 HOLLISTER AVENUE
GOLETA, CALIFORNIA 93017
AREA CODE 805 967-5511

February, 1973
volume 6, number 2

staff

James R. Fisk, W1DTY
editor

Patricia A. Hawes, WN1QJN
editorial assistant

Nicholas D. Skeer, K1PSR
vhf editor
J. Jay O'Brien, W6GDO
fm editor

Alfred Wilson, W6NIF
James A. Harvey, WA6IAK
associate editors

Wayne T. Pierce, K3SUK
cover

T.H. Tenney, Jr. W1NLB
publisher

Hilda M. Wetherbee
advertising manager

offices

Greenville, New Hampshire 03048
Telephone: 603-878-1441

ham radio magazine is
published monthly by
Communications Technology, Inc
Greenville, New Hampshire 03048

Subscription rates, world wide
one year, \$7.00, three years, \$14.00
Second class postage
paid at Greenville, N.H. 03048
and at additional mailing offices

Foreign subscription agents
United Kingdom
Radio Society of Great Britain
35 Doughty Street, London WC1, England

All European countries
Eskil Persson, SM5CJP, Frotunagrand 1
19400 Upplands Vasby, Sweden

African continent
Holland Radio, 143 Greenway
Greenside, Johannesburg
Republic of South Africa

Copyright 1973 by
Communications Technology, Inc
Title registered at U.S. Patent Office
Printed by Wellesley Press, Inc
Framingham, Massachusetts 01701, USA

ham radio is available to the blind
and physically handicapped on magnetic tape
from Science for the Blind
221 Rock Hill Road, Bala Cynwyd
Pennsylvania 19440
Microfilm copies of current
and back issues are available
from University Microfilms
Ann Arbor, Michigan 48103

Postmaster: Please send form 3579 to
ham radio magazine, Greenville
New Hampshire 03048



contents

6 strong-signal communications receiver design
Raymond Moore, K1DBR

18 rf speech clipper for ssb
Charles G. Bird, K6HTM

22 vhf fm receiver scanner
Robert L. Reifsteck, K2LZG

26 using Plessey SL600 series integrated circuits
James M. Bryant, G8FNT

38 solid-state noise blanker
John R. Megirian, K4DHC

42 RTTY receiver-demodulator for net operation
Lawrence Walrod, VE7BRK

46 HW-100 grid-current monitor
Robert R. Snow, K4MFR

50 tunable audio oscillator
Henry D. Olson, W6GXN

4 a second look **56 ham notebook**
94 advertisers index **58 new products**
83 flea market **94 reader service**



a second look

by Jim
fisk

A little over twenty-five years ago, on December 23rd, 1947, to be exact, a group of scientists at Bell Laboratories built a one-stage amplifier circuit around the world's first transistor, giving birth to a whole new era of electronics and communications. But the beginning of the story was not in 1947, but long before. There had been hints of amplification in semiconductors as early as the 1920s but few experimenters could duplicate the results. Nobody realized the effect of semiconductor impurities nor understood the action of semiconductor materials.

In 1930 Dr. Julius Lilienfeld, a German physicist, actually patented a semiconductor amplifier that could be compared to today's mosfet. Although Dr. Lilienfeld's amplifier worked, it could not be duplicated by other workers, and it slowly slipped into oblivion.

In 1939, Dr. William Shockley made an entry into his lab notebook at Bell Labs, "It has today occurred to me that an amplifier using semiconductors rather than vacuum is in principle possible." It was nearly eight years before this concept would bear fruit. A large part of this period was spent in learning more about that old bugaboo, semiconductor impurities.

The 1N21 crystal detector, developed during World War II and the workhorse of wartime radar receivers, provided some of the impetus. After the war a solid-state research team at Bell Labs, co-headed by Dr. Shockley, started experimenting with germanium and silicon, two semiconductors that were easy to work with. As one of the group says today, "We felt that the area was so fertile that you could devise an experiment in the morning, go out in the lab and try it in the afternoon, and then write a paper about it that evening."

The first device the group attempted to build was what is now called an insulated-gate fet. The device didn't work. The group scrambled around, dug

into the literature and spent long hours discussing the alternatives.

Dr. Walter Brattain tried an experiment where he covered a metal point with a thin layer of wax and pushed it down on the surface of a piece of silicon. He then surrounded the point with a drop of water and made contact to it. The water was insulated from the point by the wax layer. He found that voltages applied between the water and the silicon would change the current flowing from the silicon to the point. Power amplification had been achieved! Unfortunately, the drop of water would evaporate almost as soon as things were working well.

This led to experiments with other electrolytes that didn't evaporate so readily. Then, they discovered a thin oxide layer on the surface of the semiconductor under the electrolyte and decided to use a spot of gold as a field electrode to eliminate the electrolyte.

When this was tried, an electrical discharge between the point and the gold spoiled a spot in the middle — when they had washed off the electrolyte they had inadvertently washed off the oxide film, which was soluble in water. However, by placing the point around the edge of the gold spot they observed a new effect — when a small positive voltage was applied to the gold, holes flowed in the surface of the semiconductor, greatly increasing the flow of current. Four days later two gold contacts less than two-thousandths of an inch apart were made to the same piece of germanium and the first transistor was born.

Nine years later, in 1956, the three inventors, Dr. William Shockley, Dr. John Bardeen and Dr. Walter Brattain were awarded the Nobel prize in physics. Little did they realize that their crude laboratory device would spawn a multi-billion dollar semiconductor industry that today affects all our lives.

Jim Fisk, W1DTY
editor



TOTAL

Get total 146-148 MHz coverage without buying a crystal!

The modified Clegg FM 27B transceiver now covers the entire range of 146-148 MHz . . . and needs NO additional crystals. It's the only 2 meter rig *available now* with built-in total coverage that also offers greater than 25 watts output power, uses 10 IC devices, and has Teflon* wiring throughout. Not a single bi-polar device is in the RF path in transmitter or receiver . . . ensuring greater reliability. Accessory power supply and sub-audible tone on transmit are available too. At home or in your car, the FM 27B gives you the ultimate in total 2 meter performance. See your Clegg Dealer NOW or write or phone us today for detailed data sheet on our 2 meter leader.

Amateur Net \$479.95



Clegg DIVISION

3050 Hempland Road, Lancaster, Pennsylvania 17601

Tel. (717) 299-3671

Telex: 84-8438

CHECK THESE SPECIFICATIONS

GENERAL

POWER REQUIREMENTS: 12 to 14 VDC

Current Consumption at 13.5 VDC:

Receive: 4 amps squelched, 1.2 amps unsquelched.

Transmit: 6 amps max.

DIMENSIONS: 7 $\frac{3}{8}$ " x 3 $\frac{1}{2}$ " x 9 $\frac{1}{4}$ " deep; 4 lbs. net weight.

RECEIVER

TUNING RANGE: 146.00 to 148.00 MHz, continuously tuneable with reset capability of approx. 1 KHz to any frequency in range.

SENSITIVITY: .35 μ v max. for 20 db quieting; .1 μ v for reliable squelch action.

SELECTIVITY: 11 KHz at 3 db; Less than 30 KHz at 70 db. Adjacent (30 KHz spaced) channel rejection more than 70 db.

AUDIO OUTPUT: 2.0 watts (min.) at less than 10% THD into internal or external ohm speaker.

TRANSMITTER

TUNING RANGE AND CONTROLS: Same as RECEIVER.

POWER OUTPUT: 25 watts Min. into 50 ohm load. P/A transistor protected for infinite VSWR.

MODULATION: Internally adjustable up to 10 KHz deviation and up to 12 db peak clipping.

*DuPont trademark

designing communications receivers

for good strong-signal performance

Many modern
amateur receivers
perform poorly
in the presence
of strong signals —
here are some
sound design ideas
for solving
this problem

“Current receivers... perform poorly under exactly those conditions that are most important, when the desired signal is weak and the undesired signal is strong” is the way Squires began an article on receiver front-ends in 1963.¹ Since then, solid-state receivers have become the standard in new design, increasing the difficulty of obtaining adequate signal handling characteristics. Outstanding strong-signal performance is one of the more difficult and expensive characteristics to design into a receiver; the least expensive characteristics are sensitivity and gain. This is why most receivers are “hot” enough to rattle the walls on noise alone.

The price for low noise figures on the high-frequency bands is paid, not in dollars, but in poor to mediocre strong-signal performance. Top professional receivers in the \$5000 to \$10000 price range are often designed for noise figures of 10 to 12 dB, the excess noise-figure performance being traded for signal handling ability.

What are the symptoms of poor strong-signal performance? Under actual on-the-air conditions a receiver which cannot handle strong signals can have its performance so deteriorated that its static sensitivity and selectivity figures are meaningless. The receiver may go completely silent in the presence of a strong, unwanted station, or its gain and sensitivity may be so reduced that you can not copy the weak, desired station.

The amateur bands may appear to

Ray Moore, 116 Walnut Street, Walpole, Massachusetts 02081

be full of weak commercial stations which are really operating outside the bands — heterodynes, birdies and broadcast stations appear. Strong ssb stations produce less obvious effects which make the bands seem noisy and full of splatter. All these conditions are produced by deficiencies *within* the receiver.

There are a number of ways in which strong, undesired signals outside the i-f passband can interfere with reception. Some require only a single undesired signal to be present; others require two or more signals. Single signal effects include adjacent channel interference, image interference, i-f breakthrough, strong-signal spurious responses, desensitization and blocking. Multiple signal effects include cross-modulation and rf intermodulation.

single-signal interference

Adjacent-channel interference is caused by a strong, undesired signal close to, but outside of, the receiver's i-f passband. This is the fault of the main selectivity determining filter. The filter either has a poor shape factor or the ultimate attenuation (stop band) is not deep enough. Some filters, for instance, have skirts that go down to only 50 or 60 dB before they flatten out. One solution to this problem is cascading two or more filters. Care in matching filter center frequencies and proper isolation produce ultimate attenuations of 120 dB or more and shape factors approaching 1:1.

Image frequency interference is a function of rf selectivity and the frequency of the first i-f. Secondary images between the first and second i-f stages of multiple-conversion receivers are also possible. Many current receivers have image rejection ratios as low as 50 dB on at least one band. However, with an i-f in the megahertz range, image ratios of 100 dB or more are possible if economy is not an overriding factor. Up-conversion to an i-f above the receiver tuning range in conjunction with a front-end low-pass filter is also very effective.

I-f breakthrough occurs when a signal

on the frequency of the i-f rides through the front-end and into the i-f by brute force. The i-f rejection ratio of a receiver is a function of its rf selectivity, and runs in the range of 50 to 70 dB for amateur receivers and up to 70 to 100 dB for professional and military receivers.

The problem is much more severe with *variable* first i-f receivers than with *fixed* first i-f receivers because it is difficult to find a 500- to 1000-kHz slice of the spectrum with no strong stations, and further, because simple traps can reduce i-f breakthrough in fixed i-f receivers where band elimination filters are required for variable i-f receivers. Up-conversion with a low-pass filter is one of the most effective solutions to the i-f breakthrough problem.

Strong-signal spurious responses are produced in two ways. First, strong signals can ride through the front end and mix with harmonics of the first oscillator to produce the i-f. Second, a nonlinear rf amplifier or mixer can generate harmonics of a strong signal which beat with the local oscillator. Rf selectivity and filtering of the injection frequencies are the cure for this problem.

The best receivers have strong-signal spurious responses of 100 dB in relation to a 1- μ V desired signal. That is, it takes a 100-mV undesired strong signal to produce a receiver output equivalent to the output produced by a 1- μ V desired signal. A 0.3 mV signal (50 dB relative to 1 μ V) can produce strong signal spurious responses in less expensive receivers.

Desensitization and blocking are different degrees of severity of the same problem. In desensitization a strong signal outside the passband reduces the gain of the receiver which may make it impossible to hear a weak desired signal. In blocking, the gain is reduced to such an extent that the receiver goes silent. Both desensitization and blocking are caused by a signal which rides through and is rectified by the first active device causing a shift in the operating point of the device. If the first device is also connected

to the agc system, the rectified voltage can be fed back through the agc line to affect other stages as well. These problems are most common in the immediate vicinity of transmitters.

Professional class receivers specify desensitization and blocking in terms of the

there a lack of standard conditions and levels makes direct comparisons impossible. The undesired signal required to produce a certain level of cross-mod is specified, but the reference cross-mod level is variously given as -10 dB, -20 dB or -30 dB relative to the desired signal

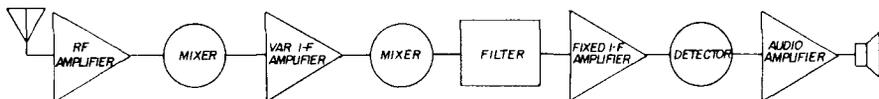


fig. 1. Signal path through a typical modern communications receiver.

unwanted signal level required to cause a 3-dB drop in receiver output when tuned to a 1 mV desired signal. 100 mV is a typical desensitization specification for such a receiver. These characteristics are seldom specified on lower priced receivers but tests have shown that some will completely block at 35 mV or less.

cross-modulation

Cross-modulation is a mixing effect that is produced when a desired signal and a strong, undesired signal are applied simultaneously to a device with third-order curvature of its input-vs-output transfer characteristic. The first and second mixers are the stages most likely to produce cross-modulation but very strong signals can also produce it in the rf amplifier. The result of cross-mod is that the modulation of the undesired signal is superimposed on the desired signal and cannot be removed by subsequent processing. Cross-mod is aggravated in the first stage of a receiver by the popular gain control methods which change the operating conditions of the device (see fig. 5). Any attenuation ahead of the offending stage is beneficial even if the desired signal is also attenuated, because 1 dB of attenuation reduces cross-modulation by 2 dB. Of course, attenuation of the undesired signal by rf selectivity without affecting the desired signal is preferred, but this is not always possible if the undesired signal is close to the passband.

Cross-modulation is seldom specified except in professional receivers and even

output, as 3% cross-mod, or as "negligible". More important, the spacing of the undesired signal from the desired signal may be anywhere from 10 to 100 kHz or may be expressed as a percentage up to 10%. Cross-mod performance is improved by use of greater rf selectivity and more linear active devices. A given active device can often be made more linear by optimizing its operating conditions.

intermodulation

Rf intermodulation (IM) is, like cross-modulation, the result of third-order curvature of a device. If there are two strong undesired signals, f_1 and f_2 , they will produce two third-order products, one at $f_1 + (f_1 - f_2)$ and the other at $f_2 - (f_1 - f_2)$. Fifth-order curvature can also produce much weaker IM products spaced

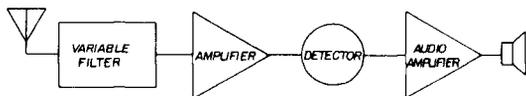


fig. 2. Ideal receiver signal path for handling strong signals.

$2(f_1 - f_2)$ from the two offending signals. As an example, two strong signals, one at 3450 kHz and the other at 3490 kHz, can produce two IM products in the 80-meter band, a third-order product at 3530 kHz and a fifth order product at 3570 kHz. Two other IM products fall outside the amateur band at 3410 and 3370 kHz. Perhaps this is why the 80 meter band on

your receiver sounds full of RTTY and other commercial stations.

There are two ways in which IM is specified in professional receivers. One is to tell how far the IM product is below the level of the two signals which cause it. Third-order IM, for example, can be

1920s which had all their tuned circuits lumped between the antenna and the first rf stage. The filter in the ideal receiver, however, must be adequate to provide adjacent channel selectivity to modern standards — a shape factor of 2:1, 2.5 kHz bandwidth, ultimate rejection greater

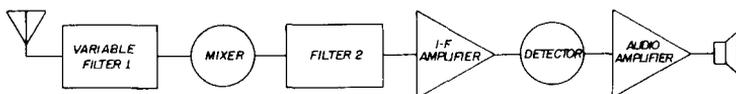


fig. 3. Compromise receiver signal path for handling strong signals.

specified as, "at least 60 dB below two 10-mV undesired signals." IM can also be specified as the undesired signal level to produce an IM product equivalent to a 1- μ V desired signal. The better professional and military receivers require from +70 dB to +100 dB relative to 1 μ V to produce third-order IM equivalent to a 1- μ V desired signal. Improvement in IM performance is accomplished by the same means as for cross-modulation.

receiver signal path

The typical modern communications receiver (fig. 1) has a signal path which is

than 100 dB, insertion loss 1 or 2 dB. Such a filter would stop the strong undesired signals before they got into the receiver, unlike the two or three tuned circuits in most receivers which allow signals 50 or 100 kHz off frequency to ride through with little attenuation. High-frequency crystal-lattice filters which meet these requirements for single frequencies are available, and receivers such as this, covering one or several fixed frequencies, are in use.

A practical, tunable receiver which can approach the ideal in performance is shown in fig. 3. The objective is to

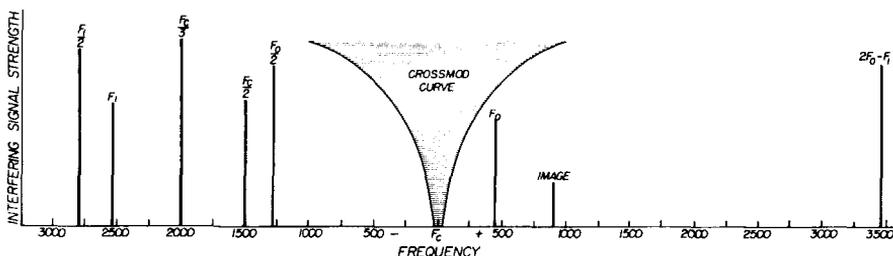


fig. 4. Plot of strong-signal responses in a typical communications receiver. Frequency f_c is the center frequency to which the receiver is tuned (3000 kHz), f_o is the oscillator frequency (3455 kHz), and f_i is the intermediate frequency (455 kHz).

not ideal from the strong-signal standpoint. The problem with this design is that four stages are exposed to strong undesired signals before the passband-determining filter can reduce them to harmless proportions.

The ideal receiver configuration for handling strong signals (fig. 2) is a throw-back to some of the TRF receivers of the

provide maximum adjacent-channel selectivity as close as possible to the antenna. The mixer must be low noise and as linear as possible; FL1 should consist of two to four tuned circuits, depending upon the noise figure of the mixer and the target noise figure for the entire receiver. The i-f must be high enough so FL1 can adequately suppress images and low enough

to be practical, say, in the range of 1.5 to 50 MHz.

Higher intermediate frequencies remove the i-f from the receiver tuning range and permit the use of up-conversion in conjunction with a low-pass filter ahead of FL1. The disadvantage of the higher frequencies is that filters, while available, may be expensive and difficult

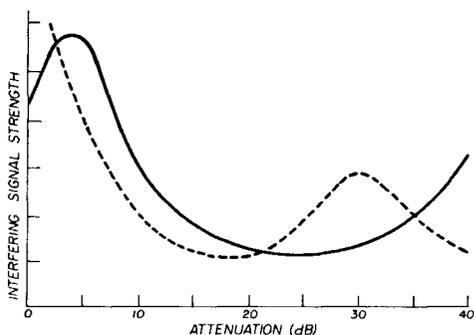


fig. 5. Interfering signal level required to produce 1% cross-modulation in two different active devices.

to locate. The stability and constant tuning rate usually associated with the variable first i-f, multiple-conversion receiver can be achieved with this configuration by deriving the injection frequency for the first mixer through the pre-mixer technique. In this case, complexity has been removed from the signal path and added to the frequency determining circuits where it can do no harm to the signal.

receiver design trends

The receiver design trends of the last twenty years have, almost without exception, been in the direction of poorer strong-signal performance. One of the innovations of that period is all solid-state receiver design. In general, semi-conductors do not handle strong signals as well as vacuum tubes, and the use of semi-conductors in stages ahead of the adjacent-channel selectivity filters degrades strong-signal performance.

Multiple conversion, another design innovation, results in two mixers and

three to five total stages before there is appreciable selectivity to protect the amplifiers and mixers from strong undesired signals. Broadband and variable i-f stages are susceptible to i-f breakthrough.

Furthermore, the newer low-noise devices, both tubes and semi-conductors, tend to be less linear than the older vacuum tubes. The low-impedance (50-ohm), tightly-coupled primaries on modern antenna coils compound the strong signal problem because they degrade the Q of the tuned circuit. They also present higher signal levels to the active device than did the old medium-impedance (200- to 500-ohm) primaries.

evaluating strong-signal performance

The best method of evaluating the strong signal performance of the receiver is that used for military and professional receivers. Two signal generators are used to plot cross-mod and spurious responses as shown in fig. 4. In plotting the cross-mod curve one generator feeds in a desired signal (10 to 100 μ V) at the frequency to which the receiver is tuned; the second generator is swept out from the desired signal frequency, first in one direction and then the other, representing a strong undesired signal. The amplitude of the undesired signal necessary to produce the reference cross-mod level is recorded at enough points to produce the curve shown in fig. 4.

The first generator is removed from the circuit and the second generator is swept through the spectrum again. Any

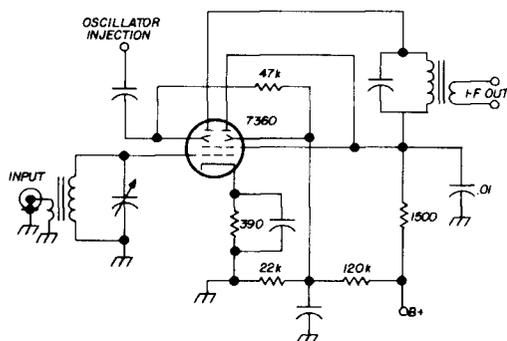


fig. 6. Unbalanced 7360 beam-deflection mixer circuit.

discrete responses such as image and i-f breakthrough are recorded. The undesired signal strength required to produce a response equivalent to a 1- μ V desired signal is recorded for the discrete responses.

Since there are an infinite number of signal combinations which can produce IM, you must be content with spot

signals: Reduce the strength of the undesired signals or, in the case of cross-mod and IM, improve the linearity of mixer and amplifier devices in the stages ahead of the adjacent-channel selectivity filter.

Reducing the strength of the undesired signals is the method used in the receiver configuration in **fig. 2**. If the undesired

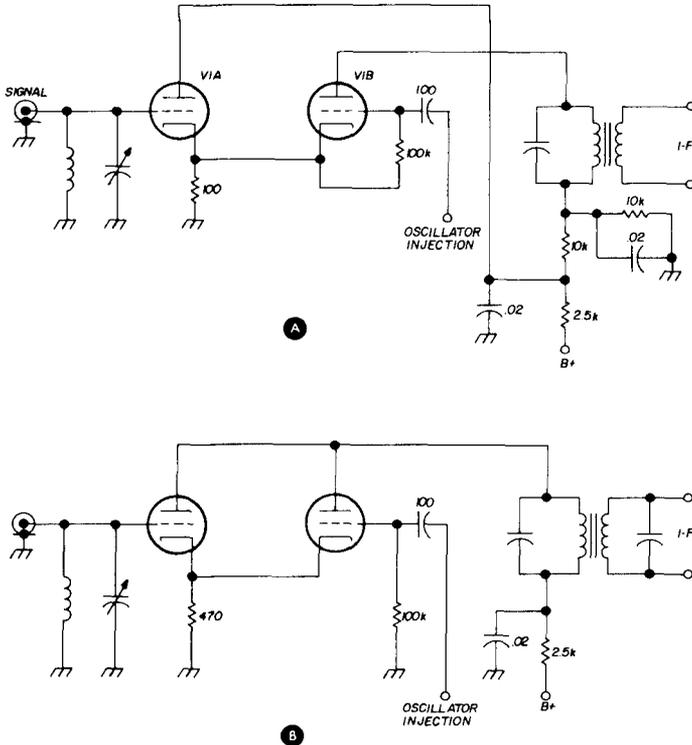


fig. 7. Two dual-triode mixer circuits. The circuit in (B) is not as sensitive as the circuit in (A), but (B) will handle larger signals. These circuits are suitable for vacuum tubes such as the 12AU7, 12AT7 or 6DJ8.

checks in evaluating this characteristic. Set one generator at f_c plus 30 kHz and the other at f_c plus 60 kHz. The amplitude of both generators must be the same. Increase the amplitude of the two generators until a response appears at f_c equivalent to that produced by a 1- μ V desired signal. The level of either generator is then the IM response level and may be expressed in dB relative to 1 μ V.

There are only two ways to improve the ability of a receiver to handle strong

signals can't get into the receiver, they can't do any damage. In most receivers you have to get along with something less than ideal rf selectivity, but strive for the maximum practical selectivity. Reducing the undesired signal by 1 dB will reduce cross-mod by 2 dB and IM by 3 dB, so even a small amount of additional selectivity can make a decided improvement.

If ideal rf selectivity isn't available then the linearity of the amplifier and

mixer devices becomes important. Not only should the most linear devices and circuits be selected, they must be optimized for strong-signal performance. Each active device has an optimum point at which it is least susceptible to cross-mod and IM. This is illustrated in **fig. 5**

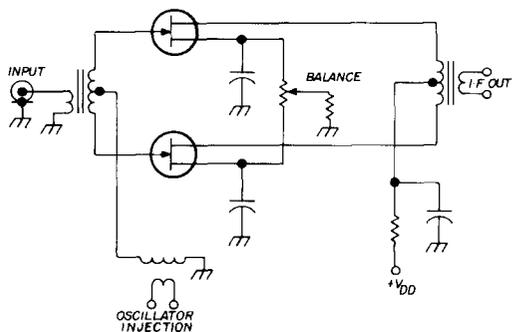


fig. 8. Balanced mixer circuit using a field-effect transistor.

which shows generalized cross-mod-vs-attenuation curves typical of active devices when attenuation is produced by changes in bias.

Most amateur receivers suppress all strong-signal effects from out-of-passband signals by a minimum of 50 dB. The suppression of military and professional receivers runs from 70 to 100 dB or more. The noise figure of amateur receivers runs from 5 to 8 dB, that of professional receivers is usually around 10 dB. The cost of amateur receivers is \$250 to \$800, professional receivers \$5000 to \$10,000 and up. Obviously, sensitivity is cheap while strong-signal performance is expensive.

It can not be stated too often that good strong-signal performance in modern receivers is the result of painstaking design work. It is not enough to pick out a signal path configuration and the circuit for each stage. Each stage must be experimentally optimized for operating point, voltages and injection levels. If there are two or more circuits under consideration for a given stage, each must be optimized, and then compared.

strong-signal performance

The following paragraphs detail the steps which are necessary in the design of a receiver with superior strong-signal performance.

First of all, determine the maximum acceptable noise figure. Many professional receivers are designed for a noise figure of 10 to 12 dB. If the input device of the receiver has a noise figure of 6 dB the designer then has an excess of 4 to 6 dB to use in providing additional rf selectivity, to keep the gain low ahead of the adjacent channel selectivity filter, and to allow optimum strong-signal biasing of stages.

For amateur work where it is possible to take advantage of the rare occasion when a 5- or 6-dB noise figure is usable the best idea is to have an auxiliary low-noise preselector that can be switched in ahead of the receiver. It is easy to add a preselector to a receiver that has sacrificed noise figure for superb strong-signal characteristics, but it is difficult to improve the strong-signal characteristics of a receiver that has been designed for low noise.

Next, select the signal-path configuration. For general use the arrangement of **fig. 3** is recommended. A low-gain rf amplifier can be added if the mixer does not have the required sensitivity. Note that it is *not* necessary to go to the variable first i-f approach to achieve the vfo type tuning we expect in modern receivers.

mixers

The mixer stage is the key to the design of a superior strong-signal receiver. If the configuration of **fig. 3** is to be used to its fullest, the mixer must provide low noise, high conversion transconductance and exceptional linearity. Fortunately, there are devices and circuits which possess these characteristics to a much greater degree than the mixers found in the average medium-priced receiver.


The problem with many mixers is that the device is biased to an operating point where it is not linear so that the required

second-order (sum and difference) frequencies are generated. However, at that point the device is also likely to be an efficient generator of third- and higher-order products which cause cross-modulation and rf intermodulation. Following are some recommended mixers which have been used in professional or military

Squires' original balanced circuit had a noise figure of 5.5 dB at 29 MHz and handled undesired signals up to 1.5 volts.

Various dual-triode mixer circuits perform well because they are low noise and require little or no gain ahead of them. The 12AU7, 12AT7 and 6DJ8 are some of the tubes which have been used.

fig. 9. Diode balanced mixer has approximately 8-dB noise figure and handles large signals well. Diodes CR1-CR4 are hot-carrier diodes; transformers T1 and T2 are toroidal types.

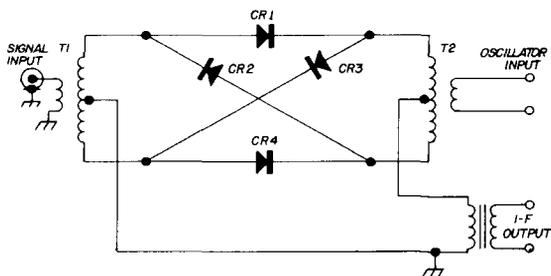

receivers or which are of unusual interest.

Squires developed a mixer circuit with the 7360 beam deflection tube in 1963 which has been used in a number of amateur receivers and at least one commercial receiver.¹ An unbalanced version of the circuit is shown in fig. 6. The tube is set up for linear operation between G1

In the circuit of fig. 7A V1B is a triode mixer with the signal injected at the cathode and the oscillator at the grid. V1A is a cathode follower which provides isolation between the signal and oscillator circuits. The 10k resistors in the plate circuit of V1B form a voltage divider to reduce the plate voltage because V1B

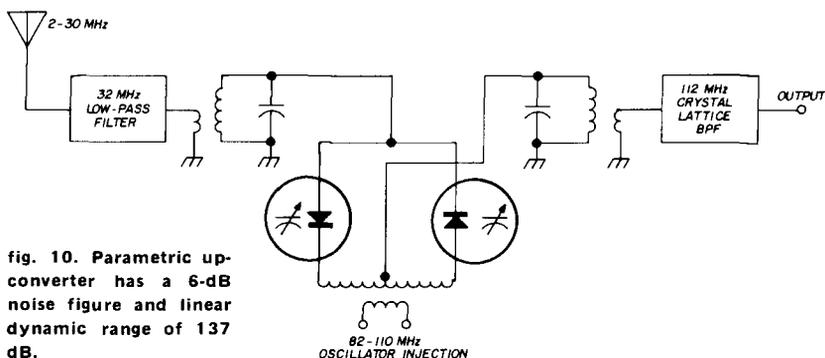



fig. 10. Parametric up-converter has a 6-dB noise figure and linear dynamic range of 137 dB.

and the plates; the signal is switched between the active plate and the grounded plate by the oscillator voltage applied to deflection plate.


Another source indicates that superior performance is obtained from the circuit with a fixed bias (about 1.9 V) and with an oscillator injection of 7.5 volts.²

must have a much lower transconductance than V1A. A somewhat different circuit is shown in fig. 7B. Sensitivity of this circuit is not as good as that of fig. 7A but it will handle larger signals.

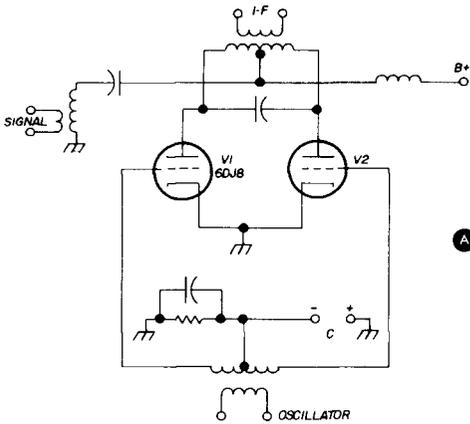The fet balanced mixer (fig. 8) is a good choice for use in the circuit of fig. 3. When used with suitable devices (such



(A)

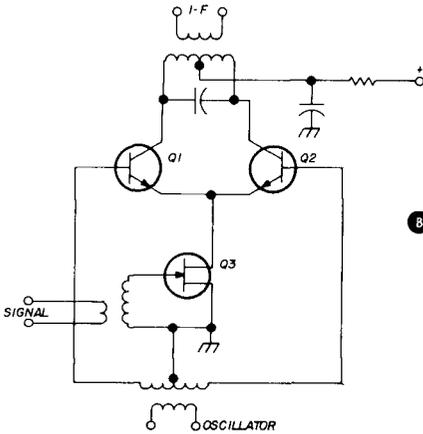

(B)

fig. 11. Vacuum-tube (A) and transistor-type (B) switching mixer circuits.

as the 2N4416) it has a noise figure of 4 to 5 dB and handles large signals fairly well. The noise figure is low enough to allow a rather elaborate rf filter to be placed between it and the antenna.

The diode balanced mixer using hot-carrier diodes in fig. 9 has a noise figure around 8 dB and handles strong signals well. However, it requires high local-oscillator power level and has conversion loss, so it must be preceded by an rf amplifier in order to achieve an acceptable overall noise figure. These are both disadvantages.

A parametric up-converter (fig. 10) is used in the National R1490/GRR17 wide dynamic range military receiver.^{3,4} The specified linearity of the circuit is 137 dB

and the noise figure is 6 dB. All external spurious responses, images, i-f breakthrough, cross-mod, IM, etc., are down more than 100 dB. The 112-MHz filter sharply attenuates all undesired signals more than a few kHz outside the i-f pass-band. Adjacent-channel selectivity is provided in a later stage at 5 MHz.

Up-conversion is advantageous because a simple low-pass filter can be used to increase the rejection of the i-f and image frequencies without the added complexity or loss that additional tuned circuits would bring. The up-conversion technique can be used with any of the other mixer circuits as well.

The 7360 mixer operates as a very linear switching circuit. Attempts have been made to improve the technique and to develop semiconductor equivalents. Perhaps the ultimate performance so far was also by Squires with a dual-triode switching mixer (fig. 11A) in a receiver that handled 3-volt rms signals within 10 kHz of the desired signal, and 25-volt signals 10% removed, without cross-mod.

He used a 6DJ8 tube and the oscillator injection had a square-wave characteristic. The tube was biased as a class-C amplifier and the oscillator had sufficient amplitude to drive the grids positive. The signal was alternately switched to ground through the two tubes by the oscillator injection voltage. A stage of rf amplification was used ahead of the mixer which worked into a 6-kHz wide filter. A somewhat similar scheme using semiconductors (fig. 11B) has been tried, but details on its performance are not available.⁵ The signal is amplified in Q3 and alternately switched to ground through Q1 and Q2 and the output transformer.

rf amplifiers

If an rf amplifier must be used, the rule is to use only enough gain to override the mixer noise, using any excess gain to provide additional rf selectivity either by adding tuned circuits or tapping down on the existing tuned circuits to improve Q. In general, the best rf amplifier devices are vacuum-tube pentodes or triodes in the cascode circuit. Next in order are fets,

and last are bipolar transistors. When receivers *must* be all solid-state, circuit designers have gone to power fets and power bipolars for rf amplifiers in order to improve strong signal performance.^{3,6}

Rf amplifiers must be adjusted experimentally to determine the best bias, plate, screen, drain or collector voltages. If the gain is higher than required it should not be reduced by changing the operating conditions, but by adding rf selectivity through additional tuned circuits, looser coupling or tapping down.

gain control

The method by which the front-end gain is controlled is important to strong-signal performance. As shown in **fig. 5**, if a conventional gain control method is used which changes the operating point of the device, it results in serious degradation in the ability of the device to handle strong signals. The preferred method of manual gain control is a resistive attenuator ahead of the first active device (**fig. 12**).

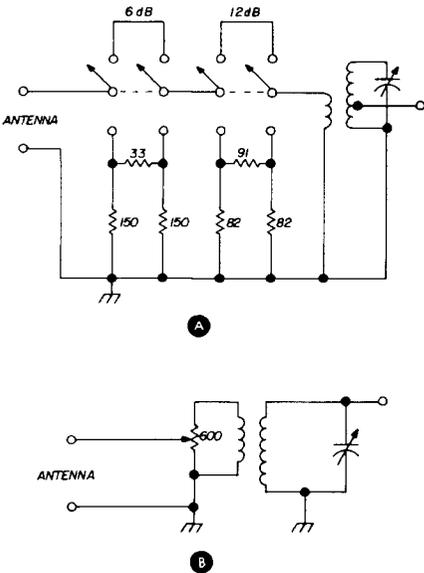


fig. 12. Two types of attenuators which may be used to control signal input to communications receivers. Step attenuator is shown in (A); simple potentiometer attenuator is shown in (B).

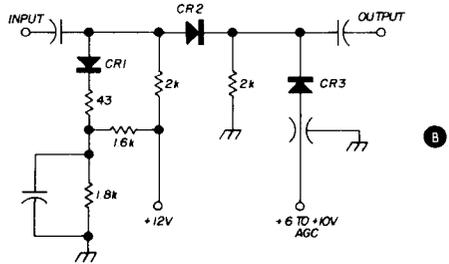
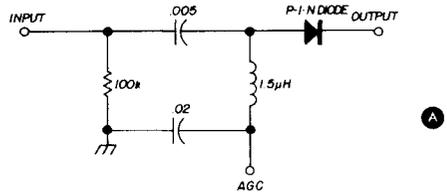


fig. 13. Agc voltage-controlled attenuator circuits using PIN diodes. In the circuit in (B), with +6 volts on the agc line, minimum attenuation is 1 to 2 dB (CR1 and CR3 off, CR2 on). With +10 volts on the agc line, maximum attenuation is 38 dB (CR1 and CR3 on, CR2 off).


voltage-controlled attenuator using PIN diodes ahead of the first stage. A single diode attenuator is shown in **fig. 13A** and a more complex three-diode version with both forward and reverse biased diodes is shown in **fig. 13B**.^{7,8} The designer must be alert to the possibility that the cross-modulation level of the diodes can be less than that of the amplifier or mixer device that they are intended to protect.

selectivity


Rf selectivity is important in the search for the ultimate in strong-signal capability since a perfect rf filter will eliminate all forms of strong signal interference. Crystal-lattice filters are available throughout the high-frequency range and are the near perfect answer for fixed frequency operation.^{9,10} Unfortunately, if you are interested in more than a few fixed channels you must go on to less perfect filters.

Helical resonators are perhaps the next best rf filters (**fig. 14B**). They are not easily adaptable to continuous tuning and

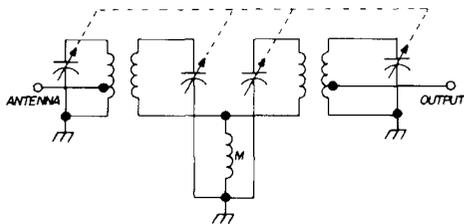they become quite bulky in the high-frequency range, but they can give Qs of 1000 or more which results in bandwidths of 1 kHz per MHz; 14 kHz at 14 MHz for example.^{10,11,12,13}



(A)

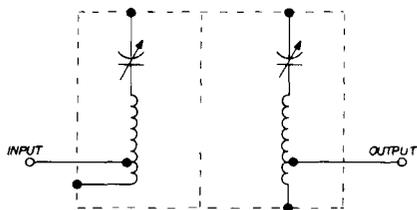

(B)

fig. 14. Four-circuit rf filter (A), and helical resonator (B).

Cascaded tuned circuits are also effective and most modern receivers have at least two such circuits between the antenna and first stage, and some have as many as four. One arrangement is shown in fig. 14A.

references

1. William K. Squires, "A New Approach to Receiver Front-End Design," *QST*, September, 1963.
2. R. K. Jeffers, "Cross-Modulation and Desensitization," Technical Correspondence, *QST*, June, 1964.
3. Pat Hawker, *Amateur Radio Techniques*, Chapter 3, "Receiver Topics," RSGB, 3rd edition, 1970.
4. GRR-17 Advertising Leaflet, National Radio Company, July, 1968.
5. Peter G. Martin, "Plagiarize and Hybridize," *Radio Communications*, March, April, May and June, 1971.
6. "Fet Transistor Key to 140-dB Dynamic Range in Broadband RF Amplifiers," *Communications Designers Digest*, February, 1969.
7. Fred L. Mergner, "PIN Diode and Fets

Improve FM Reception," *Electronics*, August 22, 1966.

8. Sam Weaver, *Controlling Cross-Modulation in TV Tuners*, TI Applications Report, Bulletin CA-113, July, 1969.
9. E. H. Conklin, "Front-End Receiving Filters," *QST*, August, 1967.
10. Paul D. Rockwell, "Station Design for DX," Part III, *QST*, November, 1966.
11. *Reference Data for Radio Engineers*, 5th edition, pp. 22-28, Howard W. Sams, 1968.
12. "The Johnson 504 and 540 Two-Meter Transceivers," *QST*, June, 1971.
13. G. R. Jessop, *VHF-UHF Manual*, RSGB, 1969.

bibliography

1. E. A. Andrade, "Recent Trends in Receiver Front-End Design," *QST*, July, 1962.
2. Joel Balogh, "Cross-Modulation in Receiver RF Pentodes," Technical Correspondence, *QST*, June, 1966.
3. Douglas A. Blakeslee, "An Experimental Receiver for 75-Meter DX Work," *QST*, February, 1972.
4. W. Bruene, et al, "Better Superhets for Sideband Reception," *Electronics*, May 10, 1963.
5. E. H. Conklin, "Strong-Signal Interference," *QST*, December, 1967.
6. E. H. Conklin, "More On Receiver Blocking," *QST*, October, 1968.
7. Jay Gooch, "Cross-Modulation and Transconductance Curves," Technical Correspondence, *QST*, November, 1962.
8. Byron Goodman, "What's Wrong With Our Present Receivers?" *QST*, January, 1957.
9. Siang-Ping Kwok, "A Unified Approach to Optimum FET Mixer Design," *Motorola AN-410*, November, 1967.
10. Henry Magnuski, "Adjacent Channel Rejection Receiver," *Electronics*, January, 1951.
11. E. W. Pappenfus, "A Discussion of Receiver Performance," *QST*, January, 1955.
12. E. W. Pappenfus, et al. *Single Sideband Principles and Circuits*, McGraw-Hill, New York, 1964.
13. William Ress, "It's a Noisy World," Technical Correspondence, *QST*, February, 1970.
14. William A. Rheinfelder, *Design of Low-Noise Transistor Input Circuits*, Hayden Book Company, 1964.
15. William Sabin, "The Solid-State Receiver," *QST*, July, 1970.
16. Wilfred N. Scherer, "Receiver Signal-Handling Capabilities," *CQ*, January and February, 1970.
17. CCIR Rpt 322, *World Distribution and Characteristics of Atmospheric Radio Noise*, 1964.
18. "FET and Schottky-Barrier Diode Allow Designers to Enforce the Square Law," *Communications Designers Digest*, February, 1969.

ham radio

Thousands...

of Drake
TR-3 and TR-4
Sideband
Transceivers
are giving
dependable
service...

many of them
since 1963!



And now **TR-4C**
the Drake
is already surpassing their record!

Now at your dealer's (no price increase)

R. L. DRAKE COMPANY
540 Richard St., Miamisburg, Ohio 45342
Phone: (513) 866-2421 Telex: 288-017





integrated-circuit speech clipper

Rf clipping
with the LM-373
i-f strip IC
provides low distortion
and superior
bandpass shaping

Almost all types of speech processors, and their vices and virtues, have been discussed in these pages. The "audio-rf-audio" low-level processor, as represented by the Comdel CSP-11, has yet to be examined in detail. The method used in the Comdel unit provides speech clipping and filtering analogous to that of rf clippers, but the processed waveform is supplied to the ssb exciter input stage at

audio level. A significant increase in average-to-peak talk power is claimed.¹

operating principles

A block diagram of the Comdel unit appears in fig. 1. A closed-loop system is used, with output at the original audio frequency. Instantaneous amplitude limiting occurs, but does not introduce any harmonic components.¹

The microphone input signal is amplified and mixed with a local-oscillator signal, which is common to the balanced modulator and product detector. Two filter stages are used, which must be capable of passing a signal for ssb service. The filtered signal is clipped, passed through another (identical) filter and applied to a product detector. The resulting audio signal, which is further processed by a low-pass filter, may be applied to an ssb exciter input stage.

The unit to be described consists basically of two ICs, a fet local oscillator, a balanced modulator, and two mechanical filters.*

*A possible source for the filters is Star-Tronics, Box 17121, Portland, Oregon 97217. The MFC-8040 and LM-373 are available from Circuit Specialists, Box 3047, Scottsdale, Arizona 85257. Helpful information on the MFC-8040 and LM-373 will be found in the bibliography at the end of the article. editor.

In fig. 2 a Motorola MFC-8040 is used as a low-noise audio stage, followed by a diode ring modulator and an usb 500-kHz Collins mechanical filter (BW = 2.75 kHz), which drives the agc stage of a National Semiconductor Products LM-373. Output from this stage at pin 9 is clipped and filtered by a second filter and reinserted at pin 4 of the LM-373.

causes the MFC-8040 to overload on loud speech. The input to this stage is therefore shunted with a level pot. A sub-miniature Allen-Bradley unit is available in a blister pack, which can be easily mounted on the circuit board.

The modulator and clipper diodes were on hand and were carefully matched for low forward resistance. There may be

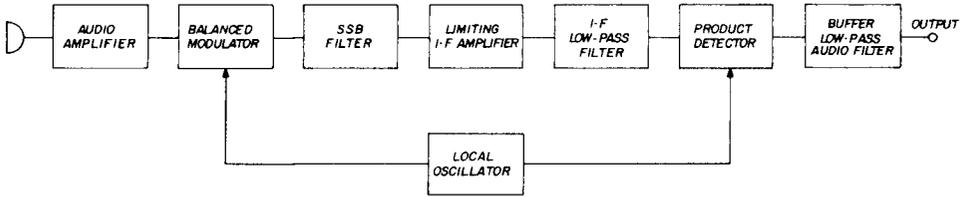


fig. 1. Block diagram of the Comdel CSP-11.

Local-oscillator output at 500 kHz is coupled to the balanced modulator and also to pin 6 of the LM-373; audio is derived from pin 7.

The beauty of the LM-373 is that its upper frequency limit is 15 MHz, thereby permitting the use of any popular filter, whether home-made with low-frequency surplus crystals or with readily available 9-MHz units.

circuit description

The schematic of the IC processor is shown in fig. 3. A microphone such as the Turner 454-C has excessive drive, which

an advantage to using hot-carrier diodes in the clipper circuit.²

No special attention was paid to obtaining carrier suppression other than observing physical symmetry in layout of modulator components, since the carrier is common to both modulator and detector. If it's desired to use the unit as an exciter base by providing the processed signal after the second filter to an external connector, then greater precision in balancing would be required. Capacitor C1 was found to be about 15 pF. The rf output may be monitored at J1 with an oscilloscope or low-frequency receiver.


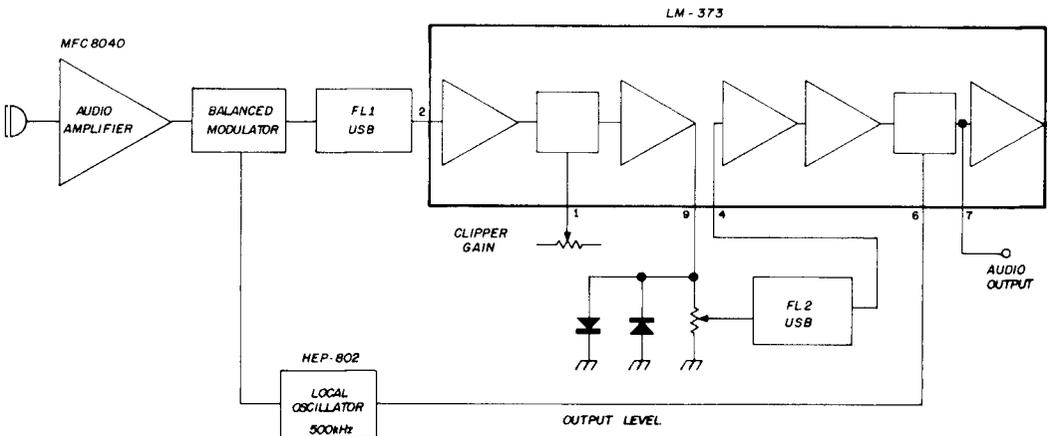


fig. 2. Block diagram of author's speech clipper using two ICs.

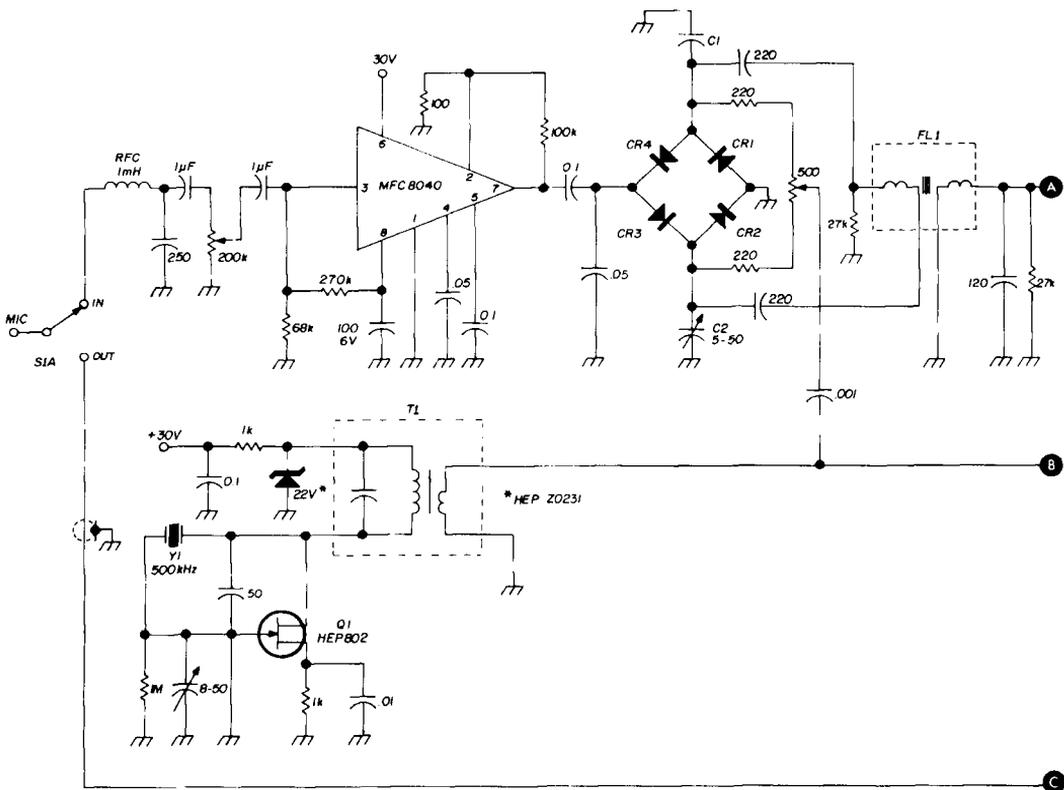

- C1 value chosen to balance with C2
- CR1-CR4 1N75 matched for low forward resistance
- CR5,CR6 1N75, matched for low forward resistance, or hot-carrier diodes

- FL1,FL2 Collins F500Z-12-6618 mechanical filter, 2.75 kHz passband
- T1 455-kHz i-f transformer (Miller 88101). See text
- Y1 500 kHz. Channel 70 FT-241 holder, marked 27.0 MHz (JAN Crystals)

fig. 3. IC speech clipper schematic.

The output-level control should be fully open for best indication of carrier balance.

carrier oscillator

The 500-kHz oscillator uses a 455-kHz subminiature i-f transformer with the slug approximately half way out of the coil form. Oscillation will cease at a point in this direction, so adjustment is fairly critical. About 9 volts of rf can be measured on the primary and about 0.5 volt on the secondary. A 22-volt zener is used to regulate the voltage and protect the HEP-802.

power supply

The point at which the clipper gain control is set is quite dependent on the voltage applied to the LM-373. The load on a 12-volt battery, for example, will


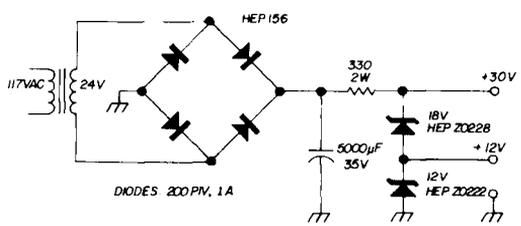


fig. 4. Power supply for the speech clipper.

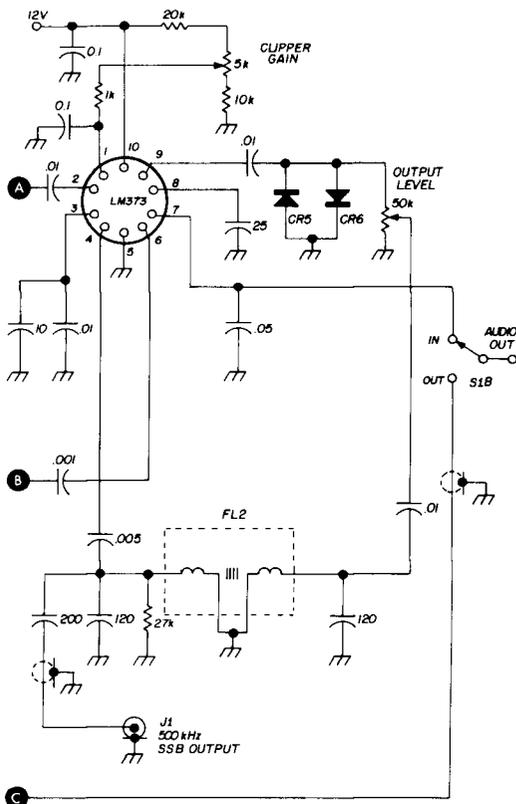

shift the clipping point counter clockwise because of voltage drop. By the same token, a 30-volt battery used for the MFC-8040 and Q1 will be quickly depleted. A suitable power supply is shown in fig. 4.

adjustments

Preliminary adjustments are made to ensure that Q1 oscillates. (This circuit and helpful hints are given by Hank Olson, W6GXN. See reference 3.)

With the output connected to an audio amplifier, the operation of the LM-373 should be checked by listening for ambient noise. If voltage is applied to the MFC-8040 but no speech is heard, you can at least be assured that the LM-373 is working if the transient generated by the make and break voltage to the MFC-8040 is heard through the remainder of the unit. The problem can be isolated at the MFC-8040 or before. An audio oscillator

is useful here. Rf filtering at the processor input is necessary.

The unit described is mounted on a 2-1/2 x 4-1/4-inch pc board and placed inside a 3 x 5 x 7-inch chassis turned on its side, with a hand-fashioned one-piece cowl placed over the sides and top. It is painted to match Drake styling.

conclusion

Performance was all that was hoped for, but as expected, not much better than that of a typical agc-type compressor in terms of additional sock to the signal. Direct comparisons were made with the speech processor described by K6PHT.⁴ Scope displays were perhaps slightly fuller with the IC clipper described here. On-the-air reports seemed to favor the clipper for over-all quality, but did not necessarily indicate its superiority in increased average-to-peak signal strength.

It appears that low-level rf clipping is beneficial mainly with regard to low distortion and superior bandpass shaping. Another possible advantage over the agc-type compressor appears to be greater dynamic range; that is, a lower threshold of background noise for the same amount of increased average-to-peak power. Judicious adjustment of the clipper gain and output-level controls bears out this contention.

references

1. W. Schreurer, K1YZW, "Speech Clipping in Single Sideband Equipment," *ham radio*, February, 1971, page 28.
2. B. Clark, K6JYO, "RF Clipper for the Collins S-Line," *ham radio*, August, 1971, page 19.
3. H. Olson, W6GXN, "Crystal Oscillators: Tube, Transistor and FET," *73 Magazine*, March, 1966, page 14.
4. R. Lee Price, K6PHT, "Simple Speech Processor for SSB," *ham radio*, April, 1970, page 22.

bibliography

1. D.A. Blakeslee, W1KLLK, "A Second Look at Linear Integrated Circuits," *QST*, July, 1971, page 31.
2. E. Noll, W3FQJ, "Circuits and Techniques," *ham radio*, August, 1971, page 52.

ham radio

vhf receiver scanner

Automatic
channel monitor
using
TTL logic

The purpose of a scanner is to allow several vhf receiving channels to be monitored automatically, thus eliminating manual switching between channels. In operation, a slow-running oscillator is turned on and off by the receiver squelch circuit. Flip-flops, controlled by the slow-running oscillator, alternately turn one receiver oscillator on and off, and the process repeats at the next receiver oscillator. When the scanned channel is active, the receiver squelch circuit stops the slow-running oscillator, which conditions the flip-flop so that the station can be monitored.

This article describes a scanner using TTL logic. Some of its features are summarized below.

1. Either positive or negative logic can be used for squelch control.
2. Oscillator switching and channel indication can be accomplished in several different ways.
3. Etched circuit board or breadboard layout can be used.
4. As many as 20 channels can be switched with the addition of compatible devices.

design considerations

It was desired to produce a versatile, inexpensive, simple, and reliable unit. TTL logic provides easy interface with a wide variety of receivers, is reliable, and has recently enjoyed price reductions.

operation

Three two-input NAND gates are used as an oscillator whose frequency is determined by a 1k resistor and 300 μ F capacitor (fig. 1). The fourth NAND gate connects the oscillator to a counter (four internally connected flip-flops). When the oscillator gate is off (LO input), the counter remains at its last count. When the oscillator gate is on (HI input), the counter proceeds with an upward consecutive count to eight. The counter is reset

Bob Reifsteck, K2LZG, 81 Bonita Drive, Rochester, New York 14616

automatically by a jumper from pin 11 to pins 2 and 3 and begins counting again from zero. This action continues until the squelch circuit gates the oscillator off. As the scanner counts, it sequentially turns on one receiver oscillator at a time by

from being fed back to the scanner. It may also be desirable to bypass the scanner output for rf with a 0.001- μ F capacitor on each output.

Note that the scanner is connected for receiving only. If the scanner is installed


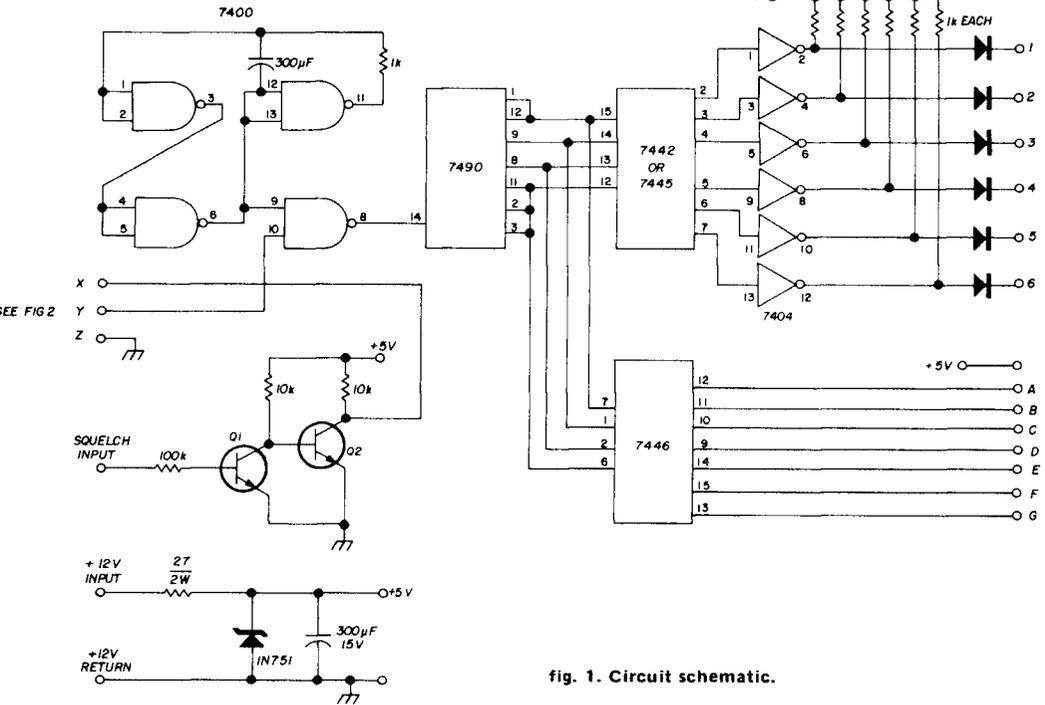


fig. 1. Circuit schematic.

either forward biasing a diode connected to a crystal, or by applying bias directly to the oscillator circuit. Either a seven-segment readout or individually marked lamps can be used as indicators to identify the channel being monitored. The seven-segment readout is driven by a special decoder-driver IC, which receives its input from the counter BCD output and translates the count to indicate the channel. Lamps may be driven directly from the decimal decoder. The oscillators can be driven from the decimal decoder directly or by an inverter following the decoder, depending on the voltage sense required to switch your receiver oscillator circuit. It is recommended that series diodes be used at the scanner output to the oscillators to prevent receiver voltages

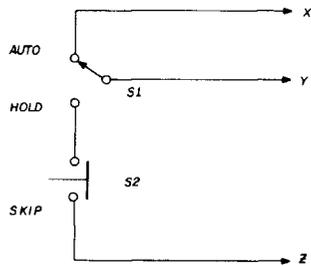in a transceiver that uses a common switch to change both receive and transmit channels, ensure that the transmit crystal does not become enabled by the scanner, or you may transmit on several



SEE FIG 1

S1 = SPDT TOGGLE
S2 = SPST NORMALLY CLOSED PUSHBUTTON

fig. 2. Suggested circuit for manual override control.

channels at the scan rate. It's best to choose a switch position for receive without crystals in either the receive or transmit socket. Use this switch position to enable the scanner. When in radio contact, switch the channel selector to

A. A +5-volt signal to enable scan and a zero-volt signal or ground to stop scan.

B. A +5-volt signal to stop scan and a zero-volt signal or ground to enable scan.

The choice of A or B depends on the voltage available from your receiver squelch circuit. For situation A, use the complete input circuit with two transistors (fig. 1). For situation B, use only one transistor and be sure to use a high-value base resistor (100k or more) to prevent loading your receiver squelch circuit.

The scanner will work without the switches, but for convenience and flexibility, switches are recommended. This is especially true if one of the monitored channels is a repeater. A toggle switch can be used to change from auto to hold, and a momentary pushbutton switch can be used to skip from one channel to another. See fig. 2.

outputs

channel indication. If you are using a seven-segment readout, wire the unit as indicated for that section. If you are using indicator lights, one end of each lamp can be tied together and connected to a positive voltage, depending on the lamps used. The other end of each lamp can then be connected to the appropriate 7445 or 7442 terminal. The 7445 can handle up to 30 volts and sink as much as 80 mA, although low-current, low-voltage lamps are preferred.

control of oscillators

This scanner can switch oscillators and indicate channels in several different ways. The standard version, shown in fig. 1, is used with a seven-segment readout and controls an oscillator similar to that indicated in figs. 3A and B by applying forward bias to a diode or by biasing the oscillator directly. If more than 4.5 volts are needed to operate an oscillator, use an open collector inverter (7406) instead of the "totem pole" output inverter (7404). The 7404 should not be operated above 5 volts. The 7406 can be operated with 30 volts on the open output (although package V_{CC} must remain at +5 volts). If you

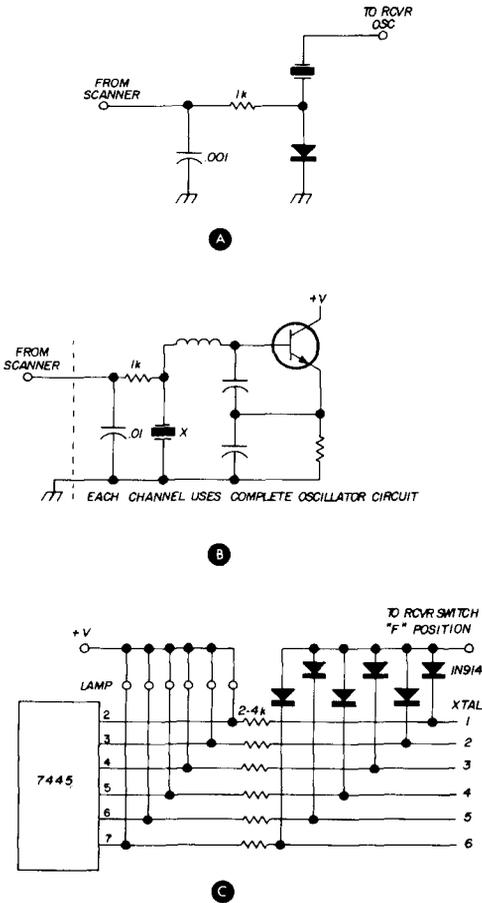


fig. 3. Receiver oscillator control circuits. Method A switches crystal directly; method B switches bias to oscillator. Circuit in C is for oscillator control in Regency receivers.

the appropriate position and disable the scanner; that is, don't put the scanner in hold and attempt to transmit!

inputs

power supply. The unit requires +12 V at 220 mA if you use the zener circuit.

squelch. Provision is made to accept either:

how to use Plessey SL600-series

integrated circuits in amateur communications equipment

A complete description
of the versatile
Plessey SL600
linear ICs,
and how to use them
in receivers
and transmitters

James M. Bryant, G8FNT, Plessey Linear Applications Engineer

The Plessey SL600 series of integrated circuits for use in transmitters, receivers and other communications systems is now in use all over the world, and Plessey continually receives inquiries from radio amateurs who want applications data on the different SL600 circuits. In the hope of satisfying this need, G8FNT, a linear applications engineer for Plessey, has prepared this article.

The Plessey SL600* series of ICs includes rf and i-f amplifiers with low cross-modulation and good agc; audio amplifiers with and without agc, high-performance balanced modulators and speech agc generators. Also included in the series is a complex circuit containing a-m and ssb detectors, and a CW-operated agc system.

This article describes some transmitters and receivers that are based on the use of SL600 ICs, but does not cover the audio sections or high-power rf amplifiers. The first part of the article describes a variety of communications systems which use Plessey ICs. The latter part of the article gives circuit details and comments on some potential causes of trouble experimenters might run into.

*The complete line of Plessey SL600 ICs is available from Circuit Specialists, Box 3047, Scottsdale, Arizona 85257. Write to them for their complete price list, or see their advertisement in this issue.

receiver systems

The simplest receiver which can be built from SL600 ICs is the direct-conversion unit shown in block form in fig. 1. This direct-conversion receiver, also known as a synchrodyne, can be used for the reception of a-m, ssb and CW. The vfo is tuned to the carrier frequency in the case of a-m and ssb, and a few hundred hertz away for CW. Upper and lower sidebands are equally well detected by this receiver, and if the audio passband is limited, it is quite selective.

However, if this simple direct-conversion receiver is used to receive an upper-sideband ssb signal adjacent to another ssb signal only 2 or 3 kHz away, the interference will be quite severe. This interference can be removed, and only one sideband detected, with the more complex phasing system shown in fig. 2.

The direct-conversion receiver in fig. 2 uses rf and audio phasing to cancel one sideband, so it is truly a single-sideband receiver. In this circuit it is necessary to have accurate phasing of the signals, and well matched gain in the two audio channels feeding the summing stage. The upper or lower sideband may be selected by reversing the audio phasing. (The rf phase may also be reversed for the same purpose, but switching the audio is easier.) The system in fig. 2 detects the

S-meter. Depending upon the sensitivity required and the audio gain available, one or two rf amplifiers may be used. The SL610 IC has a gain of 20 dB, and frequency response to at least 146 MHz. (This performance, which exceeds that shown on the SL610 data sheet, depends on very careful layout, very short leads and very great attention to coupling and

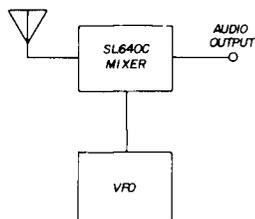


fig. 1. Block diagram of the most simple direct-conversion receiver which can be built with Plessey SL600 ICs.

decoupling of power supplies and agc. However, amateurs who use the SL610 on two meters find that the performance at these frequencies is satisfactory.)

Other ICs which may be used for the rf amplifiers are the SL611 and SL612. The SL611 provides 26 dB gain and is usable to 80 MHz; the SL612 has 34 dB gain with frequency response to 15 MHz. The amplifier you choose, here and in the other systems to be described, depends upon the frequency and the gain re-

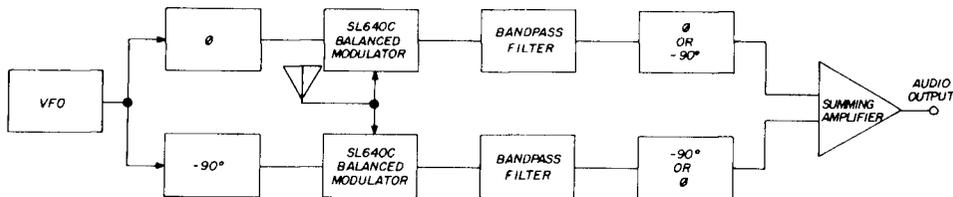


fig. 2. Block diagram of a phasing-type direct-conversion ssb receiver.

lower side-band when the upper channel phase shift is positive.

Another direct-conversion receiver is shown in fig. 3. Whereas the circuit of fig. 1 is subject to interference, is not very sensitive and has no agc, the circuit of fig. 3 has rf filters to minimize cross-modulation, an rf amplifier, agc and perhaps, an

quired. The SL612 has the extra advantage of lower current consumption and slightly lower noise figure.

conventional superhet

A much more conventional superhet receiver is shown in fig. 4. This design consists of an rf stage with agc (which

would probably be an SL610 IC), a mixer (SL640 or SL641), an i-f filter (LC, crystal or ceramic), an i-f amplifier with agc and a detector.

The i-f amplifier could be one or two stages, depending on the sensitivity re-

agc output of SL623 and the audio-derived agc provided by an SL621 connected to the ssb output of the SL623.

The i-f filter may also be switched, with a narrow bandwidth filter for ssb, and a wider one for a-m. To detect

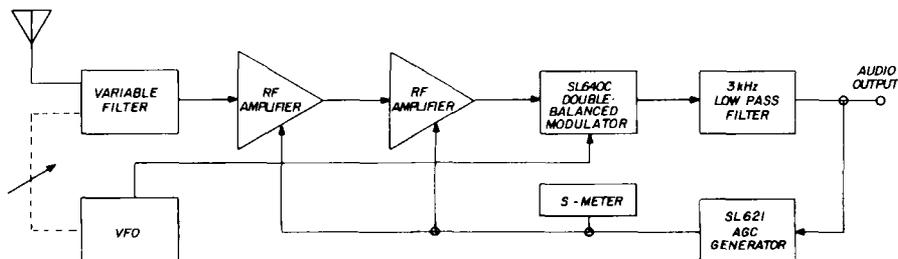


fig. 3. Practical direct conversion receiver can be used successfully on the amateur high-frequency bands.

quired, but agc would normally be applied to only one stage. An SL640 or SL641 would be suitable for the ssb and CW detector, followed by an SL621 to provide audio agc. If a-m operation is required, an SL623 could be used. This IC also generates carrier agc, and when used with a bfo, detects CW or ssb.

For fm detection either the SL432 or SAA570 may be used, but a separate carrier detector is required to provide automatic gain control.

narrowband fm, a detector such as the SL432 or SAA570 is connected to the output of the second SL612C. During narrowband fm reception agc is taken from the SL623.

Double-conversion superhets may also be designed using SL600-series ICs, but with modern filters, double-conversion superhets are rarely needed on the amateur high-frequency bands. However, they are occasionally used on uhf or where complex tuning systems are required.

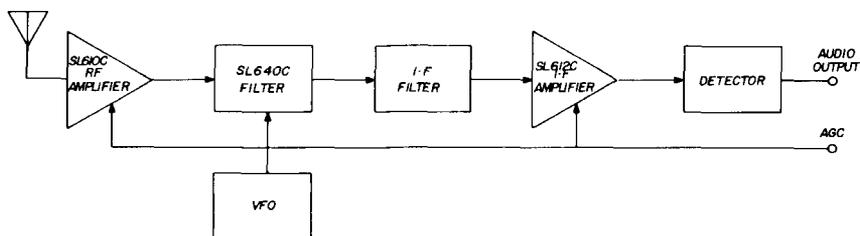


fig. 4. Layout of the basic superhet receiver.

A more complete superhet circuit which features front-end tuning and both a-m and ssb detection is shown in fig. 5. The output of the audio stage is switched between the two detector outputs of the SL623 IC. The agc line, which also drives an S-meter, is switched between the CW

Inasmuch as the same techniques are used as in the single-conversion superhets shown in fig. 4 and fig. 5, no double-conversion designs will be described here. However, it should be noted that SL600 devices have high gains, and you should avoid using too many amplifying stages.

ssb exciters

A basic filter-type ssb exciter is shown in fig. 6. The audio and a low-frequency rf signal from an oscillator (the bfo if the exciter is part of a transceiver) are mixed in an SL640 IC. The SL640, as a result of

phase shifted so that two separate, equal-amplitude audio signals with a 90° phase difference are obtained. These audio signals are applied to the signal inputs of two SL640 ICs, rf reference and quadrature signals are applied to the

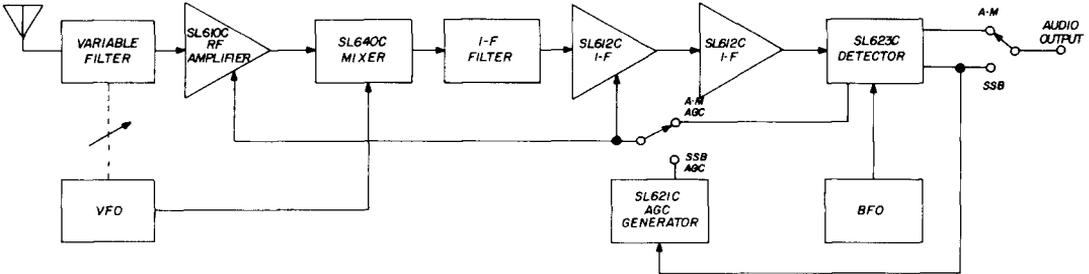


fig. 5. Complete superhet communications receiver for ssb, a-m and CW. Fm detection can also be added as described in the text.

its good carrier rejection, provides a clean dsb suppressed-carrier signal at the output. This dsb signal is passed through a narrow bandpass filter to remove one sideband. The remaining sideband is converted to the final operating frequency by another SL640. The image is removed by a filter, and the output is connected to a linear amplifier.

A more complete filter type ssb exciter with automatic level control (alc) is shown in fig. 7. In this circuit the

carrier inputs, and the two output signals are summed.

If the audio and rf reference signals are applied to one modulator, and the quadrature audio and rf signals are applied to the other, the lower-sideband outputs will be in phase and will add. The upper-sideband outputs will cancel, providing a lower-sideband output. Similarly, if the audio reference and carrier quadrature signals are applied to one modulator, and the audio quadrature and carrier refer-

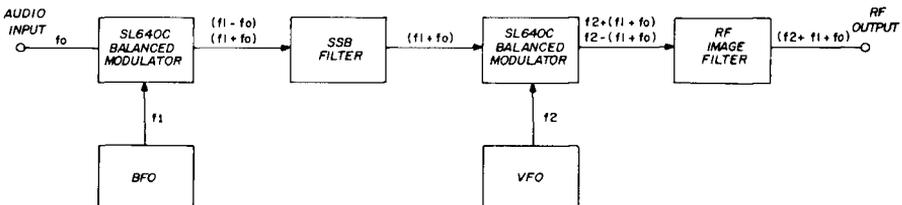


fig. 6. Basic filter-type ssb exciter.

ence are applied to the other, upper-sideband output is obtained.

This method of generating ssb appears attractive in many respects, and has the advantage that no expensive filters are required. Also, the carrier frequency may be varied so no further frequency conversion is necessary. Unfortunately, the

ence are applied to the other, upper-sideband output is obtained.

This method of generating ssb appears attractive in many respects, and has the advantage that no expensive filters are required. Also, the carrier frequency may be varied so no further frequency conversion is necessary. Unfortunately, the

phasing systems has one serious drawback: To keep the undesired sideband 40 dB below the desired sideband, the phasing, both audio and rf, must be accurate within 2° . Also, the amplitude of the rf carrier applied to one modulator must be adjusted to minimize second sideband

figs. 5 and 7 or figs. 2 and 8, you'll note that ssb transmitters and receivers of the same types are quite similar. Therefore, with a little signal switching, it is possible to make one set of SL600 ICs perform as both a transmitter and a receiver. This, of course, saves both on SL600 ICs and

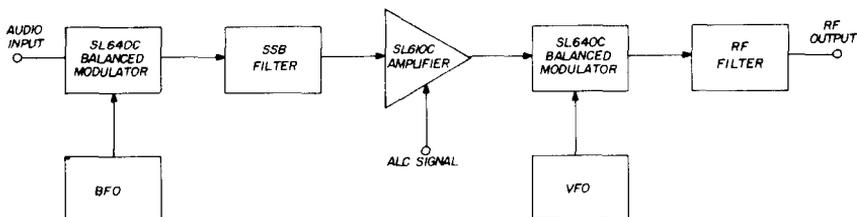


fig. 7. Ssb transmitter with automatic level control (alc).

generation, and carrier leak must be minimized in both modulators.

However, despite the adjustment problems, this method of obtaining a ssb signal is very popular, probably because no expensive filters are required. The system shown here is compatible with the direct-conversion receiver in fig. 2, and a very simple ssb transceiver can be built by combining these two systems.

amplitude modulation

Since a-m is merely double sideband with carrier, an SL640 may be used as an amplitude modulator if carrier leak is increased. If a 15k resistor is connected between pin 2 of an SL640 and ground as shown in fig. 9, there will be sufficient carrier on the output of the SL640 for a-m. By switching the resistor in and out of the circuit either a-m or dsb may be produced. If you also switch the filters following the SL640, a-m, dsb or ssb may be obtained from the same SL640 with the same inputs. With this simple arrangement you can build a multi-mode transmitter with very few components.

transceivers

If you look over the illustrations in

*Vogad is an acronym for voice-operated gain-adjusting device.

expensive filters. Fig. 10 shows the block diagram of a typical ssb transceiver based on the use of SL600-series ICs.

rf clipping

As has been noted by a number of designers, audio limiting and audio clipping are not useful techniques for increasing the average-to-peak power ratio of ssb transmitters, although audio agc is (derived, perhaps, from an SL622 vogad* circuit). If clipping is used, it must be performed on the rf ssb signal and the clipped signal must be filtered to remove splatter.

The rf clipping system shown in fig. 11 needs careful initial adjustment but yields remarkably good results. The input audio, which should be agc controlled, is con-

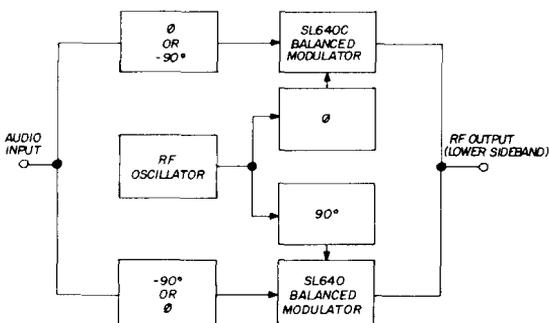


fig. 8. Phasing-type ssb exciter.

verted to ssb in the basic system; then the ssb signal is clipped by a symmetrical peak clipper. The signal is then refiltered to remove splatter and is passed through an alc amplifier and converted to the final operation frequency. The audio input level must be adjusted so that clipping is not so excessive that it destroys intelligibility.

If the clipper is replaced by a Schmitt trigger, and the audio input is given 12 dB per octave pre-emphasis above 1 kHz, a class-C power amplifier may be used. The output signal is received as ssb, although it has slight distortion. This arrangement provides a peak power equal to mean power during speech. If carrier leak is allowed to occur during pauses in speech so that the transmitter is always delivering the same power to the antenna, tvI is much reduced. In this case alC — and hence the SL610C — is not needed.

other systems

The Plessey SL600 integrated circuits may also be used in various other parts of amateur communications equipment. Fig. 12 shows a mixer vfo which mixes the output of a low-frequency vfo with a crystal-controlled signal to produce a stable high-frequency vfo. With this circuit in a multiband receiver, several

crystals may be used to tune several different bands with one vfo.

An IC agc system which is designed to stabilize the amplitude of an rf carrier is shown in fig. 13. A simple low-power IC linear amplifier is shown in fig. 14. In this circuit the value of the emitter resistor

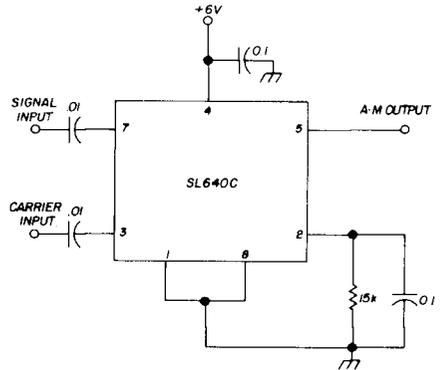


fig. 9. Amplitude modulator using a Plessey SL640 IC.

depends upon the power transistor used in the output stage.

If audio squelch is required in a receiver, the system shown in fig. 15 will provide it. This circuit is based on the fact that if pin 7 of an SL630 audio amplifier is grounded, the circuit is muted. The circuit illustrated, when turn-

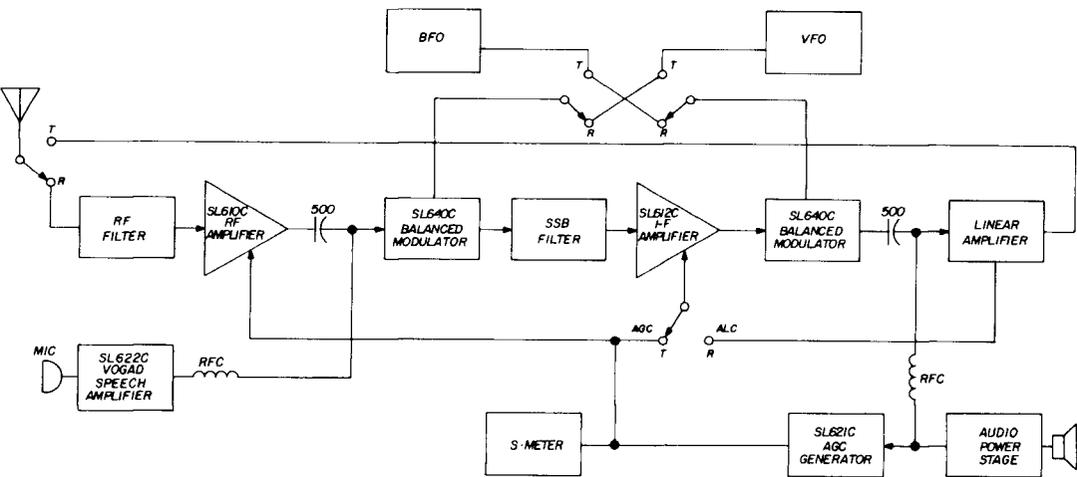


fig. 10. Complete ssb transceiver based on the use of Plessey SL600 ICs. During transmit the SL610C, SL621C and audio output stage are turned off; during receive the linear amplifier and SL622 are turned off.

ed on, insures that the SL630 is muted until the agc reaches a preset level. This prevents unwanted receiver noise when no signal is being received. The agc signal may be derived from an SL621, SL623 or

in block form in **fig. 5**. Perhaps the easiest way of explaining the use of the SL600 family of ICs is to describe this circuit and its operation in detail.

Starting from the antenna, the input

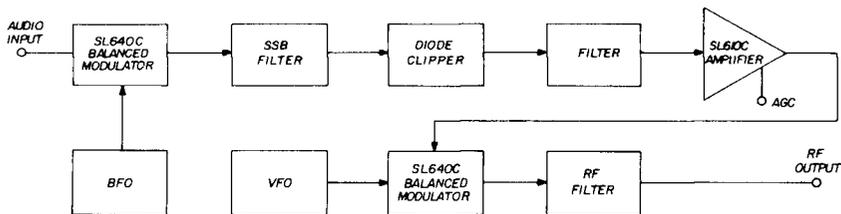


fig. 11. Ssb transmitter with rf clipping.

other sources. Any high-beta silicon NPN transistors are suitable for this circuit — a Plessey SL301C monolithic dual transistor is shown here.

A VOX system may be easily added to any transceiver which uses the SL622 as a microphone amplifier. A possible circuit

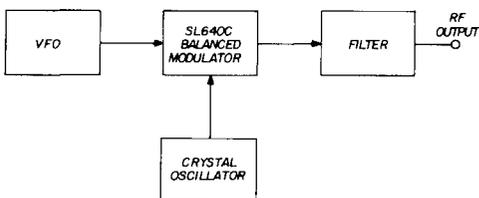


fig. 12. Basic circuit for the mixer-vfo.

is shown in **fig. 16**. It consists of an op-amp which is switched by the agc voltage of the SL622, and in turn switches the transmit-receive relay in the transceiver. The transistor may be any high-gain silicon type which can carry the relay current. However, a Darlington arrangement must be used to make sure the relay turns off again. This is because the minimum output of the op-amp can sometimes be more than 0.7-volt above the negative supply line; this is sufficient to turn on a single transistor.

communications receiver

The communications receiver circuit shown in **fig. 17** is the same circuit shown

filter depends upon the i-f and the band being tuned. It must be sufficiently narrow to provide rejection at the image frequency (that frequency on the other side of the local oscillator from the wanted frequency and spaced the same amount from the oscillator frequency). If the image frequency gets through the input and mixes with the local oscillator it will produce an unwanted i-f signal.

The SL610 rf amplifier is coupled to the input filter in such a way that the IC is never inductively terminated. This is because the SL610 can become unstable if it looks into an inductance. The input coupling is also chosen so that the input filter Q is not lowered.

If an SL610 input is connected to a source which might be inductive, the source should either be shunted with a few thousand ohms, or a few hundred ohms should be connected in series with the input to the IC. The SL610 is biased by connecting the bias pin (pin 6) direct-

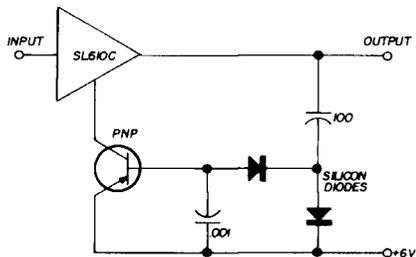


fig. 13. Carrier agc system uses one IC.

ly to the input (pin 5). (This same biasing arrangement is used with all the other rf and i-f amplifiers in this receiver.)

If an SL610, SL611 or SL612 are connected as shown in fig. 18, slightly

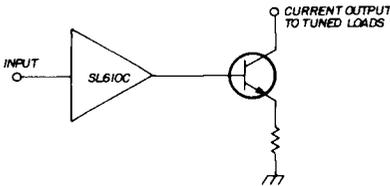


fig. 14. Low-power linear amplifier stage.

lower noise will result, but this is not usually worth the extra complexity. It is important that the input and output grounds on these devices be kept separate — output currents flowing through the input ground leads tend to produce instability.

Both the agc line and the SL610 positive supply (which is shared with the SL640 mixer) are decoupled to ground. Ideally, this is not necessary, but rf on power supply and agc lines can cause trouble with some circuit layouts. Where expense does not rule out decoupling, it is recommended. (The SL640 supply is not internally decoupled although that of the SL610 is.) To minimize the output current loop of the SL610 the SL640 ground (pin 8) should be as near as possible to the output ground of the SL610 (pin 8).

The output of the SL640C first mixer drives the input of the crystal filter. The

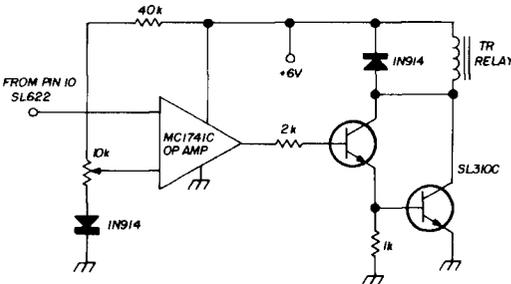


fig. 16. Simple VOX circuit for use with SL622C.

filter must be terminated by the correct impedance (pure resistance or resistance shunted by capacitance). If the resistive component is low enough, an SL641 may be used in the mixer circuit as shown in fig. 19. This is the case where SL640s are used: They may be replaced by SL641s in certain circumstances.

When the output from the SL640 is taken at pin 6, it requires an external load greater than 560 ohms. This is because the pin-6 output is a low-impedance emitter follower and it must not be used to drive capacitive loads. Some filters have transformer-type inputs with low dc resistance to ground (less than 10 ohms). In this case the terminating resistor, as long as it is larger than 560 ohms, may also be used as the load resistor. In this

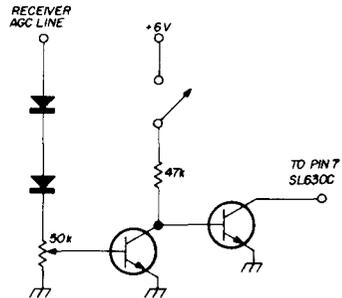


fig. 15. Audio squelch system.

case the dc blocking capacitor must *not* be used.

Pin 2 of the SL640 and SL641 must be decoupled to ground through a low-leakage capacitor (less than 0.1 μ A). The reactance of this capacitor must be less than 10 ohms at the lowest input or carrier frequency. The carrier input from the local oscillator should be 100 to 200 mV rms and should be as free from modulation as possible.

The broadband i-f amplifier following the crystal filter consists of two SL612 ICs; agc is applied to only one stage at pin 7. The SL612 has a 70-dB agc range, while the agc range of the SL610C rf amplifier is 50 dB, giving a total for two gain-controlled stages of 120 dB. If both SL612 i-f amplifiers were agc controlled,

at this point; this prevents the trouble and also reduces noise produced in the broadband i-f stages.

The output of the SL640 detector is decoupled to ground at frequencies above 4000 Hz with the 0.05 μF capacitor from pin 5 to ground. The load across pin 6 is a 1000-ohm preset potentiometer. The audio output to the amplifier is taken directly from pin 6, but the audio for the SL621 agc stage is taken from the potentiometer wiper. With this arrangement the agc threshold can be adjusted so that noise in the antenna and receiver circuits does not turn on the agc in the absence of a signal. The coupling capacitor to the SL621 should not exceed 1 μF or low-frequency instability may result.

The SL621 agc generator will usually drive a 500- μA S-meter connected in series with 5100 ohms and three silicon diodes from the agc output to ground. Occasionally, however, this is too much load for an SL621, and the transistor S-meter circuit shown in **fig. 18** is preferable. The value of the emitter resistor depends upon the meter used, and is given by the following formula:

$$R = \frac{2.7}{I}$$

where I is the full-scale current in mA and R is in kilohms. For a 1-mA meter, this works out to be 2700 ohms. With this circuit the S-meter reads linearly in dB; from zero to full scale is about 120 dB.

The power supply to the SL621 must be well decoupled; 500 μF from pin 4 to ground is usually sufficient, but if the audio output stage shares the same power

supply, this value should be increased. If a series-stabilized power supply is used, it should have a source impedance of less than 1 ohm.

The audio output stage may be an SL630, SL402, SL403 or other suitable audio power amplifier.

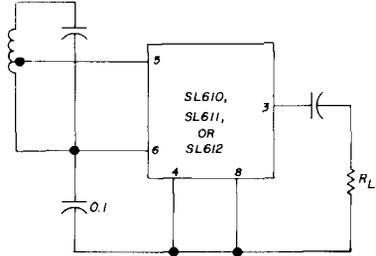


fig. 18. Low signal coupling to the SL610 SL611 or SL612.

other applications

When SL600-series ICs are used in a transmitter or a transceiver they are used in much the same way as described above. However, since transmitters often contain rather large rf fields, particular attention must be paid to shielding and decoupling. In some cases it may be necessary to decouple individual stages.

When mixing frequencies or generating ssb in a transmitter, the original input frequencies are not wanted in the output. The SL640 and SL641 have approximately 30 dB signal and carrier rejection, but this may be increased with the circuit shown in **fig. 21**. With signal, but no rf carrier, R_1 is adjusted for minimum carrier leak. All modulators used in transmitters may be adjusted in this way

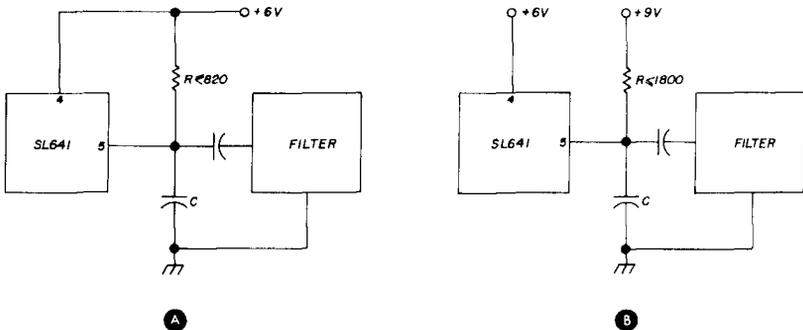


fig. 19. Circuits for matching the SL641 IC to filters.

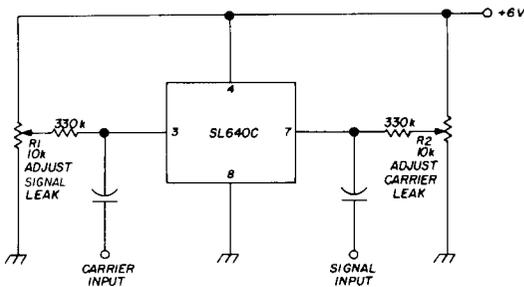


fig. 21. Signal and carrier-leak adjustment for the balanced modulator.

although it is less important in filter-type systems than in phasing systems.

The agc characteristics of the SL610, SL611 and SL612 are temperature dependent. It is unwise to use a voltage on an agc pin to set the gain of a stage. However, this may be done where agc is applied to another stage in the chain to compensate for signal variations.

The SL610, SL611 and SL612 tend to oscillate if they are required to drive a capacitive load. Such loads should be buffered by a resistance or another type of amplifier. For the SL610 and SL611 a 47-ohm buffer resistor should be used; a 150-ohm buffer resistor is used with the SL612. When an rf signal is taken from any of these SL600 amplifiers to points far removed, care must be taken to prevent instability caused by ground loops.

using the SL623

The SL623 IC combines the functions of a low-level, low-distortion a-m detector and agc generator with a ssb demodulator. It was designed specifically for use in ssb/a-m receivers, and is not used in ssb-only receivers. A typical application for the SL623 is illustrated in fig. 22. Since the agc output from this circuit is CW derived, if audio-derived agc is required for ssb operation, an SL621 should be used. In the circuit of fig. 22 the resistor between pins 2 and 5 sets the value of carrier at which agc operation begins. The bfo signal should be a clean sine wave at about 100 mV rms.

When using the SL623 all the decoupling capacitors should go to one point. Also, the positive power supply should be decoupled. The SL623 is as sensitive to ssb as the SL640, but it requires 125 mV rms of a-m to activate the agc. Therefore, greater i-f gain may be necessary. Despite statements to the contrary in the data sheet, the SL623 functions to at least 30 MHz and, with reduced performance, to over 120 MHz.

other devices

The other members of the SL600 family are the SL620, SL622 and SL630. The SL630 is an audio amplifier with

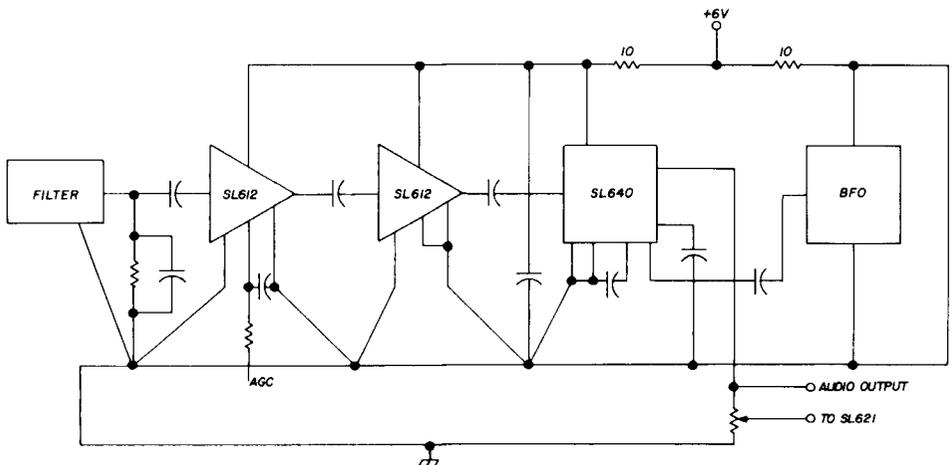


fig. 20. Proper method of grounding the ICs used in the i-f strip.

voltage-controlled gain and up to 75 mW (6-volt supply) or 200 mW (12-volt supply) output. When the SL630 is used with the SL620, which is similar to the SL621, it forms an audio agc system.¹ The SL622 is a self-contained audio agc system with an additional sidetone output which is not agc controlled. These circuits are compatible with the rest of the SL600 series, use the same power supplies and are packaged in the same T05 cases.

summary

In this article I have briefly described how the Plessey SL600-series ICs can be used in high-frequency receivers, transmitters and transceivers. It can be seen that, with the exception of power amplifiers and oscillators, high-frequency transceivers can be built with SL600 devices for all functions. Vhf and uhf transceivers can be built with SL600 ICs in all but the rf and mixer stages. These modern ICs make the design and construction of a-m and ssb equipment extremely simple, and

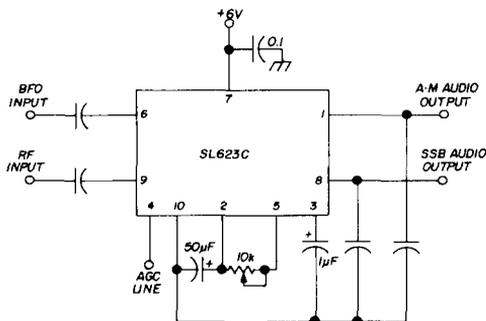


fig. 22. Suggested circuit for using the SL623C as a ssb and a-m detector.

offer the home builder the opportunity to use complex, high-performance circuits which he would not consider if he were limited to individual transistor stages.

reference

1. James Bryant, G8FNT, "Miniature Microphone Preamplifier with AGC," *ham radio*, November, 1971, page 28.

ham radio

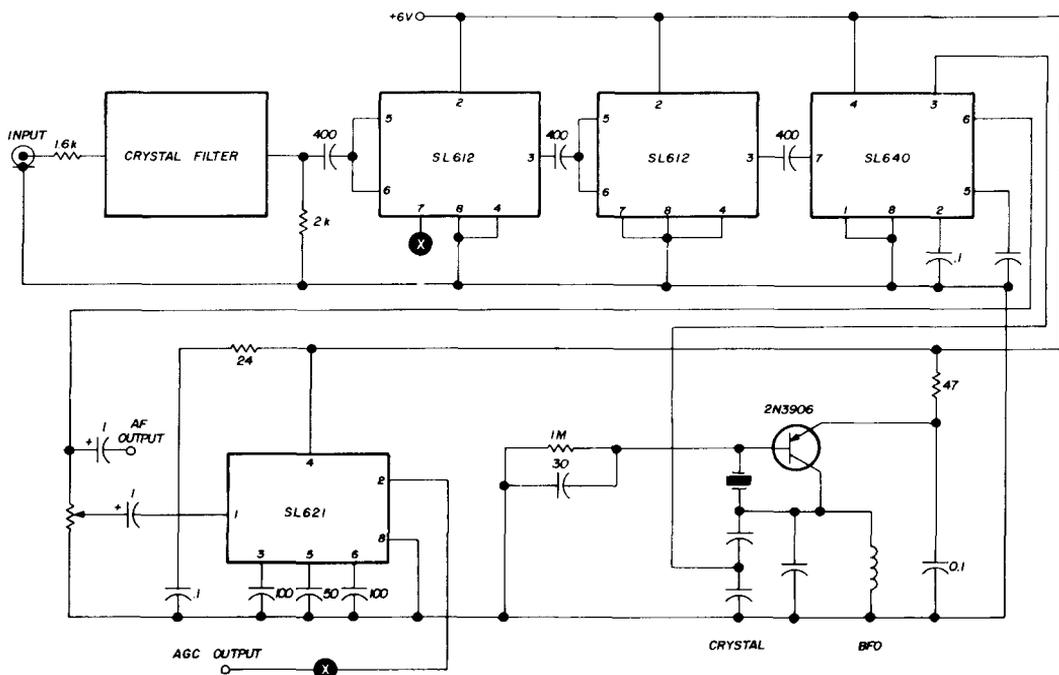


fig. 23. Complete circuit of a 10.7-MHz i-f strip, ssb detector and voice agc system.

solid-state noise blanker

Complete
construction details
for a
solid-state
noise blanker
that really works

Ray Megirian, K4DHC, Box 580, Deerfield Beach, Florida 33441

In recent years there has been a rash of articles describing noise blankers and their virtues. Although the basic principles upon which the circuits depend are not new, the refinement of noise-blanker circuitry has come a long way with the help of modern solid-state devices.

Since I'm a homebrew nut of the first order, every time an article appeared dealing with the construction of a noise blanker, I'd drop everything and start breadboarding. More often than not, the end results left much to be desired. Usually, the old fashioned noise clipper did a better job with far fewer components. This frustration soon led me to the point where I was ready to climb the walls. Just to play it safe, I went back to building sweep generators, counters and receivers without noise blankers.

As this rest cure went into its second year, I started to itch again. I found myself thumbing through my magazine collection and decided to give it another try.


the circuit

Nearly two years ago W2EGH described his version of a noise blanker, patterned after a vacuum-tube unit developed by the R.L. Drake Company.¹ This led me to assume that there was still hope since better brains than mine had done most of the hard part.


After the project finished me, I decided not to go back on the rest cure but to chance a few more weeks of cut-and-try orgies. In looking over some

here and worked well. The MPF102 fet may give some trouble due to variations in characteristics, and more than one may be needed to obtain a unit suitable for use in this circuit.

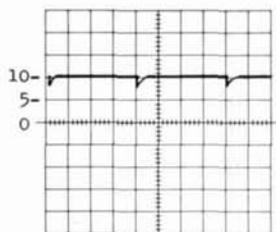
threshold control at full counter-clockwise (no blanking). With a 12-volt supply the level at TP1 should be around 11 volts. Turn the threshold control fully clockwise (maximum blanking). This may



Threshold control slightly advanced.

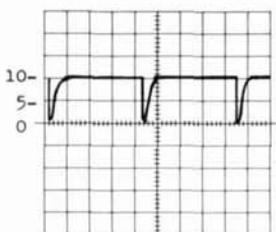

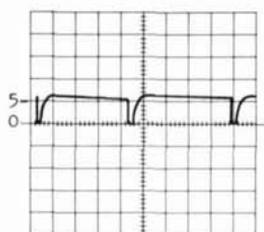Threshold control about one-third advanced.



Threshold control full on.

fig. 3. Typical performance of the solid-state noise blanker.

alignment

Transformers T1 and T2 are peaked for maximum signal in the normal manner. Gain of the CA3028 i-f amplifier may be adjusted to suit your particular requirements by choice of the bypass capacitor from pin 4 to ground. If you already have sufficient i-f gain in your

or may not cause the level to drop at TP1. The desired dc level at this time is 5 volts. Use the 10k trimmer to make this adjustment. If things don't work out as prescribed, try a different MPF102.

When I first started experimenting with blankers I built an ignition noise synthesizer, and found it invaluable for

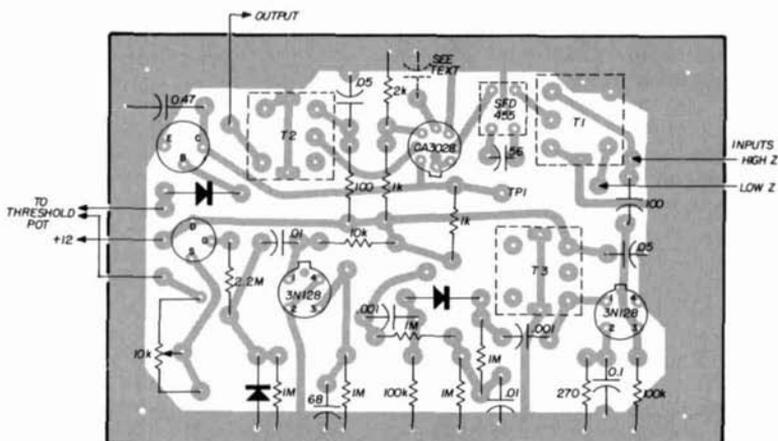


fig. 2. Full-size printed-circuit board for the noise blanker.

receiver, leave it out altogether. If you need extra gain, try values between .001 and 0.1 μ F.


The 10k trimmer and T3 are best adjusted while observing the gate output at TP1 on a dc scope. Start with the trimmer fully clockwise and the panel

testing. However, one of the small toy battery motors at idling speed will generate some nice noise pulses for test purposes. Couple this source right to the antenna. With the threshold at minimum there should be no blanking pulses present at TP1.

As the control is advanced, negative-going pulses will appear at TP1. When these pulses stretch all the way to ground, blanking of the i-f amplifier commences. Fig. 3 shows typical displays for various settings of the threshold control. Peak T3 for best sensitivity.

conclusion

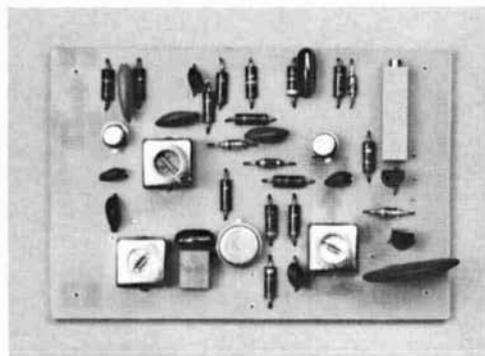Now that it's my turn to make brash statements, let me say that noise blanker performance on impulse noise is excellent, changing unreadable signals into perfect copy. Of course, you've heard all that before. The way I feel, though, is that if enough of this type of circuitry is published, perhaps eventually we'll be able to take the best from each and end



Overall photo of the assembly

up with what we've always considered to be the ultimate in performance, or at least a reasonable facsimile.

Since some of the components may be a problem with prospective builders, I will try to help out if the demand is sufficient. I refer specifically to the Murata filter, PC board and Beckman trimmer. The rest of the components are quite common and easily obtained.

I would like to hear from anyone interested in exchanging ideas along the lines presented above — if you're not on the cure.

reference

1. Frank Van Zant, W2EGH, "A Solid-State Noise Blanker," *QST*, July, 1971, page 20.

ham radio

PIV	TOP-HAT		STUD-MOUNT	
	1.5 AMP	EPOXY 1.5 AMP	EPOXY 3 AMP	6 AMP
50	.04	.06	.12	.15
100	.06	.08	.16	.20
200	.08	.10	.20	.25
400	.12	.14	.28	.50
600	.14	.16	.32	.58
800		.20	.40	.65
1000		.24	.48	.75

ZENERS

All Units Tested and Guaranteed

400 MILLIWATT UNITS — 3, 3.3, 3.6, 3.9, 4.3, 4.7, 5.6, 6.2, 6.8, 7.5, 8.2, 9.1, 18, 22, 24, 27, Volts.

1 WATT UNITS — 10, 11, 12, 13, 15, 16, 18, 20, 22, 27, 30, 33, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91, 100, 110, 120, 130, 150, 160, 180, Volts. ALL UNITS 10% — 4 for \$1.00 ppd. 5% — 3 for \$1.00 ppd.

1 AMP MOLDED BRIDGE RECTIFIER



200 Volt PIV Small Size — Manufactured By General Instrument. Ideal For P.C. Board. 50¢ Each, 3 For \$1.25 ppd.

115 VOLT AC TRANSFORMER

Secondary 12-0-12 Volts @ 800 ma. Very Nice. \$2.40 ea. ppd.



Power Transformer. 115 Volt AC Primary. Secondary #1: 32-0-32 Volt @ 1 Amp. Secondary #2: 6.3 Volts. Low Current For Pilot Lights. Size 2 1/2" x 2 1/2" x 3". Price: \$2.50 Each ppd.

6.3 Volt 1 Amp Transformer. Fully Shielded \$1.60 Each ppd.

FACTORY NEW COMPUTER GRADE CAPACITORS



10,000 MFD @ 40 Volts. Size is 2" dia. x 3" high. Just right for that power supply. \$1.75 ea. or 3 for \$4.50 ppd.



High quality American Made TO-5 Transistor sockets. Ideal for PC board use.

10¢ ea. ppd.

100 kc. XTAL. Octal Plug-in. High Quality. \$3.50 ea. ppd.

BACK IN STOCK

Unpotted Toroids. All centertapped. 88 mhy or 44 mhy. Your choice 5 for \$2.00 ppd. 15 for \$5.00 ppd.

Transformer — American Made fully shielded. 115 Volt Primary

Secondary #1 18-0-18 Volts @ 4 Amps

Secondary #2 5 Volts @ 2 Amps

A very useful unit for LV Power supply use. Price — A low \$4.75 ppd.

SEND STAMP FOR BARGAIN LIST

Pa. Residents add 6% State sales tax

ALL ITEMS PPD. USA

 **m. weinschenker**
K 3DPJ BOX 353 · IRWIN, PA. 15642

a simple receiver-demodulator

for RTTY net operation

Some ideas for
a simple but effective
receiver/demodulator
for unattended
RTTY net operation

Larry Walrod, VE7BRK, 1644 Richter Street, Kelowna, British Columbia, Canada

As more and more amateurs become interested in radio teletype and more sequential selectors become available there is bound to be an increasing interest in 24-hour standby circuits in which any amateur, so equipped, can send RTTY to any other station on the same net. This is possible even when the receiving station's operator is away from his station. To avoid tying up the regular station equipment, it is desirable to have separate gear for the net frequency. I would like to suggest an inexpensive way to set up the receiving and demodulating functions in one unit, separate from the normal station receiver and terminal unit.

You will see in **fig. 1** that I have included all the *necessary* functions for reception and demodulation. However, I have eliminated a number of the circuits usually associated with each process by combining functions in a single unit.

After building forty ssb transceivers while on a recent five-year tour of the Republic of the Philippines, I got to respect the direct-conversion receiver. Although career commitments prevented my building a finished version of this unit, I feel confident that the design suggested here will be adequate for the intended purpose.

The circuit is easy to construct with only three rf coils and two mixer input

coils. All other components are subject only to low frequencies and require no special work or critical placement on the circuit board. The design, though simple, has one advantage over many more sophisticated designs as this receiver only copies the mark and space signals. Any

above the transmitted mark frequency) could vary a considerable degree around the selected frequency without adversely affecting the operation of this unit. No oven would be necessary and almost any bargain priced crystal would do. This is not the case, though, with the two mark

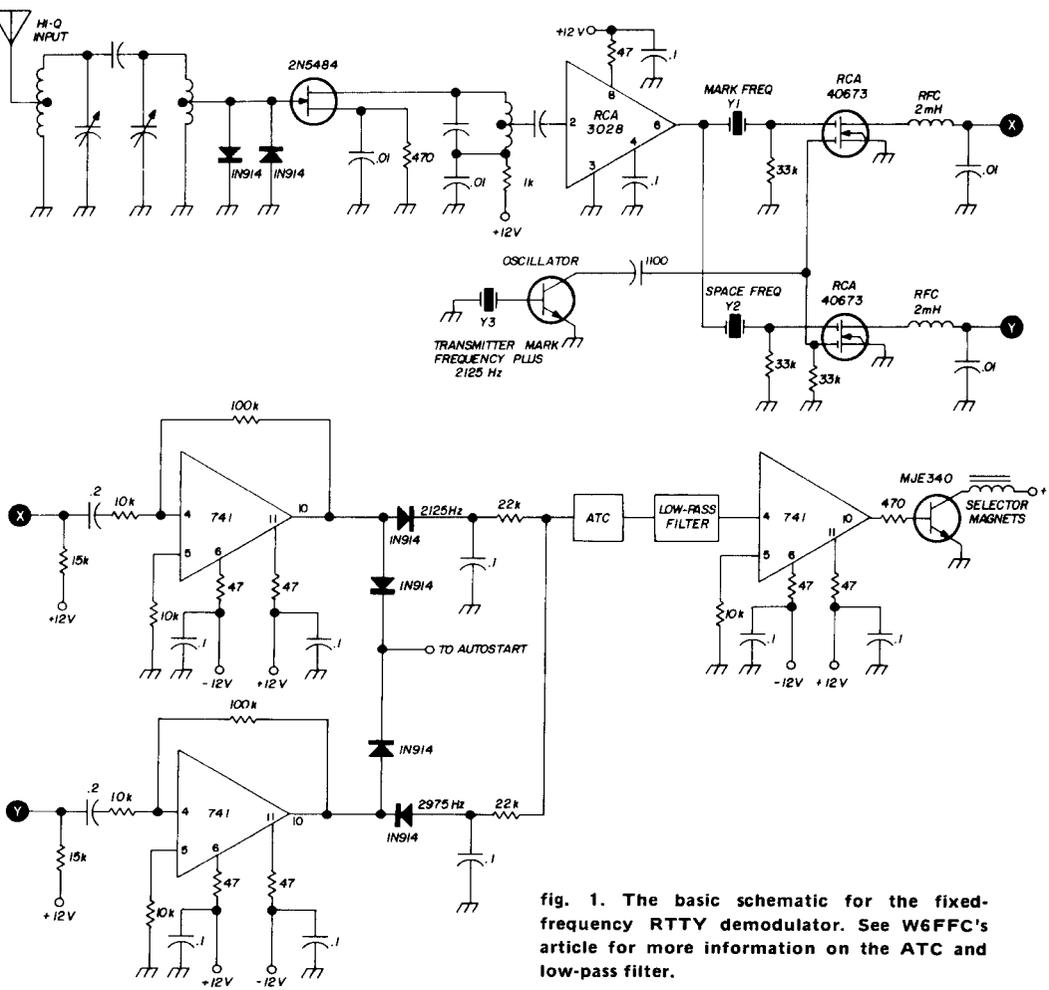


fig. 1. The basic schematic for the fixed-frequency RTTY demodulator. See W6FFC's article for more information on the ATC and low-pass filter.

garbage between these signals does not get through the receiver as would be the case in a more conventional audio band pass filter type design.

crystals

It is interesting to note that the local oscillator frequency (about 2125 Hz

and space frequency crystals in the filters at the input to the mixers. They have to be precisely adjusted and controlled – by an oven.

The cost of obtaining accurate crystals (± 20 Hz) might be a problem, but an enterprising amateur can easily get HC-6U crystals about 500 or 1000 Hz below the

required frequency and put them on frequency. Remove the metal top by mounting the two pins in a vise. While grasping the top of the case with a pair of pliers have a friend play a small propane torch flame on both sides of the case. It will be only about two seconds before the solder at the base of the case is melted enough for the top to be removed (straight up to avoid damaging the crystal).

The crystal can be inserted in an oscillating circuit and the frequency can be adjusted upwards as much as 5 kHz by very easy rubbing with a little fine sandpaper mounted over the rubber

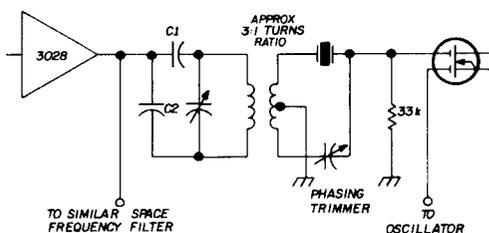


fig. 2. Suggested filter circuit for use in the circuit of fig. 1. Capacitor C1 is 15 pF and capacitor C2 is 62 pF for use on the 7-MHz band.

eraser on an ordinary pencil. Apply the sandpaper only to the plating — not on the quartz. Work a little on each side of the crystal. I have found that some crystals actually improve in activity with this treatment. Be sure to blow off any dust before making frequency checks.

Remember, though, that replacing the cover and connecting the cover to ground will have quite some effect on the final frequency. I found that grounding the case shifted the oscillating frequency of most 7-MHz crystals down about 75 Hz. If the unit is eventually to be grounded, it should be checked with the case grounded. However, when grinding and testing, you do not have to reseal the HC-6/U case each time you want to test the oscillating frequency. Just replace the cover and try it.

Also, it is not absolutely necessary to reseal the case at the end of the procedure if the crystal is going to be used in a reasonably constant atmosphere. Sealing, of course, will give far better long-term stability.

Resealing is not hard, though. There is a small vent hole near the top of the case which should be opened with a small drill and sealed *last*. Excessive heat while soldering the case to the base can lower the crystal's operating frequency by about 100 Hz. I've found a fairly effective technique is to clamp the crystal pins in a vise, install the cover (heat sunk with a large clothes pin to which a couple of brass plates have been attached) and then solder just about one quarter of the base at a time — allowing the assembly to cool between the solderings. With a little experience on this job a fellow can allow for this shift and solder the base of the case all at once (but still using the heat sink, of course). I've built about a hundred crystal filters — at first the work is very slow but it becomes easier with experience.

The balance of the circuitry is so basic and simple that it doesn't need any further treatment in this article.


reference

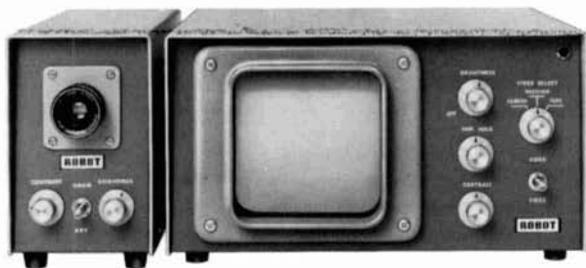1. Irvin M. Hoff, W6FCC, "Mainline ST-6 RTTY Demodulator," *ham radio*, January, 1971, page 3.

ham radio



"I spent \$1572.39 getting set up, and now I can't think of a thing to say."



Operating SSTV is easy.

True or False

How much do you really know about the newest activity in amateur radio? Take this 3 minute TRUE-FALSE quiz and see.

- | | | | | | |
|---|--------------------------|--------------------------|---|--------------------------|--------------------------|
| | T | F | | T | F |
| 1 A slow scan television picture is similar to that projected on TV. | <input type="checkbox"/> | <input type="checkbox"/> | 5 Any licensed amateur radio operator, except Novice, may operate SSTV. | <input type="checkbox"/> | <input type="checkbox"/> |
| 2 Motion can be portrayed on slow scan television. | <input type="checkbox"/> | <input type="checkbox"/> | 6 \$295 each for a Robot SSTV monitor and camera is the lowest price in the world for SSTV equipment. | <input type="checkbox"/> | <input type="checkbox"/> |
| 3 To broadcast slow scan television just add a Robot monitor and camera to your present station. No other equipment is necessary. | <input type="checkbox"/> | <input type="checkbox"/> | 7 Robot guarantees your satisfaction with all Robot equipment, or your money will be refunded. | <input type="checkbox"/> | <input type="checkbox"/> |
| 4 Slow scan occupies no more space on the band than an audio signal. | <input type="checkbox"/> | <input type="checkbox"/> | 8 New SSTV operators all suffer from lack of sleep. | <input type="checkbox"/> | <input type="checkbox"/> |

ANSWERS:

1. **False.** The slow scan television picture is a greenish-yellow color which takes 8 seconds to transmit. Like radar, the image should be viewed in a darkened room for best results. Also like radar, as the picture progresses it has the appearance of being painted onto the screen by a bright writing line except that the line moves from top to bottom. 2. **False.** Motion results in a blurred picture. 3. **True.** Robot equipment is compatible with all brands of amateur radio equipment and antenna systems. 4. **True.** The SSTV signal contains frequencies ranging from 1200 Hz to 2300 Hz. Therefore, it

is comparable to an audio signal. 5. **True.** 6. **True,** as far as we can determine. 7. **True.** 8. **True.** New SSTV operators are so enthusiastic about the fun of operating slow scan television, they hate to quit.

ROBOT

Please send your new factory direct price list.

Enclosed \$_____. Please send the following equipment via AIR or SURFACE

Instruction Books \$2

Model 70 Monitor \$295

Model 80 Camera \$295

25mm F1.4 Macro Lens \$54

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

California residents add 5% sales tax. Prices do not include shipping.

grid-current monitor for the Heath HW-100 and HW-101

A simple
circuit modification
for adding
a grid-current meter
to your HW-100

The Heath SB-line of transceivers has a meter-monitoring advantage over the less-expensive HW-100 and HW-101. It is obvious that several items have been deleted from the HW series in order to cut the price but it is not necessarily detrimental to the operation of the equipment to have fewer monitor points. It would probably be more correct to say that the SB-line incorporates some luxury features over the HW-line.

For example, the HW series uses a three-position slide switch for monitoring plate current, relative power output and

ALC. This is compared to a five-position rotary switch on the SB-line which monitors ALC, plate current, plate voltage, relative power output and grid current. The HWs are missing the high voltage and the grid current measurement.

High voltage is of less importance since the power supply puts out all it can, and it's either there or it isn't! But the grid current is a good indication of ALC operation and a definite asset in tuning and alignment. You can have this monitoring point for just a little time, a little wire and a switch.

installation

By drilling a small hole in the front panel just below the meter and between the two slide switches, and installing a dpdt switch, you can effectively lift the meter out of its regular circuit and insert

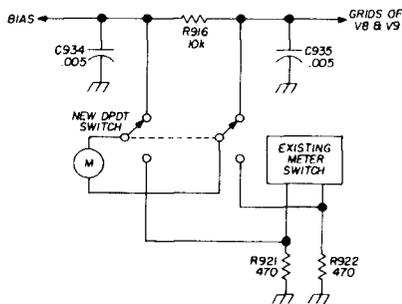


fig. 1. Grid-current monitor for the Heath HW-100 or HW-101. Only added part is S1, a dpdt switch.

Bob Snow, K4MFR, 713 Quarterstaff Road, Winston-Salem, North Carolina 27104

it into the grid circuit as shown in fig. 1. Resistor R916 does not appear on a printed board. It is located on the underside of the chassis on terminal strip BR near tube V8 of the final amplifier.

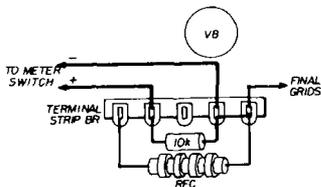


fig. 2. Location of resistor R916 under the chassis. Two new wires must be run to the added meter switch.

It is necessary to remove the cover that shields the coil assembly in order to gain access to the terminal strip. When you have located the resistor, solder a wire to each end as shown in fig. 2. Make sure the wires are long enough to reach to the meter. Route the pair of wires along the wiring harness, through the rubber grommet, to the other side of the under-chassis. Continue following along the harness to the front of the unit and feed the wires up through the hole in the board below the meter assembly.

Before connecting the pair of wires to the meter switch, check continuity from the resistor to code the wires for correct polarity, see figs. 2 and 3. Connect the wires as shown. Remove the connections from the meter and transfer them to the switch, observing proper polarity. Then connect the meter. It will be easier to

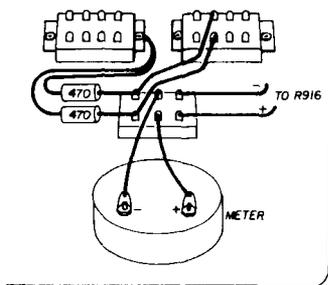


fig. 3. Modified wiring of the meter and panel switches.

make this installation if the meter is removed from the panel hole until all connections are made.

The switch should be one of the miniature types, either toggle or push-button. The momentary pushbutton is perhaps the most desirable since the added circuitry is only effective with the pushbutton depressed. At all other times the circuit remains normal.

operation

With the new switch actuated, the meter indicates grid drive, which is very helpful during tuneup. The indication is much sharper than previously when the transmitter is in the *tune* position and adjustments are being made with the *drive preselector*. The grid meter also provides an indication of ALC action during ssb transmission. No grid current (except occasional peaks) will be indi-

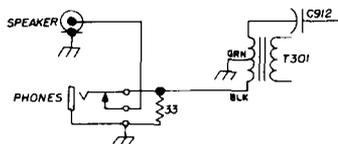


fig. 4. Simple circuit for silencing the HW-100 speaker when the headphones are plugged in.

cated during ordinary transmission if the ALC is operating properly.

Another annoying item in the HW-100 is the system of converting from speaker operation to headphone operation. The original circuitry connects the headphones in series with the speaker when the headphones are inserted in the phone jack. This is satisfactory as far as the headphones are concerned, but the speaker is not completely silenced. The circuit in fig. 4 shows a quick fix. It requires a 33-ohm resistor to be added at the phone jack and a length of wire to run between the phone jack and the 8-ohm speaker jack at the rear of the chassis. Rewiring the jack and grounding the output transformer as shown does the trick.


ham radio

W6SAI's Antenna Books

Bill Orr's Newest **WIRE ANTENNAS** for Radio Amateurs

This 192 page book describes over 40 horizontal, vertical, and multi-band trap antennas. Invisible antennas for apartment houses, high gain beam antennas. Covers novice antennas, tuners and ground systems. It's all here in this exciting new book by "the antenna expert."

Only \$3.95 ppd.

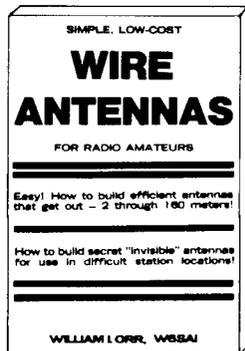

The "bible" on Quads

ALL ABOUT CUBICAL QUAD ANTENNAS

Long considered "THE BOOK" on Quads this latest edition has more information on these popular antennas than you will find anywhere else. Everything you need to design, build and adjust your Quad for top performance.

- Revised gain figures for Quads
 - Delta Quad, Swiss Quad, Birdcage Quad
 - Analysis of Quad vs. Yagi — which is best?
 - Miniature Quad construction and performance
 - Monster Quads — power gains up to 14!
 - Correct dimensions for single and multiband Quads, 6 thru 80 meters
 - Improved Tri-Gamma match feeds tri-band Quad efficiently with one line
- PLUS . . . Exhaustive detail on every aspect of quad antennas

Only \$3.95 postpaid

The complete reference on beams **BEAM ANTENNA HANDBOOK**

For many years the "BESTSELLER" on beam antennas, this handbook covers all areas of the subject, both theory and practice.

This new fourth edition has been updated to insure that the reader has the very latest information available.

It includes many special features such as:

- Correct dimensions - 6 thru 40 meters
- Are 40 meter compact beams worth the effort?
- Exclusive 25 year bibliography of important beam antenna articles

Whether you plan to build or buy — DX or rag chew — you need this book

Just \$4.95 Postpaid



comtec

BOOKS

Greenville, New Hampshire 03048

New for FM'ers

Scanner-Monitor Servicing Data

Contains comprehensive servicing data for 30 of the most popular UHF and VHF receivers now in use, including B & K, Browning, Johnson, Midland, Pace, Pearce-Simpson, Penneys, Realistic, Sonar, and Teaberry. As the first guide ever released for scanners and monitors, it is an invaluable aid for service technicians. Its last-minute information includes schematics, voltages, alignment, parts lists, crystal formula data, pictorial presentations, and general troubleshooting information.



\$4.95 Postpaid

HANDBOOKS We have all three



Radio Handbook, 19th Edition

by William I. Orr, W6SAI

Latest updated edition of this famous handbook which is the standard for engineers, technicians and advanced amateurs. Explains in detail how to design and build all types of radio equipment, RTTY circuits, latest semiconductor and computer circuitry. 896 pages; hardbound.

Only \$14.95

The Radio Amateur's Handbook

ARRL Staff

The standard reference for the radio amateur. Latest 1973 edition covers everything from the basics to such new areas as FM and slow-scan TV. The largest selling technical book ever published.

702 pages, softbound

Only \$4.50

RSGB:

Radio Communication Handbook

Amateur Radio's most complete technical reference. This book covers virtually every phase of radio theory and practise in very complete and useful detail. Whether you use HF or VHF, SSB or RTTY you need this handbook.

832 pages, hardbound

Just \$12.95

SPECIAL HANDBOOK PACKAGE

All 3 for just \$27.50

Save nearly \$5.00

CLOSEOUT SALE!

A SPECIAL PURCHASE ALLOWS US TO OFFER THE 18TH EDITION (JUST NOW SUPERSEDED) OF W6SAI'S RADIO HANDBOOK (SEE ABOVE) FOR ONLY \$7.95 WHILE THEY LAST.

comtec

BOOKS

Greenville, New Hampshire 03048

integrated-circuit

audio oscillator

This tunable wide-range
solid-state
audio oscillator
covers the
frequency range from
15 Hz to 40 kHz

Hank Olson, W6GXN, Box 339, Menlo Park, California 94025

For years I have had, sitting on the floor beside my workbench, a fine old Hewlett Packard Model 300 harmonic wave analyzer. It never was really used much because more modern wave analyzers were available at work which required less nulling and twiddling. The sheer beauty of the old HP-300 in its huge varnished oak cabinet was the only thing that prevented its being scrapped out.

Finally, in desperation for more work-shop space, the HP-300 was reduced to its component parts and carefully sorted into the various bins that make up my junk box. The cabinet was even used — as firewood (it turned out to be oak veneer). The largest and nicest component remaining was the dial assembly, drive mechanism and dual-variable capacitor unit. This trio had originally been the tuning of the HP-300, part of a Wien bridge oscillator covering 20 kHz to 40 kHz.

The more I looked at this marvel of mechanics, the more I conjured up pictures of an all solid-state audio oscillator built around it. One fine day, the design pieces — tuning assembly, cabinet, and integrated circuits — all fit together into a generator I have sentimentally called the HO-200. The original HO-200 is shown in fig. 1 with its old HP-300 dial (turned

down to remove the original etched calibration, and so it would fit on the front panel of the Bud C994 cabinet).

Since few amateurs are likely to have an old HP-300 tuning assembly, work was undertaken to build a second HO-200 that used readily obtainable components. The dual tuning capacitor for the second unit is made by the English firm of Jackson Brothers, Ltd., and is available here.* The vernier drive was made up from an old National *Velvet Vernier*, originally stripped from a tuning unit of a surplus transmitter. Such vernier drives are quite common and are integral parts of the National ACN and MCN dials. The basic planetary drives are also available as National parts AN-250 or AVD-250. The original dial of the vernier drive was discarded and a 5-inch aluminum disc fabricated to replace it. The finished dial is very similar to that of that used on the original HO-200, as can be seen in fig. 2.

the circuit

The HO-200 circuit (fig. 3) uses modern integrated circuits for its gain blocks. The $\mu A740$ of Fairchild is an operational amplifier in monolithic form which has fet inputs. The fet input feature allows the use of the large resistance values necessary when you design for variable-capacitor tuning of a Wien bridge.



fig. 1. The original HO-200 audio oscillator used a tuning dial from an old HP-300 harmonic wave analyzer.

The typical input impedance of a $\mu A740$ is 10^{11} ohms.

A low output impedance is provided by combining the $\mu A740$ with a Motorola MC1438R op amp follower. This power IC is packaged in a small diamond case



fig. 2. New HO-200 audio oscillator uses readily available parts.

for heat dissipation. The output impedance of the MC1438R is only 10 ohms, so it is capable of putting out considerable current. The MC1438R is used, as it was intended to be used, *inside* the closed loop with the op amp. (That is, the feedback to the top of the bridge is from the output of the MC1438R rather than from the output of the op amp alone.)

The power supply, which provides plus and minus 15 volts, also uses an IC — a dual regulator. The Motorola MC1468G assures that the oscillator is supplied a pair of *equal*, well-regulated voltages. The 2N5191 and 2N5194 transistors associated with the MC1468G in this dual-regulator circuit pass the major part of the current, as is done in most IC regulator circuits.


The non-linear resistance which is used to stabilize the amplitude of oscillation is not a lamp bulb, as is most common in

*The Jackson Brothers 5084/2/518H dual 518-pF tuning capacitor is available from M. Swedgal, 258 Broadway, New York, New York 10007. The price is \$5.00.

Wien bridge oscillators. Instead, a thermistor is used. Of course, since a thermistor *decreases* resistance as it is heated, it must be placed in the top leg of the bridge. This is just the opposite of the lamp bulb, which *increases* resistance with temperature and must be placed in the bottom leg of the bridge. This difference is illustrated in **fig. 4**. Other such uses of a thermistor in a Wien bridge is described in references 1, 2 and 3.

Centralab PA-300 and two PA-0 sections. The two switch wafers were spaced about 2-3/4 inches apart to allow room for the resistors. These ceramic wafer-switch sections appear to be of sufficiently good insulation for use with the high values of resistance involved. If you use series resistors as I did, teflon or ceramic standoff insulators could be used for additional terminals.

Since the common terminal of the

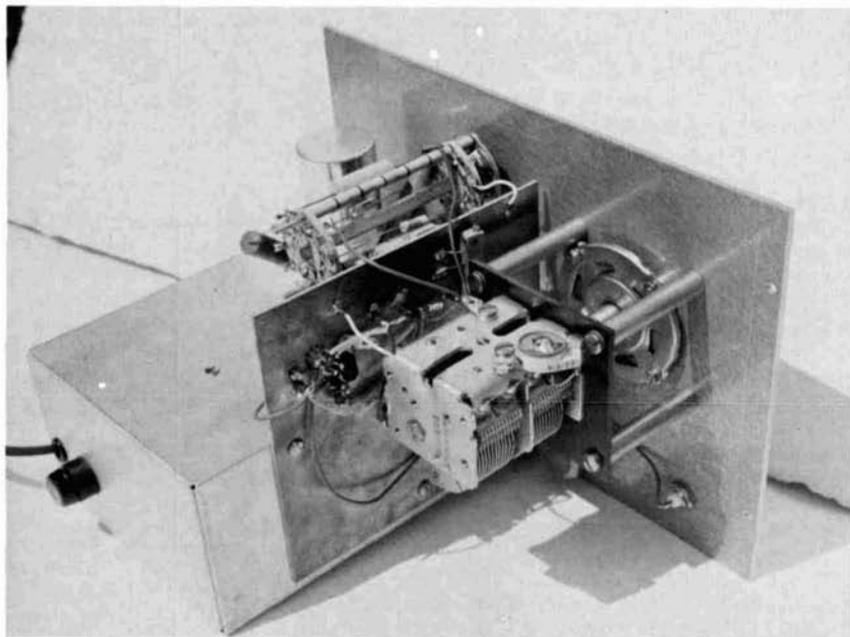

Inside view of the audio oscillator showing the tuning capacitor, range switch and copper-clad board used as a ground plane.

construction

The ranges that the HO-200 will cover are 15 to 200 Hz, 150 Hz to 2 kHz, 1.5 to 20 kHz, and 3 to 40 kHz. Range switching is accomplished by changing resistance values in the positive feedback side of the bridge. It is important to use 1% resistors here; I used deposited-carbon types. I used some series pairs of resistors to make up resistance values in order to avoid buying special values.


The resistors were mounted by soldering them to the wafer terminals of a two-wafer switch assembly made up of a

dual tuning capacitor is *not* grounded, it must be mounted in such a way that it floats above ground. I accomplished this by mounting the tuning capacitor body on a square of phenolic, and using an insulated shaft coupling for tuning. The phenolic was mechanically supported by four two-inch spacers screwed to the front panel of the HO-200.

The actual oscillator circuitry was built on a piece of copper-clad laminate, such as is used to fabricate etched-circuit boards. In this case, double-sided copper-clad board was used. The part of the

board that is above and next to the chassis is of special interest. One side of the laminate is at -15 volts and serves as a heat sink for U2. This "hot" portion of one side of the double-sided copper-clad

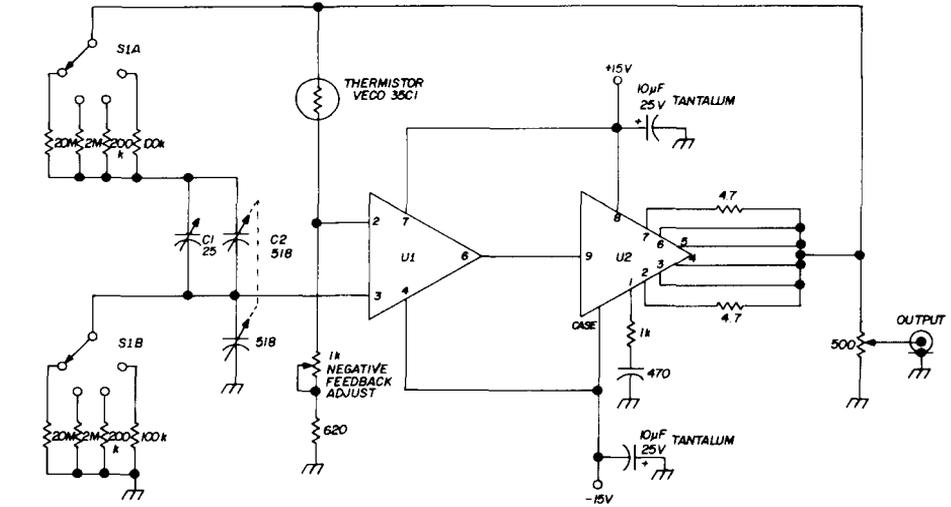at ground potential and is the side toward the tuning capacitor where the bulk of circuitry is mounted. Several small insulated standoffs are used to support components on the grounded side of the



- C1 4.5 - 25 pF trimmer capacitor
- C2 Dual 518-pF tuning capacitor (Jackson Brothers 5084/2/518HO)

- U1 Fairchild μ A740C, Signetics NE536T, National NH0042C or Intersil ICL8007C
- U2 Motorola MC1438R or MC1538R

fig. 3. Circuit of the solid-state Wienbridge audio oscillator uses two ICs. U1 is a high input impedance operational amplifier; U2 is a low-impedance output op amp follower.

laminate is isolated from the lower portion (which is bolted to the chassis) by a strip of insulation where the copper foil was peeled off. This is easily done with a rule and an X-acto knife or razor blade.

The other side of the board is entirely

board; they are fixed to the board by wetting their metal bases with solder and soldering them to the copper-foil ground plane. As can be seen from the photo of the inside of the HO-200 there are really very few components to mount; there-

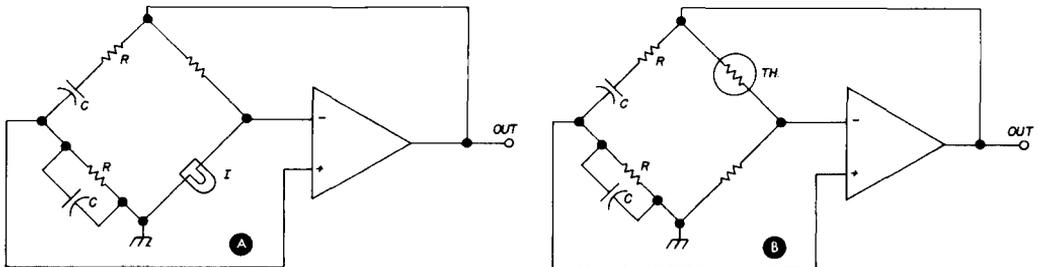


fig. 4. Use of nonlinear feedback elements in the Wien bridge circuit. The circuit in (A) uses the traditional incandescent lamp. The circuit in (B) uses a thermistor. See text.

fore, an etched circuit board was not deemed necessary.

There is one more consideration that must not be overlooked. Because the common terminal (body) of the dual tuning capacitor floats above ground, it has some finite capacitance to ground — measured to be about 10 pF in my unit. Since this is effectively in shunt with the parallel R-C branch of the bridge, a similar capacitance must be added across the tuning capacitor in the series branch

adjusted by means of the trimpot in the negative feed-back side of the bridge.

The regulated power supply is entirely located on the underside of the 5x7 chassis. This is to confine 60 Hz *electric* fields so that they will not be picked up by the high impedance circuits in the Wien bridge. One electrolytic, the positive supply filter capacitor, protrudes through the top of the chassis; but its can is grounded and so has no external 60 Hz field on it. An *aluminum* 5x7 chassis is

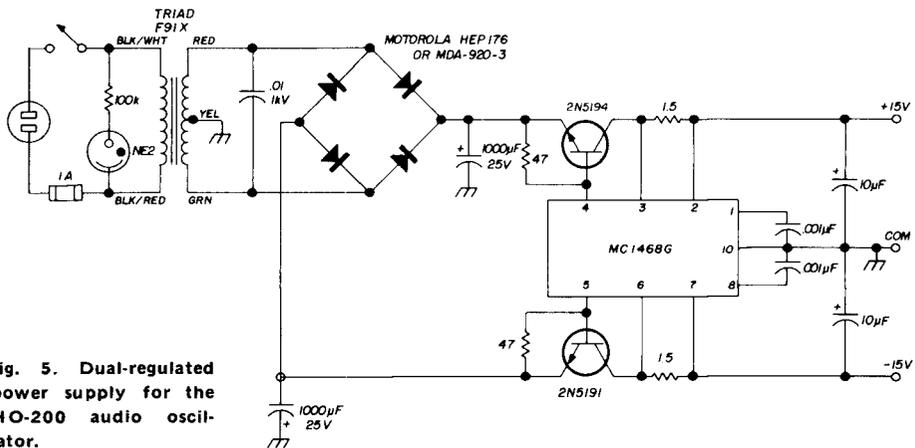


fig. 5. Dual-regulated power supply for the HO-200 audio oscillator.

of the bridge. C1 is a variable trimmer for this purpose, and should be set at about half capacitance for a start.

With the tuning dial at lowest frequency (x10 scale), measure the output voltage. Then tune to maximum frequency (x10 scale) and adjust C1 to give the same output voltage reading. The idea here is that 10 pF stray capacitance will not be much (2%) unbalance out of 518 pF at the low-frequency end (maximum capacitance), but will upset the matching of capacitance when the tuning capacitor sections are at their minimum (maximum frequency end). Therefore, C1 is best adjusted at the high-frequency end.

There is one other adjustment that can be made to the HO-200. With the output pot at maximum, you should see about 16 volts p-p at the output jack. If this amplitude is some other value, it may be

adequate here since we are only concerned with *electric* fields (not magnetic fields, too). If you want to see the great sensitivity of the circuit to stray 60-Hz fields, try operating the HO-200 out of its cabinet on the X1 scale. You will note (especially near 60 Hz and 120 Hz) severe beat phenomenon and a generally hopeless mess of waveforms.

references

1. R. Fulks, "High Performance, Low Cost Audio Oscillator with Solid-State Circuitry," *GR Experimenter*, August-September, 1962, page 15.
2. I.C. Zero, "Solid-State Wien Bridge Audio Oscillator," *Audio*, July, 1965, page 19.
3. H. Olson, "Dual Op Amp Makes Simple Sine-Wave Generator," *The Electronic Engineer*, August, 1971, page 70.

ham radio

NOW YOU CAN TRANSMIT WITHOUT TUNING!



That's right! With **SWAN's NEW FULLY SOLID-STATE TRANSCEIVERS**, there's no complicated or touchy tuning process required. You simply enjoy smooth positive dialing action of a single dual-ratio planetary control to select your frequency, while reliable broadband circuits take care of the rest. There's no tedious fine adjustments or "tweaking" to mess with—it's all automatic!

Swan was the first to provide a low cost single sideband transceiver the average ham could afford. Again, Swan leads the field with "state-of-the-art" concepts!

Tuning's just part of the great adventure you'll discover when operating one of these rugged, yet stylish, new units. For instance, you'll experience the pleasures of a built-in VOX and variable controlled noise blanking. There's a minimum of front-end overload, distortion and cross-modulation. You'll find an IF derived AGC, a 25 KC calibrator, semi-CW break-in with monitor, plus WWV receive and selectable sideband operation. And all controls are out front within an easy reach.

There's more! Now you won't have to worry about burning out your final stage. These transceivers are engineered to give infinite VSWR protection from an open to a short circuit. And the receiver section uses the latest practical state-of-the-art devices including FET's, IC's and operational amplifiers. You have your choice of 15, 100, or 200 watts P.E.P. in models designed for 12 volt DC operation across the entire 80 thru 10 meter ham band. Compatible AC power supplies and a selection of style-matched accessories are available to update your station.

CHOICE OF 3 MODELS:

SWAN SS-15 , 15 watt P.E.P.	\$579.00
SWAN SS-100 , 100 watt P.E.P.	\$699.00
SWAN SS-200 , 200 watt P.E.P.	\$779.00

ACCESSORIES INCLUDE:


SWAN PS-10 , 115V AC power supply for SS-15/SS-100	\$ 89.00
SWAN PS-20 , 115V AC power supply for SS-200/SS-100/SS-15	\$139.00
SWAN SS-1200 , 1200 watt P.E.P. Linear Amplifier (Tube Type)	\$299.00
SWAN SS-208 , External VFO	\$159.00
SWAN 610X , Crystal Controlled Oscillator	\$ 53.95
SWAN SS-16B , Super Selective Filter	\$ 79.95
SWAN WM-1500 , 4 scale in-line Wattmeter	\$ 49.95

Get the full story in **SWAN's** new 1973 catalog—send for your **FREE** copy today!



SWAN
ELECTRONICS
A subsidiary of Cubic Corporation

305 Airport Road • Oceanside, CA 92054

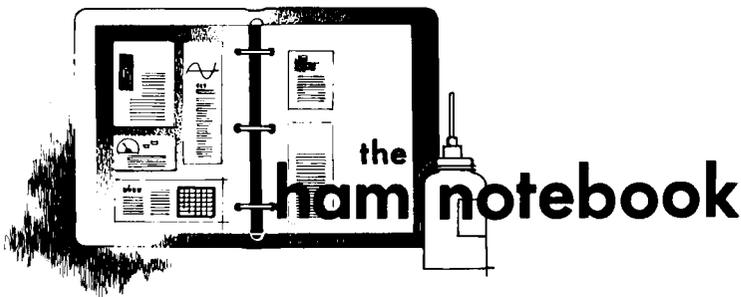

logic test probe

As a computer engineer in a small company, I sometimes have to build my own test equipment. One of the most useful pieces I have come up with for trouble-shooting digital circuits is a test probe with memory that responds to either positive or negative going pulses and/or levels. Since I work only with TTL logic, the probe is designed to work with this. Because of the memory function, it spots the presence of single control pulses with just one operation of the circuit

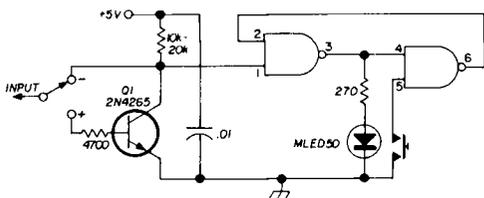


fig. 1. Circuit diagram of the logic test probe. Use IC logic of the same type you are testing, RTL, DTL, TTL, etc.

under test, while with a scope I have to trigger the circuit many times to clearly determine the presence of the control pulse. In addition, a high or low state is easily seen, simply by touching the desired point. It may be hard to believe, but I can go all day without ever turning the scope on.

There are two switches a Memory Disable switch and a Pulse Polarity switch. Memory Disable is a push-button that resets the memory to the low state when depressed. Pulse Polarity is a toggle

switch located out of the way and selects whether the probe responds to a high-level or pulse (+5v) or a low-level or pulse (ground).

The probe circuit, fig. 1, is simplicity itself, one TTL quad NAND integrated circuit, three resistors, one NPN Transistor, an LED and two switches. I used a 7400 integrated circuit, a motorola MILED 50 LED and a 2N4265 transistor. All parts are miniature and of high quality for reliable operation. Too much money has been spent for inexpensive parts to build test equipment that the owner ends up not trusting. Construction depends to a large degree on what you have on hand. I used a part from an old oscilloscope probe, a piece of 3/4-inch plastic tubing, and the plastic barrel from a ball-point pen with a piece of threaded rod melted into it. Conscientious workmanship is in order if you do as I did, and glue the two major parts together.

To use, connect the two power leads, and with the polarity switch set for positive pulses, touch the tip to the positive supply. The light should go on. Touching the tip to ground should not affect the light and only depressing the memory disable switch will let the light go off. With the polarity set to negative, touching the probe to the power supply should not cause an indication. The only way to get the light to light is to momentarily ground the probe tip. The only way to get the light off is to disable the memory.

In use, the memory switch can be held depressed and the probe will respond

only to the level touched. If an oscillator output is probed the light will dim when memory is disabled, and brighten to full brightness when the memory disable is released. This project has proven to be a real time saver and well worth the few

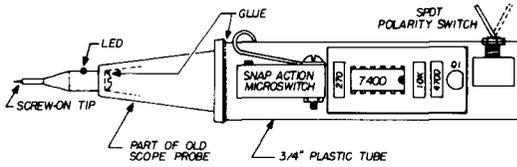


fig. 2. Construction of the logic test probe.

hours put into building it. While not everyone is deep into TTL, the applications are increasing, as I see digital repeater controls, digital circuits in RTTY applications, digital clocks, digital counters, digital volt meters and many others. This logic probe just might be the vtm of the digital world.

Bill Rossman

frequency pre-scaler

There are a couple of things which the article on frequency scaling by F.E. Emerson in the September, 1972, issue didn't point out which may be of interest to some readers. I have been using the Fairchild 95H90 IC in a remarkably similar prescaler for some time with excellent results. My particular circuit seems to yield a little more sensitivity than Mr. Emerson observes, but perhaps I just happen to have a hotter 2N5179 in the front end.

Mr. Emerson may not have considered the consequence of using this scaler with

counters that already have a good high-frequency capability such as the Heathkit IB-1101. Because the prescaler output is a square wave with quite good rise time, a counter which can count to 60 MHz or more can erroneously count the second or third harmonic of the scaled frequency. The count is reliable — it's simply wrong and is not the fault of the scaler. The simple solution to this problem is to roll off the frequency response of the scaler output. In my own prescaler I use a simple L-section filter to roll off frequencies above 30 MHz. This allows the scaler to be used up to 250 MHz and eliminates the possibility of false counting at the scaled frequency. A schematic of my own scaler, for those who are interested, is shown in fig. 3.

Ernie Guerri, W6MGI

telescoping tv masts

The majority of tv-type antenna masts currently on the market use a cotter pin under the bottom of each section that the upper section rests on. The cotter pin fits into a small slot in the upper section. However, there's always the possibility that the upper section hasn't seated properly during installation; if this happens the antenna will "windmill" back and forth, eventually wearing through the cotter pin.

As a safety measure a small hole should be drilled through *both* mast sections and an additional cotter pin installed. This prevents any rotation and could preclude renting a 40-foot ladder later to correct the problem.

Richard Mollentine, WAØKKC

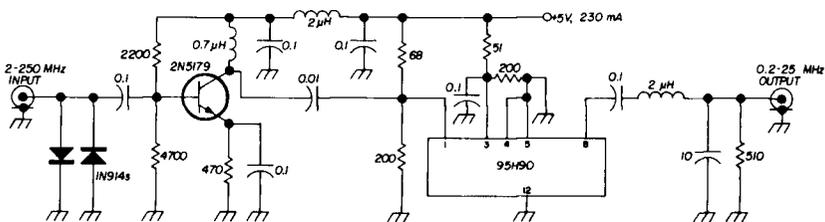


fig. 3. Frequency scaler has sensitivity of 20 mV at 175 MHz, 40 mV at 220 MHz and 90 mV at 250 MHz. All capacitors are CK06 with shortest possible leads. All unmarked pins on the 95H90 IC have no connections (do not use as tie points).

new products

rf power and vswr meter



The new ThruLine® model 4342 Dual Wattmeter-VSWR Monitor displays the three prime rf transmission measurements at once on a single meter face: Forward and reflected power are indicated by individual pointers and vswr is monitored on a third scale from the intersection of the two power pointers.

Unlike most VSWR meters, the model 4342 does not require *any* adjustments to full-scale deflection, or any switching before vswr readings can be taken: The

entire set of three transmission parameters is read out simultaneously during normal rf operations.

Power and frequency range of the new Bird Dual Wattmeter-VSWR Monitor depend on two plug-in elements selected from more than eighty choices available with the company's popular ThruLine Model 43: Full scale power levels at $\pm 5\%$ accuracy range from 10 to 5000 watts for forward indication and 1 to 500 watts for reflected, in discrete frequency bands from 2 to 2300 MHz (for increased resolution, the reverse power element is ten times more sensitive than the forward power element). Model 4342 Insertion vswr in 50-ohm systems is a low 1.035 to the point of measurement. A choice of QC Quick-Change connectors permits mating with N, BNC, TNC, UHF, C, SC, LC, HN, LT, GR type 874 and 7/8" EIA lines without the need for performance-degrading adapters.

The new Bird Dual Wattmeter-VSWR Monitor is a portable instrument weighing only 5½ lbs. Model 4342 price (with female N connectors) is \$265. Plug-in Elements are \$30 to \$75 (two required).

For more information, write to Bird Electronic Corporation, 30303 Aurora Road, Cleveland, Ohio 44139, or use *check-off* on page 94.

printed-circuit service

A valuable new service is now being offered to amateurs who build their own equipment. Most construction articles in the amateur magazines call for a circuit board. In some cases the layout is provided, but few amateurs are equipped to fabricate their own boards conveniently at home. For those who would rather concentrate on the electronics than on circuit boards, Mac McClaren, W8URX, is offering printed circuit boards, drilled and ready for parts mounting.


If he already has the artwork for the board you want, he can deliver a finished board in ten days. He offers two-week service on new items (from current magazines). He is also able to make boards

from your artwork in three weeks — write for a quote and full instructions.

All work is offered on a money-back guarantee. All shipments fob Cleveland. All boards use the very best material, G-10 epoxy, 1/16" thick with 2-ounce copper; all holes are drilled with solid carbide bits to assure burr-free holes.

For more information on this unique printed-circuit service, write to D.L. McClaren, W8URX, 19721 Maplewood Avenue, Cleveland, Ohio 44135, or use *check-off* on page 94.

heat sink

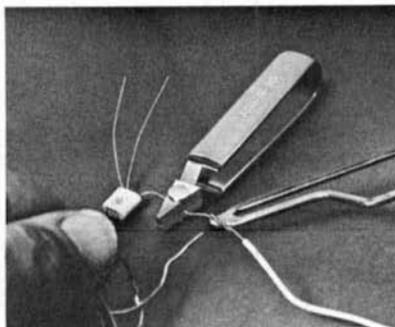

Xcelite has just introduced the no. 80 heat sink for absorption and dissipation of heat in soldering operations where adjacent, delicate electronic parts might be damaged by overheating. The manufacturer states that for optimum heat absorption and dissipation the jaws of the no. 80 heat sink are made of copper, with nickel plated surfaces to prevent solder adhesion. The spring-loaded gripping surfaces will not slip, yet have a smooth finish to prevent scratching fine wires. Exceptionally compact, this heat sink is 3-1/4-inches long in length and weighs only 1/2 ounce. An insulating cushion grip permits burn-free handling.

The no. 80 heat sink, made in the United States to highest quality standards, is now available through Xcelite's nation-wide local distributors at a list price of \$2.40. Product Bulletin 5721 contains additional information, and may be obtained by writing to Xcelite Incorporated, Orchard Park, New York 14127, or by using *check-off* on page 94.

INCREASE YOUR TALK POWER!

PROVEN ON-THE-AIR PERFORMANCE



MODEL ACA-1

\$49.95 KIT

ASSEMBLED

\$69.95

MODEL ACA-1 AUDIO COMPRESSOR features 45 DB compression range ■ Flat 20-20,000 Hz response ■ Extremely low distortion ■ Front panel compression meter and in/out switch ■ Accepts both high and low-impedance mikes ■ Easily installed in mike line ■ 110-volt a.c. or 12-volt d.c. operation ■ Only 5" W x 2 1/4" H x 4 1/2" D.

MODEL ACP-1

\$24.95 KIT

ASSEMBLED

\$34.95



MODEL ACP-1 COMPRESSOR-PREAMP has 30 DB compression range ■ Flat 20-20,000 Hz response and low distortion ■ Designed for high-impedance mikes ■ Easily installed in mike line ■ 9-volt battery operation ■ Only 4" W x 2 1/2" H x 3 1/2" D.

IDEAL FOR TAPE RECORDERS!

Try one of these compressors as an automatic recording-level control. Used by recording studios, schools, and radio-tv stations. Great for p.a. systems, too!

3-CHANNEL WWV RECEIVER

(5, 10, and 15 MHz)



\$74.95 KIT

ASSEMBLED

\$99.95

0.25 microvolt sensitivity ■ Crystal controlled ■ 110-volt a.c. or 12-volt d.c. operation ■ Compact size only 4 1/2" W x 2 1/2" H x 5 1/2" D.

Send check or money order, plus \$1.50 for shipping anywhere in U.S.A. California residents add 5% sales tax.

DEALER INQUIRIES INVITED



CARINGELLA ELECTRONICS, INC.
P.O. Box 327 □ Upland, California 91786
Phone 714-985-1540

400% MORE AVERAGE SSB POWER OUTPUT

USE A **MAGNUM SIX**
THE QUALITY R F SPEECH PROCESSOR



Collins-Heath.....\$139.95
Drake T4X/T4XB..\$154.95
Drake TR3/TR4...\$159.95
Yaesu.....\$139.95
Kenwood.....\$139.95
Add 5% Tax in Washington

- 4 TIMES THE SSB POWER ON ALL BANDS
- ADDED PUNCH FOR PILE UPS
- EXCELLENT VOICE QUALITY
- SPLATTER FREE, NARROW BAND OUTPUT SIGNAL
- SOLID STATE DESIGN
- PUT YOUR TRANSMITTER TO WORK FOR THE FIRST TIME IN ITS LIFE. POWER UP WITH A MAGNUM SIX FOR MORE ADDED POWER PER \$ THAN ANY OTHER METHOD!

Send for FREE Brochure

Communication Technology Group
31218 Pacific Highway South
Federal Way, Washington 98002



A Division of Bico Systems Inc.

NES

NURMI ELECTRONIC SUPPLY

1727 Donna Road · West Palm Beach, Fla. 33401

New Silver Plated Connectors

	1-9	10-49	50-99	100+
PL-259	.50	.45	.40	.34
SO-239	.50	.45	.40	.34
UG-175/U	.19	.15	.13	.12
UG-88/U	.60	.55	.50	.44
UG-1094/U	.60	.55	.50	.44

DIODES

HEP 170 2 1/2 Amps	1000V	.30	\$25/100
1N4004 1 Amp	400V	.15	\$13/100
1N4007 1 Amp	1000V	.20	\$18/100
1N2135 60 Amps	400V		\$3.00

Belden Coax — Factory Fresh!!!!

No. 8240	RG-58/U07/ft.
No. 8259	RG-58A/U07 1/2/ft.
No. 8219	RG-58A/U Foam08/ft.
No. 8237	RG-8/U15/ft.
No. 9251	RG-8A/U18/ft.
No. 8214	RG-8/U Foam18/ft.

Transformers — Sealed Case, 4 Screw Mount

PRI: 105/115/210/220 V	UTC No. H-134	
SEC: 6.3Vct @ 10A	5 Lbs.	\$5.00
PRI: 115V		
SEC: 800Vct @ 200Ma	12 Lbs.	\$8.00
PRI: 115V		
SEC: 6.3V @ 18A, 2.5V @ 10A	9 Lbs.	\$7.00

WE GUARANTEE WHAT WE SELL!!!!

We ship UPS whenever possible. Give street address. Include enough for postage excess refunded in cash. Florida residents include 4% tax.

ic keyer



The new Palomar Engineers IC Keyer has been given new features while retaining those that have made it popular over the years. Its relay output suits it to key all Swan, Drake, Tempo, Yaesu, Clegg, Collins, Heath, etc., and the relay is compensated to prevent dots from getting short at high keying speeds.

Low impedance ICs are used throughout to minimize rf pickup and they are heavily bypassed to make the keyer practically rf proof. The exclusive blocking-oscillator pulse generator gives instant start and never produces an unwanted dot or dash.

Up front is the precision Brown key mechanism that is adjustable for dot and dash travel and tension. On the rear deck is an input for receiver audio so that both the received signal and the keyer monitor tone can be heard on the built-in speaker or on headphones.

The unit sells for \$87.50 postpaid in USA. For more information, write Palomar Engineers, Box 455, Escondido, California 92025, or use *check-off* on page 94.

tool kit brochure


A 16-side brochure describing field engineer tool kits and cases has been published by Jensen Tools and Alloys. The brochure describes six professional tool kits, each engineer-designed to do a particular job. Included in the publication are the JTK-17 Field Engineer Kit, which contains over 100 tools in an executive attache case; the JTK-2 Electronic Technician Kit for industrial personnel; the JTK-16 Compact "Detective" Kit, which

contains 30 multi-purpose tools in a zipper case; the JTK-27/37 Electronic Lab Kit, a complete portable electronics tool kit with test instruments in two attache cases; the JTK-90 Instrument Repair Kit, emphasizing watchmakers' tools; and the JTK-80 Electronic Technician Roll-Pouch Kit, a lower priced kit for technicians, students and kit builders. Kits range in price from \$44.50 for the JTK-80, to \$555.00 for the JTK-27/37.

A variety of cases sold separately are described and range from a canvas-like roll-pouch to the Jensen Extra-Deep Deluxe Case which features a full six-inch depth and two removable tool pallets. A total of nine cases are presented.

To receive a copy of this brochure, contact Jensen Tools and Alloys, 4117 N. 44th Street, Phoenix, Arizona 85018, or use *check-off* on page 94.

450-MHz Yagi

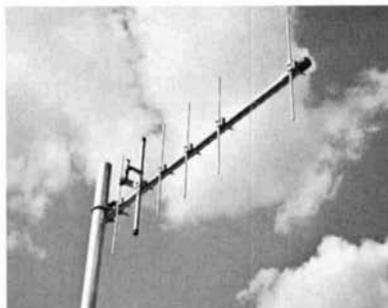

Cush Craft has just introduced a new six-element, rear-mount 450-MHz Yagi for amateur fm repeater operation. It can be used for control links and stations for monitor applications and access to 450-MHz repeaters. It is priced at \$10.95 amateur net and exhibits 10-dB gain. It has direct 50-ohm Reddi Match feed with built-in coax fitting. The boom is 35" long and overall weight is 3 lbs. Model No. A449-6 is available through all Cush Craft distributors. The antenna is also available for commercial service.

For more information, write to Cush Craft, 621 Hayward Street, Manchester, New Hampshire 03103, or use *check-off* on page 94.

SSB CONVERTER CV-591A: Get upper or lower sidebands from any rcvr. OK gtd. w/book \$137.50
 SP-600(*) RECEIVER 0-54-54 MHz continuous, overhauled, aligned, grtd, w/book 250.00

BRAND NEW FREQ-SHIFT TTY MONITOR

NAVY OCT 3: FM Receiver type, freq. range 1 to 26 MHz in 4 bands, cont. tuning. Crystal calib. Reads up to 1500 Hz deviation on built-in VTVM. Cost \$1100.00 each! In original box, with instruct. book & cord. fob Mariposa, Cal. Min. signal needed: 15 mw. Shpg wt 110 lbs 49.50

HIGH-SENSITIVITY WIDE-BAND RECEIVER

COMMUNICATIONS • BUG DETECTION
 • SPECTRUM STUDIES

38-1000 MHz AN/ALR-5: Consists of brand new tuner/ converter CV-253/ALR in original factory pack and an exc. used, checked OK & grtd main receiver R-444 modified for 120 v. 50/60 Hz. The tuner covers the range in 4 bands: each band has its own Type N Ant. input. Packed with each tuner is the factory inspector's checkout sheet. The one we opened showed SENSITIVITY: 1.1 uv at 38.4 mhz. 0.9 at 133 mhz. 5 at 538 mhz. 4 1/2 at 778 mhz. 7 at 1 ghz. The receiver is actually a 30 mhz IF ampl. with all that follows, including a diode meter for relative signal strengths: an atten. calibrated in 6 db steps to -74 db, followed by an AVC position; Pan., Video & AF outputs; switch select pass of ±200khz or ±2 mhz; and SELECT AM or FM! With Handbook & pwr. input plug, all only 375.00
 CV-253 Converter only, good used w/book 89.50

30 MHz PANADAPTER OK grtd \$137.50

Meas. Corp. #59 Grid Dipper 2.2-420 MHz, 75.00

NEMS-CLARKE #1670 FM Rcvr 55-260 MHz like new 275.00

WVW Rcvr/Comparator 2 1/2-20 MHz, w/scope 250.00

RECEIVER/COMPARATOR FOR 60 KHz WVVL standardizes to 1 part in 10 billion with inexpensive oscillators 495.00

Attention!

Buyers, Engineers, advanced Technicians:

We have the best test-equipment & oscilloscope inventory in the country so ask for your needs . . . don't ask for an overall catalog . . . we also buy, so tell us what you have. Price it.

R. E. GOODHEART CO. INC.

Box 1220-HR, Beverly Hills, Calif. 90213

Phone: Area Code 213, Office 272-5707

IDENTIFIER FOR FM REPEATERS

ID-403

- AUTOMATIC TIMING
- PLUG-IN MEMORY
- ALL SOLID STATE
- 117Vac POWER SUPPLY
- TONE BURST ENTRY OPTION

Complete, ready to go . . .
 \$199.50
 \$239.50 (with tone burst option)

WRITE FOR BROCHURE

GURTS ELECTRO DEVICES

BOX 4090 • MOUNTAIN VIEW, CALIF. 94040 • TEL. (415) 964 3136



GROTH-Type

COUNTS & DISPLAYS YOUR TURNS



- 99.99 Turns
- One Hole Panel Mount
- Handy Logging Area
- Spinner Handle Available

PRICES

	POST PAID
TC 2	\$7.00
TC 3	\$7.50
Spinner (S)	\$1.00
Add \$0.75 for Air or UPS	

Case: 2x4"; shaft 1/4"x3"
 Model TC2: Skirt 2 1/8"; Knob 1 1/8"
 Model TC3: Skirt 3"; Knob 2 3/8"

R. H. BAUMAN SALES

P.O. Box 122, Itasca, Ill. 60143

VHF-FM HEADQUARTERS FOR SOUTH FLORIDA

*Modify your Gladding 25
with our
Coincidence Detector*

- True FM Detector
- Improved Sensitivity
- Improved IF Gain
- Superior Squelch Action
- Install in just a few minutes

Complete G-10 epoxy board wired and aligned ready to install.

1 year warranty

\$19.95 ppd USA



\$349

Miida

DIGIPET 60/160

Here's the affordable professional grade counter you've been waiting for, to 160 MHz for just \$349.00 complete with scaler! And look at these features . . .


- Equiv. 8 digit display with 5 digit readout and display storage
- Overflow indicator
- Extremely compact (6.7" X 3.6" X 7.0") as shown above, with scaler, 4.5 lbs
- Both AC and DC operation (8 watts)
- Xtal stability: 1 part in 10⁶/ week
- Resolution: 1 Hz,
- Sensitivity 50 mV
- Full 1 year U.S. warranty
- Engineered & constructed for the professional.

All crystals for 2-meter fm equipment we sell: \$3.25 ea. Maximum ten day delivery.

In Stock: Standard Walkie-Talkies, Tempo Solid State Power Amplifiers.

EMPORIUM SOUNDS OF POMPANO
51 North Federal Highway
Pompano Beach, Florida 33060
305-782-3464

logic-tester probe

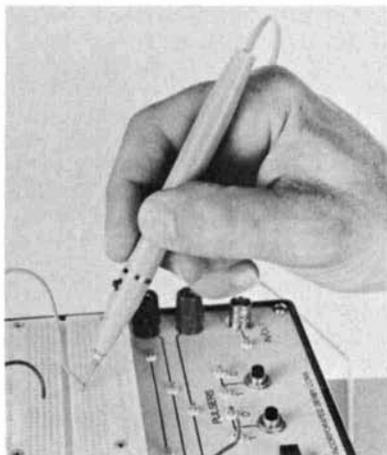

EL Instruments announced the addition to their product line of the LT-1, Logic Tester Probe. The LT-1 is a rugged, compact pencil type instrument used to determine logic levels. It operates from the dc supply of the system under test.

The logic levels are detected by an infinite life LED used as an indicator light. The LED is on at the (+) logic 1 level and off at the 0 level. The LT-1 is a high-impedance device, therefore there is no circuit loading. The frequency response is dc to 12 MHz.

The LT-1, complete with power leads, is available from stock for \$11.95. Complete information and quantity prices are available from EL Instruments, Inc., 61 First Street, Derby, Connecticut 06418 or by using *check-off* on page 94.

selective call systems

Bramco Controls Division of Lederex, Inc., offers an extensive line of selective calling encoders and decoders for attachment to mobile and base station fm equipment. The line includes units compatible with GE's Channel Guard, Motorola's Private Line and RCA's Quiet Channel selective-call systems. There are also many three, five and seven digit units compatible with the Touch-Tone systems becoming more popular daily on amateur repeaters.

The line includes a selection of mobile decoders which will activate headlights, the car horn or a latched-on signal lamp to indicate a received call while the driver is not in the vehicle. At the top of the line is a sophisticated mobile identifier system which informs the dispatcher — by means of lights and a digital readout — of the identity of the calling mobile and if the communication is routine or an emergency.

For more information on this complete line of selective calling systems write to Bramco Controls Division, Ledex, Inc., College and South Streets, Piqua, Ohio 45356 or use *check-off* on page 94.

bird wattmeter catalog

Available now is an eight-page supplement to the 1971 general catalog which lists over thirty new ThruLine[®] rf directional wattmeters, Termaline[®] rf load resistors, and a 100 watt attenuator added this year by Bird Electronic Corporation, manufacturer of instruments for rf power measurement.

Shown for the first time are 75-ohm wattmeters for uhf TV and 75-ohm loads, in addition to the usual 50-ohm equipment. The brochure introduces two new product lines: A 51,000 BTU/hour heat exchanger and an instant-output wide band 150 watt rf power source. Recognizing the substantial number of radio amateurs and boating enthusiasts in the communications industry, the supplement also shows the new economical Ham-Mate[®] and Marine-Mate[®] wattmeters.

Prices are included with equipment photos and performance specifications. General Catalog Supplement GCS-72 is available free from Bird Electronic Corporation, 30303 Aurora Road, Cleveland (Solon), Ohio 44139 or by using *check-off* on page 94.

ThruLine, Termaline, Ham-Mate and Marine-Mate are all registered tradenames of the Bird Electronic Corporation.

KW

ELECTRONICS
LIMITED

The KW2000B
the transceiver
with 160Meters

\$699 with spkr
and AC pwr supply



NOW in the USA

KW Electronics

DIVISION OF SYSTCOMS Inc

10 Peru St., Plattsburg, N.Y. 12901

F.C.C. EXAM MANUAL

The Original Test-Answers exam manual that prepares you at home for FCC First and Second class licenses. Includes Up-to-Date multiple choice tests and key Schematic diagrams. PLUS - "Self-Study Ability Test." -- ONLY: \$9.95 Postpaid.

COMMAND PRODUCTIONS P.O. BOX 26348-K
RADIO ENGINEERING DIVISION SAN FRANCISCO, CALIF. 94126

ACTIVE AUDIO FILTERS

CW: IC'S FOR SUPER HIGH PERFORMANCE


Get razor sharp selectivity
No impedance matching BW
(selectable) 180 Hz and
80 Hz Center frequency...
F = 750 Hz Skirts 60 db
down at 1/2F and 2F 4 op
amps, 2" x 3" PC Board
\$12.95 wired, tested,
guaranteed

LOW PASS:
Resistors set cutoff .5
to 20 kHz. Factory set
for 2.5 kHz; Input imp 1M;
Load > 2K; Gain = 1
Roll-off max 48db/oct, min
40 5 op amps, 2" x 3"

PC Board \$15.95 wired, tested, guaranteed

WRITE FOR FREE SPEC SHEETS! (DEALERS INVITED)

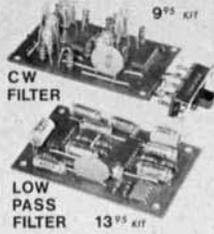MFJ ENTERPRISES P. O. Box 494
State College, Ms. 39762



STAR-TRONICS

**INDUSTRIAL AND GOVERNMENT
ELECTRONIC SURPLUS**

PARTS & PIECES FOR SCHOOLS, SHOPS, HAMS & HOBBYISTS
SEND FOR OUR LATEST ALL DIFFERENT
MONTHLY PICTURE CATALOG. NOW!

Box 17127, Portland, Ore. 97217

SPACE-AGE TV CAMERA KITS & PLANS



BE A PIONEER IN HOME TELECASTING! Build your own TV CAMERA. Model KT-1A, Series D, \$116.95 pp. Self-Service. Step-by-step construction manual. High quality. Connects to any TV without modification. Ideal for home, experimenters, education, industry, etc.

PHONE or WRITE for CATALOG.

DIAL 402-987-3771

Many other kits, parts and plans available including starter kits, focus/diff. coils, vidicon tubes, const. plans, etc.

1301 BROADWAY, N.W. **ATV Research** DAKOTA CITY, NEBR. 68731

LIMITED OFFER • NEW R-390 A/URR \$1395

The finest military digital receiver available. 5 to 32 MHz unused. In the original package with manual, accessories, and spare parts. Guaranteed. F.O.B. N. J. **MILITARY ELECTRONICS CORP.** 76 Brookside Dr., Upper Saddle River, N.J. 07458 (201) 327-7640

MINIATURE SUB-AUDIBLE TONE ENCODER \$14.95

Wired-Tested




- Compatible with all sub-audible tone systems such as Private Line, Channel Guard, Quiet Channel, etc.
- Glass Epoxy PCB, silicon transistors, and tantalum electrolytics used throughout
- Any miniature dual coil contactless reed may be used (Motorola TLN6824A, TLN6709-B — Bramco RF-20)
- Powered by 12vdc @ 3ma
- Use on any tone frequency 67Hz to 250Hz
- Miniature in size 2.5 x .75 x 1.5" high
- Complete less reed (Available in 33 freqs. for \$17.50 ea)
- Output 3v RMS sinewave, low distortion

Postpaid — Calif. residents add 5% sales tax

COMMUNICATIONS SPECIALISTS

P. O. Box 153, Brea, CA 92621

two time-zone 24-hour clocks

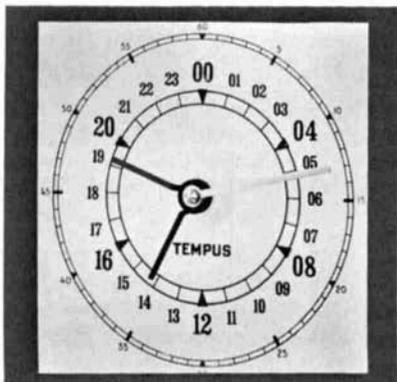

Tempus Instrument Corporation has introduced a 24-hour clock, powered by a high-quality four-jewel battery-operated clock movement made in West Germany. One regular C-size flashlight battery runs the clock for at least 18 months. The case is of scratch-resistant Acrylic material measuring 6 x 6 x 1/2 inches.

Three multi-colored hands permit simultaneous reading of hours and minutes 24 hours a day in *two* different time zones of the world. This feature makes the clock especially useful for amateur radio operators. Each clock comes with a hanger and with an aluminum bracket for use as a wall clock or desk clock.

Tempus also offers a similar model as a plain 24-hour clock with sweep second hand. All products are fully guaranteed for one year and sell for \$29.50. Additional information is available from Tempus Instrument Corporation, Villa Italia Center, Suite 594, 7200 West Alameda Avenue, Denver, Colorado 80226 or by using *check-off* on page 94.

radio shack catalog

Radio Shack's new 1973 electronics catalog features the company's complete line of experimenter's components, Realistic home entertainment products, audio equipment and Citizen Band equipment, Micronta test instruments, Archer antennas, and Archerkit and Science Fair electronic and hobby kits.

NEW 450MHz MOS FET PRE-AMP

HF 450 WIRED 29.95



150dB GAIN WITH 4.5DB NOISE FIG. SILVER PLATED G11 APOXY GLASS P.C. BOARD HAS LOW RF LEAKAGE OPERATING RANGE 406 TO 470 MHz SIZE 3 5/8 BY 1 1/8 INCHES WILL OPERATE FROM 10 TO 15 VDC

6T-HR-2 ADD 6 MORE XMIT FQS TO HR-2 (on A) KIT.....\$ 9.95 WIRED.....\$13.95
 HF-144U 17DB HI BAND MOS FET PRE-AMP KIT.....\$11.95 WIRED.....\$17.95
 HF-144H MOTRAC WIRED ONLY

HF-23 ADD 2 MORE XMIT TO HT 200 (H23 DCV DEW) KIT.....\$29.95 INCLUDES SWITCH, KNOB, P.C. BOARD and PARTS
 7F-HT 220 ADD SEVEN MORE XTALS TO HR TO YOUR KIT.....\$12.50 HF 220 (H23 FFV) TandRm COTLS @ \$ 1.00
 6F-220 SP ESCHUTCHEON \$ 6.50

WAIAL "ISO-TIP" CORDLESS SOLDERING IRON & CHARGER \$19.95

SPECIAL HR-2 or HR-212 WITH SCAN 2 and HR-2A \$229.95
 HF-144U PRE-AMP HR-212 \$259.95

CRYSTALS FOR HAM USE

HR-2 & 212	RECEIVE	\$3.99
	TRANSMIT	\$5.75
THR SCANNER	RECEIVE	\$3.99
MODAR (MOTOROLA)	RECEIVE	\$5.95
	OFF SET	\$7.95

ALL PRICES INCLUDE SHIPPING

Topeka FM Communications
 1313 E. 18 Terr. **Land Electronics**
 Topeka, Kansas 66607



The 180-page catalog, with more than half of its pages in full color, lists thousands of electronic items such as tubes, transistors, cables, tools, connectors, wire, plugs and adapters for amateurs, hobbyists, experimenters, technicians or anyone wanting a wide selection of parts, accessories and maintenance items.

Among the products being introduced as new for 1973 are stereo and four-channel amplifiers, receivers, adapters and tape decks; speaker systems, CB radios, Archerkits, Science Fair Lab kits, stereo radios, scanning monitor receivers and a miniature electronic calculator.

Catalog 227 is available free on request from any of Radio Shack's more than 1500 stores in all 50 states and Canada, or by mail from Radio Shack, Department R-26, 2617 West Seventh Street, Fort Worth, Texas 76107 or by using *check-off* on page 94.

crt terminals

A new data sheet describing the Series 200 Video Terminal Controllers, free-standing keyboards and monitors is available from Ann Arbor Terminals, Inc. The new literature emphasizes the application of Series 200 crt units in conjunction with, or as substitutes for hardcopy print-out terminals.

Features of the Series 200 equipment include noiseless operation, preview and editing capability, very high speed and exceptional reliability — features not available on electromechanical data capture terminals. Other features of Ann Arbor's line are compatibility with existing keyboards and data capture terminals and the capability for driving multiple standard TV sets or 525-line video monitors. There are many units in the line ranging from \$795 to \$1195 in single quantities.

For the new data sheet write to Ann Arbor Terminals, Inc., 6107 Jackson Road, Ann Arbor, Michigan 48103 or use *check-off* on page 94.

FROM YOUR COST CUTTER...

METERS!



5000 IN STOCK

FMeers: 0-Center 2 1/2" — \$3.95
Micro Amps 3 1/2" — \$4.95
Various Scales

Also tubes, transformers, semi-conductors relays, capacitors and test equipment.


STOP IN or WRITE for
Illustrated Catalog

BUDGET ELECTRONICS

2704 W. North Avenue, Chicago, Ill. 60647

Area Code 312 — 227-1676 or 227-0909

... THE BEST 2 METER CONVERTER

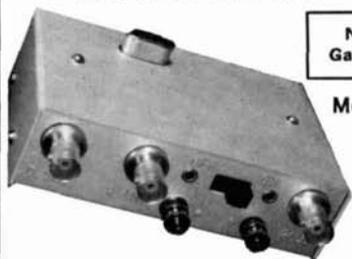

Now with
Gain Control

Model 407-A
\$49.95
ppd.

144-146 MHz in. 28-30 MHz out
or 146-148 MHz with a second crystal
available for \$5.95 each

A full description of this fantastic converter would fill this page, but you can take our word for it (or those of thousands of satisfied users) that it's the best. The reason is simple — we use three RCA dual gate MOSFETs, one bipolar, and 3 diodes in the best circuit ever. Still not convinced? Then send for our free catalog and get the full description, plus photos and even the schematic.

Can't wait? Then send us a postal money order for \$49.95 and we'll rush the 407-A out to you. NOTE: The Model 407-A is also available in any frequency combination up to 450 MHz (some at higher prices) as listed in our catalog. New York City and State residents add local sales tax.

VANGUARD LABS

Dept. R, 196-23 Jamaica Ave., Hollis, N. Y. 11423



250 MHz ELECTRONIC COUNTER

FREQ RANGE: 10 Hz to 250 MHz. **SENSITIVITY:** 100 mv from 2 MHz to 150 MHz, 200 mv from 150 MHz to 250 MHz. **RESOLUTION:** One-tenth Hz from 10 Hz to 10 MHz, 10 Hz from 10 MHz to 250 MHz. Has built-in prescaler for freqs above 10 MHz. **ACCURACY:** Two versions available, .0005% or .0002%, see below. **FEATURES:** Six digit incandescent readout with memory, two digit overrange for eight digit capability; six ranges; thru-line function measures transmitters up to 50 watts directly; self test; 1 MHz output jack; dual power supply, line or 12vdc for mobile use; polaroid filter; handle, bail, and cord holder. One year warranty. Prices are fob Reseda, Calif. Weight - 7 lbs.

Model 6-VHF-A with room temp xtal, .0005%, 15 to 30 degrees C **\$350.00**

Model 6-VHF-A with temp comp xtal (TCXO), .0002%, 10 to 40 degrees C **\$390.00**



PAGEL ELECTRONICS

6742-C TAMPA AVENUE
RESEDA, CALIF. 91335

USED TEST EQUIPMENT

All checked and operating unless otherwise noted. FOB Monroe. Money back (less shipping) if not satisfied.

Borg 1526B-Freq. stand..1/1/5MHz out- acc. of 1x10 ⁻⁹ per day	395
AIL-124C Power Osc. 200-2500 MHz	365
Boonton 190A Q-MTR 20-260 MHz	375
HP100D-Freq. stand. w/scope-Acc. 1ppm	165
HP150A - 10 MHz Scope w/152B	185
HP160B(USM105)-14MHz dual trace scope	385
HP185B-DC-1ghz samp. scope w/186B	335
HP202B-Audio Gen.-5Hz-50kHz-1.10v	75
HP212A-Pulse Gen. var. width and rate	65
HP330C-Dist. Anal. 20Hz-20kHz	225
HP522B-Freq. Counter-10Hz-120kHz-digital	45
HP540-B-Trans. Osc. for counter-to 12ghz	185
HP610B-Sig Gen.-450-1200MHz, calib. attn.	365
HP686A-Sweep Gen.-8.2-12.4ghz	625
HP803A VHF Imp. bridge 50-500MHz	195
HP2590B-Precision Trans. osc-synchronizer	975
Kintel 301-DC standard-null voltmeter	220
NE 14-20C-Freq.-counter (sim. HP524C)	209
Nems Clark 1671-FM rcvr. 175-260MHz	210
Polarad TSA-spectrum analyzer 10MHz-44ghz (plug-ins available)	325
Polarad SA84W-spectrum analyzer, band switching 10MHz-41ghz	965
Rollin 30-Stand.Sig.gen.40-400MHz-hi-pwr	585
Stoddart NM52A-RFI mtr. .375-1ghz, w/acc.	985
Tek RM15-DC-15MHz Gp scope	295
ME26D/U-(HP410B) VTVM to 700 MHz	85
SG24/TRM3 Sweep Gen. 15-400 MHz, CW, AM, FM Xtal markers, scope-Dev. to 20%	395
TS-403A-Sig. Gen. (HP516) 1.8-4ghz	385
URM-26 Stand. Sig. Gen. 3-400MHz	225
USM-16 Stand. Sig. Gen.10-440MHz AM-CW-FM Pulse-Sweep, Phase-locked osc.	625

(Send SASE for complete list)


GRAY Electronics
P. O. Box 941, Monroe, MI 48161
Specializing in used test equipment

sub-audible tone encoder/decoder

Alpha Electronic Services has announced a new two-frequency subaudible tone encoder/decoder; the model DTSS-80 continuous-tone squelch system is exceptionally useful where a need exists to have a choice of tone frequencies for the purpose of controlling or selecting repeater stations, base stations or mobile radio units. By a simple two-position switch the dual tone makes possible the employment of multiple repeaters, increasing the range capabilities of a radio communications system. The selective calling of two base stations, two groups of mobiles or special control functions are other uses that this versatile device can accomplish. Each DTSS-80 tone unit is comprised of a plug-in encoder/decoder board and two plug-in TN-91 frequency determining boards. A special model is available that plugs directly into General Electric Master mobile radio units.

For information on the DTSS-80 write to Alpha Electronic Services, Inc., 8431 Monroe Avenue, Stanton, California 90680, or use *check-off* on page 94.

plug-in socket boards

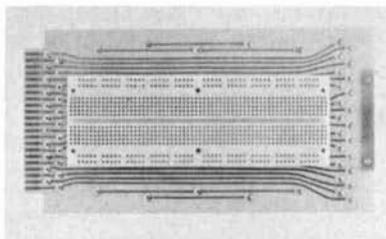

EL Instruments announces the PL-1 and PL-2, Plug-in Socket Boards. The PL-1 and PL-2 feature one or two patented EL SK-10 component sockets on a 4½ x 9 inch glass epoxy G10 pc board.

The board includes a 22 pin card edge connector and card extractor handle. There are also 44 BP-23, breadboarding pins on the board for connecting the devices on the SK-10 sockets to the card

edge connector. There is no soldering required; connections are made with standard 22 or 24 AWG hook-up wire.

The PL-1 and PL-2 are card rack compatible and have top edge test points for ease in circuit checking. The boards can be used to test prototype designs, add to existing card rack systems, update old pc card designs and many other bread-boarding functions.

The PL-1 (two SK-10 sockets), at \$42.50 and the PL-2 (one SK-10 socket) at \$29.95 are available from stock. Complete information and quantity prices are available from EL Instruments, Inc., 61 First Street, Derby, Connecticut 06418 or by using *check-off* on page 94.

standard tone burst encoder

Standard Communications Corporation has introduced the new SC-ATBE-1 five-frequency tone burst encoder for activation of coded repeater systems. The unit offers exceptional stability of $\pm 0.25\%$ over a 180° temperature range through the use of a bridged-T oscillator and quality mica capacitors. The unit comes factory preset for the five most commonly used burst tone frequencies in the 1700 to 2500 Hz range — although the frequencies can be easily changed at any time.

The burst duration can be set from 0.1 to 1.0 seconds or keyed continuously by a front panel control for testing. Units come factory preset for 0.4 seconds. Output up to 15 mV rms, sine wave, is internally adjustable for different rigs with units coming preset for use with the SR-C826M. The unit styled to match the SR-C826M, mounts under the SR-C826M and plugs directly into the rear of any Standard Communications Corporation transceiver (except the hand-held units). The unit is powered by the standard 12 Vdc. It sells for \$78.00.

More information is available from Standard Communications Corporation, 639 North Marine Avenue, Wilmington, California 90744 or by using *check-off* on page 94.

Get 'RIGHT ON' your REPEATER

with

CQC

2-Meter Crystals

TC-2M — .002% Tolerance

CRYSTEK crystals offer frequency stability over varying temperatures so you can go mobile in any environment.

If your dealer can't supply, write...



CRYSTEK

formerly Texas Crystals
Div. Whitehall Electronics Corp.


1000 Crystal Drive
Fort Myers, Florida 33901
4117 W. Jefferson Blvd.
Los Angeles, California 90016

2 METER FM

TALK POWER!

TEMPO
POWER
AMPS

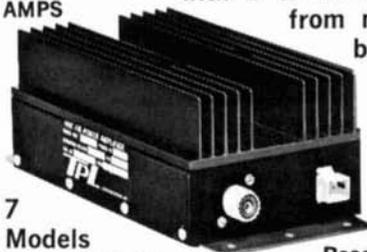up to 135 W OUT
with 1 to 25 w drive
from mobile,
base or
HT...



7
Models
from \$85.00
... in stock

Solid
State
Micro-
Strip
Circuit

Ready-to-go,
Cables supplied
all U. S. made

Send QSL or circle number for detailed brochure

E ERICKSON COMMUNICATIONS

4659 North Ravenswood Avenue
Chicago, Ill. 60640 (312) 334-3200



NEW REPEATER

2 Meter Fixed Station

Designed for the man who demands professional standards in 2 meter equipment. *REPEATER LINE* fixed station antennas are the 2 meter HAM's dream come true. With everything you need for top fixed station performance...toughness, efficiency and the gain to gain access to distant repeaters with ease. Work many stations, fixed or mobile, without access to a repeater.


The right antennas for the new FM transceivers...or any 2 meter fixed station.

REPEATER LINE Fixed Station Antennas

Tough, high efficiency antennas with a long, low radiation. For the top signal and reception you want...and the top performance your transceiver's ready to deliver.

- 267 Standard 1/4 wave ground plane. May be precision tuned to any discrete frequency between 108 and 450 MHz. Takes maximum legal power. Accepts PL-259. Constructed of heavy gauge seamless aluminum tubing.
- 268 For repeater use. Special stacked 4 dipole configuration. 9.5 db offset gain. 6.1 db omnidirectional gain. Heavy wall commercial type construction. 144 thru 174 MHz. 1.5:1 VSWR over 15 MHz bandwidth eliminates field tuning. Extreme bandwidth great for repeater use. Center fed for best low angle radiation. DC ground. Complete with plated steel mounting clamps.
- 338 Colinear ground plane. 3.4 db gain omnidirectionally. Vertically polarized. 52 ohm match. Radiator of seamless aluminum tubing; radials of solid aluminum rod. VSWR less than 1.5:1. All steel parts iridite treated. Accepts PL-259.
- 362 SJ2S4 high performance all-driven stacked array. 4 vertically polarized dipoles. 6.2 omnidirectional gain. 52 ohm. May be mounted on mast or roof saddle. Unique phasing and matching harness for perfect parallel phase relationship. Center fed. Broad band response. DC ground.
- 340 3 element high performance beam. 9 db gain. Coaxial balun. Special VHF Beta Match configuration. Unidirectional pattern. VSWR 1.5:1. 52 ohm impedance. Heavy gauge aluminum tubing and tough aluminum rod construction.
- 341 8 element high performance beam. 14.5 db gain. Coaxial balun. VHF Beta Match. Unidirectional. Boom length 14'. VSWR 1.5:1. 52 ohm feedpoint. Heavy gauge commercial type aluminum construction.
- 231 15 element high performance beam. 17.8 db gain. Coaxial balun. Beta Match. Unidirectional. Boom length 28'. VSWR 1.5:1. 52 ohm feedpoint. Extra-strength heavy wall commercial aluminum tubing.

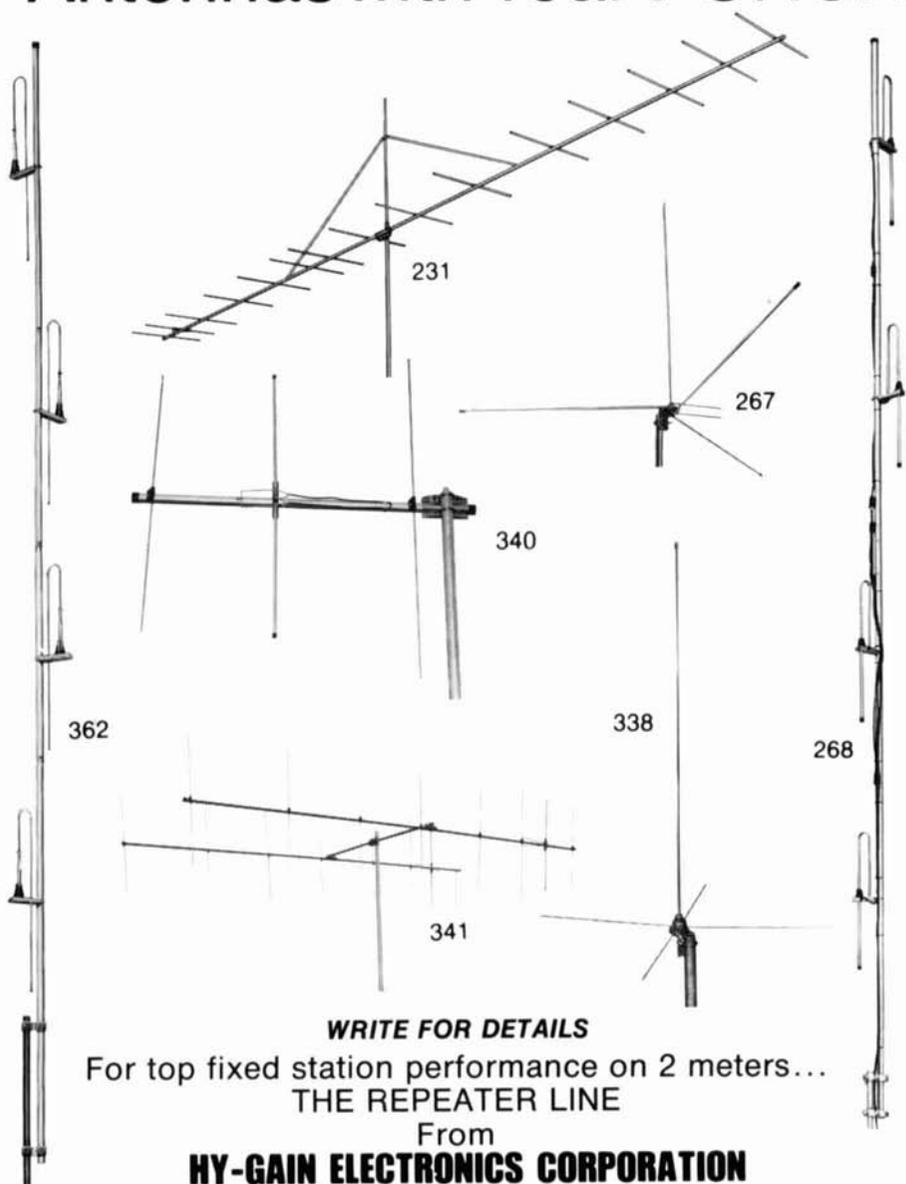LINE from **HY-GAIN** Antennas with real PUNCH!




WRITE FOR DETAILS

For top fixed station performance on 2 meters...
THE REPEATER LINE

From
HY-GAIN ELECTRONICS CORPORATION

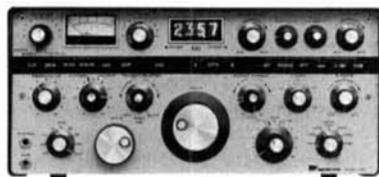P. O. Box 5407-WL Lincoln, Nebraska 68505



LATEST  **CX7A**


In stock for immediate shipment.

Write for 4 page brochure.

See Barry for the Best Deal.

- Reliability better than ever
- All modes 10-160 meters
- Broad-band tuning, instant band change
- True break-in CW
- IF shift
- Noise blanker & RF speech clipping
- 2 VFO's
- Much, much more

The incomparable
ALPHA 77 by ETO

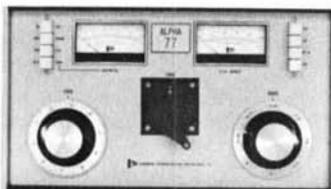

The finest amplifier ever offered for Amateur, Commercial & Military service. 3000 watts PEP continuous-duty. Perfect companion to the CX7A.

Write for information & Barry's Best Deal

DRAKE

- SPR-4new, Write W4new, \$ 61.95
 TR4/C new, \$599.95 TR22 new, \$199.95
 ML2new, \$299.95

TEN TEC

- All below is new merchandise
- ARGONAUT MODEL 505 \$288.00
 210 POWER SUPPLY \$ 24.95
 ARGONAUT 405 LINEAR AMP. 50w. out \$149.00
 250 POWER SUPPLY, powers 505 & 405 \$ 49.00
- All above in stock
- TX100 \$109.95 KR20 \$ 59.95
 RX10 \$ 59.95 KR40 \$ 89.95
 AC4 \$ 14.95 Microphone \$ 17.00
 KR1 \$ 18.95 PM2B \$ 64.95
 KR2 \$ 12.95 PM3A \$ 79.95
 KR5 \$ 34.95

CLEGG FM-27B NO XTALS
 25w out Synthesized
 2 Meter FM transceiver, \$479.95

CLEGG FM-27A \$325.00

COLLINS

- MP1 mobile supplygood, \$ 95.00
 351D2 mobile mountfair, \$ 65.00
 30L1 spare parts kit less chassis/cab. etc. \$ 99.00

HALLICRAFTERS

- SX-122Areg. \$550 net, new cond., \$350.00
 HT-32A \$195.00
 FPM-300new, \$595.00

LINEAR SYSTEMS

- SB-36 5 Band 500W SSB/CW Digital readout transceiver complete with AC power supply
 Brand new in stock, Write

DYCOMM

- 2 Meter Amplifiers (Power ratings approx.)
 BRICK BOOSTER, 2w in 35w out \$ 79.95
 SUPER BRICK, 2 in 45w out \$ 99.95
 BLOCK BOOSTER, 10 in 50w out, new, \$ 99.95
 demos, \$ 79.95
 10-0 35-0, 25-35w in 100w out \$189.95

INSTRUMENTS

- GR 1001A SIGNAL GENgood, \$425.00
 DIGIPET 60 digital freq. counter, with 160 scaler. Range 1 kHz - 160 MHz \$349.00
 FR-114U 6 digit E-put meter, frequency .1 - 10k, .0001 to 10 sec.like new, \$225.00
 SIMPSON 260-6 VOM with probes, new, \$ 68.50
 SIMPSON 270 VOM with probes & leather case new, \$ 81.00
 SIMPSON 2701 Digital Multimeter reg. approx. \$895 Special, \$595.00

12 VOLT DC POWER SUPPLIES: 110 AC INPUT

- MODEL 102, is a 4 amp overload protected power supply that automatically resets itself when the overload is removednew, \$24.95
 MODEL 104R, is a regulated power supply with the same electronic overload protection as the model 102. MODEL 104Rnew, \$34.95
 MODEL 107M is a heavier duty supply with the same features as the Model 102 but puts out 6 amps, useful for Clegg 27 series, etc.new, \$27.95

INVERTER/CONVERTER:

- MODEL 612 is a special purpose unit to provide 12 VDC negative ground power in automobiles with either 6 volt negative ground or 12 volt positive ground. 10 amp surge, 3 amp continuousnew, \$22.95

CASH PAID . . . FAST! For your unused TUBES, Semiconductors, RECEIVERS, VAC. VARIABLES, Test Equipment, ETC. Write or call Now! Barry, W2LN1. We Buy!

We ship all over the World. DX Hams only.
 Send for Green Sheet Supplement 23.

BARRY ELECTRONICS CORP.
 DEPT. H-2 — PHONE A/C 212-925-7000
 512 BROADWAY, NEW YORK, N. Y. 10012

MISC.

0-25 VDC Voltmeter by Honeywellnew, \$3.95
 2 METER VHF DUMMY LOAD/WATTMETER
 Good up to 15 watts — w/SO-239 CONNECTOR \$19.95
 1 COM IC-20 12 channels, 2 meter FM transceiver, IC-20 AC Pow. Sup., portable DC power sup., 11 sets XTALS for NYC area

STANDARD 826-M 2 meter FM transceiver, 12 channel with 10 sets Xtals for NYC area, AC pow. supplymint, \$295.00
 LAFAYETTE HA-460 6 meter transceiver with VFO, 20 watt, AC & DC pow. sup., new, \$ 95.00
 SP-600 540 kHz - 54 MHz gen. coverage receivergood condition, Write NC-400 540 kHz - 31 MHz 7 bands USB, LSB CWfair to good, \$150.00
 EF JOHNSON VALIANT II, 10, 11, 15, 20, 40, 80, 160M, 300 watts with Johnson SSB adapter \$300.00

HEATH DX-100, 10, 11, 15, 20, 40, 80, 160M 100 watts AM & CWchecked out w/manual, \$ 95.00
 HEATH HP-23A AC Supplylike new, \$ 45.00

ANTENNAS

MOSLEY LANCER "1000" mobile antenna, all coils 10, 11, 15, 20, 40, 80 good, used, complete, \$ 50.00

MOSLEY TA-36write
 2M MAGNETIC MOUNT w/RG58 & PL259 with 10 ft. RG 58 ready to go\$ 9.95
 14AVQ/WB VERTICAL\$ 47.95
 18AVT/WB VERTICAL\$ 69.95
 TH3MK3 10/15/20 Beam Super T. Bird \$144.95
 HY GAIN 2 METER, 15 element beamwrite
 A144-7 2 METER BEAM\$ 13.95
 NEW ULTRA BALUN 1:1\$ 9.95
 C.D HAM "M" ROTATORS, new, complete \$99.95
 HAM "M" CABLE @ 12¢/ft.
 C.D. TR-44 ROTATORS, new, complete \$63.95
 CABLE FOR TR-446¢/ft.
 RG-8A/U 100 ft. rolls. VHF connector PL-259 one end Type "N" (UG-21E/U) other end \$ 12.50
 RG8A/U — 65 feet with PL-259 connectors on each end\$ 9.50
 Authorized factory dealers for Antenna Specialists, CushCraft, Gam, Heights Towers, Hy Gain, Mor-Gain Antenna, Mosley, Newtronics, Tri-Ex, Rohm

DX ENGINEERING SPEECH COMPRESSORS

DIRECT PLUG-IN FOR COLLINS 32S\$79.50
 DIRECT PLUG-IN FOR KWM — 2\$79.50
 DIRECT PLUG-IN FOR DRAKE TR3 OR DRAKE TR4\$98.50

BIRD

4350 80-10M 2KW Ham Mate\$ 79.00
 4351 80-10M 1KW Ham Mate\$ 79.00
 4352 6- 2M 400W Ham Mate\$ 79.00
 43 Wattmeter\$100.00
 BIRD 43 SLUGS, spec. freq./power\$ 35.00
 MODEL 70 ROBOT SSTV Monitor in stock \$295.00

BARKER & WILLIAMSON

Dummy Load - Wattmeters - 52Ω 334A DC - 300 MHz, 1000 watts int.\$139.95
 374 DC - 230 MHz, 1500 watt\$169.95
 333 DC - 300 MHz, 250 watt int.\$ 79.95
 Transistorized Little Dipper, battery operated, 2 MHz-230 MHz continuous ±3% accuracy with modulation\$ 94.50
 ARRL B & W Kits, all available from Barry
 850A, 852 Inductors\$ 59.95
 851 Inductor\$ 29.95
 B & W MODEL 800 HiPower RF Choke \$ 5.49

Write for free Deluxe B & W Catalog

BUILDERS!

Barry has lots of James Millen and National Radio parts in stock.

Write for Barry's latest Green Sheet, No. 23.



**bind 'em
and
find 'em**

Bind your HAM RADIO'S with our handsome Ham Radio Binders then find the articles you want with our new 1968-72 Cumulative Index covering every article published in HAM RADIO from our first issue through December 1972.

Of course, if your shack is like ours you may have to find'em, bind'em and find it, but that's what this is all about. Get organized. Get maximum use from your HAM RADIO collection.

HAM RADIO

GREENVILLE, NH 03048

Please send:

-Binders at \$4.50 ea.
3 Binders for \$12.00
Cumulative Index at \$1.00
Super Package-5 Binders plus Index A \$23.50 value only \$18.50 (SAVE \$5.00)

Name..... Call.....

Address.....

..... Zip.....

The "STANDARD," by Heights

Light, permanently beautiful **ALUMINUM** towers

THE MOST IMPORTANT FEATURE OF YOUR ANTENNA IS PUTTING IT UP WHERE IT CAN DO WHAT YOU EXPECT.
RELIABLE DX — SIGNALS EARLIEST IN AND LAST OUT.



ALUMINUM

Self-Supporting

Easy to Assemble & Erect

All towers mounted on hinged bases

Complete Telescoping and Fold-Over Series available


And now, with motorized options, you can crank it up or down, or fold it over, from the operating position in the house.

Write for 12 page brochure giving dozens of combinations of height, weight and wind load.

Three men astride a Standard 80 foot tower with a 14 square foot antenna wind-load capacity (designated A80 (14 sq./ft.)). Supported only by the test base.

HEIGHTS MANUFACTURING CO.

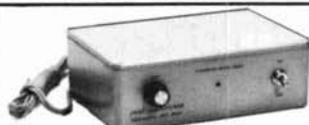In Almont Heights Industrial Park
Almont, Michigan 48003



VHF UHF

Crystal Controlled CONVERTERS for DX, FM, ATV, Space and other uses. Extremely Sensitive and free from spurious responses. With AC power supply. Choice of i-f, many in stock. Upgrade your station to JANEL.

50 MHz	2.0db NF	\$74.95
144 MHz	2.5db NF	\$74.95
220 MHz	3.0db NF	\$79.95
432 MHz	5.5db NF	\$74.95

All postpaid. Write for full details. Also preamps. Ask about our OSCAR special 435 MHz converters.

JANEL P.O. BOX 112
LABORATORIES SUCCASUNNA, N. J. 07876
201-584-6521

TEST EQUIPMENT

H-P 3526A Tape Transport. 15/16, 1 7/8, 7 1/2, 15, 60, 120 inches per second. Less Heads	\$400.00
H-P 561-B Digital Printer	\$85.00
DATATOTAL 1141-8 8-digit printer	\$25.00
APR-4 Receiver with CV-253 tuner, 38-1000 MHz. 115 v. 60 Hz. power	\$175.00
H-P 526-B Time interval plug-in	\$40.00
H-P 526-D Phase plug-in	\$90.00
Northeastern Eng. 14-22C Converter 100-220 MHz. for H-P counter	\$65.00

All in excellent condition

Send 25¢ for new 18 page catalog of surplus equipment and parts.

JEFF-TRONICS

4252 Pearl Rd., Cleveland, OH 44109

FREE Catalog

OF THE WORLD'S FINEST
GOVERNMENT SURPLUS
ELECTRONIC EQUIPMENT

And BETTER Than Ever!

Name _____
Address _____
City _____ State _____ Zip _____

Mail Coupon for Your FREE Copy, Dept. HR

FAIR RADIO SALES

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

WE PAY **HIGHEST**
PRICES FOR ELECTRON
TUBES AND SEMICONDUCTORS

H & L ASSOCIATES

ELIZABETHPORT INDUSTRIAL PARK
ELIZABETH, NEW JERSEY 07206
(201) 351-4200

CW or RTTY, whichever way you go,
**HAL HAS TOP QUALITY
 YOU CAN AFFORD!**



TOP QUALITY RTTY... WITH THE HAL MAINLINE ST-6 TU. Only 7 HAL circuit boards (drilled G10 glass) for all features, plug-in IC sockets, and custom Thordarson transformer for both supplies, 115/230 V, 50-60 Hz. Kit without cabinet, only \$135.00; screened, punched cabinet with pre-drilled connector rails, \$35.00; boards and complete manual, \$19.50; wired and tested units, only \$280.00 (with AK-1, \$320.00).*



TOP QUALITY... WITH THE HAL 1550 ELECTRONIC KEYSER. Designed for easy operation; perfectly timed CW with optional automatic ID for sending call letters, great for DX and RTTY; TTL circuitry, transistor switching for grid block, cathode keying. Handsome rugged crackle cabinet with brushed aluminum panel. With ID, only \$90.00; without ID, \$65.00.*

OTHER HAL PRODUCTS INCLUDE:

- ID-1 Repeater Identifier (wired circuit board) . . . \$ 75.00*
- ID-1 (completely assembled in 1 1/2" rack cabinet) . . . \$115.00*
- HAL ARRL FM Transmitter Kit . . . \$ 50.00*
- W3FFG SSTV Converter Kit . . . \$ 55.00*
- Mainline ST-5 TU Kit . . . \$ 50.00*
- Mainline AK-1 AFSK Kit . . . \$ 27.50*



TOP QUALITY... WITH THE HAL MKB-1 MORSE KEYBOARD.

As easy as typing a letter—you get automatic CW with variable speed and weight, internal audio oscillator with volume and tone controls, internal speaker, and audio output jack. Smooth operation; completely solid-state, TTL circuitry using G10 glass boards, regulated power supplies, and high voltage transistor switch. Optional automatic ID available. Assembled MKB-1, \$275.00. In kit form, \$175.00.*



NEW FROM HAL—TOP QUALITY RVD-1002 RTTY VIDEO DISPLAY UNIT. Revolutionary approach to amateur RTTY . . . provides visual display of received RTTY signal from any TU, at four speeds (60, 66, 75, and 100 WPM), using a TV receiver modified for video monitoring. Panasonic solid-state TV receiver/monitor, or monitor only, available. RVD-1002, \$525.00; Panasonic TV receiver/monitor, \$160.00; monitor only, \$140.00.*

TOP QUALITY... WITH THE HAL RKB-1 TTY KEYBOARD. Gives you typewriter-easy operation with automatic letter/number shift at four speeds (60, 66, 75, and 100 WPM). Use with RVD-1002 video display system, or insert in loop of any teleprinter, for fast and easy RTTY. Completely solid state, TTL circuitry using G10 glass boards, regulated power supplies, and transistor loop switch. RKB-1 assembled, only \$275.00.*

HAL provides a complete line of components, semi-conductors, and IC's to fill practically any construction need. Send 24c to cover postage for catalog with info and photos on all HAL products available.

*Above prices do not include shipping costs. Please add 75c on parts orders, \$2.00 on larger kits. Shipping via UPS whenever possible; therefore, street address required.

HAL COMMUNICATIONS CORP., Box 365 H, Urbana, Illinois 61801

NEW! 8-DIGIT MUX (Multiplex) BURROUGHS 8-DIGIT "UNIVERSAL" NEON READOUTS

PC Board Included!
Only \$19.95
 WORTH \$50.00

- Designed for use with LSI, digital clocks, calculators, frequency counters, DVM's, & precision chronometers, tool
- Eight individual Burroughs B5750's Nixie tubes mounted on a universal 4 1/2" x 1 1/2" MUX board with pin outs for digit drivers & segment.

Use all 8 readouts or any number of readouts from 1 to 8 SIMPLY, EASILY. Electrical characteristics: 17V VDC, 2 decimal points, 2 anode pins. We include schematics & instructions. • Characters 9/16" high!
 POWER TRANSFORMER FOR ABOVE Only \$1.95
 110 to 170 VAC with 6.3V tap on secondary for TTL's.

11 TRANSISTOR PHILCO AM RADIO CHASSIS

BUY 2 FOR STEREO Use as:
 Only \$5.95

- Mike amplifier
- Phone amplifier
- Tape amplifier
- Covers 555 Kcs to 1500 Kcs Broadcast band
- AC or DC

Originally design for portable phono systems, and tape cassettes
 One of the most versatile AM Radio and multi-purpose amplifiers we have seen at Poly Paks famous "Economy" price. Measures only 4 1/2" x 3 1/2" x 2" high. With tuning capacitor, IF circuitry, loopstick, ant. volume control with switch, AC and phono-mike jacks. Separate switch for changing from AM radio to amplifier. Uses either 110V plug-in adapter (not with unit) and a 9-volt battery power. Exceptional sensitivity and power. Feeds into 16 ohm speaker. Complete with spec sheets, diagrams, and hookup ideas.
 With Built-in Preamp
 Mike, Tape, Phono Inputs

8 TRANSISTOR AMPLIFIER CHASSIS Only \$3.95

Same as above, except no AM radio section. Completely wired! With built-in preamp, mike, phono and tape inputs. Color-coded wires with diagram and hookups. Works off 9VDC transistor battery. Excellent fidelity.

MAGIC "SOUND TRIGGER" \$1.98

Unique Scientific Device, "hand claps", sensitizes crystal mike amplifier, triggers SCR. Needs only 3 to 6vdc. Use as burglar alarm, intrusion device. Use with photo cell, triggers SCR's, relays, LED's. Even fiber optic light pipe may be used. With hand booklet.

LOWEST PRICES ON "TRIACS"

* Two SCRs in one case! * Most complete listing!

PRV	3 amp	6 amp	10 amp	15 amp	25 amp
50	\$.22	\$.35	\$.45	\$.65	\$.85
100	\$.35	\$.52	\$.64	\$.85	\$ 1.05
200	\$.65	\$.72	\$.88	\$ 1.25	\$ 1.45
300	\$.75	\$.89	\$ 1.10	\$ 1.45	\$ 1.85
400	\$.92	\$ 1.15	\$ 1.35	\$ 1.85	\$ 1.95
500	\$ 1.25	\$ 1.39		\$ 2.55	\$ 2.25
600	\$ 1.50	\$ 1.69			\$ 2.65

Code: J-4 6 amp TO-5, 10 amp TO-66, 15 & 25 amp stud.

SILICON TUBES

584	\$1.49
584	3.95
866	7.95

"How's Your MEMORIES For 1973?"

1101	256 Bit RAM MOS	\$3.50
1103	1024 Bit RAM MOS	8.50
2513	Character Gen. ROM	12.50
2516	Character Gen. ROM	12.50
7489	64 Bit RAM TTL	2.50
8223	Programmable ROM	8.50
8224	Programmable ROM	12.50
MMS260	1024 Bit RAM	8.88
4000	Bit Core Memory Plane	4.95

Terms: add postage, cod's 25%. Rated: net 30
 Phone Orders: Wakefield, Mass. (617) 245-1829
 Retail: 16-18 Del Carmine St., Wakefield, Mass.
 (off Water Street) C.O.D.'S MAY BE PHONED

15¢ CATALOG ON Fiber Optics, 'IC's', Semi's, Parts

POLY PAKS

P.O. BOX 942 H, LYNNFIELD, MASS. 01940

1 WATT "FLANGELESS" TOP HAT ZENERS \$5 for \$1

Volts	4.7	10.	15.
6.3	11.	30.	
8.2	12.	33.	
9.1	13.		

Type TK, Metal Case! \$1

BRAND NEW LOWEST PRICES

GENERAL ELECTRIC \$2.95 3 FOR \$6.00

3-WATT AUDIO AMP

Delivers 3 watts continuous, 10 watts peak. With heat sinks! micro-mini size: 3 1/2" x 1 1/2" x 1/2". 9 to 30V supply. High sensitivity: 8 to 16 ohms. For mono and stereo phonos, tape, FM, AM, TV, servo.

PR-263

12-DIGIT "CALCULATOR ON A CHIP"

Similar to Mostek 5001. Outperforms Texas-Nixie digit TMS1802. A 40-pin DIP. Adds, multiplies, subtracts, and divides. Use with 7-segment readouts, Nixies, and LED's. We include schematics, instructions from factory to build calculator.

Only \$12.95 3 for \$35

NIXIE COUNTING SYSTEM \$4.50 3 for \$12.00

Includes SN7490, decade counter, SN7475 latch, SN7441 BCD decoder driver, 0-to-9 Nixie tube, instructions.

LED READOUTS \$4.50 3 for \$12. \$2.95 Buy 10 Take 10%

Lowest prices on LED READOUTS 3 for \$12. 0-9 plus letters. For SN7446 or SN7447. Snaps in 14-pin DIP socket. 3 1/2" x 3 1/2" characters: 1/4" x 3/8", 5V, 20-mils per seg. characters: 1/4" x 1/4". Famous MAN-1 type. Sockets .50 ea.

GIANT SALE ON NATIONAL "IC'S"

Type	Description	Sale
DM8091	Tri-State Quad Buffer	\$1.00
DM8093	Tri-State Quad Buffer	1.00
DM8094	Tri-State Quad Buffer	1.00
DM8200	4-Bit Comparator	1.50
DM8210	8 Channel Switch	1.00
DM8220	Parity Generator Checker	1.00
DM8223	Programmable ROM	8.88
DM8250	Binary to Octal Decoder	1.00
DM8281	Preset Binary Counter	1.19
DM8288	Stretch Divide by 12	1.18
DM8502	Same as 74107	.41
DM8520	Modulo Divide by 2-16	1.50
DM8555	Tri-State Preset Counter	1.95
DM8680	Binary Counter	1.00
DM8800	Dual Voltage Translator	1.00
DM8830	Dual Diff. Line Driver	1.00
DM8845	Same as SN7445	1.45
DM8845	Same as SN7445	1.45
DM8845	Hi Amp, 7-Seg. Dec. Driver	1.95

Buy 100 Take 20% Buy 3 Take 10% Discount

NATIONAL 4 for DTL "IC'S" \$1.

DM930	4 In. Gate	
DM932	6 In. Gate	
DM932	Dual 14 In. Buffer	
DM936	Hex Inverter	
DM946	Quad 2 Input Gate	
DM962	Triple 3 In. Gate	
DM9093	Dual J-K Flip Flop	*2 for \$1.00

NATIONAL \$2.95 REGISTERS 3 for \$6.00

MMS500	Dual 25 Bit
MMS02	Dual 50 Bit
MMS05	Dual 32 Bit
MMS06	Dual 100 Bit
MMS006	Dual 100 Bit
MMS013	1024 Bit Accumul
MMS016	500/512 Bit
MMS017	Dual 500/512 Bit

PLASTIC RTL'S By Fairchild 12VDC POWER PAC

Choose Any 2 for \$1.00

- 900 Buffer
- 914 Quad 2 Input Gate
- 923 J-K Flip Flop

110 VAC to 12 VDC @ 1.6 AMP
 \$3.33 5 x 2 1/2 x 3 1/2"

HIGH POWER EPOXY RECTIFIERS

PIV	SALE	5000	2.25	1AMP
2000*	1.00	6000	2.96	
3000	1.35	8000	3.50	
4000	1.65	10000	3.95	

EPOXY SILICON RECTIFIERS *micromini

PIV	2Amp	2Amp	3AMP
50	\$.05	\$.05	\$.08
100	.06	.06	.12
200	.07	.07	.15
400	.09	.09	.22
600	.12	.12	.28
800	.15	.15	.35
1000	.18	.18	.49

EPOXY RECTIFIER SPECIAL 10 for \$1

1 AMP 1000 PIV

LINEAR Op Amps

FACTORY GUARANTEED
 FACTORY MARKED
 Buy Any 3 PAKS
 Take 10% Discount

Type	Price	
531	Hi slow rate op-amp	\$2.50
532	Micro power 741 TO-5	2.50
533	Micro power 709	2.50
536	FET input op amp	3.95
537	Precision 741 TO-5	2.50
540	7PW pwr driver amp	2.04
550	Precision 723 voltage reg.	1.17
555	Timer 2 uSeconds to 1-hour	1.00
556	5 Times faster than 741C	2.50
558	Dual 741 (mini DIP)	3.25
560	Phase lock loops	3.25
561	Phase lock loop DIP	3.25
562	Phase lock loop DIP	3.25
565	Phase lock loops (A)	3.25
566	Function generator (Mini DIP)	3.25
567	Tone decoder (Mini DIP)	3.25
595	Four quadrant multiplier	3.10
702C	Hi-gain, DC amp, TO-5	4.4
702C	RF-IF, amp, 12 ckt., TO-5	.69
709C	Operational amp (A)	.39
710C	Differential amp (A)	.39
711C	Dual diff. comp (A)	.39
723C	Voltage regulator (A)	.95
741C	Frequency comp 709 (A)	.49
741CV	Frequency comp 709 (mini DIP)	.49
747C	Dual 741C, (A)	1.25
748C	Freq. adj. 741C (A)	.45
709-709	Dual 709C (DIP)	1.00
709CG	Gold, military, DIP	.49
738-738	Dual stereo preamp	1.98
745D0	Ray line driver	.88
4250	Programmable op amp	2.50(A)

SN7400	\$2.21
SN7401	.21
SN7402	.21
SN7403	.21
SN7404	.27
SN7405	.27
SN7406	.45
SN7407	.45
SN7408	.29
SN7409	.29
SN7410	.21
SN7411	.25
SN7413	.75
SN7416	.48
SN7417	.48
SN7420	.21
SN7421	.21
SN7426	.32
SN7430	.21
SN7432	.25
SN7437	.50
SN7438	.51
SN7440	.21
SN7441	1.00
SN7442	1.12
SN7444	.44
SN7444	1.21
SN7445	1.50
SN7446	1.17
SN7447	1.25
SN7448	1.25

LOWEST PRICES ON TTL IC's

Buy 3 — Take 10% Discount

SN7450	.21	SN74123	.99
SN7451	.21	SN74141	1.45
SN7453	.21	SN74145	1.25
SN7454	.21	SN74150	1.45
SN7455	.25	SN74181	1.13
SN7460	.21	SN74183	1.25
SN7470	.32	SN74184	1.95
SN7472	.39	SN74185	1.39
SN7473	.44	SN74156	1.39
SN7474	.49	SN74157	1.25
SN7476	.44	SN74158	1.48
SN7480	.65	SN74161	1.79
SN7481	1.10	SN74162	1.79
SN7482	.88	SN74163	1.79
SN7483	1.25	SN74165	3.50
SN7486	.49	SN74174	3.20
SN7489	3.50	SN74180	1.10
SN7490	1.00	SN74181	1.50
SN7491	1.10	SN74182	1.10
SN7492	.71	SN74182	2.50
SN7493	.71	SN74183	2.50
SN7494	1.10	SN74184	1.75
SN7495	.95	SN74192	1.75
SN7496	1.10	SN74193	1.75
SN74100	1.41	SN74194	2.50
SN74107	.49	SN74195	1.19
SN74121	.49	SN74198	2.65
SN74122	.67	SN74199	2.65

NIXIE TUBE SALE

Burroughs B7971, 0-to-9, A-to-Z, 2 1/2" high characters, 170V.


ALLEN BRADLEY'S 'MICRO-POTS'

Type G, 1/2" dia. x 1 1/2" high, Mounts 17 1/2" hole, with shaft, linear, unimount pre-drilled hole.

2 for \$1

Ohms	2.5K	5.0K	7.5K	10.0K	15.0K	20.0K	25.0K	50K	75K	100K	150K	200K	250K	5 Meg
------	------	------	------	-------	-------	-------	-------	-----	-----	------	------	------	------	-------

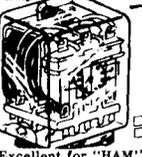We stock Locknut Bushing & Screwdriver types at same low prices.



Potter & Brumfield KAP RELAYS

Your choice 3 for \$7.98

115 VAC 3PDT	\$2.98
12 VDC 3PDT	\$2.98

Excellent for "HAM" use as antenna switching, latching, transmit, receive, etc., and 100's of commercial or industrial uses. Includes plastic dust-cover with diagram and hookup info, 11-pin plug-in base. Contacts movable, gold flashed silver, stationary overlay, with silver cadmium oxide movables. All contacts 10 amp 3PDT. Coil data: 1.16VAC 2250 ohms, 17.5 ma, 12 VDC 21 mils @ 65 ohms. Size: 2 1/4" x 1 5/16". Wt. 4 ozs. Center pin missing. Comar Mig. type equal too.

ALLEN BRADLEY'S 'TRANSISTOR' POTS

Type F. Screwdriver adjust.

Ohms	75	250	1.0K	10.0K	50.0K	250K	5 Meg						
Ohms	75	250	1.0K	7.5K	25.0K	100K	500K	2.5K	10.0K	50.0K	200K	75.0K	5 Meg

Lowest prices on LED 7-SEGMENT READOUTS

Only \$3.95

3 for \$10.

MAN-4 equal, (skinny MAN-1)

Specs same as MAN-1 type

0-9 plus letters, Snaps in 14-pin DIP socket. 3 1/4 x 3 1/4 characters: 1/4 x 3/8" 1/5V, 20-mils per seg. characters: 1/4 x 3/16" Sockets .50 ea.

INTEGRATED CIRCUIT SOCKETS

Buy Any 3 - Take 10%

14-Pin, dual in line	\$.45
16-Pin, dual in line	\$.50
TO-5, 8 or 10 pins	\$.29

'HAM' UHF 400 MC HIGH POWER TRANSISTORS

Only \$3.95

3 for \$10.

By RCA or equal 2N3632, NPN, 23 watts, 3 amps, TO-18 case, with stud mtg. VCEV max 65.

35 WATT AUDIO AMPLIFIER BASIC 2 FOR STEREO56

For Class AB use. Basic includes: Signetec 540 30 transistor high power driver TO-5 '1C' with a pair of complementary 35-watt plastic transistors, i.e. 2N5296 npn and 2N6109 pnp. With schematics, printed circuit and parts board layouts.

BURROUGHS 5755R

0-9, with right and left decimals, Neon red. Requires 1.75 volts 17 mils. 1 1/2" x 0.5" character size: 5 1/2"

ALPHA-NUMERIC 7-SEG. READOUTS

Fluorescent Blue-Green 0-9 numerals, decimals and letters. 2.50

H. W. Characters	Filament V	Socket	50c
MINI-7* 1.75 x 1.7"	.360 x .570"	1.5V AC/DC 42 mils	Socket — 50c
SLIM-7* 1.6 x 0.375"	.40 x .20"	1.5V AC/DC 42 mils	Socket — 50c

*Compatible to 7-segment driver IC's.

Dollar Stretchers

3 — "LED'S", visible, micro-miniature, axial leads	\$1
2 — "LED'S", infrared, jumbo, TO-18	\$1
3 — "LED'S", visible, jumbo, red, TO-18	\$1
1 — "LED", invisible, parabolic reflector, RCA	\$1
2 — PHOTO TRANSISTORS, with darlington amp filter, lens	\$1
2 — PHOTO TRANSISTORS, with darlington amp, 2N5777, GE#1	\$1
4 — PHOTO CELLS, Clairex, pancake, 40K-70 ohms	\$1
5 — SOLAR CELLS, round, sq, rect., sun power circuits	\$1
2 — SILICON SENSORS, TEXAS, 10-8K Matchbox, visible	\$1

TEXAS 4-WATT AUDIO AMPLIFIER

Type SN76024. Good up to 70 Hz, 4 W. into an 8-ohm load. High input impedance, VCC 9V to 24. DIP pak with heat sink, 15 transistors, 5 diodes.

3 for \$9

Only \$3.95

NATIONAL "OP" AMPS

Type	Description	Buy any 3 Take 10%
LM-300	Super 723 V. regulator	T05 \$1.49
LM-301	Hi-performance amp	
LM-302	Voltage follower T05	1.49
LM-304	Neg. voltage regulator T05	1.49
LM-305	Pos. voltage regulator T05	1.49
LM-307	Super 741	1.98
LM-308	Super gain op amp T05	1.98
LM-309H	SV 200ma V. regulator T05	1.98
LM-309K	DV 1 amp V. regulator T03	2.25
LM-350	Dual peripheral driver T05	.88
LM-370	High input amp op T05	1.49
LM-373	AM-FM USB if strip T05	3.75
LM-380	2 Watt amplifier	

KIDDE "DORANICK" REED RELAYS

Hermetically sealed 6 to 12 VDC, SPDT. Good for 100's of switching cycles. 350 DC ohms. 1.0A 250V contacts, 15 watts. 2 3/4" x 1" x 3". Wt. 4 oz.

Only \$1.49

EPOXY FULL WAVE SILICON BRIDGE RECTIFIERS

10V	2 Amp	6 Amp
50	5 Amp	9.5 Amp
100	.75	.99
200	.95	1.25
400	1.19	1.50
600	1.35	1.75
800	1.59	1.95
1000	1.79	2.25

Code: 2 amp TO-5 case
 6 Amp 1/2 x 1/2 x 3/16 sq

Terms: add postage, cod's 25%. Rated net 30.
 Phone Orders: Wakefield, Mass. (617) 245-3829
 Retail: 16-18 Del Carmine St., Wakefield, Mass.
 (off Water Street) C.O.D.'S MAY BE PHONED

15¢ CATALOG on Fiber Optics, IC's, Semi's Parts

POLY PAKS

P.O. BOX 942H, LYNNFIELD, MASS. 01940



CRYSTAL FILTERS and DISCRIMINATORS

1 27/64" x 1 3/64" x 3/4"



by
K.V.G.

10.7 MHz FILTERS

XF107-A	14kHz	NBFM	\$34.75
XF107-B	16kHz	NBFM	\$33.25
XF107-C	32kHz	WBFM	\$33.25
XF107-D	38kHz	WBFM	\$34.75
XM107-S04	14kHz	NBFM	\$15.95

10.7 MHz DISCRIMINATORS

XD107-01	30kHz	NBFM	\$18.35
XD107-02	50kHz	WBFM	\$17.55

(4 pole, in HC6/U crystal can)

CRYSTAL SOCKET (for XM107-S04) type DG1 \$15.00

VHF CONVERTERS UHF

	MM 50	MM 144	MM 220	MM 432	MM 1296
RF Freq. (MHz) +	50-54	144-148	220-224	432-436	
N.F. (typical)	2.5dB	2.8dB	3.4dB	3.8dB	COMING
Nom. Gain	30dB	30dB	26dB	26dB	SOON
	\$49.95	\$49.95	\$59.95	\$59.95	

Power 12V D. C.
Standard I.F. 28-32 MHz +
1 1/4" x 2 3/8" x 4 3/8" + connectors
Very low N. F. units on special order.
+Other ranges, amateur & commercial, to order.

si

SPECTRUM
INTERNATIONAL
BOX 1084 CONCORD
MASSACHUSETTS 01742

Many thousands of you have become very familiar with the various Radio Society of Great Britain books and handbooks, but very few of you are familiar with their excellent magazine, **Radio Communication**.

It includes numerous technical and construction articles in addition to a complete rundown on the month's events in amateur radio. Surely a most interesting addition to your amateur radio activities.

We can now offer this fine magazine to you along with the other advantages of membership in the RSGB (such as use of their outgoing QSL Bureau) for \$9.95 a year.

comtec

Greenville, New Hampshire 03048

A New Magazine?

Not really. New in the U.S.A. perhaps, but very well known in Great Britain and now being offered to you here.

RADIO CONSTRUCTOR is almost exclusively construction material. Clearly written, concise articles give you full details on:

- Audio Construction Projects
- Receiver Construction Projects
- Transmitter Construction Projects
- Test Equipment Projects
- Radio Control Projects
- ... and much more

Try a subscription to this interesting magazine, we are sure that you will not be disappointed.

ONE YEAR SUBSCRIPTION — \$7.00

Write
RADIO CONSTRUCTOR
Greenville, N. H. 03048

MOVE UP TO 220

FM COMMUNICATIONS FROM Standard



sr-c220 Solid State 220 MHz Transceiver

Pioneer the 220 MHz band with this new Standard transceiver. An all solid state radio designed to move with the growth. Features our exclusive "Astropoint" design with selectivity, intermodulation and interference rejection not found in low cost radios. 10 Watts output and 12 channels are

more than adequate for this exciting new band. Easy crystal access through "snap open" trap door. Incorporates provision for tone coded squelch (C.T.C.S.S.) and external oscillator. Included are microphone, mounting bracket, and 4 channels.

Get in on the Action Today!

sc-aRPT-4 New-220 MHz Repeater

A complete FM Repeater available exclusively for this new Amateur band.

Features:

- All solid state circuitry, with 10 Watts out.
- Carrier Operated Relay.
- Adjustable carrier delay and time out timers.
- Provision for tone squelch (C.T.C.S.S.).
- I.D. and remote control inputs.
- Plus many more exciting features.




Write for complete specifications.

 **Standard
Communications**

Standard Communications Corp. • 213 / 835 - 3134 • 639 North Marine Ave. • Wilmington, Calif. 90744

ECHO II

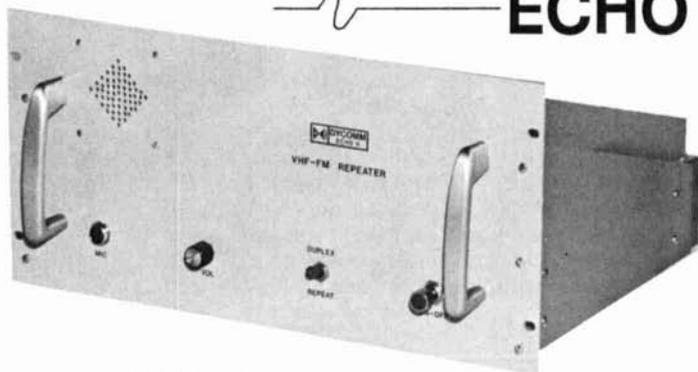

ALL
SOLID
STATE

STOCK
FREQS:
16/76
22/82
28/88
34/94

2 METER
AMATEUR REPEATER — ONLY **\$600.00**

PROVEN STATE OF THE ART DESIGN
INSTALLATIONS WORKING GREAT IN U.S., EUROPE AND ASIA
STOCK FREQS DELIVERED IMMEDIATELY, OTHERS 3-4 WEEKS
WRITE FOR FREE DATA SHEET — FULL MANUAL \$5.00

DYCOMM

948 AVENUE E P.O. BOX 10116
RIVIERA BEACH, FLA. 33404



ELECTRONICS
P.O. BOX 1672
VISTA, CA. 92083
714-726-1313



This New Frequency Counter has the following Specifications to recommend it:

Direct Counting: 10Hz to 80MHz guaranteed (1Hz to over 100MHz typical)

10MHz xtal time base

Readout: 5 digit LED plus over-range

Input Sensitivity: 100 millivolts max. on any freq.

Input Impedance: 1MΩ paralleled with 15pf.

Power Requirement: 120VAC or 12VDC

SMALL SIZE 2½"H, 5¼"W, 6¾"D.

Guarantee 1 year all parts, 90 days labor

PRICE \$250.00

FOB Vista, Ca. 92083

Y & C ELECTRONICS

P. O. Box 1672, Vista, CA. 92083, 714-726-1313

GATEWAY ELECTRONICS

8123 PAGE AVENUE
ST. LOUIS, MISSOURI 63130
314-427-6116

L.E.D. 7 SEGMENT READOUT — MAN 1
TYPE — NEW \$2.75

L.E.D. INDICATOR ONLY — NEW \$.65

IC MASTER BOARDS — PC Board with dual in-line IC Pads. Enough pads for 50-16 pin or 14 pin dual inline IC's. 10½ x 5 undrilled ship wt. 1 lb. \$2.00

VERTICAL GYROSCOPE — Aircraft type - precision made — ship wt. 7 lb. \$10.00

10 MHz CRYSTAL — Standard HC-6/U style in 24 volt oven. ship wt. 1 lb. \$2.50

THUMBWHEEL SWITCHES

— 0.5 x 2.125 x 1.78 — 10 position decimal \$2.75

— 10 position BCD & Compliment \$3.75

— End Plates (per pair) \$1.00

MINIATURE SIZE


— 0.312 x 1.3 x 1.3 — 10 position decimal \$2.00

— 10 position BCD & Compliment \$2.75

— End Plates (per pair) \$.50

\$5.00 Minimum Order
Visit us when in St. Louis

HALLETT
ELIMINOISE
 Ignition Noise Suppression Kit

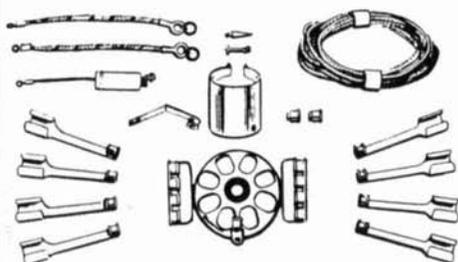

MODEL 80 - UNIVERSAL KIT FITS ALL 8 CYL. AMERICAN CARS

LIMITED

SPECIAL \$24.95

\$55.00 VALUE

Add \$2.50 for shipping & handling

LA *tronix*
 6 and 2 Meter


Sale Priced **15⁹⁵**

Gutter Mount Version \$19.95

MODEL LA 150A

Gain (2 Meters)3db
 Gain (6 Meters)Unity
 Nominal Impedance 55 ohms
 Overall Length55 in.

Add \$2.50 for shipping & handling

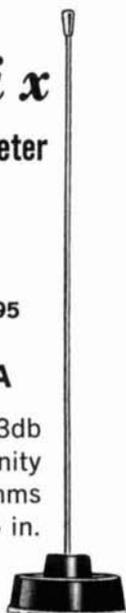

WANTED

CLEAN DRAKE GEAR

REWARD FOR	NEW	PRICE
\$195.00 2B or 2C	R4B	\$475.00
\$220.00 R4	R4B	\$475.00
\$275.00 R4A	R4B	\$475.00
\$200.00 T4	T4XB	\$495.00
\$125.00 2NT	T4XB	\$495.00
\$285.00 T4X	T4XB	\$495.00
\$ 60.00 AC3	AC4	\$ 99.95
\$ 70.00 DC3	DC4	\$125.00
\$270.00 TR3	TR4	\$599.00

A "broadband" isn't an all girl orchestra.

ITS A BALUN FROM LA-TRONIX



Mod. LA-BN330


IMPROVE YOUR ANTENNA PATTERN AND REDUCE TVI.....FOR ONLY

\$11.77

SPECIFICATIONS

BANDWIDTH.....3 THROUGH 30 MH; CONTINUOUS
 VSWR.....1:1 WHEN TERMINATED WITH A
 BALANCED 52 OHM LOAD.
 POWER RATING.....1KW DC 2KW PEP
 IMPEDANCE RATIO.....1:1 AT 52 OHMS
 INPUT CONNECTOR.....SO-239
 OUTPUT CONNECTIONS.....STANDARD TERMINAL LUGS
 WEATHER PROTECTION.....INTERNALLY SEALED

Add \$1.00 for shipping & handling

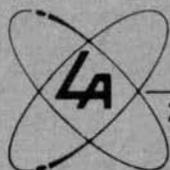

Electronix Sales

23044 S. CRENSHAW BLVD., TORRANCE, CALIF. 90505

Phone: (213) 534-4456 or (213) 534-4402

CLOSED SUNDAY & MONDAY

See LA for your SWAN needs

APOLLO PRODUCTS by "Village Twig"




**1500X-2
Rotary Antenna Switch**
Single pole, 3 position Antenna Switch. Low SWR. Use up to 30 MHz. 500 Watt handling capacity. Sloping Front Console Cab.
\$12.95




450X-S Antenna Switch
3-Position Slide Switch
Low Loss - Walnut-grain Finish Chassis - Gold Cover
\$5.95

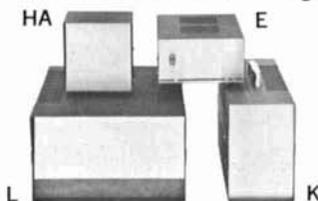700X-2 KW Wattmeter
Dummy Load Wattmeter for 52 Ohm Input. Measures RF in 4 ranges to 1000 watts. Measures modulation percentage on calibrated scale. Portable.
\$124.50



Model	Dimensions	Resale Net
"E"	6 1/2 x 3 15/32 x 7 1/16	8.25
"HA"	5 1/8 x 5 1/2 x 4 (Blank Panel)	8.95
"K"	4 3/4 x 7 3/8 x 11 W/Handle	13.50
"L"	11 1/8 x 6 1/8 x 12 3/4	20.50

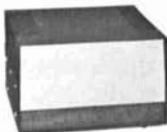

Meter O-1 MA
to fit "L" box
ppd. 5.00



"L" package enclosure
"Shadow Box" machined with: 2-SO239, 1-Pilot Light, 3-Rocker Switches, and 2-Knobs
pkg. 29.95



**2100X-2
SWR Bridge**
Large Meter - Sloping Panel Cabinet - Rubber Feet - Keep in Antenna Line up to 1 Kilowatt
\$29.95



900X-2 Wattmeter
Measures RF in 2 ranges 25 and 250 watts. 52 Ohm input.
\$29.95

**1700X-2
Vertical/Horizontal
Antenna Switch**
Allows operator to select any one of 3 antennas or dummy load. Two Antennas can be switched in simultaneously. New Sloping Front Console Cab.
12.95

APOLLO PRODUCTS

BOX 245 - VAUGHNSVILLE, OHIO 45893 - Phone (419) 646-3495 - Evening Phone (419) 646-3495

AT LAST -- A SPEECH COMPRESSOR THAT REALLY WORKS!



RPC-3M MODULE
(ONLY \$22.50)

- LOW DISTORTION CIRCUIT
- FULLY WIRED & TESTED NOT A KIT
- WORKS WITH PHONE PATCH
- INTERNAL UNITS & MODULES WORK MOBILE
- FULL WARRANTY — ONE YEAR
- INTRODUCTORY LOW PRICES (Illinois residents add 5% Sales Tax)

Write for specifications and information sheets (free)

Add \$2.00/unit shipping (RPC-3C) or Add \$1.00/unit shipping (RPC-3, 3U, 2M)



RPC-3C CABINET MODEL
(\$34.95)



RPC-3,3U INTERNAL UNIT
(\$24.95)

Rp Electronics

BOX 1201H
CHAMPAIGN, ILL.
61820



Radio Amateurs
Reference Library
of Maps and Atlas

WORLD PREFIX MAP — Full color, 40" x 28", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables . . . postpaid **\$1.25**

RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD — from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities; Boston, Washington, D. C., Miami, Seattle, San Francisco & Los Angeles. . . . postpaid **\$1.25**

RADIO AMATEURS MAP OF NORTH AMERICA! Full color, 30" x 25" — includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus informative information on each of the 50 United States and other Countries . . . postpaid **\$1.25**

WORLD ATLAS — Only atlas compiled for radio amateurs. Packed with world-wide information — includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica — a complete set of maps of the world. 20 pages. size 8 3/4" x 12" . . . postpaid **\$2.50**

Complete reference library of maps — set of 4 as listed above . . . postpaid **\$3.75**

See your favorite dealer or order direct.

WRITE FOR
FREE
BROCHURE!


RADIO AMATEUR




callbook INC.

Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

An Incomparable Pair

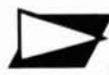 **signal/one**

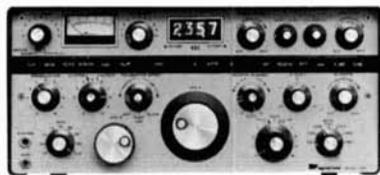

*State-of-the-Art
Equipment of the
Seventies*




**Now greater quality
and reliability
than ever before**



CX7A — DELUXE INTEGRATED STATION TOP-OF-THE-LINE	\$2395.00
CR-1200 — SINGLE VFO RECEIVER	\$1095.00
CR-1500 DUAL VFO RECEIVER	\$1650.00
CT-1500 TRANSMITTER	\$1450.00
CX-10 INTEGRATED STATION	\$1795.00
PS-10 A/C SUPPLY	\$ 210.00
SC-10 CONSOLE	\$ 350.00
400 Hz CW FILTER	\$ 69.50
250 Hz CW FILTER	\$ 160.00
CX7S SPEAKER	\$ 39.95

ALPHA 77

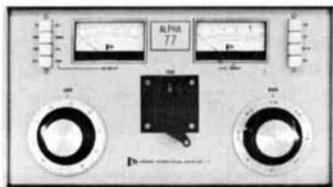

Featuring the new Giant
from Eimac, the 8877 air-
cooled grounded-grid triode,
with a conservative 1500 watts
of plate dissipation.



**VOLUME PRODUCTION
NOW ALLOWS A NEW
FACTORY-DIRECT-DEALER PRICE:**

\$1495



Extremely reliable, trouble-free operation
is the basis of our new Alpha Warranty:
12 months on all parts & labor. Tube
warranty by Eimac.

24 months on the 1500 watt power
transformer and oil-filled capacitor.

You can buy with confidence with the
longest-strongest warranty in the industry.

Phone/write DON PAYNE, K4ID, for a brochure, personalized service,
and a KING-SIZE trade-in on any gear you have — one piece — or
the whole station.

PAYNE RADIO

Box 525

Springfield, Tenn. 37172

Phone

Six Days (615) 384-5573

Phone

Nites-Sundays (615) 384-5643

The BEST CW in the world!

comes from Keyers by



MEMORY-MATIC 8000 Deluxe Keyer

The unquestioned leader in the keyer field. Up to 8000 bit easy-to-use memory capacity allows storage of up to eight complete message sequences. More features than you've ever imagined. The contesters' and traffic handler's dream keyer.

Complete details in our exciting free catalog.

MEMORY-MATIC 500B Keyer

Easy-to-use 500 or 800 bit read/write memory offers complete flexibility to automate your CW station the modern Data Eng. way. Keep up with the winners with this exciting keyer. Send for full details.

Sh. wt. 4 lbs. with 500 bit memory \$198.50
with 800 bit memory \$219.50

SPACE-MATIC 21-B

The Switchable Keyer. It's up to eight-keyers-in-one. Use the switches to make this your very own personal keyer, both today and tomorrow. Add such features as dot dash memory or adjust spacing with the turn of a switch. Completely versatile, completely perfect with everything you will ever want. Full details in our catalog.

Sh. wt. 4 lbs. \$89.50

CRICKET 1

At last — a popularly priced IC keyer with more features for your dollar than all others in its price range. Fatigue-free sending with clean, crisp CW at all speeds.

Sh. wt. 3 lbs. \$49.95

FEATHER TOUCH KEY

Replace that mechanical key with our new electronic key. Go modern with Feather Touch the electronic key that detects the mere touch of your finger. Develop a truly professional fist.

Sh. wt. 2 lbs. \$22.95

adapted to MM-8000 & MM-500B \$27.95

MST-60

Synchronize your Meteor, Tropo, or Moon Bounce communications with WWV for transmission at 15, 20, 30 and 60 second intervals with this precision Meteoric Scatter Timer.

Sh. wt. 2 lbs. \$49.50

Send for FREE Catalog ● 5 Year Guarantees

Send today or use "Check-Off" to get our exciting new catalog describing the most complete line of electronic keying equipment available plus many other exciting accessories for your station.

DATA ENGINEERING INC.



Ravensworth Industrial Park, Springfield, Va. 22151



FMS-3

The frequency marker that gives you more. Just right for band edge markers for 160 to 10 meter bands.

Sh. wt. 2 lbs. \$32.95
(less batteries)

FMS-5

Designed specifically for the FMer. This deluxe frequency standard allows precise calibration of all receive and transmit crystals in the 10, 6, 2 and 1 1/4 meter FM bands. No more off frequency operation with the FMS-5.

Sh. wt. 2 lbs. \$44.50
(less batteries)

2-METER PREAMP

Specially made for both OLD and NEW receivers. The smallest and most powerful preamp available. Provides 20dB gain to bring in the weakest signals.

Sh. wt. 4 oz. \$9.50 kit
\$12.50 wired


BROADBAND PREAMP

Unable to hear those weak signals? Been missing that rare DX? If so, it's time for our DX "getter". Give your receiver a boost. 1-30 MHz. 36dB gain 160-40 meters, dropping to 19dB on 10 meters.

Sh. wt. 6 oz. \$17.95



flea market

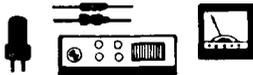

■ **RATES** Commercial Ads 25¢ per word; non-commercial ads 10¢ per word payable in advance. No cash discounts or agency commissions allowed.

■ **COPY** No special layout or arrangements available. Material should be typewritten or clearly printed and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** can not check out each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue. Deadline is 15th of second preceding month.

■ **SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

"DON AND BOB" GUARANTEED GOODIES. HyGain TH6DX 139.00; TH3MK3 114.00; Hyquad 109.00; 204BA 129.00; Mosley CL33 124.00; CL36 149.00; MCQ3B quad 91.00; Ham-M 99.00; TR44 59.95; Belden 8448 Rotor Cable 10¢/ft.; CDE parts stock; Belden 8214 RG8/U foam 16¢/ft.; 8237 RG8/U 15¢/ft.; Gladding 25 212.50; with AC 255.00; SBE144 209.00; SBE450 (list 399.00) 339.00; Leader 810M GDM 49.95; Mallory 2.5A/1000PIV epoxy diode 29¢; MOT MC1709CG (709) OPAMP T05 39¢; Clairex 604 photocell 1.00; Write quote Triex, Drake, Eimac, Leader, Clegg FM27B, Calrad; Tempo Kenwood dealer. Late Special: 21AWG hookup wire, stranded, 50¢/100 ft.; 3.00/1000 ft.; TDK C60LN cassette 1.49 ea; Shipping charges collect; Mastercharge, BAC, warranty guaranteed. Madison Electronics, 1508 McKinney, Houston, Texas 77002. (713) 224-2668.

MOTOROLA: Used radios, equipment and parts. SASE for list. W9ZPP, Box 6073, Evansville, Ind. 47712.

COLLINS mechanical filters 455 kHz., 2.4 kHz bandwidth. \$11.00 postpaid. V. Mozarowski VE3AIA. 1 Belgrave Dr., Islington, Ontario, Canada.

FOR SALE — Transceiver, brand new EICO 753 SSB/AM/CW 80, 40, 20 meters, 200 watt, transistorized, VFO, with AC supply and 12 volt DC supply \$250. Harry McCall, Sparta, N. C. 28675, work, 372-8499; home 372-8655.

HOOSIER ELECTRONICS — Your ham headquarters in the heart of the Midwest where only the finest amateur equipment is sold. Individual personal service by experienced and active hams. Factory-authorized dealers for Drake, Regency, Standard, Ten-Tec, Hy-Gain, CushCraft, Mosley, Ham-M, plus many more. Orders for in-stock merchandise shipped the same day. Write today for our low quote and try our personal, friendly Hoosier service. Hoosier Electronics, R. R. 25, Box 403, Terre Haute, Indiana 47802.

QSLs. Second to none. Same day service. Samples 25¢. Ray, K7HLR, Box 331, Clearfield, Utah 84015.

FOR YOUR FUTURE ROBYN RADIOS send your order to, Two Way Radio Sales, 1501 Monroe Street, Bogalusa, La. 70427 or 202 Farrell Street, Picayune, Miss. 39466.

DISCOUNTS! Standard Sonar, Clegg, Gladding, Geneva, Mosley, Rohn, Tri-Ex, others. Also marine and CB. Lowest prices. State needs. Arena Communications, Dept. H, 1169 N. Military Highway, Norfolk, Virginia 23502.

WANTED: tubes, transistors, equipment what have you? Bernard Goldstein, W2MNP, Box 257, Canal Station, New York, N. Y. 10013.

22nd ANNUAL DAYTON HAMVENTION will be held on April 28, 1973 at Wampler's Dayton Hara Arena. Technical sessions, exhibits, hidden transmitter hunt, flea market, and special program for the XYL. For info write Dayton Hamvention, Dept. H, Box 44, Dayton, Ohio 45401.

WORLD QSL — See ad page 92

TECH MANUALS for Govt. surplus gear only \$6.50 each: R-388/URR, R-389/URR, R-390/URR, URM-25D, RCK, TT-63A/FGC, CV-591A/URR, TS-497B/URR, TS-34A/AP, R-220/URR. Hundreds more. Send 50¢ (coin) for 20-page list. W3IHD, 4905 Roanne Drive, Washington, D. C. 20021.

UHF FET PREAMPLIFIER. 440-470 MHz. Mobile or fixed. At least 6db gain (10db typical). Power source +10V to +15V. 10ma drain or less. RCA phono type jacks. 1½ x 1½ x 1¾ inches, fully shielded. Price includes taxes. \$18.00 Prepaid U.S.A. Electronics Enterprises, 6606 Fifth Street, Rio Linda, Ca. 95673. (916) 991-2010.

TUBES save \$\$\$\$ send RFQ: Tubes International, Wainright, Ak. 99782.

TOROIDS, iron "E" powder 80-10 meters. .500" — 8/\$1.00, .940" — 4/\$1.00, 1.437" — 75¢ each or 3/\$2.00, 2.310" — \$1.50 or 3/\$4.00. Please include 50¢ postage, slightly more on large orders. Fred Barken, WA2BLE, 274 E. Mt. Pleasant Ave., Livingston, N. J. 07039.

ROCHESTER, N. Y. is the place to go for the largest Hamfest, VHF meet and flea market in the northeast, May 12th. Write WNY Hamfest, Box 1388, Rochester, N. Y. 14603.

2N3632's BRAND NEW, \$2.50 each, three for \$7, WA2K0I, L. Schoenig, 207 Woodlawn, Williamstown, N. J. 08094.

SP200 RECEIVER with power supply in running condition. \$50.00 or best offer. Other items for sale or trade also. Mike Kane, WA1PJG, 50 South Porter, Manchester, N. H. 03103, 603-622-5320.

REPAIR TV TUNERS — High earnings, complete course details, 12 repair tricks, many plans, two lessons, all for \$1. Refundable. Frank Boccek, Box 3236 (Enterprise Branch), Redding, Ca. 96001.

SELL: ART-13, 2-18MHz, 200W A1A3 with P. S. No shipping. \$60. Chas. Wallace, W11B, 8 Elaine St., Hampton, N. H. 03842.

USED MYLAR TAPES — 1800 foot. Ten for \$8.50 postpaid. Fremerman, 4041 Central, Kansas City, Mo. 64111.

HOLIDAY 1973, destination Southern Ireland. Exchange unwanted gear for guesthouse accommodation. Pursue hamming, fishing, sport, recreation interests. Des Walsh, EI5CD, Ballylynch Carriek-on-Suir, Ireland.

SAVE MONEY on parts and transmitting-receiving tubes. Foreign-Domestic. Send 25¢ for giant catalog. Refunded first order. United Radio Company, 56-HR Ferry Street, Newark, N.J. 07105.


SALES: COLLINS CC-3 CARRYING CASES for KMW-2 Power Supply and/or other accessories. Excellent condition. \$20 each FOB origin. Only 8 available. Money order or certified check to Oleg Kolen, W7LU, 2916 Oriole Drive, Sierra Vista, Ariz. 85635.

WANTED: JULY 1969, Ham Radio magazine. Andy Kalayta, 7645 N. Crawford, Skokie, Illinois 60076.

TELL YOUR FRIENDS about Ham Radio Magazine.

Semiconductor Supermart

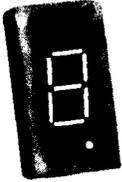• MOTOROLA • RCA • FAIRCHILD • NATIONAL • HEP • PLESSEY •



Actual Size

DIGITAL READOUT

At a price everyone can afford **\$3.20**

- Operates from 5 VDC
- Same as TTL and DTL
- Will last 250,000 hours.

The MiNiTRON readout is a miniature direct viewed incandescent filament (7-Segment) display in a 16-pin DIP with a hermetically sealed front lens. Size, and appearance are very similar to LED readouts. The big difference is in the price. Any color filter can be used.

INTRODUCING *NEW* DEVICES AT NEW LOW PRICES

LA3018 (replaces CA3018)	\$1.60
LA3046 (replaces CA3046)	\$1.60
LS370 (replaces LM370)	\$4.00
LS1496 (Improved MC1496)	\$2.00
LS3028A (replaces CA3028)	\$1.60
LP1000 (a new fun-type device to make LED flashers, audio osc, timer, etc.)	\$1.60

Coming soon the LP2000 Micro-transmitter in a 10-pin IC package.

NATIONAL DEVICES

LM370 AGC/Squelch amp	\$4.85
LM373 AM/FM/SSB IF strip/Det	\$4.85
LM309K 5V 1A regulator. If you are using TTL you need this one.	\$3.00

POPULAR IC's

MC1550	Motorola RF amp	\$1.80
CA3020	RCA 1/2 W audio	\$3.07
CA3020A	RCA 1 audio	\$3.92
CA3028A	RCA RF amp	\$1.77
CA3001	RCA	\$6.66
MC1306P	Motorola 1/2 W audio	\$1.10
MC1350P	High gain RF amp/IF amp	\$1.15
MC1357P	FM IF amp Quadrature det	\$2.25
MC1496	Hard to find Bal. Mod.	\$3.25
MFC9020	Motorola 2-Watt audio	\$2.50
MFC4010	Multi-purpose wide-band amp	\$1.25
MFC8040	Low noise preamp	\$1.50
MC1303P	Dual Stereo preamp	\$2.75
MC1304P	FM multiplexer stereo demod	\$4.95

FET's

MPPF102	JFET	\$.60
MPPF105/2N5459	JFET	.96
MPPF107/2N5486	JFET VHF/UHF	\$1.26
MPPF121	Low-cost dual gate VHF RF	.85
MFE3007	Dual-gate	\$1.98
40673		\$1.75
3N140	Dual-gate	\$1.95
3N141	Dual-gate	\$1.86

MOTOROLA DIGITAL

MC724	Quad 2-input RTL Gate	\$1.00
MC788P	Dual Buffer RTL	\$1.00
MC789P	Hex Inverter RTL	\$1.00
MC790P	Dual J-K Flip-flop	\$2.00
MC799P	Dual Buffer RTL	\$1.00
MC780/880	RTL decade counter	\$3.00
MC1013P	85 MHz Flip-flop MECL	\$3.25

MOTOROLA TUNING DIODES

Silicon voltage variable capacitance diodes in TO-92 plastic case like plastic transistors. Both standard Motorola and HEP numbers are listed; devices are same. Capacitance value is typical at -4Vdc. Tuning ratio is approx. 3:1.

MV2101/R2500	6.8 pF	\$1.10
MV2103/R2501	10 pF	\$1.10
MV2105/R2502	15 pF	\$1.10
MV2109/R2503	33 pF	\$1.10
MV2112/R2504	56 pF	\$1.10
MV2115/R2505	100 pF	\$1.10

MORE RCA IC's

CA3088E	AM rcvr subsystem	\$2.50
CA3089E	FM IF system with circuits for IF amp., Det., AF preamp., AFC, Squelch, & tuning meter	\$3.90
CA3018	Transistor array	\$1.55

NEW FAIRCHILD ECL HIGH SPEED DIGITAL IC's

9528	Dual "D" FF toggles beyond 160MHz	\$4.65
9582	Multi-function gate & amplifier	\$3.15
95H90	300 MHz decade counter	\$16.00

A 95H90 & 9582 makes an excellent prescaler to extend low frequency counters to VHF — or use two 9528s for a 160 MHz prescaler.

Box 3047H, Scottsdale, AZ 85257

CIRCUIT SPECIALISTS CO.

Please add 35¢ for shipping

FACTORY AUTHORIZED
HEP-CIRCUIT-STIK
DISTRIBUTOR

MODERNIZE FOR PEANUTS! Frame & Display QSL's with 20 pocket plastic holders. Two for \$1.00, seven for \$3.00. Prepaid, guaranteed. Universally used and approved. Order now. TEPABCO, Box 198H, Gallatin, Tennessee 37066.

PRINTED CIRCUIT DRILL BITS. Trumbull, 833 Balra Drive, El Cerrito, California 94530.

WANTED: GOOD MODEL 19 RTTY. Quote price delivered to my QTH. Cline, Box 216, Logan, Utah 84321.

FOR SALE SB 401 excellent, on 80-10. Going MARS. \$240. UHF AMP Dumont with 2 new 4cx250K's. 50¢ for photo. \$150. AL K4AVQ/3, 20 Lepore Dr., Lancaster, Pa. 717-392-4237.

FIGHT TVI with the RSO Low Pass Filter — p115 March 73 — write for brochure — Taylor Communications Manufacturing Company, Box 126, Agincourt, Ontario, Canada.

SURPLUS MILITARY RADIOS, Electronics, Radar Parts, tons of material for the ham, free catalogue available. Sabre Industries, 1370 Sargent Avenue, Winnipeg 21, Manitoba, Canada.

TECHNICAL MATERIEL CORPORATION GOODIES, TRC-500 antenna coupler \$27.50, FFR receiver (with all heads) \$100.00, AKT-7 100W 220MHz amplifier \$30.00, TS-497B \$150.00, TS-382D \$50.00, much more, SASE for 5 page list. Wanted: E and E Radio Handbooks, 14th Edition and earlier, 2M walkie, GPR-90/GSB-1 receiver. Richard Solomon, 5 Cherry St., Lexington, Massachusetts 02173.

SCALERS — Complete units. 260MHz unit \$70; high sensitivity 280MHz unit \$90. Add Calif. tax and \$1.50 shipping. Guaranteed. W6PBC, Belmont Spectrum Research, 1709 Notre Dame, Belmont, Calif. 94002.

WE BUY ELECTRON TUBES, diodes, transistors, integrated circuits, semiconductors. ASTRAL ELECTRONICS, 150 Miller Street, Elizabeth, N. J. 07207. (201) 354-2420.

SEND PERFECT C.W. WITH YOUR TELETYPE! Connect the TMC-1 into your loop and it will reproduce in perfect Morse whatever appears in the loop. 64-letter buffer memory produces smooth output even with unsteady input, giving better performance than Morse keyboards or memory keyers. All on one 4 x 6 inch circuit board. Wired and tested with tech manual, \$310, Tech manual only \$25. Write for information. Petit Logic Systems, Box 51, Oak Harbor, Washington 98277.

QSL'S — BROWNE W3CJ — 3111B Lehigh, Allentown, Pa. 18103. Samples 10¢. Cat catalogue 25¢.

TELETYPEWRITERS — Kleinschmidt — portable, fixed, sets, punches, parts, reconditioned, reasonable. Mark/Space Systems, 3563 Conquista, Long Beach, Calif. 90808. 213-429-5821.

F.C.C. TYPE EXAMS GUARANTEED to prepare you for the F.C.C. 3rd., (\$7.00), 2nd. (\$12.00), and 1st (\$16.00), phone Exams; complete package, \$25.00. Research Company, Dept. D. Rt. 2, Box 448, Calera, Alabama 35040

CANADA'S MOST UNUSUAL Surplus and Parts Catalog. Jam packed with bargains and unusual items. Send \$1. ETCO-HR, Box 741, Montreal, Canada.

1973 DESK CALENDAR, 12 x 9. Name, address, call in gold, \$2.00. Henry Morgan, 883 Diana, Akron, Ohio 44307.

RESISTORS: Carbon Composition brand new. All standard values stocked. 1/2 watt 10% 50/\$1.00; 1/4 watt 10% 40/\$1.00. 10 resistors per value please. Minimum order \$5.00. Post paid. Pace Electronic Products, Box 161-H, Ontario Center, New York 14520

RECIPROCATING DETECTOR KIT. Send SASE to, Peter Meacham Associates, 19 Loretta Road, Waltham, Mass. 02154.

RTTY SPEED CONVERTER. A drilled 4" x 6 1/2" PCB and all components except input output jacks, power supply and chassis. See Dec. '71 and Oct. '72 issue of Ham Radio. \$40.00 postpaid. PCB only \$6.00. P & M Electronics, Inc., 519 South Austin, Seattle, Washington 98108.

DIGITAL AID

Learn by doing. Draw your own digital logic diagrams. Logic drawing template with instructions for reading and drawing standard gate and flip flop symbols. Timing diagrams introduced. Send \$1.98 plus 20¢ post.

STELCOMP SCIENTIFIC
4600 Duke St.
Alexandria, Va. 22304

SUPER RIG

**STATE OF THE ART 2-METER FM
22 CHANNELS - PRICE \$289.50**

Brand new, just released INOUE IC-22. Same size as IC-20. 22 Channels, 10+ watts. Super hot recvr. Better than .4µV/20db. Order yours now or SASE for more info.

206-747-8421 evenings
NHE COMMUNICATIONS

15112 S. E. 44th — Bellevue, WA. 98006

FM Schematic Digest

A COLLECTION OF
MOTOROLA SCHEMATICS

Alignment, Crystal, and Technical Notes
covering 1947-1960

136 pages 11 1/2" x 17" ppd \$6.50

S. Wolf

P. O. Box 535

Lexington, Massachusetts 02173

WATERBAGS*

TOROIDS • TELETYPE • FAX



Toroids

88 millihenry. Never potted.
Center tapped. 5/\$2.50 ppd.
30/\$10 ppd US.

Ribbons

For all model 14-15-28-32-33-Lorenz-Mite. FRESH Black nylon, 12 per box. 1 box/\$3.50 postpaid US.

Deskfax

Transceiver Model 6500A
Checked and ready to operate on the landline-or on the air. Contains receiving and transmitting AFSK units.
SPECIAL \$15 each, 2/\$25, 7/\$50



Fax Paper

12" x 19" sheets. For RC-92 or TXC1 FAX. Or cut 'em up for use on the Deskfax 6500A. 250 sheets per package. 1 pkg/\$3, 5 pkg/\$12.

Teletype Paper

Single copy roll teletype paper. Standard 8-1/2" width. 5" diameter fits all machines. 12 rolls/\$13.

Perforator Tape

11/16" wide. FRESH. 40 rolls only \$8.

February Special!

NEW 3GP1
SCOPE TUBES
(Similar to 3AF1)
\$3.00 ppd US.

Van's W2DLT Electronics

STAMP FOR CATALOG

* LIMITED QUANTITY - New 1-gallon waterbags for camping or trips. A steal at only \$2.95 ppd US.

302H Passaic Avenue
Strling, NJ 07080
201-647-3639



DRAKE TR-22

Versatility plus!... in a 2 Meter FM Transceiver



Complete with: Dynamic Mike, O-T-S Carrying Case, 120 VAC and 12 VDC Cords, Speaker/Headphone Plug and 10 Ni-Cad Batteries.

\$199⁹⁵ Amateur Net

AA-22 Amplifier \$149.95
MMK-22 Mobile Mount \$9.95
BBLT-144D Hustler Ant. \$27.95

Over-the-shoulder, mobile, or at home

Completely transistorized, compact, portable. Capacity for 6 channels. Built-in telescoping antenna, and connector for external antenna. Use barefoot or with accessory amplifier. External 12 VDC or internal ni-cad batteries, built-in 120 VAC battery charger.

GENERAL: • Freq. coverage: 144-148 MHz • 6 channels, 3 supplied • Push-to-talk Xmit • DC Drain: Rcv, 45 mA; Xmit, 450 mA • Size: 5-3/8" x 2-5/16" x 7-1/8", 3-3/4 lbs.

RECEIVER: • Transistorized crystal-controlled superhet • 1st IF: 10.7 MHz, 2nd IF: 455 kHz • Ant. Input Imped: 50 ohms • Sensitivity: 1 μ V or less/20 dB S+N/N • Audio Output: 0.7 W • Built-in speaker.

TRANSMITTER • RF Output over 1 W • Freq. Dev. adj. to 15 kHz max., factory set to 5 kHz.

R. L. DRAKE COMPANY



DRAKE

540 Richard St., Miamisburg, Ohio 45342
Phone: (513) 866-2421 • Telex: 288-017



Indispensable to any DX'er W9IOP's SECOND OP 6th Edition - Fully computer revised

This wonderful operating aid immediately tells the prefix, continent, DX Zone, Country name, local beam heading, time differential, QSL Bureau and postal information for every recognized DX country. Don't go another day without this great tool.

Just \$2.00 postpaid

Comtec, Greenville, NH 03048

NOW

EXCLUSIVE 66 FOOT

MDR GAIN

75 THRU 10 METER DIPOLE

NO TRAPS - NO COILS - NO STUBS - NO CAPACITORS

Fully Air Tested - Thousands Already in Use



IS BACK

#16 40% Copper Weld wire annealed so it handles like soft Copper wire—Rated for better than full legal power AM/CW or SSB-Coaxial or Balanced 50 to 75 ohm feed line—VSWR under 1.5 to 1 at most heights—Stainless Steel hardware—Drop Proof Insulators—Terrific Performance—No coils or traps to break down or change under weather conditions—Completely Assembled ready to put up—Guaranteed 1 year—ONE DESIGN DOES IT ALL; 75-10HD—ONLY \$12.00 A BAND!

Model 75-10HD ... \$60.00 ... 66 Ft. ... 75 Thru 10 Meters	Model 75-40HD ... \$40.00 ... 66 Ft. ... 75 Thru 40 Meters
Model 75-20HD ... \$50.00 ... 66 Ft. ... 75 Thru 20 Meters	Model 40-20HD ... \$33.00 ... 35 Ft. ... 40 Thru 20 Meters
Model 80-40HD ... \$42.00 ... 69 Ft. ... 80-40-15 Meter (CW)	

ORDER DIRECT OR WRITE FOR FULL INFORMATION

MDR GAIN

300H Shawnee
Leavenworth, Kansas 66048

OR THRU YOUR FAVORITE DISTRIBUTOR

MEASUREMENTS CORP. MODEL 80, 2-400MHz. Mint. \$150, will deliver. Also audio sig. gen., audio triggered scope. Ten-Tec RX10 \$25, QRP rig. Eric, K1PCT, 617-646-6631, eves.

NOVICES: Heath DX-60A transmitter, HG-10B VFO. Lafayette HA-350 receiver, all for \$150.00. Will throw in all cables and T/R switch for complete setup. Mike, WA2IMC, 248 Bay Avenue, Patchogue, N. Y. 11772. Landline 516-475-8454.

HELP! Need HR March '70, '71. QST Jan, Feb., '62; July, Aug., Oct., Nov., '65; Feb., Nov., '66. Can swap with any other copy of HR or how much. Eskil Persson, SM5CJP, Frotunagrund, 1,S-19400 Upplands Vasby, Sweden.

VHF NOISE BLANKER — See Westcom ad in Dec. '70 and Mar. '71 Ham Radio.

THE LaPORTE, INDIANA AMATEUR RADIO CLUB will hold it's Annual Swap-fest and Auction on the 4th of February, 1973, beginning at Noon. Location is the Civic Auditorium, and there will be talk-in on 94, 22-82 and 3910 kHz.

NEW SCANNER BOOK from Sams. Includes comprehensive servicing data for 30 popular UHF and VHF Scanner - Monitor receivers including models by B & K, Browning, Johnson, Midland, Pace, Pearce-Simpson, Penney's, Realistic, Sonar and Teubury. Just \$4.95 postpaid from Comtec, Greenville, N. H. 03048.

TEXAS VHF-FM SOCIETY 1973 winter meeting in Brownsville February 24 and 25 at Fort Brown Hotel. Submit your reservation request now so that you may be assured of a room as space is at a premium. On Saturday afternoon, especially for the ladies, there will be a guided sight-seeing and shopping tour of Matamoros. It will be a great meeting. There will be some excellent technical talks and an in-depth discussion of the new repeater rules. For details contact Art Ross, W5KR, Meeting Coordinator, P. O. Box 3561, Brownsville, Texas 78520.

THE LAKE COUNTY (Indiana) Amateur Radio Club, Inc., proudly announces its 20th annual Radio Club Banquet to be held at the Scherwood Club, 600 East Joliet St., Schererville, Ind. The date is Saturday, February 10, 1973, and the affair starts promptly at 6:30 p.m., CST. Awards, music, speeches, food — all you can eat — entertainment, good fellowship. Bring your wife, family, or girlfriend. Tickets are \$5.00, each, and are available from Herbert S. Brier, W9EGQ, 385 Johnson St., Gary, Indiana 46402, or from other club members. Positively no tickets sold at door.

SOME MEMBERS of the Aircraft Owners and Pilots Association (AOPA) are organizing a society of "Flying Hams," to be roughly similar to other flying groups such as the Flying Doctors, etc., the purpose being to combine the two great activities of flying and hamming for mutual benefit and public service. Fly-ins and nets will be part of the activity and the use of flying repeaters has been mentioned. Additional information can be obtained from Dick Ertman (AOPA 329499), 94 Spruce Street, Apponaug, Rhode Island 02886. Comments are welcomed.

SURPLUS CERAMIC 7289 (3CX100A5) and glass 2C33A tubes. Prechecked 449mc, guaranteed ICAS. \$3 ea., \$30 doz., plus postage. Ed Howel W4SOD, Folly Beach, S. C. 29439.

BETTER BALTIMORE HAMBOREE, Sunday April 8 at 10 a.m., Calvert Hall College, Goucher Blvd. and LaSalle Road, Towson, Maryland 21204 (1 mile south of Exit 28 Beltway-Interstate 695), Food Service, Prizes, Flea Market, registration \$2.00. No table charge or percentage. INFO. Contact W4WVC at school address.

NEED IMMEDIATELY: 2 J-28 and C-42/ARC-5 junction & control units. Also wanted, 2 FT-220A & MT-71 mounting racks; Write WB8NLM, 146 Schonhardt St., Tiffin, Ohio 44883.

YOUR AD belongs here too. Commercial ads 25¢ per word. Non-commercial ads 10¢ per word. Commercial advertisers write for special discounts for standing ads not changed each month.

DIGIPET-60

Digipet-60 Frequency Counter

1 KHz-60 MHz
(130-160 MHz with
optional converter)
(Reg. \$299)

SEE NOV. '72 "CQ" REVIEW



A frequency counter with a range of 1 KHz to 60 MHz (or 130-160 MHz when used with our Digipet-60 Converter). With a resolution of 1 KHz or 1 Hz (at 1 ms. or 1 s. gate times). It can be operated on either AC or DC, with complete overload protection. Plus a stability aging rate of 1 part in 10⁶/week. And the whole unit is a mere 7" deep by 2 1/2" high!

Superb precision quality at less than kit prices. Call or write for literature and trade in or our **LOW INTRODUCTORY PRICE. 1 YEAR WARRANTY. NO ONE ANYWHERE BEATS OUR DEAL!**



AMATEUR-WHOLESALE ELECTRONICS
8817 S.W. 129 Terrace • Miami, FL 33156
Days (305) 233-3631
Nights-Weekends (305) 666-1347

HELP WANTED! Two Way radio technicians. Must have experience with GE Tube and Solid State FM Equipment. Excellent wages. Health Insurance and Pension Plan. State experience, qualifications and previous employment in this field.


**DON COOK
COOK'S COMMUNICATIONS CORPORATION**
160 N. Broadway, Fresno, Ca. 93701
209-233-8818

EK-404 DELUXE KEYS \$124.95

- ALL THE FEATURES YOU'VE ASK-ED FOR
- 115VAC AND -12VDC
- READ JAN 1972 CO AND MAR. 1972 QST FOR REVIEW OF SIMILAR EK-402 PROGRAMMABLE KEYS

WRITE FOR BROCHURES

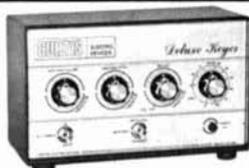GURTS ELECTRO DEVICES BOX 609 • MOUNTAIN VIEW, CALIFORNIA, 94040 • TEL. (415) 964-3136



CRYSTAL BARGAINS

Depend on . . .

We supply crystals from 16kHz to 100MHz. Over 6 million crystals in stock.



DIVISION OF BOB WHAN & SON ELECTRONICS, INC.

2400 Crystal Dr.
Fort Myers
Florida 33901
(813) 936-2397

SPECIAL

Crystals for most amateur 2-Meter F.M. Transceivers:

\$3.75 Each

Inquire about quantity prices. Order direct. Send check or money order.

For first class mail add 15¢ per crystal...for airmail add 20¢ ea.

Send 10¢ for new catalog with oscillator circuits and lists of thousands of frequencies in stock.

SPECIALS! CRYSTALS FOR:

Frequency Standards		
100 KHz (HC13/U)		\$4.50
1000 KHz (HC6/U)		4.50
Almost All CB Sets, Trans., or Rec.		2.50
(CB Synthesizer Crystal on request)		
Any Amateur Band in FT-243 (Except 80 meters)	4	for 5.00
80 Meter Range in FT-243		2.50
Color TV 3579.545 KHz (wire leads)		1.60
	4	for 5.00

NEW! FROM MATRIC

QUALITY GEAR LOADED WITH FEATURES!



MODEL 10 • KEYER MODEL 11 • PADDLE

No bulky batteries or awkward power cords with the Model 10 Keyer. Internal penlight cells and reed relay output produce a compact, portable, and versatile unit. Also available as a circuit board kit without case for custom installation.

Keyer Kit	\$21.90
Keyer Assembled	\$26.50
P. C. Board Kit	\$12.95
Sidetone Kit	\$ 4.95
Sidetone Assembled	\$ 6.95
Paddle Assembled	\$ 9.95




MODEL 20 DIGITAL DIAL

Tune your fixed or mobile transmitter, receiver, or transceiver with 100 Hz accuracy and no last digit jitter. The Model 20 Digital Dial connects to rigs with 5-5.5 Mhz VFO's with a single wire. It can also be used as a general purpose frequency counter.

Matching accessories coming soon.

Assembled and Tested	\$169.95
Crystal Time Base	\$ 29.95

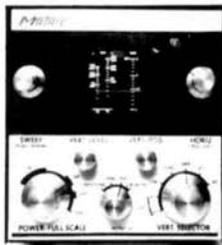

MODEL 31 MONITORSCOPE

Monitor RF output, read power output to 1500 watts, measure SWR to 3:1, and observe RTTY and trapezoid patterns all in a single instrument! The Model 31 also includes an RF actuated CW monitor, two-tone generator, and AC and DC vertical and horizontal inputs for general purpose use.

Assembled and Tested	\$169.95
----------------------------	----------



SEE YOUR DEALER OR ORDER DIRECT. PRICES F.O.B. SENECA, PA.

BOX 235 • SENECA, PA. 16346 • PHONE: AREA CODE (814) 648-5122

FM YOUR GONSET

(or your Clegg 22'er, Poly-Comm 2, PC-62, Johnson 6N2, Aerotron 500, HA-460, TX-62 or VHF-1)

- New! Plug-in modulator puts the Communicator transmitter on FM.
- No modification or rewiring on your Communicator. Just plug into mike jack and crystal socket.
- Compact self-contained modulator measures 4" x 3" x 1 1/2".



- Works with Communicator I, II, III, IV and GC-105, and other rigs listed.
- FM at a tenth the cost of a new rig.
- Frequency adjust for netting built in.
- Built-in tone burst available. Keyed by push-to-talk switch.
- \$34.50 postpaid U.S.A. \$36.50 for PC-2, PC-62, HA-460. Built-in tone burst \$10.00. Specify transmitter model and tone burst frequency. California residents add 5% sales tax. (HC-6/U crystal and 9 volt transistor battery not supplied.)
- Send for free descriptive brochure.

PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025

— PCB KITS —

RTTY SPEED CONVERTER Drilled PCB	5 & 11 VDC	\$40.00
DRILLED PCB ONLY		\$ 6.00
RTTY AFSK Gen. All Shifts & CW I.C.	9 VDC @ 7ma	\$6.60
100 KHZ XTAL CALIBRATOR Less Xtal	9 VDC @ 2ma	\$4.75
100 KHZ XTAL (Limited Supply)		\$2.50
PREAMP MICROPHONE, 26 DB Gain	9 VDC @ 1ma	\$3.50
LIMITER PREAMP For High Z Mike	9 VDC @ 1ma	\$4.80
PRODUCT DETECTOR For Your Receiver	9 VDC @ 1ma	\$3.60
1 1/2" METER KIT Less 1ma Meter	6.3VAC	\$4.75
SWR METER, Stripline, Less 200ma Meter		\$2.95
WWV CONVERTER 3.5-4.0 Mhz Output	9 VDC @ 5ma	\$5.25
Requires 6-6.5Mhz Crystal		
6 METER CONVERTER FET Front End	9 VDC @ 5ma	\$5.95
7-11 Mhz Output. Less 43 Mhz Xtal		
CW KEYING MONITOR, RF Keyed, Less Spkr.	9 VDC @ 9ma	\$4.70
POWER SUPPLY - 9 VDC @ 50ma Output	115VAC	\$4.85
6 OR 2 METER CASCODE PREAMP	80 VDC @ 4.5ma	\$4.95
Wired & Tested Less 2 ea 6CW4		
Navistors. Specify 6 or 2 Meter Model		
DRILLS, #54, 56, 58 or 60	(each)	\$4.40
Finest Quality for PCB'S, Made in USA	Three For	\$1.00

EXCEPT AS NOTED ABOVE, ALL KITS ARE NEW, 100% SOLID STATE, AND COME COMPLETE WITH AN UNDRILLED G-10 PCB (PRINTED CIRCUIT BOARD) AND ALL PCB MOUNTED COMPONENTS. KITS ARE LESS POWER SUPPLIES, CHASSIS, AND ENCLOSURE HARDWARE. SEND SELF-ADDRESSED, STAMPED ENVELOPE FOR COMPLETE DATA SHEET AND SCHEMATIC.

SATISFACTION GUARANTEED. RETURN IN 30 DAYS FOR REFUND. ALL KITS POSTPAID. INCLUDE 25¢ HANDLING CHARGE. WASHINGTON RESIDENTS ADD 5% SALES TAX.

P. M. ELECTRONICS INC.

519 SOUTH AUSTIN, SEATTLE, WASH. 98108

CUSH-CRAFT JOINS SOLID STATE SYSTEMS

Solid State Systems, Inc. has now become an authorized distributor for Cush-Craft antennas. Call or write for price and availability.

UNIVERSAL DECADE COUNTING UNITS

1. Easy to read single plane LED or Fluorescent Readout with wide angle viewing.
 2. BUD (Buttons), Readout Lamp Test, Ripple Blanking and Louster Reset are available.
 3. Plug-in Module.
 4. Meter Sockets for all IC and Relay.
 5. In-plate 6.10, 2oz Copper, Glass Epoxy Board.
 6. Four choice of 1 to 6 decades, as one P.C. Board.
 7. Grouping of 2 or more readouts on the same display board.
 8. Display board mounts perpendicular to counter/drive board.
 9. Full blown counting and counter proof functions available. See 74192.
 10. 37MHz digital input rate with 74190.
 11. Operates from 5 volt TTL compatible supply.
 12. First in a series of Universal plug-in modules, for frequency counting, time measurements, reset counting, IWM, magnitude comparison etc.
 13. P.C. Boards only are available for \$3.00 per decade.

Price (Per Decade):
 Base Unit consisting of 7490, 7417, 7418 and Type 7 Segment Readout, only \$1.00
 7490, add \$1.50
 For 7417, add \$1.25
 For 7418, add \$1.25
 For 74192, add \$1.00
 For 74190, add \$1.00
 For 74196, add \$0.75
 For Full assembled and tested unit, add \$2.50

Catalog Number	Any Quantity Per Item (Mix)		Multiples of 10 Per Item (Mix)		Catalog Number	Any Quantity Per Item (Mix)		Multiples of 10 Per Item (Mix)				
	1-999	1000 up	100-9999	10000 up		99-999	100-999	999-9999	10000 up			
7100	26	25	23	22	21	74123	1.02	1.00	1.04	.89	.83	
7101	26	25	23	22	21	74141	1.63	1.55	1.46	1.38	1.29	1.20
7102	26	25	23	22	21	74145	1.41	1.33	1.26	1.18	1.14	1.04
7103	26	25	23	22	21	74151	1.20	1.13	1.07	1.01	.95	.88
7104	28	27	25	24	22	74153	1.63	1.55	1.46	1.38	1.29	1.20
7105	28	27	25	24	22	74154	2.43	2.30	2.16	2.03	1.89	1.76
7106	52	50	47	44	42	74155	1.46	1.39	1.31	1.23	1.16	1.08
7107	52	50	47	44	42	74156	1.46	1.39	1.31	1.23	1.16	1.08
7108	52	50	47	44	42	74176	1.62	1.53	1.45	1.36	1.28	1.19
7109	32	30	29	27	26	74177	1.62	1.53	1.45	1.36	1.28	1.19
7110	26	25	23	22	21	74180	1.20	1.13	1.07	1.01	.95	.88
7111	28	27	25	24	22	74482	1.20	1.13	1.07	1.01	.95	.88
7112	58	55	52	49	46	74492	1.98	1.87	1.76	1.65	1.54	1.43
7113	58	55	52	49	46	74493	1.98	1.87	1.76	1.65	1.54	1.43
7114	52	50	47	44	42	74499	2.41	2.62	2.50	2.31	2.10	2.03
7115	52	50	47	44	42							
7116	32	30	29	27	26							
7117	26	25	23	22	21							
7118	26	25	23	22	21							
7119	30	29	27	26	24							
7120	30	29	27	26	24							
7121	30	29	27	26	24							
7122	30	29	27	26	24							
7123	30	29	27	26	24							
7124	30	29	27	26	24							
7125	30	29	27	26	24							
7126	34	32	31	29	27							
7127	34	32	31	29	27							
7128	34	32	31	29	27							
7129	34	32	31	29	27							
7130	34	32	31	29	27							
7131	1.73	1.61	1.55	1.46	1.37	74817	.88	.84	.79	.75	.70	.66
7132	1.25	1.21	1.14	1.07	1.01	74820	.88	.84	.79	.75	.70	.66
7133	1.25	1.21	1.14	1.07	1.01	74822	.88	.84	.79	.75	.70	.66
7134	1.25	1.21	1.14	1.07	1.01	74830	1.00	.95	.90	.85	.80	.75
7135	1.25	1.21	1.14	1.07	1.01	74850	.88	.84	.79	.75	.70	.66
7136	1.25	1.21	1.14	1.07	1.01							
7137	1.16	1.10	1.01	.98	.92	74851	.88	.84	.79	.75	.70	.66
7138	1.16	1.10	1.01	.98	.92	74864	.88	.84	.79	.75	.70	.66
7139	1.16	1.10	1.01	.98	.92	74865	.88	.84	.79	.75	.70	.66
7140	1.16	1.10	1.01	.98	.92	74872	.88	.84	.79	.75	.70	.66
7141	1.16	1.10	1.01	.98	.92	74874	1.82	1.73	1.63	1.54	1.44	1.34
7142	1.16	1.10	1.01	.98	.92							
7143	1.16	1.10	1.01	.98	.92							
7144	1.16	1.10	1.01	.98	.92							
7235	1.16	1.10	1.01	.98	.92							
7236	1.16	1.10	1.01	.98								



Go all the way into the **REPEATER**

There's nothing half-way about the new Hy-Gain *REPEATER LINE*. Designed for the man who demands professional standards in 2 meter mobile equipment, the *REPEATER LINE* is the 2 meter HAM's dream come true. It's got everything you need for top performance... toughness, efficiency and the muscle to gain access to distant repeaters with ease. Reaches more stations, fixed or mobile, direct, without a repeater.


The right antennas for the new FM transceivers...or any 2 meter mobile rig.

Rugged, high riding mobiles. Ready to go where you go, take what you dish out...and deliver every bit of performance your rig is capable of.

- 261 Commercial duty 1/4 wave, claw mounted roof top whip. Precision tunable to any discrete frequency 108 thru 470 MHz. Complete with 18' of coax and connector. 17-7 ph stainless steel whip.
- 260 Same as above. Furnished without coax.
- 262 Rugged, magnetic mount whip. 108 thru 470 MHz. Great for temporary or semi-permanent no-hole installation. Holds secure to 100 mph. Complete with coax and connector. Base matching coil for 52 ohm match. 17-7 ph stainless steel whip.
- 263 Special no-hole trunk lip mount. 3 db gain. 130 thru 174 MHz. 5/8 wave. Complete with 16' coax. Operates at DC ground. Base matching coil for 52 ohm match. 17-7 ph stainless steel whip.
- 264 High efficiency, vertically polarized omnidirectional roof top whip. 3 db gain. Perfect 52 ohm match provided by base matching coil with DC ground. Coax and connector furnished.
- 265 Special magnetic mount. 3 db gain. Performance equal to permanent mounts. Holds at 90 mph plus. 12' of coax and connector. Base matching coil for 52 ohm match. 17-7 ph stainless steel whip. DC ground.
- 269 Rugged, durable, continuously loaded flexible VHF antenna for portables and walkie talkies. Completely insulated with special vinyl coating. Bends at all angles without breaking or cracking finish. Cannot be accidentally shorted out. Furnished with 5/16-32 base. Fits Motorola HT; Johnson; RCA Personalfone; Federal Sign & Signal; and certain KAAR, Aerotron, Comco and Repco units.

2 meter mobile! with

LINE from **Hy-gain**

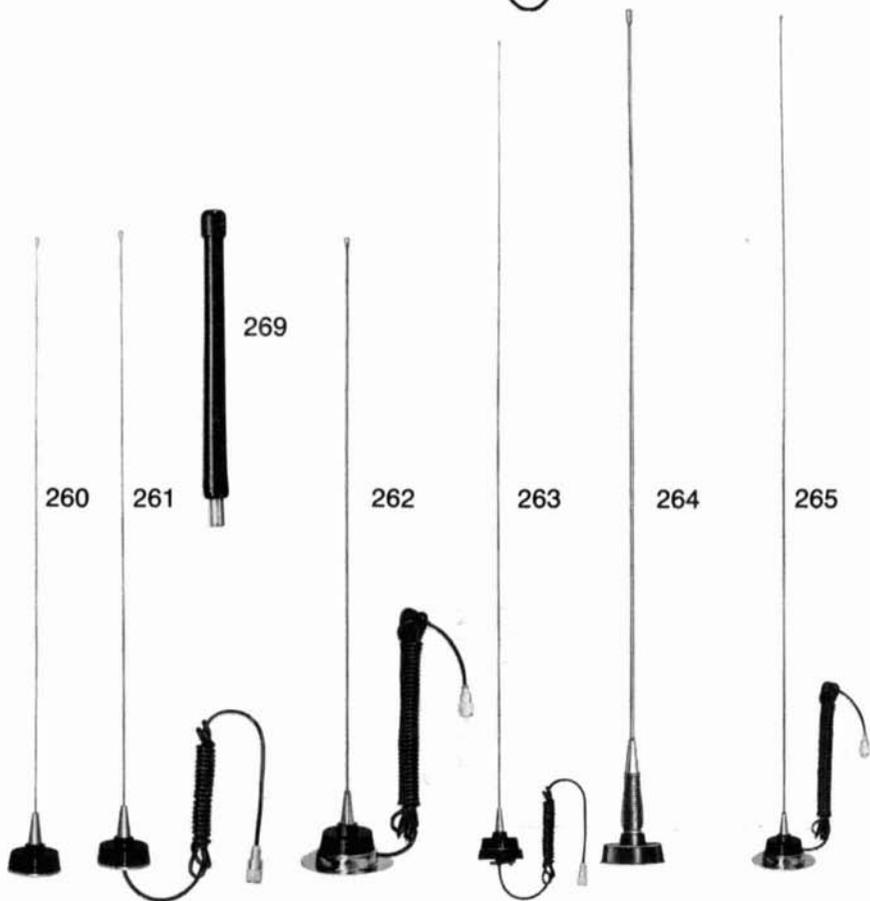

Top performance for 2 meter mobiles
THE REPEATER LINE
from

HY-GAIN ELECTRONICS CORPORATION

BOX 5407-WK / LINCOLN, NEBRASKA 68505

WRITE FOR DETAILS

know this sign



To most people this is a symbol from Greek mythology. But to hundreds of thousands of active amateurs, Pegasus is the symbol of the Radio Amateur CALLBOOK the single most useful operating reference for active amateur stations. The U.S. Edition lists over 285,000 Calls, Names and Addresses in the 50 States and U.S. possessions while nearly 200,000 amateur stations in the rest of the World are listed in the DX edition.

Both editions contain much other invaluable data such as World Maps, Great Circle Maps, QSL Managers around the World, ARRL Countries list and Amateur Prefixes around the World, Time information, Postal Information and much, much more. You can't contest efficiently, you can't DX efficiently, you can't even operate efficiently without an up to date CALLBOOK.

To make the CALLBOOK even more valuable, three supplements are issued each year which bring your copy completely up to date every three months. These are available at a modest extra cost. Full details in every CALLBOOK.

Get your copies of the big new 1973 CALLBOOKS today.

US CALLBOOK
(less service editions)
Just \$8.95

DX CALLBOOK
(less service editions)
Just \$6.95

US CALLBOOK
(with service editions)
\$14.95

DX CALLBOOK
(with service editions)
\$11.45

Mail orders add 50¢ per CALLBOOK postage and handling.

See your favorite dealer or send today to:

WRITE FOR FREE BROCHURE **RADIO AMATEUR callbook INC.**
Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

WORLD QSL BUREAU

THE ONLY QSL BUREAU to handle all of your QSLs to anywhere; next door, the next state, the next country, the whole world. Just bundle them up (please arrange alphabetically) and send them to us with payment of 5¢ each.

5200 Panama Ave., Richmond, CA USA 94804

WANTS TO BUY

All types of military electronics equipment and parts. Call collect for cash offer.

SPACE ELECTRONICS division of
MILITARY ELECTRONICS CORP.

76 Brookside Drive, Upper Saddle River
New Jersey 07458 • (201) 327-7640

Central New York Specialty Headquarters

FM by STANDARD COMMUNICATIONS
and **CLEGG**

ANTENNAS by HY-GAIN

Quality-Selected Used Ham Gear

Write for listing, updated twice monthly

CFP ENTERPRISES

866 Ridge Road
Ludlowville, N. Y. 14862

STATE OF THE ART . . . FM . . .

INOUE IC-20 12 ch., 1 or 10 watts, mobile complete with mike, mount, & 6 Xtaled ch., module cost. \$269.50*

INOUE IC-21, mobile/base unit with AC/DC supply, 24 ch., SWR & Disc. meter, RIT, Calib., mike. \$359.50*

*Customer servicing & warranty inc. Many Xtals avail.
*Write for special after Christmas package price—Save Dollars!

Write or Phone (206-747-8421) for more info. or send cashiers check to: NHE Communications, 15112 S.E. 44th, Bellevue, WA 98006.

ULTRA-BAL 2000

- Advanced design BALUN •
- No radiation from coax, more power to antenna
- Less noise on receive
- Full 2kW - 3 to 30 Mcs., 1:1 or 1:4 ratios.
- Encapsulated ultra weather-proof
- Mil type 2KV Teflon insulation over silver plated wire for ultra low loss.



Specify ratio desired \$ 8.95 ppd.

K.E. Electronics

Box 1279, Tustin Calif. 92680

TTL OPERATING RULES _____ \$ 0.50

MINITRON 5-VOLT 16-PIN DIP READOUT
7-SEGMENT W/RH DECIMAL _____ \$ 3.25
± 1 W/RH DECIMAL _____ \$ 3.25

DIGITAL CLOCK SEMI-KIT _____ \$ 32
15 IC'S & 4 MINITRONS (ONLY) + RED FILTER & INSTR.

DIGITAL CLOCK INSTRUCTIONS ONLY _____ \$ 1.50


QUAD OP AMP LM 3900 _____ \$ 1.15

REGULATOR 5-VOLT 1-AMP UA 7805 _____ \$ 2.50


Arizona Semiconductor

PO BOX 112 GOODYEAR, ARIZONA 85338

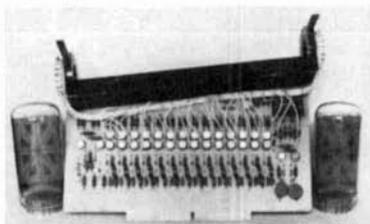GIANT B-7971 NIXIES (2) with 2 sockets and driver board containing hi voltage transistors. Complete plug-in board as removed from operational equipment. Schematics included. Unbelievable but true . . . just \$2.50 for the complete package. #72S-10 \$2.50



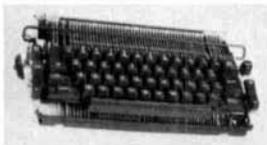ALPHA-NUMERIC keyboard removed from unused IBM Selectric machines. Bargain price at only \$8.00



Please add postage for above.

JOHN MESHNA JR. ELECTRONICS P. O. Box 62 E. Lynn, Mass. 01904


15¢ IC BONANZA

Brand new DTL dual inline (DIP) package, factory marked ceramic type. The price is too good to be true. Fully guaranteed and with specs.

- 930 Dual 4 input NAND gate similar to 7420
- 931 Clocked flip flop similar to 74110
- 932 Dual 4 input Expand Buff similar to 7440
- 933 Dual 4 input expander similar to 7460
- 936 Hex Inverter similar to 7405
- 945 JK Flip Flop similar to 74110
- 946 Quad 2 input gate similar to 7400
- 962 Triple 3 input gate similar to 7410

15¢ each

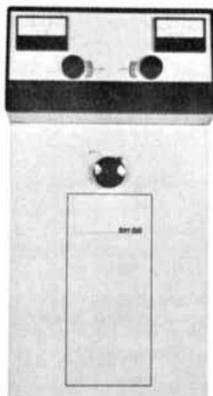Buy \$100 worth and deduct 10%
24 hour delivery guaranteed



THE HENRY 3K-A

COOL AND EASY MAX. LEGAL POWER • SSB CW, RTTY or SSTV THROUGH COMMERCIAL RATINGS • 3.5 TO 30MHz • CONTINUOUS DUTY • SILVER PLATED Pi-L PLATE TANK • DC

RELAYS • ALC • BUILT IN SWR BRIDGE • OUTPUT POWER 2 KW MIN. IN COMMERCIAL SERVICE • THE FINEST COMMERCIAL GRADE AMATEUR LINEAR AMPLIFIER AVAILABLE ANYWHERE IN THE WORLD AT ANY PRICE FOR ONLY \$995. THE HENRY 3K-A. THE LINEAR FOR THE CX-7A

YOU will never know how little it costs to own THE incomparable CX-7A or Henry 3KA until YOU write or phone us and let us know the trade in deal YOU WANT. We usually say yes! NO ONE ANYWHERE BEATS OUR DEAL.



*Credit terms available on export orders to qualified firms.

signal/one CX-7A

* exclusive export agent for signal/one



signal/one

- 160-10 Meters — 300 Watts
- Transceiver or split frequency with two built in VFOs — CW keyer built in
- IF shift — new superior QRM remover
- IF noise blanker — digital nixie frequency readout — superb computer grade construction
- FSK keyer — adjustable output power — broadband tuning — output wattmeter and reflected power meter **\$2395**

AMATEUR-WHOLESALE ELECTRONICS
8817 S. W. 129 Terrace-Miami, FL. 33156

Telephone — days (305) 233-3631
— nights and weekends call (305) 666-1347

Use your Master Charge card

Advertisers check-off

... for literature, in a hurry —
we'll rush your name to the companies
whose names you "check-off"

INDEX

- | | |
|------------------------|---------------|
| —Alpha | —Jan |
| —Amateur-Wholesale | —Janel |
| —Ann Arbor | —Jeff-Tronics |
| —Apollo | —Jensen |
| —Arizona | —K. E. |
| —Barry | —KW |
| —Bauman | —L. A. |
| —Bird | —MFJ |
| —Bramco | —Matric |
| —Budget | —McClaren |
| —CFP | —Meshna |
| —Bitcil | —Military |
| —Caringella | —Mor-Gain |
| —Circuit Specialists | —NHE |
| —Clegg | —Nurmi |
| —Command | —PM |
| —Communications | —Pagel |
| Specialists | —Palomar |
| —Comtec | —Poly Paks |
| —Cook's | —RP |
| —Crystek | —Callbook |
| —Curtis | —Radio Shack |
| —Cush-Craft | —Raytheon |
| —Data | —Robot |
| —Drake | —Savoy |
| —Dycomm | —Solid State |
| —Ehrhorn | —Space |
| —Eimac | —Spectrum |
| —EL | —Standard |
| —ESP | —Star-Tronics |
| —Erickson | —Stelcomp |
| —Fair | —Swan |
| —Gateway | —Tempus |
| —Gray | —Topeka FM |
| —H & L | —Van's |
| —HAL | —Vanguard |
| —Ham Radio | —Weinschenker |
| —Heights | —Wolf |
| —Henry | —World QSL |
| —Hy-Gain | —Xcelite |
| —International Crystal | —Y & C |

Limit 15 inquiries per request.

February 1973

Please use before March 31, 1973

Tear off and mail to
HAM RADIO MAGAZINE — "check off"
Greenville, N. H. 03048

NAME.....
CALL.....
STREET.....
CITY.....
STATE..... ZIP.....

Advertisers iNdex

ATV Research	64
Amateur-Wholesale Electronics	87, 93
Apollo Products	80
Arizona Semi-Conductor	92
Barry	70, 71
Bauman, R. H. Sales	61
Budget Electronics	65
CFP Enterprises	92
CTG Bitcil	60
Caringella Electronics	59
Circuit Specialists Co.	84
Clegg Division of ISC	5
Command Productions	63
Communications Specialists	64
Comtec	48, 49, 76, 86
Cook's Communications Corporation	87
Crystek	67
Curtis	61, 87
Data Engineering, Inc.	82
Drake, Co., R. L.	17, 86
Dycomm	78
Ehrhorn Technological Operations, Inc.	1.
Eimac, Div. of Varian Assoc.	Cov. IV
Emporium Sounds of Pompano	62
Erickson Communications	67
Fair Radio Sales	72
Gateway Electronics	78
Goodheart Co., Inc. R. E.	61
Gray Electronics	66
H & L Associates	72
HAL Communications Corp.	73
Hann Radio	71
Heights Manufacturing Co.	72
Henry Radio Stores	Cov. III
Hy-Gain Electronics Corp.	68, 69, 90, 91
International Crystal Mfg. Co. Inc.	96
Jan Crystals	87
Janel Labs	72
Jeff-Tronics	72
K. E. Electronics	92
KW Electronics	63
L. A. Electronix Sales	79, 95
MFJ Enterprises	63
Matric	38
Meshna, John, Jr.	93
Military Electronics	64
Mor-Gain, Inc.	86
NHE Communications	85, 92
Nurmi Electronic Supply	60
PM Electronics Inc.	88
Pagel Electronics	66
Palomar Engineers	88
Payne Radio	81
Poly Paks	74, 75
RP Electronics	80
Radio Amateur Callbook	80, 92
Raytheon Company	2
Robot Research	45
Savoy Electronics	Cov. II
Solid State Systems, Inc.	89
Space-Military Electronics	92
Spectrum International	76
Standard Communications Corp.	77
Star-Tronics	63
Stelcomp Scientific	85
Swan Electronics	55
Topeka FM Engineering	64
Van's W2DLT	85
Vanguard Labs	65
Weinschenker, M.	41
Wolf, S.	85
World QSL Bureau	92
Y & C Electronics	78



"2" Rigs in one!

THE CTR-144 by **COMCRAFT**
FIRST AM-FM TWO METER TRANSCEIVER

No longer is it necessary to choose between AM and FM on two meters. Now you can have both in one compact unit. Join the gang on the new FM repeaters yet still be able to "rag chew" with old friends either AM or FM anywhere in the two meter band.

ALL SOLID STATE - NO TUBES
MADE IN AMERICA



Compare These Features

TRANSMITTER:

- Built-in VFO (Frequency converted for stability)
- AM and FM both crystal and VFO
- Four transmit crystal positions (8 MHz)
- 12 watt input AM and FM
- High level transmitter modulation on AM
- Bandpass coupled transmitter requiring only final tune and load
- Three internal transmit crystal sockets with trimmers for netting
- One transmitter crystal socket on the front panel
- Deviation limiting
- 146.94 MHz crystal included

RECEIVER:

- Double conversion
- Crystal controlled first conversion
- MOS FET receiver front-end
- Integrated circuit limiter and discriminator for FM
- Envelope detector and series gate noise clipper for AM
- Built-in squelch for both AM and FM

GENERAL:

- Separate transmitter and receiver tuning
- Built-in 115VAC power supply
- Direct 12VDC operation for mobile or portable operation
- Optional portable rechargeable snap-on battery pack available
- "S" Meter also used for transmitter tune up
- Military style glass epoxy circuit boards
- Anodized lettering and front panel
- Baked epoxy finish on the cabinet
- 47 transistors, 22 diodes, 1 integrated circuit
- Dimensions: 10¼"W x 6¼"H x 7½"D

All this for just **\$459.95**

plus

FREE SHIPPING IN U.S.A.
5 FREE CRYSTALS (\$29.50 VALUE)



Electronix Sales

23044 S. CRENSHAW BLVD., TORRANCE, CALIF. 90505

Phone: (213) 534-4456 or (213) 534-4402

CLOSED SUNDAY & MONDAY

See LA for your SWAN needs

for the EXPERIMENTER!

INTERNATIONAL EX CRYSTAL & EX KITS
 OSCILLATOR • RF MIXER • RF AMPLIFIER • POWER AMPLIFIER



1. MXX-1 TRANSISTOR RF MIXER

A single tuned circuit intended for signal conversion in the 3 to 170 MHz range. Harmonics of the OX oscillator are used for injection in the 60 to 170 MHz range. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering)\$3.50



2. SAX-1 TRANSISTOR RF AMP

A small signal amplifier to drive MXX-1 mixer. Single tuned input and link output. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering)\$3.50



3. PAX-1 TRANSISTOR RF POWER AMP

A single tuned output amplifier designed to follow the OX oscillator. Outputs up to 200 mw, depending on the frequency and voltage. Amplifier can be amplitude modulated. Frequency 3,000 to 30,000 KHZ.....\$3.75



4. BAX-1 BROADBAND AMP

General purpose unit which may be used as a tuned or untuned amplifier in RF and audio applications 20 Hz to 150 MHz. Provides 6 to 30 db gain. Ideal for SWL, Experimenter or Amateur\$3.75



5. OX OSCILLATOR

Crystal controlled transistor type. Lo Kit 3,000 to 19,999 KHZ, Hi Kit 20,000 to 60,000 KHZ. (Specify when ordering).....\$2.95



6. TYPE EX CRYSTAL

Available from 3,000 to 60,000 KHZ. Supplied only in HC 6/U holder. Calibration is $\pm .02\%$ when operated in International OX circuit or its equivalent. (Specify frequency)\$3.95

for the COMMERCIAL user...

**INTERNATIONAL
 PRECISION RADIO CRYSTALS**

International Crystals are available from 70 KHz to 160 MHz in a wide variety of holders. Crystals for use in military equipment can be supplied to meet specifications MIL-C-3098E.

CRYSTAL TYPES: (GP) for "General Purpose" applications
 (CS) for "Commercial Standard"
 (HA) for "High Accuracy" close temperature tolerance requirements.



**write for
 CATALOG**



CRYSTAL MFG. CO., INC.
 10 NO. LEE • OKLA. CITY, OKLA. 73102

Amateur FM Comes of Age



TEMPO/CL 220

As new as tomorrow! The Tempo Commercial Line VHF transceivers offer commercial performance at amateur prices. Both units include an audio limiter to assure constant deviation at all times and an instantaneous impulse squelch. Microphone, power cord, mounting bracket and one pair of crystals is included.

- Frequency Range: 220-225 MHz (2 MHz operating range)

- Number of Channels: 12 channel capability for transmit and receive
- RF Power Output: 10 Watts or 3 Watts.
- Audio Output: 2 Watts minimum w/internal speaker (at less than 10% distortion)
- The price: \$329.00 w/out power supply

TEMPO/CL 146

- Frequency Range: 146-148 MHz
- Same general specifications as CL 220
- The price: \$279.00



TEMPO/fmp

Truly mobile, the Tempo/fmp 2 meter 3 watt portable gives amateurs 3 watts, or a battery saving 1/2 watt, FM talk power anytime. With a leather carrying case included, this little transceiver will operate in the field, in a car, or at home with an accessory AC power supply. The battery pack is included. The price: \$225.00 (Accessory rechargeable battery available: \$22.00)



TEMPO/fmv 2

So much for so little! This little 10 Watt VHF FM transceiver offers high quality performance and features usually found only on more expensive units. Features such as AFC on receive and separate switchable Transmit/Receive sections. Includes mounting bracket, heavy duty power cord and provisions for accessory AC power supply. Frequency: 146-148 MHz, 11 channels, 25 KHz channel spacing. 13.8 VDC \pm 10% operation (standby -100 ma, receive -150 ma, transmit -3.0 amp.) \$199.00



TEMPO/TPL high power fm amplifiers

MODEL NUMBER	POWER INPUT	POWER OUTPUT (min)	BAND	PRICE
TPL1002-3	5 to 25W	100-135W	2M	\$220.00
TPL1002-3B	1-3W	80W	2M	\$235.00
TPL802	5W	80W	2M	\$180.00
TPL802B	1 to 3W	80W	2M	\$195.00
TPL502	5 to 15W	35-55W	2M	\$105.00
TPL502B	1 to 3W	45W	2M	\$130.00
TPL252-A2	1W	25W	2M	\$ 85.00
TPL445-10	1 to 2.5W	12W	440MHz	\$125.00
TPL445-30	4W	30W	440MHz	\$215.00
TPL445-30B	1W	30W	440MHz	\$235.00
TCP 12A Control Head . . .				\$32.00



TEMPO/fmh

So much for so little! 2 watt VHF/FM hand held. 6 Channel capability, solid state, 12 VDC, 144-148 MHz (any two MHz), includes 1 pair of crystals, built-in charging terminals for ni-cad cells, S-meter, battery level meter, telescoping whip antenna, internal speaker & microphone. \$189.00

TEMPO/6N2


The Tempo 6N2 meets the demand for a high power six meter and two meter power amplifier. Using a pair of Eimac 8874 tubes it provides 2000 watts PEP input on SSB and 1000 watts input on CW and FM. Completely self-contained in one small desk mount cabinet with internal solid state power supply, built in blower and RF relative power indicator.

Prices subject to change without notice.

Henry Radio

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
 931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
 Butler, Missouri 64730 816/679-3127

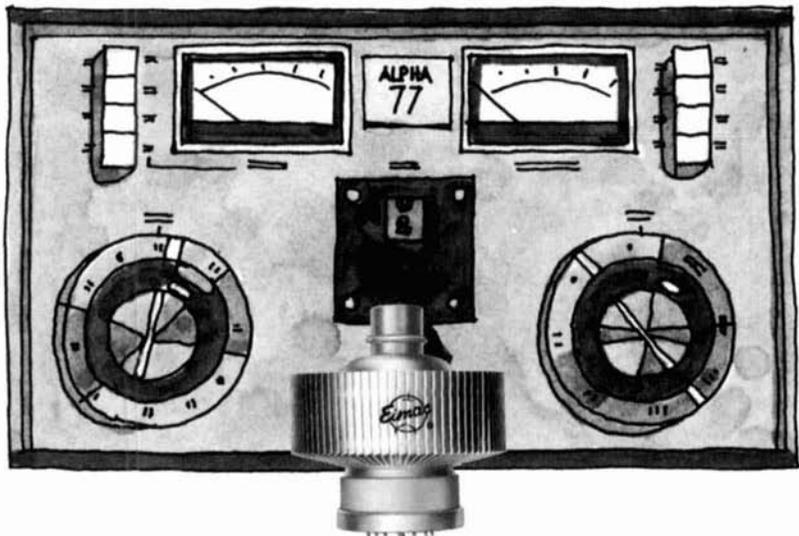AVAILABLE AT SELECT DEALERS THROUGHOUT THE U.S.



**The no-compromise
Alpha 77
is powered by
the no-compromise
EIMAC 8877.**

No corners were cut in designing the rugged Alpha 77 amplifier. Rated for continuous commercial service, it loafs along at the maximum legal amateur power limit.

And, no corners were cut in designing EIMAC's air-cooled 8877 ceramic/metal, high-mu triode, the Alpha 77 power tube. The 8877 is conservatively rated at 1500 watts plate dissipation up to 250 MHz and requires less than 65 watts PEP drive signal for the legal power input limit. This impressive power gain is achieved with 3rd order intermodulation distortion products -38 decibels below one tone of a two equal-tone drive signal.

This compact, rugged, high-mu power triode has a maximum plate voltage rating of 4000 and a maximum plate current rating of one ampere in commercial service. While the 8877 is primarily designed for superla-

tive linear amplifier service demanding low intermodulation distortion, its high efficiency also permits excellent operation as a class C power amplifier, oscillator, or as a plate modulated amplifier. The zero bias characteristic is useful for these services, as plate dissipation is held to a safe level if drive power fails, up to a plate potential of 3 kV.

The Alpha 77 is the ultimate power amplifier for the 70's. That's proven by the choice of the 8877, another example of EIMAC's ability to provide tomorrow's tubes today. For additional information on this tube or other products, contact EIMAC Division of Varian, 301 Industrial Way, San Carlos, California 94070. Phone (415) 592-1221. Or contact any of the more than 30 Varian/EIMAC Electron Tube and Device Group Sales Offices throughout the world.

