

Special Issue: **CITIZENS BAND RADIO**

ELECTRONICS ILLUSTRATED

By the Publishers of **MECHANIX ILLUSTRATED**

MAY • 354

50 PAGES OF CB FEATURES!
10 CONSTRUCTION PROJECTS!

Build This Low-Cost

TINY-TALKIE ▶

for LICENSE-FREE Operation
on the Citizens Band

How to Buy a Transceiver
By Len Buckwalter, 1W5733

Setting Up Your First Station
By Tom Kneitel, 12Q1747

How to Service Your CB Equipment
By Herb Friedman, 2W6045

Plans for FOUR CB Antennas
By Charles Tepfer, 2W4223

Add a Tune-Up Meter • Add an S-Meter

How to Organize a CB Club • The License-Free Band

Plans for a Safe Mobile Mike • Build a CB Signal Generator


Choose the Right Antenna for Your Rig • How to Tune Your Output



COMPLETE PLANS FOR THIS MODEL ROCKET TRANSMITTER!

Training Kits Extra Charge

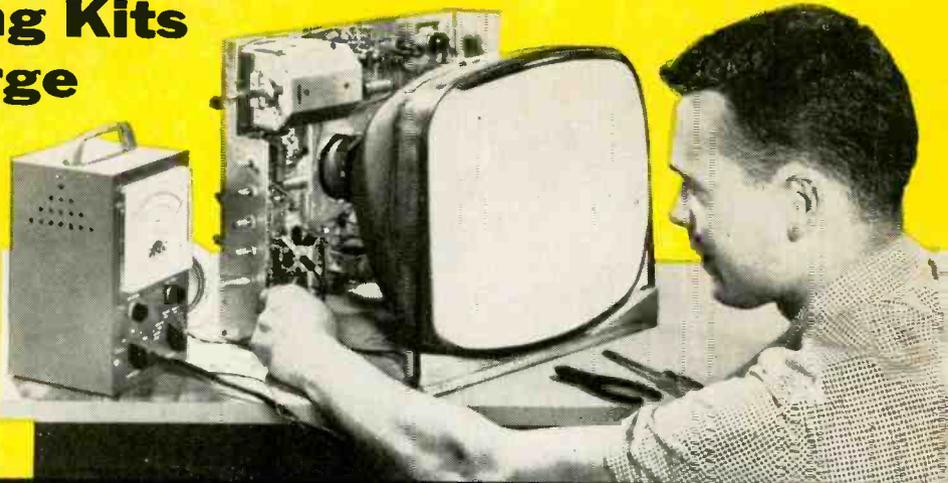practical—based on
DING methods. Be-
ated lessons designed
or men without pre-
e—you get special
give actual practice,
he things you study.
o keep without extra
le, you get all parts,
icture tube, to build
l vacuum tube volt-
re. Read course de-
4-PAGE CATALOG.
today.



START AND A BRIGHT FUTURE Electronics Radio Television SPARE TIME

Fast Growing Field of Electronics Needs More Trained Technicians

New developments are creating more and more job opportunities for men with Electronics training, and these are better than average jobs. Take NRI training at home in your spare time. Hold your present job while training. Prepare now for a brighter future.


Added Income in Spare Time Starting Soon

Soon after enrolling we show you how to earn extra money in spare time, repairing sets. Many use this extra money to pay for their NRI course, or buy things they normally couldn't afford. Some have found better paying jobs within a year. Others have started their own businesses.

Train With the Leader—Get Started Fast

NRI is the oldest and largest school of its kind. For 45 years, NRI has featured the best training for beginners—for men without previous experience. Mail postage-free card for 64-page Catalog. Read success stories. See equipment you get. Find out about 60-day trial enrollment offer.

Convenient monthly terms. ACT NOW.

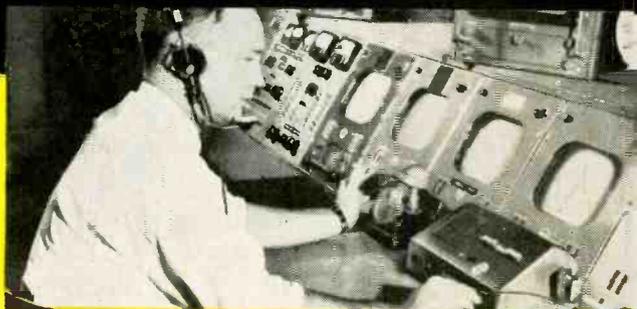

NRI Graduates help build, install, operate and service electronic equipment for the "Space Age" we live in—equipment used in offices, factories, the military. Others are inspectors, laboratory technicians, etc., or work with the Government and Armed Forces.




From Radio-TV Servicing and Broadcasting to missile: NRI graduates share in the gigantic Electronics industry. Interesting jobs await you in studios, on ships and planes in your own Radio-TV business. Mail coupon today.

NRI PREPARES YOU FOR JOBS LIKE THESE

Electronic Technician • Service Technician • Assistant Engineer
Cameraman • Civil Service Specialist • Computer Technician
Computer Programmer • Designer • Field Technician • Field Maintenance Man • Plant Parts Inspector • Instrument Technician • Laborator Technician • Radio Operator • Transmitter Engineer • Airlines Technician

MAIL
CARD
NOW

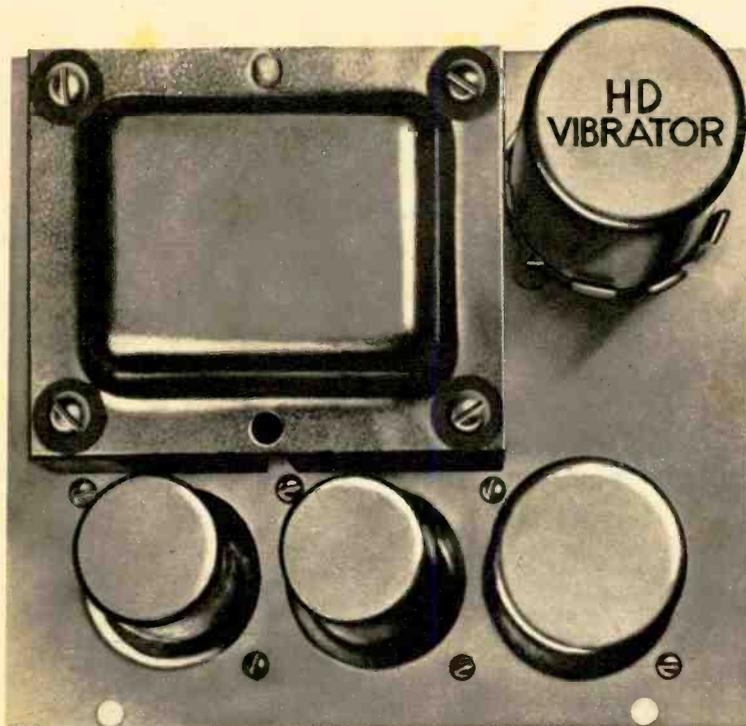OLDEST & LARGEST HOME STUDY RADIO-TV SCHOOL
National Radio Institute
WASHINGTON 16, D. C. ESTABLISHED 1914



CB MOBILITY?

This rugged power supply with heavy duty vibrator is the heart of e.c.i. Courier 1's versatility for mobile or base use. It is one of five key components in the Courier 1 unitized chassis . . . and offers built-in 110 volt power for base station use and built-in 12 volt power for mobile use. Add to this an extremely effective noise limiter plus cadmium plated metal parts for marine use. Want more good reasons why CB experts say Courier 1 is great? See for yourself. Check these features:



write for free brochure

\$189.50

Slightly higher west of Rockies

- 12 CHANNEL TRANSMITTING
- 23 CHANNEL TUNABLE RECEIVE
- 4 POSITION FIXED RECEIVE
- BUILT-IN SQUELCH
- LOWEST NOISE FRONT END (NUVISTOR)
- ELECTRONIC SWITCHING (NO RELAYS)
- MORE THAN 3 WATT OUTPUT
- BETTER THAN 15 WATT CAPABILITY
- FRONT PANEL RF GAIN CONTROL
- BUILT-IN "S" & "RF" METER
- FULLY MODULATED (100%)
- ENTIRE UNIT SLIDES OUT ON TRACKS

(Limited to 5 watts input by present FCC regulations)



e.c.i. electronics communications, inc. 325 no. macquesten pkwy. mt. vernon, n.y.

May, 1962

ELECTRONICS ILLUSTRATED

ROBERT G. BEASON Editor
 Larry Klein Technical Editor

Murray Cooper Art Editor
 Linda R. Grossman Editorial Assistant

CONTRIBUTING EDITORS

Robert Hertzberg, W2DJJ Amateur Radio
 Len Buckwalter, 1W5733 Citizens Band
 C. M. Stanbury II SWL-DX
 Harvey Pollack Special Projects

Richard A. Markoff, M.D. Medical Electronics
 Harry Kolbe Audio
 John Milder Audio
 David Muirhead Audio

May, 1962

A Fawcett Publication

Vol. 5, No. 3

In This Issue:

Special CB Features

How to Get the Most Out of Citizens Band Radio	29
How to Buy a Transceiver	30
CB Hit Parade	33
Choose the Right Antenna	35
Your First Station	38
How to Form a CB Club	40
Make Your Club Worthwhile	43
CB Corner	51
The License-Free Band	57

Special CB Projects

EI Tiny-Talkie	46
How to Build 4 CB Antennas	52
CB Thru Your Car Speaker	61
An Earphone for Your Transceiver	61
CB Signal Generator	62
Kit Report: EI Builds a 5-Watt Transceiver	65
A Safe Mobile Mike	68
CB Servicing Made Easy	70
Add an S-Meter	74
Flyweight Transmitter for Model Rockets	76
Add a Tune-Up Meter	80
Tune Your Transmitter Output	81

General Features

America's Super-Secret Satellite	86
EI's Electricity Contest	96

Radio: Amateur • SWL

Scrambled-Call DX	90
The Listener	92
Ham Shack	97

Audio & Hi-Fi

A Stereo Boom for FM	89
Hi-Fi Record Guide	99

Regular Departments

Feedback from Our Readers	4
Electronics in the News	10
Electronic Marketplace	19
Good Reading	84
Tech Editor's Test Bench: Tools	85
Electronic Brain	98

Ralph Daigh Editorial Director
 James Boynton Advertising Director
 Al Allard Art Director
 Ralph Mattison Associate Art Director
 George H. Carl Production Director
 Larry Elsinser Editor-In-Chief
 Phyllis Bendremer Production Editor
 Benita Rockwood Asst. Production Editor
 John F. Webster Advertising Manager

ELECTRONICS ILLUSTRATED is published bi-monthly by Fawcett Publications, Inc., Fawcett Place, Greenwich, Conn. W. H. Fawcett, Jr., President; Gordon Fawcett, Secretary and Treasurer; Roger Fawcett, General Manager; Roscoe K. Fawcett, Circulation Director; Donald P. Hanson, Assistant General Manager.

EDITORIAL AND ADVERTISING OFFICES: 67 West 44th Street, New York 36, N. Y.
 ADDRESS ALL MAIL: Subscriptions, change of address, Form 3579 to Subscription Dept., Fawcett Bldg., Greenwich, Conn.; and all editorial and advertising to Fawcett Publications, Inc., 67 W. 44th St., New York 36, N. Y.

Second-class postage paid at Greenwich, Conn., and at additional mailing offices.
 Subscription price \$4.00 for 12 issues in the U. S. and possessions and Canada. All other countries \$6.00 for 12 issues. Foreign subscriptions and sales should be remitted by International Money Order in U. S. funds payable at Greenwich, Conn.

Printed in U.S.A. Copyright 1962 by Fawcett Publications, Inc.
 Permission hereby granted to quote from this issue of this magazine on radio or television provided a total of not more than 1,000 words is quoted and credit is given to the title of the magazine and issue, as well as the statement, copyright 1962 by Fawcett Publications, Inc.

Member of: Audit Bureau of Circulations

Magazine Publishers Association, Inc.




Profits That Lie Hidden in America's Mountain of Broken Electrical Appliances

By J. M. Smith President, National Radio Institute



And I mean profits for you — no matter who you are, where you live, or what you are doing now. Do you realize that there are over 400 million electrical appliances in the homes of America today? So it's no wonder that men who know how to service them properly are making \$3 to \$5 an hour — in spare time or full time! I'd like to send you a Free Book telling how you can quickly and easily get into this profitable field.

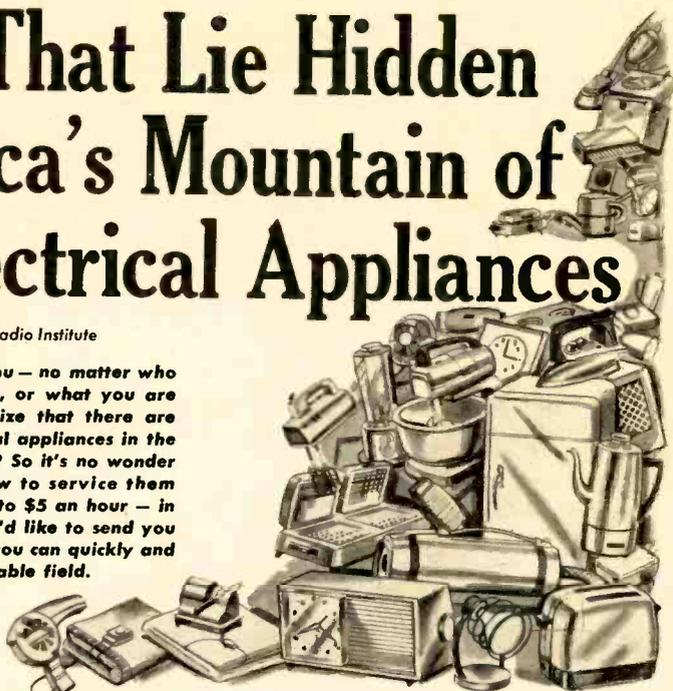

THE COMING OF THE AUTO created a multi-million dollar service industry, the auto repair business. Now the same thing is happening in the electrical appliance field. But with this important difference: anybody with a few simple tools can get started in appliance repair work. No big investment or expensive equipment is needed.

The appliance repair business is booming — because the sale of appliances is booming. One thing naturally follows the other. In addition to the 400,000,000 appliances already sold, this year alone will see sales of 76 million new appliances. For example, 4,750,000 new coffee makers, almost 2,000,000 new room air conditioners, 1,425,000 new clothes dryers. A nice steady income awaits the man who can service appliances like these. And I want to tell you why that man can be you — even if you don't know a volt from an ampere now.

A Few Examples of What I Mean

Now here's a report from Earl Reid, of Thompson, Ohio: "In one month I took in approximately \$648 of which \$510 was clear. I work only part time." And, to take a big jump out to California, here's one from

J. G. Stinson, of Long Beach: "I have opened up a small repair shop. At present I am operating the shop on a spare time basis — but the way business is growing it will be a very short time before I will devote my full time to it."

Don't worry about how little you may now know about repair work. What John D. Pettis, of Bradley, Illinois wrote to me is this: "I had practically no knowledge of any kind of repair work. Now I am busy almost all my spare time and my day off — and have more and more repair work coming in all along. I have my shop in my basement."

We Tell You Everything You Need to Know

If you'd like to get started in this fascinating, profitable, rapidly growing field — let us give you the home training you need. Here's an excellent opportunity to build up "a business of your own" without big investment — open up an appliance repair shop, become independent. Or you may prefer to keep your present job, turn your spare time into extra money.

You can handle this work anywhere — in a corner of your basement or garage, even

on your kitchen table. No technical experience, or higher education is necessary. We'll train you at home, in your spare time, using methods proven successful for over 45 years. We start from scratch — tell you in plain English, and show you in clear pictures — everything you need to know. And, you will be glad to know, your training will cost you less than 20¢ a day.

FREE BOOK and Sample Lesson

I think that our 24-page Free Book will open your eyes to a whole world of new opportunities and how you can "cash in" on America's "Electrical Appliance Boom."

I'll also send you a Free Sample Lesson. It shows how simple and clearly illustrated our instruction is — how it can quickly prepare you for a profitable future in this big field. Just mail coupon, letter, or postcard to me: Mr. J. M. Smith, President, National Radio Institute, Dept. KE2, Washington 16, D.C. (No obligation, of course — and no salesman will call on you.)

EARN WHILE YOU LEARN with this APPLIANCE TESTER

— Yours at No Extra Charge

Your NRI Course comes complete with all the parts to assemble a sturdy, portable Appliance Tester that helps you earn while you learn. Easy-to-follow manual tells how to assemble and use the Tester right away. Locate faulty cords, short circuits, poor connections, etc. in a jiffy; find defects in house wiring, measure electricity used by appliances; many other uses.

With this Tester you save time and make money by doing jobs quicker, making sure appliances operate correctly after repairs.



MAIL THIS FOR FREE BOOK and SAMPLE LESSON

Mr. J. M. Smith, President
NATIONAL RADIO INSTITUTE
Dept. KE2, Washington 16, D.C.

Tell me how I can "cash in" on the "Electrical Appliance Boom." Send me your illustrated FREE BOOK that outlines the whole NRI Course, tells what opportunities are open to me, answers my questions, describes success of other students, and much more. Also send me the FREE SAMPLE LESSON so I can see how clear and easy your instructions are. I am particularly interested in:

- Spare Time Earnings Business of My Own Better Job
I understand there is no obligation on my part; and no salesman will call on me.

Name.....
Address.....
City..... Zone..... State.....

Accredited Member National Home Study Council



FEEDBACK

from our readers

Write to: Letters Editor, Electronics Illustrated.

67 West 44th St., New York 36, N. Y.




● Red Bug

I am curious about your description of the listening device they found in our Moscow embassy (HOW RUSSIAN SPY RADIOS WORK, January '61 EI) as compared to the description given at the same time by a "big weekly picture magazine." They printed the same picture you did of Henry Cabot Lodge and the Great Seal and said the spy gadget was a hidden microphone. You said it wasn't a hidden microphone, but a special kind of tuned-cavity gismo. Who takes the honors for stupidity here?

Bill Sheffield
Seattle, Wash.

The picture-magazine people win the laurels without a struggle, Bill. EI was correct.

● Panic in the Bedroom

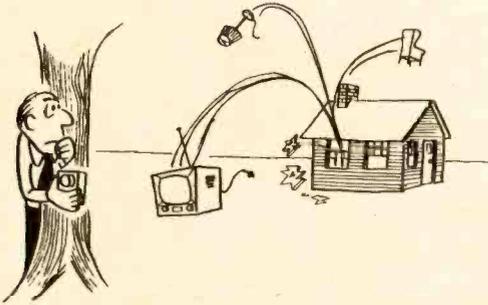

That Panic Button you told how to build in your November issue has uses you didn't even mention. It knocks down houses better than a wrecking ball. I completed mine one night and took it upstairs and set it off beside my sleeping wife. Her reaction was instantaneous. She picked up a \$15 alarm clock and threw it. She missed me but, unfortunately, not an \$8.70 window that got in the way.


I withhold my name for reasons of safety.

Name Withheld
Los Angeles, Calif.

My face is red. I wired and rewired the Panic Button several times and it still didn't work. Then I found the trouble—a bad pushbutton. I just wish it had another stage of amplification to get a little more volume. This I am working on. Anyway, it works like a charm.

Dutch Meyer
Technical Director
KMSO-TV
Missoula, Mont.

● Downside Up

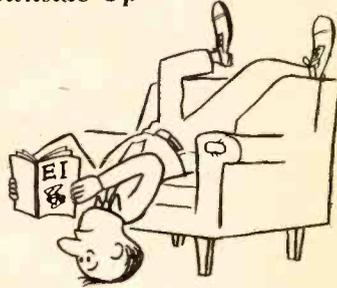

The cover of your January issue, having to do with your special articles on Short-Wave Listening, was quite colorful. Posted on the wall were some QSL cards, including the rarest one of all. I'm talking about the one reading NS6ZO. Maybe it's from Mars or someplace like that. Or should it be turned upside down to read OZ9SN, from Denmark?

Richard Frost, K1JVG
Burlington, Mass.

Could be, Dick. Could be.

Your Special Issue on SWL made a mistake on the Lafayette HE-30 receiver. The price was listed as \$99.95 for the kit. Shouldn't that be \$79.95?

Paul Justyna
No Address Given

Yes, the price should be \$79.95. Thanks for writing, Paul . . . wherever you are.

[Continued on page 6]

men
17-55

**JOB OPPORTUNITIES!
EXCITEMENT!
MONEY!**

All this
can be
Yours as a trained

Electronics TECHNICIAN

**OVER 6,000 FIRMS HAVE EMPLOYED
DeVRY TECH GRADUATES!**

Thousands of companies in the United States and Canada who have employed DeVry Tech men prove two most important facts: (1) Electronics is one of the biggest, fastest growing opportunity fields of our time; and (2) DeVry Tech graduates are "WANTED" MEN.

Whether DeVry Tech prepares you in spare time at home or in its modern Chicago or Toronto Laboratories, your training is designed to get you ready to meet the exacting standards of industry. You get practical training that not only helps to fit you for a job or a service shop of your own—but also gives you a foundation for a career that can be profitable the rest of your life.

You work over 300 learn-by-doing experiments at home, using DeVry Tech's exclusive Electro-Lab method. You build and KEEP valuable equipment. With another DeVry Tech exclusive, you have the benefit of training movies that you can show over and over until basic points are crystal clear. Special texts guide you every step of the way as well.

HOW DeVRY TECH CAN "BLUEPRINT" YOUR CAREER!

DeVry's faculty not only know how to teach Electronics, but they also understand men. They most likely know the type of problems you face. From this staff you get help, advice and understanding. It is this "human" side of DeVry's program that has caused many of our graduates to say: "DeVry Tech not only trains you for a job, they actually help you blueprint a profitable future!"

NO ADVANCED EDUCATION NEEDED!

Why don't you write for FREE FACTS today? Learn how you TOO can be a member of the great fraternity of DeVry Tech graduates across the continent. . . . men who were properly trained, encouraged, appreciated and understood! SEND IN COUPON NOW!

EFFECTIVE EMPLOYMENT SERVICE

DeVry Tech's effective Employment Service is available to all graduates without additional cost.

**2 FREE BOOKLETS
Send Coupon TODAY!**

"One of North America's Foremost Electronics Training Centers"

Accredited Member of
National Home Study Council



**DeVRY TECHNICAL
INSTITUTE**
CHICAGO • TORONTO



TELEVISION



COMPUTERS



MICRO-WAVES



RADAR



BROADCASTING

LET DeVRY HELP
YOU PREPARE
AND BLUEPRINT
A SOLID
CAREER IN
THIS
FAST-GROWING
FIELD!



DeVRY TECHNICAL INSTITUTE
4141 Belmont Ave., Chicago 41, Ill., Dept. EI-5-5
Please give me your 2 FREE BOOKLETS, "Pocket Guide to Real Earnings" and "Electronics in Space Travel," also include details on how to prepare for a career in one or more branches of Electronics.

Name _____ Age _____
Street _____ Apt. _____
City _____ Zone _____ State _____
 Check here if you face military service.
2075 Canadian residents address: DeVry Tech of Canada, Ltd.
970 Lawrence Avenue West, Toronto, Ontario



CITIZEN BAND CLASS "D" CRYSTALS

All 22 Frequencies in Stock

3rd overtone. .005% tolerance—to meet all F C C requirements.
Hermetically sealed HC6/U holders. 1/2" pin spacing—.050 pins. (.093 pins available, add 15¢ per crystal).

\$2.95 EACH

The following Class "D" Citizen Band frequencies in stock (frequencies listed in megacycles): 26.965, 26.975, 26.985, 27.005, 27.015, 27.025, 27.035, 27.055, 27.065, 27.075, 27.085, 27.105, 27.115, 27.125, 27.135, 27.155, 27.165, 27.175, 27.185, 27.205, 27.215, 27.225.

Matched crystal sets for all CB units. . . . \$5.90 per set. Specify equipment make and model numbers.

RADIO CONTROL CRYSTALS IN HC6/U HOLDERS
Specify frequency. 1/2" pin spacing . . . pin diameter .05 (.093 pin diameter, add 15¢) . . . \$2.95 ea.

FUNDAMENTAL FREQ. SEALED CRYSTALS

in HC6/U holders
From 1400 KC to 2000 KC. .005% Tolerance. . . . \$4.95 ea.
From 2000 KC to 10,000 KC any frequency
.005% Tolerance \$3.50 ea.

SEALED OVERTONE CRYSTALS

Supplied in metal HC6/U holders
Pin spacing .486, diameter .050
15 to 30 MC .005 Tolerance \$3.85 ea.
30 to 45 MC .005 Tolerance \$4.10 ea.
45 to 60 MC .005 Tolerance \$4.50 ea.



QUARTZ CRYSTALS FOR EVERY SERVICE

All crystals made from Grade "A" imported quartz—ground and etched to exact frequencies. Unconditionally guaranteed! Supplied in:

FT-243 holders	MC-7 holders	CR1A/AR holders	FT-171 holders
Pin spacing 1/2"	Pin spacing 3/4"	Pin spacing 1/2"	Pin spacing 3/4"
Pin diameter .093	Pin diameter .125	Pin diameter .125	Banana pins

MADE TO ORDER CRYSTALS • SPECIFY HOLDER WANTED

1001 KC to 2600 KC:	
.005% Tolerance	\$4.50 ea.
2601 KC to 9000 KC:	
.005% Tolerance	\$2.50 ea.
9001 KC to 11,000 KC:	
.005% Tolerance	\$3.00 ea.

Amateur, Novice, Technician Band Crystals

.01% Tolerance . . . \$1.50 ea.—80 meters (3701-3749 KC), 40 meters (7152-7198 KC), 15 meters (7034-7082 KC), 6 meters (8335-8650 KC) within 1 KC
FT-241 Lattice Crystals in all frequencies from 370 KC to 540 KC (all except 455 KC and 500 KC) 50¢ ea.
Pin spacing 1/2" Pin diameter .093

Matched pairs ± 15 cycles \$2.50 per pair
200 KC Crystals, \$2.00 ea.; 455 KC Crystals, \$1.25 ea.; 500 KC Crystals, \$1.25 ea.; 100 KC Frequency Standard Crystals in HC6/U holders \$4.50 ea.; Socket for FT-243 crystal 15¢ ea.; Dual socket for FT-243 crystals, 15¢ ea.; Sockets for MC-7 and FT-171 crystals 25¢ ea.; Ceramic socket for HC6/U crystals 20¢ ea.

Write for new free catalog #961 complete with oscillator circuits

ASK YOUR PARTS DEALER FOR TEXAS CRYSTALS

See big red display . . . or order from our Florida plant.

NOW! Engineering samples and small quantities for prototypes now made either at Chicago or at Ft. Myers Plant. 24 Hour Service!

IN CHICAGO, PHONE GLADSTONE 3-3555

RUSH ORDER. Use coupon for 1st Class shipment

TEXAS CRYSTALS

Dept. E-52, 1000 CRYSTAL DRIVE, FORT MYERS, FLORIDA
For extra fast service, Phone WE 6-2100

ATTACH THIS COUPON TO YOUR ORDER FOR SHIPMENT VIA 1ST CLASS MAIL AT NO EXTRA COST
TERMS: All items subject to prior sale and change of price without notice. All crystal orders must be accompanied by check, cash or M.O. with PAYMENT IN FULL.

E-52

FEEDBACK

Continued from page 4

May I compliment you on your very interesting articles on SWL and DX? I gain much needed information from your magazine.

Stephen Sauer, WN9ASZ
Age 14
Indianapolis, Ind.

Your January '62 issue was a masterpiece as far as we SWL's are concerned. I'm glad your magazine realizes the tremendous scope and potential of our hobby.

Ken MacNeilage
Editor
American Shortwave
Listeners Club
Cranford, N. J.

EI thanks the several dozen readers who wrote us complimentary letters about our January issue.

● Indian Offer



I read your magazine with keen interest. I would like your readers to know I have organized a sort of tape-friendship club for exchanging tapes and I can send tapes anywhere in the world on such subjects as classical, instrumental and vocal Indian musics, Indian marriage, religious ceremonies, villages, streets and ways of cooking.

Ambika Shrivastava
30 Pagnispaga
Indore City (M.P.)
India

● The New ARMY

Reader Tom Duignan's suggestion in your January FEEDBACK column that Amateur Radio Monitors (ARM's) de-

[Continued on page 110]

"I SAW MYSELF 10 YEARS FROM NOW!"



It happened one payday . . .

Fred worked on the line next to me. Nice guy. Married. Two children. Been on the same job 10 years.

As we walked away from the pay window together he said, "Funny. Each week I get to feel like I'm letting my family down. You know. Not getting ahead so I can give them the things they need."

His words hit me all of a sudden. I could see myself saying the same thing—10 years from now!

Not only that. I could see the same job. Same thin paycheck. Same worries.

I thought about Fred all day. Then that night

I saw an ad for I.C.S. It told about the job opportunities that open up with I.C.S. training. How people had found new careers and job success.

I mailed the coupon and that was the start. In just a few months my boss discovered I was an I.C.S. student. He was so pleased he decided to move me off the line. A year and two raises later I was made an assistant supervisor.

What about Fred? He's still working on the line. Still hoping for the future.

I told him about I.C.S. But so far he hasn't done anything. I guess some people never will.

How about you?

For Real Job Security—Get an I. C. S. Diploma!

I. C. S., Scranton 15, Penna.

Accredited Member,
National Home Study Council

INTERNATIONAL CORRESPONDENCE SCHOOLS



BOX H7390D, SCRANTON 15, PENNA.

(In Hawaii, reply P.O. Box 418, Honolulu)

(Partial list of courses)

Without cost or obligation, send me "HOW TO SUCCEED" and the opportunity booklet about the field BEFORE which I have marked X (plus sample lesson):

ARCHITECTURE and BUILDING CONSTRUCTION

- Air Conditioning
- Architecture
- Arch. Drawing and Designing
- Building Contractor
- Building Estimator
- Carpenter Builder
- Carpentry and Millwork
- Heating
- Painting Contractor
- Plumbing
- Reading Arch. Blueprints

ART

- Commercial Art
- Magazine Illus.
- Sign Painting and Design'g
- Sketching and Painting

AUTOMOTIVE

- Automobile
- Auto Body Rebuilding and Refinishing
- Auto Engine Tuneup
- Auto Electrical Technician
- Diesel Engines

AVIATION

- Aero Engineering Technology
- Aviation Engine Mech.
- Reading Aircraft Blueprints

BUSINESS

- Accounting
- Advertising
- Bookkeeping and Cost
- Accounting
- Business Administration
- Business Management
- Clerk Typist
- Creative Salesmanship
- Managing a Small Business
- Professional Secretary
- Public Accounting
- Purchasing Agent
- Real Estate Salesmanship
- Salesmanship
- Salesmanship and Management
- Traffic Management

CHEMICAL

- Analytical Chemistry
- Chemical Engineering
- Chem. Lab. Technician
- General Chemistry

- Oil Field Technology
- Pulp and Paper Making

CIVIL ENGINEERING

- Civil Engineering
- Construction Engineering
- Highway Engineering
- Professional Engineer (Civil)
- Reading Struc. Blueprints
- Sanitary Engineer
- Sewage Plant Operator
- Structural Engineering
- Surveying and Mapping
- Water Works Operator

DRAFTING

- Aircraft Drafting
- Architectural Drafting
- Drafting & Machine Design
- Electrical Drafting
- Electrical Engineer Drafting
- Industrial Piping Drafting
- Mechanical Drafting
- Sheet Metal Drafting

ELECTRICAL

- Electrical Appliance Servicing
- Electrical Engineering

- Electric Motor Repairman
- Elec. Engr. Technician
- Elec. Light and Power
- Practical Electrician
- Practical Lineman
- Professional Engineer

HIGH SCHOOL

- Good English
- High School Diploma
- High School General
- H. S. College Prep. (Eng'g & Science)
- High School Math
- High School Science
- Short Story Writing

LEADERSHIP

- Aircraft Foremanship
- Industrial Supervision
- Personnel-Labor Relations
- Supervision

MECHANICAL and SHOP

- Diesel Engines
- Gas-Elec. Welding
- Heating and Air Conditioning
- Industrial Engineering
- Industrial Instrumentation

- Industrial Safety
- Machine Shop Practice
- Mechanical Engineering
- Plumbing and Heating
- Professional Engineer
- Quality Control
- Reading Shop Blueprints
- Refrigeration and Air Conditioning
- Tool Design
- Tool Making

RADIO, TELEVISION

- General Electronics Tech.
- Industrial Electronics
- Practical Radio-TV Eng'g
- Radio-TV Servicing
- TV Technician

RAILROAD and General Railroad

- Steam and Diesel Power
- Combustion Engineering
- Power Plant Engineer
- Stationary Diesel Engr.
- Stationary Steam Engines

TEXTILE

- General

Name _____ Age _____ Home Address _____

City _____ Zone _____ State _____ Working Hours _____ A.M. to P.M. _____


Occupation _____

Canadian residents send coupon to International Correspondence Schools, Canadian, Ltd., Montreal, Canada. . . . Special low monthly tuition rates to members of the U. S. Armed Forces.

SEND FOR
YOUR

ALLIED

MONEY-SAVING 1962 ELECTRONICS CATALOG

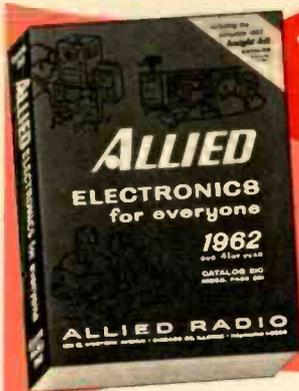

Free

444 PAGES
World's Biggest
Most Complete!

NO MONEY DOWN
New Credit Plan
Gives You 50% More
Buying Power!

SAVE MOST ON EVERYTHING IN ELECTRONICS

world's largest selection of famous name brands

Send today for this **FREE** Catalog—the world's biggest, featuring *everything* in Electronics for modern living. Largest selection of all famous name brands, including products and values available only from ALLIED. Whether you're a kit builder, experimenter, hi-fi fan, Amateur, technician or student, you'll save most on:

- **KNIGHT-KITS®**—Best in Build-Year-Own
- Everything in Stereo Hi-Fidelity
- New Multiplex Stereo FM
- New All-Transistor Stereo Hi-Fi
- **KNIGHT®** Super-Value Stereo Hi-Fi
- Tape Recorders & Phono Equipment
- Citizens Band 2-Way Radios
- TV Tubes, Antennas, Accessories
- Parts, Tubes, Transistors, Tools, Books
- Amateur Station Equipment
- Public Address & Intercom
- Latest Test & Lab Instruments

SAVE MOST on everything in Electronics at ALLIED—the world's largest electronic supply house. Get fastest service, expert personal help, easiest-pay terms. Send coupon today for **FREE 1962 ALLIED CATALOG**.

*Satisfaction Guaranteed
or Your Money Back*

ALLIED RADIO


ALLIED RADIO, Dept. 86-E2
100 N. Western Ave., Chicago 80, Ill.

Rush **FREE 1962 ALLIED Catalog**.

Name _____
PLEASE PRINT

Address _____

City _____ Zone _____ State _____

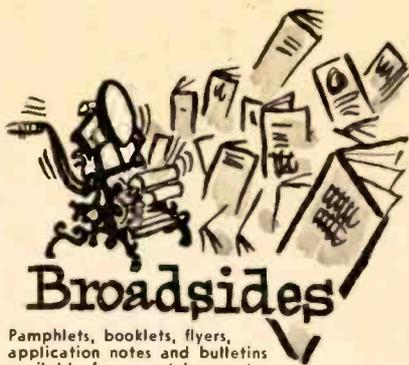

Pamphlets, booklets, flyers,
application notes and bulletins
available free or at low cost.

A third revision of the Atomic Energy Commission's catalog of **Technical Books and Monographs (1947-62)** is available free from the AEC Div. of Technical Information Extension, Box 62, Oak Ridge, Tenn. Books listed are Commission-sponsored and cover such areas as medicine, chemistry, engineering, etc., as they relate to atomic energy.

Two new Scott hi-fi amplifiers are described in a **Guide to Custom Stereo**. Write to H. H. Scott, Inc., Dept. P., 111 Powdermill Rd., Maynard, Mass. It's free.

The method used in transmitting and receiving stereo FM programs is illustrated in a color wall chart put out by Harman-Kardon for its dealers. Free copies are available from the company's Sales Dept., Plainview, N. Y. Requests must be on a dealer's letterhead.

Whether you like the classics or jazz, children's stories or foreign languages, you'll probably find what you're after in Allied's new **Discount Stereo Record and Tape Catalog**. For a free copy write to Allied Radio Corp., 100 N. Western Ave., Chicago, Ill. Ask for catalog No. 211.

EICO's newest catalog covers their line of kits and wired products ranging from stereo hi-fi equipment to CB and ham gear. Free copies are available on request from EICO, 33-00 Northern Blvd., Long Island City, N. Y.

The uses of near-ultraviolet energy, referred to as **Black Light**, are discussed in a new booklet by General Electric. A free copy can be had from GE's Inquiry Bureau, Nela Park, Cleveland 12, Ohio.

Solder, Its Fundamentals and Usage is free for the asking from Kester Solder Co., 4201 Wrightwood Ave., Chicago, Ill.

What Does F.C.C. Mean To You?

What is the F.C.C.?

F. C. C. stands for Federal Communications Commission. This is an agency of the Federal Government, created by Congress to regulate all wire and radio communication and radio and television broadcasting in the United States.

What is an F.C.C. Operator License?

The F. C. C. requires that only qualified persons be allowed to install, maintain, and operate electronic communications equipment, including radio and television broadcast transmitters. To determine who is qualified to take on such responsibility, the F. C. C. gives technical examinations. Operator licenses are awarded to those who pass these examinations. There are different types and classes of operator licenses, based on the type and difficulty of the examination passed.

What are the Different Types of Operator Licenses?

The F. C. C. grants three different types (or groups) of operator licenses—commercial radiotelePHONE, commercial radioteleGRAPH, and amateur.

COMMERCIAL RADIOTELEPHONE operator licenses are those required of technicians and engineers responsible for the proper operation of electronic equipment involved in the transmission of voice, music, or pictures. For example, a person who installs or maintains two-way mobile radio systems or radio and television broadcast equipment must hold a radiotelePHONE license. (A knowledge of Morse code is NOT required to obtain such a license.)

COMMERCIAL RADIOTELEGRAPH operator licenses are those required of the operators and maintenance men working with communications equipment which involves the use of Morse code. For example, a radio operator on board a merchant ship must hold a radioteleGRAPH license. (The ability to send and receive Morse is required to obtain such a license.)

AMATEUR operator licenses are those required of radio "hams"—people who are radio hobbyists and experimenters. (A knowledge of Morse code is necessary to be a "ham.")

What are the Different Classes of RadiotelePHONE Licenses?

Each type (or group) of license is divided into different classes. There are three classes of radiotelePHONE licenses, as follows:

(1) **Third Class RadiotelePHONE License.** No previous license or on-the-job experience is required to qualify for the examination for this license. The examination consists of F. C. C. Elements I and II covering radio laws, F. C. C. regulations, and basic operating practices.

(2) **Second Class RadiotelePHONE License.** No on-the-job experience is required for this examination. However, the applicant must have already passed examination Elements I and II. The *second class* radiotelePHONE examination consists of F. C. C. Elements II. It is mostly technical and covers basic radiotelePHONE theory (including electrical calculations), vacuum tubes, transistors, amplifiers, oscillators, power supplies, amplitude modulation, frequency modulation, measuring instruments, transmitters, receivers, antennas and transmission lines, etc.

(3) **First Class RadiotelePHONE License.** No on-the-job experience is required to qualify for this examination. However, the applicant must have already passed examination Elements I, II, and III. (If the applicant wishes, he may take all four elements at the same sitting, but this is

not the general practice.) The *first class* radiotelePHONE examination consists of F. C. C. Element IV. It is mostly technical covering advanced radiotelePHONE theory and basic television theory. This examination covers generally the same subject matter as the *second class* examination, but the questions are more difficult and involve more mathematics.

Which License Qualifies for Which Jobs?

The **THIRD CLASS** radiotelePHONE license is of value primarily in that it qualifies you to take the *second class* examination. The scope of authority covered by a *third class* license is extremely limited.

The **SECOND CLASS** radiotelePHONE license qualifies you to install, maintain, and operate most all radiotelePHONE equipment except commercial broadcast station equipment.

The **FIRST CLASS** radiotelePHONE license qualifies you to install, maintain, and operate every type of radiotelePHONE equipment (except amateur, of course) including all radio and television stations in the United States, and in its Territories and Possessions. This is the highest class of radiotelePHONE license available.

How Long Does it Take to Prepare for F. C. C. Exams?

The time required to prepare for FCC examinations naturally varies with the individual, depending on his background and aptitude. Grantham training prepares the student to pass FCC exams in a minimum of time.

In the Grantham *correspondence course*, the average beginner should prepare for his *second class* radiotelePHONE license after from 300 to 350 hours of study. This same student should then prepare for his *first class* license in approximately 75 additional hours of study.

In the Grantham *resident course*, the time normally required to complete the course and get your license is as follows:

In the **DAY course** (5 days a week) you should get your *second class* license at the end of the first 9 weeks of classes, and your *first class* license at the end of 3 additional weeks of classes. This makes a total of 12 weeks (just a little less than 3 months) required to cover the whole course, from "scratch" through *first class*.

In the **EVENING course** (3 nights a week) you should get your *second class* license at the end of the 15th week of classes and your *first class* license at the end of 5 additional weeks of classes. This makes a total of less than 5 months required to cover the whole course, from "scratch" through *first class*, in the evening course.

HERE'S PROOF that Grantham Students prepare for F. C. C. examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

Name	License	Weeks
James C. Bailey, 217 Bohrends Ave., Juneau, Alaska	1st	12
Edward R. Barber, 907 S. Winifred, Tacoma, Wash.	1st	20
M. A. Dill, Jr., 20 Cherry St., Gardiner, Maine	1st	12
Bernhard G. Fokken, Route 2, Canby, Minn.	1st	12
Thomas J. Hoof, 216 S. Franklin St., Allentown, Pa.	1st	22
Clyde C. Morse, 7505 Sharronlee Dr., Mentor, Ohio	1st	12
Louis W. Pavek, 838 Page St., Berkeley 10, Calif.	1st	16
Wayne Winsauer, 2009 B St., Bellingham, Wash.	1st	12

To better serve our many students throughout the nation, Grantham School of Electronics maintains four separate schools—located in Los Angeles, Seattle, Kansas City, and Washington, D. C.—all offering the same resident courses in F. C. C. license preparation. (Correspondence courses are conducted from Hollywood.)

The Grantham course is designed specifically to prepare you to pass FCC examinations. All the instruction is presented with the FCC examinations in mind. In every lesson test and pre-examination you are given constant practice in answering FCC-type questions, presented in the same manner as the questions you will have to answer on your FCC examinations.

Why Choose Grantham Training?

The Grantham Communications Electronics Course is planned primarily to lead to an F. C. C. license, but it does this by **TEACHING** electronics. This course can prepare you *quickly* to pass F. C. C. examinations because it presents the necessary principles of electronics in a simple "easy to grasp" manner. Each new idea is tied in with familiar ideas. Each new principle is presented first in simple, everyday language. Then after you understand the "what and why" of a certain principle, you are taught the technical language associated with that principle. You learn more electronics in less time, because we make the subject easy and interesting.

Is the Grantham Course a "Memory Course"?

No doubt you've heard rumors about "memory courses" or "cram courses" offering "all the exact FCC questions". Ask anyone who has an FCC license if the necessary material can be memorized. Even if you had the exact exam questions and answers, it would be much more difficult to memorize this "meaningless" material than to learn to understand the subject. Choose the school that teaches you to thoroughly understand—choose Grantham School of Electronics.

Is the Grantham Course Merely a "Coaching Service"?

Some schools and individuals offer a "coaching service" in FCC license preparation. The weakness of the "coaching service" method is that it presumes the student already has a knowledge of technical radio and approaches the subject on a "question and answer" basis. On the other hand, the Grantham course "begins at the beginning" and progresses in logical order from one point to another. Every subject is covered simply and in detail. The emphasis is on making the subject easy to understand. With each lesson, you receive an FCC-type test so you can discover daily just which points you do not understand and clear them up as you go along.

For further details concerning F. C. C. licenses and our training, send for our **FREE** booklet, "Careers in Electronics". Clip the coupon below and mail it to the School nearest you.

Get your First Class Commercial F. C. C. License Quickly by training at



GRANTHAM SCHOOL OF ELECTRONICS

1505 N. Western Ave.
Los Angeles 27, Calif.
(Phone: HO 7-7727)

408 Marion Street
Seattle 4, Wash.
(Phone: MA 2-7277)

3123 Gillham Road
Kansas City 9, Mo.
(Phone: JE 1-6320)

821-19th Street, N.W.
Washington 6, D. C.
(Phone: ST 3-3614)

MAIL COUPON NOW—NO SALESMAN WILL CALL →

May, 1962

Accredited by the National Home Study Council



(Mail in envelope or paste on postal card)

To: **GRANTHAM SCHOOL OF ELECTRONICS**
NATIONAL HEADQUARTERS OFFICE
1505 N. Western Ave., Hollywood 27, Calif.


Please send me your free booklet telling how I can get my commercial F. C. C. license quickly. I understand there is no obligation and no salesman will call. 28-E

Name _____ Age _____

Address _____

City _____ State _____

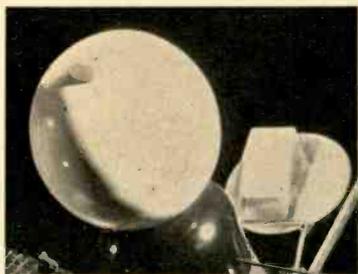I am interested in: Home Study, Resident Classes




Moon Ball . . . Those hefty (96.5 lbs.) white balls we've been shooting at the moon on the nose of Ranger spacecraft are jam-packed with instruments and radio equipment. (See OUR AMAZING NEW ROBOTS, July '61 EI.) The job of the 25-inch spheres is to gather data on such things as temperature, moonquakes and other lunar conditions. The moon balls are produced by Ford's Aeronutronic Division. They have a thick outer shell of balsa and a 12-inch inner survival sphere in which the scientific instruments are stored.

Designed to withstand the fantastic lunar climate, the survival area is protected by an insulating vacuum and a shot of water that is supposed to keep the temperature fairly constant.

According to the standard flight plan, the capsule separates from the Ranger at 25 miles from the moon's surface and slows down to about 150 mph by the use of retrorockets before landing on the green cheese. The Ranger isn't so lucky. The builders don't plan to hear from it again after it takes a 5,000-mph swan dive into the face of the man in the moon.

Hot Stuff . . . RCA has developed a thermoelectric material that generates electricity more efficiently than any of its kind. The substance is an alloy of germanium and silicon. A multi-layered sandwich measuring a foot square produces up to 10 kilowatts of electricity when heated to 1800° F. The RCA people envision self-contained, silent generators using the heat of a nuclear source, solar energy or a flame to power equipment in remote areas or outer space (see THESE GENERATORS HAVE NMP! March '62 EI). Our photo shows an RCA researcher testing a small model of the new generator in a vacuum chamber.

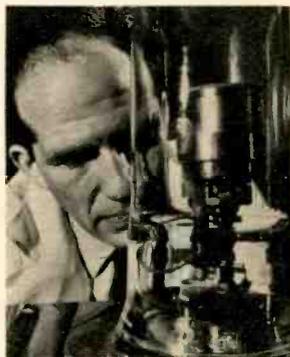

Cleaner Wasteland . . . Westinghouse has built a new TV picture tube that eliminates those annoying horizontal lines. The left side of our photo shows a cleaned-up vast wasteland image, while on the right is the normal line-filled image.

Westinghouse does it by subjecting the electron beam in the picture tube to a high-frequency wobbler signal that jiggles the scanning spot up and down to fill in between the lines. A split-focus grid in the electron gun permits the simple combination of the wobbler and the regular horizontal sweep.

Pocket Rocket . . . The unhappy dogface slogging through a ground war used to have just one defense against strafing planes—he dived into the ditch. But the Army and Marines are changing things. The GI of today can whip out a 20-pound guided missile capable of tracking down and destroying any strafers. The missile's called Redeye.



BUILD 10-25 RADIO

CIRCUITS AT HOME

with the New
PROGRESSIVE RADIO "EDU-KIT"®

A Practical Home Radio Course

BUILD

- ★ RECEIVERS
- ★ TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ SIGNAL TRACER
- ★ AMPLIFIER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed
- ★ EXCELLENT BACKGROUND FOR TV
- ★ SCHOOL INQUIRIES INVITED
- ★ Sold in 79 Countries

only
\$14.95
up



Reg. U.S.
Pat. Off.

Training Electronics Technicians Since 1946

YOU DON'T HAVE TO SPEND HUNDREDS OF DOLLARS FOR A RADIO COURSE

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing. THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL.

You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester, Square Wave Generator and the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build Receiver, Transmitter, Square Wave Generator, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for television, Hi-Fi and Electronics.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the small price you pay. The Signal Tracer alone is worth more than the price of the entire Kit.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worthwhile investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide a steadily learned, thorough and interesting background in radio.

You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to reg. ar. broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional radio technician.

Included in the "Edu-Kit" course are Receiver, Transmitter, Code Oscillator, Signal Tracer, Square Wave Generator and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instruction necessary to build several different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, hardware, tubing, punched metal chassis, Instruction Manuals, hook-up wire, solder, selenium rectifiers, volume controls and switches, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electronic soldering iron, and a self-powered Dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator. In addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

FREE EXTRAS

- SET OF TOOLS
- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS
- ALIGNMENT POOL
- WRENCH SET
- VALUABLE DISCOUNT CARD
- CERTIFICATE OF MERIT
- TESTER INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE & QUIZZES
- TELEVISION BOOK & RADIO TROUBLE-SHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE & FCC AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of trouble in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

FROM OUR MAIL BAG

J. Statatits, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself; I was ready to spend \$240 for a course, but I found you ad and sent for your Kit."

Ben Valerio, P. O. Box 21, Magna, Utah, writes: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the past seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different Kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Robert L. Shuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Trouble-shooting Tester that comes with the Kit is really swell, and finds the trouble, if there is any to be found."

Choose From These Popular "Edu-Kit" Models

- # 10A: 10 Circuits \$14.95
- # 15A: 15 Circuits \$19.95
- # 16A: 16 Circuits (includes Printed Circuitry) \$22.95
- # 20A: 20 Circuits (includes Printed Circuitry and 4 Advanced Circuits) \$26.95
- # 25A: 25 Circuits (includes Printed Circuitry and 9 Advanced Circuits) \$30.95

UNCONDITIONAL MONEY-BACK GUARANTEE

Please RUSH my Progressive Radio "Edu-Kit" to me.
BE SURE TO INCLUDE all the FREE EXTRAS and BONUS RESISTOR and CONDENSER KITS WORTH \$7.00.

- MODEL desired _____ Price _____
- Send "Edu-Kit" postpaid. I enclose remittance in full.
 - Send "Edu-Kit" C.O.D. I will pay postage.
 - Send me FREE additional information describing "Edu-Kits."


Name _____
Address _____

PROGRESSIVE "EDU-KITS" INC.

1186 Broadway, Dept. 541AE, Hewlett, N. Y.

COMPLETE SERVICE TRAINING

... written so you can understand it!

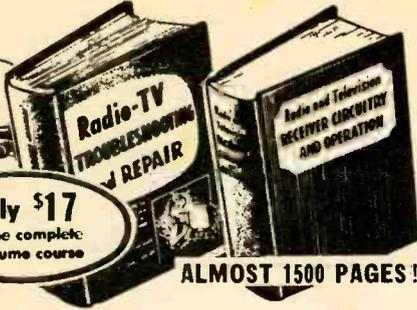

Only \$17
for the complete
2-volume course

ALMOST 1500 PAGES!

Fix any TV or Radio Ever Made

EASIER - BETTER - FASTER!

No complicated theory or mathematics! These famous Ghirardi books get right down to brass tacks in showing you how to handle all types of AM, FM, and TV service work by approved professional methods. Almost 1500 pages and over 800 clear illustrations show how to handle every phase of troubleshooting and servicing. Each book is co-authored by A. A. Ghirardi whose manuals have helped train more servicemen than any other books or courses of their kind!

1—Radio and Television Receiver TROUBLESHOOTING AND REPAIR

A complete guide to profitable professional methods. For the beginner, it is a comprehensive training course. For the experienced serviceman, it is a quick way to "brush up" on specific jobs, to develop improved techniques or to find fast answers to puzzling service problems. Includes invaluable "step-by-step" troubleshooting charts that show what to look for and where. 820 pages. 417 illustrations, price \$10.00 separately. (708578)

2—Radio and Television Receiver CIRCUITRY AND OPERATION

This 689-page volume is the ideal guide for servicemen who realize it pays to know what really makes modern radio-TV receivers "tick" and why. Gives a complete understanding of basic circuits and circuit variations; how to recognize them at a glance; how to eliminate guesswork and useless testing in servicing them. 417 illus. Price separately \$9.00. (708214)

Special low price . . . you save \$2.00

If broken into lessons and sent to you as a "course," you'd regard these two great books as a bargain at \$100 or more! Under this new offer, you buy both books for only \$17.00 . . . you save \$2.00. No lessons to wait for. You learn fast—and right!

STUDY 10 DAYS FREE!

Dept. PR-52, HOLT, RINEHART & WINSTON, INC., (823900)
Technical Div., 383 Madison Ave.,
New York 17, N. Y.

Send books below for 10-day FREE EXAMINATION. In 10 days I will either remit price indicated (plus postage) or return books postpaid and owe you nothing.

Radio & TV Receiver TROUBLESHOOTING & REPAIR (Price \$10.00 separately) (708578)

Radio & TV CIRCUITRY & OPERATION (Price \$9.00) (708214)

Check here for MONEY-SAVING COMBINATION OFFER

Save \$2.00. Send both of above big books at special price of only \$17.00 for the two. (Regular price \$19.00 . . . you save \$2.00.) (709006)

SAVE! Send cash with order and we pay postage. Same return privilege with money promptly refunded.

Name _____

Address _____

City, Zone, State _____

Outside U.S. Add \$1.50 for TROUBLESHOOTING & REPAIR, \$9.50 for CIRCUITRY & OPERATION; \$18.00 for both. Cash only, but money refunded if you return books in 10 days. (Above offer expires January 15, 1963)

...electronics in the news

As you might deduce from its name, Redeye has an eye in the nose which detects infrared energy given off by a plane's engine and steers the missile to its target. Two pop-out fins control flight. The Redeye measures just 4 feet 3 inches from eye to tail, is 3 inches in diameter and can be shoulder-fired like a bazooka. Its guidance system was developed by General Dynamics of Pomona, Calif.

Bee-Bob SOS . . . A new sound has been added to the maritime distress frequency of 2182 kc. It's a distinctive alert signal adopted recently by the Coast Guard, consisting of two modulating tones—one at 2,200 cycles and the other at 1,300—which alternate four times each second for 45 seconds. When the bee-bop signal is heard, it means the Coast Guard has received a distress message and all stations must clear the




frequency to facilitate communications with the ship or plane that is in trouble. Since the signal is so new, the Coast Guard wants reports (send them to CG headquarters in New York or San Francisco) from anyone who hears the signals as to readability, listener's location, time, date and how well the bee-bop quieted traffic on the frequency.

The little transistorized signal generator is shown in our photo.

**want to
double
your pay?**

**Move Ahead
in
ELECTRONICS**

*Get All
3 Free!*

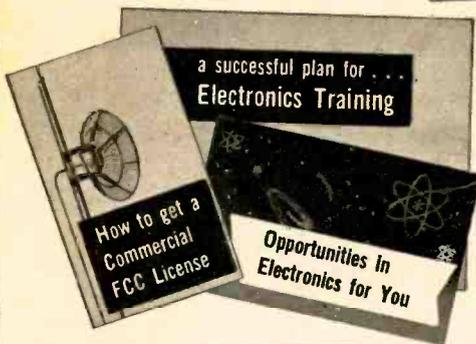


**Get This Handy Pocket
Electronics Data Guide**

Free...

Puts all the commonly used conversion factors, formulas, tables, and color codes at your fingertips. Yours absolutely free if you mail the coupon today. No further obligation!

**TO GET THIS FREE GIFT,
MAIL COUPON TODAY!**

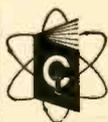FIND OUT how the FCC license helps you get a better job or increase your pay on your present job



MAIL COUPON TODAY

Cleveland Institute of Electronics

Cleveland Institute of Electronics
Desk EI 39, 1776 E. 17th St., Cleveland 14, Ohio

Please send Free Career Information prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below:

- | | |
|---|---|
| <input type="checkbox"/> Military | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radio TV Servicing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Manufacturing | <input type="checkbox"/> Telephone Company |
| <input type="checkbox"/> Amateur Radio | <input type="checkbox"/> Other |

**Your FCC License
Or Your Money Back**

Completion of the Master Course (both Sections) will prepare you for a First Class Commercial Radio Telephone License with a Radar Endorsement. Should you fail to pass the FCC examination for this license after successfully completing the Master Course, you will receive a full refund of all tuition payments. This guarantee is valid for the entire period of your enrollment agreement.

**Cleveland Institute Announces
A New and Dynamic Technician Training
Program in Computers, Servo
Mechanisms, Magnetic Amplifiers, and
Others.**

Other advanced fields covered include Basic Math, A. C. Circuit Analysis, Pulse Circuitry, Color TV, Radar, Advanced Measuring Techniques, Industrial Electronics, Instrumentation, Automation, Radio Telemetry. Send for information today.

**Accredited by the
National Home Study Council**

In what kind of work are you now engaged?

In what branch of Electronics are you interested?

Name Age

Address

City Zone State


EI-39



EMC's UNBEATABLE VALUES!!!

You get the most
per measurement dollar!

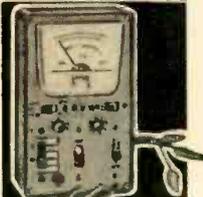All New precision instruments . . . satisfaction guaranteed! Best quality! By far the best value obtainable in wired or kit form!



with complete instruction pair of test leads.

EMC NEW MODEL 212 . . . TRANSISTOR ANALYZER . . .
Checks DC current gain in 3 ranges to 200. Tests for leakage. Checks all transistors as oscillators both in and out of circuit. Can be used to signal trace AF, IF or RF circuits. Checks condition of diodes. Tests battery voltage on 0-12 scale. Checks DC current drain on 0-80 ma scale. Supplied manual, transistor listing and Model 212 . . . **\$18.50 Wired**
Model 212 Kit . . . **\$13.50**



EMC NEW MODEL 213 TUBE TESTER . . .
Completely modern! Completely flexible! Completely new! Checks all the new 12 prong (Compactron), Nuvisor, Novar, and 10 prong tubes, in addition to octal, loctal, miniature, and 9 prong tubes. Tests each tube for shorts, leakages, intermittents, opens, as well as for quality. Each section of multi-purpose tube is checked separately. Magic eye, Voltage Regulator and HI-FI tubes are also tested. Unique switching arrangement makes the checker obsolescent proof. Supplementary tube listings supplied periodically at no cost to keep instrument up to date. It comes complete with instructions and tube charts in ring bound manual.

Model 213 (in bakelite case with strap) . . . **\$28.90 Wired**

Model 213 Kit . . . **\$18.90**

Model 213P (in wood carrying case) . . . **\$32.25 Wired**

Model 213 P Kit . . . **\$21.90**



EMC NEW MODEL SA SOCKET ADAPTOR . . .
Enables user to check 12 pin Compactron, Nuvisor, Novar and 10 pin tubes with any type tube tester including mutual conductance type.

Model SA . . . **\$9.45 Wired**

Model SA Kit . . . **\$4.95**

Yes, tell me more, send me **FREE** a detailed catalog of the Complete EMC Line. EL-5


NAME _____
STREET _____
CITY _____ STATE _____

EMC Electronic Measurements Corp.
625 B'way, New York 12, N. Y.
Ex. Dept., Pan-Mar Corp., 1270 B'way, New York 1, N. Y.

...electronics in the news

Sparkling Development . . . Ever since the transistor revolutionized radio, everyone from do-it-yourselfers to big business has been trying to cash in on the invention. The automobile industry is hard at work on a transistorized ignition system. A few models have been developed and some put on the market, but in our opinion *none* of them is practical from a cost-benefit standpoint.

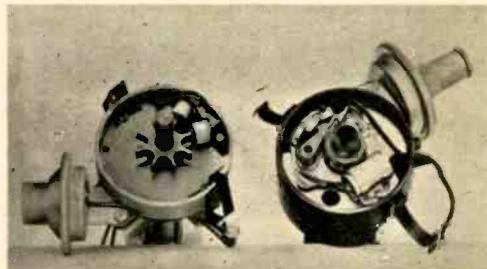Motorola has announced development of the newest transistorized ignition design. In place of the conventional mechanical breaker arm, points and condenser you find in normal distributors (right, in photo), the Motorola device (left, in photo) uses a pulse generator



which consists of a small, spoked wheel rotating past a pair of electromagnets without touching them. The pulses created by this cutting of magnetic lines of force trigger an amplifier that fires the regular ignition coil. Because there is no direct contact, distributor breakdown from wear is virtually eliminated. Dwell time is constant at all speeds, Motorola says, and battery drain is low.

The apparatus is still in the testing stage and there are no concrete marketing plans. Motorola has not announced any cost figures so a close evaluation is impossible.

The New Giant Size . . . That black cylinder held by the young man in our photo is neither a chunk of gas pipe nor a telescope. It is just a plain resistor. But don't ask to see the rest of the radio that goes with it. The giant component, made of glass by the Corning Works, is designed to serve as a dummy load for testing transmitters of 10,000 to 40,000 watts in the Project Mercury tracking

The Same School That Originated The RTS BUSINESS PLAN

...NOW
Proudly
Presents...

A SPECIAL COMPACT COURSE COVERING ALL THREE PHASES OF **ELECTRONICS**

The Entire Course Is Made
Up Of The Following:

- 35 LESSONS COVERING BASIC AND INTERMEDIATE ELECTRONICS
- 9 EQUIPMENT KITS COMPLETE WITH TUBES AND BATTERIES
- SOLDERING IRON
- 25 LESSONS COVERING THESE ADVANCED ELECTRONIC SUBJECTS:
 - Thyratron Tubes • Semiconductors • Electronic Symbols and Drawings • Voltage-Regulators • Electronic-Timers • Control Systems • X-Rays • Photoelectric Devices • Dielectric Heating • Geiger Counters • Pulse Circuitry • Clippers and Limiters • Multivibrators • Electronic Counters • Radar • Magnetic Amplifiers • Analog-Computers • DC Amplifiers • Digital Computers • Storage Systems • Input and Output Devices • Servomechanisms • Telemetering
- 60 EXAMINATIONS
- UNLIMITED CONSULTATION SERVICE
- KIT MANUALS
- DIPLOMA UPON GRADUATION

AND MUCH MORE...

**BASIC • INTERMEDIATE • ADVANCED
DESIGNED FOR THE BUSY MAN OF TODAY**

This is MODERN training for the MODERN man. You'll find no "horse and buggy" methods here. Every page of this streamlined course is devoted to important Electronics principles and practical projects. You'll be amazed how fast you grasp Electronics the RTS way. RTS has combined modern THEORY and PRACTICE to make this the finest training program of its kind available!

SATISFIES NOVICE, TECHNICIAN OR HOBBYIST

Whether you're new to Electronics or an old "pro," chances are you'll find this to be the ideal course for you. The novice will appreciate the completeness of the training. It starts with the most basic considerations, covering each important point thoroughly, yet concisely. The technician will enjoy the practical review of fundamentals and profit from the 25 advanced subjects covered.

RTS GIVES YOU "TOP MILEAGE" FOR YOUR TRAINING DOLLAR

The price quoted below buys EVERYTHING — there are no extras to pay for. RTS has gone "all out" to give you the best training value in America. Why pay hundreds of dollars for training such as we offer when it's available for this LOW PRICE? If you can find a better training bargain... BUY IT!

CAN BE COMPLETED IN MONTHS INSTEAD OF YEARS

Some students will complete this course with "Jet-Like" speed but we allow up to two years if your circumstances require it. You study at your own rate. You are ENCOURAGED but not pushed. You'll find the lessons professionally written but easy to understand. LET US SEND YOU ONE OF THESE LESSONS ALONG WITH YOUR CAREER BOOKLET SO YOU CAN SEE FOR YOURSELF. NO OBLIGATION!

COMPLETE
COST...
INCLUDES ALL KITS,
TUBES, BATTERIES, ETC.
\$125.00*

***TERMS ALSO AVAILABLE**

AS LITTLE AS...

\$5.00 DOWN

\$5.00 PER MONTH

THE FIRST TRAINING KIT IS SENT
IMMEDIATELY UPON ENROLLMENT

DON'T LOSE OUT — FIND OUT!

RTS ELECTRONICS DIVISION Dept. E1-52

815 E. ROSECRANS AVENUE LOS ANGELES 99, CALIFORNIA

Rush me full information by return mail. (Please Print)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

NO SALESMAN WILL CALL ON YOU!

RTS' Membership in
The Association of
Home Study Schools
is your assurance of
Reliability, Integrity and
Quality of Training.



RTS ELECTRONICS DIVISION
815 E. ROSECRANS AVENUE
LOS ANGELES 59, CALIFORNIA

Est. 1922



L 201A

Rush
Coupon
for **FREE
FACTS!**

Get Into One Of Today's
TOP OPPORTUNITY FIELDS

ELECTRICITY —ELECTRONICS TELEVISION RADIO · ELECTRONICS

Train in the New Shop-Labs of Oldest,
Best Equipped School
of Its Kind in U.S.
Founded 1899

in Chicago—Electrical and Electronic Center. Prepare for a better job and a successful future. Train on real equipment — no advanced education or previous experience needed. Lifetime employment service to graduates. Part time employment help to students. Finance Plan—enroll now, pay most of tuition later.

FREE BOOK—Mail Coupon or write to address below for Big Free Illustrated Book—"Guide to Careers."

Information comes by mail. No obligation
and NO SALESMAN WILL CALL.

COYNE ELECTRICAL SCHOOL

Chartered as an Educational Institution Not for Profit
1501 W. Congress Pkwy., Chicago 7, Ill., Dept. 52-A

COYNE ELECTRICAL SCHOOL, Dept. 52-A
1501 W. Congress Pkwy., Chicago 7, Ill.

Send **FREE** Book, "Guide to Careers" and details of all training you offer. I am especially interested in

Electricity Television Both Fields

Name _____

Address _____

City _____

State _____

(I understand no salesman will call)

KUHN

"LEADERS IN SPECIALIZED
RECEIVING EQUIPMENT"

MOBILE FIXED CONVERTERS

- POLICE
- FIRE
- COMMERCIAL
- CITIZEN'S BAND

**345A
Complete
\$29.95**



A new high gain
Crystal Controlled
Converter. Excellent
sensitivity
Rugged
construction... Easy
to install. De-
signed for stan-
dard transistor
car radios. Re-
quires no high
voltage supply.
2-54 MC or 150-
162 MC.

KUHN CONVERTERS . . . the most advanced line
. . . designed for optimum performance.

**348A
Complete
\$34.95**



Transistorized, di-
rectly tunable Converter.
Powered with self-contained
mercury cell. Excellent sen-
sitivity and stability. Designed
for car, home or portable re-
ceivers. Two types available:
Aircraft VHF 115-130 MC or
150-162 MC.



**344A
Complete
\$23.95**

A new low cost
Crystal Controlled Converter
designed for use with standard
transistor car radios. Operates
directly from 12V DC. Rugged
construction. Good sensitivity.
Range 2-54 MC.

315A Complete \$14.95



A low cost Tunable Con-
verter for any 10 MC
area of: 26-34 MC. Air-
craft VHF, or 150-160
MC. Easily installed. For
use with home or auto
sets.
315A Directly Tunable
Converter. Available in
four ranges: 26-30 MC,
30-50 MC, 115-130 MC,
or 150-160 MC. Com-
plete \$21.95

ORDER TODAY or
SEND FOR FREE
CATALOG . . . con-
taining complete
information on a
full line of:
CONVERTERS AND
RECEIVERS FOR
EVERY APPLICATION



20 GLENWOOD
CINCINNATI 17,
OHIO

...electronics in the news

network. It also can be used as a power dissipating termination for big transmitting antennas. The resistor, measuring 4 feet in length and 5 inches in



diameter, is made up of a tin oxide film fused into the glass. Various models have 140 to 300 ohms resistance or 70 to 600 ohms impedance.

ITEMS . . . New York got its first all-stereo FM broadcasting station in WTFM, operating on 103.5 mc. Transmitter and studio are on Long Island. Enough other FM stations are broadcasting stereo part-time to give New Yorkers some variety in their multiplex.

With all those satellites careening around the globe you need a score card to tell which one is doing what. The Air Force Research Labs have devised a system that can display six orbital tracks at the same time on a large cathode-ray tube. The tracks are superimposed on a projection of the world. When a light beam is pointed at one of the spots representing a satellite, computer-stored information flashes on the screen, giving the craft's identification, exact location and other data.

The Coast Guard has set afloat in Chesapeake Bay the first nuclear-powered navigation buoy ever built. The 7-ton, 26-foot-high buoy is topped by a blinking light. Power comes from a drum-size generator in its base, under the waterline. The generator consists of

The Fisher KX-200 80-Watt Stereo Control-Amplifier StrataKit, \$169.50.*



It has four things that others haven't.

1. StrataKit Construction. Assembly by totally error-proof stages (strata). Each stage corresponds to a *separate* fold-out page in the Instruction Manual. Each stage is built from a *separate* transparent packet of parts. Major components come already mounted on the extra-heavy-gauge steel chassis. Wires are *pre-cut* for every stage—which means every page. Result: Absolutely equal success by the experienced kit builder or the completely unskilled novice!

2. Built-In d'Arsonval Meter. For laboratory-accurate adjustment of bias and balance. Assures peak performance from the start; permits 'touching up' for continued peak performance throughout the years, regardless of tube aging. No other single-chassis control-amplifier kit has this vital feature.

3. Third-Speaker Output with Volume Control. Blends the two stereo channel outputs to feed a third loudspeaker system—at *any* desired volume level. Ideal for center-channel stereo fill-in or for a mono extension speaker in another room of the home. A Fisher exclusive among control-amplifier kits.

4. The Fisher Name. No comment necessary.

USE THIS COUPON FOR FURTHER INFORMATION

Fisher Radio Corporation
21-55 44th Drive, Long Island City 1, N. Y.

Please send me without charge the complete Fisher StrataKit catalogue.

NAME _____

ADDRESS _____

CITY _____

ZONE _____

STATE _____

EI-511



*Walnut or Mahogany cabinet, \$24.95. Metal cabinet, \$15.95. Prices slightly higher in the Far West.

YOU NEED THIS

FREE GIANT B-A CATALOG



SAVE UP TO 50% ON B-A SELECTED KITS

HI-FI AND STEREO SYSTEMS & COMPONENTS

TOP VALUES IN POWER AND HAND TOOLS

30 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

BURSTEIN-APPLEBEE CO.

Dept. EI, 1012 McGee St., Kansas City 6, Mo.

Rush me New 1962 B-A Catalog No. 621


Name

Address

City State

SEND FOR IT TODAY

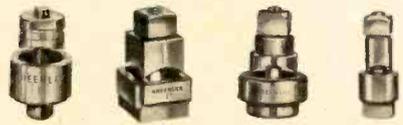QUICKLY CUT HOLES
in metal, plastics,
hard rubber...



GREENLEE CHASSIS PUNCHES

Make smooth, accurate openings in 1½ minutes or less ... for sockets, plugs, controls, meters, panel lights, etc. Easy to use ... simply turn with wrench. Many sizes and models. Write for literature.



GREENLEE TOOL CO. 1915 Columbia Ave., Rockford, Illinois

...electronics in the news

60 pairs of thermoelectric elements heated by strontium-90. It should keep sending up juice for about 10 years.

The sparsely inhabited Very Low Frequency band may in a few months be jumping with life like the short-wave frequencies. The Navy has announced plans to build a 2,000,000-watt-or-over VLF transmitter in Australia and NATO is putting up another big rig in England. Like the Navy VLF stations at Cutler, Me., and Jim Creek, Wash., the new transmitters are designed for communications with ships and submarines. Meanwhile, the Air Force has carried out research showing VLF to be immune to such man-made ionosphere disturbances as high-altitude nuclear explosions, which wreck SW communications. The reason, of course, lies in the fact that VLF communications are by groundwave instead of skywave (see **THE INCREDIBLE BASEMENT OF RADIO**, November '61 EI).

Signals transmitted in the visible light and infrared spectra are not limited to line-of-sight use, the Naval Research Lab has found. Both types of signals have been transmitted as much as 200 miles at night. The over-the-horizon shots were possible because tiny particles in the low atmosphere scatter the signals, reflecting a portion back to earth.

A New Jersey company, United States Radium Corp., has patented a type of **radioactive lantern** or flashlight. The lights use radioactive tritium gas (or krypton gas) in the bulbs, producing a bright beam of light for a long period of time. When marketed commercially, the lights will carry the brand name of Isolite.

Pilot Radio, maker of radios and hi-fi components since 1919, has been acquired by **Jerrold Electronics** of Philadelphia. Jerrold also has picked up Harman-Kardon (hi-fi) and Taco (TV antennas) in recent months.

Successful orbit of amateur radio satellite **OSCAR** (**THE HITCHHIKING HAM**, March '62 EI) set amateurs to designing OSCARS II and III.



Electronic Marketplace

The Winner . . . H. H. Scott, it turns out, saddled the winner in a little race of interest mainly to those in the hi-fi trade. The stakes were the marketing of the first stereo FM tuner kit. Scott's winning (by a few days) entry was the LT-110 multiplex kit.

One of the nagging questions faced by kit manufacturers was what to do about the hard-to-align multiplex section. Scott's solution was to build and




align the critical section and mount it on the chassis, along with the pre-wired front-end. The builder merely puts together the rest of the components and connects them to the already-mounted units. Only the simplest additional alignment is needed.

The LT-110 uses the time-switching type of circuitry. Claimed IHFM sensitivity is 2.2 microvolts. Kit price is \$159.95. H. H. Scott, Inc., 111 Powdermill Rd., Maynard, Mass.

Soundly Controlled . . . Zenith's latest Space Commander remote TV control takes the ups and downs out of televiewing. From across the room you can turn on the set, change channels, adjust volume control to three levels and kill the sound while the picture stays on (during windy commercials). These com-

FREE CAREER BOOKLET

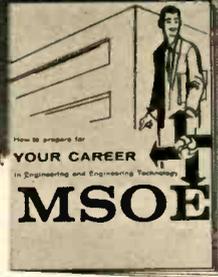

To guide you to a successful future in

ELECTRONICS RADIO-TV COMPUTERS ELECTRICAL ENGINEERING

This interesting pictorial booklet tells you how you can prepare for a dynamic career as an Electrical Engineer or Engineering Technician in many exciting, growing fields:

**MISSILES • AVIONICS • AUTOMATION
SALES • DEVELOPMENT
ELECTRICAL POWER • ROCKETRY
RADAR • RESEARCH**

Get all the facts about job opportunities, length of study, courses offered, degrees you can earn, scholarships, part-time work — as well as pictures of the Milwaukee School of Engineering's educational and recreational facilities. No obligation — it's yours free.

MILWAUKEE SCHOOL OF ENGINEERING

MAIL COUPON TODAY!

Milwaukee School of Engineering
Dept. EI-562, 1025 N. Milwaukee St., Milwaukee, Wis.

Please send FREE "Your Career" booklet

I'm interested in

Electronics Radio-TV Computers
 Electrical Engineering Mechanical Engineering

Name..... Age.....

PLEASE PRINT

Address.....

City..... Zone..... State.....

I'm eligible for veterans education benefits.

Discharge date..... MS-117

Build your own superb
SCOTT KITS!



**HAVE
FUN...
SAVE
MONEY**

Have fun... save money... build the best! Now you can get world-famous Scott stereo components in kit form. Think of it... you can build the fabulous new LT-110 FM Multiplex Stereo Tuner... your choice of two complete stereo amplifiers, or a preamp and separate power amp... all from H. H. Scott!

Write today. Find out about these exciting Scott kits.

**Choice of 3 Booklets
FREE**



H. H. Scott, Inc. 111 Powdermill Road, Maynard, Mass. Dept. 130-05
Send me the booklets checked below:
 20-page "Guide to Custom Stereo" Complete technical information on kits 16-page booklet explaining FM Stereo

Name _____
Address _____
City _____ Zone _____ State _____

Export: Morhan Exporting Corp., 458 Broadway, N.Y.C.



studying antenna system in Tri-State's electronics lab

learn more... earn more

College graduates enjoy higher income... sure advancement. Major corporations visit us regularly to interview and employ seniors. **BACHELOR OF SCIENCE DEGREE IN 27 MONTHS** in Electrical, Mechanical, Aeronautical, Chemical, Civil Engineering. **IN 36 MONTHS** B. S. Degree in Business Administration. Small classes. Campus. Dorms. Founded 1884. Low costs. Enter June, Sept., Jan., Mar. Write J. A. McCarthy for Catalog and "Your Career" Book.

TRI-STATE COLLEGE

4852 College Avenue

Angola, Indiana

Marketplace


mands are transmitted by a hand-held control via ultrasonic pulses.

The little command-signal generator has four pipes that produce varying tones from 37.75 to 41.25 kc. The ultra-



sound is picked up by a special microphone on the TV set and fed to a transistorized circuit containing stepping relays and a motor, which do the tuning. Zenith has 8 Space Commander models at varying prices. Zenith Radio Corp., Chicago 39, Ill.

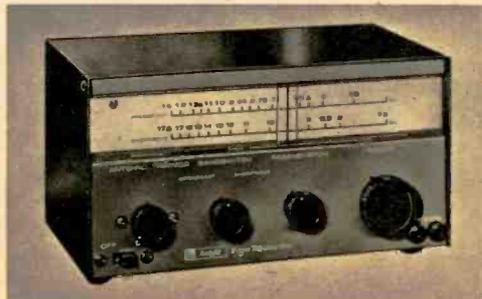Shelter Special... Allied is pushing its new battery-powered DX'er receiver kit as fallout shelter equipment. The transistorized regenerative set runs on four penlight cells and tunes the broadcast band plus a section of the short-wave band from 7.5 to 17.5 mc. Controls on the front panel include an antenna




BUILD THE FINEST *Professional Quality*

CUSTOMIZED

TV KIT

On Easy "Pay
As You Wire"
Terms. Only \$15
for the Starting
Package!

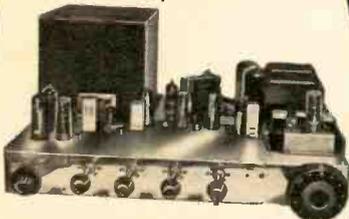The
"PROFESSIONAL"
Series—designed for
the perfectionist seeking
the finest in TV performance.
Easy to assemble. No technical
knowledge required. An ideal
"Learning" Kit with a Complete
Course of Study is available.



Also available:
**WIRED
CHASSIS**
for custom
installations
with a choice



of vertical or horizontal
controls and the newest
19", 23" or 27"
Picture Tube.

A few of the *Professional Quality* Features:

Choice of push-pull 10-watt audio or output
to your Hi-Fi system . . . D.C. restoration
. . . Ultra-linear sweep circuits . . . Newest
Standard Coil Model PKO Automatic Fine
Tuner . . . Super-sensitivity for fringe areas
. . . Complete line of Accessories for Custom
Installations.
Choice of 19", 23" or 27" CRT. Prices range
from \$119 to \$199.

U.S. Armed Services and over 4000 schools and
colleges have selected Transvision Receivers for
educational television.

Interested in Electronics?

Learn the basic principles of elec-
tronics from the Course available with the Kit.



TRANSVISION - New Rochelle, N.Y.
NE 6-6000

START NOW — MAIL THIS COUPON —

Dept. E1

TRANSVISION Electronics, Inc., New Rochelle, N.Y.

Send Free 8-page Catalog

Enclosed is \$2. for Assembly Instructions so that I might
see how easy it is to assemble the Transvision Kit. I understand that this will be refunded if I purchase a kit.

Enclosed is \$15 for the Starting Package. I understand that I can buy packages one at a time
as I wire. (Models range from \$119 to \$199.)

Name..... Address.....

City..... Zone..... State.....

Marketplace

trimmer and regen knob. Price is \$19.95.
Allied Radio, 100 N. Western Ave., Chi-
cago 80, Ill.

Ten Thousand Microfarads . . . That's
the amount of filtering capacitance
you'll find in EICO's new battery elimi-
nator and charger (model 1064) and it's
what makes the instrument's DC output
ripple-free. The 1064 can be used for
servicing or experimental work with
transistors, battery rejuvenation, etc.
The unit delivers 6 volts at 20 amps or
12 volts at 10 amps. It's fully adjustable
and metered. Price for the kit is ap-
proximately \$44; wired, around \$53.
EICO, 33-00 Northern Blvd., Long
Island City 1, N. Y.



Breadboarding Deluxe . . . If you're the
type who dreams up some novel circuit
and then forgets it before you get it
built, the 23-CSL Circuit Builder may
be for you. With this gadget you can
have the project hooked up, wired and

operating while it's still fresh in your
mind. No soldering, spring clips or
jumper wires are involved in the quick
assembly, re-design and disassembly.

Here's the secret. The 9½ x 12½-inch

EASIEST TO BUILD LAYER BUILT COLOR GUIDE

Grommes

DE LUXE HI-FIDELITY
KITS



**101GTK
FM TUNER**

Finest tuner kit offered! "Standard Coil" tuning unit is pre-wired, pre-aligned and can be tuned-in as soon as completed, without professional adjustments. Better reception than tuners costing 2 or 3 times as much. Latest circuits, matched crystal diode detector, Foster Seeley Discriminator, AFC, Electronic Tuning Eye. Quiet, drift-free. Simply and successfully assembled by anyone with screwdriver, pliers and soldering iron. Step-by-step instructions. Model 101GTK, only\$66.00



20 WATT STEREO AMP.
De Luxe stereo at half the cost! Two 10 watt channels with 2 pre-amps. 40 watts peak. Fre. Res. ± 1 DB. 20-20,000 CPS. 4 inputs. Output: 4, 8, 16 ohms. Automatic Loudness Control. **20LJK\$59.50**



10 WATT AMPLIFIER
With built-in pre-amp. 20 watts peak. Fre. Res. ± 1 DB. 20-20,000 CPS. 4 inputs. Output: 4, 8, 16 ohms. Automatic Loudness Control. **LJ6K\$27.50**

Many other kits available—
At dealers or sent prepaid with check or M.O.

FREE!

GROMMES Div. of Precision Electronics, Inc.
9101-T King Ave., Franklin Park, Ill.
Please rush details on Grommes Kit Line.

Name.....
Address.....
City..... State.....

GIANT CB SALE!!!

Closing out our stock of CB kits. Originally advertised at \$39.95 up. Complete with power supply, tubes, crystal, cabinet, wire, instructions, etc. Less microphone. Note: transmitter must be tuned and tested by or under supervision of person holding a first or second-class FCC license. All sales final at this price. Thousands now in use. Rush your order in today while the supply lasts.

- 110 VOLT CB TRANSCEIVER KITS **\$19.95**
- 12 VOLT CB TRANSCEIVER KITS **\$22.95**
- 6 VOLT CB TRANSCEIVER KITS **\$22.95**
- 3-Element CB BEAM ANTENNA Reg. \$19.95 (3 or more, \$10.99 ea.; 6 or more, \$9.99 ea.) SALE (mounts vertically or horizontally) Model BA-27 **\$11.99**
- CB-SPECIAL GROUND PLANE ANTENNA Reg. \$12.98 all aluminum—Model GP-27 (3 or more—\$7.99 ea.; 6 or more, \$6.99 ea.) SALE **\$8.99**
- COMMAND HOT-ROD CB ANTENNA Reg. \$11.98 4-ft. Continuously loaded fiberglass whip + trunk lid mount SALE **\$8.69**
- COMMAND CORSAIR Model CCB-1 Reg. \$19.98 Bumper mount + heavy spring + 102" st. steel whip SALE **\$8.99**
- COMMAND CORSAIR II Model CBB-2 Reg. \$22.95 double bumper mount + spring + 102" st. steel whip SALE **\$9.99**
- COMMAND STANDARD II Model CS-2 Reg. \$9.98 heavy duty body mount + spring + 102" st. steel whip SALE **\$6.89**
- GENERATOR NOISE SUPPRESSOR Model GNS Reg. \$3.98 tuneable for CB band (3 or more—\$1.49 ea.) SALE **\$1.99**
- 11-PC. CB SILENCER KIT Model NN-1 Reg. \$8.95 spark plug & distributor suppressors + gen. cond. and GNS SALE **\$3.49**
- RG8u COAXIAL CABLE 100 feet for **\$7.99**
- RG58u COAXIAL CABLE 100 feet for **\$2.99**

Check items wanted. Return ad or order with check or money order (include postage, excess returned). Sorry no C.O.D. Beam and Ground planes shipped express collect.

GROVE ELECTRONIC SUPPLY COMPANY


4101 W. Belmont Ave., Chicago 41, Ill.

Rush items checked Send latest CB sale Catalog

Name..... (please print)
Address.....
City..... Zone..... State.....


Marketplace

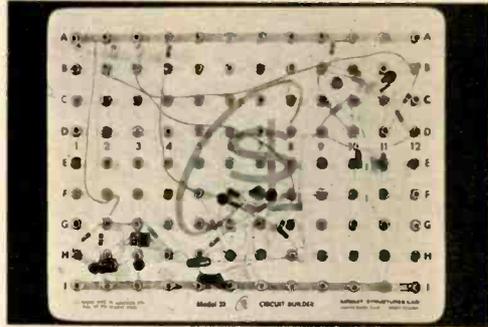board has 108 gold-plated cells. Inserted in each cell is a rubber core designed to hold as many as seven wires of varying sizes in firm contact with the metal cell



liner. The unit is priced at \$15. Circuit Structures Lab, Box 36, Laguna Beach, Calif.

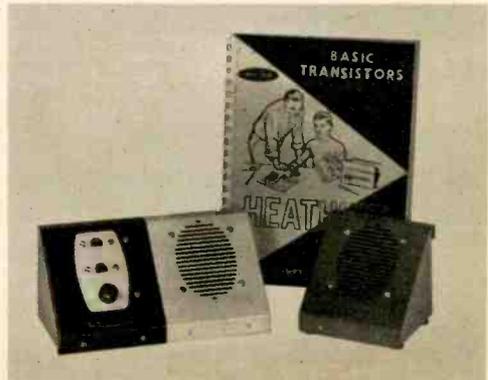Teach Yourself . . . If you're itching to get your hands on a transistorized something-or-other but lack basic knowledge of transistors, here's your chance to learn by doing. Heathkit's new EK-3 transistor education kit gives the newcomer an opportunity to assemble



a two-transistor receiver, a wireless broadcaster, an audio amplifier and a test oscillator. A special textbook makes it easy to sail through the course and you end up with a little intercom (the last project) to show for it. The kit goes for about \$17. Heath Co., Benton Harbor, Mich.

Marketplace

All About Tapes . . . *Tape-Log* is the title of a new catalog devoted solely to pre-recorded four-track stereo tapes, listing over 1,500 tapes by number, title, performers and price. It includes the complete libraries of 38 major tape producers, with new releases added each



issue. The log is published four times a year at 60¢ a copy or \$2 for a one-year subscription. Available from hi-fi

dealers or directly from the publisher, Danken Associates, 8244 Vista Del Mar, Playa Del Rey, Calif.

Music Center . . . A full stereo FM tuner, with a transistor/nuvistor circuit, a 40-watt all-transistor stereo amplifier and an automatic clock timer are combined in one compact cabinet to form the Knight All-In-One Music Center. Optional equipment, such as a record



player, tape deck and microphone, may be added. The timer turns the equipment on and off at pre-set times. The size is 4 7/8" x 13 1/4" x 8 inches deep. The model number is KN-310MC and the price is \$255. Allied Radio, 100 N. Western Ave., Chicago 80, Ill.

TV-RADIO Servicemen or Beginners . . .

Send for *Coyne's*
7-Volume Job-Training Set
on 7-Day **FREE TRIAL!**



The First
Practical
TV-RADIO-
ELECTRONICS
Shop
Library!

**Answers ALL Servicing Problems QUICKLY . . .
Makes You Worth More On The Job!**

Put money-making, time-saving TV-RADIO-ELECTRONICS know-how at your fingertips—examine Coyne's all-new 7-Volume TV-RADIO-ELECTRONICS Reference Set for 7 days at our expense! Shows you the way to easier TV-Radio repair—time saving, practical working knowledge that helps you get the BIG money! How to install, service and align ALL radio and TV sets, even color-TV, UHF, FM and transistorized equipment. New photo-instruction shows you what makes equipment "tick." No complicated math or theory—just practical facts you can put to use immediately right in the shop, or for ready reference at home. Over 3000 pages; 1200 diagrams; 10,000 facts!

SEND NO MONEY! Just mail coupon for 7-Volume TV-Radio Set on 7-Day FREE TRIAL! We'll include the FREE BOOK below. If you keep the set, pay only \$3 in 7 days and \$3 per month until \$27.25 plus postage is paid. Cash price only \$24.95. Or return set at our expense in 7 days and owe nothing. Either way, the FREE BOOK is yours to keep. Offer limited, so act NOW!

"LEARNED MORE FROM THEM THAN FROM 5 YEARS WORK!"

"Learned more from your first two volumes than from 5 years work."
—Guy Bliss, New York

"Sweet set for either the serviceman or the beginner. Every service bench should have one."
—Melvin Mesbruch, Iowa

FREE DIAGRAM BOOK!

We'll send you this big book, "150 Radio-Television Picture Patterns and Diagrams Explained" ABSOLUTELY FREE just for examining Coyne's 7-Volume Shop Library on 7-Day FREE TRIAL! Shows how to cut servicing time by reading picture-patterns, plus schematic diagrams for many TV and radio sets. Yours FREE whether you keep the 7-Volume Set or not! Mail coupon TODAY!



Like Having An Electronics Expert Right At Your Side!

VOL. 1—EVERYTHING ON TV-RADIO PRINCIPLES! 300 pages of practical explanations; hundreds of illustrations.

VOL. 2—EVERYTHING ON TV-RADIO-FM RECEIVERS; 403 pages; fully illustrated.

VOL. 3—EVERYTHING ON TV-RADIO CIRCUITS! 336 pages; hundreds of illustrations, circuit diagrams.

VOL. 4—EVERYTHING ON SERVICING INSTRUMENTS! How they work, how to use them. 368 pages; illustrated.

VOL. 5—EVERYTHING ON TV TROUBLESHOOTING! Covers all types of sets. 437 pages; illustrations, diagrams.

VOL. 6—TV CYCLOPEDIA! Quick and concise answers to TV problems in alphabetical order, including UHF, Color TV and Transistors; 868 pages.

VOL. 7—TRANSISTOR CIRCUIT HANDBOOK! Practical Reference covering Transistor Applications; over 200 Circuit Diagrams; 410 pages.

BOOKS HAVE BRIGHT, VINYL CLOTH WASHABLE COVERS

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL
1455 W. Congress Parkway, Dept. S2-E1, Chicago 7, Ill.

Yes! Send me COYNE'S 7-Volume Applied Practical TV-RADIO-ELECTRONICS Set for 7-Days FREE TRIAL per offer. Include "Patterns & Diagrams" book FREE!

Name Age


Address

City Zone State

Check here if you want Set sent C.O.D. Coyne pays postage on C.O.D. and cash orders. 7-Day Money-Back Guarantee.

Coyne

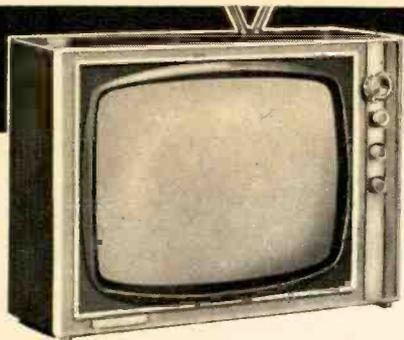Educational Book Publishing Division
ELECTRICAL SCHOOL
1455 W. Congress Parkway Dept. S2-E1, Chicago 7, Illinois



NOW... BUILD YOUR OWN TOP QUALITY TV SET

Save money as you enjoy constructing your own fine table-model TV set. Anyone can build it—no technical knowledge or skill needed. The "Custom 70" is *Performance Guaranteed* by NRI—the top name in Electronics training for nearly 50 years. Picture tube has 206 sq. in. of viewing area. All-American parts. Quality "slim-line" cabinet. Everything included at one low price. Package payment plan. Tear out this ad, write your name and address in margin and mail to CONAR INSTRUMENTS, 3939 Wisconsin Ave., Washington 16, D.C. Conar will rush pictures and facts.

EE2C

CONAR instruments A Division of NATIONAL RADIO INSTITUTE

**WIN!
WIN!
WIN!
WIN!**

YOU CAN BE ONE OF THIS YEAR'S WINNERS IN

**TRUE'S FREE
\$100,000 CONTEST!**

PRIZES GALORE 21-1962 STATION WAGONS!
SCORES OF BOATS!
DOZENS OF OUTBOARD MOTORS!

FREE ENTRY BLANKS AND CONTEST RULES IN
TRUE
THE MAN'S MAGAZINE
at your newsstands

ENTER NOW! ENTER NOW! ENTER NOW!

Marketplace

QSA? . . . Next time someone asks, "What is the strength of my signals?" (that's what QSA means), you won't have to guess at the answer if you equip your short-wave receiver with the Lafayette TM-59 S-meter. The meter uses a VTVM-type Wheatstone bridge circuit and can be added to any transformer-operated superheterodyne having AVC. The unit employs a single



6C4 tube. About \$8. Lafayette Radio, Syosset, N.Y. [Continued on page 103]

FREE

FOR YOU and 2 Friends RADIO SHACK'S

all NEW

1962

Electronics CATALOG



Yes, Radio Shack is publishing an all new special Spring and Summer Catalog for 1962 and we want you and your friends to see, shop from it, and save money on everything electronic. It's a big one—144 pages in size carrying thousands of new items, thousand more of up-to-date designs in standard equipment, and new low prices on other thousands of items wanted by everybody interested in electronics, from amateur to pro. Everyone is guaranteed to give you satisfaction or your money back! No Money Down Credit Terms. So mail the card attached to this ad or send the coupon below for your FREE copy and add the names of two of your friends who are interested in saving money on high quality electronic things. And, remember too, we'll also send you FREE a copy of every additional money-saving sale book we issue during the next 12 months! Shop and Save all year at Radio Shack.

NEW! FREE
144 Pages
Spring and Summer
1962 Catalog

 10-Transistor Portable Radio \$29.95	 "Electrostat-2" 2-way Speaker System \$54.95
 \$99.95 value 2-speed Tape Recorder \$54.95	 Realistic Stereo Amplifier Kit \$10.95
 New Realistic Tube Checker Kit \$15.95	 Electronic Thermometer Kit \$19.95

Here are just a few of the electronic values you'll find in Radio Shack's new Catalog! It has everything—Stereo, Hi-Fi Tape Recorders, Tapes, Records, Ham Gear, Test Equipment, Electronic Parts and Accessories and, of course, fine quality Kits of all types to help you save more money and gain more satisfaction from your hobby.

RADIO SHACK CORP.
730 Commonwealth Ave., Boston 17, Mass.

RADIO SHACK Corp. Dept. 62E8C
730 Commonwealth Ave., Boston 17, Mass.
Without obligation send me FREE AND POSTPAID, your NEW
Electronics Catalog plus every new issue for 1 full year.

Your Name _____

Address _____

City _____

State _____

FILL IN NAMES OF 2 INTERESTED FRIENDS

62E8D

Name of a Friend _____

Address _____

City _____

State _____

62E8E

Name of a Friend _____

Address _____

City _____

State _____

BEST BUYS IN STEREO AND MONO HI-FI

New Transistorized Stereo/Mono 4-Track Tape Deck RP100 Semikit (electronics in kit form) Kit \$299.95 Wired \$399.95



New FM-AM Stereo Tuner ST96 Kit \$89.95 Wired \$129.95 Incl. FET

New 70-Watt Integrated Stereo Amplifier ST70 Kit \$94.95 Wired \$149.95



New 40-Watt Integrated Stereo Amplifier ST40 Kit \$79.95 Wired \$129.95



28W Integrated Stereo Amplifier HF81 Kit \$69.95 Wired \$109.95

FM Tuner HFT90 Kit \$39.95 Wired \$65.95 Incl. FET Metal Cover \$3.95



AM Tuner HFT94 Incl. FET Kit \$39.95 Wired \$65.95



Stereo Preamp HF85 Kit \$39.95 Wired \$64.95

Stereo Power Amplifiers



	Kit	Wired
100W HF89:	\$99.50	\$139.50
70W HF87:	\$74.95	\$114.95
28W HF86:	\$43.95	\$74.95



New FM-Multiplex Autodaptor MX99 Kit \$39.95 Wired \$64.95 Cover Optional, \$2.75 (Patents Pending)



Bookshelf Speaker System HFS1 Kit \$39.95 Wired \$47.95

BEST BUYS IN CITIZENS TRANSCEIVERS, HAM GEAR, RADIOS

Citizens Band Transceivers from Kit \$59.95 Wired \$89.95



New 60W CW Transmitter #723 Kit \$49.95 Wired \$79.95

NEW Walkie-Talkie Citizens Band Transceiver #740 Kit \$54.95 Wired \$79.95. Complete with rechargeable battery & charger.



BEST BUYS IN TEST EQUIPMENT

New Metered Variable AC Auto-Transformer Bench Supplies Model 1073 (3 amps) Kit \$35.95 Wired \$47.95 Model 1078 (7 1/2 amps) Kit \$42.95 Wired \$54.95



Peak-To-Peak VTVM #232 & Uni-Probe® Pat. #2,790,051 Kit \$29.95 Wired \$49.95



VTVM #221 Kit \$25.95 Wired \$39.95

DC-5 MC 5" Scope #460 Kit \$79.95 Wired \$129.50



5" Push-Pull Scope #425 Kit \$44.95 Wired \$79.95

Tube Tester #625 Kit \$34.95 Wired \$49.95



RF Signal Generator #324 Kit \$26.95 Wired \$39.95



1000 Ohms/Volt V-O-M #536 Kit \$12.90 Wired \$16.90




6- & 12V Battery Eliminator & Charger #1050 Kit \$29.95 Wired \$38.95 Extra-filtered for transistor equip. #1060 Kit \$38.95 Wired \$47.95



NEW AC Volt-Watt Meter #260 Kit \$49.95 Wired \$79.95



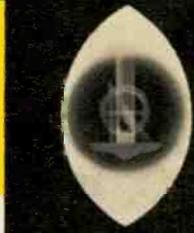
Multi-Signal Tracer #145A Kit \$19.95 Wired \$28.95



EICO

EXCELLENCE IN CREATIVE ELECTRONICS

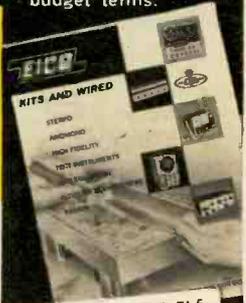Over 2 MILLION EICO instruments in use throughout the world. Compare, take them home — right "off the shelf" — from 1500 neighborhood dealers, most of whom offer budget terms.



EICO, 3300 N. Blvd., L.I.C. 1, N.Y. EI-5
 Send free Catalog describing over 80 top-quality products, free Stereo Hi-Fi Guide, free Short Course for Novice License, name of nearest EICO dealer. Send new 36-page GUIDEBOOK TO HI-FI for which I enclose 25¢ for postage & handling.

Name.....
 Address.....
 City..... Zone..... State.....
 Add 5% in the West

how to get the most out of CITIZENS BAND RADIO

THE TITLE above sums up the theme of this Special Issue of EI. By devoting more than 50 pages to Citizens Band radio, including ten exciting construction projects, we have attempted to show you how you can get maximum usefulness out of CB, and at the same time enjoy yourself. Gathered together here are articles prepared by the foremost writers on all phases of CB.

Len Buckwalter, 1W5733, EI's Contributing Editor on CB, gives you a basic guide for buying a transceiver and tells you how to get maximum power from your transmitter. Herb Friedman, 2W6045,


a prolific EI contributor, advises you on choosing your antenna and contributes a valuable article on CB servicing. Tom Kneitel, 12Q1747, nationally noted for his CB activities, gives you a blueprint for setting up your first station. Charles Tepfer, 2W4223, prominent electronics writer and editor, tells you how to build four CB antennas. And Fred Maynard, 11Q0846, veteran electronic applications engineer, designed and built EI's Tiny-Talkie.

Other authors tell you how to form a CB club and how to make it worthwhile, explain operations on the License-Free Band, give you how-to instructions for building a variety of accessories and cover other phases of Citizens Band radio.

As you've probably discerned already, this issue covers CB from beginning to end . . . from assessing your needs and buying your equipment to operating and servicing your gear so that the inherently useful Citizens Band is of maximum service to you.

We are proud of our Special Issue on Citizens Band radio and we believe it represents a major contribution to the efficient use of the service. We would remind you that every issue of EI includes top-flight CB

[Continued on page 100]

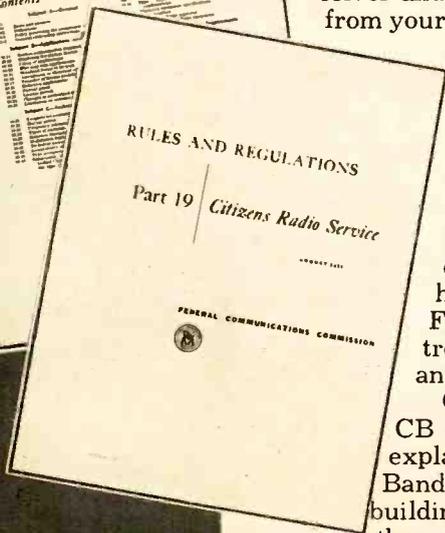



HOW TO BUY A TRANSCEIVER

To get the kind of equipment that best suits your particular needs, you must know what to look for.

By Len Buckwalter, 1W5733




THE CITIZENS BAND marketplace offers more variety than you'd expect to find in an oriental bazaar. From the simplest four-tube for cousin Lem down on the farm to elaborate multi-channel rigs for tough city conditions, there's a transceiver for every application.

Choosing the right unit begins with two questions: Under what conditions will it operate? Which features do you require? The answer to the first is a personal one determined by you. To help answer the second, here are some major factors which account for the differences in equipment.

Let's face it—all popular CB radios except handie-talkies have the same

transmitter power: five watts input to the final stage. Small differences that do exist are meaningless in terms of range.

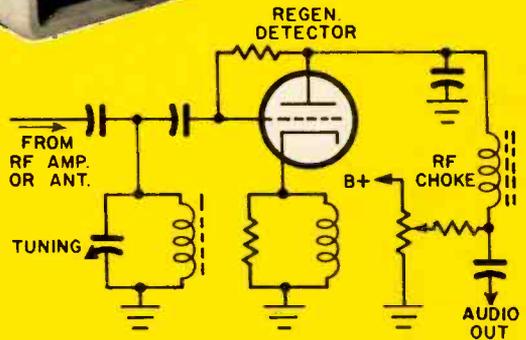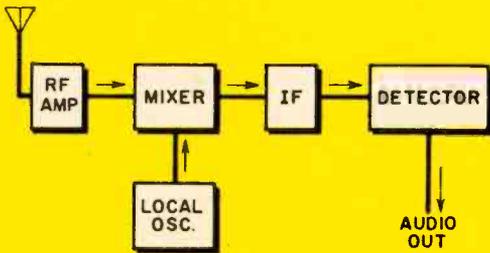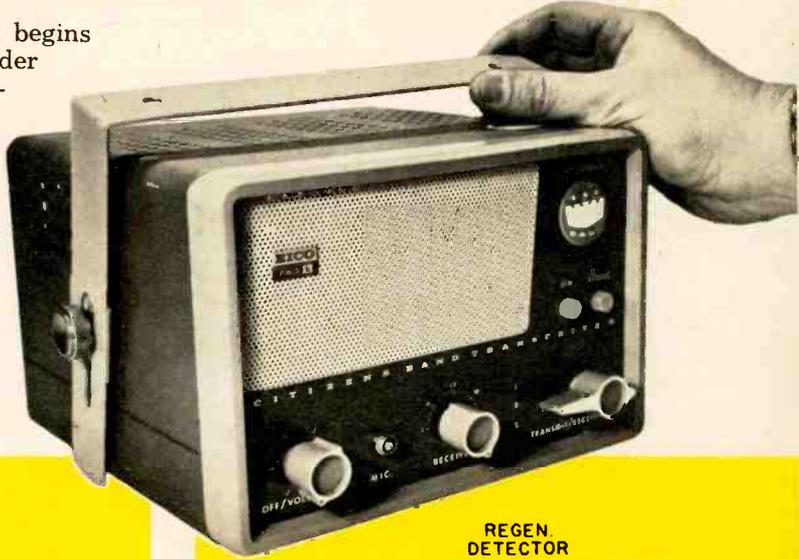In the receiver sections, one must split hairs in discussing *sensitivity* (ability to pull signals out of background



Superheterodyne receiver (left) has local oscillator and mixer; superregenerative circuit (typical schematic at right) is cheaper but less efficient. EICO 762 transceiver above is superhet type, costs \$69.95 as kit.

noise) from one rig to the next, regardless of price.

But in the receiving section we do come to a basic split that perhaps makes for the most important consideration of all. The major difference between CB units occurs in the type of receiver circuitry—superregenerative or superheterodyne. Both are fairly equal, as just mentioned, in terms of sensitivity. But, the superregen takes second place in *selectivity*.

The stronger a station is in a superregen receiver, the more space it takes up on the dial. Twist the tuning knob over several channels and you still won't be able to reject this type of interference. Broad receiver response to powerful signals of interfering stations can punch a temporary, though large, hole in your tuning range.

But the superregen has earned a well-deserved niche in CB radio. You can't beat it on a price-vs-performance basis. These sets fall into the attractive around-\$50 range. Especially in sparsely populated areas where CB is not too active, they perform admirably. Remember, too, that a possible method of avoiding an interfering station is simply to wait until it stops transmitting. FCC rules hold that CB stations must limit their transmissions to the shortest practicable duration. And then it's your turn.

The more costly superhet largely overcomes the problem of interference from stations operating on adjacent channels. It has several more tuned stages which sharpen the response, or bandpass. However, don't look to the superhet to cut out interference on your own channel. In spite of high selectivity, all stations on the same channel are admitted equally into the receiver.

Among features which improve the performance of the superhet is its number of stages. Greatest variation is in the intermediate frequency (IF) strip. All channels are converted to an amplifying IF frequency for circuit efficiency, but sets with more than a single IF stage offer improved selectivity.

For ultimate performance, there is the dual-conversion model. Not only does it have several IF stages, but it juggles the received signal in a manner which rejects images. These are stations operating out of the Citizens Band but, under certain conditions, are amplified in the IF strip of the more basic single-conversion receiver. Look for the dual-conversion feature if you wish to get top receiver performance.

When planning your CB layout ask yourself whether you will need to communicate on more than one channel. Multi-channel performance frees you from being tied to a single transmitting frequency. If the basic channel is



Large press-to-talk bar is handy feature of the Allied Knight-Kit C-27 transceiver; kit costs \$79.95.



Five-channel operation is offered by Lafayette HE-15A, which lists at \$59.50, factory wired.



Superregen tuning knob gives approximate channel markings. Heathkit CB-1 (kit) sells for \$42.95.

blocked by other signals, you can flip to one or more alternates. Many sets permit a choice of five transmitting channels and there are now rigs on the market that will give you all 23 channels.

At present there is a move to reserve channels for specific communications: marine, distress, Civil Defense, traveling, etc. If your interests cover more than one, get a multi-channel set.

Many business concerns find multi-channel operation boosts efficiency by letting them talk to one group of stations to the exclusion of others, such as trucks on one channel, automobiles on another.

Most receivers are continuously tunable over the 23 CB channels. This is fine for single-channel work but it creates a problem in multi-channel systems. The dial marking on most sets is only approximate. Changing channels quickly can be a hit-or-miss affair. Imagine riding in a mobile unit and trying to find your master station, which might have switched to an alternate channel. Unless the signals are strong, you can't re-tune precisely.

Crystal-controlled superhet receivers provide a neat solution. Instead of a smooth tuning control, a multi-position switch selects the channel with positive snap action. Any chance for error is eliminated, since the crystals in the receiver are highly accurate tuning devices. Crystal control enjoys wide ac-

ceptance in commercial communications equipment, especially when tuning must be done by non-technical people. CB sets which feature this function usually include the continuously tunable dial also. Superregen receivers cannot be crystal-controlled.

Without a noise limiter in a superhet, mobile reception is often obliterated. Auto and boat ignition systems are vigorous generators of noise in the 27-mc Citizens Band. Reducing this interference at the source (spark plugs, distributor, etc.) only attacks the noise produced by *your* vehicle. The noise limiter in a CB unit cuts down electrical interference radiated by other vehicles. Don't look for a noise limiter in the superregen. It's not needed because this type of circuit is self-limiting.

Another source of noise is countered by the squelch control. Communicating via CB is often on a non-schedule basis. Messages are transmitted at unpredictable times. Long standby periods with the receiver volume turned up is a source of distraction and annoyance from atmospheric noise and hiss.

The squelch circuit kills all sound in the speaker until a signal is received. The squelch circuit then is immediately disabled, and it remains off for the duration of the other station's transmission.

These are the key features found in CB units today. There are some others that require no explanation but should be considered. Power supplies are packaged in various combinations of 6, 12 and 117 volts. The shape and mounting style of a CB set can affect its position under a car dashboard. If push-to-talk operation is desirable, be sure your set has this feature.

Transceiver kits are now pretty much bug-free, and they offer a way to acquire CB equipment at a modest cost. All of them come with the frequency-determining section in pre-built form. All you have to do is add the other components as supplied by the manufacturer. Most construction manuals make this easy.

Choosing CB equipment with features to cover the application you have in mind can result in an economical purchase that gives you an efficient system of communications.

CB Hit Parade

Pictured below and on the preceding three pages are the current best sellers among transceivers, and others with features that are much discussed by CBers.



RCA Mark VII Radio-Phone has continuously-tunable super-het receiver, crystal-controlled transmitting and receiving on any 4 channels, push-to-talk mike, built-in squelch. Mounting bracket. \$189.50. RCA, Harrison, N. J.



Hallicrafters CB-3 Littlefone has 8 crystal-controlled transmit-receive channels, output indicator on front panel, push-to-talk, squelch, noise limiter. Operates on 117 VAC, 12 VDC. \$149.50. Hallicrafters Co., Chicago 24, Ill.




Poly-Comm N has a Nuvistor RF stage, dual-conversion IF (455 kc) for increased selectivity; 4 crystal-controlled transmit-receive channels, automatic gain control, adjustable squelch. \$189.50. Polytronics Lab, Clifton, N. J.



Realistic TRC-27A has provision for 3 crystal-controlled transmit-receive channels, push-to-talk with dynamic mike, pi-network output, adjustable squelch and automatic noise limiter. \$89.95. Radio Shack, Boston 17, Mass.



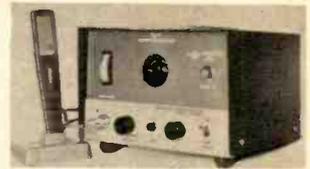Cadre 500 is an all-transistor set with 15 transistors and 7 diodes; 5 crystal-controlled transmit-receive channels, squelch control on front panel, automatic noise limiter. Weight is 6 lbs. \$199.95. Cadre Industries, Endicott, N. Y.



Browning 23/S-Nine transmitter offers 23-channel operation, built-in SWR indicator, push-to-talk, speech clipper. Price is \$144 with one crystal, \$189 with 23 crystals. Matching receiver is model R-2700. Browning Labs, Laconia, N. H.



Kaar TR327 features 4 crystal-controlled channels, has an antenna loading control on front panel and an S-meter indicating level of received signal. \$189. Another version has broadcast band. Kaar Engineering, Palo Alto, Calif.



Gonset G-15 Communicator is a new model with dual-conversion receiver, 4 crystal-controlled transmit-receive channels, an adjustable squelch, push-to-talk mike and an S-meter on the front panel. \$199.50. Gonset, Burbank, Calif.



Courier I has a triple-conversion receiver with 262-kc final IF stage for high selectivity, 4 fix-tuned receiving channels, 12 transmitting channels, Nuvistor converter, squelch and noise limiter. \$189.50. E.C.I., Mount Vernon, N. Y.

Continued on next page

CB Hit Parade

Continued from preceding page



The Viking Messenger features 4 crystal-controlled transmit-receive channels, squelch control on the front panel, noise limiter, push-to-talk. Set measures 5 $\frac{1}{8}$ x 7 x 11 $\frac{3}{8}$ inches deep. \$144.95. E. F. Johnson Co., Waseca, Minn.



Executive Model 100 has dual-conversion receiver (455-kc IF), 12 transmit channels, 2 crystal-controlled receive channels, crystal filter to cut interference and adjustable squelch. \$199.50. Intl. Crystal, Oklahoma City, Okla.



A new type of boom microphone for mobile operation mounts on ceiling of car, swivels down near driver's head. A foot-operated push-to-talk assembly similar to dimmer mounts on floor. AC Spark Plug, Milwaukee, Wis.



CB-4 Littlefone is a new 100-mw handi-talkie with 7 transistors and a diode. It weighs in at 1 $\frac{1}{2}$ lbs., has 38-in. telescoping antenna. List price, \$89.95. Hallcrafters, Chicago 24, Ill.




Model 520 antenna tester is an in-line instrument (it may be left connected in the transmission line) that gives you an SWR figure, your actual RF output and your reflected power. Price is \$42.95. Seco Electronics, Minneapolis, Minn.




The Olson RA-442 transceiver has 5 crystal-controlled transmit channels, superhet receiver, built-in S-meter and output power indicator, front-panel squelch control and a noise limiter. \$89.50. Olson Radio, Akron 8, Ohio.



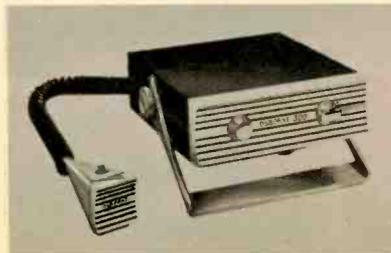
CB loading coil to make shortened mobile whips perform like resonant quarter-wave antennas is encapsulated in epoxy. It fits standard whip threads. Two models, for whips of 92, 96 in. \$5. Creative Products, Cincinnati 36, Ohio.



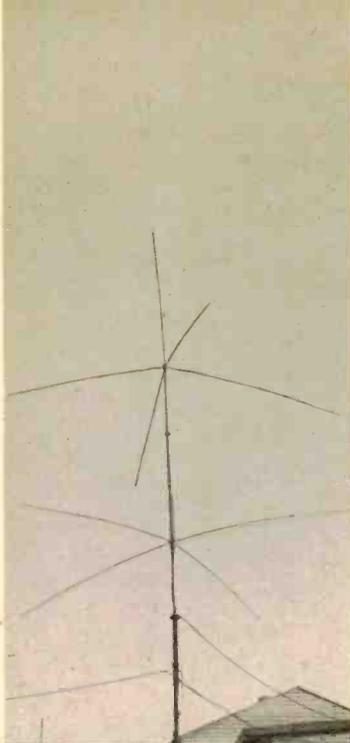All-transistor Osborne 300 transceiver has 9 transistors, 4 crystal-controlled transmit-receive channels, noise limiter, mounting bracket. It measures 1 $\frac{1}{8}$ x 6 x 7 inches and weighs 3 $\frac{3}{4}$ lbs. \$149.50. Osborne Electronics, Hawthorne, Calif.



CHOOSE THE RIGHT ANTENNA

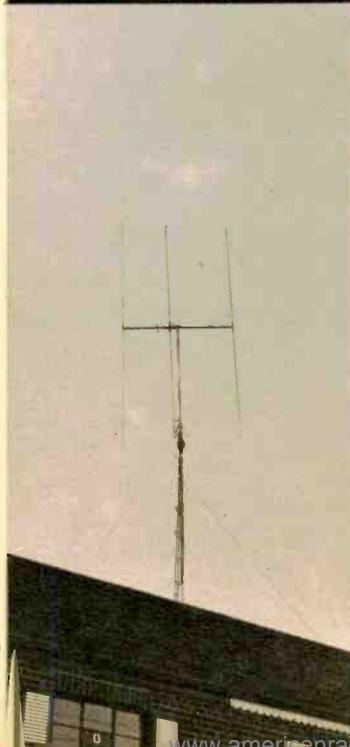

By Herb Friedman, 2W6045

AN IMPORTANT fact that many Citizens Band licensees realize only vaguely is that the effectiveness of their rigs is determined mainly by the antenna. The best receiver cannot reject co-channel interference, nor can a hot transmitter be heard if the signal has difficulty clearing the antenna.

But a good antenna *can* reject co-channel interference and *can* make a five-watt rig put out a signal equivalent to 40 or 50 watts. No antenna can do everything for you but it is possible to get one that combines enough desired characteristics to suit your requirements.

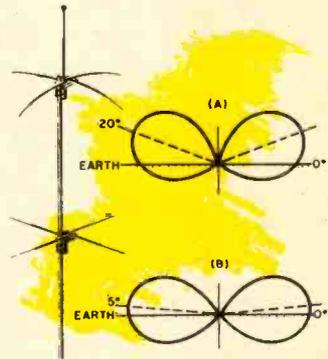


Fig. 1. Vertical radiation pattern of Ground Plane antenna (A); with an isolating skirt (B).

The *Ground Plane* antenna (see Fig. 1) is the least expensive and easiest to mount. It has a quarter-wavelength (about 9 feet) vertical radiator and four radials at its base. These are connected to the coaxial cable shield and through the mounting clamp to the grounded mast.

The GP is non-directional, radiating equally in all directions. Because of re-radiated currents induced in the mast and transmission line, it has a vertical radiation angle (wave angle) of about 20° , meaning the radiated energy is directed upward that much from the earth.

A 20° wave angle is low, but not low enough for optimum CB use. To lower it to a more usable 5° , an isolating skirt is

added. This consists of four additional radials a quarter-wave below the main radials. The skirt reduces the effects of antenna currents in the mast and transmission line. (Note that the GP antenna's radiation patterns are used as the standard reference for all antennas.)

The *Coaxial* antenna (see Fig. 2) costs about twice as much as the GP

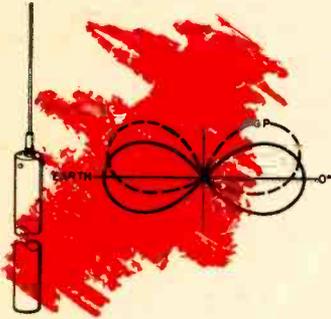


Fig. 2. Vertical radiation pattern of Coaxial antenna with Ground Plane pattern as reference.

but mounts easily and is unobtrusive. It has a quarter-wave radiator mounted on a coaxial skirt (or lower radiator). The transmission line's hot lead connects to the top radiator, the shield to the skirt. The skirt acts as a shield around the transmission line, sharply reducing the effects of antenna currents. A properly designed coax has a vertical radiation angle close to 0° . It is non-directional horizontally. The coax does best in open country and from high base antenna locations.

The *Non-Directional Beam* antenna (see Fig. 3) is merely a vertical radiator

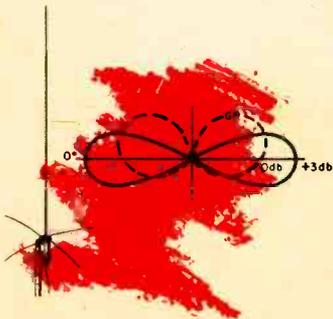


Fig. 3. The vertical radiation pattern of the Non-Directional Beam antenna; note gain of 3 db.

with short radials at the base, but it is different in that the radiator is longer than a quarter-wave. The design may vary a little according to the manufacturer but all accomplish the same thing: they compress the vertical signal, resulting in a signal pushed out at the sides. This pushout gives you a gain of about 3 db (in comparison to the GP's 0 db), making five watts do the work of ten. The N-D beam's obvious advantage is its gain.

The *Directional Beam* antenna (see Fig. 4) concentrates a major portion of

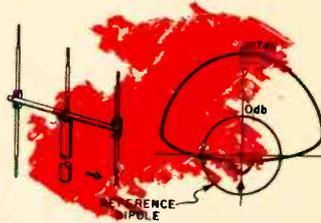


Fig. 4. The horizontal radiation pattern of the Directional Beam shows a forward gain of 7 db.

its radiated energy in one direction. The energy pressed into the forward direction is taken from the rear and side radiation. In a typical high-quality model consisting of a coaxial center element (which is the same as the plain coax antenna) plus reflector and director elements, the forward gain is 7 db, making a five-watt do the work of 25 watts. As a side effect—because energy is removed from all directions except forward—receiving sensitivity to the rear and sides is reduced sharply. By careful adjustment of antenna direction, you can use this characteristic to phase out an interfering signal.

Directional beams normally are vertically or horizontally polarized (in a vertical beam the elements are vertical to the earth). Since there is a loss in signal when working cross-polarized (horizontal antenna vs vertical antenna), it is best to use the same polarization in both base and mobile units. In practice, a horizontal antenna is less susceptible to noise.

It is not recommended that horizontal antennas be turned on end to form verticals. When you do this your transmis-

sion line runs too close and parallel to the beam's radiating element and you have trouble because of re-radiated antenna currents induced in the transmission line.

Directional beams come in various sizes from three elements up, the bigger ones offering more gain and a narrower signal beam. One typical six-element beam offers a gain of 11 db, making five watts the equivalent of 62. But, of course, you pay for that gain in your purchase price.

A beam that differs from the usual design is the *Cubical Quad* (see Fig. 5), which uses lightweight wire loops instead of the usual tubular elements. A

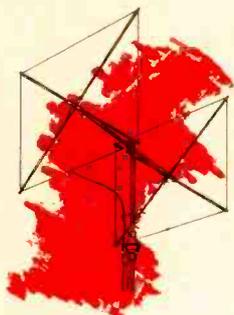


Fig. 5. Cubical Quad antenna uses wire loops for elements. It is polarized in both planes.

quad offers up to 10 db gain, meaning five watts are equivalent to 50. It is claimed that the quad radiates in both polarizations, but there is some disagreement as to whether the claim is valid. We are inclined to believe it is. There simply are not enough data available to give quad radiation patterns.

It is often said that choosing a *Mobile* antenna is as critical as picking out a base job. This is not necessarily true but you do have additional factors to consider: loss of trade-in value on your car due to holes, the use of a short antenna if you pass low overhangs frequently and inconspicuousness.

Mobile whips range from the full-length (108 inches) quarter-wave through short, loaded models to miniatures for top or cowl mounting. Don't be confused by the many models available. Differences are more a matter of mounting convenience than electrical

efficiency. Just remember: *the longer the whip, the more efficient it is.*

The best antenna and the best mounting spot would be a 108-inch whip bolted in the center of your roof. Unfortunately, this is impractical unless you live in the desert. Next best for all-around performance is a whip on the rear bumper. It is possible to improve the performance of this standard rig by lengthening the whip, raising its area of high current and high radiation (see

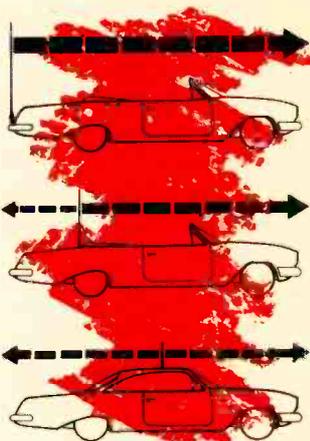


Fig. 6. Relative strength of radiation to the front and rear as mobile whip moves to car top.

MORE FROM YOUR MOBILE WHIP, September '61 EI).

A car's body has a great effect on mobile signals. The area of maximum radiation is toward the car's longest physical length from the antenna. Fig. 6 shows how the maximum radiation pattern is toward the front with a bumper-mounted whip. When the antenna is moved to the rear deck there is some radiation to the rear but more to the front. A roof-top mount gives equal radiation in each direction.

Although those ring and slot and cone and hoop antennas are interesting, especially from the standpoint of experimentation, they are unproved as yet. On the other hand, the characteristics of whips are well known and when you install one you can be pretty sure about what it will (and won't) do. It's still the best bet for day-to-day use. ●



YOUR FIRST STATION

An expert's advice
for the beginning CBer.

By Tom Kneitel, 12Q1747



AFTER you have decided to go into Citizens Band radio and your transceiver is sitting in its carton on the kitchen table, you begin wondering where to locate your shack and how to arrange it.

The operating location should—first of all—be a convenient place. If you spend most of your time downstairs, for instance, don't haul your equipment to the second floor so you have to charge up the stairs every time you get a call on the air. A desk or table is the best place to put your rig—not too near the edge, where it can get knocked off. The immediate area around it should be open so the set can receive ventilation through the air ducts in its cabinet.

Never stick your equipment on any makeshift location, and stay away from such hot spots as radiator covers. High temperatures can wreck a transceiver in short order.

The drawing at the end of this article shows a neat shack arrangement that makes for efficient communications. It represents a kind of composite of several well-arranged CB shacks I have seen.

The clock is a must item for your log entries and to keep the length of your messages within legal limits. Locating your telephone nearby is a big convenience (if you can swing it with your wife). The shelf above the desk holds the many books you are going to want and need. In the way of test equipment, you will find a signal strength meter and a dummy load antenna the handiest. Perhaps you'll want to add an SWR bridge, EI's CB Signal Generator and other gear later. Spare tubes should be a requirement in every shack. Minimum tools include screwdrivers, pliers, wire cutters and strippers, soldering gun or iron and a small penlite.

Once you have your shack set up, you're ready to tackle the antenna problem. Another article in this issue deals in detail with antenna selection. Probably best (and lowest priced) for general communications are the ground plane and coaxial types. In mounting, keep your antenna clear of nearby buildings, trees, TV antennas and phone and power lines. These absorb and re-

flect your signal and can add noise.

Final link in the transceiver-antenna chain is the coaxial lead-in. Various cables are available but the one you select should be of the same impedance as the antenna. Two widely used types are RG-58A/U, which costs about 5½ cents a foot, is rated at 50 ohms impedance, is thin and flexible and easily handled; and RG-8/U, which costs about 13 cents and is rated at 52 ohms. The former is good for short lead-ins, the latter for runs upwards of 100 feet.

The lead-in should be as short as possible, the coax must not be kinked or spliced, and you should use coax connectors at both ends.

After you have been on the air a while, you can expect to have some trouble with component failure. Tubes are the most likely to go first. For that reason, it's a good idea to have a supply of duplicates ready for plugging in at the first sign of difficulty.

In this little operation, you simply turn the set on and take a look at the tubes. If any have an unnaturally bright glow or none at all, you've probably found the culprit. If all tubes appear normal, tap each one lightly with a pencil eraser. Then try replacing the tubes one at a time until the set operates (tubes that read good even on a tube tester can be fouling up the works).

If tube-changing doesn't help, you

can examine the mike, lead-in, power cord and other obvious points where there might be failure. After that, if you're still off the air, you need to go deeper (see CB SERVICING MADE EASY in this issue).

Your transmitting crystals should be checked for frequency drift once a year. This must be done by a commercial radiotelephone or radiotelegraph licensee. You can find one in the classified phone book under the heading, Radiotelephone Equipment Service.

In the way of general maintenance, you should keep your shack as clean as possible. About every three months take the cabinet off the transceiver and either blow or vacuum-clean the dust out of it. Your antenna should be taken apart once a year or so for a thorough cleaning. Use an all-purpose liquid cleanser to get the grime off the insulators, connectors and radials. If your antenna is mounted on a metal mast, it should be coated with corrosion-resistant paint. A wooden mast can be weatherproofed with spar varnish.

These hints for setting up and maintaining your CB equipment can make operations easier for you. But whether the Citizens Band gives you what you expect from it is determined entirely by your efficient use of the service. In that category, you are pretty much on your own.

A bird's-eye view of an efficient CB shack shows transceiver on desk at left, clock in center and phone and pad at the right. Spare tubes, test equipment and books are on shelf. Tool rack is mounted above the shelf.





Ottawa 5 Watters Radio Club -
By-Laws and Constitution

Preamble

We the members of the Citizen Band Radio Club of Ottawa, Illinois feel that it is our natural right and moral duty for members to associate with one another in meetings so that they may discuss and democratically handle their problems and to abide by the FCC rules (Section 19) and club rules therein.

Oath

Do you _____ swear of your own free will and accord in the presence of these members to agree to abide

how to form a CB CLUB

Article III

To establish and maintain among the members a spirit of loyalty and cooperation that will guarantee the rights of others. To inspire friendship among the members and to have each of them realize that this cause in which they have enlisted their service is worthy of thought and effort and only by full cooperation and support by all members can the purpose of the club be realized.

Article IV

The membership of this club shall be unlimited and open to all race, creed and religion.

By-Laws

Article I

Membership of this club shall be confined to those who are interested in Citizen Band Communications.

Article II

No person who is a member of any subversive organization or who advocates the overthrow of the U. S. Government shall become a member of this organization.

Article III

Initiation fee shall be \$.50 and shall be paid on the day of registration.

By H. B. Morris

IF YOU HOLD a Citizens Band license or are interested in getting one you almost certainly have heard about CB clubs. Scattered across the country are more than 300 Citizens Band groups with anywhere from a dozen to more than 200 members each. Some of them are active, vital organizations with scores of activities. Others were miscreants to begin with and now totter into oblivion. Seldom has a field of interest fostered so many clubs so fast as has CB, and seldom have so many faded so soon.

Yet there are worthy goals for CB clubs, and if they are properly organized and run they should be excellent organizations that hold the interest of their members and help improve the CB



Banner guides CBers to big Eyeball QSO held at Norwalk, Conn. Clubs usually direct these fetes.

service for all the licensees.

Are you interested in joining a CB club? If you are, the chances are good that there is one in your area, especially if you live in a large community. (See our offer of a free list of CB clubs on the third page of this article.) However, if there isn't a club within a reasonable distance, you and a few fellow CBers can form your own. And you'll have the blessings of the Federal Communications Commission, which favors formation of clubs interested in helping police the Citizens Band. They would rather see CBers keep their own house clean than issue a bunch of restrictive new rulings.

Actually, starting a club is almost *too* easy. This is one reason why so many fizzle and die. Remember that the urge to share your interest in CB with others is enough to bring a group together, but it will never hold them. Over the long haul you'll need better reasons.

The goals of any club should include promoting and improving the CB service, enlightening members on FCC regulations, setting up self-policing on the band and extending technical assistance to those who need it. Clubs also can set aside channels for specific purposes (calling, boats, travel, etc.) and coordinate emergency communications.

Any CB club also must have some

sort of social activities that include wives and girl friends. Dances, picnics and other outings are popular. But a CB club organized for *purely* social (or hobby) purposes is doomed to failure.

"Eyeball QSO's" and other special annual or periodic events are enjoyable and keep interest high. Specific ways to make a CB club *worthwhile* are discussed in another article in this issue.

One of the ways a CB club benefits both members and the service lies in the fact that a unified voice carries more weight with local and federal authorities than do individual voices. Members get their collective viewpoints heard and, on the other side, officials learn the desires of CBers (and good ones *do* want to know).

If your club is to be successful it must be run on a formal basis. Let's say that the basic idea is first discussed by three or four CBers. From this informal group should emerge plans for the first general meeting at a place convenient for all. Don't overlook any means of publicizing the idea to assure a good showing. On-the-air talk is bound to spread the word rapidly, but also post notices in places CBers frequent: electronic parts stores, equipment retail houses, boat marinas, etc. Send typed announcements (releases) to local papers and radio stations.



CB manufacturers often display at (and help pay for) big club events. Browning booth is shown.



Guaranteed to be a popular club activity is a Swap Shop for selling and trading used CB gear.

Make it clear that the first meeting will include election of *temporary* officers. This dispels any feeling that the club will be controlled by a self-appointed few. Best way to conduct the first (and future) meetings is according to the time-tested Robert's Rules of Order (get a copy at a book store or library).

Call the meeting to order on time and after a brief explanation of the purpose of the assembly, ask for nominations for a temporary chairman (who is just that—temporary). He gets things rolling by selecting a temporary secretary to record proceedings and then appoints a committee to work out the first draft of a club constitution and bylaws.

During the first meeting there are many topics for consideration: a club name, a permanent meeting place, dues, suggestions for the constitution and discussion about what the club's major activities will be. Every person should have an opportunity to air his views.

Much detail work will be done by committees in such areas as monitoring, Civil Defense, technical assistance and publicity.

Too much emphasis cannot be placed on working out the constitution. It must serve as a solid foundation, determining how the club is structured and how permanent officers are elected, among other things. One way of getting ideas for a

**FREE LIST OF CB CLUBS
IS AVAILABLE FROM EI**

Before trying to form a new CB club, make sure there isn't an existing one in your area that you haven't heard about. For a free list of all major CB clubs in the country, send a stamped, self-addressed envelope to EI, Dept. C, 67 West 44th St., New York 36, N. Y.

constitution is to look over what other clubs are using. Most organizations are happy to extend a helping hand.

All this parliamentary procedure might sound like an unnecessary chore, but without it your meetings can deteriorate into a mass of petty arguments and squabbles.

At your second meeting you should elect permanent officers, vote on a club name, etc., and later will come plans for a monitoring setup, a newsletter and other activities. But your first concern is that first meeting. It can be the key to success or failure for your new club.

Finally, look beyond the basic business of the club for ways to keep interest at a high level. Try to have a feature event at every meeting—talks by club members, a lecture by an outside authority, movies, a swap shop or an equipment auction.

Good luck! 



Tri-State Radio Club set up radio control point near entrance to jamboree at Fort Mountain, Ga.



A Norwalk (Conn.) CB Association QSO attracted licensees from New York and all of New England.

Prince Prais Auxiliary Ur

CBers RESPOND IN EMERGENCY

12:30 a.m., December 31, 1960, an emer
in from 18A6238, Vern Peeler, on ch
traveling on the

Motorist Helps Radio

CB AIDS WVCG

A tightly knit and
Police Corps won
ense of

C-Bers Aid Manhunt For Kidnapp

Members of the
Radio Association,
over 25 were comm
for their action a
in the capture of
Erie area man wh
9 year old youngst
ened to kill the b
Shortly after 1
night the Penn
Police contacted

make your club WORTHWHILE



Your CB group can be a vital part of community life
if it takes up outside activities in the right way.

By Edwin Frederick, 2W4580

A CITIZENS BAND club is likely to be one of two types: a social and hobby organization dedicated to putting away a few cups of coffee, chewing the fat and having a couple of laughs with the gang, or it may be a useful club that plays a vital part in community life. In the long run, you'll find that those that play together *don't* stay together. It is the useful clubs that remain active and successful.

Another article in this issue discusses the formation of a CB club and the planning of an all-around schedule of intra-club activities. We are concerned here with ideas for making a club *worthwhile* in its relations with other organizations and the community.

The CBer of today is more likely to be interested in public service than was his counterpart of two or three years ago. In those days there weren't many CBers and it was enough just to sit around and talk about this marvelous new band. But now the horizons have widened, CBers are numerous and their equipment has improved to where they can be of use to their communities.

As a starter, your club should decide which fields of public service attract its members—patrolling highways during bad weather, assisting police in handling crowds, working with Civil Defense, etc. The only limiting factor is the amount of work members are willing to contribute.

The key leaders in any kind of public service are two officers who normally are appointed rather than elected. One usually bears a title like emergency coordinator, CD liaison officer, rescue director or public safety coordinator. The other is the public information director. Let's consider the first man:

It is the emergency coordinator's duty to keep in touch with local authorities regarding their needs and his organization's ability to meet those needs. He must keep a dossier on each member, including name, address, business and home phones, call sign, type of equipment and occupation. He must know when members are out of town and not subject to call, and he must know the special skills of his members—locksmiths, auto me-

C-B Travelers To The Resc

Earl G. Harsdorf, Pre
of the Ramsey County Five
ers Club of St. Paul, Minn
ropped us a line on hov
-B radio came in handy d
s trip to Chicago recently

While traveling along the r
came on an accident on hi
12 near Hudson, Wiscons
as a bad accident involv
semi-trailers and a lar
farm tractor. There were
badly injured persons. Ear
he was able to contac
49, Jerry Bovee, of St
and he in turn contacted
Highway Patrol by pho
balance wa

he '5 Watters'

Club Uses Tiny Radi Equipment

A good n
Monterey C
ing minlatt


Citizens Band Radio Advances Plans

Find Lost B

The C-B Cruiser's
California were



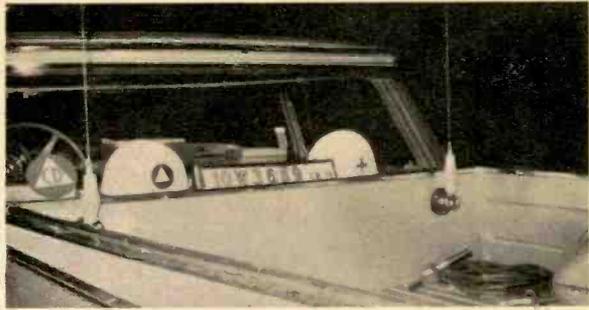Many members of the Lubbock (Tex.) CB Club wear distinctive lettered uniforms on emergency duty.



A glance tells you the owner of this car is a CB licensee who is active in Civil Defense work.

chanics, doctors, plumbers, electricians and so on.

If your organization decides to help motorists during blizzards, tornadoes, floods and other disasters, the emergency coordinator should first talk with the highway patrol or state police, telling them about his organization and its proposed method of operation—the roads they can patrol, the equipment the vehicles can carry (radios, flares, first-aid kits, etc.) and so forth. Your club *never* should take to the highways for mercy missions without clearing the operation with the proper authorities, who may have special requests, such as certain roads to patrol or certain isolated families who should be called on.

Regardless of arrangements, you will want to have your base stations on the air at all times during emergencies. One station must be selected as control station, which will issue *all* orders to mobile units.

If you decide that your cup of tea is holding back crowds at parades, helping with clothing pickups and other functions involving the public, your coordinator should work with the chief of police.

Communications during these tasks will be mainly mobile-to-mobile (hand-talkies are useful). Base stations usually relay messages.

Many misunderstandings exist about the role of CB in Civil Defense. Contrary to what you may hear, CBers are *not* allowed to conduct radio roll-calls in the name of a Civil Defense drill. They must be sworn-in CD members to

begin with, and their CB operations are used only as a supplement to a branch of CD other than communications. Your club representative must find out where the CD people can use workers who just happen to have (as a bonus) two-way radio to aid them.

Club members may turn up in the auxiliary police, the messenger service, the medics, fire patrol or transportation units. Above all, do not demand (or expect) to have CBers placed in the communications division of a Civil Defense setup solely on the basis of their owning CB gear. But if members of your club are involved in CD work, their radio equipment is bound to be put to use in times of emergency.

Typical decals used by CBers on their vehicles. Decals of helpful clubs get police recognition.



Remember that your basic purpose here is not to jockey your CB equipment around. It is to be a Civil Defense worker who aids his community.

The public information director (or press officer) has the job of letting the public know about the club, its activities and its good deeds. He maintains contact with the newspapers and radio stations and should be able to express himself well.

Before each club function he should prepare short press releases (with careful attention to spelling, punctuation and grammar), stating when and where the meeting will be held and its purpose. His own name and phone number must be on the release as the source of further information.

The releases should be received by the news media a day or two before the function (weekly newspapers require more advance time). The press officer should find out whether the news media want him to call them after the function to tell them what happened, or to write a press release on the subject.

During emergency operations, he should phone in any news about the CB club's participation.

Between club functions, the press officer can work up ideas for feature stories about how some members use their equipment in unusual ways,

strange occupations that go with the CB avocation, elaborate base-station layouts and the like. He should first determine whether his media want just ideas for their own writers to work up, or whether they prefer full-length stories.

In other public relations areas, all club members share the responsibility of spreading the good word. Such things as window decals, we-helped-you cards to be given to motorists, lettered jackets and other paraphernalia all help to publicize the club.



Latest innovation in this line is complete uniforms—usually fatigues with insignia and lettering. Though flamboyant, they have a useful purpose. They keep your clothing underneath clean when you're doing the dirtier type of emergency work.

In general terms, you should guard against your club's going stagnant. Its members should be aware of the community's changing needs and be willing to keep pace with those changes. And keep the community aware that the club's members are available to serve them when they are needed. Don't be afraid to toot your own horn. When your club does a good deed, let the whole community know about it.

If your club is truly useful to the community, it will be a group you can be proud of.

We-helped-you cards, handed to motorists who have been assisted, make friends for CB clubs.

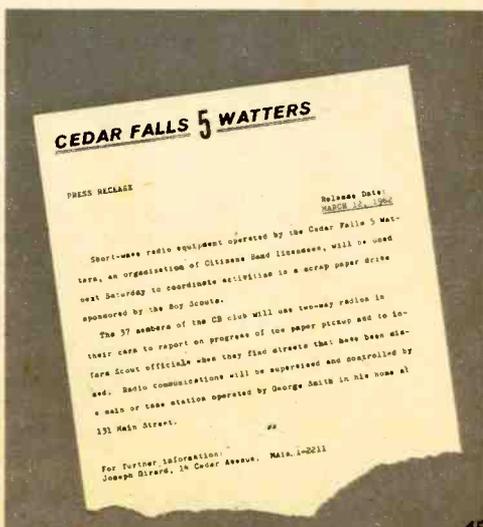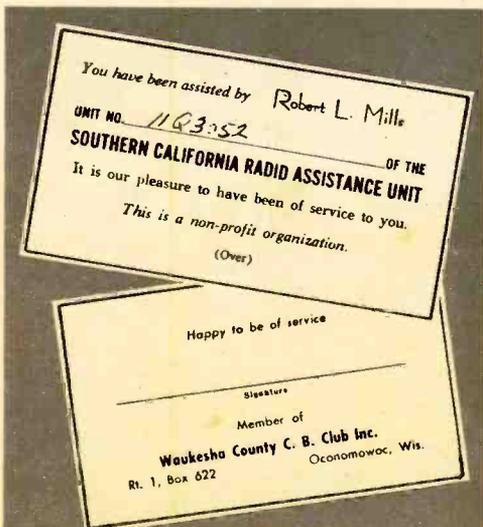A good press release is on letterhead, is short and it tells whom to call for more information.





TINY TALKIE


Smallest build-it-yourself CB transceiver features three transistors in low-cost circuit.

By Fred Maynard, 11Q0846 Motorola Semiconductor Products


FEW COMMUNICATIONS devices in history have gained popularity so quickly as the handi-talkie, the hand-size transceiver born of World War II equipment. For short-range contacts between fishing parties, hunters, antenna installers, power linemen, construction workers and the like, handi-talkies have proved invaluable. And they require no FCC license.

EI now presents the build-it-yourself Tiny-Talkie, a transmitter-receiver that is so small ($3\frac{1}{4} \times 2\frac{1}{8} \times 1\frac{5}{8}$ inches) it fits into the palm of your hand. Like its bigger brother, the Tiny-Talkie can be used in a wide range of applications, fits into a pocket and does not need an FCC ticket (see THE LICENSE-FREE BAND in this issue). You just glue the Certificate of Compliance included in this article on the back of the Tiny-Talkie and you're on the air.

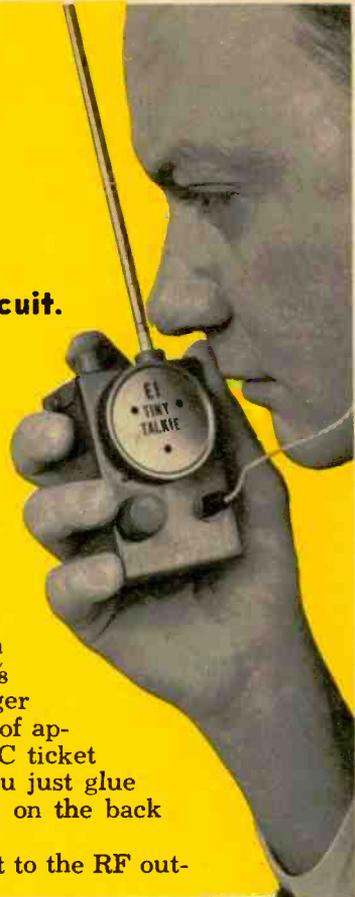The Tiny-Talkie has a 100-milliwatt maximum input to the RF out-



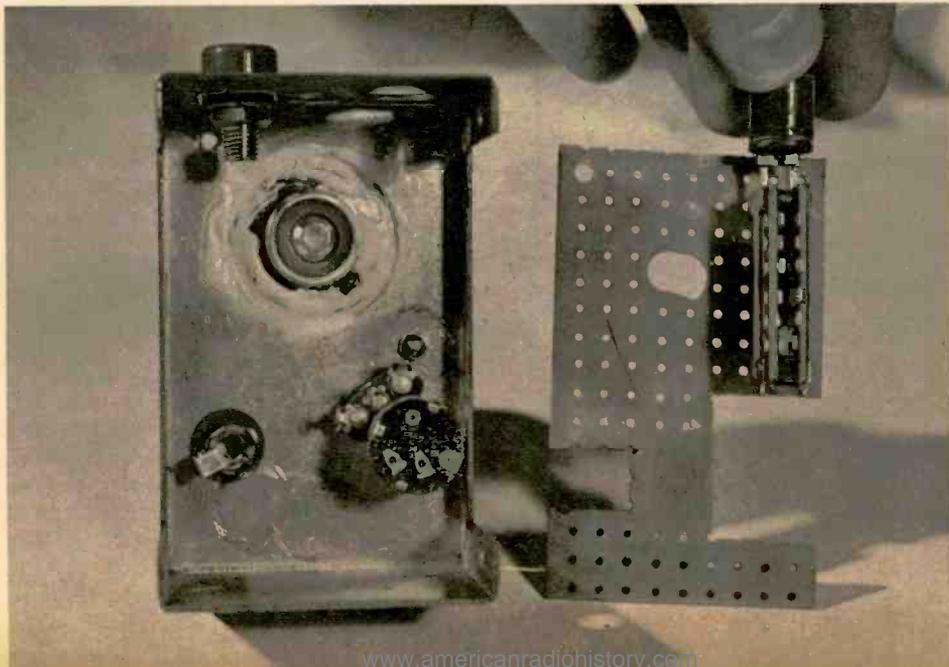Cabinet with parts mounted. Make sure the perforated board fits in cabinet before starting to wire it.



PARTS LIST

Resistors: 1/2-watt, 10% unless otherwise indicated
 R1, R4—100,000 ohms
 R2—10,000 ohms
 R3/S2—15,000-ohm miniature potentiometer with SPST switch
 R5—1,000 ohms
 R6—470,000 ohms
 R7—220 ohms
 R8—2,200 ohms
 Capacitors: Miniature ceramic types unless otherwise indicated
 C1—3.5-12 mmf ceramic trimmer (Centralab 827-B)
 C2, C8—7-35 mmf ceramic trimmer (Centralab 827-D)
 C3, C6, C10—.001 mf C4, C7, C11—.005 mf
 C9—5 mf, 25-volt miniature electrolytic
 L1, L4—15-microhenry subminiature RF choke (J. W. Miller No. 70F155A1 or same series as National below)
 L2, L3—1.2-microhenry choke (J. W. Miller No. 70F126A1) or 1.3 microhenry (National B20407-4)
 Q1, Q2—2N741 transistor Q3—2N1192 transistor
 S1—DPDT spring return miniature toggle or push-button switch (Lafayette 4PDT SW-92 shown)
 Microphone—Carbon 1,500 ohms (Available @ \$1 postpaid from Dart Electronic Devices, 6409 New Utrecht Ave., Brooklyn 19, N. Y. Model 33-PA)
 XTL—CB miniature transmit crystal (channel 2-23) ± .005% tolerance, third overtone
 J1—Banana jack with insulating washers
 J2—Miniature phone jack with insulating washers
 B1—Two 6.5-volt mercury batteries (Eveready E-165 or equiv.)
 Misc.—2,000 to 3,000-ohm magnetic earphone; 38- to 42-inch telescoping antenna; 3 transistor sockets; 3/4" x 2 1/8" x 1 1/8" Minibox (Bud CU-2101-A)

The above parts (less batteries, flea clips and perforated board) are available as a package from Allied Radio, 100 N. Western Ave., Chicago 80, Ill. Stock No. 74M999. Price is \$20.95. Allow postage for 3 lbs.

put (Q1) and can be used for virtually any legal purpose. Its range runs up to about 1,000 feet, depending on conditions.


Using an ingenious three-transistor circuit, the Tiny-Talkie can be constructed at about half the cost of a larger commercial handi-talkie (see special offer in the Parts List).



If desired, you can substitute some standard-size components (for C1, C2, C8, S1, CH1 and CH4) and construct slightly larger units for only \$25 to \$30 a pair. The battery also is a size-determining factor. Nine-volt mercury batteries are the smallest but have limited life. A 12-volt supply improves the range and 15- to 18-volt batteries do even better, although these increase the overall size of the unit.

Construction. Follow the pictorial carefully. As in all high-frequency circuits, it is important that leads be short, direct and well separated.

Using the photos as guides, drill 3/8" holes in the Minibox for jacks J1 and J2. Drill a 1/4" hole for pot R3. With a Greenlee socket punch or equivalent, make a 1 1/2" hole to mount the carbon

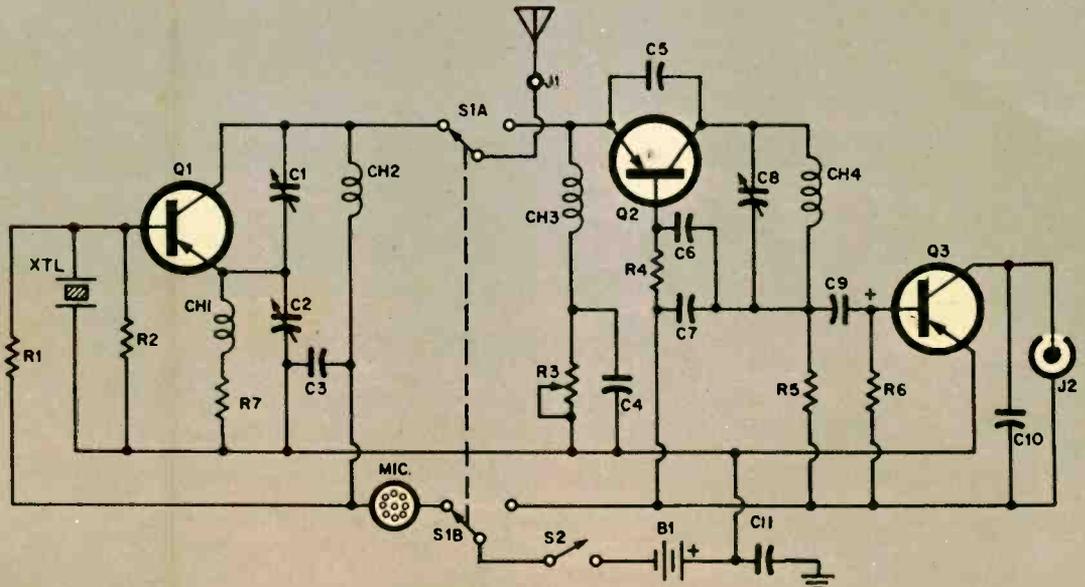Complete schematic of Tiny-Talkie. Transistors Q2 and Q3 make up receiver; Q1 serves transmitter.



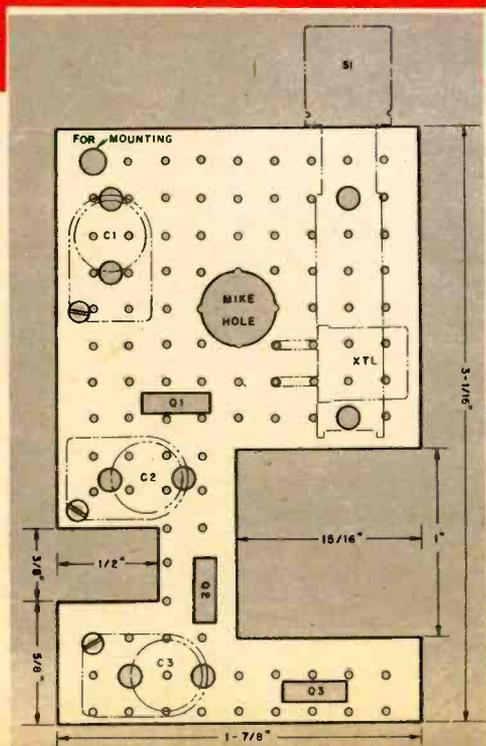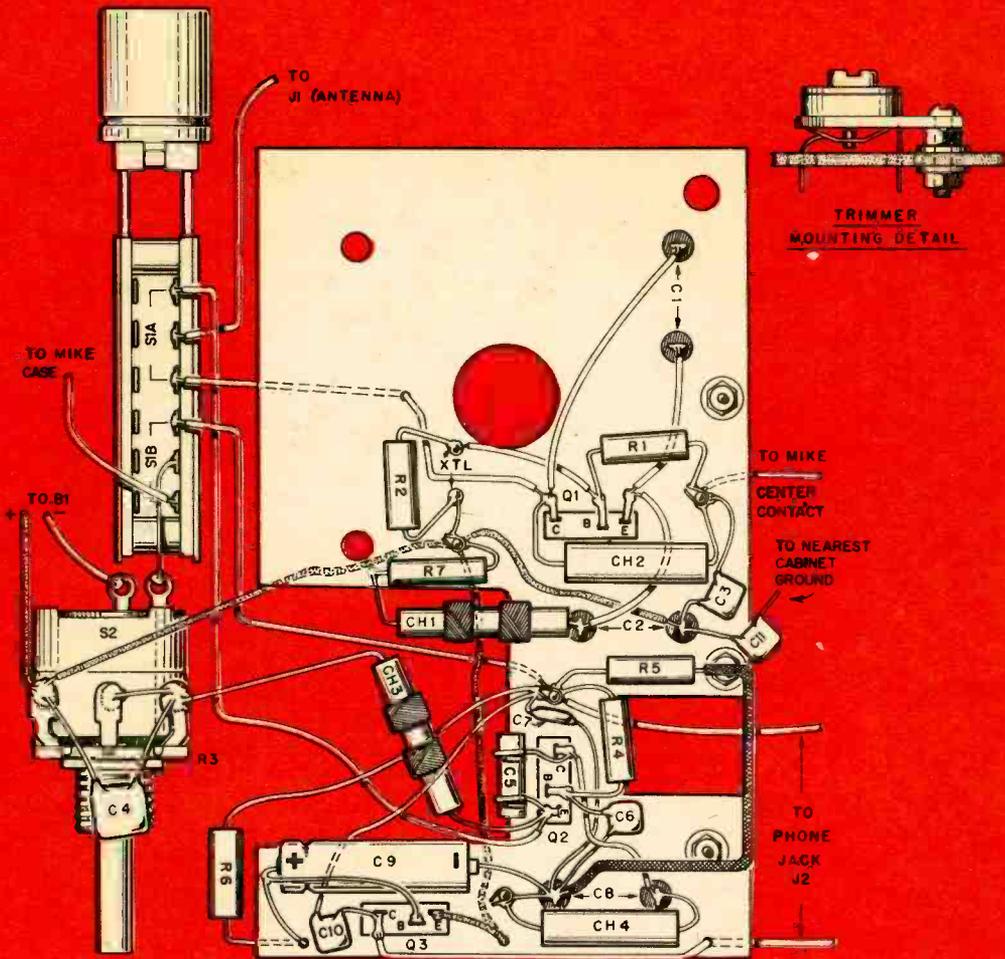

Bottom side of board (above) faces rear of front panel. Switch shown as S1 is one of the several suitable types. Slight parts rearrangement may be necessary if other type switch is used. For clarity, some leads are shown longer than necessary. In practice, keep leads as short as possible.

Location of the major parts are shown on actual size template. Use a hacksaw blade and file to shape the board to the required dimensions.

mike. Epoxy cement is used around the hole's perimeter to hold the microphone in place. It need not be insulated from the case.

Mount pot R3 loosely (it will be tightened later after its lugs are positioned when the perforated board is in place) and mount J1 and J2, using fiber shoulder washers.

The location and size of the hole for S1 will depend on the type switch used. The one shown is Lafayette's SW-92, which requires a $\frac{1}{2}$ " hole.

Cut out a piece of perforated board to the approximate dimensions shown. Make sure the board fits the Minibox, clearing J2, R3 and the microphone's rear contacts. The board should be about $\frac{3}{8}$ " away from the front panel and parallel to it.

Using the photos and template as guides, drill and file $\frac{3}{32}$ " holes for the lugs of trimmer capacitors C1, C2 and C8 and rectangular holes for transistor sockets Q1, Q2 and Q3. If switch SW-92 is used, employ shoulder eyelets or sleeves to mount it about $\frac{1}{4}$ " above the perforated board. This spacing is necessary since the crystal (XTL) is mounted beneath it. After S1 is mounted, determine the location of the hole that must be drilled for its button.

For mounting XTL, use two pin clips removed from a seven- or nine-pin tube socket. Bend the socket pins 90 degrees, crimp the lugs and force them through adjacent holes in the perforated board. The spacing will be correct for a miniature crystal. Do not solder to the crystal pins. Don't mount the crystal yet.


Mount the flea clips in the positions indicated and mount C1, C2 and C8 about $\frac{1}{8}$ " above the board as shown. Drill three holes in the back of the Minibox opposite the screws of trimmers C1, C2 and C8 so they can be adjusted with the cabinet back on.


Using thin insulated wire, such as Alpha No. 407A, proceed with the wiring. Take care not to overheat parts or insulation. Use thin spaghetti or insulation stripped from other wires on the component leads. Keep all parts against the perforated board or you may have trouble getting the board to lie flat in the case.

After the board wiring is completed, run 5-inch leads for connection to R3, J1, J2, the mike and the battery holder. This will allow you to check the circuit's operation before the board is installed and may save trouble later.

Transmitter Adjustments. Plug in

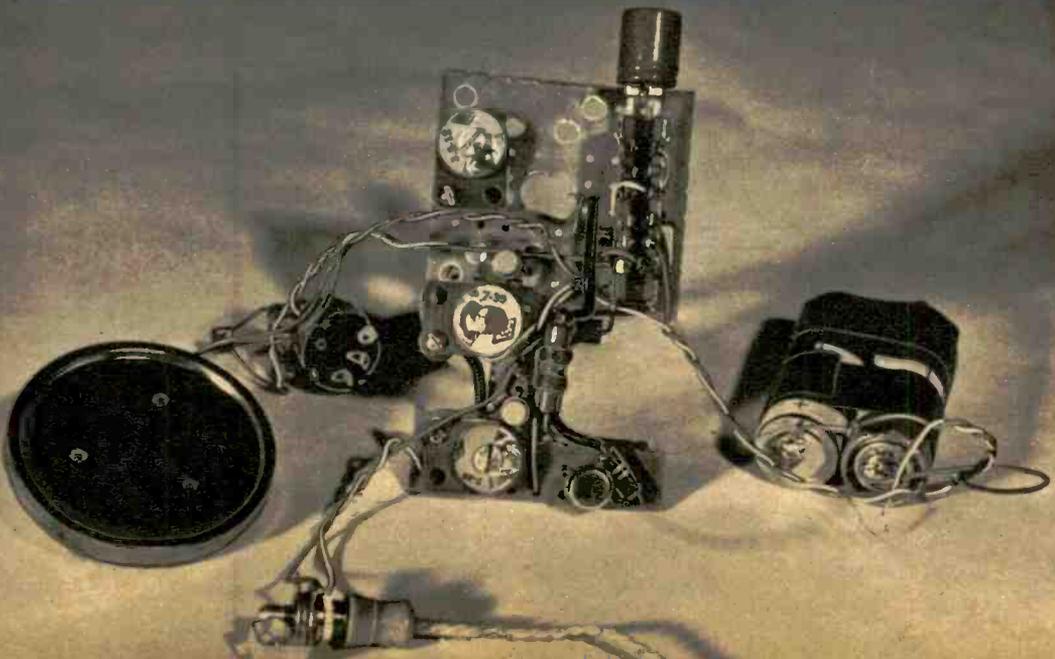Complete unit is laid out for testing before permanent installation in its miniature aluminum cabinet.



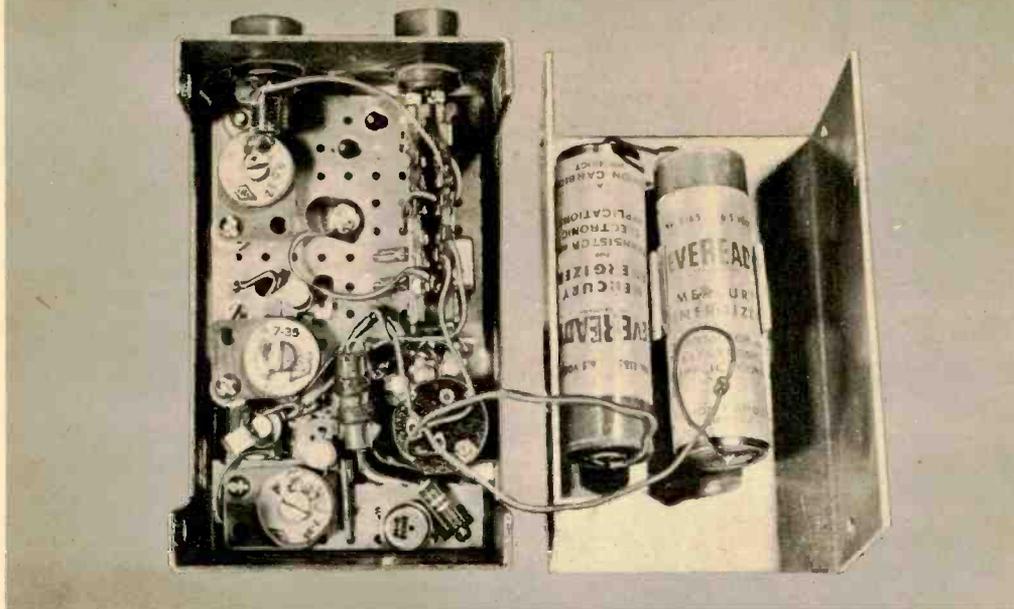

Completed Tiny-Talkie chassis installed in cabinet. Batteries are mounted in clips on cover.

the crystal (any *transmitting* crystal for channels 2-23), transistors and earphone and connect the microphone and R3. When installing battery B1 be sure that its polarity is correct. Attach a three-foot length of wire to the antenna lug on S1 and strap S1 (with electrical tape) in the *talk* position.

You can check the circuit for oscillation by putting a milliammeter in series with a battery lead. A 6-ma reading is about right.

Peak the transmitter output by adjusting C1 and C2 with an alignment tool while monitoring the RF output with a field-strength meter. As an alternative, you can use a #48 pilot lamp as a dummy antenna. Connect the lamp between the antenna and the positive terminal of B1. In subdued light, adjust C1 and C2 for brightest bulb glow.

Receiver check. Release S1. You should hear a sizzling in the earphone at most settings of R3. This is the characteristic noise of a superregenerative receiver and assures you that it is operating. When a signal is received the noise is reduced or disappears.

Final Assembly. Mount the circuit board in the box and secure it with a 3-48 x 1/2" screw and nut through the front panel. A 1/4" to 3/8" spacing sleeve is used between the board and the panel. Disconnect the long leads installed for

testing, cut them to length, and reconnect them. Position R3 and tighten its mounting nut. Repeat the transmitter adjustments before closing the case to compensate for detuning from capacitive and other loading effects of the metal box.

Field testing. The Tiny-Talkies, if used as a pair, must be tuned to each other. The best way is to work outdoors with a friend. Separated 50 to 100 feet, one person should talk into his unit while C8 and R3 on the other unit are adjusted for best reception. When both are tuned you should be able to walk farther apart and still maintain contact. It may be necessary to make further receiver adjustments as distance is increased.

Theory of Operation. The circuit shown in the schematic consists of two sections. To the left of S1 is the transmitter, which has a crystal-controlled oscillator/modulator Q1. The receiver, to the right of S1, includes a stable superregenerative detector (Q2) and audio amplifier (Q3). The antenna and battery are switched from one circuit to the other.

The transmitter utilizes Heising modulation and achieves 30% modulation. This figure tends to lessen the effective power but good modulation

[Continued on page 103]



CB CORNER

By Len Buckwalter
1W5733

citizens band news and comments

A CHAT WITH THE FCC . . . Some of the Federal Communications Commission's views on Citizens Band radio, expressed informally and off-the-cuff, were gathered by this department in a chat with Paul W. Gilligan, Assistant Engineer-in-Charge of the FCC office in Boston. Far from sounding like the fine print of Part 19, Gilligan had some lively comments about CB. They covered everything from a "3,000-mile" license to the practices of some CBers who police the band with a tape recorder.

Gilligan's big point: Many violations on the band are not intentional but stem from the CBER's being unaware of the responsibilities tied to the license. The "3,000-mile" ticket pointed this up. A young chap appeared at the Boston office to file for a new license and triggered off a comedy of errors. It developed that he was operating in the area with a borrowed call. Its prefix was No. 11, which indicates California. Shocked was Gilligan's word to describe the fellow's reaction when told that you can't have a base station 3,000 miles away. Of course, the license borrowing wasn't too well received, either.

When asked why CB radio was needed, the chap replied: "I might have to

take my wife to the hospital and need the radio to receive the message *fast*." The bewildered fellow was not hauled off to the pokey but was filled in quickly on some basic rules of the band. This is an extreme example, but it emphasizes the point about knowing regulations.



FCC engineer Paul W. Gilligan addressing a group of Citizens Band licensees in New England area.

TVI . . . Gilligan also sounded off about CB interference with television (the files in Boston are bulging with TVI complaints). Much of it is produced by second-harmonic output of the CB transceiver, he says. This energy, in the vicinity of 50 mc, shows up as wavy lines on a television screen. In really bad cases, the voice is heard in the TV's speaker. Gilligan had several suggestions: Don't operate with the case

of the transceiver removed. This destroys important shielding that confines some of the harmonic signal. And do a fine-adjustment job on the filter of the unit, following the instructions in the manual. Good grounds also are important, and a filter at the antenna terminals of the TV set may be tried. If you receive a letter from the FCC concerning TVI, answer it! You will be called upon to state what you're doing to correct the condition.

Other observations by Gilligan:

QSL cards for CB are pointless. Why confirm a short-range contact?

Civil Defense activities are fine but must be conducted under the jurisdiction of a local CD director.

Don't take an unreasonable length of time to test on the air. Thirty or 40 seconds should be enough. Use a dummy load when possible.

Help people in distress (stranded motorists, etc.) . . . [Continued on page 102]




HOW TO BUILD

Easy-to-follow
instructions complete
in this issue!

- **Directional Beam**
- **Ground Plane**
- **Coaxial**
- **Cubical Quad**

by Charles Tepfer, 2W4223

CB ANTENNAS

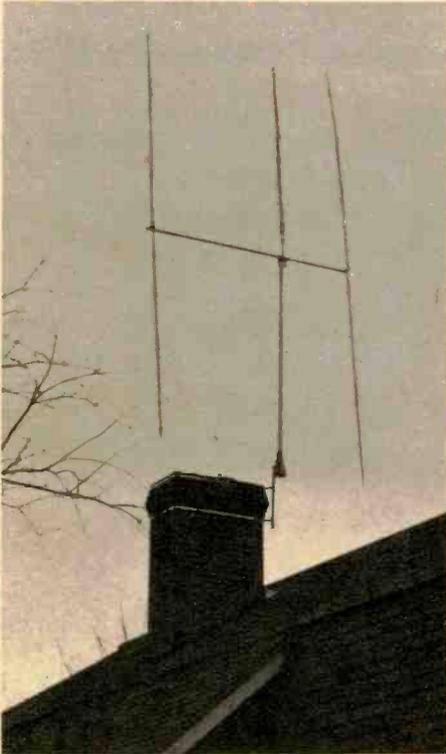

THERE ARE two basic approaches to Citizens Band base station antenna design. One aims at concentrating every watt possible in a narrow radiation pattern. The other is willing to sacrifice some gain in favor of omnidirectionality. But, no matter what your needs are, you can save a pile of dough and multiply your effective radiated power with one of the antennas described below. Once you have the materials, any of the four designs shown will take only a few evenings of work with hack-saw, drill and plane.

Since antennas really are tuned circuits, the size of their elements are relatively critical. EI's antenna designs use no element-shortening (and power-losing) loading coils, which makes them easier to build and more efficient. Strong-but-light stock aluminum tubing and rods are used wherever possible.

DIRECTIONAL BEAM

The most efficient base antenna you can build is a directional beam. There are many types but all are multi-element, with two or more sets of arms in the same plane. One element (the *driven* one) is the active transmitter and receiver. The others are parasitic and shape and direct the radiation pattern of the antenna into a beam. The more elements, the sharper the beam. Like a searchlight, beam antennas have high radiation (and pickup) in front and little to the sides and rear. Relative to the standard half-wave dipole, the gain of the beam is 3 to 5 db for the simpler jobs to 10 db or more for rigs with more than five elements.

El's beam is a full-size, three-element unit. The *driven* element is a nine-foot half-wave coaxial radiator. The other elements are a *director* (16' 10"), shorter than and in front of the driven


element, and a longer (18' 6") *reflector* behind it. The elements are mounted vertically to produce vertically polarized signals, matching the polarization of mobile whips and base station antennas of the ground-plane and other non-directional types (most CB antennas fall in these categories).

The coaxial vertical radiating element is constructed first. The solid rod top portion (see Fig. 1, point A) is 9' of 3/8" Reynolds do-it-yourself aluminum listed by them as Item 3A. Since Item 3A comes in 8' lengths, you must add 12", plus 4" for the part of the rod that projects into the nose plug—a total of 16"—to its length. Make a 4" sleeve of 1/2" thinwall aluminum tubing and slip this over the joint to hold the two sections together. Fasten it to both sections by drilling 3/32" holes through rod and sleeve and inserting 3/4" nails, flattening both ends. For a tight fit, wrap a couple of layers of aluminum foil

Author's directional beam before installation. Size may be judged by comparison with the windows.



Fig. 1. Diagram showing length and spacing of beam's elements. See text and pictorial for details.

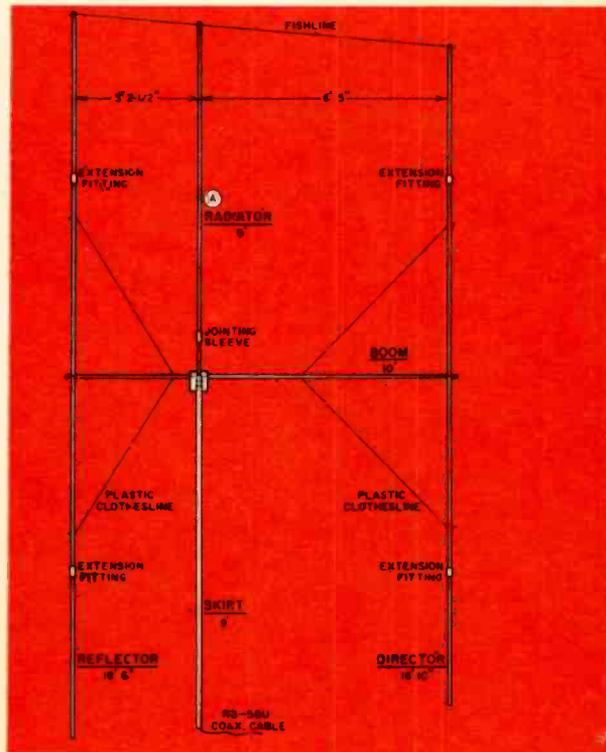


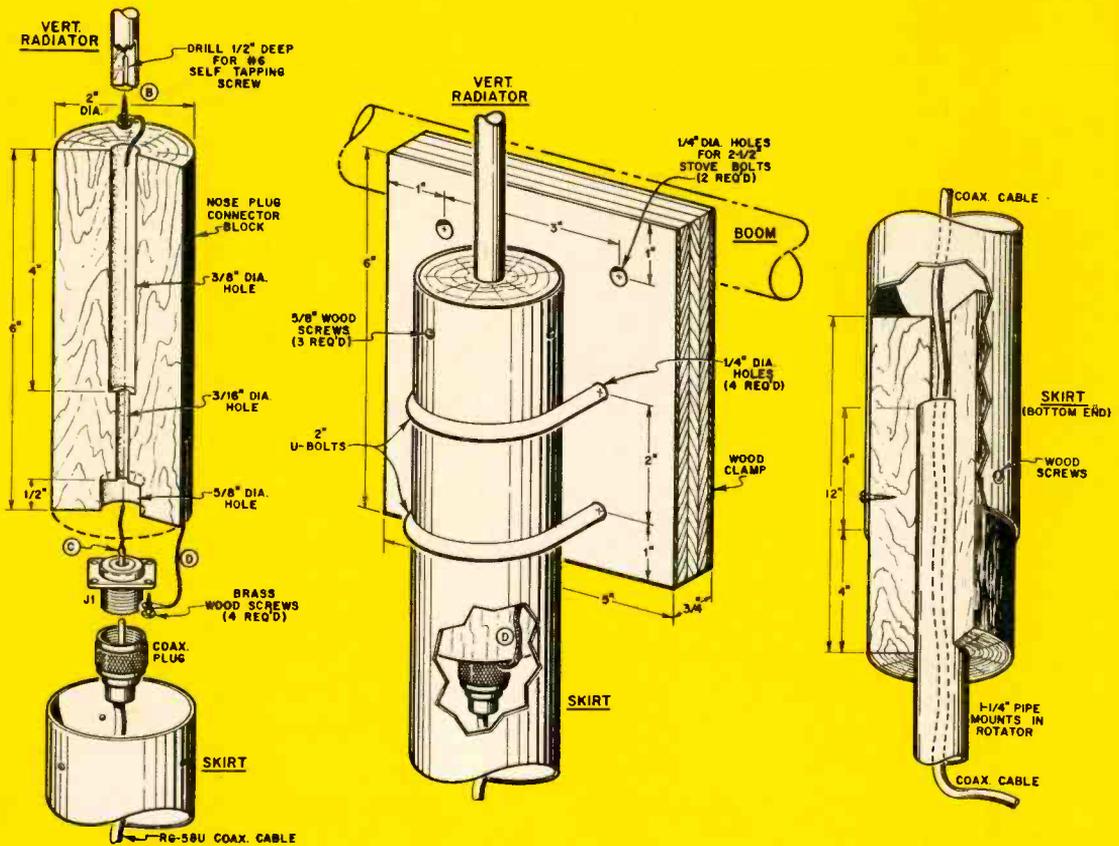


Fig. 2. Construction details of directional beam antenna showing the installation of the two skirt plugs.

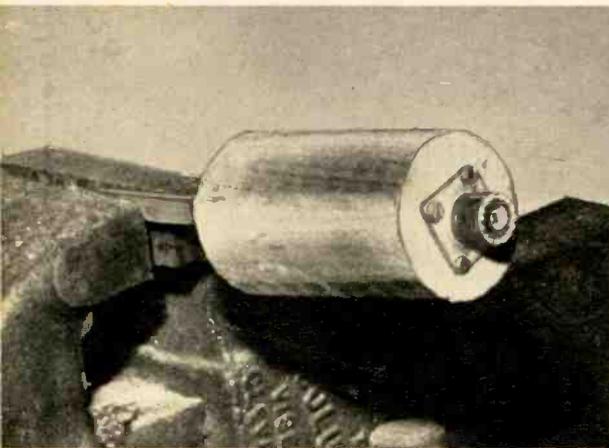

Wooden plug to be installed in the top of the skirt. Note mounting of the coaxial connector.

around the rod ends before inserting them in the sleeve.

Using a $\frac{1}{8}$ " drill, make a half-inch deep hole (Fig. 2, point B) in the bottom end of the rod. A $\frac{1}{2}$ " #6 self-tapping sheetmetal screw is threaded into the hole. This screw will be used later.


The 2" inside-diameter EMT thin-wall aluminum tubing for the skirt comes in 10' lengths, so a foot must be cut off. The top and bottom skirt plugs are trimmed from 4" x 4" scrap wood or other insulator that will make a snug fit. Follow Fig. 2 for drilling and dimensions, then give the plugs two coats of spar varnish for waterproofing. Connect a 7" length of stranded hookup wire to the screw previously placed in the bot-

[Continued on page 101]

THE COAXIAL

The half-wave coaxial antenna consists of a quarter-wave vertical element above and in line with another quarter-wave vertical tube which encloses the transmission line. The center conductor of the transmission line is connected, via a coax connector and socket, to the top rod; the shield of the transmission line is connected to the bottom tube (skirt). The latter prevents the transmission line from radiating, keeping the radiation of the antenna close to the earth for maximum effectiveness.

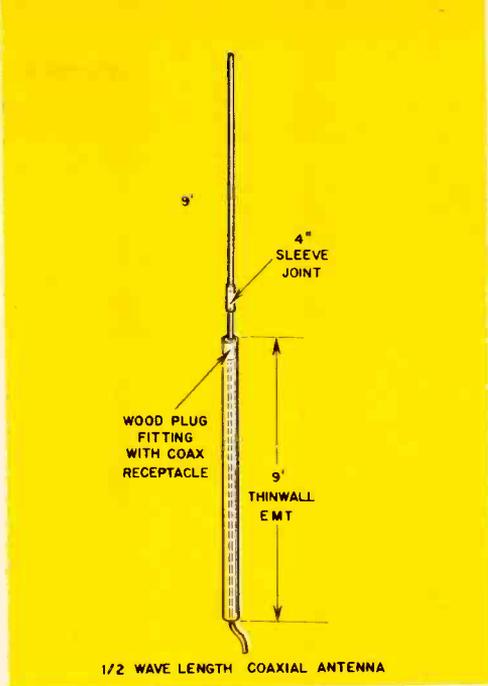The construction of this antenna is the same as for the driven element of the 3-element beam except the bottom plug may be omitted. This is an omnidirectional antenna and requires no rotor for wide coverage.



THE GROUND PLANE

This popular omnidirectional antenna requires comparatively little room. The four horizontal equal-length rods furnish an immediate ground for the vertical radiator and keep the radiation pattern close to the ground.


The wood block which serves as the base for the elements is a short length of 4 x 4-inch stock. Drill $\frac{3}{8}$ " holes, $1\frac{1}{2}$ "

deep on the top and four sides, to hold the driven element and radials; drill a $\frac{5}{8}$ " well on the bottom for the coax socket. Drill a $\frac{3}{16}$ " tunnel between the well and the hole on the top for the wire from the vertical radiator to the inside terminal of the coax socket.

Use a right-angle mast mount that has the central portion cut out (one is available for 34¢ from Allied Radio, type 8800-U). Fit the coax socket through this cutout onto the well on the bottom of the block and fasten with wood screws. Connect an insulated wire from each radial to the screws holding the socket to the block. Notch the top of the skirt as shown to allow these wires to pass through.

The vertical radiator and horizontal radials are made from $\frac{3}{8}$ " solid aluminum rod 9' long. Since such rod normally is supplied in 8' sections, sleeve fittings will be required to lengthen the rods. Fit them as described in the Directional Beam construction.

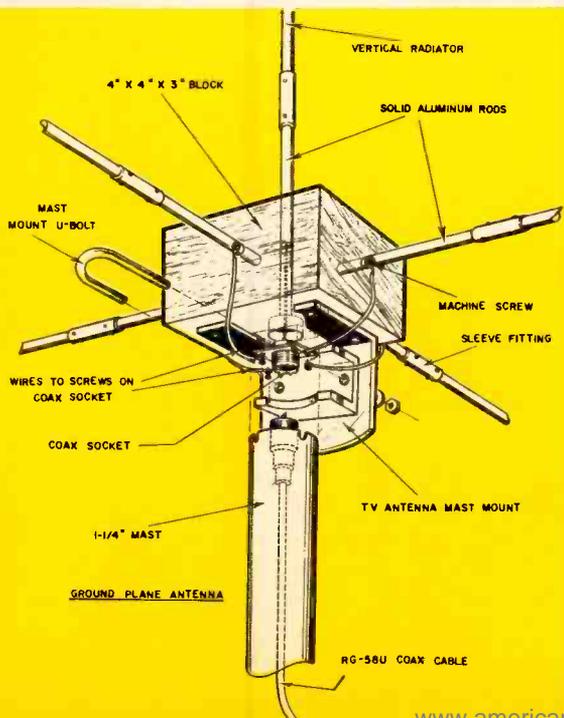
In building any of these antennas, closely follow the dimensions given. Do not use metal parts where the plans specify use of wood or other insulator. Use spar varnish on all wood and spray all exposed connections and terminals with acrylic protective spray.




THE CUBICAL QUAD

This unusual-looking antenna acts like a full-wave two-element directional beam with the front loop as the driven element and the rear loop as the reflector. The optimum spacing between the front and the rear loops for highest gain is about 80 inches on the 11-meter band, but 50 inches is a reasonable compromise giving a gain of about 5 db.

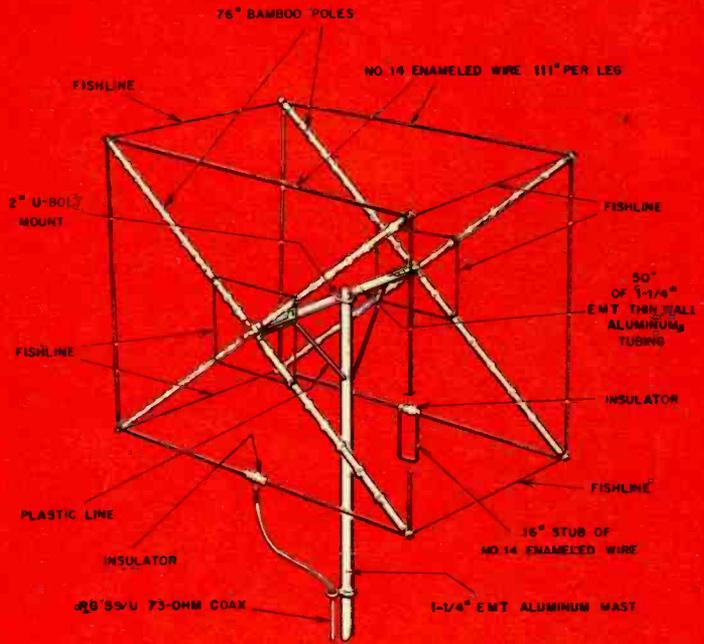
The C-Q requires a rotator to work mobile rigs, but its beam is not as sharp as the first antenna described. Since part of each element is vertical and part horizontal, the C-Q is



QUAD ANTENNA FOR CB

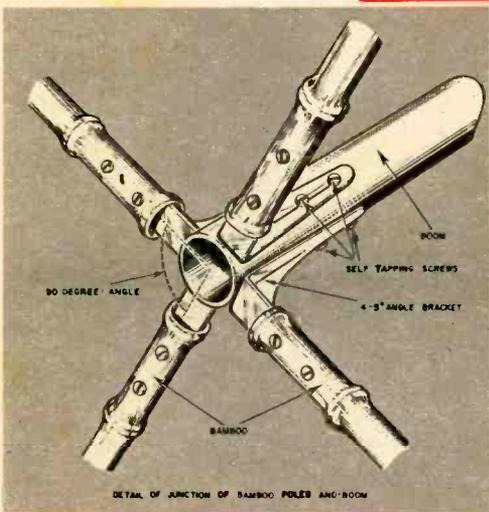

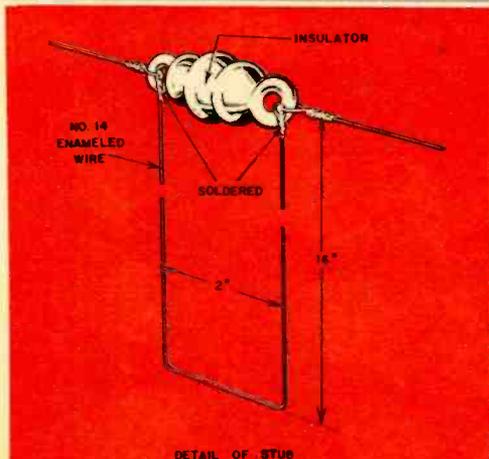DETAIL OF JUNCTION OF BAMBOO POLES AND BOOM



DETAIL OF STUB

polarized horizontally and vertically.

Bamboo poles are used to support the loops because the wires must be insulated from the boom and mast, and bamboo is both light and strong. Ordinary fishing poles (without splits) will do, but they must be of equal length. Use a 20-pound test fishline to keep the arms from vibrating and changing the loop spacing.

Use 1¼" EMT thinwall aluminum tubing for the mast and boom. Standard 5" angle brackets (with bolts through the rod and brackets) hold each bamboo rod to the boom. Each rod must be 90 degrees from the adjacent rods. If the bracket will not fit into the end of the bamboo rod, bolt it to the outside of the rod. In either case, wrap picture wire around both the rod and bracket for extra strength. Spray the wire with a rust arrester.

Each vertical and horizontal section of the loop must be equal in length, so don't pull the poles together while wiring the antenna.

The "stub" is used to tune the reflector to 27 mc. About 75 feet of No. 14 enameled or Formvar wire will be needed for the loops.

Electronics Illustrated



the LICENSE-FREE band

Here are the facts on using the increasingly-popular handi-talkie rigs that do not require an FCC ticket.

By David Walker



THE FAMOUS BC-611 Handi-Talkie of World War II has come a long way. That power-hungry five-tuber is now a neat transistorized package that fits in your palm. And FCC regulations permit anyone to buy or build one of these little transceivers for almost any purpose, and to operate it without any kind of license.

As a result of these two factors, handi-talkies have become immensely popular. They are being manufactured by the thousands, and in this issue EI presents plans for building your own.

But exactly where do the handi-talkies fit into the radio picture? Can a handi-talkie be used on any CB frequency, or anywhere else?

Strictly speaking, handi-talkies stand apart from the CB service as "low power communication" devices, regulated by Part 15 of the FCC rules (CB

is regulated by Part 19). All restricted radiation devices are taken care of by Part 15—wireless mikes, phono oscillators, garage-door openers, etc.

There is more than one License-Free Band (one falls in the broadcast frequencies, for instance) but the one we're mainly concerned with here is separate from, but overlaps much of, the Citizens Band. It begins at 26.97 mc and runs up to 27.27 mc, as compared to the 26.965-27.255 mc spread of CB (see chart). Since the overlap begins between CB channels 1 and 2, you can use any regular CB crystal, except for channel 1, in handi-talkie rigs. Actually, crystal control is not required, but it is advisable for useful operation.

Other technical regulations state that handi-talkie power is limited to 100 milliwatts and the antenna must be a single element not over five feet in

length—hence telescoping monopoles.

Anyone—citizen or alien, young or old—may use a handi-talkie for any legal purpose without filling out a single FCC form. You can chat idly by the hour and call CQ to your heart's content. There are just a couple of reservations.

The unit must bear a Certificate of Compliance that says it meets Part 15 requirements. Such certificates are attached to wired units at the factory but can be filled out and mounted by those who build their own. The second catch is that license-free rigs can talk only to other similar units. If they contact a licensed CB station, they fall under the regulations of Part 19 and licensing, station identification, etc., are required.

In practice, handi-talkies usually are used in mixed systems that include CB units. They then pick up a second certificate, FCC form 452-C. Most are technically qualified for class D operation, having crystals of .005% frequency tolerance and other CB features.

The range of handi-talkies varies greatly, being easily affected by local interference. In a relatively quiet area you can count on about a mile, which is tripled over water. In a mixed system of CB base station and handi-talkie the range is greater because of the increased




The License-Free and Citizens Bands are not the same but the two do overlap on most frequencies.

power and the improved antenna at the base station.

Aside from amusement and experimentation values, handi-talkies have serious uses. They increase the versatility of almost any setup. Our lead art shows EI Tiny-Talkies (the smallest units we've seen yet) being used by two fishing parties. They also are employed by hunters, power line and transmitting tower repairmen, TV antenna installers, on construction jobs and in many other applications.

They answer a need that is not met by any other equipment—a reliable communications system that you can slip into your pocket.

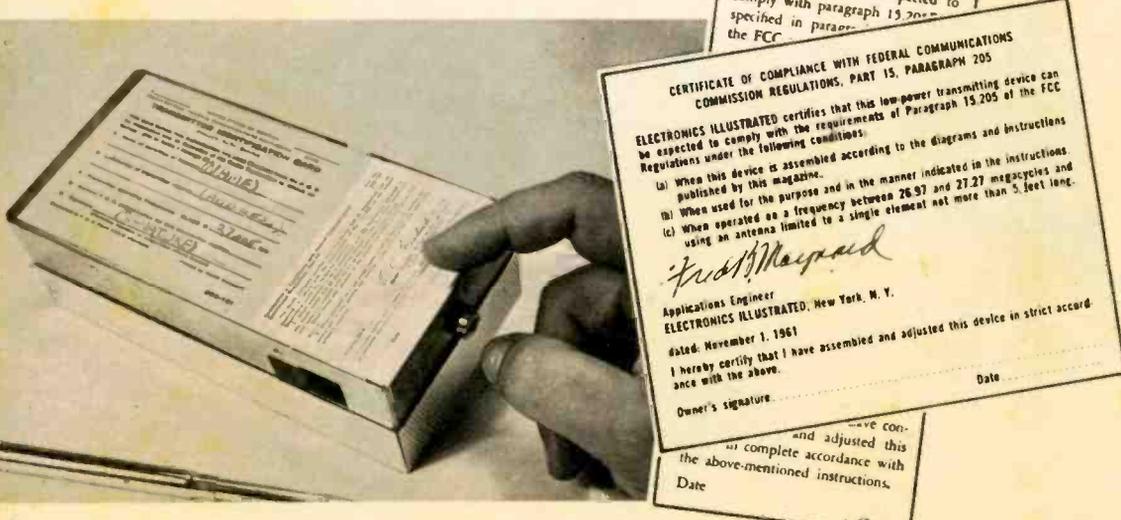Whether a handi-talkie is home-brewed, built from a kit or commercially manufactured, it must bear a Certificate of Compliance stating that it meets requirements of Part 15.




NOW... RCA OFFERS A COMPLETE SELECTION OF HOME TRAINING COURSES IN ELECTRONICS



ELECTRONIC FUNDAMENTALS


40 theory lessons! 40 experimental lessons! 40 service practice lessons! Course includes 12 kits to build a Multimeter, AM Receiver and Signal Generator.

**2
new
courses
now
available**

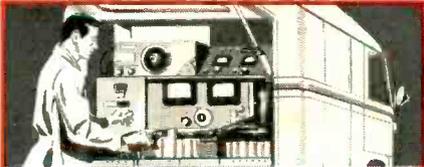


COMMUNICATIONS ELECTRONICS

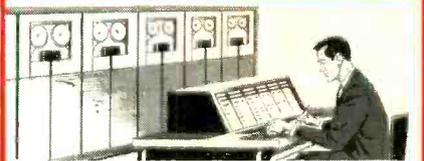9 study groups! 18 lessons! Covers oscillators, power amplifiers, AM, FM, SSB, Mobile Radio—prepares you for an FCC license!



COMPUTER PROGRAMMING

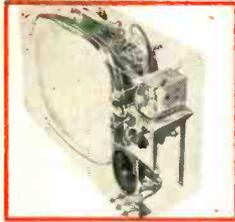5 study groups totaling 11 complete lessons, in principles and techniques of programming business computers! High School graduation and 1 year business experience required.



TELEVISION SERVICING

10 study groups totaling 27 lessons plus 6 complete kits for construction of a modern television receiver!

COLOR TELEVISION

2 study groups totaling 11 complete lessons! Includes the theory in installation, and servicing of modern color television receivers!



AUTOMATION ELECTRONICS

5 study units of 4 lessons each! Covers electronic devices used in industry to achieve automatic control of production systems and processes!



TRANSISTORS

5 Study groups totaling 10 complete lessons! Fundamentals, applications, and construction of transistor transmitters and receivers!

Practical work begins with the very first lesson! Voluntary tuition plan! No long-term contracts to sign! No monthly installment payments. Pay only for one study group at a time if and when you order it!

**Build your future
in electronics now!
SEND FOR THIS
FREE HOME STUDY
CATALOG TODAY!**



Just fill out this card and drop it in the mail. ▶

RCA INSTITUTES, INC., Dept. EI-52
A Service of Radio Corporation of America, 350 West Fourth Street, New York 14, N. Y.



The Most Trusted Name in Electronics

RCA INSTITUTES, INC., Dept. EI-52

A Service of Radio Corporation of America
350 West Fourth Street, New York 14, N. Y.
610 South Main Street, Los Angeles 14, Calif.

Without obligation, rush me the FREE 64-page illustrated book describing your electronic training program (check one). No salesman will call.

Home Study School Los Angeles Resident School
New York Resident School

Name..... Age.....
(please print)

Address.....

City..... Zone..... State.....

Veterans: Enter discharge date.....


CANADIANS—Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Enclose this card in envelope and mail to: RCA Victor Company, Ltd., 5581 Royalmount Ave., Montreal 9, Quebec.

RCA TRAINING CAN BE THE SMARTEST INVESTMENT YOU EVER MAKE

HOME STUDY SCHOOL.

With RCA Institutes Home Study training, you set your own pace in keeping with your ability, finances and time. All equipment and components provided are brand new and of prime quality . . . and you never have to take apart one piece to build another.

Most Important To You, RCA offers a liberal Voluntary Tuition Plan—the most economical home study method available *because you pay only for lessons as you order them* . . . one study group at a time! If you drop out at *any* time, for *any* reason, you do not owe RCA one penny! No other obligations! No monthly installment payments! Licensed by the New York State Education Department. See reverse side for list of courses.

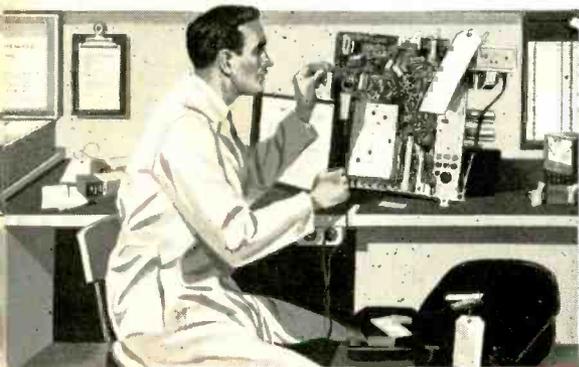

RESIDENT SCHOOLS

If you prefer you may attend classes at one of RCA Institutes Resident Schools in either Los Angeles or New York City. Co-educational Day and Evening Classes. Free placement service. The following courses are available at either resident school:

CHOOSE FROM THIS LIST . . .

	Course	Qualifications	Length of Course
A	Advanced Electronic Technology (T-3)	High School grad. with Algebra, Physics or Science	Day 2 1/4 yrs. Eve. 6 3/4 yrs. (N.Y.) 4 1/2 yrs. (L.A.)
B	Television and General Electronics (V-7)	2 yrs. High School with Algebra, Physics or Science	Day 1 1/2 yrs. Eve. 4 1/2 yrs. (N.Y.) 3 yrs. (L.A.)
C	Radio and Television Servicing (V-3)	2 yrs. High School with Algebra, Physics or Science	Day 9 mos. Eve. 2 1/4 yrs. (N.Y.) 1 1/2 yrs. (L.A.)
D	Transistors	Radio background	Eve. 3 mos.
E	Electronic Drafting (V-11 V-12)	2 yrs. High School with Algebra, Physics or Science	Eve. Basic: 1 yr. Advanced: 2 yrs.
F	Color Television	Television background	Eve. 3 mos.
G	Radio Telegraph Operating (V-5)	2 yrs. High School with Algebra, Physics or Science	Day 9 mos. Eve. 2 1/4 yrs. (N.Y.) 1 1/2 yrs. (L.A.)
H	Computer Programming (C-1)	College Graduate or Industry Sponsored	Eve. 24 weeks Sat. 30 weeks
I	Technical Writing (V-10)	High School Graduate	Day 9 mos. (L.A.) Eve. 2 1/4 yrs. (L.A.) 3 mos. (N.Y.)
J	Automation Electronics (V-14)	Background in Radio Receivers and Transistors	Eve. 9 mos. (N.Y.) Sat. 44 weeks (L.A.)
K	Digital Computers	Electronics background	Eve. 3 mos. (L.A.)
L	Preparatory Math & Physics (P-0)	1 yr. High School	Day 3 mos. or 6 mos.
M	Preparatory Mathematics (P-DA)	1 yr. High School	Eve. 3 mos.

FIRST CLASS
PERMIT NO.
10662
NEW YORK, N. Y.

BUSINESS REPLY MAIL


No Postage Stamp Necessary if mailed in U. S.

Postage will be paid by —

RCA INSTITUTES, INC., Dept. EI-52
350 West Fourth Street
New York 14, N. Y.

SEND FOR THIS FREE
ILLUSTRATED BOOK
DESCRIBING RCA
RESIDENT
SCHOOLS.

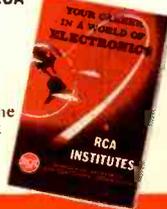Fill in the
other side of the
card and check
Resident
School.



RCA INSTITUTES, INC., Dept. EI-52
A Service of Radio Corporation of
America, 350 W. 4th St., N. Y. 14,
N. Y., 610 S. Main St., Los Angeles, Cal.




The Most Trusted Name
in Electronics


AN EARPHONE for your transceiver



UNLIKE communications receivers, most CB transceivers do not have an earphone jack. This is regrettable considering the QRM on the band. Think of the convenience of being able to monitor CB without disturbing family or friends and being able to read a signal over the background noise in your immediate environment. High quality miniature earphones are available from a number of distributors and some even include a miniature matching jack. The jack is so small that you will have no trouble finding an open area close to the speaker on your rig's panel in which to mount it. If connected as shown in the diagram, plugging in the earphone will automatically disconnect the speaker.

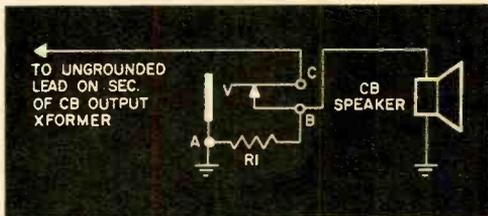


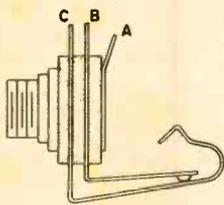You can use any impedance earphone (8 ohms to 100,000 ohms), but with an earphone other than the 8-ohm type it's a good idea to install a 47-ohm, 1-watt resistor (R1) as shown to prevent damage to the unloaded output transformer.



The volume heard in the earphone will be controlled by the transceiver's gain control. However, because of the efficiency of these earphones you will need a lot less gain when substituting for the speaker. Never have the gain turned up high when plugging in the earphone as you may damage the earphone—or your ear.

CB Thru Your Car Speaker

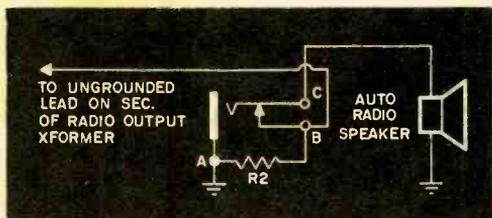

WITH THE same jack installation shown above on your CB rig and the hookup at left added to your auto radio speaker you can feed the output of your CB transceiver directly into your car radio's speaker. Simply connect the two jacks by a jumper wire with a standard miniature phone plug on both

ends. The wires need not be shielded and may be of any convenient length. The greater fidelity and sensitivity of your auto radio speaker will be of decided advantage in helping those hard-to-hear mobile messages get through. Normal operation of the auto radio is restored when the plug is removed.

Both the adaptations shown assume that one side of the speaker voice coil of your auto radio and transceiver is grounded. The jacks themselves have their A terminals grounded because they are mounted to the panels without insulating washers.

The car radio need not be switched on when you're using its speaker for the CB transceiver. Since the output transformer of the auto radio will be unloaded if the set is accidentally switched on, R2 (about 47-ohms) will prevent damage.

—Morris Moses



For Alignment



For Tuning



For Xtal Checking



For Troubleshooting



CB SIGNAL GENERATOR

BECAUSE THE Citizens Band occupies such a narrow spread of frequencies it is difficult, if not impossible, to get a standard RF generator to produce a signal accurate enough for CB work. The 23 CB channels together occupy only a hair-width space on the dial of a standard signal generator.

But you'll have no trouble putting a narrow-band signal right where you want it with EI's CB Signal Generator. This crystal-controlled instrument was designed *especially* for CB use. It employs standard CB crystals to provide the on-the-nose signals you need when recalibrating tuning dials, aligning RF amplifiers or in general troubleshooting.

It will cost about \$8 to build our signal generator, not counting the crystals. But you can use your own overtone transmit crystals for frequency calibration. Lacking these, you can buy overtone crystals almost anywhere for the change in your pocket.

b
y
H
e
r
b
C
e
n
a
n

To aid in signal identification and to allow for signal spotting with the antenna connected, the generator has a built-in tone modulator which puts out a raucous signal easily distinguished from normal QRM.

Construction

The CBSG is built with easily obtainable components (even the tapped oscillator coil is a stock item) and can be adjusted without instruments.

The front panel of a standard Bakelite case serves as a chassis. Before mounting any components cut all the required holes. The battery clamp is a piece of scrap aluminum bent for a snug fit around the battery.

Prepare Q2 by cutting the center shield lead short; likewise, the black lead of oscillator transformer T1. With the exception of coil L1, mount all components on the panel, then mount L1 with a lockwasher between the panel and coil form. Since L1's threads are delicate, do not tighten the mounting nut too much. T1 is mounted directly on a terminal lug. Pass a piece of bare wire

through one of T1's frame tabs and wrap the wire around the terminal lug (see pictorial) used for battery positive. When the wires at this terminal are soldered, T1 will be mounted rigidly.


Wire in all components (observe polarity of C1 and D1) except the negative battery lead to SW1. To avoid heat damage to the transistors and diode, attach an alligator clip to the leads before soldering them into the circuit.


Adjustment

Set SW1 and SW2 to the *off* position. Set L1's slug full counter-clockwise. Connect a milliammeter of approximately 0-10 range between the free battery lead and SW1.

Turning on SW1 will result in a 3-4 ma reading. If the meter reads reverse-off-scale, interchange the meter connections. Plug in a crystal and with an alignment screwdriver rotate L1's slug clockwise until the meter dips. It is possible that at the beginning of rotation the meter will rise slightly but this is not the adjustment point. Proceed with adjustment until the meter definitely

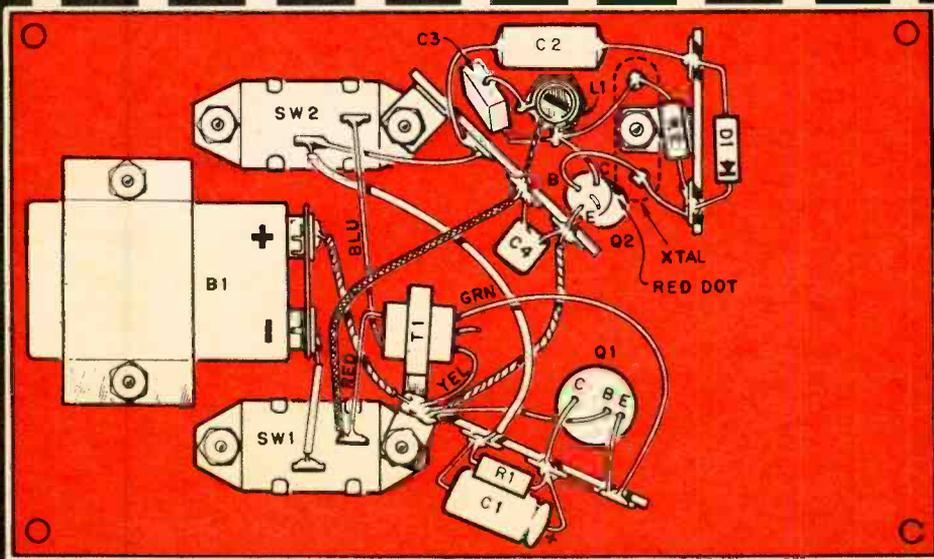All components are mounted on the panel of a standard Bakelite cabinet. The layout is not critical.



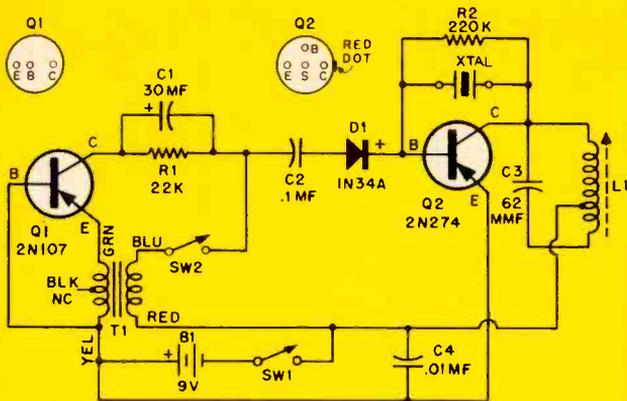

PARTS LIST

- R1—22,000 ohms, 1/2 watt
 - R2—220,000 ohms, 1/2 watt
 - C1—30 mf, 15 VDC miniature electrolytic
 - C2—.1 mf, low voltage miniature
 - C3—62 mmf, 200 VDC silver mica
 - C4—.01 mf, low voltage miniature
 - L1—Oscillator coil (Lafayette HP-62)
 - T1—Subminiature transformer, 10,000 ohm primary, 2,000 ohm CT secondary (Lafayette TR-98)
 - Q1—2N107 transistor
 - Q2—2N274 transistor
 - D1—IN34A crystal diode
 - XTAL—Overtone transmit crystal, see text
 - SW1, SW2—SPST slide or toggle switch
 - B1—9-volt battery, Burgess 2U6 or equiv.
 - Misc. Bakelite case and panel (6 1/4" x 3 3/4" x 2"), terminal strips, socket to match crystal, etc.
- A kit of the parts listed above (less crystal) is available from Lafayette Radio, 111 Jericho Tpke., Syosset, N. Y. Stock no. SP-254, \$7.78. Include postage for 1 1/2 lbs. A Lafayette overtone crystal, stock no. HE-830, is \$2.25 (specify channel desired)

Modulator transistor Q1 may be switched off by SW2. Oscillator Q2's frequency is set by xtal.

dips. After SW1 is adjusted, turn on SW2. The meter will rise about .4 ma indicating the modulator is working. If the readings are excessively high (or low) check for an open or shorted connection. If everything checks out, remove the meter from the circuit and solder the battery lead directly to SW1.

If you do not have a meter available the CBSG can be adjusted by using a transceiver (or receiver) of accurate calibration. Place the CBSG near the receiver's antenna jack and set the receiver to the frequency of the CB crystal. Turn on both SW1 and SW2. From full counter-clockwise, adjust L1's slug until the tone is heard in the receiver—rotate the slug a quarter turn past the setting where the tone first is heard. (L1's proper setting occurs approximately midway between full-in and full-out.)

Once the oscillator is tuned it will work with all overtone crystals. However, if you have aligned the CBSG by the receiver method with one crystal it is possible that overtone crystals of a different manufacture may not oscillate. In that case rotate L1's slug a quarter turn in either direction to start oscillation.

Using The CBSG

Recalibration of a tuning dial which has drifted is an easy task for the CBSG.

Place it near the transceiver's antenna jack and turn the power on. If your transceiver is S-meter equipped, tune the receiver until you get a reading on the S-meter. The CBSG will produce up to an S-9 signal, depending upon its distance from the transceiver.

For easy spotting, turn on the CBSG's modulation. The easily distinguished signal has sidebands extending over several channels. This makes the signal easy to spot when the receiver has drifted far off calibration. To recalibrate, set the receiver to the CBSG's operating frequency with gain turned up full. Then adjust the receiver's oscillator trimmer or slug until the tone is at maximum or the S-meter peaks. For the most accurate adjustment move the CBSG away from the antenna jack so you work with the weakest possible signal fed to the receiver.

RF Peaking

In a similar manner the receiver's RF amplifier can be peaked while being fed from the antenna (the best way). Place the CBSG near the unit's antenna and tune in the signal; adjust the slug or trimmer on the antenna input coil and RF amplifier's plate circuit for maximum tone or S-reading. Even with strong QRM, the distinctive tone of the CBSG can be spotted easily.

THE NEWCOMER to Citizens Band radio, shopping around for his first transceiver, is faced with almost too much of a good thing. How does he choose amongst the multitude of rigs available in every price range?


If you are interested in a transceiver for your car and are the build-it-yourself type, the Heathkit GW-10 can be a good choice. One of the most compact sets available, it is only 15 inches wide (including the side-mounted mike), 4½ inches high and 5¾ inches deep, including knobs.

Heath's under-dash mounting procedure is one of the easiest around, guaranteed not to strain either your dash or your temper. Only two screws through the GW-10's slotted cover are required and the unit is light enough that no fire wall brace is required.

The GW-10 is available in two versions: the GW-10A, which incorporates a 117-volt AC power supply, and the GW-10D, which has a vibrator power supply for 6- or 12-volt DC operation. We built the GW-10D. The transmitter section, consistent with FCC regulations,



HEATH GW-10 TRANSCEIVER

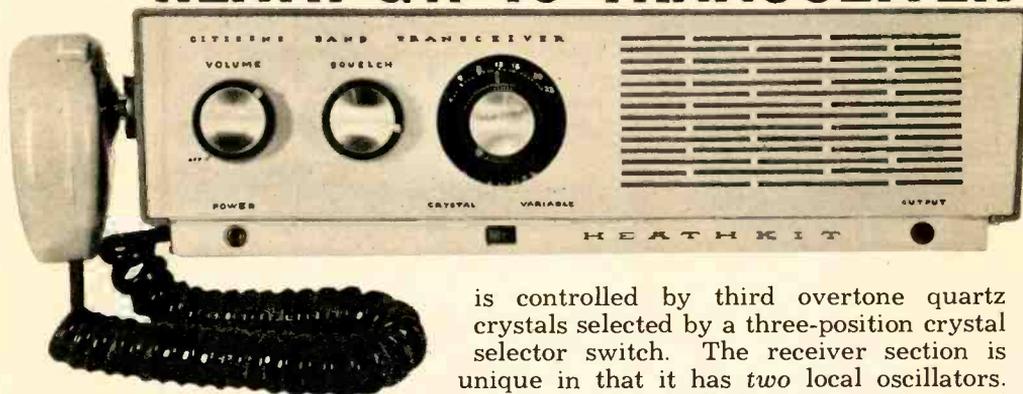


is controlled by third overtone quartz crystals selected by a three-position crystal selector switch. The receiver section is unique in that it has *two* local oscillators.

One is crystal-controlled and hence fix-tuned to a single channel according to what receiving crystal you install. (If you have enough crystals you naturally can tune any channel.) The second oscillator may be switched in to provide continuous tuning across the entire band (see the schematic).

An automatic series gate noise limiter minimizes impulse-type interference, such as ignition, lightning, etc. An adjustable squelch that silences the receiver during standby and a push-to-talk mike button are two nice features of the unit.

Construction. The construction manual and pictorials are clear and easy to follow. But the compactness of the unit may cause trouble for the newcomer to kit building. In order to get everything in, component leads must be kept short and carefully dressed. A pencil type soldering iron is mandatory, and care must be taken to prevent burned insulation or heat-damaged components when soldering.

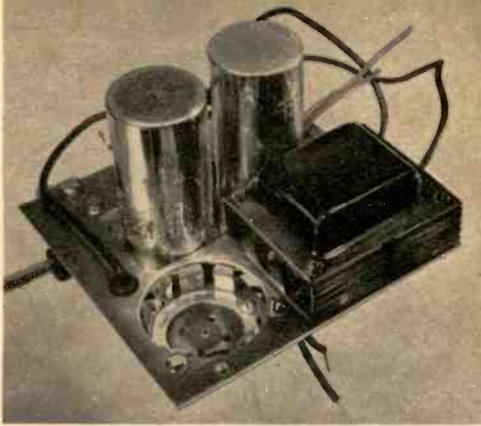Tuning Up. We followed a combination of the Heath instructions and the data given elsewhere in this issue for transmitter tune-up. The receiver alignment is straightforward and should present no problems. We departed from the manual on only one point. Since it often is difficult to tune in a CB station and get a constant signal,



Vibrator power supply subassembly for mobile use. GW-10 has option of 6, 12 VDC or 117 VAC.

we used EI's CB Signal Generator (described elsewhere in this issue) for accurate receiver calibration and alignment.

If you are neat, follow the manual faithfully and take the little extra care and time this kit requires, you will wind up with an excellent CB transceiver which, at \$62.95 for the kit, easily holds its own with the higher-priced factory-wired units.

The New GW-11

Advertised, but not yet available at


the time of this report, is the new Heath GW-11. Physically identical to the GW-10, the GW-11 preserves all the fine mounting provisions of the GW-10.

New features include electronic switching of the antenna (thus eliminating a relay and its possible troubles), a tuning meter mentioned above and a new RF power output stage.


The new output circuit deserves discussion. In the GW-10, a single 6AU8 triode-pentode tube serves as both the oscillator and RF output. In the GW-11 the triode section of the 6AU8 continues in the role of oscillator but the pentode section that previously was the RF output now serves as an RF driver. The recipient of this souped-up drive is a newly incorporated 5763 commercial-type power tube. Used far below its maximum rating, the 5763 in this application provides high reliability. The price of the new rig in kit form is \$66.45.

We wonder, considering the potential of the 5763 tube, whether Heath in the near future doesn't intend to bring out a 6- and 10-meter ham transceiver based on the GW-11.

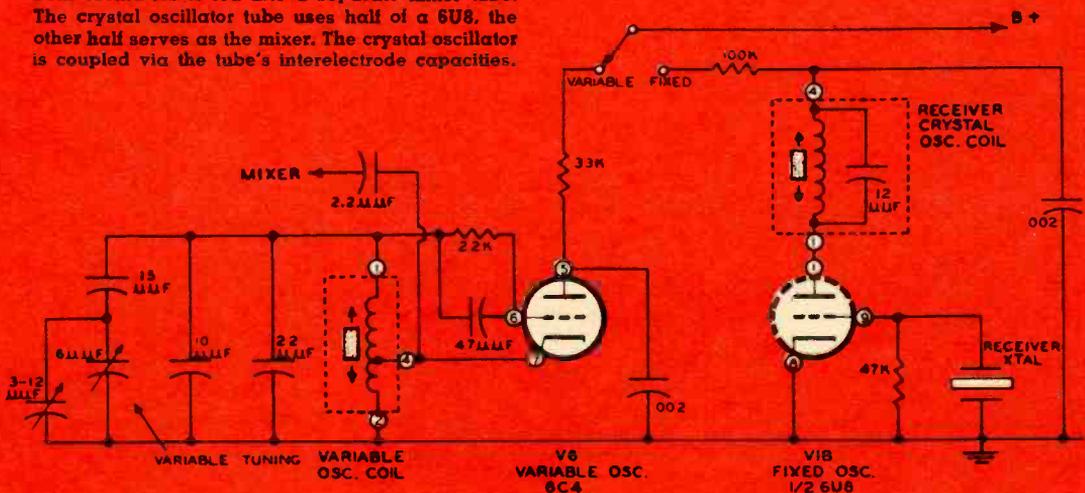Partial schematic of receiver oscillator. Note choice of variable or crystal controlled tuning. Output of both oscillators is fed into a separate mixer tube. The crystal oscillator tube uses half of a 6U8, the other half serves as the mixer. The crystal oscillator is coupled via the tube's interelectrode capacities.



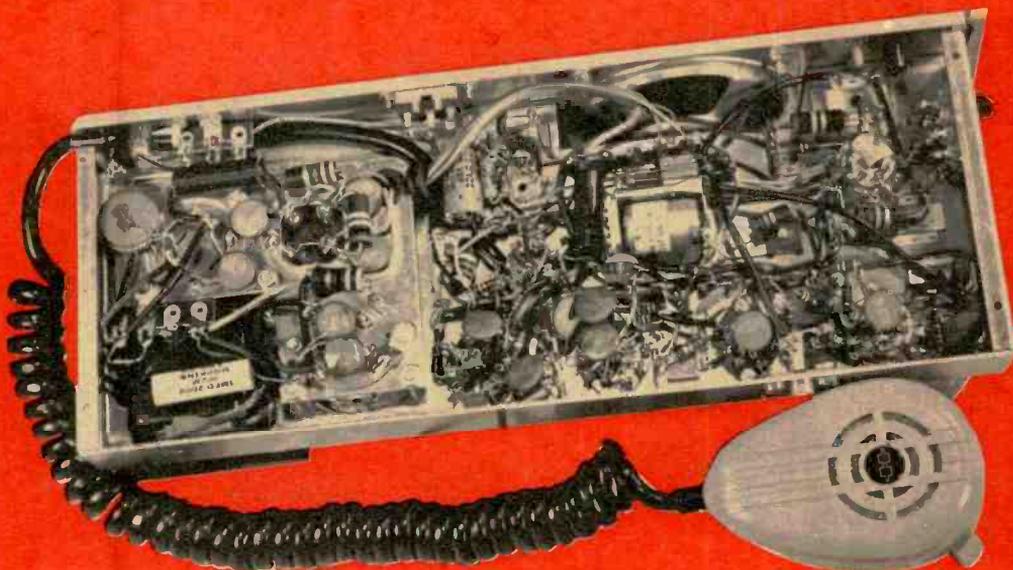**Underchassis view of the completed transceivers.
The compact design requires careful construction.**




Completed unit before installation in its case. In-line fuse holder is seen near the mike.



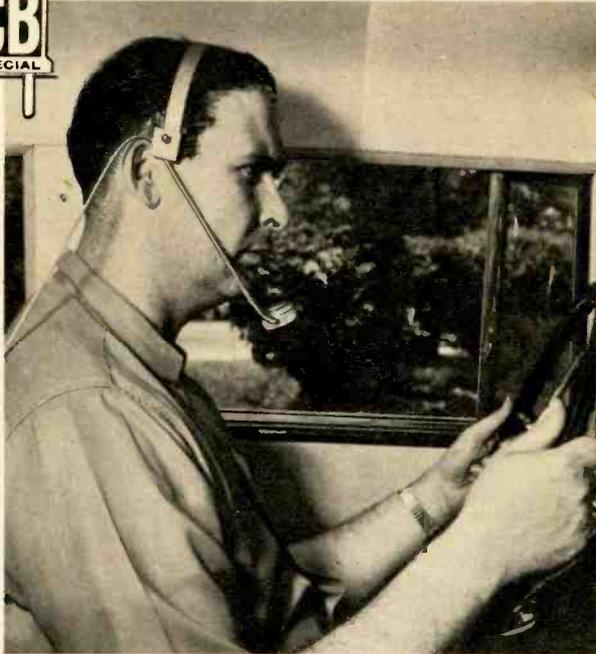Plenty of leg room remains after underdash installation. Because of unit's light weight, no fire wall brace is required.





for CB'ers and Hams

A SAFE MOBILE MIKE

For messages on the move and safety, too . . .

build EI's under-\$5 boom microphone.

By F. David Herman

If you have to transmit while traveling, EI's boom microphone adds some safety to a not-so-good procedure.

First of all, you drive with both hands on the wheel. The microphone remains a fixed distance from your mouth, regardless of which way you look, and you have a special push-to-talk switch-box at your fingertips. With the specified switch, the transmitter can be either locked in the ON position or a spring return can be used for a quick break.

Construction. The microphone boom assembly is built of scrounged components: a ladies headband hair clip, a couple of pieces of scrap plastic, nine inches of $\frac{3}{16}$ " copper tubing and a hard plastic screw-on bottle cap.

A half-inch from one end of the hair clip drill a 6-32 hole (#28 drill). Drill another 6-32 hole through the two plastic pieces as shown. Clamp the two pieces together and drill a $\frac{3}{16}$ " hole angled through the pair for the copper tubing. The block serves as a swivel to permit adjustment of the microphone position.

About $6\frac{1}{2}$ " from one end, bend the copper tubing in an arc. Make certain

you do not crimp the tubing because the microphone cable must be able to pass through it.

If you have one of the modern, small, ceramic microphones, you can remove the element for use in the boom. Or you can purchase a small replacement element.




Drill a $\frac{3}{16}$ -inch hole in the side of the bottle cap which serves as a base for the microphone element. Drill slowly to avoid shattering the cap. The parts are then fitted together with epoxy cement.

Attach the boom to the headband with a 6-32 screw, lockwasher and either an acorn or thumbnut.



Pass an eight-foot length of extra thin
[Continued on page 102]

PARTS LIST

- SW1—Switch, 4PDT three-position spring-return (Lafayette SW-68)
- PL1—Plug to match transmitter input jack
- PL2—Microphone connector (Amphenol 75MCIFA)
- J1—Jack to fit PL2 (Amphenol 75PCIM)
- Minibox, $3\frac{1}{4}$ "x2 $\frac{1}{8}$ "x1 $\frac{1}{8}$ "
- 8 feet thin microphone cable (Alpha type 1702, 0.125 OD)
- Microphone Cartridge available from Custom Electronics, 2929 Fulton St., Bklyn, N. Y., \$3.50 postpaid
- Misc. hardware—See text and pictorials

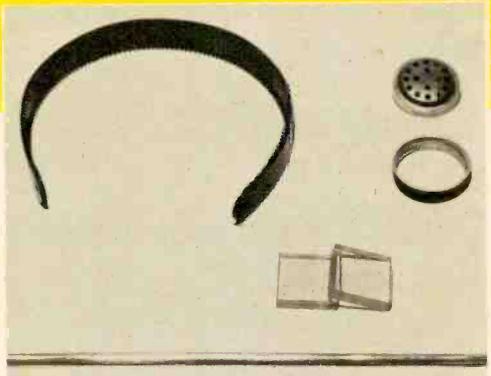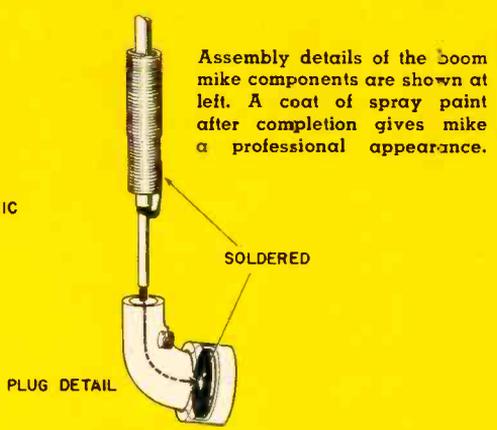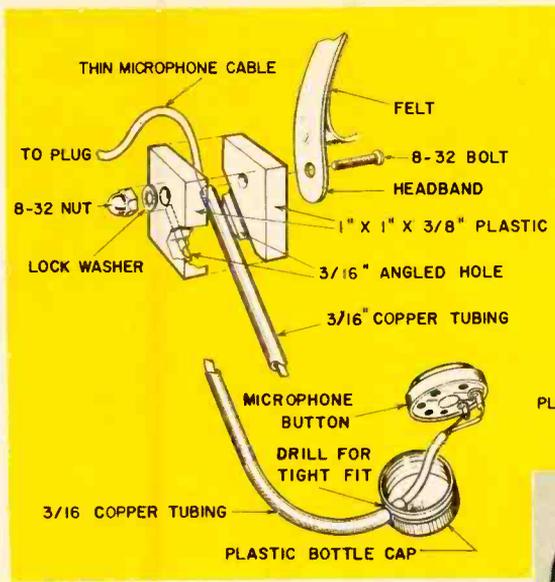

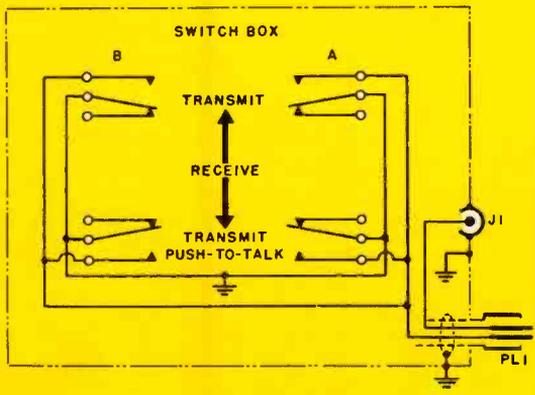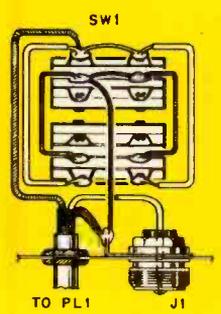Raw material of the boom assembly includes a woman's hair clip, a couple of pieces of plastic, a microphone cartridge and a plastic bottle cap.



Wiring of S1 as viewed from rear. Section B of switch may be used for other circuits.

Mike boom connects to push-to-talk switch box. Large suction cup bolted to Minibox forms a convenient stable means of mounting on the dash.





SERVICING MADE EASY

By Herb Friedman, 2W6045



Part I

IS your Citizens Band rig developing the aches, pains and complaints common to all aging electronic equipment? Although CB hasn't been with us too long, for many rigs overhaul time has come—or is long past due! As a CBer, you can save yourself quite a few dollars—and add to your fund of technical experience—by servicing your own rig.

Because most CB sets get along nicely without sophisticated circuitry, a few relatively inexpensive instruments and homebrew gadgets will handle almost every problem you'll come across. Of course, there are several worthwhile specialized CB service instruments and later in the series we will take a look at the job they can do.

Preliminary Tests. As in all electronic servicing, there are a few basic checks that should be made first. All cables and connecting wires should be inspected for breaks, fraying and possible shorts. In the case of mobile power cables, check the wires where they enter an inline fuse holder since vibration can cause the wire strands to break at the fuse terminals. And, of course, check the fuses. If a new fuse blows, carefully check the tubes for shorts. If the fuse blows only on mobile, check the vibrator and buffer capacitor. More on this section of the transceiver and its troubles later.

Since tube failure is the most frequent cause of equipment failure, a com-

plete tube check should precede any servicing. Remember, however, that the tube testers aren't infallible; if a tube tests good but the meter pointer moves erratically when the tube is tapped, try a new tube from a spare set. RF, IF and oscillator tubes have been known to test good and still not do the job in a specific circuit.

The above checks cover most equipment failures. Anything more complicated means trouble-shooting. Fear not. The nature of a transceiver with its separate circuits simplifies the pinpointing of trouble and localization is 90% of any service job.

Figure 1 shows the interrelations of the various circuits in a transceiver. With the exception of the power supply, the failure of a particular section does not prevent the other circuits from functioning. This is what makes transceiver servicing relatively easy. Now let's take a look at some common trouble symptoms and see how they can be handled.

Receiver Inoperative. First, check to see if the transmitter also is defective. Plug in the RF dummy load lamp recommended by the manufacturer (or a power output meter) and turn on the transmitter. A dead transmitter indicates that the section common to the receiver and transmitter is defective. That section is the power supply.

Two types of supplies are in common use—the voltage doubler and the full-wave rectifier (Figs. 2A and 2B). With transceiver power off and a VTVM or VOM set to the OHMS range, connect the common lead to the chassis and the other probe

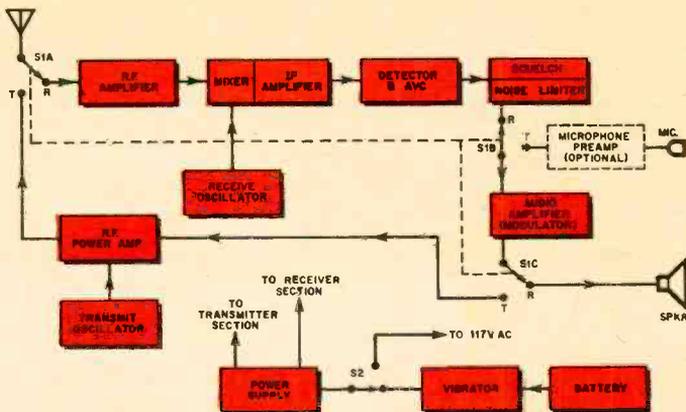


Fig. 1. Block diagram showing switching of a typical transceiver.



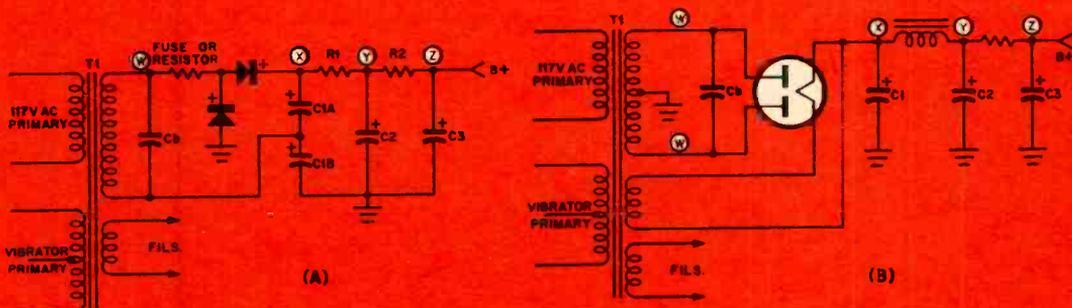


Fig. 2. Two types of standard CB transceiver power supplies. Doubler circuit (A) uses silicon diode rectifiers; full-wave circuit (B) has a rectifier tube.

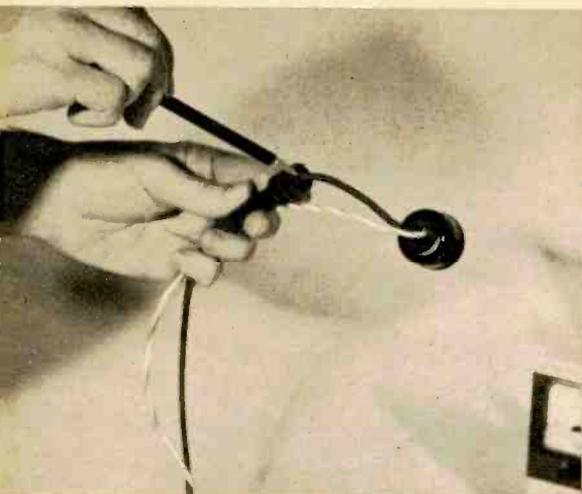In-line fuse holder is a prime suspect to check for broken wires or a bad electrical contact.



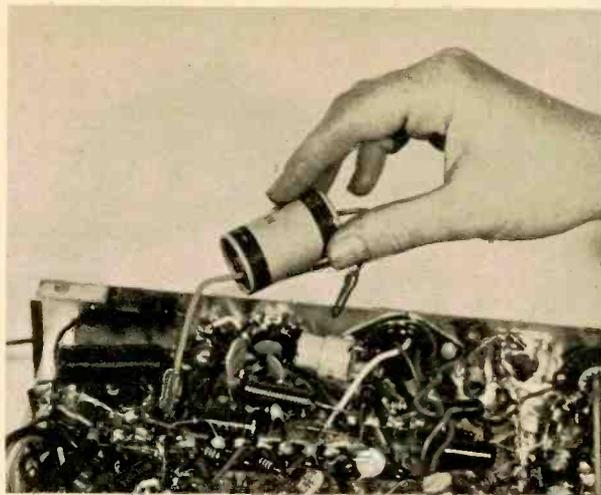The quickest way to check an electrolytic for low capacitance is to shunt it with another unit.



to points X, Y and then to Z in Figs. 2A and 2B. At each point, the meter needle will kick and then settle down to a high value, usually over 150,000 ohms. If the meter reads a low resistance, electrolytic capacitor C1, C2 or C3 probably is shorted or leaky. Temporarily disconnect the leads at the positive terminals of each capacitor and check it with your ohmmeter. Where a resistance filter is used such as in Fig. 2A, a shorted C2 or C3 will tend to overheat or burn out R1 and/or R2.

If one section of a multi-section can is defective, replace the unit since a defective section is a good indication that the others will go shortly.

If the capacitors check out, set the meter to its 300-500 VDC range, connect the common lead to ground and the DC probe to B+ (point Z). Turning on the transceiver should result in the DC reading indicated in the transceiver's service manual. If there is no DC indication, move the probe to X. If there's no DC at X the high-voltage secondary winding of T1 is open, a fuse in series with the secondary is blown or the silicon rectifiers (Fig. 2A only) are defective.

To check the possibilities, set the VTVM to a 300-500 VAC range, connect the common lead to ground and the probe to W. If AC is present at W but

no DC (B+) at X, the rectifiers are defective, or C1B may be open. If no AC is present at W check the wiring, fuses, C1B and the switch feeding transformer T1. If the power wiring is okay, T1 is defective.

Severe Hum in Loudspeaker. The first check in this case is to turn the set's volume control down but not off. If the volume control doesn't appreciably affect the hum, it's a good bet that your transceiver has an open filter capacitor (C1, C2, C3 in Fig. 2). Since failure of any filter capacitor can cause the hum, each one must be tested individually. Using clip leads or the test capacitor shown, connect a capacitor of equal or higher capacity and voltage rating across the suspected unit. When the hum is eliminated or diminishes substantially, you've found the culprit. Note that this test will work only with capacitors which are open or have lost capacity. Shorted or leaky units will cause other symptoms and are checked as in the *Receiver Inoperative* section.

Fuse Blows on Mobile Only. The fact that the transceiver operates on the AC line indicates a problem in the mobile power supply. In modern CB transceivers, the power transformer has extra windings for the vibrator. Therefore, first check the vibrator. If it tests okay, the difficulty is most often buffer

An RF signal generator will also supply an audio tone for signal tracing after the detector stage.



capacitor C_b (see Figs. 2A, 2B). C_b is subjected to high peak voltages and must be replaced with an *exact* duplicate in rating and capacity. In fact, it's a good idea to replace C_b whenever you replace the vibrator.

Once we eliminate the power supply as the possible source of breakdown, troubleshooting becomes easy because the operating sections can make the defective sections stand out like a sore thumb.

No Reception. Since this fault could be due to several defects, let's first check the RF output. The logic of this will become clear shortly. Connect a visual RF indicator (dummy load lamp) or a CB power meter to the antenna jack, turn on the transmitter and speak into the microphone. If the load lamp lights—indicating RF output—but does not change in intensity with modulation (a power meter will wiggle with modulation), this indicates a fault in the audio section. Since the audio section is common to the transmitter and receiver (see Fig. 1), the lack of reception is due to the same defect. Notice that before the transmitter was tested, the lack of reception *could* have been due to a fault in *any* part of the receiver.

To further localize the trouble, an audio signal from an RF signal generator or other instrument is used as an

audio signal source. (Even an FM tuner will serve.) With the transceiver off, connect the signal source's ground lead to the transceiver chassis. Connect the hot lead through a .05 mf, 600-volt capacitor to the plate (Z) of audio output tube V₁, Fig. 3. A signal, although weak, should be heard in the speaker. Silence indicates a defective output transformer (T₂), speaker or C₄.

Check the speaker first. Set your meter to the low-ohms range and connect the leads across the speaker terminals. At the instant of contact a click should be heard in the speaker. If the speaker passes the click test, check for an open winding in T₂ or a short in C₄.

If the output transformer and speaker
[Continued on page 105]

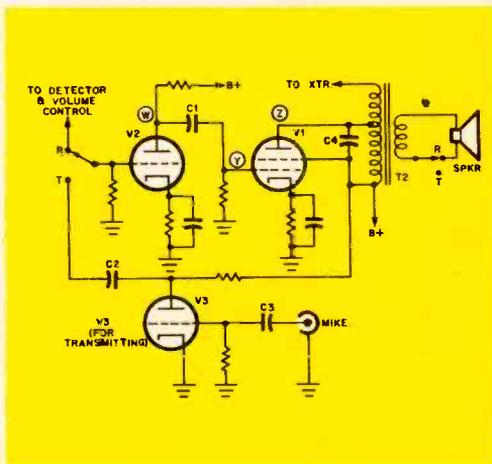


Fig. 3. Typical audio stage. With T-R switch on receive, mike preamp (V₃) is out of the circuit.

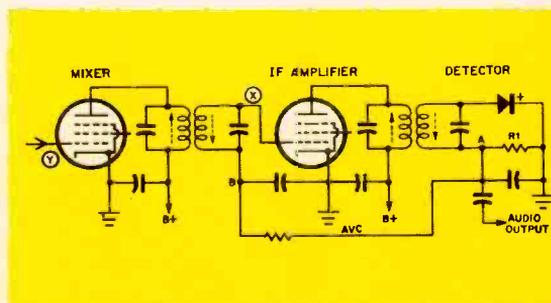



Fig. 4. Mixer, IF and detector stages. There may be several IF's or combined tube functions.



You have your test equipment built in

when you . . .

ADD AN S-METER

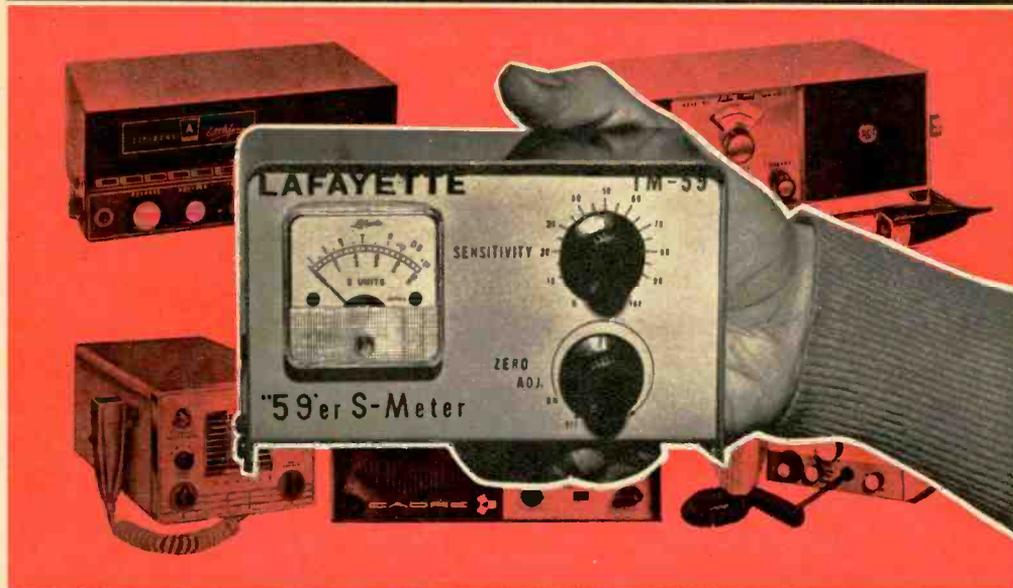

By Bert Mann

FOR a \$10 investment you can build into your Citizens Band transceiver a major part of the test equipment necessary to insure peak performance. An easily installed vacuum-tube S-meter will enable you to align your receiver, calibrate the tuning dial, tune up your mobiles and assist other stations making antenna adjustments.

Because the S-meter circuit shown is essentially a VTVM, connecting it to your transceiver's AVC circuit will cause no undesirable effects.

The current drain of the S-meter is low. It can be connected to any CB unit without fear of power supply overload.

Several mail order houses sell a meter movement with a scale calibrated in S-units. If you own one of these meters you can add the tube driver circuit as shown. However, the complete vacuum-tube S-meter unit shown in the lead photo can be obtained for not much more than the cost of the parts (see Parts List).

Installation. Mount a four-contact jack or socket at any convenient spot on the transceiver chassis, preferably near the last IF transformer. Wire the jack as shown. The filament lead (4) is wired to any 6-volt point; or a 12-volt point through R6. The instruction with the Lafayette TM-59 calls for 39-ohm resistors in series with 6C4's filament for 12-volt operation. Longer tube life, particularly in mobiles, will result if you use a 43-ohm resistor for R6.

A handy spot for the B+ lead (1) tap is the B+ side of the audio output

tube's screen grid resistor. If your rig has no screen grid resistor connect the B+ lead to the screen grid terminal. The AVC lead (2) is connected to point A, but it may be easier to find point B, which is located after the AVC filter (Rf and Cf.) Rf usually has a value of 1 to 3 megohms and Cf is usually a .05 mf capacitor. While AVC systems have some differences, they all have Rf and Cf. Ground (3) goes to the nearest chassis ground point. This completes the receiver wiring.

The cable from the S-meter should be connected to a plug (PL1) matching the socket (J1) installed on the transceiver.

Adjustment. Disconnect the transceiver's antenna and short-circuit the antenna jack with a piece of wire. Rotate *Zero Adj.* control R5 for zero meter

indication. Reconnect the antenna, tune in a *strong* signal and adjust sensitivity control R3 for an S-9 reading. With S-9 as a normal strong signal setting, close mobiles won't slam the meter needle. Note that when the meter is first turned on the needle normally goes full scale, then falls to zero.

Using the S-M. As a true indicator of received signal strength and RF and IF gain, the S-M can serve in a number of roles.




● **Alignment.** In conjunction with the CB Signal Generator described else-
[Continued from page 104]

Four-contact socket J1 is installed on chassis at a spot convenient for internal connections.

PARTS LIST

Resistors: 10% tolerance
 R1—560 ohms, 1 watt
 R2—330 ohms, 1 watt
 R3—1,000 ohm potentiometer
 R4—33,000 ohms, 2 watts
 R5—3,000 ohm linear potentiometer
 R6—39 or 43 ohms, 2 watts (see text)
 M1—0-1 ma S-meter
 V1—6C4 tube
 PL1—Amphenol 71-45
 J1—Amphenol 78-545

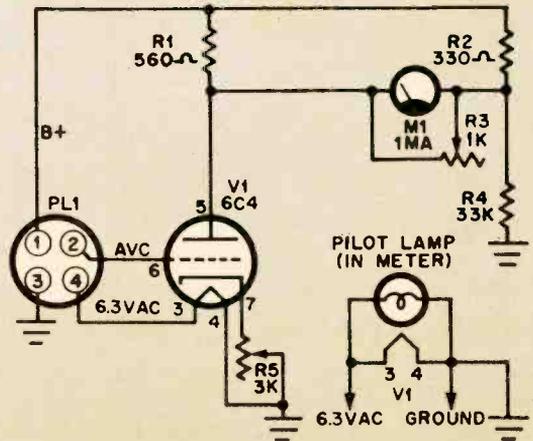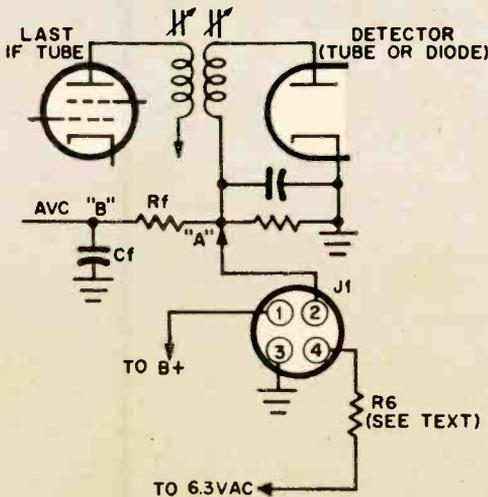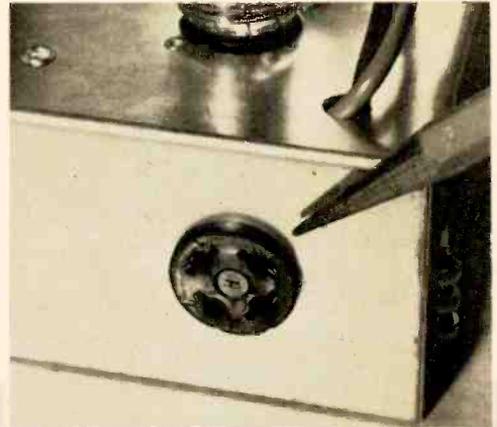Complete S-Meter—Stock #TM-59 (Lafayette Radio)



S-meter schematic is at right. Power and AVC take-off points in transceiver are shown at left.



Flyweight

TRANSMITTER for model rockets

By G. Harry Stine

President, National Association of Rocketry

OUR YOUNG ROCKETEERS, having learned to build and shoot their rockets safely are now interested in instrumenting their birds. Most basic instrumentation is a telemetry system which transmits data from a rocket in flight to a receiving station on the ground.


EI's Flyweight Transmitter is an excellent basic telemetry system particularly suited to model rockets. It is simple to build, inexpensive, weighs only 1½ ounces including battery and can transmit data supplied by a variety

of transducing elements or sensors.

The Flyweight Transmitter also is rugged enough to withstand flight after flight because it's constructed on a sliver of perforated board that fits snugly into the ¾-inch tube of a recoverable model rocket. The transmitter's 50-milliwatt power rating makes it eligible for the license-free part of the Citizens Band—channels 2 through 23 (see **THE LICENSE-FREE BAND** in this issue), and a miniature CB crystal can be used in the circuit. EI supplies the Certificate of Compliance (see cut).

1. The antenna, a length of wire through rocket nose plug, is attached to transmitter's output.

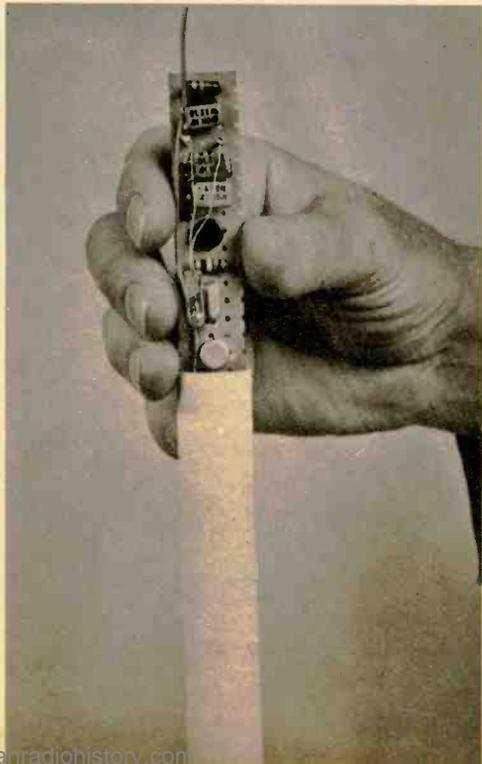2. Transmitter, with battery hooked up and its circuit operating, is inserted in rocket tube.





Hams, of course, can operate this transmitter on any amateur band. It has been tested with good results on both 10 and 40 meters. A strong signal has been received at a distance of 1,500 feet on a National NC-303 receiver.


The Flyweight Transmitter incorporates a multivibrator (Q1 and Q2) whose audio output frequency is determined by sensor Rs. The output of the "multi" modulates crystal controlled RF output transistor Q3.

Most of our tests have been conducted with a miniature photo resistive cell as the sensor. Besides light intensity, such a cell can give you the spin rate of a rocket. A small hole in the side of the rocket tube admits a burst of light each time it faces the sun. This causes a rapid shift in tone. Other possible sensors include a thermistor for temperature, an accelerometer or a miniature altimeter.


Wave-trap L3-C4, shown in the schematic only, is optional but may be used to cut spurious radiation. C4 is a 3-30 mmf ceramic trimmer capacitor and L3 is a 1.5 microhenry choke (Miller #4604).

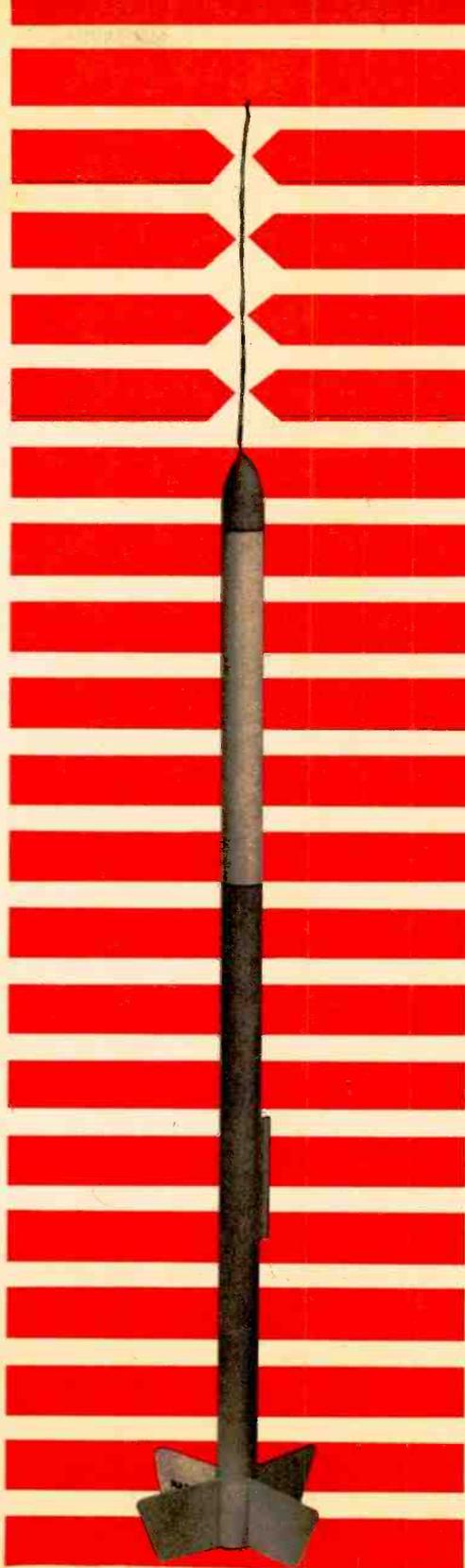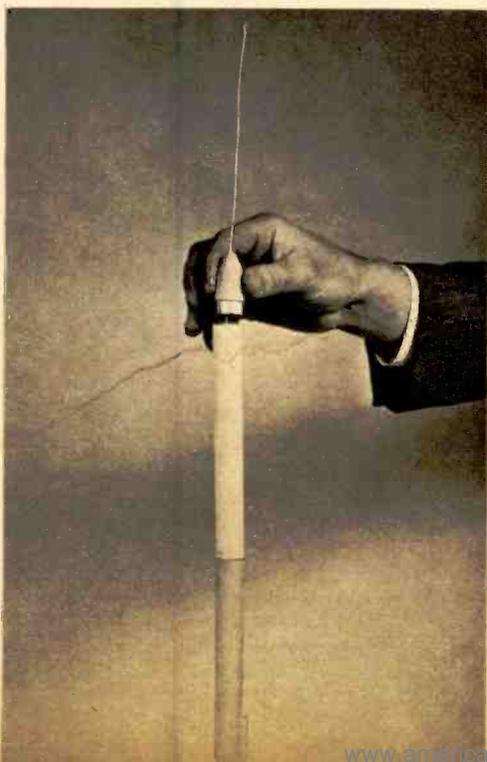3. As last step, nose plug is fitted snugly in tube and rocket is ready for launching stand.



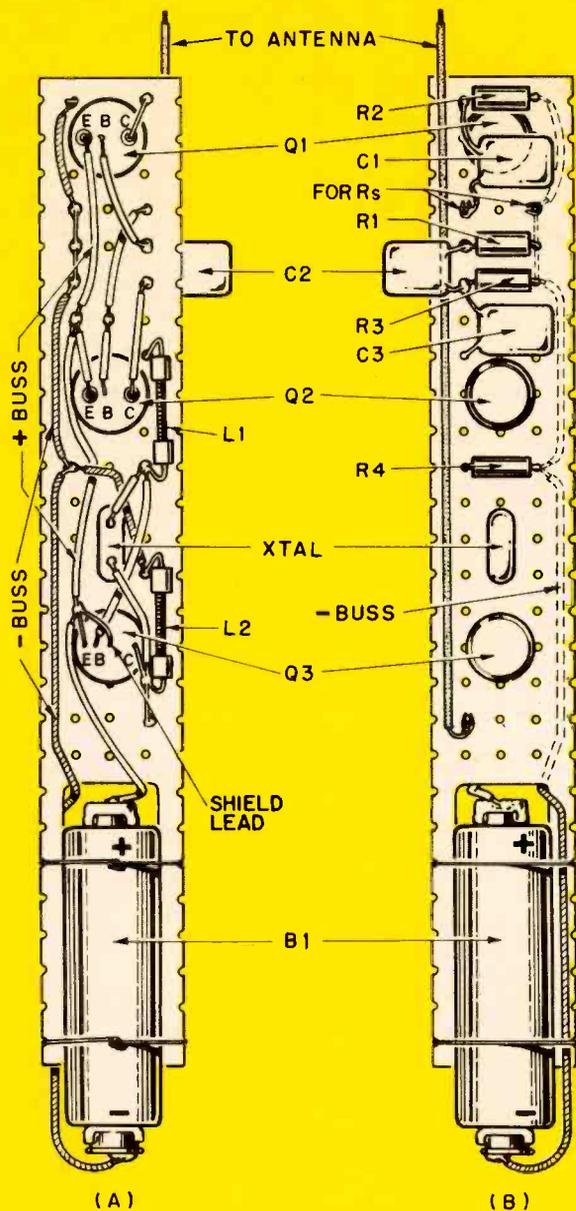

Pictorials show both sides of transmitter. C2, normally over R1-R3, is folded out for clarity. Wires hold battery in place; the negative terminal is rig's on-off switch, is unsnapped between flights as in the photo below. Picture shows photo-resistive cell as sensing element Rs. Layout here does not include C4 and L3 —miniature ceramic trimmer and RF choke which may be used to cut down spurious radiation (see the schematic). They are installed in series with lead to antenna.

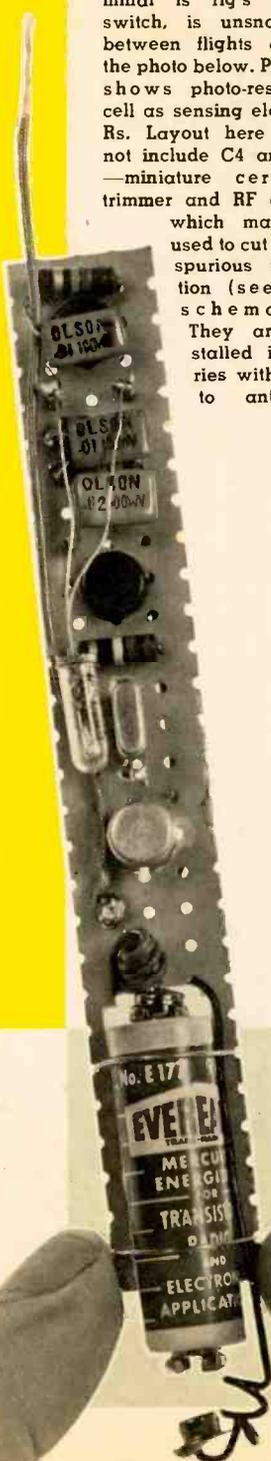

These components work in series and the trimmer is tuned to pass the CB frequency you are using.

A rocketeer should concentrate on just getting a signal from his rocket in flight before trying for meaningful data. Quantitative telemetered signals can be simply listened to, or you can tape record them for later study. To make the signals meaningful, it is first necessary to test any given sensor and plot the results (for later comparison) of


changing temperatures, light intensity, etc.

Although this transmitter may work with any type of *amateur* rocket, it was designed specifically for *model* rockets, a term denoting a certain kind of bird as defined by the National Association of Rocketry. A model rocket is made of non-metallic materials, has a parachute recovery system, weighs only a few ounces (our test rocket with engine and transmitter aboard weighed in at 2 $\frac{7}{8}$ ounces!) and uses a commercially-made rocket engine (18 types ranging in thrust up to 50 pounds are currently on the market). Model rocketeers *never* mix fuel or make their own engines. This is why they boast a perfect safety record.

For detailed information on model rocketry and facts about becoming an Association member, write to the National Association of Rocketry, Suite 1962, 11 West 42nd St., New York 36, N. Y.

In constructing the transmitter, cut and sand the perforated board so it slips inside the rocket tube snugly enough to be held in place during flight (if you get it too loose, wedge in bits of sponge rubber for a tight fit). Using the parts as templates, cut holes for the battery, the three transistors and the crystal. Carefully crack the cases off L1 and L2 (if they have cases) with a vise.

Glue Q1, Q2, Q3 and the crystal in place and solder in the other components. Have another person hold the leads with tweezers to conduct heat

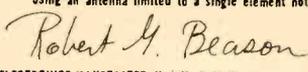CERTIFICATE OF COMPLIANCE WITH FEDERAL COMMUNICATIONS COMMISSION REGULATIONS, PART 15, PARAGRAPH 205	
ELECTRONICS ILLUSTRATED certifies that this low-power transmitting device can be expected to comply with the requirements of Paragraph 15.205 of the FCC Regulations under the following conditions:	
(a) When this device is assembled according to the diagrams and instructions published by this magazine.	
(b) When used for the purpose and in the manner indicated in the instructions.	
(c) When operated on a frequency between 26.97 and 27.27 megacycles and using an antenna limited to a single element not more than 5 feet long.	
	
ELECTRONICS ILLUSTRATED, New York, N. Y.	
dated: November 1, 1961	
I hereby certify that I have assembled and adjusted this device in strict accordance with the above.	
Owner's signature.....	Date.....

Certificate of Compliance, signed and mounted on transmitter, permits license-free operation.

away from the components. Wires are soldered directly to the crystal pins and transistor leads so exercise care to avoid heat damage.

The transmitter's antenna is an 8- or 9-inch piece of 16- or 18-gauge buss wire stuck through a hole in the nose.


When making a flight, the rocket is prepared first by putting the parachute and motor in place (information is available on this phase from the NAR). The transmitter output lead is attached to the antenna and the negative battery lead is snapped in place to start the circuit operating. The transmitter and nose plug are then inserted in the tube and the rocket is placed on the firing stand and fired.




After recovery, the negative battery terminal should be disconnected to stop the transmitter.

Simplicity of circuit makes Flyweight Transmitter easy to build but parts must be close-spaced.

PARTS LIST

Resistors: 1/2 watt or smaller, 10%
 R1, R4—220,000 ohms
 R2, R3—15,000 "
 R5—sensing element (see text)
 Capacitors: Miniatures, 10-volt or higher rating
 C1, C2—.01 mf
 C3—.02 mf
 C4—3-30 mmf ceramic trimmer (see text)
 L1, L2—1 microhenry choke
 L3—1.5 microhenry choke (see text)
 Q1, Q2—2N107 transistor or equiv.
 Q3—OC170/2N1516 or 2N384 transistor
 Misc.—piece perforated board, cut to fit tube (see text), flea clips, battery clips, etc.

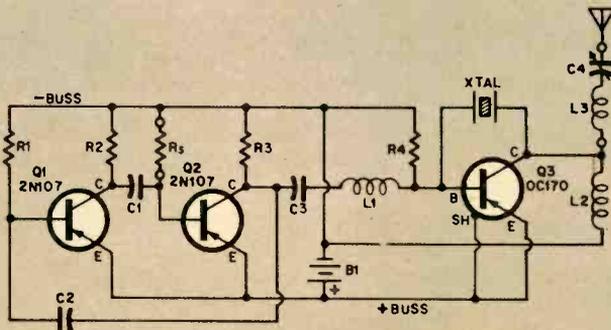

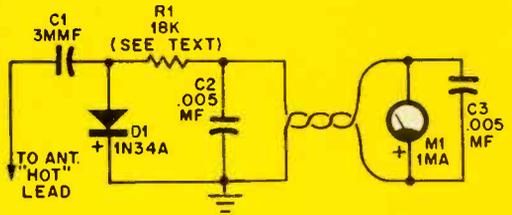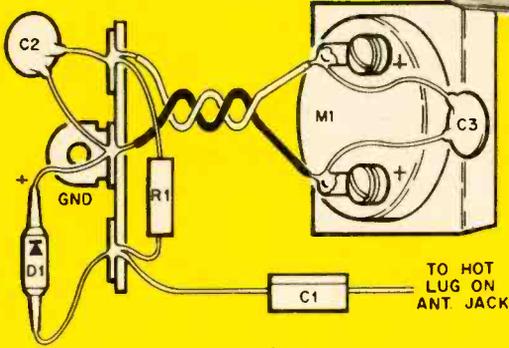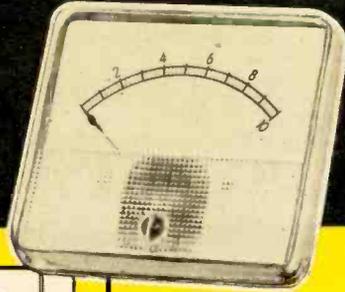

ADD A TUNE-UP METER

to peak your transmitter's RF output.

By Chet Stephens

BECAUSE a Citizens Band transmitter has limited output to begin with, it is important that every milliwatt of RF power possible be squeezed into the antenna. This can be done only if the transmitter is tuned to the antenna. Take a tip from the more expensive CB rigs. For under \$5 and about an hour's work you can build in a tune-up meter which enables you to see directly the effects of your transmitter tuning.

A sample of the power fed into the transmission line is rectified and applied to meter M1. Since the DC fed to the meter is proportional to the RF power output, you know for sure that when the meter peaks the transmitter is tuned.

Construction. Transceivers are compact and there isn't much room for extras, so a small, easy-mount meter is used. For the specified meter the mounting hole is cut with a 1½-inch chassis punch.

With R1, D1, C1 and C2 mounted

near the antenna jack, the meter leads are not critical as to length or layout. Solder a 3-lug terminal strip (center lug grounded) to the chassis near the jack. Mount all the components and wires to the terminal strip as shown in the pictorial. To protect diode D1 from heat damage, attach an alligator clip to each lead. Then solder in all the components. C3 is connected directly across the meter terminals.

Note: It is possible that a transmission line with a high Standing Wave Ratio (SWR) will cause the meter to read off-scale. If this occurs, change R1 to 36,000 ohms. If the meter reads backwards, reverse the leads.

PARTS LIST

- C1—3 mmf silver mica capacitor
- C2,C3—.005 ceramic disc "
- R1—18,000 ohm, ½ watt resistor (see text)
- D1—1N34A diode
- M1—Any 0-1 ma 1½" DC meter movement

A hand holding a screwdriver, with the tip of the screwdriver pointing towards a dashed arrow that points to a coil in a circuit diagram.

for
maximum
power

TUNE YOUR TRANSMITTER OUTPUT

By Len Buckwalter, 1W5733

FOR TOP performance, any Citizens Band transceiver must be carefully tuned and adjusted for its individual installation. Who can do this tuning and adjusting? What equipment is needed? What are the critical adjustments and how are they made?

Recent major changes in Federal Communications Commission rules now permit *anyone* to tune the transmitter output portion of a CB transceiver. (Such tuning formerly required a commercial license.) This means a CBer can make periodic adjustments to insure that his transmitter always puts out maximum power. A manufacturer can tune a transceiver's oscillator stage perfectly, but he has no way of knowing the optimum output stage settings for each antenna setup. This will vary with antenna type, location and even the body style of a car in the case of mobiles.

Finding the Adjustment Points. The transmitter's oscillator and radio-frequency (RF) output stages shown in Fig. 1 and 2 are typical of today's CB transceivers. Both oscillator and RF functions usually are served by one dual-section tube, such as a 6AW8 or 6AU8. In the crystal oscillator, the primary frequency-determining element is the crystal, but the most important item insofar as tuning is concerned is coil L1. The inductance of L1 is set by a threaded brass shaft emerging from


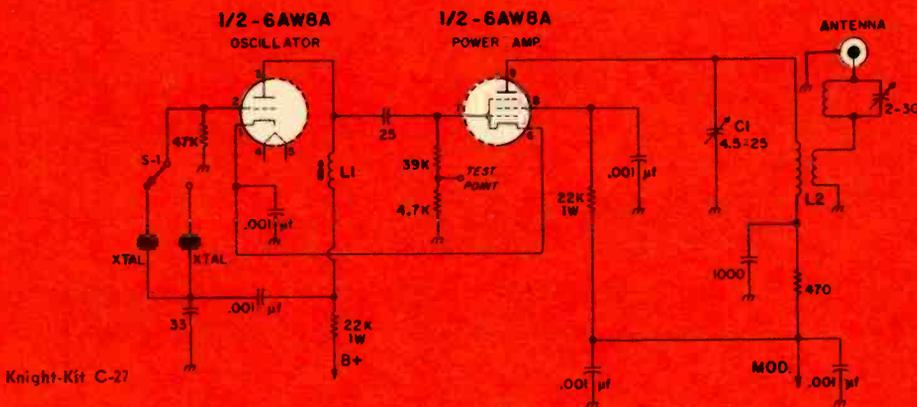
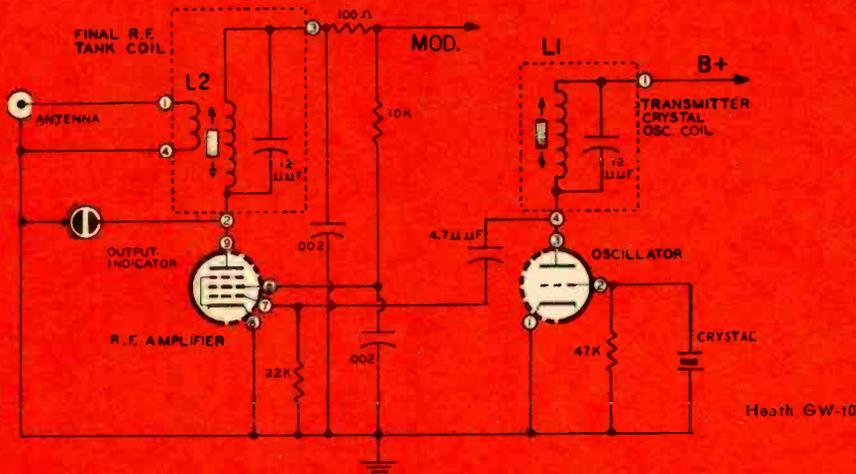


Fig. 1. Partial schematics of two typical oscillator-output stages. Note that in the C-27 a variable capacitor (C1) tunes tank coil L2 instead of the usual slug.

Fig. 2. Capacitors C6 and C7 serve as the tuning elements in an antenna matching pi-network.

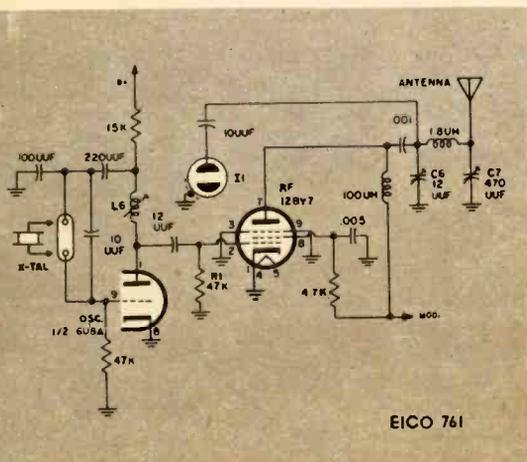

the coil form. Tampering with this component can lead to faulty operation and it is the manufacturer's job to preset and seal the oscillator components against tampering.

At the RF amplifier or output stage we find the heart of the problem. The vital component is coil L2 which has considerable influence over how much power is fed to the antenna. It is legally permissible and very much advisable to adjust L2's slug for optimum match between the transmitter and the specific antenna used.


An output circuit variation now coming into favor is the pi-network shown in Fig. 2. Its advantage over the circuits of Fig. 1 is its ability to transfer power into antennas not cut precisely for 27 mc. The pi-network has two tun-

ing adjustments, both variable capacitors. The plate capacitor (C6 in Fig. 2) is always nearest the plate of the tube (in this case, pin 7), and the antenna-loading capacitor (C7) is nearest the antenna side of the output coil.

Meters, tools, etc. Although the adjustment shaft of a transmitter output coil is usually slotted, it's best to use a recessed blade alignment tool (such as the Walsco 2519) as the slot in the soft brass shaft won't take too much abuse. If your rig has a pi-network output, tuning is accomplished with two screw-headed variable capacitors. A standard insulated screwdriver will serve here.

The next item of importance is an RF indicator. It may come as a surprise, but the standard dummy load technique using a #47 bulb as an RF indicator is fine for troubleshooting—but will *not* provide optimum match to an antenna. You need a piece of equipment known as a field-strength meter, wavemeter or radio-field indicator. They all have one important asset: they indicate the RF power *after* it is radiated from the antenna. Thus, you get a direct, although relative reading of transmitter tuning and performance.

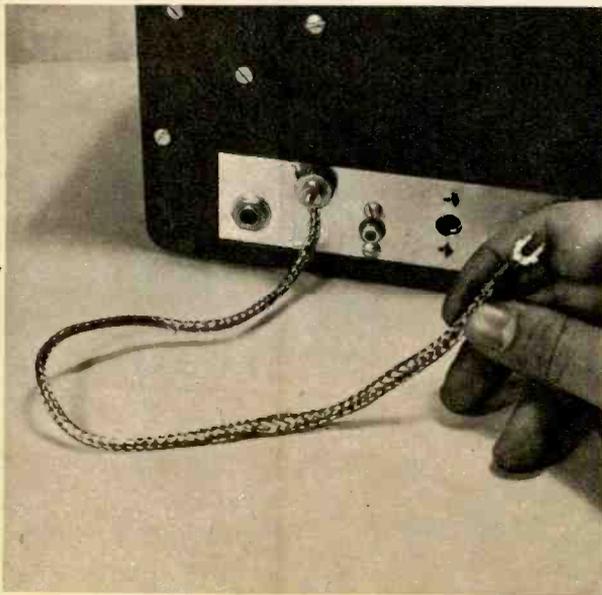Bad grounding causes poor tuning. Connect short heavy wire or braid to water pipe or car chassis.



The value of any indicating device is enhanced if you take a reference reading when the transmitter is known to be operating at maximum efficiency. Then, during routine maintenance at a later date, you have a standard of comparison. It's important that the indicator be the same distance and position relative to the antenna whenever a check reading is taken. For a particularly sensitive indicator try building EI's Transistorized Field Strength Meter (Sept. '61 issue).

Adjusting Transmitter Output. As a starting point, it's a good idea to make sure the transmitter is capable of delivering its rated power. Virtually all CB units have a jack for the insertion of a milliammeter to read the plate current of the final RF tube. Follow the instructions given in your unit's manual, but don't confuse *input* power with *output* power. The FCC allows a maximum power input of 5 watts, and this is what the milliammeter helps to determine. Since the circuit is not 100 percent efficient, output power will always be less than 5 watts, averaging from 3-3.5 watts if the tune-up is carefully performed. This assumes that you are using a standard CB antenna with the manufacturer's coaxial cable (usually 52 ohms).

Ground rules. Optimum tune-up is achieved when the transmitter and antenna are located in their final operating positions. Check the grounds, too. If the rig is installed on a table top, a heavy wire, as short as possible, must be run from the case of the unit to the nearest cold water pipe ground. A long ground wire becomes part of the radiating system and makes tuning critical and unstable.

For an under-dash mobile installation, run a heavy ground lead to the car frame. It is necessary, in most instances, to remove the transceiver case to get to the tuning adjustments. Nevertheless, try to keep all leads short and the transceiver itself as close as possible to the actual mounting position.

It takes two to tune up. Tuning a transmitter output is often a two-man job; one person at the antenna with the

[Continued on page 102]



GOOD READING

By John Milde

SCIENCE IN THE CAUSE OF MAN.
By Gerard Piel. Alfred A. Knopf,
New York. 298 pages. \$5

It is doubtful that any review can do this book full justice. On the surface, the volume is a collection of essays and lectures by Mr. Piel, editor and publisher of the *Scientific American* since 1948. But as interesting and wide-ranging as the essays themselves are, their unifying theme is even more interesting and challenging. For what Mr. Piel is after is a reconciliation of pure science with mankind's other concerns; above all, he pleads for the proper understanding and use of science in a democratic society.

Since science in this century has brought man to the point where he can, with equal ease, destroy himself or build an incredibly full, rich new world, pure science is, he says, a social science, a matter for the concern and understanding of all informed citizens. His plea for world disarmament is underscored by one of the most devastating descriptions—accomplished in less than a paragraph of well-chosen words—of an H-bomb attack ever put on paper.

There is no longer any doubting Mr. Piel's contention that science must become a fully humanistic pursuit. Neither scientists nor any other intelligent citizens can afford to stand aloof while the world drifts toward destruction, governed only by some vague law of inertia. Books like Mr. Piel's—and those of Leo Szilard—deserve an audience made up of everyone who really cares whether our world will survive and move forward.

THE BIRTH OF BROADCASTING.
By Asa Briggs. Oxford University
Press, New York and London. 415
pages. \$10

This is the first of six projected volumes on the history of broadcasting in the United Kingdom. Although the project might seem of fairly limited interest

to the American reader, it should draw the attention of at least two groups of readers. For the "radiophile," there is a nostalgic recounting of the magic of the early broadcasting era, when listeners and performers alike felt that they were involved in some kind of sorcery and didn't always believe what they heard. Secondly, in the story of the growth of the British Broadcasting Company there is a good deal to interest anyone who has wondered what American broadcasting would have been like if it had developed non-commercially. Certainly there is ample proof in this volume that *state-sponsored* broadcasting



needn't be *state-controlled*. It's doubtful that the publishers of this volume (and those to come) expect to have a best-seller on their hands, but there is a good deal of interest here for many readers.

Our photo, taken from the book, shows a broadcast from a studio in the early days of broadcasting in Britain. The big box on legs at the right is the microphone. The photo has been retouched heavily.

BASIC RADIO. By Marvin Tepper.
John F. Rider, New York. 776
pages. \$13.85

Although the six volumes involved here are available separately, they are
[Continued on page 114]



Tech Editor's

Test Bench

by Larry Klein




IF YOU'RE an electronic hobbyist, you use tools. Your workbench may include nothing more than a soldering iron, screwdriver and some pliers but if you're like me—to see a new tool is to want it. Along with the junk I've bought in past years, I've found some novel tools which, as the phrase goes, no hobbyist should be without.

Shown on this page are four tools that are unique, not too expensive . . . and they're really useful. Let me introduce them before going on with this discussion. From top to bottom they are a wire-stripper manufactured by the K. Miller Tool Co., an Adel

metal-nibbler for cutting holes in chassis and the like, Ungar desoldering tips for a soldering iron and a pair of soldering tweezers made by Oryx of England.

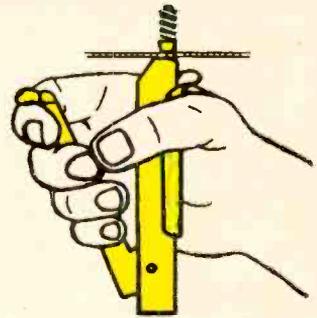The Strip Act . . . The time is long past when a pocket knife was the recommended tool for stripping wire. All kinds of inventors seemed convinced that it was a better stripper, rather than a mouse trap, that the world wanted. It started with a simple little 39¢ device that screwed on the workbench. It wasn't much for stripping wire but it sure could take a hunk out of your elbow if you leaned






on it. Of course you remember the stripper that

resembled ice tongs gone electronic. If the insulation was soft, the wire hard and your touch right you just *might* get the job done with the wire intact. Still available is a gripper-stripper that looks like a medieval torture instrument. It grips the wire, slices the insulation and slides it off the wire. To my mind, the gripper-stripper is more of a luxury, assembly-line item. I find that for the hobbyist the Miller stripper is one of the most

effective devices yet made. It is equally competent with zip-cord, coax or even 300-ohm flat line. The price is under a dollar. After long-nose and cutting pliers and your soldering gun or iron, this should be the next tool you buy.

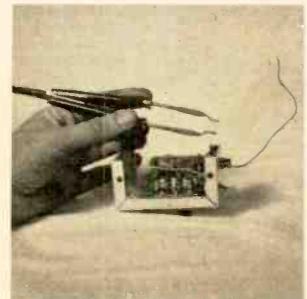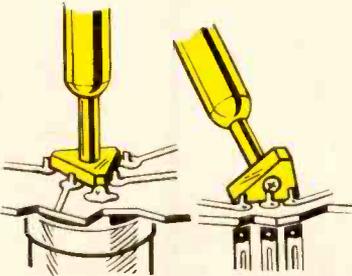Nibbler Notes . . . In the days before aluminum was common the do-it-yourselfer spent many a noisy evening sawing and chiseling steel chassis. I imagine a lot of projects were AC/DC only because of the effort of cutting out transformer mounting holes. The aluminum chassis makes hole-cutting [Continued on page 110]



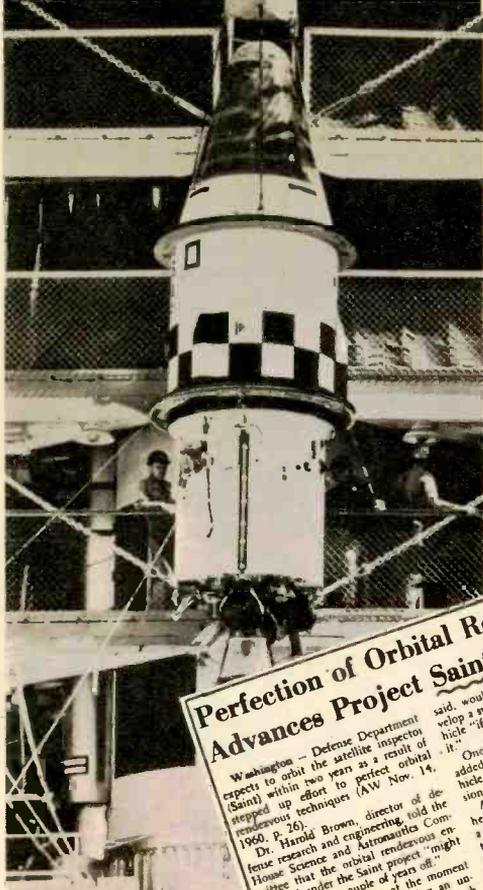

Atlas with Midas II satellite, which uses same test bed as Saint, lifts off at Cape Canaveral.

(possibly) electronic fire-power controls.

One of Saint's most difficult jobs would involve maneuvering into the right position. It could be launched near a suspicious spaceship, but then would be on its own. Best guess as to what would happen next is that the Saint would come in above and just ahead of the second satellite, then decelerate with retrorockets until it was within a few feet.

The problems involved in the rendezvous technique may be solved sooner than expected because of a new Project Mercury research program wherein two-man capsules will have the job of getting together in outer space. Data developed in this program will be available for Project Saint, of course.

Once alongside another satellite, a Saint could use its detectors to determine quickly exactly what its neighbor was carrying. This information would be transmitted to earth for a decision on whether to destroy or not. Such will be the Saint's talents that it can tell
 [Continued on page 112]

Super-secret Saint probably will look much like this Agena satellite vehicle. Trade press and newspaper clippings below show Project Saint has been mentioned occasionally in articles.

Perfection of Orbital Rendezvous Advances Project Saint Timetable

Washington — Defense Department expects to orbit the satellite inspector (Saint) within two years as a result of stepped up effort to perfect orbital rendezvous techniques (AW Nov. 14, 1960, p. 26).

Dr. Harold Brown, director of defense research and engineering, told the House Science and Astronautics Committee that the orbital rendezvous envisioned under the Saint project "might be as little as a couple of years off."

He said the military is developing an unmanned satellite to identify it but is concentrating on developing an orbiter to another satellite to identify it.

... would be used to design and develop a system for capturing a target vehicle "if you were within say a mile of it."


One possible way to do this, Row added, is to home in on the target vehicle and then reach it under vision.

Another method now being he said, is to hook onto it a line over it—much like techniques used by ship.

Asked how much of rendezvous work is like to see inverted answered \$8 million million re-

... over ... Au ... Bal ...
 ... Division for de-
 ... development.
 As of now there is no hardware ready, even for test contract to build the final stage vehicle and the inspection payload.
 The system is called "Saint." When the program was set up the letters stood for the words "satellite inspection technique." However, the Ballistics Missile Division now calls it the "Satellite Inspection System."

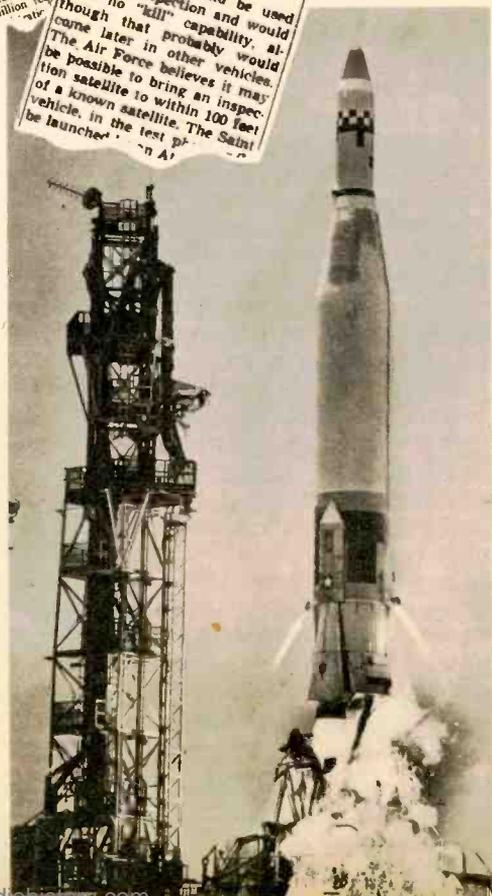For Inspection Only.
 The vehicle would be used only for inspection and would have no "kill" capability, although that probably would come later in other vehicles. The Air Force believes it may be possible to bring an inspection satellite to within 100 feet of a known satellite. The Saint be launched in the test phase.



A Stereo BOOM FOR FM

EI's build-it-yourself adaptor is a popular project.

LAST YEAR when a system of stereophonic broadcasting was approved for FM radio, some doubters wondered whether this multiplex technique would ever get off the ground. But they were silenced in a hurry. Stereo has given both FM and hi-fi a push comparable to the one stereo records provided for the high fidelity market a few years ago.

By the end of 1962 something like 200 of the country's almost-900 FM stations will be carrying at least some stereo programming. Every major population center will enjoy music-in-depth.

Virtually all equipment manufacturers have come out with adaptors for monophonic tuners, and with tuners containing built-in multiplex units. Both makers and dealers were pleasantly surprised by the way equipment sold. Adaptors and multiplex tuners have been carted home almost as fast as they were built and delivered.

EI was the first publication of any type to publish plans for a build-it-yourself adaptor, coming out with the EI Stereo FM Adaptor in our January '62 issue. The project gained wide popularity. In the first two months after publication we learned of more than 200 readers who were building the EI unit, and there were many others we did not hear about, of course.

EI's adaptor proved to be a great bargain. Through arrangements with the Audio Workshop, 732 Broadway, New York 3, N. Y., a set of five coils specially aligned for the EI unit, along with a matching pair of diodes, were offered for just \$8. (As the stereo market firmed up, the retail price of the package—without special alignment—was set at *more than \$10!*) The coils and diodes still are offered by the Audio Workshop but the price (as of March 1, 1962) was increased to \$10. It's still quite a bargain for the do-it-yourselfer. A printed cir-


cuit board for the EI adaptor is available from the Workshop at a new price of \$3.

Back copies of the January issue, containing the adaptor plans (and of the March '62 issue, carrying plans for adding a filter system), are available at 50¢ each from the EI Circulation Dept., Fawcett Building, Greenwich, Conn.

The performance figures for the EI adaptor, we have found, match those of the better commercially-made units and exceed those for many others. Channel separation at 50 and 400 cycles per second is a superb 36 db. At 5,000 cps the separation figure is 28 db and at 10 kc it is 14 db. These figures mean channel A program material at normal listening levels is not audible, or barely so, in channel B.

Distortion in the unit measures less than 0.75%. Spurious 38-kc subcarrier appearing at the output is less than -40 db. Sensitivity also proved better than we expected when we said the unit would work with any FM tuner supplying .5 volts of signal from its multiplex output jack. In later tests, the unit worked well with tuners having an output as low as .15 volts.

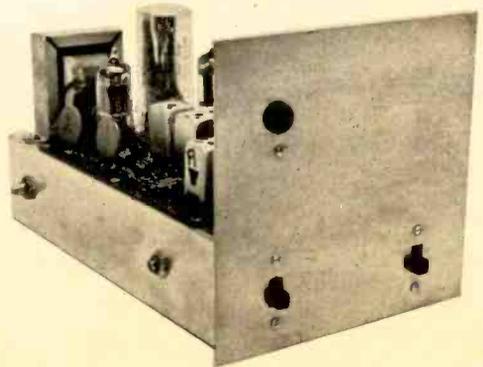EI Stereo FM Adaptor built with printed-circuit board has noise-filter and power switches on its attractive front panel, along with pilot light.




Scrambled-Call DX



Bagging 2 stations with the same call is a neat trick!

By C. M. Stanbury II

THE DISTINGUISHING mark in the world of radio is the system of call signs employed throughout the globe. According to the system, no two stations should have the same call sign. But it happens that GRK is a short-wave transmitter used by the BBC, and GRK also identifies a radio beacon at Grey Air Force Base, Tex. GSH is another BBC station . . . and an FAA weather

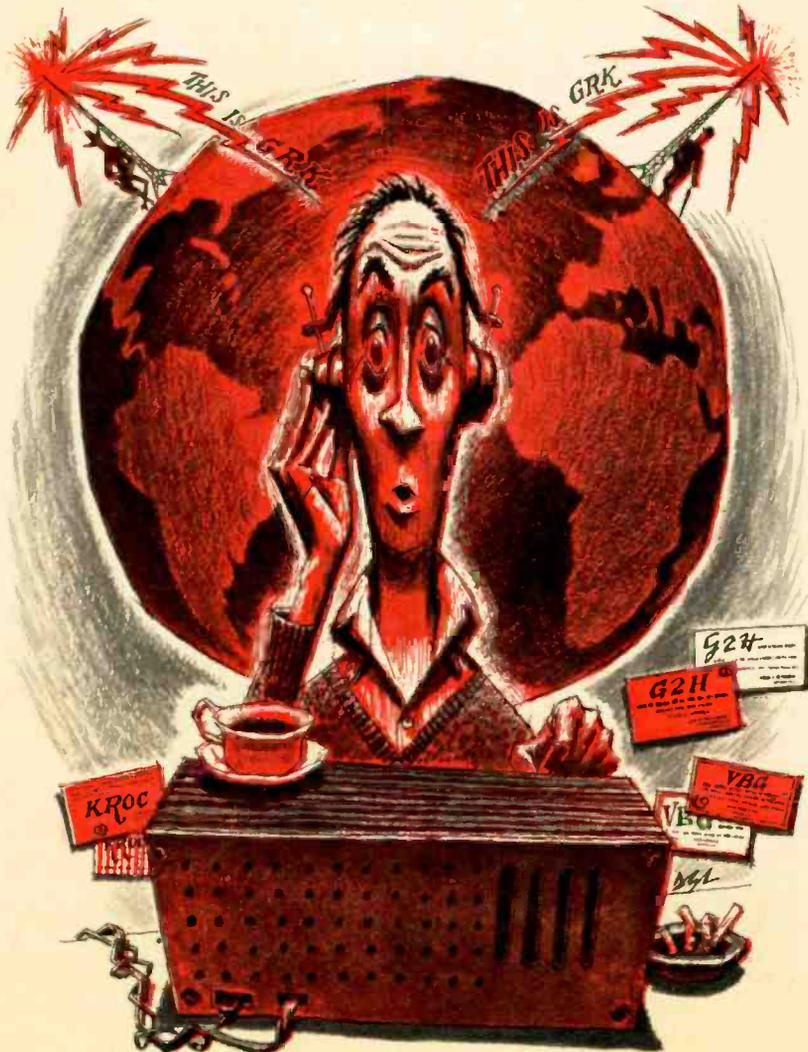station at Goshen, Ind. What happened to that call sign system? In a few words, international aeronautics threw a monkey wrench by abandoning call signs in favor of location identifiers for long-wave, VHF and UHF facilities (mainly beacon, control and weather stations). Thus, KROC is easily identified by the people who use it as an FAA control and weather station at Rochester, N. Y. To



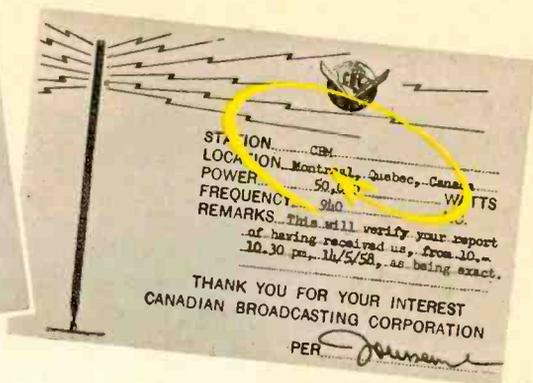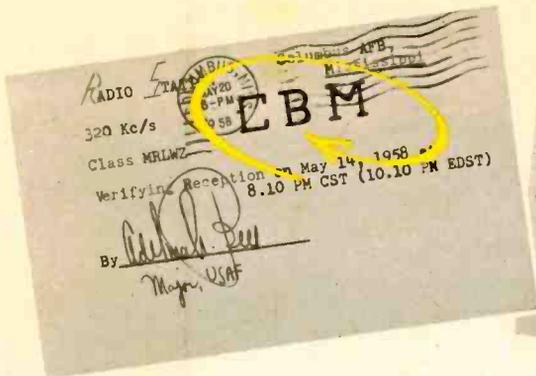

The author's QSL cards from the two CBM's verify reception on the same day and at the same hour.

make things doubly confusing, KROC also identifies a broadcast station at Rochester, Minn. Anyway, under the aeronautical system, you get a hint at a station's location along with its call sign.

There are now a dozen or so of these Siamese twins using the same call signs, and that leads to an interesting prospect for DXers—getting QSL cards from both stations in matching pairs. If you really want to make it difficult for yourself, log the stations on the same day and at the same hour (or minute). All this nets you some really rare QSL cards.

At the bottom of this page we list nine of the pairs of stations with scrambled calls that can be received best in North America (the KROC's aren't listed).

In order to bring in most aeronautical stations, you'll need a receiver that goes down into the long waves (most likely

or up to the VHF ranges. At night LW signals have a 1,000-mile east-west range and South American beacons come in clearly in the U. S. and Canada.

One of the most likely pairs to start you off is the two CBM's—a broadcaster at Montreal, Que. (940 kc), and an Air Force beacon at Columbus, Miss. (320 kc).

The secret is to zero in on one station so you know exactly where to find it and then go searching for its mate. As a general rule, try for the higher frequencies during daylight and those below 7 mc at night. Once you have a pair hooked, switch back and forth to copy enough program data for a meaningful report. In the case of beacons, note the length of time it takes to transmit the identifier and the period of silence between ID's. Some beacons and utilities require you to prepare your own QSL card for their verification.

SCRAMBLED-CALL DX GUIDE

STATION	LOCATION	FREQ. (kc)	TYPE	STATION	LOCATION	FREQ. (kc)	TYPE
CBM	Columbus AFB, Miss.	320	Range	CBM	Montreal, Que.	940	Broadcast
CLT	Charlotte, N.C.	307	Aeradio	CLT	Havana, Cuba	2760	Marine
CMH	Columbus, Ohio	391	Range	CMH	Santiago, Cuba	339 2973	Beacon Aeradio
GRF	Gray AFB, Wash.	216	Beacon	GRF	BBC, England	12095	Broadcast
GRK	Grey AFB, Tex.	323	Beacon	GRK	BBC, England	7185	Broadcast
GSH	Goshen, Ind.	320	Aeradio	GSH	BBC, England	21470	Broadcast
HOU	Houston, Tex.	332	Aeradio	HOU	David, Panama	1025	Broadcast
HYF	Hayfield Lake, Calif.	329	Beacon	HYF	Fort De France, Martinique	314 2966	Beacon Aeradio
VBG	Vandenburg AFB, Calif.	524	Beacon	VBG	Toronto, Ont.	2182	Marine



LISTENER

Notes for the short-wave listener and DXer

By C. M. Stanbury II

TOP STORIES OF 1961 . . . Probably the two outstanding DX stories of 1961 were the issuance of Vostok II QSL's by the Soviet Academy of Sciences (Astrosviet, Box 88, Moscow) and the demise of Radio Swan. Facilities of the latter have been taken over by a quasi-commercial Miami group, Radio Americas (Box 352, Miami 1). Anti-Castro commentaries (including relays from WRUL) are still prominent, backed by music, news and paying English-language programs.

Among those who heard and verified Cosmonaut Titov in Vostok II, J. Reid Meloy of Rochester, N. Y. achieved extra honors by getting confidential information from the Reds. Mr. Meloy picked up Titov using Morse code on 9019 kc, an unannounced frequency that had been noted previously but not verified by monitors of Vostok I. The 9019 frequency is just 1 kc above the channel used by the Cuban air force. If Titov was in contact with Cuba the ground station was on a different channel because the satellite's carrier remained on throughout its pass.

At any rate, Meloy and those who originally noted this frequency have helped open up new DX territory.

The Lost Cosmonaut . . . Even more spectacular space reception is reported by William Pee, British correspondent for the broadcasting organization which produces and sponsors the program, The World Tomorrow. It is heard around the world on a great variety of stations. Mr. Pee's account, as given on the program, runs as follows:

"One night just before Gagarin's flight, I turned on the wireless and tuned to the space band. First I picked up a signal which I took to be a Russian satellite. The sound was like the usual bleep-bleep, but each tone was slightly

longer than usual. The signal was cut and a man's voice began speaking in Russian. The person was agitated. It was obvious he was hysterical. I woke my wife and told her to listen. In my opinion the man we were listening to had gone out of his mind. When the news came of the Gagarin space flight we were puzzled because his flight was a day or



TOP STORY OF '61 was issuance of this QSL card for Vostok II carrying Titov (that's his photo).

two after we heard the signals."

This World Tomorrow account received wide publicity, particularly when it was broadcast by WMIE (1140 kc) in Miami, Fla.

While there has been much speculation about a "lost" spaceman who supposedly went up before Gagarin, Mr. Pee's account unfortunately is full of

[Continued on page 105]

DON'T TURN ANOTHER PAGE until you clip out this coupon!

It could be the turning point in your life!

Make More Money Soon... with Electronics!

GET 2

"PROFITS FROM ELECTRONICS"



SHOWS YOU "WHERE AND HOW"



ADDED BONUS

FREE BOOKS

"FCC PREP BOOK"

Central Technical Institute's 64-page book on electronics is packed with free information on amazing career opportunities for you in: Industrial Electronics, Automation, Radio, Color TV, Radio-TV Broadcasting, Electrical Wiring, Appliance Servicing, Communications Electronics, Radar, Missiles, Computers, Nuclear Energy, and many others! This free book tells all about Central Technical Institute's different NEW Home Study Course, "PRACTICAL ELECTRONICS." This Home Study course is so complete, it even contains instructions on how to set up and run your own

This handy 31-page book tells you all you need to know to pass the 3rd class FCC Radiotelephone examination, qualifying you to operate radio-telephone transmitting stations used by airlines, police, railroads, emergency services, etc.

electronics servicing business. FREE "PROFITS FROM ELECTRONICS" book also contains full information on Central's new Instant Kits, below. All you need do to get this valuable book is fill in your name and address on the above coupon, and MAIL IT TODAY!

GET INTO THE DYNAMIC, \$11,000,000,000 FIELD OF ELECTRONICS!
Gain Higher Income! New Prestige! A Fine Future!



BUILD CENTRAL'S NEW INSTANT KITS®

Central Technical Institute's new INSTANT KITS are designed to teach you as you build. Each inexpensive kit comes complete, ready to assemble . . . in only a few short hours of building and learning, you have a piece of test equipment that meets commercial standards, can be used in your business, or sold to customers at a profit. And Central Technical is developing new kits for you to build. See the sample selection below:



VOM Tester

Appliance Tester

Transistorized Volt-Ohmmeter Tester

4-Transistor Portable Radio

Transistor Signal Generator

Transistor Photoelectric Switch

Transistor Code Oscillator

All-Purpose 5" Oscilloscope

YOU CAN EARN EXTRA MONEY SOON!
 Study at home in spare time—no High School diploma required!

With a sincere desire to get ahead, make more money and enjoy an interesting career . . . you can earn while you learn, keep your present job, and set your own pace. Find out how much fun electronics can be! See how you can add to your income! High income, prestige, and security for you and your family can be yours! Don't let a 4c stamp stand in your way. MAIL THE ABOVE COUPON TODAY and GET YOUR 2 FREE BOOKS NOW. The little time you spend mailing this coupon may be one of the best investments you'll ever make!

MAIL THIS NOW!

Please give me my **TWO FREE BOOKS ON ELECTRONICS** and tell me how I can cash in on opportunities in electronics.

Name..... Age.....

Address.....

City..... Zone..... State.....

CENTRAL TECHNICAL INSTITUTE

1644 WYANDOTTE, DEPT. E152C

KANSAS CITY 8, MO.

Accredited Member National Home Study Council



CLIP OUT THIS COUPON, FILL IN YOUR NAME AND ADDRESS, AND MAIL TODAY FOR 2 FREE BOOKS PACKED WITH EXCITING INFORMATION ON ELECTRONICS.

NO OBLIGATION!

START A BUSINESS OF YOUR OWN OR QUALIFY FOR A HIGH PAY CAREER!

Over 50,000 successful graduates since 1931!

"THANKS to my Central training, I have my First Phone (FCC) Ticket, which gives me an advantage over my competitors. I am a franchised RCA dealer, employ a bookkeeper and usually two servicemen." R. R. "Jack" Merrill, Pryor, Oklahoma.

Superintendent of Communications for the K. C. Southern Railway Company is Central graduate Lawrence D. Fry, with 15 years of railroad communications experience. "Central is a fine school," says Mr. Fry. "I've always recommended it, and have sent several students to Central."


Field Service Representatives for the Bendix Computer Division, L. A., California, are Central graduates E. John Kempf, left, and Robert Young. Mr. Kempf was employed as a maintenance man before he became interested in radio and TV. His first project was building test equipment at home. After enrolling with Central, he began to make extra money repairing radios, auto radios, etc. "The field of Computers is expanding, and there's a real need for trained technicians," he says. "I have found the work to be both profitable and interesting!"



Central Technical Institute

1644 WYANDOTTE, KANSAS CITY 8, MISSOURI

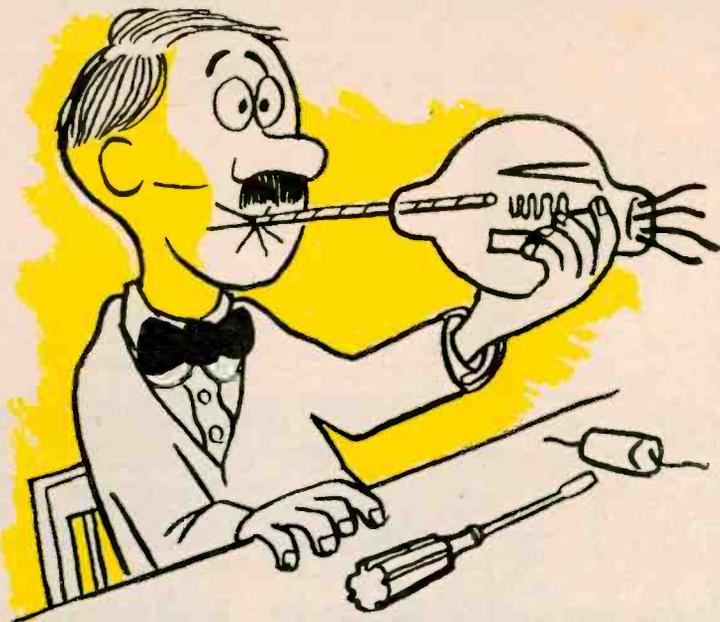RESIDENT TRAINING—Central also offers a full-time ECFD Accredited Technical Institute program at its resident school in Kansas City, Missouri. Mail the coupon at page top for information.



EI's ELECTRICITY Contest

IN THIS ISSUE and the next, EI is publishing the final two winning answers to the question, "What is electricity?" In the following issue will appear the answer given by an authority in the field. As with all other definitions

of electricity, neither the expert's nor those of our contest winners are likely to be accepted universally. But the contest has stirred our readers to interesting and constructive thought on the subject.

What is Electricity ?

" Electricity may be considered a medium by which energy can be conveyed from one location to another. The energy being conveyed is that of free electrons, which have broken away from their atoms, after reaching a certain energy level.

Robert W. Johanson
1418 N. Astor
Milwaukee 2, Wisconsin



The Ham Shack

By Robert Hertzberg, W2DJJ



HAM GROUPS . . . Amateur radio has expanded to such an extent that it now supports several varied special-interest and honorary organizations within the framework of the American Radio Relay League. Here are some of the *active* groups worth knowing about:

Quarter Century Wireless Association. Open to amateurs who have held tickets continuously for 25 years or more. Nine chapters scattered around the country. Membership up to 3,000 and still growing. Initiation fee \$3, annual dues \$2. Secretary is Ralph Barber, W2ZM, 244 Forest Ave., Locust Valley, L. I., N. Y.

Single Side Band Amateur Radio Association. For anyone interested in SSB.



Has gone from 20 members in 1951 to about 1,300 in 1962. \$3 annual fee includes excellent bi-monthly bulletin. Address: 12 Elm St., Lynbrook, L. I., N. Y.

Antique Wireless Association. With ham radio now celebrating its golden anniversary, old wireless equipment is becoming valuable to collectors. The Old Timer's Bulletin, published four times a year, is heartwarmingly nostalgic. \$3 a year. Write to Bruce Kelley, W2ICE, Main St., Holcomb, N. Y.

The QCWA celebrated its 15th anni-

versary and the 50th anniversary of ham radio by adopting a handsome gold and blue banner for display at dinner meetings. Our photo shows John DiBlasi, W2FX (left), president of the organization, and Ralph Barber, W2ZM, secretary, with the banner at a recent QCWA get-together.


New Qth . . . Butch Griswold, who achieved international fame as KØDWC (see HIGH FLYING HAM, November '61 EI), has moved East and is now K3RBA. To be formal about it, address him as Lieutenant General Francis H. Griswold, USAF, Commandant, The National War College, Washington 25, D. C.

Doggy Dog . . . Mention of K2HAM in a recent HAM SHACK moved K9AMC to call my attention to what is probably the most exclusive ham identification of all, K9DOG. It belongs to Charlie Saulka of Chicago. I wonder if he answers with a growl or just woof-woof?

Nothing for Nothing . . . Multi-element beams for the 2-meter band are so small, light and inexpensive and provide so much gain that some hams are going overboard on them. Stacking beam above beam is about the only way of making a small transmitter work like a big one but there is a hidden price to pay: the more elaborate the antenna, the sharper the signal in the aimed direction and the weaker it becomes in all other directions. This often means that while you can work station A 25 miles away when your beam is pointed that way, you can't raise station B a fraction of a mile in the opposite direction. For local rag-chewing and net operation, it is helpful to add a ground plane.

[Continued on page 104]

ELECTRONIC BRAIN

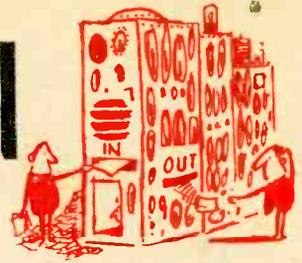

Have a question on electronics? Send it to Electronic Brain, Electronics Illustrated, 67 West 44th St., New York 36, N. Y. Enclose a stamped, self-addressed envelope for prompt reply.

Coil Inductance

Can a 2.5 millihenry RF choke be reduced to 1 millihenry by cutting it half? (National R-50, 4 sections.) If not, how could I reduce its inductance to 1 mh?

D. C. Fleming

Columbia, Mississippi

The inductance of a coil varies directly as the square of the number of turns. For example, if a coil of N turns has an inductance of, say, 3 millihenrys, then a coil of $2N$ turns (twice as many) would have an inductance of 9 millihenrys. Thus, you cannot reduce a 2.5 mh coil to 1.0 mh by cutting it in half.

If you remove one of the four banks of turns, the inductance would decrease from 2.5 mh to 1.44 mh. To bring it down to 1.0 mh, you would then have to remove about $\frac{1}{8}$ of the next bank. Of course, the best way to carry the operation through would be to take periodic readings of inductance as you remove turns, using a bridge or a Q-meter.

6-12 Volt Auto Radio Conversion

Is there a practical method by which a 6 volt car radio can be used with a 12 volt car battery without tapping to the center of the battery?

James M. Houck

Greencastle, Indiana

Electronic and auto parts supply stores stock a power resistor that is intended for this application.

The average 6 v. automobile radio of the vibrator type draws from 6 to 8 amperes depending upon the number of vacuum tubes it has. Say your radio draws 6 amperes; then, to obtain a voltage drop of 6.3 volts (from a nominal 12.6 volts to 6.3 volts), the resistance necessary would be given by:

$$R = E/I = 6.3/6 = 1.05 \text{ ohms} \\ \text{(approximately)}$$

or for an 8 ampere radio

$$R = 6.3/8 = 0.8 \text{ ohms (approx.)}$$

Since power may be found from $P = E^2/R$, then in the first case:

$$P = (6.3)^2/1.05 = 39.7/1.05 = \\ 40 \text{ watts}$$

And in the second case

$$P = (6.3)^2/0.8 = 49.6 \text{ watts}$$

If you cared to experiment, you could easily cut a low resistance like either of these from an old conical heating coil, possibly two or three inches of length measured to the correct resistance, and wrap it in a layer of sheet asbestos. We feel that we should emphasize, however, that any resistive method of cutting down voltage is a power-waster. In the case of the 6 volt auto radio, the resistor uses as much power as the radio itself.

Beatnik Oscillator

While listening on about 47 mc on a home-made regenerative receiver, I tuned my grid-dip meter to about the same frequency. I then heard regular broadcast stations. How come?

John Crawford
Chicago, Ill.

Your grid-dip meter turned your regenerative receiver into a temporary superheterodyne. Since a grid-dip meter is an oscillator and can radiate a signal over a few feet, suppose that it were producing a frequency of 48 mc while your receiver was tuned to 47 mc. If your receiver input stage has some non-linearity—as no doubt it has—it can act as a mixer. Thus, 48 mc from the grid-dip meter heterodyning a broadcast station of 1,000 kc (1 mc) would give rise to a difference frequency of 47 mc containing the original modulation of the broadcast station. Your receiver would then reproduce this in the same manner as any other signal it is tuned to.


The conversion efficiency in this kind of transfer is bound to be very low. This is the reason why this effect is not often noticed. ☉

HI-FI RECORD GUIDE

by Warren DeMotte

I DON'T KNOW what they fed the orchestra of the Royal Opera House, Covent Garden, and conductor Georg Solti, but they tear through their recording of *Gaite Parisienne* (see cut below) like a pride of lions. The gay melodies of this popular ballet never had it so brilliant, in playing or in electronic reproduction. It's somewhat bigger than life but breathlessly exhilarating. To fill up the disc, the Ballet Music from *Faust* is trotted out. Wrong word! Solti whips it into a gallop, and who would have thought there was so much life left in the familiar old tunes?

A few months ago, Angel released a splendid recording of Francis Poulenc's *Concerto for Organ, Strings and Timpani*. Now RCA Victor presents the piece done by the Boston Symphony Orchestra and organist Berj Zamkochian under the baton of Charles Munch. This is a performance of intense, tightly-knit music and a hi-fi man's delight. The deep, deep growls of the organ's low notes are guaranteed to vibrate your floorboards—if your speaker system can reproduce them.

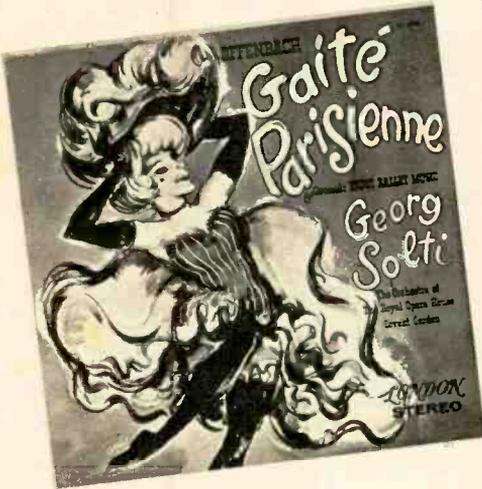

Less sensational sound, but even more impressive for its natural spaciousness, is offered in the new Ansermet recording of Manuel de Falla's ballet, *The Three-Cornered Hat*. Listening to it is like sitting in a good seat in an acoustically fine concert hall. When the timpani are struck at the opening of the piece, and the brass and castanets follow, the instrumental individuality is startling in its clarity, yet as the music progresses it is obvious that each instrument is in perfect perspective with relation to the orchestral mass. This is superior engineering and it is mighty effective when heard on a good stereo system.

The electronic engineers have their fun with something called the Electro-Sonic Orchestra under the direction of Dick Jacobs. The ensemble consists of violins, violas, cello, guitar, piano, organ, drum and two or three other instruments, but they don't sound like you'd expect them to because no open microphones were used in making the recording. Each instrument had its own contact mike (here called a transducer) with its own volume control and all of them were fed into a mixing unit before taping.

By means of the many controls, the sound of an individual instrument could be intensified, diminished, blended with its fellow instruments, made to wander from speaker to speaker or even to turn somersaults. It's weird but fascinating to hear the melodious strains of *Itsy Bitsy Teenie Weenie Yellow Polkadot Bikini*, *Volare* and *Mack the Knife* knifing through the sonic concoctions dreamed up by these imaginative sound chefs.

Easier on the ears but essentially no less a test for timbre discrimination is the recording of *The Chordettes* singing 12 hit songs from recent movies, headed by *Never on Sunday*. The four girls are joined by an orchestra conducted by Archie Bleyer and their presentations are delightful. It is a shame that the name of the skillful arranger is nowhere mentioned. [Continued on page 112]

Citizens Band Radio

Continued from page 29

feature articles and construction projects.

Citizens Band radio, now approaching its fourth birthday, has made notable advances in the last year or so. The band in a good many areas of the country, at least, has been cleaned up and now is used more and more for the purposes for which it was intended.

This is due partly to the aging process. A good many of those chatterboxes who once inhabited CB have grown up with the service and have gained respect for the rules, or perhaps they have tired of their new toy and are now enjoying other playthings.

In the early days, when the FCC seemed to be looking the other way, many CBers found immense pleasure in just chatting about their equipment. But that subject now is about talked out. Standard transceivers and antennas can be discussed only so long, and then the subject is exhausted. If someone tells you he has an HE-15, a CB-3, a GW-10 or a G-15 you're likely to know all about the rig and any discussion is pointless.

Many violations used to be due to pure ignorance. New licensees often did not understand the rules of Part 19, or made no effort to learn them. Then there was the business of experimenting to see just how far you could go. The FCC's answer, though long in coming, left no one in doubt. A flock of new rules, citations and other missives mailed directly to CBers had the effect of making everyone wary, and of quieting the band.

CB today could be said to be in the good graces of the FCC. Though anyone in Washington is quick to tell you that there are still too many problems and too many violations, federal officials generally are pleased at the progress that has been made and they have great hopes for the future.

The FCC certainly recognizes that it did sire this infant called CB and, though the child may be a bit of a brat, it cannot be disowned and no one particularly wants to bar the door. They

just wish the kid would take on some manners.

Not long ago we had an interesting talk at the FCC offices in Washington with the two men most responsible for regulation of the Citizens Band: Curtis B. Plummer, young chief of the Safety and Special Radio Services Bureau, and Ivan H. Loucks, chief of the Land Transportation Division. Mr. Loucks is the man who comes directly to grips with CB. You could call him chief administrator of the service.

What does Mr. Loucks think of the Citizens Band and the way things are going on the band?

"CB has proved to be a useful service," says the chief. "We have problems in enforcing the rules, sure. But this is only part of the FCC's overall job of enforcement. We have a good many other services to worry about, too. By and large, we do catch the worst cases on the Citizens Band, and we do write citations."

And then Mr. Loucks, talking of the future of CB, volunteered a surprising opinion.

"The FCC *wants* to see the organization of Citizens Band clubs," he said. "I'm talking about business-type clubs, not the purely social ones, which we oppose. But good CB clubs can organize in such a manner that they can help us enforce the rules through self-policing programs.

"That's why we support clubs. It's a matter of self-policing, and members can make available information to each other. Pass the word, so to speak. There can be mutual assistance for solving QRM problems. Clubs could do a great job."

Mr. Loucks went on to say that reports of violations from individuals necessarily get little attention. However, when a club with a self-policing program makes such a report, things happen.

"For instance," he said, "if a club reported a man getting drunk on Saturday night and carrying on illegally on the air, we'd take positive action."

As a general rule, CB licenses are issued to individuals and businesses. But if any club acquires a clubhouse

and has need for a station at that location, it will have no trouble getting a license, Mr. Loucks made clear.

So that is the FCC's official stand on CB clubs. EI gives its support to the formation of clubs, and elsewhere in this issue we tell you how to form your own club and how to make it worthwhile.

—R.G.B. 

Four CB Antennas

Continued from page 54

tom end of the radiator rod (Fig. 2-B). Thread this wire through the plug, slide the vertical radiator into the top end of the plug and use epoxy cement to hold it in place. Then cut the wire short and solder it to the center terminal (Fig. 2-C) of coax socket J1. Use small brass wood screws to mount J1 to the bottom of the plug, fitting it into the $\frac{5}{8}$ " well. Connect a $5\frac{1}{2}$ " length of bare stranded wire to one of J1's mounting screws (Fig. 2-D). Install the bottom skirt plug as shown in Fig. 2. Before installing the top (nose) plug and male coax connector, run the coax cable through the rotator mounting pipe, the just-installed bottom plug and the skirt. Then solder the connector on the cable and plug this connector into J1 and tighten it securely. Next, fit the top plug into the top of the skirt dressing the bare wire between the side of the plug and the wall of the tubing as in Fig. 2-D. Fasten the plug with three $\frac{5}{8}$ " wood screws through $\frac{1}{8}$ " holes drilled in the skirt as in Fig. 2. Use vinyl tape liberally around the top of the nose plug for waterproofing.

The *director* and *reflector* are made from 10' lengths of $\frac{1}{2}$ " EMT thinwall aluminum tubing. For the *director*, use extension fittings and add a 3' 5" piece of $\frac{1}{2}$ " tubing to each end of a 10' length. For the *reflector*, add a 4' 3" piece to each end of a 10' section.

The boom is a 10' length of $1\frac{1}{4}$ " EMT tubing. Drill $\frac{1}{4}$ " holes through ends of the boom to accept the U-bolt clamps for the *reflector*, *director* and the wood clamp plate for the driven element as shown.

Make the wood clamp plate of $\frac{3}{4}$ " ex-

terior grade plywood and drill the holes as in Fig. 2. Give the wood plate two coats of spar varnish for waterproofing. Mount the reflector and director on the same side of the boom as the driven element for best balance.

After the antenna is assembled, drill $\frac{3}{16}$ " holes in the director and reflector and $\frac{1}{4}$ " holes in the boom to accept the plastic clothesline struts. (Avoid changing antenna element spacing with these struts since it is critical.) Also drill $\frac{1}{8}$ " holes near the top of the *vertical* rod, the *reflector* and *director*, and thread 20-pound test monofilament nylon fishline through these holes (making a knot at each element) to reduce element vibration and changes in spacing. Use spaghetti tubing through the holes to keep the nylon line from chafing.

Standard TV antenna hardware with 2" U-bolts may be used for mounting. When buying the rotator, make sure to get one which can accommodate the $1\frac{1}{4}$ " pipe. I used the standard Channel Master automatic TV rotator with built-in 2" U-bolts.

Attach the rotator to the mast first. Then mount a stub mast on your chimney, a tripod, etc. Use a good length (3 feet or so) of sturdy cast iron pipe for the mast and no guying will be needed. Remember that the highest point on the antenna must be not more than 20 feet above an existing structure. The antenna is 18 feet. Therefore, the mast can only go 2 feet above the chimney or whatever it is mounted on.

And there you have it—a high-gain vertical beam antenna guaranteed to give your signals the long reach you want.

PARTS LIST: CB BEAM

- 10 feet—2" EMT Thinwall aluminum tubing
- 40 feet— $\frac{1}{2}$ " EMT Thinwall aluminum tubing
- 10 feet— $1\frac{1}{4}$ " EMT Thinwall aluminum tubing
- 4—extension fittings for $\frac{1}{2}$ " EMT thinwall tubing
- Available at any large electrical supply house
- 8 feet— $\frac{3}{8}$ " solid aluminum rod (Reynolds "Do-it-yourself" aluminum Item 3A)
- 4 feet— $\frac{3}{8}$ " solid aluminum rod (Reynolds "Do-it-yourself" aluminum Item 3)
- 1—coaxial cable socket receptacle (Amphenol 83-1R)
- 1—coaxial cable plug (Amphenol 83-1SP)
- 1—coaxial cable plug adapter for RG 58U (Amphenol 83-168)
- Length of RG 58U cable from antenna to CB rig
- 1—set of heavy duty TV antenna chimney mounts (or other suitable mounting hardware)
- 2—1" U-bolt assemblies
- 2— $2\frac{1}{2}$ " U-bolt assemblies (2" U-bolts may be used)
- 20 feet—plastic clothesline
- 20 feet—20 lb. test (or higher) monofilament nylon fishline
- 18 inches—iron pipe, $1\frac{1}{4}$ " OD (for bottom plug of skirt)
- Total cost of parts: about \$20

Tune Your Transmitter Output

Continued from page 83

RF indicator in hand, the other adjusting the transmitter. When shouting won't serve, some other means of communication is necessary. If an intercom or equivalent isn't available, a serviceable signalling system is easily devised with a piece of cord strung out between the two points. The fellow on the roof yanks on the cord once or twice, depending on the ups and downs of the FS meter.

In a mobile installation, try placing the indicator on the rear window shelf of the car. This will locate it within a foot or so from the whip antenna—and can make tuning a one-man job since the meter will be visible from the front seat. Meters such as the EI unit mentioned earlier are sensitive enough to provide readings while sitting atop the dashboard. Equipped with a magnetic base, they will provide constant monitoring of transmitter power.

In any transmitter tuning job, keep the FS meter the maximum distance away from the antenna. This keeps interaction between the antenna and the indicator to a minimum. It's a good idea also to hold the FS meter at arm's length to prevent body capacity from upsetting the readings.

Note that maximum energy occurs at the base of the mobile whip or ground plane antenna. On half-wave (17-odd feet long) antennas, the power will be concentrated at the mid-point, where the feedline enters. Take care that you don't burn out your FS meter by getting too close to the antenna when tuning.

Peaking the Pi. As mentioned earlier, the transceiver with the pi-network (Fig. 2) requires two adjustments and there is a definite order in which they should be made. Start by setting capacitor C6 for a peak indication on the RF indicator. Then adjust antenna capacitor C7 for a slight increase in output. Go back to C6 and repeat the peaking adjustment.

You will come to a point at which the antenna capacitor produces no further increase in output (the antenna

elements are fully loaded). When this happens, the last step *always* should be to peak reading with the plate capacitor.

Finally, adjust the 54-megacycle trap provided by most manufacturers to reduce harmonic interference to TV. The second harmonic energy of a CB transmitter (on 54 mc) is not very strong, but might disrupt reception on Channel 2. Using a TV receiver as an indicator, the trap is adjusted for minimum disturbance to the picture while someone talks into the CB microphone.

CB Corner

Continued from page 51

But this should be only an occasional, incidental activity.

Use CB radio in *any* manner if life or property are in danger.

On the subject of clubs, Gilligan says these organizations should take on the responsibility of enlightening their members on rules and regulations and institute programs of self-policing.

Still on the subject of policing, Gilligan turned to those indignant CBers who spot violations on the air and tape-record them as evidence to present to the FCC (or somebody). Monitoring and self-policing are dandy, says Gilligan, but when you record CB, ham and other such transmissions and divulge the contents to *any* third party, the FCC included, you are violating the secrecy provisions of the Communications Act. This can easily send you up the river, while the errant CBer you're copping on normally would just get a license suspension. So forget the idea of recording violations!

In the next issue we'll take a look at one of Paul Gilligan's most interesting official activities—the mobile monitoring of the Citizens Band.

A Safe Mobile Mike

Continued from page 69

microphone cable through the tubing and cap. The microphone element is set in the cap with plastic cement. Connect microphone connector PL2 to the free

end of the cable and the boom is completed. For greater comfort, the headband can be lined with a strip of felt.

The Switchbox. Push-to-talk switch SW1 mounts in a Minibox which has a large rubber suction cup (available from auto supply stores) attached to its cover. For the usual three-wire control circuits, wire SW1 as shown. For four-wire or special control circuits, section B (shown in parallel with section A) can be used separately.

Operation. Put on the boom and adjust the headband to a comfortable position. Adjust the swivel so the microphone is about one inch under your lips and tighten the swivel nut. With the microphone in this position you talk across it, avoiding sharp pops and hisses. It is also out of the line of vision.

Connect the switchbox to the microphone and transmitter. ●

Tiny Talkie

Continued from page 50

percentage and quality is maintained.

High sensitivity and stable regeneration are achieved by using the choke-loaded emitter of Q2 as both the antenna input and the oscillator of the super-regen circuit. The rate of oscillation is controlled by R3 which can be set for maximum sensitivity.

The demodulated RF signal appears across collector-load resistor R5 and is amplified by Q3. Best listening quality is obtained with a set of double ear-phones of about 2,000 ohms impedance. ●

CERTIFICATE OF COMPLIANCE WITH FEDERAL COMMUNICATIONS COMMISSION REGULATIONS, PART 15, PARAGRAPH 205

ELECTRONICS ILLUSTRATED certifies that this low-power transmitting device can be expected to comply with the requirements of Paragraph 15.205 of the FCC Regulations under the following conditions:

- (a) When this device is assembled according to the diagrams and instructions published by this magazine.
- (b) When used for the purpose and in the manner indicated in the instructions.
- (c) When operated on a frequency between 26.37 and 27.27 megacycles and using an antenna limited to a single element not more than 5 feet long.

Fred Maynard Applications Engineer

ELECTRONICS ILLUSTRATED, New York, N. Y.

dated: November 1, 1961

I hereby certify that I have assembled and adjusted this device in strict accordance with the above.

Owner's signature..... Date.....

Marketplace

Continued from page 24

And In This Corner . . . Eighteen transistors that pack a 50-watt audio output punch put the Realistic TA-208 integrated stereo amplifier in the heavy-



weight class. The unit has a full array of controls for inputs and outputs. The kit runs about \$140, the assembled unit, \$190. Radio Shack Corp., 730 Commonwealth Ave., Boston 17, Mass.

Wireless Intercom . . . The AC power line in the home or office is the transmission medium for this new Heathkit intercom. Just plug in two or more units and you're in business. The outfit is



great for baby-sitting and temporary hookups, as well as for permanent installations in offices or the home. The kit has an all-transistor circuit, a self-contained power supply, squelch circuit for full quieting and pilot lights indicating standby or talk. The model GD-51 sells for \$23. Heath, Benton Harbor, Mich.

Marketplace

Ham Shack

Wall-to-Wall Short Wave . . . The National NC-105 is a ham-SWL receiver with a tuner output jack that enables you to pipe the audio through any external amplifier and speaker system to achieve plaster-cracking sound. The set



also has a 5-inch built-in speaker. It offers continuous coverage from 550 kc through 30 mc in four bands, has band-spread tuning, S-meter, noise limiter and selectivity control. The NC-105 sells for about \$120 in a steel cabinet. A walnut enclosure costs extra. National Radio Co., Melrose 76, Mass.

Who's Got The Button? . . . Yardney Electric has introduced a unique hermetically-sealed, rechargeable silver-cadmium storage battery not much bigger than a button on your overcoat. It has a flat voltage discharge characteristic, low internal resistance and the



ability to hold up for thousands of charge/discharge cycles. The battery should excite the imagination of designers of all kinds of miniature and cordless electronic gear from pocket transceivers to portable TV sets. Yardney Electric Corp., New York 13. 

Continued from page 99

Grandfather Ticket . . . Occasionally you hear mention of an *Amateur Extra Class* license. The word *extra* implies that the ticket carries operating privileges beyond those of the General Class, but that is not true. This class was set up some years ago primarily to honor pre-World War I hams and is issued to them without examination if they can prove they held amateur licenses during or prior to April 1917.

Younger hams who have been Generals for at least two years can obtain the Extra Class document by taking a special FCC examination. This includes a code test at 20 words a minute and a written test on advanced radio theory.

Portable vs Mobile . . . Many hams seem not to make a distinction between these two types of operation. If you merely transport your equipment from your home to a summer camp, bungalow, ranch, etc., without hooking it up in the car, the temporary new installation is portable. In identifying yourself on the air you say, "This is W2DUX portable 3," on phone or, "W2DUX/3," on CW, the last number to show the call area of the temporary location. If you hook up the rig in the car and use it along the way it becomes mobile and you add that word to your call.

Incidentally, mobile means not only an automobile, but takes in anything that moves, including human beings and animals. There are many mobiles in boats and private planes, some on motorcycles and bicycles, and even a few on horseback. 

Add An S-Meter

Continued from page 75

where in this issue, the S-M will give you the equipment necessary for keeping your CB receiver tuned to peak performance. Consult your manual for the manufacturer's recommended alignment procedure.

- **Dial Calibration.** To adjust your

tuning dial, set it to the frequency of the CB Signal Generator. Now adjust receiver oscillator trimmer and/or coil slug for maximum S reading. The dial will now be in exact calibration. By inserting your transmit crystals in the Generator you can check the calibration across the dial.

● **IF Alignment.** When the dial is accurately calibrated you can then use the received signal for IF alignment. Set the S-M sensitivity control to maximum and move the generator away from the transceiver until the S-M reads between S-3 and S-7. If you do not have a CBSG use a received signal of known accuracy. Starting with the last IF transformer, the one feeding the detector, peak the IF's for maximum S reading. Next, tune in a signal in the center of the band (channels 9-12) and peak the RF coils for maximum S reading.

● **Antenna Tuning.** Another good use for the S-M is in assisting the tuning of another station's antenna, particularly beams.

Theory. Meter movement M1 is connected as the indicator of a four-arm (Wheatstone) bridge. One arm of the bridge is V1. To balance the bridge for a no-signal condition, V1's bias is set with R5 so that V1's DC resistance is in the same ratio to R1 as R4 is to R2. When a received signal develops negative AVC voltage, V1's DC resistance increases, thus unbalancing the bridge and causing current to flow through the meter. The very high input impedance of V1 eliminates any possibility of loading down the AVC Line. ⚡

Service Made Easy

Continued from page 73

check good, turn on the transceiver and feed the audio signal to the input grid (Y) of V1. If the output stage is operating properly, a clean signal will be heard in the speaker. If the tone is distorted, disconnect the Y end of C1 and check for leakage. The best way to do this is to connect the leads of your VOM between the free end of C1 and ground. With the set on, the presence of positive voltage at C1 indicates leakage and that

replacement is in order. A positive voltage at Y (with C1 still disconnected) may indicate a gassy V1. Check this by replacing V1 with a good tube.

Next, move the AF signal lead to the plate of V2 (W). If the tone is not heard, coupling capacitor C1 probably is open. Trace the signal back to the grid of V2 and other audio amplifiers which may precede V2. Failure of the tone to be heard from any grid indicates the defective stage. The audio section can be checked right back to the volume control and detector. Resistance and voltage measurements will pin-point the defective component.

No Reception; Modulation Okay. Since the modulation check indicated the audio section is working, the trouble must be *before* the audio amplifier.

Set your RF generator to provide a modulated RF signal at the IF frequency indicated in the transceiver manual. Connect the generator's RF ground lead to the transceiver chassis and the RF hot lead in series with a .001 mf, high-voltage (500 or above) disc capacitor to the grid (X) of the last IF amplifier tube (Fig. 4). With the generator's RF output control and the transceiver's volume control both set to maximum, a loud tone in the speaker indicates proper operation of the IF stage. If your transceiver has two IF stages perform the same test on the first IF amplifier, but reduce the RF input signal to prevent overloading the stage. The IF section can be checked as far back as the grid (Y) of the mixer tube by the same technique.

To test the mixer, connect the generator's RF lead to Y through a 5 mmf capacitor.

If the tone is heard, even though reduced in volume, it means that the IF strip is okay.

Next month we'll continue with this series, tackling the receiver oscillator section. ⚡

The Listener

Continued from page 92

flaws. Besides being indefinite about the date, Mr. Pee describes the satellite's

signal as a bleep-bleep, and Russia has not used that type of transmission since the first Sputniks. The signals from the Vostoks and the experimental space-ships immediately preceding them resembled a click with periods of a superimposed tone (A2) lasting much longer than a single bleep. The Soviets also use separate channels for voice (or code) transmissions and when not in use, there is no signal at all.

Language Problem . . . The great barrier for DXers who sample foreign utility stations is language. Many foreign broadcasters have English programs but marine stations, police, etc., invariably communicate in their own tongue. These stations can be reported and verified but their actual operations remain a mystery for many because of the language problem.

One channel which overcomes this difficulty is the 2752 kc ship-to-ship frequency for the Gulf of Mexico, the Caribbean and Western South America. Vessels are of Central American or West Indian registry and all use English. This is the place to listen for inside news on hurricanes and other disasters, pro- and anti-Castro doings and other off-trail stories. Such ships as the Malinda, Nespas and KirkDeal were the first news sources for the Belize hurricane disaster late last year (the British Honduras Broadcasting System, 830 and 3300 kc, was destroyed).

Power here averages 75 watts or less but on what is normally a clear channel reception is fair throughout North America. Then 2752 kc has its share of DX, too. Stake Bay Radio on Cayman Brac, 175 miles west of Jamaica, is a real catch because the Caymans are without a broadcast station and the aeradio at Grand Cayman is seldom heard at a distance. Best time to try for Stake Bay (or any other transmitter on this channel) is shortly after sunset.

Stake Bay is operated by R. B. Kirkconnell & Bro., with C. G. Kirkconnell as officer-in-charge. Unlike many operators on this frequency, he verifies readily. This same firm also operates small motor vessels bearing names beginning with Kirk.

Easy Time Conversion

THE fact that most international broadcasting stations and certain other communications media use Greenwich Mean Time (GMT) gives them a common time reference and helps keep things running smoothly on the airwaves. But it's not particularly helpful to some Short-Wave Listener out in the boondocks (or on Park Avenue) who merely wants to know the time *by his clock* when a certain program from Berlin or Melbourne or Peking comes on the air. Too often the SWLer depends on finger-counting or tries to figure out in his head what time it is in Greenwich, England, when his own clock reads—say, 7 o'clock in the evening. The handy chart we present here will make such calculations easy for DXers anywhere in the United States and the more populous parts of Canada. And it works either way—GMT-to-local time or vice versa. Just add an hour during Daylight Saving Time.—Ken Boord

ET TIME CONVERSION CHART

GMT	EST	CST	MST	PST
0000	1900	1800	1700	1600
0100	2000	1900	1800	1700
0200	2100	2000	1900	1800
0300	2200	2100	2000	1900
0400	2300	2200	2100	2000
0500	0000	2300	2200	2100
0600	0100	0000	2300	2200
0700	0200	0100	0000	2300
0800	0300	0200	0100	0000
0900	0400	0300	0200	0100
1000	0500	0400	0300	0200
1100	0600	0500	0400	0300
1200	0700	0600	0500	0400
1300	0800	0700	0600	0500
1400	0900	0800	0700	0600
1500	1000	0900	0800	0700
1600	1100	1000	0900	0800
1700	1200	1100	1000	0900
1800	1300	1200	1100	1000
1900	1400	1300	1200	1100
2000	1500	1400	1300	1200
2100	1600	1500	1400	1300
2200	1700	1600	1500	1400
2300	1800	1700	1600	1500

are you standing still in electronics while this man advances?

Find out why—and do something about it—if you have the ambition to want a career instead of just a job.

LET'S LOOK AT THE FACTS. There's something wonderful about knowing how a circuit works or what a filter capacitor does. If you've ever fixed a TV set, built a radio or used a voltmeter, you've tasted the thrills of electronics.

This excitement may have led you to a job in electronics. But the glamour fades if you are stuck in the same job year after year. You'll be bored with routine and unhappy about prospects for future earnings. You'll discover, as have many men, that simply working in electronics does not assure a good future.

If electronics is the "field of opportunity," how is this possible? No question about it, electronics offers many opportunities, but only to qualified men. In any career field, it is how much you know that counts. This is particularly true in the fast moving field of electronics. The man without thorough technical education doesn't advance. Even men with intensive military technical training find their careers can be limited in civilian electronics.

ADVANCED TECHNICAL KNOWLEDGE IS THE KEY to success in electronics. If you have a practical knowledge of current engineering developments, if you understand "why" as well as "how," you have what employers want and pay for. With such qualifications, you can expect to move ahead.

CREI OFFERS YOU, for study at home, a complete program in electronic engineering technology designed to prepare you for a rewarding, well-paying career in electronics. CREI equips you with a practical working knowledge of advanced and up-to-date electronic developments that will put you on the level of specialization where men are most in demand.

CREI MEN LIKE MEARLE MARTIN, JR. hold positions as associate engineers, engineering aides, field engineers, project engineers and technical representatives.


WHEN YOU ENROLL IN A CREI HOME STUDY PROGRAM, you study courses to which a number of today's leading engineers and scientists have made substantial contributions. You are guided and assisted by CREI's staff of experienced instructors. You study texts that are specifically prepared for home study use.

Through CREI, you have a choice of programs covering every field of electronics:

RADAR • COMPUTERS • SERVOMECHANISMS • INSTRUMENTATION • AERONAUTICAL AND NAVIGATIONAL • COMMUNICATIONS • TELEVISION • AUTOMATION AND INDUSTRIAL ENGINEERING TECHNOLOGY • NUCLEAR ENGINEERING TECHNOLOGY

Programs are available for men, such as engineers, who already have extensive technical knowledge, as well as for men with limited technical training or experience.

THE HIGH CALIBRE OF A CREI HOME STUDY EDUCATION is attested to by America's biggest corporations, where CREI students and alumni attain positions ranging from engineering technicians to top officials. Such companies are National Broadcasting Company, Pan American Airways, Federal Electric Corporation, The Martin Company, Northwest Telephone Company, Mackay Radio, Florida Power and Light and many others. They not only recognize CREI Home Study educational qualifications but often pay all or part of CREI tuition for their employees.

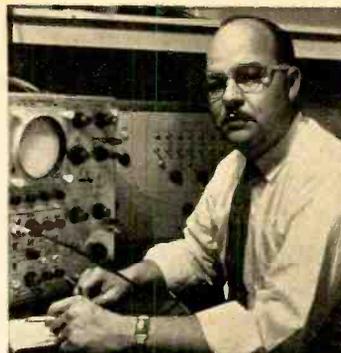

CREI graduate Mearle Martin, Jr. has progressed from Junior Technician to licensed Senior Engineer. He is now Field Support Manager, Marketing Division of Tektronix, Inc., Portland, Oregon.

CREI HOME STUDY PROGRAMS are the product of 35 years of experience. Each program has been developed with the same painstaking skill and care that CREI put into its electronics courses for the Army Signal Corps, its special radio technician courses for the Navy, and its group training programs for leading aviation and electronics companies. For those who can attend classes in person, CREI maintains a Residence School in Washington, D. C.

YOU CAN QUALIFY for a CREI Program, if you have basic knowledge of radio or electronics and are a high school graduate or the equivalent. If you meet these qualifications, write for FREE 58-page book describing CREI Programs and career opportunities in advanced electronic engineering technology. Use coupon below, or write to: The Capitol Radio Engineering Institute, Dept. 1705-K, 3224 Sixteenth St., N. W., Washington 10, D. C.

Mail coupon today for FREE 58-page book

THE CAPITOL RADIO ENGINEERING INSTITUTE

Founded 1927

Dept. 1705-K, 3224 Sixteenth St., N.W., Washington 10, D.C.

Please send me details of CREI Home Study Programs and Free Book, "Your Future in Electronics and Nuclear Engineering Technology." My qualifications are noted to obtain immediate service.

CHECK Electronic Engineering Technology Nuclear Engineering Technology
FIELD OF GREATEST INTEREST: Servo and Computer Engineering Automation and Industrial Electronic Engineering Technology
 Aero and Navigational Engineering Technology

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Employed by _____

Type of present work _____

Education: Years High School _____ Other _____

Electronics Experience _____

Check: Home Study Residence School G.I. Bill # 23



Put your money in quality parts . . . get

HEATH

THE MOST ADVANCED STEREO TUNER KIT AVAILABLE



Here's the kit tuner you've asked for, the Heathkit AJ-41! AM, FM or Stereo FM Multiplex. Self-contained with Multiplex Adaptor built-in! New FM squelch circuit hushes between-station noise. Stereo Indicator light shows when FM station is broadcasting stereo. Separate tuning meters for AM & FM. Broad-band circuitry. Cathode follower outputs. Preassembled tuner, prealigned coils, circuit boards.

Kit AJ-41, no money down, \$11 mo. . . \$119.95
Assembled AJW-41, \$18 mo. . . \$189.95

Heathkit — always first with the finest, guarantees success with any of these new kits



New 9-transistor CITIZENS BAND WALKIE - TALKIE

Superheterodyne receiver—crystal-controlled transmitter; built-in squelch and noise-limiter; portable-battery powered; 1-3 mile operating range; easy circuit board assembly. 2 lbs. Kit GW-21 . . . \$44.95 each, \$84.95 a pair



The World at your Fingertips—only \$24.95 —Covers 140 kc to 18 mc in 4 bands to receive aircraft, broadcast, amateur, police, and foreign stations. Regen. circuit; transformer isolated.

Kit GR-81, no money down, \$5 mo. \$24.95



Powerful SSB mobile AMATEUR TRANSMITTER and RECEIVER—Complete SSB facilities! 90 watts, 80 through 10. Loaded with extras for top performance —easy assembly—convenient operation! Kit HX-20 . . . \$199.95; HR-20 . . . \$134.50
GH-12 Mike Illustrated . . . \$6.95



New miniature HI-FI SPEAKER SYSTEM

—AS-81 Series—65-14,500 cps response from 6" woofer and 3" tweeter in factory assembled cabinet just 10 3/4" W x 6 1/2" H x 6 3/4" D. Available wal., mahog. or unfin. from \$17.50



Step saving WIRELESS INTERCOM—No more connecting wires between stations. just plug in nearest outlet, works with units on same power line. All transistor circuit; built-in AC power supply. "All-master" system. any station may originate a call. Standby squelch circuit. Overload diode. Indicator lights. Beige color.

Kit GD-51-2 (pair) no money down, \$5 mo. \$45.90




ELECTRONIC TACHOMETER for In-boards, outboards or cars—Transistor circuit; dual range, 0-4000 & 0-8000 rpm, switch-selected; usable with coil-distributor or magneto systems; price to be announced.

better performance, more satisfaction with

KIT[®]



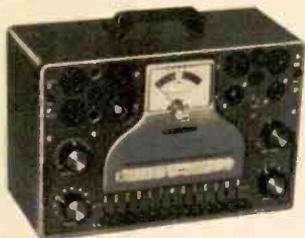**TWO NEW HEATHKIT
TUBE TESTERS AND MODERN
TUBE DATA SUBSCRIPTION SERVICE**



TUBE CHECKER IT-21: Successor to famous Heathkit TC-3. Tests all tube types including new compactron, nuvistor, novar and 10-pin types! Built-in roll chart. Individual tube element switches. Tests for quality, shorts, leakage, open elements and continuity. **\$44.95**



MUTUAL CONDUCTANCE TUBE TESTER TT-1A: Deluxe tube testing facilities! Includes adapter in lid for testing new compactron, nuvistor, novar and 10-pin tube types. Indicates Gm to 24,000 microhoms. Constant current heater supplies. Ultra-sensitive grid current test. Direct reading ohmmeter leakage test. Built-in calibration circuit & roll chart. Professional-quality throughout. **\$149.95**

ADAPTER KIT TTA-1-1: Converts earlier model TT-1 to TT-1A. Consists of new cabinet lid, sockets and selector switches and necessary tube test data. **\$14.95**

NEW TUBE SUBSCRIPTION DATA SERVICE: Up-to-date supplements on all new tube types will be automatically mailed quarterly to all subscribers. New roll chart mailed annually. A valuable service to past and present Heathkit tube checker owners! State your tube checker model upon ordering.

TC-3 series \$1.50 per year, TT-1 series \$2.50 per year.



**WORLD'S BIGGEST
KIT CATALOG—FREE**

Use the coupon opposite to send for your free copy of the new 1962 Heathkit catalog. It's the world's biggest catalog devoted to electronic kits. 100 pages, over 250 different kits, with complete descriptions, schematics, big photographs, and full specifications. Send for yours now!



HEATH COMPANY
Benton Harbor 39, Michigan

Yes, send me my free 1962 Heathkit catalog

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Order direct by mail or see your Heathkit dealer.

Ship Parcel Post Express C.O.D. Best Way

Ordering instructions: Fill out the order blank. Include charges for parcel post according to weights shown. Express orders shipped delivery charges collect. All prices F. O. B. Benton Harbor, Mich. A 20% deposit is required on all C.O.D. orders. Prices subject to change without notice. Dealer and export prices slightly higher.

ITEM	MODEL NO.	PRICE

FEEDBACK

Tech Editor's Test Bench

Continued from page 6

served more attention was excellent. I'm an ARM and I'd like to see more about this hobby.

David G. Lee
San Francisco, Calif.

As far as ARM's are concerned, I found Mr. Duignan's letter very interesting. I think it is a special challenge to pick up radio amateurs in foreign countries.

Bruce P. Tio
Southport, Conn.

Yes, I'm for the ARM's. I've had good luck as an ARM recently, picking up KC4, KR6, KG6 and KH6 transmissions.

Roger W. Byrd
San Francisco, Calif.

EI was overwhelmed by the response to Reader Duignan's letter. We're convinced we should do an article on the subject. It will appear in a future EI.

● Tape Tricks

Why not publish an article on building a small, portable tape recorder?

Mark Davis
Levittown, N. Y.

Unfortunately, Mark, the first piece of equipment you need to build a tape recorder is a precision lathe. The second requirement is considerable knowledge of and interest in metal machining. The large amount of mechanical (vs electronic) work required puts such a project outside the interests of most of our readers.

● Not So Tony

I read in your November '61 issue about building a Tone Call/Squelch unit for CB. It happens that I have here some commercially-made tone call-squelches I paid almost \$50 for and they DO NOT work. Perhaps I have the wrong serviceman or something.

Clyde Stevens, 17W5764
Grand Island, Neb.

Not the wrong serviceman, Clyde. Just the wrong tone call-squelch. You should try EI's unit. It WORKS.

Continued from page 85

easy, particularly if you have Greenlee punches. However, there are some jobs even punches won't handle. When the cutout must be large (as for a subchassis assembly) or must have squared-off corners, it's still difficult to do a neat job. Difficult, that is, unless you happen to own an Adel nibbler.

This nibbler is one of those rare tools that does exactly what you hope it will. It takes a nice square bite out of any aluminum chassis up to 16 gauge and steel up to 18 gauge. Transformer mounting holes, for example, can be made by drilling a $\frac{7}{16}$ " pilot hole. Then, with a squeeze per bite, you nibble away. As a bonus, the nibbler turns out to be ideal for shaping perforated boards, too.

Solder, Sweat and Tears . . . At one time almost all electronic parts were coaxial—that is, their two leads came out of the center of their opposite ends. The exceptions were components that normally mounted above-chassis, such as can filter capacitors, tubes, etc. Now, in the days of printed circuits, almost all components find themselves in an above-chassis position.

What has this to do with soldering? If you have occasion to remove a defective printed circuit board tube socket, you'll find yourself with an interesting problem. In order to get the socket off the board you'll have to unsolder all nine pins (and perhaps the center shield) *simultaneously*. An insoluble problem? Not if you have an Ungar pencil iron and a set of their screw-in desoldering tips. These special tips are a dream for printed board work and can solve once unsolderable problems.

Another interesting solder tool (I don't want to call it an iron) is made by the Oryx Company of England. They call them soldering tweezers. Although these tweezers are specialized, if miniature work is your meat you might take a look at them. The pair I have operates from the 6-volt winding of a filament transformer and develops considerable heat at the joint.

LAFAYETTE is America's Citizens Band Headquarters



Ship to Shore
HE-29A



On the Farm



Construction Work



**NO LICENSES,
TESTS OR
AGE LIMITS**

9 -TRANSISTOR PORTABLE CITIZENS BAND "WALKIE TALKIE" T.M.

39.95
2 for 78.88
NO MONEY DOWN

**PORTABLE—
POCKET SIZE**
Only
6 3/8 x 3 1/4 x 1 5/8"



- Completely Wired—Ready to Operate • Fully Transistorized—9 Transistors plus 1 Diode • Uses Inexpensive Penlight Batteries
 - No License, Tests or Age Limits • Comes with Leather Carrying Case, Earphone, Antenna, Batteries and Crystals
- As simple and easy to use as the telephone—and twice as handy. Receives and transmits up to 1.5 miles under average conditions. Weighs only 18-oz. and slips into your pocket. Push-to-talk button operates built-in speaker as sensitive microphone.

NEW LAFAYETTE HE-20B Citizens Band TRANSCEIVER

Now With 8 Crystal Controlled Channels

- Pi-Network for Greater Power Output • Calibrated "S" Meter • Series Gate Noise Limiter • Tuneable Superhet Receiver over all 23 Channels • 8 Crystal-Controlled Transmit Positions • 8 Crystal-Controlled Receive Positions • Dependable Push-To-Talk Ceramic Microphone & Relay • Illuminated Dial • Built-in 12-Volt Power Supply • Complete with Matched Crystals for Channel 9

109⁵⁰
**NO MONEY
DOWN**



Made in U.S.A.

NEW LAFAYETTE HE-15B Citizens Band TRANSCEIVER



**ONLY
59⁵⁰**
**NO MONEY
DOWN**

- Completely Wired—Not A Kit • Now with 8 Crystal Controlled Transmitting Positions • Tuneable Receiver Over Full 23 Channels
- High Output Ceramic Microphone • Complete with Transmitting Crystal for Channel 9

A compact, precision transmitter and receiver covering up to a 20 mile or more radius, depending upon conditions. The HE-15B features an effective full-wave variable noise limiter, planetary vernier tuning. RF and microphone jack on front panel, 12 tube performance from 4 dual-function tubes, 2 single-function tubes, 2 rectifiers.

HE-19	Telescoping Whip Antenna	Net 3.95
HE-16W	Power Supply for 12 Volts	Net 10.95
HE-18W	Power Supply for 6 Volts	Net 10.95

LAFAYETTE ALL-IN-ONE CITIZENS BAND MOBILE ANTENNA

The Scoop Buy for
Citizens Band Mobiles

HE-800WX

6.95

- Chrome Swivel Base • Stainless Steel Spring • 102 1/2" Stainless Steel Whip for Optimum 11-Meter Performance
- Chrome swivel ball mount base designed for mounting on any surface. Stainless steel spring holds rod in properly adjusted position and prevents rod damage from shocks and blows. Stainless steel whip for maximum resiliency and strength.



LAFAYETTE RADIO

SEND FOR LAFAYETTE'S
NEW 1962 CATALOG

FREE!

Catalog 620
348 Giant
Size Pages



OTHER LOCATIONS

- JAMAICA, N. Y.
165-08 Liberty Avenue
- NEW YORK, N. Y.
100 6th Avenue
- BRONX, N. Y.
542 E. Fordham Rd.
- BOSTON, MASS.
110 Federal Street
- NEWARK, N. J.
24 Central Avenue
- PLAINFIELD, N. J.
139 W. 2nd Street
- PARAMUS, N. J.
182 Route 17

LAFAYETTE RADIO, DEPT. EIE-2
P.O. BOX 10,
SYOSSET, L. I., N. Y.

Send FREE 1962 Catalog 620 featuring
the full line of Lafayette C.B. Equipment

\$ _____ Enclosed for Stock No. _____

Name _____

Address _____

City _____ Zone _____ State _____

ATTENTION

ALL BUILDERS, EXPERIMENTERS & CITIZENS BAND ENTHUSIASTS

Don't miss the Citizens Band Signal Generator construction project in this issue.

Build this exciting project for only \$7.78. All parts available under stock number SP-254 from . . .

LAFAYETTE RADIO

Mail Order & Sales Center

111 Jericho Turnpike
Syosset, L. I., New York

Over 15 Years
Selling Electron Tubes
Direct to You . . .
At Low, Low Prices!

RAD-TEL'S
BRAND NEW TUBES
UP TO 75% OFF

One Year Guarantee — Fast One Day Service

FREE! Trouble Shooting Guide!
Tube and parts circular!
Send today!!

Over 500 types in stock at all times.

Not affiliated with any other mail order tube company.

RAD-TEL TUBE CO.

DEPT. EI-562 55 CHAMBERS STREET, NEWARK 5, N. J.

America's Super Secret Satellite

Continued from page 88

whether a satellite is carrying a nuclear bomb and whether the bomb is armed.

The detection system for an A- or H-bomb would involve the inter-relationship of mass and weight and their resistance to change in motion. The heavier a body is, the more it resists change. The Saint, moving beside another satellite, would simply fire jets of gas against its neighbor. From the reaction of the second body, it could determine whether a weapon was aboard.

In the basic orbital tests the Saint components were mounted in the Agena satellite vehicle. The early shots were in the Discoverer series from Point Arguello, Calif., using Thor boosters. (The Agena vehicle, carrying different equipment, also was used as a test bed for the Midas satellite shots.)

The outside physical shape of the final Saint (pictured in our lead illustration) probably will be roughly the same as the Agena B vehicle, a new and larger version of the first Agena. Advanced test shots are likely to use a combination of the Agena B and the Atlas D booster. The Atlas D may give way to the powerful Titan II rocket for final rendezvous tests.

Hi-Fi Record Guide

Continued from page 99

He deserves credit for much of the good taste and musicianship displayed.

Another view of the movies appears in 50 Years of Movie Music from Flickers to Wide Screen, produced by Robert Franklin and directed by Jack Shaindlin. The cumbersome title is no misnomer. From the tinny piano accompaniments of the flickers of yore, with their characteristic music for the chase, slapstick and newsreels, through theme songs like Charmaine to the integrated score for The Man with the Golden Arm—this is the history of movie music, imaginatively set forth in the stereo sound of today.

When Lester Young died three years

TRAIN WITH THE LEADER



FOR YOUR FCC LICENSE

Prepare for your First Class FCC License through NRI's special and up-to-date FCC home-study course. Qualify for better paying jobs and growing opportunities open to you with your FCC "Ticket." Train with NRI—oldest and largest school of its kind. **MAIL NOW** ➔

National Radio Institute
Washington 16, D. C.

BEK

Send me information on NRI's special FCC License training. (No representative will call. PLEASE PRINT)

Name Age

Address

City Zone ... State

Accredited Member National Home Study Council

ago, a giant passed from the jazz scene. Fortunately, he was recorded extensively and from his many discs eight of his big numbers have now been put on one record and released as *The Essential Lester Young*. Undoubtedly, this is the most effective introduction to the work of the great tenor saxophonist. The 12-minute version of *Lester Leaps In* is alone a textbook of his individual style.

If the *Twist* is still with us when these lines are published, then *Doin' the Twist*, with Louis Prima, Sam Butera and the Witnesses, will surely be pounding along. A lot of energy has been expended in these sacroiliac-menacing performances of Marie, *Route 66*, *Tag That Twistin' Dolly*, some other numbers and, of all things, *Glow Worm*.

For those moments when the sap runs high, 28 songs have been taken from the four notorious *Dalliance* discs (in which Ed McCurdy sings pungent songs of Elizabethan England) and issued in a two-record album yclept *The Best of Dalliance*. The warning is on the album cover: *For Mature Libidos Only!*

Another economic enticement is the complete *Nutcracker Ballet* on two discs offered as *Demonstration Records*. Maurice Abravanel leads the Utah Symphony Orchestra in a flowing rendition of Tchaikovsky's charming music and the recording permits every triangle tinkle and cymbal crash to be heard distinctly.

Not at all sure that every listener knows what every instrument in the orchestra sounds like, or should sound like, Capitol has issued a two-record

album titled *Instruments of the Orchestra*. Spoken commentary is by Yehudi Menuhin, and he and other top-notch musicians, solo and in ensemble, demonstrate the capabilities of the various instruments.

The narration is well written and expressively spoken and the musical examples are well chosen and beautifully played. Despite the educational nature of these recordings, there isn't a dull moment in them. They are a must for the serious listener, and particularly for children. Audiophiles should find them especially useful as a reference in determining the fidelity of other recordings—or of their own hi-fi systems. A 56-page book, written by John Hosier and published by the Music Department of the Oxford University Press, accompanies the records.

Records discussed in this column, with monaural discs listed first and stereo versions just below:

Offenbach: <i>Gaite Parisienne</i>		
<i>Solti, Royal Opera House Orch.</i>	London CM-9285	\$4.98
	CS-6216	5.98
Poulenc: <i>Concerto for Organ, Strings and Timpani</i>		
<i>Munch, Boston Sym. Orch.</i>	RCA Victor LM-2567	4.98
	LSC-2567	5.98
Falla: <i>The Three-Cornered Hat</i>		
<i>Ansermet, Suisse Romande Orch.</i>	London CM-9292	4.98
	CS-6224	5.98
The Electro-Sonic Orchestra	Coral CRL-57381	3.98
	CRL-757381	4.98
Never on Sunday <i>The Chordettes</i>	Cadence CLP-3056	3.98
	CLP-25056	4.98
50 Years of Movie Music	Decca DL-9079	4.98
	DL-79679	5.98
The Essential Lester Young	Verve V-8398	4.98
	(monaural)	
<i>Doin' the Twist Louis Prima</i>	Dot DLP-3410	3.98
	DLP-25410	4.98
<i>The Best of Dalliance Ed McCurdy</i>	Elektra EKL-213	4.98
	(monaural—2 discs)	
Tchaikovsky: <i>The Nutcracker</i>		
<i>Abravanel, Utah Sym. Orch.</i>	Vanguard SRV-123/4	3.96
	SRV-123/4-SD	5.96
	(2 discs)	
<i>Instruments of the Orchestra</i>	Capitol HBZ-21002	9.96
	(monaural—2 discs)	

Good Reading

Continued from page 84

meant to be taken together as a complete course in basic radio. The separate volumes present the fundamentals of DC electricity, AC electricity, electron tube circuits, AM and FM receivers, transistors and transmitters. The entire presentation has been well thought out and virtually everything worth understanding—for the beginner—is thoroughly covered. But this reviewer, for one, has some doubts about the pictured-text presentation. The illustrative technique is a little too reminiscent of the Army classroom. Those who have sat through Army training courses need no further explanation.

INDUSTRIAL ELECTRONICS MADE EASY. By Tom Jaski. Gernsback Library, New York. 288 pages. \$3.95

This book seems to be aimed primarily at the student who is thinking of making a career in industrial elec-

tronics. And it is a good, readable guide to a complicated field. While it's just not feasible in a book of this kind to cover computers, data recorders and the like in any real detail, there is enough information on them—and on the overall subjects of control systems and servo techniques—to give a student an initial feel of the subjects. In addition, the author points out ways in which technicians and servicemen may be able to apply their current knowledge and skills to free-lance servicing of industrial equipment. For anyone considering a career in electronics or thinking of changing his current focus, this is a potentially useful volume.

And make note of . . .

ELECTRONIC GAMES AND TOYS YOU CAN BUILD. By Len Buckwalter. Howard W. Sams, New York & Indianapolis. 128 pages. \$2.50

DETECTOR AND RECTIFIER CIRCUITS. By Thomas M. Adams. Howard W. Sams, New York & Indianapolis. 128 pages. \$2.95

Special GET-ACQUAINTED OFFER

6 issues of
ELECTRONICS ILLUSTRATED
for only **\$1.98**



Read the electronics hobby magazine that gives you authoritative feature and construction articles on:

- Citizens Band Radio
 - Amateur Radio
 - Short-Wave Listening
 - Audio & Hi-Fi
 - Electronics Theory
 - Kit Building
- And many other exciting subjects!

YES, I want to take advantage of your special get-acquainted offer. Please enter my subscription right away.

- I enclose \$1.98 Bill me
 New order Re-order

NAME

ADDRESS

CITY.....ZONE.....STATE.....

Mail to: Electronics Illustrated
Circulation Department
Fawcett Bldg., Greenwich, Conn.


New Fallout Checker

THE USUAL radiation exposure meter is a film badge that can be used only once and requires photographic developing. But now scientists at the Naval Research Laboratory have invented a new type of dosimeter. It keeps a constant record of the radiation exposure of its wearer—whether from a luminous watch dial or A-bomb fallout. It can be used more than once and is easier to read than film.

At the heart of the dosimeter is a glass or glass-and-metal tube containing a white powder (a type of calcium fluoride) coated on a metal holder. The powder traps electrons emitted by

atomic radiation. Later, current is applied to the holder and the resulting heat boils out the electrons which, when returning to the trapping material, give off light. A photomultiplier tube measures the light and produces a radiation reading. The term given to the process is *thermoluminescence*. Pictured above is a miniature version of the tube.

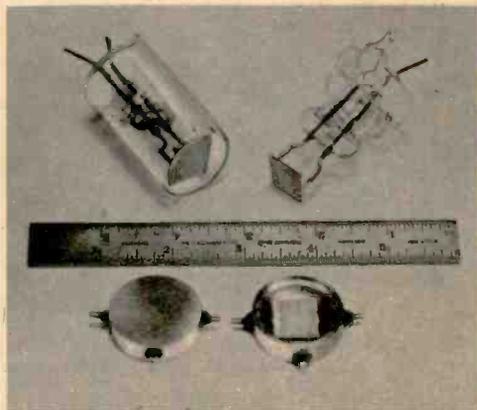Heart of Navy's exposure meter is a small tube (we show four models) containing white powder.



NEW...
The World's
most advanced
11 meter
two-way radio...


General is in command with the new MC 5

- 3.25 watts minimum output. • New High Power Modulation system for unparalleled "Ta k-Power." • New Zener Diode shunt noise-clamp and series gated limiter circuit for highest noise limiting ever achieved.
- Largest Power supply ever built for CB use. • New ultra-low drift oscillators for unsurpassed stability.
- New Hi-level Tone-Signal. • 15 watt construction. • Net Price including microphone and crystal... \$199.95. 90 day warranty. F.O.B. Burbank, California. • FREE—Write for schematic and complete technical data.

Under present rules part 19.32 the FCC does not provide for more than five (5) watt input in the Citizens Radio Service (26.965-27.225 MC Band).

Your dealer or write:

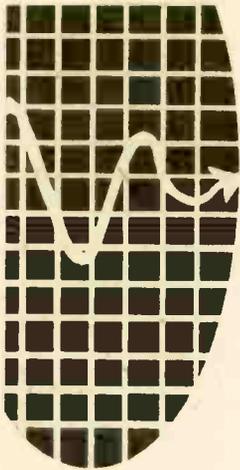General Radiotelephone Company, DEPT. E5
3501 Burbank Boulevard, Burbank, California



ELECTRONICS ILLUSTRATED

Classified Ads

Your advertisement can reach this mail-buying audience for only 50¢ per word . . . payable in advance (Check or M.O. please) . . . minimum 10 words. Closing dates are the 20th of 4th preceding month i.e. copy for the September issue must be in our office by May 20th. Mail to ELECTRONICS ILLUSTRATED, 67 West 44th St., New York 36, N. Y. Word count: Zone number free. Figure one word: Name of state (New Jersey), name of city (New York); sets of characters as in key (14-D); also abbreviations as 35MM, 8x10, D.C., A.C.

SAVE MONEY • ORDER BY MAIL

• • • FOR SALE

SUPERSENSITIVE DIRECTIONAL microphone picks up a whisper at great distances. Used by investigators to record faint sounds without being detected. Easily constructed for about \$7.00. Step by step plans \$1.95. Dee Company, Box 7263-C, Houston 8, Texas.

EXCELLENT BUYS on Tubes and equipment all listed in the "Green Sheet." Send .25¢ for your copy today. Cash paid for unused tubes. Write. Barry Electronics Corp., 512 Broadway, Dept. E1, NYC 12, NY.

CONVERT ANY television to sensitive, big screen oscilloscope. Only minor changes necessary. Plans \$1.95. Relco, Box 10563E, Houston 18, Texas.

• • • BUSINESS OPPORTUNITIES

VENDING MACHINES—No selling. Operate a route of coin machines and earn high profits. 32-page catalog free! Parkway Machine Corp., Dept. 33, 715 Ensor St., Baltimore 2, Md.

HOMEWORK. TYPING. \$20-\$70 Weekly. Details Free. Crystalco, 20 Southmountain, Millburn E1-1, New Jersey.

• • • EMPLOYMENT OPPORTUNITIES

PRINTING - ADVERTISING SALESMEN. Excellent moneymaking sideline selling Decalomania Name Plates. Advertising Specialties. Sign letters, Automobile initials. Free Samples. "Ralco"—E1, Box 1, Boston 19, Mass.

• • • EDUCATION & INSTRUCTION

BACCALAUREATE DEGREE Correspondence Course Directory; \$2.00. College Research, North Highlands 4, Calif.

• • • HI-FI

HI-FI & TEST Equipment; new & used at a discount. Send stamped envelope for free list. Audio Workshop, 732 Broadway, NYC.

RECORDERS, HI-FI! Free Wholesale Catalogue. CARSTON, 125-G East 88, NYC 28.

• • • TAPE RECORDERS

LEARN WHILE Asleep with your recorder, phonograph or amazing new "Electronic Educator" endless tape recorder. Details free. Sleep-Learning Research Association, Box 24-E1, Olympia, Washington.

TAPE RECORDERS Hi-Fi Components. Sleep Learning Equipment, tapes. Unusual values. Free Catalog. Dressner, 1523Z Jericho Tpke., New Hyde Park, N. Y.

NEW CONCEPT of self-hypnosis teaches you quickly, easily. New tape! New record! Free literature. McKinley-Smith Co., Dept. T-3, Box 3038, San Bernardino, Calif.

RENT STEREO Tapes—over 2500 different—all major labels—free catalog. Stereo-Parti, 811-AY Centinela Ave., Inglewood 3, California.

• • • RADIO & TV

TV SHOP Billboards. Key circuit symbols, resistor, wiring codes, helpful time-saving hints. 10 2/3x6 1/4 wall-mounting billboards, assorted colors. \$1.00. Millett, 5208 Longton, Cleveland 24, Ohio.

PLANS DISTANCE Crystal Set (SW record 5800 miles)—25¢. 24 page Handbook for same—50¢. Catalog. Laboratories, 1131-K Valota, Redwood City, California.

DIAGRAMS FOR Repairing Radios \$1.00, Television \$2.00. Give make, model. Diagram Service, Box 672E1, Hartford 1, Conn.

DIAGRAMS—FOR T.V. \$2., Radio \$1. Hiett Diagrams, Box 816, Laredo, Tex.

• • • PERSONAL

BORROW CASH By Mail—For any purpose. How much do you need? Repay 24 monthly payments. Free loan application. American Loan Plan, Dept. E1-3142, City National Bldg., Omaha 2, Nebraska.

• • • MISCELLANEOUS

ELECTRONIC KITS assembled, wired and tested by Naczas Kit Service, Dept. 1, 18 Wolf Street, Manchester, New Hampshire "Where Quality Excels."


"**HOMEBREWING!** BEERS, Wines." Complete instructions \$1 (guaranteed). Crystalco 28-BE12, Millburn, New Jersey.

youth wants to DO



IN WHAT we call the good old days our youngsters were supposed to be seen but not heard. Fortunately, things have changed until today our youth actually is encouraged to be inquiring and to experiment with home-made gadgets. Partly as a result, we now have tots of less than 10 who get ham licenses and scientists in their thirties who win Nobel Prizes. In these two photographs we show four young people who wanted to do something and did it. At left are researchers Lloyd Cross and Jerald Cook, both in their mid-twenties, who used an 85-foot radio telescope at the University of Michigan to obtain the world's first definite temperature reading of Saturn's surface.

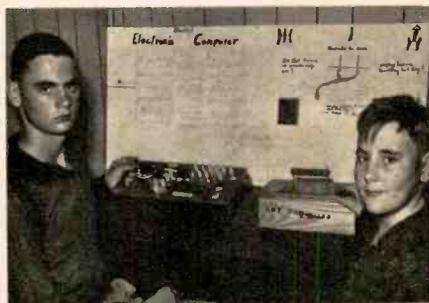The scope is in the background. The reading was 283 degrees below zero. At right are Bob Swaine, 14, and his 12-year-old brother Stan of Milton, Fla. Bob successfully built EI's rather complicated Electronic Computer (January '60 issue) as his entry in the West Florida Regional Science Fair. Brother Stan designed an electric hot dog cooker.



MICRO

ELECTRON TUBE
FABULOUS LOW PRICES!
LARGE, SELECT STOCKS!
DEPENDABLE, FAST SERVICE!

37

¢ ea.

FOR *any* TUBE LISTED

\$35 PER HUNDRED ASSTD.

Ann Surplus Tubes!

MICRO

ELECTRON TUBE CO. Dept. EI-5, P. O. Box 55 Park Sta., Paterson 3, N. J.



- Each and every tube is tested in our own laboratory for mutual conduction and life test.
- We guarantee FREE replacement for one year of any tube purchased from us which fails to function efficiently under any or all operating conditions. Prompt refunds are made on any defective merchandise.
- The advertised tubes are not necessarily new, but may be electrically perfect factory seconds or used tubes—each is clearly so marked.

0A2	5X6	6BH6	6SF5	7Z4	198CG6
0Z4	5Y3GT	6BJ6	6SF7	12A8	19J6
1A7GT	5Y4Q	6BK5	6SJ7	12AQ5	19T8
1B3GT	6A7	6BK7	6SK7	12AT8	24A
1N4C	6AB4	6BL7GT	6SL7GT	12AT7	25AV5
1NSGT	6AC7	6BN6	6SN7GT	12A7	25B05
1L4	6AF6	6B06GT	6SQ7	12A6	25DN6
1L6	6AG3	6B07	6S7	12A7	25L6GT
1M9GT	6AQ7	6B55G	6T6	12AV7	25W4GT
1O5GT	6AR6	6B6	6T7	12AV7	25W4GT
1R8	6AN4GT	6B6	6T8	12AX4GT	25Z6
1R8	6AN6	6B27	6T8	12AX7	26
1U4	6AK5	6C4	6V6	12AZ7	35A5
1V2	6AL5	6C5	6W4GT	12B4	35B8
1U4	6AL7	6C6	6W6GT	12BA7	35C5
1X2	6AM5	6C86	6X4	12B6	35L6GT
2A3	6AN6	6C86	6X5	12B7	38W4
2AF4	6AQ5	6CF6	6X6	12C8	39/44
3BC8	6AQ6	6CG7	6Y6	12C8	35Z6GT
3BN6	6AQ7GT	6CL6	6Y6	12BH7	37
3Z5	6AR5	6CM6	7A4/XXL	12B06	43
3C8	6ASB	6CM7	7A5	12B06	45
3CF8	6AT5	6CN7	7A6	12B7	50A5
3C50	6AT5	6CS6	7A7	12B7	50B5
3LFA	6AU4GT	6CU6	7A8	12C45	50C5
3Q4	6AU5GT	6DE6	7B4	12J5	50L6GT
3B4	6AU6	6D06	7B5	12K7	50K6
3V4	6AUS	6F6	7B6	12L6	56
4BQ7A	6AV5GT	6H6	7B7	12L6	56
4B27	6AV6	6J4	7B8	12M7	57
5A5	6AW8	6J5	7C4	12S07	71A
5AT8	6AX4GT	6J7	7C5	12S17	75
5AV8	6AX5GT	6K7	7C6	12S27	77
5AW4	6B8	6K6GT	7C7	12S7GT	78
5BK7	6B8	6K8	7E6	12S7	78
5J8	6C5	6K7	7E7	12V4GT	78
5T6	6BC8	6L7	7F7	12W6GT	78
5U4C	6RD6	6N7	7F7	12X4	78
5U8	6BE6	6Q7	7F8	12X4	78
5V4Q	6BF5	6S4	7M7	12Z3	78
5V6GT	6BF6	6S8GT	7N7	14A7/12B7	78
	6BC6G	6SA7	7Q1	14B6	80
		6SC7	7X7/XXFM	1407	84/624
			7Y4	19	11723
				19AU4GT	11726

WRITE EI-5 FOR OUR FREE COMPLETE LIST OF TUBES & SPECIAL PURPOSE TUBES

THE KIT BUILDERS

by *Rodriguez*

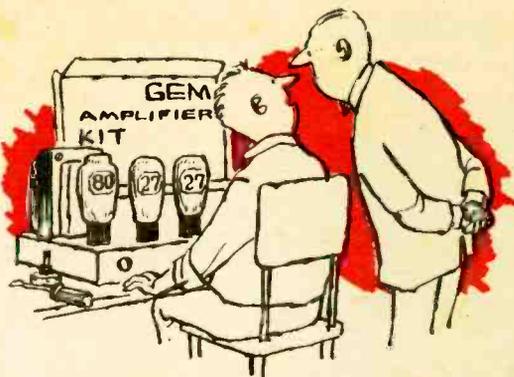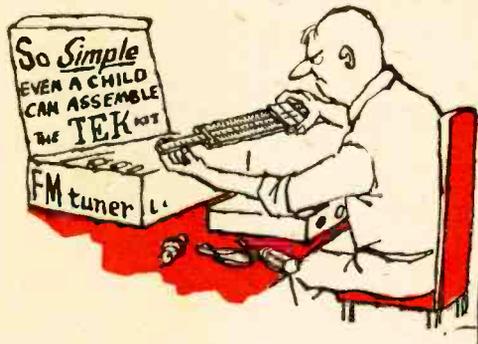


"They're an old, OLD reliable company."



"Now wind the transformer. Primary is 2,100 turns. Secondary is 8,455 turns . . ."

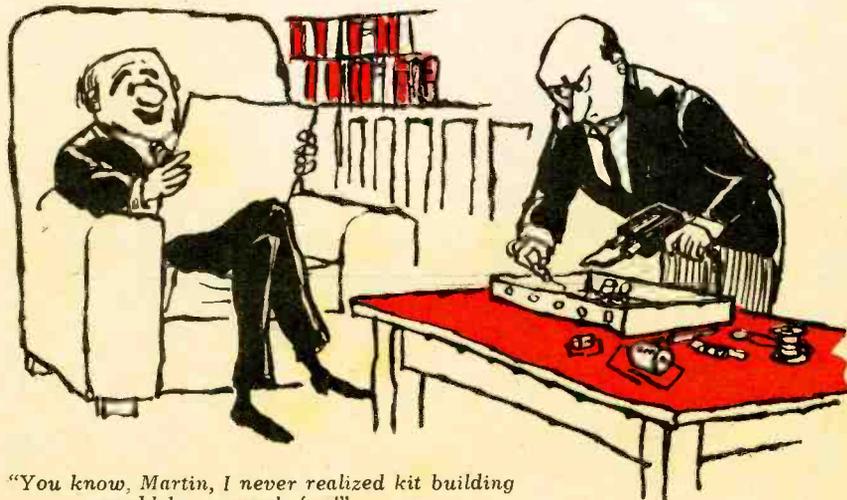"Volume control? Well, you just sort of move away from it."



"You know, Martin, I never realized kit building could be so much fun!"

NOW!
at a price
you can afford!

MAKE MORE MONEY in ELECTRONICS TELEVISION-RADIO

**BETTER...MORE COMPLETE...LOWER COST...
WITH NATIONAL SCHOOLS SHOP-METHOD
HOME TRAINING!**

BETTER... Training that is proved and tested in Resident School shops and laboratories, by a School that is the **OLDEST** and **LARGEST** of its kind in the world.

MORE COMPLETE... You learn **ALL PHASES** of *Television-Radio-Electronics*.

LOWER COST... Other schools make several courses out of the material in our **ONE MASTER COURSE**... and you pay more for less traiping than you get in our course at **ONE LOW TUITION!**



These two **FREE** books will show you how!

You get all information by mail... You make your own decision... at home! **NO SALESMAN WILL CALL**

TOP PAY... UNLIMITED OPPORTUNITIES LIFETIME SECURITY CAN BE YOURS!

You are needed in the Television, Radio, and Electronics industry! Trained technicians are in growing demand at excellent pay—in **ALL PHASES**, including Servicing, Manufacturing, Broadcasting and Communications, Automation, Radar, Government Missile Projects.

NATIONAL SCHOOLS SHOP-METHOD HOME TRAINING, with newly added lessons and equipment, trains you in your spare time at home, for these unlimited opportunities, including many technical jobs leading to supervisory positions.

YOU LEARN BY BUILDING EQUIPMENT WITH KITS AND PARTS WE SEND YOU. Your National Schools course includes thorough Practical training—**YOU LEARN BY DOING!** We send you complete standard equipment of professional quality for building various experimental and test units. You advance step by step, perform more than 100 experiments, and you build a complete TV set from the ground up that is yours to keep! A big, new TV picture tube is included at no extra charge.

EARN AS YOU LEARN. We'll show you how. Many students pay for their course—and more, while studying.

GET THE BENEFIT OF OUR OVER 50 YEARS EXPERIENCE

APPROVED FOR GI TRAINING



ACCREDITED MEMBER



NATIONAL TECHNICAL SCHOOLS
World-Wide Training Since 1905

Write to Dept. R4Y-22
4000 So. Figueroa Street
Los Angeles 37, California

YOU GET...

- 19 Big Kits—**YOURS TO KEEP!**
- Friendly Instruction and Guidance
- Job Placement Service
- Unlimited Consultation
- Diploma—Recognized by Industry
- **EVERYTHING YOU NEED FOR SUCCESS!**

RESIDENT TRAINING AT LOS ANGELES
If you wish to take your training in our famous Resident School in Los Angeles—the oldest and largest school of its kind in the world—check special box in coupon.

SEND FOR FREE FULLY-ILLUSTRATED BOOK AND ACTUAL LESSON TODAY.

Your own copy of "Your Future in Electronics-Television-Radio" will be mailed to you at once. No salesman will call; there is no obligation. Cut out card along dotted lines, fill in name and address, then mail today.

NO POSTAGE NECESSARY

FIRST CLASS
Permit No. 3087
Los Angeles, Calif.

BUSINESS REPLY MAIL
NO POSTAGE STAMP NECESSARY IF MAILED IN THE UNITED STATES

— POSTAGE WILL BE PAID BY —

NATIONAL TECHNICAL SCHOOLS
WORLD-WIDE TRAINING SINCE 1905
4000 So. Figueroa Street
Los Angeles 37, California

Dept. R4Y-42

Name _____ State _____
Address _____ Zone _____
City _____
 Check if interested only in Resident Training at Los Angeles



ONLY AMERICAN BASIC SCIENCE CLUB OFFERS YOU A

COMPLETE ELECTRONICS LAB

that builds 65 electronic projects

plus a **BASIC RADIO COURSE** for only

\$15.80

TROUBLE SHOOTING WITH THE SIGNAL TRACER

A VALUABLE ELECTRONICS LAB

Containing parts by RCA, MALLORY, PYRAMID, GE, CENTRALAB, STACKPOLE, TRIM and other reliable manufacturers. Retail value of parts alone is MORE THAN 25 DOLLARS

A COMPLETE ELECTRONICS COURSE

The manuals are expertly written, clearly illustrated... making it easy for you to build 65 projects in electronics, step-by-step. You gain a valuable electronics background that will enrich your life and help shape your future! Basic enough for beginners... rewarding enough for experts. Nowhere else is a course of this scope available at this LOW PRICE!

ENTHUSIASTIC MEMBERS WRITE:

"Basic principles unforgettably learned" ... It is only after having completed the experiments in your kits that I can say I have truly and unforgettably learned the basic principles of electronics. JOHN R. KANIA, 2 Berkeley Ave., Yonkers 5, N. Y.

"Your kits are interesting and rewarding" ... I am an electronics student in the Air Force and find your kits interesting and rewarding. We have not covered anything in the school that you have not covered in the kits. JOHN G. DILL, Keester Air Force Base, Biloxi, Miss.

"far ahead of friend taking another course" ... A friend of mine is taking a correspondence course in electronics, and I have learned more from your first two kits than he has in twenty lessons. RAY P. BILODEAU, 139 Exchange St., Leominster, Mass.

"the number of concepts presented is amazing" ... Your kits offer a range of experiments usually performed only in the better high school and college laboratories. The number of concepts presented, and the clarity and concreteness of their development is amazing. R. M. HELM, Professor of Physics, East Carolina College, Greenville, N. C.

Complete Lab and Course comes in 4 kits... one a month

KIT 1 — MAGNETISM AND ELECTRICITY

Builds 26 Projects including:
 • Electroscopes • Electro Magnet
 • Galvanometer • AC Buzzer • Demagnetizer • Relay • Solenoid
 Coin Tosses

Subjects include:
 • Magnetic Fields • Electron Theory • Electric Charge • Direct Current • Electro-Chemistry • Alternating Current • Inductance • Transformer Principles

FREE with kit 1 — Surprise "Mystery Box"

KIT 2 — RESISTANCE, CAPACITANCE AND RECTIFICATION

Builds 18 Projects including:
 • Strobe Light • Thermocouple
 • Wheatstone Bridge • Voltmeter
 • AC Rectifier • DC Power Supply

Subjects include:
 • Ohm's Law • Power Formulas
 • Rectification • Resistance • Neon Glow Tubes • Capacitance • Filter Circuits

FREE with kit 2 — Electric Soldering Iron

KIT 3 — AMPLIFIERS AND OSCILLATORS

Builds 14 Projects including:
 • Two Stage Amplifier • Capacitance • Burglar Alarm • Proximity Detector • High Speed Strobe Light • Ripple Tank Wave Generator • Code Practice Oscillator

Subjects include:
 • Vacuum Amplifier Tubes • Voltage Amplification • Oscillator Circuits • Frequency and Wave Length Sound Waves, Pitch and Resonance

FREE with kit 3 — "Steps to a Ham License" Manual

KIT 4 — AUDIO AMPLIFICATION AND RADIO

Builds 7 Projects including:
 • Microphone and Audio Amplifier • Broadcast Radio • Short Wave Radio • Signal Tracer • Transmitter

Subjects include:
 • Audio Amplifiers • Amplitude Modulation • Radio Theory • Regenerative Circuits • Tuning Circuits

FREE with kit 4 — Radio-TV Service Manual

ALL THE EQUIPMENT FOR ALL THE ABOVE — Only \$15.80

SEND \$2.00 WITH ONLY COUPON PAY \$3.45 FOR EACH KIT YOU RECEIVE (ONE A MONTH FOR 4 MONTHS)

Your Satisfaction or Your Money Back... AND You May Cancel at any time without obligation. These "No Risk" assurances because we know you will be

SURPRISED! AMAZED! DELIGHTED!

AMERICAN BASIC SCIENCE CLUB, Inc.
 501 E. Crockett, San Antonio 6, Texas

Start sending me A.B.S.C.'s "Electronics Lab" in four kits, one each month. If not satisfied on inspection of first kit I may return it for immediate refund. (I choose the plan checked)

- () I enclose \$2.00 and will pay \$3.45 plus COD postage on arrival of each kit. I may cancel unshipped kits at any time.
- () I enclose \$15.80, full payment, POSTAGE PAID, for all four kits. I may cancel at any time and get full refund on unshipped kits.

NAME _____
 ADDRESS _____
 CITY and STATE _____

MAIL THIS MONEY-SAVING COUPON NOW!