

electronics today international

MAY 1976

30p


SOUTH AFRICA 60c
CANADA \$1

CASSETTES OFFER SIX C90's: £2.99

EXPANDER COMPRESSOR
TEMPERATURE METER
ELECTRONIC GAME
TOUCH SWITCH

VIEWDATA

Communications system
of the future

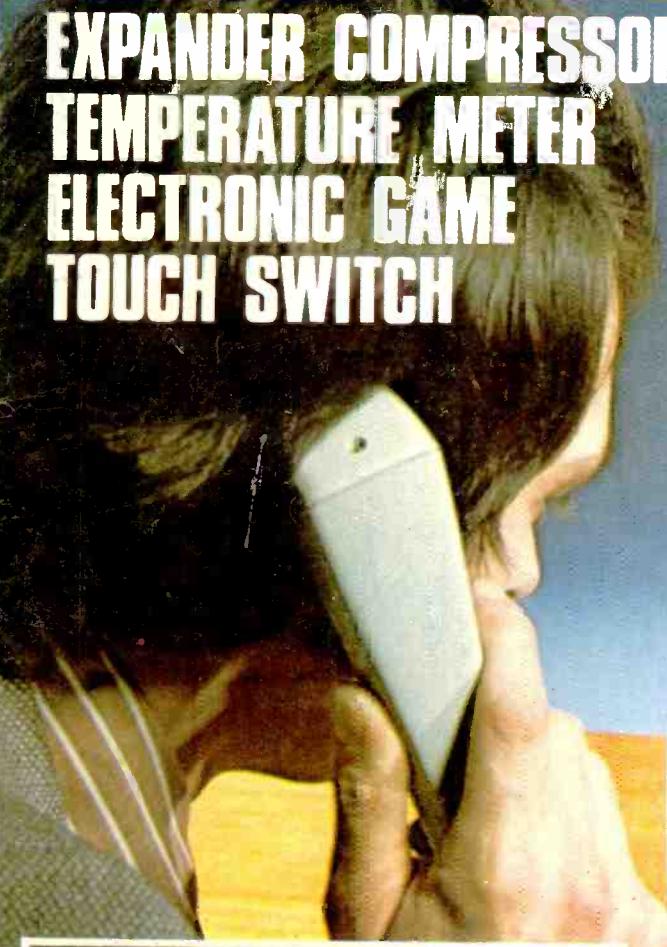

NEWS . . . CONSTRUCTION . . . DEVELOPMENT

DATA SHEET SPECIAL:
AUDIO AMP IC'S

AUDIO

15 - 240 Watts!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack — Multi-function equalization — Low noise — Low distortion — High overload — Two simply combined for stereo

APPLICATIONS: Hi-Fi — Mixers — Disco — Guitar and Organ — Public address

SPECIFICATIONS:

INPUTS: Magnetic Pick-up 3mV, Ceramic Pick-up 30mV, Tuner 100mV, Microphone 10mV, Auxiliary 3.100mV; Input impedance 47kΩ at 1kHz


OUTPUTS: Tape 100mV, Main output 500mV R.M.S.

ACTIVE TONE CONTROLS: Treble ± 12dB at 10kHz, Bass ± at 100Hz

DISTORTION 0.1% at 1kHz, Signal/Noise Ratio 68dB

OVERLOAD 38dB on Magnetic Pick-up, SUPPLY VOLTAGE ± 16-50V

Price £4.75 + £1.19 VAT P&P free.

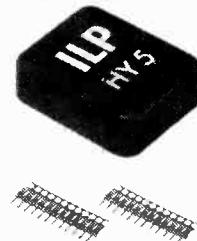

HY30 15 Watts into 8Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete Kit — Low Distortion — Short, Open and Thermal Protection — Easy to Build

APPLICATIONS: Updating audio equipment — Guitar practice amplifier — Test amplifier — audio oscillator

SPECIFICATIONS:

OUTPUT POWER 15W R.M.S. into 8Ω; DISTORTION 0.1% at 15W

INPUT SENSITIVITY 500mV FREQUENCY RESPONSE 10Hz-16kHz — 3dB

SUPPLY VOLTAGE ± 18V

Price £4.75 + £1.19 VAT P&P free.

Available
June '76

HY50 25 Watts into 8Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion — Integral Heatsink — Only five connections — 7 Amp output transistors — No external components

APPLICATIONS: Medium Power Hi-Fi systems — Low power disco — Guitar amplifier

SPECIFICATIONS: INPUT SENSITIVITY 500mV

OUTPUT POWER 25W RMS into 8Ω LOAD IMPEDANCE 4-16Ω DISTORTION 0.04% at 25W at 1kHz

SIGNAL/NOISE RATIO 75dB FREQUENCY RESPONSE 10Hz-45kHz — 3dB

SUPPLY VOLTAGE ± 25V SIZE 105 50 25mm

Price £6.20 + £1.55 VAT P&P free.



HY120 60 Watts into 8Ω

The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: Very low distortion — Integral heatsink — Load line protection — Thermal protection — Five connections — No external components

APPLICATIONS: Hi-Fi — High quality disco — Public address — Monitor amplifier — Guitar and organ

SPECIFICATIONS:


INPUT SENSITIVITY 500mV

OUTPUT POWER 60W RMS into 8Ω LOAD IMPEDANCE 4-16Ω DISTORTION 0.04% at 60W at 1kHz

SIGNAL/NOISE RATIO 90dB FREQUENCY RESPONSE 10Hz-45kHz — 3dB SUPPLY VOLTAGE ± 35V

SIZE 114 50 85mm

Price £14.40 + £1.16 VAT P&P free.

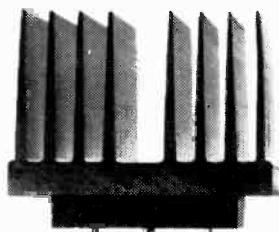

HY200 120 Watts into 8Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown — Very low distortion — Load line protection — Integral heatsink — No external components

APPLICATIONS: Hi-Fi — Disco — Monitor — Power slave — Industrial — Public Address

SPECIFICATIONS:


INPUT SENSITIVITY 500mV

OUTPUT POWER 120W RMS into 8Ω LOAD IMPEDANCE 4-16Ω DISTORTION 0.05% at 100W at 1kHz

SIGNAL/NOISE RATIO 96 dB FREQUENCY RESPONSE 10Hz-45kHz — 3dB SUPPLY VOLTAGE ± 45V

SIZE 114 100 85mm

Price £21.20 + £1.70 VAT P&P free.

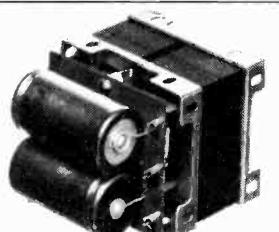

HY400 240 Watts into 4Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4Ω! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown — Very low distortion — Load line protection — No external components

APPLICATIONS: Public address — Disco — Power slave — Industrial

SPECIFICATIONS:

OUTPUT POWER 240W RMS into 4Ω LOAD IMPEDANCE 4-16Ω DISTORTION 0.1% at 240W at 1kHz

SIGNAL/NOISE RATIO 94dB FREQUENCY RESPONSE 10Hz-45kHz — 3dB SUPPLY VOLTAGE ± 45V

INPUT SENSITIVITY 500mV SIZE 114x100x85mm

Price £29.25 + £2.34 VAT P&P free.

POWER SUPPLIES

PSU36 suitable for two HY30's £4.75 plus £1.19 VAT P/P free.
PSU50 suitable for two HY50's £6.20 plus £1.55 VAT P/P free.
PSU70 suitable for two HY120's £12.50 plus £1.00 VAT P/P free.
PSU90 suitable for one HY200 £11.50 plus £0.92 VAT P/P free.
PSU180 suitable for two HY200's or one HY400 £21.00 plus £1.68 VAT P/P free.

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd

Crossland House

Nackington, Canterbury

Kent CT4 7AD

Tel (0227) 63218

Please Supply _____
Total Purchase Price _____

I Enclose Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number _____

Name & Address _____
Signature _____

electronics today

international

MAY 1976

VOL 5. No. 5.

Features

VIEWDATA	10
Access to 1,000,000 pages of information via your telephone!	
FROZEN SIGNALS	19
Oscilloscopes with a better memory than us!	
ETI MICROFILE	46
Memories are made of this!	
PACEMAKERS	52
Nuclear fuel on the beat	
CMOS — PART FOUR	57
Shifting, storing and looping signals!	
ELECTRONICS IT'S EASY	64
Further into the depths of logic circuitry	
TECH-TIPS	72
Our regular ideas forum	

Projects

TOUCH SWITCH	14
Absolutely safe 240V AC operation!	
MARKER GENERATOR	25
Low cost accurate design	
EXPANDER COMPRESSOR	29
Putting back into records what studios take away	
TEMPERATURE METER	49
Converts any analogue or digital voltmeter to an accurate thermometer	
ELECTRONIC GAME	62
Basic electronic contest, easily expanded and complicated!	

Data Sheet

AUDIO POWER AMPLIFIERS	39
From 1W to 100W, the chips are down!	

News

NEWS DIGEST	6
ELECTRONICS TOMORROW	70

Information

PREVIEW OF THE JUNE ETI	38
PROJECT BOOK 3	56
ETI BOOK SERVICE	45
PULSAR	63
ETI SPECIALS	69
READER SERVICES INFORMATION	82

Special Offer

CASSETTE OFFER	37
Good quality cassettes at an incredible price	

COVER:- Viewdata in operation on a GPO receiver. Our thanks go to the Post Office for arranging this special photograph for ETI. Many thanks also to Tektronix for providing the storage scope photos.

EDITORIAL AND ADVERTISEMENT

OFFICE
36 Ebury Street
London SW1W OLW
Telephone: 01-730 8282

HALVOR W. MOORSHEAD
Editor

ROBERT C. EVANS
Advertisement Manager

LES BELL, G4CFM
RON HARRIS
Editorial Assistants

JEAN BELL
Production

INTERNATIONAL EDITIONS

COLLYN RIVERS
Editorial Director

AUSTRALIA
Modern Magazine Holdings Ltd
Ryne House, 15 Boundary Street
Rushcutters Bay 2011
Sydney, Australia.

FRANCE
DENIS KACOB
Editor in chief
CHRISTIAN DARTEVILLE
Editor
Electronique Pour Vous International,
17 Rue de Buci
Paris, France.

PUBLISHED BY
Electronics Today International is normally published on the first Friday of the month prior to the cover date

PUBLISHERS
Modern Magazines (Holdings) Ltd
36 Ebury Street, London SW1W OLW



DISTRIBUTORS
Argus Distribution Ltd

PRINTERS
QB Newspapers Limited, Colchester

READERS' QUERIES These can only be answered if they relate to recent articles published in the magazine. Rarely can we supply information in addition to that published. Written queries must be accompanied by a stamped addressed envelope, and telephone queries must be brief, not before 4pm and can only be answered subject to the availability of technical staff.

BACK NUMBERS: Back numbers of many issues are available for 40p each, plus 15p postage.)

SUBSCRIPTIONS Great Britain £5.00 per annum.
Overseas £5.50. Canada \$10.

COPYRIGHT: All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur, a correction will be published as soon as possible afterwards in the magazine.

READER SERVICES See page 82 for details of all ETI Reader Services and other information

PROJECTS BOOK 3
page 56

BI-PAK

SEMICONDUCTORS

COMPONENTS

CARBON RESISTOR PAKS
These Paks contain range of Carbon Resistors, assorted into the following groups:-

R1 50 Mixed 100 ohms -	
820 ohms 1/4W	0.60
R2 50 Mixed 1K ohms -	
82K ohms 1/4W	0.60
R3 50 Mixed 10K ohms -	
82K ohms 1/4W	0.60
R4 50 Mixed 100K ohms -	
820K ohms 1/4W	0.60
R5 30 Mixed 100K ohms -	
820K ohms 1/4W	0.60
R6 30 Mixed 1K ohms -	
8.2K ohms 1/4W	0.60
R7 30 Mixed 10K ohms -	
82K ohms 1/4W	0.60
R8 30 Mixed 100K ohms -	
820K ohms 1/4W	0.60

These are unbeatable prices.

LOW COST CAPACITORS

500 μ F	50V Elect	0.09 each
01 μ F	400V	0.03 each

REPANCO CHOKES & COILS

RF Chokes	CH1 2.5mH	0.27
	CH3 7.5mH	0.29
	CH5 1.5mH	0.26
	CH2 5.0mH	0.28
	CH4 10mH	0.31
COILS	DRX1 Crystal set	0.29
	DRR2 Dual range	0.42

CARBON POTENTIOMETERS

Log and Lin 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M.

VC 1 Single Less Switch	0.20
VC 2 Single D.P. Switch	0.40
VC 3 Tandem Less Switch	0.60
VC 4 1K Lin Less Switch	0.20
VC 5 100K Log anti-Log	0.60

HORIZONTAL CARBON PRESETS

0.1 Watt 0.05 each
100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M.

REPANCO TRANSFORMERS *

240V. Primary. Secondary voltages available from selected tapings 4V, 7V, 8V, 10V, 40V, 50V and 25V-0.25V.
Type Amps Price P&P
MT50/½ ½ £3.00 0.45
MT50/1 1 £4.00 0.48
MT50/2 2 £5.00 0.60

COIL FORMERS & CORES

NORMAN ¼" Cores & Formers 0.07p
¾" Cores & Formers 0.09p

SWITCHES

DP/DT Toggle 0.28p
SP/ST Toggle 0.22p

FUSES

20mm, 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A QUICK BLOW

*0.05p each
Anti-surge 20mm only *0.8p each

VEROBORDS *

VB 1 containing approx. 50sq. ins. various sizes all 0.1 matrix *0.60p
VB 2 containing approx. 50 sq. ins. various sizes all 0.15 matrix *0.80p

DECON-DALO 33PC MARKER

Etch resistant printed circuit marker pen. Full instructions supplied with each pen *0.92p

BATTERY HOLDERS *

Takes 6 H.P. 7's complete with terminal clip and lead *0.31p each

V.A.T.

ALL PRICES EXCLUDE V.A.T.

Please add 8% to all prices marked *. Remainder add 25%. Do NOT add V.A.T. to prices marked †.

INSTRUMENT CASES



(In 2 sections, Black Vinyl covered top and sides and bezel)

No. Length Width Height Price

BV1	8"	5 1/4"	2"	£1.25
BV2	11"	6"	3"	£1.62
BV3	6"	4 1/4"	1 1/4"	£0.92
BV4	9"	5 1/4"	2 1/4"	£1.39

ALUMINIUM BOXES

No. Length Width Height Price

BA1	5 1/4" x 2 1/4"	1 1/4"	1"	£0.45
BA2	4" x 4"	1 1/4"	1"	£0.45
BA3	4" x 2 1/4"	1 1/4"	1"	£0.45
BA4	5 1/4" x 4"	1 1/4"	1"	£0.54
BA5	4" x 2 1/4"	2"	1"	£0.45
BA6	3" x 2"	1"	1"	£0.39
BA7	7" x 5"	2 1/4"	1 1/4"	£0.79
BA8	8" x 6"	3"	1"	£1.02
BA9	6" x 4"	2"	1"	£0.65

(Each complete with 1/2" deep lids & screws)

PLEASE ADD 20p POSTAGE AND PACKING FOR EACH BOX

COMPONENT PAKS

Pak Qty Description Price

No. C1 200 Resistors mixed values approx. count by weight .60

C2 150 Capacitors mixed values approx. count by weight .60

C3 50 Precision Resistors mixed values .60

C4 75 1/4W Resistors mixed preferred values .60

C5 5 Pieces assorted Ferrite Rods .60

C6 2 Tuning Gangs. MW/LW VHF .60

C7 1 Pak Wire 50 metres assorted colours .60

C8 10 Reed Switches .60

C9 3 Micro Switches .60

C10 15 Assorted Pots & Pre-Sets .60

C11 5 Jack Sockets 3 x 3.5mm, 2 standard Switch Type .60

C12 30 Paper Condensers preferred types mixed values .60

C13 20 Electrolytic Trans. types .60

C14 1 Pack assorted Hardware Nuts/Bolts, Grommets,etc. .60

C15 5 Mains Side Switches, 2 Amp .60

C16 20 Assorted Tag Strips Panels .60

C17 10 Assorted Control Knobs .60

C18 4 Rotary Wave Change Switches .60

C19 2 Relays 6-24V Operating .60

C20 Sheets Copper Lamine approx. 200 sq. ins. .60

Please add 20p post and packing on all component packs, plus a further 10p on pack nos. C1, C2, C19 & C20.

AVDEL BOND

SOLVE THOSE STICKY PROBLEMS!

with

CYANOACRYLATE G2 ADHESIVE

The wonder bond which works in seconds. Bonds plastic, rubber, transistors, components, permanently, immediately!

OUR PRICE ONLY 70p *
for 2 gm phial

CABLES * Per Metre

CP 1 Single lapped screen *0.08

CP 2 Twin Common Screen *0.11

CP 3 Stereo Screened *0.12

CP 4 Four Core Common Screen *0.21

CP 5 Four Core individually screened *0.28

CP 6 Microphone Fully Braided Cable *0.11

CP 7 Three Core Mains Cable *0.11

CP 8 Twin Oval Mains Cable *0.08

CP 9 Speaker Cable *0.06

CP 10 Low Loss Co-Axial *0.14

ANTEX EQUIPMENT

SOLDERING IRONS

x25 25 watt	£2.45
Model G. 18 watt	£2.70
CCN 240. 15 watt	£2.90
SK2 Soldering Kit	£3.90

BITS AND ELEMENTS *

Bit No.	Length	Width	Height	Price
102	for model CN240	3/32"	*42p	
104	for model CN240	3/16"	*42p	
1100	for model CCN240	3/32"	*42p	
1101	for model CCN240	3/8"	*42p	
1102	for model CCN240	1/4"	*42p	
1020	for model G240	3/32"	*42p	
1021	for model G240	1/8"	*42p	
1022	for model G240	3/16"	*42p	
50	for model X25	3/32"	*44p	
51	for model X25	1/8"	*44p	
52	for model X25	3/16"	*44p	

ELEMENTS *

Model ECN	£1.10*
Model EG 240	£1.35*
Model ECCN 240	£1.55*
Model EX 25	£1.20*

SOLDERING IRON STAND

ST3 Suitable for all models	£1.10
Antex heat shunt	*10p

PLUGS

PS 1 D.I.N. 2 Pin (Speaker)	0.10
PS 2 D.I.N. 3 Pin	0.11
PS 3 D.I.N. 4 Pin	0.14
PS 4 D.I.N. 5 Pin 180°	0.15
PS 5 D.I.N. 5 Pin 240°	0.15

PS 6 D.I.N. 6 Pin	0.16
PS 7 D.I.N. 7 Pin	0.17
PS 8 Jack 2.5mm Screened	0.17
PS 9 Jack 3.5mm Plastic	0.11
PS 10 Jack 3.5mm Screened	0.17
PS 12 Jack ¼" Screened	0.20
PS 13 Jack Stereo Screened	0.33
PS 14 Phono	0.09
PS 15 Car Aerial	0.14
PS 16 Co-Axial	0.14

PS 21 D.I.N. 2 Pin (Speaker)	0.13
PS 23 D.I.N. 3 Pin	0.19
PS 24 D.I.N. 5 Pin 180°	0.19
PS 25 Jack 2.5mm Plastic	0.15
PS 26 Jack 3.5mm Plastic	0.15
PS 27 Jack ¼" Plastic	0.28
PS 28 Jack ¼" Screened	0.32
PS 29 Jack Stereo Plastic	0.28
PS 30 Jack Stereo Screened	0.35
PS 31 Phono Screened	0.17
PS 32 Car Aerial	0.20
PS 33 Co-Axial	0.20

PS 35 D.I.N. 2 Pin (Speaker)	0.07
PS 36 D.I.N. 3 Pin	0.09
PS 37 D.I.N. 5 Pin 180°	0.09
PS 38 D.I.N. 5 Pin 240°	0.10
PS 39 Jack 2.5mm Switched	0.11
PS 40 Jack 3.5mm Switched	0.11
PS 41 Jack ¼" Switched	0.19
PS 42 Jack Stereo Switched	0.28
PS 43 Phono Single	0.07
PS 44 Phono Double	0.09
PS 46 Co-Axial Surface	0.09
PS 47 Co-Axial Flush	0.19

PS 48 D.I.N. 2 Pin (Speaker)	0.07
PS 49 D.I.N. 3 Pin	0.09
PS 50 D.I.N. 5 Pin 18	

BI-PAK

High quality modules for stereo, mono and other audio equipment.



OUR PRICE ONLY

£19.95 Fitted with Phase Lock-loop Decoder

The 450 Tuner provides instant program selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls.

Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T461.

The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.

PUSH-BUTTON STEREO FM TUNER

**MPA
30**

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new M.P.A. 30, a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only.

It is provided with a standard DIN input socket for ease of connection. Full instructions supplied.

£2.65

STEREO PRE-AMPLIFIER



A top quality stereo pre-amplifier and tone control unit. The six push-button selector switch provides a choice of inputs together with two really effective filters for high and low frequencies, plus tape output.

MK. 60 AUDIO KIT: Comprising 2 x AL60's, 1 x SPM80, 1 x BTM80, 1 x PA100, 1 front panel and knobs. 1 Kit of parts to include on/off switch, neon indicator, stereo headphone sockets plus instruction booklet. **COMPLETE PRICE £27.55.**

TEAK 60 AUDIO KIT: plus 62p postage.

Comprising Teak veneered cabinet size 16½" x 11½" x 3¾" other parts include aluminium chassis, heatsink and front panel bracket plus back panel and appropriate sockets etc. **KIT PRICE £9.20** plus 62p postage.

SPECIFICATION:

- Harmonic Distortion Po = 3 watts f = 1KHz 0.25 %
- Load Impedance 8-16ohm
- Frequency response ± 3dB Po = 2 watts 50Hz-25KHz
- Sensitivity for Rated O/P - Vs = 25v. RL = 8ohm f = 1KHz 75mV RMS

AL10 3w R.M.S. £2.30

AL20 5w R.M.S. £2.65

PA100

OUR PRICE
£13.50

Frequency Response + 1dB 20Hz
20KHz Sensitivity of inputs
1. Tape Input 100mV into 100K ohms
2. Radio Tuner 100mV into
100K ohms
3. Magnetic P.U. 3mV into
50K ohms
P.U. Input equalises to RIAA curve with
1dB from 20Hz to 20KHz.
Supply — 20-35V at 20mA.

Dimensions
299mm x 89mm x
35mm.

AL10- 20-30

AUDIO AMPLIFIER MODULES

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S.

The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the home.

**VAT
ADD
25%**

POSTAGE & PACKING

Postage & Packing add
25p unless otherwise
shown. Add extra for
airmail. Min. £1.00

STEREO 30

COMPLETE AUDIO CHASSIS

7+7 WATTS
R.M.S.



P & P 45p

£15.75

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel knobs, main switch, fuse and fuse holder and universal mounting brackets enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available. Ideal for the beginner or the advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty (can be installed in 30 mins).

TRANSFORMER £2.45 plus 62p p & p
TEAK CASE £3.65 plus 62p p & p

AL 60

25 Watts (RMS)

★ Max Heat Sink temp 90C. ★ Frequency response 20Hz to 100KHz ★ Distortion better than 0.1 at 1KHz ★ Supply voltage 15-50v ★ Thermal Feedback ★ Latest Design Improvements ★ Load — 3,4,8, or 16 ohms ★ Signal to noise ratio 80db ★ Overall size 63mm. 105mm. 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

NEW

PA12

NEW PA12 Stereo Pre-Amplifier completely redesigned for use with AL10/20/30 Amplifier

Modules. Features include on/off volume, Balance, Bass and Treble controls. Complete Frequency Response 20Hz-20KHz (-3dB). Bass and Treble range 12dB. Input Impedance 1 meg ohm. Input Sensitivity 300mV. Supply requirements 24V-5mA. Size 152mm x 84mm x 33mm.

with tape output
£6.50

£3.95

Power supply for AL10/20/30,
PA12, SA450 etc.

OUR PRICE £1.20

£3.00

Stabilised Power Supply Type SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (R.M.S.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size: 63mm. 105mm. 30mm. Incorporating short circuit protection.

**Transformer BMT80
£2.60 + 62p postage**

BI-PAK

P.O. BOX 6, WARE, HERTS.

news digest

COMPETITION WINNERS



The winners of our Heathkit competition receive their prizes from Mr. R. Smith of Heathkit (far right) and our editor Hal Moorshead (far left).

ROCKETING COSTS

At the time when Britain is wallowing in poverty, news of the two super-powers space budget does seem slightly insulting. In 1975 the USA spent approximately \$5,000m (£2500m) on their space programme. The USSR, of course, will not tell us capitalists how much they spent. However the American Astronautical Society estimates the Russians as spending roughly three times as much — £7500m! At this rate why do they need fuel? Burning money MUST be cheaper.

62LB OF LSI

Rockwell International produced more than two million "large-scale integrated" (LSI) semiconductors in January of this year. Although the confetti-sized "chips" contained the equivalent of 20 billion transistors, they weighed only 62 pounds.

The original cost of designing each ranged from nearly \$100,000 to more than \$250,000, and production prices can be less than \$2 or more than \$50 depending on quality and complexity.

At \$2 each, two million chips are worth \$40m. Since the most expensive is worth \$50, the maximum value possible is \$100m. Gold is presently at \$2120 per pound, i.e. \$131,440 for 62lb which all means that 62lb of LSI is worth its weight in gold — 760.8 times over. Anyone fancy an LSI ring?

A RUB OFF OF THE NEW BLOCK

A new method of cleaning PCBs prior to etching has appeared. The item is called a 'Polifix Abrasive Block', and is exactly that. Consisting of silicone rubber with very fine-grade abrasives, non-metallic, implanted, it works like a giant pencil rubber, and will remove grease, fingermarks etc. from the copper. After rubbing with this block the copper is then 'keyed' ready to accept etch resist.



Obviously it could be used to clean veroboard as well, and the makers claim it will clean ANY metallic, plastic or painted surface.

From component suppliers in pack of 2 — £1.50.

SHRINKING FINANCES

Barclays Bank are about to install new microfilm equipment to replace their present computer output system. The new machines will now produce up to 70% of the total output. So now you know who to blame if your balance looks smaller this year.

MULTI-FAMILY LOGIC PROBE

Designed to simplify and speed logic circuit testing the new 545A Logic Probe from Hewlett-Packard indicates digital states and pulses in both CMOS and TTL logic. A single lamp indicator displays high or low level or detects bad level and open circuit conditions. Operation is with a slide switch. CMOS logic threshold levels are variable and set automatically.

Featured in the Model 545A is a built-in pulse memory which will catch intermittent pulses. When a logic change occurs, the indicator lamp turns on and remains lighted until the memory is reset.

Pulse stretching is provided so the operator can see fast pulses as short as 10 nanoseconds with the blinking display. Pulse trains to a frequency of 80MHz are detected in TTL logic, and to 40MHz in CMOS logic.



The 545A is fully protected against voltage overload. UK price as yet unknown to us, but the probe sells in the US for £82.

Hewlett-Packard Limited, King Street Lane, Winnersh, Wokingham, Berkshire RG11 5AR.

CZECH ON CALCULATOR PRICES

A typical dour Czech day. The rain sleet across Prague. Somewhere in the back streets well away from the patrols and the populace, Ivan scuttles into a dingy corner shop.

There, amid the Western papers and naughty mags, he spots the object of his desires.

Eyes alight he lifts the proscribed machine from the rack, and carries it reverently to the counter, behind which stands the owner.

"How much?" he stammers, hands shaking.

"Novus 650 comrade? To you, £172. Crossed the border this morning right under the army's

noses." he looks around furtively, and leans across the counter, whispering.

"Interested in the REAL thing eh comrade?" Ivan nods. The man reaches below the counter and produces a battered show box. Ivan's eyes are wide by now, riveted to the lid as it lifts. Inside lies a full frontal scientific, a HP 45.

Ivan faints.


Now before you dismiss this as merely the alcoholic follies of the ETI staff, following a party, let us inform you dear reader, that whilst we may be guilty of slight embroidery, our flight of fancy is based on fact.

It seems our Eastern friends consider pocket calculators to be highly prized items, and will pay vast sums to acquire them. What would cost you or I £7, our Ivan would need £172 to own. For that HP 45 you could possibly get a weekend with Siberian Sue, belle of the Balkans.

The reason behind this black marketing and smuggling is that calculator ships are not produced behind the ferric curtain and the machines are banned from importers lists by the governments, to preserve foreign exchange as their value is so high.

I wonder how they count it?

PUT PEN (AND PEN) TO PAPER

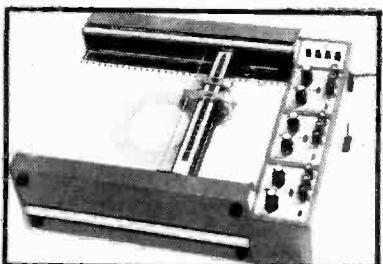

The WX446 2-pen Recorder allows the recording of two variables in the Y axis against one variable in the X axis.


A choice of input amplifiers is available with switched ranges giving a maximum sensitivity of 50 microvolts/cm, 0.5mV/cm or 10mV/cm. The minimum output is 1 Megohm.

The recorder features electrostatic paper hold down; servo free switch, which allows the pen carriage to be moved manually when making notes on the chart; push to operate zero and vernier controls, and optional fibre or jewel-tip pens.

Environmental Equipments Limited, Eastheath Avenue, Wokingham, Berkshire RG11 2PP.

TV TAKES A DIVE

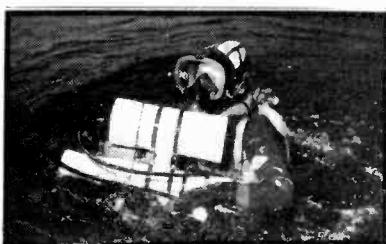
Following a two-year study into working with television underwater, EMI Electronics Limited, of Feltham, Middlesex, has introduced a new, highly sensitive underwater television system that requires little artificial lighting.



Designated the MTV3-U, this system is some 2500 times more sensitive than a standard closed-circuit TV system and comprises a rugged cylindrical-shaped camera and a control console for remotely monitoring and controlling the camera's video output from the surface.

EMI Limited, 135 Blyth Road, Hayes, Middlesex UB3 1BP.

AN EYE FOR ENERGY

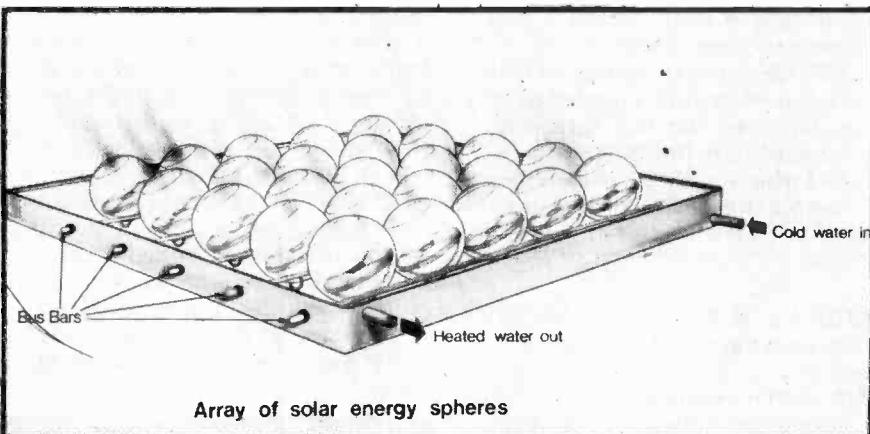

Football-sized plastic eyeballs that move to keep looking at the sun and convert the light directly into electricity are being developed by a British research establishment. Standard Telecommunications Laboratories, are working on what researchers there refer to as "solar eyeballs" which automatically follow the movement of the sun by a new type of self-contained magnetic drive.

Each one of the eyes can give up to one volt, but greater output is possible by using several of the units. To allow them to move freely, the eyeballs are floated in a water tank, the sunlight shines through ball's lens and on to the solar cell. As the sun moves,

CORDLESS HEADPHONES

Those long trailing headphone cords may soon be a relic of the past. Sennheiser, Siemens and Beyer all have cordless systems either in production or under development.

Beyer's system is now available in the USA and that from Sennheiser should be on the market very soon.

In all these systems an infra-red transmitter is connected to the audio amplifier output and floods the listening area with harmless and invisible infra-red radiation.

The infra-red carrier is modulated by a frequency modulated carrier of about 90kHz. The frequency modulated signal is of course multiplexed to accommodate the two separate channels of a stereo system. The infra-red signal is received by small sensors mounted on the individual head sets. In fact this system is now available in Britain, but only for use from television receivers. The set in question is made by Normende and sells at £750. Further details from Vessco, Unit 4, Blackwater Way, Aldershot.

light tends to wander off the solar cell, which is surrounded by four gas reservoirs rather like four large petals. When the sunlight touches any one of these the gas inside expands and moves a small magnet inside the eyeball. This reacts with an outside field and the unit is 'nudged', aligning it with the sun again.


STL researchers emphasise that the device is still under development and cannot forecast when it could be offered for sale. However, it is tentatively predicted that for a peak output of one kilowatt cost would be about £350 to £500.

STC Labs, London Road, Harlow, Essex.

news digest

HEATHKIT ENTER THE EDUCATIONAL MARKET

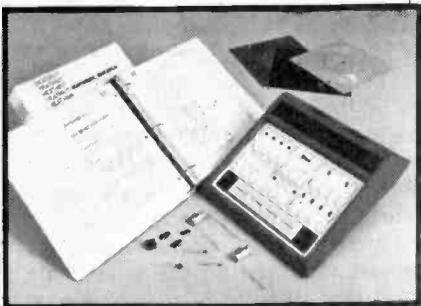We have news that Heathkit are about to enter the educational electronics market with a series of "individual Learning Programmes". These are designed as a series of separate progressive courses. The user who has a fairly good background knowledge could opt to start with a more advanced course.



The various 'programmes' available are designed to follow each other. As an example of cost the Fundamentals course — which includes three separate sections — will sell for about £90 including an experimenter/trainer — a type of super breadboard.

Other courses so far announced include Digital Techniques which, incidentally is so up-to-date that it includes microprocessors.

ETI has not yet studied any of these courses as, at the time of writing they have not yet been officially announced, but Heathkit's approach to kits makes them an ideal initiator for such a scheme. We hope to report on one of these courses in the near future.


BUDDY CAN YOU SPARE AN MPU?

RCA have been without success in finding a second-source for their CDP 1800 microprocessor in the USA. Motorola and Intersil are believed to be amongst those hardening their hearts to RCA pleas for a supplier.

HONEYWELL PASSES ITS 'A' LEVELS

Honeywell computers have gained entrance to Aberdeen University, replacing an ICL 4/70, which has presumably been sent down. This is the first time that Honeywell have managed to sell to a British university, who have traditionally tended to buy from IBM or the British firm ICL. Aberdeen give their main reason for buying the Level 66 machine as being the advanced 'database' system it incorporates. This is a field with which the University has been closely involved.

POT OF LIGHT

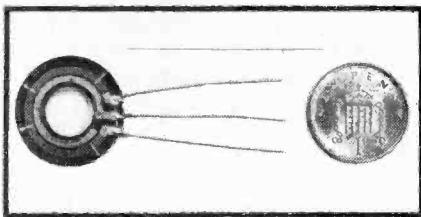

This new device titled the MPC 1054 consists of a photoconductive cell manufactured in circular form with an effective stroke of 290 degrees and has a variable output resistance relative to the position of light falling upon the cell. It therefore acts as a conventional potentiometer but the output is completely isolated from the input so electrical noise or interference cannot be transferred from one part of the circuit to the other. Light passes through a slit 1mm wide to fall on the photoconductive cell and as this light moves around the cell area the resistance is varied relative to the position of the light.


Photain Controls Limited, Unit 18, Hangar 3, The Aerodrome, Ford, Sussex.

PORTABLE PRINTING CALCULATOR

A printing calculator which fits easily into a briefcase has been introduced by Hewlett-Packard. Operated by rechargeable battery or mains the HP91 weighs less than two and half pounds including batteries. The HP91 is priced at £310 including VAT.

The calculator is a more powerful version of the widely-used HP45 pocket calculator with all the pre-programmed functions of the HP45.

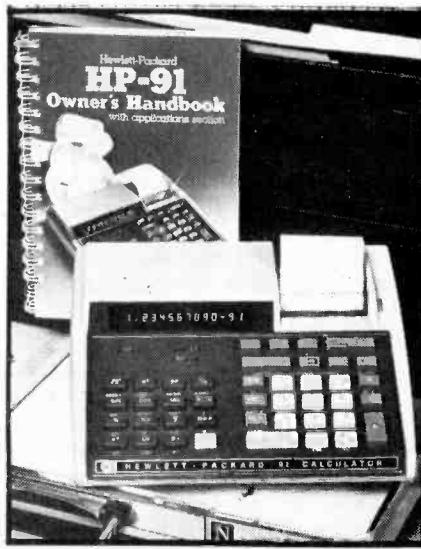Hewlett-Packard Limited, King Street Lane, Winnersh, Wokingham, Berks.



DOWN TO EARTH WARNING SYSTEM

A ground proximity warning system, which will alert pilots when they are dangerously near ground or water, will become mandatory for British public transport aircraft from 1st January 1977. A suitable system, designated AD 2610, will be produced by Marconi-Elliott.

The system gives a computer-generated audible command to "pull up" if the aircraft approaches the ground too quickly. It takes inputs of flap and undercarriage position, radio altitude, barometric rate of descent and ILS glide path deviation in making assessment. The system actually "speaks" the words "pull up . . . pull up . . . pull up" until the pilot recovers the situation safely. The design is considered to be the most advanced in the world and can be programmed to meet specific safety requirements.

STOPWATCH STOP PRESS

Marshalls have informed us that the price for the Stopwatch kit is £3.50 not £2.50 as shown in our last issue. We also heard from our readers that all is not well with the Novus 650. It has been modified. New models are not convertible. Yet do not despair, we have arranged with Novus to supply a large number of the older type to readers through us. If you intend to build the project your safest course is to order the calculator through us.

However should you wish to purchase from a shop check the serial number before buying. Models earlier than 80000 are likely (but not guaranteed) to work.

A few readers are having trouble getting a Novus 650 to count at the required rate for this project. To cure this hang-up it is necessary to change the resolution to 1/50th sec, and make the device add '2' at each increment. The modification needed is as follows;

Increase C5 to 0.1uf, R7 to 150k, and C8 to 0.015uf. Take the wire from pin 8 IC2 to pin 17 IC3, and connect it to pin 16 IC3 instead.

Bi-Pre-Pak Price Correction

Bi-Pre-Pak of Westcliff-on-Sea ask us to bring to your attention a wrongly quoted VAT rate from their "Super Spark MK.V" advertisement in this, and last, months ETI. The advertisement shows 25%, whereas the correct rate is only 8% making VAT 64p and 84p respectively and not £1.99 and £2.62 as readers might be led to believe.



FREE Brochure on New KITS

Whether professional,
student, teacher or amateur,
the field of electronics can open
up a new world for you.

Please add 15p to cover postage plus 10" x 12" self-addressed envelope.



CROFTON don't just sell kits, we offer you a technical back up service to ensure your success

The following is a selection of some of the more popular kits -

- ★ Mullard CCTV Camera
- ★ PE CCTV Camera
- ★ The 'Mistral' Digital Clock
Kit £12.50 incl. VAT + p.&p. 50p
Built £18.00 + p.&p. 50p
- ★ Electronic Ignition
- ★ Sound Operated Flash
- ★ PW Tele-Tennis Game
- ★ U.H.F. Modulator
- ★ Bench Power Supply
- ★ Wobbulator
- ★ All ETI Top Projects
- ★ Many of the Elektor Projects

NOTE: PCBs for most published projects available to order

CROFTON ELECTRONICS LTD

Dept. C, 35 Grosvenor Road, Twickenham, Middx. 01-891
1923

ETI PCB's

TITLE	PROJECT NO.	ISSUE	BOARD NO.	TOTAL INCL.	TITLE	PROJECT NO.	ISSUE	BOARD NO.	TOTAL INCL.
Int. Stereo Amp. 25 watts/chan.	Int. 25	Oct. 1975	Int. 25	£4.21	Tape Slide Synchroniser	513	Top Project No. 2	026	
Dual Power Supply Wide Range Variable	105	Apr. 1972	014	£1.48	Digital Stop Watch	520	Jan. 1974	520A	£2.05
12V Power Supply	107	Oct. 1973	022	£1.09	Electronic One Arm Bandit	529	Sept. 1975	529A	50p
Thermocouple Meter	111	Jan. 1973	111	£1.43	Temp. Controller	530	Mar. 1975	530	85p
Dual Beam Adaptor	113	Dec. 1973	113	£1.57	Photo Timer	532	Sept. 1975	532	87p
Impedance Meter	114	Oct. 1974	114	£1.00	Digital Display	533	Oct. 1975	533A	68p
Digital Voltmeter	116	June 1975	116	£1.01	Radar Intruder Alarm	702	June 1975	702	88p
Simple Freq. counter	117	Oct. 1975	117A	68p	Light Dimmer		Apr. 1975		£1.13
The Revealer	118	Nov. 1975	118	68p	Intruder Alarm		Sept. 1973		68p
Brake Light Warning	303	Oct. 1972	007	68p	Digital Alarm Clock				94p
Automatic Car Theft Alarm	305	Aug. 1972	019	99p	Timetronic Utiliboard	5017	Nov. 1975	AA/BB	£1.68
International Battery Charger	309	Nov. 1973	309	98p					
Electronic Ignition	312	May 1975	312	£1.72					
CDI/Tacho									
Auto Amp	314	May 1975	314	75p					
ET Four Input Mixer	401	Top Project No. 2	005A	67p					
Super Stereo	410	Top Project No. 2	025	£1.51					
100W Guitar Amp Master Mixer	413	Feb. 1973	413	£1.73					
	414	Top Project No. 1	414A	£1.44					
			414B	£1.52					
			414C	£1.52					
Stage Mixer	414	July 1975	414E	£1.89					
			414F	£1.78					
Mixer Pre-Amp	419	Dec. 1973	419	91p					
International 420 Four Channel Amp	420	Apr. 1974	420A	76p					
			420B	£1.11					
			420C	£1.21					
			420D	£1.21					
Discrete SO Decoder	420E	June 1974	420E	£1.59					
Int. 422 Stereo Amp 50 watts/Chan.	422	Aug. 1974	422	2.97					
Plus Two Add on Decoder Amp	423	Nov. 1974	423	91p					
Stereo Rumble Filter	426	Jan. 1975	426	76p					
Simple Stereo Amp	429	Mar. 1975	429	76p					
Line Amp	430	July 1975	430	76p					
Photographic Timer	512	Aug. 1972	023	76p					

The above mentioned are a few of the more popular boards - for prices of any boards not mentioned phone or write, sending 15p. Prices include VAT and P & P.

CROFTON ELECTRONICS LTD.
Dept. C, 35 Grosvenor Road, Twickenham, Middx. 01-891
1923

Sparkrite mk2

Capacitive discharge electronic ignition

VOTED BEST
OF SYSTEMS
TESTED BY
'POPULAR
MOTORING'
MAGAZINE



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRIDES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded: Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For CRYPTON tuning and fitting service — 'phone (0922) 33008.

PRICES INCLUDE VAT, POST AND PACKING.

Improve performance & economy NOW

POST TODAY!

**Quick installation
No engine modification
required**

**Electronics Design Associates, Dept.,
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652**

Name

Address

ET 1/5

I enclose cheque/PO's
for £

Cheque No.

Mk. 2 DIY Ass. Kit @ £11.80 QUANTITY REQ'D.

Mk. 2 Ready Built Negative Earth @ £14.97

Mk. 2 Ready Built Positive Earth @ £14.97

Ignition Changeover switches @ £4.30

R.P.M. Limit systems in above units @ £2.42

Send SAE if brochure
only required.

VIEWDATA

Trials are currently being conducted by the British Post Office linking your TV set via the existing telephone lines to a central computer. In a few years from now you may be able to summon up information from literally millions of 'pages' for display on your TV. Angus Robertson reports.

EVEN TODAY you can use your telephone other than for speaking to someone else: you can have a bedtime story (01-246 8000) or find out about skiing conditions in Scotland (031-246 8041) but this is mundane compared to Viewdata service that is being planned.

Virtually everyone has a TV set, most people have access to the telephone and viewdata is a marriage of the two: a new type of information service.

In many ways Viewdata is not unlike Teletext; relatively simple digital codes instruct a character generator in, or adjacent to, the user's TV to provide the display. However, Viewdata, unlike Teletext, has the potential for two way communication and will allow the user to enter data into the system as well as receive it.

Only information requested by the customer is transmitted to the Viewdata receiver unlike Teletext where the entire programme content is being transmitted continually, and the receiver 'catches' a page as it is broadcast. The maximum capacity of broadcast Teletext as included in field blanking at present, is 800 pages per TV channel and this gives a worse case access time of about three minutes for a particular page. Increasing page capacity would increase this access time and the service would thus deteriorate. However, with Viewdata, data base size is only limited by the cost of the computers and disc storage involved; ultimately many millions of pages could be available with an access time of only a couple of seconds.

Information suppliers

At this stage, the marketing phase of Viewdata has just begun but over the next two to three years the Post Office hope to finalise the service available to subscribers. The PO does not intend to supply information for the Viewdata network — it will just provide the hardware for information storage and the means for subscribers to



How a Viewdata receiver might be used. In the current experiment 200 pages are available. This prototype design — one of many — incorporates the 'phone with the receiver probably useful in commerce. Domestic installations are unlikely to incorporate the two as only a simple wire need be run from the phone's junction box to the TV.

gain access to this data base. The idea is for information to be supplied by commercial and other organisations who will either have terminals for inserting information into the data base or have their own computers connected, via a date link, to the Viewdata computers and data base.

Possible services

Information available should include news, entertainment, holidays, education, professional information, telephone directories, classified advertising, shopping hints, a calculation service, and reference material. It will be possible, for instance, for restaurants to advertise the daily menu and eventually for a subscriber to reserve a table and order the meal over the Viewdata system. Similar reservation systems could operate for hotels and theatres. It will also be possible to send messages to other Viewdata subscribers.

Although an alphanumeric keypad will be available, enabling subscribers to compose messages, those with only a numeric keypad should be able to use pre-written messages such as "Please meet me at the station at —", the time being inserted using the numeric keypad. The user number of the called subscriber is also inserted, the message stored in the system; it may prove possible to arrange for a light to be operated on the call subscriber's receiver. When this is noticed and the Viewdata centre called, the stored message is received.

Classified advertising also has considerable possibilities. Using the special editing facilities authorised information suppliers could undertake to have an advert written and inserted into the Viewdata data base where it could be classified by subject (Ford Cortinas, 1974 registered). Potential customers would select the particular heading of interest, see the advertisement and

could then reply either using the telephone or Viewdata. When the sale is completed, the advertiser would remove the advert from the data base so as not to be bothered by other would be purchasers. This ability to convey decisions might eventually become available, but is not considered likely in the first stages.

Another interesting interactive service would be games, either with another subscriber or with the computer. A game similar to *Mastermind* has been demonstrated where the player has to guess a four digit number with help from the computer. Chess might be another possibility. Unfortunately, games and such interactive services make considerable demands on computer processor time, moreso than simple information retrieval, and the availability of these services depends upon the cost of computer time being considerably reduced and on their not adversely affecting normal retrieval operations.

Operation

The following system will be employed to obtain information from the Viewdata system. Using the telephone dial (or keypad) the Viewdata centre is called — an automatic dialer might even be provided. A characteristic high pitched tone is received when the computer answers and a button is pressed which connects the Viewdata receiver to the telephone line. The subscriber is greeted by the computer and a subscriber identification number requested — later this might be signalled automatically like a telex answerback. Upon proper identification being received (for charging purposes etc), the Viewdata index is displayed, listing ten different categories of information.

Using the numerals on the keypad (fig. 1), the digit appropriate to the selection is pressed. A further index will be displayed and selection takes place until the desired page is located. In theory, six index selections would accommodate up to a million pages. To go back one page *0 is keyed, while the start again *#. Each page is individually numbered and may be directly selected using *(page number)#. The system is so designed that each step is explained with instructions on how to proceed displayed on each page. If an uncertain subscriber gets lost, simply keying *# enables the start to be reached from where a full explanation may be found.


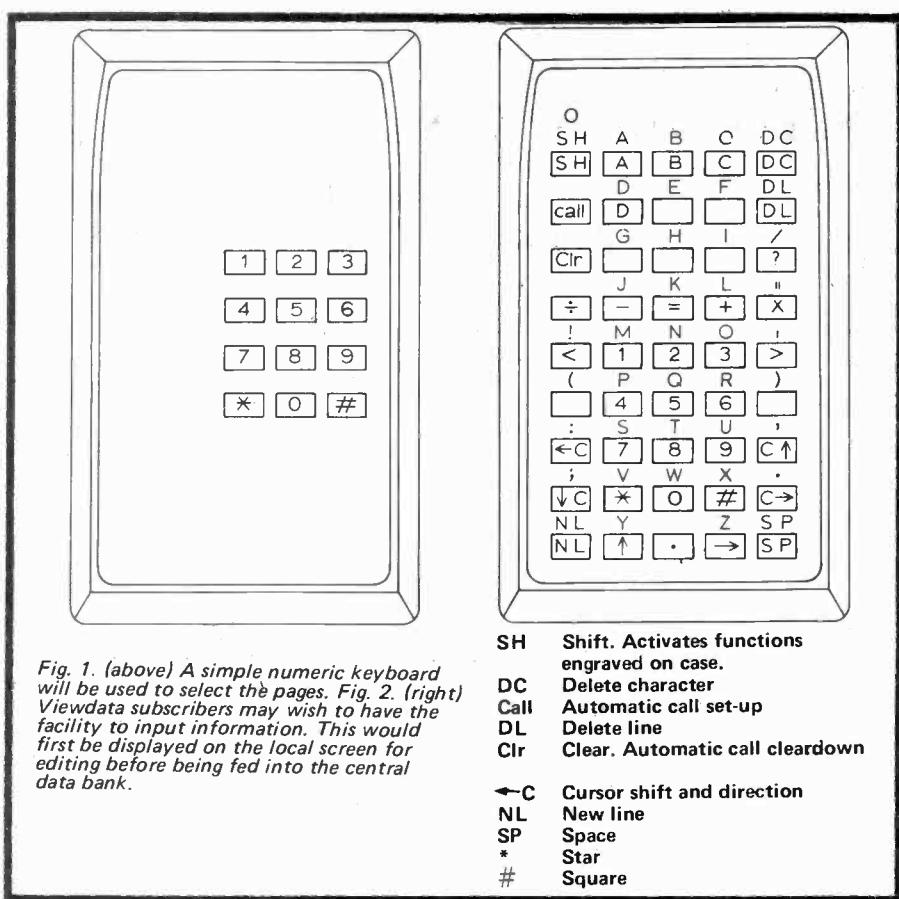


Fig. 1. (above) A simple numeric keyboard will be used to select the pages. Fig. 2. (right) Viewdata subscribers may wish to have the facility to input information. This would first be displayed on the local screen for editing before being fed into the central data bank.

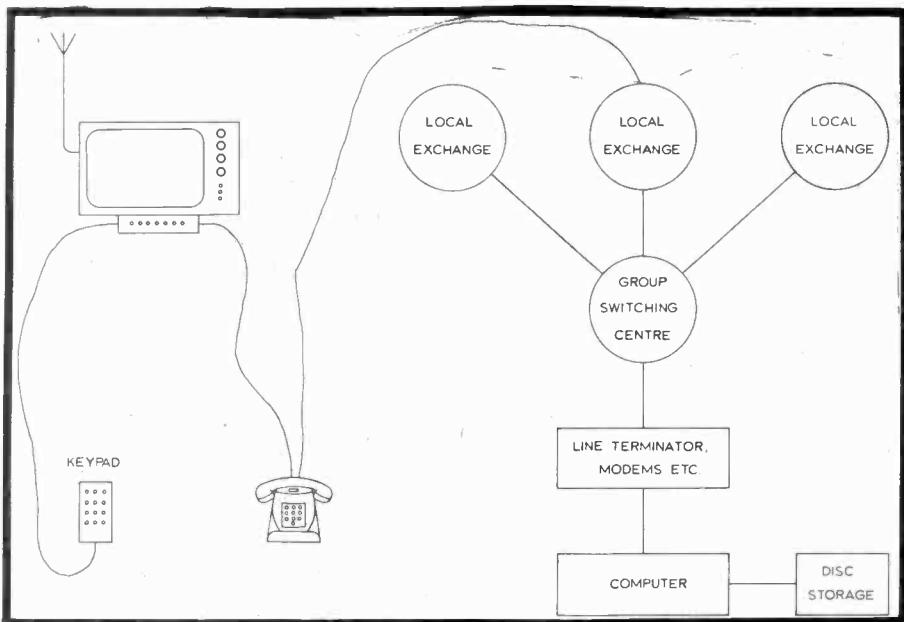

The GEC computers (rights) which are planned for use with Viewdata.

Fig. 3. (below) The connections of the telephone and TV to the central data store.



VIEWDATA

The 12 keys on the numerical keypad provide all the facilities required for Viewdata operation. However, to compose complex messages, perform calculations and such activities, an alphanumeric keypad, Fig. 2, could be supplied (this layout is still provisional). This new approach to keypad design is necessary since the standard *qwerty* typewriter layout is the wrong format for a hand held keypad. It is also considered simpler to operate for those unfamiliar with a typewriter. A keyboard layout similar to that of the typewriter would be available for business environments. The same data code used for display is used by the keypad for transmission to the computer. Keypad characters are returned by the computer to the receiver so that it does not need to display characters directly. Of course, no direct connection between keypad and decoder is necessary — either ultrasonics or infra red could be used.

Two further possibilities exist to complement the receiver. A cassette recorder could be used to store Viewdata information for later viewing. This would also enable a large amount of information to be 'dumped' by the decoder, this taking only a maximum of eight seconds for each page while connected to the computer instead of the time required to read each page while on the line to the computer. Since both telephone and Viewdata charges may be charged on a duration basis, this could offer substantial savings in cost for the subscriber. Additionally information could be printed out as hard copy for permanent storage.

Viewdata system

Figure 3 shows how the Viewdata system is engineered. Either a Viewdata only or Viewdata/Teletext decoder may be used. Although initially these are extra units which might be hardwired into the TV receivers (or monitors), it should be possible to buy or rent self contained sets from normal retail companies eventually. The PO will only be supplying the telephone instrument and a line access unit, which will interface and isolate the telephone line from the receivers.


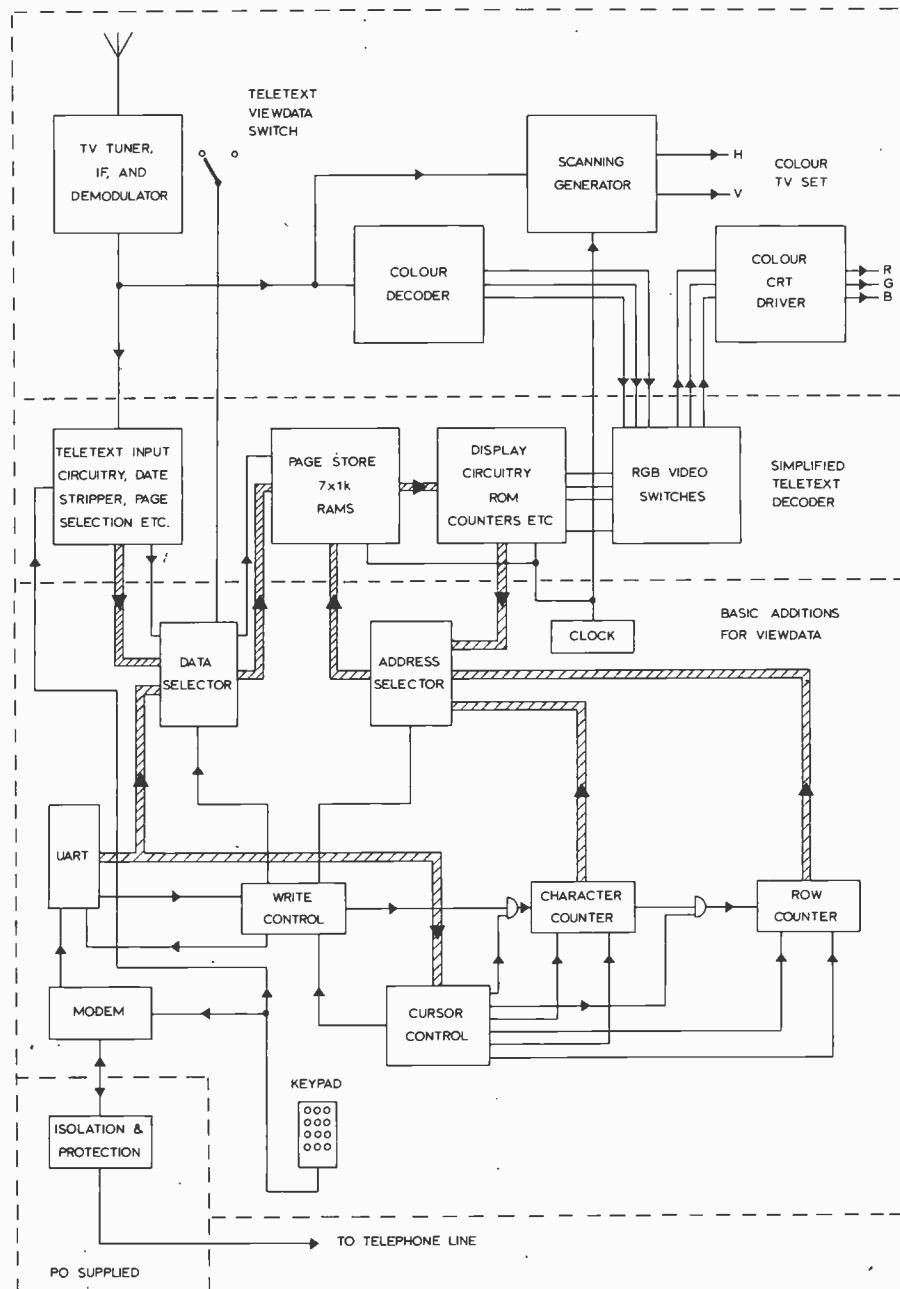


Fig. 4. (above) Block diagram of the circuitry necessary to receive Viewdata.

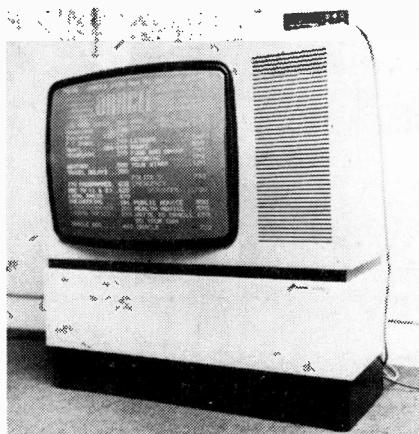

A Rank prototype receiver displaying Teletext. It is proposed to add Viewdata facilities as little additional circuitry is necessary. The Post Office hope that Teletext receivers will incorporate the Viewdata facility when the former become available.

Naturally the PO has no desire to receive any of the lethal voltages, using the TV sets down their lines and are going to take steps to protect themselves!

During the present pilot trial data is sent down the phone line using the Datel 600 system. In this, the digital information from the computer is frequency shift modulated using a 1,200 baud (bits per second) circuit between computer and subscriber and a much slower circuit of 75 baud for the keypad computer circuit. A modem (MOdulator DEModulator) is used at either end of the telephone circuit to effect this frequency shift modulation and demodulation. It is possible that the send speed may be increased to 2,400 baud at some later date.

The page format for Viewdata is identical to Teletext with 24 rows of 40 characters on each page with seven colours and full graphics facilities. Storage and display circuitry is common between Teletext and Viewdata decoders, see Fig. 4. The TV set is shown at the top, a simplified Teletext decoder in the centre with the basic additions required for Viewdata at the bottom. Serial digital data is accepted by the UART (Universal Asynchronous Receiver/Transmitter, a standard IC) which detects any errors in transmission (parity) and converts the data to parallel format for further manipulation.

The data selector allows this information to be stored while the cursor control keeps tabs on the characters and rows received. This information is fed, via the address selector, to the page store RAM which supplies characters to the display circuitry where alphanumerics and graphics are generated. Since the receiver may be operated while broadcast signals are not being transmitted, a clock with dividers is used to synchronise the line and field scanning generators. Unlike Teletext systems, TV synchronising information is not transmitted by Viewdata.

Decoded video is intercepted in the receiver before the CRT drivers



Another prototype Viewdata receiver.

and either Teletext or Viewdata electronically substituted. This means that colour characters may be displayed without using an expensive colour encoder but does mean that the Teletext/Viewdata decoder must be wired into the set. It would however be possible to display monochrome pictures using an RF modulator and plugging into the aerial socket but this would degrade the quality and increase the cost.

Although the basic character format of Viewdata is identical to Teletext, changes have been made in the use of control characters (carriage return, line feed etc), to provide compatibility with CCITT ISO-7 characters for line transmission. Since this does not provide for the necessary control bits for transmitting colour and graphics, an escape sequence is used which acts like a shift key on a typewriter and

changes the meaning of following characters.

The Viewdata centre is presently located at the Post Office Research Centre but eventually, depending upon demand, computers will be installed adjacent to many at the computer centre group switching centres, see Fig. 3. Line termination consists of automatic answering and a modem. This currently twin interfaces to the GEC 4080 computers which have a present disc storage of 5 Mbytes (about 5,000 pages) but another 70 Mbytes are planned to be added later this year. When a page is selected, this is transferred at high speed into a core memory in the computer from where it is read out at slow speed to the Viewdata subscriber. Future systems will use a line card with a page of memory and dedicated hardware to remove pressure from the computer core storage.

A pilot trial is currently taking place in which manufacturers of terminal hardware and potential information suppliers are working with the PO in developing the system. A market trial is due to start in September 1977 with a sample of 500 members of the public connected to the system and if this trial is successful, the full Viewdata service will open in the latter half of 1978.

BARGAIN SALE

Ideal for students, mathematicians and scientists

ACCRON 897 Scientific

(Pocket size)



Main Features

- 8 digits, LED display
- Basic Arithmetic Functions (+ - x / ÷) plus V, 1/x
- Trig and inverse trig functions (Sin/Cos/Tan/Sin⁻¹/Cos⁻¹/Tan⁻¹)
- Logarithms (LN/LOG/e^x/y^x)
- Change sign key (CHS)
- Free floating decimal point
- Battery saving device
- Degree/Radian selection
- Reverse polish notation
- Error indication
- Independent memory
- Cancel last memory



ACCRON 861

(Pocket size)

- Main Features:
- 8 digits, green display
 - Basic Arithmetic Functions (+ - x / ÷) plus % and V
 - + - change sign
 - Automatic constant
 - Free floating decimal point
 - Chain calculations
 - CE cancel last entry key
 - Overflow indication

PRICE:

£5.95
inclusive
VAT



ACCRON 877

(Desk Top)

- Main Features:
- 8 digits, green display
 - Basic Arithmetic Functions (+ - x / ÷) plus % key
 - Low power consumption
 - Automatic constant
 - Four keys' memory
 - Chain calculations
 - Overflow indication

PRICE:

£12.95
inclusive
VAT

PRICE:

£10.95
inclusive
VAT

Include 50p P&P
Please allow 14 days
for delivery



ORDENDALE LTD. Tel: 01-723 0243.
367 Edgware Road, London, W21BS

I enclose my cheque for £ to cover the cost of my:


897 861 877 calculator
(please tick)

Name

Address

1 YEAR GUARANTEE ON YOUR
'ACCRON' CALCULATOR

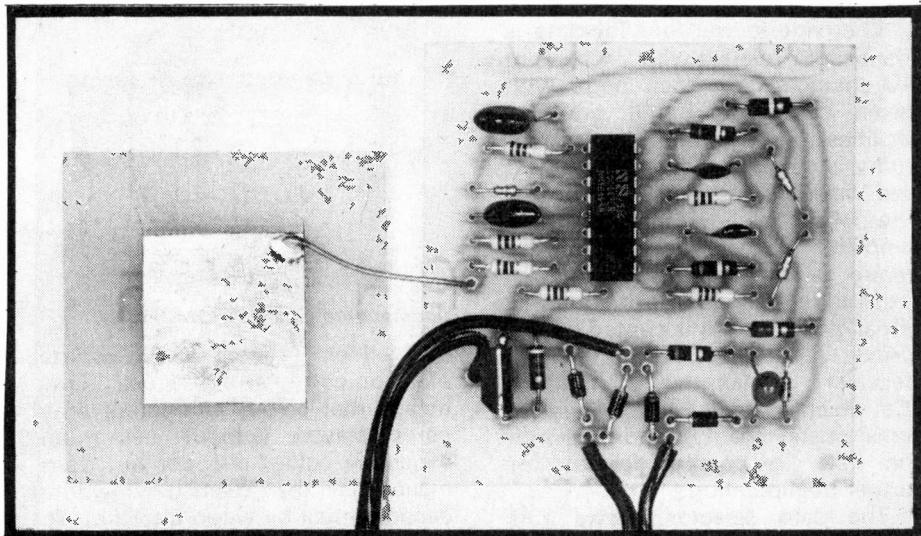New 240V design offers toggle action and complete safety.



TOUCH SWITCH

TOUCH switches are fascinating devices and have been in use for many years in lift controls. The circuit used in lifts usually consists of a high-frequency oscillator which has a touch plate connected to the tuned circuit. When the plate is touched the additional capacitance introduced either detunes the oscillator thus changing the frequency, or couples the oscillation into the detector and switching circuitry. This approach, whilst effective, is very expensive and thus touch switches of this type are not widely used.

Most of the touch switches published in electronics magazines to date have required the sensing element actually to be touched — usually via a series resistor of about one megohm or higher. Such circuits rely on body resistance to activate the switch, and are therefore not safe for use in controlling devices operated on 240 Vac.

In the touch switch described in this project, it was specified that the action of the switch should be touch-on touch-off, and that no actual contact with the circuit be made (for safety reasons). These constraints led us to use a capacitive circuit. The touch plate is in effect a capacitor. When this plate is touched, the input of the first stage is capacitively referenced to earth, however as the supply rails to the control circuit are floating at rectified 240 Vac the 50 Hz waveform effectively appears at the input of the control circuit and initiates the switch action. The actual contact plate is a piece of single-sided printed-circuit board arranged so that the *non-copper side* is touched — the copper on the other side is connected to the control circuit. Thus a full 1.6 mm of

insulation is always between the user and the circuitry at mains potential.

CONSTRUCTION

A touch switch may be constructed (and used) in many different ways. It may be mounted within the base of a lamp; fitted onto a conventional switch-plate to control overhead lights; or mounted in a piece of electronic equipment. It is however unlikely that the switch would be used as a separate unit and for that reason housing details have not been provided.

As stated above the touch plate is constructed from a piece of printed-circuit board as detailed in the drawing. The touch-plate need not be exactly as shown but can be any convenient shape or size. However make sure that the copper surface of the plate cannot touch any of the external metal surfaces and that it cannot be touched by the fingers. If the unit is to built into a lamp that has a plastic base a piece of aluminium foil may be glued to the *inner* surface of the base to act as the pickup plate.

If the plate is too large or the lead

connecting it to the circuit too long, stray capacitance to ground may be sufficient to prevent the switch operating. If the lead is more than about 50 mm long shielded cable should be used (shield connected to '0' volts not to ground). If a large plate is used the gain of the first stage should be reduced by changing the value of R2. (Try 3.3 M first and if this is not effective try 1 M).



The circuit given in the main circuit diagram supplies the load with pulsating dc and is therefore suitable to drive resistive loads (such as light bulbs) only. If an inductive load must be supplied the slightly more complex alternative circuit (shown in the insert) must be used. In this circuit the load must be inserted in the neutral lead if the switch is to operate correctly. Thus it is essential to ensure that the active and neutral are connected correctly. To make the changes required for inductive loads it is necessary to instal a link between D4/D6 and the anode of the SCR. The resistor R11 is removed from the board and D8 and the new R11 are glued to the board with epoxy cement.

SPECIFICATION

Mode of Operation
Triggering Mode
Power

touch-on, touch-off
capacitance
450 VA resistive
450 VA inductive*


*alternative circuit for load.

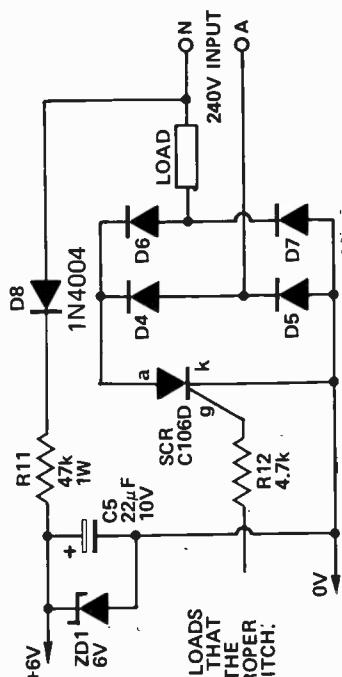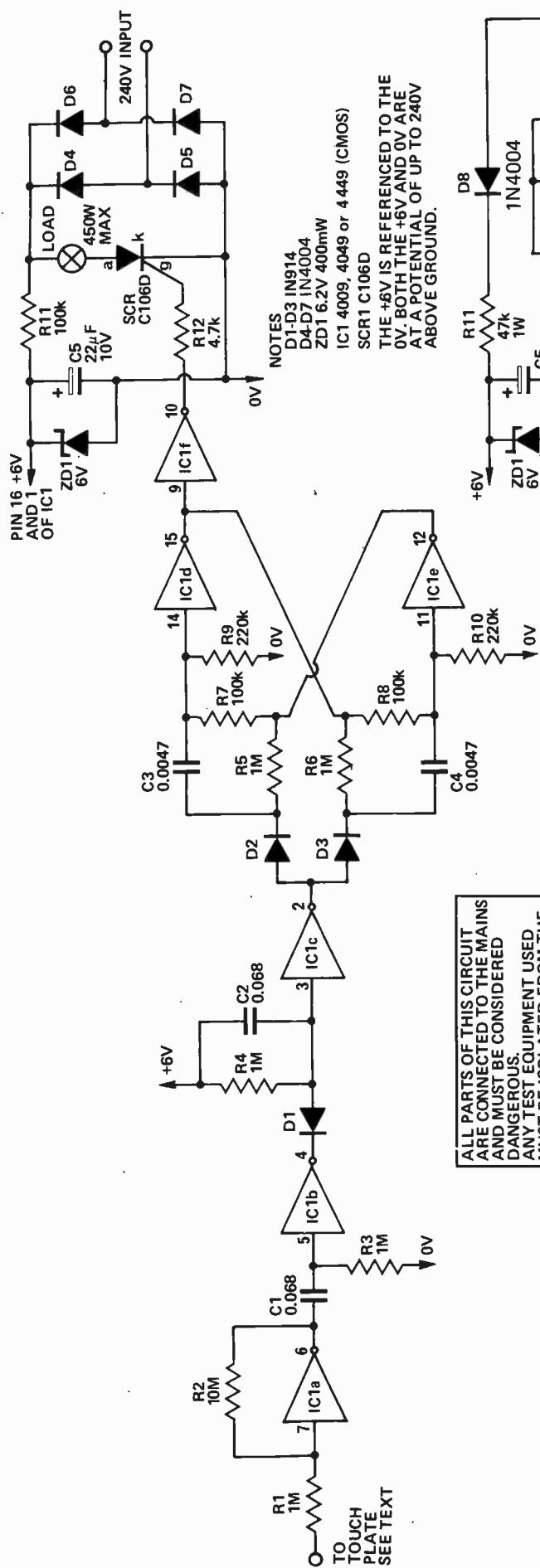

PARTS LIST - ETI 539

R1,3,4, 5,6	Resistor	1M 5% ½W
R2	"	10M " "
R7,8,11	"	100k " "
R9,10	"	220k " "
R12	"	4.7k " "
C1,2	Capacitor	0.068µF Polyester
C3,4	"	0.0047µF Polyester
C5	"	22µF 10V electro
D1-D3	Diode	1N914 or similar
D4-D7	"	EM404 or similar
ZD1	Zener Diode	6.2V 400mW
SCR	C106D	
PCB	ETI 539	
Case to suit		

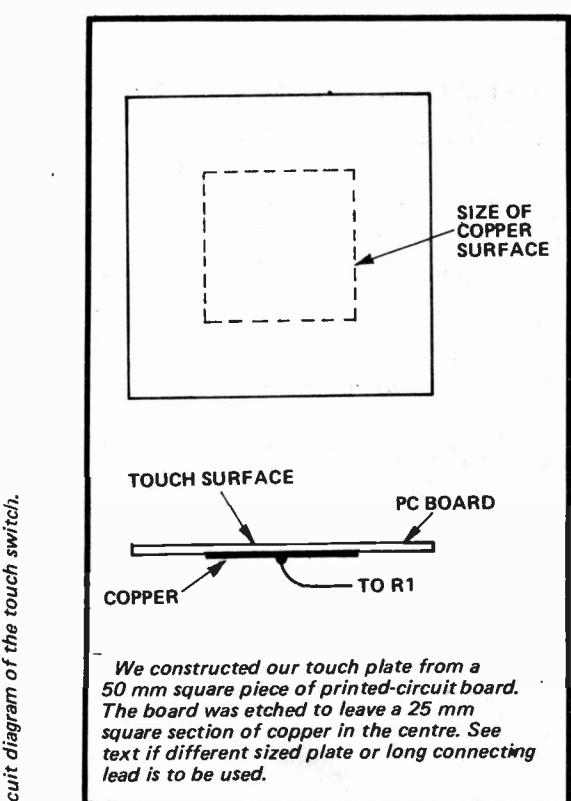For inductive loads change R11 to 47k 1W add D8 - 1N4004



We constructed our touch plate from a 50 mm square piece of printed-circuit board. The board was etched to leave a 25 mm square section of copper in the centre. See text if different sized plate or long connecting lead is to be used.

Circuit diagram of the touch switch.

HOW IT WORKS

POWER SUPPLY

The 240 Vac is rectified by diodes D4 to D7. The output of the diode bridge is then reduced, smoothed and regulated to 6 volts dc by R11, ZD1 and C5. The load is connected after the rectifier and has power switched to it via the silicon-controlled rectifier, SCR. Note particularly that the load is supplied with pulsating dc and therefore the type of load used with this circuit must be resistive, for example, an incandescent lamp. For inductive loads such as transformers etc, the load circuit must be modified as shown in the small diagram.

DETECTOR

The detector is formed by one section of a CMOS hex inverter, IC1a, in which the gain is set by the ratio of R2/R1. The touch plate is connected to the input of the detector and touching it effectively adds a capacitor to ground. However the '0' volt line (due to the diodes D4 to D7) when referenced to ground is effectively 50 Hz 240 volt rectified. The touch plate capacitance introduced therefore couples this waveform into the input of the

detector and over-drives the amplifier so that the output is a 50 Hz squarewave. If the plate is not touched the capacitance is very much lower and hence the output of the amplifier is very much lower in level. The sensitivity may be altered by changing the value of R2 (lower value gives less sensitivity).

LEVEL SHIFTER

The output of IC1a is centred about 3 volts, and C1, R3 and IC1b are used to provide level shift such that the output of IC1b is normally high at +6 volts until the plate is touched. When the plate is touched the output of IC1b oscillates between +6V and 0 V at a 50 Hz rate. The hex-inverter IC has diodes internally which connect each input to ground. Thus these diodes prevent the inputs from being driven below -0.6 volts.

PULSE STRETCHER

The 50 Hz output from IC1b is not in a convenient form and must be converted into a signal which is only high and stays high whilst the plate is touched. This is performed by a pulse stretcher and inverter consisting of IC1c together with R4 and C2. The

output of IC1c is normally low and goes high and stays high whilst ever the plate is touched.

FLIP FLOP



To meet our mode of operation requirement the circuit needs to be held on after the finger is removed from the plate and only switched off when the plate is touched a second time. Thus a toggle action is required and this is obtained by incorporating a flip flop formed by IC1d and IC1e. Cross coupling of gates normally provides an RS flip flop which may take up any state if both inputs are taken high together. For this reason the capacitors, resistors and diodes at the inputs to the flip flop are used to provide steering logic to ensure that correct toggle action is obtained.

BUFFER

To prevent loading the flip flop, and because a spare section of the hex inverter is available, a buffer amplifier is inserted between the flip flop and the SCR. The SCR used is a C106D which is a sensitive gate type. This particular SCR will operate reliably with the 1 mA gate current provided. The SCR specified will be used – don't try substitutes.

TOUCH SWITCH

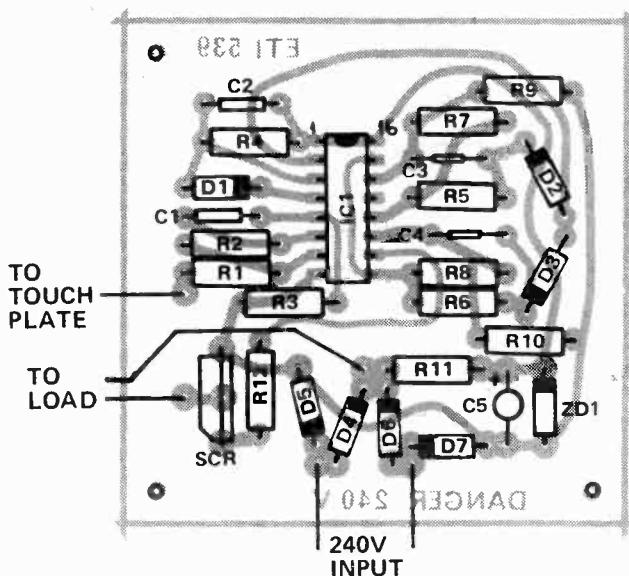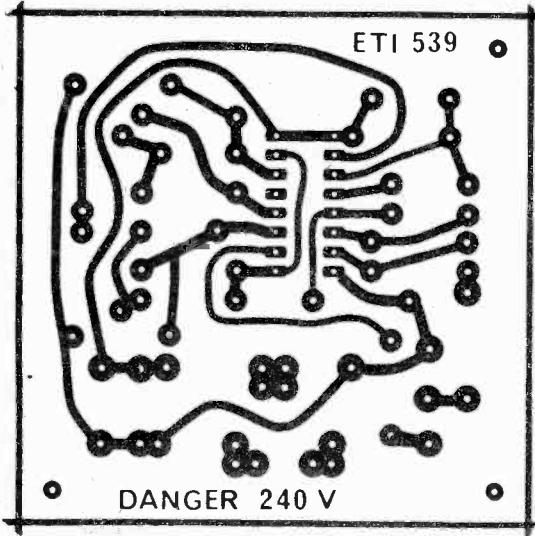Printed-circuit board layout for the touch switch. Full size 68 mm by 68 mm.



How the components are positioned on the board.

ELECTROVALUE

**the good components service
with a still more up-to-date catalogue**

In relatively few years, Electrovalue has risen to a position of pre-eminence as mail-order (and industrial) suppliers of semi-conductors, components, accessories, etc. There are wide ranges and large stocks to choose from as well as many worthwhile advantages to enjoy when you order from Electrovalue.

CATALOGUE 8 ISSUE 2

Second printing now ready, revised and up-dated on prices, etc. 144 pages. New items. Opto-electronics. Diagrams of components, applications, I.C. circuits. Post free 40p, including voucher for 40p for spending on order over £5 list value.

DISCOUNTS

On all C.W.O. mail orders, except for some items marked NETT.

5% on orders list value **10%** on orders list value
£10 or more £15 or more

FREE POST & PACKING

On all C.W.O. mail orders in U.K. over £2 list value. If under, add 15p handling charge.

PRICE STABILIZATION POLICY

Prices are held and then reviewed over minimum periods of 3 months, next review due April 1st.

QUALITY GUARANTEE

On everything in our Catalogue — No manufacturer's rejects, seconds or sub-standards merchandise.

ELECTROVALUE LTD


All communications to: Section 5/4, 28 ST. JUDE'S ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Telephone Egham 3603. Telex 284475. Shop hours 9.5-30 daily, 9.1 p.m. Sat.

NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 3NA. Telephone (061) 432 4945. Shop hours daily 9.5-30 p.m.; 9.1 p.m. Sat.

See our other advertisement for CMOS, Kits, etc.

DISPLAYS

High quality displays from major manufacturers backed by our usual no-quibble guarantee.

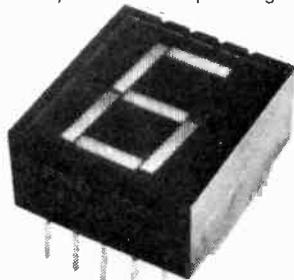

FND 500
Outstanding value:
Only £1.02 each, for
this high quality display

Part No.	Manufacturer	Colour	Type	Size	Price
FND 500	Fairchild	Red	Common Cathode LED	0.5"	£1.02
TIL 322	Texas Instr.	Red	Common Cathode LED	13mm	£1.20
TIL 321	Texas Instr.	Red	Common Anode LED	13mm	£1.30
XAN 654	Xiton	Green	Common Cathode LED	0.6"	£1.75
XAN 652	Xiton	Green	Common Anode LED	0.6"	£1.75
MAN3M	Monsanto	Red	Common Cathode LED	0.13"	48p
5LT01	Futaba	Green	Phosphor Diode	0.5"	£5.80

Note: TIL 322s, the Texas Instrument pin-for-pin equivalent of the FND500's, may be supplied instead of FND500's — please state if you would not want this substitution, e.g. if you want FND500's to match a previous purchase.

DISPLAY PCBs: See our other advertisement in this issue. Display PCBs for the FND500 are also suitable for the TIL322 with no modification.

Ask for display data sheet if required — free on request.
ADD VAT at standard rate (now 8%) — 25p p&p on all orders.

SINTEL

53a Aston Street, Oxford
Tel: 0865 49791

ENGINEERS

FREE

YOURSELF FOR A BETTER JOB WITH MORE PAY!

This 44-page FREE book shows how!

Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 44-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

ELECTRICAL & ELECTRONICS

- Practical Radio & Electronics (with Kit)
- Electronic Engineering Certificate
- General Elect. Eng. Certificate
- C & G Elect. Installations
- Elect. Install. & Work
- C & G Elect. Technicians

AUTO & AERO

- Motor Mechanics
- C & G Motor V Mechanics
- General Auto Engineering
- A.M.I.M.I.
- Air Registration Board Certs.
- MAA/IMI Dip.

MECHANICAL

- A.M.S.E. (Mech.)
- General Mech. Eng.
- Inst. Engineers & Technicians
- Maintenance Engineering
- Welding

MANAGEMENT & PRODUCTION

- Computer Programming
- Inst. of Cost & Management Accts.

DRAUGHTSMANSHIP & DESIGN

- General Draughtsmanship
- A.M.I.E.D.
- Electrical Draughtsmanship

RADIO AND TELECOMMUNICATIONS

- Colour TV Servicing
- C & G Telecoms. Technician's Cert.
- C & G Radio, TV & Electronics Mech. Certificate
- Radio & TV Engineering Course
- Radio, Servicing & Repairs
- Radio Amateur's Exam.

CONSTRUCTIONAL

- Heating Ventilating & Air Conditioning
- Architectural Draughtsmanship & Design
- L.I.O.B.
- Carpentry & Joinery
- Plumbing Technology
- General Building
- Painting & Decorating

G.C.E.

-58 'O' & 'A' Level Subjects
—over 10,000 Group Passes!

Aldermaston College

Dept. TET 14, Reading RG7 4PF

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5EJ. Tel. 01-628 2721.

NAME (Block Capitals)

ADDRESS

Postcode

Other subjects of interest

Age

Accredited by C.A.C.C.

Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

INTRODUCTORY PRICES

In addition to National, Mostek and Caltex clock chips, we are now selling a range of General Instruments chips.

Until 30th April, 1976, we are pleased to offer the following special prices:

AY-5-1202 + Futaba 5LT01

The AY-5-1202 chip interfaces directly with the 5LT01 to provide the basis for a very simple electronic clock. The hours and minutes can be in 12 or 24-hour format and 50 or 60 Hz can be used as the timing source. The rest of the circuitry is very simple and low in current requirements — a 100mA transformer with a 20v winding will be adequate.

Special price £9.50

AY-5-1230 + Futaba 5LT01

Basically this chip is similar to the 1202 but has many additional features. Mainly it has an ON/OFF programmable alarm which can be used in seven segment mode to drive the 5LT01 or in BCD mode to drive logic or TV display chips.

Special price £10.00

MK50253 + Futaba 5LT01

12 or 24-hour 6-digit alarm chip. Snooze facility.

Special price £10.50

COME AND SEE US AT SEMINEX

March 22nd-26th. Stand 11. Imperial College, SW7

Please send SAE for free ticket and new catalogue.

MISTRAL CLOCK KIT

Uses AY-5-1202 + Futaba 5LT01. Complete kit including case

£11.58

CHEVIOT ALARM CLOCK

24-hour 4-digit alarm clock, 0.5" green display, tilt to snooze. Finished clock — not kit

£21.85

PRICE LIST

CLOCK CHIPS

ALL PRICES EXCLUDE VAT AT 8%

NATIONAL

MM5309 7 seg + BCD with reset	1.9
MM5311 7 seg + BCD	5.69
MM5312 7 seg + BCD. 4 digit only	5.69
MM5313 7 seg + BCD	4.88
MM5314 7 segment	5.69
MM5315 7 seg + BCD with reset	4.88
MM5316 Non-mpx alarm clock	5.69
MM5318 7 seg + BCD (external digit select)	10.17
MM5371 Alarm clock 50Hz	3.36
MM5377 Car clock, crystal controlled, LCD	8.14
MM5378 Car clock, crystal controlled, LED	7.21
MM5379 Car clock, crystal controlled. Gas discharge	6.73

MOSTEK

MK50250 Alarm clock (12Hr+60Hz/24Hr+50Hz)	5.60
MK50253 Alarm clock (12Hr+50Hz/24Hr+50Hz)	5.60
MK50204 Stopwatch/Calculator	11.19
MK50395 UP/DOWN Counter—6 Decade	14.50
MK50396 UP/DOWN Counter—HHMMSS	14.50
MK50397 UP/DOWN Counter—MMSS.99	14.50

CALTEx

CT7001 Alarm/calender. 7 segment	5.60
CT7002 Alarm/calender BCD	7.30
CT7003 Alarm/calender 7 seg. Gas discharge	7.30
CT7004 Alarm/calender 7 seg	7.30
CT6002 LCD/CMOS. Clock/watch chip	15.00

DISPLAYS

LITRONIX	1.9	FUTABA PHOSPHOR DIODES	1.9
DL707, 704, 701	4.88	5LT01	5.80
DL727, 728, 721	5.69	5LT03	5.80
DL747, 746, 750	4.88		
	5.69		
	10.17		
	3.36		
	8.14		
	7.21		
	6.73		
	6.73		

FILAMENTARY DISPLAYS

Minitron 3017F 2.00

Itoka 2.5" 8.00

Itoka 5" 24.80

Liquid Crystal 1.50

Swarovski 3½ digit watch disp 10.00

MHI DISPLAY KITS

MHI-707/4 (digit) 0.3"	1.9	MHI-727/6 0.5"	12.00
MHI-707/6 0.3"	6.60	MHI-747/4 0.6"	9.80
MHI-727/4 0.5"	9.50	MHI-747/6 0.6"	14.70

PAYMENT TERMS

Cash with order. Access, Barclaycard (simply quote your number and sign). Credit facilities to accredited account holders. Pro-forma invoices can be issued.

Please send 20p for post and packing.

ALL PRICES EXCLUDE VAT AT 8%

MHI CLOCK KITS

MHI-5309	1.9	MHI-50396	19.50
MHI-5311	7.35	MHI-50397	19.50
MHI-5314	7.35	MHI-7001	10.00
MHI-5318	6.60		
MHI-5378	7.35		
MHI-50250	15.10	MHI CASE Please include 25p post + packing)	2.95
MHI-50253	8.35		
MHI-50204	8.35		
MHI-50395	14.00	SOCKETS	0.60
	19.50	18 pin	1.00
		24, 28 or 40 pin	1.00
		Soldercon strip sockets	0.30



BYWOOD ELECTRONICS
68 Ebberns Road
Hemel Hempstead
Herts HP3 9QRC
Tel. 0442 62757


FROZEN SIGNALS

Storage oscilloscopes let engineers 'see' into circuits more clearly. In this article, Ian Sinclair explains how they work and what they do.

IN A SMALL electronics laboratory, an engineer is watching an oscilloscope intently. The oscilloscope is displaying the mains waveform, and he is watching it for intermittent pulses which have been the cause of faulty triggering of thyristors in a power pack. After 30 minutes, his attention is slackening; it is unlikely that he will gain anything from the morning's work. In another laboratory a few miles away, the same problem is being solved. The engineer is working on a power pack, glancing at the oscilloscope only occasionally, for the intermittent spike on the waveform, when it occurs, will remain displayed for several minutes, bright enough to be photographed with a simple camera.

In the air traffic control room of a small airfield, the ATC officer is watching the radar pattern. Two planes show as dots glowing brightly when the revolving trace comes round then fading rapidly. The room is dimly lit so that the after-trace can be seen at all; it is difficult to remember which is the most recent part of the trace. On a busier airfield, the ATC officer works in normal lighting watching a screen when the traces remain at high brightness, fading with time so that the brightest part of the trace is the most recent. Moving echos stand out well from these from fixed objects, and the whole of the traces can be erased by the press of a button.

In each of these cases, the improvement is due to the substitution of a storage tube for a normal cathode ray tube. This is a tube similar in style to the conventional cathode ray tube but which offers the advantages of trace (or picture) storage, a persistence which can be controlled, the ability to erase a stored trace rapidly, very high screen brightness and complete choice of phosphor colour. These characteristics are due not to the phosphor of the tube but to its

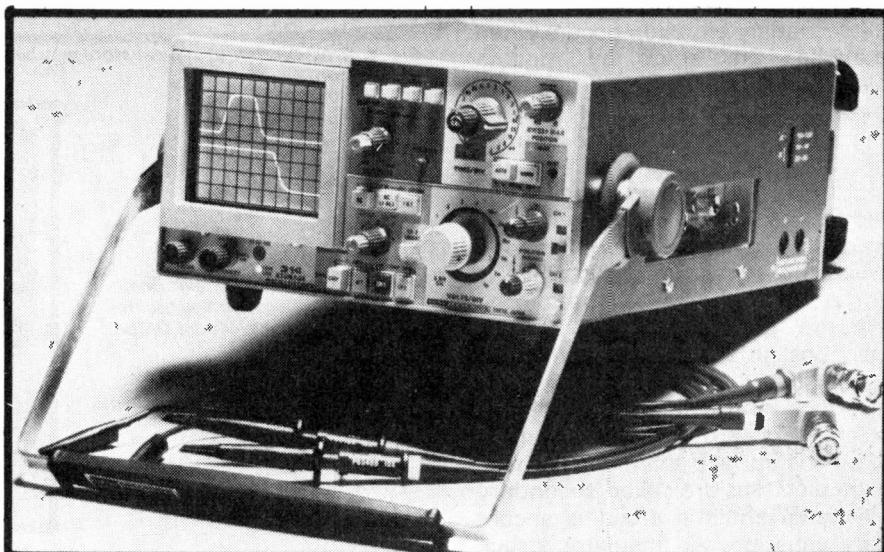

Tektronix Model 314 storage oscilloscope with a bandwidth of 10MHz.

electronic construction, and its working depends on three important physical principles: capacitor charging, coplanar grid control, and secondary emission.

PHYSICAL PRINCIPLES:

Capacitors consist of non-conducting materials sandwiched between conductors. When electronic charge (electrons) is taken from one conductor and placed on the other the capacitor is said to be charged and a voltage can be measured between the conductors.

The capacitance of the arrangement is the ratio Q/V , where Q is the amount of charge and V the voltage. When the charge is allowed to flow back or is otherwise neutralised the

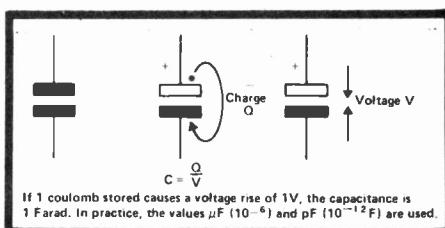


Fig. 1. Capacitor charging.

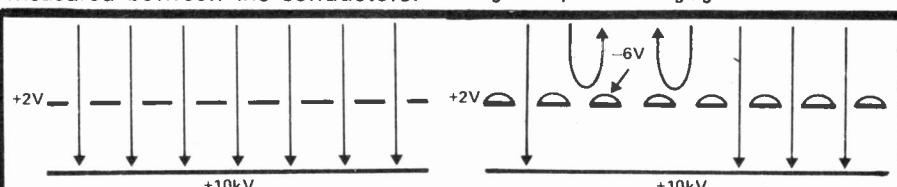


Fig. 2. Coplanar grid effect.

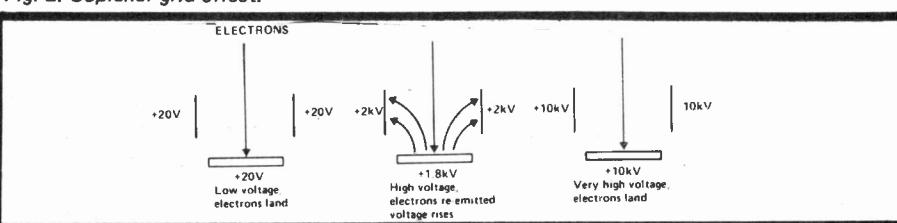


Fig. 3. Secondary emission.

capacitor is discharged and there is no longer a voltage between the conductors. Capacitor charging is vital to the storage tube, as it is the method of storing the signal information.

Coplanar grid effect is a method of controlling an electron stream by changing the voltage on a metal mesh. When the mesh is at a voltage slightly positive to the cathode of an electron gun, electrons pass freely through the holes of the mesh. A small negative voltage is enough to prevent this flow of electrons even if there is a positive voltage electrode on the other side of the mesh.

Secondary emission occurs when materials are struck by moving electrons. If the electrons are moving slowly they either stick to the surface they strike or bounce off. If the surface is an insulator, the electrons which land on it will reduce its voltage until no more electrons can land. This will happen when the voltage at the surface is about the cathode voltage of the electron gun. At faster speeds, electrons hit the surface with such energy that they can dislodge other electrons, and if there is a positive electrode nearby, more electrons leave the surface than hit it. These extra electrons are called secondary electrons, and the effect is secondary emission. An insulator struck by fast moving electrons loses more electrons in this way than it gains, and so rises in voltage (as it is losing negative charge, equivalent to gaining positive charge) until the voltage is about the same as that of the positive electrode near it. It cannot rise further as this would cause electrons to land (they could go nowhere else) and so cause a fall in voltage.

THE STORAGE TUBE

Fig. 4 shows the cross-section of a type of storage tube, showing how the electrodes are arranged. The screen has placed about 1cm away from it and parallel to it a fine wire mesh (about 500 meshes per inch in each direction) called the storage mesh. On the side remote from the screen, this wire is coated with an insulator with good secondary emission characteristics. The screen is a conventional aluminised phosphor screen as might be found on any other CRT. About 3mm from the storage mesh is another mesh, the collector, made of coarser wire angled to minimise the moire patterns which appear when two meshes are nearly in line.

The flood gun is an electron gun which is neither focused nor

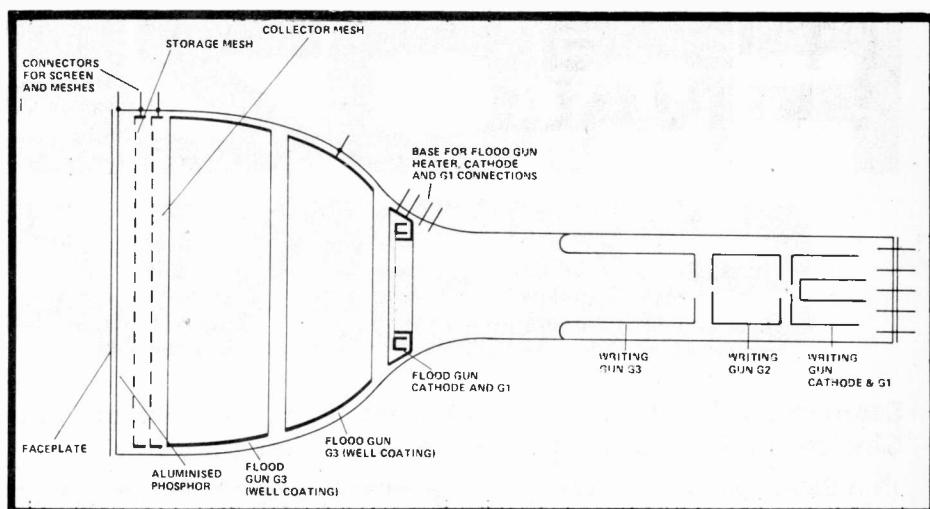


Fig. 4. Cross-section of typical storage tube (in this case, using magnetic deflection for writing gun).

Telequipment dual-trace storage oscilloscope, Model DM64.



deflected. Instead the electrons are spread out to form a parallel beam about the diameter of the storage mesh and uniform in density. The effect of the flood gun is, as its name suggests, to flood the screen with electrons so that the screen is uniformly bright. The brightness level of the screen depends on the rate at which electrons reach it, and this can be controlled by altering the voltage on the storage mesh, whose normal voltage is slightly more positive than the cathode of the flood gun. The voltage on the metal mesh is not the only one affecting electrons, however, as the surface of the insulator deposited on the mesh may be at a different potential. Because of coplanar grid effect, the potential of the insulator may take over control of the electron stream from the potential of the metal mesh.

INSULATOR POTENTIAL

We cannot change the potential of the insulator surface directly, but we can make use of the fact that the metal mesh will act as one plate of a capacitor and an electron beam hitting the insulator can act as another. Loss of electrons by secondary emission then completes

the picture of possible action at the insulator surface.


The charging and discharging of the insulator surface by flood gun electrons enables us to cut off the electron beam without permanently changing any of the supply voltages. Imagine a positive going pulse applied to the metal storage mesh; raising its potential by about 10V for a short time. By normal capacitor action the potential of the surface of the insulator will rise also by about 10V, and, in the absence of any other effect, would continue to follow exactly the potential variations of the metal mesh. There is another effect, however, the stream of electrons from the flood gun. Electrons, approaching a surface which is about ten volts positive, will land on the surface, and the negative charge of the electrons will steadily reduce the potential of the insulator surface until electrons can land no longer usually when the surface is at or slightly below flood gun cathode potential.

All of this takes place rapidly if there is a good supply of electrons from the flood gun, so that the potential of the surface of the insulator can be reduced rapidly to


FROZEN SIGNALS

cathode potential level while the metal part of the mesh is still held at +10V. Once the insulator surface has reached flood gun cathode potential electrons will no longer land on it, but will reflect. The collector mesh held at +200V, will then collect such reflected electrons and the potential of the insulator surface remains stabilised at about cathode potential.

When the potential of the metal mesh is lowered again from +10 to zero, the insulator will obediently also drop in voltage by 10V, ending up at -10V. This is similar to the previous change, except that now there are no electrons to land on the insulator, since it is too negative to allow electrons to approach.

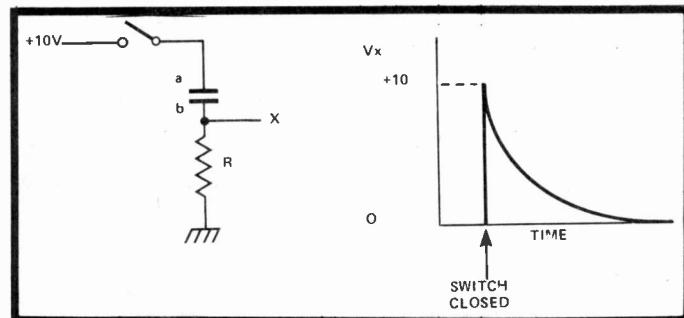

*Fig. 5 (below).
Equivalent circuit,
showing what happens
when a 10V potential
is applied to the
circuit.*

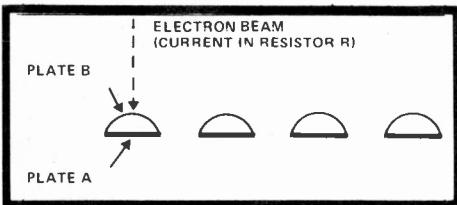


POSITIVE CHARGING

There are, in fact, only two ways in which the potential of the insulator surface can rise again with only the flood gun on. One is by leakage; if the resistance of the insulator is not very high, the stored charge maintaining the surface at -10V will steadily leak away through the resistance so enabling the potential of the surface to rise again. We can choose to use insulating materials whose insulation resistance is so high that the change of voltage by leakage is negligible, even for times of several months.

The other way in which the potential of the insulator surface can rise is by the landing of positive ions. These are particles very much heavier than electrons and carrying

positive charge, and they are formed when atoms of a gas are struck by electrons. The energy of the electrons splits up the gas atoms into positive ions and more electrons; if left alone these will recombine, giving out their energy in the form of light, a process used in neon lamps. In tubes such as the storage tube, despite the high vacuum, there are still large numbers of particles which will be split up by electrons to form positive ions, and the positive ions obeying the usual laws of electrostatics will be attracted to any negative potentials. In the storage tube, ions formed on the gun side of the collector mesh are not likely to cause any trouble, since they will be repelled from the storage mesh, but

When the potential on the insulator surface is negative and the flood beam is creating ions the ions will land on the insulator, raising the potential until it once again reaches flood gun cathode potential. It is unlikely to go much higher as there are more than enough electrons around to land on any positive surface and neutralise the effect of ions. The effect on the action of the mesh is that the steadily rising potential on the insulator will allow an increasing number of electrons to pass through the spaces in the mesh, so that the screen, which would be completely dark when the potential on the insulator was -10V would brighten up as the ions landed, ending up at full brilliance.

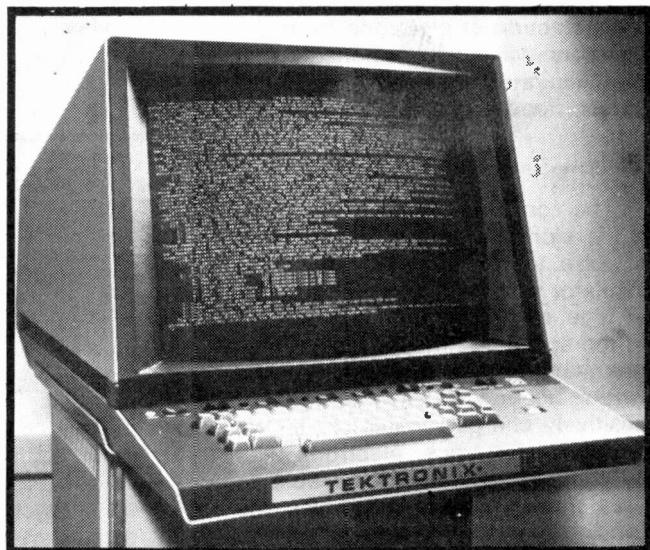

*Fig. 6 (left) Action of insulator on mesh,
shows similarity to
equivalent circuit.*

*Tektronix computer
terminal, fitted with
a 19" storage CRT.*

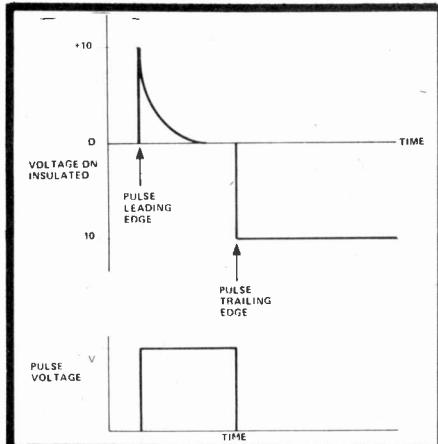


Fig. 7. Complete effect of single pulse on insulator.

there will still be a few ions formed in the space between the storage mesh and the collector mesh.

To summarise, a brief positive-going pulse on the metal mesh causes the insulator surface to end up negative (about as far below cathode potential as the pulse peak was above it), so cutting off the electron beam to the screen. Over a longer time as ions land on the insulator, the screen will brighten up and gradually attain full brilliance. The brightening up process takes about ten minutes, but can be delayed indefinitely if the flood gun is switched off (as for example by biasing the collector mesh negatively) when the display does not have to be viewed.

WRITING

So far, we have considered only the action of the flood gun which enables us to see how the insulator surface can be changed in potential without any direct connection being made. The action of the writing gun gives us another method of chang-

ing the insulator potential. The writing gun is a conventional CRT type of electron gun which is focussed and deflected; the deflection method may be electrostatic or magnetic, the focus is usually electrostatic. The gun is arranged so that the beam focusses on the insulator surface, and the cathode of the writing gun is about 2.5kV more negative than the cathode of the flood gun. This potential difference ensures that electrons from the writing gun which hit the insulator cause secondary emission of more electrons. The emitted secondary electrons then land on the collector mesh leaving the insulator surface more positive. The greatest potential which the insulator can reach during this process is that of the collector; if the writing beam is scanning across the insulator the action of electrons from the flood gun will in practice ensure that the insulator potential will not exceed flood gun cathode potential.

ACTION:

The complete action of the tube is therefore as follows. By applying a pulse to the storage mesh, the insulator surface is given a negative voltage, cutting off the electron flow to the screen. With the insulator in this state a trace scanned by the writing-beam will leave a track of positively charged insulator. In the region of this track, electrons will, by coplanar grid effect, be able to pass through the mesh holes, so causing the trace to appear on the screen. The trace will be stored, and will not decrease in brilliance; what limits its useful life is the decreasing contrast as the rest of the screen gradually brightens up around it. The brilliance of the trace depends on the phosphor efficiency and the screen voltage (typically 10kV) used and can be high enough for the tube to be usable in direct sunlight. The storage period can be extended if the flood beam is turned off while the tube is not being viewed.

ERASING:

Any trace or picture "written" with the writing gun can be erased. Total erase can be carried out by the same process as was used to clear the screen ready for writing, by applying a single positive pulse of about +10V amplitude and time exceeding 100ms. It is also possible to carry out a continuous erase, using repetitive pulses applied to the storage mesh. The pulses used must be of lesser width, a few μ s for example, and often of smaller

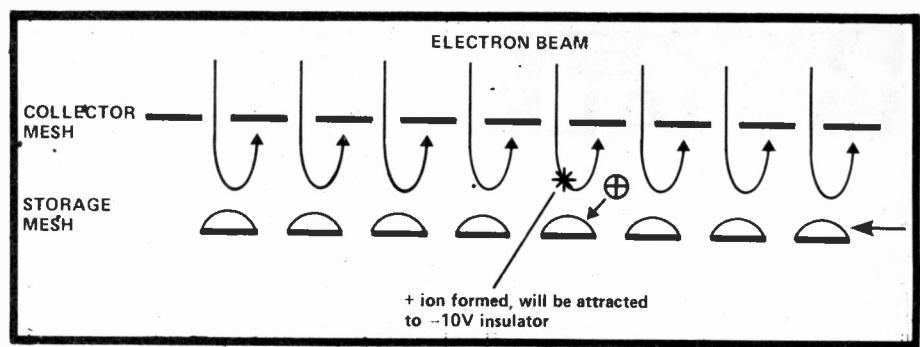


Fig. 8. Ions being formed and landing.


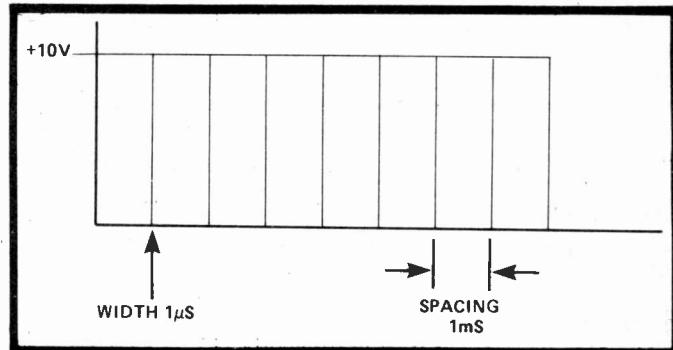


Fig. 9. Continuous erase pulses.

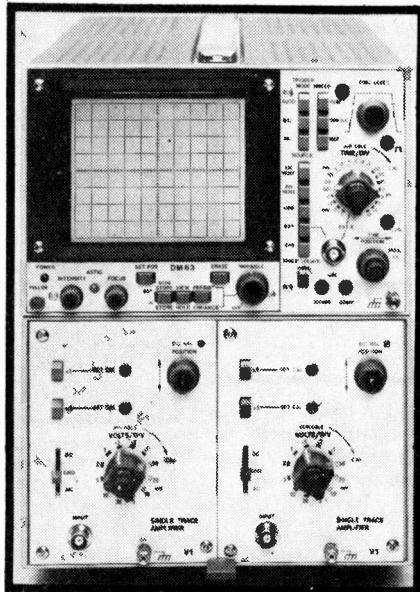

Telequipment dual-beam storage oscilloscope, Model DM63.

amplitude. Their effect is to erase continually, so that the trace fades out with the screen never reaching full brilliance. This is in many ways a more satisfactory display as the background brilliance of the unwritten part of the screen can be kept steady and fairly low. The unwritten portion can never be completely dark, as each pulse peak momentarily raises the screen to full brilliance, but the effect of the pulse train is simply of a faint glow on the whole screen, with newly written traces very bright, and older traces steadily fading into the background. This type of display is of particular use for radar, as moving targets show up as trails whose head is bright fading towards the tail.

Stationery echoes are of uniform brightness, enabling the operator to distinguish them instantly from the moving targets.

Selective erase is also possible on a more elaborate tube. If a third electron gun, similar to the writing gun, in every way but operated at a much more negative cathode potential of about 10kV relative to flood gun cathode, is added it can be used to bombard selected areas of the insulator surface with high energy electrons. At such high energies, the electrons, penetrate more deeply into the material and are retained so that the potential of the insulator is made more negative. Where such a beam is scanned, therefore, the insulator will be driven negative again sufficient to cut off the flood beam if necessary, and so giving the ability to erase selected portions of a picture or trace.

APPLICATIONS:

The use of this type of storage tube in an oscilloscope greatly extends the range of use of the oscilloscope, for very low speed timebases and for transients. Conventionally, low timebase speeds are handled by pen-and-chart recorders, but these cannot respond to the high speed of a sudden transient. CRT's operating at low timebase speeds do not have a long enough persistence trace to enable the complete trace to be easily seen. The storage tube, with its ability to leave a bright trace at the lowest timebase speeds and also to record short pulses which arrive during the

FROZEN SIGNALS

slow timebase covers the whole range of needs. At the other end of the scale, transients (pulses arriving at random) can be displayed on a fast timebase if the transient is used to trigger the timebase and the display delayed until the timebase has started. In this way, transients can be caught examined and photographed; a process difficult to achieve by other methods.

CONSTRUCTION:

The writing gun follows conventional oscilloscope or television cathode ray tube techniques, and is located in the narrow bore section of the tube in the usual way. The flood gun can be made in a variety of shapes, the most favoured method being annular, with a ring-shaped cathode G₁ and G₂ structure surrounding the end of the writing gun tube. In this way, the writing gun can be located at the centre of the tube and still permit the flood gun to operate as if it too were at the

centre. The electrode controlling the callimation of the flood gun that is the degree of the spread of the beam, is usually a carbon coating over the large diameter portion of the tube.

The two meshes are the critical portions. The storage mesh is of nickel, a metal which possesses adequate strength and which can be electroformed in a relatively stress-free state. The mesh is usually 400-700 mesh per inch in fineness and is stretched on a nickel-alloy frame. The insulator chosen is generally magnesium fluoride, which combines good insulating and dielectric properties with high


secondary emission and which is also comparatively easy to deposit on nickel by evaporation.

The collector mesh can be coarser in pattern and woven; stainless steel is suitable here, since this material is readily available in the form of woven mesh.

The screen is a completely conventional high-brilliance phosphor deposited and aluminised in the usual way. Since the storage properties of the tube do not depend on the phosphor, any type and colour can be used.

CONCLUSIONS:

Storage tubes have enabled us to study a much wider range of effects, particularly in biological waveforms and in the study of transients, than was previously possible, and have also considerably extended the ease of use of radar systems. Some of the early storage tube oscilloscopes, such as the "Remscope", are now appearing on the second-hand market, so making the unique characteristics of these devices more accessible to laboratories which could not previously afford the expenditure. It seems very likely that there are other applications which will now open out for storage tubes and storage oscilloscopes.

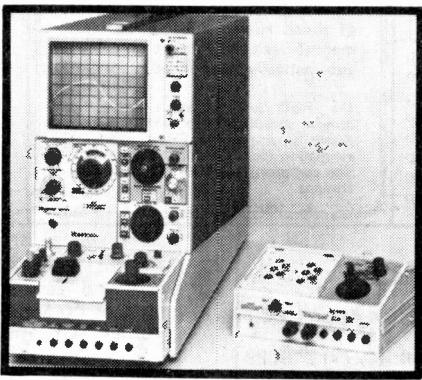

Tektronix type 577 curve tracer with storage CRT.

LYNX ELECTRONICS (LONDON) LTD

Transistors	BC183	10p*	BF337	32p	CRS1-10	25p	2N697	12p	
AC126	15p	BC183L	10p*	BFW60	17p*	CRS1-20	35p	2N706	10p
AC127	16p	BC184	11p*	BFX29	26p	CRS1-40	40p	2N929	14p
AC128	13p	BC184L	11p*	BFX30	30p	CRS1-60	65p	2N930	14p
AC129	25p	BC207B	12p*	BFX84	23p	CRS3-05	34p	2N1131	15p
AC141	18p	BC212	11p*	BFX85	25p	CRS3-10	45p	2N1132	16p
AC141K	28p	BC212L	11p*	BFX88	26p	CRS3-20	50p	2N1304	20p
AC142	18p	BC213	12p*	BFY50	20p	CRS3-40	60p	2N1305	20p
AC142K	28p	BC213L	12p*	BFY51	18p	CRS3-60	85p	2N1711	18p
AC176	16p	BC214	14p*	BFY52	19p	MJ480	80p	2N2102	44p
AC176K	25p	BC214L	14p*	BFY64	35p	MJ481	£1.05	2N2369	14p
AC187	18p	BC237	16p*	BFY90	65p	MJ490	90p	2N2369A	14p
AC187K	25p	BC238	16p*	BR100	20p	MJ491	£1.15	2N2484	16p
AC188	18p	BC300	34p	BRY39	40p	MJE340	40p*	2N2646	50p
AC188K	25p	BC301	32p	BXS19	16p	MJE371	60p	2N2905	18p
AD140	50p	BC323	60p	BXS20	18p	MJE520	45p	2N2905A	22p
AD142	50p	BC327	18p*	BXS21	20p	MJE521	55p	2N2926R	10p*
AD143	46p	BC328	16p*	BYS95A	12p	OAS	50p*	2N2926	9p*
AD149	45p	BC337	17p*	BT106	£1.00	OAO	8p	2N2926Y	8p*
AD161	35p	BC338	17p*	BT107	£1.60	OA91	8p	2N2926G	10p*
AD162	35p	BC70	12p	BT108	£1.60	OC41	15p	2N3053	15p
AL102	95p	BCY71	18p	BT108	£1.00	OC42	15p	2N3054	40p
AL103	93p	BCY72	12p	BT116	£1.00	OC44	12p	2N3055	50p
AF114	20p	BD115	55p	BU105	£1.80*	OC45	10p	2N3440	56p
AF115	20p	BD131	36p	BU105	£1.00	OC70	10p	2N3442	£1.20
AF116	20p	BD132	40p	BU126	£1.60	OC71	10p	2N3570	80p
AF117	20p	BD135	36p	BU126	£1.60	OC72	22p	2N3702	10p*
AF118	50p	BD136	39p	BY206	15p*	OC84	14p	2N3703	10p*
AF139	33p	BD137	40p	BY207	20p*	SC40A	73p	2N3704	10p*
AF239	37p	BD138	48p	BYX36-300	SC40B	81p	2N3705	10p*	
BC107	14p	BD139	8p	BD139	12p*	SC40D	98p	2N3706	10p*
BC107B	16p	BD181	85p	BYX36-600	SC40F	65p	2N3707	10p*	
BC108	13p	BD182	92p	BYX36-900	SC41A	65p	2N3714	£1.05	
BC109	14p	BD183	97p	BYX36-900	SC41B	70p	2N3715	£1.15	
BC109C	16p	BD232	60p*	BU216	£1.60	SC41D	70p	2N3716	£1.25
BC111	19p*	BD233	48p*	BU233	18p*	SC41E	85p	2N3717	£1.60
BC125	18p*	BD237	55p*	BU237	21p*	SC41F	60p	2N3722	£1.60
BC126	20p*	BD238	60p*	BYX38-	ST2	20p	2N3733	£2.10	
BC141	28p	BD184	£1.20	300	50p	TIP29A	44p	2N3819	28p*
BC142	23p	BDY20	80p	BYX38-	52p	TIP30A	52p	2N3904	16p*
BC143	23p	BDY36	60p	600	55p	TIP31A	54p	2N3906	16p*
BC144	9p*	BDY60	60p	BYX38-	64p	TIP32A	64p	2N4124	14p*
BC147	9p*	BDY61	65p	900	60p	TIP34	£1.05	2N4290	12p*
BC148	9p*	BDY62	55p	1200	65p	TIP41A	68p	2N4348	£1.20
BC149	9p*	BF178	28p	1200	65p	TIP42A	72p	2N4870	35p*
BC152	25p*	BF179	30p	BZX61 series	IN2069	14p	2N4871	35p*	
BC153	18p*	BF194	10p*	zeners	20p	IN2070	16p*	2N4919	70p*
BC157	9p*	BF195	10p*	20p	IN4001	4p*	2N4920	50p*	
BC158	9p*	BF196	12p*	BZX83 or	IN4002	5p	2N4922	58p*	
BC159	9p*	BF197	11p*	zeners	11p*	IN4003	6p*	2N4923	64p*
BC160	32p	BF224J	16p*	C106A	40p	IN4004	7p*	2N5060	20p*
BC161	38p	BF224	17p*	C106B	45p	IN4005	8p*	2N5061	25p*
BC168B	9p*	BF257	30p	C106D	50p	IN4006	9p*	2N5062	27p*
BC182L	11p*	BF258	35p	C106F	35p	IN4007	10p*	2N5064	30p*
		CRS1-05	25p	2N696	14p	2N5496	65p		

DIGITAL DISPLAYS & LED'S

DL704	99p	DL747	1.75	-2 RED LED ONLY .	13p
DL707	99p	DL750	1.75	GREEN CLEAR	15p

THYRISTORS

8A (TO92)	.8A (TO105)	.1A (C106 type)	3A (TO220)	6A (TO220)	8A (TO220)	10A (TO220)
50	20	25	35	41	42	47
100	25	25	40	47	48	54
200	27	35	45	58	60	68
400	30	40	50	67	68	98
600	65	70	1.09	1.19	1.26	

TRIACS (PLASTIC TO-220 PKGE, ISOLATED TAB)

4A	6.5A	8.5A	10A	15A
(a)	(b)	(a)	(b)	(a)
100 V	0.60	0.60	0.70	0.70
200 V	0.64	0.64	0.75	0.75
400 V	0.77	0.78	0.80	0.83
600 V	0.96	0.99	0.87	1.01

N.B. Triacs without internal trigger diac are priced under column (a). Triacs with internal trigger diac are priced under column (b). When ordering please indicate clearly the type required.

74 TTL mixed price*

1-24	25-99	100+	1-24	25-99	100+
7400	14p	12p	10p	7445	85p
7401	14p	12p	10p	7447	81p
7402	14p	12p	10p	7448	75p
7403	15p	12p	10p	7447A	95p
7404	16p	13p	11p	7470	30p
7493	16p	13p	11p	7472	25p
7409	16p	13p	11p	7473	30p
7410	16p	13p	11p	7474	32p
7413	29p	24p	20p	7475	47p
7417	27p	22p	20p	7476	32p
7420	16p	13p	11p	7482	75p
7427	27p	22p	18p	7483	£1.00
7430	16p	13p	11p	7486	32p
7432	27p	22p	18p	7488	£2.92
7437	27p	22p	18p	7489	£2.88
7441	75p	62p	50p	7490	49p
7442	65p	55p	43p	7491	65p

301A 8 pin DIL	35*	3900 14 pin DIL	70*	565 14 pin DIL	£2.00*
307	55*	708/14 pin DIL	35*	566 8 pin DIL	£1.50*
309K	1.60	741 8/14 pin DIL	28*	567 8 pin DIL	£2.00*
380 14 pin DIL	90*	748 8 pin DIL	36*	CA3046 14 pin DIL	50*
381 14 pin DIL	1.60*	555 8 pin DIL	45	CA3045	85*

Matching charge 20p per pair. P & P 20p.—Overseas 80p.

MM5314 £3.75 MM5316 £5.25
(Basic clock chip giving 6 digit display)
(Sophisticated device including alarm, similar to CT 7001)

NATIONAL CLOCK CHIPS


MM5314 £3.75 MM5316 £5.25
(Basic clock chip giving 6 digit display)
(Sophisticated device including alarm, similar to CT 7001)

HIGHAM MEAD, CHESHAM, BUCKS. Tel. (02405) 75151

VAT—Please add 8% except items marked * which are 25%

tecknowledey in consumer ICs - and their applications.

SGS Audio ICs

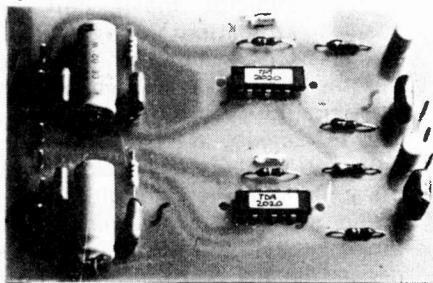

The much heralded TDA2020 is here. And just to make sure that you don't go wrong, so is the SGS application test circuit PCB for a stereo 15 + 15 (RMS) Hi Fi amplifier.

Prices :	IC	AUDIO	DISCRETES
TBA810AS	+HS	1.09	ZTX107/8/9 14p
TCA940E	+HS	1.80	ZTX413(LN) 17p
TDA2020		2.99	ZTX212/3/4 16p
FM LINEAR	ICS		BD 535 npn 7A/60v 52p
			BD536 pnp 53p
MC1350		0.70	BD377 npn 3A/50v 29p
CA3089	+QC	1.94	BD378 npn 32p
TBA120	+QC	1.00	BD515 npn 2A/45v 27p
MPX LINEAR	ICS		BD516 pnp 30p
			BD609 npn 10A/90v 70p
MC1310P	+LED	2.20	BD610 pnp 102p
CA3090AQ	+LED	3.75	

We've moved

To accommodate expanded R & D facilities, AMBIT has moved sales and administration to 25 High St. Brentwood. The existing 37 High Street premises are retained for the engineering activities.

One of the first products of this move has been the development of a TV sound tuner, from an "off air" system, using its own varicap UHF TV tuner, with ICF amplifiers and block filters by TOKO. And then one of our best ever circuits - an electronic touch tuner, with scanning mode, and facilities for 6 preset stations. The unit is suitable for use with FM, and now AM of course, and offers a complete tuner system without any moving parts. Selection is by means of touch tuning in all cases, with manual scan and preset switching automatically interlocked.

Our R&D facilities are available for general consultancy to OEMs: further details on application. Standard project estimation fee, including project evaluation comment date is £15.00 payable in advance.

Modules & Kits

New modules:

8011	Totally touch tuned varicap controller built £14.99.
8005	Larsholt tunerset accessory unit, with pilot tone filter and audio stages, rectifier, IC stabilizer, meter driver circuits. £4.99 (kit)
8001	55kHz low pass filter (mpx birdy filter) £2.35 built £1.75 (kit)
2001	Stereo scratch and rumble filter, with continuously variable operating frequencies. £5.80 (built) £4.60 (kit)
3000	Stereo control preamp - a wide dynamic range, low distortion AF preamp, with vol, bal, bass and treble controls. kit £5.78
2020k	The TDA2020 stereo amp kit photographed on the left. £7.85
7700	TV off air UHF sound tuner - built £26.00 (4 preset stations)

9000 kit	AM/FM mpx tuner chassis, with mech. tuner	£17.50
7004 kit	MW/LW varicap tuner module, inc. ferrite rod	£9.95
7252	HiFi MOSFET tuner module by Larsholt	£24.00
7253	HiFi FET tuner module inc decoder	£24.00
5600	Hi Q MOSFET varicap tunerhead by TOKO	£11.25
EC3302	FET tunerhead from TOKO	£5.00

Complete FM Tuner kits, inc case, for use with the above modules: details SAE please. Prices range from £40 - £60.

Amongst our various accessories for entertainment electronics is a range of FM tuning, frequency and sig. strength meters with 12v, 50mA bulb. £2.50 ea.



ambit international
25 high street, brentwood,
essex. cm14 4rh.
Trade Mark
tel: (0277) 216029
tlx: 995194

Free price list with an SAE, catalogue of modules and parts 40p., including postage and VAT.

General Terms: CWO please, official bodies and companies please note min. invoice £7.50. PP for CWO orders 22p per order. (UK and Eire). Overseas customers please include sufficient for postage. VAT is not included, and must be added at 25%, in stock orders despatched within 48 hours.

ANDROMEDA ELECTRONICS LIMITED

3 WORCESTER ROAD, MALVERN, WORCESTERSHIRE.

TEL 63703

TRANSISTORS	2N3819	39p	74121	36p	RESISTORS	100uF/10V	13p	100uF/25V	18p
	TIS43	30p	74123	£1.02p	½W Carbon Film 1Ω/10mΩ	220uF/10V	16p	150uF/25V	18p
AC127	30p	TIC44	43p			E24 SERIES 2p each	470uF/10V	18p	220uF/25V	32p
AC128	30p	RCA40871	60p	DIODES		½W Carbon Film 10Ω-10mΩ	15uF/16V	12p	470uF/25V	36p
AC176	30p	RCA40872	70p			E24 SERIES 2p each	33uF/16V	13p	1000uF/25V	53p
AC187	33p		AAY39	3p		68uF/16V	14p	6.8uF/40V	12p
AC188	33p	DIGITAL I.C.S.	AAZ13	3p	CAPACITORS	220uF/16V	18p	33uF/40V	15p
AD161	53p		IN270	3p	MIN. CERAMIC PLATE 63V	1000uF/16V	49p	100uF/40V	18p
AD162	53p	7400	14p	1N914/4148	3p	2.2, 3.3, 4.7, 5.6, 6.8	10uF/25V	12p	220uF/40V	36p
AF117	24p	7401	15p	1N4001	3p	8.2, 10, 15, 22, 33, 47,	25uF/25V	14p	250uF/64V	38p
BC107	10p	7402	15p	1N4004	5p	68, 82, 100, 150, 180, 270,	47uF/25V	15p		
BC108	14p	7403	15p	1N4007	8p	330, 470, 560, 680, 620,				
BC109	15p	7404	18p	400V/1Amp		1000, 1500, 1800, 3300,				
BC177	15p	7405	18p	Bridge	40p	4700pF 5p each				
BC178	16p	7406	43p	I.R.200V/5Amp						
BC179	17p	7407	43p	Bridge	£1.50p					
BC182L	14p	7408	18p	Zeners: All values 3.30-33vts		POLYESTER 250V				
BC212L	16p	7409	20p	400mW	14p	0.01, 0.015, 0.022, 0.033				
BD131	54p	7410	15p	1.3W	29p	0.047, 0.068, 0.1uF	6p			
BD132	54p	7420	15p	TIL209 L.E.D.	35p	0.1, 0.15uF	7p			
BF180	45p	7430	15p	TIL211 L.E.D.	39p	0.22, 0.33uF	9p			
BF181	45p	7440	15p			0.47uF	15p			
BF182	36p	7441	92p	LINEAR I.C.S.		1.0uF	24p			
OC45	12p	7447	92p							
2G306	10p	7470	29p	741 8Pin D.I.L.	36p					
2N1613	22p	7472	18p	SIGNETICS NE555	79p					
2N1711	29p	7473	36p	NATIONAL LM380	£1.35p	ELECTROLYTIC	100uF/4V	12p		
2N3055	78p	7474	33p	NATIONAL LM340-06T		100uF/6.3V	12p			
2N3703	14p	7490	39p	(6V/1Amp Regulator)	£1.30p	150uF/6.3V	13p			
2N3704	15p	7493	50p			22uF/10V	12p			

MINIMUM ORDER 40p. PLEASE - FREE CATALOGUE WITH EVERY ORDER
ALL ORDERS PROCESSED IN UNDER 24 HOURS - TRADE ENQUIRIES WELCOME
ALL PRICES INCLUDE V.A.T. AND POSTAGE - NO HIDDEN EXTRAS.

MARKER GENERATOR

Ergo-E 706

Accurate crystal-controlled markers for tuning and aligning communications receivers.

A LIMITATION of most low priced communications receivers and conventional radios is that tuning accuracy cannot be guaranteed. This means that when waiting for a short-wave station to come on the air we may well miss the beginning of the transmission because we have been tuned to the wrong frequency. The traditional method of overcoming this problem has been to use a marker generator or crystal calibrator. Such instruments generate a series of accurately known and harmonically related signals which are tuned by the receiver in order to determine the accuracy of the dial. The marker generator may also be used to perform the periodic calibration and alignment required by most sensitive receivers.

Although it is possible to build a generator which could be set to any desired precise frequency this approach is uneconomical. The more practical method is to have an oscillator running at an accurately known frequency and to generate harmonics of this frequency. For example a basic frequency of 1 MHz would have harmonics at 2 MHz, 3 MHz, 4 MHz... and so on.

The marker generator must supply a stable and accurate signal without the necessity of elaborate initial setting up. This requirement leads to the obvious need for a quartz crystal as the basic frequency-determining element.



A slice of quartz crystal has the property that when a voltage is applied to either side of the crystal, the crystal will be mechanically strained and conversely, when mechanical strain is applied a voltage appears across the crystal. The crystal has a natural frequency of resonance and it is thus equivalent to a tuned circuit with a very high 'Q'.

The cheapest available crystals operate at 4 MHz and to obtain the frequency intervals that we require we used CMOS ICs to divide down from the higher frequency. To ensure maximum operating speed the CMOS ICs need to be operated from a 10 volt supply. Some exceptional devices will work on six volts but the level of higher harmonics is then reduced somewhat.

To cover as much of the dial as we can in an effective manner the

harmonics should be spaced reasonably close together and should extend to 30 MHz. Ideally a harmonic should fall within the pass-band of a receiver no matter what frequency is tuned. We therefore selected a minimum spacing of 10 kHz as being the most practical. Unfortunately the inaccuracies of many receivers can, in the high bands, exceed 200 kHz thus several harmonics may be within the pass-band at any one time making it impossible for the operator to determine to which harmonic he is tuning. To overcome this problem the marker generator is switchable to provide harmonics spaced at intervals of 4 MHz, 2 MHz, 1 MHz, 100 kHz and 10 kHz.

To produce the series of harmonics required it is necessary to generate a series of very narrow pulses at a repetition rate equal to the spacing required. That is, 10,000 narrow pulses per second will produce the harmonic series 10 kHz, 20 kHz, 30 kHz up through 29 990 kHz and 30 000 kHz.


CONSTRUCTION

We mounted our unit in a commercially available aluminium box having dimensions of 150 mm wide by 75 mm high and 100 mm deep. The printed-circuit board is mounted on the rear panel of the box but spaced

SPECIFICATION

Harmonic Spacing	Five switchable outputs 4 MHz, 2 MHz, 1 MHz, 100 kHz and 10 kHz.
Harmonic Range	useable to 30 MHz
Accuracy	dependent on calibration.

MARKER GENERATOR

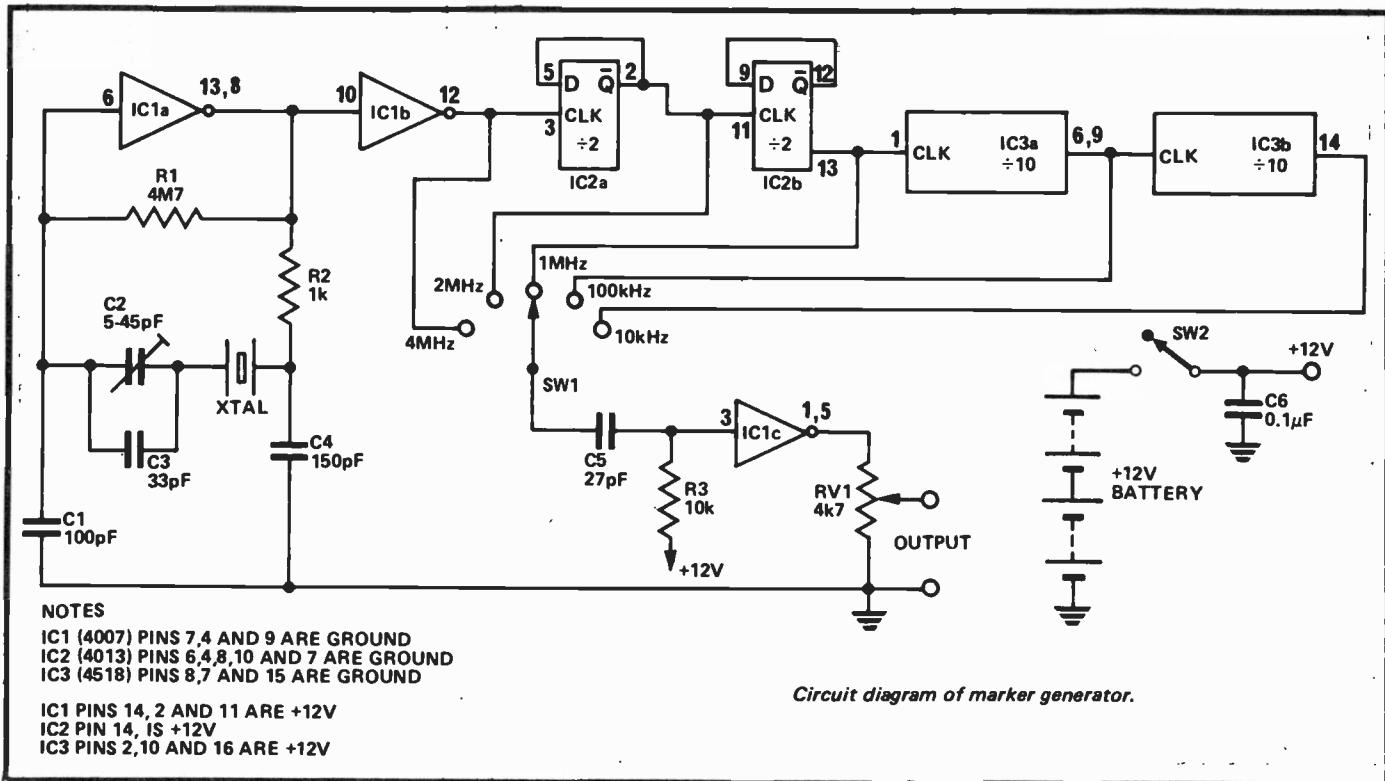

HOW IT WORKS - ETI 706.

The marker generator is a constant-frequency oscillator driving into a CMOS divider chain. Switchable outputs from the divider chain are selected to drive a pulse generator.

The oscillator is IC1a in which R1 biases the IC into linear operation. The crystal determines the basic frequency of operation at 4 MHz in conjunction with C1, 2, 3 and 4 which appear to the crystal as one parallel capacitor. The capacitor C2 is used to tune the oscillator exactly to frequency as explained in the text. The resistor R2 adds extra phase shift but also reduces the gain. Thus if the oscillator is slow in starting reducing R2 may help. The output of the oscillator is buffered from the rest of the circuit by IC1/b.

IC2 is a CMOS dual type D flip flop that divides the 4 MHz by four to provide an output of 1 MHz, the 2 MHz also being brought out.

A further dual division by 10 is provided by IC3 which therefore provides outputs of 100 kHz and 10 kHz.

The required output is selected by SW1 and applied to C5 and R3 which differentiate the squarewave output of the divider. The waveform is then amplified and squared by IC1/c to provide an output train of narrow pulses, the amplitude of which may be varied by means of RV1.

from it by four 19 mm long machine screws. Also mounted on the rear panel are the two output terminals. The two switches and the potentiometer are mounted on the front panel whilst the battery holders are clamped to the bottom of the box by means of a clamp made from a scrap piece of aluminium.

With the exception of the ICs, mount all components and fit all links to the printed-circuit board. After checking that all are correct, mount the ICs, double checking their orientation before soldering. Fit all flying leads to the board allowing about 150 mm of free length.

Drill the box with all the required holes and fit all the components such as the switches, the potentiometer and the output sockets. Fit the printed-circuit board to the rear panel with C2 to the top of the box and route the leads to their respective points as detailed in the component overlay. Note that one of the screws through the wafer of SW1 has an earth lug underneath it which is used as the common earth point.


Fit the batteries and connect them up but do not switch on until a final wiring check has been carried out. Ten minutes of your time at this stage could save you the cost of a new set of ICs.

USING THE GENERATOR

Say for example, that we wish to

PARTS LIST - ETI				
R1	Resistor	4M7	1/4W	5%
R2	"	1k	"	"
R3	"	10k	"	"
RV1	Potentiometer	4k7	lin	
C1	Capacitor	100pF	Ceramic	
C2	"	5-45pF	Beehive Trimmer	
C3	"	33pF	Ceramic	
C4	"	150pF	Ceramic	
C5	"	27pF	Ceramic	
C6	"	0.1μF	Ceramic	
IC1	Integrated Circuit	4007 (CMOS)		
IC2	"	4013 (CMOS)		
IC3	"	4518 (CMOS)		
XTAL one 4.0000 MHz quartz crystal 30pF load				
SW1 Rotary Switch 1 pole 5 position SW2 Toggle Switch SPST One pair of Terminals PC Board ETI 706 Aluminium Box 150mm, 75mm, 100mm.				
Two knobs Eight AA size batteries Two 4xAA size Battery Holders Nuts and Bolts.				

tune a signal that we know to be on 13.250 kHz. First select 4 MHz on the marker generator and connect its output to the aerial socket of the receiver. Tune the receiver to the marker which will be found at 12 MHz (third harmonic of 4 MHz). Once located confirm that it is indeed coming from the marker generator by switching it on and off. Now switch to the 1 MHz markers and tune upwards to locate the 13th harmonic at 13 MHz. Now select 100 kHz markers and tune upwards through two markers to locate 13.2 MHz. Finally select the 10 kHz

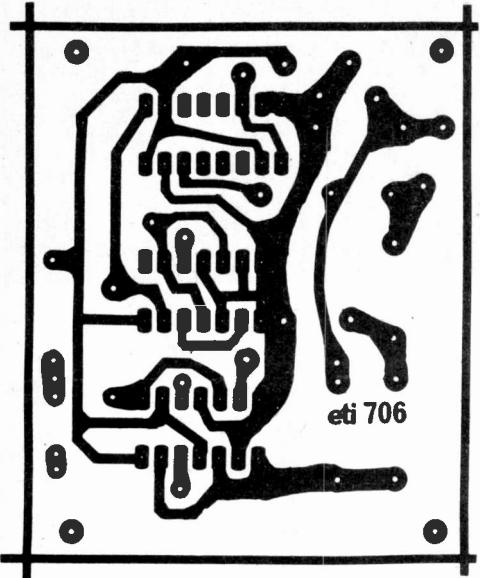

Printed-circuit layout. Full size 70 x 58mm.

markers and tune up through a further five markers to locate 13 250 kHz. Note that if this tuning procedure is carefully carried out it is quite simple to locate any position on the dial with great accuracy.

THE CRYSTAL.


Crystals are supplied to work within specified tolerances. The tighter the tolerances the more expensive the crystal. However the crystal oscillator may be placed exactly on frequency (within small limits) by varying the amount of capacitance in parallel with it.

When purchasing a crystal you must tell the manufacturer what capacitance it will be working with and he will grind your crystal to be within the specified limits when it is used with that particular capacitance. This marker generator has been designed to work with crystals that are ground for 30 pF capacitance.


CALIBRATION

The marker will be sufficiently accurate for most people with C2 set to half value. For those who want greater accuracy the generator must be calibrated against a signal of known accuracy.

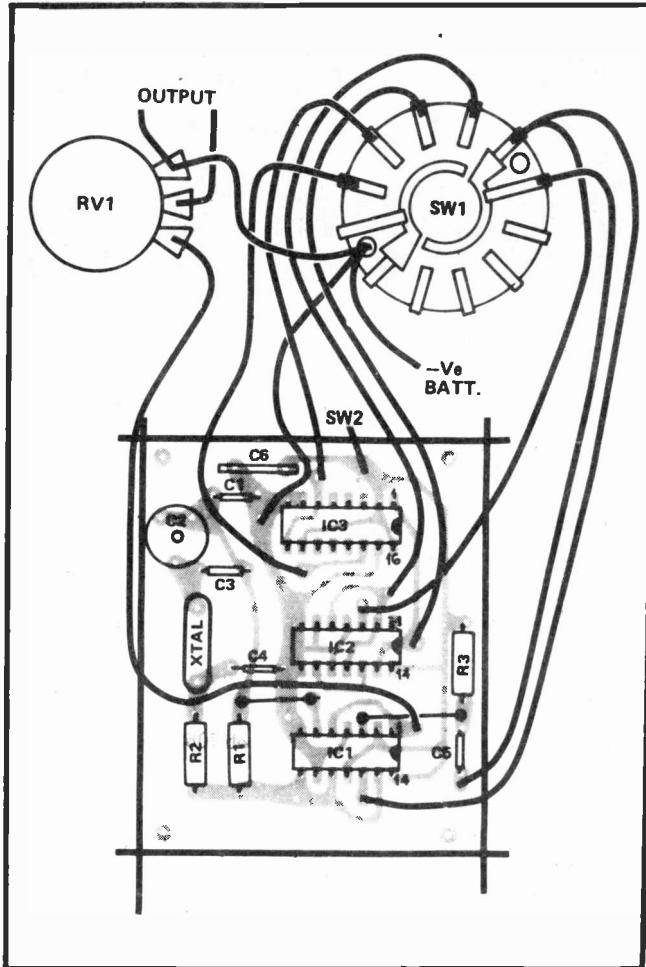The generator may be aligned against one of these frequencies by the zero-beating technique. First tune in the signal and then connect the generator. A whistle will now be heard and C2 should be tuned to the point where the beat frequency has dropped so low that it cannot be heard. The generator is now spot on frequency and it should be noted that this calibration is independent of the generator.



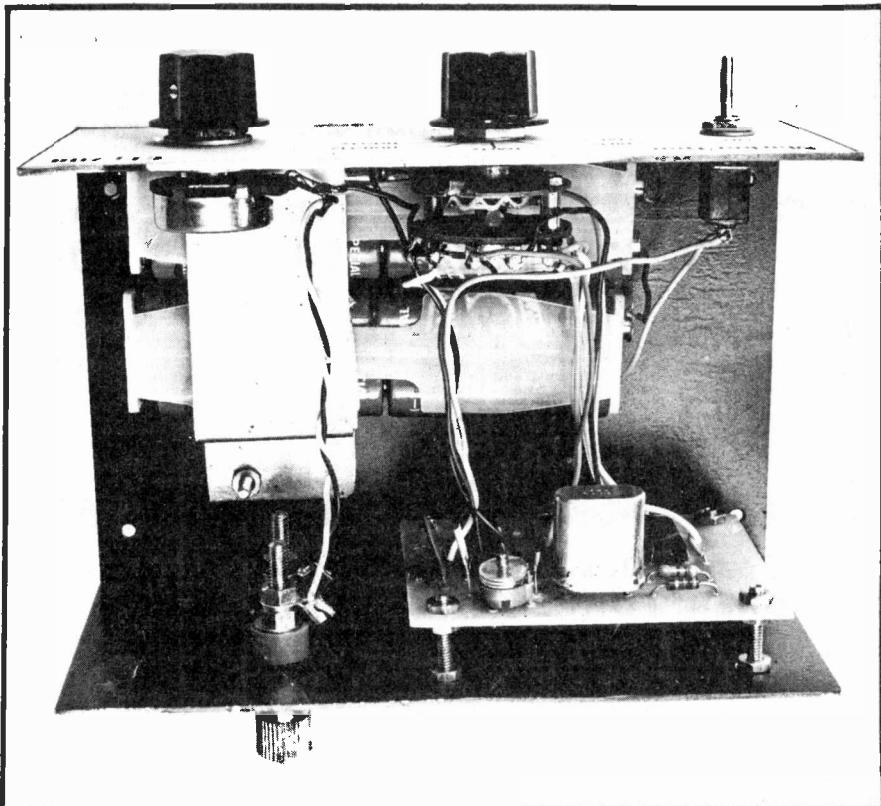Internal view of the completed marker generator. Note that the board is mounted with the crystal and C2 towards the top of the box.



Internal view of the generator. Note the crystal in the right foreground.

Marshall's

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat

Trade and export enquiries welcome

A. Marshall (London) Ltd Dept: ETI
 42 Cricklewood Broadway
 London NW2 3ET Tel: 01-452 0161/2
 Telex: 21492
 & 85 West Regent St Glasgow G2 2QD
 Tel: 041-332 4133
 & 1 Straits Parade Fishponds Bristol
 BS16 2LX Tel: 0272 654201/2
 & 27 Rue Danton Issy Les Moulineaux
 Paris 92 Tel: 644 2356
 Catalogue price 25p

Top 500 Semiconductors from the largest range in the UK

2N456	0.80	2N3390	0.45	2N5295	0.48	AF115	0.35	BC207	0.27	BF160	0.23	LM309K	1.88	OC35	1.16
2N456A	0.85	2N3391	0.28	2N5296	0.48	AF116	0.35	BC208	0.11	BF163	0.32	LM571	1.50	OC42	0.50
2N457A	1.20	2N3391A	0.19	2N5297	0.50	AF117	0.35	BC212K	0.16	BF165	0.40	LM300	0.98	OC45	0.32
2N480	4.00	2N3393	0.15	2N5457	0.29	AF118	0.35	BC214L	0.18	BF167	0.25	LM391	2.07	OC71	0.17
2N481	4.38	2N3393	0.15	2N5458	0.26	AF124	0.35	BC237	0.18	BF177	0.29	LM7097099	0.98	OC72	0.25
2N482	5.00	2N3394	0.15	2N5459	0.29	AF125	0.30	BC238	0.15	BF178	0.35	8DIL	0.38	OC81	0.25
2N693	5.20	2N3402	0.18	2N5492	0.58	AF126	0.28	BC239	0.15	BF179	0.43	14DIL	0.40	ORP12	0.55
2N696	0.22	2N3403	0.19	2N5494	0.59	AF127	0.28	BC251	0.25	BF180	0.35	LM710	0.47	R53	1.80
2N697	0.16	2N3414	0.20	2N5496	0.61	AF139	0.65	BC253	0.25	BF181	0.36	LM3900	0.61	SL414A	1.80
2N698	0.62	2N3415	0.24	2N6027	0.45	AF186	0.46	BC257	0.15	BF182	0.35	LM723C	0.66	SL610C	1.70
2N699	0.85	2N3416	0.21	2N5777	0.45	AF200	0.65	BC258	0.16	BF183	0.55	LM741T099	0.40	LP 1173	6.68
2N706	0.14	2N3417	0.29	3N128	0.73	AF239	0.65	BC259	0.17	BF184	0.30	8DIL	0.40	LP 1181	3.94
2N706A	0.16	2N3440	0.59	3N139	1.42	AF240	0.90	BC261	0.25	BF185	0.30	SL612C	1.70	LP 1182/2	4.32
2N708	0.17	2N3441	0.97	3N140	1.00	AF279	0.70	BC262	0.25	BF194	0.12	LM702C	1.00	LP 1184/2	7.18
2N709	0.42	2N3442	1.40	3N141	0.81	AF280	0.79	BC263	0.25	BF195	0.12	LM748B6D	0.44	SL623	4.59
2N711	0.50	2N3638B	0.15	3N200	2.49	AL102	1.00	BC300	0.38	BF196	0.13	LM7805	1.88	SL640C	3.10
2N718	0.23	2N3638A	0.15	40361	0.40	AL103	1.00	BC301	0.38	BF197	0.15	14DIL	0.73	SL641C	3.10
2N718A	0.28	2N3639	0.27	40362	0.45	BC107	0.14	BC303	0.54	BF198	0.18	LM7805	2.50	LP 1185	5.56
2N720	0.57	2N3641	0.17	40363	0.88	BC108	0.14	BC307	0.17	BF200	0.40	LM7812	1.99	SN76013N	1.95
2N914	0.22	2N3702	0.11	40389	0.46	BC109	0.14	BC308A	0.15	BF225J	0.23	LM7815	1.99	SN76023N	1.60
2N916	0.28	2N3703	0.12	40394	0.56	BC113	0.15	BC309C	0.20	BF244	0.21	LM7824	1.99	SN76033N	2.92
2N918	0.32	2N3704	0.15	40395	0.65	BC115	0.17	BC317	0.12	BF245	0.45	MC1303	1.50	ST2	0.20
2N929	0.25	2N3705	0.15	40406	0.44	BC116	0.17	BC318	0.12	BF246	0.58	MC1310	2.50	TA4300	1.84
2N930	0.26	2N3706	0.15	40407	0.35	BC116A	0.18	BC337	0.20	BF247	0.65	MC13300P	0.70	TA4263	1.20
2N1302	0.19	2N3707	0.18	40408	0.35	BC117	0.21	BC338	0.20	BF254	0.19	MC135IP	0.80	TA4350	1.96
2N1303	0.19	2N3708	0.14	40409	0.52	BC118	0.14	BC339	0.20	BF255	0.19	MC1352P	0.80	TA4550	0.32
2N1304	0.26	2N3709	0.15	40410	0.52	BC119	0.29	BC341	0.85	BF257	0.47	MC1466	3.50	TA611C	2.18
2N1305	0.24	2N3710	0.15	40411	0.25	BC121	0.35	BC342	1.15	BF258	0.53	MC1469	2.75	TA621	2.03
2N1306	0.31	2N3711	0.15	40594	0.74	BC125	0.16	BC343	0.85	BF259	0.55	ME0402	0.20	TA661B	1.03
2N1307	0.30	2N3712	1.20	40595	0.84	BC126	0.23	BC344	0.70	BF260	0.24	ME0404	0.13	TA661B18	2.25
2N1308	0.47	2N3713	1.20	40601	0.67	BC132	0.30	BC345	1.00	BF261	0.24	ME0412	0.18	TA655	1.69
2N1309	0.47	2N3714	1.30	40602	0.61	BC134	0.13	BC346	1.00	BF262	0.24	ME0414	0.11	TA8410	0.98
2N1671	1.54	2N3715	1.80	40603	0.58	BC135	0.13	BC347	0.97	BF263	0.24	ME0420	0.14	TA8620	0.80
2N1671A	1.67	2N3716	1.80	40604	0.58	BC136	0.16	BC348	0.97	BF264	0.24	ME0424	0.14	TA8920	1.79
2N1671B	1.85	2N3717	2.20	40636	1.10	BC137	0.17	BC349	0.97	BF265	0.24	ME0426	0.14	TU1209	0.30
2N1672	0.27	2N3772	1.80	40659	1.00	BC140	0.68	BC350	0.30	BF266	0.25	ME0428	0.14	TIP29A	0.49
2N1807	0.60	2N3773	2.65	40673	0.73	BC141	0.68	BC351	0.32	BF267	0.25	ME0429	0.14	TIP30A	0.58
2N202	0.60	2N3779	3.15	AC126	0.20	BC142	0.23	BC352	0.34	BF268	0.30	ME0430	0.14	TIP31A	0.62
2N2147	0.78	2N3790	2.40	AC127	0.40	BC143	0.25	BC353	0.22	BF269	0.30	ME0431	0.14	TIP32A	0.74
2N2148	0.64	2N3791	2.35	AC128	0.35	BC147	0.14	BC354	0.15	BF270	0.35	ME0432	0.14	TIP33A	0.86
2N2160	0.90	2N3792	2.60	AC151V	0.27	BC148	0.09	BC355	0.15	BF271	0.28	ME0433	0.14	TIP34A	0.98
2N2218A	0.47	2N3794	0.10	AC152V	0.49	BC149	0.15	BC356	0.15	BF272	0.28	ME0434	0.14	TIP35A	2.90
2N2219	0.42	2N3810	0.37	AC153	0.35	BC153	0.18	BC357	0.15	BF273	0.28	ME0435	0.14	TIP36A	3.70
2N2219A	0.52	2N3820	0.29	AC153K	0.40	BC154	0.18	BC358	0.23	BF274	0.28	ME0436	0.14	Veroboard	0.1
2N2220	0.25	2N3823	1.58	AC154	0.25	BC157	0.16	BC359	0.23	BF275	0.23	ME0437	0.14	Copper	0.1
2N2221	0.18	2N3904	0.19	AC176	0.41	BC158	0.16	BC360	0.40	BF276	0.21	ME0438	0.14	Plain	0.15
2N2221A	0.21	2N3906	0.19	AC176K	0.40	BC160	0.78	BC361	0.50	BF277	0.21	ME0439	0.14	£ p	£ p
2N2222	0.20	2N4036	0.67	AC187K	0.35	BC167B	0.15	BC362	0.21	BF278	0.75	ME0440	0.14	£ p	—
2N2222A	0.25	2N4037	0.42	AC188K	0.40	BC168B	0.15	BC363	0.22	BF279	0.74	ME0441	0.14	£ p	—
2N236B	0.17	2N4058	0.18	AC1Y	0.24	BC168C	0.15	BC364	0.22	BF280	0.28	ME0442	0.14	£ p	—
2N2369A	0.22	2N4059	0.15	AC1Y	0.27	BC169B	0.15	BC365	0.26	BF281	0.30	ME0443	0.14	£ p	—
2N2369	0.22	2N4060	0.15	AC2Y	0.22	BC169C	0.15	BC366	0.71	BF282	0.20	ME0444	0.14	£ p	—
2N2646	0.55	2N4061	0.15	AC2Y	0.26	BC170	0.15	BC367	0.87	BF283	0.25	ME0445	0.14	£ p	—
2N2647	0.98	2N4062	0.15	AC2Y	0.20	BC171	0.16	BC368	0.80	BF284	0.21	ME0446	0.14	£ p	—
2N2904	0.40	2N4126	0.28	AC2Y	0.58	BC172	0.12	BC369	0.80	BF285	0.18	ME0447	0.14	£ p	—
2N2905	0.45	2N4289	0.34	AD142	0.57	BC177	0.19	BC370	0.24	BF286	0.24	ME0448	0.14	£ p	—
2N2905A	0.47	2N4290	0.9	AD143	0.68	BC178	0.18	BC371	0.24	BF287	0.24	ME0449	0.14	£ p	—
2N2906	0.50	2N4492	1.10	AD149V	0.74	BC179	0.21	BC372	0.21	BF288	0.24	ME0450	0.14	£ p	—
2N2906A	0.33	2N4492	0.83	AD150	0.63	BC182	0.12	BC373	0.29	BF289	0.55	ME0451	0.14	£ p	—
2N2907	0.22	2N4492	1.00	AD162	0.64	BC183L	0.12	BC374	0.35	BF290	0.24	ME0452	0.14	£ p	—
2N2907A	0.24	2N5191	0.96	AF106	0.40	BC184	0.13	BC375	0.35	BF291	0.24	ME0453	0.14	£ p	—
2N2926	0.20	2N5192	1.24	AF109R	0.40	BC184L	0.13	BC376	0.20	BF292	0.24	ME0454	0.14	£ p	—
2N3053	0.25	2N5195	1.46	AF114	0.35	BC186	0.25	BC377	0.25	BF293	0.27	ME0455	0.14	£ p	—
2N3054	0.60	2N5245	0.29	BC187	0.27	BF154	0.16	BC378	0.27	BF294	0.27	ME0456	0.14	£ p	—
2N3055	0.75	2N5294	0.48	BF159	0.27	BF295	0.27	BF296	0.27	BF297	0.27	ME0457	0.14	£ p	—

"15% DISCOUNT FOR 100 MIX"

GET A GREAT DEAL FROM MARSHALLS. TV SPARES FOR BONA FIDE DEALERS, ITT, MULLARD, NATIONAL AND MOTOROLA. SEND FOR OUR NEW TWO PART CATALOGUE ON YOUR HEADED PAPER, £1.00 INCLUDING POST AND PACKING. REFUNDABLE WHEN YOU PLACE YOUR FIRST ORDER OVER £10.00.

MAIL ORDER
 ALL PRICES EXCLUDE VAT
 POSTAGE & PACKING 25p

MICRO-MIN SWITCHES 2P 2W
 60p. 1P 2W 50p. SUB MIN
 SWITCHES 1P 2W 55p. 2P 2W
 60p. 2P 2W CENTRE OFF 60p. 1P
 ON/OFF 45p.

Potentiometers
 Linear or Log

Single Double,
 25p 75p
 Rotary Pots
 55p —
 Rotary Switched
 45p 75p

Full range of Capacitors stocked. See catalogue for details

AUDIO EXPANDER-COMPRESSOR

ELECTRONICS TODAY INTERNATIONAL 443

Increase dynamic range of tape recordings or reduce record surface noise with this versatile unit.

MANY OF US have tapes in either the reel to reel format or on cassettes which leave a lot to be desired in terms of signal to noise ratio. It is not that we necessarily made a bad job of the recording in the first place, but rather the limitations of our equipment and tape were generally just a little bit too much compared with what is available today. And because the signal to noise ratio is so poor, many of these tapes (and quite a few records as well) tend to lie on the shelf because of their audible inadequacies. Apart from this it is by no means unknown for commercially pre-recorded tapes and records to be below an acceptable standard.


Many people arbitrarily think that this problem is what the Dolby system is intended to resolve. But this is not so. The Dolby system helps *maintain* the original signal to noise ratio when recording from one medium to another but it has very little to offer when faced by *existing* inadequacies.

DYNAMIC RANGE

Another problem that plagues many of us is the poor dynamic range of our tape recorders or of the pre-recorded material that we buy. For example, the majority of cassette recorders are hard pressed to offer even a 55 dB dynamic range. Many of them offer little more than 40 dB. As if this were not bad enough, few records have a dynamic range exceeding 50-55 dB and even this is soon degraded to 40-45 dB after a dozen or so playings in a dusty environment.

THE SOLUTION

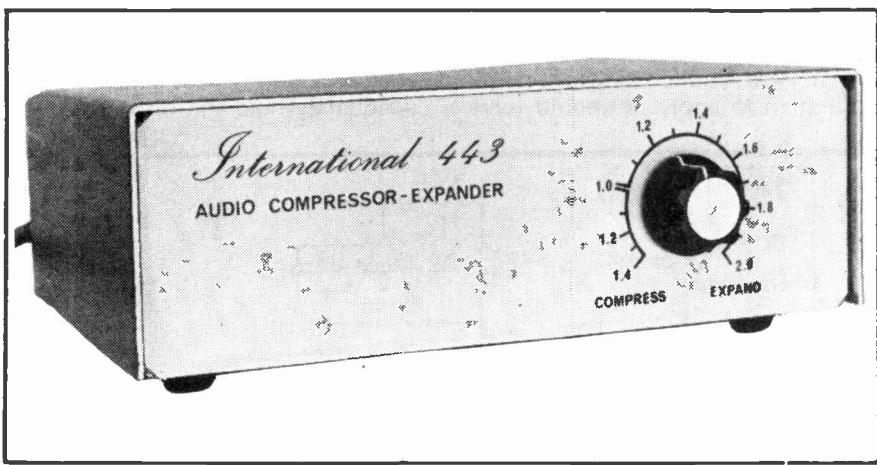Audio volume expansion is the simplest and most effective way of increasing the apparent signal to noise ratio of a worn or noisy recording. There is also no more effective way of preserving the full dynamic range of a sound than by recording with volume compression, and replaying with equal volume expansion. However, for these applications, the compression



and expansion must be done in a precise and reproducible manner; which is by no means as simple as it first appears.

The Compressor-Expander described here is relatively inexpensive to build, yet its performance is quite adequate for all practical purposes. It is sufficiently versatile to interface with most existing audio equipment, at nominal signal levels from about 25 millivolts to 1 volt.

CONSTRUCTION

Due to the relative complexity of the circuit a double-sided printed-circuit board has been used to simplify the construction, and we strongly recommend that this board be used. A single-sided board would be much larger and would require a great number of wire links.

Begin construction by assembling the components to the board in accordance with the component overlay Fig. 2. Take particular care with the orientation of components as marked on the overlay. When soldering component leads to the top of the printed-circuit board use a soldering iron which has a small tip and use a small gauge of solder (1 mm recommended). Take care not to bridge solder between the IC pads. It is easy to miss soldering connections on the component side of the board and these should be double checked.

Take care to insert the electrolytics with the polarity as marked on the overlay and even more care with the orientation of the diodes. A reversed diode can result in the destruction of one or more of the dual transistors.

The resistors in the signal side of the circuit and those in the current-sink circuit should be 2% or better. Alternatively they may be selected from 5% values. In selecting values an ordinary multimeter (operated at about the centre of the range) suffices. The resistors in question are all values between R37 and R65.

For best results the two 12 volt zeners should also be matched but in practice any slight discrepancy may be compensated by using the normal stereo-balance control.

A value of 1 microfarad for C5 allows compression or expansion to follow the signal amplitude so rapidly that the ear is unlikely to detect the attack or release, which is virtually complete in about 20 milliseconds. However, with this value, low frequency signal components (50 Hz or lower) will not be averaged out in obtaining the gain control voltage, and severe intermodulation and 3rd harmonic distortion will result. At the other extreme, a value of 4.7 microfarads for C5 will prevent this distortion right down to the lower audible limit, but the attack and release time

AUDIO EXPANDER-COMPRESSOR

(about 100 milliseconds) is so long that the effects can be audible, although not necessarily unpleasant. A value of C5 equal to 4.7 microfarads will be found quite acceptable by most people.

Potentiometer R₁ is used to match the signal levels of the compressor-expander with those of the associated equipment. Potentiometer R₃₄ should be a wire-wound type; and for the front-panel calibration to apply, it should have

an effective electrical rotation of 280°, and the midpoint of rotation should be set opposite the 1.0 index line.

Capacitor C5 should be chosen in accordance with the particular compromise that suits the user of the unit. Alternatively a switch may be used to select different values.

The box used in our prototype measured 200 × 125 × 63 mm and, although a little cramped did adequately hold the unit. The next

larger box available was thought to be too big. The printed-circuit board is mounted at the rear of the box to allow room for the front panel potentiometer to be mounted. The board is mounted on 6 mm spacers and the transformer is then mounted directly onto the rear panel together with the phono input and output sockets.

POWER SUPPLY

The output of the transformer is rectified by a full-wave bridge to provide ±22 volts, as set by the Zener diodes. The voltages obtained from the MC1468L regulator are the ±15V required for correct operation of the compressor-ex-

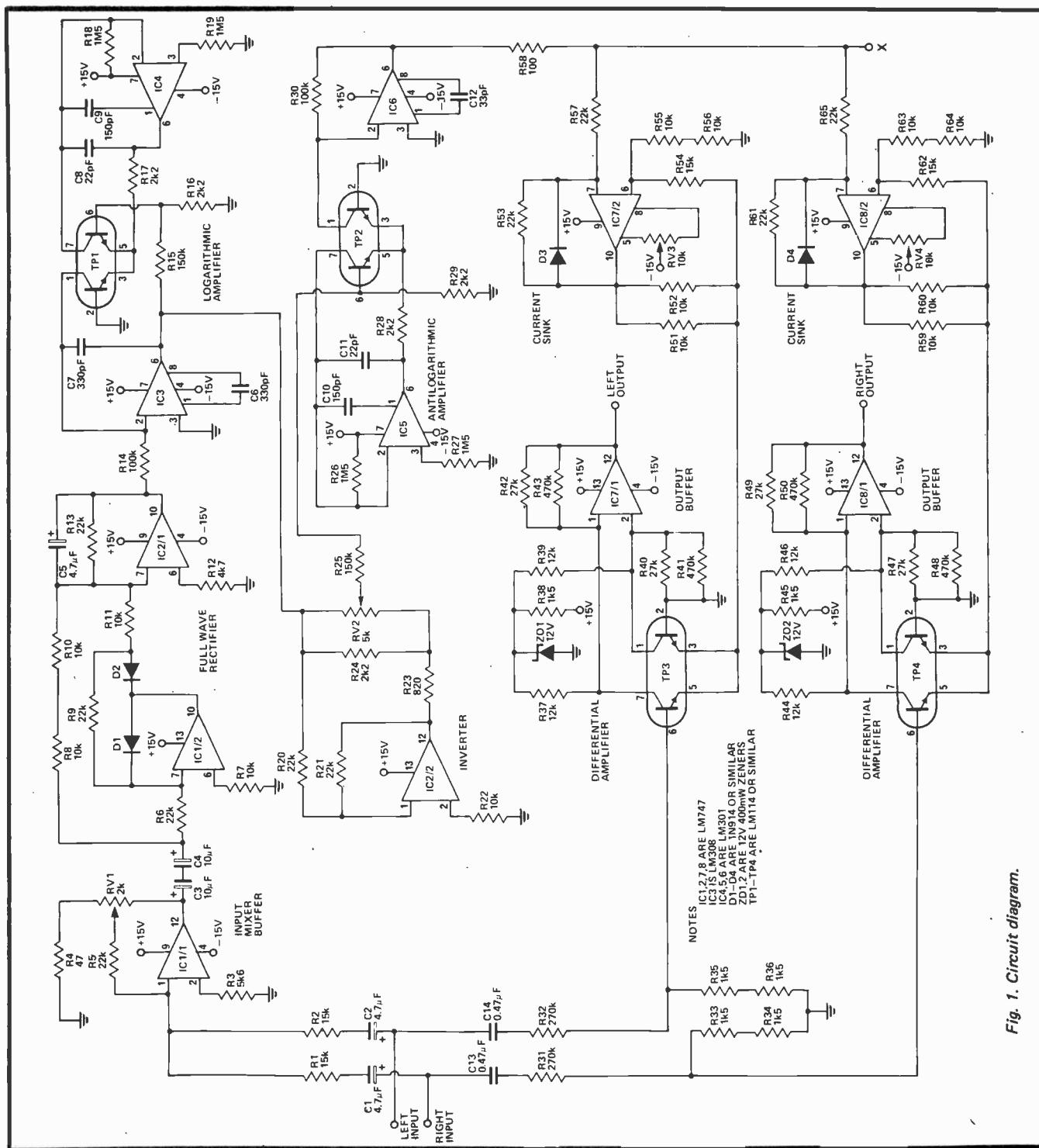


Fig. 1. Circuit diagram.

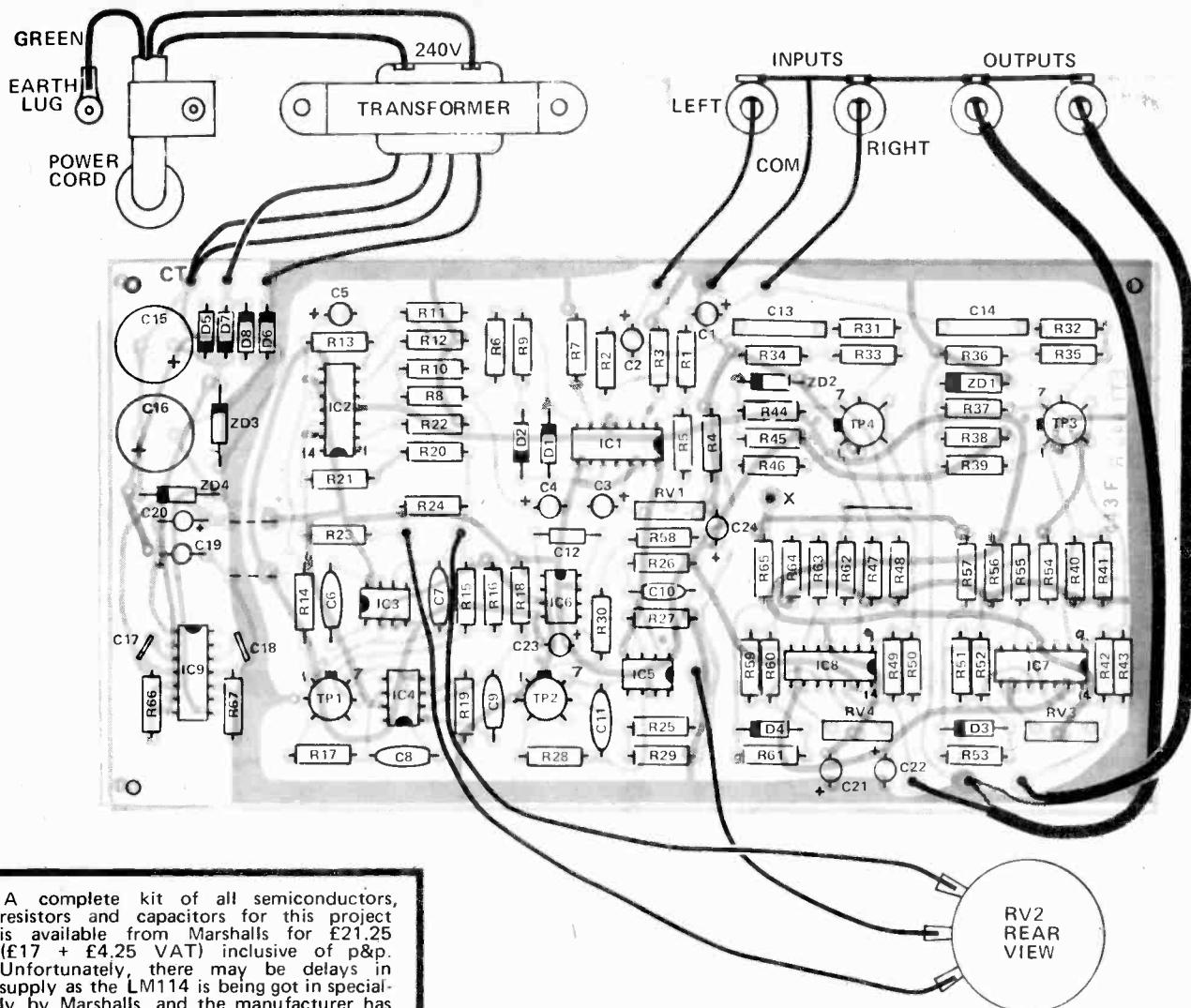


Fig. 2. Component overlay (not full size)

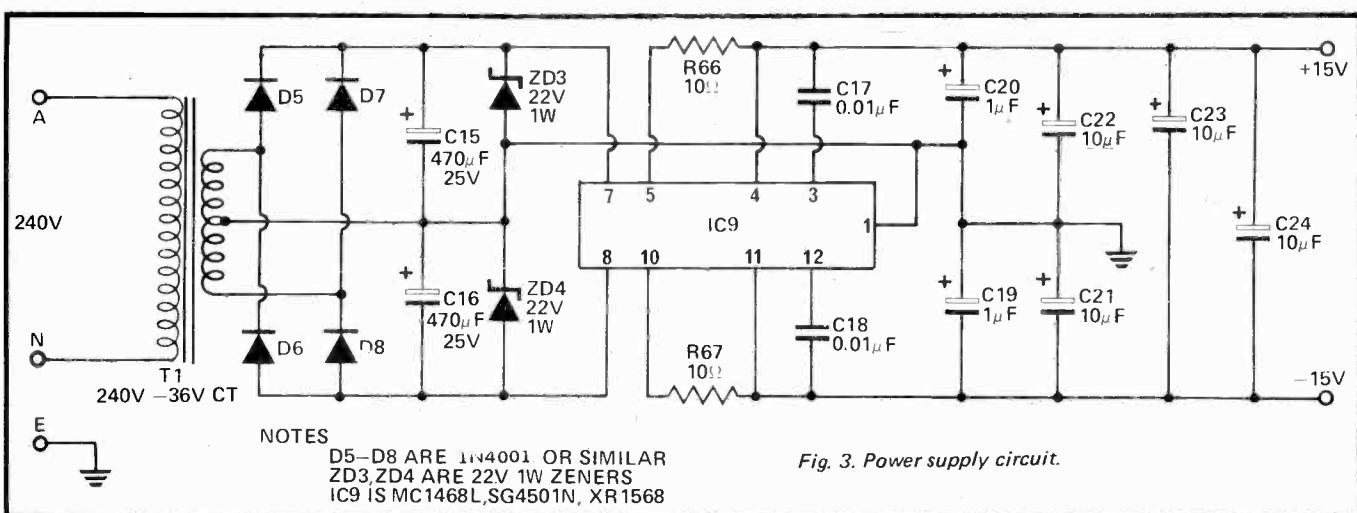


Fig. 3. Power supply circuit.

pander.


SETTING UP

With the power supply connected (check for correct polarity), apply a strong (about 1 volt) audio signal to both stereo inputs, while the point


marked 'X' is shorted to ground. Monitor the left channel output with a high sensitivity meter (or amplifier) and adjust RV3 to the point where the output JUST disappears. Repeat with the right channel and RV4. This procedure balances out

the input offset voltage of the current sinks, and ensures that the audio gain will be controlled correctly at the low end. Remove the input signal and the short circuit.

RV1 is set by the following

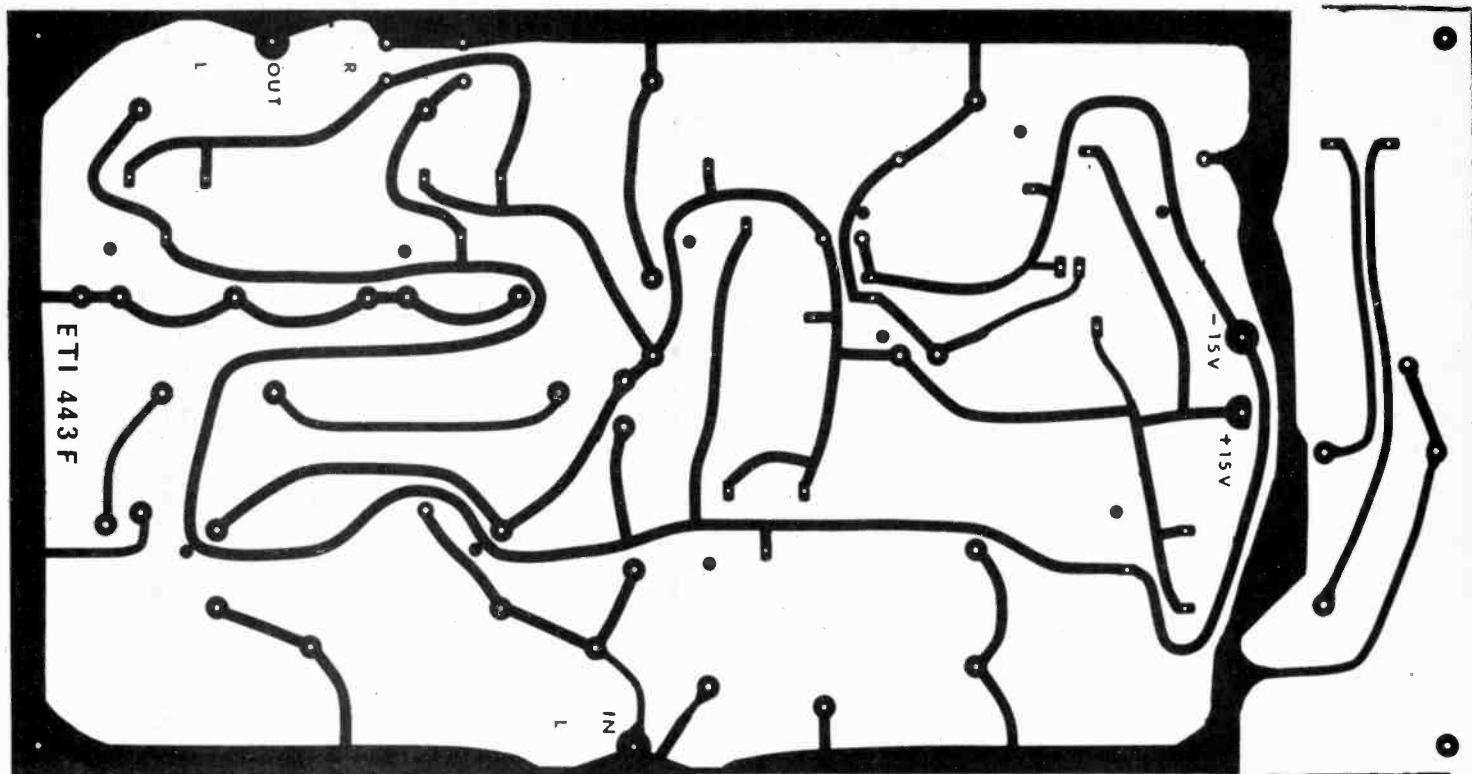

Double-sided PCB pattern (full size).

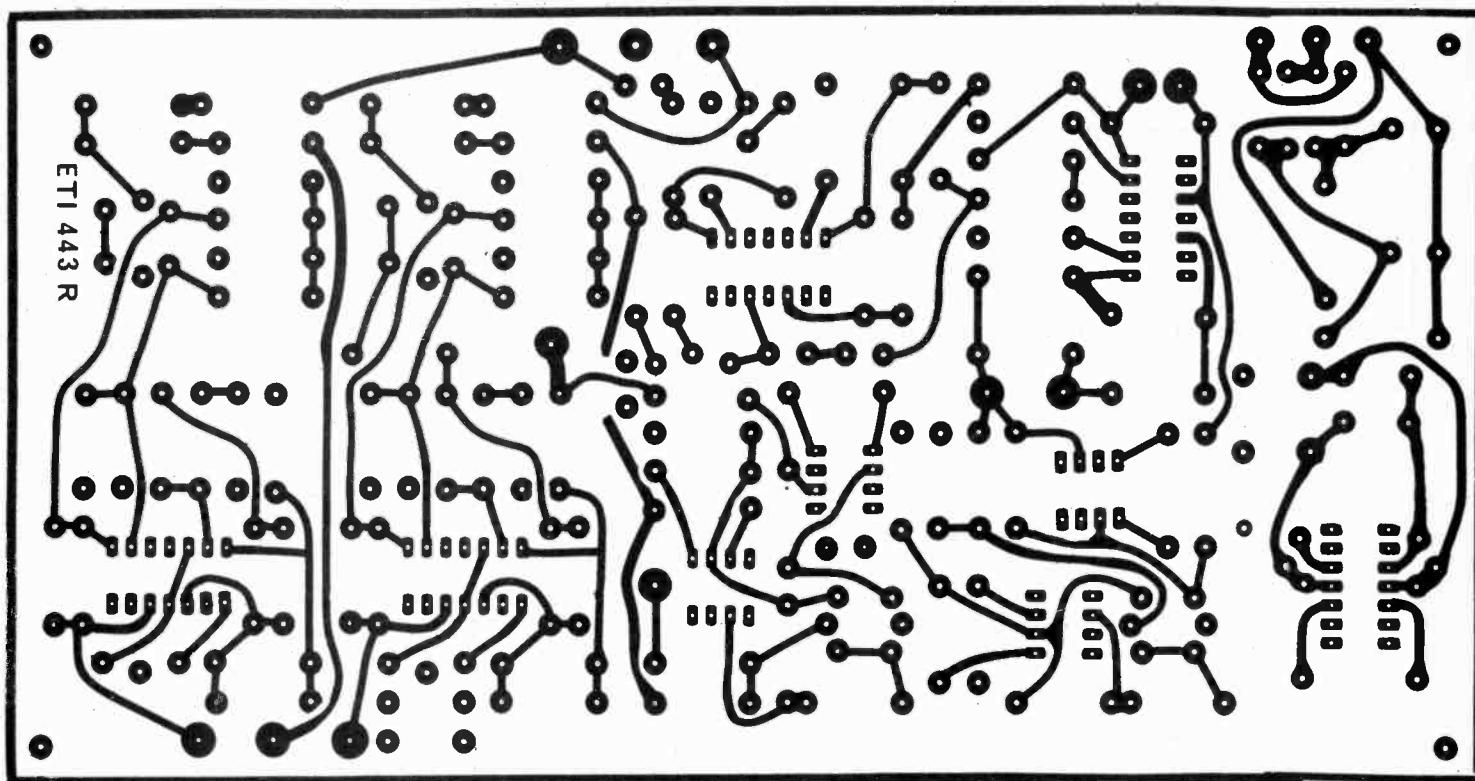

procedure:

- (1) Connect the compressor-expander to its associated equipment, and supply an input of moderate level (e.g. music of average loudness). RV1 should be fully clockwise when viewed from the input edge of the board.
- (2) Turn the compress-expand control to full compression, and adjust RV1 to bring the output up to its original level (loudness).

(3) Turn the compress-expand control towards the expansion end, and note any obvious change in output level.

(4) If a decrease in level occurs, turn RV1 slightly anticlockwise; if an increase occurs, turn RV1 slightly clockwise.

(5) Repeat steps (3) and (4) until the level remains reasonably constant over the whole range of compression and expansion. Note that this

adjustment is subjective, and it does not need to be done with any great accuracy.

If RV1 cannot be adjusted as described, it means that the signal level is outside the optimum range of the compressor-expander. Somewhat higher signal levels can be accommodated by increasing the value of R1 and R2, whilst for lower signal levels, R4 should be decreased. If correct adjustment of

RV1 is obtained well towards the anticlockwise end, then an improved signal-to-noise ratio results if R34 and R36 are increased to 18K, and the stereo outputs are each attenuated by a 470 ohm/3.9K divider. However, this modification is not essential.

With no input signal applied adjust RV2 such that the voltage at its wiper is zero volts. Now fit the knob such that the pointer lines up with the 1.0 calibration. Now check that the potentiometer travel approximately matches the scale. If not reverse the two outside leads to it.

HOW TO USE

The use of a compressor-expander need not be confined to those situations where such a device is really needed. Practically all tapes and many records become more listenable with a small amount of expansion. On the other hand, background music is far less obtrusive if the volume is compressed to some extent. The key to listening pleasure lies in the handling of the compress-expand control. Don't move it far from the 1.0 position unless there is some definite reason.


HOW IT WORKS

The heart of an audio compressor-expander is invariably a voltage controlled amplifier; that is, an amplifier whose gain is set by means of an applied voltage. This voltage itself must be derived from the amplitude of the audio input signal, averaged over some preset period, and modified to give the required compression or expansion characteristics. In the circuit of Fig. 1, each portion of the circuit is identified according to its function. These portions, in turn, are grouped into three main sections; an AC to DC converter, a power function generator, and a stereo analogue multiplier.

The two channels of stereo input are mixed in buffer amplifier IC1/1, and the gain of this stage is set so that an output of about 1 volt is given by a signal which corresponds to moderate loudness. Amplifiers IC1/2, and IC2/1 are used to obtain precision full-wave rectification of the mixed input, and the resulting positive DC voltage is stored in capacitor C5. The choice of value for C5 is important, and it will be discussed in detail later on.

Amplifiers IC3 and IC4 together with the transistor pair TP1/1 constitute a logarithmic amplifier. With the components shown, the behaviour of this amplifier is described by the

AUDIO EXPANDER-COMPRESSOR

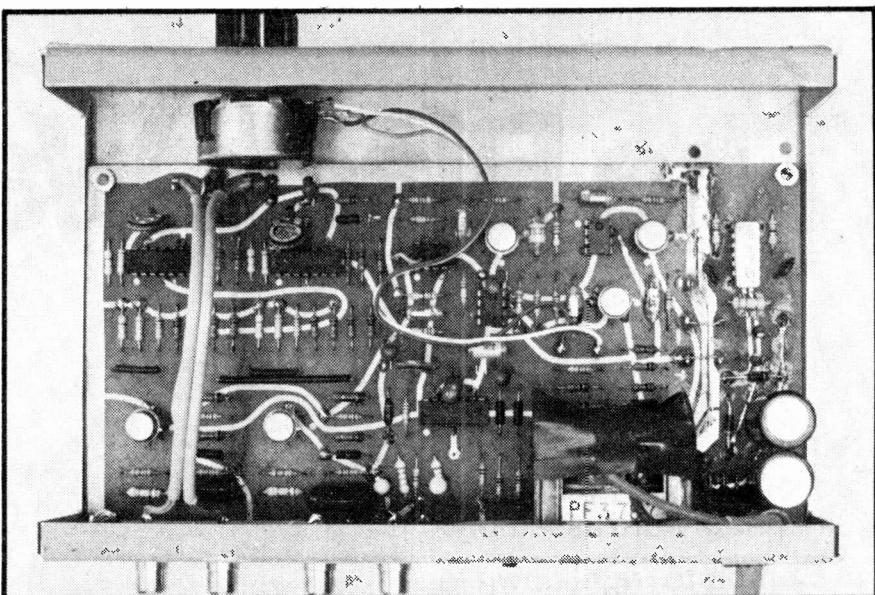

Interior of the unit.

One final word of warning — this device is quite capable of outputting a signal of 10 volts. It would be wise to ensure that your amplifier is capable of accepting this voltage without damage.

equation:

$$E_{\text{out}} = -4.151 \log E_{\text{in}}$$

The inverse of E_{out} is obtained from amplifier IC2/2 and by connecting the compression-expansion control potentiometer as shown between the input and output of this stage, any voltage between E_{in} and $-0.3E_{\text{in}}$ can be obtained. IC5, IC6 and TP₁ are combined as an antilogarithmic or exponential amplifier which is the exact inverse of the logarithmic amplifier, so that the effect of all these operations on the input signal is to give to a positive DC output voltage, equal in magnitude to the input voltage raised to the power k, where k can have any value from -0.3 to 1.

In the analog multiplier sections, this voltage (E_{out}) is converted to current by amplifiers IC7/2 and IC8/2 thus setting the effective gain of the differential amplifiers TP₃ and TP₄. These are directly coupled into the output buffers IC7 and IC8/1 so that the stereo signals reaching the outputs have been amplified by a factor which depends on the average amplitude of the signals, and the compression-expansion control setting. The actual voltage gain can vary from 0.0004 to 14, which represents a power gain range of 97dB.

PARTS LIST — ETI443

R1, R2	15k
R3	5k6
R4	47R
R5, R6, R9, R13, R20, R21	22k
R7, R8, R10, R11, R22	10k
R12	4k7
R14, R30	100k
R15, R25	150k
R16, R17, R24, R28, R29	2k2
R18, R19, R26, R27	IM5
R23	820R
R31, R32	270k
R33, R34, R35, R36	1k5
R66, R67	10R
All 1/2W, 5%	
R37, R39, R44, R46	12k
R38, R45	1k5
R40, R42, R47, R49	27k
R41, R43, R48, R50	470k
R51, R52, R55, R56, R59, R60, R63,	
R64	10k
R53, R57, R61, R65	22k
R54, R62	15k
R58	1k
All 1/2W, 2% (may be selected from 5% resistors)	
RV1	2k trimmer
RV2	5k wirewound pot
RV3, RV4	10k trimmer
C1, C2, C5	4.7μF 25V tantalum
C3, C4	10μF 25V tantalum
C6, C7	330pF
C8, C11	22pF
C9, C10	150pF
C12	33pF
C13, C14	0.47μF polyester
C15, C16	470μF 25V electrolytic
C17, C18	0.01μF polyester
C19, C20	1μF 25V tantalum
C21, C22, C23, C24	10μF 35V tantalum
TP1, TP2, TP3, TP4	
LM114	Dual transistor or equivalent
IC1, IC2, IC7, IC8	LM747
IC3	LM308
IC4, IC5, IC6	LM301
IC9	MC1468L or equivalent
D1, D2, D3, D4	1N914
D5, D6, D7, D8	1N4001
ZD1, ZD2	12V, 400mW
ZD3, ZD4	22V, 1W
T1	240V/36V CT transformer
PCB ETI 443	
4 Phono sockets	
4 6mm spacers	
chassis and cover	200x63x125mm
approx	
nuts, bolts and assorted hardware	


The Black Watch kit

£14.95!

* **Practical**—easily built by anyone in an evening's straightforward assembly.

* **Complete**—right down to strap and batteries.

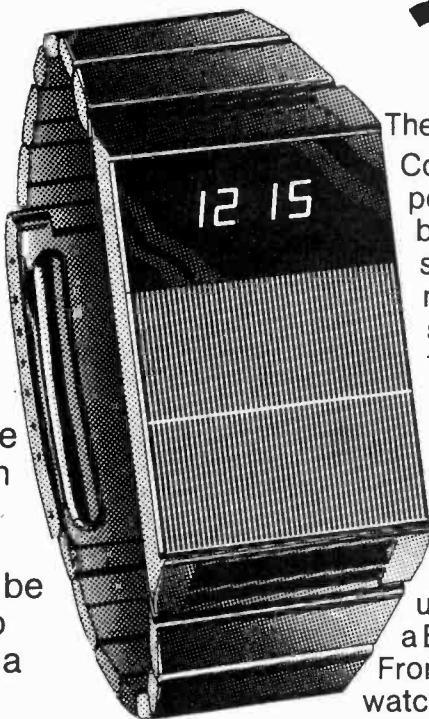* **Guaranteed**. A correctly-assembled watch is guaranteed for a year. It works as soon as you put the batteries in. On a built watch we guarantee an accuracy within a second a day—but building it yourself you may be able to adjust the trimmer to achieve an accuracy within a second a week.






The Black Watch by Sinclair is unique. Controlled by a quartz crystal, and powered by two hearing aid batteries, it uses bright red LEDs to show hours and minutes, and minutes and seconds. And it's styled in the cool prestige Sinclair fashion: no knobs, no buttons, no flash.

The Black Watch kit is unique, too. It's rational — Sinclair have reduced the separate components to just four—and it's simple: anybody who can use a soldering iron can assemble a Black Watch without difficulty. From opening the kit to wearing the watch is a couple of hours' work.

Touch and tell

Press here for hours and minutes... here for minutes and seconds.

Batteries easily replaced at home.

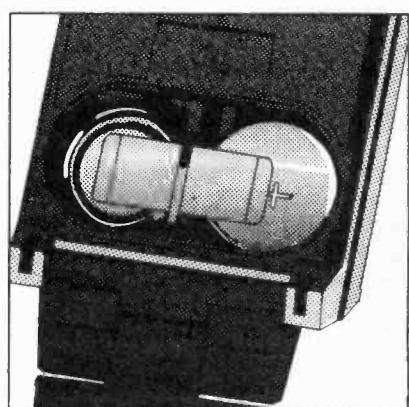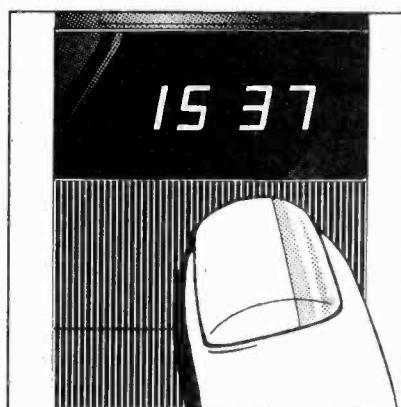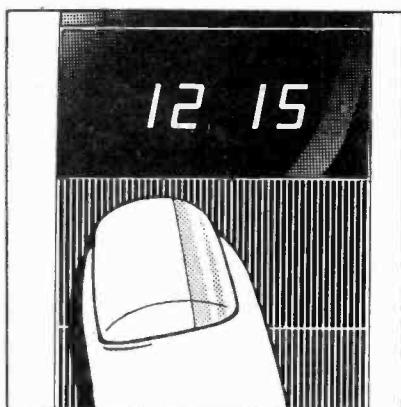

The specialist features of the Black Watch

Smooth, chunky, matt-black case, with black strap. (Black stainless-steel bracelet available as extra—see order form.)

Large, bright, red display—easily read at night. Touch-and-see case—no unprofessional buttons.

Runs on two hearing-aid batteries (supplied). Easily re-set using special button—no expensive jeweller's service.

The Black Watch—using the unique Sinclair-designed state-of-the-art IC.

The chip...

The heart of the Black Watch is a unique IC designed by Sinclair and custom-built for them using state-of-the-art technology—integrated injection logic.


This chip of silicon measures only 3 mm x 3 mm and contains over 2000 transistors. The circuit includes

- a) reference oscillator
- b) divider chain
- c) decoder circuits
- d) display inhibit circuits
- e) display driving circuits.

The chip is totally designed and manufactured in the UK, and is the first design to incorporate *all* circuitry for a digital watch on a single chip.

...and how it works

A crystal-controlled reference is used to drive a chain of 15 binary dividers which reduce the frequency from 32,768 Hz to 1 Hz. This accurate signal is then counted into units of seconds, minutes, and hours, and on request the stored information is processed by the decoders and display drivers to feed the four 7-segment LED displays. When the display is not in operation, special power-saving circuits on the chip reduce current consumption to only a few microamps.

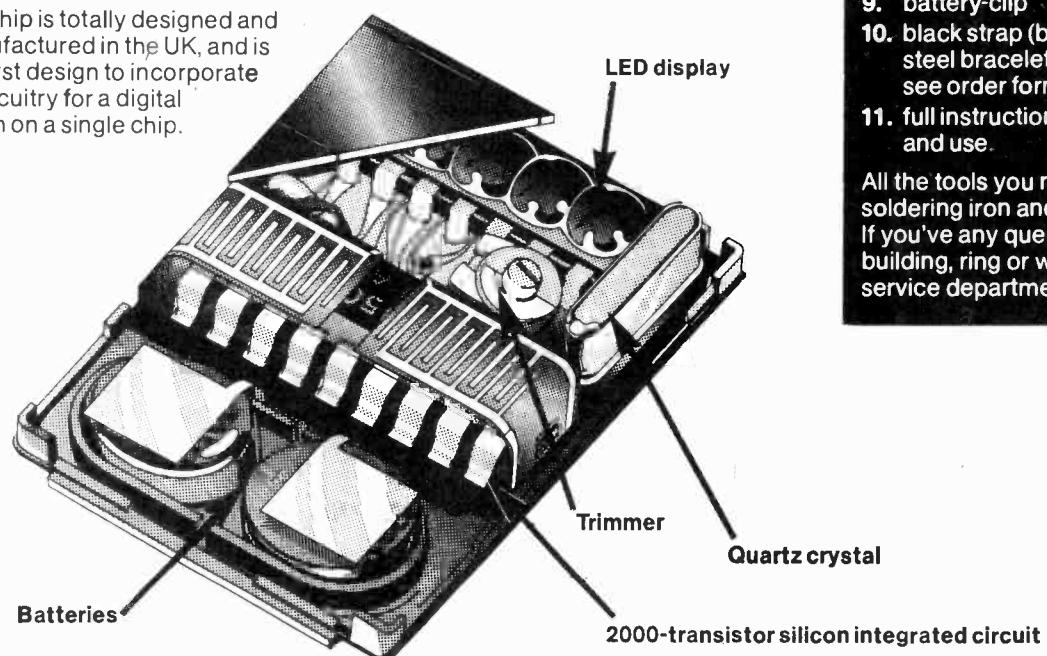

Take advantage of this no-risks, money-back offer today!

The Sinclair Black Watch is fully guaranteed. Return your kit in original condition within 10 days and we'll refund your money without question. All parts are tested and checked before despatch—and correctly-assembled watches are guaranteed for one year. Simply fill in the FREEPOST order form and post it today!

Price in kit form: £14.95 (inc. black strap, VAT, p&p).

Price in built form: £24.95 (inc. black strap, VAT, p&p).

Sinclair

Sinclair Radionics Ltd,
London Road, St Ives,
Huntingdon, Cambs., PE17 4HJ.
Tel: St Ives (0480) 64646.

Reg. no: 699483 England. VAT Reg. no: 213817088.

Complete kit

£14.95!

The kit contains

1. printed circuit board
2. unique Sinclair-designed IC
3. encapsulated quartz crystal
4. trimmer
5. capacitor
6. LED display
7. 2-part case with window in position
8. batteries
9. battery-clip
10. black strap (black stainless-steel bracelet optional extra—see order form)
11. full instructions for building and use.

All the tools you need are a fine soldering iron and a pair of cutters. If you've any queries or problems in building, ring or write to Sinclair service department for help.

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me

Total £

- (qty) Sinclair Black Watch
kit(s) at £14.95 (inc. black
strap, VAT, p&p).
..... (qty) Sinclair Black Watch(es)
built at £24.95 (inc. black
strap, VAT, p&p).
..... (qty) black stainless-steel
bracelet(s) at £2.00
(inc. VAT, p&p).

* I enclose cheque for £.....
made out to Sinclair Radionics Ltd
and crossed.

* Please debit my *Barclaycard/Access/
American Express account number
.....

Name (please print)

Address

Signature

FREEPOST—no stamp required.

ET 1/5

* Delete as required

ANOTHER FABULOUS ETI OFFER



6 C90

DINDY SUPER CASSETTES

Plus stand

£2.99

Offer closes
31st May

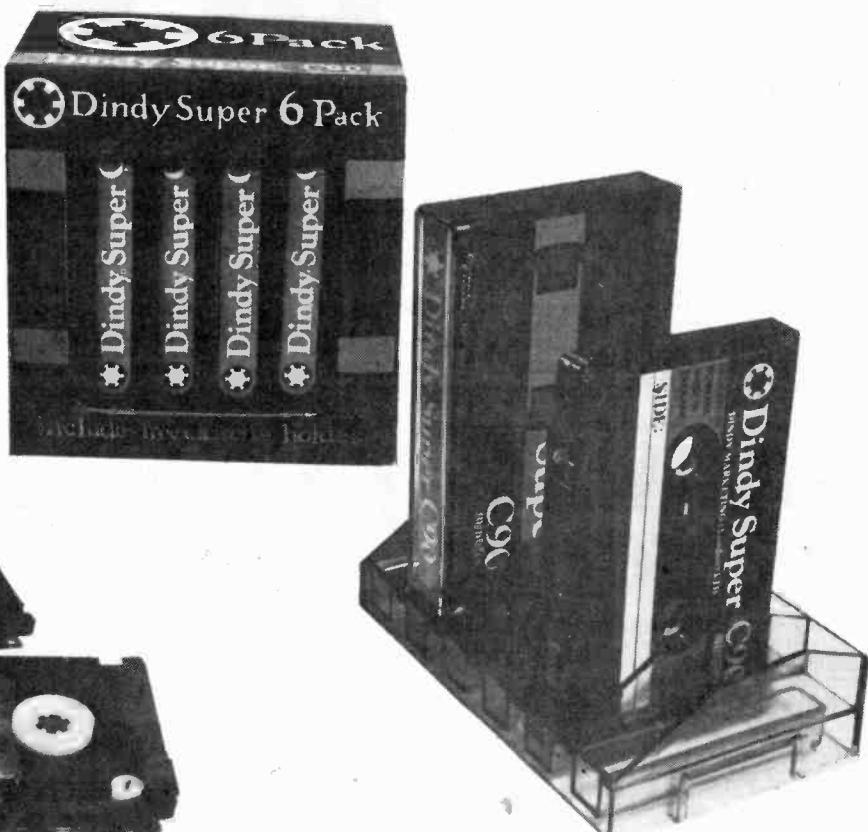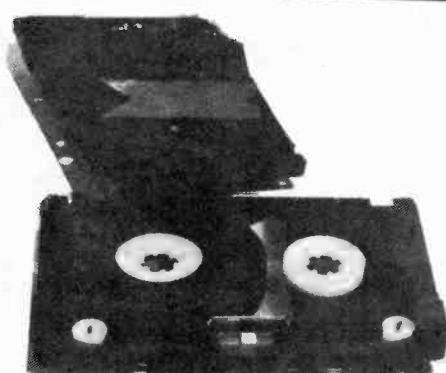

ETI have made arrangements with Dindy for an offer on C90 cassettes. We have inspected and tested these and were impressed with the good value. The Dindy cassettes are designed to combine performance and reliability into a unit which offers unbeatable value.

The Dindy philosophy is that fine attention to detail is necessary in order to produce a cassette that meets all the demands of today's audio enthusiast. That is why Dindy cassettes feature:

- A five year replacement parts guarantee.
- High output tape with high modulation tolerance.
- Extended frequency response.
- Improved magnetic stability.
- High quality screw type cassette casing.
- Separate roller pins.
- Flanged plastic rollers.
- Siliconised shims.
- Two point hub fixing.

CUT COMPLETE COUPON

To: ETI/DINDY CASSETTES OFFER
ETI Magazine,
36 Ebury Street,
London SW1W 0LW.

Please find enclosed my cheque/P.O. for £2.99 payable to Electronics Today International. IMPORTANT: Please write your name and address on the back of your cheque and P.O.'s.

This coupon will be used to dispatch your cassettes. The offer is strictly limited to one pack per coupon.

Orders will be dispatched as soon as possible but please allow 21 days for delivery. We regret the offer is only open to UK readers.

OFFER CLOSES MAY 31st 1976

FOR OFFICE USE

NAME

ADDRESS

PLEASE USE
BLOCK CAPITALS

NAME

ADDRESS

electronics today

international

JUNE ISSUE

ON SALE MAY 7th

30p

TECH-TIPS SPECIAL

Tech-Tips is one of the most popular features in ETI and twice before we have produced bumper versions of this; we have another planned for the June issue - 6-8 pages crammed with ideas for the experimenter. Virtually all Tech-Tips are submitted by ETI readers and are of course paid for if they are used: payment varies depending on the quality but averages £6. Tech-Tips 'fans' may like to know that we are planning a 'special' feature many of the 300 plus ideas that have been produced in the past.

WAA-WAA PROJECT

Usually waa-waa circuits are simple, cheap and not very dramatic. Ours is cheap, sophisticated and extremely effective. It includes facility for single or 'auto-run' operation. We have dispensed with the expensive pedal normally found, and have substituted two easily obtained foot switches, which are much cheaper. The unit can act as a treble booster if required, and the speed of the 'auto-run' is fully variable. Total cost we estimate to be well under £10! (including case).

ETI READER OFFER VIDEOSPORT TV GAMES UNIT

ETI and Henry's Radio have got together to bring you an exceptionally good offer on the built Videosport Mk2 TV games unit. When we got the sample at ETI it disrupted the office for hours - there was such a queue to have a go.

The Video is absolutely complete and plugs into the aerial socket on your own TV (it is mains operated). There are three games: Tennis, Football and Hole-in-the-Wall (can be multiple or solo game). Players can move both horizontally and vertically. Recommended price is over £40; Henry's recently reduced the price to £29.50 but ETI readers only next month can get it for £22.50 all inclusive.

Garden Watering

A simple project which measures the dryness of the soil and which can be connected to an automatic watering system.

AUXETOPHONE

The first real gramophone, and hi-fi of its day, it began the march to modern music reproduction in the home. One intriguing feature is an amplified violin - dated 1903!


LASER COMMUNICATIONS

The old saying that the laser was a discovery searching for a use is no longer true and today intensive research is being undertaken in several countries. More exciting is the use of optical fibres which can contain the laser beam with its enormous information carrying capacity.

Britain is well up with the leaders and the feature in next month's ETI has been written by Professor Gambling of the University of Southampton where much of the research is being conducted.

SELECTING CLOCK CHIPS

MOS clock chips are being released onto the home constructor market at an alarming rate and it is becoming possible to be up to the minute. However ETI has taken a hand and produced a sweeping survey. If you're about to spring into building a clock, take the time to read this first. We gathered up information on over 45 chips, sorted it out and present it next month. The format allows quick reference for the man of the minute, or a detailed specification for those with an hour or so on their hands.

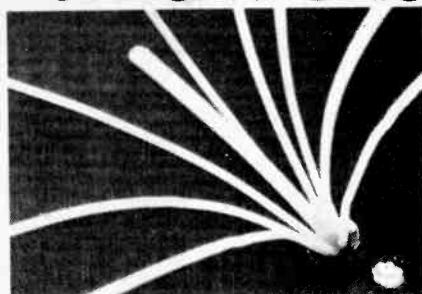

DATA SHEET

Devices planned for next months Data sheet include the AF100 universal active filter, LM3909 1.3 volt IC flasher, oscillator, trigger or alarm SN16880N logarithmic level detector/indicator and FX209 MOS delta-modulator.

Make sure of your copy

Do you find it difficult to buy ETI? You needn't, almost all newsagents will be happy to reserve a copy for you if you ask but get him to keep it under the counter - if he puts it on display it may be sold before you call for it!

ELECTRONICS-IT'S EASY


Sales of Electronics-It's Easy Volume 1 are going well but newer readers will still find a gap between the finish of this and the current series. This will shortly be corrected as Volume 2 is nearly ready and will bring the reader right up to date.



ETI DATA SHEET SPECIAL

Mullard TCA760 1W

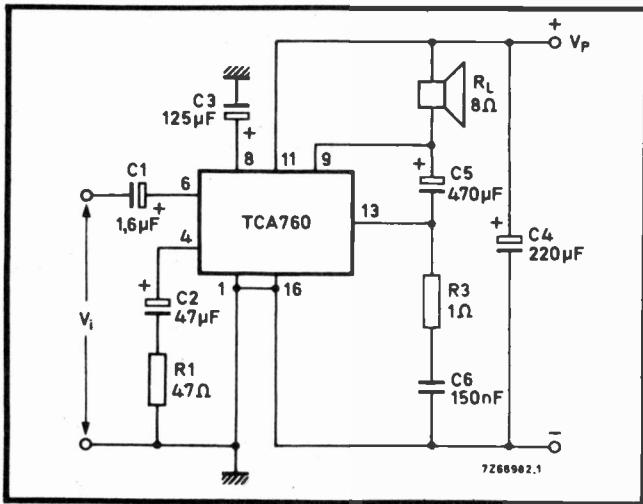The TCA760 is a monolithic integrated audio amplifier for applications in battery and mains-fed equipment. Due to special internal circuitry (stabilization, temperature correction, high a.c. feedback of 20dB) the cross-over distortion is negligible over the entire supply voltage range (5 to 14V). Presetting the bias is not required, it is internally adjusted.



Supply voltage V_{11}	6	6	9	V
Load resistance R_L	4	8	8	Ω
A.F. output power at onset of clipping	0,45 0,42	0,35 0,33	0,9 0,8	W 1) W 2)
Sensitivity for $P_o = 50$ mW V_i for $d_{tot} = 10\%$ V_i	1,4 4,8	2,0 7,0	2,0 10	mV mV
T_{amb} (maximum)	70	95	60	°C
Supply current for full output power	185	125	190	mA
Quiescent current I_{tot}	10,0	10,0	10,0	mA
Value of R_1	47	47	47	Ω
R_2	100	100	100	Ω
R_3	1	1	1	Ω
C_1	1,6	1,6	1,6	μF
C_2	47	47	47	μF
C_3	125	125	125	μF
C_4	470	220	220	μF
C_5	1000	470	470	μF
C_6	150	150	150	nF
C_7	47	47	47	μF
Input impedance $ Z_i $	15	15	15	k Ω

SGS TBA820 2W


The TBA820 is intended for use as low frequency class B amplifier with wide range of supply voltage: 3 to 16V. Main features are: minimum working voltage of 3V, low quiescent current, low number of external components, good ripple rejection, no cross-over distortion, mounting compatibility with TAA611.

Output power:

$$P_o = 2 \text{ W at } 12 \text{ V} - 8\Omega \bullet P_o = 1.6 \text{ W at } 9 \text{ V} - 4\Omega \bullet$$

Input sensitivity	$P_o = 1.2 \text{ W}$ $V_s = 9 \text{ V}$ $R_L = 8 \Omega$ $f = 1 \text{ kHz}$ $R_f = 33 \Omega$ $R_t = 120 \Omega$	16 60	mV mV
Input resistance		5	M Ω
Frequency response (-3 dB)	$V_s = 9 \text{ V}$ $R_L = 8 \Omega$ $R_f = 120 \Omega$ $C_B = 680 \mu F$ $C_B = 220 \mu F$	25 to 7k 25 to 20k	Hz Hz
Distortion	$P_o = 500 \text{ mW}$ $V_s = 9 \text{ V}$ $R_L = 8 \Omega$ $f = 1 \text{ kHz}$ $R_f = 33 \Omega$ $R_t = 120 \Omega$	0.8 0.4	% %

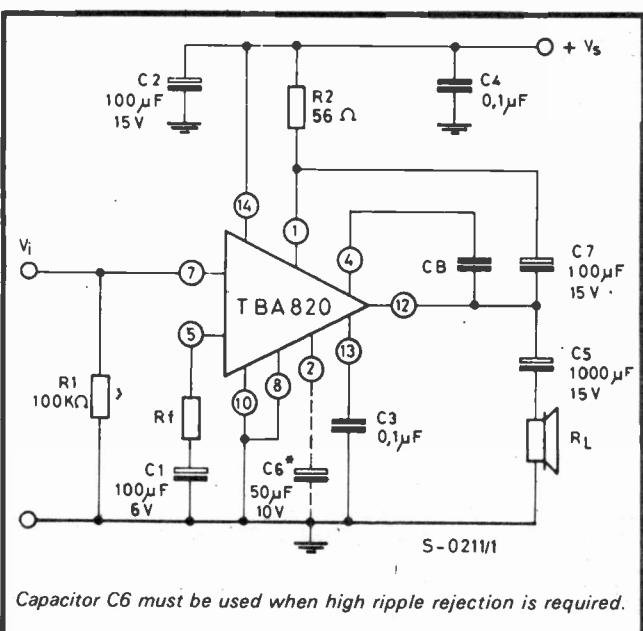SGS ATES, Planar House, Walton Street, Aylesbury.




AUDIO AMPLIFIER ICs

NATIONAL LM377 DUAL 2W


The LM377 is a monolithic dual power amplifier which offers high quality performance for stereo phonographs, tape players, recorders, and AM-FM stereo receivers, etc. The LM377 will deliver 2W/channel into 8 or 16Ω loads. The amplifier is designed to operate with a minimum of external components and contains an internal bias regulator to bias each amplifier. Device overload protection consists of both internal current limit and thermal shutdown.

PARAMETER	CONDITIONS	TYP
Total Supply Current	$P_{OUT} = 0W$	15 mA
	$P_{OUT} = 1.5W/\text{Channel}$	430 mA
DC Output Level		10 V
Supply Voltage		V
Output Power	T.H.D. = < 5%	2.5 W
T.H.D.	$P_{OUT} = 0.05W/\text{Channel}, f = 1\text{ kHz}$	0.25 %
	$P_{OUT} = 1W/\text{Channel}, f = 1\text{ kHz}$	0.07 %
	$P_{OUT} = 2W/\text{Channel}, f = 1\text{ kHz}$	0.10 %
Offset Voltage		15 mV
Input Bias Current		100 nA
Input Impedance		MΩ
Open Loop Gain	$R_S = 0\Omega$	90 dB
Output Swing		$V_S - 6$ V _{P-P}
Channel Separation	$C_F = 250\mu\text{F}, f = 1\text{ kHz}$	70 dB

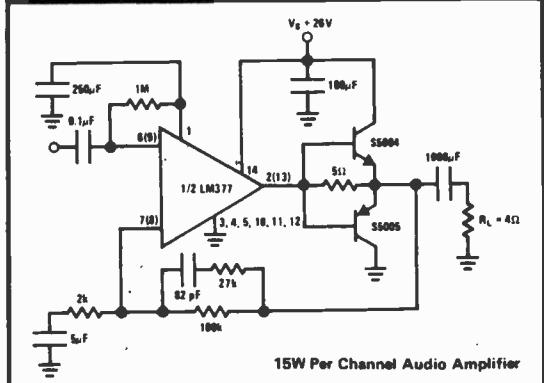National Semiconductors Ltd, Larkfield Estate, Greenock, Scotland.
Typical advertised price: £2.71



15W Per Channel Audio Amplifier

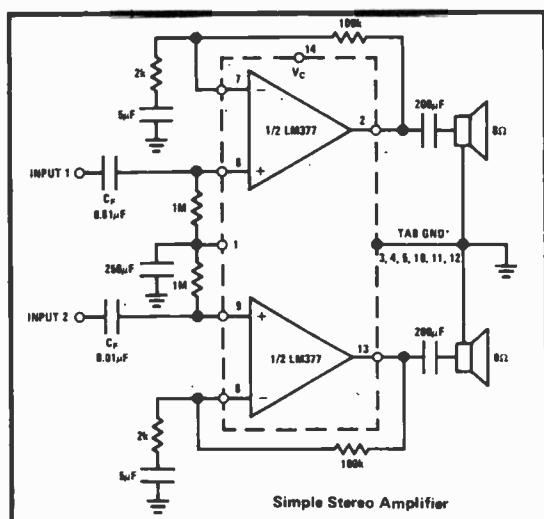


Simple Stereo Amplifier


NATIONAL LM378 DUAL 4W

The LM378 will deliver 4W channel into 8 or 16Ω loads. The amplifier is designed to operate with a minimum of external components and contains an internal bias regulator to bias each amplifier. Device overload protection consists of both internal current limit and thermal shutdown. The LM378 is basically very similar to the LM377, and the above table applies to both I.C.s, with the obvious exception of the output power. The 15W amp and the stereo amplifier are realisable with either chip.

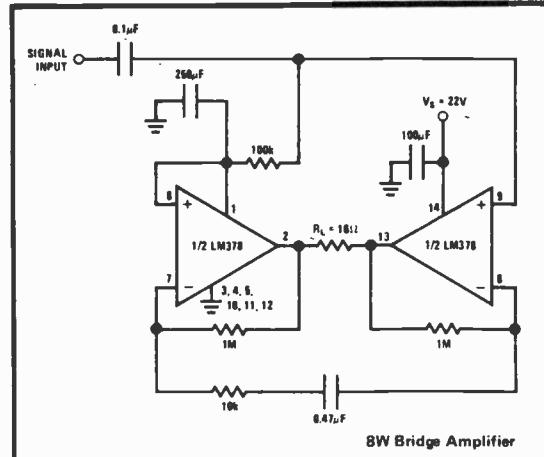National Semiconductors Ltd, Larkfield Estate, Greenock, Scotland.



8W Bridge Amplifier



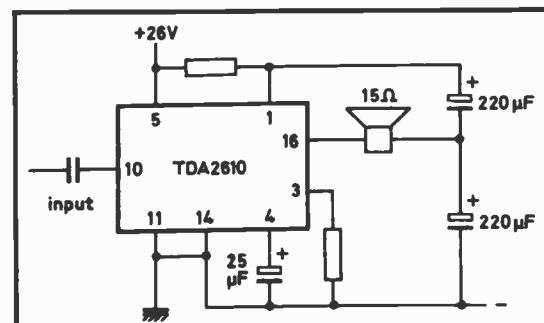


Mullard Ltd, Mullard House, Torrington Place, London SW1

NATIONAL LM384 5W

In order to hold system cost to a minimum, gain is internally fixed at 34 dB. A unique input stage allows inputs to be ground referenced. The output is automatically self-centering to one half the supply voltage.

PARAMETER	CONDITIONS	TYP	UNITS
Input Resistance (Z_{IN})		150	k Ω
Bias Current (I_{BIAS})	Inputs Floating	100	nA
Gain (A_V)		50	V/V
Output Power (P_{OUT})	THD = 10%, $R_L = 8\Omega$	5.5	W
Quiescent Supply Current (I_Q)		8.5	mA
Quiescent Output Voltage (V_{OUTQ})		11	V
Bandwidth (BW)	$P_{OUT} = 2W, R_L = 8\Omega$	450	kHz
Supply Voltage (V^+)			V
Short Circuit Current (I_{SC})		1.3	A
Total Harmonic Distortion (THD)	$P_{OUT} = 4W, R_L = 8\Omega$	0.25	%

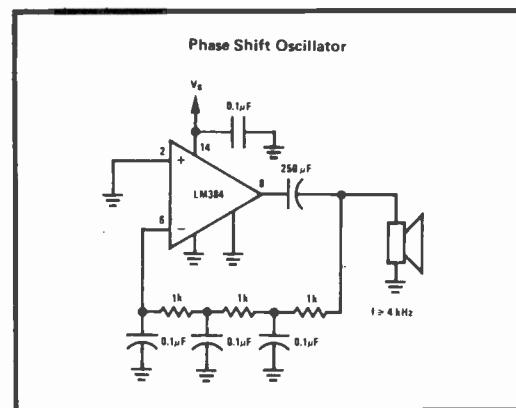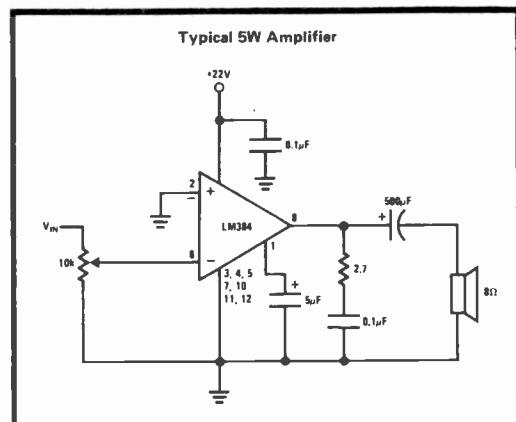
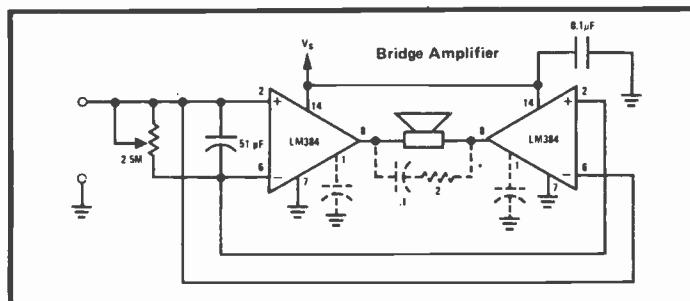


PLESSY SL414A/SL415A 3W/5W

The SL415A and SL414A are robust high gain audio power amplifiers each with a separate pre-amplifier. The circuits have guaranteed power outputs of 5W and 3W respectively.


Typical advertised price: SL414 £1.80,
SL415 £2.75.

Supply voltage		
SL414A	18	V
SL415A	24	V
Power into 15Ω load		
SL414A	2.2	W
SL415A	3.8	W
Pre amp. voltage gain		
	24	dB
Main amp. voltage gain		
	26	dB
Main amp. o/p impedance		
	0.2	Ω
Distortion		
Pre amp.	0.1	%
Main amp.	0.3	%
Noise level		
	-75	dB
Ripple rejection		
	30	dB
Input impedance		
Pre amp	20	M Ω
Main amp	100	M Ω

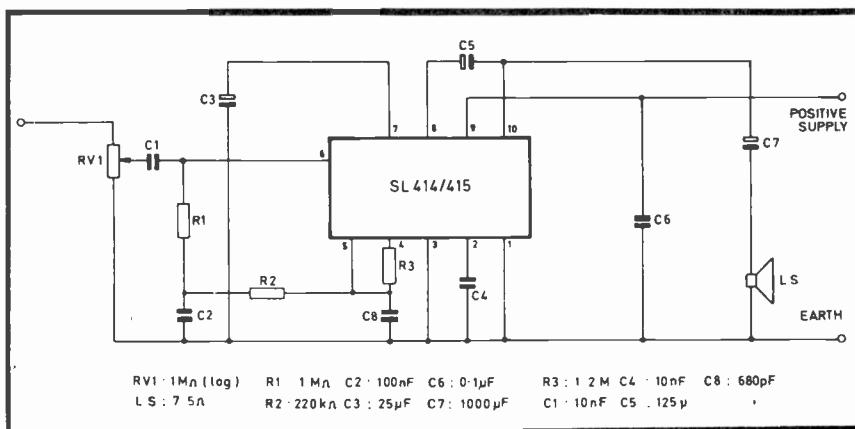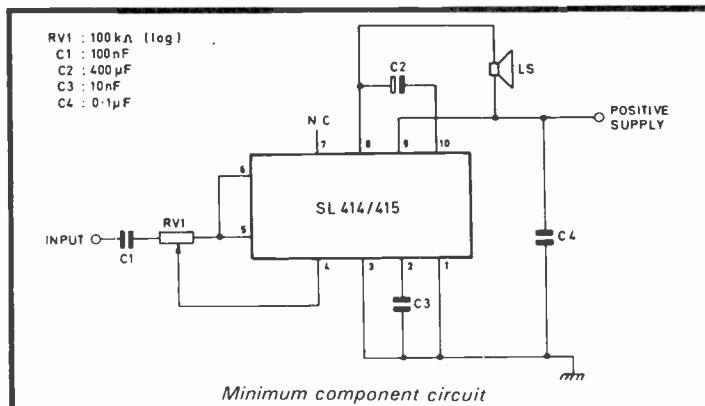

NATIONAL LM379 DUAL 6W

The LM379 will deliver 7W/channel to an 8Ω load. The amplifier is designed to operate with a minimum of external components and contains an internal bias regulator to bias each amplifier. Device overload protection consists of both internal current limit and thermal shutdown. The LM379 may be used to advantage in any of the circuits given earlier for either the LM377 or the LM378 amplifier ICs. The circuit below delivers 14W r.m.s. into a 16Ω load.

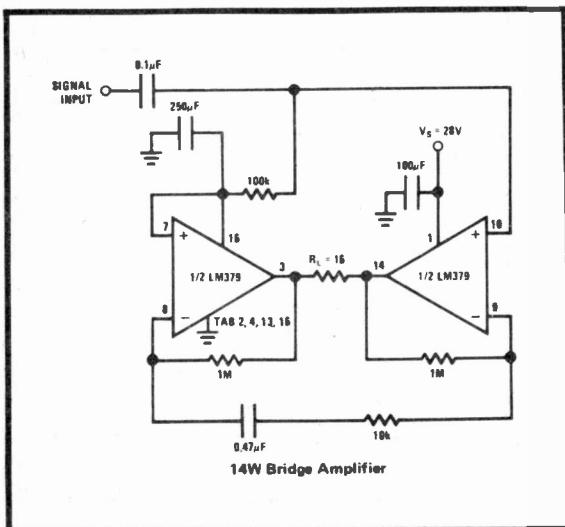


National Semiconductors Ltd, Larkfield Estate, Greenock, Scotland.


PARAMETER	CONDITIONS	TYP
Total Supply Current	$P_{OUT} = 0W$	15 mA
	$P_{OUT} = 1.5W/\text{Channel}$	430 mA
DC Output Level		14 V
Supply Voltage		10 V
Output Power	$T.H.D. = 5\%$	6 W
	$T.H.D. = 10\%$	7 W
T.H.D.	$P_{OUT} = 1W/\text{Channel}, f = 1\text{ kHz}$	0.07 %
	$P_{OUT} = 4W/\text{Channel}, f = 1\text{ kHz}$	0.2 %
Offset Voltage		15 mV
Input Bias Current		100 nA
Input Impedance		MΩ
Open Loop Gain	$R_S = 0\Omega$	90 dB
Channel Separation	$C_F = 250\mu F, f = 1\text{ kHz}$	70 dB
Ripple Rejection	$f = 120\text{ Hz}, C_F = 250\mu F$	70 dB
Current Limit		1.5 A
Slew Rate		1.4 V/μs
Equivalent Input Noise Voltage	$R_S = 600\Omega, 100\text{ Hz} - 10\text{ kHz}$	3 μVrms

SGS TDA 2010 12W

The TDA 2010 is a monolithic integrated operational amplifier in a 14-lead quad in-line plastic package, intended for use as a low frequency class B power amplifier. Typically it provides 12 W output power ($d=1\%$) at $\pm 14\text{ V}/4\Omega$; at $V_S = \pm 14\text{ V}$ the guaranteed output power is 10 W on a 4Ω load and 8 W on a 8Ω load (DIN norm 45500). The TDA 2010 provides high output current (up to 3.5 A) and has very low harmonic and cross-over distortion. Further, the device incorporates an original (and patented) short circuit protection system, comprising an arrangement for automatically limiting the dissipated power so as to keep the working point of the output transistors within their safe operating area. A conventional thermal shut-down system is also included. The TDA 2010 is pin to pin equivalent to TDA 2020.

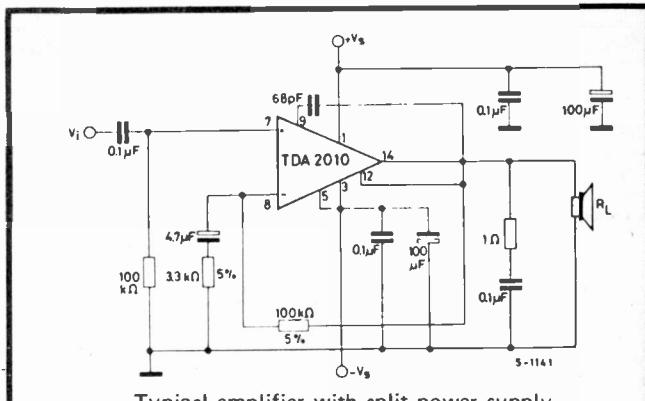

Parameter	Min.	Typ.	Max.	Unit
R_i Input resistance (pin 7)		5		MΩ
V_s Supply voltage	± 5	± 18		V
P_o Output power		12		W
V_i Input sensitivity	220		250	mV
				mV
B Frequency response(-3 dB)	10 to 160,000			Hz
d Distortion		0.1		%
* Thermal shut-down case temperature		120		°C

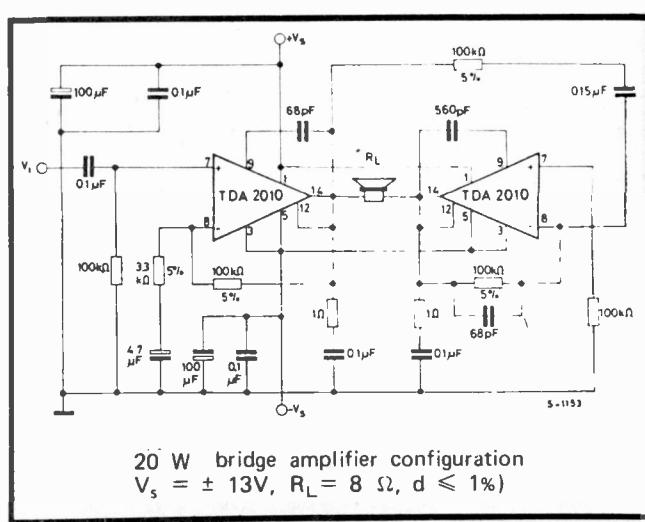


20 W bridge amplifier configuration
 $V_s = \pm 13\text{ V}$, $R_L = 8\Omega$, $d \leq 1\%$



SGS TDA 2020 20W

The TDA 2020 is a monolithic integrated operational amplifier in a 14-lead quad in-line plastic package, intended for use as a low frequency class B power amplifier. Typically it provides 20 W output power ($d=1\%$) at $\pm 18 \text{ V}/4\Omega$, the guaranteed output power at $\pm 17 \text{ V}/4\Omega$ is 15W (DIN norm 45500). Being a pin-pin replacement for the 2010, all circuits given here, for either device, can apply to both. The PCB layout similarly is applicable to both circuits.

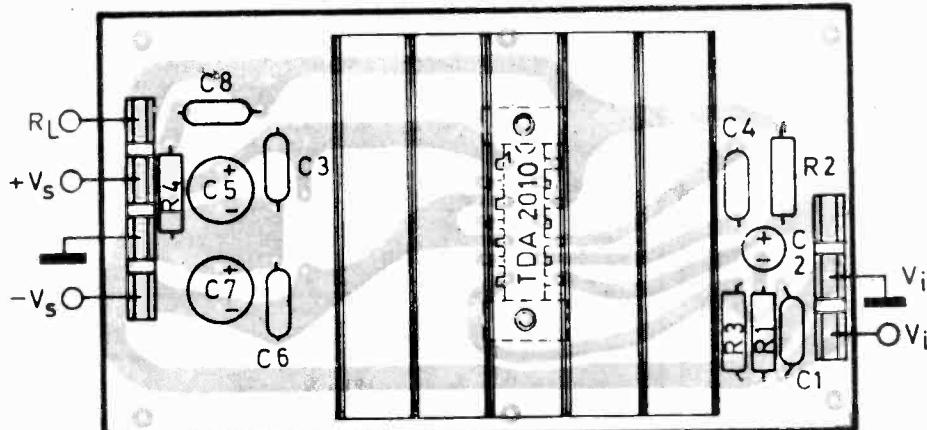Heatsink guidelines are to be observed. Pin 5 is electrically connected to the copper slug on both devices and should be connected to most negative point.




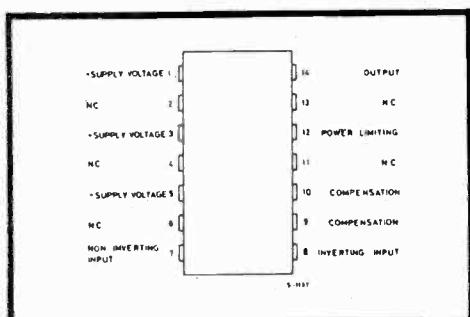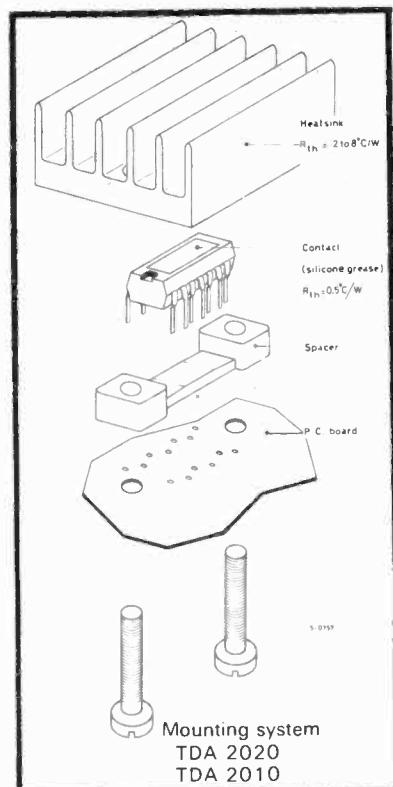Printed circuit board layout – TDA 2010/20 with split supply rails




Parameter	Test conditions	Min.	Typ.	Max.	Unit
P _o	Output power	d = 1% T _{case} ≤ 70 °C f = 40 to 15,000 Hz V _s = ± 17V R _L = 4 Ω V _s = ± 18V R _L = 4 Ω V _s = ± 18V R _L = 8 Ω	15	18.5	W
			20		W
			16.5		W
	d = 10% T _{case} ≤ 70 °C f = 1 kHz V _s = ± 17V R _L = 4 Ω V _s = ± 18V R _L = 8 Ω	24		W	
		20		W	
V _i	Input sensitivity	G _v = 30 dB P _o = 15W V _s = ± 17V R _L = 4 Ω V _s = ± 18V R _L = 8 Ω		260	mV
			380		mV

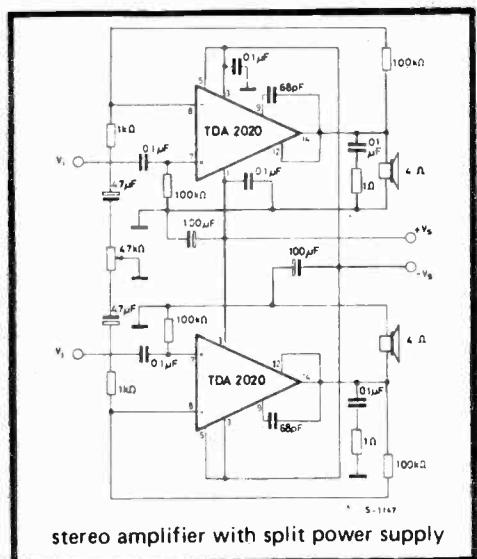SGS ATES, Planar House, Walton Street, Aylesbury.
Typical advertised price: TDA 2010 £3, TDA 2020 £3.75.



stereo amplifier with split power supply

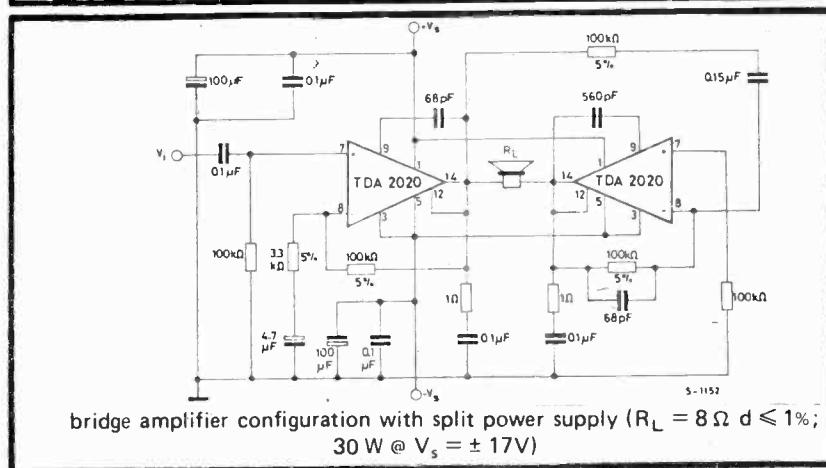

bridge amplifier configuration with split power supply ($R_L = 8\Omega$ $d \leq 1\%$;
 $30\text{ W} @ V_s = \pm 17\text{ V}$)

For a more detailed description of the TDA 2020 and related performance refer to SGS-ATES Application Note n. 130.

ILP HY200 100W

The HY200 is a 100 Watt amplifier of hybrid construction with an integral heatsink. Internally the HY200 features open and short circuit protection with the added feature of thermal shutdown when the heatsink rises above a predetermined temperature, with these features the HY200 can be installed into any equipment with the confidence that it is virtually indestructible under any operating conditions. The low distortion and high signal to noise ratio together with wide band width makes the HY200 an amplifier of true hi-fi performance and these factors coupled with its robustness make it suitable for hi-fi, group, disco, PA, etc:

NOTES OF OPERATION

No input capacitor is required due to an internal capacitor of 250 volt working.

Output is directly coupled to loudspeaker via a *quick blow* fuse of 3 amps.

The amplifier can only be used on a split line power supply, i.e. 45-0-45 VDC.

The thermal shutdown operates at approximately 70°C and will turn the amplifier on again when the heatsink has cooled by 10°C. Under operating conditions the temperature of the heatsink should be between 30-60°C depending upon the type of signal and output power used.

It is recommended that the HY200 is mounted with the fins vertical and unrestricted airflow around them.

POWER SUPPLY REQUIREMENTS

MAXIMUM SUPPLY VOLTAGE: 50-0-50 VDC

RECOMMENDED SUPPLY: 45-0-45 VDC

SUPPLY CURRENT: 2ADC

SPECIFICATION

Output power 100 watts into 8Ω

Input sensitivity 500mV R.M.S.

Input impedance 100KΩ

Signal/noise ratio 96 db at 100 watts

Power bandwidth 10Hz — 45KHz ± 3db

Distortion 0.05% typical

Weight 1 kilo (2.2lb)

No circuits are given here for the HY200, but the device is so simple to connect, that we did not feel this would be a drawback. Only five connections are provided to the IC, Input, Output, Earth and two supply rails. These are colour coded, and ILP provide data with each HY200. So you didn't really need any circuits, now did you?

P.E. CAR CLOCK KIT AVAILABLE

Send s.a.e. for details/prices, etc.

ADVANCED ALARM CLOCK KIT

Complete kit including attractive slim case with perspex panel for 6 digit alarm clock with bleep alarm, snooze and automatic intensity control, high brightness display driving; uses MK50253 IC and Jumbo 0.5in red LEDs. Kit also includes PCBs, active and passive components, IC skt., min. transformer, switches, flat cable, loudspeaker, mains cable and plug. Full instructions. Crystal control/battery back-up and touch switch snooze and alarm are optional add-ons £27.31

SIMPLE & ATTRACTIVE 4-digit CLOCK KIT

(As featured in January Everyday Electronics) Ideal kit for the less experienced constructor; kit includes IC, pleasing ½" green display with colon, PCB, miniature transformer, slim white case with perspex front panel, and all other components except mains cable and plug. Full instructions £15.69

CRYSTAL TIMEBASE KIT

All components including PCB (47mm x 59mm) to provide 50cps for clock ICs giving time accurate to a few seconds a month. Kit includes PCB, 32.768 kHz miniature watch crystal, trimmer, 3 CMOS ICs and sockets, Cs. Rs. £6.28

STOPWATCH

Complete Kit for Stopwatch (as in December ET1); choose 6 digit range from tens of hours to milliseconds. Contents Verocase 75/1410J, red perspex front panel, Manganese batteries, clips, transistors, diodes, wiring pins, screws, sockets, pin-header, CMOS, resistors, capacitors, 5 12MHz crystal, trimmer, PCBs, 6 x MAN3M displays. With instructions, component layout, etc. £31.80

STOPWATCH WITH ONE LATCH: As above, but kit also includes facility to repeatedly freeze one set of displays with count continuing on the other set £47.71

ADD VAT at 8% to all Prices in this advertisement. 25p P&P on all orders. Free on orders over £3. Orders sent by 1st Class Post. Exports No VAT. 35p (Europe) £1 (Overseas) for Air Mail P&P (any excess refunded). Full Price List and Data with any order or on request (phone or send s.a.e.)

Official Orders welcomed, written phoned or telexed, from Univas Polys Nat Inds Govt Departments, Companies, etc. Fastest Delivery for R&D.

53a Aston Street, Oxford
Tel. 0865 49791
Telex: 837650. A/B ELECTRONIC OXFD

SINTEL

CMOS

CMOS from the leading manufacturers only

CD4000A	0.17	CD4028A	0.74	CD4053A	0.77	CD4086B	0.59
CD4001A	0.17	CD4029A	0.94	CD4054A	0.95	CD4089B	1.27
CD4002A	0.17	CD4030A	0.46	CD4055A	1.08	CD4093B	0.66
CD4006A	0.97	CD4031A	1.82	CD4056A	1.08	CD4094B	1.53
CD4007A	0.17	CD4032A	0.88	CD4057A	20.35	CD4095B	0.86
CD4008A	0.79	CD4033A	1.14	CD4059A	10.64	CD4096B	0.86
CD4009A	0.46	CD4034A	1.56	CD4060A	0.92	CD4099B	1.50
CD4010A	0.46	CD4035A	0.97	CD4061A	16.43	CD4502B	0.98
CD4011A	0.17	CD4036A	1.82	CD4062A	7.33	CD4510B	1.12
CD4012A	0.17	CD4037A	0.78	CD4063B	0.90	CD4511B	1.28
CD4013A	0.46	CD4038A	0.88	CD4066A	0.58	CB4514B	2.56
CD4014A	0.83	CD4039A	2.86	CD4067B	2.95	CD4515B	2.56
CD4015A	0.83	CD4040A	0.88	CD4068B	0.18	CD4516B	1.12
CD4016A	0.46	CD4041A	0.59	CD4069B	0.18	CD4518B	1.03
CD4017A	0.83	CD4042A	0.69	CD4070B	0.18	CD4520B	1.03
CD4018A	0.83	CD4043A	0.83	CD4071B	0.18	CD4527B	1.30
CD4019A	0.46	CD4044A	0.77	CD4072B	0.18	CD4532B	1.16
CD4020A	0.92	CD4045A	1.15	CD4073B	0.18	CD4555B	0.74
CD4021A	0.83	CD4046A	1.10	CD4075B	0.18	CD4556B	0.74
CD4022A	0.79	CD4047A	0.74	CD4076B	1.27	MC1450B	2.37
CD4023A	0.17	CD4048A	0.46	CD4077B	0.18	MC1452B	0.86
CD4024A	0.64	CD4049A	0.46	CD4078B	0.18	MC1453A	6.04
CD4025A	0.17	CD4050A	0.46	CD4081B	0.18	MC14553	4.07
CD4026A	1.42	CD4051A	0.77	CD4082B	0.18	MC1456B	1.21
CD4027A	0.46	CD4052A	0.77	CD4085B	0.59	MCM14552	8.05

RCA 1975 CMOS Databook: 400 pages of data sheets and 200 pages of circuits, applications and other useful information £2.67 (Add no VAT—post free)

Motorola McMOS Databook (Volume 5, Series A)

£2.77 (Add no VAT—post free)

CLOCK ICs	DISPLAYS	VEROCASES
MK50253	£5.60	DL704E 85p 75 1410J £2.64
MK50250	£5.00	FND500 £1.02 (205 x 140 x 40mm)
MM5314	£4.44	FND5000 95p 75/1411D £2.94
AY51202	£4.76	MAN3M 48p (205 x 140 x 75mm)
AY51224	£3.66	5LT01 £5.80 Flat Cable
MK5030M	£12.50	L C D £9.40 20-way £1 per m.

DISPLAY PCBs (each fits neatly into Verocase J) for clock with 6 x FND500, for clock with 6 x DL704, for counter with up to 8 x FND500, for counter with up to 8 x DL704 these four are £1.35 each. for clock with 4 x FND500 90p.

IC SOCKET PINS. Lowest cost sockets for CMOS, TTL, ICs, Displays Strip of 100 pins for 50p, 400 for £2, 1,000 for £4, 3,000 for £10.50.

TECHNICAL BOOKS FROM ETI

CALCULATORS

99 WAYS TO KNOW AND USE YOUR ELECTRONIC CALCULATOR

L. Frenzel £4.00

SCIENTIFIC ANALYSIS ON YOUR POCKET CALCULATOR

Smith £8.25

COMPUTERS

BEGINNERS' GUIDE TO COMPUTER LOGIC

G. Stapleton £1.95

Grasp quickly computer codes, digital logic ops and switching circuits

COMPUTER CIRCUITS AND HOW THEY WORK

B. Wells £1.80

Become acquainted with the various parts of a computer and its technology

COMPUTER TECHNICIANS HANDBOOK

B. Ward £2.60

This giant volume compares to a 1,000 hour course on computer mechanics.

CONTROL ENGINEERING

N. M. Morris £3.45

This is the 2nd edition of a highly successful book, keeping fully abreast of developments in control engineering.

DIGITAL ELECTRONIC CIRCUITS AND SYSTEMS

N. M. Morris £2.60

The ideal book for the enthusiast confused by logic and digital techniques.

INTRODUCTION TO DIGITAL LOGIC

A. Potton £3.35

Up to date book using integrated circuits with emphasis on practical design methods.

ELECTRONICS

ACTIVE FILTER COOKBOOK

D. Lancaster £9.40

Everything you need to know to build and use active filters.

ELECTRONIC ENGINEERS REFERENCE BOOK - 4th EDITION

L. W. Turner £25.60

A completely new and up-to-date reference book for all engineers and students.

BASIC MATHS COURSE FOR ELECTRONICS

H. Jacobowitz £1.75

Quick short cut way to learn the language of maths as applied to electronics.

BEGINNERS GUIDE TO ELECTRONICS

T. L. Squires £2.55

Short cut for those wishing to obtain a quick acquaintance with modern electronics.

BEGINNERS GUIDE TO TRANSISTORS

J. A. Reddiough £2.55

Covers the basic theory and practice of modern transistors.

DESIGNING WITH TTL INTEGRATED CIRCUITS

Texas Instruments £5.70

Covers the entire family of TTL and practical applications of circuits in digital systems.

ELECTRONIC CIRCUIT DESIGN HANDBOOK

EEEMA £5.00

Circuit designers cookbook containing 639 winning designs.

ELECTRONIC MEASUREMENTS SIMPLIFIED

C. Hallmark £2.10

Covers just about every conceivable test or measurement you will need.

ELECTRONICS POCKET BOOK

P. McGoldrick £4.15

ELECTRONICS AND PHOTOGRAPHY

R. Brown £2.20

Practical circuit projects devoted to photography.

ELECTRONICS SELF TAUGHT

J. Ashe £2.20

Covers basic principles of electronics includes a large number of simple circuits.

ESSENTIAL FORMULAE FOR ELECTRICAL AND ELECTRONIC ENGINEERS

N. M. Morris £1.20

Handy reference book, includes a section on S1 units, resistor colour codes and preferred values.

HOW TO BUILD ELECTRONIC KITS

V. Capel £2.10

Instructs the kit builder on how to check components, how to assemble and how to cure faults.

FIRE AND THEFT SECURITY SYSTEMS

B. Wells £1.90

Selection and installation, home maintenance and business security devices.

HANDBOOK OF IC CIRCUIT PROJECTS

J. Ashe £1.75

From hi-fi circuits to complete digital counters in a single package.

HOW TO READ ELECTRONIC CIRCUIT DIAGRAMS

B. Brown £1.85

Everything you need to know from basic circuit components to integrated circuits.

HOW TO BUILD PROXIMITY DETECTORS AND METAL LOCATORS

J. Shields £3.00

A practical do-it-yourself book.

HOW TO USE IC CIRCUIT LOGIC ELEMENTS

J. Streater £3.00

Helps those unfamiliar with digital logic circuits.

INTEGRATED ELECTRONICS

J. Millman £5.25

Using an IC approach the text leads the reader step by step from semiconductor physics to devices, models, circuits and systems.

INTEGRATED CIRCUIT POCKET BOOK

R. C. Hibberd £3.90

Technology and fabrication of unipolar and bipolar IC's are discussed digital and linear IC's covered from a circuit point of view.

IC OP-AMP COOKBOOK

W. Jung £7.50

Covers the basic theory of IC op amps in great detail, also includes 250 practical circuit applications.

INDEXED GUIDE TO MODERN ELECTRONIC CIRCUITS

R. Goodman £2.25

Practical Schematics with concise theory and troubleshooting information.

INTRODUCING AMATEUR ELECTRONICS

I. R. Sinclair £1.60

The book for the complete novice of any age.

INTRODUCING ELECTRONIC SYSTEMS

I. R. Sinclair £1.75

Provides a basic insight into what makes electronics tick.

INSTALLING AND SERVICING ELECTRONIC PROTECTIVE SYSTEMS

H. Swearer £2.10

Covers installation and servicing of all electronic security systems.

LINEAR ELECTRONIC CIRCUITS AND SYSTEMS

G. Bishop £2.55

Illustrates the use of the op amp in many different applications.

LINEAR INTEGRATED CIRCUIT APPLICATIONS

G. Clayton £4.90

A practical approach is emphasised throughout, encouraging the reader to try out devices himself.

LINEAR IC PRINCIPLES EXPERIMENTS AND PROJECTS

E. M. Noll £5.50

An introduction to one of electronics most exciting devices.

110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR

R. M. Marston £2.85

Outlines the essential characteristics of op amps and presents useful projects.

110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR

R. M. Marston £2.85

Introduces the reader to FET's, SCR's and IC's with full construction details of many useful circuits.

110 COSMOS DIGITAL IC PROJECTS FOR THE HOME CONSTRUCTOR

R. M. Marston £3.10

A companion to the author's previous books.

110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR

R. M. Marston £2.85

All the projects have been devised built and fully evaluated by the author.

110 THYRISTOR PROJECTS USING SCR'S

R. M. Marston £2.85

A companion to the author's previous books.

OPERATIONAL AMPLIFIERS DESIGN AND APPLICATIONS (Burr Brown)

G. Tobe £5.00

Covers the entire field of operational amplifiers.

PIN POINT TRANSISTOR TROUBLESHOOTING IN 12 MINUTES

L. Garner £2.85

Complete information on circuit operations, troubleshooting charts and service procedures.

PRACTICAL TRIAC/SCR PROJECTS FOR THE EXPERIMENTER

R. Fox £2.15

Thyristor theory and practical circuits with low cost SCR, TRIACs and DIACs.

PRINCIPLES OF TRANSISTOR CIRCUITS

S. Amos £4.40

Generally accepted as being a standard textbook on fundamental principles underlying the design of circuits and using transistors.

RAPID SERVICING OF TRANSISTOR EQUIPMENT

G. King £2.85

A systematic guide to the servicing of transistor radio, television, tape and hi-fi equipment.

SEMICONDUCTOR CIRCUIT ELEMENTS

T. D. Towers £6.00

Gives readers an account of all semiconductor devices commercially available for each device it covers a general description, circuit diagram symbols and working principles.

SOLID STATE CIRCUIT GUIDE BOOK

B. Ward £2.15

Step by step instructions to design circuits to your own specifications.

TRANSISTOR CIRCUIT DESIGN

Texas £5.75

Comprehensive guide to the characteristics and uses of various types.

TRANSISTOR POCKET BOOK

R. Hibberd £3.65

Comprehensive guide to the characteristics and uses of various types.

TTL COOKBOOK

D. Lancaster £5.50

Complete and detailed guide to TTL how it works, how to use it and practical applications.

UNDERSTANDING ELECTRONIC CIRCUITS

R. Sinclair £4.00

Describes various circuits encountered today with a strong emphasis on fault finding and servicing procedures.

UNDERSTANDING ELECTRONIC COMPONENTS

R. Sinclair £4.00

Explains about components and bridges the gap between elementary textbooks and unapproachable advanced treatments.

UNDERSTANDING CMOS INTEGRATED CIRCUITS

R. Melen £3.30

Begins with basic digital IC's, covers semiconductor physics, CMOS fabrication technology and design.

UNDERSTANDING SOLID STATE CIRCUITS

N. Crowhurst £1.90

Written to service the interests of anyone at sub-engineering level.

SEMICONDUCTOR DATA

INTERNATIONAL TRANSISTOR SELECTOR

T. D. Towers £3.45

If it takes you longer than one minute to find out all about transistors, then you need a copy of this book.

POPULAR VALVE/TRANSISTOR SUBSTITUTION GUIDE

£2.15

Substitution data for both valves and transistors in one new volume.

RADIO VALVE AND SEMICONDUCTOR DATA

A. M. Ball £2.50

Characteristics of 1 000 valves, cathode ray tubes, transistors, diodes, rectifiers and optical semi-conductors. This new edition (1975) is right up to date and over 450 000 copies have been sold.

TRANSISTOR EQUIVALENTS DATA BOOK

£3.00

DIODE EQUIVALENT DATA BOOK

£2.65

TEST EQUIPMENT AND OSCILLOSCOPES

BASIC ELECTRONIC TEST PROCEDURES

I. M. Gottlieb £2.35

Shows how to get accurate measurement with VOM's meters and oscilloscopes.

ELECTRONIC TEST EQUIPMENT

R. Kitchen £5.00

Explains the principles and requirements of particular types of test equipment including typical circuitry.

HOW TO TROUBLESHOOT AND REPAIR ELECTRONIC TEST EQUIPMENT

M. Horowitz £2.15

Packed with practical data on repair of all types of instruments.

HOW TO TEST INSTRUMENTS IN ELECTRONIC SERVICING

F. Schunaman £2.15

The all-in-one test instruments application handbook.

HOW TO USE VECTORS, OSCILLOSCOPES AND SWEEP SIGNAL GENERATORS

S. Prentiss £1.95

A practical guide that tells how to use modern TV test instruments.

HOW TO USE YOUR VDM VTVM AND OSCILLOSCOPE

M. Clifford £1.85

Tremendous value in helping to select instruments best suited to individual needs.

THE OSCILLOSCOPE

G. Zwick £2.10

Starts from the first principles and takes the reader to an advanced level.

PRACTICAL TEST EQUIPMENT YOU CAN BUILD

W. Green £2.15

For technicians, radio/TV service operators and serious experimenters.

RADIO, TV AND AUDIO TEST EQUIPMENT

G. King £4.95

A practical guide to test instruments and applications, concerned largely with the oscilloscope.

TEST INSTRUMENTS FOR ELECTRONICS

M. Clifford £1.65

Easy modifications to your VOM/VTVM and scope with the aid of this book.

WORKING WITH THE OSCILLOSCOPE

A. Saunders £1.85

Includes workshop test projects with large size drawings.

SERVICING WITH THE OSCILLOSCOPE

(January 1976) £5.00

Includes a unique series of photographs showing oscilloscope traces to be found in normal and faulty equipment stereo radio colour TV Circuits servicing is dealt with.

HOW TO ORDER

All prices are correct at the time of going to press but are subject to alteration without notice. All prices include postage. Please print your name and address clearly and list each title and price separately. Cheques and postal orders should be made payable to ETI Book Service. Books are sent on seven days' approval against a full cash remittance, plus postage. Book stock is not held at ETI's London offices and orders should be sent to: ETI BOOK SERVICE, 25 COURT CLOSE, BRAY, MAIDENHEAD, BERKS.

eti microfile

MEMORIES ARE MADE OF THIS

WE HAVE ALREADY SEEN in *Microfile 1* (March 1976) that the key concept of the microprocessor is that its operation is controlled by a sequence of bit patterns held in memory, in an identical manner to the operation of the full-scale digital computer. Micro systems almost always incorporate two types of semiconductor (MOS or bipolar) memory.


For programs which are permanently resident in the system and must not be erased when power is lost (e.g. traffic light control programs, micro-computer load/monitor programs) the program is held in *Read Only Memory (ROM)* which is preprogrammed before the system goes into operation and is then only changed in exceptional circumstances (such as the discovery of a program fault or *bug*). For the storage of intermediate results, and programs which are not permanently resident in the system, *Random Access Memory (RAM)* is used which can be both read from, and written into, by the processor.

ROM

Read Only Memory chips are available in several types and are made by many manufacturers. The main type used by manufacturers of equipment using microprocessors in high volume runs is *Mask Programmed ROM*, which is programmed during manufacture by the specification of a metallization mask pattern worked out by computer from a punched paper tape or deck of punched cards. This is the cheapest form of ROM in large quantities, but of course is unalterable once made and no company would ever go to ROM without thoroughly testing their programs for bugs. Mask-programmed ROM is uneconomic in small quantities and impossible for one-offs. Typical devices are the Motorola MCM6830, Intel 8308, and AMD Am2961.

PROM

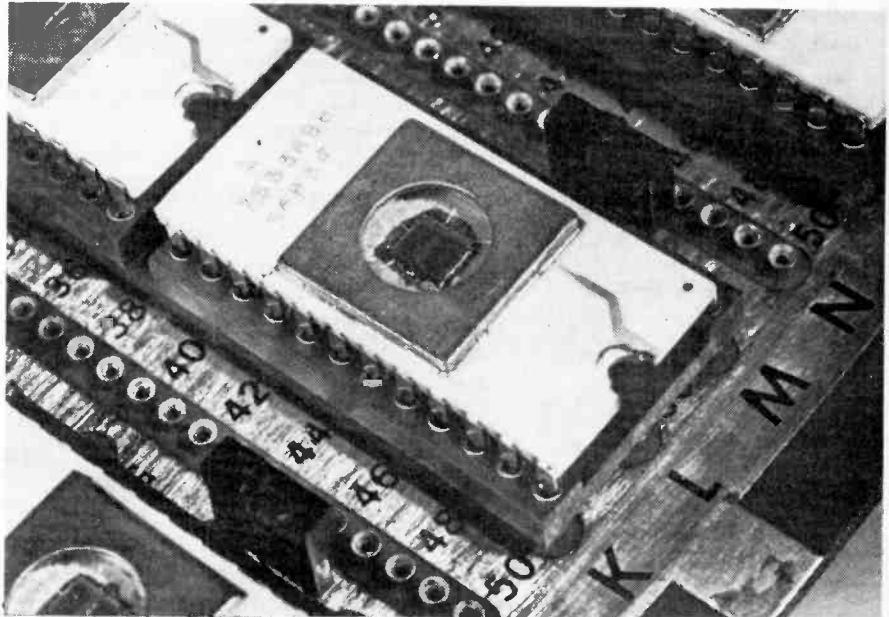Programmable Read Only Memory is used in small-volume systems and for development work. These PROMs (often called fusible-link PROMs) are programmed simply by blowing small links made either of nichrome or polysilicon. This is done by selecting the address of the bit to be programmed



The AMI S6830 EPROM.

in the normal manner, and applying a short, (on the order of a few hundred microseconds) high current pulse at the output pin. Once programmed, the chip can be plugged into the system and, hopefully, the program will run. AMD's Am2971 is typical of the genre.

EPROM

The Erasable PROM can be 'wiped clean' by lifting the cover from a transparent quartz window on the top of the chip and exposing it to an ultra-violet source for around ten minutes. The EPROM can then be reprogrammed by a similar method to a fusible-link PROM. The device in fact operates by trapping charge in a floating gate avalanche injection MOSFET. This device is extremely useful in prototyping systems but it is a bit pricey for production use. AMI's S6830, which was mentioned last month is a good choice of EPROM


for micro systems, or alternatively Intel's 2708, 2704 and 8702 are in fairly common usage.

EAROM

Electrically Alterable ROM can be repeatedly erased and reprogrammed electrically, considerably more quickly than EPROM, e.g. erasure takes only 100 mS. Some EAROMs (e.g. NCR1105) are erasable by row, so that complete erasure and reprogramming is not necessary.

GENERAL ORGANIZATION

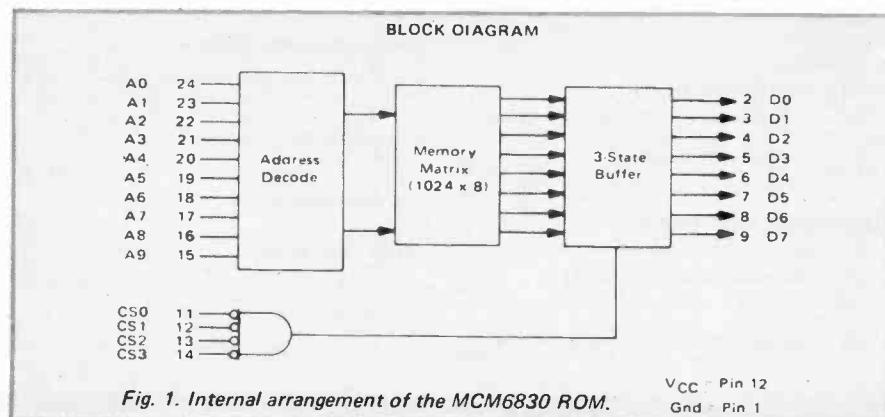Most of the devices mentioned above are byte-wise organised, i.e. when a specific address on the chip is selected, the processor puts 'read' out on the control bus and VMA goes high, then 8 bits in parallel are output onto the data bus. Note on figure 1 that the output to the data bus goes via a set of three-state output buffers. Three-state logic (Tri-state logic is a National



trademark) was explained in ETI in October 1972, and we made reference to it last month when discussing the Halt, DBE and TSC control signals of the MPU. As far as memory is concerned, if the chip select inputs of the ROM (or RAM) chips are not enabled, the output buffers stay in the high-impedance mode and isolate the chip from the bus. Thus, as many chips as required can be wire-ORed onto the data bus, and they are only in a low impedance (0 or 1) state when selected.

RAM

There are two types of RAM: static and dynamic. If data is stored in a static RAM, provided power is kept on the device and all other signals are kept constant, the data will be maintained. However, a dynamic RAM uses the parasitic capacitance of MOSFET gates with a storage cell to store the data. Therefore, due to junction leakage currents, this is only possible for a short time and so the data has to be refreshed once every 1mS, typically. This is done by cycling through the low-order address lines ($A_0 - A_4$).

Static RAM is, in general slower in operation, and is smaller. Once again, byte wise organised memories are most suitable for ease of use in MPU systems, and these can only be found in static types. The Motorola M6800 family includes a 128 byte static RAM, MCM6810, which is easy to use in a 6800 system. As in the case of ROM, three-state buffers are provided on the chip, but in the case of RAM they are bi-directional. Note that some chips do not have three-state buffers (e.g. AMD Am2970, Am2950) and so are more difficult to design into bus-oriented systems.

Dynamic memories offer higher density storage, at the penalty of increased circuit complexity. 4k (4096 bit) dynamic RAMs are now the industry standard and are commonly available in 22 pin and now 16 pin DIL packages. However, additional memory refresh circuitry must be provided so that one would regard a card of around 8k bytes of dynamic RAM as a convenient 'building block' for memory systems, with static RAM being used for smaller memory boards, which can be simply extended when required. Dynamic RAM is of course organised as 4k x 1 bit rather than byte oriented, hence one should use 8 x 4k chips to make a 4k byte memory system.

ADDRESSING MEMORY

Most 8 bit microprocessors, including the M6800 which we have used as an example, have a 16 bit address bus. Consequently they can address up to

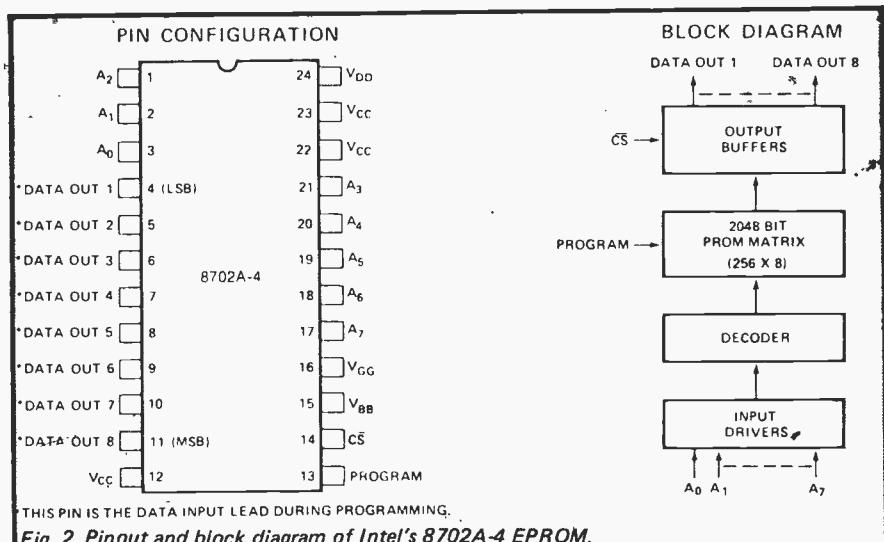


Fig. 2. Pinout and block diagram of Intel's 8702A-4 EPROM.

65k of memory directly over the 16 lines of the address bus. However, as some of you will have noticed, the MCM6830 ROM has only 10 address inputs, and the MCM6810 RAM has only 6. This is where the chip select inputs come in handy. Using them one can position a chip anywhere in memory, for example starting at address 2048 or at 0 simply by connecting the CS and CS (NOT CS) inputs to the address bus lines that are left over. Only when all the CS inputs are at 1 and the CS inputs at 0 will the chip be enabled. One can, for example, arrange that the CS inputs of a 6830 ROM be connected to bits 14 and 15 of the address bus, while the CS inputs of 1 6810 RAM are connected to bits 14 and 15. This means that the ROM starts at address 49152 i.e. C000 HEX, while the RAM starts from zero and goes up to address 127 or 007F HEX.

In addition, one should note that Q2 of the system clock should be applied to CS so that the chip is only enabled during Q2 of the clock cycle. It is also good practice to connect VMA to a CS input. Of course, if one runs out of CS inputs one can always AND signals before applying them to a CS, or alternatively NAND them and then apply that signal to CS.

Bringing together then our knowledge of the bus configuration of an

M6800 system we end up, (Fig. 4) with a minimum system consisting of the MPU, 1 ROM, 1 RAM, 1 PIA (Peripheral Interface Adaptor), and 1 ACIA (Asynchronous Communication Interface Adaptor). The last two units are the I/O devices of the 6800 series, but no special instructions exist to handle data input/output. Instead, the devices sit on the buses and are written into and read from exactly as if they were memory locations. Hence the connections from the PIA and ACIA to the are CS and CS inputs, RS (Register Select) to address one of the internal registers on the chip and E (Enable) inputs which are normally connected to Q2 of the system clock, and the I/O chips look to the processor like memory.

THE PIA

The Peripheral Interface Adaptor (MC6820) is the parallel I/O device of the 6800 microcomputer system, and gives 16 independent lines which can be used to control lamps, relays or used for parallel interface with other units. There are two almost identical halves to the PIA which each have 8 input/output lines, each of which is independently programmable as an input or output as well as two control lines in each half of the devices. Internally, the device has

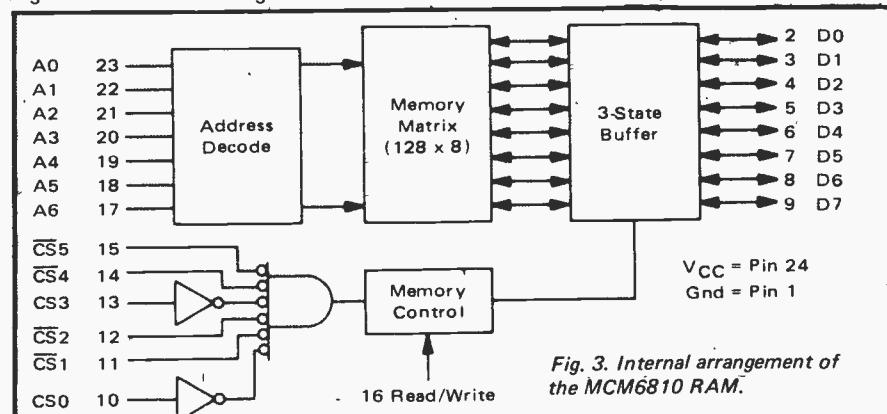


Fig. 3. Internal arrangement of the MCM6810 RAM.

microfile

served registers. If we consider section A of the PIA, Data Direction Register A (DDRA) controls the direction of data through each corresponding peripheral data line. If a particular bit of DDRA is set at '1', the corresponding line will be an output, if set at '0', it will be an input.

The Control Register A (CRA) is pretty complex in organization and so we won't go into it in depth here. It controls the operation of the control lines CA1 and CA2, as well as monitoring interrupts. Output Register A, when addressed, latches the information on the MPU data bus, and puts it on the peripheral data lines.

The PIA, as can be seen, is an extremely versatile device for parallel I/O. For serial I/O, the MC6850 Asynchronous Communications Interface Adaptor provides an even more impressive list of functions, including Parity, Overrun and Framing Error detection. Full details of both these devices can be found in the Motorola M6800 Systems Reference and Data Sheets book which many readers will already have.

Most microprocessor systems have their own I/O devices. For example Intel's 8080 has the 8255 Programmable Peripheral Interface and the 8251 Programmable Communication Interface.

We shall return to I/O devices in greater detail later.

NEWS

Intel are holding a 'Microcomputer Fair' at the Hilton Hotel, Park Lane on May 4th. There will be 4 simultaneous seminars and an exhibition of components and equipment. Over 20 papers will be read, some introductory and some on more advanced topics for experienced engineers. The fee of £15 covers entry, literature, morning coffee, a 3 course lunch at the Hilton, and afternoon tea. Intel have emphasized that numbers will be limited and all bookings will be dealt with in strict rotation.

Intel Corporation (UK) Ltd, Broadfield House, 4 Between Towns Road, Cowley, Oxford OX4 3NB.

MICRO-BASED EQUIPMENT

Several new products have been introduced this month which use microprocessors, including a new desktop calculator from Hewlett-Packard. The 9825 embodies special features for use in engineering and science as an integral part of a test/measurement system using the HP Interface Bus, or simply as a powerful stand-alone calculator. Important abilities of the


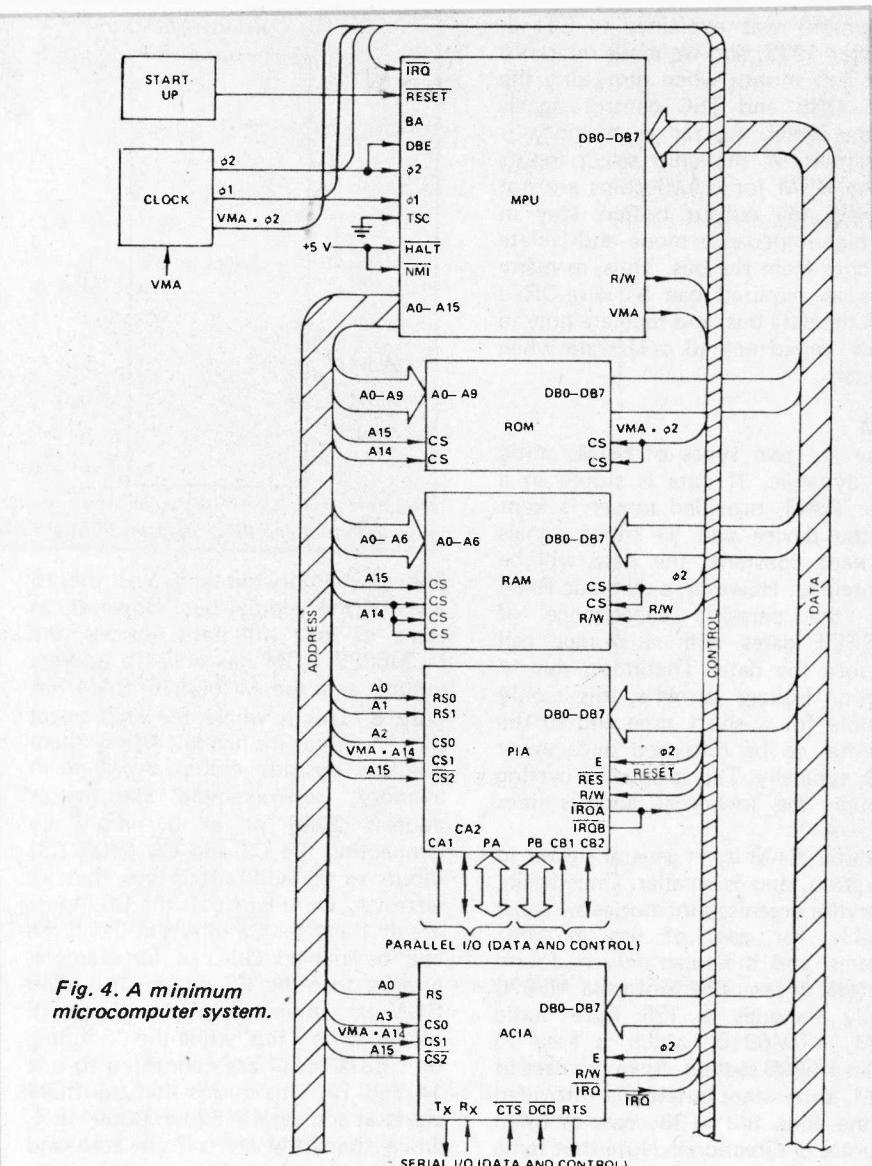


Fig. 4. A minimum microcomputer system.

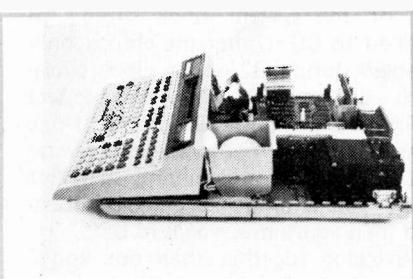

calculator include: vectored two-level priority interrupt, which gives a secondary benefit in the form of a 'live' keyboard which can be used while the calculator is running another program; direct memory access with input speeds up to 400,000 16-bit words per second; high-performance bi-directional tape drive; multi-dimensional arrays; automatic memory dump and load; internal calculation range of $\pm 10^{15.1}$ and optional plug-in ROMs.

The microprocessor at the heart of this machine is of HP design and manufacture and is a hybrid 3-chip


processor consisting of a 16-bit parallel binary processor chip, an I/O chip, and an extended math chip which gives floating point and hardware multiply capability. The 16 X 16 bit binary multiply time of 6 μ s is an indication of the speed of this processor. It's yours for only £3,955 plus VAT.

Hewlett-Packard Ltd., King Street Lane, Winnersh, Wokingham, Berks, RG11 5AR.

Fluke International have introduced a new microprocessor-controlled data logger with the ability to scan 60 channels in the mainframe and up to 1000 with extender options. The Summa II 2240A is fully programmable in range, function, skip, alarm limits, date/time, interval and fixed data, all from the front panel. Complete programs can be listed from memory — the program storage has a data retention of a minimum of five years.

Fluke International Corporation, Garnett Close, Watford, WD2 4TT.

TEMPERATURE METER

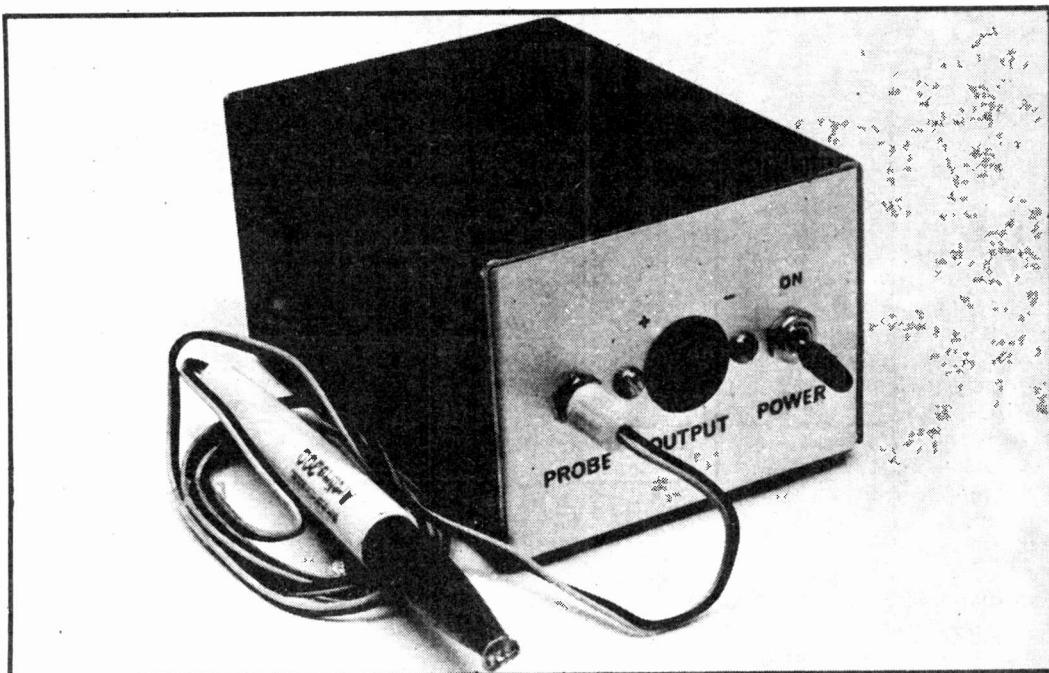

Converter connects to any analogue or digital meter.

OUR original design concept for this unit was as a complete instrument based on our ETI 533 digital display (October 1975 and Top Projects No.3) sensor — this generating a temperature-proportional voltage which in turn is supplied to a voltage-to-frequency converter. We planned to use a timebase to generate the necessary strobe and reset pulses. However the cost and complexity of this arrangement was such that we decided against it.

What finally emerged was a simple temperature-to-voltage converter which can be used in front of any analogue or digital meter. The converter provides an output of 10 mV/degree which can be either Celcius or Farenheit depending on calibration. If a dedicated digital readout is required we suggest our ETI 118 digital voltmeter (October 1975 and Top Projects No. 3).

CONSTRUCTION

Whilst a printed-circuit board is by no means essential, using one certainly makes construction easier and improves the appearance. The potentiometers as shown in our prototype are single turn presets which

are quite adequate if an analogue meter is to be used for the readout. However if a digital meter is to be used the extra accuracy of the readout would warrant ten-turn presets being used for RV1 and RV2, as setting accuracy is considerably improved.

The converter quite readily fits into a small aluminium case. Two nine volt batteries are used to power the unit and battery drain is low enough to ensure a life of many months.

A 3.5 mm jack is used to connect the sensor to the unit and the output to the meter is provided via an inexpensive two-pin speaker socket.

The probe is constructed by mounting the sensor-diode into the tip of a ball-point pen casing, or similar. The method may best be understood by reference to the drawing.


CALIBRATION

To calibrate the instrument, two accurately known temperatures are required. One may be water or oil at room temperature (ice water should not be used as there the temperature may vary several degrees between different points in the solution). The high temperature is best obtained by heating oil or water and allowing it to stabilise at around 80°C. A second smaller heat conductive container filled with water is then immersed in the larger container. This simple procedure prevents errors due to circulating currents in the larger volume of water. An accurate mercury-in-glass thermometer should be used to measure temperatures during the calibration procedure as detailed below.

SPECIFICATION

RANGE	0 to 100°C 32 to 212°F
OUTPUT	10 mV/degree
ACCURACY	± 1°
RESPONSE TIME	3 seconds

TEMPERATURE METER

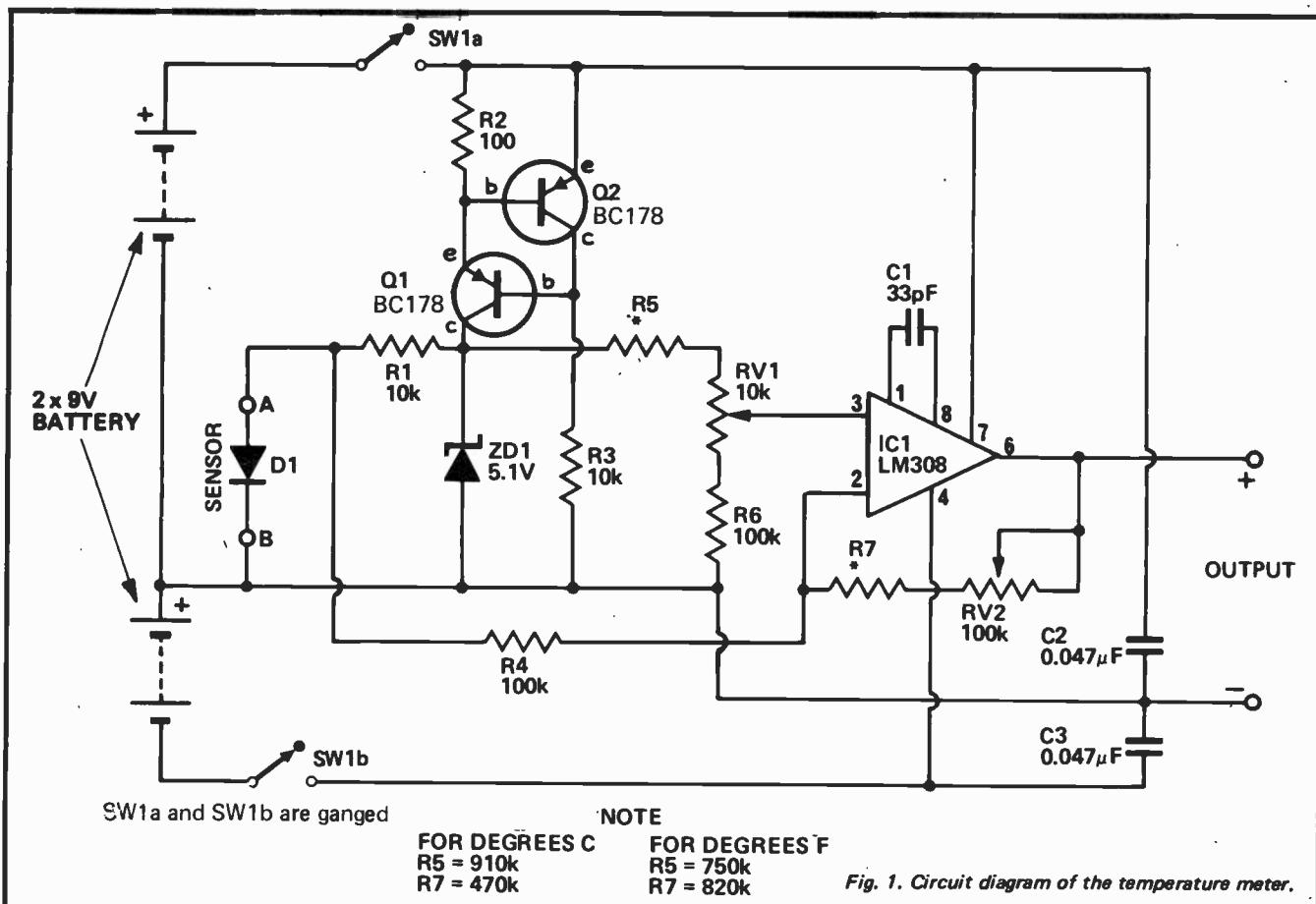

1. Place the sensor and thermometer into the cool solution, allow a little time for stabilisation, and then measure the voltage from the converter and the temperature. Record these two readings.

2. Place the sensor and thermometer into the hot solution and measure the voltage and temperature as before. The voltage change between the first and second readings should be equal to the temperature change times 10 millivolts.

3. If the voltage versus temperature is not as specified in step 2 adjust RV2 and repeat steps 1 and 2 until it is. Note that varying RV2 changes the

voltage at both the hot and the cold positions. It is the correct slope, or rate of change that we are after at the moment.

4. When the correct rate of change has been set as above place the sensor and thermometer into the cool solution and adjust RV1 to obtain a reading of 10 mV per degree. That is if the solution is at 25°C adjust RV1 to obtain a reading of 0.25 V.

Due to the spread of diode characteristics from one device to another the necessarily small adjustment range of RV1 and RV2 may not allow all diodes to be

calibrated with the resistor values specified. If this is found to be the case it may be necessary to change the value of R5, R6 or R7.

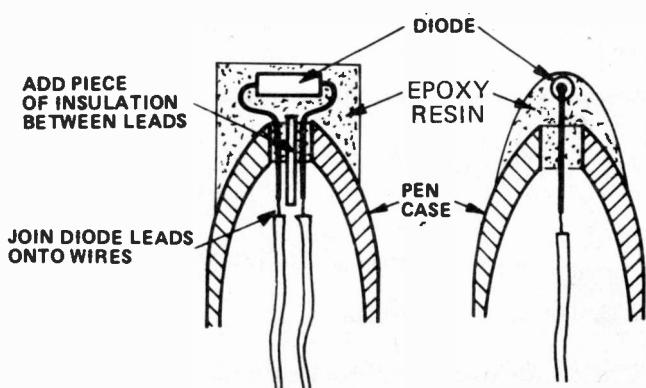


Fig. 2. This diagram shows how the sensor is mounted into a ball-point pen casing or similar.

PARTS LIST

R1,3	Resistor	10k	1/2W 5%
R2	"	100	1/2W 5%
R4,6	"	100k	1/2W 5%
R5,7	"	See Fig. 1 and test.	
RV1	Potentiometer	10k *	trim type
RV2	"	100k *	"
*for digital readout a multiturn trim potentiometer is recommended.			
C1	Capacitor	33pF ceramic	
C2,3	"	0.047μF polyester	
D1	Diode	1N914	
ZD2	Zener Diode	5.1V, 400mW	
Q1,2	Transistor	BC558, BC178	
IC1	Integrated Circuit	LM308	
Metal box			
Two 9V batteries (PP3 etc)			
Two pole toggle switch			
PC board ET1130			
3.5mm plug and socket			
Two pin plug and socket for output			

HOW IT WORKS — ETI 130.

A forward biased diode has a temperature coefficient of about $-2 \text{ mV}/^{\circ}\text{C}$. That is the normal voltage across a silicon diode of nominally 0.6 volts will decrease by two millivolts for every degree C increase in temperature. This change with temperature is sufficiently linear over the range of 0 to 100°C to use it as a temperature sensor.

What the ETI 130 circuit does is to amplify this voltage and to provide offset compensation for the normal 0.6 volt drop across the diode.

Transistors Q1 and Q2 provide a constant-current source of about 5 mA into the zener diode ZD1 such that a very stable five volt reference is obtained which is independent of the battery supply voltage. (V supply greater than 6 V.) The forward bias current through the sensor diode is about 0.5 mA as provided by R1. This current is low enough to prevent errors due to self heating of the sensor diode.

The voltage across the sensor diode is amplified by IC1 (a very high input-impedance operational amplifier) whose gain is fixed at the ratio of $(R7 + RV2)/R4$. The necessary offset is provided by RV1 which is adjusted to cancel the normal 0.6 volt drop across the diode. By selecting the correct values for R5 and R7 as shown on the circuit diagram the indication of temperature in degrees C or F may be obtained.

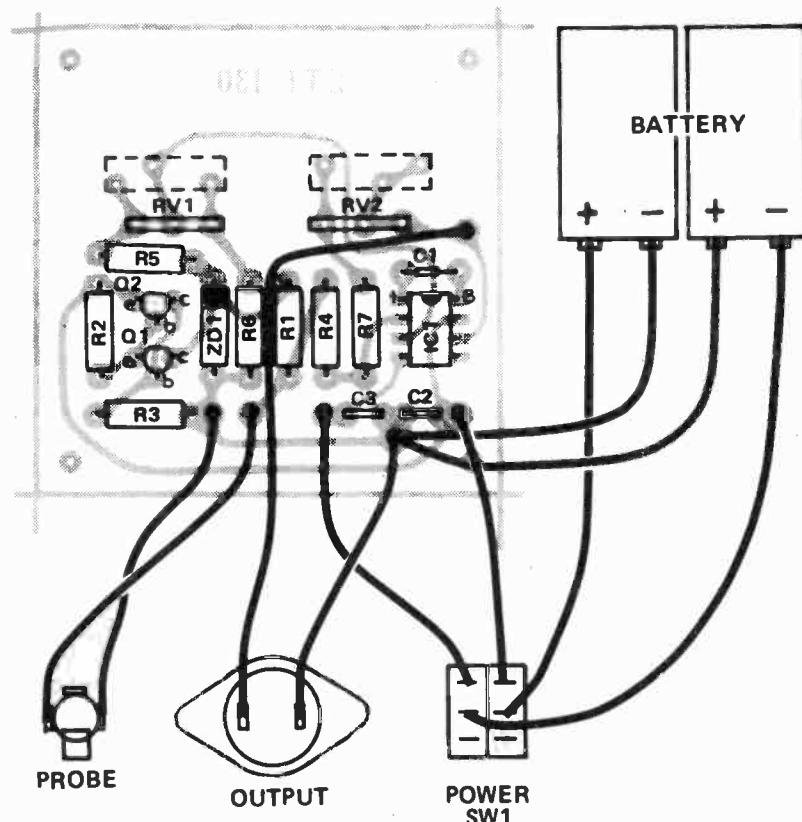


Fig. 3. Component overlay and interconnection diagram.

ETI 130


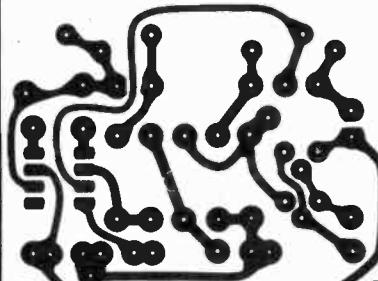


Fig. 4. Printed circuit pattern. Full size 63 x 63 mm.

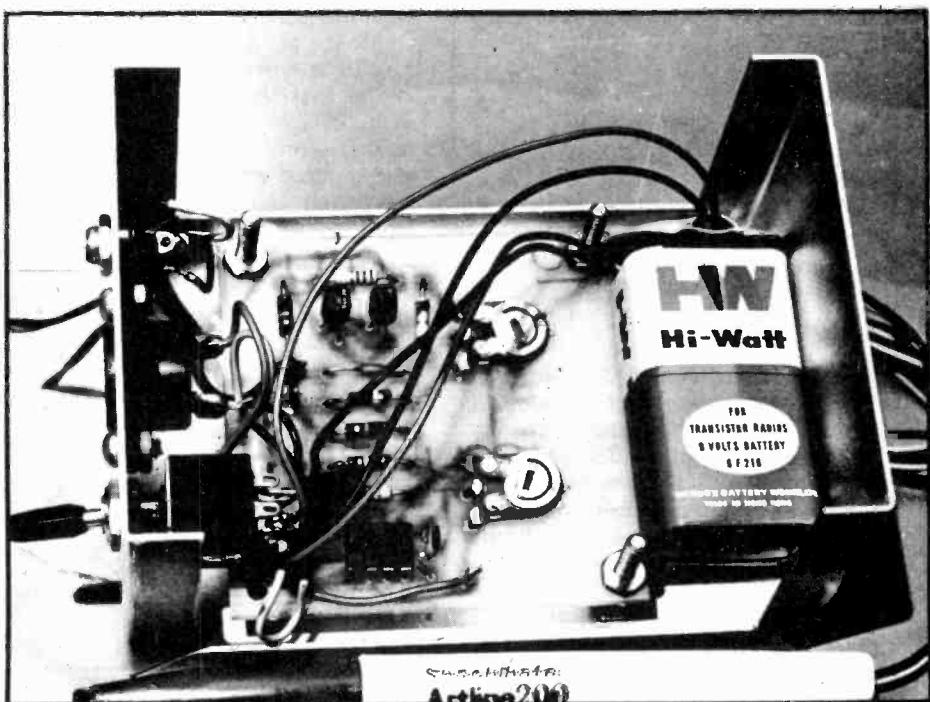


Internal view of the completed temperature converter. Note also the probe at front.

A SUBJECT CLOSE TO OUR HEARTS

NUCLEAR PACEMAKERS

ELECTRICAL IMPULSES are at the heart of us all. More specifically two masses of nerves — an upper one on the heart muscle called the sinoatrial, and a lower known as the atrio-ventricular — set up impulses which cause the muscular contraction. When the electrical conduction between them is impaired the heart beat is slowed down and, in extreme cases the patient may die. During the last few years artificial pacemakers have been developed to provide the electrical impulses needed and thus drive the heart at a normal rate. (Up to 250 μ W at about 5V are needed). The present units employ mercury cells with a life of about two years, and replacement involves an operation.

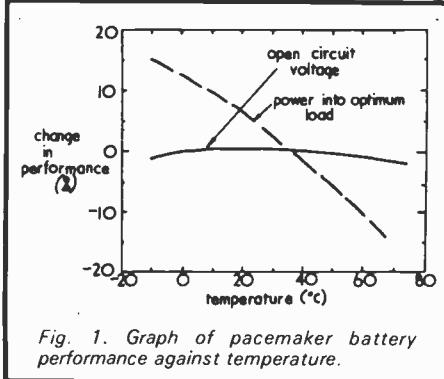

It would be better to reduce the number of these replacements by increasing the life of the unit.


ATOMIC FUEL

Dr J. Myatt at the AERE Harwell laboratories has in fact developed power sources for this purpose fuelled by plutonium 238, using its thermal energy and converting it to electric power by a thermoelectric module with a life expected to be of the order of ten years or more.

For safety the fuel has two stages of hermetic sealing. Elaborate care has been taken to ensure shock immunity.

Since the battery produces only about 0.25V while the pacer circuit needs 5V, a DC/DC converter

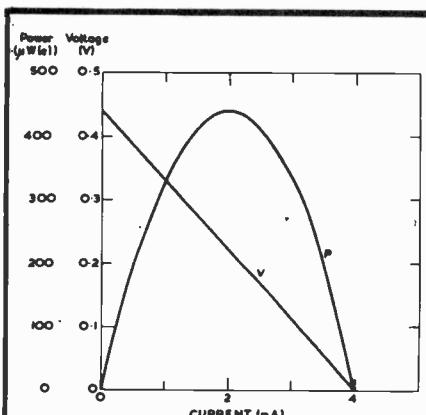
is used to amplify the voltage, using Zener diodes to stabilise output voltage at either 5.5V or 6.7V.



RISKS INVOLVED


This approach to powering the battery needs a very critical examination of the risks involved for both the patient and the public.

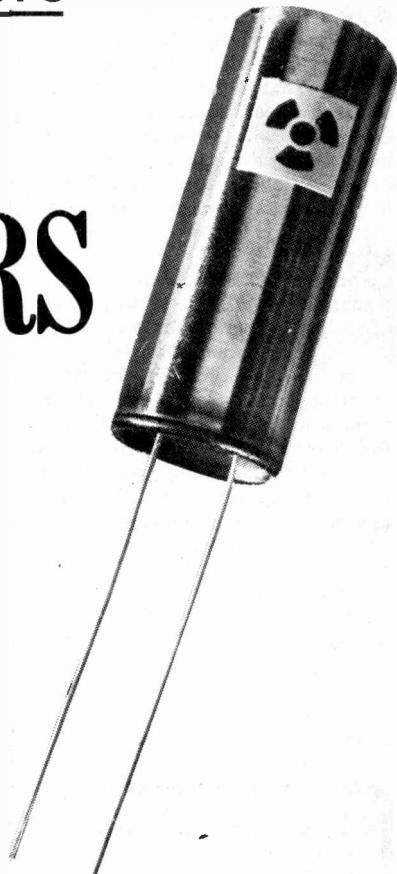Most of the emission from Pu238 is alpha particles, absorbed in the first few thousandths of an inch of the capsule. However, neutrons and gamma radiation are also emitted and must be kept at a low level. Using the isotope at a high level of purity helps with this.




but there are practical limits to the gamma shielding possible.

The organs most sensitive to radiation are the eyes, gonads, and bone-marrow, all of which are a good distance from the source centre and should therefore receive only a very low dose. Whether this dose is acceptable will depend on the views of the health authorities. Since the intensity follows the inverse square law, radiation danger to the public is considered negligible, even for the patient's spouse. The battery is able to withstand shock, accidental mechanical damage, and even cremation!

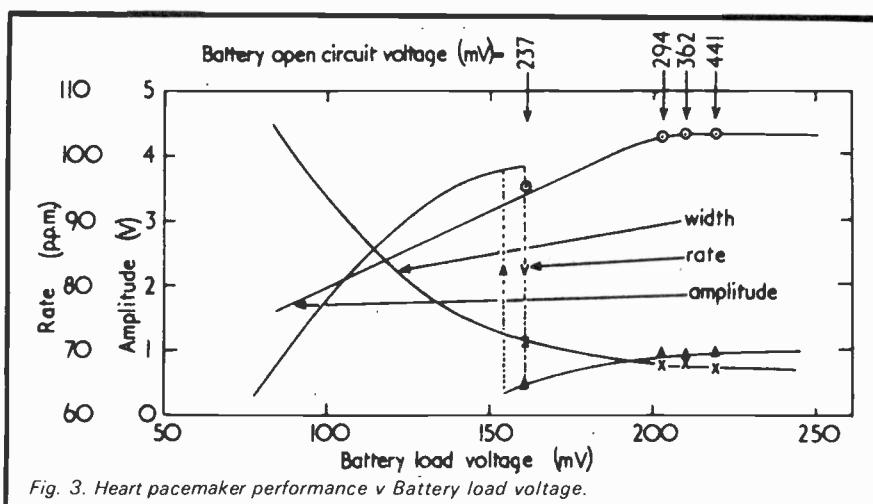

Build it yourself!

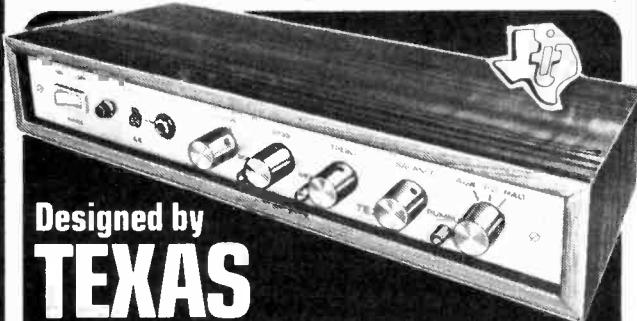

Designed by
TEXAS

Featured by PRACTICAL WIRELESS
SOLE U.K. DISTRIBUTORS - HENRY'S

Build the Texan stereo amplifier, then you can be doubly proud! For a start, you'll own a superb home entertainment unit. And have had all the pleasure of doing it yourself, with the Henry's kit.

Look at the Texan specification

Incorporating fully integrated stereo preamp and power amp, with 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fibe PCB; Gardeners low-field low-line mains transformer; all facilities and controls. Slim design, chassis 14½" x 6" x 2" overall. 20 watts per channel RMS, less than 0.1% distortion at 1 kHz.

THE NATURAL FOLLOW-ON - THE TEXAN FM TUNER KIT!

KIT PRICE
£25.95
Inc. VAT +
50p p&p.

Built and tested £30.95 inc. VAT + 50p p&p.

Build the matching Texan stereo tuner! Features advanced varicap tuning, Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre PCB to the cabinet itself. Excellent spec: 2.5 uV aerial sensitivity, 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.

KIT PRICE
£35.00
Inc. VAT + £1 p&p.

Built and tested
£45.00 inc. VAT
+ £1.00 p&p.

VIDEO SPORT

... all the electronic excitement
you could wish for!


★ OVER
10,000
ALREADY SOLD
★ IDEAL
GIFT

An up-to-the-minute game. Plugs into your own TV aerial socket. Switch on. And you're away! Choose your game - football, tennis or hole-in-the-wall. Absolutely safe. For you. Your children. And your TV. Mains powered.

List Price £42.50 inc. VAT +
50p p&p.

HENRY'S PRICE-ONLY £29.50

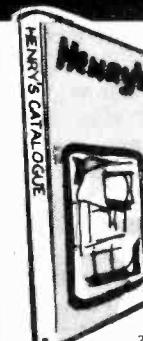WHATEVER YOU DO, DON'T FORGET
YOUR LATEST **HENRY'S CATALOGUE!**



For this new edition, we have made hundreds of changes and additions. It has over 200 pages, containing virtually everything for amateurs and professionals. And you'll have no bother at all finding everything you want, because there's a complete alphabetical index as well as a section index. Together, they put you right on course for the items you need. From Sinclair projects to educational kits. Oscilloscopes to panel meters. Coils to capacitors. Transistors to valves. Loudspeakers to microphones - all at competitive prices. Over 200 pages of vital statistics - just for you! So send now for your copy.

**ONLY
50p**

20p Carr./pack

FREE to Educational Establishments when ordered on official headed notepaper.

- Over 5000 items inside!
- Every copy contains a free 50p voucher.
- Many new items.
- Over 200 pages.

HENRY'S

404/6 EDGWARE ROAD, LONDON W2 01-402 8381

LOWER SALES FLOOR, 231 TOTTENHAM CT. RD., LONDON W1 01-636 6681

94/96 UPPER PARLIAMENT STREET, NOTTINGHAM. 0602-40403

NEW MIDLANDS STORE All mail to Henry's Radio, 303 Edgware Road, London W2

NOW METAC introduce SUPER 2 YEARS GUARANTEE COVER

QUARTZ CRYSTAL

ELECTRONIC WATCH

The very latest in DIGITAL Time keeping The ultimate in accuracy



8 SEPARATE FUNCTIONS

1 12:00

2 12:30

3 :36

4 TU

5 TU 26

£21.95
+ £1.80 VAT

18ct GOLD PLATED ADJUSTABLE BRACELET

6 MORNING A.M. INDICATOR
7 AFTERNOON P.M. INDICATOR
8 AUTOMATIC FADE OUT

This new generation of advanced **DIGITAL QUARTZ WATCHES** has now been perfected to enable them to be made available to everyone. Science and space technology has produced integrated circuits containing thousands of transistors in a single package, there are no moving parts to oil or give mechanical trouble. You have our **TWO YEAR GUARANTEE** which enables you to wear your watch with CONFIDENCE.

LIQUID CRYSTAL CONTINUOUS DISPLAY UNIQUE BACK LIGHT for night time illumination

GREAT LCD VALUE

This impressive model incorporates the famous OPTEL display this ensuring maximum reliability and long life. It really is good value (just look in the jewellers stores at similar models). Metac believes that finally the general public will find our continuous display watches preferable, it runs for more than a year on a miniature battery and with the backlight facility the easy to read display is visible all the time. And with METAC you can be assured of consistent after sales service for the life of your super accurate quartz watch.



6 FUNCTIONS

1 12:00

2 12:30

3 :36

4 :16

5 2:36

PM INDICATOR

£38.84

+ £3.11 VAT
Gold plated
Bracelet

£36.40

+ £2.91 VAT
Stainless Steel
Bracelet

REMEMBER: with every WATCH you get METAC SUPER COVER

★ DOUBLE GUARANTEE 2 FULL YEARS

★ **REFUND** in full all money paid immediately upon request for period of **21 DAYS** if not entirely satisfied with the product.

★ **REPLACE** or repair at our discretion any watch developing a fault for a period of **TWO YEARS** from date of purchase.

★ **FREE** calibration check at end of 1st year; 2nd year and 3rd year.

★ **FREE** advising service on all technical aspects of Electronic Timing to wearers of METAC watches.

Mail order customers please add 58 pence per order to cover postage and insurance.

METAC INTERNATIONAL

CROSS LANE, BRAUNSTON, NORTHANTS
Tel. Rugby 890672

Please supply the following . . .

Name

Address


I enclose cheque

postal order money order

I wish to pay by Barclaycard/Access and my number is

Signature

Money refunded in full if not satisfied

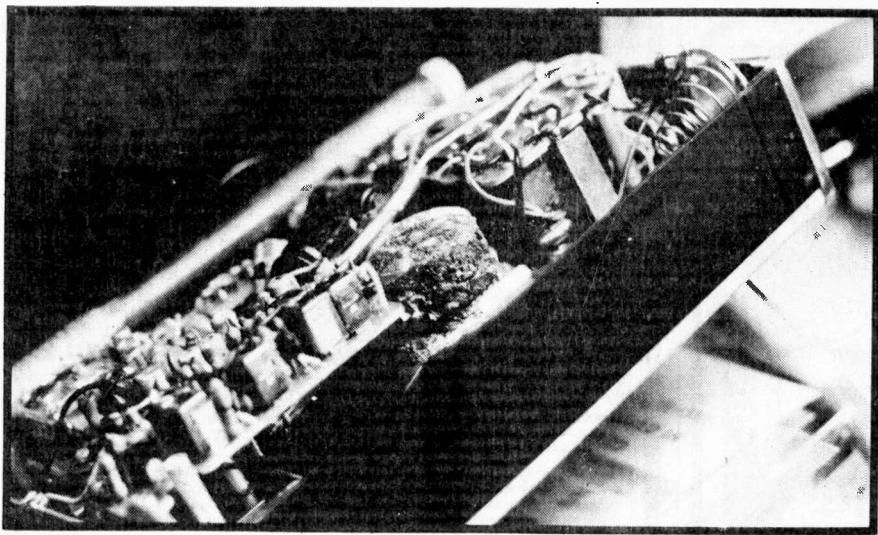

ASSAULT BY BATTERY

MOST PEOPLE are aware of what happens when they leave exhausted batteries in a hand-torch: the chemical content of the cells eats its way through the casing and starts to attack the body of the torch itself.

If left for a prolonged period, the damage and corrosion becomes so extensive that it is impossible to which consequently has to be scrapped.

The situation becomes much worse and considerably more expensive when battery corrosion affects electronic equipment. Transistorised tape recorders and radios are the most common victims, having been set aside and forgotten for a while, during which time corrosion can cause considerable damage.

The owner of apparatus so damaged is usually caught out completely, and quickly takes it to a servicing organisation in the hope that things can be rectified easily. Unfortunately, the devastation caused by corrosion can be so severe that some equipment has to be written off. This certainly applies to small transistor radios, where the economics of repair would be out of proportion to the value of the apparatus.

In the case of more expensive equipment, a rigorous approach can save it on many occasions.

The battery compartment will have suffered most; if it is a separate item it should be replaced in its entirety. Fortunately this compartment often serves to contain the bulk of the corrosion, and provided the caustic fluid has not escaped into the remainder of the equipment, there is a good chance that the repair will be 100 per cent effective.

If fluid has penetrated into the remainder of the equipment the situation will inevitably be much more

serious. Printed panels, switches, coils and transformers are particularly vulnerable, and a preliminary examination should be carried out to see to what extent these components have been affected. Note that the fluid can penetrate underneath larger components and seep through, causing damage at a later date. It is essential that all traces of corrosive material be removed, even if to do so involves the removal of components from a printed panel.

If a panel has been badly saturated, but not extensively eaten away by corrosive fluid, it is best to remove all inductive components and switches, then wash it off thoroughly in fairly hot water. A small toothbrush is useful for scrubbing, and a hair-dryer can be used for drying off afterwards. Healthy components will survive this treatment unscathed; sick looking ones may well be damaged and should be replaced.

Switches affected should always be replaced, and this also applies to RF and IF coils, ferrite rod windings and transformers, all of which may cause trouble at a later date even though they may appear to have survived superficially.

Repairs such as these usually take up a large amount of time, and often some expensive components, so the economics of any one repair should be assessed early on, so that work is not commenced precipitately on a job which will ultimately be uneconomic. Fortunately, assessment is not too difficult when one bears in mind the foregoing points. It is relatively easy for an experienced engineer to say that possibly three hours work will be required, plus a switch bank, battery box, several IF transformers and a loudspeaker. A quick mental totting-up will yield a figure which can

then be compared with the value of the repaired apparatus.

Do remember though that this sort of repair can never be guaranteed. It is possible for 'green spot' corrosion to occur in coils after a period of time, even if they appear to have escaped initial damage, and a customer should be made aware of this.

Spares availability plays a major part in the success or otherwise of a repair. This is true to the extent that a relatively cheap transistor radio of obscure origin, may need to be written off if there is any possibility of damage beyond the area of the battery compartment.

Standard battery compartments, of Japanese origin, are now easily available and can be used as standard replacements.

Portable tape recorders, when affected by battery corrosion, can present further problems in addition to those mentioned above. The mechanical side of the machine can be adversely affected, and in particular castings can be eaten away. The effects on ball-races, flywheels, and motors (let alone rubber drive belts!) must be seen to be believed. In any event, a complete stripping down operation is often the only sure approach, a process which is obviously time-consuming and expensive.

If ever the point should be made that prevention is better than cure, it applies in the case of damage by battery corrosion. Whenever equipment is being put away for a period, the batteries should be removed as a precaution. If it is obvious that the batteries are flat, they should be removed *straight away*. Do not wait until you have purchased new ones; you could slip up and break your leg on the way home, and by the time you are discharged from hospital, your pocket calculator could be a write-off!


CHROMASONIC electronics

Dept. 7, 56, Fortis Green Road,
Muswell Hill, London, N10 3HN.
telephone: 01-883 3705

C-MOS

	1-24	25-99	100up
CD4000AE	19p	17p	14p
CD4001AE	19p	17p	14p
CD4002AE	19p	17p	14p
CD4004AE	£1.59	£1.33	£1.06
CD4007AE	23p	19p	15p
CD4008AE	£1.75	£1.46	£1.17
CD4009AE	Use	CD4049*	
CD4010AE	Use	CD4050*	
CD4011AE	19p	17p	14p
CD4012AE	19p	17p	14p
CD4014AE	59p	50p	46p
CD4014AE	£1.75	£1.46	£1.17
CD4015AE	£1.75	£1.46	£1.17
CD4016AE	55p	48p	44p
CD4017AE	£1.29	£1.07	93p
CD4018AE	£1.89	£1.56	£1.25
CD4019AE	80p	66p	53p
CD4020AE	£1.97	£1.64	£1.31
CD4021AE	£1.75	£1.46	£1.17
CD4023AE	19p	17p	14p
CD4023AE	£1.83	£1.53	£1.27
CD4024AE	£1.26	£1.05	84p
CD4025AE	19p	17p	14p
CD4026AE	£2.79	£2.33	£1.86
CD4027AE	98p	82p	65p
CD4028AE	£1.53	£1.28	£1.02
CD4029AE	£1.89	£1.56	£1.15
CD4030AE	71p	59p	47p
CD4033AE	£1.75	£1.46	£1.17
CD4040AE	£2.01	£1.69	£1.34
CD4043AE	£1.49	£1.24	99p
CD4046AE	£2.15	£1.79	£1.44
CD4049AE	69p	58p	46p
CD4050AE	69p	58p	46p
CD4051AE	£2.78	£2.32	£1.85
CD4057AE	£2.78	£2.32	£1.85
CD4056AE	£2.12	£1.76	£1.41
CD4060AE	£2.39	£1.99	£1.55
CD4066AE	£1.13	94p	75p
CD4068AE	26p	24p	19p
CD4069AE	28p	24p	19p
CD4070AE	28p	24p	19p
CD4071AE	28p	24p	19p
CD4077AE	71p	59p	47p
CD4081AE	28p	24p	19p
CD4087AE	28p	24p	19p
CD4085AE	£1.78	£1.06	85p
CD4086AE	£1.28	£1.06	85p
CD4093AE	£1.56	£1.20	£1.04
CD4099AE	£2.95	£2.46	£1.96
CD4511AE	£2.36	£1.79	£1.44
CD4528AE	£1.30	£1.08	87p

3½ DECADE DVM I.C.

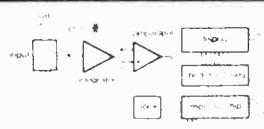

This state-of-the-art MOS LSI chip contains all the logic necessary for a 3½ decade, dual slope integrating, automatic polarity detecting DVM. Supplied with free data and circuit booklet.

OUR PRICE ONLY £6.59 *


(Data and Circuit Booklets alone 20p.)

The AY-5-1224 tick-tock

Another marvel from G.I. A 16 pin 17-24 hr. Clock I.C. with 25 pin capability and low external parts count. Supplied with manufacturers detailed leaflet £3.95p inc. VAT. (Leaflet alone 20p. Full Kit (excluding case) available towards end of 1975. Phone C' for details.)


MULLARD MODULES

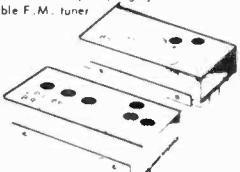Still make the simplest, highly reliable F.M. tuner



LP1186 Varactor front end £8.60
LP1185 I.F. Strip £6.95
LP1400 Multiplex decoder £9.02

I.C. SOCKETS

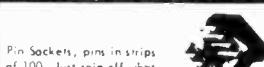

Pin Sockets, pins in strips

of 100. Just snap off what you need. 65p per strip.

*

Dual in line.

8 pin 13p. 24 pin 20p. 105

14 pin 15p. 28 pin 30p. 8 pin 31p

16 pin 15p. 36 pin 39 p. 10 pin 35p

FREE CIRCUITS

Our 8 Page A4 Audio I.C. Booklet is supplied FREE with purchases of Linear I.C.'s worth £1. or more. (35p. if sol. alone) Contains circuits and pin connections

15 Amplifiers 250 mW to 20 watts

5 Audio Pre-Amplifiers

1 Tape Pre-Amplifier

1 Power Driver

1 Instrument Amplifier (Bifilar)

1 General Purpose Mini Amplifier

1 D.C. Controlled Gain Control

1 Micro-mini radio (2 1/2 C's)

PHOTO-DARLINGTON



Vdeo 25v 2N5777

Vbco 25v

Vebo 8v

11 250 mA

Pd 2500W

Hfe 2500

£35p.

LINE-O-LIGHT



NEW LED Linear Cursors

each device contains 10 light emitting diodes in a 20 pin dual-in-line package. Ideal for solid state analogue meters or dials.

Type 101 RED £2.26. Complete with leadlet.

74 TTL

24 25-99 100

14p 12p 10p

14p 12p 10p

14p 12p 10p


16p 13p 11p

16


Now we bring you...

TOP PROJECTS No.3

WHICH INCLUDES ...

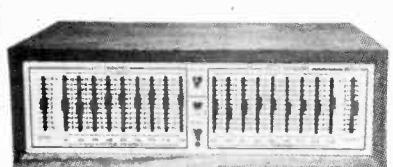

GRAPHIC EQUALISER

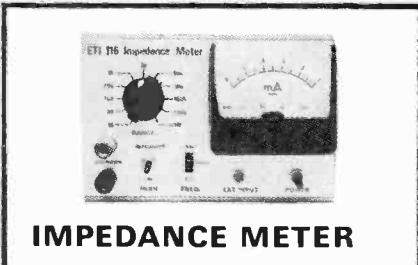

IMPEDANCE METER




BIKE SPEEDO




RADAR
INTRUDER ALARM



INTERNATIONAL 25

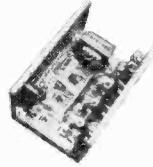

COLOUR ORGAN

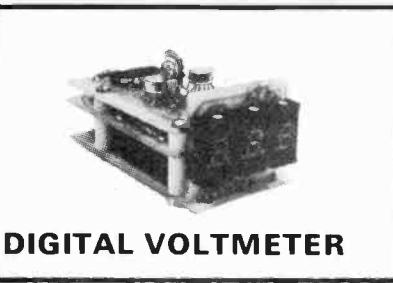

DIGITAL VOLTMETER




STEREO FM TUNER




LINE AMPLIFIER




LIGHT DIMMER

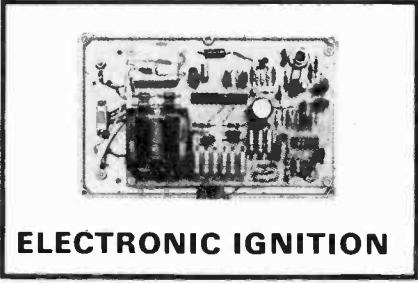


ELECTRONIC IGNITION

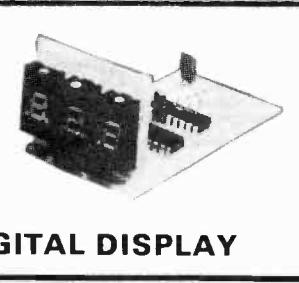

DIGITAL DISPLAY

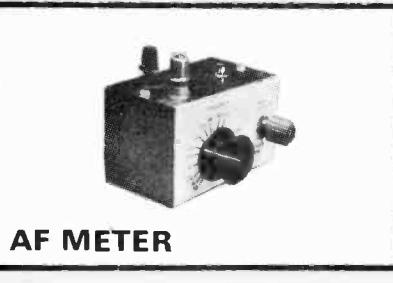

AF METER

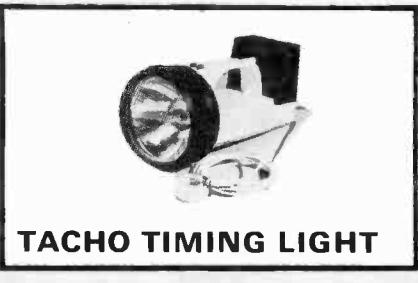

TACHO TIMING LIGHT

PLUS MANY MORE

Available from your newsagents or direct from ETI. Please send £1.20 to cover cost plus postage and packing. Make cheques and P.O.'s payable to ETI Magazine and please write Top Projects No. 3 and your address on the back of your cheque.

TOP PROJECTS No. 3
ETI Magazine,
36 Ebury Street,
London SW1W 0LW

ON SALE AT YOUR NEWSAGENTS MID-MARCH: £1.00

CMOS

We will continue our discussion of CMOS this month by considering several diverse topics briefly including shift registers, memories and the phase locked loop.


SHIFT REGISTERS

WE HAVE already seen how flip-flops may be cascaded to form shift registers and, as you might guess, these are available already connected in a single IC. As usual we will start with some pin-out diagrams.

Referring to fig. 1 we start with the 4015A, a dual four stage serial input parallel output (SIPO) version. The two parts "A" and "B" are independent and each consists of four D-type flip-flops with outputs Q1-Q4 and data is transferred from each one to the next and from the data inputs to the first on the rising edge of the clock pulse. A high input to the reset clears all the outputs to zero.

The 4006A is an 18 stage device with the registers so arranged that 4, 5, 8, 9, 10, 12, 13, 14, 16, 17 and 18 stage registers may be produced. These are serial-in-serial-out (SISO) devices. It should be noted that the clock input is common to all the stages so that although two separate five stage registers could be produced they would have to share the same clock.

Finally in fig. 1 we have the 4014A and 4021A which are both eight bit registers with the same pin connections. The 4014A works as follows: On the rising edge of the clock pulse, the data is all shifted down and a new datum accepted from the serial input if the parallel/serial input is low. If instead it is high, no shift occurs and instead each stage of the register adopts the state present at the parallel inputs. The 4021A is similar in almost all respects except that when the Parallel/serial is taken high the stages are jammed asynchronously (i.e. it does not wait for the clock transition like the 4014A). We mentioned earlier that the 4042A quad D latch is often used for temporary storage but for many

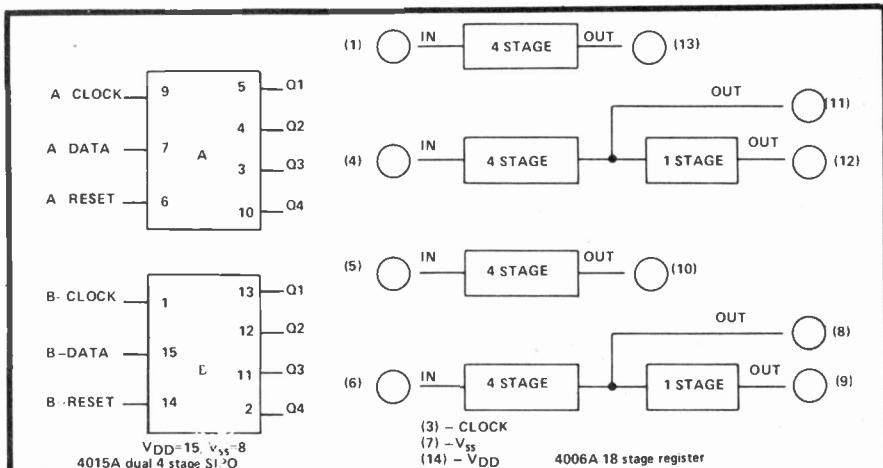

applications a shift register is superior, giving options of serial or parallel operation. As far as eight bit data manipulation is concerned, the ultimate shift register must surely be the 4034A whose pinout is given in fig. 2. It is described as a bi-directional bus register because the two data lines "A" and "B" are interchangeable in that if the A/B input is high the A lines are inputs and the B lines are outputs, whereas when A/B is held low the reverse applies. When the parallel/serial input is high then data is accepted from the parallel inputs (on the positive clock transition when Asynch / synch is low, asynchronously otherwise) whereas when parallel/serial is low data is accepted from the serial input and shifting is performed on the positive clock transition. The only other feature is the A-enable input which enables the A lines when it is high thus allowing several registers to feed a common bus. Designers of large digital processing systems will find many applications of this device.

Applications of shift registers in data storage and conversion are not really very interesting out of context and so we will look briefly at counters. The connection of shift registers (under the guise of a sequence of flip-flops), to form Johnson counters, has already been

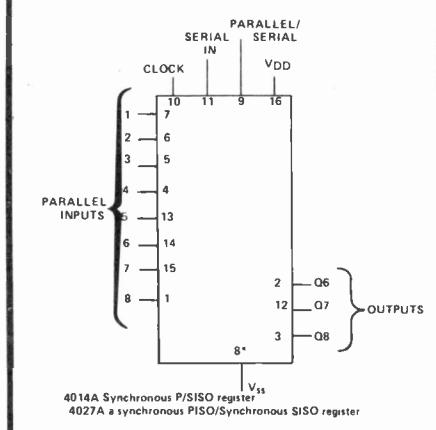


Fig. 1. Pinouts of four small shift registers.

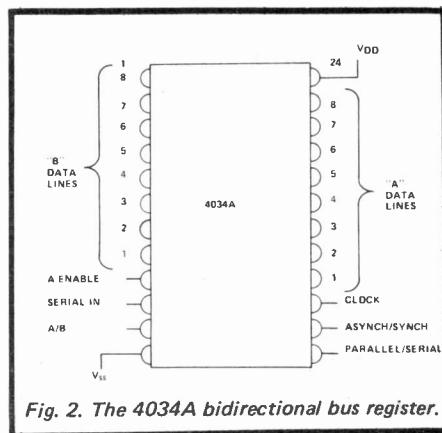


Fig. 2. The 4034A bidirectional bus register.

CMOS

considered but it is worth noting that in the same way as we produced digital to analogue converters from counters we can also produce waveform synthesisers from Johnson counters (see fig. 3(a)). The calculation of the required value of each register is rather tedious because each is on for half a complete cycle. Nevertheless, an eight stage register gives sixteen separate values out but not all of these are independent. On occasions this method is superior to the single bit approach. The circuit in fig. 3(b) is not complete because the single bit must be inserted to start with. If the application will tolerate switches in the starting sequence it is a trivial design exercise but if complete auto-starting is required it becomes quite interesting.

These small registers we have been considering are by no means the top end of the range. Fig. 4 gives the pinouts for some high capacity registers. The 4031A is a single sixty-four stage shift register, the only addition being a Q output and mode and recirculation connections. When the mode control is low the recirculation input is inoperative and data accepted from the data input. When mode is high, however, data is accepted from the recirculation input instead. Thus if the Q output is connected to the recirculation input a register is formed with a control input which will either recirculate its contents continually or accept new data, depending on the control signal. You might well wonder why the recirculation input is not internally connected to the Q output. This is not done because it would generally reduce the versatility of the device and, more particularly, would prevent the formation of multi-chip recirculating registers like the one shown in fig. 5(a). The 4013A is positive edge triggered and it has also got a delayed clock output which, as the name implies is a replica of the clock signal delayed by several hundred nano-seconds so that the cascading method shown in fig. 5(b) may be used. The addition of the flip-flop if recirculation is required should be noted as without it this method will not work. The cascading method in Fig. 5(a) must be used for highest speed operation although it requires higher clock drive.

Having said so much about the

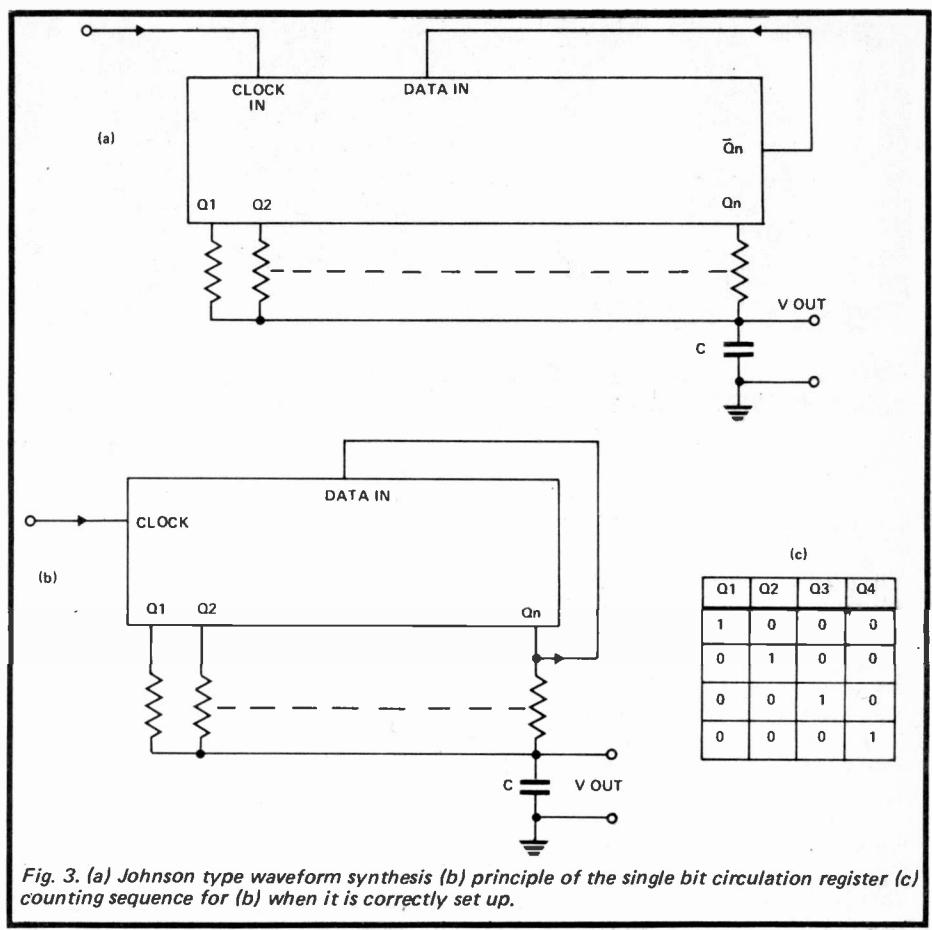


Fig. 3. (a) Johnson type waveform synthesis (b) principle of the single bit circulation register (c) counting sequence for (b) when it is correctly set up.

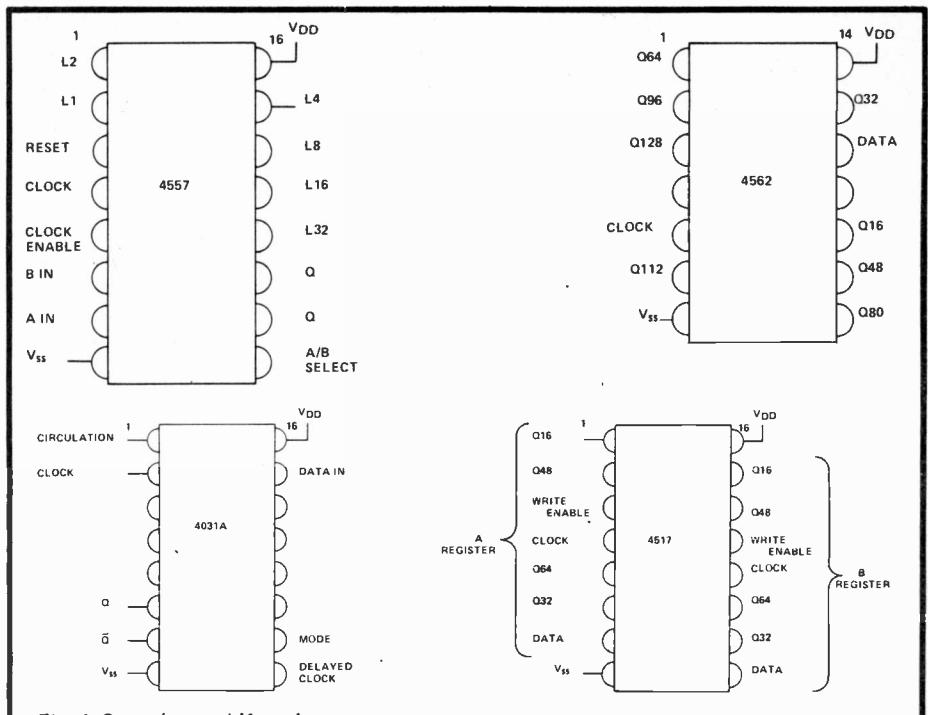


Fig. 4. Some larger shift registers.

4031A there is less to say about the next three devices. The 4517 is dual sixty-four bit register, the two devices being distinguished in the pin diagram by the suffices 'A' and 'B'. During normal operation the device is positively edge triggered, data is entered at the data pin and

outputs are available at Q16, Q32, Q48 and Q64. This is with the write enable low. When it is high however data is entered at the data, Q16, Q32 and Q48 pins (the Q16 pin acting as a data input to stage 17 etc) thus allowing complete filling of the device in sixteen clock periods.

The 4562 is a straight forward one hundred and twenty eight stage positive edge triggered device with no additions except outputs every sixteen stages throughout. The 4557 is an altogether more interesting device. Basically, the length of the shift register between the A and B inputs and the Q and Q outputs is equal to the sum of the L inputs which are high plus one. Thus if L32 and L4 are the only ones held high the shift register will be of length $32 + 4 + 1 = 37$. The reset input clears all stages to zero when it is taken high. The A/B select input is used to decide whether the A or B inputs will be used as the data source, when it is low B is used, when it is high A is chosen instead. It should be clear from our previous discussion how a recirculating register could be formed. As for the clocking, when the clock enable is low the device behaves as a conventional positive edge triggered register, but if negative edge operation is required this can be achieved by holding the clock at logical one when a falling edge at the enable input will operate the device. Using this device as a Johnson counter would lead to an interesting binary programmable symmetric frequency divider. Before we leave the subject of shift registers we will point out that all those we have considered are static devices which means that they maintain their state even if they are not clocked for some time. A two hundred stage dynamic shift register is available but there is not really time to describe it here. Its type number is 4062A.

MEMORIES

Of course, a shift register can be used as a memory. The disadvantage is that it is a serial access device which means that a lot of unwanted information must often be passed by while the piece we require is arriving. Random access memories (RAMS) avoid this problem because access is by a set of address lines, the signal on which determines which bit of the memory is to be written to or read from. We intend here just to give brief details of one available device (see fig. 6). The 4061A two hundred and fifty six bit static RAM has been chosen as our example because it is simple enough for a brief description of its features to be given easily. A0 to A7 are the eight binary address lines necessary to specify any one bit and these should only be changed while the chip enable input is high. Only when the chip enable

has returned to zero can read and write operations be performed, reading when "read/write" is low, writing otherwise. The buffering of the outputs is such that the data in line may be tied to either data out or data out if desired. It should also be noted that the V_{ss} and V_{dd} pins are unconventionally positioned so that the devices are compatible with other MOS memories. Of course, there are a few other pieces of timing protocol to be observed. For example, the chip enable signal should not go low too soon after an address change but we will not go into these here as anyone who uses this device in a system will doubtless be obtaining data sheets for other devices anyway.

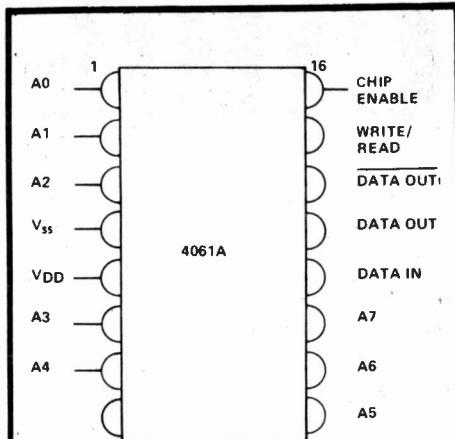


Fig. 6. The 4061A static 256 bit random access memory (RAM).

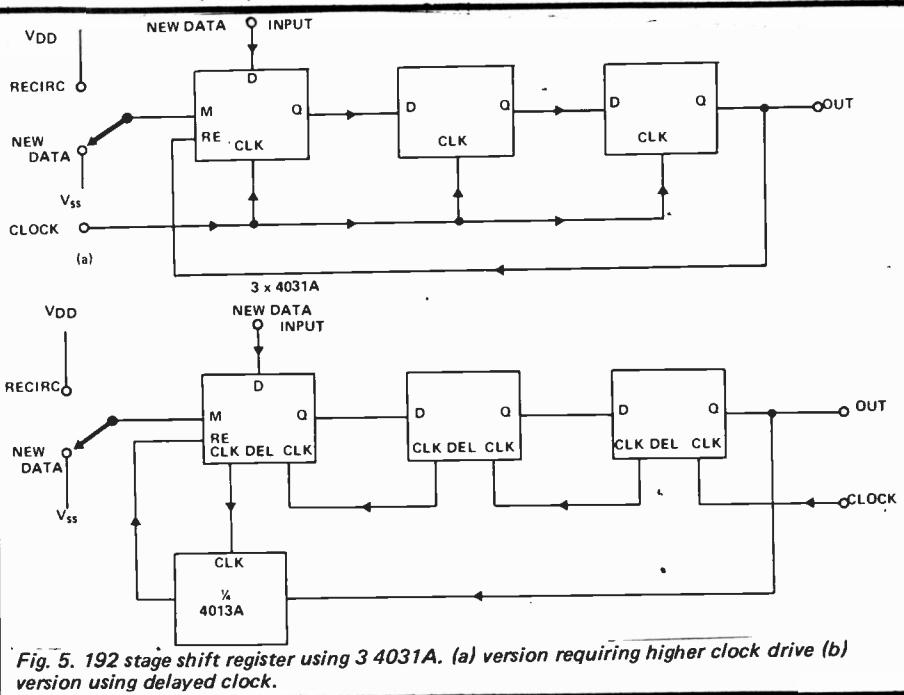


Fig. 5. 192 stage shift register using 3 4031A. (a) version requiring higher clock drive (b) version using delayed clock.

THE 4046A PHASE LOCKED LOOP

The possibilities of combining linear and digital circuitry on the same chip has made the fabrication of the 4046A phase locked loop possible in CMOS. As usual we will discuss this device with reference to its pin diagram which is given in fig. 7.

A zener diode of 5.2V is provided at pin 15 for supply regulation if required although the circuit will operate at any value of V_{dd} between five and fifteen volts. The chip contains two phase comparators with outputs at pins 2 and 13. The first of these is an exclusive OR network which requires a 1:1 mark space ratio at the input to work effectively, will lock onto harmonics of the input frequency but makes up for a lot by having good noise rejection and it also leaves the

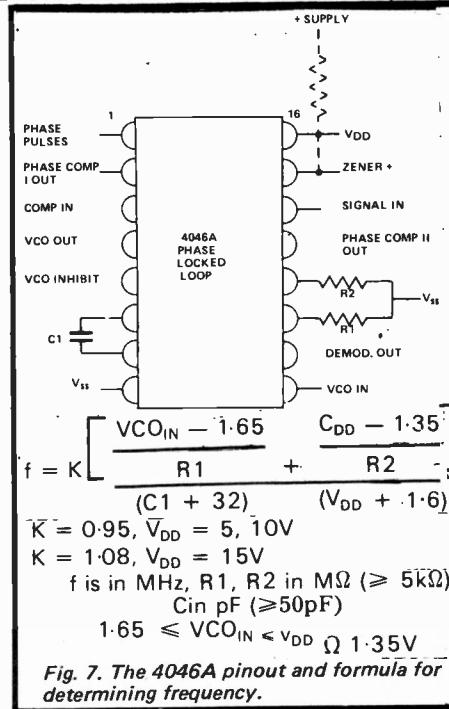


Fig. 7. The 4046A pinout and formula for determining frequency.

CMOS

voltage controlled oscillator running in mid-range with no input connected. In contrast to this, phase comparator 2 can handle pulses and leaves the oscillator running at minimum frequency. The output from one of these phase comparators is generally connected via a low pass filter to the input of the V.C.O. In passing we will mention that when the first phase comparator is used, the capture range (that is the range of frequencies that will pull the loop into lock) can be made less than the lock range (the range over which the loop will follow an already locked input) by using an appropriate low pass filter. In the case of comparator 2 however, the lock and capture ranges are identical.

The frequency of the V.C.O. for given R₁, R₂ and C₁ is given in fig. 7. The highest frequency attainable is over 1MHz but the supply voltage may need to be a full fifteen volts to achieve this with the cheapest plastic encapsulated devices. For experimenting purposes this description of the oscillator is probably sufficient but if it is required to design for specific frequency ranges, the R.C.A. data sheet on the device gives graphs which are easier to use than the somewhat cumbersome formula. Basically the smaller R₂ is, the smaller the range the VCO may be swept over. If pin 12 is left open, the frequency can be swept from a negligible value to a megahertz or over.

If the signal in is within CMOS logic levels ("0" $\leq 30\% V_{DD}$, "1" $\geq 70\% V_{DD}$) then it may be directly coupled to the signal input but if capacitive coupling is used signals at least as low as 1.5V p-p will be accepted. The inhibit input saves power by disenabling the VCO when it is taken high and the "DEMOD OUT" terminal provides a buffered copy of the "VCO IN" signal for use as an output in demodulation set-ups. If this is used a resistor of 10k Ω — 1M Ω should be connected between it and V_{SS}. Perhaps we can save time by giving one or two examples of the use of the 4046A rather than talking about it further. Fig. 8 shows an F.M. demodulator designed to operate with a centre frequency of 10kHz. It uses phase comparator 1 for good noise rejection and the formula for the capture range shows that the values used give $\pm 400\text{Hz}$. As R₂ is infinite the circuit will track

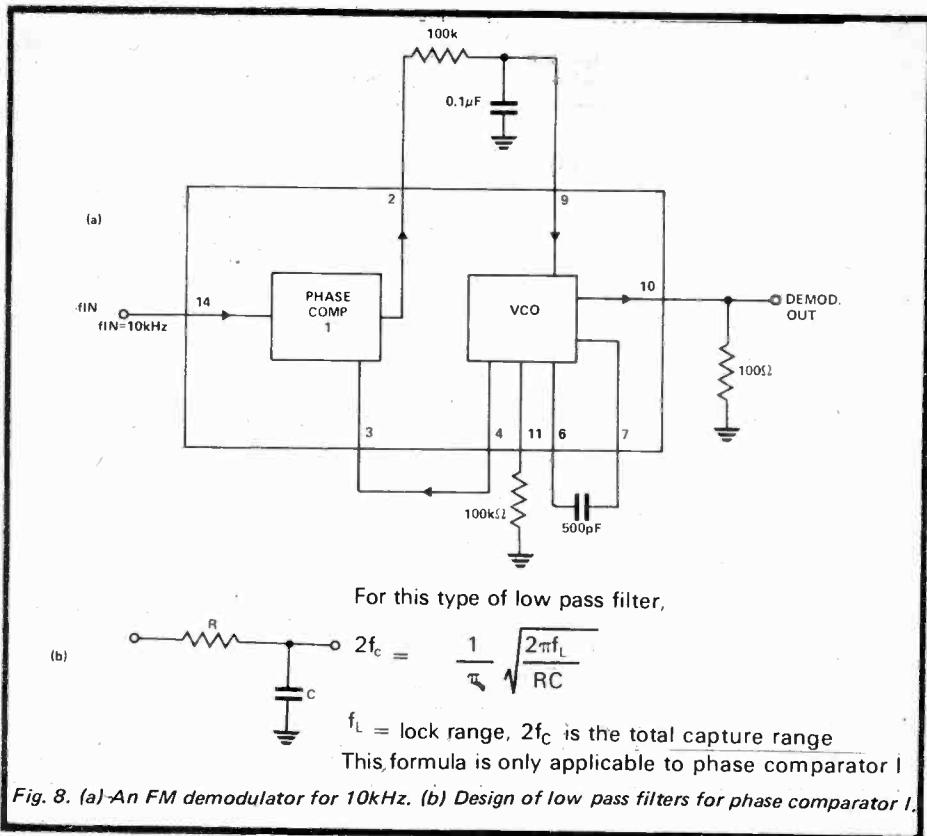


Fig. 8. (a) An FM demodulator for 10kHz. (b) Design of low pass filters for phase comparator I.

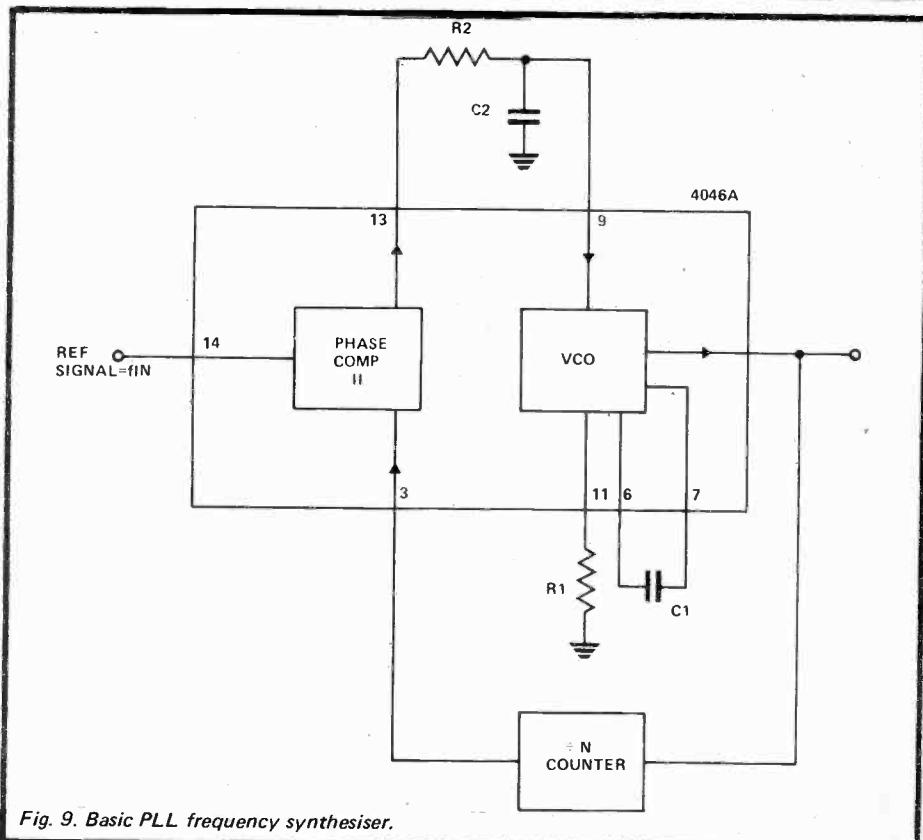


Fig. 9. Basic PLL frequency synthesiser.

over a very wide range and the linearity obtainable is very high.

Fig. 9 shows the outline design of a frequency synthesiser. The second phase comparator is used because it will deal with non symmetric output from the divider and will not lock onto harmonics. The V.C.O. is set with the pin 12


resistor infinite for maximum range. Three to nine hundred and ninety nine kilohertz in one kilohertz steps can easily be achieved. The low pass filter should be optimised for minimum settling times. The divide by N counter has been shown as a block as these have been discussed at length previously.

Continuous Display LCD Watches

UNIQUE ALTERNATING DISPLAY FEATURE

The watch normally displays HRS. and MINS. with MONTH, DAY and SECONDS on demand. The owner selects the feature where the HRS. and MINS. or MONTH and DAY display alternately for 2 second intervals until owner resets to normal display. During the alternating cycle seconds are still available on demand.

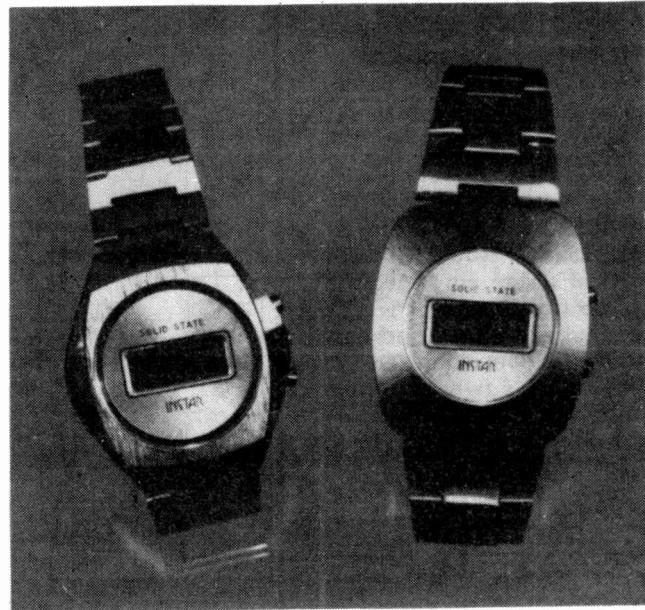- *Finest American MOS technology
- *Quartz accuracy
- *Multi-function:
 - Hrs., Mins.
 - Month, Day
 - Seconds
 - Alternating display
 - Back-light
 - Programmed 28, 30, 31 day months
 - A.M./P.M. indication for ease of date setting
- ***All important: U.K. factory manufacturing and servicing facilities.



1113-10

1113-20

£34.50 INCL. V.A.T. & P&P.

Watch despatched with matching Gold plated bracelet, in presentation box with instruction booklet and guarantee.

To: Leetronic, Lee Instrumentation Ltd, Newport, Gwent. NP1 8YZ
Print - FREEPOST - no stamp required

Please forward _____ (qty) model _____ at _____ each

TOTAL: £ _____

I enclose

Name cheque _____

Address postal order _____

..... money order _____

Barclaycard/Access no. _____

Leetronic

Watch Division,
Lee Instrumentation Ltd,

Bedwas,
Newport,
Gwent. NP1 8YZ
TEL: (0222) 885756-7-8
TLX: 497084

Reg. no: 639437 VAT Reg. no: 133 8154 80

REFLEX ACTION

An electronic duel to see who's quickest to the trigger



REFLEX ACTION IS a simple electronic game sufficiently competitive to keep two children amused for several hours (it will probably find usage amongst the adults of the household as well!). The device is both cheap and easily constructed, consisting as it does of four LED's, two switches, and the necessary amount (small!) of circuitry.

RULES OF THE GAME
Battle is joined by both contestants attempting to beat the other in operating their switch when the 'win' lamp comes on. The circuit will then indicate the winner by lighting that person's LED. Both lamps can never be on at the same time, and will only remain lit as long as the switches are held closed. If a player tries to anticipate by pressing his switch before the 'win' lamp the 'disqualified' signal will operate, and the opposition is awarded a point.

THE WORKS

The circuit is shown in Fig.1, and consists of a multivibrator, and nine two input TTL NOR gates (7402's). The contest switches feed a latch circuit, the inputs of which are normally high. Pressing either switch causes that input to go low, taking the output high. The other switch now has no effect. Hence if both buttons are operated apparently simultaneously, the latch will set on the first switch closing, and ignore the second.

This same circuitry runs the 'disqualify' LED. In this case the latch inputs are the clock multivibrator, (which also lights the win lamp in the first place) and the NOR gate G3. This gate gives a low output when either contest switch is depressed. A

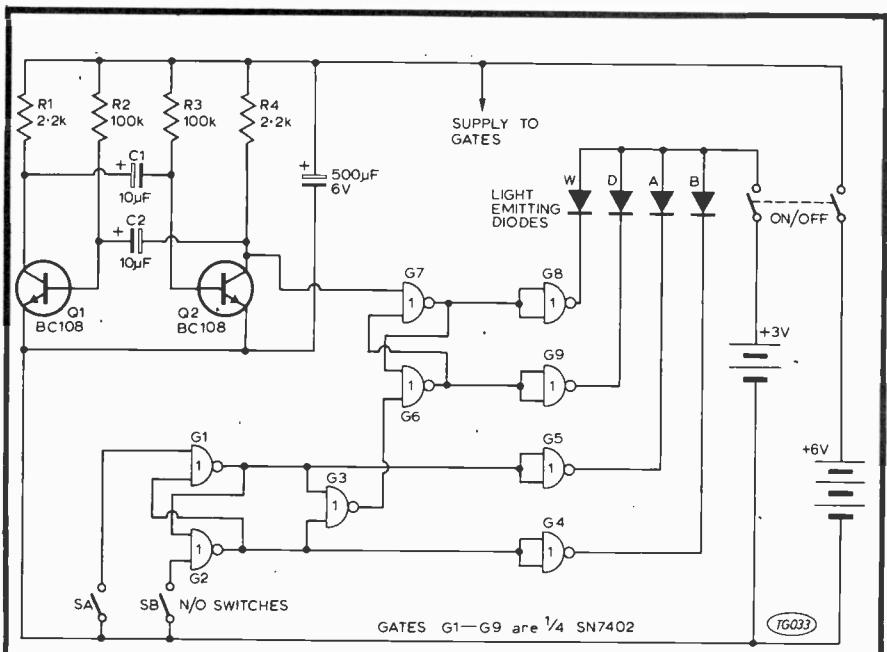


Fig. 1. Complete circuit of the game

500μf capacitor decouples the supply, and the LED's are run from a separate 3V battery, to avoid poor regulation interfering with the operation of the logic or clock.

CONSTRUCTION

A veroboard layout is given in Fig.2, although this is not critical and may be altered if the whim should take you. Note that on our layout, some of the tracks beneath the IC's have been used to make interconnections. The prototype used spring metal making onto bolt heads for the contest switches, but micro-switches would be better, though not to your pocket!

A double pole switch is essential for the power supply, as two batteries are employed. If you intend to power the device via a transformer, the supply voltage should be changed to 5V, and must be stabilised. This is because TTL packs run from an absolute maximum of 7V, which must not be exceeded.

COMPLICATIONS


If the game as it stands is too simple for you, there are some interesting refinements to the basic circuit which should not be too difficult to add.

For example, any number of switches can be added in parallel with Sa and Sb, making this a team game. In this case it is the fastest member of each team who scores the point. You can argue amongst yourselves as to it was!

To prevent the addition of phantom points, counters can be arranged to keep score automatically. Loaded from the players LED's, each one would count up by one every time that LED came on. A NAND gate, with one input inverted, and fed from the contest switches and the disqualifying lamp, would add one to the appropriate score when ever a player jumped the gun.

This modification could also be done using the spare gates in the fourth 7402. We'll leave the details to our readers ingenuity!

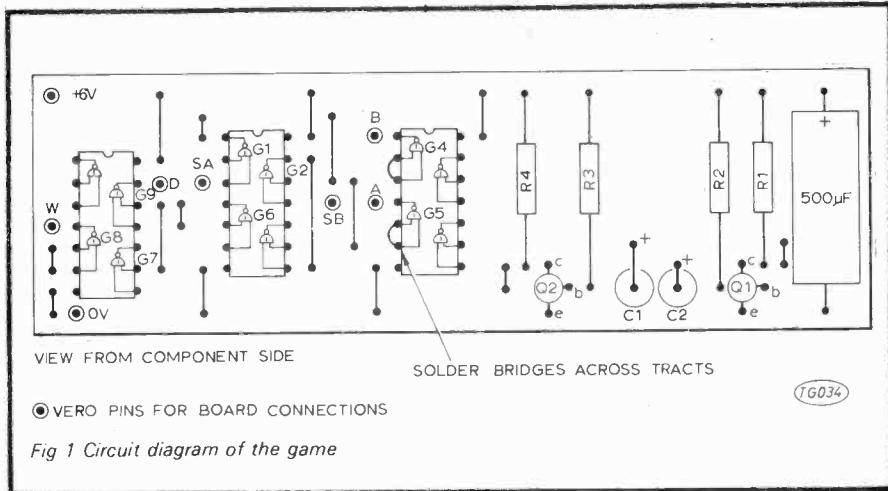A circuit of this nature lends itself easily to additions, and no doubt you can think of many more, but don't forget to try playing the game whilst you're trying!



PARTS LIST

R1,4	2k2	1/4W	5%
R2,3	100k	1/4W	5%


C1,2	10uf	9V	electrolytic
C3	500uf	9V	electrolytic

IC1-3, SN7402N

LED's TIL 209 or similar

Sa,Sb push to make

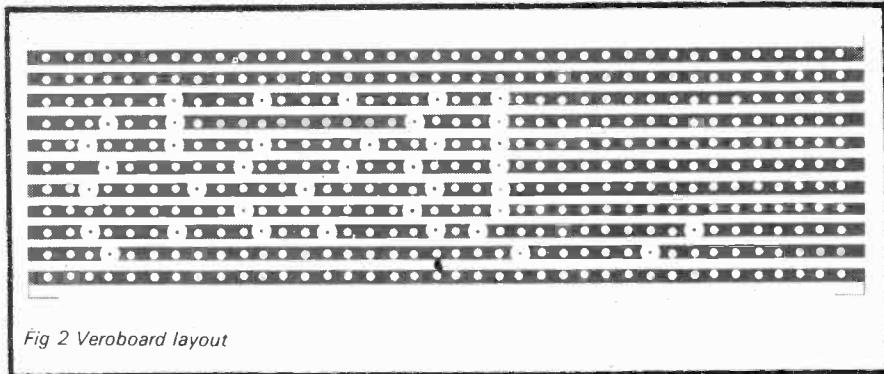Double pole battery switch
Case to suit
6V battery
3V battery



PULSAR, £13.95

WE ARE REPEATING OUR SPECIAL OFFER ON THIS DIGITAL ALARM CLOCK. WHEN WE RAN IT LAST YEAR IT PROVED TO BE ONE OF OUR MOST SUCCESSFUL OFFERS EVER! OUR PRICE INCLUDES VAT AND POST & PACKING.

Pulsar shows the time 0.7in high on bright Planar Gas Discharge displays (there is a brightness control on the back). The dot on the left of the display shows AM/PM, and the flashing (1Hz) colon shows that the alarm and clock are working.

A beeper alarm sounds until the clock is tipped forwards. Then the "snooze" facility can give you 5 minutes sleep before the alarm sounds again, and then another 5 minutes, etc, until you switch the alarm off. The clock also features a mains-failure indicator.

We have a large number of units in stock for this offer but please allow 28 days for delivery.



PULSAR OFFER
ETI MAGAZINE
36 Ebury Street,
London SW1W 0LW.

I enclose cheque/P.O. for £13.95 (payable to ETI) for a Pulsar Alarm Clock.

NAME

ADDRESS

Those not wishing to cut their magazine may order on their own notepaper.

Full size = 5in across and 3½in deep.

ELECTRONICS

-it's easy!

PART 27

Integrated circuit forms of logic functions.

NOW that we have a basic understanding of switching circuits and the algebra used to mathematically describe logical operations we can look at the modern methods used in solid-state circuitry to produce the various logic functions in integrated circuit packages.

LOGIC FAMILIES

DIODE LOGIC - DL:

Previously it was explained how a single diode could be used as a switch by altering the bias or the input signal level. If more than one diode feeds the

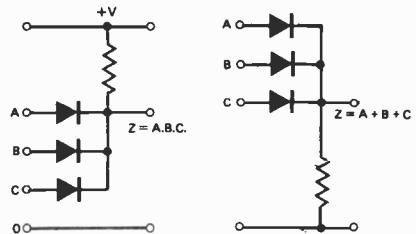


Fig. 1. The implementation of AND and OR gates using diode logic.

bias node the circuit becomes a gate. Three input AND and OR gates are shown in Fig. 1. The circuits are the same; the different class of gate arising because of different bias conditions in each case. Fig. 13 of the previous part showed the use of diode logic.

Diode logic is the simplest form of solid-state logic, it is not available in integrated form but is often used in discrete designs to obtain logic functions at high, or unusual (compared to standard IC logic) voltage levels.

RESISTOR-TRANSISTOR LOGIC - RTL:

Logic gating operations can also be obtained using transistors acting as switches in various ways. Fig. 2. shows a typical RTL NOR gate for which $Z = A + B + C$. Base current appearing at A, B or C will cause the respective transistor to switch to the ON state taking the output to ground which is a '0' in a positive logic system.

This family was the first to be used in the now more usual integrated-circuit form based on the planar manufacturing technique (one in which a mask is used to selectively diffuse impurities into a pure substrate in order to produce and separate active device junctions).

RTL is based on a supply of 3.6 V. Propagation delay is 12 nS for a medium power gate and 40 nS for a low power gate. It is a reasonably economic family to use but needs more space than the alternatives developed since. This form of logic was very much in vogue in the early 1960s but, although still manufactured by some companies for replacement purposes, is an obsolete type not used in new design.

DIODE-TRANSISTOR LOGIC - DTL:

This was the next family developed. The devices of the family use resistors, diodes and transistors. Initially DTL logic was constructed with discrete components. These designs were then integrated as shown in Fig. 3. Later devices used transistor input logic instead of diodes, thus reducing the input current requirement and allowing higher fanouts. Typical noise immunity (for a 5 V supply level - the standard used) is around 1 V. The delay time for a pulse signal to travel through, that is, the propagation delay between input change causing output change, is around 30 ns. Output is > 3.5 volts for a '1' and < 0.4 volts for a '0'.

It has a generally lower speed and lower noise immunity than other families. The advantages of DTL are the reasonably high fanout of 10 and the ease of interfacing or coupling a stage to the TTL family to be considered next.

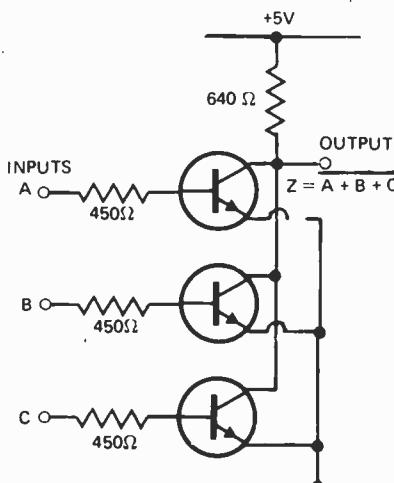


Fig. 2. Typical RTL circuit of a NOR gate: any logical '1' input will give a logical '0' output.

A similar family is HTL (high threshold logic) which uses 15 V supply lines and zener diodes. This is useful in situations where high noise levels occur because this logic is more immune to noise effects than is DTL.

TRANSISTOR-TRANSISTOR LOGIC - TTL:

This is the most popular logic family in current use. It has higher speed and driving capability than DTL. The propagation delay is around 12 ns which is quite fast enough for the majority of computing applications.

A typical TTL gate circuit for $Z = A \cdot B \cdot C$ is shown in Fig. 4. Note how the diode input gate has been replaced with a multi-emitter transistor. This multi-emitter technique reduces the input capacitance thus speeding up the switching time, as well as simplifying manufacture. In TTL the supply is +5 V, the output switching between around > 2.4 for a 1 to < 0.4 for 0 (in positive logic). Fig. 5. shows a TTL signal switching state with time.

For all of its popularity TTL is not ideal, especially for the fastest circuit operation or where the lowest power consumption is required. Another difficulty with TTL is that switching transients occur (see Fig. 5) at the transitions. It is also not particularly suitable for large-scale integration by virtue of the relatively large amount of space and power required by each gate function.

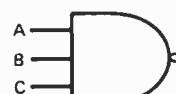
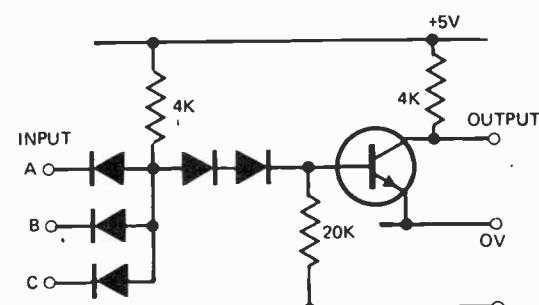


Fig. 3. An early integrated circuit design for a NAND gate in diode-transistor logic - DTL.

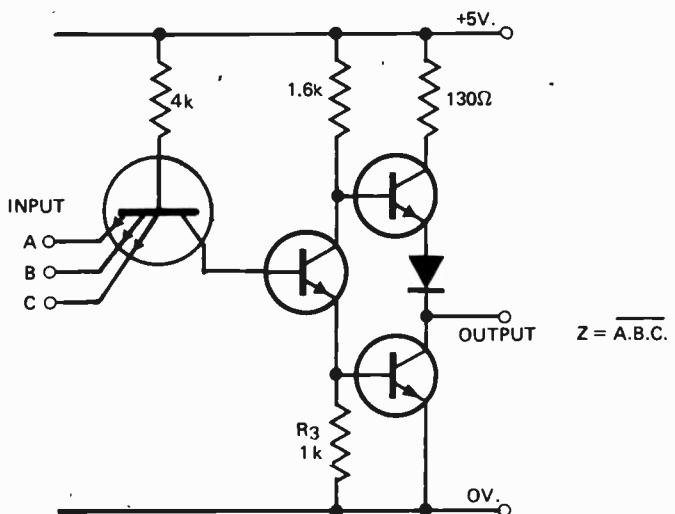


Fig.4 Typical output signal from TTL, note the transient ringing at each transition.

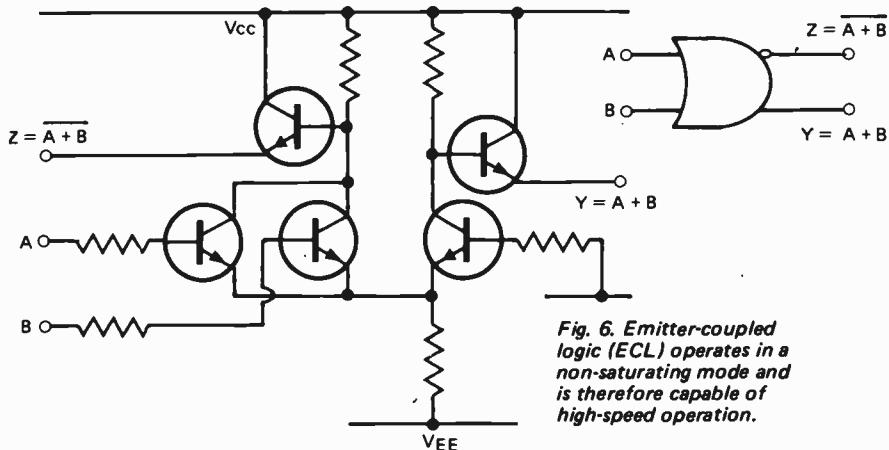


Fig. 6. Emitter-coupled logic (ECL) operates in a non-saturating mode and is therefore capable of high-speed operation.

EMITTER-COUPLED LOGIC

- ECL:

A typical ECL stage is shown in Fig. 6. As this operates in the linear mode, that is, without allowing the active devices to go into saturation, it gives high-speed 2-3 ns switching times. It, however, needs a moderate power requirement, is not particularly noise immune and needs an extra power supply line. Supply voltages used for ECL vary but when typical supply rails of 0 V and -5.2 volts are used the output is -1 volt for the '1' state and -1.6 volts for the '0' state.

Each of the above logic families is based on the use of the transistor semiconductor junctions — the so-called bi-polar technique. Around 1970 ECL emerged as a possible future contender to TTL and at the same time another quite different kind of semiconductor active device became freely available — the field effect transistor FET. A variation of this is the insulated-gate field-effect transistor IGFET. Fig. 7 lists the symbols of the basic FET structures used in logic. This technique is manufactured using metal-oxide-semiconducting materials;

abbreviated to MOS. Hence, the MOSFET is a metal-oxide-semiconductor field-effect-transistor. They can be made in the two complementary ways, P or N, of which the first is most conventional giving the PMOS technique. With improvements in technology the NMOS technique is also being used for very complex circuit blocks.

The attraction to manufacturers and users of MOSFET devices is that the packing density of the active devices is the highest of all types — much better than TTL. It is, however, not as fast as TTL but adequate for a large part of the consumer market. FETs have extremely high input impedance, 1.0 TΩ (1 000 000 M Ω) is common.

THE CMOS FAMILY


IC device designers went a step further in the early 70's to produce yet another family — the complementary metal oxide semiconductor logic — CMOS. This combines both the P and N, MOS technique in a complementary manner to produce a more ideal switching action than PMOS — Fig. 8 illustrates the difference between the two. Fig. 9 is the schematic of a CMOS two-input



Fig.5 In the TTL (transistor-transistor logic) form of NAND gate a multi-emitter transistor replaces the diodes of DTL.

FIELD-EFFECT TRANSISTORS (FET_s)

n-channel junction gate (JFET)

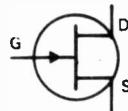

p-channel



three terminal depletion-type insulated gate (IGFET)



three terminal depletion-type IGFET, substrate tied to source




four terminal depletion-type IGFET



four terminal enhancement-type IGFET



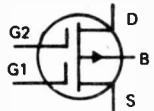five terminal dual-gate depletion-type IGFET



five terminal dual-gate enhancement-type IGFET

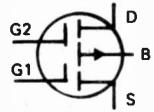
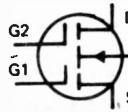


Fig. 7. The symbols used for the various types of FET device.

ELECTRONICS -it's easy!

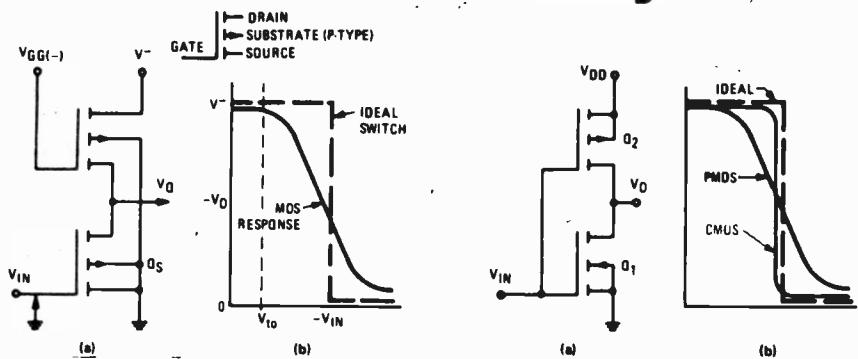


Fig. 8. A comparison of PMOS and CMOS inverters.

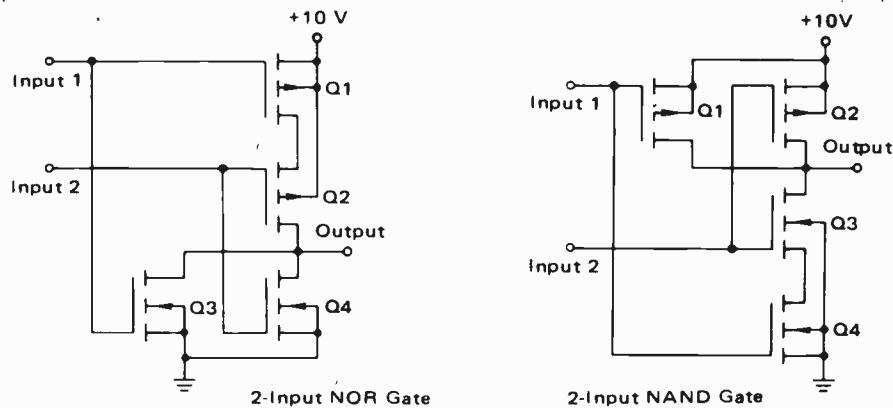


Fig. 9 (a). A CMOS 2-input NOR gate.
(b). A CMOS 2-input NAND gate.

NOR gate. One of the most significant advantages of CMOS is its low power dissipation. Because of the extremely high off-resistance of MOS transistors, and because only one transistor of the series-inverter CMOS pair is ever on at the one time, the dc current drain of a CMOS inverter is in the low nano-ampere range as compared to 0.2 millamps for a low-power TTL inverter. At the system level a CMOS system typically requires one-twentieth to one-thirtieth the power required by an equivalent TTL system. In fact torch batteries are adequate to run quite complex CMOS devices.

Because of the complementary configuration CMOS has high common-mode noise immunity (such as power supply variations). It will operate with supplies from 3 V to 16 V and needs only a single positive supply. In addition the high packing density has allowed the building of low cost large-scale-integrated (LSI) packages. Interfacing to conventional transistor logic is easy because it has a low output impedance. It generates

low noise because of nicely conditioned rise and fall times. The fan-out factor of 50 is the highest of all logic because of the extremely high input impedance. Its speed is better than PMOS but not quite up to that of TTL — propagation delays being from 12 to 60 nanoseconds depending upon supply voltage used.

We have merely glossed over these various kinds of device because we are mainly concerned here with digital systems in general. To design systems requires little in-depth understanding of the manufacturing method used for the actual logic element. The logic IC is merely a black-box with certain input-output characteristics as stated on a data sheet.

Why do new families keep emerging? The facts are that there is still a cost saving to be had and the market is huge. The estimated value of the total market for IC devices in 1975 ran to around £200 000 000. CMOS offered new horizons in cost savings in manufacture. As a bonus from the power requirements of CMOS systems, the so-often neglected power supply

cost drops remarkably.

We have all experienced the remarkable increase in the use of active devices in the last decade or so. A transistor radio now costs £1 to make commercially — and there the semiconductors are but a small part of the cost. (Just one common thermionic valve costs more than this today!) A calculator using hundreds of devices can be bought for £5. Minicomputers and microprocessors are rocketing down in price — tens of thousands of elements for a few hundred pounds. It might be argued that reducing the price will soon reduce the makers' total income but as prices fall, applications for digital circuitry widen at an even faster rate, thereby keeping up an expanding demand.

THE DUAL-IN-LINE PACKAGE

The most commonly used form of IC logic package in small batch production is the dual-in-line (DIL) arrangement with 8, 14 or 16 pins. Large-scale integration LSI used by specialist manufacturers will vary in number of connection, but systems based on these require very large volume sales to make a large special system economic. Thus LSI chips are largely restricted to computers or very high volume runs such as calculators and digital clocks.

The number of connections decides the available combination of functions or inputs and outputs. Assuming a need for two power-supply terminations, of which one is the common for all functions, a 14 pin device will have 12 pins available to produce various combinations of input. Fig. 10 shows the main units that are marketed. Available are the sextuple inverter (6 inverters with one input and one output each); the quad 2 input NAND (four two-input NAND gates); the quad two-input NOR, triple three-input NAND, dual four-input NAND, single eight-input NAND plus other more special combinations such as a more powerful dual four-input NAND buffer and others to be discussed below. Each gate function is a quite separate entity on the substrate; when schematic circuits are drawn the individual gates can appear anywhere on the system schematic.

As well as gates there are several other basic digital-system building blocks. These are the flip-flop, (more correctly called the bistable), the monostable, the astable and the Schmidtt trigger. Let us look at each in turn.

LOGIC DIAGRAMS AND TERMINAL CONNECTIONS FOR SN7400 SERIES

P = positive supply voltage
 \emptyset = earth

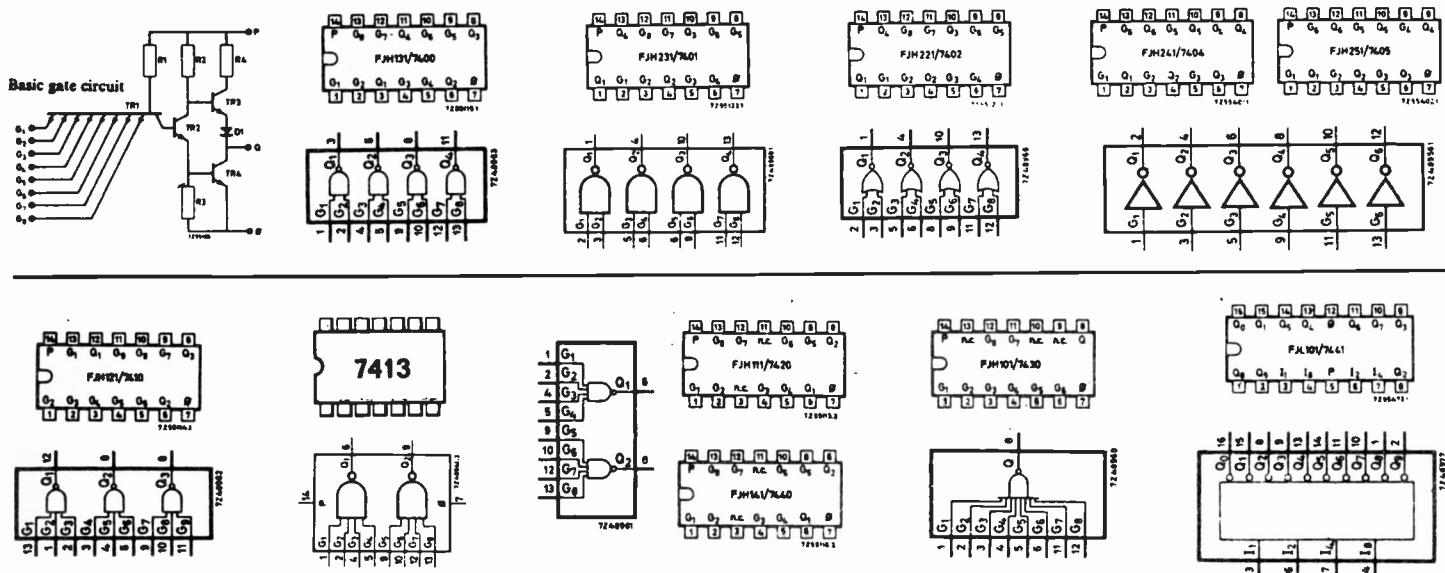


Fig. 10. The basic logic gates of the TTL family.

THE FLIP-FLOP

Gates are used to perform logical arithmetic, such as, allow event A to occur when B or C have operated. Digital systems can be greatly enhanced by the addition of blocks that remember and count the digital numbers. It is quite possible to use the gates we have discussed to form counting stages but it is more economical to build specific circuitry that will count pulses and/or store values in a binary form. The basic block of modern counting technique is the flip-flop — FF or bistable — one of the multivibrator family.

The most elementary flip-flop circuit is repeated from Part 20 as Fig.11. It consists of two-transistors and several resistors which are dc coupled in such a way that each stage provides a signal which controls the state of the other. In essence the characteristic behaviour is that one stage will be held ON when the other is OFF, or vice versa. To reverse the situation a pulse or change in input signal level (which can be applied to either the base, emitter or the collector) will cause the system to toggle over to the other state. Because of the heavy degree of positive feedback provided, the circuit does not dwell in the in-between state. State change is very rapid — nanoseconds in well designed IC flip-flops.

A decade ago flip-flops were built from two, or in the faster toggling circuits, four transistors. Considerable effort was expended to provide a fast, reliable flip-flop action. Today a typical IC equivalent, see Fig.12 uses many active elements for less cost than two discrete transistors. As discrete designs play no real part today we will only give the characteristics of the

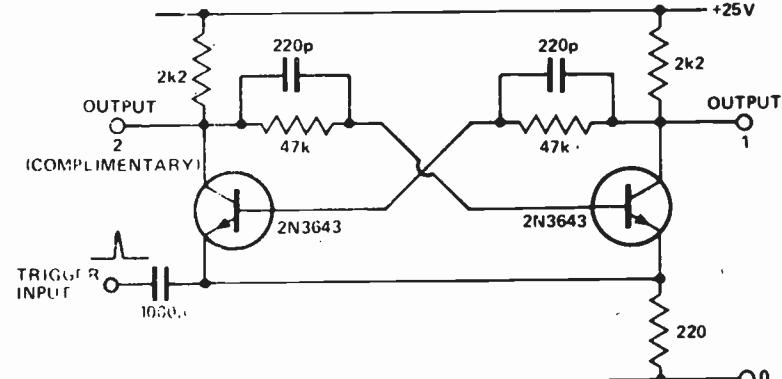


Fig. 13. A basic flip-flop built with discrete components.

flip-flop, not its design details.

Flip-flops provide a counting action because each pulse at its input causes the system to switch over one state — the output, therefore, switches state at each second input pulse providing a divide by two action. The output is a switched level which can then be used to pulse a following stage dividing by two again and so through cascaded flip-flops.

The most commonly used flip-flop symbol is given in Fig.13. Outputs are denoted by the symbol Q. A flip-flop has two outputs, one of which is the inverted value of the other, that is, Q and \bar{Q} . The pulsing input is denoted T for trigger. As well as these connections we need a set and reset input denoted S,R. (Although often only R is provided). These enable the flip-flop to be set up on demand with the output Q set to either 0 or 1 state as is needed. This is essential firstly because a flip-flop can come up in any state when the power is energised, and secondly because it may be necessary to set counterstages to a given binary number.

Some flip-flops provided in IC form

also may contain three-input AND gates that feed the set and reset inputs. These are known as the J and K inputs giving the name J-K flip-flop. The JK flip-flop overcomes an ambiguous output state, when both inputs are high, that occurs with the RS flip-flop. We will see, when counting systems are discussed, why the reset ability is vital in many counters. Fig. 16 gives the schematics of some of the available flip-flop ICs.


THE MONOSTABLE

If one of the bias resistors of the bi-stable circuit is replaced by a capacitor, as shown in Fig.14, the circuit provides a different action from the normal flip-flop. When triggered the circuit changes state, but only stays toggled in the changed state for a time decided by the product of the values of the capacitor and its "charging" resistor R. ($T = 0.7RC$) Hence a pulse input will cause the output to change state and remain there for a chosen time interval before it triggers back to the original state.


The monostable, also called a one-shot or single-shot provides, as we

FLIP FLOPS

R-S (set-reset) flip-flop

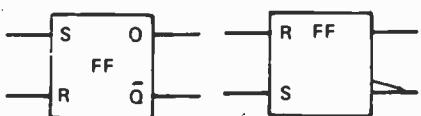

Toggle flip-flop

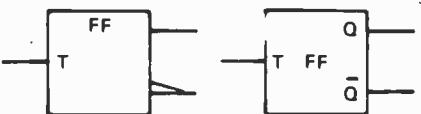

J-K flip-flop



D-type flip-flop



Fig. 12


saw in Part 20, an output pulse having a designed length and height which remains the same irrespective of the input pulse shape. It, therefore, finds application as a pulse reshaper. As the duration is fixed it can also be used to generate a pulse that is delayed from the triggering pulse by the length of the monostable pulse. Monostables are available in IC form, and can provide pulses of duration from 20 ns upwards to minutes or more by appropriate choice of values.

THE ASTABLE


If both feedback paths use capacitive coupling the circuit becomes self-toggling with the stages alternating in state without being externally driven. We considered this circuit in Part 20 when discussing signal generation. The astable is important in digital systems for it provides the square wave signal that increments the digital system along pulse by pulse. It acts as the 'clock' regulating a digital system's sequential operations.

Astables are not usually produced directly in IC form, for the same action is obtainable with other elements, for instance, with the next element to be

DIP (TOP VIEW)

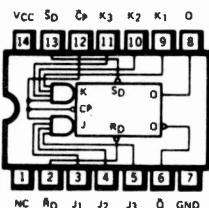

SCHEMATIC DIAGRAM

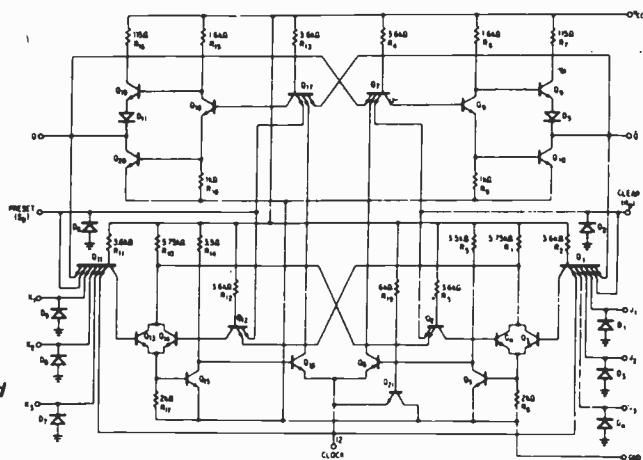

Component values shown are typical.

LOGIC DIAGRAM

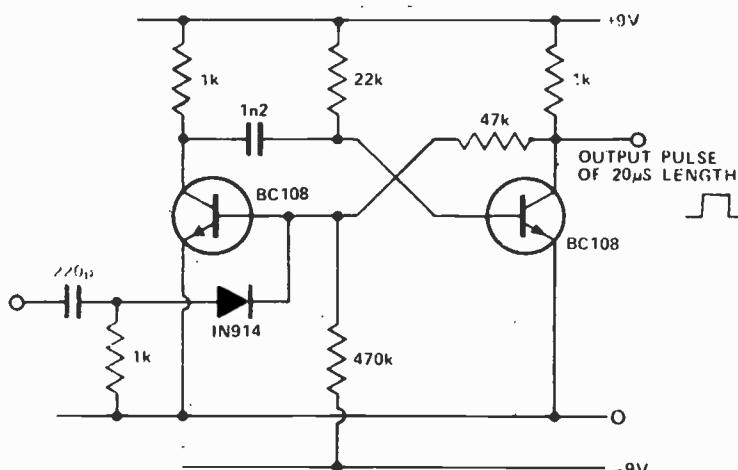
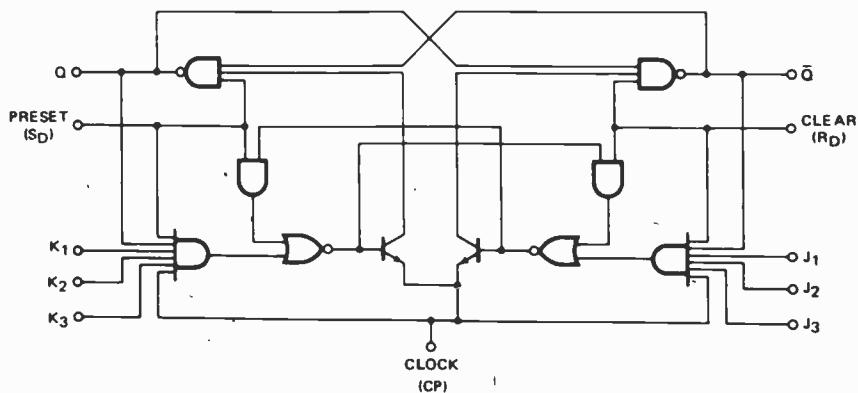


Fig. 14 A basic monostable constructed with discrete components.

considered, the Schmitt trigger. Fig. 15a shows a clock source based on a Schmidtt trigger IC. Fig.15 shows one based on two NAND gates.

THE SCHMITT TRIGGER

This unit, also introduced in Part 20, toggles over from one state to the other at a certain input voltage level. It remains in the opposite state until the

voltage falls below the threshold level. The Schmitt trigger is used to produce digital signals from analogue signals providing the two necessary binary levels at the output which indicates whether the analogue signal is above or below the threshold and, which are compatible with the rest of the digital system.

The Schmitt function is available in


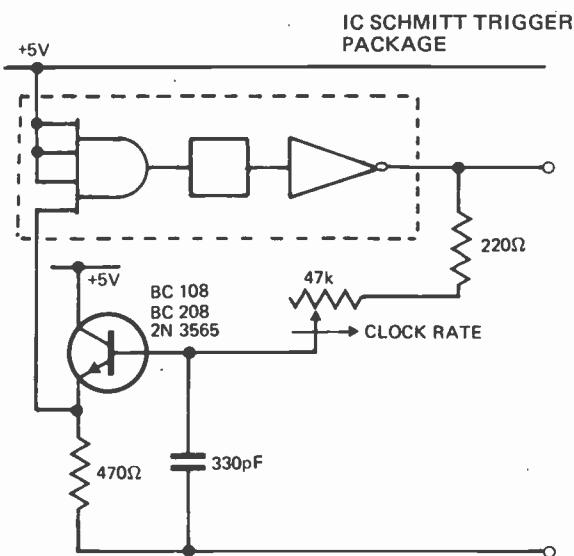


Fig. 15a LEFT: A Schmitt trigger combined with a transistor provides an astable multivibrator action.

Fig. 15b BELOW: Astable action may also be produced with two NAND gates.

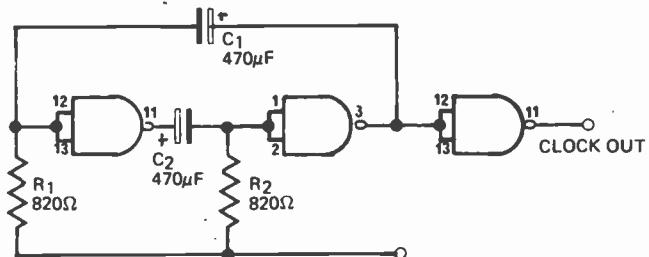

IC form as a dual-in-line pack. It has a four input AND gate feeding the actual trigger circuit and is buffered with an inverter. The Schmitt trigger is readily identified in Fig.15. Its preferred symbol is given in Fig.16.

YOUR LIBRARY

There are a bewildering number of digital ICs and to identify them correctly it is wise to have a good range of manufacturers' catalogues and application notes.

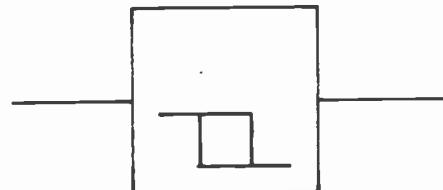


Fig. 16 Standard Schmitt trigger symbol.



SPECIALS

Electronics — It's Easy — the first thirteen parts of our popular introductory series and a good way to begin finding out more about your hobby. £1.20 + 15p p&p.

Project Book Two — contains 26 popular projects from the pages of ETI, first published July 1975. 75p + 15p p&p.

4600 Synthesiser — complete reprint of our superb synthesiser design produced by Maplin, who can also supply the parts. £1.50 + 15p p&p.

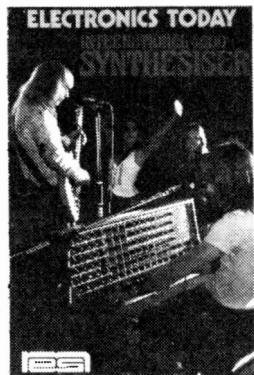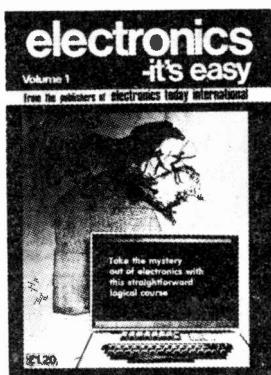We regret to say that Projects Book One is now completely sold out, and we cannot accept any more orders.



To ETI Specials, ETI Magazines, 36 Ebury Street, London SW1W 0LW
Please send me the following special publications (please mark quantities required)

TOP PROJECTS BOOK TWO

(75p)

ELECTRONICS-ITS-EASY

(£1.20)

INTERNATIONAL 4600

(£1.50)

POSTAGE AND PACKING is 15p for the first, 10p for subsequent (overseas 20p and 15p)

Please send me the issues indicated above, I enclose

which includes postage

NAME
ADDRESS

ELECTRONICS TOMORROW

by John Miller-Kirkpatrick

IT HAPPENED with audio amplifiers, and now with digital clocks — the modular revolution — or how to build a digital clock the very easy way. For some time various digital clock kits have been on the market, some have come and gone whereas others have developed into more complex units. Right from the days of the TTL clock unit it has been a race for retailers to keep up with technology. I think that the first digital clock kit using LSI circuits was based on the Timtronic which was an article in ETI some three years ago, this kit was reasonably simple to build but cost of components added up to over £30.

FIRST ATTEMPTS

One of the first successful complete clock kits using LSI must have been from Pulse Electronics. This used the famed MM5314 chip with drivers and displays, all presented with transformer, etc, in a pleasant perspex case. Although I have never seen the kit version the finished clock that I saw about a year ago looked quite attractive, and I have heard that the kit is relatively easy to build. It was quite a bargain at about £16 when it first appeared. At about the same time as the Pulse clock kit came onto the market General Instruments announced their CPD-1 clock, available as a module or as a fully built clock. (Many of you might recognise this as the ETI Pulsar although it went out under various disguises):

This clock module was beset with many problems in its early days as the chip was of the new NMOS type and was very prone to static problems. GI had not fully tested the clock in anything other than a laboratory environment and although the electronics may have been good the unit suffered from components physically moving during transit with the result that the clocks

failed to work. All of these problems were eventually solved late last year, some 14 months after I had seen the first prototype.

The thing that the Pulse kit and the CPD-1 clock did do was to set the prices for this type of product at about the £15 area. This has the advantage from the customer's point of view that prices are now settling at a level which was not far from what must be the eventual digital clock price of £9.95. Thus unlike calculators and digital watches the cost of buying or building a clock now is not much different than the expected price this time next year.

This was confirmed late last year by the introduction of the Mistral clock kit from Imtech at £12.50. Simple to build with simple functions — 12/24 hour readout, 50Hz input and easy setting. This has now been followed by the Mistral 2 which is a complete clock, with functions similar to the Pulsar, but with the Futaba 5-LT-01 display which is green whereas the Pulsar has an orange display. The Mistral 2 has been dropped down stairs and even subjected to the GPO test — throwing it across a room — it still seems to work!


Another clock, out just before Christmas from Carmen (the Hair Curler people), is in a slim vertical case, again with the Futaba display, but this time with optional filters to alter the colour. A very attractive clock but too highly priced at a RRP of £30. However, this points to the idea that we might see digital clocks from other similar names that you might not normally associate with clocks. (Smiths, Timex, Westclocks, etc have not yet appeared on a digital clock at all).

THE REASON FOR ALL THIS HISTORY

Now most of the regular Electronics Tomorrow readers may well

have guessed that the above is in fact a lead in to yet another new product. This time from National Semiconductors, who recently announced the MA1001 clock module, although it has been mentioned before it is only now that we can bring you all of the thrilling details. But first to whet your appetite, the one off price — £8 and that means that you can now build a clock for less than £10.

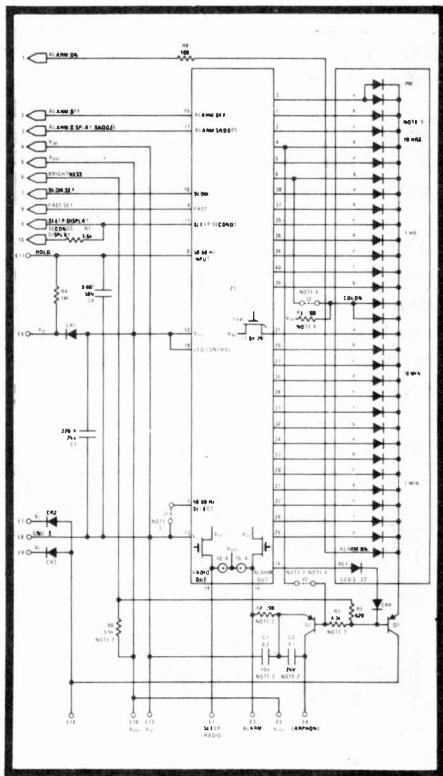The MA1000 series starts with the MA1001 combining a monolithic MOS LSI integrated clock circuit, four digit 0.5" LED display, power supply and other discrete components on a single printed circuit board to form a complete



electronic clock 'movement'. The user need only add a transformer and switches to construct a pretested digital clock for applications in clock-radios, alarm or instrument panel clocks. Timekeeping can be from 50 or 60 Hz inputs and 12 or 24 hour display formats may be chosen. Direct (non-multiplexed) LED drive eliminates RF interference.

FEATURES

Features include alarm on indicator, PM indicator, flashing colon, Sleep and Snooze timers and a variable brightness control. Alarm clock options include a switched output and/or a transistor oscillator circuit for use with low cost

earphone audio transducers. Power failure is indicated by flashing the entire display on and off at a 1Hz rate — this is reset by using either of the fast or slow setting controls. The outputs for controlling clock radios are —

Sleep: a positive current source controlled by the sleep timer (max 59 minutes). This output can be used to switch on an NPN power transistor for controlling a radio or other appliance. Alarm: a positive current source controlled by the alarm enable and comparator circuit, this output can be used to drive radios or appliances in a similar manner to the sleep output. The alarm output is disabled for a period of 10 minutes by the snooze button. Alarm Tone: some versions of the module use the Alarm output to enable an oscillator which is capable of driving a small earphone type transducer.

VERSIONS AND STANDARDS

The MA1001 is just becoming available in this country but do check that the suffix indicates the module you want, as some of the options are interchangeable (eg 60Hz conversion to 50Hz is a simple link but 12/24 hour option is not).

The various models presently

available are —
 MA1001B switched alarm output, 50Hz, 12 hour.
 MA1001D switched alarm output, 50Hz, 24 hour.
 MA1001F Tone alarm output, 50Hz, 12 hour.
 MA1001H Tone alarm output, 50Hz, 24 hour.

The standard for the UK will be either the F or H versions as these have both the switched and tone alarm outputs. The oscillator can be built onto the PCB if the B or D versions are the only ones available and all of the 60 Hz versions can be easily altered to 50Hz. I would personally be very interested to hear from readers whether they prefer 12 or 24 hour readout and any other points of preference on the subject of clocks.

MPUs, CPUs, Teletext, Viewdata, Uncle Tom Cobley and all . . .

What if we had a Teletext and/or Viewdata installed in most households already, what about a small microprocessor unit possibly connected to the same unit? Apart from the usual household chores you could program the MPU to do it could record Open University programs from Teletext, enable you to swap software via Viewdata, you

could communicate with computers and other microprocessors all over the world, you could even possibly design your own cartoons or news items for CEEFAX and transmit them to the BBC via Viewdata. Now that information is available on all these three I would like to hear from any readers who have built and used any of them, what comments have you got to make on Teletext or MPUs, what do you think of Viewdata, what problems have you had? Whether you are a manufacturer or user of MPUs or Teletext or even if you are just interested in them what are the average consumer applications going to be in a few years' time — make some predictions and let's see how right you are in a couple of years.

REFERENCES

1. MH9 — Bywood Electronics, 68 Ebberns Rd, Hemel Hempstead, HP3 9QRC.
2. Pulse Electronics, 202 Skefford Rd, Clifton, Shefford, Beds.
3. CPD-1, G.1.C.P.D., Berk House, Basing View, Basingstoke, Hants.
4. Mistral — Imtech Products Ltd, Imp House, Ashford Rd, Ashford, Middx.
5. MA1001 — Bywood or National Semiconductors (UK) Ltd, 19 Goldington Rd, Bedford.

6-Digit Digital Clock Kits

- 12/24 HOUR
- 50/60 HERTZ
- BRIGHT DISPLAYS
- SLOW TIME SET
- FAST TIME SET
- TIME HOLD



£6.95*

+90p Airmail p&p

If you have been considering building a digital clock kit but were discouraged by the high prices, we have just removed your last excuse. Why pay over £12 when you can get one for about half that price?

KIT COMPRISSES:

- 1 — National MM5314 Clock Chip, 12/24 hour, 50/60 Hz option.
 - 6 — Bright red common cathode displays, 0.27" character height.
 - 7 — NPN Segment driver transistors.
 - 6 — PNP Cathode driver transistors
 - 9 — Carbon resistors
 - 5 — Diodes
 - 2 — Disc caps
 - 1 — Electrolytic filter cap
 - 3 — Switches for time setting functions
 - 2 — Etched, drilled and plated p.c. boards.
 - 1 — Illustrated assembly instructions manual
- All you provide is a 9-12v ac/200 m/a Transformer and case of your choice.

OPTIONAL JUMBO DISPLAYS

You can have 6 — 0.5" Jumbo displays with a suitable board instead of the 0.27" types. Clock kit with 6 jumbo displays £10.95* + 90p airmail p&p

★ ORDERING INFORMATION

The above prices shown in British £s are approximate equivalents of the following U.S. Dollar prices and should be used as a guide only:
 Clock kit with 6 — 0.27" displays: U.S. \$16.50 post paid.
 Clock kit with 6 — 0.50" displays: U.S. \$24.75 post paid.
 Remittance by BANK DRAFTS or INTERNATIONAL MONEY ORDERS IN U.S. FUNDS. SENT ANYWHERE IN THE WORLD.

NO ELECTRONICS KNOWLEDGE REQUIRED TO BUILD THESE KITS

sabtronics
INTERNATIONAL

P.O. Box 64683, Dallas, Texas 75206, U.S.A.

tech-tips

CAR BATTERY WATCHDOG


In winter, motorists are apt to emerge from work to face the inconvenience and perhaps expense of a totally flat battery due to having left their headlights switched on when parking.

This circuit provides an audible warning if the ignition is switched off with the lights left on, in the form of a few seconds of output of varying pitch. No switches are required and standby current is very small.

The audio oscillator is normally biased off, but when the ignition switch is opened it is temporarily biased on by the charging action of R1, R2, C1.

D1 in conjunction with R3, prevents damage to T1 due to spikes on the ignition line, etc. The fuses are an optional precaution against short circuits across ignition or lighting supplies.

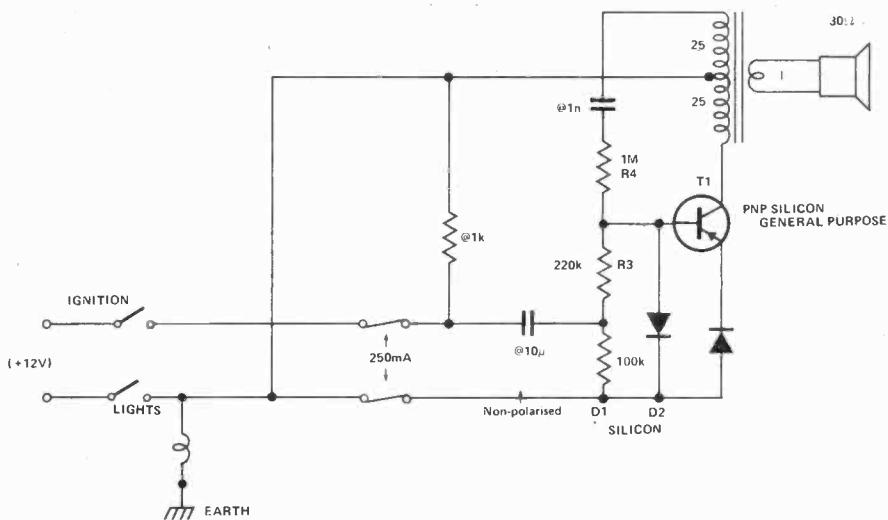The oscillator circuit will no doubt depend, as will the transducer, on the contents of the experimenter's junk



box. Basic requirements are that it should not be self-sustaining when the ignition switching transient in the base circuit has died away. The ratio R3/R4 was of course chosen to achieve


this in the circuit shown, assisted by D2.

For negative earth operation T1 would of course be NPN and D1 and D2 would be reversed.

STATION INDICATOR FOR FM TUNERS

Modern FM equipment using varicap tuners generally have four stations pre-tuned and selected by push buttons in addition to a continuously variable control. Most users of such tuners would presumably have the pre-set pushbuttons set to BBC Radios 1,2,3,4. It is, then, quite a simple matter to utilise the unused switch positions which, more often than not, exist in the pushbuttons to set up a display of 1,2,3 or 4 on a 7 segment LED using blocking diodes and limiting resistors as shown in the diagram. Any general purpose diode capable of carrying 5mA is suitable. A suitable display would be the inexpensive MAN3M which is quite large enough for such an application.

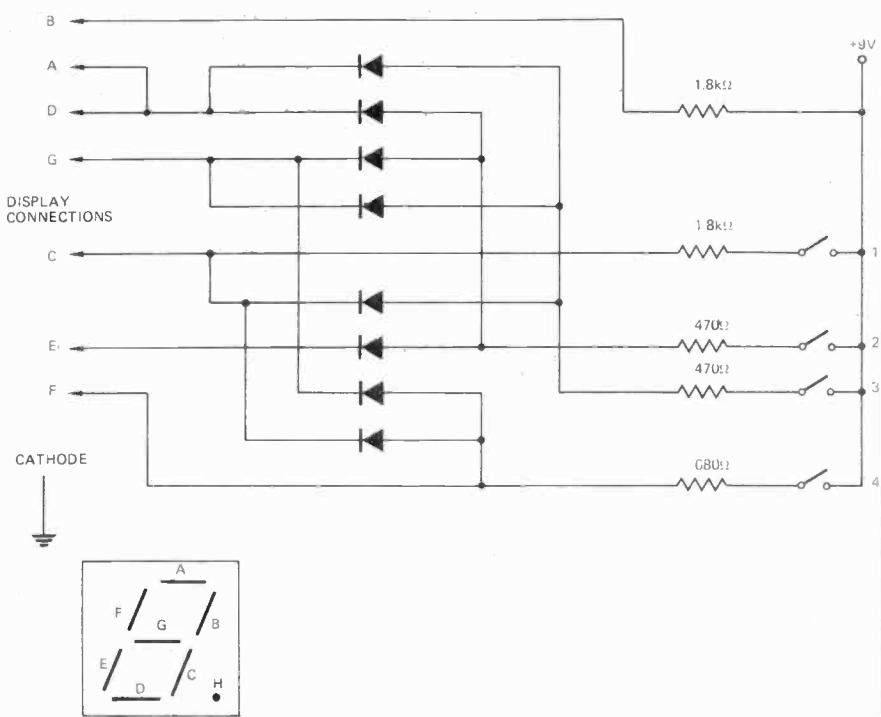Some users may have a local radio station pre-tuned, this can be indicated with the character "L" using the F,E and D segments of the display. Other alpha characters that can be formed with a 7 segment display are A C E F H L O P S U Y b d g h.



THE 'MISTRAL' 1 DIGITAL CLOCK

★ COMPLETE KIT ★



- Pleasant green display - 12/24 Hour readout
- Silent Synchronous Accuracy - Fully electronic
- Pulsating colon - Push-button setting
- Building time 1 Hr. - Attractive acrylic case
- Easy to follow instructions - Size 10.5x5.7x8 cm
- Ready drilled PCB to accept components

KIT PRICE £10.25

+ 8% VAT
P&P inc.

THE 'MISTRAL' 2 DIGITAL ALARM CLOCK

★ Fully Built, Tested and Guaranteed ★
WITH SLEEP-OVER FEATURE



- Soft Green Display
- 24 Hour Alarm
- 10 Minute Repetition
- Alarm Set Indicator
- Accurate Silent Timekeeping
- British Designed and Built

**COMPLETE CLOCK
£12.99**

+ £1.04 VAT
P&P inc.

1419 - ADVANCED



SPECIFICATION

- 14 digit LED display
- 10 digit mantissa with sign and 2 digit exponent with sign for data entry or results (10^{-99} to 10^{99})
- Automatic selection of correct notation for result display (scientific or floating point)
- Dome keyboard for excellent response and preventing double entry input
- BASIC FUNCTION (+ - \times \div) AND MEMORY
- Algebraic mode operation
- Constant operations
- Repeat operations
- Chain operations
- Change sign operation
- Display and Y-register exchangeable
- One accumulating memory
- Display and memory exchangeable
- SPECIAL FUNCTION
 - Trigonometric functions (\sin , \cos , \tan)
 - Inverse trigonometric functions (\sin^{-1} , \cos^{-1} , \tan^{-1})
 - Hyperbolic functions (\sinh , \cosh , \tanh)
 - Inverse-hyperbolic functions (\sinh^{-1} , \cosh^{-1} , \tanh^{-1})
 - Radian or degree selectable
 - π constant
 - Logarithms (ln, log)
 - Anti-logarithms (e^x , 10^y)
 - Combinatorial functions ($n!$, $\binom{n}{r}$)
 - Normal distribution function ($P(x)$)
 - Gamma function ($\Gamma(x)$)
 - Group operations ($\sum \pm 0 \times [x]$)
 - Group controls (K^x , K_1 , Σ , ΣG)
 - Power function (y^x)
 - Reciprocal ($1/x$)
 - Square root (\sqrt{x})
 - Square (x^2)
 - Sum of squares (Σx^2)
 - Summation (Σx)
 - Item count (n)
 - Mean value (X)
 - Mixed chain operations with parentheses approach (up to two levels)

PRICE £25.89

P&P 75p + VAT £2.13



Cash, Cheque or Postal Order or if you wish to use Barclaycard or Access, simply quote name, address and card number when ordering.


PRICE £55.63

P&P 75p + VAT £4.51



PRICE £40.80

P&P 75p + VAT £3.32

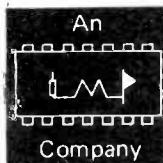

IMTECH PRODUCTS LTD

IMP HOUSE, ASHFORD ROAD
ASHFORD, MIDDX. TW15 1XB ET
telephone ASHFORD 44211 (4 lines)
telex 936291 WESSIMP ASHFORD

tech-tips

SOUND OPERATED FLASH

The circuit shown enables near instantaneous synchronisation between sound and flash. The latching facility has been incorporated so that the flash is not retriggered.


Resetting is by S1. With S2 closed, resetting occurs after a time after a time determined by $1.1 \times C_2 \times R_3$. This approximately equals five seconds as shown.

D1 indicates triggering and is used when setting the sensitivity:- set VR1 to zero and increase VR2 until D1 just fails to light. A sharp snap of the fingers causes it to light. S2, R3 and C2 may be omitted if not required.

The output from IC1 via R4 and Q1 activates the read relay, used for its simplicity and speed of action. The relay itself is connected across the flash sync leads.

The unit maybe battery powered e.g. PP3, as it consumes a mere 15mA or so.

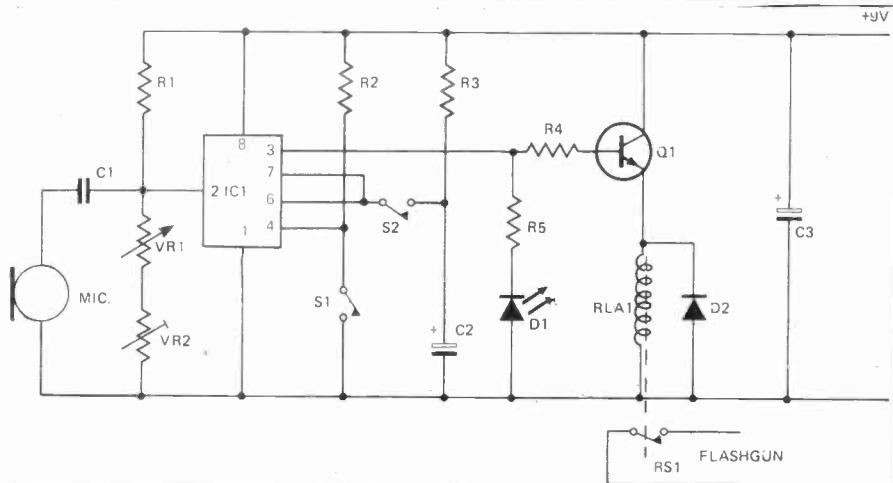The circuit has been built as the result of many modifications to other circuits. I find it an interesting toy and in its simplicity, should cost less than £2.



COMPONENTS * (see text)

Resistors		Capacitors	
R1	330kΩ	C1	10nF
R2	22kΩ	C2	4.7μF, 10V*
R3	1MΩ	C3	100μF, 10V
R4	4k7Ω	MISC.	crystal mike insert
R5	560Ω	S1	push to make switch
Potentiometers		S2	spst switch
VR1	50kΩ lin	RLA1	reed relay coil
VR2	250kΩ preset	RS1	normally open reed switch
Semiconductors			
IC1	NE555		
Q1	BC108		
D1	TIL209 LED		
D2	1N914		

OP AMP CHECKER


This circuit allows a quick and accurate GO/NO GO test to be made on 741 op-amps.

A 1kHz square wave is generated by the astable multivibrator Q1 and Q2 and the associated components R1-R4 and C1-2. This is fed into pin 3 of a standard 8 pin DIL or TO99 IC socket.

Assuming a working IC has been inserted this signal will enter its non-inverting input and appear amplified at the output, pin 6.

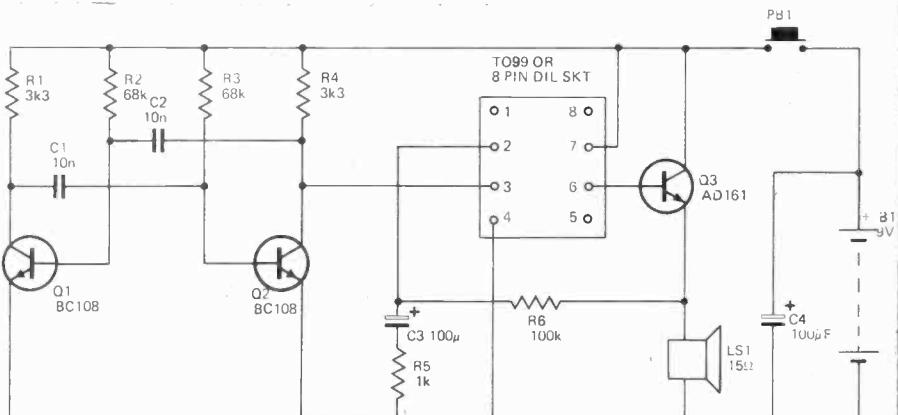Q3, an inexpensive germanium power transistor is connected as a class A output stage whose load is a 15Ω speaker.

R5 and R6 form the feedback loop to the inverting input whilst C3



isolates this pin from ground.

The battery employed should be a large type and periodic checking of its voltage must be made since a 741 will not work below 6V.

On pushing the test button a good IC will produce a loud note from the speaker. A faulty one will produce little or no output and should be discarded.

IDENTIFYING SURPLUS IC's

In checking unmarked surplus IC's, a clue can be gained as to the identity of the IC if the ground pin can be located first. In epoxy encapsulated IC's, the truncated part of the lead frame can be seen at both ends, perhaps partially covered by moulding

flash. This is generally connected to the substrate. In TTL and most linear IC's, this is the most negative pin (ground). In PMOS (clock and calculator chips) this is V_{ss}, the most positive pin. An ohmmeter can find which pin is connected to the substrate by touching one probe to the

frame and the other to each pin in turn.

Another clue to whether the IC is linear or digital is the fact that most digital IC's have diode protection against reverse bias at inputs. Knowing the ground pin, this can be checked rapidly.

TELETYPE 28 — for £20 only

Must go due to lack of space
Information supplied. Carriage £2.50 VAT 8%

SELECTION OF STABILIZED POWER UNITS

Solartron 0-12V 1amp £7.
Solartron 12-2V 1amp £12.
Solartron 1.5-13.5V 1amp £8.
Roband 21-27V 3amp £10.
Roband 9-12V 5amp £10.

Coutant 35V 2amp £16.
Coutant 28V 2amp £14.
Roband 4-14V 3amp £8.
Coutant + and - 10-12V 3amp twice £22.

Venner 10V 1amp £6.
APT 12-15V 2amp £15.
APT 22-27V 3amp £10.
Farnell 0-12V 2amp £8.
Coutant 20V 2amp £12.

BUNKER-RAMO 240V input
Outputs + 12V 5amp
minus 3.8V 25amp
minus 24V 25amp
Price £45 each

ALWAYS A LARGE QUANTITY OF TEST EQUIPMENT, SPECIALISED UNITS, CHASSIS, ETC. CALL AND SEE

Ex-Ministry Pye Receiver R3129 £6 ea.
Ex-Ministry VHF Receiver R7303 Multichannel £8 ea.
Ex-Ministry STC HF Receiver Units with Plug-in coils £7 ea.
Ex-Ministry Marconi Radio Jammer type HG10. Battery operated £12.
Multi Range Millivoltmeter by Airmec. Sensitivity down to 10mV full scale. £7 ea.
Marconi Sensitive Valvevoltmeter TF1100 £12 ea.
Rohde & Schwarz 10-280MHZ High Gain Wide Band Amplifier £15 ea.

Marconi Calibrator Scopes etc TF345 £15 ea.
Pulse & Bar TV Waveform Generator £15.
Airmec Counter 6 digit. Standard 240V input. Large bright display £12 ea.
Airmec Crystal Oscillator 100KHZ, 1MHZ. Crystal Oven, Standard mains £15 ea.
Furzehill Valve voltmeter V200. 10mv to 1000V full-scale Volts & db scale £18 ea.

FHACHI RAMP MODULE FX21.
24 Volt DC input for 18 volt saw tooth output. Requires only external capacitor and 100K ohm potentiometer to control frequency range up to 100KHZ (eg 50 mfd electrolytic gives sweep of approx 1 cm per second). In or out sync capability. Price £5.75. P&P. 20p.

FHACHI VCO MODULE FX11 — 10HZ-100KHZ. Size 2 x 1½ x ¾". H. Input 12V to 24V DC (not centre tapped). 18V input giving 10V constant amplitude output. Requires only 1 meg ohm potentiometer to tune entire range — or can be swept with a saw tooth input. Price £5.75. P.P. 20p.

TYPICAL of our LISTED ITEMS—now going out in all parcels or S.A.E.
Item 47 IMHOFF Cabinet handles with Pivoting recessed Handle. Brand new £1 per pair P&P 40p.

Item 49 DIVIDER UNIT T4517 100KHZ input — 100KHZ, 10KHZ, 1KHZ output 18-24V DC £6 ea.
Item 50 Gallender-Griffiths Bridge type 2146 £7.

Item 56 RELEAS-O-MATIC Balance by Oertling. Needs attention but worthwhile. £15.

Item 61 ROHDE & SCHWARZ MULTI COUPLER 29-68MHZ £7.
Item 63 AIRMEC TELEVENT 877 £12.
Item 79 HEWLETT PACKARD LOW FREQUENCY OSCILLATOR £15.

GRATICULES. 12 cm. by cm. in High Quality plastic. 15p each. P & P 8p.

*Beehive Trimmer 3/30 pf
Brand new. Qty. 1-9 13p ea P & P 15p
10-99 10p ea P & P 25p. 100-999 7p ea
P & P free.

HIGH-VALUE — PRINTED BOARD PACK.
Hundreds of components, transistors, etc.—no two boards the same—no short-leaded transistor computer boards £1.75 post paid

* TELEPHONES

MODERN STYLE 706 BLACK OR TWO-TONE GREY £3.75 each P & P 45p HANDSETS — complete with 2 inserts and lead. £1.25 each. P & P 37p DIALS ONLY 50p each P & P 25p.

MODERN STANDARD TELEPHONES IN GREY OR BLACK WITH A PLACE TO PUT YOUR FINGERS LIKE THE 746. £3.00 each P & P 45p.
As above but discoloured. Grey only. £2 ea P & P 45p

*1000pf FEED THRU CAPACITORS. Only sold in packs of 10-30p P & P. 15p

P.C.B. PACK S & D. Quantity 2 sq. ft.—no tiny pieces. 50p plus P & P 20p

*METERPACKS — 3 different meters for £2. P & P 55p.

*CAPACITOR PACK 50 Brand new components, only 50p. P & P. 27p.

FANTASTIC VALUE
Miniature Transformer. Standard 240V input. 3Volt 1amp output. Brand new 65p each P & P 20p Discount for quantity

RESETTABLE COUNTERS — 4 digit by Stonebridge/Sodaco. 1000ohm coil. £2 ea P & P 35p.

FIBRE GLASS PRINTED CIRCUIT BOARD.
Brand new. Single or Double sided. Any size 1½p per sq in Postage 20p per order.

**DON'T FORGET
YOUR MANUALS
S.A.E. WITH
REQUIREMENTS**

LOW FREQUENCY ANALYSER

50Hz—50kHz
ASSEMBLY AND INSTRUCTION INFORMATION S.A.E.
PRICE £27. P. & P. 75p
Board, modules and all components (excluding 24V.P.U.)

EX-MINISTRY. CT436. Double Beam Oscilloscope DC-6 megs. Max Sensitivity 10mv/cm. Small compact. Size 10x10x16 in. Suitable for Colour TV servicing. Price £95 each including copy of manual.

**SOLARTRON OSCILLOSCOPE
TYPE CT316.** DC — 6 mc/s. Size 8½" x 11" x 20". Very fine condition in Ministry transit cases. Complete with copy of manual. £45 each.

20HZ to 200KHZ

SINE AND SQUARE WAVE GENERATOR

In four ranges. Wien bridge oscillator thermistor stabilised. Separate independent sine and square wave amplitude controls. 3V max sine, 6V max square outputs. Completely assembled P.C. Board, ready to use. 9 to 12V supply required. £8.85 each. P. & P. 35p. Sine Wave only £6.85 each. P. & P. 35p.

WIDE RANGE WOBBLULATOR

5 MHZ to 150 MHZ (Useful harmonics up to 1.5 GHZ) up to 15 MHZ sweep width. Only 3 controls preset RF level sweepwidth and frequency. Ideal for 10.7 or TV IF alignment filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6.3V AC and use within minutes of receiving. All this for only £6.75. P. & P. 35p (Not cased, not calibrated.)

TRANSISTOR INVERTOR TYPE B

Input 12V DC Output 1.3kV DC 1.5mA. Price £4.70 P. & P. 36p. Other types as previously advertised still available. Other combinations possible S.A.E. with your requirements. No telephone calls.

LOW FREQUENCY WOBBLULATOR

Align receivers, filters, etc. 250KHZ to 5MHz effective to 30MHz on harmonics. Order as LX63. Price £8.50 P. & P. 35p. LX63E extends down to 20KHZ with external capacitors. Price £11.50 P. & P. 35p. Use with GP Scope. Requires 6.3V AC input. Automatic 50Hz sweeping. (Not cased, not calibrated.)

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH.

2 Hz to 8 MHz. Hook up a 9 volt battery and connect your scope and have two traces for ONLY £6.25. P. & P. 25p.
STILL AVAILABLE our 20 MHz version at £9.75. P. & P. 25p.

Unless stated — please add £2.50 carriage to all units

VALUE ADDED TAX not included in prices — Goods marked with * 25% VAT, otherwise 8%
Official Orders Welcomed, Gov./Educational Depts., Authorities, etc., otherwise Cash with Order

Open 9 a.m. to 5.30 p.m., Mon. to Sat.



CHILTMED LTD



7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College, King's Road). Tel.: Reading 582605

tech-tips

STABILISED BENCH POWER SUPPLY

The heart of this voltage stabiliser is a 741 op amp which is used as a non-inverting amplifier.

A novel feature is that the input reference voltage ZD1 is contained within the feedback loop of the amplifier. This produces an extremely stable output which can be varied merely by altering the values of R4 and R2.


An economical, high performance supply can be built using this circuit and the accompanying table.

Briefly the supply works as follows. The reference voltage across ZD1 is directly coupled into the non-inverting input (pin 3) of the IC. After amplification the output from the IC is coupled into the power Darlington consisting of Q1 and Q2 connected in the emitter follower mode. This ensures that a low output impedance, less than 1Ω , is presented to the load.

R4 provides current for the zener diode from the stabilised output thus placing the reference voltage in the feedback loop. Overload protection is provided by Q3 and R5. When current exceeds a level determined by R5, Q3 turns hard on earthing pin 3 of the IC. This has the effect of turning it hard off.

The output voltage is defined by the ratio of R2 to R1. For simplicity R1 is kept constant and the value of R2, R4 and R5 can be obtained from the table to suit various output volt-

Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items. ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS Electronics Today International, 36 Ebury Street, London SW1W 0LW.

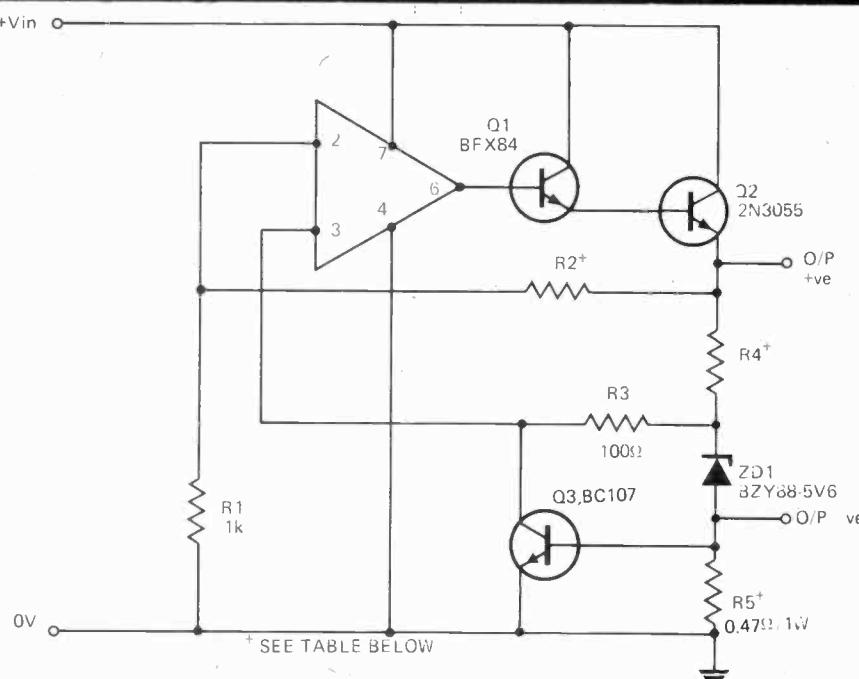

Vout	R2	R4	VIN
6V	68Ω	82Ω	
7.5V	330Ω	390Ω	12V DC
9V	620Ω	680Ω	
12V	1k2	1k2	20V DC
15V		1k8	
18V	2k2	2k2	30V DC
24V	3k3	3k9	

I LIMIT	R5
1.1A	0.47Ω
650mA	1Ω
325mA	2.2Ω
100mA	6.8Ω

ages and current limits.

Construction is not critical and as long as the usual precautions of keeping the output away from the input is observed no trouble should

be experienced.


A point to watch however, is to fit Q2 to an adequate heatsink since it may be called upon to dissipate several watts.

AUTOMATION FOR REAR WIPERS

Many estate cars are now fitted with rear washer/wiper sets without any sort of automation. This circuit provides an end-of-cycle stop, a delay of 1 minute, 4 minutes, or continuous

operation, and, from RLA2, a measured squirt of water at the start of each cycle. The circuit has been slightly modified to use a standard auto 3-way toggle, on which the first pole has no connection. One of the

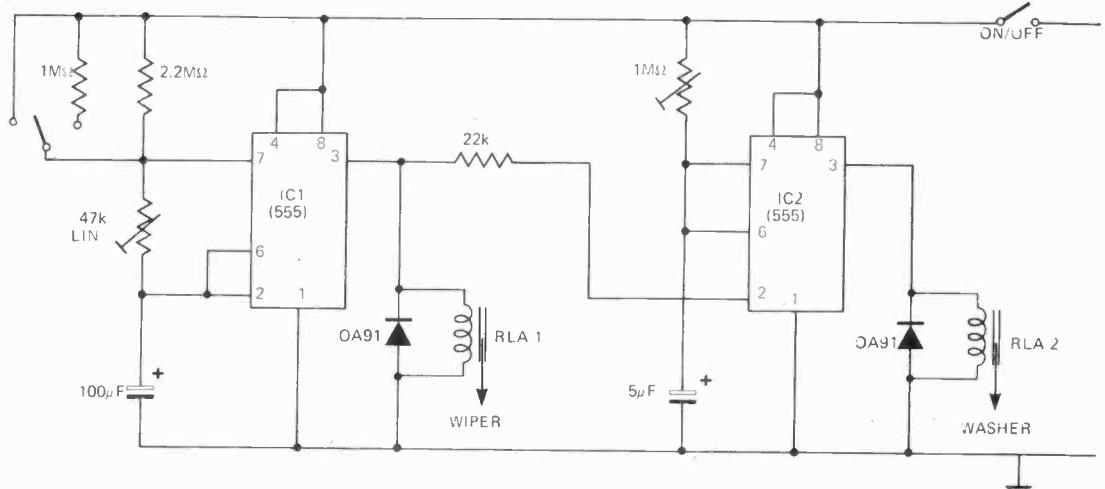many published spike suppression circuits should be used to protect the IC's. The circuit uses no more switches than manual control and requires less concentration from the driver.



BUILD THE
TREASURE TRACER
MK III
 METAL LOCATOR



AS SEEN
 ON BBC-1
 & BBC-2
 TV

- Genuine 5 silicon transistor circuit, does not need a transistor radio to operate.
- Incorporates unique varicap tuning for extra stability.
- Search head fitted with Faraday screen to eliminate capacitive effects.
- Loudspeaker or earphone operation (both supplied).
- Britain's best selling metal locator kit. 4,000 already sold.
- Kit can be built in two hours using only soldering iron, screwdriver, pliers and side-cutters.
- Excellent sensitivity and stability.
- Kit absolutely complete including drilled, tinned, fibreglass p.c. board with components siting printed on.
- Complete after sales service.
- Weighs only 22oz; handle knocks down to 17" for transport.

Send stamped, self-addressed envelope for literature.

Complete kit with pre-built search coil **£12.50**
 Plus 85p P & P
 Plus £1.00 VAT (8%)

Built, tested and Guaranteed **£17.50**
 Plus 85p P & P
 Plus £1.40 VAT (8%)

MINIKITS ELECTRONICS,
 6d Cleveland Road, South Woodford,
 LONDON E18 2AN
 (Mail order only)

Wilmslow Audio

*THE firm
 for
 speakers!*



Baker Group 25, 3, 8, or 15 ohm	£8.64
Baker Group 35, 3, 8 or 15 ohm	£10.25
Baker Deluxe, 8 or 15 ohm	£13.75
Baker Major, 3, 8 or 15 ohm	£11.87
Baker Regent, 8 or 15 ohm	£10.00
Baker Superb, 8 or 15 ohm	£18.12
Celestion MH 1000 horn, 8 or 15 ohm	£13.50
EMI 2 1/4" tweeter 8 ohm	£0.77
EMI 8 x 5, 10 watt, d/c, roll/s 8 ohm	£3.95
Eiac 59RM 109, 15 ohm, 59RM114 8 ohm	£3.44
Eiac 6 1/2" d/c roll/s 8 ohm	£4.06
Eiac TW4 4" tweeter	£1.75
Fane Pop 15 watt 12" 8 or 16 ohm	£5.25
Fane Pop 55, 12", 60 watt 8 or 16 ohm	£15.50
Fane Pop 60 watt, 15" 8 or 16 ohm	£17.25
Fane Pop 70 watt 15", 8 or 16 ohm	£18.75
Fane Pop 100 watt, 18" 8 or 16 ohm	£25.95
Fane Crescendo 12A or B, 8 or 15 ohm	£34.50
Fane Crescendo 15, 8 or 15 ohm	£47.50
Fane Crescendo 18, 8 or 15 ohm	£62.95
Fane 807T 8" d/c, rolls/s, 8 or 15 ohm	£5.75
Fane 801T 8" d/c roll/s 8 ohm	£9.95
Goodmans 8P 8 or 15 ohm	£5.95
Goodmans 10P 8 or 15 ohm	£6.25
Goodmans 12P 8 or 15 ohm	£13.95
Goodmans 12P-D 8 or 15 ohms	£16.95
Goodmans 12P-G 8 or 15 ohms	£15.95
Goodmans Audition 200, 8 ohm	£13.90
Goodmans Axent 100, 8 ohm	£8.44
Goodmans Axiom 402, 8 or 15 ohm	£20.00
Goodmans Twinaxiom 8" 8 or 15 ohm	£10.55
Goodmans Twinaxiom 10" 8 or 15 ohm	£10.95
Kef T27	£6.06
Kef T15	£6.94
Kef B110	£8.37
Kef B200	£9.50
Kef B139	£16.95
Kef DN8	£2.31
Kef DN12	£5.99
Kef DN13	£4.50
Richard Allan CG8T 8" d/c roll/s	£8.50
STC 400 1 G super tweeter	£6.56
Baker Major Module, each	£14.75
Goodmans Mezzo Twinkit, pair	£14.75
Goodmans DIN 20, 4 ohm, each	£14.75
Helme XLK30, pair	£19.00
Helme XLK 33, pair	£24.00
Helme XLK 40, pair	£35.00
Helme XLK50, pair	£56.00
Helme XLK 60, pair	£56.00
Kefit 1, pair	£33.00
Kefit III, each	£48.00
Peerless 3/15 (3 sp. system) each	£17.19
Richard Allan Twinkit, each	£14.95
Richard Allan Triple 8, each	£22.50
Richard Allan Triple, each	£27.95
Richard Allan Super Triple, each	£32.50
Wharfedale Linton 2 kit (pair)	£23.12
Wharfedale Glendale 3 XP kit, pair	£58.00
Wharfedale Dovedale 3 kit, pair	£63.12
Wharfedale Super 10 RS/DD	£15.00
Castle Super 8 RS/DD	£10.31
Jordan Watts Module 4, 8 or 15 ohm	£17.06
Tannoy 10" Monitor HPD	£75.00
Tannoy 12" Monitor HPD	£81.95
Tannoy 15" Monitor HPD	£97.95

Prices correct at 6.2.76

INCLUDING VAT AT 25% ON HI-FI
 8% ON PRO AND PA

Cabinets for PA and HiFi, wadding, Vynair, etc.
 Send stamp for free booklet "Choosing a Speaker"

FREE with all orders over £10 — "HiFi
 Loudspeaker Enclosures" Book

All units are guaranteed new and perfect

Prompt despatch

Carriage, Speakers 50p each, 12" and up 75p each,
 tweeters and crossovers 30p each, kits 80p each (£1.60
 pair)

WILMSLOW AUDIO

Dept. ETI

Swan Works, Bank Square, Wilmslow,
 Cheshire SK9 1HF. Tel. Wilmslow 29599
 (Discount HiFi, PA and Radio at
 10 Swan Street, Wilmslow)

WOULD
 YOU LIKE
 IT ON YOUR
 DOORMAT
 EVERY MONTH?

electronics today international APRIL 1976 30p
 SOUTH AFRICA CANADA

Convert your calculator to a STOPWATCH

MICROPROCESSORS how the chip works
 CA3130—extra data
 NOISE GENERATOR
 AUDIO MILLIVOLTMETER
 5V POWER SUPPLY

SPACE ENVIRONMENT

NEWS CONSTRUCTION DEVELOPMENTS AUDIO

Our sales have gone up by 34% in the past year or so, but still some people are having trouble getting hold of ETI. If you're not sure of getting yours easily, why not take out a subscription? Twelve issues dropped through your door every month by the friendly neighbourhood postman.

To ensure a regular flow of our amazing articles, pulsating projects and nubile news just fill in the coupon below. We will do the rest!

Cut

ETI Subs, Electronics Today,
 36 Ebury Street, London SW1W
 OLW.

I enclose £5.00 (£5.50 overseas
 subscriptions except Canada: \$10) for
 the next twelve issues of ETI.

Please start with
 the issue.

Please tick if this is a renewal

Name

Address

CHIP SHORTAGE



A new slant on the potato shortage from CBM. This is their new calculator IC, which contains ALL the circuiting for an 8-digit machine with memory including the digit drivers. This makes the case look somewhat deserted on the inside!

SURROUND SOUND OF CONCORDE

British Airways has fitted a distinctly different headphone 'stereo' entertainment to its supercraft. This is based on a 'dummy head' recording system which simulates a sound field much more accurately than conventional stereo. This was specially recorded for B.A. by Emison, and includes some Concorde propaganda of course, by Michael Bentine Esq. The only trouble is that the stethoscope headphones in use do not have channels marked on them, and correct orientation is vital to the creation of a binaural field. So many people will completely miss the point of the whole show. Next time you're in Concorde take note.

BOXING CLEVER

Wembley Stadium have ordered the world's biggest computerised box office accounting system. It will be used for events held in the Empire Pool, in the theatre of the newly-built Conference Centre and selected events in the main Wembley Stadium and the Squash Centre.

The system is based on a 64 kilobyte GEC 2050 computer. Two 4.8 + 4.8Mbyte fixed/exchangeable cartridge disc units for database storage and a thermal printer are included in the configuration. The value of the order is in excess of £100,000.

WANNA BUY A DIRTY CRYSTAL?

It seems that as demand for digital watches increases to ever greater heights, the supply for crystals are failing to keep pace. This has gotten to such a state that a black market is now thriving!

Companies are believed to be 'double ordering' to ensure their supplies thus worsening the situation still further. The black marketing, especially on low-grade quartz (what else?), is freely admitted by suppliers. However nobody knows exactly who is selling what to whom and when. Perhaps the CIA are in need of a crystal division.

NEW SPEAKER IN THE HOUSE

Ever been to Luton? A few of us brave men of the press gathered our courage about us to do so recently at the invitation of Acoustic Research, much as it seems that Luton is the last place to launch a new range of loudspeakers.



The whims of manufacturers wax strange indeed at times.

Acoustic Research are an offshoot of the American giant, although they have been left to themselves in developing this new range. Their latest brood is designated "Advanced Development Division", and is based on the AR 10π and AR 11 speakers.

The major innovation incorporated in these speakers is a magnetic fluid, employed as a filler in the gap between coil and magnet assembly. Claimed advantages are greatly increased heat dissipation, and a self-centering effect generated on the coil. A very high local magnetic field is generated around the coil by the technique, which is said to improve linearity of the motor system. Because of the fluid, the inner suspension, or

spider, can be dispensed with, without impairing the cone behaviour under drive. The new midrange unit used in some of the ADD speakers takes advantage of this.

ADD price list


	PRICE
	inc VAT
AR-10π	per pair 432.50
AR-11	" "
AR-12	" "
AR-14	" "
AR-16	" "
AR-7X	81.25

Due to the increased heat dissipation the new models show an improved power handling capability over their ancestors. They also deliver a better transient response and the smaller models offer very good value for money.

With Hi-Fi 76 now looming ever larger on the horizon, why did not AR release the range there where it could be judged directly against its peers? Another nail in the exhibition worlds coffin.

AUTO IC TESTER

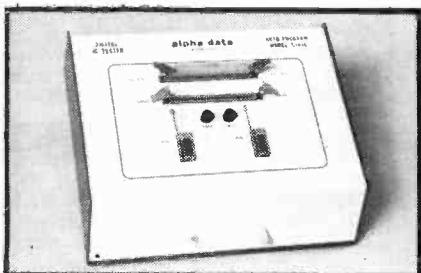The Alpha C1416 can test up to 500 devices per hour and is designed to test virtually all types of digital CMOS, TTL and DTL circuits. Insertion of a standard IC into the comparison socket accomplishes internal self programming, thus obviating the usual need for manual programming by skilled technicians.



Plug in cards provide +5V power and ground to the appropriate device pins. The remaining pins are driven HI or LO from individual test circuits incorporating specially designed current limiters. Should the driver be applied to a device "output" the output state will be unaffected because of the current limiter.

In a 14 pin IC 12 drivers are connected to the 12 logic lines of the device and 12^{1/2} logic states are successively applied to both the comparison device and the unit under test. Test time required is approximately 1 second, and green and red lights indicate pass or fail for the IC. Details from Telonic Altair U.K. 2 Castle Hill Terrace, Maidenhead, Berks SL6 4JR.

New Course in Digital Design

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation . . .

Each of the 6 volumes of this self-instruction course measures 11 $\frac{3}{4}$ " x 8 $\frac{1}{4}$ " and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

After completing this course you will have broadened your career prospects and considerably increased your fundamental understanding of the changing technological world around you.



£3.95 plus 50p p&p

Design of Digital Systems contains over twice as much information in each volume as the simpler course. Digital Computer Logic and Electronics. All the information in the simpler course is covered as part of the first volumes of Design of Digital Systems which, as you can see from its contents, also covers many more advanced topics.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee - no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

Design of Digital Systems

A Self-Instruction Course in 6 Volumes

- 1 Computer Arithmetic**
- 2 Boolean Logic**
- 3 Arithmetic Circuits**
- 4 Memories & Counters**
- 5 Calculator Design**
- 6 Computer Architecture**



£5.95

plus 50p packing and surface post anywhere in the world (VAT zero rated). Payments may be made in foreign currencies. Quantity discounts are available on request.

To: Cambridge Learning Enterprises,
FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR

*Please send me set(s) of Design of Digital Systems at £6.45 each, p&p included

*or set(s) of Digital Computer Logic and Electronics at £4.45 each, p&p included

*or combined set(s) at £9.75 each, p&p included

Name.....

Address.....

.....

*delete as applicable.
No need to use a stamp—just print FREEPOST on the envelope.

ETI 4

MINI-ADS

FOR DETAILS ON ADVERTISING IN
MINIADS, OR ELSEWHERE IN ETI,
CONTACT BOB EVANS, 01-730 8282

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections, Printed circuit boards, top quality for individual designs.

Popular E.T.I. boards always in stock. Prompt service.

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES

MASONS ROAD
STRATFORD-ON-AVON
WARWICKS. Tel. 4879

ELECTRONIC COMPONENTS, CHORLEY

164-166 LYONS LANE, CHORLEY, LANCS.
PR6 0PJ

BARGAINS

New Carbon Film Resistors 200 for £1
Min. Continental Relays 6-12v
2 & 4 pole Change-over, 24v Each 55p

TRANSISTORS

All Brand New Full Spec.

R.C.A. 2N3055 — @ 43p
P.N.P. 2N3055 — @ 53p
BC108 — @ 10p
BFY51 — @ 16p
F.E.T. 2N3819 — @ 18p
BC184 — @ 10p

ELECTROLYTIC CAPS
4.7μF 63v-8p 33μF 40v-12p
10μF 63v-8p 47μF 40v-15p
15μF 63v-9p 47μF 40v-15p
22μF 25v-10p 50μF 40v-15p. 40v-15p. etc.

Very Special Offer 1000μF Can/50v @ 50p
PRICES INCLUDE VAT
Many other bargains. Catalogues 20p
Same Day Despatch
Please include P.P. 20p on each complete order

PRECISION POLYCARBONATE CAPACITORS

All High Stability — Extremely Low Leakage

VALUE	(mm)	PRICE	PRICE	RANGE	%	%	%
0.1μF	12	12p	0.47μF	67p	50p	43p	
0.22μF	33	16p	1.0μF	82p	62p	52p	
0.25μF	33	16p	2.2μF	96p	75p	61p	
0.47μF	33	19p	4.7μF	£1.62	£1.13	94p	
0.5μF	33	19p	8.7μF	£1.96	£1.38	£1.13	
0.68μF	33	19p	10μF	£2.40	£1.95	£1.64	
1.0μF	50.8	19p	15μF	£3.22	£2.79	£2.24	
2.0μF	50.8	25p	22μF	£4.28	£3.68	£3.08	

*TANTALUM BEAD CAPACITORS — Values available: 0.1, 0.2, 0.22, 0.47, 0.68, 1.0μF at 15V / 25V or 35V; 10μF at 16V / 20V, or 25V; 22μF at 6V or 16V; 33μF at 6V or 10V; 47μF at 3V or 6V; 100μF at 3V. ALL at 10p each, 10 for 50, 50 for 4.

TRANSISTORS & I.C.'s	AC128	BC268A/384* 10p	OC71	12p
AC176	14p	*BC547/558A 12p	*2N2926G 11p	
AD149	40p	BCV72 12p	*2N2930 11p	
AFT15	30p	BD131/132 22p	*2N2928Y 11p	
AF209	30p	BF115/167 22p	2N3054 50p	
BC115/7/8/9	9p	BF173 24p	2N3055 50p	
BC114	12p	BF178 26p	2N3702/7 12p	
BC147/8/9/10	12p	BF184 22p	2N3702/7 12p	
BC153/154	12p	BF194/195* 12p	2N3702/7 12p	
BC157/8/9	12p	*BF196/197* 12p	2N3702/7 12p	
BC177	16p	BF200 27p	2N3702/7 12p	
BC182/183L	11p	BF205 27p	2N3702/7 12p	
BC183/183L	11p	BFY50/51 25p	2N3702/7 12p	
BC184/184L	12p	BFY84/86/88 20p	NE555 61p	
BC212/212L	11p	BFY85 26p	741C 32p	
BC213/213L	11p	BR101 41p	ZN414 £1.15	
BC214/214L	11p	GET872 25p	SN76013ND	
BC267	12p	OC44/OC45 14p	£1.50	

POPULAR DIODES — IN914 6p, 8 for 15p, 18 for 30p; IN916 8p, 6 for 45p, 14 for 90p; 1544 5p, 11 for 50p, 24 for £1.00; IN4148 5p, 6 for 27p, 12 for 48p; IN4001 54p; 002 6p; 003 6p; 004 7p; 006 8p; 007 8p.

LOW PRICE ZENER DIODES — 400MW. Tol. ±5% at 5mA. Values available: 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V. All at 7p each; 5 for 33p; 10 for 65p. SPECIAL OFFER 100 Zeners for £6.00.

*RESISTORS — High stability, low noise carbon film 5%. 1W at 40°C, 1/2W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK. 10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.

SILICON PLASTIC RECTIFIERS — 1.5 amp, brand new wire ended DO27, 100 P.I.V. 7p (for 26p), 400 P.I.V. 8p (for 30p).

BRIDGE RECTIFIERS — 2.5 amp, 200V 40p, 350V 45p, 600V 55p.

*SUBMINIATURE VERTICAL PRESETS — 0.1W only. ALL at 5p each: 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 88kΩ, 100Ω, 250kΩ, 680kΩ, 1MΩ, 2.5MΩ, 5MΩ.

PLEASE ADD 15p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF SEA/AIR MAIL.

PLEASE ADD 8% VAT to all items except those marked with * which are 25%.

Send S.A.E. for lists of additional ex-stock items
Wholesale price lists available to bona fide companies

MARCO TRADING (Dept. D3)

The Old School, Edstaston, Nr. Wem, Shropshire
Tel. Whixall (Shropshire) (STD 094872) 464/5
(Props: Mini-cost Trading Ltd.)

THE SCIENTIFIC WIRE CO.

Copper - Nickel Chrome - Eureka - Manganin Wires

Enamelled - Silk - Cotton - Tinned Coverings

No minimum charges or quantities
Trade and Export enquiries welcome
S.A.E. Brings List

P.O. BOX 30, LONDON, E4 9BW

LED s	0 125	0 2	INFRA RED
RED	16p	18p	550μW
G/Y	27p	33p	Axial lead 49p
OR	27p	33p	1.5mW £1.10

OPTO-ISOLATORS	SCRs	50V 100V	400V
IL4 1.5kV, 150kHz £1	T051A	25p	27p
4350 2.5kV 5MHz £2.25	T066 3A	27p	35p

TRIAC T05 2A 400V 60p

Data free with all OPTO

AC125/6/7/8/15p	2N2926(G)	12p	VOLTAGE REGS.
AD161/162 40p	2N3053	15p	5V 7805 Plastic
AFT117	20p	2N3054	12V 7812 1 Amp
AF124/5/6/7	34p	2N3055	15V 7815 all
BC107/8/9 9p	2N3702/3/4 12p	18V 7818 £1.50	
BC109C	12p	2N3903/4 5/6	723 DIP14 50p

16p BRIDGE RECTS.

2.33V 9p ZENERS BYZ88

2.33V

CAR IGNITION TRANSFORMERS

If you're thinking of building your own capacitor-discharge ignition system why not use one of our quality ignition transformers?

This unit, with tag connections and two-hole clamp fixings, may be used in the ETI circuit or in the up-to-date thyristor circuit we supply FREE with every transformer.

Total inclusive price: £1.95p.

ORDERS TO:

PADEC COMPONENTS
P.O. BOX 71
SOUTHEND-ON-SEA
ESSEX SS2 5DZ

Treasure Locator Kits by:
DETECTOR PRODUCTS

Suppliers to the UK & Abroad
Circuits & Instructions £2
Complete Kit £12
Total £14 incl. VAT p&p

Solid aluminium frame with an efficient Faraday screen. For enquiries please send s.a.e. to:

DETECTOR PRODUCTS
58a King Street, Blackburn, Lancs.
Tel. 62561 or 54105

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact **COLES-HARDING & CO.**, P.O. Box 5, Frome, Somerset. Immediate settlement.

CJL

CJL LTD. P.O. BOX 34, CANTERBURY, CT11YT

ALL PRICES INCLUDE P&P AND V.A.T.

ANTEX SOLDERING IRONS

(with slide on & off bits)	£2.30
15W 'C' miniature irons	£0.45
3/32", 1/8", 3/16" bits-each	
'C' Elements	£1.10
16W 'G' miniature irons	£0.45
3/32", 1/8", 3/16" bits-each	
'G' Elements	£1.35
15W CCN Low leakage irons	£2.70
3/32", 1/8", 3/16" bits-each	
'CCN' Elements	£1.50
25W X25 Low leakage irons	£2.30
3/32", 1/8", 3/16" bits-each	
'X25' Elements	£0.47
'SK1', 'SK2', Soldering Kits	£1.15
	£3.85

ST3 Stands-for all models £1.10

SOLDER In Bib dispenser £0.45

WIRE STRIPPER & CUTTER £0.85

HAND DRILLS Leytool precision,

compact, 5/16" chuck £3.99

AERIALS Extend 15-120cm £1.50

CASSETTE 'Head Demagnetisers'

Shaped pole-saves time £3.65

EARPHONES Stethoscope £1.25

MICROPHONES Dynamic £2.15

PRINTED CIRCUIT KITS-All

items for producing p.c.'s £3.99

SIGNAL INJECTOR-Audio through

video signals, self contained £4.25

SPEAKERS -75mm dia. 8A £1.00

Greenbank Electronics

FREE!

Data and suggested circuits for AY-5-1224 and MK 50253 clock chips, details of PCB's and component kits for AY-5-1224, data sheets for LED 0.3" and 0.6" displays.

NEW!

PCB TO SUIT AY-5-1224 clock chip 95p

4 DIGIT KITS

Kit includes: PCB, AY-5-1224 chip, 4 LED digits, transistors, diodes, resistors, capacitors, solder pins (success guaranteed), with 0.3" digits £9.95 (0.6" high digit version also available).

CLOCK CHIPS

AY-5-1224 4 digit 12/24 hour £3.66

MK 50253 4/6 digit alarm clock £5.50

LED DISPLAYS (ECONOMY TYPES)

DL-704E 0.3" common cathode 85p

DL-747E 0.6" common anode £1.70

Add 8% VAT to all prices, post, etc. 10p + VAT per order

GREENBANK ELECTRONICS (Dept. T12E)

94 New Chester Road, New Ferry

Wirral, Merseyside L62 5AG

Tel: 051-645 3391

START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS

This unique instruction manual shows step by step how to rewind motors, working part- or full-time, without previous experience. Everything you need to know easily explained, including where to obtain materials, how to get all the work you need, etc.. etc.

A goldmine of information and knowledge. Only £3.65 + 25p P&P from Magnum Publications, Dept. ET5, Brinksway Trading Estate, Brinksway, Stockport, SK3 0BZ. Overseas Distributors wanted.

AUDIO-OPTICS Audio-Visual Equipment Sales and Installations

Reg. No. 1858305

J. R. WHYTE

Public Address System Hire

Audio Equipment Serviced

Kingston Blount, 19 Middle Way, Chinnor, Oxon.

Tel: 52683

FULL SPEC. NEW DEVICES, BY RETURN

BC107	10p	ZTX504	25p	LEOS W/CLIP 0.125"
BC108	10p	2N3055	40p	TIL209 (Red)
BC109	10p	2N3819	39p	MV5174 (Orange)
BC182L	10p	IN914	4p	MV5274 (Green)
BC183L	10p	IN4148	4p	MV5374 (Yellow)
BC184L	10p	IN4002	4p	0.2" Red
BC212L	14p	IN4003	5p	REGULATORS TO-220
BC214L	14p	IN4007	9p	7805 (5V)
TIP29A	46p	3A/800V	15p	7812 (12V)
TIP30A	49p		15p	7824 (24V)
TIP31A	51p	1A/200V	26p	CAPACITORS
TIP32A	55p	2A/600V	33p	10mfd/12V
TIP34A	72p		33p	100mfd/6V
TIP42A	73p	OIL I.C. #	25p	VAT INC. P&P 20p
TIP295S	64p	741 8 pin	49p	LED Audio-Optics
TIP305S	49p	555 Timer	7-SEG.	7-SEG.
TIS430(U)	26p	DISPLAYS	19. Middleway	19. Middleway
ZTX300	15p		£1.15	Chinnor, Oxon
ZTX304	25p	0.5"	£1.49	Tel. Kingston Blount 52683.
ZTX500	15p	Display Data		S.A.E. Please

P.C.B.s and COMPONENTS FOR E.T.I. PROJECTS

P.C.B.s

Calculator Stopwatch

Audio Noise Generator

Audio Millivoltmeter

Switching Reg. Supply

Audio Level Meter

Active Crossover

Active Crossover

Logic Probe

Logic Pulser

Logic Tester

Tone Burst Generator

Exposure Meter

New projects available at £1.25 per sq. cm. for single sided board or 1.5p per sq. cm. for double sided (min. 35p)

All boards are Fibre Glass and price inc. drilling and tinning.

COMPONENTS

Resistors, 1/4w 5% (E12) 1.3p, 2% 4.3p.

Diodes, IN4002 5p, IN914 5p. L.E.D.'s TIL 209 16p (Red only).

Transistors, BC107, 8, 9, 10p, BC177, B, 9, 19p.

BD135 50p, BD136 50p, BD139 70p, BD140 76p.

OPR 12 L.D.R. 78p.

Min. Toggle Switch S.P.D.T. 70p, D.P.D.T. 95p. Min. Push Button Switch, push to make S.P. 50p, D.P. 75p.

All prices inc. VAT. Please add 15p postage on components. P.C.B.s post free. Send a s.a.e. for full list of boards and components.

Mail orders, please, to: **D.B.M. PRODUCTS**

Unit 14, Southern Road, Aylesbury, Bucks.

PLEASE MENTION ETI WHEN REPLYING TO ADVERTISEMENTS

Now there's a better way to keep your ETI copies



We reckon ETI is worth keeping: and our surveys indicate that a staggering 97% of readers keep their copies for at least three months. Now we can offer you a binder which holds 12 issues whose quality befits the magazine: excellent. Send £2.00 (which includes VAT and postage) to:

ETI BINDERS, 36 EBURY STREET, LONDON SW1W 0LW.

INDEX TO ADVERTISERS

Ambit	p.24
Andromeda	p.24
B.H. Components	Mini-ad
B.I.E.T.	p.17
Bi-Pak	pp.4, 5
Bi-Pre-Pak	p.83
Bywood	p.18
Cambridge Learning	p.79
Chiltmead	p.75
Chromasonics	p.55
Crofton	p.9
E.D.A.	p.9
Electrovalue	p.17
Fordendale	p.13
Greenbank	Mini-ad
Henry's	p.53
I.L.P. Electronics	p.2
Imtech Products	pp.73, 82
Island Devices	Mini-ad
Kinnie Components	p.36
Lee Instrumentation	p.61
Lynx Electronics	p.23
Maplin	p.84
Marco Trading	Mini-ad
Marshall's	p.28
Metac	p.53
Minikits	p.77
Pulse Electronics	Mini-ad
Ramar	Mini-ad
R.F. Equipment	
Spares	Mini-ad
Sabtronics	p.71
Sinclair	pp.34, 35
Sintel	pp.17, 44
Technomatic	p.36
Wilmslow Audio	p.77

Be an ETI Guy (or Gal)!



A couple of issues ago we announced the ETI T-Shirt—the response has been enormous. Made in cotton (yellow with black printing) these are available in three sizes suitable for both sexes.

Send your cheque and P.O. for £1.50 (payable to Electronics Today International) and state Small, Medium or Large. ETI T-SHIRTS, 36 EBUARY STREET, LONDON SW1W 0LW.

DIGITAL CLOCK

MATCHED CHIP & DISPLAY

DISPLAY

Only Price
£6.36


Inc. VAT

£9.56

Incl. VAT, Post & Packing

FUTABA 5-LT-01. 7 SEGMENT

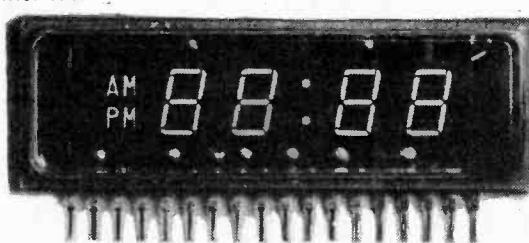Phosphor Diode. 12.5mm Digit
AM/PM and colon




CHIP

Only Price
£5.50

Inc. VAT

CALTEX CT7001. MOS LSI

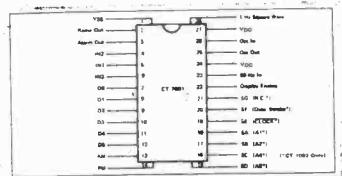28/30/31 Day Calendar
24-hour Clock
Snooze Alarm
Clock Radio Feature
Easily Settable Counters



TRANSFORMER — £2.50 INC. VAT

Payment with order

IMTECH PRODUCTS LTD.

IMP HOUSE, ASHFORD ROAD, ASHFORD, MIDDX.
Telephone: Ashford 44211
Telex: 936291

electronics today
international

reader services

SUBSCRIPTIONS

The annual subscription to ETI for UK readers is £5.00. The current rate for readers overseas is £5.50. Canadian subscription rate is \$10 per year. Send orders to ETI SUBS Dept. . .

BACK ISSUES

The cost of a back issue is 40p. Postage and packing costs an additional 15p for the first and 10p for each subsequent copy. Send orders to ETI BACK ISSUES Dept. . . We cannot supply certain back issues (April, May, June, July, November and December 1972; January, February and November 1973; March, September and November 1974; January, June, August, September and November 1975).

SPECIAL ISSUES

At present we have three Special Issues available: Top Projects 2, Electronics It's Easy (Parts 1 to 13), and International 4600 Synthesiser (published by Maplin). The prices are 75p, £1.20 and £1.50 respectively; postage and packing is an additional 15p per issue. Top Projects 1 is now sold out. Send orders to ETI SPECIALS Dept. . .

BINDERS

Binders, for up to 13 issues, are available for £2.00 including VAT and carriage. Send orders to ETI BINDERS DEPT. . .

T-SHIRTS

ETI T-shirts are available in Large, Medium, or Small sizes. They are yellow cotton with black printing and cost £1.50 each. Send orders to ETI T-SHIRTS Dept. . .

PCBs

PCBs are available for our projects from companies advertising in the magazine, such as Ramar and Crofton, who do an excellent service.

EDITORIAL QUERIES

Written queries can only be answered when accompanied by an SAE, and the reply can take up to three weeks. These must relate to recent articles and not involve ETI staff in any research. Mark your letter ETI QUERY . . . Telephone queries can only be answered when technical staff are free, and never before 4 pm.

NON-FUNCTIONING PROJECTS

We cannot solve the problems faced by individual readers building our projects unless they are concerning interpretation of our articles. When we know of any error we print a correction as soon as possible at the end of News Digest. Any useful addenda to a project will be similarly dealt with. We cannot advise readers on modifications to our projects.

BOOKS

ETI Book Service sells books to our readers by mail order. The prices advertised in the magazine include postage and packing. Send orders to ETI Book Service, 25 Court Close, Bray, Maidenhead, Berks.

MINI-ADS & CLASSIFIEDS

This is a pre-payment service — rates on application to ADVERTISING

ADDRESS FOR ETI DEPARTMENTS—

36 EBUARY ST, LONDON SW1W 0LW

PLEASE MARK REVERSE OF EACH CHEQUE
WITH NAME & ADDRESS AND ITEMS
REQUIRED.

ALLOW 10 TO 14 DAYS FOR DELIVERY



COMPLETE WITH
DISCOUNT
VOUCHERS
WORTH 20p

HAVE YOU
GOT YOURS?

CATALOGUE NO. 4
FULLY
ILLUSTRATED

- ★ DISCOUNTS
- ★ ALL NEW STOCK
- ★ SATISFACTION GUARANTEE
- ★ DEPENDABLE SERVICE

B H COMPONENT FACTORS LTD.

LEIGHTON ELECTRONICS CENTRE, 59 NORTH ST.,
LEIGHTON BUZZARD, BEDS. LU7 7EG. Tel. (05253) 2316.



Stirling Sound Products

FROM BI-PRE-PAK

BECAUSE OF DEMAND AND RE-ORGANISED PRODUCTION, THE SUPERB SS.125 HI-FIDELITY POWER AMP NOW COSTS £6.25 inc. Postage & VAT

OUTPUT

25 watts R.M.S. into 8Ω using 50V
22 watts R.M.S. into 4Ω using 33V
(Low imp. not less than 4Ω)

DISTORTION

Less than 0.05% at all power levels
(from 10Hz to 10kHz)

FREQUENCY RESPONSE

± 1dB 15 Hz to 30 KHz [4Ω]
± 1dB 10Hz to 30 KHz [8Ω]

HIGH Z INPUT

100 Kohms [40dB gain/100x]

INPUT SENSITIVITY


150mV for 25W.R.M.O. out

SIZE

[inc. heat-sink type mounting platform] 4½" x 3" x ¾" high (120 x 76 x 22 mm)

Not only is this Stirling Sound's best audio amplifier yet; it rightfully qualifies as one of the best of its kind yet made available to constructors. Intended above all for high-fidelity, the characteristics of the SS.125 are such that it can be used in many other applications where dependability is the prime consideration. The SS.125 integrates well with other S.S units as well as those of other manufacturers. Incorporates new circuitry using a complementary long-tailed pair input and full complementary output circuits to give standards of performance.

Designed and made for constructors who appreciate quality and value!

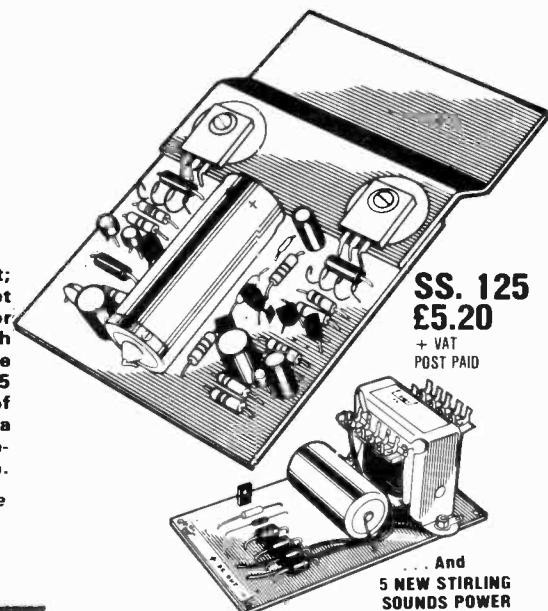

SS. 125
£5.20

+ VAT
POST PAID

... And
5 NEW STIRLING
SOUNDS POWER
SUPPLY UNITS

Robustly designed units in each of which is a stabilised take-off point to provide for tuner, pre-amp and control stages. Size — 5½" x 3" x 2½" high (P/P add 50p on any model)

SS 312	12V/1A	£3.75*
SS 318	18V/1A	£4.15*
SS 324	24V/1A	£4.60*
SS 334	34V/2A	£5.20*
SS 345	45V/4A	£6.25*

Transformers for SS334 and SS345 are supplied with transformers separate from PCBs. Add 50p for P/P any model

A new Stirling Sound C.D.I. Unit for your car. Super Shark Mk. 2

Even better than the original version, thousands of which are in use saving motorists appreciable time and money for petrol. Very easy to install. The Stirling Sound model incorporates switch for instant change to conventional ignition, instant adaption to pos or neg. earth return, anti-burglar immobilising switch, pre-set control for rev. limitation. There are no exposed parts, the unit, on p.c.b. being housed in strong enclosed metal box. With instructions and leads.

Size 7½" x 4¾" x 2½" ex. switches (193 x 117 x 54mm) (P/P add 50p)

BUILT &
KIT £7.95 TESTED £10.50

A NEW X-HATCH GENERATOR

Operates at R.F. level

For colour and mono TV Plugs into aerial socket of set. Operates without need for transmissions. 4 push-button operation. Runs on 4 self-contained penlite type batteries. Will fit into a large pocket. Strong plastic case.

BUILT £27.50* KIT £25*

A USEFUL CATALOGUE — FREE

Send us a large S.A.E. with 10p stamp and we will send you the latest Bi-Pre Pack catalogue free by return. Packed with useful info. It's a real money saver.

TO STIRLING SOUND (BI-PRE-PAK) LTD. 222 WEST ROAD. WESTCLIFF-ON-SEA. ESSEX SS0 9DF

Please send

Inc VAT

NAME

ADDRESS

for which I enclose £

(ETI 4)

Order your Stirling Sound products from

BI-PRE-PAK LTD

Co Reg No 820919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 9DF.
TELEPHONE: SOUTHEND (0702) 46344

FACTORY — SHOEBURYNESS, ESSEX

More than just a catalogue!

PROJECTS FOR YOU TO BUILD

4-digit clock, 6-digit clock, 10W high quality power amp., High quality stereo pre-amp., Stereo Tuner, F.M. Stereo decoder, etc., etc.

CIRCUITS ... Frequency Doublers, Oscillators, Timers, Voltmeters, Power Supplies, Amplifiers, Capacitance Multiplier, etc., etc. . . .

Full details and pictures of our wide range of components, e.g. capacitors, cases, knobs, veroboard, edge connectors, plugs and sockets, lamps and lampholders, audio leads, adaptor plugs, rotary and slide potentiometers, presets, relays, resistors (even 1% types!), switches, interlocking pushbutton switches, pot cores, transformers, cable and wire, panel meters, nuts and bolts, tools, organ components, keyboards, L.E.D.'s, 7-segment displays, heatsinks, transistors, diodes, integrated circuits, etc., etc., etc. . . .


Really good value for money at just 40p.




The 3600 SYNTHESISER

The 3600 synthesiser includes the most popular features of the 4600 model, but is simpler. Faster to operate, it has a switch patching system rather than the matrix patchboard of the larger unit and is particularly suitable for live performance and portable use.

Please send S.A.E. for our price list.

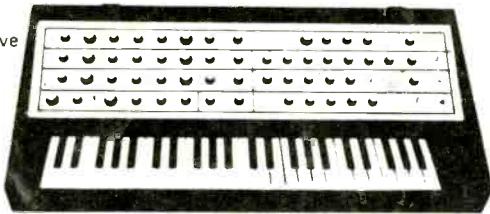

The 4600 SYNTHESISER

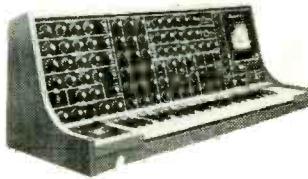

We stock all the parts for this brilliantly designed synthesiser, including all the PCBs, metalwork and a drilled and printed front panel, giving a superb professional finish. Opinions of authority agree the ETI International Synthesiser is technically superior to most of today's models. Complete construction details in our booklet available now, price £1.50, or S.A.E. please for specification.

GRAPHIC EQUALIZER

A really superior high quality stereo graphic equaliser as described in Jan. 1975 issue of ETI. We stock all parts (except woodwork) including all the metal work drilled and printed as required to suit our components and PCB's S.A.E. for price list or complete reprint of article — price 15p.



ELECTRONIC ORGAN

Build yourself an exciting Electronic Organ. Our leaflet MES51, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops. Leaflet MES52, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range. Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MES53 priced at 35p (pre-publication price 15p.)



NO MORE DOUBTS ABOUT PRICES

Now our prices are GUARANTEED (changes in VAT excluded) for two month periods. We'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an s.a.e. and we'll send you our latest list of GUARANTEED prices. Send us 30p and we'll put you on our mailing list — you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next GUARANTEED period before the prices are implemented! — plus details of any new lines, special offers, interesting projects — and coupons to spend on components to repay your 30p.

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff-on-Sea, Essex. Please address all mail to



MAPLIN ELECTRONIC SUPPLIES

P.O. Box 3 Rayleigh Essex SS6 8LR.

I enclose Cheque/P.O. value _____
For _____ copy/copies of your Catalogue
Name _____
Address _____

ETI

MAPLIN ELECTRONIC SUPPLIES P.O. Box 3 Rayleigh
Essex SS6 8LR.