

29 Windsor

PRACTICAL

JULY 1986 • £1.25

ELECTRONICS


SCIENCE AND TECHNOLOGY

MICROMOUSE-
ALTERNATIVE
ROBOTICS

RS-232
BREAKOUT BOX

ECHO REVERB
SOUND EFFECTS

PASSIVE I.R.
DETECTOR

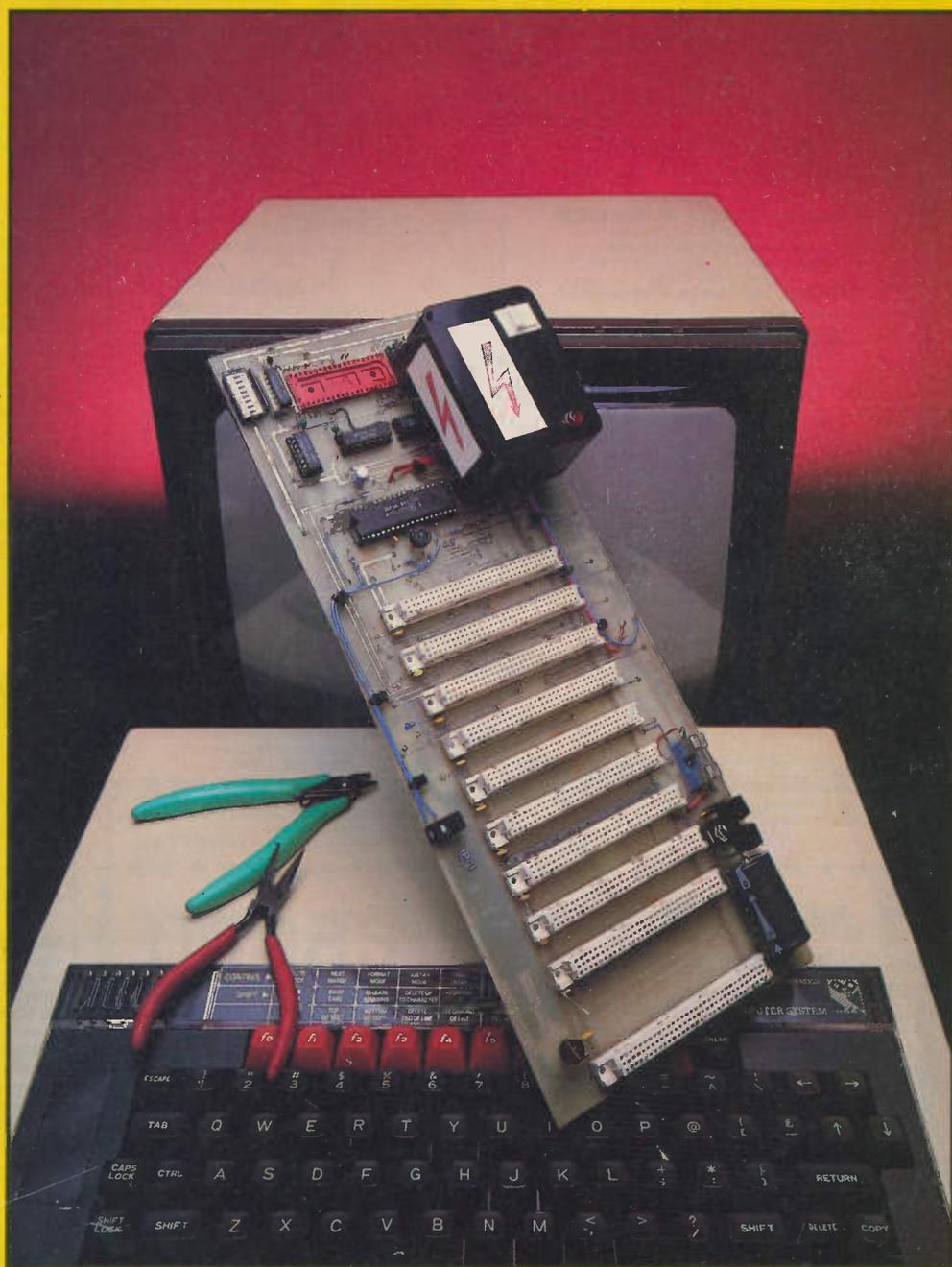

HOBBYBUS IN ACTION—HOW TO
CONNECT THE BUS TO YOUR COMPUTER

Full kits include pcb's, hardware, cases (unless stated otherwise), IC sockets, wire, nuts & bolts. Article reprints extra 70p each.

THIS MONTH'S KITS - S.A.E. OR PHONE FOR PRICES

GUITAR TRACKER June 86	£34.62
DRY BATTERY CHARGER	Send for details
STEBUS PROJECT	SEND FOR LIST
NOTCHER EFFECTS UNIT May 86	£29.98
TTL LOGIC CHECKER May 86	£19.95
SOUND ACTIVATED SWITCH Apr 86	£39.57
SCRATCH & RUMBLE FILTER (Stereo) Apr 86	£17.99

DIGITAL CAPACITANCE METER

A superb instrument with a five digit 0.5 inch LED display giving direct readout of pF, nF and uF from 1pF to 1,000uF. Exceptionally easy to use. A crystal timebase eliminates setting up procedures. Ideal for schools, labs, and industry as well as electronics enthusiasts from beginners to experts. Complete kit - including PCB, case, all components and hardware, £35.98. Reprints of article 70p.

PHOTOGRAPHIC TRIGGER UNIT Apr 86	£33.98
TEMPERATURE/ANALOGUE INTERFACE Apr 86	£41.78
SPECTRUM HARDWARE RESTART (uncased) Mar 86	£27.14
AMSTRAD I/O. Mar 86	£23.03
FIBROPTIC AUDIO LINK Mar 86	£26.34
FIBROPTIC CABLE 80p/metre.	
LOGIC PROBE Feb 86	£13.48
COMPUTER MOVEMENT DETECTOR Feb 86	£16.60
SPECTRUM SPEECH SYNTH & 8-BIT I/O PORT Jan 86	£28.19
HIGH PERFORMANCE STEPPING MOTOR DRIVER Dec 85	£20.98
EXTRAS: Transformer £5.98, Case £2.95, BBC lead & plug £1.98, Motor-1035 £14.50	
COMMODORE USER PORT EXPANDER Nov 85	£10.91
MODEL RAILWAY TRACK CONTROL Nov 85	£41.04
'SQUINT' ROBOT EYES Nov 85	£8.68

TOUCH CONTROL PSU Oct 85	£28.38
MODULATED SYNDROM Oct 85	£26.58
GENERAL PURPOSE ROBOT INTERFACE, fully populated board Sept/Oct 85	£74.98
RS232 TO CENTRONICS CONVERTER Sept 85	£44.95
CAR BOOT ALARM Sept 85	£11.72
COMPUTER ENVELOPE SHAPER Aug 85	£22.19
VOLTMETER MEMORY ADAPTOR July 85	£10.98
STYLUS KEYBOARD FOR COM 64 Jun 85	£9.55
SYNTHESIZER INTERFACE FOR COM 64 Jun 85	£15.69
AMSTRAD SYNTHESIZER INTERFACE May 85	£25.38
CYLINDER THERMOSTAT May 85	£21.77
BBC POWER CONTROL INTERFACE Apr 85	£20.98
GUITAR ACTIVE TONE CONTROL less case Sept 83	£11.97
PROGRAM CONDITIONER June 83	£18.67
AUTO TEST SET May 83	£34.62
WIPE DELAY Apr 83 less relay	£8.24
BATTERY TESTER Apr 83	£13.25

EDUCATIONAL SETS




ADVENTURES WITH ELECTRONICS

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec Breadboard. Gives clear instructions with lots of pictures. 16 projects - including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects. Adventures with Electronics £3.58. Component pack £20.98 less battery.

HIGH PERFORMANCE STEPPING MOTOR DRIVER

As featured in December issue
Kit including PCB, I.C. & All Parts £20.98
Transformer 30V 18VA £5.98 extra
Case (houses PCB only) £2.95 extra
Lead & Connector for BBC Computer £1.98
Motor - 1035 £14.50
TEA1012 also available separately £6.88. Data £1.00

STEPPER MOTOR

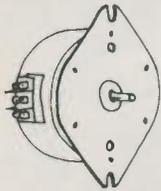


BBC TO 1035 STEPPER MOTOR INTERFACE KIT £13.99 PCB, driver IC, components, connectors and leads included. Demonstration software, listings, circuit diagram, pcb layout and construction details given. Requires unregulated 12Vdc power supply.
INTERFACE KIT (ref PE) £13.99.
OPTIONAL POWER SUPPLY PARTS £4.67.
1035 STEPPER MOTOR 48 Steps. 12V £14.50.



DC MOTOR SETS

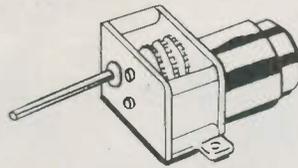MOTOR - GEARBOX ASSEMBLIES 1.5V-4.5V. Miniature precision made. Complete with quality electric motors. Variable reduction ratios. Long 3mm dia output shafts.
Small unit - type MGS (3-2200rpm) £3.49
Large unit - type MGL (2-1150rpm) £3.98



PULLEY WHEELS - metal 3mm bore	
10mm dia	£1.75
20mm dia	£1.84
30mm	£1.99
METAL COLLAR with screw - 3mm bore	24p
FLEXIBLE SPRING COUPLING 3mm L31mm	68p
FLEXIBLE METAL COUPLING 3mm	£2.98
FISCHERTECHNIK DC MOTOR SETS	
SMALL TYPE 187	£9.85
LARGE TYPE 185	£9.90
DC MOTOR 1.5V-4.5V RPM 4,400-8,700	
Shaft dia 2mm L10mm. Body 29x38mm	
DC MOTOR TYPE - DC28	£1.98
FLEXIBLE STEEL SPRING DRIVING BELT	47p
12" long. Joins to itself or 2 or more can be joined where long lengths are needed.	

BBC HEART RATE

BBC Heart Rate Monitor - Ready Built £35.99

Practise relaxation or monitor fitness with this plug-in heart rate monitor. Connects directly to a BBC computer. Programs give continuous heart rate displays, bar charts, graphs etc. Supplied with sensor, software & instructions - ready to plug in and use.

PE HOBBYbus

Kit including double sided p.c.b. excluding DIN sockets £49.98.
DIN 41612 a+c sockets £2.20 each or 10 for £18.

MICROPROCESSOR TRAINER AND SINGLE BOARD COMPUTER

68000

A new single board training and evaluation system for the 16-bit 68000 Series Microprocessor. A standard working system in kit form costs just £99.00 including VAT. Programs are developed and written with the aid of an on-board monitor program. The system is programmed and run via an RS232 link from either a standard terminal or a BBC Computer programmed to act as a terminal (we can supply the necessary software). Optional extras include a line by line assembler, a peripheral I/O port and timer, and a G64 bus interface. Full sets of technical literature, programming information and manufacturers' data sheets are available to accompany the system.

AVAILABLE FROM STOCK NOW
PHONE OR WRITE FOR FULL DETAILS REF PE6

68705 MICROCONTROLLER TRAINER

A stand-alone unit with hexadecimal keyboard and 9-digit seven-segment display. Uses a control oriented 68705 microprocessor with a comprehensive monitor system. A bank of 8 LEDs and switches allows I/O control programs to be run before connecting to 'real' external circuits. An A/D-D/A board is also available along with full support literature. An excellent introduction to machine code programming right down to 'bit' level. Used in many educational establishments. A complete system costs under £50.
All in stock - Phone or write for details Ref PE6

68000 COMPONENTS

68000 P8	£21.20
68230 P8	£6.99
68681	£9.60
64 pin I.C. socket	98p
6116 (250n)	£1.99
6264 (250n)	£3.99
27128 EPROM	£3.88
MC1488	56p
MC1489	59p

FUN WITH ELECTRONICS

Enjoyable introduction to electronics. Full of very clear full colour pictures and easy to follow text. Ideal for all beginners - children and adults. Only basic tools needed. 64 full colour pages cover all aspects - soldering - fault finding - components (identification and how they work). Also full details of how to build 6 projects - burglar alarm, radio, games, etc. Requires soldering - 4 pages clearly show you how.

COMPONENTS SUPPLIED ALLOW ALL PROJECTS TO BE BUILT AND KEPT.

Supplied less batteries & cases.
FUN WITH ELECTRONICS, COMPONENT PACK £16.98
BOOK EXTRA £1.75.
Book available separately.

LOGIC TUTOR

A specifically designed test bed for the practical side of the 8-part educational series 'Introduction to Digital Electronics' Practical Electronics Oct 83-May 84. Full kit includes screen printed pcb, power supply, connector strips and turned pin sockets (less case).

£34.98
REPRINTS EXTRA 70p EACH

INTRODUCTION TO ELECTRONICS

An introduction to the basic principles of electronics. With lots of simple experiments. Uses soldering. Lots of full colour illustrations and simple explanations. A lovely book. Ideal for all ages.

INTRODUCTION TO ELECTRONICS COMPONENT PACK £9.99
BOOK EXTRA £2.45
Book also available separately.

CATALOGUE

Brief details of each kit, book contents, and illustrations and descriptions of our range of tools and components are all included.

Robotics and Computing section included. Our advert shows just a selection of our products. Up to date price list enclosed. Official orders welcome. Catalogue & Price List - Send £1 in stamps etc or add £1 to your order. Price list only 9x4 SAE. Catalogue free to schools/colleges requested on official letterhead.

HOW TO ORDER

MAGENTA ELECTRONICS LTD.
PE7, 135 HUNTER ST.,
BURTON-ON-TRENT
STAFFS, DE14 2ST.
MAIL ORDER ONLY.
0283 65435, Mon-Fri 9-5.
ADD 80p P&P TO ALL ORDERS.
PRICES INCLUDE VAT.
SAE ALL ENQUIRIES.
OFFICIAL ORDERS WELCOME.

OUR PRICES INCLUDE VAT

Access/Barclaycard (Visa) by phone or post.
24 hr Answerphone for credit card orders.



OVERSEAS: Payment must be sterling.
IRISH REPUBLIC and BFPO: UK PRICES.
EUROPE: UK PRICES plus 10%.
ELSEWHERE: write for quote.



Editor: Richard Barron
Consultant Editor:
 Nick Hampshire
Editorial Assistant:
 Mary-Ann Hubers
Advertisement Manager:
 Alfred Tonge
Publisher: Angelo Zgorelec

Readers' Enquiries

All editorial correspondence should be addressed to the editor and any letters requiring a reply should be accompanied by a stamped addressed envelope. Please address editorial correspondence to: **Practical Electronics, 16 Garway Rd., London W2 4NH. Tel. 01-727 7010**

We regret that lengthy technical enquiries cannot be answered over the phone.

Advertisements

All correspondence relating to advertisements, including classified ads, should be addressed to: **The advertisement manager, Practical Electronics, 25 Glenhurst Avenue, Bexley, Kent DA5 3HQ. Tel. (0322) 521069.**

PE Services

Practical Electronics offers a wide range of services to readers including: p.c.b.s, books, subscriptions, back numbers, and software listings. However, due to increased administration costs we can no longer provide photocopies of articles over three years old. Also the availability of back numbers is rapidly declining.

In order to avoid disappointments, in the future, we suggest that you take out a subscription. Not only will you avoid missing an issue but you will also save money and in most cases receive your copy before it is in the local newsagents.

PE EDITORIAL TEL. 01-727 7010

**ADVERTISEMENT DEPT
 TEL. (0322) 521069**

CONSTRUCTIONAL PROJECTS

- PASSIVE IR DETECTOR** by R. A. Penfold 10
Fun with fresnel lenses for light control or burglar detection
- 200MHz COUNTER** Part Two by Mike Delaney 20
Construction and applications of a professional spec. test instrument for the hobbyist
- DRY CELL CHARGER** by Rod Cooper 16
Better Use Of Batteries constructional project
- RS232 BREAKOUT BOX** by John Lewis 32
Give yourself a break—Sort out your computer's communication
- PE HOBBY BUS** Part 3 by R. A. Penfold 34
Computer connections and software for Z80-based micros
- ECHO-REVERB** by M. P. Horsey 38
Produce crazy crescendo, erie echo and raucus reverb

NEWS AND REVIEWS

- NEWS AND MARKET PLACE** 4
What's new, what's happening and what's to come
- READERS' LETTERS** 7
What you say and what you think
- NEWS LATEST** 60
Last minute news items
- COMMENT** 57
A personal point of view

REGULAR FEATURES

- BBC MICRO FORUM** by Ray Stuart 50
- SPACEWATCH** by Dr Patrick Moore OBE 44
News from space and the sky this month
- INDUSTRY NOTEBOOK** by Nexus 58
What's happening inside industry
- ROBOTICS REVIEW** by Nigel Clark 31
The latest from the world of industrial and educational robots
- THE LEADING EDGE** by Barry Fox 15
The technology behind the technology

SPECIAL FEATURES

- BETTER USE OF BATTERIES** Part 2 by Rod Cooper 16
Dry cell technology and practical charging details
- ALTERNATIVE ROBOTICS** by Professor John Billingsley 26
Robotics for the hobbyist—fun and interest with technical excellence
- PRACTICAL MICROMOUSE** by A. Dibley 28
Tips and techniques for practical robot design using a ZX81

PE SERVICES

- PCB SERVICE** P.c.b. list and prices for PE projects 54
- BOOK SERVICE** A selection of the latest electronics titles 56
- SUBSCRIPTIONS AND BACK NUMBERS** 53
- BAZAAR** Free readers' ads 55

OUR AUGUST 1986 ISSUE WILL BE ON SALE FRIDAY, JULY 4th, 1986 (see page 57)

© Intrapress 1986. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

WHAT'S NEW...

Two from Thandar

Thandar Electronics have announced the addition of two further digital multimeters to their range, designated the TM357 and TM358.

The TM357 is a 3.5 digit l.c.d. multimeter with facilities to read a.c./d.c. voltage, current, resistance and diode test. A continuity buzzer is also provided.

The TM358 is a 3.5 digit l.c.d. multimeter which, besides incorporating similar ranges to the TM357, has the additional feature of conductance and transistor *hfe* measurement.

Details from: Thandar Electronics Ltd, London Road, St. Ives, Huntingdon, Cambs PE17 4HJ.



IEEE option scope

Paxton Instruments of Letchworth, Herts, announce the introduction of the HM208 digital storage oscilloscope with IEEE option.

This is a 20MHz realtime oscilloscope in addition to the 20MHz sampling frequency in the digital storage mode. The storage memory size is $4 \times 1K \times 8$ -bit; if, however, used in the single channel mode, channel 1 resolution becomes $2K \times 8$ -bit.

The HM208 IEEE also has a second page memory facility which enables captured signals to be saved for later reference, whilst freeing the original memory for separate storage of channel 1 and/or channel 2.

Details from: Paxton Instruments, Unit B1, Pixmore Industrial Estate, Pixmore Avenue, Letchworth, Herts.



Plug it!

Latest in the line of safe, compact, mains adaptor products from Masterpiece is the Masteradapta.

Now available from leading high street and diy stores at under £10, this adaptor is designed to plug directly into a 13A mains socket and accept four miniature 6A, 3-pin plugs which are compatible with other Masterplug adaptors. This gives an extremely neat and compact arrangement for operating up to four low power appliances (less than 1500W each) from a single 13A mains socket.

Details from: Masterpiece Products, Masterpiece Cabinets Ltd, Annscroft, Shrewsbury SY5 8AN.



Fast gates with power

Hitachi have made another technology and production breakthrough with their new HG28 series of gate arrays.

The gate arrays now feature a combination of super high speed and low power dissipation. At 0.8ns/gate the new series has broken through the 1ns gate barrier and has achieved this, not only with no compromised power, but with a particularly low power dissipation—just 0.22mW (typ. at 10 MHz) for an internal gate.


Details from: Hitachi Electronic Components (UK) Ltd, 21 Upton Road, Watford, Herts WD1 7TB.

In civvy street

The comprehensive Oryx soldering iron range has been extended by the introduction of the Oryx 15W 240V lightweight iron. This low cost iron is based on a successful unit Oryx has built for a national public service organisation, which has used a similar device for many years.

Now in 'civvy' colours of orange and black and presented in a point-of-sale transparent package, this unit will serve all aspects of the market from the hobbyist through to industrial applications. The temperature is set at 350°C nominal from a wire-wound element in a tubular ceramic insulator. The soldering tip is iron plated for long life.

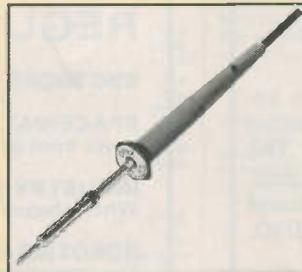Details from: Greenwood Electronics, Portman Road, Reading, Berks RG3 1NE.




Switches

West Hyde have announced an extensive series of miniature switches for p.c. mounting. The range comprises over 80 different versions including push-button, toggle and rotary types. Very small dimensions mean that a large number of devices can be fitted into a small front panel area.

Of particular interest are a VDE-approved mains toggle switch needing only 10×10 mm of panel space, a contactless Hall effect push-button switch, and a variety of binary-coded rotary switches.

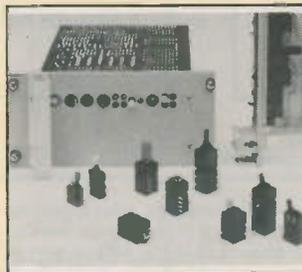Details from: West Hyde Developments Limited, 9-10 Park Street Industrial Estate, Aylesbury, Bucks HP20 1ET.



Triplet and Metex are back

Triplet analogue multimeters and Metex digital multimeters are now available from Alpha Electronics Ltd and reflect the recent growth at Alpha that has necessitated a move to larger premises at Atherton, just outside of Bolton.

Alpha have become the exclusive UK outlet for the Triplet 60 Series of analogue multimeters, said to be extremely robust and reliable. Model 60 is designed with 'user safety' in mind. High impact case, large easy to read taut-band mirror scale meter and unique fuse protection on all ranges give an instrument that is both mechanically and electrically robust.

Details from: Quiswood Ltd, 21 Eastbury Court, Lemsford Road, St Albans, Herts AL1 3PS.



Miniature power relays

Specialist component distributors, Selectronic of Witney, have introduced the ORA miniature power relay, manufactured by the Original Electric Manufacturing Company.

The ORA relay is a p.c.b. s.p.d.t. device. Three types are available: the ORA operates at 3A, the ORAM at 5A and the ORAH at 7A. The relays are available with six nominal coil voltages, ranging from 3 to 48 V d.c. Nominal currents range from 120 to 13mA for the normal version and 66 to 9mA for high sensitivity types.

Details from: Selectronic Ltd, The Old Stables, 46 Market Square, Witney, Oxon OX8 6AL.

WHAT'S HAPPENING...

Flexible transceiver test set

Marconi Instruments' versatile 2955 Radio Communications test set, now available on hire from Instrument Rentals, has all the facilities needed for the rapid in-field testing of transmitters, receivers and duplex R.T. links in one convenient unit.

The test set is suitable for all types of FM, AM, and phase-modulated mobiles and base equipment, up to a frequency of 1GHz and a CW output power of 30W; power levels of up to 100W may be measured for short periods. Speed of measurement results from the use of microprocessor control; for instance, a simplex transceiver may be checked in under three seconds.



For ATE applications, or when a link is required to a PC, all functions except on/off may be remotely controlled via the integral IEEE-488 GPIB interface.

Details from: Instrument Rentals, Dorcan House, Meadfield Road, Langley, Slough, Berks SL3 8AL.

Compact switching

Norbain Electro-Optics Ltd has launched a new series of low-cost compact switching relays, originally designed for the automotive market, which provide an economical solution to low voltage, high current switching applications such as in alarm circuits.

Designated the ZC Series and manufactured by Schrack, the new relays offer a range of contacts including a special contact suitable for switching 6 x 21W lamp loads.

Featuring a contact voltage rating of 110V a.c. and a mechanical life of $\geq 10^7$, the ZC Series has operate and release times of ≤ 10 within an ambient temperature range of -40°C to $+80^\circ\text{C}$.

Details from: Norbain Electro-Optics, Boulton Road, Reading, Berks RG2 0LT.



Rad-hard CMOS brochure

A new brochure on radiation hardened CMOS technology is available from Harris. 'Radiation Effects on CMOS' describes the importance of radiation hardened semiconductors in many of today's high-tech systems for commercial, industrial and defence applications.

A new concern for radiation-resistant tactical weaponry is addressed in the book by describing in detail how far major systems can be protected and from what types of radiation. The brochure explains the radiation hardening process, defines types of radiation, and discusses the major concern in CMOS—ionization radiation.

Details from: Harris-MHS Semiconductor Sales Ltd, Eskdale Road, Winnersh, Wokingham, Berkshire RG11 5TR.



15th Edition tester

IEE Wiring Regulations 613.3 and 613.2 define the test requirements for 'Continuity of protective conductors' and 'Continuity of ring final circuit conductors' while appendix 15 gives suitable standard methods of testing.

25CCT, a new conduit continuity tester from TMK Test Instruments, meets these 15th Edition requirements and is therefore ideal for measuring the impedance of protective conductors where part of the protective conductor is a ferrous material. This new instrument, designed and manufactured in the UK, is also extremely useful for ring main measurements and ascertaining earth fault loop impedance (E.F.L.I.).

Details from: Harris Electronics, 138 Grays Inn Road, London WC1X 8AX.

New source for Texas optoelectronics

Texas Instruments, long-established manufacturers of optoelectronic products, have ceased production of their avalanche photo diodes, high power GaAs infra-red diodes, transimpedance amplifiers and hermetic displays range of products. This entire opto range operation has been taken over by Texas Optoelectronics Inc, whose products are available in the UK exclusively from GCA Electronics.

Former TI staffman Mike Bender has joined the company, which can offer the entire former TI optoelectronics range, including those which conform to the various military standards. The company also intends to continue the ongoing development of these devices and to produce new products in the near future.

Details from: GCA Electronics Ltd, Unit 2, Gt. Haseley Trading Estate, Gt. Haseley, Oxon OX9 7PF.

DRAM modules from Hitachi

Hitachi, the largest supplier of memories in Europe, has introduced five new DRAM memory modules (including both pinned and socket types) which save board space and dramatically increase memory density.

The modules are all available with three variations of speed, 120, 150 and 200ns. The DRAMs are all PLCC versions, mounted on an epoxy p.c.b. with either edge connectors for socketing or pins for mounting upright.

The major advantage of modules is that they allow high density packaging without the need for investment in surface mounting equipment. The five new modules allow $\times 4$, $\times 5$, $\times 8$ and $\times 9$ organisations which give flexible word-bit configurations.

Details from: Hitachi Electronic Components (UK) Ltd, Hitec House, 221-225 Station Road, Harrow, Middlesex HA1 2XL.




Microprocessor test instrument

New from Gould Electronics is the K115 logic analyser, designed for design, debug and test in microprocessor applications. It provides 32 or 64 channels at 20MHz for state and timing in 8-, 16- and 32-bit applications and a direct link to either four or eight channels at 5 nanoseconds, or eight or 16 channels at 10ns.

A major feature of the K115 is the ability to go from state to timing and back on the main channels simply by pushing a button, thus avoiding the need to reconfigure the hardware.

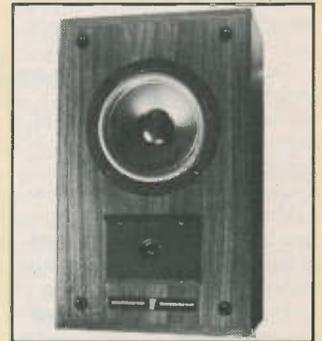Details from: Gould Electronics Ltd, Roebuck Road, Hainault, Ilford, Essex.



Woofers and tweeters developments

The popular model 18 speaker is a firm favourite with domestic buyers and many recording studios who use them as desk monitors, while the AR8 was conceived as a more cost-effective alternative to the popular 18. They have now been improved.

The improved versions from Teledyne have been designed by carefully engineering woofers and tweeters to have intrinsically low coloration and even, well-controlled frequency responses.

The woofers' carefully-designed carbon-loaded polypropylene cones, selected surrounds, dust caps and magnet assemblies provide both units with responses which are very flat up to the crossover area, where they roll off naturally and gently. So, because there are no uneven response trends to compensate for and no requirement to 'roll off' the woofers at high frequencies, there is no need for crossover components of any kind.

Details from: Teledyne Acoustic Research, High Street, Houghton Regis, Dunstable, Beds.

WHAT'S TO COME...

After integrated circuits, integrated mechanics

Engineers have started to use the techniques of semiconductor manufacture to produce mechanical microstructures. The production of miniature mechanical devices has reached the practical limits of miniaturisation using traditional production methods, machining, stamping, welding, soldering, hand assembly, etc. The methods used in fabricating i.c.s are providing a solution to the manufacture of certain microminiature devices. The first devices being constructed in the research labs using these techniques are sensors. The kind of sensors produced so far include accelerometers, pressure sensors, strain gauges and even gas chromatograph.

These mechanical devices are all fabricated on blocks of silicon using the techniques of photomasking, etching and deposition developed for i.c. manufacture. Silicon is used as a substrate for two reasons, first because the methods used in fabricating devices with this material are very well known and secondly because it allows any associated electronics to be fabricated on the same silicon slice.

Much of the advanced research into integrated mechanics is being carried out at Stanford University in California, although several Japanese research centres and Delft University in Holland are now starting work in this area. This is an area of research in which we can expect to see very considerable advances over the next decade.

Amorphous Silicon Devices

Researchers at the university of Dundee are making significant advances in the development of semiconductor devices using amorphous silicon. Amorphous silicon has potentially major advantages over crystalline silicon and gallium arsenide. It is much cheaper to produce, can be deposited onto a wide range of different substrates in films as thin as 1 micron and over quite large areas. The amorphous silicon is deposited onto the substrate by decomposing silane gas in a plasma. The resulting film of silicon can be doped by adding small

amounts of phosphine or diborane gas to the silane in order to produce n-type or p-type layers. The resulting amorphous silicon layers have no ordered crystalline structure and only have semiconducting properties because the silicon is alloyed with hydrogen as a result of the silane decomposition.

The Dundee University team have developed the equipment necessary to produce amorphous silicon devices and amorphous silicon FET devices, these are likely to find immediate application in the production of addressable liquid crystal display panels. They have also demonstrated a non-volatile memory based on a p-n-i configuration.

New techniques required for 4Mbit memory chips

Texas Instruments, Toshiba and NEC have all recently demonstrated preliminary laboratory versions of 4Mbit dynamic random access memory chips. The design and fabrication of these super memory chips, each with over 8.5 million components contained on a one cm square silicon chip has posed a whole new and often very complex range of problems for chip designers. The main problem is that in order to retain fast access time it is essential to keep the chip fairly small. This is achieved by reducing the circuit geometries. In order to produce 4Mbit DRAMS

1 micron geometry CMOS will be used. However, DRAMS retain their memory contents by retaining a charge on a capacitor fabricated in silicon on each individual memory cell. With larger geometries and planar fabrication such as capacitor with the required capacitance (about 50fF) does not pose a problem. The solution adopted by designers has been to construct capacitors vertically within the silicon slice creating a so-called 'trench capacitor'. This approach considerably reduces the surface area of the chip occupied by capacitors and therefore allows the far higher component densities essential for fabricating 4Mbit and larger DRAMS. These 4Mbit DRAMS will be on the market within a couple of years, and already the R and D departments are looking at the next challenge—64Mbit DRAMS.

New capacitors used as energy storage devices

A new technique has been developed for making high energy density capacitors. This technique promises to allow them to be used as very economic replacements for NiCad batteries in energy storage applications requiring low drain, such as CMOS RAMs, microprocessors and timers. The devices are known as DLCs or Double Layer Capacitors and exhibit an energy density of up to 500 times that of a standard aluminium electrolytic capacitor. This high charge density allows a 1 farad capacitor to be constructed which has a volume of only about 1 cubic centimetre.

These DLC capacitors have been developed by Sohio Maxcap. The secret of their

construction lies in the replacement of aluminium as the electrode material with activated carbon. The activated carbon has a very high surface area, over 1000 square metres per gramme, and the device's charge capacity is proportional to surface area. The working voltage of such a device is very low, and this necessitates the use of the double layer technique which creates a stack of activated carbon and electrolyte units to achieve the required voltage rating. A 5 volt capacitor requires about six units.

Capacitors fabricated using DLC will find many applications. They are ideal for providing back-up power to CMOS memories. A single 1 farad 5 volt DLC will keep a CMOS RAM card backed up for several months.

POINTS ARISING

PE HOBBY BUS (MAY 1986)

On the circuit diagram and the components list R10 and R11 should read 2K2 not 10k. Also on the circuit diagram and the p.c.b. overlay, R15 and C22 should be transposed, i.e. fit R15 in the place of C22 and fit C22 in the place of R15.

BOOK REVIEW (APRIL 1986)

The book entitled *Designing IC Circuits with Experiments* was written by Delton T. Horn and not Delton T. Hall, as stated.

COUNTDOWN

If you are organising any electrical, computing, electronic, radio or scientific event, big or small, drop us a line. We shall be glad to include it here. Address details to Countdown, Practical Electronics, 16 Garway Road, London W2 4NH.

NOTE: some exhibitions detailed here are trade only. Please check details and dates before setting out, as we cannot guarantee the accuracy of the information presented here.

Amateur Radio and Electronics Hobby Fair, July 5, 6, Wembley. F

British Laboratory Week, Sept 23-25, Olympia. C

ITAME, Sept 23-25. C

College. B

Milan Fair, Sept 4-8, Milan (Trade only).

Hitachi Electronic Components Summit, June 9, Wembley. D

Official Acorn User Exhibition, July 24-27, Barbican. E

Amateur Electronics Exhibition, July 12-20. Esplanade, Penarth. A

A B.A.E.C. ☎ 0222 707813

B Imperial College ☎ 01-589 5111

C Evan Steadman ☎ 0799 26699

D HPS ☎ 0494 40176

E Editionscheme ☎ 01-394 4667

F Amateur Radio Promotions ☎ 021-421 5516

BOOKS AND LETTERS PAGE

Sir

Whilst I applaud your decision to support the STE bus, to IEEE 1000, I am appalled that you should also introduce your own non-standard 'standard'. You adduce no reason for introducing it, and, with over 150 eight-bit buses in existence, the world really doesn't need another. If you had to have a second, would it not have been better to approach your opposite number at Elektor, for permission to use the Elektor bus? Then you could have built on their good work, in a system that already offers several CPUs, memory and IO cards, instead of encouraging people merely to re-invent the wheel. In the electronics world, the principle of second sourcing is regarded as both desirable and professionally mature, whereas the 'not invented here' syndrome is not just unprofessional, but actively anti-professional.

R. J. Larkin, Dept. of Electronics and Communications Engineering, North London Poly.

Dear Mr. Larkin

Whilst not wishing to comment on projects published in other journals, we would like to point out that many eight-bit buses presently available are extremely limited in the use as a hobbyist project. The Hobby Bus is not designed simply as an eight-bit processor bus but a universal peripheral bus which may be connected to any home micro with the minimum of effort or modification.

In addition, the PE Hobby Bus is able to support both an on-board processor as well as a host micro, thus giving rise to a very flexible and useful system. Can other Hobbyist buses offer so much compatibility whilst retaining flexibility?

Editor

Dear Sir

I wish to make a security lamp that is switched by way of a Passive Infra Red Detector.

I am an idiot. I will also need the circuits as well as the detector. Perhaps one of your readers know of such equipment and also suppliers. Better still why not publish a constructional project for this type of security lamp.

J. R. Atkins, Hurstpier Point, Sussex.

Dear Mr. Atkins

See this issue. By the way—any sceptical readers' who think that this letter is a plant—it's not, honestly. It's just a coincidence.

Editorial

Dear Sir

I have read much about the peripheral equipment that can be attached to my ZX81 to enable me to drive some home-made electronics, but I have not found out how to do the actual attaching.

J. A. Ratcliffe, Cambridge.

Dear Mr. Ratcliffe

There is an edge connector at the back which has all the required connections.

Editor

Dear Sir

I have been unable to find newsagents who stock your Practical Electronics magazine. I used to take it regularly until it got hard to find. Have you ceased publication?

J. S. Smith, Edgbaston, Birmingham.

Dear Mr. Smith

We have not ceased publication—we're still going strong. Recently we have changed our distributors and there should be no further problems regarding availability.

Editor

Dear Sir

With all due respect to your position I feel your answer to the letter from Des M Reed (letter's page PE April 1986) shows a very restricted knowledge of the electronics industry related to recording. Bulk erasers are standard equipment for anyone involved seriously in magnetic recording, and while they are not cheap any quality hi-fi dealer should know of their existence.

I trust you are not going to make a habit of giving such ill-informed answers in future.

Brian Hayter, Principal Technician, Educational Technology Dept, Bulmershe C.H.E.

Dear Mr. Hayter

We are not 'quality hi-fi dealers'. Nevertheless, you are right, we should have informed Mr. Reed that such devices are available. They are, however, rarely available cheaply from normal hi-fi retail outlets.

Editor

Dear Sir

Having 'taken' PE for many years, it is with regularity that one reads of how informative, innovative and absolutely 'essential' reading the periodical is to those of us who have an interest, keen or slight etc.

To this end therefore, I wonder why, during the whole of '85—all 12 issues—PE did not appear to publish even one p.c.b. foil design. 'Tis true, that component overlay designs were featured—some 53 or so I recall. However, an overlay design is not a foil design. Attempting to separate the two for U V artwork, becomes an impossible task, except for the more simple circuits.

I look forward to your comments re the above. Remaining a loyal subscriber meanwhile.

G. I. Hunter

Dear Mr. Hunter

Thank you for your letter of 3rd February. It is an Editor decision with Practical Electronics not to fill the magazine with either p.c.b. foil designs or software listings. P.c.b.s are available from the PCB Service and we will provide any reader who so desires with copies of the foil design for any project.

Editor

Dear Sir

I was very pleased to see that your April issue carried a Photographic Trigger Unit project.

You say that you don't know of anyone who makes a cable type camera release system. Mazof of: PO Box 256, London N19 4SL make a relay camera trigger. Mr. R. Sahota, Hayes, Middx.

Dear Mr. Sahota

Thanks for your help in this matter, we're sure it will be useful to a number of readers.

Editorial

OP-AMPS (second edition)

J. Brian Dance—Newnes Technical Books. ISBN 0-600-33372-8
102 pages paperback. £4.95

Subtitled 'Their Principles And Applications', this book is an updated version of the first edition and thus describes a wider range of devices including programmable, FET input and high power types.

The basic operating principles of op-amps are described in detail with plenty of practical applications to back up the theory. Also included is a section devoted to high power circuits, as high power audio amplifiers are of great interest to many readers.

At the back of the book are three very useful sections. The glossary of terms briefly defines the key words and phrases used in the book and an index of devices refers to the pages in which the devices appear. Finally, a complete cross referenced index makes this publication easy to use as a design aid or reference book.

OSCILLOSCOPES

Ian Hickman—Newnes Technical Books. ISBN 0-600-33373-6
124 pages paperback. £5.50

The first edition of this book was published in 1981. There have been many improvements to oscilloscope design since then, largely due to the developments in integrated circuit technology. Digital oscilloscopes are far more popular and widely available. This new edition covers this subject thoroughly.

The book subtitled 'How To Use Them How They Work', describes in depth the principles of real time oscilloscopes, digital instruments and logic analysers. There are many photos and diagrams, essential to understanding the subject.

'Oscilloscopes' is aimed at the user and potential user. It offers advice on how to choose and operate oscilloscopes and highlights the common pitfalls. It should be appealing to anyone wishing to know about the subject, from the student to the technician.

BBC Micro Computer System

BBC Master Series	
AMB15 BBC MASTER Foundation computer 128K.....	£415 (a)
AMB12 BBC MASTER Econet computer 128K (only ANFS).....	£348 (a)
AMC06 Turbo (65C102) Expansion Module.....	£87 (b)
ADF13 Rom Cartridge.....	£13 (d)
ADF10 Econet Module.....	£49 (c)
ADJ22 Ref. Manual Part I.....	£14.50 (c)
ADJ23 Ref. Manual Part II.....	£14.50 (c)
ADJ24 Advanced Ref. Manual.....	£19.50 (c)
UPGRADE KITS	
Econet Kit.....	£55 (d)
1770 DFS Upgrade for Model B.....	£43.50 (d)
1.2 OS ROM.....	£7.50 (d)
DNFS ROM.....	£17.50 (d)
ADFS Rom for B with 1770 DFS & B Plus.....	£26 (d)
64K Upgrade Kit for B Plus.....	£35 (d)

ECONET ACCESSORIES	
Econet Starter Kit.....	£85 (d)
Econet Socket Sat.....	£34 (c)
File Server Level I.....	£75 (d)
File Server Level II.....	£210 (d)
Printer Server Rom.....	£41 (d)
10 Station Load Sat.....	£26 (c)
Adv. Econet User Guide.....	£10 (d)
ACORN ADD-ON PRODUCTS	
Z80 2nd Processor.....	£329 (a)
6502 2nd Processor.....	£169 (a)
Teltext Adaptor.....	£125 (b)
IEEE Interface.....	£278 (b)
COMMUNICATIONS ROMS	
Terminator.....	£25 (d)
Communicator.....	£49 (d)
Commstar.....	£28 (d)
DATABEEB.....	£24 (d)
BBC FIRMWARE & SOFTWARE	
Database Management Systems	
Word Processors	Languages
Spreadsheets	Utilities
For full details on the wide range of above packages please write to us.	

TORCH UNICORN products including the IBM Compatible GRADUATE in stock. For detailed specification or information on our comprehensive BBC range please write to us.

DISC DRIVES

These are fully cased and wired drives with slim line high quality mechanisms. Drives supplied with cables manuals and formatting disc suitable for the BBC computer. All 80 track drives are supplied with 40/80 track switching as standard. All drives can operate in single or dual density format.

PD800P (2 x 400K/2 x 640K 40/80T DS) with built in monitor stand.....	£279 (a)	3.5" DRIVES
PD800 (2 x 400K/2 x 640K 40/80T DS).....	£249 (a)	1 x 400K/1 x 640K 80T DS TS35.....
TS400 1 x 400K/1 x 640K 40/80T DS.....	£109 (b)	1.....
PS400 with psu 1 x 400K/1 x 640K 40/80T DS.....	£129 (b)	2 x 400K/1 x 640K 80T DS TD35.....
		2.....
		PS35 1 with psu.....
		£129 (b)
		PD35 2 with psu.....
		£209 (b)

3M FLOPPY DISCS

High quality discs that offer a reliable error free performance for life. Each disc is individually tested and guaranteed for life. Ten discs are supplied in a sturdy cardboard box.

5 1/4" DISCS	3 1/2" DISCS
40 SS DD £12 (d)	40T DS DD £16 (d)
80T SS DD £21 (d)	80T SS DD £22 (d)
	80T SS DD £30 (d)
	80T DS DD £38 (d)

DISC ACCESSORIES

FLOPPICLENE Disc Head Cleaning Kit with 20 disposable cleaning discs ensures continued optimum performance of the drives... 3 1/2" £16 (d), 5 1/4" £14.50 (d)

Single Disc Cable.....	£6 (d)	Dual Disc Cable.....	£8.50 (d)
10 Disc Library Case.....	£1.80 (c)	30 Disc Case.....	£6 (c)
40 Disc Lockable Box.....	£14 (c)	100 Disc Lockable Box.....	£19 (c)

MICROVITEC

All 14" monitors now available in plastic or metal cases, please specify your requirement.

14" RGB	14" RGB with PAL & Audio
1431 Std Res.....	£179 (a)
1451 Med Res.....	£235 (a)
1441 Hi Res.....	£375 (a)
Swivel Base for Plastic 14" Microvitecs.....	£20 (c)
20" RGB with PAL & Audio	
2030CS Std Res.....	£380 (a)
2040CS Hi Res.....	£685 (a)

KAGA TAXAN 12" RGB

SUPERVISION III with amber/green option..... £345 (a)
 MITSUBISHI XC1404 14" RGB Med Res IBM & BBC Compatible..... £249 (a)

MONOCHROME MONITORS:

SANYO DM8112CX Hi Res 12" Green Screen.....	£95 (a)
KAGA KX1201G Hi Res 12" Etched Green Screen.....	£99 (a)
KAGA KX1203A Hi Res 12" Etched Amber Screen.....	£105 (a)
PHILIPS BM7502 12" Hi Res Green Screen.....	£75 (a)
PHILIPS BM7522 12" Hi Res Amber Screen.....	£79 (a)
Swivel Base for Kaga Monochrome fitted with Digital Clock.....	£21 (c)

SPECIAL OFFER
 2764-25 £2.00
 27128-25 ... £2.50
 6264LP-15... £3.40

ATTENTION
 All prices in this double page advertisement are subject to change without notice.
ALL PRICES EXCLUDE VAT
 Please add carriage 50p unless indicated as follows:
 (a) £8 (b) £2.50 (c) £1.50 (d) £1.00

ACCESSORIES

EPSON	
FX plus sheet feeder.....	£129.00 (b)
LX80 Sheet feeder.....	£49.00 (b)
Paper Roll Holder.....	£17.00 (d)
FX80 Tractor attachment.....	£37.00 (c)
Interfaces: 8143 RS232.....	£28.00 (c)
8148 RS232 + 2K.....	£57.00 (c)
8132 Apple II.....	£80.00 (c)
8165 IEEE + cable.....	£85.00 (c)
Serial & Parallel Interfaces with larger buffers available.	
Ribbons: RX/FX/MX80.....	£5.00 (d)
RX/FX/MX100.....	£10.00 (d)
LX80.....	£6.00 (d)
Spare pens for H180.....	£7.50/set (d)
FX80 Tractor Attachment.....	£37 (c)
KAGA TAXAN	
RS232 Interface + 2K Buffer.....	£85 (c)
Ribbon KP810/910.....	£6.00 (d)
JUKI:	
RS232 Interface.....	£85 (c)
Spare Daisy Wheel.....	£14.00 (d)
Ribbon.....	£2.50 (d)
Sheet Feeder.....	£182 (a)
Tractor Feed Attachment.....	£129 (a)
BROTHER HRI15:	
Sheet Feeder.....	£189 (a)
Tractor Feeder.....	£99 (a)
Ribbons Carbon or Nylon.....	£4.50 (d)
Red Correction Ribbon.....	£2.00 (d)
BBC Printer Lead:	
Parallel (42).....	£7.00 (d)
Serial.....	£7.00 (d)
Printer Leads can be supplied to any length.	

PRINTERS

EPSON	
LX-80NLO.....	£195 (a)
FX85 (80col) NLQ 8K RAM.....	£315 (a)
Optional Tractor Feed.....	£20 (c)
FX105 (126col).....	£449 (a)
JX80 4 colour printer.....	£435 (a)
LQ800 (80col).....	£595 (a)
LQ1500 (136col) 2K buffer.....	£875 (a)
LQ1500 (136col) 32K buffer.....	£950 (a)
PLOTTERS	
Epson H180: A4 4 colour Plotter.....	£345 (a)
Hitachi 672: A3 4 colour Plotter.....	£465 (a)
TAXAN KAGA:	
KP810 80 Col NLQ.....	£225 (a)
KP910 156 Vol NLQ.....	£339 (a)
JUKI 6100 Daisy Wheel.....	£289 (a)
HR15LX (Serial).....	£295 (a)
HR15LX (Serial).....	£365 (a)
Paper:	
2000 Sheets Fanfold:	
9-5" x 11".....	£13 (b)
14-5" x 11".....	£18.50 (b)
Labels: (per 1000)	
3-5" x 1 1/8" Single row.....	£5.25 (d)
2 7/8" x 1 1/8" Triple row.....	£5.00 (d)

MODEMS

All modems listed below are BT approved

MIRACLE 3000: A new range of microprocessor based modems offering of up to 2400 baud, full duplex. Features include 'HAYES' protocol compatibility, auto answer, auto dial, speed buffering, printer port, data security option etc. Mains powered. WS3000 V2123 (V21 & V23).....	£295 (b)	Auto Dial Card.....	£30 (d)
WS3000 V22 (as above plus 1200 baud full duplex).....	£495 (b)	Auto Answer Card.....	£30 (d)
WS3000 V22bis2400 (as above plus 2400 baud full duplex).....	£650 (b)	SK1 Software Control Kit.....	£10 (d)
MIRACLE 2000 A world standard modem covering V21, V23 (bell 103/113/108 outside UK) and including 75, 300, 600, 1200 baud ratings. Optional Auto dial, auto answer cards, complete control from computer keyboard. WS2000.....	£105 (b)	GEC DATACHAT 1223: BABT approved modem complying with CCITT V23 standard. Supplied with software.....	
			£86 (b)
		Data Cables for above modems available for most computers.	

Serial Test Cable Serial Cable switchable at both ends allowing pin options to be re-routed or linked at either end using a 10 way switch making it possible to produce almost any cable configuration on site. Available as M/M or M/F.....	£24.75 (d)
---	------------

Serial Mini Patch Box Allows an easy method to reconfigure pin functions without rewiring the cable assy. Jumpers can be used and reused.....	£22 (d)
---	---------

Serial Mini Test Monitors RS232C and CCITT V24 Transmissions, indicating status with dual colour LEDs on 7 most significant lines. Connects in Line.....	£22.50 (d)
--	------------

GANG OF EIGHT

INTELLIGENT FAST EPROM COPIER

Copies up to eight eproms at a time and accepts all single rail eproms up to 27256. Can reduce programming time by 80% by using manufacturer's suggested algorithms. Fixed Vpp of 21 & 25 volts and variable Vpp factory set at 12.5 volts. LCD display with alpha moving message. £395 (b).

SOFTY II

This low cost intelligent eprom programmer can program 2716, 2516, 2532, 2732, and with an adaptor, 2564 and 2764. Displays 512 byte page on TV — has a serial and parallel I/O routines. Can be used as an emulator, cassette interface. Softy II.....

Adaptor for 2764/2564.....	£25.00 (c)

UV ERASERS

All erasers with built in safety switch and mains indicator.
 UV1 B erases up to 6 eproms at a time.....

UV1 B as above but with a timer.....	£59 (c)
UV140 erases up to 14 eproms at a time.....	£71 (b)
UV141 as above but with a timer.....	£88 (b)

I.D. CONNECTORS

(Speedblock Type)			
No of ways	Header	Recep- tacle	Edge Conn.
10	90p	85p	120p
20	145p	125p	195p
26	175p	150p	240p
34	200p	160p	320p
40	220p	190p	340p
50	235p	200p	390p

D CONNECTORS

No of Ways			
	9	15	25
MALE:			
Ang.Pins	120	180	230
Solder	60	85	125
IDC	175	275	325
FEMALE:			
St Pin	100	140	210
Ang.pins	160	210	275
Solder	90	130	195
IDC	195	325	375
St Hood	90	95	100
Screw	130	150	175
Lock			

TEXTTOOL ZIF

SOCKETS:	24-pin	£7.50
	28-pin	£9.00
	40-pin	£12

EDGE CONNECTORS

2 x 6-way (commodore) 0.1".....	300p
2 x 10-way 0.156".....	150p
2 x 12-way (vic 20).....	350p
2 x 18-way.....	140p
2 x 23-way (ZX81).....	175p
2 x 25-way.....	225p
2 x 28-way (Spectrum).....	200p
2 x 36-way.....	250p
1 x 43-way.....	260p
2 x 22-way.....	190p
2 x 43-way.....	395p
1 x 77-way.....	400p
2 x 50-way (S100conn).....	600p

EURO CONNECTORS

DIN 41612	Plug	Socket
2 x 32 way St Pin	230p	275p
2 x 32 way Ang Pin	275p	320p
3 x 32 way St Pin	260p	300p
3 x 32 way Ang Pin	375p	400p
IDC Skt A + B		400p
IDC Skt A + C		400p
For 2 x 32 way please specify spacing (A + B, A + C).		

MISC CONNS

21 pin Scart Connector.....	200p
8 pin Video Connector.....	200p

AMPHENOL CONNECTORS

Solder			
36 way plug	500p	475p	ZDC
36 way skt	550p	500p	
24 way plug			
IEEE	475p	475p	
24 way skt			
IEEE	500p	500p	
PCB Mtg Skt Ang Pin			
24 way 700p		36way 750p	

GENDER CHANGERS

25 way D type	
Male to Male.....	£10
Male to Female.....	£10
Female to Female.....	£10

RS 232 JUMPERS

(25 way D)	
24" Single end Male.....	£5.00
24" Single end Female.....	£5.25
24" Female Female.....	£10.00
24" Male Male.....	£9.50
24" Male Female.....	£9.50

DIL SWITCHES

4-way 90p	6-way 100p
8-way 120p	10-way 150p

RIBBON

(grey/metre)			
10-way	40p	34-way	160p
16-way	60p	40-way	180p
20-way	85p	50-way	200p
26-way	120p	64-way	280p

DIL HEADERS

Solder		
14 pin	40p	100p
16 pin	50p	110p
18 pin	60p	-
20 pin	75p	-
24 pin	100p	150p
28 pin	160p	200p
40 pin	200p	225p

TECHNOLINE VIEWDATA SYSTEM
 Using 'Prestel' type protocols for information and orders phone 01-450 9764. 24 hour service, 7 days a week.

LINEAR ICs

COMPUTER COMPONENTS

A07581	£15	LM383	385p
ADC0808	1190p	LM707	35p
AM7910DC	£25	LM710	48p
AN103	3200p	LM711	100p
AV-1-9050	100p	LM723	30p
AV-1-9100	450p	LM725CN	250p
AV-3-8910	450p	LM733	30p
AV-3-8912	500p	LM741	22p
CA3019A	100p	LM747	70p
CA3028A	100p	LM748	30p
CA3046	70p	LM1011	480p
CA3069	325p	LM1014	110p
CA3080	90p	LM1801	250p
CA3080E	90p	LM1830	250p
CA3096	75p	LM1871	300p
CA3096E	210p	LM1872	300p
CA3096AQ	375p	LM1886	550p
CA3130E	80p	LM1889	450p
CA3130T	100p	LM1917	30p
CA3140E	45p	LM3302	90p
CA3140T	100p	LM3900	200p
CA3160E	90p	LM3909	150p
CA3161E	200p	LM3911	180p
CA3162E	600p	LM3914	350p
CA3189E	270p	LM3915	340p
CA3200A	150p	LM3916	340p
CA3200Q	270p	LM3960	150p
CA3200T	150p	LM3961	150p
CA3200TQ	150p	LM3962	150p
CA3200TQ	150p	LM3963	150p
CA3200TQ	150p	LM3964	150p
CA3200TQ	150p	LM4052	150p
CA3200TQ			

PASSIVE INFRARED DETECTOR

BY R. A. PENFOLD

Lighten up with Fresnel lenses and body heat!

ALTHOUGH passive infra-red sensors have been in common use for some time now, they seem to have received relatively little attention in the electronics press. Probably the main reason for this is the lack of availability of suitable sensors. Virtually any semiconductor opto device has good sensitivity at infra-red wavelengths, and many popular opto devices actually have optimum sensitivity in the infra-red part of the spectrum. However, they peak at typical wavelengths of around 0.7 to 1 micron, which is close to the visible light spectrum (about 0.4 to 0.7 microns). For passive infra-red detection it is longer wavelength infra-red radiation that is of interest, and it is wavelengths of around 7 to 14 microns which must be detected.

Passive infra-red detectors do not operate by simply detecting body heat or a lack of it, but by detecting movement of the heat source. This method has to be adopted as the d.c. shift produced by the introduction of a heat source is too small to be detected reliably. Fig. 1 illustrates the basic arrangement that is used, with a fresnel lens being used to divide the area covered by the sensor into zones of good and bad sensitivity. An alternative to the special lens is a simple grille of some kind, but the lens has the advantage of providing much greater sensitivity. Anyone moving across the

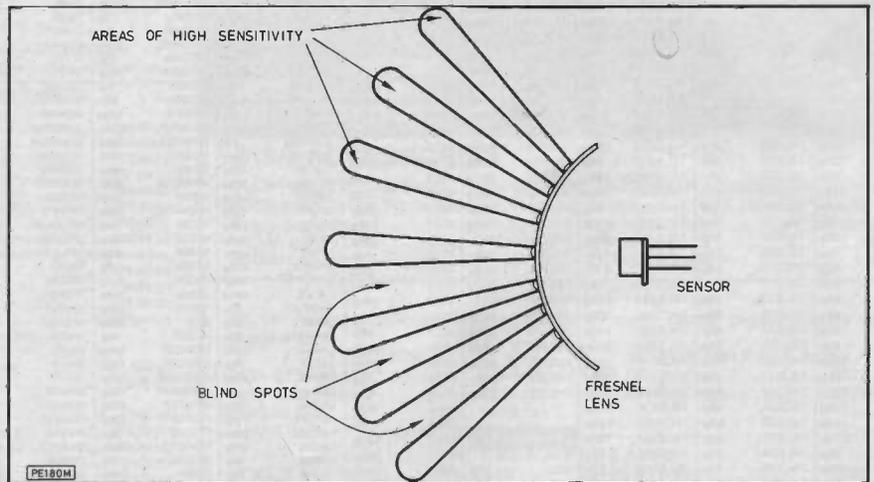


Fig. 1. Basic d.c. shift arrangement

monitored area generates small variations in the output voltage from the sensing device as they move from areas of good sensitivity to the "blind" spots. Provided this signal is above the noise level it can be detected and used to operate a relay or other switching device.

SENSORS

While not being the most widely available of components, passive infra-red detectors, or pyro-electric sensors as they are often called, are available to the home constructor and other small quantity users, as are suitable fresnel lenses. The most widely used type of sensor is the dual opposed type which use the arrangement outlined in Fig. 2. The sensing elements are made from crystals which have the property of producing reverse charges on opposite faces when heated, rather like the more familiar Piezo-electric sensors do when deformed. Having the sensing elements connected so as to oppose one another may seem pointless, since, on the face of it, they will simply cancel out one another and produce no output signal. As far as any background heat is concerned this is indeed the case, but the heat produced by someone moving across the monitored area will be directed first to one element, and then to the other. This gives an output signal

first of one polarity, and then a signal of equal strength but of the opposite polarity. This system gives a relatively strong a.c. output signal to the subsequent circuitry and minimises problems with noise.

The output from the sensors is at a very high impedance, and a built-in field effect transistor connected in the source follower mode provides buffering. The output from the sensor is very low at typically under one millivolt peak to peak, and a high level of amplification is needed in order to bring the signal to a usable level.

SYSTEM OPERATION

The circuit described here was designed primarily with automatic light switching in mind. However, it could easily be adapted for use in other

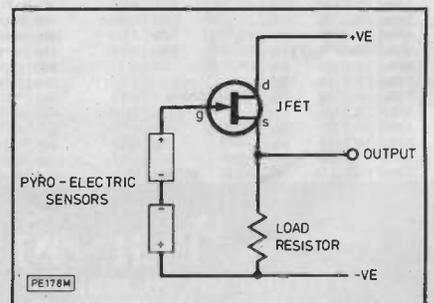


Fig. 2. Dual opposed arrangement

PASSIVE INFRA-RED DETECTOR

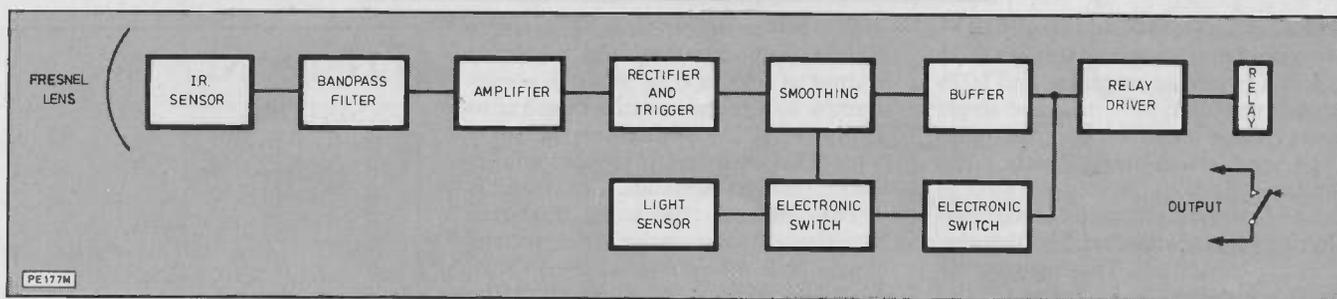


Fig. 3. System block diagram

applications, such as intruder alarms, automatic doors, etc. The block diagram of Fig. 3 shows the various stages which make up the unit.

Obviously the fresnel lens and the pyro-electric sensor appear at the input of the unit, and these are followed by a bandpass filter. Only a very narrow bandwidth is required, and the wanted signals from the sensor are at very low frequencies in the region of 1Hz. By restricting the bandwidth of the system to the minimum requirement any problems with noise that is either picked up by sensor or generated by it are minimised. The next stage is a high gain amplifier which boosts the signal by over 80dB, giving an output of a few volts peak to peak when the unit is activated.

operating continuously when someone is in the room, and to avoid having it continually flashing on and off. The smoothing circuit has a high output impedance, and a buffer stage is therefore used to match it to the subsequent circuit which is a relay driver stage. A pair of normally open relay contacts are used to switch on the light, activate the burglar alarm, or whatever.

The unit as described so far is suitable for many applications, but is less than ideal for automatic lighting control. The problem is simply that it will switch on the light whenever anyone enters the room, even during broad daylight. This problem is overcome by incorporating a light level detector in the design. If the intensity of the ambient light is above a certain thresh-

where it does receive light from outside, but does not pick up a significant amount of light from the controlled lamp. This is not usually a very convenient way of doing things in practice though.

An alternative is offered by this circuit in the form of a second inhibit circuit. This one disables the light detector circuit whenever the lamp is switched on. This prevents the photocell circuit from switching off the lamp and producing oscillation, but it enables the photocell circuit to inhibit the unit if someone enters the room during daylight hours. There is one minor flaw in this arrangement in that the lamp will not be switched off if someone is in the room, and the ambient light level increases to the point where the

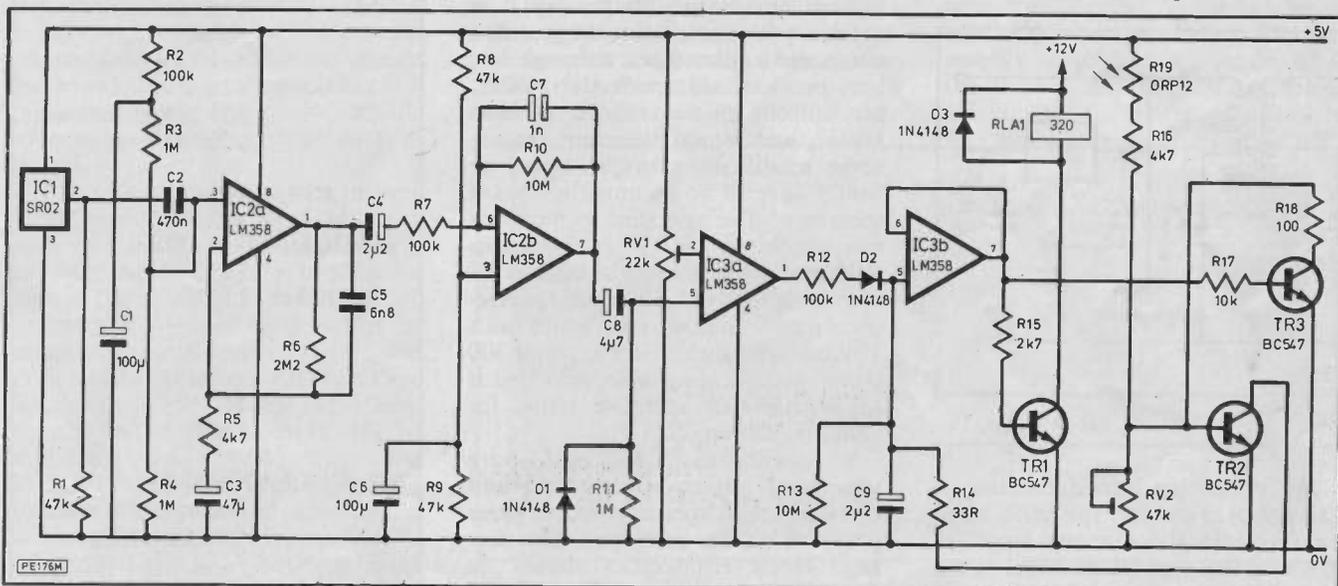


Fig. 4. Main circuit diagram

The amplified signal is rectified and used to drive a trigger circuit. The latter produces a positive output pulse whenever the positive input signal level exceeds a preset threshold level. A smoothing circuit at the output of the trigger circuit has a long decay time of about half a minute, but a much shorter attack time. With no output from the trigger circuit it obviously provides zero output voltage, but with occasional pulses from the trigger stage the smoothing circuit maintains a strong positive output level. The idea of this is to have the controlled light

old level, by way of an electronic switch the light level detector holds the output of the smoothing circuit at zero volts. The circuit is thus inhibited and the light can not be switched on.

This in turn leads to a second problem, which is that of the photocell circuit detecting the light from the controlled lamp, and inhibiting the circuit as soon as the lamp is switched on. This would result in the circuit oscillating with the lamp being switched on and off continuously. The most simple solution to this problem is to have the photocell remotely located

lamp-light is superfluous. However, this is something which is unlikely to occur in practice anyway.

CIRCUIT OPERATION

The main circuit of the unit is shown in Fig. 4, but the mains power supply circuit is shown separately in Fig. 5.

IC1 is the pyro-electric sensor, and R1 is the discrete load resistor for its source follower buffer stage. The SR02 requires a supply voltage of between 2.2 and 10V, and in this case it is powered from a stabilised 5V supply. It has a 50/50 degree field of view.

PASSIVE INFRA-RED DETECTOR

The output from IC1 is amplified by a two stage amplifier, and this has IC2a as a non-inverting amplifier and IC2b as an inverting type. These two stages have voltage gains of approximately 53dB and 40dB respectively. The bandpass filtering is incorporated in these two amplifiers, with the highpass filtering being supplied by the d.c. blocking capacitors. The highpass filtering is obtained by including C5 and C7 in the feedback circuits.

IC3a functions as the rectifier and trigger stage. IC3a is really just operating as a voltage comparator, with R11 biasing the non-inverting input to the 0V supply and VR1 providing the inverting input with a preset reference voltage. This sends the output of the trigger stage low under quiescent conditions. If the unit is activated, and the output signal from IC2b is strong enough, on positive output half cycles the input to the non-inverting input will take this input positive of the inverting input, and the output will trigger to the high state until the voltage at the inverting input subsides below the reference potential. VR1 is given a setting that provides good sensitivity but which does not result in the unit being prone to spurious triggering.

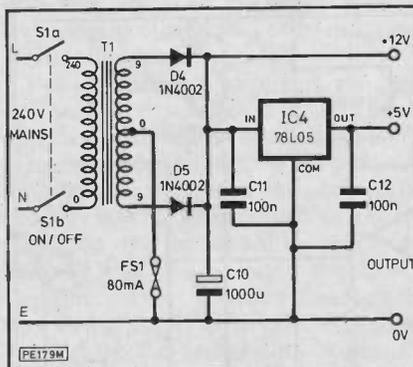


Fig. 5. Power supply

The smoothing circuit consists of R12, D2, R13 and C9. The buffer stage is a conventional operational amplifier non-inverting type (IC3b). TR1 is the relay driver transistor and it operates as a simple common emitter switch. D3 is the usual protection diode. R19 is a cadmium sulphide photoresistor, and if the ambient light level is strong enough it biases TR2 into conduction. TR2 then clamps C9 via current limiting resistor R14, and prevents any significant charge from accumulating on C9. VR2 is the sensitivity control, and it enables the light level at which the inhibit circuit comes into operation to be varied over very wide limits. TR3 is switched on when the relay and relay driver are activated, and it then practically short circuits the base of TR2 to the 0V supply rail, so that this device can not switch on.

The power supply circuit must provide a well smoothed and regulated output at +5V and supply a few milliamps to the main circuit, and also supply a +12V output for the relay which has far less stringent smoothing and regulation demands. The circuit is a conventional type using push-pull rectification and monolithic voltage regulator IC4 to provide the +5V output. The relay is fed direct from the unregulated but smoothed supply. This might fall to somewhat less than 12V under full load, but it will still be adequate to drive the relay properly (which requires a minimum drive potential of 9V). Note that FS1 must be an antisurge type and must not be of the more common "quick-blow" variety (which would almost certainly "blow" as C10 initially charged up at switch-on).

CONSTRUCTION

The exact form that the unit takes must depend to some extent on its intended application, but whatever its proposed use the printed circuit layout of Fig. 6 should be suitable. Construction of the board is largely straightforward, but there are a few points which are worthy of note.

As with any project that utilizes a printed circuit mounting relay it is definitely advisable to use the specified component. Other types, although they may be electrically perfectly suitable, are unlikely to have the same base layout, and would therefore require some modification to the board or would have to be mounted off-board somehow. The specified component can handle up to 10A at the mains voltage and with a resistive load, or 3A with an inductive load. From the electrical stand-point any relay which has a 12V coil with a resistance of about 300 ohms or more is suitable, provided it has contacts of adequate rating for your application of course.

It is essential that C3, C4, and C8 are very good quality components, and tantalum capacitors are used in these positions on the prototype. Low leakage radial electrolytics should be equally suitable though. R19 can be an ORP12, MPY76C, or virtually any cadmium sulphide photocell in fact, as VR2 gives sufficient adjustment range to render the precise characteristics of the cell unimportant. In some applications the inhibit circuit will be unnecessary, and R19, R14, R16 to R18, VR2, TR2 and TR3 can then be omitted.

A plastic box which has approximate outside dimensions of 180mm by 100mm by 55mm makes a good housing for this project. It is used vertically, with the printed circuit board mounted on the rear panel so that IC1 is as close to the top of the case as possible, and centred left to right. This leaves suffi-

COMPONENTS . . .

RESISTORS

R1,R8,R9	47k (3 off)
R2,R7,R12	100k (3 off)
R3,R4,R11	1M (3 off)
R5,R16	4k7 (2 off)
R6	2M2
R10,R13	10M (2 off)
R14	33
R15	2k7
R17	10k
R18	100
R19	(l.d.r.) ORP12 or MPY76C
All resistors	1/4W 5% carbon

POTENTIOMETERS

VR1	22k sub-min hor preset
VR2	47k sub-min hor preset

CAPACITORS

C1,C6	100µ 10V radial elect (2 off)
C2	470n miniature polyester
C3	47µ 10V radial elect or tant
C4	2µ 25V radial elect or tant
C5	6n8 miniature polyester
C8	4µ7 25V radial elect or tant
C9	2µ 25V radial elect
C10	100µ 16V radial elect
C11,C12	100n ceramic (2 off)

SEMICONDUCTORS

IC1	SR02 IR detector
IC2,IC3	LM358 (2 off)
IC4	78L05 (+5V 100mA regulator)
TR1-TR3	BC547 (3 off)
D1-D3	1N4148 (3 off)
D4,D5	1N4002 (2 off)

MISCELLANEOUS

S1	Rotary mains switch
FS1	80mA antisurge
T1	9-0-9 volt 100mA secondary, mains primary
RLA	320R 12V coil, 10 C/O contacts, PCM (Maplin YX97F)

Case about 180 x 110 x 55mm; printed circuit board PE115; CE24 fresnel lens; printed circuit fuse mounting clips (2 off); control knob; 8-pin d.i.l. i.c. holder (2 off); mains lead and plug; connecting wire, solder, etc. The CE24 lens, SR02 IR sensor, and MPY76C are available from Chartland Electronics Ltd., PO Box 83, Cobham, Surrey, KT11 2QB.

PASSIVE INFRA-RED DETECTOR

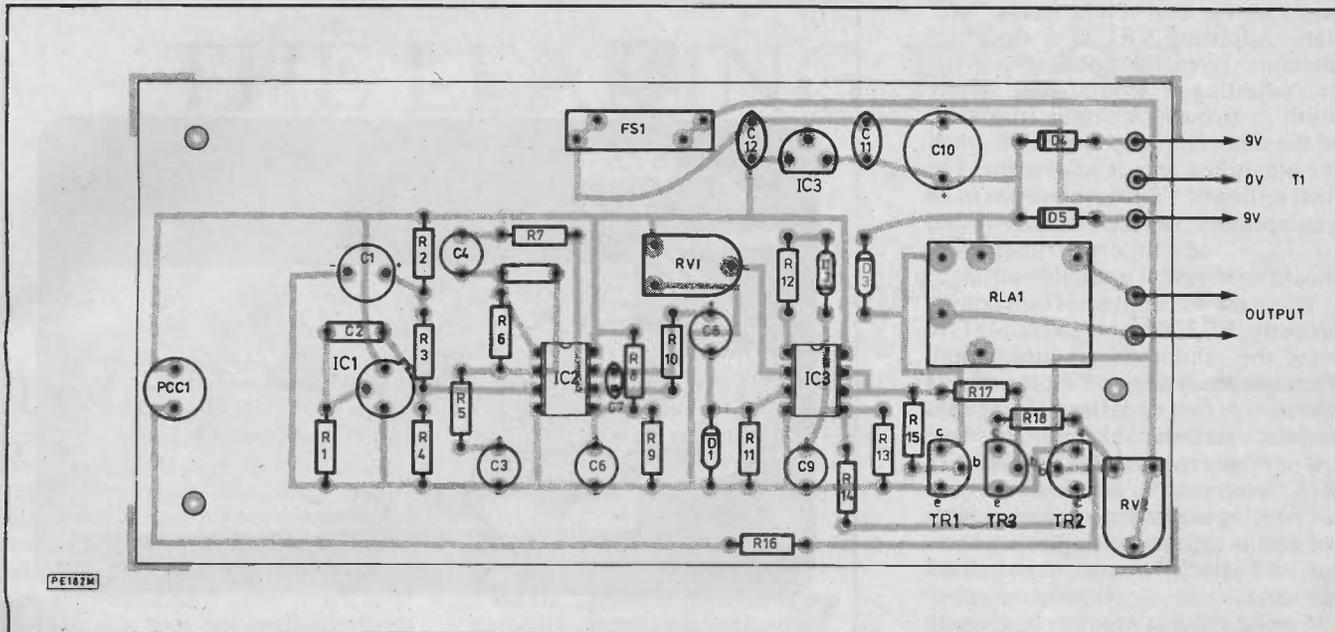


Fig. 6. P.c.b. constructional details

cient space for the mains transformer to be mounted just below the circuit board. A soldertag is fitted on one of T1's mounting bolts, and the mains earth lead must be connected to this. S1 is fitted on the left hand side panel, near the bottom of the unit. If the unit is to be wall mounted the holes for the mains lead and the output lead should be drilled in the base panel, but if it is to be free-standing they must obviously be made in one of the side panels.

The only awkward aspect of construction is the mounting of the fresnel lens. As supplied this is a flat piece of flexible plastic which must be given the correct curvature by its mounting. Experiments with various types of mounting mostly proved to be less than totally reliable, and the method which seems to work best is the most simple one. A cutout measuring 47 millimetres wide by 45 millimetres high is made in the front panel, and this should be positioned such that IC1 is beneath the centre of the cutout. The sides of the cutout are bevelled on the reverse side of the panel at about 45 degrees. Using a good quality general purpose adhesive the side edges of the lens are then glued to these bevelled edges. The lens can be carefully curved to roughly the right shape prior to fitting it in place, and once fixed it seems to retain the correct curvature. Note that the lens is designed to have the smooth surface facing outwards. If desired, some plastic or card can be cut to shape and used to fill in the gaps above and below the lens. Apart from giving a neater appearance, this seals the unit from any air turbulence which might encourage spurious triggering. IC1 should be about 30 millimetres below the front of the lens, and spacers

must be used when mounting the printed circuit board so that IC1 is brought to the correct position. This will be easier if the leads of IC1 are not cropped short, as otherwise a lot of spacers might be required.

The lens will probably allow adequate light for R19 to pass through into the case, but if necessary a hole can be drilled just above the lens to permit additional light to reach R19.

fully, and the normal safety precautions should be observed.

ADJUSTMENT AND USE

Start with VR2 set in a fully clockwise direction so that the inhibit circuit is disabled, and with VR1 at a roughly middle setting. At switch-on the unit will not function as it takes a minute or so for the capacitors to settle

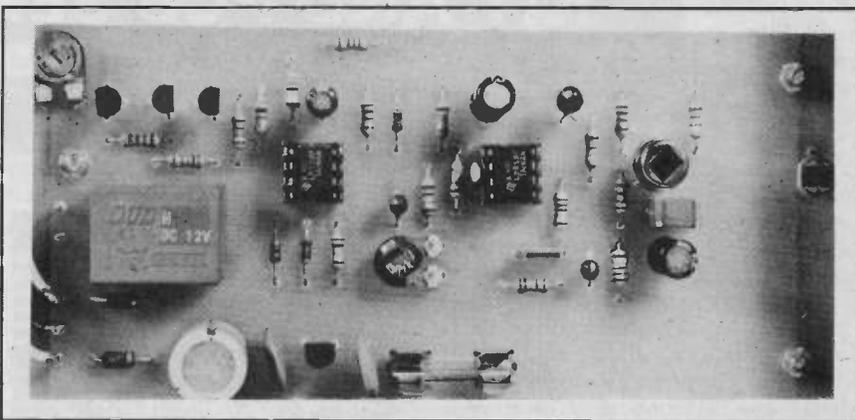


Photo 1. P.c.b. details

To complete the unit the small amount of hard wiring is added. In some applications (intruder alarms for instance) the switching action of the relay will be all that is required, and a twin lead can be used to wire the unit into the alarm or other circuit. Where the unit is to be used to control a mains load it is probably best to wire things up so that the output from the unit is a switched mains supply, including an earth lead in cases where the controlled equipment requires it. It is quite easy to wire up the unit in this way, but whenever dealing with the mains supply it is wise to proceed very care-

down and take up their normal working charges. This is a consequence of the high gain and low operating frequency range of the amplifiers in the unit, and as the unit will normally be left running continuously, or at least for long periods of time, it is not really a major drawback. Once the settling time has elapsed the unit should activate the relay when anyone goes within the monitored area. The relay should remain switched on while someone stays within this area, but bear in mind that it is movement rather than presence that is detected, and someone remaining still for half a minute or so

PASSIVE INFRA-RED DETECTOR

might let the unit return to the "off" state. Adjusting VR1 in a clockwise direction gives increased sensitivity, but adjusting it too far will simply result in frequent spurious triggering, or the relay failing to switch off when the monitored area is left vacant. The final setting of VR1 therefore has to be a compromise between sensitivity and reliability, and a little experimentation should soon reveal a suitable setting.

When the main circuit is functioning properly VR2 can be backed-off to bring the inhibit circuit into action. The easiest way to give VR2 the correct setting is to first have the ambient light at the lowest level which must activate the inhibit circuit. With one lead of R18 temporarily disconnected (remembering to disconnect the unit from the mains before working on it) back-off VR2 just far enough to switch off the relay.

Careful thought needs to be given to the positioning of the unit. The pyroelectric sensor seems to be totally immune to light, but it should not be positioned in direct sunlight (which has a significant content in the long infra-red part of the spectrum). Neither should it be placed where radiators or other heat sources are likely to give problems. Remember that it is most sensitive to someone moving across its field of view, and has

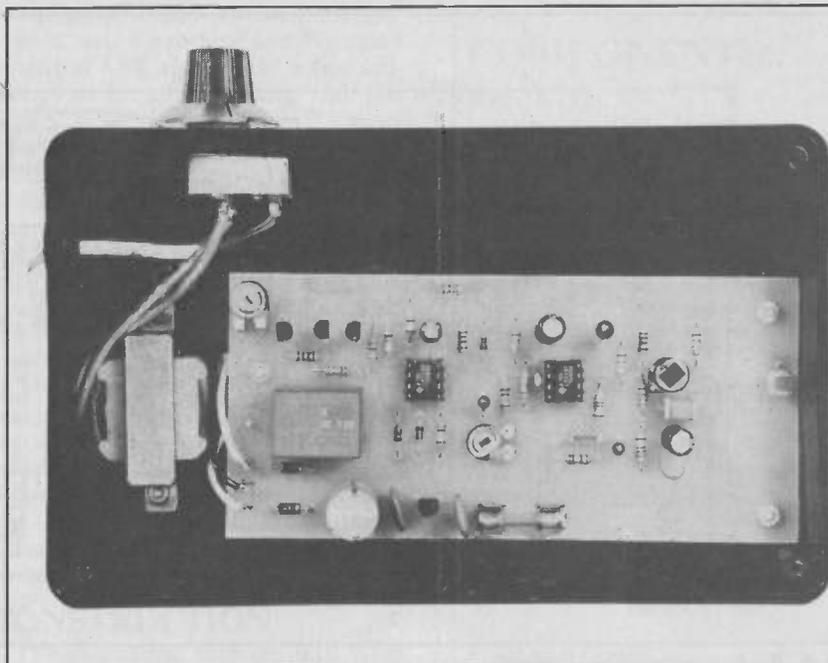


Photo 2. Internal construction details of the Passive IR detector showing the p.c.b. and transformer mounting details

minimum sensitivity to someone moving directly towards or away from the unit. Sensitivity is quite good, and if positioned at a height of about 1.5 to 2 metres in the corner of a room, it should cover practically all of even a

large room. The prototype worked well in a room measuring approximately 7 metres by 4 metres. Units of this type are less than ideal for use outside where air currents can cause spurious triggering. **PE**

KIT AND PCB SERVICE

AUDIO EFFECTS

	Unboxed	Boxed
Blow Box	SET 214 £24.83	£29.33
Flanger	SET 153 £23.95	£28.45
Frequency Changer	SET 172 £40.06	£45.56
Frequency Doubler	SET 98 £10.80	£15.30
Fuzz (Smooth)	SET 209F £15.08	£19.58
Guitar Modulo	SET 196 £19.06	£23.56
Guitar Overdrive	SET 56 £23.54	£29.04
Hand Clapper	SET 197 £22.19	£26.69
Multi-Processor	SET 189 £53.53	£61.33
Reverb - Stereo	SET 203 £32.04	£36.54
Rhythm Generator	SET 240 £54.49	£59.99
Ring Mod (Simple)	SET 179 £19.40	£23.90
Storm Effects	SET 154 £18.10	£23.60
Tom-Tom Synth	SET 190 £14.87	£19.37
Tremolo	SET 136 £11.12	£15.62
Vibrato	SET 137 £23.55	£29.05
Wah (Auto & Manual)	SET 140 £18.86	£24.36
Wah (Triggered)	SET 58 £14.34	£18.84

CONTROLLERS

Bass Boost	SET 138B	£9.12	£13.62
Compander	SET 238	£18.49	£22.99
Envelope Shaper	SET 174	£20.70	£25.20
Fader (Voice Op)	SET 167	£17.72	£22.22
Graphic Equaliser	SET 217	£20.83	£25.33
Guitar To Synth	SET 173	£35.91	£41.41
Headphone Amp Mono	SET 156M	£13.57	£18.07
Headphone Amp Stereo	SET 156S	£22.15	£26.65
Hum Cut	SET 141	£12.31	£16.81
Microphone Pre-amp	SET 144	£10.43	£14.93
Mixer 4 channel Mono Simple	SET 256	£15.49	£19.99
Mock Stereo	SET 213	£19.87	£24.37
Sustain	SET 222	£20.81	£25.31
Tone Control	SET 139	£15.51	£21.01
Treble Boost	SET 138T	£9.12	£13.62
Vocoder	SET 152	£72.15	£79.95
Vodafone Robot Voice	SET 155	£13.81	£18.31

OTHERS

Metronome	SET 143	£16.85	£21.35
Roger (2-Gong)	SET 126	£12.13	£16.63
Roger (Single)	SET 127	£9.41	£13.91
Sirens (Drum Trig)	SET 199	£19.25	£23.75
Sirens (Multi)	SET 151	£16.66	£21.16
Voice Op Switch	SET 123	£15.91	£20.41



PE & EE KITS

	Unboxed	Boxed
Chorus Flanger (PE*)	SET 235 £54.49	£59.99
Cybervox (EE*)	SET 228 £39.26	£44.76
Disco Light Control (PE*)	SET 245F £67.00	£62.50
Echo-Reverb (PE*)	SET 218 £52.16	£57.66
Mixer 4ch Mono (PE*)	SET 228M £44.45	£49.95
Mixer 4ch Stereo (PE*)	SET 228S £82.15	£89.95
Noise Gate (PE*)	SET 227 £22.11	£26.61
Phaser (PE*)	SET 226 £36.86	£42.36
Reverb - Mono (EE*)	SET 232 £22.85	£27.35
Ring Modulator (PE*)	SET 231 £40.08	£45.58
Signal Gen (PE*)	SET 233 £41.46	£46.96
Thunder & Lightning (PE*)	SET 250T £28.00	£29.50
Wind & Rain Storm (PE*)	SET 250W £26.00	£29.50

COMPUTER PROJECTS

Scope Simulator (PE)	SET 247	£39.00	£44.50
Dig Delay & Mics (PE*)	SET 234	£162.00	£198.50
Mini Sampler (PE*)	SET 246	£69.50	£75.00
Rhythm Gen (Computer)	SET 185	£29.14	£34.64
Synth To Computer	SET 184	£21.65	£26.15

FOOT PEDALS

Linkafex Chorus	SET 204	£37.26	£42.96
Linkafex Delay	SET 206	£36.39	£42.09
Linkafex Equaliser	SET 216	£19.73	£25.43
Linkafex Flanger	SET 207	£29.22	£34.92
Linkafex Fuzz	SET 209L	£17.54	£23.24
Linkafex Modulo	SET 211	£19.71	£25.41
Linkafex Overdrive	SET 215	£19.43	£25.13
Linkafex Phaser	SET 205	£28.68	£34.38
Linkafex Sustain	SET 223	£20.77	£26.47

PCB SERVICE

Chorus Flanger (Jan 85) PCBs 235A-B	(SET)	£9.06
Dig Delay-MCS (June 85) PCBs 234A-E	(SET)	£29.50
Disco Light (Dec 85) PCBs 245A-B	(SET)	£7.17
Echo-Reverb (Sep 84) PCBs 218A-B	(SET)	£8.14
Mini Sampler (Jun 85) PCBs 234A-B	(SET)	£11.00
Mixer (Jan 86) PCB 229A	(EACH)	£3.10
Noise Gate (May 85) PCB 227A		£4.35
Phaser (Oct 84) PCBs 226A-B	(SET)	£7.44
Ring Mod (Dec 84) PCB 231A		£5.27
Scope Simul (Dec 85) PCB 247A		£3.33
Signal Gen (Feb 85) PCB 233A		£4.53
Storm Effects (Jun 86) PCB 250A	(EACH)	£8.07

* = Kit as Published

PARTS & CATALOGUE

Boxes - Linkafex Robust Diecast, SET 234 19 inch steel rack, others Black Steel & Aluminium. All kits include PCBs, parts, instructions. Free wire & solder with boxed sets. Further details in Catalogue of over 70 kits - Send 9 x 4 S.A.E. (Overseas Catalogue send £1.00 or 5 IRCS).

ORDERS & POST

Mail order, CWD, CHU, PO, Access, Visa. Details correct at press, E&OE. Add 15% VAT. Add P&P - unboxed kits £1.00 each, SET 234 £3.50. Other boxed kits £1.50 each. PCBs add 70p total regardless of qty. Insurance 50p per £50. Overseas P&P in catalogue.

Text photocopies - DDL-MCS £1.50, others 50p each. Send large stamped envelope.

PHONOSONICS, DEPT. PE67,
8 FINUANCE DRIVE, ORPINGTON,
KENT BR5 4ED.
Tel: ORPINGTON 37821
(STD 0689, LONDON 66)

THE LEADING EDGE

BY BARRY FOX

Compact competition increases as demand exceeds supply

TO THE casual observer compact disc, the five inch laser-read digital audio gramophone record, looks like a licence to print money. After a slow start three years ago, five million players have now been sold round the world. Discs are in short supply and sell like hot cakes even though they cost over £10 each.

There are now ten pressing plants around the world in full production, with several more just coming on stream. Polygram's plant in Hannover, West Germany, is the largest in the world. Polygram admits that even with this year's production capacity of 50 million discs from Hannover alone, it is still a seller's market. "Marketing is increasing more rapidly than capacity," says Dieter Soine, in charge of production at Hannover. "It takes a minimum of six weeks to turn orders round".

So far city money feels safe in investing in compact disc. But the situation could soon change. New plants are popping up like mushrooms. Britain's only plant so far, Nimbus in Wales (with six million discs per year capacity) is opening a second Welsh factory, with capacity aimed at between 20 and 25 million a year. Thorn-EMI's plant at Swindon, built to press the largely unsuccessful VHD videodisc format, was scheduled to start producing saleable CDs by the end of April with a formal opening in May.

Disctec, a spin off from PR Records, is now installing clean room and pressing equipment in a new building on the Southwater Business Park at Horsham in West Sussex. Disctec raised £9 million from Investors in Industry, The Robert Fleming merchant bank, the Prudential and Coal Board Pension Fund. Phil Race of Disctec says he hopes to be producing at a rate of four million a year by September, and doubling next year. He could well be right, because the plant is run by Jim Johnston who built and de-bugged Thorn-EMI's factory.

Disctec is sufficiently confident to be advertising in the electronics press for staff to fill sixty jobs.

Mysteriously, head-hunting firm IPS is offering at least £60,000 a year for a director of operations in another, unnamed, plant. The right man for the

job could get £100,000. Nimbus and Disctec deny placing the ad. It could be Philips which is secretly converting part of its under-used Laservision videodisc plant at Blackburn to CD production. Or it could be yet another British firm planning to move into compact disc.

All the Japanese pressing plants are currently increasing production, for instance JVC is aiming for thirty million discs a year and Denon is nearing twenty-five million. Polygram has the largest CD factory in the world at Hannover. It was the first in the world because Polygram is 90% owned by Philips who invented the CD system (Siemens has the other 10%). Sony, who joined forces with Philips and improved the system, has a factory in Japan and another in Indiana, US. It was originally a joint venture with CBS, but Sony tired of the high reject rates, bought out CBS and now runs it solo. Sony has just struck a deal with the Austrian government to build a new factory near Salzburg. MPO has a factory in France and Sonapress has converted its video disc facility in Germany to CD, using Japanese presses. Tape firm ICM in Switzerland has bought CD presses from Philips and Polygram. More presses have been sold to Korea. Warner talks about pressing in Germany and America. And so it goes on . . .

Pressing discs are more difficult than making microchips—the data pits for CD are much smaller than the circuit lines on an IC. Anyone still only thinking about disc production is already too late, unless they are a large company able to withstand losses as they climb the learning curve. By the time any new venture is on stream disc supply will be matching demand and the rich pickings (factories currently charge £2 a disc pressed) will be gone. Polygram admits to a reject rate of 15%, even after nearly five years of experience. Some factories are throwing away more than they sell. Sony claims a reject rate of between 10% and 5% for its Japanese plant.

Player production is comparatively easy. The heart of a CD player is a very small motor-driven turntable, with solid state laser optics mounted on a tiny swinging arm and a package of half a

dozen highly integrated circuit chips. All come from Japan, or from Philips and its British subsidiary Mullard (Philips still has to buy its solid state lasers from Sharp in Japan). So CD is ideal for mass production.

This is why the coming of CD has shifted the balance of power in the hi fi industry away from small specialist firms to the major manufacturers. And that is why the major manufacturers wanted CD—they had lost their share of the hi-fi market to small firms.

The best a specialist hi fi firm can do is buy a package of optics and electronics from Philips (or the Japanese) and build it into a different box. Some firms even use the Philips box and a different label. Amstrad and Binatone sell budget players made from Philips components. Three British hi fi firms are now making specialist CD players. All come from the Cambridge area where most British hi fi firms are.

Meridian, Cambridge Audio and Mission all offer an 'improved' version of the basic Philips package. Because there is nothing that can be done with integrated chips and optics, all these firms seek to improve the sound by modifying, or adding to, the analogue circuitry in the player which works with chips. The main modification is to the filters which get rid of spurious sounds made by the digital processing. But there is dispute over how serious this problem really is.

Philips engineers are tactful, but unenthusiastic, about these modifications to their package. Jos Timmermans of Philips factory in Hasselt, Belgium (which makes 15 000 CD players a day) says he and his engineers have measured and listened to the modified players. They can detect differences in sound created by tweaking the circuits used around the Philips chip set. A slight roll-off, says Timmermans, may "give a softer sound and suit local taste . . . but it's a niche market".

This is a polite way of saying that tweaked players can disguise the slightly harsh sound you get from less-than-perfect discs. A new chip set due soon from Philips and Mullard will improve the sound without filtering. Needless to say Philips' own factories will get the chips before anyone else. PF

BETTER USE OF DRY BATTERIES

PART TWO BY ROD COOPER

We have the technology!
—for cost-cutting dry cell charging

* ACTUALLY Pg 434
WW OCT 51!!
RE ACTIVATING
DRY BATTERIES

WHY bother to recharge dry cells when sealed NiCd cells are available? Part One last month listed some of the shortcomings of NiCds. These are:

- 1) Much lower capacity (about 50% less than alkaline-manganese dry cells)
- 2) Sealed sintered NiCds discharge themselves rapidly on standing
- 3) Premature failure of NiCds due to dendrite formation
- 4) Fall-off in performance due to electrolyte decomposition
- 5) Electrolyte leakage—the spreading white corrosive deposit found on the tops of NiCds
- 6) Higher initial cost.

For better reliability, better charge retention and superior capacity (in the case of alkaline-manganese) dry cells are often to be preferred. Systems for recharging dry cells have been around for many years, but have never been popular due mainly to the black propaganda put out by the manufacturers, but also due to the fact that cells used to be cheap enough to throw away. The dry cell market is worth about £100 million per year in the U.K. alone, so we can hardly blame the manufacturers for trying to protect their own interests. If recharging were to be generally adopted, this market would shrink to under £20 million per year. The saving in raw materials and industrial effort would be enormous. However, the idea that it is dangerous to recharge dry cells seems to have taken root in the U.K., assisted I am sorry to say by the dissemination of the manufacturers propaganda by the technical press.

It is easy to disprove this notion—simply recharge a dry cell using the circuit in Fig. 9 and note the total absence of danger! Fortunately there is now plenty of other evidence from people who have been practising recharging for several years to show that recharging can be perfectly safe—sometimes achieving 20 recharges per cell.

In this respect the conservation-conscious Japanese are—typically—way ahead of us. In Japan they have *actually made it illegal* for a

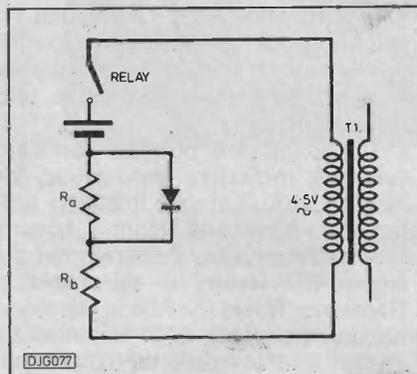


Fig. 6. Biased a.c. current method

manufacturer to claim that dry cells are not rechargeable, following a celebrated court case in 1975. The words “not rechargeable” or “dangerous to recharge” have disappeared from the sides of batteries sold in Japan, but curiously the same products sold in this country still bear this wording, specially for export. In Japan, recharging of dry cells is officially condoned, saving Japan a small fortune in the process. If only we could follow their example in this country—but unfortunately vested interest will ensure this does not happen.

What are the facts? In the U.K. it is said that there exists a danger of explosion if a dry cell is recharged. I will shortly show that this is utter nonsense.

I should make it absolutely clear at this point that there are five golden rules for recharging dry cells, as follows:

- 1) Recharge cells individually, not connected together as a battery. This restricts the technique to single cells—AA, C and D. This is because if a fault developed in one cell, the other cells being charged could be given an excessive current. A constant current technique could be used to overcome this but would be difficult to implement using the method about to be described—the Periodic Current Reversal Method.

- 2) Limit the current, so that if a faulty cell goes short-circuit it cannot dissipate excessive power.

3) Limit the time of recharge so that overcharging does not occur.

4) Do not allow cells to become fully discharged. For the best results, it is necessary to stop short of full discharge, and recharge fairly soon. Discharged cells that are left for weeks do not accept a recharge. This is because irreversible chemical changes take place inside the cell.

5) Most important of all, do *not* use d.c.

The bad effects of using d.c. were detailed in an article in Wireless World of August 1955 by R. W. Hallows, and readers who want more information can find this magazine in most reference libraries. Basically, using d.c. results in overheating and also erosion of the zinc electrode, giving erratic results and generally poor figures for the number of recharges possible. In contrast, using a biased a.c. current such as that used in Fig. 6 gives negligible heating of the cell and causes no zinc erosion.

It uses the Periodic Current Reversal (PCR) process already mentioned to keep the zinc in a hard, compact state rather than the spongy form produced by d.c., and is a development of methods used in the electroplating industry for many years to give hard, shining non-dendritic plating of certain metals. PCR consists of applying a small current in the reverse direction to the main recharging current at regular intervals—in the case of Fig. 6 at 10 millisecond intervals as the mains frequency is used. A typical waveform produced by this circuit is shown in Fig. 7. Note that the forward-charge time is less than the reverse-charge time because of the 1.5V pedestal

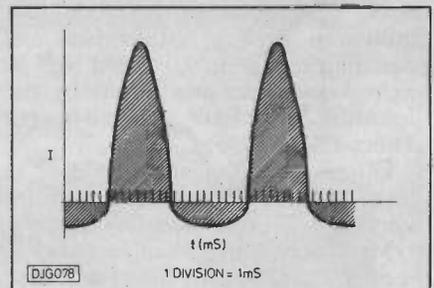


Fig. 7. PCR waveform

BETTER USE OF DRY BATTERIES

voltage presented to the forward current by the cell itself. The ratio of forward to reverse charge is about 4 or 5 to 1.

SAFETY

Recharging is safe provided you follow the rules about limiting time, current and not using d.c., because dry cells from responsible manufacturers have a built-in pressure release system. This fact is not well publicised, probably because it could be abused by non-technical people. Usually it consists of a weak spot in the case which can burst in a controlled fashion if internal pressure becomes too great. There are variations on this theme—for example the release mechanism in the Duracell range is a wax plug in a small release vent at the bottom of the case (Fig. 11) which when forced out allows gases to escape into the bottom of the case and eventually to seep to atmosphere. (The outer case is not air-tight like the inner case.)

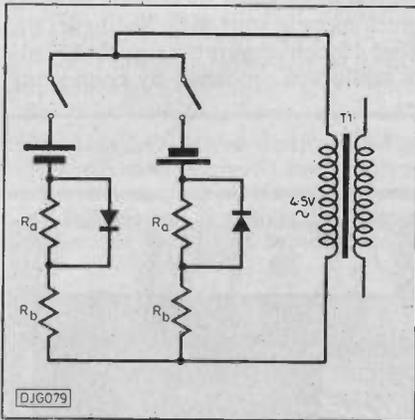


Fig. 8. Balanced-pair charging

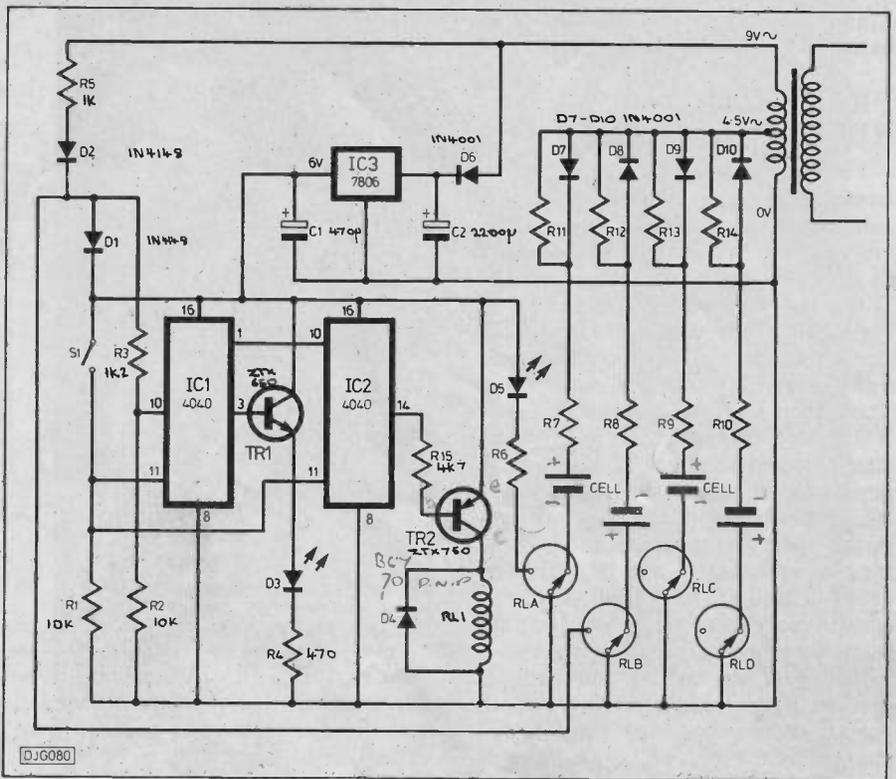


Fig. 9. A practical charging circuit

Clearly the capability of any vent mechanism is limited and would not prevent a cell that had, for instance, been thrown on a fire from disintegrating with considerable force. Why, then, do manufacturers put a safety vent there? It can't be to allow recharging of their batteries! There are two reasons. Firstly if one cell in a battery is accidentally put in the wrong way round, it can be driven in reverse by the other cells, and this can generate gas pressure by decomposing the electrolyte. Secondly, if one cell in a bat-

tery is exhausted before the others, the cells that still have some charge left can again drive this cell in reverse with the same results. This often happens when half-used cells are put in with fresh cells, and would lead to frequent accidents if it were not for the safety vent.

However, having a safety vent does provide a convenient safety factor for recharging if the proper methods are used. I have done some experiments to show what outrageously high currents need to be used to cause cell damage. The results are shown in Photos 1 and

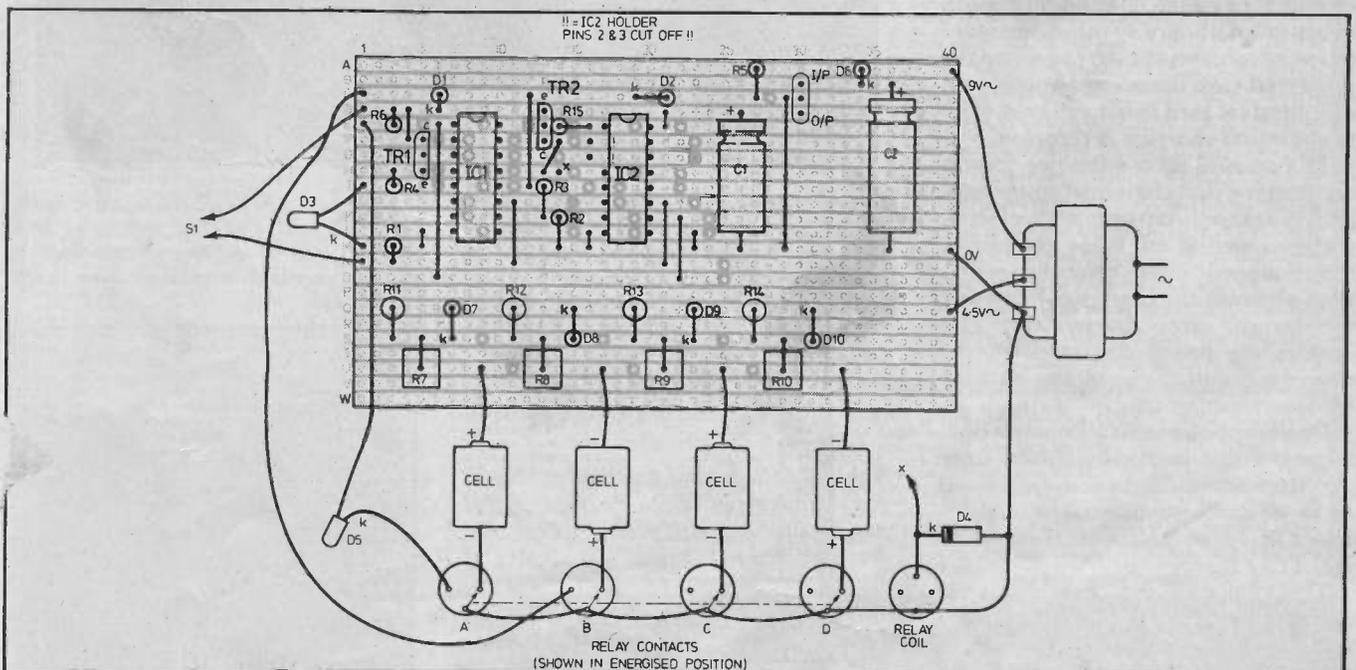


Fig. 10. Stripboard layout

BETTER USE OF DRY BATTERIES

2 and they show that recharging is basically a very safe process.

PRACTICAL RECHARGING CIRCUIT

The circuit shown in Fig. 6 is unbalanced and gives an undesirable d.c. component in the transformer. Cells are therefore charged in balanced pairs as shown in Fig. 8.

The complete charger is shown in Fig. 9. The component values are for D size ordinary zinc-carbon cells, and Table 2 gives values for other sizes. The circuit works as follows; IC1 and IC2 form a timing circuit to limit the charging time to about 12 hours. This period was chosen as it gave the possibility of overnight charging without pushing the charge-acceptance of the average zinc-carbon cell too far. The CA4040 used for IC1 and IC2 is a 12-stage binary counter, and two are cascaded to give a 24-stage counter.


If IC1 is fed with a 50Hz signal derived from the transformer secondary, then the output from stage 22 will change state every 11 hours 39 minutes. The 50Hz signal is obtained via R5 and D2. D1 prevents the input from exceeding the line voltage, assisted by potential divider R3 and R2. Switch S1 is a momentary push-button type which starts the count. The output of IC2 is low when S1 starts the count, turning transistor TR2 hard on and energising the relay. This relay is a 4-pole change-over type. The cells are connected to the charging circuits D5, R11, R7, etc.

At the first change of state after 11 hours 39 minutes, the output goes low, turning the relay off, stopping further charging. To prevent the next change of state turning the relay back on again in another 11 hours 39 mins, one set of the relay contacts is used to ground the input and stop the count. Another set of contacts is used to light an l.e.d. (D5) to show that charging is complete.

TR1 and D3 form a flashing indicator showing that charging is in process and is taken from output 5 of IC1, giving a period of 0.32 seconds. A centre-tapped mains transformer is used to power the charging circuit and the control circuit separately. This enables the power dissipated in the charging circuit to be kept low by using the lower voltage tap.

One point of practical construction; keep the cell holders separate from the electronics. Then if a faulty cell leaks, no damage will be done. A strip-board layout of the circuit is shown in Fig. 11.

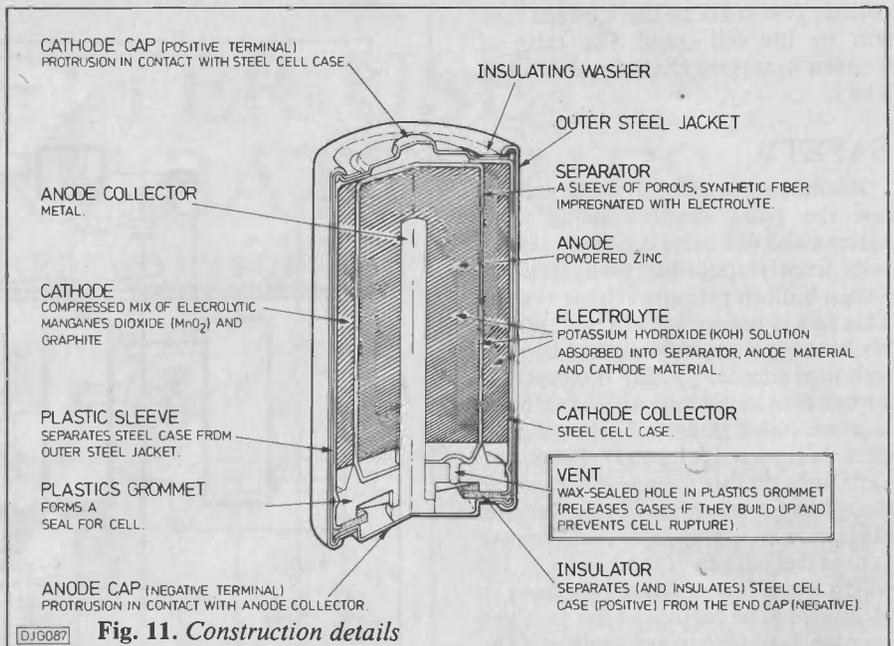The values of the charging-circuit resistors in the table of Fig. 7 are for ordinary zinc-carbon cells. The energy delivered to each cell with the values given is less than the rated capacity, thus avoiding overcharging. If you look



back to rule 4 you will recall that some capacity had to remain in discharged cells for the recharging process to be effective, so when this is taken into account, a nearly-full charge can be expected for a zinc-carbon cell.

For alkaline-manganese cells, the energy delivered will fall far short of the cell capacity since these cells have so much more to start with. So, these cells need a much longer recharge time. This is easily accomplished by connecting

Photo 1. Cells 1 to 4 are different types and make of cell which have been overcharged by a factor of ten times to show how safe it is. The recharge current was 1 amp (five times that recommended) for 24 hours (twice as long as that recommended). To make the test more severe, plain smoothed d.c. was used. Result: no sign of leakage, no sign of splitting or bursting. Cell No. 2 developed a slight bulge after 8 hours but nothing further happened. This cell was sectioned and compared with an uncharged cell.



Photo 2. Another set of cells was charged at 0.2 amp using PCR for 5 days, an overload of ten times the recommended rate. No sign of leakage or splitting of the case was seen. A sectioned view of one of these cells shown below on the right compared with an uncharged cell on the left, confirms no distortion of the case or internal components.

As all these tests have been repeated many times it is safe to say that recharging with PCR at 1/10 of the charge rate used is harmless provided the rules set down in the text are adhered to.

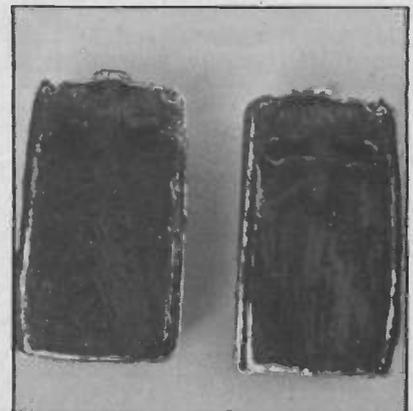


Table 2. Alternative component values for various types of cell. It is advisable not to alter any component values unless specified in the text.

Cell size	D	C	AA	
R7,R8,R9,R10	6R8	12R0	47R0	5W
R11,R12,R13,R14	68R	120R	470R	2W

BETTER USE OF DRY BATTERIES

the base of TR2 via R15 to pin 15 of IC2 instead of pin 14. This doubles the timing period to 23 hrs 18 minutes—about a half-charge for an alkaline cell. This is fine for topping-up half-discharged cells. If you have nearly fully discharged the cell, then you can use pin 1 of IC2 for a 46 hr 36 minute charge, giving a full or near-full recharge.

It is not recommended to alter the charging-circuit resistors. **PE**

A PRACTICAL CASE STUDY

The two CB radios in Photo 3 illustrate what can be used by combining the methods described in Part 1 and Part 2 of this series of articles. The radio on the left is powered by a PP3 alkaline-manganese dry battery and lasts for about 8 hours with careful use at a cost of £1.89. (This radio refused to work on zinc-carbon PP3.)

The radio on the right has been converted to run on a single "C" size of alkaline-manganese cell and a Verkon V12 dc/dc converter. It gives about 6 hours duration, but at a cost of only 69p—a 50% saving. However, as we have just seen, single cells are suitable for recharging but PP3 batteries are not. The Verkon/single cell set-up will cost at least ten times less to run.

In a year's operation, this particular radio saved a total of over £20, more than it originally cost to buy.

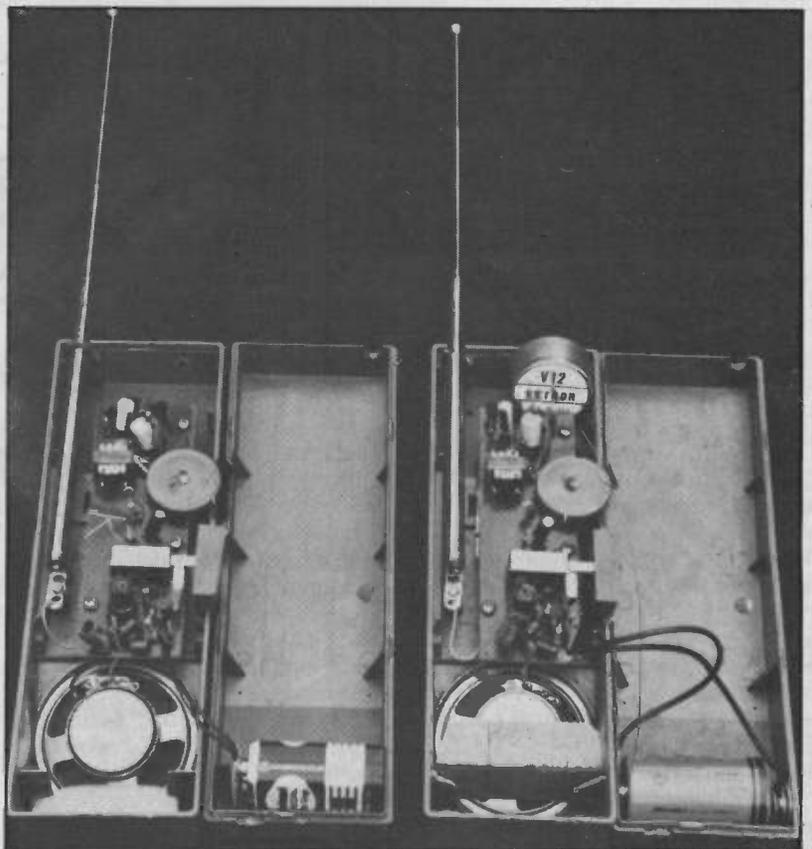


Photo 3. Practical case study—cheap CB operation

BI-PAK BARGAINS

VALUE PACKS

Pak No	Qty	Description	Price
VP1	300	Assorted Resistors Mixed Types	£1.00
VP2	300	Carbon Resistors 1/2-1/2 Watt Pre-Formed	£1.00
VP3	200	1/8 Watt Min Carbon Resistors Mixed	£1.00
VP4	200	1/2-1 Watt Resistors Mixed	£1.00
VP5	200	Assorted Capacitors All Types	£1.00
VP6	200	Ceramic Caps. Miniature - Mixed	£1.00
VP7	100	Mixed Ceramic Disc. 1pf-56pf	£1.00
VP8	100	Mixed Ceramic Disc. 68pf-015pf	£1.00
VP9	100	Assorted Polyester/Polystyrene Caps.	£1.00
VP10	60	2200 Caps. Metal Foil Mixed	£1.00
VP11	50	Electrolytics - All Sorts	£1.00
VP12	40	Electrolytics - 47mf-150mf Mixed Vts.	£1.00
VP13	30	Electrolytics - 150mf-1000mf Mixed Vts.	£1.00
VP14	50	Silver Mica Caps. Mixed Values	£1.00
VP15	25	01/250V Min Layer Metal Caps.	£1.00
VP16	50	Wirewound Res. Mixed Wound Values	£1.00
VP17	50	Metres PVC Single Strand Wire Mixed Cols.	£1.00
VP18	30	Metres PVC Multi Strand Wire Mixed Cols.	£1.00
VP19	40	Metres PVC Single/Multi Strand Wire	£1.00
VP20	6	Rocker Switches 2a 240V	£1.00
VP21	10	Assorted Switches Slider/Push Etc.	£1.00
VP22	200	3/4 Inches Total Copper Clad Board	£1.00
VP23	10	40mm Slider Pots, 100K Lin	£1.00
VP24	10	125" Cler Showing Red LED's	£1.00
VP25	10	Mixed Shape and Colours LED's	£1.00
VP26	15	Small 125" Red LED's	£1.00
VP27	15	Large 2" Red LED's	£1.00
VP28	10	Rectangular 2" Red LED's	£1.00
VP29	30	Assorted Volts Zeners 250mw-2w	£1.00
VP30	10	Assorted Volts Zeners 10w Coded	£1.00
VP31	10	5a SCR's T066 50-400v Coded	£1.00
VP32	20	3a SCR's T066 Up To 400v Uncoded	£1.00
VP33	200	Sil. Diodes Like IN4148	£1.00
VP34	200	Sil. Diodes Like DA200/BAK13/18	£1.00
VP35	50	1a IN4000 Diodes All Good Uncoded	£1.00
VP36	100	Sq Inches Total Copper Fibre-Glass Board	£1.00
VP37	8	Black Pointer Knobs 1/4w Std	£1.00
VP38	100	Sil. Trans NPN Plastic Coded Data	£3.00
VP39	100	Sil. Trans PNP Plastic Coded Data	£3.00
VP40	40	TTL I.C.'s All New Gates - Flip Flop - MSI Data	£4.00
VP41	40	CMOS I.C.'s All New Inc Data	£4.00
VP42	10	Black Heatsinks FR TO-3 TO-220 Drilled	£1.00
VP43	4	Power-Fin Heatsinks 2 x TO-3 2 x TO-66	£1.00
VP44	15	Ass. Heatsinks TO-18 TO-3 TO-18-220	£1.00
VP45	50	BC107/8 NPN Transistors Good Uncoded	£1.00
VP46	50	BC177/8 PNP Transistors Good Uncoded	£1.00

Pak No	Qty	Description	Price
VP47	5	Pairs NPN/PPNP Plastic Power Trans. Data 4a	£1.00
VP48	30	Asst. Sil. Rects. 1a-10a Mixed Vols	£1.00
VP50	60	NPN Sil. Switching Trans TO-18 - TO-92	£1.00
VP51	60	PNP Sil. Switching Trans TO-18 - TO-92	£1.00
VP52	25	Asst. Audio Plugs Phone-Din-Jack Etc.	£1.50
VP53	25	Asst. Audio Sockets Phone-Din-Jack Etc.	£1.50
VP54	20	Asst. I.C. Dtl Sxts, 8-40 Pin	£2.50
VP55	10	I.C.'s 4116 Memories	£2.00
VP56	100	Semiconductors From Around the World	£4.00
VP57	25	Opto Special Pack. Assorted	£5.00
VP58	10	Hybrid LED Colour Displays	£4.00
VP59	20	Asst. I.C.'s Coded, Linear, Etc.	£2.00
VP60	100	All Sorts Transistors, NPN/PPNP	£1.00
VP62	1	Electronic Buzzer, 3v, 25MA	£0.95
VP63	1	Electronic Buzzer, 6v, 25MA	£0.95
VP64	1	Electronic Buzzer, 9v, 25MA	£0.95
VP65	1	Electronic Buzzer, 12v, 25MA	£0.95
VP66	1	TECASBOTY '86, Bargain Pack	£8.00
VP67	1	Telephone Pick-Up Coil	£1.25
VP68	1	Pillow Speaker	£1.45
VP69	1	2 Metre Metric/Inches Tape	£1.75
VP90	1	Electronic Sign, 12v DC	£6.50
VP95	1	Small Plastic Vise, with suction base	£1.75
VP96	1	Signal Injector, Push Button Operation	£2.50
VP97	1	Logic Probe	£10.50
VP98	1	Current/Pol Checker	£3.25
VP99	1	Universal Tester with Ceramic Buzzer	£5.00
VP100	1	Electrical Circuit Tester	£1.00
VP101	1	Battery Checker, suitable all types of batteries	£4.50
VP102	1	12 Piece Tool Kit and Case	£7.50
VP103	1	6 Piece "Stanley" Screwdriver Set	£3.50
VP104	1	Ratchet Screwdriver Kit, 4 blades	£1.75
VP107	1	Piezo Buzzer, miniature 12v	£1.25
VP108	1	Piezo Buzzer, Miniature 240v	£1.25
VP110	1	Antenna Switch, 2 way	£4.50
VP114	1	Antenna Switch, 3 way	£4.75
VP115	1	High Pass Filter/Suppressor, CB/TV	£0.50
VP116	1	Low Pass Filter, VHS/TV Band	£3.00
VP120	1	FM Monitor, 2 meter Band	£4.50
VP127	1	Remote Control Switch	£1.00
VP128	1	Miniature FM Transmitter/Babyphone	£5.50
VP130	6	RED 7 Seg. CC 14mm x 7.5mm RDP	FND353 LED £2.00
VP131	4	GREEN 7 Seg. CA 8" LDP	XAN8520 LED £2.00
VP132	5	RED 7 Seg. CC 8" LDP	XAN8940 LED £2.00
VP133	6	RED Over-Flow 6" 3 x CA 3 x CC	6630/50 LED £2.00
VP134	5	GREEN Over-Flow 6" CA	XAN8530 LED £2.00
VP135	5	RED 7 Seg. CA 3"	XAN3061 LED £2.00
VP136	3	DUAL RED 7 Seg. 5" CA DL527 DPR	DISPLAYS LED £2.00
VP137	3	DUAL RED 7 Seg. 5" CA DL727 DPR	DISPLAYS LED £2.00

Pak No	Qty	Description	Price
VP138	20	Assorted LED Displays - Our Mix with Data	£6.00
VP139	1	Pick-Up Tool, spring loaded	£1.75
VP140	50	Precision Resistors 2-1% Tol.	£1.00
VP141	40	IN4002 Sil. Rects. 1a 100v Preformed Pitch	£1.00
VP142	4	40a Power Rectifiers Silicon T048 300PIV	£1.00
VP143	5	BY187 12KV Sil. Diodes in carriers 2.5mA	£1.00
VP144	4	100K in Multi-Turn Pots, ideal vari. cap tuning	£1.00
VP145	10	Assorted Pots, inc Dual & Switched Values	£1.00
VP146	25	Solid Tantalum Caps, Mixed Values	£1.00
VP147	1	Pair Opto Coupled modules	£0.80
VP148	30	Presets, Horizontal and Vertical, mixed values	£1.00
VP150	20	BC1838 Sil. Trans. NPN 30v 200mA Hfe240+	T092 £1.00
VP151	25	BC1718 Sil. Trans. NPN 45v 100mA Hfe240+	T092 £1.00
VP152	15	T1330 Sil. Trans. NPN 40v 400mA Hfe100+	T092 £1.00
VP153	15	T1591 Sil. Trans. PNP 40v 400mA Hfe100+	T092 £1.00
VP154	15	MPSA56 Sil. Trans. PNP 80v 800mA Hfe 50+	T092 £1.00
VP155	20	BF495 Sil. Trans. NPN eqvt. BF173 H.F.	T092 £1.00
VP156	20	BF495 Sil. Trans. NPN eqvt. BF173 H.F.	T092 £1.00
VP157	15	ZTX500 Series Sil. Trans. PNP Plastic	£1.00
VP158	15	ZTX107 Sil. Trans. NPN eqvt. BC107 Plastic	£1.00
VP159	15	ZTX108 Sil. Trans. NPN eqvt. BC108 Plastic	£1.00
VP160	20	E5024 Sil. Trans. PNP eqvt. BC214L	T092 £1.00
VP161	25	BC183L Sil. Trans. NPN 30v 200mA	T092 £1.00
VP162	5	SJE5451 Sil. Power Trans. NPN 80v 4A Hfe20+	£1.00
VP163	2	NPN/PPNP pairs Sil Power Trans like SJE5451	£1.00
VP164	4	2N6289 Sil. Power Trans. NPN 40v 7A Hfe30+	£1.00
VP165	6	BFT33 NPN Sil. Trans. 80v 5A Hfe50-200 T039	£1.00
VP166	5	BFT34 NPN Sil. Trans. 100v 5A Hfe50-200 T039	£1.00
VP167	1	BUY89C NPN TO3 VCB 50V 10A 100w Hfe15+	£1.00
VP168	10	BC478 eqvt. BCY71 PNP Sil. Trans. T018	£1.00
VP169	10	BX521 eqvt. BC394 NPN Sil. Trans. 80v 50mA T018	£1.00
VP170	10	Assorted Power Trans. NPN/PPNP Coded & Data	£1.00
VP171	10	BF355 NPN TO-39 Sil. Trans. eqvt. BF258 225v 100mA	£1.00
VP172	10	SM1502 PNP TO-39 Sil. Trans. 100v 100mA Hfe100+	£1.00
VP173	150	De-soldered Sil. Trans. from boards. 10mm leads. Good.	£1.00

BI-PAK BOOK BARGAINS 1986

"NO VAT"

- BPX1 4 Different popular books on Electronics Projects. Hours of interesting reading and construction. Normal Retail £8.00. Bi-Pak Special Offer £6.00.
- BPX2 IC Projects Book, including IC Outputs. Book, Digital, CMOS and Op Amps & TTL Data Book. Normal Retail £6.50. Bi-Pak Special Offer £4.00.
- BPX3 3 Computer Books on Programming - Micro Processors - ZX81 etc. Normal Retail £8.00. Bi-Pak Special Offer £2.50.
- BPX4 1 International Transistor Equivalents Guide, Babani Publ. Latest edition BP65. Plus "FREE" with Bi-Pak's compilations, 10 popular Sil. Trans, valued over £1.00. Bi-Pak Special Offer £2.95.
- BPX5 1 IC 555 Projects Book (Timer) 187 pages, over 50 project circuits to build and Data, etc. on IC555 Timers. Plus "FREE" with Bi-Pak's compilations, 4 x IC555, valued at £1.20. Bi-Pak Special Offer £2.50.

PLEASE NOTE "NO VAT" ON BOOKS.

Use your credit card. Ring us on 0763-48851 NOW and get your order even faster. Goods normally sent 2nd Class Mail.

Remember you must add VAT at 15% to your order. Total Postage add £1.00 per Total order.

BI-PAK

Send your orders to Dept PE BI-PAK PO BOX 6 WARE, HERTS

TERMS CASH WITH ORDER, SAME DAY DESPATCH. ACCESS, BARCLAYCARD ALSO ACCEPTED. TEL 0763-48851. GIRO 388 7006 ADD 15% VAT AND £1.00 PER ORDER POSTAGE AND PACKING

MULTIFUNCTION COUNTER

PART 2 BY MIKE DELANEY

The counter takes shape build it—test it—use it!

THIS month, the final part of this project, deals with all the necessary details to build and get the counter working.

When first setting up, and *before* inserting any of the chips, it is necessary to test the trigger threshold of the overvoltage, 'crowbar', circuit, and this is done using an external bench supply in place of the mains supply of the circuit. The procedure will be fully explained later.

R105 and D101 are both mounted on the front panel. Had it not been necessary to blank the display in HF and 0-01 mode then these components would not have been necessary, the meter's own display would have been indication enough of power-up. Again, the brightness of the l.e.d. can be adjusted to your own taste by changing the value of the resistor. In amongst the line-up of i.c.s on the circuit diagram is C20, a 10 μ tant. This is important as it decouples the supply to the TTL chips.

Connections between the two boards are conveniently positioned, and in the prototype push-on connectors were used, though this was mainly for convenience. The edge connections are numbered and lettered. The system used should leave no doubt as to whether it's a real, or a hook-up fault. A1 goes to A1, and so on.

On the circuit diagram these connections appear in boxes. At first it may appear a little confusing as to which 'D' is which, but a little thought will soon make it clear.

CONSTRUCTION

Figs. 5 and 6 show how the p.c.b.s should look when completed, refer to them while mounting the components.

It is very easy to solder a component in wrongly, but a different job to remove it! *A quick double-check is a good idea.*

If you do not have the p.c.b.s plated-through, that is, all the holes have a covering of tracking running through them, then you have a bit more work to do at this stage. Starting with the smaller board, determine which is the front—it's printed on, bottom left.

Locate and solder in R105 first. This is the only resistor mounted on this side.

There are quite a lot of stitch-throughs needed on this board. I think the easiest way of deciding which is a component hole, and which is a stitch, is to mount all the components first. If this is the way you wish to work, then now is the time to mount the displays. These are easy to locate. The danger is that you will get one upside-down. If this should happen I would suggest writing off the display by cutting the legs off it and removing these one at a time. It seems expensive, but it's cheaper than a new p.c.b.!

Before soldering the displays in place have a quick squint along them, lining them up soldier-fashion, just to make the display look that bit better when it's done. Having done the display, now position the switches. Be careful to make sure that you have the momentary switch, S104, in the right place, and the right way up, that is in the off position with its lever in the up position. Double check and line them up again before soldering. Do not solder in D101 yet, since its finished position is dependent upon the spacing between the p.c.b and the fascia panel.

Turn the board over and mount the turret tags, resistors and capacitor, push-on connectors, and S105 and 106. This should leave only the stitch-

NOTE: This project is a 200MHz counter, not 20MHz as indicated on the cover of the June issue

through's and the l.e.d. to go. Solder in the stitch-throughs and carefully check the board. Connections to the switches are all made from the display board. Studying the layout drawing will help, but again, I goes to 1, A to A and so on. Now on to the counter board.

Once again, get it right way up and proceed in the same way as you've just done with the display. Use sockets for all the i.c.s except the prescaler. In my prototype I found that a socket appeared to increase noise pick-up and, of course, sockets are not a good idea with high frequencies.

Start with the diodes, then the resistors, and slowly build up the height of the board. The last soldered component to fit is the mains transformer. *Do not fit any i.c.s yet*, and don't bother with the FS2 either. Note also that some of the components must be soldered on both sides. This is most important if yours is a non-plated-through p.c.b. These have also been marked, so should offer no great problem. Having completed this, check for errors, eg, caps reversed, missing stitch-throughs, components soldered on both sides when necessary, and so on.



MULTIFUNCTION COUNTER

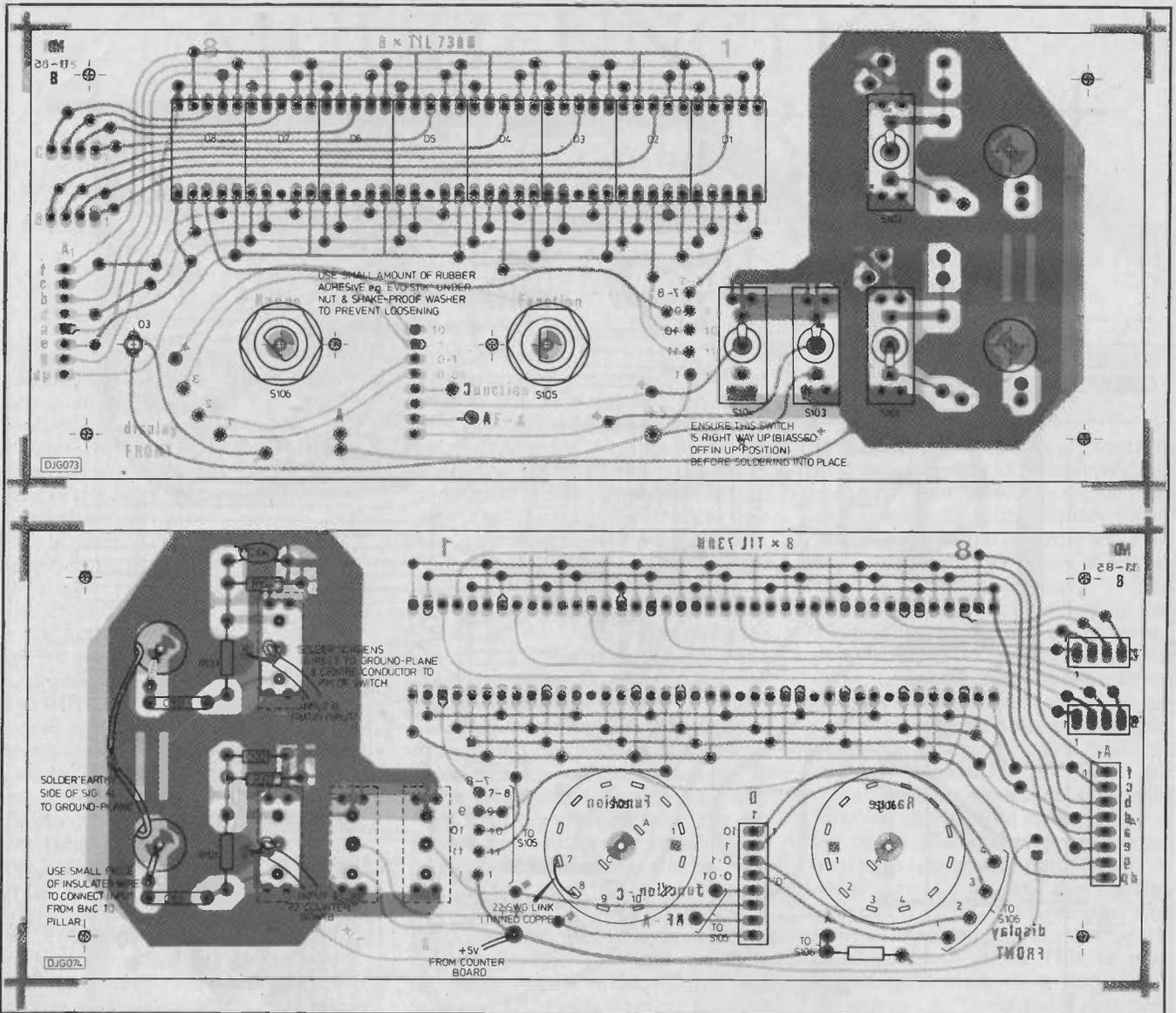


Fig. 6. Front panel p.c.b. layout details, front and rear. (less than actual size)

loads as well. If you are not sure the one you have is suitable, short the output leads together. If the PSU starts to smoke, or the leads melt then it probably is not suitable, and don't send me the bill!

2. A 20K ohm/V or better d.c. meter with a 10V range. If you can get hold of one of the digital jobs, so much the better.

Proceed as follows: Connect the meter from the GND loop to the 5V loop and the PSU, set on 4V, low to the E connection and high to the output side of the FS2 clip. Check that the meter reads 4V. Slowly increase the output of the PSU, carefully monitoring the voltage, until it suddenly goes to zero. This is the switching threshold of the thyristor. It will be necessary to remove the supply to unlatch the thyristor. This can also be achieved by shorting out the leads to the board. Reduce the voltage to 5V and repeat. Do this until you are sure you've got it right.

The answer you should have must lie between 5.25 and 5.9V. Unfortunately, with this type of circuit there is not a lot you can do if it isn't. Selecting another zener is the only way. If the answer you have is less than 5.2V then the crowbar may latch on 'good' voltages, and if it doesn't switch until the input exceeds 6V then it may allow the 7216 to be damaged in any case. A lot will depend on the gate requirements of the particular CSR you are using. One possible solution might be to replace the single zener with a 4V7 type in series with a forward conducting silicon diode. Any one in the 1N4001 range will be suitable in this position.

Having said this, the author had no trouble with any CRS in the recommended range. The crowbar turn-on varied by less than 200mV over a sample of six CSRs tried. Having satisfied yourself that this bit of the circuit is functioning correctly, remove the PSU, meter and link from the under-

side and install the regulator. When fitting it smear a little heatsink compound on it first, and don't bother fitting any insulating washer. Bolting it down before soldering it in place will reduce any strain on its internal connections. Replace the meter and PSU and check the voltage on the 5V loop is 5V \pm 100mV. If this is okay, power down and fit all the chips, needless to say... with care!

FINAL TEST AND SET-UP

Having checked the crowbar circuit it is now time to run the rest of the circuit. Recheck the orientation of the i.c.s and then connect the two p.c.b.s together. Make sure that the TP4 link is in place and apply the power again. The display should remain blank for about one second after this, and then all the eight digits should light all segments and decimal points. D101 should also light.

The display should be stable, not visibly strobing through. Checking the

MULTIFUNCTION COUNTER

current consumption should show a steady flow of about 250mA. Disconnect and reconnect the supply and check that all digits come and go together and one or two do not show a tendency to surge in their brightness. If this occurs, the probable cause is the master oscillator and will need sorting out before proceeding. If all appears well, disconnect the PSU and carefully cut and bend apart the TP 4 loop. Reconnect the supply and check the display as before, but now change the range and confirm this is working. *Do not forget that in HF-01 the display should be completely blanked.*



Recheck the current. With three zeros lit the consumption should be in the region of 130mA. If it should differ by any large amount check for overheating components first, then remove the power and give both boards a close visual check. So far you have determined the counter, display, switches with their associated logic, and wiring between the two boards is okay. All that's left to test are the two input amplifiers.

On the display board connect the input side of C101 and C102 to 0V with short lengths of insulated wire. Connect the meter between 0V and TP1. Set it to 10V d.c. Connect the PSU and monitor the voltage on TP1 while adjusting VR1 gently from end to end. The voltage should swing between .5V and 4V. Set to 1.5V to start with, and if you have a 'scope, check the amount of noise present on TP1. This should be less than 10mV of high frequency, and about this much low frequency. Any more than this will effect triggering on low amplitude signals.

Repeat this with Amp B, this time adjusting VR201. This establishes that the d.c. coupling in the amps is correct, and sets it to be near the switching threshold of IC4a and IC4b.

To set the amps to optimum sensitivity a sine wave audio generator will be needed. Remove the shorts from the display board and make a temporary connection to the BNC sockets. Remove the meter and set the generator to 1KHz at 100mV RMS. Deselect the attenuator (X1), and select LF & 1 Sec gate time. Trigger selection does not matter at this stage. Connect the generator to input A, and carefully adjust VR1 until the display shows 1.000, and is stable. Try rocking the pot back and forth to get the feel of the span. Now, by gradually reducing the input voltage and adjusting the pot it should be possible to get a stable display with as little as 20mV RMS input.

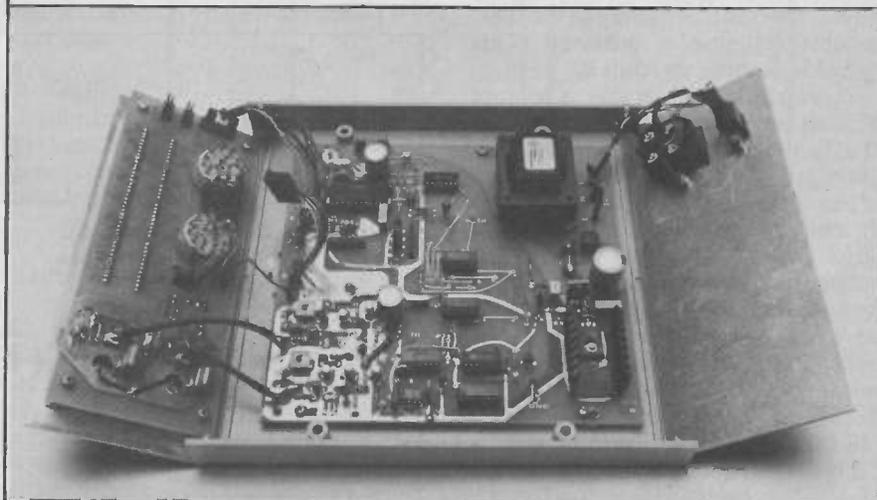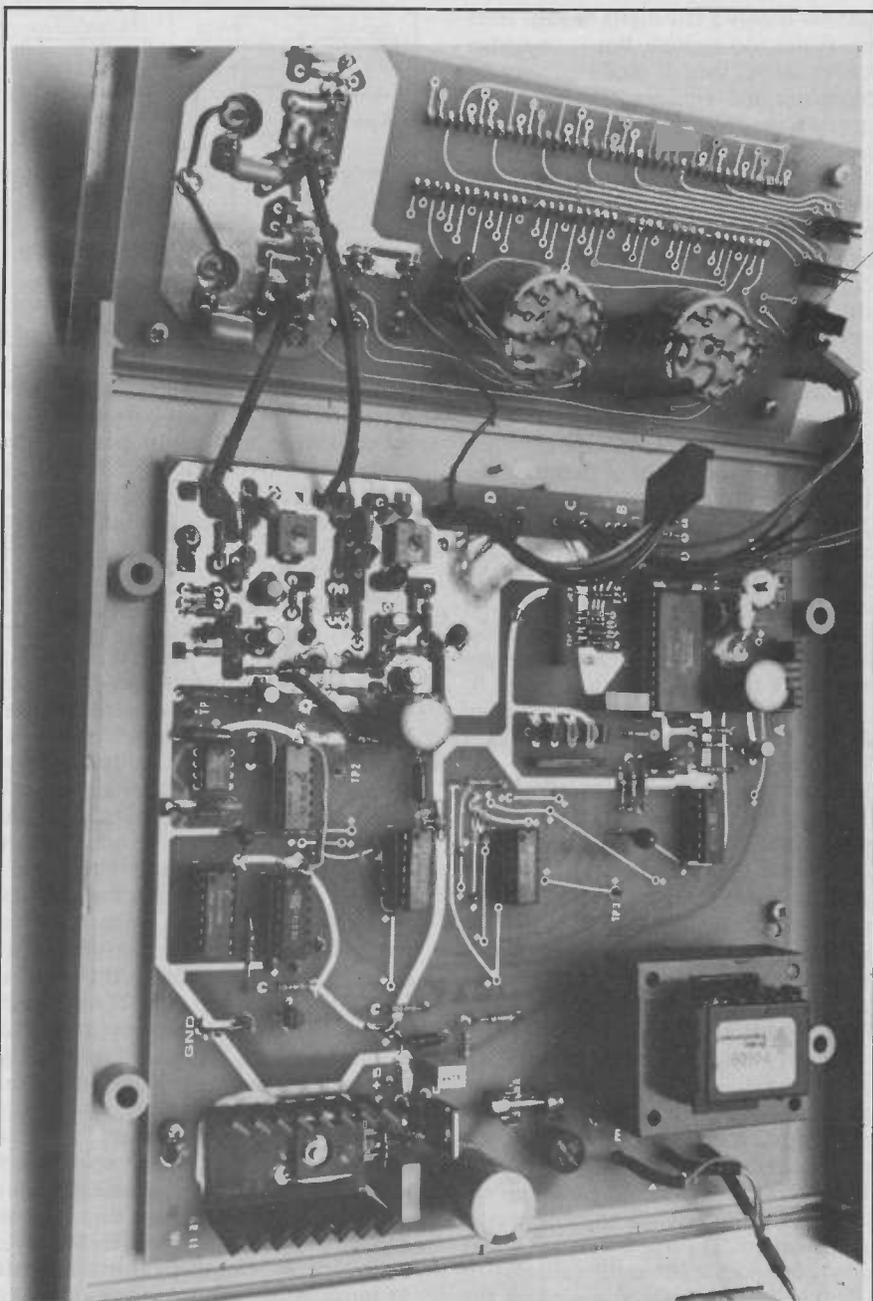Having thus set for maximum sensitivity check that changing from positive to negative edge triggering does not alter the display. If it is found that the display changes at this stage, pro-



Photos illustrating the constructional details of the Multifunction Counter—a professional looking project, indeed!

MULTIFUNCTION COUNTER

vided it is only a few digits of shift then this is not too serious, but if one edge proves noisy, then it could equally be the generator causing the problem. Increase the frequency and make sure the display tracks it in both polarities.

Select $\cdot 1$ and $\cdot 01$ ranges in turn and check digit shift d.p.s and correct frequency. Lastly check the 10s range and make sure this reads more or less right (don't forget the master oscillator has still to be set up). The reason for leaving this range till last is that it takes so long between readings that it is like watching paint dry if you try to test on this range! Increase the output from the generator and select X50. Depending on how much voltage is present in this mode the counter may trigger. Don't be too upset if it can't quite make it though, mine won't either. HF cannot be checked yet, so select Period and 1s. With an input of 1KHz at 100mV RMS the display should read 1.000 (1.000ms). Again, change ranges and check the display each time.

Select Unit. This time the display should cycle up, the least significant figure will be a blur, but the higher decades should change in sequence. Increase the frequency and check the higher decades. If you have access to a 1MHz oscillator, connect this in place of the audio generator, and check the count into all the digits. When in overflow the decimal point on digit 8 (most sig.) should light, but this will not effect the counting sequence. Check Reset gives eight zeros.

Remove the PSU and short the two inputs together, so that both will be measuring the same signal. Turn Function switch to Ratio, attenuators off, and Range to 10s. Power up, and check display reads $\cdot 000$. Set generator to 1KHz at 100mV RMS and connect it to the inputs. Do not touch VR1, but slowly adjust VR201 until a display of 1.000 is obtained. Once again, set the output of the generator lower and adjust the sensitivity until the best possible response is achieved. This completes setting up Amp B.

Checking the HF section is a more difficult problem. The main complication is the requirements of the pre-scaler, which cannot handle sine waves of less than 10MHz. So it is necessary to look for an oscillator which will satisfy this. The author used a CB radio, suitably dummy-loaded and tapped, and this worked fine. There is no reason why some other type of transmitter should not be used, but if you wish to use a CB (Fig. 7) then the frequencies ought to be on channel 1 (27.60125MHz). Channel 40 is 27.99125MHz, with a channel spacing of 10KHz. Select HF/1s, and check that the display is about right. Of course, it must be a good working set, not one which has been 'doctored'.

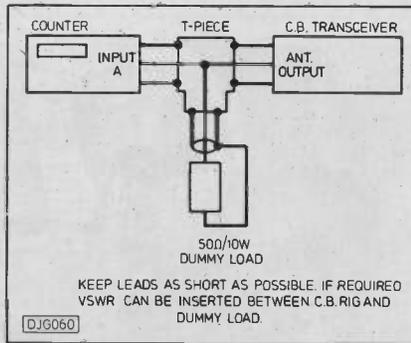


Fig. 7. CB test connections

Check the other ranges, paying particular attention to the dp position on each. When in the $\cdot 01$ range the display must blank completely. This completes Amp A and B tests.

MASTER OSCILLATOR

Only one more set-up procedure remains, that is the Master Oscillator, and is unfortunately the most difficult of all. The problem is how to set the frequency when you do not have access to an off-air or similar quality standard oscillator. This is the 'chicken or the egg' problem in this project. Using a good quality RF generator is one possibility (the CB rig again). The colour crystal in a domestic TV set is 4.43361875MHz, but great care is needed by an experienced hand to actually delve into the workings of a CTV, they can kill you! The actual source I leave to your ingenuity, so assuming that a stable and accurately known frequency is to hand, carry on as follows.

Apply the power and select Frequency range and time as appropriate for the input. Allow the instrument about 10 minutes to warm up, this is long enough at this stage, since this is only a 'ball-park' check. Apply the test signal to input A and wait until the display settles. Carefully and slowly adjust TC1 until the display is correct. It will

be easier to do this with the instrument in the 1s range, or faster as the 10s changes so slowly. From this quick check it should be clear whether or not the counter oscillator will trim in. If it will not quite make it, due to spreads in the value of the caps in the oscillator circuit, try changing the value of C16. Increasing it to, say, 56p will increase the display from 1000.0005 (1MHz) in the 10s range, to 1000.0250. At last, this all but completes the setting up. If all has gone well then it only remains to mount the counter into its case, connect front and back panels, and insert both fuses without mixing them up.

Before connecting the mains, put the meter on the 0V loop, and to either end of the fuse on the counter board. Make sure the leads are secure, then put one hand in your pocket before plugging in the mains. Check the voltage at this point is approximately 12V d.c. Leave the counter running for about 5 minutes, then switch off and REMOVE THE MAINS PLUG. Then check to make sure the rectifier has not overheated. I cannot overstress the importance of being very careful while you are doing this... DON'T take any risk with the mains. It WILL kill you! Now for the last quick tweak! Loosely put the case together, so you can have easy access to the oscillator trimmer cap TC1. Switch on and leave the counter for 10 minutes to settle down. Input your reference oscillator again, and with great care tweak the trimmer to get the correct reading. Leave the counter on, with its case together for about 30 mins, then check again. Hopefully the difference will be less than a digit. This has proved to be the case with the author's prototype when used with an Advance OFS 2 B off-air standard. Now the only things left to do are to bolt it together, and learn how to use it! I wish you luck, and much pleasure! If, however, you've got some problems, the next section should help you to sort them out.

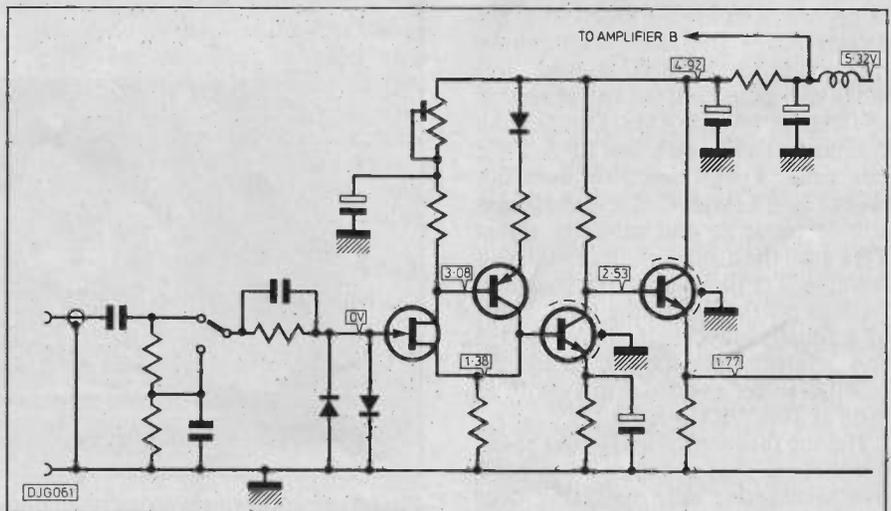


Fig. 8. Fault finding guide

FAULT FINDING

Do not attempt any tests with the unit connected to the mains if you can avoid it. The test equipment you will need to carry out these tests is as follows:

1. Bench power supply, giving 15V at 250mA.
2. A d.c. meter with a 1V and 10V range, and an input impedance of at least 20,000 ohms/V.
3. Utopia, or a 'scope. Whichever is easier!

But before you start rushing around measuring every node you can lay your hands on, sit down and list out the symptoms. Try changing the positions of all the switches one at a time, observing and recording as you go. Half an hour spent looking closely at your assembling is time well spent. To help with finding faults on the input amps, Fig. 8 shows some typical readings around the semiconductors, but treat these as a guide only. The results you see should be in the 'Ball Park' area. In all the tests connect the PSU as you did for initial testing, and remove FS2. If your problem is that nothing is happening at all, and even the l.e.d. on the front panel is out, check the supply coming out of the regulator. This must lie between 4.75 and 5.25V, and should be stable. The regulator circuit can be isolated from the rest of the circuit by cutting the 5V loop. If doing this allows the voltage to rise to 5V, then suspect a short on one of the boards. The boards should be separated to find which one is faulty. If it becomes necessary to take a knife to the track I suggest the easiest place for the 'First Incision' might be adjacent to R25.

Obvious causes of high current consumption are i.c.s in wrongly, short circuit tantalum caps, wrong polarity transistors and solder bridges, though not in that order. Having cleared this type of fault do not forget to repair any cut tracks, and then recheck the crowbar circuit.

It is very tempting in this kind of circuit, having a clever chip, that is the first bit to suspect. This leads to some 'headless chicken antics', often resulting in the device being damaged in any case. The price paid seems to have a direct bearing upon the degree of panic which ensues. So here are a few pointers.

The 7216B is probably okay if the display is showing any intelligible numbers. An oscillator fault should be suspected if only one, very bright digit is displayed. Due to the very high impedance of the oscillator the load of a 'scope probe is enough to stop it, so it's a go/no go situation. Component values are high on the list of suspects if the oscillator is faulty, so check them carefully. The only way the oscillator accuracy can be checked is with a known and stable input to the counter. If the display is showing some zeros then this tells you that not only is the 7216 probably okay, but so is quite a lot of the logic, plus the segment lines as well.

I have included TP6 especially to help with checking the DD and segment lines. Also the Function, Range and associated logic switches, along with the d.p. drive can be checked by using this point to trigger a dual-beam 'scope. Consider the 14016s as relays, with an input, common output and independent enable lines and you won't go far wrong. I have also included two TPs, 3 and 5, to help in signal tracing through the switches. To test the signal switching, first ensure that the input amps will set up correctly on TPs 1 and 2. You should see at least 3-5V swing (d.c.) on these when taking the pots from end to end.

After this, it is a fairly straightforward process to check and trace the signal and switch paths from the input amps to points A and B. This can be done with the d.c. meter, as long as you

d.c. couple the input by soldering a small piece of wire across C101 and C102. Connect the meter at 0V loop and point A or B, depending upon which amp you are checking. After that it is just a case of treating the whole lot as a logic process, and the highs and lows can be traced through manually by first applying +5V, and then 0V to the input.

If you should be tempted to try and feed signals directly into the 7216, note

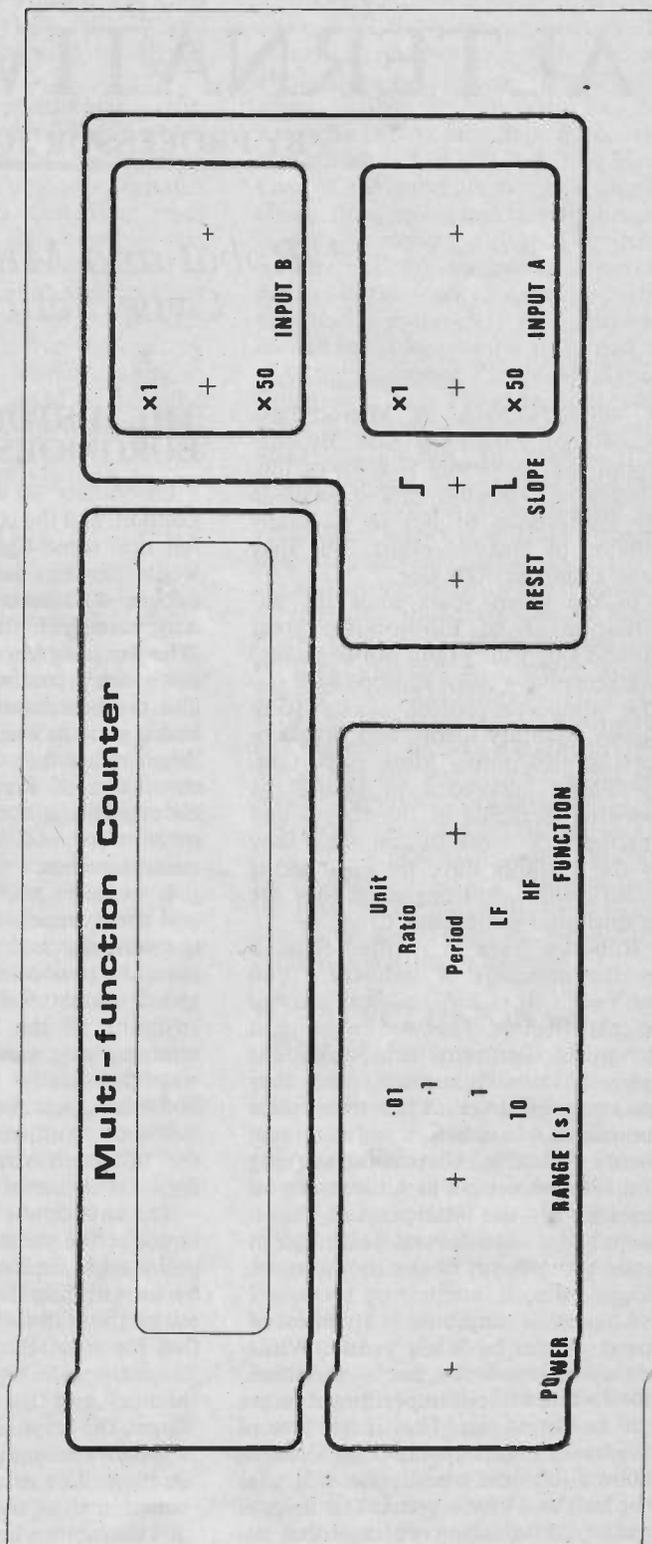


Fig. 9. Front panel marking details which may be used to produce a quality sticker or panel using a photographic process. A forthcoming feature in PE will describe this process in detail

that this must not exceed $V + (5V)$ or go below 0V, or the counter will be damaged. As you can see from the circuit diagram, the TPs allow easy access to about 90% of the logic, sufficient to find any fault. PE

ALTERNATIVE ROBOTICS

BY PROFESSOR JOHN BILLINGSLEY

Robot and Micromouse—the Cybernetic Challenge

CONTESTS such as Micromouse, Robot Ping-Pong and Build-a-Robot can be viewed as a lot of fun. They have to be enjoyable to persuade the contestants to put in so many months of creative effort. But they have a more serious side.

In the seven years since the announcement of Euromouse, great numbers of young (and not-so-young) engineers have come to grips with on-line computer control, sensor technology, stability theory and problem-solving algorithms. More important, they have succeeded in taking the essential elements of the theory and making them work in practice. Many of the entrants have no engineering qualifications, but engineers they are in spirit and achievement.

Robotics research is often fettered by the demands of industry. "You can't use this technique—it might not be cost effective. That one might upset the workforce." No such limitations apply to the enthusiasts, and they incorporate novelties in their mice sometimes years before industry sees them as valuable. Adaptation, learning and responsiveness to sensors are all essential to the Micromouse. Voice output was used several years ago; it enables the status of the mouse to be diagnosed.

Although Euromouse is a contest of speed, it can be taken gently. While exploring, the mouse can sit and think for a while without imperilling its score for its fastest run. That is not true of Robot—the robot ping-pong contest. Here a moment's hesitation will miss the ball and lose a point. The level of vision coordination which Robot demands goes far beyond any industrial robotic task. But is it beyond the bounds of reason for robots to lob components to each other? A bricklaying robot might well be kept supplied by hod-carrier with an accurate serve!

The then Director of the Science and Engineering Research Council's Robotics Initiative pronounced that games such as ping-pong were clearly beyond the possibilities of robot technology. The contestants are obviously not sophisticated enough to realise this; they seem likely to succeed.

THE HISTORY OF EUROMOUSE

Euromicro '80 was to take place in London, and the conference organisers felt that some lighthearted attraction would leaven the serious technical papers. An account appeared in the American IEEE Spectrum magazine of 'The Amazing Micromouse Maze Contest', with prizes for the fastest first run and the best learning run. The maze had a start in one corner and an exit target in another, and although a size constraint of fourteen feet was declared, the actual size and shape of the maze were not too clear from the announcement.

It seemed a good idea, all the same, and the European version of the contest was launched. Then the Spectrum accounts took on a sour note. A high speed 'dumb' wall-follower was outstripping all the brighter mice, and attempts were made to outlaw it—but was that really playing the game? Something was clearly wrong with the rules—after all, following the wall is the optimum strategy to reach the opposite corner of an unknown maze.

The answer was of course to put the target at the centre of the maze. The paths could be highly connected, and by surrounding the centre with closed routes the wall-followers could be baffled for ever. By declaring the maze dimensions (16 by 16 for binary convenience) and the coordinates of the target, the emphasis could be placed on control, navigation, mapping and strategy. The mice have certainly excelled in all of these.

Two months before the first London contest, a trial heat was held at the Open Day of Portsmouth Polytechnic. It taught everybody a lot. The first lesson was that mouse-builders are shy to show off their creations unless perfect. From two hundred applications, the number of contestants prepared to appear dwindled to two—and they were both Polytechnic students! Much pleading by telephone the night before the event brought the numbers up to just five.

Plessey's 'Fred' and Marconi's 'Meryl' were far from complete. Al-

though they were both impressive in terms of their construction and concept, one could only spin in circles while the other was good-humouredly driven by manual switches to entertain the sizeable audience. Algernon's guidance circuitry was crossed, so that it could only run straight into the first wall; one of the Portsmouth mice had processor problems and bounced about at random. Only 'Freewheelin' Franklin' made any real progress—and that was marred by a loose photocell connection. And yet the event was an enormous success. The audience seemed more delighted by the disasters of the mice than by their successes. Among the spectators was Nick Smith; he had left his mouse at home.

Also in the audience were five delegates from the Japan Science Foundation, who took the rules back to Tokyo and built up their own contest to great heights.

The next two months were well spent, and the European finals at Euromicro 80 were quite a different matter. Mice arrived from all over Europe, 'Midnight Sun' from Finland, 'Lami' from Switzerland, 'Superlite' from Germany and 'Yamahico II' from Japan. 'Fred' now took on a rodent shape, 'Meryl' was under full control and a new mouse 'Ancomical' was entered by ICL's amateur computer club. Technology ranged from 'Brainy Bricks', made from Lego, to 'Pascal', sawn down from a toy car and struggling to clear the corners with three-point turns. Lami was marvellously engineered with tyres made of cross-mounted micro-wheels. These allowed it to perform a virtuoso display of driving in a circle whilst pointing North. The novel wheels unfortunately demanded an absolutely flat surface, and an uneven joint in the maze-base marred Lami's contest performance.

One mouse was built around a CMOS processor. The body of aluminium had been carved out with tin-snips, and the wall-sensors were metal flaps which closed contacts salvaged from a relay. With no previous electronic experience, Nick Smith had put together 'Sterling Mouse', the first mouse to reach the centre and 'know' it



had succeeded. The strategy had its roots in Dynamic Programming, but was simple enough in essence that the calculations could be carried out as a delay routine between motor steps.

An Easter workshop was organised by the ICL computer club, where ideas were exchanged and advances were made. Thezeus and Thumper appeared at Wembley in 1981, founding a dynasty of winners. Thumper combined ingenuity with superb craftsmanship, with ingenious swivelling wheels which allowed it to manoeuvre without rotating. Thezeus established the practice of building a small personal computer into the micromouse—albeit with sawn-off keyboard. Fifteen mice took part in the Paris Euromicro finals, and Thumper became the new European champion. The rules had again been changed slightly, giving each mouse fifteen minutes in which to perform, the best run being counted. This put a premium on learning ability, and the time achieved for the best run had by now been cut to below a minute.

The 1982 British finals were held at the Computer Fair, Earls Court, the first of three such years. Two new 'Thezeii' beat Thumper into third place, but all three times were below one minute. The University of Tampere in Finland played host to the 1982 European finals; they snatched victory from Thezeus-4 by a mere two second margin in forty seconds, and retained the title the next year in Madrid.

At last in Copenhagen, at Euromicro 1984, Britain won the title back in the shape of 'Enterprise', grandson of Thumper. The shortest path was seventy squares in length, covered in an amazing twenty-seven seconds. David Woodfield (Enterprise) and Alan Dibley (Thezeus-5) won travel prizes donated by the Japan Science Foundation

to join teams from Finland and Germany in the Japanese 'All World' contest in Tsukuba, held in August 1985.

Tsukuba was a spectacular event, preceded by a Japanese Final in which more than fifty mice vied for a chance at the world title. Further contestants arrived from South Korea and from the United States. No expense was spared, and the contest culminated in the presentation of yard-high trophies and huge cardboard cheques—with some pretty impressive figures on them. All the top honours went to Japanese mice, five out of six from the same Fukuyama club. Britain's Enterprise claimed seventh place, and the rest of the world trailed in the distance.

MOUSEATHON

A few months later a 'Mouseathon' was arranged in Boston, to help wake up America to what had been going on in the Micromouse world. Three British mice were imported, Enterprise, T6 and good old Thumper, to meet a visiting team from the Fukuyama club. Their mice were Noriko 1, Noriko 2, Noriko 3 and Noriko 4—quadruple honour to the name of their club president's wife. Based on the same chassis they carried varieties of motors, d.c. and stepper, and various extra sensors, such as home-made gyroscopes to help in cornering. When it came to the crunch Noriko 1 put up the best time, just half of that of the fastest British competitor.

I asked the winner a question, and obtained an answer which was hugely revealing of the Japanese approach. "Do you renumber your mice, so that the best is always Noriko 1?" "No, Noriko 1 is the oldest. It still has stepper motors. It is best because we have had longest to develop it!" So the technology of the winner was essentially that of the 'wheelchair' which had won the 1980 British final. But the refinements were fantastic.

ROBOT PING-PONG

In November 1981, a micro-robotics conference at Imperial College provoked the question "What can follow Micromouse when solving the maze is seen as easy?" Three-dimensional mazes were suggested, along with non-cartesian shapes and walls which move. All these are possibilities, although there are still plenty of challenges in the contest as it is. A contest of a different type was needed, and the solution was robot ping-pong. Playing very safe, I named a date five years off for the first heat—but it is all happening in four.

A group of entrants met in Portsmouth on 19th January, 1985, to exchange ideas and polish up the rules.

Three very primitive pieces of machinery arrived, two bat mechanisms and a vision system. Nothing really worked, although an oscilloscope trace showed a peak where the ball might just be. Less than two months later, the contest was introduced on BBC's 'Micro Live'. One of the mechanisms now leaped about, threatening mayhem to the presenter who stood too close. The vision system put up an excellent screen display of the track of a real bouncing ball, and a completely new arm succeeded in taking a swipe at the ball.

At the European Personal Robotics Congress in July 1985 the Robots did battle in earnest, although the best rally was just one hit. In Brussels that September they met again at the Euromicro Conference, and although the rallies were no better at least two of the machines showed consistency in tracking and hitting the ball when it was first served. One found its way to Strasbourg, to perform before the President of the European Parliament at the Europe 2000 exhibition. Not only did it defeat Murphy's law by hitting the ball perfectly, the ball rebounded from a wall, hit the spinning lenses of the novel vision system, and convinced the President that it had hit the ball twice!

The early Robots are erratic in their performance, to say the least. But from the first few tentative efforts, a whole new technique of dynamic robot interception is starting to emerge.

IN CONCLUSION

In Britain, Micromouse has grown up on a shoestring budget, begging space at annual British exhibitions and scrounging prizes from the exhibitors. It is none the worse for that. In Japan, however, there is a permanent Micromouse Secretariat. They were present at the 1984 Euromicro finals in Copenhagen, and awarded seven or more European participants free air flights to take part in the Japanese finals. The maze used at the European Personal Robot Congress was flown in by the Japan Science Foundation, so that any incompatibilities could be sorted out before Tsukuba, and mazes have been sent to South Korea and the United States. Could the importance which the Japanese obviously give to such contests be linked with their industrial success, perhaps in chicken-and-egg fashion?

Micromouse, Robot and Build-a-Robot will continue to give qualified and unqualified engineers alike the opportunity to innovate. Their ideas may spin off into industrial applications, the contestants may themselves be recruited by marketers of new robotic products. In all events, they enhance the awareness and ability of each participating country to exploit the rushing tide of technology.

PI

PRACTICAL MICROMOUSE

BY A. DIBLEY

Q. Is a ZX-Robot a Cybernetic Sinclair?

IF YOU want a new challenge to exercise your mind and not damage the pocket too much, try to get a self contained mobile robot to the middle of a ten-foot square maze.

The task is to build a mechanism to travel through, and solve an unknown maze. The maze has 256 squares (16 x 16) with 18cm sides and 5cm high walls, 1.2cm thick. Floor is matt black, walls are gloss white with red tops. You have 15 minutes to perform. During this time the mouse can make up to ten runs, starting at a corner square with an outside wall to the left, aiming to reach one of the four middle squares which are the 'target'. No outside 'intelligence' or power supply is permitted. Manual assistance is penalised, but a mouse in trouble can be rescued and restarted at the start square. Each run from start to target is timed. Fastest run counts. No strategies like trails of bread-crumbs or 'blast through the walls in a bee-line for the middle' are permitted.

Here are some hints to help you over the first difficult steps, or give you some ideas for later stages. They are based on methods I have used with varying success in six different working mice and several trial-and-error dead-end developments. These techniques may be usable on any project that needs an interface between a micro and a mechanism. They are as simple as possible. All are economical in parts and build-time.

THE ON-BOARD COMPUTER

First, consider the electronic bits. I used Sinclair ZX80s on two mice, and ZX81s on three others. Some pundits said that ZXs seemed unsuitable, but I believe that opinion was based on a misunderstanding of the requirements. You will spend many more hours developing the mouse than competing with it, so a lot of consideration must be given to the requirements of that experimental period. This applies to many hobby projects of this kind. Most of the following points are valid for several other less common micros, so while you read, think of the hardware

that you know about which is lying around unused. Consider:

Cost. A second-hand ZX80 or ZX81 will not break the bank. And if you inadvertently destroy it, you can replace it cheaply.

Convenience of software preparation. You can start by using mainly BASIC with a small amount of machine-code to drive the output ports. Or use a separate 16K ZX81 system to write the code with an assembler, transferring it to the mouse via tape. (Hints. Always run machine-code in FAST mode. If you use a ZX80 on the mouse, install a ZX81 ROM to give it compatibility with the ZX81 development system.)

Convenience of software modification during development. The BASIC interpreter is an excellent on-board operating system, allowing you to examine or change storage with PEEKs and POKEs and useful display/alter routines in BASIC.

Size. The ZX80 and 81 are the smallest easily available processors. **Availability.** There are thousands of them around.

Power consumption. The whole mechanism can be run for around half-an-hour on a set of 500mAh nickel cadmium cells.

Program loading via the cassette interface is a bit tiresome, but once you have it sorted out it is not as bad as people say. Do not connect the EAR cable while SAVEing, and keep the cassette recorder away from the TV set. The final version of code can be burnt into a ROM and called with a couple of hand-entered-statements, but this is hardly worth it, considering the likely working life of the mechanism during competitions, as each run lasts a maximum of 15 minutes.

The normal Sinclair 16K RAM-pack is cumbersome for mouse use. 2K of storage can be fitted to the ZX81 by removing the two 2114 chips and fitting a 24-pin socket to take a 6116. Remove link L1 and make link L2.

To fit 4K of RAM to a ZX81, begin as for 2K. Piggy-back two 6116 chips, commoning all pins but 18 and 20, which must be bent out sideways to allow them to be wired direct to the circuit shown in Fig. 1. It is possible to

get all code, maps and variables into 2K of RAM though 4K will hold useful on-board dump and formatted display utilities to assist in development.

Fig. 2 shows a simple output system expandable to 8 bits, using TTL chips. Thezeus, the grandfather of my mouse-tribe, used only three output bits for all functions. (Note that I referred to the mouse as a man-mouse. The majority of successful mice have been male. I offer this as an observation only, and do not dare to make further comment on the matter.)

The circuitry between the 7474s and the output device depends on the load. A simple one-transistor driver stage will operate a small motor direct, but do not forget the reversed diode or other suitable suppression across any such inductive load. 7474s have an inverted output as well, which is very useful for driving more complicated output devices.

I glue the extra chips to the ZX board with the legs pointing upwards and make connections directly to the pins, to save weight, size and complications like plugs and sockets. There is not much space in most mouse chassis for luxuries like neat wiring systems.

The Z80 lines are soldered straight to the printed wiring on the Sinclair board. All the connections needed are available on the edge connector. There is no Micro-Mouse prize for elegance of circuit design.

All of the 74xx chips can be LS types or equivalent CMOS to save a little power. The 7474s can be piggy-backed like the 6116s, commoning all clock lines, all reset lines, and all voltage lines.

Use two power on-off switches, one for the processor, one for the output devices, motors, servos etc. Use a double throw switch for output power, the 'off' contact can be used to reset

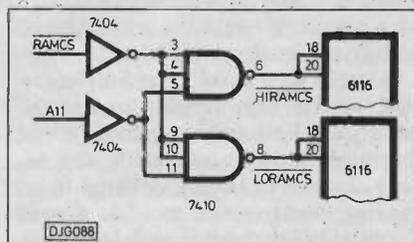


Fig. 1. ZX 4K RAM

the 7474s to prevent glitch problems during RAM-loading and preparation.

The ZX80 can be made smaller by cutting off the keyboard with a hacksaw and reconnecting the printed wiring with a plug and socket. The ZX81 can be removed from the case and the keyboard similarly connected. The board may still be too big to fit into the lower body of the mouse (depending on the way your design travels) and it must be carried above wall height but the importance of top-weight becomes significant only when the mouse reaches speeds of, say, 20 cm/sec or more. The keyboard is only needed when the mouse is not moving. To provide the start and stop functions necessary for control during a contest use a couple of small switches to act in place of the appropriate keys.

floor and the white walls. They all had problems which I did not want to solve and my philosophy was to use simple methods that I can make to work, but if you like them, use them.

Other hints are:

Read the input ports often enough to ensure that nothing important is missed. The sensor used to measure distance travelled must be read frequently enough to ensure that no pulses can slip between read commands. About one pulse per 2mm is frequent enough.

Pulse the infra-red emitters on for about a millisecond before you read the sensors. Some are very slow and the Sinclair circuitry seems to slow things more. Drive them as hard as you dare, to overcome the flood-lights at the competition site.

respectively FE, FD, FB, F7, EF, DF, BF, 7F from lower left clockwise. The A register will contain the input in the low-order 5 bits, with a 1-bit for unmade keys, and a 0-bit for closed keys.

Get a book about assembler programming for the ZXs.

THE ELECTRICS

Now consider the motor and steering systems.

DC motors. Can be cheap. Use simple transistor driver stages, which can be software-pulsed for speed control.

Stepper motors. More expensive and more complex to drive, but reduce the need for feedback systems. Fast, light, efficient steppers are expensive, but getting cheaper.

Radio-control servos, as used in model planes/boats/cars. Because they are driven by TTL style pulses in their natural environment, and powered by about 5V, they can easily be driven by pulses developed by a micro.

The pulses needed to drive most servos are positive-going, between about 0.8 and 2 milliseconds long, and repeated about every 20 milliseconds. Short pulses drive the servo to a point near one end of the travel, long pulses drive it to a point near the other end. Middling length drive pulses, about 1.2 or 1.5 milliseconds, put the servo at the midpoint. Different makes of R/C gear use different standards, but all are suitable, since the difference can be accommodated by software. Some have a gearbox which will allow the output to revolve continuously if the internal feedback potentiometer is replaced with a fixed external one. Then the output shaft can be driven in either direction as a drive motor and stopped by not providing any pulses. The speed can be varied by altering the rate at which the pulses are delivered, but the control is poor.

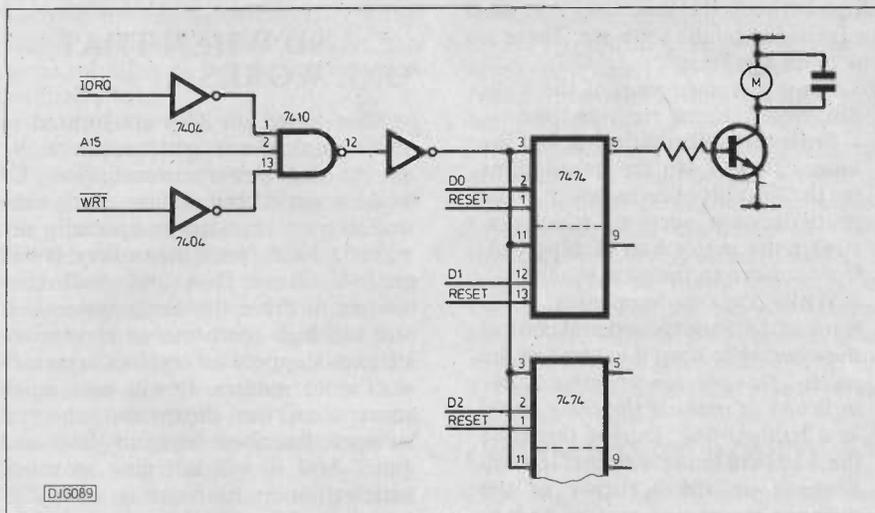


Fig. 2. Simple output system

SENSORS

Next to be considered are inputs. The ZX80 and 81 are provided with a 40-bit input system which is called a keyboard. Since it is there already, use this circuitry for sensor functions. The keyboard is arranged as 8 half-rows of five keys each. By connecting a switch between one-of-eight wires and one-of-five wires and using a short routine (now is the time to get familiar with Z80 assembler code) you have built a very economical sensor. It is necessary to make sure that none of the sensors are 'closed' when you need to use the keyboard in the normal way.

The only other types of sensors I have used successfully are infra-red, reflecting from the top of walls or from shiny segments on drive wheels, or with the beam interrupted by walls or a slotted disk. The maximum permitted horizontal dimension of 25cms allows sensor systems to overhang the walls.

Other builders have used sonar, infra-red reflected from the sides of walls, and a CCD camera to see the difference between the black maze

Use the circuit of Fig. 3 to amplify weak signals to operate the keyboard. Only used for reflected or long range systems. Any small-signal transistor will do the job. The diode provides a small fixed sensing threshold. a.c.-coupled circuits might be more effective to combat high levels of background infra-red.

Use a switch or micro-switch as a sensor if possible. Adjustments are easy if you can hear or see the sensor working.

It is unlikely that you will be using enough power to cause appreciable wheel-spin on the drive wheels, so the distance measuring emitter(s) may be fitted to the drive-wheel(s). The best tyre material is buff-coloured rubber bands (honestly), stuck with cyano-acrylate.

Use LD A,\$EF
IN A,0

for instance, to read the keys 6 to 0 (the top right half-row) into the A reg. The half-rows are addressed by the absence of one bit in the byte loaded to the A reg. That means that the addresses of the half-rows are

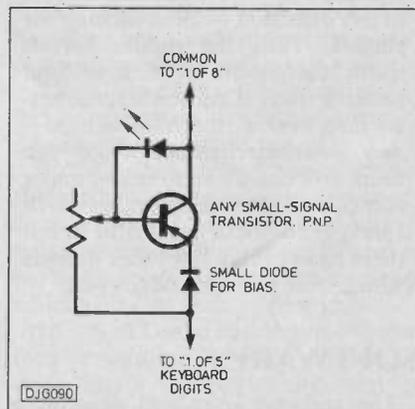


Fig. 3. Signal amplification

Whatever electrical bits you use, try to find ones that will work on the same supply as the micro. You do not need the complication of two sets of flat batteries 10 minutes before the competition starts. If your design is fussy about voltage, and goes 'off-tune' when the cells get a bit low you will need to fit a 7805 5V regulator fed by six cells. 500mA size cells will probably be big enough, since they only have to run for 15 minutes in the competition plus preparation- and waiting-time. Have some spares on charge, or make a voltage-sensitive charger that allows the battery to be topped up fast but safely. *If you use high-rate charging, use only vented cells.* If an overcharged unvented cell explodes it will damage the mouse and may cause injury.

THE CHASSIS

Before you can make much progress in the design, you must make the basic decision on the type of mechanism to build. Choose from:

Tricycle with one driven rear wheel. Steering two front wheels may be complicated if it will steer round corners as well as make corrections on straights. Thezeus is a tricycle mouse but uses a foot which lifts the whole mouse from the floor and revolves in multiples of 90 degrees to turn at corners or dead ends. This means that the steering has only to turn enough to make minor corrections in straight running.

Tricycle with one steering front wheel. It may be rear-wheel drive or front wheel drive. Rear drive needs a differential in the axle or two drive motors. Front drive might need the motor mounted on the steered part.

Wheelchair style, with one driven wheel each side, and idlers or skids front and rear for balance. Steering and turning is done by independent control of the drive motors.

'Thumper' style, named after one of the 'greats' of Micro-Mouse, this is one in which all wheels can be swivelled so that the mouse travels in any direction without turning the chassis. Thus the mouse travels north, east, south or west without rotating itself. This needs some better than average mechanical bits.

Any other mechanism which you think you can make to move under control. All the working mice which I have seen are of types 1 to 4, but there have been a few other designs which were not fully developed.

SOFTWARE

The software used will depend on the processor chosen. On the ZX80s I used hand-assembled code, entered

byte-by-byte, very patiently. It taught me Z80 coding as no other method could. On the ZX81s I used the Bug-Byte ZX81 assembler because there was not any choice at the time. It is a simplified but extraordinarily fast assembler with restrictions on label naming, and no advanced functions, but its simplicity is an advantage in some ways, and is not a limitation in software systems of the size of a mouse control program.

Later mice have software in EPROMs. I use a 48K Spectrum with the Ultraviolet Assembler (which assembles in COLOUR!) and a CAMEL BLOPROM-SP EPROM blower as a very economical but effective development system.

More important than the details of how to get the code on board is the necessity to understand the relationships between the functions that must be provided by the software. These are the main sections:

Draw a storage map of the walls discovered during running time.

From this information 'solve' the maze. That is, do the calculations for the next bit of code, which is the route-decision section, which instructs the motor and turning control to move to the next square.

While this is happening, keep track of distance moved and control the steering to keep it centred in the paths. *Do not underestimate the difficulty of making the thing travel in a straight line.* During this time the walls are being watched to keep a check on the accuracy of the distance measuring system and to provide input to part 1, so we have completed the software loop.

Error recovery. Scope for interesting fiddles here. For instance, to overcome the problems associated with the rule that no manual input is allowed between runs, it is possible to make the software detect the fact that the mouse has been lifted from the maze after a disaster.

Speeding up along previously explored straight runs. Deciding if and when the shortest route has been discovered, and confirm it by trying it. Then re-run it with the speed controls turned up faster, to try for a quicker time. There is nothing to lose.

Anything to amuse the audience—The best known mouse in the world is probably Dave Woodfield's Thumper. It talks to the audience and to itself while it is exploring the maze. A very difficult act to follow.

On the subject of amusing the audience, put a hairy mouse on board to give the mechanism a little crowd-appeal and make him photogenic. Even if it does not win, the mouse has his photograph in the reports, and is remembered and recognised.

When I started making mice I used the techniques I knew from building model aircraft and boats. The main structures were made from thin plywood, balsa and card. It can be drilled, sanded, carved, glued, pinned, screwed and thrown away if it is not quite right. No machine shop facilities are needed to make complex shapes. Even wheels were custom made by turning plywood discs on a small modeller's lathe, but an electric drill can be used instead. Bearings and steering mechanisms were made with brass tube, piano-wire, solder and pins. Epoxy and cyanoacrylate (super-glue) adhesives are wonderful for construction methods of that kind. It is also useful to be the sort of person who never throws away anything that looks as if it will be useful for something or other at some time in the future.

... AND WHEN THAT ONE WORKS

Mice based on ZXs are limited in their maximum performance by weight and power consumption. To build a world class mouse needs time and money invested in specially designed CMOS based controllers. It will probably have D-A and A-D converters to drive the servo systems. It will use high performance rare earth-magnet steppers or coreless armature d.c. servo motors. It will cost much more than the cheap and cheerful devices described here, in cash and time. And it will not give as much satisfaction in its building as a ZX-based machine. That is my excuse for abandoning the chase for ever more speed, because once you have mastered the art (I think it is an art) of getting a mouse to the centre target with reasonable reliability, you will want to make a faster one, then a still faster one, then ... You have been warned. **PL**

THE CHALLENGE

The object of this article has been to encourage more entries to the Micro-Mouse contests. There are hundreds of computer clubs and school electronic groups who might like to focus the expertise of members on a new challenge. Is there a group in your area that might be encouraged with some sponsorship? Will we see new games on the leader board at the next Championships? There is a competition class for previously unplaced entries, so don't worry about competing against the old hands. Rules and entry details are obtainable from the I.E.E. Computer and Control Section at Savoy Place. AND ENTRY IS FREE ... what an irresistible bargain.

ROBOTICS REVIEW

BY NIGEL CLARKE

Micros and robots— the stuff that dreams are made of

MANY makers of small robots have harboured dreams of repeating the successes of the early days of the home computer boom and of developing the machine which brought robotics into the home and made fortunes for the people involved. They would become the Sir Clive Sinclair of the robot world but without making the same mistakes as the market matured and sales fell.

In the early days the dream was no doubt fostered by the close relationship with home computers. Most machines were controlled by micros so if the product was right and the price low enough sales would take off.

Unfortunately the dreams did not become reality. Despite the undoubted interest in robots both fictional and factual they have failed to achieve the large sales which were hoped for. They have tended to split into two separate areas, toys and educational. Some of the toys, particularly in the Tomy range, have been quite sophisticated with a certain amount of memory for routines but others have been little more than plastic models like the best-selling Transformers.

Any robot which was capable of anything more serious, be it an arm or a buggy, controlled by either a dedicated controller or by a micro, was considered too complex just to be taken home and played around with. The middle ground remained open for exploitation.

The problem for anyone wishing to occupy that middle ground was that if the home computer pattern was to be followed then playing games would have to be catered for. While fine in theory the practice has been slower in being achieved.

Because of their price and software orientation, buggies have been seen as the most likely robots with which to play games. And now InterGalactic Robots of London, a company which has long promoted games—playing robots, is hoping to be able to announce a specially-written game for its Zero buggy.

Details are limited but it is being described as a robot video game with control and scoreboard on the screen and Zero playing the game on a table.

The first version is being written for the Commodore 64.

Another manufacturer looking to break out of the educational market is Clwyd Technics with its school-designed Trekker. The possibility of selling through retail outlets in the High Street is being considered and to increase its appeal a talking version is being developed. A prototype is already completed with production now being looked at.

In the meantime both manufacturers are hoping to build on the success of their machines throughout the world. In common with a number of other robot manufacturers they are finding a ready market in many countries in Europe as well as the US and Australasia. And IGR is now having talks with the Chinese government to set up a deal to introduce Zero into their schools.

COMMUNIST ROBOT

During the last three months the company has received enquiries from a number of socialist countries and the Chinese deal appears to be going well. It is expected that the agreement will be for Zeros to be made in China under licence with as many of the components as possible being made there.

IGR is also adding to Zero's facilities by the provision of a remote control system. It will be radio rather than infra-red and is expected to be ready by the end of June.

The makers of Trekker are expanding its possible market by developing a version which will work on three of the Commodore machines, C128, C64 and Vic. At present it is only available for the BBC B.

They have also been asked to prepare a Danish version using Comal.

All the developments are keeping the children of the school in North Wales, where Trekker was first made, very busy. Alex Whittaker, the teacher in charge of the project, said the response since the launch last year had been very good and it was now on sale in 14 countries. The only problem was in persuading people that Trekker was all they needed, instead of the usual extras, to enable the buggy to be linked to the BBC.

One buggy which will not be following in the footsteps of Zero and Trekker, at least not for a while, is the one which had been planned by Memoco Electron of Leicestershire. The company has been involved in other electronic projects away from robotics since the beginning of the year and work on the buggy has been suspended.

The Electron arm, however, is another of the British products doing well abroad. Bob French, the owner, said that large orders kept coming from all over the world for the arm, which is a programmable version of the Tomy Armatron.

To increase its capabilities a version of Logo is being written for it.

The Electron has five axes and a gripper, interfaces for C64, BBC B and Spectrum and can be controlled from a keyboard or by joystick. The company's achievement in adapting the arm has been recognised by its being given a Midland Industrial Design (Midas) award.

At Cybernetics Applications of Andover the ever-growing range has continued to expand with the addition of an expansion board which can provide an extra 16 inputs and 16 outputs. The prototype has been completed and a production model is expected soon with a price of about £120.

The board will allow extra sensors to be attached to the Cybernetic range and increases the number of arms which can be networked.

Cybernetic now has four arms, the hydraulically-powered Neptune and Naiad, the mechanical Mentor and the Serpent scara. In addition it has a work cell with conveyor and sorting table.

There have been further delays affecting two arms which had been expected to be launched last year.

L. W. Staines of Essex does not think the market is ready for its two-armed Troll robot. It is now intending to delay its announcement until September when it is bringing out a catalogue which will also include its Ogres.

HCCS of Gateshead is still trying to find a solution to the problem of designing a gripper which can be manufactured at a reasonable cost but also be robust enough to fit the rest of the machine. PT

RS232 BREAKOUT BOX

BY JOHN LEWIS

Communication trouble? Give yourself a break!

TO THE uninitiated, serial communications between computers and peripherals appears to be a black art. RS232C, or V24 as it should more properly be called in Europe, is supposed to be a standard—but unfortunately there are so many different flavours that what should be a simple connection often turns out to be a mammoth undertaking. The professionals use a breakout box to link and cross switch the various combinations of connections but these boxes tend to be expensive and beyond the pocket of the person who only rarely needs to

join up a printer or modem to his computer.

The RS232 standard connector is a 25-way, D-type connector and has been specified for a wide range of asynchronous (unlocked) and synchronous (clocked) circuits between, Data Terminal Equipment (DTE) and Data Circuit-terminating Equipment (DCE). These are jargon for Computers—DTE devices, and peripherals—DCE devices, such as modems and printers.

The full definition of the interface is given in Table 1 which looks highly complex and confusing. In fact most people will only ever use six or seven of the possible 25 connections, for printers; meaningful communication can be established with as few as three.

The most important ones are pins 1, 2, 3, 4, 5 and 7—Ground, Transmitted Data, Received Data, Request to Send, Clear to Send and Signal Ground. In some instances pin 20—Data Terminal Ready—may take the place of CTS. In some instances you may not need to connect both 1 and 7 since they are both earth lines and most likely are internally connected anyway. If you have a choice connect 1, since that's the screen over the cable which will prevent any interference from your signals affecting other equipment and vice versa.

The signals on all these lines are fairly self-explanatory. Received and transmitted data is as expected. Request to Send indicates that the DTE is ready to send data whilst CTS shows that the DCE is ready to receive it. DTR signifies that the terminal is ready and that the peripheral should be connected to the circuit; in some instances, for example with printers it is used to signal that the printer is ready and in these instances takes on the role of CTS.

computer needs to be told to stop sending until the printer has cleared the backlog. The way to do this is for the printer to turn off its acceptance of the CTS handshake. The computer then stops sending data until such time that CTS is turned on again by the printer. This way the peripheral can keep in step with the data being transmitted by the computer or DTE. Not all programs or machines use hard-wired handshakes, some use software implemented ones known as XON and XOFF. These are special control codes which are transmitted along the data transmission lines to control the sending of data in much the same way as RTS and CTS operate. Obviously if XON and XOFF are used you don't need RTS, CTS or DTR. Needless to say the two types of handshaking are not compatible so if you find that you seem to be losing data at a peripheral, check the handshaking employed by the computer, the application being run and the peripheral.


It should be easy to connect a computer to a modem since the convention for specifying these two devices is quite standard. The computer is a DTE whilst the modem is a DCE and the connections are straight through. Pin 1 from the computer goes to pin 1 on the modem, pin 2 to pin 2 and so on. The difficulty comes when you are not sure whether the peripheral is configured as a DTE or as a DCE, for example if you are trying to connect two computers together they are both DTE devices. So here it's necessary for the Transmit data terminal from one to be joined to the Receive data terminal on the other, and RTS on one to be joined to CTS on the other.

Table 1. RS232 pin specifications

PIN NO	FUNCTION	ABBREVIATION
1	GROUND	FG
2	TRANSMITTED DATA	TXD
3	RECEIVED DATA	RXD
4	REQUEST TO SEND	RTS
5	CLEAR TO SEND	CTS
6	DATA SET READY	DSR
7	SIGNAL GROUND	SG
8	DATA CARRIER DETECT	DCD
9	POSITIVE TEST VOLTAGE	
10	NEGATIVE TEST VOLTAGE	
11	EQUALISER MODE	QM
12	SECONDARY CARRIER DETECT	SDCD
13	SECONDARY CLEAR TO SEND	SCTS
14	SECONDARY TRANSMITTED DATA	STD
15	TRANSMITTER CLOCK	TC
16	SECONDARY RECEIVED DATA	SRD
17	RECEIVER CLOCK	RC
18	UNASSIGNED	
19	SECONDARY REQUEST TO SEND	SRTS
20	DATA TERMINAL READY	DTR
21	SIGNAL QUALITY DETECT	SQ
22	RING INDICATOR	RI
23	DATA RATE SELECTOR	
24	EXTERNAL TRANSMITTER CLOCK	ETC
25	UNASSIGNED	

HANDSHAKING

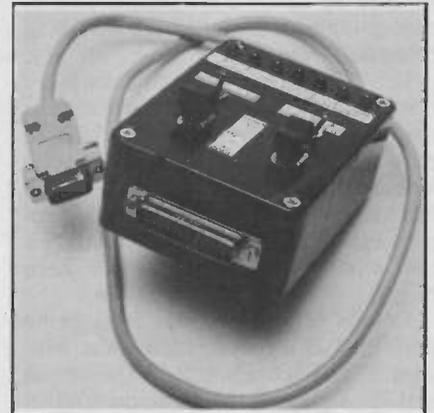RTS, CTS and DTR perform the essential 'handshaking' between the various devices being connected together. The purpose of handshaking is to ensure that the data being sent from, say, the computer does not exceed the capacity of, say, a printer to receive it. Should the printer not be able to cope with the amount of data being sent the



RS232 BREAKOUT BOX

Just this sort of problem arose when I was trying to transfer text files from a BBC B micro to my Macintosh. Not having a breakout box I improvised initially with an old S-DEC board and wire jumpers which worked but wasn't a permanent solution. Not wishing to go to the expense of buying a breakout box I built one out of odds and ends from my scrap box. The presumption made was that I knew the configuration for my permanent micro—the Macintosh—so didn't need to do any fancy switching on that side of the circuit. It was the input side which was unknown and so any indicators and switches only needed to operate there. The circuit for the solution is given in Fig. 1. It allows you to interchange TXD and RXD and also RTS and CTS. In those cases where DTR is used this can be switched in place of CTS. When testing input signals, or to overcome the use of XON/XOFF, it is useful to be able to fool the other micro that it is getting the right handshaking signals. This is achieved by linking RTS and CTS on the input side. To monitor the status of various input lines, i.e.d.s are provided. In addition to the signals already mentioned it can be useful to see if carrier detect (DCD) and data set ready (DSR) are in use. These are usually only found on modems and are used to inform the DTE that a carrier signal is present and that the modem itself is operational.

CONSTRUCTION AND USE

Building this simplified breakout box should cause no problems. The main switches are of the changeover, centre off type, the others are just changeovers. I used rocker type switches for the two main ones but toggle ones are just as acceptable. There is nothing special about the i.e.d.s or resistors either. I hardwired the connection to the Mac into the box and used a 25-way D-connector for the input. You can if you wish hardwire the input side into the box—whether you put a male or female connector on its end is up to you since there is no convention as to what should be on the back of any piece of equipment. (For those of you who did not do biology at school a male connector is the one with pins sticking out.) In any case a gender changer will be a necessity to cope with the situations not covered by the connector you have fitted. (Again in case you didn't know a gender changer allows a male connector to be connected to another male connector or a female connector to a female connector.) If you intend doing a lot of RS232 link-ups it could be worthwhile investing in a length of 25-way ribbon cable which has male and female connectors on both ends.

Using the breakout box is simple, just fiddle with the switches until you get data being transmitted! However, if you wish to be more scientific there is a logical way to proceed. Let us suppose you are trying to get another computer to talk to yours. Firstly plug the output lead into the serial port of your own computer. Put the two main switches in the centre off position and switch in the RTS/CTS link to fool it into thinking that it is getting the right handshaking. Plug the free lead into the serial port on the other computer, using the gender changer if necessary. Load a text file on the other computer and print this to the serial port. You should see some of the i.e.d.s on the breakout box start to flash or come on. Now look at the Data i.e.d.s. If Data 1 i.e.d. is flashing then the data switch will need to be put in the cross over position, if Data 2 flashes then select straight through. If neither data light flashes then try switching the CTS/DTR switch to DTR. If the Handshake 1 i.e.d. is illuminated then select cross over on the Data switch; if Handshake 2 is on then use straight through. Cancel the Print command on the other computer, put the switches in the correct position; ready your host computer to accept data via the serial port and you can start printing the text file required.

COMPONENTS...

SWITCHES

S1,S2 double pole double throw (d.p.d.t.) centre off (2 off)
S3,S4 single pole double throw (s.p.d.t.) (2 off)

SEMICONDUCTORS

D1-D7 i.c.d. (7 off)

RESISTORS

R1-R8 1k $\frac{1}{4}$ W 5% (8 off)

MISCELLANEOUS

Multicore screened cable (9-way);
25-way D-type connector (2 off);
box, Veroboard, etc.

300 and 1200 for modem work and 9600 for communication with printers. If the baud rates of transmitter and receiver are not the same then garbled transmissions will result. The other parameters to watch are the number of data bits—usually 8 but may be seven—and the number of start and stop bits, usually 1 and 1 or 2 respectively. These can be altered when setting up your computer and you must ensure that they are the same on both sides of the link.

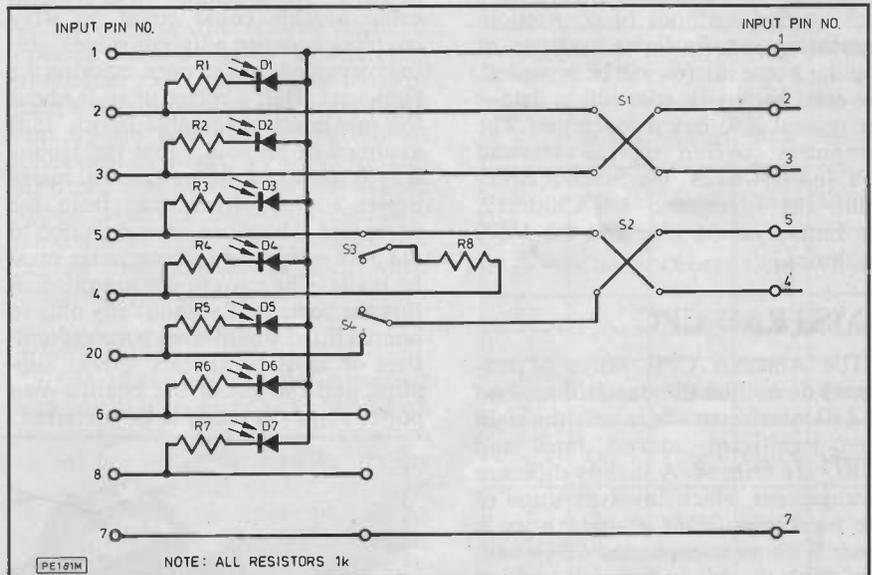


Fig. 1. Circuit diagram

In connecting to peripherals, the same technique is used except this time the DTR i.e.d. may be illuminated. The usual positions are cross over to connect computer to computer and computer to printer and straight through for modem work.

If after all this you still can't communicate or get garbage then you need to check the baud rate and data stream set-up. The baud rate is the speed at which data is transmitted—it can range from 75 baud (used in Prestel) to 19,200 baud. The common values are

There are variants on the RS232 interface such as the RS422. The main difference is in the voltage levels used. A true RS232 works on +12 and -12 volts whilst some of the others work on TTL voltages. In the majority of instances you can interconnect between them with no problems since the chips sets used today have been designed to have wide tolerance limits.

With the breakout box set up you should have trouble-free communication between your computer and anything designed for its serial port. **PI**

THE PE HOBBY BUS

PART THREE BY R. A. PENFOLD

Connection details and programs for the Spectrum, Amstrad, MTX, MSX and the Enterprise

ALTHOUGH the PE Hobby Bus project should connect successfully to virtually any computer which has the control, data, and address buses available, it is impossible to have a standard method of connection. Apart from differences in the type of microprocessor used in various computers, and consequent differences in the control bus structure, the available address range for input/output devices varies from one machine to another. Those who are experienced at interfacing projects to their computers can no doubt work out a suitable method of connection for themselves, but for those without the necessary experience, and those who have an unwillingness to risk experimenting with untried methods of connection, interfacing details for a number of popular home micros will be provided. We start here with connection details for several Z80 based machines. The computers covered are the Amstrad CPC464/664/6128, the Sinclair Spectrum, the Memotech MTX500/512, the Enterprise 64/128, and the MSX machines.

AMSTRAD CPC

The Amstrad CPC range of machines do not use the standard method of Z80 interfacing where only the eight least significant address lines and $\overline{\text{IORQ}}$ are utilized. A slightly different arrangement which involves some of the most significant address lines is used. With an unexpanded CPC464 it is possible to use a very simple method of interfacing where A10 and $\overline{\text{IORQ}}$ going low is used to activate the add-on device, with the lower address lines being available if a number of registers must be addressed. With machines that have disc drives and (or) the communications interface things are a little more stringent. In addition to A10 it is possible to decode A8 and A9 to give four pages of input output address range (&F8, &F9, &FA, and &FB). The eight least significant address lines must be decoded to place user add-ons at addresses in the range of &**E0 to &**FF.


There is no definitive way of connecting the Amstrad computers (or any others for that matter) to the Hobby Bus, but the suggested method is to use A0 to A4 as the lines which select the PIA and each of the seven slots, plus the four addresses within each slot. The address decoder responds to A5 to A7 going high while A10 and $\overline{\text{IORQ}}$ are low. Suggested basic connection details for the Amstrad machines (and the others) are provided in Table 1. Obviously other lines, such as the clock and interrupt types, can also be connected as suggested in the Hobby Bus circuit diagram. Initially though, it is probably best just to make the basic connections and to get the system up and running. Do not use a long connecting cable as this could result in stray coupling between adjacent cables, giving corrupted data or even crashing the computer. Half a metre or so is about the maximum acceptable length. It is assumed in Table 3.1 that the Hobby Bus is powered from its own mains power supply rather than from the computer. Therefore, no connection to the +5V output of the computer must be made. The current consumption of just the basic unit without any plug-in boards fitted would stretch the capabilities of most computers' power supplies, and the use of the board's own power supply is much to be preferred.

Connection to the 'floppy disc' port of the CPC464, or 'expansion' port of the CPC664/6128 is via a 2 by 25 way 0.1 inch pitch edge connector. As it is unlikely that a type fitted with a suitable polarising key will be obtainable, it is advisable to clearly mark the top edge of the connector as such. Connection details are provided in Fig. 3.1. Check and double check all connections very carefully, and if possible use multicoloured ribbon cable as this minimises the risk of muddling up any of the leads.

For the decoder to function properly the appropriate links must be fitted to the printed circuit board, and the eight d.i.p. switches must be given the correct settings. Details of the links and switch settings are given in Tables 3.2 and 3.3 respectively. In Table 3.2 a 'X' indicates that no link is needed, while '0V' means that the appropriate link terminal should be connected to the 0V rail. Suitable 0V connection points are provided near the link terminals.

MODIFICATION

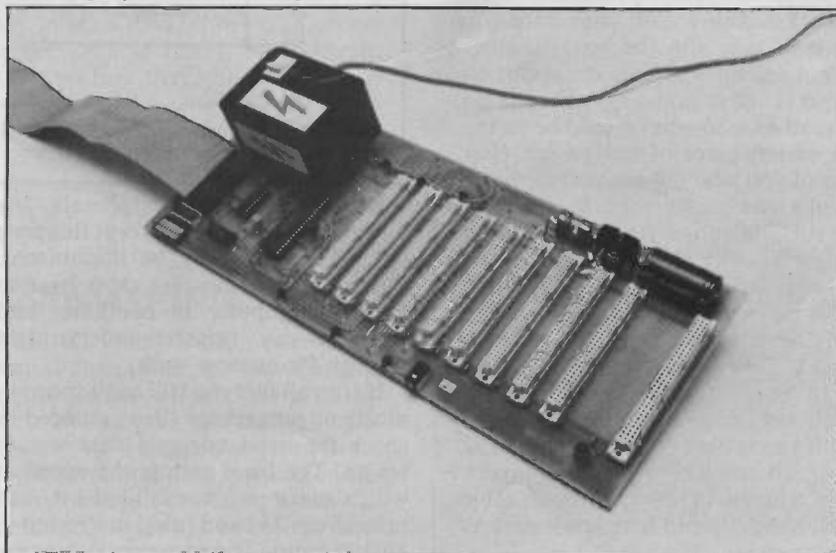With the suggested method of connection and the board unmodified, the $\overline{\text{RD}}$ input for the 8255 PIA is obtained by inverting the WR line using IC6c. With Z80 computers a $\overline{\text{RD}}$ line is available on the control bus, and it is



THE PE HOBBY BUS

Table 3.1. Basic connection details for the computers

SK11 Pin Nos.	Amstrad	Spectrum	MTX	Enterprise
1	A4	A10	A4	A4
2	WR	WR	WR	WR
3	A0	A6	A0	A0
4	A3	A9	A3	A3
5	A1	A7	A1	A1
6	A2	A8	A2	A2
7				
8				
9				
10				
11				
12				
13				
14				
15				
16				
17	A6		A5	
18	A7		A6	
19	A10	A5	A7	A7
20	IORQ	IORQ	IORQ	IORQ
21	A5			
22				
23				
24				
25	GND	GND	GND	GND
26				
27	D0	D0	D0	D0
28	D1	D1	D1	D1
29	D2	D2	D2	D2
30	D3	D3	D3	D3
31	D4	D4	D4	D4
32	D5	D5	D5	D5
33	D6	D6	D6	D6
34	D7	D7	D7	D7
35				
36				
37				
38				
39	RD	RD	RD	RD
40				

not necessary to generate one in this way. In practice the PIA seems to operate more reliably if the real RD signal is used in place of the synthesised one. To do this it is first necessary to disconnect the output of IC6c from pin 5 (the RD input) of IC7. This can most easily be achieved by omitting the through-pin situated roughly half way between link 5 and C16, or removing it if it has already been fitted. An insulated link wire is then fitted on the underside of the board from the point left vacant by the through-pin to pin 5 of IC4, being careful not to produce any accidental short circuits. It is recommended that this modification should be implemented when using the unit with any Z80 based computer.

Table 3.2. The links required for each computer

Link No.	Amstrad	Spectrum	MTX	Enterprise
1	X	0V	X	0V
2	X	0V	X	0V
3	X	X	X	X
4	X	X	X	X
5	0V	0V	0V	X
6	0V	0V	0V	X
7	0V	0V	0V	X
8	X	0V	0V	X
9	X	X	X	X

8255 PIA

There is insufficient space available here to permit a detailed explanation of how the 8255 is programmed to function in its various operating modes. However, in this context it will normally only be used in mode 0, which provides three eight bit ports (designated 'A', 'B', and 'C' by the chip manufacturer). Ports A and B can each be set as eight inputs or eight outputs. Port C can also be set as all inputs or all outputs, but it can also have split operation. This effectively divides it into two 4-bit (nibble) ports, with one nibble set as outputs and the other set as inputs. These are called port 'CL' (C Lower) and 'CU' (C Upper). Table 3.4 shows the number which must be written to the control register in order to set each of the sixteen mode 0 options. Table 3.5 gives the addresses of the four PIA registers, plus those of each slot. Note that as address lines A8 and A9 are not decoded, equivalent addresses in pages &F9, &FA, and &FB can also be used. In fact echoes appear at other addresses, but only addresses in these four Amstrad approved pages should be used when accessing the Hobby Bus.

TESTING

Connect the unit to the computer and switch it on prior to switching on the computer. The simple program shown below can be used for testing purposes. This sets port C for split operation, with the upper port set as outputs and the lower port set as inputs. This enables D2 to be controlled and S2 to be read. D2 should flash on and off, while the value printed on-screen should be either 0 or 4 depending on the setting of S2. The

program also provides output pulses on outputs 1 to 7 of IC8, and it should be possible to detect these with a logic probe or oscilloscope.

```

5 REM AMSTRAD TEST PROG
10 OUT &F8E3,147
20 OUT &F8E2,64
30 PRINT INP(&F8E2) AND 4
40 OUT &F8E4,0
50 OUT &F8E8,0
60 OUT &F8EC,0
70 OUT &F8F0,0
80 OUT &F8F4,0
90 OUT &F8F8,0
100 OUT &F8FC,0
110 OUT &F8E2,0
120 FOR D = 1 TO 100:NEXT
130 GOTO 20
    
```

SPECTRUM

The Spectrum is another machine which uses a slightly non-standard method of Z80 input/output mapping. The basic idea is to take one of the least significant address lines low in order to activate input/output devices, and some of the most significant address lines are used if a device has more than one register. Address lines A0 to A4 are reserved for internal hardware or for Sinclair add-ons such as the Interface 1. However, all the other address lines are free for user add-ons.

The recommended method of interfacing is to use A5 and IORQ going low

Table 3.3. DIP switch settings for each computer

'S' No. Marked No.	Amstrad	Spectrum	MTX	Enterprise
S3 1	Closed	Closed	Closed	Closed
S4 2	Closed	Closed	Open	Closed
S5 3	Closed	Closed	Closed	Closed
S6 4	Open	Closed	Closed	Closed
S7 5	Open	Closed	Closed	Closed
S8 6	Closed	Closed	Closed	Closed
S9 7	Closed	Closed	Closed	Closed
S10 8	Open	Closed	Closed	Closed

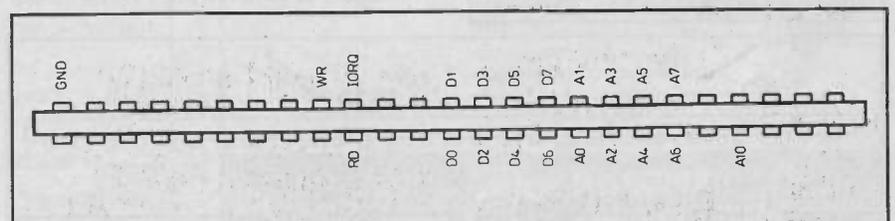


Fig. 3.1. CPC464 connection details

THE PE HOBBY BUS

to activate the address decoder, and to have the PIA and slots selected using A6 to A10 inclusive. One consequence of the Spectrum's rather topsy-turvy address bus organisation is that, as can be seen from Table 3.5, the Hobby Bus does not reside at 32 contiguous addresses. Although at first sight the addresses may seem to be almost randomly scattered through the input/output map, they are in fact spaced 64 addresses apart. Fig. 3.2 gives connection details for the Spectrum's expansion port.

Table 3.4. The control number needed to set the 8255 in the various mode 0 options

Control Number	Port A	Port B	Port CC	Port CU
128	OUT	OUT	OUT	OUT
129	OUT	OUT	IN	OUT
136	OUT	OUT	OUT	IN
137	OUT	OUT	IN	IN
130	OUT	IN	OUT	OUT
131	OUT	IN	IN	OUT
138	OUT	IN	OUT	IN
139	OUT	IN	IN	IN
144	IN	OUT	OUT	OUT
145	IN	OUT	IN	OUT
152	IN	OUT	OUT	IN
153	IN	OUT	IN	IN
146	IN	IN	OUT	OUT
147	IN	IN	IN	OUT
154	IN	IN	OUT	IN
155	IN	IN	IN	IN

The program given below is suitable for testing purposes. It flashes D2 on and off, but there is no bitwise AND function in Sinclair BASIC it reads port A rather than S2. Taking PA7 to 0V should give readings of 127 or less—taking it to +5V should give readings of 128 or more. Pulses are provided at the outputs of IC8.

```

5 REM SPECTRUM TEST PROG
10 OUT 63711,147
20 OUT 63647,64
30 OUT 63775,0
40 OUT 64031,0
50 OUT 64287,0
60 OUT 64543,0
70 OUT 64799,0
80 OUT 65055,0
90 OUT 65311,0
100 PRINT IN 63519
110 OUT 63647,0
120 PAUSE 20
130 GO TO 20
    
```

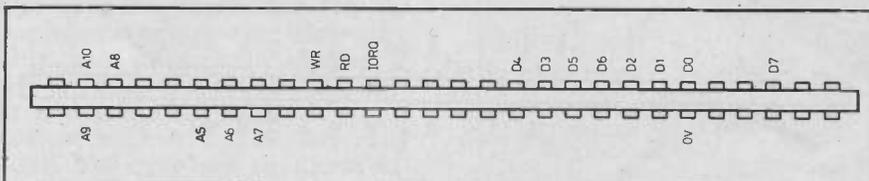


Fig. 3.2. Spectrum connection details

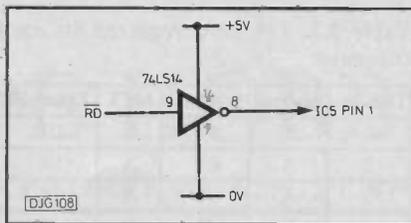


Fig. 3.3. For use with the MTX machines, pin 1 of IC5 must be driven from the RD line via an inverter

MTX500/512

The Memotech machines use standard Z80 interfacing with IORQ and the eight least significant address lines being used, giving an address range of 0 to 255. There are some unallocated addresses from 16 to 30, but there is insufficient space here for the Hobby Bus. Address from 32 upwards are unused internally, and are free for use on a machine which has no expansion other than the internal RS232C port. The suggested method of connection and switch settings place the Hobby Bus at addresses from 128 to 159, but by altering the settings of S4, S6, and S7 the unit can be placed in other 32 address blocks, and can be placed where it will not interfere with other add-ons.

A slight problem arose when using the Hobby Bus with an MTX500, in the form of corrupted data when reading the PIA, and occasional system crashes when accessing the unit. This seems to be due to a problem with spurious enabling of IC5 when it is set to the send mode (and is placing data onto the computer's data bus). The same problem did not occur with other

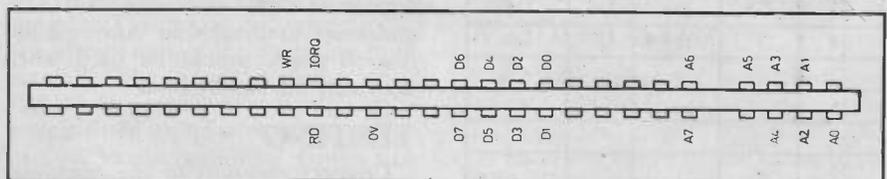


Fig. 3.4. MTX connection details

Z80 based computers, except in a much milder form on the Enterprise and CPC6128 where it caused very occasional glitching during read operations. However, this simple modification will completely cure the problem and can be used with an MTX computer or any other Z80 machine which exhibits the same problem. All that is necessary is to drive pin 1 of IC5 from

Table 3.5. The PIA and slot addresses for various computers

DEVICE	Amstrad (Hex)	Spectrum	MTX	Enterprise
8255 (A)	F8E0	63519	128	0
8255 (D)	F8E1	63583	129	1
8255 (C)	F8E2	63647	130	2
8255 (con)	F8E3	63711	131	3
SLOT 1	F8E4	63775	132	4
SLOT 1	F8E5	63839	133	5
SLOT 1	F8E6	63903	134	6
SLOT 1	F8E7	63967	135	7
SLOT 2	F8E8	64031	136	8
SLOT 2	F8E9	64095	137	9
SLOT 2	F8EA	64159	138	10
SLOT 2	F8EB	64223	139	11
SLOT 3	F8EC	64287	140	12
SLOT 3	F8ED	64351	141	13
SLOT 3	F8EE	64415	142	14
SLOT 3	F8EF	64479	143	15
SLOT 4	F8F0	64543	144	16
SLOT 4	F8F1	64607	145	17
SLOT 4	F8F2	64671	146	18
SLOT 4	F8F3	64735	147	19
SLOT 5	F8F4	64799	148	20
SLOT 5	F8F5	64863	149	21
SLOT 5	F8F6	64927	150	22
SLOT 5	F8F7	64991	151	23
SLOT 6	F8F8	65055	152	24
SLOT 6	F8F9	65119	153	25
SLOT 6	F8FA	65183	154	26
SLOT 6	F8FB	65247	155	27
SLOT 7	F8FC	65311	156	28
SLOT 7	F8FD	65375	157	29
SLOT 7	F8FE	65439	158	30
SLOT 7	F8FF	65503	159	31

the RD line of the computer via an inverter, as shown in Fig. 3.3.

It is not difficult to implement this modification in practice, and there is provision for an extra d.i.l. i.c. on the Hobby Bus printed circuit board. It is quite easy to wire in the 74LS14, but note that the track feeding into pin 1 of IC5 must be cut close to IC5 so that this pin is only driven from the output of the additional inverter, and is cut off from IC3's output.

The MTX expansion port is a 2 by 30 way 0.1 inch pitch edge connector, but a Spectrum type connector is a better choice as it has a suitable polarising key, and no connections are made to the parts that a Spectrum connector cannot reach. Wiring details are provided in Fig. 3.4.

THE PE HOBBY BUS

The MTX test program is given below. Like the Spectrum program, it reads port A rather than S2.

```
5 REM MTX TEST PROG
```

```
10 OUT 131,147
20 OUT 130,64
30 PRINT INP(128)
40 OUT 136,0
50 OUT 140,0
60 OUT 144,0
70 OUT 148,0
80 OUT 152,0
90 OUT 156,0
100 OUT 130,0
110 FOR D = 1 TO 100:NEXT
120 GOTO 20
```

ENTERPRISE

The Enterprise 64 and 128 both use the standard system of Z80 interfacing, and addresses below 128 are all left unused. The address decoder can therefore respond to just \overline{IORQ} and A7 going low. Connections to the Enterprise expansion port are made by way of a 2 by 33 way 0.1 inch pitch edge connector, as shown in Fig. 3.5. The Enterprise test program is shown below, and this uses the BAND (binary AND) function to read S2.

```
5 REM ENTERPRISE TEST
```

```
PROG
10 OUT 3,147
20 OUT 2,64
30 PRINT IN(2) BAND 4
40 OUT 4,0
50 OUT 8,0
60 OUT 12,0
70 OUT 16,0
80 OUT 20,0
90 OUT 24,0
100 OUT 28,0
110 OUT 2,0
120 FOR D = 1 TO 100
130 NEXT
140 GOTO 20
```

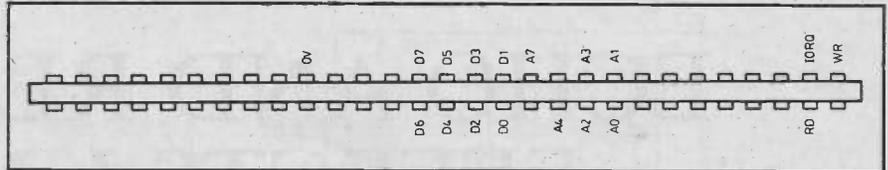


Fig. 3.5. Enterprise connection details

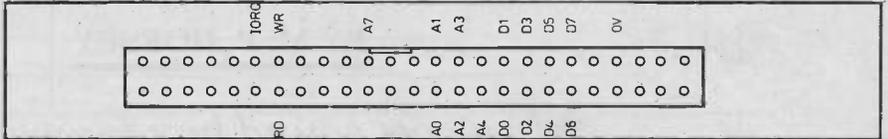


Fig. 3.6. MSX connection details

MSX MACHINES

The unit has not yet been tried with an MSX computer, but like the Enterprise computers these have the lower half of the input/output map left vacant, and user add-ons are interfaced to them in exactly the same way. The MSX expansion port connector is a different type though, and a 50 way IDC header socket is required. Fig. 3.6 shows the necessary connections to this. Next month details of 6502 base computers will be given together with news of a range of exciting add-ons for the Hobby Bus including SBC's, IO and memory cards. **PE**




Amateur Radio & Electronics Hobby Fair

To be held at Wembley Conference Centre, Saturday 5th & Sunday 6th July 1986

- ★ The first Two Day Fair to be held in the South of England. A major new event in the Amateur Radio Calendar.
- ★ Over 200 retail & manufacturers stands – plus lots more.
- ★ See future publications for more details.

The Organisers are: Amateur Radio Promotions, Woodthorpe House, Clapgate Lane, Birmingham B32 3BU – Telephone: 021-421-5516.

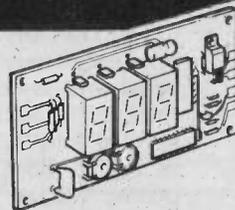DIGITAL VOLTMETER MODULE WITH HIGH BRIGHTNESS LED DISPLAY



- * High accuracy $\pm 0.1\% + 1$ digit.
- * Operates from single supply 7-12V.
- * Reads -99mV to 999mV which is easily extended.
- * Large Bright 0.43" LED Displays.

Only
£14.95
+ VAT

We are pleased to once again offer this tried and tested Digital Voltmeter module which is suitable for use in a wide range of test equipment. Supplied with full details describing how to easily extend the basic range, measure current resistance and temperature. The module, which is fully guaranteed, has been supplied to Electricity Authorities, Government Departments, etc. etc.


TEMPERATURE MEASUREMENT KIT DT10

A simple though effective module which, when constructed, provides a linear output of 10mV per °C over the temperature range +100°C to -10°C. The unit is ideal for use in conjunction with the above DVM module, providing an accurate digital thermometer suitable for a wide range of applications.



Only
£2.95
+ VAT

DUAL POWER SUPPLY PS 209

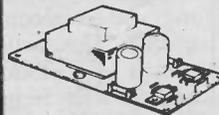

This fully built mains power supply provides two, 9V stabilised outputs up to 250mA each. The unit is ideally suited for use with the Digital Voltmeter and the Temperature Measurement unit DT10.

£5.65
+ VAT

Order by post, order by phone
Add 15% V.A.T. to all prices
U.K. orders add 70p post & packing
Export orders - post & packing at cost



RISCOMP LIMITED Dept. PE17,
51 POPPY ROAD,
PRINCES RISBOROUGH,
BUCKS
Tel: (084 44) 6326

ECHO AND REVERB EFFECTS UNIT

BY M. P. HORSEY

A low-cost sound box for weird and wonderful effects—crazy crescendo, erie echo and raucous reverberation

VARIOUS devices are employed to enable sound reverberation or echo effects. These include multiple head tape recorders and metal springs. In recent times 'bucket-brigade' delay line integrated circuits have become available. For example the type TDA 1022 provides theoretical delays of up to 51 milli-seconds. Unfortunately, the actual delay possible is very much less, and a number of these i.c.s have to be cascaded together.

A new bucket-brigade delay line i.c. has become available, which provides delays of three times longer duration. This i.c. is a type TDA 1097. While a little more expensive, only two such i.c.s are required to provide reverberation and echo effects.

A variety of sound effects can be obtained with this circuit. While designed for reverberation, the time delay can be sufficiently long to produce echo effects. In addition, the feedback may be increased to produce a crescendo effect—ideal for producing weird sounds.

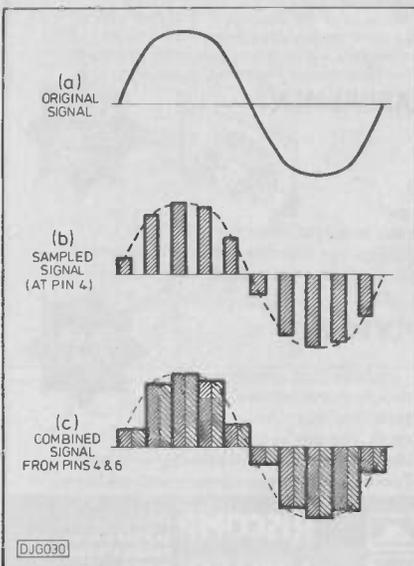


Fig. 1. Audio sampling

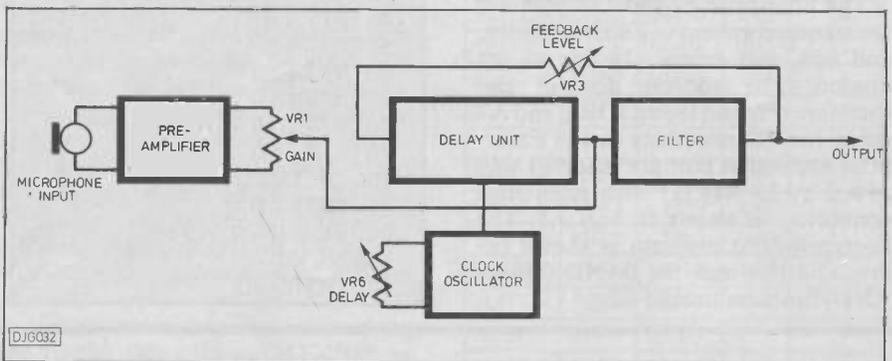


Fig. 2. System block diagram

PRINCIPLE OF OPERATION

The TDA 1097 is a 1536 stage delay line. Each 'stage' is a capacitor, fabricated with associated circuitry within the i.c. The audio (analogue) signal is divided into 'samples'—as illustrated in Fig. 1. Each sample represents a precise voltage, and is stored in the first capacitor CO, or 'stage'. Between successive capacitors is an electronic switch which transfers the charge from one capacitor to the next. Thus the 'sample' is transferred along the capacitors, rather like water being passed from one bucket to the next—as in the old method of fire-fighting. Hence the name 'bucket-brigade' delay line.

The time taken for samples to travel from one end to the other depends upon the number of stages and the rate at which the electronic switches operate. In this i.c. the number of stages is fixed at 1536. However, several i.c.s may be connected in 'series' if required. The switching rate is determined by a clock pulse fed to pins 1 and 2. The frequency of this clock pulse may be from 5kHz to 100kHz. However, in practice this frequency should be at least twice the maximum audio frequency required.

The circuit described is intended for the human voice, and the maximum

audio frequency chosen was 8kHz. The clock frequency is variable and ranges from about 12kHz upwards. At a clock frequency of 20kHz a delay of 38 milli-seconds per i.c. is provided. Thus with two i.c.s a delay of up to 76 milli-seconds is possible. Since the output is fed back into the i.c., reverberation can continue for some time.

ELECTRONIC FILTER

If electrical charges are to be passed from capacitor to capacitor it will be apparent that only alternate capacitors can actively hold the samples at any one time. The audio signal will therefore be very 'split up' as indicated in Fig. 1(b). Filtering such a signal is difficult—and would result in only half the maximum possible audio signal frequency indicated above. This fragmented audio signal is taken from the main output pin 4. An output is also provided from the PREVIOUS stage at pin 6. The charges at this stage fill in the gaps as shown in Fig. 1(c). Thus if pins 4 and 6 are connected together, the combined output provides greater continuity of signal and simplifies filtering.

This combined output is fed to an active filter comprising a 741 op-amp i.c. and associated resistors and capacitors. The effect of this circuit is to cut

ECHO/REVERB UNIT

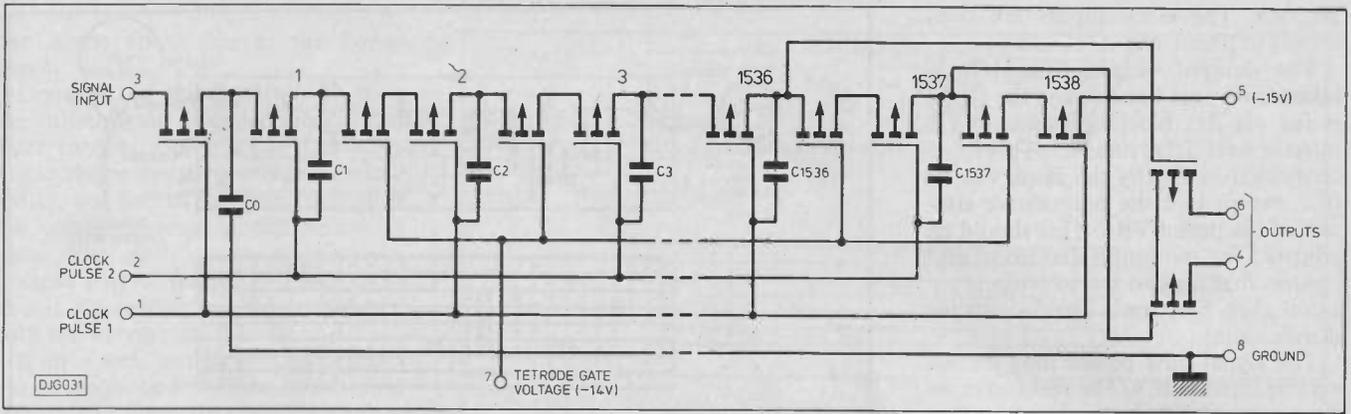


Fig. 3. Internal details of the TDA 1097

off all frequencies above 8kHz. Thus the 'bumpy' wave of Fig. 1(c) is reduced to a smooth audio wave similar to the input.

CIRCUIT ARRANGEMENT

It is important to note that the circuit employs a POSITIVE EARTH arrangement as shown in Fig. 4. This is unusual, and may cause confusion to the unwary observer. The arrangement will not affect the way in which the circuit is connected to other equipment, such as a power amplifier. The project consists of three main sections. These comprise the power supply, pre-amplifier, delay circuit and filter. A moving coil microphone may be connected to the input, and the output is sufficient to drive a power amplifier.

Larger input signals could be applied at capacitor C6 if required.

Variable resistor VR1 acts as a microphone level control; VR3 controls the amount of feedback and hence the total reverberation time, and VR6 controls the clock frequency, and hence the length of time for which the audio signal is delayed in IC2 and IC3.

MICROPHONE AMPLIFIER

A high gain amplifier (Fig. 4) based on a 741 i.c. increases the very low signal level produced by a moving coil microphone. The microphone signal is fed via d.c. blocking capacitor C1 to the non-inverting input of IC1. Resistors R1 and R2 hold this input at about -7 volts. The output from IC1 is fed back to the inverting input via R3, to

reduce the gain to an acceptable level. The frequency range is set by C2, C3 and R4. The output passes via d.c. blocking capacitor C4 to VR1—the microphone level control.

DELAY AND FILTER CIRCUITS

The amplified audio signal passes via R5 and C6 to the filter circuit comprising IC4 and associated components (described later). Part of the output from IC4 passes via VR3 and C9 to the input of the bucket-brigade delay line IC2. The d.c. voltage at pin 3 is held at -7 volts by means of VR2 and R9. Capacitor C7 decouples the junction between VR2 and R9. Pin 5 of IC2 is connected to -15 volts; pin 8 to zero volts, and pin 7 to about -14 volts as set by the resistor chain R6, R7, VR2

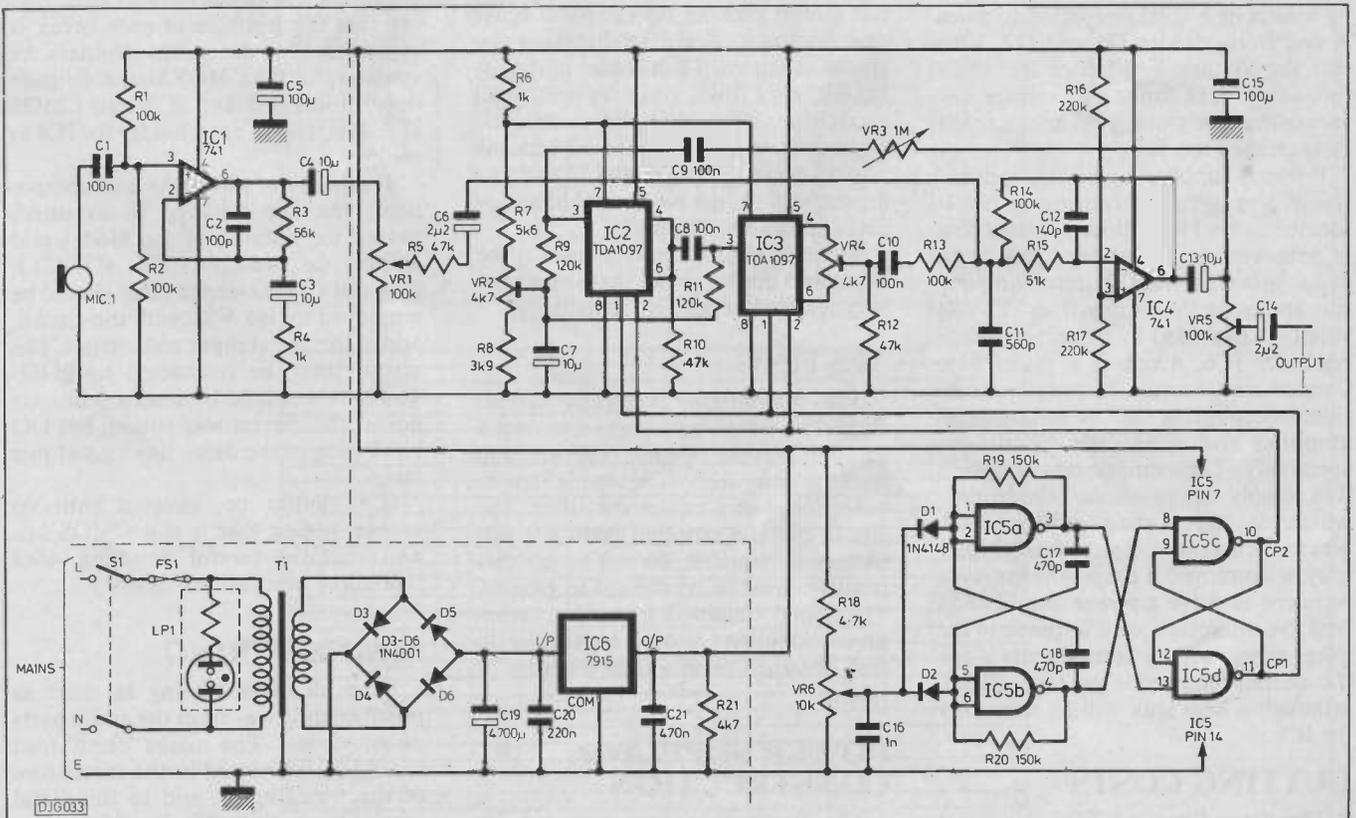


Fig. 4. Complete circuit diagram

ECHO/REVERB UNIT

and R8. The clock inputs are connected to pins 1 and 2.

The delayed output from IC2 is taken from pins 4 and 6, and the signal is fed via d.c. blocking capacitor C8 into the next delay line IC3. This i.c. is connected in exactly the same way as IC2, except that the outputs are connected via preset VR4. This should be adjusted for minimum distortion and ensures that the two sets of outputs are equal. (See 'Electronic filter' above for clarification).

The signal now passes into the inverting input of IC4. The resistor/capacitor network filters the signal, so that frequencies above about 8kHz are cancelled out. Pin 3 is held at about -7 volts by R16 and R17. Part of the output from pin 6 travels via VR3 and C9 to the input of IC2 as previously described, to complete the feedback loop. VR2 sets the feedback level and thus the length of time for which the signal reverberates.

The output from IC4 is also fed to the output socket via d.c. blocking capacitors C13 and C14. Preset VR5 allows the circuit to be correctly matched to a range of power amplifiers.

CLOCK SIGNALS

An inexpensive CMOS 4011 i.c. is used to supply the two antiphase clock pulses required by the delay line i.c.s. The arrangement of resistors and capacitors and use of all four gates provides a very clean symmetrical output wave, the frequency of which may be varied by means of a voltage applied to gates A and B via diodes D1 and D2. VR6 sets the voltage and hence the clock frequency. R18 limits the voltage, ensuring that the clock frequency cannot be increased too far.

Power is supplied by a fairly conventional arrangement comprising transformer T1 and four diodes. Smoothing is achieved by capacitor C19, with capacitors C20 and C21 removing any tiny spikes on the supply. The -15 volt supply is provided by negative voltage regulator IC6, which is a type 7915. Capacitors C5 and C15 provide additional decoupling for the microphone amplifier and delay/filter circuits respectively. The components specified will supply up to about 60mA. d.c., which is more than sufficient. A greater current output transformer may be employed if the power supply is required to drive a power amplifier as well. No alteration need be made to the other power supply components if the d.c. output required is less than 1 amp, although a heat sink will be necessary for IC6.

CUTTING COSTS

The delay line i.c.s TDA 1097 are rather expensive and some construc-

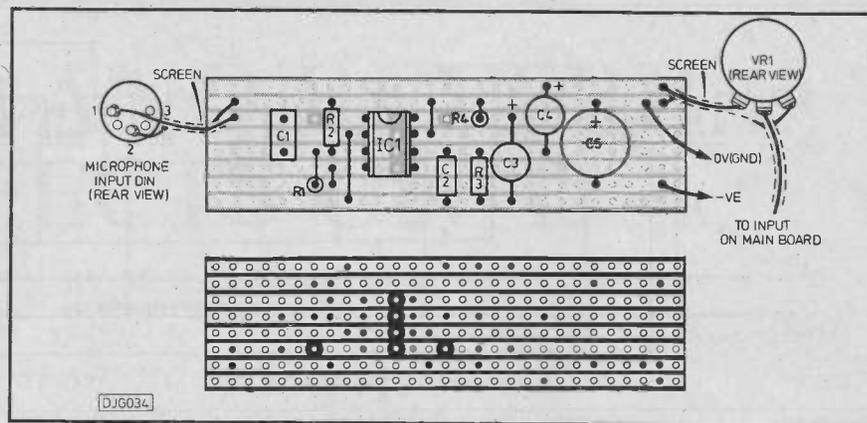


Fig. 5. Amplifier construction details

tors may prefer to build the circuit with one rather than the two shown. It is recommended that the circuit be built with all the i.c. holders and wire links, so that the second TDA 1097 may be added later. If only one delay line i.c. is used, leave out IC2 and C8, and take C9 to pin 3 of IC3 instead of IC2. The maximum delay possible will now be halved, but quite interesting reverberation effects can still be obtained.

MICROPHONE AMPLIFIER CONSTRUCTION

The microphone amplifier circuit is sensitive to electrical interference, and it seemed prudent to construct it separately (Fig. 5), to allow additional screening. As with all amplifiers, neatness of wiring is important to prevent the circuit picking up electrical noise and feedback. Begin by breaking the tracks as shown. Then solder in the i.c. holder, wire links, resistors and small capacitors. Note that the electrolytic capacitors must be connected with the correct polarity. Plug in the 741 i.c. the correct way round. No special handling precautions are required.

Screened cable should be used at the input and output. Note that the screen is connected to positive (earth).

TESTING

The microphone amplifier circuit should be tested separately. Connect a suitable moving coil microphone, and feed the amplifier output to the tape or tuner input of a power amplifier. The circuit may be powered from a 9 volt battery if required; do not forget that positive must be connected to ground. The signal obtained from the microphone amplifier should be similar to that obtained from a tape recorder or tuner.

POWER SUPPLY CONSTRUCTION

The few components required for the power supply may be mounted on a

piece of stripboard near the mains transformer as shown in Fig. 6. A heat sink is not required for IC6 as it is working well below its rated current output. A 100mA minus 15 volt regulator is available, and may be used if preferred. There is little price advantage however. Make sure that the large electrolytic capacitor C19 is connected with the correct polarity—noting POSITIVE/EARTH again. Note that track C is deliberately left unconnected.

MAIN CIRCUIT CONSTRUCTION

The delay line, filter and clock pulse generator are constructed on a single piece of stripboard as shown in Fig. 7. Label the stripboard carefully, and break the tracks where indicated, noting that the position of each break is critical in both directions. Holders are essential for the CMOS bucket-brigade delay lines, IC2 and IC3 and CMOS IC5. It is wise to use a holder for IC4 as well.

The holders, wire links and components may be soldered in as usual, noting the polarity of the diodes and electrolytic capacitors C6, C7, C13, C14 and C15. Screened cable should be employed to link VR2 with the circuit, and at the signal input and output. The screen must be connected to POSITIVE. IC4 should be inserted into its holder the correct way round, but DO NOT plug in the delay line i.c.s at this stage.

IC5 should be inserted into its socket, noting that it is a CMOS i.c., and requires careful handling. (See 'Handling precautions' below.)

MAINS WIRING

Keep all mains wiring as short as possible and away from the audio parts of the circuit. The mains 'earth' lead should be connected to the metal core of the transformer, and to the metal case of the project. The 'earth' connection should also be joined to the 'posi-

ECHO/REVERB UNIT

tive' (zero volts) line of the power supply.

Connect the power supply to both the microphone amplifier and delay/filter circuits. Connect the voltmeter across the power supply as before, and switch on. Switch off immediately if the voltage appears to fall below 15 volts. The likely cause of this is a bridged pair of tracks, or other short circuit—or either circuit connected with the wrong polarity.

If all is well, switch off and connect the microphone amplifier to the main circuit, and the main circuit output to a power amplifier. Set VR1 and the presets to about mid way.

Switch on the supply and speak into the microphone. The signal from the microphone amplifier should pass through the filter circuit and be heard via the power amplifier. No reverberation will occur as the delay line i.c.s have not yet been fitted. Adjust preset VR5 for good matching into the power amplifier and set VR1 for a reasonable microphone volume level.

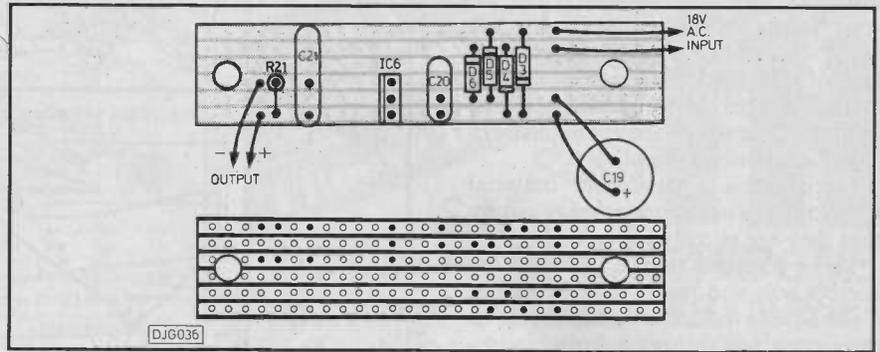


Fig. 6. Power supply construction details

The clock oscillator may be checked at this stage if an oscilloscope is available. Alternatively a high impedance earpiece may be connected across CP1 and CP2. When VR6 is turned fully clockwise (maximum delay, minimum frequency) a high pitched sound should be heard.

If all is well, switch off and short circuit the power supply to ensure that the capacitors are discharged before fitting IC2 and IC3.

HANDLING PRECAUTIONS

All CMOS i.c.s should be handled with care, as the static electricity which appears on insulated materials—including the human body—can easily destroy the i.c. The high cost of the bucket-brigade delay line i.c.s makes careful handling even more imperative.

Store the i.c.s in their original packaging material until the moment of

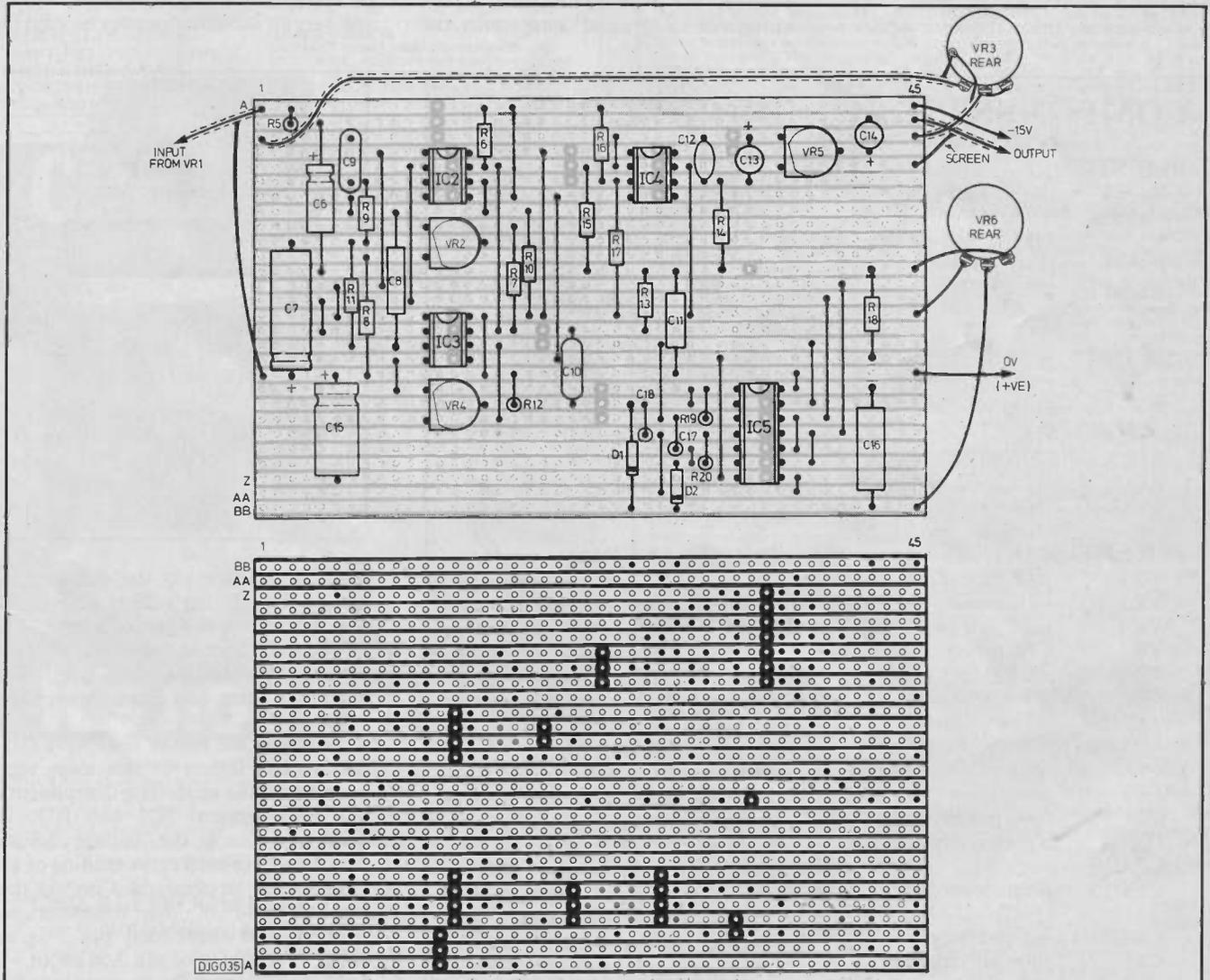


Fig. 7. Main circuit construction details

ECHO/REVERB UNIT

insertion into their holders. 'Earth' your hands by touching an earthed metal object (for example the metal case of a power unit plugged into the mains). Proper earthing straps which fit around the wrists are available from some components suppliers.

Place the i.c. packaging material against the destination socket to ensure that they are equally charged.

Make sure that the i.c. is facing the correct way and insert into its socket. Once fitted, the other components in the circuit will protect it from electrostatic effects, PROVIDING no alterations are made. If any further soldering is required, first remove IC2 and IC3, taking the same precautions as before and returning them to their original protective packaging.

FINAL TESTING

The circuit may now be tested. Set reverberation control VR3 to minimum resistance (maximum feedback). Switch on and adjust the delay control (VR6) to maximum delay (fully clockwise). A high pitch whistle may be heard. Turn up VR6 a little until the noise can no longer be heard. Any sound made into the microphone

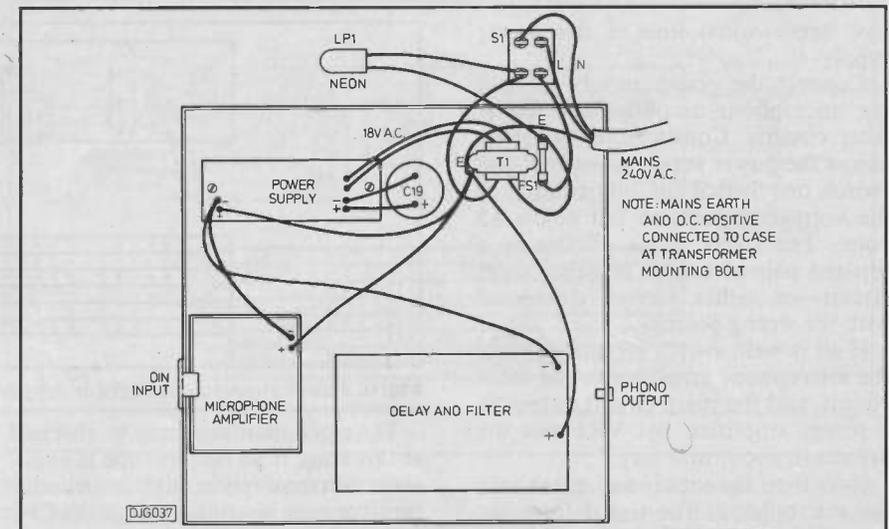


Fig. 8. Wiring diagram

should reverberate. Adjust VR3 so that the reverberation decays rather than increases.

Adjust preset VR2 so that the voltage between its sliding contact and ground is -7 volts. In other words connect the POSITIVE lead of the voltmeter to 'ground' and touch the

negative lead to the sliding contact of VR2 whilst adjusting VR2 for a 7 volts reading. Preset VR4 should be adjusted so that the two sets of signals from pins 4 and 6 of IC3 are equal. In the absence of an oscilloscope VR4 should be set for minimum distortion. Alternatively an oscilloscope may be used to

COMPONENTS ...

RESISTORS

R1,R2,	100K (4 off)
R13,R14	
R3	56K
R4,R6	1K (2 off)
R5,R10,	47K (3 off)
R12	
R7	5k6
R8	3k9
R9	120K
R11	120K
R15	51K
R16,R17	220K (2 off)
R18,R21	4k7 (2 off)
R19,R20	150K (2 off)

POTENTIOMETERS

VR1	100K linear pot.
VR2	4.7K preset
VR3	1M linear pot.
VR4	4.7K preset
VR5	100K preset
VR6	10K linear pot.

CAPACITORS

C1,C8,	100n polyester (3 off)
C10	
C2	100p polystyrene
C3,C4,	10µ electrolytic (4 off)
C7,C13	
C5,C15	100µ electrolytic (2 off)
C6,C14	2µ2 electrolytic (2 off)
C11	560p polystyrene
C12	140p polystyrene

C16	1n polystyrene
C17,C18	470p polystyrene (2 off)
C19	4700µ electrolytic
C20	220n polyester
C21	470n polyester

SEMICONDUCTORS

IC1,IC4	741 op-amp (2 off)
IC2,IC3	TDA 1097 bucket-brigade delay line i.c.
IC5	CMOS 4011B
IC6	Regulator i.c. ±15V type 7915
D1,D2	Diodes type 1N4148 (2 off)
D3-D6	Diodes type 1N4001 (4 off)

MISCELLANEOUS

T1	mains transformer 18V (or 15V) 100mA secondary
LP1	mains neon with integral resistor
S1	mains toggle switch
FS1	fuseholder and 200mA fuse

Stripboards: 45 holes by 28 tracks (plus extra for mounting holes); 29 holes by 8 tracks, 28 holes by 6 tracks; i.c. holders; din socket (for microphone) 5-way; phono socket (for output); knobs, 3 off; mains cable; screened cable, connecting wire; grommets; screws; nylon nuts and bolts; metal cases as described; wire; solder; etc.



monitor the signal at the sliding contact of VR4. Using a fairly high time-base setting the two sets of component frequencies should be visible. VR4 should now be adjusted until the heights of these two sets of waves are equal.

Assuming the earlier tests were successful, any failure at this stage suggests a mistake in the few components and links around IC2 and IC3. If necessary, check the voltage across pins 5 and 8 of each i.c. A reading of 15 volts should be obtained. Connect the positive lead of the voltmeter to 'ground' and check that pin 7 is at about -14 volts, and pin 3 at about -7 volts. If all is well the circuits may be fitted into a suitable case.

PF

NEW SPECIAL OFFER EACH MONTH
ORDERS REC'D BY 4P.M. DESPATCHED
SAME DAY

FREE TO SCHOOLS & COLLEGES
THESE ITEMS ARE ONLY A FRACTION
OF OUR RANGE
ALL ORDERS SUBJECT TO 15% VAT &
65P P&P



ELECTRONIC COMPONENT SUPPLIERS
LATEST CATALOGUE

SEND £1 NOW (£2.50 OVERSEAS) FOR YOUR COPY INCLUDING A 50P VOUCHER, ORDER FORM, PRE-PAID ENVELOPE & SPECIAL OFFERS

ELECTRICAL	ADAPTORS These very high quality British made 2-Pin European Adaptors are ideal for driving radios, cassette recorders, TV games, calculators etc. The adaptor fits the UK shaver socket.
4-way Extension Socket 3-Pin Sockets Fused and with Neon Indicator	REF D.C. Volts Current 1+ 10+ 100+
As above but with lead	EDB 4-5V 200ma 50p 45p 32p
Twin Extension Socket White Nylon	EM3 6V 200ma £1.00 50p 55p
2-way Multiplug 13A Outlets	EM9 6V 400ma £1.50 £1.25 85p
3-way Multiplug 13A Outlets	
13A Plug White Fused EACH 46p	
Single Extension Lead on Carrier	
13A Socket on 15 metre cable	P&P 45p each £2.25 for 10 £4.95 for 100

3-CHANNEL CHART RECORDER £40 EACH + £10 P & P	JULY SPECIAL OFFER UNIVERSAL BATTERY CHARGER TO CHARGE PP3, AA, C & D TYPE NI-CADS	TRANSFORMERS-240 4-5-0-4-5 400mA 6-0-6 350mA
---	--	---

PICK-UP TOOL 75p EACH 5 FOR £3.00	ONLY £4.25 WITH ORDER OF £10 OR OVER	50p EACH 10 OFF 40p 100 OFF 30p + P&P 45p for 1 £1.60 for 10 £5.00 for 100
--	---	--

WIRE STRIPPERS 75p EACH 5 FOR £3.00	RESISTOR KITS 1/2 WATT RESISTORS 5 OFF EACH VALUE £3.35 10 OFF EACH VALUE £5.75 1/4 WATT RESISTORS 5 OFF EACH VALUE £4.75 10 OFF EACH VALUE £7.95	B.T. APPROVED MASTER SOCKET £2.85 SECONDARY SOCKET £1.95 ADAPTOR 10/3A £2.95 ADAPTOR 95A/BT £3.25 DUAL OUTLET LJM4: MASTER £4.80 SECONDARY £2.85 BELL TONE RINGER £7.50 4-CORE CABLE 15p per meter CABLE CLIPS 75p per 100 SELECTION OF 'PHONES	NI-CADS RECHARGEABLE CELLS AA (HP7) 95p EACH 10 for 85p EACH C (HP11) £2.14 EACH 10 for £1.98 EACH D (HP2) £2.30 EACH 10 for £2.10 EACH PP3 £3.75 EACH 10 for £3.65 EACH	GAS SOLDERING IRON ORYZ PORTASOL £13.90	EQUIVALENT BOOKS DIODES VOL. 1 £9.95 DIODES VOL. 2 £9.75 BOTH—£18.70 IC CMOS £7.50 IC TTL £7.55 IC LIN VOL. 1 £5.95 IC LIN VOL. 2 £5.99 BOTH—£9.99 THYRISTORS £9.99 TRANSISTORS A-Z £4.90 TRANSISTORS 2N-3N £5.10 BOTH—£9.00
--	--	---	---	--	--

MARCO TRADING
DEPT PE7 THE MALTINGS,
HIGH STREET, WEM,
SHROPSHIRE SY4 5EN
TEL: (0939) 32763 TELEX: 35565

SERVISOL PRODUCTS
SOLDA-MOP STANOARD GAUGE—74p LIGHT GAUGE—70p
INDUSTRIAL REEL—£2.90 TAPE HEAD CLEANER—£1.10 SUPA
FREEZE-IT—£1. SWITCH CLEANING LUBRICANT—£1.24 AERO-
KLENE—£1. SILICONE GREASE SPRAY—£1.50 EXCEL
POLISH—£1.

For KITS & COMPONENTS
Choose the easy way - with



Send SAE now
for our FREE CATALOGUE
or ring: 01-567 8910 for
the LOWEST prices on -

- | | | |
|--------|-----------------|----------|
| CMOS | TRANSFORMERS | BOOKS |
| TTL | CONNECTORS | TOOLS |
| LINEAR | REGULATORS | BOXES |
| TRIACS | MICROPROCESSORS | PCBs |
| SCRs | SPEAKERS | CRYSTALS |
| LEDs | HEATSINKS | SWITCHES |
| NICADS | MULTIMETERS | RELAYS |

AND LOTS LOTS MORE
or choose from our range
of over 30 kits . . .

HOME LIGHTING KITS DISCO LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300W of lighting.

TDR300K Remote Control
£14.95

Dimmer MK6 Transmitter for above **£4.50**

TD300K Touchdimmer **£7.75**

TS300K Touchswitch **£7.75**

TDE/K Extension kit for 2-way switching for TD300K **£2.50**

DL1000K - This value-for-money 4-way chaser features bi-directional sequence and dimming. 1kW per channel. **£15.95**

DLZ1000K - A lower cost uni-directional version of the above. Zero switching to reduce interference. **£8.95**

Optional opto input allowing audio 'beat' / light response (DLA/1) 70p

DL3000K - 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel. **£12.95**

HOME CONTROL CENTRE



DVM/ULTRA SENSITIVE THERMOMETER KIT

Based on the ICL 7126 and a 3 1/2 digit liquid crystal display, this kit will form the basis of a digital multimeter (only a few additional resistors and switches are required - details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading 0.1°. The kit has a sensitivity of 200mV for a full-scale reading automatic polarity and overload indication. Typical battery life of 2 years (PP3). **£15.50**

This kit enables you to control up to 16 different appliances by means of coded pulses in the mains wiring which may be decoded by special receivers anywhere in the house. The transmitter may be controlled manually or by the computer interface enabling your favourite micro to make your coffee in the morning, switch lights anywhere in the house, or your electric blanket in your bedroom. Just think of the possibilities - and no wiring!

This kit comprises a transmitter with pre-drilled box and two receivers.

XK112 **£42.00**

Additional receivers
XK111 **£10.00**

MK4 PROPORTIONAL TEMPERATURE CONTROLLER

Uses "burst-fire" technique to maintain temperature to within 0.5°C. Ideal for photography, incubators, wine-making, etc. Max load 3kW (240V AC). Temp range up to 90°C **£6.50**

ELECTRONIC LOCK KIT

With hundreds of uses in doors, garages, car anti-theft devices, electronic equipment, etc. Only the correct easily changed four-digit code will open it! Requires a 5V to 15V DC supply. Output 750mA. Fits into standard electrical wall box. Complete kit (excl. front panel) **£11.50**

XK101 **£11.50**

Electronic lock mechanism for use with the above kit. 70150 **£14.95**

STAR BUY

6 x 741	90p
6 x 555	90p
2 x 556	70p

TK ELECTRONICS
13 BOSTON RD
LONDON W7 3SJ

SEND 9"x6" S.A.E. OR CALL AT SHOP
MON-FRI 9-5pm
SATURDAY 10-4pm

ORDERING INFORMATION:
ALL PRICES EXCLUDE VAT

FREE P&P on orders over £20 (UK only), otherwise add 75p + VAT. Overseas P&P: Europe £2.75. Elsewhere £6.50. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 529314002.

LOCAL AUTHORITY AND EXPORT ORDERS WELCOME
GOODS BY RETURN SUBJECT TO AVAILABILITY

CRICKLEWOOD ELECTRONICS LTD

FREE!
catalogue

It's no secret...

...that there is a real difference at Cricklewood Electronics. That's why you should never be without the **FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE**, for sheer variety, competitive prices and service from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your **FREE** copy now (no SAE required). You have nothing to lose.

CRICKLEWOOD ELECTRONICS LIMITED
40 Cricklewood Broadway, London NW2 3ET
Tel: 01-450 0995/01-452 0161
Telex: 91 4977

VISA **ACCESS** **MASTERCARD** **AMEX**

PE

SPACEWATCH

BY DR PATRICK MOORE OBE

*Light on the dark comet
and future cometary encounters*

THE space scene during the first half of 1986 has been dominated by four vehicles—three successful, one tragic. There have been the immensely valuable unmanned craft, Voyager 2 to Uranus and Giotto to Halley's Comet (not forgetting, of course, the other members of the Halley armada, two Japanese and two Russian). In the field of manned flight, the Soviet authorities have sent up their Mir space-station, which is much the most ambitious so far. The disaster of the *Challenger* Shuttle is, of course, uppermost in all our minds, and quite apart from the human tragedy it has dealt a devastating blow to the whole of American space research. As a tribute to the crew, it has been officially announced by the LAU Minor Planet Centre that seven asteroids will be named in honour of the crew members: 3350 Scobee, 3351 Smith, 3352 McAuliffe, 3353 Jarvis, 3354 McNair, 3355 Onizuka and 3356

Resnik. All these asteroids were discovered between 1980 and 1984 by E. Bowell and N. Thomas at the Lowell Observatory in Arizona.

(Other asteroids have recently been named after contemporary astronomers: 1945 Wesselink, 2561 Roman, 3225 Hoag and 3299 Hall—the third of these after the current Director of the Lowell Observatory. I cannot resist adding that Asteroid 2602, discovered by Bowell in 1982, has been officially named 'Moore' after me!)

The first two cosmonauts of the Mir station, taken there by Soyuz 15, are Leonid Kizim and Vladimir Solovyov, and it may be of interest to say something about them.

Kizim was born at Krasny Liman, in the Donetsk region, on 6 August 1941. In 1963 he graduated from the Chernigov pilots' school, and then, after a spell in the Air Force (during which he became a test pilot) he joined the

cosmonauts unit. In 1980 he commanded Soyuz 3 and the orbital station Salyut 6. His second flight, lasting 237 days, was made in 1984 as commander of Salyut 6; he was joined by Solovyov, who had been born in Moscow on 11 November 1946 and had become a cosmonaut in 1978.

The Mir station is presumably permanent. How long Kizim and Solovyov will stay in it remains to be seen, but it has been suggested that the Russians are seriously considering a manned mission to Mars—in which case it is essential to carry out long-term experiments under conditions of zero gravity.

THE DARK COMET

It will take years to evaluate all the results obtained from the Giotto encounter with Halley's Comet on 13 March, but already some surprising

The Sky This Month

HALLEY's Comet remains well above the horizon this month; but it has faded so much that telescopes of some size are now needed to show it, and we must reconcile ourselves to the fact that the main part of the current apparition is over. Though the comet will be tracked for some years yet, it will not again be a naked-eye object until the year 2061.

Of the planets, Mercury is an evening object, at elongation on the 25th, but it will be best seen around mid-June, low above the WNW horizon as soon as the sky becomes dark enough. Venus, however, cannot possibly be missed in the west after sunset, as its magnitude is -3.4—much brighter than any other object in the sky apart from the Sun and the Moon. Mars, in Sagittarius, is brightening, and will be at opposition on 10 July; at present its magnitude is -2, superior to any star (even Sirius), though from British latitudes it is rather inconveniently low. Saturn is not far from Mars, and the rings are wide open, so that telescopically the planet is a glorious sight. Jupiter continues to be seen in the south-east during the early hours of the morning.

The Ophiuchid meteor shower appears from the 17th to the 26th, but the expected hourly rate is not high. There are no eclipses during June; the Moon is new on the 7th and full on the 22nd.

Evening skies are dominated by what is now usually called the Summer Triangle, consisting of the three brilliant stars Vega (in Lyra), Altair (in Aquila) and Deneb (in Cygnus). This was a nickname which I used

in a television Sky at Night programme over twenty years ago, and it seems to have passed into the literature, though it is completely unofficial—and is naturally inapplicable to the southern hemisphere, where the Triangle is seen in evenings during winter!

It is interesting to compare the three stars. Vega is a glorious blue, and is near the zenith; Altair is easily recognised by the presence of a fainter star to either side; Deneb, in the Cross of Cygnus, is much the faintest of the three, but it is also much the most remote, and is at least 60,000 times the power of the Sun. Were it as close to us in Altair, it would cast shadows. Appearances can be deceptive.

Antares, low over the southern horizon, also has a fainter star to either side, but there is no danger of confusion with Altair, if only because Antares is so red; its name means 'the Rival of Mars'. It is rather interesting to compare the two, which is easy at the moment because they are not very far apart—though of course Mars is very much the brighter of the two. Look also for the starclouds in Sagittarius, following Antares round; they are magnificent in binoculars, and of course they indicate the direction of that mysterious region, the centre of the Galaxy.

The Great Bear is high up, and so is Arcturus, in Boötes (the Herdsman), a lovely light orange colour. Arcturus is fractionally brighter than Vega, and is surpassed by only three stars, all in the southern hemisphere of the sky (Sirius, Canopus and Alpha Centauri).

SPACEWATCH

facts have come to light—and of these, the most remarkable is the colour of the nucleus. Instead of being ice-bright, as most people had expected, it has proved to be black. The albedo is no more than 2 per cent, and there are not many objects in the Solar System as dark as that. The nucleus is also somewhat larger than had been anticipated; it is some 12 kilometres long by 8 kilometres broad.

There still seems little doubt that Fred Whipple's 'dirty iceball' theory is essentially correct; nothing else can explain the characteristics of comets. But it is now clear that the dark 'dust' layer is much deeper than expected, and acts as an effective insulator; otherwise the ices would evaporate much more quickly than they actually do. And what is the nature of the dark material? Is it organic—perhaps some sort of 'tar'? This is at least possible, and it brings us straight on to the theories proposed by Sir Fred Hoyle and his colleague Professor Chandra Wickramasinghe.

Just before the Giotto encounter, when I was at Darmstadt (headquarters of the European Space Organization) Professor Wickramasinghe rang me up, and repeated his contention that the nucleus of Halley's Comet would prove to be dark. I admit that I was somewhat sceptical, and almost

everyone else at Darmstadt shared my view; but Wickramasinghe was right, and we were wrong.

According to the Hoyle-Wickramasinghe viewpoint, comets are carriers of life. They roam around the cosmos, and it was a comet which brought life to Earth in the first place—together with most of the water in our oceans. This is not all. Comets are essentially organic, and may deposit viruses in our atmosphere, resulting in epidemics. From a medical standpoint this idea has been regarded as outrageous, and something not to be taken seriously; neither have astronomers in general been at all impressed. Yet the Halley revelations make one think very hard indeed. As I have said elsewhere, Hoyle and Wickramasinghe have won the first round.

"he was right and we were wrong"

Of course, it would be hopelessly premature to suggest that the 'outlandish' theories about diseases from space have been proved simply by the fact that the nucleus of Halley's Comet is black rather than bright, but it is also true to say that before the Giotto pass it was thought very unlikely that organic materials would be found in any quantity. The essential need now is to

find out just what the dark material really is.

Also, are comets genuinely interstellar—as is believed not only by Hoyle and Wickramasinghe, but also by other eminent astronomers, notably Victor Clube and Bill Napier of Edinburgh? The accepted theory is that comets were 'left over', so to speak, when the planets were formed, more than 4.5 thousand million years ago, so that the 'dirty iceballs' are now orbiting the Sun at a distance of at least a light-year, and enter the inner Solar System only when they are perturbed by some agency or other. The concept of the Oort Cloud (named in honour of Jan Oort, who also was at Darmstadt) has not been seriously challenged over the past few decades, but there is no proof of its existence.

For the moment we can only await the full analyses of the Giotto findings, and hope for more cometary encounters in the foreseeable future.

If Hoyle and Wickramasinghe prove to be correct in all their views, we will have to do some radical re-thinking. Most authorities will still doubt whether this will be necessary, but it must also be admitted that their theories sound rather less outlandish now than they did before that exciting night when Giotto passed right through the coma of Halley's Comet. **PF**

Universal Semiconductor Devices Ltd.

17 GRANVILLE COURT, GRANVILLE ROAD, HORNSEY, LONDON N4 4EP, ENGLAND. TEL. 01-348 9420/9425 * TLX. 25157 usdco g



WE OFFER ONE OF THE LARGEST RANGES OF SEMICONDUCTORS AT HIGHLY ECONOMICAL PRICES. THE FOLLOWING SEMICONDUCTOR TYPES ARE AVAILABLE FROM STOCK. IF WE DON'T STOCK WHAT YOU NEED THEN WE CAN GET IT FAST FROM OUR FACILITIES IN WEST GERMANY AND USA UPON REQUEST.

TRANSISTORS - BIPOLARS - GERMANIUM AND SILICON

SMALL SIGNAL

POWER

DARLINGTONS - ALL SHAPES AND SIZES

VHF/UHF DEVICES - ALL SHAPES AND SIZES



FETS - POWER MOSFETS
UNIUNCTIONS



DIODES - GERMANIUM AND SILICON
RECTIFIERS AND BRIDGES
OPTO-ELECTRONIC DEVICES
LEDS OF ALL SHAPES AND SIZES



THYRISTORS AND TRIACS - ALL

SHAPES

SIZES

RATINGS



INTEGRATED CIRCUITS:
CONSUMER - DIGITAL/ANALOGUE
MICROPROCESSORS AND PERIPHERALS
IC SOCKETS



JAPANESE COMPONENTS - VAST RANGE OF DISCRETES AND CONSUMER IC'S.

MAIL ORDER CUSTOMERS: PLEASE SEND FOR OUR COMPREHENSIVE PRICE LIST, ENCLAVING £1.00 IN STAMPS, CHEQUE OR POSTAL ORDER. SYSTEM 'A' AMP, ALL SEMICONDUCTORS AVAILABLE. AMP AND PREAMP, £90. AMP ONLY, £75.

CATALOGUE SENT FREE OF CHARGE, WHEN REQUESTED ON OFFICIAL LETTERHEAD (WITHOUT REFUND), TO OEM'S, SCHOOLS, COLLEGES, UNIVERSITIES, GOVERNMENT INSTITUTIONS, COMPUTER FIRMS, ELECTRONIC REPAIR FIRMS AND DISTRIBUTORS.

SPECIAL DISCOUNTS AND PAYMENT TERMS ARE AVAILABLE TO ABOVE INSTITUTIONS.

PLEASE ENQUIRE FOR QUANTITY DISCOUNTS.

WE WELCOME TELEPHONE AND TELEX ENQUIRIES!

CMOS	4089	80p 74LS55	17p 74LS257	42p 280HCTC 600p	LINEAR IC'S	LM301	25p
4000	13p 4089	18p 74LS73	22p 74LS258	42p 280AS10 660p	AN-214P	200p	680p LM311
4001	13p 4085	48p 74LS74	22p 74LS259	58p 280AS10/1700p	AN-240P	150p	150p LM324
4002	13p 4098	50p 74LS76	26p 74LS266	28p 280AS10/2700p	AN-360	120p	120p LM339
4006	36p 4099	45p 74LS78	28p 74LS273	52p 280ADART 880p	AN-7110	140p	140p LM348
4007	13p 4501	30p 74LS83	43p 74LS279	40p	AN-7114	160p	160p LM360
4008	36p 4502	30p 74LS85	45p 74LS280 140p		AN-7120	140p	140p LM382
4009	20p 4503	32p 74LS86	30p 74LS293 30p	7400	AY3-1270	680p	680p LM387
4010	21p 4504	55p 74LS90	32p 74LS293 30p	7400	AY3-3600	300p	300p LM393 DIL
4011	13p 4505	200p 74LS91	76p 74LS365 37p	7401	AY3-8910	360p	360p LM723
4012	13p 4506	60p 74LS92	38p 74LS366 37p	7402	AY3-8912	400p	400p LM741 DIL
4013	19p 4507	33p 74LS93	30p 74LS367 36p	7403	AY3-3600	570p	570p LM741 MET
4014	36p 4510	37p 74LS95	47p 74LS368 36p	7404	CA270	400p	400p LM747
4015	18p 4511	40p 74LS96	60p 74LS374 55p	7406	CA3046	60p	60p LM748
4016	18p 4511	40p 74LS96	60p 74LS374 55p	7406	CA3048	190p	190p LM1458
4017	31p 4512	42p 74LS109 34p	74LS375 57p	7407	CA3080	280p	280p LM3900
4018	33p 4513	80p 74LS112 36p	74LS399 80p	7408	CA3086	55p	55p M-5151SBL
4019	28p 4515	75p 74LS113 32p	74LS870 72p	7409	CA3089E	150p	150p M-5151E
4020	35p 4516	40p 74LS114 38p		7413	CA3090AQ	300p	300p M-51517L
4021	36p 4517	120p 74LS122 40p		7414	CA3130E	80p	80p MB372
4022	36p 4517	120p 74LS122 40p		7417	CA3130S	100p	100p MB3730
4023	13p 4519	30p 74LS124 85p	2114 200p	7420	CA3140E	38p	38p MB3756
4024	26p 4520	38p 74LS125 36p	27256 400p	7421	CA3189E	250p	250p MC1327
4025	13p 4521	90p 74LS126 36p	2532 330p	7425	CA3240E	80p	80p MC1465
4026	60p 4522	50p 74LS132 40p	2716 200p	7430	HA-1156W	110p	110p MC555
4027	18p 4526	40p 74LS133 34p	2732 280p	7437	HA-1197	150p	150p SAS560
4028	29p 4527	44p 74LS136 34p	2784 240p	7447	HA-1308W	170p	170p SAS570
4029	35p 4528	40p 74LS138 35p	2784 240p	7447	HA-1309	60p	60p SA76110N
4030	17p 4529	75p 74LS139 35p	27128 260p	7450	HA-1342	22p	22p SA76115
4031	90p 4532	52p 74LS145 83p	4116, 75p	7451	HA-1368WR	180p	180p T2800
4032	54p 4531	80p 74LS147 120p	8116, 110p	7454	HA-1386	25p	25p TA-7120
4033	60p 4553	190p 74LS148 90p	8116, 180p	7470	HA-1377	220p	220p TA-7137P
4034	80p 4555	29p 74LS148 90p	6284-15 250p	7473	HA-1389	140p	140p TA-7146P
4035	45p 4556	38p 74LS153 40p	6502 300p	7474	HA-1392	230p	230p TA-7193P
4036	180p 4557	190p 74LS154 90p	6802 220p	7475	HA-1397	25p	25p TA-7201
4037	75p 4583	30p 74LS155 41p	6809 748p	7480	LA-1201	85p	85p TA-7203
4038	48p 4584	30p 74LS156 47p	6821 140p	7482	LA-1352	120p	120p TA-7204
4039	190p 4585	42p 74LS157 30p	6840 310p	7486	LA-1385	30p	30p TA-7205
4041	36p	74LS158 48p	6850 110p	7489	LA-3301	120p	120p TA-7210
4042	30p	74LS160 48p	8080A 400p	7490	LA-3350	120p	120p TA-7222AP
4043	36p	74LS161 50p	8080A 400p	7490	LA-4038	200p	200p TA-7300P
4044	38p	74LS162 48p	8155 390p	7493	LA-4031	140p	140p TA7509
4045	72p	74LS163 46p	8155 360p	7495	LA-4032	140p	140p TA8120S
4046	45p	74LS164 43p	8224 270p	7497	LA-4050	130p	130p TA8395
4047	45p	74LS164 43p	8224 270p	7497	LA-4051	180p	180p TA8396
4048	27p	74LS164 43p	8224 270p	7497	LA-4100	120p	120p TA8520
4049	18p	74LS168 92p	8228 270p	74111	LA-4101	100p	100p TA8530
4050	20p	74LS168 92p	8243 250p	74118	LA-4102SK	140p	140p TA8540
4051	36p	74LS170 80p	8250 850p	74119	LA-4112	250p	250p TA8560
4052	37p	74LS171 74p	8251 300p	74123	LA-4125	210p	210p TA8750
4053	37p	74LS171 74p	8251 300p	74123	LA-4140	70p	70p TA8800
4054	54p	74LS172 74p	8253 340p	74125	LA-4201	120p	120p TA8A10S
4055	52p	74LS173 74p	8256 1200p	74126	LA-4220	120p	120p TA8A20
4056	52p	74LS175 74p	8257 370p	74132	LA-4420	140p	140p TA8A30
4060	40p	74LS200 15p	8259 370p	74141	LA-4422	130p	130p TA8A50
4063	52p	74LS21 15p	8271 4400p	74145	LA-4430	70p	70p TA8A70
4066	20p	74LS22 15p	8271 4400p	74145	LA-4460	170p	170p TA8A90
4067	130p	74LS22 15p	8272 1300p	74155	LA-4461	180p	180p TA8A90
4068	13p	74LS26 16p	8279 650p	74157	LA-5112	120p	120p VAI110
4069	13p	74LS27 16p	8282 400p	74180		50p	50p Please add 50p and VAT at 15%. Govt. Colleges. etc. unless stated.
4070	13p	74LS28 16p	8283 400p	74184		50p	50p Quotations given for Large Quantities.
4071	13p	74LS30 16p	8284 400p	74187		50p	50p Same Day Despatch
4072	13p	74LS32 17p	8285 1000p	74173		50p	50p All brand-name Components
4073	13p	74LS33 17p	8285 1000p	74173		50p	50p All values are new and unused
4074	13p	74LS33 17p	8285 1000p	74173		50p	50p Ring for items not listed. We stock 3,000 items
4075	13p	74LS37 16p	8285 1000p	74173		50p	
4076	45p	74LS38 17p	8285 1000p	74173		50p	
4077	13p	74LS40 16p	8285 1000p	74173		50p	
4078	13p	74LS42 16p	8285 1000p	74173		50p	
4081	13p	74LS47 56p	8285 1000p	74173		50p	
4082	13p	74LS48 56p	8285 1000p	74173		50p	
4085	40p	74LS51 16p	8285 1000p	74173		50p	
4086	32p	74LS54 16p	8285 1000p	74173		50p	

SEMICONDUCTOR CIRCUITS

BY PETER FINCH

The Intel 8052AH-Basic microcomputer chip —a versatile, programmable controller

A new product launched by Intel reminded me of the first microprocessor based computer I owned over ten years ago. It was one of the very first micro computers produced, an 8080 with 4K of memory, in an early S100 crate with front panel, data and address indicators and switches. When one switched on, a simple boot program had to be loaded into the machine using the front panel switches—a tedious task. The boot program allowed one to load a program from paper tape via an attached ASR33 teletype terminal. One of the first pieces of software I acquired for this system was a small 3K Basic interpreter. It was a very limited version of Basic, integer only, had no functions and took 30 minutes to load the paper tape. Having loaded the Basic one had less than 1K of RAM to use for Basic programs—a very limited system.

Intel have now put a whole computer system with a full 8K Basic interpreter onto a single chip. This new chip is the ideal solution for anyone wishing to put a microprocessor into a project but who for a variety of reasons may be unwilling to write the controlling program in machine code. Basic programs are much easier and quicker to write and also more easily modifiable.

The 8052AH-Basic chip contains an 8Kbyte full featured Basic interpreter on a ROM which is part of the processor chip. The version of Basic employed differs slightly from the fairly standard Microsoft Basic found on many home computers. The Intel Basic is designed primarily for running real time control applications and there are therefore many new commands which are processor specific I/O handling commands. Although the 8052AH-Basic does support full floating point arithmetic it is not designed as a number crunching processor.

I think this chip would make the ideal basis for a simple single board computer which could be used as the basis of a wide range of projects. It could amongst many different applications be the processor controlling a

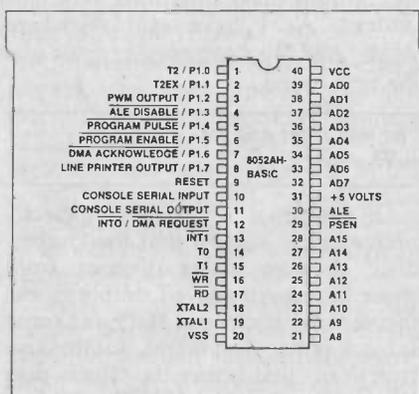


Fig. 1. Pin-out diagram

small mobile robot, it could run a household control system, or it could be the basis of a remote data acquisition system. The serial communications links on the chip could be connected to a home micro and used to transfer programs and data. Programs could be written and debugged on the home micro first before being either down loaded into RAM or committed to EPROM.

SYSTEM HARDWARE DESIGN

The 8052AH-Basic is an enhanced version of the 8051 and owes its origin to the ever popular 8080 microprocessor with which it shares a common instruction set. Inspection of the internal architecture of the 8052AH-Basic shows that besides having 8Kbytes of ROM in which Basic resides, and 256 bytes of scratchpad RAM, the chip also includes two 16-bit counter/timers, a serial communications port and a parallel I/O port. A pin out diagram and a basic description of the pin functions is shown in Fig. 1 and Table 1 respectively.

SYSTEM SOFTWARE

The most important feature of the 8052AH-Basic is its resident software. This is, after all, a 'software on silicon' product. The resident Basic interpreter—Basic-52—is specifically designed

to address the needs of process control, measurement and instrumentation applications. The rationale for using a Basic interpreter is simply that Basic programming is well understood and much simpler and easier to write and understand than comparable assembly language programs.

All the standard Basic commands and functions are included in Basic-52 such as full floating point arithmetic and transcendental operations. There are in addition a considerable number of unique features which allow the user to perform tasks which normally require assembly language routines. These include bitwise logical operators such as AND, OR, and EXCLUSIVE-OR as well as hexadecimal arithmetic and built in radix conversion. There are also a range of machine specific statements which are designed for real time control applications. These statements can initialise counters and timers, control a real time clock, handle interrupts, examine and modify memory locations as well as performing all serial and parallel I/O functions. These special machine specific statements allow every feature of the 8052 to be utilised directly from a Basic program with no need to resort to assembly code. A complete list of the commands and statements of Basic-52 are shown in Table 2.

The serial channels are very important on chip features since they allow the communication of programs and data between the chip and an external terminal. On power up the Basic-52 sets its baud rate to match the baud rate of the attached terminal. Timer2 is used as a baud rate generator. In addition to the terminal serial input and output lines there is also a serial printer port. This port is output only and can be software set to any required baud rate, it is a useful additional feature of the 8052 chip.

All direct I/O operations are performed through the eight lines of Port 1 on the 8052AH-Basic chip. The eight lines of this port can only operate in the output mode under Basic-52 since there are no statements to input any

Table 1. 8052AH pin designation and brief description

<p>VSS Circuit ground potential.</p> <p>VCC Circuit supply voltage. 5 volts \pm 10% relative to VSS.</p> <p>AD0-AD7 The multiplexed low-order address and data bus used during accesses to external memory. External pullup devices (\sim10K Ω) are required on these pins if the MCS BASIC-52 EPROM/E²PROM programming feature is used.</p> <p>A8-A15 The high order address bus used during accesses to external memory.</p> <p>PORT 1 A general purpose quasi-bidirectional 8-bit input/output port. The individual pins on PORT 1 all have alternate functions which may or may not be implemented by the user. The alternate functions are as follows:</p> <p>PORT 1.0 (T2) Can be used as the trigger input to TIMER/COUNTER 2. A one (1) must be written to this port pin output latch in order for this function to operate. Details of the T2 trigger function are covered in the Microcontrollers Handbook. Order Number 210918-002.</p> <p>PORT 1.1 (T2EX) Can be used as the external input to TIMER/COUNTER 2. A one (1) must be written to this port pin output latch in order for this function to operate. Details of the T2 trigger function are covered in the Microcontroller Users Manual.</p> <p>PORT 1.2 (PWM OUTPUT) This pin is used as the PWM output port when the PWM statement is executed. PWM stands for Pulse Width Modulation and is used to generate pulses of varying duty cycle and frequency.</p> <p>PORT 1.5 (PROGRAMMING ENABLE) When the EPROM/E²PROM programming feature is implemented, this pin is used to enable the EPROM programming voltage. This pin remains active (logically low (0)) during the entire EPROM programming process. On E²PROM devices that do not require any special programming voltage, this pin is not used.</p>	<div style="border: 1px solid black; padding: 5px; margin-bottom: 10px;"> <p>8052AH-BASIC is an 8052AH device, however, MCS BASIC-52 assumes a particular hardware configuration. The following pin description outlines the pin functions defined by MCS BASIC-52.</p> </div> <p>PORT 1.6 (DMA ACKNOWLEDGE) When the DMA feature is implemented as described in the MCS[®] BASIC-52 users manual, this pin functions as an active low DMA ACKNOWLEDGE output.</p> <p>PORT 1.7 (LINE PRINTER OUTPUT) This pin functions as a serial output port when the LIST # or PRINT # command and/or statement is used. This enables the user to make a "hard copy" of a program or to print out results of a calculation.</p> <p>RESET A high (2.5 volts) on this pin for two machine cycles while the oscillator is running resets the device. An external pulldown resistor (\sim8.2K) from RESET to VSS permits power-on reset when a capacitor (\sim10uf) is connected from this pin to VCC.</p> <p>ALE ALE (address latch enable) is an output pin that is used to latch the low order address byte during Read, Write, or program fetch operations to external memory.</p> <p>PSEN This pin (Program Store ENable) is a control signal that is used to enable external program memory. In MCS[®] BASIC-52, this pin will always remain inactive (logically high (1)) unless the user is running an assembly language program in external memory.</p> <p>XTAL1 Input to the inverting amplifier that forms the oscillator.</p> <p>XTAL2 Output of the inverting amplifier that forms the oscillator, and input to the internal clock generator. Receives the external oscillator signal when an external oscillator is used.</p> <p>PORT 1.3 (ALE DISABLE) This pin is used to disable the ALE signal to the external address latch when the EPROM/E²PROM programming feature is used. In a system, this pin is logically anded with ALE.</p>	<p>PORT 1.4 (PROGRAMMING PULSE) When the EPROM/E²PROM programming feature is used, this pin provides the proper programming pulse width to program EPROM and INTEL[®] EPROM[®] devices. MCS BASIC-52 actually calculates the proper programming pulse width from the system crystal value (XTAL) to assure the proper timing of this pulse. When used to program E²PROM devices, the length of this pulse is not critical. This pin is active in the logical zero (0) state.</p> <p>RD A control signal that is used to enable READ operations to external data memory. This pin is active low (0).</p> <p>WR A control signal that is used to enable WRITE operations to external data memory. This pin is active low (0).</p> <p>T1 This pin can be programmed to be an external input to TIMER/COUNTER 1.</p> <p>T0 This pin can be programmed to be an external input to TIMER/COUNTER 0.</p> <p>INT1 This pin is the external interrupt 1 pin. It is active low and interrupts on this pin may be handled in either BASIC or in assembly language.</p> <p>INT0/DMA REQUEST This is the external interrupt 0 pin. It is active low and may be optionally programmed to function as a DMA request input pin. The DMA REQUEST pin is used by E²PROM devices during programming.</p> <p>CONSOLE SERIAL OUTPUT This is the serial output pin to the console device. Standard ASCII codes are used as well as a standard asynchronous frame.</p> <p>CONSOLE SERIAL INPUT This is the serial input pin that receives data from the console device. Standard ASCII codes are assumed to be the input and the data is assumed to be transmitted using a standard asynchronous frame.</p>
--	---	--

data from this port. Any of the logical operations may be performed upon this byte wide output port in order to manipulate individual lines. However, each of the individual pins on this output port have alternate functions which may or may not be implemented by the user, a list of these alternate functions is shown in Table 1.

A minimal amount of extra hardware is required in order to support Basic-52. A very simple system consists of the 8052AH-Basic, 1Kbytes of external memory, a latch to demultiplex the address and data lines, and the appropriate serial port drivers. As an interesting extra feature Basic-52 can program an EPROM or EEPROM connected to the address and data bus lines using a program pulse line from the 8052. This program line is derived from one of the user port lines and with the addition of a transistor, a gate and a couple of passive components to give the required voltage level is used by Basic-52 to generate the programming

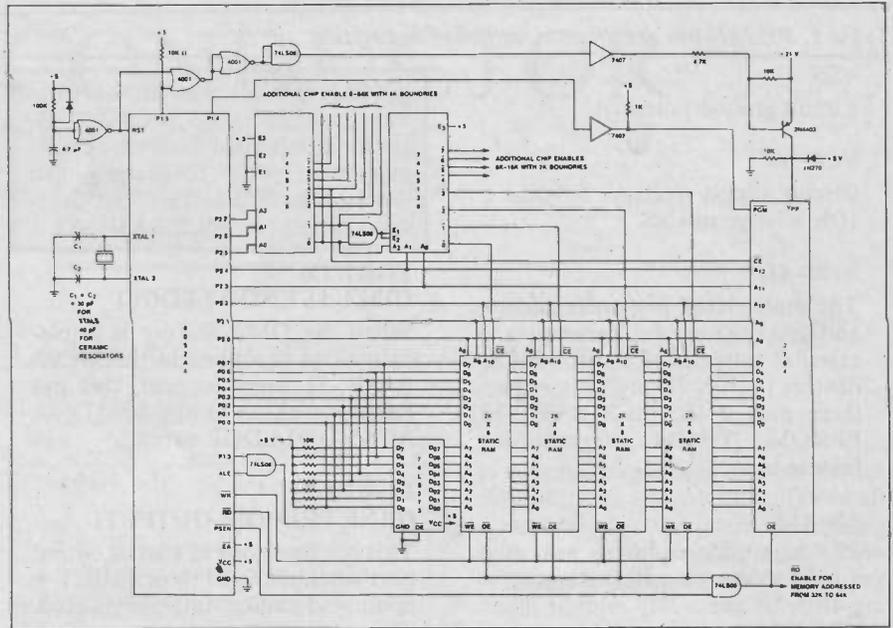


Fig. 2. Minimal system circuit diagram

Table 2. MCS[®] Basic-52 software feature set

COMMANDS	STATEMENTS	OPERATORS
RUN	BAUD	ADD (+)
LIST	CALL	DIVIDE (/)
LIST#	CLEAR	EXPONENTIATION (**)
NEW	CLEAR#	MULTIPLY (*)
NULL	CLOCK0	SUBTRACT (-)
RAM	CLOCK1	LOGICAL AND (.AND.)
ROM	DATA	LOGICAL OR (.OR.)
XFER	READ	LOGICAL X-OR (.XOR.)
PROG	RESTORE	LOGICAL NOT
PROG1	DIM	ABS ()
PROG2	DO-WHILE	INT ()
FPROG	DO-UNTIL	SGN ()
FPROG1	END	SQR ()
FPROG2	FOR-TO-STEP	RND
	NEXT	LOG ()
	GOSUB	EXP ()
	RETURN	SIN ()
	GOTO	COS ()
	ON-GOTO	TAN ()
	ON-GOSUB	ATN ()
		=, >, <, =, <>
	IF-THEN-ELSE	ASC ()
	INPUT	CHR ()
	LET	CBY ()
	ONERR	DBY ()
	ONEXT1	XBY ()
	ONTIME	GET
	PRINT	IE
	PRINT#	IP
	PH0.	PORT1
	PH0.#	PCON
	PH1.	RCAP2
	PH1.#	T2CON
	PUSH	TCON
	POP	TMOD
	PWM	TIME
	REM	TIMER0
	RET1	TIMER1
	STOP	TIMER2
	STRING	TIME
	UI0	XTAL
	UI1	MTOP
	UO0	LEN
	UO1	FREE
		PI

pulses. A circuit diagram for a minimal system is shown in Fig. 2.

USING THE 8052AH-BASIC

The concept of 'software on silicon' devices has been around for several years with devices like the Z8. But these were usually in software terms fairly limited devices owing to the limited amount of ROM available on chip. The 8052 with 8Kbytes of on chip ROM has broken this limitation and I am confidently expecting to see other versions of this chip become available supporting other languages such as Forth. Having the system control software already on the chip makes this device very easy to use, and because the applications software is written in Basic the time taken to implement a system using this device can be minimal.

I think that the great advantage of this processor chip to the amateur is in developing ideas which require a microprocessor without having to invest large amounts of time in software development. In this way projects can be tried out and the hardware developed, later, when the project is working. The software could be rewritten in machine code on any one of the single chip microcomputers now available. This chip is expensive (in one off quantities £50 each) but considering its power and versatility this is not a lot to pay for what is basically a small computer especially if it is used in prototyping applications.

For prototyping purposes the chip can be incorporated into a simple system on a single card incorporating either 8 or 16Kbytes of RAM memory and an EPROM socket with program-

ming circuitry plus the line drivers required to implement an RS232 communications link. A simple system like this would easily fit onto a single Eurocard and could be attached via the address and data bus to the hardware system under development. The serial I/O lines could be used to download programs and data from a home micro like the BBC. When the software was fully debugged it could be committed to EPROM using the inherent ability of the 8052AH-Basic to programme EPROMs.

CONCLUSION

In conclusion I think that this chip should find a considerable number of applications from everyone wishing to use microprocessors to control a project. In the past people have tended to use a small cheap micro like the ZX81 as the controller, but this always had the limitation of confining the user to the inherent limitations of the computer. By using a chip like the 8052AH-Basic the user is freed from many if not all of these limitations. I intend to use

*The 8052AH-Basic is available from:
Rapid Recall Ltd, Rapid House,
Denmark St, High Wycombe, Bucks. Tel.
0494 26271.*

this chip in future projects and I am certain that it will become a very powerful component in the armoury of many electronics and computer system designers as a very cost and time effective way of developing micro-processor based projects. **PE**

CROFTON PM101

ONLY £40.00
Inclusive VAT and carriage £49.45 total.



This 9 inch metal cased, monochrome monitor offers you the chance to obtain a high quality product at a budget price!

THE VIDEO SPECIALISTS

Crofton

Be sure to ask for our various catalogues. We have a full range of products including:

- 1—Discrete listening devices
- 2—Plugs/sockets/connectors/leads
- 3—Television accessories
- 4—Security products
- 5—Computer products
- 6—NEC cased and uncased monitors

THE NOVEX 1414

ONLY £100.00
Inclusive VAT and carriage £128.80 total.



This superb metal cased 14 inch RGB/COMPOSITE COMPUTER COLOUR MONITOR is unbelievable value at this price!

SPECIAL SUMMER OFFER

IF YOU WOULD LIKE ALL OUR CATALOGUES—PLEASE SEND A 38p 9 x 12 S.A.E.

SPECIAL OFFERS

MONITOR KITS Brand new professional 12 inch. P31 anti-glare panel tube with T.T.L. 12v pcb. Easy to convert to composite. **ONLY £30.** ZX81 Full sized keyboard in metal case **£13.80.** COMPUTER DESKS **£20.**

PHILIPS BM7502	£87.97
PHILIPS BM7522	£90.27
PHILIPS CT2007	£235.57

All inclusive price

CROFTON ELECTRONICS

35 GROSVENOR ROAD, TWICKENHAM, MIDDLESEX TW1 4AD
SALES & SERVICE: P.O. BOX 6, KINGTON HR5 3SX. ☎ LYONSHALL (05448) 557

CCTV camera at attractive prices

ALL OUR PRICES INCLUDE VAT, CARRIAGE & INSURANCE AND CAN ONLY BE HELD AS LONG AS STOCKS LAST!

PHONE YOUR ORDER NOW!

MOST MAJOR CREDIT CARDS ACCEPTED
OFFICIAL ORDERS FROM APPROVED INDUSTRIAL OR EDUCATIONAL ESTABLISHMENTS WELCOME.

Delivery within 28 days.

★ SECURITY MODULES ★

A COMPLETE SECURITY SYSTEM FOR ONLY £39.95 + V.A.T.

contains:
Control Unit CA 1250
Enclosure & mechanical fixings HW 1250
Key Switch & 2 Keys KS 3901
L.E.D.'s LED 1
5W Horn Speaker HS 588
4 high quality surface mounting Magnetic Switches MS 1025

With only a few hours of your time it is possible to assemble and install an effective security system to protect your family and property, at the amazingly low cost of £39.95 + V.A.T. No compromises have been made and no corners have been cut. The outstanding value results from volume production and direct supply. Assembly is straightforward with the detailed instructions provided. When installed you can enjoy the peace of mind that results from a secure home. Should you wish to increase the level of security, the system may be extended at any time with additional magnetic switches, pressure pads or ultrasonic sensors. Don't wait until it's too late—order today.

Order Code: CS 1370

EXTENDED SYSTEM CS 1480 Price £62.50 + V.A.T.

This system contains, in addition to the CS 1370, an ultrasonic detector type US 5063 + its enclosure, an additional horn speaker and a further 2 magnetic switches. This system represents outstanding value for money for the high level of security provided.

Order Code: CS 1480


DIGITAL ULTRASONIC DETECTOR US 5063



Only £13.95 + V.A.T.

- * Adjustable range up to 25ft.
- * 3 levels of discrimination against false alarm.
- * Crystal controlled.
- * Low-consumption 12V operation.
- * Built-in delays & fixed alarm time.

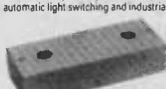An advanced ultrasonic movement detector which employs digital circuit techniques to provide a superior performance for security, automatic light switching and industrial applications.



Suitable metal enclosure
£2.95 + V.A.T.

ALARM CONTROL UNIT CA 1250



£19.95 + V.A.T.

The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing an installation or simply controlling a single magnetic switch on the front door.

- * Built-in electronic siren drives 2 loud speakers
- * Provides exit and entrance delays together with fixed alarm time
- * Battery back-up with trickle charge facility
- * Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
- * Anti-tamper and panic facility
- * Stabilised output voltage
- * 2 operating modes full alarm/anti tamper and panic facility
- * Screw connections for ease of installation
- * Separate relay contacts for external loads
- * Test loop facility

Suitable enclosure for CA 1250 as shown in Complete Security System - HW 1250
Price £9.50 + V.A.T.

INFRA-RED SYSTEM IR 1470



£25.61 + V.A.T.

The IR 1470 provides an invisible beam of light which, when interrupted energises a built-in relay in order to operate external switches or equipment. Ideal for use in security, photographic, or industrial applications.

Suitable power supply and timed switching unit for use with IR 1470, etc.
Price £13.95 + V.A.T.

RISCOMP LIMITED

Dept PE17
51 Poppy Road
Princes Risborough
Bucks. HP17 9DB
Princes Risborough
(084 44) 6326

BBC MICRO FORUM

BY RAY STUART

Memory magic and minor modifications

IN THE April issue of BBC Micro Forum we discussed the 1MHz bus and indicated that an extra 32K (or 64K) bytes of RAM can be added to the system. In this month's BBC Micro Forum we will look at the interface circuitry required to implement this extra RAM. In addition we will discuss the problem of interfacing devices from outside the 65XX range of chips.

The 1MHz bus should be buffered so that bus lines are only loaded by one LSTTL load, and terminated with 2K2 resistors as discussed in the April issue. Fig. 1 shows one method of buffering the 1MHz bus. The uni-directional lines of the address and control buses are buffered by 74LS244s and the bi-directional data bus by a 74LS245. The buffered outputs are identified by prefixing them with 'B', thus the buffered A1 line is called BA1. The BR/W line is used to control the direction of data via the 74LS245.

EXTENDED PAGE MEMORY CIRCUIT

The full circuit diagram for the extended page memory is shown in Fig. 2. The 1MHz bus lines are terminated by 2K2 resistors as described above, however, the buffering arrangements are slightly different. The bus lines are buffered by IC1 to IC4. The data and address lines are each buffered by a 74LS245. The 5 control lines (RST, NPFC, NPFD, 1MHzE and R/W) are buffered by two 74LS04 i.c.s. The inverted R/W line, available on IC1 pin 6 is used to indicate the data flow direction. This signal is fed to pin 1, the direction control input of IC3 the data bus buffer. As the address bus only operates in one direction, its direction control input is tied to Vcc.

Although this buffer circuit is different to that shown in Fig. 1, its function is the same. In this case the control lines are buffered by two 74LS04s as the following circuit requires both the normal and inverted forms of the reset line, RST, and the R/W line. Both NPFC and NPFD, the page select lines are 'cleaned' by ICs 5 & 6 both 74LS02s as described in April's BBC Micro Forum.

It will be noted that the NPFC line is inverted before being used as part of the decoding circuit for address

&FCFF, the paging register. This decoding is performed by IC7, a 13-input NAND gate whose output is used to activate an 8-bit latch type 74LS273. This latch therefore holds the value present on the data bus when data is written to address &FCFF. Thus the output of the 74LS273 provides the upper eight address lines necessary to address up to 64K bytes of additional RAM.

The upper three address lines (A15, A14 and A13), are decoded into eight chip select lines by IC9, a 74LS138, together with the BNPFD line. Thus the chip select lines are only valid, and hence the RAMs enabled, when an address between &FD00 and &FDFE is accessed. In the April BBC Micro Forum it was stated that Acorn have recommended that only the upper half of the possible 64K bytes of RAM

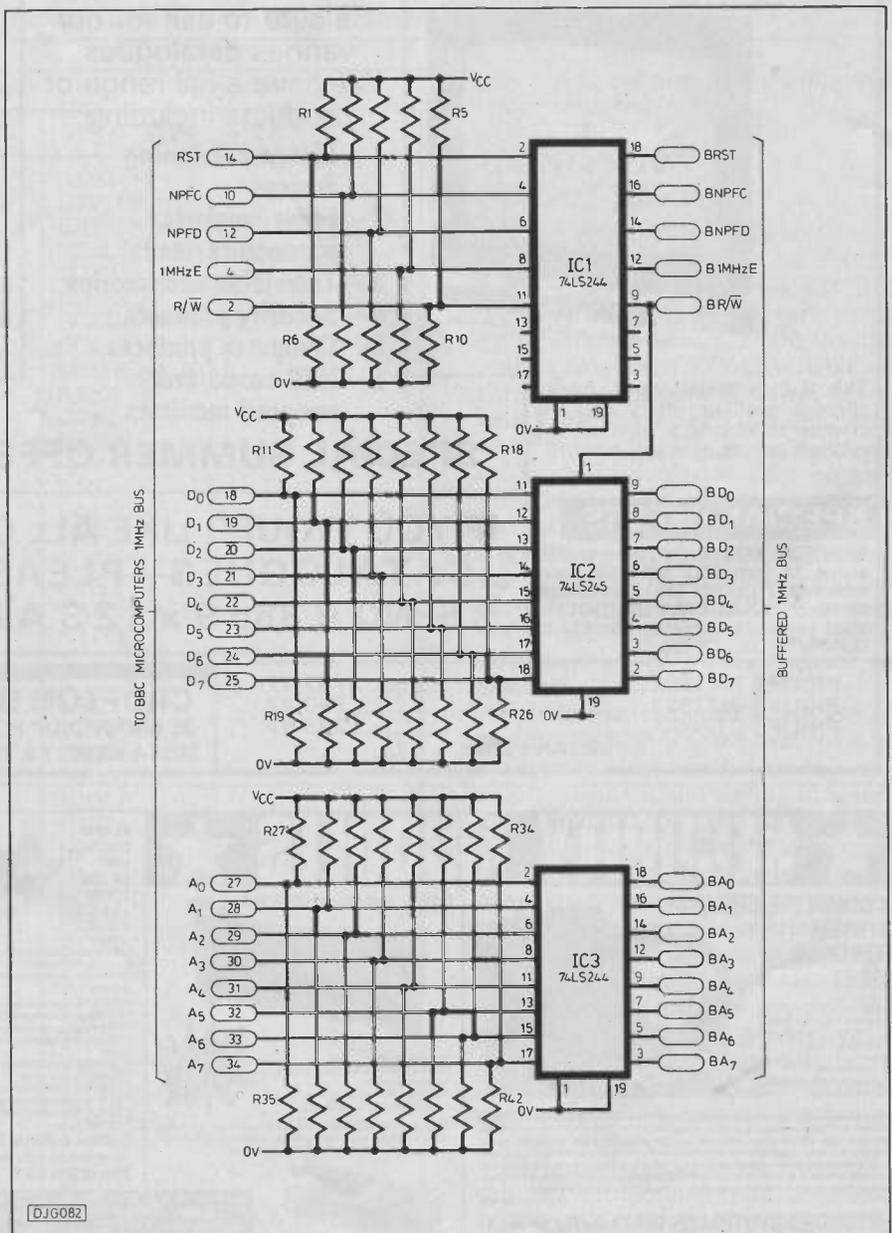


Fig. 1. Bus buffers

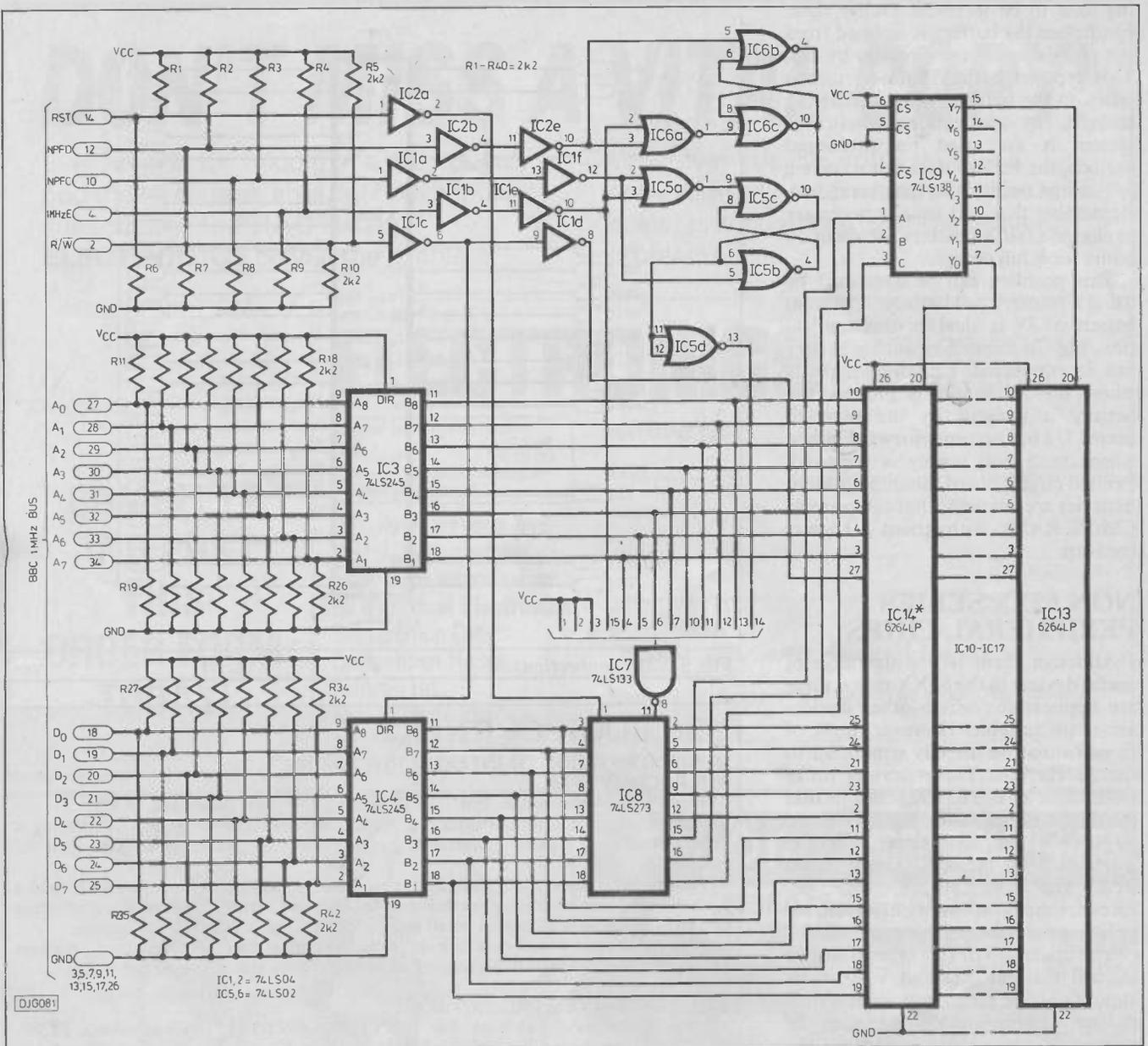


Fig. 2. Extended page memory

should be allocated to user applications. This block of RAM consists of IC10 to IC13 (all 6264LPs). However, if the RAM circuit is not to be used with other 1MHz peripherals, then the full 64K bytes can be used. In this case IC14 to IC17 provide the additional 32K byte of RAM.

Acorn also specify that the paging register, IC8 in this circuit, should be reset to &00 whenever the BBC micro-computer is switched on or a break command is issued. The RST line from the 1MHz bus is therefore inverted and fed to IC8 pin 1, the chip's reset input.

Addressing a specific memory location within the extended page memory consists of two stages. Firstly the paging register has to be set to the upper byte of the address. This is achieved by writing this value to address &FCFF. When this has been set, up to 256 bytes can be accessed by reading or writing to NPDF (&FD00-&FDFF). The soft-

ware procedures required for this were described in the April BBC Micro Forum.

BATTERY BACK-UP

The RAMs used in this circuit are low power devices that only require about 50 microamps per chip in order to retain their data. Thus it is possible to add battery back-up to the RAMs allowing data to be stored whilst the BBC system is switched off. There are two possible methods of providing battery back-up, rechargeable NiCad battery or primary lithium battery.

A 3-6V NiCad battery can be added by means of the circuit shown in Fig. 3a. When the circuit is powered by a 5V supply, diode D2 is reversed biased and therefore no current flows from the battery to the RAMs. However, current determined by R1 flows into the battery thereby charging it. If the

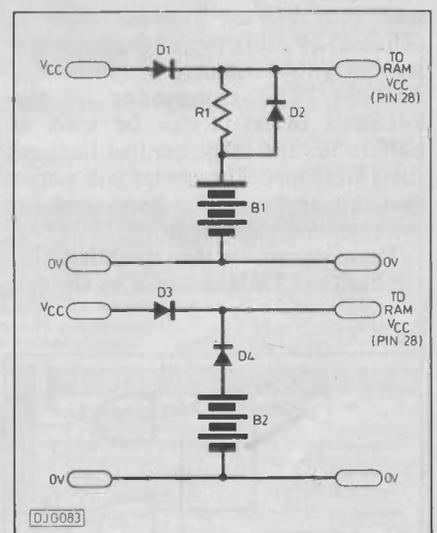


Fig. 3. Battery back-up

5V supply is removed the battery is connected to the RAMs thereby allow-

ing data to be retained. Under these conditions the battery is isolated from the remainder of the circuitry by D1. This type of battery back-up circuit relies on the battery being sufficiently charged. In applications where the system is not used for prolonged periods, the battery does not receive a full charge resulting in data being lost. Remember that it is usually necessary to charge a NiCad battery for about 14 hours for a full charge.

This problem can be overcome by using a primary cell battery. A lithium battery of 3V is ideal for this application. Fig. 3b shows how such a battery can be connected. Under normal use where the 5V supply is present, the battery is isolated by the reversed biased D4 but becomes forward biased when the 5 volt supply is removed. Printed circuit board mounted lithium batteries are available that can provide CMOS RAMs with about 10 years back-up.

NON 65XX SERIES PERIPHERAL CHIPS

Although there is a wide range of useful devices in the 65XX range, there are applications where other devices are more suitable. However, most of these cannot be directly connected to the 1MHz bus. These devices differ from those of the 65XX series in that they require separate read (RD) and write (WR) inputs as opposed to the single R/W of the 65XX range. Intel 82XX and Zilog Z80-XXX series devices are the most commonly available peripheral devices of this type.

The operation of this type of device is such that the RD and WR inputs should only be taken low when a read or write operation is undertaken. In order to achieve these conditions the circuit shown in Fig. 4 is used. The R/W line is required in both the normal and inverted versions. This is achieved by using two of the six inverters (1a & 1b) contained within a single 74LS04. The remainder of the 74LS04's inverters can be used as buffers for the other control lines on the 1MHz bus. The reader will notice that this approach has been used for the extended page memory.

These signals are then qualified with the buffered 1MHzE signal by the two

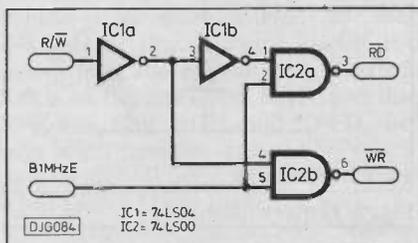


Fig. 4. \bar{R} and \bar{W} conditioning

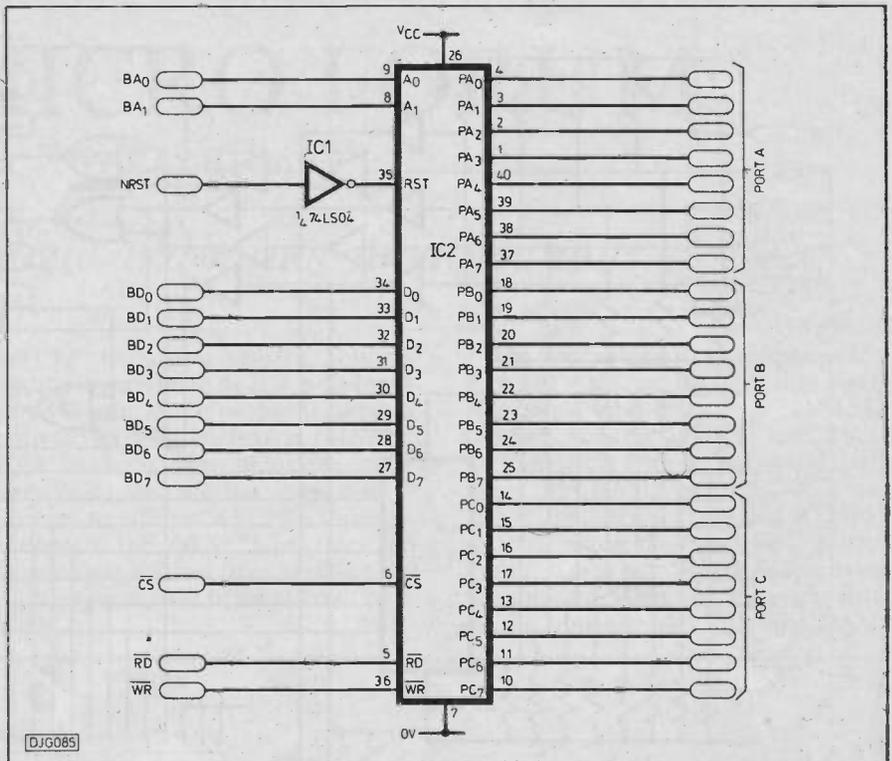


Fig. 5. 8255 connections

BBC BOOK CORNER

BEGINNERS GUIDE TO INTERFACING THE BBC MICROCOMPUTER

Martin Phillips—Macmillan. ISBN 0-333-38652-3 170 pages paperback. £6.95.

As the title suggests, this book is for beginners. Some prior knowledge of programming is required but only a basic understanding of physics is needed to get to grips with the electronics.

The first few chapters introduce simple electronic principles and familiarise the reader with the BBC user and digital ports. Following chapters deal with various home interface projects, each one described in detail and backed by substantial software listings.

A useful appendix section is included which contains three fully explained programs for: calculating values, interpreting resistor colour codes and designing the user port.

THE TRANSDUCER PROJECT BOOK

Michael J. Andrews—Tab Books Inc. ISBN 0-8306-1992-5 130 pages paperback. £7.95

The Transducer Project Book is suited to the beginner. There is a minimal amount of electronics involved with each project but the principles which are used, are fully explained at each stage.

Transducers, nowadays, are often associated with computers. Most of the projects in this book can be built and used without the need for computer interfacing or indeed a computer. Only a small section is devoted to computer applications.

NAND gates (2a & 2b). The outputs from these two gates are the RD and WR required by the 82XX and Z80-XXX series of chips.

A typical, and useful, device from this range is the Intel 8255. This device provides three ports designated Ports A, B and C. Each port provides eight bits and can be programmed as input or output. In addition Port C can be configured to provide handshaking facilities. Fig. 5 indicates how this device can be connected to the 1MHz bus. The internals of the 8255 can be considered as four consecutive memory locations, one of which sets the operating mode of the device. If we assume that these locations are XX00 to XX03 inclusive, then their functions are as shown in Table 1.

Table 1. 8255 Register functions

Address	Function
XX00	CONTROL REGISTER
XX01	PORT A REGISTER
XX02	PORT B REGISTER
XX03	PORT C REGISTER

In order to configure the device a control word is written into the control register, a method similar to that used by the 6522 VIA inside the BBC microcomputer. Should one wish to further investigate this, and other 80XX or Z80-XXX series devices one should consult the relevant data sheets. This concludes the BBC Micro Forum series—watch out for *Micro Forum*. [P]

DON'T MISS A VITAL COPY!

Ever been in the middle of a project only to find the next issue sold out? An annual subscription to **PRACTICAL ELECTRONICS** solves the problem.

Wherever you live you'll receive a copy regularly each month. It's the quick, practical way to solve delivery problems.

SUBSCRIPTION RATES

U.K. £14.00
Overseas £16.00

**COMPLETE
AND POST
THIS
ORDER FORM
TODAY!**

PRACTICAL

ELECTRONICS

SUBSCRIPTION ORDER FORM

Annual Subscription Rates
U.K. £14.00
Overseas £16.00
Students: Deduct £1 and quote Student Number

POST COPIES TO

NAME _____

ADDRESS _____

POST CODE _____

I enclose my cheque/PO payable to Intrapress for £.....

Please Note: Subscriptions cannot be ordered by phone

Signature _____

Complete this form and post it, with payment or credit card authorisation to: **Practical Electronics** Subscription Dept. Competition House, Farndon Rd., Market Harborough, Leicester LE16 9NR.



Amateur Radio & Electronics Hobby Fair

To be held at Wembley Conference Centre, Saturday 5th & Sunday 6th July 1986

- ★ The first Two Day Fair to be held in the South of England. A major new event in the Amateur Radio Calender.
- ★ Over 200 retail & manufacturers stands – plus lots more.
- ★ See future publications for more details.

The Organisers are: Amateur Radio Promotions, Woodthorpe House, Claggate Lane, Birmingham B32 3BU – Telephone: 021-421-5516.

SAXON MOSFET AMPLIFIERS

UNBEATABLE PRICES!!!



SLAVE MODEL

AP 100 100W RMS £69
AP 200 200W RMS £89



2 INPUT GENERAL PURPOSE MODEL

AP 100S £79
AP 200S £99



P.A. MODEL

- ★ 6 INPUTS
- ★ 3 CHANNELS
- ★ ECHO IN/OUT

- ★ TREBLE/BASS EACH CHANNEL
- ★ INDIVIDUAL VOLUMES
- ★ MASTER PRESENCE

AP 100M £99
AP 200M £119

Write or phone for a **FREE BROCHURE** on these incredible amplifiers

P.E. HYPERCHASER


£84.95



4 CHANNEL PSEUDO INTELLIGENT LIGHT UNIT

- ★ 16 Programmes
- ★ Manual/Auto Programme
- ★ Individual Dimming
- ★ Manual Flash Buttons
- ★ Strobe Outputs
- ★ Sound To Light

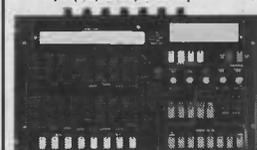Not just a light unit but a sophisticated & comprehensive effects unit. A full kit of parts including P.C.B., Facia, Case, etc. Reprint of article on request.



P.E. STAR DESK

£209

8 + 4 CHANNEL LIGHT MIXING DESK

- ★ 8 Channel Twin Preset Mixer
- ★ 4 Independent Channels
- ★ 8 Programmes
- ★ 1KW Output/Channel (can be boosted to 2KW/Ch)
- ★ Timed Crossfade
- ★ Strobe Outputs
- ★ 4/8 Channel Sequences
- ★ Manual Flash Buttons
- ★ Soft/Hard Sequence

A truly magnificent unit ideal for clubs, groups, drama, etc. A full kit of parts inc. PCB, Facia, Case, etc. Reprint of article on request.



CROYDON DISCO CENTRE

327 Whitehorse Road, Croydon, Surrey CR0 2HS
(01) 684 8007 9am-5pm. Mon-Sat. (Closed Wed.)



All prices include VAT and Post & Packing. Please allow 14 days for delivery

P.C. BOARDS

Printed circuit boards for certain PE constructional projects are now available from the PE PCB Service, see list. They are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to: **PE PCB Service, Practical Electronics, Practical Electronics Magazines, 16 Garway Road, London, W2 4NH.** Cheques should be crossed and made payable to Practical Electronics Magazines.

Please note that when ordering it is important to give project title, order code and the quantity. Please print name and address in Block Capitals. Do not send any other correspondence with your order.

Readers are advised to check with prices appearing in the current issue before ordering.

NOTE: Please allow 28 days for delivery. We can only supply boards listed here.

TELEPHONE ORDERS (24-HOUR SERVICE)

You can now order your printed circuit boards by telephone, quoting your Access credit number. The number to ring is: 0268 710722. In stock items will be despatched within 24 hours of receipt of order. If you ring out of office hours, please state your order, credit card number and address clearly, as the order is recorded on an answering machine.

PROJECT TITLE	ORDER CODE	COST
MAR '84 Spectrum Autosave	430-01	£2.90
MAY '84 Sustain Unit	405-02	£2.90
Audio Signal Generator	405-03	£4.28
"	405-04	£2.90
JUNE '84 Cross Hatch Generator	406-01	£3.52
JULY '84 Simple Logic Analyser I	407-01	£7.73
EPROM Duplicator	407-02	£3.74
Alarm System	407-03	£3.19
Oscilloscope Calibrator	407-04	£4.23
AUG '84 Comm. 64 RS232C Interface	408-01	£3.02
Field Measurement	408-02	£3.19
"	408-03	£2.90
Simple Logic Analyser II	408-05	£2.93
SEPT '84 Parallel to Serial Converter	409-01	£2.92
Through the Mains Controller	409-02	£2.90
"	409-03	£2.90
OCT '84 Logic Probe	410-01	£2.90
NOV '84 Computer DFM Adaptor	411-01	£2.90
DEC '84 Ni-Cad Charger	412-01	£2.90
JAN '85 Outrider Car Computer (Set of 2)	501-01	£9.10
FEB '85 Modular Audio Power System		
Pt-1: Power Amp Board	502-01	£4.19
Spectrum DAC/ADC Board	502-02	£3.69
MAR '85 Modular Audio Power System		
Pt-2: Pre-Amp/Line Driver	503-01	£5.00
Main Board	503-02	£5.12
Heart Beat Monitor—Main Circuit Board	503-03	£8.90
—Detector	503-04	£6.62
Low Cost Speech Synthesiser	503-05	£3.42

Power Control Interface	504-01	£3.36	
Disc Drive PSU	504-02	£6.54	
Modular Audio Power System	APRIL '85		
Pt-3: Test Signal Source	504-09	£4.20	
Power Supply	504-10	£4.17	
Amstrad Synthesiser Interface	505-01	£4.23	
Rugby Clock Pt-2	504-03	£24.22	
"	504-04	£9.06	
"	MAY '85		
"	504-05	£5.12	
"	504-06	£9.54	
"	504-07	£5.40	
"	504-08	£10.24	
CBM64 Music Keyboard			
Keyboard	JUNE '85	506-02	£4.55
Main PCB		506-03	£3.50
MTX 8 Channel A to D	JULY '85	507-01	£3.92
Voltmeter Memory Adaptor		506-01	£3.28
AUGUST '85 Envelope Shaper		508-01	£3.73
SEPT '85 Car Boot Alarm		509-01	£2.90
RS232 To Centronics Converter		509-03	£4.95
OCT '85 Touch Control PSU		001	£3.17
Exp. with Robots (double-sided)		004	£16.91
Modulated Syndrum		005	£3.80
CBM User Port Expander		006	£3.93
Model Railway Track Control		010	£5.44
*Bytebox: ROM Board (double-sided)		002	£12.75
ZIF Socket		003	£2.90
RAM Board	NOV '85	007	£4.95
Battery Backed RAM		008	£3.74
EPROM Board		009	£2.93
*Special Price—Complete set of 5 boards		00A	£23.00
DEC '85 Model Railway Rec Board—A		016	£3.90
Track Control Rec Board—B		017	£4.86
Rec Board—B Ext		018	£3.93
Test Load		019	£2.90
Exp. with Robots		022	£3.71
Spectrum Speech Synth & 8-Bit I/O Port (double-sided)	JAN '86	023	£6.49
Burglar Alarm			
Main Board		020	£4.97
Bell Driver	FEB '86	021	£2.90
Logic Probe		024	£4.20
Computer Movement Detector		509-02	£3.20
Clock Timer		027	£6.38
Fibre Optic Audio Link			
Transmitter	MAR '86	025	£2.99
Receiver		026	£3.23
Set of two boards		00B	£5.87
Hardware Restart (double-sided)		508-02	£6.98
Temperature/Analogue Interface		101	£3.30
Sound Activated Switch		102	£5.30
Photographic Trigger Unit			
Transmitter	APRIL '86	103	£3.45
Receiver		104	£4.03
Set of two boards		00C	£6.63
IEEE1000 PSU		105	£4.62
Scratch and Rumble Filter		106	£4.51
Notcher Effects Unit		107	£5.16
Logic Checker	MAY '86	108	£4.09
D.F. Beacon Timer		109	£5.31
STEBus Backplane		110	£10.90
Guitar Tracker		111	£5.92
Thermocouple Interface		112	£2.90
PE Hobby Board	JUNE '86	113	£22.81
BBC Light-pen		114	£2.90
JULY '86 Passive IR Detector		115	£3.54
200MHz counter			
Main board		116	£16.26
Display board		117	£12.35
Set of two boards		00D	£25.88

PE PCB ORDER FORM

Please supply the p.c.b.(s) listed on the enclosed form. Remittances should be sent to: **PE PCB Service, Practical Electronics, Intrapress, 16 Garway Road, London, W2 4NH.** Cheques should be crossed and made payable to Practical Electronics Magazines. Printed circuit boards for certain PE constructional projects are now available from the PE PCB Service, see list. They are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £2 per board for overseas airmail.

Board description	Code	Qty	Price
Name & Address:			

PE BAZAAR

A free readers' advertising service

Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules. I enclose a cut-out valid date corner.

Signature Date

Please read the RULES then write your advertisement here—one word to each box. Add your name, address and/or phone no.

COUPON VALID FOR POSTING BEFORE AUGUST, 1986 (One month later for overseas readers.)

SEND TO: PE BAZAAR, PRACTICAL ELECTRONICS, 16 GARWAY ROAD, LONDON, W2 4NH.

RULES Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Items related to electronics only. No computer software. PE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a cut-out valid "date corner". Ads. will not appear (or be returned) if these rules are broken.

Name & Address:			

Laser 2mW HE-NE scanner head and control desk, spirographic effects, little used, and data £300. Mr. D. J. Grubb, 2 Blanquettes Ave, Worcester. Tel: (0905) 51150 evenings.

HP 141/A storage scope, U/S but repairable, tube soft, good case, manual controls intact, salvage price £75. G. Hunt, 22 Usk Road, Reading, Berks. RG3 4HG. Tel: 0734 421119.

Practical Electronics Nov. 1964 to Dec. 1968 Vol. 1/1 to Vol. 4/12 in binders, offers. Mr. A. Robson, 2 Links Ave, Cromer NR27 0EQ. Tel: 0263 513303.

Wanted July 1984 issue of Practical Electronics. Mr. C. H. M. Limb, "Greyfriars", 1 Manor Farm Lane, Tidmarsh, Nr. Pangbourne, Reading, Berks. RG8 8EY. Tel: (07357) 2635.

Wanted construction and operational manual for heathkit valve worbulator, model HFWI, circuit alone would be useful. J. R. Ault, 23 Newton St., West Bromich, West Midlands B71 3RG.

Magazines in excellent condition, P.E. 1972 to 1983, E.T.I. 1973 to 1983, offers? B. C. Jackson. Tel: 051-355 9579.

Mags in good condition, P.E. 1972 to 1983, E.T.I. 1973 to 1983, offers? B. C. Jackson. Tel: 051-355 9579.

CBM C16 with recorder, p.u., tapes

and manual, new, £50 wanted. Data on Rochar A1149 counter. J. Galvin. Tel: Crudwell (06667) 7820 Wilts.

For sale Apple II Europlus computer + hardware and software equipment. Price £2,500. Nurudin Javen, 17 Ch Vert, Van doeuvres 1253, Geneva, Switzerland.

Valves B76, B9G, 50 approx. \$10. Yamaha organ C55. Akai reel to reel 4000DS V.G.C. Realistic offers. Mr. G. E. Lumley, Guildy Hall, Muker, Richmond, North Yorkshire DL11 6QG.

Learn about microprocessors, Open University course PT502, computer plus books, £150. Mr. Slater, rear 25 Newmarket St., Colne, Lancs. BB8 9BJ.

Sound city 150W PA, £30. Valve volt-meter 100µv-1000V AC/DC, 100 MR, £25. Astro-wars, £16. Simon A. J. Winder, 291 Sheffield Rd, Glossop, Derbyshire SK13 8QY. Tel. (04574) 3972.

Laser 2MW spirographic scanner head/controller, £300. Also two 5MW HE-NE laser tubes/power supplies £200 and £275. Mr. D. J. Grubb, 2 Blanquettes Ave., Worcester. Tel: (0905) 51150.

P.E. Feb. 85 modular audio system stereo 80W each channel, complete

working, £25. P.P. £10. L. T. Hill, 14 Rothesay Terr., Bedlington, Northumberland.

Wanted Electronics & Wireless World December 1985. Will pay reasonable price and airmail postage. S. Shaw, P.O. Box 1404, Randfontein 1760, South Africa.

Radio constructor. Tse Ying Choi, Rm 2, 32/F, Blk B Cheung wo Court, Kwun Tong, Kowloon, Honk Kong.

Changing hobby, all components must go, resistors, capacitors, transistors, transformers, pots, switches. SAE brings details. Mr. I. Spearman, 18 Queensway, Shelley, Ongar, Essex CM5 0BN. Tel: 0277 362197.

Heathkit complete course from A.C. to microprocessor and trainers and oscilloscopes 5MHz s/trace, write for details, £730 o.n.o. James Bonner, Ballyargus, Redcastle, co. Donegal, Ireland.

Sharp MZ-700, 64k Computer complete with data recorder, manual and games. Only £85 for the lot. Tel: (01) 986 2658 after 6pm. S. Akhtak 79 Mayola Road, London E5 0RF.

Laser 2mW HE-NE scanner head and control desk, spirographic effects, little used, and data £300. Mr. D. J. Grubb, 2 Blanquettes Ave, Worcester. Tel: (0905) 51150 evenings.

PE BAZAAR
JULY '86

PE SERVICES

BOOK SERVICE

DIGITAL IC EQUIVALENTS AND PIN CONNECTIONS BP140

A. Michaels
Shows equivalents and pin connections of a popular user-oriented selection of European, American and Japanese digital ICs. Also includes details of packaging, families, functions, manufacturer and country of origin.
0 85934 115 1 256 pages 1985 £4.95

LINEAR IC EQUIVALENTS AND PIN CONNECTIONS BP141

A. Michaels
Shows equivalents and pin connections of a popular user-oriented selection of European, American and Japanese linear ICs. Also includes details of functions, manufacturer, and country of origin.
0 85934 116 X 320 pages 1985 £4.95

INTERNATIONAL DIODE EQUIVALENTS GUIDE BP108

A. Michaels
Designed to help the user in finding possible substitutes for a large user-orientated selection of the many different types of semiconductor diodes that are available. Besides simple rectifier diodes, also included are zener diodes, LEDs, diacs, triacs, thyristors, OCIs, photo and display diodes. Also wherever possible, material type, function or type of diode, and country of origin are shown.
0 85934 083 X 144 pages 1982 £2.25

INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE BP85

A. Michaels
Helps the reader to find possible substitutes for a popular user-orientated selection of European, American and Japanese transistors. Also shows material type, polarity, manufacturer and use.
0 85934 060 0 320 pages 1981 £2.95

ELECTRONIC SCIENCE PROJECTS BP104

O. Bishop
These projects range in complexity from a simple colour temperature meter to an infra-red laser. There are novelties such as the electronic clock regulated by a resonating spring, and the oscilloscope with solid-state display. There are scientific measuring instruments such as a pH meter and an electro-cardiometer. All projects have a strong scientific flavour. They way they work, and how to build and use them are fully explained.
0 85934 079 1 144 pages 1982 £2.25

PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE BP53

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.R.I.M.
Written not for the family bookshelf but for the electronics enthusiast's workshop bench. Its aim is to bridge the gap between complicated technical theory, and "cut-and-try" methods which may bring success in design but leave the experimenter unfulfilled.
0 900162 70 8 256 pages 1979 £2.95

ESSENTIAL THEORY FOR THE ELECTRONICS HOBBYIST 228

G. T. Rubaroe, T.Eng.(C.E.I.), Assoc. I.E.R.E.
The object of this book is to supply the hobbyist with a background knowledge tailored to meet his or her specific requirements and the author has brought together the relevant material and presented it in a readable manner with minimum recourse to mathematics.
Many formulae having a practical bearing are presented in this book and purpose-designed examples are employed to illustrate their applications.
0 900162 69 4 128 pages 1977 £2.50

HOW TO DESIGN ELECTRONIC PROJECTS BP127

R. A. Penfold
There is a lot of information available on various circuit building blocks in catalogues, books, magazines, etc., but there is little information that helps the amateur user to integrate building blocks into practical projects. The aim of this book is to help the reader to put together projects from standard circuit blocks with a minimum of trial and error, but without resorting to any advanced mathematics.
0 85934 102 X 128 pages 1983 £2.25

PRACTICAL ELECTRONIC BUILDING BLOCKS - BOOK 1 BP117

R. A. Penfold
BOOK 1 contains: Oscillators - sine-wave, triangular, square-wave, sawtooth, and pulse waveform generators operating at audio frequencies, including simple voltage-controlled types, L-C and crystal RF oscillators. Timers - simple monostable circuits using ICs, the 555 and 7555 devices, etc. Also precision long timers using the ZN1034E. Miscellaneous - noise generators, rectifiers, comparators and triggers, etc.

R. A. Penfold
BOOK 2 contains: Amplifiers - low level discrete and op-amp circuits, voltage and buffer amplifiers including DC types. Also low-noise audio and voltage controlled amplifiers. Filters - high-pass, low-pass, 6, 12, and 24 dB per octave types. Also voltage-controlled filters. Miscellaneous - IC power amplifiers, mixers, voltage and current regulators, etc.
Book 1: 0 85934 092 9 128 pages 1983 £1.95
Book 2: 0 85934 093 7 112 pages 1983 £1.95

POPULAR ELECTRONIC CIRCUITS - BOOK 1 BP80

R. A. Penfold
Contains a wide range of circuits which are accompanied by a short text giving a brief introduction, circuit description and any special notes on construction and setting-up that may be necessary.
0 85934 055 4 160 pages 1980 £1.95

POPULAR ELECTRONIC CIRCUITS - BOOK 2 BP98

R. A. Penfold
Again, provides a wide range of designs for electronic enthusiasts who are capable of producing working projects from just a circuit diagram without the aid of detailed constructional information. However, where relevant, any special setting-up procedures are described.
0 85934 073 2 160 pages 1982 £2.25

IC 555 PROJECTS BP44

E. A. Parr, B.Sc., C.Eng., M.I.E.E.
Every so often a device appears that is so useful that one wonders how life went on before without it. The 555 timer is such a device. Included in this book are basic and general circuits, motorcar and model railway circuits, alarms and noise-makers as well as a section on the 556, 558 and 559 timers.
0 85934 047 3 176 pages revised edition 1982 £2.50

POWER SUPPLY PROJECTS BP76

R. A. Penfold
Mains power supplies are an essential part of many electronic projects.
The purpose of this book is to give a number of power supply designs, including simple unregulated types, fixed-voltage regulated types, and variable-voltage stabilised designs, the latter being primarily intended for use as bench supplies for the electronics workshop. The designs provided are all low-voltage types for semiconductor circuits.
0 900162 96 1 96 pages 1980 £2.50

ELECTRONIC MUSIC PROJECTS BP74

R. A. Penfold
Provides the constructor with a number of practical circuits for the less complex items of electronic music equipment, including such things as fuzz box, waa-waa pedal, sustain unit, reverberation and phaser units, tremolo generator, etc.
The text is divided into four chapters as follows: Chapter 1, Guitar Effects Units; Chapter 2, General Effects Units; Chapter 3, Sound Generator Projects; Chapter 4, Accessories.
0 900162 94 5 112 pages 1980 £2.50

MORE ADVANCED ELECTRONIC MUSIC PROJECTS BP174

R. A. Penfold
Intended to complement the first book (BP74) by carrying on where it left off and providing a range of slightly more advanced and complex projects. Included are popular effects units such as flanger, phaser, mini-chorus and ring-modulator units. Some useful percussion synthesizers are also described and together these provide a comprehensive range of effects including drum, cymbal and gong-type sounds.
0 85934 148 8 128 pages 1986 £2.95

A PRACTICAL INTRODUCTION TO MICROPROCESSORS BP123

R. A. Penfold
Provides an introduction which includes a very simple microprocessor circuit which can actually be constructed so that the reader can experiment and gain practical experience.
0 85934 098 8 96 pages 1984 £1.95

MICRO INTERFACING CIRCUITS - Book 1 BP130

R. A. Penfold
Both books include practical circuits together with details of the circuit operation and useful background information. Any special constructional points are covered but PCB layouts and other detailed constructional information are not included.
BOOK 1 is mainly concerned with getting signals in and out of the computer.
BOOK 2 deals primarily with circuits for practical applications.
Book 1: 0 85934 105 4 112 pages 1984 £2.25
Book 2: 0 85934 106 2 112 pages 1984 £2.25

AN INTRODUCTION TO COMPUTER PERIPHERALS BP170

J. W. Penfold
Covers such items as monitors, printers, disc drives, cassette recorders, modems, etc., explaining what they are, how to use them and the various types and standards. Helps you to make sure that the peripherals you buy will work with your computer and with each other.
0 85934 144 5 80 pages 1985 £2.50

EASY ADD-ON PROJECTS FOR SPECTRUM, ZX81 & ACE BP124

O. Bishop
Describes how to build a number of electronic projects which you can use with your Spectrum, ZX81 or Jupiter Ace microcomputer. The projects include a Pulse Detector, Picture Digitiser, Five-key Pad, Model Controller, Bleeper, Lamp Flasher, Light Pen, Magnetic Catch, Lap Sensor, Photo-flash, Games Control and six more projects that make up a Weather Station. All are fairly simple and inexpensive to construct.
0 85934 099 6 192 pages 1983 £2.75

EASY ADD-ON PROJECTS FOR THE AMSTRAD CPC 464, 664, 6128 AND MSX COMPUTERS BP171

O. Bishop
The projects of books BP124 and BP134 adapted for use with the Amstrad CPC 464, 664, 6128 and the MSX range of machines. Again the Address Decoder is constructed as a separate item that can be used with any of the projects.
0 85934 145 3 196 pages 1986 £2.95

EASY ADD-ON PROJECTS FOR COMMODORE 64, VIC-20, BBC MICRO AND ACORN ELECTRON BP134

O. Bishop
Similar in style to BP124 except, of course, many of the projects have been modified, where necessary, to operate with the different machines.
0 85934 109 7 208 pages 1985 £2.95

A Z-80 WORKSHOP MANUAL BP112

E. A. Parr, B.Sc., C.Eng., M.I.E.E.
This book is intended for people who wish to progress beyond the stage of BASIC programming to topics such as machine code and assembly language programming, or need hardware details of a Z-80 based computer.
0 85934 087 2 192 pages 1983 £2.75

AN INTRODUCTION TO COMPUTER COMMUNICATIONS BP177

R. A. Penfold
Provides details of the various types of modem and their suitability for specific applications, plus details of connecting various computers to modems, and modems to the telephone system. Also information on common networking systems and RITTY.
0 85934 151 8 96 pages 1986 £2.95

PRACTICAL COMPUTER EXPERIMENTS BP78

E. A. Parr, B.Sc., C.Eng., M.I.E.E.
This book aims to fill in the background to the microprocessor by constructing typical computer circuits in discreet logic.
0 900162 98 8 96 pages 1980 £1.75

PE BOOK ORDER FORM

Please supply the book(s) listed on the enclosed form. Remittances should be sent to: PE Book Service, Practical Electronics, Practical Electronics Magazines, 16 Garway Road, London, W2 4NH. Cheques should be crossed and made payable to Intrapress.

The books offered by the PE Book Service are a selection chosen to offer variety and are not necessarily recommended or endorsed by PE editorial staff. From time to time, the book list will be changed and new titles added as they become available.

Please allow 28 days for delivery

Book description	Code	Qty	Price
Post and packaging 50p (overseas £1)			
Name & Address:			

COMMENT . . .

Where Are All The Women Engineers?

LAST year the female membership of the Institution of Electrical Engineers for the first time exceeded the 1,000 mark. This was hailed as a milestone, but after taking into account that the organization's total membership is over 85,000, one realises there is small cause for celebration.

The scarcity of women engineers in Britain has long been a recognized problem. As early as 1919 the Women's Engineering Society was trying to alleviate it by encouraging women to enter the male-dominated field. With the "boiler suits and spanners" image that engineering had, and entrenched stereotypes about men and women's roles, the organization had its work cut out.

It was helped with its task five years later by the creation of the Electrical Association for Women. To commemorate the 21st birthday of the E.A.W. in 1945, the association established the Caroline Haslett Memorial Trust. Named after the association's first director, the trust's aim was to provide financial help for women to become engineers and scientists.

In a further effort to attract women to the engineering profession, the Trust collaborated with the Institution of Electrical and Electronics Engineers in 1978 to introduce the Girl Technician Engineer of the Year award. Every year since then a prize of £250 has been given to an outstanding female technician engineer under the age of 30 in the hope that she will serve as a model for other women to emulate.

Despite these encouraging developments, however, the number of women

engineers has been slow to rise. When the Committee of Inquiry into the Engineering Profession published its report in 1980, it commented on the problem: "... less than half of the current stock of engineers are women. Engineering has thus been recruiting from only half of the population. Girls now comprise a little over three per cent of all engineering students, which is a marked improvement on past showing but is still minimal considered that . . . 42 per cent of graduate scientists from universities are women. We would welcome an increase in the proportion of women graduating in engineering and urge all concerned to work towards this goal."

Four years later, the Engineering Council took up the call. In conjunction with the Equal Opportunities Commission, the council named 1984 "Women Into Science and Engineering (WISE) Year" and launched a campaign in schools to encourage girls to consider careers in the science and engineering professions.

Ron Kirby, the council's Director of Public Affairs, says that stereotyped attitudes about engineering being an unsuitable profession for women has been the biggest obstacle the campaign faced. "Slowly we're getting the message across that engineering is not a dirty job," he said. "New technology and computerization is giving it the right image of being a clean job." That, in addition to an increasing willingness among employers to hire women engineers, makes him optimistic about the future of women in the profession.

But he admits the current figures don't bear that optimism out. A mere

one per cent of the 505,000 registered and chartered engineers in Britain are women. That compares with three per cent in Western Europe and nine per cent in America.

That's hardly a good record for a country desperately trying to keep pace with its industrial competitors. If Britain wants to avoid becoming what the Prince of Wales earlier this year called a "fourth-rate country" things must change. To keep up with the competition (Japan has five times the number of engineering graduates as Britain), Britain can no longer afford to "recruit from only half of the population."

Clearly the profession and the government, by giving awards and launching educational campaigns, have done their part. What more must be done to remedy this situation?

Attitudes are difficult to change but stagnation and decline await the society that refuses to adapt them to fulfil its needs. Britain needs more engineers and women can go a long way towards filling that gap. The attitude that certain professions are "unsuitable" for women is outdated and it's time parents and teachers recognized that. They must provide encouragement for young girls who show promise in the science fields and convince them that a career in those fields is within their grasp. Britain has a woman at the head of its monarchy and leading its government. Where are all the women engineers?

MARY-ANN HUBERS . . .

NEXT MONTH . . .

THE NUCLEAR ISSUE—Informative comment plus a Geiger Counter constructional project

BETTER USE OF BATTERIES—The failure mechanisms and secrets of sealed nickel cadmium cells

CAD IN ELECTRONICS—Computer aided design, manufacture and testing is now available to the hobbyist. In the first of a series of articles, PE looks at its use in Industry

COMPUTER AIDED CHIP TESTER—Automatic test equipment project for CMOS and TTL logic devices

FIBRE OPTIC DATA LINK—Designed for serial digital communication using the RS232 standard

INDUSTRY NOTEBOOK

BY NEXUS

Expectations of expert systems and fewer feather beds

WHETHER artificial intelligence (AI) can be considered a part of electronics or vice versa is a matter for academic debate. Certainly they are interdependent. What is more important from the industrial point of view is whether AI can give the computer manufacturing sector a much needed pick-me-up.

In the USA the electronics industry is heavily weighted towards computer manufacturing and the trading in this sector has been very depressed during 1985/86. Honeywell, for example, recently reported a 40% drop in after-tax profits and National Cash Register a corresponding fall of 26%. Even the giant IBM admitted to a downward slide of 7%. In the UK we have seen Sinclair Research in severe financial difficulties, with Sir Clive himself taking a big pay cut and virtually working for his bankers, and various other firms like Systime and ACT experiencing all kinds of troubles affecting their revenues.

THE BIG LEAGUE

If you like statistics you may be interested in how big some of the major electronics/electrical companies have become. Britain's largest manufacturing company, GEC, now has annual sales of about £5.5 billion and employs over 160,000 people. But the multinational giant Philips tops this with sales of £14 billion per annum, while West Germany's Siemens generates as much as £16 billion p.a. and employs 350,000 people (240,000 within Germany). Hewlett-Packard, which is purely electronic and specialises in instruments and computers, has sales revenues of £4.7 billion and employs 84,000 people.

All these big established companies have a policy of ploughing back a certain proportion of their sales income into R&D—very necessary in the fast moving technology of electronics. Philips, for example, allocates 7% of its revenues, which comes to the colossal R&D expenditure of nearly £1 billion per year.

But whether AI can actually do anything for computer manufacturing is somewhat unclear at the moment. First of all we don't really know what it is, except in very academic terms. It has been described as a body of technique by which the power of the computer may be harnessed to simulate human thought. Of course, existing computer applications are already simulating the purely logical and calculating processes of human thought. But AI is concerned with other, less mechanistic mental processes, such as inference, that can be used for solving problems. I suppose the boldest, riskiest form of inference is that intuitive process we call a hunch.

EXPERT SYSTEM

At present the form of AI which has really got off the ground is the expert system. The essence of this is that the computer stores empirical knowledge provided by the practical experience of many human experts in a given field. It can then be interrogated to answer questions, solve problems or draw conclusions, using a set of rules provided in the software. For example, in a medical diagnosis expert system, if the doctor writes in a group of symptoms which are not at all common or familiar to him, the expert system will list the probabilities with which this particular group is associated with different known illnesses.

Two other fields where uncertainties reign and all professional decisions are to some extent gambles are insurance and marketing. Both, I see, are now the subject of 'Alvey clubs' in the UK. These clubs are groups of people with common interests who get together under the aegis of the national Alvey programme for advanced information technology. It has a special section for intelligent knowledge-based systems (IKBS).

The latest club is the Econometric Model Building Expert System Club, or EMEX for short. Here the idea is to combine the knowledge of commercial experts to form econometric models of various markets, which can be interro-

gated when difficult commercial decisions have to be taken. The Henley Centre for Forecasting provides the econometric expertise needed, while an AI firm called Expert Systems International Ltd contributes particular skills in 'knowledge engineering' and the design of expert systems.

As for the electronic hardware needed for AI, this seems a pretty open question at present. But listen to Prof. Edward Feigenbaum, a director of Sperry. At a recent conference he said: "Knowledge engineering is software critical. Some tasks can be run on a microcomputer while others are too slow on a Cray." However, he was able to envisage an ideal machine which had 'embedded code, high speed chip processors and lots of memory'. Not surprisingly, he cited a Sperry product, the Explorer, as one example of such a system. Others were Texas Instruments and Sun microcomputers. But some authorities on AI think a fundamentally new type of hardware will be needed to get optimum results—perhaps with many Transputer-like processors working in parallel with continuous communication.

"Knowledge engineering is software critical"

Already forecasts are being made of the sales revenues that might be expected from AI products. People in the USA are predicting revenues of £3-7 billion by the year 1990, rising to a staggering £700 billion by the end of the century. This implies a lot of money going into AI research in the meantime. As an example, Britain's STC has just signed a £6.5 million contract for research into building knowledge-based systems. This comes under the EEC's Esprit programme for Europe and includes as partners the companies Scicon, Scientific Control Systems and Cap Gemini Sogeti (a French software house). The Esprit projects, as you may have gathered, are run jointly by academia and industry. Here the academic partners are the University of Amsterdam and the Polytechnic of the South Bank in London.

DEFENCE SPENDING

Much as I applaud most of the activities of the UK electronics industry, I'm glad to hear that in future I won't have to contribute quite so much towards its upkeep out of my own pocket. I refer, of course, to the money we all have to pay through income tax, to fund the Ministry of Defence's spending on military equipment. This spending is now running at about £8.5 billion a year.

The Government has decided to cut the notorious 'cost-plus' system by which it pays its electronics and other contractors. Under this scheme it has been giving the contractors interim payments of up to 100 per cent of costs as the work proceeds. And often these payments continue even when the contract falls several years behind schedule—as with the Nimrod early warning radar project I discussed in the March issue.

Then the Ministry pays the contractor his profit on top. But the firm doesn't always have to wait till the job is finished before it gets that. The MoD has been in the practice of making interim payments of profit as well. George Younger, the man who succeeded Michael Heseltine as defence minister after the Westland affair, has

described the whole system as 'generous'. Many people who earn their living under somewhat harsher commercial conditions will consider this a polite euphemism for feather-bedding.

When you think how strongly the present government is wedded to the idea of the completely free market, in which all trading is ruled by the prevailing market forces, it's surprising that the 'cost-plus' system has been allowed to continued for so long. At least, it shows that all those ex-ministers and military men on the boards of the leading companies have been doing a good lobbying job for their employers.

PCB INVENTORS

The printed circuit has become such an established and familiar method of electronic construction that one tends to forget it was actually thought up as a new idea by someone at some time. I'm therefore glad to see that one of the pioneers of the p.c.—if not "the" inventor of the technique—has been given a well-deserved accolade for his work in this field. Dr Paul Eisler has received the Institute of Circuit Technology Award in recognition of his achievements over some 25 years. During this time he has filed over 50 patents.

Meanwhile the industry continues to profit from the original invention. Where would computer and telecoms manufacturers be today without the p.c.b.? Frost & Sullivan, the market forecasters, reckon that in Western Europe alone the sales of p.c.b.s will rise from a 1984 figure of £900 million to £1.75 billion by 1990. They predict that sales of multi-layer circuits will continue to grow rapidly, at the expense of single- and double-sided boards. The flexible type of boards are likely to remain with their present 5% of the market.

Long before the present style of p.c. started to replace wired connections in electronics, a British inventor of Hungarian origin, John Sargrove, built an automatic machine for making simple radio sets without conventional wiring. It was called ECME (Electronic Circuit Making Equipment) and was intended to churn out huge quantities of cheap radios for the Kuomintang regime of Chiang Kai-shek in China. These were to be distributed to the Chinese people to facilitate Chiang's political propaganda through broadcasting. But when the Kuomintang regime was militarily defeated by Mao Tse-tung's communists, no more money was forthcoming from China and the ECME project had to fold. PE

ENGINEERING TECHNICIANS COMMUNICATIONS AND ELECTRONICS

A Planned Career in Technology in the Cotswolds

Starting Pay Package up to £10,685

- **VACANCIES** at Engineering Technician level.
- **CHALLENGING WORK** in the field of technical support of highly sophisticated communications and computer systems.
- **STRUCTURED TRAINING** programme for new entrants.
- **OPPORTUNITIES** for gaining experience in a wide variety of technical roles.

- **EXTENSIVE ENGINEERING FACILITIES**
- **CAREER PLANNING** aided by regular assessments of performance.
- **ADVANCEMENT** opportunities on the basis of proven ability.
- **OVERSEAS** service (voluntary).
- **FLEXIBLE** working hours with up to six weeks leave.
- **RELOCATION EXPENSES** in most cases.

Applicants should normally possess a BTEC Ordinary National Certificate/Diploma or higher qualification in Telecommunications, Electronics or similar discipline; or an acceptable equivalent qualification. An aggregate of at least 4 years relevant training and

experience is required; registration with the Engineering Council as an Engineering Technician (Eng. Tech) would be an advantage.

SALARY SCALE: £6,599 – £9,135 (under review) plus a special pay addition of £1,550 p.a. at all points on the salary scale.

INTERESTED? Then send for full details and application form to the address below, quoting Ref: T/945/86



THE RECRUITMENT OFFICE, GCHQ, ROOM A/1108
OAKLEY, PRIORS ROAD, CHELTENHAM, GLOS GL52 5AJ
OR TELEPHONE (0242) 32912/3

NEWS LATEST . . .

Xicor have announced a new device the E2POT, an eight pin digitally controlled potentiometer. The chip allows the digital control of an on chip ladder network of resistors which form a 99 step potentiometer. Three pins control the 'wiper' position and the last position of the wiper is automatically stored in a non volatile register. This allows the device to be set and to retain this setting until changed. The chips are available in three decades of resistance range, starting at 10K.

Fujitsu have just launched a range of 1Mbit CMOS EPROMS. They are available in four versions and all have access times of between 150ns and 250ns coupled with low power consumption. Probably the most useful of the versions is the MBM27C1000 which is organised as 128K x 8bits in a 32pin package.

One way of overcoming the problem of easy communications between a computer and a human user is to use a touch screen. This technology has been available for some time and is a standard on one of the Hewlett Packard personal computers where it compliments the keyboard and other input devices like tablets and mice. The standard way of creating a touch screen has been to use a matrix of infra-red beams and detectors just in front of the screen, these are scanned like a keyboard to see if any are broken by a finger touching the screen. However, R.H.Technical Industries Ltd have produced a new low cost alternative. This uses a transparent membrane touch switch which can be placed in front of the screen. This device should open up opportunities for software companies to produce low cost user friendly interactive software for a wide range of personal computers.

'Smart cards' which incorporate an electronic circuit have been much in the news recently as a replacement for the ordinary plastic credit card with its magnetic stripe. The 'smart card' is intended to be one of the central components of the so called 'cashless society'. The card incorporates a microprocessor and associated memory and is virtually tamper proof and unforgeable. Fujitsu have just launched a range of 'smart cards' and memory cards. The Fujitsu 'smart cards' incorporate an 8 bit microprocessor with either 64K or 256K of EPROM memory imbedded into a thin plastic card the size of a normal credit card. Secure data areas can be created in different parts of memory thereby ensuring proof against forgery or illegal data transaction. The 'memory cards' are designed to store data in an easily transportable form, they can hold up to 8M of CMOS memory which is again embedded into a credit card size sheet of plastic. Both card types have electrical connections along one edge of the card and receive electrical power from the reading device.

Mullard have launched what is believed to be a 'world first' in flat CRT TV tube technology. The screen is 19cms diagonal but only 5cms deep and has been dubbed by Mullard 'Slimscreen'. It is a high technology folded optics cathode ray tube which gives a flat TV display with a conventional 4:3 aspect ratio. The tube offers high resolution plus good screen brightness and contrast. Currently these tubes are only available in a monochrome version but colour versions are being developed and should be announced in the near future.

FULL-TIME TRAINING COURSES

2 YEAR

**B-TEC National Diploma (OND)
ELECTRONICS &
COMMUNICATIONS ENGINEERING**
(Television & Computing)

15 MONTHS

**B-TEC National Certificate (ONC)
ELECTRONIC EQUIPMENT SERVICING**
(Television & Video)

15 MONTHS

**B-TEC National Certificate (ONC)
COMPUTING TECHNOLOGY**

9 MONTHS

**B-TEC Higher National Certificate (HNC)
COMPUTING TECHNOLOGY
& ROBOTICS**

HIGH PERCENTAGE OF COLLEGE BASED
PRACTICAL WORK

SHORT COURSES WITH PREVIOUS
KNOWLEDGE

NO EXTRA CHARGES FOR OVERSEAS
STUDENTS

Prospectus from:

**LONDON ELECTRONICS
COLLEGE**

Dept: AA, 20 Penywern Road,
London SW5 9SU. Tel: 01-373 8721

SERVICE SHEETS

SERVICE MANUALS. - Television, Audio, Video, Vintage, Test, etc. SAE enquiries: MAURITRON (PE), 8 Cherry Tree Road, Chinnor, Oxon.

BELLS TELEVISION SERVICES for service sheets of Radio, TV, etc £1.50 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

ESR ELECTRONIC COMPONENTS

- Full range of components
- Motors & Servos
- Robot Arms & Interfaces
- Velleman Electronic Kits

Send for New Catalogue 60p inc. P&P

13A Station Rd, Cullercoats, North Shields,
Tyne & Wear NE30 4PQ Tel. 091 251 4363

Carbon Film Resistors 1/4W E24 series 0-51R to 10MΩ - 1p
100 off per value - 75p 1000 off in even hundreds per value - £7
Metal Film 1/4W 10R0 to 1MΩ 5% E12 series - 2p 1% E24 series - 3p
8C107/8/9 - 12p 8C547/8/9 - 8p 8C557/8/9 - 8p 8C182L, 184L - 10p
8FY50/51/52 - 20p 2N3055 - 50p TIP31A, 32A - 25p TIP 41, 42 - 40p

Tantalum bead subminiature electrolytics (Mfids/Volts)
0-1/35, 0-22/35, 0-47/35, 3-3/16, 4-7/16 - 14p 4-7/35 - 15p
2-2/35, 4-7/25, 10/6 - 15p 4-7/35, 6-8/16 - 16p 10/16, 22/6 - 20p

Aluminium Electrolytics (Mfids/Volts)
1/50, 2-2/50, 4-7/25, 4-7/50, 10/16, 10/25, 10/50 - 5p 22/16, 22/25 - 6p
22/50, 47/16, 47/25, 47/50 - 6p 100/16, 100/25 - 7p 100/50 - 12p
100/100 - 14p 220/16 - 18p 220/25, 220/50 - 10p 470/16, 470/25 - 11p
1000/25 - 25p 1000/35, 2200/25 - 22p 4700/25 - 70p

Miniature Polyester Capacitors 250V Wkg. Vertical Mounting
-01, -015, -022, -033, -047, -068 - 4p 0-1 - 5p 0-15, -22 - 6p 0-47 - 8p

Mylar Capacitors 100V Wkg. Vertical Mounting E12 Series
1000p to 8200p - 3p -01 to -068 - 4p 0-1 - 5p 0-15, 0-22 - 6p

Subminiature Ceramic Plate 100V Wkg. E12 Series Vertical Mounting
2% 1P8 to 47P - 3p 56P to 330P - 4p 10% 330P to 4700P - 4p

Polystyrene Capacitors 63V Wkg. E12 Series Axial Mounting
10P to 820P - 3p 1000P to 10,000P - 4p 12,000P - 5p
1N4148 - 2p 1N4002 - 4p 1N4006 - 6p 1N5404 - 14p W01 bridge -
25p 0A91 - 6p

Zener diodes E24 series 3V3 to 33V 400mW - 8p 1 watt - 12p
L.E.D.'s Red, Green & Yellow 3mm & 5mm - 10p 8mm - 35p
20mm fuse 0-1A to 5A quick blow - 5p 5P Anti Surge - 8p
High Speed drills 0-8mm, 1-0mm, 1-3mm, 1-5mm, 2mm - 25p
Expo Reliant drilling machines 12V d.c. with improved 3-jaw chuck £6.50
Nicsads AA - 80p HP11 - £2 PPS - £4.20 Universal Chargers - £6
Glass reed switches single pole make contacts - 8p Magnets - 12p

VAT inclusive. Return postage 20p (free over £5). Lists free.

THE C.R. SUPPLY CO.,
127 Chesterfield Road,
Sheffield S8 0RN. Tel. 557771.

HEATHKIT U.K. SPARES AND SERVICE CENTRE. Cedar Electronics, Unit 12, Station Drive, Bredon, Tewkesbury, Glos. Tel. (0684) 73127.

TURN YOUR SURPLUS capacitors, transistors, etc into cash. Contact COLES HARDING & CO., 103 South Brink, Wisbech, Cambs. Tel. 0945 584188. Immediate settlement.

CLEARING LABORATORY, scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders etc. Tel. 0403-76236.

MAPLIN ELECTRONIC piano 61 note keyboard. Three voices - piano, clavichord, honktonk. Partially constructed. £100. M. Settle. Cartref. 17 Littlefields Avenue, Banwell, Weston Super Mare, Avon BS24 6BQ.

PANEL METERS Sirens Service Aids, Microphones Tools Transformers Test Equipment. Send £1 for Fully Illustrated 170 pages Catalogue. M. Dziubas, 158 Bradshawgate, Bolton, Lancs.

TOP QUALITY power supply units. Ex-video, unboxed. Various outputs including 5V, 12V. Only £10 + £2 P&P. V.S.E., 212 Dudley Hill Road, Bradford 2, W. Yorks. (0274) 636652.

COMPONENT PANELS. Ex-equipment. Each pack (13 panels) includes:- CPU, I/O ports, rams, battery, 23 LEDs, 11 7-seg and drivers, many more chips, 29 push buttons, 6MHz crystal. Numerous:- Transistors, diodes, resistors, capacitors, chokes, pots, plugs, sockets, etc., etc. All this for £12 per pack +£1 P&P. V.S.E. 212 Dudley Hill Road, Bradford 2, W. Yorks. (0274) 636652.

REPAIRS we repair anything from PC-xt's to lasers. Fast turnaround. W.T.S. Electronics. 5-9 Portland Rd., Luton, Beds. Tel 24hrs. (0582) 458375.

STANDARD BCO Thumbwheel switches £1.75 per decade, end cheeks 80p pair. P&P 25p. All +VAT. Mail order only. Noyes Electronics, 13 Bowfell Close, Tilehurst, Reading RG3 6QR.

THE SCIENTIFIC WIRE COMPANY				
811 Forest Road, London E17. Telephone 01-531 1568				
ENAMELLED COPPER WIRE				
SWG	1lb	8 oz	4 oz	2 oz
8 to 34	3.63	2.09	1.10	0.88
35 to 39	3.82	2.31	1.27	0.93
40 to 43	6.00	3.20	2.25	1.61
44 to 47	8.67	5.80	3.49	2.75
48	15.96	9.58	6.38	3.69
SILVER PLATED COPPER WIRE				
14 to 30	9.09	5.20	2.93	1.97
TINNED COPPER WIRE				
14 to 30	3.97	2.41	1.39	0.94
Fluxcore				
Solder	5.90	3.25	1.82	0.94

Prices include P&P VAT. Orders under £2 add 20p.
SAE for list of copper and resistance wire.
Dealer enquiries welcome.

WHO CAN PUT A PRICE ON A PEACE OF MIND

PROFESSIONAL EQUIPMENT AT LOW! LOW! PRICES.
HOME SECURITY IS NOW AVAILABLE AT TRADE PRICES
ADVANCED SECURITY PRODUCTS LTD
2 Ealing Road, Aintree,
Liverpool L9 0HU, Merseyside.
Tel: 051-525 3440
FREE CATALOGUE
PHONE OR S.A.E.

CABINET FITTINGS

Fretcloths, Coverings, Handles, Castors, Flight Case Locks & Parts, Jacks, XLRs, Bulgins, Reverb Trays, P & N mic Stands, ASS Glassfibre Horns, CELESTION POWER Speakers.

ADAM HALL SUPPLIES LTD.

Send 30p cheque/
P.O. for illustrated
catalogue: Adam Hall (PE Supplies),
Unit G, Carlton Court, Grainger Road,
Southend-on-Sea.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for

insertions. I enclose Cheque/P.O. for £.....
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)

NAME

ADDRESS

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number £1.00 extra. Semi-display setting £8 per single column centimetre (minimum 2.5 cms). All cheques, postal orders, etc. to be made payable to Intrapress and crossed. Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to Practical Electronics, 16 Garway Road, London W2 4NH. Tel. (0322) 521069.

Master Electronics - Microprocessors - Now! The Practical Way!

- Electronics - Microprocessors - Computer Technology is the career and hobby of the future. We can train you at home in a simple, practical and interesting way.
- Recognise and handle all current electronic components and 'chips'.
- Carry out full programme of experimental work on electronic computer circuits including modern digital technology.
- Build an oscilloscope and master circuit diagram.
- Testing and servicing radio - T.V. - hi-fi and all types of electronic/computer/industrial equipment.



New Job? New Career? New Hobby?

SEND THIS COUPON NOW.

FREE! COLOUR BROCHURE

Please send your brochure without any obligation to

OR TELEPHONE US 062 67 6114
OR TELEX 22758 (24 HR SERVICE)



NAME _____ I am interested in

ADDRESS _____ ELECTRONICS

PE 7 _____ MICROPROCESSORS

_____ RADIO AMATEUR LICENCE

_____ CITY & GUILDS EXAMS

Other Subjects _____

British National Radio & Electronics School P.O. Box 7, Teignmouth, Devon, TQ 14 0HS

MAKE YOUR INTERESTS PAY!

More than 8 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your FREE information pack on the course of your choice (tick one box only).

Electronics	<input type="checkbox"/>	Radio, Audio and TV Servicing	<input type="checkbox"/>
Basic Electronic Engineering (City & Guilds)	<input type="checkbox"/>	Radio Amateur Licence Exam (City & Guilds)	<input type="checkbox"/>
Electrical Engineering	<input type="checkbox"/>	Car Mechanics	<input type="checkbox"/>
Electrical Contracting/Installation	<input type="checkbox"/>	Computer Programming	<input type="checkbox"/>
GCE over 40 'O' and 'A' level subjects			<input type="checkbox"/>

ICS Name _____ P. Code _____
Address _____
International Correspondence Schools, Dept ED576, 312/314 High St.,
Sutton, Surrey SM1 1PR. Tel. 01-643 9568 or 041-221 2926 (24 hrs).

INDEX TO ADVERTISERS

Adam Hall Supplies Ltd.	61
Bi-Pak Components	19
B.K. Electronics	IBC
B.N.R.E.S.	62
Cricklewood Electronics	43
Crodar	53
Crofton Electronics	49
C.R. Supply Co.	61
Cybernetic Applications	62
Grandata	45
ICS Intertext	62
London Electronics College	62
Magenta Electronics	IFC
Maplin Electronics	OBC
Marco Trading	43
Phonosonics (Becker)	14
Riscomp Ltd.	37,49
Scientific Wire Co.	61
Technomatic	8 & 9
T.K. Electronics	43
Universal Semiconductor Devices	45

Amateur Radio & Electronics Hobby Fair

To be held at Wembley Conference Centre,
Saturday 5th & Sunday 6th July 1986

Practical Electronics will be exhibiting a range of
top quality electronic projects and robots

The Organisers are: Amateur Radio
Promotions, Woodthorpe House, Clapgate
Lane, Birmingham B32 3BU—Telephone:
021-421 5516

NEPTUNE I, II
2.5 Kg at 1120mm
Hydraulic using water

MENTOR
1 Kg at 420mm
DC servos

ROBOTS from only £435!

UK's WIDEST Range of low cost robotic & FMS equipment

WORKCELL COMPONENTS
indexing table
expandable conveyor
sensors gauges etc

Cybernetic Applications
West Portway Ind. Est.
Andover, Hants
SP10 3PE

Tel. 0264 50093
Telex 477019


SERPENT I, II
2 Kg at 400 or 650mm
DC servo/pneumatic SCARA

NAIAD
water hydraulic/
DC servo/
pneumatic
500gm at 500mm with see through perspex cylinders

OMP POWER AMPLIFIER MODULES

OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof. **Supplied ready built and tested.**

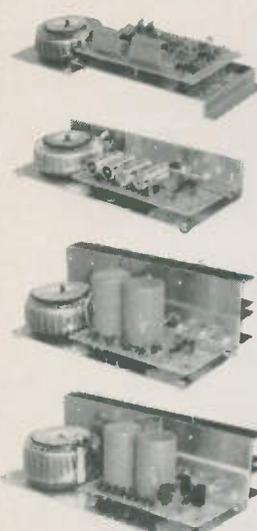

OMP100 Mk II Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz -3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV at 10K, Size 355 X 115 X 65mm. **PRICE £33.99 + £3.00 P&P.**

OMP/MF100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 80, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 X 123 X 60mm. **PRICE £39.99 + £3.00 P&P.**

OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 250, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 X 150 X 100mm. **PRICE PRICE £62.99 + £3.50 P&P.**

OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 350, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 X 147 X 102mm. **PRICE £79.99 + £4.50 P&P.**

NOTE: Mos Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV) If required, P.A. version (50KHz bandwidth & Input Sensitivity 775mV) Order - Standard or P.A.



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.F.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. **PRICE £8.50 + 50p P&P.**

LOUDSPEAKERS 5" to 15" up to 400 WATTS R.M.S. Cabinet Fixing in stock. Huge selection of McKenzie Loudspeakers available including Cabinet Plans. Large S.A.E. (28p) for free details.

POWER RANGE
 8" 50 WATT R.M.S. Hi-Fi/Disco.
 20 oz magnet, 1 1/2" ally voice coil. Ground ally fixing escutcheon. Res. Freq 40Hz. Freq. Resp. to 6KHz. Sens. 92dB. **PRICE £10.99** available with black grille £11.99 P&P £1.50 ea.
 12" 100 WATT R.M.S. Hi-Fi/Disco.
 50 oz magnet, 2" ally voice coil. Ground ally fixing escutcheon. Die cast chassis. White cone. Res. Freq. 25Hz. Freq. Resp. to 4KHz. Sens. 95dB. **PRICE £28.60 + £3.00 P&P ea.**

McKENZIE
 12" 85 WATT R.M.S. C1285TP Lead guitar/keyboard/Disco.
 2" ally voice coil. Ally centre dome. Res. Freq. 45Hz. Freq. Resp. to 6.5KHz. Sens. 98dB. **PRICE £28.76 + £3.00 P&P ea.**
 12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone.
 Res. Freq. 45Hz. Freq. Resp. to 14KHz. **PRICE £29.80 + £3.00 P&P ea.**
 15" 150 WATT R.M.S. C15 Bass Guitar/Disco.
 3" ally voice coil. Die cast chassis. Res. Freq. 40Hz. Freq. Resp. to 4KHz. **PRICE £54.99 + £4.00 P&P ea.**
 10" 60 WATT R.M.S. 1060GP Gen. Purpose/Lead Guitar/Keyboard/Mid. P.A.
 2" voice coil. Res. Freq. 75Hz. Freq. Resp. to 7.5KHz. Sens. 99dB. **PRICE £19.15 + £2.00 P&P.**
 10" 200 WATT R.M.S. C10200GP Guitar, Keyboard, Disco.
 2" voice coil. Res. Freq. 45Hz. Freq. Resp. to 7KHz. Sens. 101dB. **PRICE £51.00 + £3.00 P&P.**
 15" 200 WATT R.M.S. C15200 High Power Bass.
 Res. Freq. 40Hz. Freq. Resp. to 5KHz. Sens. 101dB. **PRICE £59.45 + £4.00 P&P.**
 15" 400 WATT R.M.S. C15400 High Power Bass.
 Res. Freq. 40Hz. Freq. Resp. to 4KHz. Sens. 102dB. **PRICE £85.00 + £4.00 P&P.**

WEM
 5" 70 WATT R.M.S. Multiple Array Disco etc.
 1" voice coil. Res. Freq. 52Hz. Freq. Resp. to 5KHz. Sens. 89dB. **PRICE £19.99 + £1.50 P&P ea.**
 8" 150 WATT R.M.S. Multiple Array Disco etc.
 1" voice coil. Res. Freq. 48Hz. Freq. Resp. to 5KHz. Sens. 92dB. **PRICE £29.49 + £1.50 P&P ea.**
 10" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 92dB. **PRICE £33.49 + £2.00 P&P ea.**
 12" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 94dB. **PRICE £41.49 + £3.00 P&P ea.**

SOUNDLAB (Full Range Twin Cone)
 5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1" voice coil. Res. Freq. 63Hz. Freq. Resp. to 20KHz. Sens. 86dB. **PRICE £9.99 + £1.00 P&P ea.**
 6" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1" voice coil. Res. Freq. 56Hz. Freq. Resp. to 20KHz. Sens. 89dB. **PRICE £10.99 + £1.50 P&P ea.**
 8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1 1/2" voice coil. Res. Freq. 38Hz. Freq. Resp. to 20KHz. Sens. 89dB. **PRICE £12.99 + £1.50 P&P ea.**
 10" 60 WATT R.M.S. Hi-Fi/Disco etc.
 1 1/4" voice coil. Res. Freq. 35Hz. Freq. Resp. to 15KHz. Sens. 89dB. **PRICE £16.49 + £2.00 P&P.**

PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) **Price: £8.62 + 75p P&P.**
3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) **Price: £14.49 + 75p P&P.**
SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). **Price: £17.82** Transmitter 80 x 50 x 15mm (9/12 volt). **Price: £11.29** P&P + 75p each. S.A.E. for complete list.

POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME, SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER VISA/ACCESS/C.O.D. ACCEPTED

PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E. 28p STAMP FOR CURRENT LIST

BURGLAR ALARM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. **FULLY GUARANTEED.**

Control Unit - Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch - off - test - armed. 30 second exit and entry delay.

Indoor alarm - Electronic swept freq siren 104dB output.

Outdoor Alarm - Electronic swept freq siren 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions. **SAVE £138.00** Usual Price £228.85

BKE's PRICE £89.99 + £4.00 P&P

Why buy a collection of self-assembly boards!

IDEAL for Workshops, Factories, Offices, Home, etc. Supplied ready built.



OMP LINNET LOUDSPEAKERS

The very best in quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinylite with protective corners, grille and carry handle. All models 8 ohms. Full range 45Hz - 20KHz. Size 20" X 15" X 12". Watts R.M.S. per cabinet Sensitivity 1W 1mtr dB

OMP 12-100 Watts 100dB. Price £149.99 per pair.

OMP 12-200 Watts 102dB. Price £199.99 per pair. Delivery, Securicor £8.00 per pair



OMP 19" STEREO RACK AMPS



Professional 19" cased Mos-Fet stereo amps. Used the World over in clubs, pubs, discos etc. With twin Vu meters, twin toroidal power supplies, XLR connections, MF600 Fan cooled. Three models (Ratings R.M.S. into 4ohms). Input Sensitivity 775mV

MF200 (100 + 100)W. £169.00 Securicor
MF400 (200 + 200)W. £228.85 Delivery
MF600 (300 + 300)W. £274.85 £10.00

1 K-WATT SLIDE DIMMER

- * Control loads up to 1Kw
- * Compact Size 4 3/4" X 1" X 2 1/2"
- * Easy snap in fixing through panel/cabinet cut out
- * Insulated plastic case
- * Full wave control using 8 amp triac
- * Conforms to BS800

* Suitable for both resistive and inductive loads. In numerous applications in industry, the home, and disco's, theatres etc. **PRICE £13.99 + 75p P&P**

BSR P295 ELECTRONIC TURNTABLE


* Electronic speed control 45 & 33 1/3 r.p.m. * Plus/Minus variable pitch control * Belt driven * Aluminium platter with strobed rim * Cue lever * Anti-skate (bias device) * Adjustable counter balance * Manual arm * Standard 1/2" cartridge fixings * Supplied complete with cut out template * D.C. Operation 9-14v D.C. 65mA **Price £36.99 - £3.00 P&P.**



ADC Q4 mag. cartridge for above **Price £4.99 ea. P&P 50p.**

PIEZO ELECTRIC TWEETERS MOTOROLA

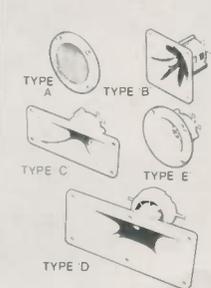
Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series) **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. **Price £4.90 each + 40p P&P**
TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. **Price £5.99 each + 40p P&P**
TYPE 'C' (KSN6016A) 2" X 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. **Price £6.99 each + 40p P&P**
TYPE 'D' (KSN1025A) 2" X 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. **Price £9.99 each + 40p P&P**
TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. **Price £5.99 each + 40p P&P**
LEVEL CONTROL Combines on a recessed mounting plate. Level control and cabinet input jack socket 85 X 85 mm. **Price £3.99 + 40p P&P**


STEREO DISCO MIXER

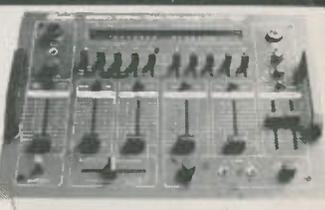STEREO DISCO MIXER with 2 X 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features 5 Inputs with individual faders providing a useful combination of the following - 3 Turntables (Mag), 3 Mics, 4 Line plus Mic with talk over switch, Headphone Monitor, Pan Pot. L & R Master Output controls Output 775mV. Size 360 X 280 X 90mm **Price £134.99 - £3.00 P&P**



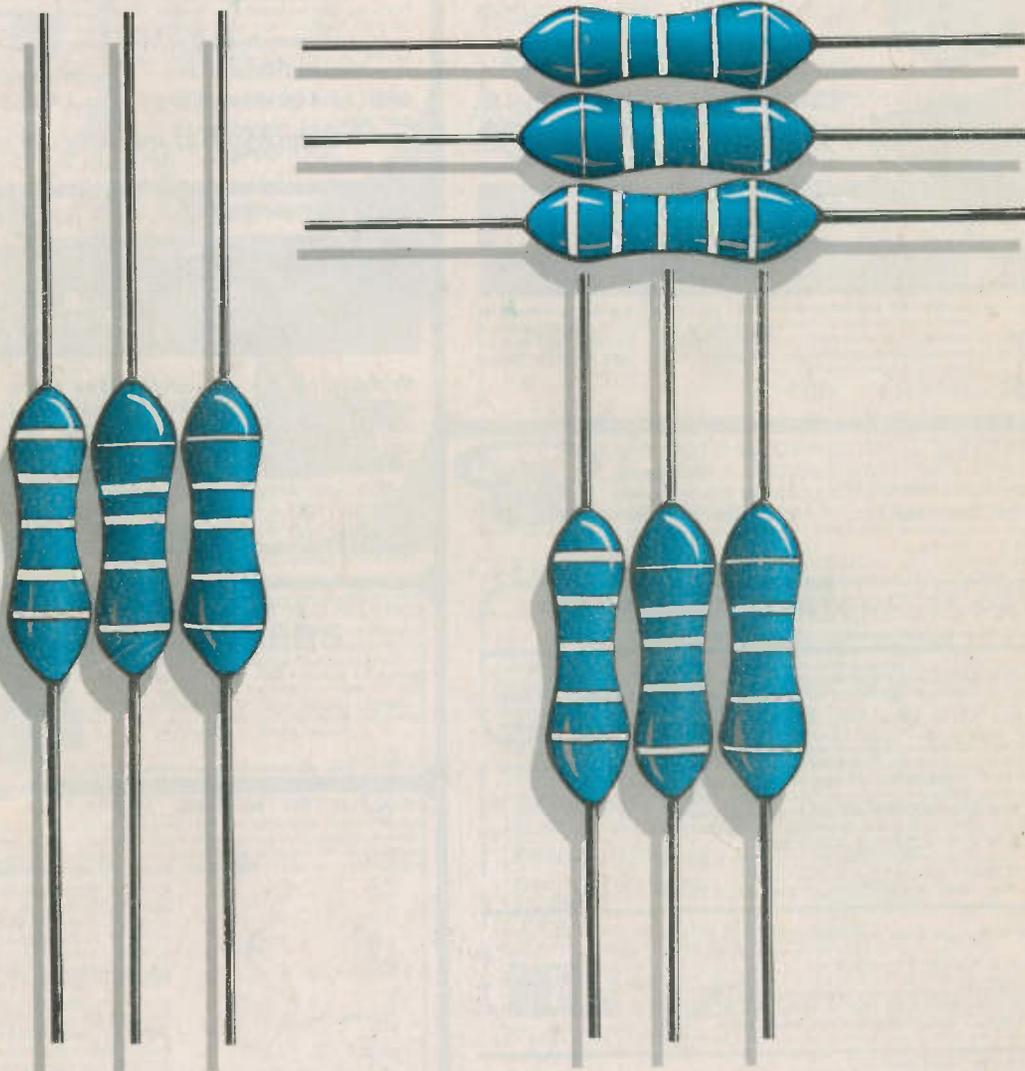B. K. ELECTRONICS Dept PE
 UNIT 5, COMET WAY, SOUTHBEND-ON-SEA,
 ESSEX, SS2 6TR TEL: 0702-527572

**Lowest possible prices?
 Top quality components?
 Fast reliable service?
 Large range?**



Maplin it's irresistible.

Pick up a copy of our new 1986 catalogue from any branch of W.H. Smith for just £1.45.


Or post this coupon now, to receive your copy by post for just £1.45 + 40p p & p. If you live outside the U.K. send £2.50 or 11 International Reply Coupons. I enclose £1.85.

Name

Address

.....

.....

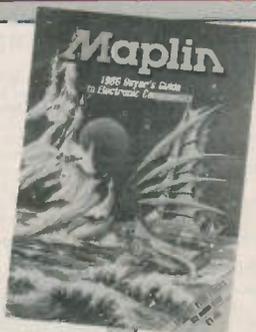

MAPLIN ELECTRONIC SUPPLIES LTD.

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 552911

SHOPS

- BIRMINGHAM Lynton Square, Perry Barr, Tel: 021-356 7292.
- LONDON 159-161 King Street, Hammersmith, W6.
 Telephone: 01-748 0926.
- MANCHESTER 8 Oxford Road, Tel: 061-236 0281.
- SOUTHAMPTON 46-48 Bevois Valley Road, Tel: 0703 225831.
- SOUTHEND 282-284 London Rd, Westcliff-on-Sea, Essex.
 Telephone: 0702-554000

Shops closed all day Monday.