

RECEIVING BAND  $\nabla$  SIGNALS

# Practical Television 13

JULY: 1958

AND TELEVISION TIMES

EDITOR: F.J. CAMM

## Contents


HEATER-CATHODE TUBE SHORTS

ITV IN DIFFICULT AREAS

UNIVERSAL ALIGNMENT METHOD


A 600 Mc/s OSCILLATOR

A CUBICAL AERIAL FOR TV

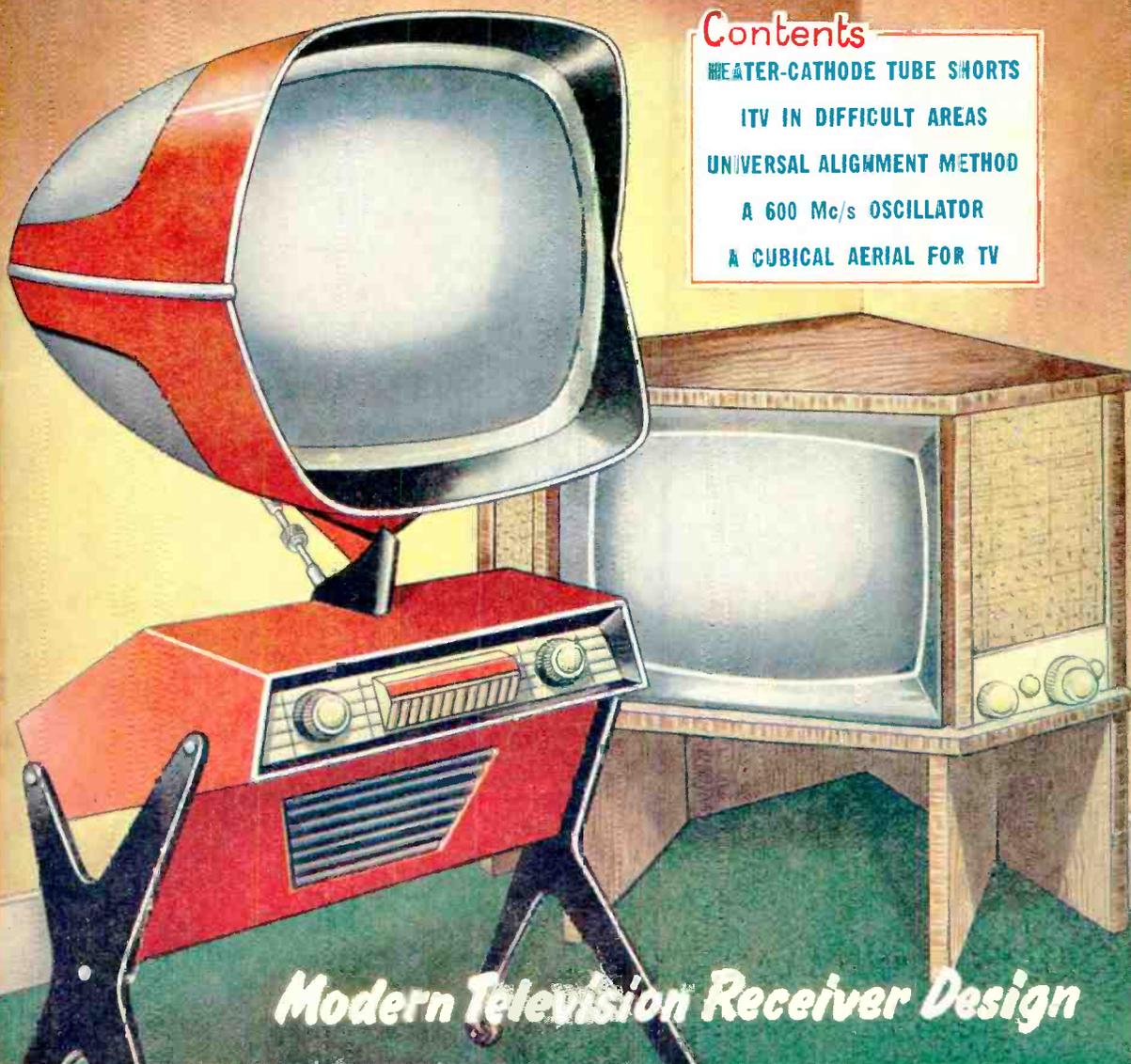

*Modern Television Receiver Design*

# Build your own Aerials...

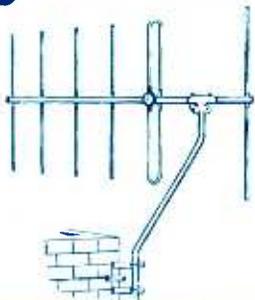

**Fringevision Ltd.**

MARLBOROUGH, WILTS. Phone : 657/8

## AT HOME

**AERIAL FITTINGS FOR BAND III, BAND I & RADIO F.M.**  
Useful formulæ and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above to —

## SOMETHING NEW!!

### A PRE-AMP FOR BOTH I.T.V. AND B.B.C.

Following the success achieved by our Band III Pre-amp, we introduce a combined unit designed to overcome the difficulties experienced in situations where reception of both I.T.V. and B.B.C. is extremely poor.



Units now available :-  
"DUAL BAND"

- ★ Co-ax Inputs for Bands I and III.
- ★ I.T.V.—amplified.
- ★ B.B.C.—amplified.
- ★ Single Output to Receiver.

Price £9.10.0 C.W.O. or C.O.D.

"SINGLE BAND"

- ★ Co-ax Inputs for Bands I and III.
- ★ I.T.V.—amplified.
- ★ B.B.C.—Diplaxed.

★ Single Output to Receiver. Price £6-6-8, C.W.O. or C.O.D. Please state channels required.

Both Units have a high signal to noise ratio, and will produce excellent results in localities where the signal is normally unusable.

Units have Built-in Power Packs 200-50 v. A.C. Dimensions : 6 x 4 x 2½ in. (Fly Lead, 3/6 extra).

**"AIRVISION"**

(Electronic Equipment Manufacturers)

14 BOULTON RD., SOUTHSEA, HANTS.

## TELEVISION TUBES

WE OFFER

**MULLARD — COSSOR — EMITRON**

Etc., From Stock

**12" TUBES - - £5 10.**

**14" MULLARD TUBES £6**

(Or equivalent)

**14" MAZDA TUBES £6 10.**

**17" TUBES - - £7 10.**

Please add 12/6 Carriage and Insurance.

All Tubes Guaranteed for 6 months.

**MARSHALLS for TELEVISION**

131 St. Ann's Road, Tottenham,  
London, N.15.

Callers welcome.

STAmford Hill 3267

# SPECIAL OFFER!!! EY51 10/6

**SMALL  
TYPE  
ONLY**

**BRITISH  
MADE**

**EXPRESS SERVICE !!!**  
C.O.D. ORDERS RECEIVED BY 3.30 P.M., EITHER BY LETTER, PHONE OR WIRE, DESPATCHED THE SAME AFTERNOON, ALL ORDERS RECEIVED BY FIRST POST DESPATCHED SAME DAY.

**ANY ORDER UP TO £10 INSURED AGAINST DAMAGE IN TRANSIT FOR ONLY 6s. EXTRA. ORDERS OVER £10 INSURED FREE.**

IA3	3/-	6AU6	10/6	6L6G	9/6	12AH7	8/-	35/51	12/6	D63	5/-	ECC91	5/6	GZ30	10/6	PCL82	12/6	UBC41	8/6
IA5	6/-	6B4G	6/6	6L18	13/-	12AH8	10/6	35A5	11/-	D77	6/6	ECC80	13/6	GZ32	12/6	PCL83	17/6	UBF80	9/6
IC5	12/6	6B7	10/6	6N7	8/-	12AT6	10/6	35L6GT	9/6	DAC32	11/-	ECC82	13/6	GZ34	14/-	PEN40DD		UBF89	10/6
ID6	10/6	6B8GTM	4/6	6O7G	10/-	12AT7	8/-	35W4	9/6	DAF91	8/-	ECH35	9/6	H30	5/-		25/-	UCC85	10/6
IH5	11/-	6B8M	5/-	6Q7GT	11/-	12AU7	7/6	35Z4	7/6	DAF96	10/-	ECH42	11/-	H63	12/6	PEN45	19/6	UCH42	11/-
IL4	6/6	6BA6	7/6	6R7G	10/-	12AX7	9/-	35Z5GT	9/-	DF33	11/-	ECH81	9/-	HABC80		PEN46	7/6	UCH81	11/6
ILD5	5/-	6BE6	7/6	6SA7GT	8/6	12BA6	9/-	41MTL	8/-	DF91	7/-	ECL80	14/-		13/6	PL82	10/-	UCL82	15/6
ILN5	5/-	6B8E	7/6	6SC7	10/6	12BE6	10/6	50C5	12/6	DF96	10/-	ECL82	12/6	HK90	10/6	PL83	11/6	UF41	9/-
IN5	11/-	6BR7	11/6	6SG7GT	8/-	12E1	30/-	50L6GT	9/6	DH63	10/-	EF36	6/-	HL23	10/6	PM2B	12/6	UF80	10/6
IR5	8/-	6BW6	9/6	6SH7	8/-	12J5GT	4/6	72	4/6	DH76	7/6	EF37A	8/-	HL41	12/6	PM12	6/6	UF85	10/6
IS5	8/-	6BW7	8/-	6S7	8/-	12J7GT	10/6	77	8/-	DH77	8/6	EF39	6/-	HL133DD		PM12M	6/6	UF89	10/6
IT4	7/-	6BX6	8/-	6SK7GT	8/-	12K7GT	7/6	78	8/6	DK91	8/-	EF40	15/-		12/6	PY80	9/-	UL41	10/6
IU5	10/-	6BY7	8/-	6SL7GT	8/-	12K8GT	14/-	80	9/-	DK92	12/6	EF41	9/6	HVR2	20/-	PY81	9/-	UL46	15/-
2A7	10/6	6C4	7/-	6SN7GT	7/6	12Q7GT	7/6	83V	12/6	DK96	12/6	EF42	12/6	HVR2A	6/-	PY82	9/-	UL84	11/6
2D13C	7/6	6C5	6/6	6S57	8/-	12SA7	8/6	85A2	15/-	DL2	15/-	EF50(A)	7/-	KF35	8/6	PY83	9/6	UY41	8/6
2X2	4/6	6C6	6/6	6U4GT	14/-	12SC7	8/6	150B2	15/-	DL33	9/6	EF50(E)	5/-	KL35	8/6	QP21	7/6	UY85	10/6
3A4	7/-	6C8	12/6	6U5G	7/6	12SG7	8/6	220P	10/6	DL66	15/-	EF54	5/-	KT2	5/-	QP25	15/-	V1507	5/-
3A5	12/6	6C9	12/6	6U7G	8/6	12SH7	8/6	807	7/6	DL92	7/6	EF73	10/6	KT33C	10/6	QS150/15		VLS492A	6/-
3B7	12/6	6C10	12/6	6V6G	7/-	12S7	8/6	956	3/-	DL94	9/-	EF80	8/-	KT44	15/-		10/6	VMP4G	15/-
3D6	5/-	6CH6	12/6	6V6GTG	8/-	12SK7	8/6	1203	7/-	DL96	10/-	EF85	8/-	KT63	7/-	QVO4/7	15/-	VP2(7)	12/6
3Q4	7/6	6D6	6/6	6X4	7/-	12SQ7	8/6	4033L	12/6	DL510	10/6	EF86	17/6	KTW61	8/-	R2	10/6	VP4(7)	15/-
3Q5GT	9/6	6E5	12/6	6X5GT	6/6	12SR7	8/6	807	12/6	DM70	8/6	EF89	10/6	KTW62	8/-	R12	10/6	VP13C	7/-
3S4	7/6	6F6G	7/-	6Z4/84	12/6	12YA	10/6	7193	5/-	EAS50	2/-	EF91	7/6	KTW63	8/-	SD6	12/6	VP41	7/6
3V4	9/-	6F6GTM	8/-	6Z5	12/6	14R7	10/6	7475	7/6	EAT76	9/6	EF92	6/6	KTZ41	8/-	SP4(7)	15/-	VR105/30	
5U4G	8/6	6F8	12/6	6/30L2	10/-	14S7	10/6	9002	5/6	EABC80	9/-	EL32	5/6	KTZ63	10/6	SP41	3/6		9/-
5V4G	12/6	6F12	7/6	7A7	12/6	19AQ5	11/-	9003	5/6	EAC91	7/6	EL41	11/-	L63	6/6	SP42	12/6	VR150/30	
5X4G	12/6	6F13	12/6	7B7	8/6	19H1	10/6	9006	6/6	EAF42	10/6	EL42	11/6	LN152	14/-	SP61	3/6		9/-
5Y3G	8/-	6F16	9/6	7C5	8/-	20D1	16/-	AC6PEN	7/6	EB34	2/6	EL81	15/6	LZ319	10/-	SU61	10/6	VT61A	5/6
5Y3GT	8/6	6F17	12/6	7C5	8/-	25L6GT	10/-	AC/HL/		EB41	8/6	EL84	10/6	MH4	7/6	TP22	15/-	VR501	5/6
5Y4	12/6	6F32	10/6	7H7	8/-	25Y5	10/6	DDD	15/-	EB91	6/6	EL91	5/6	MHL4	7/6	U16	12/-	W76	7/6
5Z2	10/6	6G6	7/6	7Q7	9/-	25Y5G	10/6	AC/PA	8/6	EB33	7/6	EM34	10/6	MHLD6	12/6	U18/20	12/6	W81M	6/6
5Z4GT	12/6	6H6GTG	3/6	7S7	10/6	25Z5	10/6	AC/VP1	15/-	EB34	10/6	EM80	10/6	M4	12/6	U22	8/6	X61	12/6
6A8	10/-	6H6GTM	3/6	7Y4	8/-	25Z4G	10/-	AL60	10/6	EBF80	10/6	EM81	10/6	M6	6/6	U25	15/6	X63	10/6
6AB7	8/-	6J5G	5/-	8D2	3/6	2B07	7/6	ATP4	5/6	EBF89	9/6	EN31	34/9	MU14	10/6	U31	10/6	X65	12/6
6AB8	14/-	6J5GTG	5/6	8D3	7/6	30	7/6	AZ31	10/6	EC52	5/6	EY51		OA10	12/6	U43	10/6	X66	12/6
6AC7	6/6	6J5GTG	6/-	9D2	4/-	30C1	10/6	BL63	7/6	EC70	12/6	EY51	(Small)	OA70	5/6	U45	10/6	XD(1.5)	6/6
6AG5	6/6	6J6	5/6	10C1	15/-	30F5	8/-	CK505	6/6	ECC31	15/-	EY51	(Large)	OA71	5/6	U50	8/6	XFW10	6/6
6AJ8	9/-	6J7G	6/-	10F1	19/6	30FL1	10/6	CK506	6/6	ECC32	10/6	EY56	15/6	OC72	30/-	U52	8/6	XFY12	6/6
6AK5	8/-	6J7GT	10/6	10F9	11/6	30L1	9/-	CK523	6/6	ECC33	8/6	EZ35	6/6	P61	3/6	U76	7/6	XH(1.5)	6/6
6AK8	9/-	6K6GT	8/-	10F18	12/6	30P2	13/6	CV63	10/6	ECC35	8/6	EZ40	8/6	P215	10/6	U107	11/10	XSG(1.5)	6/6
6AL5	6/6	6K7G	5/-	10LD3	8/6	30P16	10/-	CV85	12/6	ECC81	8/-	EZ41	10/6	PABC80	15/-	U251	15/-	Y63	7/6
6AM5	5/-	6K7GT	6/-	10LD11	16/9	30PL1	19/6	CV271	10/6	ECC82	7/6	EZ80	9/6	PCC84	9/-	U404	10/6	Z63	10/6
6AM6	7/6	6K8G	8/-	10P13	17/6	31	7/6	CV428	30/-	ECC83	9/-	EZ81	10/6	PCC85	12/6	UABC80		Z66	20/-
6AQ5	8/6	6K8GT/G	11/6	11E3	15/-	33A/158M	DI			ECC84	10/-	FW4/500		PCF80	10/6	UAF42	10/6	Z77	7/6
6AT6	8/6		11/-	12A6	6/6		30/-	D42	10/6	ECC85	9/6			PCF82	12/6	UB41	12/7	Z729	17/6

**NEW METAL RECTIFIERS, FULLY GUARANTEED**

RM-0	6/-	RM-5	24/-	WX6	3/6	14A163	38/-	14RA	2-1-16-1	21/-	18RA	1-1-8-1	4/6	
RM-1	7/-	W4	3/6	14A86	18/-	14B130	35/-	16RC	1-1-16-1	8/6	18RA	1-1-16-1	6/6	
RM-2	7/6	W6	3/6	14A97	25/-	14RA	1-2-8-2	19/-	16RD	2-2-8-1	12/6	18RA	1-2-8-1	11/6
RM-3	9/6	WX3	3/6	14A100	27/-	14RA	1-2-8-3	23/6	16RE	2-1-8-1	8/6	18RD	2-2-8-1	15/-
RM-4	20/-	WX4	3/6	14A124	28/-									

Full technical details free on receipt of S.A.E.

**TERMS OF BUSINESS — CASH WITH ORDER OR C.O.D. ONLY. POST/PACKING CHARGES 6d. PER ITEM; ORDERS VALUE £3 OR MORE POST FREE. EACH ADDITIONAL VALVE 6d. EXTRA. C.O.D. ORDERS 2/6 EXTRA. WE ARE OPEN FOR PERSONAL SHOPPERS MON.-FRI. 8.30-5.30. SATS. 8.30-1 P.M.**

**ALL VALVES, NEW, BOXED, TAX PAID, AND SUBJECT TO MAKERS' GUARANTEE. FIRST GRADE GOODS ONLY, NO SECONDS OR REJECTS. GOODS ARE ONLY SOLD SUBJECT TO OUR TERMS OF BUSINESS, OBTAINABLE FREE ON REQUEST. CATALOGUE OF OVER 1,000 DIFFERENT VALVES 3d.**

## BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS

38 CHALCOT ROAD, LONDON, N.W.1

Primrose 9090

PLEASE ENQUIRE FOR ANY VALVE NOT LISTED. 3d. STAMP PLEASE.

# EMI "HIS MASTER'S VOICE" MARCONIPHONE · COLUMBIA


## Announce NEW PRACTICAL WAY OF LEARNING AT HOME

**NEW** — completely up-to-date methods of giving instruction in a wide range of technical subjects specially designed and arranged for self-study at home under the skilled guidance of our teaching staff.

**NEW** — experimental outfits and lesson manuals are despatched on enrolment and remain the student's property. A tutor is allotted to each student for personal and individual tuition throughout the course.

Radio and television courses, with which specially prepared components are supplied, teach the basic electronic circuits (amplifiers, oscillators, detectors, etc.) and lead, by easy stages, to the complete design and servicing of modern Radio and T/V equipments.

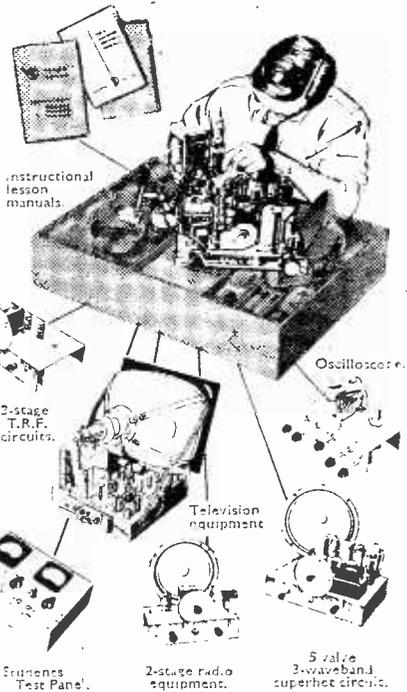If you are studying for an examination, wanting a new hobby or interest, commencing a career in industry or running your own full-time or part-time business, these practical courses are ideal and may be yours for moderate cost. Send off the coupon to-day for a free Brochure giving full details. There is no obligation whatsoever.



*Courses with Equipment*

**RADIO · SHORT WAVE RADIO  
TELEVISION · MECHANICS  
CHEMISTRY · PHOTOGRAPHY  
ELECTRICITY · CARPENTRY  
ELECTRICAL WIRING · 'HI-FI'  
DRAUGHTSMANSHIP · ART etc.**

E.M.I. Institutes  
at Hayes  
England.



# EMI INSTITUTES

Fill in for **FREE BROCHURE**  
E.M.I. INSTITUTES, Dept. 138X, London, W.4.

Name \_\_\_\_\_ Age \_\_\_\_\_  
(If under 21)

Address \_\_\_\_\_  
\_\_\_\_\_


I am interested in the following subject(s) with  
without equipment:  
(We shall not worry you with personal visits)

**FREE**

BLOCK  
CAPS  
PLEASE

JUL 5 8  
10107

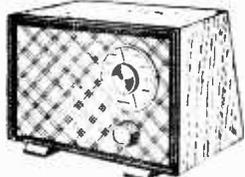*The only Home Study College run by a World-wide industrial organisation*



**THE SKYSEARCHER**

This is a 2-valve plus-metal receiver set useful as an educational set for beginners, also makes a fine second set for the bedroom, work-shop, etc. All parts, less cabinet, chassis and speaker, 19 8. Post and ins. 2 6. Data free with parts or available separately. 1 6. 3-valve battery version also available at the same price.




**TV Masks**  
Latest type grey crystal  
14in 10 - 17in 12 -  
Plus 1 - post.

**Simplex Transistor Kit**



Makes ideal bedroom radio, uses one transistor and one crystal diode. Complete less case 19 6, case 5 - extra, post and ins. 1 6.

**T.V. SERVICE SHEETS**

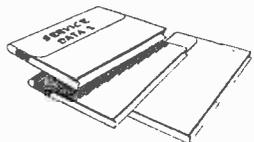

107 sheets covering the most popular post-war Televisions by leading makers—Cosmor, Ekco, Ferguson, Pye, etc. £1 post free.


**Unused and Boxed Valves**

American list, others in stock. Enquire or order C.O.D.

1A4	9-	6C4	6 6	6TH8	12-
1A6	9-	6C6	6 6	6U5	8 6
1A7	12/6	6C8	5-	16V6	9 6
1C5	12/6	6D5	6 6	6X5	7 6
1D7	9-	6E5	9 6	6Z5	15-
1F6	12/6	6F5	9 6	7A7	9 6
1H5	10-	6F8	9 6	7C7	9 6
1LD5	3/6	6G6	7 6	7Y7	9 6
1T1	7/6	6H6	2 6	7Y1	8 6
1R5	7/6	6J5	5-	22Y5	10-
1S3	7/6	6J7	6-	22Z4	9 6
1T5	8-	6K6	7-	22Z6	10 6
2A5	12/6	6L5	9-	27	10-
2A6	12/6	6L6	9-	28D7	3 6
2A7	12/6	6L7	10 6	36	10-
2X2	4/6	6N7	8 6	39 41	10-
3A1	4-	6P8	9-	41	9 6
3A5	7-	6Q6	9-	42	8-
351	6-	6Q7	9-	43	10-
3V4	9-	6R7	9-	57	10-
5V3	8-	6S47	9-	58	10 6
5R1	9 6	6SC7	9-	71	9 6
5U1	8-	6SH7	6-	73	12 6
5Z3	15-	6SJ7	8 6	78	8 6
5Z1	9/6	6SK7	6-	81	8 6
6A7	12/6	6S7	9-	83	12 6
6A8	10-	6SN7	7 6	87	8 6
6B1	5-	6SQ7	9-	1623	10 6
6B3	4-	6S87	9-	954	3 8

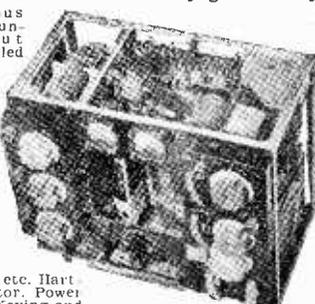
**Famous Transmitter virtually given away**

The famous R1154N—unused but slightly soiled and not tested. Covers 200-500 Kcs. 3-5.5 Mc.s. and 5.5-10 Mc.s. Has unique 'click stop' mechanism (7 stops) and permits selected frequency to be held.



returned to, etc. Hartley Oscillator, Power Amplifier, Keying and Speech. Wonderful breakdown value, meters, relays, switches. Complete with valves—real bargain at 29 6 plus 10 - carriage.

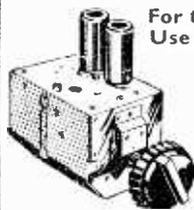**For the Best from Band III Use Our Turret Tuner**



Brand new stock, not surplus, with coils for Band I and III complete with valves. Model 1 I.F. output 33 33 Mc.s. Series heaters Model 2 I.F. output 16 19 Mc.s. Parallel heaters. With instructions and circuit diagram 79 6. With knobs 3 6 extra, post and insurance 2 8.



**Coil Pack Snip**

Covers the Medium Waveband 200-550 metres and two short wavebands 35 120 metres and 14-42 metres, for 465 Kc. tuning coil meter. Extremely well made, supplied complete with diagram of connections. Only 9 6, plus 1 6 post and insurance.

**Super Sensitive (2,000 O.P.V.) Multimeter**

Ranges: D.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000. A.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000. D.C. milliamps 0-5, 0-100, 0-500. Ohms 0-50,000 with internal batteries, 0-500,000 with external batteries. All the essential parts including metal case, 2in. moving coil meter, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions, price 32 6, plus 2 6 post and insurance.

**Latest AVO Testmeter**



Can be yours for only 10 - deposit and 19 payments of 10 - weekly. Like all AVO meters it is a very fine instrument; it has a sensitivity of 10,000 ohms per volt and 19 most useful ranges as follows—D.C. volts 0-1,000 (seven ranges), A.C. volts 0-1,000 (five ranges), D.C. Current 0-1 amp. (5 ranges), resistance 0-2 megs. (2 ranges). (Complete with test leads). Immediate delivery. Cash price £9.10.0.

**FREE GIFT**—All purchasers will receive Range Extender scale and data which add capacity 0.1 m.f. in two ranges. Inductance 0-100 henrys, etc., etc.

**Summer Sale Bargains**

- 7 Valve 5 Waveband superhet chassis. H.F. stage and magic eye. Unused but may be slightly soiled and need servicing—less valves, power pack and tuning scale. Contains really fine coil pack which alone would cost twice what we are asking for the whole unit. Price with circuit diagram, £2.15.0. Carriage and Insurance 7 6.
- 4 Valve Superhet (chassis, Lona and medium wave complete with valves, but not scale. Unused but slightly soiled and may need servicing (no data available). 29 6, plus insurance 3 6.
- 10 Valve Superhet. 1' meter ex Government but unused, complete with valves, easily converted for Band III. 39 6, carriage and packing 7 6.
- Isolation Transformer. 150 watt, mains in, isolated mains out, makes servicing safe. 29 6.
- Filament Transformer. 6.3 volt 34 amps, tapped primary, 8 6.
- Transistor Suitable A.F. or low R.F., new tested, O.K. most circuits 6 6.
- Widge Output Transformer, standard pentode matching. 4 6.
- Widge Output Transformer, special for battery sets, pentode matching. 4 6.
- 14in. T.V. Cabinet by famous maker cost over £1 to make, new and perfect. 15 -, carriage 4 6.
- Metal Model set, 250 v. 60-80 milliamps, ideal for mains set or instrument or to replace that expensive valve. 4 6.
- Constructors' Parcel. 3-valve superhet chassis, 15 x 15 x 2 with three waveband scales, pulleys, drive head, etc., 9 6, plus post and insurance 1 6.
- Toggle Switch. Standard metal body, type with round dolly, fixing ring and on/off indicating plate. 1 5 or 1 2 - doz.
- For Extra Power Plugs. 7.029 three-core cable, 500v. grade. 70 - for 100 yd. coil, carriage 5 -.
- Thin Pavolin Panels. Size 8in. x 5in. 2 4 doz.
- Midget I.F. coils 465 Kc.s but with feed back winding for economy circuits. 6 6 pair.
- Mains Transformer. Standard 230 v. Input 250-0-250 at 80 mA., 6.3 v. at 5 A. 12 6.
- Connecting Wire P.V.C. Covering. All colours. Sale price 2 6 per 100 ft. coil or 5 coils different colours. 10 - the lot.
- 50 Assorted Resistors. Well mixed and useful values; and 1 watt. 5 - for 50.
- Ditto but 1 watt. 6 6 for 50.
- .1 mfd 350. Small tubular metal case condensers made by DuBilier. 2 6 doz.
- Loudspeaker 8in. energised field. 9 6, carriage 3 6.
- 6ft. Untearable Mains Lead. Type of lead fitted to electric razors makes fine lead for test meters and any other devices where subject to continuous bending. Twin figures eight construction, soft cream P.V.C. covered. Normally costs 2 - per yard—we offer three leads for 2 -.
- Welding Transformer. 12v.-50 amp. continuous rating—intermittent rating for spot welding—exceeds 2,000 amps. 45 -, carriage and packing 5 -.
- Metal Rectifier. Equivalent of RM5-250 mA., 250 v., 12 6.
- Cathode Ray Tube VCR517. 7 6, carriage, etc. 3 6.
- Thermal Delay Vacuum Relay with book of interesting circuits 4 6.

**ELECTRONIC PRECISION EQUIPMENT, LTD.**

Post orders are dealt with from Eastbourne, so for prompt attention please post your orders to 66, Grove Road, Eastbourne, marked Department 7.

42-46, Windmill Hill, Ruislip, Middx. 66, Grove Road, Eastbourne, Sussex. 29, Stroud Green Rd., 268, London, Road Finchbury Park, N. London. PHONE: ARCHWAY 1049 Phone: CRO. 6558  
Half day, Wednesday. Half day, Saturday. Half day, Thursday. Half day, Wed.

# CERAMICS

## for all electronic applications

Silvered Ceramic Condensers cover a variety of useful shapes, including Pearls, Discs, Beads and Tubes, and have many applications in R.F. circuits — particularly where ultra-high frequencies are present, when their low inductance and excellent power factor are of special advantage. A wide choice of negative and positive temperature co-efficients permits the temperature compensation of other components, and frequency stabilisation of tuned circuits.

### HI-K CERAMIC DISCS

for decoupling purposes in T.V. and spark suppression in small electrical apparatus—extremely low inductances. Up to 10,000 pF at 500 v. D.C. working. Finished in a moisture-resisting compound that does not soften or crack up to 100°C.

### LOW-K TUBULARS

with the choice of four temperature co-efficients and a wide range of capacity values, serve many purposes in general circuitry.


### HI-K TUBULARS

combine high capacity with small physical size: used widely as by-pass condensers in T.V. and other H.F. receivers where low inductance is of special value.
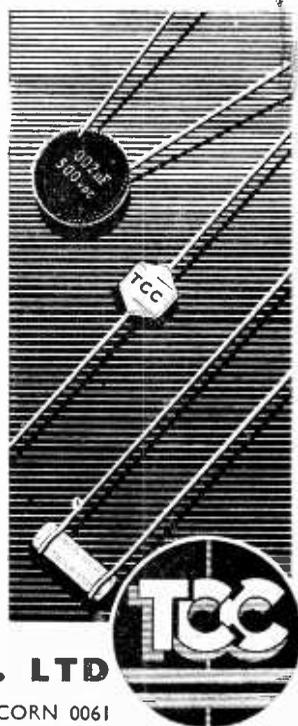
### LOW-K PEARLS

of up to 10 pF capacity and

**LOW-K DISCS** of up to 50 pF. with high negative temperature co-efficient permitting compensation of other components and frequency stabilisation in tuned circuits.



## THE TELEGRAPH CONDENSER CO. LTD


RADIO DIVISION: NORTH ACTON · LONDON · W.3 · Telephone: ACORN 0061



Regd. Trade Mark

## Signal Generator
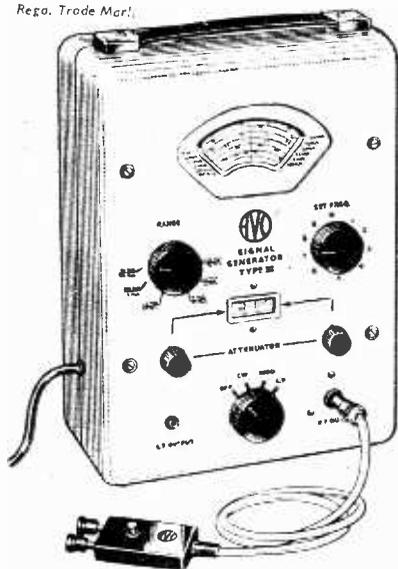
### FOR BANDS I, II & III ... ON FUNDAMENTALS



#### The "AVO" Signal Generator Type III

An inexpensive A.M. Signal Generator of entirely new design, for the Service Engineer. Provides six frequency bands covering 150 kc s-220 Mc s. Accuracy  $\pm 1\%$ .

150 kc/s — 500 kc/s	} Continuous wave or modulated at 1,000 c/s. L.F. signal available for test purposes.
500 kc/s — 1.6 Mc/s	
1.6 Mc/s — 5.5 Mc/s	
5.5 Mc/s — 18 Mc/s	
18 Mc/s — 70 Mc/s	
70 Mc/s — 220 Mc/s	

A new type of attenuator ensures close adherence of the output to the attenuator calibration. The instrument provides a force output of 250 mV, whilst the following outputs are available via the attenuator:—

Minimum to 100  $\mu$ V,  $\times 1$ ,  $\times 10$ ,  $\times 100$ ,  $\times 1,000$ .  
Output impedances—80  $\Omega$ , 200  $\Omega$  and 400  $\Omega$ .

This instrument operates on 100-120, 200-267V, 50-60 c/s A.C. mains. It is light and compact and employs double-screening to ensure minimum radiation.

Write for a free copy of the latest Comprehensive Guide to "Avo" Instruments.

List Price **£33**

**AVO LTD.**


Telephone: VICToria 3404 (9 lines)

AVOCET HOUSE · 92-96 VAUXHALL BRIDGE ROAD  
LONDON · S.W.1





# Practical Television

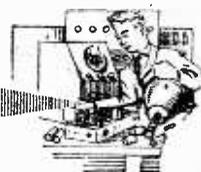

## & TELEVISION TIMES

Editor : F. J. CAMM

Vol. 8 No. 96

EVERY MONTH

JULY, 1958

## TELEVIEWS

### BBC v. ITV

ACCORDING to Television Audience Measurement (TAM), during April 70 per cent. of the total time spent viewing television in the homes which have a choice of BBC and ITV was devoted to watching ITV, or 3 per cent. more than in March. This does not necessarily mean that ITV are putting out programmes which appeal to the majority, but it can mean that their programmes are appealing to a higher proportion of the teenage group. Much as we may criticise BBC programmes, it cannot be said that the quality of the ITV programmes is better than the BBC. The BBC programmes, in general, appeal to a more adult audience, and because of lack of advertising, especially advertising of a cheapjack nature (and much of the ITV advertising matter comes within this description), their programmes are more compact and cohesive. The ITV programmes are no more advanced technically than the BBC. The latter, in any case, has a quarter of a century of experience behind it.

It would be a mistake, we think, for the BBC to change the style of its programmes in order to recapture some of its loss of audience, and thus start a sort of war with ITV. Experience has shown that pop singers are very popular but only for a very short time and it may be that the public will tire equally quickly of advertising programmes.

### SALES OF TV RECEIVERS

IN March, 1958, the last period for which figures are available, sales of TV receivers by retailers to the public were above those for March, 1957. But the sales of radio receivers and radiograms were lower. During March, 1958, 88,000 TV receivers were sold, 82,000 radio receivers and 16,000 radiograms. Thus, TV shows an increase of 11 per cent. over the comparable period for 1957, whilst radio shows a decrease of 1 per cent. and radiograms 20 per cent. In the first quarter of 1958, the total sales of TV receivers were 318,000.

### ANOTHER PRACTICAL TV SPONSORED LECTURE

READERS will remember that last year this journal, in conjunction with Mullard Ltd., sponsored at the Caxton Hall a film show of radio and television interest. There have been numerous requests for a similar yet different programme and we are pleased to announce that arrangements are now completed for the evening of Thursday, January 22nd, 1959. There will be no charge for admission, but the seating capacity is limited to 500. Readers wishing to attend should apply now. —F. J. C.

Our next issue, dated August, will be published on July 22nd.

Editorial and Advertisement Offices :  
PRACTICAL TELEVISION

George Newnes, Ltd., Tower House,  
Southampton Street, Strand, W.C.2.

© George Newnes Ltd., 1958.

Phone : Temple Bar 4363.

Telegrams : Newnes, Rand, London.  
Registered at the G.P.O. for transmission  
by Canadian Magazine Post.

### SUBSCRIPTION RATES

including postage for one year

Inland - - 19s. per annum  
Abroad - - 17s. 6d. per annum  
Canada - - - 16s. per annum

### CONTENTS:

	Page
Televiews ... ..	561
A TV Pattern Generator ...	562
Receiving Band V Signals... 567	567
ITV in Difficult Areas ...	570
Heater-cathode Tube	
Shorts ... ..	574
The Cubical Quad Aerial ...	576
A Universal Alignment	
Method ... ..	580
Modern TV Receiver Design	582
Servicing Television Re-	
ceivers ... ..	585
Underneath the Dipole ...	589
Telenews ... ..	593
Correspondence ... ..	597
News From The Trade ...	598
Your Problems Solved ...	601

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles, published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

THE oscillator is a modified "cathode Hartley" circuit, the modifications of interest being the inclusion of R1 in the oscillatory circuit and the omission of the usual grid condenser and leak for automatic bias. The purpose of R1 is to stabilise the output of the oscillator, so that to whatever frequency L and C are tuned, that frequency is maintained accurately and at constant amplitude. Its value depends on the Q of the LC circuit, and with the coils to be described shortly a maximum value of 10,000 ohms was found to be appropriate. The resistance is made variable in order to adjust R.F. amplitude.


R2 and the radio frequency choke are arranged to have together a D.C. resistance about right for the standing bias needed on the grid of the valve. The idea is to operate the valve under Class A conditions as nearly as possible, and so a total resistance of about 200 ohms is required for the valve specified—half an ECC81. The R.F. choke should have a self-resonant frequency of less than 100 kc/s however, and if the choke used is big enough for this it may have enough D.C. resistance without the inclusion of R2. If on the other hand its resistance is appreciably higher than 300 ohms, a suitable choke will have to be wound instead. It is better to have rather too high than too low a resistance, so that the valve cuts off rather than runs into grid current under oscillatory condition.

It is important to realise that this oscillator must operate only between the line sync pulses. During sync pulses it has to be cut off altogether. What is more, each time it oscillates the oscillations must start in the same phase. The reason for this is the need for vertical bars to traverse the whole length of the TV picture. Any delay in starting oscillations would result in an irregular edge to the vertical bars, and while this would not matter unduly if picture line linearity were the only quality to be investigated, it would rule out any possibility of the apparatus giving "fine detail" bars at 3 Mc/s. It is for this reason that the more usual grid condenser and leak have been omitted and a "keying" stage (stage e) incorporated.

**The Keying Stage (Stage e)**

The other half of the ECC81 is connected as shown in Fig. 8. The operation is simple enough. When V1 grid is positive V1 conducts heavily and damps the LC circuit so that oscillations stop. When V1 grid is driven negative V1 is cut off, V1 cathode drops sharply in potential—with the

# A TV Pattern Generator

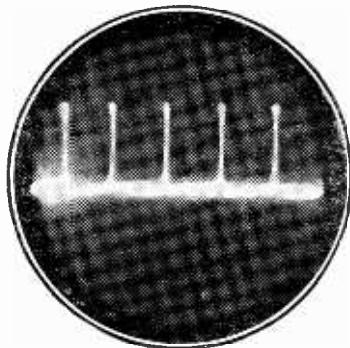

This Useful Apparatus Duplicates the BBC Waveform for Test Purposes. By D. R. Bowman  
(Continued from page 532 June issue)

grid of V2. The condenser C cannot change its charge instantaneously however and it is thus left at a positive potential—i.e. at the peak of a cycle. The result is that C always starts off by discharging (through L) and therefore oscillation always begins in the same phase.

If the output from the gating stage is now applied to the grid of the "keying" stage, the oscillator will function in a series of bursts of R.F. oscillation coincident with the duration of line scan pulses and will be cut off for the rest of the time.

**Combining R.F. Oscillations and Sync Pulses (Stage g)**

The apparatus so far described has succeeded in producing the necessary elements, and it now remains for these to be combined into a form suitable for modulating the main R.F. oscillator. It has to be remembered that at the receiver 30 per cent. modulation in black level; it

therefore follows that the sync pulses must occupy the first 30 per cent. of the modulation envelope, the R.F. signal the remaining 70 per cent. The problem of combining the R.F. and sync pulses thus involves clamping both these signals to a definite level.

This is the first that has been heard of clamping or D.C. restoration in this circuit; the reason is that, so far, all the clamping needed has been at zero level and the grid of a triode or other valve has been suitable. In this case clamping has to be effected at a level other than zero, so a clamp diode must shortly figure in the circuit.

Fig. 10 shows the long-tailed pentode pair used


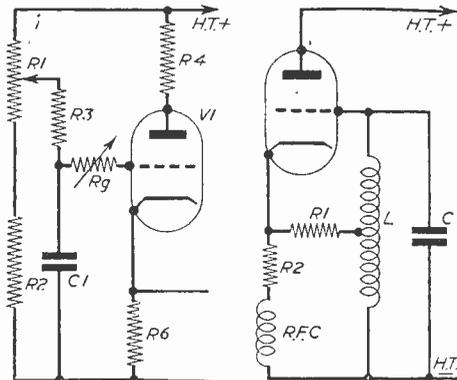


Fig. 6. (Left).—Modified Fig. 2, to give variable fly-back time. Fig. 7. (Right).—R.F. oscillator for vertical bar generation (see previous article).

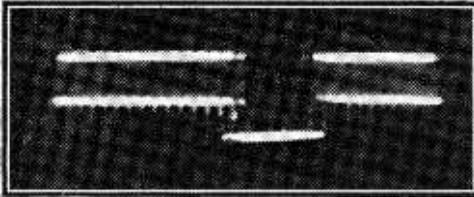



Details of the frame sync pulse. The interruption of the R.F. by each line pulse can be seen in this illustration



Another view of the final wave-form shown on page 563.

The vertical bar generator and the associated keying stage should be totally enclosed in a good screening can—coils, switch, etc. The adjustment of VR2 can enable square-topped R.F. to be developed in the gating stage, but the harmonics so generated can be contained easily by screened leads at P and Q (in the main circuit diagram). If VR2 is adjusted to give sine waves only, very few harmonics are generated as the ECC81 stage is running under very nearly Class A conditions.

The multivibrators give very little trouble, about the only special precaution needed being to adhere to a logical layout. The phase-splitter stage may be offset from the three 6SN7's in line, and is then conveniently placed for supplying input to the gating stage (d). Fig. 9 shows the layout recommended, looking down on top of the chassis from above.

**Power Supplies**

A very well-smoothed power supply is needed for the H.T. input. It should consist of at least two filter sections, and a final smoothing capacitor of 100  $\mu$ F or more is not too much. It is quite important that no hum modulation occurs, and a ripple of  $\frac{1}{2}$  volt or less must be the aim. Prefer-

ably, too, the power pack should be stabilised, because variations in H.T. voltage can and do cause material variations in multivibrator speed. About 50 mA at 250 v. is the supply current, and R50 should be so chosen that the voltages given on the complete circuit diagram are obtained. Approximately 1,000 ohms 3 watt will be needed.

**Alternative Components and Valves**

Some readers may wish to use "near values" for some components, so it is fair to state what limits must be imposed. C1, C3 and C5 must be within the normal manufacturing tolerance unless the constructor is prepared to re-design the multivibrators. With C4 and C6 rather smaller values may be used—but not much smaller and certainly not larger. R7 is fairly critical, but 4.7 K. will do instead and doubtless a 5.6 K. would also suffice. R24 and R27 are not quite so critical, but too much departure is not recommended. R6, R11,


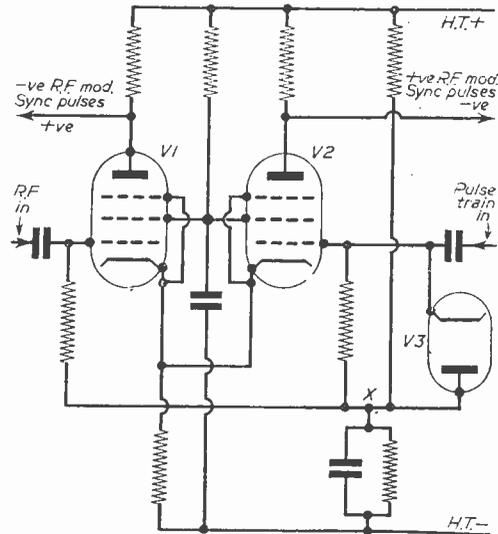


Fig. 10.—Pulse mixing stage.

R18 and R26 may be 20 per cent. tolerance, but R10 and R12 should preferably be matched to within 5 per cent. from the constructor's stock; this is more important than the actual value.

R31 controls the size of the sync pulses and 1.8 K is the "design centre." It may need a little alteration depending on how good or how poor the X65's are. R39 and R42 should be matched from stock to within 10 per cent., but the actual value is not important within 20 per cent.

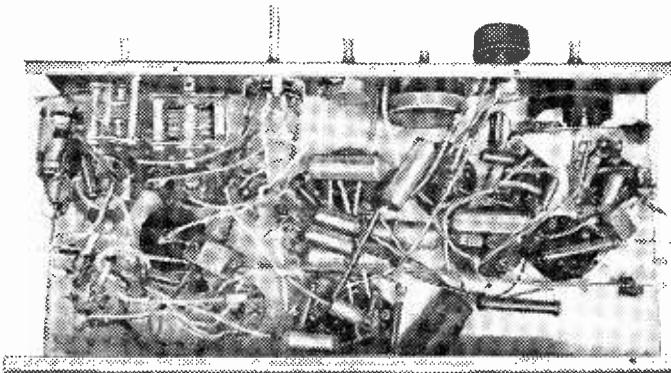Capacitors C2, C7, C8, C9, C10, C13, C16, C19, C21, C23 may all be larger than that specified—by as much as 100 per cent. if convenient—but should not be much smaller. All the electrolytic capacitors may be of higher value if handy.



An underside view of the Generator.

Concerning valves, the query is certain to be raised whether miniature valves may be used instead to get a smaller apparatus. The 6J6 is an attractive possible substitute for the 6SN7, and if used might be even an improvement. If this is done, some change in R7 may be needed. Certainly a 6C4 could be used instead of the 6J5 without component change.

In the gating stage, the X65's have been used because they were available to the writer. X79's should be usable instead with little current change, apart from ensuring that the screen voltage is right. Pentode substitutes for the X65's are not recommended because this would entail major changes in the design of the gating stage. 6AM6 valves should be usable in stage (g) (V7 and V8), but R40 may need adjustment. A 6AM6 might be suitable instead of the EF50 in the final stage, though re-design might be needed; at all events the suppressor characteristic should be plotted and R47 altered if necessary to suit.

**Setting Up the Circuit**

This circuit is not difficult to adjust, providing an oscilloscope is available. The following procedure assumes one is being used.

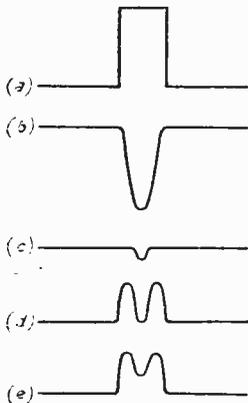


Fig. 11.—Variation of waveforms referred to in the text.

(1) Remove the two X65 valves and the ECC81.

(2) Set the oscilloscope to "external sync" and inject 50 c.p.s mains.

(3) Apply mains input to the Y amplifier terminals, using 6.3 or 4 v. and adjust the timebase to display three or four complete cycles.

(4) Adjust the sync control until the trace barely locks. Remove Y input.

(5) Connect Y input to the point labelled GATE B2 on the circuit diagram, and adjust R21 until V4 is running at exactly 50 c.p.s. No sync, or very little, should be needed. If difficulty is found in getting an exact lock to 50 c.p.s use 100,000 ohms (R50) inserted as shown in the circuit diagram.

(6) Increase the oscilloscope timebase speed until just two V4 pulses are seen. Change sync from "external" to "work" and so allow V4 to control timebase synchronisation.

(7) Adjust sync control for a bare lock.

(8) Adjust R15 until 14 or 15 pips are seen between the 50 c.p.s pulses.

(9) Remove oscilloscope input from "Gate B2" and connect through 50-100 pF condenser to V3 second anode (R19). Adjust Y amplifier to get

good amplitude, and reduce the connecting condenser as far as possible while still getting pips 1/2 in. high.

TABLE 2—COIL CONSTRUCTION

L1—600 turns No. 34 s.w.g. enam. tapped at 300 turns. Windings pile-wound between cheeks 1/2 in. apart. Aladdin former 0.4 in. diameter with iron dust slug. Adjust iron core so that with 500 pF in parallel resonance indicator shows 100 kc/s.
L2—134 turns in 4 layers, 35, 34, 33 and 32 turns, centre tapped as nearly as possible. No. 34 s.w.g. enamelled wire. Iron core adjusted with 500 pF in parallel to give resonance at 500 kc/s. Same former.
L3, L4, L5—36 turns No. 36 gauge enam. close-wound (L4), one end interleaved with 15 turns No. 36 gauge wire (L3). Five turns No. 24 gauge wire spaced one diameter (L5) separated from "cold" (interleaved) end by 1/16 in. Former 0.3 in. dia. with "purple" iron core.

TABLE 3.—R.F. OUTPUT RANGES (APPROXIMATE)

Fundamental 7-16 Mc/s	2nd harmonic 14-32 Mc/s	3rd harmonic 21-48 Mc/s	4th harmonic 28-64 Mc/s	5th harmonic 35-80 Mc/s
--------------------------	----------------------------	----------------------------	----------------------------	----------------------------

(10) Increase oscilloscope timebase speed until two pips from V3 are visible, adjusting sync for a base lock.

(11) Adjust R1 until 15 or 14 pips are visible between the V3 pips.

The multivibrators should now be running at the correct speeds.

(12) Replace the ECC81, and remove V4.

(13) Connect oscilloscope Y amplifier input to V5-V6 anodes, and adjust timebase speed to about 50 per sec. Check that practically nothing is seen of pips at all. If large pips are seen, even at small Y amplifier setting, check the X65's for goodness. Small pips may indicate not quite equal amplification by the separate X65's, or small differences in the waveforms from the phase-splitter anode and cathode. These do not matter much, especially if they are in pairs, but whole pips of considerable amplitude indicate some fault. Fig. 11 shows what is acceptable generally; if (a) and (b) (derived from V2 cathode and anode respectively) are of slightly different amplitude, an output of (c), (d) or (e) may be obtained.

(14) Replace V4. Set oscilloscope timebase to about 10 sweeps per sec. (just flickering). Connect Y amplifier, set at low gain, to cathode end of R.F.C. (stage f, V9) through 50 pF condenser sync amplifier at minimum—the waveform now will only by a miracle give proper sync and it is not worth the trouble; careful adjustment of speed

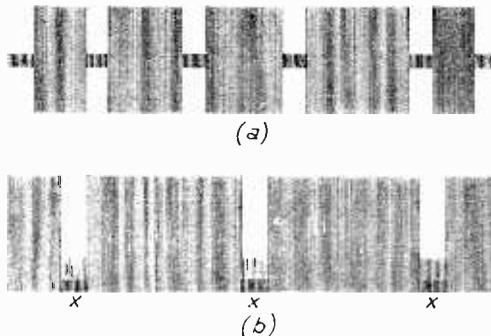


Fig. 12.—Final waveforms.

will keep the trace steady enough to see. Preferably, set S1 to top frequency—about 1 Mc/s or more. Fig. 12 (a) shows the waveform produced.

(15) Transfer the oscilloscope Y input to anode of V7. Fig. 12 (b) should now be seen. Check that the R.F. occupies 70 per cent. and the sync pulses 30 per cent. of the vertical height of the trace. Adjust the value of R7 if necessary, but try adjusting VR2 first.

(16) Transfer the oscilloscope to V5-V6 anode. Set the oscilloscope to about 500 sweeps per sec. and check line pulses. Set sweep to 50 c.p.s. and investigate the width of the frame sync pulses (Fig. 12 (b) "x"); each should contain 6-10 line pulses inverted; to correct, adjust VR1.

(17) Connect output of C25 to the input of a TV receiver known to be good; tune C24 and C25 for raster. Set S1 to low frequency, and adjust VR2 for best definition of the vertical bars displayed. Check over all settings of S1 and

C15. At this stage there is little to go wrong, and the generator should be found to "go like a bomb." Here it is worth while listening on a sound receiver to this "vision" signal; an exact audible lock to 50 c.p.s. can easily be obtained.

Besides its primary use as a pattern generator, this device can be used as a very stable source of accurate square pulses of a good range of frequency. These are often needed in the experimenter's laboratory, and for those who intend to use the multivibrators only for such a purpose only one word of advice is offered—use a cathode-follower after each multivibrator.

The amateur may also find the vertical bar generator circuit a highly stable master-oscillator for many purposes. The need here is to keep VR2 as high as will allow of oscillation at all. The keying stage is also recommended; if used with a morse key, closure of the key should connect the grid of the keying stage to about 20 volts negative.

**SOUTHERN TELEVISION** studios are at the Television Centre, Southampton, formerly the Plaza cinema which has been very extensively modified. The trans-

mitter, built on a commanding site on Chillerton Down, Isle of Wight, will be conveniently placed to give service to the 2½ million inhabitants of the D-shaped reception area. The transmitter is a 4 kW Marconi Wireless Telegraph Co. design and construction fed to an aerial with a gain of x25 towards the land, and hence the E.R.P. will be approximately 100 kW. The aerial is erected on a mast 700ft. high at a point 550ft. above O.D. Channel II is used. It is expected to cover beyond Weymouth in the west, Brighton in the east and Newbury in the north, at the extent of the service area. A standby transmitter of similar power will be installed, and the aerial is arranged for parallel feed by the two transmitters to separate halves should such an arrangement be ultimately required, which would double the power.

### The Studios

The theatre building has been used as a shell and houses two studios of 3,250 sq. ft. and 600 sq. ft. respectively in what was formerly the auditorium. There is also a small booth for an announcer in picture. The former stage houses dressing rooms and offices, the foyer more offices.

### The Main Stage

The main stage is equipped with four E.M.I. cameras (C.P.S. Emitron) and there are spacious control rooms.

The vision control room has a partition for segregating the camera control and lighting control area from the main vision control staff; it is elevated about 5ft. above the studio floor. A sound control room with a sliding partition is adjacent. M.W.T. sound equipment is provided, with echo and fold-back facilities.

## Southern Television

### TECHNICAL DETAILS

Common studio equipment includes Mole Richardson microphone booms, Vinten "Pathfinders" and "Pedestals" and Cintel picture monitors.

The announcers' booth will be equipped with a M.W.T. studio vidicon feeding direct to master control. The sound channel includes an advanced type of limiter amplifier (M.W.T.) to simplify sound control.

### Telecine Facilities

A large telecine area will be ultimately equipped with four Cintel multiplexed flying spot, optically compensated scanners. These are flying spot machines and hence allow preview of associated sources during transmission. The total machines involved are four 35mm., and four 16mm. and two slide scanners, grouped as four units. The telecine area also houses a combined clock and caption device incorporating a M.W.T. industrial camera. When this is switched on an associated tape deck for sound is activated, Gramophone turntables are also provided in this area.

### O.B. Facilities and Links

An O.B. vehicle of ample size is provided with E.M.I. cameras (C.P.S. Emitron) and their associated equipment, as it is expected to range widely over the area for O.B.s. Three modern E.M.I. (ML4a) Links are provided on a frequency in the 7,000 Mc/s range. Communications are by Pye "Ranger" 15 watt equipment. Owing to the situation of the studios in a saucer shaped depression, a M.W.T. BD 40J Link is available for the relatively short run home.

### Film Handling

Film handling is carried on by a department with 16mm. and 35mm. projection facilities, cutting and editing equipment, magnetic striped 16mm. camera equipment and rapid processing plant.

# Receiving Band V Signals

A 600 MC/S OSCILLATOR FOR BAND V

By D. R. Bowman

**L**AST November the BBC began V.H.F. television broadcasting experiments on the present 405 line standard; vision was on 654.25 Mc/s and sound on 650.75 Mc/s. In April this year the 625 line standard was due to be adopted, with vision on the same frequency and sound—frequency modulated at  $\pm 50$  kc/s—on 659.75 Mc/s.

Experimenters within the "optical" range of the Crystal Palace aerials will no doubt wish to attempt reception of these new broadcasts, and the oscillator here described may be of help to those who wish to "get started" in this direction.

It will be realised that reception of signals in the 650 Mc/s range represents about the limit at which more or less conventional valves will work. At higher frequencies disc-seal or "lighthouse" valves have to be used, while above about 1500 Mc/s the klystron is the device of choice as a local oscillator. This sort of thing gets rather far from the pocket of the average experimenter, even if his technical knowledge and skill—not to mention patience—are not too far stretched by such techniques. However, those bridges will no doubt be crossed when we come to them; for the present, conventional or near-conventional methods and apparatus may be used, even for the frequencies of the new transmissions.

The experimental receiver of choice at the moment will consist of a superheterodyne circuit comprising a "front end" of oscillator and crystal mixer. Following this will be either an I.F. amplifier operating at about 60 Mc/s or, using the double superheterodyne, a R.F. and mixer stage accepting input at about 100 Mc/s with a conventional I.F. amplifier at 10-40 Mc/s. The latter enables current V.H.F. (Band II) receivers to be pressed into service in preliminary work on Band V.

## R.F. Amplification

R.F. stages are omitted because of the difficulty in amplifying at 600 Mc/s and over. Though some gain can be obtained by the use of suitable triodes in suitable circuits, one is unlikely to "get started" in this way. The silicon crystal mixer is entirely satisfactory as a first stage.

The oscillator stage is important, not only as the means of converting R.F. at 660 Mc/s to a manageable I.F., but also because it is the source of nearly all the noise generated by the receiver. It must be stable in frequency—not a simple matter to arrange.

In deciding on the source of oscillation more than one choice is open. For a received frequency of 659.75 Mc/s the requirement is plainly for a 600 Mc/s source rather than one above the signal frequency. It may be generated directly, or an oscillator may be run at 200 or 300 Mc/s using third or second harmonics respectively for supply to the mixer. In the interests of frequency stability a crystal-controlled oscillator working at 30 Mc/s or so, followed by several multiplying stages, has strong claims to consideration.

For simplicity—among other reasons—the oscillator chosen consists of a single triode operating at about 600 Mc/s. With due care its output is sufficient—over 3 volts—and its frequency stability good enough to enable the sound transmission to be heard without noticeable drift (after a ten minute "warm-up" period) when fed into the V.H.F. receiver described in *Practical Wireless*, December, 1955. For this purpose the receiver input was slightly re-adjusted to accept a lower frequency R.F. input. Since the oscillator works at a fixed frequency, the I.F. amplifier has in any case to be adjustable to receive whatever I.F. is produced.

## The Circuit

Fig. 1 shows the theoretical diagram. The valve is an Acorn, type 955, and the transmission lines L1 and L2 consist, in the final state of the oscillator, of pieces of 6 B.A. copper rod. C1 is 25 pF ceramic N700K, while C2 and C3 are 50 pF silver-mica. R is 22,000 ohms. The R.F. chokes consist of about 10 turns of No. 22 gauge tinned copper wire (bare), with turns spaced by the wire diameter. Three such chokes are needed; they are all self-supporting, and the former on which they are wound is a half-watt resistor 0.2in. diameter.

This is readily seen to be a conventional Lecher-line circuit. It oscillates readily and the important details are the constructional ones, which are now given.

## Construction

The materials required are a piece of copper sheet  $4\frac{1}{2}$ in.  $\times$  2in., about 3in. of 6 B.A. copper


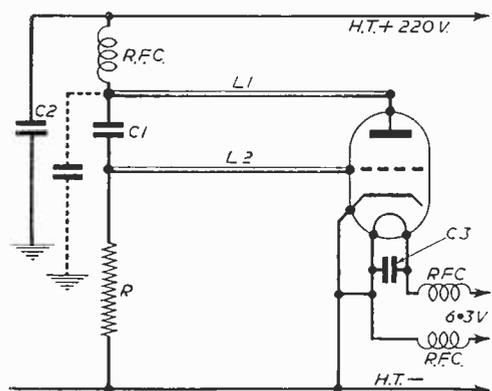


Fig. 1.—The theoretical diagram of the oscillator.

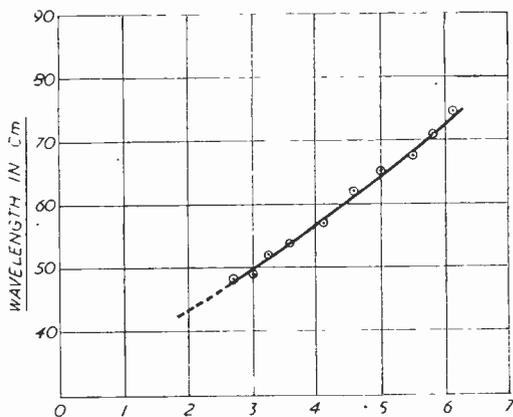(or brass) rod, a three-tag board on feet for mounting at right-angles to a chassis, a soldering tag, an insulated tag (chassis mounting) and the components given above. In addition, silver-plating apparatus, as described in PRACTICAL



LECHER LINE LENGTH IN Cm.  
(This length includes valve pins, up to the glass, connections to lecher lines, and length of connecting leads of condenser C<sub>1</sub>)

Fig. 2.—Graph compiled by the author.

TELEVISION, August, 1957, is needed, and some No. 22 s.w.g. and 20 s.w.g. tinned copper wire, together with a piece of Perspex sheet  $1\frac{1}{2}$  in.  $\times$  1 in. 10-12 cm. of tinned copper wire, No. 20 s.w.g., are straightened carefully. This is best done by fixing one end of a much larger piece to a firm support, such as a door-knob, and pulling hard on the other end until it "gives" a little. The 12 cm. length is then snipped into halves.

An Acorn valve, type 955, is then prepared as follows. If the electrodes are already brightly tinned, only burnishing is needed. If they are dull or not tinned they are scraped carefully with a sharp knife until bright. An instrument-type soldering iron is brought to as high a temperature as possible without "burning"; auxiliary heating is necessary and this is supplied by a gas jet or a small blowlamp. The end 5mm. of one of the Lecher wires, 20 s.w.g. wire, prepared as above, is next tinned.

Have ready a piece of cotton-wool soaked in water. With the tinned end of one of the Lecher wires still in contact with the hot iron, bring it up to the *inside* of the anode pin of the 955 and solder on. This should take half a second or less, and the wet cotton-wool is then placed on to the join to give instant cooling. Repeat the process with the other Lecher

wire, soldering this time to the *inside* of the grid pin of the Acorn. Before these operations are performed sufficient practice needs to be had with oddments of wire: the valve only needs to be cracked once to be useless.


Holding the anode and grid pins, in turn, with a pair of pliers, bend the Lecher wires so that they run parallel. They should now be about 1 cm. to 1.5 cm. apart.

Next, polish the copper sheet with metal polish and bend the ends over to form a chassis  $3\frac{1}{2}$  in.  $\times$  2 in. Wash the chassis now very thoroughly in detergent and hot water, swabbing firmly with cotton-wool. After a light pickling in dilute nitric acid (1 part acid to 3 parts water) silver plate heavily. At the same time, and in the same way, silver plate 7 cm. of No. 6 B.A. copper or brass rod. If preferred, after the plating operation, polish both chassis and rod with *plate* polish (not metal polish).

Fix the 3-tag strip to one end of the chassis and, using the technique described previously, solder the cathode terminal of the Acorn to the middle tag. Solder R.F. chokes from each heater pin to the outer two tags, connecting one heater pin direct to the middle tag also. Connect one 50 pF condenser between the other heater pin and the cathode tag. The leads to the condenser must be cut so that the total length of condenser and leads is as short as possible and not over 1 in. Connect heater supplies to the outer tags and check that the valve heater lights up.

Using gentle heat—about 100 deg. C.—bend the Perspex so as to form a bracket standing  $1\frac{1}{2}$  in. off the chassis. Drill holes to take fixing bolts and the ends of the Lecher wires. Do not fix yet; but pass the Lecher wires through the holes and solder C<sub>1</sub> directly across the ends, leaving  $\frac{1}{2}$  in. of the condenser leads for attaching the R.F. choke and R.

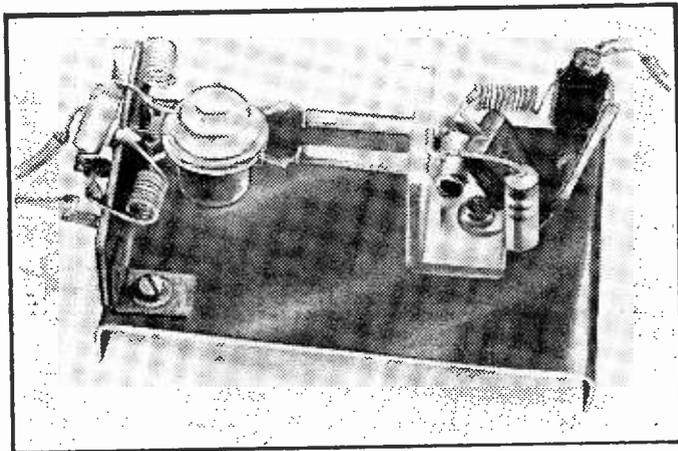Attach the other end of the choke to an insulated tag; connect C<sub>2</sub> across from this end to the nearest earth point and connect a lead for H.T.+ . Solder R between the end of the other Lecher wire (the grid wire) and the same



A photograph of the completed unit.

earth point. Switch on the power supplies and touch one end of a miniature neon lamp on the anode or grid end of one of the Lecher wires. A characteristic bluish-red glow indicates that the oscillator is working.

### Adjustments

Adjustment to the required frequency is obtained by snipping down the Lecher wires, about 3 mm. at a time, and re-soldering C1 in position, meanwhile measuring the wavelength. This technique will be described shortly. When the Lecher wire length has been adjusted, the length right up to the glass of the Acorn is found by measurement. Snip off the wires, leaving about  $\frac{1}{4}$  in. attached to each valve pin. Next enlarge the holes in the Perspex bracket to take the 6 B.A. rod, a smooth fit without forcing. Cut two lengths of 6 B.A. rod such that when soldered to the wires left on the valve pins the length is about 2 mm. less than the previous Lecher wires. Solder the rods into position as new Lecher wires. Push the holes in the Perspex bracket over the free ends of the Lecher rods, solder C1 across these ends and attach R and the R.F.C. as before. Fix the Perspex bracket to the chassis so that C1 is right up against the Perspex. Check the wavelength of the oscillator once more; it should be very nearly the required value.

### Measuring Wavelength

To measure wavelength, proceed as follows. Across the room stretch two parallel bare wires, 18 or 20 gauge, about an inch apart, to form a transmission line. These wires need to be very securely fixed and stretched taut. About 8ft. will be needed, but a longer line is better than a shorter. One end is short-circuited—in fact, the transmission line is best made from a single length of wire 16ft. or more in length. Using a piece of twisted flex (the shorter the better) fashion a loop which can be coupled inductively to the Lecher wires by placing it about  $1\frac{1}{2}$  in. above them. The other ends of the flex are connected to one transmission line wire, one to the other, about 15 cm. from the short-circuited end.

### Plotting a Graph

Using a valve-voltmeter with V.H.F. probe attached, find the position of the standing waves on the transmission line and adjust the position of the flex coupling connections to get a good voltage. Move the probe along the line and, with a strip of gummed paper as a "rider," mark the position of voltage minima. Plot about three or four minima near the middle of the line—avoid the ends and do not use paper-clips to mark the minima; they affect the measurements at these frequencies. The distances between the minima are measured carefully with a metre rule. The distance between minima is half a wavelength.

Careful snipping down of the Lecher wires, with measurement each time, will result in an increase in frequency of the oscillator, which is shown by the minima getting nearer together.

When the distance is 25 cm., the oscillator is running at 600 Mc/s.

The graph (Fig. 2) shows the results achieved by the author with one particular 955. In its final form it oscillated at a frequency of 606.1 Mc/s—corresponding to a wavelength of 49.5 cm. when the Lecher wires were 3.0 cm. in length. This particular Acorn oscillated well, with H.T. supply of 220 volts, at a frequency of 636 Mc/s. and might have gone higher.

### Harmonics

With the Lecher lines about 5-6 cm. long as first installed, and before the cutting down operation is completed, spuriously "short" standing waves may easily be obtained on the transmission line. This is due to harmonics and the fact of their occurrence can be recognised by the minima being poor as well as close together. As shortening of L1 and L2 proceeds however, the oscillator output diminishes and the harmonic content of the R.F. decreases greatly. As a result, voltage minima suddenly seem to be farther apart. At this stage the oscillator, though producing a good output still, cannot be greatly increased in frequency; care is needed now to shorten L1 and L2 by only a very small amount each time.

Harmonics on the line, and the poor minima mentioned above, can be eliminated if correct matching of the oscillator to the line is arranged. This is, however, unnecessary here, since the purpose of the oscillator is not to feed a transmission line but to supply R.F. to a crystal mixer. A very small loop inductively coupled to L1, L2 will readily give the energy transfer needed.

*Note.*—In the photograph an extra condenser is connected between the end of the anode Lecher line (at the R.F.C. end) and the nearest earth point. This is of 50 pF and was used to prevent standing waves appearing on the H.T. lead. It may not be necessary; try it without first. If required, it is shown dotted in the circuit diagram.

## PRACTICAL WIRELESS JULY ISSUE NOW ON SALE PRICE 1s. 3d.

The current issue of our companion paper, PRACTICAL WIRELESS, which is now on sale, contains the following principal articles :

- A Beginner's Constructional Course
- A Hi-Fi A.M. Receiver
- A Radio Jack
- Standard Musical Pitch
- A Mains-Battery Portable
- Single Track Stereo Sound
- A Pocket Transistor Receiver
- Review of the Cossor Pocket Receiver Model 561
- Short-Wave Section

# ITV in Difficult Areas

SOME PRACTICAL HINTS ON COPING WITH DIFFICULT RECEPTION

By B. L. Morley

**T**RANSMISSIONS in Band III have provided a new set of problems from the viewers' point of view. Generally speaking it can be said that the coverage of the transmitters is greater than was at first anticipated, but one of the major disappointments has been the fact that at some places quite near to the transmitters reception can be very difficult.

The latest transmitter to be brought into operation—the TWW transmitter at St. Hilary, South Wales—has followed this general pattern, but in spite of the fact that it is the most high-powered Band III station in the world, there are many places quite close to it where reception is well-nigh impossible. This is in part due to the rather difficult terrain; the hills and the valleys of South Wales cause obstruction and ghosting, and even in near-by Bristol we have certain areas where reception is almost impossible.

It has been found that the signals from Band III transmitters are not refracted to the same extent as those on Band I. They tend to keep to straighter lines and to throw deep shadows. We then have the situation where houses on one side of the street obtain perfect reception with the simplest of aerials, while houses on the other side find things very difficult.

## Pre-amplifiers

One of the most important things to realise is that an amplifier cannot amplify nothing, and if no signal is received with the usual aerial array, then it is useless fitting a pre-amplifier. The golden rule is always to attend to the aerial system first, and then to think about pre-amplifiers.

There is also a limit to the usefulness of pre-amps. In Band III valve noise is the predominant factor. In many cases a pre-amplifier will boost up the signal but at the same time produce so much noise that the picture is useless due to "snow" effects.

If first-class pre-amplifiers of the grounded grid type (cascode circuitry) are used then about two complete stages is roughly the limit which can provide useful amplification.

A good guide on the utility of a pre-amp can be judged from the existing picture. The first point to note is the amount of snow present. (By snow we mean the speckled white dots which appear on the screen superimposed on the picture.) In mild cases it makes the background of the picture appear "dirty" and in severe cases it makes the picture appear as though action is taking place in a severe snow-storm.

Where an existing receiver is working to the limit, yet the Band III picture is weak but free from snow, then a pre-amplifier can be of real help. Where the receiver is working to the limit and the weak picture is troubled with snow then it is likely that a pre-amplifier will increase the snow to such an extent that the receiver is better without it.

Generally speaking, cascode type pre-amps are better than the straightforward R.F. type in Band III.

Let me repeat this important fact: always try to improve the aerial system first. When the limit has been reached in this direction, then consider fitting a pre-amp.

## Mast-head Pre-amplifiers

In some cases the fitting of a pre-amplifier at the mast-head may be of value, but its functions must be understood clearly. A mast-head pre-amp will not give greater gain than a pre-amp at the receiver.

Its main function is to provide an increased signal to the feeder. Where the feeder is long and passes through an area of high interference, then a mast-head pre-amplifier can be used. It will then give a high signal-to-noise ratio at the receiver, so far as the noise picked up in the feeder is concerned.

If conditions are such that the aerial has to be sited at some distance from the receiver (at the bottom of the garden, for instance) then a pre-amp at the mast is a good investment.

Bearing this fact in mind, we can exercise a much greater freedom in positioning the aerial, and where this necessitates a long feeder, then a pre-amp can be fitted, not necessarily at the mast-head, but as near the mast end of the feeder as can be conveniently managed.

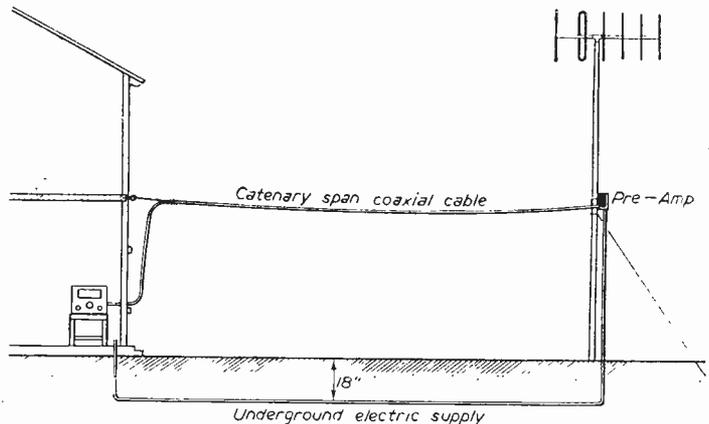


Fig. 1.—Remote aerial with pre-amp.

If a pre-amplifier has its own power supply then all that is necessary is to arrange an underground feed for this supply.

### Remote Aerial System

Fig. 1 shows a typical layout for a remote aerial. The aerial has been fitted on a tall mast

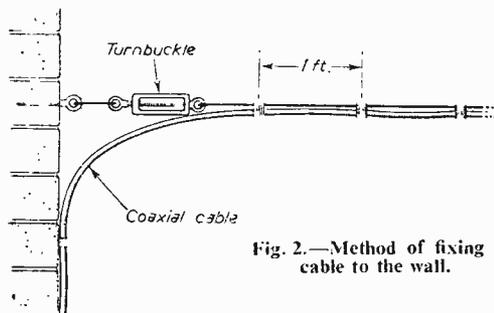


Fig. 2.—Method of fixing cable to the wall.

at the bottom of the garden. At a convenient height a catenary span has been erected to carry the cable to the television receiver. The height of this span will depend upon local circumstances, but it is a wise thing to ensure it is erected above the height of the washing line.

The line supporting the cable can be galvanised iron or steel such as is used for clothes lines, or any strong wire which will take the strain.

In judging the height of the span it is important to realise that there is likely to be a considerable dip in the wire, the amount of dip depending upon the length of the span. If the span is very long then a small post can be erected at the centre point so that the dip can be taken up, and the strain on the supporting wire eased.

The fixture on the mast will be determined by the wire used and the nature of the mast. Precautions must be taken to avoid slipping of the wire. If the mast is of wood then the loop of wire round the pole can be kept in place by a strong staple. If the pole is metal then a bolt can be inserted to prevent the loop slipping up or down.

If stranded wire is used, then two turns should be taken round the mast, and then the wire unstranded at the free end, winding each strand tightly, one by one, over the main wire.

A turnbuckle should be inserted so that the wire can be made taut.

At the house end the fixture will again depend upon the length of the span and the pull likely to be exerted. In the simple case a screw-eye can be driven into the brickwork by means of a plugged hole and the wire terminated on this. However, it is always best to avoid a direct pull if possible and if the screw-eye can be mounted round the corner of the house so that the pull of the wire is at 90 deg. to the fixture, then a much stronger termination is achieved.

A turnbuckle should be inserted at this end also, so that the wire can be stranded and made taut.

Having erected the wire the cable can be fastened to it by use of insulation tape at intervals of about 1ft. It is very important to avoid acute bends of the cable at each end. Don't bring the

cable off at an acute angle but make a gradual bend as shown in Fig. 2.

It is a wise precaution to fit an additional guy from the point of the mast where the catenary wire is attached to the ground using a good anchorage buried deeply.

The pre-amplifier can be fitted in a ventilated but weather-proof container on the mast at the point where the catenary span is fitted.

The power supply can be run directly underground: it is preferable not to fit this cable to the catenary wire but to run it entirely separately. The cable can be run in conduit buried at about 18in. deep where it will be free from normal digging operations. If polythene cable is used it could be buried directly in the ground without the conduit if low voltage (*not* mains voltage) is used by employing a transformer at each end.

In either case it is a wise precaution to cover the cable with tiles, bricks or half-round asbestos guttering.

The supply should be fused at the house end in each leg of the supply using  $\frac{1}{2}$  amp fuses, and a double pole switch employed. All mains voltage wiring should be fitted by a competent electrician. It is unwise to take risks. All installations must be up to the standards laid down by the electricity regulations.

### The Standard Installation

In most cases where television is installed an aerial system is erected on the chimney. This is normally the highest convenient point for an aerial to be fitted. It is not always the best.  Transmitter

Under normal conditions where adequate signal strength is available it answers very well but where signal conditions are difficult some other position may prove to be better.

However, at this stage let us consider producing the best results from this popular aerial position.

The most notable difference between Band I and Band III aerials is in the size of the individual elements. A dipole for Channel 1, for instance, is over 10ft. long, while a dipole for Channel 10 is less than 2½ft. The net effect of this is that there is less element area presented to the signal by the Band III aerial than is the case with the Band I aerial and, apart from all other considerations, the pick-up quality of an aerial depends to some extent upon the amount of element area in it.

To achieve a similar pick-up from a Band III aerial to that of a Band I aerial we must therefore employ more elements.

This is one of the basic reasons for the

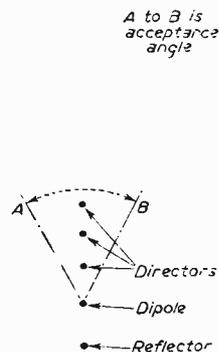


Fig. 3.—Showing the narrow acceptance angle of a five element array.

increased number of elements and greater complexity of the Band III system. Where a simple "X" type of aerial is sufficient for Band I it is probable that a five-element aerial is required for Band III.

Fortunately so far as the physical considerations are concerned the shorter length of the individual elements of the Band III aerial enables us to construct high-gain arrays which are not unwieldy.

The popular five-element array consists of three directors, folded dipole (for accurate matching) and reflector.

The normal method of erection is with the directors facing the direction of the transmitter. It is surprising to note that aerials fitted by novices are often fitted in reverse, with the directors pointing away from the transmitter.

The directors are, of course, the shortest elements of the array.

The standard five-element array has a fairly narrow acceptance angle. By "acceptance angle" we mean the angle through which the aerial can be rotated without the signal falling off appreciably. A simple dipole will receive signals at equal strength from all points of the compass; a yagi array such as the five-element array will also receive signals from all points of the compass, where signal strength is adequate, but the strength of the signal rapidly falls off as the aerial is turned away from the direction of the transmitter.

This is shown in Fig. 3. As an average figure it can be said that if the aerial is rotated through

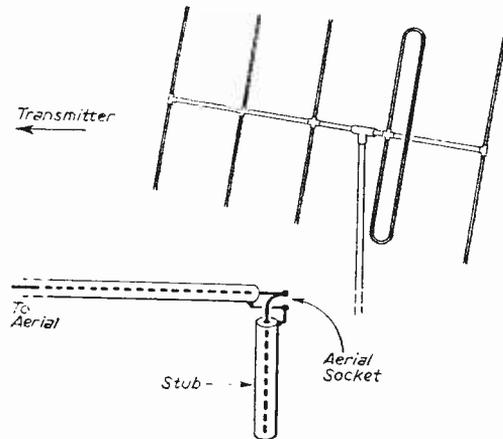


Fig. 5 (Top).—Tilting the aerial. Fig 6 (Bottom).—Using a stub.

an angle of plus or minus 20 deg. there will be little change in observable signal strength. We thus have an arc of 40 deg. to play with.

Where signal conditions are good it is not necessary to align the aerial accurately by compass on the transmitter.

This fact enables us to tackle one of the difficulties of Band III reception. That is the reception of ghost signals. A ghost signal is one which produces a second image on the television screen slightly displaced from the first and to the right

of it (looking at it from the front of the screen). In the simple case the aerial can be rotated until the ghost is reduced to negligible proportions.

In cases where the signal picked up by the aerial is weak then it is worth while rotating

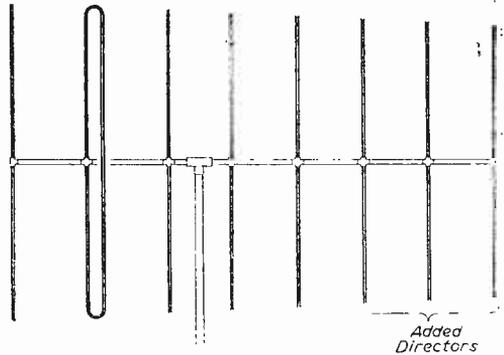


Fig. 4.—Adding directors to a yagi array.

the aerial round all points of the compass to try to find a stronger signal. Band III signals are very prone to reflect from solid objects and it is quite possible to produce a stronger signal with the aerial pointing away from the transmitter. It is well worth trying.

If a standard five-element array proves to be not quite strong enough, then it is possible to add up to three further directors without appreciably spoiling the matching, where the aerial is constructed on the 0.2 wavelength spacing principle. Make the first new director of the same diameter material as the existing and make it 5 per cent. shorter than the front director. Mount it at exactly the same distance in front of the front director as the front director is from its mate.

This process can be repeated making the next new director 5 per cent. shorter than the first new one, and repeat the process once again with a third new director, as shown in Fig. 4.

A limit is set to this process by the amount of mismatch introduced. Where signals are weak then an array with more directors may be required.

With a multi-director array the acceptance angle is very narrow and the aerial must be aligned on the point from which the strongest signal is obtained quite accurately. This in itself poses some problems which will be dealt with later.

### Double Arrays

The question is often asked, "What is the advantage of the double array?" In the first instance an array which has been doubled usually provides about an extra 3db gain. There is sometimes the thought that if an aerial gives, say, 10db gain, then two of them mounted together will produce twice this amount, that is 20db. This is far from the truth; the extra gain is about 3db.

Double arrays, however, beside giving an extra 3db are also helpful in discriminating against ghost signals, particularly those coming from an

angle of 90 deg. to the main signal. A very useful array for this purpose is one which combines the features of the double array together with a slot aerial. Greater gain can often be obtained from a multi-director array, but greater gain is not always preferred to better discrimination against ghost signals.

There is a limit set to the gain obtainable with a double array. Adding more directors means an increase in the overall length of the array and a point is reached where the two arrays side by side will affect each other. Two eight-element arrays mounted side by side are about the practical maximum which can be achieved. If more gain is required, then it is best to use a straight yagi array with more directors.

### Aerial Alignment

To get the best from Band III it is necessary to align the aerial to the strongest signal point. This involves some difficulties when the aerial is

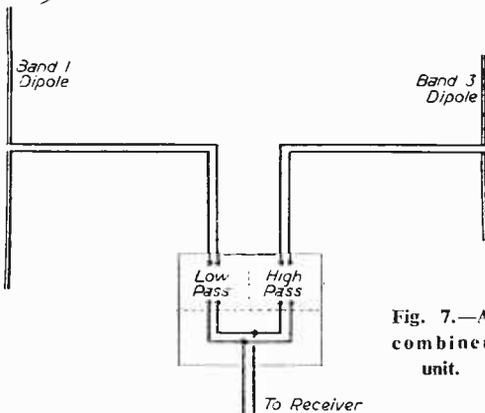


Fig. 7.—A combiner unit.

remote from the television set, for example, when it is erected on the chimney.

Undoubtedly the best solution to the problem is the establishment of two-way communication between the man on the aerial and one at the receiver. Dealers and aerial-riggers may find it worth while to invest in a pair of headphones and breastplate transmitter for the man on the roof, and an ordinary telephone for the man at the receiver. The man on the roof can then be kept accurately informed of the results of his movements.

One snag which must be taken care of is the operation of the A.G.C. in the receiver, and it is as well for this to be made inoperative until the aerial has been accurately aligned.

Where fading is experienced great care must be taken to distinguish between a signal varied in strength by a natural fade, and one varied in strength by movement of the aerial.

Simple two-way communication is not at all difficult for the amateur to contrive and use can be made of mikes and phones and even amplifiers. When on the roof all sorts of extraneous noises are heard which are not apparent in the room below, and even a slight breeze will whistle round a pair of phones, howling like a small gale. Phones should sit tightly on the ears and there

should be plenty of flex available to allow easy movement.

### Tilting the Aerial

When passing over rugged terrain it is possible for the vertically polarised signals to become tilted and it may be possible to obtain a stronger signal by tilting the aerial up slightly, see Fig. 5. About 5 per cent. is the limit of useful tilt but in town areas it may be worth while to give a greater tilt than this. Further consideration should be given to tilting sideways as well as in the upward direction. With two operators checking the signal as described, then it should be possible to arrive at a position which gives the maximum signal.

It can be noted that where indoor aerials are used the effect of tilt is very pronounced and can be employed to obtain an improvement in signal level.

### Search for the Signal

Under difficult situations the chimney may not always be the best position on which to erect an aerial. For those who have the patience then a real search can be instituted to find the best signal.

For this work it is almost essential to have two operators equipped with telephonic communication.

In built-up areas particularly the signal can become distorted and twisted out of its normal path and a difference of only a few feet in the position of the aerial can often produce large differences in the signal.

Contrary to accepted opinion, the highest position of the aerial is not always the best in these cases. The writer has known cases where the lowering of an aerial by 6ft. produced a worth-while signal. If the aerial can be erected at a great height well above the influence of near-by buildings, then, of course, we expect to obtain a greater strength of signal, but in built-up areas—especially those where houses have been built on hills and the surrounding area is of a hilly nature—then the normal accepted laws do not appear to apply.

In dealing with Band III we have found that shadows can be thrown for a considerable distance and at times it almost seems that the signal can be bent round corners!

If, in an accepted good-signal area, difficulty is experienced with the normal type of installation, then alternative situations must be sought. Try another chimney; try making the aerial higher; try fixing it lower; try on the eaves of the house; try on the apex; try to get away from the house entirely and erect the aerial on a pole in the garden. The further the aerial is from near-by objects, the more likely is the signal to conform to the accepted standard. An aerial erected on a 30ft. pole in the garden will often produce better results than one erected 40ft. from the ground on the chimney.

Don't always accept the orthodox, try unorthodox methods. A dipole moved about the house in different positions in different rooms may produce a worth-while signal. An aerial in the attic may get a signal where an aerial on the chimney has failed.

(To be continued)

# Heater-cathode Tube Shorts

OVERCOMING A COMMON FAULT, OR NEW TUBES FOR OLD

By T. Deakin

**A** HEATER-TO-CATHODE short in a television tube need not necessarily imply that a new tube is automatically required. In fact any remedy that can prolong the life of a partially unserviceable tube is welcome, bearing in mind the prohibitive cost of such a component.

Shorts of this nature, whether temporary or permanent, are embarrassing because most set manufacturers arrange that the cathode of the tube is the element to which the picture information is applied. The grid, normally used for this purpose in valve circuitry, is merely employed as a beam current, or brilliance, control. Thus when the thin insulation between heater and cathode breaks down, or provides an intermittent contact between the two electrodes, the video signal (and the sync as well as a rule) is fed to the low impedance heater chain via the short. The net result is loss of signal and sometimes sync.

Now this arrangement is not obstinacy on the part of set manufacturers, nor is it a ruse, as imagined by some, to sell more tubes.

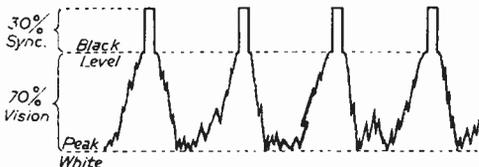


Fig. 1.—Video and sync waveform at the tube cathode.

At the video output stage the signal consists of both video and sync, and in a video stage feeding the cathode of a tube will appear as shown in the waveform of Fig. 1.

This waveform is also coupled to the sync separator which, at its simplest, is of the leaky-grid detector variety. The waveform charges up a condenser so that the positive peak of the waveform is at earth potential at the grid of this type of separator. If the signal amplitude is large enough (which of course it will be if the same signal is also driving the tube), then only the sync part of the signal is amplified, the remainder being beyond the cut-off bias level of the sync separator. By this means a series of negative-going pulses appear in the anode circuit for integration and differentiation in frame and line timebase circuits respectively.

This arrangement economises on the number of stages required and is widely used by set manufacturers.

## Cures for the Trouble

One popular remedy for the fault with which this article deals is well known and involves the use of an isolating transformer with a special low-capacity winding.

The tube heater is then supplied separately

from the rest of the heater supplies and though the heater-cathode short still remains, very little of the signal developed at the video anode is lost as a result of the good degree of isolation that the low capacity winding provides from earth.

Such transformers are readily available from radio component suppliers.

They are not easily wound by the constructor, however, and an electronic rather than electromagnetic solution is more easily and cheaply available to the reader with the usual kit of radio spares.

In its simplest form the circuit requires three diode additional stages and the assembly can either be mounted as a neat sub-unit at the back of the receiver cabinet or suspended as a "gorse bush" type of construction from the neck of the tube. This latter method will appeal to the reader with the least time at his disposal, either by his own inclination or the demands of the rest of the household.

## Tube Modifications

The first step consists of changing the role of grid and cathode of the tube. Because the cathode is held at the voltage level of the heater, all further attempts at control of this electrode must be abandoned.

Instead, the functions of brilliance control and modulation of the tube must be combined at the grid, and both involve some additional circuitry.

A large proportion of television sets are wired with the heaters of the valves and tube in series for A.C./D.C. operation. Step No. 1 involves moving the tube to the earthy end of this line up. (If the set is a superhet receiver using an X78 frequency changer, the latter stage must always be at the earthy end of the heater chain, and the tube heater must be connected immediately before

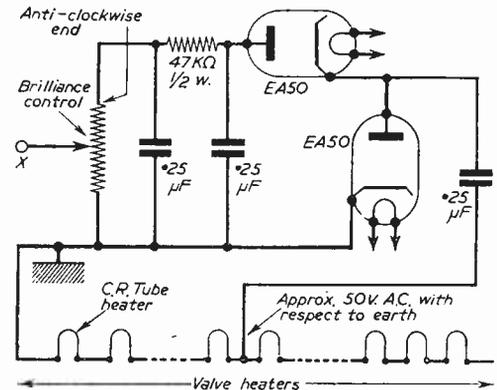


Fig. 2.—Bias line derived from the heater chain for brilliance control.

this stage.) In the worst case (i.e., a dead short) the cathode will be at approximately earth potential.

For control of brilliance the grid must be negative with respect to the cathode (and hence earth) and this involves supplying a bias rail.

This is easily achieved on A.C./D.C. sets working on A.C. and Fig. 2 gives the necessary details.

Here it will be seen that a voltage doubling rectifying system gives a negative bias rail. The

final R.F. stage, through the detector and interference limiter. It will be seen that normally the output is direct coupled via the 68K and 100K divider resistors to the cathode of the tube. The 0.22  $\mu$ F condenser couples the A.C. component of the video waveform with no attenuation, while the direct coupling provides the correct D.C. level for the signal.

The interference limiter is simply a diode whose cathode is maintained at a controllable level set by the 0.1M potentiometer.

When interference transients appear at and above the peak white level of the signal they appear at and above the peak white level of the signal at the grid. At some particular setting of the limiter control, these positive-going excursions of interference will cause the video output stage grid level to exceed the control potential and the diode will conduct. On conduction the .047  $\mu$ F capacitor is now connected between grid and anode of the video stage, and the interference is very effectively degenerated due to integration by feedback.

Now the simplest way of inverting the waveform is to reverse the connections to both the detector diode and the interference limiter diode. That is, connections made formerly to the cathodes of the diodes must now be made to the respective anodes, and vice versa.

This solution entails a certain amount of work under the chassis, changing valve base connections, and as this circuitry is generally screened and is somewhat inaccessible as a result in the average set, the alternative solution may appeal to some readers, particularly as certain types of set may not function so well with the first solution.

### Large Screen Sets

Large screen sets fall into this category where the amplitude of the drive feeding the cathode of the tube is excessively large.

The circuit of Fig. 3 shows how the video output stage cathode is maintained at an artificially high positive level by current from the brightness and frame and line hold and height controls being fed through the cathode resistor. Bias for this stage therefore is not entirely due to the cathode current alone.

Now the grid waveform of the video stage in a set in which cathode tube modulation is employed is the reverse of that shown in Fig. 1. That is, the peak white signal level is positive-going while the sync is negative-going.

As only a limited amount of gain is available in a video output stage, the large amplitude of output signal demands a fairly high input level at the grid.

(To be continued)

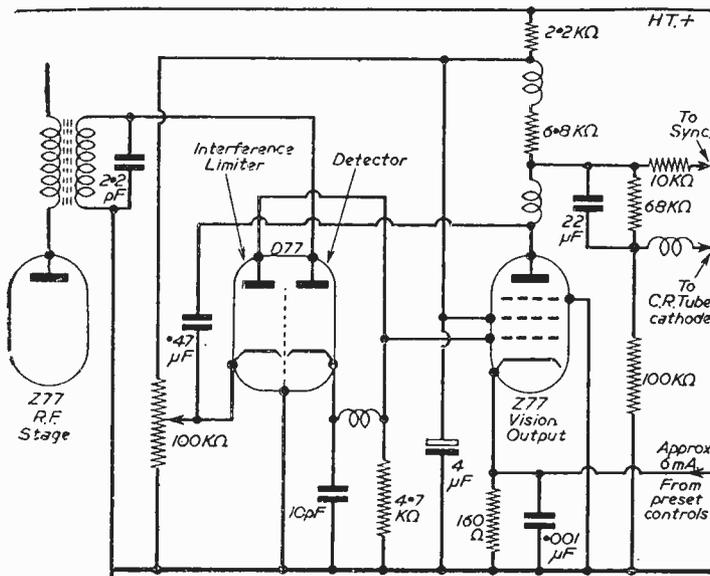


Fig. 3.—A circuit of a typical detector and video output stage modulating tube cathode.

A.C. supply is taken from a tapping on the heater chain. Its level should not be critical and will be governed in the final instance by the effectiveness of the brilliance control on the picture. Obviously if the brilliance cannot be decreased sufficiently, the tapping level on the heater chain should be increased.

If EA50 diodes are used in the voltage doubling circuit then some space can be saved by wiring them in directly by their valve pins rather than using the appropriate valve holders. The heaters should be connected in parallel, and then included in series with the main heater chain, assuming the latter is a 0.3A line up. Alternatively a double diode of the D77 or EB91 variety can be used. The heater is 0.3A and is wired in series directly.

With the tube grid being modulated rather than the cathode, the video waveform must be inverted so that, at the grid, peak white level is now the positive limit of the waveform.

The grid waveform, in fact, must look like that of Fig. 1 inverted. There are two ways of doing this and some experimentation may be necessary to determine the best results.

### Inverting the Waveform

Fig. 3 shows a typical video output circuit from

# THE CUBICAL QUAD AERIAL

AN AERIAL THAT IS BECOMING POPULAR IN AMATEUR TRANSMITTING CIRCLES

By S. A. Money

**I**N recent years a new and rather interesting type of aerial, known as the Cubical Quad, has become popular in amateur transmitting circles. This aerial, which is compact, has quite high gain and is simple to construct, and seems to have great possibilities as a television aerial. Its size and shape make it highly suitable for use as a loft aerial when lack of space prevents the use of conventional dipole or slot aeriels.

The original version of the quad aerial is believed to have been developed and used by the broadcast station HCJB in Quito, Ecuador, and first came into prominence in 1948.

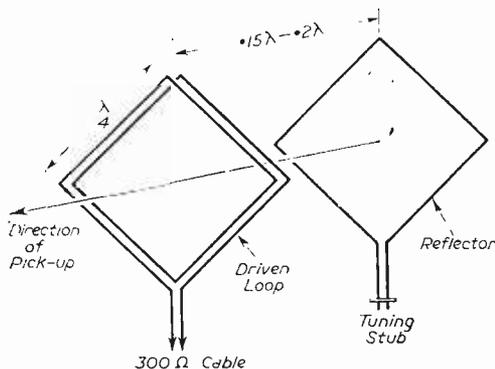


Fig. 1.—The original quad aerial.

In its original form the quad aerial consisted of two diamond-shaped loops, one acting as the driven element and the other as a reflector. The sides of the loops were made a quarter of a wavelength long and the feeder cable was connected to one of the corners of the driven loop. The reflector was placed about 0.2 wavelength behind the driven loop and was usually fitted with a shorted stub for tuning. In order to match the driven loop to a 300 ohm feeder it was usual to make it with two turns to step up the impedance.

A later development of the quad aerial, known as the cubical quad, made use of two square loops with the feeder line connected at the centre of one of the sides of the driven loop. This arrangement is much better for matching to the feeder since the impedance is found to be about 75 ohms. This type of aerial was also found to have slightly higher gain. Power gains of up to 10dB over a simple dipole have been claimed for this aerial, though a gain of 8dB seems to be a more reasonable figure.

The space required for a cubical quad aerial is a cube with sides of a quarter wavelength. For Band I the sides would be about 4ft. to 5ft. long and for Band III about 15in. long. The loops are made from coaxial cable and the supports are of wood. Total cost of a Band I aerial

should not be more than about 20s. and the aerial can be built and fitted in a couple of hours.

## Principle of Operation

The driven loop behaves approximately as a pair of half-wave dipoles spaced a quarter of a wavelength apart. If the loop is fed at the centre of one side, as shown in Fig. 2, the current distribution will be as shown by the dotted lines and the direction of flow as shown by the arrows. It is seen that the peaks of current occur on the vertical sides of the loop and that the currents in these sides flow in the same direction. Radiation will therefore be mainly from these two sides. Since the currents cancel on the horizontal sides there will be little or no radiation from them. This loop will therefore be vertically polarised. For reception maximum pick-up will occur on the vertical sides of the square and the loop will act as two vertical dipoles spaced a quarter wave apart, one being fed at the centre and the other at the ends. Maximum pick-up will be in a direction perpendicular to the plane of the loop.

If the loop is fed at the centre of the lower side, the aerial will become horizontally polarised with maximum pick-up on the horizontal sides of the square.

By placing another loop at a distance of 0.2 wavelength behind the first, as shown in Fig. 3, a two-element array is formed. If the second loop is made about 5 per cent. larger than the first it will act as a reflector, in the same way as the reflector of an H aerial, and the gain and directivity of the aerial will be increased.

## Gain and Impedance

The power gain of a single loop, fed at the centre of one side, is about 1dB over a simple dipole. If the aerial is close to the ground, or the roof of the building, the gain drops to about zero and in some cases the aerial may be worse than a dipole.

(Continued on page 579)

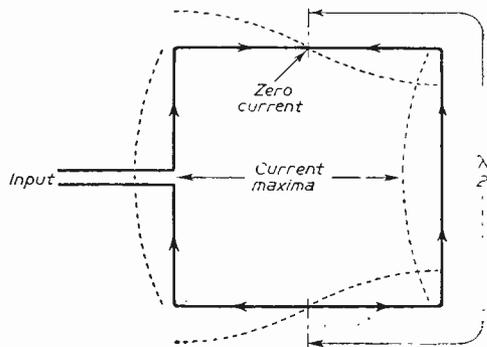


Fig. 2.—Current distribution around the loop.




Our specialist buying knowledge and reputation ensure a square deal... and enable us to

# offer the best for your money!
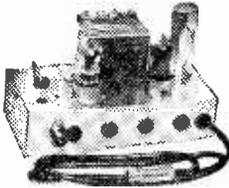
## BAND 3 T/V CONVERTER—180 Mc/s - 205 Mc/s


Suitable for London, Birmingham, Northern, Scottish and Welsh ITA Transmissions.



Mk. 2 Model as illustrated. Latest Cascode circuit using ECC84 and EF80 valves giving improved sensitivity (+ 18 db) over standard circuits. Built-in Power supply AC 200-250 v. Dimensions only 6 1/2 in. x 3 in. Ht. 4 in. Simple and easy to fit—only external plug in connections, wired, aligned and tested ready for use. State Channel required. Guar. Bargain Offer—good results or full refund,

only £3.19.6. Carr. & Pack. 2/6. Band 1, Band 3 Change-over Switch and B.B.C. aerial socket, 8/- extra. CONVERTER ACCESSORIES Band 1-Band 3 Cross-over Unit, 7/6. Var. Attenuators 6db-36db., 7/6. BBC Pattern Filter, 8/6. Band 3 Aerials—outside: Single Dipole with 4 yds. co-ax., etc., 13/9. 3 Element Beam, 27/6. 5 Element, 25/-, etc.

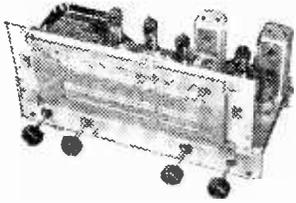**Volume Controls** 80 ohm **COAX**  
Log. minis, 10,000 ohms  
—2 Megohms. Long  
spindles. 1 year  
guarantee. Midget Edi-  
swan type.  
No Sw. D.P.Sw.  
3. 4/9  
Lunar Ratio, 10,000  
ohms — 2 Megohms.  
Levs. switch, 3/- each.  
Coax plugs, 1/2. Coax  
sockets, 1/- each.  
13. Outlet boxes, 4/6.



NEW BOXED	VALVES	GUARANTEED	ALL
1R5, 1T4	70 DEF6	9/- EP41	10/6 PUF82 10/6
185, 184	70 DK96	9/- EP80	10/6 PLS3 12/6
384, 3V18	10L96	9/- DPS6	13/6 PL14 14/6
3Z4	90 35L6	10/6 EP91	8/6 PLS2 10/6
6AT6	80 EABC9	9/6 EL41	10/6 PLS3 11/6
6K7	80 EB91	8/6 EL84	11/6 PYS6 9/6
60	80 EHC41	10/6 EM45	11/6 PYS1 9/6
6Q7	80 EHC93	9/6 EY31	12/6 PYS2 8/6
68N7	80 ECC84	12/6 EY86	14/6 PYS3 10/6
6V6	70 ECF20	12/6 EY40	8/6 U22 8/4
6X4	70 DCF22	12/6 EY80	8/6 U25 12/4
6X3	70 ECH42	10/6 EY81	8/6 U42 10/6
7C5	90 ECH51	10/6 MUI4	8/6 UP41 10/6
7Y4	80 ECL40	12/6 PC81	10/6 UY41 10/6
DAP96	90 ECL82	12/6 PCF80	10/6 UY41 8/6

### RECORD PLAYER CABINETS



**ALL-WAVE RADIOGRAM CHASSIS**  
3 WAVEBANDS 5 VALVES  
S.W. 16 m.—50 m. LATEST MIDGET  
M.W. 200 m.—500 m. B V A  
L.W. 800 m.—2,000 m. SERIES  
Brand new and guar. A.C. 200-250 v., 4 pos. W.C. sw. Short-Medium-Long-Gran. P.L. socket. High Q dust core coils. Latest circuit technique, delayed AVC and neg. feedback O.P. 4 watts. Chassis size 13 1/2 x 5 1/2 x 2 1/2 in. Dial 10 in. x 4 1/2 in. Hor. or Vert. station names. Walnut or ivory knobs to choice. Aligned and calibrated ready for use. Sensitivity and Quality at Low Cost.  
Chassis isolated from mains. **BARGAIN 9 1/2 gns.**  
Carr. and Ins., 4/6. **PRICE 9 1/2 gns.**  
8 or 10 in. speakers to match, 20 - and 25 -  
7 Valve De Luxe, push-pull EL41 version, 7 watt output, with H Duty Output Transformer, £12.10.0. Carr. & ins., 5/-.

Contemporary style, rexine covered cabinet in mottled red with cream interior, size 18 1/2 x 13 1/2 x 8 1/2 in., fitted with all accessories, including speaker, buffer board and plastic fret. Space available for all modern amplifiers and autochangers, etc. Uncut record player mounting board 13 x 12 in.

Cabinet Price, **£3. 3. 0.** Carr. and Ins., 5/6.  
**2-VALVE AMPLIFIER Mk. 1.**  
200-250 v. A.C. Modern circuit with High Gain EL84 output and double wound Main Transformer, variable tone and volume controls, wired and tested with 6 in. Speaker and O.P. Trans. complete with knobs and drilled ready to fit Buffer Board in above cabinet. Only **£3.12.6.** Carr. & Pack. 2/6.  
**2-VALVE AMPLIFIER Mk. 2.**  
200-250 v. A.C. Specification as above but a higher fidelity and greater output (approx. 5 watts) is obtained by using latest Twin Stage Triode-pentode Valve EC152 and negative feedback Tone Control. Complete wired and tested as above **£3.19.6.** Carr. & Pack. 2/6.  
**SPEAKER FRET.**—Expanded Bronze, stainless metal X 8 in., 2/3; 12 x 8 in., 2/-; 12 x 12 in., 4/6; 12 x 16 in., 8/-; 24 x 12 in., 0/-, etc.  
**TYGAN FRET** (Murphy pattern) 12 in. x 12 in., 2/-; 12 x 18 in., 3/-; 12 x 24 in., 4/-, etc.

**RECORD PLAYER BARGAINS**  
4 sp. BSR (TU9), 92 8. 4 sp. COLLARO JUNIOR, **£4.10.0.** 4 sp. GARRARD (1 S.P.), **£7.15.0.** Carr. & ins. 3/6.  
**AUTO CHANGERS.**—4 sp. BSR (UAS), **£8.10.0.** 4 sp. COLLARO, **£8.15.0.** 4 sp. GARRARD (1C1214H 2), **£10.5.0.** Carr. & ins., 4/6.  
All above units are latest models and are fitted with modern styled 1/2 weight Xtal. P.C. with turnover head and twin sapphire styli.

**TV TUBES—RECONDITIONED**  
All Tested and Guarant. 6 months.  
**GENUINE OFFER.**—all tubes Reconditioned and Re-vacuumed and virtually as good as new.  
12 in. Mullard, Mazda, etc., **£8.10.0.** (As available).  
14 in. Mullard, Mazda (Rect.), **£7.0.0.**  
17 in. Mullard, Mazda (Rect.), **£8.10.0.**  
Carr. & ins. 12/6.

**COMPREHENSIVE STOCKS—QUICK DELIVERY**  
**I.F. TRANSFORMER—465 kc/s.**  
Brand new ex-manufacturer's midget I.F.T. size 2 1/2 in. x 1 1/2 in. dust core tuning. Litz wound coils. High Q. Bargain offer, 7/6 pair.

**SPECIAL PRICE PER SET**  
1R5, 1T4, 185, 184 or 384, or 3V1 ... 27/6  
DK96, DAP96, DAP96, DL96 ... 35/-  
GR5, GR7, GR7, 6V6, 5Z4 or 6X3 ... 35/-

**ELECTROLYTICS ALL TYPES NEW STOCK**

Tubular Wire Ends	22 F 32 350 v. B.E.C.	5 g
25 25 v., 20 12 v. 10	Case Types, Clips 31. ea.	
25 50 v. T.C.C.	2 - 8/500 v. Dub.	
50 50 v., 4 500 v. 2 -	8-8/450 v. T.C.C.	4/6
100 25 v., 2 450 v. 2 -	8-16/450 v. Hunts	5/-
4 50 v. T.C.C.	2 3 16+16/450 v. T.C.C.	5/6
8-8 450 v. B.E.C.	4 8 22 350 v. B.E.C.	4/-
8+16 450 v. T.C.C.	5 32+32 275 v. Hunts	4/6
16/450 v. B.E.C.	3 6 32+32 450 v. T.C.C.	6/6
16 500 v. Dub.	4 - 250 250 v. B.E.C.	8/6
18+16 450 v. T.C.C.	6 80 350 v. T.C.C.	6/6
32 350 v. B.E.C.	4 - 60+100 350v. B.E.C.	11/6
32 500 v. Dub.	5 - 80+250 275v. B.E.C.	12/6
50+50 250 v. B.E.C.	6 100-200 275v. B.E.C.	12/6

**G.R.T. Heater Isolation Transformers**  
New improved types—mains prim. 200/250 v. tapped.  
All Isolation Transformers now supplied with alternative 10 foot, plus 25%, and plus 50% loost taps, at no extra charge.  
2V. .. 2A type 12/6 (P. A.P. 1/6)  
6.5V. .. 1A .. 12/6 ..  
10.5V. .. 1A .. 12/6 ..  
15V. .. 3A .. 12/6 ..  
Other voltages in course of production.  
Small size and tag terminated for easy fitting.

**JASON F.M. TUNER UNFT 87-105 Mc/s.**  
Designer Approved Kit of parts to build this modern highly successful unit, drilled chassis and superb type 4V1. Coils, caps, and all quality components, etc. for only 5 gns., post free. Set of 4 spec. EP11's or equiv. valves, 30/-, post free. Illustrated handbook with full details, 2/-, post free. FREE WITH KIT. 45 he. alignment screw, 7/6 plus 2/- P. & P.

**TRANSFORMER & COIL WINDING CAPACITY AVAILABLE FOR PROTOTYPES & SMALL RUNS.**


Listed above are only a few items from our very large stock. Send 3d. stamp today for Complete Bargain List.

Terms: C.B.O. or C.O.D. Kindly make cheques, P.O.s, etc., payable to T.R.S. Post Packing up to 1lb. 7d., 1lb. 11, 3lb. 1/6, 5lb. 2/-, 10lb. 2/9. Hours: 9 a.m.-6 p.m. 1 p.m. Wed. Open all day Saturday.



**RADIO COMPONENT SPECIALISTS** (Est. 1946)  
70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)  
50 yards Thornton Heath Station.  
Buses: 130A, 133, 152, 156 and 193

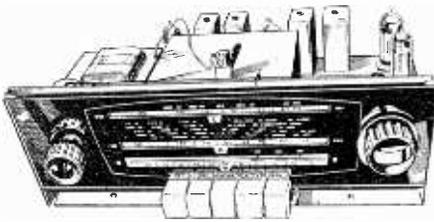**WONDERFUL OFFER OF A.M.-F.M. CHASSIS BY FAMOUS MANUFACTURER**



WORTH TWICE THE PRICE.

Why buy a F.M. Tuner at the same price? Only 50 available at £12.10 (P. & P. 8/-). UNUSED. Tapped input 200-225 v. and 226-250 v. A.C. ONLY. Chassis size 15" x 6 1/2" x 5 1/2" high; 7" x 4" Elliptical speaker. Dial 1 1/2" x 4" in gold, red and deep brown. Pick-up. Extension speaker, Ac., E., and Dipole sockets. Five "piano" push buttons—OFF, L.W., M.W., F.M. and Gram. Covers 1,000-1,900 M.; 200-550 M.; 88-108 Mcs. Aligned and tested. With all valves. Valves EZ80 rect., ECH81, EF89, EABC80, EL84, ECC85. Cabinet to fit, polished, with back, 47/6.

TERMS:—£5 Down and 4 Monthly Payments of 42.-

GRAMOPHONE AMPLIFIER with 6 1/2" (or 7" x 4") SPEAKER

**£4. 7. 6**

ECC81 valves.

With metal cabinet as illustrated. Stove enamel grey hammer finish. 5" x 7 1/2" x 4 1/2".



FINAL OFFER of last few hundred of highly successful High Gain Band 3 I.T.A. T.V. Converters (over 20,000 sold in 2 years). (After this batch we are supplying only the Moulded Case design to use materials already in stock.) Walnut Finish Cabinet, 5/- extra. Fully Guaranteed. 2 valves. Internal Power Pack with Metal Rectifier. All exactly as in previous issues of P.T. and P.W. (Post 3/-; C.O.D. 2/-) Write for details of our 2 Valve + Rectifier Portable Guitar Amplifier in Carrying Case. Less than £8.

**WHY PAY MORE? ONLY 60/-(POST 3/-)**  
Mains and Output Transformers. Metal Rectifier. ECL82 Valve. Tone and Volume Controls. On-off switch. Plenty of Volume. Fully Guaranteed. Two Knobs supplied.

**BATTERY ELIMINATOR.** Converts your Battery Set to Mains. For 4 Low Consumption Valves (DK96 range). 90 v. 15 mA. and 1.4 v. 250 mA., 42.6 (2/6 Post). 200-250 v. A.C. Size 5 1/2" x 3 1/2" x 2".

Post Orders to Camberley, please. Delivery by return. Terms:—One-third down and balance plus 7/6 in four equal monthly payments. Postage with down payment.

**GLADSTONE RADIO**

82B, High Street, Camberley, Surrey, and 3, Church Road, Redfield, Bristol. Tel.: 51207.

**REVACUUMED T.V. TUBES • SAME DAY VALVES • SERVICE**

SIX MONTHS' STRAIGHT GUARANTEE

All Guaranteed New and Boxed

1.4v. midget. 1R5, 1S5, 174, 3S4, 3Q4, 3V4, DAF91, DF91, DK91, DL92

DL94: ANY 4 for 27/6.					
1A7GT	19/6	6V6GT	7/6	DAF96	8/6
1C5GT	13/6	6X4	7/6	DF80	10/6
1D5	12/6	6X5GT	6/6	DF83	11/6
1H5GT	11/7	7B6	12/6	EF86	14/6
1N5GT	11/7	7B7	8/6	EF91	6/9
1R5	8/6	7C5	8/6	EF92	5/6
1S5	7/6	7C6	8/6	EL33	18/9
1T4	7/6	7H7	8/6	EL38	22/6
3A5	10/6	7S7	9/6	EL41	9/6
3Q4	7/6	7Y4	8/6	EL42	11/6
3Q5GT	9/6	12A4H8	9/6	EL44	11/6
3S4	7/6	12A7E	8/6	EL48	8/9
3V4	8/6	12A7T	8/6	EL84	10/6
5U4G	8/6	12A7U	8/6	EF51	11/6
5V4G	11/9	12AX7	8/6	EF86	15/6
5Y3GT	7/6	12J7GT	10/6	EZ40	7/9
5Z4G	9/6	12KTGT	7/6	EZ41	10/3
6AL5	5/9	12RBGT	12/6	EZ80	6/6
6AM5	5/6	12Q7GT	7/6	EZ91	9/6
6AM6	6/9	12Z3	7/6	FW4500	10/6
6AQ5	7/6	14S7	12/6	GZ32	11/6
6AT6	7/3	19AQ5	7/6	KT33C	8/6
6BA6	7/6	25A9G	13/6	KT63	6/6
6BE6	7/6	25L6GT	8/6	MC14	6/6
6BH6	9/6	25Z4G	9/6	N18	7/6
6BJ6	7/6	25Z6GT	9/6	PC81	9/6
6BR7	8/6	35L6GT	9/6	PCF80	9/6
6BW6	7/6	35Z4GT	7/6	PF82	10/6
6BW7	7/6	35Z5GT	8/6	PCL82	10/6
6CD8G	25/6	43	12/6	PCL83	12/6
6F6G	6/6	50CD6G	18/9	PEN44	11/9
6K7G	4/6	50L6GT	8/6	PEN48	11/9
6L6	6/6	AZ31	11/6	PEN36C	14/6
6Q7GT	7/9	B98	15/6	PEN46	6/6
6Q7GT	9/6	CL33	16/9	PL36	15/6
6SL7GT	7/6	D77	5/6	PL38	22/6
6SN7GT	7/6	DAC32	11/6	PL81	16/6
6U4GT	11/6				
6V8G	7/6				

**Mullard**

in.	£	s.	d.
14 MW 36-22	5	10	0
14 MW 36-24	5	10	0
14 MW 36-44	5	10	0
14 AW 36-21	5	10	0
16 MW 41-1	7	0	0
17 MW 43-43	7	10	0
17 MW 43-64	7	10	0
17 MW 43-69	7	10	0
21 MW 53-20	10	10	0
21 MW 53-80	10	10	0

**Mazda**

in.	£	s.	d.
14 CRM 141	5	10	0
14 CRM 142	5	10	0
14 CRM 143	5	10	0
15 CRM 153	6	10	0
17 CRM 171	7	10	0
17 CRM 172	7	10	0
21 CRM 211	10	10	0
21 CRM 212	10	10	0

**Brimar**

14 C14BM	5	10	0
14 C14FM	5	10	0
17 C17BM	7	10	0
17 C17M	7	10	0

**Cossor**

14 141K	5	10	0
17 171K	7	10	0
17 172K	7	10	0

14 in. Marconi, Emitron, Ferranti, G.E.C. £5 10 0.  
17 in. Marconi, Emitron, Ferranti, G.E.C. £7 10 0.

Carriage and Insurance 12/6 (U.K.). Cash with order. Personal Callers Welcome.

**VIDIO REPLACEMENT CO.**

HALES ST., DEPTFORD HIGH ST., LONDON, S.E.8  
Telephone: TIDEWAY 4506

**READERS RADIO**

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16 STA. 4587

For a square loop the input impedance is about 100 ohms, which would give some mismatch if used with 80 ohm cable. This type of aerial has been tried at some 20 miles from the Rowridge

turns is merely to alter the impedance of the driven loop.

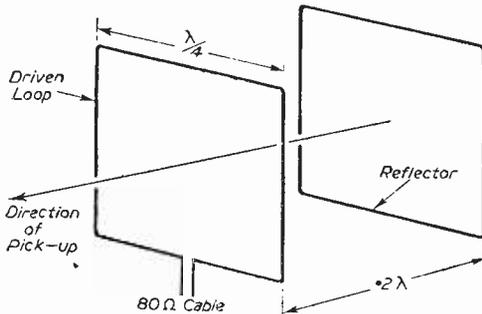


Fig. 3.—The cubical quad aerial.

transmitter and gives about the same performance as a dipole. The power gain, in this case, was probably lost due to mismatching of the cable.

When a reflector is added the power gain over a simple loop is about 7dB, and over a dipole about 7dB to 8dB. This is an unusually large increase in gain for the addition of a reflector and is probably due to the type of elements used.

With a reflector spaced 0.2 wavelength behind the driven loop the impedance becomes about 75 ohms, which gives a good match into 80 ohm coaxial cable. For correct matching the cable should be of the balanced twin type, but the use of coaxial cable does not appear to affect the performance of the aerial unduly.

If the spacing between the reflector and the driven loop is reduced the impedance falls, becoming about 50 ohms for a spacing of 0.1 wavelength. The gain also falls off slightly as the spacing is reduced.

If the driven loop is made up with two turns the input impedance is increased by a factor for four, in the same way as for a folded pipe. Using a two-turn loop also increases the bandwidth of the aerial. The reflector need not be altered since the object of doubling the

**Dimensions**

The length of wire in the driven loop is made about 0.97 of a wavelength at the frequency for which the aerial is designed to work. The reflector loop is made about 5 per cent. longer, in the same way as the reflector in an H aerial. The dimensions for the two loops and the spacing between them for each of the television channels are given in Table I. These dimensions have been calculated for frequencies at the centre of each channel. The table also gives the diagonal length of each of the loops since this dimension is very useful when constructing the support for the aerial.

**Construction**

The aerial elements are mounted on a wooden framework consisting of two X-shaped frames, to support the two loops, and a cross-beam to give the desired spacing between the loops. This is shown in Fig. 4.

The frames supporting the loops are made from

TABLE I

Dimensions for the Television Channels

Channel	Driven Loop		Reflector		Spacing
	Side	Diagonal	Side	Diagonal	
1	5' 6"	7' 9 1/2"	5' 9 1/2"	8' 2 1/2"	4' 1 1/2"
2	4' 9"	6' 9"	4' 11"	6' 11"	3' 7"
3	4' 4"	6' 1 1/2"	4' 7"	6' 5 1/2"	3' 3"
4	4' 0"	5' 7 1/2"	4' 2"	5' 11"	3' 0"
5	3' 8"	5' 2 1/2"	3' 10"	5' 5"	2' 9"
6	16"	22 1/2"	16 3/4"	23 1/2"	12"
7	15 1/2"	22"	16 1/4"	23"	12"
8	15 1/4"	21 1/4"	16"	22 1/4"	11"
9	14 3/4"	20 3/4"	15 1/2"	21 3/4"	11"
10	14 1/4"	20 1/4"	15 1/4"	21 1/4"	11"
11	14"	19 3/4"	14 3/4"	20 3/4"	10 1/2"
12	13 3/4"	19 1/4"	14 1/4"	20 1/4"	10 1/4"
13	13 1/2"	19"	14 1/2"	20"	10 1/4"

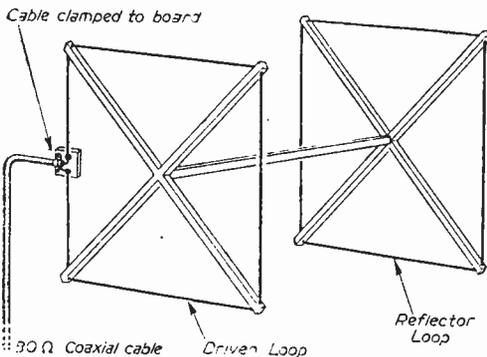


Fig. 4.—Constructional details.

1in. X 1in. wood. Two lengths are cut to about 1in. greater than the required diagonal for the loop. At a point 1/4in. from each end a hole is drilled to take the wire of the loop. The size of this hole will depend upon the thickness of wire used. A half-lap joint is made at the centre of each length of wood and the two are fitted together to form a right-angled cross.

The cross-beam is made from 2in. X 1in. wood and its length is made the same as the desired spacing between the two loops. The two cross elements are then screwed to the ends of this beam. At least two screws should be used at each end, to prevent rotation of the cross relative to the beam, and the screws are driven through the halved joint so that this is also made secure.

Coaxial cable is used for the loops, with the outer screen connected as the loop element. This gives larger diameter elements and tends to improve the bandwidth of the aerial. Quite good results can, however, be obtained when using ordinary flexible wire for the loops.

The wire is threaded through the holes drilled

(Continued on page 586)

# A Universal Alignment Method

A FORM OF ALIGNMENT PROCEDURE SUITABLE FOR THE MAJORITY OF SETS

By H. Peters

LET it be said at the beginning that this article is not intended to supplant or disparage the official alignment instructions which have been carefully worked out by the manufacturers for their individual receivers and wherever

sensitivity, or an oscilloscope. A damping unit, constructed from a large and small crocodile clip, a 680 ohm resistor, and a .001 mfd. (or greater) ceramic condenser. For receivers with vision A.G.C. the control line must be tied down to a steady value, and this can be done with a battery and a 10 to 50 K. ohm pot, as in Fig. 1(b). A grid bias battery is suitable, but a discarded 7.5 v. block from the portable radio is just as good.

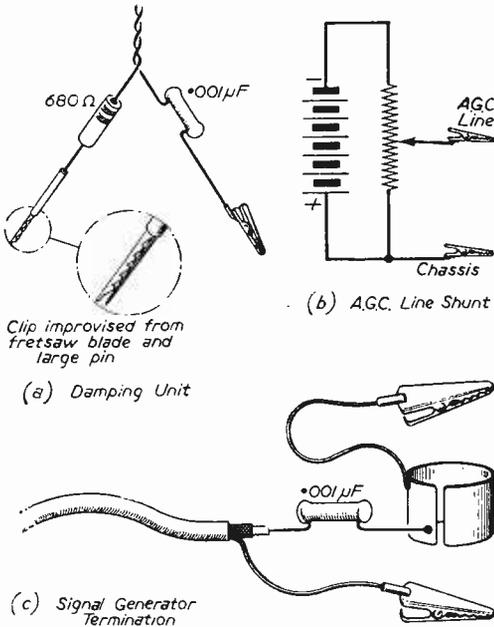


Fig. 1.—Extra equipment required.

practicable these should be rigidly followed. There are, however, several occasions when this is not possible, either because the instructions are not available, or because they involve using special equipment which is not to hand. On older receivers the specified sensitivity and bandwidth will probably be impossible to achieve without replacing so many valves and components that the job becomes uneconomic. It has been the writer's experience that the average viewer is far more contented with a nice creamy noise-free picture with a bandwidth of between 2-2.5 mc/s which is not riddled with sound on vision and which doesn't drift noticeably, rather than resolve an outstanding 3 megacycle grating and have to continually adjust the fine tuner and hold controls. To this end, and to save time when dealing with unfamiliar equipment, a form of alignment procedure has been devised which has so far produced satisfactory results on the majority of sets aligned.

## Equipment Required

The equipment required is simple. A modulated signal generator covering 7 to 40 megacycles and Band I. A multimeter with 1,000 ohm-per-volt

## Injection Points

To save time in finding the correct injection point the signal can be applied from the generator by means of a clip slid over the valve instead of the screening can (Fig. 1(c)). A greater signal is naturally needed than for direct injection, but it does simplify the equipment needed and is particularly useful where the set to be aligned works after a fashion (which is usually the case). The signal generator clip can then be pushed over the mixer valve and left in this position throughout the alignment. If the set is faulty or hopelessly out of alignment the signal will need to be injected at each successive grid starting at the last I.F. and working forward. As most modern sets have the chassis connected to the mains it is essential to ensure that the polarity is correct before connecting the signal generator. The chassis connection should be made to a soldered chassis point in preference to the chassis itself which may have oxidised to give poor contact.

## Meter Points

As long as the meter can give a good clear indication of maximum signal there is no objection to attaching it to any of several points in the circuit. A.G.C. and A.V.C. lines should be avoided, however, as the sound and vision A.G.C. systems are usually connected and this gives rise to misleading results.

On the sound I.F. strip the simplest place to insert the meter is across the loudspeaker

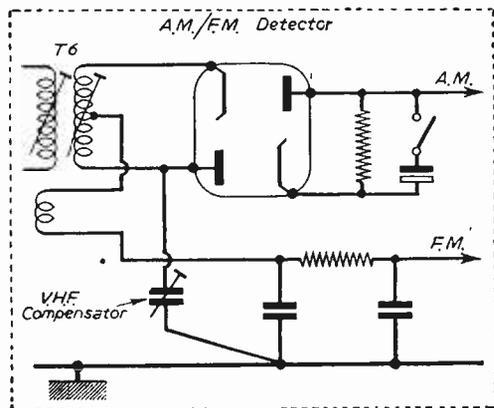


Fig. 2a.—Details of AM/FM detector.

terminals, on the lowest voltage A.C. range. Alternatively the meter can be connected across the D.C. side of the demodulator where a negative reading of between 1 and 10 volts should be expected. On the vision strip a suitable place to attach the meter is on the tube cathode or video amplifier anode (usually connected together). Here a standing positive voltage of between 60 v. and 120 v. is usual, which decreases with the applied signal. Thus when indicating maximum the meter needle moves backwards.

Another vision take-off point is at the output from the detector diode, where about 6 positive volts is to be expected.

**Sound.**—Assuming the majority case (i.e., where the set works up to a point), remove the aerial, or change to a vacant channel position, turn up sensitivity and contrast and inject a strong modulated signal at sound I.F. frequency using the clip pushed over the mixer valve. With the meter set to give a useful sound output indication and using a non-metallic trimming tool (see "Word of

Warning" farther on) tune T6 Fig. 2 secondary, T6 primary, T5 secondary, T5 primary, T4 secondary, and T4 primary (if tunable) in that order for maximum sound reducing the sig. gen. output progressively to prevent A.G.C. action. If this produces instability it denotes a fault in the strip such as a cracked ceramic decoupling condenser, or overcoupled coils in the I.F. transformers designed to give bandpass tuning. Eliminate faulty decouplers by bridging each in turn with a known good one before retuning the sound I.F.'s for bandpass as follows:

**Bandpass Sound I.F.'s.**—Connect the damping unit across T6 primary and tune T6 secondary for maximum. Transfer the damping unit to T6 secondary and tune T6 primary for maximum. Repeat with T5 and T4, damping the primary and tuning the secondary and then vice versa. To make this operation easier a condenser is fitted in series with the damping resistor and this can be taken to a central chassis point.

(To be continued)


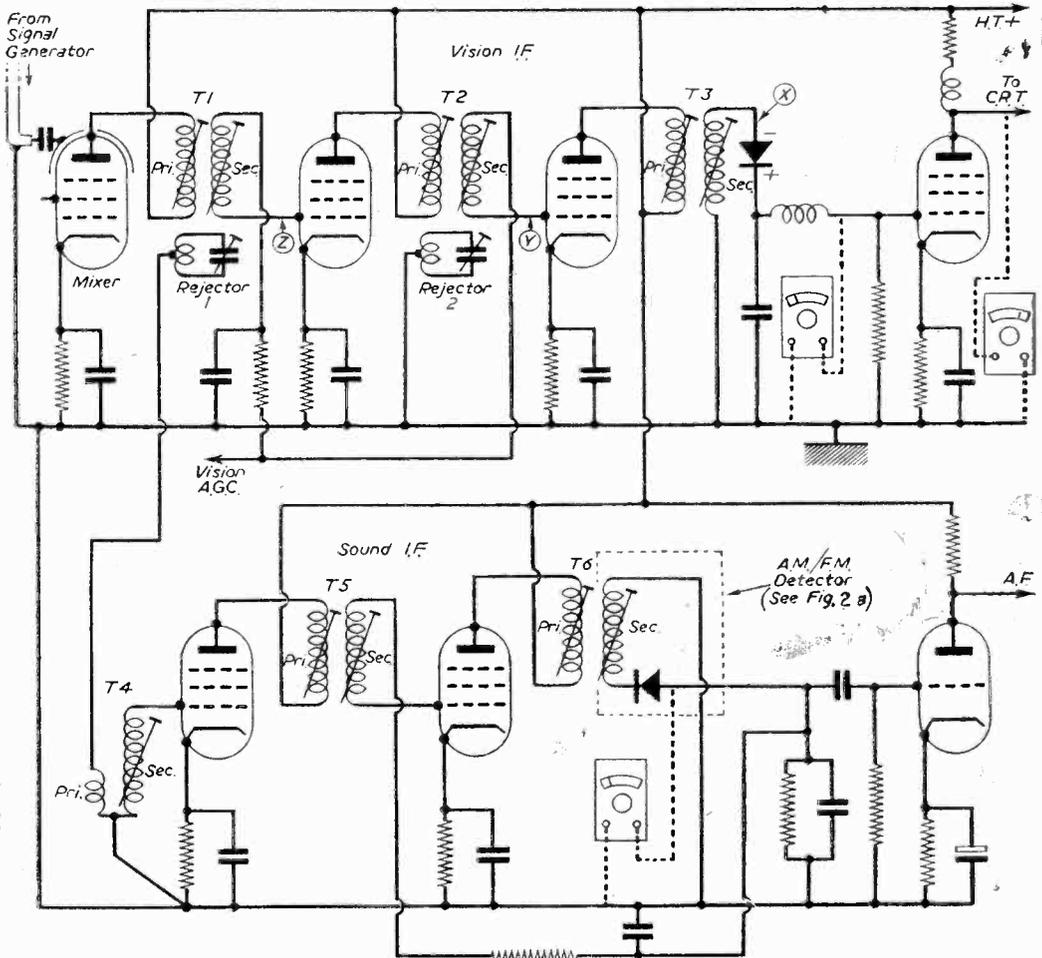


Fig. 2.—The circuit to which the text refers. (Typical but not practical.)

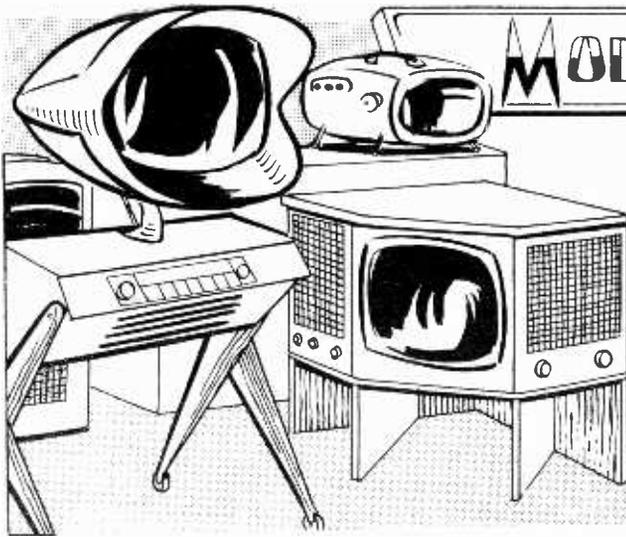

# MODERN TELEVISION

THIS ARTICLE, REPRODUCED FROM OUR FREE RECEIVER DESIGNED BY M. CH. BAUD. A F

to the base. Four chrome fillets, masking the joints of the angles, are arranged vertically between the two wood panels. Two black plastic plates conceal the chassis under the buttons and complete the assembly.

### Circuit Details

The entry circuit is of the symmetrical type, the aerial coil being coupled to the centre of the grid coil. The first stage, cascode, is neutrodyne by capacity, a solution which allows saving of a coil. The connecting circuit between the plate of the first triode and the cathode of the second is by a series coil, as is usually the case. The connection between the cascode and the frequency changer is by a classical band filter.

The oscillator is a Colpitts, fed with H.T. by means of a stop-coil with centre connection. The means of selecting vision and sound frequency have been mentioned above.

A sound rejector is placed in the cathode circuit of each of the three EF80 medium frequency vision amplifiers, the first rejector allowing selection of sound and controlling the grid of the first corresponding F.M. amplifier.

Video detection is by means of a diode crystal type G60 (Westinghouse) placed, together with the load resistance and the stop-coil, in the F.M. case.

The video stage comprises a single series correction coil, strongly damped, in the anode circuit of the EL83, together with a load resistance coil of 1,500 $\Omega$  (diameter 7 mm., length 50 mm.). A series correction coil with the load resistance has been suppressed to avoid unpleasant super-oscillation. This is a matter of taste, but we prefer a light degrading to a super-oscillation, however mild it may be.

The second F.M. sound stage has been largely "dampened." This stage required, at all costs, to detect by the grid and the C.A.V., and has been installed merely to stabilise it.

The L.F. detection and pre-amplification are done by a EABC80, one of whose diodes is not used. The diode with separate cathode is used to obtain negative tension, as will be seen later.

### Tone Control

Tone control is obtained by varying the scale of a selective back-reaction. The two speakers (17 cm.) are connected in parallel, giving an assembly with impedance of the order of 2.75  $\Omega$ . An output transformer for 2.5  $\Omega$  on the secondary suits very well.

The conversion of the H.T. is done by two PY82 valves, heated by a separate secondary giving 19 volts, one end of which is earthed. This potential of 19 volts is also converted, to "negative," by the separate cathode diode of the EABC80, then filtered and used as stabilised potential for the grid of the

### General Conception

THE ideal television set, like the ideal woman, does not exist. Nevertheless, in what follows, I will describe an apparatus that has been specially built for personal requirements. The set is built on a triangular chassis, and is a corner cabinet.

The feature that stands out is the F.M. amplification, vision and sound, designed to avoid clouding on band 10, which is used on some Continental transmissions. For this we have a F.M. circuit for sound on 36 Mc/s, and for vision F.M. on 47.15 Mc/s. The F.M. vision circuits are super-coupled transformers, the coupling regulated so as to obtain a total band of about 9 Mc/s. There is no tendency to cloud (a fault found in most commercial television sets), because the M.F. harmonics fall outside the band received, that is, between 189 and 200 Mc/s.

The erasing is done on anode 1 of the tube, which is a 43 cm., so that the modulation electrode becomes free for the application of anti-parasites by inversion of the signal, and possibly for push-pull operation of the tube, which may be tried later.

Correction of the video stage has been reduced to avoid all tendency to "silhouette." The response curve of this stage, verified by spot wobbler, is practically linear to near 12 Mc/s.

The L.F. part has been carefully studied and is furnished with a selective back-reaction to improve the response curve. The two speakers (Gego, type high fidelity sub-cone) are placed on each side of the screen and ensure excellent sound.

In the H.F. part there is a fine tuner, but only to obtain maximum gain from the oscillator section.

The controls shown are: fine tuning contrast, brilliance, volume of sound. The four small adjustable buttons correspond to concentration, tonality, line and image frequency. Finally, inside the chassis, there are two potentiometers for linearity and the one controlling the height of the image.

The cabinet consists of two triangular panels 20 mm. thick, of white oak lined with black and attached to the base with screws. The speakers are mounted on Isorel baffles, covered with tissue and also fixed

# RECEIVER DESIGN

THE CONTEMPORARY "TELEVISION" DISCUSSES A SPECIAL OTHER ADVANCED FRENCH DESIGN IS SHOWN OVERLEAF

6BQ6, and also for control of vertical linearity by displacement of the operative point of the pentode ECL80.

The separator stage uses a pentode ECF80, the triode of which acts as a vision detector and amplifier. The frame blocking oscillator uses the triode of the ECL80 and, with the mounting used it is practically impossible to detach the vertical timebase. There is nothing special to say about the vision power amplifier (pentode ECL80), which operates without fatigue with a high tension of 250 volts and includes a linearity correction by means of feed back.

On the side of the lines, one of the triodes of the 12AU7 amplifies and defines the synchronisation tops, while the other is mounted as a blocked oscillator. In regard to the final stage, using a 6BQ6, the E.H.T. and the deflection system, the arrangement is quite standard practice and we have not found it necessary to reproduce it entirely. The equipment used is of the brand OREGA. The screen tension of the 6BQ6 has been adjusted so as to have a T.H.T. of 14 kV.

A resistance of  $10\Omega$ , placed on the earth return of the 6BQ6 cathode, allows the measurement of the cathode output of the tube without modifying its operation and without disconnecting anything.

The erasing impulse is applied to the anode A1 of the tube-images. This impulse is selected with appropriate amplitude, and phase, at the "foot" of the roller grid of the blocked image oscillator.

It should be noted that the output sound transformer, firstly located on the F.M. plate, near the final valve EL84, has had to be taken off and placed much further away because its presence caused "sound on vision" by induction on the last F.M. vision transformer as soon as the level of sound was increased. Also, the image output transformer, placed under the tube, distorted the image by magnetic radiation.


## F.M. Coils

The super-coupled M.F. vision transformers are made on LIPA formers of 8 mm. diameter, normal model. The primary L1 comprises 15 turns, whereas the secondary L2 has about 12. The two rollers are arranged in "bees nests," and the coil L2 is arranged by interposing a layer of paper to slide along the tube.


The number of turns indicated above has been voluntarily fixed at a too high value, adjustment for the frequency of the F.M. band transmitted being done by progressive uncoiling of the turns, to allow for correct trimming.

At the beginning of the adjustment operation coils L1 and L2 are separated by at least 8-10 mm. Then they are brought together progressively, while adjusting agreement by the nut L2, until the desired curve is attained, and without touching the nut of L1. The spacing between L1 and L2 is normally of the order of 1 to 3 mm.

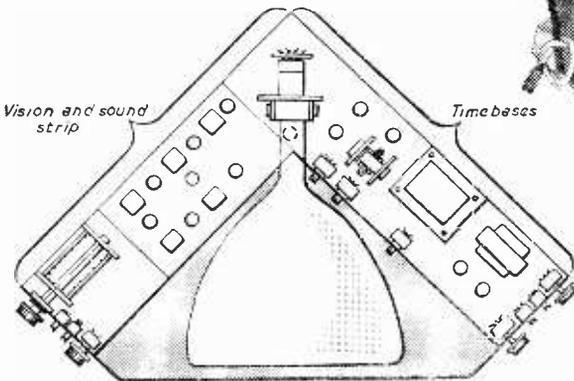This operation, which sounds complicated on paper, is relatively easy if use is made of a spot wobbler or a wobble-scope. The same result can be achieved with a non-wobbled generator and an output voltmeter by the point to point method, but more time is required. One should, of course, begin with the pre-detection transformer and move towards the input.




Plan view of the receiver.

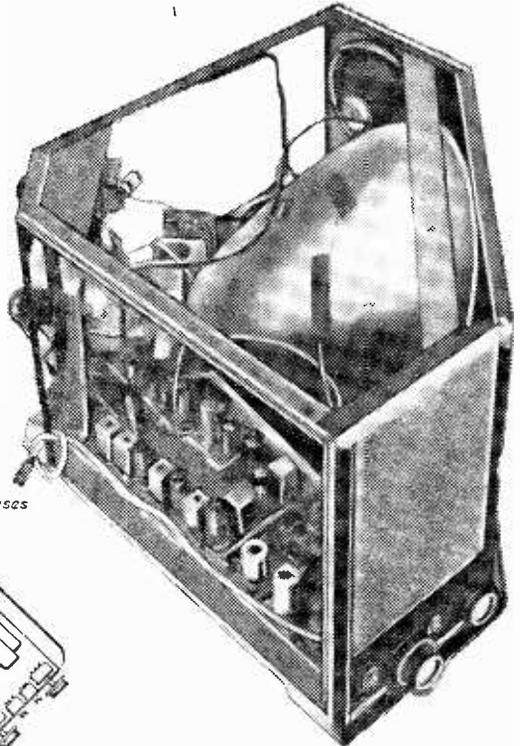

A side view showing the interior.
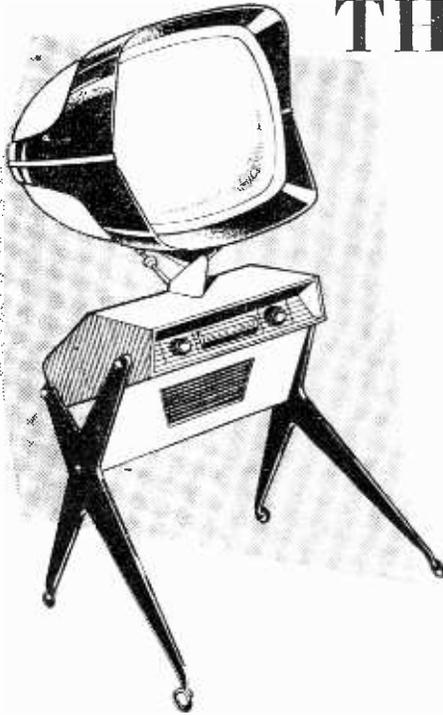
# THE TELEAVIA

ANOTHER FRENCH RECEIVER DESCRIBED IN  
OUR FRENCH CONTEMPORARY



A French design with panoramic screen.

**T**HE French firm of Teleavia which has already upset aesthetic preconceptions in regard to television cabinets with its visiered case has now produced the Teleavia with panoramic screen.

What are the real arguments in favour of this product, compared to table cabinets? Should the console be moved as easily as the tables on castors on which television cabinets are often placed? The shape of these pieces of furniture, their size and weight, are major obstacles to their mobility, even though they are on castors. Is the sound reproduction better? For table cabinets, the argument is that the loudspeaker, or loudspeakers are situated on the actual axis of the image. But this advantage is paid for dearly because it must not be forgotten that, to reach up to the axis of the screen, nowadays situated at some 80 cm. from the floor, one would practically need to have a cupboard.

This makes it necessary to look at television while seated in a low armchair. This requirement can be very inconvenient, and not even always possible.

These were the ideas that caused "Teleavia" to solve the problems posed, and they have done it in a particularly audacious way.

The thing that strikes one at once, in examining the "Teleavia" cabinet, is the large 54 cm. cathode tube, totally enclosed in truly aerodynamic fashion by two plastic half-shells. This assembly rests on a very low cabinet containing the chassis, connected to it by an articulated system allowing the screen to be aimed in all directions.


The cabinet itself is supported by two legs equipped with semi-spherical rollers. On the front face of the cabinet an attractive gold instrument panel groups together all the control buttons. The loudspeaker is

mounted on a large baffle located between the legs. The ensemble is very harmonious in appearance and comprises two tints.

Let us examine the advantages of this assembly: the most important of these is the mobility of the screen both horizontally and vertically. As the screen is at an average height of 1.15 metres from the ground, it can be adjusted perfectly towards spectators, whatever may be their position in relation to the apparatus. Now here is a sensible thing. Furthermore, this directional movement allows the screen to be adjusted, if necessary, so as to eliminate undesired reflections impairing view. The mask of the tube discretely emphasises the surround of the screen, without excessive heaviness, so giving the impression of a much larger image.

The centre of gravity of the console has been particularly carefully studied, and movement is very easy. The sound comes from the axis of the picture, which reinforces the effect of presence.

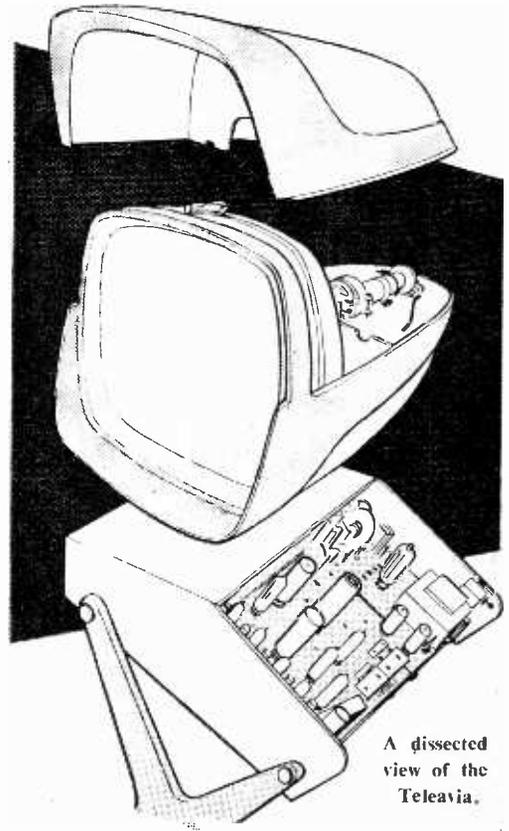It should also be noticed that by this arrangement the cathode tube is particularly well protected from dust.



A dissected  
view of the  
Teleavia.



# Serviceing TELEVISION RECEIVERS

No. 39—A SELECTION OF MODELS IN THE G. E. C. RANGE

By F. E. Apps

critical. In cases of this sort a slight adjustment of L18, auto transformer to grid of V3, will cure the trouble. L18 is directly behind sensitivity control on the sub deck.

### Additional Notes on Models BT1746 and BT4743

Some of these models are fitted with G.E.C. 7201A tubes and others with Mullard 36-24 tubes. Besides having different bases there are several other points that should be noted if tubes are changed over. The Mullard tube has an ion trap whereas the G.E.C. use a magnet to correct neck cut-off, i.e., corner shadowing. Should a Mullard tube be fitted in place of a G.E.C. the following circuit corrections should be made. Delete C73 and C96.

### Adjustment of Beam Centering Magnet

The adjustment of this magnet (on G.E.C. tubes 6901A and 7201A only) is different from that of an ion trap. The magnet should be positioned not for maximum brightness but for freedom from neck shadowing. The magnet should be positioned as near the cap of tube as possible and then rotated and, if necessary, moved slightly forward along the neck with further rotation until best position is found. Do not go too far forward, otherwise it will be impossible to centre the picture. The brightness should not be affected if magnet is correctly positioned. The arrow on magnet should point towards the screen.

### Changing of Valve V2

This valve, the frequency changer, may be either a PCF82 or an LZ319. If a PCF82, C23 is 16 pfd, but if an LZ319 it should be 10 pF.


**T**HERE are many other models marketed by the G.E.C. that have an identical chassis, with some minor modifications, to the 1746. They are the BT4743, which is a console model with a 14in. tube, the BT5643, which has a 16in. tube and has a different valve line-up. Here V11, V13, V15 and V17 are PL82, KT36, U25 and PL82. Some components have different values. They are R49 the cathode bias resistor of the sound output valve, which now becomes 270 ohms and the line output valve screen feed resistor which is now 1.8K ohms. Also C79 and R71 across L32 width coil become a single 12K ohm resistor only, and a 50 pF 5Kv P.S.M. capacitor is fitted from V14, booster diode, cathode, to chassis.

Model 2745 has a 7401A, 17in. tube, and the differences in circuit from 1746 are R51, C68 and C96 which are missing. The first two are in brightness circuit and the other C96 from heater of EHT rectifier U43 to ground. R50 22K now goes direct to the slider of brightness control. R55 to vision interference limiter becomes 100K and R58 connected to hot end of brightness control becomes 56K. Some 2745 receivers have a Mullard 43-64 tube, in which case pins 7 and 11 of the tube are connected.

Model 8640 has a 16in. 6901A tube. With this model R51 and C68 are missing. R50 is connected to slider of brightness control. R55 is 100K and R58 is 56K ohms.

Model 1252 has a 14in. tube, 7203A, and although the chassis are similar the I.F. frequency is different from the 1746, which is 35.625 Mc/s. In the 1252 it is 36.15 Mc/s. In some of these sets the video amplifier cathode bypass is 1200 pF or sometimes two 815 pFs in parallel.

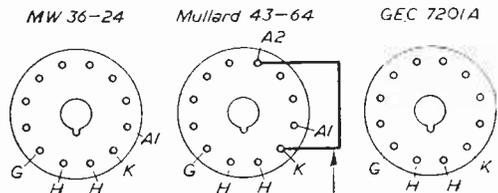Models 5248, 5347 and 8245 are all consoles with 17in. tubes but with a different style of cabinet. The Band III A and B core adjusting screws on the tuner units are fitted with slotted plastic knobs. Vision may be troublesome to eliminate, especially as oscillator setting is very



In Model 2745 pins 7 and 11 are joined  
Cathode ray tube base connections.

### Alignment Notes for Model BT1252

For Band III channels adjust oscillator trimmer for maximum sound. Adjust aerial and R.F. trimmers for maximum picture brightness. Readjust oscillator for maximum sound on vision. Readjust aerial and R.F. trimmers for optimum picture.

### For Band I Channel

Adjust gauged tuning control to give best sound with optimum picture. When making last adjustment turn control in anti-clockwise direction and then a slight turn clockwise. Number of turns in a clockwise direction for any Channel 1 to 5 are as follows, starting from Channel 1 as zero, i.e., as when despatched. Channel 2, 4½ turns; Channel 3, 6¾ turns; Channel 4, 9¼ turns; Channel 5, 11¾ turns. The Band I core adjusting screws are connected together by a bar. This bar is controlled by a fourth screw at the end of the gauging mechanism. Thus all three tuning cores

are operated together. The screw is accessible through a hole in side of base board assembly near the fine tuner control. The oscillator core for Band I should not be touched. This has been pre-set in the factory and normally will remain O.K.

### The I.F. Link in Model 1252

This "link" consists of L12 and L18, is very critical and normally should not be touched or adjusted. Should they, however, be altered accidentally, readjustment can be made as follows. Connect a D.C. voltmeter to anode of video valve and chassis. Connect an A.C. voltmeter across primary winding of output transformer. Feed an unmodulated signal of 36.15 Mc/s into I.F. input socket of I.F. sub deck and adjust L18 for maximum vision response. Reconnect the I.F. "link" between tuner and I.F. subdeck and feed an unmodulated signal at I.F. vision frequency, i.e., 34.65 Mc/s. to control grid of V2A (pin 2), then adjust L12 for maximum vision response.

## CLOSED CIRCUIT TV

To Make Passenger Announcements at West London Air Terminal

FOR the first time in Europe television is to be used to make passenger announcements at an air terminal. West London air terminal, the London air terminal of B.E.A. and most other European air lines, has installed a closed-circuit television system so that flight announcements and general information can be presented to passengers in a more personal manner. Attractive announcers will be seen giving details of flight departures, which will be followed by a caption repeating the information for the assistance of passengers.

When the screens are not required for announcements they will be used for advertising purposes. Mr. I. C. Pannaman, of Audio and Video Rentals, Limited, the firm which is providing and operating the system, said today: "Other air terminals have already shown an interest in the use of television for making passenger announcements, and it is expected that several other places in the British Isles will follow the lead given by Air Terminals, Ltd., who run the terminal for B.E.A." The installation consists of eight 21in. contemporary Pye receivers—five in the upstairs passenger lounge, and three in the main hall on the ground floor. A small studio with a miniature Pye television camera will be staffed by one camera operator and an announcer. The "station" will be in use from six o'clock in the morning until 10 o'clock at night.

### Revolutionary Results

Although television is already firmly established in industry and research, it is as a public relations and advertising medium that some revolutionary results are likely in the near future. Already, for example, Madame Tussaud's in Blackpool have installed a TV system to show holiday makers on the promenade the attractions inside the waxworks. Pictures of the controversial Epstein statue, "Genesis," as well as a wide variety of figures, are displayed on screens in the window to entice the public into the establishment.

The new West London air terminal installation provides another example of how the scope of

"poster" advertising may well be widened in the near future to include a second and third dimension of sound and movement.

## CUBICAL QUAD AERIAL

(Concluded from page 579)

in the support arms and in the case of the reflector loop the ends are soldered together. For the driven loop the two ends are supported on a small board and connected to the feeder cable. A small perspex or paxolin board is used to support the cable joint, and the two ends of the loop and the end of the feeder cable are clamped to this board with cable buckles or some similar form of clamp. The two ends of the loop are then soldered to the core and screen of the cable with the lower end of the loop connected to the screen. In the case of vertically polarised aerials the joint to the cable is made exactly halfway up one of the vertical sides of the aerial. For horizontally polarised aerials the joint is made at the centre of the bottom side of the aerial loop.

For indoor installations the cable should be taken off at right angles to the loop. In the case of outdoor installations the cable is taken back to the centre of the boom and clamped there before it runs down the mast.

After the cable joint has been soldered the join should be covered with wax to keep out moisture. If the aerial is to be used outside, the woodwork should be painted to protect it against the weather.

An alternative method of construction which may be used in the loft is to support the two loops at their corners by means of cords fixed to the rafters and joists in the loft. The two loops must be placed at the correct spacing and must be aimed in the right direction.

The aerial should be positioned with the cross beam pointing in the direction of the station and the driven loop nearest to the station. In cases where ghosting or ignition interference are present the position of the aerial may have to be altered to reduce these effects, provided there is sufficient signal available.

# NEW 1958 EDITION

COLOSSAL VALUE!

NEWNES

## Radio and Television Servicing

# OVER 2000 POPULAR MODELS

Claim yours now  
**7 Days' FREE Examination**

TELEVISION AND RADIOMEN—this is your opportunity to possess the biggest money-maker in radio. Here, ready for immediate use, are over 3,600 circuit, component and layout diagrams—TV receivers and converters from single-station sets to the latest 13-channel *printed-circuit* models; radios, radiograms, portables, car radios, record-reproducers, including transistor and VHF/FM models. **And in addition—LARGE QUICK-REF FOLD-OUT CHARTS and Valve & Picture-Tube Data.** It's yours **FREE** for 7 days—Hurry, send the coupon to-day!

6 VOLUMES  
**3,600**

CIRCUIT, COMPONENT & CHASSIS DIAGRAMS

### TELEVISION SERVICING DATA for—

Acc, Alba, Ambassador, Argosy, Baird, Banner, Beethoven, Brayhead, Bush, Champion, Cossor, Decca, Defiant, Ekco, E.M.I., English Electric, Ferguson, Ferranti, G.E.C., H.M.V., Invicta, K-B, McCarthy, McMichael, Marconiphone, Masteradio, Murphy, Pam, Peto Scott, Philco, Philips, Pilot, Portadyne, Pye, Rainbow, Raymond, Regentone, R.G.D., Sobell, Spencer-West, Stella, Strad, Ultra, Valradio, Vidor, White-Ibhotson.

**3,500 PAGES**

PLUS


**2 YEARS' POSTAL ADVISORY SERVICE**

★ **FREE** ★  
**Handy Enlarger**

Just what you need to follow intricate circuits easily—magnifies small print, too. Sent boxed with lens polisher.

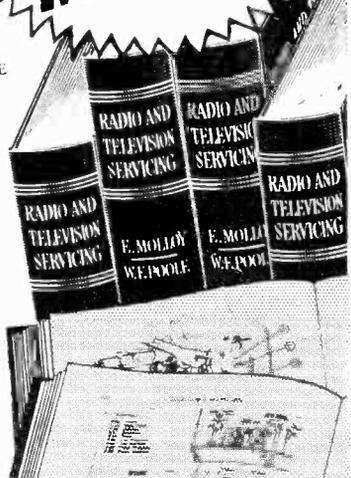
### RADIO SERVICING DATA for—

Acc, Alba, Ambassador, Argosy, Armstrong, Banner, Beethoven, Berce, Bush, Champion, Cossor, Decca, Defiant, Eddystone, Ekco, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, H.M.V., Invicta, K-B, McCarthy, McMichael, Marconiphone, Masteradio, Motorola, Murphy, Pam, Peto Scott, Philco, Philips, Pilot, Portadyne, Pye, Pye Telecommunications, Radiomobile, Raymond, Regentone, R.G.D., Roberts' Radio, Sobell, Stella, Strad, Ultra, Vidor, Webeor.



"One glance only was enough to convince me of its worth" (J. F. B., Leicester).  
"A boon and a must" (J. S., Manchester).  
"Has more than repaid the cost in a short period" (E. J. S., Wolvercote).

## ACT NOW

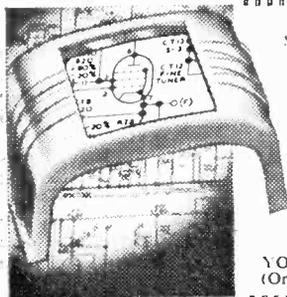

George Newnes, Ltd., 66-69 Great Queen Street, London, W.C.99.  
Send RADIO & T.V. SERVICING without obligation to purchase. I will return it in 8 days or send 10/- deposit 8 days after delivery, and you will then send the ENLARGER. Thereafter I will send twenty monthly subscriptions of 10/- paying £10 10s. 0d. in all. Cash price in 8 days £10.

NAME .....  
ADDRESS .....  
OCCUPATION .....  
YOUR SIGNATURE ..... (Or your Parent's Signature if under 21)  
Place X where it applies  
House-OWNER  
Householder  
Living with Parents  
Lodging Address

# LASKY'S RADIO

## MAKER'S SURPLUS COMPONENT BARGAINS

- WIDE ANGLE 33 mm.**  
 Line E.H.T. trans. Ferro-cube core, 9-16 kv. .... 25/-  
 Scanning Coils low imp. line and frame. .... 25/-  
 Ferro-cube cored Scanning Coils and Line Output Trans., 10-15 kv. EYSL winding. Line Trans. with circuit dia. part. .... 50/-  
 Frame Output Transformer Scanning Coils low imp. line and frame. .... 6/6  
 Frame of line block osc. Transformer. .... 4/6  
 Focus Magnets Ferro-cube P.M. Focus Magnets, Iron Cored. .... 19/6  
 Duomas Focaltisers. .... 22/6  
 300 ma Smoothing Chokes. .... 15/-

### STANDARD 35 mm.

- Line O.P. Trans. No. E.H.T. 12 6  
 Line Output transformers 6.9 kv. E.H.T. and 6.9 v. winding. Ferro-cube. .... 19/6  
 Scanning coils. Low imp. line and frame. .... 12/6  
 Ditto by Irganic. .... 14/9  
 Frame or line block oscillator transformer. .... 4/6  
 Frame output transformer 7/6  
 Focus Magnets: Without Vernier. .... 12/6  
 With Vernier. .... 17/6  
 200 ma Smoothing Cores 10/6

## Another Lasky Special! WOLSEY BAND 3 CONVERTER

LIST  
 £19/16  
**LASKY'S PRICE**  
**£5/19/6**



Post & Pkg. 3/6

Available on Credit Sales terms: 25/- deposit and five monthly payments of 25/-.

The famous WOLSEY is a Converter of the highest efficiency and TUNABLE OVER ALL 13 CHANNELS. Incorporates own power supply for 200-250 v. A.C. mains. 2 valves, cascade R.F. amplifier PCC34 and PCF80, metal rectifier. Handsome ivory plastic Case, 7 1/2" x 3 1/2" x 4 1/2". Brand new in maker's cartons. Limited quantity only. Send to-day!

**13-CHANNEL ADAPTOR** (superhet Front End Tuner) at 49/6, post 3/6. See June advt. for details. Few only left.

**C. R. TUBES**, new, unused. 14", £14.19.6. 17", £16.19.6. 12", £8.19.6. 9", £5.17.6. Carr. & ins. 22/6.

MAIL ORDERS TO HARROW ROAD, PLEASE  
**LASKY'S (HARROW RD.) LTD.**  
 42, TOTTENHAM COURT ROAD, W.1.  
 Telephone: MUSSEUM 2805.

370, HARROW ROAD, PADDINGTON, W.9.  
 LADbroke 4075 and CUNNINGHAM 1079.  
 Open all day SATURDAY. Half day Thursday.

## SPEAKER BARGAIN

Special Purchase of Plessey P.M. Speakers, 5" round or 7" x 4" elliptical. Lasky's Price **14/6** Post 1/6.

## SPECIAL OFFER OF SOLDERING IRONS

SOLON, ex-Govt., new and unused. Pencil bit. 65 watts, 220-250 v. A.C./D.C. List 27/6. Lasky's Price **16/6** Price

Post 1/6. Spare Bits, 1/- each. Spare Element (state voltage), 5/9.



## COLLAR 4-SPD. MIXER AUTO-CHANGERS

RC. 456, incorporates auto and manual control. Complete with Studio crystal P.U. and sapphire stylus. List £13/17/- Lasky's Price **£7.19.6** Post 3/6.

RC. 457 or "Continental," £8.19.6. Post 3/6.

B.S.R., type UA8, 4-spnd., with latest B.S.R. full-f P.U., £7.19.6. Post paid.

# RADIO SUPPLY CO. (LEEDS)

(opposite

LTD., Dept. N, MAUDE ST. parish church school), LEEDS 2.

Post Terms C.W.O. or C.O.D. NO C.O.D. under £1. Postage 1/9 extra under £2. 2/9 under £5. Open to callers 9 a.m. to 5.30 p.m. Sats. until 1 p.m. S.A.E. with enquiries, please. Full list 6d.; Trade list 5d.

## R.S.C. TRANSFORMERS

- Fully Guaranteed Interleaved and Impregnated.  
**Primaries 200-230-250 v. 60 c/s screened**  
**FOR SHROUDED PENTODE THROUGH**  
 230-0-230 v 80 ma. 6.3 v 4a. 5 v 3a ... 16/9  
 350-0-350 v 80 ma. 6.3 v 4a. 5 v 3a ... 18/9  
 200-0-250 v 100 ma. 6.3 v 4a. 5 v 3a ... 23/9  
 350-0-350 v 100 ma. 6.3 v 4a. 5 v 3a ... 23/9  
 350-0-350 v 150 ma. 6.3 v 4a. 5 v 3a ... 29/9  
**FULLY SHROUDED UGRIGHT**  
 250-0-250 v 80 ma. 6.3 v 2 a. 5 v 2 a ... 17/9  
 250-0-250 v 100 ma. 6.3 v 4a. 5 v 3a ... 26/0  
 250-0-250 v 100 ma. 6.3 v 6 a. 5 v 3 a ... 31/-  
 For R1355 Conversion ... 23/9  
 350-0-350 v 100 ma. 6.3 v 4a. 5 v 3a ... 29/9  
 350-0-350 v 150 ma. 6.3 v 4a. 5 v 3a ... 33/9  
 425-0-425 v 200 ma. 6.3 v 4a. C.T. 6.3 v 4a, C.T. 5 v 3a ... 49/9  
**FLAMELESS TRANSFORMERS**  
 All with 200-250 v 50 c/s Primaries: 1.5 a, 5/9; 6.3 v 2 a, 7/6; 0-1-5.3 v 2 a, 7/9; 12 v 1a, 7/11; 6.3 v 3a, 8/11; 6.3 v 6a, 17/9.  
**CHARGER TRANSFORMERS**  
 200-250 v 0-9-15 v 1 a, 11/9; 0-9-15 v 3 a, 16/9; 0-9-15 v 5 a, 18/9; 0-7-15 v 6 a, 22/9.

- OUTPUT TRANSFORMERS**  
 Standard Pentode 5.00 to 5 ohms ... 4/9  
 Small Pentode 5.00 to 3 ohms ... 3/9  
**SMOOTHING CHOKES**  
 250 ma 5 h 50 ohms ... 11/9  
 100 ma 10 h 250 ohms ... 8/9  
 80 ma 10 h 350 ohms ... 5/6  
 67 ma 10 h 400 ohms ... 4/11  
**SELENIUM METAL RECTIFIERS**  
 250 v 250 ma, 11/9; 120 v 40 ma, 4/11;  
 612 v 2 a F.W., 4/11; 240 v 50 ma, 3/9;  
 612 v 2 a F.W., 8/9; 612 v 4 a, 14/9; 250 v 80 ma, 7/9; 612 v 6 a F.W., 18/9; 612 v 10 a, 25/9; 612 v 15 a, 35/9; 21 v 2 a, 14/9.  
**CO-AXIAL CABLE IN.**  
 75 ohms 14/36 ... 8.1. yd.  
 Twin-screened Feeder ... 11d. yd.

**BATTERY SET CONVERTER KIT**  
 All parts for converting any normal type of Battery Receiver to A.C. mains 200-250 v. 50 c/s. Supplies 120 v, 90 v or 60 v at 40 ma. Fully smoothed and fully smoothed L.T. of 2 at 0.4 a to 1 a. Price, including circuit, 49/9. Or ready for use, 9/9 extra.

**ALL DRY RECEIVER BATTERY ELIMINATOR KIT**—All parts for the construction of a unit (metal-case 51-41-2in.) to supply Battery Portable receivers requiring 90 v and 1.5 v. Fully smoothed. From 200-250 v 50 c/s mains. Price, inc. point-to-point wiring diagrams, 39/9. Or ready for use, 49/9.

**EX-GOVT. DOUBLE WOUND STEP UP/STEP DOWN TRANSFORMERS**  
 100-0-100-220-240 v to 5-0-75-115-135 v or REVERSE. 8j-10j watts. Only 12/9, plus 2/9 post. 100-0-100-220-240 v to 9-0-110-122-136-148 v or REVERSE. 20j watts, 35/9, plus 7/6 carr. Both 50 c/s.

**EX-GOVT. CASES**, Well ventilated, black crackle finished, undrilled cover. Size 14 x 10 x 8 in. high. **IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE.** OR COVER COULD BE USED FOR **AMPLIFIER**. Only 9/9, plus 2/9 postage. Size 13j x 8j x 6 1/2 in. with undrilled perforated cover finished stoved grey enamel, 7/9, plus 2/9 post.

## EX-GOVT. VALVES (NEW)

1R5	7/9	6J5	4/9	6AT6	7/9
1T4	7/9	6KT6	3/9	DF36	8/9
1S5	7/9	6QT6	9/11	EBC33	6/9
3S1	8/9	6XSGT	7/9	EB31	8/9
5Y3G	7/9	6SN7CT	8/9	ECC91	4/6
5U4G	8/9	6L8G	11/9	EP80	4/9
6J5G	4/9	8J7	7/9	EP50	4/9
6K8G	9/9	12A6	7/9	EL32	3/9
6STJGT	6/9	2524G	9/9	EL81	10/6
6V8G	7/9	35Z4	6/9	EL91	11/9
6U5G	3/9	MH1	4/9	KT66	10/9
				SP61	2/9

## EX-GOVT. MAINS TRANSF.

Removed from New ex-Govt. units. Primary 0-200-130-230 v. Secs 275-0-275 v 100 ma, 6.3 v 7 a, 5 v 3 a **21/9**

- All 200-250 v 50 c/s input.  
 230-0-230 v 80 ma, 12.6 v 1.5 a, 5 v 2 a ... 11/9  
 250-0-250 v 150 ma, 5 v 3 a ... 16/9  
 350-0-350 v 160 ma, 6.3 v 5 a, 5 v 3 a ... 27/9  
 400-0-400 v 250 ma, 5 v 2 a, 5 v 2 a ... 15/9  
 450-0-450 v 150 ma, 6.3 v 5 a, 6.3 v 1 a, 5 v 3 a ... 20/9  
 450-0-450 v 250 ma, 6.3 v 3 a, 6.3 v 1 a, 5 v 6 a ... 49/9  
 12.5 v 3 a, 5 v 3 a ... 13/9

## EX-GOVT. SMOOTHING CHOKES


- 80 ma 10 h 150 ohms ... 3/11  
 100 ma 5 h 100 ohms Tropicalised ... 3/11  
 100 ma 8-10 h 100 ohms Parmeko ... 6/-  
 120 ma 12 h 100 ohms ... 9/9  
 150 ma 6-10 h 150 ohms Trop. ... 6/9  
 150 ma 10 h 150 ohms ... 11/9  
 100 ma 20 h 230 ohms ... 19/9

## ELECTROLYTICS (NEW)

Tabular	1/9	Can Type	2/11
8 mfd 450 v	1/9	8-8 mfd 450 v	2/11
16 mfd 450 v	2/9	8-16 mfd 450 v	3/11
8-16 mfd 500 v	4/11	16-16 mfd 450 v	4/11
25 mfd 25 v	1/3	32-32 mfd 350 v	4/9
50 mfd 12 v	1/3	32-32 mfd 450 v	5/9
50 mfd 50 v	1/9	150 mfd 450 v	5/9
100 mfd 25 v	2/9	100-100 mfd 350 v	5/9
3,000 mfd 6 v	3/9	100-200 mfd 275 v	6/11
6,000 mfd 6 v	3/11		

**BATTERY CHARGERS**—For mains 200-250 v 50 c/s. Output for charging 6 v or 12 v at 1 amp. In strong metal case. Only 27/9. Above can also be used for electric train power supply.

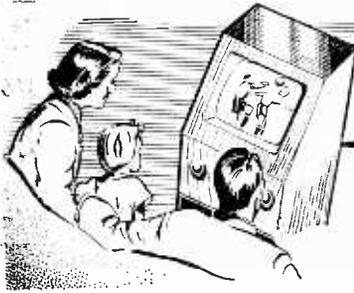**D.C. SUPPLY KIT**—Suitable for Electric Trains. Consists of mains trans. 200-250 v 50 c/s. A.C. 12 v 1 a Selenium F.W. Bridge Rectifier. 2 Fuseholders. 2 Fuses. Change Direction Switch. Variable Speed Regulator. Partially drilled Steel Case. and Circuit. **29/9**



## UNDERNEATH THE DIPOLE

TELEVISION PICK-UPS AND REFLECTIONS

By Iconos

**The George Mitchell Glee Club**  
**O**NE of the brightest and slickest musical half-hours of the week is the George Mitchell Glee Club. This is notable for its professional polish in all departments, particularly the very original production work of Russell Turner and the dance arrangements of Dennis Bettis. The producer is not afraid of playing with technical tricks, such as "inlay" and "overlay," which are cleverly introduced into some of the musical numbers. I particularly liked the electronic trick which gave the effect of little figures, cut out of newspaper, dancing and singing. But, of course, the backbone of the show is the fine singing of the George Mitchell vocalists, whether in a straight number or in a speeded-up comedy sound effect.

### Versatile Engineers

**T**HE Wales and West I.T.A. Station is now running very smoothly, steadily gaining "customers" both in the number of viewers and the lengthening of the queue of advertisers wishing to book space. Walter Kemp, the genial young engineer who did such a lot of development work for the BBC and for High Definition Films on telerecording, combines the job of Chief Engineer with that of General Manager of the studios. Assisted by a first-class engineering team, he selected and installed what he considered to be the best equipment for each particular job in the electronic chain rather than give the technical equipment contract to one firm as a "package" deal. Thus, when I visited the station recently I was interested to see a mixture of Marconi, Pye and E.M.I. television cameras and control equipment, with E.M.I.

and Cintel telefilm apparatus, all operating together in a first-class manner. Kemp has added a small 16mm. film department, which secures news shots, puts them through an automatic developing apparatus about the size of a large home washing machine, and adds them as a local supplement to the Independent Television News. The main studio, 60ft.  $\times$  80ft., is first-class, too, with about 40 dimmed lighting circuits controlled through one of those fascinating Strand Electric organ controls. Here the lighting engineer sits and does his job by pressing keys and pushing pre-set memory tabs of lighting arrangements. He is the equivalent of the lighting cameraman of the film studios, a man who must have a feeling for composition, tonal values and artistic expression, backed up by sound knowledge of electronics. There aren't many of this type of art-crafty engineers about.

### Telecine Equipment

**I** WAS agreeably surprised at the quality of the telecine transmissions I saw, both of 16mm. and 35mm. film. The Cintel flying-spot scanner was excellent as usual, but I was particularly interested in the highly satisfactory results on the E.M.I. Vidicon telecine equipment, of which there are two at this studio. It now appears to me that, given a really good print, first-class quality and sharpness can be obtained with 16mm. film. The major difference seems to be in a slight unsteadiness which seems to haunt the 16mm. picture. This is probably due to the fact that almost all the 16mm. projectors used for telecine in this country are designed for occasional home or classroom use, not for heavy duty professional opera-

tion, hour after hour, week after week.

### Jack Hylton

**J**ACK HYLTON, famous impresario and ex-dance band leader, has certainly gone into television in a big way. His various live and filmed television features have steadily grown in popularity, particularly his *Monday Show* and *Thursday Show*. Hughie Green achieved a terrific come-back in the *Double Your Money* programmes, and Jack Hylton, always a shrewd judge of top-talent, recently starred him in *The Monday Show*. Hughie is a fine commentator and interviewer, able to draw the best out of his interviewees and ever ready with the impromptu "ad-lib" line or gag, if the interview shows signs of flagging. This was hardly the case when he was interviewing that grand old actor, A. E. Matthews, or the taxi-driver Fred Borders. The rapid exchange of observations and opinions was an exposition of the television interview at its liveliest best. Jack Hylton has gradually built up a fine programme organisation of script writers, producers and production personnel and his influence in the I.T.A. field will continue to grow. It is significant that he is one of the largest shareholders in T.W.W., a programme company which is quite independent but has an arrangement for interchange of programmes with Granada.

### Television Society

**T**HE Television Society's annual dinner at the Dorchester was one of the pleasantest social events of the year, attended by professional and amateur television engineers and their ladies, who mingled with guests from the stage.

screen, art, advertising and equipment worlds. Sir George Barnes, the new President, introduced the speakers, which included Sir Charles Wheeler, President of the Royal Academy, Sir Harold Bishop, the BBC's Director of Technical Services and Sir Donald Wolfitt.

One of the high-spots of the evening was the presentation of the Society's medal to Cliff Michelmore, as the television personality of the year. As was to be expected, Cliff responded with an "off the cuff" speech given in that pleasant relaxed manner which has won for him such a large circle of viewers for *Tonight*. Not many interviewers—or actors, for that matter—succeed in achieving the blessed state of complete relaxation in front of the television camera, and at the same time do their particular job in hand. Ludovic Kennedy, Perry Como, Tony Hancock and Mac Hobbey are a few of the people who have achieved it. Notice that they are all men!

This television function formed a suitable prelude to the first European Television Exhibition, which commenced a day or so later, not far away, in Park Lane House.

### The I.T.A. Network

IT is quite natural that advertisers prefer to book commercial "slots" with the provincial area programme companies at peak viewing times, when they expect their commercials to be fitted into slots in well-established programmes, known to have high audience ratings by the Nielsen or TAM organisations. The Independent Television Authority keeps a fatherly eye on the activities of the provincial programme companies and insists that the quota of programmes of local origin shall not be less than 15 per cent. of the total programme time each week. This means that Cardiff, Manchester, Glasgow and the other provincial I.T.A. centres must put on at least  $5\frac{1}{2}$  hours of local material a week. It doesn't sound much, but it is not easy to achieve without a large staff, plenty of equipment and adequate stage space for rehearsals as well as the actual shows. Week after week, top viewing ratings have been taken by "The

Army Game" (Granada), "Take Your Pick" (A-R) and "Emergency Ward 10" (A-TV), and it is only natural that these and similar programmes should be largely sought—and bought—by the other programme companies.

### Regional News

SINCE the Independent Television News started operations, its popularity has grown and the average weekly time allocated to it has increased from 160 minutes to 185 minutes. In the Midlands, Northern and Welsh areas, the local programme companies add about five minutes a day of local news supplement, a popular item which contributes about half-an-hour a week to the 15 per cent. local programme quota. This is either locally shot 16mm. film or live news or interviews in the local studio, 16mm. film, processed in the local studio, with its sound recorded on a magnetic strip on the same film, opens up great possibilities for increasing local news coverage and providing "open air" items for regional non-advertising magazines. It is a very economical operation, since only negative picture is required—positive pictures being obtained from transmission, merely by a phase reversal switch.

### The Provincial Touch

BOTH the BBC and the I.T.A. programme organisations have taken practical steps to reduce the near-monopoly of the television programmes by their London Studios. Almost every month, the BBC or I.T.A. seem to be announcing the opening of new television studios in provincial centres. Nevertheless, the regional influence is not often felt, especially during the peak hours of viewing. Local contributions seem to be principally confined to the day or early evening, restricted to the area of origin and rarely networked to the nation.

As might be expected, the I.T.A. programme companies in provincial regions "rubber stamp" the London network programmes less than the BBC provincial centres. Indeed, quite a lot of Granada, A-TV and ABC-TV network presentations come from their studios in Manchester and Birmingham. It

is significant, however, that Granada's London "branch" studio at the Chelsea Palace is often used for "Granada From the North" programmes, and this important theatre studio has also been hired by ABC-TV. Programmes from T.W.W. and Scottish Television are not often seen in the London area, though some of them are highly popular in their own areas.

### Developing Machine

A very simple developing machine has been designed by Newman and Guardia Limited, which develops, fixes, washes and dries either 35mm. film or 16mm. film at the rate of 40ft. per minute. There is a special 16mm. only model which does the job at double this speed. Called the "Lawley Junior," it is the 1958 model of a type of processing machine which has been used in cinema film laboratories for many years. Its automatic temperature control of developing solution and drying compartment, its continuous recirculation of the developing solution to provide agitation and a compressed air device to prevent carry-over of solutions from tank to tank, make this a simple device to operate. Making prints from the negative, if they are required, is a much more complicated operation, requiring additional equipment and a highly skilled technician. Printing is, therefore, usually handled by one or other of the established film laboratories.

### "Spectacular" Shows

THE word "spectacular," used as a noun, is a product of the American television world. It is the ambition of many artistes, male and female, to be engaged for one of the American networked "Spectaculars," particularly if it carries their own name in the title. A spectacular implies elaborate staging, precision dancing by a large troupe, top-class script writing, experienced stooges suitable for building up the star and—most important of all—a specially orchestrated musical background, with a fine orchestra and possibly a choir. How wonderful it is for a performer to "lean back" and wallow, completely relaxed, in the luxury of all this dressing.

**All the experts  
use—**



- ★ Reliable
- ★ Speedy
- ★ Long-lasting

**A model for every purpose**

65 watt round pencil fit

Leaflets on request from:

**W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.**  
Engineering Sales Department  
59-62 High Holborn, London, W.C.1.

Telephone: CHAncery 4361  
Telegrams: "Henlectel, Ho'b, London"

**FOR 25 YEARS THE BEST**



*A practical book on conversion—*

# T.V. CONVERSION FOR I.T.A. by C. E. Lotcho

**T**HIS book provides information on the conversion of those television sets which receive B.B.C. programmes only so that they will receive both B.B.C. and I.T.A. stations. Included in the Reference Data given in Section 3 are the sound and vision intermediate frequencies of many hundreds of television models. The book contains over 170 illustrations and circuit diagrams, and is fully indexed.

With 170 illustrations  
and circuit diagrams!


**CONTENTS** Section 1—General Principles:—Conversion Methods; Aerial Installations for Bands I and III; Interference Problems. Section 2—Conversion Data:—Aerialite; Aiba; Banner; Bush; Cossor; Ducca; Defiant; E.M.I.; Ekco; English Electric; Ferguson; Ferranti; G.E.C.; H.M.V.; Invicta; Kolster-Brandes; Marconiphone; Masteradio; Murphy; Peto Scott; Philips; Pilot; Pye; Rainbow; Sobell; Spencer West; Tele-mechanics; Teletron; Ultra; Valradio; Vidor. Section 3—Reference Data:—B.B.C. Television Transmitters; I.T.A. Television Transmitters; Frequencies of Television Transmitting Stations; Television Receiver Intermediate Frequencies; Models Aligned to the Upper Side Band; General Index; Index to Receiver Models; Index to Universal Converters.

**25s. FROM ALL BOOKSELLERS**

... or in case of difficulty 26s. 3d. by post from the publishers  
**GEORGE NEWNES LTD.,** Tower House, Southampton  
Street, London, W.C.2.

**NEWNES**


## SIGNAL GENERATORS

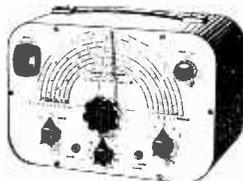

£1.19.6 or 25- deposit and 6 monthly payments of 21.6. P. & P. 5- extra. Coverage 100 Kcs-100 Mcs on fundamentals and 100 Mcs to 200 Mcs on harmonics. Metal case 12in. x 6 1/2in. x 5 1/2in., grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 220-250. Internal Modulation of 100 c.p.s. to a depth of 30%; modulated or unmodulated R.F. output continuously variable. 10 millivolts.


C.W. and mod. switch, variable A.F. output. Incorporating magic-eye as output indicator. Accuracy plus or minus 2%.

£4.19.6 or 25- deposit and 4 monthly payments of 21.6. P. & P. 5- extra. Coverage 120 Kcs-84 Mcs. Metal case 10in. x 6 1/2in. x 4 1/2in. Size of scale, 6 1/2in. x 3 1/2in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30%; modulated or unmodulated R.F. output continuously variable 10 millivolts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%.

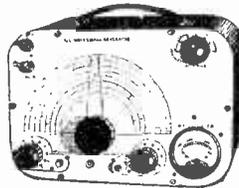
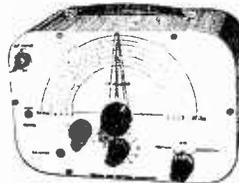
## SIGNAL & PATTERN GENERATOR

25- deposit plus P. & P. 5- and 6 monthly payments of 21.6. Cash £6.19.6 plus P. & P. 5-. Coverage 7.6 Mcs-210 Mcs in five bands, all on fundamentals, slow-motion tuning, audio output, 8 vertical and horizontal bars, logging scale. In grey hammer finished case with carrying handle. Accuracy ±1%. A.C. mains 200-250 v.




## COMMERCIAL TELEVISION CONVERTER SUITABLE ANY T.V. (Except Philips, Bristol area and Valley areas Wales) WITHIN 35 MILES OF I.T.A. TRANSMITTER, ALL CHANNELS TO SET.

Complete with built-in power supply, 200-250 v. A.C. mains. Crackle finish case 5 1/2in. long, 3 1/2in. wide, 4 1/2in. high. Incorporating gain control and band switch. Plus, with cover removed. Complete with Walsey 3 element I.T.A. outside or loft aerial, 36 ft. I.T.A. lead and 2 plugs. (Walsey 5 element 10/- extra.) 25- deposit plus P. & P. 5-, and 4 monthly payments of £1.5.6. Cash £5.17.0 plus P. & P. 5-, converter only £3.19.6 plus P. & P. 2.6.



## AC/DC POCKET MULTI-METER KIT

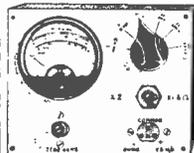

Comprising 2in. moving coil meter scale calibrated in AC DC volts, ohms and milli-amps. Voltage range AC DC 0-50, 0-100, 0-250, 0-500, milli-amps 0-10, 0-100. Ohms range 0-100Ω. Front panel range switch, wire-wound pot (for ohms zero setting) toggle switch, resistors and metal rectifier. Base movement 2 mA. In grey hammer finished case.

19/6 Plus Built and tested 7.6 P. & P. 1.6. extra.

Point to point wiring diagram 1-1/2 ft. with kit.

**PORTABLE AMPLIFIER.**—Size 6 1/2in. long, 5in. high, 2 1/2in. deep. Will suit any type of crystal pick-up. Output approx. 2 watts. Incorporating ECC83 double triode, Cossor 12zB1 output pentode and contact cooled rectifier. Fully isolated mains transformer for 230-250 v. A.C. mains. Bass, treble and volume controls. 49.6 plus P. & P. 3.4. 5in. speaker and 0.4 P. Transformer, if purchased with above, 19.6, plus P. & P. 1.6.

**COLLARO 4-SPEED AUTOMATIC CHANGER** Model 37 suitable for use with above amplifier. Type "O" pick up, size 12in. x 1 1/2in. Min. clearance above board 5in., below 2 in. 10 records. A.C. mains, 200-250 v., turnover crystal head. Brand new, fully guaranteed. £8.19.6, plus P. & P. 5-. Or 25- deposit plus P. & P. 5- and 7 monthly payments of £1.5.0.

**RADIO & T.V. COMPONENTS (Acton) LTD.**  
23, HIGH STREET, ACTON, LONDON, W.3  
All enquiries S.A.E. GOODS NOT DESPATCHED OUTSIDE U.K.

**FOR VALVES**  
**GUARANTEED ALL TESTED BEFORE DESPATCH**

AC6PEN 0/8	BCR21 24.4	EZ30 8.9	PCLE8 14.6	UABC80 10.6	Z750 9.8	6BER 8	6K7HT 7	6D20 12.8	6EK30T 13.6	6EFL 11.6
AC7H1 3/8	BCR45 10.6	EZ81 11.10	PL48 27.10	UAF42 10.6	1A5 3.8	6BG6G 24.4	6K7M 6.9	7B7 8.9	6E7M 13.6	6EFL 11.6
ATP4 34.9	BCR81 9	EZ90 8	PL82 8.6	UB41 9.6	1A7 12.8	6BG6 9	6K8G 8.6	7C5 8	6E7GT 8.6	6EFL 11.6
AZL1 12.6	BCR80 13.6	EZ44 2	PL88 11.8	UBC41 10	1C2 11.8	6BR7 11.6	6K25 20.11	7D6 13.6	6E7GT 8.6	6EFL 11.6
CBL21 24.4	BCR82 12.6	FW4 306	PL88 11.8	UCB80 9.6	1C5T 12.6	6BW6 8.6	6L6G 9	7H7 9	6E7GT 8.6	6EFL 11.6
CH35 24.4	EF26 8.6	H30 5	PL88 11.8	UC84 20.11	1D5 12.6	6B47 10	6L7 7.8	7A7 9	6E7GT 8.6	6EFL 11.6
CL28 20.2	EF27 8.6	GZ2 12	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
CY1 17.6	EF30 6.6	H30 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
DAF96 10.6	EF40 13.6	K40N 9	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
DF96 10.6	EF41 9.9	KK22 23	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
DH63 9	EF42 14	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
DK96 10.6	EF50 4	KT23 10	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
DL86 10.6	EF54 8.6	KT26 27.10	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
DM70 8.6	EF54 10	KT25 12.6	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
EA50 1.6	EF80 9	KT66 15	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
EABC80	EF85 9	KT66 15	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EF86 13.6	KT66 15	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EF89 10	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EA24 10.6	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB4 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB41 9.6	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB42 14	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB43 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB44 9.6	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB45 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB46 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB47 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB48 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB49 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB50 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB51 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB52 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB53 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB54 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB55 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB56 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB57 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB58 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB59 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB60 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB61 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB62 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB63 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB64 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB65 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB66 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB67 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB68 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB69 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB70 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB71 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB72 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB73 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB74 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB75 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB76 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB77 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB78 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB79 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB80 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB81 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB82 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB83 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB84 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB85 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB86 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB87 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB88 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB89 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB90 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB91 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB92 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB93 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB94 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB95 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB96 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB97 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB98 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB99 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6
	EB100 2	KT24 5	PL88 11.8	UCF80 23	1D6 12.6	6C4 7	6N7 7.6	7A7 9	6E7GT 8.6	6EFL 11.6


**PUBLICATIONS**  
**No. 138. HOW TO MAKE AERIALS** REPRINT No. 5. TV FAULT FOR TV. (Band 1 & 2) and V.H.F. (Band 2). Data for all Channels. Ten different designs for local and fringe areas, each 2/6.  
**No. 140. TELEVISION SERVICING FOR BEGINNERS.** \*40 pages of information, each 4/6.  
**No. 142. MODERN TV CIRCUITS AND FAULT FINDING GUIDE.** \* Many interesting Circuits included, each 4/6.

**REPRINT No. 11. QUALITY AMPLIFIERS FOR A.C. MAINS.** Articles describing a number of amplifiers selected for their quality of performance and ease of construction.  
*All publications plus 4d. each postage*

**ALPHA RADIO SUPPLY CO.**  
 103 LEEDS TERRACE WINTOUN STREET LEEDS 7

**TERMS:** Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 1/-; 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated. Minimum C.O.D. fee and postage 3/-. All single valves postage 6d. Personal shoppers Monday-Friday 9 a.m. to 5 p.m. Saturdays 10 a.m. to 1 p.m.

**REBUILT TUBES**  
**SEND YOUR DUD MULLARD AND MAZDA TUBES TO US FOR REBUILDING**  
 Via B.R.S. (Parcels) Ltd., or BRITISH RAILWAYS.  
 MULLARD - 12" £7.10 14" £8.10  
 EMITRON, COSSOR & CATHODEON 17" £10.10 21" £12.10  
 MAZDA - 14" £8.10 15" & 17" £10.10  
*Carriage and Insurance 15/- each tube. FULLY GUARANTEED SIX MONTHS*  
**Line Output Transformers and Deflector Coils**  
 Most types can be supplied. State set make, model number and part required. S.A.E. please.  
**BRAYHEAD TUNER CONVERTERS**  
 Foremost in performance, design and reliability. Instruction booklet supplied.  
**CONVERTERS £6.19.6.** Plug-in Adapter if needed 7/6. Postage and packing 2/6. State set make, model number and channels required.  
 Terms C.W.O. or pro forma  
**PRIME ELECTRICS (Dept W/2)**  
 36, QUEENSDALE ROAD, LONDON, W.11. (Near Shepher

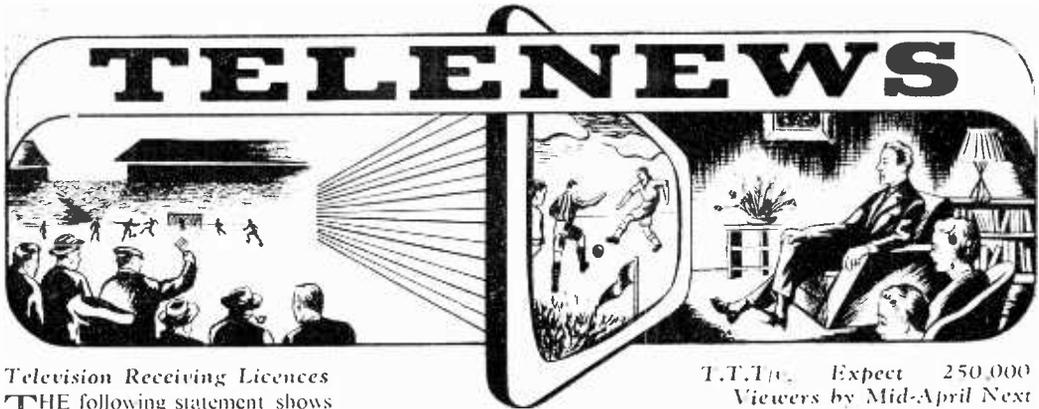

**Television Receiving Licences**

THE following statement shows the approximate number of Television Receiving Licences in force at the end of April, 1958, in respect of receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London Postal ... ..	1,589,544
Home Counties ... ..	1,002,897
Midland ... ..	1,308,321
North Eastern ... ..	1,312,820
North Western ... ..	1,140,843
South Western ... ..	632,285
Wales and Border Counties ... ..	469,814
Total England and Wales ... ..	7,456,524
Scotland ... ..	604,068
Northern Ireland ... ..	86,741
Grand Total ... ..	8,147,333

**Subliminal Messages**

PLANS to test subliminal perception have been announced by an independent television station in Los Angeles. During the next three months it will flash "public service" messages such as "Drive Safely" on screens at speeds impossible to see conscientiously.

If it is found that viewers absorb the messages similar experiments will be made with commercial advertisements. The three major television networks have said they will not allow this technique at least until the Federal Communications Commission has given its verdict.

**Television Relay for Hawick**

AT Hawick, in Scotland, a radio and television relay system has recently been completed by Relay Systems (Hawick) Ltd. This installation gives subscribers in Hawick, previously regarded as a poor area for television reception, a choice of BBC and Commercial television programmes and two alternative sound broadcast pro-

grammes. All the cables for the system were supplied by British Insulated Callender's Cables Limited and were manufactured in their plastic-cables factory at Helsby.

The first cable to be erected was the main feeder from the mast-mounted aerial array sited on a hill outside the town, where good signal strengths were available, to an amplifying and distribution station near the centre of the town.

**Pye Industrial TV Camera**


THE Pye industrial camera, which has a specially sealed housing, has been designed for outdoor observation at an explosives factory. The camera and its various attachments are remotely controlled.

Some of the facilities with which the camera is provided include a weather-proof housing that is also explosive dust-proof, a remotely controlled lens change unit, and a demisting device which blows warm air on to the polished plate-glass window.

T.T.T. Expect 250,000 Viewers by Mid-April Next Year

A POTENTIAL audience of 250,000 for Tyne Tees Television transmissions is expected by mid-April next year, states Mr. Peter Paine, sales controller, in a letter to leading advertising agents.

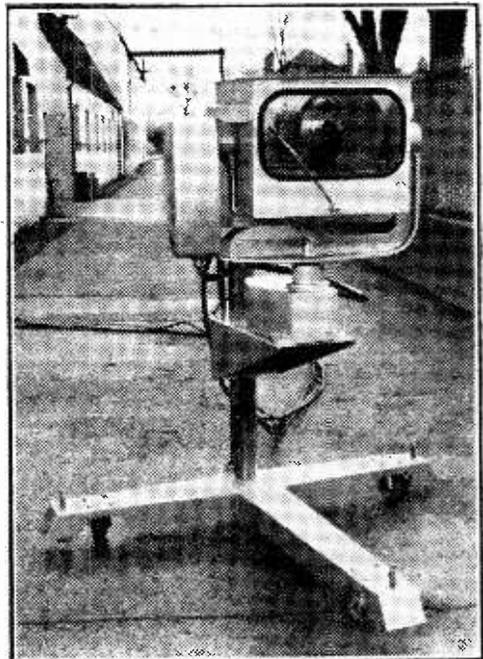It is estimated that the Tyne Tees transmission area contains 2.66 million people (approximately 880,000 homes), of whom 2.5 million live in the primary service area, and that 20 per cent. of all homes will be able to receive the transmission on opening night, January 15, 1959.



The special Pye industrial camera.

**Southern Television**

WHEN Southern Television, the new independent TV station for the south goes on the air from August 30, its transmissions will cover an area of more than 3,500 square miles and a population of between two-and-three-quarter and three million.

The expected area of coverage stretches from Weymouth in the west to Brighton in the east and northwards to Newbury in a rough D-shape.

Already television dealers are reporting good reception of test signals in towns throughout the region, from Brighton to Bournemouth, and Swanage to Southampton. This early test signal is at a very low power, of one kilowatt from a temporary mast only 75ft. high. Full power test signals of 100 kilowatts from the main 750ft. high mast are due to go out from August 1.

The signal now going out is designed to help dealers adjust sets and align aerials ready for Southern Television's opening night programme on August 30.

**First European Television Exhibition**


SEATED at his desk in Post Office Headquarters, Mr. Ernest Marples, the Postmaster General, opened the first European Television Exhibition, which was being held several

miles away, without even moving from his chair. He was using a system of closed circuit television.

At the exhibition which was

crossroads, and the control of unattended level crossings.

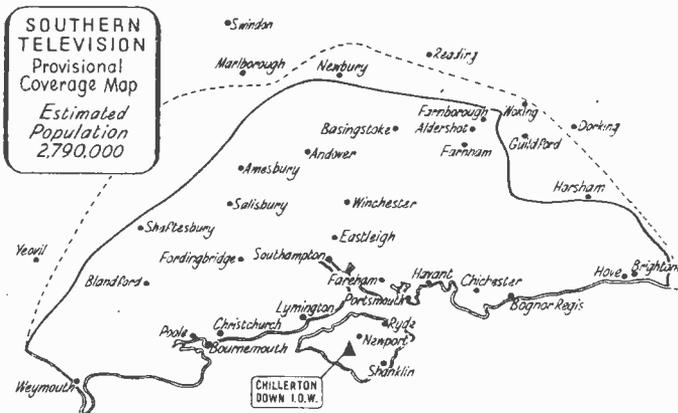Exhibitors from several European countries took part in the exhibition, including a Finnish



A map showing the coverage of Southern Television.

held at Park Lane House, the guests saw Mr. Marples on nine TV monitor sets placed in key positions in the various sectors of the exhibition.

The closed circuit equipment was installed by Pyc. In recent months there has been an increasing demand for closed circuit television from industry. It is already being used for observation of radioactive materials, guided missiles at the moment of launching, for traffic control at

company that makes TV films for Russia.

**19 Million Can Watch TV**

FOURTEEN MILLION more people can watch ITV programmes to-day than two years ago, reports Television Audience Measurement Limited. To-day's total is over 19 million, compared with 12 million this time last year and only five million in May, 1956.


**Extended Hours For Test Signals**

SOUTHERN TELEVISION arranged with the Independent Television Authority to increase the hours of transmission of the test signal from Chillerton Down, Isle of Wight.


It came into operation on May the 19th, and signals now go on the air for 12 hours daily from 10 a.m. to 10 p.m. from Monday to Saturday inclusive. (There will be no transmission on Sundays.)

This major extension from 37½ to 72 hours each week has been made to help retailers within the Southern Television region during what will be an extremely busy time, and it is hoped that they will be able to take full advantage of it.

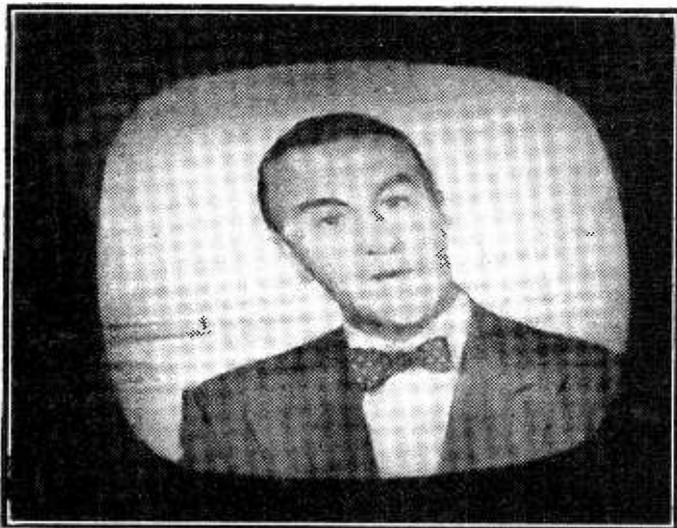These hours of transmission will continue during the broadcasting of the full-power signals of 100 kilowatts E.R.P. scheduled to begin in August.



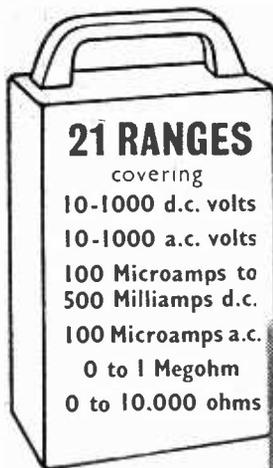Mr. Marples as seen on the monitor sets at the First European Television Exhibition.



*Yours the easiest way!*

How would you like to have one of the famous M.I.P. Series 100 Multi-Range Test Sets on your bench almost by return of post. It's easy, you just send 47/6 as deposit and pay the rest in six monthly instalments of £1.16.0. The cash price is £12.7.6. Post the coupon for full details.



**MULTI-RANGE TEST SET - SERIES 100**


To MEASURING INSTRUMENTS (PULLIN) LTD.  
 Electrin Works, Winchester Street, Accon, London, W 3.  
 Please send illustrated leaflet of the series 100 Test Set with details of new easy payment scheme   
 Ditto, Series 90   
 \* Please indicate instrument required.  
 NAME .....  
 ADDRESS .....  
 D758

★ *There is also the SERIES 90*

Terms for the Series 90 Test Set (19 self-contained ranges ac/dc 200 micro-amps 5,000 ohms per volt)

Deposit 35/- and six monthly payments of 28/10. (Cash price £9.15.0.)

GD14

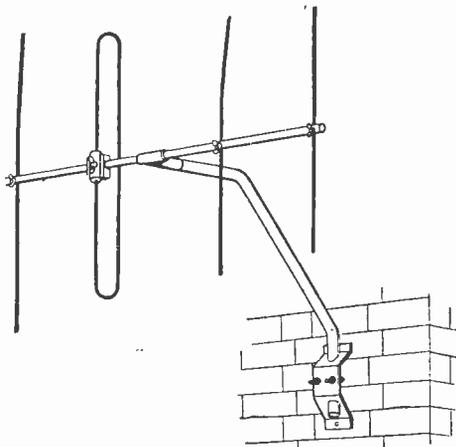


**SPECIAL OFFER THIS MONTH LIMITED QUANTITY**

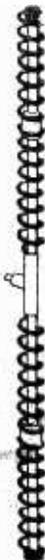**SPIRAL**

The easiest possible dual-band aerial to fit. Just plug it into the set. Ideal for ranges up to 10/15 miles, depending upon locality. Bargain offer 19/11 post free.

Double 4-element Aerials, array only, complete with Cross-over unit. Matching Stubs wired to folded dipoles. Few only, 79/6.



This powerful 4-element, pre-assembled, wide spaced Band III beam Aerial by a leading manufacturer. Supplied complete with cranked pole and wall fixing brackets, can also be loft mounted. Listed at 55/6.

Our price, Brand New, in maker's sealed carton, 39/6.


4-element Aerials, array only, for mounting to 1 1/2 in. diameter mast, 25/-.

Cellular polythene Co-axial Cable at 8d. per yard supplied if required.

Terms: Cash with order or C.O.D.  
 Carriage on aerials 2/6 extra.  
**MAIL ORDER ONLY.**

**G. C. EQUIPMENT CO. LIMITED**  
 2, Park Row, Leeds, 1
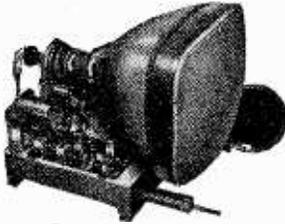
### 17in. T.V. CHASSIS, TUBE & SPEAKER, £19.19.6



Latest improved circuits. Higher E.H.T. (brilliant picture). Improved sensitivity (for greater range). Chassis is easily fitted into any cabinet. 17" rectangular tube on adapted chassis. Less valves. 12 months' guarantee on tube. 3 months' guarantee on valves and chassis. With Valves. £25 19/6. Valve line-up 6SN7G, 6V6, EY51, 2-3D2s, EL33, EL14 and 7-6F1s. Turret tuner. 50" extra. Spare B.C.C. channel supplied at 7/6

and L.T.A. channel required. Extra each. Ins. Carr. (incl. tube) 2/-.

### 14in. T.V. CHASSIS, TUBE & SPEAKER, £13.19.6

As above with 14" round tube. Less Valves. 3 months' guarantee. With Valves. £19 19/6. Turret Tuner. 50" extra. Ins. Carr. 25/-.

### POPULAR RADIO OR RADIOGRAM CHASSIS, 39/9

A.C. or A.C./D.C. 3 waveband and gram. 5 valve superhet. International octal. Ideal cabinet gram, but still giving high quality output. 4 knob control. 8 p.m. speaker. 7.9 extra. Set of knobs 2" extra. Chassis size: 15 1/2" x 7 1/2" x 3 1/2". Less Valves. Ins. Carr. 4/6.



### INSULATING TAPE, 1/8. Finest quality. 75" x 1" wide. Post Pd.

**SOLO SOLDERING TOOL, 19/6**  
110 V. or 6 V. (Special adaptor for 200 240 V.). 10" extra Automatic solder feed. Includes a 20 ft. reel of ERSIN 60/40. Solder and spate parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Instantly ready for use and cannot burn. In light metal case with full instructions for use. Post 2/6.

Open SATURDAY—ALL DAY.  
Liverpool Street Station—Main  
Park Station—10 minutes.  
FREE CATALOGUE.

### T.V. RECTANGULAR TUBES 12 MONTHS' GUARANTEE

17in. £7.10.0      14in. £5.10.0

6 months' full replacement, 6 months' progressive. Made possible by the high quality of our tubes. Ins. Carr. 15/6. Convert your 9", 10", 12" tube to 14", 15", 16" (round tubes). Our special offer for these sizes, £5. Details on how to "Do-it-Yourself" in our free catalogue. 12 T.V. Tubes. £6. 3 months' guarantee on all round tubes. 15/6 Ins. Carr. on all tubes.

### EXTENSION SPEAKERS, 2/9


Extensions in Cabinets. Complete. Fitted with 8" P.M. Speaker "W.B." or "GOOD-MANS" of the highest quality. Standard matching to any receiver. (2-5 ohms.) Flex and switch included. Money refunded if not completely satisfied. Ins. Carr. 3/6.



**8" P.M. SPEAKER, 8/9.** Ideal for kitchen and bedroom extension. Let the lady of the house enjoy that Radio or T.V. programme. Complete with O.P. trans. 10" - P. & P. 2/9.
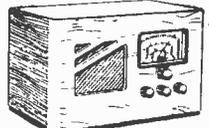
### HOME RADIO, 79/6

A.C. D.C. Universal mains 5 valve octal s/het. 3 waveband receiver can be adapted to gram. P.U. In an attractive wooden cabinet. 9 1/2" x 18 1/2" x 11 1/2". Ins. Carr. 7/6.



**GANG CONDENSERS, 1/9.** 2 and 3 gang 500 pF Standard Salvaged. Tested. P. & P. 1/3.

**SOUND & VISION STRIP 25/6**  
Sound I.F. 10.5 Mc/s Vision I.F. 11 to 14 Mc/s Less valves. Valve line up 6-8F1s, 2-6D2s. Any single channel 1-5 supplied. a turret tuner is easily fitted. Power Pack Supply 200 V. H.T. 6.3 V. heaters. P. & P. 2/5.

## DUKE & CO.

(Dept. 2) 621, ROMFORD ROAD,  
MANOR PARK, E.12.  
Tel.: ILF 6001-3

**H.S.R.A.-speed Type AC8 Record Changer** £3.12.6. 3/6 carriage.

**Ion-trap Magnets, 5/-.** 7in. x 4in. P.M. Speakers. 16/-.

**Air-spaced Coaxial Cable, 9d. per yd.** 70/- per 100 yds.

**Sapphire Stylus Replacement Needles.** Standard or L.P. All types at 6/-, including T.C.4, H.G.P. 37, H.G.P. 54, Scudio "O", G.C.2, T.C.8. Please state cartridge number when ordering or enquiring. Postage 3d.

**Television Aerials.** Band III 3 element. 29/6; 5 element. 39/6; 8 element. 59/6; B.C.C. Single Dipole. 32/6. We carry large stocks of all types of aerials. Send S.A.E. with your enquiry and we will reply by return.

**Television Tables.** Walnut finish 20in. x 20in. x 21in. high. Packed flat in carton, only 4 wing nuts to assemble. 72/6.

**Electrolytic Condensers, 8 8 mfd. 350 v., 2/6; 10 mfd. 450 v., 3/6; 16 mfd. 450 v., 4/6; 32 mfd. 450 v. 3/6. Polished Aluminium Kettles.** Fully guaranteed, 59/6.

**Crossover Boxes for T.V. 12/-; Conax Plugs, 1/-; Fuses 1/10in., 500 mA. 1 amp. 1.5 amp., 2 amp., 3 amp., 5 amp. 4/- per doz.**

Valves		
OZ4	5/-	6SN7 6/-
1A5	3/-	6B3G 3/6
1LN5	2/6	1025 5/6
2N2	2/6	807 5/6
3D8	2/6	6H6 1/6
6J5	4/-	EB91 6/-
12J5	4/-	EL38 21/6
EL33	15/-	6CD6G 12AT7 10/-
6SL7	6/-	248 CL33 17/6
		126

**MAIL ORDER ONLY—NO CALLERS**

Terms: C.W.O. or C.O.D. Minimum C.O.D. charge 3/6. Postage and Packing per valve, 6d.; other items, under £2, 19/-; £5, 2/-; Aerials 3/- carriage.

**ELECTRO-SERVICES & Co.**  
221 BATTERSEA PARK ROAD,  
LONDON, S.W.11.      MAC 8155

### ● 1958 EDITION

## RADIO AMATEUR'S HANDBOOK

32/6 by The A.R.R.L. Post 1/9

**TELEVISION RECEIVER SERVICING, Vol. 2.** Receiver and Power Supply Circuits. By E. A. W. Spreadbury. 21/-, Postage 1/-.

**TV AND RADIO TUBE TROUBLES.** By S. Heller. 23/-, Postage 1/-.

**THE OSCILLOSCOPE AT WORK.** By A. Haas and R. W. Hallows. 15/-, Postage 9d.

**TELEVISION PRINCIPLES AND PRACTICE.** By F. J. Camm. 25/-, Postage 1/3.

**PRACTICAL TV AERIAL MANUAL FOR BANDS I AND 3.** By R. Laidlaw. 5/-, Postage 6d.

**HIGH FIDELITY SOUND REPRODUCTION.** By E. Molloy. 20/-, Postage 1/-.

**TV FAULT FINDING.** A Data Publication. 5/-, Postage 6d.

## THE MODERN BOOK CO

BRITAIN'S LARGEST STOCKISTS  
of British and American Technical Books

19-23 PRAED STREET,  
LONDON, W.2

Complete catalogue 6d.  
Phone: PADDINGTON 4185.  
Open 6 days 9-6 p.m.

## FIRST-CLASS TELEVISION and RADIO COURSES . . .

### GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how!

### FREE GUIDE

- The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams, Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc., together with particulars of our remarkable Guarantee of SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

### FOUNDED 1885—OVER

.....150,000 SUCCESSES.....

**NATIONAL INSTITUTE OF  
ENGINEERING**  
(Dept. 462), 148, HOLBORN,  
LONDON, E.C.1.

# CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

## PROJECTION TV

**SIR.**—You have rightly said on a number of occasions that the TV tube looks wrong, and that a thing which looks wrong is wrong. Yet many of the firms who market projection television receivers have discontinued them. From this, I must conclude that it is a failure, and I am wondering whether you have had second thoughts on the matter. The disadvantage that the picture becomes blurred when side viewing and is only clearly visible to those who are looking square on to the picture is, I know, one of the greatest disadvantages, but I should have thought that it would not be beyond the ability of our designers to overcome this. I am also aware that, as you increase picture size, brilliance is diminished because it has not yet been found possible to amplify light as we can amplify sound. The greater cost of projection TV receivers is a further disadvantage but I cannot believe that this is the main reason for its decline since hire purchase terms would make its purchase fairly easy. Friends of mine who have owned such receivers have told me that they were frequently in trouble with them and that maintenance and replacement cost were frequent and high.—E. N. (Enfield).

*[We have not changed our views on this matter and we think that when it is possible to produce a projection TV set at a price comparable with that of, say, a 21in. direct vision receiver, it will regain its popularity. The recent announcement that a method of amplifying light has been discovered may eliminate the criticism that the pictures are less brilliant and improvements in the optical system may eliminate the side viewing dimness. The optical system in its present form is the main drawback. A more compact design of receiver is possible by means of projection TV than with direct vision TV, and although many receivers have been withdrawn from the market, experiments continue.—ED.]*

## BEGINNER'S GUIDE TO TELEVISION

**SIR.**—I became a reader of PRACTICAL TELEVISION after reading an announcement of your new series, now completed, entitled "A Beginner's Guide to Television." I was fascinated by the simplicity of that series because I had previously read a series for beginners in your companion journal *Practical Wireless*. That series was later reprinted in book form and I treasure my copy of it. Is there a possibility of the TV series being produced in similar form?—A. S. T. (Ipswich).

*[As announced last month, "A Beginner's Guide to Television" will be published on July 17th at 7s. 6d., by post 8s. 3d.—ED.]*

## COLOUR TV

**SIR.**—Having recently visited America and watched some of the colour TV programmes, I can only say that, unless we can do something better, colour TV receivers in this country would be a flop, especially in view of the expense involved. It seems to me as crude as the Baird 30-line system of TV, and I certainly would not pay the very high price asked for one. The colour was crude and rather resembled some of the coloured horror comics published in America. I was told by dealers that the demand for them was practically non-existent, and those they had sold had been a continuous source of trouble.

One dealer said that it had been marketed too soon. I know that experiments are continuing in this country, but the BBC is not yet ready for it, and I do not think the public is either. Most people seem satisfied with a monochrome picture. Personally, I should like

to see the BBC spend its money on improving the programmes, and some of them are in need of it, rather than waste thousands of pounds on colour TV. It is my view also that colour TV will not depend upon a mechanical system as at present.  
A. H. (Rotherham).

### SPECIAL NOTE

Will readers please note that we are unable to supply Service Sheets or Circuits of ex-government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

## HOME-BUILT TV RECEIVERS

**SIR.**—I recently looked in on a home-constructed receiver installed in a friend's house and I was so astonished at the perfect results that I enquired the source of his design. My friend informed me that he had built it from the pages of your journal, and that it was called the "Supervisor." I was filled with a desire to build one myself and as a result I have become a regular reader of your paper and intend to build one of your receivers myself this autumn. I have been a reader of your companion journal *Practical Wireless* from its first issue, when it was a weekly, and I have every volume bound. I often browse through them with great interest. I also took your pre-war monthly publication, PRACTICAL TELEVISION, until it ceased publication owing to the war. I also have several of Mr. Camm's books on radio and television, and one which intrigues me at present is his "Television Principles and Practice" from which I learned all I know about television. His output seems so tremendous that at one time I thought he was a mythical character, until I met him at the Caxton Hall last year at the showing of the Mullard films. More power to you.—A. J. B. (Harrow).

### WIRE AND WIRE GAUGES


3/6, or 3/9 by post  
From George Newnes Ltd., Tower House,  
Southampton Street, Strand, London, W.C.1

# News From the Trade
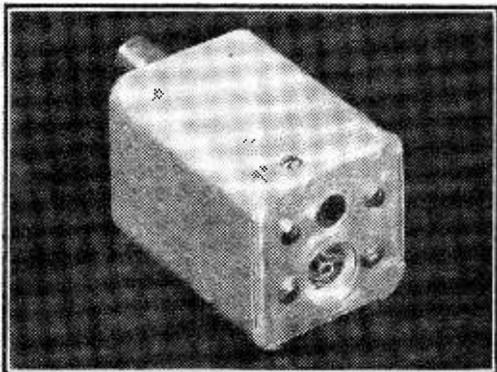
## Picture Equaliser Unit

THIS is a small tunable filter unit which provides adjustable attenuation to Band I signals with only a very small loss on Band III. The unit plugs directly into the coaxial aerial socket on the receiver, the aerial feeder lead then being plugged into the socket provided on the equaliser.

When setting up the procedure is to insert the unit and then adjust the controls on the receiver for normal Band III reception. The receiver is then switched to Band I and the screw core on the



The Labgear picture equaliser unit.

equaliser adjusted until Band I reception is similar to that obtained on Band III. No further adjustment is required and the set can be switched from BBC to I.T.A. without needing any readjustment of the sensitivity or contrast controls.

In many areas the Band I signal is so strong that patterning interference results and, in addition to its normal function, the Labgear PE13 frequently removes this form of trouble.

The retail price of the unit is 10s. 6d. and initial supplies should be available this month.

## 13-Channel Turret Tuner

TWO Bakelite resins have played an important part in the development of the Fireball 13-channel turret tuner being used in many of the new television sets. The tuner is made by A. B. Metal Products Ltd., Abercynon, Glamorgan.

Based on an American patent the circuits, selectors and other components were specially designed and chosen for British television by Mr. J. K. Brown, the company's Chief Product Engineer, to make the Fireball, the first British tuner with 13 channels—the maximum number so far announced; nine being in daily use. It is less than a third of the size of earlier turret tuners developed to meet the rapid expansion of BBC and ITV services.

The tuner assembly is only 2in. deep and a fraction over 3in. in diameter; the control spindle projecting a further 2in. to the front and the valve


shields and terminal lugs another 3in. to the top. The terms "top" and "front" are relative as the tuner may be installed in any position.

The heart of the tuner is a circular, white plate moulded from Bakelite alkyd DX18926 through which are mounted 104 metal pins. Between these lie the selector coils. On the reverse side the pin heads are arranged radially in sixes and pairs to mate with the selector arm, also moulded from Bakelite alkyd DX18926 which carries the corresponding eight metal contacts.

A feature of the manufacture of the plastic disc, apart from its high electrical stability and resistance to heat, frequency loss and tracking, is its intrinsic strength and lack of brittleness necessary for the insertion of the 104 pins. Raised identifying channel numbers 1-13 are part of the moulding.

Two further components made of Bakelite material, Phenolic Black X17165 form the fine adjustment mechanism of the tuner. The first moulding is a collar bearing a cam-shaped rear face, rigidly fixed to the outer "fine tuning spindle." The second is a spring-loaded ferrule carrying two teeth, one of which bears on the cam surface of the first moulding causing it to move in and out of the tuner by the rotation of the spindle, while the second tooth engages with the moving plate of a book condenser to give the fine tuning adjustment.

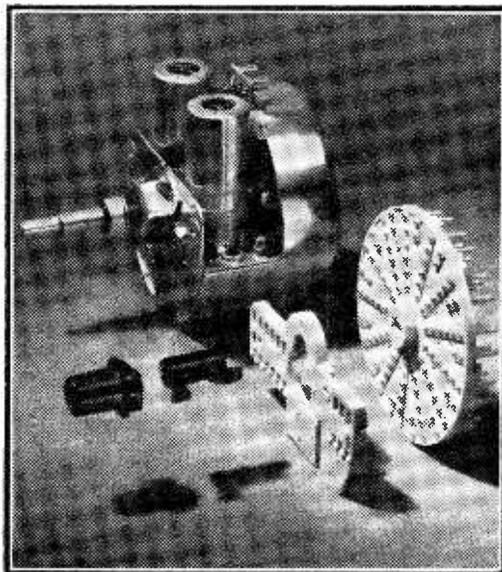Three firms are manufacturing the mouldings. Kent Mouldings, of Footscray, Sidcup, Kent, and Cosmocord Ltd., Waltham Cross, Herts, making the Bakelite alkyd DX18926 parts, and Prestmare Ltd., of Raynes Park, London, making the X17165 Phenolic parts.



An exploded view showing the positions in the Fireball tuner occupied by the mouldings.

## BAR-VACS

(Tel. RIP 1591)

**8 WILMINGTON GARDENS,  
BARKING, ESSEX**

### REBUILT TUBES

	12 in.	14 in.	17 in.	21 in.
MAZDA	£8	£10	£12	£14
MULLARD	£8	£10	£12	£14

**GUARANTEED SIX MONTHS**  
P.P. & INS. 12/6. TERMS C.W.O.  
PLEASE SEND S.A.E. FOR ANY ENQUIRIES

# EDDY'S (Nottm.) LTD.

(DEPT. P.T.)

**172, ALFRETON ROAD, NOTTINGHAM**

**MIDGET BATTERY ELIMINATORS.** To convert all types battery portable to mains operation. 57/6 each, plus Post and Packing, etc., 2/6. Smaller than H.T. battery alone. Please state make and model No.

**SINGLE PIECE THROAT MIKES,** 1/- each. Post, etc., 6d. each. Could be used for electrifying musical instruments.

**B.S.R. 4 SPEED AUTO-CHANGE UNITS.** Turnover crystal cartridges 200-250 volts A.C. Special Price, £7.19.6. Postage and Packing, 5/- extra.

**ALL ABOVE ARE NEW AND GUARANTEED.**

AZ1	12/11	ECC84	8/11	MU14	8/6	ID5	10/6	6J5G	2/11
AZ31	12/11	ECC85	8/11	PCF80	12/6	1R5	7/11	6K7G	2/11
CY31	12/11	EB91	5/11	PCC84	9/-	1S5	7/3	6K8G	7/11
DAF96	9/6	ECH35	10/11	PEN36C	17/6	1T4	7/3	6L6G	5/11
DF96	9/6	ECH42	9/11	PL81	16/6	3Q5GT	9/6	6Q7G	8/11
DK96	9/6	ECH81	8/11	PL82	9/6	3V4	8/6	6SN7GT	
DL96	9/6	EF80	8/6	PY80	9/11	5U4G	6/6		5/11
EABC80	8/6	EF86	12/6	PY81	8/3	5Z4G	9/11	6V6G	5/11
EBC41	9/6	EF91	6/11	PY82	8/6	6AT6	7/6	25A-6G	
EBF80	9/6	EL84	9/-	TDD4	12/6	6B8G	2/11		12/11
ECC81	8/11	EV86	15/-	UCH42	8/11	6F1	13/11	35W4	7/6
ECC82	8/11	EZ80	8/3	UF41	8/-	6F13	13/11	954	1/6
ECC83	8/11	HY90	7/6	UY41	7/6	6F15	13/11	955	3/11

Any Parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers' risk.

**SURPLUS, NEW AND GUARANTEED VALVES.**  
All tested before despatch.  
Cash with order or C.O.D. only.

Postage and Packing 6d. per valve extra. Over £3 Free.  
S.A.E. with enquiries.

## St. Mary's Electronics

(Tel. AMBassador 9795)

**18, PRAED STREET, LONDON, W.2.**

### REBUILT TUBES

	12 in.	14 in.	17 in.	21 in.
MAZDA	£8	£10	£12	£14
MULLARD	£8	£10	£12	£14

P.P. & INS. 12/6.

**GUARANTEED SIX MONTHS**  
TERMS : C.W.O.

PLEASE SEND S.A.E. FOR ANY ENQUIRIES

## SHORT-WAVE RECEIVER

10-60 Mc/s (5-30 Metres)

RECEPTION SET TYPE 203



Complete with 6 valves, 2-6K8C, 2-EF39, 6Q7G and 6V6G. Internal mains power pack and 6 v. vibrator pack. Built-in 6" speaker. Muirhead slow-motion drive. B.P.O. and R.F. stage. Provision for Phones and Muting and 600 ohms. Combined Input 100/250 v. A.C. or 6 v. D.C. All sets in new condition and air tested. I.F. Frequency 2 Mc/s.

**£6/19/6** Carr. 15 6.

BE PREPARED TO LISTEN TO THE SATELLITES

## TRANSISTORS (PNP)

**RED-SPOT** 800 Kc/s Audio Frequency, 7/6.  
**WHITE-SPOT** 2.5 Mc s R.F. and I.F. Amp., 15/-.  
**NR102** Audio Amplifier 21/-.

## "TRANSISTOR-8"

COMBINED CAR-RADIO & PORTABLE PUSH-PULL SUPERIET  
Can be built for **£11/10/-**

Send for Free Booklet and Price List. Car Radio Conversion Components, 8/- extra.

We can supply all these items including Cabinet for **£11/10/-**. All parts sold separately.

## "EAVESDROPPER"

**THREE TRANSISTOR POCKET RADIO**

(No Aerial or Earth required)  
Variable Tuning. Total cost, as specified including Transistors, Transformers, Coils, Condensers and Battery, etc., with circuit and plastic case. **70/-** POST FREE.  
All items sold separately.  
With Balanced Armature, 73 6. With Acos Mike, 82/6. With 10oh Impedance Hearing Aid, 86/-.

## PYE 45 Mc/s STRIP TYPE 3583

Complete with 10-EF30's, EB91 and EA50 valves. Unit is in new condition.

**ABSOLUTE BARGAIN! 39/6**  
Including modification data.

## R.F. UNITS

Type 25 Switched Tuning 20 to 30 Mc s. Unit includes 33P41, 10 -, carriage 2 6.  
Type 25. Variable Tuning from 50 to 65 Mc/s. Including 2-EF34's and EC32. 25 -, carriage 2 6.

## JUST ARRIVED!

**MIXER UNIT TYPE 79**  
Frequency range 172 to 190 Mc s.

This unit comprises VCR139A tube : 5U4 : 2-EB91 : VU120 : EF55 : 7-EF50/s : and 4-EA50 Valves.  
Standard 200-250 50 c/s mains input.  
Complete at the bargain price of **£5/10/-** Carriage 5/-.

## QUARTZ CRYSTAL UNITS IN STOCK

Frequency ranges from 100 kc s to 36.7 Mc/s. SEND FOR FREE LIST

LOOKING FOR GOOD VALVES AT CHEAP PRICES ? SEND FOR OUR VALVE LIST.

SEND STAMPS FOR NEW 1958 28-PAGE CATALOGUE  
OPEN MONDAY to SAT. 9-6. THURS. 1 o'clock.

## HENRY'S RADIO LTD.

5 HARROW ROAD, EDGWARE ROAD, LONDON, W.2  
TEL. : PADDINGTON 1008-9

# PREMIER RADIO CO.

(Regd.) B. H. MORRIS & CO. (RADIO) LTD.  
 207, EDGWARE ROAD, LONDON, W.2.  
 Telephone: AMBassador 4033. PADddington 3271/2.

23, TOTTENHAM COURT ROAD, LONDON, W.1.  
 Telephone: MUSeum 3451.

## The "Petite" PORTABLE



May Be Built For  
**£7.7.0**  
 plus 3 - p. & p.  
 ★ Size only 8in. x 8in. x 4½in.  
 Batteries Extra.  
 HT 10/- (Type B126)  
 or equivalent.  
 LT 1/6 (Type AD 3 S)  
 or equivalent.  
**Battery Eliminator**  
 now available for 37/6.


## Read what a customer says about the MAYFAIR Televisor

"I am writing to tell you that this set is a complete success, it is all you claim for it—Plus.

"Some 40 miles from the station a picture was obtained with a short length of flex, while a somewhat crude loft aerial produces results which astound my neighbours with their expensive factory-made sets.

"Construction was begun in some trepidation, the groans implying that this was a somewhat risky operation to undertake, that the picture received would be an inch wide stripe on the screen, that the coils would be out of line, etc. You can imagine my delight when I switched on for the first time to find all the controls performed their various functions exactly—on sound and vision.

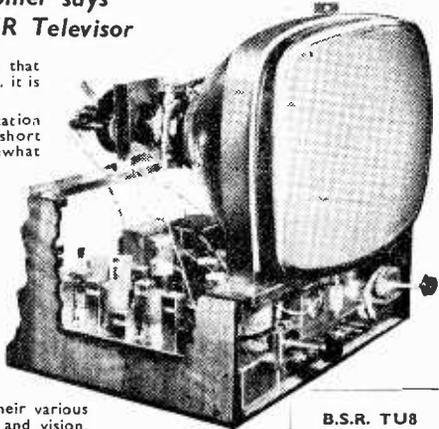This achievement on your part and mine gives added pleasure to viewing. Congratulations on an excellent circuit and kit."



B.S.R. TU8

3-speed record player £3.19.6, plus 2/6 postage and packing.

### 8-WATT AMPLIFIER

This design includes 5 miniature Valves of the latest types, an Ultralinear Output Transformer suitable for Speakers of 3 and 15 ohms and a very attractive Perspex front panel with gold lettering, complete set of parts, £8.8.0.

Built and Tested £10.19.6. Postage & Packing 5/- extra.

MAY BE BUILT FOR

**£33.7.11**

Plus cost of C.R.T. Send for Inst. Book 3/6.

**PLEASE ADDRESS ALL MAIL ORDER ENQUIRIES TO Dept. (PT3), 207 EDGWARE RD., LONDON, W.2**

This book gives you photographs, wiring diagrams and constructional details for cheap and efficient home-built T.V. receivers, with additional chapters on pre-amplifiers, E.H.T. generators, pattern generators, test gear, etc.

F. J. Camm's

# PRACTICAL TELEVISION CIRCUITS

288 pages of valuable T.V. data for only 15s. net.

With 156 illustrations

**CONTENTS** The "Argus": A £9 Television Receiver; A 3-inch Midget Televisor; A Compact Televisor; An A.C.-D.C. Television Receiver; A Combined Television and Broadcast Receiver; The "Argus" Pre-Amplifier; Low Noise Factor Pre-Amplifier; Two-Valve Pre-Amplifier; A "Spot-Wobbler"; A Black Spotter; A Variable E.H.T. Generator; A Portable E.H.T. Generator; An Alignment Aid; The Grid-Dip Meter and Bar Generator; A Pattern Generator; The Telesquare; The Practical Television "Lynx"; The Practical Television "Supervisor"; Aerial Data.

MR. CAMM states in his Preface, "This book gives constructional details of a number of the most successful television receivers which have been described in "Practical Television," the monthly journal of which I am the Editor. Every one of them has been thoroughly tested and they may be built with confidence. The circuits extend from a cheap receiver designed round the well-known VCR97 and which may be built for about £20, to more elaborate receivers designed for quality rather than for low price. In addition, the construction of test apparatus and auxiliary equipment, such as a spot-wobbler and a telesquare, and aerial design and erection have been included." Purchasers encountering difficulty in construction or adjustment of any of the receivers described may have their queries answered through the Free Advice Bureau of "Practical Television."

**15s. FROM ALL BOOKSELLERS**

... or in case of difficulty use the C.O.D. order form on the right.

**An essentially practical book by F. J. Camm**


### ORDER HERE

Please send me Cash on Delivery one copy of F. J. Camm's PRACTICAL TELEVISION CIRCUITS (15s. net).

Name .....

Address .....

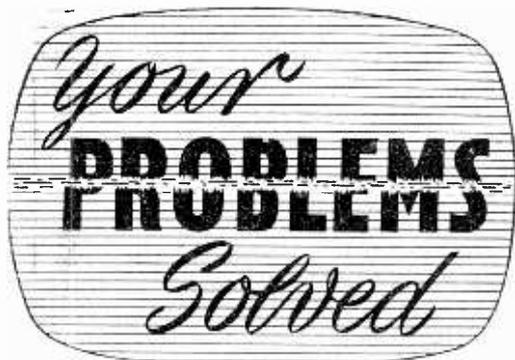Simply post this order to GEORGE NEWNES, LTD., Tower House, Southampton Street, London, W.C.2. If you prefer not to pay C.O.D. charges send a remittance for 16s. 3d.



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** The coupon from p. 605 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

H.M.V. 1804

My main fault is line tearing. Instead of a perfect outline of an object I simply get a zig-zag, also my frame begins to close up from the bottom leaving approximately three-quarters of a full screen.—H. Smith (Salford).

On the front end of the chassis are situated the valves associated with the timebases. The KT61 at one end should be replaced. If this does not cure the bottom cramping check the associated  $.1 \mu\text{F}$  linearity capacitor for leakage. The line tear is usually caused by leakage through the  $.047 \mu\text{F}$  (replace with  $.05 \mu\text{F}$ ) capacitor feeding the top cap of the centre Z63 (or KTZ63) sync separator.

EKCO T141B

These last five years when anything has gone wrong with the set I have taken all the valves out to be tested and had replacements needed, but it has now given trouble beyond me which I feel is concerning the contrast. When the set is first switched on it has an unusual "sizzling" noise. When the brightness control is turned up the screen becomes blank and bright with lines moving across it diagonally and it has no picture. If the contrast knob is turned up completely and then back again to normal the picture will right itself, but will repeat its blank and bright appearance for ten to fifteen minutes until the set is warmed up. After a short time the picture will go completely out of focus and will close in slightly about an inch from the right-hand side of the screen. Throughout a programme I have to continually refocus the set and adjust the brightness and contrast controls. After about two hours the picture seems to fade in quality and to lack contrast. Finally, twice recently the picture has closed completely, leaving a thin white line horizontally across the screen.—J. Underhill (Meir).

We cannot imagine one single fault which would give rise to all your symptoms at once,

so we expect that it is a general ageing of components. Since your sound is not affected we suggest you look for your contrast fault in the vision I.F. stage, where it may be due to a faulty .001 ceramic decoupler (check by bridging with a known good one). Another possible symptom is grid cathode leakage on the tube, but the brightness will not be controllable if this is so. We suspect your 6P28 for lack of width and focus, and the 6K25 and SP61/41 next to it for intermittent frame collapse.

MURPHY V200—1952

When I switch on, "wicker-work" forms with gradual picture formation after approximately 20 to 30 minutes. Frequent adjustment is required to line hold due to (a) herring-bone effect across screen; (b) pulling to right at top of picture; (c) picture moves to left and right with eventual break-up; (d) picture will remain clear and steady for frequent intervals. I have changed pot 20 K $\Omega$  res. 39 K $\Omega$ , 47 pF capacitor. Had PL38 tested, found O.K. Would possible coil adjustments have any effect as above on picture?—M. E. Rooney (Liverpool).

You have described the common symptom of a faulty video amplifier anode load. This is a 10 K ohm 1 watt resistor and is underneath the I.F. chassis between the double diode and a coil. This normally overheats and goes low. Other possible causes of your trouble are overloading of the R.F. stages and a low H.T. rectifier.

BUSH TV22

I wish to add a turret tuner to the above set covering channels 3 and 11. Being within eight miles of both transmitters there is no need for any increase in gain. So could you please advise whether there is a type of tuner available with leads to tuner terminated with plugs, to plug straight into R.F. stage with no modifications to set.

Also, for future reference, is there available at present a replacement for the tube MW22/16?—R. Beale (Gosport).

Suitable plug-in tuners are available in the Cyldon and Brayhead range. As an example we would quote the Brayhead 16s with B7G R.F. plug and 16BA6 I.F. adaptor. Full fitting instructions are provided. When ordering quote channels required. The MW22-16 CR1 is still available.

PHILIPS 1236-U-15

My ability in radio engineering is limited to replacement of faulty valves, C.R.T., mechanical parts and, if clearly indicated, replacement and fixing of other electrical parts. Sound is good; height and vertical hold controls at mid-position giving correct performance; interference limiter at "minimum effect" position; sensitivity at maximum; mains voltage 230v. but carousel on receiver set at 220v.; contrast control about one-third on; brightness about two-thirds on; width control extended only 20 per cent.; horizontal hold about 50 per cent.; loft aerial properly directed for maximum reception; ion trap magnet set correctly for maximum brightness. On switching on: after one minute the sound comes on; after one and a

quarter minutes a very faint picture consisting of broken or torn patterns on an almost circular raster; a few seconds later a complete picture offset 2in. to the right, still faint and raster gradually extending towards oblongity and with slightly folded edges at left; after two minutes picture jerks to correct position but only slightly brighter and still not oblong picture. After five minutes or more picture has filled screen with only a fairly acceptable picture which perhaps brightens a little more after an hour or two. Any adjustment of contrast or brightness controls progressively blots out picture and eventually turns it negative. In a darkened room the picture detail is quite good, perhaps a little fuzzy, with reasonable vertical and horizontal linearity and interlace. All above effects worsened by setting voltage carousel at the 245v. setting. After an hour or two viewing picture tends to "twitch" at the top, necessitating a small outward extension of the horizontal hold control.—W. Forrest (Romford).

We would advise you to replace the PL81 line oscillator-output valve situated in the perforated screening box on the left side chassis as viewed from the rear. We would also suggest that the cathode ray tube be replaced as the emission of the existing tube is apparently very low. Before carrying out any of the above, however, check glow of valve and tube heaters, if very low in comparison to what could normally be expected, check heater circuit thermistor associated with upstanding left side mains dropper.

#### SOBEL T121

The line output transformer has been rewound owing to no EHT at top cap on tube or cathode of EY51 except when condenser C42 is removed from H.T. line connection. A faint picture was seen at a critical setting of either brightness or contrast. PL81, EY51 and PY80 have been replaced. Sound is O.K. Oscillations on line and frame seem O.K. with your advice concerning headphones in Practical Television. ECL80 have been switched around. The line whistle is also audible when C42 is removed from H.T. line. This condenser has also been replaced. EY51 filament shows part current, but not with C42 connected. The line O.P. transformer was rewound by "Forrest" transformer of Solihull. Is it possible that this is still faulty?—F. White (Great Barr).

We doubt whether the fault is due to the line output transformer, this having been rewound by a reputable company. It could be wrongly connected, but you have no doubt checked this. We would suggest you disconnect R25 as the tube may be at fault with an internal short which only shows up when the boosted H.T. line is raised by the connection of C42. Also check R53 (7.5 K $\Omega$ ) which may have risen in value.

#### DECCA DM17

In the last three months the EY51 valve has been replaced four times. The last replacement lasted only three weeks and when an attempt to remove it was made it was found too firmly fixed to the plastic cup in which it rests.

It had obviously overheated as it had turned

the anode brown, and the heaters were found to be open-circuit on all the faulty ones. It has also burnt (melted) a hole through the bottom of the plastic cup. Could you please advise me what tests I could make to find just what is causing this?—M. O'Connell (Watford).

The fault is probably due to an intermittent short in the tube. Sometimes this can be overcome by reducing the A.1 voltage to that of the normal H.T. line, in others by rewiring the C.R.T. base as follows: Remove connection to pin 7. Remove lead to pin 10, solder to pin 7. Remove lead to pin 2, solder to pin 10. Strap pin 2 over to pin 11. Readjust ion trap magnet—maximum brilliance.

#### H.M.V. 2815

Originally picture closed down to bright horizontal line. KT33C and B36 were tested and found O.K. These were replaced and it was found that resistor from cathode of KT33C to chassis was getting very hot, colour coding burned off. The reason for this appeared to be a U.S. condenser on strip just by holder of KT33C, value uncertain, could be 8,200, 3,200 or 5,200 pF  $\pm$  1 per cent.

Local dealers suggested value of resistance 210 ohm and condenser 8,200 pF. I replaced both these and now have a picture considerably elongated and folded over at bottom. No amount of adjustment will correct this.

Could you, therefore, please advise the correct values of components and offer any suggestions re other possible causes of faults described? I have no service sheet to hand.—G. Small (Wolverley).

The capacitor referred to is, as stated, 8,200 pF. The resistor from pin 8 of the KT33C to chassis should be 2.2 k $\Omega$ . With the correct value installed, normal working should be regained. If the resistor again overheats and the KT33C is in order, check .1 mfd connected to 8,200 pF capacitor and 1 K $\Omega$  resistor.

#### EKCO T161

I get a perfect picture and intermittently it seems to jump to the left about 1/16in. and becomes all smeared, i.e., in a change from dark to light, instead of being a definite line or change the dark spreads into the light, and vice versa the light spreads into the dark. Sometimes I get a broad band of interference about 1 $\frac{1}{2}$ in. wide which clears the picture on that 1 $\frac{1}{2}$ in.—J. Nelson (Eastbourne).

You have a heater-cathode leakage on your C.R.T. This can be overcome by fitting a 2 volt low capacity isolating transformer and the easiest one is the plug-in "Nuray" which also has optional boost tappings.

#### MURPHY V240

I have a cross aerial which has given good reception of BBC and I.T.A. for the past two years. Now I find that I.T.A. has a broken picture on certain days but BBC stays perfect. The sound is good on both stations. I find that if I turn down the contrast the picture steadies

(Continued on page 605)

**EDUCATIONAL**

**FREE!** Brochure giving details of Home Study Training in Radio, Television and all branches of Electronics. Courses for the Hobby Enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds, R.T.E.B. and other Professional examinations. Train with college operated by Britain's largest Electronics organisation. Moderate fees. Write to E.M.I. INSTITUTES, Dept. PT28, London, W.4.

**A.M.I.P.R.E.**—For details of suitable study courses (only a limited number of students accepted) send for free Syllabus of Instructional Text, I.P.R.E. Conditions of membership booklet 1/-. "The Practical Radio Engineer" Journal, sample copy, 2/3; 6,000 alignment peaks for Superhets 6/-. All post free from SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.

**BUILD YOUR OWN T.V.** and learn about its operation, maintenance and servicing. Qualified engineer-tutor available while you are learning and building. Free Brochure from E.M.I. INSTITUTES, Dept. PT58, London, W.4. (Associated with H.M.V.)

**LEARN IT** as you do it—we provide practical equipment combined with instruction in Radio, Television, Electricity, Mechanics, Chemistry, Photography, etc. Write for full details to E.M.I. INSTITUTES, Dept. PT47, London, W.4.

**MATHEMATICS** for T.V. Course, 21/-; TUTORIAL MATHEMATICS, 30/-. Buchanan St., Glasgow.

**SERVICE SHEETS**

**SERVICE SHEETS** for sale and hire. Radio T.V.; s.a.c. enquiries, J. PALMER, 32, Neasden Lane, N.W.10.

**SERVICE MANUALS/SHEETS** for Radio for hire. Sale and wanted. Mixed Manuals and Sheets, 12 for 10/-; s.a.c. enquiries, W. J. GILBERT (P.T.), 24, Frithville Gdns., London, W.12.

**ENGINEER** has complete range new Radio/T.V. Service Sheets, 3/- each. State Model No. required; c.w.o., L. BRENNER, 23, Midway Close, Barnet, Herts.

**SERVICE SHEETS, Radio, T.V.,** 5,000 models Lists 1/-. S.A.E. enquiries, TELRAY, 11, Maudland Bk., Preston.

**SERVICE SHEETS, Rad. T.V., sale,** hire; s.a.c. enquiries, "RADAT," 241, Park Rd., Barnsley, Yorks.

**SETS & COMPONENTS**

**TELEVISIONS,** some faulty or needing tubes, all cheap. WILKINSON'S, 446, Goldhawk Rd., W.12. (SHE 4379.) Callers only.

**5-CHANNEL TELEVISIONS:** 12in. screen Ferguson 988, Ekco 161, etc., £22 each. A good selection of 12in. T.V.s (London) 100% condition, from £12; 9in. from £7, also 12in. T.V.s, slight faults, from £5; 9in. from £3. TYLER TELEVISION, £3. Lee High Rd., Lewisham, S.E.13. (LEE 5979.)

**UNREPEATABLE OFFER.** 12in., 5-channel T.V., £15; 14in., £22; good working order. C. EDWARDS, 1070, Harrow Rd., London, N.W.10. (Phone: LADbroke 1734.)

**RATES:** 4- per line or part thereof, average five words to line, minimum 2 lines, Box No. 1 extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

**CALLING CENTRAL SOUTHERN REGION:** Convert NOW. It's simple with the BRAYBARD TURRET TUNER. In stock for ANY AREA. State Channels, set make and model No., £6.19.6, post. ins., 2.6.

The **RADAR KILOVOLTER** measures E.H.T. 3-50 kV., £8.17.6, post. ins., 2/6. Line and Frame ass. and O.P. transformers for 500 sets. EXACT REPLACEMENTS. State make and number with enquiry (3d. stamp).

**WESTWAY RADIO**

5, Westway Way, Harrow, Middx.

**ELECTRADIO,** Co-ax, low loss, 9d. yd.; Plugs, Sockets, 1/- each. Multi-core Solder, 2/6 per packet. Stirling Band III Converter, all channels, 6 gns., post free. 18, Broadlands, Av., Keynsham, Som.

**TELEVISIONS,** 9in. models, £7/10/-; 12in. models, £13/10/-; 12in. 5-Channel models, £19/10/- each; all working; carriage paid. Send for list. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23. (FOR 5497.)

**GUARANTEED TELEVISION,** 12in., 5-Channel model's; first-class picture, £26 each, carriage paid. THE GRAMOPHONE SHOP, 19-21, Brockley Rise, London, S.E.23.

**SOUND & VISION STRIP, 25/6**

Sound I.P. 10.5 Mc. Vision I.P. 11 to 14 Mc. Less Valves. Valve Unit up, 6 6F7s, 2 6D2s. Any single channel 1-5 supplied, a turret tuner is easily fitted. Power Pack Supply 200 v. H.T. 6.3 v. heaters. P. & P. 2/6.

**12 CHANNEL TURRET TUNER £6.17.6.** Supplied with any two channels, extra channels, 7/6 each. Parrell Heaters, I.P. output 10.5-14.0 Mc. s. Post Free.

**DRK & CO., 621-3, Romford Road, Manor Park, E.12. ILE 6001.3.**

**RF27 or 26, 18/-; 25 or 24, 11/-,** brand new, post 3/6. E.W.S. CO., 69, Church Rd., Moseley, Birmingham.

**ASSIST-U-AERIAL KITS,** containing insulator and cap for 1in. boom (in. elements, 20 in. plugs, 2 in. end plugs, 2 in. grommets, suitable for construction of Band II or Band III Aerials, 6/6 complete. Send P.O. with order. ROBERT MOSS, LTD., 35, Banbury Rd., Kidlington, Oxford. Trade inquiries invited.

**RECLAIMED TUBES,** 12in., 14in., 17in., all at £5 each, guaranteed; 100 (5 channel) T.V. Ekco 161, Ferguson 988, £15 each. C. EDWARDS, 1070, Harrow Rd. (Phone: LADbroke 1734.)

**LOUDSPEAKERS** repaired promptly. MODEL LOUDSPEAKER SERVICE, Bullington Rd., Oxford.

**METERS (NEW, BOND M.O.S.)**

**Ammeters,** 6in. round, switchboard mounting, moving iron, 50 cycles A.C., scaled 0-50. Price £4, postage 3/6.  
**Ammeters,** 2in. round, moving coil, complete with shunt for basic movement, scaled 0-20. Price 10/6, postage 1/6.  
**Voltmeter,** Moving coil, 2in. round, 10,000 ohms resistance, scaled 0-50. Price 10/6, postage 1/6.  
**Voltmeters,** 2 1/2in. round, moving iron, 50 cycles, scaled 0-999. Price 15/-, postage 1/6.  
**Voltmeters,** 2 1/2in. round, moving iron, scaled 0-500. Price 17/6, postage 1/6.  
**Voltmeters,** 6in. round, moving iron, scaled 0-500. Price £5, postage 3/6.  
**Wireless Components,** Amazingly low price. Send for free list.

**SPEED ELECTRICS**

EASTWOOD NOTTS

**VALVES** from 1/6. Radio, I.V. Components, low prices. Lists 3d., J. PALMER, 32, Neasden Lane, N.W.10

**MAKE YOUR AERIALS** with our fully machined parts. Examples: Band 1, "H," complete with lashings, for £3 10/-; 5 Element, Band 3, with folded dipole, mast and clamp for 45/-. (Get further details from our illustrated lists and data on all aerials, sent for 1/- P.O. (Trade supplied). SKYLINE WORKS, Burn-sell Rd., Coventry. (Tel: 69418.)

**COMPONENTS,** Valves, Tubes, etc. Write or phone for free list. ARION TELEVISION, 4, Maxted Rd., Peckham, S.E.15 (New Cross 7152.)

**AMAZING OFFER.**—Originally £40 £200 each. Ekco, Eyc, H.M.V., Marconi, Philips, Mullard, etc., 9/10in. Televisions, complete, new working, 50/- each; carriage paid; immediate dispatch, 12in., £5 5/-; 15in., £9; Philips 17in. Projection Televisions, £3/15/-. TOMLINS, 127, Brockley Rise, London, S.E.23.

**CRM-151,** 15in. Mazda Tube, new, un-used, £24 list, £12, 47, Allport Lane, Bromborough, Wirral.

**INDICATORS,** Type 196, with one each 6in. and 3in. C.R.T.s, etc. 50/- (rail 10/-). Speakers: 5in. in case, 22/6, uncased 18/6 (p.p. 2/6). Drives: slow-motion, Admiralty, 200:1 ratio, 1 scaled 0-100, 5/6, Muirhead, 4in. dial brass, 7/3. Command Receivers: brand new, 6 valves, med. wave 10.52-13mc s., 97/6; used 82/6 (post 3/6). Conversion data and circ., to Car Radio, 1/6. I.P. Strip 373, new, with valves, 37/6. Vibrapaks, 6v. D.C. to 250v. 80mA, smoothed, cased, 22/6 (post 3/6). Vibrators, Mallory G629C 12v. 4-pin 7/6. Brand new R.F.26, 20/- (post 3/6). RF27, good cond., 18/-. Dynamos, 12v. to 250v. 60 mA, 11/6; 6v. to 250v. 80 mA, 12/6; "Command" Type 28v. to 250v. 60 mA. (sale). 7/6. Test Meters, new, 4 x 4 x 2 1/2in. read 1.5 and 3v., 60 mA, and 5k ohms, 12/6. Meters, contain 2 separate micro-amp. movements and 2 recons, new, 8/6. Cross-over needle (L/R), 100% each section, good condition, 8/6. R.F. Unit with 2 EF91, 1 EF93, motor tuned (20-35 mc s.) I.P. 15 mc s., new, 30/- (p.p. 3/6). Sets DLRs, pair, 7/6; DLR5 with thral mic., 10/6. Converters (rotary), 110v. D.C. to 50v. A.C., £3 (rail 7/6). Mic. Inserts, G.P.O. carbon, 2/6. Earpieces, inserts, 10x-amp. type, 2/6. Blocks, Greico, 10x-amp, 2/-, C.R.T.s, 6 1/2in., magnetic, El. focus, octal 4v., blue trace, 30/-. List and enquiries; s.a.c. please! Terms: c.w.o.; postage extra; immediate despatch. W. A. BENSON, 136, Ruthbone Rd., Liverpool, 15.

**CATHODE RAY TUBES** used but in good working order, with three months' written guarantee, 12in. to 17in. Mazda, Mullard and Equivalent types only, at £4/10/-, plus 12/6 for carriage and insurance. Enquiries and orders to BHP DISTRIBUTORS (LONDON) LTD., 39, Staines Rd., Hounslow, Middlesex. (Tel: HOU 5144.) Our terms are c.w.o. or c.o.d.

**TELEVISION TUBES.** Only the very best reconditioned Tubes supplied; 6-month unconditional guarantee; 12in. and 14in., all makes, £5 10/-; 15in., £6/10/-; 17in., £7/10/-. Carriage and insurance 10/- extra. C.W.O. MIDLAND TUBES LTD., 37, George St., Manchester, 1. (Continued overleaf)

**SETS & COMPONENTS**

(Continued from previous page)

**T.V. TUBES.** 14in., £3/10/-; 15in., £4; 17in., £5, all picture-tested and guaranteed 3 months. A few 12in. and 14in., suitable for testing or boosting. 25/- each; all carriage paid. **BRADLEY**, 6, Beadon Ave., Waterloo, Huddersfield.

**TELEVISION TUBES**, genuine rebuilt, new manufacturers' process, individually picture tested. 12in., £3/8/10/-; 14in., £4; 17in., £4.12; 21in., £14/10/-; 6 mths. guarantee, plus 15/- ins. P. and p. Terms: c.w.o. or c.o.d. **G. HOULT**, 25, Bond Gardens, Wallington, Surrey. (Phone: Wallington 8334.)

**CATHODE RAY TUBES**, ex-chassis, picture-tested, 3 months' guarantee. Mullard, Mazda, Brimar, etc. 9in., 12in., 14in., 15in., £3/10/-; 17in., £4; carriage and insurance, 15/-. Miniature Valves, 10/- dozen. **S.C.L.**, 77, Cranleigh Rd., Bournemouth.

**TELEVISIONS.** London only. 12in., £10; 5-channel, 12in., £14; 14in., £18; 17in., £27; 13-channel, 12in., £20; 14in., £25; 17in., £35. (Callers only.) **JOHN GILBERT TELEVISION**, 1B, Shepherds Bush Rd., London, W.6. (SHE 8441.)

**T.V. TUBES** as new, revacuumed; all makes; 6 months' straight guarantee; 14in., £5/10/-, 17in., £7/10/-; carriage and insurance 12/6 U.K. Free delivery Greater London. **VIDEO REPLACEMENT CO.**, Hales St., Deodar High St., London, S.E.8. (Tideway 4506.)

Save 30% on all outdoor aerials and fittings. Example: Double Five Array costs only 70/-. Self-contained Band III Pre-amplifiers only 60/-. Convertors 80/- complete. Fringe Area Super Low-Loss Co-axial, 14 yard. S.A.E. FOR FULL LISTS.

**G. A. STRANGE**

North Wrexall, Nr. Chippingham, Wilt. Tel.: Marshfield 235.

**WANTED**

**ALL TYPES OF VALVES REQUIRED** for cash. State quantity and condition. **RADIO FACILITIES LTD.**, 33, Chalcot Road, N.W.1. (PRImrose 9532.)

**VALVES WANTED, ECL80, EY51, EY36, PL31, PCF80, and all Miniature Types.** U25, 10C1, 10C2, 10F1, etc. 52G, 6K8G, 6V6G, brand new only; prompt cash by return. **R.H.S.**, 155, Swan Arcade, Bradford, 1.

**IMPORTANT.**—Valves wanted, new, loose or boxed; same day payment. **ROBERT**, 414, Whitefoot Lane, Bromley, Kent.

**ALL TYPES OF VALVES WANTED.** FL91, ECL80, EY51, U25, PCF80, P239, U801, etc. etc. Best cash price by return. **STAN WILLETTS**, 43, Spon Lane, West Bromwich, Staffs. (Tel.: WES 2392.)

**FOR SALE**

**TELEVISION BARGAINS:** 9in., seen working, £7/10/-; 17in., £37/10/-; new 17in. Sets, 59 gns. Aerials and Co-ax cheap. **CLAYTON'S**, of Church St., Chalvey, Slough.

**SUPERTONIC SUNLAMPS**, listed £7/10/-, 80/-. S.A.E. **SCIENTIFIC PRODUCTS CO.**, Cleveleys, Lancs.

**TELEVISIONS.** Clearance of 12in. B.E.C. sets all in good order, £12 each; carriage extra. Callers preferred. Many others. **C.C.W.**, 12, Dockhead, S.E.1. (BER 3756.)

**VALVE CARTONS.**—We can supply from 12 to 100,000 of the shelf. Plain white or printed. Miniatures, 10/-. "C.T.S." 12/-. "Gs." 14/- per 100, plus 2/- postage. Also printing done to your special requirements; quotations gladly given. **J. & A. BOXMAKERS**, 75a, Goodwin St., Bradford, 1.

**EVERYTHING FOR THE AMATEUR.**—Write for our new List catering for Home Engineers, Hi-Fi Fans, Tape Recording Fans, etc. Probably the most comprehensive in the trade. Price 1/-. **R.H.S.**, 155, Swan Arcade, Bradford, 1.

**"MAINS" FROM 12v. BATTERY.**—Brand new American Dynamotor Unit in beautiful black crackle case. Weighs about 38lb., but neat and compact. Thousands of uses, no conversion required. In seconds makes marvellous, powerful 200 250 A.C./D.C. electric motor, electric fan, dynamotor gives 250 volts at about 100 watts from 12-volt car battery, runs mains radio, bulbs, etc. Makes ideal rotary transformer, battery charger, etc. Continuous duty, quiet running, doesn't overheat; worth £25—our price 80/-, with instructions; carriage paid. Satisfaction guaranteed. Send remittance with order. Dept. 8. **SCIENTIFIC PRODUCTS**, Manor Works, Cleveleys, Blackpool.

**SCOUT MK.II EX-W.D. TELESCOPES.** 25 x 50, practically new, with case and sling, £7/15/- ea.; ditto, second-hand condition, £6/10/-. High-power Eyepieces to fit above scopes, 50x or 75x, state which, 50/- ea. Triple Power Conversion Kits for the above scopes, giving 25x and 40x terrestrial and 60 astro, 50/- extra. 6 Power Kits, giving 25, 40, 50 and 80x terr. and 60 and 120x astro, at £5 extra. If scope already purchased elsewhere send us the erector (centre lens system) from your scope when ordering triple or 6 power kits. Returned intact. **EX-Gov.** Telescopes terrestrial, all brass, in case, 30x, 24in. x 2in., weight 7lbs., near new, £4/5/- ea. Telescopic Sights, 13in. long, weight 20oz., 17/6. No. 42 Rifle Sight, 3x, 50/-, near new. Tank Periscopes, boxed, unused, 7/6, post. 2/-. Directors, with 4x optical sight, ideal for builders, etc., will lay out any angle with precision, of theodolite; sound condition, 45/- ea., cost over £80; ditto, in near new condition in leather case, £3/10/- ea.; ditto, minus case, £3/15/-. **H. W. ENGLISH**, Rayleigh Rd., Hutton, Brentwood, Essex.

**CO-AXIAL CABLE**, unbeatable offer. 8d. a yard air spaced.

**TELEVISION TABLES** cancelled order. 20" x 20", 18" legs. 4-quartered veneering, veneered both sides, in medium oak, walnut and sapele. Unrepeatable offer while stocks last. 39/-, carriage 3/6.

**MARSHALLS FOR TELEVISION**

131, ST. ANN'S ROAD, TOTTENHAM, N.15  
Phone: STAmford Hill 3267.

**SALE**

Satisfaction or Money Back Guarantee  
If returned unused within 7 days

**13 CHANNEL CONVERTERS**

For T.R.F. or Superhets. Famous make, fine tuner, 9 quick-set trimmers giving any 3 channels, output to aerial socket. Beautiful case, with PC80, PCF80, Full Instructions, £3.15.0 (Post 3/-).  
**Focus Magnets** w.a. centring, mounted, 9/6; ditto, double magnet, 12/6. **10N TRAPS**, 4/-, 15/-, 100-200 Mc/d., 25/- v.w. Super 38 mm., 15/-, 100-200 Mc/d., 25/- v.w. Conds., 5/6. **T.V. CABINETS**, 14 inch, attractive, mask, glass, front spkr., 25/-

**GUARANTEED T.V. TUBES!**

(EX EQUIPMENT)  
12in (MW31-74, 321, etc.) ..... £5.5.0  
14in. (MW36-24, CRM141, etc.) ..... £4.10.0  
17in. (MW48-64, 415, etc.) ..... £6.10.0  
17in. (CRM17 only) ..... £8.0.0  
(All guaranteed 6 months.) (Carr. & Ins. 12/6)  
Also available limited number of T.V. Tubes giving very good picture when filament volts boosted. All types 50/- each. (Carr. & ins. 12/6.)

**4 SPEED AUTO STAR GALAXY**

Modernise your radiogram or build a super record player. Famous Ultra-Modern Autochangers (as shown but less base) with Lightweight turnover Sapphire Pickups. Beautiful Cream and Chrome finish. 10 Records taken of any size or speed. For all mains voltages. Spares Available (post 4/-).

**£3-19-6!** (listed approx. £13)



Above Autochanger mounted on streamlined high-finish case, as shown, to make complete add-on Player, which will play any 10 Records through your Radio or Amplifier for all mains voltages. (Post 4/-)

**COMPLETE PLAYER in covered two-tone quality £13 Gns.**

Autochanger, excellent 3-valve Amplifier, 7-inch Speaker, beautiful reproduction (worth over £20). (Post 5/-)

**STAR GALAXY SPARES.** 10s available, low prices, including rubber idler pulleys, tone-arms, p.u. cartridges (Acos, Power Point, S-motone), etc.

**GUARANTEED RADIO VALVES.**

**BOXED, SAME DAY SERVICE.**

5U4G	6B6GU6T	12B6CC81	8	PC80	9/-
5Z4G	9-8V6G	6-EC82	6	PC80G	11/6
6AU7	5-6V6CM	6-8C82	8	PCF80	12/-
6AL5	5-6X31	6-8C84	10	PCF80E	11/6
6AM6	7-6X5GT	6-EC85	9	PC81	12/6
6BA6	6-610C1	12B6CF80	12	PL3	9/-
6BD5	6-610P9	10-8F82	12	PL3C	11/6
6C4	4-910L11	12B6E842	9	PT300	8/6
6E6	11-10P13	15-8E889	13	PT81	8/6
6F1	14-12A7T	8-8P75	4	PT82	9/6
6FL5	13-12A7T	6-8E82	8	PT83	9/6
6J5G	3-12AX7	8-6E95(A)	3	SP41	2/-
6K7G	4-812K7G	6-8E95(B)	4	SP61	2/6
6K9G	7-812Q7T	7-8E95	8	U16	9/6
6L6	15-25L6GT	8-8E95	7	U22	7/6
6L9	13-25Z6T	7-8E95	6	U24	12/6
6Q7G	9-807(BR)	3-8E91	7	U24	12/6
6S47M	7-807(A3)	5-8E93	8	U25	12/6
6S67M	5-8E91	5-8E240	8	U25	6/6
6S7M	7-8E82	7-8E260	7	U26	9/6
6SK7GT	6-8C81	9-8E26A	5	U41	8/-
6SN7GT	5-8E82	9-MU14	9	Z86	12/6

**S.A.E. FOR FREE LIST OF 500 SUPER SNIPS**

All items less 5%, and post free for a dozen. Postage 13 in £1. Min. 6d. No C.O.D.

**TECHNICAL TRADING CO.**  
350/352 Fratton Rd., Portsmouth

itself up to normal but is too faint to view in comfort. I have checked and re-tuned I.T.A. coils in drum switch but to no betterment. Also there is sound on vision (on I.T.A. only) when the contrast is turned up. I suspect a 10F1 or the 20L1 (frame oscillator). Can you help to diagnose the fault as my children prefer I.T.A. The set is nearly four years old. The signal strength is good on BBC and I.T.A.—J. Thackeray (York).

We would suspect the 20L1 turret valve or a low emission tube, the latter needing so much drive as to overload the previous stages. We suggest that before you buy any new components, however, you balance up the two sensitivity controls at the back by the aerial panel and check the setting of the ion trap under the focus dome. The rejectors are the upper cores in the two coils at the back of the row nearest the scancoils.

#### EKCO TC138

My set has failed to give either picture or sound. The raster and line whistle are both evident. All valves have been checked and are O.K., although three of the SP61s are weak. Valves are set firmly and there are no obvious loose connections, also I have tried a separate aerial rig-up, still without any signal.—F. Finbow (Sutton).

We suggest you check the local oscillator and R.F. stages. These are the 6C9 (or 6F1) and 6F1 in the front of the R.F.-I.F. strip. The local oscillator trimmer is the airspaced condenser in the largest can in that section and is best tuned with a 4BA plastic tool. Check also that you have no break in the "contrast" wiring as this feeds the R.F. valve.

#### EKCOVISION T164

I can obtain no picture unless the permanent magnet on the C.R.T. is brought further back on the neck than the makers allow for. Upon switching off the beam assumes a hazy circular form instead of a clearly defined spot before disappearing. There has recently been a breakdown of insulation on the line transformer. Is this the origin of the trouble? The sound is perfect.—C. Bentley (Derbyshire).

If your picture is the right size you have a low emission C.R.T. If it swells up with increase of brightness or contrast we suggest you change the U25 EHT rectifier. Your tube may take a boost transformer if it has not already got one.

#### PYE LV30C

An intermittent reverberant roar has appeared on sound. It is unaffected by volume control changes and either completely drowns sound or else replaces it. Sometimes the fault is present when set is first switched on but on other occasions sound is quite normal when first switched on and may continue so for an hour or more when suddenly without warning the roar

appears. Picture is normal all the time but vertical hold control has to be kept fully anti-clockwise (viewed from the rear) in order to lock picture, but for the first five minutes or so it cannot do so even in that position. Can you help, please?—R. C. Mou'd (Whetstone).

Your sound trouble is either a faulty ECL80 sound output valve or 12 mfd condenser on the H.T. side of the output transformer. Your frame trouble could be either a faulty ECL80 or the frame blocking oscillator transformer. The former valve is second from the back on the row alongside the R.F. strip, the latter valve is down near the volume control. Mullards are having trouble with this type of valve, which accounts for their early failure and scarcity.

#### FERGUSON 306T

The other day the picture of my set died away in two or three seconds until the screen was blank. I advanced the brilliance and the tube lit up with a dark and hazy picture. The sound was normal. I would like to mention one point which may have some bearing on the cause. During the time I have had the set I occasionally hear a sharp crack as though arcing was taking place (this may happen twice in a night or once in a week or so). It has been suggested to me that it was probably an ill-fitting aerial socket, or, on too low a mains tapping (it is on 240/250 volt). This cracking noise occurred, incidentally about 20 seconds before the picture faded. For some months past a  $\frac{1}{2}$  in. black band has been at the bottom of the picture when warmed up.—J. Tee (Peterborough).

We suggest you check the EY86 EHT rectifier. This is probably not connected with your gap at the bottom, which is undoubtedly due to a faulty PCL83 frame output valve. This latter is the one over the top of the C.R.T. neck and can be changed with the sound output valve on its left.

#### PYE LV20

My set is eight years old and it has given excellent service until recently. Now I get a black band at the bottom of the picture. I would be very grateful if you could advise me what is wrong.—C. J. Watts (Hornchurch).

We suggest you change the EF50 frame output valve, which is the one nearest the volume control (with the little diode in between). The EF50 which is between the volume control and the PZ30 is the frame oscillator and this can sometimes cause the same trouble. Check also the 25 mfd from the cathode of the frame output valve to chassis.

### QUERIES COUPON

This coupon is available until JULY 21st, 1958, and must accompany all Queries sent in accord with the notice on page 601.

PRACTICAL TELEVISION, JULY, 1958

P. P. COMPONENTS LTD.

219, ILFORD LANE, ILFORD, ESSEX.

Phone: ILF 0295

Table of electronic components with columns for part numbers (e.g., 1T4, 4D1, 6Y3) and prices.

FOCUS MAGNETS, 12.9. Elec. Brand new, 35 mm. P. & P. 2.3.

FOCUS MAGNET, 3.9. Ex-Plassey chassis, 35 mm. for Triode tubes. P. & P. 2.5.

T.V. MASKS 14.9. For 17in. Brand new. P. & P. 2.5.

ALLEN SCANNING COILS, 7.8. Low impedance. For 14in. or 12in. wide-angle tubes. P. & P. 1.

MAINS POWER TRANSFORMER, 9.9. 250-250 v. 250 m.a. 4 ch. heaters or 3 amp. 4 v. or 3 amp. 4 v. or 5 amp. isolated. Extra isolated winding for 2 or 4 v. Drop through type. Prim. 200-250 v. Size 4 1/2 in. x 5 in. Post 2.5.

O.P. TRANSFORMERS, 1.6. Standard size 2.5 ohms. salvage, guaranteed. Post 1.5. 20 for £1. post 5.6.

INSULATING TAPE, 1.6. 7/8 in. x 1/4 in. wide in sealed tin. Post on 1.9d.; post on 6.2.

SOLDER REELS, 1.6. 60-40. 5-core Ersin. 20ft. on plastic spool. Post 8d.

CO-AXIAL CABLE, 6d. yard. Good quality. Cut to any length. Post on 20 yds., 1.4. 65.- per 100 yds. Post 2.6.

A.M. F.M. TUNER UNIT, 7.9. Incl. 2-gang. New ex-manufacturers. Not tested. Takes ECC85 valve (not incl.). Post 1.5.

VOLUME-CONTROLS, 1.9. 1/2 neg. ohm. Long spindle. New, boxed. Post 6d.

VOLUME-CONTROLS, 12.8 doz. Assorted volume and tone controls. Stripped from working radio and T.V. chassis. Post 2.2.

T.V. SLIDER CONTROLS, 9d. 10K and 2K only. Wirewound. 4 for 2.6. Post 6d.

HEADPHONES, 1.9. Single earphone and hand C.R.R. Ideal for crystal sets, extension on T.V. or radio. Post 6d.

I.F. TRANSFORMERS, 1 - pair. 405 kc. Tested, guaranteed. Post 1.5.

GANGED CONDENSERS, 1.9. 2 or 3-gang. Salvage, guaranteed. .0005. Post 1.3.

CAR AERIALS, 6.9. Whip antenna. 50in. long, collapses to 11in.; 1-hole fixing. Post 1.5.

CHOKES

250 m.a. 4.9. Salvage, guaranteed. P. & P. 2.6 for 30 -, P. & P. 7.6.

50 m.a. 2.9. Salvage, guaranteed. P. & P. 2.6 for 20 -, P. & P. 7.6.

10 m.a. 1.9. Salvage, guaranteed. P. & P. 2.5 for 10 -, P. & P. 6.6.

8in. P.M. SPEAKER, 3.9. Can be fitted in cabinet or enclosed door, so that radio programme can be heard while busy in the kitchen. With O.P. trans. 10 -. Post 2.9.

EXTENSION SPEAKER, 29.9. In attractive polished cabinet. Fitted with 8in. P.M. speaker, mains lead and switch. Post 3.6.

CHASSIS, 1 - each. 6. or salvage, latest type, magnet valve design. For A.M. or F.M. New, cadmium plated on swg. steel. 12 1/2 in. x 7 1/2 in. x 2 1/2 in. Post 1.9. 4 for 4.5. post 3.5. 12 for 10.5. carr. 5.

DROPPERS, 9d. 750 ohms. 2 amp. Post 6d. 6 - dozen. Post 2.6.

RELAYS, 9d. (10F 1479). 150-ohms. Break 1 make 2. G.P.O. pattern. Used. Post 1.5.

CONDENSERS, 9d. 22 mfd., 450 volt working. Card-board. New. Part 1.5. 12 for 7.5. post 3.6.

R.F. FILTER UNITS, 1.9. (4 P.O.) specifications. Beautifully made in solid brass case. Fitted with in-out switch. Simply fitted in the aerial. Has 2-stage tuning. Limited stock. Post 1.3.

VALVE SCREENING CANS, 1 - doz. Latest magnet type. Aluminium. 2 1/2 in. dia. Post 6d.

NICKEL-COBALT WIRE, 1 - 0.014in. dia., on 50-yard spools; .0022 dia., on 25-yard spools. Packed in ready-use tins, with run-out mechanism, special diluted finish. Rustproof. Ideal for earliers and outdoor use. Post 2.5. 12 for £1. post 2.6.

SPRING STEEL WIRE, 6d. .014 dia., on 50-yard wood spools. Post 9d. 25 for 10.5. post 2.6

Send 2d. stamp for FREE catalogue.

NEW-MAX ELECTRONICS LTD.

For London's Finest Bargains in electronics, television and radio equipment.

500 REPOSESSD AND SHOP SOILED T.V. SETS IN STOCK. ALSO LARGE SELECTION OF TAPE RECORDERS ALL GUARANTEED.

T.V. TUBES

RECLAIMED & GUARANTEED 10in. and 12in., £6; 11in., £5; 15in. and 17in., £7.10.0.

REBUILT TUBES with 5 months guarantee. 10in., £9.10.0; 12in., £9.14in., £11.10.0; 15in., £12.10.0; 17in., £14.

BRAND NEW FULLY GUARANTEED 14in. M.W. 36-24 tubes, £16.10.0. 17in. M.W. 43-34 tubes, £17.10.0. P.P. & Insurance on all tubes, 15/-.

BRAND NEW T1291 12in. flat face 2 volt filament. Ferranti tube will replace Brimar-Mazda-G.E.C. 12in. tubes. Price £10.10.0. Guaranteed 6 months. Also Ferranti 9in. T99 brand new 4 volt filament will replace G.E.C. Mazda or Brimar. £7.0.0.

SPECIAL OFFER. The Schmidt T.V. projection optical box for 22in. picture back projection including focus and frame coils, less tube. Original price £30. Our price including P. & P., £5.10.

Orders and Callers to:

NEW-MAX ELECTRONICS LTD. 220 Edgware Road, London, W.2. PAD 5607

COVENTRY RADIO

Audio & Component Specialists Est. 1925 189-191, Dunstable Rd., Luton, Beds. HI-FI EQUIPMENT CABINETS IN STOCK

Record Housing: Nordik Range in Oak, Walnut, Mahogany.

- Speaker Enclosure ... £5.19.6
Equipment Cabinet ... £5.19.6
Record Cabinet (150 records) £4.17.6
Continental Bench ... £4.17.6
Polenaise Hi-Fi Cabinet ... £19.19.0
W.B. Prelude Speaker Cabinet £11.11.0
W.B. Prelude Equipment Cabinet £13.13.0

- W.B. Prelude Corner Speaker Cabinet ... £10.10.0
W.B. Table Equipment Cabinet £9.19.6
W.B. Senior Hi-Fi Console ... £16.16.0
W.B. Junior Hi-Fi Console ... £12.12.0
W.B. Junior Base Reflex ... £9.9.0
W.B. Standard Base Reflex ... £10.10.0
W.B. Senior Base Reflex Corner £11.11.0

- B.K. AUDIO PLAN
B.K. Speaker Cabinet ... £16.19.6
B.K. Equipment Cabinet ... £17.19.6
B.K. Record Cabinet ... £16.16.0
B.K. Continental Bench 48in ... £7.7.0
B.K. Continental Bench 72in ... £13.13.0
B.K. Set 4-Legs tilt & glide feet £2.2.0
B.K. Set 4-Legs Plain Ebონised 19.6

- SOUTHDOWN Hi-Fi Cabinet £29.10.0
R.C.A. Lowboy Cabinet ... £18.10.0
HEALS Chairside for Quad ... £29.15.0
HEALS Chairside ... £37.0.0
BREARCLIFFE Equip. Cab. £30.9.0
BREARCLIFFE Equip. Cab. £22.1.0
ARMSTRONG Equipment Cabinet £34.19.0

Leaflets available on request.

RES/CAP. BRIDGE 35/-

Checks all types of resistors and condensers. Easy to Build Up Easy to Use READY CALIBRATED Stamp for details of this and other kits. RADIO MAIL (Dept. VB) Raleigh Mews, Raleigh Street, Nottingham

RADIO AND TELEVISION COMPONENTS

We operate a prompt and efficient MAIL ORDER Service, 3d. stamp (only) for Lists.

JAMES H. MARTIN & CO. Dept. P.T. FINSTHAVILL, NEWBY-BRIDGE, ULVERSTON, LANC'S.

TRANSFORMERS?

CONTACT Forrest FIRST! Rewinding and manufacture of all types for Television, Radio and Electronic Application.

FORREST (TRANSFORMERS) LTD., Shirley, Solihull, Warwickshire. Phone: SHL 2483. Est. 34 years.

V.A.L.V.E.S. - Guaranteed

Table of vacuum tube specifications including part numbers (EA50, EB41, EB91, etc.) and prices.

TELEKIT SUPPLY BEC 3720, 104 High Street, Beckenham, Kent.

To be certain of a copy reserve one TO-DAY!

F. J. Camm's A BEGINNER'S GUIDE TO TELEVISION

THE outstanding success of F. J. Camm's 'Beginner's Guide to Radio' has prompted the writing of this companion volume. It contains a series of lessons for the student, enthusiast and teacher covering such subjects as persistence of vision and scanning; the cathode-ray tube and timebase; interlacing; the aerial; the TV camera; scanning systems; colour and stereoscopic television, etc. There is a valuable section on technical terms. With 61 illustrations.

To be published 17th July don't wait until supplies are running out! ORDER NOW. In case of difficulty Rs. 3d. by post from GEORGE NEWNES LTD., Tower House, Southampton Street, London, W.C.2.

7s. 6d. FROM ALL BOOKSELLERS

# Wanted!

## QUALIFIED MEN AND WOMEN

Industry and Commerce offer their best posts to those with the qualifications—appointments that will bring personal satisfaction, good money, status and security. As part of a modern industrial organisation, we have skilled knowledge of what is required and the best means of training personnel for present day and future requirements. We specialise also in teaching for hobbies, new interests or part-time occupations in any of the subjects listed here. Write to us to-day for further information. There is no obligation of any kind.

### PERSONAL & INDIVIDUAL TRAINING IN —

- |                                       |                         |                               |                                |
|---------------------------------------|-------------------------|-------------------------------|--------------------------------|
| Accountancy                           | Draughtsmanship         | Mathematics                   | Sales Management               |
| Advertising                           | Economics               | M.C.A. Licences               | Sanitary Engineering           |
| Aeronautical Eng.                     | Electrical Eng.         | Mechanical Eng.               | Salesmanship                   |
| A.R.B. Licences                       | Electrical Instal.      | Metallurgy                    | Secretaryship                  |
| Art (Fashion, Illustrating, Humorous) | Electronics             | Motor Eng.                    | Servo Mechanisms               |
| Automobile Eng.                       | Electronic              | Painting & Decorating         | Shorthand & Typing             |
| Banking                               | Draughtsmanship         | Photography                   | Short Story Writing            |
| Book-keeping                          | Eng. Drawing            | P.M.G. Certs.                 | Short Wave Radio               |
| Building                              | Export                  | Police                        | Sound Recording                |
| Business                              | Gen. Cert. of Education | Production Engr.              | Telecommunications             |
| Management                            | Heat & Vent. Eng.       | Production Planning           | Television Time & Motion Study |
| Carpentry                             | 'Hi-Fi' Equipment       | Radar                         | Tracing                        |
| Chemistry                             | High Speed              | Radio                         | Transistors                    |
| City & Guilds Exams                   | Oil Engines             | Radio Amateur (C & G) Licence | Welding                        |
| Civil Service                         | Industrial Admin.       | Radio Engineering             | Workshop Practice              |
| Commercial Subjects                   | Jig & Tool Design       | Radio & Television Servicing  | Works Management etc., etc.    |
| Commercial Art                        | Journalism              | Refrigeration                 |                                |
| Computers                             | Languages               |                               |                                |
| Customs Officer                       | Management              |                               |                                |
|                                       | Maintenance Eng.        |                               |                                |

Also courses for GENERAL CERTIFICATE OF EDUCATION, A.M.I.H.&V.E., A.M.S.E., A.M.Brit.I.R.E., A.M.I.Mech.E., A.M.I.E.D., A.M.I.M.I., A.F.R.Ae.S., A.M.I.P.E., A.M.I.I.A., A.C.C.A., A.C.I.S., A.C.C.S., A.C.W.A., City & Guilds Exams., R.T.E.B. Servicing Certificates, R.S.A. Certs., etc., etc. Moderate fees.




The E.M.I. Factories at Hayes, England.  
 The only Home Study College  
 operated by a world-wide  
 manufacturing organisation
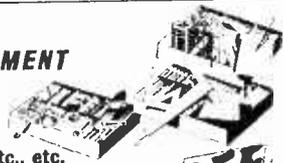
# EMI INSTITUTES

**NEW!** Courses with PRACTICAL EQUIPMENT

in RADIO · TELEVISION · MECHANICS  
 CHEMISTRY · ELECTRICITY  
 DRAUGHTSMANSHIP · PHOTOGRAPHY etc., etc.



**POST THIS TODAY**

To :- E.M.I. INSTITUTES, Dept. 138K, London, W.4.  
 NAME \_\_\_\_\_ AGE \_\_\_\_\_  
 (if under 21)  
 ADDRESS \_\_\_\_\_

I am interested in the following subject(s) with/without equipment \_\_\_\_\_

JUL 58 (We shall not worry you with personal visits)

**FREE**

BLOCK  
 CAPS  
 PLEASE

1072

-part of "His Master's Voice" Columbia, etc., etc.

# BAND III CONVERTOR for ANY SET in ANY AREA

This unit has been widely used since I.T.A. Transmissions began to convert all types of sets, Superhet and T.R.F., to receive on Band III.

Unlike many other convertors this unit is small enough to be fitted inside your cabinet, enabling the job to appear finished and perfectly safe for all to use.

The wiring is simple to follow, and alignment is not difficult. **\* IT will convert any set, any age, T.R.F. or Superhet.**

- \* IT includes station switching.
- \* IT provides pre-set contrast balancing.
- \* IT uses only one aerial input for both bands
- \* IT provides manual tuning on Band III.
- \* IT is totally screened.
- \* IT completely rejects unwanted signals.
- \* IT requires no additional power supply where either 6.3 v. or .3 amp. heater line is available.

**CONVERTOR** wired and aligned with fitting instructions ... .. £3 10 6  
**KIT** complete in every detail, less knobs ... .. £2 10 6  
**KNOBS** each ... .. 1 0  
**CIRCUIT** and instructions in detail (free with kit) 1 6  
**KITS** made up by customers checked and aligned, including post ... .. 12 6

When ordering please state present B.B.C. Station and I.T.A. Orders over £2 post free.

## C. & G. KITS

285, LOWER ADDISCOMBE ROAD,  
ADDISCOMBE, CROYDON, SURREY

Phone: ADDiscombe 5262

## RST MAIL ORDER DEPARTMENT

311 Streatham Road, Mitcham, Surrey.  
ALL VALVES LISTED ARE NEW STOCK. © Terms C.W.O. or C.O.D. Postage 3d. per valve. MITCHAM 8201

AZ1	15/6	EF40	15/-	M14	12/6	UC185	15/0	6P13	18/6
AZ51	10/6	EF41	9/6	MSP4	15/-	UF41	0/-	6J5G	0/0
B60	8/6	EF42	12/-	MT14	10/-	VF89	10/-	6J7GT	10/-
PAC32	9/9	EF80(A)	4/6	MX40	15/-	VF41	0/-	6K7	4/6
1DA91	8/-	EF80	8/-	N37	13/3	UL84	9/-	6K7GT	10/-
DAF96	9/6	EF85	7/6	N78	11/6	US	23/8	6K8GT	12/6
DD920	10/6	EF86	14/6	N142	9/6	UY41	7/6	6L1	17/6
DP23	9/9	EF89	10/-	N13	21/3	VF89	10/-	6L6G	7/6
DP91	8/6	EF91	8/6	N154	11/3	VP23	10/-	6L8	12/6
DP96	8/6	EF92	9/-	N17	8/0	WT	3/4	6L19	21/-
DH719	0/0	EP95	14/-	PC84	9/-	W77	0/0	6N7G/GT	8/-
DK91	0/-	EL38	23/6	PCF80	12/6	WRM	8/5	6S17GT	7/6
DK92	11/6	EL41	10/-	PCF82	11/6	W149	9/-	6SN/GT	8/6
DK96	3/6	EL42	10/-	PL8	12/6	W19	8/6	6T4	7/6
DL33	10/0	EL81	17/6	PL83	12/6	W27	7/6	6X5GT	8/6
DL55	15/-	EL84	9/-	PEN44	11/6	X18	11/0	6X7	12/6
DL9	8/-	EL96	5/6	PEN4V	8/6	X78	10/-	6Y4	7/6
DL66	8/9	EM80	10/-	PL86	11/6	X79	11/9	8D3	8/6
1ABC80	9/6	EM85	15/-	PL88	12/6	Z1	10/6	10F1	22/6
NAF42	10/-	EY81	10/-	PL8	10/-	Z12	8/6	10G2	18/6
BB41	10/6	EY84	13/-	PL83	12/6	Z719	8/6	10F1	22/6
EB91	5/6	EY91	9/-	PY80	8/6	10	11/9	10L1114	9/6
EB41	6	EZ35	0/6	PY81	8/6	11	8/6	10P13	22/6
EBF89	9/6	EZ40	8/6	PY82	8/6	1K1	9/-	12A18	10/6
EBF89	9/6	EZ41	10/6	PY83	8/6	1T4	8/-	12AT7	8/6
EBI21	21/-	M780	8/-	PZ30	13/6	5U4G	8/6	12AT7	8/6
EBL51	21/-	E281	8/-	R16	2/-	5Y3G1	8/6	12A17	8/6
EB91	8/6	E280	7/6	R19	19/-	Z44	10/-	12AX7	9/6
ECC33	8/6	FC2	14/6	SP41	3/6	GAMGT	0/-	12BA6	6/9
ECC40	17/6	PC4	23/6	SP61	3/6	GAL5	5/0	12BE6	9/3
ECC81	8/6	FC13	14/6	TD14	13/6	GAM6	9/-	12BH7	10/-
ECC82	9/-	PC13	19/6	TP22	12/6	GAN5	5/-	12J7G/GT	10/-
ECC85	9/-	GZ82	11/6	U78	8/-	GAQ5	7/6	12K7GT	10/6
ECC84	10/-	H30	4/9	U142	8/6	GAT6	6/3	12K8GT	10/6
ECC85	10/6	H63	10/-	U147	9/9	GBA8	8/6	12L12	12/3
ECP86	12/6	HB96	8/-	U153	9/6	GB56	8/3	12M7	8/6
ECP82	12/6	HL92	11/6	U403	9/6	GBJ6	7/6	12Q7	8/6
ECH21	21/-	HL133B	11/6	U801	27/6	GBR7	12/-	12Q7GT	8/6
ECH35	12/6	HY90	7/6	UABC80	10/-	GBV2	8/6	12R46	23/6
ECH42	9/6	KT38C	12/6	UAF42	10/-	GBV6	8/6	20L1	23/6
ECH81	9/6	KT66	16/6	UBF41	8/6	GC16G	27/-	35W4	7/6
ECL86	13/6	LZ319	12/6	UBF89	9/6	6D2	5/9	35Z4GT	8/6
EP9	21/-	MK740	12/6	UC42	4/6	6F1	19/6	50L6GT	10/6
EP37A	10/3	(or 7)	21/-	UCF81	10/6	6F12	8/6	10/-	

Quotations given for any types not listed. Obsolete and old types a speciality. Send for lists.


# LINE OUTPUT TRANSFORMERS

replacement or rewind. Send us your faulty one and we will be pleased to quote and save you money.

## AUDIO LTD.

162 Gray's Inn Rd., London, W.C.1

## 59 Gns.—'17'

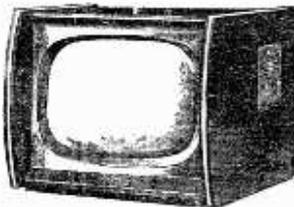

A full specification 17in. Television Receiver to Spencer-West standards now available at your Dealers. Remarkable performance and priced at 59 Gns. only, complete.

**SPENCER - WEST LTD.**  
Quay Works, Great Yarmouth  
Norfolk

Phones: Works 4794; Sales 3009  
Grams: Spencer-West, Great Yarmouth

# OPPORTUNITIES IN TELEVISION

148 pages

**Free!**

Television offers unlimited scope to the technically qualified. Details of the easiest way to study for A.M.Brit.I.R.E., R.T.E.B. Cert., City and Guilds, Television, Television Servicing, Sound Film Projection, or a Diploma Course, etc., are given in our 148-page Handbook "ENGINEERING OPPORTUNITIES" which also explains the benefits of our Appointments Dept.

**We Guarantee "NO PASS—NO FEE"**

If you are earning less than £20 a week you must read this enlightening book.


Send for your copy NOW—FREE and without obligation.

**WRITE TO-DAY!**

British Institute of Engineering Technology  
237, College House,  
29-31, Wright's Lane, **BIET**  
Kensington, W.8.
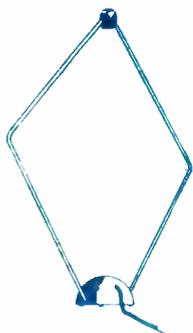
# A NEW ANTI-GHOSTING AERIAL FOR FLAT DWELLERS

(and others who cannot use an outside T/V aerial)



DEFINITELY more sensitive, more directional than any other "stand-on-the-set" aerial available. That means greater range, better contrast, less ghosting and less interference than ever before.

**COVERS ALL T/V CHANNELS—YET HAS NO SLIDING RODS OR CONTACTS TO WEAR OUT.** Finished in Black and Gold with non-slip, anti-scratch rubber base.

**LIST PRICE 39/6**

STOCKED BY LEADING T/V RETAILERS or in case of difficulty write to the sole manufacturers :

**Labgear Ltd.** WILLOW PLACE, CAMBRIDGE  
'Phone 2494. 'Grams : Labgear, Cambridge.

## YOUR OWN TELEVISION TUBE RE-BUILT

THE FOLLOWING TYPES AND SIZES ONLY.

<b>MULLARD</b> ..	12in. £7-10-0.	14in. £8-10-0.
OR EQUIVALENTS COSSOR-EMITRON-CATHODEON	17in. £10-10-0.	21in. £12-10-0.

<b>MAZDA</b> ..	14in. £8-10-0.	17in. £10-10-0.
-----------------	----------------	-----------------

All Tubes plus 15,- carriage and insurance.

### SIX MONTHS' GUARANTEE

Terms to the Trade.

Tubes can be sent to us by British Road Services (Parcels) Ltd. Carriage forward.

TERMS, CASH WITH ORDER or C.O.D.

## RE-VIEW (LONDON) LTD.

81, HIGH STREET . . . MERTON S.W.19

Telephone : CHERRYWOOD 3255

C.R.T. ISOLATION TRANSFORMER

Type A. Low leakage windings. Ratio 1:1.25 giving a 25% boost on secondary.

2 v. 10.6; 4 v. 10.6; 6.3 v., 10.6; 10.8 v., 10.6; 15.3 v., 10.6.

Ratio 1:1.25. Ratio 1:1.25.

Type B. Mains input 220/240 volts. Multi Output 2, 4, 6.3, 7.5, 10 and 12 volts.

Type C. Low capacity wound transformer for use with 2 volt Tubes with falling emulsion.

TRIMMERS, Ceramic. 30, 50, 70 pf., 9d.; 100 pf., 10p.

RESISTORS, Preferred values. 10 ohms to 10 meg.

100 to 10 meg. Ditto, 5% 100Ω - 5 meg. 0.9d.

WIRE-WOUND RESISTORS (13 10 watt; 25 ohms-10,000 ohms..... 1.3 15 watt)

12.6 PURETONE RECORDING TAPE

1,200 ft. on standard 7" Metal reels. Spare Reels 7" plastic 4 -, 7" metal, 2 3.

SUPERIOR 1,200ft. Plastic Tape on 7" Plastic Reels, 21/-

O.P. TRANSFORMERS. Heavy Duty 50 ma., 4.8. Multiratio, push-pull, 7.8. Miniature, 384, etc., 4.8.

L.F. CHOKES 15-10 H. 60.65 ma., 5/-; 10 H. 80 ma., 8.6

MAINS TRANS. 250-0-250, 30 ma., 6.3 v. tapped, 4 v., 4 v., 5 v. tapped 4 v., 2 v., ditto 250-0-250, 22.6.

HEATER TRANS. Tapped print, 200-250 v. 6.3 v. 11 amp., 7.6

ALADDIN FORMERS and core, 4 1/2", 8d.; 4 1/2", 10d.

TYANA. Migdet. Soldering Iron, 200 220 v. or 250 250 v.

MAINS DROPPERS. 3in. x 1 1/2in. 4 1/2in. 5 1/2in. 6.5 amp. 7.50 ohms, 4.3.

LINE CORD. 3 amp., 60 ohms per foot, 2 amp., 100 ohms per foot.

LOUDSPEAKER P.M. 3 OHM. 2 1/2in. square, 17.6. 3in. Goodman, 17.6.

CRISTAL DIODE G.E.C. 2- GEX34, 4-.

HIGH RESISTANCE PHONES. 4,000 ohms, 16.6 per MIKE TRANS. 30.1, 3.9 ea.; 100.1, 1.0, 10.6.

WITCH CLEANER. Flood spirit, 4.3 1/2in. TWIN GANG TUNING CONDENSERS. 365 pf.

STIGLE. 30 pF., 2.6; 100 pF., 7; 150 pF., 8.6. 50 pF. electronic iron, 500, 500 pf., 3.6.

SPEAKER FEET. Expanded Metal Silver, 15.0; 9 1/2in., 2- each.

GOLD CLOTH. 17in. x 25in., 5-; 20in. x 35in., 10-; 27in. x 50in. wide, 10-; 21in. x 30in. wide, 5- 1/2.

All Boxed VALVES New & Guaranteed

Table with 3 columns: Valve Type, Price, and Description. Includes valves like 6X4, 6X5, 6X6, etc.



1958 RADIOGRAM CHASSIS

THREE WAVEBANDS. FIVE VALVES

S.W. 16 m.-50 m. LATEST MULLARD M.W. 200 m.-500 m. ECH2, EP41, EP411, LW. 800 m.-2,000 m. E141, E249, 12-month guarantee.

A.C. 200/250 v. 4-way switch; Short-Medium-Long-gram. A.M.C. and Negative feedback 12 watts. Chassis 12 x 5 1/2 x 2 1/2in. chassis 10 x 4 1/2in. horizontal or vertical available. 2 Pilot Lamps, Four Knobs, Walnut or Ivory. Aligned and calibrated. Chassis isolated from mains.

10 gns. Carr. & Ins. 4/6.

TERMS: Deposit £5.0 and six monthly payments of £1.

MATCHED SPEAKERS FOR ABOVE CHASSIS. 8in., 17/6; 10in., 25-; 12in., 30-.

★ COLLARO ★

HIGH-FIDELITY AUTO CHANGER

Mixer Model R 458

4-SPEEDS-10 RECORDS

With Studio "O" pick-up

BRAND NEW IN MAKER'S BOXES

OUR PRICE £9.15, post free

TERMS: Deposit £5.50 and six monthly payments of £1.

Suitable Player Cabinets, 49/6.

Amplifier Player Cabinets, 43/6.

IMPORTANT NOTICE

ALL THESE RECORD PLAYERS ARE FULLY GUARANTEED AND SPARES ARE AVAILABLE

GARRARD 4-SPEED SINGLE RECORD PLAYER 48P.

AUDIO PERFECTION

Designed to play 16, 33, 45, 78 r.p.m. Records. 7in., 10in., 12in. Lightweight Kick pick-up, GC2 turnover head, two separate sapphire styl.

OUR PRICE £8.0. each. Post Free.

TERMS: Deposit £5.0 and 4 monthly payments of £1. Space required 14in. x 12in.

Builder's Player Cabinet £45

FAMOUS THIS REPRODUCER BARGAIN

Special Single Player Kits.

Build Maker's surplus stocks. 4-speed Collaro Junior gram. pick-up unit, £4 12 6.

Handsome portable case, 17in. x 14in. x 7in., £2 5 0. Rose and Cream Revue.

Ready-to-run amplifier with valves and 7in. elliptical loudspeaker, £2 12 6.

All available separately or if all purchased together, £9 15 0. complete kit, post free. £3 5 0 extra, with garnish 4 sp.

ALUMINIUM CHASSIS. 18 x 8 1/2 in. drilled.

With 4 sides, riveted corners and lattice fixing holes. 2 1/2in. holes, 7 x 1in., 4.8; 3 x 2in., 5.9; 1 1/2 x 7in., 6.9; 1 1/2 x 9in., 8.6; 1 1/2 x 11in., 10.6; 1 1/2 x 14in., 12.6; 1 1/2 x 16 x 2in., 16.6.

TRANSISTORS. Audio, 10-; R.F. 2.5 Mc/s, 21-; Mullard OC71, 20-.

HANDY VOLT METERS. 2in. Twin Range, 0-25 v., 0-250 v., D.C. with leads and leather case 12 6 complete.

CRYSTAL MIKE INSERT BY Acos, precision engineered. Size only 1 1/2in. x 3 1/2in. Bargain price 6 6. No transformer required.

TELETRON CRYSTAL SET KIT. Cabinet chassis components. Price 15- with H.F. Phones, 30-.

HI-GAIN BAND 3 PRE-AMP KIT. Cascade circuit with valve EC81. Price 29 6. With Power Pack, 49 6. Instructions only 1 6.

COSSOR COMPANION SUPERHET MODEL 527 X FOR ALL-DRY BATTERY OPERATION

S.W. 15m to 43 meters, S.W. 2 42.8 to 194 meters, Medium 187 to 17.5 meters. A fine All-wave receiver giving wide-wide reception on three wavebands. 6in. speaker. The cabinet is maroon and beige with gold trimmings. Valves: 1K32, D290, 1A1P4, 1A1P6.

OUR PRICE £6.6.0. (Battery 17 6 extra)

Linear or Log Tracks. Air-spaced 1/6 vd

Volume Controls 80 ohm

Long spindles. Guaranteed 1 year. Migdet (one insulated) in the 10,000 ohms to 2 Meg. No Sw. D.P.S.W. 3/-

COAX PLUGS ... 1.3 SOCKETS ... 1.3

BALANCED TWIN FEEDER yd. 6d. 800 100 ohms. DITTO SCREENED per yd. 1- 80 ohms only.

WIRE-WOUND POTS. 3 WATT. Pre-set Min. Type. All values 25 ohms to 30 K. 3- ea. 40 K. 2- Carbon 50 K. to 2in. 3in.

WIRE-WOUND 4 WATT. Pots 2 1/2in. Spindle Values, 100 ohms to 50 K., 5/6; 100 K., 6/6.

CONDENSERS. New Stock. .001 mfd. 7 kv. 17/6; 5.6; Ditto, 20 kv., 9/6; 100 pf. to 500 pf. Micas 6d., Tubular 500 v. .001 to 0.1 mfd., 9d.

.05, 1-1; .25, 1.6; .5, 50 v. 1.9; 1, 350 v. 9d.; 2, 2,000 v. 1.9; .1 mfd., 2,000 volts, 3.6.

CERAMIC CONDS. 500 v. .3 pf. to .01 mfd., 10d. SILVER MICA CONDENSERS. .075, .3 pf. to .400 pf. to .600 pf. to 3,000 v. 1.1. Ditto 100 pf. to 100 pf., 1.9; 1,000 pf. to 5,000 pf., 2-.

I.F. TRANSFORMERS 7/6 pair

465 Kc. Slug tuning. Miniature Can. 2 1/2in. x 1in. x 1in. High Q and good bandwidth. By Pye Radio. Data sheet supplied.

Wearite M800 I.F. 465 Kc/s 12/6 per pair

Wearite 550 I.F. 465 Kc/s 12/6 per pair

NEW ELECTROLYTIC FAMOUS MAKES

TUBULAR TUBULAR CAN TYPES

1,350 v. 2 1/2 100 250 2 1/2 8 16 250 v. 3 6

2,450 v. 2 3 8 8 500 v. 4 16 16,450 v. 5 6

4,450 v. 2 16 16,450 v. 25 20,450 v. 5 6

8,450 v. 2 3 6 32 32,450 v. 4 6

16,450 v. 3 4 16 32 32,450 v. 7 10

32,450 v. 5 6 32 50 v. 4 6 100 250 v. 11 6

25 25 v. 1 1 6 350 v. 5 6 1,000 250 v. 12 6

50 25 v. 1 8 500 12 v. 3 1,000 1,000 v. 6 6

100 20 v. 2 8 16 500 v. 8 6

SENTERCEL RECTIFIERS. E.H.T. TYPE ELY-BAK VOLTAGE

KB25 2.5 kv., 5-; KB40 4 kv., 7-; KB45 4.5 kv., 7.6; KB50 4 kv., 8-; KB100 10 kv., 14.6 50 kv. voltage, 30-; all have MAINS TYPE LEAD 500 v. 50 v. S 1/4 7/6

G.N.TACT COILED 250 v. 50 ma. 8.6; 60 ma., 8.6; 100 v., 9.6.

COLLS Wearite "P" type, 3- each. Ositor Migdet "Q" type, adj. dust core, from 4-.

TELETRON L. & Mod. T.R.F. with reaction, 3.6

FERRITE ROD MODULAR M.W. 3.8 9. M. 12.6

T.R.F. COLLS & HF 7- pair. H.F. CHOKES, 2.6

FERRITE ROD 7in. x 2 1/2in. dia., 2.6.

JASON F.M. TUNER COIL SET 26- H.F.

iron, aerial coil, Oscillator coil, two I.F. transformers, 10.7 Mc/s. Detector transformer, 4.6 heater choke. Circuit book using our 6AM2, 2-, supplied free with kit.

With Jason superior calibrated dial, £8.15 6. 1000 extra kit, 22/6 extra.

FULL WAVE BRIDGE SELENIUM RECTIFIERS

2.6 or 12 v., 11 amp., 8.9; 2 in., 11.3; 4 in., 17.6

CHARGER TRANSFORMERS. Tapped input 300 250 v. for charging at 2.6 or 12 v., 11 amps., 15 6

2 amp., 15 6; 4 amp., 22 6; 6 amp., 29 6; all 100 pf.

VALVE and T.V. TUBE EQUIPMENT

TOGGLE SWITCHES. S.P. 2-; P.P. 3.6; D.P.D.F. 4-; WAVECHANGING SWITCHES

5 p. 4-way 2 water long spindle 6 6

2 p. 4-way 3 p. 2-way short spindle 2 6

2 p. 6-way 4 p. 2-way 1 p. 4-way long spindle 2 6

2 p. 6-way 1 p. 4-way 1 p. 4-way long spindle 3 6

2 p. 6-way 1 p. 4-way long spindle 3 6

VALVE HOLDERS. Pat. Inc. Oct. 4d. EP50, EP40, 6d. 1A1P4, R.F. 1.3, Eng. and Amer. 1.3, 6, 7 and 3 pin, 1.3. MOULDED BAZDA and 1A1P4, 6d.

1K32, B.V. 100, B.V. 24, HF with core, 1.6

ACR37, 2.6. HF with core, 2.6. CERAMIC I.F. 465 Kc/s, 100 pf., 1.9; 1,000 pf., 2.6.

OUR WRITTEN GUARANTEE WITH EVERY PURCHASE. Please address all Mail Orders correctly as below.

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE RD., WEST CROYDON

OPEN ALL DAY (Wed. 1 p.m.) Catalogue 6d.

Tel. THO 865. Buses 133 or 68 pass door. 48-hour postal service, P. & P. 1/-, over £2 post free. (Export Extra.) C.O.D. Service 1/6