

TELEVISION

20p

SERVICING · CONSTRUCTION · COLOUR · DEVELOPMENTS


OCTOBER
1973

EXTRA

***BASIC
COLOUR TV
FAULTS GUIDE**



***SPECIAL
SUPPLEMENT
IN FULL
COLOUR**

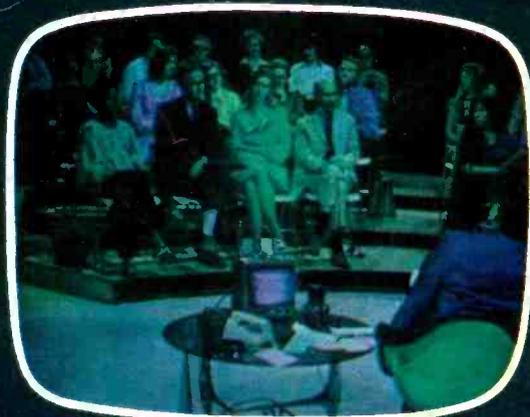

**ALSO: 110° COLOUR · VARICAP TUNING SYSTEM
SERVICING THE ITT/KB VC200 CHASSIS**

WITWORTH TRANSFORMERS

MONOCHROME TV Line out-put transformers (Discounts to Trade)

ALL ONE PRICE £5.17 EACH V.A.T. & CARRIAGE PAID

BUSH

TUG versions	TV125
TV75 or C	TV125U
TV76 or C	TV128
TV77	TV134
TV78	TV135
TV79	TV135R
TV83	TV138
TV84	TV138R
TV85	TV139
TV86	TV141
	TV145

TV91	TV148
TV92	TV161
TV93	TV165
TV94	TV166
TV95 or C	*TV171
TV96 or C	TV175
TV97	TV176
TV98C	TV178
TV99 or C	181S
TV100C	183
TV101C	183D
TV102C	183S
TV103 or D	183SS
TV105 or D or R	185S
TV106	186
TV107	186D
TV108	186S
TV109	186SS
TV112C	191S
TV113	191D
TV115 or C or R	193S
TV118	193D
TV123	
TV124	

From model TV123 to TV139 there have been two types of transformer fitted. One has pitch overwind, the other has plastic moulded overwind. Please state which type required as they are not interchangeable.

BAIRD

600	628	662	674
602	630	663	675
604	632	664	676
606	640	665	677
608	642	666	681
610	644	667	682
612	646	668	683
622	648	669	685
624	652	671	687
625	653	672	688
626	661	673	

Please quote part No. normally found on tx. base plate; 4121, 4123, 4140 or 4142.

DECCA

DR20	DR34	DR71	DR505
DR21	DM35	DR95	DR606
DR23	DM36	DR100	666TV-SRG
DR24	DM39C	DR101	777TV-SRG
DR29	DR41	DR121	
DR30	DM45	DR122	MS1700
DM30	DR49C	DR123	MS2000
DR31	DM55	DR202	MS2001
DR32	DM56	DR303	MS2400
DR33	DR61	DR404	MS2401

SOBELL

T24	ST284 or ds	1010dst	1033
SC24	ST285 or ds	1012	1038
TFS173	ST286 or ds	1013	1039
TPS180	ST287 or ds	1014	1047
ST195 or ds	ST288 ds	1018	1048
ST196 or ds	ST290ds	1019	1057
ST197ds	ST291ds	1020	1058
SC270	ST297ds	1021	1063
T278		1000ds	1022
ST282		1002ds	1023
ST283		1005ds	1032
			1066

MURPHY

V310	V430	V520
V310A	V430C	V530
V310AD	V430D	V530C
V310AL	V430K	V530D
V310CA	V440	V539
V320	V440D	V540
V330 or D	V440K	V540D
V330F or L	V470	V649D
V410	V480	TM2 Chassis
V410C	V490	V843*
V410K	V500	V849*
V420	V510	V873*
V420K	V519	V787

*Two types fitted. One has pitch overwind, the other has plastic moulded-overwind. Please state which type required as they are not interchangeable.

PHILIPS

23TG111a	G19T210	G23T210
23TG113a	G19T211	G23T211
23TG121a	G19T212	G23T212
23TG122a	G19T213	G24T230
23TG131a	G19T214	G24T232
23TG142a	G19T215	G24T236
23TG152a	G20T230	G24T238
23TG153a	G20T232	G24T300
23TG156a	G20T236	G24T301
23TG164a	G20T238	G24T302
23TG170a	G20T300	G24T306
23TG171a	G20T301	G24T307
23TG173a	G20T302	G24T308
23TG175a	G20T306	
23TG176a	G20T307	
23FG632	G20T308	

GEC

2000	2015	2022	2043	2064
2001	2017	2023	2044	2065
2010	2018	2032	2047	2066
2012	2019	2033	2048	2062
2013	2020	2038	2063	2083
2014	2021	2039		

PYE

11u Series	
12u	
13u	State Pt. No.
14u	required
15u	AL21003 or
20u	772494

V700 or A or D	
V710 or A or D	State Pt. No.
V720	required—
V830A or D or LBA	772444 or 771935

FERGUSON, ULTRA, MARCONI, H.M.V. ALL MODELS IN STOCK.

(BRC, Jellypots).

ALBA, COSSOR, EKCO, FERRANTI, K.B., PYE. ALL MODELS IN STOCK.

E.H.T. RECTIFIER TRAYS

THORN B.R.C. MONOCHROME	ORDER Ref.	
980, 981, 982	RT1	£3.30
911, 950/1, 960	RT2	£3.60
950/2, 1400-5 stick	RT3	£3.90
1400 Portable-3 stick	RT3A	£3.60
1500 20" 3 stick	RT4	£3.60
1500 24" 5 stick	RT5	£3.90
1580 Portable-2 stick	RT16	£3.50
1590, 1591	RT17	£1.30

MAKE	CHASSIS COLOUR	
DECCA	CTV19, CTV25	£6.30
DECCA	CS1910, CS2213	£6.30
DECCA	CS1730	£5.80
GEC	Dual & Single std.	£6.10
ITT-KB	CVC-1, 2, 3	£6.30
PHILIPS	G8	£6.30
PYE	691, 692, 693, 697	£6.10
PYE	713	£6.40
BUSH MURPHY	Single std plug-in	£6.30
BUSH MURPHY	Dual standard	£8.40
THORN BRC	2000	£7.30
THORN BRC	3000	£6.60
THORN BRC	8000	£4.10
THORN BRC	8500	£4.20

COLOUR TV Line out-put transformers

THORN (BRC)	BUSH	EKCO
2000 Chassis	CTV25 Mk. 1 & 2	CT102
Scan O/P Tx.	£10.10 ea.	CT104
EHT O/P Tx.		£11.70 ea.
3000 Chassis	CTV25 Mk.3	CT103
Scan O/P Tx.	CTV162	CT105
EHT O/P Tx.	£7.90 ea.	CT106
8000 Chassis	CTV167 Mk.1 & 2	CT107
	£10.10 ea.	CT108
8500 Chassis	CTV167 Mk.3	CT109
All £6.80 ea.	CTV174D	CT111
	CTV182S	CT120
	CTV184S	CT121
	CTV187CS	CT122
	CTV194S	&/T
	CTV197C	£8.90 ea.
	CTV199S	
	£7.10 ea.	
GEC		
Dual Standard		
Single Standard		
£7.90 ea.		
ITT-KB		
CVC1 Chassis		
CVC2 "		
£7.10 ea.		
CVC5 Chassis		
£8.10 ea.		
PHILIPS		
G6 Chassis D/S		
G6 " S/S		
£8.70 ea.		
G8 Chassis		
£7.90 ea.		
DECCA		
CTV19 Valve Rec.		
CTV25		
Overwind 'Coil'		
£5.10 ea.		
Primary Coil		
£3.70 ea.		
CTV19 D/S Tripler		
CTV25		
CTV25 S/S Tripler		
CS1730		
£7.80 ea.		
G8 Chassis		
£7.10 ea.		
PYE		
CTV70		
CTV71		
£11.70 ea.		
CT72		
CT73		
CT78		
CT79		
CT152		
CT153		
CT154		
£8.90 ea.		
MURPHY		
CV1912	CV2510 Mk.3	
CV1916S	CV2511 Mk.3	
CV2210	CV2516S	
CV2212	CV2610	
CV2213	CV2611	
CV2214	CV2614	
	£7.90 ea.	
CV2510 Mk. 1 & 2		
CV2511 Mk. 1 & 2		
	£10.10 ea.	

Every item listed stocked. Most newer and older models in stock. S.A.E. for quotation For by-return service contact your nearest depot. Callers welcome.

Tidman Mail Order Ltd., Dept. NA.
236 Sandycombe Road,
Richmond, Surrey.
London: 01-948 3702 or 01-940 8146

Hamond Components (Midland) Ltd., Dept. NA.
89 Meriden Street,
Birmingham 5.
Birmingham: 021-643 2148

NO HIDDEN EXTRAS - PRICES INCLUDE V.A.T. and CARRIAGE

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. Telephone: 6743

0A2	0-33	6AQ5	0-22	6P23	0-65	7B7	0-50	20D4	2-00	30C5	0-32	CY31	0-29	EBL21	0-60	EF184	0-27	HVR2	0-53	PCL83	0-54	PY500A	-80	UU12	0-20	
0B2	0-33	6AR5	0-55	6P24	0-60	7F8	1-00	20P2	0-67	30C10	0-27	D63	0-25	EG34	0-50	EF804	1-20	HVR2A	-53	PCL84	0-32	UV04/7	-63	U22	0-39	
0Z4	0-44	6AI9	1-00	6P25	0-51	7H7	0-50	20L1	0-80	30C15	0-55	DA33	0-55	EG86	0-59	EF805	0-50	HVR2B	-53	PCL85	0-32	UV04/8	-63	U23	0-39	
1A3	0-49	6AT6	0-30	6P28	0-60	7R7	1-50	20P1	0-55	30L6T	-45	DAF91	0-22	EG88	0-59	EF806	0-55	HVR2C	-53	PCL86	0-32	UV04/9	-63	U24	0-39	
1A5GT	0-49	6AT6	0-28	6P32	0-30	7V7	1-00	20P3	0-75	30L7	-45	DAI96	0-36	EG91	0-28	EF807	0-50	HVR2D	-53	PCL87	0-32	UV04/10	-63	U25	0-39	
1A7GT	0-33	6AV6	0-33	6G18A	0-75	7Y4	0-85	20P4	0-80	85A2	-43	DC90	0-60	EG92	1-50	EF808	0-50	HVR2E	-53	PCL88	0-32	UV04/11	-63	U26	0-39	
1B3GT	0-49	6AW8A	0-65	6GK5	0-65	7Z4	0-80	20P5	0-95	85A3	-43	DD4	1-00	EG93	1-50	EF809	0-50	HVR2F	-53	PCL89	0-32	UV04/12	-63	U27	0-39	
1D5	0-55	6AX4	0-55	6GU7	0-75	8WV6	0-65	23AG6	0-38	90AG	-38	DF33	0-60	EG94	0-95	EF810	0-50	HVR2G	-53	PCL90	0-32	UV04/13	-63	U28	0-39	
1D6	0-75	6BR6	0-25	6H6GT	0-18	9D7	0-40	25L6G	0-20	90AV	-38	DF91	0-16	EG95	0-88	EF811	0-50	HVR2H	-53	PCL91	0-32	UV04/14	-63	U29	0-39	
1G6	0-75	6BA8	0-19	6J5GT	0-29	10C2	0-65	25Y5	0-38	900G	-17	DF96	0-36	EG96	0-88	EF812	0-50	HVR2I	-53	PCL92	0-32	UV04/15	-63	U30	0-39	
1H5GT	0-55	6BC8	0-60	6J6	0-20	10D67	0-55	25Y6G	0-70	90CV	-16	DF63	0-44	EG97	0-88	EF813	0-50	HVR2J	-53	PCL93	0-32	UV04/16	-63	U31	0-39	
1I4	0-14	6BE6	0-20	6J74	0-24	10F1	0-65	25Z4G	0-35	90C1	-59	DF76	0-46	EG98	0-88	EF814	0-50	HVR2K	-53	PCL94	0-32	UV04/17	-63	U32	0-39	
1L1D5	0-68	6BG6G	1-05	6J7M	0-38	10F9	0-65	25Z5	0-60	150B2	-58	DF77	0-30	EG99	0-88	EF815	0-50	HVR2L	-53	PCL95	0-32	UV04/18	-63	U33	0-39	
1LN5	0-68	6BH6	0-70	6J8A	0-75	10F18	0-55	25Z6GT	-70	301	-100	DF81	0-88	EG100	0-88	EF816	0-50	HVR2M	-53	PCL96	0-32	UV04/19	-63	U34	0-39	
1N5GT	0-60	6BJ6	0-39	6K70	0-12	10LD11	-70	2917	1-00	302	-83	DK32	0-33	EG101	0-88	EF817	0-50	HVR2N	-53	PCL97	0-32	UV04/20	-63	U35	0-39	
1K6	0-28	6BK7A	0-60	6K8G	0-33	10P13	0-54	30A5	0-65	303	-75	DK40	0-55	EG102	0-88	EF818	0-50	HVR2O	-53	PCL98	0-32	UV04/21	-63	U36	0-39	
1S4	0-33	6BQ5	0-23	6L1	2-00	10P14	2-00	30C1	0-26	303	-83	DK41	0-28	EG103	0-88	EF819	0-50	HVR2P	-53	PCL99	0-32	UV04/22	-63	U37	0-39	
1N3	0-22	6BQ7A	0-50	6L6GT	0-55	12A6	1-00	30C15	0-58	305	-65	DK92	0-50	EG104	0-88	EF820	0-50	HVR2Q	-53	PCL100	0-32	UV04/23	-63	U38	0-39	
1U4	0-44	6BR8	0-90	6L7	0-34	12AC6	0-55	30C17	0-76	807	-59	DK96	0-46	EG105	0-88	EF821	0-50	HVR2R	-53	PCL101	0-32	UV04/24	-63	U39	0-39	
1U5	0-80	6BR8	0-75	6L12	0-34	12AD6	0-60	30C18	0-55	1821	-53	DL32	0-55	EG106	0-88	EF822	0-50	HVR2S	-53	PCL102	0-32	UV04/25	-63	U40	0-39	
2D21	0-14	6BS7	1-40	6L18	0-49	12AE6	0-60	30C19	0-75	061	4033X	1-25	DL92	0-28	EG107	0-88	EF823	0-50	HVR2T	-53	PCL103	0-32	UV04/26	-63	U41	0-39
20K5	0-55	6BV6	0-72	6L19	2-00	12AT6	0-28	30FL1	0-58	5702	-80	DL96	0-38	EG108	0-88	EF824	0-50	HVR2U	-53	PCL104	0-32	UV04/27	-63	U42	0-39	
3A4	0-38	6BW7	0-50	6LD12	0-30	12AT7	0-28	30FL2	0-60	6960	-80	DM70	0-30	EG109	0-88	EF825	0-50	HVR2V	-53	PCL105	0-32	UV04/28	-63	U43	0-39	
3B7	1-00	6BZ6	1-40	6L20	0-55	12AU6	0-38	30FL12	0-60	6960	-80	DM71	0-55	EG110	0-88	EF826	0-50	HVR2W	-53	PCL106	0-32	UV04/29	-63	U44	0-39	
3D6	0-19	6C4	0-28	6N7GT	0-60	12AU7	0-21	30FL13	0-50	7475	-70	DW4	500-38	EG111	0-88	EF827	0-50	HVR2X	-53	PCL107	0-32	UV04/30	-63	U45	0-39	
3Q4	0-49	6C6	0-22	6P15	0-23	12AV6	0-28	30FL14	0-68	1A834	1-00	DY87/6	0-22	EG112	0-88	EF828	0-50	HVR2Y	-53	PCL108	0-32	UV04/31	-63	U46	0-39	
3Q5GT	0-55	6C9	1-00	6P28	0-70	12AX7	0-22	30L1	0-29	A2134	0-98	DY82	0-30	EG113	0-88	EF829	0-50	HVR2Z	-53	PCL109	0-32	UV04/32	-63	U47	0-39	
3R4	0-28	6C12	0-28	6Q7G	0-44	12BA6	0-30	30L15	0-55	A3042	-75	E80CC	1-65	EG114	0-88	EF830	0-50	HVR2AA	-53	PCL110	0-32	UV04/33	-63	U48	0-39	
4C6	0-55	6C17	1-00	6Q7M	0-55	12B16	0-30	30L17	0-65	AC2/PEN	-80	E80F	1-20	EG115	0-88	EF831	0-50	HVR2AB	-53	PCL111	0-32	UV04/34	-63	U49	0-39	
3G6	0-55	6C6A	0-40	6Q7GT	0-40	12B17	0-30	30P4M1	0-95	AC2/PEN	-98	E816	1-20	EG116	0-88	EF832	0-50	HVR2AC	-53	PCL112	0-32	UV04/35	-63	U50	0-39	
6R4G Y	0-70	6C6B	0-80	6R7	0-75	12B3GT	0-33	30P12	0-89	AC6/PEN	-38	E88CC	0-60	EG117	0-88	EF833	0-50	HVR2AD	-53	PCL113	0-32	UV04/36	-63	U51	0-39	
5T4	0-30	6C6BA	0-75	6R7G	0-60	12J7GT	0-55	30P16	0-31	AC2/PEN	-80	E82CC	0-40	EG118	0-88	EF834	0-50	HVR2AE	-53	PCL114	0-32	UV04/37	-63	U52	0-39	
5U4G	0-30	6C18	0-55	6SA7	0-35	12K5	0-53	30P19	0-57	DD	0-98	E180F	0-90	EG119	0-88	EF835	0-50	HVR2AF	-53	PCL115	0-32	UV04/38	-63	U53	0-39	
5V4G	0-35	6C16	0-48	6SCTGT	0-38	12K7GT	0-38	30P4	0-65	AC/PEN(7)	-80	E182CC1	0-60	EG120	0-88	EF836	0-50	HVR2AG	-53	PCL116	0-32	UV04/39	-63	U54	0-39	
5Y3GT	0-30	6C18A	0-80	6S6GT	0-38	12Q7GT	0-45	30P11	0-57	-98	E1148	0-53	EG121	0-88	EF837	0-50	HVR2AH	-53	PCL117	0-32	UV04/40	-63	U55	0-39		
6Z3	0-53	6C17	0-75	6S1H	0-44	12SA7GT	0-55	30P12	0-29	AC/TH1	-50	E1148	0-53	EG122	0-88	EF838	0-50	HVR2AI	-53	PCL118	0-32	UV04/41	-63	U56	0-39	
6Z4G	0-34	6C15	0-75	6S1GT	0-35	12SCT	0-50	30P113	0-75	AC/TH1	0-98	E176	0-88	EG123	0-88	EF839	0-50	HVR2AJ	-53	PCL119	0-32	UV04/42	-63	U57	0-39	
6Z4GT	0-38	6C14	0-70	6S1GT	0-44	12SCT	0-38	30P114	0-75	ALB0	-78	E18C	0-80	EG124	0-88	EF840	0-50	HVR2AK	-53	PCL120	0-32	UV04/43	-63	U58	0-39	
6/30L2	0-55	613	0-60	6S2GT	0-38	12SH7	0-35	30P115	0-87	ARP3	-35	E18C91	0-38	EG125	0-88	EF841	0-50	HVR2AL	-53	PCL121	0-32	UV04/44	-63	U59	0-39	
6AR6	0-44	6D8E7	0-75	6L4GT	0-70	12SH7	0-44	35.51	0-63	ATP4	0-40	E18F42	0-48	EG126	0-88	EF842	0-50	HVR2AM	-53	PCL122	0-32	UV04/45	-63	U60	0-39	
GACT	0-15	6D76A	0-75	6L7G	0-75	12SK7	0-55	35A3	0-48	AZ1	0-40	E18F801	0-50	EG127	0-88	EF843	0-50	HVR2AN	-53	PCL123	0-32	UV04/46	-63	U61	0-39	
6AG5	0-27	6EW6	0-75	6V6G	0-17	12SQ7GT	0-55	35A5	0-75	AZ31	0-46	E1834	0-25	EG128	0-88	EF844	0-50	HVR2AO	-53	PCL124	0-32	UV04/47	-63	U62	0-39	
6AH6	0-50	6E5	0-75	6V6GT	0-27	14H7	0-55	35D5	0-70	AZ41	0-53	-80	-80	EG129	0-88	EF845	0-50	HVR2AP	-53	PCL125	0-32	UV04/48	-63	U63	0-39	
6A15	0-75	6F1	0-70	6X4	0-27	14H7	0-75	35L8GT	0-42	1336	0-60	-80	-80	EG130	0-88	EF846	0-50	HVR2AQ	-53	PCL126	0-32	UV04/49	-63	U64	0-39	
6AK5	0-27	6F6G	0-35	6X3GT	0-25	19AQ5	0-42	35W4	0-23	1319	0-29	-80	-80	EG131	0-88	EF847	0-50	HVR2AR	-53	PCL127	0-32	UV04/50	-63	U65	0-39	
6AK6	0-60	6F13	0-45	6Y6G	0-65	19GG6G	0-30	35Z3	0-50	1333	0-90	-80	-80	EG132	0-88	EF848	0-50	HVR2AS	-53	PCL128	0-32	UV04/51	-63	U66	0-39	
6AM6	0-17	6P14	0-40	6Y7G	1-00	19G6	1-40	35Z4GT	0-24	CV6	0-53	-80	-80	EG133	0-88	EF849	0-50	HVR2AT	-53	PCL129	0-32	UV04/52	-63	U67	0-39	
6AM8A	0-55	6P15	0-65	7AN7	0-29	1911	2-00	35Z5GT	0-30	CV63	0-53	-80	-80	EG134	0-88	EF850	0-50	HVR2AU	-53	PCL130	0-32	UV04/53	-63	U68	0-39	
6AN8	0-49	6P18	0-55	7B6	0-75	2011	0-55	50B5	0-35	CY1C	0-55	-80	-80	EG135	0-88	EF851	0-50	HVR2AV	-53	PCL131	0-32	UV04/54	-63	U69	0-39	

All valves are unused, boxed, and subject to the standard 90-day guarantee. Terms of business—Cash or cheque with order only. Despatch charge 8p per order up to three items, then each additional 3p extra. Orders over 45 postage free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 3p extra per order. Terms of business available free on request. Business hours Mon.-Fri. 9.30-3pm. Closed 1-2 p.m.
We do not handle seconds nor rejects, which are often described as "New and tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for a reply.

TV LINE OUTPUT TRANSFORMERS

ALL MAKES SUPPLIED PROMPTLY by our
RETURN OF POST MAIL ORDER SERVICE

All Lopts at the one price
£4.40 TRADE £4.95 RETAIL (INCLUDING V.A.T.)


- Except BUSH MODELS TV53 to TV67 TV94 to TV101
- EKCO MODELS TC208 to TC335, TV407 to TV417
- FERGUSON MODELS 405 to 438, 506 to 546.
- FERRANTI MODELS 1084 to 1092.
- HMV MODELS 1876 to 1878, 1890 to 1896, FR 20.
- MURPHY MODELS 653X to 789 OIL-FILLED
- REGENTONE MODELS 10-4 to 10-21, 1718, R2, R3, 191, 192.
- RGD 519—621, 710, 711.

ALL AT £2.75 + 28p P&P

EHT TRAYS SUPPLIED—MONO & COL.

All Lopts NEW and GUARANTEED for SIX MONTHS

E. J. PAPWORTH AND SON Ltd., 01-540 3955
80, MERTON HIGH ST., LONDON, S.W.19 01-540 3513

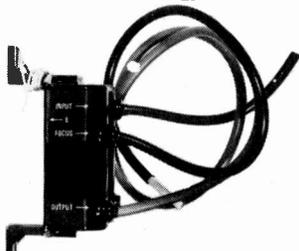SOUTHEND ELECTRONICS**COLOUR 25 KV TRIPLERS****REPLACEMENT TRIPLERS**

£1.70 + 17p VAT

**PYE CT 72 SERIES
GEC 2028 SERIES**

£3.00 + 30p VAT

200 + 200 + 100 + 32
X 80/150 D
70p + 7p VAT**E.H.T. RECTIFIRE STICKS**

10p + 1p VAT

TRANSISTOR UHF VHFTuner Units
£3.00 + 30p VAT**SIX PUSH BUTTON UHF**Tuner Units
£4.00 + 40p VAT**SIX PUSH BUTTON**UHF VHF Tuner Units
£4.00 + 40p VAT**100 MIXED W/W RESISTORS**

£1.00 + 10p VAT

300 MIXED RESISTORS

£1.00 + 10p VAT

250 MIXED CONDENSER

£1.00 + 10p VAT

40 MIXED POTS

£1.00 + 10p VAT

**G6 SINGLE STANDARD
CONVERGENCE CONTROL
PANEL INCL. 16 CONTROLS
SWITCHES ETC & CIRCUITS**

£5.00 + 50p VAT

SOUTHEND ELECTRONICS240 Rayleigh Road, Eastwood,
Leigh-on-Sea, Essex.P.P. Paid U.K. Only
NO PERSONAL CALLERS, PLEASE**PADGETTS RADIO STORE**OLD TOWN HALL, LIVERSEDEGE,
YORKS. WF15 6PQ.

TEL: HECKMONDWIKE 405285

The T.V. Graveyard of the North, as seen on T.V. Close to the
Motorway. Plenty of Free Parking Space. Est. 1935.FAMOUS R & A SPEAKERS. 30HM. 50p P & P. 12p.
NEW TOP QUALITY MAINS TRANSFORMERS. 250v-250v at
80ma. 6-3v at 4 Amp. Not to be missed at £1.80. Post paid.
Weight 10 lbs.COMPLETE UNTESTED T.V. SETS. With back and all valves.
BBC1 & ITV. 17" 90° Tube £1. 17" 110° Tube £2.20. 19" £3.30.
Carr. and Ins. on any set £1.65.

50 UNTESTED T.V. VALVES 50p. Post PAID.

¼CWT. OF EX GOVERNMENT ELECTRONIC SCRAP. Resistors,
Panels, Gears, etc. 30p. Carr. 80p19" UNTESTED BBC2 SETS. When available £6. Carriage and
Ins. £1.65.SPEAKERS. Removed from T.V. sets. all 3 ohm. 7 x 4", 8 x 2½",
6 x 4" 27p, post 11p.TOP QUALITY TAPE. Reel to reel. 5" ST. 44p. 5" LP. 55p.
5½" LP. 60p. 7" ST. 66p. 7" LP. 80p. Post on any Tape 11p. Tapes
Cassette Type. C60 35p. C90 45p. C120 55p.

JAP EARPIECE. 8 ohm Magnetic 2-5 12p. 3-5 12p.

EX EQUIPMENT VALVES. All tested on our Mullard Valve Tester
before despatch. 3 months guarantee on all Valves. Single Valves
Post 3p. Over post paid.

ARPI2	6p	PCF80	6p	PY82	10p
EB91	5p	PCC84	6p	PY33	20p
EF80	10p	PCL82	14p	U191	20p
EBF89	15p	PCL83	15p	6BW7	12p
ECC81	12p	PCL84	15p	6U4	12p
ECC82	12p	PL82	10p	6F23	20p
EF91	5p	PL83	10p	20P1	15p
EY86	22p	PL36	17p	20P3	12p
EF183	20p	PY81	10p	30F5	12p
EF184	20p	PY801	17p	30FL1	20p
		PY800	17p		

AIDS TO SERVICING

SWEEP GENERATOR/WOBBULATOR. Our New Wide range sweep generator 5 MHZ to 150 MHZ (useful harmonics up to 1.5 GMZ) up to 15 MHZ sweep width. Only 3 controls, preset RF level, sweep width and frequency. Can be used with any general purpose scope for displaying responses, 10.7, TV IF, alignment, filters, receivers and many others. Full instructions supplied. Connect 6.3V AC and use within minutes of receiving. ALL THIS FOR ONLY £6.33 P & P 27½p. Suitable miniature transformer for 240 Volt operation £1.38.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2 HZ to 8 MHZ. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY £6.05 P & P 27½p.

SOLARTRON CD711S.2
DOUBLE BEAM OSCILLOSCOPE DC—9 mc/s; 3 mv/CM; trigger delay; crystal calibrator; 4" flat faced tube. In good working condition. Only £46.75. Carr. £1.65.

SOLARTRON CD523 SINGLE
BEAM OSCILLOSCOPE 3db at 10mhz; 1mV Max sensitivity. DC coupled down to 1 volt. 4" flat faced PDA tube. TB from 1 secs per cm to 0.1 microsecs per cm plus times 5 expansion. £55. Carr. £1.65.

OPEN 9 a.m. to 6.30 p.m. ANY DAY

CHILTMEAD LTD

7/9 ARTHUR ROAD, READING, BERKS.

(rear Tech. College)

Tel.: Reading 582605/65916

COLOUR TUBES STANDARD TUBES METAL BAND TUBES TWIN PANEL TUBES

Rebuilt with new Electron
Guns to British Standard
415/1/1967.

SUFFOLK TUBES LIMITED

261 CHURCH ROAD
MITCHAM, SURREY CR4 3BH

01-640 3133/4/5

Britain's Largest Independent
TV Tube Rebuilder

CUT PRICE T.V. AERIALS

U.H.F. outdoor arrays (with clamp)
10 ele. £1.50; 18 ele. £2.50; J. Beam
MBM46 £5.50. Aerialite Supreme £5.50.
Labgear Set Top suitable for all channels
can also be wallmounted £2.50.

STEREO RADIO 2 ele. £2.50, 3 ele.
£4.00, 4 ele. £4.40, 6 ele. £6.80.

COAX. CABLE Low loss random
lengths, 2 yds.—12 yds., 5p yd.; cut
lengths 8p yd., standard cable 5p yd.

AMPLIFIERS: Pye/Labgear. Distri-
bution 6+2 outlets £16.20, 1 outlet
£10.50; Mast head/power unit £8.50.
Set back btt. op. £3.75.

ACCESSORIES: Coax plug 9p, surface
socket 30p, flush socket 50p, line
connector 14p, Diplexers v.h.f. band
1/3 50p, u.h.f. gp. A/B-CD or A-B/CD
75p, splitters 90p, plastic cape 24
yds. x 2" 25p, cable clips 7mm 30p
100, 5mm 25p 100.

LASHING EQUIPMENT: Universal
clamps 45p, lash kit 1"—1½" masts
£1.00, wall-mounting bracket 75p,
loft-mounting kit 55p.
Please add 10% V.A.T. to all items.
Please state ch. gp. clearly.

P.—P.: Aerials 50p; other items 30p.
C.W.O. to:

H. A. ELECTRIC
Dept. P.T.
2 & 4 BARDEN LANE
BURNLEY, LANCs.

TELEVISION TUBE SHOP

BRAND NEW TUBES AT
REDUCED PRICES

A31-18W	£12.50
A47-11W	£9.95
A47-13W	£12.50
A47-14W	£8.25
A47-26W	£10.75
A50-120WR	£12.50
A59-11W	£12.95
A-59-13W	£13.50*
A59-15W	£9.95
A59-23W	£14.75
A61-120WR	£16.50
AW43-80	£6.95
AW43-88, 43-89	£6.75
AW47-90, 47-91	£7.50
AW53-80	£7.50*
AW53-88, 53-89	£8.25
AW59-90, 59-91	£9.00
CME1201	£12.50
CME1601	£10.50
CME1602	£12.00
CME1705	£7.75
CME1713/A44-120	£14.50
CME1901, 1903	£7.50
CME1906	£12.50
CME1908	£7.75
CME2013	£12.50
CME2101, 2104	£8.25
CME2301, 2302, 2303	£9.00
CME2305	£14.75
CME2306	£13.50*
CME2308	£9.95
CME2413R	£16.50
MW43-80	£6.75
MW53-20, 53-80	£7.50
TSD217, TSD282	£14.00†
13BP4 (Crystal 13)	£14.00†
190AB4	£9.25
230DB4	£11.25

* These types are fully rebuilt.

† Rebuilt tubes also, at £7.00 plus
carriage and old bulb.

COLOUR TUBES	NEW	R/B
19" Unprotected	£ 25	-
A49-120X	45	-
A56-120X	72	48
A61-15X	78	52
A63-11X	-	52
A66-120X	82	55
A67-120X	85	-

SHOP-SOILED COLOUR TUBES

19", 22" & 26" NOW AVAILABLE
Brand new, with slight scratches.
Prices from £20. Callers only.
Add Carriage and Insurance: Mono-
chrome 75p, Colour £1.50.

ALL PRICES SUBJECT TO V.A.T.

TELEVISION TUBE SHOP

48 BATTERSEA BRIDGE ROAD
LONDON, S.W.11. BAT 6859
WE GIVE GREEN SHIELD STAMPS

COLOR T.V. 19" £95 25" £125

SUMMER SALE PRICES

Bush CTV25 — CTV167, PYE CT70,
THORN 2000, DECCA CTV19—25,
PHILIPS G6 etc etc, as available.

ALL with repolished cabinets.

MONO 19" Push-button
UHF tuner, Single-standardised.
£19.90

BBC 2

TV's WORKING — £10

BBC 2 Non-working — £8

VHF Working — £3

Carr. £2.50 per set. Add VAT to total
price.

G.E.C. COLOR DECODER PANELS

NEW appearance, 11" x 5½" approx.

Grade B Complete untested

£4.50 + 25p p & p

Grade C Some physical damage but
complete with DL20

£3.00 + 25p p & p (2 for £6 post paid)

XTALS — 4.43MHz

40p carr. paid

DL20 COLOR DELAY LINE

£2.50 carr. paid. (both ex-equip.)

UHF TRANSISTOR Tuners

New, untested £5 + 25p carr.

TV STANDS

TV Stands £3.25 + 50p Carr.

Please state length and depth of set,
since each stand is specially made
to your order. Supplied "in the white"
or stained and polished to your
requirements at no extra charge.

**SUMIKS 7 High Street,
Langley, Warley, Worcs.
(Near t/o No. 2, M5 M'way)**

REBUILT COLOUR TUBES

19" £22.50	22" £25.00
25" £27.00	26" £28.00

Exchange prices: Tubes
supplied without exchange
glass at extra cost, subject
to availability.

Colour Tubes demonstrated
to callers.

Carriage extra
all types.

Full range of rebuilt mono
tubes available, Standard,
Rimband and Twin Panel

- ★ Complete new gun fitted to
every tube.
- ★ 2 years' guarantee mono-
chrome, 1 year colour.
- ★ 16 years' experience in tube
rebuilding.
- ★ Trade enquiries welcomed.

**N.G.T. ELECTRONICS LTD.
(Nu Gun Teletubes)**

22-24, Anerley Station Road,
London S.E.20.

Telephone: 01-778 9178.

**Still waiting for spares Tom?
You should have phoned**



WHEREVER YOU ARE FOR BY
RETURN DESPATCH. WILLOW
VALE IS AS NEAR AS YOUR
PHONE.....

WILLOW VALE

The Wholesaler who knows what SERVICE is really about!



BY RETURN DESPATCH:- HOT LINES: 01-567 5400/2971

L.O.P.T's, TRANSISTORS, RECTIFIER TRAYS, COMPONENTS
MONOCHROME and COLOUR C.R.T's, new and re-built.
HUGE RANGE OF VALVES up to 46% DISCOUNT

A FULL RANGE OF TEST - METERS, SERVICE AIDS, TOOLS, ELECTROLUBE
and Servisol products. Multicore solders, plugs and sockets, capacitors, bias and
smoothing electrolytics, volume controls, pre-sets, $\frac{1}{2}$, 1 and 2 watt carbon film res.



We SPECIALISE in supplying the Service Engineer

Test equipment by : Labgear, Philips,
Meteronic etc. Colour bar & Pattern
generators, oscilloscopes & meters



68 PAGE CATALOGUE
FREE ON REQUEST

**Hot line
orders:- willow vale**

The Service Department Wholesalers

LONDON: 4/5 The Broadway · Hanwell · London W7 · 01-567 5400

GLASGOW: 74 Maxwellton Road · Paisley · 041-887 4949

SOMERSET: 42 West End · Street · Somerset · 045-84 2597



I would like a free copy of your catalogue:

Name

Address

TELEVISION

VOL 23 No 12
ISSUE 276

SERVICING · CONSTRUCTION · COLOUR · DEVELOPMENTS OCTOBER 1973

COLOUR FAULT FINDING

Now that colour television is a firmly established part of the British domestic scene, and the rental firms have trained their engineers to deal with the servicing problems, it is possible to stand back and take a look at the future from the service engineers' point of view.

The main point that strikes one is the question of servicing methods. It seems that the modern idea of a replacement printed board type of service operated by field "panel jockeys", backed by a second-line repair service at the works, is likely to fade out in favour of conventional on-site repairwork. There are several reasons for such a change, including the effect of VAT and the large investment that would be required to finance stocks of replacement modules for an ever increasing number of different chassis. It also seems that panel replacement can often involve additional setting-up work in order to get the replacement to operate satisfactorily with the rest of the receiver.

Followers of the TELEVISION Colour Receiver project will appreciate this latter point. Component tolerances, especially in semiconductors, can lead to the situation where the performance of one receiver differs notably from that of another of the same type. The problem is more acute with home-built receivers since the quality control and standardisation in manufacturing techniques found in a factory are not of course possible with "one-off" construction. It has also to be remembered that even highly automated assembly lines produce their share of "rogue sets".

It is only to be expected therefore that problems requiring some experience and knowledge to enable them to be sorted out can arise in constructors' sets. In this issue test figures and key waveforms for the Colour Receiver are given to help in this respect, while last month a detailed fault-finding guide to the i.f. strip was published (though you are advised to leave well alone if you have had your strip aligned by the Alignment Service). It is possible that minor amendments to individual sets will be needed to bring them into line, while the effects of different reception conditions have also of course to be taken into account.

Our centre pages this month feature a special colour television fault-finding chart which will be useful in tackling a wide variety of receivers, both commercial and home-built. This is the first time that a television magazine has provided such a service and we feel sure that readers will find the chart particularly useful to hang on their workshop wall.

M. A. COLWELL—*Editor*

THIS MONTH

Teletopics	534
110° Colour—The New RRI Chassis <i>by T. John</i>	536
Varicap Tuning System <i>by Roger Bunney</i>	540
Coping with ICs—Part 2 <i>by Harold Peters</i>	543
Fault Finding Guide—7: Timebases, Philips 19TG158A Series <i>by John Law</i>	546
Long-Distance Television <i>by Roger Bunney</i>	550
Special Supplement—Basic Colour Faults Guide	
Servicing Television Receivers— ITT/KB VC200 Chassis <i>by L. Lawry-Johns</i>	553
Thick-Film Circuits for TV <i>by Keith Pitt, B.Sc.</i>	556
The TELEVISION Colour Receiver—Part 18— Service Data	558
Television Goes to Berlin	562
Receiver Debugging—Part 3— IF and Video Responses <i>by E. J. Hoare</i>	564
Your Problems Solved	569
Test Case 130	571

THE NEXT ISSUE DATED NOVEMBER
WILL BE PUBLISHED OCTOBER 22

Hold-over: We regret that due to shortage of space in this issue we have had to hold the next instalment of "Renovating the Rentals", covering the decoder circuits in the Philips G6 colour chassis, until the next issue.

TELETOPICS



VCR AND MINI-STUDIO FROM PYE

Pye have announced two interesting new Philips products, the video cassette recorder type N1520 which can be used with a camera, and a group of items under the name "Mini-Studio" which provide a complete ready-to-use CCTV system for educational, industrial and amateur entertainment purposes.

The cassette recorder is fully compatible with all Philips video recorders and is in line with other continental brands. Attempts are being made to secure a common standard for operation and compatibility among most major continental countries under the I.E.C. classification, and to extend this to include Japanese equipment. We understand that the DIN European VCR standard is now established, with half-inch tape used.

The trend seems to be to omit u.h.f. or v.h.f. tuning circuits and provide facilities to record direct from the video signal stage. This enables the recorder to be connected to one common socket on television receivers or camera equipment, for use in studios as well as in the home.

The N1520 is classified as a "professional" recorder mainly for studio work and costs £750. It will take a European Standard video cassette that carries the VCR logo. This particular model does have an r.f. modulator so that recordings can also be played via a domestic receiver's aerial socket. Two-track dubbing and editing is provided so that it can be usefully employed in preparing educational or

industrial training programmes in conjunction with the "Mini-Studio" equipment. It is designed to CCIR standards and the colour processing is to the PAL system.


The video socket takes a nominal 1V peak-to-peak input at 75 Ω and chroma signals of 300mV peak-to-peak. The output is at the same level, but the chroma is at 270mV. Full details and technical specification can be obtained from Philips.

The "Mini-Studio" equipment shown in the accompanying photograph can be set up for use in 30 minutes by teenage children or adults, providing an inexpensive CCTV system for less than £1,500 (basic price excluding tax). It can be used with a videotape recorder—which costs from £150 extra—or for "live" performances. The equipment includes two cameras—one with electronic viewfinder—and various lenses (including zoom and standard microscopy), tripods, headsets, telecine, mounting rack with three 10cm monitors and a control unit (see below), microphone and audio mixer. The system can be used for example with a bench microscope, with class demonstrations carried out using large screen monitors.

The system conforms to CCIR waveforms. The control unit enables simple effects to be carried out: faders are provided so that when switching from one camera to another the picture from the first gradually dissolves into the picture from the second, while both horizontal and vertical wipes can be achieved and by combining them the picture from one camera can be made to appear as a corner insert. The audio mixer will cater for five channels, three for microphones. The vision mixer is three channel with mixing of two pictures, the third showing the output picture. The equipment is being handled by the Business Communications division of Pye.

FUTURE UK TV SERVICES

The Television Advisory Committee to the Minister of Posts and Telecommunications has now published the technical reports on which its recent recommendations were based. The committee recommends 1980 as the target date for the closure of the v.h.f. 405-line service. The v.h.f. bands could then be replanned, amongst the possibilities being a "maximum coverage" TV service consisting of either two programmes reaching 85 per cent of the population or a single programme using six channels to reach 99 per cent of the population, a "local" service to provide a large number of small population groups with their own TV programmes, extension of f.m. broadcasting or the mobile radio allocation or a combination of these various options.

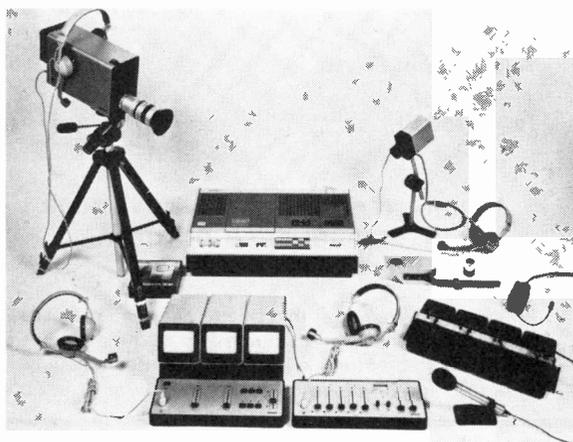

The complete Mini-Studio, together with (centre rear) a Philips N1520 video cassette recorder.

On the subject of satellite TV transmissions in Band VI (11.7-12.5GHz) the committee says that four or five national programme channels would be a feasible proposition in the early 1980s. Individual aerial/converter assemblies for such a service would probably be more expensive than setting up communal reception/distribution systems.

NEW VCR RANGE

The American owned International Video Corporation is introducing in the UK its VCR100 series one-inch videotape cartridge recorders which are aimed at the professional studio market. The VCR101C offers recording and playback in monochrome and colour (PAL or SECAM colour systems) while the VCR111C is a playback only version. The cartridge contains a single 8in. NAB reel of tape, making the machines compatible with IVC reel-to-reel recorders. The tape is automatically threaded and anchored to the take-up reel in the machine.

There are two audio channels, with the option of a.g.c. One channel can be recorded after the rest of the tape has been recorded. Cartridges are available with 1, $\frac{1}{2}$ or $\frac{1}{4}$ -hour tape playing times and cost £25 each. At the end of rewinding the cartridge is automatically ejected clear of the mechanical drive. One particularly interesting feature is the ability to delay the display of the recorded picture so that picture disturbance due to sync searching after switch-on does not appear on the screen. These machines are not compatible with European VCR types. An editing version will be made available at a later date.

SOLID-STATE SENSOR

Fairchild have introduced in the US a 500-element charge-coupled device for imaging—we take this to mean that it is a solid-state sensor giving a video output signal. Applications include slow-scan TV, document reading and optical character recognition. This is understood to be the first charge-coupled device to be brought to the market—the one-off price is quoted as \$1200.

TRANSMITTER OPENINGS

The following relay stations are now in operation: **Luton:** BBC-1 channel 55, BBC-2 channel 62. Receiving aerial group C.

Hastings: BBC-1 channel 22, BBC-2 channel 25. Receiving aerial group A.

Weymouth: BBC-1 channel 40, BBC-2 channel 46. Receiving aerial group B.

The transmissions from these stations are vertically polarised.

AERIAL NOTES

We have received from R. Smith Aerials (98 Ash Road, Luton, LU2 9AX) a copy of the catalogue of their extraordinarily comprehensive range of TV and FM aerials and fittings. There are numerous wideband and fringe u.h.f. designs, the Zodiac range for example featuring a full-wave dipole, quadruple directors mounted on twin beams and an angled reflector. Wideband u.h.f. aerial kits are available for use with touring caravans, UK maps and charts being supplied with each kit. The catalogue contains helpful advice on aerial selection and use, including



The new IVC VCR100 series of video recorders combines the user convenience of cartridge loading—insert a cartridge, close the lid and press a button—with the quality obtained by using a 1in. tape format as in conventional IVC studio-type recorders. Marketed in England and Wales by Bell & Howell A-V Ltd.

guidance on obtaining reception from two or more u.h.f. transmitters.

A new TV aerial system consisting of a 92-element lightweight beam, remote tuned masthead aerial amplifier plus optional aerial rotator unit is being introduced by Uni-Com Electronics Ltd. (36 Clarges Street, London, W1) for use in fringe areas or for receiving extra channels. Field tests have been carried out by Alpine Aerials who will be undertaking installations in London and the Home Counties.

LARGER TRINITRON

Sony have announced in Tokyo the successful development of a 27in. version of their Trinitron colour tube. The new version has a 114° deflection angle. Sony are at present selling Trinitron colour sets in the US in three sizes ranging from 5in. to 17in.

TRADE NOTES

The latest trade figures available, for May this year, show that at a time when there is said to be a build up of stocks of TV sets in the distribution pipeline imports continued to rise. Of 252,000 colour sets delivered to the trade in May (more than twice the number of monochrome sets delivered) some 29% (72,000) were imported. Taking the first five months of the year imports accounted for almost 25% of colour set deliveries in the UK. UK setmakers have now approached the Japanese television industry through BREMA requesting a cut in imports to half the current level. It seems however that recent currency realignments have already made the UK industry more competitive, while it is understood that output has now increased to a level sufficient to meet current demand. Thorn are continuing with their expansion programme, having recently acquired a new plant in Hull where subassemblies for their colour receiver plant at Bradford will be made.

ELECTROKIT'S NEW ADDRESS

Electrokit have moved to new premises at 8 Cullen Way, London, NW10.

110° COLOUR

THE NEW RRI CHASSIS

T. JOHN

We were pleased to accept an invitation recently to attend one of the series of servicing seminars being held by Rank Radio International to introduce to the trade and servicing organisations the new Bush/Murphy 110° colour chassis. It is a welcome thing indeed to see the trouble to which RRI are going to familiarise the trade with the technical details and servicing aspects of this new chassis in good time.

The chassis itself is a masterpiece in respect of making everything easy to get at. The whole thing can be dismantled into its component parts within a matter of minutes through a simple process of unscrewing, unclipping and unplugging. The aim has not been to divide the chassis into large numbers of separate, detachable panels but instead to group circuits logically and make them accessible for repair with the absolute minimum of fuss.

The first thing that struck us on examining the set was the absence of a degaussing shield, the degaussing coils resting against the rear of the tube bowl. Perhaps this had been left off in the interests of making everything readily visible for demonstration purposes? Not so however: the degaussing shield in the c.r.t. (Mullard) being used is actually built into the tube.

The tube of course is the key factor in the new chassis. RRI have decided to use the thick-neck rather than the thin-neck type of 110° tube, with Mullard Phase II circuitry. The following reasons were given for deciding upon the thick-neck tube: better purity which is more easily obtained; higher light output which is more even over the screen area; less subject to magnetic effects; requires less scan power than a thin-neck tube. To clarify this latter point, the line scan power required by both types of tube is much the same: the field scan power required with a thick-neck tube however is less than that required with a thin-neck tube using a toroidal deflection yoke.

RRI emphasise that no completely new techniques have been adopted and indeed much of the new chassis will be familiar to those acquainted with previous RBM chassis. Nevertheless modifications have been introduced and general updating undertaken while there are of course new field and line output stages, convergence and pincushion distortion correction circuits.

A varicap tuner operated by a touch-sensitive tuning unit (of the type described in our April issue—pages 250-251—this year) is used. The i.f. panel is very similar to that used in the RRI A816 mono-

chrome chassis (Bush TV309 series), with three i.c.s. The signal passes first to a BF240 transistor which acts as i.f. preamplifier then via the response shaping circuits to the i.f. amplifier i.c. (type SC9504P) which incorporates a line-gated sync-tip a.g.c. circuit and also provides an a.g.c. output for the tuner unit. This is followed by a further i.c. (type SC9503P) which acts as a low-level synchronous detector and video preamplifier. The 6MHz sound signal also derived from this i.c. is applied to the third i.c. (type TBA750) which provides intercarrier sound amplification, limiting, detection and audio preamplification.

The audio output stage consists of a single BD181 transistor in a class A circuit, giving an output of 2W. The quality of the audio obtained from this stage is excellent and an external loudspeaker socket is provided. This is arranged so that the plug can be inserted either to operate the extension speaker only or both the external and internal speakers. The audio output transistor is protected against flashovers by connecting a v.d.r. (type E299DD/P336) between its collector and chassis.

The a.f.c. circuit along with the luminance, decoder and RGB output stages are all mounted on the main signal panel. The decoder follows previous RBM practice with most of the signal processing and detection carried out by two i.c.s (which are now unpluggable) and a passive subcarrier regenerator employed. A modification here however is the inclusion of a circuit to prevent a spurious subcarrier developed by noisy low-level signals on monochrome reaching the chrominance synchronous demodulators in the second i.c.

A new contrast control circuit, now linked to the colour control so that the two track together from the signal point of view, is used in the luminance channel. This is shown in Fig. 1. The arrangement is based on the four diodes 3D6-3D9. 3D7 and 3D6 form a shunt path for the signal to chassis via 3C24 while 3D8 and 3D9 form a series path to the base of 3VT4. Adjustment of the contrast control varies the diode biasing and thus the impedances of the two paths. As the contrast control is moved to provide a more positive potential 3D8 and 3D9 con-

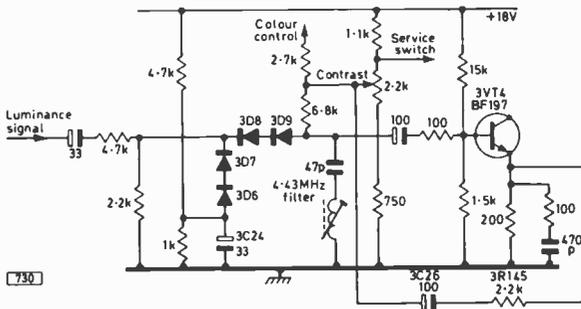


Fig. 1: Contrast control circuit. 3C26 and 3R145 form an anti-bounce network to prevent picture disturbance with rapid operation of the contrast control.

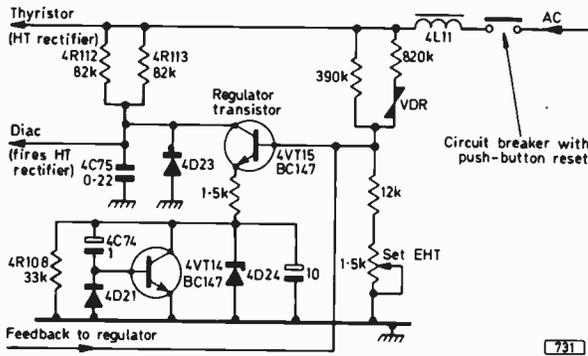


Fig. 2: Slow-start system in the power supply circuit.

duct more while 3D7 and 3D6 conduct less and vice versa.

The stabilised power supply circuit uses a thyristor and is basically the same as the circuit previously employed. Some detailed improvements have been added however including the use of a substantial choke in series with the thyristor to limit the peak repetitive current and a "slow-start" circuit to limit the initial switch-on current surge. The latter arrangement is shown in Fig. 2. 4C75 charges via 4R112 and 4R113 until the breakover voltage of the diac which fires the thyristor is reached, the charging of 4C75 being controlled by the action of the regulating transistor 4VT15. 4VT14 which provides the slow-start action is connected across the zener diode 4D24. When 4VT14 is conducting (at switch on) 4D24 is shorted and 4VT15 conducts heavily, delaying the charging of 4C75 and thus the triggering of the diac and thyristor. 4C74 is completely discharged on switching on so that a heavy current


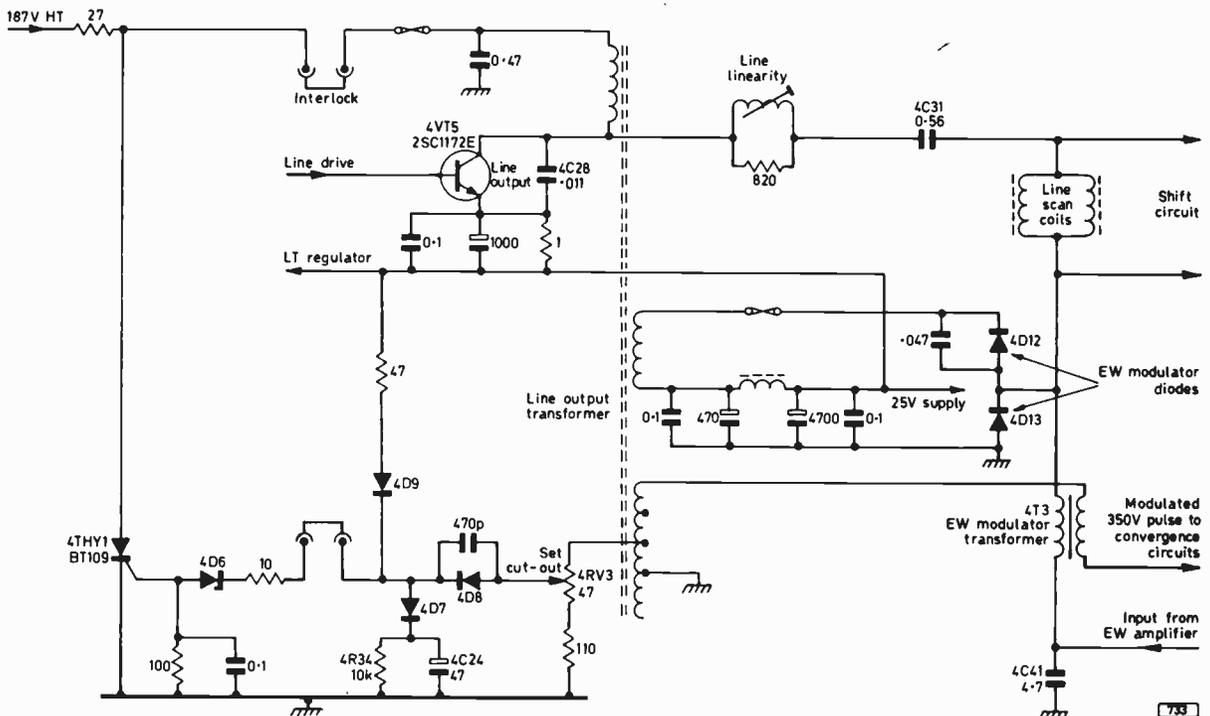


Fig. 4: Simplified circuit of the line output stage, showing the EW pincushion correction arrangements and the overvoltage protection system. The EW modulator diodes also provide the 25V supply.

Fig. 3: Line oscillator (TBA920) starter circuit: the supply to the TBA920 is from the h.t. line via 4VT2 until the line output stage comes into operation and the l.t. supply appears.

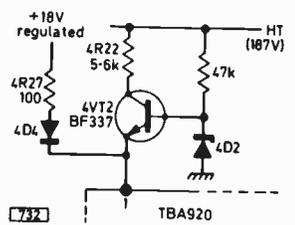

flows into it via 4VT14 base. As 4C74 charges so 4VT14 cuts off and the circuit then reverts to normal operation. On switching off 4C74 discharges via 4R108.

Another power supply modification is a circuit breaker with push-button reset. This removes the power to the receiver when the e.h.t. exceeds 28.5kV. More about this later.

A TBA920 i.c. is used as sync separator and line generator, with an external noise-canceller transistor in the input circuit of the sync separator section. The l.t. supplies are all derived from the line output stage in this chassis so the problem arises of how to start the line generator in the i.c. before the line output stage comes into operation. This is done by the line oscillator starter shown in Fig. 3. On switch on 4VT2 conducts heavily, providing the supply to the i.c. (pin 1) via 4R22 from the main h.t. line. Once the line output stage comes into operation the supply to the i.c. is via 4R27 and 4D4, the positive voltage at 4VT2 emitter then cutting it off. Zener diode 4D2 ensures that the reverse base/emitter voltage of 4VT2 is not exceeded.

The line output stage is shown in simplified form in Fig. 4. A single line output transistor (type 2SC1172E) is used, with the scan coils driven from

its collector (via the linearity control and S-correction capacitor). The line output transformer is used primarily to tune the flyback pulse. Overvoltage protection is provided by the circuit consisting of 4RV3, 4D8, 4D6, the thyristor 4THY1 and associated components, switching off the receiver in the event of the line output transistor collector voltage rising by more than 25%. The set cut-out voltage control (4RV3) is adjusted to ensure that 4THY1 fires if the e.h.t. rises 25%. During normal operation the voltage produced by the protection rectifier 4D8 is lower than the zener voltage of 4D6, thus holding off the voltage from 4THY1 gate. Should the voltage produced by 4D8 exceed 4D6 zener voltage however 4THY1 fires and the contact breaker in the power supply (Fig. 2) opens interrupting the supply to the receiver. In addition 4D9 operates the protection circuit in the event of an excess voltage appearing on the l.t. supply. 4D7, 4R34 and 4C24 provide a transient overvoltage limiter to prevent the circuit breaker coming into operation in the event of a c.r.t. flashover.

The only thing the field timebase has in common with that used in the 90° RBM single-standard chassis is the use of a silicon-controlled switch as the field oscillator. In this new circuit the s.c.s. directly controls the discharge of the capacitor which generates the field scan waveform. The waveform produced by this capacitor is first amplified by a transistor stage whose gain, and hence the height, is controlled by variable emitter negative feedback. This is followed by a three-stage direct-coupled class A amplifier using a BD183 output transistor, with choke coupling to the scan coils.

Pincushion & Convergence Circuits

This brings us to the circuit features specifically new to 110° operation, the new pincushion distortion correction and convergence arrangements. It seems that a lot of development work has gone into these over the last couple of years as a result of which they are not nearly as complex as we had at one time been led to expect. In fact RRI say that convergence is easier to adjust than in their 90° chassis, with less interaction between the controls.

Getting a good linear display is important with a colour set and we were particularly impressed with the crosshatch pattern the receivers on show displayed. Separate North/South (top and bottom) and East/West (picture sides) pincushion correction is employed. Fig. 5 is included to help clarify what is involved here. To overcome pincushion distortion at the top and bottom of the display the field deflection current must be increased at the centre of each line in the upper and lower portions of the raster. This is done by superimposing small line-frequency currents on the field deflection current. A transducer is used for this purpose and operates on the same lines as the transducer used in 90° chassis for pincushion distortion correction. In addition a second harmonic component is added to straighten the lines at the top.

To correct pincushion distortion at the sides the line scan amplitude must be reduced at the start and finish of each field scan period. To achieve this the line amplitude has to be varied parabolically at the field rate. This is done by injecting a field-rate parabolic waveform in series with the line scan coils. A

variable (by means of the E/W amplitude and keystone controls) combination of field-frequency parabolic and sawtooth waveforms is applied via a three-stage E/W correction waveform amplifier to the primary of the E/W modulator transformer 4T3 which is in series (see Fig. 4) with the line scan coils. The width control sets the bias applied to the E/W amplifier; in this way the line scan amplitude is varied linearly across the field scan.

The convergence circuits (Fig. 6) merit full description, being the first for use with 110° tubes that we have seen used by a UK setmaker. First, horizontal (line) convergence. Both the red/green and blue horizontal convergence circuits are shunt fed from the line output transformer, the convergence correction voltage waveform being modulated by the field scan (by 4T3) to give increased deflection sensitivity at the corners of the display. The operation of these circuits is based on double integration. The field-modulated line flyback waveform is first integrated by the primary windings of the red/green (5T1) and blue (5T2) amplitude transformers. Thus a substantially sawtooth waveform flows in these transformers. The second integration is performed by the horizontal convergence coils 7L9, 7L10 and 7L11 themselves. Resistors 5R2 and 5R3 provide tilt in the red/green circuit while 5R6 and 5RV3 provide tilt in the blue circuit. Diodes 5D1 and 5D2 across the red and green coils provide clamping so that static convergence is not disturbed when dynamic convergence adjustments are being made. Clamping is not required in the blue circuit: 5D3 across the blue tilt control provides waveform shaping, not clamping. The red/green differential amplitude coil 5L3 with 5R4, 5C3, 5RV1 and 5C6 form a damped resonant circuit to help shape the waveform. The coarse tilt facility is incorporated as part of each amplitude transformer to enable additional pulse voltage to be added if necessary at the bottom end of the convergence coils, giving coarse adjustment to the resistive tilt controls.

The blue lateral coils 7L7 and 7L8 require sawtooth and parabolic currents of either polarity. These are obtained from $\pm 60V$ pulses derived from the line output transformer. These pulses are applied to 5L1 and 5L2. 5L1 integrates the pulses and feeds sawtooth current to the blue lateral coils, the polarity of the current being determined by the setting of the core. Adjustment of 5L1 also alters the amplitude of the current. 5L2 in conjunction with 5C1 and 5R1 supply parabolic current to the blue lateral coils, adjusting 5L2 core altering the polarity and amplitude of the current.

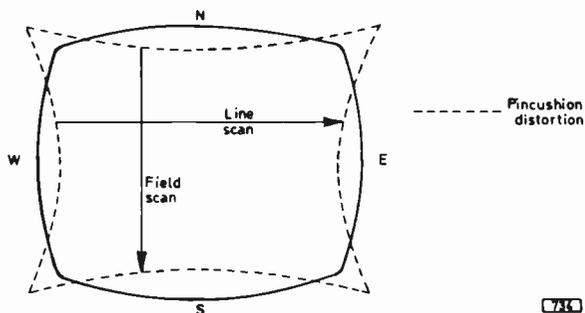


Fig. 5: Illustrating the pincushion distortion correction required.

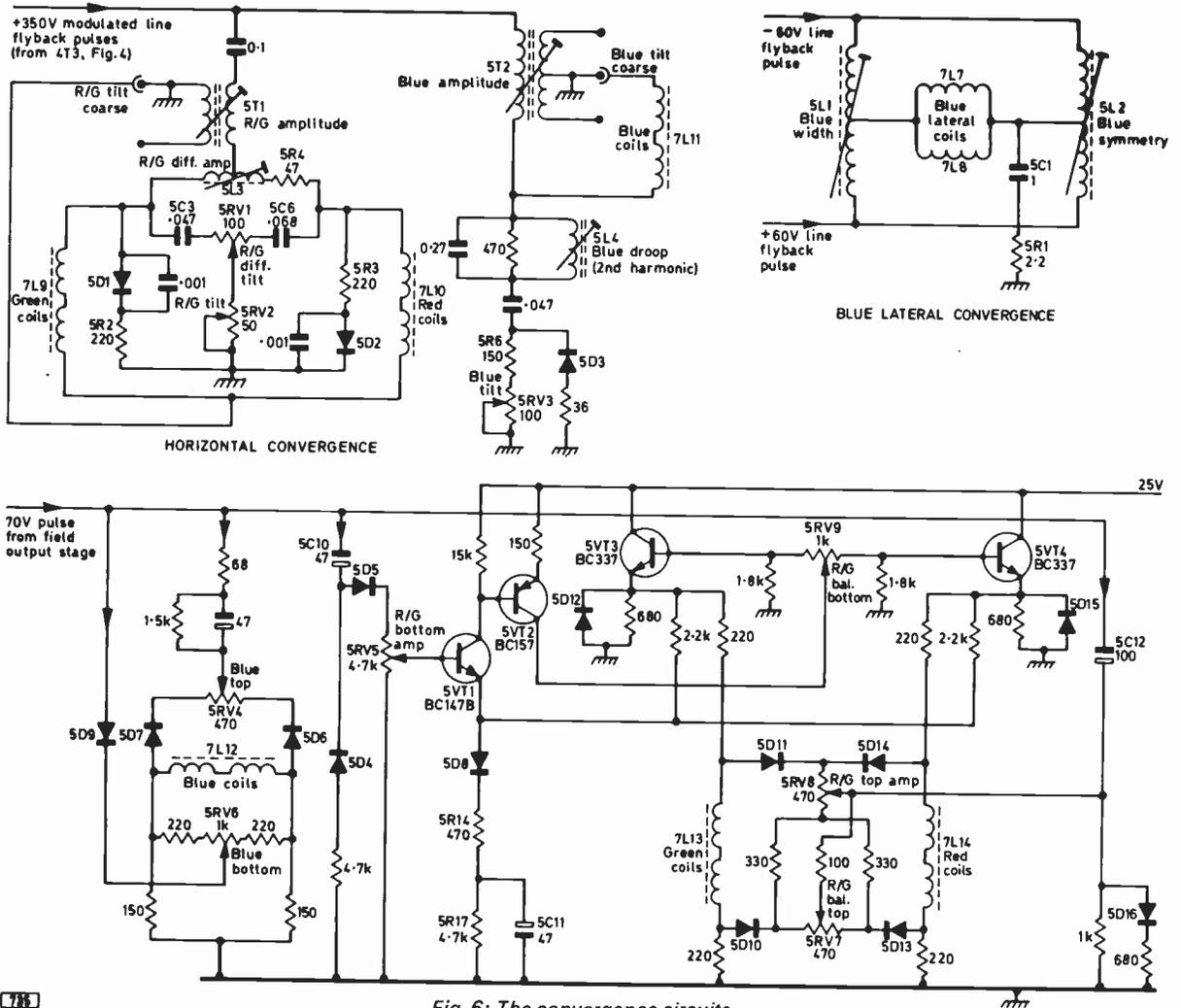


Fig. 6: The convergence circuits.

For red/green vertical (field) convergence a voltage derived from the field output transformer is applied to the red/green vertical convergence circuit in two ways. For the first half of the scan it is fed via 5C12 direct to the matrixing network (5RV8, etc.). During the second half of the scan it is fed via 5C10 to the clipper diodes 5D4, 5D5 and then to the base of 5VT1. The components in the emitter circuit of this stage provide shaping. 5VT2 inverts the resultant waveform and drives the symmetrical pair of emitter-followers 5VT3 and 5VT4. Diodes 5D12 and 5D15 bypass the field flyback pulses to chassis. The setting of the R/G bottom balance control 5RV9 in the base circuit of the emitter-followers interacts with the R/G top controls in their emitter circuits, though the opposite does not occur: for this reason vertical convergence at the bottom of the display is adjusted first followed by adjustment to the top part of the display.

The blue vertical convergence coils may require current of either polarity. This is provided by applying drive to each end of the coils (7L12). Again the bottom control affects convergence at the top so that

the bottom is adjusted first followed by correction at the top of the display.

A service switch is provided to assist when making grey-scale and purity adjustments. In the down position a blank raster is obtained to enable purity adjustments to be carried out. In the up position a collapsed raster (horizontal line) is produced which can then be resolved into its R, G and B components to enable the tube first anode controls to be accurately adjusted.

This is the first UK produced 110° colour chassis for which detailed information has been released. The initial production models we examined gave good performance and the chassis is likely to be with us for some years. It will be interesting to compare this chassis with the TCE (BRC) 4000 and the Philips, Pye 110° chassis—due for release shortly—when details of these other new chassis become available. One thing the RRI chassis does prove: the vast complexities that had been forecast with 110° operation have been overcome, undoubtedly as a result of the development work that has been steadily going on during the last couple of years.

VARICAP TUNING SYSTEM

ROGER BUNNY

As regular readers will know the author has been active in the field of long-distance television reception for some years. Earlier this year I spent some time reviewing receiving equipment with a view to completely changing the system I was using. Quite by chance supplies of v.h.f. and u.h.f. varicap tuners became readily available so I decided to adopt these for the new receiving system. The initial prototype tried out gave most encouraging results and following this a design was evolved on the basis of which a further six units were made—four for v.h.f. and two for u.h.f.

These units have now been in operation for some time and have proved most reliable. There have been no problems save for that of accurately locating channel settings. Several new receivers have also been brought into use, adapted for being fed from the varicap units. Details of the modifications made to these receivers for long-distance reception will be given in a separate article in a later issue.

The v.h.f. and u.h.f. tuners used were obtained from Manor Supplies. The u.h.f. one is the Mullard ELC1043 for which a data sheet can be obtained from Mullard Ltd. A 12V supply, a tuning voltage variable over the range 0.3-28V and a variable positive voltage for gain control (a.g.c.) are all that is needed to operate the unit. Connections are shown in Fig. 1.

The v.h.f. tuner is a Philips unit and the only information I was able to obtain on it was that available from Manor Supplies. The supply circuit for it was designed on the assumption that its requirements were very similar to those of the Mullard type ELC1042. The connections are shown in Fig. 2—note that these are not quite the same as for the ELC1042. The only additional requirement for the v.h.f. unit is a 12V feed to provide Band I/III switching.

Further information on varicap tuners and their use is given in the following issues of TELEVISION: November 1971, October 1972, May 1973.

Circuit Details

The circuit (see Fig. 3) adopted to provide the power supplies is quite simple. An inexpensive Eagle mains transformer was available with two second-

aries which when connected in phase provide an 0-48V winding. This is eminently suitable for giving the 30V required for the tuning line. A bridge rectifier (D1-D4) is used with the output taken via R1 to a split feeding the tuning voltage section and the 12V supply section. The latter is self-explanatory apart possibly for SW2 and R13: these are fitted on the v.h.f. units and serve to stabilise the current through the zener diode D5 on Band I, the current flow to chassis via R13 preventing the current through the zener rising alarmingly (the 12V Band switching supply at approximately 12mA is required on Band III only).

The maximum output obtained from the tuning voltage side of the circuit is 30V. The feed here is via the emitter-follower Tr1 (BFX85) with its associated components. The zener diode D6 holds Tr1 base at a constant voltage, the 6.8k Ω resistor R5 setting the zener current flow to chassis—in this case approximately 4mA. The use of this emitter-follower rather than a straight zener diode reduces the a.c. ripple to an absolute minimum and allows dissipation to occur in the regulator itself rather than in the zener diode—this in turn gives better overall voltage stability with variations in temperature. The value of C6 could in practice be reduced to 1,000 μ F if space in the box used to house the unit is limited.

Tuning

Tuning is carried out by means of the two carbon potentiometers VR2 and VR3. Since the graph of frequency change/tuning voltage (see Fig. 5) is not linear the use of a logarithmic potentiometer for coarse tuning is suggested in the interests of obtaining a more linear scale across the face of the meter when tuning. On the six units I constructed originally however linear potentiometers were used and al-

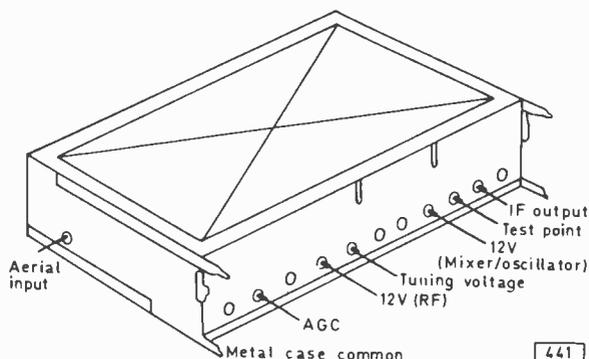


Fig. 1: ELC1043 u.h.f. tuner pin connections.

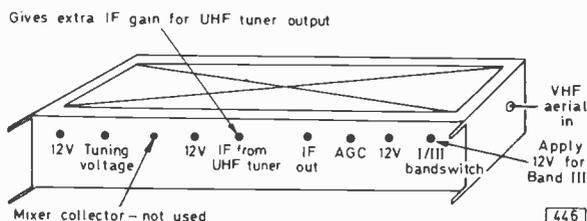


Fig. 2: Pin connections of the Philips v.h.f. varicap tuner available from Manor Supplies.

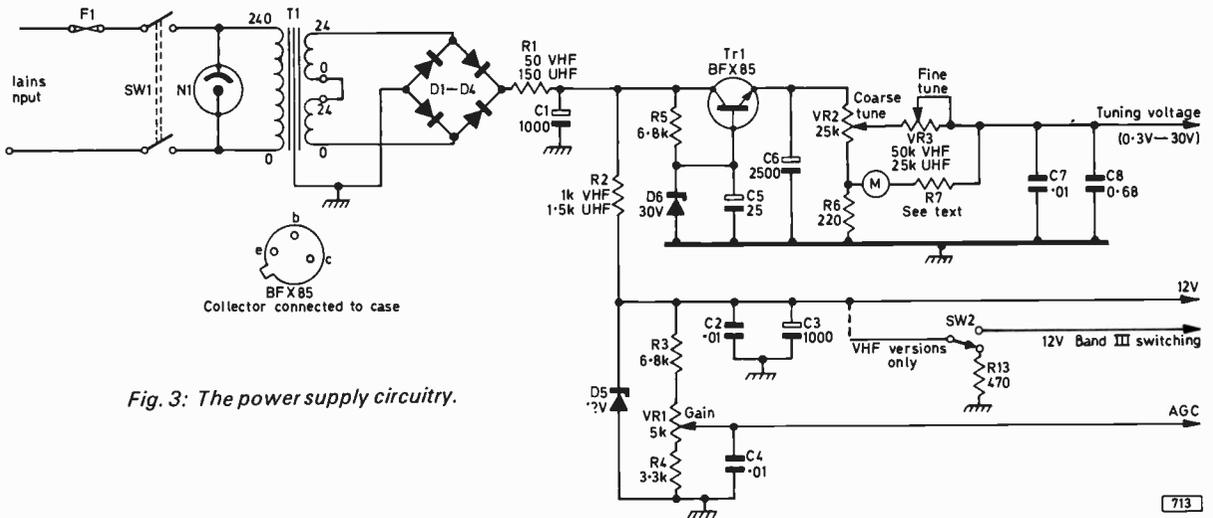


Fig. 3: The power supply circuitry.

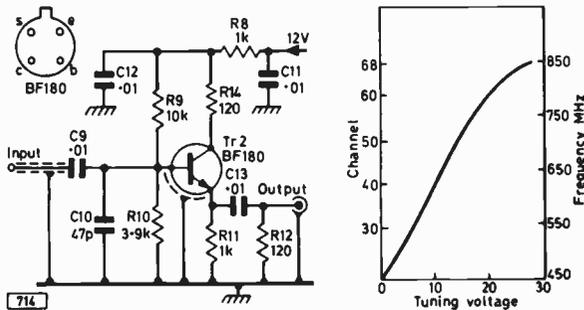


Fig. 4 (left): Emitter-follower used at the output.

Fig. 5 (right): Tuning voltage plotted against channel setting with a vision i.f. of 39.5 MHz—Mullard ELC1043 u.h.f. varicap tuner.

though scale cramping is evident with these the large meters employed allow great accuracy in tuning adjustments and ease in locating channels. This meter

is an attractive 50μA movement of some 4in. width and fits extremely well into the Eddystone diecast box used.

Resistor R7 in series with the meter consists in fact of several resistors, the exact value being selected so as to give full scale deflection with a tuning voltage of 30V. In practice different values were used for each unit constructed. As a basis however fit a 470kΩ resistor as standard and then insert extra resistors as necessary to get the correct operating point. F.S.D. should be found with 470kΩ plus another series value between 82kΩ and 130kΩ. In all cases no more than three resistors were needed. A small adjustable (skeleton preset) resistor could of course be used to set the exact value but in the interests of long term stability and freedom from any slight tendency for the preset to move the use of separate fixed resistors is recommended.

The 0.68μF capacitor C8 fitted actually at the input connection on the tuner itself is essential since hum may be noticed without it. In addition a small 0.01μF ceramic capacitor is fitted across each of the input supply connections on the tuner body for absolute stability.


R1 150 Ω * 5W W.W.	R5 6.8k Ω 2W	R9 10k Ω ½W	R12 120 Ω ½W
R2 1.5k Ω * 5W W.W.	R6 220 Ω ½W	R10 3.9k Ω ½W	R13 470 Ω 5W W.W.
R3 6.8k Ω ½W	R7 See text	R11 1k Ω ½W	R14 120 Ω ½W
R4 3.3k Ω ½W	R8 1k Ω ½W	*R1 50 Ω, R2 1k Ω, VR3 50k Ω for v.h.f. tuner.	

C1 1000μF 70V	C5 25μF 50V	C8 0.68μF 150V	C11 0.01μF 150V
C2 0.01μF 150V	C6 2500μF 50V	C9 0.01μF 150V	C12 0.01μF 150V
C3 1000μF 25V	C7 0.01μF 150V	C10 47pF 150V	C13 0.01μF 150V
C4 0.01μF 150V			

All small-value capacitors ceramic.

VR1 5k Ω lin.	D1-D4 100V p.i.v., 1A	Tr1 BFX85
VR2 25k Ω log.	D5 12V 1.5W zener	Tr2 BF180
VR3 25k Ω * lin.	D6 30V 1.5W zener	
F1 Miniature fuseholder (RS)	M 50μA f.s.d. 4" meter (Adastra T41)	SW1 DPST toggle (RS)
	N1 Mains neon (RS)	SW2 Miniature SPDT toggle (RS)
		T1 0-240V pri.; 2×0-24V sec. (Eagle MT100)

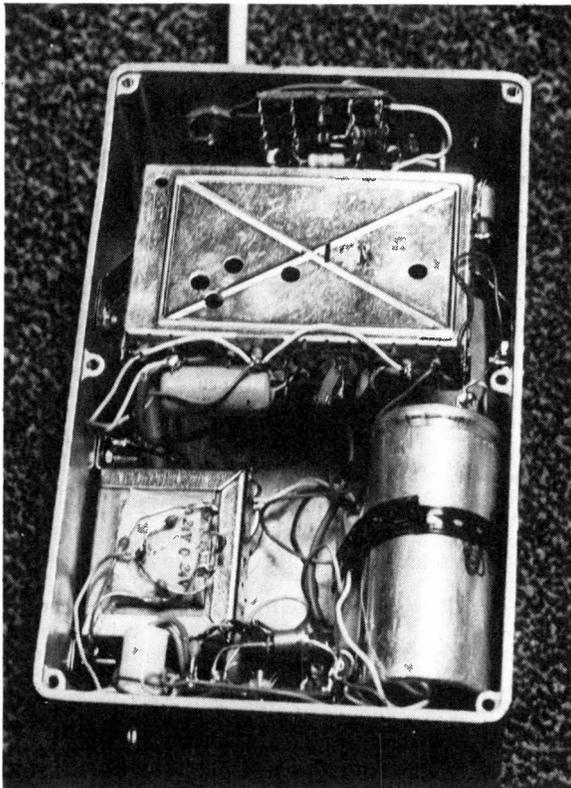Eddystone diecast box (6357P, 7½"×4½"×3"); 18-way miniature tagstrip; two coaxial sockets (Belling-Lee); 1 miniature mains input plug and socket (RS); knobs, etc.



Internal view showing constructional details.

To avoid detuning the i.f. output feed if varying lengths of coaxial feeder are used a simple emitter-follower stage (Fig. 4) using a BF180 is included between the varicap tuner i.f. output and the actual i.f. output socket of the tuning unit. This allows the varicap tuner i.f. output to be peaked exactly.

The values of R1 and R2 vary depending on whether the unit is for u.h.f. or v.h.f. use. The differences are because of the extra current required by the Band switching diodes in the v.h.f. version.

Construction

No problems should arise with the physical construction of such units, apart possibly from being able to incorporate the large smoothing electrolytics. In the units I constructed C1, C3 and C6 were strapped together using polythene cable strapping and then bolted against the wall of the box by passing a 6BA bolt through one of the holes in the strapping. The various components associated with the power supplies were mounted on half an 18-way miniature tagstrip which is mounted in turn on the inside of the front cover of the box. The other half of the tagstrip was used for the emitter-follower stage and the meter f.s.d. setting resistors. This tagstrip section is mounted on the inside of the rear wall of the box.

Commence construction by fitting the potentiometers and then working outwards. Fit the meter second to last and finally mount the tuner over this prior to wiring it into circuit. When working with the meter fitted it is advisable to tape some form of protective material over the meter face to avoid

scratches etc. Prewire the tagstrips, with all components fitted, before mounting them in the box—the flying leads required for connecting to the main components should also be pre-fitted.

As brackets or other mechanical adornments are not supplied with the tuners a method of mounting them in the diecast box must be devised. The easiest solution is to cut two strips of tin, drilled to take a 4BA bolt at one end, the other end being soldered to the body of the tuner. This operation should be done carefully since an iron of at least 60W is needed to effect good jointing. Once soldered the strips (solder a similar strip on the other side of the tuner) can be adjusted to contact the walls of the box and an appropriate hole drilled in the box side. It is a wise move to solder a 4BA nut on to the tin strip to obviate problems later when mounting the tuner in the unit—one less hand then being required to bolt the tuner in place. Alternative layouts and mounting arrangements will undoubtedly suggest themselves to the constructor but these notes and the accompanying photograph show how the author tackled the problem.

For aerial isolation purposes a 470pF 750V working capacitor should be inserted in series at the point where the aerial input enters the wall of the unit.

Operation

Provided care has been taken over construction the unit should work immediately it is switched on! In my case one didn't, the BFX85 immediately blowing its base open-circuit. The fault was traced to a bead of solder beneath the slider connection of the main tuning potentiometer contacting to chassis (this couldn't be observed visually).

The value of 50k Ω for the fine tuning potentiometer is suitable for v.h.f. although even a 100k Ω one could be fitted. Whilst tuning over Band I the coarse tuning potentiometer should prove sufficiently accurate on its own since a tuning spread of only 30MHz is required. The fine tuning potentiometer is of greater help when tuning in Band III, the rough frequency being set with the coarse tuner and the fine tuner then being used to sweep to the exact frequency. I found however that even in Band III the coarse control is sufficiently accurate by itself. The fine tuning control comes into its own at u.h.f. where it is particularly helpful for sweeping to channels adjacent to strong local signals. A weak signal is often received at a dip in the i.f. response and the fine tuning control is particularly useful for finding this. The fine tuning potentiometer has a range of just over one channel at the l.f. end of the u.h.f. band—from about channel E23. Its range gradually extends at increasing frequencies until at the h.f. end it is possible to sweep three channels.

The stability of the units is good, there being no detectable drift after the initial warm up. I normally allow 25 seconds for warming up, this being the period during which the high-value electrolytics charge. The circuit then operates normally.

If any problem is experienced in obtaining the 4in. Adastra meters or RS components these can be obtained from Ian C. Beckett, 6 Bridge Street, Buckingham. An s.a.e. should be included with the list of requirements.

The author wishes to thank Barry Raynbird of Chandlers Ford for his assistance with this project. ■

C with Coping ICs

PART 2

HAROLD PETERS

Inter-carrier Sound ICs

ALL sound i.c.s are designed to give acceptable results at 4.5, 5.5 and 6.0MHz intercarrier frequencies. Most of them work equally well at 10.7MHz too. Alignment is straightforward. Tune the detector coil—be it a slope detector or quadrature coil—for maximum undistorted f.m. sound. The input circuit, which usually consists of a bandpass pair, is not easy to tune for maximum f.m. due to the limiting action of the i.c. It is best adjusted for minimum a.m. on a reduced signal.

TAA350: This is the original sound i.c. It is a simple limiter-amplifier using an external diode for slope detection. Some gave sibilants on sound, curable by biasing the detector diode on with a little d.c. or by reducing the Q of the detector coil. The latter course reduces output somewhat which is sparse enough at 200mV peak-to-peak. The TAA350 is no longer available: it has been replaced by the TAA350A which has its pins round thus:

TAA350 pin	=	TAA350A pin
1		8
2		9
3(E)		10(E)
4		1
5		2
6		3
7		4
8(N.C.)		5(N.C.)
9		6
10(N.C.)		7(N.C.)

TAA570: This is "almost" a TAA350 but has a built-in detector and audio amplifier. Its "works" were described and illustrated last month. Pin 4 can be used as remote volume control but usually isn't. Early TAA570s gave maximum volume with pin 4 shorted to chassis. Later ones reversed this, giving maximum volume with pin 4 open-circuit. These had an identifying white spot on the case. Later still the white spot was omitted. Moral: do not cut pin 4 off until you are sure which sort your set was wired for. Get some sound first. This i.c. can produce distortion when warm. Try retuning the quadrature coil, or reduce the pin 3 external load (nominally 4.7k Ω). Output about 1.5V p-p for 50kHz deviation.

TBA120: A 14-pin QUIL package widely used in Europe. Available in many brand names. A reliable i.c.

TBA480: This is a 16-pin QUIL replacement for the TAA570. A nice reliable i.c. with about 1.2V p-p output for 50kHz deviation.

TBA750: The current sound i.c. Capable of driving a pair of output transistors directly to get over 2W output. Reliable.

SAA570: Plessey version of the TAA570. Interchangeable.

Zener ICs

Zener i.c.s are two-legged devices designed to stabilise the 30V line used for channel selection with varicap tuners. Most brands come in three voltage selections: 31-32V, 32-34V and 34-35V. This need not concern you unless you live in an area where the u.h.f. channels are 60 or higher: some tuners need the higher voltage selection to give adequate tuning at this end of the u.h.f. band.

TAA550: This is metal cased with the case at 30V. So if you feel like fitting a heatsink ensure that it is isolated from chassis. The voltage ranges are denoted by a coloured dot: red low, yellow medium, green high. These seldom go short-circuit, but can be blown open-circuit by 30V line surges. The symptoms are peculiar, being akin to a.g.c. lockout. On closer observation the tuning is seen to vary with picture content.

SN76550: Texas version of above with similar colour dot coding. Pin 2 may need removing on some sets.

ZTK33: A similar device from ITT, with the voltage selection alphabetically coded—A low, B medium, C high.

ICs for the IF Strip

TCA270: An i.f. demodulator using synchronous detection and supplying positive- and negative-going outputs. The negative-going output usually goes to the sync separator whilst the positive-going one is used for luminance and chrominance outputs. Two a.g.c. voltages are available, with their crossover level adjustable, and a.f.c. control is provided for varicap tuners.

Alignment is by adjusting the "tank" circuit (the same as a quadrature coil in a sound i.c. circuit). It is set for best response with a squarewave modulated on to an i.f. carrier. Experience indicates that a broadcast test card may be good enough for the purpose, but since the tank coil and its neighbouring a.f.c. coil are interdependent no risks should be taken this early by inveterate twiddlers. E.H.T. flashovers can kill these i.c.s off (raster but no snow, faint hiss in loudspeaker). Replacement doesn't involve realignment.

MC1330P: I.F. demodulator (synchronous) plus video preamplifier from Motorola. Used by BRC, RBM, Decca. In 8-pin DIL pack. Provides negative- and positive-going video outputs, also a.f.c. output.

MC1352P: I.F. amplifier i.c. from Motorola incorporating its own gated a.g.c. system. For use in vision

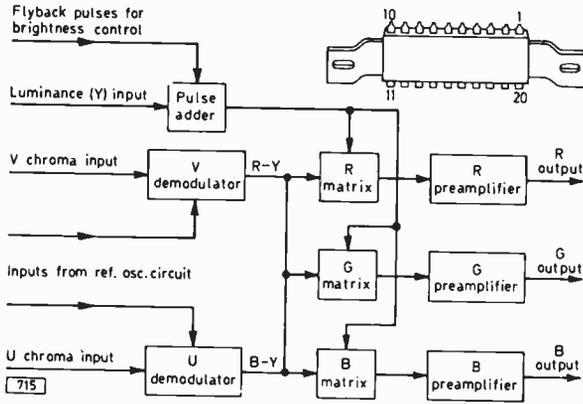


Fig. 1: Block diagram of the SL901 chrominance demodulator and matrixing i.c. used in Bush/Murphy models.

i.f. strips. In 14-pin DIL pack. Used in some chassis to partner the MC1330P.

Jungle ICs

Jungle i.c.s are so called because of their circuit complexity. They fulfil the functions of video pre-amplifier, noise limiter, sync separator, i.f. and tuner a.g.c. generator, line flywheel sync detector, field interlace detector and video blanking. It is possible for one section of these i.c.s to fail without stopping the rest.

TAA700: The first QUIL 16-pin package and the only one you cannot easily fit the wrong way round. Can be the cause of your field trouble; or can upset a.g.c.

crossover if the two a.g.c. outlets short internally, giving more "snow" than usual. If pulses from the line timebase are missing the i.c. reverts to direct sync and ungated a.g.c.

TBA550: This is the zig-zag QUIL replacement for the TAA700. The pin numbering is identical and as some printed circuit boards are pierced to take either there is qualified interchangeability. The TBA550 is more liable to chassis current feedback, to the extent that the Pye group 169 chassis at the changeover to using this i.c. had to split the metalwork at the chassis to remove an earth loop.

SBA550: Plessey interchangeable version of the above. Pinning identical.

ICs for Colour Decoding

SL901: This Plessey i.c., widely used in RBM colour sets, has 20 pins and a heatsink that bolts to chassis for maximum dissipation. U (B-Y) and V (R-Y) signals from the decoder delay line circuit are synchronously demodulated in this i.c., matrixed to produce the G-Y signal and then further matrixed with the Y signal to give R, G and B drive outputs. See Fig. 1.

TBA500: Luminance amplifier, with black-level clamp and beam limiter control.

TBA510: Chrominance amplifier with burst blanking and separate burst output.

The above pair of i.c.s is found in imported sets. The TBA560 supersedes them, saving an i.c. at the expense of extra peripheral circuitry.

TBA520 and TBA990: These are colour demodulators of successive generations. They incorporate the PAL switch and synchronously demodulate the U and V

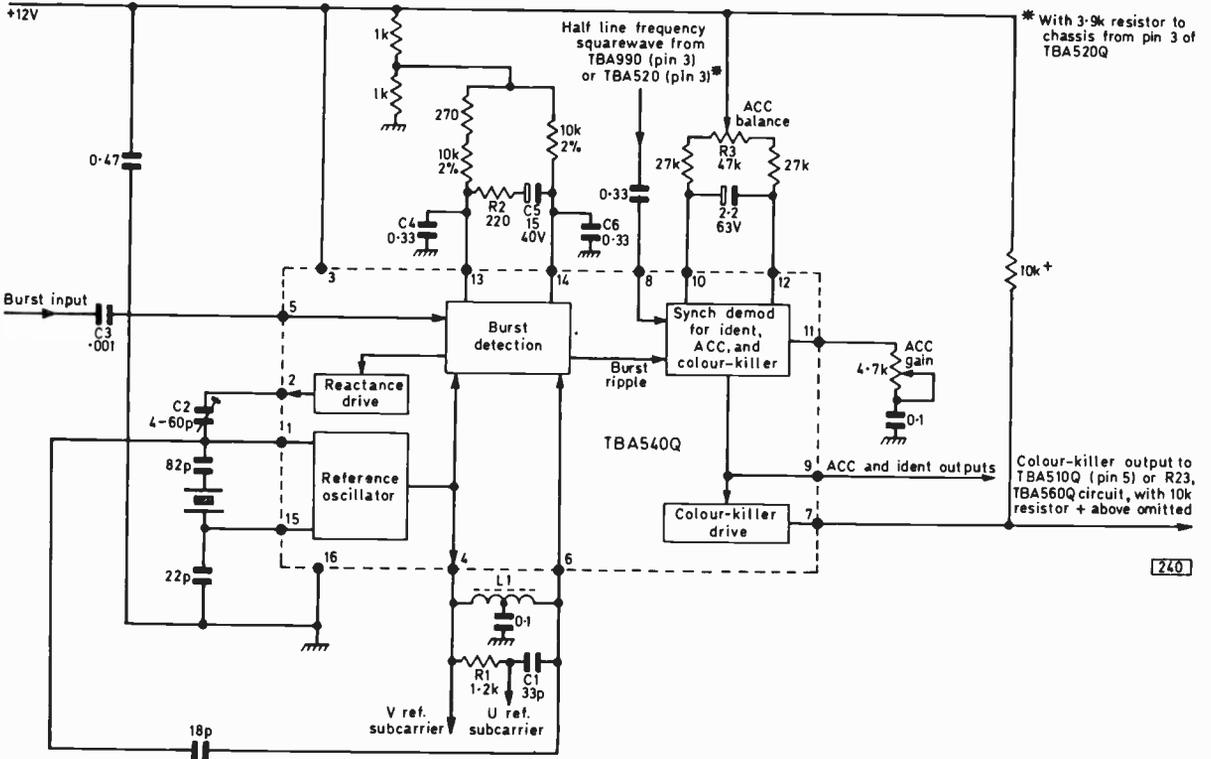


Fig. 2: Block diagram together with peripheral circuitry for the TBA540 decoder reference oscillator i.c.

FAULT FINDING GUIDE

7

John Law

TIMEBASES: PHILIPS 19TG158A SERIES

The sets in this series, sold mainly under the **Philips**, **Stella** and **Cossor** brand names, frequently appear in the workshop. Not, I hasten to say, because it is a bad chassis but because of the large number of sets sold. Far from being of poor design in fact the chassis has several unusual safety features. Apart from the usual fuse in the mains input circuit there is a 150mA fuse in the i.f., tuner and field timebase h.t. circuit and a 250mA fuse in the line timebase and sound h.t. circuit. In addition to these three fuses there are eight 1W drop-off resistors which are soldered to the underside of stand-off tags: should a fault cause excessive current through any of these resistors the solder will melt so that the resistor(s) concerned will drop from the tags thus breaking the circuit. This can prevent a serious printed panel burn-up. It also gives an immediate indication of the area of the fault.

The models in the series were fitted with 19 and 23in. tubes and originally the u.h.f. tuner was an optional extra. The common Philips Models 19TG158A, 19TG164A and 23TG164A, the Stella ST2029A and Cossor CT1974A have transistor u.h.f. tuners while the earlier Philips 19TG154A and 19TG156A together with the Stella ST2123A, ST2113A, ST1093A, ST1099A and ST2149A have valve u.h.f. tuners.

When the cabinet back is removed right- and left-hand printed panels mounted vertically in a metal frame are revealed. The space between the panels is occupied by the mains dropper sections at the top, the c.r.t. base below and a box below that secured to the bottom of the metal frame and containing the line output valve and transformer, boost diode

and e.h.t. rectifier. Each panel has a system switch mounted vertically on it. The right-hand panel contains the i.f. and video valves and components while the left-hand panel is the timebase section. The tuner units are fitted to the left of the chassis frame with the knobs protruding through the front of the cabinet. Below the knobs are the system change buttons.


This article is concerned with fault finding in the field and line timebases. The circuit of these is shown in Fig. 1 while Fig. 2 shows the layout of the timebase panel. There are four valves on the panel, an ECC82 at the top, another ECC82 below it, an ECL80 below that and at the bottom a PCL85.

The pentode section (V401b) of the ECL80 is the sync separator. From the anode of this valve line sync pulses are fed to the grid of the line sync pulse amplifier/inverter triode V403a through R401/C401 and R403. The field sync pulses are integrated through R446 and C433 and applied to V401a grid. V401a in conjunction with the triode section of the PCL85 forms the field multivibrator, the cross-coupling capacitors being C430 on one side and C432/C431 on the other. The field charging capacitor C429 charges via R438 and the height control R439 to give the forward scanning stroke and is discharged via V402a when this valve conducts briefly once each multivibrator cycle to give the flyback stroke. The field signal thus produced drives the field output pentode V402b which in turn feeds the field scan coils via the field output transformer L106/7.

Returning to the line timebase, positive going sync pulses are fed from the anode of V403a via C402 to the anode of V403b the flywheel sync phase comparator valve. Reference pulses from the line output transformer are fed via C404 and the integrating network R410/C403 to V403b grid. The resultant d.c. potential at V403b anode is filtered and used to control the line oscillator. This consists of another double-triode multivibrator, V404 (the other ECC82). The cross-coupling capacitors here are C407 and C408. The control voltage from the flywheel sync circuit controls the time-constant of V404a grid circuit—this is basically set by the hold controls. Note that the drive voltage applied via C410 to the control grid of the line output valve is taken from the anode of the a section of V404. The line output stage itself is conventional, with V500 (PL36) the line output valve, V501 (PY800) the boost diode and V502 (DY87) the e.h.t. rectifier. The boost capacitance consists of the two capacitors C415 and C416 connected in parallel. It will be seen that there are no flywheel line sync discriminator diodes, their function being performed by V403b: this valve has proved more reliable than the usual diodes but can nevertheless cause weak or complete loss of line sync.

Fault tracing and component replacement on this chassis is not difficult: the removal of two bolts at the top of the metal frame gives access to the rear of the panels while clips above the panels release them to the extent of the leads. The box containing the line output transformer and associated valves can be taken out complete after two bolts at the bottom of the frame have been removed. The only problem is to ensure that the print behind the upright panels is clean and free from dust so that it will solder well: a toothbrush with some Thawpitt together with a dentist's mirror are useful for cleaning and inspecting completed joints.

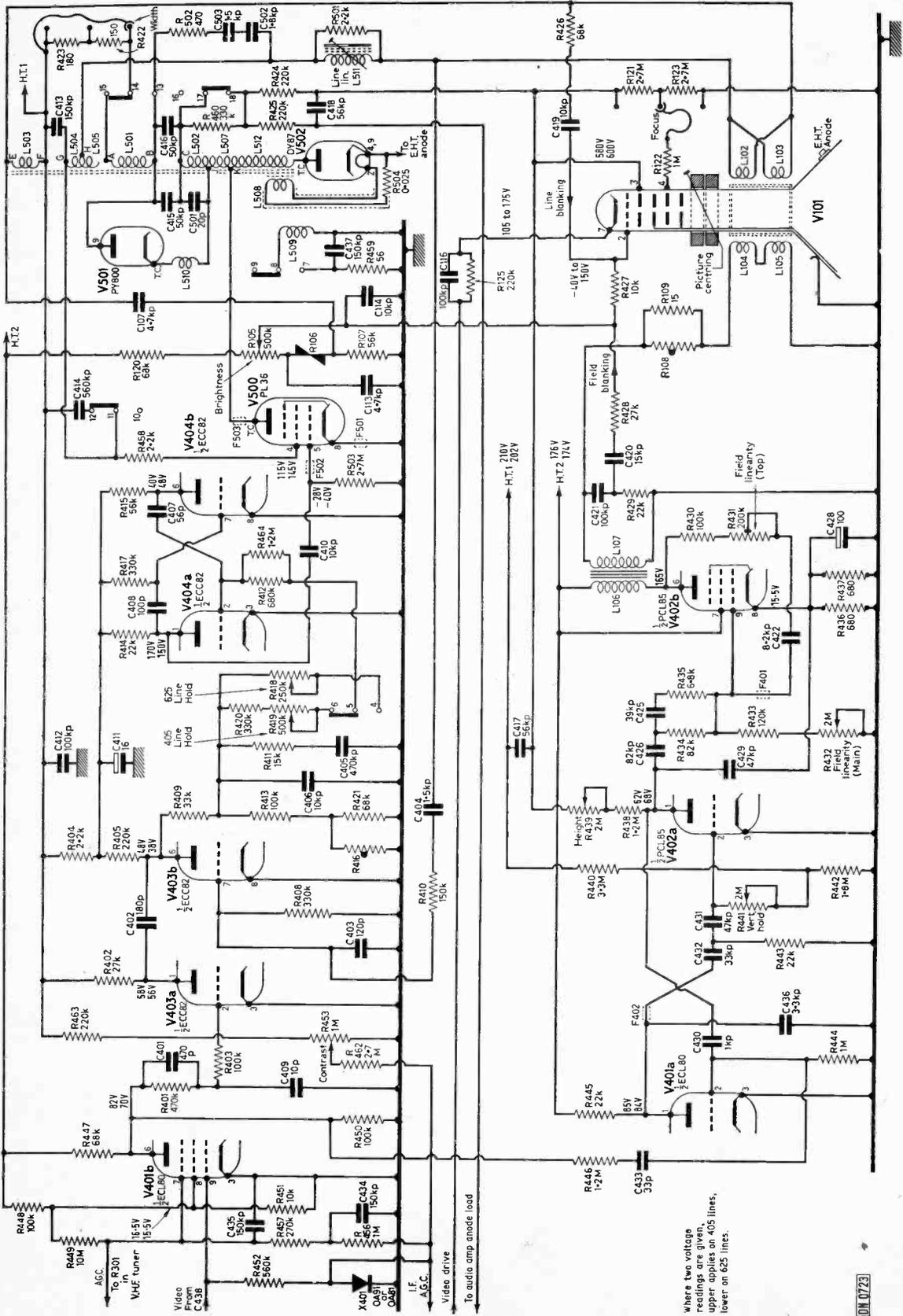The drop-off resistors are a great help in locating



Where two voltage readings are given, upper applies on 405 lines, lower on 625 lines.

Fig. 1: Timebase circuits used in the Philips 19TG158A series. Switches in 405-line position. Voltages measured with 100kΩ/V meter

a faulty circuit. Their functions are as follows:

R200 (470 Ω) is in the h.t. feed to the u.h.f. tuner. R201 and R201a (both 3.3k Ω) in parallel are in the feed to the v.h.f. tuner.

R223 (390 Ω) forms part of the sound output pentode cathode resistance.

R254 and R255 (both 3.9k Ω) in parallel feed h.t. to the video output pentode (PL83).

R436 and R437 (both 680 Ω) in parallel comprise the field output pentode cathode resistance.

If there is excessive current in the PCL85 pentode section, as a result of an interelectrode short for example, R436/7 will be over-run melting the solder so that they fall to the floor of the cabinet. Their presence there immediately indicates a fault in the field timebase therefore. Before resoldering any of the drop-off resistors it is essential to find and clear the fault. If the resistors are discoloured or have changed value fit new ones.

From the above it will be obvious that the first step in fault location on this chassis should be inspection of all the drop-off resistors. If all are in position check the three fuses. The 1.5A mains fuse FS100 is beside the voltage adjustment panel and protects the heaters, the h.t. rectifier and main smoothing electrolytics. Failure of the 250mA fuse FS202 located at the top right-hand corner of the i.f. panel will leave the heaters alight but no sound or vision since it controls the h.t. supply to the line timebase and the audio amplifier (V203 triode section). Any momentary arcing in the boost diode or line output valve will blow it. The 150mA fuse FS201 is located on the left of the i.f. panel and controls the power supply to the field timebase, the i.f. stages and the tuner units.

In dealing with field timebase troubles the valves should always be the first suspects. Remember that in this chassis there are two valves involved, the triode section of an ECL80 as well as the usual PCL85.

The field output transformer can cause a number of faults in this chassis. One is slight foldover at the top of the picture with the BBC-1 test pulse in the field blanking interval visible on the screen: in some cases the foldover is steady, in other cases intermittent. Low field amplitude with good linearity has also been traced to the field output transformer, as has creeping at the top of the raster with a 3in. gap at the bottom. The defective transformer cannot be repaired, replacement is the only answer.

In cases of low height however, first replace the PCL85 then check the value of the 1.2M Ω resistor R438 in series with the height control. This increases in value over a period of time to give lack of height.

Bottom cramping may be due to loss of capacitance in the pentode cathode decoupling electrolytic C428 (100 μ F). Similar symptoms are caused by failure of C422 (0.0082 μ F) in the linearity feedback network or C426 (0.082 μ F) in the coupling circuit.

Loss of height with low brightness has been traced to C417 (0.056 μ F) and R424 (220k Ω) which smooth the boost feed to the height control.

Poor linearity should lead to a check of the components in the linearity circuits (anode to grid and grid to chassis of the PCL85), particularly the miniature preset potentiometers (R431 and R432)—dead spots and breaks in the tracks of these components account for many linearity faults.

Complete field collapse (horizontal white line) may be caused by failure of the field multivibrator.

After checking the valves check the cross-coupling capacitors. A break in the track of the field hold control potentiometer R441 will also cause this fault.

Spasmodic height variation can be difficult to trace. Valves and potentiometer tracks should be checked first and if cleared individual components on the printed panel measured for value changes and prodded for dry-joints or internal breaks until the offending item shows up. Don't forget C421 (0.1 μ F) across the secondary of the field output transformer and R108/R109 which are in series with the field coils.

Loss of width is a common complaint and is usually cured by replacing the PL36 line output valve. It can also be caused by loss of emission in the PY800 boost diode.

If the line cannot be locked and the hold control is at one end of its track change over the two ECC82 valves at the top of the printed panel. This will often effect a cure as the line oscillator ECC82 (V404) operates under more stringent conditions than the line sync ECC82 (V403): replacement of the V404 ECC82 is of course the long term solution in this case. If the fault is confined to 405-line operation check the value of R420 (330k Ω) in series with the 405 line hold control. Another cause of lack of line locking is change of value of R402 (27k Ω). A case of ragged verticals developing some time after switching on was traced to the v.d.r. R416 being faulty—as a check it can be replaced by a 100k Ω resistor.

Loss of line drive to the PL36 can be caused by R420 going open-circuit. An open-circuit R417 (330k Ω) will also kill the drive voltage. This is the grid return resistor of V404b and is taken to the h.t. line instead of to chassis. A decrease in its value will give weak line hold with the control at one end of its track: the clue to this fault is a drop in V404b anode voltage of about 10V.

If the line oscillator goes out of lock when changing channels inspect and clean the system switch—poor contacts can give this symptom.

If there is no raster but the drive voltage is present at the PL36 grid the cause may be failure of the screen grid resistor R458 (2.2k Ω). If this component is OK however remove the top cap of the PY800 boost diode: if this results in an increase in the timebase whistle first suspect the boost capacitors C415 and C416. Then suspect the line output transformer which unfortunately often proves to be the faulty component in this chassis.

Should a picture of low brightness level balloon and disappear when the brightness control is turned up the cause is probably the e.h.t. rectifier V502 (DY87). There is however a resistor (R504) in series with its heater. This can increase in value, lowering the heater voltage and giving the same symptoms. Its value is 0.025 Ω and a replacement must come from the manufacturers. The layout of the line output section box is shown in Fig. 3.

One case where repair of the line output transformer was possible occurred with the complaint of normal picture on 625-line operation but no results on 405 lines. The customer had forgotten to mention that there was no sound either. A voltage check soon revealed that there was no h.t. voltage at the anode of the PY800 boost diode. The supply on this system is via the width resistors R423 and R422, contacts

—continued on page 557

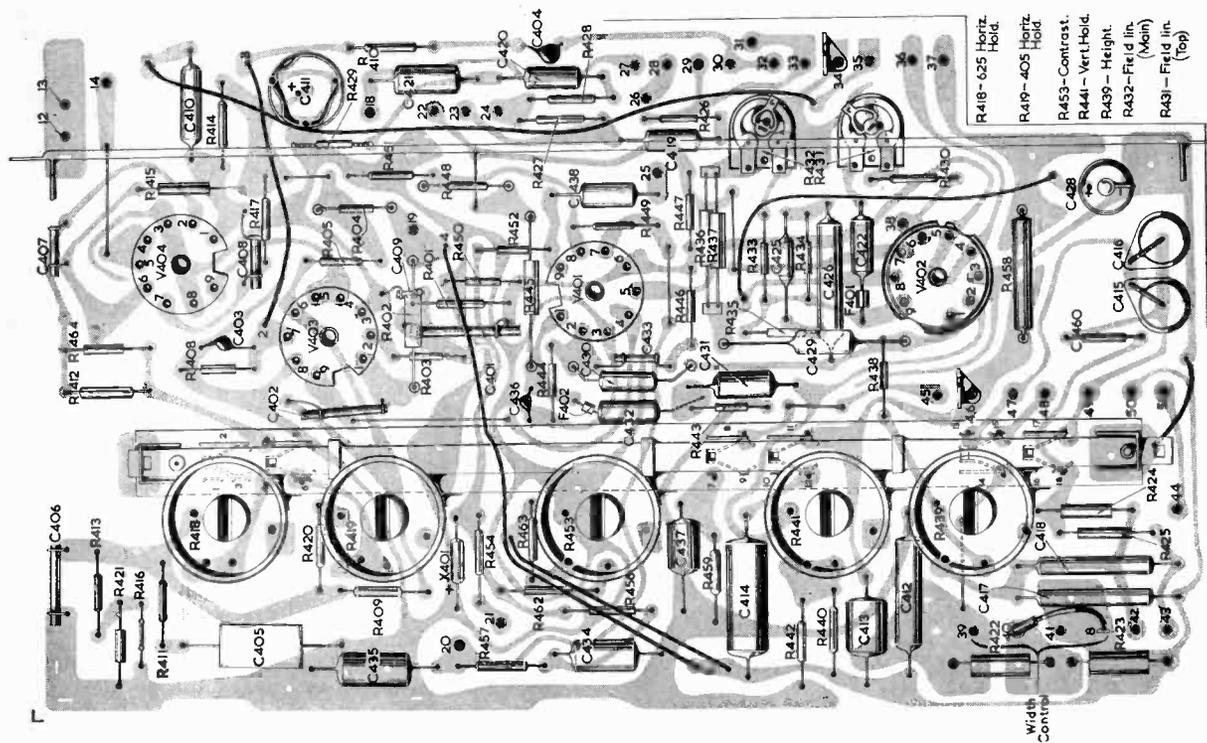


Fig. 2: Layout of the timebase printed panel, viewed from the component side.

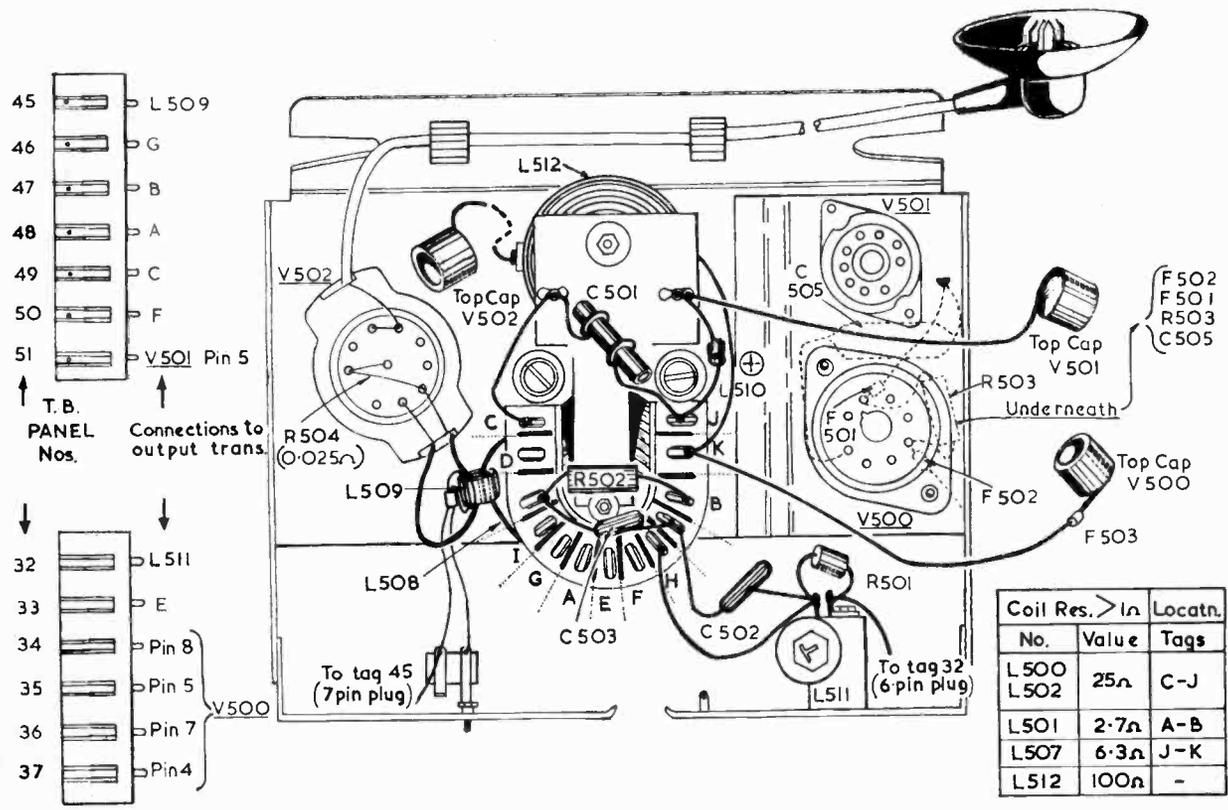


Fig. 3: Physical layout of the line output stage. When replacing the line output transformer clear the tags then unsolder the heater wires from V502 holder, accessible after prising out the top moulding. Coil d.c. resistances given where greater than 1 Ω .

LONG-DISTANCE TELEVISION

ROGER BUNNEY

SPORADIC E picked up towards the end of July following what had become a rather depressing lull. Indeed there were several really sustained and intense openings with long-skip signals and what was a most welcome visitor here—Danmarks Radio early on the 26th on channels E3 and E4. A fire destroyed the Copenhagen ch. E4 transmitters recently but within a fortnight Marconis had installed replacement units with normal service resumed. A number of mysteries have arisen and will be dealt with later. First however the log:

- 1/7/73—CST (Czechoslovakia) ch. R1 MS (Meteor Scatter); BRT (Belgium) E8, E10—both tropes (tropospherics).
- 2/7/73—DFF (East Germany) E4; TVP (Poland) R1—both MS; also improved tropes (u.h.f.).
- 3/7/73—WG (West Germany) E2—MS; NOS (Holland) E4—tropes.
- 5/7/73—TSS (USSR) R1, R2—SpE; NOS E4—tropes.
- 6/7/73—TSS R1—SpE; CST R1—MS.
- 7/7/73—TSS R1; MT (Hungary) R2; RAI (Italy) IA twice, IB; JRT (Yugoslavia) E3, E4; TVE (Spain) E2; plus unidentified signals—all SpE.
- 8/7/73—TSS R1; MT R1; CST R1; RAI IA; JRT E3 twice, E4 twice; *Albania* IC—all SpE.
- 9/7/73—DFF E4—MS; TSS R1—SpE; also improved tropospherics into ORTF (France u.h.f.).
- 10/7/73—DFF E4—MS.
- 11/7/73—DFF E4—MS; TSS R1, R2; RAI IA—both SpE; also SpE mystery pattern on ch. E2—see later!
- 13/7/73—TSS R1; TVP R1, 2, 3—all SpE.
- 14/7/73—TVP R1; CST R1; SR (Sweden) E2, 4; NRK (Norway) E2—all SpE.
- 15/7/73—CST R1; RAI IB—all MS; NOS E4—tropes.
- 16/7/73—CST R1—MS.
- 17/7/73—DFF E4; CST R1—both MS.
- 18/7/73—TSS R1, 2; TVP R1, 2; DFF E3, 4; JRT E4—all SpE.
- 19/7/73—TSS R1, 2; DFF E4; SR E2 twice, E3 twice, E4; ORF (Austria) E2a; TVE E2, 3, 4; RTP (Portugal) E2—all SpE.
- 21/7/73—DFF E4; CST R1; WG E2—all MS; JRT E3, 4; TVE E2, 3, 4—all SpE.
- 22/7/73—CST R1; RAI IB—both MS.
- 23/7/73—CST R1; SR E2—both MS.
- 24/7/73—DFF E4—MS.
- 25/7/73—TSS R1, R2 twice; TVP R1, 2; CST R1; MT R1; SR E2, 3, 4; NRK E3; WG E2; ORTF (France) F2—all SpE; DFF E4—MS.
- 26/7/73—TSS R1 twice; R2; CST R1; TVP R2; DFF E3, 4; ORF E2a; DR (Denmark) E3, 4—all SpE; NOS E4—tropes.
- 27/7/73—DFF E4—MS.

28/7/73—DFF E4—MS; CST R1—SpE, R2—MS; WG E2—MS.

More aerial activities at this end! On the 22nd the total aerial structure was removed and an extra 10ft of lattice fitted, lifting the mast itself to 40ft. Unfortunately, due to the late arrival of a new type of u.h.f. aerial the "normal" aeriels are at the time of writing out of service. A two-element Tru-match type wideband Band I array is in use facing East at 44ft. I shall be reporting on the performance of the new u.h.f. structure in due course.

Mystery Corner!

We would appreciate any suggestions and comments on the following points which have given rise to considerable speculation. A Dutch report indicates that a version of the checkerboard pattern with much smaller squares is in use on ch. E3, source unknown. It appears that Albania is using a form of small chessboard as well since Garry Smith (Derby) reports reception of this pattern on ch. IC. Garry also comments on variations of the Czechoslovakian CS U 01 pattern, with circles omitted and floating with various TSS programmes and test cards.

Older enthusiasts will recall the crosshatch/grid pattern once used by TVE. Both Graham Deaves and Ryn Muntjewerff (Holland) noted this pattern—consisting of 5 x 5 squares—from the East on ch. E2 at 0700 GMT on July 11th. For my part this signal appeared to be a long-skip one—resembling a tropospheric signal, noisy with slow fading. It came from a roughly Easterly direction and faded at 0730 with no indication of its origin. To confuse matters further George Sharples (Malta) has also seen this pattern on ch. E3.


The Finnish Fubk pattern has been noted—in fact we have an excellent photograph taken by Dieter Scheiba—carrying the identification "CNCT YLE". We are waiting news from Finland as to the purpose of this extra identification.

Finally from David Griffin via Graham Deaves (both from the Norwich area) comes a photograph showing the normal T05 Telefunken card but with an identification consisting of three very small symbols/letters immediately above the circle while below the circle are six equally small letters which resemble "CANALT"—I suspect this is "CANAL?". Channel E4 on May 26th last was the important date for this mystery—at 1520 GMT. My log indicates that the JRT/MT direction was active at the time.


PM5544 Round-up

The PM5544 test card is so widely used at present—according to the Europese Testbeeldjagers Rumania is also now using it—that to clarify the situation we are including the following list of users. At the time of writing it is reasonably accurate but the


DATA PANEL 27 – 2nd series

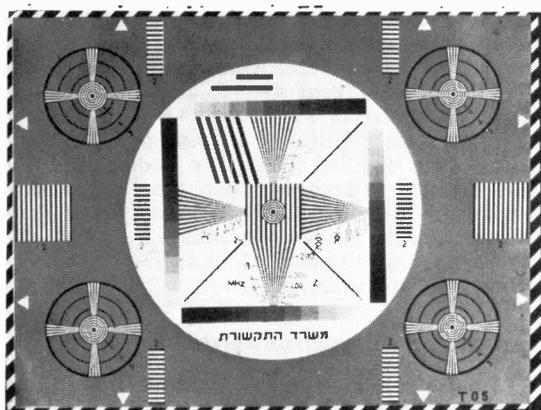


Test card used by Israel.

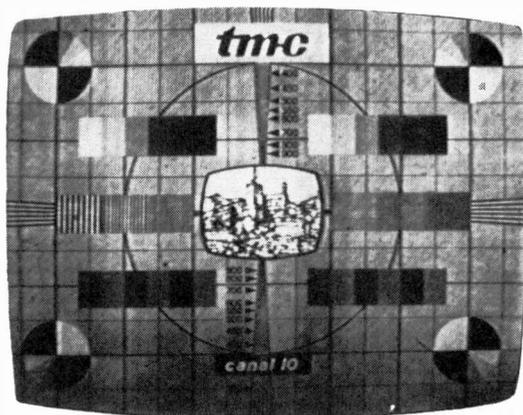

New Tele Monte Carlo test card.

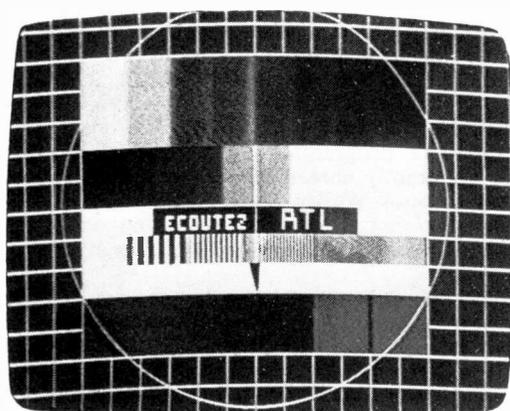

New Tele Luxembourg test card.

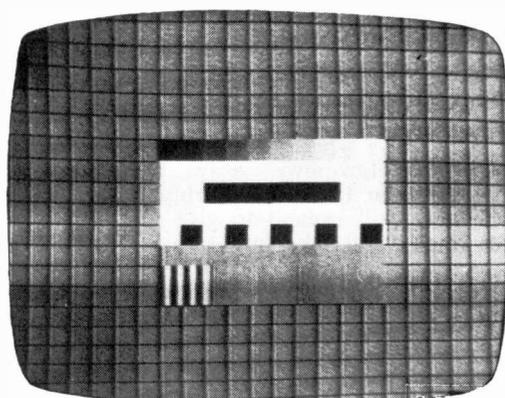

New USSR test pattern.

Photographs this month courtesy Michele Dolci, Dieter Scheiba and Ryn Muntjewerff

situation seems to change daily!

RTE (Eire), carries the identification "RTE".

BRT/RTB (Belgium), carries the identification either "BRT" or "RTB".

DR (Denmark). Identification "DR Danmarks Radio".

NRK (Norway). Identification "Norge Televerket".
SR (Sweden). Identification "SR1" or "SR2", plus "Sverige".

ORF (Austria). Identification "ORF" and either "FS1" or "FS2".

JRT (Yugoslavia). Identification "JRT Zagreb" or "JRT LJNA".

TVR (Rumania). Identification "TVR".

MT (Hungary). No identification.

NOS (Holland)—experimental transmissions only from the Lopik transmitter.

This list is provided by courtesy of the Europese Testbeeldjagers (Oudelandseweg 56, Ouddorp 3348 (ZH NL), Holland). The club incidentally is becoming quite large and with this so are the news items increasing—all too important in active SpE condi-


tions. Enquiries to the club for sample bulletins should be accompanied by two international reply coupons.

News

West Germany: As from July 1st AFN Frankfurt (American Forces Network) has taken over responsibility for the forces TV from the US Army at Wiesbaden. We understand that Siemens have received an order for the supply of 56 transmitters for the AFRTS Network in West Germany. AFN has been in operation some 30 years.

Nigeria: New transmitters under construction: Kaduna ch.E10, Kano ch.E2, Enugu chs.E3/4 (this station was received in the UK on its old ch.E2 shortly before the Biafran War), and finally Port Harcourt ch.E5.

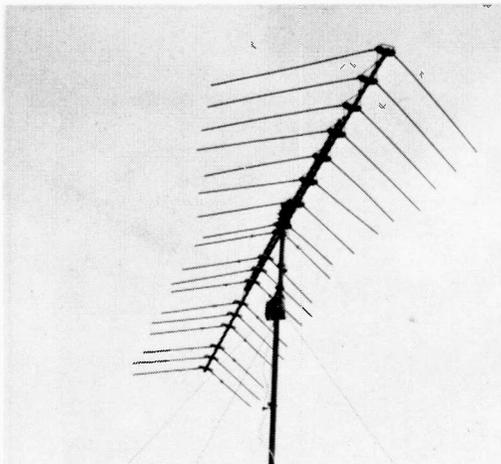Iraq: Pye TVT are to supply six transmitters to the Ministry of Information for the expansion of television in the South of the country. These will be located at Sammawa, Amarah and Basrah and use



Wideband log-periodic aerial (Bands I and III) used by Robert Fitzjohn at Yaba, Nigeria.

pairs of 10kW transmitters with 1,000ft. masts.

Poland: The first network (TVP-1) is to be expanded to cover 95% of the population by 1978, using mainly v.h.f. transmitters with local relays where necessary. The second network (TVP-2) will be expanded through main u.h.f. transmitters with low-power v.h.f. relays where necessary—all towns will have their own low-power relays by 1974 (40% coverage). Between 1976-1980 the high-power transmitter network will expand to give 95% coverage. In 1974 Poland will take into service a terrestrial station to operate with the Orbita satellite network, giving the ability to participate in long-distance television programme exchanges with other Intervention countries. There is also mention of "The third television programme," an international version of the first programme but assumed to be for external use and not to be transmitted in Poland.

Wideband UHF Aerials

Until quite recently the wideband u.h.f. aerial tended to be a low-gain log-periodic array (wideband in this context is coverage of the whole u.h.f. TV spectrum, Bands IV and V). Examples of such aerials are the J Beam Log-beam and the Antiference Troubleshooter. The situation is changing however. Wolsey now market an array which consists basically of four stacked bowtie dipoles. This gives coverage over the whole band with a gain/bandwidth characteristic as shown in Fig. 1. A number of enthusiasts have reported highly on this array which has a reasonable gain for its size, averaging 3dB up over the best log-periodics. A higher performance array is the Fuba XC391D a photograph of which was featured in the February 1973 column. The

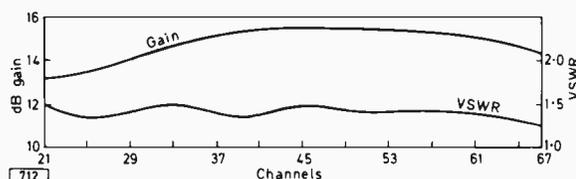


Fig. 1: Gain and VSWR characteristics of the Wolsey "Colour King" wideband u.h.f. aerial.

gain of this rises from 10.5dB at ch.E21 to 16dB at ch.E60. Within the last few days a most comprehensive list of u.h.f. arrays has arrived from R. Smith Aerials of Luton. Of particular note are the ranges of wideband u.h.f. aerials. The ZE range comprises four arrays with varying gains, the highest being that of the ZE30 which has a quoted gain of 14.5dB at E21 rising to 16.8dB at E68. A much more impressive array (visually) is used in the main Z range. This consists of a twin-boom arrangement with a twin director chain. The Zodiac 30 array has 118 directors (these are not the X-type director assemblies but separate units) and quoted gains of 15.9dB at E21 rising to a peak of 21.0dB at E68. The arrays in this range (four in fact) have a maximum gain at around E54.

From Our Correspondents . . .

Michele Dolci (Italy) confirms that Libya is operating on ch. E4. Trop signals have been received in Southern Italy by an enthusiast at Catania. The station appears to be a low-power one. There is no further news about the Tele Monte Carlo u.h.f. transmitter but a new test card is in use on v.h.f. and is included in our Data Panel this month.

Jordan "went colour" on April 27th. George Sharples tells us he has noted this country using the PM5540 test card on ch.E3. The card preceded educational programmes—during which commercials are apparently screened! Whilst on the subject of Jordan Derek Waller of Consett has received written confirmation from Jordan Television confirming his reception earlier this season—our congratulations on this.

Ryn Muntjewerff (Holland) has sent us details of a new wideband array now available in Holland and intended for TV-DXing! It is a log-periodic array covering 47-88MHz (ch.E2-1C), with eight active dipoles and one director. The length is approximately 12ft. and the aerial is for use with 300Ω balanced feeder. Ryn reports excellent results with this aerial, including strong Albanian signals on various occasions. Further information on this array can be obtained from: Benelux DX Club, Margon B.V., Eindhoven, Holland.

Robert Fitzjohn who is at present on leave in the UK from Nigeria has sent a long letter describing the exotic DX in that part of the world. There are many channels available but "it's a gamble most nights"! Apart from various locals up to about 250 miles he can view Accra ch.E4 when Ibadan leaves the air at 2200 (Accra is -1 hour GMT) and farther afield Lome, Togo on ch.K8 with 819 lines can be received (this is not listed in the 1973 WRTVHB). Signals in the area generally vary according to local weather conditions (at the time of writing it's the "rainy season"). The Fernando Poo transmitter (programmes in Spanish) can—weather permitting—be received on occasions on either ch.E11/12.

Neil Breward of Stoke-on-Trent comments that things have been really buzzing using our wideband dipole and a modified Bush receiver. A very comprehensive log shows that he received as many stations during 20 days in May as he did throughout 1972! Finally L. Allsopp (Cardiff) has forwarded a detailed log including unusually short-skip signals: he has noted the BBC-1 Scottish service with local news—the signal was typical Sporadic E with ghosting and rapid fading.

BASIC

COLOUR FAULTS

GUIDE

SPECIAL SUPPLEMENT TO 'TELEVISION' OCTOBER 1973

IN this special colour supplement we show some of the faults peculiar to colour sets, using off-screen photographs for easy recognition. These were taken from a standard British-made PAL receiver fitted with a shadowmask tube. Picture faults which are common to colour and monochrome sets, such as those affecting height, width, linearity, focus, brightness or resolution are not shown.

PURITY

The neck of a shadowmask tube contains three independent electron guns whose beams must each pass through the shadowmask to reach only the red, blue or green phosphor dots respectively, so that each gun scans a raster of one primary colour with no impurity or tainting with another colour. If a purity error is present, objects will change colour as they move across the screen and a monochrome picture will contain tinted areas. Purity errors are most visible on the red raster and therefore purity is checked by switching off the green and blue guns so that only a red raster is seen. Most sets are equipped with gun cutoff switches for this purpose; on a few (e.g. Decca CTV25) the guns can only be cut off by backing off the A1 (background colour) presets. Photo 1 shows a red raster with typical purity errors showing.

CURE: Loosen the wingnuts on the scan coil assembly and slide the coils towards the tube flare. Adjust the **purity rings** (these are two ring magnets on the tube neck, rearward of the convergence assembly. They can be adjusted to aid or oppose each other and produce a magnetic field across the tube neck at any angle) for pure red at the **centre** of the screen. A magnifying glass can be used to check that no green or blue phosphor dots are illuminated here. Now bring the scan coils rearward until the screen is uniformly red as in Photo 2. If necessary retrim the purity rings to remove any remaining purity errors in the corners. Now switch on the blue and green guns singly to check that there are no purity errors in these colours either. If pure rasters cannot be obtained the shadowmask has probably become magnetised and requires degaussing; check whether the set's automatic degaussing circuit has failed.

With all three guns switched on, a colour set should provide a good quality picture on a monochrome transmission. The grey tones in the picture should have neutral colour. If there is any overall colour tint the grey scale adjustment procedure recommended by the manufacturer should be carried out.

CONVERGENCE

There should be virtually no coloured fringes visible on the edges of objects. Presence of these means the three primary-colour rasters are not exactly converged (registered) together. There are two sets of convergence controls, for **static** and **dynamic** convergence.

Coloured fringes over the **entire** picture as shown in Photo 3 are cured by adjusting the static convergence controls on the tube neck. These are three circular magnets

which provide radial shift of the red, blue and green rasters respectively, plus a fourth **blue lateral** control for sideways movement of the blue raster. Set these static controls for correct registration at the **centre** of the screen. The cross at the centre of Test Card F is a useful aid for this. Recheck purity after static convergence adjustments.

Even with good static convergence, fringes may be visible in parts of the picture away from the centre as in Photo 4. This is cured by careful setting up of the dynamic convergence controls. A crosshatch pattern generator should be used for these critical adjustments. Failing this it is just possible to use a test card but it is humanly impossible to set up dynamic convergence on an ordinary picture. The skill of achieving a good result is only learnt by practice—a useful hint is to turn each control slightly **less** than appears to be called for at any stage of the process.

MISSING COLOURS

Complete absence of one of the three rasters leaves a picture of the complementary colour, e.g. no red raster leaves a cyan picture, Photo 5, no green raster leaves a magenta picture, Photo 6, and no blue raster leaves a yellow picture (not shown). The cause of the fault might be:-

- A beam cutoff switch at 'off', or
 - Extreme mis-setting of the grey scale controls, or
 - Incorrect A1 voltage
 - Incorrect cathode voltage
 - Incorrect grid voltage
 - Internal failure of the tube.
- } at the faulty gun, or

On a receiver with primary-colour drive to the tube cathodes the fault is very likely to lie in the relevant colour output stage.

COLOUR DECODER

A block diagram of the decoder used in PAL receivers is shown. A crystal-controlled reference oscillator (4.43 MHz approx.) feeds two synchronous demodulators which detect the two colour-difference signals R-Y and B-Y present in the composite colour signal. Subsequently G-Y is obtained by electrical summing of these two. The reference oscillator must run in phase with the modulating oscillator at the colour transmitter. To ensure this a 'burst' of about 10 cycles of 4.43 MHz is included for reference immediately after the line sync pulse on colour transmissions.

However, the special feature of the bursts in the PAL system is that on successive lines they are alternately 45° phase-advanced and 45° phase-retarded. Since the oscillator control voltage is smoothed the phase-lock loop does not attempt to follow these alternations and the oscillator runs at the average phase of the bursts. The burst phase alternations do cause the phase discriminator output to contain an a.c. component of half line frequency i.e. 7.8 kHz. This is amplified by a 7.8 kHz tuned amplifier and is a vital signal known as the 'ident'; it serves two purposes:-


BASIC COLOUR



1. Impure Red Raster



4. Poor Dynamic Convergence

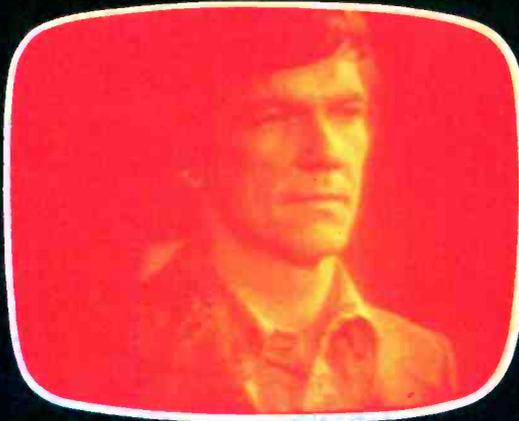

2. Pure Red Raster



5. No Red Raster



3. Poor Static Convergence



6. No Green Raster

R FAULTS



7. Reference Oscillator not locked



8. Pal Switch out of Phase



9. Dry-joint on Luminance
Delay Line


GUIDE




10. Hanover Blinds



11. Blinds removed - Compare with 10

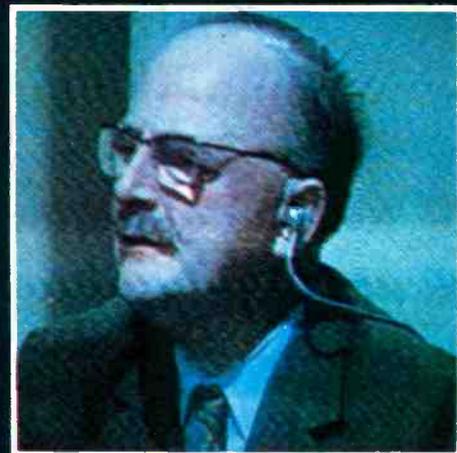

12. Sound/Chrominance
Beat Patterning

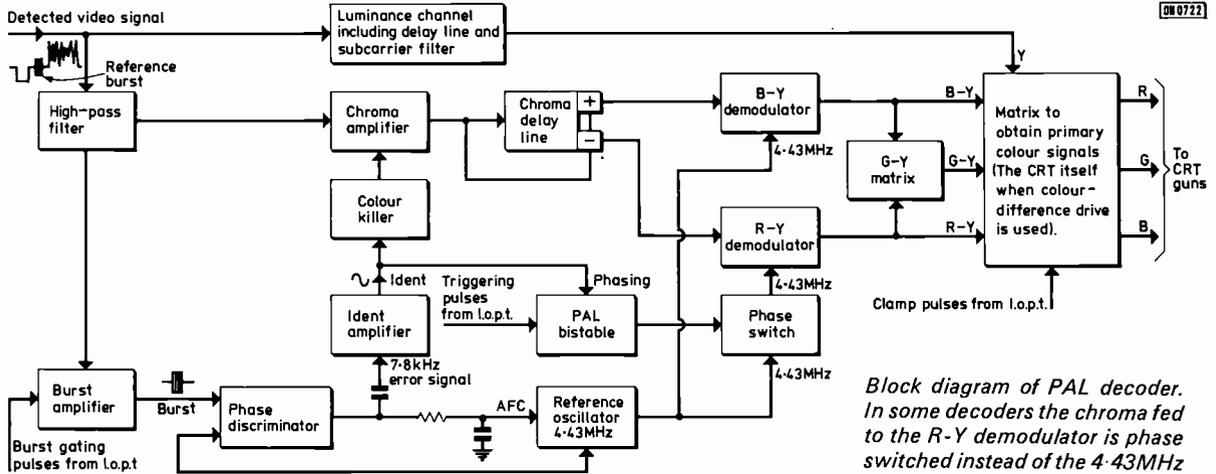

Block diagram of PAL decoder. In some decoders the chroma fed to the R-Y demodulator is phase switched instead of the 4.43MHz reference supply.

(a). It establishes the correct operating phase for the PAL bistable. This is a multivibrator which is clocked (reversed) by line pulses to run at half line frequency and operates a phase reversing switch in the reference oscillation supply to the R-Y demodulator. This arrangement is necessary because the R-Y phase is reversed at the transmitter on successive lines; without 'ident' the PAL bistable cannot 'know' in which of its two phases to start.

(b). It disables the 'colour killer'. Since ident is derived from burst, absence of ident normally means the transmission is monochrome whereupon the colour killer removes forward bias from a transistor in the chroma amplifier so that no unpleasant coloured 'noise' reaches the tube.

DECODER FAULTS

Many decoder faults upset the ident so that the colour killer operates. Therefore if a set shows a monochrome picture when the programme is known to be in colour (and the set is correctly tuned) the first step should be to artificially disable the colour killer so that the state of the decoder can be diagnosed from the screen. Ways of disabling the colour killer vary; usually a 10 kΩ resistor fitted with crocodile clips can be connected from the transistor supply rail to the base of the killer-controlled transistor to provide operating bias.

Failure of the reference oscillator to lock to the burst frequency appears as horizontal bands of colour across the screen, Photo 7. The more bands there are, the further off frequency is the oscillator.

CURE: Carefully adjust the oscillator frequency to see if it can be brought into lock to give correct colours. If the oscillator can be brought close to the correct frequency but does not lock, suspect a fault in the burst amplifier or phase discriminator. If the burst is completely lost the colour is likely to 'run through' the picture so fast it can hardly be seen. An oscilloscope is needed to check such points as the burst gate pulse timing and the burst amplifier tuning.

If the PAL bistable runs in the wrong phase, R-Y is incorrectly demodulated and the colours are wrong—in particular, faces are bright green! See Photo 8.

CURE: Interrupt the signal several times to see if the bistable phasing is sometimes correct or permanently wrong. If sometimes correct, the bistable is not receiving ident phasing and therefore has a 50/50 chance of starting correctly. Check the discriminator balance, ident amplifier and bistable phasing diode. If the bistable phase is permanently incorrect the ident amplifier is likely to be off tune.

HANOVER BLINDS

The purpose of alternating the R-Y signal phase on alternate lines is to cancel out phase errors in the signal path. In all British-made PAL sets a one-line (64 microsecond) delay is used to separate the R-Y and B-Y (not alternated) signals before demodulation. The delayed and undelayed chroma signals are summed to obtain B-Y and differenced to obtain R-Y. Accurate separation is only possible if both the amplitude-balance and the phase trim presets associated with the delay are set correctly; if there is any error there will be a difference in colour between adjacent lines—the so-called 'Hanover blind' effect, see Photo 10. In coloured areas of the picture, pairs of lines appear to crawl upward.

CURE is to trim the chroma delay presets for minimum blinds, preferably viewing a colour bar pattern, to obtain the satisfactory result in Photo 11.

A fault which can be mistaken for very severe Hanover blinds occurs if the PAL bistable sticks in one state; then there is virtually no colour on alternate lines. Often the trouble lies in the line pulse feed to the bistable.


LUMINANCE DELAY

This is a much briefer (some 0.6 microseconds) delay which is fitted in the luminance channel to compensate for the time taken by chroma to pass through the narrow-bandwidth chroma circuits and thereby ensure exact horizontal registration of colour and luminance. There is no adjustment on the luminance delay and any chroma/luminance registration error is most likely to be caused by mistuning of the chroma amplifier. Luminance delay lines often suffer from dry joints causing a characteristic double-edging effect on the luminance signal (monochrome picture), the colour being unaffected, Photo 9.

SOUND CHROMA BEATS

The sound carrier is spaced 6 MHz from the vision carrier while the chroma subcarrier is spaced 4.43 MHz from it. Therefore there is a possible beat frequency inside the video range (1.5 MHz approx.) which could be generated by interference between sound and chroma. The i.f. strip response is carefully shaped to minimise this possibility. However severe misalignment or simple mistuning of the receiver can cause 1.5 MHz patterning on the coloured parts of the picture—see Photo 12.

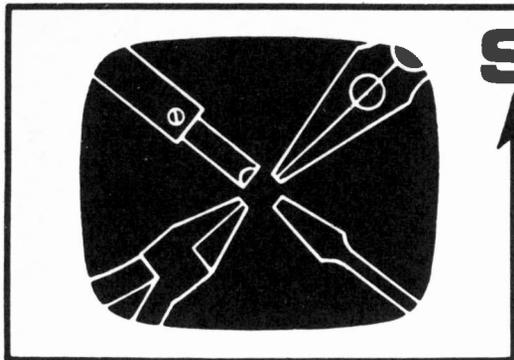The off-air colour photographs and material for this Supplement were provided by Caleb Bradley B.Sc.



SERVICING television receivers

L. LAWRY-JOHNS

ITT/KB VC200 CHASSIS

MODELS fitted with this chassis include the **KB** SV042, SV043, SV048, SV049, SV054, SV142, SV143, SV148, SV149 and SV154 and the **RGD** SV237 and SV337. It is a single-standard chassis designed to receive u.h.f. signals in Bands IV and V.

Servicing Facilities

Servicing facilities include a swing-down main board. This is held in the up position by two nylon catches which are moved outward to allow the chassis to pivot on its lower hinges. Similar nylon clips hold the tuner unit in position, so access to all parts likely to require attention is simple.

Tuner Units

One of two types of tuner unit may be found fitted—a UTA106 or a UTA108. In both the r.f. amplifier is a BF180 and the mixer/oscillator a BF181. The BF180 is the more likely one to fail, causing very poor reception marked by excessive grain. The BF181 tends to stop oscillating resulting in complete loss of signals; sometimes this initially affects one part of the band more than another (BBC-2 OK but no ITV for example). Transistor replacement is quite straightforward but requires a delicate touch to avoid moving other components—this would disturb the tuning.

Always check the transistor supply voltages before dismantling the tuner. The voltage at the 50 μ F decoupler should be 12V. If this is absent check back to the 20V line—R158, R160, D9 etc. The 20V supply is derived from the line output transformer so it isn't much good looking for voltages if there is a fault which affects the line output stage.

Mechanical Troubles

There are a couple of mechanical faults that can occur with these tuners. The UTA106 (Philips) tuner can develop poor reset accuracy due to the gear wheel at the end of the tuning capacitor shaft being loose—while the grub screw appears to be tight the screw does not mate with the shaft due to the fixing screw not bottoming on the shaft as a result of insufficient clearance in the grub screw hole. Remove the gear wheel and clear the hole so that the screw can move freely. Frequency drift and low gain with the UTA108 (Hopt) tuner can be caused by the brass collars fixing the lecher lines to the ceramic pillars developing a hairline crack—the ceramic pillars also support the tuning gang stators. Care-

fully inspect all the tuner sections and solder where necessary. This trouble could unfortunately make it necessary to have the tuner unit realigned.

Power Supplies

The forest of wire-wound resistors on the left side need sorting out in order to appreciate what doesn't work when one of them becomes open-circuit or overheats to denote trouble in a particular part of the receiver.

The mains supply is taken direct to the on/off switch, then neutral goes to chassis while live passes to a 1A delay fuse. When the fuse really shatters ("we heard a pop and everything went off"), disconnect C93, check for shorts and fit a new fuse. If the fuse holds fit a new capacitor in the C93 position, observing the a.c. voltage rating which is 300V—or 1kV d.c. From the fuse the supply is taken to R108. This leads a hard life and it is hardly surprising that it frequently fails and the set stops functioning. It is the surge limiter for both the h.t. and the heater diodes and gets a little hot under the collar therefore. R108 has a value of 20 Ω and is rated at 17W (minimum).

The supply then splits up to feed the h.t. rectifier D3 and the heater circuit rectifier D4. The output from D4 is negative and feeds the ballast resistors R105 and R109 (each 108 Ω) and the valve and tube heaters. The output of the h.t. rectifier feeds the various h.t. supply lines via a number of resistors each with its own smoothing capacitor. For example R102 feeds the audio output stage, smoothed by C83, whilst R103 feeds the field output stage, smoothed by C85. Hence either of these two circuits can cease to function while the rest of the set continues to work happily. The rest of the h.t. current has to pass through R106 however so that nothing can work if this becomes open-circuit despite the fact that h.t. is maintained to the field and sound output stages. Failure of one or more sections of the receiver is often due to one of these smoothing resistors being open-circuit, the precise one to check depending upon the symptoms.

R102 can overheat and damage the board if the PCL86 audio valve is faulty and passes excessive current: in later models R102 is mounted 15mm. off the board to prevent this.

Grid CRT Modulation

Probably the most interesting thing about this chassis is the fact that the c.r.t. is grid modulated.

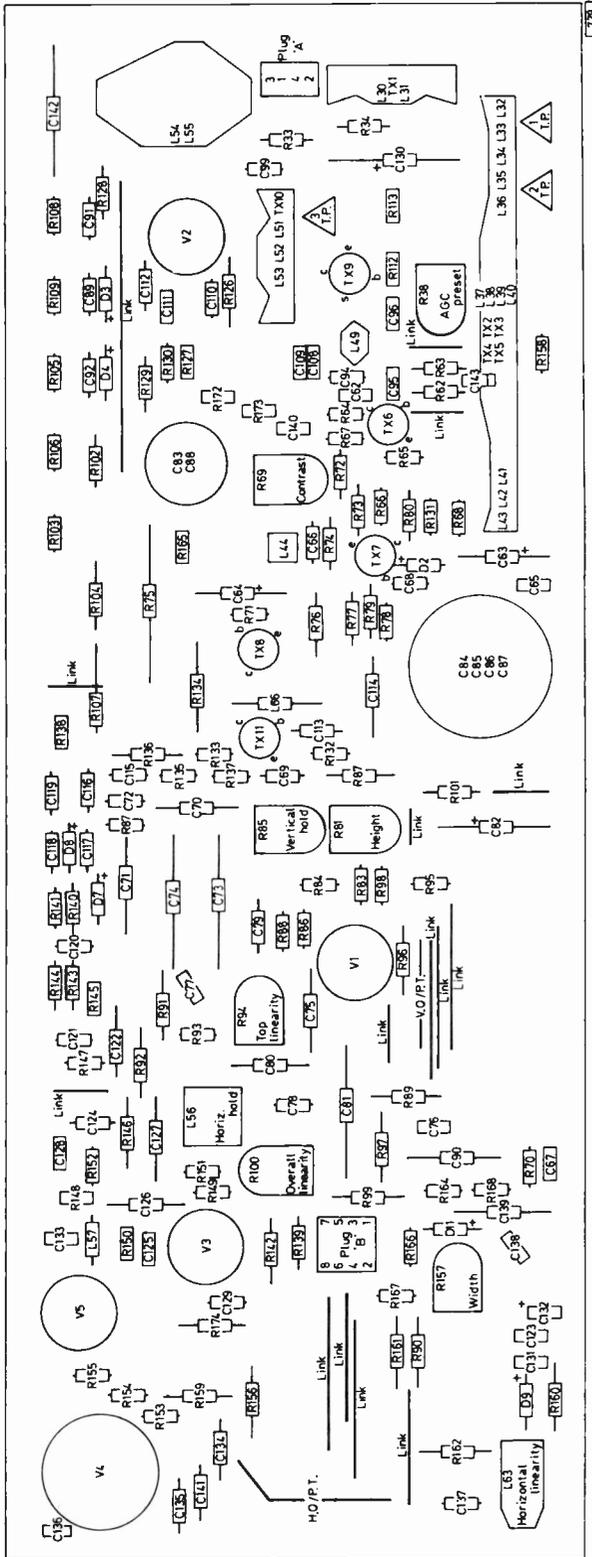


Fig. 1: Main printed board (component side).

The almost universal practice of modulating the

c.r.t. cathode is adopted to take advantage of the fact that the act of reducing the cathode voltage has the same effect as increasing the grid voltage and the first anode voltage together by the same amount, thereby gaining a little bonus when compared to swinging the grid voltage which of course leaves the voltage difference between the cathode and first anode steady. Thus when grid modulation is employed (as in colour-difference circuits) extra drive is required to produce the same contrast. There is a compensation with grid modulation however since peak white is obtained when the video amplifier is passing least current, and this you might think would result in a long and energetic life for the video output transistor. The BF119 has a habit however of becoming open-circuit, leaving a well lit screen but with no picture on it. This normally occurs when the receiver has been on for some time and the temperature in the cabinet has had time to rise.

If the complaint then is that the set performs well for a time and then loses the picture, leaving the screen well lit and the sound normal, it is quite reasonable to check the c.r.t. grid (pin 2) voltage: if this is about 200V suspect the BF119 and check it in the usual way. Suitable replacements are the BF179 or BF257. If the BF119's base voltage is below its correct working figure of 3-4V however the transistor is in order and the reason for this low voltage should be investigated.

The video output transistor is driven by an emitter-follower (BC172B), the signals developed across the emitter resistor R67 of this stage being applied to the contrast control, to R66 (a.g.c. generator input) and to R131 (sync separator input). This transistor (TX6) appears to be quite reliable.

The positive-going signals from the detector diode D1 are fed to the base of TX6 and via C95 to the sound channel.

Effect of IF Instability

At this point let us consider something which could well occur and which could be confusing. The fact that the writer has not encountered it so far doesn't mean that no one else has or will. The well known effect of oscillation in the i.f. stages, due say to an open-circuit decoupling capacitor, usually causes loss of sound and a brilliantly lit screen as the video stage is then overloaded: it is this latter condition which normally provides the clue and leads us hot foot on the trail of instability. Now spare a thought for what happens when an overlarge signal arrives at the video stage of a receiver in which the c.r.t. is grid modulated. The heavy signal drives the video amplifier into maximum current causing a large voltage drop across its load resistor (R75 here). The c.r.t. is therefore cut off as its grid voltage is low, and we are left with a blank screen instead of a bright white one to call attention to the instability. The v.d.r. R173 will prevent too much overloading of the video stage but the tube will still be cut off if the contrast and brilliance are left at their normal working settings.

Other Video Effects

The BF119 can cause a black "curtaining" effect which depends on the picture content and the contrast control setting, extending from the left-hand side of the screen to the centre. A replacement BF119 may cure the fault: alternatively its bias resistor R79

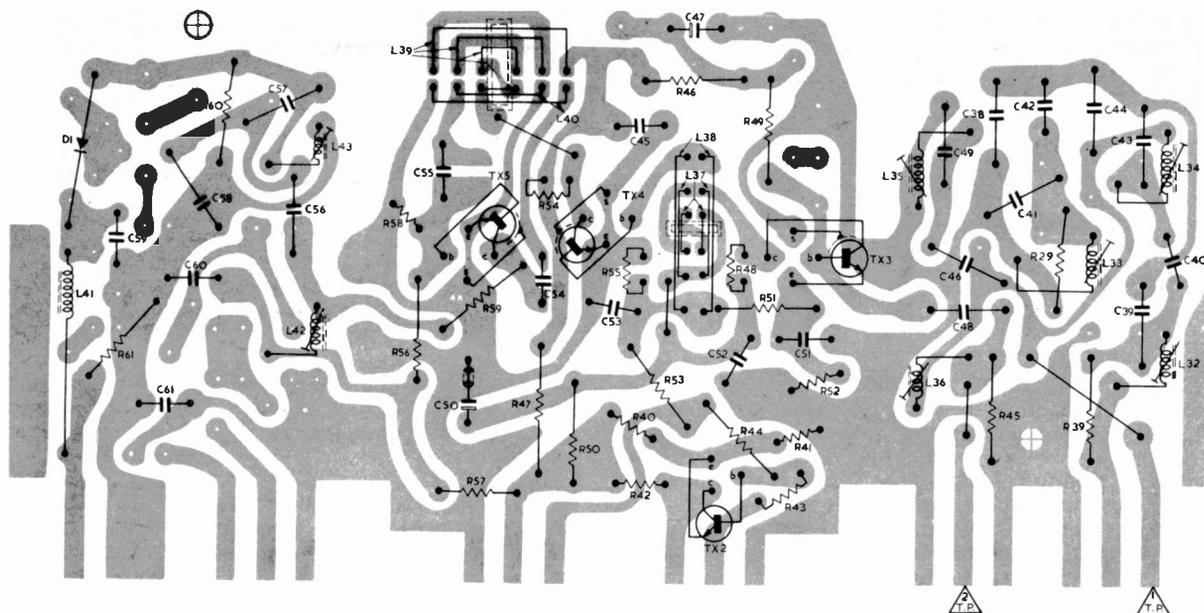


Fig. 2: Layout of the vision i.f. board—viewed from the print side.

can be increased from 100Ω to 120Ω. Do not make this value change unless this particular fault is present.

If the video drive is insufficient R63 may be reduced from 510Ω to 390Ω (5%). Change R161 to 1MΩ and R165 to 100kΩ.

IF Stages

As far as the vision i.f. transistors TX4 and TX5 are concerned there are unfortunately no emitter resistors across which to make convenient voltage measurements; voltage checks must be made in the collector circuits therefore where a higher voltage than specified indicates that the transistor concerned is not passing enough current either because its base voltage is too low or because the transistor is faulty.

In the case of TX5 the resistor across which a voltage check can be made is R57 (about 5V drop).

In the case of TX4 the voltage check should be made across R47 (about 10V allowing for signal

fluctuations). Now the voltage across R47 has a profound effect on the gain of the i.f. strip since it controls the base bias applied to the first vision i.f. transistor TX3 and hence its gain. The a.g.c. potential is derived from TX7 which operates in a fairly conventional way: it is switched on once each line by a differentiated flyback pulse from the line output transformer applied to its collector via C65 and D2, the extent to which it conducts each time depending on the amplitude of the video waveform applied to its base. As a result a negative charge proportional to the signal black level is established on C65 and filtered by R68/C63. This a.g.c. potential is applied to the base of TX4 which in addition to providing i.f. amplification acts as a d.c. amplifier/inverter producing a forward gain control potential across R47 to set the i.f. gain as we have seen. It is also applied to the a.g.c. inverter stage TX2 which produces the forward a.g.c. applied to the tuner unit. The level of the a.g.c. to the tuner is preset by R38.

CONTINUED WITH FULL CIRCUIT NEXT MONTH

COPING WITH ICs

—continued from page 545

Other ICs for TV

TBA570: Line oscillator used in continental sets, with d.c. control of sync and frequency.

TBA920: As the TBA570 but improved and with integral sync separator. A novel feature is its flywheel sync circuit with two-speed locking. A fast-acting frequency discriminator pulls the oscillator in from a wide range of mistuning. Once within frequency the fast-acting detector is replaced by a slow-acting phase discriminator which gives very clean verticals and a good steady sync. Provision is made so that by shorting down one pin the slow-acting circuit can be inhibited for VTR working.

SN76533N: Line oscillator plus sync separator from

Texas, offering similar facilities to the TBA920.


SN76013N: This 4W Texas i.c. is an audio output device with integral fan-shaped heatsink. Known colloquially as the "Flying Fin". Its gain and tonal range are adjustable by the addition of external components to the bias and feedback network on pin 2. Although the pins are conventionally numbered 1-16, pins 4, 5, 12 and 13 are missing. Peculiarities are a characteristic "plop" on switch-on, a hiss or crackle at zero volume and a variable quiescent current of typically 15-30mA. See Fig. 4.

These then are the main i.c.s in current TV use today. Our next instalment—"Four in a Box"—describes the latest four i.c. decoder using devices we have mentioned above. This decoder can be fairly described as a small printed circuit board with an i.c. in every corner, each pointing to its companion and saying "it's him!"

TO BE CONTINUED

THICK-FILM CIRCUITS FOR TV

Keith Pitt B Sc

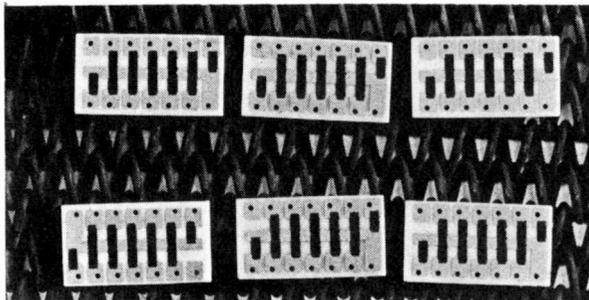

IN addition to silicon monolithic integrated circuits another technology new to television is beginning to take its place in our receivers, that of thick films. Although we will only meet this development in the form of modules of unfamiliar shapes it is of interest to know a little about it and what it can do.

Thick films got their name by contrast with thin films which are evaporated metal and metal alloy conductors and resistors. While these evaporated films are about 10 nanometres thick (0.4 microinches) thick films are between 10 and 35 micrometres (0.0005-0.0015in.) thick. They are made by first screen printing a paste on to a ceramic base or substrate and then converting the print into a glaze by firing under controlled conditions in a moving belt furnace at between 750 and 1000 deg C. Resistive, conducting and insulating glazes may be made in this way. (Dielectric films for capacitors are also possible but it is usually cheaper and easier to use miniature discrete components). Transistors and other components can be added either in a packaged form or as a chip.

Thick-film Technology

The printed glaze technology used for thick films has been borrowed partly from the artist and partly from china and porcelain manufacturers. The circuit required is first converted into a suitable layout—partitioned into layers of conductors, resistors and, if necessary, dielectrics for crossovers. Each layer is accurately dimensioned at ten times full size and then reduced photographically. A stainless steel stencil screen is used for all the stages.

A print of the pattern in the correct ink (or paste) is then transferred to an alumina substrate by means of a rubber squeegee. This is next dried in an infra-red oven to remove the solvents. At this stage the substrate may be fired immediately or alternatively taken back to the printing stage to print a second or even a third layer before firing. Generally the complete pattern of conductors and possibly crossovers is fired prior to printing the resistors. The conductors—usually a solderable mixture of silver and palladium—are fired in a cycle lasting about ten to twenty minutes with a peak at about 850 deg C. The resistive material is a mixture of precious metal oxides fired over a carefully controlled schedule taking about an hour with its peak close to 780 deg C.

The value of resistors produced from a particular paste depends on its chemical composition; by varying this a whole range of resistance from a few ohms to many megohms can be made. The process does not produce resistors right on target—they lie within a broad tolerance band. Fortunately however they

can be adjusted quickly and cheaply to within one or two per cent of the target value. Two techniques are used: first, abrading away parts of the resistor track by firing a jet of fine abrasive particles at it; secondly, cutting away part of the area by means of a laser beam. Both methods raise the resistance from the as-fired value. Lasers involve a large capital outlay but have been brought into operation recently mainly for the benefit of the television industry. The unit cost of a resistor adjusted in value this way is very low due to the fantastic speed of the computer controlled operation.

Once the resistor values have been adjusted and the thick-film network has passed electrical and optical tests it is ready for the final stages. Normally for the television industry any components or leads connected directly to a thick-film network will be soldered in place. Although there are special miniature transistors and capacitors available for use with thick-film assemblies it has been found that in practice their use makes thick films economically uncompetitive. As a result a compromise is made between space and cost saving, specially cheap versions of standard components being used instead. For one particular application a new minimum price ceramic capacitor was developed in order to remain competitive; each of the new components provided a price reduction of about five times compared with the standard types without significant loss of performance.

After device and lead attachment the completed thick-film module is resin dipped. Many of the modules in use in television sets are similar in format to those shown in Fig. 1 in which all the leads project from one side of the body and the package is mounted vertically and soldered into a printed circuit board—this is sometimes known as the single-in-line package.

Applications

For about four years several setmakers have been using multimillion quantities of discrete power resistors in thick-film form. These have values ranging from 0.1Ω to 56kΩ, dissipate up to 3W and have the pluggable tag harness which is the preferred terminal arrangement for the consumer industry. Subsequently the use of individual thick-film resistors was supplemented by networks of six resistors mounted on heatsinks for use as the red, blue and

The heading photograph at the top of the page shows thick-film resistor patterns emerging from a belt furnace after processing. These resistors are for providing bias on computer logic lines. Courtesy Middlesex Polytechnic.

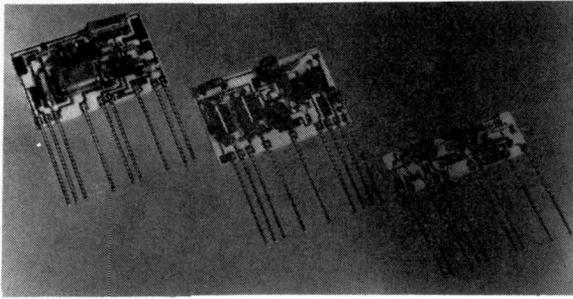


Fig. 1: Thick-film hybrid circuits for use in colour TV receivers. Courtesy Erie Electronics Ltd.

green output stage video loads (see cover photograph last month), the complete assembly dissipating 7.5W. The better thermal tracking of these resistor networks gives improved grey-scale tracking and consequently better colour reproduction.

From these the applications spread to high-value/high-voltage resistors including focus potentiometers. A thick-film glaze forms an ideal potentiometer track and a number of standard products have evolved in this field. Fig. 2 shows one commercially available range of thick-film focus assemblies for use in colour receivers. This has now become a standard line marketed by several thick-film manufacturers and has gained wide acceptance. Other applications in the potentiometer field are for field shift, line hold and shift and convergence circuitry.

More ambitiously a number of hybrid circuits have been developed for the television market. A hybrid circuit consists of a thick-film substrate with additional surface-mounted components. These assemblies are only acceptable of course if economically compatible with standard techniques. Improved reliability compared to conventional methods is another prime requirement, especially since over 60% of colour receivers are rented rather than bought. These requirements have been met and several hybrid modules are incorporated in the latest sets.

One of the first modules to appear was a field oscillator circuit; this was closely followed by a convergence system and circuitry designed for 110° tubes. Thorn Consumer Electronics (previously BRC) have been in the forefront of the application of thick films to consumer equipment as readers of TELEVI-

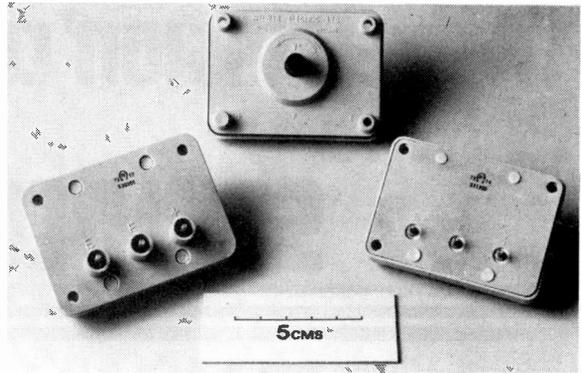


Fig. 2: High-voltage thick-film focus modules for use in colour TV sets. The circuit provides automatic focus voltage correction for wide variations in mains voltage. Courtesy Welwyn Electric Ltd.

SION will have observed—see recently reported news items. Even more recently AB Microelectronics have produced a thick-film varicap television tuner unit. This is typical of the new applications which are on their way to the market.

These examples show how the conventional component manufacturers have adapted themselves to take advantage of a newly developed technology in order to keep up with the demands of the electronics industry. Not only have thick films become widespread in television and radio, they are also beginning to spread rapidly into the automotive market.

Traditional resistor manufacturers such as Erie Electronics, Welwyn Electric and others have taken the initiative in developing thick films and applying them over a wide range of product fields. The number of television applications should continue to increase in the future. The only aspect which is not favourable is that faulty modules cannot be repaired—even in the factory—and represent a relatively high throw-away value compared with discrete components. They are easy to remove and replace however and do not therefore present any major servicing snags.

Current development work suggests that thick films will have wide applications in the r.f. field, including u.h.f., and it is possible that wired TV distribution systems will become one of the next big users. ■

FAULT FINDING GUIDE

—continued from pages 548/9

15 and 14 on the system switch and winding L501 on the line output transformer. Close inspection eventually showed that the lead-out wire from L501 had broken away from its tag. The broken lead was soldered to the tag and this restored normal working. The loss of sound was due to no h.t. voltage being available from the boost line to feed the triode section of the PCL83 audio valve—the feed is via R460, R425 and the triode anode load resistor R257 (2.7M Ω).

If the brightness control will not blank out the raster completely check the brightness control resistance chain—R120 (68k Ω), the brightness control itself (R105 500k Ω), the v.d.r. R106 and R107

(56k Ω) to chassis. Any change in resistance values here will upset the balance. Replace any resistor whose value has changed—check the v.d.r. by substitution.

The design of this chassis with its drop-off resistors and three fuses encourages a systematic approach to servicing. Remember that five minutes' close physical inspection of the printed panel for hair-cracks, dry-joints, discoloured resistors, leaking electrolytic capacitors, corroded valve bases and even the tell-tale white top of a cracked valve can save hours of plodding work with a meter.

When you make a soldered joint on the dark, rear side of the panel check it twice—and then again, preferably with a good light and a dentist's mirror—to ensure that it is a good, clean firm joint.

NEXT: BRC 1400 CHASSIS

THE 'TELEVISION' COLOUR RECEIVER

PART 18

SERVICE DATA

THE voltage data given this month for the main modules in the colour receiver should with the key waveforms shown in Figs. 1 and 2 go a long way towards sorting out any servicing problems. Data for the i.f. module was given in R. Fisher's article last month. The use of the information given depends—as with all servicing data—on the set-up conditions and the instruments employed. This should be clearly understood when you come to interpret the results you obtain from checks on your receiver.

Test Conditions

The voltage readings given are the averages of those obtained from three receivers—the prototype and two constructors' models: they are the closest that we can give at this moment as being "norms". The meter used for all the measurements was a Philips 50k Ω /V "Multitester". Meters providing a greater loading (e.g. 20k Ω /V) and those with a different meter protection system will inevitably give different readings at particular points—notably at the transistor base and emitter connections. All this is to be expected: remember that in any fault-finding procedure using voltage checks one is looking for a similar—or dissimilar—conduction state and that normally the degree of conduction is more important than the precise voltage.

All voltage measurements were taken with a mains input of 240V. Where only one voltage is given for

a particular point this is the voltage under normal operating conditions, with the receiver correctly set up and a 95% colour bar input. Where two voltages are given the second is the normal signal voltage and the first the no-signal voltage obtained with no r.f. input to the receiver and the saturation, contrast and brightness controls reduced to zero.

Waveforms

The waveforms shown (Fig. 1 and 2) are practical ones—not idealised—and were also obtained with a 95% colour bar input and with the receiver adjusted for a normal display. The possibilities of video signal level variations are greater than with simple voltage measurements because the former depend much more on the quality of the signal, the way in which the receiver has been set up and the drive levels required for the particular colour tube being used. The instrument used for monitoring the waveforms is not too important—the waveforms shown were taken using a Tektronix 7704A with 7A19, 7B92 and P6006 $\times 10$ probe.

Waveforms have not been given for the convergence circuitry. The waveforms and d.c. potentials here have in our experience been found to be of little value in fault-finding and indeed may be downright confusing. If readers prove to have any real difficulty in this area we will examine it more closely however.

VOLTAGE MEASUREMENTS

Decoder		Tr 4	base	3.45V 3.35V	
Tr 1	base		emitter	3.15V 3.05V	
			collector	14.8V 14.7V	
	emitter				
collector		Tr 5	base	5.15V 5.1V	
			emitter	4.65V 4.55V	
Tr 2	base		collector	15.1V 14.9V	
	emitter	0V			
	collector	0.02V			
Tr 3	base		Tr 6	base	3.6V 3.4V
				emitter	3.05V 2.95V
	emitter			collector	18.2V 17.6V
collector					

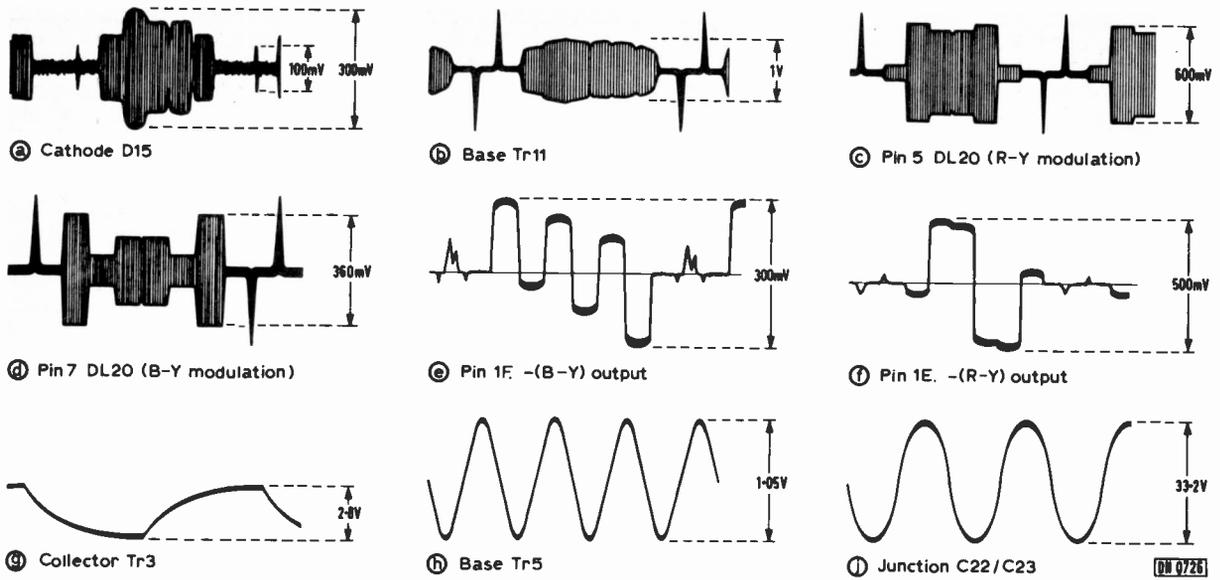


Fig. 1: Key decoder module waveforms.

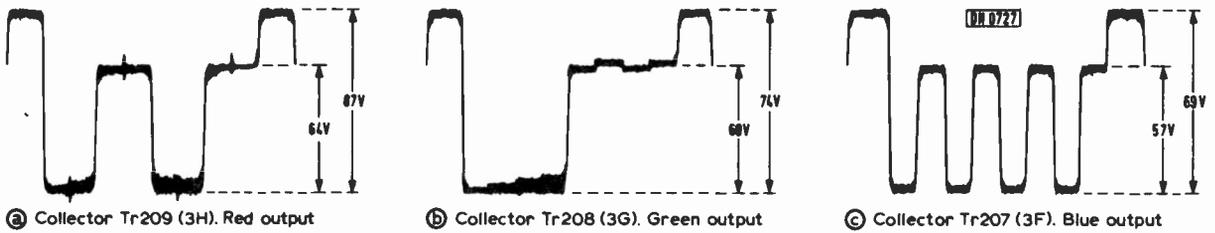


Fig. 2: RGB module waveforms.

Tr 7	base	0V
	emitter	2.7V
	collector	0.02V
Tr 8	base	2.2V
	emitter	18.3V
	collector	18.2V
Tr 9	base	0.4V
	emitter	0V
	collector	5.5V
Tr 10	base	-1.4V
	emitter	4.8V
	collector	0.02V
Tr 11	base	3.9V
	emitter	19.8V
	collector	11.3V

RBG Module

Tr 201	base	0.9V
	emitter	0.23V
	collector	12.1V
Tr 202	base	0.85V
	emitter	0.15V
	collector	3.4V
Tr 203	base	0.85V
	emitter	0.15V
	collector	3.4V
Tr 204	base	3.3V
	emitter	2.6V
	collector	14.3V
Tr 205	base	3.3V
	emitter	2.6V
	collector	20V
Tr 206	base	3.5V
	emitter	2.8V
	collector	13.9V
Tr 207	base	2.6V
	emitter	2.1V
	collector	118V

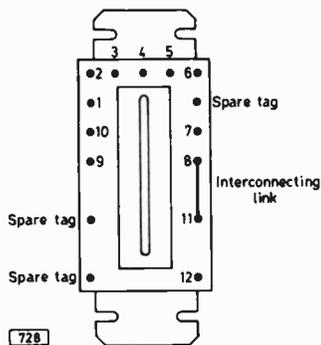


Fig. 3 (left): Tag connections to the line output transformer supplied by E. J. Papworth and Son Ltd. The $-8V$ winding must be added—or see suggestion in column on right.

Tr 208	base	2.6V
	emitter	2.1V
	collector	118V

Tr 209	base	2.8V
	emitter	2.3V
	collector	109V

Timebase Module

D 303	cathode	0.05V
-------	---------	-------

SCS 301	cathode	0.05V*
	cathode gate	0V*
	anode	4.1V*
	anode gate	6.2V*

*All voltage measurements on SCS 301 should be undertaken with great care. Meters of less than $20k\Omega/V$ should not be used at all on the anode or anode gate whilst other meters should be connected before the receiver is powered. Do not jab the meter leads on to any pin of SCS 301 while the stage is powered.

Tr 301	base	0.9V
	emitter	0.4V
	collector	63V

Tr 302	base	0.05V
	emitter	0V
	collector	1.1V

Tr 303	base	1.1V
	emitter	1.3V
	collector	0V

Tr 304	base	1.25V
	emitter	0.7V
	collector	19.6V

Tr 305	base	20.9V
	emitter	20.2V
	collector	40V

V301	pin 1—triode anode	225V
	pin 2—pentode grid	—55V
	pin 3—pentode screen	222V
	pin 6—pentode anode	173V
	pin 7—pentode cathode	0V
	pin 8—triode cathode	4.5V

V 302	pins 1, 8—grid	—76V
	pins 3, 6—screen	215V
	pin 9—cathode	2.2V

Power supplies

Some readers have expressed concern about the operating temperature of the mains transformer and have experienced difficulty in achieving the correct voltage and current ratings on load at the power supply output terminals. The manufacturers of the transformer supplied in Pack 18 have stated that "due to the excellence of the insulation these transformers are able to run safely up to $100^{\circ}C$ ". They state that even at $120^{\circ}C$ they should still operate satisfactorily.

We have conducted further tests on samples and are of the opinion that as with most transformers running at high temperatures magnetic saturation can occur. There is also the possibility of poor regulation when used under heavy loading conditions. There are two possible solutions to such problems in this project:

(1) To remove some or all of the low-voltage loads and operate them from a separate additional transformer.

(2) To replace the transformer with one having a higher power rating—and inevitably of much greater cost.

The first suggestion can be carried out by using an additional transformer to supply the c.r.t. heaters with 6.3V at 0.9A.

A thermistor such as the VA1033 will provide some protection against a surge on switch on. The transformer can be a common 1A type or the special c.r.t. type (RS Components). A rectifier diode is not necessary of course in this case. In addition a 40V d.c. supply should be made available separately for the field timebase, requiring a 33V to 40V 1.5A to 2A transformer operating with R508, C507 and another 100V 2A bridge rectifier. Change FS503 to a 1A type after removing the field timebase feed from the original circuit. The 24V winding together with R516 and D505 could be used to supply $-8V$ for the decoder panel in conjunction with an 8V zener diode connected across 6Q and 6C (cathode to chassis) plus C604. The VA1033 thermistor R517 is not necessary in this circuit.

If the h.t. voltage from the power supply is insufficient for correct operation of the boards on load the following suggestions can be tried: (1) In the case of the line timebase feed from 6G reduce R505 to 25Ω . (2) In the case of the feeds from 6H and 6I reduce R506 to $1k\Omega$.

Full details will be given next month in our new series *TELEVISION Colour Receiver Forum*. Constructors who have successfully completed the published receiver are invited to contribute brief details that could be helpful to other constructors. These will be carefully studied and we reserve the right to delete or amend any parts. Our aim is to provide a service to assist constructors who may be having difficulties.

"TELEVISION" COLOUR RECEIVER FAULT FINDING ADVISORY SERVICE

Adopt the following procedure:

- (1) Complete the coupon, supplying complete fault symptoms and details of test measurements and/or oscilloscope traces that you have made and the results.
- (2) Send your coupon and letter and two stamped self-addressed envelopes to: Fault Finding Advisory Service,

"Television", Fleetway House, Farringdon Street, London EC4A 4AD.

Letters will be dealt with in rotation and you should be prepared if there is a delay. If you have followed the instructions here you should receive an acknowledgement bearing a reference number which must be quoted in all further correspondence.

There may be occasions when an answer is best given by telephone, *but please do not ring us, we will ring you.* If you think that communication can be done better by telephone please write your evening/weekend telephone number in full on the coupon where stated. **Warning:** If we choose to telephone to help you or to ask for further information we may make a "transferred charges" call, i.e. at your expense. If you are not prepared to accept such a call do

not enter your telephone number. It would be helpful if you have access at the time to details of your receiver. **WE CANNOT ANSWER QUERIES BY TELEPHONE IN ANY OTHER WAY.**

Note: The service is being made available in this form until November 30th 1973 only, at which time the situation will be reviewed in the light of experience.

Matters Arising

In the event of it being necessary to replace the horizontal shift potentiometer R354 a wire-wound type should be used.

Electrokit have moved to new premises at 8 Cullen Way, London NW10.

**"TELEVISION" COLOUR RECEIVER PROJECT: FAULT FINDING
ADVISORY SERVICE**

Please complete the whole form in ink in capital letters, attach to your letter describing fault symptoms and send with TWO stamped self-addressed envelopes to: Fault Finding Advisory Service, "TELEVISION", Fleetway House, Farringdon Street, London EC4A 4AD.

NAME

ADDRESS

FOR OFFICE USE ONLY

1st Ref.

2nd Ref.

3rd Ref.

1st Ref. number..... (if known).

BRIEF FAULT SYMPTOMS (use additional paper if necessary) :

TEST PROCEDURES CARRIED OUT:

PLEASE TELEPHONE ME BY TRANSFERRED CHARGE CALL DURING THE EVENING OR WEEKEND BETWEEN (times)..... ON TELEPHONE NUMBER.....

I UNDERSTAND THAT THE PHONE CALL MAY BE CHARGED FROM CORNWALL OR LONDON. I HAVE READ AND UNDERSTOOD THE CONDITIONS OF THE ADVISORY SERVICE AS GIVEN IN THE AUGUST 1973 ISSUE OF "TELEVISION". I ALSO UNDERSTAND THAT THE MAGAZINE PUBLISHERS CANNOT BE HELD RESPONSIBLE FOR ANY LOSS OR DAMAGE TO THE COLOUR RECEIVER.

SIGNATURE.....

DATE.....

For Office use only.

DATE.....

NAME.....

REF

Dear Sir,

We acknowledge receipt of your form for the Fault Finding Advisory Service. This is being dealt with. Please quote the above reference number in all communications on the Colour Receiver Project.

Yours faithfully,
FOR TELEVISION MAGAZINE



WELL over half a million visitors were expected to pass through the doors of the Palace at the Funkturm, Berlin between August 31st and September 9th. The International Radio and Television Exhibition organised by AMK Berlin was in fact much more than just another exhibition: it was part of a large operation designed to show the world what Berlin has to offer. And of particular significance is that it celebrated the 50th anniversary of the commencement of broadcasting in Germany.

TELEVISION was privileged to visit many of the industry's Berlin based organisations recently, including the Sender Freies Berlin (SFB) broadcasting studios where automatic computer controlled television cameras and lighting equipment were demonstrated. SFB sends out television programmes on Channel 7 (v.h.f.) and Channel 39 (u.h.f.) in addition to three v.h.f. and two a.m. radio programmes.

Colour Sets

The colour television sets at the exhibition were overwhelmingly 110° types. It is interesting to contrast the German and UK television set markets. In the UK the custom of renting sets has assisted the rapid advance in the number of colour set installations. This has meant that in order to try to keep up with the escalating demand UK setmakers have concentrated to date on increasing production of their first single-standard chassis designed around 90°

colour tubes. In Germany the vast majority of sets are sold individually and the emphasis has been much more on the luxury end of the market—the standard tube size is 26in. and touch-sensitive tuning, remote control and so on are common features. The result is that production has been lower in volume than in the UK though the introduction of new techniques, especially 110° designs, has been much more rapid.

There are two basic approaches to 110° scanning—the use of thick- or narrow-neck tubes. German production seems to be about 80% thick neck to 20% narrow neck. The thick-neck designs use valve, transistor or thyristor (see TELEVISION March 1972) line output stages; with thin-necked designs the thyristor line output stage is generally adopted.

Remote Control

Varicap tuners with touch-sensitive tuning arrangements are commonly used. The use of sensor systems makes it easy to introduce digital control techniques. For example ultrasonic remote control, a very popular feature in Germany, enables the brightness, colour intensity, volume and programme selection to be adjusted through switching in stages up or down under the control of the contact electrodes.

Audiovisual Switch

Many German colour sets are being sold as suitable for use with videotape machines. The main problem here is that of line synchronisation. For good off-air performance the line oscillator in a TV



The photograph used in our heading at the top of the column shows the SFB transmitting tower, Berlin.

The control console in the new SFB studios—the complex programmer is in the centre.

set should have a small pull-in range so that the noise immunity is good. With a narrow pull-in range however sets will not readily synchronise with the signal from a videotape machine. The answer is to widen the pull-in range by reducing the flywheel sync time-constant when operating with a videotape signal. Such sets are sold with an "AV" (audiovisual) switch on the user control panel to enable this to be done or with provision to add a switch for this purpose later on.

Video Recording

Videocassette and disc equipment has aroused a great deal of interest in the German market and several videocassette recorder/playback machines are already in production and on sale.

Seven German companies have introduced videocassette machines and some 40,000 machines are said to have been produced so far. Machines of this type were first shown as laboratory prototypes only two years ago at Berlin. Many of the machines shown had built-in tuners and timing switches. The system is capable of providing stereo sound but this has not so far been introduced.

TED Demonstration


Telefunken demonstrated the production version of the Teldec (Telefunken-Decca) videodisc system which is to be made available under the more affectionate name TED. An earlier version of this system was described in detail in the December 1971 issue of TELEVISION: at that time the 21cm. flexible disc with a groove concentration of 130 grooves per millimeter gave approximately five minutes' playing time of monochrome programme material. Since then colour has been added and the latest development is to increase the groove density to 280 grooves per millimeter to provide ten minutes' playing time per disc. The flexible disc is held against a pressure-sensitive transducer, which is held at a fixed height, by a cushion of air beneath the disc. The system uses frequency modulation for the recorded signal. Although the system is confined to playback only, its low cost is expected to make it an attractive commercial proposition. The colour picture quality that we could see was excellent and the demonstration showed how multiple-shape picture insets could be employed. Superimposition capabilities were also shown and a useful feature is the ability to provide short excerpt repeats and stills selected by the user.

CCS System


A video recording system based on a Super-8 film scanner is being developed by NordMende and a small version was demonstrated. The intention is to go into production with this system early next year. NordMende call it the CCS (Colourvision Control Speed) system—since unlike cinema projection the film transport mechanism used in this system operates at a constant speed.

Organisation

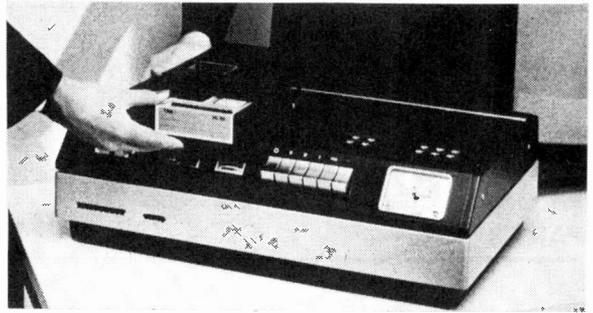
The organisation behind the exhibition was of a very high standard—let's hope British exhibition organisers took some note of it. A new computerised information retrieval system based on the



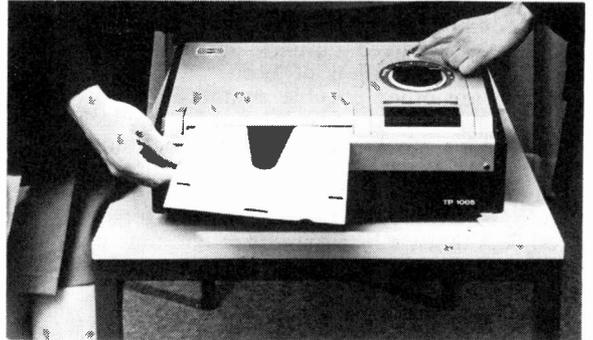One of the videocassette tape recorders now in production in West Germany.



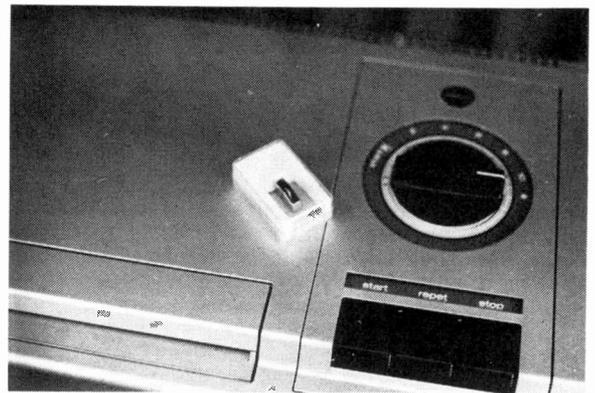The Telefunken TP1005 "TED" videodisc player. The 21cm. disc in its sleeve is inserted in the slot at the front of the player. The only controls required for operation are the start, stop and repeat buttons.



This exclusive "Television" photograph shows a close-up view of the TED player with the pick-up cartridge in its box on top.

Siemens 4004//135F computer which is installed remotely at the Berlin Dattel centre was used to help visitors find their way around the 23 halls and four pavilions. Two data terminals, screen viewers and printers were in operation at each of the three main entrances.

Full credit must go to AMK Berlin headed by Horst-Ludwig Stein the Managing Director and Wolfgang Nebe the Chairman of the Exhibition Committee. TELEVISION was represented in the Technical Press Section where visitors could see samples of recent work. ■

receiver debugging

E. J. HOARE

PART 3

IF AND VIDEO RESPONSES

A TELEVISION receiver's picture quality depends to a very large extent upon the response of its vision i.f. and video circuits. Any deficiencies in the design or alignment of the circuits will inevitably cause corresponding defects on the picture and these will show up as blurred outlines or multiple images—usually a combination of both.

There are other possible complications of course such as patterning caused by the presence of too much colour subcarrier at 4.43MHz or colour/sound beats at 1.57MHz. These can be dealt with fairly easily however as we shall see later. The main problem is to avoid the rings, smears, overshoots and preshoots that we listed in our programme of picture quality testing in an earlier series (see March 1973 issue).

If you look at even the best TV receivers you are likely to see traces of these defects. On bad receivers they are so obtrusive that however well designed the rest of the circuitry may be the picture is spoilt. There are obviously some fundamental problems involved in i.f. circuit design and in point of fact it is exceedingly difficult even to specify in proper engineering terms exactly what shape of response curves we want let alone how in practice to achieve them.

Since there is no short cut—no way of telling you just what i.f. and video responses to use in order to be sure of getting clean, sharp, picture detail—we shall have to try a different approach. Let us consider what sort of signal is present in the i.f. channel and what sort of distortion it is likely to suffer in its passage through several tuned circuits including a number of highly selective traps. Then perhaps we shall understand the nature of the problem a bit more clearly and see how to go about overcoming specific picture defects.

IF Sidebands

Suppose we take an item of picture detail consisting of a white line on a black background. The video information (drive to the c.r.t.) consists of a voltage that goes black-to-white-to-black, i.e. a squarewave in sympathy with the brightness of the image. See Fig. 1. The transition from black to white and back again is as nearly instantaneous as is possible in a television system and the edges of the squarewave are vertical. What sort of i.f. signal does this give rise to? For an answer we turn to the well known Fourier Analysis. We do not need to go into the details of this: put simply it says that any waveform can be made up by adding together a series of different sinewaves. These consist of a fundamental sinewave of a certain amplitude and frequency together with harmonics of this sinewave each having specific (clearly defined) amplitudes and phases.

Now this may sound a bit complicated but reference to Fig. 1 should dispel any mystery. It shows how a half cycle of sinewave can rapidly approach a squarewave shape by the addition of small amounts of only its third and fifth harmonics. To get a proper squarewave in television terms we need high-order harmonics in order to get the steep sides. And of course the frequency of the fundamental sinewave is that corresponding to a small part of one scanning line, i.e. a large multiple of 15,625Hz. The high-order harmonics will therefore extend out to about 5.25MHz. Thus the vision i.f. carrier at 39.5MHz has to be modulated with other sinewaves of many different amplitudes, frequencies and phases in order to convey accurately the picture information we require. This is a simplified explanation of "sidebands". In this case they extend from 39.5MHz—5.5MHz to 39.5MHz+1.25MHz, i.e. 34.0MHz to 40.75MHz, because the television signal is single sidebanded (SSB)—there is only a vestigial sideband on the upper side.

Referring to Fourier and his famous analysis again, the most important single point to emerge from our discussion so far and the waveforms shown in Fig.1 is this: we are interested in the amplitude and *phase* of each *component* of the i.f. signal in the i.f. passband; any distortion of the various signal components will alter the shape of the waveform produced at the vision detector.

Single-Sideband Operation

To make optimum use of the frequency spectrum available for television broadcasting a form of single-

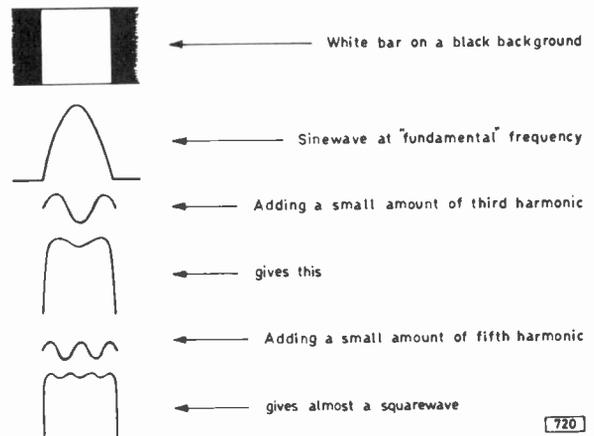


Fig. 1: A reasonable approximation to a squarewave (corresponding to a white bar on a black background) can be obtained by adding small amounts of third and fifth harmonic components to the fundamental sinewave.

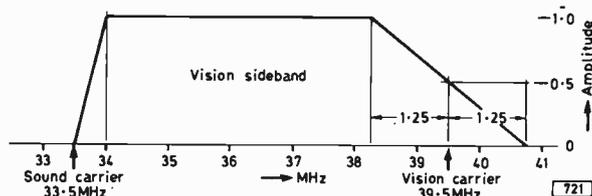


Fig. 2: The i.f. response of an "ideal" receiver matched to the vestigial sideband transmission. (Note that an amplitude of 0.5 = -6dB.)

sideband transmission is used. This is not true single-sideband operation because a vestigial sideband is present on the lower side (r.f.) or higher side (i.f.). Fig. 2 shows the i.f. response of an "ideal" receiver: the theory is that the response matches precisely the characteristics of the vestigial-sideband transmitted signal. Notice that the area of the ideal i.f. response above the vision carrier (the upper sideband) is equal to the area missing from the lower sideband: thus the overall response is equal to one complete full-amplitude sideband.

It is very difficult in practice to achieve this waveform shape exactly and it is rather doubtful whether it would give good picture quality anyway. In normal designs the i.f. response is nicely rounded, with the level at the vision carrier about 5 to 8dB below the peak of the response. It is a fairly good approximation to the ideal and avoids all sorts of circuit complexities and poor phase response which would be involved in any attempt to approach the ideal more closely.

This business of vestigial-sideband operation is rather unfortunate. You can see at once that the shape of the i.f. response is going to be critical in any quest for good picture quality. The part near the vision carrier must be shaped very carefully if a complete and undistorted sideband is to be obtained. If the slope and/or the level near the vision carrier are badly chosen there will be a bump or a dip in that part of the sideband corresponding to low video frequencies and the video response at the detector will be correspondingly distorted. A small dip is not too troublesome but a bump means that the circuits have too much response at low video frequencies and this will show up on the picture as a smear at the right-hand side of large black areas. (See Part 2 of the previous series, March 1973.)

This is the first clue in the process of hunting down the causes of poor picture responses. If you have a smear, check the slope of the i.f. response near the vision carrier. Try trimming the appropriate i.f. circuits in order to obtain a bit more attenuation at the carrier frequency. If 8dB of attenuation does not cure the trouble then either the slope of the response is wrong or else the video output circuit

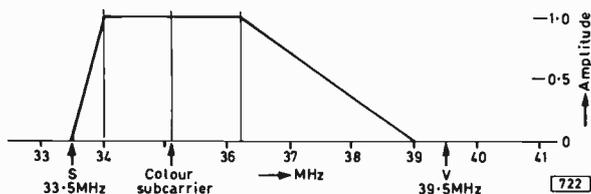


Fig. 3: The asymmetrical chrominance sidebands, shown at i.f.

has a poor amplitude response—more about that later. Meanwhile let us see what other factors govern the shape of the overall i.f. response before considering the distortions this tends to introduce.

Colour Subcarrier

The colour subcarrier has a centre frequency of 4.43MHz modulated on to the vision carrier, so the corresponding i.f. is $39.5 - 4.43 = 35.07$ MHz. The sidebands are fully maintained out to 5.5 and 3.13 MHz, i.e. 34.0 and 36.37MHz at i.f.—see Fig. 3. Now the sound carrier is at 6.0MHz, i.e. 33.5MHz i.f., so clearly we have a selectivity problem. There are two ways of extracting the colour subcarrier for feeding to the decoder. The best way and (as always) the more expensive is to use a separate chrominance detector with its own i.f. selectivity having a bandwidth of about 2.0MHz centred on 35.07MHz. It must have a high attenuation at the sound i.f. (33.5MHz) and preferably about -20dB at 37.3MHz to avoid luminance crosstalk. The response at the vision carrier must be maintained however in order to make detection possible. This approach involves some fairly clever filter circuits and is a rather complicated one.

A simple technique which is quite widely used employs a common detector for the sound, chrominance and luminance carriers. The response has to be attenuated in the region of the sound carrier, and in practice it is not very easy to avoid some attenuation at the colour subcarrier frequency also if a smooth response curve is to be achieved. Making a virtue of necessity it is usual to aim at an attenuation of 6dB. This produces quite a smooth chrominance response which can be compensated by an appropriate inverse slope at the input to the decoder to give an overall flat response.

The 6dB attenuation at the colour subcarrier frequency reduces the amount of 4.43MHz patterning which occurs in areas of the picture of high saturation. Most designers add a 4.43MHz filter in the luminance channel to reduce this patterning still further. A small loss of picture resolution is inevitable and a compromise has to be chosen according to individual preferences.

Sound Attenuation

It is essential to attenuate the amplitude of the sound carrier before the i.f. detector. The minimum amount of attenuation is determined by the need to ensure that the sound carrier is smaller than the space left by the minimum excursion (corresponding to peak white) of the vision carrier—see Fig. 1, page 444, August issue. If this is not the case the sound carrier will be severely amplitude modulated by the picture information. This produces a buzz on sound dependent upon picture content. Although f.m. sound limiters have a very good performance there is no point in asking them to achieve the impossible in removing large amounts of unnecessary amplitude modulation.

This consideration makes it desirable to attenuate the sound carrier by about 26dB relative to the peak of the response. This is adequate for monochrome receivers but for colour ones there is an additional requirement. The vision detector output will include a component produced by intermodulation between the sound and colour carriers, i.e. $6.0 - 4.43 = 1.57$

MHz, and this produces very coarse patterning on the picture. On monochrome receivers it is not too obtrusive and a sound attenuation level of 26dB is acceptable from this point of view also. On colour pictures the pattern is particularly annoying and in order to reduce it to an acceptable level the sound attenuation should lie in the range 30-40dB.

Adjacent Channel Rejection

It is necessary to be able to operate receivers in areas where a programme is transmitted on an adjacent channel, i.e. one of the two channels next door to the one you want to receive. This situation is avoided in most areas by careful transmitter planning and location but it does exist in a few places. It is particularly likely to occur in areas of high ground or where a long sea path is present between an unwanted transmitter and the receiver—the sea allows good signal propagation, hence the trouble.

In order to prevent a sound or vision carrier from an adjacent channel breaking through into the wanted i.f. passband a high attenuation is necessary at intermediate frequencies corresponding to these carriers. To protect against the adjacent f.m. sound carrier an attenuation of about 40dB is desirable at 41.5MHz while to protect against the amplitude modulated adjacent vision carrier an attenuation of about 50dB at 31.5MHz is needed.

Overall Response Shape

There are a few other refinements which can be built into the specification of an overall i.f. response but apart from commenting upon the need to avoid "returns" of the response outside the band let us summarise the requirements discussed so far. Fig. 4 shows a typical overall i.f. response curve with the appropriate attenuation at each carrier frequency and a smooth shape.

The importance of a smooth shape is this: any sudden discontinuity in an i.f. response is associated with a phase change at the frequency concerned and this may cause a displacement of the Fourier components of the signal, and hence distortion, as we discussed earlier.

Having chosen a suitable overall i.f. response curve shape the question is—will this give a good picture? The answer depends to a large extent upon the "group delay" performance.

Group Delay Response

Any sinewave passing through a tuned circuit suffers a delay, the amount by which it is delayed depending upon the bandwidth of the circuit. A narrowband circuit causes more delay than a wideband one. Hence in colour receivers a delay line is provided in the wideband luminance channel so that the total luminance signal delay time is equal to that of the narrowband chrominance channel. This ensures that both the luminance and the chrominance information arrive at the c.r.t. screen at the same time and therefore register correctly.

Now if you feed an i.f. signal with all its sidebands at their various frequencies to an ill-designed i.f. strip you will be in trouble: different frequencies will suffer different delays. Thus information corresponding to a sharp black-to-white transition or step response entering such an i.f. strip would reach

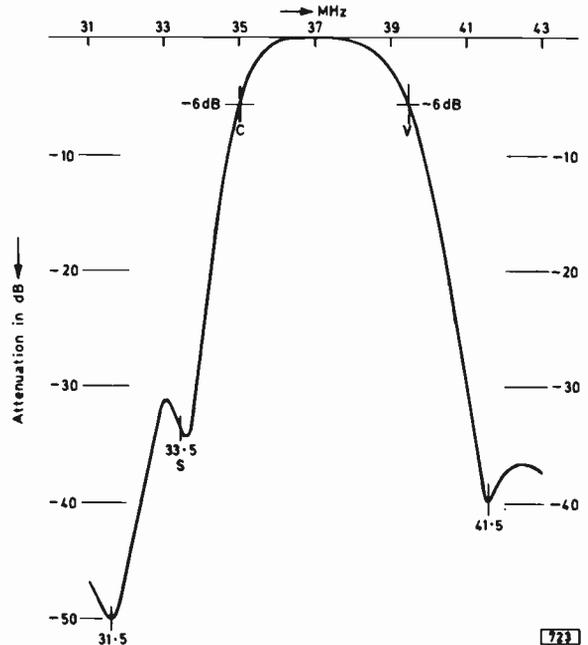


Fig. 4: A good i.f. response curve.

the detector spread out over a small period of time. The sharp transition thus becomes blurred. Sometimes the different frequencies are delayed in bunches and you then get overshoots.

A good i.f. strip is designed not to have constant phase angle characteristics but constant time delay instead, so that all frequencies are delayed by the same amount. They then all arrive at the detector at the correct instant in time. In practice it is almost impossible to achieve this over the whole i.f. passband but the best i.f. designs get near to it. They are said to have good "group delay" performance.

Fig. 5 shows a typical group delay curve for a complete i.f. strip. You will notice that at high video frequencies (34MHz) the time delay is 200nsec (0.2μsec) different from that at the carrier (which corresponds to 0Hz video). How important is this? Well a medium sized c.r.t. has a picture width of about 400mm, corresponding to a line scanning time of about 52μsec (flyback time is usually 12μsec giving 64μsec per line). So the picture displacement caused by 0.2μsec delay is $0.2/52 \times 400 =$ approximately 1.6mm. This can clearly not be ignored, but

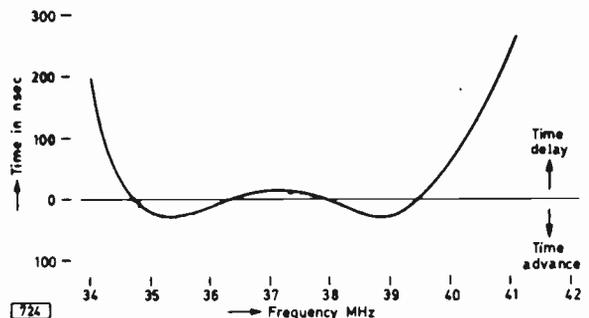


Fig. 5: A group delay curve for a complete i.f. strip.

since it occurs only at high video frequencies which cannot be properly displayed the effect on the picture will not be too serious.

Reducing IF Distortion

It is clear now that there are two fundamental requirements of any i.f. strip, bearing in mind the Fourier make-up of the signal. First each sideband component of the signal must reach the detector at the correct *amplitude* in relation to all the other signal components; secondly it must reach the detector at the right *time*. Any failure to meet these two requirements will result in distortion of the detected video signal, causing rings, smears, overshoots or preshoots. Preshoots of course are caused by a time advance instead of a time delay relative to the carrier.

Now comes the important question—how do we avoid these amplitude and time distortions? There is unfortunately no way of giving a complete answer but we can at least explore a few useful do's and don'ts.

Fig. 4 showed a good basic overall i.f. response curve. Note the attenuation of 6dB at the vision carrier frequency and the smooth slope above and below this frequency. Attenuations of less than 6dB at this frequency usually give a smeary picture because there is too much i.f. response relative to the h.f. response at about 35MHz when the vestigial sideband is added to the main sideband. So here is our first point: if there are smears on the picture pay special attention to the i.f. alignment or circuit design where it affects the response in the region of the vision carrier. If adjacent channels are not present at your particular location the adjacent sound trap at 41.5MHz can be detuned upwards to give a smoother i.f. response curve.

Our next point concerns the response at the upper end of the video passband in the region of the colour subcarrier, i.e. video frequencies of 4.5MHz. The curve here (34.5-35.5MHz) must be smooth as shown in Fig. 6. It is better to sacrifice a little bandwidth and have a smooth curve than to have a wide bandwidth and a steep flank to the response.

A steep response near a trap frequency nearly always involves a sharp change of phase and hence a group delay (or time) error. This causes overshoots or rings.

By the same token we come to our third point. Any sudden discontinuity in the response curve means a phase change and hence a time error. Now the overall curve may look very nice, but if it is achieved by adding together the responses of two or three stages with one filling in the gaps in another

you are asking for trouble. The amplitudes may add up nicely but the time errors will probably *not*. The curve of each individual stage in the i.f. strip should be as smooth as possible.

Ideal Design

The ideal design has quite a large number of separate i.f. stages, each one having a smooth response and contributing only a moderate amount of selectivity. The large amount of selectivity required overall is achieved by adding together the modest attenuations provided by each stage individually. Unfortunately this approach is too costly for commercial designs and really good picture quality is left in the hands of the amateur experimenter!

Retrimming

So if you have a receiver with bad i.f. distortion and the appropriate test gear try retrimming the i.f.s strictly to the maker's service data and see what improvement you can make. Then if you feel adventurous try retrimming individual circuits one at a time bearing in mind the principles we have discussed. Even small changes of trimming can have quite a significant effect on the picture. Go about things in a careful, systematic way and avoid the temptation to rush about with a screwdriver twiddling every core in sight.

A good technique is to note the adjustment of a circuit and then try the effect of a particular change of trimming. See what happens to the picture resolution and then retrim the circuit to its original condition. This process can be repeated on each tuned circuit in turn without any danger of getting the whole i.f. strip in a mess. The obvious warning of course is that if you are not equipped for the job or are not sure what you ought to be doing leave well alone: i.f. alignment is a tricky business.

Video Circuits

Not all picture resolution defects can be blamed on the i.f. strip. The video output stage can play an important part too. In fact an ill-designed circuit can cause most of the effects that we have been discussing in connection with the i.f. channel, but generally on a much reduced scale. (In general servicing work on old receivers however, ageing and value changes in the video circuits cause most trouble and should receive attention first.)

If the video channel bandwidth is too narrow there will be loss of resolution and you will not be able to see clearly the 4.5MHz frequency gratings of the standard test card. There is no excuse for transistor video output stages lacking in bandwidth but it is a fairly common occurrence with valve video output stages where the problems are rather more difficult. If you cannot get good resolution even when slightly overtuned check the video stage. Make sure that the lead to the c.r.t. is hanging loose and is not in a cable harness. The extra stray capacitance may be enough to lose some valuable bandwidth.

A drooping response as shown in Fig. 7(b) will cause moderate smearing unless it is compensated by too much h.f. response in the i.f. channel. A rising response—Fig. 7(c)—will tend to cause or accentuate overshoots and rings. This is partly be-

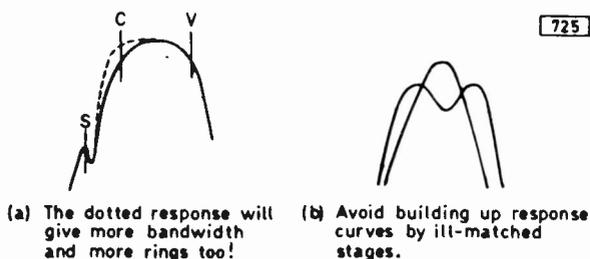


Fig. 6: All response curves should be as smooth as possible.

NEXT MONTH IN

TELEVISION

TEST SIGNAL EXTRACTOR UNIT

Quite a few test signals are present on the lines transmitted during the field flyback period. These sometimes include experimental Ceefax (BBC) or Oracle (IBA) data transmissions. The lines carrying these test or data signals should not normally be seen since they should appear above the top of the picture. They can be observed however by reducing the setting of the height control. An oscilloscope can be used to display such signals if it has facilities for strobing out particular lines. The test signals themselves are not particularly helpful for general servicing but the ability to strobe out lines can be invaluable for colour servicing since this makes the standard colour bar pattern present at the top of Test Card F available for signal tracing in PAL decoders. The unit featured next month can be used as an economical add-on unit for scopes without strobing facilities and in addition provides good, clean line and field sync pulse outputs.

TACKLING STICKY FAULTS

Most fault-finding is reasonably straightforward, a matter of clear symptoms and obvious causes. Every engineer has his ration of faults that seem to defy analysis however. There are nevertheless some common mechanisms by which these arise and a number of ways in which a goodly proportion of them can be cleared up without the need to spend hours delving into the "unknown". Next month Vivian Capel describes various steps which can provide a short-cut to solving the more obscure types of fault.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW

TO.....
(Name of Newsagent)

Please reserve/deliver the **NOVEMBER** issue of **TELEVISION** (20p), on sale **OCTOBER 22**, and continue every month until further notice.

NAME

ADDRESS.....

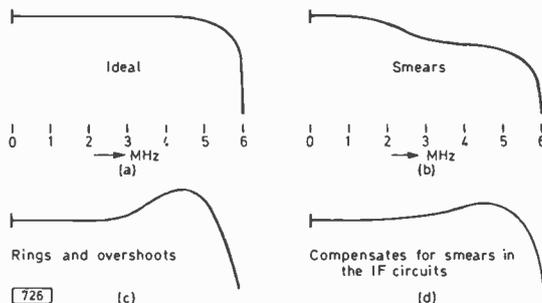


Fig. 7: The effects of different video responses.

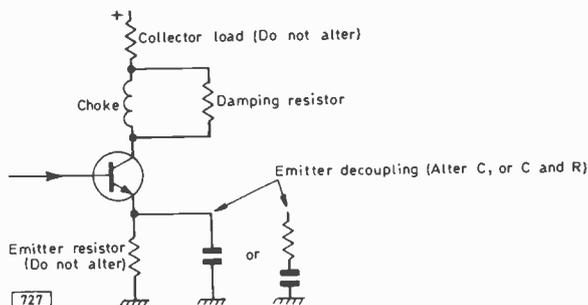


Fig. 8: The response of a video output stage can be modified by altering the damping of the peaking coil or the emitter decoupling.

cause the h.f. components of the signal are too large and partly because there will probably be a sharp fall-off at around 4-5MHz. The resultant abrupt phase changes will distort the time of arrival of the h.f. signal components which are responsible for the clean transitions from black to white and back again.


Adjusting the Video Response

Both these effects can be improved by altering the h.f. feedback of the output stage—see Fig. 8. Most designs have partial decoupling of the emitter or cathode by a capacitor of a few hundred picofarads. A larger capacitor, say increased in value by 50%, will give more h.f. gain by reducing the negative feedback at h.f. and will thus lift the response. A smaller value decoupling capacitor will result in the h.f. response falling. Similarly a choke of about 100 μ H with some parallel resistive damping will raise the h.f. response. Too much damping will reduce its effect: not enough damping may cause rings on the picture.

Remember also that too much capacitance or any high-impedance networks between the vision detector and the grid or base of the video output stage will cause loss of bandwidth, so keep an eye on both your circuit design and the physical layout. Keep leads short unless the circuit impedance is low.

As a final comment on i.f. and video problems we repeat the point made earlier. It is nearly always better to have a smooth and correct response with a small loss of bandwidth than to distort the signal in an attempt to achieve that last 0.5MHz. The improvement in picture resolution will be spoilt by the defects it introduces. Try retrimming for a good picture!

CONTINUED NEXT MONTH

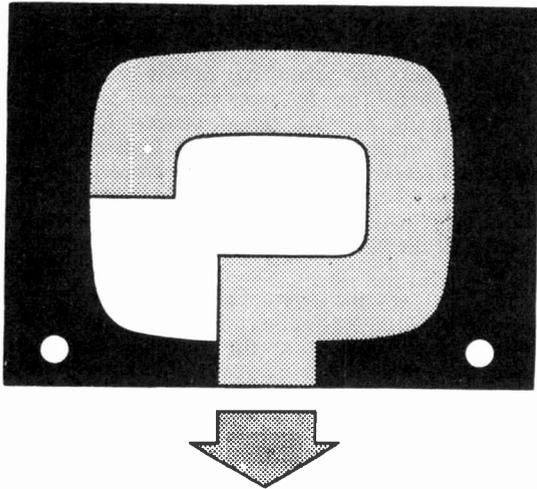

YOUR PROBLEMS SOLVED

BUSH TV56

I have modified this set for 625-line operation, using the surplus conversion unit featured in your November 1970 issue. The only modification I had to make in the line timebase was to fit a resistor in parallel with the line hold control—the timebase unit is otherwise as originally manufactured. Hum has since appeared on the raster, however, putting an S shape on the picture.—G. Hadfield (Baldock).

The h.t. supply to the line oscillator is decoupled by a $2\mu\text{F}$ electrolytic (C22). This and the main smoothing electrolytic (C33) in the supply to the timebases should be checked. The ECC83 line oscillator valve could well be at fault however.

KB SV148

When the picture first comes on it rolls downwards very fast. Then after two or three seconds it stops rolling leaving a third of the screen at the bottom blank. The picture then expands (after about three seconds) to normal. After operation for about an hour the picture is compressed at the bottom by about an inch. On examining a test card display the picture is seen to be compressed at the right-hand side by about an inch.—T. Conway (Cheam).

The rolling, etc., indicate that the PCL805 field timebase valve is in need of replacement. The right-hand side compression is a line timebase fault: the PL504 line output valve may be low emission or alternatively the line linearity and width controls may require careful setting up.

FERGUSON 3626

The main trouble with this set is field bounce. When the set is switched on the picture jumps up and down. If the hold control is adjusted the picture can be steadied somewhat so that it rolls up or down. After about an hour the jumping slows down and the picture then floats up and down. The second problem is about $1\frac{1}{2}$ in. of foldover at the bottom of the raster. The PCL85 field timebase valve and the $100\mu\text{F}$ output section cathode decoupler have been replaced without improving matters. Replacement main electrolytics and a new PFL200 video/sync valve have also been tried.—T. Jackson (Dulwich).

The trouble is in the field timebase circuit and the two faults may or may not be due to a common cause. The most likely cause of the trouble is that

★ Requests for advice in dealing with servicing problems must be accompanied by an 11p postal order (made out to IPC Magazines Ltd.), the query coupon from page 571 and a stamped, addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets or answer queries over the telephone. We cannot provide modifications to circuits published nor comment on alternative ways of using them.

the operation of the timebase is being upset as a result of one of the linearity feedback capacitors being faulty. Check C90 ($0.03\mu\text{F}$) and C88 ($0.01\mu\text{F}$) therefore. The value of the cathode bias resistor R112 (360Ω) should also be checked. This should cure the foldover: if the jitter persists check the cross-coupling capacitor C79 ($0.003\mu\text{F}$) back to the triode, the sync pulse coupler C85 ($0.001\mu\text{F}$) and the output pentode grid leak resistor R106 ($2.2\text{M}\Omega$). (BRC 900 chassis.)

GEC BT302

I have been reading your articles on servicing the GEC BT302 series in the January and February issues 1972. The value of the resistor (R105) in series with the field hold control is given as $330\text{k}\Omega$. Should this be $390\text{k}\Omega$?—T. Parkins (Liverpool).

We regret this slip: the value of R105 should be $390\text{k}\Omega$, not $330\text{k}\Omega$. The copy we had of this rather old circuit was not too clear. Fitting $330\text{k}\Omega$ should however keep the field hold control within its range. The only other mistake we know of on this circuit is that the c.r.t. heater pins are shown in the heater circuit as 7 and 8 (as on the manufacturer's original): they should of course be 1 and 8 as shown at the c.r.t. base.

ULTRA 6627

The fault on this set appears only when it has warmed up. The picture then starts shaking horizontally. If the aerial is removed for about 15 minutes (with the set still working) then put back the picture is all right for a few minutes. Increasing the brightness speeds up the shaking. The e.h.t. tray and all valves in the line timebase have been replaced and all voltages are correct.—S. Greene (Filey).

It seems to us that your model is fitted with the version of the BRC 900 chassis that incorporates a flywheel sync circuit mounted on a small panel to the left of the line output section. The preset control on this panel often gives trouble as do the sync diodes. Check this area, if necessary using a cooling solution such as Freezit to locate the component at fault—or alternatively change this small panel.

COLOUR, UHF AND TELEVISION SPARES

"TELEVISION" CONSTRUCTOR'S COLOUR SET. DEMONSTRATION MODEL, WORKING AND ON VIEW AT 172 WEST END LANE, N.W.6. ALREADY SEEN BY HUNDREDS OF CONSTRUCTORS. COMPLETE YOUR SET WITH MANOR SUPPLIES COMPONENTS. CALL, PHONE OR WRITE FOR UP-TO-DATE INFORMATION COLOUR LISTS.

SCAN PACK No. 21. Mullard or Plessey Scan Coils, Convergence Yoke, Blue Lateral, complete set for £10.00 p.p. 40p.

PRINTED CIRCUIT BOARDS, Convergence, 3 for £2.50 p.p. 30p. Decoder, I.F. amp, Time Base £1.25, Power £1.50 p.p. 25p, R.G.B. 70p p.p. 17p, Varicap, C.R.T. Base 66p p.p. 11p. Complete Set £8.25 p.p. 35p. Audio Panel & P.A. 263 £1.95 p.p. 15p.

PACKS (incl. p.p.). No. 2 £4.90, No. 5 £1.05, No. 9 45p, No. 12 31p, No. 13 35p, No. 14 £9.90, No. 15 £2.28, No. 16 £10.95, No. 17 £2.72, No. 19 £2.30, No. 21 £10.40, No. 22 £2.20, C.R.T. Base 30p. C.R.T. Shields £2.05 p.p. 55p, Varicap ELC1043 £4.50, TAA550 62p, AE Isolpanel 30p, Pack No. 23 £2.95, Pack No. 24 £1.25.

CABLE 7 x 0.2 mm. Screened 10 m for 50p. Colours 10 m for 25p p.p. 10p.

MAINS TRANSFORMER for Colour Receiver, guaranteed to give correct outputs under actual load conditions, plus additional 6.3V C.R.T. heater tapping £10.00 p.p. 70p.

C.R.T. HEATER TRANSFORMERS 6.3V 1 amp £1.10 p.p. 25p. SPECIAL OFFER I.F. Panel, leading British maker, similar design to "Television" panel. Now in use as alternative, incl. circuit, £8.90 p.p. 35p.

G.E.C. Colour decoder panels (for parts) incl. DL20, crystal and approx. 50% of resistors. Conds., diodes, transist., etc. for "Television" decoder £3.50 p.p. 30.

MULLARD at 1023/05 convergence yoke, New £2.50 p.p. 25p.

PHILIPS G6 single standard convergence panel, incl. 16 controls, switches etc., and circuits £3.75 p.p. 30p, or incl. Yoke £5.00.

PHILIPS G8 decoder panel part complete incl. I/C £2.50. I.F. Panel part/compl incl. modules £2.50 p.p. 30p.

BUSH CTV25 timebase units, line frame, E.H.T. surplus £4.50 p.p. 80p. Mk. III Quadrupler Trays/E.H.T. £8.25 p.p. 25p.

KB VCUI convergence control panels, New, complete £3.75 p.p. 25p.

VARICAP/VARACTOR ELC 1043 UHF tuner (for "Television" colour receiver) £4.50, PHILIPS VHF Varicap tuners for band 1 & 3 £2.85, Varicap tuners salvaged £1.50 p.p. 25p.

UHF 625 kits and tuners. Lists available at reduced prices. UHF tuners, transistd, £3.10, incl. s/m drive, indicator £3.85; 6 position or 4 position pushbutton £4.95, UHF/VHF transistd. tuner, latest type, incl. circuit £3.25. Cylodon valve type £1.50 p.p. 30p.

MURPHY 600/700 series UHF conversion kits in cabinet plinth assembly, can be used as separate UHF receiver £7.50 p.p. 50p.

SOBELL/GEC Dual 405/625 I.F. amp and o/p chassis incl. circuit £1.50 p.p. 30p, PHILIPS 625 I.F. panel incl. cct £1 p.p. 30p.

FIREBALL TUNERS, Ferg, HMV, Marconi. New £1.90 p.p. 25p.

TURRET TUNERS, KB "Featherlight" VC11, Philips 170 series, GEC 2010 £2.50, AB Dual Stand, suitable Ferguson, Baird, KB etc. 75p, Cylodon C 75p, Pye 110/510-Pam, Invicta, Miniature, increm. £1.95, Peto Scott 960, Decca 95/606 £1.50 p.p. 30p.

LINE OUTPUT TRANSFORMERS. Popular types available, brand new replacements, fully guar. A selection which can be supplied p.p. 30p. C.O.D. 28p.

SPECIAL OFFERS

MURPHY 849, 939, 153 2417S	£4.90	BUSH TV53/86	£1.75
PHILIPS 1768/2168, 1796/2196	£4.90	BUSH TV95/99	£2.50
PHILIPS 17TG/100 Range		EKCO 380 to 390	£2.50
STELLA 1011/1029	£4.30	EKCO 407/417	£2.50
PHILIPS 19TG111/12	£4.40	FERR 1057 to 1068	£2.50
PHILIPS 19TG121 to 156	£4.90	FERR 1084/1092	£2.50
PHILIPS 19TG170, 210 series	£4.90	FERG. 506 to 546	£1.50
BUSH TV92, 93, 105 to 186SS	£4.90	HMV 1890 to 1896	£1.50
EKCO 221 to 394, FERRANTI 1001 to 1065	£4.30	PI/SCOTT 1419 to 1725, 733 to 738	£1.75
EKCO, FERR. 418, 1093 etc.	£4.30	REG 10-6, 10-17	£2.50
DECCA DR95, 101/606, DRI, 2, 3, 121/123, 20/24, 2000	£4.70	REG 19/2, 17-18	£2.50
FERG, 305 to 436, 606 to 727	£4.30	RGD 519, 606, 610, 612, 619, 620, 711	£2.50
FERG, HMV, MARCONI		PHILCO 1010/21	£2.25
ULTRA, PHILCO 3600, 2600, 4600, 6600, 1100 series, Jell pot	£4.70		
KB VCI to VCI1	£4.40		
GEC 302 to 456, 2000 series	£4.90		
HMV 1865/9, 1870/6, 1910/1924	£4.30		
PETO SCOTT 960, COSSOR CT 1964	£4.70		
PYE 17/21, 17/S, 110 to 510, 700, 830, 1, 2, 3, 11U to 64	£4.30		
PYE 169, 569, 769 series	£5.25		
PAM, INVICTA equiv. LOPTS to above PYE	£4.30		
SOBELL 195/282/1000 series	£4.90		
Transistorised I.F. panel (salvaged)			£2.50 p.p. 25p
850 field output transformer			£1.80 p.p. 20p
850 scan coils			£4.40 p.p. 30p
THORN 850 Time Base Panel. Dual Standard	£1 p.p. 30p.		
THORN 850 Mains Droppers	30p p.p. 15p (state approx values)		

CALLERS WELCOME AT SHOP PREMISES

MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6
(Near W. Hampstead tube stn; 28, 59, 159 Bus Routes) 01-794 8751

Mail Order: 64 GOLDERS MANOR DRIVE,
LONDON, N.W.11

GEC 2040

More often than not when the set is switched on the picture comes on in monochrome. The colour appears gradually two or three minutes later, first in horizontal bands which move up and down the screen, subsequently stabilising as the correct colours. The condition seems to be sensitive to ambient temperature. It is so erratic unfortunately that it is not possible to make voltage checks.—C. Pearson (London W4).

We suspect that the reference oscillator transistor TR328 or the emitter-follower TR329 is faulty or that there is a dry-joint in the reference oscillator subassembly (PC314). It is also possible that the zener diode D325 connected across the oscillator frequency control P302 is intermittent.

BUSH TV125

We are experiencing difficulty in obtaining even spacing of the raster lines, the top half of the raster being more expanded than the bottom. Adjusting the height and field linearity controls does not help matters. The field timebase valves have been replaced. Some foldover is produced at the top of the raster when the overall field linearity control is adjusted. Another fault is that when white lettering (captions etc.) come on the screen there is a loud buzzing noise.—P. Mutford (Bicester).

The field troubles suggest a fault in the linearity feedback network and the first suspects are 3C32 (0.1 μ F) and 3C26 (0.022 μ F). If replacing these does not help check the other capacitor in the loop, 3C27 (0.1 μ F). The buzz should be minimised by adjusting the a.g.c. delay control 2RV1. If not change the final i.f. amplifier valve 2V3 (EF80).

HMV 2643

The original complaint was no picture due to absence of e.h.t. A brand new 6/30L2 line oscillator valve cured that. Unfortunately however the line hold control has to reset about every ten minutes. The sync separator and video valves have been replaced, also the line hold control and its series resistors and the anode resistors in the line multivibrator circuit but with no improvement. I would welcome any comments you can make before I get involved in the flywheel sync circuit.—E. Leatherhead (Ipswich).

There is a bias stabilising resistor in the video amplifier circuit—R26 (39k Ω) from the screen grid to cathode. This nearly always changes value, making accurate line locking difficult. If changing this does not do the trick replace the flywheel sync diodes. These are encapsulated as a common block (type BA126) but a pair of BA144 or similar diodes can be used instead. (BRC 981 chassis.)

EKCO T526

This set has developed white bars down the left-hand side of the screen, gradually disappearing towards the centre—R. Gracehorn (Petersham).

The trouble is due to the line linearity coil ringing as a result of its damping resistor R159 changing value (correct value 1.5k Ω). Note that R159 is not mounted on the printed panel with the linearity coil L32, being on the line output transformer assembly instead. (Pye group 368 chassis.)

PHILIPS 19TG156A

The picture detail is good but lacking crispness, in other words generally grey, in spite of fitting a new c.r.t. The contrast control seems to be working correctly since it has a distinct effect on the picture. The i.f. and video output valves have been replaced, also the tuner valves. The sound and raster are correct. A new h.t. rectifier has been fitted.—T. Greyson (Wolverhampton).

The OA70 vision detector diode could be faulty and we suggest you check its front-to-back resistance. This can be done by switching to 405 lines and connecting an ohmmeter from chassis to pin 2 (grid) of the PL83 video output valve. With the leads one way round the reading should show virtually a dead short-circuit. Reverse the leads and the reading should be over $4k\Omega$. If these readings are obtained the diode is OK: if a reading of $4k\Omega$ is obtained in both directions or a short is indicated in both directions the diode should be changed. Check the $250\mu F$ cathode decoupler in the video output stage as well.

BUSH TV108

The picture is perfect at times but then goes negative and dull. The e.h.t. is good and all valves have been checked.—O. Rowton (Hull).

We suspect that the c.r.t. has an intermittently faulty heater which is partially shorting at times. The normal voltage across the heater pins 1 and 8 should be about 6V but will drop to well below this when the short occurs. Sharply tapping the tube neck may clear the fault for a limited period.

QUERIES COUPON

This coupon is available until October 22 1973 and must accompany all Queries sent in accordance with the notice on page 569. Don't forget the 11p (inc. VAT) postal order!

TELEVISION OCTOBER 1973**130**

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

Q A Ferguson Model 3646 (BRC 1400 chassis) had the annoying symptom of line drift on both v.h.f. and u.h.f. The chassis employs a blocking oscillator type line generator controlled by a dual-diode fly-wheel sync discriminator via a d.c. amplifier. The latter stage consists of the triode section of a 30FL14 while the oscillator itself uses the triode section of a 30FL1.

The diodes and both valves were checked by substitution but the symptom remained and the line drift was significant after protracted periods of use. The anode voltage of the d.c. amplifier triode controls the oscillator frequency by adjusting the d.c. voltage at the grid of this stage. There are two series resistors in the feed, one of $2.2k\Omega$ and the other $330k\Omega$. Both resistors were replaced to no avail.

Subsequent voltage tests at the anode and cathode of the d.c. amplifier gave readings slightly greater than specified, the margin increasing with the operating time of the receiver. The conduction of the d.c. amplifier is varied by the discriminator output which is fed to its grid while its d.c. stability is established by a potential-divider network at its cathode.

What was the most likely cause of the trouble, bearing in mind that valve replacements failed to effect a cure? See next month's TELEVISION for the solution and for a further item in the Test Case series.

SOLUTION TO TEST CASE 129

(Page 523 last month)

It will be recalled that the c.r.t. cathode voltage was abnormally low. As the c.r.t. cathode is d.c. coupled to the anode of the PFL200 video amplifier in this model the voltage there was low as well of course. This indicated excessive valve current which was subsequently confirmed when it was observed that the PFL200 screen grid resistors were overheating.

Insufficient grid bias is the usual cause of heavy current and as the PFL200 itself checked OK this possibility was next investigated. A voltage test at the cathode indicated something less than 1V, the correct figure being 6V. The cathode bias resistor is decoupled by an electrolytic capacitor and tests on this after disconnecting one end revealed that it was of low insulation, thus reducing the effective cathode circuit resistance.

Replacing the electrolytic completely cleared the trouble and eliminated the overheating in the screen grid circuit resistors. This is a typical case where incorrect video amplifier biasing results in incorrect c.r.t. operation, making it impossible to blank out the raster completely with the brightness control. Once the video amplifier valve in this type of circuit (d.c. coupled) has been checked—preferably by substitution—the next move should be a check of the valve biasing; and when an electrolytic capacitor is used for decoupling in the cathode circuit this should figure high on the testing list.

TELEVISION CLASSIFIED ADVERTISEMENTS

The pre-paid rate for classified advertisements is 6p a word (minimum 12 words), box number 20p extra. Semi-display setting £3.50 per single column inch. All cheques, postal orders, etc., to be made payable to TELEVISION and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, TELEVISION IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD, for insertion in the next available issue.

AERIALS

GENUINE FULL SIZE 18 element TV aerial

as used by leading
TV companies

FOR ONLY
£2.20
incl. VAT

+ 35p carr



IMPERIAL TRADING (AERIALS) LTD.
the quality Aerial Specialists

Baines for High Frequency Aerials

UHF Multibeams by J Beam

MBM 18 £3.24, MBM 30 £4.40, MBM46
£6.90, MBM 70 £12.10, 2MBM 70 £28.40,
4MBM 70 £56.80, LBM 2 £6.00, LBM
2/CK £10.50, Aerial Rotator £22.00.

VHF Stereobeams

SBM 1 £2.20, SBM 2 £2.95, SBM 3 £4.40,
SBM 4 £4.80, SBM 6 £7.25, PM3 stacking
kit £2.20, JB 75/300 Balun £1.50.

Masthead Amplifiers

UHF and VHF £5.75 and £7.75, Wideband
£7.75, Setback £3.75.

Accessories: Large SAE will bring details.
Co-ax 5p and 9p

11 Dale Crescent, Tupton,
Chesterfield S42 6DR. Tel. 863755

SERVICE SHEETS

LARGE SUPPLIER OF SERVICE SHEETS

All at 40p each

(T.V., RADIO, TAPE RECORDERS,
RECORD PLAYERS, TRANSISTORS,
STEREOGRAMS, RADIOGRAMS,
CAR RADIOS)

"PLEASE ENCLOSE LARGE S.A.E.
WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to

(Uncrossed P.O.'s please, original
returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any
claims for non-delivery should be made within
7-days of posting your order.

C. CARANNA

71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service
Sheets (strictly by return of post). Please
state make and model number alternative.

Free T.V. fault tracing chart or T.V. list on
request with order.

Mail order or phone 01-458 4882

SERVICE SHEETS • MANUALS • BOOKS

SERVICE SHEETS 40p plus S.A.E. ★ SERVICE SHEET CATALOGUE 25p
OVER 12,000 SERVICE SHEETS & MANUALS IN STOCK ON COLOUR/MONO TELEVISIONS
RADIOS, RADIOGRAMS, T/RECORDERS, R/PLAYERS, ETC. S.A.E. WITH ENQUIRIES

★ COLOUR TELEVISION SERVICING MANUALS. Prices include postage. ★

ALBA TC1525 TC1626 £1.60, TC1717 TC2222 £2.10, TC2022 £2.60, TC2122 TC2126 £4.00...
BRC 2000 £3.75, 3000 3500 8000 8500 £2.10, BUSH CTV174D CTV182S CTV184S CT187CS C
TV192 CTV194 CTV196 CTV197C CTV199 CTV1026 CTV1120 CTV1122 CTV1126 CT1226C £3.25...
DECCA CTV19 CTV19G CTV22C CTV22G CTV25 CTV25C CTV2200 CTV2203 CTV2207 CTV2225
CTV2500 CTV2503 CTV2505 CTV2506 CTV2509 CTV2520 £3.75, CS1730 CS1733 CS1910 CS20
30 CS2213 CS2230 CS2520 CS2611 CS2630 30-Series CS2631 £2.60, DER 5705 5706 5707 574
2 £2.10, EKCO All Models £4.50, FERGUSON 3700 3701 3702 £3.75, Colour-Star 3703 3704
3705 3706 3707 3710 3711 3712 3713 3714 £2.10, FERRANTI CT1166 CT1167 £4.50, GEC 2028
2028A 2028B 2029 2029A 2029B 2030 2030A C2040 C2040B C2041 C2041B C2073B C2100 C210
3 C2107 C2110 C2115 £2.10, HMV 2700 2701 2702 £3.75, 2703 2704 2705 2711 £2.10, IIT/KB
CVCS CK500 CK550 CK600 CK701 CK750 Studio-100 £2.60, INVICTA All Models £4.50 each
MARCONIPHONE 4700 4701 4702 £3.75, 4703 4704 4705 4711 4714 £2.10, MURPHY CV1916S
CV1917 CV2011 CV2210D CV2211 CV2212 CV2213 CV2214 CV2215 CV2516C CV2610C CV2611
CV2614 £3.25, PHILIPS G6-D/Std G25K500 G25K501 G25K502 £1.60, G6-S/Std G22K511...
G25K512 £2.60, G26K521 G26K522 G22K523 G22K524 G26K525 G22K532 G22K533/534 £4.00,
PYE All Models £4.50 each, SOBELL 1028 1029 1040 1060 C1100 £2.10, 1028A 1028B 1029A
1029B C1040 C1040B C1060B £2.10, ULTRA 6700 6701 6702 £3.75, 6703 6706 6713/14 £2.10.
Special Offer, 1972 Edition of WORLD RADIO-TV HANDBOOK £1.50 post free, usually £2.80.
NEWNES RADIO & TELEVISION SERVICING books bought & sold (all years) Good price paid.

Send large S.A.E. for FREE booklists and book pamphlets on Radio, Television & Electronics
BELL'S TELEVISION SERVICES

ALBERT PLACE, HARROGATE, YORKSHIRE. Telephone 0423-86844

A.L.S. Service Sheet Service

10 Dryden Chambers, 119 Oxford Street
LONDON W1R 1PA

Please
always
state
Make &
Model
Number,
and
whether
TV, AMP,
RADIO,
TAPE,
etc;

SERVICE SHEET
SERVICE ONLY 30p
Plus large s.a.e.

Lists covering Mono & Colour TVs,
Radio, Tape, Record Players, Books,
Manuals, Newsletter, etc Only 5p Plus s.a.e.

COMPREHENSIVE
COLOUR TELEVISION
MANUAL. BY McCOURT
Contains Faults & Causes on most
British sets. NOW ONLY £2 post paid

"A GUIDE TO TELEVISION * * *
ALIGNMENT USING ONLY
TRANSMITTED TEST SIGNALS"
By B.R.Epton. price 30p plus S.A.E.

One title recommended from our now
extensive book list.

"SERVICING WITH
THE OSCILLOSCOPE"
(KING) (1969) 176 pages illustrated
PRICE£2 POST PAID

A S.A.E. FOR FULL LIST ----

We can supply
Manuals for most
makes of TV
both Mono and
Colour including
Bush, Murphy,
B.R.C., Ferguson,
H.M.V., Decca,
Sony, Sanyo,
Hitachi, etc.; &
Most Colour TV
require a Manual
to cover the
large amount of
information that
is necessary.
S.A.E. for quote
price and delivery

Please Note
Mail ♦
Order ♦
Only ♦
return service

OUR STOCKS
NOW EXCEED
20,000 ITEMS
covering 10,000
of makes and
models of
TV, Radio, Amps,
Recorders, etc!

SERVICE SHEETS

(1925-1973) for Radios, Televisions, Transistors, Radiograms, Car Radios, Tape Recorders, Record Players, etc. with

FREE FAULT FINDING GUIDE**PRICES FROM 5p**

Over 10,000 models available.
Catalogue 15p + SAE

Please send stamped addressed envelope with all orders and enquiries.

Hamilton Radio

47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

SERVICE SHEETS, Radio, TV etc. 8,000 models. Catalogue 15p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

FOR SALE

PYE 691/693, I.F. £11.50, C.D.A. £3.50, F.T.B. £3.50, Tube Base £2.50, Scan Coils 22"/26" £4.50. "Television" 10/71-7/73. P.W. 6/71-3/73, P.E. 4/71-10/72 £7.50. S.A.E. W. Neilson, Union, Teviot Row, Edinburgh.

FOR SALE. Philips type 1700A/15 Cabinet Television. Good example of early receivers where the image is projected via a mirror on to the screen. Complete. Offers: Hodson (Tel. 043-04 531), Briar Cottage, Gilberdyke HU15 2TJ.

Belling "Concord" T.V. Pre-amplifier. Brand New. £7. Dodd, 6 Masefield Road, Stratford-upon-Avon, Warks.

FOR SALE. Packs 1-17 for the "Television" colour television project. Only built Pack 7 (works great) rest untouched. Total cost of these modules—£85.23. Best offer over £60.00. 123 Sale Road, Wythen-shaw, Manchester M23 0LA. 061-998 2487.

BOOKS AND PUBLICATIONS

"RADIO AND TV SERVICING" all volumes available. S.A.E. for price list. Markonics, 327 Tildesley Road, London S.W.15.

LADDERS 24" £12.39. Carri. £1.10. Leaflet. Callers welcome. Home Sales, Ladder Centre, (PTT2) Haldane (North), Halesfield (1) Telford, Shropshire. Tel. 0952 586644.

WANTED

NEW BVA valves of popular types, PCL805, PY800/1, PL504, etc. Cash waiting. Bearman, 6 Potters Road, New Barnet. 449/1934-5.

SERVICE SHEETS purchased. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

"Back issues of Television" Wanted. April '72-March '73 inclusive. M. Ballantyne, 30 Abbotsford Avenue, Great Barr, Birmingham. 021-357 6258.

MAINS DROPPERS.

37-31-97-26-168 Ω 50p.
25-35-97-59-30 Ω 50p.
14-26-97-160 Ω 50p.
14-26-97-173 Ω 50p.
15-19-20-70-63-28-63 Ω 50p.
Post free. C.W.O.

Durham Supplies, 367 Kensington Street, Bradford, 8, Yorkshire.

TOP PRICES PAID for NEW VALVES and TRANSISTORS popular T.V. and Radio types KENSINGTON SUPPLIES (A) 367 Kensington Street, Bradford 8, Yorkshire.

NEWNES RADIO and T.V. Servicing 1964-1965 urgently required. Good price paid. Tel. Harrogate 86844.

SETS & COMPONENTS**Top 20 Plus Tested TV Valves**

PL504	18p	PCL84	10p
PC86	15p	PCL82	10p
30L15	15p	PFL200	10p
PL36	15p	ECC82	10p
PCL805/85	15p	EH90	10p
30FL1/2	15p	30PL13	15p

Colour Valves Fully Tested

PL509	30p	PY500/A	30p
PL508	30p	PL802	30p

Many others available including Mazda Types.

P. & P. 4p per valve, over 12 2 1/2p per valve, orders over £3 post free.

Prompt service.

S.A.E. for free list

L. & D. COMPONENTS LTD.,

71 Westbury Ave., London N22 6SA.
Tel. 01-888 2701.

TVs TVs TVs !!! 19" TVs

All in Working Order
Bush, Murphy, Ferguson, Pye,
Marconi, Thorn, etc.

£11.50 plus £2.00 Carriage

COLOUR — COLOUR — COLOUR

All Working

19" Various Makes ..	£90.00
22" Various Makes ..	£125.00
25" Various Makes ..	£140.00
11" Colour Portables ..	£75.00

Delivery Arranged

S.A.E. LISTS

ENG. 919031

LINAVALE RADIO LTD.,

48 Hoe St., London E17 4PG.
01-520 7546

SLIMLINE TELEVISION

Ex-Rental Television
Dual-Standard with UHF Tuners
complete, untested

19" Thorn 850 £4
19" Cossor 1964 £5
19" KB VV £7
19" Bush 125 £7

No scrap sets all as withdrawn from rental
Collect or send £2.00 p.p.

162 Kettering Road,
Northampton
90 Tavistock St., Bedford
Tel: Bedford 51948

For quality Hi-Fi Equipment, records and Colour Television, Visit

HANSPAL'S AUDIONICS

488 Lady Margaret, Southall, 01-578 2258;
54 St. Anns Road, Harrow, 01-863 3400.
24 hours Autophone Service. Marantz,
Pioneer, Sansui, Akai, Rotel, Nikko, Lux,
Telefunken, Sony, Sanyo, Tandberg, Hitachi,
Grundig, Scan-Dyna, KEF, TEAC, National,
Quad, Telefunken, Hitachi, Sony and Grundig
Colour T.V. Always in stock.

Up to 5 years Colour Tube guaranteed and
1 year Free Servicing and Labour. Late
evening: Friday until 7.00 p.m.

EXCELLENT CREDIT FACILITIES

**EX RENTAL
TV's BARGAIN**

23" & 19" 3 Channel with U.H.F. Tuner £3.50
19" & 25" Colour from £50.00
19" & 23" tubes guaranteed from £2
All sets complete.

EDWARDS & SONS
103 Goldhawk Road, London W.12
Telephone 743-6996

"TELEVISION" Colour Receiver. Cabinet Framework, similar to design in Oct. 1972 issue, and including later modifications. Supplied as kit, with all joints machined, ready to assemble, and complete with tube mounting brackets and bolts. £15.36 incl. VAT & p.p.

A. H. Green
21 Buchanan Drive, Luton, Beds.

COLOUR TV's

19" Decca £133
25" Decca £115
25" RBM/Phillips £120
25" Thorn £125

Fully Serviced, one months' guarantee. Delivery & Terms can be arranged. Non-Workers available.

S.A.E. details please.
T.E.S.T. P.O. Box 1,
Kirkham, Preston PR4 2RS.
Telephone 077-48 2796.

150 NEW Capacitors/Resistors/Silicon Diodes. Electrolytic. Mica. Ceramic. Carbon. Oxide etc. £1 Post Free. Whitam Electrical, 33 Drayton Green Road, London, W.13.

CHEAPER TV SETS

405 from 50p. D/S 625 from £2.50.

Colour also available.

Mon./Sat.—9.00 a.m. to 5.30 p.m.

PREMIER TV WAREHOUSE,
Bridgeworks, East Farleigh,
Maidstone.
Tel: Maidstone 26007

Components Galore. Pack of 500 mixed Components, manufacturers' surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1 + 10p P. & P. C.W.O. To: Caledonian Components, Strathore Road, Thornton, Fife.

VALVE LIST

ALL VALVES
FULLY TESTED

One valve postage 3p. Over 5 valves postage paid.

DY86-87	12p	PCF80	5p	6P23	15p
EB1	15p	PCF86	15p	630L2	15p
ECF82	10p	PCF805	25p	30F5	10p
ECF85	20p	PCL82	12p	30PL1	20p
ECL80	7p	PCL83	12p	30PL3	20p
EF80	7p	PCL84	12p	30PL13	17p
EF183	10p	PCL85	20p	MANY MORE	
EF184	10p	PCL86	17p	AVAILABLE	
EH90	15p	PFL200	25p	S. & W.	
PC6	20p	PL36	20p	ELECTRONICS	
PC88	20p	PL504	20p	114 Burnley	
PC900	10p	PY800	12p	Road	
PCC84	5p	PY801	25p	Rawtenstall	
PCC189	7p	U191	17p	Rossendale	
PCC805	15p	U26	10p	Launcs.	

EX-RENTALS

ALL SETS complete with UHF Tuners, many working:—

19" BBC2 Sets at £3
23" BBC2 Sets at £7

Working Sets to Order. Calls Only.
All Sets Re-polished

TV DISPOSALS
Tel: Bristol 626374

PRACTICAL TV 625 Receiver one only set of major parts plus chassis, instructions and diagrams. £28 plus postage. Enquiries to: 27 Hawley Road, Falkirk, Scotland FK1/1SJ.

MISCELLANEOUS

Build the Mullard C.C.T.V. Camera

Kits are now available with comprehensive construction manual (also available separately at 76½p)

Send 5" x 7" S.A.E. for details to

CROFTON ELECTRONICS

15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

SCRATCHED FACE!

Expert service for removing and repolishing your scratched tubes, colour and mono chrome. Standard charge £3.85 carriage paid. Cash with order, satisfaction guaranteed. Completed in one week and returned B.R.S.

RETUBE LTD.

North Somercotes, Louth, Lincs.
North Somercotes 300

ENGINEERS

Are you fed-up with that troublesome, inefficient desoldering gun and damaged panels? Then use our IMPREGNATED DESOLDERING BRAID. Soaks up molten solder like magic and clears small and large joints in seconds ready for component extraction. Very kind to printed panels. 6 feet for 45p post free. S.A.E. for free sample, leaflet and quantity terms.

ASHLEYS

91 Vale Road, Ash Vale, Aldershot, Hants.

NYLON Screws and Nuts for Television colour receiver modules. 75p per pack including postage. Venour, 32 Milton Road, Bentley Heath, Solihull, Warks.

ALUMINIUM SHEET to individual sizes or in standard packs, 3p stamp per detail. Ramar Constructor Services, 29 Shelbourne Road, Stratford-on-Avon, Warks.

EDUCATIONAL

COLOUR
T.V.
SERVICING

Be ready for the coming Colour TV boom. Learn the techniques of servicing colour TV sets through new home-study courses specially prepared for the practical TV technician, and approved by leading manufacturer.

Full details from ICS, (D.750U)
Intertext House, London SW8.

PHILIP H. BEARMAN

(VALVE SPECIALISTS) SUPPLIERS TO H.M. GOVT. Etc.

NEW valves by Mullard, Mazda, Telefunken etc.,

IMMEDIATE POSTAL DESPATCH, LISTS S.A.E., DISCOUNT PRICE

PRICES FROM I.4.1973 (INCL. V.A.T.)

DY86/7 33p	PC88 61p	PCL86 53p	6/30L2 80p	30PL 13 95p
DY802 37p	PCF80 43p	PL36 70p	6BW7 66p	30PL 15 95p
ECC81 40p	PCF801 53p	PL84 53p	6F23 85p	NOTE:
ECC82 37p	PCF802 55p	PL500/4 70p	6F28 60p	PRICES ARE
ECL80 43p	PCF805 73p	PY81 40p	20L1 88p	TO NEAREST
EF80 37p	PCF808 70p	PY800 40p	20P4 88p	NEW PENNY
EF183 49p	PCL82 41p	PY801 40p	30C15 84p	QUANTITY
EF184 49p	PCL83 53p	U25 80p	30FL1/2 60p	PRICES ARE
EH90 46p	PCL84 49p	U26 80p	30L15 84p	LOWER.
EY51 60p	PCL85 53p	U191 80p	30L17 84p	Enquiries welcomed
EY86/7 33p	PCL805 }	U193 40p	30PI2 84p	BY100-127 with
GZ34 63p	PCL805 (non	U251 83p	30PL1 66p	10W res. 16p
PC86 61p	BVA) 44p			

POST FREE OVER £3, BELOW THIS add 3p per valve

Large PCF80 30p. Sorry, no X78, X79 but EQUIVS. 12AH8 & 10C1
See separate Component, CRT and Transistor Lists. Many obsolete types available

(Adjacent to Post Office) 6 POTTERS RD., NEW BARNET
HERTS. Tel: 449/1934-5 any time.

Local Agents: MANOR SUPPLIES, 172 WEST END LANE, LONDON NW6
Tel: 794/8751. (Near West Hampstead Tube Station)

SOUTHERN VALVE CO. P.O. Box 144
BARNET, HERTS.

All new and boxed, Mazda & Mullard wherever possible. Lists sae. Mail order only

AZ31 62p	EZ40/1 40p	PL81A 48p	U801 90p	30PL13 75p
DY86/7 34p	EZ80 35p	PL82 37p	5Y3 35p	30PL14 80p
DY802 40p	EZ81 25p	PL83 45p	5Z4 35p	30PL15 80p
EB91 15p	GY501 75p	PL84 45p	6/30L2 60p	30P4MR 88p
ECC81 34p	GZ30 40p	PL500 58p	6AT6 30p	35W4 35p
ECC82 25p	PC86 46p	PL504 70p	6BW7 60p	50CD6G 1.25
ECC83 25p	PC88 46p	PL508 70p	6CD6G 80p	ETC., ETC.
ECC85 36p	PC97 38p	PL509 £1.40	6F24/5 60p	
ECC88 45p	PC900 45p	PL802 85p	6F28 60p	
ECH42 70p	PCC84 33p	PL805 78p	6K7/8 35p	Service & Civility.
ECH81 34p	PCC85 35p	PY32/3 47p	6V6 35p	The above types,
ECH84 50p	PCC88 60p	PY81 31p	6X4 30p	and many others,
ECL80 40p	PC289 45p	PY88 33p	6X5 35p	are in stock at
ECL82 45p	PC189 48p	PY800 31p	9D7 40p	time of going to
ECL83 57p	PCF80(L) 28p	PY801 31p	10C2 75p	press.
ECL86 40p	PCF80(Br) 38p	PY500 80p	10F1 45p	These are new
EF80 24p	PCF82 50p	UBF89 35p	10P13 70p	lower prices,
EF85 36p	PCF86 48p	UCC85 40p	12BA6 40p	including V.A.T.
EF86 30p	PCF200 45p	UCG42 50p	20L1 80p	at 10%.
EF89 30p	PCF801 48p	UCH81 40p	20P3 80p	Transistor lists
EF183 32p	PCF802 45p	UCL82 40p	20P4 80p	s.a.e.
EF184 32p	PCF805 55p	UCL83 55p	20P5 95p	All valves new
EH90 45p	PCF806 55p	UF41 50p	30C1 38p	and boxed but
EL34 54p	PCF808 50p	UF85 35p	30C15 70p	we cannot always
EL41 50p	PCH200 55p	UF89 35p	30C18 55p	guarantee any
EL42 47p	PCL82 32p	UL41 55p	30F5 75p	specific make.
EL84 30p	PCL83 45p	UL84 42p	30FL1 50p	Postage: 3p per
EL86 38p	PCL84 32p	UY41 35p	30FL2 50p	valve / post free
EL90/1 40p	PCL85 }	UY85 30p	30L1 33p	over £3.00.
EL95 40p	PCL805 }	U25 62p	30L15 75p	Tel. (Office):
EM80/1 40p	PCL86 32p	U26 60p	30L17 70p	440 8641
EM84 40p	PFL200 55p	U191 60p	30PI2 70p	Closed Thursday
EY51 45p	PL36 52p	U193 31p	30PI9 70p	& Saturday
EY86/7 35p	PL81 45p	U404 40p	30PL1 60p	afternoons.

COLOUR TELEVISION TRAINING

11 WEEKS' practical and theoretical Colour training course commences Sept. 24th for men with Mono experience. Hours 2 to 5 p.m. Mon. to Friday.

13 WEEKS' (full-time) combined Mono and Colour training course commences Sept. 10th for men with a good electronics background.

(The above courses are supplementary to the 16 months' full-time course for beginners.)

Prospectus from: London Electronics College, Dept. T.10, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.



HI-FI... all you want to know in a 16-page supplement 'EASY GUIDE TO HI-FI'

- Why radiograms are obsolete
- All about stereo sound
- What you need to buy
- How much it will cost
- Choice of equipment and where to buy
- Setting up the equipment
- Adding to the system
- Hints and tips on operation
- Fitting equipment into your furnishing scheme
- Suggested 'test' records

in the October issue out September 21

Audio

THE HI-FI MAGAZINE FOR LEISURE LISTENING

20p

LAWSON TELEVISION TUBES



NEW TUBE SPECIFICATION

THE LAWSON RANGE OF NEW TUBES ARE DESIGNED TO GIVE THE ULTIMATE IN PERFORMANCE AND LIFE. MANUFACTURED BY BRITAIN'S LARGEST CRT PRODUCER. THEY ARE EXACT REPLACEMENTS AND INCORPORATE THE VERY LATEST DESIGN IMPROVEMENTS.

REBUILT TUBES

	New Tubes £	Red Label £	Colour Tubes old glass not required
LAWSON "RED LABEL" CRTs ARE REBUILT FROM SELECTED GLASS AND ARE DIRECT REPLACEMENTS FOR ALL TYPES			
14"	3.85	—	
17"	6.87	5.47	19" £43.45
19"	7.97	5.77	
21"	9.35	7.65	22" £47.85
23"	10.70	7.97	
19" twin panel	11.28	9.07	25" £52.25
23" twin panel	17.05	10.72	
16" panorama	9.35	—	26" £54.45
19" panorama	10.32	7.65	
20" panorama	11.55	—	Carr. £1.65
23" panorama	13.15	9.63	

LAWSON TUBES

18 Churchdown Rd.

MALVERN

WORCS.

Malvern 2100

2 year guarantee

PRICES INCLUDE VAT

Carr./ins.

14"-19" 68p

20"-23" 82p

REBUILT T.V. TUBES FOR MEN OF VISION

Current types

17"	£4.00	21"	£5.00
19"	£4.00	23"	£5.00

Panorama & Rimguard types

19"	£6.00	23"	£8.00
-----	-------	-----	-------

Twin panel

19"	£7.50
-----	-------

Cash or P.O. with order, no C.O.D. Carriage 75p in England, Scotland, Wales. Add £1.25 for carriage Northern Ireland. For all enquiries please send S.A.E. Each tube fitted with new electron gun assembly. Fully guaranteed for two years against any fault except breakage.

k.s.f. Ltd.

Providence Mills, Viaduct St., Stanningly, Nr. Leeds, Yorks. Tel. Pudsey 78177

DISCOUNT COLOUR!

Perfect working order. Repolished cabinets. 30 DAY GUARANTEE!

19" DECCA £77
19" GEC £88
22" PHILLIPS/DECCA £132
25" DECCA/BUSH/GEC
BRC 2000/PYE £110

CASH and COLLECT PRICES, VAT included.

3 or over less 10% discount.

Brand New 26" Colour TV Cabinets Slight seconds without backs. All with doors in Dark Teak. Delivered for £10 cwo

Mono UHF TV's

Sold complete but unserviced with tube tested. Good cabinets, Valve tuner type inc.:-

BUSH 128, SOBELL 1000, GEC 2000, THORN 900. Singles £5 each (add £2 delivery. 6 for £25). Delivery extra.

Transistorised tuner type makes inc.:- THORN 950, BUSH 141, GEC 2010 to 2038. Philips style 70. Singles £10 each (add £2 delivery. 6 for £50). Delivery extra.

Transistors for BRC 3000 R2008 (Line) R2010 (Chopper) Singles £1 each. Any twelve £10 inclusive. Send c.w.o.

Send SAE for list of UHF tuners, valves, tubes, washing machines etc. Open 6 days every week.

TRADE DISPOSALS

1043 Leeds Road, Bradford 3. Tel Bradford (0274) 665670

and

Peacock Cross Industrial Estate, Burnbank Road, Hamilton, Tel Hamilton (06982) 29511

AERIAL BOOSTERS—£3.25

We make three types of Aerial Boosters: B45-UHF 625, B12-VHF 405, B11-VHF RADIO

VALVE BARGAINS

Any 5—50p, 10—75p, 50—£3.30:—ECC82, ECL80, EB91, EBF89, EF80, EF85, EF183, EF184, EY86, PCC84, PCC89, PCC189, PC97, PCF80, PCF86, PCF805, PCF808, PCL82, PCL83, PCL84, PCL85, PFL200, PL36, PL81, PL504, PY33, PY82, PY800, PY801, 30L15, EH90.

19" UHF/VHF (BBC2)—£6.00

Thorn-850 or Pye, with set of spare valves. Carriage £2.00 (Untested).

100 MIXED RESISTORS—65p

1 to 2 watt—10 ohms to above 1m-ohms (our choice) 100 mixed Capacitors up to 500MFD—£1.10 (our choice).

BARGAIN PARTS

Transistor UHF Tuners—£2.00, 500K-ohms V/C with Switch—20p. 50 mixed Tuner Valves—£2.25. Brand New Transistors BF115, BF173, BC171, BC153, BC135, BC113, BC117, BC115, BA102, BA129. All 10p each.

All prices include V.A.T. p. & p. 10p per order. Money back refund. S.A.E. for leaflets.

ELECTRONIC MAILORDER

(BURY) LTD.

62 Bridge St., Ramsbottom, Bury, Lancs. Tel. Rams 3036

PHILIP H. BEARMAN, 6 POTTERS RD., NEW BARNET, HERTS.

One of the finest range of new and makers rebuilt tubes in the country; every tube is tested before it leaves the premises. Delivery usually ex stock and sent securely packed daily. Commonwealth deliveries arranged.

FOR EXAMPLE: NEW TUBES TWO-YEAR GUARANTEE

		Cge.	(including insurance Mono)
CME1702, AW43-80, CRM173, MW43-80, MW43-69, CRM172, AW43-88, AW43-89, CME1705, CME1703 C17AF	17"	£6.46	55p
CME1903, CME1902, CME1901, AW47-90, AW47-91, A47-14W, C19AH	19"	£7.56	60p
CME2101, AW53-88, AW53-89, CRM211, CRM212, MW53-20, MW53-80, CME2104	21"	£8.66	65p
CME2303, CME2301, AW59-90, AW59-91 A59-15W, CME2308	23"	£10.45	65p

NEW TUBES (1601 as available)

*TSD282 (TSD217)	£13.75
A28-14W (Mullard)	£12.10
MW31-74	£3.30
TSD290/CME1201	£10.78
A31/120W-CME1220	£10.78
*13BP4	£15.40
MW36/24 & 44	£5.23
CME1602	£11.00
CME1713	£13.20
CME1906 }	£12.10
A47-13W }	
A47-11W & 26W	£9.35
A50-120W/CME2013	£11.55
†CME2306 }	£16.50
A59-13W }	
A59-11W & 25 or 23W	£12.65
CME2413/A61, 120W	£14.30

Makers Rebuilt Tubes :

CME1908 }	£6.05	CME2308 }	£8.25
.. 1903 }		.. 2303 }	
AW47-91 }	£6.05	AW59/91 }	£8.25
A47-14W }		A59/15W }	

10% V.A.T. HAS
BEEN INCLUDED
FROM 1/4/1973!

MAKERS COLOUR TUBES

17" A44/271X	4 YEAR GUARANTEE	All 90°	
19" A49.11X,	A49.191X	£53.90	
20" A51.110X	(510CKB22)	£55.00	PLUS
22" A55.14X,	A56.120X	£58.30	£1.50 Cge. + VAT
25" A63.11X, use	A63.200X	£62.70	packing and
26" A67.120X,	A66.120X	£64.90	breakage insurance

USUALLY EX STOCK EXCEPT A66.120X (short supply)

NOTE: Above prices from 1st April 1973 include 10% V.A.T.

ALL SEA
JOURNEYS
50p EXTRA

EIRE £2.00
EXTRA FOR
CUSTOMS
CLEARANCE

carriage up to 17" 55p.

* Two Year Guarantee Except TSD282 and 13BP4 1 year.

Please enquire regarding availability of rebuilds.





† Rebuild T/Panel (£13.20 (when available))
Telephone enquiries welcomed.

MONO QUANTITY DISCOUNTS IN CERTAIN CASES

OPEN SATURDAY MORNINGS
CLOSED THURSDAY AFTERNOONS

TELEPHONE: 01-449 1934/5. ALL ENQUIRIES SAE PLEASE

COLOUR TV

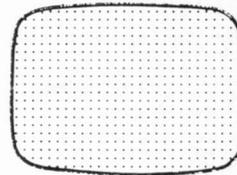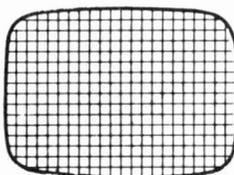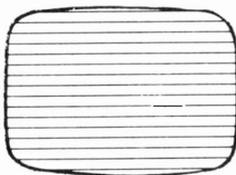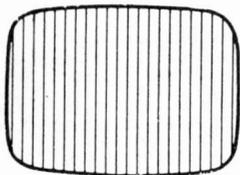

CROSS HATCH GENERATOR

Complete kit for Cross Hatch
Generator as described in
"TELEVISION" 1972
September issue

The only way to obtain 100%
convergence of colour guns
in any colour TV

£3.85

(inc 10% V.A.T.)
COMPLETE KIT POST PAID


Please send me the free
BI-PRE-PAK Catalogue
Please send me kits of parts
for Cross Hatch Generator
I enclose cheque/P.O./M.O.
for
Name _____
Address _____

BI-PRE-PAK LTD

DEPT. G. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.
TELEPHONE: SOUTHEND (0702) 46344

THE NEW UM4 "COLOURBOOSTER"

UHF/625 LINE

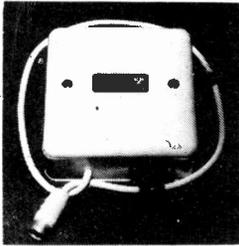

CAN PRODUCE
REMARKABLE
IMPROVEMENTS IN
COLOUR AND
PICTURE QUALITY
IN FRINGE OR
DIFFICULT AREAS
WITH SIGNIFICANT
REDUCTION IN
NOISE (SNOW).

HIGH GAIN—VERY LOW NOISE
FITTED FLY LEAD—INSTALLED IN SECONDS
HIGHEST QUALITY COMPONENTS
IVORY PLASTIC CASE $3\frac{1}{2} \times 3\frac{1}{2} \times 1\frac{1}{2}$ CORK BASE
CHANNELS: Group A, Red code 21-33
Group B, Yellow code 39-51
Group C-D, Green code 52-68

EQUALLY SUITABLE FOR BLACK AND WHITE

Also the M4 DUAL BAND VHF UNIT
BOOSTS ALL BAND III and ANY SPECIFIED
BAND I CHANNEL SIMULTANEOUSLY
NOMINAL GAIN 16-18 DB BOTH BANDS

PRICES BOTH TYPES:

Battery model £4.17 Mains version £6.50

Including VAT. Postage 9p

TRANSISTOR DEVICES LIMITED

6 ORCHARD GARDENS, TEIGNMOUTH, DEVON
Telephone: Teignmouth 4757

A. MARSHALL & SON (LONDON) LTD.,

SEMICONDUCTOR SPECIALISTS

42 CRICKLEWOOD BROADWAY, LONDON, N.W.2

Telephone: 01-452 0161/2 Telex: 21492 Cable: Coninst London

NEW LOW PRICES LARGEST RANGE BRAND NEW
FULLY GUARANTEED

★

We Supply

COMPLETE KITS for the following units:

Television Kit No. 1 **£8.42**

PAL Decoder

Television Kit No. 4 **£8.26**

I.F. Strip


Television Kit No. 8 **£6.66**

R.G.B. Board

Television Kit No. 10 **£7.50**

Time-Base

REBUILT TUBES!

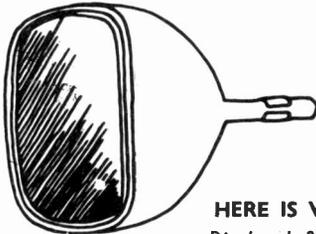

YOU'RE
SAFE
WHEN YOU
BUY FROM
RE-VIEW!

HERE IS WHAT YOU PAY:

Mono	Rimband & Twin Panel	Colour
15-17" £5.00	19" £7.00	19" £25.00
19" £5.50	23" £9.00	22" £25.50
21" £6.50	24" £10.00	25" £30.00
23" £7.50		26" £32.50

Carriage 75p

Exchange Basis
(carriage-ins. £1.50)

INC V.A.T.

Cash or cheque with order, or cash on delivery

- ★ Each tube is rebuilt with a completely new gun assembly and the correct voltage heater.
- ★ Each tube comes to you with a guarantee card covering it for Mono Tubes, two years against all but breakage.
- ★ Each tube is insured on the journey.
- ★ Each tube is rebuilt with experience and know-how. We were amongst the very first to pioneer the technique of rebuilding television tubes.

RE-VIEW ELECTRONIC TUBES

237 London Road, West Croydon, Surrey
Tel. 01-689 7735

SPECIAL OFFER

Recording Tapes Standard Play

10 $\frac{1}{2}$ " 2,400ft. £1.25 to clear

Package & Posting 20p

100-watt Guitar Amplifier—complete
kit with case and all components **£23.50**

"SCORPIO"

Capacitor discharge ignition system (as described in
Practical Electronics, Nov. 1971).

COMPLETE KIT £10.00 P. & P. 50p.

We Stock Full Range of:

Motorola consumer I.C.s

RCA Cos-Mos

Signetics popular I.C.s

★

**ALL PRICES EXCLUSIVE
OF V.A.T.**

130306

Which of these 165 career opportunities could earn you £10... £15...even £30 extra a week?

In a job you really enjoy

How to qualify in your spare time for a better job

Make yourself *worth* more and you'll earn more. It's as simple as that. There are always plenty of people to do the routine work - but, right now, key jobs are going begging for lack of suitably qualified men to fill them. *The basic qualification is technical know-how.* When you've got that, you're in demand - out in front.

Are you ambitious - willing to set aside about 60 minutes a day for home study? If you are, B.I.E.T. can give you the technical knowledge you need - change your entire future prospects.

It's easier than you think...

Make no mistake about it - you *could* do it. Most people have unused ability. A low-cost B.I.E.T. course helps you discover this hidden ability - makes learning enjoyable and so much easier than it used to be. The B.I.E.T. simplified study system gets results fast.

We've successfully trained thousands of men at home - equipped them for higher pay and better, more satisfying jobs, steered them safely through City and Guilds examinations - enabled many of them to put letters after their name.

With the help of B.I.E.T., you too could soon be on your way to better things.

OTHERS HAVE DONE IT - SO CAN YOU

Many of the successful B.I.E.T. students who get a recognised qualification never thought they had the brains to do it. But you don't need outstanding brain-power or talent - not even any special education. With enthusiasm, a little determination and a B.I.E.T. home training, ordinary, average ability will see you through. We've proved it over and over - *thousands* of times, in fact!

BEST VALUE FOR MONEY HE EVER OBTAINED.

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course" - *Student D.I.B., Yorks.*

HE GOT OUT OF A BAD JOB INTO ONE HE LOVED.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects" - *Student J.A.O., Dublin.*

HE MADE FOUR TIMES AS MUCH MONEY.

"My training with B.I.E.T. quickly changed my earning capacity and in the next few years, my earnings increased fourfold" - *Student, C.C.P., Bucks.*

FREE 76-PAGE BOOK

can put you on the road to success through a B.I.E.T. Home Study Course. It's yours for the asking, without obligation. Post coupon for your FREE COPY TODAY!



Choose from this list

- | | | | | | |
|------------------------------------|--------------------------|---------------------------------------|--------------------------|----------------------------|--------------------------|
| MECHANICAL | <input type="checkbox"/> | DRAUGHTSMANSHIP | <input type="checkbox"/> | Constructional Engineering | <input type="checkbox"/> |
| A.M.S.E. (Mech.) | <input type="checkbox"/> | A.M.I.E.D. | <input type="checkbox"/> | Construction | <input type="checkbox"/> |
| C & G Agric. | <input type="checkbox"/> | Design of Elec. Machines | <input type="checkbox"/> | Surveyors | <input type="checkbox"/> |
| Mechanics | <input type="checkbox"/> | Die & Press Tool Design | <input type="checkbox"/> | Institute | <input type="checkbox"/> |
| Diesel Eng. | <input type="checkbox"/> | Electrical Draughtsmanship | <input type="checkbox"/> | Clerk of Works | <input type="checkbox"/> |
| Eng. Inspection | <input type="checkbox"/> | Gen. Draughtsmanship | <input type="checkbox"/> | Geology | <input type="checkbox"/> |
| Eng. Metallurgy | <input type="checkbox"/> | Jig & Tool Des. | <input type="checkbox"/> | Health Eng. | <input type="checkbox"/> |
| Inst. Eng. & Tech. | <input type="checkbox"/> | Techn. Drawing | <input type="checkbox"/> | Hydraulics | <input type="checkbox"/> |
| Inst. Motor Ind. | <input type="checkbox"/> | | | Inst. of Builders | <input type="checkbox"/> |
| Mainten. Eng. | <input type="checkbox"/> | | | Inst. Works & Highway Sup. | <input type="checkbox"/> |
| Mechanical Eng. | <input type="checkbox"/> | | | Painting & Dec. | <input type="checkbox"/> |
| Sheet Metal Work | <input type="checkbox"/> | | | Public Hygiene | <input type="checkbox"/> |
| Welding | <input type="checkbox"/> | | | Road Engineer. | <input type="checkbox"/> |
| | | | | Structural Eng. | <input type="checkbox"/> |
| | | | | Surveying | <input type="checkbox"/> |
| ELECTRICAL & ELECTRONIC | <input type="checkbox"/> | RADIO & TELECOMMUNICATIONS | <input type="checkbox"/> | GENERAL | <input type="checkbox"/> |
| A.M.S.E. (Elec.) | <input type="checkbox"/> | Colour TV | <input type="checkbox"/> | Council of Eng. Inst. | <input type="checkbox"/> |
| C & G Agric. | <input type="checkbox"/> | C & G Radio/TV/Electronics | <input type="checkbox"/> | Farm Science | <input type="checkbox"/> |
| Mechanics | <input type="checkbox"/> | C & G Telecomm. Tech. | <input type="checkbox"/> | General Educat. | <input type="checkbox"/> |
| C & G Elec. Eng. | <input type="checkbox"/> | Prac. Radio Elec. (with kit) | <input type="checkbox"/> | Gen. Plastics | <input type="checkbox"/> |
| C & G Elec. Inst. | <input type="checkbox"/> | Radio Amateurs Exam. | <input type="checkbox"/> | Pract. Maths | <input type="checkbox"/> |
| C & G Elec. Tech. | <input type="checkbox"/> | Radio Servicing & Repairs | <input type="checkbox"/> | Pract. Slide Rule | <input type="checkbox"/> |
| Computer Elect. | <input type="checkbox"/> | Radio & TV Eng. | <input type="checkbox"/> | Pure & Applied | <input type="checkbox"/> |
| Elec. Maths | <input type="checkbox"/> | Trans. Course | <input type="checkbox"/> | Refrigeration | <input type="checkbox"/> |
| Elec. Science | <input type="checkbox"/> | TV Main. & Serv. | <input type="checkbox"/> | Rubber Tech. | <input type="checkbox"/> |
| Electronic Eng. | <input type="checkbox"/> | | | Sales Engineers | <input type="checkbox"/> |
| Electrical Eng. | <input type="checkbox"/> | | | Tech. Report Writing | <input type="checkbox"/> |
| Install & Wiring | <input type="checkbox"/> | | | Timber Trade | <input type="checkbox"/> |
| | | | | University Ent. | <input type="checkbox"/> |
| MANAGEMENT & PRODUCTION | <input type="checkbox"/> | AUTO & AERO | <input type="checkbox"/> | | |
| Auto. Control | <input type="checkbox"/> | Aero Eng. | <input type="checkbox"/> | | |
| Computer Prog. | <input type="checkbox"/> | A.M.I.M.I. | <input type="checkbox"/> | | |
| Electronic Data Processing | <input type="checkbox"/> | A.E.C. Cert. | <input type="checkbox"/> | | |
| Estimating | <input type="checkbox"/> | Auto Engineer. | <input type="checkbox"/> | | |
| Foremanship | <input type="checkbox"/> | Auto Repair | <input type="checkbox"/> | | |
| Inst. Cost & Man | <input type="checkbox"/> | C & G Auto. Eng. | <input type="checkbox"/> | | |
| Accountants | <input type="checkbox"/> | Garage | <input type="checkbox"/> | | |
| Inst. Marketing | <input type="checkbox"/> | Management | <input type="checkbox"/> | | |
| Metrication | <input type="checkbox"/> | MAA/IMI Dipl. | <input type="checkbox"/> | | |
| Motor Trade Man. | <input type="checkbox"/> | Motor Vehicle Mechanics | <input type="checkbox"/> | | |
| Network Plan. | <input type="checkbox"/> | | | | |
| Numerical Cont. | <input type="checkbox"/> | CONSTRUCTIONAL | <input type="checkbox"/> | | |
| Operational | <input type="checkbox"/> | A.M.S.E. (Civil) | <input type="checkbox"/> | | |
| Research | <input type="checkbox"/> | Architecture | <input type="checkbox"/> | | |
| Personnel Man. | <input type="checkbox"/> | Building | <input type="checkbox"/> | | |
| Planning Eng. | <input type="checkbox"/> | Building Drawing | <input type="checkbox"/> | | |
| Production Eng. | <input type="checkbox"/> | Build. Foreman | <input type="checkbox"/> | | |
| Quality Control | <input type="checkbox"/> | C & G Agric. | <input type="checkbox"/> | | |
| Salesmanship | <input type="checkbox"/> | Mechanics | <input type="checkbox"/> | | |
| Storekeeping | <input type="checkbox"/> | Carpentry & Join. | <input type="checkbox"/> | | |
| Work Study | <input type="checkbox"/> | Civil & Municipal | <input type="checkbox"/> | | |
| Works | <input type="checkbox"/> | Engineering | <input type="checkbox"/> | | |
| Management | <input type="checkbox"/> | | | | |

PLUS 58 'O' & 'A' LEVEL GCE SUBJECTS

tick here

Coaching for many major exams, including C & G and assistance in ONCIHNC.

IT PAYS TO BE QUALIFIED! POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept BTV05 Aldermaston Court, Reading RG7 4PF CF BTV05
Please send full details and FREE 76-Page Book, without obligation.

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____ AGE _____



Accredited by C.A.C.C. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

ACT NOW - DISCOVER FOR YOURSELF

It costs no more than a stamp to find out how we can help you. Tick the subject that interests you. Then post the coupon (or write). We'll send you an interesting 76-page book that will open up for you a whole new world of opportunity - and it's FREE.

B.I.E.T., Aldermaston Court, Reading RG7 4PF.