

UNCOMMON AERIAL SYSTEMS

Practical Wireless

3^D


Published every Wednesday by
GEORGE NEWNES LTD.

Vol. 5.—No. 108.
October 13th, 1934.

Registered at the G.P.O. as a Newspaper.

AND AMATEUR TELEVISION
EDITED BY F. J. CAMM.

Circuits for the EXPERIMENTER

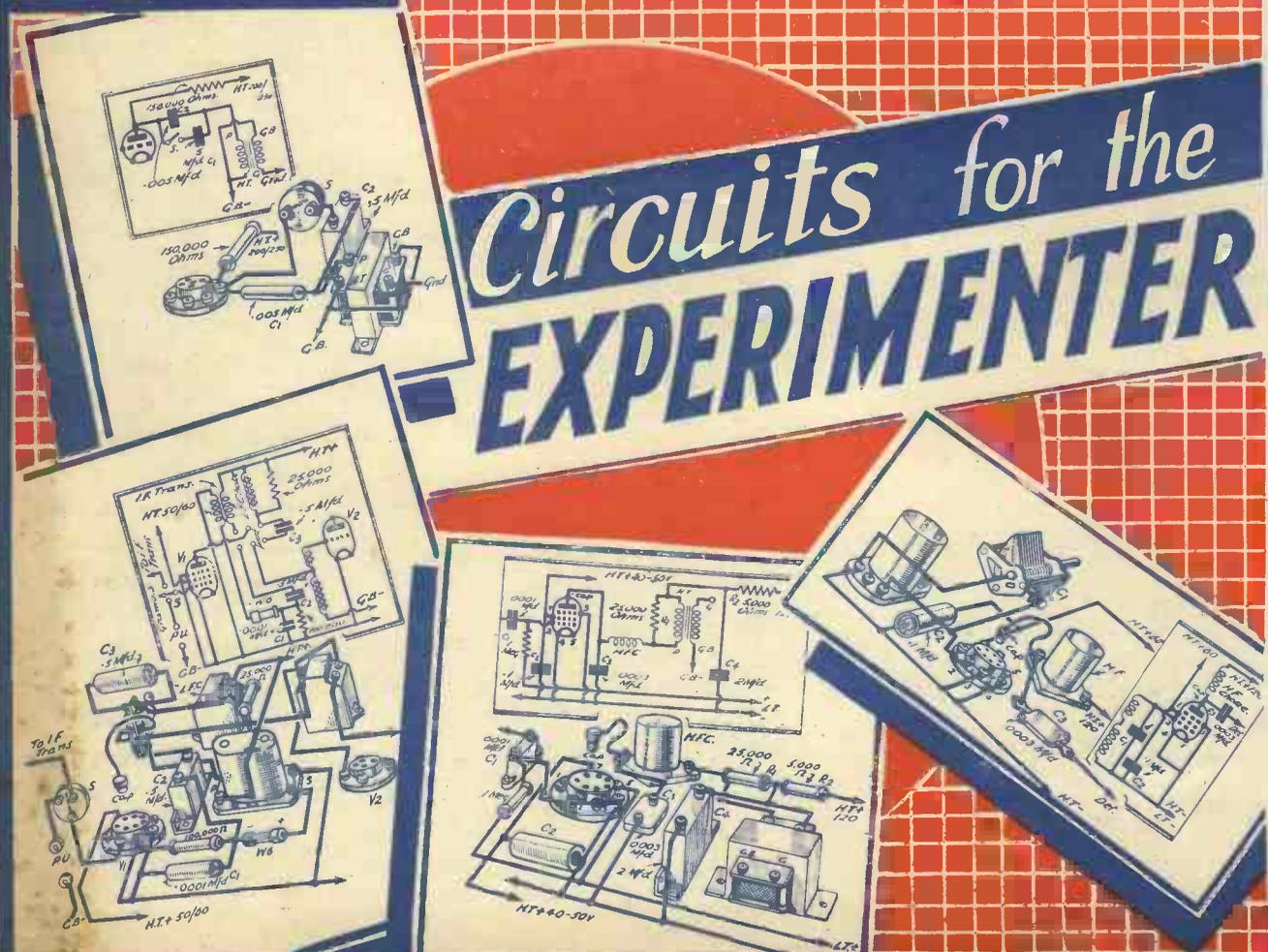


STENTORIAN SPEAKERS

PLEASE send all your HIRE PURCHASE ORDERS to The PETO-SCOTT Co. Ltd. 77, City Road, LONDON, E.C.1.

YOURS FOR

ALL MODELS

The ear alone is not enough...

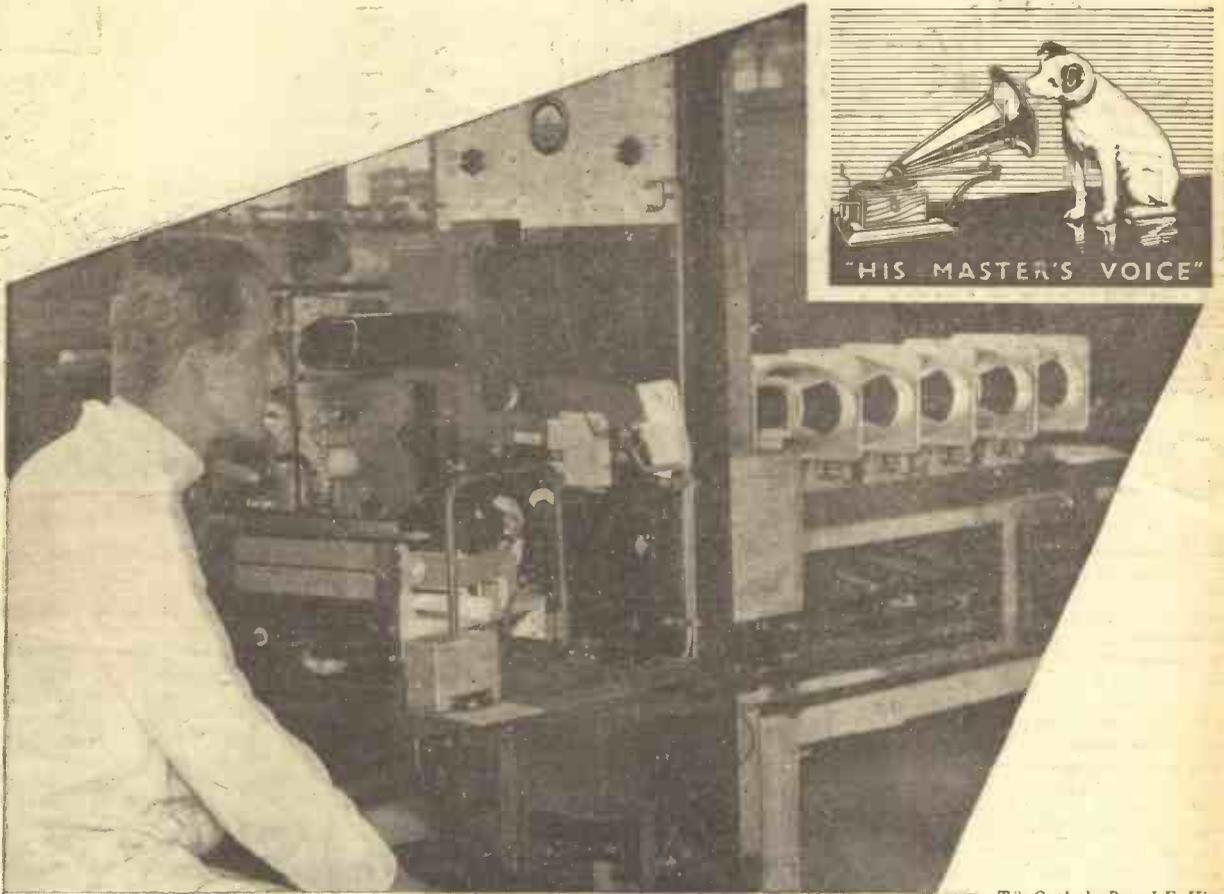

Science and sight combine to test "His Master's Voice" true-to-life tone. The Cathode Ray oscillograph is one of the wonders of science, for it turns sound into something you can see. It converts a musical composition into a graph. This has been incorporated in apparatus specially designed by "His Master's Voice" Research engineers for checking the performance of the intermediate frequency stages of "His Master's Voice" superheterodyne instruments.

The Cathode Ray I.F. Visual Ganging Apparatus is one of the hundreds of testing fixtures used in the "His Master's Voice" factories at Hayes. This apparatus gives a visual indication of the shape of the response curve, and ensures the correct adjustment of the intermediate frequency stages in each superheterodyne radio chassis. An unmodulated oscillator varying by approximately plus and minus 15 K.C. from 117 K.C. is fed into the receiver and the output from the second detector is viewed on the oscillograph. Any variation or inaccuracy in the response curve is clearly visible, and is corrected, if necessary, so that a uniform response is obtained throughout the audible range, in addition to the highest possible degree of selectivity.

"His Master's Voice"

THE GRAMOPHONE COMPANY LTD · 98-108 CLERKENWELL ROAD · LONDON · EC1

IS THE FRAME AERIAL DEAD? SEE PAGE 138



Practical Wireless

EDITOR:
Vol. V. No. 108 || F. J. CAMM || Oct. 13th, 1934.
Technical Staff:
W. J. Delaney,
H. J. Barton Chapple, Wh.Sch., B.Sc. (Hons.), A.M.I.E.E.,
Frank Preston, F.R.A.

ROUND *the* WORLD of WIRELESS

Cardiff Symphony Orchestra

THIS popular orchestra, which is composed chiefly of musicians who are not in regular employment, will be heard by West Regional listeners on October 14th. Garforth Mortimer, the conductor, evolved a scheme by which unemployed musicians in the Cardiff area could meet for weekly rehearsals, and as a result the Cardiff Symphony Orchestra came into being. The rehearsals, were held regularly from October, 1933, until May, 1934; they were then suspended as many of the members found summer engagements, but in the beginning of September they were resumed. The artist in the concert will be Clifford Deri (baritone), who won the Gold Medal at the Royal Academy of Music in July of this year; he has been appointed Sub-Professor of Singing at the Academy.

Popular Organ Recitals

REGINALD FOORT, the well-known cinema organist, will be playing at the Regal Cinema, Ferensway, Hull, throughout the first part of the winter; and one of his recitals will be broadcast to North Regional listeners on October 17th. This constitutes his first Northern broadcast.

Another well-known cinema organist, Herbert Maxwell, makes his North Regional debut on October 20th, when he will broadcast for the first time from the Regal Cinema, Durham.

Variety from Liverpool

ON October 17th, a variety entertainment from the Pavilion Theatre, Liverpool, will be broadcast from the North Regional. The programme will include the following artists: Billy Merrin and his Commanders, David Poole (ventriloquist), Jim Jessiman (comedian), Lewis and Lann (acrobatic dancers), Henri Hilton (vocalist), Con and Syd Creole (dancers), and Hilder Baker (comedienne).

"All for t'love of a Lady"

THIS is the title of a Yorkshire comedy, written specially for the radio by George Beaumont, which will be broadcast from Leeds on October 16th. Produced by Robin Whitworth, it is being presented by James R. Gregson's Yorkshire Radio

Players—including James R. Gregson, Florence Gregson, and George Beaumont himself.

When the Lights Failed

MANY singers nowadays declare that they seldom get a kick out of their performances; everything goes according to plan, and naught emerges save the critics' comments in next day's papers. Frank Titterton, however, still manages to provide a measure of excitement for himself and his

? ? ? ?

An Announcement
of the
Greatest Importance
to
Home Constructors
will appear
NEXT WEEK

audiences. At an August "Prom," when he was the soloist in the recitative and aria, "Sound an Alarm," an enthusiastic but misguided member of the audience expressed his views on the music presentation; and a day or two ago the elements themselves conspired to restrain Titterton's vocal efforts. He was singing at Buxton when a terrific storm broke over the Winter Gardens. In the middle of his solo, "Lend Me Your Aid," all the lights went out, following a terrific crash of thunder. Without a pause Titterton continued singing, and thus prevented what might have developed into a serious panic among the audience of 2,000 people.

The B.B.C. Midland Orchestra

THIS new orchestra, consisting of thirty-five players, will give a programme which includes Grieg's "Peer Gynt Suite No. 1," on October 19th, Leslie Heward conducting. The orchestra will be employed all the year round by the B.B.C. It also forms the nucleus of the City of Birmingham Orchestra, whose concerts will be relayed as usual. There are two, for instance, in the Town Hall on October 20th—a Children's Concert in the afternoon, when Harold Gray will conduct, and a Beethoven Concert in the evening, when Leslie Heward conducts, and Tom Bromley (pianoforte) and the Orchestra play the Concerto in C Minor.

Welsh Orchestral Concert

THE monthly String Orchestral Concert in the Reardon Smith Lecture Theatre of the National Museum of Wales will be given on October 17th, and an hour's relay will be taken for West Regional listeners. The strings of the Western Studio Orchestra (augmented) will be conducted by Reginald Redman, and the Cardiff Ensemble will be heard in Frank Bridge's arrangements of "Sally in our Alley" and "Cherry Ripe." An interesting item will be Introduction and Folk Tune by Reginald Redman, which was given a first performance in London a short time ago.

"The Northern Concert Hall"

UNDER this general heading, ten concerts by the Hallé Orchestra, eight by the Liverpool Philharmonic, and four by the Leeds Symphony Orchestras will be broadcast to the North Region this season. Georg Szell, the young German conductor, is to direct the Hallé orchestra in their opening concert at the Free Trade Hall, Manchester, on October 18th. The programme includes Beethoven's "Egmont" overture, Richard Strauss's symphonic poem, "Tod und Verklarung" ("Death and Transfiguration") and the Symphony No. 1 in C by Brahms. Georg Szell is only twenty-seven years old.

ROUND the WORLD of WIRELESS (Continued)


A Talk from Chipping Campden

IN the broadcast of one of the "Microphone at Large" series, which is to be given on October 17th, London Regional listeners are to share with Midland Regional listeners in the diversion of a microphone visit to the lovely old market town of Chipping Campden, in the Cotswolds.

INTERESTING and TOPICAL PARAGRAPHS

to see small groups of fishermen on the quay or in the shelters of this little Cornish village with their heads close together, bending over a line of music from a new work.

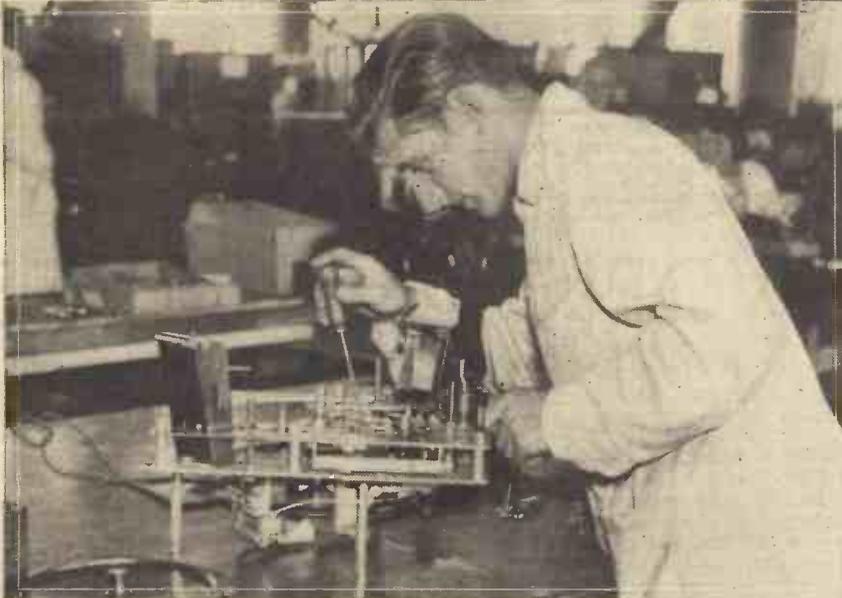ADJUSTING AUTOMATIC RADIO-GRAM MECHANISM.



Automatic mechanisms are now an integral part of medium- and higher-priced H.M.V. radio-gramophones. An engineer is seen here making a final adjustment before the automatic chassis is installed in a radio-gramophone at the H.M.V. factories at Hayes, Middlesex.

Mr. F. L. Griggs, R.A., R.E., the well-known artist, who is a local resident, will co-operate with Owen Reed, organizer of Midland Regional features. Others taking part are George Groves, an old waller expert on Cotswold stone, and Harry Keeley, who will talk of thatching, and of the times when he led an ox team for ploughing for a wage of threepence a day. It is also hoped that Polly Wayne, who is aged ninety-four, will give her reminiscences of the Dover Hill Games, an old Cotswold custom.

Out and About

ON October 17th, C. Henry Warren will give the first of his fortnightly talks in the Midland Regional programme, which are to be called "Out and About." These will include personal impressions of Midland character and of the countryside—something on the lines of Priestley's "English Journey." Mr. Warren read some of his own poems at the microphone in the Birmingham studio recently.

Loe Fishermen's Choir

THIS well-known choir will broadcast in the London and West Regional programmes on October 24th; its recital will also be included in the Empire programme. The Choir is believed to be the only one of its kind in Great Britain, being composed entirely of men connected with the fishing industry. As its members spend most of their time at sea, it is only on rare occasions that the whole Choir can be got together for practice, though it is no unusual sight

Lord Snell at the Microphone

ON October 17th, a speech of welcome by Lord Snell, Chairman of the L.C.C., to the delegates to the third international conference of the Youth Hostel Association will be relayed from the County Hall to London Regional listeners.

"Young Men in Industry"

THE first talk in this series will be given on October 15th from the Midland Regional by J. E. Irvine.

"Europe and its Peoples"

THE talk about Belgium in the Scottish School Series bearing the above title will be given on October 19th by Emeritus Professor C. Sarolea, who is a notable linguist and was a friend of the late King of the Belgians, whom he accompanied on an expedition to South America.

B.B.C. Northern Orchestra

THE North Region's new orchestra of thirty-five players will not, as previously announced, be called the North Regional Orchestra, but the B.B.C. Northern Orchestra. Conducted by T. H. Morrison and "led" by Alfred Barker, it will broadcast a concert on October 14th, featuring Louis Godowsky, the celebrated Leeds-born violinist. Another well-known Leeds artist, Zerubbabel Leikin, pianist, will broadcast on October 16th.

"During the Interval"

THE interval between the first and second parts of the opening Hallé concert on October 18th and of other

Northern Symphony concerts this season is to be filled by a new feature. It is called "During the Interval," and will take the form of a conversation between two members of the Free Trade Hall audience—not necessarily authorities on music—and will actually be relayed from the Free Trade Hall. They will, of course, discuss the concert, but not in specialized terms. Not only will the music claim their attention, but also the audience, and if any distinguished persons happen to be present these may, if convenient, be called up to the microphone to broadcast a message to listeners.

White Sails

THIS is the title of a musical play about two parties of holiday-makers on the Norfolk Broads, which will be produced by Martyn Webster on October 16th in the Midland Regional programme. The action includes the chase of a motor cruiser by a sailing yacht. Charles Hatton is the author of the book and lyrics, and Jack Hill is the composer. Hatton wrote the radio revue "Midland Masquerade" and the short play "Suicide Party" (relayed from the Birmingham Repertory Theatre), while Jack Hill is the young Birmingham pianist of "Two Jacks" and "The Three Knaves" fame.

Choral Recital from Tenbury Wells

ON October 18th there will be a choral recital from St. Michael's College, Tenbury Wells, which is a famous training centre for church musicians, and is also noted for its fine library of early scores. The programme, which is for Midland Regional listeners, will be introduced by the Warden, the Rev. E. H. Swann. The organist is Laurence Crosthwaite, B.Mus.

SOLVE THIS!

PROBLEM No. 108.

Smith worked in a boiler house attached to a large factory, and to pass a valve odd moments built up a small three-valve set which he installed in his workroom. In order to avoid charging difficulties he purchased a good car battery and connected the three cells in parallel so as to enable the accumulator to last some months without charging. He installed his set, fitted a good indoor aerial and obtained good results. After a few weeks signal strength fell off, and within a short time he could obtain no signals. Thinking that the battery had run down rather quicker than he expected, he made up a charger for his D.C. supply and connected the battery. After a suitable length of time he removed the accumulator, connected up the receiver again, but still could obtain no signals. Why? Three books will be awarded for the first three correct solutions opened. Address your envelopes to The Editor, PRACTICAL WIRELESS, Geo. Newnes, Ltd., 8-11, Southampton Street, Strand, London, W.C.2. Envelopes must be marked Problem No. 108, and must be posted to reach here not later than the first post Monday, October 15th, 1934.

Solution to Problem No. 107.

Although when Braddy tested his coupling condenser he could get no current through it, this was not a complete test, as it only proved that there was no short circuit. Actually, one of the terminals had become disconnected, and the condenser was therefore open-circuited. This was the cause of his trouble.

Books have been forwarded to the following readers in connection with Problem No. 106—

R. North, 14, Trinity Crescent, Sunningdale.
J. C. Rennie, Cardonna, Campbell Street, Wistaw, Lanarkshire.

CIRCUITS FOR THE EXPERIMENTER

Details of Some Interesting and Efficient Circuit Arrangements Are Given in this Informative Article.

OF the many multi-electrode valves that have been introduced during the past few months, the H.F. pentode is probably the most widely used, this being mainly due to the variety of duties which this valve is capable of performing; it can be satisfactorily employed as an H.F. amplifier, an I.F. amplifier, a detector, and even as an L.F. amplifier if it is followed by a suitable coupling.

Advantages of the H.F. Pentode

In receivers employing two H.F. stages, with ordinary S.G. valves, overloading of

shows a suitable circuit arrangement for a battery pentode. When a mains type is used, it is advisable to parallel-feed the transformer, using a 100,000 ohms anode resistance, a 500,000 ohms resistance between the screening grid, and H.T. of 200 to 250 volts, and a bias resistance of approximately 1,500 ohms. These values are subject to slight alteration to suit different valve types, however.

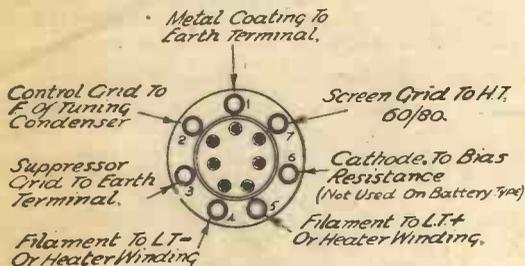


Fig. 1.—The valve holder terminal wiring of a 7-pin H.F. pentode.

the second valve often occurs. The advantage of the H.F. pentode over the ordinary S.G. valve is that a high voltage input can be handled without distortion, and therefore this type of valve is very suitable for use in the second H.F. stage. It can also be used to advantage in the first stage, of course, but unless the input voltage from the aerial is very high, the improvement obtained would not justify the substitution of a pentode for a relatively new S.G. valve.

There are four-pin battery H.F. pentodes available that can be substituted for an S.G. valve without the necessity for wiring alterations. When a seven-pin type is used, however, a seven-pin holder must be fitted in place of the four-pin type. Fig. 1 indicates the holder connections, and Fig. 2 shows a typical H.F. stage using a seven-pin pentode, and the valve electrode numbers shown in Fig. 2 correspond with the holder numbers shown in Fig. 1. The top cap of the valve cannot be shown, of course, but this is connected to the anode. When a mains pentode is fitted in place of an S.G. valve, a slight alteration of the screen-grid resistance values is necessary in most cases.

As a Detector

The H.F. pentode can generally be satisfactorily used in place of a triode detector, and this substitution should result in a marked increase of volume; Fig. 3

As an I.F. and L.F. Amplifier

Some of the modern superhets employ a Westector as second detector, followed by a pentode output valve, and it is often taken for granted

that satisfactory gramophone reproduction cannot be obtained with such a receiver. If an H.F. pentode is used in the I.F. stage preceding the Westector, however, this valve may be used as an L.F. amplifier if the switching arrange-

ment shown in Fig. 4 is used. It will be noted that when the switch is on "gram," the pentode is choke-transformer coupled to the output valve, and

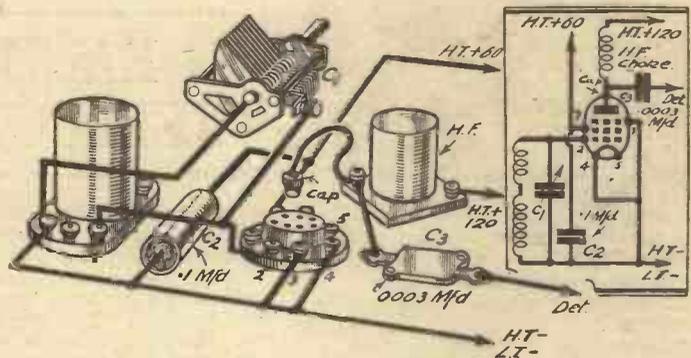


Fig. 2.—Circuit showing a typical H.F. stage using a 7-pin H.F. pentode.

therefore adequate L.F. amplification is obtained.

Bass Boosting Circuit

Some gramophone records are deficient in the bass register, and therefore, in an amplifier used for gramophone amplification, an L.F. coupling that can be adjusted to provide accentuation of frequencies below 100 cycles is desirable. This bass boosting effect may be obtained by means of the circuit shown in Fig. 5. When bass accentuation is desired, switch S should be opened; the transformer winding and the condenser C1 will then produce a resonance in the lower register. A good class transformer should be used, and the value of C1 should be carefully chosen—a capacity of approximately .005 will be found suitable. If a battery valve is used, the anode resistance shown in the diagram should be replaced by a high inductance choke, in order to avoid loss of voltage.

Push-pull Output

It is generally agreed that a well-designed push-pull output (Continued overleaf)

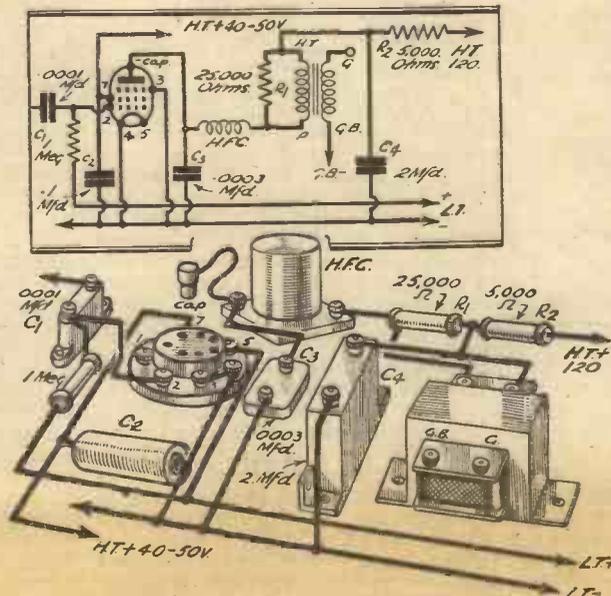


Fig. 3.—An H.F. pentode used as a detector.

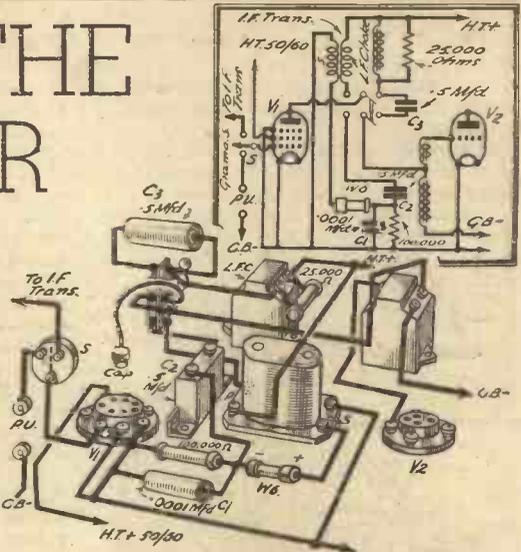


Fig. 4.—H.F. pentode used as L.F. amplifier.

(Continued from previous page)

stage provides practically distortionless amplification, this being mainly due to the absence of the harmonic distortion which is prevalent in an output stage employing a single valve—more especially if this is a pentode.

If best results are to be obtained from a push-pull stage, however, the electrical characteristics of the valves should be

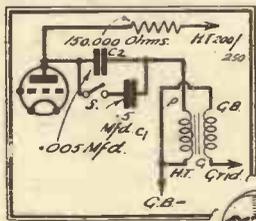


Fig. 5.—Showing bass-boosting coupling.

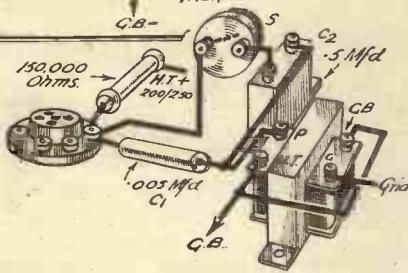


Fig. 6.—Push-pull output stage with separate L.T. supply for each valve.

alike, and uniform current must flow through the output transformer primary. The presence of D.C. in a transformer winding tends to lower the effective inductance; a push-pull output transformer primary winding is centre tapped, however, and the current is passed through the two halves in opposite directions, and, therefore, provided the current in each half is of the same value, the net effect of the direct current on the core will be zero. In order to obtain this desired effect, however, the anode current consumption of the two valves must be exactly alike. In a battery operated receiver this can be easily effected by using an input transformer having a separate secondary winding section for each valve, and adjusting the battery bias voltage until both valves pass the same current. When mains valves with automatic bias are used, the necessary adjustment is not so easily effected.

It is the general practice to fit a common bias resistance for the two valves, having a value of half that specified for one valve, but adjustment of this resistance varies

the consumption of both valves simultaneously, and therefore it is suggested that a separate heater winding, and a separate bias resistance, be used for each valve if best results are desired. The circuit arrangement of a push-pull stage of this type is shown in Fig. 6.

Variety Applause

THE question of applause at the Vaudeville Entertainments put on the ether *via* the studios at Broadcasting House is still making some of the officials "hot and bothered." I believe that what listeners most complain of is the senseless giggling and laughter at the actions of the artist rather than the spoken humour, which more often than not drowns the joke the listener is straining to hear. Personally, I do not think the fault can be placed at the door of either the artist, audience, or the sensitivity of the wireless receiver. Where the trouble actually originates is in the placing of the microphone in relation to the audience and the artist. Whenever present at one of these performances I have particularly noticed this point, and, more often than not, the audience has been much too near the mike. During the periods an outside broadcast has been relayed from one of the theatres the occasions have been very rare when a similar trouble has occurred. The reason is very plain, for the artist is facing the pick-up and the audience behind it, whereas in the studio in most cases both are facing it. If this point received the attention it deserves there would not be many complaints of interference with the transmission, and the very necessary background for realistic reproduction of this kind of entertainment would be subdued to its proper relationship.

A Phantom Lead-in

VISITING a friend who was living on one of the new estates which are springing up in all parts of the country, I was rather interested to notice on the window-pane of his dining-room a piece of tinfoil which was connected to the lead-in of his wireless receiver. On enquiry he informed me that the landlord refused to allow holes to be drilled in the window frame in order to accommodate the usual lead-in tube from the aerial to the set. In order to combat the difficulty he had attached the aerial to a piece of tinfoil fastened to the outside of the

RANDOM REFLECTIONS

window with adhesive, and another directly opposite on the inside connected to the wire of the aerial terminal of the set. The size of the foil was 9ins. square, and of course the glass window-pane was acting as a dielectric and the two pieces of foil as plates of a condenser, causing the current to flow from one plate to the other through the medium of capacity coupling. The selectivity of his receiver was quite astonishing, and it is a simple method to adopt where such difficulties occur, or even in the case of the present general system of iron frames.

Losing the Set!

I CAME across a very interesting case the other day which apparently settles a much discussed question. A problem was set for a magistrate in a North Country town with reference to a radio pirate. In short, he had been operating a receiving set without the usual Post Office licence, and, in giving judgment a fine was inflicted and the set ordered to be confiscated. Quite a number of people have been under the impression that this was an extremely harsh decision, and that the fine would meet the case. It is, however, clearly set out in Clause 3, Section I, of the Wireless Telegraphy Act, 1904, that the penalty could be justified, as the clause in question reads as follows: "If any person establishes a wireless telegraph station without a licence, or installs, or works, any apparatus for wireless telegraphy without a licence, he shall be guilty of a misdemeanour, and be liable, on conviction under the Summary Jurisdiction Acts, to a fine not exceeding One hundred pounds, or to imprisonment, with or without hard labour, for a term not exceed-

ing twelve months, and in either case be liable to forfeit any apparatus for wireless telegraphy installed, or worked, without a licence, but no proceedings shall be taken against any person under this Act except by order of the Postmaster-General, the Admiralty, the Army Council, or Board of Trade." This makes the position quite clear and should be carefully noted, not only by those who use a receiving set, but the many, who, at the present time, are experimenting with transmitting circuits without first having obtained the necessary permit to do so from the Postmaster-General.

Crystal Palace Acoustics

IN the past many great musical festivals and other functions of international importance have taken place at the Crystal Palace which would have been worthy of the attention of the outside broadcast engineers of the B.B.C. I used to wonder why a move had not been taken to broadcast some of these great entertainments until I made enquiries of a B.B.C. official, and was then told the acoustic properties of the great hall did not lend themselves towards making for a satisfactory transmission. You can imagine my surprise when I was informed the other day by an engineer of the H.M.V. Gramophone Company that the trouble with the acoustics had been defeated. He mentioned, when the competing bandmen at the recent National Band Festival were playing their test pieces in the Crystal Palace, they believed they were only playing to the thousands of people present in the building, whereas records were being made of the performances. It was feared, owing to the volume of the massed bands and the extraordinary acoustics of the building, that it might be impossible to obtain satisfactory records, and therefore the utmost secrecy was preserved. A mobile recording laboratory was hidden away in the grounds, while two microphones were built into the stage fittings. The resulting records are a revelation of perfect pick-up and reproduction. C. D. K.


ARE YOU NEW TO THE HOBBY?

Some Practical Advice on the Choice and Use of Tools for Home Construction

ALTHOUGH a wireless receiver may easily be constructed in the living-room, perhaps on the kitchen table, there is a great deal to be said for the correct method of proceeding with the task of marking out the necessary panel or baseboard and using good tools and instruments for the necessary cutting and fixing which has to be done. It must not be inferred from this that wireless receiver construction is a complicated procedure, and although many constructors do carry out the work with the aid of only a screw-driver and a bradawl, it is possible greatly to simplify the work by using good tools in the correct manner. The result of so doing will be reflected not only in the appearance of the finished work, but also in the performance.

The "Practical Wireless" Tool Kit

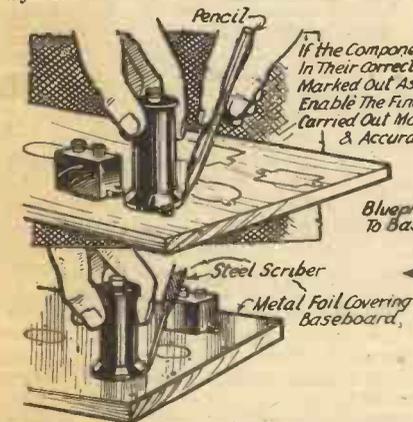Those readers who availed themselves of the tool kit which was recently presented by us will have the nucleus of a really



If the Components Are Arranged In Their Correct Positions & Marked Out As Shown, It Will Enable The Final Assembly To Be Carried Out More Quickly & Accurately.

When using a Blueprint

Blueprint Pinned To Baseboard.


The Baseboard Marked Out.

If A Full Size Blueprint Is Available The Positions Of The Components May Be Traced Through As Shown Above.

good constructor's outfit, and with the aid of these tools most normal constructional work may be carried out. If it is desired to supplement this kit, a 2ft. steel rule will be found one of the first additions. Such a rule is required when marking out the cabinet front, or squaring up a large baseboard, and it is not an expensive item. The scribe has already been given, but for those who are not fortunate enough to own the kit a nail may be used in an emergency for marking various surfaces. The small inset at the top of this page shows some of the items mentioned, together with other valuable accessories.

Using a Blueprint

Construction is greatly simplified when a blueprint is obtained, and although this is always to scale, it is not necessary to go to the extent of transferring all measurements from the paper to the baseboard. By placing the print upon the baseboard the various fixing centres may be pierced without seriously damaging the print and the components may then be mounted in the indicated positions. An alternative method is to use a sheet of carbon tracing paper. When a polished ebonite panel

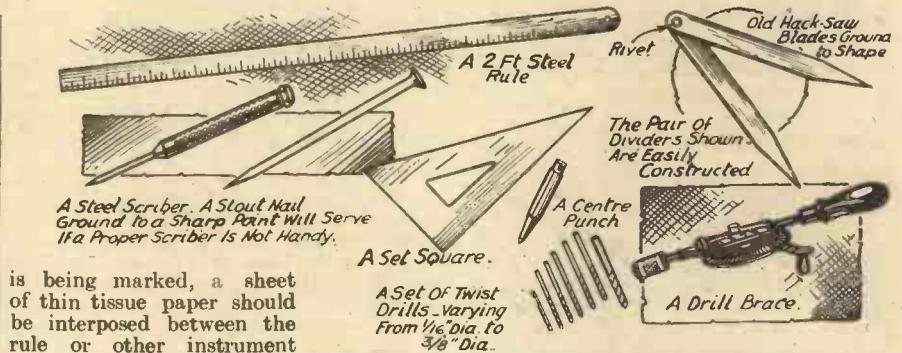

is being marked, a sheet of thin tissue paper should be interposed between the rule or other instrument in order to protect the surface of the ebonite, and a very good plan where the perfect surface of the ebonite is required on the finished article is to sandwich the panel between two thin boards (after placing thin tissue on each side of the panel) and then to carry


drilling holes of large diameter, it is often desirable to cut a number of small holes round the edge of the required piece, afterwards cleaning up the projections left when the centre-piece is removed. If a large twist drill is being employed the work should be carried out in two stages, drilling first from one side and then from the other. Slow cutting is advisable with ebonite in order to prevent the cutting instrument from binding, and also to prevent damage to the ebonite due to the heat which is generated.

Tools Which Are Valuable

Among the many tools which the keen constructor will find invaluable for his work may be mentioned the soldering iron and the brace. The actual type of iron will depend upon the means which are available for heating it, and thus the choice will be made between gas-heated, electric-heated or ordinary fire-heated types. The latter may, of course, be used in conjunction with a gas jet, although the special gas-iron will be found more convenient if a suitable gas tap is available. On this page are illustrated a number of parts with various notes relating to their use and with certain small points emphasized. To store the tools a neat rack can quickly be constructed, or a large box may be adapted as a tool box. Racks round the side of the box, or in the lid will serve to


(Continued overleaf)

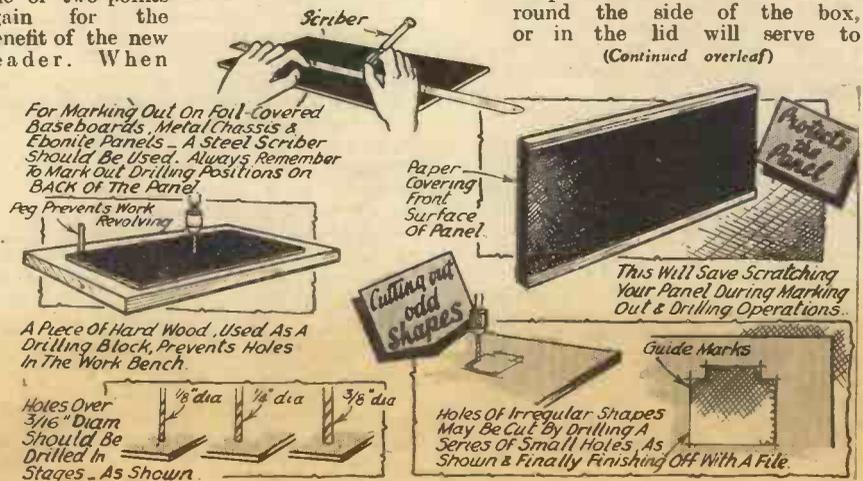out all work with the complete sandwich. When finished, the wood may be removed and the panel found undamaged. Ebonite may prove very troublesome if it is worked in the wrong manner, and although we have recently published an article on this subject, it would be as well to repeat one or two points again for the benefit of the new reader. When



SOLDERING IRONS.

STANDARD TYPE.

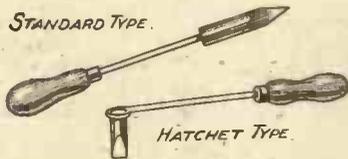


HATCHET TYPE.




AN ELECTRIC IRON.



A GAS HEATED IRON.

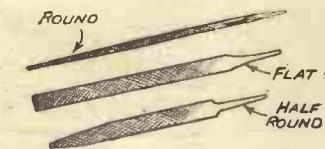

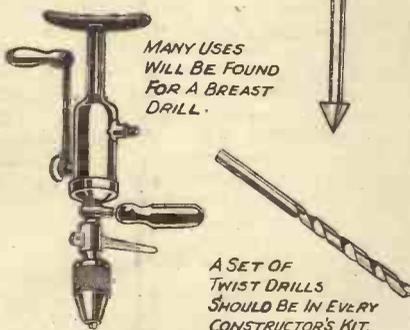A SET OF FILES WILL BE FOUND TO BE INDISPENSABLE.



MANY USES WILL BE FOUND FOR A BREAST DRILL.

A SET OF TWIST DRILLS SHOULD BE IN EVERY CONSTRUCTOR'S KIT.

(Continued from previous page)

accommodate the smaller tools and prevent them from becoming mislaid. By cutting slots in the rack which only just take the various tools there will be no danger of misplacing them with loss of time when next a special item is required and does not appear in its usual place.

A useful point which is worth noting, especially by those who do not do a great deal of work, is the inclusion of an oily rag in the tool chest. By wiping steel tools with this rag after use they are protected from rust, and to avoid soiling the work a clean rag may also be kept handy with which to wipe the tool when it is required for use.

A great deal of the information here given may seem obvious to many of our readers, but it will be found that a saving of time and temper always results in better work, and when it is desired to try out some circuit arrangement which might be described in our pages, more enjoyment will be added to the actual testing and trying of the finished work if the construction may be carried out expeditiously and without the necessity of waiting until a certain tool can be borrowed or purchased, or just lashing up the arrangement with the aid of improvised tools. Money spent on good tools is never wasted, and the handyman will no doubt find many uses in the home for the tools which are described here, in addition to their use in the pursuit of his hobby.

Beware of Cheap Tools

It should be borne in mind that certain tools rely for their efficiency upon the quality of the steel or material from which they are made, and therefore the constructor should guard against purchasing cheap tools (generally of foreign make), which will prove useless after a short time in use. For instance, some very cheap screw-drivers with a ratchet action handle are at present on the market. It will probably be found, however, that if a really tightly fixed screw is attacked with one of these instruments, the handle will twist and the blade of the driver will be distorted, or the ratchet mechanism will be destroyed. Similarly, cheap pliers can be obtained from market stalls and in popular bazaars. These are cast, and if very great force is employed in turning an obstinate nut, the handle will break off, and this may lead to a nasty cut or damage to some apparatus, owing to the sudden jolt as the pressure is removed. These are not imaginary cases, but are actual cases which have been brought to our notice, and a few extra shillings spent upon good



A JEWELLERS SCREWDRIVER IS HANDY FOR SMALL SCREWS.



A RATCHET SCREWDRIVER SAVES MUCH TIME.




A STEEL POINTED SCRIBER IS USEFUL FOR MARKING OUT THE POSITIONS OF COMPONENTS ETC..




A PATTERN MAKER'S HAMMER IS CONVENIENT FOR RADIO WORK.



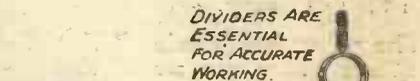A USE WILL ALWAYS BE FOUND FOR A BRADAWL & A TWIST GIMLET



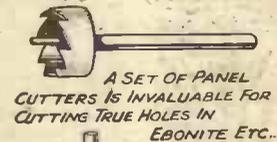DIVIDERS ARE ESSENTIAL FOR ACCURATE WORKING.



A SET OF PANEL CUTTERS IS INVALUABLE FOR CUTTING TRUE HOLES IN EBOONITE ETC..



ADJUSTABLE PANEL CUTTER.

tools will always be well repaid by long years of trouble-free service. An oil stone should, of course, find its place in the workshop or tool-case in order that those tools which require it may be kept provided with a sharp edge. A rub at frequent intervals will enable chisels, screwdrivers, and other similar tools to be kept in perfect condition.

The Variable Grid Leak

THERE are many wireless enthusiasts, even to-day, who look upon the grid leak as being a very mysterious thing both in construction and operation. It is true that it effects a very delicate operation, allowing the negative charge which accumulates on the grid to leak off at the proper rate. It has often been pointed out in the pages of PRACTICAL WIRELESS that if this charge that accumulates on the grid were allowed to reach too high a point, the efficient operation of the valve would be greatly interfered with. So it is of importance that the resistance of the leak be perfectly suited not only to the peculiar characteristics of the valve, but to the circuit in which the valve is used. Too many people overlook the importance of this device. Many receivers are unable to operate at their maximum efficiency simply because the grid leak is not of the proper resistance value. The resistance of grid leaks is measured in megohms, and a megohm is 1,000,000 ohms. Grid leaks are used having a resistance of from 25,000 to 5,000,000 ohms. When trying out a new

USEFUL HINTS

receiver, or valve in a detector circuit, it is always wise to try out several different values of grid leak in order to find the value which suits the valve used. A variable type of grid leak is undoubtedly ideal if it is possible to get a reliable one. Those old-fashioned carbon types of the past were never satisfactory, and resulted in more noises and poor reproduction than any other component which went to make up the finished receiver. It is a great pity some manufacturer does not make a speciality of a really reliable variable grid leak. For laboratory use, a simple but efficient variable leak can be made by drawing a thick line with Indian ink on a small piece of Bristol board, and using a sliding contact strip of phosphor bronze. This gives a variation over any desired limits according to size. Unfortunately a similar type could hardly be used in a general set because it would be too

susceptible to changes in atmosphere when used in that way.

Plate Voltages

THE radio experimenter who ignores the customary rules by trying out some wrinkle of his own without knowing exactly what is happening may find that his experiment proves to be a costly one. For instance, an amateur recently was experimenting with higher plate voltages than those specified by the makers. In the case in point the valve was designed for 150 volts maximum but he was running it with 350 volts, and could not understand why he got such a pretty blue glow in the valve. Of course when a valve shows the gassy blue glow of ionization it is useless for any kind of experiment. The user should be very cautious when increasing voltages above 150 on the ordinary radio valve, and particularly so in the case of the high-frequency stage. Too great a flow of current in the input circuit of a detector is not to be desired, since a great deal of distortion which is blamed on the low-frequency circuit originates in the grid circuit of the detector.

UNCOMMON AERIALS

A Single Length of Stranded Wire is Not Essential as an Aerial, and Some Interesting Variations of this Valuable Part of the Wireless Equipment are Here Described.

UNDER the Wireless Telegraphy Acts, 1904-1926, the P.M.G. permits the listener to erect an aerial the length of which shall not exceed 100 feet. In the early days of broadcasting the amateur endeavoured always to utilize the full length of 100 feet of stranded copper wire, although, as has been shown in these pages on several occasions, some variations in the horizontal length of wire are possible and also efficient. For instance, two wires arranged parallel to each other, and both supported parallel with the


considered it essential to use a length of stranded wire.

Properties of the Aerial

First of all, let us analyze the aerial system, which may be regarded as one plate of a condenser, the other plate of which is the ground, to which an earth wire runs from the wireless apparatus. The dielectric of this condenser is the air between these two plates. Bearing this fact in mind, it is not difficult to conceive many methods in which a condenser may be constructed to preserve a similar capacity to that obtained by a normal aerial and earth. Taking it as a fact that the earth must be retained, and considering the walls of the house as "earth" (owing to the fact that they are in direct contact with the ground) it is only necessary to furnish the second plate of the condenser, and obviously, this could be carried out by wrapping the 100 feet of stranded wire round a flat board and supporting it near the earth; by using a plate of metal having an equivalent surface area; or by using the wire wound round some spacing medium. Various manufacturers have, from time to time, manufactured aerials on these principles, and no doubt they will be familiar to many readers.

The "Cage" Aerial

In the simplest form, the method of arranging the 100 feet of wire in a compact manner is to be found in what is known as a cage aerial. As its name implies, a cage is formed with the wire and two end pieces. For the latter, two small wooden hoops of the type used by children are fitted with a strip of wood across the centre. These cross members are then fitted to the ends of a strip of wood (a broom-handle, for instance) so that they are about two feet apart and parallel to each other. One end of the wire is then anchored to one of the hoops, after which the wire is taken across to the opposite hoop, back again, and so on, until the total quantity of wire is used up. From one end a lead is taken to the aerial terminal of the receiver, and the cage is then erected on top of a mast clamped to the wall of the house; suspended from a horizontal pole projecting from the upper window of a house, or hung in an attic or under the roof. In view of the risk of the hoops becoming distorted due to dampness or rain, it is preferable to fit the device inside the roof under cover. The results obtained with this arrangement are quite good and

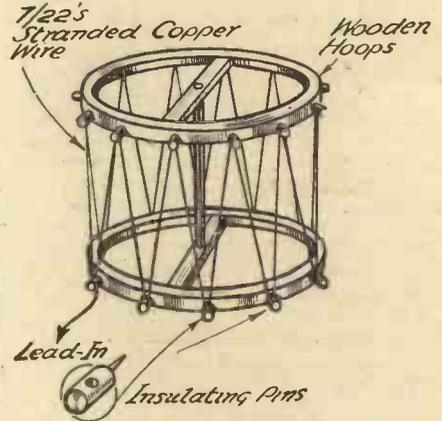


Details for constructing a simple cage-type aerial.

some latitude is possible in the size of the hoops, spacing between them, and the quantity of wire which is used. The principal advantage of this type of aerial is its non-directional property.

A "Brush" Aerial

An alternative method of using the wire is seen in the building of a brush, and a commercial aerial of this type is known as the "No-mast" aerial, illustrated on the left. The wire is cut into lengths, and these are all held at one end on a mass of metal held in a substantial insulator, which is fitted to a metal bracket for easy mounting. Again the principal advantage is the non-directional property, although

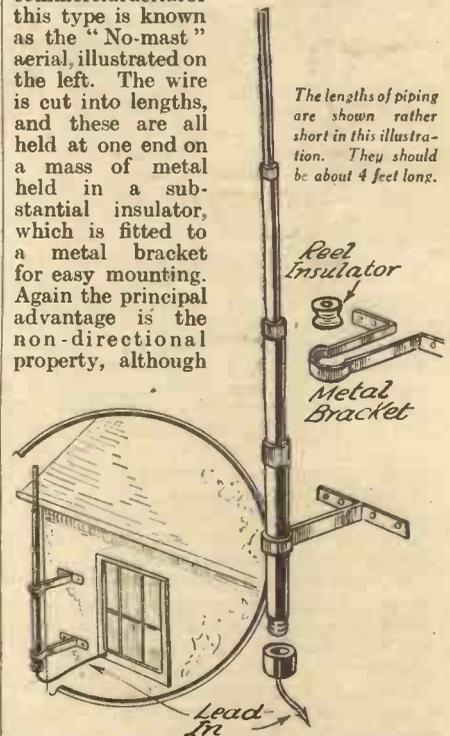


Details of construction of a vertical aerial built up from lengths of gas piping.

compactness also has a prominent place in its list of attributes.

A Plate Aerial

Instead of wire, actual metal plates may take the place of the pick-up apparatus already mentioned. That is to say, in the cage arrangement a sheet of copper may be nailed to the edges of the hoops with a leading-in wire soldered to the plate, whilst a narrow cone, or funnel, may be used to provide a modification of this scheme. Very little difference in performance will be noticed with the two types

(Continued overleaf)

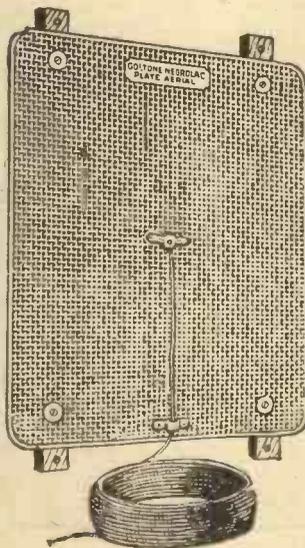

Two novel aerials; on the left a brush-type aerial (the No-mast), and on the right the Negrolac aerial.

ground, is an efficient arrangement where space is limited. An umbrella design, in which wires radiate from the top of a single mast towards the ground, has also been found to furnish good signal pick-up properties. There are, however, many other methods of "tapping" the wireless waves, in which either no wire at all, or at least very small quantities of wire, are utilized, and these will no doubt be of interest to the newcomer to wireless as well as to those who have previously



One of the latest commercial aerials, the Globe, produced by the New London Electron Works. The globe is of copper, and the lead-in is taken from the bottom of the globe.

(Continued from previous page)

of aerial, that is, plate or wire. As a variation, however, the metal may take the form of a flat plate, stretched across a wooden frame, with the latter nailed to the wall or chimney stack. A sheet, 2ft. by 18in., will be found to provide good results, and perforated zinc forms a suitable material for construction, being obtainable at the popular stores in a suitable handy roll. For the experimenter who prefers to purchase a ready-made aerial of this type, we may recommend the Negrolac Aerial manufactured by Messrs. Ward and Goldstone. This is well-made and provided with all fixing screws, etc. It costs £1 1s. 0d.


A "Ball" Aerial

Still another variation of the metal aerial is to be seen in the device which appeared for the first time at Radiolympia, and which is a product of the London Electric Wire Company. This takes the form of a ball or sphere of copper, with a suitable mounting bracket. It has all the attributes of the previous types of aerial, namely, compactness, non-directional effect, and good pick-up properties.

A Pipe Aerial

Short-wave experimenters have for years found that the vertical type of aerial proves more effective than a horizontal wire, and a very efficient and simply-erected aerial may be constructed from some lengths of gas-piping. Five 4ft. lengths of piping, varying in diameter from 1½in., and with reducing sockets for connecting each successive length, may be built up and held about eighteen inches from the wall by means of metal brackets. Insulation must be provided, either between the pipe and the bracket, or between the bracket and the wall. By fitting the brackets at suitable positions on the piping, ordinary reel insulators may be used to hold the pipe in position, a cross pin preventing the pipe from dropping through. This type of aerial should, of course, be arranged so that it projects some distance above the roof, and the leading-in wire should be anchored in a gas plug which may afterwards be screwed into the end of the lower section. A gas fitter will supply the piping and carry out the necessary tapping quite cheaply, and this aerial will be found highly effective. Many other variations of these schemes will no doubt suggest themselves to readers.

SOME EASILY-MADE MISTAKES!

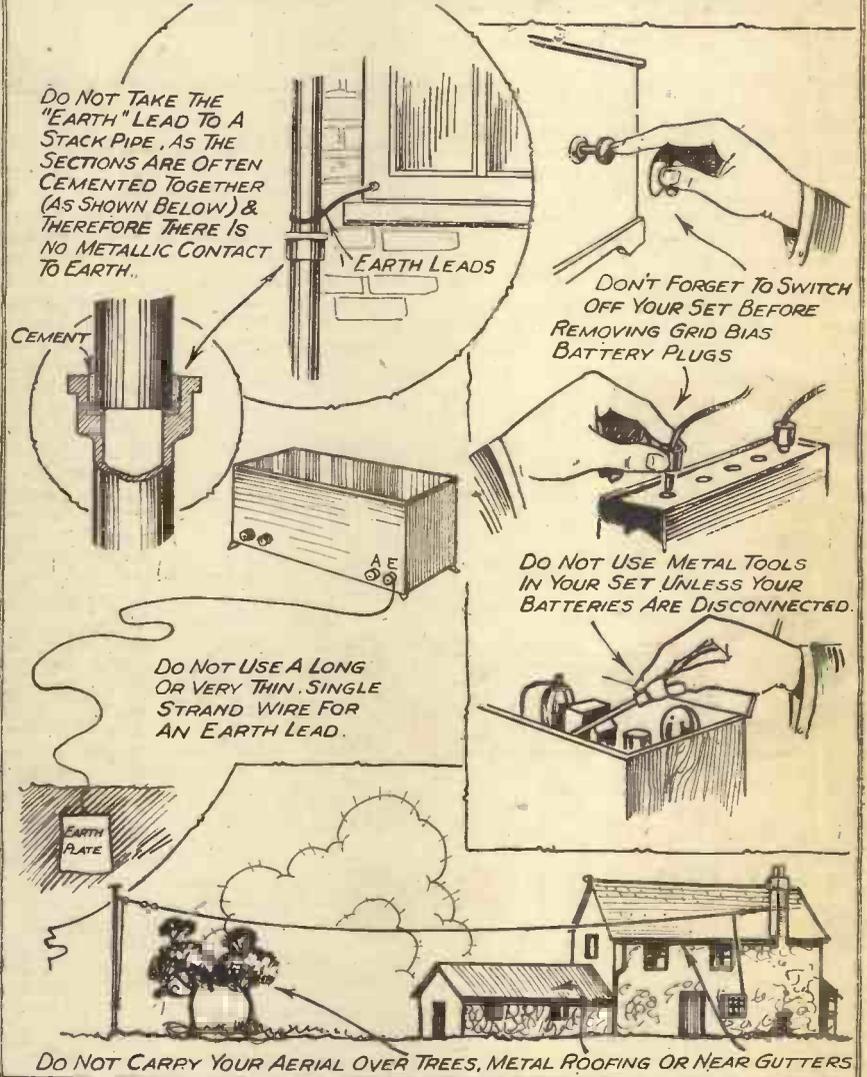

MARK TWAIN once said that while everybody talked about the weather nobody did anything about it. The reason I mention this is I have just opened three consecutive letters, each of which complain that broadcasting brings rain, wind and storm, and suggesting that something ought to be done to curtail the energy now being dissipated into the ether.

A Petition

I remember a few years ago the inhabitants of a well-known Derbyshire Spa signing a petition asking for the same curtailment, and while this was going on the West Country Press was full of letters from farmers. In the former case the excessive local rainfall was the cause, and in the latter the lack of it. Persons blame radio for everything—weather, illness, accidents, lawlessness, political topsy-turvydom, and, I suppose, insanity. One of the correspondents tells me that while radio has been developed and perfected, so have our varied weather

RADIO AND THE WEATHER


phenomena increased in violence. Another that the seasons are changed, and neither the winters nor summers are what they used to be. It is unfortunate for radio that people should advance radical theories that much of our unusual weather is due to radio activities in the ether, for such rumours spread rapidly into belief among credulous people. It seems to me the weather furnishes a topic about which many who are very ignorant believe they are very wise, and their greatest sport is to blame climatic changes on radio.

Radio Not to Blame

Weather variations have been with us from all time, and long before radio was dreamed of any unusual weather created consternation and excitement. Records which have

been kept by meteorologists of the changes in temperature, pressure, air movements, humidity, etc., near the most powerful radio stations, using the most accurate instruments for the purpose, show that no blame can be put on radio for unusual weather changes. The combined power of all the radio transmitting stations of the world which is put in the ether would hardly be enough to operate a respectable electric motor, much less affect the weather conditions. Artificial excitation is not such a simple point, and I well remember the experiments which were carried out in this connection in London during a drought some years ago, when rockets and gun-fire were employed in order to try and make the clouds discharge their much-needed moisture. The experiments did not produce any marked effects, and that the idea is futile is substantiated by the fact that no further experiments have been carried out in recent years when rain has been urgently needed by the country.

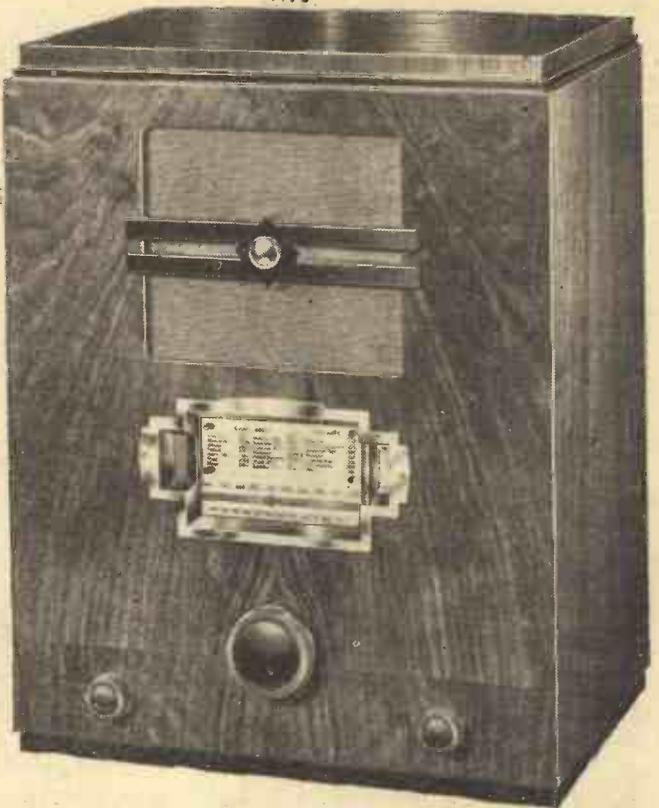A superb
de luxe RECEIVER
incorporating EVERY
up-to-date development



The
COSSOR
ALL-ELECTRIC
SUPERHET RECEIVER

Here is truly de luxe radio—an up-to-the-minute all-electric Superhet, designed and built on entirely new lines. With its neon tuning, its full A.V.C. and its many other features it brings you, with ease, real entertainment from the station of your choice, unmarred by other powerful transmissions.

De luxe in appearance as well as performance—at its modest price it sets a standard of value hitherto impossible in the world of radio.

With
**NEON TUNING INDICATOR
FULL DELAYED A.V.C.**

and
**PENTAGRID FREQUENCY
CHANGER • ENERGISED MOVING
COIL LOUD SPEAKER • MANUAL
CONTROLS FOR TONE AND
VOLUME • FIVE VALVES
(INC. RECT.) • HANDSOME
CABINET WORK**

**MODEL
535**

SPECIFICATION:

Coszor All-Electric Super-het Model 535 as illustrated, complete with five Coszor Valves, viz., Pentagrid Frequency Changer, H.F. Screened Pentode, Intermediate Frequency Amplifier, Double Diode Second Detector, High-Slope Power Pentode Output and Heavy Duty Full-Wave Rectifier, Delayed A.V.C. Illuminated Full-Vision Scale with travel pointer, calibrated in wave-lengths, Four-Way combined On-Off, Wavechange and Gramophone Pick-Up Switch, Single Knob Tuning with Neon Indicator, Volume Control with special scale, and Tone Control. Mains Energised Moving Coil Loud-speaker of the latest type, Magnificently finished cabinet of modern design, 20" high, 16" wide, and 10 1/2" deep. Complete with plug and sockets for gramophone pick-up, and for extension loudspeaker. For A.C. Mains only 200/250 volts (adjustable) 40/100 cycles.

Hit Purchase Terms. 40/- deposit and 12 monthly payments of 20/-.

Prices do not apply in I.F.S.

12 GNS



KINGS OF THE AIR

To A. C. COSSOR LTD., Melody Dept., Highbury Grove, London, N.5
Please send me, free of charge, a copy of Folder L120, which gives full details of the new Coszor Superheterodyne Receiver Model 535.

Name.....
Address.....

PRAO 13/10/34

PACKED WITH INFORMATION

the latest Ferranti literature for home constructors

Full of interest and value, these latest Ferranti lists will prove to be of service to all constructors who desire to have the most up-to-date and efficient receivers

- Wa 560. New complete Valve catalogue
- Wf 522. New list Mains Components
- Wa 561. New list Potentiometers
- Wg 550. New Speaker List
- R 2 New complete catalogue of Components
- Wi 526. New Catalogue, Radio Meters

Any of these publications will be sent on receipt of 1½d. stamp, or all of them on receipt of 3d. postage.



FERRANTI
HOLLINWOOD
LANCASHIRE
SEASON
1934 □ 1935

Dept. W.P.
FERRANTI LTD.,
HOLLINWOOD, LANCASHIRE



There was a young lady named Del
O w n e d a marvellous radio-set,
But reception was bad—
It made her quite sad—
NOW it's soldered with FLUXITE
—you bet!

See that FLUXITE is always by you—in the house—garage—workshop—anywhere where simple speedy soldering is needed. OF ALL IRONMONGERS—IN TINS 4d., 8d., 1/4d., and 2/8d. Ask to see the FLUXITE POCKET SOLDERING SET complete with full instructions—7/6. Ask also for Leaflet on Case Hardening and Hardening Tools with Fluxite.

THE FLUXITE GUN

is a handy and economical tool that enables you to put the Fluxite exactly where you want it on the soldering job. Also used to project grease into bearings, etc.—like a miniature grease gun. Just fill the nozzle portion—half fill the cap—put together and press as required. PRICE 1/6d.



ALL MECHANICS WILL HAVE

FLUXITE

IT SIMPLIFIES ALL SOLDERING

FLUXITE LTD. (Dept. W.D.), DRAGON WORKS, BERMONDSEY STREET, S.E.1.

Soldered contacts are better
ELECTRICALLY SOLDERED ARE BEST



Switch on a Solon Electric Soldering Iron and in three minutes it is ready for use. It plugs into a lampholder. Use a

SOLO
TRADE MARK
ELECTRIC
SOLDERING IRON

7/6
65 watts 7/6
125 " 22/6
240 (1lb. 1oz) 37/8
(2lbs.)

If unable to obtain, send us the name of your nearest dealer.

W. T. HENLEY'S TELEGRAPH WORKS COMPANY LTD.
Y.O.15, Dept. — HOLBORN VIADUCT — LONDON — E.C.1

MADE IN ENGLAND

HOW MUCH HIGH TENSION?

Some Interesting Sidelights on the Use of a Generous H.T. Supply

IN spite of all that has been written concerning the desirability of providing a receiver with an ample supply of high-tension energy, cases are constantly arising in which poor reproduction results from either misdirected high-tension economy or from sheer lack of knowledge on this important subject.

The value of a liberal allowance of high-tension voltage can be grasped very easily by a study of the various stages in a multi-valve-operated receiver. Consider first of all the high-frequency amplifying stages. Like all amplifying valves, radio-frequency types, whether of the screen-grid or the high-frequency pentode variety, depend for distortionless reproduction on being worked over the straight portion of their grid-volt anode-current characteristic. If, in an endeavour to economize in high-tension current, the anode voltage is reduced considerably, the effective grid bias is correspondingly shortened, and the valve will therefore fail to handle strong signals without distortion.

Affecting Over-all Performance

This point is illustrated in the diagram reproduced in Fig. 1. Here is shown a "family" of static characteristic curves for a typical screen-grid valve of the fixed- μ type, and the way in which the maximum permissible signal is limited by the value of the anode voltage can be readily appreciated. First of all, over-all performance is affected in several ways. For example, it is clear that at a reduced anode voltage there is a considerable risk of overloading the valve on strong signals, and the only alternative is to reduce the input, which in its turn will reduce the amount of power available at the output stage to operate the loud-speaker. In this connection, it must not be forgotten that

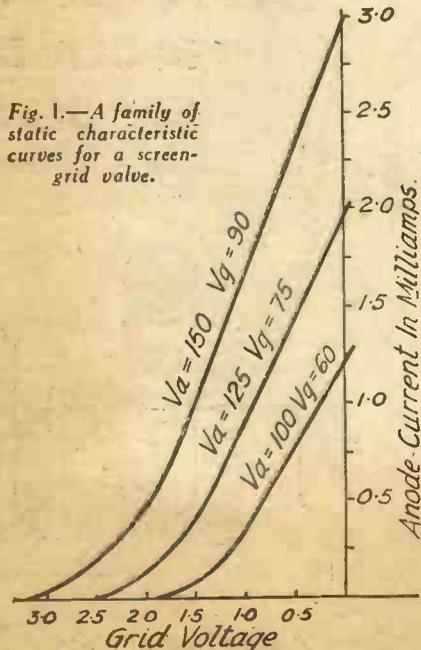


Fig. 1.—A family of static characteristic curves for a screen-grid valve.

many modern speakers lack considerably in quality when operated at low power. Then, the characteristic curves themselves show that the mutual-conductance of the valve, as represented by the slope of the curve, is considerably greater at high anode voltages than at low.

In the case of the detector stage, the value of liberality in the matter of high-tension voltage is equally marked. In the old days, when the leaky grid triode detector valve with magnetic or capacity reaction was used almost universally, the guiding precept in designing the detector stage was to use the minimum high-tension voltage which gave adequate output combined with effective and smooth reaction. These

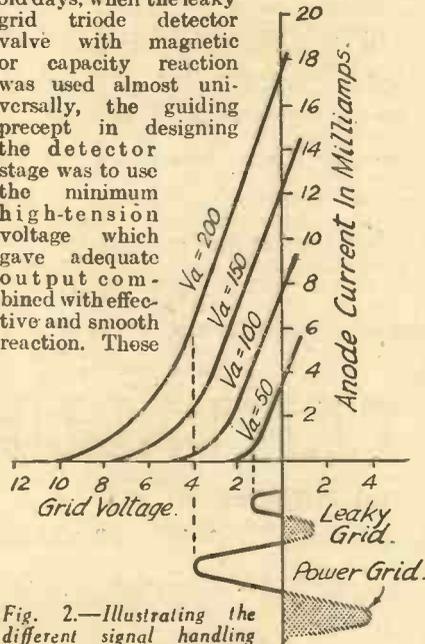


Fig. 2.—Illustrating the different signal handling capabilities of leaky-grid and power-grid detection.

were the days when two or more stages of low-frequency amplification followed the detector, and when, moreover, the efficiency of high-frequency amplification was far below what it is to-day, with the result that only comparatively small grid inputs were applied to the detector valve.

To-day, however, thanks to the screen-grid valve, and to the more recent high-frequency pentode, large stage gains are possible on the high-frequency side, and very seldom is it necessary to interpose a low-frequency amplifying stage between the detector and the output valve. This means that the detector must be able to handle comparatively large input signals and must, in addition, add its full quota of amplification in order to load the output valve.

Best Detector Conditions

With a triode-detector valve this can be achieved only by operating the valve under what is known as "power-grid" conditions. In this arrangement, the anode voltage is increased, if possible, to the maximum value for which the detector valve is rated, and as a result the anode current is correspondingly increased.

Operated under these conditions the valve will rectify quite powerful signals without distortion, and its amplifying powers are

also exploited to the full. But since power-grid detection necessitates a somewhat heavier anode current, its benefit cannot be enjoyed unless the listener is prepared to accept this additional drain upon his high-tension supply.

Fig. 2 illustrates the effect of power-grid detection when compared with the ordinary leaky-grid system, the difference in signal-handling capabilities and in anode-current consumption being illustrated very clearly.

It is, however, in connection with the output stage that the ill effects of parsimony in high-tension supply are perhaps most noticeable. It should be borne in mind that in the output stage is generated the actual power required for driving the loud-speaker. In all other stages the only effect required is to produce in the anode circuit of the valve as large an alternating voltage as possible; the power question does not enter into the matter, and the consumption of anode current is merely incidental and perhaps unfortunate. But the output valve must provide a considerable amount of alternating power, as represented by the product of the alternating voltage developed across the "load" in the anode circuit (speaker or output transformer) and the alternating portion of the anode current.

Insensitive Large Speakers

Many speakers which are noted for the fidelity of their reproduction are comparatively insensitive, that is to say, they require a larger power input to produce a certain volume of sound than some of the more sensitive but somewhat less faithful reproducers.

Most listeners know that with the normal or class "A" output valve the A.C. component of the anode current consists of variations of current strength above or

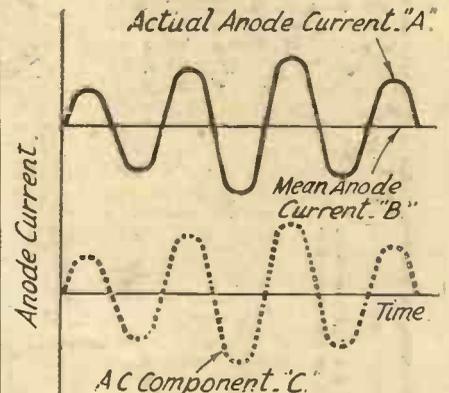


Fig. 3.—The steady or mean output current with the alternating component superimposed.

below a steady or "mean" value, which latter represents the normal anode current as measured by an ordinary milliammeter. This is shown in the familiar diagram reproduced in Fig. 3, where the top horizontal line represents the "rest" value of the anode current, while the curved line represents the actual anode current when signals are being received, and the dotted

(Continued on next page)

(Continued from previous page)

curved line shows the equivalent A.C. component. It is not difficult to understand that the actual anode current marked "A" is equivalent to a combination of the steady value "B" and the A.C. component "C." It is also clear that the amplitude of the alternating component will be limited by the value of the steady current, since the full "modulation" value is given by this mean current.

If, therefore, a really large output is required from a class "A" valve it must be of a type having a fairly large anode current in order to accommodate large variations. It is for this reason that the general quality of reproduction in mains receivers is usually so very much better than in battery sets. With mains power at a few pence per unit only, the listener can afford to be generous with his high tension. With battery operation, however, the total H.T. consumption must be limited at least to the economic maximum discharge ratio of the high-tension battery employed.

Questions of Cost

This brings to the front another aspect of the question of providing generous high tension supply. The difference in cost between expending 20 milliamps. and, say, 50 milliamps. in the high-tension circuits of a mains receiver is a mere detail—a matter of a few pence per week only.

In considering the case of the listener who has no alternative but the dry H.T. battery, it can at once be said that he will be wise to allow as heavy a consumption as he feels to be justifiable, bearing in mind the two facts that liberal H.T. makes possible improved performance all round, but at the same time adds to the cost of listening.

Most high-tension batteries, even the "standard" types of quite low capacity, will give quite a big current for a limited time, but only the battery designed for heavy discharge currents will stand up to such service for a reasonable time.

Battery Types

The "standard" type of battery should not be called upon to give more than 6 or 8 milliamps., and under this duty their life is quite satisfactory. "Power" types or so-called double-capacity batteries are usually rated for drains of the order of 12 to 15 milliamps., while the heavy-duty, triple-capacity type may be used where currents up to some 20 milliamps. are required. Each type of battery will give a reasonable life provided its recommended duty is not exceeded. The costs of the various types are in proportion to their capacities, but even so it definitely pays to use a battery at least one size larger than that indicated by the total anode current required by the set. The reason is that the useful life of a battery is not strictly inversely proportional to the drain, so that

with a loading of, say, 10 milliamps., a double-capacity battery will give more than twice the life of a single capacity battery.

All dry batteries suffer a considerable drop in voltage towards the end of their useful life, with consequent deterioration of both volume and quality of reproduction. With a large battery this deterioration is postponed, and this is another reason why it pays to be generous with your H.T. supply whenever such a course is economically possible.

Wireless at British Airports

THE Air Ministry now controls in Great Britain a comprehensive system of ground-and-air, inter-aerodrome, and meteorological communications for civil aircraft, with transmitting and receiving stations at Croydon, Heston, Lympne, Pulham, and Manchester, as well as the three new stations mentioned recently. The latter are designed particularly to cater for the growth of internal air routes.

"Wonder Bar"

THIS musical play by André Charlot, which proved very successful on the stage both in Berlin and London, and also as a cinema screen show, has been adapted for broadcasting by C. Denis Freeman, and will be heard in the National programme on October 15th and in the London Regional programme on October 17th.

MAKING A TANTALUM CHARGER

Details of a Reader's Successful Effort to Overcome Some of the Difficulties Encountered in Building a Charger

SEVERAL readers appear to have encountered difficulties in constructing the tantalum charger described in PRACTICAL WIRELESS for January 21st, 1933, and to such readers the following description of my own method may be of assistance.

A worn-out accumulator was obtained for a few pence, and the plates were removed by chipping away the pitch. The container was cleaned out thoroughly, and the lead plate was melted down in a ladle. A mould was then made from clay to the shape shown in Fig. 1. The end of the tantalum strip was bent to a V-shape, and temporarily fixed with wax in a

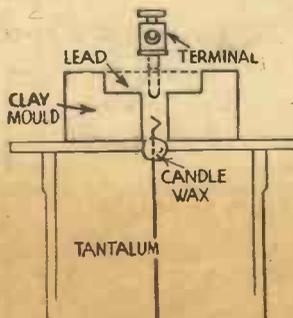


Fig. 1.—How the mould is built up from clay.

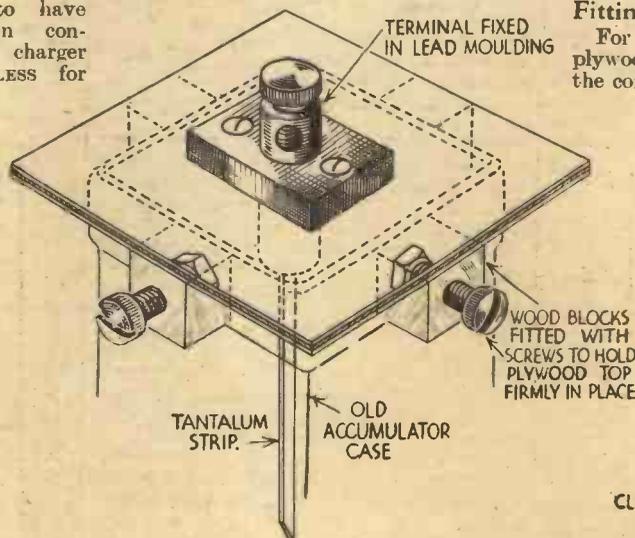


Fig. 3.—Full details of the terminal assembly.

hole in a piece of plywood supported on the top of the container. The mould was placed on the piece of plywood so that the strip projected into the circular hole in the mould. A terminal was held in the centre of the hole with pliers and molten lead from the ladle poured in, as in Fig. 2. When the lead had set the clay was broken away, and a hole was bored in each of the lead flanges for fixing.

Fitting the Top

For the top of the rectifier a piece of plywood was sawn so that it overlapped the container by an inch all round. Small wooden blocks were screwed in the centre of each side, and bolts and nuts fitted into two of them to fix the top firmly, as shown in Fig. 3.

A slit was sawn in the top for the lead plate and a hole drilled for the tantalum plate. The lead plate was fixed as shown in the previously mentioned article, except that the terminal was passed right through the top, thus firmly fixing the plate. The tantalum was fixed by two screws in the holes provided.

E. C. SWINSON.

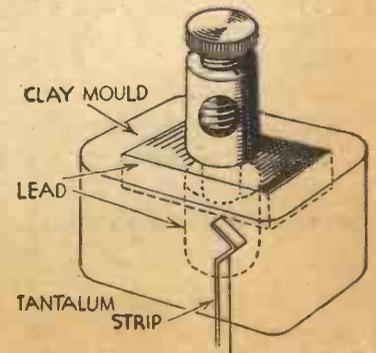


Fig. 2.—Further details of the method of fitting the terminal.



Emphatically
the set to build
The
"RAIDER"
THE
SENSATION
OF 1935 RADIO

The Circuit and Set hitherto known as "SKY RAIDER" will in future be known as the RAIDER in order to avoid possible confusion with Sets of certain other Radio Manufacturers.

Build the RAIDER and get a better Set than factory built —at less cost.

Fully described in issue No. 1 of RADIO CONTACT with which is presented

FREE full-sized BLUE PRINT and working instructions.

RADIO CONTACT is the Radio Magazine with a fresh outlook, a shilling Magazine for 3d.

Full of interesting matter for Radio enthusiasts, including :-

Description of wonderful new BATTERY VALVES. Hosts of Ideas for old sets and new. Detailed instructions for building three brilliant circuits, including the RAIDER. CONTACT World-wide Station Finder, etc.

Only a few Copies remain unsold.

Secure yours NOW from your local dealer or bookseller, or 4½d., post free, from Graham Farish Ltd., Masons Hill, Bromley, Kent.

Advt. of GRAHAM FARISH LTD., BROMLEY, KENT.

NEW iron cored coils
NEW 2 in 1 Valves
NEW type Speaker
STEEL CHASSIS
CONSTRUCTION



THE SCIENCE OF PARACHUTE JUMPING




NOT only will you learn about the principles of Parachuting, delayed drop, methods of control, and the construction of Parachutes from the October issue of this remarkable monthly magazine, but you may also read interesting facts about "Cold Light," "How Bridges are Built," the "Uses of Light Filters in Photography," "Water Divining," "How Illustrations are Made," "The Principles of Wireless Valves," "The Latest in Wireless," "Speeding up the Earth," "Wiring the House for Electric Lighting," "The Manufacture of Artificial Silk," whilst practical articles deal with "Lathe Work," "Marking Out for Machining," "New Tools, Gadgets and Accessories," "How to Build a Fuselage Model Biplane." Obtain a copy of this New Magazine Without a Rival to-day!

*On sale at all News-
agents and Book-
stalls, or by post 7½d.
from George Newnes,
Ltd., 8-11, South-
ampton St., Strand,
London, W.C.2.*

PRACTICAL MECHANICS

6^D
OCTOBER

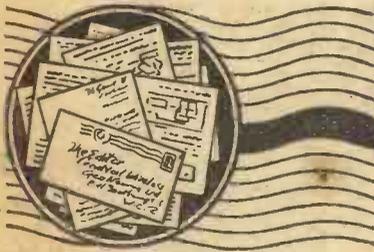


READERS' WRINKLES

THE HALF-GUINEA PAGE

Fixing an Aerial Pulley

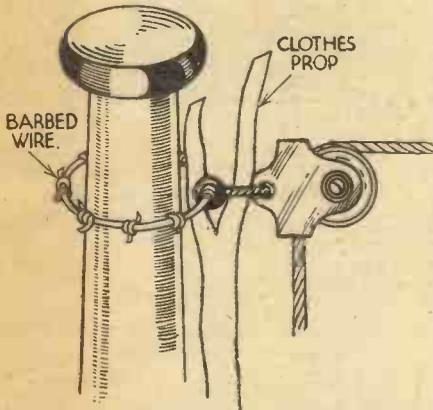IT often happens, especially during the winter months, that the aerial halyard breaks and it appears necessary to lower the mast for repairs to be made. A simpler and much less troublesome method is as follows:—




Fixing an aerial pulley to a mast after the halyard has broken

Obtain a length of barbed wire just long enough to form a loose loop round the bottom of the mast, and to the loop attach a pulley. Thread the halyard through the pulley and then with the aid of two or three clothes-props fastened together, push the loop into position at the top of the mast, as shown in the sketch. Now pull the aerial taut by means of the halyard and withdraw the clothes-props. The "barbs" of the wire loop will bite into the mast and a secure repair is the result.—F. E. MORRIS (Kilburn).

Tapping Resistors

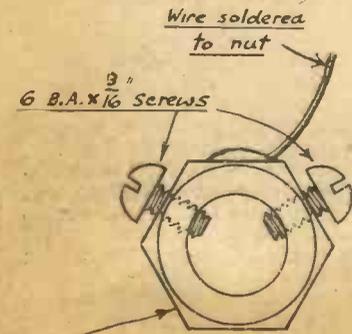IT is sometimes required to tap a carbon resistor to form a potentiometer, or when an exact value is required, as, for instance, a dropping resistance for a multi-range voltmeter. The following method will enable this to be done, for either a temporary or permanent adjustment. Drill



Brass nut drilled out to $\frac{5}{16}$ " dia

Tapping resistors by means of a nut and screws.

THAT DODGE OF YOURS!


Every Reader of "PRACTICAL WIRELESS" must have originated some little dodge which would interest other readers. Why not pass it on to us? We pay £1-1-0 for the best wrinkle submitted, and for every other item published on this page will pay half-a-guinea. Turn that idea of yours to account by sending it in to us addressed to the Editor, "PRACTICAL WIRELESS," George Newnes, Ltd., 8-11, Southampton Street, Strand, W.C.2. Put your name and address on every item. Please note that every notion sent in must be original. Mark envelopes "Radio Wrinkles." Do NOT enclose Queries with your Wrinkle.

out a $\frac{1}{2}$ in. brass nut to 5-16in. diameter, then drill and tap two faces for No. 6 B.A. screws, as shown on the sketch. The nut is threaded over the resistor, and connection made by soldering a wire to one of the other faces. The paint on the resistor should be removed where the screws make contact, and the ends of the screws should be flat, not pointed. It is also essential to see the resistor is not of the type having a porcelain or other insulated surface.—L. W. HARVEY (Brondesbury Park).

Novel Dial-lighting Arrangement

HERE is a novel dial-lighting arrangement—the cost of which is very small.

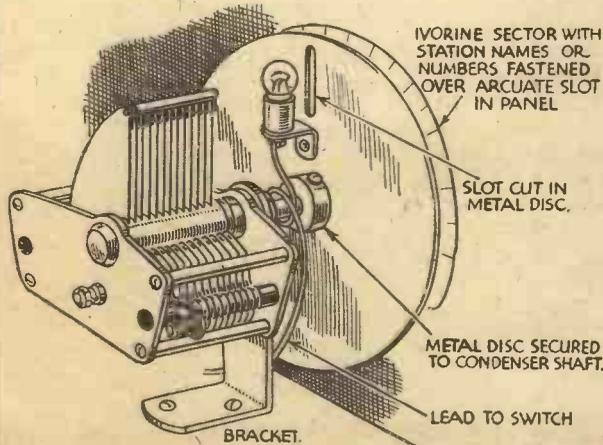It consists of a metal disc, an ivoryine full-vision scale, a small lampholder, and



An effective dial-lighting arrangement.

a L.C. screw-type bulb. A hole is drilled in the centre of the disc to suit the condenser, this hole being made to fit the spindle tightly, or a small collar can be soldered to the disc and a grub-screw fitted to grip the condenser spindle.


A slot is cut in the disc to suit the scale, large enough to show the name of the station on the scale. If numbers are used, the slot can be smaller. The lamp is fixed to the back of the disc just behind the slot, and is wired with one wire only

from the L.T. switch, the return being made via the condenser spindle. This wire is fixed to the spindle with a rubber band or tape and to the baseboard, leaving a little slack for condenser movement.

In some cases the condenser may have to be set back from the panel, but this only requires a small extension to the spindle, the condenser being fixed to a bracket on the baseboard.—THOMAS JOHNSON (Newcastle-on-Tyne).

Repairing Transformers, Speakers, etc.

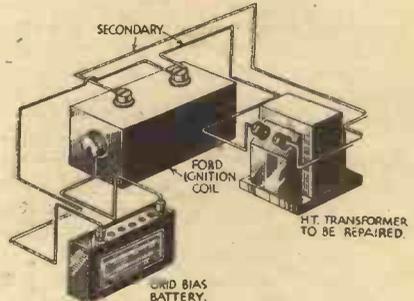SHOULD you have the misfortune to have a transformer with one of the



Method of repairing a transformer.

windings broken down, don't take it to pieces, leave it just as it is, then carry out the following scheme: Obtain a good Ford

coil, and a grid bias battery (a good 9-volt one), alternatively, if you are on A.C. current, get a bell transformer with secondary of 8 volts, and use that; then connect as shown in the accompanying sketch.


Take care to connect the secondary first, otherwise a violent shock will be felt. When the secondary is connected, join the primary to the grid battery or bell transformer, and see that the trembler at the top of the coil is working correctly. Leave on for one minute, then disconnect and test the transformer. If not repaired, connect again, and again if necessary, and you will find, if the necessary care is taken to

see that trembler is working properly, that the transformer winding is usually welded at the break at the first or second attempt. The spark gap can be regulated by the nut at end of trembler.


Do exactly the same when repairing speakers, remembering that the main thing is not to take them to pieces. This method consists actually of spot-welding, the arc which takes place at the broken point producing sufficient heat to weld the fine wire.—J. R. BURNS (Cork).

FERRANTI CAR RADIO

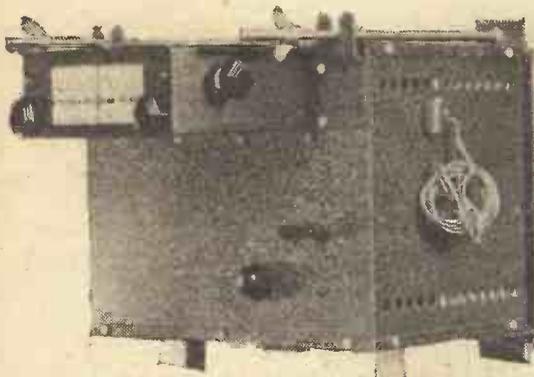Details of an Interesting Receiver
Designed for Use with a Motor-
car Lighting Battery.



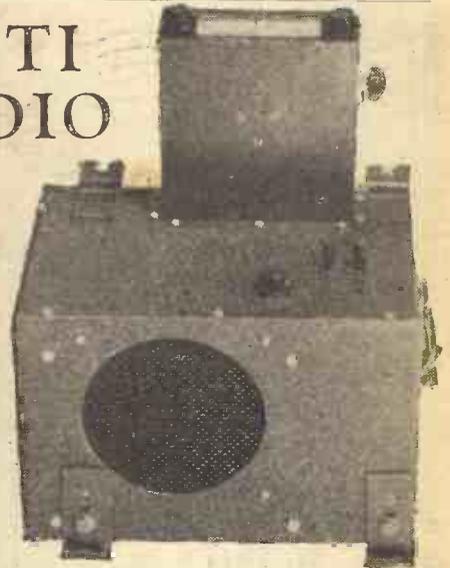This photograph shows the neat arrangement of the complete Ferranti "Motorset."



It can be seen from this photograph that the speaker grille is situated on the underside of the black steel cabinet.

THE latest apparatus designed for use entirely as a car-radio receiver is the Ferranti "Motorset," a powerful 5-valve superheterodyne which operates entirely from a normal lighting battery as found on the car of to-day. The valves are of the Universal type, and, although only five in number, they include a heptode and a double-diode-triode, so that the circuit arrangement is very similar to a normal 8-valve superhet., the heptode combining the functions of first detector and oscillator, and the double-diode-triode combining the functions of second detector, A.V.C., and first L.F. valve. The necessary high-

tension supply is obtained by means of a special double-vibrator mechanical rectifier which performs the double function of converting the current from the lighting battery into A.C. and then stepping it up to the required voltage, after which it is again rectified for the H.T. supply. In view of the utility of the new Droitwich transmitter, special attention has been paid to the long-wave performance of this Ferranti receiver.

The entire apparatus is contained in a neat steel cabinet finished in black enamel and designed for fitting below the dashboard. If desired, the entire apparatus may be removed in less than half a minute, yet the mounting is perfectly secure and shock-proof. All the valuable features found in a modern home receiver are included in this particular model, and these include an illuminated dial giving station names as well as wavelength calibrations; single knob tuning; combined

manual volume control and on-off switch; tone control; moving-coil loud-speaker delivering an output of $2\frac{1}{2}$ watts when fully loaded. The dimensions of the case are $9\frac{1}{2}$ in. high by $12\frac{1}{2}$ in. wide by 15 in. deep, and the price is 18 guineas complete.

A NEW battery receiver is announced in the H.M.V. superhet, which follows modern design in every way, employing four valves with delayed A.V.C., double pentode output, new reflecto-light dial and novel "on-off" indicator housed in a handsome walnut cabinet. The new high-power station at Droitwich has been kept well in mind when designing this model.

A New Scale Light

In order to save current, the scale is not illuminated, but is made of special material, which makes the station names and wave-length calibrations stand out clearly from the background, and gives the illusion that the scale is illuminated from behind. As the main switch is turned to "medium wave," "long wave," or "gramophone" a small transparent scale bearing the word "on" comes into view at the top and in front of the main station scale.

All the main controls are mounted on the front of the cabinet. On the left is the volume control, and on the right the master switch. This switch has four positions, MW, LW, Gram. and Off. The actual tuning control is below the scale, and beneath the tuning control is the sensitivity switch, which has a novel "push-pull" action. A pre-set reaction control, to enable the maximum sensitivity to be obtained, is mounted at the back of the cabinet.

Latest Valves

The first valve, a heptode, acts as a mixer, and is fed from a super-selective tuned circuit. The output from this valve is fed into a Litz wound I.F. transformer. The intermediate frequency is 456 kc/s; the


THE NEW H.M.V. BATTERY SUPERHET

use of this frequency practically eliminates direct second-channel interference. The secondary winding of the transformer is connected to the I.F. amplifier valve—a VS24. The primary of second I.F. transformer is joined to the anode of this

valve. Both the primary and secondary of this transformer are tapped. The primary tap is connected to the AVC diode of a double-diode-triode valve (HD21). Both the previous valves are controlled by delayed AVC. The split secondary of the transformer feeds the diode rectifier of the same valve, the rectified output being fed into the triode portion, which serves as an L.F. amplifier. The coupling between the L.F. portion of the third valve and the output valve is by means of a parallel-fed transformer, the secondary feeding the grids of the double pentode QP21. Reaction is supplied by means of I.F. feed-back from the second I.F. secondary to the anode of the first valve.

This form of regeneration in a superheterodyne receiver is not, of course, new, but it has not previously been found to be productive of good stable results over long periods. The first valve is acting at one frequency, whilst the I.F. valve is operating on a different frequency, and the coupling of the anodes of these two valves might result in all sorts of weird effects, unless certain precautions are taken. The Marconiphone engineers have carried out a great deal of experiment in this connection, and the method which has finally been adopted in this circuit may be said to be productive of good reaction effects without ill-effects.

Provision is made for the attachment of a gramophone pick-up, and the volume control acts on both radio and gramophone. This method of volume-control is to be recommended as it removes the necessity of a further control which is only brought into use at infrequent periods. It is, of course, possible to gang two controls to carry out the combined operation, but a single control acting on the L.F. side enables volume to be controlled on both radio and gramophone. The price is 11 gns.

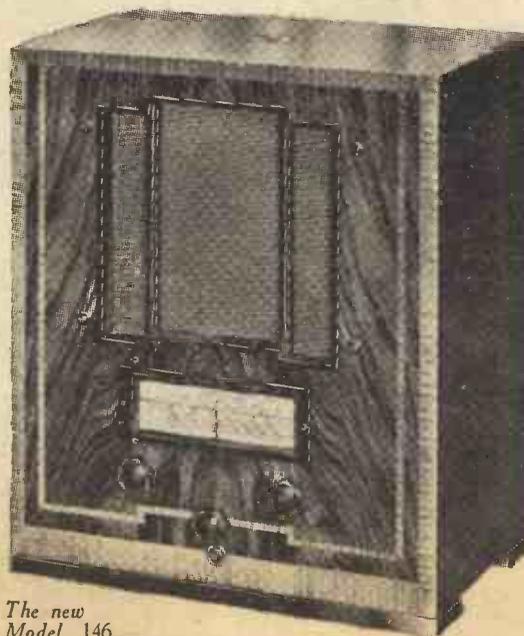

The new
Model 146
H.M.V. receiver,
which has a new type of lampless illuminated dial.

COSMOCORD BALANCED TONE PICK-UP

Exceptional high volume and delightful balanced tone entirely free from resonance are the qualities that make this pick-up so popular. All bakelite construction with swivel head for easy needle change. Complete with volume control and 5-ft. silk-covered lead. Sold under the guarantee that should it not meet with entire approval, money will be refunded.



MODEL No. 15
PRICE - 15/-

Send for new comprehensive and instructive booklet showing all products to COSMOCORD LTD. (Dept. P), Cambridge Arterial Rd., Enfield, Middx. Phone: Enfield 4022/3.

Every set a SHORT WAVE set with the


BRITISH GENERAL

ALL WAVE TUNER

This famous coil, covering all wave lengths from 14.5 to 2,000 metres, still remains the most successful of all all-wave tuners.

Its remarkable popularity is due to the superb workmanship, reasonable price and, above all, its unequalled efficiency.

Easy fixing and simple tuning.

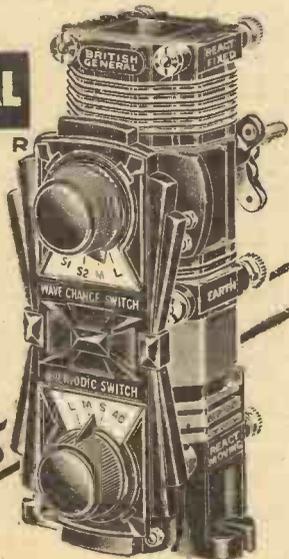

FREE WIRING DIAGRAM SUPPLIED

9/6

British General Manufacturing Co., Ltd.,
Brockley Works, London, S.E.4.
Telephone: Lee Green 5055.


From all dealers or direct.

The Pick-Up of the Future

ROTHERMEL-BRUSH

PIEZO-ELECTRIC PICK-UP

Acclaimed by the leading authorities as the greatest advance in design and performance that has ever been made, the Rothermel-Brush Piezo-Electric Pick-Up gives a response of from 42 to 8,500 cycles with an output of 2 volts R.M.S. No other pick-up available can equal this performance. There is only 1/2oz. weight on the record, thus ensuring an entire absence of wear and tear. This new and revolutionary non-magnetic and non-resonant pick-up represents the finest value available and because of its outstanding performance has been adopted as standard equipment by R.G.D. and other prominent manufacturers of high fidelity radio-gramophones.

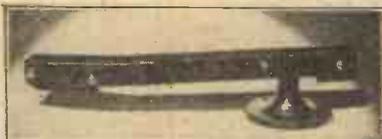

PRICE 42/-
COMPLETE.

Obtainable from all high-class dealers. If in difficulty communicate with R. A. Rothermel, Ltd.

Write for complete lists featuring Rothermel-Brush Piezo-Electric pick-ups; speakers and microphones, etc., etc., Post Free.

R. A. ROTHERMEL, LTD. (Dept. N), Rothermel House, Canterbury Road, High Road, Kilburn, N.W.6. Phone: Maikla Vale 6006.

R.A. Rothermel

Tradition



The Technical Press agrees with us in our statement that the Amplion 1935 "Lion" Speakers faithfully uphold our reputation for producing speakers that give life-like reproduction, fine tonal balance, sensitivity and the ability to handle heavy input without the slightest distortion.

"Popular Wireless" says:—

"To-day, Amplion moving coil loudspeakers are continuing to enjoy tremendous popularity, proof—if proof is wanted—that the old-time traditions associated with this famous name have been well maintained."... The Amplion "Lion" speaker, a high-class permanent magnet moving coil instrument, is an outstanding example."

Because "Lion" permanent magnet moving coil loudspeakers can be correctly matched to every class of output, they are suitable for use with any receiver."

UNIVERSAL TRANSFORMER, 1 to 20 AND 2,000 to 40,000 OHMS.

PROVISION FOR VOLUME OR TONE CONTROL AND USE OF ADDITIONAL SPEAKER.

"Lion" 7" cone, 47/6. "Lion Super" 10" cone, 55/-.

AMPLION SPEAKER, RECEIVER, AND COMPONENT LISTS, FREE.

47/6

(7" CONE)

AMPLION

LION LOUDSPEAKERS

AMPLION (1935) LTD.

82-84, Rosoman Street, London, E.C.1.

NOISE SUPPRESSION

NOISE suppression figures as an important feature of a number of modern receivers, but the meaning of the term does not appear to be generally understood. In many instances it is thought to be the same as interference suppression, whilst in other cases it is merely taken to imply that some kind of L.F. volume control is provided. In point of fact, however, noise suppression is something quite different from these, and becomes necessary only when automatic volume control is fitted. It is well known that the chief disadvantage of A.V.C. is that it renders the receiver most sensitive when it is not tuned to the wavelength of any particular transmission, the sensitivity decreasing proportional to the signal intensity when a station is tuned in. The result of this is that an efficient receiver provided with A.V.C. is very "noisy" when off tune, so that the various forms of inter-station "mush" and so-called background noises come into undesirable prominence. Because of this one hears a succession of "hisses" and the like when rotating the tuning dial whilst tuning in.

The Simplest Arrangement

When only the more powerful transmissions are required, it is possible to eliminate the inter-station noises by turning down the manual H.F. volume control, but this method does not apply when more distant stations are wanted, because the set is rendered comparatively insensitive. If the tuning condenser is fitted with a station-calibrated dial, or if the wavelength positions of a number of stations on the dial are known, the inter-station noise difficulty can perhaps best be overcome by fitting some form of visual-tuning indicator and an L.F. volume control, or even a switch to short the grid circuit of one of the L.F. valves. The complete arrangement of this system is shown in Fig. 1, which is a portion of the circuit of a mains superhet in which A.V.C. is applied to the intermediate-frequency amplifying valves. It will be

Quiet A.V.C. or Noise Suppression is Coming Into Increasing Popularity, and a Knowledge of the Underlying Principles is Desirable

seen that if the contacts of the switch connected in parallel with the secondary winding of the L.F. transformer are closed, the L.F. valve will become inoperative, and therefore the loud-speaker cannot respond to any signals tuned in. When using this arrangement, therefore, the "suppressor" switch should be set to the "on" (contacts closed) position, after which tuning can be carried out, using the visual indicator only. As soon as this shows that the station has been correctly tuned, the switch contacts are opened.

Automatic Suppression

This is not really a legitimate system of noise

suppression, but it can be employed, and it serves as an indication of the principles involved. A proper system of noise suppression must be entirely automatic so that as soon as the receiver is de-tuned the L.F. amplifier becomes inoperative. This is often referred to as Quiet Automatic-Volume Control, due to the fact that the speaker is silent during the intervals between the wavelength positions of various stations when the tuning condenser is being operated. The principle of Q.A.V.C. is not new, and there are various methods of applying it,

but it has not generally been used by the amateur. There are several reasons for this, one of which is that an H.T. voltage of high value is required (so that the system is practically limited to mains receivers), and another is that it involves the use of either an additional valve or of a multiple valve, such as a double-diode triode, double-diode pentode, triple diode, etc. The general circuit for the second detector of a superheterodyne, which comprises a double-diode triode used for A.V.C. and noise suppression (or Q.A.V.C.), is given in Fig. 2. At first glance this circuit appears to be very complicated, but if the various parts are considered separately it will be seen that the arrangement is not difficult to understand.

A Matter of Bias

First of all it will be appreciated that the two resistances R1 and R2, which are connected in series between the centre tapping on the secondary of the I.F. transformer,

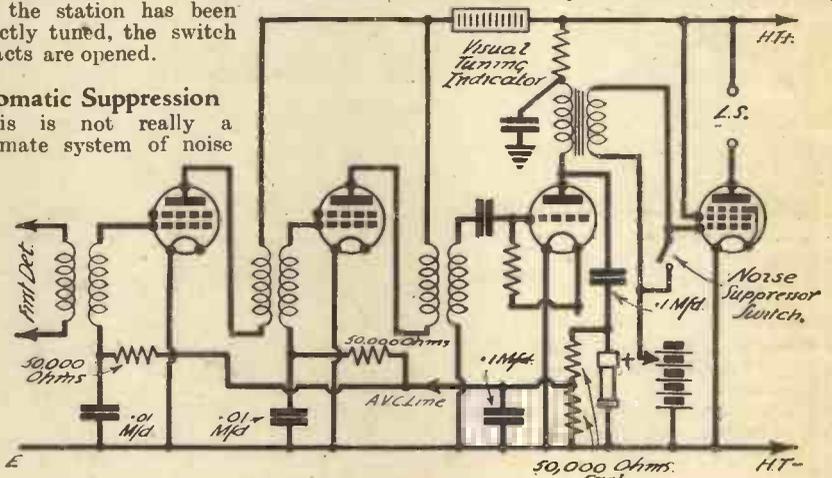


Fig. 1.—Skeleton circuit showing how a switch can be provided for noise suppression with a receiver fitted with a visual-tuning indicator. In this case A.V.C. is provided by means of a Westector. Component values are average ones.

provide the A.V.C. bias for the preceding intermediate frequency amplifier. The end of R1, which is connected to the I.F. transformer, becomes increasingly more negative as the signal strength increases, so that the bias voltage applied to the previous valve increases with signal strength. The grid of the triode portion of the double-diode triode is connected to a tapping on R2 and, therefore receives a varying negative voltage at the same time as does the grid of the I.F. valve. On all signals of more than some pre-determined minimum intensity this latter bias must be just sufficient to prevent the triode section from passing any appreciable amount of anode current. When this is so the resistance R3 does not introduce a voltage drop, with a result that the bias voltage applied to the third (output pentode) is that developed across R4 only, this resistance being chosen to provide the normal working bias voltage required by the pentode.

It will be seen that, as soon as the receiver is off tune the A.V.C. voltage is reduced to a minimum, and therefore the triode portion of the multi-electrode detector passes a certain amount of anode current. This current is drawn through R3, and thus a voltage-drop is set up across that resistance, the actual voltage being dependent upon the current passing. And it will be seen that R3 is in series with the bias resistance R4: consequently the bias then

(Continued on page 142)


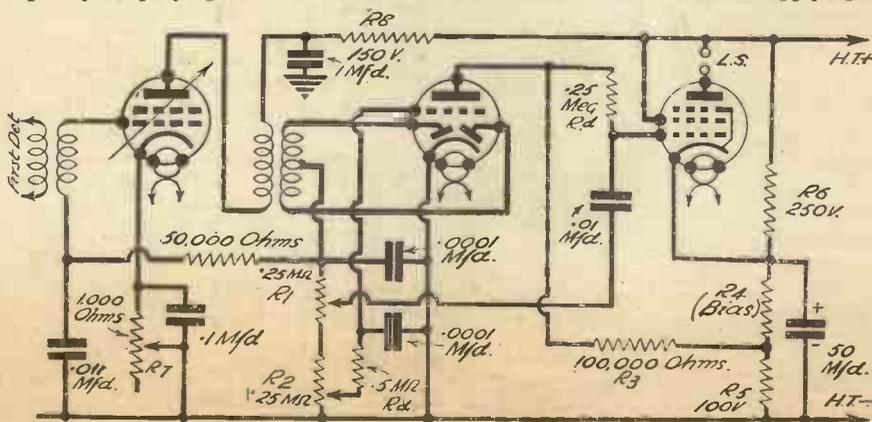


Fig. 2.—The circuit for a double-diode triode used as second detector, automatic-volume control and noise suppressor.

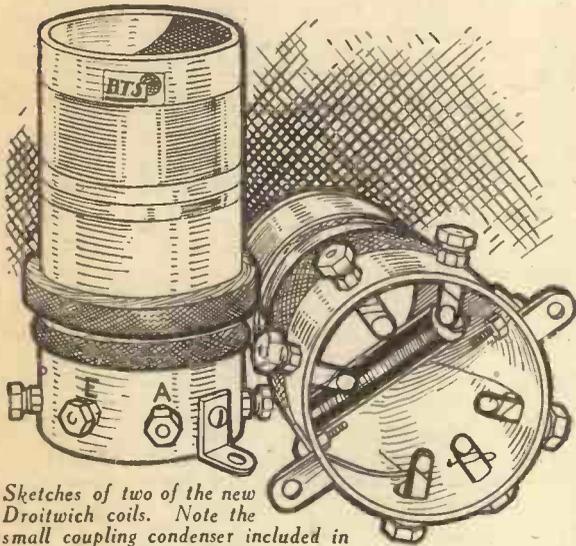

Sketches of two of the new Droitwich coils. Note the small coupling condenser included in the lower end of the coil.

Droitwich Coils

Details of a New and Cheap Type of Coil which is Being Introduced to the Home Constructor

SINCE the introduction of the iron-core coil there have been many attempts to repopularise the air-core or simple type of tuning coil, and to this end some interesting types of coil have been introduced. Obviously, in addition to low price the efficiency of the coil has also had to be of such a nature as to warrant the use of the coil in place of the iron-core type, and we have already reviewed several different types of coil in these pages.

With the advent of the Droitwich transmitter, however, some rather more care is required in the design of the coil if it is to prove of utility in all parts of the country. Hitherto, the long-wave band has been regarded as rather simple, and coils have been designed to have their maximum efficiency on the medium waves, with a long-wave performance which was satisfactory only so long as the transmissions on that band were well received. Selectivity on this portion of the tuning scale has generally been a compromise, although there are, of course, many types of coil which do give a very high standard of performance on the long waves.

In America, of course, the long waves are not employed, and the design of receivers in that country has been rendered much more simple owing to the fact that one band of frequencies only has had to be tunable, although in some cases the short-wave band has also been introduced. When, however, a receiver has to be designed to cover also the long waves there are certain difficulties in the way of giving a really high standard of efficiency of both bands.


The High-power Transmitter

In the past this has not been of great consequence owing to the power which has been employed by the long-wave stations. With the increase which is, however, being employed at Droitwich there will be serious overlapping of stations in many parts of the country. Radio-Paris, for instance, will be found to be swamped by Droitwich over a very large area in the Midlands, unless special precautions are taken. Similarly, where a powerful receiver is in use, and the coils have not been designed for selectivity on the long waves, serious difficulty may be encountered in confining the Droitwich transmitter to a narrow band on the tuning scale. British Television Supplies have tackled this question, and have developed a new tuning coil of the

air-core type, which possesses some novel features, and which, whilst employing a standard arrangement for the medium waves, has been designed on rather unorthodox lines so far as long waves are concerned. The small theoretical diagrams accompanying this article show that in addition to the

ordinary types of coil, and has been found to give greatly improved results in its long-wave performance. It has been designed for a specific purpose, and it does what is intended.

It must not be inferred from this that its performance on the medium waves is in any way lacking. The combination of condenser and coupling coil results in a very satisfactory performance both as regards signal strength and selectivity on this band, and the coil is comparable with any standard air-core coil. As a matter of fact, at the time of going to press, the manufacturers inform us that an additional refinement in the form of a centre-tap to the grid winding is to be provided so that the coil may be employed in more efficient H.F. receivers in which one or more H.F. stages are employed. This will provide yet a further aid to selectivity, and give the coil greater scope.

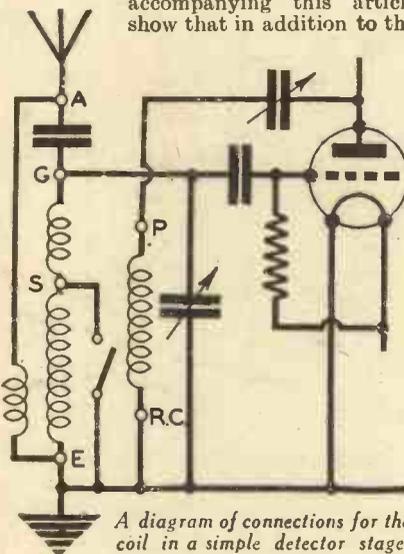

A diagram of connections for the coil in a simple detector stage.


provision of a small series condenser, a separate aerial coupling coil is employed on the long waves. No switching is required to bring this coil into use,

as it is permanently joined to the aerial terminal. The value of the series aerial condenser is .00003 mfd., which value renders it practically of no account on the long waves, but the aerial is joined also to the small primary winding. The actual arrangement of the windings, the value of the coupling condenser, and the number of turns in the primary coil have all been carefully worked out so that, on medium waves, the coil gives a performance fully up to the requirements of a modern wireless receiver, namely, good signal strength and good selectivity. On the long waves, however, the effect of the coupling coil is found to be such that the Droitwich transmitter may be confined to a narrow band without any loss of signal strength. The coil has been tested in comparison with


Coil Details

The former upon which the coil is wound is 1 1/4 in. in diameter, and the medium-wave grid coil is wound at the upper end, in solenoid fashion with enamel-covered wire. A short distance from this is the reaction winding, which is disposed to operate on both wave-bands. A short distance from this coil is the long-wave grid winding, and this is wave-wound with silk-covered wire, and a similar type of winding is arranged at the lower end of the former for the long-wave aerial-coupling coil.

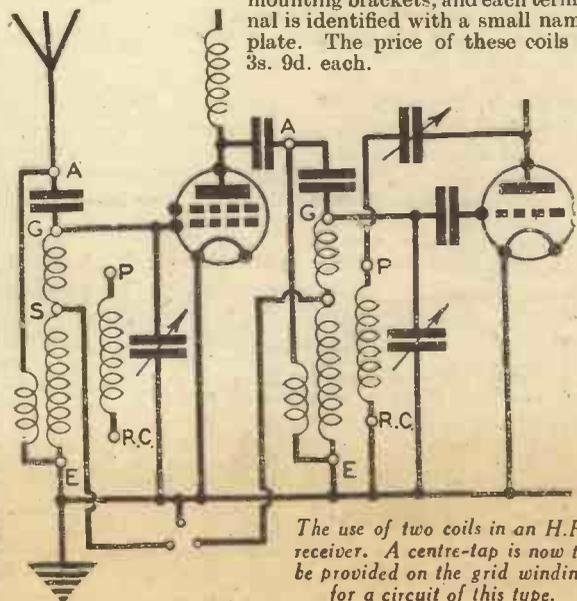Six terminals are arranged round the lower edge of the coil, together with two mounting brackets, and each terminal is identified with a small name plate. The price of these coils is 3s. 9d. each.



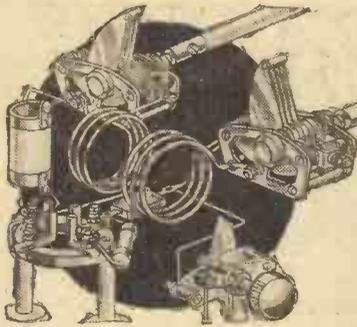The use of two coils in an H.F. receiver. A centre-tap is now to be provided on the grid winding for a circuit of this type.



Short Wave Section

ELIMINATING NOISES IN SHORT-WAVE RECEIVERS

By A. W. MANN

THE cause of hissing is often a faulty S.G.-H.F. valve. The only remedy is to fit a new valve in place of the faulty one. If used later as an S.G. detector for S.W. reception, a valve of the hissing variety is likely to be noisy in operation, and, in addition, may cause a hum to build when carrier-wave is tuned in. Of course, a dry earth or faulty earth connection will produce a similar effect.

Always check wiring against a theoretical circuit. Remember it is current practice in the interests of efficiency, short-wiring, and compactness, to enclose a number of fixed condensers in one metal container or screening box, the latter being used as a common lead to earth via the chassis. L.F. chokes, shown as separate components in diagram, are sometimes centre-tapped chokes fitted into the same screening box.

Should it be necessary to check A.C. or D.C. voltages, use meters suitable for the purpose, and not any old meter to hand. It is better to be safe than sorry.

To ignore the above advice may result in serious damage to the receiver, personal injury, and considerable expense. Be quite sure about what you are going to do, and the correct methods to adopt, otherwise it is better to place the task in the hands of an experienced person. High voltages are no respectors of persons, and will not be played about with in a haphazard manner.

Valve Rectifiers

Droning, or purring noises, heard in the speaker, superimposed on signals, may be due to a faulty rectifier valve. Place an ear to the valve envelope, and if noises are internal to rectifier, same is faulty. Fading signals will probably be experienced. Replace with new rectifier valve of same type.

Gaseous Valve Rectifiers

As the writer has had considerable experience of this type, which is a standard fitment in certain high-class American short-wave A.C. operated receivers and power packs (eliminators), information concerning them which, by the way, is difficult to obtain, is given for the benefit of Overseas

and other readers using apparatus in which the gaseous type rectifier is fitted. There are two makes in the 125 M A class, the B. H. Ratheon, and C.R.A.—125 B.H., which are interchangeable and have much to recommend them: long life, silent operation, robustness. Faults, however,

shorted. A re-wind of secondary is, of course, necessary.


Checking Power Transformer Voltages

Unless you have mains checking experience, do not attempt to check power transformer voltages, as 250, or even 275, volts each side of centre tap is quite common.

The maximum plate voltage allowable with B.H. and C.R.A. 125 rectifier, is 300 volts per plate. As these rectifiers are filamentless, continuity test on filament is impossible. The gas element replaces the filament, and to avoid a complete burn out no type of rectifier valve should be used as a replacement, other than B.H., or C.R.A. 125 types.

Detecting Interference

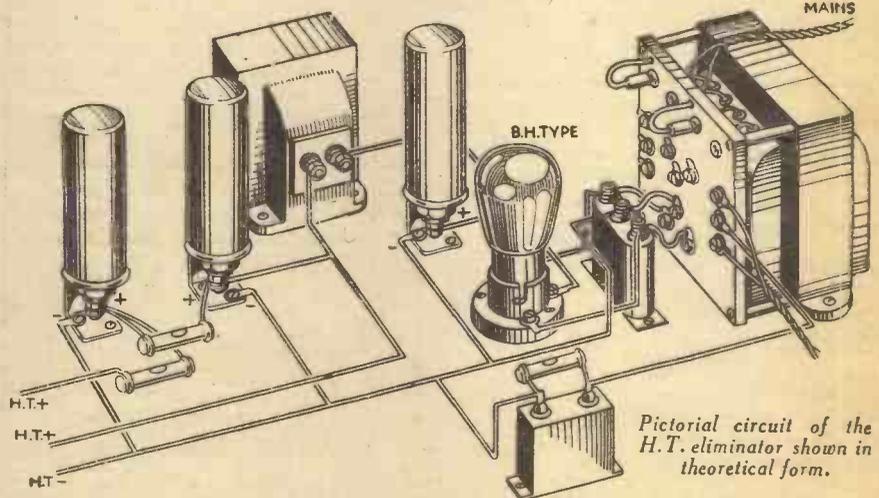If you are subject to some kind of interference, the quickest way to find out



Pictorial circuit of the H.T. eliminator shown in theoretical form.

are difficult to trace should they develop, unless one has had previous experience.

Purring Noises in Speaker

Purring noises in speaker, also internals of rectifier, together with flash-over between the twin tube elements and underside of cap, and with fading and distorted signals, until only purring noise (like a form of motor-boating is heard), denotes complete burn out. If dial-light flickers and rectifier bulb is very hot, the cause is either a burnt-out rectifier, or due to excessive voltage to plates. Check high voltage and secondary of power transformer, chokes, by-pass condensers, etc.


Should the dial-light flicker violently a few seconds after switching on, and a click be heard in power transformer, a shorted secondary winding is more than likely. This will cause excessive residual voltages to build up, and break-down the gas element of rectifier. Remove transformer, test all tappings and windings. Erratic needle movement will denote trouble when testing off load with power line connected to transformer primary.

It is possible that this effect will be noted on all windings, if secondary high voltage winding is

whether it is outside or in the set is to detach the aerial and earth and interconnect the aerial and earth terminals by means of a short piece of wire. If the interference becomes inaudible, or considerably reduced, it can generally be taken for granted the interference is not in the set, but outside. It is always advisable, where sets are operated from the mains, to interchange for test both on the aerial and earth terminals to find out whether the interference enters via the mains. If, after the aerial has been detached the noises are still heard in the same way the set should be searched for the cause. Outside interference may be caused by any kind of electrical apparatus, and many cases have been traced to electric lamps, stoves, and inefficient switches in the house. When the search for this sort of trouble commences it is always wise to switch off everything connected to the mains, except the set, and switch each in separately. Inquire of your neighbours whether they are subject to the same type of interference.

NEWNES' TELEVISION AND SHORT-WAVE HANDBOOK

Have You Reserved Your Copy Yet?

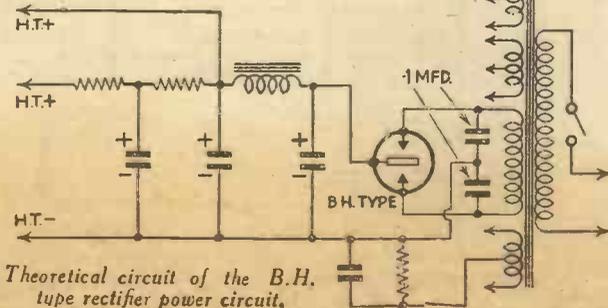

Theoretical circuit of the B.H. tube rectifier power circuit.

THE BRAIN AND RADIO
Can Wireless Signals be Heard Without the Use of a Wireless Receiver?

HAVE you met one of those peculiar people who imagine they can receive wireless messages without the aid of some kind of electrical apparatus? I met one the other day for the first time, though for years I have received letters telling of the most peculiar experiences which, on being looked into, proved to be the result of a disordered brain. However, the lady who called upon me, asking for advice, was quite a rational type of individual, and I listened patiently to her story. She was a typist in a City office, and travelled home each evening by one of the underground tubes. With all the noises which are consistent with such form of travel they did not prevent her from hearing both broadcast speech and music from the London station. She went on to say that this kind of thing did not stop with the travelling, but when she retired for the night rest was unobtainable because she was kept awake by continuous messages from relations and friends who persisted in telling of blood-curdling experiences which awaited her.

Hallucination!

I say, without doubt, that cases such as this are nothing more than a hallucination. I was, however, unable to get rid of her so easily, and in desperation I picked up a small buzzer which was lying on my table telling her to keep it in her bedroom and sound it three times before getting into bed. She went away quite satisfied and apparently relieved from a considerable amount of anxiety. What would have been the use of my explaining to her the whole theory of radio, when she was perfectly convinced in her mind that she was receiving radio messages? Like all these irrational people, she would have considered me the irrational. Radio can only be broadcast by one means, namely, electro-magnetic waves. In order to send out these waves into the ether it is necessary to use a transmitting station. These waves are of such a high frequency that it is impossible for the human ear to detect them without the aid of some detecting apparatus. When located even as close as a mile or so from the transmitting station the energy received on an elaborate aerial is so infinitesimal that it would amount to about .00001 fly-power. In order to detect such a message very delicate apparatus must be used which is capable of magnifying this weak signal enormously. A wireless receiver may be compared to a powerful microscope. To expect the brain to receive such a message without the aid of a receiving instrument is like expecting the deaf to hear sounds, or the blind to see, or you to feel something without touching it.

An Impossibility

Sound waves are of a low order of vibration, and rate from 10 to 20,000 oscillations per second, after which we can no longer hear them. Radio waves vibrate at a rate of 30,000 to millions of cycles per second, while light waves vibrate at the average rate of 600,000,000,000,000. This will show that radio waves have a vibration too high to be heard by the human ear, while they are not fast enough to be seen by the eye. Feeling any sensations for which we cannot account, sounds, mysterious sights, etc., which are not shared by others, calls for a consultation with a capable physician!

PETO-SCOTT **EVERYTHING RADIO—CASH C.O.D. or EASY TERMS**

SEND US YOUR ENQUIRIES FOR EVERYTHING RADIO . . . Miscellaneous Components, Parts, Kits, Finished Receivers or Accessories for Cash or C.O.D. or H.P. on our system of Easy Payments. Send us a list of your wants. We will quote you by return. C.O.D. orders value over 10/- sent carriage and post charges paid (GREAT BRITAIN ONLY). Any surplus refunded immediately. Hire Purchase Terms are NOT available to Irish and Overseas customers.

PILOT AUTHOR KIT
ALL PENTODE THREE

KIT "A" Author's Kit of Yours for First Specified Parts, less Valves, Cabinet and Speaker. Cash or C.O.D. Carriage Paid **£5/12/6**. Balance in 11 monthly payments of 10/3.

KIT "B" As for Kit "A" but with set of 3 specified Valves, less Cabinet and Speaker. Cash or C.O.D. Carriage Paid, **£7/13/0**. Or 12 monthly payments of 14/-.

KIT "C" As for Kit "A" but with set of 3 specified Valves and Peto-Scott specified Cabinet with Baffle-board, less Speaker. Cash or C.O.D. Carriage Paid, **£9/8/0**. Or 12 monthly payments of 17/8.

● Set of 3 Cossor Valves as specified .. **£2 0 6**
● 1 W.B. Stentorian Standard Speaker .. **1 12 6**
or 2/6 down and 11 monthly payments of 3/-.

SELECTED EASIWAY ITEMS

W.B. STENTORIAN SENIOR PERMANENT MAGNET M.C. SPEAKER. For Power, Pentode and Class B. Cash or C.O.D. Carriage Paid, **£2/20**. Send only 2/6. Balance in 11 monthly payments of 4/-.

W.B. STENTORIAN STANDARD PERMANENT-MAGNET M.C. SPEAKER. For Power, Pentode and Class B. Cash or C.O.D. Carriage Paid **£1/12/6**. Send only 2/6. Balance in 11 monthly payments of 3/-.

GRAHAM FINISH RAIDER 3. Send Complete Kit for building, including specified Valves, B.R.G. Cabinet and W.B. Stentorian Baby Speaker. Cash or C.O.D. Carriage Paid, **£7/6/8**. Balance in 11 monthly payments of 13/6.

LISSEN SKYSCRAPER THREE. Chassis model with (Lissen) S.G., Detector and Pentode Valves. Cash or C.O.D., **£3/17/6**. Carr. Paid. Balance in 11 monthly payments of 7/- only.

DROITWICH BAND CONTROL COILS
Receive Radio-Paris without interference from Droitwich with these amazing new coils. This high degree of selectivity results from the NEW WAVE WINDING, now offered the Home Constructor for the first time. Interchangeable for aerial or anode circuits.
1 pair B.T.S. Droitwich Band Control Coils 7/-. Part post and packing 6d. extra.

1935 PETO-SCOTT CLASS "B" 4. Complete Kit for building, including Valves and Peto-Scott Console Cabinet. Cash or C.O.D. Carriage Paid, **£5/13/6**. Balance in 11 monthly payments of 10/6.

BLUE SPOT "STAR" MOVING-COIL SPEAKER Complete with Universal matching Transformer. Cash or C.O.D. Carriage Paid, **£3/10/0**. Balance in 11 monthly payments of 6/6.

ATLAS C.A.25, for A.C. Mains, Class B and Q.P.P., four tappings; 60/80, 60/90, 120, 150 volt, 25 m.a. Cash or C.O.D. Carriage Paid, **£2/19/6**. Balance in 11 monthly payments of 5/6.

AMPLION

"LION" MOVING-COIL SPEAKER. With Universal Transformer, 1-20 ohms and 2,000-40,000 ohms. Cash or C.O.D. Carriage Paid, **£2/7/6**. Balance in 9 monthly payments of 5/3.

LION SUPER P.M. MOVING-COIL SPEAKER. With Universal Transformer, 1-20 ohms and 2,000-40,000 ohms. Cone diameter, 10 in. Cash or C.O.D. Carriage Paid, **£2/15/0**. Balance in 11 monthly payments of 5/-.

1935 ADAPTAGRAM

● Convert your Present Set to a Magnificent Radiogram



Here is the ideal Cabinet for converting your present set to a magnificent Radiogram. Hand french polished by leading experts of London's piano trade. Chromium fret surround. All joints mortised and tenoned. Ready to take your set, speaker, power equipment and your own gram fittings. With ready-fitted motor board. Plain front or vignette to take any panel up to 18 in. by 8 ins. or more. 1/4" drilled to your own dimensioned sketch at slight extra cost.

Model "A" as illustrated. Cash or C.O.D., **63/-**. Carriage and packing 2/6 extra, England or Wales. Yours for 8/3 and 11 monthly payments of 5/9. **63/-**

● WALNUT, OAK or MAHOGANY to choice. ●

Model "B" Spring Motor
Standard 1935 Adaptagram with Double Spring Motor, 12in. Flush-covered Turntable, Automatic Stop, B.R.G. Tone Arm with Pickup, and Volume Control Complete—Automatic Needle Cup that delivers new needles one at a time to your finger tips. **6/8**. Cash or C.O.D.

Model "C" Electric Motor
Standard 1935 Adaptagram Cabinet—Collaro or Garrard Induction Electric Motor with Tone Arm, Pickup and Volume Control—12in. Flush-covered Turntable—Automatic Stop—Automatic Needle Cup that delivers needles one at a time to your finger tips. **7/8**. Cash or C.O.D.

or 12 monthly payments of 12/-.
Loud-speaker. Compensation: Baffle-Board fitted if required, 3/6 extra.

"Simply Plug-In"

1935 PILOT CLASS B SPEAKER-AMPLIFIER KIT

● GIVE A NEW LEASE OF LIFE TO YOUR PRESENT BATTERY SET. ●

This amazing unit will give seven times the volume with mains quality from your existing battery set. B.V.A. Class B Valve, 1935 Peto-Scott Permanent-Magnet Moving-Coil Speaker, B.R.G. Driver Transformer and 7-pin Valve Holder. Peto-Scott Baffle and Baseboard Assembly, all Wires and Screws. With full-size Diagrams and Assembly instructions.



Complete Kit as illustrated. Cash or C.O.D. Carriage Paid, **45/-**. Balance in 9 monthly payments of 5/-.

CONVERTS ANY BATTERY SET


PETO-SCOTT CO., LTD., 77, CITY ROAD, LONDON, E.C.1.
Telephone: Clerkenwell 9406/7. West End Showrooms: 62, High Holborn, London, W.C.1. Telephone: Holborn 3248.
Dear Sirs.—Please send me CASH/C.O.D./H.P.

for which I enclose £.....
CASH/H.P./DEPOSIT.
NAME.....
ADDRESS.....
P.B.W. 13/10/34.

Buy by Post—its Quicker—CASH—C.O.D.—EASIWAY

IS THE FRAME AERIAL DEAD?

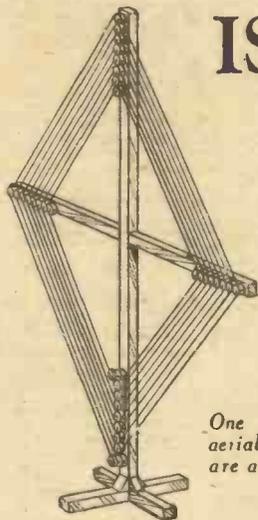An Interesting Discussion on the Merits of the Frame Aerial and Its Use with Modern Radio Receivers




One form of frame aerial in which the wires are arranged in "flat" formation.

THE frame aerial does not seem to be having a very great measure of popularity at the present time, and a visit to the majority of radio stores reveals a sad lack of display of this type of wireless accessory. Why is this? Is there anything in the device which renders it useless with modern receivers, or is it just that the present-day listener has lost sight of the various advantages which its use confers? As no doubt the majority of our readers are aware, the frame aerial possesses a very valuable feature which enables it to overcome the lack of selectivity which may be inherent in a radio receiver, and it is this important feature which enables a ship at sea to ascertain its position, or the position of a radio beacon.

How the Frame Works


The windings which are used in a frame aerial take the place of a tuned circuit, and a variable condenser is joined across the ends of this winding, which is then included in the grid-cathode circuit of a valve. Therefore, the wave-range which is covered by a frame aerial will depend upon the amount of wire which is included in its windings, and so to cover both medium and long waves, it will be necessary to use a tapped winding, with a change-over switch, in the same manner as a modern dual-range coil. This is probably one of the reasons why the frame aerial is not so popular today. A separate tuning condenser will be necessary for the frame, and in addition to the switching incorporated in the receiver,

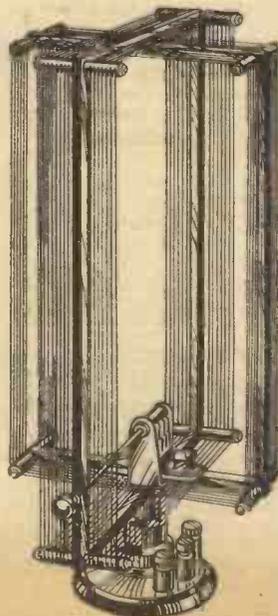

A novel commercial aerial having separate windings for medium and long waves. The change-over is effected by means of a multi-pole switch.

the wave-change switch on the frame will also have to be operated, so that two movements will be necessary to transfer from medium to long waves. This is in addition to the difficulty of tuning separate condensers for each station. Furthermore, the frame aerial will only be responsive to signals which arrive from a certain direction, and when the frame is positioned to be at right-angles to the incoming radio wave no signal will be heard. (This does not take into account the reception of a very powerful station situated at a short distance, which might be heard even when the frame is at right-angles.)


As the frame is turned so that its windings come more and more into the plane of the incoming radio wave, so the signal strength will grow, and will be at a maximum when the frame is in the same plane. This square form as is shown by this type of aerial, therefore, very valuable to those listeners who experience difficulties in cutting out a station which seriously interferes with the reception of certain stations not situated in the same direction. Naturally, when it is desired to hear a station situated, say, 500 miles away, and this station is badly interfered with by a station situated only fifty miles away in the same direction, the frame will not be of any use in reducing the interference.

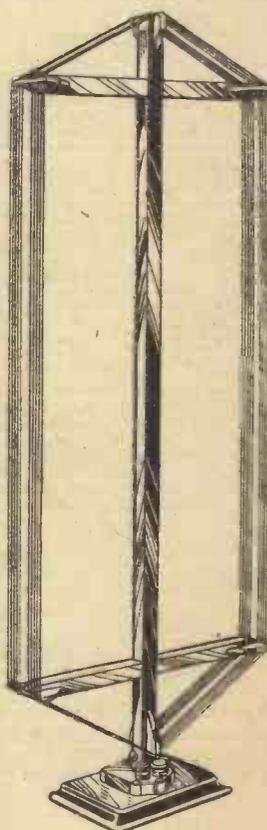

There is no necessity for the windings to be arranged in plane. This square form as is shown by this type of aerial.

The Superhet and the Frame

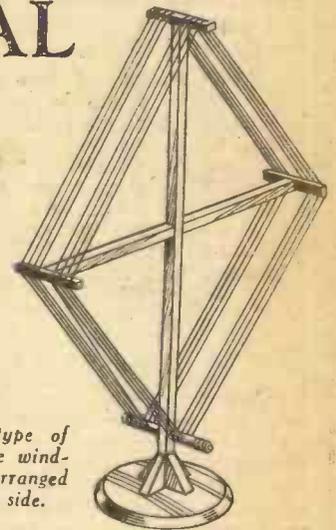
The greatest use of the superhet in the past has been in the super-heterodyne circuit, where the frame was centre-tapped, and was used in a special manner. The modern design of this type of circuit has rendered its use obsolete for this purpose,



In this type of frame the windings are arranged side by side.

but it still retains its selective property, and many listeners will probably find it of great value for receiving certain stations which are badly spoiled by interference with their present apparatus. A frame aerial may be wound in any form, as may be seen by examining the sketches of the various commercial aeriels shown on this page. For the medium wave-band from 70ft. to 75ft. of wire are required, and these may be wound in any desired form. Special thin flex is highly suitable for the aerial, and it should be passed across ebonite spacing strips at the ends of the frame-arms. Generally speaking, the length of the "sides" of the frame should not be less than 2ft., although for very small portable use a smaller size may be turned to account. Its efficiency is not so high, however, and it pays to use some dimension greater than 2ft. To make the aerial less cumbersome, the apparatus may be designed to fold up, when the ends of the frame should be firmly attached to the ebonite insulators.

For a long-wave winding about 230ft. to 250ft. should be employed, and thus for a frame aerial to cover both bands, a total of 250ft. should be employed, with a shorting switch across approximately 175ft. of the wire. It is possible to arrange a small winding in between the two sections just mentioned, in order to provide reaction effects, but the amount of wire and its disposition in relation to the long and medium windings is rather a matter for experiment and no exact details can be given.

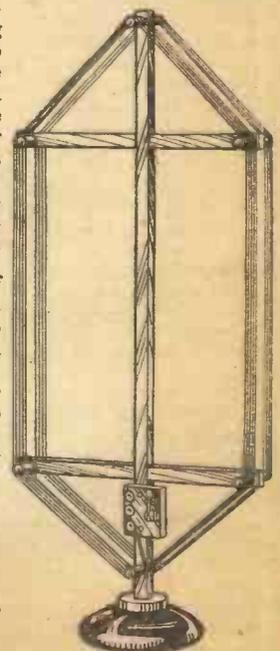

Another dual-range frame, in which a small switch changes from one band to another.

THE EASY ROAD TO RADIO.



THE BEGINNER'S SUPPLEMENT

H.F. AND L.F. COUPLING

A Simple Explanation of the Principles of Coupling Together Various Parts of the Receiver, with Some Practical Notes on Obtaining Maximum Efficiency.

THE process and method of coupling together the circuits and stages of a receiver are important points which are too often overlooked or insufficiently understood. Most experimenters and constructors realize that, if optimum results are to be secured, the coupling between the detector and L.F. stages, and also between the output valve and the speaker, must be properly matched, but they overlook the fact that the matching of high-frequency sections of the set is of even greater importance.

The question of coupling is bound up principally with such technical points as impedance (more correctly, relative impedances) and transformer ratios. It is not proposed to deal specifically with technicalities in this article, however, but to explain in simple language the main points which are involved. In the first place, it should be explained that the equivalent impedance (resistance to alternating current) of any output circuit should be similar to the impedance of the input circuit which it feeds. In other words, the impedance of the anode-coupling component used with one valve should be made to be equivalent to the impedance of the grid-filament circuit of the valve which follows it. It should also be explained that the grid-filament circuit of any valve is extremely high by comparison with the impedance of the anode-filament circuit, and also by comparison with the impedance of the aerial-earth circuit.

Matching Impedances

A transformer—of either the H.F. or L.F. type—provides the simplest means of matching impedances or securing the best coupling, because the ratio of the impedance of the secondary winding to that of the primary winding is proportional to the ratio of the secondary to the primary turns. The impedance ratio is not a simple proportion of the turns ratio, but is actually proportional to the square of the turns ratio. Thus, the impedance of the secondary winding of a transformer is equal to the square of the turns ratio multiplied by the primary impedance. For example, if the impedance of the primary winding of a so-called 1:5 transformer were 10,000 ohms the secondary impedance would be 10,000 multiplied by 5 squared, or 250,000 ohms; if the ratio of the same transformer were reduced to 2:1, the secondary impedance would become 40,000 ohms.

Impedance More Important than Ratio

It would appear from this that optimum

results would be obtained when the ratio of an L.F. transformer were made as high as possible, since then the secondary impedance would be greatest. In practice, however, this is not always the case, because increasing the ratio introduces

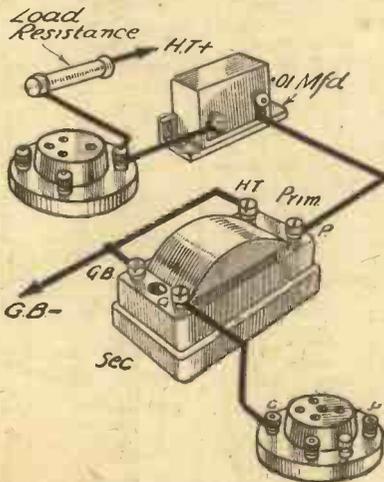


Fig. 1.—Showing the usual connections for parallel-fed transformer coupling.

other factors, not least of which is that of voltage step-up. A transformer increases the A.C. voltage flowing through the primary and decreases the accompanying

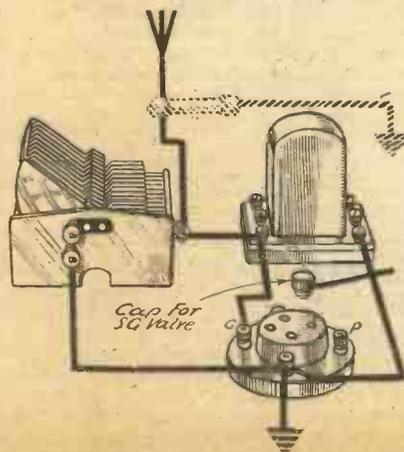


Fig. 2.—When the aerial is connected directly to the "grid" end of the first tuned coil, its low impedance acts as a parallel resistance across the grid-filament circuit of the valve, as shown in broken lines.

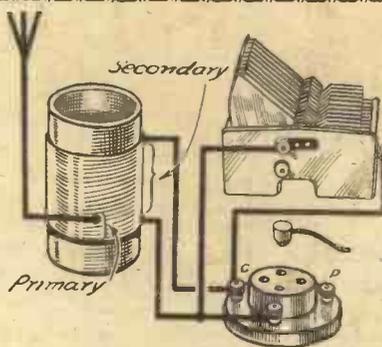


Fig. 3.—When a separate aerial winding is employed, this acts as the primary winding of a step-up transformer and assists in securing correct H.F. matching as explained in text.

current, but if the voltage is increased beyond certain limits the valve fed by the secondary circuit is in danger of being overloaded. Another difficulty introduced by the use of a high ratio is that of self-capacity which develops between the many turns of the secondary winding. In practice it is therefore generally better to use a transformer with a high primary inductance (which is the principal factor governing the impedance) and to have a moderate step-up ratio.

But the constants of the transformer are not governed only by the secondary impedance, but also by the primary impedance. The latter must be chosen to match the valve in whose anode circuit it is connected, and the value of the impedance in ohms should be equal to twice the A.C. anode-filament impedance of that valve. Thus, if the rated impedance of a detector valve is 15,000 ohms, the primary winding of the transformer connected in its anode circuit should be 30,000 ohms (at a frequency of about 1,000 cycles).

The above explanation shows why better results and greater amplification are often secured by replacing a high-ratio L.F. transformer by one of lower ratio. It also serves to explain the reason for the increased popularity of resistance-capacity transformer coupling with which the circuit is as shown in Fig. 1. In this case the primary winding of the transformer is not connected in the anode circuit of the valve, its place being taken by a fixed resistance. Because of this it is possible to employ a transformer with fewer turns, but with an equally-high step-up ratio without introducing the difficulty of self-capacity.

Finding the Best Ratio

The very same idea of coupling, or matching, applies when feeding the loud-speaker, because the impedance of its speech coil is usually between 2 and 10 ohms, whilst the impedance required in the anode circuit of the last valve is generally something like 10,000 ohms. In this case a step-down transformer is required, and the correct ratio can readily be determined by making use of the information given above. It can be seen that the correct ratio can be found by dividing the impedance required in the anode circuit by the impedance of the speech coil, and taking the square root of the answer. For example, if the impedance required (called the optimum load) were

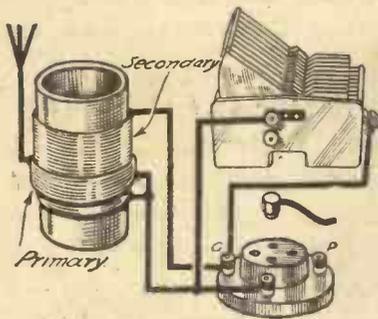


Fig. 4.—The use of a tapping for the aerial gives the same effect as that shown in Fig. 3. The virtual "primary" and "secondary" windings are shown in this drawing.

10,000 ohms and the impedance of the speech coil were 10 ohms, the ratio required would be the square root of 1,000, or approximately 32 to 1; actually a ratio of 30 : 1 would be chosen as being the nearest available.

Efficient Aerial Coupling

Turning now to the coupling of the aerial to the first valve, it can be seen that the same principles apply. The minimum grid-filament impedance of the valve might be considered to be 500,000 ohms, whilst the aerial-earth impedance is generally in the nature of a few hundred ohms. If the aerial were connected directly to the "grid" end of the first coil, as shown in Fig. 2, the result would be the same as if a low resistance were connected across the ends of the coil, and this would have the effect of "damping" the tuned circuit, making selectivity very poor and considerably reducing the signal output from the valve. On the other hand, if the aerial were connected to the end of a second small coil placed near to the grid coil, as shown in Fig. 3, conditions would be entirely changed. Supposing, for instance, that the grid coil consisted of 100 turns and the aerial coil of 10 turns, a step-up ratio of 1:10 would result, and the "impedance effect" of the aerial circuit on the grid circuit would be multiplied by 100. It can be seen that this would give better coupling, and one could expect an improvement in both selectivity and signal strength.

Auto-transformer Coupling

Although there are factors which tend

to counteract the theoretical improvement to be obtained by the use of a small and separate aerial winding, the fact remains that, if the winding is carefully chosen to suit the aerial characteristics, a decided improvement can be secured. The aerial impedance cannot readily be measured by the amateur, but it is by no means a difficult matter to vary the size and position of the separate aerial winding until optimum results are secured. An alternative to the separate winding which gives precisely the same effect is the use of a tapping-on the grid coil for aerial connection. This is shown in Fig. 4, from which it will be seen that the turns between the aerial tapping and earth represent the primary of the H.F. transformer, the total turns on the coil acting as the secondary. This arrangement is known as an auto-transformer and is frequently used on the L.F. side in conjunction with resistance-feed.

When using home-made coils, or when modernising a receiver, it is well worth while to experiment with various aerial tappings until that which gives the best coupling is found. Trials can easily be made by connecting the aerial lead to a pin, which can be pushed through the insulation of different turns so that it makes contact with the inner wire. When

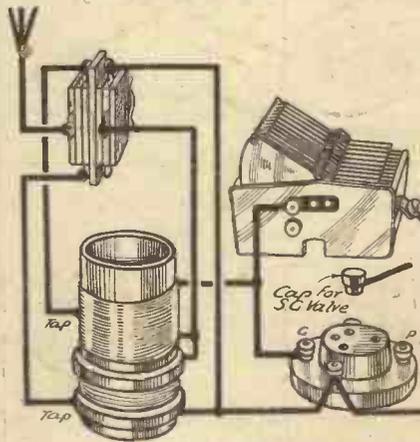


Fig. 6.—Best results are obtained by tapping both long and medium wave windings and using a double-pole wavechange switch connected as shown above.

the best position has been found, the appropriate turn can be lifted slightly away from the former with a knife blade,

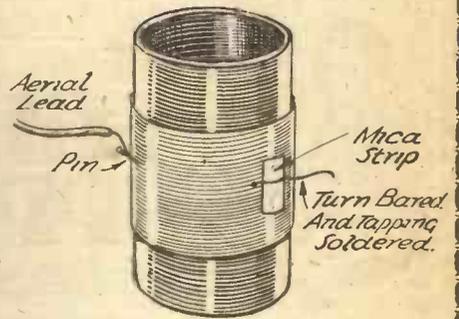


Fig. 5.—The optimum tapping point can be found by connecting the aerial lead to a pin which can be connected to various turns. After that a permanent tapping can be made as shown.

a strip of mica placed under it and a tapping soldered on. See Fig. 5. This should be repeated on the long-wave winding where possible and the two tappings brought out to a combined transfer and wavechange switch as shown in Fig. 6. Incidentally, it should be mentioned that this system is used on most up-to-date coils, and it is not generally to be recommended that any alteration should be made.

It will be understood from the explanation given above why improved reception is often secured by employing a pair of impedance-matching transformers in conjunction with a screened lead-in for obviating electrical interference. The transformer connected between the aerial and the lead-in gives a step-down effect, while that between the lead-in and the aerial terminal on the set steps-up the signal voltages. By carefully choosing the ratios of these two transformers it is possible to secure an optimum coupling when the aerial-earth impedance is exactly matched to the grid-filament impedance of the first valve in the receiver.

The principles explained in connection with the coupling of the aerial to the first valve apply with equal force to the coupling circuit employed between the H.F. valves, and between the last H.F. stage and the detector. It is for this reason that it is in many cases possible to secure much-improved reception by using tuned-transformer coupling and carefully experimenting to find the most suitable number and position of turns for the primary winding.

WE have already explained the necessity of using a condenser of the non-inductive type in various parts of the wireless circuit. It has been explained how the property of inductance is brought into a condenser owing to the manner in which the component is built up. On the normal wave-band the effect of the condenser is very marked, but when dealing with the lower frequencies the inductance due to the coil-like formation of the plates has a comparatively small effect on the impedance of the condenser. In this case it is the capacity which is the ruling factor, so that to obtain a low impedance path for L.F. currents it is necessary merely to use a condenser of large capacity.

How a Condenser is made Non-inductive
To overcome the deleterious effect of

HOW A CONDENSER IS MADE NON-INDUCTIVE
Concluded from p. 104, October 6th issue.

inductance in a paper condenser used in H.F. circuits they are made "non-inductive" by taking a connection from each turn of the rolled-up foil instead of just connecting two wires to the ends of the foil. (The difference was illustrated in Fig. 6.) Extra care is also taken with the disposition of the connecting wires within the case, since even a straight wire has self-inductance. They are therefore wound together to form a non-inductive pair, so that the inductance of the one wire neutralizes that of the other. In this way it is possible to reduce the in-

ductance of the condenser to negligible proportions. In fact, the small residual inductance present is usually masked by that of the external wiring which connects the condenser to other components in the receiver.

The mica condenser is, of course, non-inductive and needs no modification to the normal method of assembly. It is only when the dielectric plates are wound as in a paper condenser that this trouble of inductance arises. It is becoming very common to-day to design fixed condensers in a tubular form in order to produce a compact component for use with the modern small receiver, and it is here again that inductance must be avoided. When purchasing a fixed condenser therefore, make quite certain that the condenser is non-inductive unless you are sure that its position in the circuit does not render this precaution necessary.

HOW'S YOUR WATCH?

If you meet with an ardent radio fan, one who likes to do a bit of experimenting or generally playing about with his set or moving-coil loud-speaker, ask him the time. He is sure to tell you the history of a wonderful timekeeper suddenly developing a "one day fast and the next day slow" kind of attitude. Of course, if after reading this, he hits you, you will realize how many times he has been asked the question and is feeling very fed up. A mad watch is apt to lead to all sorts of serious situations and excuses. If you have a timepiece of which you are very proud and particularly one of the wrist type, put it away when you start tinkering with your radio set, otherwise you will find yourself, next morning, perhaps, waiting for the 8.30 train at 7.30 a.m. Many people do not realize the caution that is necessary when dealing with magnetic current apparatus, and particularly the more powerful moving-coil loud-speakers. Once the hair spring of

the watch becomes magnetized the only thing to do is to take it to a firm of experts and have it "demagged." That is, of course, if you do not know how to tackle the job with a coil of wire and some A.C. juice. Dr. Charles Edouard Guillaume received the Nobel Award in Physics about twelve years ago for finding a new alloy called "elinvar." When a hairspring of a watch is made from this new alloy it is unaffected by temperature changes and cannot be permanently magnetized. Such watches are being made in America for the use of electricians and radio service men, and can be worn near electrical apparatus without any ill effects. Unless they are held deliberately in an exceptionally strong magnetic field they are immune to magnetization. Even in that case a watch equipped with this type of hair spring resumes perfect running immediately it is removed from a magnetic field of such strength as to permanently magnetize every steel part, and which would put out of action any ordinary type of watch. A little precaution is often

better than a cure, so accept this word of warning for the protection of that family heirloom.

AN IMPORTANT EVENT!

See Next Week's Issue.

FINDING FAME UPSIDE DOWN

If a popularity vote was taken of broadcast artists there is little doubt Claude and Jack Hulbert would be very close to the top of the poll. Claude jumped into the limelight not merely head first, but on his head. That was when he played in "Tell Me More," in which he introduced those atrocities, "Oxford Bags," to a long-suffering British manhood. On that occasion he stood on his head on the stage and sang a song! Claude now delights great London audiences and millions of radio listeners. It is not generally known that Jack, his brother, made his debut when still at Cambridge.

A REVELATION!

For quality reception, Greater Output, and Current Economy, Ostar-Ganz H.F. Pentode and Pentagrid Valves (Austria) are revelations of efficiency. Made on the famous Universal High Voltage System, they build BETTER Sets at LESS cost. Performance unapproachable by any other Universal or D.C. Valves. Indirectly heated cathodes. NO Mains Transformers, NO Barretters. NO cut-down Resistances. SUPREME FOR SHORT-WAVE RECEIVERS. Manufacturers! Constructors! Write for interesting leaflet "C."

UNIVERSAL KITS

The only up-to-date proposition for home constructors is to build up a Universal All-wave Receiver Kit for A.C. D.C. or Universal Amplifier Kits for Dance Halls or public address. We also offer you the finest value in Radiograms. Write for leaflet "C," giving particulars of all our models to—

EUGEN J. FORBAT,
28/29, Southampton St.,
Strand, London,
W.C.2.
Phone: Temple Bar 8638.



THE LAST WORD IN RADIO

Universal ALL WAVES SUPERHET SEVEN.
The set that works on any mains, any voltage, any wave band, truly Universal. Receives all important stations in the world from 13 to 2,000 metres. Employs delayed A.V.C., fluid-light tuning indicator, and all the other latest refinements in Radio design.

Table Radiogram Model ... 30 Gus. Table Model ... 26 Gus.
Chassis complete with Valves ... 22 Gus.

Universal ALL WAVES SUPERHET FIVE.
For any mains, any voltage, any wave band. Covers a range from 19 to 2,000 metres. Reception obtainable from any part of the world, to any part of the world. The sets with easy control for perfect quality.

Table Radiogram Model ... 24 Gus. Table Model ... 18 Gus.
Chassis complete with Valves ... 14 Gus.

Special Features:—Great Output. Most economical in cost. NO BARRETTERS, RESISTANCES, MAINS TRANSFORMERS. Completely hum-free. Mains insulated. Write for interesting leaflet "C" to:—**UNIVERSAL HIGH VOLTAGE RADIO LTD., 28-29, Southampton Street, London, W.C.2. Phone: TEMple Bar 4885.**



A sudden noise—or an equally aggravating silence . . . inefficiency somewhere in your set! Take your AvoMinor and find out at once. The AvoMinor is an investment in permanent security, for it is a precision instrument, accurate to a critical degree, and made to stand up to hard usage and even abuse. It is, in fact, a younger brother of the famous Avometer, the instrument used by all the leading manufacturers and their service engineers. With the AvoMinor you can test circuits, valves, components, batteries and power units with the dependable accuracy of the technical expert.

There is no substitute for the AvoMinor. It is a moving coil combination testing meter—ten accurate instruments in one. Supplied in convenient case with leads and interchangeable testing prods and crocodile clips, and complete instruction booklet adequately illustrated.

Fully descriptive Folder post free from:—

THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.
Winder House, Douglas Street, London, S.W.1. Telephone: Vic. 3404/7

TEN ACCURATE METERS IN ONE

- | | |
|-----------------|----------------|
| CURRENT | VOLTAGE |
| ● 0-6 milliamps | ● 0-6 volts |
| ● 0-30 " | ● 0-120 " |
| ● 0-120 " | ● 0-300 " |

- RESISTANCE**
- | | |
|-----------------|-----------------|
| ● 0-10,000 ohms | ● 0-60,000 ohms |
| ● 0-1,200,000 " | ● 0-3 megohms |

40' Size 4" x 3" x 1 1/2"
Total Resistance: 100,000 ohms.
Full scale deflection on 3 milliamps.

Deferred Terms if desired.

THE D.C.

AVOMINOR
REGD. TRADE MARK
TELLS THE WHOLE TRUTH

"RADIO SERVICING SIMPLIFIED"
Everyone should have this invaluable new book. It explains every phase of fault-finding step by step in non-technical language. The comprehensive information and numerous diagrams make testing a matter of straightforward procedure.
2/6
Post free 2/9



"Good...that's found the fault...
what a good thing I bought myself a
PIFCO ROTAMETER"

A whole night's job becomes but a few minutes' work with the Pifco ROTAMETER.

The new De-Luxe moving coil model is amazingly accurate—it has a resistance of 200,000 ohms. The voltage scale registers up to 400 volts. In fact the ROTAMETER is a complete testing set in one handy-sized bakelite case.

Ask your dealer to show you one now or write for new Pifco Testmeter Folder, describing all instruments, to PIFCO LTD., SHUDEHILL, MANCHESTER, or 150 Charing Cross Rd., London, W.C.2



42/-

9 SEPARATE METERS IN ONE

- | | |
|---|--|
| <p>ROTAMETER</p> <ul style="list-style-type: none"> 1—0.8 volts. For low-tension voltage test. 2—0.30 volts. For grid-bias voltage test. 3—0.250 volts. For high-tension voltage test. 4—BATTERY TEST. 5—0.20 M.A. For individual valve test. 6—0.100 M.A. } For testing current taken 7—0.250 M.A. } by total valves in set. 8—FILAMENT AND RESISTANCE TEST (4,000 ohms). For D.C. and rectified A.C. 9—Plug-in test for valves. | <p>ROTAMETER-DE-LUXE.</p> <ul style="list-style-type: none"> 1—0.5 volts. 2—0.20 volts. 3—0.100 volts. 4—0.400 volts. 5—0.10 milliamperes. 6—0.50 milliamperes. 7—0.250 milliamperes. 8—Resist./valve test. 9—Plug-in test for valves. |
|---|--|



29/6

PIFCO ROTAMETERS

PIFCO ON THE SPOT WILL TRACE YOUR TROUBLES LIKE A SHOT

Build it with your own hands **LISSEN**
"SKYSCRAPER" BAND-PASS 3
WRITE FOR FREE CHART
LISSEN LIMITED, ISLEWORTH, MDDX.

362 VALVES
THE VALVE WITH THE SIX MONTHS GUARANTEE!

PIANO CABINETS
65/- RADIO-GRAM 35/- NO MIDDLE PROFITS.
Finest Radio Furniture as supplied to B.B.C.
PICKETT'S
LIST FREE.
GABINET (P.R.) WORKS, Bexleyheath, Nr. London.

10,000 MOTORS: Spring and Electric, for RADIOGRAMS or GRAMAPHONES in stock.
Thousands of components: Tone-arms, soundboxes, pick-ups, all types horns, pedestal-portable cabinets, fittings, hinges, lidstays, springs for all motors, gears, repairs, accessories. Portable Gramos from 12/6. Violins, strings for all instruments. Big trade discount. Radio goods to order. List free. 64 page Catal. "How to make them." 2d. Establ. 30 yrs. **THE REGENT FITTINGS CO.** (D.285) 120, Old St. London E.C.1.



Radio and Relaxation

Can Wireless Music Aid the Nerves?

A SHORT time ago I sat in one of the B.B.C. studios listening to the Wireless Military Band playing a well-known composition. A few nights afterwards, when visiting a friend, I heard the same band and composition rendered through his radio receiver, to which was attached an excellent mains excited moving-coil speaker. The lady of the house asked the lord and master to please lower the volume. I suppose the volume coming from the speaker was affecting her nerves. In my mind, I wondered whether had she been sat in the studio listening she would have found the music pleasant and a decided aid to relaxation. The majority of set owners never pause to analyse as I did, why, in one case, the result may be nerve-racking and in the other, restful. He may have the finest of radio sets, and be proud of drawing the attention of his friends to the bass response and mellowness of tone from the speaker, but if it continually jars upon the nerves, then there must be something very much wrong with either the set or the way it is handled.

NOISE SUPPRESSION

(Continued from page 134)

applied to the pentode will be equal to the sum of the voltage dropped across R3 and R4. The actual voltage need not be considered, for it will obviously be considerably greater than the normal figure, the result being that the valve is heavily over-biased and cannot function.

Approximate values of the various resistances and condensers are given in Fig. 2, but it must be explained that these might have to be modified slightly according to the particular valves employed; they are, nevertheless, sufficiently accurate as to serve as a basis for experiment. It should also be added that R1 is a variable potentiometer and serves as a normal manual L.F. volume control, in addition to providing the A.V.C. voltage. R2 is also shown as a potentiometer, since it is always best to adjust this carefully in order to secure the most suitable "cut-out" position for the actual receiver in use. The values of resistances R4, R5, and R6 are not indicated, but, instead, the voltage which they are required to drop is shown; the values can, therefore, be calculated according to the valves and H.T. voltage employed.

In practice it is frequently better to replace the double-diode triode by a double-diode pentode, or even to use a separate valve for noise suppression. The reason for this is that a valve is required which has a sharp bend towards the bottom of its grid volts-anode current curve, so that it gives a so-called "trigger" effect. In other words, the anode current must change from maximum to minimum with a very small change in applied grid-bias voltage. The resistance marked R7 is simply a manual-volume control working on the variable-mu valve, and is not a part of the automatic-volume control circuits. The resistances marked R3 are for decoupling only, and do not call for any particular consideration.

A maximum (smoothed) high-tension voltage of at least 350 is required for satisfactory results with an arrangement like that illustrated, and decoupling resistances of fairly high value should be used in the anode circuits of all except the last two valves, in order to limit the voltages supplied to the anodes to a maximum of 200.

RADIO CLUBS AND SOCIETIES

Club Reports should not exceed 200 words in length and should be received First Post each Monday morning for publication in the following week's issue.

SLADE RADIO

THERE was a lecture on "H.F. currents in connection with electro-medical apparatus," by Mr. L. G. Coads at a recent meeting of this society. After describing how the flow of electricity through the body raised the temperature, he went on to deal with the galvanic effect. The system used for H.F. treatment was described together with the apparatus and the circuit. Diathermic systems came next, and their uses were described. During the evening demonstrations with H.F. and diathermic apparatus were given, and it was shown how current flowing through the body could be made to light a lamp. The effect of H.F. apparatus on reception with an A.C. wireless receiver was also demonstrated. A short description of the H.F. knife was given and at the conclusion of the lecture a large number of questions were raised.—Hon. Sec., 110, Hillarles Road, Gravelly Hill, Birmingham.

THORNTON HEATH RADIO SOCIETY

THE eleventh annual general meeting of this society was held at St. Paul's Hall, Norfolk Road, on Tuesday, the 25th ult. In his opening remarks the Chairman, Mr. S. J. Meares, welcomed the Vice-President, Mr. Ernest Scratchley, and said that in his recollection he had attended every annual general meeting of the society.

Before vacating the chair Mr. Meares informed the members that Mr. Scratchley had decided to resign his position as Vice-President of the Society, and then asked Mr. Scratchley to give his reasons for making this decision.

Mr. S. J. Meares, Mr. J. T. Webber, and Mr. O. L. Crossley were again elected to fill the offices of Chairman, Hon. Secretary and Hon. Treasurer respectively. Mr. Meares then outlined the future policy of the society, which he said must cater for those members who were interested in short waves and television. Some discussion ensued, as a result of which it was decided to alter the name of the society in such a way as to indicate that these subjects were also included, but it was left to the Committee to decide upon the new name. Hon. Secretary, Mr. Jas. T. Webber, 368, Brigstock Road, Thornton Heath.

INTERNATIONAL DX'ERS ALLIANCE

THIS go-ahead society has still further increased its activities by expanding its S.W. Section, and Captain H. L. Hall has been appointed to take charge of this branch. The ever growing importance of short-wave work, coupled with the fact that the I.D.A. numbers many S.W. enthusiasts among its members, has led the society to take this important step. The current issue of the *Globe Order*, the official organ of the society, gives full particulars of the new venture, together with other information of special interest to DX fans throughout the world. All inquiries should be addressed to Richard L. Rawles, Blackwater, Isle of Wight, England.

ANGLO-AMERICAN RADIO & TELEVISION SOCIETY. THE society wishes to make it clear that it cannot guarantee to answer letters when a stamped addressed envelope is not enclosed. Those desiring to join may do so by sending their names and addressed to H.Q.

The first winter lecture to be held under the auspices of the West Middlesex and East Buckinghamshire Branch of the Anglo-American Radio and Television Society will be given by Mr. J. Louis Orton on October 31st, 1934. The lecture will be given in aid of the funds of the branch. Full particulars may be obtained from Mr. Leslie W. Orton, "Kingsthorpe," Willowbank, Uxbridge.

SENSATIONAL OFFER TO EVERY READER

"DO IT YOURSELF!"

A golden opportunity to obtain a complete Householder's Guide. This money-saving book will enable you to carry out successfully the many jobs that make an up-to-date, well-run home. Full details in

TIT-BITS

NOW ON SALE — — — 2^D

WORK WAITING FOR TRAINED RADIO MEN

••• Trained men are constantly needed. We give the training that brings success. We have done so for others; we can do the same for you.

Study at home and prepare yourself for well-paid employment. Our Courses cover the whole theory of modern radio and are specially prepared to teach the student how to turn his knowledge to practical use. Special attention is given to modern servicing methods.

You cannot hope to succeed unless you know your job. You cannot just "pick it up." You must be trained by radio experts who know the sort of knowledge you need and will help you if you experience any difficulties.

Our training is praised and recommended by leading radio manufacturers and the Technical Press. One very reasonable fee (which can be paid by instalments if desired) covers the whole Course. There are no additional expenses. You do not have to buy text books or apparatus.

Are you ambitious, with an eye to the future? If so you will send at once for a free copy of our latest prospectus and learn how we can train you for success, as we have trained others.

Read what these T.C.R.C. students say:

"I have much pleasure in announcing an increase in salary and promotion."—J. A.

"I start work on Thursday. I thank you for all the valuable help you have given me."—G. F.

"I am pleased to say that I have secured a post since the starting Course which promises good prospects for the future."—R.H.W.

"He engaged me at a big increase in salary to what I am now getting. I cannot thank you enough and I feel I couldn't have got this situation without your help."—A. G.

"Mr. . . . gave me a job which has great possibilities. I feel I can never thank you sufficiently for the extreme trouble you have taken in helping me."—P. L.

"Since enrolling I have taken over practically all the battery set work for a local dealer"—J. T.

And many more which prove that the T.C.R.C. training does genuinely give you the ability to obtain radio work and earn good money.

TURN YOUR SPARE TIME INTO MONEY.

If you do not require full-time employment, we can train you to earn money in your spare time. Set designing, inventing, demonstrating, installation, maintenance, servicing, set building, writing for the Press, accumulator charging, and many other interesting occupations which will not interfere with your ordinary occupation, can bring you in additional money and prepare you for full-time employment in the future, should you need it. Make your hobby pay; we will teach you how.

To: T. & C. Radio College,
Cromwell House, High Holborn, London, W.C.1.
Please send me free copy of your latest Prospectus (1d. stamp if posted in unsealed envelope.)

Name

Address
Pr.21

TECHNICAL & COMMERCIAL RADIO COLLEGE

CROMWELL HOUSE,
HIGH HOLBORN, LONDON, W.C.1

Telephone: Chancery 7054 & 7055.

DROITWICH BAND CONTROL COILS

FULLY DESCRIBED BY
MR. F. J. CAMM ON PAGE 135


DO YOU receive RADIO-PARIS without interference from DROITWICH? Only if you have fitted B.T.S. BAND CONTROL COILS. No other coils give that high degree of selectivity characteristic of modern commercially manufactured Sets. It is the result of the NEW WAVE WINDING, for the first time made available to the Home Constructor by B.T.S. Interchangeable for Aerial or Anode Circuits... makes a wonderful improvement in selectivity to many PRACTICAL WIRELESS DESIGNS... See what Mr. F. J. Camm recommends in this issue.

3/6 EACH

OBTAINABLE FROM ALL RADIO DEALERS In case of difficulty send direct... postage refunded



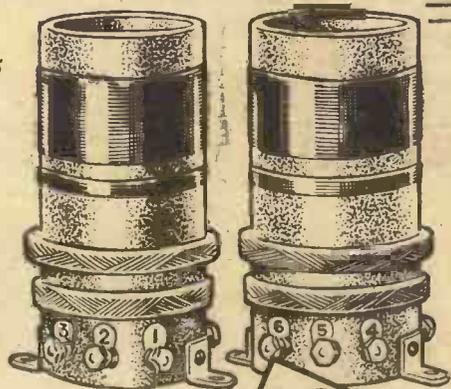BRITISH TELEVISION SUPPLIES, LTD., BUSH HOUSE, LONDON, W.C.2
Telephone: TEMPLE BAR 0134. Telegrams: TELEVIEW, BUSH, LONDON.



See the New Winding - it gives Band Control



By JACE

Pifco's New Premises

THE illustration given below shows Pifco House, the new premises of The Provincial Incandescent Fittings Co., Ltd., particulars of which were given in a recent issue.

The End of Morse Telegrams

AFTER seventy years, the last morse telegram was dispatched a few days ago from the Central Telegraph Office. In future all telegrams will be sent by automatic teleprinter machines, which can send 100 telegrams of average length an hour—more than double the capacity of the old morse instruments. An operator can be trained in six months to send eighty telegrams an hour.

Wireless for Empire Airways

THE five new D.H. 86 four-engined aeroplanes for the Singapore-Brisbane section of the England-Australia air route, which is expected to be opened by QANTAS Empire Airways Limited, in December this year, are being fitted with Marconi transmitting and receiving equipment to enable them to maintain constant wireless contact with the ground or with ships and coast stations. They will also carry the Marconi "homing" device, type A.D.32d, as an aid to navigation.

The sets with which they are being fitted are of a special type, known as the A.D.37 c/38b, designed particularly for long-distance routes of this nature. Transmission and reception, by telephony or telegraphy, can be carried out on either short or medium wavelengths (40 to 80 and 500 to 1,600 metres), an arrangement which enables regular communication to be maintained under severe atmospheric conditions and over great distances.

The A.D. 37/38 apparatus was used with conspicuous success on the survey flight for this air route carried out by Major H. G. Brackley, Air Superintendent of Imperial Airways Limited, in the aeroplane *Astraea* in the summer of last year, when messages were exchanged between the ground and the aeroplane at distances of up to 3,500 miles.

The "Homing" Device

THE Marconi "homing" device is one of the latest aids to air navigation, requiring no special ground organization.

It enables a pilot to set a direct course towards any suitable wireless transmitting station along the route, and has proved simple and efficient in actual operation on the Indian and African air routes.

Centenary of Birmingham Town Hall

ACCORDING to a recent B.B.C. announcement, the whole of the concert which is to celebrate the Centenary of Birmingham Town Hall will be broadcast from the Midland Regional on October 4th. Birmingham Festival Choral Society, the City of Birmingham Choir, and the City of Birmingham Orchestra will be heard in Handel's Coronation Anthem, Coleridge-Taylor's "Hiawatha's Wedding Feast," and Mendelssohn's "Thanks be to God." The conductors are Harold Gray, G. D. Cunningham, and Leslie Heward respectively. Frank Titterton, the tenor soloist, is a native of Birmingham. The orchestra will give Purcell's Trumpet Voluntary and Elgar's Enigma Variations. G. D. Cunningham, the City Organist, will play Bach's Fugue in E flat. In the interval a local veteran will relate his reminiscences of Town Hall concerts during the past fifty-five years. Birmingham Town Hall was designed by Hansom, who went bankrupt before it was completed; he afterwards invented the hansom cab. The building has seen several notable first performances—Mendelssohn's "Elijah," conducted by the composer, who appeared three times at the Triennial Festival; Elgar's "Dream of Gerontius," "The Apostles," and "The Kingdom." Jenny Lind and Patti have both sung there, and Dickens once gave



Pifco House, the new headquarters of Pifco, Ltd.

readings. A great festival to celebrate the Abolition of Slavery, the launching of Joseph Chamberlain's Tariff Reform Campaign, and the presentation of the Freedom of the City of Birmingham to Mr. Lloyd George after the Great War are notable events in the history of the Town Hall. During the Boer War, Mr. Lloyd George had to make his escape from the rear of the building disguised as a policeman!

Choosing a Set

A REQUEST was recently sent to me asking if I would recommend a really efficient commercial all-mains receiver, the outstanding merits to be selectivity

and fidelity of reproduction. I studied the district in which it would be required to operate, got particulars of the acoustic properties of the room, and, together with other information, I found the operator had a musical ear, for he was a teacher of music. This was a problem which required careful thought, because too much selectivity and perfect reproduction do not run very well together in harness. However, I decided on a receiver and advised the inquirer to arrange with the manufacturers for a demonstration in the home and under the actual conditions it would be required to operate. The set had two stages of variable- μ high-frequency amplification, power detector, and a push-pull output. This was coupled to what I consider to be the finest and most faithful energized moving-coil loud-speaker. Eventually I received a letter which did not contain any thanks for the trouble I had taken, but upbraided me for suggesting such an instrument. The set was selective, but the heavy bass reproduction made him feel positively ill. He could not listen to it with the least pleasure. The letter went on to say he had visited the local radio store and had been induced to allow the storekeeper to make him up a three-valve set from a well-known kit, together with a cone speaker. This was giving perfect satisfaction at about one-eighth of my suggested cost. I am left wondering whether the musical ear has lost much of its keyboard perfectibility or whether it is a case of jingling coins covering up the desideratum.

Your very last chance

IF you have not yet reserved your Presentation Copy of Newnes' TELEVISION and SHORT WAVE HANDBOOK under the terms of our special offer, you can still do so—but you must HURRY!

This offer is on the brink of closing, but we want as far as possible every one of our readers to possess this unique work; hence this "eleventh hour" reminder.

OUR GREATEST GIFT OFFER

NEWNES'
TELEVISION
AND
SHORT WAVE
HANDBOOK

Yours for only 2/6 and Nine P.W. Gift Tokens

This remarkable book, which has been specially written by Mr. F. J. Camm and is packed with up-to-date information on television, was described at length in last week's *Practical Wireless*. The same issue contained the Simple Conditions of our offer and the necessary Reservation Form. Please turn to it (or ask your Newsagent for a copy), fill in and post the Form at once—and thus make sure of obtaining your Presentation Copy of this unique Handbook.

SUPPLEMENT TO "PRACTICAL WIRELESS"

AMATEUR TELEVISION

TELEVISION SIGNAL DISTORTION AND CORRECTION

By H. J. BARTON CHAPPLE, B.Sc., A.M.I.E.E.

(Continued from October 6th issue)

AS well as phase and attenuation distortion there is a third type of distortion which is sometimes present in transmission circuits for television signals. This arises when a line of one characteristic impedance is joined to another of a different characteristic impedance without adequate compensation at the junction. A pulse of current provided by a television signal on reaching such a junction is partly transmitted and partly reflected, the phase of this reflected pulse depending on whether the signal is propagated from a line of less to greater or greater to less impedance.

To overcome the effects of reflection, which, if several uncompensated discontinuities occur in sequence, gives rise to "echoes" or "ghosts" in a reconstructed television image, somewhat as indicated in Fig. 1, a compensating network is used. This presents an impedance in one direction equal to the characteristic impedance of one line, and in the other an impedance equal to that of the other, and a network of this character is called a transducer.

sideband difficulty, without resorting to extremely low wavelengths, is akin to inventing perpetual motion machines.

Even when the correct characteristic is provided at the transmitting end of a radio link, it is still necessary to pay attention to the radio set employed for feeding the signals to the television receiver. For example, the best means to obtain tuning efficiency is to use two or more tuned circuits connected up by one of the band-

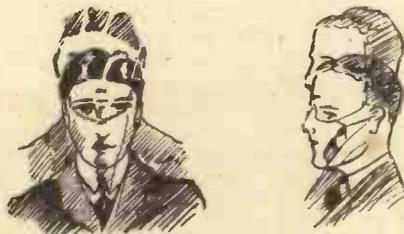


Fig. 1.—A television image with its echo or ghost image.

On the Radio Side

When the television signals are transmitted by radio, although the various forms of line distortion just discussed are not present in the actual radio link, another set of equally, and sometimes greater, deleterious effects is noticeable. First of all, at the radio transmitter itself precautions must be taken to ensure the correct handling of a wider range of frequency components than is required for the transmission of sound. To obtain a recognizable image reproduction the full 9 kilocycles channel width is necessary even with the normal thirty-line B.B.C. transmissions, and if this frequency band could be increased to 20 kc/s then the reproduction would improve considerably, especially if equalization for aperture distortion in the actual television transmitter itself is effected.

Added to this is the necessity for dealing with a number of inconstant and random distortions depending on conditions largely beyond human control. Of these, night fading (image dims or vanishes), atmospheric interference (light streaks or splashes right across the image), and frequency shift (image blurring) can be very largely reduced by taking due precautions, such as automatic volume control, balanced circuits, and crystal control. Others, however, like skip distance, night-phase distortion, and "echo" are almost beyond human control, although there is reason to believe that even these effects may be minimized or perhaps obviated by the use of aerial arrangements of special form.

An Artificial Limitation

The most serious form of distortion in the television service is the artificial one of imposing the 9-kilocycle sideband width. This sets a limit upon the amount of intelligence which can be propagated per second in so certain a manner that searching for a system of television which will overcome

pass tuning schemes. This, of course, reduces the possibility of "cutting" the higher frequencies so essential for detail in the image, although there is an artificial

NEW TELEVISION TRANSMISSION TIMES.

The times of the television transmissions are being altered and the new hours are as follows:

Week commencing October 8th. One transmission only, on Saturday, 4.30 to 5.15.

Thereafter there will be two transmissions per week: Wednesday evening, 11.0 to 11.45, and Saturday afternoon, 4.30 to 5.15.

method which has been suggested for obtaining an extended band-pass in radio receivers, as shown in Fig. 2.

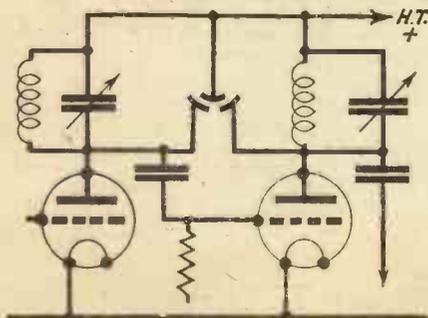


Fig. 2.—An artificial method for obtaining extended band-pass in radio receivers.

IT WAS THIS FREE BOOK WHICH LED ME TO SUCCESS

ENGINEERS!

JOHN WILSON AMALGAMATED ENGINEERING COMPANY

BE ADVISED IN TIME.

A FEW LETTERS AFTER YOUR NAME WILL MAKE ALL THE DIFFERENCE TO YOUR FUTURE CAREER

This is the day of the specialist. The man who is just a mechanic cannot go far. It is the man who can use his head rather than his hands, and has some letters after his name to prove his mental ability who gets the well-paid jobs.

Let us show you how, in the privacy of your own home, we can quickly prepare you for those salary-increasing qualifications, such as A.M.I.Mech.E., A.M.I.E.E., A.M.I.A.E., A.M.I.W.T., etc.

We Guarantee "NO PASS—NO FEE." Send to-day for our unique 256-page Guide "ENGINEERING OPPORTUNITIES." Among a host of interesting matters this guide gives details of all recognised Examinations and outlines over 100 Courses in all branches of Civil, Mech., Elec., Motor, Radio, and Aero Engineering, etc. This book must benefit you. Send for your copy to-day, FREE and without obligation. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, 390, SHAKESPEARE HOUSE, 29-31, OXFORD STREET, LONDON.

NEW SERVICE FOR HOME CONSTRUCTORS.

H.P. WITHOUT TEARS!

YOUR SIGNATURE ALONE OUR GUARANTEE

NO GUARANTEES. NO REFERENCES. IMMEDIATE DESPATCH ON RECEIPT OF DEPOSIT. FREE. Fill in coupon and post in id. envelope to-day; for (1) full particulars of this revolutionary new system; (2) supply of EasyPAY special order forms; (3) the huge EasyPAY Budget, covering your every radio requirement.

MR.

.....

.....

(S.W.)

EASYPAY RADIO
6, CONDUIT STREET
REGENT STREET
LONDON W.1

MAYFAIR
3163-4

EASYPAY UTILITIES LTD.

FREE ADVICE BUREAU COUPON

This coupon is available until October 20, 1934, and must be attached to all letters containing queries.

PRACTICAL WIRELESS, 13/10/34.

THE WIRELESS CONSTRUCTOR'S ENCYCLOPAEDIA

(2nd Edition)

By F. J. CAMM

(Editor of "Practical Wireless.")

Obtainable at all Booksellers or by post 5/6 from Geo. Newnes, Ltd., 8-11, Southampton Street, Strand, London, W.C.2.

5/-

REVIEWS OF LATEST RECEIVERS

IN 1927 A. C. Cossor introduced the first Melody-Maker, and it proved a very popular kit set. Each year the receiver has been brought up to date, and the two newcomers, introduced just before the Olympia Exhibition, are excellent examples of present-day design and embody every possible improvement and many advanced features. The two new kits are exactly similar in appearance, but one is an A.C. Mains model while the other is intended for battery working.

The Circuit

The circuit of the mains model employs three valves and a rectifier. The first is a Cossor MVSG acting as a high-frequency amplifier with high-efficiency iron-cored coils in both grid and anode circuits. These coils are very robust and at the same time exceptionally efficient, a combination not easy of attainment.

The defector stage is particularly interesting as it employs the Cossor MS/PEN, a high-frequency screen-grid pentode acting as power-grid detector. The advantages of such a detector are threefold—the stage amplification is much greater than that available from a triode; the selectivity is greater for all reasonable settings of reaction and, in addition, quality is improved, partly due to the low inter-electrode capacity of the valve and also due to the use of resistance coupling instead of the more usual transformer arrangement.

The output valve is a Cossor 41MP feeding a mains-energized moving-coil loud-speaker with an output transformer specially designed to suit the valve, which when thus correctly loaded is capable of an undistorted output of something over 1 watt.

Simple Control

The controls are provided for single knob tuning (with trimmer), selectivity (reaction), volume, and switching. An ingenious arrangement is incorporated so that when the wavechange switch is in the long- and short-wave position, only the appropriate section of the dial is illuminated, while the gramophone position is indicated by the illumination of both scales. The gramophone position on the switch allows the pick-up to be permanently connected to the receiver and obviates the nuisance of having to withdraw a plug and jack.


The chassis is of heavy-gauge steel, sopper plated on the underside, the latter to ensure that good contact is made with such wires as are earthed direct to the base plate. The constructional chart is an outstanding example of clear and fool-proof instruction, and assembly is also facilitated by the clean cut holes in the chassis and the ease with which all the parts fit together.

A considerable saving of time is effected in wiring, as the length of each piece of systoflex and flexible wire is already correctly made as shown on the chart.

With customary thoroughness a small spanner is included for forgetting at the awkward fixing nuts, a large spanner for tightening up the large component nuts, and a special small screw-driver for tightening grub screws.

Test Results

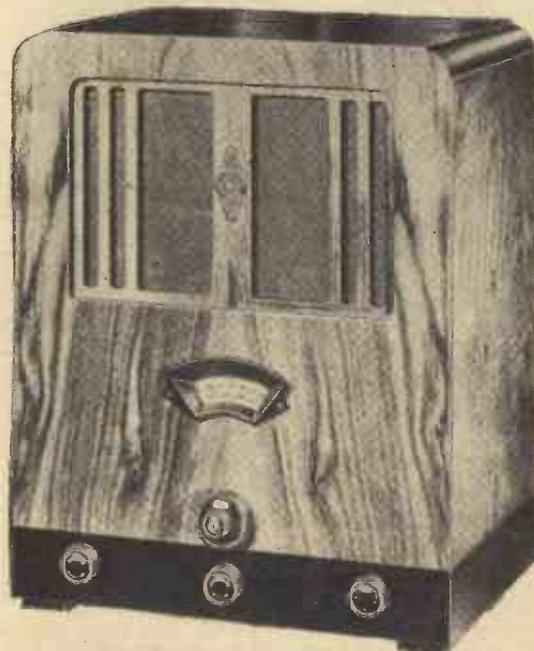On test the performance reached a high standard, selectivity and sensitivity being present at the same time in a remarkable



The Cossor 1934/35 All-mains Melody-Maker in its attractive cabinet.

degree, thus justifying the makers' claim that the set is more selective than had hitherto been thought possible when using only three valves.

Reproduction is excellent, and the increase of top brilliance due to the pentode detector is most noticeable. Mains hum is absent, and cannot be heard at a distance of eighteen inches from the speaker, even during an interval.

The cabinet is well finished in walnut and black and conveys the idea of a relatively expensive factory built receiver rather than a kit of parts.

The Cossor All Mains Melody-Maker, which is known as model 357, is sold complete with four valves (including rectifier) and every conceivable item required from the smallest screw to the ready finished

cabinet. It has terminals for a gramophone pick-up and plug and socket for extension loud-speaker and is suitable for use on A.C. Mains only 200/250 volts (adjustable) 40/100 cycles.

In addition to this kit set, Messrs. Cossor also supply some other highly efficient receivers in which novel and up-to-date features are included. These range from a simple battery set to all-mains radio-gramophone. The all-mains radio-gram model 536 employs four A.C. valves, consisting of variable-mu, S.G., H.F. pentode as a detector, and a pentode-output stage with a valve acting as a full-wave rectifier. A loud-speaker of the mains-energized moving-coil type is fitted and the circuit embodies the useful features described in the preceding paragraphs. That is to say, single-knob tuning, full vision scale calibrated in wave-lengths, combined on-off wave-change gramophone switch, and volume control. The motor is of the induction type, perfectly silent in operation, and accommodating up to 12-in. records. The pick-up and tone arm are of advanced design and give really high-class reproduction from standard gramophone records. The console cabinet in which this receiver is fitted measures 3ft. by 1ft. 6in. by 1ft. 5in. deep and is thus highly suitable for the modern

house, in which it will be perfectly in keeping with normal furnishing methods.



The chassis of the new Cossor Melody-Maker is made of blue steel, and employs a rather unusual form of mounting for the rectifying valve.

CATALOGUES RECEIVED

To save readers trouble, we undertake to send on catalogues of any of our advertisers. Merely state, on a postcard, the names of the firms from whom you require catalogues, and address it to "Catalogue," PRACTICAL WIRELESS, Geo. Neumes, Ltd., 8-11, Southampton St., Strand, London, W.C.2. Where advertisers make a charge, or require postage, this should be enclosed with applications for catalogues. No other correspondence whatsoever should be enclosed.

MAGNAVOX.
 AN attractive booklet recently issued by the Benjamin Electric Ltd. contains full technical particulars of the new Magnavox Model Sixty-Six Loud-speaker. This is a mains-energized moving-coil model with an 11in. diameter cone having a number of corrugations spaced about 3/16in. apart across the diaphragm. This arrangement makes a considerable difference to the behaviour of the speaker at medium and high frequencies. This new speaker is finished in ebony and chromium plate, and is available in either D.C. or A.C. types. There are two D.C. models, having 700 and 2,000-ohm field coils respectively, each model being supplied complete with hum neutralizing coil and tapped transformer. The A.C. model (for 200 to 240 volts, any frequency) includes a Westinghouse rectifier and full smoothing circuit. The current consumption is 25 watts.

DUBILIER CONDENSERS
 A FULL range of these well-known components is given in a new season's booklet just issued by the Dubilier Condenser Co., Ltd. The condenser and resistance requirements of the latest modern practice are adequately represented. Included in the range are mica condensers for use where operating conditions demand large capacities and high voltages; paper dielectric condensers; non-inductive condensers; high voltage and low voltage dry electrolytic condensers. A range of metallized resistances, ten-watt wire-wound resistances, car radio suppressors, and anti-interference devices is also dealt with in the booklet. The particulars of each component are set out in a concise and categorical manner making for quick reference, thus making the booklet particularly useful to experimenters and set constructors, who are advised to write for a copy.

TALKS FOR DISCUSSION GROUPS
 A NEW B.B.C. pamphlet entitled "Talks for Discussion Groups" is now available. In this pamphlet details are given of the various series which have been planned for the coming winter in the National programme, and are specially devised to meet the needs of those who listen in discussion groups. This is the first time that talks have been deliberately arranged for this purpose, although in the past there have been a number of series which have been recommended to groups. During this autumn the three series will be: Poverty in Plenty; Freedom and Authority in The Modern World; The Child, The Parent, and The Teacher.
 Two other series to be broadcast after Christmas, of which details will be found in the pamphlet, are "Markets and Men" and "The Artist and his Public," by Mr. Eric Newton. An outline is also given of a special series in the Scottish Regional programme called "Changing Scotland." The pamphlet, which also contains syllabus of nearly every talk, together with special questions for discussion, suggestions for group leaders, maps, etc., can be obtained from any B.B.C. station, price twopenny (post free). Free copies are being supplied to leaders of wireless discussion groups.

BOOKS RECEIVED.

"**RADIO COMMUNICATION: History and Development.**" by W. T. O'Dea, B.Sc., A.M.I.E.E., price 2s. 0d. post free. This book is a brief and profusely illustrated Science Museum Handbook which traces the history of radio communication from what were inexplicable phenomena in 1780 up to the latest modern developments. Some of the subjects covered are: early experiments, types of detector, the growth of commercial telegraphy, the thermionic valve, telephony and broadcast transmission, the development of the broadcast receiver, television, loud-speakers, and microphones. The illustrations include historical apparatus from the museum collections and elsewhere, early and modern transmitters, and several drawings and diagrams. Technicalities have been reduced as far as possible to a concise description of cause and effect, so that the majority of those interested in the story of radio science should not find this handbook too difficult to follow. At the same time it should provide a valuable supplement to the text-books of the radio student.

A MOMENTOUS ANNOUNCEMENT IN NEXT WEEK'S ISSUE!

LUCERNE S.G.3

BUILD IT YOURSELF
FREE FULL-SIZE BLUEPRINT
and ASSEMBLY INSTRUCTIONS
with every KIT

Expressly
 Designed
 for Modern
 Broadcast
 Conditions



Designed by PETO-SCOTT, specialists in KITS of Parts for the Home Constructor since 1919.

EFFICIENCY.—The Peto-Scott Lucerne S.G.3 stands unparalleled among modern Kit sets for selectivity, range, volume and tone under even the most difficult reception conditions.

SIMPLICITY.—The operation of the Lucerne S.G.3 is simplicity itself, the capture and separation of stations a matter of ease to the least radio-minded. Equally simple is the assembly of the Kit, requiring no experience and a few everyday tools.

ECONOMY.—Outstanding value for money and extremely low running costs make the Lucerne S.G.3 a most economical investment for those desiring a home-assembled set with which to enjoy Radio programmes to the full under the existing conditions of the Ether.



BEAUTIFUL CABINETS.—Two beautiful Walnut cabinets (a Console Model as illustrated and a Table Model) are available for the Lucerne S.G.3 at the constructor's choice.

SEND FOR FOLDER L6

KIT "A"
39/6

YOURS FOR 2/6

Comprising complete kit of parts, including ready drilled walnut panel and valves, cabinet and 11 month-ly payments of 2/6
 Metalex baseboard; less speaker, Cash or C.O.D., Carriage Paid 3/6
 3/9

KIT "B" As Kit "A" but with set of 3 B.V.A. Valves: S.G., Detector and Super Power, less Cabinet and Speaker, Cash or C.O.D. Carriage Paid 23 8s. 6d. YOURS for 5/- and 11 monthly payments of 6/6.

KIT "C" As Kit "A" but with valves and Peto-Scott Walnut Table Cabinet less Speaker, Cash or C.O.D. Carriage Paid 24 2s. 0d. YOURS for 5/- and 11 monthly payments of 7/6.

KIT "CC" As Kit "A" but with valves and Peto-Scott Walnut Console Cabinet as illustrated, less speaker, Cash and 11 monthly payments of 8/3 or C.O.D. Carriage Paid, 24 7s. 0d.

Type S.L., required add 1/6 to cash prices or add 1/6 to deposit and each monthly payment.

PETO-SCOTT Co. Ltd. 77, CITY ROAD, LONDON, E.C.1
 West End Showrooms— Phone: Clerkenwell 3406/7
 62, High Holborn, London, W.C.1. Phone: Holborn 3243
 EST. 1919.

GET A DIX-ONEMETER

The ideal of multi-range moving coil meters. Microamps to 20 amps, milli volts to 1,000 volts. 50 ranges on one meter. Two clear scales with mirror and knife edge pointer.

ONLY **55/-**



Remarkably low price for a meter worth £10. For Novice or expert. Test Booklet Free.

The High-grade Radio Tester. Low Price. High Value. INSTRUMENT IN CASE, 60/- MULTIPLE, EACH, 6/6. COMPLETE RADIO OUTFIT **£4.17.6**

LESDEX Measuring Instruments, 2 1/2in. bakelite case, flush panel, any reading, A.C. or D.C.; from 6/- each; ask for full range instrument list.—"N."

MAINS TRANSFORMERS for bells, models, lamps, etc.: 3-5-8 volts 230 volts double, 3/6; 110 volts, 2/6. Postage 6d.


TELESCOPES, 9-mile distance. Naval Gun Sighting Telescopes, internal focus ring, 2 1/2in. long, 2in. dia., weight 6lb., magnification 6, for short and long range. Cost £25. Sale, 17/6. Officers' Spotting Telescopes, 17in. x 1 1/2in., 25/- each.

Double Current **DYNAMOS**, cost Govt. £15. Two comma. D.C., 6-8 volts, 3-5 amps and H.T. 400-600 volt., 100 m.m., 3 1/2in. dia. 12in. long, 17lb., 4,000 revs., ball bearings. Guaranteed 12 months. Sacrificed at 22/6. Carriage 2/6. Charging Dynamos 16/18 volts, 10 amps, slant enclose ball bearings 25/-. Full auto switch-board, 22/6.

MOTORS 220 volts, Small A.C. or D.C., 17/6. Hundreds of splendid Bargains. List "N" FREE.

ELECTRADIX RADIOS, 218, UPPER THAMES STREET, LONDON, E.C.4.

WHEN BUYING A PIPE YOU LOOK AT THE GRAIN

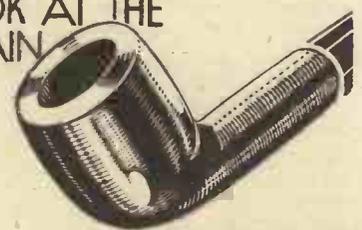


WHEN BUYING A RECEIVER LOOK AT THE VALVEHOLDERS

To enjoy a smoke, a pipe must have a flawless bowl and correctly designed air channels. For continuous enjoyment of radio, you must fit well designed and reliable valveholders—"CLIX."

SPECIFIED FOR THE "ALL PENTODE THREE"

Send for our New 1935 Folder "N." Free

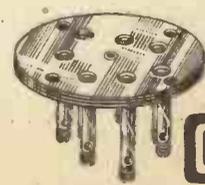

CLIX

LECTRO LINX, LTD.
 79A ROCHESTER ROW LONDON S.W.1

● **H.T. THAT LASTS YEARS** ●
 "14 months" going every day on a 3v. set and still kicks up 80v.—E. K. Reading. Install a Standard Wet Battery. Replenish at long intervals—thats all. All Standard Battery Spares, 120v., 2,500 m.a., £2 complete. CARR. PAID.—Write Wet H.T. Battery Co., 95, Dean Street, London, W.1.

ANNOUNCEMENT

★ to men who want careers in RADIO



In the sign language of the Broadcasting Room this symbol means "Announcement."

The I.C.S. Radio Courses cover every phase of radio work, from the requirements of the youth who wishes to make wireless engineering his career to the man who wants to construct and maintain a broadcasting set for his home.

The Radio industry is progressing with amazing rapidity. Only by knowing thoroughly the basic principles can pace be kept with it. Our instruction includes American broadcasting as well as British wireless practice. It is a modern education, covering every department of the industry.

OUR COURSES

Included in the I.C.S. range are Courses dealing with the Installing of radio sets and, in particular, with their Servicing, which to-day intimately concerns every wireless dealer and his employees. The Operating Course is vital to mastery of operating and transmitting.

There is also a Course for the Wireless Salesman. This, in addition to inculcating the art of salesmanship, provides that knowledge which enables the salesman to hold his own with the most technical of his customers.

Then there are the Preparatory Courses for the City and Guilds and I.W.T. Exams.

We will be pleased to send you details of any or all of these subjects. Just fill in, and post the coupon, or write in any other way.

International Correspondence Schools, Ltd.,
Dept. 94, International Buildings,
Kingsway, London, W.C.2.

Without cost, or obligation, please send me full information about the Courses I have marked X

- COMPLETE RADIO
- RADIO SERVICING
- RADIO EQUIPMENT
- RADIO SERVICING AND SALESMANSHIP
- WIRELESS ENGINEERING
- WIRELESS OPERATORS
- EXAMINATION (state which)

Name Age

Address

PRACTICAL LETTERS FROM READERS

The Editor does not necessarily agree with opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

An Invention Wanted

SIR,—I have read all your issues since No. 1, and have also seen many other wireless journals. I am, however, afraid I have never seen a device described which would suit a scheme which I have for long desired to make up. I have a commercial set, not fitted for an extra loud-speaker. I have connected an ordinary output filter to the set, and have arranged to disconnect the internal speaker when an extra one is in use. I only run one wire to the additional listening point and take a return earth wire from the extra speaker to a convenient earth point. I have tried many volume control devices across this extra speaker, but only with the result that tone of reproduction is spoiled. Is there absolutely no way of controlling the amplification of the set by means of a device situated at a distance, without extra wires running all over the place? I have looked through your wrinkles, but cannot say that I have seen an efficient solution yet. Perhaps one of your readers has met this problem and found a solution; if so, I should be glad to know of it.—R. PULSON (Highbury).

[We have not the advantage of knowing how it is possible to control the amplification of a receiver with only one extension wire, but maybe a reader has found some volume control method which would be suitable for Mr. Pulson.—ED.]

Cost of Maintenance

SIR,—I have had some argument with friends regarding the cost of operation of mains receivers. Is it true that these take more current than a normal lighting circuit? I heard of a case where a listener had purchased a good mains unit from one of your advertisers, but he found that in one week it consumed more current than he normally used for lighting all over the house. What is the normal rating of a set, surely it is not so high as some people make out? It would be a good idea if in future you gave the loading of the mains sets you described as well as certain other details which are of interest to the keen experimenter. The cost is one of the points which every constructor wishes to know before undertaking the building of a set.—T. HARRIS (Pimlico).

[The loading of a good radio-gramophone should not be in excess of 100 watts, and the case you mention rather points to the fact that a defective mains unit was being used. About 60 watts is the average loading of a good mains receiver, although a small set may take only 15 watts. We will bear your other remarks in mind.—ED.]

“Alternative Connections”

SIR,—I notice you have published my letter re alternative connections in the September 22nd issue of PRACTICAL WIRELESS, with your remarks that no mistake was made. May I point out again that there is an error. The article definitely states that Fig. 1 passes the A.C. through the speaker to filament negative, and that Fig. 2 passes the A.C. back through the

H.T. This is exactly the reverse, for how can the A.C. component get to earth but through the resistance of the H.T. battery? Fig. 2 is the one that does this. I have taken the trouble to go through numerous periodicals, and in no one case have I seen Fig. 1 even mentioned, while Fig. 2 is the one shown as the more practical circuit.—H. V. WATLING (Colchester).

[In his previous letter Mr. Watling stated that Figs. 1 and 2 should have been reversed, and with this we agree. If this is done, however, the statements made in the article are quite correct.—ED.]

Short-wave Superhets

SIR,—Since PRACTICAL WIRELESS first came out, you have published circuits and details of sets, and these have been of a very high standard. You have not, however, published full constructional details of a good short-wave set. Why not? The average price of a commercial short-wave set is £20, and I think a great saving can be obtained by the home constructor if you published constructional details of a short-wave set.

In your issue of March 17th, 1934 (No. 78), was published a circuit of a short-wave superhet which had 2 H.F. pentodes, det., pentode output and automatic volume control, which, according to the author, really did function well on the short-wave. With a set of this type results are practically certain, and it would be welcome to the constructor who thinks tuning on the short waves is a fine art: It would also induce many others to try the short wave. Now what about it, “P.W.”? You cannot afford to shelve this question when so many of us, especially British constructors in our colonies, are asking for such a set. When our colonists write, you say “We have the matter in hand,” and then no more is heard from you. If you can design such good sets as the Fury Four Super, etc., then why do you not design a really good super short-wave set on the lines of the above?—E. R. SMITH (Peckham).

[We have published constructional details of short-wave sets, but have so far not found a reliable solution to the problem of designing a superhet to function on all wavebands. When we do we shall, of course, give complete details.—ED.]

NOTICE!

The Editor will be pleased to consider articles of a practical nature suitable for publication in PRACTICAL WIRELESS. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, Geo. Newnes, Ltd., 8-11, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.


Facts and Figures

Components Tested in our Laboratory

BY THE PRACTICAL WIRELESS TECHNICAL STAFF

A New Rola Speaker

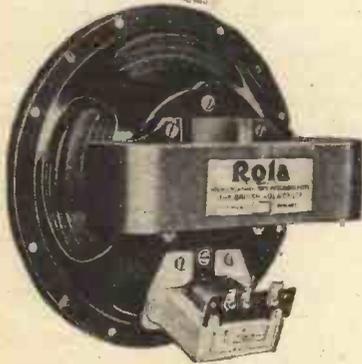THE Rola speakers have been exceedingly popular for some considerable time, and they have many novel features which set them in a class by themselves. With the general improvement which has taken place in the design of loud-speakers during the past year certain modifications have been introduced to the Rola models, and



The Rola FR6-P.M. moving-coil loud-speaker.

one of the latest type is shown in the accompanying illustration. At a first glance there does not appear to be any radical change in construction between this model and some of the older patterns, but a closer inspection reveals that the cone has been remodelled so that one of the principal causes of trouble with moving-coil speakers has been overcome. We refer to the difficulty occasioned by dust in the air gap. Hitherto, the end of the pole-piece could be seen at the apex of the cone, but in these new models a small "blister" appears at the apex. Although of similar material to that employed for the cone, this small addition is exceedingly thin, and it should not be touched with the fingers in view of the possibility of damage. It closes the air gap from the front, but its shape, thickness, and exact position have received very careful attention, and it makes no difference to the high standard of reproduction which is the hall-mark of the Rola speaker. In addition, a special metal-paper-fabric assembly at the rear of the cone serves to protect the gap from the rear, and it is thus impossible for dust or other foreign matter to find its way into this vulnerable part of the speaker. There are other small refinements to be found in the complete speaker, and in performance it gives full proof of the care which has been taken in design. Reproduction has that peculiar brilliancy for which the Rola speakers are famous, speech being remarkably life-like when the speaker is operated from a good receiver. No trace of boominess or artificial resonance can be detected throughout the complete musical scale, but the lowest and the highest notes appear

in all their beauty, with the middle register correctly proportioned at all times. The transformer which is fitted is provided with terminals for power or pentode output circuits and covers a wide range of impedances. The price is 39s. 6d., and the speaker may be obtained with an energized winding, but with all the other characteristics of the permanent magnet, for 35s.

Formo Iron-core Coil

A VERY efficient and neat coil has been produced by the new Formo Company, and our artist's impression of this coil is given on this page. The actual size of the steatite base which is fitted to this coil is 2½in. by 1½in. and the overall height of the coil and screen is only 2½in. A number of novel features are to be found in this coil, the steatite base being only one of them. Hitherto, this type of base has been fitted only to short-wave coils, but the high efficiency of the iron-core coil warrants the inclusion of a base of this nature in order to remove all possibility of losses being introduced, and so nullifying the advantages of the iron-core. As a further aid to the maintenance of efficiency the former of the coil is made from trolitul, a celluloid-like substance which has extremely low losses. Litz wire is employed

for the medium-wave winding, and in every way the losses have been kept down to a minimum, with the result that the coil has a very high standard of performance.

High selectivity, high stage gain, and simplicity of connection are some of the leading features, and it will be found highly desirable when using these coils to take every precaution to keep down losses in the variable condenser and other parts of the tuned circuit in order that full advantage may be taken of these unique properties. The coil is made in three types, T.1—an aerial transformer

without reaction; A.1—an aerial coil with reaction; and P.P.1—an H.F. intervalve coil with reaction. Thus, any type of circuit (except a superheterodyne) may be constructed with the coils, and the price of either type is 5s.

Drydex Price Reductions


AS from September last the price of the Drydex Pen Torch, type 2 PT5, has been reduced to 1s. 6d., including the battery. In addition, a number of new radio batteries are introduced and are now available. These include, amongst others, two 144-volt batteries (one of 141 volts, plus 3 volts grid bias, and one of 135 volts, plus 9 volts grid bias) at 17s.; one 114 volt (108 volts H.T., plus 6 volts G.B.) at 10s. 6d.; one 120 volt at 15s. 6d.; one 24-volt G.B. battery at 2s. 9d.; one 124½ volt (120 volt H.T., plus 4½ volts G.B.) at 14s. 6d.; one 126 volt (120 volt H.T., plus 6 volts G.B.) at 12s.; and a 135 volt (120 volt H.T., plus 15 volts G.B.) at 17s. Although each of these batteries has been designed primarily for a commercial receiver, they will be found extremely useful to the constructor and experimenter, owing to the inclusion of the grid-bias battery, and the removal of the necessity of wondering when to replace this battery. It also ensures that when the H.T. battery is exhausted the grid bias will also be renewed with the removal of the risk of damaging valves due to a discharged G.B. battery.

50 Tested Wireless Circuits

By F. J. CAMM
(Editor of "Practical Wireless")


Obtainable at all Bookstalls or by post
2/9 from Geo. Newnes, Ltd., 8-11,
Southampton St., Strand, London, W.C.2

2/6

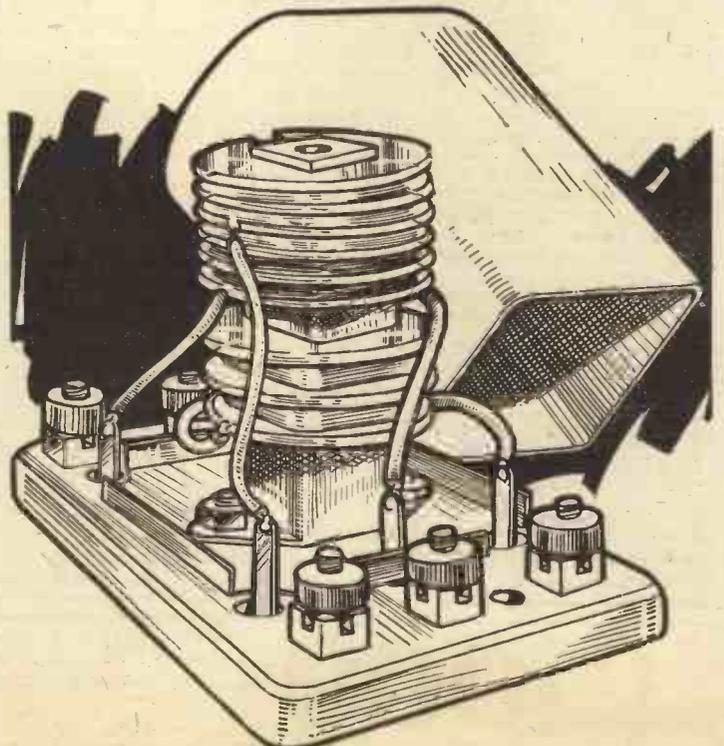

The novel iron-core coil produced by Formo. This illustration is nearly double the size of the actual coil.

REPLIES TO

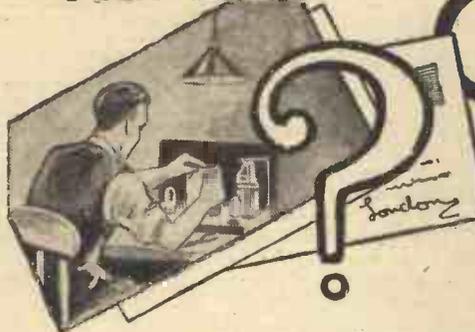LET OUR TECHNICAL STAFF SOLVE
YOUR PROBLEMSQUERIES and
ENQUIRIESThe coupon on Page
145 must be attached
to every query

by Our Technical Staff

If a postal reply is desired, a stamped addressed envelope must be enclosed. Every query and drawing which is sent must bear the name and address of the sender. Send your queries to the Editor, PRACTICAL WIRELESS, Geo. Newnes, Ltd., 8-11, Southampton St., Strand, London, W.C.2.

SPECIAL NOTE

We wish to draw the reader's attention to the fact that the Queries Service is intended only for the solution of problems or difficulties arising from the construction of receivers described in our pages, from articles appearing in our pages, or on general wireless matters. We regret that we cannot, for obvious reasons—

- (1) Supply circuit diagrams of complete multi-valve receivers.
- (2) Suggest alterations or modifications of receivers described in our contemporaries.
- (3) Suggest alterations or modifications to commercial receivers.
- (4) Answer queries over the telephone.

Please note also that all sketches and drawings which are sent to us should bear the name and address of the sender.

Special Gang Condensers

"In a wireless publication reference is made to ganged condensers in which the different sets of moving vanes can be separately adjusted. Please let me have the name of some reliable firms making condensers of this type."—Dr. W. R. T. (Broadstairs).

So far as we can ascertain, this type of condenser is not now manufactured. If, however, this query meets the eye of any firm who does market such a condenser, and they will communicate with us, we shall be pleased to mention the fact in our pages.

Two-valve Mains Receiver

"May I inquire if you have had, or will have in the near future, a design of the following nature? Two-valve for A.C. mains; output about 3 watts. A few stations with perfect reproduction rather than a host of programmes at very indifferent quality. Overall dimensions as small as possible and cost kept as low as possible."—E. A. R. (Leicester).

The nearest we have to your requirements is the A.C.-D.C. Two, described in PRACTICAL WIRELESS No. 30 and obtainable in blue-print form—Blue Print No. 31. This is designed primarily for universal operation on any type of mains, and gives really high quality with low cost of construction. In addition, it is very compact, and contains a loud-speaker in its cabinet, which measures 17in. high, 11in. wide, and 9in. deep.

A Magnet Problem

"Is it possible to pass an electric current through an energized magnet without any effect on its magnetic qualities?—H. B. O. (Hove).

We are afraid your query is not quite clear to us. What do you refer to as an "energized magnet"? Do you mean an electro-magnet with an energizing winding? If so, it is, of course, necessary to pass a current through the winding in order to magnetize the core. However, if you will repeat your query and give fuller details, we shall be pleased to assist you.

Detector Merits

"I am building a receiver, but am rather uncertain regarding the type of detector to employ. I can choose between crystal, Westector, diode, anode-bend, grid leak, etc., but cannot decide which to adopt. Can you help me when I tell you that I require only a few stations with really high quality? I am going to use a paraphase amplifier after the detector."—T. G. (Balham).

The diode will no doubt prove most suitable for you, although an anode-bend rectifier will serve if only powerful stations are received. Personally we should prefer a modern double-diode-triode, so that you may obtain the advantage of the triode portion of that valve with the good rectification properties of the diode.

Manufacturer's Name Wanted

"I should be glad if you could give me the address of the makers of the Brown screen-grid D.C. mains set. I have one to repair and should like to get the circuit."—P. J. S. (Belfast).

The receiver was made by S. G. Brown, Ltd., Victoria Road, Acton, London, W.3, but this firm no longer manufactures wireless receivers. However, they may be able to assist you concerning the circuit details of the receiver in question.

Wearite Products

"I am anxious to get into touch with the makers of a Wearite transformer which I have got, but I cannot find their name in

the London 'phone directory. Could you please let me know their address?"—W. T. (Bloemfontein).

The makers of Wearite components are Messrs. Wright and Weaire, Ltd., 140, High Road, Tottenham, London, N.17. Their advertisements have appeared in our pages on many occasions.

A Droitwich Problem

"I have heard a lot about the new Droitwich station, but I cannot hear it on my set. I have tried several nights when they have supposed to be on, but have only been able to hear Daventry. Can you tell me exactly at what point on the dial I shall hear the station, or is it possible that I am not in the direct range?"—G. T. (Bournemouth).

Droitwich transmits on exactly the same wavelength as Daventry, and at present takes the place of the latter station during the period of transmission. Eventually it will take over completely the present Daventry transmissions. You should adjust your set to the Daventry setting, and you will probably notice that the only difference when Droitwich is transmitting is the increased signal strength. No adjustment of tuning should be necessary.

A Charging Point

"I am building a small charging point, but wish to insert some form of safety device to prevent damage due to the charging current falling below that of the cells on charge. I believe it is possible to fit a kind of automatic cut-out, and should be glad of details."—H. F. T. (Hull).

A small magnet with an armature arranged in the electrical circuit will prove suitable. The strength of the magnet, the weight of the armature, and other details will depend upon the particular charging scheme which you are adopting. A low-priced cut-out may be obtained from Messrs. Ward and Goldstone for 17s. 6d., suitable for 1, 2, 4, and 8 amps. Larger values are obtainable at proportional prices.

THE QUERIES COUPON APPEARS
ON PAGE 145

£1000
FREE
INSURANCE

SAVE THE SET!

Thunder... fierce lightning... no need to switch off the set! Don't worry—with a Pix Arrestor you are dead safe and covered by £1,000 insurance. Practical Wireless says: "Signals are unaffected by this connection, but a powerful static discharge will pass through the lower resistance circuit to earth." A moment's job to fix. Pix, London, S.E.1.

LIGHTNING IS DANGEROUS

INCLUDING
FREE 1/-Lightning
Insurance

Miscellaneous Advertisements

Advertisements are accepted for these columns at the rate of 3d. per word. Words in black face type and/or capitals are charged double this rate (minimum charge 3/- per paragraph). Display lines are charged at 6/- per line. All advertisements must be prepaid. Radio components advertised at below list price do not carry manufacturers' guarantee. All communications should be addressed to the Advertising Manager, "Practical Wireless," 8, Southampton Street, Strand, London.

PREMIER SUPPLY STORES

Offer the Following Manufacturers' Surplus New Goods at a Fraction of the Original Cost; all goods guaranteed perfect, carriage paid over 5/-, under 5/- postage 6d. extra, I.F.S. and abroad, carriage extra. Orders under 5/- cannot be sent C.O.D. PLEASE SEND FOR ILLUSTRATED CATALOGUE POST FREE.

STOPENDOUS Purchase of Set Manufacturers' Stock. All electric 3 Valve (S.G. Det. Pen.) Set in Walnut Cabinet with moving-coil speaker 200-250 volt 40-60 cycles. Chassis built. 200-2,000 metres with 4 valves, £4/19/6.

ALL Electric 3-stage Amplifiers, 200-250v., 40-60 cycles, 10 watts, undistorted output, complete with 5 valves, £7/7/-. Suitable speakers, pick-ups and microphones can be supplied.

TYPE 4480, 9in. diameter, permanent magnet, 4 watts, 7 ohms speech coil, 13/6. Multi-ratio transformer, 4/6 extra.

PREMIER SUPPLY STORES announce the Purchase of the Complete Stock of a World Famous Continental Valve Manufacturer; all the following standard mains types, fully guaranteed, 4/6 each, H.L., power, High, Medium, Low, magnification, Screen Grid. Directly heated Pentodes, 1 watt, 3 watt and 4 watt A.C. outputs.

THE following Type, 5/6 each; 350 v. and 500 v., 120 milliamper full wave rectifiers, 2 1/2 watt indirectly heated pentode.

THE following American Types at 4/6; 250, 227, 112, 171, 210, 245, 26, 47, 24, 35, 58, 55, 37, 80 and the following types, 6/6 each: 42, 77, 78, 25Z5, 36, 38, 83, 39, 44, 53, 6B7, 2A5, 2A6, 2A7, 2B7, 5Z3, 6C6, 6A4, 6D6, 6E7.

ELIMINATOR Kits, including transformer, choke, Westinghouse metal rectifier. Condensers, resistances and diagram, 120v., 20 m.a., 20/-; trickle charger, 8/- extra; 150v., 30 milliamper, with 4v., 2-4 amps. C.T., L.T., 25/-; trickle charger, 6/6 extra; 250v., 60 milliamper with 4v., 3-5 amps. C.T., L.T., 30/-; 300 v. 60 m.a. with 4 volts, 3-5 amps., 37/6; 200v. 60 m.a. with 4v. 3-5 amps. L.T., 27/6.

PREMIER chokes, 40 milliamper, 25 hys., 4/-; 65 milliamper, 30 hys., 5/6; 150 milliamper, 30 hys., 10/6; 60 milliamper, 80 hys., 2,500 ohms, 5/6; 25 milliamper, 20 hys., 2/9.

ALL Premier Guaranteed Mains Transformers have Engraved Terminal Strips, with terminal connections, input 200-250v., 40-100 cycles, all windings paper interleaved.

PREMIER H.T.7 Transformer, output 135v. 80 m.a. for voltage doubling, 8/6; 4v. 3-4a., C.T. L.T., 2/- extra; with Westinghouse rectifier giving 200 v. 20 m.a., 17/6.

PREMIER H.T.8 and 9 Transformers, 250v., 60 m.a. and 300 v. 60 m.a. rectified, with 4v. 3-5a. and 4v. 1-2a., C.T. L.T. and screened primary, 10/- with Westinghouse rectifier, 18/6.

PREMIER H.T.10 Transformer, 200v. 100 m.a. rectified with 4v. 3-5a., and 4v. 1-2a., C.T. L.T. and screened primary, 10/-; with Westinghouse rectifier, 19/6.

PREMIER Mains Transformer, output 250-0-250v. 60 m.a., 4v. 3-5a., 4v. 2-3a., 4v. 1-2a. (all C.T.) with screened primary, 10/-.

PREMIER Mains Transformers, output 350-0-350v. 90 m.a., 4v. 3-5a., 4v. 2-3a., 4v. 1-2a. (all C.T.) with screened primary, 10/-.

PREMIER Auto Transformers, 100-110/200-250v. or vice versa, 100-watt, 10/-.

WESTERN ELECTRIC Mains Transformers, 300-0-300v. 65 m.a., 4v. 1-2a., 4v. 2-3a., 6/6; 500-0-500v., 150 m.a., 4v. 3-5a., 4v. 2-3a., 4v. 2-3a., 4v. 1a. C.T., 4v. 1a. C.T., 19/6.

SPECIAL Offer of Mains Transformers, manufactured by Phillips, input 100-200v. or 200-250v. output 180-0-180 volts 40 m.a., 4v. 1 amp., 4v. 3 amps., 4/6; 200-0-200v., 4v. 1a., 4v. 3a., 4/6.

PREMIER L.T. Charger Kits, consisting of Premier transformer and Westinghouse rectifier, input 200-250v., A.C. output 8v. 1/2 amp., 14/6; 8v. 1 amp., 17/6; 6v. 2 amp., 27/6; 30v. 1 amp., 37/6; 2v. 1/2 amp., 11/-.

B.T.H. Trusped Induction Type (A.C. only) Electric Gramophone Motors. 100-250v.; 30/- complete.

COLLARO Gramo. Unit consisting of A.C. motor. 200-250v. high quality pick-up and volume control, 49/-; without volume control 46/-.

SPECIAL Offer of Wire Wound Resistances, 4 watts, any value up to 50,000 ohms, 1/-; 8 watts, any value up to 15,000 ohms, 1/6; 15 watts, any value up to 50,000 ohms, 2/-; 25 watts, any value up to 50,000 ohms, 2/6.

CENTRALAB Potentiometers, 50,000, 100,000 1/2 meg. any value, 2/- 200 ohms, wire wound, 1/-.

(Continued at top of column three)

Easy Terms

Why wait weeks for that new Radio accessory? You'll get it quicker from N.T.S. Any items advertised in this journal on Easy Terms. Strict Privacy Guaranteed. Cash or C.O.D. if preferred. Orders over 10/- carriage and C.O.D. Charges paid. SEND FOR QUOTATIONS FOR ANYTHING IN RADIO YOU ARE NEEDING.

WESTENTORIAN SENIOR

SENT ON 7 DAYS' TRIAL

Type PMS1. For Power, Pentode and Class B. Send only 2/6 for 7 days' trial. If approved, balance in 11 monthly payments of 4/-. Cash or C.O.D. Carriage Paid, £2/2/6.




W.B. Stentorian Standard. Cash in 7 days, £1/12/6, or 2/6 deposit and 11 monthly payments of 3/-.

ROLA CLASS 'B' SPEAKER-AMPLIFIER


SENT ON 7 DAYS' TRIAL

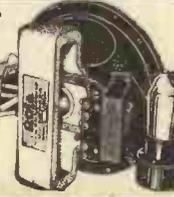Complete Class B Amplifying Unit, with Valve and Rola P.M. Moving-coil Speaker. Send only 5/- for 7 days' trial. If approved, balance in 11 monthly payments of 8/3. Cash or C.O.D. Carriage Paid, £3/6/6.




LISSEN BAND-PASS SKYSCRAPER 3 KIT

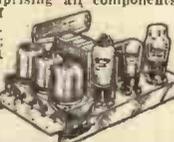Complete Kit for building, comprising all components, including set of Lissen valves. Send only 9/-; balance in 11 monthly payments of 9/3. Cash or C.O.D. Carriage Paid, £4/19/6.



TELSEN S G 3 KIT

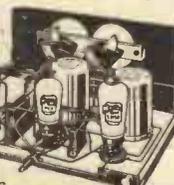Complete kit of parts for building, lens valves. Send only 2/6. Balance in 8 monthly payments of 5/-. Cash or C.O.D. Carriage Paid, £1/19/6. Kit with Valves, Cash Price, £3/11s. 5/- deposit & 11 monthly payments of 6/6.



ATLAS ELIMINATOR

Send for it on 7 DAYS' FREE TRIAL

Model C.A.25. Suitable for all outputs, including Class "B" and Q.E.P. Send only 5/- for 7 days' trial. If approved, Balance payable in 11 monthly payments of 5/6 (or cash in 7 D.O. Model 15/25B. Cash 4/5/6, or C.O.D. Carriage Paid £2/19/6. £1/19/6, or 2/6 down and Carriage 10 monthly payments of 4/3. Paid.



Model C.A.12. Send 5/- only for 7 days' trial; if approved, balance in 10 monthly payments of 5/3. Cash or C.O.D. Carriage Paid, £2/12/6.

SEND FOR LATEST LIST

New Times Sales Co

56, LUDGATE HILL, LONDON, E.C.4. Dear Sirs,

(a) Please send me..... (b) I enclose Cash/Deposit..... NAME..... ADDRESS.....

Pr. W. 13/10/34

FIRST WITH EASY TERMS IN 1924

(Continued from foot of column one)

EDISON Bell Double Spring Gramophone Motors, complete with turn-table and all fittings, a really sound job, 15/-.

WIRE Wound Potentiometers 1,000, 2,500, 50,000, 90,000, 150,000, 200,000, 500,000, any value 2/- each; 1,000 ohms wire-wound semi-variable resistances, carry 150 m.a. 2/-.

POLAR Star, manufacturers' model, 3-gang condensers, fully screened, 7/6; with trimmers.

AMERICAN Triple Gang 0.0005 Condensers, with trimmers, 4/11; Utility Bakelite 2-gang 0.0005 screened with unknob trimmer, 3/6; Polar Bakelite condensers, 0.00035, 0.0003, 0.0005, 1/-.

BRITISH Radiophone 110 kc/s Intermediates, 3/-; Cosmocord Pick-ups, with arm and volume control, 12/-.

MAGNAVOX D.C. 152, 2,500 ohms, 17/6; D.C. 154, 2,500 ohms, 12/6; D.C. 152 magna, 2,500 ohms, 37/6, all complete with humbucking coils; please state whether power or Pentode required; A.C. conversion kit for above types, 10/-; Magnavox P.M. 7in. cone, 18/6.

RELIABLE Canned Coils with Circuit accurately matched, dual range, iron-cored, 3/6.

RELIABLE Intervalve Transformers, 2/-; multi-ratio output transformers, 4/6.

C.C. Electrolytic Condensers, 550v. working, 650v. peak, 8 mf., 4/-; 4 mf. or 8 mf. 440v. working, 3/-; 15 mf. 50v. working, 1/-; 25v. working, 25 mf., 1/3; 6 mf. 50v. working and 2 mf. 100v. working, 6d.; 8+4 mf., 450v. working, 4/-; 50 mf., 50v. working, 2/9.

C.C. Condensers, 250v. working, 1mf., 1/3; 2 mf., 1/9; 4 mf., 3/-; 4 mf., 450v. working, 4/-; 4 mf., 750v. working, 6/-.

WESTERN ELECTRIC Condensers, 250v. working, 1 mf., 1/-; 2 mf., 2/6; 4 mf. 2/- 400v. working, 1 mf., 1/-; 2 mf., 1/6.

M.V. Condensers, 400v. working, 4+4+1+1+1+1+1+0+1+0+1+0+1-0.1, 4/9; 4+2+1+1+1+1+1+0+5, 3/9.

DUBILIER Condensers, 8 or 4 mfd. dry electrolytic 450v. working, 3/-.

VARLEY Constant Square Peak Coils, band-pass type BP7, brand new in maker's cartons with instructions and diagrams, 2/4.

VARLEY H.F. Intervalve Coils BP8 band-pass complete with instructions in original cartons, 2/6.

SCREENED H.F. Chokes by One of the Largest Manufacturers in the Country, 1/6.

PREMIER British-made Meters, moving iron flush mounting, accurate, 0-10, 0-15, 0-50, 0-100, 0-250 m.a., 0-1, 0-5 amps. all at 6/-.

LARGE Selection of Pedestal, table and radio-gram cabinets, by best manufacturers, at a fraction of original cost, for callers.

THE Following Lines 6d. each, or 5/- per dozen.—Chassis valve holders, 5-, 6-, or 7-pin, screened screengrid leads, any value 1-watt wire end resistances, wire end condensers, 0.0001 to 0.1 Bulgis 3-amp. main switches. Cydon capacitors, double trimmers.

PREMIER SUPPLY STORES

20-22, High St., Clapham, S.W.4. Telephone: Macaulay 2188. Nearest Station, Clapham North Underground.

EAST ANGLIAN SUPPLIES, for genuine manufacturers' surplus by makers of repute, new goods, satisfaction assured, by return. Over 5/-, carr. paid.

ELECTROLYTICS, 450v. working, 8 mfd., 3/-, 4s., 2/9; 8+4+4, 4/9; 25v. 25 mfd., 1/2. Tubulars, up to .1, 4/6 doz. .0003 reaction, with knob, 1/2.

COILS.—Colvern T.D. (list 8/6), 4/6; others, manf. C type, 1/4, 2/-. Chokes, H.F., 3d., screened, 1/6; L.F., 30 hv. 60 ma., 4/9; 30 ma., 3/3. Vol/controls, 10,000 ohm, graded, switch and knob, 3/-; 25,000, 50,000, no switch, 2/4.

25 MA. ELIMINATORS, 200-250 input, D.C., 10/6; A.C., 21/- Post free. 4 tappings, guaranteed.

L.F. TRANSFORMERS, 3:1, 5:1, 2:1; "B" drivers, 4/3; Mains, 325-0-325, 4v. 2a., 4v. 4a., C.T. screened primary, 12/6.

HEAVY sheet aluminium for chassis, any size, 2/- sq. foot. Interference suppressors, recommended by G.P.O., very efficient, 3/6.

HUNDREDS of lines. Ask for quotation for H.F. speakers, chassis, gangs, kits, cabinets, anything. The firm you can rely on.—East Anglian Supplies, 23, Hampton Rd., Ipswich.

REPAIRS.—REWINDING. Any component, mains transformers, etc., rewound. New cones/coils fitted any speaker. Guaranteed, quick service.—Write Dept. C. WEEDON P.L.R. Co., 80, Lonsdale Avenue, London, E.6.

VARLEY Constant Square Peak Band-Pass Coils, type B.P.5. Complete, all accessories and instructions. New, boxed, 2/4. (List, 15/-)

ERICSSON 3-1 L.F. Transformers, new and guaranteed, 2/3. (List, 17/6)

VOLUME Controls, 50,000 ohms, New, 1/3.

CELESTON Energised M.C. Speaker, 2,500 ohms. Model D.C. 2054, with universal transformer. List price, £2/5/0. Our price, 12/6.

PIONEER RADIO CO., LTD., Coptic Street, London, W.C.1. Museum 9607.

CONSTRUCTORS of coils, chokes, transformers. Send for 1934-35 lists.—Lumen Electric Coy., 9, Scarsbrick Ave., Liverpool 21.

SOUTHERN RADIO'S Bargains.—Set manufacturers' guaranteed surplus.
VARIABLE Condensers.—Lotus 3-gang 0.0005, 12/6; Lotus 2-gang, 0.0005, 8/6; Lotus Dyblock single, 0.0005, 4/9 (list 9/6); all these condensers are complete with dials, escutcheons, knobs, fully screened with trimmers, and boxed; Hydra block condensers, 16 mfd. (2+2+8+2+1+1), 1,000 v. D.C., 7/- each; Dubilier 4 mfd. (2+1+1), 1,000 v. D.C., 2/9; 4.5 mfd. (2.25+2.25), 1,000 v., for mains noise suppression, 3/-; fixed 4 mfd., 2/3; 2 mfd., 1/6; 1 mfd., 1/-; Utility Midget 2-gang variable condensers, 0.0005, with concentric trimmers, 3/5; T.C.C. 0.1+0.1, 1/3 each.
SPEAKERS.—Blue Spot permanent magnet, with universal transformer for power, super power, pentode and Class B; 23/- (list 39/6).
E.C. Stork Speaker in Cabinet; 19/6 (list £3/15).

T.400 Kits, all specified proprietary components; (£2/19/6 (list £4/17/6)).
REGENTONE A.C. Eliminators. Type W5A, combined with trickle charger. 20 milliamps. Brand new and sealed, 39/6 (list £4/12/6).
IGRANIC Superhet Coils, set of 4 (1 Osc., 2 I.F., with pig tails, a L.F. plain); 12/6 (list 50/-).
ISSEN Superhet 3 Coils Kit, screened, ganged on base with wave change and filament switches; type L.N.5181, for battery or mains; 12/6 (list 30/-).
VARLEY Constant Square Peak Coils, complete with all accessories, new, boxed, B.P.5; 2/4.
VARLEY H.F. Inter-valve Coils B.P.6; 2/3.

FRAME Aerials.—Lewcos dual wave superhet, 9/- each (list 27/6).
PICK-UPS.—Marconi No. 19 (1934), 22/6 each (list 32/6).
READY Radio Instant Transformers, for matching any valve to speaker; Junior model, ratios 1 : 2, 1 : 1, 14 : 1, 2 : 1, 3 : 1, 7/6 (list 27/6); Senior model, ratios 10 : 1, 12 1/2 : 1, 14 : 1, 16 : 1, 20 : 1, 25 : 1, 12/6 (list 37/6).

RECREIVERS.—Lissen 2-valve A.C. sets. Universal Model, type L.N.8014, 100/250 volts. Complete with valves and speaker in attractive bakelite cabinet, £2/19/6 each (list £6/6/0). D.C. models, L.N.8012, 200/250 volts as above, £2/19/6.

BOTOLPH Light weight Portable Receivers, complete with 5 Mullard valves, Exide batteries and accumulator, overall size 13in. x 11in. x 8in., £2/19/6 (list £8/8); a real suitcase portable.

MULLARD Radio for the Million, "Station Master Three" battery kits, complete with cabinet and 3 Mullard valves (screen grid, H.L., power), brand new in original sealed cartons; £2/19/6 complete.

MISCELLANEOUS.—Westinghouse metal rectifiers, H.T. 6, 7, 8, 9/3 each; Ferranti chokes, 20 henry 60 m.a., 6/9 each; Lewcos superhet, 8-way bases, complete with valve holders, grid leak, fixed condenser type "48", 2/- each; Lissen base turntables, 1/6 (list 5/-); Lewcos coils, H.P.F./R., 4/-; T.B.F./C., 3/3; O.S.C./126 (Extensor), 3/3; T.O.S./E., 3/3; Morse tapping keys, with buzzer and flashlight signals, complete with battery and bulb, 2/- each.

LISSEN General Purpose Output Chokes 28 Henrys, 20 M.A. and 18 Henrys, 60 M.A. type L.N.5301, 6/- each (list 12/6).

IGRANIC Resistance-fed Transformer Units, 4/6 each (list 10/6).

BRAND New American Valves. All Types Available. Please Ask for Quotations.
ALL Goods Guaranteed and Sent Carriage Paid.

BRANCHES at 271-275, High Rd., Willesden Green, N.W. 10, and at 49, Lisle St., W.C.2. Please send all post orders to 323, Euston Rd., N.W.1.

SOUTHERN RADIO, 323, Euston Rd., London, S.W.1 (near Warren St. Tube). 'Phone: Museum 6324.

VAUXHALL.—Magnavox Permanent Magnet Loudspeakers, universal, suitable for Class B power or pentode; 7in. cone, 17/6; 10in. cone, 23/-; Energised 2,500 or 6,500, 10in. cone, 22/-; 7in. cone, 15/3. All new with humbucking coils.

VAUXHALL.—U.S.A. Rola Energised 8in. diameter, 2,500, 6,500 ohms, 17/6; 10in. diameter, 25/-; P.M. 8in. diameter, 28/-; 10in. diameter, 33/-.

VAUXHALL.—Radiophone Radiopaks, Band-pass or R.F. superhet, with Lucerne wavelength station-named scales, medium and long, complete, 32/6.

VAUXHALL.—Radiophone I.F. transformers, with terminals, 0/-; Radiophone volume controls, with switch, 3/6.

VAUXHALL.—Coils, set of three on base with switch, 10/6. Three-gang condensers, with covers—superhet, 14/6; ordinary type, 12/6. Disc drives, complete, 4/9.

VAUXHALL.—Pickups, 8/-—£2. Write for quotation. State make, B.T.H. Collaro Motors, 32/6. Gramophone switches, 3/6.

VAUXHALL.—Westinghouse Rectifiers, H.T.8., 9/6; H.T.9., 10/-; Westectors', W4, WX0, 5/9.

CASH with Order, post paid over 2/6, or c.o.d.; all goods unused manufacturers' surplus; guaranteed perfect. Lists free.

VAUXHALL UTILITIES, 163a, Strand, W.C.2. 'Phone: Temple Bar 9338. (Facing Bush House, over Denny's.)

ALL goods advertised in last week's issue still available.

WARD, 2nd floor, 45, Farringdon Street, London, E.C.4. Telephone: Holborn 9703.



150 volts at 15-50 ma.

When buying a Mains Unit, be sure you get the products of SPECIALISTS. Heyberd have specialised in Mains Apparatus for over a decade, and have recently marketed a remarkable mains unit.

1. Voltage regulation practically constant at 150 volts throughout the whole range of current.
2. Suitable for any set and specially suitable for Class "B" working.
3. Absolutely free from all hum and background.
4. GUARANTEED THREE YEARS.

These are some of the remarkable features of the New Heyberd Mains Unit—Model 15/50.

MODEL 15/50—Output 150 volts at 15-50 ma. H.T.1 Variable 40-110 v. H.T.2 Variable 60-130 v. H.T.3 Fixed 150v. Employs Westinghouse Metal Rectification. PRICE 88/6

Post Coupon

for Heyberd handbook on Mains Working

I enclose 3d. stamps for New Handbook of Mains Equipment. Packed with Technical Tips, Service Hints and diagrams

Mr. _____

Address _____

PRA.

F.C. HEYBERD & Co.,
 10 FINSBURY STREET, LONDON, E.C.2
 One minute from Moorgate Stn

WOBURN RADIO OFFER FOLLOWING MANUFACTURERS' SURPLUS:

UTILITY CONDENSERS, air spaced, 0005 with dial and escutcheon, 3/6. Merzhom Electrolytics, 8mfd., 600v., 2/9. Dubilier 2mfd., 1000v. test, 1/3. Wego, 750v. test, 1 mfd. 1/-, 2mfd. 1/2, 4mfd. 2/3. Popular iron core cored coils, 2/6. Eston iron core coils, 2/6. H.F. Chokes, 10d. Binocular, 1/2. S.W. Chokes, 10d. Tubular Condensers: 0.1, 0.01 and 0.02, 6d. Toggles, 6d. Polymet 0001 tag condensers, 1/3 half doz. Edison 002, 005, 006, 3d. Chassis mounting valve holder 4/5 pin, 1/3 half doz. Igranit tubulars 001, 4d. Class B Drivers and Chokes, 8/6 pair, with B.V.A. Valve and 7 pin holder, 17/-; Rothermel wire wound resistances with switch, 10,000, 25,000 and 50,000, 3/6. Astra differentials 0002, 1/2. Polar 00035 mica reactions, 1/2. Columbia L.F. Transformers, 3/1 and 5/1, 3/-. Westinghouse Rectifiers. H.T. 5, 6, 4/6. Eston Morse Keys, with code, 3/6. Lissen Output Transformers, 23/1, 3/6. Western Electric microphones, very sensitive, boxed, 2/3. Microphone transformers 85/1, 2/3. Marconi transformers, Push-Pull, 4/-. Microphone transformers (Ideal), ratio 100/1, 3/6. Sistoflex 7 yds., 6d.; screened flex, 3d. yd. Ormond twin gang 0005 condensers mica dielectric, with trimmer, and disc drive and escutcheon, 3/9. British Radiophone straight line dials with escutcheon and twin dial lights, 3/9.

RESISTANCES: Bargain parcels of 13 wire wound 1 1/2 watt, resistances accurate 1% values 100 ohms to 50,000, at 3/9 each, postage 2d.

WR.C. Eliminators: 150v. 30 m.a. Three positive H.T. Tappings. Guaranteed 12 months. A.C. Model with Trickle Charger (2v. 4v. 6v. 1 amp.), 32/6. A.C. Model, 21/-. Universal A.C./D.C. Model, 21/-. D.C. Model, 9/6. (Carriage extra 1/- on each).

NEW Trade List now ready, enclose heading and stamp.

WOBURN RADIO CO., 9, Sandland Street, Bedford Row, W.C.1. Holborn 7289.

RADIO CLEARANCE, 94, High Holborn, W.C.1, offers the following stupendous bargains; limited quantities only; all goods carriage free.—'Phone: Holborn 4631.

RADIO CLEARANCE Offers Plessey Triple Gang Condensers, 2x0.0005 and 110 K/c oscillator section, complete with knob, drive and escutcheon; 7/6 post free.

RADIO CLEARANCE Offers Plessey 110 K/cs Intermediate Frequency Transformers: 3/-, post free.

RADIO CLEARANCE Offers 8,000 ohm Volume Controls, log. type, with Q.M.B. switch, by G.E.C.; 2/6 post free.

RADIO CLEARANCE Offers Mains Transformers, unshrouded, manufacturer type, primary 200-250, secondary 320-0-320v. at 70 m.a., 2-0-2v. at 2 1/2 amps., 2-0-2v. at 3 amps.; 8/6 post free.

RADIO CLEARANCE Offers Mains Transformers, shrouded, with terminals, primary 200-250v., secondary 320-0-320v. at 70 m.a., 2-0-2 at 2 1/2a., 2-0-2 at 4 1/2a., 9/6, post free.

RADIO CLEARANCE Offers Mains Transformers, shrouded, with terminals, primary 200-250v., secondaries 320-0-320 at 70 m.a., 2-0-2 at 2 1/2a., 2-0-2 at 6 1/2a., 10/6 post free.

RADIO CLEARANCE Offers Steel Chassis cadmium plated, drilled ready for use, 3-valve, 5-valve, or 7-valve type; 1/6 post free.

RADIO CLEARANCE Offers Set of Band-Pass Coils, manufacturer's type, with circuit diagram, suitable for tuned grid or tuned anode; set of 3 coils. 4/6, post free.

RADIO CLEARANCE Offers "Central" Potentiometers, 25,000, 50,000 ohms; 1/6 each, post free.

RADIO CLEARANCE Offers Set of Super-Het. Coils, comprising Band-Pass and oscillator 110 K/cs for cathode injection with circuit diagram; 4/6, post free.

RADIO CLEARANCE Offers Parallel Feed Transformers, ratio 6-1, by well-known manufacturer, 3/-.

RADIO CLEARANCE Offers T.C.C. Condensers 0.5 mfd., 800-volt, D.C. working, 2/- each; T.C.C. condenser, 1 mfd., 250-volt, D.C. working, 1/- each; T.C.C. condensers, 1 mfd., 450-volt, D.C. working, 1/3 each; T.C.C. condensers, 1 mfd., 800-volt, D.C. working, 3/- each; T.C.C. condensers, 2 mfd., 450-volt, D.C. working, 2/- each; T.C.C. condensers, 4 mfd., 450-volt, D.C. working, 3/- each; T.C.C. condensers, 4 mfd., 500-volt, D.C. working, 3/6 each; T.C.C. condensers, 6 mfd., 250-volt, D.C. working, 3/- each; T.C.C. condensers, 4 mfd. block, 0.5, 0.5, 0.5, 0.5, 0.5 0.5, and 1 mfd., 250-volt, A.C. working, 2/- each.

RADIO CLEARANCE Offers Phillips Eliminator Transformers, 150 volts at 30 milliamps, 4 volts, 1 amp., various inputs, 1/6; Phillips smoothing chokes, 14-28 henries, 120 milliamps, 2/-.

RADIO CLEARANCE Offers 5-valve A.C. 200-250 volts Super-Het. Chassis, partly incomplete, with circuit diagram. Components worth 50/-. Price, post free, 25/-.

RADIO CLEARANCE Offers L.F. Transformers, 3:1 and 5:1, manufacturers type, 1/6 each, post free.

RADIO CLEARANCE Offers L.F. Transformers (shrouded), 3:1 and 5:1, Price, post free, 1/9 each.

RADIO CLEARANCE Offers Magnacore Class B Chokes. Price, 2/11, post free.

RADIO CLEARANCE Offers Magnacore Q.P.P. Choke. Price, post free, 2/11 each.

RADIO CLEARANCE Offers 1/25th h.p. Motors (Gilbert), 100-115 volts A.C., for Television. Suitable for 200-250 volts if used with 700 ohm resistor or 80 watt lamp. Price 17/6 each, post free.

RADIO CLEARANCE Offers Variable Power Resistances by well known maker, 0-100 ohms. Price 3/- each, post free. Exceptional value.

RADIALADDIN (Disposals) Ltd. Exchange your old set for any new model, balance cash or H.P. Write for free quotation to largest radio exchange in U.K. Also clearance sale of reconditioned sets and radiograms at gift prices £1 to £10. Write for list.—46, Brewer Street, Piccadilly Circus, W.1. Gerrard 4055.

WANTED good modern wireless parts, sets, eliminators, meters, valves, speakers, etc. Spot cash waiting. Exchanges, send or ring. We pay more than any other dealer. Open 9-8.—University Radio, 142, Drummond St., Euston, N.W.1.

HIGHEST possible allowance made on used wireless goods in exchange for new sets, components, or Peto-Scott kits. All latest receivers supplied on easiest of terms.—R. Wigfield, Furlong Road, Goldthorpe, Yorks.

ELIMINATORS, 25 m.a., D.C. 10/-, A.C. 21/-, Transformers, 3-1, 5-1, 1/0. British-made valves H.F., L.F., and Dect., 1/9. Power 2/-, S.G. 5/-, Carriage Paid Cash with Order.—Radio Electrical Supplies, 237, Camberwell Road, London, S.E.5.

ALL 35/- Pentode Three. Solely Specified Kit, £3.15.6 Cash (7/7 monthly). Television Disc Receiver Kit, complete with full instructions, Receivers, Kits, Components. Lowest Prices Cash or H.P. Lists Free.—"Melfo-Rad," Queen's Place, Hove.

SURPLUS RADIO SNIPS!

At the "GOLD-MINE" STORES, of London.

Listed supplementary to the "RADIO-GOLD-MINE," now available. Enclose 3d. stamps for COPY TO-DAY, the greatest surplus lists in Radio.

- 79/6 GRAMPLION A.C. SUPERHET CHASSIS, with A.V.C. double-diode-triode; 18 only. Worth 8 gns.
- 69/6 BRITISH RADIOPHONE, 5-VALVE A.C. SUPERHET KITS. Amazing limited offer. Complete with cadmium plated chassis, diagrams, etc.
- 22/6 CL.B. III SEALED KITS. An unprecedented bargain.
- 18/6 S.G. III KITS. Complete in sealed cartons. Full diagrams.
- 17/6 A.C. ELIMINATOR KITS, 25 ma. State mains voltage.
- 12/6 SHORT-WAVE III VALVE KITS. Will tune in the world.
- 10/6 WEARITE MAINS TRANSFORMERS, 320,0.320, 70 ma., 4v., 4.5a. C.T., 4v., 2.5a C.T. (list 32/6).
- 10/6 CLASS B CONVERSION KITS. Complete in sealed cartons.
- 10/6 STRAIGHT III KITS. In sealed cartons, with full instructions.
- 10/- SAMPLE BARGAIN COMPONENTS Parcel. Guaranteed value, 30/-—40/-.
- 8/6 SHORT-WAVE ADAPTOR KITS, complete to last screw. Full instructions.
- 6/10 BLUE SPOT 66K SPEAKER UNITS. List 15/-.
- 6/6 D.C. ELIMINATOR KITS, with full instructions and sundries. Sealed.
- 5/11 UTILITY TWIN-GANG Condensers, with S.M. disc drive (list 12/6).
- 5/- SAMPLE BARGAIN SUNDRIES PARCEL. Guaranteed value, 15/-—20/-.
- 4/11 A.V.C. UNITS (list 10/-), with full instructions for any battery receiver.
- 4/11 H.T. 8, H.T. 9 MAINS TRANSFORMERS, boxed.
- 3/11 WESTINGHOUSE L.T. RECTIFIERS, 1/2 amp., 4-volt, 6-volt.
- 3/6 BRITISH RADIOPHONE SUPERHET COILS all types. Complete set with diagrams, comprising 2 I.F. Oscillator, 2 B. Pass, 16/6.
- 3/6 WESTERN ELECTRIC MIKES (list 21/-) a real quality microphone.
- 3/3 FAST- AND SLOW-MOTION air-spaced variable condensers.
- 2/11 BRITISH RADIOPHONE VOLUME CONTROLS, 10, 50, 100,000 ohms.
- 2/11 COLUMBIA L.F. TRANSFORMER, 3 : 1, 5 : 1 (list 10/6).
- 2/6 IRON-CORED DUAL-RANGE COILS, with diagrams.
- 2/6 AMPLION SUPER-CONE UNITS. (Worth 7/6).
- 2/3 VARLEY SQUARE PEAK DUAL-RANGE COILS (list 15/-), boxed with full diagrams.
- 1/11 L.F. CHOKES, 20 hen., 30 hen. Worth 5/6.
- 1/11 SCREENED DUAL-RANGE COILS with 6-terminal base.
- 1/11 MICROPHONE TRANSFORMERS. 100 : 1, Worth 3/-.
- 1/10 READY RADIO SHORT-WAVE COILS. 6-terminal base (list 6/6).
- 1/2 ASTRA DIFFERENTIALS, .0001, .00015, .0003, 20 hen. Chokes (list 8/6), 1/11d.
- 1/2 TELSEN MICA DIELECTRIC Variable Condensers, .0003, .0005.
- 11d. BROWNIE DUAL-RANGE COILS, with reaction. Helsby 2-mfd. condensers, 11d.
- 9d. S-WAVE H.F. CHOKES. Med. and long waves 10d. Glazite, 3d. 10-ft. roll.
- 7d. MICROPHONE BUTTONS, very sensitive, worth 3/-. V. holders, 4, 5 pin, 3d.; 7 pin, 6d.
- 6d. ERIE 1-WATT RESISTANCES. All sizes, 100 ohms to 500,000 ohms. 5/- doz.
- 4d. 1-WATT RESISTANCES, all sizes, 250-100,000 ohms, 1-5 megs, 2 watt, 9d.
- 4d. SPECIAL OFFER, SPAGHETTI RESISTANCES. All sizes, 1,000-70,000 ohms. Or 3/- doz.
- 3d. each. FIXED CONDENSERS .0001 to .0005, .001 to .006: .1, 2, 6d.
- 3d. ONLY, POST FREE—Enclose 3d. stamps to-day for your October number of "THE RADIO GOLD-MINE." By far the most comprehensive lists of up-to-date surplus goods (kits, components and accessories) yet produced, with a general price level lower than ever before. Avoid delay. Send (enclosing 3d. Stamps) to-day.

LONDON EAST CENTRAL TRADING COMPANY (Dept M. 129), 23, Bartholomew Close, London, E.C.1. Immediate delivery, 24-hour service. Cash or C.O.D. Secure your Copy of the Oct. "Radio Gold-Mine" to-day. Shop sales only, 24, Aldersgate St., E.C.1. Telephone all depts.: NATIONAL 7473.

THE 'GOLD-MINE' STORES
"RADIO MARKET OF THE WORLD."

MONEY-BACK SATISFACTION GUARANTEE

All Goods supplied by **OLYMPIA RADIO LIMITED** carry the above guarantee.

DECONTROLLED MODELS

- EKCO S.H. 25 chassis only. Complete with Valves and Speaker. Brand new. A wonderful job. Our Price, 28/15/0d.
 - BEAUTIFUL Walnut Cabinet to suit the above chassis. Our price, 25/-.
 - EKCO Model 74, Console Superhet. Beautiful Walnut Cabinet. Absolutely complete. Ready to work from A.C. mains. List price, 18 guineas. Our price, 13 guineas.
 - MARCONI 2-valve Battery Receiver. Self-contained Speaker, All Batteries. Complete with Marconi Valves, H.T. and ACC. List price, 4 guineas. Our price, 42/6.
 - MCMICHAEL TWIN SUPERVOX 4-valve A.C. Bandpass Receiver. Westinghouse Rectifier. Twin Energized Speaker. Interference Switch, etc. List price, 18 guineas. Our price, 13 guineas.
 - COLUMBIA 4-valve Screen Grid Battery Receiver. Complete with all Valves and Batteries. A remarkable job. List price, 16 guineas. Our price, 12/5/0.
 - SPECIAL BARGAIN—ATLAS P.M. Moving Coil Speakers. Output Transformer suitable for Pentode or Power Valve. An astounding bargain. List price, 42/-. Our price, 14/11.
- THE above is only a small selection from our thousands of Receiver and Component Bargains. Send your requirements—we will quote. Write for lists. Post free on application.
- TERMS—CASH with Order, or C.O.D. We Pay Carriage. Everything guaranteed O.K. or money refunded. Please mention this paper when replying.

OLYMPIA RADIO LIMITED
Mail Order Dept. 40a, Shudehill, MANCHESTER.
BRANCHES in all Principal Towns.

DICTIONARY OF WIRELESS TERMS by **Ralph Stranger**

TWO AND SIXPENCE

● The author who is a master of lucidity has produced in this book a valuable and fully explained synopsis of technical terms that everybody can understand. It will prove indispensable to everybody who reads technical books and journals. Fully illustrated throughout.

Obtainable at all Booksellers, or by post 2/10 from George Newnes, Ltd., 8-11, Southampton Street, Strand, London, W.C.2.

ADVERTISEMENT INDEX

	Page
Amplion (1932) Ltd.	133
Automatic Coil Winder and Electrical Equipment Co., Ltd.	141
B.T.S.	143
British Institute of Engineering Technology	Page i
Page i Television Supplement	
British General Manufacturing Co., Ltd.	133
Cosmocord, Ltd.	133
Coscor, A. C., Ltd.	125
Easypay Utilities, Ltd.	Page i
Electradix Radios	147
Eugen Forbat	141
Ferranti, Ltd.	126
Fluxite, Ltd.	126
General Electric Co., Ltd.	Back Cover
Graham Farish, Ltd.	129
Hayberd, F. C. & Co.	152
International Correspondence Schools	148
Lectro Linx, Ltd.	147
Lissen, Ltd.	142
New Times Sales Co.	151
Peto-Scott, Ltd.	Front Cover Strip, 137, 147
Picketts	142
Pifco, Ltd.	142
Pix	150
Regent Fittings Co.	142
Rothermel, R. A., Ltd.	133
Technical & Commercial College	143
The Gramophone Co., Ltd.	Inside Front Cover
362 Radio Valve Co., Ltd.	142
W. T. Henley's Telegraph Works Co., Ltd.	126
Wet H.T. Battery Co.	147

BIRMINGHAM RADIOMART.—Sensational Purchase of brand new and guaranteed perfect 1934 goods.

RADIOMART.—Lissen 3-gang bandpass coils screened and switched on aluminium base with book and circuits; unbroken boxes. Listed, 26/-; for 7/6, Ditto 2-gang for SG3. Listed 17/6; for 5/11.

RADIOMART.—Utility super-quality 3-gang air-spaced ball-bearing fully screened with trimmers. List price, 24/-; straight or superhet, 6/6.

RADIOMART.—Utility 2-gangs as above, 5/10. Utility dials to fit either, 2/-.

RADIOMART.—Utility single .0005, or .0003, with full size disc drive walnut knob escutcheon, 2/-.

RADIOMART.—Igranite smoothing chokes 20hy. 100ma 260 ohms, heavy stalloy core, 2/9.

RADIOMART.—Edgewise visual tuning meter 6ma. Illuminated 2 1/2 x 1 1/2 in. only similar RGD, 5/9.

RADIOMART.—Radiophone logarithmic potentiometers 10,000 ohms. wirewound, with mains switch, 2/-; 5,000 no switch, 2/-.

RADIOMART.—Clarion, 10/6; full vision dials wavelength scale, moving spotlight, complete beautiful oxidised escutcheon, 2/9.

RADIOMART.—Screened ironed dual range coils with reaction, circuits, 2/11. Igranite short-wave ditto, 3/3.

RADIOMART.—Igranite Parvo 3 1/2-l. List, 8/6; 2/11. Philco "Class B" driver, 2/9. Voltra, 8/6; L.F., 2/-; Ericsson, 15/-; L.F., 1/6.

RADIOMART.—Erie, 1-watt colour-coded resistances all values, 8d. Truwind wirewound colour-coded, 2/- dozen, our assortment only.

RADIOMART.—Aerovox 8x8 mfd. 435v. dry electrolytics, 3/6. Hellesen wet 8mfd. 435v., 2/9.

RADIOMART.—Cadmium 5-valve chassis, 1/6. Grey cellulose, 4-valve, 9d. Postage, 6d. extra.

RADIOMART.—Magnum Radiogram dissolvers, 2/9. Wirewound potentiometers: Magnum 25,000, Colvern 15,000, 1/6.

RADIOMART.—Metvick H.F. chokes, 9d. Lewcos screened anode leads, 3d. Belling Lee plain terminals, 1/- dozen.

RADIOMART.—Telsen differentials boxed complete knob, 0.0001, 0.00015, 1/-; 0.0003, 0.00035, 1/3.

RADIOMART.—Telsen wirewound potentiometers 10,000, 50,000, 1/6. Telsen mains transformers 50, 25 cycle, 12/6.

RADIOMART.—Non-inductive tubulars wire-ended 1,500v.t. 0.1mfd. 0.01, 0.02, 0.05, 6d. Philips ditto 0.0001, 0.001, 2d.; 0.25, 0.5, 9d.; TCC 0.25, 1/3.

RADIOMART.—Metvick transformer kit, laminations clamps sectional bobbin terminals complete, 3/6.

RADIOMART.—Erie, 50,000, 100,000, 250,000 potentiometers, 1/6; 400 ohm potentiometers, 6d.

RADIOMART.—Utility 1934 mica variables 0.0005 10d.; 0.0003, 8d.; 0.0002, 0.0001, 6d.; 0.0003, differentials, 1/6.

RADIOMART.—Brand new condensers eminent maker 5mfd. 500v. working, 3/6; 350v. working, 2/9.

RADIOMART.—Utility super quality 3-gang air-spaced ballbearing fully screened with trimmers. List price, 24/-; straight or superhet, 6/6.

RADIOMART.—Utility 2-gangs as above, 5/10. Utility dials to fit either, 2/-.

RADIOMART.—Lewcos and Varley spaghetti 600, 1,000, 1,500, 2,000, 5,000, 30,000, 40,000, 75,000, 4d.; 3/6 dozen.

RADIOMART.—Boxed Lissen, 12/0; heavy duty chokes 25hy. 70ma., 32hy. 40ma., either 4/6.

RADIOMART.—Epoch moving coil speech transformers 10-1, 12 1/2-1, 18-1, 25-1, any ratio, 2/3.

RADIOMART.—G5M1. Short-wave specialist. Years of transmitting and receiving experience. Quality only.

RADIOMART.—Short-wave H.F. chokes, 9d.; Frequentite valveholders, 6d.; Frequentite anode connectors, screened, 1/-.

RADIOMART.—Microvariables 15, 40, 100mfd., 1/3. Super all brass 0.0001, short-wave pigtail 1/9.

RADIOMART.—Igranite jacks with plug, 1/-; jacks only, 3d.; Lewcos 6-way cable, 4d. foot.

RADIOMART.—Fye low-loss short-wave valveholders 4-pin baseboard, 4d.; Eddystone I.F. transformers, 2/-.

RADIOMART.—Western Electric, 21/-; microphones, 2/9; transformer, 2/6; Beehive standoff insulators, 8d.

RADIOMART.—Milliammeters animeters flush nickel 2 1/2 in., 5/9; super ditto 2 1/2 in., 6/9. Read A.C. or D.C. All ranges.


RADIOMART.—List contains hundreds similar bargains. All guaranteed new and perfect in every respect. Owing to cost stamp essential. No Stunts. No Disappointments. No Junk.

RADIOMART.—Orders over 6/- post free.—The Square Dealers, 19, John Bright Street, Birmingham.

PEARL & PEARL

ALL bargains advertised in last week's issue are still available.—PEARL & PEARL, 190, Bishopsgate, E.C.2.

Revitalise your set

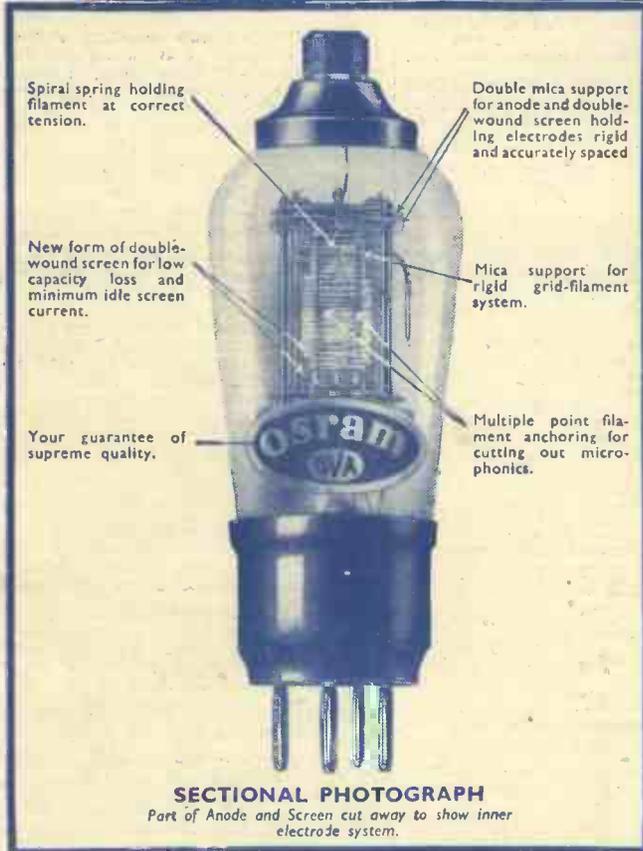

3 2-VOLT SCREEN-GRID VALVES mean —

- 1** GREATER SENSITIVITY WITH COMPLETE STABILITY—owing to low capacity and higher impedance.
- 2** ENTIRE ABSENCE OF MICROPHONICS— due to latest multiple anchored filament.
- 3** H.T. CURRENT CONSUMPTION FROM 1.5 M.A. ONLY.

S23 A low H.T. non-microphonic screen-grid valve for kit sets and portables employing one or more screen grid valves. Mutual conductance 1.1 ma/volt
Price 12'6

S24 A high slope, non-microphonic screen-grid for all single stage H.F. sets using screened coils. Mutual conductance. 1.4 ma/volt
Price 12'6

VS24 A "variable mu" screen-grid to give full and distortionless control of volume with only a 9 volt bias battery. Mutual conductance 1.5 to 0.01 ma/volt
Price 12'6

These Valves can be supplied metallised or plain.

Osram

2 VOLT BATTERY

Valves

MADE IN ENGLAND

SOLD BY ALL RADIO DEALERS

WRITE for the OSRAM VALVE GUIDE
(1934 Edition) sent post free.

Advt. of The General Electric Co., Ltd., Magnet House, Kingsway, London, W.C.2.