

FURTHER STEPS TO HIGH QUALITY— See page 10.

A
NEWNES
PUBLICATION

Edited by
F.J.CAMM
Vol. 16. No. 391.

Practical Wireless and

3!

EVERY
WEDNESDAY
Mar. 16th, 1940.

★ **PRACTICAL TELEVISION** ★

Contents

Mains Transformers



Headphone Hints



Thermion's
Commentary



Practical Hints



Reaction Backlash and
Threshold Howl



Steps to High Quality



Practical Television



Readers' Letters




RADIO IN THE SERVICES

**IF YOU WANT THE BEST SHORT WAVE SETS or COMPONENTS
GO TO YOUR DEALER AND INSIST ON EDDYSTONE**

"Eddystone" products are made for outstanding performance. They are used by the Fighting Services—have been employed in Arctic and Tropical Expeditions—in fact whenever utter reliability and the highest efficiency is essential "Eddystone" is used. YOU, too, will obtain the best results if you insist on "Eddystone." Do so to-day.

LONDON SERVICE: WEBB'S RADIO, 14, SOHO STREET, W.1, 58, VICTORIA ST., ST. ALBANS. BIRMINGHAM SERVICE: WEBB'S RADIO, 41, GARRS LANE.

64 Pages of WAR HUMOUR

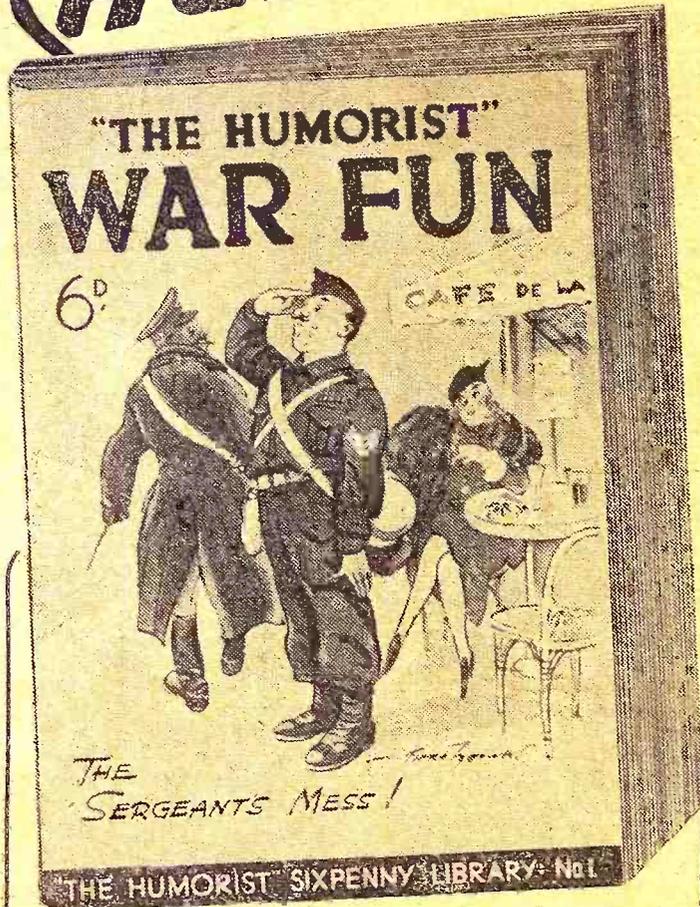

The good humour of the British soldier is proverbial! In the face of privation and discomfort Tommy is always ready to crack a joke and laugh at those of his fellows. Here is a big, breezy collection of some of the best humour produced since the war started.

THE WIT OF THE WORLD'S BEST LAUGHTER-MAKERS

- BERT THOMAS,
- LEES,
- WALLIS MILLS,
- A. C. BARRETT,
- TREYER EVANS,
- G. S. SHERWOOD,
- PETER PROBYN,
- HYNES,
- BACHELOR,
- FERRIER, etc.

WAR FUN


6^D.

At all Newsagents and Bookstalls.

George Newnes, Ltd.

Hundreds of Laughs

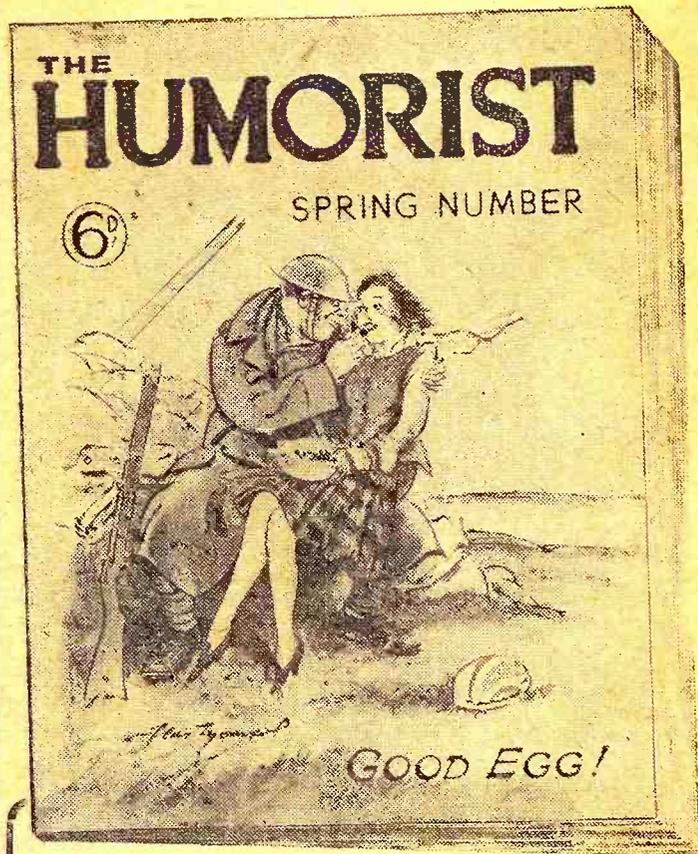By the World's Best Artists and Humorous Writers



A GREATLY ENLARGED NUMBER!

ALL THE BEST ARTISTS

- | | |
|----------------|----------------------|
| Bert Thomas | Batchelor |
| Treyer Evans | Arthur Ferrier |
| Lees | D. L. Ghilchik |
| Wallis Mills | Peter Probyn |
| G. S. Sherwood | Bertram Prance, etc. |

ALL THE BEST HUMOROUS WRITERS

- | | |
|----------------------|---------------------|
| K. R. G. Browne | F. Keston Clarke |
| Will Scott | Colin Howard |
| Denis Dunn | "Artemas" |
| J. Jefferson Farjeon | A. P. Garland, etc. |


HUMORIST

Spring Number

Order a copy from your newsagent to-day. Out Friday, March 15.

6^D.

George Newnes, Ltd.

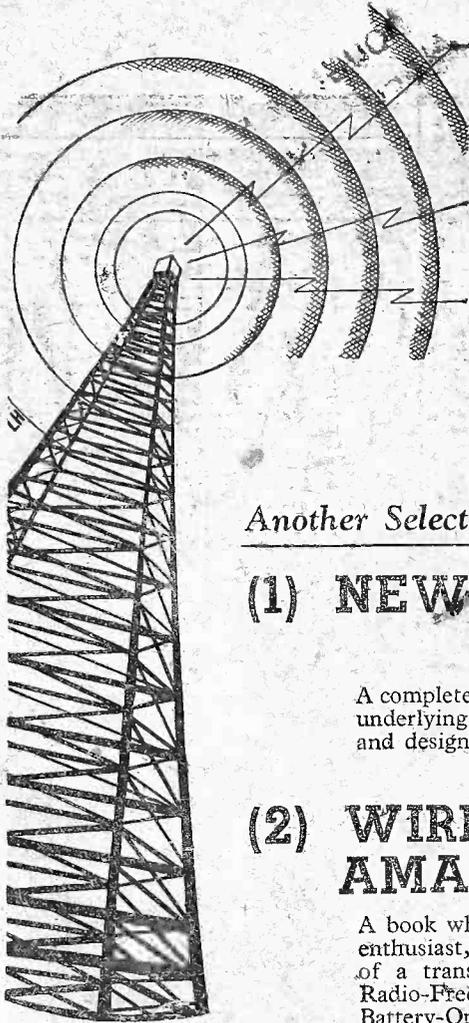

R-A-F W-A-N-T-S R-A-D-I-O M-E-C-H-A-N-I-C-S

The Air Minister announced recently that he wants radio mechanics. Recruits selected are given the rank of Leading-Aircraftman and paid at the rate of 5/6 a day, plus allowances. This is an opportunity for young men, and Newnes' Practical and Authoritative Wireless Books will help you gain the knowledge required.

Another Selection of Radio Books Published by PRACTICAL WIRELESS

(1) NEWNES' SHORT-WAVE MANUAL

By F. J. Camm

A complete work on the whole subject of short waves, this book deals thoroughly with the problems underlying the design of short-wave apparatus, the special circuits which yield the best results, and designs for receivers based on those circuits. Useful tables are included.

5/- net. (By post 5/6)

(2) WIRELESS TRANSMISSION FOR AMATEURS

By F. J. Camm

A book which covers fully and clearly the whole field of wireless transmission for the amateur enthusiast, from the obtaining of an amateur transmitting licence to the construction and operation of a transmitter. With 120 illustrations. Contents:—Valves, Transmitting Circuits, The Radio-Frequency Power Amplifier, Modulation Systems, Electronic Radiation, One-Valve Battery-Operated Transmitter, Aerials, Station Layout, Frequency Meters, Making Coils, etc.

5/6 net. (By post 5/10)

(3) THE OUTLINE OF WIRELESS By Ralph Stranger

Here is a book which covers the theory and practice of Wireless Reception from A to Z, and makes everything plain, even to the most "non-technical" reader. Contents: Matter and Energy. Electrified Matter. Electronic Currents. Magnetism and Electro-Magnetism. Batteries and Accumulators. Wireless Waves. Wireless Communication and Broadcasting. Over 800 pages, fully illustrated.

10/6 net. (By post 11/-)

(4) WIRELESS COILS, CHOKES AND TRANSFORMERS

By F. J. Camm

Contents:—Types and Principles. Resistance, Inductance, and Capacity. Choice and Use of Coils. A simple Tubular Coil. Screened Coils: Materials and Construction, Circuits, A Band Pass Unit, Ganging and Switching. Screened Superhet Coils. Short-Wave Coils. Screened Short-Wave Coils. Adjusting and Testing Coils. Coil Troubles and Remedies. 465 kc/s I.F. Transformers. An All-Wave Tuner. Coil-Winders. Selectivity. Aerial and Earth Systems. Preventing Breakthrough. H.F. Chokes. L.F. and Smoothing Chokes. Low-Frequency Transformers. Making Mains Transformers. Coil Data and Formulae. With 126 illustrations.

2/6 net. (By post 2/10)

(5) DICTIONARY OF WIRELESS TERMS

By Ralph Stranger

Indispensable to every wireless enthusiast who reads technical books and journals. It is a comprehensive work of reference for those wishing to understand the more advanced and serious books on wireless, but who do not possess any technical knowledge. 160 pages, well illustrated.

2/6 net. (By post 2/10)

SEND THIS COUPON TO-DAY

Ask your bookseller to get you the book or books you require at the usual price, thus saving postage. Alternatively, send the form to the publishers, with postal order (plus 6d. extra on each book to cover postage), and the book or books will be sent direct to you.

To the Publisher, GEORGE NEWNES, Ltd. (Book Dept.), TOWER HOUSE, SOUTHAMPTON ST., LONDON, W.C.2. Please send me by return the book or books encircled below. I enclose Postal Order for the necessary amount.

1. 2. 3. 4. 5.

P.O. Value.....No. is.....

Name.....

Address.....

..... P.W. 23/3/40

Practical and Wireless

★ PRACTICAL TELEVISION ★

EVERY WEDNESDAY

Vol. XVI. No. 391. Mar. 16th, 1940.

EDITED BY
F. J. CANN

Staff:

W. J. DELANEY, FRANK PRESTON,
H. J. BARTON CHAPPLE, B.Sc.

ROUND THE WORLD OF WIRELESS

Direct Coupling

MANY attempts have been made in the past to obtain improved quality by departing from normal methods of coupling in the L.F. stages. Generally speaking there are only resistance-capacity and transformer coupling, and although these may be combined, the principles remain the same. In each case the grid of the amplifying valve is isolated from the H.T. supply, either by a condenser or through the fact that the two transformer windings are electrically separate. Many years ago a system was developed in which the grid was joined direct to a battery, and it was claimed that a great improvement was obtained, due to the lack of a time constant in the grid circuit. Since those days many attempts have been made to improve on the arrangement, and in this issue we give constructional details of an amplifier in which the grid is actually connected, through resistances of course, to the H.T. positive line. This system, known as direct-coupling owing to the fact that the preceding anode is joined direct to the following grid, has advantages when it is properly made up, and we hope that the details given will enable readers who are interested in this arrangement to try out the scheme.

Licence for Valves

IN last week's issue we published a list of valves which can only be obtained when a licence form has been sent to the postal authorities. The form in question was previously only obtainable from Head Post Offices, but supplies have now been sent to all branch and sub-offices and it is thus possible to obtain the form from any normal post office. This does not include the smaller type of office which is found in conjunction with general stores, etc.

Gerald Cock

THE B.B.C. announce that Mr. Gerald Cock, M.V.O., has been appointed its North American representative in the place of Mr. Felix Greene. The appointment of North American Representative is made for a limited period. Mr. Greene in the normal course would have returned to England last autumn, but his replacement was delayed by the war.

Mr. Cock, who is the B.B.C.'s Director of Television, lived for some years in America and revisited New York last spring. The war-time suspension of the television service has made it possible for him to succeed Mr. Greene as the B.B.C.'s representative in New York.

Lemmy Caution Calling

BEN WRIGHT has been chosen to create the radio character of Lemmy Caution in a new series of short plays specially written for broadcasting by Peter



Jimmy Leonard, WLW announcer, who makes things not too easy and not too hard for contestants on "Marathon Melodies," radiated by that station to NBC on Fridays at 10.30 p.m., E.S.T. Leonard grew up in Florida, and made his radio debut with his good friend Red Barber, the sports announcer. Others on the "Marathon Melodies" show with him are Sylvia Rhodes, vocalist, and Josef Cherniavsk, orchestra.

Editorial and Advertisement Offices:
"Practical Wireless," George Newnes, Ltd.,
Tower House, Southampton Street, Strand,
W.C.2. Phone: Temple Bar 4363.
Telegrams: Newnes, Rand, London.
Registered at the G.P.O. as a newspaper and
for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in PRACTICAL WIRELESS. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

Cheyney. He will be heard in the Forces broadcast on March 14th.

"Lemmy Caution Calling," is the title of the series, and the first episode is "The Big Shot." The series should provide some good, rousing dramatic fare for listeners in the various Services, for they are full of action and based on strong gangster situations, with the celebrated Lemmy as the "G" man whose aim is to bring the criminals to the electric chair.

The Bing Boys

"THE Bing Boys are Here," "The Bing Girls" and "The Bing Boys on Broadway," three brilliant, colourful shows of the last war, are the subjects of the Keith Ayling and Leslie Baily programme, the second in the series "The Story Behind the Show," to be heard on March 15th. The collaborators have prepared a most interesting script, and it is hoped to have in the studio George Robey, the original Lucifer Bing; Violet Lorraine; Clifford Grey, the lyric writer; and Nat D. Ayer, the composer. They will revive some of the high spots of the shows to which went the fathers and mothers of men now in uniform.

"The Bing Boys are Here," was produced at the Alhambra on February 12th, 1916, and ran for 378 performances. The third of the shows, "The Bing Boys on Broadway," was still running after the war was over. Most people will have some outstanding memories of these great productions.

At the "Black Dog"

"AT the 'Black Dog,'" the popular feature which started in the Empire Programme over two years ago and which ultimately became a regular fixture in the Home Programme, will be revived for the Forces on March 15th. Later on, it may take its place in the Home Service. There was always a wonderful feeling of spontaneity about the series, and the friendly atmosphere of a small pub was most successfully conveyed to listeners. No scripts were used, and those taking part would probably have an hour or so to get to know each other before actually going on the air.

The Visitors' Book at the "Black Dog" is a grand mixed bag and includes the names of film stars, musicians, radio artists, churchmen, writers, footballers and people from every conceivable trade or profession. Gracie Fields has been there, and other famous names which come to mind at random are A. F. Tschiffely, the great horseman and writer; Valerie Hobson, one of the best of our British film stars; George Allison, the well-known football manager; S. I. Hsiung, the author of "Lady Precious Stream"; Leslie Howard; Jean Batten, the airwoman; Primo Carnera; and F. S. Smythe of the Everest expeditions.

Designing Mains Transformers - 3

How to Select Suitable Core Stampings, and How to Assemble the Transformer - - - By L. O. SPARKS

WHEN selecting stampings, it is preferable to use those of a square rather than a shallow oblong shape, as the former will invariably give a better voltage regulation figure. In addition to this important consideration, the completed transformer will be more rigid and the construction, generally speaking, more satisfactory. Insulation is one item which calls for particular consideration; bearing in mind the voltages developed across the H.T. secondary windings, it is absolutely essential to see that adequate insulation is provided between layers. It is not sufficiently appreciated by many amateur transformer constructors that a single short-circuited turn can cause currents to flow large enough to burn out the rest of the windings or, at least, ruin all insulation beyond repair.

One naturally thinks of the H.T. secondaries carrying high voltages, but the winding used for the heater of a rectifying valve is so often given no more consideration than the other L.T. windings that a word of warning would not be amiss. It must be appreciated that the rectifier heater is the supply point for the H.T. positive line and that the maximum voltage (A.C.) of the H.T. secondary winding will have to be considered with respect to the heater and the primary of the transformer.

When carrying out the winding operations, try and maintain a constant examination of the wire, as any defective insulation must be made good, and on no account should minute kinks be allowed to pass on to the bobbin. Tapping loops or points also call for special care. If they are brought out through holes in the cheeks of the bobbins, see that the wire does not cut into other turns and that a strip of insulating material is placed above and below the tapping wire.

Screened Primary

In most modern radio transformers it is usual to provide a screen between primary and secondary windings to assist in preventing the passage of high-frequency currents between the two sections. It is not a difficult matter to embody a suitable screen as this need only consist of a strip of copper foil, the width of the bobbin, long enough to go round the primary winding *except* for, say, 1/16th inch. In other words, the foil must not be allowed to form a *complete* loop, a small gap being left between its two ends. The primary winding should be covered with empire cloth or dry paper before placing the foil in position, and another strip of insulating material placed over the screen before winding on the secondary. When cutting the foil, leave a narrow strip on one edge to be brought out to form its connection to earth.

General Assembly

When all windings are finished, it is advisable to mark all leads with some means of identification, thus preventing any errors in that direction. Once they are marked, they should be twisted together lightly so that they form the least obstruction to the assembly of the stampings around and through the bobbin.

Before starting the assembly, sort out the stampings into their respective groups so that alternate shapes can be picked up easily and quickly, although there is no need to rush this part of the work. It is advisable to take a little time over the matter and see that the stampings are packed together in the proper manner and as tightly as possible. Sufficient material must be available, and used, to fill the core aperture of the bobbin, and a little light tapping is permissible to get the last two or three stampings in position, but don't go to the extremes and use sufficient force to cut into the bobbin.

Once a compact body has been built, clamping bars, preferably of metal, must be fixed in position across two sides of the assembly, these being held in position

marked points but it also removes the risk of the original wires breaking off, usually just inside the cheek of the bobbin, by the movement likely to be caused when connections are made or undone. Fig. 2 shows a simple method of mounting a terminal strip which should, of course, be made from reasonably stout insulating material. Ebonite about 1/4 in. thick, or fibre 1/4 in. thick, are the most suitable materials, as they are easy to work and have good insulating properties. The example shown makes use of sockets for the individual connections, but there is no reason why terminals should not be used, in fact they would, no doubt, provide an easier and quicker method for most experimenters.

Bobbins

Although these can be purchased, most constructors prefer to make their own according to the core and stampings being used. Providing a little care is taken in the selection of the material, its marking out and the actual construction, it is not so difficult as it might appear at first sight.

Cardboard, even when it is stiff and thick, is not satisfactory. It does not possess sufficient rigidity and, if it is thick enough to be strong, it makes a very clumsy looking bobbin. The best material is sheet prespahn or bakelised board, as these are strong, rigid and easy to work.

The centre of the bobbin should be marked out and cut as shown in Fig. 2, the dotted lines indicating the folding points which, to obtain a neat bend, should be scored with a penknife. Don't let the ends overlap, otherwise a pronounced bulge will be produced. If they butt together and, when the former is folded to shape, fit firmly into the cheeks, covered with a layer of empire cloth, a neat and strong job will be made.

The cheeks should just fit on to the ends of the centre former, but it is essential to see that all measurements are accurate. There are several good adhesives on the market for cementing all the parts together, but don't be too impatient over this part of the work, do give the adhesive time to set firmly.

Final Remarks

Whenever possible, meter tests should be applied to all windings, with and without current loads, before putting the transformer into active use. The voltage and current of the various windings should be checked and, if a meggar is available, insulation tests applied between all windings and the core and all windings.

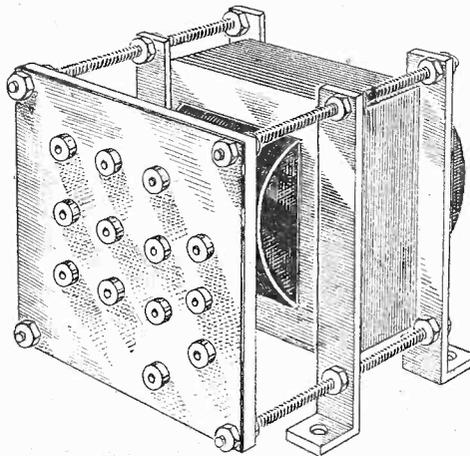


Fig. 1.—Showing how the clamping strips are made and fixed, and a suggestion for a terminal board.

by nuts and bolts as indicated by Fig. 1. The bolts or threaded rod must be strong enough to allow a reasonable pressure to be exerted, as it is essential for the clamps to be really tight to prevent any possible vibration of the stampings. Pronounced hum can be introduced into radio apparatus by failure to attend to this item. The clamping strips can be bent at right angles at one end to form feet for fixing purposes if so desired.

Terminal Strip

Most experimenters find it more advantageous to fit a proper terminal strip for the connections to the various windings than to leave loose wire ends. This is to be recommended, as it not only allows frequent connections to be made to clearly

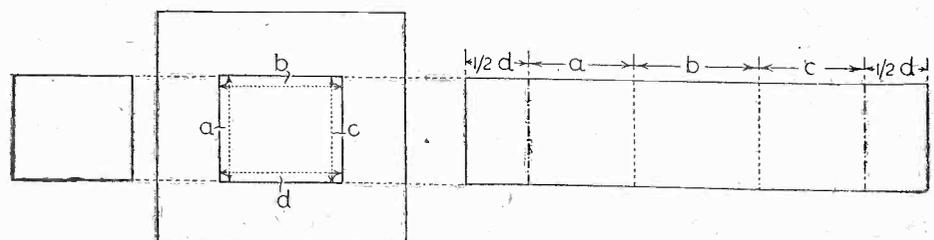


Fig. 2.—The insulating material for the bobbin should be marked out as shown above. Accurate dimensions are essential.

Radio in the Services

A Refresher Course for the Radio Mechanic—1

By Frank Preston

THE announcement, made in these pages a fortnight ago, that the R.A.F. were encouraging applications from those wishing to enrol as radio mechanics has created a considerable amount of interest among readers. Large numbers have inquired about the test which they will be asked to undergo should they apply for enrolment; most are anxious to have a fairly clear idea as to the standard of radio knowledge required. It is suggested that those who are interested should make inquiries at their local recruiting office, but it is possible to pass on the information obtained from representatives of the Royal Air Force.

Keen Constructors Encouraged

The main requirement is for keen amateurs and from those who have had some experience as service engineers. It is by no means essential that applicants should have an extensive knowledge of


can be obtained at any R.A.F. recruiting office. It will be better, instead, to consider the matter of the type of questions which may be asked. Quite naturally, it is impossible to state what questions will be asked, or even what questions previous applicants have been required to answer. But it is evident that a fair knowledge of the superhet is necessary; at least the recruiting officer with whom the matter was discussed laid emphasis on the superhet.

questions and suggested replies it should be found that many other points are brought to mind. Those points also should be settled without delay, preferably by working out a suitable answer and then by checking it by making reference to one of the books referred to above.

Some Questions and Answers

Let us start with a few fairly simple questions; others of a slightly more

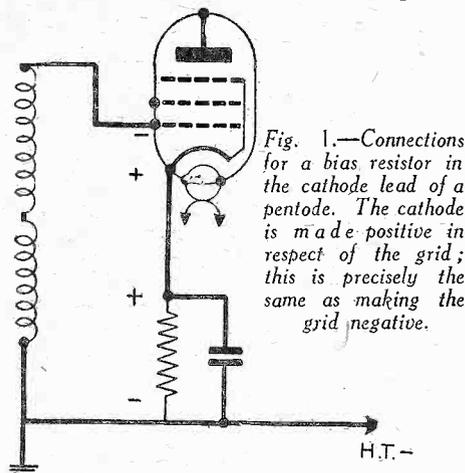Those making application for enrolment as radio mechanics are required to pass a test. Success in this may mean immediate promotion. At the end of this article are some questions of a type which may be asked (it is not suggested that any of them have been asked) along with what can be considered suitable replies



That fact will, I know, tend to upset a few readers because there is still a small minority who look upon the superhet as a very complicated arrangement which is difficult to understand. The majority know that this idea is false.

Nevertheless, it is a fact that it is impossible to have anything like a sound knowledge of superhet operation if a simple "straight" circuit is not understood first, and if the underlying principles of design of all the widely-used components are not known. It would therefore be almost useless to commence an intensive study of the superhet before making quite sure that you have a fair working knowledge of simpler circuits.

Helpful Books

Obviously, it would not be possible in the course of two or three articles to pretend to give a complete course in wireless, and it is therefore suggested that those who wish to "start at the beginning" should obtain a copy of "The Practical Wireless Encyclopaedia." Other books which will also be extremely useful are "Everyman's Wireless Book," "Sixty Tested Wireless Circuits" and "Coils, Chokes and Transformers." Any or all of these can be obtained from any bookseller or direct from The Publisher, George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2, who can also supply a catalogue of wireless books.

Instead of attempting to provide a complete course of instruction in this series, I shall simply ask and answer a number of questions which are, in my opinion, of a type which may be asked by the examining officer. The questions will not be graded in order of difficulty, or in any other order for that matter, but will be taken almost at random. It is not suggested that any reader who learned all the questions and answers by heart would stand the remotest chance of passing the examining officer. But I believe that any reader who can make an intelligent attempt at them would have excellent prospects. This is because to answer them the reader must know far more of his subject than is wrapped up in the actual answers. In reading the

advanced nature will be given in later articles of this series.

How is grid-bias applied to an indirectly-heated valve, and how can the value of the bias resistor be found when the characteristics of the valve and its associated circuit are known?

Bias is obtained by making use of the voltage drop across a resistor included between the cathode of the valve and the earth or H.T.—line, as shown in Fig. 1. Since the H.T. current for the valve flows through the resistor, there is a drop in voltage or potential across it. The voltage is proportional to the value of the resistor, in ohms, and the current passing through it.

It is generally necessary to by-pass the resistor by means of a fixed condenser; this provides a free path for H.F. or audio-frequency currents. The condenser may have a value of about 1 mfd. for an H.F. or I.F. valve, but the value should be increased up to, say, 25 mfd. (electrolytic) for an L.F. valve.

The value of the resistor is found by dividing the required G.B. voltage by the anode current (expressed in amps.). Thus, if the required G.B. voltage were 10 and the total H.T. (anode plus screen) current were 8 mA. or 8/1,000 amp., the resistance

wireless theory, but they should have a fairly sound understanding of the fundamental principles. An ability to reason and apply logical methods of deduction are essential, but that is tantamount to saying that sound common sense, blended with a certain amount of experience in radio construction, testing and fault-finding, is required. The recruiting officer approached was anxious to make it clear that they are prepared to give earnest consideration to all applicants who can be classed as successful home constructors; naturally, additional ability is appreciated and will greatly increase the possibility of rapid promotion, with the consequential increase in pay.

A point which should not be overlooked is that all successful applicants will be given a course of training in the particular type of work which their duties will entail. This means, in effect, that the keen amateur will have an excellent opportunity to learn more about his hobby, so that he can turn it to successful account as a profession—first in the Services and later, no doubt, in civilian life.

Knowledge of the Superhet

It is not necessary here to go any more deeply into the question of prospects and requirements, for additional information

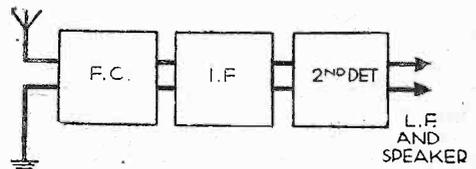


Fig. 2.—Essential parts of a superhet, where rectangles are used to indicate the stages.

should have an ohmic value of ten times 1,000/8, which equals 1,250 ohms.

What is meant by the term "intermediate-frequency amplification"?

This term, used in superhet practice, refers to amplification which takes place between the frequency-changer and the second detector (see Fig. 2). In a superhet the aerial or input circuit is tuned to the frequency of the signal being received,

(Continued on page 13)

Comment, Chat and Criticism

Listening to Music—2

Further Notes on How to Derive Pleasure and Instruction from
Listening to Good Music, by Our Music Critic, MAURICE REEVE

UNQUESTIONABLY the greatest aid to the full understanding and comprehension of a work of music of any pretension—next to key—is a grasp of the plan, or form, to which it is written. Nothing can be entirely formless and at the same time intelligent. And the abstract qualities of music render this problem of even greater importance than usual—great as it is in all things. Naturally, the harmonic and melodic patterns and weavings are almost entirely ruled by the type of framework into which they are going to be fitted. A composer sets out to write a symphony or sonata just as a builder sets out to build a house. Not a note of the one or a brick of the other is laid until the plan has been decided upon and studied in the fullest detail. But owing to the "concrete" character of a house, and to our lifelong usage of it, as opposed to the "abstract" qualities of music, the house is to us as a language is, something which we can understand, and of which we can use the amenities. With a major work of music, however, it is, for the opposite reasons, impossible to find our way about it with any reasonable prospect of deriving either benefit or pleasure, without first studying the "plans" with a modicum of care.

"Sonata" form is a subject I hope to deal with shortly in a separate article. It is by far the most important of the forms, and is used for the construction of almost all the major works of music outside of opera and church music. Even a slight acquaintance with it will throw a beam of light on a symphony, sonata, or quartet that will rescue it for us from a veritable "black-out" and enable us to view it in the brilliant sunshine.

Rhythm and Accent

With form is linked up rhythm and accent, the construction of a phrase and of different types of phrases (themes, melodies, subjects, according to their character and allotted place in the scheme), and the recurring rhythmic pulse and accents.

A knowledge of harmony would complete, or round off, our knowledge of key as discussed in the last article. It takes us far beyond the mere recognition, anticipation and blending of keys as colours do the ability to trace a single line of notes (part or voice) through the texture. Then we follow two lines together and so on, until we hear the whole pattern as we would see one if looking at a carpet.

I think the facility for picking up these branches of listening (also the faculty to recognise the tones of the different instruments in an orchestra), will be greatly enhanced if the basic principle of key and key recognition are first mastered. The incentive will most certainly receive an added impetus and encouragement, because, when all is said and done, key *is* music. It is the heart and the core, and in thousands of cases it is the *only* thing that matters—in the small forms such as songs, carols, and ditties of all sorts. It is only when we

begin to climb the ladder of, shall I say, musical sophistication, and its ever-enlarging horizons, that these other subjects, more especially form, enter.

I would like to conclude this brief sketch by getting back to its title, "Listening to Music." What we have done so far, as necessary here as anywhere, is to gather the material together essential for good, keen and intelligent listening; now enters that element which to many will seem the most urgent, the complete enjoyment of great music. "For," they may well say, "although you have helped us to understand the niceties of a symphony, and the polyphony of a quartet, you have not given us any guarantee that we will enjoy these things when we hear them. That is what we want the ability to do, rather than to criticise and be scholarly." True, my friends. You want to be like thousands are who watch cricket, who, whilst wishing to intelligently understand what is going on, don't wish to feel as though they were umpiring a test match. They want to browse on the grass round the boundary, quietly smoking, or drinking lemonade.

Mental Attitude

This will depend on the correct mental state we approach great music in, no matter how advanced or elementary our knowledge of it may be. It seems there are two requirements here. Firstly, never begin to listen to it in a totally unprepared frame of mind as you would always be when anything comes upon you unawares. Never be casual about it; always try to ascertain beforehand that it is taking place at such and such a time, and that you will be there. For, I am afraid, it is not a "hardy" plant which we can casually confront with pleasure, like so much of the entertainment we get nowadays. It is not entertainment at all. It is a forced, hot-house plant of the most exotic perfumes and colourings, and, like all such things, cannot stand the frequent icy blasts of casualness and promiscuity which surround many other art forms. The air which we frequently give to a radio item of "That sounds nice; we'll leave it on for a bit and see what it's like," is absolutely fatal. If, under such conditions, you should succeed in obtaining any mental reaction to the work at all, it would almost bound to be unfavourable. If, on the other hand, it should be favourable, this happy state would not be reached until the work was nearing its conclusion, upon which the effect would immediately evaporate. The result would of necessity be that, long before the next item had also been brought to an end, your favourable impressions of the former item would almost, if not entirely, have evaporated. Certainly your ability to retain even a slight recollection of a beautiful theme or other striking passage would be very small.

In fairness to the music, make adequate preparation for listening to it, and be certain that you will at least be in a mood and a frame of mind for appreciating it. You cannot enjoy excellent food or wine

unless you are hungry for it, and it is the same with good music.


Secondly comes the all-important question of the proper frame of mind, or mental state, in which we should try to be when listening to good music. How should we approach the music? What should we look for in it or expect from it? Should we expect anything? You may reply that all this will depend on what the music is. We couldn't avoid looking on Beethoven's third symphony from even a slightly different angle than the one from which we view his seventh. And we certainly can't avoid thinking of Beethoven or Mozart in a very different light from Tchaikowsky or Ravel, and expecting something quite different from each.

Treating Music as Absolute

But I have, personally, always adopted the principle, and a few exceptions here and there will only serve to emphasise the general soundness of the idea. Treat all good music as "absolute," as I defined that word in a previous article. Certainly do not look for stories and programmes where none exist, or ever did exist. And even in such classic examples of programme music as Beethoven's Pastoral Symphony they are much more enjoyable and satisfying when divorced from their programme. At least, I find them so. I do not suggest for one moment that it is not helpful, as it is certainly interesting, to know of the story or motive which inspired the work. Even such an extraneous and unnecessary appendage as the "Napoleonic dedication to the Eroica Symphony" is helpful. But what I mean is this: forget all about Napoleon, cows, cuckoos or thunderstorms when listening to either of those works. Concerning the former, at any rate, the pastoral loveliness pervading every bar of it obtrudes itself with such an ample sufficiency that there should be no possible need for anyone to want to refer to their programme notes to see what it is all about.

Of course some works must stand or fall by the realism with which they portray what they set out to paint if for the very reason that they intended from the outset to do little else. Operatic music comes into this category. All Wagner's genius would not have been sufficient to place him in his pre-eminent position had he failed to sweep us off our feet with the marvellous realism of his canvases. The Venesbury music, the "Ride of Valkyries," and a hundred other examples, are as vivid as any painting, providing we know the story they set out to portray. They are the supreme examples of programme music, unmatched in their ability to transport us to the scenes and places they describe. But the fact that they do this to millions of people whilst listening to them in the concert hall, without any aid whatever from scenery, costume or words, is surely proof positive that *all* music can, and should, be listened to as I have tried to advocate in this article.

ON YOUR WAVELENGTH

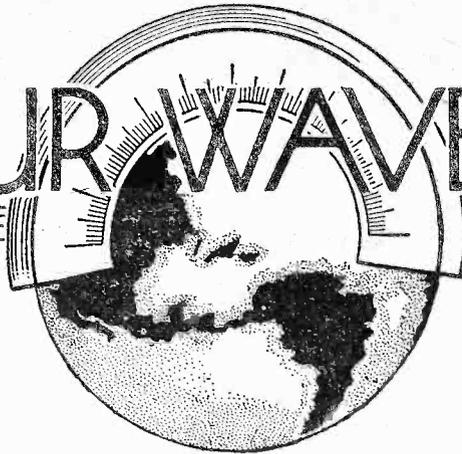

The QSL Exchange

YOU will remember that I raised the question some weeks ago of the QSL exchange. I expressed the opinion that it was unfair for a reader to adorn his den with verification cards which he had not obtained in the orthodox way, but merely by exchanging them with other short-wave fans. I said that a den so adorned was intended to give the impression that the owner of the den himself had received programmes from the stations represented, and had obtained verifications. Thus the whole value of the verification card was lost.

Since that time both sides have expressed their views in the correspondence page, and we have received about an equal quantity of letters from those in favour and from those against. I am asked to exercise my casting vote, and I now say that the motion that we should continue to publish requests for QSL exchanges is lost. Therefore, will readers please note that we cannot publish further offers to exchange. It is not my wish that the QSL card shall have no greater value than a cigarette picture.

Wireless as a Profession

THE recent broadcast appeal for those with technical knowledge of radio to join the new wireless trade created in connection with the Services has produced to date nearly 15,000 applications. Our recent survey of radio careers was a much-appreciated feature, and we are still receiving large numbers of letters from readers who want to enter the radio trade as a profession, or to study for it. The suggestion has been made that we should run a regular feature dealing with radio careers. I therefore invite the opinion of my readers on this suggestion so that I can lay mass evidence, if any, before the Editor.

I understand that a large number of those who have already applied for the vacancies which have been advertised are readers of this journal, who have paid graceful and grateful tribute to the Editor and for the technical knowledge supplied by PRACTICAL WIRELESS and the technical books we issue in connection with it. Those who wish to obtain a first-class knowledge of radio cannot do better than study our series of handbooks which include "The Practical Wireless Encyclopædia" (now, unfortunately, increased in price to 7s. 6d., but worth ten times the price), "The Practical Wireless Short-wave Manual," "Everyman's Wireless Book," "The Short-wave Manual" (a new volume), "Wireless Transmission for Amateurs" (now increased in price to 3s. 6d.), "Wireless Coils, Chokes and Transformers," "Sixty Tested Wireless Circuits," "Television and Short-wave Handbook," "Workshop Calculations, Tables and Formulae," and "The Practical Mechanics Handbook." A catalogue of our technical books will be sent free to any reader applying to the Manager of the Book Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

By Thermion

Those engaged in the manufacturing side should certainly take each week our new companion weekly, *Practical Engineering* (4d. every Thursday).

Distortion

ONE of the queries which frequently arises in letters addressed to me personally concerns the cure and forms of distortion. For perfect reproduction the sound issuing from the loudspeaker should be an aural replica of what is taking place in the broadcasting studio. When this fails to happen, as judged by a critical ear, or by movements of a tell-tale needle inserted at correct points in the power feeds, distortion is taking place. It is not generally believed that the high-frequency section of a wireless receiver is often the cause of distortion blamed on the low-frequency side. The introduction of so many high-powered broadcasting stations has made the question of selectivity rather an acute one. When a station is sending out speech or music it broadcasts, in addition to the carrier wave, other frequencies which are known as sidebands. These are spaced equally on either side of the carrier frequency, and may extend as far as 7,000 to 8,000 cycles either side.

A receiver of the ordinary type boasting of razor-edge selectivity cuts off a large section of these sidebands, or at least reduces their amplification to such an extent that they compare very unfavourably with the amount of amplification accorded to the lower frequencies. Anyone musically inclined will realise that the higher frequencies bring about the brilliance or timbre, and if they are not present, then quality must to a certain extent be reduced.

If the constructor of a wireless receiver finds himself in a cleft stick, owing to his desire for adequate selectivity without cutting sidebands, he can adopt what has come to be known as band-pass tuning.

In the modern arrangement we have three main types. In every case it will be noticed that there are two tuned circuits, and energy is transferred from one circuit to the other by a mutual magnetic interaction, a coil common to both tuned circuits, or a carefully controlled capacity coupling.

The frequency response of each circuit is thus combined, and it is possible to make the complete circuit accept frequencies over quite a wide range and almost wholly reject the others. In other words, brilliance and reproduction are maintained, together with selectivity.

Another very marked cause of distortion

is the use of "shoddy" components of doubtful origin. Too often is a set blamed for distortion when the fault is located in the fact that it is being starved of its H.T.

Returning now to the question of frequency distortion, the items chiefly responsible for this are the methods of coupling between the valves and the loudspeaker itself. Taking the first-named, it must be remembered that if L.F. transformers are employed, the primary or input winding must have an adequate primary inductance. This does not necessarily mean that the transformer with the largest size is going to give the best results. Modern development has produced transformer cores which are quite small compared to the early types. It is also necessary to maintain the inductance high even when quite large anode currents from the valve pass through the primary winding, so in this case it is necessary to learn whether a manufacturer guarantees the inductance in henries to be a certain value up to a given current, and then take steps not to exceed that current.

With inadequate primary inductance in transformers, there will be a loss of the bass frequencies, so that even if you have the most perfect sound reproducer coupled to the set, if the bass frequencies are lost they will not be heard from the loudspeaker.

Wireless for the Blind Fund

IT is interesting to note that during the ten years since its inception in 1929 to the end of last October, nearly £166,000 had been collected for the British Wireless for the Blind Fund. Of this sum, £151,500 was expended on sets and accessories for blind listeners, and there was a balance of nearly £2,000 in hand.

All sets provided by the Fund, says the annual report, are of modern loudspeaker type. Their distribution is carried out by 150 local welfare agencies.

B.B.C. Handbook for 1940

THE B.B.C. is taking its part in the dissemination of news all over the world in counteracting falsehood, in helping to make known the British point of view, but there is another side to the radio war. The B.B.C.'s war-time job is also to learn what is being said about Britain by others. It has to listen night in, night out, to the "news" and the propaganda broadcast from Germany and it has also to keep track of what neutral countries are thinking. The B.B.C. is not only the Voice of Britain; it has become the Ear of Britain. An article entitled "Listening Post, 1939," in the B.B.C. Handbook for 1940, which was published on March 4th, traces the growth of the new Monitoring Service which records, translates, summarises and distributes daily some two hundred broadcasts in twenty-five languages.

Listeners who are interested in the story of events behind the microphone can obtain the B.B.C. Handbook from booksellers and bookstalls, or direct from the B.B.C. Publications Department, The Grammar School, Scarle Road, Wembley, Middlesex, or on application to any Regional Office. Its price is two shillings, or 2s. 4d. by post.

Headphone Listening

Precautions to be Taken When Using Headphones with a Mains Set, and Points About Matching

IN the earlier days of radio headphones were the only practicable means of reproduction, since the power output of the set was too small for any other means. As loudspeakers became more efficient and less costly, headphones passed out of general use. The disadvantage of being tied to the set by 'phones contributed to their displacement, since several

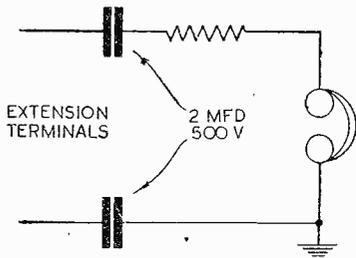


Fig. 1.—One method of 'phone isolation, with high impedance extension.

people could listen simultaneously to a speaker.

There are, nowadays, many circumstances in which the use of headphones is an advantage. Some people may switch off the set because of the nuisance caused to others who may not want to listen. Again, for a deaf person to hear in comfort, the volume level of the set speaker must be raised to a level unbearable for those with normal hearing. As shown by the Queries Section of this journal there are many people wanting a safe and efficient method of using headphones with their sets.

Precautions To Be Taken

The connection of 'phones to any set is subject to several important precautions, especially if the set is mains operated. Indiscriminate connection is highly dangerous and must be rigorously discouraged.

The chief precaution to be taken is against the risk of shock to the wearer of the 'phones, due to the contact of the metal headband or other metal parts of the 'phones with the listener's head. It is essential to earth efficiently one side of the 'phones, so that the voltage at the earpieces cannot rise to a dangerous value. For this to be done the 'phones must be isolated from the set. The two methods recommended for this are shown in Figs. 1 and 2. Either condensers are used, one 2 mfd. 500 volts working at least in each lead, or, better still, a transformer of suitable ratio is fitted between the 'phones and the output from the set. Two condensers should be used, since in some A.C.-D.C. sets a mains leakage may occur across some internal component in the set, or it may not be possible to earth one side of the speaker circuit. The transformer method is the better: the transformer used should be dependable and efficiently insulated.

Matching 'Phones To Set

It is desirable for the apparent volume from the 'phones to be the same as that from the speaker, so that the two units may be used simultaneously. It is more difficult to match 'phones to the set than it is to match extension speakers, where it is merely a question of matching impedances. With 'phones the impedance does not concern us; but only a fraction of the power output is required, and so if the 'phones are used alone the surplus power must be dissipated in some way. The volume of the speaker and 'phones varies with their sensitivities, and so the following details are not critical, but will give good results with average units.

The most readily accessible place for any connection to the set is the extension speaker socket. Here any output impedance from 1 ohm to about 20,000 ohms may be encountered.

If the output is of high impedance, then either a suitable step-down transformer between 'phones and the output, or else a high resistance in series with the 'phones will be needed to reduce the volume to bearable limits. To give a typical case, a battery output pentode of impedance about 11,000 ohms would need a step-down transformer of ratio 7-1 to match 'phones of 4,000 ohms overall resistance. If the

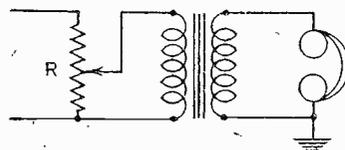


Fig. 3.—Volume control circuit for either high or low impedance extensions. For impedance Z value of $R=2Z$ ohms.


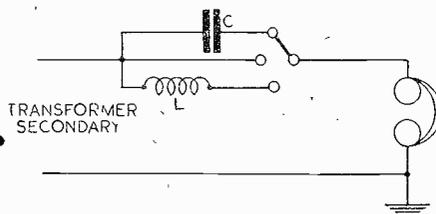


Fig. 4.—Simple type of tone control for use in conjunction with Fig. 2.
C .01 to .1 mfd.
L .3 to 12 henries.

other method is used a 500,000 ohm variable resistance is suitable. This serves as a rough volume control.

The extension impedance is commonly of the order of 5 ohms. For 'phones of 4,000 ohms a step-up transformer of ratio about 3-1 will serve.

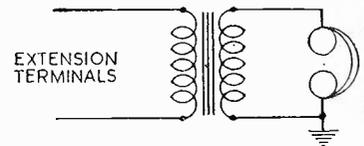If 7.5 or 15 ohm impedances are required, then a transformer of ratio 1-1 will be suitable. Here it is advisable to reduce the overall resistance of the 'phones from



LOW IMPEDANCE EXTENSION - STEP UP
HIGH IMPEDANCE EXTENSION - STEP DOWN

Fig. 2.—An alternative method of phone isolation, with low impedance extension.

4,000 ohms to 1,000 ohms by changing them from the usual series connection to parallel. In doing this care must be taken that the two positive and the two negative 'phone terminals respectively, are connected together. Otherwise the sounds fed to each ear will be out of phase, with unpleasant results.

For high impedance extensions the transformer ratio is roughly $\sqrt{\frac{Z}{200}}$ and for low impedance extensions is $\sqrt{\frac{200}{Z}}$ where Z is the extension impedance.

For high impedance a step-down, and for low impedance a step-up, transformer is used.


The ratio is not very critical, and may even be twice or half as much.

'Phones Used Alone

It has been assumed so far that the load on the output stage is being maintained by the connection of either the set speaker, or some extension simultaneously with the 'phones. If the 'phones alone are to be connected, as may frequently be the case, some means of dissipating the unwanted power is to be incorporated. The primary or secondary of the 'phone transformer is shunted by a suitable resistance, and since this must be capable of dissipating the full power output of the set, it is best placed across the primary of the transformer. It should be of about 3 or 5 watts rating. Here again the value of the resistance is not critical, but it should be about twice the extension impedance value. A potentiometer is used, this also serving as a volume control for the 'phones. Fig. 3 shows a suitable arrangement for both high and low impedance extensions. This will give a range of volume both below and above the set speaker volume, whether speakers are connected simultaneously or not. The 'phone transformer need not be expensive; since its power handling capacity is small, a midget type will be suitable.

Tone Control

Since the normal tone controls of the set will work just as well with 'phones as with the set speaker, there is no need to fit any additional control for the normal listener. The frequency range of normal 'phones is not wide, but with a transformer of suitable ratio most people will be satisfied by the quality of reproduction. If some degree of tone control is required, however, and deaf persons may need either bass or treble lift, this is easily incorporated as shown in Fig. 4. With low impedance extension, a transformer of higher step-up, and with high impedance one of lower step-down, ratio than usual is used, with an inductive or reactive network between the 'phones and the transformer secondary. Experiment must determine the best values of the components for individual requirements. The condenser capacity may be .01 to .1 mfd., and the choke .3 to 12 henries. The 'phones should be paralleled as described before to give a resistance of 1,000 ohms, since then the effect of the inductive impedances will be improved.

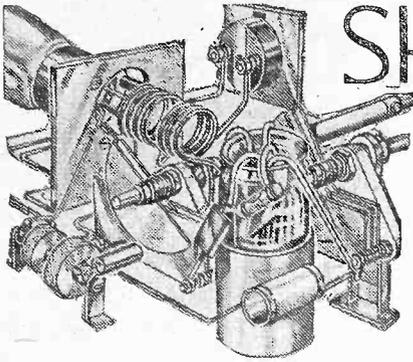

SHORT-WAVE SECTION

SHORT-WAVE REACTION EFFICIENCY

Points Which Underline the Design of an Effective Reacting Detector Circuit
By W. J. DELANEY

MANY listeners attempt to use a simple single-valve set for short-wave work and succeed in obtaining only a few long-distance stations. Others, as may be seen from the extensive logs published in our correspondence columns from time to time, succeed with a similar simple set in obtaining signals from the farthest ends of the earth. In many cases, of course, local conditions and existing climatic conditions will play a large part in the performance of a receiver, but with a simple detector stage the efficiency of the reaction circuit is of the utmost importance. A detector valve without reaction is very little better than a crystal receiver, but when reaction is applied the results are comparable with

control is needed to take the set out of oscillation as is needed to take it into oscillation. This can be accomplished quite easily. Before dealing with the effects and the cure, however, there is another trouble which is often experienced in a reaction circuit, and that is where as soon as the set has broken into oscillation as already mentioned a high-pitched howl also sets in, and cannot be stopped until the set has been taken out of oscillation. This, from the fact that you are trying to work on the "threshold of oscillation," and that a howl is set up, gives rise to the term "threshold howl," and also is fairly easily cured.

Detector Anode Circuit

To understand fully the causes of the two effects just described, let us look at the anode circuit of the detector valve. There will usually be an H.F. choke connected direct to the anode, and then, between the low-potential end of the choke and the H.T. supply there will be a pair of 'phones, a transformer primary or a resistance—dependent upon the type of receiver in use. Across the choke and the anode component, whatever it may be, there will be a voltage drop, dependent upon the anode current of the valve. If, now, you include a milliammeter in the anode circuit of a valve which is provided with a reaction control, you will see that with no reaction there will be a steady anode current reading dependent upon the H.T. voltage and the particular characteristics of the valve. If, now, the reaction control is set hard over, so that the valve oscillates, you will find that the anode current reading has fallen. This is, in fact, the method of testing for oscillation,

as by earthing the grid of the valve, by touching it with the finger, the oscillation will cease and the meter needle will rise to the original reading, or a point very near it. Now from standard electric formulae we know that the voltage drop across a resistance is dependent upon the current flowing through it, and the greater the current, the greater the voltage drop, or the difference in potential between the ends of the resistance.

From this it will therefore be obvious that under certain conditions there will be a given anode voltage applied to the detector valve, but as reaction is advanced and the valve passes into an oscillating condition, the actual voltage applied to the anode will vary, the H.T. voltage increasing as reaction increases, due to the lowered anode current and the consequent reduced voltage drop across the anode load. There is thus a double effect on the valve. Whilst you are increasing the coupling between the anode and grid—or, in other words, increasing reaction—the H.T. is automatically increasing and the two combine to produce the sudden bursting into oscillation already referred to. Turning back the reaction control does not reduce the oscillation until a large adjustment has been made, as it has no effect on the H.T. whilst the oscillation is taking place, and thus a relatively large movement is necessary to produce stability, and this is at a

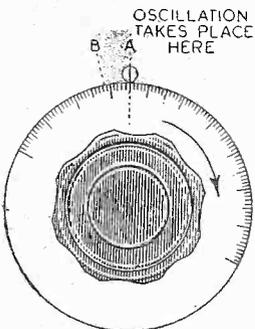


Fig. 1.—Reaction backlash is shown by an overlap of the control. Oscillation should cease at the same point as that at which it commences.

the addition of a good H.F. stage to the crystal. Owing to the peculiar working of reaction circuits, however, very few listeners realise how valuable this part of the set can prove. The reaction control should operate exactly the same as an L.F. volume control in a receiver, building up signal strength gradually, and just as smoothly taking the set out of oscillation. But how often is this effect found? Try the control on your receiver, with the set tuned to a very weak distant station. What do you find? Probably, as the control is turned the signal builds up and suddenly there is a "plop" as the set goes into oscillation. What happens then? You turn the control in the opposite direction until the set comes out of oscillation, and when this has been accomplished you have a given signal strength. But on advancing the reaction control again you can obtain an increase to the point where the oscillation occurs. But owing to the overlap, or backlash as it is called, you find you have to try three or four times before you can get the reaction control to the exact point where signals are at maximum and oscillation or howling does not set in.

Threshold Howl

This overlap is indicated in Fig. 1, where the point of oscillation on an imaginary dial is indicated and the point to which the control has to be turned to stop oscillation is also shown. The ideal condition is that where the same movement of the

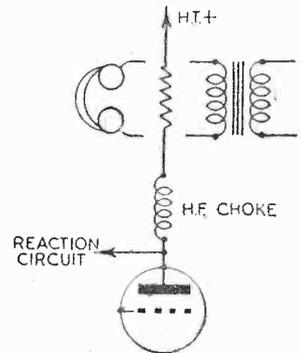


Fig. 2.—Typical anode circuit indicating the components which are found there. This explains the reasons for threshold howl.

point beyond that at which the set went into oscillation.

Cures

The threshold howl is due to the fact that when the valve bursts into oscillation a momentary change in anode current takes place and this stops the oscillation, but the reaction control is in such a position that the change in the H.T. voltage due to the cessation of oscillation again causes a condition of oscillation, which just as quickly ceases again. This oscillation and stopping takes place fairly rapidly and produces the howl already referred to. It is obvious from these remarks that the first and most important factor to be watched is the H.T. voltage applied to the anode. This must be of such a value that the changes which take place due to the oscillation have the least effect. The voltage varies according to the valve, and tests may have to be carried out to find the best working voltage, although the valve-makers usually give the necessary value on their data sheets. Next, the value of the grid leak and condenser must be so selected that the working point on the curve of the valve also takes up a position where the effects just mentioned are at a minimum. Thus, there are three essential points to be watched—H.T., value of grid leak, and grid condenser. A little experiment should enable suitable values to be found where, with the particular valve in use, the valve goes smoothly into oscillation and just as smoothly slides out.

A VALUABLE TECHNICAL LIBRARY!

- PRACTICAL WIRELESS ENCYCLOPÆDIA
7/6, or 8/- by post.
- EVERYMAN'S WIRELESS BOOK
5/-, or 5/6 by post.
- TELEVISION AND SHORT-WAVE HANDBOOK
5/-, or 5/6 by post.
- THE HOME MECHANIC ENCYCLOPÆDIA
3/6, or 4/- by post.
- SIXTY TESTED WIRELESS CIRCUITS
2/6, or 2/10 by post.
- COILS, CHOKES AND TRANSFORMERS
2/6, or 2/10 by post.
- PRACTICAL WIRELESS SERVICE MANUAL
6/-, or 6/6 by post.
- PRACTICAL MECHANICS HANDBOOK
6/-, or 6/6 by post.
- WORKSHOP CALCULATIONS, TABLES AND FORMULÆ
3/6, or 3/10 by post.
- SHORT-WAVE MANUAL
5/-, or 5/4 by post.
- WIRELESS TRANSMISSION FOR AMATEURS
3/6, or 3/10 by post.
- DICTIONARY OF METALS AND THEIR ALLOYS
5/-, or 5/4 by post.

All obtainable from GEORGE NEWNES, LTD.,
Tower House, Southampton Street, Strand, W.C.2

NEW SERIES

RADIO ENGINEER'S POCKET-BOOK

No. 23.

INTERNATIONAL "Q" CODE

Table with 3 columns: Abbrev., Question, Answer for Advice. Includes codes QRA through QRU.

No. 24.

INTERNATIONAL "Q" CODE

Table with 3 columns: Abbrev., Question, Answer for Advice. Includes codes QRV through QTR.

No. 25.

MISCELLANEOUS INTERNATIONAL ABBREVIATIONS

Table with 4 columns: Abbrev., Meaning, Abbrev., Meaning. Includes codes like ABT, AGN, ANI, etc.

No. 26.

QSA CODE (Signal Strength)

Table with 2 columns: Code, Description. Includes QSA1 through QSA5.

QRK CODE (Audibility)

Table with 2 columns: Code, Description. Includes QR1 through QR9.

RST CODE (Readability)

Table with 2 columns: Code, Description. Includes R1 through R5.

(Signal Strength)

Table with 2 columns: Code, Description. Includes 1 through 9.

(Tone)

Table with 2 columns: Code, Description. Includes 1 through 9.

No. 27.

INTERNATIONAL MORSE CODE.

Table with 2 columns: Letter, Morse Code. Includes A through Z and Number Code.

No. 28.

INTERNATIONAL AMATEUR CALL-SIGNS

Table with 4 columns: Code, Country, Code, Country. Includes AC4, AR, CE, etc.


PRACTICAL ENGINEERING — THE NEW WEEKLY PRICE 4d. EVERY THURSDAY.

Practical Hints

Speaker Volume Control

DURING my experiments I found the necessity for a tone control, volume control, and switch on each low-impedance extension speaker, so I connected them as in the diagram below.

I have not seen low-impedance speakers

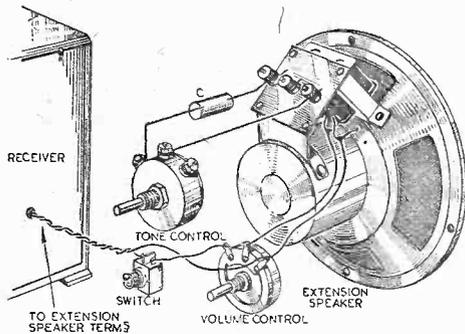

A volume control arrangement for an extension speaker.

connected like this, and I believe it is original. The volume control can be varied according to the impedance of the speech coil.—R. JOHNSON (Yatesbury).

Adjustable Nut Tweezers


ONE of the troubles that I find particularly annoying when "doctoring" a wireless chassis is that when replacing a component on the chassis after testing, bolts are sure to slip and fall on to the chassis, so that it either has to be turned upside down or the missing bolts have to be fished for with a pair of long-nosed pliers, which, owing to their breadth, cannot always be used in the limited space in a wireless chassis.

I decided to cure this trouble and have evolved an instrument of reasonable efficiency, the design of which I enclose.

The instrument itself should be constructed of some fairly thick metal which has some degree of springiness. The two pieces of metal marked D and E are of thin tin, and are bent over the strips, so as to form sliding collars.

The size of the holes drilled depends on the size of the threaded bar used, so is not marked in sketch.

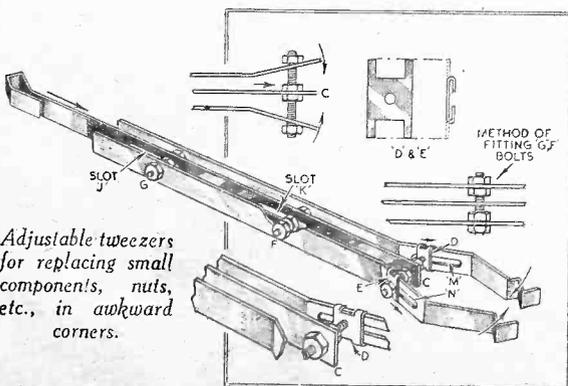The width between the jaws is controlled by the middle bar, which is moved backwards and forwards between the two outer bars. The distance between the two



Adjustable tweezers for replacing small components, nuts, etc., in awkward corners.

THAT DODGE OF YOURS!

Every Reader of "PRACTICAL WIRELESS" must have originated some little dodge which would interest other readers. Why not pass it on to us? We pay £1-10-0 for the best hint submitted, and for every other item published on this page we will pay half-a-guinea. Turn that idea of yours to account by sending it in to us addressed to the Editor, "PRACTICAL WIRELESS," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Put your name and address on every item. Please note that every notion sent in must be original. Mark envelopes "Practical Hints." **DO NOT** enclose Queries with your hints.

SPECIAL NOTICE

All hints must be accompanied by the coupon cut from page iii of cover.

pairs of bolts at F and G, which keep the two outer bars rigidly connected, should be just enough to allow the middle bar to slide smoothly. The longest of the three bars at the extreme end of the strip C should be about an inch long and should be rigidly connected at the middle to the strip C, while the ends should be passed through the bolt holes in the tin collars and anchored outside by bolts, the loosening and tightening of which controls the width between the jaws.

The best way of making the inch-long slots at J, K, M, and N is to drill a row of holes close together after which the burr should be filed down.—J. R. WOOD (Aberdeen).

A Station Indicating Extension Speaker System

HAVING built a new radiogram, using the original receiver chassis only, it occurred to me that it would be well worth while converting the original receiver cabinet into a self-indicating extension speaker, retaining the original appearance by keeping the control knobs as they were.

To carry out this idea properly, I decided that some sort of remote control scheme was necessary with regard to the station indicating lights, this being effected by simply attaching an extension shaft to the receiver tuning condenser, a simple ebonite cam and contact assembly being incorporated on this shaft.

A separate switch was fitted to the receiver to interrupt the extension lighting arrangement, and in view of the short leads between the receiver and the extension speaker, very little voltage drop occurred through the resistance of the flex, the leads being taken through the skirting boards and wall, as is depicted in the inset drawing.


The diagrammatical illustration shows the method I adopted for the station indicating lights in the extension speaker cabinet, and the following is briefly the way it is constructed.

The housing for the bulbs comprises two tin strips "A" and "B," these having been bent to form a box when soldered together. Into this box I soldered four separating pieces of tin, as indicated by a, b, c and d.

An ebonite strip provides the mount for the five bulbs which, by the way, are 2 volt .06a type: this ebonite strip is finally secured to the housing by bending over the tin lugs provided, and indicated by "X."

Each bulb holder is fitted with a 6BA screw nut and shakeproof washer, the connections 1-5 being made by soldering, whilst a common contact "W" is made by soldering a length of heavy gauge copper wire across all holders. The housing is secured to the inside of the cabinet by two brass angle strips, these being soldered to the housing, as shown.

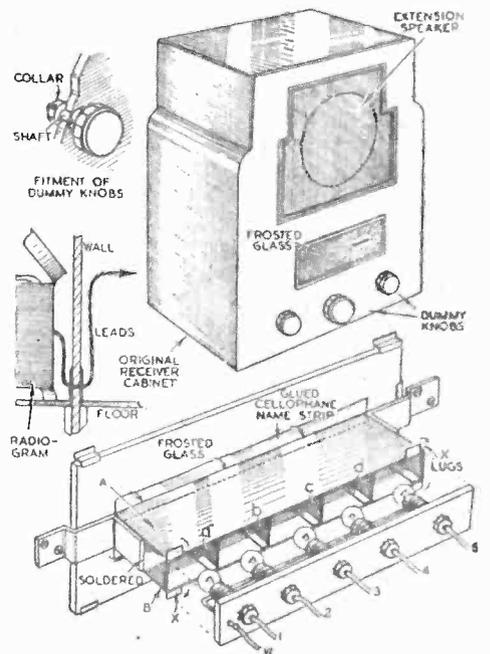The knobs are rendered dummy by using short lengths of 1/4 in. brass rod, brass



A novel method of station indication for an extension speaker system.

collars securing these internally, as illustrated. The use of thick frosted glass gives a really attractive appearance, enhanced by the station lighting, the names of the stations being printed in indian ink on a Cellophane strip, as depicted.—J. L. HARBURN (Loughton).

The PRACTICAL WIRELESS ENCYCLOPEDIA

By F. J. CAMM : 6th Edition

(Editor of "Practical Wireless") 7/6 Net

Wireless Construction, Terms, and Definitions explained and illustrated in concise, clear language

From all Bookellers or by post 8/- from George Newnes Ltd., Tower House, Southampton Street, Strand, London, W.C.2.

FURTHER STEPS

A New Receiver Using Direct C

It is refreshing to note that in war-time a deep interest is still being taken in high-quality reproduction, and that designers are paying careful attention to both the amplifier and the loudspeaker.

The object of this article is to call attention to a simple yet effective method of coupling low-frequency valves with a view to attaining a really high standard of reproduction. For gramophone work I do not think it can be excelled, but it especially commends itself to those who wish to obtain the best possible results from the B.B.C. Home Service transmissions.

Before describing the amplifier, I feel it necessary to say a word on the subject of linear rectification of radio signals. The diode is still very popular with high-quality enthusiasts, but there are numbers of listeners who are unable to load the diode sufficiently; that is, the signal input is not enough to ensure linear rectification even with the assistance of a stage of high-frequency amplification. If the high-frequency amplifier is developed beyond a certain point of efficiency, distortion is inevitable. The leaky-grid detector is sensitive but is easily overloaded, while anode-bend detection introduces its own form of distortion. The negative feed-back detector requires skilful design and complicates the circuit unduly. What is left? There is the crystal, to which many of us are still attached; but the crystal does not like a big input, and we may very easily fall between two stools, with the crystal on the one hand overloaded and the diode on the other hand underloaded, if we try one or the other. A complete solution of the problem occurred to me about a year ago, and this was to employ both crystal and diode together in series. What could be simpler? It is almost impossible to overload this combination, and a small signal input does not produce distortion. I have accordingly adopted this method of detection in the receiver under consideration.

L.F. Coupling

The most generally used methods of coupling low-frequency valves are transformer and resistance-capacity coupling. In these methods the anode of the valve is coupled to the grid of the next valve through a core in the case of the transformer or through a condenser in the case of resistance coupling. In the latter case it is not possible to get the best results except by push-pulling each stage thus coupled, as probably most readers are aware. Many amateur constructors hesitate to build such an amplifier because of the difficulties involved. But even better results are obtainable if a suitable form of what is called "direct coupling" is employed. In this method of coupling the anode of the valve is directly connected to the grid of

the following valve, so that the voltage applied to the anode of the first valve is the same as that applied to the grid of the second valve. Since the grid of the latter valve has to be kept negative in respect of the cathode, it is necessary to apply a positive voltage to the cathode. Thus direct coupling is a method by which the potentials of anode, grid and cathode are carefully balanced or proportioned to enable the valve to function as a low-frequency amplifier. In order to accomplish this it is usual to employ a potential voltage divider or a number of potentiometers connected in series, and to tap off the required voltages for each electrode. The

those who have access to electric light mains supply can avail themselves of this method of coupling. It is also most desirable to have a separate high-tension source for the output stage, and this means employing two eliminators as indicated in the diagram. The first two valves of the amplifier have their anodes supplied from a small high-tension eliminator giving a maximum output of 250 volts, and this eliminator can also be used for supplying the voltage to the high-frequency stage where such exists. For this purpose a Westinghouse metal rectifier type H.T.15 is quite satisfactory. The output valve requires an anode voltage of at least 360, after deducting the voltage dropped through the auto-bias resistor and the output choke. There must be quite a number of amateur constructors who already employ a similar output stage, and these will only be asked to make a few simple alterations.

Having stated the disadvantages thus early, I now feel less compunction in describing the main features of the circuit. Let us take a look at the diagram in Fig. 1. This shows the last two stages of the amplifier, represented by V3 and V4. When working out the direct coupled circuit it is necessary to plan from the output stage backwards. We will suppose that from a high-tension source of 250 volts a voltage of 130 is dropped through the resistances R6 and R7. It then follows that 120 volts are applied to the anode of V3. If we connect the anode of V3 to the grid of V4 (ignoring the grid-stopper R11 for the moment), then a positive voltage of 120 is applied to the grid of V4. It will now be necessary to make the grid of V4 negative in respect of its cathode, in other words, to bias the valve sufficiently to enable it to function on its straight line characteristic. This is done by applying to its cathode a positive voltage in excess of the positive grid voltage. If we apply approximately 150 volts to the cathode we shall achieve our object, and the simplest way to do this is to insert an auto-bias resistor R10 in the cathode circuit of V4 in the usual manner. The value of R10 must, however, be much larger than that


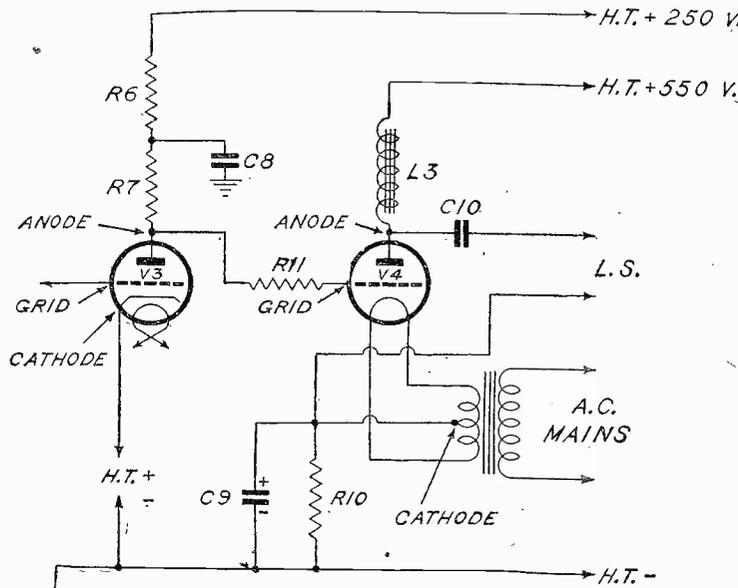


Fig. 1.—The last two stages of the amplifier described in this article.

maximum voltage may be anything from 400 to 2,000. The only resistances employed are those required for the anode circuits of the amplifier. It is obvious that such a system of coupling is beyond the resources of the average amateur, and I have worked out a simpler method which I hope will prove attractive to readers. The advantages derived from the direct method are (1) the elimination of the coupling condenser; (2) absence of the "time constant factor"; (3) response to a very wide range of frequencies; (4) faithful reproduction of transients; (5) a straight-line response characteristic; (6) absence of harmonic distortion, and (7) simplicity of design.

Disadvantages

It is only fair, however, to mention the disadvantages from the constructional point of view. It is necessary to employ a high-voltage output stage; and the circuit will naturally make a more direct appeal to those who happen to possess an output valve of the PX25 class, or who obtain a permit for acquiring one. The second disadvantage is the necessity of using indirectly-heated A.C. valves in the early stages of the amplifier, so that only

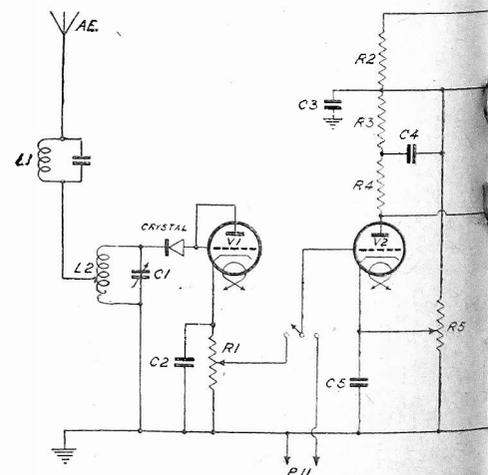

PRACTICAL TELEVISION

March 16th, 1940.

Vol. 5.

No. 194.

Caption Scanning

IN every television service which provides high-definition television pictures for radiation into the home, the necessity for some form of caption scanner will be immediately apparent. The visual announcement of items, names of artists and so on are frequently interspersed with the words spoken by the announcer, so as to add variety to the mode of presentation, and the equipment necessary for such a purpose as this can take a variety of forms. In the low-definition television days, Broadcasting House had its simple caption scanner built up from equipment resembling very much a mirror drum receiver. The beam of light from a small projection lamp was directed against the mirrors of the revolving drum and then focused on to the caption drawn in rough detail, because of the 30-line picture dissection, and the light reflected from the moving spot area, as it traced rapidly over the caption, was reflected on to photo-electric cells to generate the required television signal. A similar spot-light method has been used very successfully for high-definition working but the mechanical system has been replaced by a projection type of cathode-ray tube. This tube can be the straight through projection type, where the light area of the fluorescent screen formed by the impact of the beams of electrons is projected right through the screen and focused on to the caption cards or solid objects. A pair of photo-electric cells "collects" the reflected light or if a transparency is being televised, then a single cell placed behind serves as the light signal convertor. As an alternative to this, the cathode-ray tube can take the indirect form, where the screen is an opaque fluorescent coating mounted inside the glass envelope at an angle to the scanning beam. In this case a correction has to be applied electrically to overcome any trapezoidal scanning or focusing distortion.

Special Cells

UNDER service practical conditions the caption scanner of this form, comprising cathode-ray tube, power supplies, first stage amplifiers, scanning and focusing circuits, object platform and photo-electric cells, can be built into a single rack, or if preferred, into smaller interconnection units when transport from place to place becomes necessary. To obtain the best results from this apparatus it is essential to employ specially sensitive photo-electric cells, which have a mush or noise level very low in comparison with the main vision signal generated by the cells and scanning equipment. Then, again, it is advantageous to make these cells sensitive to the particular colour of the scanning spot, as this improves the efficiency of the combination. In some cases, it is found better to make up a caption scanner from an image dissector tube, but this is only applicable to transparencies and cannot handle the variety of subjects undertaken with the modern spotlight scanner. The

keen experimenter will find an outlet for his capabilities if he applies his skill to building up his own caption scanner for transparencies, using the standard form of relatively small diameter cathode-ray tube. For home use, small interconnected units are naturally to be preferred, and some time ago apparatus of this character was described in detail in these columns. It is as well to remember that with this home-built equipment, in addition to transparencies such as films or lantern slides, relatively flat solid objects can be held in position against the face of the transmitter cathode-ray tube, and they will then appear as shadowgraphs on the receiver screen. Useful experimental information covering a very wide field can be derived from apparatus set up in this way, and although very elaborate equipment would naturally prove somewhat costly, the home constructor need not be put to much outlay if he uses components or power units already in his possession. In laying out the apparatus in units, it is necessary to avoid the possibility of stray electric or magnetic fields upsetting the regular formation of the scanning fields on the cathode-ray tubes. Furthermore, the

A neat pre-amplifier unit for extending the range of reception of a television receiver.

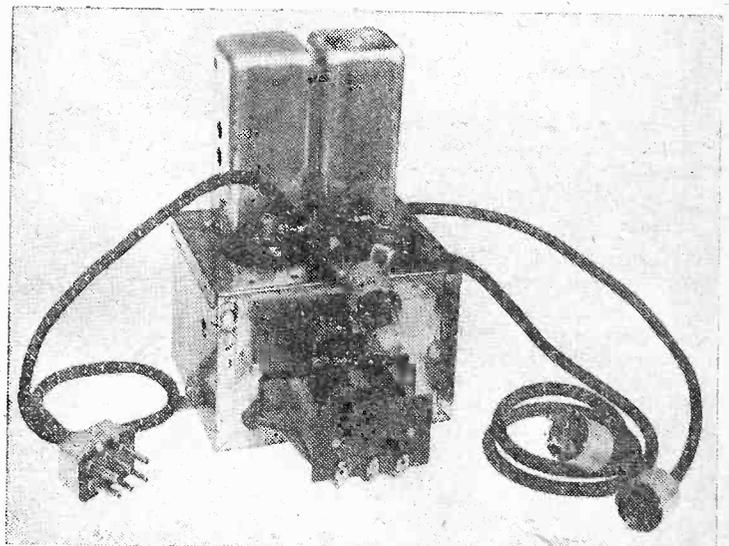


photo-electric cell and amplifier must be accommodated in a metal screened case and a reliable earthing system employed to remove any traces of hum that would otherwise be apparent on the screens if due care was not taken.

The "T" and "B" Problems

THE increased use of the iconoscope form of television camera has brought into prominence once more the two terms "tilt" and "band," to which reference is so often made but the significance of which is frequently lost sight of by those endeavouring to understand the operation of the equipment at the transmitting end. The terms have come into common use as far as television engineers are concerned, but

unless well versed in the intricacies of camera technique they fail to convey any real meaning to the lay mind. There is no doubt that the choice of such terms is unfortunate, but like many other radio terms that have become well established both in conversation and literature, there seems little opportunity at this juncture of remedying matters. These two terms came into use because of the graphical representation of certain inherent characteristics of the iconoscope. Due to certain defects, it is found that when a picture is being produced by this piece of electronic apparatus there is a gradual change of illumination from left to right which had no relation to the light and shade changes of the picture itself. The datum line of the illumination graph is therefore inclined or tilted in an upward direction. This has to be rectified at the transmitting end, and since the measure of tilt is not constant, the only reliable method of countering the defect is to electrically introduce a countering effect so as to keep this line horizontal and arrange for this degree of tilt nullification to be undertaken manually. It is quite a tricky operation and the engineer charged with this responsibility has to maintain a constant watch on the picture to ensure that his manipulation of the control is within the necessary limits. Another inherent defect in the same equipment is the fact that the illumination is greater or less in the middle of the picture than at the edges. A plotted characteristic will therefore show a concave or convex line, that is one with a bend in it, hence the significance of the term. The combination of the two is represented by a tilted, bent line and electrically this "bend" has to be countered by manual operation in just the same way as tilt. By a suitable combination of these controls it is possible to ensure that

the general brightness of the picture is made uniform over the area of the picture. A failure to attend to these two features would tend to spoil the received picture very materially, and it is a good thing that the rectification of these two points is the onus of the transmitting engineers and not of the viewers, otherwise the receive controls would be complicated and continually need adjustment.

A New Book

NEWNES SHORT-WAVE MANUAL

A Complete Treatise on the Design, Construction and Operation of all Short-wave Equipment.

Price 5/- or 5/6 by post

from George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

A RESISTANCE PROBLEM

SIR,—As the unfortunate possessor of a surname which Radio now associates with individuals of an inquisitive turn of mind, I cannot refrain from commenting on Dr. Fleming's article on "A Resistance Problem," which appeared in your February 17th issue, and which raises some interesting points.

It is not necessary to introduce determinants or even simultaneous equations to prove the example he gives.

As he states, the points a and b are, from symmetry, at equal potential. Likewise points b and f. Hence the current divides equally at the point A. Similarly the currents in the three branches at B are equal.

Also from these results, it follows that the potential drop across ac is equal to that across ab, hence the current also divides equally at point a. Similarly for the remaining points.

Thus assuming that the total current is 6i, the distribution is that shown above.

Considering the path AacB, the voltage drop is $2ir + ir + 2ir = 5ir$, and if R is the equivalent resistance of the frame, this $= 6iR$, whence $R = 5r/6$.

Another case besides those mentioned, of course, is the one where connections are made to opposite corners of the same face.

A more interesting problem arises where the cube has sides of sheet metal with points of current entry and exit at opposite adjacent or alternate corners.


Or if this is found to be too easy, some readers may like to consider the case of a solid cube, particularly for adjacent corners.

As my radio namesake might well say, this last is "a fine old how-d'ye-do to bump into."—R. C. WALKER (Caversham).

* * * * *

MR. WALKER'S letter does not make any point against me. The problem of the resistance of a skeleton cube of unit wires between diagonal corners happens to be one in which the component resistances are symmetrically placed with respect to the

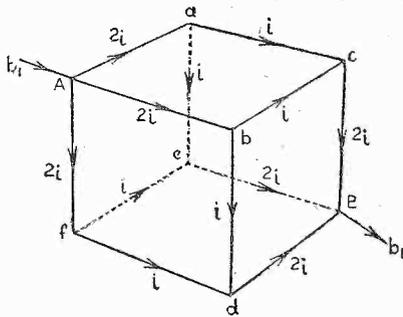diagonal line, and therefore the joint resistance can be found by the empirical method Mr. Walker uses. I gave a perfectly general method of dealing with problems in networks of conductors to the Physical Society of London in June, 1885, and it was published



Mr. Walker's arrangement of the resistance cube.

in the *Philosophical Magazine*, for September, 1885, or 55 years ago. I employed this method in solving the cube problem submitted to me. An empirical method, able to deal only with a few cases, is of no value compared with a mathematical method which is valid for all cases. Take, for instance, the problem of the Wheatstone's Bridge. Let Mr. Walker find an expression for the electric current through the bridge or galvanometer circuit when the resistances of the four arms of the bridge are P, Q, R, S ohms and the voltage in the Conjugate circuit is 1 volt.

My method, as described in the Paper referred to, enables the expression for the bridge current to be written down at once as the quotient of two determinants and I doubt whether any empirical method will so easily solve this problem.—SIR AMBROSE FLEMING.

DO NOT CONCENTRATE ON WAR

Do not concentrate your thoughts upon war subjects. You will find it very worrying and very bad for the nerves.


Read, write, sketch, paint, study your vocation; anything that will occupy your mind and your time. Make use of the long dark nights by concentrating upon something useful. During the last war many people learned how to write short stories, etc.; to-day a number of them are world-famed authors.

By becoming efficient in your vocation you can give the best service to your country and to yourself. The more you increase your earning power the better it is for the country and for yourself personally.

War or no war, earning power always brings its possessor to the front. It is no use waiting for better times. The ideal opportunity never arrives. We have to make the best of existing conditions. Therefore, delay is useless; it is worse, it is harmful.

DO ANY OF THESE SUBJECTS INTEREST YOU?

- | | |
|---|--|
| Accountancy Examinations | Metalurgy |
| Advertising and Sales Management | Mining, all subjects |
| Agriculture | Mining, Electrical Engineering |
| A.M.I. Fire E. Exams | Motor Engineering |
| Applied Mechanics | Motor Trade |
| Army Certificates | Municipal and County Engineer |
| Auctioneers and Estate Agents | Naval Architecture |
| Aviation Engineering | Novel Writing |
| Banking | Pattern Making |
| Blue Prints | Play Writing |
| Boilers | Police, Special Course |
| Book-keeping, Accountancy and Modern Business Methods | Preceptors, College of Press Tool Work |
| B.Sc. (Eng.) | Pumps and Pumping Machinery |
| Builders' Quantities | Radio Communication |
| Building, Architecture and Clerk o. Works | Radio Service Engineering |
| Cambridge Senior School Certificate | Road Making and Maintenance |
| Civil Engineering | Salesmanship, I.S.M.A. |
| Civil Service | Sanitation |
| All Commercial Subjects | School Attendance Officer |
| Commercial Art | Secretarial Exams. |
| Concrete and Structural Engineering | Sheet Metal Work |
| Draughtsmanship. All branches. | Shipbuilding |
| Engineering, All branches, subjects and examinations | Shorthand (Pitman's) |
| General Education | Short Story Writing |
| G.P.O. Eng. Dept. | Speaking in Public |
| Heating and Ventilation | Structural Engineering |
| Industrial Chemistry | Surveying |
| Institute of Housing | Teachers of Handicrafts |
| Insurance | Telephony and Telegraphy |
| Journalism | Television |
| Mathematics | Transport Inst. Exams. |
| Matriculation | Weights and Measures Inspector |
| | Welding |
| | Wireless Telegraphy and Telephony |
| | Works Managers |

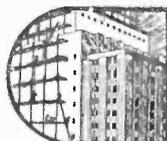

If you do not see your own requirements above, write to us on any subject. Full particulars free.

RADIO IN THE SERVICES

(Continued from page 3)

while the oscillator circuit is tuned to a frequency which is higher or lower than the signal frequency by a definite amount. As a result, the frequency of the received signal is changed to one equal to the difference between the input and oscillator frequencies. This is the intermediate frequency, and it is approximately 465 kc/s in most modern superhets. The I.F. amplifier is similar in all major respects to an H.F. amplifier, with the exception that it is pre-tuned.

If the loudspeaker was silent, despite the fact that the set was switched on, how could you tell whether the fault lay in the speaker or in the set itself?

With a battery-operated set, a rough check of the speaker could be made by disconnecting it and holding a lead from one of its terminals against the negative terminal of the L.T. accumulator, while the other lead was touched against the positive terminal. If the speaker was in working order a pronounced click would be heard as the contact was made, and again as it was broken. Absence of these clicks would point to a fault in the speaker, its built-in transformer or one of the connecting leads.

STUDY AT HOME IN YOUR SPARE TIME

JOURNALISM

Short Story, Novel and Play Writing.

There is money and pleasure in Journalism and in Story Writing. No apprenticeship, no pupilage, no examinations, no outfit necessary. Writing for newspapers, novels or pictures, is not a gift; it is a science that can be acquired by diligent application and proper guidance. It is the most fascinating way of making pastime profitable. Trained ability only is required, we do the training by post. Let us tell you all about it.

DEPARTMENT OF LITERATURE 104

EVERY DEPARTMENT IS A COMPLETE COLLEGE; EVERY STUDENT IS A CLASS TO HIMSELF

IF YOU ATTEND TO THIS NOW IT MAY MAKE A WONDERFUL DIFFERENCE TO YOUR FUTURE

COUPON—CUT THIS OUT


TO DEPT. 104, THE BENNETT COLLEGE LTD., SHEFFIELD.
Please send me (free of charge) Particulars of (Cross out line which Your private advice about } does not apply)

.....

PLEASE WRITE IN BLOCK LETTERS

Name

Address

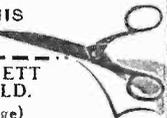

ELECTRADIX SIGNAL GEAR.

Morse Keys, Practice Sets, Buzzers, etc.




L.R. SOLO PHONES. The extra receiver you want on your phone line. For use with buzzer Morse. A circuit tester with a pocket cell. Single Earpiece, 40 ohms, metal hook loop, with cord, 1/3. Ditto D.3 60 ohms, with cord, 1/6. W.E. 1,000 ohms, with cord, 2/-. 2,000 ohms Earpiece, with cord, 2/6.

L.R. DOUBLE HEADPHONES. Pilot Signaller 120 ohm. Phones. All leather headbands with slide adjustment chin strap and 4ft. cord. Comfortable 3/6. Sullivan 120 ohms, aluminium headbands, 3/9, cords 1/6 extra.

H.T. BATTERY SUPERSEDER. 85v. at 6 ma for H.T. from your 2-volt battery, no H.T. batteries. 7in. x 4 1/2in. x 3in. Bakelite finish. Vibrator and Metal Rectifier, by S. G. Brown. Sale 37/6. Full guarantee. Type S, for larger sets. Can be supplied for either 2-volt, 4-volt, or 6-volt battery. Model 10, output D.C. 120 volt, 10 ma, 2 taps 65/-; Model 20, output D.C. 135 volt, 20 ma, 3 taps, 70/-; VIBRATORS, 6/12 volt car type, 4 amp., 10/-.



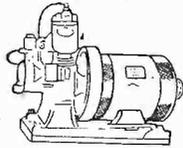
A.R.P. PETROL ELECTRIC GENERATING SETS FOR LIGHTING AND CHARGING FOR £16 ONLY.



A 500-watt, single cyl., 2-stroke, water-cooled, self-oiling Stuart Turner engine; mag. ign. coupled to 50/70 volts, 10 amps. shunt dynamo, 1,000 r.p.m., £16. No increase in price, these are £40 sets ready for immediate delivery.

FOR £12. A 150-watt engine and dynamo on similar lines but coupled to 25/30 volts, 6 amps. dynamo.

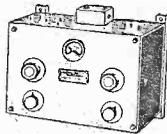A.C. MAINS CHARGERS. LESDIX TUNGAR CHARGERS. Two models of these famous sets. One for 70 volts 6 amps, with meters and controls, etc., will handle 100 cells a day, £7/17/6. Another fine Tungar for two 5 amp. circuits with meters and variable volt controls, 70 volts, 10 amps., for 200 cells, bargain, £12/15.



A.C./D.C. DAVENSET, Type G.C. House, Garage Wall Type Charger, 3 circuits, output D.C. 25 volts 6 amps. Trans. tapped for 15 volt, 20 volt, 25 volt. Two independent circuits, max. cell capacity 40 radio cells, £6/5.

PHILLIPS Model 1087 with valve for 24 volts 10 amps. Steel case, £7/10.

DAVENSET A.S.C.4. 4 circuit charger for up to 80 cells. List Price £32. Four sets of Auto-charge regulators and indications on panel with switch volt control. Four circuits of 1 amp., 1 amp., 2 amps., and 2 amps., or three of 1 amp., 2 amps., and 2 amps., or one of 50 volts 6 amps. Fine steel clad set complete in details that will quickly earn its cost, £14/10.

D.C. CHARGING OFF D.C. MAINS, £14. Davenset DC2 steel-cased 200/250 volt charger, large meters, wheel controls, 2 circuits, 1 amp. and 3 amps., as new. Sale price £5/10. Charging resistances, all sizes in stock. State load required.

230/230 volts MAINS CONVERSION UNITS. For operating D.C. from A.C. mains screened and filtered, 120 watts output, £2/10s.

TELESCOPES. Navy Telescopes, small gun type, 25/-; **MAGNETIC 1 1/2in. COMPASS with Plain Scale.** Bevel glass, brass body, 9d.

MOVING COIL MIKES. Torpedo P.M. moving-coil mike, model T.M., needs no battery, directional correct frequency response, ideal for P.A. and recording, 55/-; Table stand, 7/6. Transf., 7/6. Epoch type ditto, a robust and handsome P.M. M.C. mike, 35/6; with table stand, 42/6. Transformer, 7/6.

MIKE FLOOR STANDS, 26in., 12/6; 37in., 15/-; 48in., 18/6.

POWER ALTERNATORS, H.F., 50 cycles, 20 amps., 10 volts, £3/10. Ditto, double, type W, 500 cycles, 100 volts, 3 amps., and 70 volts, 3 amps. D.C., £5/10.

RADIO ROTARY CONVERTERS. For A.C. Receivers on D.C. mains to 230 v. A.C. output. In silence cabinet, with filter. All sizes in stock from 15 watts upwards, 30, 50, 100, 200, 400 and 800 watts; 1 kw., 1 1/2 kw., etc. Also battery operated 50-watt size in 12 volts and 50 volts input. T.V.T. Sets 6 volts to A.C., 25/-.

MEGGERS, 100 volts, 200 volts, 500 volts, and 1,000 volts from £6/10s.

RELAYS. Ultra-sensitive moving coil Relay, 1,000 ohms, coil closes circuit on 50 micro amps., 60/-; 2,000 ohms, 5 ma. lightweight magnetic Relay, 10/6.

5/- EMERGENCY PARCELS of useful stand-by electrical and radio repair material and apparatus, 10 lbs. for 5/- Post Free.

Send for 1940 Bargain List "N."

ELECTRADIX RADIOS

218 Upper Thames Street, London, E.C.4

Telephone: Central 4611

FURTHER STEPS TO HIGH QUALITY

(Continued from page 11)

for reasons of stability, and a 0.1 microfarad is quite satisfactory.

Should the constructor be troubled with mains hum—and some mains are more “noisy” than others—a complete cure can be effected in 99 cases out of a 100 by interposing between the mains and the eliminator input a step-down transformer with a screened primary, the screen being connected to earth. The anti-hum transformer has its primary winding connected to the mains. If, for instance, the voltage of the mains is 230 A.C., then the primary is wound to take this. The secondary is wound to step the 230 volts down to 210 volts, and the lower voltage is that supplied to the eliminator transformer primary. The voltage can, of course, be stepped up again as required and applied to the rectifier valve.

The transformers and chokes in my own amplifier and eliminator were made and supplied to me by Mr. N. Partridge, of King's Buildings, Dean Stanley Street, Westminster, S.W.1.

The detector, as already explained, consists of an ordinary crystal and a valve in series. Any A.C. valve can be used for the diode, the grid being strapped to the plate. The crystal can be omitted, or short-circuited by means of a switch, when it is desired to use the diode alone. The potentiometer R1 acts both as the output load and a volume control. Its value is half a megohm, and C2 is the usual high-frequency by-pass shunt of 0.0001 microfarad. L1 is a wave trap, which may be necessary in some districts. I can recommend the traps made by Messrs. Postlethwaite Bros., of Kinver, Staffs. The object of the trap is to cut out any one powerful interfering station by rejecting that particular wavelength. If “fading” is experienced, it is advisable to use an indoor aerial and a stage of high-frequency amplification. This, of course, is said with particular reference to existing conditions.

Provision has been made for the insertion of a gramophone pick-up in the grid of V2 by means of the usual change-over switch. A separate volume control must, of course, be employed for the pick-up.

In conclusion, I hope that at least some of my readers will be able to try out this amplifier. Its exceptional qualities will help to cheer the listener during black-out hours, and I venture to predict a new thrill for him.

IMPRESSIONS ON THE WAX

ONE of the most interesting records issued by the Decca Company this month is *Decca F 7355*. On to this single 10in. disc they have condensed the whole of “Runaway Love,” the musical show that is now running at the Saville Theatre, London.

This record was actually recorded in the theatre and features the original artists—George Gee, Luanne Shaw, Eric Fawcett and Hal Gordon, ably abetted by Billy Mayerl and his Multitone Piano Orchestra. No fewer than seven tunes are included on the one record.


Irving Berlin Album

THE versatility of Paul Whiteman is well displayed in a new Brunswick album devoted to the music of Irving Berlin. The album has five records. The first is by the full orchestra, the second by his Swing Wing Group, the third by his Bouncing Brass, the fourth by his Sax Sockette and the fifth by his Swinging Strings. Thus each department of the orchestra becomes a band of its own. To pick out one side only sounds unfair; nevertheless, the large band record of “Alexander's Ragtime Band” is good. The Modernaires vocal quartet sing specially written words which tell the life story of the tune and by means of ingenious recording we hear the song as it was played in its youth—*Brunswick O 2859-63*.

Making a Valve-tester

IN our issue dated February 24th we published a wiring diagram for the valve panel of this valve-tester. Two small draughtsman's errors occur in the wiring of this, and will be found on the octal valve-holder and on the holder immediately to the right of it. There was an additional contact on this latter holder which should not be there, and this is indicated by the broken lines on the corrected diagram shown herewith. The octal valve base should be wired as shown also in this diagram.

The rest of the connections are correct,

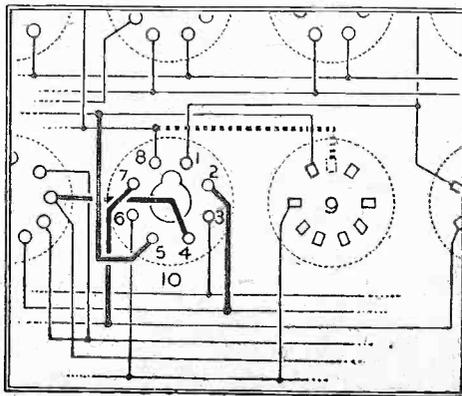

Corrected diagram of part of the valve-tester.

and although in one or two exceptional cases the filament sockets may not be those shown, these are so rare that the use of the separate panel would rectify the matter.—(F. D. L.).

RADIO CLUBS & SOCIETIES

Club Reports should not exceed 200 words in length and should be received First Post each Monday morning for publication in the following week's issue.

CLAYESMORE RADIO CLUB

Hon. Sec.: A. W. G. Wilson, Clayesmore School, Iwerne Minster, Dorset.

VERY little constructional work has been done this term, as most of the members are now seniors, and are finding themselves with plenty of work of another kind on their hands. However, a S.G.-Det.-Pen. mains set has been built by Cox, and although it has only, as yet, worked on gramo owing to the lack of a pair of coils, it should be working well shortly. The secretary has constructed a 3 1/2-watt quality amplifier for use with microphone and gramophone.

Other members of the club and the secretary have gained valuable knowledge in power amplifier practice while operating the school cinema.

A 15-25 watt amplifier is to be put under construction shortly for Speech Day, next term. It should be finished shortly after Easter.


Open to Discussion

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

Listening Contest for Club Members!

SIR,—I was at a local radio club meeting recently when one of the members suggested a listening contest between the club's members. As some of us know, there is a DX contest coming off soon in America, which would be ideal for such a purpose. I don't know whether any other club is

your invitation to put the matter "Open to Discussion," in your columns, I find it necessary to ask you to add a further instalment to my original letter. I do not wish to commence an argument in writing with your readers, but in view of Mr. H. W. Darvill's letter, published in March 2nd issue, I think that a few details will show that in the majority of cases published, it is not one of a S.W.L. exchanging with a S.W.L. as he suggests, or nomenclative errors.

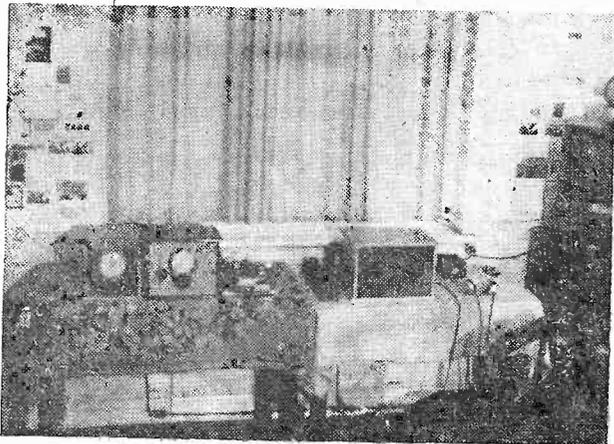

On the left is Mr. S.E. Janes's den—minus his transmitter.

On the right is seen Mr. G. B. Cotton, of Liverpool, in his radio room.



doing anything like this, but I think it would relieve the monotony, and provide an opportunity for trying out the new receivers which a lot of us have been building.

What do other club members think of the idea?—G. F. SWAYSLAND (Gravesend).

Readers' Dens

SIR,—I enclose a photo of my den taken on Saturday morning, March 2nd. It is interesting to compare this with the one appearing in the January 13th issue of PRACTICAL WIRELESS, and to note the difference resulting from a visit by the G.P.O. and the removal of my transmitter.—S. E. JANES (Croydon).

SIR,—I have received my B.L.D.L.C. certificate and am very pleased with it. I enclose a snap of my den, which may interest other readers. My RX is a straight three using an Eddystone coil, and the set runs off A.C. mains 230v. The aerial points due south and is 40ft. long, and 26ft. high.

Of late I have been experimenting with a frame aerial, and have had fair results. The first TX received was the Irish station testing on 31.27 m. Several others came through at good strength, but I could not listen long enough to pick up the call sign. In fact I did not think a frame aerial would be of any use on the short waves.

If James Stitt should happen to read this letter I would be glad to hear from him.

Wishing PRACTICAL WIRELESS much success in the future.—GEO. B. COTTON (Liverpool).

Exchanging Q.S.Ls.

SIR,—Referring to my letter, which you so kindly published in your issue of February 17th, 1940, on the "Exchanging of Q.S.Ls. by post," and bearing in mind

During the last 13 issues of PRACTICAL WIRELESS I have noted 18 letters on this Exchange business. Six of these only are S.W.Ls. offering to exchange with S.W.Ls., which I also agree is harmless, though at the same time is a little off the true line.

However, of these six, two offer to Q.S.L. 100 per cent. in return which cannot or should not be done by a S.W.L., for no "Ham" would call himself a S.W.L. in error. If he does make this mistake why does he not quote his call sign? Then again, I ask, can a Ham rightly send his Q.S.L. in exchange for a S.W.L. without having received anything, for the usual S.W.L. does not transmit.

Moreover, of the 18 cases quoted, 10 wish to send their S.W.L. cards not only to S.W.Ls. but A.As. and Hams in order to get a Q.S.L. in return. Out of these 12 I mention, 2 say they will Q.S.L. in return.

Now I think it would be much clearer if these "fans" who wish to Q.S.L. in return, would quote the call signs with their signatures and addresses, and if this was made a rule we should all know where we stand.

On these grounds I venture to say that if Mr. Darvill cares to examine his back issues of PRACTICAL WIRELESS he will conclude that 12 out of 18 readers could not make a nomenclative error as he suggests and I still contend that this Q.S.L. exchange business is not only a ramp but a dishonourable action in the view of genuine S.W.Ls., A.As. and Hams.

I strongly appeal to all those readers who conscientiously work at their RX, furnish genuine useful reports to all parts of the world, and who hope to get a Q.S.L. back for their trouble, to put their heads together with the help of our worthy editor to put a stop to this growing exchange business

with other than S.W.Ls., as in fact the Q.S.L. should not be used for other than verification of wireless reception of the other fellow's transmission.

I trust, Mr. Editor, that I have made the position as I see it, quite clear, and hope for your valuable support to maintain the value of a Q.S.L. used in the correct manner by authorised persons.—F. W. J. COOPER (Belmont, Middlesex).

[See note in *Thermion's Commentary*, page 5.—Ed.]

Correspondents Wanted

SIR,—I should like to correspond with any reader of your paper aged about 16-20 years who is interested in short-wave radio. My receiver, which is under construction, will be a 5-valve mains short-waver. I should like to take this opportunity of congratulating you on your excellent paper which I have only just

started reading.—J. M. GOYMOUR (24, Goring Road, Ipswich, Suffolk).

SIR,—I would like to correspond with a young reader of PRACTICAL WIRELESS who is interested in short-wave wireless.—D. E. PARRISH ("Goodwood," Hadnock Road, Monmouth).

Prize Problems

PROBLEM No. 391.

MARSHALL had a three-valve battery receiver operated from dry batteries. He decided to include auto-grid bias and obtained an appropriate resistance and condenser which he joined between his H.T. negative plug and the earth terminal of his set. When he switched on signals were very distorted, but in spite of verification he found that the resistance was of the correct value and was not defective. What was wrong? Three books will be awarded for the first three correct solutions opened. Entries must be addressed to The Editor, PRACTICAL WIRELESS, Geo. Newnes, Ltd., Tower House, Southampton Street, Strand, London, W.C.2. Envelopes must be marked Problem No. 391 in the top left-hand corner and must be posted to reach this office not later than the first post on Monday, March 18th, 1940.

Solution to Problem No. 390.

When Bradley connected the filaments in series he restricted the current through the entire filament circuit and accordingly the valves were all under-run. This would give the same effect as when using a run-down L.T. battery.

The following three readers successfully solved Problem No. 389 and books have accordingly been forwarded to them: F. Y. Fairhall, Canterbury Bell, Sandhurst, Kent; N. C. Hughes, 13, Broadway, Kettleby, Wellington, Shrops; T. Woodward, 50, Lillington Street, S.W.1.

LATEST PATENT NEWS

Group Abridgments can be obtained from the Patent Office, 25, Southampton Buildings, London, W.C.2, either sheet by sheet as issued on payment of a subscription of 5s. per Group Volume or in bound volumes price 2s. each.

Abstracts Published.

ELECTRICAL MUSICAL INSTRUMENTS.—Selmer and Co., Ltd., H., and Davis, B. No. 501685.

In a piano, with or without a soundboard, and having electro-static pick-up means feeding a loudspeaker, the pick-ups consist of screws 3 (Fig. 1) with flat plate-like heads 3a opposite each string C or set of strings sounding a note. In an upright, some of the screws 3 of the middle range of strings may be behind the strings. The screws 3 screw for adjustment into insulating strips 2b on the iron frame 1, or into a wooden bar mounted on the piano body, and are connected by a lead or a metal strip.

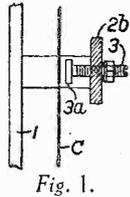


Fig. 1.

Reference has been directed by the Comptroller to U.S.A. Specification 2027074.

TRANSFORMERS; COUPLING COILS.—Michaelis, E. No. 507655.

In inductively coupled oscillatory circuits the coupling is adjusted without effecting detuning by movement of a magnetic dust core in relation to the windings. The

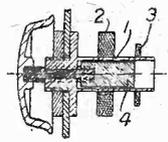


Fig. 2.

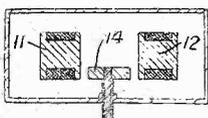


Fig. 4.

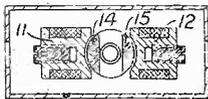


Fig. 5.

coils 2, 3, Fig. 2, of a back-coupled oscillator, for example, may be mounted on an insulating former 1 within which the whole of the core 4 or a part thereof is so moved in relation to the windings that any detuning arising from change in coupling is compensated by change in self inductance of the coil 2. In a modification in which a part only of the core is moved to effect a change in coupling, Fig. 3 (not shown), the remaining part is independently movable to serve as a "balancing pin." Fig. 4 shows the invention applied to a frequency filter of adjustable band width in which the coils are mounted on fixed cores 11, 12 and the movable part 14 is adjusted laterally. In an alternative arrangement the fixed cores are axially bored to receive independently and axially movable core parts. Fig. 5 shows another form in which movable core parts 14, 15 are mounted for rotation with respect to fixed parts 11, 12 carrying the windings.

CONVERTING.—Telefunken Ges. Fur Drahtlose Telegraphie. No. 504923.

In an arrangement for supplying a load such as a wireless receiver with A.C. from either a D.C. or an A.C. source and comprising a transformer and vibratory interrupter, the transformer primary is divided into two symmetrical parts L1, L2 which may be connected at will either through the interrupter P to a D.C. source a, b so as to function alternately, or directly to an A.C. source (Fig. 6). In the latter case, either one part alone or the two

parts in parallel may be used. The moving contacts of the interrupter are spring-mounted on a vibrating reed F, Fig. 7, so that they dwell on the fixed contacts and thus cause the current produced in the winding parts L1, L2, when the arrangement operates on a D.C. source, to be of rectangular wave form. Thus, when the arrangement operates on an A.C. source of a frequency, not more than half the frequency of the interrupter, the voltage produced in the secondary of the transformer is equal to that which is produced when the arrangement operates on a D.C. source of the same voltage as the R.M.S. value of the A.C. source. Symmetrical tappings g, h may be provided on the winding parts L1, L2 for adapting the arrangement to different voltages.

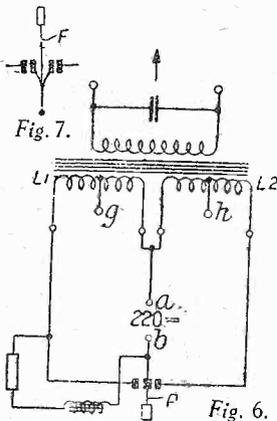


Fig. 6.

Reference has been directed by the Comptroller to Specifications 2824/08, [Class 38], 344, 948 and 359331.

NEW PATENTS

These particulars of New Patents of interest to readers have been selected from the Official Journal of Patents and are published by permission of the Controller of H.M. Stationery Office. The Official Journal of Patents can be obtained from the Patent Office, 25, Southampton Buildings, London, W.C.2, price 1s. weekly (annual subscription £2 10s.).

Latest Patent Applications.

- 3138.—Hazeltine Corporation.—Television synchronizing-signal separators. February 19th.
- 3139.—Hazeltine Corporation.—Television receiving-apparatus. February 19th.

Specifications Published.

- 518128.—Rudkin, E. P.—Wireless receiving system.
- 518031.—Standard Telephones and Cables, Ltd.—Indicator systems for wireless apparatus or the like.

Printed copies of the full Published Specifications may be obtained from the Patent Office, 25, Southampton Buildings, London, W.C.2, at the uniform price of 1s. each.

PRACTICAL MECHANICS HANDBOOK

By F. J. CAMM.

400 pages, 6/- or 6/6 by post from GEORGE NEWNES, LTD., Tower House, Southampton Street, Strand, W.C.2.

There's MONEY FOR YOU in Radio

We can train you for a well-paid position. Without interfering with your present occupation, you can study at home in your spare time and become a qualified Radio Engineer.

Radio Electricians, Mechanics, Service Engineers, Inspectors, Instructors and Technicians are urgently needed by Radio Firms and the Government, and the demand for such men will continue and increase.

There are also excellent opportunities for spare-time money-making.

Our Home-Study Courses are praised and recommended by leading Radio Authorities. Hundreds of students of all ages who are now in well-paid positions owe their success to our training. Many of them knew nothing about radio before they joined our College.

LOOK TO YOUR FUTURE. Even if you are satisfied with your present position, you cannot be sure of your future. Safeguard yourself against misfortune by becoming a trained man.

If you are liable for Military Service, send for details of our new Radio Mechanic's Superhet Course (write M.S. in top corner of coupon).

POST COUPON NOW and learn how you can get better pay or profitable spare-time work.

T. & C. RADIO COLLEGE
FAIRFAX HOUSE (F.W.),
HIGH HOLBORN, LONDON, W.C.1

(Post in unsealed envelope, 1d. stamp.)

Please send me free details of your Home-Study Radio Courses.

NAME

ADDRESS

P.W.

TAYLOR

PRECISION INSTRUMENTS

Our range includes:—

UNIVERSAL METERS

- 70 Ranges of A.C. and D.C. Volts and Amps, Ohms, Capacity, Inductance and Decibels. Strongly constructed, well-balanced Moving Coil Meter. Hand-calibrated for extreme accuracy.
- Model 80A. 2,000 O.P.V., AC/DC .. 11 Gns.
- „ 80B. 5,000 O.P.V., DC .. 13 Gns.
- „ 80C. 20,000 O.P.V., DC .. 15 Gns.
- 32 Ranges of A.C. and D.C. Volts, Amps, and Ohms. All-metal construction, incorporating Hand-calibrated Moving Coil Meter.
- Model 90. 1,000 O.P.V., AC/DC .. £8 15 0
- 17 Ranges D.C. Model 95. 1,000 O.P.V. £6 10 0

VALVE TESTERS

- Taylor Model 45 Valve Tester accurately checks all English, Continental and American Valves, from 0.25 milliamperes per volt and up to 24 MA/volt. Over 1,000 readings: 17 Valve Holders £13 2 6
- Portable Model £13 18 0
- Bench Model 13 Gns.
- Model 40 checks over 800 English and American Valves for slope, filament continuity, cathode, leakage and shorts.
- Standard Model £9 9 0
- Portable £9 19 0

SIGNAL GENERATORS

- Taylor Precision-Built, mains-operated Signal Generator, covers 0.5 to 3,000 metres, 100 kc. to 45 mc. in 6 bands, directly calibrated. Almost constant output: low harmonic content. MODELS FOR A.C., A.C.-D.C. or BATTERY OPERATION .. 11 Gns.

OSCILLOSCOPES

- These instruments use a 3-in. hard type Cathode Ray Tube, have separate built-in amplifiers for both the horizontal and vertical anodes, as well as a linear time base.
- Model 30 18 Gns.
- Model 35 (with frequency modulated oscillator) 22 Gns.

TAYLOR INSTRUMENTS ARE BRITISH MADE AND FULLY GUARANTEED.

Full particulars of any instrument sent on receipt of your name and address pinned to this advertisement.

TAYLOR ELECTRICAL INSTRUMENTS, LTD.
419-422, Montrose Avenue,
TRADING ESTATE, SLOUGH, BUCKS.

Phone: Slough 20001

NOTE NEW ADDRESS

Practical Wireless BLUEPRINT SERVICE

These Blueprints are drawn full size. Copies of appropriate issues containing descriptions of these sets can in some cases be supplied at the following prices which are additional to the cost of the Blueprint. A dash before the Blueprint Number indicates that the issue is out of print.

Issues of Practical Wireless ... 4d. Post Paid
 Amateur Wireless 4d. " "
 Wireless Magazine 1/3 " "

The index letters which precede the Blueprint Number indicates the periodical in which the description appears: Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.

Send (preferably) a postal order to cover the cost of the blueprint, and the issue (stamps over 6d. unacceptable) to PRACTICAL WIRELESS Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

PRACTICAL WIRELESS	No. of		
Date of Issue.	Blueprint.		
CRYSTAL SETS.			
Blueprints, 6d. each.			
1937 Crystal Receiver ..	PW71		
The "Junior" Crystal Set ..	PW94	27.3.38	
STRAIGHT SETS. Battery Operated.			
One-valve : Blueprints, 1s. each.			
All-Wave Unipen (Pentode) ..	PW31A		
Beginners' One-valver ..	PW85	19.2.38	
The "Pyramid" One-valver (HF Pen) ..	PW93	27.8.38	
Two-valve : Blueprint, 1s.			
The Signet Two (D & LF) ..	PW76	24.9.38	
Three-valve : Blueprints, 1s. each.			
Selectone Battery Three (D, 2 LF (Trans)) ..	PW10		
Sixty Shilling Three (D, 2 LF (RC & Trans)) ..	PW34A		
Leader Three (SG, D, Pow) ..	PW35	22.5.37	
Summit Three (HF Pen, D, Pen) ..	PW37		
All Pentode Three (HF Pen, D, (Pen), Pen) ..	PW39	29.5.37	
Hall-Mark Three (SG, D, Pow) ..	PW41	12.6.37	
Hall-Mark Cadet (D, LF, Pen, RC) ..	PW48	16.3.35	
F. J. Camm's Silver Souvenir (HF Pen, D (Pen), Pen) (All-Wave Three) ..	PW49	13.4.35	
Cameo Midget Three (D, 2 LF (Trans)) ..	PW51		
1936 Sonotone Three-Four (HF Pen, HF Pen, Westector, Pen) ..	PW53		
Battery All-Wave Three (D, 2 LF (RC)) ..	PW55		
The Monitor (HF Pen, D, Pen) ..	PW61		
The Tutor Three (HF Pen, D, Pen) ..	PW62	21.3.36	
The Centaur Three (SG, D, P) ..	PW64	14.8.37	
F. J. Camm's Record All-Wave Three (HF Pen, D, Pen) ..	PW69	31.10.36	
The "Colt" All-Wave Three (D, 2 LF (RC & Trans)) ..	PW72	18.2.39	
The "Rapid" Straight 3 (D, 2 LF (RC & Trans)) ..	PW82	4.12.37	
F. J. Camm's Oracle All-Wave Three (HF, Det., Pen) ..	PW78	28.8.37	
1938 "Triband" All-Wave Three (HF Pen, D, Pen) ..	PW84	22.1.38	
F. J. Camm's "Sprite" Three (HF Pen, D, Tet) ..	PW87	26.3.38	
The "Hurricane" All-Wave Three (SG, D, Pen, Pen) ..	PW89	30.4.38	
F. J. Camm's "Push-Button" Three (HF Pen, D (Pen), Tet) ..	PW92	8.9.38	
Four-valve : Blueprints, 1s. each.			
Sonotone Four (SG, D, LF, P) ..	PW4	1.5.37	
Fury Four (2 SG, D, Pen) ..	PW11	8.5.37	
Beta Universal Four (SG, D, LF, Cl. B) ..	PW17		
Nucleon Class B Four (SG, D (SG), LF Cl. B) ..	PW34B		
Fury Four Super (SG, SG, D, Pen) ..	PW34C		
Battery Hall-Mark 4 (HF Pen, D, Push-Pull) ..	PW46		
F. J. Camm's "Limit" All-Wave Four (HF Pen, D, LF, P) ..	PW67	26.9.36	
"Aome" All-Wave 4 (HF Pen, D (Pen), LF, Cl. B) ..	PW83	12.2.38	
The "Admiral" Four (HF Pen, HF Pen, D, Pen (RC)) ..	PW90	8.9.38	
Mains Operated.			
Two-valve : Blueprints, 1s. each.			
A.C. Twin (D (Pen), Pen) ..	PW18		
A.C.-D.C. Two (SG, Pow) ..	PW31		
Selectone A.C. Radiogram Two (D, Pow) ..	PW19		
Three-valve : Blueprints, 1s. each.			
Double-Diode-Triode Three (HF Pen, DDT, Pen) ..	PW23		
D.C. Ace (SG, D, Pen) ..	PW25		
A.C. Three (SG, D, Pen) ..	PW29		
A.C. Leader (HF Pen, D, Pow) ..	PW35C	7.1.39	
D.C. Premier (HF Pen, D, Pen) ..	PW35B		
Unique (HF Pen, D (Pen), Pen) ..	PW36A	28.7.34	
Armada Mains Three (HF Pen, D, Pen) ..	PW38		
F. J. Camm's A.C. All-Wave Silver Souvenir Three (HF Pen, D, Pen) ..	PW50	11.5.35	
"All-Wave" A.C. Three (D, 2 LF (RC)) ..	PW54		
A.C. 1936 Sonotone (HF Pen, HF Pen, Westector, Pen) ..	PW56		
Mains Record All-Wave 3 (HF Pen, D, Pen) ..	PW70		
Four-valve : Blueprints, 1s. each.			
A.C. Fury Four (SG, SG, D, Pen) ..	PW20		
A.C. Fury Four Super (SG, SG, D, Pen) ..	PW34D		
A.C. Hall-Mark (HF Pen, D, Push-Pull) ..	PW45		
Universal Hall-Mark (HF Pen, D Push-Pull) .. PW47			
SUPERHETS.			
Battery Sets : Blueprints, 1s. each.			
£5 Superhet (Three-valve) ..	PW40	5.6.37	
E. J. Camm's 2-valve Superhet ..	PW52		
Mains Sets : Blueprints, 1s. each.			
A.C. £5 Superhet (Three-valve) ..	PW43		
D.C. £5 Superhet (Three-valve) ..	PW42		
Universal £5 Superhet (Three-valve) ..	PW44		
F. J. Camm's A.C. Superhet 4 ..	PW59	31.7.37	
F. J. Camm's Universal £4 Superhet 4 ..	PW60		
"Qualitone" Universal Four ..	PW73	16.1.37	
Four-valve : Double-sided Blueprint, 1s. 6d.			
Push Button 4, Battery Model ..	PW95	22.10.38	
Push Button 4, A.C. Mains Model ..			
SHORT-WAVE SETS. Battery Operated.			
One-valve : Blueprint, 1s.			
Simple S.W. One-valver ..	PW88	23.12.39	
Two-valve : Blueprints, 1s. each.			
Midget Short-wave Two (D, Pen) ..	PW38A		
The "Fleet" Short-wave Two (D (HF Pen), Pen) ..	PW91	27.8.38	
Three-valve : Blueprints, 1s. each.			
Experimenter's Short-wave Three (SG, D, Pow) ..	PW30A	30.7.38	
The Prefect 3 (D, 2 LF (RC and Trans)) ..	PW63		
The Band-Spread S.W. Three (HF Pen, D (Pen), Pen) ..	PW68	1.10.38	
PORTABLES			
Three-valve : Blueprints, 1s. each.			
F. J. Camm's ELF Three-valve Portable (HF Pen, D, Pen) ..	PW65		
Parvo Flyweight Midget Portable (SG, D, Pen) ..	PW77	8.6.39	
Four-valve : Blueprint, 1s.			
"Imp" Portable 4 (D, LF, LF, (Pen)) ..	PW86	19.3.38	
MISCELLANEOUS.			
Blueprint, 1s.			
S.W. Converter-Adapter (1 valve) ..	PW48A		
AMATEUR WIRELESS AND WIRELESS MAGAZINE CRYSTAL SETS.			
Blueprints, 6d. each.			
Four-station Crystal Set ..	AW427	23.7.38	
1934 Crystal Set ..	AW444		
150-mile Crystal Set ..	AW450		
STRAIGHT SETS. Battery Operated.			
One-valve : Blueprint, 1s.			
B.B.C. Special One-valver ..	AW387		
Two-valve : Blueprints, 1s. each.			
Melody Ranger Two (D, Trans) ..	AW388		
Full-volume Two (SG, det, Pen) ..	AW302		
Lucerne Minor (D, Pen) ..	AW426		
A Modern Two-valver ..	WM409		
Three-valve : Blueprints, 1s. each.			
£5 5s. S.G.3 (SG, D, Trans) ..	AW412		
Lucerne Ranger (SG, D, Trans) ..	AW422		
£5 5s. Three: De Luxe Version (SG, D, Trans) ..	AW435	19.5.34	
Lucerne Straight Three (D, RC, Trans) ..	AW437		
Transportable Three (SG, D, Pen) ..	WM271		
Simple-Tune Three (SG, D, Pen) ..	WM327	June '33	
Economy-Pentode Three (SG, D, Pen) ..	WM337	Oct. '33	
"W.M." 1934 Standard Three (SG, D, Pen) ..	WM351		
£3 3s. Three (SG, D, Trans) ..	WM354	Mar. '34	
1935 £6 6s. Battery Three (SG, D, Pen) ..	WM371		
PTP Three (Pen, D, Pen) ..	WM389		
Certainty Three (SG, D, Pen) ..	WM393		
Minutube Three (SG, D, Trans) ..	WM396	Oct. '35	
All-Wave Winning Three (SG, D, Pen) ..	WM400		
Four-valve : Blueprints, 1s. 6d. each.			
65s. Four (SG, D, RC, Trans) ..	AW370		
2HF Four (2 SG, D, Pen) ..	AW421		
Self-contained Four (SG, D, LF, Class B) ..	WM331	Aug. '33	
Lucerne Straight Four (SG, D, LF, Trans) ..	WM350		
£5 5s. Battery Four (HF, D, 2 LF) ..	WM381	Feb. '35	
The H.K. Four (SG, SG, D, Pen) ..	WM384		
The Auto Straight Four (HF Pen, HF, Pen, DDT, Pen) ..	WM404	Apr. '38	
Five-valve : Blueprints, 1s. 6d. each.			
Super-quality Five (2 HF, D, RC, Trans) ..	WM320		
Class B Quadradyne (2 SG, D, LF, Class B) ..	WM344		
New Class B Five (2 SG, D, LF, Class B) ..	WM340		

Mains Operated			
Two-valve : Blueprints, 1s. each.			
Consoelectric Two (D, Pen) A.C. ..	AW403		
Economy A.C. Two (D, Trans) A.C. ..	WM286		
Unicorn A.C.-D.C. Two (D, Pen) ..	WM394		
Three-valve : Blueprints, 1s. each.			
Home Lover's New All-Electric Three (SG, D, Trans) A.C. ..	AW383		
Mantovani A.C. Three (HF, Pen, D, Pen) ..	WM374		
£15 15s. 1936 A.C. Radiogram (HF, D, Pen) ..	WM401	Jan '36	
Four-valve : Blueprints, 1s. 6d. each.			
All Metal Four (2 SG, D, Pen) ..	WM326	July '33	
Harris' Jubilee Radiogram (HF Pen, D, LF, P) ..	WM386	May '35	
SUPERHETS.			
Battery Sets : Blueprints, 1s. 6d. each.			
Modern Super Senior ..	WM375		
'Varsity Four ..	WM395	Oct. '35	
The Request All-Waver ..	WM407	June '36	
1935 Super-Five Battery (Superhet) ..	WM379		
Mains Sets : Blueprints, 1s. 6d. each.			
Heptode Super Three A.C. ..	WM359	May '34	
"W.M." Radiogram Super A.C. ..	WM366		
PORTABLES.			
Four-valve : Blueprints, 1s. 6d. each.			
Holiday Portable (SG, D, LF, Class B) ..	AW393		
Family Portable (HF, D, RC, Trans) ..	AW447		
Two H.F. Portable (2 SG, D, QP21) ..	WM363		
Tyers Portable (SG, D, 2 Trans) ..	WM367		
SHORT-WAVE SETS. Battery Operated.			
One-valve : Blueprints, 1s. each.			
S.W. One-valver for America ..	AW429	15.10.38	
Rome Short-Waver ..	AW452		
Two-valve : Blueprints, 1s. each.			
Ultra-short Battery Two (SG, det, Pen) ..	WM402	Feb. '36	
Home-made Coil Two (D, Pen) ..	AW440		
Three-valve : Blueprints, 1s. each.			
World-ranger Short-wave 3 (D, RC, Trans) ..	AW355		
Experimenter's 5-metre Set (D, Trans, Super-regen) ..	AW433	30.6.34	
The Carrier Short-waver (SG, D, P) ..	WM390	July '35	
Four-valve : Blueprints, 1s. 6d. each.			
A.W. Short-wave World-beater (HF Pen, D, RC, Trans) ..	AW436		
Empire Short-waver (SG, D, RC, Trans) ..	WM313		
Standard Four-valve Short-waver (SG, D, LF, P) ..	WM383	22.7.39	
Superhet : Blueprint, 1s. 6d.			
Simplified Short-wave Super ..	WM397	Nov. '35	
Mains Operated			
Two-valve : Blueprints, 1s. each.			
Two-valve Mains Short-waver (D, Pen) A.C. ..	AW453	13.1.40	
"W.M. Long-wave Converter" ..	WM380		
Three-valve : Blueprint, 1s.			
Emigrator (SG, D, Pen) A.C. ..	WM352		
Four-valve : Blueprint, 1s. 6d.			
Standard Four-valve A.C. Short-waver (SG, D, RC Trans) ..	WM391	Aug. '35	
MISCELLANEOUS.			
S.W. One-valve Converter (Price 6d.) ..			
Enthusiast's Power Amplifier (1/6) ..	AW329		
Listener's 5-watt A.C. Amplifier (1/6) ..	WM387		
Radio Unit (2v.) for WM392 (1/-) ..	WM392	Nov. '35	
Harris Electrogram battery amplifier (1/-) ..	WM398		
De Luxe Concert A.C. Electrogram (1/-) ..	WM399		
New style Short-wave Adapter (1/-) ..	WM403	Mar. '36	
Trickle Charger (6d.) ..	WM388		
Short-wave Adapter (1/-) ..	AW462		
Superhet Converter (1/-) ..	AW456		
B.L.D.L.C. Short-wave Converter (1/-) ..	AW457		
Wilson Tone Master (1/-) ..	WM405	May '36	
The W.M. A.C. Short-wave Converter (1/-) ..	WM406	June '36	

In reply to your letter

Auto-grid Bias

"I wish to fit auto-grid bias as recently described in your pages but am doubtful about one point. In my set H.T.— leads to a fuse-bulb, which in turn is anchored to the metal chassis. Will this affect the scheme in any way? To put it another way, am I right in assuming that the resistor would be in parallel with the fuse-bulb, and would this be in order?"—E. J. W. (Liverpool, 4).

THE bias resistor must not be in parallel with the fuse. In your case you must disconnect the fuse-bulb holder from the chassis and connect it instead to one side of the bias resistor and condenser. The other side of the resistor and condenser is then joined direct to the chassis. The grid return lead, that is, the grid leak or G.B. terminal of the L.F. transformer, is then connected to the junction of the fuse and bias resistor.

Resistance Wattage Rating

"I am fitting up a small mains unit and am rather doubtful regarding the wattage of the two resistors which I have to include for H.T. dropping. Can you tell me how to work out the rating so that I shall obtain the correct types of component and avoid burning out?"—A. F. (Amersham).

THE wattage of a resistor is calculated from the current which flows through it and therefore your first task is to ascertain the current at each part of your circuit. You can do this with a milliammeter connected in series when using a battery supply. The value of the resistor is then calculated by taking the voltage to be dropped and dividing this by the current in milliamps and multiplying the answer by 1,000. The wattage is then calculated in either of two ways. Firstly, you can multiply the current by the voltage dropped across the resistor, or you can multiply the resistance in ohms by the current squared. In each case the current is expressed in amps., 1 milliamp being .001 amps.

Doublet Aerial

"I wish to put up a doublet receiving aerial for use mainly on 30 metres. Could you give me some measurements for a horizontal aerial of this type? I understand that it will also operate on 15 metres and multiples of the fundamental, and I should be glad if you would confirm this."—J. H. (Birmingham).

THE exact measurements need not be rigidly adhered to as they will be in odd inches. We suggest you try an arrangement consisting of two lengths of 25ft. of standard stranded wire, with a 6in. supporting rope in the centre. Each end of each wire must, of course, be well insulated. From the centre ends of the two wires take a twisted leader to the receiver, and ordinary flex may be used for this purpose. The aerial will operate quite well on 15 metres and so on, the efficiency dropping off below 15 metres. Further

details regarding short-wave aerials will be found in our new Short-Wave Manual, price 5s.

Battery Connections

"I wonder if you have ever published any hint or suggestion for simplifying battery connections? I have a four-valve battery set which has four separate H.T. positive connections, and one negative connection, and I use a multi-cable battery cord. Unfortunately, one of the plugs is always coming out, and as the battery is underneath the set in a cupboard I find it awkward when getting no signals to have to grope down and find the battery and see which plug is out. I wonder if you can assist me, therefore, to overcome this little difficulty?"—L. E. R. (Watford).

RULES

We wish to draw the reader's attention to the fact that the Queries Service is intended only for the solution of problems or difficulties arising from the construction of receivers described in our pages, from articles appearing in our pages, or on general wireless matters. We regret that we cannot, for obvious reasons—

- (1) Supply circuit diagrams of complete multi-valve receivers.
- (2) Suggest alterations or modifications of receivers described in our contemporaries.
- (3) Suggest alterations or modifications to commercial receivers.
- (4) Answer queries over the telephone.
- (5) Grant interviews to querists.


A stamped addressed envelope must be enclosed for the reply. All sketches and drawings which are sent to us should bear the name and address of the sender. Requests for Blueprints must not be enclosed with queries as they are dealt with by a separate department. Send your queries to the Editor, PRACTICAL WIRELESS, George Newman, Ltd., Tower House, Southampton Street, Strand, London, W.C.2. The Coupon must be enclosed with every query.

THE trouble should not arise if you use good plugs. The standard split plug may be opened with a penknife blade so that it fits tightly, although perhaps you have obtained the solid type of plug which is intended for a slotted socket, not the solid socket found on batteries. The only hint we can offer for battery connections is to mount a strip of ebonite near the set, and connect the leads to this, making the strip with plugs and fitted sockets to the receiver so that the entire strip may be plugged in when battery connections are needed. This saves taking out each plug separately when tests are being carried out, but your trouble is undoubtedly due to the unsuitability of the plugs you are using.

Unusual Components

"I have recently had a small set given to me and I have dismantled it to use up the parts. I am familiar with most of them, but there are two items which I have never seen before and which I cannot understand. One is a small thing like a hollow cone with wires at each end and it is enamelled. It is about 3/8in. in diameter and 1/2in. overall length. The other is a small, bell-shaped metal thing with a rubber across one end,

(Continued on following page.)

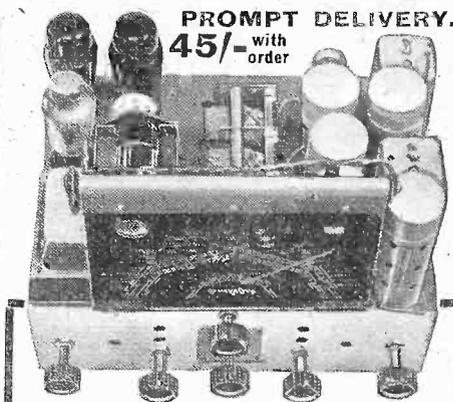

PROMPT DELIVERY. 45/- with order

PASSED A.I. BY EXPERTS!

MODEL 8810 (Illustrated) "SUPER HET-STRAIGHT" 10-valve High Fidelity Radiogram chassis. All-wave, incorporating 2 independent circuits, Superheterodyne and Straight, having R.F. pre-amplifier, R.C. coupled push-pull Triode output capable of handling 8 watts. CASH PRICE £13.4.0 or WITH ORDER 45/- and 10 monthly payments of 29/-.

ARMSTRONG QUALITY CHASSIS

Advanced design includes many refinements usually found only in most expensive sets.

★ WRITE FOR Full Specifications, Price Lists and Most Favourable Terms for full 1940 Armstrong Range.

SUNBEAM Electric SHAVEMASTER with the new '475' Head gives a perfect shave. 100-250 V., A.C. or D.C., 8/- post free, or 10/- down and 8 monthly payments of 10/-.

★ WE SUPPLY on most favourable terms all well-known Sets, Speakers, Valves, etc., domestic Electric Equipment. Cash or C.O.D. orders sent by return.



All communications to enquire on address— "WINDEN," ARDINGLY RD., BALCOMBE, SUSSEX

Would get it QUICKER and on BETTER TERMS from L.R.S.



FOR THE RADIO SERVICE MAN, DEALER AND OWNER

The man who enrolls for an I. C. S. Radio Course learns radio thoroughly, completely, practically. When he earns his diploma, he will KNOW radio. We are not content merely to teach the principles of radio, we want to show our students how to apply that training in practical, every-day, radio service work. We train them to be successful!

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 94A, International Buildings, Kingsway, London, W.C.2.

Please explain fully about your instruction in the subject marked X.

- Complete Radio Engineering
- Complete Radio
- Radio Service Engineers
- Elementary Radio
- Television

If you wish to pass a Radio examination, indicate it below.

- Inst. of Wireless Technology
- P.M.G. Certificate for Wireless Operators
- Provisional Certificate in Radio Telephony and Telegraphy for Aircraft
- City and Guilds Telecommunications

Name.....Age.....

Address.....

IN REPLY TO YOUR LETTER

(Continued from previous page.)

and there are no tags or wires attached to it. I should be glad if you could help me to identify these items."—J. G. T. (Kentish Town).

ALTHOUGH the descriptions are brief, we think we identify the two components as a small ceramic type fixed condenser and a grid-bias cell. We imagine that the set is of American origin, and the small condenser would have a capacity of a few mmfd. The other item is a Mallory grid bias cell, which is generally mounted in a small clip near a grid terminal and applies a bias of 1.5 volts or thereabouts.

American Valve Data

"I have one or two American valves and I am not certain regarding the connections. Is there any book available in this country which gives the connections and data relative to various American valves? If so, could you tell me where I could obtain one?"—J. M. (Ilfracombe).

DATA and base connections for a large number of American valves may be found in the back of the catalogue issued by the Premier Radio Company, price 6d. Messrs. Holliday & Hemmerdinger, of 74-78, Hardman Street, Manchester, 3, can also supply the receiving valve manual issued by the Radio Corporation of America, and this gives the characteristics and connections of all their valves, which are standardised throughout America.

REPLIES IN BRIEF

The following replies to queries are given in abbreviated form either because of non-compliance with our rules, or because the point raised is not of general interest.

L. R. (Bangor). The transformer is specially designed for the purpose and will therefore be quite satisfactory.

H. T. E. (York). The article in this issue will answer all the points raised by you.

B. K. (Easingstone). A pre-set would be preferable, and you should try and obtain one of the type which has a locking adjustment so that the setting may be made permanent.

T. G. (E.C.3). The Eddystone component would be perfectly suitable. Make certain that you obtain one of the latest types, as they have been modified recently.

R. J. (Boxmoor). 1.5 volts will be insufficient. Try at least 6 volts. A good G.B. battery will be adequate from the current point of view.

E. S. (Southwark). 36 S.W.G. enamel wire will be suitable at about 2,000 turns. Be careful with the insulation.

L. R. (Bletchley). Ordinary grease is unsuitable. Use a graphite preparation and use it sparingly.

S. P. (Cambridge). We regret that we cannot grant you space in our editorial columns, and can only suggest that you insert a small advertisement. We would be inundated with similar requests if we permitted our editorial space to be used for the purpose outlined in your letter.

S. J. B. (Bristol, 5). We refer you to our blueprint list published weekly.

W. A. (Riverstown). Perhaps now that the valve tester has been completed, the various details about which you were uncertain have been cleared up. See especially the final article on the subject.

W. J. (Wellingboro'). We regret that we cannot supply a blueprint of a receiver utilising the coil in question.

M. H. B. (Rugby). The coils are not now on the market, but standard 6-pin plug-in coils could be substituted.

L. W. (Sparkbrook). The unit is probably overloaded by your 5-valve set. The unit is intended primarily for addition to a simple two or three-valve set.

G. J. (Stepney). Class B usually does not require negative grid bias, and, therefore, perhaps you are trying to use the set in the wrong manner. We cannot deal fully with your query without further details.

L. A. D. (E.B.). There is no frequency to D.C. mains and therefore we think you are under some misapprehension regarding your supply. If the mains are 50 cycles we think you will find they are A.C. In any case, the mains transformer will be burnt out if connected to a D.C. supply.

The coupon on page iii of cover must be attached to every query.

Classified Advertisements

ADVERTISEMENTS are accepted for these columns at the rate of 2d. per word (minimum charge 2/- each paragraph). Series discounts of 5 per cent. for 13, 10 per cent. for 26 and 15 per cent. for 52 insertions are allowed. All advertisements must be prepaid.

EACH paragraph will commence with the first word printed in bold face capitals. Additional words in bold face capitals are charged at 4d. per word.

ALL communications should be addressed to the Advertisement Manager, "Practical Wireless," Tower House, Southampton Street, London, W.C.2.

CABINETS

A CABINET for Every Radio Purpose. Surplus Cabinets from noted makers under cost of manufacture. Radiogram Cabinets from 30/-. Undrilled table, console and loudspeaker cabinets from 4/6. Inspection invited.

H. L. SMITH AND CO., LTD., 289, Edgware Road, W.2. Tel.: Pad. 5891.

COMMUNICATION RECEIVERS

THE famous HALLICRAFTER SX23, released by the makers only in July, 1939, can still be supplied by Webb's Radio at

PRE-WAR PRICES. We fortunately had good supplies delivered in August. NO price increase on present stock of this model only, £35 10s., H.P. terms available. Write for descriptive booklet.—P. Webb's Radio, 14, Soho Street, London, W.1. Phone: Gerrard 2089.

CONVERTERS

E.D.C. Rotary Converter, 200-250 D.C. to 200-250 A.C. 120 watts in silence, cabinet with filter, perfect £5/15/-, 180-watt ditto, £7/15/-.—Johnson Engineering, 80, Great Portland Street, W.1.

LITERATURE

NEW Edition. American Amateur Relay League Handbook. 500 pages of up-to-the-minute technical information, 7/- post free. 1940 Jones Handbook; approximately 700 pages dealing with every aspect of Short-wave Radio, 8/6, post free.—Webb's Radio, 14, Soho St., London, W.1. Phone: Gerrard 2089.

LOUDSPEAKER REPAIRS

LOUDSPEAKER repairs, British, American, any make. 24-hour service, moderate prices.—Sinclair Speakers, Pulteney Terrace, Copenhagen Street, London, N.1.

REPAIRS to moving coil speakers. Cones/coils fitted or rewound. Fields altered or wound. Prices quoted, including eliminators. Pick-ups and speaker transformers rewound, 4/6. Trade invited. Guaranteed satisfaction. Prompt service.

L.S. Repair Service, 5, Balham Grove, London, S.W.12. Battersea 1321.

MISCELLANEOUS

BE TALLER!! Inches put you Miles Ahead!! Details Gd. stamp.—Malcolm Ross, Height Specialist, Scarborough.

MORSE EQUIPMENT

FULL range of Transmitting Keys, Practice Sets, Oscillators, Recorders and other Radio Telegraph Apparatus, designed and manufactured by T. R. McElroy, World's Champion Telegraphist. Sole distributors: Webb's Radio, 14, Soho Street, London, W.1. Phone: Gerrard 2089.

MORSE TRAINING

WIRELESS Code Courses. "Book of Facts" Free.—Candler System Co. (L.O.), 121, Kingsway, London, W.C.2.

MORSE Code easily learnt by gramophone records. All speeds 2-15 words per minute. Full particulars. Stamp.—Masters, Forest Way, Pound Hill, Crawley.

NEW CHASSIS

ARMSTRONG CO. recommending the following economically priced Radio Chassis for good quality reproduction.

ARMSTRONG Model AW38.—8-valve All-wave Radio-gram chassis, incorporating the latest circuit, including 6 watts push-pull output. Price £8/8/0 + 5% war increase.

Armstrong Co. have many other models of equal interest, please write for catalogue. Armstrong Manufacturing Co., Warrlers Rd., Holloway, London, N.5.

NEW LOUDSPEAKERS

3,000 Speakers from 6/6 each, P.M. and energised 4in. to 14in., including several Epoch 18in.—Sinclair Speakers, Pulteney Terrace, Copenhagen Street, London, N.1.

PUBLIC APPOINTMENTS

AIR MINISTRY.

AERONAUTICAL INSPECTION DIRECTORATE. Vacancies exist for unestablished appointments as Examiners in the General Engineering and W/T and Instrument Branches.

QUALIFICATIONS.

All candidates must have good general education, be able to read drawings, understand specifications, use micrometers and other measuring instruments.

(a) Applicants for the General Engineering Branch must have had practical experience in an engineering works. An elementary knowledge of materials testing is desirable.

(b) Applicants for the Instrument Branch must have knowledge of physics and training in light engineering or instrument making. Candidates with knowledge of optical instruments are also required.

(c) Applicants for the W/T Branch must have practical knowledge of W/T and electrical equipment with technical training in radio communication equal to City and Guilds final examination standard.

APPLICATIONS from candidates previously interviewed and declared unsuccessful will be considered provided the necessary additional experience has been gained.

ACCEPTED candidates will undergo a period of training in inspection as applied to the above subjects, not exceeding three months, and will be paid £3 10s. 0d. weekly during training. Subsistence allowance of £1 5s. 0d. weekly during training is payable to married men normally residing outside the training area. On successful completion of training, candidates will be appointed as Examiners at a salary of £246 9s. 0d. per annum (payable monthly, in arrear) if service is satisfactory, and must be prepared to serve in any part of the United Kingdom.

NORMAL age limits 25 to 55.

CANDIDATES should indicate on their applications for which vacancy they wish to be considered—a, b or c.

APPLICATION must be made on Form 786, copies of which can be obtained on application, by postcard only, to: The Inspector-in-Charge, A.I.D. Training School (I.C.S./REC. 52), Brandon Steep, Bristol, 1.

RADIO MAP AND GLOBE

WEBB'S Radio Map of the World, enables you to locate any station heard. Size 40" by 30" 2 colour heavy Art Paper, 4/6. Limited supply on Linen, 10/6. **WEBB'S** Radio Globe—superb 12" full-colour model. Radio prefixes, zones, etc. Heavy oxidised mount. Post Paid, 27/6.—Webb's Radio, 14, Soho Street, London, W.1. Phone: Gerrard 2089.

RECEIVERS AND COMPONENTS

SOUTHERN Radio's Bargains.

ALL Guaranteed. Postage Extra. 5/- Parcel of useful Components, comprising Condensers, Resistances, Volume Controls, Wire, Circuits, etc. Value 25/-, 5/- per parcel.

15/- Service Man's Component Kit. Electrolytic Condensers, Volume Controls, Resistances, Tubular, Mica, Paper Condensers, Valve Holders, etc. 120 articles contained in strong carrying case, 9" x 7" x 7", 15/- the Kit.

21/- Small Trader's Parcel of Components. 150 Articles comprising all types Condensers, Valve Holders, Resistances, Chokes, Coils, Wire, etc. Value 85/-, 21/- the parcel.

5/- 100 Wire-end Resistances, assorted capacities. 1 and 1 watt, 5/- per 100.

ORMOND Loud-speaker Units, 2/6; Crystal Sets, 5/6; Westectors Type W2, 2/6; Crystal Detectors, 2/-; Crystals, 6d.; Marconi V24 Valves, 9d.

2/- Tool or Instrument Carrying Cases, ex Government Stock; Wood, 9" x 7" x 7", 2/-.

SOUTHERN Radio, 46, Lisle Street, London, W.C. Gerrard 6653.

5/- Bargain parcel comprising Speaker Cabinet, 2 Drilled Chassis, condensers, resistances and many other useful components. Worth £2. Limited number. Postage 1/-.—Bakers Sellhurst Radio, 75, Sussex Road, South Croydon.

BANKRUPT Bargains. Brand new 1939 models, makers' sealed cartons, with guarantees, at less 40 per cent. below listed prices; also Midgets, portables, car radio. Send 1/4d. stamp for lists.—Radio Bargains, Dept. P.W., 26L-3, Lichfield Road, Aston, Birmingham.

RADIO Exchanges. Wanted good second-hand radio sets in exchange for brand new 1939/40 models leading makes with guarantees and cash adjustment. Send 1/4d. stamp for list of makes. Radio Exchanges, 610, Kingsbury Road, Erdington, Birmingham.

RECEIVERS AND COMPONENTS

AMAZING offer. 5-valve A.C. all-wave superhet. chassis. Latest Mullard valves: T.H.4.B., V.P.4.B., T.D.D.4., P.E.N.A.4., L.W.4/350V. Ranges: short-wave 16-18 metres. Med-wave 200-560 metres. Long-wave 300-2,200 metres. Size of chassis, 14 1/2" long, 7 1/2" deep; height over all, 8 1/2". Control tuning at side, volume on/off at side, wave change. Provision for pick-up. Complete with valves and knobs, £4/17/6. Special speaker, 1,500 ohms field, 10/6.

RICE-KELLOGG Senior 12" moving coil speakers, 20 watts, 1,000 ohms, 11 ohms speech coil. Without speech transformer, 32/6; with transformer tapped 3,000 ohms and 7,000 ohms, 35/-.

GRAMPIAN 10" 10 watt, 2,500 ohm energised speaker. Heavy cast frame, 15/- each. With heavy-duty pentode speech transformer, 17/6 each. Heavy-duty speech transformers, pentode matching, 2/11 each.

ROTARY converters, complete with smoothing and suppression, 6v. or 12v. input, 240v. 40 m.a. output, 17/6.

PLESSEY 2-gang straight condensers, 1/6 each. Ditto, 3-gang, 2/- each.

POLAR 100,000 volume controls, with S.P. switch, 1/6 each. Metal chassis drilled 15" x 6" x 1 1/2" and 1 1/2" x 8" x 2 1/2", 1/6 each. Push back wire, 12yds. 1/-.

ROLA P.M. speakers, latest type 7 1/2" cone with pentode transformer, boxed, 14/6 each. Clock-faced dials, 5" x 3 1/2", with printed 3-wave scale, ox-copper escutcheons and glass, 3/6 each. Ditto, less escutcheons, 2/6 each. Horizontal dials, with plain scale 7 1/2" x 3 1/2" and pointer, 1/- each. 33yds. 3-way screened cable, 1/6.

PLESSEY mains transformers, 350-0-350, 90 m.a. 4v. 2.5 amps., 4v. 6 amps., 8/6 each.

FILAMENT transformers, input 200-250v., output 4v. 4 amps., 4v. 6 amps., 4/11 each.

G.E.C. mains transformer. American windings, 350-0-350v., 65 m.a., 5v. 2 amps., 6.3v. 2.5 amps. Suitable for replacements in G.E.C. models, 5/0 each. 24 mfd. can type electrolytics, 450v. working, 1/- each.

TRANSFORMERS.—Bobbins (less laminations), 350-0-350—90 m.a. 4v. 2 amps., 4v. 4 amps., 1/6.

CHASSIS mounting valve holders, American, 4-, 5-, 6-, and 7-pin, 4d. each. Octals 6d. each. Locals 10d. each. 7-pin English type, 3d. each.

POLAR N.S.F. 1 watt resistances, 4d. each, 3/9 dozen. All sizes up to 2 meg.

WEARITE mains transformers, R.C.B. type, 350-0-350v. 80 m.a., 5v. 2 amps., 6.3v. 5 amps., 6/11 each. Type R.C.1, 250-0-250v. 80 m.a., 4v. 2.5 amps., 4v. 4 amps., 9/11 each. Type R.C.2, 350-0-350v. 120 m.a., 4v. 2.5 amps., 4v. 4 amps., 12/6 each. Type R.C.3, 350-0-350v. 150 m.a., 4v. 2.5 amps., 4v. 2 amps., 4v. 4.5 amps., 15/- each. Type R.C.4, 500-0-500 v. 150 m.a., 4v. 2 amps., 4v. 2.5 amps., 4v. 2.5 amps., 4v. 5.6 amps., 21/- each. Type R.C.5, 100 watt auto. step-up or step-down, 100-110v., 200-250v., 12/6 each. All windings centre-tapped inputs, 200-250v.

WEARITE 110 k/c I.F. transformers, 1/- each.

AMERICAN C.T.S. volume controls, finest made, divided spindles, length 2 1/2" with switch, 2,000, 5,000, 10,000, 25,000, 100,000, 250,000, 500,000 and 1 meg., 2/6 each. Wire-wound 5 watt (less switch), 2,000, 5,000, 10,000, 20,000, 25,000 ohms, 2/- each.

B.I. wire-end type, bias electrolytics, 50 mfd. 12v., 1/6 each. 50 mfd. 50v., 2/- each. Tubular wire-end non-inductive paper, all sizes up to 0.1. 5d. each, 4/9 dozen.

PLESSEY energised speakers, 6" cone, 2,500 and 1,500 ohm field, 5/11 each.

MAINS units (standard telephones), fitted in metal safety cases, A.C. mains, input 200-250v., output 240v. 40 m.a., less valve (any type 350v. valve rectifier), 5/6 each.

SPEAKER cabinets finished black rexine, circular fret, metal grill, size 8 1/2" x 9 1/2" x 4 1/2", 4/6 each.

MEDIUM and long-wave iron-cored coil unit with valve holder and sundry resistances, 6d. each (no circuit).

SPECIAL .01 and .25 tubulars, wire ends, mixed only, 4/6 dozen (not less). Special mixed tubulars, useful sizes, our selection, 2/6 dozen.

BATTERY output pentodes, well-known make, 3/11 each.

BATTERY double diode triode, well-known make, 3/6 each.

RAYTHEON first-grade valves, largest stockists, all types in stock, including glass series, glass octal series, metal series, bauton series, single-ended metal series, and resistance tubes, all at most competitive prices; send for valve lists. Please write your address in block letters. All orders must include sufficient postage to cover. Hours of business: 9 a.m.—6 p.m. weekdays, Saturdays 9 a.m.—1 p.m.

RADIO CLEARANCE, LTD., 63, High Holborn, London, W.C.1. TELEPHONE: HOLborn 4631.

BANKRUPT Bargains. Please state requirements for quotation. Portables, dry and accumulator types A.C. and A.C./D.C. mains sets up to 10 valves. 10v. chassis all-wave with speaker and valves, £6/17/6. All types of valves and service goods.—Butlin, 6, Stamford Avenue, Brighton.

RECEIVERS AND COMPONENTS

COULPHONE Radio. Ormskirk. Will all clients please note new prices of Collaro Motors. These are due to manufacturers' price increases.

COULPHONE Radio, 22, Grimsshaw Lane, Ormskirk, Collaro A.C. Motors, 12" turntable, 27/6; with pick-up, 42/6. Rola G.12 energised speakers, 52/6, P.M., 65/- Brand new goods. 14d. stamp list.

LONDON Central Radio Stores, 23, Lisie Street, W.C.2. Gerrard 2969.

PHILIPS Step-down transformers, input 200-240 volts, output 6 volts, 3 amps., 2/9 each. B.I. Condensers 4 mfd., 450 volts working, resin oil filled, 3/3 each: 25 mfd., 1,000 volt working, 2/3 each: 1 mfd. ditto, 2/3. Valves, S.P.210, 4/3, Universal Pentode 35/20, 4/3 each.

EX-G.P.O. Multi-Contact Relays used in automatic exchanges, new condition, suitable for automatic tuning. Complete with contacts, 2/3, post free.

SCRAP your H.T. battery with Mallory vibrator converter, 12v. 150v., 30m.a., 18/9; listed £5/5/0. Or Genomotor, 12v. 250v., 50m.a., 25/- Postage 1/3.—Aeronautical Radio, 47, River Road, Littlehampton.

VAUXHALL Skeleton metal rectifiers, HT10, 11/-; HT9, 9/- Valveholders, 7-pin, 6d.; 5-pin, 5d. Volume controls, 2/-; with switch, 3/-.

VAUXHALL T.C.C. cardboard containers: 8 mfd. 500 v., 2/-; 6 plus 4 mfd. 350 v., 1/9; 50 mfd. 50 v., 1/9. Rola sin. P.M. speaker with transformer, 14/9. Other sizes in stock.

VAUXHALL Bar type condensers, straight 0.0005 mfd., 2-gang, 6/6; 3-gang, 8/6. Full-vision drives, station names, 6/-.


VAUXHALL Iron-cored coils on base with switch, terminals, circuit, 2-gang, 12/6; 3-gang, 19/6. 1-watt resistors, 4d.

VAUXHALL Utilities, 163a, Strand, London, W.C.2. Write for free list.

SCIENTIFIC SOCIETIES

R.S.G.B. reduced war-time subscriptions. Details and current issue "T. and R. Bulletin." Is.—10, Ashridge Gardens, London, N.12.

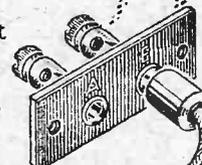STRIPS
Chassis socket
STRIPS
and **PANELS**
for all
purposes.



GLIX

British Mechanical Productions Ltd.,
1, Church Road, Leatherhead, Surrey.

"ENGINEERING OPPORTUNITIES" FREE!



This unique Hand-book shows the easy way to secure A.M.I.C.E., A.M.I.Mech.E., A.M.I.E.E., A.M.I.A.E., A.M.I.W.T., A.M.I.R.E., and similar qualifications. **WE GUARANTEE—"NO PASS—NO FEE."** Details are given of over 150 Diploma Courses in all branches of Civil, Mech., Elec., Motor, Aero, Radio and Television Engineering, Building, Government Employment, etc.

Write for this enlightening Hand-book to-day FREE and post free. **British Institute of Engineering Technology,** 409, Shakespeare House, 17, 18, 19, Stamford Place, W.1.

FREE ADVICE BUREAU COUPON

This coupon is available until March 23rd, 1940, and must accompany all queries and hints.

PRACTICAL WIRELESS, 16/3/1940.

PREMIER RADIO

Special Offer of Record Auto-Changer Units for A.C. Mains by famous manufacturer. Play 8 records. Latest type Magnetic Pick-up, Auto-stop, Start and Rejector. Limited number only at £4/19/6, Carriage Paid.

Special Offer of Dual Rang Screened Coils by well-known manufacturer. Aerial or H.F. coil. Accurately matched suitable Band-Pass. Medium and long-wave operation. Complete with full diagrams, 2/9 each.

PREMIER SHORT-WAVE KITS for OVERSEAS NEWS

Incorporating the Premier 3-Band S.W. Coil. 11-90 Metres without coil changing. Each Kit is complete with all components, diagrams and 2-volt valves. 3-Band S.W. 1-Valve Kit, 14/9. 3-Band S.W. 2-Valve Kit, 22/6.

DE LUXE S.W. KITS

Complete to the last detail, including all Valves and coils, wiring diagrams and lucid instructions for building and working. Each Kit is supplied with a steel Chassis and Panel and uses plug-in coils to tune from 13 to 170 metres.

- 1 Valve Short-Wave Receiver or Adaptor Kit 20/-
- 1 Valve Short-Wave Superhet Converter Kit 23/-
- 1 Valve Short-Wave A.C. Superhet Converter Kit 26/3
- 2 Valve Short-Wave Receiver Kit 28/-
- 3 Valve Short-Wave Screen Grid and Pentode Kit 68/-

REPLACEMENT VALVES FOR ALL SETS

EUROPA MAINS VALVES. 4 v., A.C. Types, A.C./H.L., A.C.L., A.C./S.G., A.C./V.-M.S.G., A.C./H.P., A.C./V.H.P. (5-pin), all 5/3 each. A.C./H.P., A.C./V.H.P. (7-pin), 7/6; A.C./Pens-I.H., 7/6; A.C./P.X.4, 7/3; Oct. Freq. Changers, 8/6; Double Diode Triodes, 7/6; 350 v. F.W. Rect., 5/6; 500 v. F. W. Rect., 6/6; 13 v. 2 amps. Gen. Purpose Triodes, 5/6; H.F. Pens and Var-Mu. H.F. Pen., Double Diode Triodes, Oct. Freq. Changers, 7/6 each. Full and Half-wave Rectifiers, 6/6 each.

TRIAD HIGH-GRADE U.S.A. VALVES, all types in stock. Standard tubes, 5/6 each. Octal Base tubes, 6/6 each.

PREMIER BATTERY CHARGERS for A.C. Mains. Westinghouse Rectification complete and ready for use. To charge 2 volts at 1 amp., 11/9; 6 volts at 1 amp., 19/-; 6 volts at 1 amp., 22/6; 12 volts at 1 amp., 24/6; 6 volts at 2 amps., 37/6.

PREMIER 1940 HIGH FIDELITY AMPLIFIER KITS

Each Kit is complete with ready-drilled chassis, selected components, specially matched valves and full diagrams and instructions.

	Kit of parts with valves.	Completely Wired and Tested.
4-watt A.C. Amplifier	£2 - 6 - 6	£3 - 4 - 0
4-watt A.C./D.C. "	£2 - 6 - 6	£3 - 4 - 0
6-watt A.C. "	£6 - 2 - 6	£7 - 0 - 0
8-10 watt A.C./D.C. "	£5 - 5 - 0	£6 - 2 - 6
15-watt A.C. "	£6 - 14 - 0	£8 - 2 - 6

Black Crackle Steel Cabinet 15/- extra.

PREMIER Short-Wave Condensers all-brass construction, with Trolital insulation. 15 mfd., 1/9; 25 mfd., 1/10; 40 mfd., 2/-; 100 mfd., 2/3; 160 mfd., 2/7; 250 mfd., 2/11.

PREMIER SHORT-WAVE COILS, 4- and 6-pin types, 13-26, 22-47, 41-49, 78-170 metres, 2/- each, with circuit. Special set of S.W. Coils, 14-150 metres, 4/9 set, with circuit. Premier 3-band S.W. coil, 11-25, 19-43, 38-86 metres. Suitable any type circuit, 2/11.

Coil Formers, 4- and 6-pin, plain or threaded, 1/2 each.


UTILITY Micro Cursor Dials. Direct and 100: 1 Ratios, 4/3.

Jelly Type High Voltage Condensers, Imp. 8,000 v. working, 7/6 each.

Orders 5/- and over sent Post Free. Under 5/- please add 6d. postage.

YOU MUST HAVE A PREMIER 1940 CATALOGUE
111 PAGES - - - PRICE 6d.
GET YOUR COPY TO-DAY!

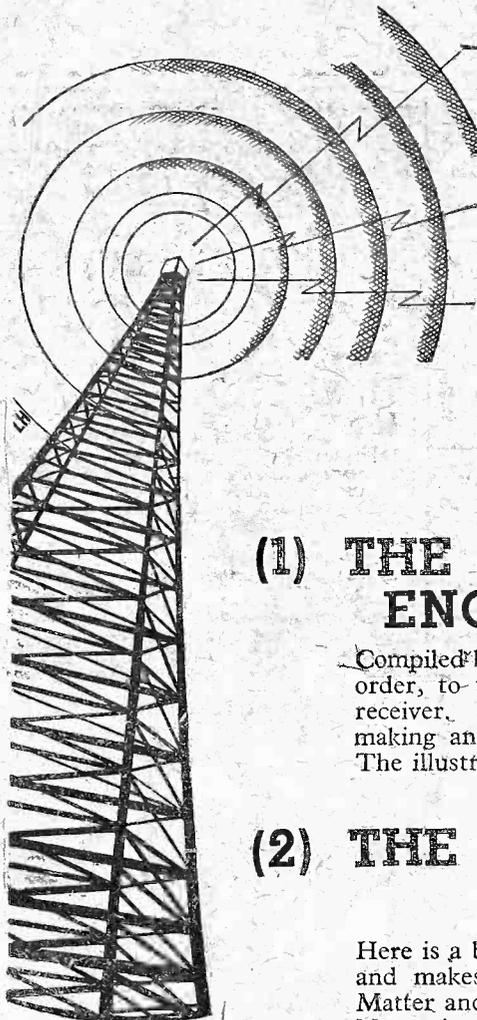ALL POST ORDERS TO: Jubilee Works, 167, Lower Clapton Road, London, E.5. *Amberst 4723*
CALLERS TO: Jubilee Works, or our NEW PREMISES, 169, FLEET STREET, E.C.4. *Central 2893*
or 50, High Street, Clapham, S.W.4. *Macaulay 2981*



R-A-F W-A-N-T-S R-A-D-I-O M-E-C-H-A-N-I-C-S

The Air Minister announced recently that he wants radio mechanics. Recruits selected for this specialised trade are given the rank of Leading-Aircraftman and paid at the rate of 5/6 a day, plus allowances. This is an opportunity for young men, and Newnes' Practical and Authoritative Wireless Books will help you gain the knowledge required.

(1) THE PRACTICAL WIRELESS ENCYCLOPÆDIA

By F. J. Camm

Compiled by an acknowledged expert, this volume forms a complete guide, in alphabetical order, to the construction, operation, repair and principles of every type of wireless receiver. It includes definitions, explanations, formulæ, and complete instructions on the making and testing of various wireless components.

The illustrations include a complete series of circuits for every type of modern receiver. 7/6 net. (By post 8/-)

(2) THE OUTLINE OF WIRELESS

By Ralph Stranger

Here is a book which covers the theory and practice of Wireless Reception from A to Z, and makes everything plain, even to the most "non-technical" reader. Contents: Matter and Energy. Electrified Matter. Electronic Currents. Magnetism and Electro-Magnetism. Batteries and Accumulators. Wireless Waves. Wireless Communication and Broadcasting. Over 800 pages, fully illustrated. 10/6 net. (By post 11/-)

(3) EVERYMAN'S WIRELESS BOOK

By F. J. Camm

A Radio Consultant for the Listener, Expert and Amateur Constructor, with Special Chapters on the Principles of Radio Telephony, Installation and Systematic Fault-finding. With 200 Illustrations and Diagrams. General Principles of Wireless Receivers. Testing. Special Remedies for Local Conditions. Noises, their Cause and Remedy. Equipment Troubles. Short-Wave Troubles. Improving the Quality of Reproduction. Accumulators and Batteries, etc. 5/- net. (By post 5/6)

(4) THE MATHEMATICS OF WIRELESS

By Ralph Stranger

This brilliant and experienced writer on Wireless has a happy knack of making even the driest and most abstruse topic interesting. He has a characteristic way of handling mathematics which appeals irresistibly to those to whom previously the subject has seemed both difficult and dull.

The book deals with: Arithmetic. Algebra. Powers and Roots. Differential Calculus. Integral Calculus. Trigonometry. The Slide Rule. Logarithms. Efficiency. Curves and Graphs in Wireless.

5/- net. (By post 5/6)

(5) PRACTICAL WIRELESS SERVICE MANUAL

By F. J. Camm

A complete, practical and up-to-date work on the testing and servicing of all types of wireless receivers, packed with valuable information for both the amateur and professional serviceman. With over 200 illustrations.

6/- net. (By post 6/6.)

SEND THIS COUPON TO-DAY

Ask your bookseller to get you the book or books you require at the usual price, thus saving postage. Alternatively, send the form to the publishers, with postal order (plus 6d. extra on each book to cover postage), and the book or books will be sent direct to you.

To the Publisher, GEORGE NEWNES, Ltd. (Book Dept.), TOWER HOUSE, SOUTHAMPTON ST., LONDON, W.C.2. Please send me by return the book or books encircled below. I enclose Postal Order for the necessary amount.

1. 2. 3. 4. 5.

P.O. Value.....No. is.....

Name.....


Address.....

..... P.W. 16/3/40

Practical Hints

A Bandsread Drive

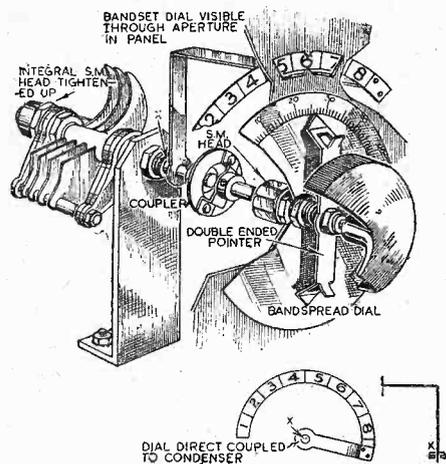BELOW, I give details of a very simple mechanical bandsread drive, which I devised for use in my short-wave receiver. The condenser which I had previously used had an integral reduction device of 8-1, and by coupling this to an additional slow-motion driving head, as shown in the



A simple mechanical bandsread drive.


sketch, a total reduction (in my case) of 72-1 was obtained. The pointer traversing the "bandsread" dial must be double ended, and by providing it with suitable projectors it can be used for more rapid "band-setting." This pointer is fastened to the usual place on the driving head, i.e., to the condenser through its integral reduction device.

The "band-set" dial is home constructed, and is divided into a number of divisions equal to the reduction rates of the condenser's integral device (in my case 8). The actual position of the dial depends on the form of mounting, etc., and a suggestion is given in the sketch. The dial is coupled direct to the condenser vanes.

In order to eliminate possible slipping, it is best to tighten up the condenser's integral reduction device slightly, and then if the knob is rotated when the vanes are all in (or out), it will only be the additional driving head that slips. For the same reason, care must be taken if the pointer is used as a quick "band-setter," as suggested. —J. W. HORWOOD (West Bergholt).

A Screened Input Jack

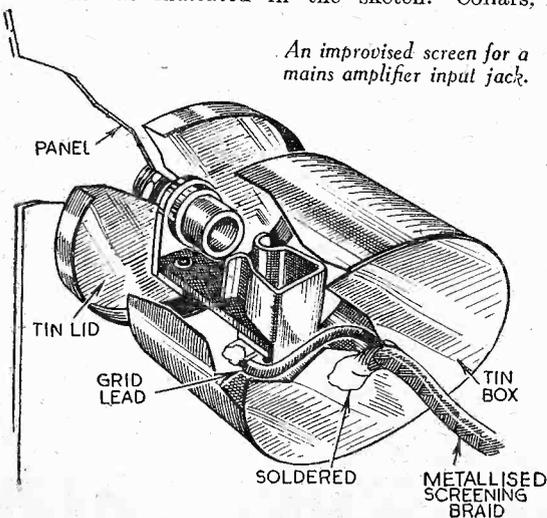BEING unable to obtain a shielded jack for a mains-driven amplifier at short notice, I hit on the following dodge. I obtained an empty mustard tin, of oval shape, about 1 1/2 in. deep. First, I drilled a 3/16 in. hole in the centre of the lid (to take the neck of an ordinary single circuit jack), and then I drilled another 3/16 in. hole in the bottom of the tin for the output grid lead.



An improvised screen for a mains amplifier input jack.

THAT DODGE OF YOURS!

Every Reader of "PRACTICAL WIRELESS" must have originated some little dodge which would interest other readers. Why not pass it on to us? We pay £1-10-0 for the best hint submitted, and for every other item published on this page we will pay half-a-guinea. Turn that idea of yours to account by sending it in to us addressed to the Editor, "PRACTICAL WIRELESS," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Put your name and address on every item. Please note that every notion sent in must be original. Mark envelopes "Practical Hints." DO NOT enclose queries with your hints.

SPECIAL NOTICE

All hints must be accompanied by the coupon cut from page iii of cover.


It was but a minute's work then to push the jack through the lid (using it instead of one of the spacing washers) and screw it up tight to the panel. I then pushed the lead through the hole in the bottom of the tin—pushed the box on to the lid, and the jack was completely enclosed and screened. The remainder of the grid lead between the screening box and the valve pin was covered with metallised braiding, soldered at one end to the box, and earthed to chassis at the other. This removed the last vestige of hum, and also has the merit of cheapness.—JAS. THRELFALL (Blackpool).

Preventing Aerial Leakage to Earth

THE accompanying sketch shows a dodge for minimising aerial leakage to earth due to rain, or moisture accumulating during misty weather.

The vertical aerial, A, is supported by brackets, B, fixed to the chimney stack. The aerial rod is insulated from these brackets at the points marked C. To keep the insulating material reasonably dry for preventing leakage I used the two halves of a circular wool container, which can be purchased at any cheap stores for 6d. A hole is made in the centre of each part, and also a slot in each to fit over the brackets, as indicated in the sketch. Collars, D,

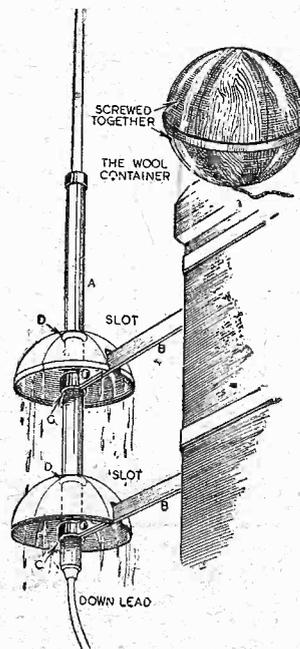are also fitted to support the semi-circular shields, the joints at these points being



A novel dodge for preventing aerial leakage to earth.

sealed with bitumen.—L. BURTON (Sheffield).

Join Newnes' Practical Group!

PRACTICAL MOTORIST

The owner-driver's journal which tells you how to repair, overhaul and obtain the best performance from your car.

3d.—Every Friday.

PRACTICAL MECHANICS

The only English journal of its type. It deals with every branch of Science, Mechanics, Invention, Model-making, Chemistry, Astronomy, Photography.

7d.—Every month.

THE CYCLIST

The leading weekly for every Cyclist, Clubman, Utility Cyclist or Tourist. Join "The Cyclist" Road Club and also take advantage of the FREE Insurance.

3d.—Every Wednesday.

PRACTICAL ENGINEERING

The new weekly journal for those engaged in all branches of the Engineering and kindred industries.

4d.—Every Thursday.

ility Amplifier

Useful Unit Especially Gramophone Records

as the latter is more positive than H.T. negative (see dotted connections, Fig. 1).

A cheaper, and probably just as simple, means of smoothing the bias to the output valve is to decouple it by means of a resistance and 12-mfd. electrolytic condenser, as shown in the theoretical diagram. It is important that this resistance should not exceed a value of 250,000 ohms with the P.X.4 valve, and 100,000 ohms is a good value to use and quite effective.

It should be noted that the current of the M.H.4 valve also flows through the biasing resistance, but it is so low as to make no appreciable difference to the bias voltage developed across the resistance. Actually, the bias developed is just under 4 per cent. higher than the correct bias for the P.X.4 valve, but this does no harm. Slight over-biasing is far preferable to under-biasing.

Should it be decided to run other valves from the same filament winding, it will be necessary to take into account their total current consumption and to alter the value of the biasing resistance accordingly. For example, suppose the total consumption of the valve in use rose to 60mA and that the resistance was kept at a value of 900 ohms. It is quite a simple matter to calculate from Ohm's Law that the voltage developed across the resistance would be 54 volts, and this would mean that the P.X.4 valve was greatly over-biased. In this case, it would be necessary to use a resistance with a value of only 700 ohms to obtain a bias of 44 volts.

The fact that the earth line, or chassis, is positive in respect of the true H.T. negative does not affect the bias applied to the M.H.4 valve. This is an indirectly-heated valve and derives its bias from the voltage drop across a resistance in the cathode circuit. The grid is taken to chassis and thus becomes more negative than the cathode by the amount of the voltage developed across the resistance. The fact that the chassis itself is more positive than H.T. negative does not affect the question of the grid-bias applied to this valve at all, but does result in a potential difference between the heater and cathode of the indirectly-heated valve by an amount equal to the voltage developed across the resistance in the H.T. negative lead. The insulation between the cathode and heater, however, is more than sufficient to withstand this, and there is no fear of breakdown in this direction.

The H.T. power supply is obtained from a Westinghouse metal rectifier type H.T.16 connected in the voltage-doubler circuit, with an A.C. voltage input of 205 volts. This gives an output of 310 volts at 52mA (the current of the P.X.4 and M.H.4. valves)

and is smoothed by a choke of 250 ohms D.C. resistance and an 8 mfd. electrolytic condenser. The smoothed H.T. voltage is just over 290 volts. This arrangement allows of the use of a permanent-magnet type of loudspeaker.

Voltage Doubler

Note that the negative side of the voltage-doubler condensers is taken to H.T. negative and not chassis.


The voltage-doubler condensers are of the

paper type, 500 v. D.C. working. Actually, the voltage they have to withstand never exceeds 400 volts, so that it is possible to substitute them with the cheaper electrolytic type. If it is desired to do this, it is advisable to obtain the condenser manufacturers' approval, when the type of rectifier in use, input voltage and load current, should be specified.


For those who wish to use a mains-energised loudspeaker, the input to the rectifier may be increased to 240 volts, and there is a tapping on the mains transformer to allow of this. In this case, the unsmoothed output of the rectifier at 52mA is some 390 volts, which, after being smoothed by a speaker field of 2,500 ohms D.C. resistance, leaves a voltage of approximately 265 volts for the amplifier valves.

(Continued on next page).

WIRING DIAGRAM OF THE AMPLIFIER

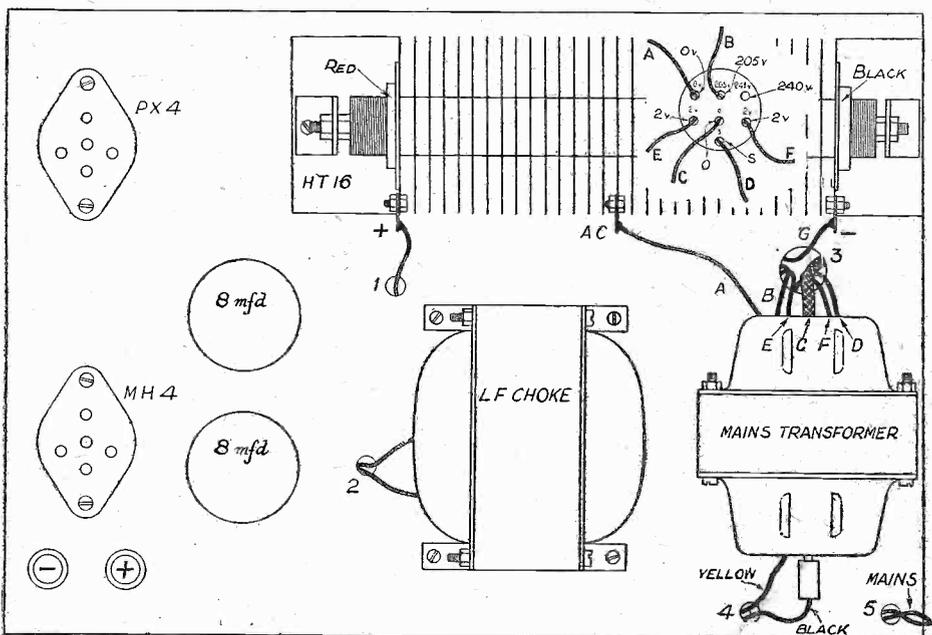

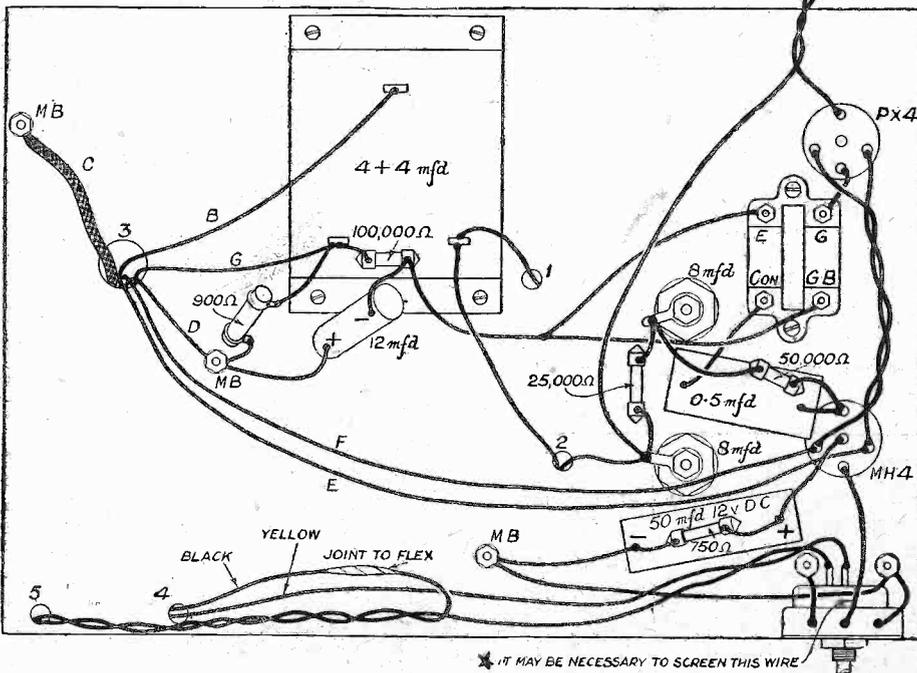Inset on the metal rectifier are the code connections for the transformer end plate.



** IT MAY BE NECESSARY TO SCREEN THIS WIRE*

A SIMPLE QUALITY AMPLIFIER

(Continued from previous page).

As the action of the Westinghouse metal rectifier is instantaneous, a surge voltage of some 600 is produced when first switching on. The use of a directly-heated output valve limits this surge to matter of seconds only, but, even so, it is more than sufficient to break down the normal type of dry electrolytic smoothing condenser. For this reason, it is absolutely necessary to use surge-proof condensers such as the Dubilier type O281 style A, or else to incorporate a thermal-delay switch to prevent the H.T. voltage reaching the condensers until the valves have had time to warm up, when the fact that they would take their full current immediately the H.T. was applied would prevent any large voltage surge.

Owing to the high mutual conductance of the two valves used in the amplifier, there may be some slight tendency to parasitic oscillation, which can be cured by the usual grid-stopper resistances. These were not found at all necessary in the experimental amplifier constructed.

When the volume control is turned full on, slight motor-boating may occur, depending on the "goodness" of the valves in use. This may be cured by reducing the value of the coupling condenser from 0.5 mfd. to 0.25 mfd., or by the inclusion of a stopper resistance in the grid circuit of the M.H.4, but it should seldom be necessary to have the set working full out, unless the amplifier is operating in a very large room.

Constructional Details

Construction is so simple as to need little comment. The set is constructed on an aluminium chassis, this being very substantial, easy to work, and providing good shielding and a convenient earth-return circuit, besides being very much nicer to

look upon than the wooden baseboard type. The components are mounted as shown in the diagram (page 403). Make sure when mounting the rectifier that it does not rotate on its spindle and short to chassis through the cooling fins. Also, when the set is in use, take great care not to touch the rectifier at all, as the fins are connected to the actual rectifying washers, and are thus alive.

The rectifier, mains transformer, etc., are first mounted in position, the resistances and small condensers being suspended in the actual wiring, which is an extremely simple job. Once the chassis itself has been built, it should be possible to mount the components, wire up and have the amplifier ready for testing within the hour.

Having completed the wiring, there is little to be done beyond settling down to enjoy gramophone record reproduction.

There is no fuse in the amplifier, so it may be desirable, at least if you have any doubts at all as to the correctness of your wiring, to insert a 250 mA. fuse between the rectifier negative terminal and the bias resistance.

The simplest way to test the receiver is to connect a moving-coil voltmeter across the bias resistance (positive connection to chassis), switch on, and note whether or not a voltage is produced across the resistance. A reading should be obtained almost immediately.

Detector Unit

A simple detector unit for use with the amplifier is shown in Fig. 2, and consists of an AC/HL type valve tuned by an un-screened Bulgin coil type C.69, of which only the medium-wave windings are used. The long-wave grid winding is shorted out as indicated in Fig. 2, but don't connect terminal 4 of the reaction winding to earth,

or you will short-circuit the H.T. supply. Leave this terminal free.

The usual 0.0001 mfd. grid condenser and 500,000 ohm grid leak are used, and the anode circuit is decoupled by a 25,000 ohm resistance and 8 mfd. condenser, and the usual load resistance of 50,000 ohms is also incorporated. The rectified voltages developed across this resistance are fed to the amplifier via the 0.05 mfd. condenser and 100,000 ohm H.F. filter resistance. H.F. filtering is completed by the two 0.0001 mfd. condensers. Reaction is also employed in the usual manner with the reaction condenser on the "earthy" side of the reaction condenser to avoid hand capacity effects.

Note that the detector valve is operated without any cathode bias.

The selectivity of such a unit is of course very low. Used near the transmitter it will allow of the best quality reproduction without any interference, nearby stations being "swamped" by the local. In more distant areas, however, it may be found necessary to use a 0.0001 mfd. pre-set condenser in the aerial lead and to adjust this, at the same time advancing the reaction control to a point just below oscillation, in order to increase selectivity. Used in this fashion, the unit is giving a good account of itself in the west of England.

The tuning condenser and the reaction control may conveniently be pre-set so that it is only necessary to switch on to receive the B.B.C. Home Service.

An efficient unshielded coil, such as the one suggested above, allows maximum stage gain to be employed, and it has been found possible, by careful adjustment of the aerial series and reaction condensers, to receive three or four foreign broadcasts with but very little interference. The unit is, however, intended for "home consumption" only.

NEW SERIES

RADIO ENGINEER'S POCKET-BOOK

No. 1

No. 2

No. 3

Frequency Formula
Formula for frequency is: $f = \frac{10^6}{2\pi\sqrt{LC}}$ where L=inductance in microhenrys and C=capacity in microfarads.

Wavelength of Tuned Circuit.
Formula for the wavelength of a tuned oscillatory circuit is: $1884.96\sqrt{LC}$, where L=inductance in microhenrys and C=capacity in microfarads.

Inductance
The formula for inductance in microhenrys is: $L = \frac{9.86D^2N^2K}{1000}$, where L=inductance, D=diameter of coil in centimetres, l=length of coil in centimetres, N=number of turns per centimetre, and K=a constant. See table.

Inductance Reactance
Calculated from the formula $2\pi fL$, where f=frequency and L=the inductance.

This Table shows the Value of K, which must be Calculated from D/l

D/l	K	D/l	K
4.00	.3654	1.25	.6381
3.75	.3743	1.00	.6884
3.5	.3944	.90	.7110
3.25	.4111	.80	.7351
3.00	.4292	.70	.7609
2.75	.4545	.60	.7885
2.5	.4719	.50	.8181
2.25	.4972	.40	.8499
2.0	.5255	.30	.8838
1.75	.5579	.20	.9201
1.5	.5950	.10	.9588

Capacity of Variable Condensers
 $C = \frac{.0885NS}{1,000,000 d}$
Where N=Number of moving vanes.
S=Area of one moving vane in square centimetres.
d=Air gap between moving vanes and fixed vanes in centimetres.

H.F. Transformer Ratio. $(n) n^2 = \frac{R}{R_0}$
R being the dynamic resistance of the tuned circuit and R₀ the A.C. resistance of the valve.

Stability in Screen-Grid Stages.
One Stage.
Stable if $\frac{\omega g C_0}{\sigma_1(\sigma_2 + \sigma v)}$ is less than 2.
C₀=residual anode-grid capacity in farads.
=.001 x 10—12 for Cossor S.G. Valves (all types).
=.0045—10—12 for Cossor MS/Pen A.
 σ_1, σ_2 =conductance of grid and anode* circuits respectively.
=1/R where R=dynamic resistance in ohms.
 σv =anode filament conductance of valve.
=1/R₀.

Two Stages.
Assuming identical tuned circuits throughout, and ignoring damping effects of valves on tuned circuits.
Stable if $\frac{\omega C_0 g}{\sigma^2}$ is less than 1.14 (Tuned Angle).
or if $\frac{\omega C_0 g}{\sigma^2}$ less than 1.14n² (Tuned Transformer).
where σ =conductance of tuned circuit (secondary) and n=transformer ratio.
* In the case of transformer coupling, or its equivalent, replace σ_2 by $n^2\sigma$, where n=transformer, ratio, σ =conductance ($= \frac{1}{R}$) of tuned secondary.

Wavelength-Frequency Conversion Table.
Metres to Kilocycles.

Metres.	Kilocycles.	Metres.	Kilocycles.
5	60,000	370	810.8
6	50,000	380	789.5
7	42,857	390	769.2
8	37,500	400	750
9	33,333	410	731.7
10	30,000	420	714.3
25	12,000	430	697.7
50	6,000	440	681.8
100	3,000	450	666.7
150	2,000	460	652.2
200	1,500	470	638.3
205	1,463	480	625
210	1,429	490	612.2
215	1,395	500	600
220	1,364	510	588.2
225	1,333	520	576.9
230	1,304	530	566
235	1,277	540	555.6
240	1,250	550	545.4
245	1,225	560	535.7
250	1,200	570	526.3
255	1,177	580	517.2
260	1,154	590	508.5
265	1,132	600	500
270	1,111	650	461.5
275	1,091	700	428.6
280	1,071	750	400
290	1,034	800	375
295	1,017	850	352.9
300	1,000	900	333.3
310	967.7	950	315.9
320	937.5	1,000	300
330	909.1	1,250	240
340	882.3	1,500	200
350	857.1	1,750	171.4
360	833.3	2,000	150

Note.—To convert kilocycles to wavelengths in metres, divide 300,000 by the number of kilocycles. To convert wavelengths in metres to kilocycles, divide 300,000 by the number of metres. One megacycle = 1,000,000 cycles or =1,000 kilocycles. Thus, 30,000 kilocycles = 30 megacycles.