


FITTING A "BABY ALARM"



Vol. 28 No. 548
JUNE 1952

EDITOR:
F.J. CAMM

PRACTICAL WIRELESS

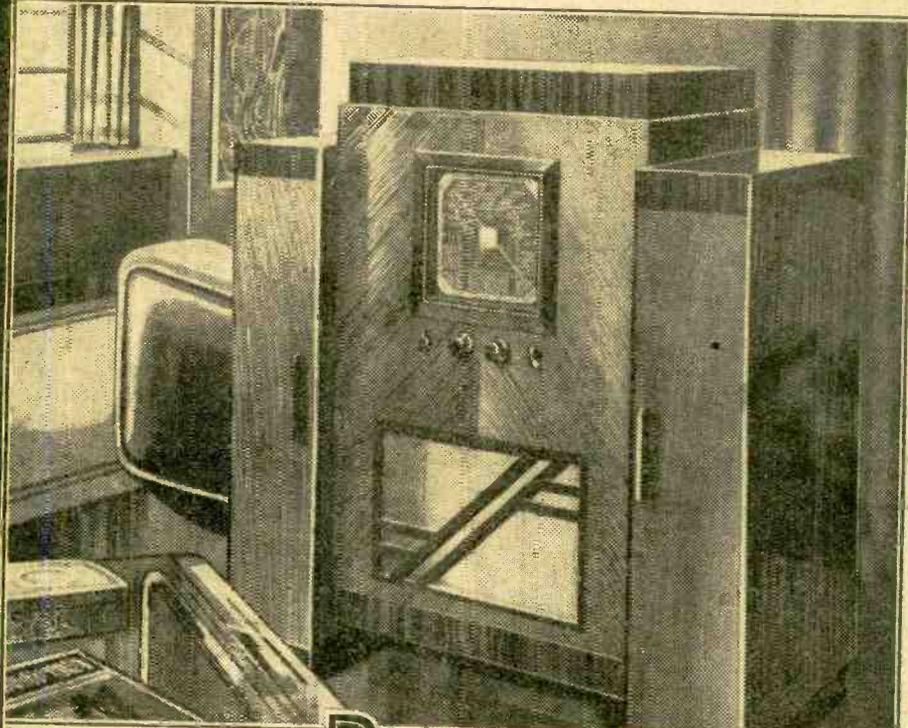


BUILDING THE **PW** 3-SPEED AUTOGRAM

IN THIS ISSUE:

PRESENTING TECHNICAL
INFORMATION
87G CIRCUITS
A MODIFIED FOLDED "V" BEAM

VARIABLE FREQUENCY
OSCILLATORS
A VOICE-OPERATED RELAY
RECEIVER DESIGN AT V.H.F.

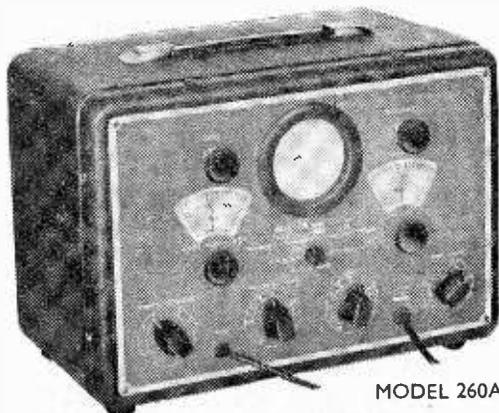

MODEL 260A

THE NEW WINDSOR TELEVISION WOBULATOR

- * Carrier Frequency 5-70 Mc/s. 10-140 Mc/s. (on 2nd harmonic)
- * Bandwidth 0-5 Mc/s. total. 0-10 Mc/s. (on 2nd harmonic)
- * Sweep Frequency 50 c.p.s. sinusoidal, return trace blacked out automatically
- * Output Adjustable from 0-10 mV. approx. Fixed and variable attenuators are fitted. Output impedance 75 ohms

PRICE £36. 15. 0d/

TAYLOR ELECTRICAL INSTRUMENTS LTD.
419-424, Montrose Avenue, Slough, Bucks. Tel.: Slough 21381


G2AK This Month's Bargains G2AK

MINI FOUR. All parts, Chassis, Kit, etc., from stock.
MIDGET SPEAKERS, W.B., 2½in., 1616; Philips, 3in., 151-; W.B., 3½in., 1916; Sin., 161-; Elac, 6½in., 1716; P. & P., 11-
TEST PRODS, for test meters. Red and black, 416 pair.
ELAC FOCUS UNITS, for triode and tetrode tubes. P.M. type; List, 30/- . Our price, 20/-, post free.
SPECIAL TRANSFORMER OFFER. Varley or Woden. 0-250 Tapped Primary. 350/350, 80 mA. 4v. 2.5 A. C.T., 4v. 5 A. C.T., 17/6 each. P. & P., 11/6. Limited Quantity.
SELENIUM RECTIFIERS, 250 v. 60 m.a. D.C. output. New, 7/6 each.
MORSE PRACTICE SETS, with double-action buzzer, output for 'phones excellent key; require only 4½ v. battery. As new, 7/6, P. & P., 11-
MIDGET OUTPUT TRANSFORMERS for personal portables, 6/- . Standard pen., 5/6. Mike trans. for M.C. mikes, 2/- ; for carbon, 1/3 each.
XTAL DIODES, 3/9 each Germanium diodes, 4/6 each.
POTENTIOMETERS. 20 k. and 25 k. W.W. 5 w., 2/- each. Carbon, 50 k., 100 k., 1 meg. and 2 meg., 11/6 each. 500 ohm H.D. toroidal, 3/6 each.
TWIN FEEDER. 300 ohm H.D. Twin, 5d. yd. Standard K25, 300 ohm., 9d. yd. K24 150 ohm, 9d. yd. Coax. T.V. cable, ½in., 11/3 yd. Packing and postage on cables, 1/6.
SPECIAL VALVE OFFER. Kit of 4 midget 1.4 v. valves, 1 each 1S5, 1R5, 1T4 and 1S4, 35/- or 9/6 each, separately. Postage free on all orders over £1 except where specifically stated. **PLEASE PRINT YOUR NAME AND ADDRESS.**

CHAS. H. YOUNG, G2AK

All callers to 110 Dale End, Birmingham
CENTRAL B135

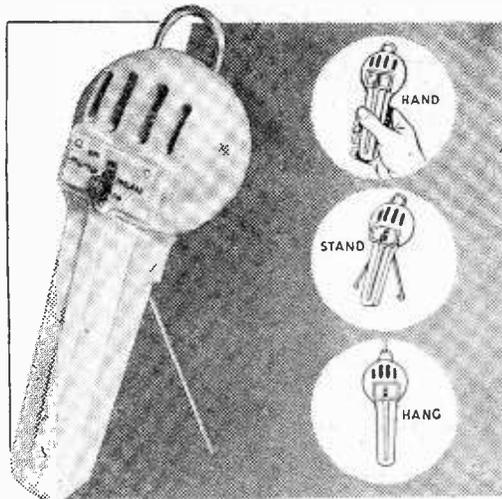Mail Orders to 102 Holloway Head, Birmingham
MIDLAND B254



cos MIC 30

"Hand-stand" MICROPHONE

A new universal microphone of the crystal type
selling at the moderate price of £4. 4.

COSMOCORD LTD., ENFIELD, MIDDLESEX

If you can SOLDER

you can have the thrill and satisfaction of building the

"VIEWMASTER" TELEVISOR

and what is more, save pounds by doing your own maintenance!

- Up-to-date design.
- Appearance and performance as good as the commercial article.
- Backed by famous manufacturers.
- Designed by an expert, using STANDARD components.
- For 9in. or 12in. Cathode Ray Tubes.
- Foolproof, stage-by-stage wiring instructions.

Send to
SMITHS of Edgware Road
The Component People

for Construction Envelope, which contains an explanation of T.V. reception, full-size working drawing of metal-work, 6 stage-by-stage building and wiring instruction sheets, price list of parts, etc. (State which station you wish to receive.)

Price 7/6 post free.
Over 50,000 already sold!

We can supply any or all of the parts required, including aerial, cabinet, etc., and help you if in any difficulty.

H. L. SMITH & CO., LTD.
287/9 Edgware Road, London, W.2.

Tel.: Paddington 5891. Hours 9 till 6 (Thursday 1 o'clock)
Near Edgware Road Stations, Metropolitan and Bakerloo



CONDENSERS

The abbreviated ranges of two popular types given here are representative of the wide variety of T.C.C. Condensers available.

'VISCONOL CATHODRAY' CONDENSERS

Cap. Range: '0005mfd. to 1 mfd.
Voltage Range: 750 to 25,000 at 60°C.

Cap. in μ F.	Max. W/kg. at 60°C.	Dimens. (Overall)		Type No.
		Length	Dia.	
'0005	25,000	5 $\frac{3}{8}$ in.	1 $\frac{1}{2}$ in.	CP.57.HOO
'001	6,000	2 $\frac{1}{2}$ in.	$\frac{3}{8}$ in.	CP.55.QO
'001	12,500	3 in.	1 $\frac{1}{2}$ in.	CP.56.VO
'01	6,000	3 in.	1 $\frac{1}{2}$ in.	CP.56.QO
'1	7,000	6 $\frac{1}{2}$ in.	2 in.	CP.58.QO
'25	5,000	5 $\frac{1}{8}$ in.	2 $\frac{1}{2}$ in.	CP.59.MO

Regd.

MOULDED MICA CONDENSERS

Stacked Foil. Capacities from 50 to 10,000 pF
Voltage Ratings, 350 to 2,500 v. D.C. Working.

MOULDED SILVER MICA CONDENSERS



Capacities from 10 to 10,000 pF.
Voltage Ratings, 350 v. D.C. Working.

WAX PROTECTED SILVERED MICA CONDENSERS

Capacities from 5 to 12,000 pF.
Voltage Ratings, 350 v. D.C. and 750 v. D.C. Working.

THE TELEGRAPH CONDENSER CO. LTD.

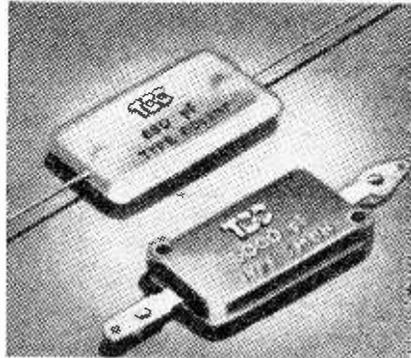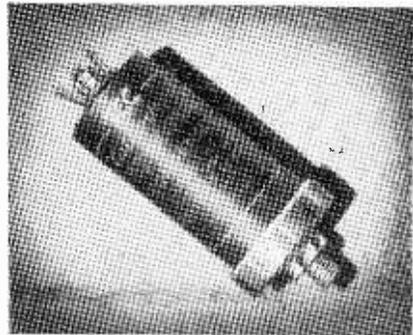Radio Division: North Acton, London, W.3 Tel: Acorn 0061



RADIO MAIL

4, RALEIGH STREET, NOTTINGHAM

INTRODUCING A RESISTANCE-CAPACITY BRIDGE AT 30/- ONLY

Note the following points

LESS THAN ONE FIFTH THE COST OF A COMMERCIAL INSTRUMENT OF SIMILAR RANGE.

THREE CAPACITY RANGES, TESTING UP TO 50 MFD. THREE RESISTANCE RANGES, TESTING UP TO 5 MEGOHMS.

EASILY AND QUICKLY ASSEMBLED WITH THE SIMPLE INSTRUCTIONS AND CIRCUIT DETAILS SUPPLIED.


NO CALIBRATING NECESSARY AFTER ASSEMBLY.

ALL CALIBRATIONS, SWITCH RANGE MARKINGS, TERMINAL FUNCTIONS, ETC., READY LAID OUT ON A HANDSOME ESCUTCHEON COVERING THE ENTIRE OPERATING PANEL.


THIS IS THE FIRST TIME THAT AN INSTRUMENT OF THIS CALIBRE HAS BEEN AVAILABLE AT SUCH A LOW PRICE. ORDER NOW WHILE SUPPLIES LAST.

STAMP FOR LIST AND WITH ALL ENQUIRIES PLEASE

DUKE'S

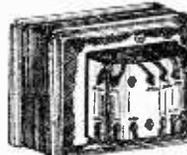

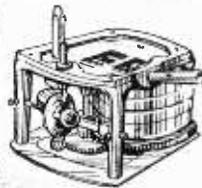TRANSFORMERS. Mains (Salvage). 200-0-200, 6.3 v., 3 A., tapped for 250, 210, 110 v. Price 12/6. Post 2/-. Also standard O.P. Trans. at 3/9. Post 1/-.



GRAMOPHONE MOTORS.

Unused. Made by E.M.I. Need cleaning, but in working order. Complete, but no winder handles. Ideal for building your gramophone, wire recorder, saucepan stirrer, wool, cotton or wire re-winders or anything requiring a strong spring motor. Speed control down to 33. Two main springs alone worth price of 25/9. Post and packing, 2/3.

VALVES. Salvaged, ECL80, 6AB8, 11/9. W142, U142, UF41, 10/9. EF36, EB91, Z77, 6F6, 1LC6, 6V6, 77, PP225, 12SJ7, 6F7, ECC31, 37, 6Q7, IT4, IR5, 8/9. OZ4, Pen220A, VP210, 8D2, 9D2, 15D2, SP2, KT32C, Pen383, VP133, 6/9. We are London's largest stockists. Stamp for complete list.

SALVAGE RADIO CHASSIS. Price 27/17/6 each. Write now for details, valve line-up, etc., of these 1952 all-wave radiogram chassis, with latest pin type midget valves, which were made to sell at three times this price. Many satisfied customers. Also Record Changer units. All units tested and guaranteed.



EXTENSION SPEAKERS. 6 in. in new type baffle stand, polished, with metal fret. Price 19/6. Post 1/- Other types and sizes in stock.

C.W.O. Money Back Guarantee. Stamp for Catalogue.
or GRA 621, Romford Road,
C.O.D. **DUKE'S** 6077 London, E.12.



'AVO'

Registered Trade Mark.

Precision ELECTRICAL TESTING INSTRUMENTS

A dependably accurate instrument for testing and fault location is indispensable to the amateur who builds or services his own set.

The UNIVERSAL AVOMINOR

(as illustrated) is a highly accurate moving-coil instrument, conveniently compact, for measuring A.C. and D.C. voltage, D.C. current, and also resistance; 22 ranges of readings on a 3-inch scale. Total resistance 200,000 ohms.
 Size: 4 1/2 ins. x 3 1/2 ins. x 1 1/2 ins.
 Net weight: 18 ozs.

Price: £10 : 10 : 0

Complete with leads, interchangeable prods and crocodile clips, and instruction book.

The D.C. AVOMINOR

is a 2 1/2-inch moving coil meter providing 14 ranges of readings of D.C. voltage, current and resistance up to 600 volts, 120 milliamps, and 3 megohms respectively. Total resistance 100,000 ohms.
 Size: 4 1/2 ins. x 3 1/2 ins. x 1 1/2 ins.
 Net weight: 12 ozs.

Complete as above
 Price: £5 : 5 : 0

D.C. Voltage
 0-75 millivolts
 0-5 volts
 0-25 "
 0-100 "
 0-250 "
 0-500 "

A.C. Voltage
 0-5 volts
 0-25 "
 0-100 "
 0-250 "
 0-500 "

Resistance
 0-20,000 ohms
 0-100,000 "
 0-500,000 "
 0-2 megohms
 0-5 "
 0-10 "

D.C. Current
 0-2.5 milliamps
 0-5 "
 0-25 "
 0-100 "
 0-500 "

GARANTEE: The registered Trade Mark "Avo" is in itself a guarantee of high accuracy and superiority of design and craftsmanship. Every new AvoMinor is guaranteed by the Manufacturers against the remote possibility of defective materials or workmanship.

Sole Proprietors and Manufacturers :-

AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.
 Winder House, Douglas Street, London, S.W.1. Phone: VICTORIA 3404-9

LASKY'S RADIO

MAINS TRANSFORMERS

All 200-250 volts 50 c.p.s. primary.

Finest quality, fully guaranteed.

MBA/2. 350-0-350 v. 80 mA., 6.3 v.

3 a., 5 v. 2 a. Both filaments tapped at 4 volts. An ideal replacement trans.

Price 21/-

MBA/5. 350-0-350 v. 125 mA., 6.3 v.

4a., 5 v. 3 a. With mains tapping board

Price 22/6

MBA/6. 350-0-350 v. 100 mA., 6.3 v.

3 a., 5 v. 2 a. With mains tapping board

Price 22/6

MBA/7. 250-0-250 v. 80 mA., 6.3 v.

3 a., 5 v. 2 a. Both filaments tapped at 4 volts. Price 21/-

AT/3. Auto transformer. 0-10-120-

200-250-250 volts, 100 watts. Price 19/6

ATA. Auto transformer. 100 volts and

250 volts. Step up; or down. 60 watts

Price 9/6

Postage 1/6 extra per transformer.

ACOS REPLACEMENT PICK-UP CARTRIDGES

LASKY'S PRICE 10/6 each. Post

6d. extra.

SPECIAL BUY. BRAND NEW T.C.C. T/V CONDENSERS

32 + 100 mfd., 450 v.w. LASKY'S PRICE 8/6 each.

.04 mfd. 12.5 Kv. LASKY'S PRICE, 10/6 each.

Postage 6d. per item extra.

EX A.M. COMMUNICATION RECEIVER TYPE E1155

BRAND NEW IN WOOD TRANSMIT CASE. Aerial-

tested before despatch. Supplied complete with 10 valves.

Circuit: B.F.O., A.V.C., R.F. Amp., Two I.F. stages, magic

eye, etc. 5 frequency ranges: 15.5-7.5 Mc/s; 7.5-3.0

Mc/s; 1,500-600 Kc/s; 500-200 Kc/s; 200-75 Kc/s.

LASKY'S £12/19/6

Carriage (in wood case) 7/6 extra. Full modification data

and circuit details supplied.

POSTAGE STAMP TRIMMERS AND PADDING CONDENSERS

Faxolin

3-35 pf. 40-80 pf.

30-100 pf.

LASKY'S PRICE 6d. each.

6/- per doz.

Ceramic

3-35 pf. 40-80 pf.

30-100 pf.

LASKY'S PRICE 9d. each.

7/6 per doz.

550 pf. and 350 pf. Ceramic. LASKY'S PRICE 1/- each,

10/6 per doz.

MINIATURE TWO-GANG TUNING CONDENSERS.

Type A. .0004 mfd. With trimmers, and Perspex dust

cover. Size: 1 1/2" wide, 1 1/2" high, 2 1/2" deep. 1" spindle.

LASKY'S PRICE 8/6. Postage 9d. extra.

Type B. .0005 mfd. With trimmers. Size as A above.

LASKY'S PRICE 8/6. Postage 9d. extra.

GERMANIUM X-TALS. Wire ends. Supplied with circ-

cuit. B.T.H. Type. LASKY'S PRICE 3/11 each.

Post. 3d. G.E.C. Type. LASKY'S PRICE, 4/3 each.

Post. 3d.

NEON TUNING INDICATORS

LASKY'S PRICE 2/6 each. Postage 4d.

extra.

CONDENSER SPECIALS

8 mfd. 500 v. w. 3/-

8 mfd. 450 v. w. 2/6

8 x 8 mfd. 500 v. w. 4/6

12 mfd. 50 v. w. 1/-

16 mfd. 450 v. w. 4/11

16 mfd. 500 v. w. 5/3

16 x 16 mfd. 450 v. w. 5/6

24 mfd. 450 v. w. 6/11

25 mfd. 25 v. w. 1/6

20 x 40 mfd. 350 v. w. 6/11

32 mfd. 450 v. w. 5/11

32 mfd. 500 v. w. 6/6

32 x 32 mfd. 350 v. w. 5/6

50 mfd. 12 v. w. 1/9

50 mfd. 50 v. w. 3/9

50 mfd. 350 v. w. 4/11

55 mfd. 350 v. w. A.C. 17/6

12 x 12 mfd. 350 v. w. 3/11

16 mfd. 350 v. w. 2/11

Postage extra.

COILS. Long. medium and short

Ae. H.F. and Osc. Wearite type "P."

PRICE 3/- per coil. Post 3d. extra.

Osmor type "Q." Latest type miniature,

dust cored. Price 4/- per coil. Post 3d.

extra.

SETS OF BUTTON BASE VALVES.

Comprises one each of the following

valves: 1R5, 1T4, 1S3, 3B4. Complete

with bases.

LASKY'S PRICE 40/- the set. Post 1/6

extra.

LASKY'S RADIO, 370, HARROW ROAD, PADDINGTON, LONDON, W.9.

(Opposite Paddington Hospital.)

(Lasky's (Harrow Road) Ltd.)

'Phone: Cunningham 1979 and 7214.

TERMS: Pro Forma Cash with Order, or C.O.D. on post items only. Postage and packing extra, unless otherwise stated.

All goods fully insured in transit.

Practical Wireless

EVERY MONTH
VOL. XXVIII, No. 548 JUNE, 1952

Editor E. J. CAMM

20th YEAR
OF ISSUE

COMMENTS

By THE EDITOR

TV EFFECTS ON RADIO

THE BBC's Audience Research Department, in a recently-published analysis, makes a statement that there is less radio listening as a result of the development of TV, that there is less cinema-going, and less reading. From these facts it is concluded that TV is changing the life of the nation. Some of the conclusions reached are not justified by facts, however. It simply is not true to say that the public is reading less. The circulations of newspapers and periodicals and the sales of books, both technical and non-technical, have never been higher, and it thus must be true to say that the public is reading more, possibly because TV keeps them at home. Owners of TV receivers at present are restricted in programme time and, presumably, they are reading when not viewing or going to the cinema.

According to trade reports, it is true that the sales of TV receivers are now in excess of the sales of radio receivers, but that is what one would expect at the commencement of a new form of entertainment. TV in 1947 was an entertainment which could only be indulged in by the well-to-do and by constructors sufficiently skilful to be able to build a TV receiver. In the short space of four years viewers have grown in numbers from just over a quarter of a million to well over a million and a quarter. It is obvious that as the service expands, the demand for TV receivers will go up. This does not mean that TV will eventually entirely supersede radio. There are certain aspects of each which the other cannot supplant. In other words, sooner or later everyone will own a TV as well as a radio receiver. Radio has continued to expand, as the licence figures show, for 30 years, but there are still some hundreds of thousands of homes without radio. It is obvious, however, that in the passage of time absorption point must be reached and that the demand for commercial broadcast receivers must decline. Money is not now so plentiful that people can afford to scrap a receiver and purchase a new one every two years or so. They are compelled to make everything they purchase last as long as possible. There is no sign that purchase tax will be removed, and therefore no indication that the spending power of the public will be increased for some years to come. This is a fact of which the trade should

take cognisance. On the other hand, because of high costs more and more sets are being built by constructors, as the demand, ever increasing, for our blueprints shows. The free blueprint of the Mini-Four, recently presented with this journal, was phenomenally successful, and the demand for components and kits and cabinets from the suppliers has been higher than for any pre-war receiver.

Hundreds of thousands of those who received radio training during the war have entered the ranks of constructors and augmented the demand for components. The industry, which was largely built up as a result of constructor demand, might usefully once again turn to the manufacture of components for constructors and thus make good from this source what they are losing from the sales of receivers.

A large amount of Government surplus equipment is on the market at low prices and constructors are drawing their components from this source. This, however, cannot last for ever.

One good thing has developed from the advance of television and that is the change that has now taken place which separates in important particulars TV and sound broadcasting. For example, the control of TV outside broadcasts and drama is divorced from sound-radio. The two are now under separate control and TV is achieving the self-government and autonomy which its development needs and deserves.

QUERIES

MAY we once again stress that we cannot undertake to answer queries over the telephone. They must be submitted in the ordinary way through the post and be accompanied by a stamped, addressed envelope for reply, and the hints coupon which appears in every issue. We are sure that readers will understand that if everyone with a query transmitted it by telephone the editorial lines would be occupied for twenty-four hours a day and for seven days a week!

Another point. While we are always delighted to help readers encountering problems in the normal course of their radio studies and experiments, we regret that we cannot undertake to deal with modifications of the surplus material which is on the market.—F. J. C.

ROUND the WORLD of WIRELESS

Broadcast Receiving Licences

THE following statement shows the approximate numbers of licences issued during the year ended February 29th, 1952.

Region	Number
London Postal ..	2,407,000
Home Counties ..	1,678,000
Midland ..	1,773,000
North Eastern ..	1,964,000
North Western ..	1,661,000
South Western ..	1,086,000
Welsh and Border Counties ..	747,000
Total England and Wales ..	11,316,000
Scotland ..	1,135,000
Northern Ireland ..	211,000
Grand Total ..	12,662,000

"Marabu" Equipped with Radio Dolphin

THE 26-ton yacht *Marabu*, which will join in the Newport-Bermuda six hundred miles race on June 21st, has just been fitted by Rees Mace Marine Ltd. with the Pye "Radio Dolphin" marine radio telephone.

The demand for the low cost "Radio Dolphin" sets has increased so much that Rees Mace are expanding their installation and fitting-out staffs in all depots. A "Radio Dolphin" set can now be installed within 24 hours anywhere in Great Britain or the Channel Islands.

Amplification System Accepted

PAMPHONIC REPRODUCERS LIMITED, of Westmoreland Road, London, N.W.9, state that their system of D.S.R. (Delayed Sound Reinforcement) which was recently reported in these columns, has now been approved by the Dean and Chapter of St. Paul's Cathedral and a permanent installation is now under way.

British Radio Aids Baltic Shipping

FOR the benefit of shipping in the treacherous coastal waters around Sweden, the Swedish "Trinity House" has installed V.H.F. radio equipment at certain pilot stations of importance along

the coastline. The combined transmitting-receiving equipment, for use within a radius of ten miles, is designed by Marconi's Wireless Telegraph Co., Ltd.

Because of prevailing fogs and other navigational hazards it is often difficult for the pilot cutters to catch pilot-seeking vessels. The new wireless installations will establish a short distance ship-to-shore network, primarily between the pilot cutters and their land stations. At the Bramo lighthouse, off Sundsvall in the Bothnia, a fixed radar station in addition to the V.H.F. communication equipment facilitates manoeuvring in and out of the pilots' waters.

Plessey Social Club

ON Friday, March 14th, Mr. T. White Wilson, executive director of the Plessey company, opened the company's new social club premises at Cricklade Road, Swindon.

The building, with a main hall to accommodate 200 people, provides facilities for billiards, darts, table tennis and card games for the 2,700 employees of the Swindon works.

Twice a week informal dances are held.

Technical Training

MR. A. V. ALLDAY, general works manager of the E.M.I. factories at Treorchy (Rhondda), had a word to say on opportunities for technically trained young men when he spoke at Glamorgan Technical College, Pontypridd, on April 1st.

On behalf of the association, Mr. Allday, a member of the education com-


mittee of the Industrial Association of Wales and Monmouthshire, was presenting certificates to two engineering students.

Industrial progress in South Wales since the war had been faster than in the London industrial belt, he said, and this meant ever-increasing opportunities for young men with the necessary technical training.

Marconi Apprentices Win Awards

SEVEN apprentices of Marconi's Wireless Telegraph Co., Ltd., who have recently completed courses in the company's training school, have been successful in the 1952 Physical Society Craftsmanship and Draughtsmanship Competition for Apprentices and Learners. The competition has a nation-wide coverage.

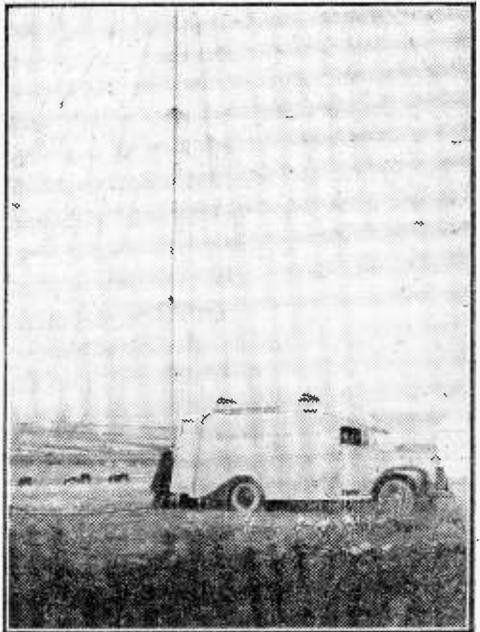The apprentices have gained awards in every class for which they



The Marconi V.H.F. survey team during their first tour covering the mountainous districts of North Wales. The Commer headquarters van, coupled to the two dipoles at the top of the 80ft. mast.

had entered, and were awarded first prizes in all draughtsmanship classes. There were 11 Marconi entries.

In addition, a 21-year-old student apprentice of Marconi's Wireless Telegraph Co., Ltd., George Brown, has won the Whitworth Prize for his performance in the Ordinary National Certificate, 1951, for the Institute of Mechanical Engineers.

The prize is awarded to those who attain more than 90 per cent. in their examination marks, and this year there were only 18 recipients of the prize out of 6,235 entrants in Britain.

Lee Products at B.I.F.

LEE PRODUCTS (GREAT BRITAIN), LTD., will be on show, as usual, at this year's B.I.F. (Stand No. H.17), Olympia, May 5th-16th. Gordon S. Lee, chairman and managing director, states that it will be the sixth successive B.I.F. at which this company has exhibited, and they are the only radio component manufacturers with this record.

The idea was first considered during 1946 when details of a proposed resumption of the annual pre-war B.I.F. were received from the Board of Trade, and it was decided to participate. Results from this and subsequent fairs were astonishingly successful particularly from overseas where substantial orders were received from Australia, New Zealand, South Africa, South America, India, Greece, Turkey, and many other countries. Also, a host of contacts were made, many by Mr. Lee himself, with other possible buyers and agents of numerous nationalities, many of whom were to be seen again and again at subsequent B.I.F.s.

A full range of "Elpico" radio and TV component parts will be exhibited, for which a new illustrated catalogue will be available.

B.S.R.A. Exhibition

ON Saturday, May 17th, and Sunday, May 18th, 1952, the British Sound Recording Association will be holding an exhibition at the Waldorf Hotel, Aldwych, London, W.C.2, from 10.30 a.m. to 6 p.m. on both days. The official opening will be on Saturday, May 17th, at 2.30 p.m., by John Snagge, Esq., O.B.E.

Admission is free to members, and non-members may gain ad-

mission by catalogue available at the door priced 1s. 6d., or post 1s. 8d., from the Hon. Secretary, R. W. Lowden, "Wayford," Napoleon Avenue, Farnborough, Hants, after May 1st.

A number of firms will demonstrate high-quality recording and reproducing equipment using disc, tape and wire. Some of the latest types of loudspeakers will also be demonstrated on both days.

Mr. Ian Baxter

MR. IAN BAXTER has been appointed a director of J. Bull & Sons, the mail order house. Mr. Baxter is now in his tenth year with the company and acted as general manager prior to joining the board.

B.I.R.E.

THE following Institution meetings will be held during May, 1952:

London Section. — Wednesday, May 7th, at 6.30 p.m., London School of Hygiene & Tropical

general meeting to be followed by a programme of technical films.

Radio Component Manufacturers' Officers


MR. HECTOR V. SLADE, M.B.E., T.D., A.M.I.Mech.E. (deputy managing director of the Garrard Engineering & Manufacturing Co., Ltd., Swindon), was elected chairman of the Radio & Electronic Component Manufacturers' Federation in succession to Mr. W. F. Taylor (Telegraph Condenser Co., Ltd.). Vice-chairman is Mr. P. D. Canning (Plessey Co., Ltd.) and treasurer is Mr. C. M. Benham (Painton & Co., Ltd.).

BBC Engineering Division Appointments

THE BBC announces the following new appointments in the Engineering Division:

Mr. H. W. Baker, A.M.I.E.E., becomes Superintendent Engineer Television Studios.

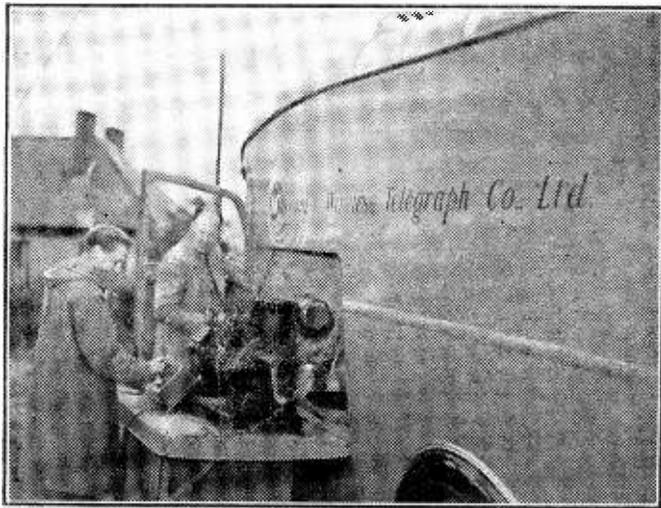Mr. T. H. Bridgewater, M.I.E.E., becomes Superintendent Engineer



Two of the engineers preparing the generator plant on its special table at the side of the Commer headquarters van, shown opposite.

Medicine, Keppel Street, Gower Street, W.C.1. An Aerial Analogue Computer. An "Instantaneous" Radiation Pattern Tracer and "Design Apparatus" for Directional Arrays. W. Saraga, Dr.Phil., D.T. Hadley and F. Moss, B.Sc

North-eastern Section. — Wednesday, May 14th, at 6 p.m., Neville Hall, Westgate Road, Newcastle-upon-Tyne. Annual

Television Outside Broadcasts.

Mr. H. Walker, O.B.E., A.M.I.E.E., becomes Head of Technical Operations, Television Service.

Mr. M. H. Hall becomes Engineer - in - Charge Television Studios.


Mr. W. D. Richardson becomes Engineer - in - Charge Television Outside Broadcasts.

Fitting a "Baby Alarm"

DETAILS OF THE ARRANGEMENT AND THE VARIOUS METHODS WHICH ARE AVAILABLE

By W. J. Delaney (G2FM)

MANY readers have a child who may need attention during the evening and find that their radio pleasures are restricted due to the need for having the volume turned so low, in case the child cries or calls for attention, that the strain of listening for a call above the radio becomes unbearable, and in many cases they have to deny themselves of the pleasures of the evening programme. Others try to listen, and in a break in the broadcast hear the child screaming, probably due to the fact that it has been crying for some time. The use of a

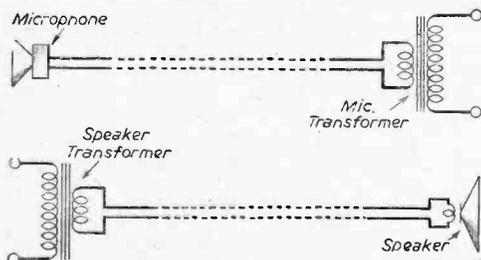

Extension leads from room to room should always be on the low (impedance) resistance side, whether in the input or the output circuit.

"baby alarm" overcomes these difficulties and is adopted by many listeners, and details have been touched upon from time to time in these pages. Briefly, it consists of some device by means of which the child's call can be heard above the radio signal—either as a separate reproduction, or superimposed on the broadcast, and it is fairly simple and costs very little to fit. In essentials it consists of a microphone which may be suspended over the child's bed or cot, or placed on a suitable stand near the sleeping place, and it is coupled to an amplifier and loud speaker. As the normal broadcast receiver contains both the amplifier and the speaker, it is obvious that it may be possible to make use of these and this leaves only a microphone to be obtained. Unfortunately, however, some radio circuits do not lend themselves to the combined simultaneous use, and a separate amplifier and speaker then may become necessary. However, let us examine the position stage-by-stage.


Microphones

Firstly, the microphone may be of any desired type, and there are two which are simplest and most popular. These are the carbon or transverse current, and the moving-coil. The former consists of a container housing carbon granules which are moved by the movement of a diaphragm, and a current flowing through the carbon is thus modified or varied as the resistance of the carbon varies. The moving-coil operates in the same manner as the modern moving-coil loudspeaker, only in the reverse direction. The

diaphragm moves a small coil which is suspended in a magnetic field, and the current through the field is varied by the moving coil. There are other types, but they are more expensive and are not needed for the present purpose. It is obvious that we are not concerned with high quality, and anything which will transfer any noise near it to the loudspeaker in the distant room will be sufficient signal to indicate that attention is needed. Ex-government components of both types are readily available, but it must be remembered that with the carbon type a current must be passed through it and this calls for a battery. As most ex-government items are sold without any technical data, the exact voltage which must be applied will have to be determined by experiment, but it is usually between 4.5 and 9 volts. Ordinary flash-lamp or torch cells may readily be used and the current taken is very small so that they last quite a long while. If it is desired, a switch can be placed in the battery circuit so that it may be "opened" during the day and thus the drain reduced, but this is hardly necessary with most types of microphone.

Input Circuit

The output from the microphone has to be fed to a valve and the grid circuit of a valve is of high impedance. Carbon microphones are of low impedance, but moving-coil mikes may be of either low or high impedance, and thus the first requirement here is a matching transformer. Small microphone transformers are also available ex-government as well as new, and the ratio will again have to be found by experiment. Once more, as quality is not a consideration, accurate matching may be dispensed with, but a low-resistance mike must have a transformer between it and the amplifier. As long leads in a grid circuit will pick up hum and perhaps interfere with performance, it is desirable to mount the matching transformer right on the amplifier chassis, as close to the valve as possible and this means that any leads running between the two rooms will be on the low-resistance side. As there may be a battery in this circuit, or in any case, in view of the low impedance

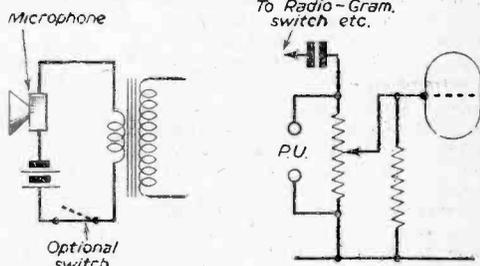


Biasing is carried out as shown here.

Some pick-up sockets are wired in this manner.

of this part of the arrangement, the wires from the mike to the amplifier should be fairly stout, parallel-laid plastic-covered bell-wire being ideal. Do not use thin instrument wire (cotton or double-cotton covered), and try to avoid running the wires parallel with any A.C. electric-light wiring.

Using a Broadcast Receiver

We must now consider the amplifier, and in many cases, as already mentioned, the broadcast receiver may be called into use. Many receivers (especially older models) have a pair of pick-up terminals or sockets on the back, to which a gramophone pick-up may be joined, and no radio-gram switching is provided. With this type of receiver one is expected to detune the radio when listening to records. In this type of set, the secondary of the mike transformer is just plugged into the pick-up sockets and any noise picked up by the microphone will be heard over the radio signal when the receiver is working. If a faint cry is too weak to be heard

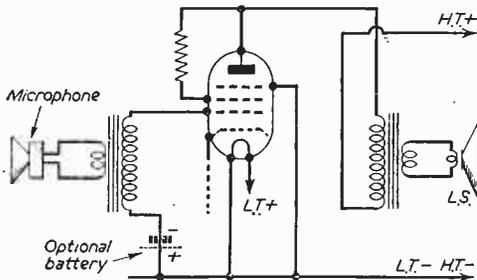

An amplifier for either battery or mains use may be made up on the lines shown here.

above a loud signal, the mike will have to be placed closer to the bed or cot, and if this is not satisfactory a separate amplifier will have to be used. Some receivers have radio-gram switching, and these may be used provided one switches periodically from radio to gram. This is obviously not so convenient as those receivers in which the mike is permanently connected. An examination of the radio circuit may show that the mike transformer secondary may be joined across the volume control in a permanent position, where the radio-gram switch does not have any effect on the radio. Usually, the L.F. volume control operates on both radio and gram, and the switch in many cases merely short-circuits the radio input, and thus anything across the volume control will always be in circuit (Fig. 4). In many cases the inclusion of the transformer secondary will not seriously affect radio reproduction. In extreme cases it may be necessary to make up an adaptor which may be plugged into a valveholder on the L.F. side, and in which a lead may be connected to the grid socket. In this way the valve may be reinserted in the top of the adaptor and the mike thus connected to a suitable point.

If there are no pick-up sockets (such as is the case in many D.C. receivers) it will be undesirable to connect the microphone transformer without first making certain that there is no risk of one of the feed wires becoming "live." By connecting the secondary direct to the chassis as already mentioned, and only running the primary leads to the distant point,

however, there should be little risk, as these wires are isolated from the receiver.

Separate Amplifier

If a separate amplifier has to be built up, this may be either battery or mains operated, and the same principles as with the receiver will apply. The loudspeaker has to be matched to the output valve by a transformer, and the primary is joined to the output valve and thus carries current. Obviously, therefore, the leads here should be as short as possible to avoid loss, and therefore the output secondary should be the extension line. This has little effect upon the matching, as the low-impedance output is usually only a matter of a few ohms and a fair length of twin bell-wire may be added without seriously affecting volume.

The other great advantage of extending the input side of the mike transformer, and the output side of the speaker transformer is that it is less likely to pick up hum which might drown weak signals. If, however, it is found that the long mike leads have to be run in such a manner that hum is introduced it may be necessary to use a screened pair, but in most cases the additional expense of such leads will not be justified.

Books Received

"Microphones," by the staff of the Engineering Training Department British Broadcasting Corporation. Published by Iliffe and Sons Limited, price 15s. (postage 5d.). Size D8vo. 8½ x 5½, 114 pages, 78 illustrations. Cloth bound with jacket.

THIS book, originally written as a textbook for use in training BBC engineers, has now been made available by the BBC for general publication. It will prove of great interest and value to all concerned with microphones in sound engineering, in which field the Corporation's engineering division has, of course, gained an almost unique experience over many years.

The book should be of particular value to students, but its specialized nature assumes that the reader already has a basic knowledge of electrical engineering and, in particular, of alternating current theory.

"Wireless and Electrical Trader Year Book : Radio, Television and Electrical Appliances," 1952, 23rd edition. Published at 10s. 6d. post free (with a reduction to subscribers to *Wireless and Electrical Trader*) by Trader Publishing Co. Ltd. Size D8vo. 8½in. x 5½in., 264 pages. Bound paper boards.

SINCE the "Wireless and Electrical Trader Year Book" was first published in 1925, it has become firmly established as the retailers' invaluable reference book to the radio and electrical industries.

In the 1952 edition, data of practical use to dealers in the new television areas and general reference and technical information have been carefully selected. Features include condensed specifications of current 1952 commercial television receivers (with such valuable facts as valves used, I.F. values, etc.), and information on valve and cathode-ray tube base connections, with over 200 valve base diagrams. These alone are invaluable to radio and TV service engineers.

Presenting Technical Information

AN ACCOUNT OF EFFORTS TO ACHIEVE STANDARDISATION OF TECHNICAL TERMS, ABBREVIATIONS AND CIRCUIT PRESENTATION

By John Scott-Taggart, M.I.E.E., M.I.Mech.E., F.Inst.P., F.I.R.E.†

THE need to "talk the same language," first realised by our arboreal ancestors, led to only the most moderate success. The Tower of Babel—or lack of adequate communications—prevented prehistoric grunts from developing into a universal language. With less excuse, fifty years of radio have failed to produce a universally agreed technical vocabulary even in the English tongue. Vigorous attempts, however, are now being made to stop the rot. This article sets out some of the standards we are told to follow in our use of technical terms, abbreviations, mathematical and graphical symbols, and in our presentation of circuit diagrams.

Nobody really enjoys being regimented, but the complexity of modern society has made us readier to accept rules and regulations; a generation that agrees to spending three months in gaol for sprinkling sugar on a doughnut should not cavil at a few technical rules. Who makes these regulations and what is the penalty for breaking them? The chief authority in this country is the British Standards Institution whose committees include representatives of the Fighting Services, the Post Office, Ministries, Industries, and Old Uncle Tom Cobley‡ and all. After incredibly long periods of gestation, booklets and pamphlets emerge and are sold at an incredibly high price. Probably not one in ten thousand technicians has ever seen one of these precious publications. A major tactical blunder has been the failure to consult adequately with and obtain the co-operation of technical publishers. The result is that few, if any, electronic journals and textbooks adhere completely to the Standards. Obviously, the publishers either disagree with the decisions or allow a wide discretion to their authors. In addition to the B.S.I. there are standards committees of large public bodies such as the Fighting Services, the Post Office, the BBC and the various learned societies such as the Royal Society, the Institution of Electrical Engineers (I.E.E.), the Institute of Physics. These bodies have, in the past, made parochial rules which have sometimes conflicted with the B.S.I. or with each other, but in major matters they are becoming increasingly willing to agree.

As regards enforcement of the rules, the Governmental bodies can rely on their disciplinary powers. The learned societies either edit the manuscripts or compel their members to alter them. Even the most influential scientist would have his paper rejected if he refused to comply. Many learned societies now issue booklets on the preparation of papers—and these are so fearsome and intimidating that some independent spirits might tend to lose heart.

In general, radio and electrical concerns go their own way, using their own terms, circuit conventions etc. Clearly, a great deal of propaganda will be necessary to change this chaos. Firms having con-

tractual relations with Government departments are being urged to keep to the standardised conventions; it is clearly undesirable that commercial blueprints and handbooks should differ in presentation from the Service handbooks. The Services and the Post Office have always tried to give some sort of unity to their publications, even if the unity has not been like anyone else's unity. The Navy clung desperately to the jar as its unit of capacitance, as if blind to the use of the microfarad by the rest of the world. It needed an Admiralty Fleet Order of 1937 to admit the microfarad wine to the old bottles.

Periodically, the tired bleat arises: "Does it really matter?" No more, perhaps, than if every member of the Fighting Services designed his own uniform (a privilege confined to American five-star generals). No one wants to change the technical phraseology habits of a lifetime, and sales-resistance to standardisation is in the megohm range. Authors and publishers of textbooks may have their works rendered old-fashioned overnight by the publication of a new standard.

On the whole, the committees are human. They "prefer" certain terms without anathematising common alternatives. A much stronger line is taken as regards graphical symbols; the symbols are printed and you must use them. Abbreviations (e.g. db, kc/s) are likewise laid down. The learned societies go further and give rules for spelling and punctuation and tell you when to spell out words in full.

It is now much too late to say you disagree with some of the standards decisions. We all disagree with some and the "standard" is usually the result of a compromise. Some decisions cry aloud to Heaven for amendment and in about ten years' time they will, no doubt, be altered. Meanwhile, we must take the rough with the smooth. A start must be made somewhere and to condemn standardisation because one disagrees with an occasional decision, or because one feels finality has not been reached, is like objecting to the rule of law because the law will later be altered. Most of the published decisions will hold good for many years. The chief trouble is that our standards are being constantly bedevilled by the Americans. As they publish many more technical books than we do and as their research facilities are so colossal, the pressure of transatlantic conventions is almost overpowering. In the end they often win the day (our shining new word radiolocation was no sooner minted than it was ousted by radar). Unfortunately, the best American conventions are often better than ours.

Spelling

Rules for spelling have been laid down by most bodies, but there is no single universal standard. Some authorities use the ending -ize and others -ise, some -exion and others -ection. All these endings are correct, but should clearly be consistent in a book or journal. Some think -ize and -exion give "tone";

* Based, by permission, on an article by the same author in the "Naval Radio and Electrical Review."

† Admiralty Signal and Radar Establishment.

‡ Also spelt Cobleigh, Cobligh—another case for standardisation.

others dislike these endings because they are unnecessary educational traps and are regarded as snobbishly archaic. Many printers insist on these endings and will alter your spelling without your permission.

The suffix "ize" is used (if at all) where it derives from the Greek (e.g. realize, harmonize, economize, recognize, minimize, polarize, ionize, synchronize, synthesize, stabilize) and in invented words. Never should the following words be terminated with -ze:

advise	disguise	incise	premise
analyse	electrolyse	mortise	prise
comprise	excise	paralyse	revise
despise	hydrolyse	practise	supervise
devise	improvise		

If, therefore, you favour -ize, you must remember the above exceptions. Thus, "harmonic analyzer" is wrong. The ending -exion is optional in reflexion, inflexion, deflexion, connexion; the Institute of Physics insists on -ize and -exion; the I.E.E. likes -ize but insists on reflection, inflection, deflection, connection; B.S.I. use -ize but not -exion.

Compound words are the biggest headaches. The history of terms consisting of two words follows a pattern: The words are first separate, then hyphenated, then joined. This has happened to headmaster and waveguide but, absurdly enough, the time must be ripe for each step. If, like most Americans, we boldly joined words together we should avoid present anomalies. Why, seven years after B.S. 204 : 43 spelt it waveguide, should the Institute of Physics insist on wave-guide? And why should B.S.I. use wave-trap if it likes waveguide? Why carrier wave and spacing-wave? On the first page of the Inter-Services Glossary we have radiotelegraphy, radio communication, telecommunication. Why does not the B.S.I. adopt afterglow, timebase and flyback (after all, they give feedback, flashover and even pushbutton)?

A hyphen is usual in adjectival terms such as maximum-voltage setting, low-resistance path, solid-dielectric plug; a plurality of hyphens may be necessary, e.g. barium-oxide-coated cathode. Hyphens are becoming increasingly popular but one wonders whether "5-Y battery" is justifiable although "10-amp fuse" is commonly found. These hyphens are correct only when the terms are adjectival. There seems to be a case for nouns such as series-resistance, dielectric-constant, tuning-capacitance, hand-capacitance.

There is a growing tendency to use lower-case (small) letters instead of capitals in abbreviations such as e.m.f., a.c., d.c., r.m.s., p.d., h.t., l.f. The B.S.I. favours capitals, but they are fighting a losing battle; the Royal Society and the I.E.E. require lower-case letters to be used. Incidentally, the I.E.E. favours spelling-out units, e.g. 5 volts, 300 ohms. Other than technical considerations are sometimes involved. The insertion of Greek letters is an additional printing expense. The aesthetic appearance of a page is sometimes a consideration; some publishers dislike the percentage sign % and use per cent. The absence of Greek letters on most typewriters discourages the use of Ω in reports, although μ can be faked by the typist. There is a convention that the initial letter of a lower-case abbreviation should not be a capital; this means that A.c., E.m.f., L.f. are undesirable and a sentence may have to be recast to avoid starting in this way

(e.g. after a full-stop); in fact, it is usually undesirable to begin any sentence with an abbreviation.

Technical Terms

Changes in some terms are inevitable. When an art settles down, the technical terms, hurriedly suggested perhaps by an inventor, are found inadequate or even vulgar. Radio has long since shed its swaddling-clothes but many of its nurses are still alive; it is not surprising that much of the

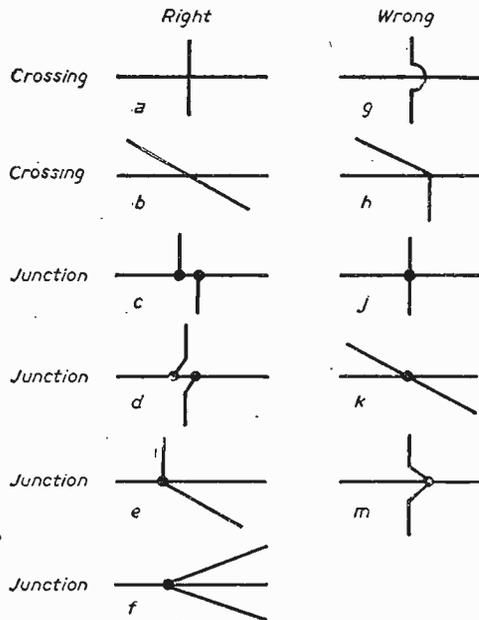


Fig. 1.—Crossings and junctions in circuit wiring.






























baby-talk has survived. There are few terms which could not be hotbedded, but usually at the expense of brevity.

The concrete nouns resistor, inductor and capacitor have replaced resistance, inductance and condenser. Resistor, after a fight, was accepted, but some die-hards will cease to use the word condenser only on their death-beds. The abstract noun is capacitance, not capacity. Feedback is now officially accepted but before negative feedback became popular it was regarded as a vulgarism on a par with tickler coil. The Services now call a wavemeter a frequency meter, although in B.S. 204 wavemeter is preferred.

Popular terms are, in general, on the way out. Superlatives have had a chequered career and terms like very-low, very-high, ultra-high, super-high and extremely-high frequency make one reach for the book to find out what they mean or whether they even exist. There are many electricians still alive who called 50 cycles per second "high frequency" when 25 cycles per second was becoming obsolete. The Services—for the moment—recommend that one should, where possible, speak of millimetre, centimetre, decimetre, metre, short, medium and long waves.

The coded radio frequency bands in B.S.204 : 1943 are:—

STANDARDISED SYMBOLS

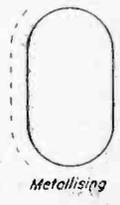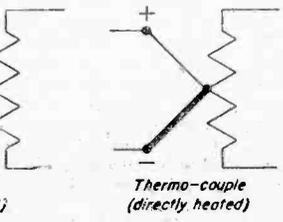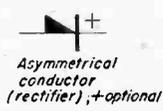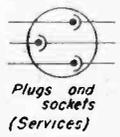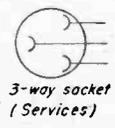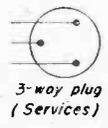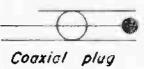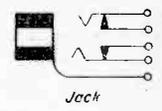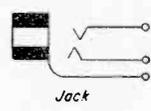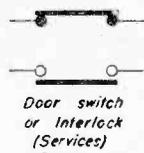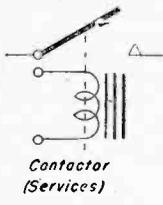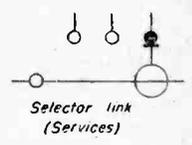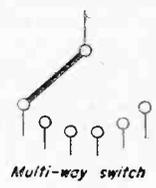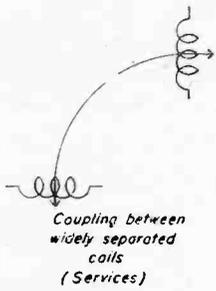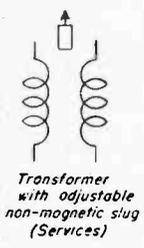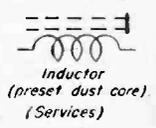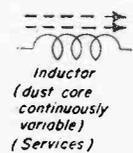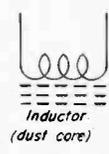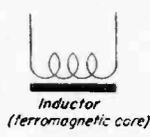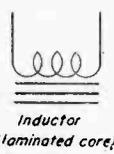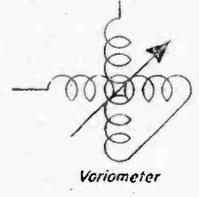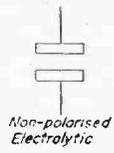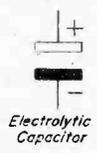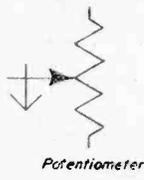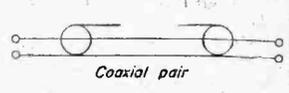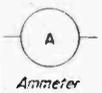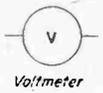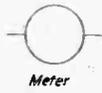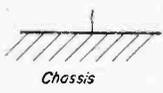

VLF very low freq. Below 30 kc/s.
 LF, low freq. 30-300 kc/s.
 MF, medium freq. 300-3 000 kc/s.
 HF, high freq. 3 000-30 000 kc/s.
 VHF, very-high freq. 30 000-300 000 kc/s.
 UHF, ultra-high freq. 300 000-3 000 000 kc/s.
 SHF, super-freq. 3 000 000-30 000 000 kc/s.
 The Services also use this code; super-frequency, however, is called super-high frequency, and covers frequencies greater than 3 000 Mc/s.

The term cat's whisker is still blessed by standards committees, as is keep-alive electrode. Push-pull is less favoured than balanced valve operation. Grid-leak is retained although obviously unsuitable if there is negative bias preventing grid current (why not grid-resistor?). As regards the multi-vibrator family, the official terms are stable trigger circuit, flip-flop and multivibrator, although better terms would be monostable, bistable and astable relaxation circuits. One-shot multivibrator is rightly deprecated. The word indiarubber is replaced by rubber and V.I.R. cable becomes V.R. cable.

Radiolocation now covers D.F. as well as radar. Radar covers both the ordinary echo system and secondary radar (where there is automatic re-transmission) provided the delay in evoking the retransmission is sufficiently short and precise for the range to be measured.

Transmitter blocker is the term to be used for what has been called A.T.R. switch and anti-T.R. box; but T.R. switch is retained. The designation of waveguide modes (H or TE, E or TM) is still undecided in this country, although most Americans have chosen TE and TM; the order of the subscripts has, however, been standardised (though our standard is, almost inevitably, different from the American one). Voltage standing wave ratio is minimum/maximum; in America it is maximum/minimum. The American term grounded-grid triode is preferred by the Services. The word oscilloscope is now almost always used in this country, although it does not appear in any B.S. glossary; oscillograph does appear, but is rarely used.

jargon may be mentioned. A vivid picture is conjured up by "the cathode sits at earth, the anode dropping till it bottoms." But is it English? Such loose shorthand as "R charges C2" has confused many.

B.S. 204 : 43 defines electrode D.C. resistance as the ratio of the D.C. component of the electrode voltage to the D.C. component of the electrode current. (The purists may object to D.C. resistance, but here is B.S. authority for it.) Electrode impedance is the ratio of a small alternating change in electrode voltage to the corresponding alternating change in electrode short-circuit current, no intentional variation being introduced into the other conditions. The reciprocal is electrode admittance. Slope resistance (preferred to electrode A.C. resistance and electrode differential resistance) is the resistive component of the electrode impedance when measured at a sufficiently low frequency. A variable-mu valve is one in which the mutual conductance can be altered smoothly over a wide range by variation of grid bias.

Transconductance (from one electrode to another) is defined as the quotient of the in-phase component of the short-circuit alternating current of the second electrode divided by the alternating voltage of the first electrode, all other electrode voltages being maintained constant. (The I.E.E. prefers active current to in-phase component of the current.) Mutual conductance is the "control-grid to anode" transconductance measured at a sufficiently low frequency.

Deflector plates (X1, X2 for horizontal deflector, Y1, Y2 for vertical deflector) and deflector coils (usually designated X for horizontal and Y for vertical deflector) are the correct terms. There are important rules for numbering deflector plates (see B.S. 530 : 48). The pattern appearing on the screen of a C.R.T. is called the trace. Time base is the deflection of the spot which is defined in relation to time. Time-base generator is preferred to time base when describing the apparatus for producing the necessary voltage or current for establishing a time

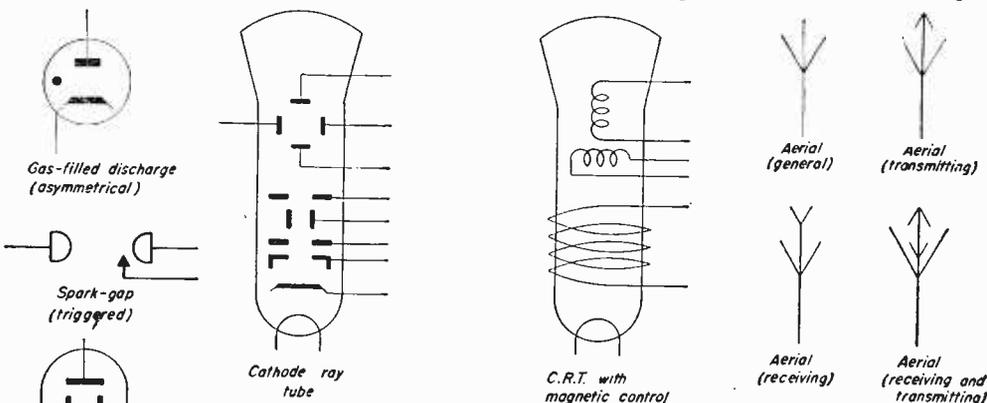


Fig. 2.—Further theoretical symbols.

The I.E.E. accepts such horrors as *outage* and *throughput*, but scorns the very useful word *circuitry*. Wattage is called jargon but is "acceptable"; one wonders when they accepted voltage. The question of laboratory

base. Electron gun is the system of electrodes which produces an electron beam. Accelerator (preferred to anode), modulator electrode (preferred to control electrode and grid) and focusing electrode are electrodes in a C.R.T.

(To be continued.)

B7G BATTERY MINIATURES

POPULAR CIRCUITS MAKING USE OF THESE SMALL VALVES

By F. G. Rayer

A LARGE number of readers appear to be interested in building up portable and "personal" receivers employing the all-glass, button-based miniature valves now available. These valves are economical and efficient, and it is proposed to discuss some of the circuits which will be found satisfactory for use with them, indicating suitable component values, and the kind of results which may be expected. These circuits may be copied exactly as they stand, or used as a basis for receivers of similar type.

screen grid voltage $67\frac{1}{2}$. The maximum anode and screen voltages of the 1S5 are 90 in each case. Except when small batteries are used, these maximum figures must not be overlooked.

In all the following circuits a 1.5 volt dry battery is used for filament supply, and any of the equivalent types described may be used, though the type numbers actually shown are readily available.

A Two-valver

This is a good starting point for a small "local station" set, and the circuit in Fig. 1 is particularly straightforward. With an ordinary dual-range coil and aerial and earth, good loudspeaker results will be obtained. Used with a frame aerial whose perimeter is preferably not less than 3ft., moderate speaker reproduction can be obtained from local stations; headphones may be used for distant reception, or if circumstances make a speaker undesirable.

A few points require note. The intervalve coupling transformer should best be of good quality and high impedance, in view of the pentode detector. A poor transformer will reduce volume. If size is no object, an ordinary 5in. or 6in. speaker is best. If a midget speaker is used it should be of reliable manufacture and supplied with a matching transformer suitable for use with it. Some midget speakers have 15 ohm speech-coils, and if used with the usual 2-3 ohm speaker transformer will give very poor results. Also make certain the transformer is definitely intended for use with a high-impedance battery-type pentode.

If headphones are to be used, a 1T4 may be used for output. This will reduce both filament and H.T. consumption. The auto-bias resistor may remain at the value shown (700 ohms).

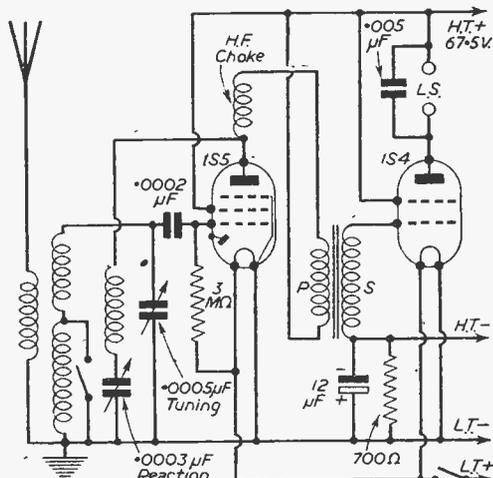


Fig. 1.—A two-valver for speaker and 'phones.

Valve Types and Equivalents

Four main valve types are available in this range. The 1R5 is a frequency-changer, and satisfactory frequency changing may be attained with anode and screen voltages as low as 20, which makes it suitable for receivers embodying miniature batteries. A.V.C. can be applied. The Marconi-Osram equivalent is the X17; the Mullard equivalent the DK91. As with the 1T4 and 1S5 types, the filament is rated at 1.4 volts .05 amp.

The 1T4 is a V.M. pentode for radio-frequency amplification. Its equivalents are the W17 and DF91. It may also be used in the intermediate stages of L.F. amplifiers, or for output purposes where small power is required (as when phones are operated).

The 1S5 (equivalents are the ZD17 and DAF91) is a diode-pentode, suitable for detection and L.F. amplification in superhets and straight receivers. The 1S4 is a beam output tetrode, giving outputs of up to .075 watt, with 45 volts on anode and screen. (Output is increased to .18 watt with $67\frac{1}{2}$ volts, and .27 watt with 90 volts.) Its equivalent is the DL91, and its output sufficient for speaker operation in small portables. It has a 1.4 volt .1 amp. filament. As with the 1R5 and 1T4, the maximum anode voltage is 90, and maximum

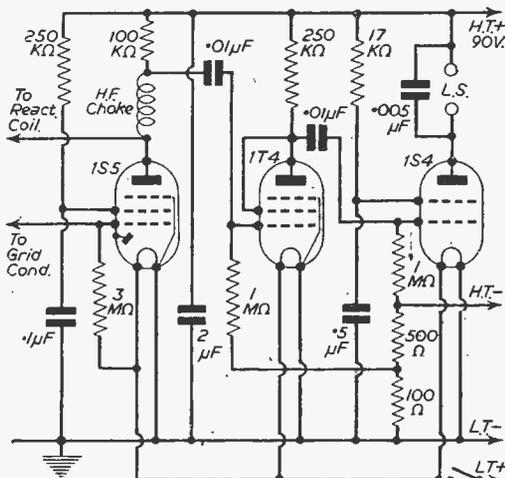


Fig. 2.—Resistance capacity coupling in a 0-v-2 circuit.

indicated in Fig. 5. These are to be taken as viewing the sockets of the holders from below, and only one or two points require mention.

Due to the method of supporting electrodes by the valve pins themselves, some electrodes have duplicate connections. This is so with the 1S4 anode, and either socket may be used, as convenient. All valves except the 1S5 have duplicate filament negative pins; these are joined internally, and also go to the suppressor grids in 1R5 and 1T4, and internal shield, in the 1S4.

Finally, the 3S4 should be mentioned. This has a tapped filament, and with sections wired in parallel it is the equivalent of the 1S4. With filament sections in series, the filament is rated at 2.8 volts .05 amp. (as against 1.4 volts .1 amp. when in parallel).

The circuits given are the result of practical experiment and testing, and may be made up with confidence.

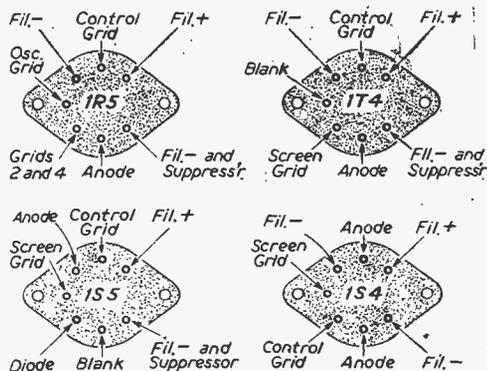


Fig. 5.—Valve base connections for the valves described in this article.

Handy Velocity Microphone

By W. A. Little

SO many war-surplus radio parts are now available that the average experimenter very often has a box full of what his wife calls "junk," which he does not wish to lose, yet can find little use for in the workshop. Here is a way of proving that it is not junk, and also providing yourself with an inexpensive ribbon microphone.

The materials required are:

- A small milliammeter (with a burnt movement),
- Some silver cigarette paper,
- A miniature input or output transformer,
- An old hacksaw blade,
- A cigarette tin and a few screws and washers.

Last of all you will want a gauze kitchen sieve of about 1½ in. in radius.


Construction

Remove the meter from its case by removing the three screws at the rear of it. Take off the dial and remove the two screws which hold the horseshoe magnet in place. Now the rest of the meter may be returned to the "junkbox" while the magnet is retained. Take an old miniature hacksaw blade (one with a blade about ½ in. in breadth), and break off ten squares ¼ in. by ¼ in. and hammer these flat. Pile these on to the poles of the magnet—five each side. The magnet will usually retain these in place, but if the microphone is to be subject to rough usage it would be as well to cement these pole pieces in place with a little adhesive.

The Ribbon

The ribbon is made as follows: From a sheet of foil from a cigarette packet, cut a strip 1½ in. in length, by ¼ in. in breadth. Place this between two sheets of corrugated cardboard and press the two together. Carefully remove the corrugated ribbon of metal from the cardboard and mount it on the two screws as shown in the diagram. The ends of the ribbon are clamped between two flat, thin, tin washers which may be cut from a cigarette tin;

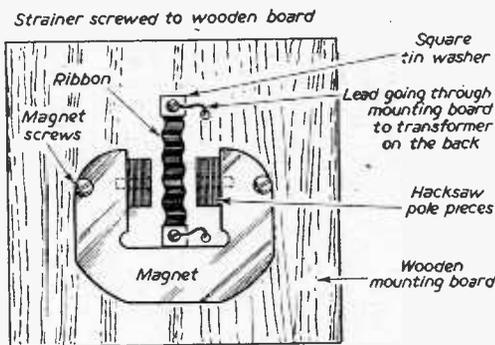and which are themselves mounted on two thick washers which raise the ribbon well clear of the mounting board. Solder a lead to each side of the ribbon holder and connect these to the low-impedance winding of the transformer. Mount the magnet so



Details of the microphone.

that the ribbon lies on the edge of the strongest part of the field, and screw it into place.

The sieve may now be screwed down to cover the whole. This gives it a professional appearance and protects the delicate ribbon from damage. The microphone is now ready for use. The output from the high-impedance winding of the transformer should be fed to a pre-amplifier or high-gain amplifier, and it will then provide sufficient power to satisfy the average experimenter.

NOW READY!

The Entirely New 12th Edition of The Famous Standard Work

THE PRACTICAL WIRELESS ENCYCLOPEDIA

By F. J. CAMM

Price 21/-, or 21/10 by post from:

GEORGE NEWNES LTD., Tower House,
Southampton Street, Strand, W.C.2.



On Your Wavelength

By Thermion

When is L.P.R. Not L.P.R.?

A READER propounds the question which titles this paragraph. He has purchased some L.P.R. records and finds the following:

- 1st side, 14 mins. 12 secs.
- 2nd side, 12 mins. 50 secs.
- Total 27 mins. Cost 39/6 (12 in.).
- 1st side, 11 mins. 45 secs.
- 2nd side, 15 mins. 5 secs.
- Total 26 mins. 50 secs. Cost 39/6 (12 in.).
- 1st side, 14 mins. 30 secs.
- 2nd side, 12 mins. 30 secs.
- Total 27 mins. Cost 29/6 (10 in.).

From these timings, he says, it would seem that the first two recordings could have been made on a 10in. record and he asks why they were spread to 12in. at an extra cost of 10/- each. This is a matter for the manufacturers who, I am sure, have a satisfactory answer. Like my reader I have a fair collection of 12in. and 10in. L.P. discs. One of them plays for 42 minutes (21 minutes each side). My reader seems disappointed and says that there is little advantage in forsaking the tried and trusted 78 r.p.m. My own experiences with L.P.R. are that the machine needs to be set very accurately with a spirit level, that the slightest walking causes the pick-up to jump and that they are more finicky than 78 r.p.m. records. The price, too, does not bear an accurate ratio to the increased playing time. That is to say, you can obtain longer playing time from an equivalent expense in 78 r.p.m. records. It would be unfair, however, in these comparatively early days of L.P.R. to be unduly critical. Those best qualified to know say that L.P.R. is inevitable, that the records last much longer because of the lower surface speed and that they are of vastly superior tonal quality. The price of a record is not, moreover, decided by its playing time. There are other factors such as royalties.

A Collector of Old Sets

MY recent reference to old time radio receivers has elicited a letter from Dr. Michael J. Dunn, of Bristol, who says that he has been searching for some of the early receivers but says that the genuine antiques of radio are extremely rare, especially in working condition. He adds that radio dealers throw them straight into the dustbin, and even when they are obtainable the price for a complete set without valves is from 2/6 to 5/-. He purchased a single-valve, complete with coils and valve, for 2/- and upon connecting it up found that it was in perfect working order and received English and foreign stations. His best find was a valve marked "Osram, valve receiving, R2A." This is one of the earliest valves and was produced for the forces in the 1914-18 war. It is, of course, a bright emitter, with a rated voltage of

3.8 with a current consumption of 1.2 amps! It is a helium-filled triode requiring a maximum anode volts of 38. At anything in excess of this it delivered a delightful blue glow! One could read by some of these early valves.

Magnetic Tape Recording.

MR. C. PARKER, of Bath, responds to my invitation to readers to send details of their experiments with magnetic tape recordings which has the advantage of continuity of playing and ability to erase a bad or no longer required recording. The tape recorder need not be dearer than the disc equivalent. A half hour programme, recorded from the radio, may be recorded on tape with ease, and a response of 10,000 c/s running on an 11in. spool at 15in. per second is possible, whereas to record the same programme on discs without a break requires two turntables and numerous discs. It would seem the tape recorder should be cheaper than a disc and very much cheaper than a twin turntable outfit.

The lack of literature on the subject is probably responsible for so little having been done by the amateur constructor. Most of the published matter is theoretical dealing with hysteresis curves, coercivity, etc. This reader gives the following specifications of what he considers to be ideal:

1. A.C.-operated 230 v. 50 cycles.
2. Two speeds. One for hi-fi reproduction of music, and a slower one for occasions where hi-fi is not required, i.e., speeches, parties, etc.
3. Dual-purpose amplifier giving adequate playback output, say 8 watts.
4. Standard 1/2 in. tape in preference to wire.
5. Erase head.
6. Combined record/playback head if saving in cost justifies it.
7. Desirable response on the fast speed, 50 to 10,000 c/s.

I understand that a tape recorder is the subject of experiment in the P.W. laboratory.

The R.E.C.M.F. Components Show

THE 1952 Components Show, organised by The Radio and Electronics Component Manufacturers Federation, mirrored the process in component design which has taken place during the past year. Although the exhibition is a private one and, indeed, was organised during the war, it has become of increasing interest to designers and manufacturers of radio and television receivers and of radar and electronic equipment. It attracts overseas buyers of components. This year it was obvious that the armament programme was responsible for some of the components shown. The specifications of some of them are much higher than is required for ordinary domestic apparatus. Components suitable for the home constructor were not so conspicuous as in former years for this reason.

TRANSMITTING TOPICS



Variable Frequency Oscillators

CONSIDERATIONS IN TRANSMITTER DESIGN By O. J. Russell, B.Sc. (G3BHJ).

TWO previous articles have covered fairly completely the subject of ordinary crystal oscillators. However, it is not intended to cover more than certain considerations involved in the various stages of amateur transmitters. For those who prefer a specific design, it is hoped later to describe complete units which will illustrate the practical realisation of design practice.

It is certainly very true that a number of relatively minor points may decide the correct functioning of a piece of equipment. This is very true even of a simple and "sure-fire" item, such as a crystal oscillator. Thus the oscillator valve may greatly influence the ease and certainty with which the oscillator will key satisfactorily, especially when operating on harmonics. In point of fact the 6AG7 is an extremely satisfactory valve to use for both crystal oscillators and variable frequency oscillators (V.F.O.s), as the isolation between the anode

in a V.F.O., and this means not only freedom from drift during a period of use, but also dynamic stability in the sense of freedom from chirp under keying. For this reason it is as well to put the cart before the horse, and to emphasise the test routine desirable in checking a newly constructed V.F.O. It might be said that a V.F.O. with a fundamental frequency in the 1.7 or the 3.5 Mc/s band will sound perfectly steady and chirp-free if monitored upon its fundamental frequency. However, as recommended with crystal oscillators, it is desirable to check a high harmonic of the oscillator, and for this reason the 14 Mc/s or the 28 megacycle harmonic should be monitored. With a normal communication receiver there is no difficulty in locating these harmonics. A rapid check may be made, using the receiver B.F.O., and it will be found that a clear steady note under keying on a low harmonic may deteriorate to an unsteady, chirpy note on the next harmonic. Thus on 3.5 Mc/s the note on a quick check may sound rock steady and equal to crystal; on 7 Mc/s chirp and drift may be imperceptibly slight, yet on 14 Mc/s the same oscillator will sound chirpy with detectable drift; while on 28 Mc/s it will sound rough, chirpy and have a marked degree of drift.

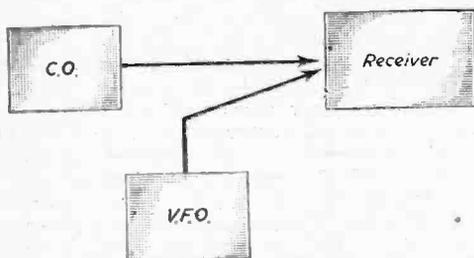


Fig. 1.—Test Set-up for checking V.F.O. A harmonic of the V.F.O. is checked against a harmonic from a crystal standard. In this way V.F.O. defects are multiplied by the order of the V.F.O. harmonic.

and grid circuits is superior to other popular tetrode and pentode oscillator valves. This superior isolation greatly reduces "pulling" effects, so that frequency is little affected by loading changes in the anode circuit.

Stability

Stability is, of course, the most desirable feature

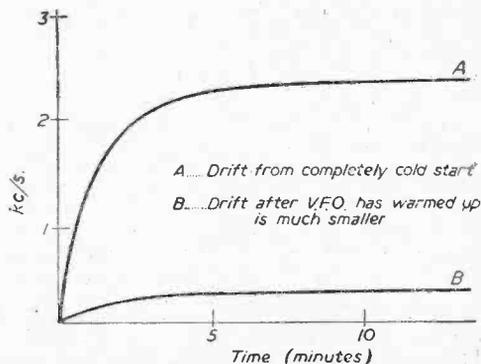


Fig. 2.—This graph shows the differences in starting up from cold and after being warmed up.

Observation will soon convince the experimenter that a degree of chirp and drift that is tolerable on one frequency becomes intolerable when these defects are doubled by moving to the next highest amateur band. There is in fact about a two-to-one difference between a passable note and a bad, chirpy one. This is quite apart, of course, from such items as A.C. ripple and hum modulation, as no serious amateur is likely to feed a V.F.O. from an unbalanced, badly-smoothed power pack. However, a little listening upon the C.W. section of the 20-metre band should soon prove that it is by no means "easy" to produce a good V.F.O. signal at 14 Mc/s. Yet on 7 Mc/s signals are by contrast much better, and a really bad note is seldom encountered.

The aim of the V.F.O. constructor should be to produce as satisfactory a performance as possible before actually going on the air. Even here there is a trap for the unwary, for when coupled up to a transmitter operating at a reasonable level of R.F. power, interaction, loading effects on the V.F.O. and R.F. feedback effects may cause the overall stability to be much worse than when the V.F.O. alone is being tested. For that reason the ultimate test of a V.F.O. is the functional one of operation in a complete transmitter. In view of the complete monitoring of the bands, quite apart from questions of courtesy and regard for others, such a test should not be performed while radiating a signal. The transmitter can just as easily operate into an artificial load of a high-power lamp bulb, so that direct functional testing can be carried out without causing unnecessary Q.R.M. Even then the final proof will need an air test, as direct R.F. pickup of energy radiated from the aerial can cause disturbing effects. However, if a systematic series of tests is carried out *before* attempting to radiate a signal, then it will be easy to effect improvements stage by stage, rather than be faced with correcting a bad signal with no guide as to *how* the defect is caused.

All this may seem very tedious to the newly licensed amateur anxious to get on the air. However, it should be realised that most amateurs in the past slowly advanced through the difficulties of evolving a stable transmitter. Nowadays, with a V.F.O. controlled installation a virtual necessity for competitive D.X. working, the newcomer has to try to telescope the results of experience into a short period, and has little time to spend on laborious trial and error. Unless he is prepared to start on the right lines, he is likely to take the path of least resistance and radiate a less-than-perfect signal. This is, in fact, by no means a monopoly of the newcomer, and anything which helps to ameliorate some of the worse effects of imperfect notes is welcome today. It is fatally easy to "get on the air" at all costs, and be so eager to operate, that a poor note is overlooked and the job of correcting it put off indefinitely. To start "right" is thus ultimately a great saver of time, and an even greater contribution to pleasant listening for others.

With this object in mind, we can consider a simple test set-up for checking the stability and performance of a V.F.O. Under the licence conditions, an approved form of wavemeter should be available and this almost invariably contains a crystal check oscillator. It is much more satisfactory to use a crystal oscillator for checking purposes than the B.F.O. of the station receiver. A receiver itself contains—if, as is certain, a superhet is used—its own V.F.O. in the shape of the

mixer oscillator. If the receiver B.F.O. is used, the receiver stability sets a limit. To avoid complications, therefore, switch off the receiver B.F.O. and locate a suitable crystal harmonic. This should preferably be one lying in the 28 Mc/s band to give a critical and sensitive check on stability. At any rate, choose as high a harmonic as possible. If the test crystal is a high-stability 100 kc/s or 1,000 kc/s standard crystal, this will give excellent results, but an amateur band crystal used in a very low-power, under-run crystal oscillator can be used if nothing else is available. Locate the crystal harmonic upon the receiver and, with the B.F.O. switched *off*, tune the V.F.O. so that one of its harmonics beats with the crystal. The crystal oscillator, allowed to warm up for some ten minutes or so, will maintain frequency to a high degree of precision to within a few cycles over long periods. Having located the V.F.O. to beat with the crystal harmonic, tune the V.F.O. to zero beat and switch it off. After allowing a few minutes for cooling, switch on again and observe the drift from a cold start. At 28 Mc/s it is quite likely that drift will exceed a kilocycle, and may even be enough to take the note out of the audible range. With the V.F.O. warmed up, the effect of keying can be noticed and chirp and ripple noted. It is likely that a neon-stabilised power supply will be used, and the effect of removing stabilisation can be observed. A large amount of the drift on warming up from cold is due to the heating effect of the valve heater. When the cathode has been warm for a considerable time under these various tests, the amount of drift likely in a period of transmission can be checked. To do this keep the heater

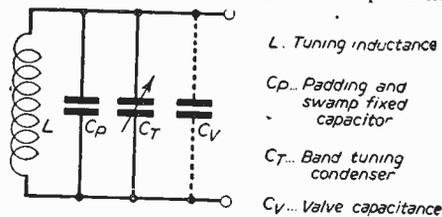


Fig. 3.—V.F.O. tuned circuit.

alight, but keep the key up so that the oscillator draws no current. Then depress the key, and notice the degree of drift occurring over a period of a couple of minutes. This will be far less than the drift from a cold start, as shown by the curves of Fig. 2. If a large amount of drift does occur under these conditions, it indicates that the V.F.O. valve is running with too much power input, so that the heat dissipated at the anode contributes appreciable drift. The cure, apart from circuit modifications, is to reduce the power level of the valve to minimise heating. In the interests of stability a V.F.O. should be lightly loaded and run at a low-power input.

Design Factors

The above tests have been placed first before considering V.F.O. circuit designs, because it is essential that careful tests be made upon the operation of a V.F.O. at the start. With a systematic test procedure, optimum performance can be obtained during construction and will obviate many pitfalls. We can now consider some of the design factors before referring to actual V.F.O. circuits. In point of fact, if the correct design precautions are taken there is little to choose between *any* of the popular oscillator

circuits. However, certain circuits enable satisfactory results to be obtained conveniently.

Before considering the oscillator circuits themselves, consider a tuned circuit. A tuned circuit in some form is an essential part of a V.F.O. A crystal oscillator derives stability from the fact that the crystal is mechanically a stable device, and is equivalent to a very high Q circuit. A high Q circuit in a V.F.O. assists stability and, other things being equal, the V.F.O. with the higher Q circuit has the higher stability. It must be remembered that the oscillations in the V.F.O. frequency-determining tuned circuit are maintained by a valve. The influence of the valve on the tuned circuit largely contributes to instability. Thus, the valve by itself has a physical capacity which must be included in the total tuning capacity resonating the tuning coil. When the valve warms up due to the heater, and also due to the anode dissipation, its physical capacity changes slightly, and this will affect the operating frequency. Electrically, however, the total effective capacity of the valve will also vary with the cathode emission, the reflected effects of the loading on its anode with the current drawn, and with electrode potentials. These electrical variations are extremely important in determining stability. Thus, variations produced by overall variations in the H.T. supply are a case in point. Neon stabilisers are commonly employed in order to minimise these changes.

The successful design of a V.F.O. largely depends upon minimising the effects of the variations in valve capacity effects, and there are several ways in which

this can be done. Thus, if Fig. 3 is studied, it will be seen that we have a swamping fixed capacity to pad out the tuning range so that the variable tuning condenser just comfortably covers the required tuning range. An additional small capacity represents the total effective valve capacity. There are several artifices for minimising the effects of the varying effective valve capacity. The most obvious one is the use of very large values of total tuning capacity, so that the valve capacity is as small a fraction as possible of the total. That this is seldom appreciated is shown by the fact that in a normal oscillator circuit for an 80-metre V.F.O. the total tuning capacity may be made as much as 1,000 pF. Incidentally, it is easy to show that, provided the oscillator circuit is designed for a constant L.C. ratio, there is no advantage to be gained by using a very low-frequency V.F.O. and multiplying up. The intrinsic stability of the final signal due to valve capacity changes is no greater than a V.F.O. operating on a higher frequency with fewer multiplication stages. The only gain is the greater freedom from pulling and feedback due to the use of more isolating multiplier stages. A further means of reducing instability due to valve effects is very loosely to couple the valve to the tuned circuit. Practical circuits use either or both of these methods to obtain high stability, as we shall see later. It is, of course, essential that the tuned frequency determining circuit of a V.F.O. should be mechanically designed to minimise vibration and possibility of movement. Wiring should be carried out with heavy-gauge wire.

(To be continued)

North East Broadcasting

THE Postmaster General, the Right Honourable The Earl De La Warr, received representatives of the North East of England to discuss the possibility of providing a television station at Pontop Pike and to improve sound broadcast reception. The deputation consisted of:

Alderman Wm. McKeag, The Lord Mayor of Newcastle upon Tyne.
 Lord Ravensworth, Rural District Councils (Rothbury).
 Alderman E. Hill, South Shields County Borough Council.
 Councillor D. Richmond, Borough Councils (Hartlepool).
 Councillor Dr. K. Mitchell, Urban District Councils (Hexham).
 Mr. C. W. Hurley, Deputy Clerk of Northumberland County Council.
 Mr. A. S. Ruddock, Clerk of the Whitley Bay Urban District Council.
 Lord Lambton, Miss Irene Ward, M.P., Sir Fergus Graham, M.P., Mr. R. Speir, M.P.

Alderman McKeag, Lord Mayor of Newcastle upon Tyne, said that the North East felt that they had had a raw deal both in regard to television and the sharing of a sound wavelength with Northern Ireland.

Lord De La Warr said he felt quite unable to attempt to controvert the Lord Mayor in what he said about the difficulties from which the North East was suffering in relation to its broadcast services. For that reason he regretted deeply that at the present moment demands on material and skilled labour could give no hope of rectification of the position.

"Frig." Interference

THE Postmaster General's Advisory Committee on Wireless Interference from Refrigeration Apparatus, which was appointed to sit under the chairmanship of Dr. F. T. Chapman, as announced in the House of Commons on July 26th, 1950, has presented its Report.

The Committee considered the abatement of interference with reception in both the sound and television wavebands caused by the various types of refrigeration apparatus.


The Committee's recommendations for limits of permissible interference from refrigeration apparatus are based on the assumption that reasonable precautions will be taken to minimise the susceptibility to interference of receiving installations. The Committee consider it unnecessary to specify requirements in terms of the direct radiation of interference energy. They recommend that the voltage of interference from refrigeration apparatus injected for continuous periods of not less than 1/5 second or more frequently than once in any two-second period into the electricity supply mains, measured in the manner and with the apparatus described, should not exceed 1,500 microvolts for the waveband 200-1,605 kilocycles per second (the major part of the broadcast band) or 750 microvolts for the waveband 40-70 megacycles per second (the present television band).

The Committee recommend that these requirements should be specified for both new refrigeration apparatus and for that in use and recommend that six months should elapse between the promulgation of any regulations and the time of their coming into force.

TRIBUTE TO OUTSTANDING PERFORMANCE

★
CHOSEN
FOR THE
"P.W."
MINI-FOUR

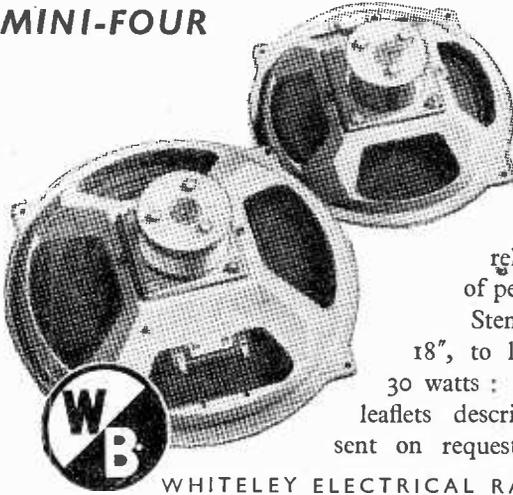Leading designers
consistently specify
Stentorians



Again and again, Stentorian Chassis are specified in new radio and television receivers for the amateur constructor — proof of their reliability and of the unvaryingly high standard of performance.

Stentorians are available in ten sizes, from 2½" to 18", to handle every output from 300 milliwatts to 30 watts: if you have not had copies of our latest leaflets describing the full range, these will gladly be sent on request.

WHITELEY ELECTRICAL RADIO CO. LTD MANSFIELD · NOTTS

HENRY'S

"PYE" 45 MC/S STRIP. Special purchase of M.O.S. Type 3583 Unit, size 15in. x 8in. x 2in. Complete with 45 mc/s Pye Strip, 12 Valves, 10 EF50, EB34 and EA50. Volume controls and a host of Resistors and Condensers. Sound and vision can be incorporated on this chassis with minimum of space. New condition. Price £5. carriage paid.

FOUR SECTION CHASSIS adaptable for the "Argus" Television lay-out, 21/- carr. pd.

CATHODE RAY TUBES. VCR97 Brand New. Guaranteed Full Picture, 45/- carriage paid; VCR19A. Suitable for Scopes, 35/- carriage paid; 3BP1. Brand New. Suitable for Scopes, 25/- carriage paid.

9in. ESCUTCHEON. Brown Bakelite. Suitable Plate glass and Mask for 9in. Tube. Price 7/6 each.

INDICATOR UNIT TYPE 182A. This unit contains VCR517 Cathode Ray 6in. Tube, complete with Mu-Metal screen, 3 EF50, 6 SP81 and 1 5UG valves, 10 wire-wound volume controls and quantity of resistors and condensers. Suitable either for basis of Television (full picture guaranteed) or Oscilloscope. Offered BRAND NEW (less relay) in original packing case at 79/6. Plus 7/6 carriage.

★ SEND S.A.F. FOR 28 PAGE CATALOGUE ★

★ A COMBINED SIGNAL TRACER AND AUDIO OSCILLATOR ★

An easy-to-build unit that can be used for I.F. and Audio signal tracing, without any switching or tuning, including variable output oscillator for amplifier checking. Highly sensitive, responds to signals picked up from an ordinary receiving aerial. The circuit is that of a high-gain 2-stage, resistance-coupled audio frequency amplifier, employing 3 miniature 1.4 valves, with a 3-inch speaker in the output of the Power Amplifier Stage. An added advantage being that as this Unit is "All-Dry" it can be used with safety on A.C. or A.C./D.C. mains and Battery sets. The completed Kit with portable cabinet (size 6in. x 7in. x 6in.) and battery weighs only 4 lbs. We shall be pleased to supply a complete Kit for the construction of the above, right down to the last nut and bolt, including 2-1T4 and 1-134 Valves, 9in. Speaker and Portable case and All-Dry Battery for £4/10/6. Concise instructions and circuits supplied. If preferred, circuit and instructions only can be supplied for 1/6. If required this Unit will be assembled and tested for an extra charge of 15/-. This is a highly efficient instrument, and a MUST for every radio man.

RECEIVER UNIT TYPE 159. Containing VR91, VR92, VR65 and 24v. Selector Switch. New condition 15/- (Post 1/6).

E.H.T. TRANSFORMER FOR VCR97. Input 230v. Output 2,500v. 4v., 2-0-2, 45/-.

E.H.T. TRANSFORMER FOR 5CP1. Input 230v. Output 3,250v. 6.3v. at 0.6ma., 2-0-2v., 45/-.

WALKIE-TALKIE TYPE 46. Containing 6 Valves, 2 of VP23, HL23/DD, QP25, TP25, ATP4, 3 I.F.T.'s 1.6 Mcs. Mike and Intervalve Trans. Aerial Rods, etc. Metal case, size 12in. x 6in. x 4in. In new condition but less transmitting components removed by the MOS. Price including carriage 35/-. Limited quantity.

No. 38 "WALKIE-TALKIE" TRANS./RECEIVER. Complete with throat mike, phones, junction box and aerial rods in canvas bag. Freq. range 7.4 to 9 mc/s. All units are as new and tested before despatch. As. supplied to Overseas Police Forces, £4/19/6. Carriage 2/6.

PUSH-PULL OUTPUT TRANSFORMER. U.S.A. potted type primary 10,000 Ω, sec. 2 Ω, 8 Ω, 15 Ω, 15 watts, 21/-.

GERMANIUM CRYSTAL DIODES, complete with full wiring circuit and diagram, 4/6.

METAL RECTIFIERS, S.T.C. 300 volts, 75 m.a., 6/-; G.E.C. 6 volts, 1 amp., 4/-; Westinghouse 12 volts, 2 amp., 12/6; Pencil

Type E.H.T. 600v. 1 m/a., 4/7; Pencil Type E.H.T. 1,000 v. 1 m/a., 6/-; 12v. 3i amps., 17/6.

S.T.C.R.M.2, 125v. 100 m/a., 4/6.

G.E.C. 1 m/a Meter Rect., 11/6.

EX.-GOVT. Valves. THE FOLLOWING ARE BRAND NEW :- EF50 Red Sylvania. Original Boxes (U.S.A.), 10/- English Types. Original boxes, 8/6. EF50 Ex Units, Guaranteed, 6/-. At 8/6 each :- EF50, EF54, EF55, CV66, EF9, EP36, EF39, EK32, EL32, EBC33, 6KTGT, 6J7GT, 6L7GT, 6SK7GT, 6SJ7GT, 6B8GT, 6N7GT, 6J5GT, 6C5GT, 6AC7GT, 6SA7GT, 6SH7GT, 6D8, 6C6, 12SA7GT, 12SK7GT, 12SJ7GT, 12SQ7GT, 12C8, 12SR7GT, 12SH7GT, 12AGT, 14A7GT, 12Q7GT, 7A7GT, 7C7GT, 7H7GT, 7B6GT, 41MP, 955, 9001, 9002, 9003, 1239A, 22D7, 9D2, 4D1, 15D2, RECTI-FIERS AT 5/- each :- VU11, VU13, VU120A, OZ4 6X5. At 8/6 each :- 524G, U50, 5Y3C. At 10/- each :- 6F7, ACPEFN, MU14, 6AM/6, 6V6GT, 5U4G, 6Q7, U52, 6AGS, PEN48, 5R4, EF91, 80. At 12/6 each :- 12K9GT, 6K9G, KT33C, 6SN7GT, 43, 6J6, 6L6, (1622 Metal). Also at 11/- :- 35L8GT, 50L8GT, KT61, VR92, D1, 3/6 :- EB34, 3/6 :- VR65 (SP61), 5/- :- RL18, 5/- :- 854, 5/- :- 6H8, 5/- :- S130, 7/6. VR150/30 and VR106, 8/6; FX25, 10/-.

ALL DRY BATTERY VALVES. 3V4, 1C5, 1T4, 1S5, 1R5, 1LN5GT, 1S4, 3S4, all at 10/- each. SP2, VP2, TDD2A, VP23, HL23/DD, all at 8/6. 2155G, KT2, PEN220A, 6/-, T2 (Super-power), 4/-, HIVAC XH, 7/6.

5 HARROW ROAD, PADDINGTON, LONDON, W.2 TEL : PADDINGTON 1038/9, 0401.

COMMUNICATIONS RECEIVER TYPE R.1155.
—YOURS FOR £417/6 DEPOSIT.


We have just bought a new consignment of these and can guarantee them to be absolutely unused (not just in re-cracked cases). This set as most will know is considered to be one of the finest communications receivers available to-day. The frequency range is 75 kc/s to 18 mc/s. It is complete with 10 valves and is fitted in a black metal case. Made for the R.A.F. so obviously a robust receiver which will give years of service. The price is £14/10/-, or will be sent against deposit of £417/6 and balance over 12 months. If you cannot call to collect please include an additional 10/- to cover cost of transit and carriage. This partly returnable to you if and when you return the transit case.



MAINS POWER PACK FOR R.1155
 With Pentode output stage. Plugs into socket on receiver so no internal modifications are required. Price £5/10/-, complete with 8in. speaker ready to work. carriage 3/6.

PERSONAL RADIO CABINETS.
 Correct dimensions to take P.W. "Mini Four" and similar midget superhet or TRF. Internal dimensions 6 1/2in. high x 5 1/2in. wide x 3in. deep. With special plastic grained finish. Price 15/9, plus 1/6 postage and packing. De luxe model covered with brown crocodile leathercloth and banded with grey lizard leathercloth as illustrated. Price, 22/6, plus 1/6 postage and packing.

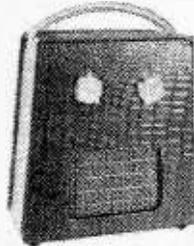EQUIP YOUR DEN
 You often need to measure the capacity of small condensers, so why not make a unit to do this. We can supply circuit diagram and all parts, total cost being only 10/-, battery model: 25/-, mains model. Circuit separately 1/6, refunded if you buy the kit.



PRECISION EQUIPMENT

The Famous Bennett College can help your career through PERSONAL POSTAL TUITION

in any of these subjects:
 Accountancy Exams. ★ Aircraft Eng. & Radio ★ Architecture ★ Auditing ★ Book-keeping ★ Building ★ Carpentry ★ Chemistry ★ Civil Service ★ Commercial Art ★ Commercial Arithmetic ★ Company Law ★ Costing ★ Diesel Engines ★ Draughtsmanship ★ Electric Wiring ★ Engineering (Civil; Electrical; Mechanical; Motor; Steam; Structural) ★ Jigs, Tools & Fixtures ★ Journalism ★ Languages ★ Mathematics ★ Mining ★ Modern Business Methods ★ Plumbing ★ Police ★ Press Tool Work ★ Quantity Surveying ★ Radio ★ Salesmanship ★ Secretarial Exams. ★ Shorthand ★ Surveying ★ Telecommunication ★ Television ★ Works Management ★ Workshop Practice
 and GENERAL CERTIFICATE OF EDUCATION

SUCCESS WILL BE YOURS

As a Bennett College Student your own Personal Tutor will coach you until you qualify, at your pace, with no time wasted. You will learn quickly, easily.

SEND TODAY FOR A FREE PROSPECTUS

TO THE FAMOUS *Subject* **BENNETT COLLEGE**

Dept. F.104, Sheffield.

Please send me your prospectus on my subject.

Name

Address

Age (if under 21)


PLEASE WRITE IN BLOCK LETTERS

RECEIVER TYPE 2573

Receiver portion of the TRI196, undoubtedly one of the most useful little receivers that has ever been offered from Government Surplus Stores, because once the existing tuning unit is removed a standard coil pack can be fitted which makes a very efficient superhet at a very small figure. Alternatively for breaking up there is a pair of standard 465 kc/s dust cored I.F. transformers which would cost 12/6-15/- and dozens of other items, tuning condensers, coils, preset condensers, pot meters, etc., etc. The price is only 9/6, plus 1/6 post, and packing, less valves. Or 27/6, plus 2/6 post, and packing and insurance with valves. The valves are as follows:—2 VR53, 2 VR56, 1 VR57 and 1 VR55.


THE SUPERIOR FIVE

A.C. mains superhet built by one of our famous manufacturers—Covers, long-wave 800-2,200 metres. Medium-wave 200-500 and short-wave 16-50 metres. Made on heavy gauge chassis, size 15 1/2x8 1/2 edge-lit dial, printed and calibrated in three colours, size 7 1/2in. square 8in. p.m. speaker—two speed tuning—B.V.A. valves types 6K8, 6V7, 6R7, 6V6 and 6X5—Pick-up and speaker sockets—delayed A.V.C.—I.F. filter—4 watts unfiltered output—circuit diagram and 12 months written guarantee. Price: complete ready to work, £10/19/6. HIRE PURCHASE Terms: £3.10/- deposit then nine monthly payments of £1. Non callers please add 10/6 to cover carriage and insurance.

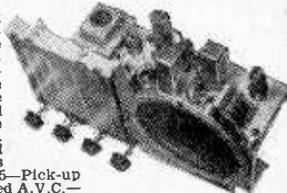

SUPERIOR FIVE CABINET

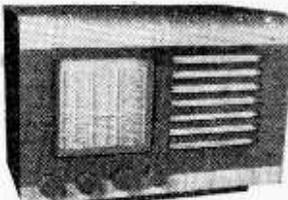Beautifully veneered, full grained and highly polished. dimensions 15in. wide, 10in. deep x 12 1/2in. high. Takes our "Superior Five" also the set being advertised by Lasky Radio. In the cabinet the set will look well worth £18 to £20. Price 35s. each. Post., packing and insurance 7/- extra.



Orders are dealt with by our Ruislip depot. To avoid delay, address to: E.P.E., Ltd. (Dept. 7), Windmill Hill, Ruislip, Middx. Include extra 2/6 under £2; 1/9 under £1.

152-153 FLEET STREET, E.C.4, and at WINDMILL HILL, RUISLIP MANOR, MIDDX.

CLYDESDALE

Bargains in Ex-Services Radio and Electronic Equipment

COMPONENTS FOR THE CONSTRUCTOR MANUFACTURERS' SURPLUS

RADIO CABINET
 A handsome walnut finish wooden cabinet well ventilated with removable back panel. External dimensions. Ht. 9 1/4 x 17 x 8 ins. approximately. External appearance facing cabinet. Speaker opening right side. Ht. 5 1/2 ins. Lth. 4 1/2 ins. Dial opening, left side. Ht. 3 1/2 ins. Lth. 5 1/2 ins. Internal dimensions. Ht. 8 1/2 ins. x 7 1/2 ins. approximately.

CLYDESDALE'S 25/- each POST PRICE ONLY PAID
 8 INS. P.M. LOUSPEAKER

With transformer, standard chassis type. Brand new in original carton.

CLYDESDALE'S 17/6 each POST PRICE ONLY PAID
 3 GANG VARIABLE CONDENSER
 Cap. per section. 0.0005 mfd.

Size—4 x 2 1/2 x 2 1/2 ins. with standard spindle.
CLYDESDALE'S 7/6 each POST PRICE ONLY PAID

PARMEKO MAINS TRANSFORMER, Type 5084
 Primary 200, 230, 250 Volts, 50 Cycles. Secondary 450-0-450 Volts, 200 mA, 23 Volts, 4 amps, 5 Volts, 4 amps.

Dimensions: 4 1/2 x 4 1/2 x 3 1/2 ins. Shrouded. Weight 13 lbs.
CLYDESDALE'S 49/6 each POST PRICE ONLY PAID

PARMEKO OUTPUT TRANSFORMER, Type AF.5084 I.A.
 28 Watts.
 Primary 6,600 ohms C.T. Secondary 3.5, 5, 7.5 or 15 ohms.
 Dimensions: 3 1/2 x 2 1/2 x 3 1/2 ins. Shrouded. Weight 3 lbs.

CLYDESDALE'S 39/6 each POST PRICE ONLY PAID

NEW LIST OF EX-SERVICE ITEMS No. 8B. Price 1/6. PRICE CREDITED ON FIRST PURCHASE OF 10/- OR OVER.

Order direct from: **CLYDESDALE SUPPLY CO. LTD.**

2, Bridge St., Glasgow, C.5. 'Phone: SOUTH 2706/9
 Visit our Branches in Scotland, England and N. Ireland

Radio Receiver Design at V.H.F.—8

By G. P. Lowther

(Continued from page 215, May issue).

NOTE that a 600Ω or 75Ω resistor would cause a drop of only 3 db since the terminated or working impedances across A and B and C and D are 300Ω and 37.5Ω respectively.

Since unbalanced (i.e., with a single central conductor) coaxial cable is generally used for aerial feeders, an unbalance-balance device should be used to connect it to a balanced antenna, e.g., a centred dipole, or energy loss will result, but in practice this is usually ignored, the central conductor and outer sheath being taken to the two halves of the dipole.

Polarisation

This is of far less importance at V.H.F. than at lower frequencies where transmission is via the sky wave. Generally speaking the receiving and transmitting arrays should be in the same plane though twisting often occurs in towns, horizontal polarisation usually being best for long distances. Between 30 Mc/s and 100 Mc/s it has been found to give improvements in signal level and S/N of about 6 db when the transmitting aerial was more than a few wavelengths above earth. Vertical directivity is only important when phase relationships are upset by multi-path propagation.

Practical Circuits

—R.F. Stage

This is often dispensed with, the signal being taken directly to the frequency-changer, but if greater sensitivity is required it may be added with advantage. Above about 150 Mc/s, frequency-changers are very noisy and in the absence of an R.F. stage the S/N deteriorates considerably unless a strong signal is available. The R.F. stage may take the form of a grounded-grid amplifier as in Fig. 25 or a straight pentode; examples are shown later. If only a comparatively narrow band of frequencies is to be received, e.g., an amateur band, the response curve of the R.F. stage can be made sufficiently flat to obviate the need for tuning while still giving worthwhile gain.

This month the frequency-changer is dealt with.

(a) Diode

There are various ways in which the signal, oscillator and I.F. circuits can be connected to the diode, examples being given in Figs. 43 and 44.

The diode must be specially designed for use at V.H.F., e.g., EB91 (half section). It may be combined in the same envelope with a triode as oscillator, an example being the Mullard EAC91. A suitable circuit will be shown later.

(b) Triode

This valve enables the R.F., B.O. and I.F. circuits to be associated with separate electrodes, thus avoiding the necessity for decoupling to prevent interaction. This type of valve is capable of giving slightly greater efficiency than the diode as a result. Either a special H.F. triode may be used or a V.H.F. pentode strapped as a triode. This is inadvisable at the highest fre-

quencies, however, as the grid-cathode (input) capacity is raised.

Since the oscillator frequency appears across the tuned grid circuit, voltage of oscillator frequency will appear on the grid if this circuit offers appreciable impedance to it. This is minimised by using a high intermediate frequency.

The circuit of Fig. 45 utilises an RL18.

Two triodes may be combined in one envelope, e.g., 12AT7.

(c) Pentode

A pentode may be used in a similar manner to the triode; alternatively the oscillator frequency may be injected into the suppressor grid, though a level of the order of 40 volts is required.

(d) Multi-electrode Valves

The most satisfactory valves in this class are triode-hexodes and triode-heptodes. With careful circuit design they will give quite good results up to between 50 Mc/s and 100 Mc/s depending on the valve.

Beat Oscillator

If a self-oscillator is used without multiplication a Colpitt's circuit gives the best results. A modification for series tuning will be shown next month. If the inductance L_1 is replaced by 2in. to 3in. of wire, this circuit will oscillate up to about 600 Mc/s using an RL18.

Note.—That since series tuning is employed "L" comprises all the external inductance between the anode and grid.

L_2 , L_3 , L_4 and L_5 are all H.F. chokes consisting of 5 to 10 turns on a $\frac{1}{4}$ in. former.

Fig. 47 shows a Hartley oscillator followed by a doubler. The inductances described give a range (final frequency) of 50 Mc/s to 90 Mc/s.

L_1 consists of $6\frac{1}{2}$ turns of 18 S.W.G. wire on a $\frac{1}{2}$ in. former tapped 2 turns from the "hot" end.

L_2 consists of 2 turns of 18 S.W.G. wire on a $\frac{1}{4}$ in. former. (This coil can be self-supporting.)

A crystal oscillator may be used in conventional circuits multiplying up to the final, or a sub-harmonic of the final frequency and injecting into the frequency changer. The R.F. circuits need not be tuned as reception will be over a limited band. The I.F. frequency will thus vary according to the frequency of the incoming signal and may be selected by

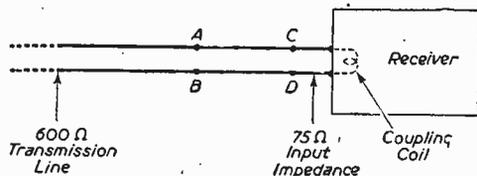


Fig. 42.—Effects of matching and mismatching may be checked as shown here.

feeding the frequency changer output into a normal selective receiver, this being tuned to the short waves. Care must be taken that a harmonic of the crystal does not fall within the R.F. band.

I.F. Stage

A high intermediate frequency is necessary in order to avoid second channel interference. Thus, if an I.F. of 465 Kc/s were used with a signal frequency of 100 Mc/s, second channel interference would be experienced on 99.07 Mc/s (assuming the oscillator frequency to be below the signal frequency as is usual at V.H.F.). With one tuned circuit at 100 Mc/s having a Q of, say, 50, it may be calculated that the

design at V.H.F. a complete mechanical layout—including the position of all wiring—would have to be given, as well as the make of components to be used. Since the whole aim of this brief introduction to V.H.F. is to enable the more advanced amateur to design his own equipment, this would be undesirable as well as impracticable. Probably the greatest

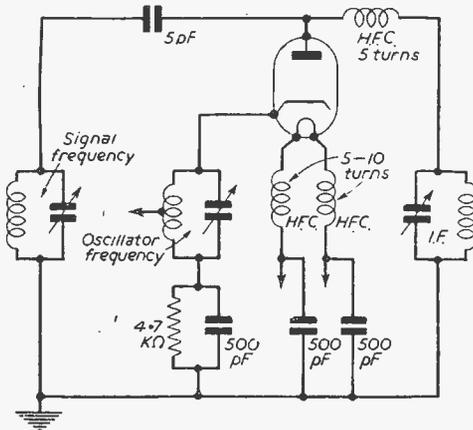


Fig. 43.—One useful diode circuit.

image response would be only 3 db below that of the wanted signal. I.F.s of 5 Mc/s to 40 Mc/s are commonly used. The disadvantage of a high intermediate frequency—apart from design technique and reduction in gain—is the resultant lack of selectivity. This, of course, is only a disadvantage if narrow-band transmissions are being received with interference from another station, and is best overcome by using triple detection, e.g., a converter.

Full winding data for I.F. transformers will not be given here as it obviously depends on the frequency, value of tuning capacity, diameter of former, use of iron core, etc., but the following information will serve as a rough guide:

½ in. former, air cored.
Wire—24 s.w.g. d.w.s.

Frequency (Mc/s)	No. of turns	Tuning capacity (max.)
3	50	50 pF
6	36	30 "
10	25	30 "
30	8	20 "

Spacing of primary and secondary windings must be found by trial and error, but will be about ¼ in.

V.H.F. Units

It must be emphasised that the circuits which follow, though based on proved design and capable of giving good results, will not necessarily do so without adjustment or modification. For foolproof

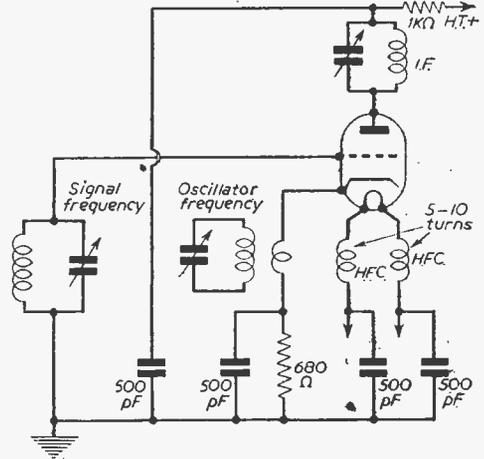


Fig. 45.—Triode oscillator circuit.

difficulty likely to be encountered in radio design at these high frequencies is that of uncontrollable self-oscillation. The following hints should enable this to be overcome:

- (i) Stop the oscillation by resistively damping the tuned circuits; this is practically always successful if the damping is sufficient.
- (ii) Reduce the regeneration that is leading to oscillation.
- (iii) Reduce the damping and then repeat (ii) continuing until the damping is as light as possible compatible with stability.

(To be continued.)


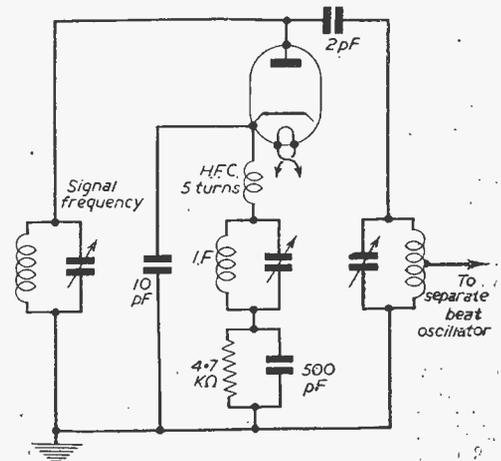


Fig. 44.—An alternative to the arrangement shown in Fig. 43.

A NEW "P.W." DESIGN

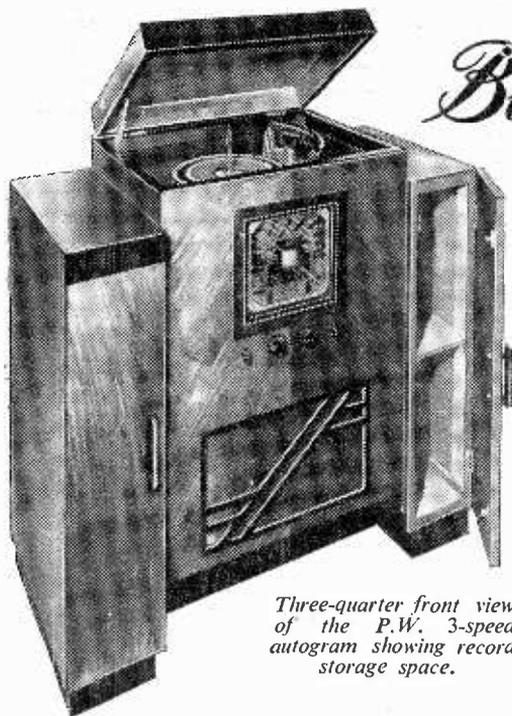

Three-quarter front view of the P.W. 3-speed autogram showing record storage space.

Building the **P.W. 3-SPEED** *Autogram*

AN EFFICIENT MODERN DESIGN
COVERING FROM 15-50, 190-520 AND
800-2000 METRES, AND PLAYING MIXED
10IN. AND 12IN. RECORDS AT 78 OR
33 $\frac{1}{2}$ R.P.M. AS WELL AS 7IN. DISCS
AT 45 R.P.M.

IN response to many requests for an up-to-date radiogram for inclusion in our Blueprint service, the P.W. 3-speed Autogram has been designed in such a manner that it may be included in an existing cabinet. As will be seen from the illustration on page 266, the main tuner and gram. pre-amplifier was built on a baseboard to take the place of an older receiver in the cabinet which was used, but chassis-form construction was retained, and for those who prefer that method a simple standard metal chassis may be used and either stood upon a shelf or bolted into position. The main amplifier with the power-pack is built as a separate unit and is attached to the floor of the cabinet, whilst a modern Ediswan-Plessey auto-changer is fitted on to the motor-board.

Several features were considered in designing this receiver, mainly accessibility and interchangeability, so that if at any future date it is desired to make changes in any part of the equipment no difficulty should be experienced. Furthermore, it may be desired by some to construct the receiver from the first in an alternative form, and the design lends itself very well to this.

Main Features

Taking first the main features (as distinct from the circuitry), the equipment is in three separate sections, interconnected by plugs and sockets. The motor-board, with auto-changing mechanism, will take a stack of eight records, 10in. and 12in. mixed, at 78 r.p.m.; a stack of 10 records, 10in. and 12in. mixed, at 33 $\frac{1}{2}$ r.p.m. and a stack of eight records, 7in., at 45 r.p.m. This particular unit employs a


single pick-up head which may be set with the aid of a small knob to suit whatever type of record is to be played. The point is of the "permanent" type and should play a total of 4,000 records without replacement. Any desired record may be rejected and the mechanism works very well indeed. Power from the mains for the turntable is obtained from a short lead plugged into a mains socket on the receiver/pre-amp. chassis, and this is so connected that the motor is only "live" when the receiver is switched on. There is thus no risk of the motor being left running with undue wear on the stylus unless the set is being listened to. Screened leads are taken to the pick-up sockets at the rear of the chassis and these, as will be seen from the circuit on page 264, are fed to a separate single-stage pre-amplifier, which is not in circuit on radio. Peculiarities in some of the circuit details here will be mentioned later. The radio unit is a superhet without R.F. stage, designed to give a few stations at really high quality rather than a large number of stations at indifferent quality. For this reason special arrangements have been adopted in the detector stage to retain a measure of A.V.C. (which is not usually regarded as ideal from a quality point of view), and in the values of certain components. Tuning is effected by the now popular and well-tried Osmor coil unit, which we have used on more than one occasion and which is easy to mount, very simple to trim and gangs very well throughout all three ranges. With it we have also used the maker's full-vision dial which, being designed in conjunction with the coils, provides the user with an accurate setting for any desired station as well as adding a pleasing appearance to the finished receiver. There are four controls—main tuning, combined on/off and volume, wave-change and radio-gram. The volume control is operative on both gram and radio and the output from the control is taken via a length of standard coaxial cable to a socket on the main amplifier chassis.

used in this combination gives a rising bass and treble, with a cut-off round about "surface noise" level, and the gain, with the special low-microphony pentode used, is sufficient fully to load the input of the main amplifier. It will be noted that across the pick-up there are a fixed condenser and two resistors in parallel, and it may be wondered why a single resistor was not employed in place of these two. The reason is that some listeners may prefer to use old records which have a much higher output level

than modern discs, and it may be found that the 6BR7 is overloaded, giving rise to a form of distortion which might be described as "throaty." This may be overcome by replacing R24 by either a normal .5 MΩ volume control or by two separate fixed resistors in series, with the output taken from the junction of them. The values will, of course, be chosen to give the desired reduction in output. If a standard variable is used in place of the tapped resistors it should be mounted on the chassis, adjusted

COMPONENTS FOR AMPLIFIER

- | | | | |
|-----------------------------------|-------------|---|---|
| One type PTM13A mains transformer | } Woden. | One 240 Ω, 3 w. Welwyn. | } Belling & Lee. |
| One type PCF18 L.F. choke (Ch.1) | | One plug and socket (L604/S and L734/P). | |
| One type PCF17 L.F. choke (Ch.2) | | Four I.O. valveholders. Clix. | |
| Condensers— | | One 3-pin mains plug and socket (P162) | } Bulgin. |
| Three .1 type CE37N (350 v.v.) | } T.C.C. | One fuseholder (type F141) and fuses (1 amp.) | |
| One .1 type 543 (500 v.v.) | | One 8-pin plug (type P112) | |
| One 8 μF type CE25P (450 v.v.) | | One 6SN7 valve | |
| One 16+8 μF type CE28P (450 v.v.) | } Brimar. | Two 6V6 valves | |
| One 32 μF type BR3250. Dubilier. | | One 5Z4 valve | |
| Resistors— | | One W.B. 10in. Stentorian L.S. and transformer. Whiteley Electrical. | } Clix. |
| Two 100 Ω | } Dubilier. | One miniature 2-pin plug and socket. | |
| One 1 K Ω | | Metal chassis, 15in. x 8in. x 2½in. Insulated Connecting wire, bolts and nuts. Stern's Radio. | |
| One 10 K Ω | | } 1 w. | One multi-speed auto record changer. Ediswan-Plessey. |
| Four 47 K Ω | | | |
| Two 220 K Ω | | } 1 w. | |
| Two 1 M Ω | | | |
| One 10 K Ω | | | |
| Two 33 K Ω | | | |

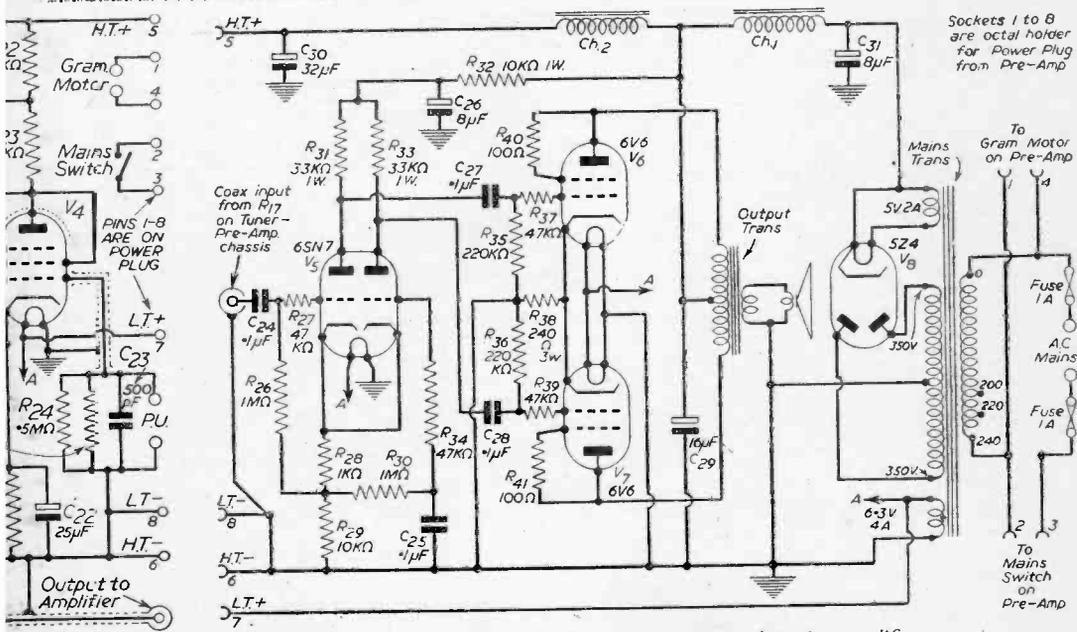

Circuit of the power pack and main amplifier.

to the desired level when the receiver is first put into operation and then left alone.

There is scope for the constructor to experiment with quite a range of values in this particular stage, and as it operates only on records it is possible to set it up for either one particular type of record (for those who prefer one make), or as a compromise for all types. It is in the latter connection that the values given have been selected, and it will hardly be necessary to inform those who find their main interest in record playing, that there is quite a difference in the reproduction of say, Parlophone and Decca discs. The latter, with the *ffir* characteristics may prove too "toppy" for some and an adjustment of R25 and C23 should be carried out in this case. On the other hand, some discs may find improvement by accentuated bass, and experiment with the tapping point between R18 and R19 should be carried out, together with a modification of C18. In other words R18 and R19 may both be increased or reduced in value, preferably keeping the total value roughly between 100 K Ω and 220K Ω , noting the effect of the variation in the tapping point. The values chosen here, as in the previous case, are those which we feel


are the most suitable compromise and no criticism has so far been made concerning the quality of reproduction by those who have heard the Autogram.

Valve Screening

It is possible to obtain small valve screens which fit into the valveholder for the type of valve specified, and in some cases it has been found necessary to screen the entire valve to prevent hum. Provided that the wiring, as shown on the blueprint or in the next issue, is followed there should be no need to make use of this screen, although if the valveholder when purchased is supplied with the screen there is no objection to using it, as it has no deleterious effect upon performance.

Additional Stage

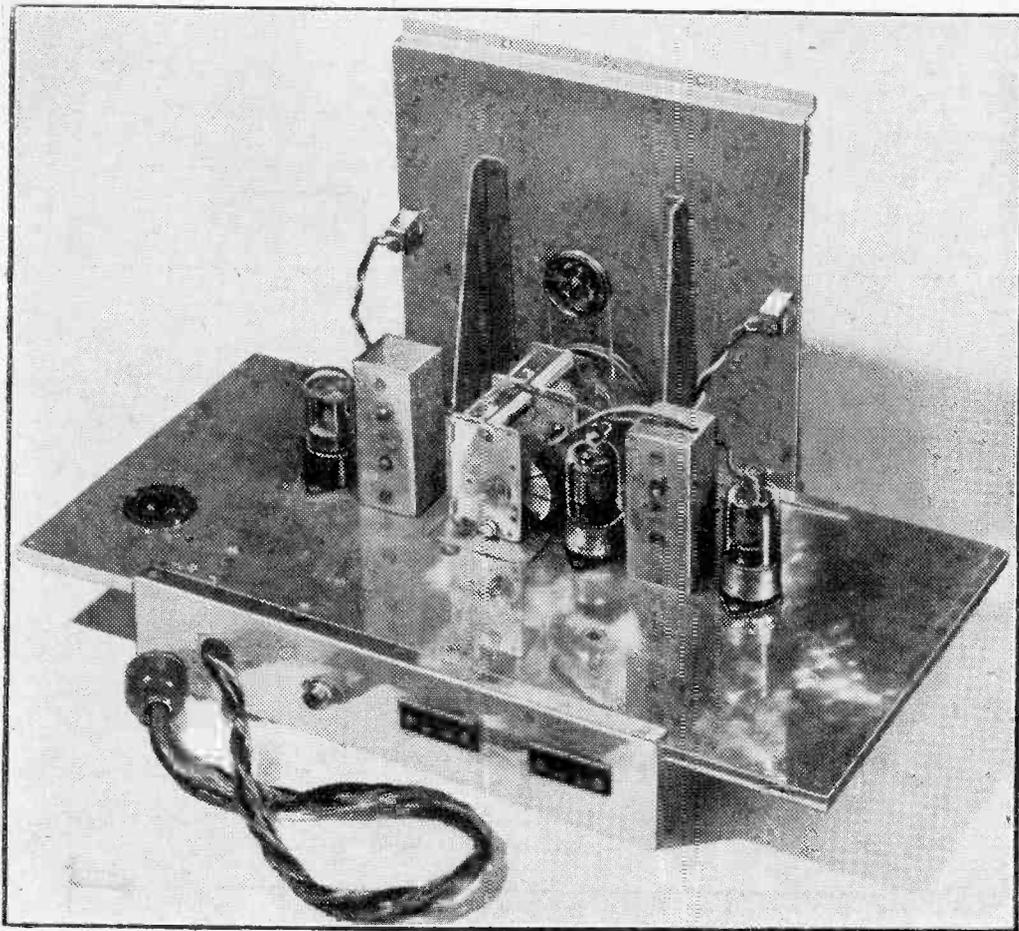As already mentioned flexibility has been considered in this design and it may be thought that there is insufficient L.F. gain in the combination to give adequate signals on weak stations. This criticism can be upheld, but must be considered against the question of quality of reproduction, which is usually poor when a weak station is received, either because



The finished tuner and gramophone pre-amplifier.

of the low signal-to-noise ratio or because of interference. As there is thus very little entertainment value in such a signal, it is not worth while providing additional gain, but at a later date it is quite a simple matter to include a further stage before V5, and it will be noted that space has been left on the amplifier chassis for this purpose. Such a stage is quite critical, however, and there are a number of considerations which must be borne in mind. Firstly, it will follow the gramophone amplifier and this means that records will be reproduced very much more loudly. It may easily then be possible to overload the output stage. Secondly, any distortion introduced in the new stage will be heard on records also, and it would not be practicable to include the gramo. pre-amplifier between the new stage and V5. We tried the circuit in this connection and using a 6BR7 with components to give a very low stage gain, obtained some improvement on the weaker stations but generally the difference on records and the main entertainment stations was such that it was not considered worth while to fit it.

Constructional Work


As already mentioned the main tuner is built on a baseboard of the metal-covered type, merely because this particular old receiver had that type of construction, but the layout was so arranged that the rear runner may be considered, with a similar runner in the front, as the sides of a standard chassis, measuring 12in. by 9in. by 2½in. deep, and this is the arrangement which is specified. The shelf to

accommodate such a chassis must be so positioned that the large full-vision dial assembly will not foul the motor-board and this will call for individual attention according to the type of cabinet being used. The chassis for the main amplifier measures 15in. by 8in. and is also 2½in. deep, and this will have to have cut-outs in it to clear the terminals of the mains transformer and chokes. Details of these are given on the full-size blueprint which may be obtained for 3/6d. and a small reproduction will be given in the next issue for those who are unable to wire up from a theoretical circuit.


The mains socket for the gramophone motor will, of course, be mounted on the side of the chassis if this method of construction is adopted, and there is no reason why it should not be placed at the opposite end of the chassis if desired. The main interconnecting cable may be constructed from standard coloured plastic-covered flex to facilitate identification and the two theoretical circuits show the plugs and sockets in standard theoretical form with the numbers as carried on the Bulgin octal plug—which are, of course, the standard B.V.A. markings for octal valveholders. When the cable has been constructed and the socket wired a special check should be carried out as it is easy to introduce a short-circuit in this part of the operation, and should this be across the mains leads a nasty accident may occur.

Once again it should be pointed out that the particular items specified in the list of components are those which we actually used in the prototype receiver, and this does not mean alternatives cannot be used. We have, however, chosen those parts for their values, physical dimensions, etc., and cannot enter into correspondence as to the suitability or alternatives, as generally it is desirable to make up a receiver using them in order to pass a reliable opinion as to their suitability.

(To be continued.)

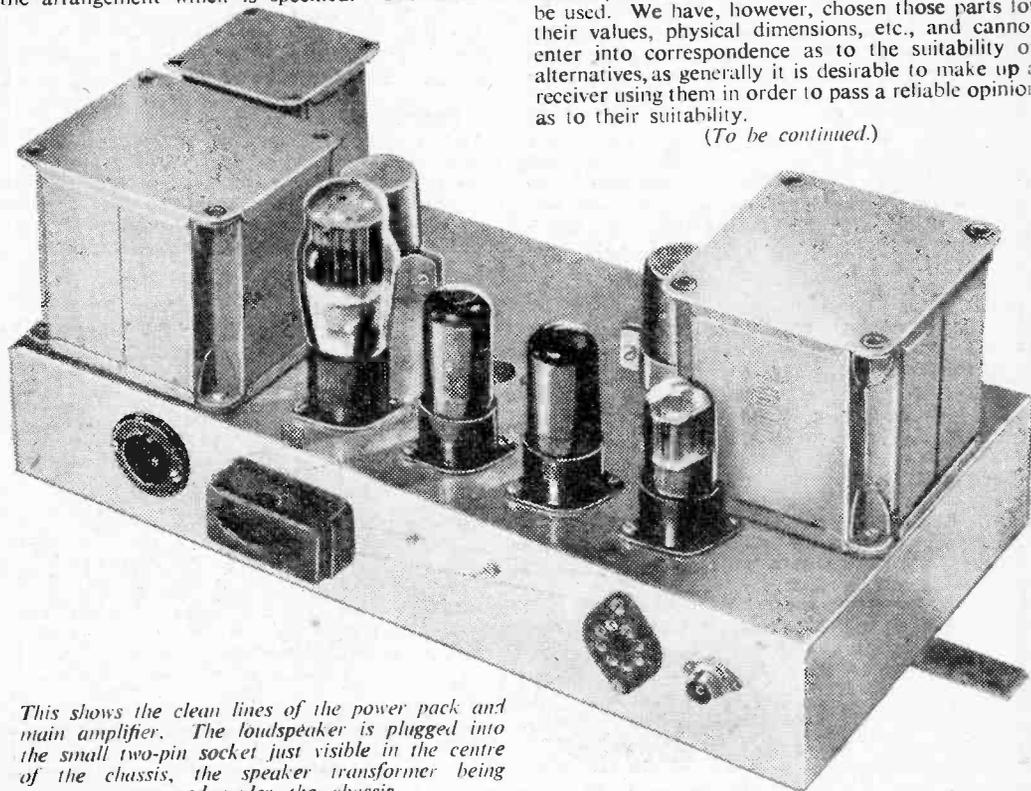

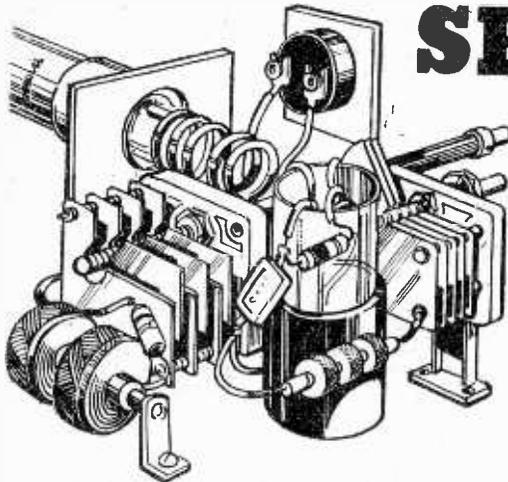This shows the clean lines of the power pack and main amplifier. The loudspeaker is plugged into the small two-pin socket just visible in the centre of the chassis, the speaker transformer being screened under the chassis.



SHORT-WAVE SECTION

A Modified Folded-“V” Beam

DETAILS OF AN INDOOR SHORT-WAVE AERIAL

By A. W. Mann

IT is safe to assume that apart from an efficient receiver the most successful DX listeners have an efficient aerial for use in conjunction with it.

Opinions are divided as to which is the most suitable and efficient type of receiver. Readers who listen to discussions over the air on various amateur bands are apt to be misled so far as receivers are concerned, as they usually overlook the fact that the opinions expressed are based on the exacting requirements of the transmitting amateur.

Some, for example, swear by the AR88 and AR77 ; others favour the HRO. One also finds opinions which differ in several respects concerning these receivers. On the other hand, I have heard the R1155 described as doing all that was required after a little modification. The availability of ex-Service receivers has thus placed the amateur and short-wave listener in a position to use highly efficient equipment which otherwise he would never have been able to afford.

The best advice one can give, so far as the short-wave listener is concerned, is to buy and try what you can afford.

activity problems and their solution do not fit in with space factors.

I am aware of one amateur transmitter who must perform use an oddly-shaped aerial system which does not conform to the textbook by any stretch of imagination. At first he regarded his position as a hopeless one. So far as practical results are concerned this is far from being the case.

When one has no choice in the matter the only thing to do is to erect the best aerial one can, in the space available. This may be based on original ideas, or on the ideas of others who are similarly situated. If the results obtained show promise, follow a long-term policy, for by so doing a true sense of values will be acquired.

In the April, 1950, issue of PRACTICAL WIRELESS I described in detail an original type of indoor short-wave receiving aerial, which was devised with the idea of obtaining a useful amount of pick-up together with variable directivity. This folded-“V” beam aerial has provided me with some valuable data during the past two years.

Aerials

Aerial discussions on the amateur bands are centred on the transmitting types which are equally good for receiving.

Here again, the opinions expressed are of little value to the short-wave listener. When writing about short-wave receivers and aerials one should take into consideration the fact that it is but the minority who can afford the more expensive types of communication receivers, and that the average reader's location does not allow aerial systems based on textbook recommendations to be erected.

Few, for example, have the space required to erect a half-wave horizontal doublet. Among those who have it is probable that broadside direc-

The Modified Aerial

Fig. 1 shows the indoor folded-“V” beam in its

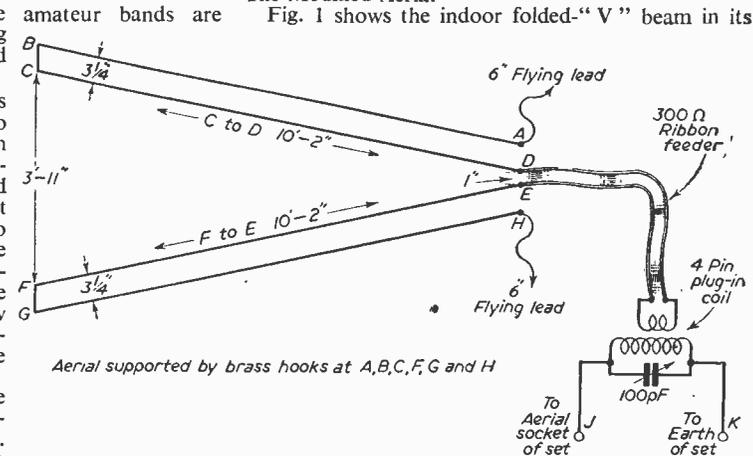


Fig. 1.—General form of the folded-“V” aerial.

modified form. For the benefit of new readers it may be as well to describe briefly the salient features of the original model.

The aerial consisted of one unbroken length of stranded, insulated aerial wire. That is from A to B, continuing to B-C, C-D, D-E, E-F, F-G and G-H, continuing with a 6in. length of flying lead at A and H. In this case the aerial was also tuned by means of a suitable tuning unit of simple construction.

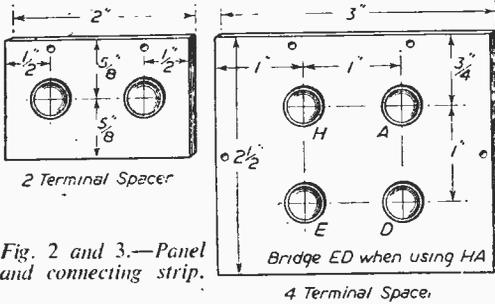


Fig. 2 and 3.—Panel and connecting strip.

A single down-lead is used, and the following coupling or tapping combinations are available. Between E and D, at H or A, and with the flying leads H and A coupled together, the down-lead can be coupled to the mid-point. In this way variation of directivity is possible.

Modifications

Examine now the modified version as shown at Fig. 1. While the free ends A and H are retained, a different type of down-lead is used. Also, we do not employ a single length of wire, but introduce a break between E and D. Thus we have, in effect, two separate aerials of "U" shape and in "V" formation.

A divided aerial of this type requires a twin feeder as the coupling medium. In order to obtain a satisfactory match we decided to use 300-ohm ribbon feeder as advertised in this journal. While heavy duty ribbon is used in the original model, the lighter and more flexible 300-ohm ribbon would, I think, be better.

Coupling

If the receiver with which the aerial is to be used has provision for doublet coupling, the twin leads can be coupled directly to the appropriate sockets. Many home-constructed receivers can be adapted, as will be shown later. Where this is impossible, as in the case of the R1116, R1116A and R1155A receivers, a suitable coupling device must be used. This may be of the fixed or variable type respectively. We prefer the latter, and although in adopting it an additional control is introduced, its inclusion will prove to be warranted.

A modified version of the 1083 tuner was at first considered, but as these are now scarce it was decided to use one which could be built with standard components and four-pin type plug-in short-wave coils covering the tuning range of the receiver to be used.

The Tuner

Theoretical details of the tuner will be found at Fig. 1. The components required are one 100 pF. tuning condenser with slow-motion dial; two ter-

minals or sockets; one coil base. The complete unit can be built on a small panel and baseboard assembly.

This tuner and the feeder recommended will be found to provide an excellent match between the aerial and receiver input, the aerial being inductively coupled to the tuned circuit.

Four-pin base connections are as follows: Reaction winding sockets to twin feeder; top of grid winding to fixed vanes of tuning condenser; bottom of grid winding to moving vanes. Leads between J and K should be taken direct from the coil base sockets and not from the tuning condenser terminals.

Queries Answered

Before dealing with the practical application of the aerial system it occurs to the writer that there are certain points about which questions may be asked, because it must be borne in mind that we are not dealing with an aerial specially designed for one band operation, but rather with one intended for general coverage purposes.


The first question might be: *Can the length of the legs be increased where space will allow?* The answer is "yes." Increased pick-up will result with some loss in selectivity, but the angle and other dimensions must not be altered.

Wherever possible the exact specification should be adhered to. *Can other than the 300-ohm feeder line be used?* The answer to this is definitely "no."

Fig. 2 shows the form of spacer required, which consists of two terminals mounted on suitable insulating material. The spacer shown at Fig. 3 will allow the "V" to be taken to E and D and the flying leads to H and A. The terminals E and D should be bridged with a short piece of wire when the feeder is coupled to H and A. Strong directional effects are obtained with feeder as shown and A and H joined together.

The Set Up

The aerial ready for use, we couple the down-lead to the tuner, as previously described. If the receiver is in a cabinet or screening box and has wave-change switching (such as the R1116, R1116A) the tuner unit can stand on top of the set, the connection on the aerial side of the tuner being coupled direct to the aerial socket of the set. The earth side connection, however, need not be taken direct to the earth terminal, but to the nearest earthed point of the screening box. The receiver, should be earthed.

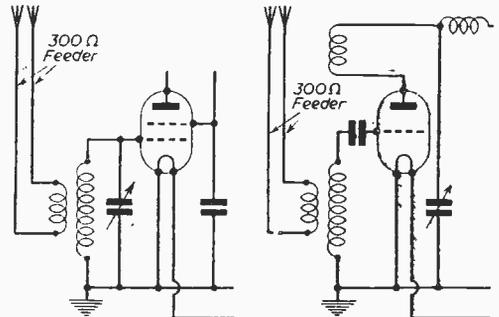

Figs. 4 and 5.—Connections to the input stage of two types of receiver. The grid coil in the right-hand circuit is, of course, turned in the usual way.

When using this form of coupling with an R1155A receiver (unmodified) the feeder connections should be taken to the aerial and earth points of the Jones plug. The shortest possible lead is allowable from the internal aerial and earth tags of the plug, while the receiver is directly earthed from some part of the screening box. Tuned coupling as A, Fig. 1, is the better method.

Tuning Procedure

This is as follows. Set aerial tuner condenser to half-way position, tune in the desired transmission on the receiver for maximum signal strength. Follow by tuning the aerial tuner. This will improve the matching of the aerial to receiver input, and further increase the gain.

Alternative Connections

As previously mentioned, alternative connections

can be made to the flying leads H and A. This will be found to have some directivity effect.

At the moment the writer is using spring clip connections between feeder to aerial. It is intended however to arrange matters so that quick changes can be made from the receiver operating position.

T.R.F., etc.

Fig. 4 and Fig. 5 show how the aerial down-leads should be connected to T.R.F. receivers, using plug-in four-pin coils, and regenerative receivers using the six-pin type plug-in coils respectively.

The writer will be pleased to hear of the results obtained by those short-wave listeners who give it a trial. In the meantime the problems relative to outdoor aerials for erection in limited space are being studied, and certain ideas will be tried out in practical form, with various types of receivers. If successful they will be dealt with in a future article.

Automatic and Manual Tuning

DUAL TUNING COMBINED IN ONE RECEIVER

By S. W. Clements

MOST of the time, the average domestic receiver is tuned either to the Home Service or the Light Programme, and therefore both may advantageously be pre-set. But there is always that odd occasion when the flexibility of manual tuning is required to tune a station on another wavelength for a particular programme, or for touring the short waves. The average superhet, normally tuned by a twin-gang variable condenser, can be modified to receive one medium-wave and one long-wave station pre-set, with the alternative of complete manual tuning, at a cost of a shilling or two.


The components required are a 6-pole 2-way switch and 4 trimmers. It may be necessary to wire small fixed condensers across the trimmers to give the necessary capacity.

Space must be provided on the panel for the extra control; next to the wavechange switch. This can usually be effected by moving the tuning control, either to the centre of the dial or above it. Alternatively, a little-used tone control may be dispensed with or put at the side or back. The lay-out is immaterial provided that the new master switch is adjacent to the existing wavechange switch. The four trimmers should be mounted at the rear of the chassis where they can be easily adjusted. The wiring of the switches and trimmers is shown diagrammatically, and it will be seen that the connections to the wavechange switch remain as before except where poles X and Z are linked to the master switch. Note that the top tags on the twin gang are now unused because the grid cap of the frequency changer is connected to the switch.

When the wiring is completed, set the wavechange switch to "manual" and the master switch to "medium" and tune in the local station, if it is desired to have this pre-set. The alteration to the wiring may cause some small adjustment to the aerial and oscillator trimmers on the coil-pack. When the station is properly tuned, turn the master switch to "auto" and adjust trimmers 1 and 3 at the rear

of the chassis until the same station is received. A non-metallic screwdriver or trimming tool should be used. The station should be heard at a volume at least as great as the manual setting and, in fact, if the twin gang is not fitted with trimmers the pre-set volume may be appreciably greater. Carry out the same procedure on long wave with the Light Programme, using trimmers 2 and 4. An indication of the capacity required can be obtained by observing what part of the vanes of the twin gang are in mesh when the station is tuned manually.

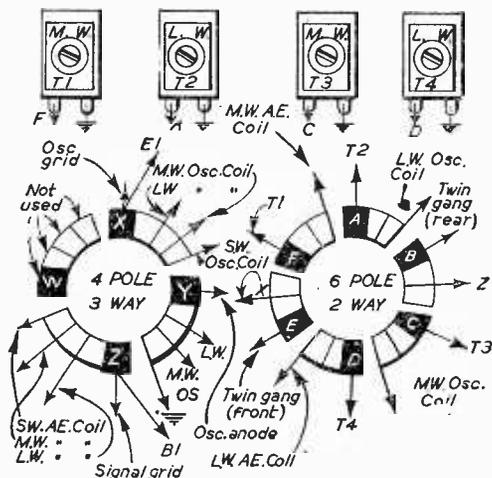The modification is now complete. With the master switch at "manual," the letters "L" and "M" on the wavechange switch stand for "Long" and "Medium"; when set to "auto," they stand (in my case), for "Light" and "Midland." There is no provision for a pre-set station on the short wave.



Details of the coil and switch connections.

Three Waveband Coil Pack, iron cored coil 16-50, 180-550, 1,000-2,000 metres' I.F. frequency, 465 kc/s. Size 4 1/2 in. x 1 1/2 in. x 2 in., 24/- Post paid. Double-ended Perspex trimming tool given free with each pack.

Constructor's parcel comprising 5 valve Superhet chassis with valveholder and I.F. cut-outs, size 13 1/2 in. x 6 1/2 in. x 2 1/2 in., complete with scale (new wavelength) size 1 1/2 in. x 5 1/2 in., 2 pulley wheels, drive spindle, drum, pointer, back-plate and 5 international octal valveholders, 11/6 post paid.


6 Iron-cored Coils on Alladin formers, 13-50, 198-550, and 950-2,000 meters, I.F. frequency 465 kc, tuning condenser .0005, 8/6.

Waterhouse 5in. Extension Speaker complete with volume control in a really pleasing cabinet in gold and green, ideal for bedrooms, etc., 23/6.

Mains or Battery Superhet Portable Coils, comprising medium-wave frame aerial and long-wave loading coil, used as aerial coils. Midget iron-cored screened L/M osc. coils, complete with circuit, I.F., frequency 465 kc/s., 9/6.

Metal Rectifier, 250 v. 60 mA., latest midget Selenium, 6/6.

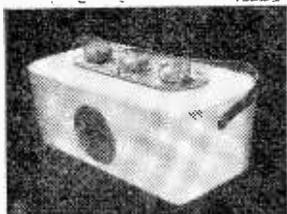Output Transformers. Standard type 5,000-ohms imp., 2-ohms speech coil, 4/9; Push-Pull 6 v. 6 matching 10-watt 2-ohms speech coil, 6/9. Miniature type 42-1, 3/3.



PERSONAL PORTABLE CABINET in cream - coloured plastic; size 7 x 4 1/2 x 3 in. Complete 4-valve chassis. Scale and 3 knobs. Takes miniature 90 v. and 7 1/2 v. batteries, 9/-

2 1/2 in. P.M. Speaker to fit above, 13/6. Miniature output transformer, 5/-.

Miniature wave-change switch, 1/6.

Miniature 1-pole 4-way used as Volume and Off, 1/6.


4 B7G valve holders, 2/-.

Midget twin gang 1/2 in. dia., 1/2 in. long and pair medium and long-wave TRF coils 1 1/2 in. long x 1/2 in. wide, complete with 4-valve all-dry mains and battery circuit, 8/6.

Condenser Kit, comprising 11 miniature resistors, 3/6.

The above receiver (less valves and batteries) could be built for approximately 49/-.

Point to Point Wiring Diagram, 1/-.

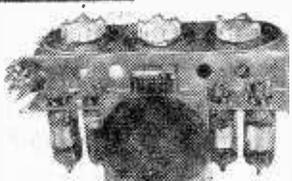

View of chassis as it would look when assembled with valves inserted.

Midget Bakelite Cabinet, 7 in. x 5 1/2 in. x 5 in. c/w 5-valve S.H. chassis, med. long wave scale and back (takes std. twin-gang condenser and 3 1/2 in. speaker), 15/-.

P. & F., 1/6.

Wave-change Switches, 6-pole 3-way, 2/-; 3-pole 2-way, 1/2; 4-pole 3-way, 1/9; 5-pole 2-way midget, 1/9. P. & P., 3/3. each.

Pre-Aligned Midget 465 kc/s., 4/120, 9/- per pair.

Miniature 465 kc/s. I.F.'s Q.120, per pair, 10/-.

465 kc/s. Midget I.F.'s, Q.120, size 1 1/2 in. long, 1 in. wide, 1 in. deep. Pre-adjustable iron-dust cores, pair, 12/6.

Iron-cored 465 kc/s. Whistle Filter, each 2/6.

Valve-holders. Paxolin international octal, 4/4. each. Moulded international octal, 7/4. each. EF50 ceramic, 7/4. each. Moulded B7G slightly soiled, 6d. each.

Trimmers, 3-40 pf., 5d.; 10-110, 10-250, 10-450 pf., 10d.

Twin-gang .0005 Tuning Condensers, 5/-.

With trimmers, 7/8.

Midget .00037 dust cover and trimmers, 8/6.

Constructor's Parcel, comprising chassis 10 1/2 x 5 1/2 x 2 1/2 in., with speaker and valve-holder cut-outs, 5 1/2 in. P.M. speaker with transformer, twin gang with trimmers, pair T.R.F. coils long and medium, iron cored, four valve-holders, 20 K. volume control and wave-change switch. Post paid, 21/-.

P.M. SPEAKERS

	with trans.	less trans.
2 1/2 in.	13/6
3 1/2 in.	11/6
5 in. ...	15/-	12/6
6 1/2 in. ...	14/6	11/6
8 in. ...	17/-	14/6

Post and packing on each of the above, 1/- extra.

Terms of business:—Cash with order. Dispatch of goods within three days from receipt of order. Where post and packing charge is not stated, please add 6d. up to 10/-, 1/- up to £1 and 1/6 up to £2. All enquiries and Lists, stamped, addressed envelope.

D. COHEN

RADIO AND TELEVISION COMPONENTS
23, HIGH STREET, ACTON, W.3.


(Opposite Granada Cinema)

Hours of Business: Saturdays 9-6 p.m. Wednesdays 9-1 p.m. Other days 9-4.30 p.m.

Speed-up
SOLDERING
with



SOLDEGUNS

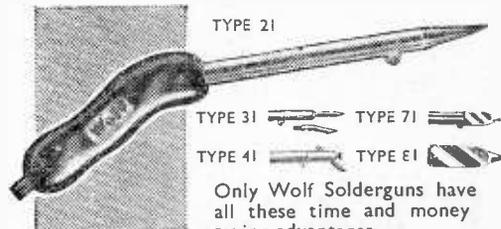

TYPE 21

TYPE 31

TYPE 71

TYPE 41

TYPE E1

Only Wolf Solderguns have all these time and money saving advantages—

Off-straight Easy-grip Handle · Perfect Control · Low Current Consumption · Models for every purpose from Fine Instrument to Heavy Industrial Soldering · Localised Heat · Maintains Correct Heat · Quicker Heat-up


AUTOMATIC SOLDERING



TYPE 51

Win new efficiency and economy with Wolf Automatic Soldergun. Its auto-feed, trigger solder-feed action, and perfect balance make it indispensable to all modern assembly.

SOLDERING IRONS

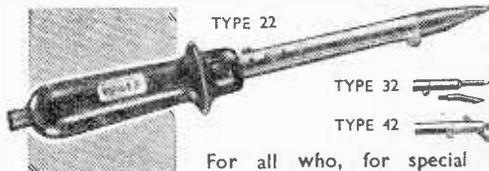

TYPE 22

TYPE 32

TYPE 42

For all who, for special reasons, prefer the conventional straight type handle. Identical as regards elements and bits to Wolf Solderguns but with round hard wooden handle with heat deflecting skirt.

It pays to Solder with **Wolf**

ELECTRIC SOLDEGUNS & SOLDERING IRONS

★ Obtainable from all high class stockists and ironmongers

WOLF ELECTRIC TOOLS LIMITED · PIONEER WORKS
WANGER LANE · LONDON · W.5 Telephone: PERIVALE 5637-4

MODERN ELECTRICS LTD.

164, Charing Cross Road, London, W.C.2

Phone: TEMple Bar 7587

Immediate delivery from stock
Export enquiries welcomed


CONNOISSEUR 2-speed Motors ...	£ s. d.
22 18 6	
CONNOISSEUR Pickups—Std. and Microgroove Standard ...	10 0 8
ACOS, G.P.20 PIU ...	4 11 5
ACOS, LP, and Std. Heads ...	3 11 4
DECCA, Pickup ...	3 15 4
DECCA, Motors—331 and 78 speed ...	3 18 6
331-45 and 78 speed ...	6 8 6

TEST GEAR

AVO— Model 7 ...	19 10 0
Model 8 ...	23 10 0
D.C. Minor ...	5 5 0
Uniminor ...	10 10 0
Univ. Bridge ...	26 0 0

SIGNAL GEN.— Wide Band ... 30 0 0
Valve Tester ... 60 0 0
Electronic Test Meter ... 40 0 0

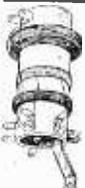TAYLOR. ALL TAYLOR TEST GEAR IN STOCK. Still available on H.P. Send S.A.E. for catalogue and terms.



One coil, 4 circuits. Simple receivers from a crystal set to a 3 valver. Full circuits enclosed.

T.R.I. Coil. 5/- P.P. 6d.

HILLFIELDS RADIO
8, BURNHAM ROAD,
WHITLEY, COVENTRY

Established over 30 Years

ELECTRADIX RADIOS

for **RADIO, ELECTRICAL AND MECHANICAL APPARATUS & LABORATORY INSTRUMENTS**


Write Dept. G.

214, Queenstown Road, London, S.W.8

Telephone: MACaulay 2159

PRECISION DRAWING INSTRUMENTS


Nickel Plated

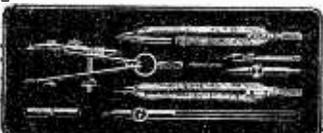

Locking instruments case, 7½" x 3½" Leatherette covered, Lined interior. PRICE 15/11d. plus 6d. postage. Set (B) Compass and attachments, pen, ink, tinting tray, etc., 7/6d. plus 6d. postage.

Set (A) Compass and attachments penholder, etc., 6/2d. plus 6d. postage. (Trade inquiries invited.)

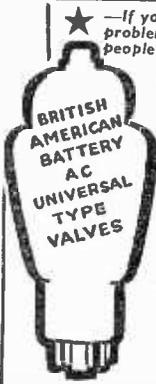BAZAAR SUPPLY COMPANY
(Dept. P.W.2.) 31, Theobalds Road, W.C.1.



★ —If yours is a (RARE) valve problem **BULLS** are the people most likely to solve it.

"DEMOBBED VALVES" Manual 2/9

Post free

Giving Equivalents of British and American Service and Cross Reference of Commercial Types with an Appendix of E.V.A. Equivalents and comprehensive Price List. We have still some Valves left at PRE-BUDGET rates which are actually sold at the old price. 12B8, 10/8, post 1/-.

EXPORT

to all parts of the Commonwealth and beyond—safely packed, fully insured (no C.O.D.) and free

CONDENSER TESTERS AND RECTIFIER UNITS. Plugs straight into A.C. mains, 200/240 v., and is indispensable for examination of condensers. Very slight and intermittent leakages which cannot be discovered by conventional instruments can be traced by this unit. Complete 39/6. Post 1/- Supplies are becoming limited

PIFCO ALL-IN-ONE RADIOMETER. A.C. and D.C., test everything in radio. Complete with test leads, 27/6. Post 1/6.

TAYLOR 7-range multimeters. A.C./D.C., 0.5-30-150-300 v. 0-30 ma.—300 ma./a-3 amperes precision M/I movement 50/- Real Colours throughout. Not just surface sprayed!

NEW: COLOUR FILTERS FOR TELEVISION SCREENS. For viewing in three delightful colours graduating from blue at the top, red in centre to green at the bottom. Gives a three-colour pastel shade picture on any black and white screen. 9in. and 10in., 10/9; 12in., 12/6; 15in., 19/6. Post 1/-.

AMERICAN TYPE ELECTRIC SPRAYERS. British made. Just plug in and spray. No vacuum cleaner or compressor needed. Easier than a brush and twice as fast. A.C. model, 24/15/-. Post 1/6.

"WIRELESS WORLD" Radio Data Charts, 7/6.

1,000 MFD. 12 V. BLOCK CONDENSERS, brand new surplus, 7/6.

ROD ANTENNAS, 1-foot sections, interlocking and extending, copper plated steel, 2/6 dozen. 50P. 12/6. SUE150A, 9/6

A.C./D.C. NEON TESTER, TYPE 400. This new model is specially designed for one-pole tests on mains, incorporating a highly sensitive neon tube—striking voltage 100/500 v. A.C./D.C. Also suitable for indicating polarity on D.C. current, when the glow of the lower electrode will indicate the negative pole, 11/3.

TAYLOR ON EASY TERMS. EASY TERMS up to 10 months—and very near Cash Price on all TAYLOR METERS.

EX-W.D. CHASSIS, with brand new valves, 11B5, 12A4, 12B5, 1T4, and circuit diagram showing conversion to excellent Personal Portable, 52/6, post 1/6.

RESISTOR COLOUR CODE INDICATORS, accurate, disc type, 1/3.

ADGOLA 3/16in. DIA. BIT SOLDERING INSTRUMENT. Miniature type to meet every requirement for Radio, Television, etc., 22/6, post 1/4.

JUNEREO PATENT MULTI-PURPOSE TOOL. REDUCED. It punches, bends, shears and threads. Specially designed for Model Making, Metal Working and Home Repairs. (Formerly 20/- now 10/-). With "Xakto" slide gauge (formerly 27/6) now 17/6. On APPROVAL one week. Refund guaranteed. NOW 10/- TAP FREE. Post 1/6.

TUBES VCR97, 22. AOREX, 30/-. 511 12in.. 24/10/-.

(Kindly mark EASY TERMS. 28-page illustrated Catalogue 5d. Stamps.



246, HIGH ST., HARLESDEAN, WINDR

JOHN FARMER

414. METERS, m.c. 30-0-30m/a. 2in. scale, 2 1/2in. dia. A superior job, brand new. 12/6, post 6d. 415. CARRIBERLEY 3L METERS m.c., graduated 0 to 10, pointer zero at 10, 2m/a full scale deflection, 2 1/2in. square panel mounting, provision for scale illumination. Brand new, 15/-, post 6d. 266. MORGANTHER VOLUME CONTROLS, fitted switch 250v. 1 amp. 1" shaft x 2 1/2" Brand new latest type. (a) Meg (b) 1 Meg (c) 1 Meg (d) 2 Meg. All at 5/6 each post 3d. 426. CO-AX. CABLE, 80 ohms. 7/0076. PVC covered, 7/32in. dia., the latest manufacture for T.V. aerials, 1/3 per yard; 100 yd. coils 45/-, post 1/6. 403. VHF SWITCH UNITS, fitted 4 position switch, 1 input and 2 output Pvc plug connectors for std. Pvc sockets. Ideal for use when one aerial feeds two receivers, switch provides for both sets on or off. Or for either set on and the other off. Size 4in. x 3 1/2in. x 1 1/2in. 7/6 each, post 11d. 443. ELECTROLYTIC CONDENSERS, midget, 8-16 MFD, 450v. D.C. wkg. 4/9, post 3d. 446. BIAS CONDENSERS, All current, manufacture. (a) 50 mfd. 50v wkg. 2/-, post 3d. (b) 25 mfd. 550v wkg. 2/-, post 3d. 368. AUTO TRANSFORMERS, single phase 50 cycles, 100w., tappings 0-10-120-230-250, other voltages available are 110-190-220-240v. All terminations marked. A superior job, 21/-, post 3d. 18. MULTIPLE I.T. TRANSFORMERS. Pri. 220-220-240v. 300, 30v at 2a, tapped at 3-4-5-6-8-9-10-12-15-18-20 and 24V. These very popular transformers are still only 22/6, post 1/2. 349. BERCO POTS, 50 ohms, wire wound, 1 1/2in. dia., panel mfg., fitted 1in. long, 1in. shaft, ideal for low imp. speaker control. Will carry up to 1a. 2/6 each, post 4d. A copy of our 1952 catalogue sent free with all orders. Otherwise price 6d. on request.

JOHN FARMER (Dept. A.3),
194, HARBORNE PARK RD.,
HARBORNE, B'HAM 17

Tel.: HARborne 1309.

NEW BOXED VALVES POST FREE

10/-	6/6	7/6
6C7GT, KT61,	6K7, 6C5,	EL32, EK32,
KT63, 5Z4,	EC31, 9D2,	6J7, 6X5,
5Y4, U89,	SP2, 6T5,	KTW67, EF39,
6V8, EF91,	12J5, HD21,	VME14G, EF39,
6SN7, 50L6,	D63, 6B8,	GAG7, 6K6,
35L6, 25L6,	6D6, VR101,	MHD4, MH4,
155, 1R5,	3Q5, SP2,	EF8, 1C5,
1T4, 3V4,	6SS7, KT2,	P61, KTW63,

12/6: 6K8GT, 6L6, KT66, ECL80, X65, X61M, ACDC AMPLIFIER KIT Complete kit, less valves, for 3-valve M/c Gram amplifier, 49/6 post free.

"THIS MONTH ONLY" OFFERS
Midget 500K. V/cntrs. 1/5p. 3T/sw. 4/- Standard 465 I.F. trans., 5/9 pair. Mini-Four Speaker, 3 1/2in. W/trans., 19/6. Condensers. 16 mfd.-500v. Card/tub., 3/6.

RADIO UNLIMITED
ELM ROAD, LONDON, E.17
Phone: KEY 4813.

SPECIAL OFFER

Moving Coil Headphones & Tannoy Mike
12/6
POST FREE



Stamp for Lists.
BOLD & BURROWS
12, Verulam Road,
St. Albans, Herts.
Tel.: St Albans 5951

A Voice-operated Relay

USES AND A RECOMMENDED CIRCUIT

Described by W. S. Fowler, M.A.

THE voice-operated relay has three main uses. The first is to provide absolute interference and "mush" limitation below a desired level. For instance, in an aircraft, when the radio operator is merely listening out for base calls of fairly good strength, the relay is adjusted so that it "shorts out" all signals below this strength. The result is that the wireless operator is not distracted from other duties by being compelled to listen to constant "mush" and to weak, unwanted stations. Instead, the set remains dead quiet until the relay is energised by the comparatively powerful signal of the base, or by an accompanying aircraft.

The second use of the voice-operated relay is that it can act as an automatic monitor on any desired frequency in conjunction with a tape or wire recorder. The apparatus is set up, the receiver is tuned to the desired frequency, and the recording mechanism is automatically started and stopped by the voice-operated relay, when it is energised by an incoming signal.

The third use of the relay is that it can provide a switch over from "receive" to "transmit" without the operation of any manual controls on the part of the operator. As soon as the operator begins to speak into the microphone the relay switches over the set from "receive" to "transmit." When he stops speaking the set goes automatically back to "receive."

There are no doubt many other uses to which the relay can be put and, once the principle is understood and the circuit has been built, the reader can experiment for himself.

Principle and Circuit of the Relay

The principle upon which the operation of the relay depends is simply the fact that varying grid voltages in a valve result in varying anode currents. The more negative the grid is made with respect to the cathode, the less anode current flows. Finally, a point is reached at which no anode current flows. This is known as the "cut off" voltage.

The relay used in the circuit is a sensitive one, needing only a few millamps to operate it. The relay to be found in the government surplus TR5043 transmitter-receiver works very well, but a home-made relay can be constructed from an old earphone. The relay is inserted between the anode, and H.T. + of any A.F. amplifier triode. A 6J5 serves the purpose very well. The relay takes the place of the normal anode load of the valve.

A variable resistance is inserted in the cathode lead of the valve (about 3-5 K Ω). By adjusting this, the negative bias on the grid of the valve can be altered until there is insufficient anode current flowing to close the relay.

Finally, a positive voltage is applied to the grid by tapping off a portion of the rectified A.F. signal from the receiver via a fairly large condenser and resistance (a suitable C.R. value is given by a .05 μ F condenser and a 1 M Ω resistor).

When a signal of sufficient strength is received the condenser and resistance supply a steady positive

voltage to the grid, in exactly the same manner as an A.V.C. circuit (with reversed polarity) operating on a variable-mu valve. This acts in opposition to, or cancels out, part of the existing negative voltage on the grid, and the result is a flow of anode current sufficient to operate the relay. The precise point at which the relay operates can be controlled by adjusting the variable resistance.

The points of the relay are, of course, connected appropriately according to the purpose for which the relay is being used, i.e., they may serve to break a short-circuit in the A.F. output, if the circuit is being used to act as a noise suppressor, or they may serve to switch on a motor if the relay is being used to monitor a frequency. Again, they may be connected so as to switch over from "receive" to "transmit."

The circuit diagram below shows a suggested arrangement for using the relay to monitor a desired frequency. A proportion of the rectified signal is tapped off from the diode load (1 M Ω volume-control) and serves to alter the bias on the 6J5 valve, in order to close the relay and thus operate the recorder mechanism when the required signal is received.

(Continued on p. 282)

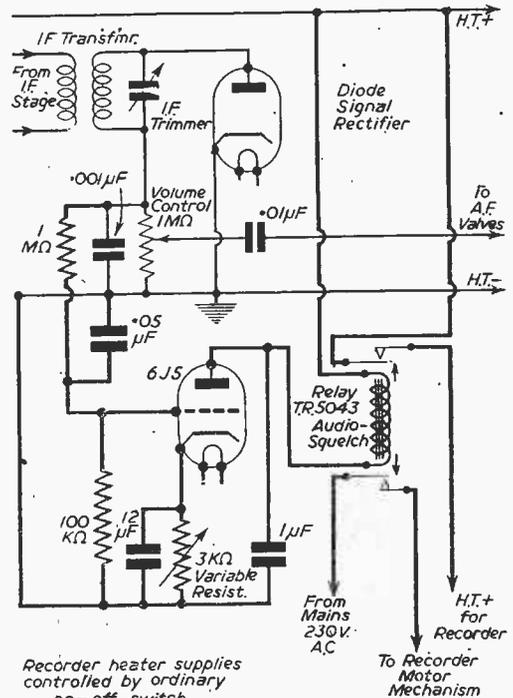


Fig. 1—Circuit of a superheterodyne-controlled relay for various purposes.

Simplified Set Construction

ADVICE FOR THE BEGINNER IN RECEIVER BUILDING

By Henry G. Russell


ALTHOUGH many readers may be competent technicians capable of reading a theoretical circuit and wiring up a receiver without hesitation, there are many who, like the writer, only occasionally build a set, and have to tread warily when following a circuit.

Until a year ago I invariably slipped up somewhere, usually in the omission of a connection, or using the wrong resistance in the right place or the right one in the wrong place. I also found that much time was spent in ascertaining the value of a resistor from the colour code.

I have since simplified my procedure, and find set construction much quicker with satisfactory results first time.

Marking Resistors

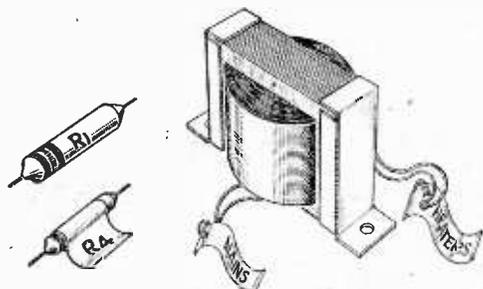With the circuit before me, I sort out all the resistors and find their values from a resistance chart. These are either marked on the resistor body with Indian ink or, where they are of the $\frac{1}{4}$ -watt variety, I stick on the resistor a piece of adhesive paper upon which is marked either its value or its number in relation to its place on the circuit, such as "R4" or "100K Ω R5".



Figs. 1 and 2.—Labelling components and leads.

The same procedure is followed with components such as coils, I.F. transformers, from mains transformers and so on, so that when I am ready to mount the components, or begin wiring, everything is marked exactly as on the circuit. This means that where the diagram is marked L1, I just take the coil marked L1; or instead of looking for a .002 μ F capacitor I take the one marked C3, or whatever it is. This preliminary marking can be done at odd moments, saves much time, and greatly reduces the margin of error; no longer is it necessary to look up the value of a component in the list of parts, which is marked on the circuit with a number.

Foolproof Wiring

Possibly more errors are made in constantly looking from circuit to set than in the correct choice of resistors and condensers. In a maze of lines and shapes it is easy to miss a vital connection, but if the following method is used there can be no errors in wiring.

If you are using a blueprint, buy a small tube of students' ultramarine water-colour. This costs about

4d. A cheap camel-hair brush is good enough for applying the colour. As each connection is made, paint over the line with the blue water-colour. It will be obvious now that if you have completely wired the set, there will be no white lines remaining on the print; if you have missed a connection it will be seen immediately.

If you are wiring up from a circuit published in PRACTICAL WIRELESS, then the connections should be painted over with some Chinese white.

Having completed the job, wiring can be cross-checked by marking over the blue lines painted in on the blueprint with white, as these are seen on the set, or with black pencil or paint over the white lines made on the "P.W." circuit. Even when you feel that a slip-up has occurred somewhere the obliterating paint-lines can be easily washed off, ready for a fresh start. For the not-too-knowledgeable amateur, this simplified method will lead to surer and quicker radio construction.

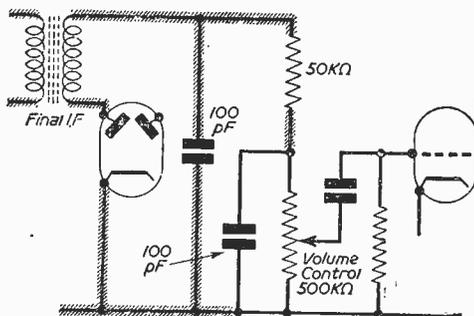


Fig. 3.—Marking off the circuit when wiring.

B.I.F. Catalogues Flown Overseas

ADVANCE consignments of the 1952 British Industries Fair catalogue have been flown overseas to assist foreign buyers in planning their visits to the Fair, which will be held in London and Birmingham from May 5th to 16th.


The catalogue is in two parts—one for the lighter industrial sections at Earl's Court and Olympia in London, and one for the heavier engineering section, at Castle Bromwich, Birmingham. The complete catalogue weighs some 3½ lb. and runs to more than 1,400 pages.

Up to the time of going to press, the balance of 20,000 catalogues in the advance edition will have been dispatched to United Kingdom government offices in 63 countries for distribution to prospective visitors to B.I.F. The final edition of the catalogue, bringing the total circulation up to 65,000, will be available on May 5th, the day the Fair opens.

The B.I.F. Catalogue is valued not only as an aid to preplanning a buyer's itinerary at the Fair, but as a book of reference for British industry. Over 2,000 firms are listed. By means of cross-reference indexes, it is possible to find all the exhibitors showing any given range of production.

The "PRACTICAL WIRELESS" MINI FOUR BATTERY PORTABLE

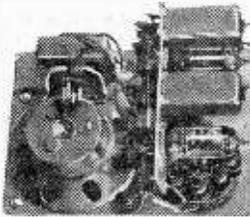A 4-valve battery superhet receiver designed to receive 4 Pre-Set Stations, three on medium waveband and one on long waves to suit local conditions. Each station is obtained on the set by the turn of a rotary switch. No tuning is necessary.



It is of midget size, being only 4 1/2 in. x 6 1/2 in. x 4 1/2 in. when completely built, and is very easily assembled from diagrams supplied. Cost of all components to completely build the set, including a drilled and cut chassis and panel, and new valves, 29/10/0 (or less valves for 28/7/6). Plus Portable Carrying Case, 16/6. A blue print showing complete practical component layout and wiring diagram, together with an individual component price list, is available separately, 1/6. Our Mains Units available in kit form are suitable for use with this set.

THE "WIRELESS WORLD" 3-VALVE SET

A Midget 3-valve T.R.F. Receiver for operation on A.C. mains, covering long and medium wavebands. We are able to supply all of the components to build this set, as designed, and specified in the Feb. 1950 issue, including the drilled chassis, valves and moving coil speaker, etc., at the following prices:—
 To construct complete chassis, less dial and drive assembly, 25-5/0. Ditto, including dial and drive assembly, 28.
 To construct the complete set, including dial and drive assembly and cabinet, 27/3/6.
 Overall size of cabinet is 7 1/2 in. x 5 1/2 in. x 1 1/2 in.
 A reprint of the designer's article, giving Circuit and Assembly Instructions (this is available separately for 9d.), together with a Practical Component Layout is included with each of above assemblies.



A QUALITY "PUSH-PULL" AMPLIFIER KIT

A Kit of Parts to build a 6-8 watt Push-Pull Amplifier for operation on A.C. mains 200-250 volts. Incorporates a simple arrangement to enable either a magnetic crystal, or lightweight pick-up to be used.


A 10-watt Output Transformer is designed to match from 2 to 15 ohm speakers. Tone control is incorporated. The overall size of the assembled chassis is 10 1/2 in. x 7 1/2 in. high. Price of kit complete in every detail, including drilled chassis and valves, 26/12/6. Component layout is supplied. Price of assembled chassis, supplied ready for use, 28/2/6.



"PERSONAL SET" BATTERY ELIMINATOR

A complete kit of parts to build a Midget "Aldry" Battery Eliminator, giving approx. 60 volts and 1.4 volts. This Eliminator is for use on A.C. mains and is suitable for any 4-valve Superhet Receiver requiring H.T. and L.T. voltage as above, or approx. to 63 volts.

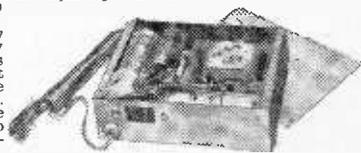The kit is quite easily and quickly assembled and is housed in a light aluminum case, size 4 1/2 in. x 1 1/2 in. x 3 1/2 in. Price of complete kit, with easy to follow assembly instructions, 42/6. In addition we can offer a similar COMPLETE KIT to provide approx. 90 volts and 1.4 volts. Size of assembled Unit 7 in. x 2 1/2 in. x 1 1/2 in. Price 47/6.




★ Send 9d. P.O. for our STOCK LIST, showing many KITS OF PARTS for Sets and Battery Chargers and "hundreds" of Wireless Components. When ordering please include 1/6 to cover cost of postage and packing.

STERN RADIO LTD., 109 & 115, FLEET STREET, E.C.4.

Telephone: CENTRAL 5814 & 2820

PRATTS RADIO

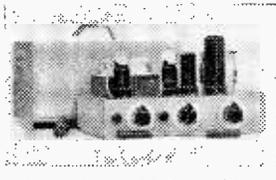1070 Harrow Road, London, N.W.10
 Tel: LADbroke 1734.



(Nr. Scrubbs Lane)
AMPLIFIERS READY TO USE

MODEL AC10E (as illustrated), 10 watt, 4 valve unit neg. feedback, separate mike and gram inputs, 2 faders and tone control, input volts, mike .002 gram 21 v. 210-7-8.
MODEL AC18E, 6-valve unit with p/pull output of 181 watts, separate mike stage and separate mike

and gram inputs, 2 faders and tone-control, feedback over 3 stages. Input volts, mike .003 gram 3 v. 215-5-0. **MODEL AC32E**, 12-18-0. **MODEL L10E**, D.C.A.C. mains p/pull output of 10 watts. Spec. as AC18E. 212-18-6. All above are complete with cases and chrome handles. Outputs match 3, 8, 15 ohm speakers. **MODEL AC8C**, 5-valve chassis with p/p pull output of 10 watts. For record or radio reproduction. Output to 3, 8, 15 ohms. H.T. and L.T. supply for feeder. 210-10-0.
MODEL AC4C (A.C.) or **MODEL L4C** (D.C./A.C.) 3-valve 4 watt amplifier chassis for records, etc. Output to 3 ohms. 25-15-0. All units are carriage paid. As supplied to hundreds of domestic and industrial users since 1945. Stamp for fuller details.
 Rohermel D104 Crystal Microphone 25-5-0. Acos 22-1, 22-2, 26-6-0. Collaro Record Players (A.C. only) with motor turntable pick-up and auto-stop. Magnetic. 26-9-6; Crystal. 26-15-6.
SPEAKERS, Rola 10in., 35/-; 8in., 30/-; Gramplan 12in., 27/-; Goodmans 12in., 28-12-6. Microphone cable, 1/6 yd. Stylus needles, play 6,000 records, 6/6. Jack plugs, 1/9 each.
COILS, Denco L.M. wave T.R.F. with reaction, 6/6; Wearite "P" coils, 3 each; Weymouth "H", 3/6 each; Weymouth I.F.S. 15/- pair; Wearite standard, 10/- each; Miniature, 10/6 each.
TRANSFORMERS, ETC., 2 x 350 v., 0-4-5 v., 2 a., 0-4-6 v., 4 a., 19/6; ditto, 2 x 250 v., 19/6. Speaker Transformers, 6/6 to 3 ohms, 4/3; 1/6 p/p to 3, 8, 15 ohms, 19/6. 1S4/3S4 Miniature type, 5/3.
TUBES, 60 m.a., 15 hy., 300 ohms, 5/3; 100 m.a., 20 hy., 400 ohms, 16/6; 150 m.a., 10 hy., 200 ohms, 16/6; 90 m.a., 10 hy., 180 ohms, 13/6.
V.A.R. CONDENSERS, Solid dielectric, .0003 or .0005, 4 each; **FIXED CONDENSERS** (only 1951 stock offered), 8-8, 4/9; .0002, .0003, 8d.; .0005, .001, .002, .006, 9d.; .01, .05, .1 mfd., 10/4.
MISCELLANEOUS, 6K7, 6T7, 6J5, all 7/6; 1S5, 1S4, 3S4, 1T4, 1R5, all 9/6 each; 3 a. droppers, 800 ohms, 4/6; 2 a., 1,000 ohms, 4/6. B7G bases, 8d. Lincrod, 3a. 60 ohms, 1/4. 74 ft. cable. All goods new. Post paid over 11. C.W.O. or C.O.D.

FREE TO AMBITIOUS ENGINEERS!

This 144-page Book

Have you sent for your copy?



'ENGINEERING OPPORTUNITIES' is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £14 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.
 Electrical Eng.
 Civil Engineering
 Radio Engineering
 Automobile Eng.
 Aeronautical Eng.
 Production Eng.
 Building, Plastics,
 Draughtsmanship
 Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I. Mech. E.
 A.M.I.C.E.
 A.M.I.P.E.
 A.M.I.M.I.
 L.I.O.B.
 A.F.R. Ae.S.
 B.Sc.
 A.M. Brit. I.R.E.
 CITY & GUILDS
 GEN. CERT.
 OF EDUCATION
 etc., etc.

--- FREE COUPON ---
 Please send me your FREE 144-page "ENGINEERING OPPORTUNITIES"

NAME
 ADDRESS
 Subject or Exam.
 that interests me
 British Institute of Engineering Technology,
 409B, Shakespeare House,
 1719, Stratford Place, London, W.1

BIET

PREMIER RADIO CO.

(REGD.) B. H. MORRIS & CO. (RADIO) LTD. ESTAB. 40 YEARS

HEAD OFFICE & MAIL ORDER (Dept. P.W.), 207, EDGWARE ROAD, LONDON, W.2

OPEN TILL 6 P.M. SATURDAYS

Phones : AMBASSADOR 4033 & PADDINGTON 3271/2

TERMS OF BUSINESS :—CASH WITH ORDER OR C.O.D. OVER £1. Please add 1/- for Post Orders under 10/-, 1/6 under 40/-, unless otherwise stated.


BALANCED ARMATURE LOW RESISTANCE HEADPHONES, Type 1, 5/11 pair. Type 2, 8/11 pair.
HIGH RESISTANCE HEADPHONES, 12/6 pair.

LIGHTWEIGHT HIGH RESISTANCE HEADPHONES, 14/6 pair.
BRAND NEW R1155 RECEIVERS, in original cases, complete with 10 valves, £12/10/-, 7/6 Packing and carriage.

THREE PIECE AERIALS—Brand New.
12ft.—3 4ft. screw-in sections of copper-plated steel, highly flexible with non-stick screw jts., tapering in. to 4in. Brand new in container. 8/9. Also plug-in type 3/9. Packing and carriage, 1/6. Insulated Base, 2/6.

EX-R.A.F. TRANSMITTER T1154 SERIES
A medium High Powered Transmitter for C.W.—M. C. W. 3 Frequency Ranges 10-5.5 mc/s. 5.5-3 mc/s. 500-200 kc/s. 7 Stop Mechanism is arranged so that predetermined frequencies can be held or returned to. Complete with 4 valves—2 PT15 pentodes in parallel driven by an ML6 in a series fed Hartley oscillatory circuit. A further ML6 valve provides a 1200 cycle slide tone to enable the operator to log his transmission on C.W. Price 39/6, plus 10/- Pkg. & Carr.

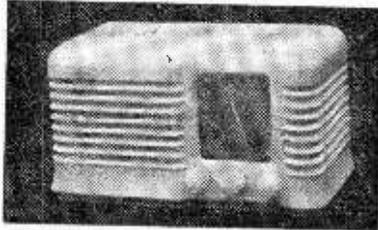BUILD A PROFESSIONAL-LOOKING RADIO AT LESS THAN HALF TO-DAY'S PRICE



We can supply all the parts to help you.
Bakelite Cabinet (Brown or Ivory), 17/6. Packing and insurance, 2/6.
Punched Chassis, 3 valve plus rectifier T.R.F. 3/9
Engraved Glass Dial, 180-550 and 800-2,200 m. with station names, new wavebands, 1/6
T.R.F. COILS 180-550, 800-2,200 metres, pair 6/6
Drum (2 1/2 in. diam.) 1/8
Driving Head 1/8
Double Pointer 4d.
Spring 3d.
Nylon Cord (yard) 6d.
Dial Front Plate 2/6

SEND 1/6 FOR EASY-TO-FOLLOW POINT-TO-POINT DIAGRAMS AND CIRCUIT DIAGRAM, which show you how YOU can build the Receiver illustrated at HALF TO-DAY'S PRICE.

THE COMPLETE KIT to construct a 3-valve plus rectifier TRF Receiver for use on 200/220 v. A.C. mains can be supplied at 26 9s. 6d., plus 2/6 packing and carriage.
Each Kit is complete in every detail, nothing has to be made or improvised. Easy-to-follow point-to-point diagrams are supplied, making construction very simple. The Dial is illuminated and the Receiver, housed in a Bakelite Cabinet size 12in. x 5in. x 6in., presents an attractive appearance. The valve line-up is 717A—H.F. Pentode, V R 116—Detector, ATP4—Output, and Metal Rectifier.
Waveband coverage is for the medium and long bands. Choice of Walnut or Ivory-coloured Cabinet.
EX U.S.A. V.I.F. AERIAL, with Untuned Detector Stage consisting of VR2 Valve. Brand new 5"-CRYSTAL MICROPHONE.
An entirely insulated crystal microphone which can be safely used on A.C./D.C. amplifiers. High impedance. No background noise, really natural tone. The ideal Mike for tape, wire and disc recording and sound projectors. Price 22/6.

IMPORTANT ANNOUNCEMENT : We cannot accept responsibility for, or guarantee any kit or component sold as a Premier product by firms other than ourselves. All prices quoted are those ruling at the time of submitting advertisement copy, and are subject to alteration without notice.

SHORTAGE OF RADIO & T.V. ENGINEERS

The demand of Industry for our trained students is still greater than we can supply—and is likely to remain so for many years. We offer

FULL TIME DAY COURSE

1 year course in Principles and Practice of Radio and Television.

Next course commences 25th August.

Write for FREE BROCHURES giving details of the above, of our 3-year course, and of others.

E.M.I. INSTITUTES—the only college which is part of a great industry.

E.M.I. INSTITUTES (Dept. 32A)

10, PEMBRIDGE SQUARE, LONDON, W.2.

Tel : BA15water 5131/2.

Associated with "H.M.V." MARCONIPHON COLUMBIA ETC.

1A.1a

SPARKS' DATA SHEETS

are the Safest, Simplest and Finest Constructional Sheets of Guaranteed and Tested Radio Designs.

SPARKS' SETS SET THE STANDARD

ANNOUNCING MY NEW 'E' SERIES ECONOMY PLUS EFFICIENCY

HERE ARE THE FIRST TWO

THE "ENTERPRISE" A Very Efficient 3-Valve Plus Rect. TRF. Med/Long-wave Receiver for A.C. Mains. 4½ Watts of Quality on Radio and P.U. Good Range and Selectivity for a circuit of this type. External or Mains Aerial. A Fine, Economical Set for the Home. D/Sheet, etc. 3/2½. Post Paid.

THE "ENSGN" For those who want Good Quality from their "Local" Stations. In areas where high selectivity is not essential. Plus most pleasing P.U. reproduction, this Model is THE one. 4½ Watts output. Med/Long-waves. External or Mains Aerial. Valves 637, 639 Plus Rect. Easy and Economical to Build. D/Sheet, etc. 3/2½. Post Paid. Many other Designs Available.

STAMP FOR LIST COMPONENTS SUPPLIED
L. ORMOND SPARKS, (P),
48A, HIGH STREET, SWANAGE, DORSET

THE POCKET LOUDSPEAKER SET

This is the title of a forthcoming publication giving constructional details of a midget loudspeaker receiver small enough to fit in the jacket pocket. This receiver is fully self-contained, no aerial, earth or external power supply being required. The midget batteries used are of the new layer type specially produced by a famous British maker for this class of receiver. Only one single-gang midget condenser is used for tuning, and the receiver requires no alignment. The midget components chosen are current British production, not surplus or foreign. You can reserve your copy of the very full instructions and large clear drawings by sending 3/6 to the address below. Your copy will then be posted immediately upon publication.

SWIFT RADIO (W),

137, COTHAM BROW, BRISTOL, 6. Orders by Post Only.

Programme Pointers

By Maurice Reeve



THE once popular Quiz seems rather less in favour just now than recently, but the programmes which turn themselves into public forums for the airing and discussion of anything of topical moment never were in such vogue. "We Beg to Differ," "Dear Sir," "Any Questions?" and "Taking Stock"—this political discussion on Friday evenings takes on different titles—readily come to mind. The first three are entertainment pure and simple, even when serious problems come under review.

"We Beg to Differ"

I think this earns pride of place. It maintains its highly sophisticated standards remarkably well, whilst the clever handling of its questions with a cheeky insouciance is on a uniformly high plane. It was most interesting to observe, however, that no adequate substitutes could be found for the original company of John Clements, Kay Hammond and Co., and they were promptly recalled *in toto* in order to save the show. As with *Itma*, it was they or nobody.

"Dear Sir"

This is the reading of correspondents' letters by various people who are, I presume, supposed, by their several voices and general personalities, to resemble the actual writers. It doesn't always come off. This is usually on Thursday evenings, and "We Beg to Differ" on Monday evenings.

"Any Questions?"

But the most pretentious of these programmes would seem to be Freddie Grisewood's "Any Questions," in which the former announcer presides with great tact and charm over a team of four able "discussion men" who vary from week to week, but who include Ralph Wightman as often as not. As with Wilfred Pickles's "Have a Go!," "Any Questions?" is held in a different public hall each week, though the range of its travels is much more limited than the former, being, for the most part, let to wander up and down and round about an area of country which roughly corresponds to Hardy's Wessex.

When I hear questions debated such as "What would members of the team do if they woke up one morning and found they had changed their sex?," I wonder whether this usually diverting, amusing, yet instructing programme will eventually go the way the Brains Trust did, which, you will remember, was killed by the fatuity and imbecility of a large number of the questions which were put to it. Also, politics sometimes become a trifle acerbated, calling upon a gentle rebuke from the Question Master. But let us not anticipate these troubles enlarging themselves. At present it is a very competent and rewarding show.

Family Chronicles

The two family chronicles, "Mrs. Dale's Diary" and "The Archers," are as lusty as ever. Mrs. Dale, of course, has proved herself the feminine counterpart of Tennyson's "Brook." I haven't heard whether she was pleased at the windfall which dropped into the lap of her overworked and underpaid husband at the hands of Mr. Justice Bankwarts. Pleased she must have been; I should have referred to the degree of her pleasure.

The Archers continue to unfold daily their totally unsophisticated, uneventful and unruffled existences in pleasant quarter-hour snippets. Both these features rather remind one of popping into a newsreel theatre for an hour to watch similarly unimportant though pleasant events unfold themselves. Their whole charm and attraction would be spoiled if their compass were enlarged so that, instead of hearing about Rosie the sow's bonny family or Boris Archer's tiff with her boy friend, we were given someone absconding in an aeroplane and its subsequent wreck.

Mr. Dennis Arundell is one of the most versatile men now before the public. The range of his activities, hobbies and interests seem almost boundless. And he is an effective broadcaster. His present series, "Opera Roundabout," is a most acceptable pastiche of that most unapproachable and expensive form of entertainment. In forty minutes Mr. Arundell gets through a vast amount of operatic lore, reminiscences, interviews, recordings and whatnot. The operatic world is by reason of its musical associations, an even wider and all-embracing one than the theatrical. Mr. Arundell gathers it all together with great skill and very pleasing results.

Concerts

The most notable concerts of the past few weeks have been twelve, conducted for the BBC by the distinguished Italian Vittorio Gui. Eschewing the Latin theatricalities of his countryman, de Sabata, he is more the type of the most famous of all Italian maestros, Toscanini. Gui and the BBC Orchestra put in some sterling work. They also gave a Stravinsky concert at the Albert Hall under Cameron. The programme was largely of unfamiliar works, except for the glorious Symphony of Psalms.

Care must be taken to guard against the "Queen Elizabeth" joke, now that our Sovereign bears this illustrious title. One, in a recent "Music Hall" bill, was in questionable taste to say the least.

The best plays, and very good by virtue of being by masters of their craft, were "You Never Can Tell," "Caesar and Cleopatra," "The Prodigious Snob" (Moliere's "Le Bourgeois Gentilhomme"), and St. John Ervine's "Friends and Relations."

Converting an A.C. Bridge

By J. S. Kendall

OFTEN the amateur comes across a bridge circuit that is driven either from a buzzer or separate audio oscillator, and uses a pair of phones as a detecting device. Quite a lot of people object to phones and a visual tuning indicator is a favourite alternative, but for its use one side of the bridge must be earthed. Look for a moment at a typical bridge circuit, Fig. 1. In (a) the input is earthed, whilst in (b) one side of the phones that are used as the indicator are earthed. If compared carefully it will be seen that the balance formula holds good in both cases. It is quite a simple matter to turn the bridge on its side, as it were, in order to use the earthed detector, but this means that the tone must be applied between two non-earthed

A short article on how bridges that are not at the moment driven, off the A.C. mains can be converted to work from them. Full circuits are given.

to eliminate, or at least reduce, the harmonic content. The case of the 1,000-cycle supply is a different matter. A suitable oscillator is shown in Fig. 3. This is the well-known Franklin circuit. The valve is the popular 6SN7GT now widely available on the ex-W.D. market, but if size is of consequence the Mullard ECC40 can be used. The circuit compensates itself to a very large extent for the load drawn. The transformer used should have as low resistance windings as possible in order to obtain a high Q. The tuning of the circuit is done by varying the capacity of the condenser marked "?".

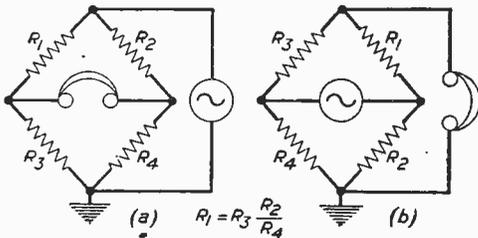


Fig. 1.—Typical bridge circuits.

points; this is quite simply effected with the aid of a close-ratio transformer.

If a buzzer of fairly low frequency was used in the original, a 50-cycle wave will be convenient. This can be obtained from the smoothing circuit, as is shown in Fig. 2, but if the rectification is full-wave, the frequency feed to the transformer will be doubled to 100 cycles! A wave obtained in the foregoing manner is of very poor shape and contains a very large proportion of harmonics. The condenser shown dotted should be joined in circuit to tune the output of the transformer to the required frequency

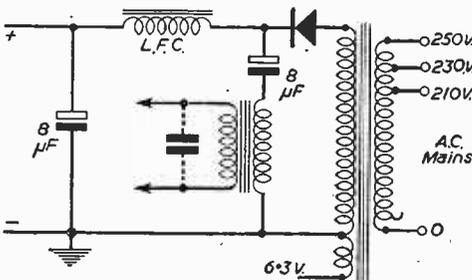


Fig. 2.—Obtaining a 50-cycle wave.

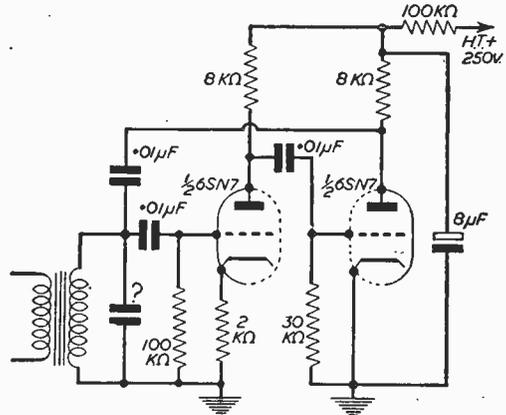


Fig. 3.—Suitable oscillator circuit.

There is a very large range of visual tuning indicators, but the writer's favourite for bridge work is the Y61, as it works over such a small voltage range. If greater sensitivity is required, the circuit shown in Fig. 5 can be used, as it gives an amplified result, but as the tube is only about one-tenth as sensitive as the Y61, there is very little advantage to be gained.

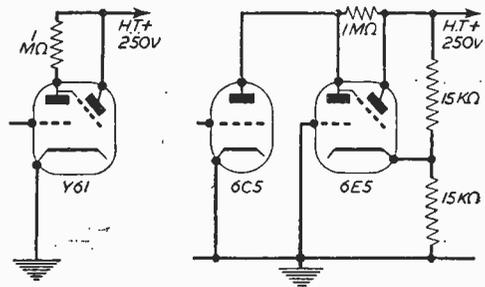


Fig. 4.—A visual indicator.

Fig. 5.—Improved indicator circuit.

"BURGOYNE"



MAGNETIC RECORDING HEADS
For Superior Performance at Lower Cost—Record, Playback and Erase Heads giving first-class frequency response.

★ High Impedance. ★ Positive Fixing Method. ★ Half Track Width. ★ Totally enclosed with Tape Guide. ★ Wide Frequency Range.

Record/Playback **39/6** EACH, OR Set of 2 for 23/- or deposit and 12 monthly Erase. payments of 8/-, OR Set of 3 for 38/6 deposit and 12 monthly payments of 10/-.

DISTRIBUTED EXCLUSIVELY BY M.O.S.

AMPLION ALL-PURPOSE TEST METER

★ HIGHEST QUALITY MOVING COIL METER MOVEMENT.
★ SELF-CONTAINED INTERNAL BATTERY.

★ 10 RANGES.

Who would have thought that all these features—and more—could be made available in a high-grade all-purpose multi-range Test Instrument for so small a cost! The outstanding sensitivity of this precision moving coil instrument makes it ideal for all who require a universal test meter for professional or amateur use.

£5 CASH
or 2/- deposit and 12 monthly payments of 10/-.
High-grade Leather Case if required, 15/- extra.

SENSITIVITY. 1,800 ohms per volt on all D.C. and A.C. ranges.
RANGES. 10 v. 100 v. and 500 volts D.C. and A.C.
• 50 ma. and 500 ma. D.C.
• Resistance up to 200,000 ohms (3,000 ohm centre with self-contained battery).
• 5,000 volts range with a separate H.T. test prod. (8/6 extra).
• Supplied with test prods.

"BURGOYNE" TAPE TABLE

★ Precision built. ★ 3 motors with ample reserve of power. ★ Fast re-wind facilities. ★ Tape speed: 7 1/2 in. per second. ★ Heavy precision balanced flywheel. ★ High fidelity heads—perfect alignment. ★ Half track width with high impedance heads. ★ Negligible "wow" and "flutter." ★ Take up spool supplied. ★ Circuit diagram included. ★ For use on A.C. mains.

£16/10
CASH or £6/10/0 Deposit and 12 monthly payments of 20/- Plus 10/- curr. & packing.

AVO Precision Electrical Testing Instruments

A dependably accurate instrument for testing and fault location is indispensable to the engineer who builds or services his own equipment.

	Cash	Deposit	H.P.	12 Monthly Payments of
Model 7 and 40 Avometers	£19 10 0	£26 0 0		25/6
Universal Minor	£10 10 0	£3 10 0		15/-
Signal Generator, Mains or Battery				
Universal Bridge	£30 0 0	£10 0 0		37/6
Electronic Testmeter	£40 0 0	£9 0 0		32/6
Valve Characteristic Meter	£50 0 0	£16 0 0		52/6
D.C. Avometer	£5 5 0	£1 15 0		8/2
Model 8 Avometer	£23 10 0	£7 15 0		30/-

The full range of AVO test gear as previously advertised is still available, but we would remind you that supplies are now getting very difficult owing to the shortage of raw materials and the re-armament programme. Buy now on our easy Hire Purchase terms while we have stocks!

PULLIN MULTI-RANGE TEST SET Series 100

The universal testing set for Service Engineers. Sensitivity 1,000 ohms per volt. Strong metal case with carrying handle—complete with leads having detachable bulldog clips and test prods. Size 9in. by 5 1/2 in. by 4 in.

RANGES.
AC/DC Volts: 10, 25, 100, 250, 500, 1,000.
D.C. Milliamps: 2.5, 10, 25, 100, 500.
AC/DC Microamps: 100 Microamps 10 volt range.

Resistance ranges: 0/1 Meg. (13,500 ohms mid-scale).
0/10,000 ohms (130 ohms mid-scale).
£11/11s. CASH or 40/- Deposit and 12 monthly payments of 20/-.



MAIL ORDER SUPPLY CO.,
THE RADIO CENTRE
33 TOTTENHAM COURT ROAD, LONDON, W.1.
MUSEum 6667

THE HAM'S SHOP

65, DONECALL STREET, BELFAST

DEFINITELY THE CHEAPEST RADIO AND ELECTRICAL SHOP IN UNITED KINGDOM

- ROD AERIALS, 12ft., 5/6. WHY PAY MORE!
- MAINS TRANSFORMERS, 425-0-425v., 6.3v. at 10a. 5v. at 8a., £2. 250-0-250v., 6.3v. and 5v., at 16/-, 350-0-350v., 6.3v. and 5v. at 17/6. 350-0-350v., 6.3v. and 5v. (H.M.), £15/-.
- FIL. TRANSFORMERS, 6.3v., 5a., at 7/6.
- ELECTROLYTIC CONDENSERS, 32 mfd., 3/-; 50 mfd., 50v., 1/3 and 1/6; 10-10 mfd., 450v., at 4/6; 5 mfd., 2,000v., 5/-; and 6 mfd., 2,000v., 5/-.
- TUBULAR CONDENSERS, 1 and 25, 4d.
- MICA CONDENSERS, .001 to .0001, 6d. each.
- VOLUME CONTROL, 1, 1 meg., with switch, 3/6.
- RECTIFIERS, 280v. 80 ma., 5/6 each.
- T.V. RECTIFIERS, J.50, 7/6.
- REEL FOR TAPE RECORDERS, 2/-.
- TAXOY AMPLIFIERS, 60 watt, £4 each.
- VALVES from 4/6.
- LOUDSPEAKERS from 10/-.
- S.M. DIALS, 1154, 7/6.
- CRYSTAL DIODES FOR CRYSTAL SETS, 3/- each. (Cannot be repeated.)
- VALVEHOLDERS, B7G, 10d. each.
- T.V. TUBES, VCR97, 32/6 each.
- T.V. TUBES, G.E.C. 9in., £4 each.
- ALADDIN FORMERS AND CORES, 10d. each.
- SLIDE RULES, 5/- each.
- PLUG AND SOCKETS, 3-pin, 2/6.
- IRON ELEMENTS, 1/8 each.
- TRANSMITTERS, 1154, 12/6 (while they last). (Less meters and resist.)
- SPEAKER GAUZE, 1/6 per square foot.
- SYSTELEX, All sizes, from 2d. per yd.
- TRANSFORMERS, 1F., 455, 10/- pair.
- TUBING FOR TELEVISION.
- CO-AX CABLES, 1/3 per yard.
- CHASSIS WITH COMPONENTS, 6/- each.
- RESISTANCES, from 4d. each.
- CHOKES, 50 ma., 4/6.
- CHOKES, 160 ma., 15/-; 80 ma., 7/6.
- DIALS, S.M., 5/-.

ALL PARTS FOR TELEVISION.
THOUSANDS OF OTHER BARGAINS TOO NUMEROUS TO MENTION.



THIS FREE 104 PAGE BROCHURE

describes the Courses of Training offered by E.M.I. Institutes—the only Postal College which is part of a world-famous Industrial Organisation.



- Aero. Eng. • Motor Eng. • Draughtsmanship • Elect. Eng. • Prod. Eng. • Management Languages • Refrigeration Eng. • Civil Service • General Cert. of Education • Radio, TV and Electronics • University Training • Maths. • Mech. Eng. • Heating and Ventilation Eng. • Public Speaking • Police • Telecommunications, etc. etc. • Special Courses for A.M.I.Mech.E., A.M.I.C.E., A.M.I.P.E., A.M. Brit. I.R.E., A.F.R.Ae.S., City & Guilds Examinations, etc.

E.M.I.

Institutes
associated with
MARCONIPHONE
COLUMBIA
H.M.V.
ETC.

COURSES FROM
£1
PER MONTH

Post this for a FREE copy of "Successful Careers" to E.M.I. Institutes, Dept. 32, 43 Grove Park Road, Chiswick, London, W.4.

Name

Address

I.C.9

LYONS RADIO LTD.

3 GOLDHAWK ROAD Dept. M.P.
SHEPHERDS BUSH, LONDON, W.12

Telephone: SHEPherds Bush 1729

RECEIVERS, TYPE R.1155.—One of the best known and most popular of ex-Gov. communications receivers. Frequency range in 5 switched bands covers 17-100, 200-500, 500-4,000 metres. Magic eye tuning, with B.F.O., A.V.C., R.F. amplifier, two I.F. stages, etc. Power requirements approx. 220 v. D.C. at 60 mA. and 6.3 v. at 3 A. In new condition and aerial tested before despatch. PRICE, £12/10/-, carriage 7/6.

R.1155 POWER PACK/OUTPUT-STAGE.—A unit to operate the R.1155 direct from A.C. mains and to provide for a speaker output. Assembled in an enclosed metal case, approx. 10 x 6 1/2 x 5 1/2 in. Employs 5Z4 rectifier and 6V6 output valves. Fitted with all leads and plugs clearly marked for immediate connection. PRICE £57/6, carriage 3/6.

SPECIAL OFFER.—Receiver type R.1155 together with power pack output-stage unit. PRICE £16/16/-, carriage 10/-.

CATHODE RAY TUBES TYPE VCR97.—Brand new and unused in maker's original crates. All tested by us to ensure functioning properly and that full TV picture obtainable. PRICE 39/6, carriage 5/-.

MOVING COIL SPEAKERS.—Brand new by famous maker (radio manufacturers surplus). 8in. light weight (only 51 ozs.).

Supplied with high perm. mag. PRICE 17/6. 6in., 15/8. 3in., PRICE 14/-.

AMPLIFIER UNITS, TYPE A1185A.—These units for conversion, as described in the April issue of "Practical Wireless."

Supplied with 2 valves, EL32 (VT52) and 6BQ8 (VR55), PRICE 21/-, or less valves. 7/6, post 2/-.

POWER UNITS, TYPE 87.—Rotary converter units for 24 v. D.C. input and having a twin D.C. output of 250 v. at 50 mA. and 6.5 v. at 2.5A. Can be operated in reverse from D.C. mains or 6 v. Totally enclosed in neat metal cases, 8 1/2 x 6 1/2 x 4 1/2 in. In good condition and working order. PRICE 9/6, post 2/-.

DIPOLE AERIALS FOR ALL CHANNELS

These television Dipole Aerials consist of 2 elements of strong 3/16 in. diameter tubing and a heavy bakelite insulator.

Price for all stations, 17/6 Each, plus 2/6 Packing & Carriage. Don't be disappointed! Stocks are rapidly drying up and, although your station may not yet be in operation, we recommend that you obtain one of these aerials now!

POLYETHYLENE DIPOLE INSULATORS.—With moulded in brass studs to take 3/16 in. i/d dia. tubing. 5/- Each, plus 1/6 Packing & Carriage. Another line that will be unobtainable shortly.

SEND S.A.E. & 3d. IN STAMPS FOR OUR CLEARANCE LIST.

WALTON'S WIRELESS STORES
48, Stafford St., Wolverhampton

LONDON CENTRAL RADIO STORES

SPECIAL OFFER

VCR97 TUBES. 4v. Heater, 2 kv. As new, in original crates, 32/6, 5/- carriage.

TELESONIC 4-VALVE BATTERY PORTABLE (Fixed Range). Type YA4915. Including three XH and one XP Hivac midjet valves. Can be adapted for Deaf Aid or Midjet Receiver, but we do not supply information on this point. Batteries required 3v. L.T., 97v. H.T. In metal case, size 5 1/2 x 7 x 2 in. Weight 4lb. Less batteries, 45/-, Carr. & pkg. 2/6.

2-VOLT VIBRATORS. Type R76C. 7-pin self-rectifying. Output 200v. at 60 M.A. Made by Electronic Laboratories, Inc., 7/6.

NEW BLOWER MOTORS. 24v., 22/6, post & packing 1/6.

EX-G.P.O. TABLE MICROPHONE with plug and lead, 9/6 each, post & packing 2/-.

NEW NIFE ACCUMULATORS. 2.5v. 2 1/2 amp. for 8 hours. 4 1/2 in. x 1 1/2 in. Flat. 6/6. 9d. post, etc.

SELECTOR SWITCHES. 3 Bank, 19/6; 6 Bank, 1/2 Wipe, 27/6; 8 Bank, 1/2 Wipe, 42/6; 8 Bank, Full Wipe, 47/6.

WALKIE-TALKIE. Trans. and Receiver, Type 38 M.K. 11. Range 7-9 mcls. Requires 3v. L.T. 120 to 150 H.T., complete with 4 ARP12, 1 ATP4 valves, 1 pair Truvox Mikes, 1 pair Headphones and Aerial, also Battery Junction Box, Wiring Diagram with Set. £4/10/-, 2/6 carriage. Less Batteries.

AC DC GEARED LAMINATED MOTORS 24 volt unshrouded. Size 5 in. x 3 1/2 in. x 2 in. 22/6.

ROCKMAN SOLDERING IRON 200-250 volt. Gun Shape 19/6.

Having Long Contract we can still supply Reconditioned Philco Sets.

PHILCO SETS RECONDITIONED GUARANTEED (UNIVERSAL MAINS)

ALL-WAVE TABLE MODEL. Medium or Dark Walnut Cabinet. Excellent Performance. 5-Valve, £8/15/-.. Size 18 1/2 x 14 x 9 1/2. Carriage and packing 10/6 extra.

LARGE TABLE MODEL in Light Walnut. With Large Dial in Metres and Frequency 2-Waveband. Exceptional High Gain. 115/-.. 10/6 carriage and packing. 5-Valve. Size 19 x 16 x 10 1/2.

MEDIUM TABLE MODEL known as Cathedral Model. 2-Waveband, 110/-.. 10/6 carriage and packing. 5-valve. Size 19 x 14 x 10.

Carriage charges relate to Inland only.

WE WANT TO BUY RADIO EQUIPMENT—AMPLIFIERS—TAPE RECORDERS—TELEVISION TEST EQUIPMENT—COMPONENTS

LONDON CENTRAL RADIO STORES
23, LISLE STREET, W.C.2

Phone/Grams: GERrard 5969

NORMAN H. FIELD,

68, HURST ST., BIRMINGHAM, 5,
Mail Order Dept.

64-65, CHURCH LANE,
WOLVERHAMPTON.

VALVES

At 11/8: 6BQ8, 5R4G, ECC32, 5Y3/5Z4, 6V6GT, 6Q7, X61, 6SN7, KT66, 6F6, 807, 6K6. At 10/-: 1616, 6SQ7, PEN46, 50Y6/GT. At 9/-: 6F7, ARP6, 6X5, KT83, 1T4, 1S4, 1R5, 1S5. At 8/6: VR52, EL32, VR55, 12SL7, AT 7/6: 7B7, 7T, 6K7, 6J7, VR150, 6C6/GT, 707, VR119, 6Y7/G, 7C5, 0Z4, 12A6, 12A7, VR136. At 7/-: 6B8, 6B8C, 1G6/GT/C, 1A5/GT, 6K7G, VR53, EF39, EF36. At 6/6: 6AB7, ARP12, VP23. At 5/6: 6SS7, 12J5, RK34, 6SH7, VR91, EF50, 3D6, 7Y11, VT501. At 5/-: 6L6, 12SK7, 6SK7/GT, 2A3, VU133, 1625, VT51, PEN20A, VR118, KT2. At 4/6: VR65, SP61, 6J/5G, 6J5GT, 12SH7, 12H6, VU120. At 3/6: RKR72, ARP3, 9D2, 6H6. At 3/3: VR18, OC34, RK34, VU133, 2155G, VU111, HLZ, VR21, VR65, P81, VR85A, SP41. At 2/6: VR54, EB34, VR92, EA50, VR78, D1, CV6.

SPECIAL OFFER !
KIT OF VIEWMASTER VALVES
AT HALF PRICE
£6.4.0

VIEWMASTER

Coil Kits, Holme Moss and Birmingham: 14 Coils and 1 R.F. Choke, 21/6.

Plessey Focus B.T. 72004, 22 8. Scanning Coils, 29/3.

Width Control, 7/6. Heater Transformer, 25 6. Frame Transformer, 19/6.

Micadisc 800 p.p., 1/6 each.

E.H.T. TRANSFORMERS.—2,500v. 5M'A. 4v. 2amp., 0-2.4v. 4amp., 210-250v. 50 cycles. Completely wax impregnated, 45/- each.

Please include something for post. Money Back Guarantee.

ARMY MORSE KEY and Buzzer Practice Set, 6/6.

TYPE 18 TX CHASSIS, partly stripped, but can easily be put into working order; less valves, 15/9.

BLACK BAKELITE INSTRUMENT CASES, complete with strap and 1/2 in. plate glass front. 3 1/2 in. x 3 1/2 in. x 2 in. Take any meter up to 2 1/2 in., 3/6.

NEW UNSPILLABLE EXIDE PO-2 accumulators, 11A.H. 4 1/2 x 3 1/2 x 2 1/2 in., 19/6.

TRI196 CIRCUIT AND CONVERSION DATA. 1/3. 1147A or B, 1/6.

New IN34 CRYSTAL DIODES, 5/6.

P.M. SPEAKERS, 8in. Rola 20/-.

MULTIMETERS, 2 1/2 in. Supplied as a Kit with black bakelite cases, 6in. x 4 1/2 in. x 1 1/2 in. and resistors for D.C. ranges 0-3, 0-30, 0-150, 0-300, 0-600 volts and 60 m/A. Scale also reads ohms 0-5,000 with 1 1/2 volt Battery, 24/6.

6v. VIBRATOR PACK in black steel case, 7 1/2 x 5 1/2 x 3 1/2 in. Output 200 v. 40 mA., 22/6.

SELENIUM RECTIFIERS. H.W. 250v. 120 mA., 9/-.. F.W. 6 or 12v. 4 A., 26/-; 3 A., 14/6; 1/2 A., 5/6.

3-GANG .0005 MFD. VARIABLE CONDENSERS, 3/6.

TRANSFORMERS, 200-240 volts, tapped 3-4-5-6-8-9-10-12-15-18-20-24 and 30 volts at 2 amps., 21/6 Post Paid.

BLACK POLISHED BAKELITE PANELS. 16 1/2 in. x 7 1/2 in. x 1/2 in., 3/-.. Red or Light Blue, 3/6. All Post Paid from:

THE RADIO & ELECTRICAL MART
253b, Portobello Road, London, W.11.
Phone: Park 6026.

OPEN TO DISCUSSION

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

High-gain Amplifier

SIR,—A friend and I each individually tried an SP61 as a "high-gain" amplifier, using the resistance values given in Mr. Kemsey-Bourne's article in the August, 1951, PRACTICAL WIRELESS. These values of 50 K and 200 K Ω for plate and screen respectively, gave most disappointing performance. Far from providing a voltage gain of 150, the tube gave far less amplification than a 6J5 or L63. When, however, the values were changed to .5 M Ω and 2 M Ω , the tube worked as it should. We recommend bypassing the screen with a 0.05 μ F to ground; 2 K Ω also would be a more suitable value for the cathode resistor.

Perhaps Mr. Kemsey-Bourne has some explanation to offer: some factor we overlooked. We can hardly credit that the amplifier was worked to full output from a low-level mike. The only, and yet fantastic, explanation seems to be that the very efficient AC2PEN did most of the amplification.

As a student I appreciate your excellent magazine, especially as regards the very modest price. American magazines retail at 3s. 9d. to 5s. here (monthlies).—C. E. LATSKY (Cape Town, S. Africa).

The Modern Switch-tuned Feeder

SIR,—The coils specified for the above feeder in the April issue are our old type, which have now been superseded by a new range. Exact equivalents for those specified are available, however, and these are listed below. Tag-rings are fitted to make connections easier, but the new coils are otherwise the same as the old ones.

Perhaps this information will be of help to readers:

"P.W." circuit ref.	Osmor Type No.
L1.2	QA5
L3	QA6
L4.5	QO8
L6	QO9
H.F.C.	QC1

Retail price, 4s. each. (Data leaflet supplied free on request).—Osmor Radio Products, Ltd. (Croydon).

Club for Tredegar?

SIR,—I have recently been enrolled a corporate member of the R.S.G.B., and for a long time I have been thinking of forming a Radio or Television Society in this district. When I first tried I had no real success, but I should be grateful if you would mention in PRACTICAL WIRELESS or *Practical Television* that I should be very pleased to hear from anyone in this district who may be interested. May I take this opportunity of saying a big thank

you for the portable radio blueprint in the PRACTICAL WIRELESS, March, 1952.—K. BRYANT ("Glan Howy," Park Place, Tredegar, Mon).

Magnetic Wire Recording

SIR,—I refer to "Thermion's" paragraph in the April issue of PRACTICAL WIRELESS and write to show that I, for one, would be very pleased to see an article on the construction of this type of equipment. I have been experimenting with recording over the last 12 months, but my results as far as reproduction of music goes are far from being good. I should, therefore, be very pleased to receive from "Thermion," or any reader, suggestions for improvement in quality. The whole of the equipment is home made, including the combined record, playback and erase head.

The reproduction of the amplifier alone on both speech and music is of good quality. From either a gramophone pick-up, wireless signal or microphone. But reproduction of music from the wire (recorded from the wireless) is of very poor quality; the notes not being clear and crisp by any means, no matter what the type of recording wire used.

I have tried various values of resistors from 0-250 ohms in series with the record winding of the head, but with music, on playback I still get distortion and a definite preponderance of bass notes. Various degrees of bass cut have been tried, but these merely produce a result varying from that described above, to a tinny sort of reproduction.

My present oscillator is a 6V6, and oscillates in the order of 30 to 50 kilocycles. Both air and iron-cored oscillator coils have been tried, and varying amounts of oscillator current fed into the record head, but without showing any improvement in quality. For erasing I use a permanent magnet, because the oscillator, although it will light a three-watt lamp with considerable brilliance, refuses to erase effectively.

The recording head which I use is of the low-impedance type, and the magnetic material is Mu-metal, one single lamination 0.048in. thick. My wire speed is 2ft. per second.

I have tried other variations, but without producing any noticeable improvement in quality. These are:

- (1) Increasing the wire speed.
- (2) Recording at different volume levels.
- (3) Trying recording heads made from different qualities and thicknesses of Mu-metal, and having various gap widths and number of turns.
- (4) Using wire on which recordings had not previously been made, and recording on each length of wire once only, then playing back.

Although my mechanical arrangement for winding

and laying the wire is by no means perfection, I feel sure I ought to get better results than I do. I shall be pleased if any reader who can offer any suggestions will be so kind as to communicate with me either direct, or through the columns of this excellent journal.—V. MORLEY, 220, Bolton Road, Walkden, Nr. Manchester.

Amateur Results

SIR,—I have studied the T.R.F. receiver by K. Berry, of November issue, and I thought you would be interested in my slight alterations *re* valves and coils used in my layout. First I have used four-volt valves: Marconi VMPGA, MH4, MSP Cossor, ACPEN2 and MU14. Coils used, 6-pin B.T.S., which I have a range from 9.5 to 2,200 metres. I broke up the ST900 and I am using same panel and position of coils as original; having rebuilt Mr. Berry's circuit in this style I have been through 17-80 metres. Results on 40-50 O.K., and no trouble to receive 80-250 the same. 185-580 good, with some slight breakthrough on 247 and 325, but only after 6.30 p.m. Using Eddystone for next band 500 to 1,700 better still, and on 850-2,200 B.T.S. as much as a W.B. 12in. Stentorian would give in a cabinet 39in. by 26in. by 22in., bottom part boxed off and padded with linen-covered flock and front of cabinet main fret for 12in. speaker over a lower one 15in. by 6in. boxed 7in. I used a Collaro pick-up unit complete, and I get great pleasure from this set. Quality is really grand and general tuning very sharp.—F. J. PORTER (Portsmouth).

Progress (?)

SIR,—I must agree wholeheartedly with A. E. Attwood (February issue) regarding battery sets. I am still relying on my old 12-year-old simply because I cannot find anything on the market to come up to it for selectivity and wide range of stations. Most new sets are powerful on the main stations but when I want A.F.N. or some weak one I am glad I have an old one to turn to.

I am a reader of your paper for some years now and I find one thing missing, that is, a page or so devoted to very poor amateurs like myself, these to consist of a sort of tuition for beginners. I find your paper a little advanced for a new reader.—JAMES WINTERS (Co. Tyrone).

[We gave a short series for the beginner last year and will shortly be giving another.—Ed.]

Balanced Twin Speakers

SIR,—I recently became interested in high-quality reproduction and after building a well-known and much advertised amplifier, also invested in a pair of special speakers. I am most disappointed in the results, most people agreeing that the reproduction is "too squeaky." This puzzled me for a time, and after some messing around I have come to the conclusion that we listeners have for so long been used to lack of the higher frequencies in our normal radio reproduction, that when we do hear it we do not like it. I am not getting too much top, as I took the trouble of going to several high-class musical concerts in order to note most carefully the "balance" of the orchestras involved, and I must say that there is more "brilliance" in the real

thing than I am getting on my installation. Have any other readers any comments in this connection?—G. HURRELL (N.W.9).

A Simple Phase Inverter

SIR,—I would like to thank D. W. Mynett for bringing to notice the phase inverter amplifier described in the April number. I have made use of it with a 6SL7, my set being universal, .3 amp. valves. I fed it straight from the diode, through the volume control, made the anode loads 220 K Ω and the cathode coupler 6,600 ohms. The triode section of the 6Q7 is now disconnected and earthed, but it could just as well be used as an infinite impedance detector. The result as compared with 6Q7 amplifier and 6J5 inverter is a better high-rate response without loss of bass, and better results on piano transients with no change in maximum volume of the set. It is a very economical circuit.—J. J. WIDDEN (Aberdeen).

Condenser Testing

SIR,—Referring to "a D.C. supply for experimental use" in the article "Preparing for the Season" of February, 1952, I beg to offer an addition to the circuit which may interest readers. By the addition of a wire-wound 50,000 Ω potentiometer resistance across the D.C. supply, condensers down to 0.0005 μ F can be tested and quicker results obtained on larger condensers up to 10 μ F. By lowering the P.D. across the condenser the neon lamp flickers more readily.

Having no 400 v. power pack, I arranged a "voltage doubler" circuit which gives an output of approx. 380 v. D.C. full wave. The rectifier used is ex war disposal and of unknown rating, but as a selenium rectifier could be identified by its 33 radiators of 1in. diameter and is about 7in. long. The neon lamp used is an "Osglim" fitted with a high internal series resistance. The condensers used are each 0.5 mfd. 1,000 v. D.C. Test.

This voltage doubles circuit, plus the potentiometer resistance has been very useful in "recharging" small H.T. batteries. When a "Batterymax" of 90 v. drops to 80 v. or so, I recharge at 4 mA. and the voltage is restored to 90 v. in about six hours.—K. COOMBS, A.M.I.E.E., A.M.I.Mech.E. (Cape Town).

A VOICE-OPERATED RELAY

(Continued from page 273.)

The only point which needs emphasis is that in all circuits the relay has a slight time-lag, since it will not operate until the condenser-resistance unit has built up the required voltage. This, however, merely results in a slight "clipping" of the call-signal or the first words spoken, which are usually unimportant.

If the relay opens again too quickly, i.e., at the end of a sentence instead of the end of the transmission, then experiments will be necessary to alter the C.R. factor until it provides a sufficiently slow discharge to hold the relay closed for the required time. The factors governing this are, of course, exactly the same as those which operate in a normal A.V.C. circuit, and no difficulty should be experienced in finding suitable values.

RI155 COMMUNICATIONS RECEIVER.

—Another quantity of these famous Bomber Command Receivers have just become available, and we take pride in offering them as the finest sets of this type that we have seen, being BRAND NEW IN MAKER'S CASES, and in immaculate condition. A world station getter, this set covers 5 wave ranges, 18.5-75 mcs., 7.5-3.0 mcs., 1,500-600 kcs., 500-200 kcs., 200-75 kcs., and is easily adapted for normal mains use, full details before despatch. ONLY £11.19.6 (carriage 10/6). A factory-made set comes pack with output stage, which covers the RI155 immediately can be supplied for £5.10.0.

INDICATOR UNIT TYPE 6.—Contains 6in. C.R. Tube, VCR97, 4 valves EF50, 1 of EB34, and 1 of EA50. The unit recommended for conversion to the "Wireless World" General Purpose Oscilloscope, full details supplied (or available separately, 1/-) ONLY 79.6 (carriage, etc., 7/6).

INDICATOR UNIT TYPE 6c.—Contains 5in. C.R. Tube, VCR97, 2 valves EF50, 1 of EB34, ONLY 51. (carriage, etc., 5/-).

MODULATOR TYPE 67.—Contains fully-smoothed normal A.C. Mains power pack, transformer being 345 v.-0-345 v. at 200 ma., 6.3 v. 5 a., 6.3 v. 20 ma., 5v. 2 a. Also contains 6 valves SP81, 3 of EB50, 2 of EB34, and 1 of 524. Complete in metal case, size 18in. x 8 1/2in. x 7 1/2in. ONLY 72/6 (carriage, etc., 5/-).

CLASSIS OF POWER UNIT 529.—Contains large transformer (not normal supply), 8 valve holders, 3 block condensers, 3 1/2 mfd. 500 v. condensers, 8 other tubular condensers, 14 resistors, potentiometer, chokes, etc. Complete in grey metal case, size 12in. x 8 1/2in. Brand New. ONLY 49/- (carriage, etc., 3/6).

100 MICROAMPS METER.—2in. Flush Mounting. Widely calibrated scale of 15 divisions marked "Yards," which can be re-written to suit requirements. These movements are almost unobtainable today, and being BRAND NEW IN MAKER'S CARTONS, are a "snip" at ONLY 39/6.

50 MICROAMPS METER.—2in. Flush mounting. Another movement which is in short supply and is also BRAND NEW IN MAKER'S CARTON. ONLY 45/-.


VCR97 (C.R. TUBES).—All guaranteed tested full screen for Television use. In maker's crates. ONLY 45/- (carriage paid), 6in. MAIN HEATING LENS FOR VCR97 TUBE.—First grade oil filled. ONLY 25/- (postage 2/-).

TRANSFORMERS.—Manufactured to our specification, and fully guaranteed. Normal Primaries: 425 v., 0-425 v., 200 ma., 6.3 v. 6 a., 6.3 v. 3 a., 0-2-4-6.3 v. ONLY 72/6. 425 v. 0-425 v., 200 ma., 6.3 v. 4 a., 6.3 v. 4 a., 5 v. 3 a. ONLY 50/- 350 v. 0-350 v. 160 ma., 6.3 v. 6 a., 6.3 v. 3 a., 5 v. 3 a. ONLY 42/6 250 v. 0-250 v., 100 ma., 6.3 v. 6 a., 5 v. 3 a. ONLY 32/6. The above are fully shrouded, upright mounting. Universal Mounting 350 v. 0-350 v., 80 ma., 0-4-6.3 v. 4 a., 0-4-5 v. 2 a. ONLY 18/6. Top shrouded drop through 350 v. 0-250 v., 70 ma., 6.3 v. 3 a., 5 v. 2 a. ONLY 16/6. The following are in flush mounting: EHT for VCR97 Tube, 2,500 v. 5 ma., 2 v. 0-2 v. 1.1 a., 2 v. 0-2 v. 2a. ONLY 37/6. EHT 5,500 v. 5 ma., 2 v. 1 a., 2 v. 1 a. ONLY 72/6. EHT 7,000 v. 5 ma., 4 v. 1 a. ONLY 92/6.

PLEASE ADD 1/6 PER TRANSFORMER POSTAGE.
TRANSFORMER, for use on trains, models, etc., giving outputs of 3 v., 4 v., 5 v. 6 v., 8 v., 10 v., 12 v., 15 v., 3 v. 3 a., 20 v., 24 v., 30 v., at 2 amps., from normal mains input. ONLY 17/6 (postage 1/-).
TRANSFORMERS.—Ex W.D. and Admiralty, built to more than 50% safety factor, with normal A.C. Mains Primaries. All Brand New and Unused, 300 v. 0-300 v., 200 ma., 5 v. 3 a., 6.3 v. 5a. C.T., 20 v. 750 ma., 70 v. 100 ma. Weight 12lb. ONLY 42/6 (postage, etc., 2/6). 330 v. 0-330 v., 100 ma., 4 v. 3 a. Weight 7 lb. ONLY 22/6 (postage, 1/6). L.T. 5 v. 0-5 v., 5 a., 2 v. 0-2 v., 5 a., 5 v. 0-5 v., 5 a. By using combination of windings will give various voltages at high current. Weight 11lb. ONLY 35/- (postage, etc., 2/6). L.T. 6.3 v. 7.7 a., 4.2 v. 2.5 a., 4 v. 1 a. ONLY 19/6 (postage, 1/6). EHT 1,400 v. 2 ma., 520 v. 10 ma., 300 v. 10 ma., 2 v. 1.5 a. ONLY 21/- (postage, 1/6). Cash with order, please, and print name and address clearly. Amounts given for carriage refer to inland only.

U.E.I. CORPORATION

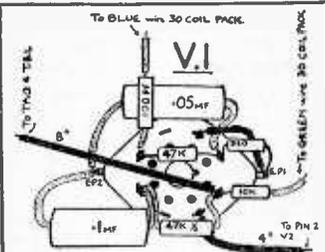The Radio Corner,
 138 Gray's Inn Rd., LONDON, W.C.1
 Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn Station (Chancery Stn.) and 5 mins. by bus from King's Cross.



This is a small reproduction of a simple sub-assembly from one of our series of unique LIFE-SIZE, "Easy-as-A-B-C" Construction Blueprints. If YOU could wire this unit then you are proficient to make any of the GUARANTEED CIRCUITS given in our "HOME CONSTRUCTOR'S HANDBOOK," knowing that failure is impossible! The latest issue of our famous book is AGAIN ENLARGED to contain a host of FULL-PAGE circuits, with descriptions, illustrations, full parts lists, and much useful information, hints, formulae, etc.

- 3 Valve, 3 wave FEEDER.
 - 4 Valve, 3 wave FEEDER (with hi-fi switching).
 - 5 Valve, 3 wave A.C. SUPERHET.
 - 5 Valve, 3 wave A.C./D.C. SUPER.
 - Feeder amplifier and Power Pack.
 - 6 Valve, 3 wave A.C. SUPERHET.
 - 6 Valve, 3 wave A.C./D.C. SUPER.
 - SIGNAL TRACER.
 - 4 Valve BATTERY SUPERHET.
 - 5 Watt AMPLIFIER.
 - 10 Watt High Quality AMPLIFIER.
 - SIGNAL GENERATOR.
- Ask for the nominal price of 2/6!
 SEND NOW for YOUR copy, obtainable by MAIL ONLY from

RODING LABORATORIES
 694, Le3 Bridge Road, London, E.10.
 (Mail office W. J.)

"YOU CAN RELY ON US"

FOR CLEAN COMPONENTS AT COMPETITIVE PRICES

I.F. TRANSFORMERS.—RS/GB, 485 kc/s, 12/8 pair; midret Wearite M800, 21/- pair; super midret, RSRS, 485 kc/s, 21/- pair.

VOLUME CONTROLS.—Standard, less switch, 2/9; with switch 4/3; Midret types, 3/6 and 5/- with switch; Wirewound types, Colvern preset, 3/6; standard, 5/6 All standard valve stocked.

VALVE HOLDERS.—Int. octal, 6d.; Mazda octal, 6d.; British 5 and 7 pin, 6d.; loctal, 1/3; B7G, 1/-; EF50 (ceramic), 1/-; UX American, 6d.; B12A (duo-decal), 2/6; Noval (8BA), 1/-; 8BA, 1/3.

FIAMENT TRANSFORMERS.—200-240 v. tapped to 6.3 If amp. midret, 8/6; multi-secondary, 5 v. to 30 v. at 2 a., tapped primary, 24/-.

COILS.—Wearite "P" coils, 3/- each, full range; Weymouth "H" coils, 3/6, "K" coils, 4/9; CT2W2, 10/6 pair; C83W3, 12/3 pair; MWLW TRF pair with reaction, 7/8; Viewmaster coils for London, 22/-; Birmingham, 28/-; Holme Moss, 28/-; Electronic Holme Moss coils, 19/6; 1.5 Viewmaster choke coil, 2/-.

RECTIFIERS.—WX8, 3/7; WX3, 3/7; WJ38, 1/-; 14A8, 18/6; 38 EHT 100, 27/10; 5 ma 12 v. 1/-; 12 v. 1 a., 7/6.

HIGH VOLTAGE CONDENSERS.—New T.C.C. 001 6 kV., 4.8 μf, 12 v., 7/6; .1 mfd. 5kV., 12/6; .01 mfd. 6 kV., 7/6; .01 mfd. 5 kV., surplus, 3/6.

HIGH IMPEDANCE HEADPHONES.—New American surplus, unused, 12/6 pair.
CERAMIC TRIMMERS.—50 pf., 9d.; 100 pf., 1/-; 150 pf., 1/-; 250 pf., 1/7; 500 pf., 2/-; 750 pf., 2/3; 1,000 pf., 2/6.

SPEAKER TRANSFORMERS.—Standard Pentode, 4/6; Midret Pentode, 4/-; Triode type, 4/6; Super Midret for IS4, 5/4 valves, 5/-; push-pull new transformers, PAX1 for two PX4 in p.pul., 10 watts, 33/-; 15 watt, push-pull, 6L6, primary 5,000 secondary 15, 7.5, 7.5 or 2.5, 42/-; Multi-ratio OP transformers, MR7, 14, 18, 19, 22, 25, 1, also 26, 30, 33, 44; 66, 100 v. 1/4, centre-tapped, 7-10 watts, 18/9; Wharfedale, Type "P", 30, 45, 60, 90 to 1, 8/6; Elstone multi-ratio, 8/6.

MAINS TRANSFORMERS.—SR350 80 ma 200/230/250 v. to 350/0/350 v. 6.3 v. 4 a. tapped at 4 v., 5 v. at 2 amps tapped at 4 v. 28/6. SR250 80 ma/a. SR350, 200/250 v. 250 v. 28/6 60 ma. Trans., 250/0/250 6.3 v. 3 a., 5 v. 2 a., small dimensions, 22/6.

SWITCHES.—4 pole 2 way, 4/-; 3 pole 1 way, 4/-; 2 pole, 6 way, 4/-; 1 pole 12 way, 4/-; 6 pole 3 way, 4/3; 4 pole 4 way, 3/6.

MISCELLANEOUS.—Octal valve cans, 1/6; Viewmaster envelope, 5/-; London, Birmingham, Holme Moss (state when) easy built television, 2/8; E.P.H. Germanium crystals, 5/6; Qmax cutters, 11in., 14/6; 1in., 11/3; 1 1/2in., 15/6; 1in., 11/3; all sizes stocked; Solon soldering iron, pencil bit, 22/6; oval bit, 21/-; State voltage.

VALVES.—EL32, 8/-; 6K7, 8/-; 12K6, 10/6; 6H6M, 4/6; KT61, 10/6; KT68, 12/6.

TUBULAR CONDENSERS.—.001, .002, .005, .01, .02, .05, 1, 6d.

MICA.—.0001, .0002, .0003, .0005, .001, .002, .005, 6d.

4V RECTIFIER NEW—EQUIVALENT TO R3, 1W4/350, etc., 10/-.

RADIO SERVICING CO.

444, WANDSWORTH ROAD, CLAPHAM, LONDON, S.W.8

Telephone: MACaulay 4155.
 77, 77A, 19F Buses; S.R. Station, Wandsworth Road.

SAMSON'S SURPLUS STORES

M.C.R.I. POWER PACKS. Input 100-240 v. A.C./D.C. Output 90 v. 7 1/2 v. 37/6. Post 1/6.

PAINTON ATTENUATORS. 5,000 ohms in 75 ohm steps. 10/6. Post 1/6.
MASTER VOLTMETERS. 0-20 v. A.C. Moving Iron 6in. mirrored scale by Metro-Vickers. 22/6. Carriage 1/6. VCR97 Basis. 2/6. Postage 6d.

30ft. LENGTHS OF CO-AXIAL CABLE with Pye sockets on each end. 8/6. Post 1/6.

ALKALINE CELLS by Britannia Battery Co. 2.5 v. 10 AH, 12/6, post 1/-; 2.5 v. 21 AH, 15/-, post 1/6.

FIL. TRANSFORMERS. Prim. 200-240 v., Sec. 6.3 v. 15 amps., 19/6, post 1/6; Prim. 200-240 v., Sec. 6.3 v. 2 amps., 12/6, post 1/-; Prim. 200-240 v., Sec. 12 v.-24 v. 1 amp., 13/6, post 1/-; Prim. 200-240 v., Sec. 9 v.-15 v. 1 amp, 13/6, post 1/-.

DESYNN TRIMMERS, type No. 167, 12 volt. 10/6. Post 9d.

STC 20,000 ohm 10 watt pots. 3 1/2 inch diam. 10/6. Post 1/-.

169/171, Edgware Road, London, W.2. Tel. PAD. 7851
 125, Tottenham Court Road, W.1 Tel. EUS. 4982

All orders and enquiries to our Edgware Road branch, please. Open all day Saturday at the Edgware Road branch.

—THE MODERN BOOK CO.—

- The Radio Amateur's Handbook, 1952. By the A.R.R.L. Price 30s. 0d., postage 1s. 0d.
- P. H. Brans' Vade-Mecum, 1952. Price 25s. 0d., postage 9d.
- Feedback, by N. H. Crowhurst. Audio Handbook No. 2. Price 3s. 6d., postage 3d.
- Television Principles and Practice, by F. J. Camm. Price 25s. 0d., postage 9d.
- Magnetic Recording, by S. J. Begun. Price 25s. 0d., postage 3d.
- Everyman's Wireless Book, by F. J. Camm. Price 12s. 6d., postage 6d.
- Practical Wireless Encyclopaedia, by F. J. Camm. Price 21s. 0d., postage 9d.
- Handbook of Line Communication, by The Royal Signals. Volume One. Price 20s. 0d., postage 1s. 0d.
- Television Engineering, by D. G. Fink. Price 72s. 6d., postage free.
- Practical Wireless Service Manual, by F. J. Camm. Price 8s. 6d., postage 6d.
- Principles of Radio, by K. Henney and G. Richardson. Price 44s. 0d., postage 1s. 0d.
- Brimar Radio Valve and Telephone Manual, No. 4. Price 5s. 0d., postage 6d.
- Amplifiers, by N. H. Crowhurst. Audio Handbook No. 1. Price 3s. 6d., postage 3d.
- Radio Amateur Call Book. Winter, 1951. Price 21s. 0d., postage 9d.
- Radio Valve Data, compiled by the 'Wireless World.' Price 3s. 6d., postage 3d.
- We have the finest selection of British and American radio books in the country. Complete list on application.
- 10-23, FRAED STREET, (Dept. P6), LONDON, W.2. PADDINGTON 4185.

Amateur Radio Enthusiasts
THE INCOMPARABLE

GLOBE-KING

SINGLE VALVE S.W. RECEIVER
WORLD WIDE RANGE 11-100 METRES — CRYSTAL-CLEAR NOISE-FREE RECEPTION — ELECTRIC BAND - SPREAD TUNING — EXTREMELY LOW RUNNING COSTS.
Catalogue Free. Stamp for postage.

JOHNSONS (RADIO)
46, FRIAR STREET, WORCESTER

TRANSFORMERS

- No. 1. 250-0-250v. 80 ma. 0-4v. 5a. 6.3v. 3.5a. 0-4.5v. 2a. 17/-
- No. 2. As No. 1 but 350-0-350v. 17/-
- No. 3. 28v. 2.5a. tapped to give almost any voltage up to 25v. Ideal for chargers, models, W.D. motors, etc., 16/6.
- No. 4. 4v.-9v.-20v. 4 amp. For 2, 6 and 12 volt chargers, 16/6.
- No. 5. Auto wound, 10-110-200-230-250v. 150 watts. For general voltage changing, up or down, 16/6.
- No. 6. 250-0-250v. 100 ma. 6.3v. 3.5a., 5v. 2a. 22/-
- No. 7. Television Auto with overwind, 0-200-230-250-280v. 500 ma. 6.3v. 7a. 0-2-6.3v. 2a., 38/6.



All types upright or drop through. No others available. Primaries on 1, 2, 4 and 6 tapped 200-230-250v. Intertwined, Impregnated, Screened, Guaranteed.

Terms: C.W.O., C.O.D., or pro forma. Postage 1/6 1 to 3.

HILLFIELDS RADIO,
8, BURNHAM ROAD,
WHITLEY, COVENTRY



Save Money!

by using components and apparatus of

PROVED RELIABILITY

Second-hand and ex-Government material may appear beguilingly cheap—but ultimately you will realise it pays best to buy new and guaranteed stock. Everything sold by Webb's is backed by our

Guarantee of Satisfaction

A SELECTION OF ITEMS FROM WEBB'S UNRIVALLED STOCK OF APPARATUS FOR "QUALITY" REPRODUCTION

"STENTORIAN" S812.
An Bin. L.S. Unit at reasonable price recommended by Webb's for use as treble reproducer in a dual speaker system. (Available 15 or 3 ohms) £1 17 0

VITAVOX "K12/20."
The famous heavy duty 12in. L.S. unit for bass reproduction, listed at £14.00 — Webb's have some in stock at the old price of £11 0 0

GARRARD "A.C.6."
A precision-made 78 r.p.m. gram motor. Call and see how to make it give 33 r.p.m. £6 15 10



14, SOHO ST., OXFORD ST., LONDON, W.1.

Telephone: GERrard 2089
Hours: 9—5.30, Sats. 9—1.

G.E.C. & B.T.H. GERMANIUM CRYSTAL DIODES

G.E.C. GLASS TYPE 5/16in. x 3/16in. B.T.H. LATEST TYPE MOULDED IN THERMO-SETTING PLASTIC Both Wire Ends for Easy Fixing. 4/6 each, postage 2 1/2d.

SILICON CRYSTAL VALVE
3/6 each, postage 2 1/2d. Fixing Brackets 3d. extra. Wiring instructions for a cheap, simple but high quality Crystal Set included with each Diode and Crystal Valve

COPPER INSTRUMENT WIRE ENAMELLED, TINNED, LITZ, COTTON, AND SILK COVERED.

Most gauges available. B.A. SCREWS, NUTS, WASHERS, soldering tags, eyelets and rivets. EBONITE AND BAKELITE PANELS. TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES, ERIE & DUBILIER RESISTORS. Latest Radio Publications. SEND STAMP FOR LISTS.

CRYSTAL SET
INCORPORATING THE SILICON

CRYSTAL VALVE
Adjustable Iron Cored Coil.

RECEPTION GUARANTEED
Polished wood cabinet, 15/-, post 9d. A REAL CRYSTAL SET, NOT A TOY

POST RADIO SUPPLIES
33 Bourne Gardens, London, E.4

COILS

Dual wave H.F. with reaction for Summer All-dry Portable (June, '51), 4/3. Pr. TRF. for AD3 band 3. Aug., 6/6. Pr. TRF. Midget for A.C. mains Midget, Oct./Nov., 6/6. Pr. TRF., less reaction, 5/6. Medium wave layer wound Crystal Set Coil, 1/6. L and M.W. Crystal set Coil, pile wound, 3/-. Complete set of Coils and Chokes for Viewmaster, from 17/6. High "Q" Miniature IFTS, 465kc. 13/6 pair. Miniature Coil Packs, L.M.S. size 1 1/2in. x 2 1/2in. x 2 1/2in., complete with circuit, 27/6. Trade terms available. Mail order only. — T. G. HOWELL, 29, McWilliam Road, Brighton, 7.

14

TESTED CIRCUITS

of Superhets, T.R.F. Sets, Feeder Units, Amplifiers, Power Pack, Signal Tracer, etc., which

YOU CAN MAKE

are contained in our

NEW

CONSTRUCTORS HANDBOOK
PRICE 2/6 ONLY

Other notable inclusions in this Handbook are the DETAILED DIAGRAMS and INSTRUCTIONS for building our **POPULAR SUPERHET COIL PACK** and, of course, pages of Servicing and Constructional Information, Formulae, etc. Full Illustrated Catalogue of our extensive stock sent with each Handbook.

Get Your Copy TODAY

obtainable only from

SUPACOILS

98, GREENWAY AVENUE, LONDON, E.17.

News from the Trade

T.C.C. Revised Retail Prices

IGNITION CONDENSERS.—All types listed at 4s. each now increased to 5s. each. All types listed at 5s. each now increased to 6s. 6d. each.

"Caradio" Interference Suppressors.—The following types have all been increased to price indicated. S. 6485, 7s.; S. 6536, 8s.; S. 4481, 6s.; S. 4494, 6s.; S. 6585, 7s.; S. 6586, 7s.; S. 6775, 6s.; S. 6537, 6s.

"Hikonal" Energy Storage Condensers.—The following new list prices will apply to all of the following standard types: HK. 15, £5; HK. 28, £8 15s.; HK. 33, £10; HK. 34, £22; HK. 50, £15 10s.—Telegraph Condenser Co., Ltd., North Acton, W.3.

Two New Ekco Export Sets

E. K. COLE, LTD., announce the introduction of two new radio receivers for the export market — the A172 and the A173. The former is an extremely high quality 5-valve superhet all-wave table model designed for use in European and Near East countries. It is housed in an attractive and substantial horizontal cabinet, in walnut veneer, with a tuning scale carrying approximately sixty station names on medium waves alone. A slightly sloping front presents the scale and controls at a natural angle.

The A173 is a high grade 6-valve superhet incorporating an electronic tuning indicator and covering five wave ranges with band spreading on 11-13-16, 19-22-25, 27-31-38 metres. Suitable for use in medium tropical countries, it is contained in a handsome walnut veneer cabinet of entirely new design. Negative feedback in the output stage, and a high grade speaker ensure excellent quality reproduction.

Both receivers operate on 100-135 volts and 200-250 volts A.C.—E. K. Cole, Ltd., Southend-on-Sea.

Ingenious New Sequence Valve

A SPECIAL pneumatic valve for controlling the sequence of operations involved in retracting and, subsequently, lowering an aircraft's undercarriage has recently been designed by the Aircraft Division of The Hymatic Engineering Company.


When the pilot of an aircraft fitted with this automatic sequence valve operates the "undercarriage down" control, the valve sets in motion the following series of events: first, the undercarriage doors open; then, just as this ram stroke is completed, it opens a lock, releasing the leg and allowing the undercarriage ram to lower the wheel. This movement completed, the valve clicks over mechanically, the doors shut around the leg and at the same time the valve is positioned for the next undercarriage sequence.

On the selection of "undercarriage up," the valve controls the reverse procedure. The doors open, the wheels retract, and the doors shut.

The basic principles of the valve, which has an

operating pressure of 750 p.s.i., are simple and fool-proof. Contained in its lightweight magnesium alloy casing are four on-off valves which, when operated by the internal switching mechanism, feed shuttle valves controlling the air flow to the door actuating rams. The movement of the switching mechanism is effected by the undercarriage leg through a slotted link to a lever mounted on the central serrated spindle.

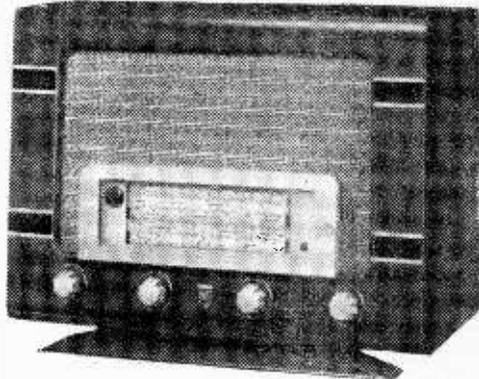Measuring approximately 6½ in. H x 5 in. L x 2 in. W, the complete unit weighs only 1.14 lb.—The Hymatic Engineering Co., Ltd., Redditch, Worcs.



Ekco Model A173—Export only.

World's First Five Core Solder

A CLOSELY guarded secret, disclosed at the opening of the R.E.C.M.F. Exhibition on April 7th, was the development by Multicore Solders, Ltd., of the world's first five core solder.

This new type of Ersin Multicore Solder has five separate cores of flux with each core situated very close to the circumference of the wire. Extremely rapid melting of the solder and quick liberation of the flux is achieved by the flux area being concentrated in the outer 10-per cent. area of the cross section of the wire.

Advance samples of the new five core Ersin Multicore Solder were shown at the exhibition, including wire in 22 s.w.g. which was little thicker than a hair. When magnified the five separate cores could be clearly seen.

Production of bulk supplies of Multicore five core solder will commence later in the year when new plant is installed at Multicore Works at Hemel Hempstead. Initial supplies incorporating Ersin Flux will be allocated to export and defence contracts. Substantial orders for the new five core Ersin Multicore Solder have already been received from U.S.A.—Multicore Solders, Ltd., Multicore Works, Maylands Avenue, Hemel Hempstead, Herts.

Editorial and Advertisement Offices: "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4363. Telexgrams: Newnes, Baud, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

BOOKS

R.S.G.B. Amateur Radio Call Book, 6,000 British Isles Callsigns, 56 pp., 3/9; **Transmitting Licence**, 32 pp., 1/-; **Service Valve Equivalents**, 32 pp., 1/3; **Simple Transmitting Equipment**, 52 pp., 2/3; **Receivers**, 96 pp., 3/9; **Valve Technique**, 104 pp., 4/9; **V.H.F. Technique**, 96 pp., 3/9; **Television Interference**, 40 pp., 2/3; **R.S.G.B. Bulletin**, current issue, 1/6. Five recent issues 2/6. Prices include postage. **RADIO SOCIETY OF GREAT BRITAIN**, 28, Little Russell St., London, W.C.1.

I.P.R.E. TECHNICAL PUBLICATIONS: 5,500 Alignment Peaks for Super-heterodynes, 5/9, post free. Data for constructing TV Aerial Strength Meter. 7/6. Sample copy The Practical Radio Engineer, quarterly publication of the Institute, 1/- membership and examination data 1/- Secretary, I.P.R.E., 20, Fairfield Rd., London, N.8.

BRITISH SHORT WAVE LEAGUE is devoted to the interests of amateur radio enthusiasts. Publishes 12-page "BSWL Review," monthly (members only). Offers many services and activity departments. World wide membership. Founded 1935. Apply for details to: **BRITISH SHORT WAVE LEAGUE**, 55, Victoria St., London, S.W.1. (Abbey 2384).

ALL MAGAZINES.—We can arrange subscriptions to any British or foreign wireless and TV magazine. Send today for our free booklet giving details and prices. **WILEN LTD.** (Dept. 40), 101, Fleet St., London, E.C.4.

RECEIVERS & COMPONENTS

TELEVECTION RADIO, Bridwell Rd., St. Budeaux, Plymouth, offer Valves, 6V6, etc., Electrolytics (good makes), Components, etc., brand new; surplus to requirements; £1 and £2 parcels; amazing value; hurry; send now!

EDDYSTONE 640 Receiver, with 8in. Speaker; sound condition, £20. R. MANNING, 34, Chandos Rd., E. Finchley, N.2.

HOME CONSTRUCTORS, short wave Radio, Television; send for free list; Components, Valves, Kits, Speakers, etc. **THE RADIO EQUIPMENT COMPANY** (P.W. Dept.), Castor Rd., Brixham, Devon.

RELIABLE MAIL Order Service.—V/Controls, 3/-; miniature, 3/9; with switch, 5/-; miniature, 5/3. Transformers, 350v, 21/-. Condensers (branded makes only), 8 and 16 mfd at 500v, 4/- and 6/6; 10pf to 0.5, 11d. each, all values. Television: Viewmaster instructions, 5/-, and all components supplied. **C.T.S. ELECTRONICS**, 44, Lower Church St., Croydun.

SAVE ££££££££. Assemble your own receiver. The total cost of all components, including all valves and bakelite cabinet for a 2 WB (M and L) are £5/5/- for T.R.F., and £6 for Superhet. Our new book of instructions gives full working diagrams, point to point wiring of both receivers and order forms for components, 1/6. Thousands of bargains available. Our latest list 3d. stamps. **SUSSEX ELECTRONICS, LTD.**, Princes Works, Brighton.

MIDGET Components: V/trls., 500K SP/sw, 4/-; DP/sw, 5/3; 465 I.P.Ts, 18/6; O/trns., 5/3; Valves, 1T4, 1S5, 1R5, 1I/- ea.; 1S4, 9/-; set of 4, 39/6; BTG Hiders, 9d.; 0005 Twin-3, 9/6; Midget Droppers, 2 and 3 1/6; HF Chokes, 5/3; Midget W/change, 1P/12W, 2P/6W, 3P/4W, 4P/3W, 4/9 ea. Lists available. **STRANGE**, 52, Pendlestone Rd., London, E.17.

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines, Box No. 6d. extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

RADIO SUPPLY CO., 15, Wellington Street, Leeds.—Brand new Electrolytics, Tubular, 350v, 8 mfd, 1/9; 16 mfd, 2/6; 450v, 8 mfd, 2/3; Can, 350v, 8-8 mfd, 3/9; 12-12 mfd, 3/3; 24 mfd, with Clip, 2/11; 16-32 mfd, 5/3; 32 mfd, 4/3; 32-32 mfd, 6/6; 32-32 mfd, 6/6; 32-32 mfd, plus 25 mfd, 25v, with Clip, 7/6; 50 mfd, plus 250 mfd, 12v, 4/11; Can, 450v, 8-8 mfd, 4/6; 8-16 mfd, 4/6; 16 mfd, 2/11; 16-16 mfd, 5/3; 32 mfd, 5/3; 40 mfd, with Clip, 5/3; 32-32 mfd, 6/11; Can 500v, 8-8 mfd, 4/9; 8-16 mfd, 5/3; 12-6 mfd, 3/11; 16-16 mfd, 5/9; Can 6v, 1500 mfd, 3/9. R.S.C. Charger Transformers (Primaries 200-250v), 0-8-15v 1.5a, 14/9; 0-8-15v 3a, 16/9; 0-8-15v 6a, 22/9; Fil. Trans. (Primaries 200-250v), 6.3v 2a, 7/6; 0-4-6.3v, 2a, 7/9; 12v, 1a, 7/11; 6.3v 6a, 17/6. Brand new P.M. Speakers, all 2-3 ohms, 5in. P.W., 11/9; 5in. Goodmans, 13/9; 5in. Rola with Trans., 15/9; 6in. P.W., 13/11; 6in. Goodmans, 16/9; 5in. Plessey, 14/11; 8in. Rola, 17/6; 10in. Goodmans, 27/9. Chassis, undrilled, 16 s.w.g., Aluminium Receiver type, 10-54-2in., 3/9; 11-16-2in., 4/3; 12-8-2in., 5/3; 16-8-2in., 8/11; Amplifier type, 12-8-2in., 7/11; 16-8-2in., 10/11; 20-8-2in. 13/6. Ex-Gov. Items. T.C.C. Block Paper, 4 mfd, 600v, 2/9; Smoothing Chokes, tropicalised, 50 m.a., 50 h., 1000 ohms, 4/6; 90 m.a., 8 h., 100 ohms, 4/6. L.T. type, 4/6; c.w.o. or c.o.d. over £1; post 1/- under £1. 1/6 under £3. All goods guaranteed. Full list 4d.

FOR SALE, Walkie-Talkies, type 58 MK I, new condition at £15 each; TR5043 all valves (SCR522) at £15 each; Head Phones, DLR 2 brand new at 8/6 pr.; Buzzer Keys, No. 8, 5/8; Guarantee Valves, 203, 20/-; 805, 30/-; 807, 15/-; 813, 85/-; 866A, 16/6; VTAC (21spec.), 25/-; CV6 (E148), 2/6; 954, 2/6; 955, 3/6; 9004, 4/6; 3V4, 6/6; ATP4, 4/6; DK40, 6/6; 6K7G, 7/6; EB34, 3/6; 6B8G, 8/6. R. GILFILLAN & CO., 52, South St., Worthing, Sussex. (Tel.: Worthing 8719).

TUNING CONDS., 15pf, 50pf, 100pf, 150pf, 300pf, 1/6; 500pf, 3/-; Twin, 4/6; 4 gang, 3/-; Solid, 3/6; 465Kcs, I.P.S., 6/6 pr. List 2d. **CARTER'S**, 578, Washwood Heath Rd., Birmingham, 8.

REPAIRS AND REWINDS

LOUDSPEAKERS repaired promptly. **MODEL LOUDSPEAKER SERVICE**, 34a, Bullington Road, Oxford.

A SCOTTISH Winding Service.—All types of Transformers, Chokes, Field Coils, etc. Rewound and manufactured to highest standards. Write for details: **WILFLO PRODUCTS**, 230-254, Brand St., Glasgow, S.W.1. (Telephone: Ibrox 0140.)

RADIO AND T/V Constructors. For Components, Technical Advice, Receiver Alignment, Rewinds, etc., contact **GLYNDON RADIO SERVICE**, 63, Glyndon Rd., S.E.18. (WOO 2749.) S.A.E. for list.

VACUUM CLEANERS and Gram. Motors, repairs our speciality. Armature rewinds, new bearings and commutators fitted, also transformers rewound, speakers repaired. Competitive prices. Trade enquiries invited, 14 days c.o.d. service. Send s.a.e. for price lists to: **A.D.S. CO.** (V.E.M. Dept.), 261-3, Lichfield Rd., Aston, Birmingham, 6. Est. 1935.

ALUMINIUM cylindrical screw-cap Containers; ideal for storing small nuts, bolts, condensers, resistances, etc., hundreds other uses, 1 3/16in. diam. x 2 1/2in., 1/9 doz.; 1 7/16in. diam. x 2 1/2in., 2/3 doz., plus 6d. postage and packing (any quantity). **W. F. J.**, 225, Wennington Rd., Southport.

EX SERVICES, controls remote type 10 rack mounted panel Amplifier and Power Pack (less valves), suitable, slight modification, gramophone or public address amplifier; mains operated, 200/250 volts, AC; 2 PX 25's in push pull, price £4. Write for leaflet. **THE RADIO EQUIPMENT COMPANY** (Dept. P.W.), Castor Rd., Brixham, Devon.

LR PHONES, Mike Trans., Tone Trans., 1/6; 5 x 20, 1/-; Resistor Panels, Coils, Vholders, .001, 4d. Post extra. S.A.E. lists. **ANNAKIN**, 25, Ashfield Place, Otley, Yorks.

VALVES

VALVES wanted, types 1R5, 1S5, 1T4, 1S4, 6K7, 6Q7, 6V6, 5Z4, 6K8, 805, 807, 811, 813 and 832; highest prices paid instantly. Box 211, c/o **PRACTICAL WIRELESS**.

UNIQUE OFFER of new 1.4 volt bat. Valves, ideal for that T.R.F. job. Set of 3 for 12/6, comprising 1 each of 1L5, 1LD5, 3D6, post free. R. **ARMES**, 15, Lebanon Gardens, Wardsworth, S.W.18.

WANTED, Valves, small or large quantities, 6K8, 6V6, 5Z4, 6AC7, 1R5, 1S5, FW4/500, 6Q7, 12K8, 80, VU39, EBC33, 3S4, etc., etc. Prompt cash. **WM. CARVIS**, 103, North Street, Leeds, 7.

"VIEWMASTER" Valves, as specified, all guaranteed brand new and boxed, comprising 5 EF50, 1 KT61, 1 6P25, 1 EBC33, 1 EB91, 2 6K25, 1 6P25, set of 12, £6/12/6. PL38, EY51, 18/6; ECH21, 13/6; KT61, ECL80, EC91, 12/6; DAC32, 50L6GT, 5Z4G, UP41, UBC41, 10/6; EP91, 6F12, 6AM6, AZ31, UX41, 10/-; 6V6GT, 9/6; EB91, 6AL5, 9/-. Miniature all-dry battery types, 1S5 (DAF91), 1R5 (DK91), 1T4 (DF91), 3V4 (DL94), 8/9 each; EP39, EF50, EP8, KT2, 7/6; HVR2A, 6K7G, 2D4A, 6/6; 9D2, 4/6. All valves guaranteed brand new and boxed. P.M. Speakers, Elac and Celestion, 2in. and 3in., Plessey 5in. and Truvox 6in., 12/6; Plessey 8in., 13/6. C.W.O. Post paid 40/-. **READERS RADIO**, 24, Colberg Place, Stamford Hill, London, N.16.

ARP12, 5/6; AR8, 5X4, 5Y4, VR150/30, VR105/30, 8/-; ARP12, soiled, 2/9; all post free. R. G. **FANCOURT**, Kibburn, Derby.

BARGAINS.—Valves, 1S4, 1T4, 210VPT, 210DPT, 5Z4M, IC5, CT8, at 9/-; 6SN7, 6F6C, 6L6GT, EC90, FM24D, 6AC7, at 10/-; Phocell 931A, p.h. network, 25/-; EA50, 7193, EB34, 1P6, VR21, at 2/6; 6C4, 6J5G, 12SK7, EF39, EF36, 6SH7, 9001, ARP2, ATP4, 955, 954, 956B, 6AC7, 9D2, RK34, KTW63, KTW61, at 5/6; EF50, EF54, EC52, CV66, 12SR7, AC6Pen, 717A, 721A, 6K7G, SP47, VS110A, at 6/-; 2X2, VR65(A), 9004, 9006, DV3, VR135, VU120A, VU111, 6H6, CV63, V70, at 4/-; Resistors, 4w 4d., 4w 5d., 1w 6d., 2w 9d., above 1/- Everything for the radio constructor in stock. Bargain stock list 1d. and s.a.e. Postage extra. C.W.O. Immediate delivery. **W. A. BENSON**, 308, Rathbone Road, Liverpool, 13.

VALVES UNLIMITED.—Brand spanking new Valves, 5Z4, 6C6, 6D6, 12A7, 6S7, 81, each; VR150/30, 6SA7, GJ5, 12A6, KTW61, 12SK7, 6SGA, 5/6 each; c.w.o. prices include postage; post orders only, 13, George St., Portsmouth, Hants.

HANNEY OF BATH offers the following brand new goods from stock:—Collaro Three-speed Autochangers, complete with 2 Hi-Fi crystal heads, type 3RC521 for 7-, 10- and 12-inch records, mixed, £18/14/1; type 3RC522, specification as 3RC521, but allows 10- and 12-inch records to be mixed, £21/4/4. Goodmans Axiom 50 Speakers, £10/5/6; Audiom 60, £8/12/6; Rola G12 Speakers, £8/5/-. W. B. Stentorian Speakers, all 3 ohm speech coil, 2 1/2in. 18/6, 3 1/2in. 19/6, 5in. 21/-. 6in. 24/6. 8in. 32/6, 9in. 36/9, 10in. 44/6. Special—50-watt potted output Transformers, with tapping plugs, allowing the desired ratio to be selected immediately without soldering; suitable for PX4. 6V6, 6L6 and KT66 valves, either in push-pull or single-ended, 47/3. Viewmaster Television: coils now available for all channels including Wenvoe, 30/-. Morganite Resistors, 35/3; type Q Pots, 5/- each; 6 Colvern Pots, 22/6; 5 Westinghouse Rectifiers, £3/9/-; Bulgin, 13/6; T.C.C. Condensers, 147/1; Bellini-Lee L707, 8/9; G.E.C. type G neon, 3/6; W.B. Chassis, 18/6 each type; WB103, 42/-; WB103A, 52/6; WB104, 15/6; WB105, 32/6; WB106, 25/6; WB107, 32/6; WB108, 33/6; WB109, 22/6; WB110, 10/-; WB111, 5/9; WB112-9in., 21/-; WB112-12in., 21/6. Complete set of parts for any channel, £31. Kit of 12 Valves exactly to specification, £2/10/4. All makes of G.P.T. in stock, 9in. and 12in. Send 6d. stamp for our complete list; c.w.o. or c.o.d. All goods post free over £2, but 2/- is added to c.o.d. orders under £5. L. F. HANNEY, 77, Lower Bristol Rd., Bath. (Telephone: 3811.)

A £1 in the hand—Send me that list of Valves you have for disposal and I will by return post offer you the best price for them. No lot too small or too large. NORMAN H. FIELD, 68, Hurst St., Birmingham, 5.

FREE LIGHT with the "Lite" Wind-charger; Plans 2/9, Propellers 35/-; H. JAMIESON & CO. (Dept. P.W.), Midtaphouse Works, Liskeard, Cornwall.

GENUINE BARGAINS! Decca Gram. Motors for A.C. mains with turntable, adjustable, 33 1/3 or 78, £4; ditto giving 33 1/3, 45 and 78, instantly switchable, £6/10/-. Lightweight Pick-up to match, fitted Acos GP crystal cartridges, price with std. or L.F. head, £2/14/6, with both heads, £4/6/-. Record Player Cases, rexine covered, house above or similar units, cut motor board, measures 14 1/2in. x 12 1/2in. x 5in. internally, price 50/-. Collaro Autochangers, latest models, take plug-in pick-up heads; single speed with magnetic head, £12/1/-; with GP27 crystal, £13/4/-; 8-speed model with dual-purpose GP27, £15/15/6, or with 2 sep. GP27, £19. Garrard 78 r.p.m. centre-drive, var. spd. induction type gram. motors, 12in. turntable, £6/7/6. Bass Reflex Cabinet Kits, stand 30in. high, give superb bass and top, all 1/2in. thick patent acoustic timber, fully cut, full instructions, etc.; 8in. speaker model, £5/7-10in. 9/7/6, 12in. 10/7/6, carr. 7/6; ready built, 7/6 extra. N.R.S. Symphony Amplifiers provide independent control of bass, middle and top, also scratch cut, 5-watt model for 2/3 ohms £10/4/6, 15 ohms £10/12/6; 10-watt push-pull triodes model, £13/7/6 and 15 ohms, tapped output, £16; distortion and hum entirely negligible in either model; 12-watt P.A. Amplifier, gram. and mike inputs, £12/4/6; all above for A.C. only. 8-watt push-pull AC/DC P.A. Amplifier, £16; Collaro AC/DC gram. units to match, £14. All above prices include carriage. Full bargain catalogue, two 21d. stamps. **NORTHERN RADIO SERVICES**, 16, Kings College Rd., London, N.W.3.

SOUTHERN RADIO'S wireless bargains. Walkie-talkie (transmitter-receiver), type 38 Mark II, complete with 5 valves, throat microphone, headphones and aerial, 7mc/s amateur band, suitable for field use; powerful superhet receiver; modulated transmitter; guaranteed ready for the air, less batteries, £4/12/6. R.3515 Television Units, complete with 21 valves, 6 stage 14 mc/s I.F. strip, ideal for T.V. conversion; brand new, in original wooden cases, £3/10/-; carriage 7/6. G.E.C. "Miniscope" M861B Miniature Cathode-ray Oscilloscopes, 1 1/2in. tube, time base etc., etc.; brand new, in maker's sealed cartons with leatherette carrying case, £15/10/-, plus 5/- carriage. Lufbra Hole Cutters, adjustable from 1/2in. to 3 1/2in., for use on wood, metal, plastic, etc., 5/9. Lufbra Fly Cutters, 14/6. Throat Microphones, magnetic type, complete with long lead and plug, 4/6. 2-pole A.C. Motors, 110 volts to 240 volts 50 cycles, 2,740 r.p.m., suitable for magnetic tape recording; size 1/2in. x 2 1/2in. x 3in., 30/-, Westcoaters, type WX6 and W112, 1/- each, 1 1/2-dia. Marconi Aerial Filter Units, type "916" in conformity with P.O. specification; full instructions for fixing; 4/- Contactor Time Switches, 10-hour movement, 2 impulses per second, thermostatic control in soundproof cases, 11/6. Visual Indicator Unit, Type 3 (10Q/4), contains two moving coil movements, two neons, etc., easily convertible to very efficient A.C. meters, 11/-. Conversion fully described in "W.W." Sept. 1951. **SOUTHERN RADIO SUPPLY, LTD.**, 11 Little Newport St., London, W.C.2. (GERARD 6653.)

WANTED, copies of P.W. December, 1948, February and April, 1949; offers to Box No. 220, c/o PRACTICAL WIRELESS.

SYNCHRONOUS MOTORS, 200-250V. A.C., 50 cycles, clock type, 12/6 each, 1/- postage; suitable for model engineers. **UNIVERSAL ELECTRICAL**, 21 1/2, City Rd., London, E.C.1.

TAPE RECORDINGS, ETC.

MIDDLESBROUGH Viewmaster TV. constructional details, 5/-, plus 4d. post. Tape Recorders, Valves, etc. Send for lists. **PALMERS OF MIDDLESBROUGH, LTD.**, 114, Waterloo Rd., and 106, Newport Rd.

EMITAPE—Secure your Recording Tape from "His Master's Voice" Showrooms, 363, Oxford St., W.1. (Mayfair 1240.)

TAPE RECORDING.—Revolutionary design of our Line-A-Tone Tape Recording Panels; no threading of tape, fast rewinding, fast forward, halts on all bearings, 3 speeds by lever control, heavy duty 4-pole winding motor, complete freedom from wow and flutter; in fact this panel embodies all the requirements of the professional recordist. The price still remains at £20 ex works. Production on this, the latest in Tape Recording, has just commenced. We advise you to place your order at once. Temporary leaflets are available, giving details. Trade enquiries invited. **MORECAMBE SOUND SERVICE**, "Sealand Works," Cross Cop, Morecambe.

—YOU READ MUSIC?—

Then how about making yourself an electronic organ. Constructional data available—full circuits, drawings and notes. It has 5 octaves, 2 manuals and pedals with 24 stops—uses 4 valves. With its variable attack you can play Glissandos and Swings. Write **NOW** for free booklet and further details to **C. & S.**, 10a, Duke Street, Darlington, Durham.

EX-W.D. unused Fluorescent Lighting Sets for 12 and 24 volts D.C. input, 230V. A.C. output; Rotary Converter, Choke, P.F. Condenser, Leak Transformer for 85 watt Sodium Lamps; the whole enclosed in metal box; £5 to clear. **A. J. PHILPOTT**, Fountain Sq., Penton, Stoke-on-Trent.

WALNUT Radiogram Cabinets, Stamp details. **E. WISKER**, 501, Hale End Rd., Highams Park, E.4.

CABINETS for Viewmaster, Radiograms, L.S., etc.; special jobs. All enquiries to **ASHDOWN**, 98, Hertford Road, N.9. (TOT. 2621.)

WALNUT Radiogram Cabinets of distinction; stamp details. **R. SHAW**, 69, Fairlop Rd., E.11.

CRYSTAL SET COILS, dual range, with circuit, 2/6, post 3d. Trade supplied. **RADIO EXPERIMENTAL PRODUCTS, LTD.**, 33, Much Park St., Coventry.

EVERYTHING for radio constructors. Condensers, Coils, Valves, Resistors, etc. Send stamp for list. **SMITH**, 98, West End Road, Morecambe. Quick service.

SITUATIONS VACANT

The engagement of persons answering these advertisements must be made through a Local Office of the Ministry of Labour or a Scheduled Employment Agency if the applicant is a man aged 18-64, inclusive, or a woman aged 18-59, inclusive, unless he or she, or the employment, is exempted from the provisions of the Notification of Vacancies Order, 1952.

APPOINTMENTS IN CIVIL AVIATION. Radio mechanics are required at Ministry of Civil Aviation aerodromes and radio stations in various parts of the United Kingdom. If you have had practical experience in the maintenance of radio or radar equipment, apply to any Employment Exchange, quoting Order No.: Kings Cross, 576.

A. J. WHITTEMORE (AERADIO) LIMITED. Croydon Airport, require Radio Engineer with practical knowledge of R.A.F. or Fleet Air Arm Radio or Radar equipment. Application should be made to a Ministry of Labour and National Service local office or scheduled employment agency.

EDUCATIONAL

A.M.I.MECH.E., A.M.Brit.I.R.E., City and Guilds, etc., on "no pass, no fee" terms; over 95% success. For details of exams and courses in all branches of engineering, building, etc., write for 144-page handbook—free. **B.I.E.T.** (Dept. 242B), 17, Stratford Place, London, W.1.

SEE THE WORLD.—Radio Officers urgently required. We train most in shortest period. Training fees payable after appointments secured. Scholarships available. Boarders accepted. Prospectus free from Britain's leading college. **WIRELESS COLLEGE**, Colwyn Bay.

MERCHANT NAVY and Air Radio.—Here is an opportunity to train as Radio Officer. The big liners are open to you, but you must qualify for the P.M.G. Certificate. Day, Evening and "Radiocerts" postal courses. Estd. 30 years; s.a.e. for prospectus from Director, **THE WIRELESS SCHOOL**, 21, Manor Gardens, London, N.7. (Tel.: ARC. 3694.)

THE INSTITUTE of Practical Radio Engineers have available Home Study Courses, covering elementary, theoretical, mathematical, practical and laboratory tuition in radio and television engineering; the text is suitable coaching matter for I.P.R.E., Technical entry and progressive exams. Tuitionary fees at pre-war rates are moderate. The Syllabus of Instructional Text may be obtained, post free, from the **SECRETARY**, Fairfield Road, Crouch End, N.8.

Practical Wireless BLUEPRINT SERVICE

PRACTICAL WIRELESS

No. of
Blueprint

CRYSTAL SETS

- Blueprints, 1s. each.
1937 Crystal Receiver .. PW71*
The "Junior" Crystal
Set PW94*

STRAIGHT SETS

Battery Operated

- One-Valve : Blueprints, 2s. each.
The "Pyramid" One-
valver (HF Pen) .. PW93*

Two-valve : Blueprints, 2s.
The Signet Two. (D &
LF) PW76*

Three-valve : Blueprints, 2s. each.
Summit Three (HF Pen,
D, Pen) PW37*
The "Rapide" Straight
3 (D, 2 LF (RC &
Trans)) PW82*
F. J. Camm's "Sprite"
Three (HF, Pen, D,
Tet) PW87*

Four-valve : Blueprints, 2s. each.
Fury Four Super (SG,
SG, D, Pen) PW34C*

Mains Operated

- Two-valve : Blueprints, 2s. each.
Selectone A.C. Radio-
gram Two (D, Pow) PW19*

Three-valve : Blueprints, 2s. each.
Double - Diode - Triode
Three (HF Pen, DDT,
Pen) PW23*

Four-valve : Blueprints, 2s. each.
A.C. Fury Four (SG, SG,
D, Pen) PW20*
A.C. Hall-Mark (HF
Pen, D, Push-Pull) .. PW45*

SUPERHETS

- Battery. Sets : Blueprints, 2s. each.
F. J. Camm's 2-valve
Superhet PW52*

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

- One-valve : Blueprint, 2s.
Simple S.W. One-valver PW88*
Two-valve : Blueprints, 2s. each.
Midget Short-wave Two
(D, Pen) PW38A*
Three-valve : Blueprints, 2s. each.
Experimenter's Short-
wave Three (SG, D,
Pow) PW30A*
The Perfect 3 (D, 2 LF
(RC and Trans)) .. PW63*
The Band-spread S.W.
Three (HF Pen, D
(Pen), Pen) PW68*

PORTABLES

- Four-valve : Blueprint, 2s.
"Imp" Portable 4 (D,
LF, LF, Pen) .. PW86*
The "Mini-Four" All-
dry (4 valve superhet) PW

MISCELLANEOUS

- Blueprint, 2s.
S.W. Converter-Adapter
(1 valve) PW48A*
Blueprint, 3s. 6d.
The P.W. 3-speed Auto-
gram.

TELEVISION

- The Practical Television Receiver,
(3 sheets) 10/6
The "Argus" (6in. C.R. Tube) 2/6

AMATEUR WIRELESS AND WIRELESS MAGAZINE

STRAIGHT SETS

Battery Operated

- One-valve : Blueprint, 2s.
B.B.C. Special One-
valver AW387*
Two-valve : Blueprints, 2s. each.
A modern Two-valver.. WM409*

Mains Operated

- Two-valve : Blueprints, 2s. each.
Consoelectric Two (D,
Pen), A.C. AW403

SPECIAL NOTICE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk beside the blueprint number denotes that constructional details are available, free with the blueprint.
The index letters which precede the Blueprint Number indicate the periodical in which the description appears: Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.
Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

- One-valve : Blueprints, 2s. each.
S.W. One-valver for
America AW429*
Two-valve : Blueprints, 2s. each.
Ultra-short Battery Two
(SG, det Pen) .. WM402*
Four-valve : Blueprints, 3s. each.
A.W. Short-Wave World-
beater (HF Pen, D, RC,
Trans) AW436*
Standard Four - valver
Short-waver (SG, D,
LF, P).. .. WM383*

Mains Operated

- Four-valve : Blueprints, 3s.
Standard Four-valve A.C.
Short-waver (SG, D,
RC, Trans) WM391*

MISCELLANEOUS

- Enthusiast's Power Am-
plifier (10 Watts) (3/-) WM387*
Listener's 5-watt A.C.
Amplifier (3/-) .. WM392*
Harris Electrogram
battery amplifier (2/-) WM399*
De Luxe Concert A.C.
Electrogram (2/-) .. WM403*

HINTS COUPON

This coupon is available until June 2nd, 1952, and must accompany all Practical Hints.

PRACTICAL WIRELESS, June 1952.

ALPHA OFFERS

1 WATT RESISTORS at 6d. each.

100 kΩ, 47 kΩ, 50 kΩ, 150Ω, 33 kΩ, 22 kΩ, 6 kΩ, 230Ω, 39 kΩ, 560 kΩ, 47 kΩ, 690 kΩ, 1 megΩ, 330 kΩ, 40 kΩ, 10 kΩ, 1 kΩ, 56 kΩ, 330 kΩ, 330Ω, 5 kΩ, 80 kΩ, 8 kΩ.

MOULDED MICA CONDENSERS

.01, .001, .002, .003, .005, .0001, .0002, .0003, .0005, .00020, .00050, All 5/6 doz.

BAKELITE CASE CONDENSERS

25 mfd. 600 v., .02 mfd. 3 kv., .001 mfd. 4 kv., .01 mfd. 4 kv. All 1/2 each.

PANEL MOUNTING PRESS SWITCH

2-hole fixing type, 1/3 each.

WIRE-WOUND VOLUME CONTROLS

5Ω, 200Ω, 1 kΩ, 5 kΩ, 15 kΩ, 20 kΩ, 25 kΩ, 35 kΩ, 50 kΩ, 2/9 each.

SPEAKERS

3" Elac, 3Ω, 13/8; 5" Goodman, 3Ω, 11/8; 5" Plessey, 3Ω, 12/8; 8" Plessey, 3Ω, 14/8; 12" Truvox, 57/8; 10" Goodman, 32/8; 10" Rola, 32/8; 8" Goodman, 16/8.

STANDARD CAN CONDENSERS

15 mfd. 500 v., 8/9; 8 mfd. 450 v., 1/11; 24 mfd. 450 v., 4/8; 8 x 8 mfd. 450 v., 4/8; 16 x 8 mfd. 450 v., 4/8; .32 x .32 mfd. 450 v., 7/8.

EX EQUIPMENT VOLUME CONTROLS

All in good condition carbon type, 200 kΩ, 10 kΩ, 1 megΩ, 50 kΩ, 5 kΩ, 500Ω, 20 kΩ, 25 kΩ. 1/2 each.

VIEW MASTER ENVELOPES

For Holme Moss or Kirk o' Shotts, 5/- each.

VALVES

All Guaranteed.

Majority in Maker's Cartons.

0Z4	8/-	6L6G	11/8	DD13	8/9	VR137	5/9
1T4	9/-	6N7GT	7/8	ECL90	12/8	EL32	7/9
1A5	9/-	6QT9	11/8	EB341	11/8	VU111	4/8
184	9/-	6SA7GT	9/8	EL41	11/8	VU120A	4/-
185	9/-	68G7	7/8	E1143	2/-	UT41	10/8
1C5GT	8/8	68H17	7/-	FW3/500	9/8	UCH42	12/8
2A3	7/9	68J7	9/8	GE25	4/6	UL41	11/8
2158G	4/-	68K7	7/-	H63	9/8	Y63	9/-
2X3	6/8	68N7GT	11/8	KWV61	8/9	W21	9/-
3A4	9/-	68Q7	9/8	KT66	11/8	E1438	3/9
3D6	8/8	6U7G	9/-	KT263	7/8	7475	3/9
354	10/8	6V6GT	9/8	KT330	11/8	KT91	10/-
42	9/8	6V60	9/8	KT741	6/9	7Y4	9/-
5U40	9/-	6X5GT	9/-	KT90	11/-	7B7	9/-
5Y3G	9/6	6AM6	11/8	ML4	8/9	7C5	9/-
5Y8GT	9/6	6AL5	9/-	ML6	4/-	7C6	9/-
5Z4M	9/6	77	7/9	MH41	7/9	X18	10/-
5Z4G	10/8	783	9/8	4D1	4/9	VM4B	12/6
6A3GT	7/9	78	9/-	6P1	4/9	EL50	9/8
6B8	7/9	80	9/6	YP41	9/-	6U5	9/8
6C5GT	7/8	954	2/9	DH73M	9/8	APV4	9/6
6C6	7/8	955	5/-	PM2A	7/8	SP2	9/-
6D6	7/8	306	3/8	PM302	7/8	EA30	7/8
6E3M	9/-	9D3	4/9	EF33	7/6	with holder	3/-
6F60	9/-	12A6	7/8	EB34	3/-	Holder	3/-
6G6G	7/8	19H6	7/8	EF36	7/8	KT92	9/6
6H6	4/8	12K3	9/8	EK32	7/8	807	11/6
6J5GT	5/8	12817	7/8	SP61	4/-	UB41	9/-
6J7M	8/8	TP26	8/8	SP41	4/-	EB41	9/-
6J7J	7/9	VP23	8/8	EF39	6/8	CV135	9/-
6PEN25	8/6	128K7	8/-	EP50 SYL-	8/8	DHTT	9/-
HL23DD	8/6	1622	11/6	VANIA	8/6	W77	9/-
6K7G	5/8	AC6/PEN	7/9	V872	4/-	U78	9/-
6L5GT	6/8	CV6	2/-	DDL4	4/8	IU5	11/-
6K8G	12/6	CV9	4/-	EP8	7/8	6BE6	12/6

1 WATT RESISTORS AT 31d. each.

10 kΩ, 15 kΩ, 350 Ω, 1.8 megΩ, 270 Ω, 100 kΩ, 680 kΩ, 1,500Ω, 4.7 kΩ, 47 Ω, 470 Ω, 470 kΩ, 47 kΩ, 300Ω, 43 kΩ, 35 kΩ, 80 kΩ, 20 kΩ, 8 kΩ, 50 kΩ, 150 kΩ, 20 Ω, 330 kΩ, 1 kΩ, 5 kΩ, 1 megΩ, 56 Ω, 56 kΩ, 680 Ω.

ENAMELLED COPPER WIRE

14 s.w.g., 1/9 per lb.
16 s.w.g., 1/9 " "
36 s.w.g., 2/9 " "
40 s.w.g., 3/- " "

MAINS TRANSFORMERS

Hdf shrouded drop through type. Prim. 200/250v. Sec. 250-0-250v., 80 mA, 6.3v. 2a., 5v. 2a.
As above. Sec. 350-0-350v. 80 mA, 4v. 4a., 5v. 2a., all at 18/8 each.

STANDARD THREE-WAY MOUNTING

Prim. 200/250v. Sec. 350-0-350v. 80 mA, 0-4v., 3a. 6.3v. 4a., 0-4-5v. 2a., 10/- each. Chassis mounting type waxed dipole, all leads to a tag board on top. Prim. 200/250v. Sec. 350-0-350v. 80 mA. Two 6.3v. 4a. winding ov. 3a. 25.6 each.

Postage on all mains transformers, 1/8 each.

OUTPUT TRANSFORMERS

GOODMANS STANDARD 4/9 each. A.W.F. Power/Foutdo 3/11 each.

ROLA MIDGET 4/6. PERSONAL SET TYPE 4/8 each.

WAXED TUBULAR CONDENSERS

WIRE ENDS 3 mfd. 500v., .003 mfd. 1,000 v., .01 mfd. 3 kv., .1 mfd. 500v. all 4/4, each, 4/- doz.

SPECIAL OFFERS

T.C.C. Micropack 8 mfd. 250v., 1/8 each. Morganite 1 meg. v/c with S.P.S., 3/- each. Erie 1 meg. v/c D.P.S., 4/3 each. Both with lin. spindles.

TERMS: Cash with order or C.O.D. Full list available. Send 3d. in stamps. Postage: 6d. under 10/-, 1/- under 20/-, 1/6 under 40/-.

ALPHA RADIO SUPPLY CO., 5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS, I.



HOME STUDY

backs radio experience with sound technical knowledge

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an I.C.S. Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to Students who wish to prepare themselves for a job in this field. Courses of Instruction include the following:

Complete Radio Engineering, Radio Service Engineers Radio Service and Sales, Advanced Short-Wave Radio Elementary Electronics, Radar, Radio and Television Technology

And the following Radio Examinations:

British Institution of Radio Engineers
P.M.G. Certificates for Wireless Operators
City and Guilds Telecommunications
C. & G. Radio Servicing Cert. (R.T.E.B.)

Write today for our FREE "Radio" booklet, which fully describes the above I.C.S. Courses. Fees are moderate and include all books required. **GENEROUS DISCOUNT TO H.M. FORCES**

RADIO EXCHANGE CO.

ERICSSON'S HIGH RESISTANCE PHONES, first grade, 4,000 ohms resistance, attractively finished in silver and black; BRAND NEW, in presentation boxes, 17/6 (3d. post).

LOW RESISTANCE PHONES, very sensitive, 5/11 and 7/6.

VIBRATOR PACK 21, delivering approx. 140v. at 40mA, fully smoothed from 6v. input; in NEW condition, 17/6.

ACCUMULATORS, multiplate, 7AH 2v., in celluloid cases, 31in. x 11in. x 4in., 7/6.

MIDGET AMPLIFIERS, 5in. x 3in. x 31in.: with two 12SH7's and one 12SJ7, 12/6.

POWER PACK, with 52A VU120 (5 kv.) EHT rectifier, two transformers, choke, etc. in NEW condition, 16/6. Our 200 250v. 50 cps. conversion data to deliver EHT or 450v. 50 mA., 2/3.

60v. BATTERIES, two for 8/11 (post 1/8).

NEW RECEIVERS, Type P40/S450B, with 4 EF54's (RF mixer, Xtal Osc. multipliers), EB93's (2.9 mc/s IFs), EB34 (det.), 6J5 and 8V6 audio, EC32 Xtal. osc. for 85-96 mc/s. Attractive grey cases measuring 11 1/2in. x 4 1/2in. x 5 1/2in. ONLY 6/9 with circuit, post 2/-.

TRANSMITTER 21. Sending speech, CW or MCW, complete with valves, control panel and key. PA coils (not formers) and relays, stripped by M.O.S.; may easily be replaced with aid of our circuit and instructions. Tune 4.2-7.5 and 18-31 mc/s. In first-class condition, 25/-.

CARRON MICROPHONES. In attractive hemispherical black cases with switch; these have an excellent frequency response. NEW and boxed, 5/- (6d. post).

9 CAULDWELL STREET, BEDFORD

Phone: 5568

International
CORRESPONDENCE SCHOOLS

Dept. 170a, International Bldgs., Kingsway, London, W.C.2.