

RADIO & ELECTRONICS CONSTRUCTOR

DECEMBER 1977

Volume 31 No. 4

Published Monthly (1st of Month)
First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone 01-286 6141 Telegrams
Databux, London

© Data Publications Ltd., 1977. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £6.50 (U.S.A. and Canada \$12.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Web Offset.

| | |
|---|-----|
| CMOS CAPACITANCE EVALUATOR by Bruce Woodland | 204 |
| BRR, BRR ... BRR, BRR ... TELEPHONE BELL SIMULATOR — "A USEFUL STAGE PROP" (Suggested Circuit) by G. A. French | 209 |
| NEWS AND COMMENT | 212 |
| THE EMITTER FOLLOWER (Notes for Newcomers) by F. T. Jones | 214 |
| HI-FI IN THE 1920's by H. Ross McDonald | 216 |
| WATER WARNING UNIT—A Useful Sensing Device (Special Series Blob-a-Job No. 6) by I. R. Sinclair | 218 |
| SHORT WAVE NEWS — For DX Listeners by Frank A. Baldwin | 222 |
| SIMPLE METAL LOCATOR by R. A. Penfold | 224 |
| OP-AMP TRANSISTOR TESTER D. V. Henderson | 232 |
| TRADE NEWS | 235 |
| MODIFIED MAINS CURRENT MONITOR by T. K. Wong | 236 |
| BETTER TV SOUND by J. P. Macaulay | 238 |
| NEW PRODUCTS | 239 |
| IN YOUR WORKSHOP — TV RECEIVER FAULTY CONTRAST CONTROL CIRCUIT | 240 |
| RADIO TOPICS by Recorder | 246 |
| THE STORY OF THE DETECTOR by D. P. Newton | 248 |
| ELECTRONICS DATA No. 28 (For the Beginner — Operational Amplifiers) | iii |

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maide Vale, London W9 1SN

The *Radio & Electronics Constructor* is printed by Swale Press Ltd.

THE JANUARY ISSUE
WILL BE PUBLISHED ON
2nd DECEMBER

THE 'NUTS & BOLTS' OF THOSE PROJECTS!

TRANSFORMERS

MINIATURE MAINS Pri 240V
with two independent secondary windings.

| No. | Type | Price |
|------|------------------------|--------|
| 2024 | MT280 0-6v, 0-6v RMS | £1.30* |
| 2025 | MT150 0-12v, 0-12v RMS | £1.30* |

MINIATURE MAINS Pri 240v

| No. | Secondary | Price |
|------|-----------------|-------|
| 2021 | 6v-0-6v 100mA | 90p* |
| 2022 | 9v-0-9v 100mA | 90p* |
| 2023 | 12v-0-12v 100mA | 90p* |

1 amp MAINS Pri 240v

| No. | Secondary | Price | |
|------|-----------------|--------|---------|
| 2026 | 6v-0-6v 1 amp | £2.70* | p&p 30p |
| 2027 | 9v-0-9v 1 amp | £2.20* | p&p 30p |
| 2028 | 12v-0-12v 1 amp | £2.60* | p&p 30p |
| 2029 | 15v-0-15v 1 amp | £2.75* | p&p 30p |
| 2030 | 30v-0-30v 1 amp | £3.45* | p&p 30p |

STANDARD MAINS Pri 240v

Multi-tapped secondary mains transformers available in 1/2 amp 1 amp and 2 amp current rating. Secondary taps are 0-19-25-33-40-50v.

Volts available by use of taps: 4, 7, 8, 10, 14, 15, 17, 19, 25, 31, 33, 40, 50, 25-0-25 volts.

| No. | Rating | Price | |
|------|---------|--------|---------|
| 2031 | 1/2 amp | £3.42* | p&p 30p |
| 2032 | 1 amp | £4.40* | p&p 50p |
| 2033 | 2 amp | £5.45* | p&p 86p |

AUDIO LEADS

| | | |
|------|---|--------|
| S127 | 5 pin DIN plug to 4 phono plugs length 1.5m | £1.30* |
| S128 | 5 pin DIN plug to 5 pin DIN socket length 1.5m | £1.05* |
| S129 | 5 pin DIN plug to 5 pin DIN plug mirror image length 1.5m | £1.05* |
| S130 | 2 pin DIN plug to 2 pin DIN socket length 5m | 80p* |
| S131 | 5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5 length 1.5m | 83p* |
| S132 | 2 pin DIN plug to 2 pin DIN socket length 10m | 98p* |
| S133 | 5 pin DIN plug to 2 phono plugs connected to pins 3 & 5 length 1.5m | 75p* |
| S134 | 5 pin DIN plug to 2 phono sockets connected to pins 3 & 5 length 23cm | 88p* |
| S135 | 5 pin DIN socket to 2 phono plugs connected to pin 3 & 5 length 23cm | 88p* |
| S136 | Coiled stereo headphones extension cord extends to 7m | £1.75* |
| S124 | 3 pin DIN plug to 3 pin DIN plug length 1.5m | 75p* |
| S125 | 5 pin DIN plug to 5 pin DIN plug length 1.5m | 75p* |
| S113 | 3-5mm Jack to 3-5mm Jack length 1.5m | 75p* |
| S114 | 5 pin DIN plug to 3-5mm Jack connected to pins 3 & 5 length 1.5m | 85p* |
| S115 | 5 pin DIN plug to 3-5 Jack connected to pins 1 & 4 length 1.5m | 85p* |

G.P. SWITCHING TRANS.

TO18 SIM. TO 2N706/8

BSY27/28/95A. All usable devices. No open and shorts. ALSO AVAILABLE IN PNP similar to 2N2906. BCY 70.

20 for 50p, 50 for £1, 100 for £1.80, 500 for £8, 1,000 for £14.

When ordering please state NPN or PNP

SIL G.P. DIODES

300 mW 40 PIV (min) SUB-MIN

FULLY TESTED

Ideal for Organ builders

30 for 50p, 100 for £1.50, 500 for £8, 1,000 for £14

L.E.D.'s

| Type | Size | Order no | Colour | Price |
|--------|-------|----------|--------|-------|
| TIL209 | .125" | 1501 | RED | .12p |
| TIL211 | .125" | 1502 | GREEN | .25p |
| TIL213 | .125" | 1503 | YELLOW | .25p |
| FLV115 | .2" | 1504 | RED | .12p |
| FLV310 | .2" | 1505 | GREEN | .25p |
| FLV410 | .2" | 1506 | YELLOW | .25p |

2nd Grade L.E.D.'s

A pack of standard sizes and colours which fail to perform to their very rigid specification, but which are ideal for experiments.

Order no. 1507 £0.90

L.E.D. CLIPS

| Pack of | Size | Order no. | Price |
|---------|-------|-----------|-------|
| 5 | .125" | 1508/125 | .15p |
| 5 | .2" | 1508/2 | .18p |

NUTS & BOLTS

BA BOLTS — packs of B.A. Threaded cadmium plated screws, slotted cheese head. Supplied in multiples of 100.

| Type | No. | Price | Type | No. | Price |
|--------|-----|-------|--------|-----|-------|
| 1" OBA | 839 | £1.60 | 1" 4BA | 845 | £0.51 |
| 1" OBA | 840 | £0.83 | 1" 4BA | 846 | £0.38 |
| 1" 2BA | 842 | £0.89 | 1" 4BA | 847 | £0.33 |
| 1" 2BA | 843 | £0.54 | 1" 6BA | 848 | £0.50 |
| 1" 2BA | 844 | £0.63 | 1" 6BA | 849 | £0.30 |
| | | | 1" 8BA | 850 | £0.33 |

BA NUTS — Packs of cadmium plated full nuts in multiples of 100.

| Type | No. | Price | Type | No. | Price |
|------|-----|-------|------|-----|-------|
| OBA | 855 | £0.90 | 4BA | 857 | £0.42 |
| 2BA | 856 | £0.60 | 6BA | 858 | £0.38 |

BA WASHERS — flat cadmium plated plain stamped washers supplied in multiples of 100.

| Type | No. | Price | Type | No. | Price |
|------|-----|-------|------|-----|-------|
| OBA | 859 | £0.20 | 4BA | 861 | £0.15 |
| 2BA | 860 | £0.15 | 6BA | 862 | £0.12 |

SOLDER TAGS — hot tinned supplied in multiples of 100.

| Type | No. | Price | Type | No. | Price |
|------|-----|-------|------|-----|-------|
| OBA | 851 | £0.42 | 4BA | 853 | £0.30 |
| 2BA | 852 | £0.36 | 6BA | 854 | £0.30 |

INSTRUMENT CASES. In two sections, black vinyl covered top and sides and bezel.

| No. | Length | Width | Height | Price |
|-----|--------|--------|--------|--------|
| 155 | 8" | 5 1/2" | 2" | £1.62* |
| 156 | 11" | 6 1/2" | 3" | £2.12* |
| 157 | 6" | 4 1/2" | 1 1/2" | £1.30* |
| 158 | 9" | 5 1/2" | 2 1/2" | £1.76* |

ALUMINIUM BOXES. Made from bright ali., folded construction each box complete with half inch deep lid and screws.

| No. | Length | Width | Height | Price |
|-----|--------|--------|--------|--------|
| 159 | 5 1/2" | 2 1/2" | 1 1/2" | £0.82* |
| 160 | 4" | 4" | 1 1/2" | £0.82* |
| 161 | 4" | 2 1/2" | 1 1/2" | £0.82* |
| 162 | 5 1/2" | 4" | 1 1/2" | £0.70* |
| 163 | 4" | 2 1/2" | 2" | £0.64* |
| 164 | 3" | 2" | 1 1/2" | £0.44* |
| 165 | 7" | 5" | 2 1/2" | £1.04* |
| 166 | 3" | 6" | 3" | £1.32* |
| 167 | 6" | 4" | 2" | £0.86* |

BRIDGE RECTIFIERS

SILICON 1 AMP

| Type | Order No. | Price |
|---------|-----------|-------|
| 50vRMS | BR1/50 | £0.28 |
| 100vRMS | BR1/100 | £0.30 |
| 200vRMS | BR1/200 | £0.32 |
| 400vRMS | BR1/400 | £0.38 |

SILICON 2 AMP

| Type | Order No. | Price |
|-------|-----------|-------|
| 50v | BR2/50 | £0.45 |
| 100v | BR2/100 | £0.48 |
| 200v | BR2/200 | £0.52 |
| 400v | BR2/400 | £0.58 |
| 1000v | BR2/1000 | £0.68 |

FUSE HOLDERS & FUSES

| Description | Order No. | Price |
|----------------------------------|-----------|--------|
| 20mm x 5mm chassis mounting | 506 | £0.07* |
| 1 1/2" x 1 1/2" chassis mounting | 507 | £0.10* |
| 1 1/2" car inline type | 508 | £0.20* |
| Panel mounting 20mm | 509 | £0.22 |
| Panel mounting 1 1/2" | 510 | £0.24 |

QUICK BLOW 20mm

| Type | No. | Type | No. | Type | No. |
|-------|-----|------|-----|--------|------|
| 150mA | 611 | 1A | 615 | 3A | 619 |
| 250mA | 612 | 1.5A | 616 | 4A | 620 |
| 500mA | 613 | 2A | 617 | 5A | 621 |
| 800mA | 614 | 2.5A | 618 | ALL 5d | EACH |

ANTI-SURGE 20mm

| Type | No. | Type | No. | Type | No. |
|-------|-----|------|-----|--------|------|
| 100mA | 622 | 1A | 625 | 2.5A | 628 |
| 250mA | 623 | 2A | 626 | 3.15A | 629 |
| 500mA | 624 | 1.6A | 627 | 5A | 630 |
| | | | | ALL 7p | EACH |

QUICK BLOW 1 1/2"

| Type | No. | Type | No. | Type | No. |
|-------|-----|-------|-----|--------|------|
| 250mA | 631 | 500mA | 632 | 800mA | 634 |
| | | | | ALL 7p | EACH |

| Type | No. | Type | No. | Type | No. |
|------|-----|--------|------|------|-----|
| 1A | 635 | 2.5A | 638 | 4A | 641 |
| 1.6A | 636 | 3A | 639 | 5A | 642 |
| 2A | 637 | ALL 6p | EACH | | |

Just a selection from our huge stocks!

SEE OUR 1977 CATALOGUE

126 pages packed with valuable information.

ORDER NOW ONLY 50p plus 15p p&p

SWITCHES

| Description | No. | Price |
|--|------|--------|
| D.P.D.T. miniature slide | 1973 | £0.10* |
| D.P.D.T. standard slide | 1974 | £0.12* |
| Toggle switch S.P.S.T. 1/2 amp 250v AC | 1975 | £0.33* |
| Toggle switch D.P.D.T. 1 amp 250v AC | 1976 | £0.36* |
| Rotary ON-OFF mains switch | 1977 | £0.42* |
| Push switch — Push to make | 1978 | £0.13* |
| Push switch — Push to break | 1979 | £0.18* |

| ROCKER SWITCH | Colour | No. | Price |
|---|----------|------|--------|
| A range of rocker switches SPST — moulded in high insulation. Material available in a choice of colours ideal for small apparatus | RED | 1980 | £0.22* |
| | BLACK | 1981 | £0.22* |
| | WHITE | 1982 | £0.22* |
| | BLUE | 1983 | £0.22* |
| | YELLOW | 1984 | £0.22* |
| | LUMINOUS | 1985 | £0.22* |

| Description | No. | Price |
|--|------|--------|
| Miniature S.P.S.T. toggle 2 amp 250v AC | 1958 | £0.50* |
| Miniature S.P.S.T. toggle 2 amp 250v AC | 1959 | £0.55* |
| Miniature D.P.D.T. toggle 2 amp 250v AC | 1960 | £0.65* |
| Miniature D.P.D.T. toggle centre off — 2 amp 250v AC | 1961 | £0.85* |
| Push button S.P.S.T. 2 amp 250v AC | 1962 | £0.85* |
| Push button S.P.S.T. 2 amp 250v AC | 1963 | £0.68* |
| Push button D.P.D.T. 2 amp 250v AC | 1964 | £0.80* |

MIDGET WAFER SWITCHES

Single-bank wafer type — suitable for switching at 250v AC 100mA or 150v DC in non-reactive loads make-before-break contacts. These switches have a spindle 0.25" dia and 30° indexing.

| Description | Order No. | Price |
|---------------|-----------|--------|
| 1 pole 12 way | 1965 | £0.48* |
| 2 pole 6 way | 1966 | £0.48* |
| 3 pole 4 way | 1967 | £0.48* |
| 4 pole 3 way | 1968 | £0.48* |

MICRO SWITCHES

| Description | Order No. | Price |
|---|-----------|-------|
| Plastic button gives simple on-off action | | |
| Rating 10 amps 250v AC | 1969 | £0.20 |
| Button gives 1 pole change over action | | |
| Rating 10 amp 250v AC | 1970 | £0.25 |

DISPLAYS

| LED Type | Order No. | Price |
|-------------------|-----------|-------|
| BDL707 .3" single | 1510 | £0.80 |
| BDL747 .6" single | 1511 | £1.60 |
| BDL727 .5" double | 1512 | £1.80 |

COLD CATHODE ITT 5087 ST

Side viewing indicator tubes. Displays 0-9 and decimal points. Wide viewing angle — operates from 180v with 16k series anode resistors — character height 16.5mm pin connections supplied.

Order No. 1513 Price £0.60

VOLTAGE REGULATORS

Positive Regulators TO220 case

| | | | |
|--------------|-------|--------------|-------|
| MVR 7805 5v | £1.25 | MVR 7815 15v | £1.25 |
| MVR 7812 12v | £1.25 | MVR 7824 24v | £1.25 |

Negative Regulators TO220 case

| | | | |
|--------------|-------|--------------|-------|
| MVR 7905 5v | £1.85 | MVR 7915 15v | £1.85 |
| MVR 7912 12v | £1.85 | MVR 7924 24v | £1.85 |

ORDERING

Please word your orders exactly as printed, not forgetting to include our part number.

VAT

Add 12 1/2% to prices marked*
Add 8% to others excepting those marked†. These are zero rated.

BI-PAK

Dept. R.C.8, P.O. Box 6, Ware, Herts
COMPONENTS SHOP: 18 BALDOCK STREET, WARE, HERTS

SEMICONDUCTORS — COMPONENTS

BABANI BOOK OFFER

Purchase books to the value of £5.00 from the list below and choose any 50p pak from this page FREE.

| | | |
|------|--|------|
| BP2 | Handbook of Radio, TV & Industrial & Transmitting Tube & Valve Equivalents | 60p |
| BP3 | Handbook of Tested Transistor Circuits | 40p |
| BP6 | Engineers and Machinists Reference Tables | 40p |
| BP7 | Radio & Electronic Colour Codes and Data Chart | 13p |
| BP10 | Modern Crystal and Transistor Set Circuits for Beginners | 35p |
| BP14 | Second Book of Transistor Equivalents | 95p |
| BP15 | Constructors Manual of Electronic Circuits for the Home | 50p |
| BP16 | Handbook of Electronic Circuits for the Amateur Photographer | 60p |
| BP18 | Boys and Beginners Book of Practical Radio and Electronics | 60p |
| BP22 | 79 Electronic Novelty Circuits | 75p |
| BP23 | First Book of Practical Electronic Projects | 75p |
| BP24 | 53 Projects Using IC741 (or equivalents) | 75p |
| BP26 | Radio Antenna Handbook for Long Distance Reception and Transmission | 85p |
| BP27 | Giant Chart of Radio Electronic Semiconductor and Logic Symbols | 60p |
| BP29 | Major Solid State Audio Hi-Fi Construction Projects | 85p |
| BP32 | How to Build Your Own Metal & Treasure Locators | 85p |
| BP34 | Practical Repair & Renovation of Colour TVs | 95p |
| BP35 | Handbook of IC Audio Pre-amplifier & Power Amplifier Construction | 95p |
| BP36 | 50 Circuits Using Germanium, Silicon & Zener Diodes | 75p |
| BP37 | 50 Projects Using Relays, SCRs and TRIACS | 1.10 |
| BP39 | 50 (FET) Field Effect Transistor Projects | 1.25 |
| 129 | Universal Gram-motor Speed Indicator | 8p |
| 160 | Coil Design and Construction Manual | 30p |
| 161 | Radio, TV and Electronics Data Book | 60p |
| 196 | AF-RF Reactance—Frequency Chart for Constructors | 13p |
| 202 | Handbook of Integrated Circuits (ICs) Equivalents and Substitutes | 75p |
| 205 | First Book of Hi-Fi Loudspeaker Enclosures | 60p |
| 213 | Electronic Circuits for Model Railways | 85p |
| 214 | Audio Enthusiasts Handbook | 85p |
| 216 | Electronic Gadgets and Games | 85p |
| 217 | Solid State Power Supply Handbook | 85p |
| 219 | Solid State Novelty Projects | 85p |
| 220 | Build Your Own Solid State Hi-Fi and Audio Accessories | 85p |
| 222 | Solid State Short Wave Receivers for Beginners | 95p |
| 223 | 50 Projects Using IC CA3130 | 95p |
| 224 | 50 CMOS IC Projects | 95p |
| 225 | A Practical Introduction to Digital IC's | 95p |
| 226 | How to Build Advanced Short Wave Receivers | 1.20 |
| RCC | Resistor Colour Code Disc Calculator | 10p |

THYRISTORS

| 800mA TO18 CASE | | | 7 AMP TO48 CASE | | |
|-----------------|------------|-------|-----------------|-----------|-------|
| Volts | No. | Price | Volts | No. | Price |
| 10 | THY600/10 | £0.15 | 50 | THY7A/50 | £0.48 |
| 20 | THY600/20 | £0.16 | 100 | THY7A/100 | £0.51 |
| 30 | THY600/30 | £0.20 | 200 | THY7A/200 | £0.57 |
| 50 | THY600/50 | £0.22 | 400 | THY7A/400 | £0.62 |
| 100 | THY600/100 | £0.25 | 600 | THY7A/600 | £0.78 |
| 200 | THY600/200 | £0.38 | 800 | THY7A/800 | £0.92 |
| 400 | THY600/400 | £0.44 | | | |

| 1 AMP TO5 CASE | | | 10 AMP TO48 CASE | | |
|----------------|-----------|-------|------------------|------------|-------|
| Volts | No. | Price | Volts | No. | Price |
| 50 | THY1A/50 | £0.26 | 50 | THY10A/50 | £0.51 |
| 100 | THY1A/100 | £0.28 | 100 | THY10A/100 | £0.57 |
| 200 | THY1A/200 | £0.32 | 200 | THY10A/200 | £0.62 |
| 400 | THY1A/400 | £0.38 | 400 | THY10A/400 | £0.71 |
| 600 | THY1A/600 | £0.45 | 600 | THY10A/600 | £0.99 |
| 800 | THY1A/800 | £0.58 | 800 | THY10A/800 | £1.22 |

| 3 AMP TO66 CASE | | | 18 AMP TO48 CASE | | |
|-----------------|-----------|-------|------------------|------------|-------|
| Volts | No. | Price | Volts | No. | Price |
| 50 | THY3A/50 | £0.28 | 50 | THY18A/50 | £0.64 |
| 100 | THY3A/100 | £0.30 | 100 | THY18A/100 | £0.68 |
| 200 | THY3A/200 | £0.33 | 200 | THY18A/200 | £0.62 |
| 400 | THY3A/400 | £0.42 | 400 | THY18A/400 | £0.77 |
| 600 | THY3A/600 | £0.50 | 600 | THY18A/600 | £0.90 |
| 800 | THY3A/800 | £0.66 | 800 | THY18A/800 | £1.39 |

| 5 AMP TO66 CASE | | | 30 AMP TO94 CASE | | |
|-----------------|-----------|-------|------------------|------------|-------|
| Volts | No. | Price | Volts | No. | Price |
| 50 | THY5A/50 | £0.38 | 50 | THY30A/50 | £1.18 |
| 100 | THY5A/100 | £0.46 | 100 | THY30A/100 | £1.43 |
| 200 | THY5A/200 | £0.50 | 200 | THY30A/200 | £1.83 |
| 400 | THY5A/400 | £0.57 | 400 | THY30A/400 | £1.79 |
| 600 | THY5A/600 | £0.69 | 600 | THY30A/600 | £3.50 |
| 800 | THY5A/800 | £0.81 | | | |

| 5 AMP TO220 CASE | | |
|------------------|------------|-------|
| Volts | No. | Price |
| 400 | THY5A/400P | £0.67 |
| 600 | THY5A/600P | £0.69 |
| 800 | THY5A/800P | £0.81 |

| No. | Price |
|------------|-------|
| BT101/500R | £0.90 |
| BT102/500R | £0.90 |
| BT106 | £1.25 |
| BT107 | £0.93 |
| BT108 | £0.98 |
| 2N3228 | £0.70 |
| 2N3525 | £0.77 |
| BTX30/50L | £0.33 |
| BTX30/400L | £0.46 |
| CI06/4 | £0.60 |

SUPER UNTESTED PAKS

| Pak No. | Qty. | Description | Order No. | Price |
|---------|------|-------------------------------|-----------|-------|
| U50 | 100 | Germ. gold bonded OA47 diode | 16130 | £0.60 |
| U51 | 150 | Germ. OA70/81 diode | 16131 | £0.60 |
| U52 | 100 | Silicon diodes 200mA OA200 | 16132 | £0.60 |
| U53 | 150 | Diodes 75mA IN4148 | 16133 | £0.60 |
| U54 | 50 | Sil rect top hat 750mA | 16134 | £0.60 |
| U55 | 20 | Sil rect stud type 3 amp | 16135 | £0.60 |
| U56 | 50 | 400mW zeners D07 case | 16136 | £0.60 |
| U57 | 30 | PNP trans BC107/8 plastic | 16137 | £0.60 |
| U58 | 30 | PNP trans BC177/178 plastic | 16138 | £0.60 |
| U59 | 25 | PNP TO39 2N697/2N1711 silicon | 16139 | £0.60 |
| U60 | 25 | PNP TO59 2N2905 silicon | 16140 | £0.60 |
| U61 | 30 | PNP TO18 2N706 silicon | 16141 | £0.60 |
| U62 | 25 | PNP 8FY50/51 | 16142 | £0.60 |
| U63 | 30 | PNP plastic 2N3906 silicon | 16143 | £0.60 |
| U64 | 30 | PNP plastic 2N3905 silicon | 16144 | £0.60 |
| U65 | 30 | Germ. 0071 PNP | 16145 | £0.60 |
| U66 | 15 | Plastic power 2N3055 NPN | 16146 | £1.20 |
| U67 | 10 | TO3 metal 2N3055 NPN | 16147 | £1.20 |
| U68 | 20 | Unijunction trans IS43 | 16148 | £0.60 |
| U69 | 10 | 1 amp SCR TO39 | 16149 | £1.20 |
| U70 | 8 | 3 amp SCR TO66 case | 16150 | £1.20 |

Code Nos. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

COMPONENT PAKS

| Pak No. | Qty. | Description | Order No. | Price |
|---------|------|--|-----------|-------|
| C1 | 200 | Resistor mixed value approx (count by weight) | 16164 | £0.60 |
| C2 | 150 | Capacitors mixed value approx. (count by weight) | 16165 | £0.60 |
| C3 | 50 | Precision resistors. Mixed values | 16166 | £0.60 |
| C4 | 80 | W resistors mixed preferred values | 16167 | £0.60 |
| C5 | 5 | Plates assorted ferrite rods | 16168 | £0.60 |
| C6 | 2 | Tuning gangs. MW/LW VHF | 16169 | £0.60 |
| C7 | 1 | Pak's wire 50 m tars assorted colours single strand | 16170 | £0.60 |
| C8 | 10 | Reed switches | 16171 | £0.60 |
| C9 | 3 | Micro switches | 16172 | £0.60 |
| C10 | 15 | Assorted pots | 16173 | £0.60 |
| C11 | 5 | Metal jack sockets 3 x 3.5mm 2 x standard switch types | 16174 | £0.60 |
| C12 | 30 | Paper condensers preferred types mixed values | 16175 | £0.60 |
| C13 | 20 | Electrolytics trans. types | 16176 | £0.60 |
| 14 | 1 | Pak assorted hardware - nuts/bolts, gromets, etc. | 16177 | £0.60 |
| C15 | 5 | Mains slide switches assorted | 16178 | £0.60 |
| C16 | 20 | Assorted tag strips and panels | 16179 | £0.60 |
| C17 | 15 | Assorted control knobs | 16180 | £0.60 |
| C18 | 4 | Rotary wave change switches | 16181 | £0.60 |
| 19 | 2 | Relays 6-24V operating | 16182 | £0.60 |
| C20 | 1 | Pak. copper laminate approx 200 sq. in. | 16183 | £0.60 |
| C21 | 15 | Assorted fuses 100mA-5 amp | 16184 | £0.60 |
| C22 | 50 | Melres PVC sleeving assorted size | 16185 | £0.60 |

SLIDER PAKS

| Pak No. | Qty. | Description | Order No. | Price |
|---------|------|-------------------------------------|-----------|-------|
| S1 | 6 | Slider potentiometers, mixed values | 16190 | £0.60 |
| S2 | 6 | Slider potentiometers, all 470 ohms | 16191 | £0.60 |
| S3 | 6 | Slider potentiometers, all 10k lin | 16192 | £0.60 |
| S4 | 6 | Slider potentiometers, all 22k lin | 16193 | £0.60 |
| S5 | 6 | Slider potentiometers, all 47k lin | 16194 | £0.60 |
| S6 | 6 | Slider potentiometers, all 47k log | 16195 | £0.60 |

CERAMIC PAKS

Containing a range of first quality miniature ceramic capacitors. Unrepeatable value.

| Pak No. | Qty. | Description | Order No. | Price |
|---------|------|---|-----------|-------|
| MC1 | 24 | miniature ceramic capacitors, 3 of each value 22pF, 27pF, 33pF, 39pF, 47pF, 68pF and 82pF | 16160 | £0.60 |
| MC2 | 24 | miniature ceramic capacitors, 3 of each value 100pF, 120pF, 150pF, 180pF, 220pF, 270pF, 330pF and 390pF | 16161 | £0.60 |
| MC3 | 24 | miniature ceramic capacitors, 3 of each value — 470pF, 560pF, 680pF, 820pF, 1,000pF, 1,500pF, 2,200pF and 3,300pF | 16162 | £0.60 |
| MCA | 21 | miniature ceramic capacitors, 3 of each value — 4.700pF, 6.800pF, 0.015µF, 0.022µF, 0.033µF, 0.047µF | 16163 | £0.60 |

LINEAR PAKS

Manufacturer's "Fall Outs" which include Functional and part-Functional Units. These are classed as "out of spec" from the maker's very rigid specifications, but are ideal for learning about ICs and experimental work. U72-30 Assorted Linear Types. 709, 741, 747, 748, 710, 588, etc.

ORDER No. 16227 **£1.60**
U76SD FM STEREO DECODER
 5 ICs 78110 equivalent to MC1310P-MA767. Data supplied with pak.
 ORDER No. 16229 **£1.60**
U76A AUDIO POWER OUTPUT AMPLIFIERS
 8 assorted types. SL403, 76013, 76003, etc. Data supplied with pak.
 ORDER No. 16228 **£1.00**

74 SERIES PAKS

Manufacturer's "Fall Outs" which include Functional and part-Functional Units. These are classed as "out of spec" from the maker's very rigid specifications, but are ideal for learning about ICs and experimental work. 74G-100 Gates assorted 7400-01-04-10-50-60, etc.

ORDER No. 16224 **£1.20**
74F-30 Flip-Flops assorted 7470-72-73-74-76-104-109, etc.
 ORDER No. 16225 **£1.20**
74M-30 MSI Assorted Types. 7441-47-90-154, etc.
 ORDER No. 16226 **£1.20**

VEROBOARDS PAKS

V81—Approx. 30sq.in. various sizes. All 0.1in matrix.
 ORDER No. 16199 **80p**
 V82—Approx. 30sq.in. various sizes. 0.15in matrix.
 ORDER No. 16200 **80p**

ELECTROLYTIC PAKS

A range of paks each containing 18 first quality, mixed value miniature electrolytics.

EC1—Values from 0.47µF to 10µF.
 ORDER No. 16201 **80p**
 EC2—Values from 10µF to 100µF.
 ORDER No. 16202 **80p**
 EC3—Values from 100µF to 680µF.
 ORDER No. 16203 **80p**

C280 CAPACITOR PAK

75 Multigrad C280 capacitors, mixed values ranging from 0.01µF to 2.2µF complete with identification sheet.
 ORDER No. 16204 **£1.20**

CARBON RESISTOR PAKS

These paks contain a range of Carbon Resistors, assorted into the following groups:

R1-60 mixed 1W 100-820 ohms.
 ORDER No. 16213 **80p**
 R2-60 mixed 1W 1-8.2k
 ORDER No. 16214 **80p**
 R3-60 mixed 1W 10-82k
 ORDER No. 16215 **80p**
 R4-60 mixed 1W 100-820Ω
 ORDER No. 16216 **80p**
 R5-40 mixed 1W 100-820
 ORDER No. 16217 **80p**
 R6-40 mixed 1W 1-8.2k
 ORDER No. 16218 **80p**
 R7-40 mixed 1W 10-82k
 ORDER No. 16219 **80p**
 R8-40 mixed 1W 100-820k
 ORDER No. 16220 **80p**
 R9-60 mixed 1W 1-10M
 ORDER No. 16230 **80p**
 R10-40 mixed 1W 1-10M
 ORDER No. 16231 **80p**

WORLD SCOOP JUMBO SEMICONDUCTOR PAK

Transistors, Germ and Silicon Rectifiers, Diodes, Triacs, Thyristors, ICs and Zeners.

ALL NEW AND CODED
 Approx. 100 pieces. Offering the amateur a fantastic bargain PAK and an enormous saving - identification and data sheet in every pak.
 ORDER No. 16222 **£2.25**

ORDERING

Please word your orders exactly as printed, not forgetting to include our part number.

VAT
 Add 12½% to prices marked*
 Add 8% to others excepting those marked†. These are zero rated.

POSTAGE
 Postage and packing add 25p unless otherwise shown. Add extra for air-mail. Minimum order £1.

Just a selection from our huge stocks!

SEE OUR 1977 CATALOGUE

126 pages packed with valuable information

ORDER NOW
ONLY 50p
 plus 15p p&p

BI-PAK


Dept. C.11. P.O., Box 6, Ware, Herts.

SHOP 18 BALDOCK STREET, WARE, HERTS
 AT: OPEN 9 to 5.30 Mon./Sat.


BLOB-BOARD OFFER

Save 25% on your Blob-a-Job Boards


Buy 3 and get 1 FREE

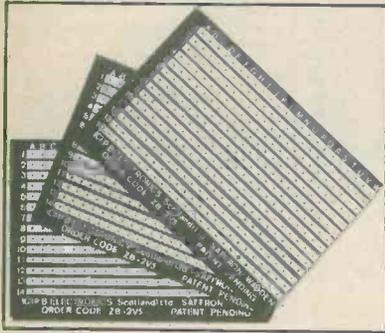

No 1
Used for Blob-a-Job projects
Voltage Stabilizer + Signal Injector
& others
2V5 Size 2.5 x 3.75
Pack of 3 2V5 + FREE 21C Blob
Board
ONLY £0.82p

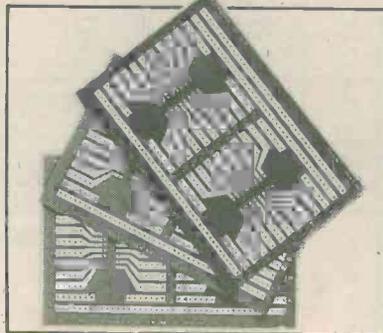

No 2
Blob-a-Job projects
12 Note Generator
Seconds Flasher & others
21C Size 4.8 x 3.2
Pack of 3 21C + FREE 2V5 Blob
Board
ONLY £1.21

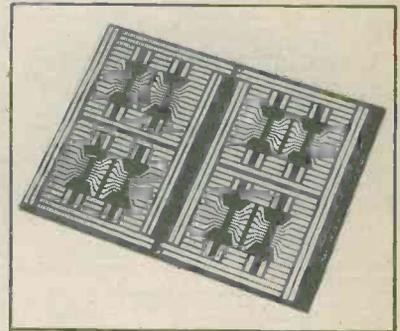


No 3
The Blob Board used for 'Digital
Electronics by Experiment' now
running in Electronics Today
International.
8IC Size 9x7
Pack of 3 8IC + FREE 8D Blob
Board
ONLY £4.99




No 4
FREE S-DeC
with 1Q Blob Board

Blob Board £2.25

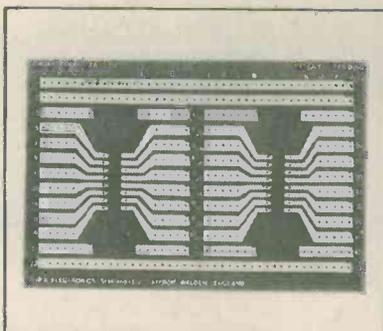


No 5
Special offer
Pack of 3 2V + FREE 21C Blob
Board
ONLY £0.75.

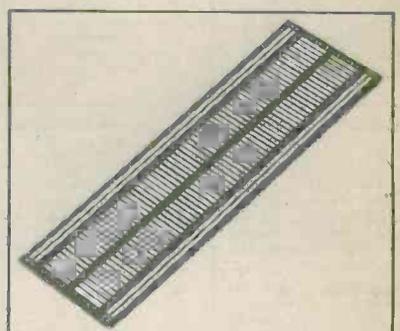

No 6
New Blob-in-Board
matches stripboard layouts
Size 5x2
Introductory offer
Pack of 3 1S
ONLY £0.50

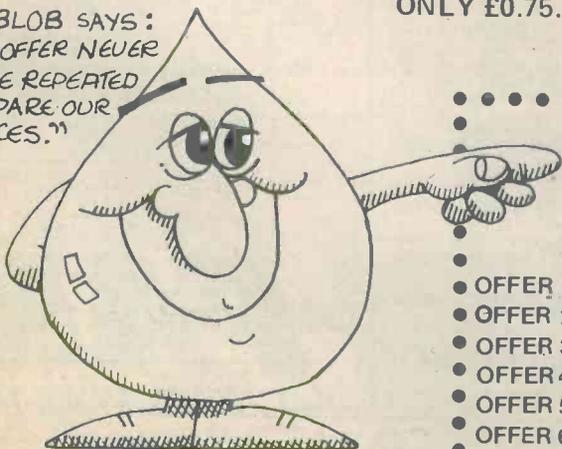MR. BLOB SAYS:
"THIS OFFER NEVER
TO BE REPEATED
COMPARE OUR
PRICES."



ORDER FROM MR BLOB NOW
and get free Mr. Blob Sticker Limited Offer

To: Mr. Blob
PB P.B. Electronics, 57 High Street,
Saffron Walden, Essex.

Please rush me.

- OFFER 1 ... packs of 3 2V5 + FREE 21C for only £0.82
- OFFER 2 ... packs of 3 21C + FREE 2V5 for only £1.21
- OFFER 3 ... packs of 3 8IC + FREE 8D for only £4.99
- OFFER 4 ... packs of 1Q + FREE S DeC for only £2.55
- OFFER 5 ... packs of 3 2V + FREE 21C for only £0.75
- OFFER 6 ... packs of 3 1S for only £0.50

all Blob sizes approx. inch.
all prices inclusive of VAT (8%) and post

SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 Silicon transistors plus 2 power out-pull transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30kHz ± 3 db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £15.00. P. & P. £1.20.

DE LUXE STEREO AMPLIFIER

A.C. Mains 200-240 v. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line-up: 2 x ECC83 Triode Pentodes, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" x 4". Overall height including valves 5". Ready built and tested to a high standard. £12.40. P. & P. £1.30.

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets and 5 pin din tape rec./play socket are mounted on the printed circuit panel, size approx. 9 1/2" x 2 1/2" x 1" max. depth. Supplied brand new and tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically), at only £29.00 plus 50p P. & P. Mains transformer with an output of 17V a/c at 500 mA can be supplied at £1.50 plus 40p P. & P. if required. Full connection details supplied.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-5-10-15-20-25-30-35-40-50V. half wave at 1 amp. or 1.0-1.0-2.0, 2.0-2.0, 3.0-3.0V at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2.00. P. & P. £1.00.

MAINS TRANSFORMER. For power supplies. Pri. 200/240V. Sec. 9-0-9 at 500 mA. £1.50. P. & P. 65p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. £1.65. P. & P. 65p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £2.35. P. & P. 90p. Pri. 200/240V. Sec. 23v. at 1.5 amp, 6v at 6 amp, 9v at 50 mA. £2.00 + 65p P. & P.

ALL PURPOSE POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v, and 7v, and 9v, and 12v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Ready built and tested. Price £8.75. P. & P. 95p

STEREO-DECODER SIZE 2" x 3" x 1 1/2"

Ready built. Pre-aligned and tested. Sens. 20-560mV for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6.00 plus 20p P. & P. Stereo beacon light if required 40p extra.

QUALITY RECORD PLAYER AMPLIFIER MK. II A top quality record player amplifier employing heavy duty double wound mains transformer. ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 8 ohm speaker. Size 7in wide x 3in deep x 6in high. Ready built and tested. PRICE £7.00. P. & P. £1.25. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £8.00. P. & P. £1.30.

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER




200/240V Mains operated Solid State A/M/F/M Stereo Tuner. Covering M.W. A.M. 540-1605 KHZ, VHF/FM 88-108 MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Voltage Indicator. Built-in Pre-amps with variable output volume adjustable by pre-set control. Max o/p Voltage 600 mV RMS into 20K. Simulated teak finish cabinet. Will match almost any amplifier. Size 8 1/2" w. x 4 1/2" h. x 9 1/2" d. approx. LIMITED NUMBER ONLY at £28 + £1.50 P. & P.

SPECIAL OFFERS

Mullard LP1159 RF-IF Double Tuned Amplifier Module for nominal 470kHz. Size approx. 2 1/2" x 1 1/2" x 2 1/2" 7-6V + earth. Brand new pre-aligned. Full specification and connection details supplied. £2.25 + P. & P. 20p.

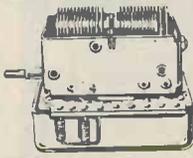Pye VHF/FM Tuner Head covering 88-108MHz/10.7MHz IF output 7-6V + earth. Supplied pre-aligned, with full circuit diagram. Connection details supplied. Beautifully made with precision-ganged FM Gang and 323 P1 + 323 P1 AM Tuning Gang only £3-15 + P. & P. 35p.



PRECISION MADE

Push Button Switch bank. 8 Buttons giving 16 S/P C/O interlocked switches plus 1 Cancel Button Plus 3 d/p c/o. Overall size 5" x 2 1/2" x 1". Supplied complete with chrome finished switch buttons 2 for £1.80 + 20p. P. & P.

HI-FI LOUSPEAKER SYSTEM MK II

Beautifully made simulated teak finish enclosure now with most attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 9" deep (approx.). Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, H.F. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 ohm, 8 ohm or 16 ohm impedance (state which). Handling power 10 watts R.M.S.

OUR PRICE £12.00 each. Carr. £2.20

Cabinet Available Separately £7-60 each. Carr. £1.60. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £11-10 each. Carr. £2.20.

LOUDSPEAKER BARGAINS

5in. 3 ohm £2-00, P. & P. 35p. 7 x 4in. 3 ohm £2-35, P. & P. 48p. 10 x 6in. 3 or 15 ohm £3-20, P. & P. 75p. 8 x 5in. 3 ohm with high flux magnet £3-00, P. & P. 60p. Tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms, £2-00 + 25p, P. & P. 2" PLASTIC CONE HF TWEETER 4 ohm, £3-50 per matched pair + 50p P. & P.

HIGH POWER HI-FI 8 ohm Dome Tweeter. 1" voice coil. Magnet size 3" dia. Suitable for use in up to 50 watt systems. £4-50 each + 60p P. & P.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price £1-50 yd. length. P. & P. 50p per yd. (min. 1 yd.). S.A.E. for samples.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20kHz. Can be mounted on ceilings, walls, etc. and used with or without baffle. Send S.A.E. for details. Only £8-40 each. P. & P. 90p for one, £1.10 for two.


Now also available 8"-8 ohm. 10 watts r.m.s. 20 watt peak 40 Hz-20,000 Hz. Overall depth 1". Ideal for Hi-Fi or for use in cars £5.25 + P. & P. (one 65p, two 75p).

SONOTONE STAHC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2-36. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2-86. P. & P. 18p.

LATEST CRYSTAL T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo 78. £1-80. P. & P. 18p.

LATEST T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1-58. P. & P. 18p.

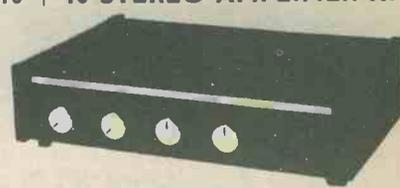HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise levels with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response ± 3 dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: ± 3 dB 12-15,000 Hz. Bass, boost approx. to ± 12 dB. Treble cut approx. to -16 dB. Negative feedback 16dB over main amp. Power requirements 35v. at 1-0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E. AMPLIFIER KIT £13.50 P. & P. 80p POWER PACK KIT £5.50 P. & P. 95p CABINET £5.50 P. & P. 95p

Special offer—only £23.75 if all 3 units ordered at one time plus £1.25 P. & P.

Full after sales service. Also available ready built and tested £31.25. P. & P. £1.50.




3-VALVE AUDIO AMPLIFIER HA34 MK II. Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £8.50. P. & P. £1.40.

HEL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £8.00. P. & P. £1.40.

10/14 WATT HI-FI AMPLIFIER KIT

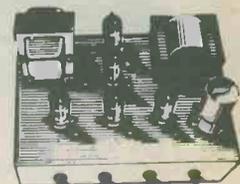A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram. Flow records and announcements to follow each other.



Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 25p x SAE (Free with parts). All parts sold separately. ONLY £13.50. P. & P. £1.40. Also available ready built and tested £18.00. P. & P. £1.40.

SPECIAL LINES OFFERED SUBJECT TO STOCK AVAILABILITY

Limited number of British Manufacturer's Surplus professional 100 watt RMS SAE amplifiers. Special features: 2 separate power modules, 1 for Bass response, and 1 for mid. range/tweeter. 5 stage LED display for power o/p indication. A/c mains i/p switchable for 110 or 240V. Can easily be converted to stereo. AVAILABLE TO PERSONAL CALLERS ONLY—PLEASE PHONE TO CONFIRM AVAILABILITY. Brand new and tested only £33.75.

OUR PRICES INCLUDE VAT AT CURRENT RATES

HARVERSON SURPLUS CO. LTD.

(Dept. REC) 170 HIGH ST., MERTON, LONDON, SW.19. Tel: 01-540 3985.


A few minutes from South Wimbledon Tube Station. SEND SAE WITH ALL ENQUIRIES. FOR PERSONAL CALLERS ONLY. WE CAN NOW OFFER A FULL REPAIR SERVICE ON ALL HI-FI EQUIPMENT, DISCO, CASSETTES, CAR RADIO, ETC.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. F. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

NEW for electronic design engineers!

FIX-PRINT for printed circuits

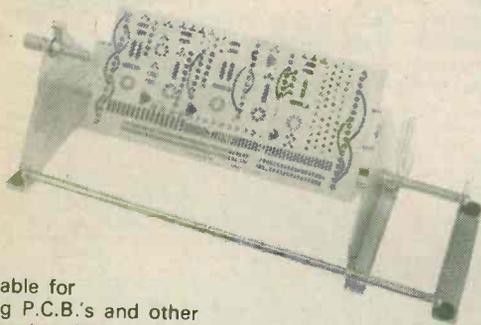


Invaluable for holding P.C.B.'s and other panels when inserting and soldering components. Can be adjusted to suit work up to 280mm, rotating to gain access to reverse side and locks in any position. All metal.

Price **£10** inc. VAT. p&p **£1**

Write or phone for full details

S2 Drill Stand

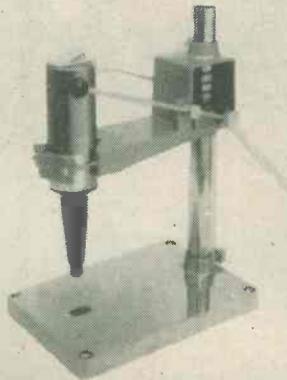

Robust, all metal with ample throat dimensions. Adjustable height cantilever with lever actuated feed. Spring return. Will accept both P1 & P2 drills
Price **£18.50** inc. VAT. p&p **106p**

P2 Drill **£16.50**. p&p **86p**

S1 Drill Stand



Constructed to take the popular P1 drill and ensure a high degree of accuracy in all types of electrical precision work.

Price **£5.13** inc. VAT. p&p **38p**
P1 Drill **£9.67**. p&p **38p**



PRECISION PETITE LTD

119a HIGH STREET TEDDINGTON MIDDLESEX TW11 8HG

TEL: 01-977 0878

LATEST BOUND VOLUME No. 29



of
"Radio & Electronics
Constructor"

FOR YOUR LIBRARY

Comprising
776 pages
inc. index

AUGUST 1975
to JULY 1976

PRICE **£3.10** P&P **90p**

BOUND VOLUME No. 27 (August 1973 to July 1974)

PRICE **£2.40** p. & p. **90p**

BOUND VOLUME No. 28 (August 1974 to July 1975)

PRICE **£2.75** p. & p. **90p**

Limited number of these volumes still available

We regret all other volumes are now completely sold out.
Available only from

DATA PUBLICATIONS LTD., 57 MAIDA VALE, LONDON, W9 1SN

STIRLING SOUND

POWER SUPPLY UNITS IN A RANGE OF

9



Made in our own Essex factory

MONEY SAVING MODELS FROM 12-70V WITH LOW-VOLTAGE TAKE-OFF POINTS

Specialisation coupled with designing and producing a series of keenly priced power amplifiers enables us to offer the following power units at really keen prices. ALL MODELS (except SS. 312) INCLUDE A STABILIZED LOW-VOLTAGE TAKE-OFF POINT (13-15V) FOR PRE-AMPS, TUNERS, ETC. Prices include V.A.T. and postage is free in U.K. Rated outputs are quoted unloaded.

| | | | | | |
|--------|--------|-------|--------|--------|--------|
| SS.312 | 12V/1A | £8.60 | SS.345 | 45V/2A | £10.75 |
| SS.318 | 18V/1A | £6.95 | SS.350 | 50V/2A | £11.75 |
| SS.324 | 24V/1A | £7.65 | SS.360 | 60V/2A | £12.75 |
| SS.334 | 34V/2A | £8.75 | SS.370 | 70V/2A | £14.75 |

SS.310/50 Stabilized unit, variable output from 10V to 50V/2A. Protected against short circuiting. £17.75

SS.300 Stabilizing unit for adding to standard power units. Output adjustable from 10 to 50V/8A. £5.50

■ PAY THE PRICE YOU READ AND NO MORE

To simplify ordering (and save you trouble and money) you just pay the price you read. The goods are sent post free in the U.K. and V.A.T. is included

■ £10.50 BUYS A KIT TO BUILD A CAPACITY DISCHARGE UNIT FOR YOUR CAR

Stirling Sound's 'Super-Spark' Mk. 5 available in kit form or ready-built includes instant revert-to-normal switch and the one model is adaptable to + or - earthing. Fit one now and don't be afraid of winter with starting problems, battery drain and engine strain. You can save on petrol and engine wear too as well as get livelier performance from your car.



Very easy to fit

- Rev. limiting control
- On-off immobilizer switch
- Return-to-normal-ignition switch

S.A.E. brings leaflet Complete kit of parts with metal case and leads

£10.50

Built and tested, in metal case

£12.75

All prices quoted include V.A.T. with goods sent post free in U.K. Owing to time between sending our ad in this journal and its appearing to the public, prices may be subject to alteration without notice E & O.E

Stirling Sound

All orders and communications to
37 VANGUARD WAY, SHOEBURNESS, ESSEX
Telephone: (03708) 5543

Shop: 220-224 WEST RD, WESTCLIFF-ON-SEA, ESSEX
Telephone (0702) 351048

STIRLING SOUND, 37 VANGUARD WAY · SHOEBURNESS, ESSEX

Please sendvalue £

NAME

ADDRESS

MY ACCESS/BARCLAY CARD No. IS RC12
(Block letters please)

WIRELESS TIME :



approx. ¼ full size digits shown here

National's MA1012 LED digital clock module is a complete clock & alarm unit, operating from 50 or 60 Hz mains, and offering all the features you would expect: Hours-minutes display in bright 0.5" leds with optional seconds, sleep and snooze alarms, fast and slow setting, AM/PM indicator, switched alarm outputs - but best of all *no RFI*. Thus the MA1012 is suitable for use in any radio/tuner applications, and requires just 1.75 x 3.75 x 0.7" total. (Ex. transformer). £9.45 per module, isolating mains transformer £1.50 each. (*8% vat) Two modules, and two transformers for £20.00 (+8% vat)

In the latest *Ambit* catalogue: more TOKO coils, chokes, filters etc., data on the short wave coil sets, a revised price list, micro-microphone inserts, special offer lines etc.

DETECKNOWLEDGEY

Metal locator principles and practise, including some of the facts and information manufacturers of £100+ detectors would rather you didn't know. £1.00 each.

The Bionic Ferret 4000 - a VCO metal locator based on the PW seekit, including all parts, plasticwork, ready wound coil etc. Inc. free copy of *detecknowledgey*. £34.26 in pp and VAT at 8%.

Special announcement. The Bionic Radiometer metal locator is at last to be released. A full VLF discriminator, with simultaneous display of ferrous, non-ferrous and foil objects. With a little practise, you can actually find objects obscured by junk. Outperforms units costing £150+. Digital control. Demo available at Brentwood, on sale soon for less than £75.SAE info:

COMPONENTS

Herewith the list of first quality parts and modules for wireless, inc. Europe's largest range of signal coils and inductors. ½m in stock!

| | | | | | | |
|-----------|----------|-------|---------|-----------|-------|--------------------------------|
| CA3089E | FM IF | 1.94 | BC413 | lo noise | 0.18 | MFL 2.4 kHz ssb mech. |
| KB4402 | FM IF | 1.94 | 40238 | shld RF | 0.25* | filter for ssb gen/IF 455kHz |
| HA1137W | FM IF | 2.20 | BF224 | 6ghz RF | 0.22 | with matching transf's. 9.95 |
| TBA120 | FM IF | 0.75 | BF274 | 7ghz RF | 0.18 | MFH series 4/5/7kHz band- |
| TBA120S | FM IF | 1.00 | ZTX212 | 50v/.3w | 0.17 | width @ 455kHz 1.95 |
| sn76660n | FM IF | 0.75 | ZTX213 | 30v/.3w | 0.16 | MFK series 7/9kHz bw 1.65 |
| ua720 | AM rad | 1.40 | ZTX214 | 30v/.3w | 0.17 | Modules/tunerheads etc. |
| CA3123E | AM rad | 1.40 | ZTX451 | 60v/1w | 0.18 | EC3302 3cct v/cap fm 7.50 |
| HA1197 | AM rad | 1.40 | ZTX551 | 60v/1w | 0.18 | EF5600 5cct v/cap fm 12.95 |
| TBA651 | AM rad | 1.81 | BD515 | 45v/10w | 0.27 | EF5800 6cct v/cap fm 15.25 |
| MC1350 | agc gain | 1.00 | BD516 | 45v/10w | 0.30 | EF5801 (5800+osc op) 17.45 |
| ua753 | fm gain | 1.80 | BD535 | 60v/50w | 0.52 | 8319 4 v/c, mos mixer 11.45 |
| LM1496 | Bal mix | 1.25 | BD536 | 60v/50w | 0.53 | 7252 complete fm mono |
| MC1310P | mpx dec | 2.20 | BD609 | 80v/90w | 0.70 | tunerset.afc,agc,mute 26.50 |
| KB4400 | as above | 2.20 | BD610 | 80v/90w | 1.20 | 7253 complete fm stereo |
| ca3090aq | mpx dec | 4.35 | BF256 | 1ghz fet | 0.34 | tunerset.afc,agc,mute 26.50 |
| HA1196 | mpx dec | 4.20 | E176 | p ch swt | 0.38 | 7020 10.7MHz fm if 6.95 |
| LM380 | 2w AF | 1.00 | MEM614 | (40822) | 0.38* | 7030 linear phase fm if 10.95 |
| LM381 | preamp | 1.81 | MEM616 | (40673) | 0.67* | 93090 ca3090aq dec 8.36 |
| tda2020 | 15w AF | 2.99 | MEM680 | no-noise | 0.75* | 92310 1310 decoder 6.95 |
| tca940E | 10w AF | 1.80 | BA102 | vfh varic | 0.30 | 91196 ha1196 decoder 12.99 |
| tba810as | 7w AF | 1.08 | BA121 | vfh varic | 0.30 | 91197 mw/lw v/cap tun.11.35 |
| LM301an | op amp | 0.39* | BB104 | dual var. | 0.45 | 7122 3 v/c mw (OR lw) tuner |
| ua741 | op amp | 0.34* | BB105 | uhf varic | 0.40 | KIT 15v tuning 9.00 |
| LM3900 | op amp | 0.68* | mvam2 | dual AM | 1.48 | 810k 7w af kit comp. £3 |
| 7805uc | 5v/tamp | 1.55* | mvam15 | 15v/AM | 1.05 | 940k 10w af kit 3.95 |
| tda1412 | 12v/% A | 0.95* | mvam125 | 25v/AM | 0.90 | tda2020k pr. tda2020 ics, |
| 78M20 | 20v/% A | 1.20* | | | | psb, heatsinks for pa 9.35 |
| 78M24 | 24v/% A | 1.20* | | | | All mpx decoders feature |
| ua723cn | variable | 0.80* | | | | TOKO pilot tone filters. |
| NE550a | as above | 0.80* | | | | Tuners: complete |
| taa550b | 32v ref | 0.50* | | | | Larsholt signalmaster Mk 8 |
| ic18038cc | sig gen | 4.50* | | | | Best fm tuner kit under £100 |
| NE555v | timer | 0.70* | | | | Looks as good as it sounds. |
| NE566v | vco | 2.50* | | | | Full instructions 86.95 |
| NE567v | tone dc | 2.50* | | | | Audiomaster amp. Matching |
| NE560B | hf pll | 3.50* | | | | 25+25w rms amp. 79.00 |
| NE561B | hf pll | 3.50* | | | | carriage on above £3 extra ea. |
| NE565K | hf pll | 2.50* | | | | Misc. |
| MC1312 | quad | 1.50 | | | | FX1115 beads, 100.25 |
| 11C90 | 650mhz | 14.00 | | | | MW/LW ferrite rod ant 0.90 |
| ZTX107 | 50v/.3w | 0.14 | | | | min. foil trimmers (see pl) |
| ZTX108 | 30v/.3w | 0.14 | | | | 221 100k pots for tuning.45 |
| ZTX109 | 30v/.3w | 0.14 | | | | RFchokes: 1uH to 120mH |

VAT is extra at 12½%, except where otherwise shown (*8%). PP now 25p per order. Catalogue 45p (inc). Pse send A5 or larger SAE with enquiries. Price lists free with an SAE. Full range of components etc available to callers at our new easy-to-get-to-premises.

ambit INTERNATIONAL

Number 2, Gresham Road, Brentwood, Essex. CM14 4HN
telephone (0277) 216029

Our new premises are only 200 yards from Brentwood station - with parking facilities outside the door !!

TRADE COMPONENTS

JUST A FEW BARGAINS ARE LISTED - SEND STAMPED ADDRESSED ENVELOPE FOR A QUOTE ON OTHER REQUIREMENTS. PAY A VISIT. OVER 90% OF STOCK BELOW QUANTITY WHOLESALE PRICE. ALL PRICES INCLUDE THE ADDITIONAL DISCOUNT IN LIEU OF GUARANTEE. MINIMUM ORDER GOODS VALUE £1.00.

Goods sent at customer's risk, unless sufficient payment for registration (1st class letter post), or compensation fee (parcel post) included.

| VALVE BASES | |
|--------------------------|-----|
| Printed circuit B9A-B7G | 5p |
| Chassis B7-B7G | 9p |
| Shrouded chassis B7G-B8A | 10p |
| B12A tube | 10p |

Speaker 6" x 4" 5 ohm ideal for car radio 70p

| TAG STRIP - 6 way 3p | |
|--------------------------------|-----|
| 5 x 50pF or 2 x 220pF trimmers | 20p |
| 9 way 5p Single 1p | |

BOXES - Grey polystyrene 61 x 112 x 31mm, top secured by 4 self tapping screws 32½p

Clear perspex sliding lid, 46 x 39 x 24mm 10p

ABS, ribbed inside 5mm centres for P.C.B., brass corner inserts, screw down lid, 50 x 100 x 25mm orange 48p; 80 x 150 x 50mm black 70p; 109 x 185 x 60mm black £1.10

Used 999 ALARM UNIT. 12 volt includes loop cassette tape player, 2 x d.p.t.d., 1 x 4 p.d.t. miniature relay. Reed relay, solenoid, 35 marked semiconductors, caps, resistors, pots, terminal strip etc.

£2.00 plus £1.40 p&p

| SWITCHES | | |
|----------|--------------|-------------------|
| Pole | Way | Type |
| 1 | 2 | Sub. Min. Slide |
| 6 | 2 | Slide |
| 2 | 1 | Rotary Mains |
| 2 | 1 (or 1p 2W) | Micro with roller |
| 2 | 3 | Miniature Slide |
| 1 | 2 | Toggle |

S.P.S.T. 10 amp 240v. white rocker switch with neon. 1" square flush panel fitting 30p

S.P.S.T. dot 13 amp, oblong, push-fit, rocker 15p

Sidleen/AFA Very High Security barrel Key Switch. 2 tubular keys £1.50

AUDIO LEADS
3 pin din to open end, 1½ yd twin screened 35p
Twin phono—open end, 4ft., twin screened 35p

COMPUTER & AUDIO BOARDS/ASSEMBLIES
VARYING CONTENTS INCLUDE ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKES ETC.

3lb for 85p + £1.00 post and packing
7lb for £1.95 + £1.40 post and packing

| | | | |
|--------------------------------|----|------------------|-----|
| 1k horizontal preset with knob | 3p | 3" Tape Spools | 3p |
| | | 1" Terry Clips | 4p |
| | | 12 Volt Solenoid | 30p |

TV KNOB
Dark grey plastic for recessed shaft (quarter inch) with free shaft extension 5p

ENM Ltd. cased 7-digit counter 2½ x 1½ x 1½" approx. 12V d.c. (48 a.c.) or mains 75p

ZM1162A INDICATOR TUBE
0-9 Inline End View. Rectangular Envelope 170V 2.5M/A £1

REGULATED TAPE MOTOR
9v d.c. nominal approx 1½" diameter 60p

3.5mm metal stereo plug 20p

Ferric Chloride, Anhydrous mil. spec. 1lb bag 40p

Car type panel lock and key 40p
18 volt 4 amp charger, bridge rectifier 79p
GC10/4B £3.00

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

Aluminium Knobs for ¼" shaft. Approx. ⅝" x ⅜" with indicator Pack of 5. 50p

JAP 4 gang min. sealed tuning condensers 20p

ELECTROLYTICS MFD/VOLT. Many others in stock 70- 200- 300- 450-
Up to 10V 25V 50V 75V 100V 250V 350V 500V MFD.

| | | | | | | | | |
|------|-----|-----|-----|-----|-----|-------|-----|-----|
| 10 | 4p | 5p | 6p | 8p | 10p | 12p | 16p | 20p |
| 25 | 4p | 5p | 6p | 8p | 10p | 15p | 18p | 20p |
| 50 | 4p | 5p | 6p | 9p | 13p | 18p | 25p | — |
| 100 | 5p | 6p | 10p | 12p | 19p | 20p | — | — |
| 250 | 9p | 10p | 11p | 17p | 28p | — | 85p | £1 |
| 500 | 10p | 11p | 17p | 24p | 45p | — | — | — |
| 1000 | 13p | 22p | 40p | 75p | — | £1.50 | — | — |
| 2000 | 23p | 37p | 45p | — | — | — | — | — |

As total values are too numerous to list, use this price guide to work out your actual requirements

8/20, 10/20, 12/20, 22/50 Tubular tantalum 20p each
16-32/275V. 100-100/150V. 100-100/275V 30p;
50-50/385V. 12,000/12V, 32-32-50/300V, 20-20-20/350V 60p; 700 mfd/200V £1.00; 100-100-100-150-150/320V £2.00.

RS 100-0-100 micro amp null indicator Approx. 2" x ¾" x ¾" £1.50

INDICATORS
Bulgin D676 red, takes M.E.S. bulb 30p
12 volt or Mains neon, red pushfit 18p
R.S. Scale Print, pressure transfer sheet 10p

CAPACITOR GUIDE - maximum 500V

Up to .01 ceramic 3p. Up to .01 poly 4p. .013 up to .1 poly etc. 5p. .12 up to .68 poly etc. 6p. Silver mica up to 360pF 8p, then to 2,200pF 11p, then to .01 mfd 18p.
8p. 1/600; 12p. .01/1000, 8/20. 1/500, 22/900. 4/16. 25/250 AC (600VDC) 40p. 5/150, 10/150, 40/150.

Many others and high voltage in stock.

FORDYCE DELAY UNIT
240 volt A.C./D.C. Will hold relay, etc., for approx. 15 secs after power off. Ideal for alarm circuits, etc. £1

CONNECTOR STRIP
Belling Lee L1469, 4 way polythene. 6p each

1½ glass fuses 250 m/a or 3 amp (box of 12) 6p
Bulgin, 5mm Jack plug and switched socket (pair) 30p

Reed Switch 28mm. body length 5p

Aluminium circuit tape, ⅝" x 36 yards—self adhesive. For window alarms, circuits, etc. 60p

MAINS DROPPERS
66+66+158 ohm, 66+66+137 ohm 5p
17+14+6 ohm, 266+14+193 ohm 5p
285+575+148+35 ohm }
25+35+97+59+30 ohm }

5½" x 2½" Speaker, ex-equipment 3 ohm 30p
2 Amp Suppression Choke 30p
3 x 2½ x 1½" } PAXOLINE 4p
4½ x 1½ x 1½" } 1p
PCV or metal clip on MES bulb Holder 4p
VALVE RETAINER CLIP, adjustable 2p

OUTPUT TRANSFORMERS
Sub-miniature Transistor Type 25p
Valve type, 40p

STYLII 15p

ER5SB/5MX/HC1/HC2/ER2. Compact X2/XC/SX. Garrard

GCM21T/22T/GKM24T/GKS25/GP59. B.S.R. C1/FX1M/

ST3/CS80/TC8/OP and T, and many other sapphire types.
Send sample required with payment and s.a.e if in doubt.

KEY EDIT and display boards with up to 132* 12V bulbs, 38 d.t.l. and t.t.l. i.c.'s and other components. (*A few bulbs may be broken).

£2.00 plus 75p p&p

Crouzet 30-minute timer-programmer, multi-variable contacts £6.00 plus £1.00 p&p

ACOS DUST JOCKEY record cleaner £1.00

Wood cased 8-12V buzzer £1.50 plus 80p p&p

36p

McMurdo 8 or 12 or 18-way plug and socket, ex-equipment

THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11
Open 10 a.m. till 7 p.m. Tuesday to Saturday. VAT receipts on request.
Terms: Payment with order Telephone: 01-223 5016

SEMICONDUCTORS

Full spec. marked by Mullard, etc. Many other types in stock

| | |
|---------------------|-----|
| AC128/176 | 8p |
| ACY28 | 19p |
| AD149 | 40p |
| AF116 | 16p |
| AF124/6/7 | 25p |
| AF133 | 20p |
| AF178/80/81 | 30p |
| AF239 | 30p |
| ASY27/73 | 30p |
| BC107/8/9 + A/B/C | 6p |
| BC147/8/9 + A/B/C/S | 6p |
| BC157/8/9 + A/B/C | 6p |
| BC178A/B, 179B | 12p |
| BC184/LC | 9p |
| BC186/7 | 20p |
| BC213L/214B | 10p |
| BC261B | 8p |
| BC327/8, 337/8 | 8p |
| BC547/8/8A/8C | 10p |
| BC556/6/7/8/9 | 9p |

| | |
|-------------------|-----|
| BCX32.36 | 12p |
| BCY40 | 50p |
| BCY70/1/2 | 12p |
| BCZ11 | 28p |
| BD113 | 50p |
| BD115/6 | 31p |
| BD131/2/3 | 35p |
| BD135/6/7/9 | 30p |
| BD140/142 | 30p |
| BD201/2/3/4 | 80p |
| BD232/4/5/8 | 49p |
| BDX77 | £1 |
| BD437 | 50p |
| BF115/167/173 | 15p |
| BF178/9 | 20p |
| BF180/1/2/3/4/5 | 15p |
| BF194/5/6/7 | 6p |
| BF194A, 195C | 6p |
| BF200, 258, 324 | 20p |
| BF202/3 | 30p |
| BF336 | 27p |
| BFS28 Dual Mosfet | £1 |

| | |
|------------------------|-----|
| BFW10/11 F.E.T. | 40p |
| BFW30 | £1 |
| BFW57/58 | 17p |
| BFX: 2/29/30 | 20p |
| BFX84/88/89 | 17p |
| BFY50/51/52 | 13p |
| BFY90 | 50p |
| BR101 | 30p |
| BRY39/56 | 26p |
| BSV64 | 30p |
| BSV79/80 F.E.T.s | 80p |
| BSV81 Mosfet | 90p |
| BSX20/21 | 14p |
| BSY40 | 27p |
| BSY95A | 12p |
| CV7042 (OC41/44 ASY63) | 5p |
| GET111 | 40p |
| ON222 | 20p |
| TIP30/3055 | 45p |
| TIS88A F.E.T. | 23p |
| TX300/341 | 7p |
| 2N393 (MA393) | 30p |
| 2N456A | 50p |
| 2N929 | 14p |
| 2N987 | 40p |
| 2N1507/2219 | 15p |
| 2N2401 | 30p |
| 2N2412 | 70p |

| | |
|-------------------------|-----|
| 2N2483 | 23p |
| 2N2904/5/6/7/7A | 15p |
| 2N3053 | 14p |
| 2N3055 R.C.A. | 50p |
| 2N3704 | 8p |
| 2N3133 | 20p |
| 2N3553 | 50p |
| 2N4037 | 34p |
| 2N6036 (Plastic 2N3055) | 30p |
| 2SA141/2/380 | 31p |
| 2SB135/6/457 | 20p |
| 40250 (2N3054) | 30p |

OTHER DIODES

| | |
|----------------------|-----|
| 1N916 | 6p |
| 1N4148 | 2p |
| BA145 | 14p |
| Centercel | 24p |
| BZY61/BA148 | 10p |
| BB103/110 Varicap | 20p |
| BB113 Triple Varicap | 37p |
| BA182 | 13p |
| OA5/7/10 | 15p |
| BZY88 11 to 33 volt | 8p |
| BZX61 Up volt | 15p |
| BR100 Diac. | 15p |

NEW B.V.A. VALVES

| | |
|-------|-----|
| EB91 | 34p |
| ECL80 | 34p |
| PCC84 | 34p |
| 6SN7 | 50p |
| 6AT6 | 50p |
| EZ81 | 40p |

TRANSFORMER
 Ferromag C core. Screen-85-105-115-125-200-220-240v
 Input: output 17v 1A x 2 + 24-0-24v 1.04A + 20v
 1mA. These current ratings can be safely exceeded by 50%. £3.50 + £1.00 p&p

WOODS 240V A.C.
 Approx. 2,500 r.p.m. continuous rated 5 or 6in. FAN (ex-computer)
 £3.80 plus £1 p&p

INTEGRATED CIRCUITS

| | |
|----------------------|-------|
| TAA700 | £2.00 |
| TBA800 | £1.00 |
| 741 8 pin d.l.l. op. | 24p |
| SN76013N | £1.20 |
| TAD100 AMRF | £1 |
| CA3001 R.F. Amp | 50p |
| CD4013 CMOS | 36p |
| TAA300 1wt Amp | £1 |
| TAA550 Y or G | 22p |
| TAA263 Amp | 65p |
| 7400 | 10p |
| 7402/4/10/20/30 | 14p |
| 7414 | 56p |
| 7438/74/86 | 24p |
| 7483 | 69p |
| LM300, 2-20 volt | £1 |
| 74154 | 90p |
| TBA5500 | £1.50 |

BRIDGE RECTIFIERS

| Amp | Volt | Part | Price |
|-------|------|-----------|-------|
| 1.600 | 140 | BYX10 | 30p |
| 1.4 | 42 | OSH01-200 | 26p |
| 0.6 | 110 | BY164 | 40p |
| 5 | 400 | EC433 | 6p |
| | | Texas | 90p |

RECTIFIERS

| Amp | Volt | Part | Price |
|--------------|------|---------|-------|
| IN4004/5/6 | 1 | 4/6/800 | 5p |
| IN4007/BYX94 | 1 | 1250 | 5p |
| BY103 | 1 | 1,500 | 18p |
| SR100 | 1.5 | 100 | 7p |
| SR400 | 1.5 | 400 | 8p |
| REC53A | 1.5 | 1,250 | 14p |
| LT102 | 2 | 30 | 10p |
| BYX38-300R | 2.5 | 300 | 40p |
| BYX38-600 | 2.5 | 600 | 45p |
| BYX38-900 | 2.5 | 900 | 50p |
| BYX38-1200 | 2.5 | 1,200 | 55p |
| BYX48-300R | 2.5 | 300 | 26p |
| BYX49-600 | 3 | 600 | 35p |
| BYX49-900 | 3 | 900 | 40p |
| BYX49-1200 | 3 | 1,200 | 52p |
| BYX48-300R | 6 | 300 | 40p |
| BYX48-600 | 6 | 600 | 50p |
| BYX48-900 | 6 | 900 | 60p |
| BYX48-1200R | 6 | 1,200 | 80p |
| BYX72-150R | 10 | 150 | 35p |
| BYX72-300R | 10 | 300 | 45p |
| BYX72-500R | 10 | 500 | 55p |
| BYX42-300 | 10 | 300 | 30p |
| BYX42-600 | 10 | 600 | 65p |
| BYX42-900 | 10 | 900 | 80p |
| BYX42-1200 | 10 | 1,200 | 95p |
| BYX46-300R* | 15 | 300 | £1.00 |
| BYX46-400R* | 15 | 400 | £1.50 |
| BYX46-500R* | 15 | 500 | £1.75 |
| BYX46-600* | 15 | 600 | £2.00 |
| BYX20-200 | 25 | 200 | 60p |
| BYX52-300 | 40 | 300 | £1.75 |
| BYX52-1200 | 40 | 1,200 | £2.50 |
| HAS310AF* | 1.25 | 1,250 | 40p |

***Avalanche type**

| Amp | Volt | TRIACS | Price |
|-----|------|-------------|-------|
| 6 | 800 | Plastic RCA | £1.20 |
| 25 | 900 | BTX94-900 | £4.00 |
| 25 | 1200 | BTX94-1200 | £6.00 |

Greenpar 50 ohm BNC line plug, round or flanged chassis socket or t.n.c. or u.h.f. plug, all 50p each

| | |
|--|-----------|
| RS 2mm Terminals Blue & Black | 5 for 40p |
| Chrome Car Radio fascia | 15p |
| Rubber Car Radio gasket | 5p |
| DLI Pal Delayline | 50p |
| Relay socket Take miniature 2PCO relay | 10p |
| B9A valve can | 5p |
| 0-30, or 0-15, black pvc, 360° dial, silver digits, self adhesive, 4 1/2" dia. | 10p |

OPTO ELECTRONICS

| Diodes | Photo transistor |
|------------|------------------|
| TIL209 Red | 12p |
| BPX40 | 50p |
| BPX42 | 80p |
| BPY10 | 80p |
| (VOLIAC) | |
| BPY68 | 80p |
| BPY69 | 80p |
| BPY77 | 80p |

PHOTO SILICON CONTROLLED SWITCH BPX66 PNP 10 amp £1.00

.3" red 7 segment L.E.D. 14 D.I.L. 0-9+D.P. display 1.9v 10mA segment, common anode 61p
 Minltron 3" 3015F filament £1.10

CQY11B L.E.D.
 Infra red transmitter £1
 One fifth of trade

Plastic, Transistor or Diode Holder 1p
 Transistor or Diode Pad 1p
 Holders or pads 50p per 100

Philips Iron Thermostat 15p
 MoMurdo PP108 8 way edge plug 10p

TO3 HEATSINK
 Europelec HP1 TO3B individual 'curly' power transistor type. Ready drilled 12p

Tested unmarked, or marked ample lead ex new equipment

| | | | |
|-----------|-----|-----------------------------------|-----|
| ACY17-20 | 8p | OC200-5 | 8p |
| ASZ20 | 8p | TIC44 | 24p |
| ASZ21 | 30p | 2G240 | £1 |
| BC186 | 11p | 2G302 | 5p |
| BCY30.34 | 8p | 2G401 | 5p |
| BCY70/1/2 | 8p | 2N1711 | 25p |
| BY126/7 | 4p | 2N2926 | 4p |
| HG1005 | 10p | 2N598/9 | 6p |
| HG5009 | 3p | 2N1091 | 8p |
| HG5079 | 3p | 2N1302 | 8p |
| L78/9 | 3p | 2N1907 | £1 |
| M3 | 10p | Germ. diode 1p | |
| OA81 | 3p | GET120 (AC128 in 1" sq. heat sink | 15p |
| OA47 | 3p | 2G5872 | 12p |
| OA200-2 | 3p | 2S3230 | 30p |
| OC23 | 20p | | |

KLAXON 12-24v 2-tone transistorized Alarm Sounder. Note, pitch and duration variable. Weatherproof alloy case. £10.00 p&p £1.30

THYRISTORS

| Amp | Volt | Part | Price |
|-----|------|----------------------------|-------|
| 1 | 240 | BTX18-200 | 30p |
| 1 | 400 | BTX18-300 | 35p |
| 1 | 240 | BTX30-200 | 30p |
| 15 | 500 | BT107 | £1 |
| 6.5 | 500 | BT101-500R | 90p |
| 6.5 | 500 | BT109-500R | £1.00 |
| 20 | 600 | BTW92-600RM | £3.00 |
| 15 | 800 | BTX95-800R Pulse Modulated | £8.00 |
| 30 | 1000 | 28T10 (Less Nut) | £3.00 |

PAPER BLOCK CONDENSER
 0.25MFD 800 volt 60p
 1MFD 250 volt 30p
 2MFD 250 volt 40p
 4MFD 250 volt 40p

I.C. extraction and insertion tool 32p

CHASSIS SOCKETS
 Car Aerial 9p, Coax 6p, 5 pin 180° 9p, 5 or 6 pin 240° din 6p, speaker din switched 10p, 3.5 mm switched 5p, stereo 1/4" jack enclosed 15p.

CRAZY OFFERS

| | | |
|------------------|----------|-----|
| 2000 mfd. | 50v | 16p |
| 2500 mfd. | 40v | 30p |
| 8 mfd. | 500v | 6p |
| 400 mfd. | 16v | 4p |
| .1 mfd. | 350/500v | 1p |
| .1 mfd. | 1500v | 2p |
| 2200 mfd. | 25v | 30p |
| 1000 mfd. | 200v | 25p |
| 10000 mfd. | 15v | 12p |
| 1250 mfd. | 35v | 10p |
| 6800 mfd. | 10v | 6p |
| 32+32 mfd. | 275v | 8p |
| 16+32 mfd. | 350v | 12p |
| 8+8 mfd. | 350v | 8p |
| 150 mfd. | 35v | 4p |
| 100 mfd. | 70v | 4p |
| 1 mfd. non-polar | 350v | 3p |
| 680 mfd. | 100v | 10p |
| 15 mfd. | 160v | 3p |
| 4700 pf. sub min | 500v | 1p |
| 4700 mfd. | 53v | 70p |
| 250 mfd. | 300v | 18p |
| 4700 mfd. | 40v | 35p |
| 25000 mfd. | 25v | 20p |
| 1000 mfd. | 63v | 30p |
| 1500 mfd. | 70v | 16p |
| 500 mfd. | 150v | 16p |
| 250 mfd. | 50v | 5p |
| 12000 mfd. | 12v | 12p |

G.E.C. 5% Hi-stab. capacitors .013, .066, .061, .066, .069, .075, .08, .089 2p each

Push-to-Break or Push-to-Make Panel Switch 24p

ENAM. COPPER WIRE SWG. PER YD.
 24 3p
 26 to 42 2.5p

GARRARD
 GCS23T Crystal Stereo Cartridge 66p
 Mono (Stereo compatible), Ceramic or crystal 60p

HANDLES
 Rigid light blue nylon 6 1/2" with secret fitting screws 5p

Belling Lee white plastic surface coax outlet box 20p

Miniature Axial Lead Ferrite Choke formers 2p

RS 10 Turn Pot 1% 250, 500 Ω, 1K, 50K £1.50

Copper coated board 10" x 9" approx 25p

TIE CLIPS
 Nylon self locking 3 1/2" 2p

Geared Knob 8-1 ratio 1 1/2" diam, black 70p

KLIPPON 25A 440v
 TERMINAL BLOCKS professional leaf spring clamp, strip of 12 for 15p or twin with clip-over cover 7p

POSTAL ORDERS means quicker service — unless a fee is paid for special clearance it is 15 days* to ensure cheques are not returned 'unpaid'. Postal order postage charge is offset by it now costing up to 16p bank charges on every cheque written out. * Timed from banking at Barclays till G.P.O. deliver returned cheque.

SMALL ORDERS, ENCLOSE SUITABLE STAMPED ADDRESSED ENVELOPE
 LARGE ORDERS, ADD SUFFICIENT FOR POSTAGE, PACKING, INSURANCE, ETC.
 TOTAL GOODS PLUS CARRIAGE, ADD V.A.T.

MAIL ORDER CUSTOMERS ONLY ADD 8% VAT-I PAY BALANCE ON 12 1/2% ITEMS
 ALL ENQUIRIES, ETC., MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE

THE MODERN BOOK CO

RADIO AND TV SERVICING 1976/1977 Models

by R. N. Wainwright

£10.20

MAKE THE MOST OF YOUR POCKET CALCULATOR

by L. Jansson PRICE: 95p

THE POCKET CALCULATOR GAME BOOK

by E. Schlossberg PRICE: £1.10

ADVANCED APPLICATIONS FOR POCKET CALCULATORS

by J. Gilbert PRICE: £3.90

INTRODUCTION TO COMPUTERS

by K. London PRICE: £1.35

BUILD YOUR OWN WORKING ROBOT

by D. L. Heiserman PRICE: £3.80

INTRODUCTION TO MICRO-PROCESSORS

by D. Aspinall PRICE: £5.30

MICROPROCESSORS/MICRO-PROGRAMMING HANDBOOK

by B. Ward PRICE: £4.00

UNDERSTANDING MICRO-PROCESSORS

by Motorola PRICE: £3.75

T.V. ENGINEERS' POCKET BOOK

by P. J. McGoldrick PRICE: £5.10

COLOUR T.V. PICTURE FAULTS

by K. J. Bohlman PRICE: £2.80

COLOUR T.V. WITH PART REF. TO THE PAL SYSTEM

by G. N. Patchett PRICE: £5.60

THE CATHODE-RAY OSCILLOSCOPE & ITS USE

by Patchett PRICE: £3.90

THE OSCILLOSCOPE IN USE

by I.R. Sinclair PRICE: £2.80

SERVICING WITH THE OSCILLOSCOPE

by G. J. King PRICE: £4.95

BASIC ELECTRONICS I-V

Schools Council PRICE: £7.60

BEGINNER'S GUIDE TO ELECTRONICS

by T. L. Squires PRICE: £2.60

OP-AMP CIRCUIT DESIGN & APPLICATIONS

by J. Carr PRICE: £3.90

99 ELECTRONIC PROJECTS

by H.Friedman PRICE: £2.65

110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME

CONSTRUCTOR

by R. M. Marston PRICE: £2.80

T T L COOKBOOK

by D. Lancaster PRICE: £6.60

ELECTRONIC CLOCKS & WATCHES

by M. Robbins PRICE: £5.00

BEGINNER'S GUIDE TO AUDIO

by I. R. Sinclair PRICE: £3.00

IMPROVING YOUR HI FI

by J. Earl PRICE: £3.85

CASSETTE TAPE RECORDERS

by J. Earl PRICE: £5.20

RADIO CONSTRUCTION FOR AMATEURS

by R. H. Warring PRICE: £2.75

STEREO F.M. RADIO HANDBOOK

by P. Harvey PRICE: £2.90

RADIO SERVICING POCKET BOOK

by V. Capel PRICE: £3.25

ILLUST. TEACH YOURSELF RADIO

by D. Gibson PRICE: £1.90

FOUNDATIONS OF WIRELESS & ELECTRONICS

by M. G. Scroggie PRICE: £4.40

THE PRACTICAL AERIAL HANDBOOK

by G. J. King PRICE: £6.20

RADIO & AUDIO SERVICING HANDBOOK

by G. J. King £5.45

WORLD RADIO TV HANDBOOK

by J. M. Frost PRICE: £5.70

THE RADIO AMATEUR'S HANDBOOK 1977

by A.R.R.L. PRICE: £6.70


PRICES INCLUDE POSTAGE

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone 01-723 4185

Electronics for nuts...

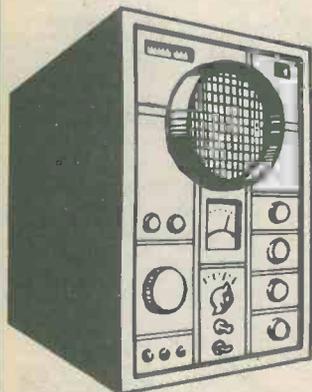


We take you step by step through all the fundamentals of electronics and show you how easily the subject can be mastered using our unique Lerna-Kit course.

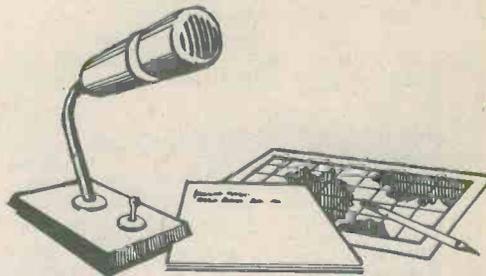- (1) Build an oscilloscope.
- (2) Read, draw and understand circuit diagrams.
- (3) Carry out over 40 experiments on basic electronic circuits and see how they work.

Electronics for hams.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.



Free!

Brochure without obligation to:

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

REC12


Block caps please

**new
book**

from **NEWNES-BUTTERWORTHS**

RADIO CIRCUITS EXPLAINED

Gordon J.
KING

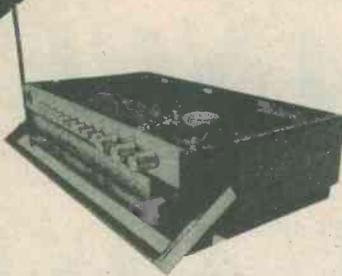

- ★ Circuits in modern radio receivers are examined — from the simple transistor set to the specialised hi-fi receiver.
- ★ Written by one of the best known authors in radio and electronics.
- ★ Invaluable to the Radio and Audio Technician, student and the enthusiast.
- ★ Richly illustrated, with a minimum use of mathematics.

CONTENTS: Block and flow diagrams — R. F. amplifier and mixer circuits — Frequency changer and r.f. oscillator circuits — Intermediate frequency circuits — Detector circuits — Audio amplifier circuits — Power amplifier circuits — Power supply circuits — Stereo coding and circuits for decoding — Index.

Available now 160 pages

£5.50

RECENT TITLES

**BEGINNER'S GUIDE TO
RADIO — 8th Edition**

Gordon J. King

1977 240 pages £2.75

**BEGINNER'S GUIDE TO
INTEGRATED CIRCUITS**

I. R. Sinclair

1977 192 pages £2.75



Order now from your local bookseller or from
NEWNES TECHNICAL, Borough Green,
Sevenoaks, Kent TN15 8PH



I'd been reading Home Radio's adverts for years and kept telling myself I must send off for a copy of their famous catalogue. But being an expert procrastinator I kept putting it off. I muddled along, picking up bits here and there, often calling at several shops before locating a particular component I needed.

If only I'd got a Home Radio catalogue in the first place — what time, energy and frustration I would have saved myself! I really do wonder now how I managed — this catalogue really has solved my component buying problems. In its 200 pages I hardly ever fail to locate just the piece I need. Not surprising when you consider it lists over 5,000 items, nearly 2,000 of them illustrated. Home Radio Components Ltd. do everything possible to make ordering quick and easy, and with their simple Credit Scheme I can order by phone any time of day or night, and settle up once a month.

Don't dilly dally like I did — take the plunge now by sending the coupon below with £1.40, and in a few days you can start on a wonderful new era of simplified component buying.

Please write your Name and Address in block capitals

NAME

ADDRESS



**POST
THIS
COUPON**
with cheque
or p.o. for
£1.40

HOME RADIO (Components) LTD., Dept. RC
234-240 London Road, Mitcham, Surrey CR4 3HD

Regd No 912966 London


HOME RADIO (Components) LTD. Dept. RC, 234-240 London Road, Mitcham, CR4 3HD, Phone: 01-648 8422

CMOS

CAPACITANCE

EVALUATOR

By Bruce Woodland

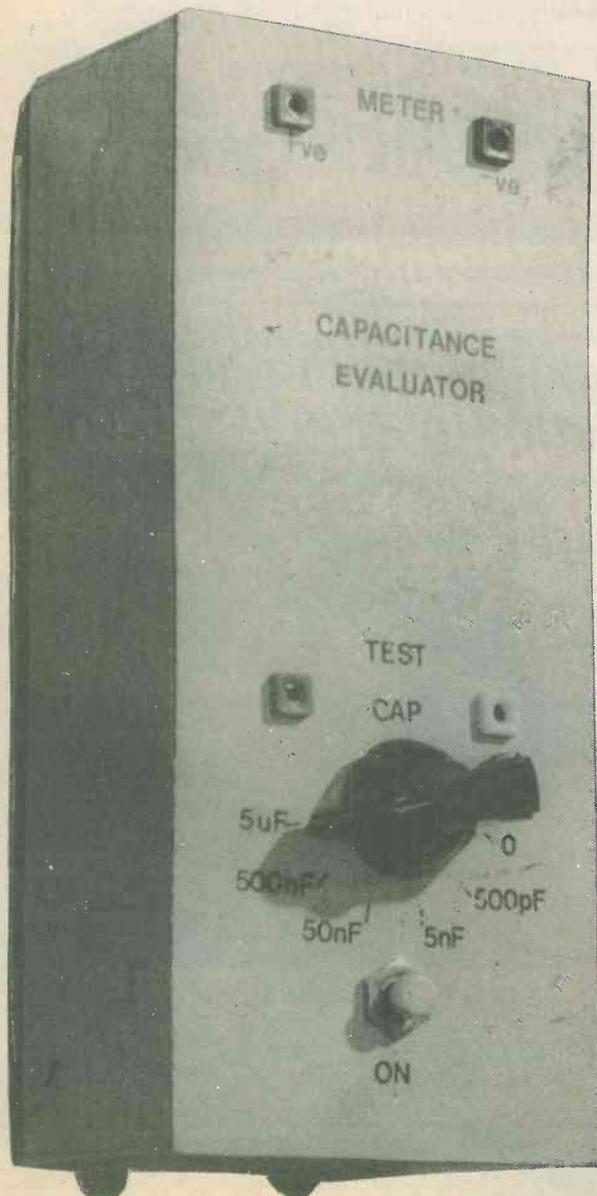

This low cost instrument incorporates a quad 2-input CMOS NAND gate and is capable of measuring capacitance from 50pF to 5 μ F. Capacitance is indicated by a moving-coil meter which can be plugged in as required, thereby conferring a significant economic advantage.

The high input impedance of CMOS logic integrated circuits permits quite sophisticated circuit elements to be developed from just a few gates. The unit described here exploits this versatility. An oscillator and a "single shot" monostable are built around four NAND gates form a linear scale capacitance meter. This can be used to determine the value of any non-polarised capacitor between 50pF and 5 μ F.

As only two active devices, the CMOS package and a p.n.p. transistor, are needed and since the meter movement need not be an integral part of the unit its cost is minimal.

PRINCIPLE OF OPERATION

The CMOS i.c. has four NAND gates and two of these, G1 and G2, appear with associated components in a rectangular wave oscillator. See Fig. 1. The falling edge of its output waveform triggers a monostable incorporating the remaining two gates, G3 and G4. The period of time during which the monostable is on after triggering is directly related to the value of the capacitance being measured and the associated timing resistor, R5, R6 or R7. The monostable output is low when it is on and this output is coupled to the meter via the buffer emitter

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5% unless otherwise stated)

- R1 68 Ω
- R2 270k Ω
- R3 27k Ω
- R4 27k Ω
- R5 10k Ω 2%
- R6 100k Ω 2%
- R7 1M Ω 2%
- R8 see text
- VR1 100k Ω pre-set potentiometer, 0.1 watt, horizontal skelton

Capacitors

- C1 20 μ F or 22 μ F electrolytic, 10V Wkg.
- C2 0.33 μ F (see text)
- C3 3,300pF (See text)
- C4 100pF polystyrene

Semiconductors

- IC1 CD4011
- TR1 2N4062K (see text)
- D1 BZY88C7V5

Switches

- S1 (a) (b) 2-pole 6-way, miniature rotary
- S2 push-button, miniature, press to make

Sockets

- SK1-SK4 insulated sockets (see text)

Battery

- BY1 9 volt battery type PP3 (Ever Ready)

Meter

- M1 external meter (see text)

Miscellaneous

- Materials for case (see text)
- Battery connector
- 4 plugs
- 2 crocodile clips
- Pointer knob
- 14 way i.c. holder
- Materials for printed circuit board
- Nuts, bolts, etc.

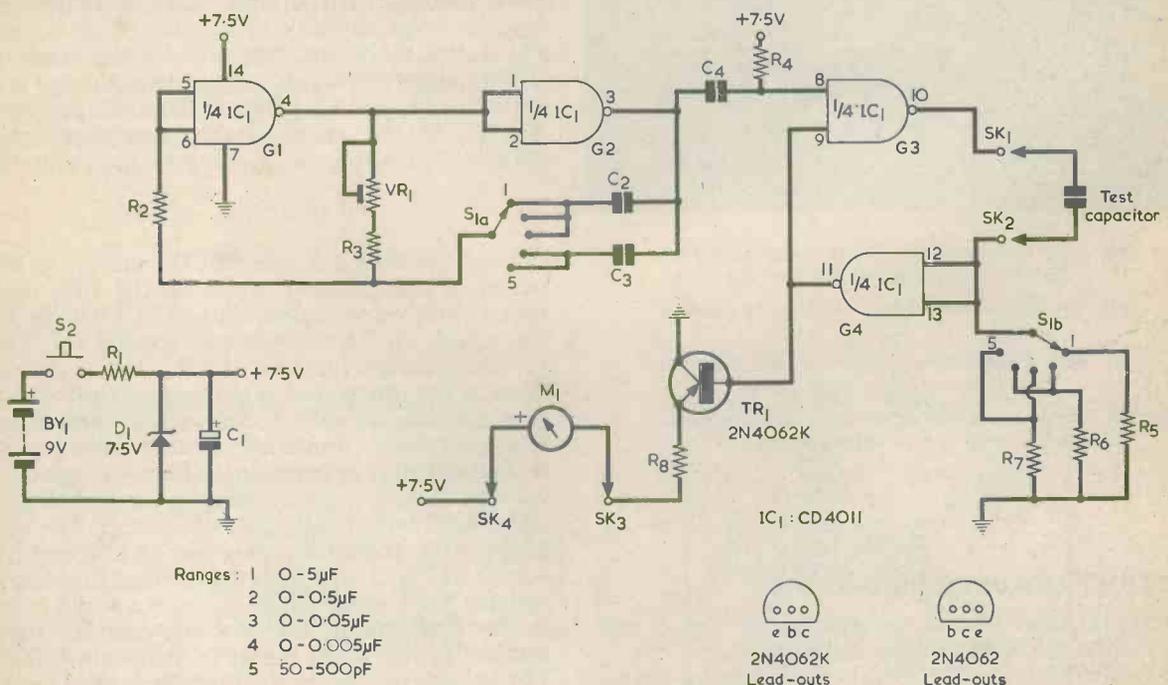


Fig. 1. The circuit of the CMOS capacitance evaluator. Meter M1 is an external meter, and can consist of a multimeter switched to a low current range

follower, TR1, allowing a relatively insensitive meter movement to be used without loading the output of the monostable. The magnitude of the meter reading is proportional to the length of the on period and hence a linear scale of capacitance results.

The oscillator repetition time is arranged to be fractionally longer than the monostable on period when maximum test capacitance for a range is connected. This results in a slight overload if the test capacitance is out of range. With the component values specified the monostable on period for maximum test capacitance should approximate to 90% of the oscillator repetition time, ensuring that meter overload can never exceed some 10%.

On ranges 1, 2 and 3, oscillator frequency is controlled by C2 and the monostable on period by R5, R6 or R7. Ranges 4 and 5 have oscillator frequency controlled by C3 and the monostable by R6 and R7.

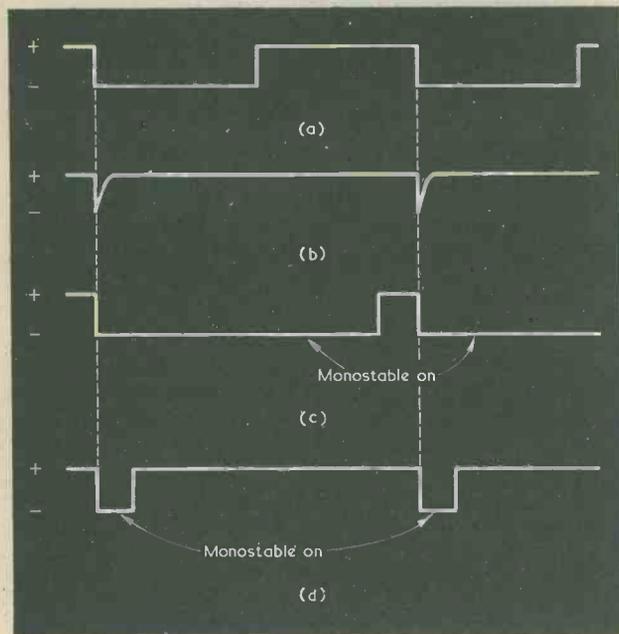


Fig. 2(a). The waveform at the output of the oscillator incorporating G1 and G2
 (b). The differentiated pulse applied to pin 8 of G3
 (c). The monostable output when the test capacitance has a high value
 (d). The monostable is on for a much shorter period with a low test capacitance

OUTPUT WAVEFORMS

Examination of the waveforms in Fig. 2 will clarify the principle of the instrument.

The waveform in Fig. 2(a) is the output of the oscillator at pin 3 of G2. This is differentiated by C4 and R4 giving the negative-going trigger pulse shown in Fig. 2(b). (Fig. 2(b) omits the small positive-going differentiated pulse given when the oscillator output goes high.)

If the test capacitor has a value near the maximum value of a range the monostable output, at pins 9 and 11 of C3 and G4, has the waveform il-

lustrated in Fig. 2(c). Note the extended time in which the monostable is on and its output is low. The monostable output waveform for a fairly small value of test capacitance is shown in Fig. 2(d). The output is low for only a short period.

PRACTICAL CONSIDERATIONS

Unfortunately, transfer voltages of CMOS gates are subject to considerable variation, ranging from about 30% to 70% of supply voltage. Whilst this makes little difference to the oscillator, the on time of the monostable is only predictable within fairly wide limits. The oscillator frequency thus needs to be adjustable, hence the pre-set variable resistor VR1, which is adjusted to the required value as described later.

A test capacitance of 50pF is about the lower limit for reliable results with this circuit. Indeed, the monostable will refuse to trigger if a test on less than about 20pF is attempted.

To ensure that the accuracy of the capacitance meter is not compromised by falling battery voltage, the simple zener stabilizing circuit incorporating R1 and D1 is utilised. C1 is a bypass capacitor for the stabilized voltage. The unit is powered by a 9 volt battery type PP3, this being quite suitable as current is only drawn from it when S2 is pressed to take a capacitance reading.

SUITABLE METERS

M1 is an external meter which is connected to the circuit at sockets SK3 and SK4. Any moving-coil meter movement having an f.s.d. of 5mA or less can be used, and it is preferable if this has a scale graduated 0-5 so that capacitance indications can be read directly. Naturally, the larger the meter the more accurate will be the readings. A multimeter switched to a low current range is quite suitable. The value of R8 will depend upon the sensitivity of the meter to be used and can be calculated from

$$0.9 (6.9 \text{ volts} - V_m)$$

divided by the f.s.d. value of the meter. In the expression, the 0.9 term caters for the 10% overload factor referred to earlier whilst the 6.9 volts term is the supply of 7.5 volts minus the 0.6 volt drop in the base-emitter junction of TR1. V_m is the voltage drop in the meter and is only significant when this is a multimeter switched to a low current range. Due to their universal shunt circuits, many testmeters drop a surprisingly high voltage on their current ranges, a quite common figure being of the order of 1 volt at full-scale deflection. The voltage dropped by the multimeter can be checked by the circuit of Fig. 3, in which the current limiting fixed resistor has a value which permits a slight overload in the multimeter, thereby allowing the variable resistor to adjust the meter to full-scale deflection. The voltage across the multimeter is then read by a separate voltmeter. With a panel-mounting single range meter movement the V_m term can be ignored.

If a panel-mounting 0-1mA meter having negligible V_m is to be used, R8 is equal to 0.9 times 6.9 volts divided by 1mA, which calculates as 6.2k Ω . However, to allow for component tolerances the next lowest preferred value should be selected,

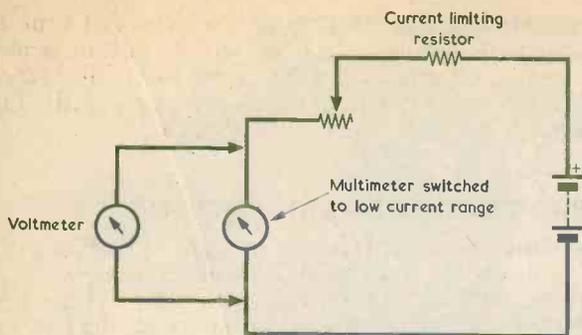


Fig. 3. The voltage dropped across many multimeters when these are switched to a low current range can be surprisingly high. This circuit enables the voltage dropped by a particular multimeter to be checked. The current limiting resistor must have a value which ensures that an excessive current cannot flow through the multimeter

whereupon R8 may be 5.6k Ω . The value of R8 can be similarly calculated for other meters.

COMPONENTS

The three resistors in the monostable circuit, R5, R6 and R7, are close tolerance components and are shown in the Components List as 2% types. No problems should be experienced in obtaining the values required in 2%; indeed, the values are fairly widely available in the closer tolerance of 1%. C2 and C3 should also be close tolerance. The 3,300pF capacitor required for C3 is listed by Maplin Electronic Supplies in 1% polystyrene, and such a capacitor would be an excellent choice here. It is a little more difficult to find a source of a close tolerance 0.33 μ F capacitor for C2, but a 5% carbonate component, again listed by Maplin Electronic Supplies, will be adequate in practice.

The transistor employed in the TR1 position in the prototype is a 2N4062K, which is not as readily

available as the normal 2N4062 and which has the rather unusual lead-out layout shown in the inset in Fig. 1. For convenience, Fig. 1 also shows the lead-out layout for the standard 2N4062, which may alternatively be used. If a 2N4062 is fitted to the author's printed circuit layout its leads are liable to cross each other and so should be covered with lengths of sleeving to prevent short-circuits. However, the choice of transistor for TR1 is not very critical and most small signal p.n.p. silicon transistors would be suitable.

VR1 is an 0.1 watt horizontal skelton potentiometer having 0.2 in. spacing between track tags and 0.4 in. spacing between track and slider tags. S1(a) (b) is a 2-pole 6-way rotary switch with no connections made to the sixth position. A 14 way i.c. holder is specified, and the CD4011 is fitted into this after wiring has been completed and checked out. In the prototype, SK1 to SK4 were insulated sockets suitable for 2mm. banana plugs.

CONSTRUCTION

The layout of the capacitance meter is by no means critical, and construction can proceed in any reasonable manner. However, the following details of the prototype instrument may be helpful.

The unit is housed in a home-made plywood case having internal dimensions of 5 $\frac{1}{2}$ in. long by 2 $\frac{1}{4}$ in. wide by 1 $\frac{1}{2}$ in. deep. Its front panel and four sides are covered by Formica. The back is cut from a sheet of aluminium and has flanges bent down at the ends to facilitate a push fit.

The printed circuit board, which is reproduced full size in Fig. 4, is mounted behind the front panel by means of four countersunk 6BA bolts and nuts, the bolt heads being covered by the Formica. Brass $\frac{1}{4}$ in. spacing washers are fitted over the bolts between the board and the front panel. The board is oriented such that R8 is at the top. The two switches and four sockets are also mounted on the front panel, in the position shown in the photograph. SK3 and SK4 are at the top, whilst SK1 and SK2 are just above S1 (a) (b). A simple

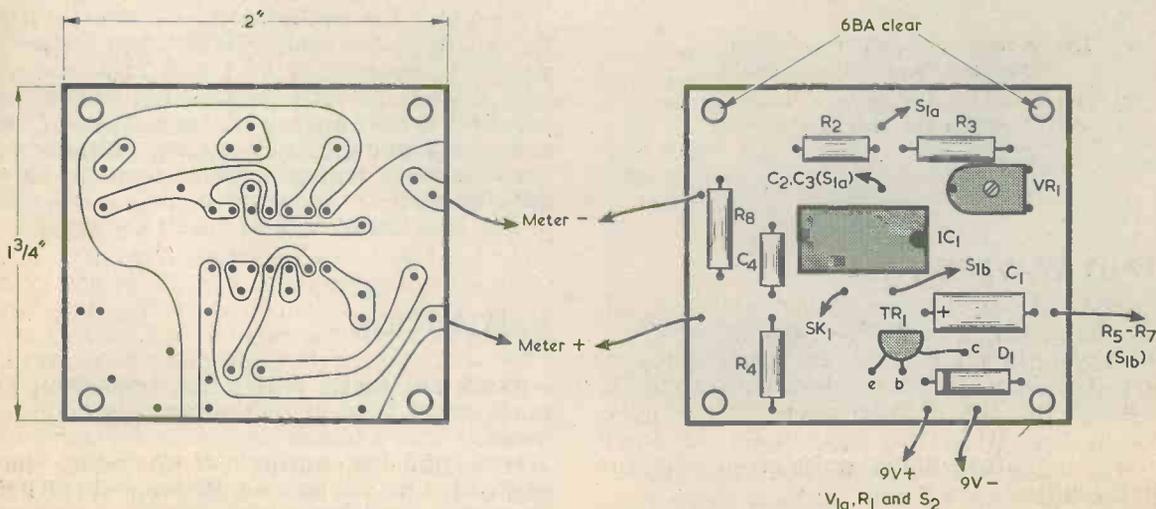


Fig. 4. The printed board layout employed in the prototype. This is reproduced full size for tracing


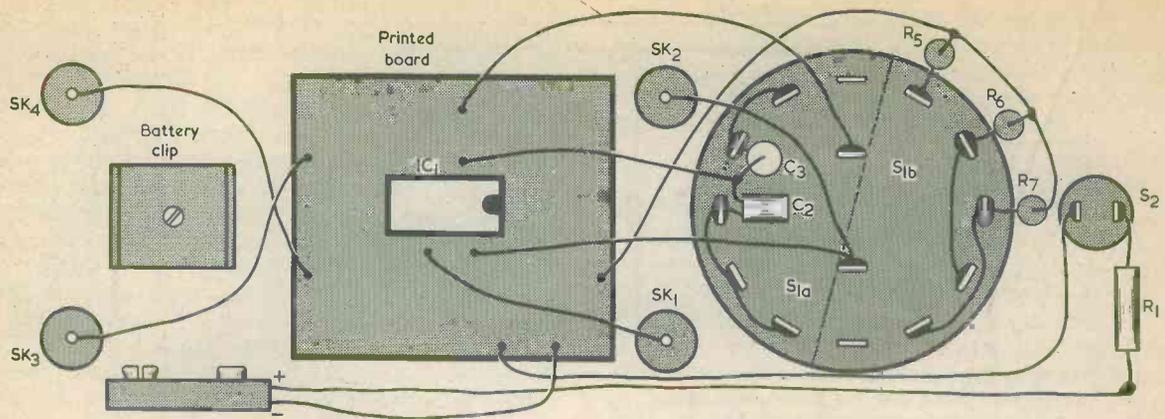


Fig. 5. Illustrating how the printed board connects to S1 (a) (b) and to the four sockets. Capacitors C2 and C3 and resistors R5 to R7 are soldered to the tags of S1 (a) (b)

home-made metal U-clamp to secure the battery is mounted to the back of the front panel above the printed board.

Resistor R1 is soldered to one tag of S2, with the positive battery lead connected to its free end. C2,

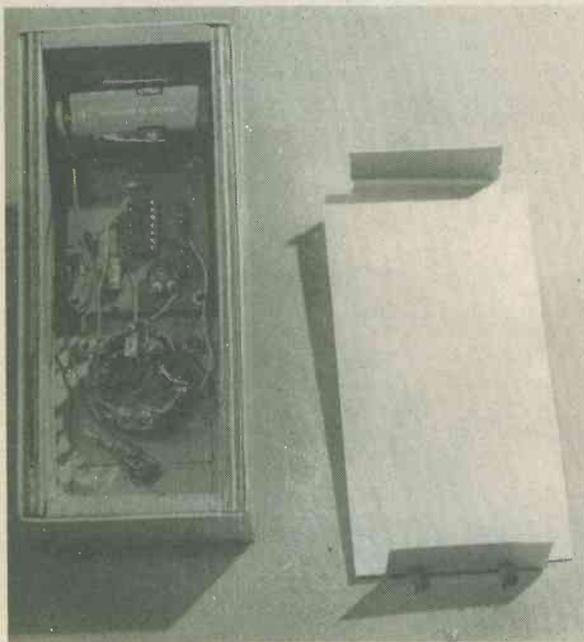C3 and R5 to R7 are soldered to the tags of S1 (a) (b), as illustrated in Fig. 5. The leads to S1 (a) (b) and to SK1 and SK2 must be kept as short as is reasonably possible and should not be twisted together. The most suitable test probe leads consist of 4in. lengths of insulated flexible wire terminating in crocodile clips at one end and plugs suitable for SK1 and SK2 at the other end.



The components and battery inside the evaluator case. The case bottom is simply a piece of aluminium sheet with flanges which fit inside the top and bottom of the case to provide a push fit

SETTING-UP

A close tolerance capacitor is required for setting-up the instrument, this having a value which is near the maximum of any range. The better this component, the more accurate will be the results obtained. Only one range has to be set up, the adjustment holding good for all the other ranges.

First plug the meter into SK3 and SK4, then set S1 (a) (b) to the appropriate range. Connect the standard capacitor to SK1 and SK2, and adjust VR1 so that it inserts maximum resistance into circuit (this is fully anti-clockwise in Fig. 4). Press S2 and slowly reduce the resistance inserted by VR1 until the meter reads the correct value for the standard capacitor.

The instrument is then ready for use.

PRECAUTION

Since the meter reading is dependent on the mark-space ratio of the monostable output, it is possible that a totally erroneous indication can be given if the test capacitance is greater than the maximum for the range selected. It is important, therefore, to always start with the highest range selected and then work down as required through the lower ranges.

BRR, BRR - - - BRR, BRR - - - TELEPHONE BELL SIMULATOR

By G. A. French

"A USEFUL STAGE PROP" (Suggested circuit)

In both amateur and professional theatrical work, the action of a play frequently requires that a telephone be caused to apparently ring on stage. It is, of course, quite an easy matter to make an electric bell ring by means of a simple circuit incorporating a battery and a push-button, but it is surprisingly difficult to operate the push-button so that the ringing of the bell takes place realistically with the familiar "brr, brr . . . brr, brr" rhythm of the standard Post Office ringing cycle.

This difficulty can be readily eased if an electronic circuit is employed to control the bell. All that is then required is that the electronic unit be switched on, whereupon the bell will ring in the normal telephone manner until the unit is switched off again. A circuit capable of meeting this requirement is described in the present article.

OPERATING PRINCIPLE

There are many ways of designing an electronic device which will provide the necessary ringing pattern, and one of the simpler ap-

proaches consists of employing two 555 timer i.c.'s, one of these controlling the bell directly whilst the second inhibits and enables the first i.c. to produce the requisite gaps between each pair of ringing periods. However, before turning to electronic details it is first desirable to examine the Post Office ringing cycle itself.

This is illustrated in Fig. 1, in which the ringing of the bell is indicated by the waveform rising to the "On" level. The bell rings for a period of 0.4 second, is silent for 0.2 second, rings again for 0.4 second and is then silent for 2 seconds. After that the cycle commences once more, with a second pair of 0.4 second ringing periods which have a gap of 0.2 second between them. The total cycle length is 3 seconds.

Fig. 2 shows a standard circuit for a 555 timer i.c. when it is used as a continually running astable multivibrator. At the instant of switch-on capacitor C is discharged and it then commences to charge via RA and RB in series. Under this condition the output voltage at pin 3 is high. When the voltage across the capacitor is equal to two-thirds of

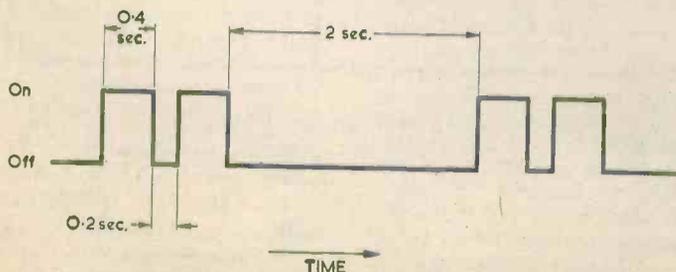


Fig. 1. The Post Office telephone ringing waveform. The bell sounds when the waveform rises to the "On" level

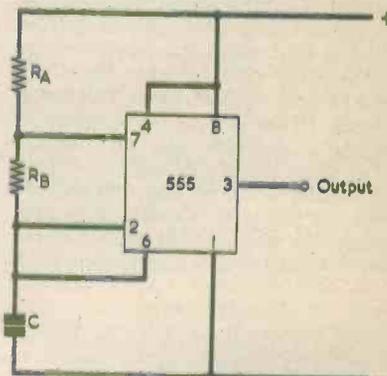


Fig. 2. A standard 555 astable multivibrator circuit. Points in this which are applicable to the telephone bell simulator are discussed in the text

the supply voltage the comparator connected to pin 6 of the i.c. triggers the internal flip-flop, causing both the output at pin 3 to go low and the internal discharge transistor connected to pin 7 to turn on. The capacitor now discharges via RB on its own until the voltage across it falls to one-third of the supply voltage. A second comparator, at pin 2, returns the flip-flop to its previous state, the output at pin 3 goes high again and the discharge transistor connected to pin 7 turns off. The capacitor once more charges via RA and RB in series until the voltage across it reaches two-thirds of the supply voltage. Thus the cycles proceed.

The length of time in a cycle during which the capacitor charges and the output is high is equal to 0.7 times the product of C and the sum of RA and RB, where time is in

seconds, capacitance is in microfarads and resistance is in megohms. The period during which the capacitor discharges is equal to 0.7 times the product of C and RB.

We can use a 555 timer to generate a series of pulses having an on period of 0.4 second and an off period of 0.2 second. Another 555 i.c. can then control the pulse generator so that it is only allowed to produce two pulses at a time and is then inhibited such that 2 seconds elapse before it is allowed to produce a further two pulses. The period during which the pulse generator is enabled, or is allowed to produce pulses, can be given either when the output of the controlling 555 is high, the first enable period immediately after switching on will be longer than all the subsequent enable periods because, during this initial period, the capacitor voltage has to rise from zero to two-thirds of the supply voltage instead of rising from one-third of the supply voltage. If we make the enable period correspond to that when the output of the controlling 555 is low then all enable periods will be of the same length. It then becomes feasible to design a circuit with no control other than an on-off switch. When the switch is closed there is a short wait (in practice about 3 seconds) before the first enable period starts and the bell commences to ring with

the standard "brr, brr . . . brr, brr" rhythm.

CIRCUIT DIAGRAM

The full circuit of the telephone bell simulator appears in Fig. 3. Here, IC1 is the controlling 555 whilst IC2 is the pulse generator. Let us assume for the moment that diode D1 and resistor R3 are not coupled to capacitor C3, whereupon IC2 is always enabled and is capable of oscillating continuously.

The period during which C3 charges and the i.c. output is high is equal to 0.7 times the product of the value of C3 and the sum of the values of R4 and R5. This calculates as 0.38 second. The time in each cycle when C3 discharges is given by 0.7 times the product of the value of C3 and that of R5, which is equal to 0.19 second. Thus, the output at pin 3 of IC2 is high for 0.38 second and is low for 0.19 second. The i.c. output drives a relay which is energised when the i.c. output is high, causing the electric bell to sound for about 0.38 second and to be silent for about 0.19 second. These periods are more than adequately close to the Post Office ringing and silent times of 0.4 and 0.2 second.

If we now take into account diode D1 and resistor R3 we can see that IC2 is enabled and is allowed to generate ringing pulses when the output of IC1 is low. Under this condition, diode D1 is reverse biased and capacitor C3 is free to charge via R4 and R5 and to discharge via R5. When the output of

IC1 goes high, IC2 is inhibited. This is because D1 is now forward biased and it causes the voltage across C3 to be taken to a level higher than two-thirds of the supply voltage. IC2 cannot then oscillate, its output is in the low voltage state and the relay is de-energised.

The upper waveform of Fig. 4 shows the voltage on the upper terminal of C3 with respect to the negative supply rail, whilst the lower waveform is the corresponding ringing waveform. In passing it should be mentioned that the output of a 555 does not go fully to the positive supply rail when it is in the high condition, but to a voltage of around 1 volt or more below it. In Fig. 4 it is assumed that this voltage is 0.8 volt and that a further forward voltage of 0.6 volt is dropped across D1, causing a voltage of 10.6 to appear across C3 during the inhibit period. (Resistor R3 has little effect on circuit operation and merely limits the initial charging current in C3 when IC1 output goes high).

During the inhibit period the upper terminal of C3 is in consequence at 10.6 volts and the output of IC2 is low. Also, the internal discharge transistor connected to pin 7 of IC2 is turned on. At the end of the inhibit period the output of IC1 suddenly goes low, allowing C3 to discharge into R5. The discharge continues until C3 voltage reaches one-third of the supply voltage at 4 volts, whereupon the IC2 flip-flop changes state, C3 commences to charge via R4 and R5, and the first

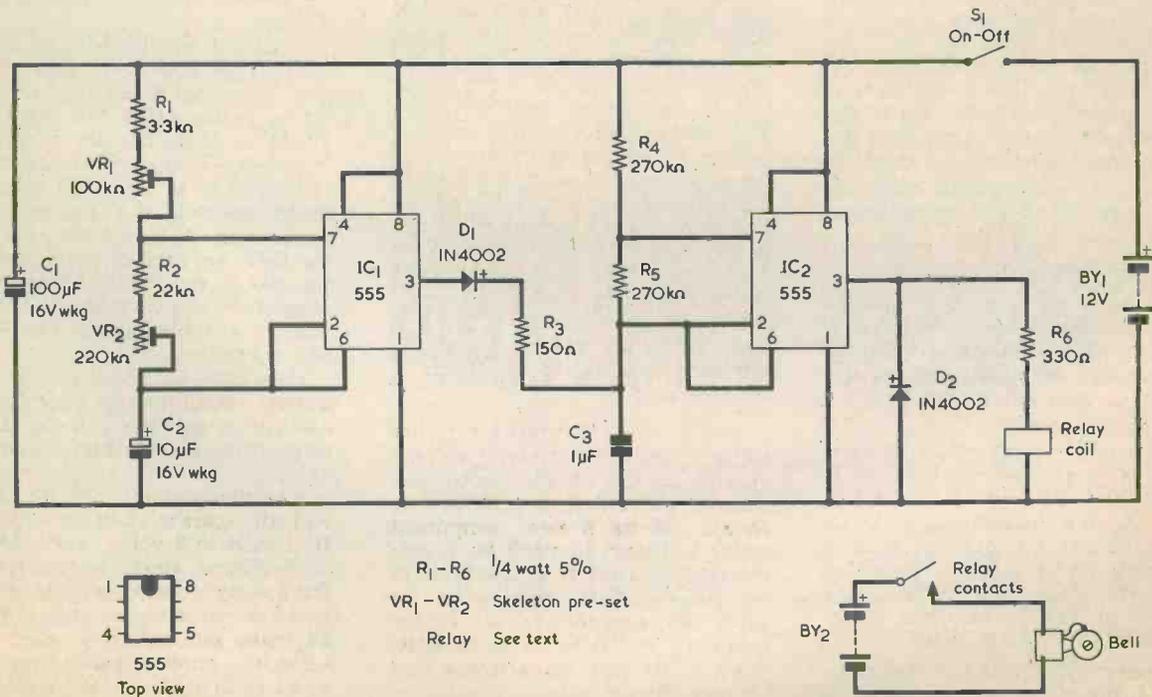


Fig. 3. The complete circuit of the telephone bell simulator. The relay contacts cause the bell to ring with the standard Post Office rhythm

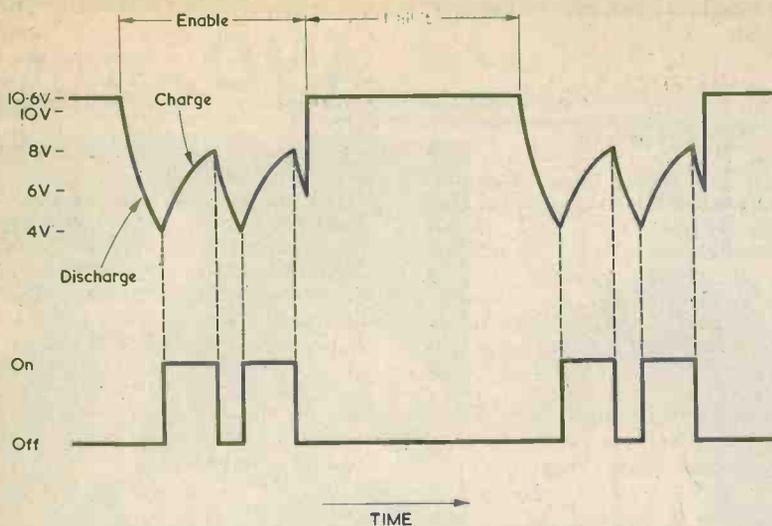


Fig. 4. The upper waveform illustrates the voltage on the upper terminal of C3 whilst the lower waveform is the corresponding ringing waveform. The length of the enable period is controlled by VR2 and that of the inhibit period by VR1

ringing pulse starts. The pulse continues until C3 voltage reaches two-thirds of the supply potential at 8 volts and then commences to discharge again. At 4 volts, the next ringing pulse starts, to terminate with the C3 voltage at 8 volts. C3 starts to discharge once more, but the enable period comes to an end before the capacitor voltage reaches 4 volts. The voltage is abruptly taken up to 10.6 volts, with IC2 consequently inhibited.

The sum of the enable and inhibit periods is 3 seconds. In practice the enable period (IC1 output low) is equal to about 1.4 seconds and the inhibit period (IC1 output high) is equal to about 1.6 seconds.

CONTROL PERIODS

The enable and inhibit periods produced by IC1 are controlled by C2, R1, VR1, R2 and VR2. If C2 had a value of $10\mu\text{F}$ exactly an enable time of 1.4 seconds (when C2 discharges) would be given by a total value in R2 and VR2 of $200\text{k}\Omega$ and an inhibit time of 1.6 seconds (C2 charging) when the total value of R1, VR1, R2 and VR2 is $230\text{k}\Omega$. However, it is necessary to make C2 an electrolytic capacitor, with a tolerance on its value of, typically, -10% to $+50\%$. As a result a wide degree of adjustment has to be provided in VR1 and VR2.

After construction has been completed, the adjustment procedure is carried out in the following manner. VR1 is initially set to insert about $25\text{k}\Omega$ and VR2 to insert about $100\text{k}\Omega$

into circuit, after which the unit is switched on by means of S1. The relay should now commence to operate. If VR2 is adjusted it will be found that as its resistance increases the relay operates more than twice during the enable periods and that, as its resistance decreases, the relay operates twice with the second energising period being shorter than the first. The correct setting of VR2 is between that which just allows two full relay energising periods and that which just allows a very short third energising period to take place. The setting should be somewhat closer to the first state of affairs than to the second condition, but it is not at all critical. If the capacitor employed for C2 has an exceptionally low value within its tolerance it may not be possible for VR2 to insert enough resistance to cause the relay to operate three times. Should this occur, the value of R2 can be increased to $47\text{k}\Omega$ or $68\text{k}\Omega$ as required. The possibility of this happening is, however, quite low.

If VR2 is set to insert a very low value of resistance the relay will not operate, as the enable periods are then too short. A final point is that, should C2 be a new component which has been in stock for a considerable period, it is desirable to let IC1 oscillate unadjusted for some 30 seconds to allow the capacitor to "form" and to settle down to its final capacitance and leakage current values.

After VR2 has been adjusted, VR1 is set up for a ringing cycle length of 3 seconds. The easiest way

of determining the cycle length is to count the number of cycles in a 30 second period whilst observing a watch having a sweep second hand or an l.c.d. digital second read-out. Since the inhibit period is only a little longer than the enable period the final setting in VR1 may be fairly close to that which gives zero resistance. Again the setting is not critical.

FURTHER POINTS

A few further points need to be dealt with. A supply voltage of 12 volts at BY1 rather than the usual 9 volts is recommended for two reasons. The first of these is that, during the inhibit period, the upper terminal of C3 is about 1.4 volts below the potential on the upper supply rail and this voltage difference could be significantly higher with some specimens of the 555 or when high temperature conditions prevail. A supply voltage of 12 volts nominal ensures that the upper terminal of the capacitor is taken well above two-thirds of the supply voltage even when the latter has dropped, due to an aging battery, to as low as 9 volts. The second reason is that the higher voltage ensures reliable relay operation when the relay coil has the resistor, R6, in series with it. To prevent the appearance of a high back-e.m.f. across the relay coil on de-energising it is necessary to connect a reverse diode across it, the diode in Fig. 3 being D2. However, such a diode, when connected directly across a relay coil, can cause contact release on de-energising to be sluggish. This effect is reduced to a negligible order in the present circuit by the inclusion of R6.

The relay should be a light quick-acting type and a suitable component here is the 6 volt nominal Open Relay with 410Ω coil which is available from Maplin Electronic Supplies. The operate voltage range of this relay is 4.8 to 35 volts. Its make contacts are connected in series with BY2 and the bell, and the bell can, of course, be wired to the rest of the circuit by way of a long length of 2-core flex. BY2 has a voltage suitable for the particular bell employed.

Capacitor C2 should be a good quality modern component. The author employed a Mullard miniature electrolytic capacitor here.

As already mentioned, the circuit will still operate when the voltage of BY1 falls to 9 volts. Since the 555 i.c.'s change states at fractions of the supply voltage, settings in VR1 and VR2 which have been made at 12 volts will still hold good at 9 volts. The current drawn from BY1 at 12 volts is about 12mA with the relay de-energised and about 25mA with the relay energised.

ELECTRONIC KITS AT THE INTERNATIONAL HANDICRAFTS EXHIBITION — OLYMPIA

The Philips range of electronic kits were shown for the first time at the International Handicrafts and D.I.Y. Exhibition, at Olympia, by SST Distributors (Electronic Components) Ltd. — part of the Philips group of UK companies.

Philips electronic kits are already well established in Europe. Now they are available by post in Britain from S.S.T. Distributors (Electronic Components) Ltd., West Green Road, Tottenham, London, N17 0RN.

The kits enable the electronics hobbyist to tackle a wide variety of constructional projects from a small multi-purpose amplifier to a studio-quality mixer unit.

Every kit contains all the components needed to complete a project, and all kits are sold with a money-back guarantee. Prompt postal delivery from S.S.T. is ensured.

In addition to the complete range of Philips kits, S.S.T. also supply the unique Breadboard and Blob-Board range from P.B. Electronics Ltd. These boards, as most readers will know, enable the constructor to prove his circuit design and then construct it in the simplest possible way.



Putting together a hifi-stereo amplifier. This is one of the many projects offered by the Philips range of electronic kits.

NEW MANUFACTURING FACILITIES FOR MINIATURISED PORTABLE RADIO TELEPHONES

A complete new production line for manufacturing and testing miniaturised CQP 800 portable radio telephones is now fully operational at Storno Limited's manufacturing facilities at Camberley, Surrey.

The Storno CQP 800, it is claimed, represents a new concept in the field of personal radios as its performance and reliability exceed many of the most advanced and larger sized mobiles. It is constructed from expandable modular thick film hybrid integrated circuits which permits the user to alter the facilities originally provided, or incorporate additional modules to increase the number of channels available.

The modular components are currently produced by Storno's parent company in Copenhagen. However, a company spokesman emphasised that the new CQP 800 production facilities embrace



Test technician aligns the CQP 800 and checks transmit watts and receiver sensitivity across the complete frequency band.

much more than assembling modules produced in Denmark.

Substantial amounts of new, test and quality control equipment, including infrared soldering systems; a hot and cold environmental test chamber; radio-telephony test sets; multi-frequency vibrator and a 'burn-in' test facilities have been installed at Camberley.

Initially, the mother board is fixed to the side panels, and then wired to the head module. A Q.C. inspector visually checks each stage of production before the various modules are pushed into the pins on the mother board. A function test is made of the complete unit.

At this stage the equipment is put through a series of environmental tests, the first of which is a 'burn-in' on the customer's transmitter and receiver cycle for any given length of time, depending on contract requirements. After the 'burn-in' the equipment is checked for transmit watts and receiver sensitivity across the complete frequency band.

A compressor unit and vibration table working with a programmer unit is used to test the sets under varying forces on all planes; much more severe than would be encountered in normal use.

The equipment is checked once again to ensure it conforms to its specification limits, and then air tested after the parameter has been recorded on a test certificate. A final Q.C. inspection prior to the sets being despatched completes the manufacturing process.

Storno CQP 800's are being increasingly used in the UK. Earlier this year several thousand personal sets and associated CQP 800 base stations were ordered by the Metropolitan Police and the Royal Air Force.

COMMENT

AN ARTIFICIAL EAR?

Scientists and Doctors in Cambridge and London have taken a first step towards the creation of an artificial ear to enable completely deaf people to hear, the science and industry unit of BBC World Service recently reported.

Over the past year, six completely deaf patients in Britain have been fitted with a thin wire electrode temporarily and painlessly implanted in their inner ears. Linked to a microphone the electrode has enabled them to hear parts of the speech of someone speaking nearby.

This is far from being an artificial ear, it produces only a crude sensation of sound in the user's brain, but patients are already finding that the device adds considerably to the effectiveness of lip reading.

A thin wire is implanted on to a membrane-covered opening to the cochlea, the inner ear. Depending on the wavelength of the sound, these shake different areas of sensory hairs in the walls of the cochlea, which in turn create the sensation of sound by stimulating the auditory nerve.

We regret that, as notified in our last issue, it has become necessary to increase to 45p the cover price of 'R. & E.C.'; to meet increased costs of production.

A glance at the 17 articles in this issue shows an impressive list of practical articles for the constructor, plus much useful information and general news of benefit to readers whether technically advanced or just commencing to enjoy our hobby.

Incidentally, we shall be very interested to learn of any unusual finds by readers who construct and use the Simple Metal Locator.

We have not previously commented on the Government's Central Policy Review Staff (the 'Think Tank') proposals for an eight hour cut in the present 24 hour cycle of the BBC's World Service.

Among other programme reductions, the proposals include:

- no transmissions to North America, Australia, New Zealand, Western and Southern Europe
- no broadcasting at all between 2000 and 0400 GMT and therefore no service for the large evening audiences in Europe, Middle East, Africa, Western Hemisphere.
- no breakfast listening in S.E. Asia, Australia, Indian Subcontinent, USSR East of Moscow, Iran, the Gulf, East Africa

To withdraw from a dominant role in world broadcasting seems very foolish. To quote the *Sunday Times*: "... Even the Tankers admit that 'External broadcasting can justifiably be claimed to be one of the UK's success stories.' Why then seek to limit it?"

EXHIBITED AT THE INTERNATIONAL RADIO AND TV EXHIBITION BERLIN




The Heinrich Hertz Institute for Communications Technology Berlin GmbH exhibiting and demonstrating a future communications system (Two-way Cable TV) at the International Radio and TV Exhibition 1977 Berlin, as shown in the photograph.

This technical system is intended as a communications aid (programme transmissions) and partner (computer dialogue) for private subscribers.

I.E.A. 78

IEA 78 — The 12th Instruments, Electronics and Automation Exhibition — will be staged at the National Exhibition Centre, Birmingham, from 13 to 17 March 1978, occupying the largest hall there, Hall 5, with three impressive sections for Electronic Components, Process Control Instrumentation and a General classification.

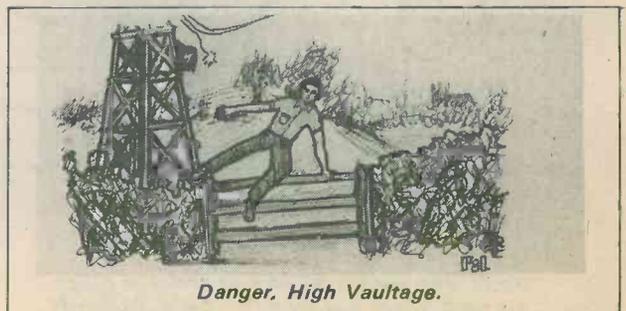Products will include professional and industrial electronics, active and passive components, process control and scientific instrumentation, machine tool control and automation, computer techniques and data handling. IEA 78 will be the only internationally recognised trade fair in 1978 covering the electronic and instruments industries in the United Kingdom.



NOTES FOR NEWCOMERS

THE EMITTER FOLLOWER

by F. T. Jones

Examines one of the basic transistor configurations.

The emitter follower (or common collector, because the collector is common to both the input and output circuits) configuration is one of the most useful in transistor circuit design. Fig. 1(a) shows a basic emitter follower circuit with an n.p.n. transistor whilst Fig. 1(b) illustrates the circuit with a p.n.p. transistor. A bias resistor for the base is assumed.

VOLTAGE GAIN

An input signal may be applied to the base of the emitter follower via a coupling capacitor. If the signal takes the base negative the emitter goes negative by virtually the same amount; taking the base positive causes the emitter to go similarly positive. In consequence the voltage gain of the emitter follower is almost exactly equal to unity, which is another way of saying that the output signal voltage at the emitter is the same as the input signal voltage at the base. The voltage drop inside the transistor between the base and the emitter stays at very nearly the same figure for all emitter currents within the range which the transistor can handle. With germanium transistors the voltage drop is typically 0.1 to 0.2 volt, whilst with silicon transistors it is of the order of 0.6 volt. The voltage drop increases slightly with increasing

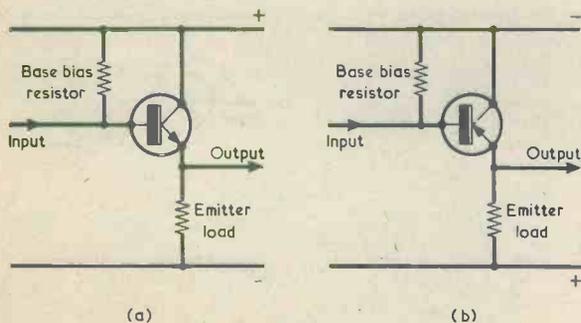


Fig. 1. The emitter follower or common collector configuration with (a) an n.p.n. transistor and (b) a p.n.p. transistor

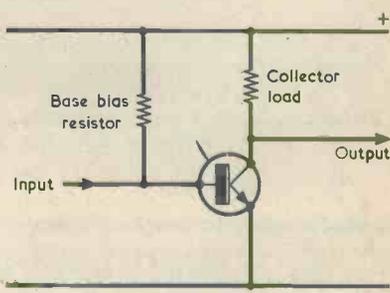


Fig. 2. An n.p.n. transistor in the common emitter mode

emitter current, with the result that the voltage gain is not precisely unity but is very slightly lower than this. For most practical applications it can be considered as being unity.

From the point of view of voltage the emitter "follows" the base. This explains the term "emitter follower".

CURRENT GAIN

In a transistor connected in the common emitter mode, as in Fig. 2, an increase in base current causes an amplified increase in collector current. This is the current gain of the transistor and under d.c. conditions can be defined by the term hFE. If a transistor passes a collector current of 10mA when the base current is 0.1mA we say that the transistor has an hFE of 100 (at the collector current concerned).

In an emitter follower an increase in base current similarly causes the collector current to increase, and both the collector and the base current in the transistor flow through the emitter. Under d.c. conditions the emitter current is the collector current of hFE times the base current plus the base current itself, whereupon static current gain becomes equal to hFE + 1. In most instances the error involved in stating that the emitter follower gain is equal to hFE is negligibly small.

The fact that the emitter follower provides current gain makes it suitable for driving a relatively heavy current through its emitter load when only a small current is available at its base. The input impedance at the base is approximately equal to the emitter load impedance, or resistance, multiplied by the h_{FE} of the transistor.

EMITTER FOLLOWER CIRCUITS

The emitter follower features extensively in Class B a.f. amplifier output stages, which have the basic circuit shown in Fig. 3(a). Two emitter followers, one n.p.n. and one p.n.p., have their bases coupled to the collector of a driver transistor. As the collector voltage of this transistor goes positive and negative with signal voltage so also do the bases of the two output transistors. When the driver transistor collector goes positive the p.n.p. transistor cuts off and the n.p.n. emitter follower causes an equal signal voltage to be applied across

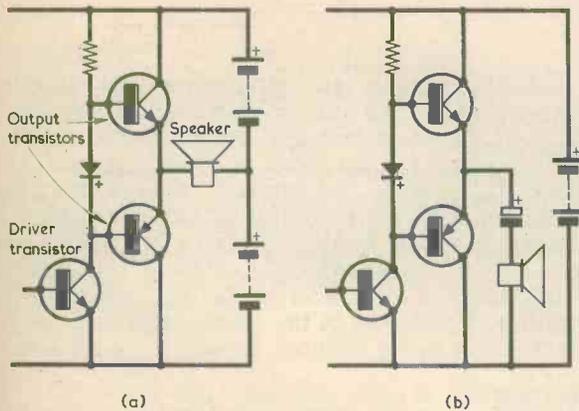


Fig. 3(a). A Class B a.f. amplifier output stage. The two batteries have equal voltages
(b). In practice a single battery can be used, the speaker being connected to either the positive or negative rail and coupled to the output emitters via a high value electrolytic capacitor

the speaker. The p.n.p. transistor similarly feeds negative-going signal voltages to the speakers. The diode between the two output transistors bases ensures that both the transistors are passing emitter current when there is either no signal or only a low signal voltage from the driver transistor, thereby obviating crossover distortion. Components other than diodes may be connected between the two bases to perform a similar function. There is no necessity to return the speaker to a mid-voltage point between the two batteries, as is done in Fig. 3(a), and it is normally more convenient to use one battery and couple the speaker to the output emitters via a large value electrolytic capacitor, as in Fig. 3(b).

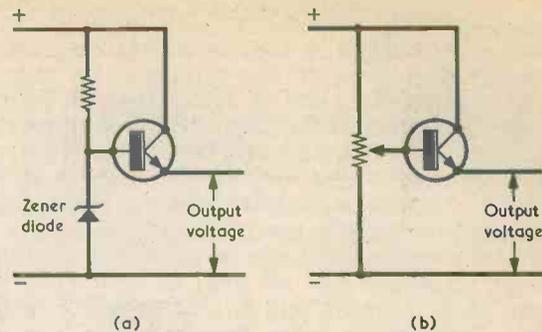


Fig. 4(a). A voltage stabilizing circuit incorporating an emitter follower
(b). A very simple variable voltage supply. The output current can be considerably higher than the current flowing in the potentiometer

The emitter follower performs many useful services in power supply circuits. In Fig. 4(a) it provides a relatively steady voltage for varying output currents, the output voltage being equal to the zener diode voltage less the voltage drop inside the transistor between its base and emitter. The advantage of the circuit is that the output voltage remains reasonably steady for widely varying output currents, whilst only a small current needs to flow in the resistor coupling to the zener diode and in the zener diode itself. A very simple variable voltage supply is given by the circuit of Fig. 4(b). The output voltage can be varied by adjusting the potentiometer and the advantage is that the current in the potentiometer can be much lower than the output current of the circuit. The emitter follower plays a similar role in more complicated power supplies having a much higher performance than the simple circuits of Fig. 4.

DARLINGTON PAIR

Two emitter followers in tandem form a "Darlington pair" and this is shown in Fig. 5(a) for

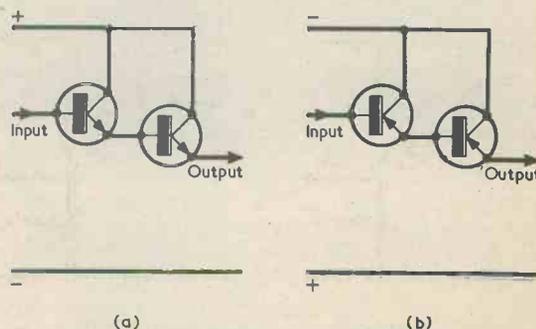


Fig. 5. The Darlington pair. In (a) this consists of two n.p.n. emitter followers whilst in (b) it is given by two p.n.p. emitter followers

n.p.n. transistors and in Fig. 5(b) for p.n.p. transistors. The voltage at the emitter of the second transistor now "follows" the voltage at the base of the first transistor, and is lower than it by the voltage drop between the base of the first transistor and the emitter of the second transistor. With two silicon transistors this drop is of the order of 1.2 volts (i.e. 0.6 volt in each transistor). The current gain is approximately the product of the gains of the two transistors, and can be exceptionally high. If each transistor has an h_{FE} of 300 times the overall static current gain is about 90,000 times.

The Darlington pair configuration is encountered in high output current applications such as those given in a.f. output stages. If only a small output current is required from the Darlington pair the input current, with modern small signal silicon transistors, can be extremely low. Fig. 6

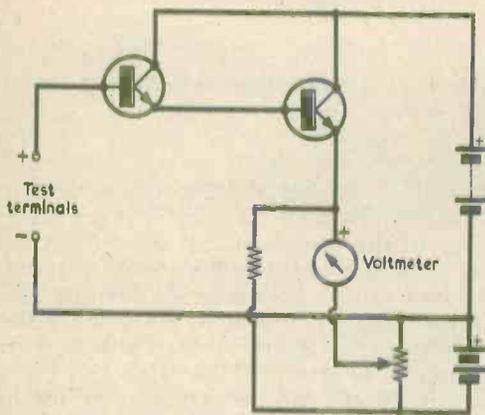


Fig. 6. An electronic voltmeter having a very high input resistance can be made up with two small silicon transistors in a Darlington pair. The lower battery has a voltage of 3 volts and the potentiometer a value of $1k\Omega$.

shows a Darlington pair employed in an electronic voltmeter where the main load is an ordinary moving coil voltmeter having a resistance of, say, $10,000\Omega$ per volt. Both transistors are small silicon types. The input resistance at the base of the first transistor is, in practice, of the order of tens or even hundreds of megohms (although this assumes leakage currents in the transistors which are lower than manufacturers' specifications).

This input resistance is higher than that encountered in bipolar operational amplifiers such as the 741, although it is not as high, of course, as that at the input of a CMOS op-amp such as the CA3130. In Fig. 6 the negative terminal of the moving coil meter is taken to the slider of a potentiometer. This is adjusted to cancel the base-emitter voltage drop in the Darlington pair and is set up such that the moving coil meter reads zero when there is zero voltage across the test terminals. The resistor between the emitter of the second transistor and the negative end of the potentiometer linearises low voltage readings and eases zero-setting by the potentiometer. It can have a value equal to about one quarter of the resistance of the voltmeter, and it also provides part of the Darlington pair output load. ■

HI-FI in the 1920's

by H. Ross McDonald

Drawing back the veil from over
half a century ago

The photograph accompanying this article shows one of the few quality amplifiers of the early 1920's. It was manufactured by the Western Electric Company around 1923 to 1924, and was intended to provide loudspeaker results from a crystal set with an economy of battery power. I understand that a 2-valve version was used by the early British Broadcasting Company (not yet a Corporation) as a portable studio microphone pre-amplifier. The model in the photograph employs 3 valves, these being "Weco" types.


VALVES

The "Weco" valve originated in America and cost about £1. 12s. in the U.K. (in 1977 that equals about £7.50). They are about 2in. long by $\frac{1}{2}$ in. in diameter and do not have socket pins like the majority of valves; they are instead bayonet fitting like an electric light bulb. They were intended for dry cell working and had a filament consumption of 1 volt at 0.25 amp. The maximum anode voltage was 80 volts.

I have made some quick measurements with the three valves in the set but, as I have no access to the original curves and do not know how many hours the valves have run, the figures may not be representative. I found that, at 70 volts h.t. and -1 volt grid bias, anode current is 4 to 5 mA, amplification factor is 6 to 7, mutual conductance is 0.45 mA per volt and anode impedance is about $15k\Omega$.

CONSTRUCTION

The amplifier is very well made, and is enclosed in a neat French-polished mahogany box measuring 5 by 5 by 10in. The lid has three small circular windows which allow the user to see if the valves are alight. Every surface that can be plated or polished has been so treated. The grid bias batteries made by Ever Ready are "specials" with unusual terminations, so obviously a fairly long production run was envisaged.

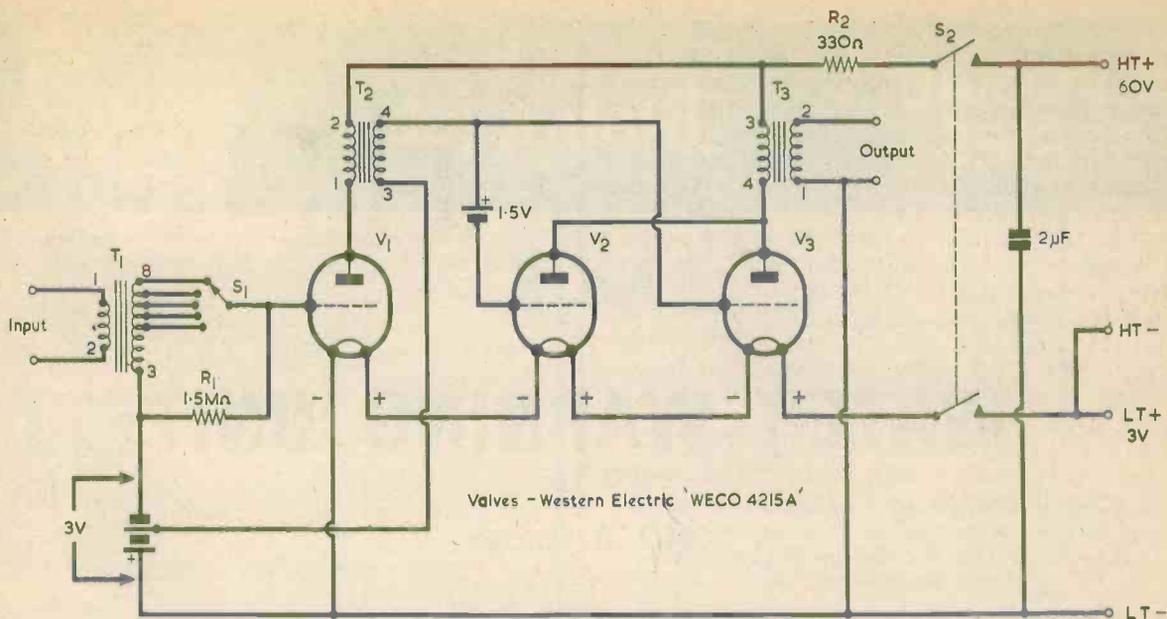

The circuit of the amplifier, S1 is a 5-position switch which functions as a volume control, whilst S2 is the on-off switch. Note that the 2 μ F capacitor, a paper dielectric component, is connected across the h.t. supply before the on-off switch

CIRCUIT


The circuit requires little comment. Since V2 and V3 are in parallel it is really a 2-valve amplifier. Because of the different filament potentials, a separate 1.5 volt cell is used to bias V2. This is rather an unusual arrangement as the 1.5 volt cell is floating at signal potential. Volume control is given by S1, which selects different taps in the secondary of transformer T1. The secondary circuit is damped by R1.

PERFORMANCE


I checked the amplifier with a 250mV input from a good sine wave source, assuming 2k Ω to be a reasonable output load and examining the results on an oscilloscope. At 1kHz the amplifier gave an output of 14 volts. There was very little output at 100Hz (1.3 volts) or at 10kHz (0.8 volt) but the output is sensibly uniform from 300Hz to 8.5kHz — certainly better than any loudspeaker of the period.

So, between 300Hz and 8.5kHz output power is 72 to 98 milliwatts with minimum sine wave distortion. I did not try a square wave source — too much copper and iron! The total d.c. power consumption, including filaments, was 1.3 watts.

Trying to simulate contemporary conditions I connected up to a 1924 horn loudspeaker and to my fine B.T.H. crystal set which, if one can find the right spot on the galena detector, will give 350mV on Radio 4. The results were quite gratifying, considering the basic simplicity of the equipment. Even now the amplifier really does what it was intended to do by the makers — "Give good clear loudspeaker volume from a simple crystal set".

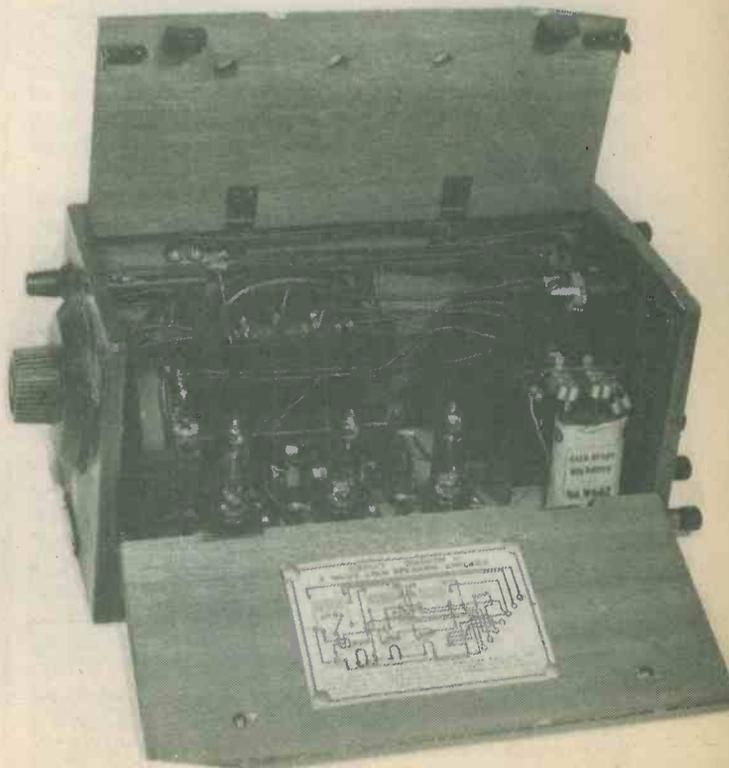

Now considerably more than 50 years old, this beautifully preserved a.f. amplifier is still working and can drive a 1924 h.c.m. loudspeaker with an input from a crystal receiver of the same period.

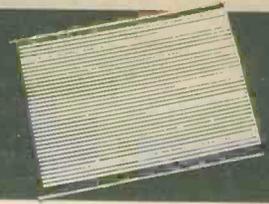

No. 6

WATER WARNING UNIT

By I. R. Sinclair

A circuit which offers audible warning when the presence of water is sensed by a detector strip.

This is a circuit which sounds a warning when a drop of water bridges two adjacent tracks on a piece of Blob Board. It can be used as a "wash-day alarm" to sound a warning of rain on the clothes line, a "drip alarm" to warn of leaks from washing machines, or a container alarm to warn of boiling-over pots or too vigorous fermentation of beer or wine.

CIRCUIT ACTION

The action of the circuit is simple. TR1 and TR2 in Fig. 1 are connected as a high gain current amplifier with the base of TR1 connected to one track of a spare piece of Blob Board which acts as the water detector. See Fig. 2. The adjacent track on the detector strip connects through a 100kΩ resistor, R1, to the positive supply.

The emitter of TR1 is connected to the base of TR2 so that any base current in TR1 will be greatly amplified by the two transistors. In turn, TR2 emitter supplies bias to the bases of TR3 and TR4.

These last two transistors are connected as a multivibrator where output frequency is decided by the values of coupling capacitors and base resistors that are used. The ideal frequency for our purpose is around 500Hz, since this gives a penetrating note that can be heard over other sounds at a distance. The effect of a drop of water bridging the two tracks of the detector strip is to allow some current to flow into the base of TR1, whereupon the multivibrator is biased on. The effect of varying resistance at the detector strip will be to alter the pitch of the note, making it more noticeable. The circuit is very sensitive, and even breathing on the detector is enough to sound the alarm.

For an indoor alarm the use of a small high-resistance speaker of 75Ω or more as a load for TR4 is quite adequate, and the circuit then has a battery consumption of 8mA. when the alarm

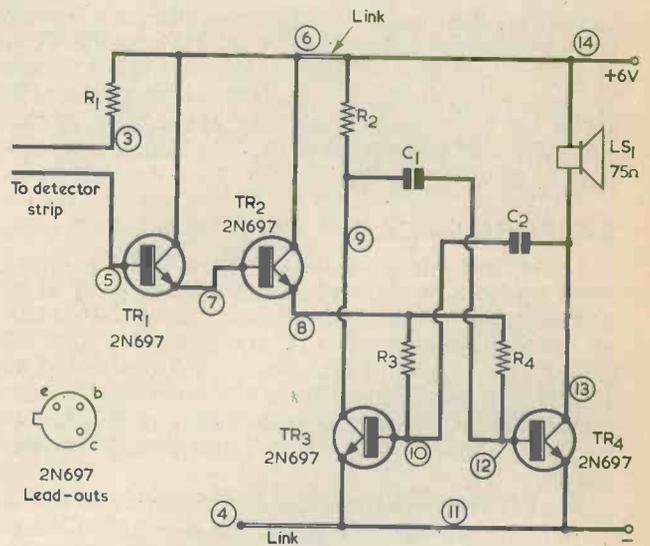


Fig. 1. The circuit of the water warning unit. The circled numbers indicate the Blob Board tracks at which connections are made.

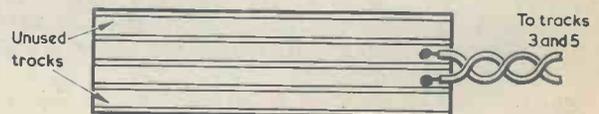


Fig. 2. The detector strip. This consists of a small piece of Blob Board and causes the main circuit to be activated when the two centre tracks are bridged by moisture.

COMPONENTS

Resistors

(All $\frac{1}{4}$ watt 10%)

- R1 100k Ω
- R2 2.2k Ω
- R3 68k Ω
- R4 68k Ω

Capacitors

- C1 0.02 or 0.022 μ F polyester
- C2 0.02 or 0.022 μ F polyester

Semiconductors

- TR1 2N697
- TR2 2N697
- TR3 2N697
- TR4 2N697

Speaker

- LS1 Moving-coil, 75 Ω or 80 Ω

Blob Board

- Blob Board type ZB-2V5

Miscellaneous

- 6 volt battery
- On-off switch
- Small piece Blob Board (for detector strip)

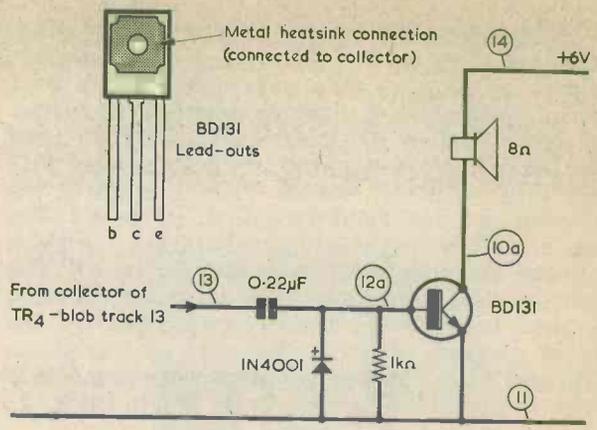


Fig. 3. An add-on output stage which gives a higher volume of warning tone. This is optional and the parts required are not included in the components list.

sounds. For outdoor use more power may be needed. This is easily provided by the additional stage shown in Fig. 3, but the current when the alarm sounds will rise considerably, to some 100mA or so, the actual current depending on the hFE value of the BD131. Only the simple indoor version is described in detail here, but the add-on power stage is outlined so that this stage can be added later or built right away, as may be required. The add-on power stage consists of a small power transistor coupled to the output of the multivibrator and having no bias so that it only passes collector current when the multivibrator operates. Its collector load consists of an 8 Ω speaker rated at not less than 3 watts.


Returning to Fig. 1 it may be thought that R4 in the base circuit of TR4 has rather a high value when the collector load for this transistor is a 75 Ω speaker. The circuit has, however, been checked in practice with a wide range of transistors in the TR4 position and has functioned satisfactorily in all cases. The high value of R4 keeps supply current consumption to a low level.

CONSTRUCTION

The most suitable Blob Board for this circuit is the ZB-2V5 board with its fourteen lines of tracks, and the circuit diagram of Fig. 1 shows the track numbering for each part of the circuit. Note that two tracks are used for the positive line, and these must be connected as shown. Having two positive supply tracks makes it easier to use transistors with short leads.

Start in the usual Blob Board way by measuring out your components against the tracks on the Blob Board to which they will connect, cutting leads to length as needed and shaping the leads so that the components can be mounted either horizontally or end-on. The author used disc ceramic capacitors

for C1 and C2. This type of capacitor has a relatively wide tolerance on value and constructors who prefer closer tolerance components may employ polyester capacitors instead. Polyester capacitors are shown in the Components List. Remember that components can be placed anywhere on the board as long as they connect to the correct tracks. Once the leads have been cut and shaped the ends can be tinned, ready to blob on the board.

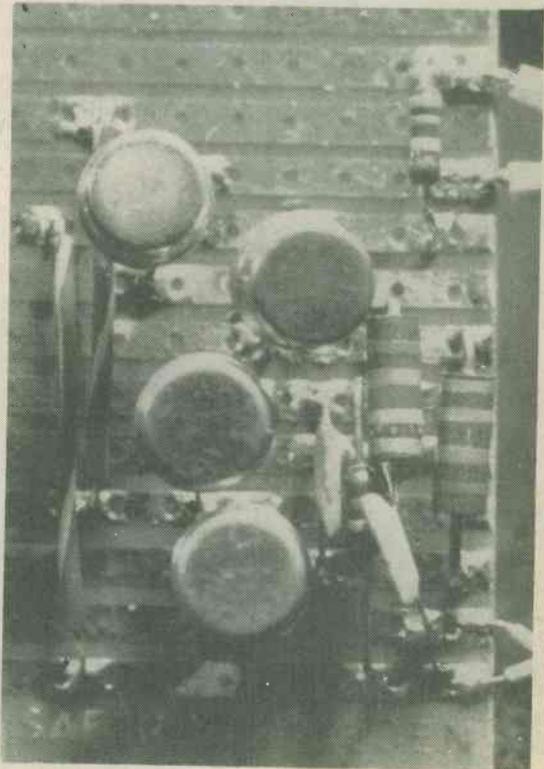

The components for the water warning unit are readily assembled on the Blob Board. The tinned tracks allow soldered connections to be made quickly and reliably.

As usual with this type of board, it is an advantage to start at the end opposite the track numbers so that the numbers are always visible. Leave some room for attaching the insulated wires to the detector strip, which may be several metres away if need be. Commence by blobbing on the transistors TR1 and TR2, with the base of TR1 on track 5, the collector on track 6 and the emitter on track 7. The base of TR2 is then also blobbed to track 7, with its collector on track 6 and its emitter on track 8. The resistors and capacitors can be mounted next, blobbed between the tracks as indicated in the layout diagram of Fig. 4, followed by transistors TR3 and TR4. The positive supply line connects to track 14 and the negative supply line to track 11.

A link wire connects track 4 to the negative supply and this prevents moisture on the board itself from setting off the alarm. Track 4 acts as a guard and ensures that any leakage from track 3 is to the negative supply rail, so that TR1 cannot be turned on.

can be mounted using thick tinned copper wire connecting to tracks 13 and 14 and the speaker tags. A case can then be made, large enough to hold the battery as well, the Blob Board with the detector strip on the top acting as a lid. An on-off switch in series with the positive supply can be mounted on one side of the case. The bottom of the case should not be boxed in but fitted with a coarse wire mesh or speaker grille and four short legs. There is then no risk of damage to the speaker if the box is placed on a wet surface, as is most likely. To hang the box on a clothes line, two wire hooks can be attached to the top of the case to hold it correct way up.

These are only suggestions and, doubtless, the keen constructor will devise alternative means of housing the unit and of positioning the detector strip and the speaker. Since the current drawn is very small until the alarm sounds, battery life is good. A suitable battery for the circuit of Fig. 1 would consist of four HP7 cells in series.


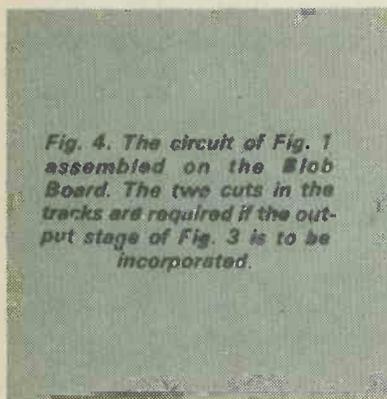


Fig. 4. The circuit of Fig. 1 assembled on the Blob Board. The two cuts in the tracks are required if the output stage of Fig. 3 is to be incorporated.

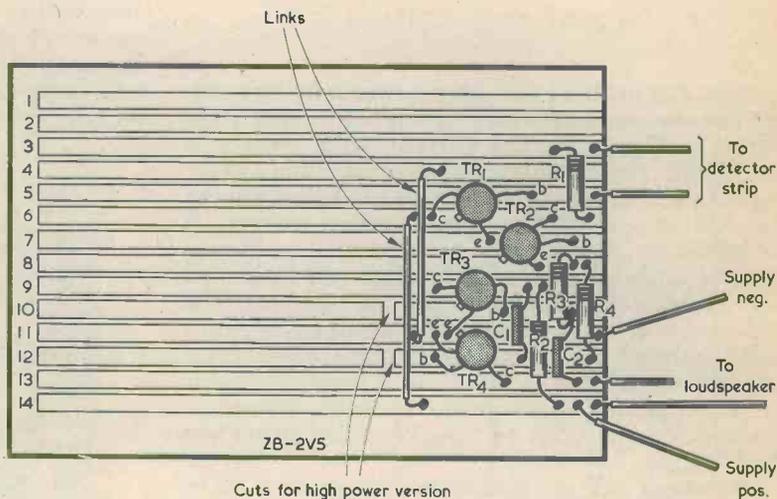

POSITIONING

The main problem is to suitably position the loudspeaker and the detector strip, and this depends on how the circuit is to be used. It is possible to build all the parts into one unit which can be hung on a clothes line; alternatively the detector can be placed under a washing machine, with the main unit on the wall and the loudspeaker in the hall. If the unit is being used to detect spillage of liquid, it is obviously better to have the main unit separated from the detector strip to avoid damage to the unit if spillage is too great. For a clothes line water detector, a neat solution is to mount the detector strip on the back of the Blob Board on which the circuit is assembled. The loudspeaker

ADD-ON STAGE

The circuit of the add-on power stage is given in Fig. 3. The loudspeaker of Fig. 1 is replaced by a $2.2k\ \Omega$ resistor connected between tracks 13 and 14, and the collector of TR4 couples to the base of the BD131 via a $0.22\ \mu\text{F}$ capacitor. There is ample room on the Blob Board for the additional transistor and components, though the tracks have to be cut as shown in Fig. 4. The new tracks which are now isolated from the existing ones, are referred to by the numbers 10a and 12a. The circuit with the add-on stage may be powered by two Ever Ready 3 volt No. 800 batteries connected in series.

DIRECT SUPPLY SERVICE TO READERS


TOWERS INTERNATIONAL TRANSISTOR SELECTOR

(NEW REVISED EDITION)



This is dead! 

Would this replace it?

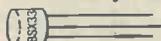

If it takes you longer than 1 minute to find out all about these transistors then you need a copy of TOWER'S INTERNATIONAL TRANSISTOR SELECTOR. Its one of the most useful working books you will be offered this year. And probably the cheapest!


In it you will find a really international selection of 13,000 transistor types — British, Continental European, American and Japanese. And we think that they will solve 90% of your transistor enquiries.

Current and widely used obsolete types were carefully selected and arranged in Numero-Alphabetical order by an author who was uniquely qualified to do the job. With his compendium, all you need to know is the type number and you can learn all about a transistor's specification; who made it and where to contact them; or what to use to replace it.

Price **£5.00** inc P&P

TOWERS INTERNATIONAL FET SELECTOR

(JUST PUBLISHED)

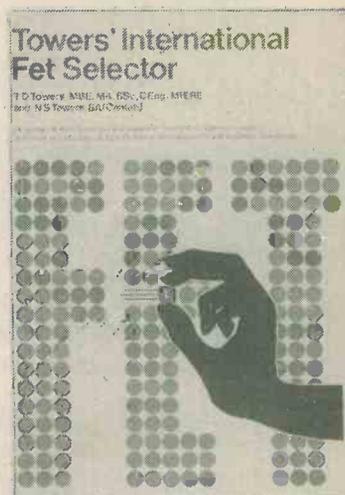

If you deal with field effect transistors, or fet's — whether as a student, a hobbyist, a circuit engineer, a buyer, a teacher or a serviceman — you often want data on a specific fet of which you know only the type number.

Specifications apart, you may be even more interested in where you can get the device in question. And perhaps more important still (particularly with obsolete devices), you may want guidance on a readily available possible substitute.

This fet compendium, a comprehensive tabulation of basic specification, offers information on:

1. Ratings
2. Characteristics
3. Case details
4. Terminal identifications
5. Applications use
6. Manufacturers
7. Substitution equivalents (both European and American)

The many fet's covered in this compendium are most of the more common current and widely-used obsolete types.

It is international in scope and covers fet's not only from the USA and Continental Europe, but also from the United Kingdom and the Far East (Japan).

Price **£4.00** inc P&P

(Please allow 21 days for delivery)

**Tower's
International
Transistor
Selector**

by **T. D. Towers**
MBE, MA, BSc, C Eng, MIERE
£5.00
inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME

ADDRESS

.....

.....

.....(Block capitals)

**Tower's
International
FET
Selector**

by **T. D. TOWERS**
MBE, MA, BSc, C Eng, MIERE
£4.00
inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME

ADDRESS


.....

.....

.....(Block capitals)

SHORT WAVE NEWS

FOR DX LISTENERS

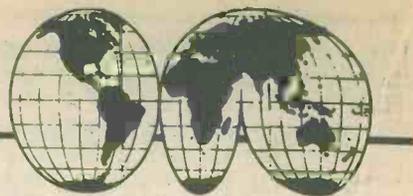

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

The 90 metre band (3200 to 3400kHz) can offer a varied diet of Dx for those who are prepared to dig amongst the QRM, who are patient and who are incurable insomniacs — well, we all have our failings!

As a guide to what may be heard, a few recent loggings on this band are featured below.

● BRAZIL

Radio Olinda, Pernambuco, on **3285** at 0043, OM with songs in Portuguese, announcements with echo-effect, identification at 0045. The schedule on a 24-hour basis and the power is 1kW.

● ECUADOR

Radio Iris, Esmeraldas, on **3380** at 0047, orchestral music with announcements in Spanish. The schedule is from 1100 to 0500 and the power is 10kW.

Radio Zaracay, Santo Domingo, on **3390** at 0053, OM in Spanish with a talk about music. The schedule is from 1000 to 0500 (but sign-off sometimes varies to 0845) and the power is 10kW.

● VENEZUELA

Radio Barcelona, Barcelona, on **3385** at 0050, Latin American dance music, OM in Spanish. Schedule is from 1000 to 1200 and from 2100 to 0400 and the power is 1kW.

Radio Universidad, Merida, on **3395** at 0058, OM in Spanish, local-style pops. The schedule is from 1000 to 0400 and the power is 1kW.

● GUATEMALA

La Voz de Nahuala, Nahuala, on **3360** at 0344, OM in Spanish, local pops. The schedule is from 1100 to 1300 and from 2230 to 0430 and the power is 1kW.

The saga will be continued next month.

CURRENT SCHEDULES

Whilst the schedules published here are correct at the time of writing, they may be subject to change at short notice.

● BANGLADESH

"Radio Bangladesh", Dacca, has an External Service in which a programme in English is directed to Europe from 1230 to 1300 consisting of a newscast and news commentary on **15520** and on **17890**. A further programme in English may be heard from 1815 to 1915 on **9495** and on **11620**.

● TAIWAN

The "Voice of Free China", Taipeh, presents a programme in English to Africa, the Middle East and Europe from 2130 to 2230 daily on **9510**, **9600**, **11860**, **15225** and on **17720**.

● ITALY

"RAI — Italian Radio and Television", Rome, in the current schedule, lists a programme in English for the U.K. from 1935 to 1955 on **7275**, **9710** and on **11800**. For insomniacs, "Nocturne from Italy" is on the air from 2230 through to 0500 on **6060**, the programme consisting of musical items with newscasts in Italian and English every hour on the hour.

● INDONESIA

"The Voice of Indonesia", Jakarta, radiates programmes in English intended for South East Asia and the Pacific from 0100 to 0200, 0800 to 0900 and from 1400 to 1500 on **9585** and **11790**.

● SAUDI ARABIA

The "Broadcasting Service of the Kingdom of Saudi Arabia", Jiddah, has a programme in English for North Africa from 1900 to 2200 on **11855**.

● PORTUGAL

"Radiodifusao Portuguesa", Lisbon, transmits a programme in English to Europe from 2030 to 2100 on **6025** and on **9740**.

AROUND THE DIAL

● NIGERIA

Lagos on a measured **15118** at 0628, African drums interval signal, identification and Nigerian news in English at 0630 then a religious programme until 0700 identification and "Weekend Magazine" with a further newscast at 0730. **15120** is the listed frequency, the above programme also in parallel on **7275** but not heard. Some interference at times from the Vatican transmitter on **15120**.

● VATICAN

Vatican City on **9645** at 0640, light music with announcements in Italian, French and English. Also on **7250** at 1345 with news of the Catholic world in English.

● PORTUGAL

Lisbon on **9670** at 0646, YL with a religious talk in English.

- **TANGIER**
UN Tangier on **9630** at 0630, news of United Nations proceedings in English; into a programme in Hebrew at 0635.
- **CAPE VERDE**
Voz de Sao Vicente on a measured **3931** at 2128, OM in Portuguese, light music Portuguese style.
- **SAO TOME**
Radio Nacional de Sao Tome on a measured **4807** at 2020, YL's with songs, local music in typical style.
- **CANADA**
Sackville on **17760** at 1945, OM with "Saturday Magazine" which included a talk on Canadian pops in the English programme scheduled for Europe from 1930 to 2000 on this channel and in parallel on **5995, 9530, 11855** and on **15325**.
- **ECUADOR—2**
HCJB Quito on **17755** at 2000, identification, 4 pips time-check then "DX Party Line", a programme for Dxers. Also in parallel on **15310**.
- **SOUTH AFRICA**
RSA Johannesburg on **17780** at 0600, identification followed by news of African affairs in English. This transmission is intended for West Africa and is scheduled from 0600 to 0700 on this channel and in parallel on **11900** and **15220**.
- **AUSTRALIA**
Melbourne on **17870** at 0617, OM with horse racing commentary in English, the programme presumably intended for African consumption.
- **PAKISTAN**
Karachi on **15115** at 1047, local songs and music in the World Service programme directed to the U.K. in Urdu, scheduled from 0830 to 1100. A newscast in English read at slow-speed followed at 1100 after station identification. Also heard in parallel on **17665**.
Karachi on **21590** at 1115, OM and YL alternate in the Burmese programme for Burma (where else!) scheduled from 1100 to 1200. Identification in English and sign-off at 1200.
- **MALAYSIA**
Tebrau (BBC Relay) on **3915** at 1824, OM with a commentary on world affairs in English. This transmitter relays programmes in Burmese, Chinese, Indonesian and Vietnamese in addition to English. The schedule is from 1000 to 1100, 1130 to 1445, 2230 to 2345; the English programmes being from 1500 to 1830.
- **WEST GERMANY**
"Radio Deutsche Welle — the Voice of Germany", Cologne, on **15150** at 1945, OM with the history of Morocco in English in a programme for African consumption. Station identification and sign-off (English programme) at 2000. This transmission can also be heard in parallel on **9765** and **11905** and is scheduled from 1930 to 2000.
VOA Munich on **3980** at 0300, station identification and a newscast in English.
- **BULGARIA**
Sofia on **9700** at 1938, OM with local news in the English programme directed to the U.K. from 1930 to 2000; also in parallel on **11720**.
- **CONGO**
RTV Congolaise, Brazzaville, on **4765** at 2130, identification and announcements in English by OM, local newscast in English until 2145.
- **CHINA**
PLA Fukien Front on **4330** at 2049, YL in Chinese in the Network 1 programme intended for Taiwan and Offshore Islands scheduled from 1058 to 0155.
PLA Fukien Front on **4380** at 2250, Chinese orchestral music in the Amoy Network 2 programme to Taiwan and Offshore Islands scheduled from 0230 to 1900.
Radio Peking on **3920** at 2104, OM in Chinese in the Home Service 1 programme, scheduled on this channel from 1100 to 1735 and from 2000 to 0100.
Radio Peking on **4460** at 2104, YL in Chinese in the Home Service 1 programme, scheduled here from 2000 to 2315.
Radio Peking on **9860** at 1751, Chinese orchestral music in the English programme for East and South Africa, scheduled from 1700 to 1800.
- **CAMEROON**
Yaounde on **4925** at 2051, local music and songs, identification in French at 2100. Also in parallel on **4750**. Listed **4972** but no trace of this channel at the time the foregoing transmissions were logged.
- **LIBYA**
Mebo II (a ship anchored off the Libyan coast) on **6206** at 2031, U.K. pop records with announcements in English. Test transmission announced until 2300.
- **NORTH KOREA**
Radio Pyongyang on **6575** at 2115, YL in the English programme to Europe, scheduled from 2000 to 2150.
Radio Pyongyang on a measured **11533** at 1820, OM in the Arabic programme intended for Africa and the Middle East, scheduled from 1700 to 1900. Also logged in parallel on a measured **6338**.
- **VENEZUELA—2**
Radio Tachira, San Christobal, on **4830** at 0005, a programme of pops in the local style, OM announcer in Spanish. The schedule is from 1000 to 0500 and the power is 10kW.
Radio Popular, Maracaibo, on **4810** at 0305, YL with love song (they also have their troubles apparently!) in Spanish, guitar music, identification 0315. Schedule is from 1000 to 0500 and the power is just 2kW.
- **NOW HEAR THIS**
Radio Alfonso Padilla Vega, Padilla, Bolivia, on a measured **3481** at 0150, YL with songs in Spanish, OM announcer. The schedule is from 2215 to 0245 (Sundays until 0200) and the power is 0.3kW.

SIMPLE LOCATOR

R. A. n




Back garden treasure hunting. Wielding the metal locator is the author's brother, photographer J. W. Penfold

- ★ A low cost design offering adequate depth metal and pipe detection
- ★ There are only two active devices in the circuit: a field-effect transistor and a CDS

The metal locator which forms the subject of this article has been designed to incorporate a minimum of components and to be as simple to use as possible. It has only two active components: a field-effect transistor and an operational amplifier. The presence of a metal object in the vicinity of the search coil is indicated by an increase in the deflection of the meter which is fitted to the unit. Power is obtained from an internal 9 volt (PP3) battery, and the detector is thus completely self-contained.

When one considers the simplicity of its circuit the detector performs quite well, but it would be naive to expect it to have a performance equal to that of a multi-transistor unit costing several times as much. Small objects, about the size of a 5p piece, can be detected at depths of up to about 1in. or so. Larger objects can be detected at greater depths, with the absolute maximum being about 1ft. for a fairly large and thick sheet of metal. It should be pointed out that although metal detectors having a meter to monitor the output are easier to use than the more common b.f.o. types, with which the presence of a metal object is indicated by a change in the pitch of an audio output tone, a certain amount of skill is still needed in order to obtain optimum results. This is really just a matter of practising sufficiently with the detector.

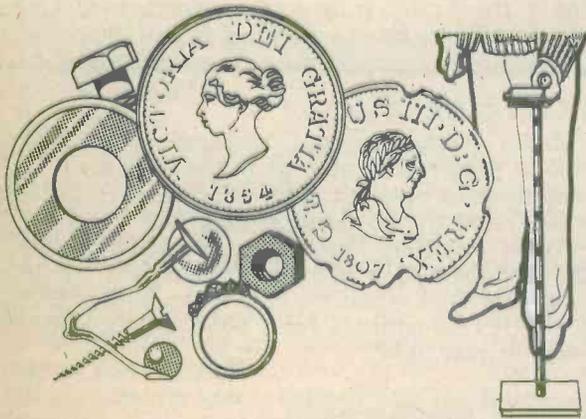

METAL ATOR

By
Penfold

quate sensitivity for general pur-

eg in the circuit, these being a
MOS operational amplifier.


OPERATING PRINCIPLE

If a piece of metal is placed near an unscreened coil, there will be a small change in the inductance of that coil. It is on this basic principle that most metal detectors operate.

Probably the most common method of detecting the change in inductance is to use the search coil in an r.f. oscillator whose output is heterodyned with a second, reference frequency, oscillator. The resultant beat note is at an audio frequency which alters as the search coil inductance changes.

A different and even simpler method is to once more use the search coil in an r.f. oscillator circuit but, this time, to monitor the d.c. bias level in the oscillator by means of a sensitive voltmeter. It may not be appreciated by some readers that the biasing of an oscillator is not completely controlled by the values of the bias components. For example, an oscillator circuit which has the feedback path open and is therefore not oscillating may draw a supply current of say, 2mA; if the feedback path is closed so that oscillation takes place the consumption may decrease or increase considerably according to the type of circuit used. Similarly, changes in operating frequency may alter current consumption and also vary the circuit potentials. This is the system which is employed in the present design.

DECEMBER 1977

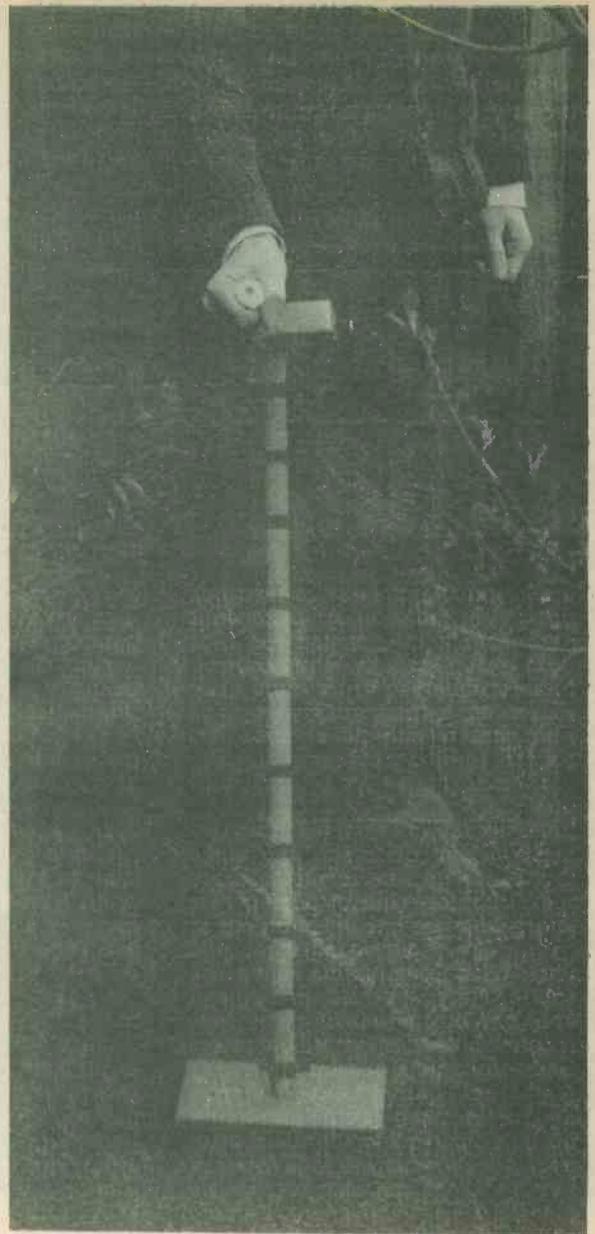

The simple metal locator in use. Its neat design enables it to be easily carried whilst observing the meter, and yet the requirements for constructing the wood and hardboard framework are minimal

LICENCE

It is necessary to obtain a Pipe Finder/Metal Detector Licence before the metal locator may be used, and an application form for this can be obtained from The Home Office, R1 Division, Radio Regulatory Department, Waterloo Bridge House, Waterloo Road, London SE1 8UA. The expression "Home Built" should be entered in Section 3(ii) of the application form and the equipment may be described as "Metal Locator, R. & E. Constructor, December 1977". The operating frequency should be entered in the application form as "75kHz". As was mentioned earlier, the operating frequency must not exceed this figure. The licence fee at the time of writing is £1.20, and the licence is valid for 5 years from the date of issue.

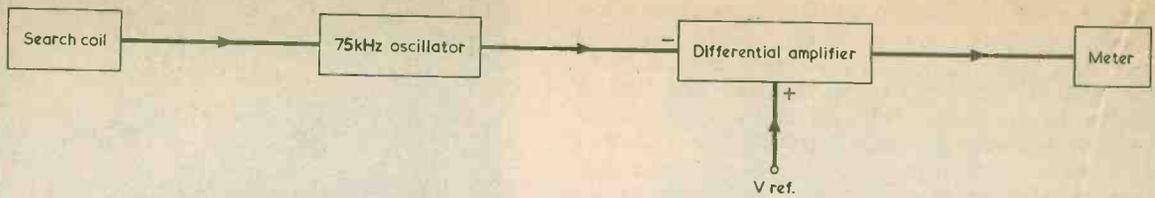


Fig. 1. Block diagram illustrating the sequence of operation of the metal locator. As the search coil approaches a piece of metal its inductance changes, causing a fall in oscillator bias voltage. This fall in voltage is amplified by the differential amplifier to give a corresponding deflection in the meter

A block diagram of the metal locator is shown in Fig. 1. The oscillator has to operate at a frequency within the range of 16 to 150kHz, except for the band 90 to 110kHz, as otherwise the unit cannot be licensed in the U.K. and it would be illegal to use it. In the present metal locator the oscillator operates at a frequency of 75kHz. The operating frequency must not exceed 75kHz, and this fact will be assured by carefully following the coil winding details which are given later.

At a suitable take-off point a potential from the oscillator is fed to the inverting input of a high gain differential amplifier. The non-inverting input of the differential amplifier is connected to a reference voltage which is very slightly higher (i.e. more positive) than the normal output voltage from the oscillator. The output voltage of the differential amplifier is equal to its voltage gain multiplied by the voltage difference at its inputs. If the inverting input voltage is fractionally lower than that at the non-inverting input there is a small output voltage from the differential amplifier, this

causing a slight deflection of the meter connected to that output. It should be noted that the gain of the differential amplifier is extremely high and that the voltage across its inputs is extremely small.

When a piece of metal is placed near the search coil the operating frequency of the oscillator is slightly increased, giving a corresponding reduction in the output voltage passed to the differential amplifier. The voltage difference at the inputs of the differential amplifier increases, resulting in an increase in the deflection of the meter. In general the changes in the output potential of the oscillator are of a very small order, but they are greatly amplified by the differential amplifier and therefore produce a significant meter deflection.

THE CIRCUIT

As can be seen from the circuit diagram in Fig. 2, few components are required for the metal locator. TR1 is the oscillator transistor, and this field-effect device is connected in the common drain

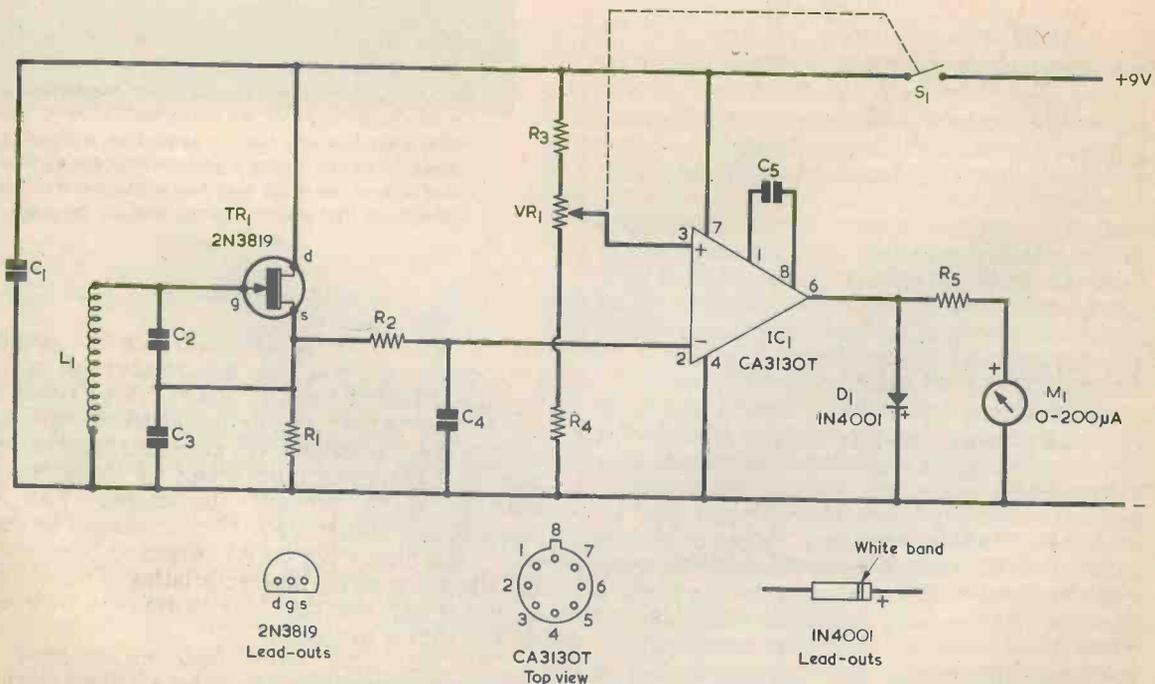


Fig. 2. Few components are required for the metal locator, as is evident from this circuit diagram. In the inset showing the 2N3819 lead-outs, the lead-outs point towards the reader. On the other hand, the CA3130T lead-outs point away from the reader

mode, or source follower configuration as it is often termed. R1 is the source load resistor and the search coil, L1, provides a bias path for the transistor gate. C2 and C3 in series form the tuning capacitance for the search coil and also provide a capacitive tap into the tuned circuit. The source of TR1 connects to this tap, which provides the necessary positive feedback for the circuit to oscillate.

The output voltage from the oscillator is taken from TR1 source and is connected to the inverting input of the differential amplifier by way of R2, which forms an r.f. filter in conjunction with C4. The differential amplifier is an i.c. operational amplifier type CA3130T. The reference voltage at its non-inverting input is obtained from a potential divider consisting of R3, VR1 and R4. VR1 is adjusted to provide a small deflection of the output meter. C5 is the compensation capacitor for the CA3130T.

It is not desirable to feed the meter direct from the i.c. output without some means of overload protection since the i.c. can provide quite a high output current which could easily damage the

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

- R1 4.7k Ω
- R2 100k Ω
- R3 3.3k Ω
- R4 560 Ω
- R5 470 Ω
- VR1 5k Ω potentiometer, linear, with switch S1

Capacitors

- C1 0.1 μ F type C280 (Mullard)
- C2 0.001 μ F ceramic plate
- C3 0.0068 μ F polyester or polystyrene
- C4 0.015 μ F type C280 (Mullard)
- C5 220pF ceramic plate

Inductor

- L1 search coil (see text)

Semiconductors

- IC1 CA3130T
- TR1 2N3819
- D1 1N4001

Meter


- M1 0-200 μ A level meter (see text)

Switch

- S1 s.p.s.t. toggle, part of VR1

Miscellaneous

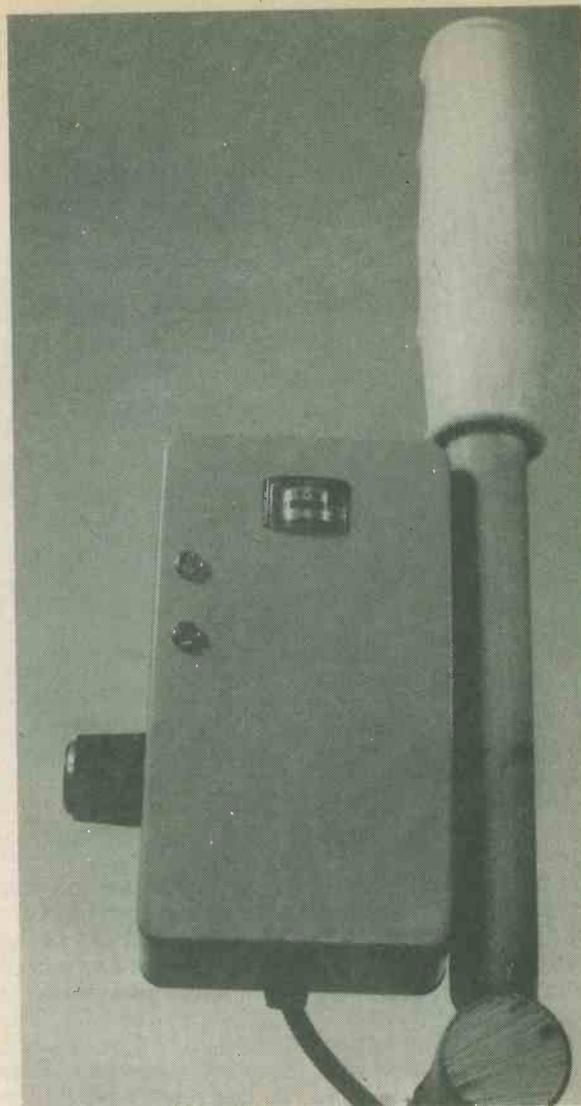
- Plastic case type DC2 (see text)
- 38 s.w.g. enamelled copper wire (for L1)
- 9 volt battery type PP3 (Ever Ready)
- Battery connector
- Control knob
- Veroboard, 0.1in. matrix
- Veropins (see text)
- Wood, hardboard, etc., for frame
- 2-core flex (see text)
- Solder, wire, etc.



The metal locator electronics are housed in a small plastic case screwed to one side of the handle. At the top can be seen the indicating meter. The two screw heads which are visible are those of the 6BA screws which secure the Veroboard component panel inside the case

meter. Silicon diode D1 provides the protection required because it becomes conductive when the voltage across it reaches about 0.5 volt and limits any further significant positive excursion of the i.c. output. Series resistor R5 provides further protection and the combined effect of these two components is to prevent the meter from being dangerously overloaded. The i.c. cannot be damaged by the limitation on its output voltage given by D1 since one of the characteristics of the CA3130T is that it can withstand an output short-circuit for an indefinite period.

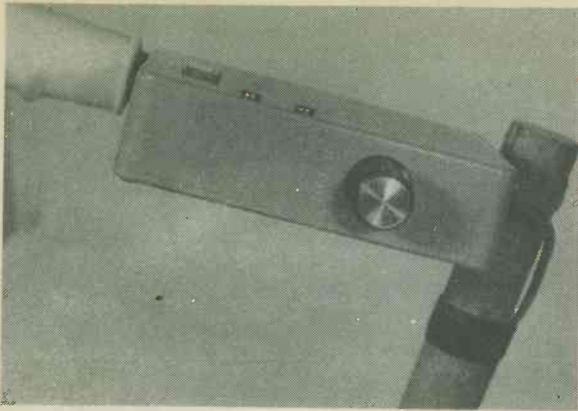Readers who have had experience with operational amplifiers may be a little surprised at the fact that it is possible to resolve a near-zero output from the open-loop CA3130T by means of a simple standard potentiometer at the non-



Potentiometer VR1, which provides the reference voltage for the differential amplifier, is mounted on the side of the plastic case

inverting input. However, the comparator circuit is a little less critical than would be expected at first sight because the voltage from the oscillator at the inverting input is not pure d.c. but has a small amount of residual a.c. on it. This tends to "broaden out" the adjustment settings in VR1. The setting of this potentiometer is still rather critical, however, and more experienced readers may, after they have become used to the operation of the metal locator, ease this effect by experimentally increasing the value(s) of R3 and/or R4 as required with their particular unit. The values specified for R3 and R4 in the Components List nevertheless allow satisfactory operation to be achieved.

S1 is the on-off switch and is ganged with VR1. C1 provides the only supply decoupling which is required. The circuit has a current consumption from the 9 volt battery of approximately 3mA only.

COMPONENTS

Most of the components are standard types, but a few require additional comment. The meter employed for M1 is a 0-200 μ A level meter, and a suitable type here is the miniature level meter available from Maplin Electronic Supplies. This has dimensions of 23 by 22 by 26mm. and an internal resistance of 1,200 Ω . The metal locator components are housed in a plastic case with approximate dimensions of 111 by 60 by 27mm. The plastic case type DC2, also available from Maplin Electronic Supplies, will be satisfactory here. The search coil connects to the remainder of the electronics by a length of 2-core flex. Although the self-capacitance of this flex is largely swamped by C2 and C3, it would be preferable to employ the same type as that used in the prototype. This is twin p.v.c. covered flexible cable with a "figure 8" section, normally recommended for loudspeaker connections and having a current rating of 2 amps.

WOODWORK

Details of the wooden structure for the metal locator are shown in Fig. 3. Commence by cutting out the three pieces of hardboard which form the basis of the search coil. 3mm. thick plywood may alternatively be employed. The 7 by 5in. piece is positioned centrally between the two 8 by 6in. pieces, so that the latter overlap by $\frac{1}{2}$ in. all round. These three parts are glued together using a generous amount of a good adhesive. The pole section is a length of 1in. diameter timber such as a piece of broom handle. This is cut to length and the lower end is cut to the specified angle before it is screwed to the search coil former.

The handle consists of a piece of round dowel about 10in. long overall. This is filed down to about $\frac{3}{8}$ in. diameter at one end so that it will fit into a hole of the same diameter drilled in the upper part of the pole. The handle is glued to the pole.

The search coil consists of 100 turns of 38 s.w.g. enamelled copper wire wound around the middle of the three hardboard pieces which make up the former. A small hole is drilled at the centre and towards the rear of the upper one of the three pieces, and two short lead-out wires are passed through this. The wooden framework and the coil are then varnished. It should be noted that the coil will not give its final correct performance until the varnish has dried and set.

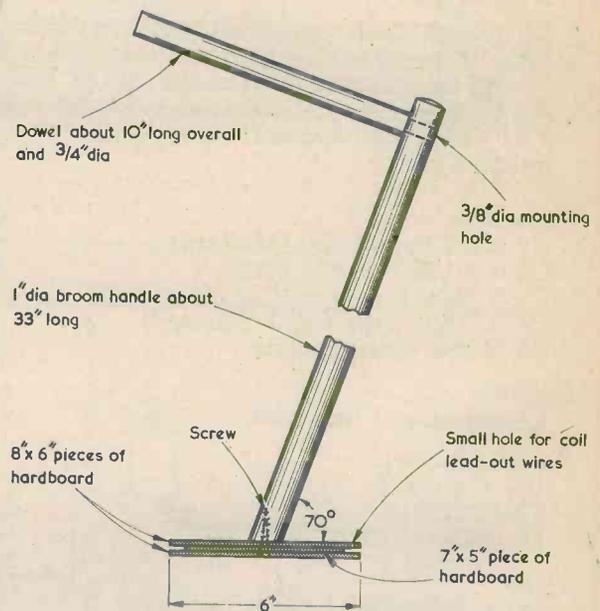


Fig. 3. The wood and hardboard sections of the metal locator

CONSTRUCTION

Most of the components are assembled on a piece of Veroboard of 0.1in. matrix having 21 holes by 9 copper strips. This panel is illustrated in Fig. 4, which also shows details of the other wiring. A panel of the appropriate size is cut out with a hacksaw, after which the two 6BA clear holes are drilled out. Next the 9 breaks in the copper strips


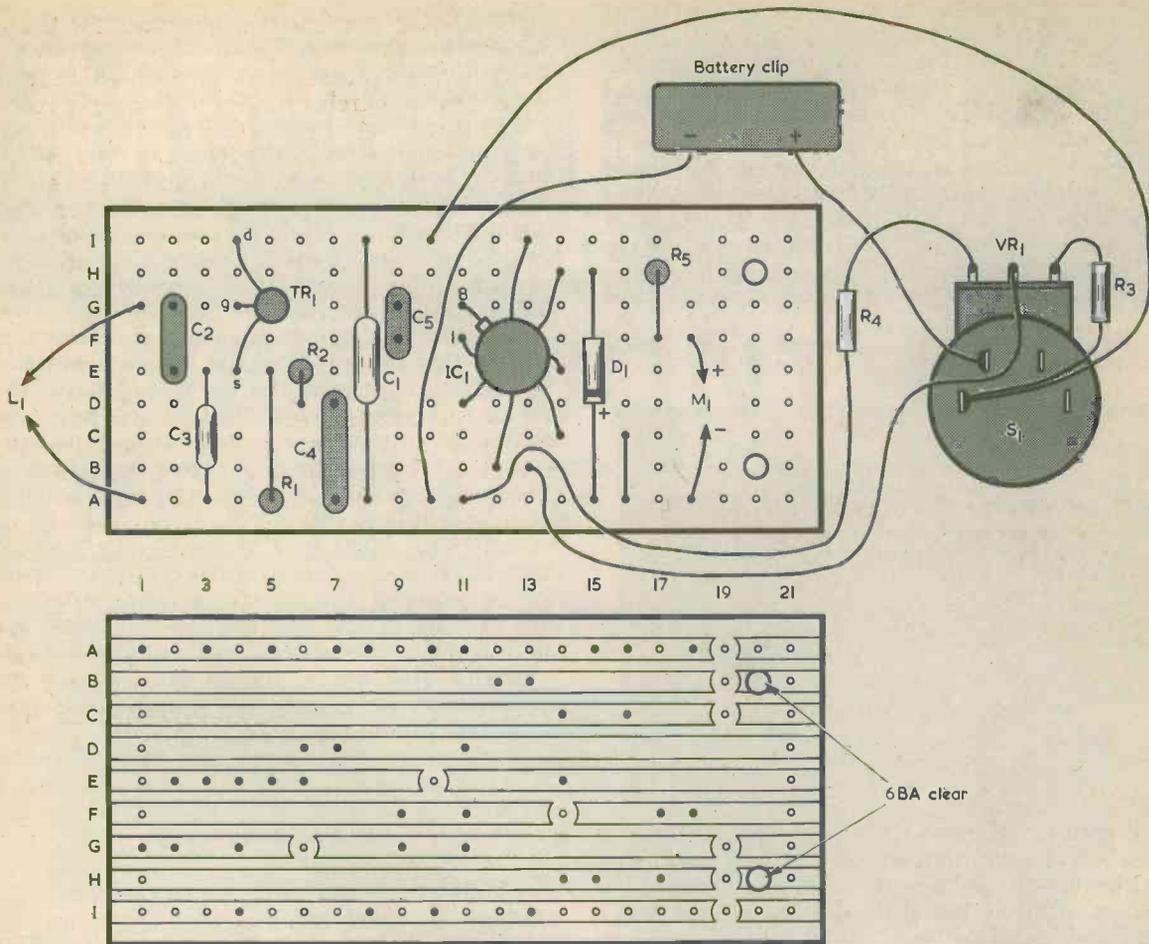


Fig. 4. Most of the components are assembled on a Veroboard panel. This diagram shows the component and copper sides of the panel

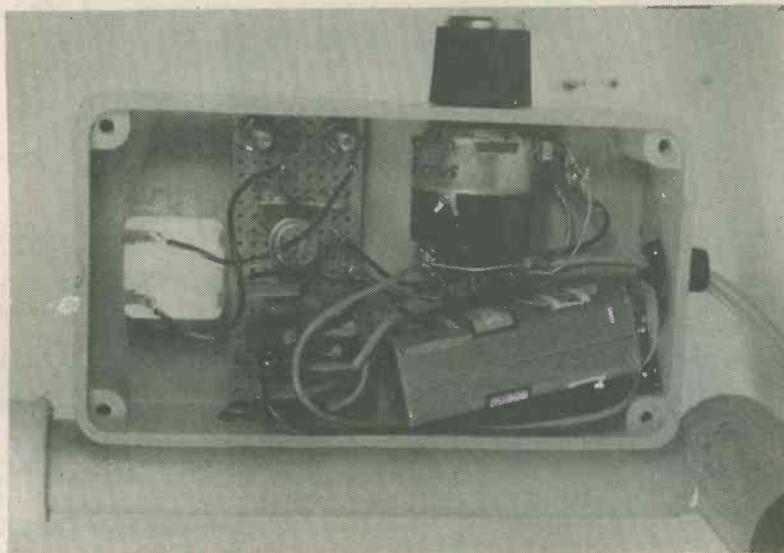

The plastic case with cover removed. There is ample space for the meter, the component panel, the potentiometer and switch, and the battery

are made after which the components are soldered in position. Although not essential it helps considerably to solder in Veropins suitable for 0.1in. Veroboard at the points where external connections are made. Since IC1 is a CMOS device it is essential that all soldering be carried out with an iron having a reliably earthed bit.

The plastic case is secured on the left hand side of the handle by means of two woodscrews passed through holes drilled in the case side. The relative positions of the case and the handle are clearly shown in the photographs. The case lid is on the



A closer look at the component panel. Most of the few components which are required for the metal locator are assembled on this

plastic grommet. The wire to the search coil passes through this.

The easiest method of assembly consists of making all the holes required in the case and of then fitting the meter, VR1/S1 and the grommet. The case is then screwed to the wooden handle, after which the assembled Veroboard panel is mounted with two 6BA bolts and nuts. Short spacing washers are fitted over the bolts between the panel and the inside case surface. The final wiring is then completed. It will be observed that R4 is wired between the panel and VR1, and that R3 is wired between VR1 and S1. When the case lid is secured in place, a piece of foam rubber or plastic between the lid and the battery will hold the latter in place.

The twin wire from the Veroboard panel to the search coil passes down the wooden pole and is secured at intervals by insulating tape wound around the two. A piece of tape also secures it to the top of the coil former at the point where it connects to the coil lead-outs. This piece of tape protects the joints and prevents any accidental short-circuits. If a more robust method of connection is required the junctions may be insulated with tape and held down with a soft plastic homemade clamp secured with two small woodscrews.

Finally, the metal locator will be very much easier to use and control if a handlebar grip is fitted to the handle. Such a grip should be available at any cycle shop. The grip will probably be found to be an extremely loose fit, and this situation can be rectified by wrapping a few layers of insulating tape over the handle.

TESTING

When the unit has been switched on, there should be no deflection of the meter until VR1 is sufficiently advanced clockwise. There is only a very limited range of adjustment in VR1 between the positions which give nil deflection and full-scale deflection of the meter needle, and VR1 needs careful setting up in order to produce an intermediate reading. The meter can be set up for approximately half f.s.d. or less, and a positive meter deflection should be produced when the search coil is placed near a metal object. The metal locator is then ready for use.

underside, so that the meter is mounted in what would conventionally be considered the bottom surface of the case. The meter requires a small rectangular mounting hole which can be made with a fretsaw or a miniature file. The meter can be held in place as a tight push fit or it can be secured with adhesive. Two 6BA clear holes for mounting the Veroboard panel are also required in this surface of the case. The meter is positioned near the top end of the case (i.e. furthest away from the wooden pole) with the board immediately below it. VR1/S1 is positioned with its body below the Veroboard panel on the side opposite that which is secured to the handle, and the battery fits into the remaining space below the panel. The layout can be clearly seen from the photographs of the case. A hole of about $\frac{5}{16}$ in. diameter is drilled at the bottom of the case and is fitted with a rubber or




"It's on the floor somewhere, I can still hear it playing!" — "You'd better build the metal locator in R. & E. C.1"

RADIO & ELECTRONICS CONSTRUCTOR

NEXT MONTH'S SPECIAL FEATURES

THE "DUETTE" STEREO AMPLIFIER

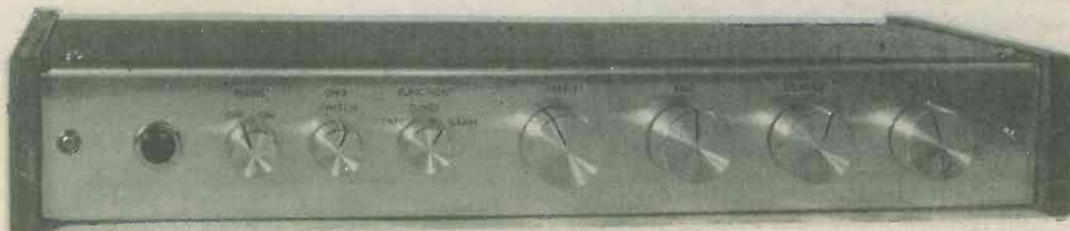


2 WATT OUTPUTS FROM ONE CHIP

- Simple Circuitry incorporating LM377 I.C.
- High Quality
- Suitable for Gram, Tuner and Tape Inputs

PHOTOFLASH SLAVE UNIT

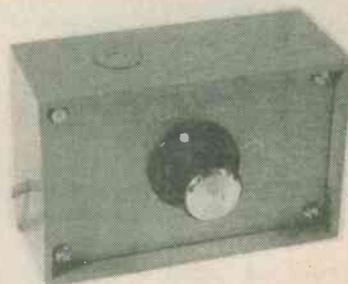A highly sensitive and quick-acting unit which causes a second electronic flashgun to be triggered by a primary photoflash



MANY OTHER ARTICLES

ON SALE 2nd DECEMBER Avoid disappointment. ORDER NOW

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is 58p, inclusive of postage and packing.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

OP-AMP TRANSISTOR TESTER

By
D. V. Henderson

A low cost circuit which enables the current gain of small-signal silicon transistors to be measured with a high degree of accuracy.

The transistor tester whose circuit is described in this article employs no meter yet gives accurate indications of current gain for small-signal silicon bipolar transistors. Equally accurate indications are possible with germanium small-signal transistors when these have low leakage currents. Gain measurement is made at a collector current of about 4mA with about 4 volts between the collector and emitter of the transistor being tested. Germanium and silicon power transistors may also be checked, bearing in mind that the test is being carried out at a relatively low collector current.

OPERATING PRINCIPLE

The principle of operation of the tester can be introduced by means of the circuit shown in Fig. 1(a). Here, a 9 volt supply is coupled to an n.p.n. transistor under test, which is connected as an emitter follower. The emitter load resistor, R_1 , has a value of $1k\Omega$ and the base connects to the positive rail via a $1M\Omega$ variable resistor, VR_1 . If we assume that there is zero voltage drop in the

base-emitter junction of the transistor then it becomes possible to adjust VR_1 such that 4.5 volts is dropped across R_1 , with a further 4.5 volts dropped across VR_1 .

The current flowing in VR_1 is equal to the current in R_1 divided by the current gain of the transistor in the emitter follower mode. Since equal voltages are dropped across the two resistors it follows that the current gain becomes equal to the resistance inserted into circuit by VR_1 divided by the resistance of R_1 . This last resistor has the round figure value of $1k\Omega$, whereupon the current gain of the transistor is equal to the number of kilohms inserted into circuit by VR_1 . If VR_1 inserts $100k\Omega$ the transistor has a current gain of 100 times, should VR_1 insert $200k\Omega$ the gain is 200 times, and so on.

A simple example will illustrate this relationship. The current flow in R_1 when there is 4.5 volts across it is 4.5mA. If the transistor has a current gain of 100 times the base current flowing via VR_1 is 0.045mA. The resistance inserted into

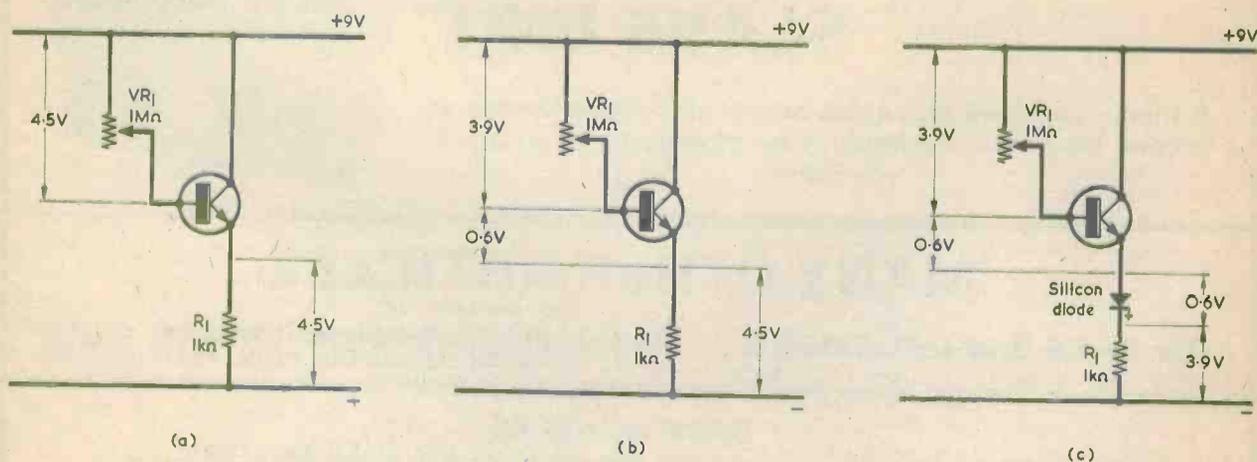


Fig. 1(a). Assuming zero voltage drop across the base-emitter junction of the transistor, VR_1 can be set up to give the voltages shown here
 (b). In practice there is a significant voltage drop across the base-emitter junction of a silicon transistor
 (c). The voltage drop can be compensated for by inserting a silicon diode in series with the emitter. VR_1 may now be adjusted for a symmetrical voltage pattern

circuit by VR1 has 4.5 volts dropped across it and must therefore, from Ohm's Law, be equal to 4.5 volts divided by 0.045mA. This works out as 100k Ω . If the transistor has a current gain of 200 times the voltage conditions in Fig. 1(a) are given when VR1 inserts 200k Ω because, obviously, the base current now required is half that for the previous example.

To sum up, we can find the current gain of the transistor in Fig. 1(a) by adjusting VR1 so that 4.5 volts appears across R1. The current gain of the transistor is then equal to the number of kilohms inserted by VR1. If this variable resistor has a scale which has been previously calibrated with the aid of an ohmmeter, we can read off the transistor current gain directly from the scale.

For the circuit of Fig. 1(a) to be of use it is necessary to monitor the voltage across R1. This can be done by connecting a voltage comparator to the emitter of the transistor. If we have the voltage comparator give an indication when the voltage at the emitter is precisely half that of the supply then the same relationship between the resistance inserted by VR1, the resistance of R1 and the current gain of the transistor will hold good at supply voltages other than 9 volts. The supply will not then need to be stabilized and can consist of a 9 volt battery which is discarded when its voltage falls to, say, 7 volts. For the time being, however, we shall continue our explanation with a supply of 9 volts.

A further point is that we are talking in terms of the current gain of the transistor when used as an emitter follower. This can be considered as being virtually equal to hFE, the static base to collector current gain of the transistor. Actually, it is equal to hFE + 1 because both the collector and base currents flow in the emitter. For transistor gains above 50 or so, the + 1 factor can be ignored.

SILICON TRANSISTORS

In Fig. 1(a) we assumed that there is zero volts drop across the base-emitter junction of the test transistor. With germanium transistors there is, in practice, a voltage drop of about 0.15 volt. This is sufficiently small when compared with the other voltages in the circuit to be considered negligible, whereupon the circuit as it stands is suitable for finding the current gain of germanium transistors. Some small-signal germanium transistors have leakage currents which could cause inaccurate gain readings to be given, although the later production of these devices seems to be relatively free from this shortcoming. In any event, germanium transistors are largely disappearing from the electronic scene, and silicon transistors do not give any serious difficulties so far as leakage currents are concerned.

On the other hand, silicon transistors exhibit a relatively high forward voltage drop across the base-emitter junction, and this is large enough to be a significant factor here. Typically, the voltage drop is about 0.6 volt. If we put a silicon transistor in the circuit of Fig. 1(a) and set up VR1 for 4.5 volts at the emitter we will obtain voltage figures similar to those shown in Fig. 1(b). There will now be 0.6 volt across the base-emitter junction of the transistor and only 3.9 volts across VR1. The voltages across R1 and VR1 are manifestly dissimilar and their previous relationship with transistor current gain no longer holds good.

A solution is shown in Fig. 1(c), in which a forward biased silicon diode is inserted between the transistor emitter and R1. This diode will give a voltage drop of around 0.6 volt whereupon, when VR1 is adjusted for 4.5 volts at the transistor emitter, the voltages in the circuit will be those shown in the diagram. Both VR1 and R1 have equal voltages across them, with the result that the resistance inserted by VR1 once more becomes equal to R1 multiplied by the current gain of the transistor. In practice the voltage across the diode will be slightly higher, by about 0.1 volt, than the voltage drop in the base-emitter junction, but the error introduced will be much less than if the diode were omitted. An advantage given by the inclusion of the diode is that the voltages around the central voltage point now become symmetrical, and a voltage comparator working to half supply voltage can be coupled to the transistor emitter. The circuit will then allow accurate gain measurements to be made at supply voltages other than 9 volts, and no inaccuracies will result due to falling battery voltage.

FULL CIRCUIT

The full circuit of the op-amp transistor tester appears in Fig. 2, where it will be seen that the voltage comparator is a 741 operational amplifier. This has its non-inverting input connected to the emitter of the test transistor, and its inverting input to the junction of the two equal value resistors R3 and R4. Thus, when the non-inverting input goes positive of the half-supply voltage the i.c. output goes highly positive, and when the non-inverting input goes negative of half-supply voltage the output goes highly negative. In the first state the red light-emitting diode, LED2, is illuminated, and in the second state the green l.e.d., LED1, is lit

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 5% unless otherwise stated)

- R1 1k Ω 2%
- R2 18k Ω
- R3 10k Ω 2%
- R4 10k Ω 2%
- R5 470 Ω
- R6 470 Ω
- VR1 1M Ω potentiometer, linear

Semiconductors

- IC1 741 in 14 pin d.i.l.
- D1-D4 1N4002
- LED 1 light-emitting diode, green
- LED 2 light-emitting diode, red

Switches

- S1 s.p.s.t., toggle
- S2(a)(b)(c) 3-pole 3-way, rotary

Battery

- BY1 9 volt battery

Miscellaneous

- 3 terminals
- 2 pointer control knobs
- Suitable plastic case

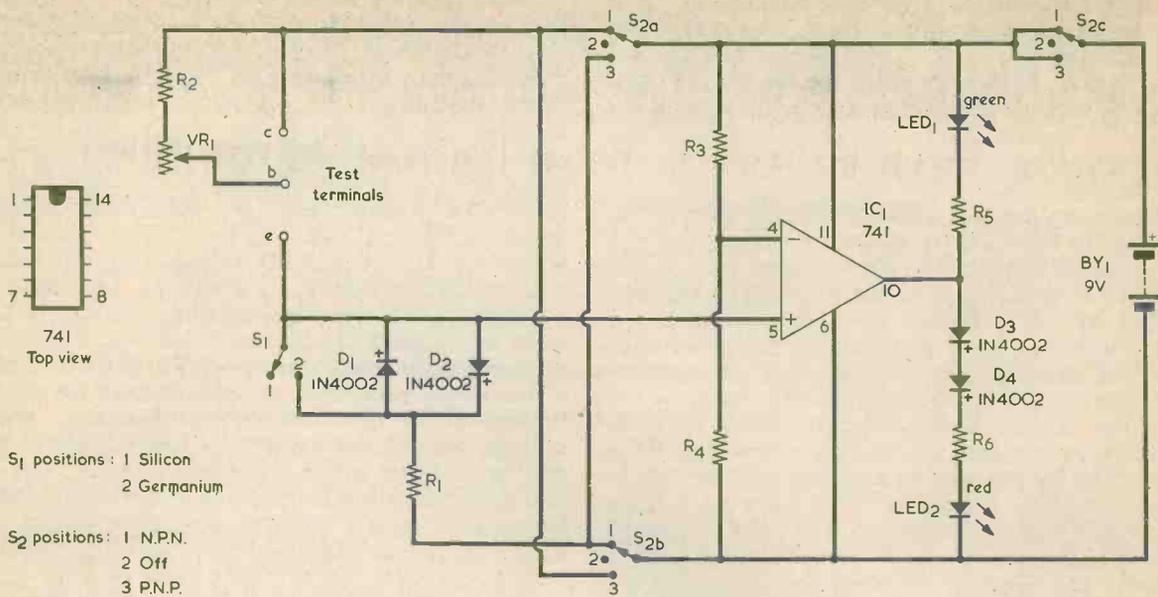


Fig. 2. The circuit of the op-amp transistor tester. This can be assembled in any convenient plastic box large enough to take the 9 volt battery and the components

up. Silicon diodes D3 and D4 are inserted in series with the feed to LED2 because, in its low state, the 741 output is still about 2 volts positive of the negative supply rail. Without the two diodes and their forward voltage drop the red l.e.d. would be partly illuminated when the 741 output is low.

VR1 and R1 carry out the same function as they did in Fig. 1. R2 is now, however, inserted in series with VR1 to limit the maximum current which can flow in the potentiometer to 0.5mA. This protects the potentiometer and the transistor under test. The diode in series with the emitter in Fig. 1(c) now appears as D2. D1, connected across it with reverse polarity, caters for the situation when p.n.p. transistors are being tested. When S1 is in position 1, the two diodes are in circuit and the tester can be used to check silicon transistors. Putting S1 to position 2 short-circuits the diodes and the tester may then be employed for germanium transistors.

S2(a) and S2(b) give supply polarity reversal. In position 1 the upper test transistor rail is positive and the lower rail is negative. Setting the switch to position 3 reverses the polarities. On-off switching is achieved with S2(c). It is necessary to have a central "Off" position because most rotary switches have a make-before-break action. If the polarity reversing switch employed adjacent fixed contacts on a rotary switch the battery would be momentarily short-circuited each time the switch was operated.

VR1 has a scale calibrated in terms of transistor gain. This is marked up by connecting an ohmmeter between the slider of VR1 and the upper end of R2, so that the resistance of R2 as well as that inserted by VR1 is taken into account. The scale is marked "100" at 100k Ω , "200" at 200k Ω and so on. Intermediary markings at "150", "250", etc., may also be entered on the scale, if desired.

VR1 should be wired up to insert zero resistance into circuit when its spindle is turned fully anti-clockwise. The numbers on the scale will then increase with clockwise rotation.

All the components are readily available. VR1 is a standard carbon potentiometer and could, with advantage, be a moulded track type. Switch S2(a)(b)(c) is specified as 3-pole 3-way. A 4-pole 3-way switch can be used here, with no connections made to one of the poles. The current consumption of the tester is about 10mA with a test transistor connected and VR1 adjusted; in consequence the 9 volt battery may be a PP6 or a larger type, such as the PP9. The 741 is shown in the 14 pin d.i.l. form. The 8 pin d.i.l. version may alternatively be employed. This has its inverting input at pin 2, its non-inverting input at pin 3 and its output at pin 6. Positive and negative supplies connect to pins 7 and 4 respectively.

To check the gain of a transistor this is connected to the test terminals with VR1 set to insert maximum resistance. S1 and S2 are then set to the appropriate positions. With an n.p.n. transistor the green l.e.d. will light up. VR1 is then turned slowly anti-clockwise until a setting is reached where the green l.e.d. extinguishes and the red l.e.d. lights up. The current gain of the transistor is then read off from the scale of the potentiometer. With a p.n.p. transistor the red l.e.d. will be initially lit, giving way to the green l.e.d. when VR1 slider reaches the appropriate point along its track. Due to the very high gain of the 741 op-amp it will be virtually impossible for VR1 to resolve a setting at which both l.e.d.'s are alight. VR1 need only be adjusted to the position at which changeover takes place.

No harm will result if VR1 is adjusted to a low resistance, if the test terminals are short-circuited or if the test transistor is connected incorrectly. All the currents which can flow are limited to safe values by R1 and R2. ■

Trade News . . .

MINIATURE WELDING TORCH FROM BRITISH ROTOTHERM



This precision engineered miniature welding torch — believed to be one of the smallest units of its type commercially available — is now being marketed in this country by The British Rototherm Company Limited, the sole U.K. agents.

A precision engineered welding torch, which is expected to find wide application in electronics, is now being marketed in this country by The British Rototherm Company Limited, the sole U.K. agents.

Manufactured by the Tescom Corporation of the U.S.A. and aptly named "The Little Torch" it is not much larger than a fountain pen yet boasts the capabilities of more conventional welding and soldering equipment whilst having a considerably higher degree of accuracy.

Its ability to solder, weld or braze components as fine as .001 in. wire makes it particularly suitable for many applications in electronics. In the United States it is currently used for such tasks as repairing vacuum tubes, soft soldering silver wire in diodes and 'balling' 0.001 in. gold wire. In many applications of this type "The Little Torch" has replaced a more expensive process such as electric welding or is operating at a faster rate than a conventional soldering iron.

With tip orifice sizes as small as 0.003 in., which are jewelled for precise flame control, and flame temperatures up to 6300 deg. F. it can weld, solder and braze to such tolerances that it can be safely used in areas where in the past the risk of heat damage to adjacent components would have precluded the use of a torch.

From the operator's point of view its compact size, lightweight aluminium alloy body and interchangeable tips, which swivel through 360 deg., allow it to be handled very precisely in confined situations.

It operates on oxygen and a range of fuel gases including acetylene, hydrogen, l.g.p. and natural gas at pressures from 2 to 4 lbs./sq. in. Gas consumption ranges from 0.023 to 2.54 cub. ft.hr.

Surprisingly, "The Little Torch" is not expensive. British Rototherm expect to sell it complete with case, five tip sizes and 6 ft. of twin hose for less than £30.00.

Further information on "The Little Torch" can be obtained direct from The British Rototherm Co. Ltd., Margam, Port Talbot, West Glamorgan, South Wales, SA13 2PW.

WIRE STRIPPING HAND TOOL

Eraser International have available from stock in London, the Rush model PD2 wire stripping hand tool.

The Rush model PD2 wire stripper is designed to strip round, square and rectangular wire up to gauges of 2 SWG.

The PD2 is designed for stripping film type insulations from wires commonly used in transformers and electric motors. It will also strip wires insulated with asbestos and glass type coverings. Wires are stripped by a brushing action generated by two counter rotating wire brush wheels.

The machine is fully adjustable for different wire sizes and is ideally suited for production use.

Further information is available from Eraser International Ltd., 213 Hampton Court Parade, East Molesey, Surrey, KT8 9HB.



ENGINEER'S RESISTOR PACK

The home constructor or service engineer can now buy his resistors in quantity from Home Radio in the form of an Engineer's Resistor Pack. Values from 4.7Ω to $1.5\text{ M}\Omega$ (20 of each) are separately packed in individual clear plastic tubes. There are additional resistors of the more popular values making a grand total of 1600 in all. The resistors are mostly 5% tolerance and either $\frac{1}{4}$ or $\frac{1}{2}$ W rating. Each tube is clearly marked and the backing cards can be left in the original box supplied to give quick access to any value of resistor required. The Pack costs £17.50 plus 12½% VAT plus 85p post, packing and insurance. Available from Home Radio (Components) Ltd., 234 London Road, Mitcham, Surrey CR4 6HD.

MODIFIED MAINS CURRENT MONITOR

by T. K. Wong

There is no risk of leaving mains operated bench equipment switched on if this current monitor is inserted in the bench supply. Its l.e.d. warning lamp lights up for even very small mains currents.

A mains current monitor which causes an l.e.d. to be lit whenever any current is drawn from the a.c. mains was described in the "Suggested Circuit" which appeared in *Radio and Electronics Constructor* for December 1976. The present article describes an improved current monitor which has been developed from the previous circuit.

ORIGINAL CIRCUIT



For convenience, the earlier circuit is reproduced in Fig. 1. The mains transformer primary in this is connected permanently across the mains supply and the two output leads at the right connect to the supplied equipment, which could for instance be the equipment on a service engineer's or experimenter's work bench. The current being monitored flows through rectifier D4 on half-cycles when the live side of the mains is negative and through rectifiers D2 and D3 in series on half-cycles when the live side of the mains is positive. The rectifiers are all silicon types, with the result that there is a voltage drop of about 0.6 volt when D4 conducts and a drop of about 1.2 volts when D2 and D3 conduct. These small voltage drops should have no effect on standard mains powered equipment.

The mains transformer has a 6.3 volt secondary and is so wired that the upper end of this secondary is positive when the live side of the mains is positive. On half-cycles when the live side is negative, rectifier D1 is non-conductive and the circuit is inoperative. The only effect given then is that 0.6 volts is dropped across D4 when the supplied equipment draws current.

If when the live side is positive no current is drawn, there is no voltage drop across D2 and D3 and, therefore, no base bias current for TR1. This transistor does not conduct and LED1 is extinguished. If, on the other hand, a current is drawn, there is a 1.2 volt drop in D2 and D3, causing current to flow into TR1 base via R3. TR1 passes collector current and the l.e.d. becomes illuminated. The l.e.d. is only alight on half-cycles when the live input is positive but persistence of vision gives the impression of continual illumination.

The circuit is very sensitive, and the l.e.d. will light up for load resistances across the monitored supply which are as high as $1M\Omega$. In consequence, in addition to the circuit indicating that equipment is switched on and is drawing current it will also detect insulation leakage in the monitored supply.

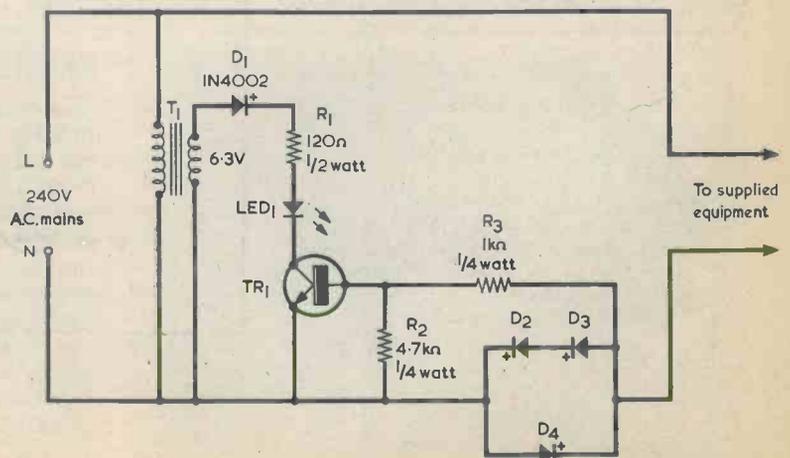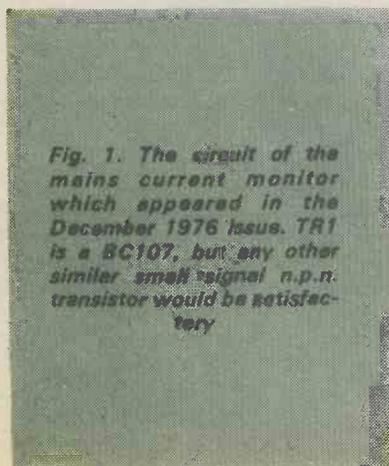The diodes D2, D3 and D4 should have ade-



quate forward current ratings. Rectifiers rated at 3 amps will, for instance, be satisfactory for loads up to 720 watts. They can have low reverse voltage ratings as the reverse voltages applied across them are very small.

MODIFIED VERSION

The modified version of the circuit now to be described introduces several advantages. Firstly, it is more economical as it dispenses with the mains transformer, which is rather an expensive item nowadays. Secondly, it is physically smaller in size and, thirdly, it eliminates a possible source of induced hum which could be given by the transformer.

The modified circuit is shown in Fig. 2. and it functions in the same manner as the previous circuit insofar that a voltage is dropped across D2 and D3, causing the transistor to be biased on, on positive live half-cycles when the monitored equipment draws current. Instead of using a step-down transformer to power the circuit, a half-wave rectifier, D1, is employed. This conducts on positive (live) half-cycles and supplies current to ZD1 and the transistor-l.e.d. circuit. If no current is drawn by the supplied equipment TR1 will not conduct, and all the current from D1 will flow into the zener diode. When the supplied equipment draws current, TR1 turns on and, except for very low load currents, will divert all the current passed by D1 away from the zener diode. The l.e.d. will then be fully illuminated.

On negative (live) half-cycles D1 will not be conductive. Any voltage from this rectifier due to leakage current cannot be applied to the transistor-l.e.d. circuit because ZD1 then acts as a normal forward biased silicon diode.

DESIGN NOTES

At first sight it may seem rather difficult trying to design a zener regulator with peak voltage of up to 340 volts! However, there is one point to note: the circuit operates from a half-wave rec-


tifier circuit feeding a "resistive" load. The average d.c. level will therefore be 0.45 times the r.m.s. value of the mains voltage, or 108 volts in this case. If we know the current we wish to pass through the l.e.d. we can find the value of R1 by working to these figures, ignoring voltage drop in the l.e.d. and the transistor when conducting. A suitable l.e.d. current will be 10mA, and 108 volts divided by 10mA gives a resistance for R1 of 10.8k Ω . In practice a value of 10k Ω will be satisfactory. The average power dissipated in R1 will be around 1 watt and, to conform to good practice, a resistor with a larger power rating should be used.

D1 will have to withstand a peak inverse voltage of 340 volts, thus a diode in the 1N4004 to 1N4007 range could be used.

The zener voltage was found to be of secondary importance and zener diode voltages between 5.6 and 20 were tested in the circuit without any significant effect on its performance. In general, the zener diode mainly ensures that the voltage across the l.e.d. and the transistor does not rise to an excessive value on positive half-cycles when the transistor is turned off. The zener diode power rating can be modest and 400mW diodes will be quite satisfactory, particularly for zener voltages below 10. A peak current approaching 34mA will flow through the diode for a short while in each cycle but such a current is well within maximum zener current ratings for diodes in the BZY88 series. Readers who prefer firmer specifications can employ a BZY88 having a voltage of 7.5, 8.2, 9.1 or 10 volts in the ZD1 position.

The l.e.d. used was a TIL209 and, with an average current of 10mA flowing through it, the brightness was found to be sufficient. Some constructors may prefer larger diodes. Again, the maximum current rating of the diode should not be exceeded (40mA for a TIL209) which it is not in this circuit. Transistor TR1 was a BC169C but most common small-signal n.p.n. silicon transistors would be suitable here.

Fig. 2. The modified mains current monitor. This offers economies in components and takes up a smaller space. The resistors may have a tolerance on value of 10%.

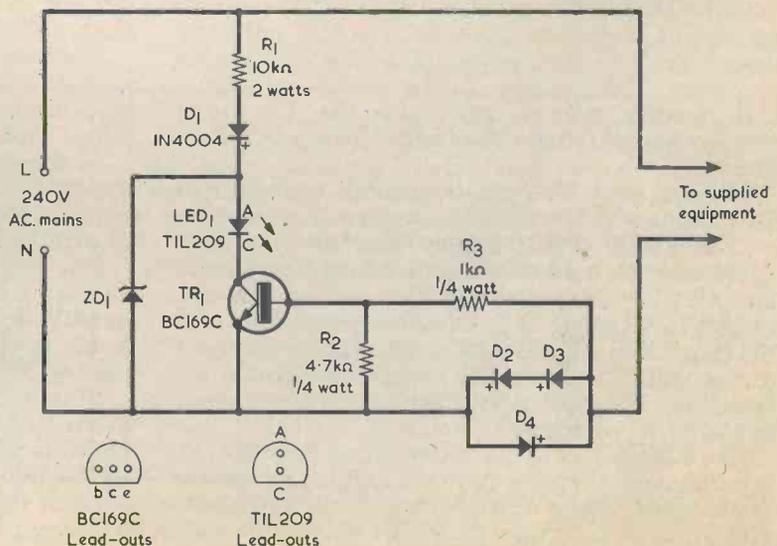

ASSEMBLY

Assembly of the circuit should follow usual construction and safety practice. Since some of the circuit points are at live mains potential it is essential that the components be contained in a housing which ensures that there is no risk of accidental shock. If the case is metal it must be reliably earthed. A small amount of heat will be generated as there will be a continual dissipation of approximately 1 watt.

For interest, a comparison was made between this power figure and the power consumption of a small 6 volt transformer. The power consumed by the transformer off load measured at 1.7 watts, although the power figure will vary according to the quality of the transformer used. This finite power consumption of a transformer off load may come as a surprise to some readers, but it is to be expected of practical non-ideal components. ■

BETTER TV SOUND

by J. P. Macaulay

How to obtain improved television sound quality, simply and safely, from many portable TV receivers.

Those who have had the good fortune to hear and see the stereo-TV joint broadcasts will appreciate the extra dimension that stereo adds. However, it is not so widely appreciated that the sound channel of the normal TV broadcast, although in mono, is of the same order of quality as the Band II f.m. radio broadcasts.

This fact is certainly not exploited by TV manufacturers, judging by the inferior size and quality of the speaker provided in the average set. It was the author's enjoyment of these joint programmes that promoted this short article, and it is aimed at those who possess a portable TV having an earphone socket.

TAKE-OFF POINT

Many currently available portable TV's feature an output socket on the side which is normally meant for the connection of a low impedance earphone. This facility can be used to provide a high quality take-off point for the TV sound without having to modify or add circuitry to the existing set.

Modern portables are invariably transistor or i.c. designs which, unlike the larger sets, do not use a live-chassis power supply and are therefore operated from a more or less standard transformer and rectifier arrangement. This means that the chassis is not likely to be at mains potential as with the larger sets. In any case, a set with an earphone socket will not have a live chassis or it would not satisfy the stringent safety regulations which apply to electrical equipment on sale in the U.K.

The easiest way to get better sound from the TV is to run a pair of wires from the earphone socket to the auxiliary input of a hi-fi amplifier. The sleeve of the jack plug fitting into the TV earphone socket will normally connect to the TV chassis. The other

end of the wire connecting to the plug sleeve should connect to the chassis of the amplifier. With a stereo amplifier, the two non-earthly input points should be paralleled.

When the input impedance at the auxiliary input is fairly high, say above $10k\Omega$, the output emitter followers of the internal TV amplifier will work virtually in Class A. The reason for this is simple. With a low impedance load like the internal speaker the output transistors operate in Class B; however, the low quiescent current which flows in all Class B amplifiers is sufficient, when working into a high impedance, for no extra current to be taken from the TV power supply. Thus, the current which flows in the high impedance load is sufficiently small to be provided by the quiescent current in the output pair and these operate in push-pull Class A.

Further, the output capacitor in the TV set has negligible effect on the low frequency response, thus improving the overall quality of the output signal available from the earphone socket.


As the output from the earphone socket is at low impedance it is not necessary to use screened wire for the connection to the hi-fi amplifier. Any kind of wire including thin 2-core flex is suitable.

It is difficult to describe the enhancement of TV viewing which results from a satisfactory sound quality, but the scheme can be safely said to be a good investment, especially when watching musical programmes.

Finally, it must be stressed that the connection to the hi-fi amplifier must only be carried out with portable television sets which have an earphone socket fitted by the receiver manufacturer. On no account should any attempt be made to obtain an a.f. signal from a TV receiver which does not have such a socket installed. ■

New Products

COMPATIBLE CRYSTAL OSCILLATOR

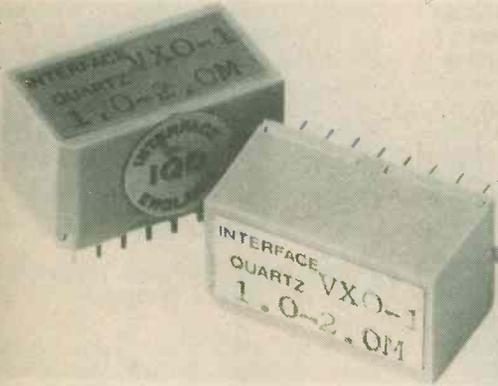


Introduced in the Autumn Verospeed Catalogue is a TTL Compatible Crystal Oscillator with both normal and complementary outputs at 1 MHz and 2 MHz mounted in dual line configuration. The device operates from a supply voltage of 5v ($\pm 0.25V$) and draws 35 mA max. The temperature coefficient is 1ppm/ $^{\circ}C$ max or less than ± 50 ppm drift over the operating temperature range (0-70 $^{\circ}C$). Rise and fall time 20 nS max. Available to order code 90-6287H price £9.36 on a guaranteed ex-stock basis from Verospeed, 10 Barton Park Industrial Estate, Eastleigh, Hants. SO5 5RR.

RANGE OF SCREWDRIVERS

Thunder Screw Anchors Ltd. announce the introduction of a range of cabinet handled and 'continental' handled screwdrivers together with a mains tester and a selection of spiral ratchet screwdrivers. The cabinet handle range includes screwdrivers of electricians, engineers and crosspoint types with blade sizes from $\frac{3}{16}$ " x 3" to $\frac{3}{8}$ " x 10", a total of 15. The continental range includes chubby, pozidriv, crosspoint and electricians patterns. Spiral ratchets are available with or without locking device, and with or without a magazine to hold bits.



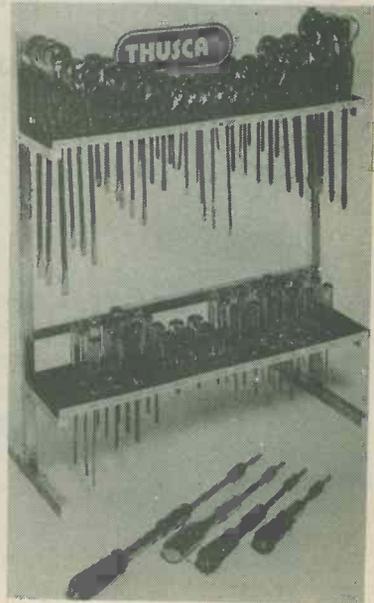The screwdrivers, as shown in photograph, are made from high quality steel and are extremely competitively priced. Further details from Thunder Screw Anchors Ltd., Industrial Estate, Southwater, Horsham, Sussex. RH13 7HQ.



CAR REAR SCREEN HEATER

The Rainbow Rear Screen Heater, an Italian invention from the 1976 Turin Motor Show, is an entirely new concept in rear screen heating employing a new revolutionary method of fixing which gives "Total Visibility" to the driver and is indistinguishable from a standard fitting.

Carrying an Italian patent, No. 165006 with U.K. patent pending, the Rainbow finishes, once and for all, the unsightly small square stuck to a window which clears only a portion of the screen and which ceases to function if a single filament, which carries a weak resistance, should break. The Rainbow will continue to operate even in the unlikely event of 2 filaments breaking.

Fixing time is approximately 20 minutes — a grooved adhesive plastic strip, 30cm long, is cut to length (rule provided) and placed at each end of the screen. The filaments are run horizontally across the whole width of the screen, thin metal strips slot into the grooves giving electrical contact — all that remains is to connect up with the plugs, cable and illuminated warning switch!


When fitted, the Rainbow gives the same heat as a standard fitting and breakage of filaments is nullified by their high-tack adhesion. Should a filament be accidentally damaged it is easily replaced as 13 metres of filament are supplied — ample for the largest rear screen.

The Rainbow comes in an attractive bubble-pack containing everything, including a switch with warning lamp, electrical contacts and cable etc. Full fitting instructions are printed on the reverse of the pack.

The recommended retail price is only £4.95 plus V.A.T., and is available from all leading accessory shops, or in case of difficulty, from Macgilwood Ltd., 39/41 High Street, Gt. Dunmow, Essex.



In your work shop

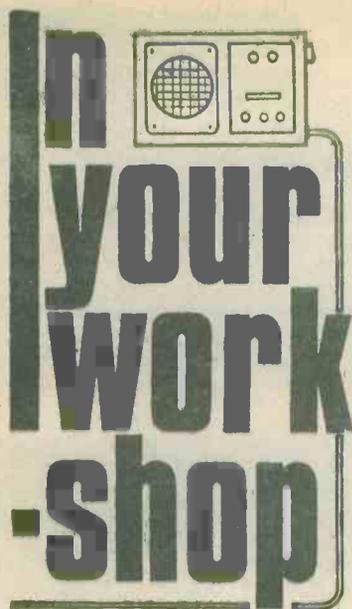

This month Dick sets out on the repair of a television receiver having a faulty contrast control circuit. As always Smithy offers assistance, but events do not turn out quite as he had anticipated.

Cheerfully, Dick selected a 14 inch black and white television receiver from the "For Repair" rack and carried it over to his bench. It had its own loop aerial at the back and he decided to check its performance with this, rather than use the Workshop aerial. He connected the set to the mains and switched on. Almost immediately the sound channel of one of the local TV transmissions became audible from the speaker. As he waited for the picture tube to warm up he adjusted the volume control of the receiver. Both the sound quality and output power available were completely acceptable.

Shortly afterwards, a pale raster appeared on the screen. Dick looked at it closely and was just able to make out a weak picture which was firmly synchronised both for line and frame. He put his hand out to the brightness control but all that this could do was to increase the brightness of the raster and make the weak picture even less discernible.

Dick next tried the contrast control. He rotated it experimentally to find that it had no effect whatsoever on picture amplitude. The picture remained at its same weak level for all settings of the control.

Frowning, he checked the type number of the receiver, switched it off, then made his way to the filing

cabinet in which the service manuals were kept.

CONTRAST FAULT

At his own bench Smithy, working at a backlog of paperwork, permitted himself a quick grin as he heard his assistant's footsteps pass behind him, followed by the sound of the filing cabinet drawer being opened. This little scene represented what, to him, amounted to a major victory in the constant battle of wills with his assistant. For years Dick had looked upon the consultation of a service manual as the last resort in the tracking down of a snag. As a result he would sometimes, to Smithy's mind, needlessly waste time by ploughing on guided only by instinct in search of a fault, instead of taking out the service sheet and finding the trouble by logical reasoning. To be honest, Smithy had to admit that, in compensation, his assistant possessed an abundance of the two necessary prerequisites of a successful service engineer: a nose for faulty components and good luck.

But now, as a result of Smithy's continued admonitions, Dick had completely changed his servicing approach. If the service manual was available he consulted it as soon as he started on a repair job.

Smithy returned contentedly to his paperwork. He was ordering new components to stock the spares cupboard, employing a technique which would have sent the average stores accountant into a shivering decline. Smithy's dictum was simply to get in plenty of everything: not only did this mean that there was less risk of a spare part not being immediately to hand when it was needed but it also meant that Smithy had to do his paperwork much less frequently.

As he added a dozen 0.1 μ F capacitors type C280 to his list he was aware of a quiet moan from the other side of the Workshop. He paused, then returned to his task. A dozen 0.47 μ F C280's mightn't be a bad idea, either. He entered them in his list.

Once more there was the low moan.

Alarmed, Smithy turned round, to see his assistant slumped despondently on his stool staring down at something on his bench. Smithy rose hurriedly and walked over to Dick's side, noticing that the object of Dick's gaze was the service manual he had just selected, which was now opened out at its circuit diagram. Once again the moan issued from Dick's lips.

"For goodness' sake," said Smithy irately, "I thought you were having a seizure or something."

Dick gazed up mournfully at the Serviceman.

"I reckon I should have one, too," he grumbled, "after seeing the

contrast circuit in this set. I can't even begin to understand it."

Smithy glanced briefly at the circuit. (Fig. 1.)

"There's nothing very complicated there," he stated. "It's just a 470 Ω pot in the emitter circuit of the video output transistor."

"That's not all there is to it," retorted Dick. "What about that pre-set contrast control? There's a 4.7k Ω pre-set pot there and for the life of me I can't fathom out what it does in the circuit."

"Dash it all," snorted Smithy, "that pot is just in a gated a.g.c. circuit. And a pretty simple gated a.g.c. circuit, at that."

He looked at his assistant's downcast face then sighed helplessly.

"All right," he said resignedly, "tell me what's happened up to now."

"Well," said Dick, "I got this set onto my bench, plugged it in to the mains and switched on. The sound came on right away but when the picture came up it was locked but very weak. What's more, it stayed at the same weak level at all settings of the contrast control. So I did what you're always telling me to do. I went and got the service manual."

Smithy nodded his approval.

"Very good. A few minutes with the manual can often save you ages in finding a fault."

"Can it? If I hadn't got that manual out I would by now have been happily poking around inside this set looking for the fault."

"What good would that do if you didn't know where to look?"

"Instead of which," continued Dick, ignoring the Serviceman's remark, "I'm sitting here like a lemon gazing at a circuit which I simply cannot understand. What does that pre-set contrast control do, Smithy?"

"It sets up the gated a.g.c. contrast level," replied Smithy. "And it's very doubtful whether it has anything to do with the fault you've got in that set."

"Still," persisted Dick, "how does it work?"

GATED A.G.C.

"Well," said Smithy reluctantly, "if we're going to talk about gated a.g.c. we want to clear up a few background details first. To start off with, why do we use gated a.g.c.?"

"Search me," said Dick cheerfully. Now that the Serviceman was beside him to offer assistance his spirits were rising visibly.

"You need gated a.g.c.," said Smithy, "to ensure that any impulsive interference which is picked up by a TV receiver doesn't generate an excessively high a.g.c. voltage. We're talking about 625 line television reception, and in the 625 line video signal the line sync

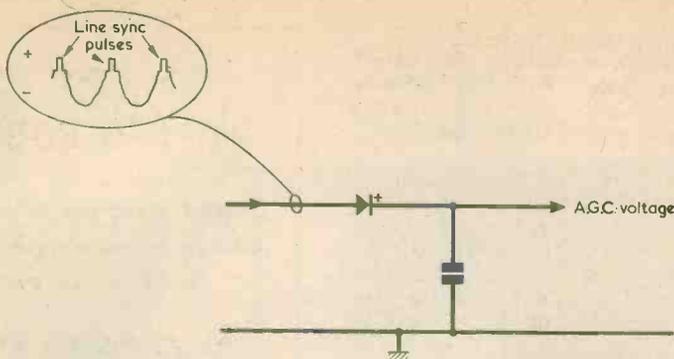


Fig. 2. Theoretically, a simple circuit of this nature, in which the detected 625 line signal is applied to a diode, could be employed to produce an automatic gain control voltage

pulse tips correspond to maximum signal amplitude. It would be quite possible in theory to have an a.g.c. circuit in which the detected video signal was simply applied via a series diode to a capacitor. The capacitor would charge up to the line sync pulse tip level and the voltage across it would correspond to signal voltage. That voltage could be used as an a.g.c. voltage controlling the gain of one or more of the preceding stages in the receiver. If the signal amplitude at the diode increased so would the a.g.c. voltage, and this would cause the gain of the preceding stage or stages to be reduced and bring the signal level down again." (Fig. 2.)

"That sounds fine by me. What's wrong with a system like that?"

"It's no use in practice," replied Smithy, "because it's wide open to impulsive interference. If impulsive interference of sufficient strength got into the system the interference pulses would also be rectified by the diode and the a.g.c. voltage would go up, reducing the gain of the receiver. Gated a.g.c. gets over this snag very largely by employing an a.g.c. voltage producing circuit which is only operative when line sync pulses are present. Unless interference pulses appear at the same time as the line sync pulses, which is unlikely, the a.g.c. voltage producing circuit ignores them completely."

"Well," commented Dick, "that makes sense. But the gating circuit required for producing the gated a.g.c. voltage seems to me to have a lot more in it than just a simple diode and capacitor."

"That's fair comment," admitted Smithy. "Anyway, let's have a look at what goes on in the particular gated a.g.c. circuit you've got here. If we go back to the video detector, we see that this is connected so that the detected video signal appearing after it has negative-going line sync pulses. This signal is applied to the base of

the video driver transistor which, so far as the video signal is concerned, is an emitter follower. The output at the emitter will therefore be a signal which also has negative-going line sync pulses, and this is passed on to the base of the video output transistor. It is also applied, via a 15 Ω and 820 Ω resistor, to that 4.7k Ω pre-set contrast pot which has been causing you so much anguish."

"Now, don't be like that, Smithy."

"Stap me," snorted Smithy. "It's you who makes me like that."

"You've been taking those niggly pills again!"

"I have *not* been taking any niggly pills. For goodness' sake stop interrupting and let me get on with this explanation. As you can see, the slider of that pre-set pot goes to the base of the BF238 gated a.g.c. transistor, the emitter of which goes straight down to deck."

"To deck?"

"To chassis. If you next look at the line output transformer you'll see that there's a winding on it which, by flyback rectification, gives 95 volts positive for the brightness control and the focus electrodes of the picture tube, as well as for the video output transistor collector load."

"That's a funny way of setting about things, isn't it? Couldn't the 95 volts be derived from the mains?"

"This," pronounced Smithy, "is one of the many small portable black and white TV's which are being produced these days for operation from the mains or from a 12 volt accumulator. The mains supply line in the set is at about 11 volts stabilized and any higher voltages that are required are taken from windings on the line output transformer."

"Oh, I see. Well, that seems fair enough."

"Darned right it's fair enough! Now that line output transformer

winding also connects, via a 5.6k Ω resistor, to a clamp diode. This does not conduct during flyback pulses when the upper end of the winding goes positive, but it does conduct between pulses when the winding upper end goes negative. The result is that you get a nice series of positive-going pulses, synchronised with the picture line sync pulses, at the upper end of the diode, with the waveform staying at chassis potential between pulses. This waveform is applied via a 5.6k Ω resistor to the emitter of the video output transistor and also, via another diode and a 470 Ω load resistor, to the collector of the BF238 transistor." (Fig.3.)

"This," remarked Dick, looking more closely at the circuit, "is beginning to get more interesting. Things are beginning to slot into place."

"Good," said Smithy, pleased now with his assistant's attention. "From what we have seen, the BF238 can only act as a transistor during the periods when the positive-going pulses from the line output transformer winding are present because that's the only time when it has a positive collector supply. When these pulses are present so also are the negative-going signal line sync pulses from the video driver transistor emitter. In consequence, the current flowing into the base of the BF238 during these periods depends upon the amplitude of the signal. If the amplitude increases, the line sync pulse tips go further negative and less current flows into the base. The collector current decreases and the collector voltage goes positive. If the signal amplitude decreases, the signal line sync pulses go less negative and more current flows into the transistor base. Its collector voltage then goes negative."

FORWARD A.G.C. BIAS

"Hey," said Dick excitedly, "just let's hold things here for a few moments. What you're saying is that if signal amplitude at the video emitter increases the collector of the BF238 goes positive."

"That's it."

"And if signal amplitude at the video emitter decreases the BF 238 collector goes negative?"

"You've got it."

"Humph!"

"But," Smithy reminded him, "these voltages at the collector of the BF238 only appear when line sync pulses are present. Between the pulses the collector drops down to around chassis level. Now, the collector connects to another diode which in turn connects to a 2.2k Ω resistor coupled to a potential divider consisting of a 10k Ω and a 3.9k Ω resistor across the supply lines, and the a.g.c. voltage is taken from the junction of the diode and

the 2.2kΩ resistor. In the absence of signal, when there are no line sync pulses at all, this potential divider provides a standing a.g.c. bias. When a signal comes along the collector of the BF238 goes positive during line sync pulses and the diode conducts, causing the a.g.c. line to go positive as well. The positive voltage from the diode is in the form of pulses, and these are smoothed out in the a.g.c. line by a 0.1μF capacitor, a 1kΩ resistor and a 0.01μF and 10μF capacitor in parallel. And so you get an a.g.c. output which goes smoothly positive as signal strength increases. The amount by which it goes positive is controlled by the pre-set contrast control pot, which can be adjusted such that useful a.g.c. control is given over the normal range of signal strengths likely to be received. What the pot does is to adjust the current which flows into the base of the BF238 when signal line sync pulses are present."

"What happens," asked Dick, "at the base of the BF238 between sync pulses?"

"The base-emitter junction of the BF238 merely acts as a forward biased silicon diode," explained Smithy. "The voltage at the emitter of the video driver transistor goes more positive during the periods between line sync pulses, which merely means that a larger current flows into the base. This has no effect on a.g.c. operation because the BF238 cannot act as a transistor until it gets a positive supply for its collector, and this positive supply only appears when line sync pulses are present."

"Humph!"
Dick absorbed this information, then turned his attention to the i.f.

amplifier stages in the circuit.

"There's something else here," he remarked. "You said just now that the a.g.c. voltage goes positive as signal strength increases."

"I did."
"But," said Dick triumphantly, "That can't be true! The controlled i.f. transistors are n.p.n. types, which means that their gain increases when the a.g.c. line goes positive. The a.g.c. line would have to go negative and not positive to reduce the gain of those transistors."

He pointed to the transistors in question. (Fig.4.)

"Ah," said Smithy imperturbably. "Now what you're saying would be true if we were talking about a.g.c. control in a transistor radio. In present-day TV sets i.f. gain is controlled by what is known as 'forward a.g.c.', with which i.f. gain is reduced by increasing the base current of the controlled transistors. What this does, roughly, is to reduce the impedance of the base-emitter junction inside the transistor and thus reduce the signal voltage which appears across that junction. This only works with transistors which are specially designed for forward a.g.c. operation, and the BF196's used in this circuit are forward a.g.c. types. The system has the advantage that a high a.g.c. voltage reduces transistor gain without reducing its linearity of operation, with the result that strong signals don't cause cross-modulation."

"Humph!"
"I wish," said Smithy irritably, "you'd stop saying 'humph' every time I impart a bit of information to you. It's even more annoying than those ghastly jokes you keep

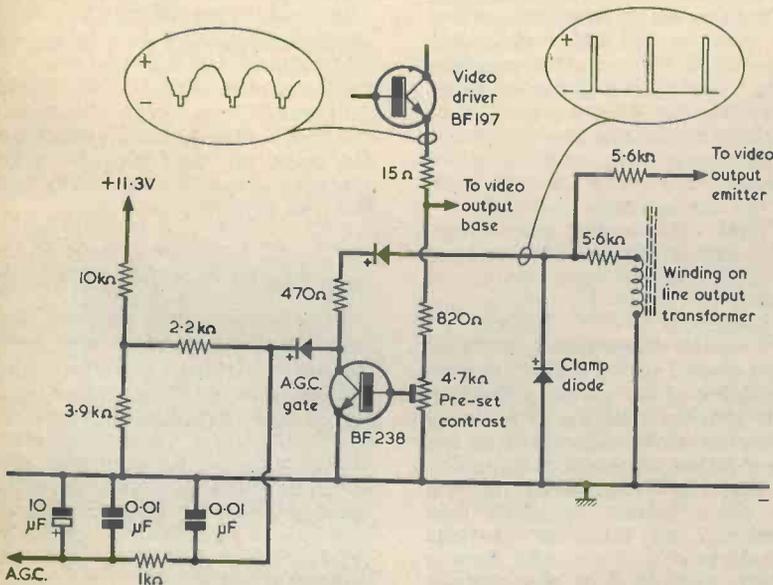


Fig. 3. The gated a.g.c. section of the circuit, illustrating the waveforms which are applied to the BF238 transistor

THE MODERN BOOK CO.

Largest selection of English &
American radio and technical
books in the country

19-21 PRAED STREET

LONDON W2 1NP

Tel: 01-723 4185/2926

MORSE IMPROVEMENT

C90 Cassettes (A) 1-12 w.p.m. with simple exercises. (B) 12-14 w.p.m. computer produced professional level operator material including international symbols.

Price each: complete with instruction and exercise booklets £4 including postage.

Morse Key and Buzzer Unit suitable for sending practice and DIY tape preparation.

Price £4 including postage.

MHEL ELECTRONICS (Dept. R)

12 Longshore Way, Milton,
Portsmouth (UK), PO4 8LS

JEFFRIES

For

Hi-Fi Equipment

Tape Recorders

Television

Transistor Radios

6A ALBERT PARADE
VICTORIA DRIVE
EASTBOURNE, SUSSEX

PEATS for PARTS

ELECTRONIC COMPONENTS

RADIO & TELEVISION

For the convenience of Irish
enthusiasts we supply:

Radio & Electronics
Constructor Data Books
Panel Signs
Transfers

Also a postal service

PEATS

the world of electronics
25 Parnell Street, Dublin 1. Telephone 749972

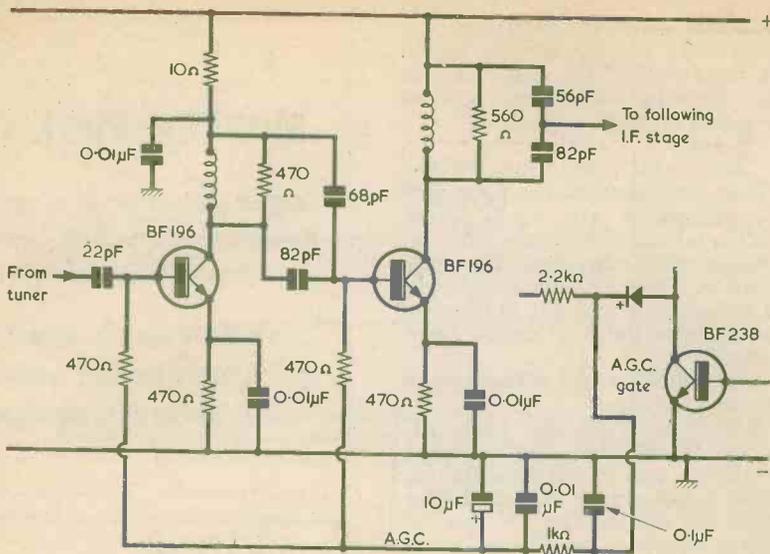


Fig. 4. The first two i.f. transistors in the television receiver are those whose gain is controlled by the a.g.c. voltage. Their gain decreases as the a.g.c. voltage goes positive

coming out with."

"I haven't heard any new jokes recently," confessed Dick. "Apart, that is, from those I've heard on B.B.C. sound radio."

"I would remind you," said Smithy hastily, "that this is a respectable establishment. You certainly aren't going to repeat any of those jokes here."

BLANKING PULSES

"Okeydoke," said Dick equably. "Let's get back to the circuit. There's another thing here that's puzzling me."

"What's that?"

"You inferred just now that those positive pulses from the line output transformer winding had a value of 95 volts. Isn't that rather a high voltage to apply to the collector of the BF238 a.g.c. transistor?"

"The pulses are reduced in voltage by the time they get to the collector," said Smithy. "There is a 5.6kΩ resistor in series between the winding and the clamp diode, and a further 5.6kΩ resistor from the clamp diode to the emitter of the video output transistor. On their own these resistors cause a sizeable drop in pulse amplitude. Then there is a further drop due to the collector current drawn by the BF238. As a result, the pulse voltage at the BF238 collector is at quite a low level, and is well within the collector voltage rating of the transistor."

Dick turned his attention to the

video output section of the circuit. (Fig. 5.)

"I hadn't thought about that 5.6kΩ resistor connecting to the video output transistor emitter," he remarked thoughtfully. "Why are the positive flyback pulses from the line output transistor applied there?"

"To give line blanking," replied Smithy. "The pulses drive the emitter positive during line flyback, whereupon the video output transistor collector goes positive as well. This causes the picture tube cathode to go positive too, so that the tube is cut off during line flyback. There are also positive-going flyback pulses from the frame timebase, and these are applied to the video output emitter by way of a 0.22μF capacitor and an 18kΩ resistor. They cause the tube to be cut off during frame flyback."

"That video output emitter circuit," said Dick musingly, "has got the 470Ω customer operated contrast control pot in it. How does that work, Smithy?"

"It varies the amount of signal degeneration in the emitter circuit. When the slider of the 470Ω contrast pot is at the top of its track nearly all the emitter load of the video output transistor is bypassed by the 100μF electrolytic, and so the video output transistor has maximum gain. When the pot slider is at the bottom of the track there is hardly any bypass capacitance across the emitter load at all, and the video output transistor has minimum gain. Correct contrast is

given at some setting between these two extremes. Don't worry about the 3,300pF and the 560pF capacitors in the emitter circuit. They're merely there to increase the video output transistor gain at the higher video frequencies so that it has a flatter response over the video frequency range. Any more questions?"

Dick pondered for a moment.

"Nope," he said finally, "there's nothing else I can think of."

"Good," said Smithy briskly. "Well now, we can next observe the usefulness of getting out the service manual at an early stage during a repair. For a start we can tell from the service manual circuit that the video signal is getting up to the video driver stage at good strength and that it is certainly appearing at the collector of the video driver transistor."

"How do we know that?"

"Because we're hearing the sound channel. The 6MHz inter-carrier sound signal must therefore be appearing at the 6MHz sound take-off transformer in the video driver collector circuit. From this it's fairly safe to assume that the emitter circuit of the video driver transistor is also all right, particularly as we're getting frame and line sync. So we'll look for a snag in the video output stage."

Smithy smiled smugly at his assistant.

"It's all," he remarked condescendingly, "a process of logical deduction. You take a look at the service manual, consider the known facts and then proceed to make your diagnosis. A few minutes' time is all that's needed and then, my boy, it's nothing more than logical deduction."

"A few minutes?" repeated Dick incredulously. "Blimey, we've been nattering away here for nearly an hour."

"Ah yes," conceded Smithy, "but that's because you let yourself be side-tracked by that pre-set contrast control circuit."

"Humph!"

"Just," said Smithy icily, "get the back off that set and start checking around. You'll soon find that I'm right."

CONTRAST CONTROL FAULT

Dick removed the receiver plug from the mains and then unscrewed the back of the set. He put it to one side and peered in.

"Ye gods," he breathed.

Surprised at his assistant's reaction, Smithy pushed him to one side and looked into the recesses of the receiver. He blanched.

"Well," he stuttered weakly, "you are supposed to look for obvious faults first."

"You mean," scoffed Dick, "use logical deduction?"

"Well, yes."

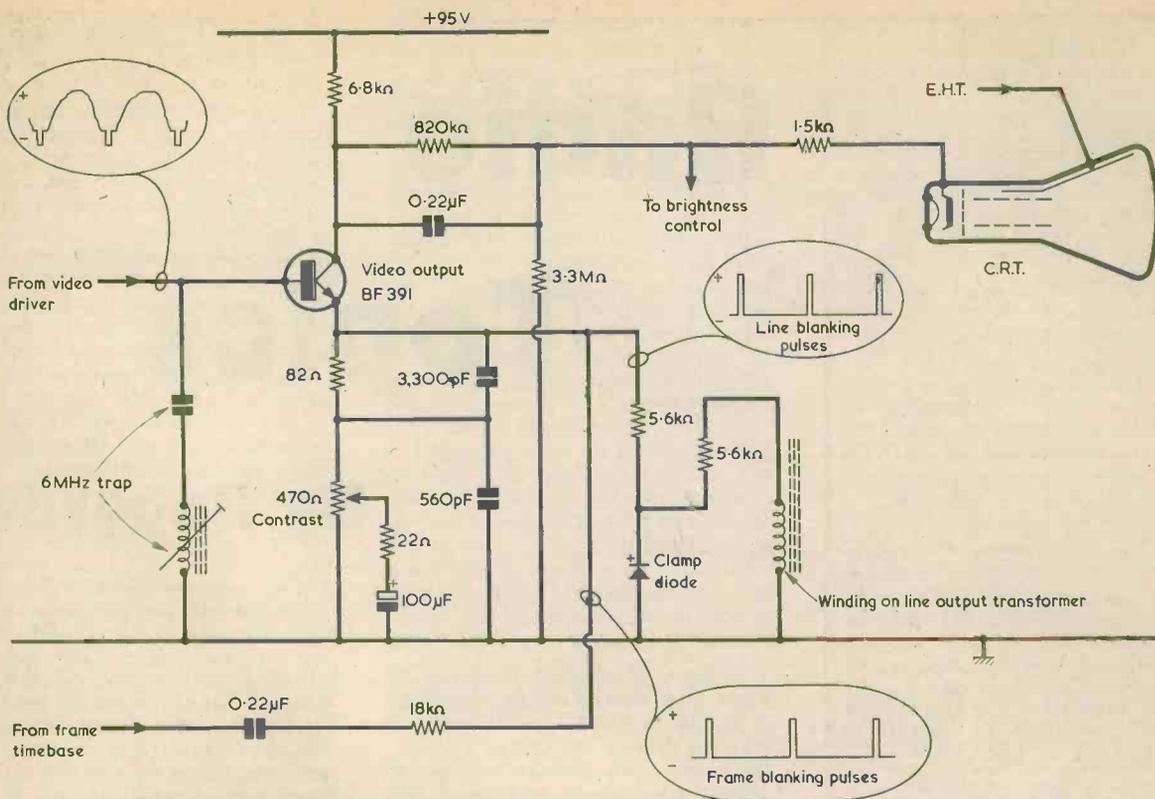


Fig. 5. Blanking pulses from the line output transformer winding and from the frame timebase are applied to the emitter of the video output transistor

"Logical deduction my Aunt Fanny!" snorted Dick. "All that's wrong with this set is that the wire has come off the slider tag of the contrast control! If I'd been working in my old way I'd have seen that the contrast control wasn't working and the very first thing I'd have done would have been to check the wiring to it without thinking any further. No service manual, no worries about pre-set contrast controls and sync pulses, no nothing. And certainly not no flaming logical deduction!" (Fig. 6.)

Even this parade of double negatives did little to diminish

Smithy's embarrassment. Dick picked up his soldering iron and quickly resoldered the offending wire to the tag of the contrast potentiometer. He then reconnected the receiver to the mains, switched it on and waited for the tube to warm up. It now reproduced a perfectly respectable picture and Dick was able to adjust the control so that it gave an impeccable contrast level.

"From now on," he pronounced resolutely, "I'm going to do servicing my way. And that means digging around quietly and following my nose until I've run the snag down to earth. In future I'll get out

the service manual only when I'm good and ready for it!"

For once, Smithy had no comment to make. Shot down, verily, irretrievably, in flames, he returned crestfallen to his bench and listlessly resumed the task of completing his components order. He heard Dick return the now serviceable television receiver to the "Repaired" rack and, glancing round surreptitiously, saw him pick up a record player from the "For Repair" rack. Cheerlessly, he proceeded with his list, and the Workshop fell into a despondent stillness.

"Hey, Smithy!"

Smithy's heart leaped. He forced his voice into its usual unexpressive tone: "Hello!"

"Could you come over here for a moment, please?"


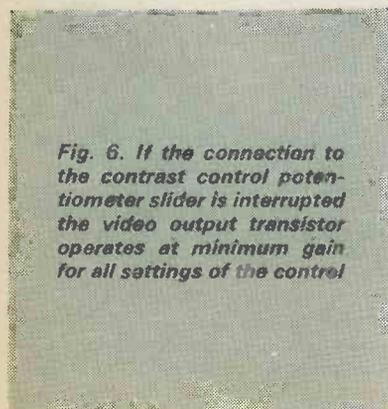


Fig. 6. If the connection to the contrast control potentiometer slider is interrupted the video output transistor operates at minimum gain for all settings of the control

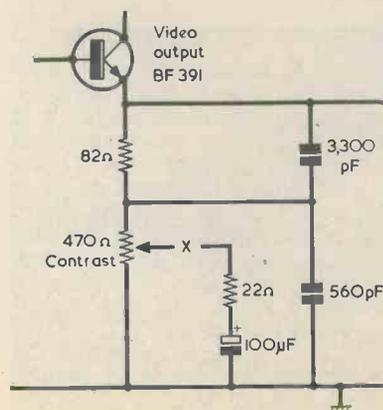

EDITOR'S NOTE

The diagrams accompanying this feature are slightly simplified versions of the appropriate sections of the circuit employed in the Thorn Consumer Electronics 1691 series of monochrome television receivers. The contrast control "fault" was devised for the feature.

GAREX

2-metre RECEIVER NR56: fully tunable 144-146 MHz, also 11 xtal positions for monitoring specific channels. Compact, sensitive, ideal for fixed or mobile listening. Built-in L.S., 12v DC operation. £54.00 inc. VAT. Crystals, if required: £2.50 each. All popular 2m. channels in stock. Credit terms available. s.a.e. details

Experimenter's H.T. transformer; multitap primary, 5 sec. windings: 35V 200mA, 75/115V 150mA, 50V 500mA, 150V 300mA, 170/220V 300mA, Wt. 6kg. £5.50

Relays: GPO type 2400 (medium size): 200+200 Ω coil (12-24V), 8A contacts. 4PCO+1M Type 3000 (large): 2k Ω coil (24V) 1B+3M, 2k Ω coil (24V) 2PCO, 8A contacts. 100+100 Ω coil (3-12V) 4PCO.

All new, 70p each, any 5+: 45p

Neons min. wire end. 65p/10; £4/100

Slide Switches min DPDT 18p ea; 5+: 18p
2 pole, 3 position 22p each; 5+: 18p

Resistor Kits E12 series, 22 Ω to 1M Ω
57 values, 5% carbon film, $\frac{1}{4}W$ or $\frac{1}{2}W$.
Starter pack, 5 each value (28p) £2.95
Mixed pack, 5 each $\frac{1}{4}W$ + $\frac{1}{2}W$ (570) £5.40
Standard pack, 10 each (570) £5.40
Giant pack, 25 each (1,425) £13.25

I.C.'s (new, full spec.) CD4001AE 25p

SN76660 75p NE555 55p 723(TO5) 75p

709 (TO5), 741 (DIL-8) Op. amps 30p each

BNC Cable mtg socket 50 Ω 20p; 5+: 15p

PL259 UHF Plug & Reducer 68p; 5+: 60p

SO239 UHF Socket panel mtd. 55p; 5+: 45p

Nicad rechargeable cells HP7 size £1.10

each; 4+: £1.00; 10+: 93p. Brand new.

We stock amateur V.H.F. equipment and

mobile aerials, s.a.e. details.

Distributors for J. H. Associates Ltd.

(switches and lamps)

PRICES INCLUDE UK POST, PACKING & VAT

Mail order only Sole Address:

GAREX ELECTRONICS

7 NORVIC ROAD, MARSWORTH,

TRING, HERTS HP23 4LS

Cheddington (STD 0296) 668684

Radio Topics

By Recorder

It isn't, of course, necessary to know what goes on inside a machine to be able to operate it. For instance you can drive a car armed with little more than the knowledge of what the pedals do and where the petrol goes. The chap at the garage will be able to fix most of the faults the car may have but he will not be fully aware of the many facets which went into that car's production: the choice of the precise metal formulations to be used, the design of the presses which turn out the bodywork, the specifications for the paints with which the body is covered, the choice of wire enamel or other insulation in the dynamo or alternator windings, the moulds from which any plastic components are made, and so on.

All the products of our continually developing technology appear at the ends of long chains of knowledge and experience. If you consider an item made of aluminium you first go back to the designer who selected the grade and hardness of the metal, then further to the smelter at which the aluminium was produced and, eventually, work right back to the people who dig the bauxite out of the ground.

INTEGRATED CIRCUITS

So it is, increasingly, with electronic components these days, including in particular digital i.c.'s. It is relatively easy to comprehend the internal circuit of a NAND gate or a NOR gate, but when we get to the more complex i.c.'s the profusion of the devices inside the chip make it impossible to determine precisely what goes on without a prolonged study. I've just opened my Texas Instruments T.T.L. Data Book at random, to encounter the 74192 and its associated family. This is a 16 pin d.i.l. integrated circuit described as a Synchronous 4-


bit Up/Down Counter (Dual Clock With Clear). Don't let the Up/Down term throw you; this merely means that if you feed positive-going pulses to the Up pin the counter counts up, and if you feed them to the Down pin the counter counts down.

The internal circuitry of the device is also shown. There aren't any individual transistors, diodes or resistors to be seen as the circuit would then assume enormous proportions; the parts are instead "condensed" into the symbol outlines for NAND gates, inverters and so on, with interconnecting lines between them. The circuit shows ten NAND gates, six AND gates, four OR gates, four OR gates with inverting inputs, four inverters and four flip-flops. Confronted with an array like that, the best plan unless you have the time to linger is simply to accept the fact that the i.c. gives the outputs it is intended to do and leave it at that. And yet the 74192 is relatively a simple logic i.c., at least several orders of complication below the circuitry to be found in a microprocessor chip.

So with electronics we are now well into the stage where a logic circuit designer does not have to bother his head overmuch with what goes on inside the i.c.'s he uses. He can simply leave that to the people one step back in the chain: those who design and develop the integrated circuits. A further step has been added in the series from raw materials to final product.

Incidentally, if you are used to digital integrated circuits which draw relatively low currents, these more complicated t.t.l. types are liable to occasion a little surprise. The current drawn by the 74192 at a supply voltage of 5 volts is 65mA typical and 102mA maximum. A

MORSE MADE EASY

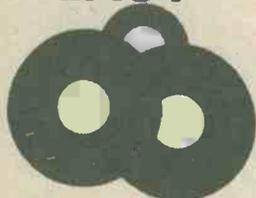

BY THE RHYTHM METHOD!

These courses, which have been sold for over 23 years, have been proved many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them! Not a series of dots and dashes which later you will have to translate into letters and words.

Using scientifically prepared 3-speed records you automatically learn to recognise the code. RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18-W.P.M. in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books.

For Complete Course send £5.00 including P.P.I. etc. (overseas surface mail £1 extra).

Now available Shrouded Morse Keys

£2.50

THE MORSE CENTRE

Box 8, 45 Green Lane, Purlay, Surrey.

I enclose £5.00 or large s.a.e. for explanatory booklet.

Name.....

Address.....

powerful i.c. in terms of logic, but it requires quite a lot of power in terms of electricity.

CURRENT FLOW

Turning to much simpler matters we have received several letters recently from newcomers to the hobby who, understandably, are puzzled by the direction in which electric current is supposed to flow. Does it flow from negative to positive or does it flow from positive to negative?

There is a story here, and I hope that I won't introduce any glaring historical inaccuracies if I make this as simple as possible.

In the early days of electricity when cells and batteries were starting to appear and it became possible to detect and then measure the current which flowed from them, decisions had to be made. It was obvious that the two terminals of a cell or battery had an opposite electrical effect and so one terminal was described as the positive terminal and the other as the negative terminal. So far so good. The next question which had to be answered was: in what direction does the current from a battery flow? and that was when the whole mix-up began, because it was decided that electric current flows from positive to negative. A whole engineering science was built up on this assumption, introducing laws which determined such things as the polarity of the magnetic field around a coil through which an electric current flows. In the early 1900's thermionic diodes appeared on the scene and it became evident that electric current consisted of a movement of electrons. And, oh dear, these electrons went from negative to positive!

It was virtually impossible to revise the existing framework of electrical science which was based on the concept of electricity flowing from positive to negative, and so the idea of electricity flowing in this

direction continued, and has continued right up to the present day. Nearly all electrical engineering calculations are based on the convention that electricity flows from positive to negative. When it is necessary to discriminate between the conceptual flow of current from positive to negative and the true flow from negative to positive we refer to the former as "conventional current flow" and to the latter as "electron current flow". Nearly all the references to current flow in *Radio & Electronics Constructor* apply to conventional current flow; where the reference is to electron current flow this is stated explicitly.

Although it's a bit mind-bending at first, you soon get used to the anomaly. Indeed, it's a lot easier to do so when dealing with transistors where everything is hidden away in a solid-state block than it was with valves where you could see the space across which the electrons travelled! Don't forget that current does just the same amount of work regardless of the direction in which it is assumed to flow.

LOGIC PROBE

A new low cost circuit-powered logic probe suitable for digital applications in both d.t.l./t.t.l. and CMOS modes is being introduced into the U.K. by Continental Specialities Corporation of New Haven, Connecticut, U.S.A.

This probe, the LP-1, appears in the second photograph and is the size of a fountain pen. It combines the functions of pulse detector, pulse stretcher and memory circuit, allowing those employing it to obtain an instant picture of static and dynamic circuit conditions. The ability of the probe to detect pulses as short as 50 nanoseconds, coupled with its stretching and latching ability, means that single-shot, low repetitive rate, narrow pulses are readily detectable and visible. Such pulses can be nearly

impossible to see, even with a fast oscilloscope.


The user simply connects the clip leads to the circuit's power supply, sets the Logic Family switch to the proper position ("TTL/DTL" or "CMOS"), thereby establishing the correct logic level for the family under test, and then touches the probe tip to the circuit point. Two level detector l.e.d.'s — "HI" (logic 1) and "LO" (logic 0) — plus a blinking pulse detector l.e.d. indicate the activity at the point being checked. By using the Pulse/Memory switch the user can select indication of pulse transitions, or storage of low-rep-rate or single-shot events.

In operation, logic 1 levels trigger the "HI" l.e.d., logic 0 levels trigger the "LO" l.e.d., and in the "PULSE" position of the Pulse/Memory switch, the "PULSE" l.e.d. blinks three times a second to indicate pulse transitions. This pulse-stretching feature allows high-rep-rate transitions to be observed. At high frequencies the LP-1 probe simultaneously indicates whether or not signals are symmetrical. Pulse trains with duty cycles less than 30% will activate the "LO" l.e.d., while duty cycles of more than 70% will activate the "HI" l.e.d.

The input impedance on both d.t.l./t.t.l. and CMOS modes of 100k Ω virtually eliminates loading problems in the circuit under test, and input impedance is constant for both high and low states in both logic families.

The LP-1 probe is housed in a rugged moulded plastic case with built-in strain-relieved power cables and protection against reverse polarity and overvoltage. Further information is available from Continental Specialities Corporation, 44 Kendall Street, Box 1942, New Haven, Connecticut 06509, U.S.A. ■

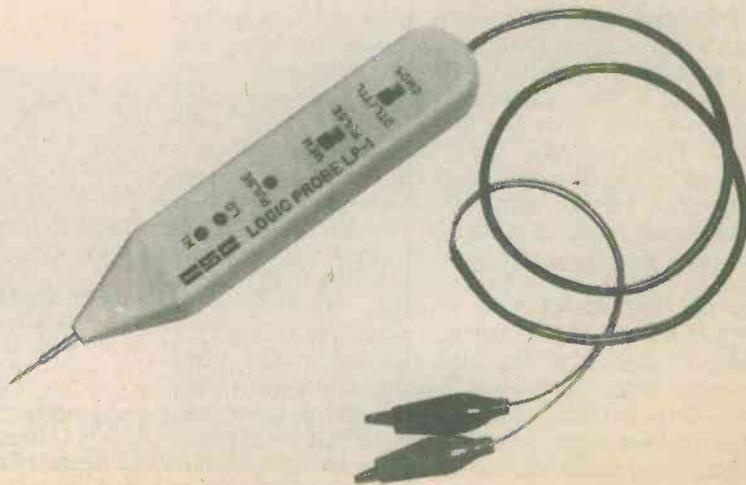The Continental Specialities digital probe type LP-1. This provides the functions of pulse detector, pulse stretcher and memory circuit, and indicates both static and dynamic conditions at the circuit point being monitored



THE STORY OF THE DETECTOR

By D. P. Newton

Before the advent of the valve, radio equipment was awe-inspiringly primitive both in its assembly and in its operation.

The problem of detecting radio signals has been solved in many complex and ingenious ways but one device, in essence very simple, is especially surprising in that it could actually be made to work at all! It consisted of a short insulated tube with two metal plugs separated by a few millimetres. As is shown in Fig. 1, the gap was

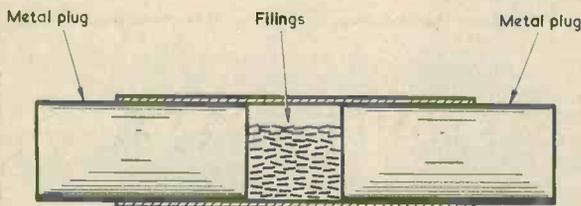


Fig. 1. The basic construction of the coherer, employed as a detector with the early spark transmitters. The metal filings "cohered" to present a low resistance when a radio signal was applied

loosely filled with filings of a metal such as nickel. In this state the resistance between the two plugs was relatively high but, when a radio signal was applied to it, the resistance became suddenly small and continued to be low after the end of the radio signal. This "coherer", as it was known, was largely due to a gentleman called Branly in 1890, three years after Hertz's demonstration of radio waves. In a series circuit with a 1.5 volt cell and a galvanometer it can be used to show the presence of radio waves, the galvanometer being deflected as the waves affect the filings. However, its limitations as a detector are obvious; it needs a shake to reset it to the high resistance state after the radio wave has ceased. Mechanical means were devised to do this, and although the coherer was employed for many years in the reception of spark transmitters there was an obvious need for a detector in the more modern sense of the word.

CRYSTAL DETECTOR

A true detector needs to do a lot more than the coherer. In the early days of radio there was no amplification, and the detector had to extract the useful information from the carrier wave by rectifying the current it produced in the aerial circuit. Some crystals, either in contact with a fine wire "cat's whisker" or in contact with another crystal, have this ability. These were the most delicate, and often perverse, parts of the "crystal sets" in which they were used. Crystals of galena, silicon, zincite or bornite were employed, the cat's whisker being scraped over the surface until a sensitive part was located. Fig. 2 shows the general idea.

Of course the first device we would really call a valve was invented by Sir John Ambrose Fleming and patented in 1904. In 1883, Edison had discovered that an extra electrode in a light bulb would give a current if it was connected to the positive terminal of the filament battery but not if connected to the negative terminal. See Fig. 3. The effect was enhanced when the electrode was made more positive with respect to the filament. Fleming was quick to see the use of such a device as a detec-

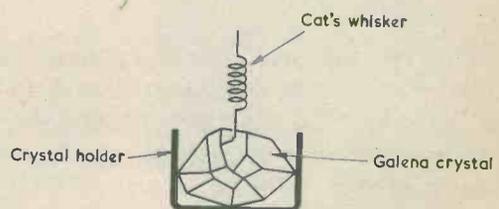


Fig. 2. The crystal detector. This functions as an inefficient and temperamental rectifier, with connections being made to the cat's whisker and the metal crystal holder

tor of radio waves. With a circuit like that of Fig. 4 he fed radio waves to his special "light bulb" and was able to obtain a direct current through a sensitive mirror galvanometer. It was then a short, but no less ingenious, step for the American Lee de Forest to later add another electrode, the grid to make the triode amplifier.

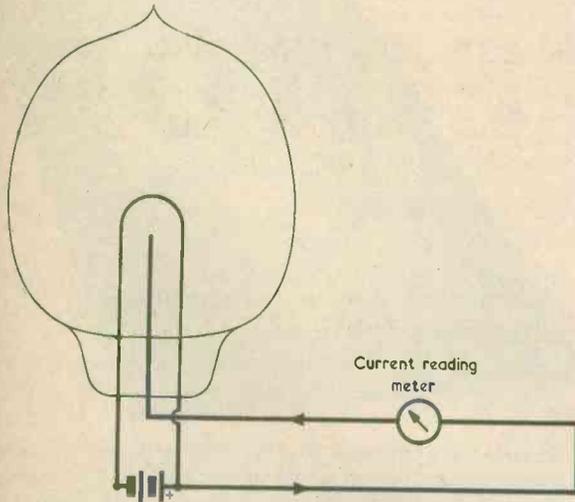


Fig. 3. The "Edison Effect". If a second electrode was placed in a filament bulb, current flowed when it was coupled to the positive terminal of the filament battery

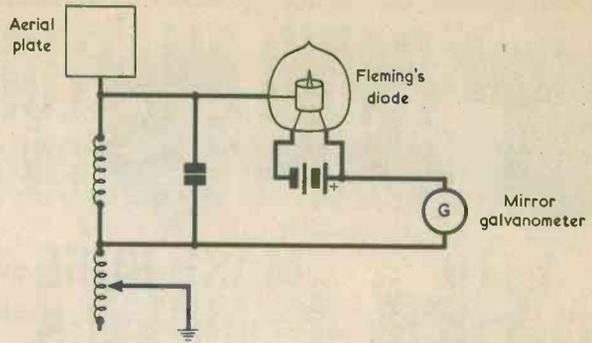


Fig. 4. Fleming developed the "Edison Effect" to produce a thermionic diode capable of rectifying, and thereby detecting, radio waves.

With the advent of the reliable valve, the cat's whisker and crystal fell out of favour except as an object of scientific study. While thermionic valves became more complex, the peculiar action of these crystals was analysed and a new material developed: the semiconductor. Three years after Fleming's death, Barden and Brattain, in 1948, produced the first practical transistor. By placing two cat's whiskers near one another on a piece of germanium, a semiconductor, the amplifying action of a triode was achieved and the early crystal set, albeit in a new guise, had come of age. ■



UNDERSTAND DATA PROCESSING

DATA PROCESSING, by Oliver & Chapman, is now in its Third Edition — first published 1972.

200 pages $9\frac{3}{4}'' \times 6\frac{3}{4}''$ **PRICE £2.50**
Inclusive of postage

The primary aim of this outstanding manual is to provide a simplified approach to the understanding of data processing — (previous knowledge of the subject is not necessary).

The 40 chapters and appendices cover the following topics: Introduction to Data Processing; Organisation and Methods; Conventional Methods; Introduction to EDP and Computers; Hardware; Computer Files; Data Collection and Control; Programming and Software; Flowcharts and Decision Tables; Systems Analysis; Applications; Management of EDP, etc.

Available from:


D.P. PUBLICATIONS
4 AMPORT CLOSE, WINCHESTER, HANTS SO22 6LP

Essential for the Short Wave Enthusiast

THE RADIO AMATEUR OPERATOR'S HANDBOOK

13TH EDITION

MAKE SURE OF YOUR COPY **NOW!**

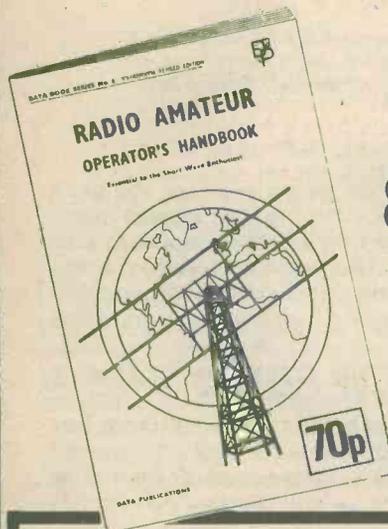

88 PAGES ONLY 70p P. & P. 13p

- ★ AMATEUR PREFIXES
 - ★ AMATEUR CODES
 - ★ LOCAL TIME CONVERSIONS
 - ★ 8 MAPS
 - ★ FREQUENCY/WAVELENGTH CONVERSION TABLES
 - ★ HOME OFFICE REGULATIONS
- MANY OTHER ESSENTIAL ITEMS

SIMPLE SHORT-WAVE RECEIVERS



If you are interested in the hobby of receiver construction and short wave listening this is the book for you. It covers the whole field of s.w.l'ing from construction to operating - both Broadcast and Amateur bands. It explains how the circuits work, how to assemble the parts, how to wire-up the circuits with point-to-point wiring diagrams, step-by-step instructions and how to test and operate the completed projects.

by F. A. Baldwin

- ★ FOUR DESIGNS - 1, 2 and 3 Valves
 - ★ INTRODUCTION TO SHORT WAVE LISTENING - 14 Comprehensive Sections
 - ★ WORKSHOP PRACTICE
 - ★ SOLDERING NOTES
 - ★ RECEIVER AND BENCH POWER SUPPLIES
- etc. etc.

140 Pages **80p** P. & P. 20p

TO DATA PUBLICATIONS LTD 57 Maida Vale London W9 1SN

Please supply copy(ies) of "Radio Amateur Operators Handbook", Data Book No. 6
 Please supply copy(ies) of "Simple Short Wave Receivers", Data Book No. 19
(Please tick which book is required)

I enclose cheque/crossed postal order for

NAME

ADDRESS

BLOCK LETTERS PLEASE

SMALL ADVERTISEMENTS

Rate: 10p per word. Minimum charge £1.50
Box No. 25p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions nor can they accept responsibility for the *bona fides* of Advertisers. (Replies to Box Numbers should be addressed to: Box No. — *Radio and Electronics Constructor*, 57 Maida Vale, London, W9 1SN.

RESISTORS: E12, 5% 1/3 W — 1p. Diodes 4148 — 3p, 4004 — 5p, LM555CN — 38p. VAT inclusive. 15p postage. Cleveland Supplies, P.O. Box 20, Redcar, Cleveland.

FOR SALE: Small electrolytics 10 μ F-220 μ F. £2/100, £15/1000. Same unmarked £1/100, £8/1000. J. Bruere, 17 Heald Close, Shawclough, Rochdale, Lancs.

BOOKS TO CLEAR: *Introductory Radio — Theory and Servicing*, 1948 (With Teacher's manual) by H. J. Hicks, £1.50. *Klystron Tubes*, by A. E. Harrison, 1947, £1.50. *An Approach to Audio Frequency Amplifier Design*, 1957, G.E.C. Publication, £1.25. *Television Engineers' Pocket Book*, 1954, by Molloy & Hawker, 50p. All prices include postage. — Box No. G329.

CLEARANCE OF NEW COMPONENTS. Our mix of values. Carbon resistors: 100/50p. Zeners: 10/40p. 1A silicon diodes: 25/50p. Bridge rectifiers: 5/£1. Glass Neons: 5/15p. Capacitor discharge transformers (ETI): £1.50. 2N3055: 48p. 1.6A, 400V triacs: 30p. TAG 1/500: 40p. 1mF/600V d.c.: 50p. Plus 15p P. & P. Padec Components, P.O. Box 71, Southend-on-Sea, Essex.

OUTSTANDING HI-FI FM TUNER. Comprises 7 transistor superhet design with vericap tuning, AFG. Latest silicon circuitry, full coverage 88-102MHz. Supplied built and tested with metal-front panel and instruction sheet. Only £9.95 + 30p P. & P. Gregg Electronics, 86-88 Parchmore Road, Thornton Heath, Surrey.

TREASURE HUNTERS! Construct 11-transistor metal detector giving £300 performance. 10 page illustrated plans, send £1. C. H. Lucas, 241 Upminster Road South, Rainham, Essex.

WANTED: Large and small quantities of transistors, I.C.'s, displays, etc., etc., Call any Saturday to: 306 St. Paul's Road, London N.1. Telephone: 01-359 4224.

AUDIO ACCESSORIES: leads, plugs, sockets, cartridges, styli. Send s.a.e. for free list. Barras Electronics, 11 North Street, Coventry, CV2 3FP. Telephone: 441141.

WANTED: Desk-FAX machine, complete or spare parts, with literature, manuals, etc., in the series TR100/1 and TR102/1, made by Creed & Co. Ltd. Details to Box No. G335.

ANTIQUÉ WIRELESS: For valves, radios, components and service sheets, 1920 to 1950. Contact The Vintage Radio Shop, 1977 Full Catalogue 70p. 64 Broad Street, Staple Hill, Bristol BS16 5NL. Telephone: (0272) 565472.

TIRRO ELECTRONICS the mail order division of Ritro Electronics UK, offers a wide range of components for the amateur enthusiast. Large s.a.e. or 20p brings list. Grenfell Place, Maidenhead, Berks., SL6 1HL.

(Continued on page 252)



Wilmslow Audio

THE firm for speakers!

SEND 10P FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST

ATC • AUDAX • BAKER • BOWERS & WILKINS • CASTLE • CELESTION • CHARTWELL • COLES • DALESFORD • DECCA • EMI • EAGLE • ELAC • FANE • GAUS • GOODMAN'S • HELME • I.M.F. • ISOPON • JR • JORDAN WATTS • KEF • LEAK • LOWTHER • MCKENZIE • MONITOR AUDIO • PEERLESS • RADFORD • RAM • RICHARD ALLAN • SEAS • TANNOY • VIDEOTONE • WHARFEDALE

WILMSLOW AUDIO DEPT REC

SWAN WORKS, BANK SQUARE, WILMSLOW
CHESHIRE SK9 1HF

Discount HiFi Etc. at 5 Swan Street and 10 Swan Street
Tel: Wilmslow 29599 for Speakers Wilmslow 26213 for HiFi

THE IDEAL CHRISTMAS PRESENT

S • R • B

MINIATURE
SOLDERING IRON
for HOBBY or TRADE

PRICES: (including VAT and P and P)

Irons £3.70 each

Bits 41p each

AS ADVERTISED ON TV

Stands £3.90 each

Solder 28p & 56p

(Bit type 20 fitted as standard).

18 watts of power at 240v. straight to the bit

BIT SIZES:
19 (1.5 mm) 20 (3.0 mm)
21 (4.5 mm) 22 (6.0 mm)

Trade Enquiries Welcome

From your Local Dealer or Direct from the Manufacturers:

S. & R. BREWSTER Ltd.
86-88 UNION ST · PLYMOUTH Tel 0752-65011

NEW STYLE SELF-BINDER

(Max format 7½" x 9½")

for "Radio & Electronics Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.



PRICE **£1.20** P.&P. 30p
including V.A.T.

BINDERS FOR THE NEW FORMAT
NOT YET AVAILABLE

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 251)

FOR SALE: Complete 9.5mm cine "Wide screen" outfit — Cameras, projector, screen, etc. S.A.E. for details. Box No. G336.

SILICON SOLAR CELLS: Booklet 75p. — Data on cells in stock 20p or s.a.e. for current price list. Edencombe Limited, 16 Prince's Avenue, London NW9 9JB.

FOR SALE: capacitors, mixed, ceramic, poly, mica, 100 — £1. Mullard C280's, 100 — £1. ½W resistors, assorted, 100 — 75p. BC107/8/9 assorted, untested, 40 — £1. 2N3055 — 25p. P. & P. 25p. S.A.E. for list. Galloway, 10 Osborne Gardens, Falkirk, FK1 5EU.

TV REPAIRS SIMPLIFIED. Full repair instructions individual British sets £4.50; request free circuit diagram. Stamp brings details of unique TV publications. Auserec, 76 Churches, Larkhall, Lanarkshire.

FOR SALE: Copies of "Hi-Fi News" January 1975 to October 1975 inclusive, plus December 1975 and January 1976. Mint condition. Offers? Box No. G338.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. — both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £3.75 per annum. (U.K. and British Commonwealth), overseas \$10.00 or £4.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

FOR SALE: Used t.t.l. i.c.'s. 90% good. £4/100 gates, bistables. J. Bruere, 17 Heald Close, Shawclough, Rochdale, Lancs.

R.E.C. KITS. Pocket Radio, August. £6.98. Case 72p. LED VU Meter, August. £6.10. Verocase £2.98. Sound Switch, July. £6.25. Verocase £2.98. Multimeter Booster, June. £3.50. Case £1.20. Continuity Checker (Wirewound potentiometer), September, £2.50. Case £2.26. Prices inclusive. **ELECOLIT** Conductive Paint £2.70. New **Bigger COMPONENTS & HARDWARE CATALOGUE** — 2 x 9p stamps. **MAGENTA, RLIO**, 61 Newton Leys, Burton-on-Trent, Staffs., DE15 0DW.

BOOKS TO CLEAR: *The Radio Constructor* Vol. 15 August 1961 to July 1962, Bound, £2.30. *Short Wave Magazine*, Bound, Volume VIII, March 1950 to February 1951, £2.00. *Newnes Television & Short Wave Handbook*, by F. J. Camm, 1935, £2.00. All prices include postage. Box No. G340.

WHAT OFFERS? Complete set 4V a.c. valves. Details supplied. Smithy, Camp Road, Ross-on-Wye, HR9 5NJ. Telephone: 3198.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. — The Holborn Direct Mail Company Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

(Continued on page 253)

SMALL ADVERTISEMENTS

(Continued from page 252)

ELECTRONIC TIME DELAY KIT. Uses: Nite-lite, Extractor fan, Auto music, etc. Times secs/mins/hrs. Mains powered, 1100W output! (No case). Send £9. S.A.E. details. L. O. Green, 4 Gurney Road, Costessey, Norwich, Norfolk, NR5 0HA.

MAGAZINE COLLECTORS. Disposing of very early issues of *Radio Constructor*. Various odd issues dating from 1950 to 1975 at 25p each. S.A.E. for list. Prices include postage. Box No. G341.

INTERESTED IN BARGAIN OFFER. Quantity Mullard FX2243 ferrite cups with DT2206 former or similar Siemens. Lomnicky, 28 Caerleon Drive, Andover, Hampshire, SP10 4DE.

ADVICE SOUGHT to rectify frequency shift present on Trio 9R-59DE communication receiver. Can anyone help please? K. V. Mahalingham, P.M.B. 5373, Ibadan, Nigeria.

STAMP FOR LISTS of new and used components. Box No. G343.

THE RADIO AMATEUR INVALID & BEDFAST CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. Rita Shepherd, 59 Paintain Road, Loughborough, Leics., LE11 3LZ.

LOW DEFINITION TELEVISION (Baird style), healthy, and living at 1 Burnwood Drive, Wollaton, Nottingham. Annual subscription, L.D.T.V.A., £1.00.

FOR SALE: 213 copies of R.C., P.E., P.W. from 1958 including 9 complete years. Offers ? Box No. G345.

TIDY THOSE WIRES for a professional finish. Self locking nylon cable ties, 15p/10 plus 15p P&P. L. O. Green, 4 Gurney Road, New Costessey, Norwich, Norfolk, NR5 0HA.

FOR SALE: Chess playing computer game. Stamp for details. Box No. G346.

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo, etc. With free fault-finding guide. From 50p and s.a.e. Catalogue 25p and s.a.e. Hamilton Radio, 47 Bohemia Road, St. Leonards-on-Sea, Sussex.

300 PAIRS OF S/H SPEAKERS in 9" x 14" teak cabinets. From £3.50. Edwards, 103 Goldhawk Road, London W12. Telephone: 743 6996.

ELECTRONIC WIRING REQUIRED. Prototypes, production runs, p.c.b.'s, cable forms. High standard work. Reasonable rates. Telephone: Maidstone 30302.

INTERESTED IN OSCAR? Then join AMSAT-UK. Newsletters, OSCAR NEWS Journal, prediction charts, etc. Details of membership from: James Keeler, G4EZN, Church Farm Cottage, Banningham Road, Aylesham, Norfolk, NR11 6LS.

WANTED in any condition: Wireless set No. 18, 21, 22, 46, 48, 58, 68 and R109. Will be collected. Also wanted working instruction books of British wireless sets. PAOPCR, 28 Smetana Laan. Schiedam, Holland.

INVENTORS: "Profit from your Invention". Sources of finance and other assistance. Details: Large s.a.e. Delta (RE), 15 St. Mary Street, Southampton, Hampshire.


(Continued on page 254)

V-Q

WAS MADE FOR YOU

VERO

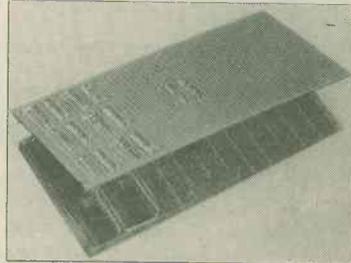VERO QUAD BOARD was designed to provide a simple circuit board capable of accepting nearly all types of integrated circuits, plus transistors, resistors, capacitors and many other components.



ASK FOR V-Q — IT WAS MADE FOR YOU

No track cutting. 1,624 holes on 0.1" x 0.1" matrix. Packed complete with layout sheet. Fits Vero Plastic Cases 1237, 1238 and 1239. Costs about 90p from your local shop or mail order company.

Send for our booklet describing many other products made for you, S.A.E. 7" x 9" plus 10p to:


VERO ELECTRONICS LTD. RETAIL DEPT.
INDUSTRIAL ESTATE, CHANDLERS FORD,
HANTS. SO5 3ZR.

BUILD YOUR OWN TELEVISION GAME

(SIX GAMES)

BASED ON THE AY-3-8500 I.C.

- ONLY **£10.50** BLACK AND WHITE KIT — over five thousand sold
- ONLY **£16.60** COLOUR KIT — this is our latest kit and gives a yellow bat, blue bat, red boundary and a green field.
- ONLY **£8.60** OUR COLOUR CONVERTER — makes your exiting black and white television game into colour. Only half an hour approximately assembly time — no extra parts are required.
- ONLY **£5.50** SPARE AY-3-8500 CHIPS WITH OUR CIRCUIT DIAGRAM.

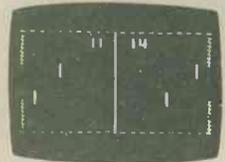

(Please note that we do not supply loudspeakers, switches or boxes.)

TIFAX UNITS FOR SALE £99.00

All the above prices include VAT, post and package

★ **SPECIAL INTRODUCTORY BONUS** ★

We will give **50p OFF** an order if this advertisement is received with your order.

Send to: **TELECRAFT, 53 WARWICK ROAD, NEW BARNET, HERTS.**
Technical advice and information given on Tel: 01-440 7033.
Personal callers are welcome seven days a week.


.....
.....
.....
Please tick in box appropriate item required and send your order with this advertisement.

ALL CHEQUES AND POSTAL ORDERS MADE PAYABLE TO "TELECRAFT"

PLAIN-BACKED SELF-BINDERS

for your other magazines

(max. format 7½" x 9½")

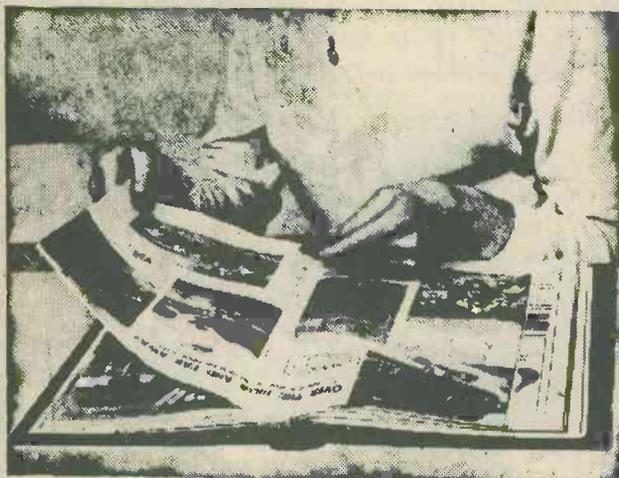

The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

COLOURS: MAROON OR GREEN

(If choice not stated, colour available will be sent)

PRICE **£1.15** P. & P. 30p

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 253)

FREQUENCY LIST TRANSFERS. We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32Mc/s at every 500Kc/s points. Each frequency is repeated. Two sheets for 5p., five sheets for 10p., postage 7p. Data Publications Ltd., 57 Maida Vale, London, W9 1SN.

LOW COST BOXES and instrument cases. a range of aluminium boxes from as little as 48p including p&p. High quality range of Instrument Cases from 85p including p&p. Sheet aluminium standard and cut to size. Self-tapping screws, BA nuts, bolts, and washers. Send a self stamped addressed envelope for pamphlet to Harrison Bros., P.O. Box 55, Westcliff-on-Sea, Essex SS0 7LQ.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St Quadrant, Brighton, Sussex, BN1 3GJ.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: — The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

SPONSORS required for exciting scientific project. Norwich Astronomical Society are building a 30" telescope to be housed in a 20' dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, The Manse, Back Lane, Wymondham, Norfolk.

ESSEX GARDENERS. Buy your Bedding and rock plants, shrubs, etc., also cacti from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only. Monday to Saturday.

THE DALESFORD SPEAKER BOOK

By R. F. C. Stephens

This book is a must for the keen home constructor. Latest technology DIY speaker designs. Contains full plans for infinite baffle and reflex designs for 10-100 watts, also unusual centre-bass system for those who want hifi to be "heard and not seen". £1.95 (£2.20 post paid. \$5 Overseas).

VAN KAREN PUBLISHING,
5 SWAN STREET, WILMSLOW, CHESHIRE.

FANTASTIC VALUE

AM/FM ST TUNER MODULE MW/LW/FM

Varicap tuning, ready built and tested. Brief spec. FM section, supply volts 20-40 sensitivity 1uV for 30 dB S/N selectivity 3 dB 300 KHz ST. Sep @ 1 KHz 30 dB min. Provision for signal strength and centre zero meters. Interstation muting switchable or continuously adjustable. AFC switchable AM section. Sensitivity 10uV 20 dB S/N @ 1 MHz, band coverage MW/LW. Provision for signal strength meter. Price £40.00, which includes tuningpot, switches and instructions. VAT is 12½% extra, p&p 50p. A ready screen-printed dial and ass will be available shortly. Send s.a.e. for details of tuner or remittance with order.

HUNTER AUDIO PRODUCTS

Market Street, Shipdham, Norfolk IP25 7LZ

Telephone: (036282) 584

TRADE ENQUIRIES WELCOME

For Semi-Conductors

including

- Small Signal Transistors
- Power Semi-conductors
- TTL, CMOS, I.C.s
- Linear I.C.s
- Signal and Power Diodes
- Zener Diodes
- Magneto Resistors
- Hall-effect devices
- Magnetic Proximity Switches
- Opto-electronic devices

Go to

ELECTROVALUE

TO MAKE THE BEST OF

For passive components

including

- Plastic Film Capacitors
- Electrolytics
- Semi-precision capacitors
- Transformers
- Pot Cores
- R. M. Cores
- Ring Cores, etc.

Go to

ELECTROVALUE

THE PROJECTS YOU BUILD

The Open Door to Quality

It's the Electrovalue Catalogue No. 8 (4th edition black and white cover) with completely up-dated prices. 144 pages, well illustrated. 40p post free with 40p voucher (usable on orders for £5 or more. Send for yours now and order in confidence. **GOODS SENT POST FREE IN U.K. FOR C.W.O. ORDERS.** Keenly competitive prices plus **ATTRACTIVE DISCOUNTS** and only best quality goods.

ELECTROVALUE LTD

(Dept. RC12) 28 St. Jude's Road, Englefield Green
Egham, Surrey TW20 0HB
Tel. Egham 3603. Telex 264475
North: 680 Burnage Lane, Burnage, Manchester
Tel. (061) 432 5945

MULLARD FERRITE CORES — LA3 100 to 500 kHz, 75p; LA5 30 to 100 kHz, 100p; LA7 10 kHz, 100p LA13 for W.W. Oscilloscope, £2.00.

SPECIAL OFFER — Metallised Polyester Capacitors by Erie, Mullard, etc. Values include: .01/160V, .01/250V, .015/160V, .022/160V, .033/160V, .047/160V, .068/160V, .1/160-250V, .22/160V, etc. This is a bargain not to be missed. 100 for £3.00. 1N4148 **SWITCHING DIODES**, 10 for 30p; 50 for £1.25; 100 for £1.50; 1,000 for £12.50.

TRANSISTORS — All branded BC147, BC148, BC149, BC157, BC158, BC159, BF194, BF195, BF196, BF197, 10p each or 100 for £7.50.

Please note all prices include UK Postage and appropriate VAT @ 8% or 12½%

XEROZA RADIO

306 ST. PAUL'S ROAD, Highbury Corner, London N1
Tel: 01-226 1489

PRINTED CIRCUITS AND HARDWARE

Comprehensive range Constructors' hardware and accessories. Selected range of popular components. Printed circuit boards for individual designs. Drawing materials for printed circuits. Resist coated laminate, epoxy glass for the d.i.y. man. Full processing instructions, no unusual chemicals required.

Send 15p for catalogue

Ramar Constructor Services

Masons Road · Stratford-on-Avon · Warwks CV37 9NF

SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please insert the following advertisement in the issue of RADIO & ELECTRONICS CONSTRUCTOR

| | | | |
|---|--|--|--|
| ➔ | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |

15 words at 10p
= £1.50

**ALL WORDING
IN
BLOCK LETTERS
PLEASE**

I enclose remittance of being payment at 10p a word. MINIMUM £1.50
Box Number, if required, 25p extra

NAME

ADDRESS

Copy to be received four weeks prior to publication. Published on the 1st of every month.

RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price 40p each, p&p 13p

Issue(s) required

Annual Subscription

Price **£6.50**, post free, commence with.....issue

Bound Volumes:

| | |
|-----------------------------------|-------------------------------------|
| Vol. 27. August 1973 to July 1974 | Price £2.40 , post & pkg 90p |
| Vol. 28. August 1974 to July 1975 | Price £2.75 , post & pkg 90p |
| Vol. 29. August 1975 to July 1976 | Price £3.10 , post & pkg 90p |

CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,
maroon only

Price **£1.20**, post & pkg 30p

With no title on spine, maroon

Price **£1.15**, post & pkg 30p

With no title on spine, green

Price **£1.15**, post & pkg 30p

Max. Format 7½" x 9½"

Prices include V.A.T.

DATA BOOK SERIES

| | |
|--|----------------------------------|
| DB5 TV Fault Finding, 132 pages | Price 90p, P. & P. 20p |
| DB6 Radio Amateur Operator's Handbook, 88 pages | Price 70p, P. & P. 13p |
| DB17 Understanding Television, 504 pages | Price £3.25 , P. & P. 70p |
| DB19 Simple Short Wave Receivers 140 pages | Price 80p, P. & P. 20p |

STRIP-FIX PLASTIC PANEL SIGNS

| | |
|------------------------|---------------------------------|
| Set 3: Wording — White | Price 75p, P. & P. 8p |
| Set 4: Wording — Black | Price £1.00 , P. & P. 8p |
| Set 5: Dials | Price 38p, P. & P. 8p |

Prices include V.A.T. on Panel Signs

I enclose Postal Order/Cheque for.....in payment for.....

NAME

ADDRESS

..... (BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable through your local bookseller

Data Publications Ltd., 57 Malda Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS