


RADIO & ELECTRONICS CONSTRUCTOR

AUGUST 1979
50p

**IMPORTANT
ANNOUNCEMENT**

SQUARE WAVE TRANSISTOR TESTER

*WITH AUTOMATIC
POLARITY SWITCHING*

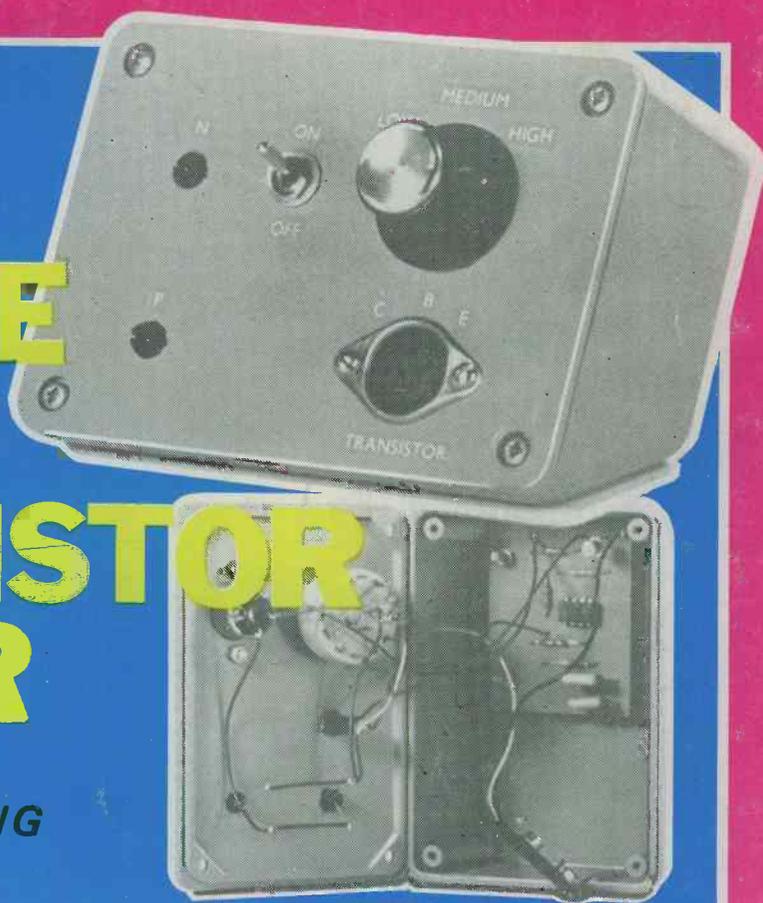

BEGINNER'S MEDIUM WAVE RADIO RECEIVER

A PROJECT WITH
PARTICULAR
APPEAL TO THE
NEWCOMER

Also inside
ANNUAL INDEX

LIBRARY
PART ONE: A comprehensive
jargon-free explanation
of microprocessors

DIODES/ZENERS			
QTY.			
1N914	100v	10mA	.05
1N4005	600v	1A	.08
1N4007	1000v	1A	.15
1N4148	75v	10mA	.05
1N4733	5.1v	1 W Zener	.25
1N753A	6.2v	500 mW Zener	.25
1N758A	10v	"	.25
1N759A	12v	"	.25
1N5243	13v	"	.25
1N5244B	14v	"	.25
1N5245B	15v	"	.25

SOCKETS/BRIDGES			
QTY.			
8-pin	pcb	.20	ww .35
14-pin	pcb	.20	ww .40
16-pin	pcb	.20	ww .40
18-pin	pcb	.25	ww .95
20-pin	pcb	.35	ww .95
22-pin	pcb	.35	ww .95
24-pin	pcb	.35	ww .95
28-pin	pcb	.45	ww 1.25
40-pin	pcb	.50	ww 1.25
Molex pins	.01	To-3 Sockets	.25
2 Amp Bridge	100-prv		.95
25 Amp Bridge	200-prv		1.50

TRANSISTORS, LEDS, etc.			
QTY.			
2N2222	(2N2222 Plastic .10)		.15
2N2222A			.19
2N2907A	PNP		.19
2N3906	PNP (Plastic Unmarked)		.10
2N3904	NPN (Plastic Unmarked)		.10
2N3054	NPN		.45
2N3055	NPN 15A 60v		.60
T1P125	PNP Darlington		1.95
LED Green	Red	Clear	Yellow .15
D.L.747	7 seg 5/8" High com-anode		1.95
MAN72	7 seg com-anode (Red)		1.25
MAN3610	7 seg com-anode (Orange)		1.25
MAN82A	7 seg com-anode (Yellow)		1.25
MAN74	7 seg com-cathode (Red)		1.50
FND359	7 seg com-cathode (Red)		1.25

9000 SERIES			
QTY.		QTY.	
9301	.85	9322	.65
9309	.35	9601	.20
9316	1.10	9602	.45

MICRO'S, RAMS, CPU'S, E-PROMS			
QTY.		QTY.	
8T13	1.50	2107B-4	4.95
8T23	1.50	2114	9.50
8T24	2.00	2513	6.25
8T97	1.00	2708	10.50
74S188	3.00	2716 D.S.	34.00
1488	1.25	2716 (5v)	59.00
1489	1.25	2758 (5v)	23.95
1702A	4.50	3242	10.50
AM 9050	4.00	4116	11.50
		6800	13.95
MM 5314	3.00	6850	7.95
MM 5316	3.50	8080	7.50
MM 5387	3.50	8212	2.75
MM 5369	2.95	8214	4.95
TR 1602B	3.95	8216	3.50
UPD 414	4.95	8224	3.25
Z 80 A	22.50	8228	6.00
Z 80	17.50	8251	7.50
Z 80 PIO	10.50	8253	18.50
2102	1.45	8255	8.50
2102L	1.75	TMS 4044	9.95

C MOS	
QTY.	
4000	.15
4001	.15
4002	.20
4004	3.95
4006	.95
4007	.20
4008	.75
4009	.35
4010	.35
4011	.20
4012	.20
4013	.40
4014	.75
4015	.75
4016	.35
4017	.75
4018	.75
4019	.35
4020	.85
4021	.75
4022	.75
4023	.20
4024	.75
4025	.20
4026	1.95
4027	.35
4028	.75
4029	1.15
4030	.30
4033	1.50
4034	2.45
4035	.75
4037	1.80
4040	.75
4041	.69
4042	.65
4043	.50
4044	.65
4046	1.25
4048	.95
4049	.45
4050	.45
4052	.75
4053	.75
4066	.55
4069/74C04	.35
4071	.25
4081	.30
4082	.30
4507	.95
4511	.95
4512	1.10
4515	2.95
4519	.85
4522	1.10
4526	.95
4528	1.10
4529	.95
MC 14409	14.50
MC 14419	4.85
74C151	1.50

LINEARS, REGULATORS, etc.			
QTY.		QTY.	
MCT2	.95	LM323K	5.95
8038	3.95	LM324	1.25
LM201	.75	LM339	.75
LM301	.45	7805 (340T5)	.95
LM308	.65	LM340T12	.95
LM309H	.65	LM340T15	.95
LM309K (340K-5)	1.50	LM340T18	.95
LM310	.85	LM340T24	.95
LM311D	.75	LM340K12	1.25
LM318	1.75	LM340K15	1.25
LM320H6	.79	LM340K18	1.25
LM320H15	.79	LM340K24	1.25
LM320H24	.79	LM373	2.95
7905 (LM320K5)	1.65	LM377	3.95
LM320K12	1.65	78L05	.75
LM320K24	1.65	78L12	.75
LM320T5	1.65	78L15	.75
LM320T12	1.65	78M05	.75
LM320T15	1.65		
		LM380 (8-14 Pin)	1.19
		LM709 (8-14 Pin)	.35
		LM711	.45
		LM723	.40
		LM725	2.50
		LM739	1.50
		LM741 (8-14)	.35
		LM747	1.10
		LM1307	1.25
		LM1458	.65
		LM3900	.50
		LM75451	.65
		NE555	.45
		NE556	.85
		NE565	.95
		NE566	1.25
		NE567	.95

- T T L -			
QTY.		QTY.	
7400	10	7482	.75
7401	15	7483	.75
7402	15	7485	.55
7403	15	7486	.25
7404	10	7489	1.05
7405	25	7490	.45
7406	25	7491	.70
7407	55	7492	.45
7408	15	7493	.35
7409	15	7494	.75
7410	15	7495	.60
7411	25	7496	.80
7412	25	74100	1.15
7413	25	74107	.25
7414	.75	74121	.35
7416	.25	74122	.55
7417	.40	74123	.35
7420	.15	74125	.45
7426	25	74126	.35
7427	25	74132	.75
7430	.15	74141	.90
7432	.20	74150	.85
7437	.20	74151	.65
7438	.20	74153	.75
7440	.20	74154	.95
7441	1.15	74156	.70
7442	.45	74157	.65
7443	.45	74161	.55
7444	.45	74163	.85
7445	.65	74164	.60
7446	.70	74165	1.10
7447	.70	74166	1.25
7448	.50	74175	.80
7450	25	74176	.85
7451	.25	74180	.55
7453	.20	74181	2.25
7454	.25	74182	.75
7460	.40	74190	1.25
7470	.45	74191	1.25
7472	.40	74192	.75
7473	.25	74193	.85
7474	.30	74194	.95
7475	.35	74195	.95
7476	.40	74196	.95
7480	.55	74197	.95
7481	.75	74198	1.45
		74221	1.00
		74367	.85
		75108A	.35
		75491	.50
		75492	.50
		74H00	.15
		74H01	.20
		74H04	.20
		74H05	.20
		74H08	.35
		74H10	.35
		74H11	.25
		74H15	.45
		74H20	.25
		74H21	.25
		74H22	.40
		74H30	.20
		74H40	.25
		74H50	.25
		74H51	.25
		74H52	.15
		74H53	.25
		74H55	.20
		74H72	.35
		74H74	.35
		74H701	.75
		74H103	.55
		74H106	.95
		74L00	.25
		74L02	.20
		74L03	.25
		74L04	.30
		74L10	.20
		74L20	.35
		74L30	.45
		74L47	1.95
		74L51	.45
		74L55	.65
		74L72	.45
		74L73	.40
		74L74	.45
		74L75	.85
		74L93	.55
		74L123	.85
		74LS00	.30
		74LS01	.30
		74LS02	.30
		74LS04	.30
		74LS05	.35
		74LS08	.35
		74LS09	.35
		74LS10	.35
		74LS11	.35
		74LS20	.30
		74LS21	.35
		74LS22	.35
		74LS32	.35
		74LS37	.35
		74LS38	.45
		74LS40	.40
		74LS42	.75
		74LS51	.45
		74LS74	.45
		74LS76	.50
		74LS86	.45
		74LS90	.65
		74LS93	.65
		74LS107	.50
		74LS123	1.20
		74LS151	.85
		74LS153	.85
		74LS157	.85
		74LS160	.95
		74LS164	1.20
		74LS193	1.05
		74LS195	.95
		74LS244	1.70
		74LS367	.95
		74LS368	.95
		74S00	.35
		74S02	.35
		74S03	.25
		74S04	.25
		74S05	.35
		74S08	.35
		74S10	.35
		74S11	.35
		74S20	.25
		74S40	.20
		74S50	.20
		74S51	.25
		74S64	.15
		74S74	.35
		74S112	.60
		74S114	.65
		74S133	.40
		74S140	.55
		74S151	.30
		74S153	.35
		74S157	.75
		74S158	.30
		74S194	1.05
		74S257 8123	1.05
		8131	2.75

CABLE ADDRESS: ICUSD

TELEX: H 697827

HOURS: 9 A.M. - 6 P.M. MON. thru SUN.

INTEGRATED CIRCUITS UNLIMITED

7889 Clairemont Mesa Blvd. • San Diego, California 92111 U.S.A.

NO MINIMUM

COMMERCIAL AND MANUFACTURING ACCOUNTS INVITED

ALL PRICES IN U.S. DOLLARS. PLEASE ADD POSTAGE TO COVER METHOD OF SHIPPING.
ORDERS OVER \$100 (U.S.) WILL BE SHIPPED AIR NO CHARGE.

PAYMENT SUBMITTED WITH ORDER SHOULD BE IN U.S. DOLLARS.

ALL IC'S PRIME/GUARANTEED ALL ORDERS SHIPPED SAME DAY RECEIVED.

CREDIT CARDS ACCEPTED:

Phone (714) 278-4394 BarclayCard / Access / American Express / BankAmericard / Visa / MasterCard

SPECIAL DISCOUNTS

Total Order	Deduct
\$35-\$99	10%
\$100-\$300	15%
\$301-\$1000	20%

RADIO & ELECTRONICS CONSTRUCTOR

AUGUST 1979
Volume 32 No. 12

Published Monthly
(3rd of preceding Month)

First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LDNDDN W9 1SN

Telephone 01-286 6141 Telegrams Databux, London

© Data Publications Ltd., 1979. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £7.50, Overseas £8.50 (U.S.A. and Canada \$18.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production— Web Offset.

THE "DORIC" 9 WAVEBAND PORTABLE — Part 1 by Sir Douglas Hall, Bt., K.C.M.G.	726
NEWS AND COMMENT	732
MULTIPLE 555 CIRCUITS — Suggested Circuit by G. A. French	734
SQUARE WAVE TRANSISTOR TESTER by R. A. Penfold	737
VISUAL METRONOME WITH DOWNBEAT by Paul M. Jessop	742
HOW MICROPROCESSORS WORK — Databus No. 1 by Ian Sinclair	744
SHORT WAVE NEWS — For DX Listeners by Frank A. Baldwin	748
BEGINNER'S MEDIUM WAVE RADIO by I. M. Attrill	750
AN ENTREE TO SOLDERLESS BREADBOARDING	754
BUG HUNTING — Tune-In To Programs by Ian Sinclair	755
PROBLEMS WITH SYNC — In Your Workshop	758
NEW PRODUCT — Z.I.P. D.I.P. Socket	763
SIREN SOUNDER — Double Deccer Series by Ian Sinclair	764
RADIO TOPICS by Recorder	766
ANNUAL INDEX	774
BOOTSTRAPPING — Electronics Data No. 48 For The Beginner	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The *Radio & Electronics Constructor* is printed by Swale Press Ltd.

**THE SEPTEMBER ISSUE
WILL BE PUBLISHED
ON 6th AUGUST**


<p>MOTORS 1-5 to 6VDC Model Motors, 20p. Sub. Min. "Big Inch" Precision motors, 115VAC 3 rpm, 30p. 12VDC 5 Pole Model Motors 35p. 8 track 12VDC motors, new £1.25. Cassette Motors 6VDC ex. equip., 85p. Crouze geared motor, 115VAC 4 rpm new 95p. Smiths clock motor, synchronous 240VAC 1 rev per hour £1.75.</p>	<p>TRANSFORMERS All 240VAC Primary (postage per transformer is shown after price). MINIATURE RANGE: 6-0-6V 100mA, 9-0-9V 75mA and 12-0-12V 50mA all 73p each (15p). 12-0-12V 100mA 90p (15p). 0-8V, 0-6V, 280mA £1.10 (20p). 0-4-6-9V 200mA these have no mounting bracket, 65p (15p). 12V 500mA 95p (22p). 12V 2 amp £2.75 (45p). 15-0-15V 3 amp Transformer at £2.50 (54p). 30-0-30V 1 amp £2.75 (54p). 20-0-20V 2 amp £3.50 (54p). 0-12-15-20-24-30V 2 amp £4.50 (54p). 20V 2.5 amp £2.20 (54p).</p>	<p>FETS/SCRS ETC Union carbide N channel FET similar to 2n3819 15p each. 3N140 or BFV61 types 40p each. M203 dual matched pair of single gate mosfets in one can 40p. 2N5062 plastic (TO92) SCR 100V 800mA 18p each. BX504 Opto isolators, 4 lead infra red led to photocell 25p each.</p>	<p>AEROSOL SERVICE AIDS, SERVISOL Switch Cleaner 226gm 54p. Freezer 226gm 65p. Silicone Grease 226gm 68p. Foam Cleanser 370gm 55p. Plastic Seal 145gm 55p. Excel Polish 240gm 40p. Aero Klene 170gm 45p. Aero Duster 200gm 58p.</p>	<p>TOOLS SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.75 (spare nozzles 65p each). Good Quality side cutters, insulated handles, 5" £1.35. Good Quality snub nosed pliers, insulated handles, 5" £1.35. Antex Model C 15 watt soldering irons, 240VAC £3.60. Antex Model CX 17 watt soldering irons, 240VAC £3.60. Antex Model X25 25 watt soldering irons, 240VAC £3.60. Antex ST3 iron stands, suits all above models £1.40. Antex heat shunts 12p each. Servisol Solder Mop 45p each. Neon Tester Screwdrivers 8" long 40p each. Miyama IC test clips 16 pin £1.75.</p>
<p>SEMICONDUCTORS All full spec. devices. 741 8 pin 6 for £1. No. 555 Timers 22p each. TBA800 audio IC's 50p. 741S (wide bandwidth) 35p. LM380 80p. ZN414 Radio IC 75p. LM3900 40p each. TIL305 alpha numerical displays £2.50. Miniature LDR's (same spec. as ORP12) 30p.</p>	<p>TRIAC/XENON PULSE TRANSFORMERS 1:1 (gpo style) 30p. 1:1 plus 1 sub. min. pcb mounting type 60p each.</p>	<p>DIODES IN4001 10 for 35p. IN4004 10 for 45p. IN4007 10 for 50p. BY127 10 for 75p. IN914 (numbered) 100 for £2.50. IN4148 (numbered) 100 for £2.25.</p>	<p>SURPLUS BOARDS No. 1, this has at least 11 C106 (50V 2.5A) plastic SCR's, one relay a unijunction transistor and tantalum capacitors £1.95. No. 2 I.F. Boards, these are a complete I.F. board assembly made for car radios, 465Khz, full set of I.F.'s and oscillator coils, trimmers etc., 40p each. No. 3 Lamp flasher board, suitable for low load 240VAC applications, approx. 1 flash per second but can be varied via preset pot. 38p each.</p>	<p>SWITCHES Sub. miniature toggles; SPST (8 x 5 x 7mm) 45p. DPDT 8 x 7 x 7mm 50p. DPDT centre off 12 x 11 x 9mm 75p. PUSH SWITCHES, 16 x 6mm, red top, push to make 14p each, push to break version (black top) 16p each. SLIDE SWITCHES, all DPDT; 15 x 8 x 12mm 12p, 16 x 11 x 9mm 12p, 22 x 13 x 8mm 12p, 22 x 13 x 8mm centre off 13p. Multipole slider, double action 12 tags 29 x 9 x 11mm 24p.</p>
<p>PROJECT BOXES Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 53p. 95 x 71 x 35mm 62p. 115 x 95 x 37mm 72p.</p>	<p>MICROPHONES ECM105 Condenser, Omni Directional, 600 ohms, on/off switch £2.95. EM506 Condenser Cardiod, Uni directional, 600 or 50K ohms 30-18Khz, heavy chromed copper case £12.95. DYNAMIC Stick mike, 5,000 ohms, on/off switch, fitted with std. jack £2.95. EM104 Sub. miniature tie pin condenser microphone, 1,000 ohms imp., 50-16Khz., uses deaf aid battery (supplied) £5.25. STANDARD CASSETTE MIKES, 200 ohms, fitted with 2.5/3.5mm jacks, on/off switch £1.25.</p>	<p>MURATA MA401 40Khz Transducers. Rec./Sender £3.25 pair.</p>	<p>POWER SUPPLIES SWITCHED TYPE, plugs into 13 amp socket, has 3-4.5-6-7.5 and 9 volt DC out at either 100 or 400mA, switchable £3.25. HC244R STABILISED SUPPLY, 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £5.25.</p>	<p>MICRO SWITCHES Standard button operated 28 x 25 x 8mm make or break, new 15p each. Roller operated version of the latter, New 19p each. Light action micro, 3 amp make or break 35 x 20 x 7mm, 12p each. Cherry plunger operated micro, 2 normally open, 2 normally closed, plunger 20mm long (40 x 30 x 18mm) 25p each.</p>
<p>VERO POTTING BOXES 49 x 71 x 24mm, available in black or white with lid and 4 screws 39p each.</p>	<p>REPLACEMENT CRYSTAL INSERTS 35mm diam. x 10mm deep 45p each</p>	<p>ELECTRICAL ITEMS 12 way Choc Blocks 2 amp or 5 amp 18p per strip. 13 amp Rubber Extension Sockets, white 38p each. 13 amp Plastic Fused Plugs (foreign) 25p each.</p>	<p>TOSHIBA LEDS TLG113 0.2" Green 13p. TLG115 0.2" Green diffused lens 14p. TLG1070 0.2" Green Flat top 14p. TLR120 0.2" Clear 17p. MAN3A min. (3MM) 7 segment LED displays Comm. anode 40p.</p>	<p>ROCKER SWITCHES 2 amp SPST, single nut mounting, various colours (red, green, white, blue, yellow, black) 19p each. 250VAC 6amp rocker (all white) 21 x 15 x 13mm 17p each.</p>
<p>VERO 'HAND HELD BOX' White ABS, 2.4" x 3.7" tapered, with screws 65p each.</p>	<p>RIBBON CABLE 8 way single strand miniature 20p per metre.</p>	<p>PUSH BUTTON TV TUNERS UHF, not varicap, transistorised new £2.25</p>	<p>BUZZERS MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, four voltage types available, 6-9-12 or 24VDC, 75p each. LOUD 12VDC BUZZER, Cream plastic case, 50mm diam. x 30mm high 60p. GPO OPEN TYPE BUZZER, adjustable, works 6-12VDC 25p each. SIRENS 125mm diameter gold coloured horn, high pitched wailing note of varying frequency, 12VDC £7.45.</p>	<p>TAPE HEADS Mono cassette £1.60. Stereo cassette £3.40. Standard 8 track stereo £1.75. BSR MN1330 1/2 track 50p. BSR SRP90 1/2 track £1.95. TD10 tape head assembly - 2 heads both 1/2 track R/P with built in erase, mounted on bracket £1.20.</p>
<p>MULTIMETERS Big price reductions on pocket size testers. Model KRT100, 1,000 ohms per volt, mirror scale, range selector switch 1,000 volts AC/DC, 100K resistance, 150mA DC current £4.65. Model KRT101, same spec. as the KRT100 but range selection is via prod insertion £3.75.</p>	<p>SPECIAL OFFER SEMICONDUCTORS Plastic voltage regulators, 1 amp all now reduced in price, 7805, 7812, 7815, 7824 all 75p each. 7905, 7912, 7915, 7924 all 99p each. 2N3055 - 36p. 1,000 volt 2 amp wire-ended bridge rectifiers, 37p. 723 14 pin regulators 40p each.</p>	<p>TELEPHONE PICK UP COIL Sucker type with lead and 3.5mm plug 55p</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>RELAYS Clare Elliot sub. min. sealed relay 10 x 10mm 2 pole C/O, 1.250 ohm coil, new 75p. Miniature encapsulated reed relay U.1 matrix mounting, single pole make, operates on 12VDC 50p each. Continental series, sealed plastic case relays, 24VDC 3pole change over 5 amp contacts, new 65p. Printed circuit Mtg., Reed relay, single make, 20mm x 5mm. 6-9VDC. coil, 33p each. Metal Cased Reed Relay, 50 x 45 x 17mm, has 4 heavy duty make reed inserts, operates on 12VDC 35p each.</p>
<p>CONTINUITY TESTERS Tubular with probe and croc. fly lead £1.35, with batts.</p>	<p>DOE TO VAT INCREASE PLEASE ADD 4% TO PRICES</p>	<p>DUE TO VAT INCREASE PLEASE ADD 4% TO PRICES</p>	<p>REPLACEMENT CRYSTAL INSERTS 35mm diam. x 10mm deep 45p each</p>	<p>BUZZERS MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, four voltage types available, 6-9-12 or 24VDC, 75p each. LOUD 12VDC BUZZER, Cream plastic case, 50mm diam. x 30mm high 60p. GPO OPEN TYPE BUZZER, adjustable, works 6-12VDC 25p each. SIRENS 125mm diameter gold coloured horn, high pitched wailing note of varying frequency, 12VDC £7.45.</p>
<p>MORSE KEYS Beginners practise key 95p. All metal fully adjustable type £2.45.</p>	<p>DOE TO VAT INCREASE PLEASE ADD 4% TO PRICES</p>	<p>DOE TO VAT INCREASE PLEASE ADD 4% TO PRICES</p>	<p>REPLACEMENT CRYSTAL INSERTS 35mm diam. x 10mm deep 45p each</p>	<p>BUZZERS MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, four voltage types available, 6-9-12 or 24VDC, 75p each. LOUD 12VDC BUZZER, Cream plastic case, 50mm diam. x 30mm high 60p. GPO OPEN TYPE BUZZER, adjustable, works 6-12VDC 25p each. SIRENS 125mm diameter gold coloured horn, high pitched wailing note of varying frequency, 12VDC £7.45.</p>
<p>MINIATURE LEVEL METERS 1 Centre Zero 17 x 17mm 75p. 2 (scaled 0-10) 28 x 25mm 75p. 3 Grundig 40 x 27mm £1.25.</p>	<p>DOE TO VAT INCREASE PLEASE ADD 4% TO PRICES</p>	<p>DOE TO VAT INCREASE PLEASE ADD 4% TO PRICES</p>	<p>REPLACEMENT CRYSTAL INSERTS 35mm diam. x 10mm deep 45p each</p>	<p>BUZZERS MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, four voltage types available, 6-9-12 or 24VDC, 75p each. LOUD 12VDC BUZZER, Cream plastic case, 50mm diam. x 30mm high 60p. GPO OPEN TYPE BUZZER, adjustable, works 6-12VDC 25p each. SIRENS 125mm diameter gold coloured horn, high pitched wailing note of varying frequency, 12VDC £7.45.</p>
<p>JUMPER TEST LEAD SETS 10 pairs of leads with various coloured croc clips each end (20 clips) 80p per set.</p>	<p>DOE TO VAT INCREASE PLEASE ADD 4% TO PRICES</p>	<p>DOE TO VAT INCREASE PLEASE ADD 4% TO PRICES</p>	<p>REPLACEMENT CRYSTAL INSERTS 35mm diam. x 10mm deep 45p each</p>	<p>BUZZERS MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, four voltage types available, 6-9-12 or 24VDC, 75p each. LOUD 12VDC BUZZER, Cream plastic case, 50mm diam. x 30mm high 60p. GPO OPEN TYPE BUZZER, adjustable, works 6-12VDC 25p each. SIRENS 125mm diameter gold coloured horn, high pitched wailing note of varying frequency, 12VDC £7.45.</p>
<p style="text-align: center;">PROGRESSIVE RADIO 31 CHEAPSIDE, LIVERPOOL 2.</p>				

THREE FOR FREE FROM CSC

ELECTRONICS BY NUMBERS
FREE PROJECTS
 No 1, No 2,
 & No 3.

ELECTRONICS BY NUMBERS LED BAR GRAPH UNIVERSAL INDICATOR

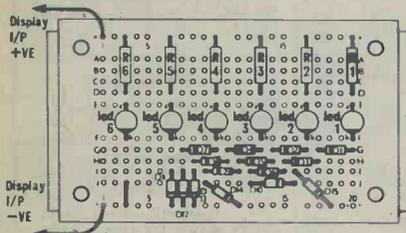Now using **EXPERIMENTOR BREADBOARDS** and following the instructions in "Electronics by numbers" ANYBODY can build electronic projects. Look at the diagram and select R1, this is a resistor with a value between 120 to 270 ohm. Plug it into holes X20 and D20, now take LED 1 and plug it into holes E20 and F20. Do the same with the Diodes e.g. plug D7 into holes G7 and G10.



YOU WILL NEED

EXP. ANY EXPERIMENTOR BREADBOARD
D1 to D15 - Silicon Diodes (such as 1N914)
R1 to R6 - From 120-270 ohm resistors ¼ watt.
LED1 to LED6 - Light emitting diodes.

LED BAR GRAPHS are replacing analogue meters as voltage-level indicators in many instances.

This circuit uses the forward voltage drop of diodes to determine how many LEDs light up. Any type of diode can be used but you must use all the same type. For full working details of this circuit fill in the coupon. If you have already built the Two-transistor Radio and the Fish'n'clips projects you will find that you can reuse the components from these projects to build other projects in the series.

FILL IN THE COUPON AND WE WILL SEND YOU FREE OF CHARGE FULL COPIES OF "ELECTRONICS BY NUMBERS" PROJECTS No 1, No 2 and No 3.

PROTO-CLIP TEST CLIPS.

Brings IC leads up from crowded PC boards. Available plain or with cable with clips at one or both ends.



- PC - 16 pin. £2.75.
- PC - 16 pin with cable. £6.00.
- PC - 16 with cable and 16 pin clips at both ends. £10.25.


EXPERIMENTOR BREADBOARDS.

No soldering modular breadboards, simply plug components in-and out of letter number identified nickel-silver contact holes. Start small and simply snap-snap boards together to build breadboard of any size. All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP.4B.


EXP.325. The ideal breadboard for 1 chip circuits. Accepts 8,14,16 and up to 22 pin-IC's. **ONLY £1.60.**




EXP.350. £3.15. 270 contact points with two 20-point bus-bars.

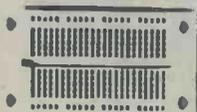

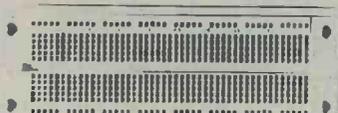EXP. 300. 550 contacts with two 40-point bus-bars. **£5.75.**



EXP. 650 for Micro-processors. **£3.60.**

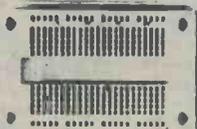


EXP 4B. More bus-bars. **£2.30.**



ALL EXP.300 Breadboards mix and match with 600 series.

PROTO-BOARDS.

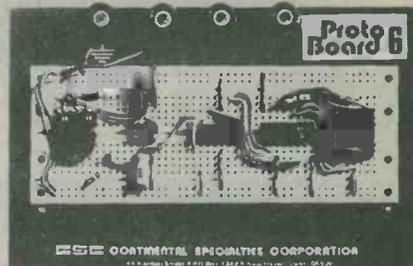THE ULTIMATE IN BREADBOARDS FOR THE MINIMUM COST. TWO EASILY ASSEMBLED KITS.



PB.6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips. **PROTO-BOARD 6 KIT. £9.20.**



PB.100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy. **PROTO-BOARD 100 KIT £11.80.**

HOW TO ORDER AND RECEIVE FREE COPY OF TWO-TRANSISTOR RADIO PROJECT, FISH'N'CLIPS AND LED BAR GRAPH.

CSC UK LTD. Dept. 16T2, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ. It's easy. Give us your name and full postal address, in block capitals. Enclose cheque, postal order or credit card number and expiry date. OR telephone 0799 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post that night.

EXPERIMENTOR BREADBOARDS.	CONTACT HOLES.	IC CAPACITY 14 PIN.DIP.	UNIT PRICE INCLUDING POSTAGE AND V.A.T. (15%)
EXP. 325	130	1	£ 2.70
EXP. 350	270	3	£ 4.48
EXP. 300	550	6	£ 7.76
EXP. 650	270	use with 0.6 pitch Dip's Bus-Bar Strip	£ 4.99
EXP. 4B.	Four 40 Point Bus-Bars		£ 3.51
TEST CLIPS			
PC. 16.			£ 4.03
PC.16-18.			£ 8.05
PC. 16-18 Dual Clip.			£12.94
PROTO-BOARDS.			
PB. 6.	630	6	£11.73
PB. 100.	760	10	£14.72
NAME			
ADDRESS			



Europe, Africa, Mid-East: **CSC UK LTD.**
 Dept. 16T2, Unit 1,
 Shire Hill Industrial Estate,
 Saffron Walden, Essex CB11 3AQ,
 Telephone: SAFFRON WALDEN 21682.
 Telex: 817477.

**FILL IN COUPON & RECEIVE FREE COPY OF
 ELECTRONICS BY NUMBERS PROJECTS Nos 1, 2 AND 3**

SEMICONDUCTORS - COMPONENTS

CERAMIC PAK

16160 - 24 - 3 of each value - 22pf
27pf 33pf 39pf 47pf 56pf 82pf **£0.67**
16161 - 24 - 3 of each value - 100pf
120pf 150pf 180pf 220pf 270pf 330pf
390pf **£0.67**
16162 - 24 - 3 of each value - 470pf
560pf 680pf 820pf 1000pf 1500pf
2200pf 3300pf **£0.67**
16163 - 24 - 3 of each value - 4700pf
6800pf 01uf 015uf 022uf 033uf
047uf **£0.57**

ELECTROLYTIC PAKS

A range of paks each containing 18
first quality, mixed value miniature
electrolytics.

16201 - Values from 47mFD -
10mFD **£0.65**
16202 - Values from 10mFD -
100mFD **£0.65**
16203 - Values from 100mFD -
680mFD **£0.65**

CARBON RESISTOR PAKS

These paks contain a range of Carbon
Resistors assorted into the following
groupings.

16213 - 60 mixed $\frac{1}{2}$ W 100 ohms - 820
ohms **£0.67**
16214 - 60 mixed $\frac{1}{2}$ W 1K ohms - 82k
ohms **£0.67**
16215 - 60 mixed $\frac{1}{2}$ W 10K ohms - 83K
ohms **£0.67**
16216 - 60 mixed $\frac{1}{2}$ W 100K ohms -
820K ohms **£0.67**
16217 - 40 mixed $\frac{1}{2}$ W 100 ohms - 820
ohms **£0.67**
16218 - 40 mixed $\frac{1}{2}$ W 1K ohms - 82K
ohms **£0.67**
16219 - 40 mixed $\frac{1}{2}$ W 10K ohms - 82K
ohms **£0.67**
16220 - 40 mixed $\frac{1}{2}$ W 100K ohms -
820K ohms **£0.67**
16230 - 80 mixed $\frac{1}{2}$ W 1 Meg - 10 Meg
ohms **£0.67**
16231 - 40 mixed $\frac{1}{2}$ W 1 Meg - 10 Meg
ohms **£0.67**

COMPONENT PAKS

16164 - 200 Resistor mixed value approx
(Count by weight) **£0.67**
16165 - 150 Capacitors mixed value
approx (Count by weight) **£0.67**
16166 - 50 Precision resistors. Mixed
values **£0.67**
16167 - 80 $\frac{1}{2}$ W resistors. Mixed
values **£0.67**
16168 - 5 pieces assorted ferrite rods
£0.67

16169 - 2 Tuning gangs MW/LW
VHF **£0.67**
16170 - 1 Pack wire 50 metres
assorted colours single strand **£0.65**
16171 - 10 Read switches **£0.67**
16172 - 3 Micro switches **£0.67**
16173 - 15 Assorted pots **£0.67**
16174 - 5 Metal jack sockets 3 x
3.5mm 2 x standard switch types **£0.67**
16175 - 30 Paper condensers - mixed
values **£0.67**
16176 - 20 Electrolytics **£0.67**
types
16177 - 1 pak assorted hardware -
Nuts, bolts, gromets etc. **£0.64**
16178 - 5 Mains slide switches
assorted **£0.67**
16179 - 20 Assorted tag strips and
panels **£0.65**
16180 - 15 Assorted control knobs
£0.67

16181 - 3 Rotary wave change
switches **£0.67**
16182 - 2 Relays 6-2 v
operating **£0.67**
16183 - 1 Pak copper laminate approx
200 sq inches **£0.66**
16184 - 15 Assorted Fuses 100mA 5
amp **£0.65**
16185 - 50 metres PVC sleeving
assorted size and colours **£0.66**

METAL FOIL CAPACITOR PAK

16204 - Containing 50 metal foil
capacitor like Mullard C250 series
Mixed values ranging from 0.1uf - 2.2uf.
Complete with Identification
sheet **£1.35**

SLIDER PAKS

16190 - 5 slider potentiometers mixed
values **£0.67**
16191 - 6 slider potentiometers all 470
ohm **£0.67**
16192 - 6 slider potentiometers all 10K
ohm 1in **£0.67**
16193 - 6 slider potentiometers all 10K
ohm 1in **£0.67**
16194 - 6 slider potentiometers all 47K
ohm 1in **£0.67**
16195 - 6 slider potentiometers all 47K
log **£0.67**

TRANSISTORS

BRAND NEW - FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	£0.23	AD140	£0.64	BC120	£0.43	BC23B	£0.18	BF127	£0.98	TS43	£0.24
AC113	£0.21	AD142	£0.91	BC125	£0.19	BC251	£0.17	BF152	£0.26	TS60	£0.20
AC115	£0.21	AD143	£0.81	BC126	£0.25	BC251A	£0.18	BF153	£0.27	UT46	£0.22
AC117	£0.32	AD149	£0.84	BC132	£0.20	BC301	£0.38	BF154	£0.24	2N706	£0.11
AC117K	£0.32	AD161	£0.37	BC134	£0.20	BC302	£0.31	BF155	£0.38	2N707	£0.52
AC121	£0.21	AD182	£0.37	BC135	£0.17	BC303	£0.30	BF156	£0.32	2N708	£0.15
AC122	£0.16	AD161/	£0.37	BC136	£0.20	BC304	£0.41	BF157	£0.32	2N1302	£0.18
AC125	£0.19	162	£0.75	BC137	£0.20	BC327	£0.18	BF158	£0.28	2N1303	£0.18
AC126	£0.19	ADT140	£0.59	BC139	£0.35	BC328	£0.17	BF159	£0.32	2N1304	£0.18
AC127	£0.19	ADT14	£0.27	BC140	£0.32	BC337	£0.17	BF160	£0.34	2N1305	£0.19
AC128	£0.17	AF115	£0.27	BC141	£0.30	BC338	£0.17	BF162	£0.34	2N1306	£0.27
AC128K	£0.28	AF126	£0.32	BC142	£0.24	BC440	£0.33	BF163	£0.34	2N1307	£0.27
AC132	£0.21	AF117	£0.27	BC143	£0.24	BC441	£0.33	BF178	£0.28	2N2369	£0.15
AC134	£0.21	AF118	£0.43	BC145	£0.52	BC460	£0.41	BF165	£0.54	2N1309	£0.32
AC137	£0.21	AF124	£0.32	BC147	£0.08	BC461	£0.41	BF167	£0.27	2N1711	£0.22
AC141	£0.32	AF125	£0.32	BC148	£0.08	BC467	£0.22	BF173	£0.22	2N2219	£0.22
AC142	£0.21	AF127	£0.34	BC149	£0.08	BC476	£0.22	BF176	£0.41	2N2221	£0.22
AC142K	£0.32	AF139	£0.37	BC151	£0.25	BC547	£0.11	BF177	£0.28	2N2222	£0.22
AC151	£0.21	AF178	£0.64	BC152	£0.23	BC548	£0.11	BF179	£0.26	2N2711	£0.24
AC153	£0.23	AF179	£0.64	BC153	£0.28	BC549	£0.11	BD239A/	£0.22	2N2712	£0.24
AC153K	£0.32	AF180	£0.64	BC154	£0.21	BC550	£0.18	240AMP	£1.00	2N2714	£0.24
AC154	£0.21	AF181	£0.64	BC155	£0.21	BC556	£0.18	BF180	£0.32	2N2904	£0.19
AC155	£0.21	AF186	£0.54	BC158	£0.11	BC557	£0.18	BF181	£0.32	2N2905	£0.19
AC156	£0.21	AF239	£0.41	BC159	£0.11	BC558	£0.14	BF182	£0.32	2N2906	£0.17
AC157	£0.27	AL102	£1.29	BC160	£0.28	BC559	£0.16	BF183	£0.32	2N2907	£0.22
AC165	£0.21	AL103	£1.27	BC161	£0.41	BCY30	£0.59	BF184	£0.22	2N2923	£0.17
AC166	£0.21	AL126	£0.41	BC167	£0.17	BCY31	£0.59	BF185	£0.22	2N2924	£0.17
AC167	£0.21	ASV2	£0.84	BC168	£0.14	BCY32	£0.59	BF186	£0.29	2N2925	£0.17
AC168	£0.27	ASV2	£0.84	BC169	£0.19	BCY33	£0.59	BF187	£0.29	2N2926	£0.17
AC169	£0.21	ASV29	£0.41	BC169C	£0.41	BCY34	£0.58	BF188	£0.43	2N2927	£0.09
AC171	£0.27	ASV50	£0.32	BC170	£0.10	BCY70	£0.18	BF194	£0.11	2N2928	£0.09
AC176	£0.19	ASV51	£0.32	BC171	£0.10	BCY71	£0.18	BF195	£0.11	2N2928R	£0.09
AC176K	£0.28	ASV52	£0.32	BC172	£0.10	BCY72	£0.18	BF196	£0.11	2N2928G	£0.09
AC178	£0.27	ASV54	£0.32	BC173	£0.10	BCZ10	£0.66	BF197	£0.14	2N2929	£0.09
AC179	£0.27	ASV55	£0.32	BC174	£0.17	BCZ11	£0.66	BF198	£0.16	2N3053	£0.17
AC180	£0.21	ASV56	£0.32	BC175	£0.39	BCZ12	£0.65	BF199	£0.16	2N3055	£0.43
AC180K	£0.30	ASV57	£0.32	BC177	£0.17	BD115	£0.54	MJE340	£0.49	2N3402	£0.24
AC181K	£0.30	ASV73	£0.32	BC179	£0.17	BD116	£0.88	MJE2955	£0.97	2N3403	£0.24
AC187	£0.19	AU104	£1.51	BC180	£0.27	BD121	£0.70	MJE3055	£0.85	2N3404	£0.33
AC187K	£0.30	AU110	£1.51	BC181	£0.28	BD122	£0.70	TIP29A	£0.43	2N3405	£0.47
AC188	£0.18	AU113	£1.51	BC182	£0.10	BD131	£0.38	TIP29B	£0.46	2N3702	£0.09
AC188K	£0.30	BC107	£0.09	BC182L	£0.10	BD132	£0.38	TIP30A	£0.43	2N3703	£0.09
AC197	£0.37	BC107A	£0.09	BC183	£0.10	BD131/	£0.38	TIP30B	£0.45	2N3705	£0.08
AC198	£0.37	BC107B	£0.11	BC184	£0.10	132MP	£0.88	TIP30C	£0.48	2N3706	£0.08
AC199	£0.37	BC107C	£0.11	BC184	£0.10	BD133	£0.38	TIP31A	£0.48	2N3707	£0.08
AC200	£0.37	BC108	£0.09	BC184L	£0.10	BD135	£0.41	TIP31B	£0.45	2N3708	£0.08
AC201	£0.37	BC108A	£0.09	BC186	£0.24	BD136	£0.38	TIP31C	£0.48	2N3709	£0.08
AC202	£0.37	BC108B	£0.10	BC187	£0.24	BD137	£0.38	TIP32A	£0.43	2N3710	£0.08
AC203	£0.37	BC108C	£0.11	BC207	£0.12	BD138	£0.38	TIP32B	£0.45	2N3711	£0.08
AC204	£0.37	BC109	£0.09	BC208	£0.10	BD139	£0.38	TIP32C	£0.48	2N3772	£1.73
AC205	£0.37	BC109A	£0.10	BC209	£0.14	BD140	£0.38	TIP31A	£0.48	2N3773	£1.73
AC206	£0.37	BC109B	£0.11	BC210	£0.10	BD139/	£0.38	TIP41B	£0.50	2N3819	£0.18
AC207	£0.37	BC109C	£0.11	BC212	£0.10	140MP	£0.88	TIP41C	£0.52	2N3820	£0.38
AC208	£0.37	BC113	£0.18	BC213	£0.10	BF115	£0.24	TIP42A	£0.48	2N3821	£0.65
AC209	£0.37	BC114	£0.18	BC213L	£0.10	BF117	£0.24	TIP42B	£0.50	2N3823	£0.65
AC210	£0.37	BC115	£0.18	BC214	£0.10	BF118	£0.24	TIP42C	£0.52	2N3903	£0.11
AC211	£0.37	BC116	£0.18	BC214L	£0.10	BF119	£0.64	TIP2955	£0.85	2N3904	£0.11
AD130	£0.75	BC119	£0.27	BC225	£0.29	BF121	£0.56	TIP2955	£0.85	2N3905	£0.11
				BC226	£0.41	BF123	£0.56	TIP3055	£0.54	2N3906	£0.11
				BC227	£0.18	BF125	£0.56				

74 SERIES TTL IC's


Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
7400	£0.10	7422	£0.17	7448	£0.80	7489	£1.84	74123	£0.43	74174	£0.70
7401	£0.12	7423	£0.20	7449	£0.80	7490	£0.88	74136	£0.58	74175	£0.87
7402	£0.12	7425	£0.20	7451	£0.12	7491	£0.88	74141	£0.59	74176	£0.83
7403	£0.12	7426	£0.25	7453	£0.12	7492	£0.38	74145	£0.59	74177	£0.83
7404	£0.12	7427	£0.26	7454	£0.12	7493	£0.32	74150	£0.59	74178	£0.83
7405	£0.12	7428	£0.28	7460	£0.12	7494	£0.32	74151	£0.52	74181	£0.63
7406	£0.12	7429	£0.28	7461	£0.12	7495	£0.54	74153	£0.52	74182	£0.76
7407	£0.12	7430	£0.28	7472	£0.22	7496	£0.54	74154	£0.88	74184	£0.76
7408	£0.12	7431	£0.32	7473	£0.22	7497	£1.00	74155	£0.54	74185	£0.76
7409	£0.12	7432	£0.23	7474	£0.27	74100	£0.42	74156	£0.54	74186	£0.73
7410	£0.12	7433	£0.23	7475	£0.21	74101	£0.42	74157	£0.54	74187	£0.87
7411	£0.18	7434	£0.23	7476	£0.27	74102	£0.26	74160	£0.83	74193	£0.83
7412	£0.18	7441	£0.13	7476	£0.48	74107	£0.39	74161	£0.87	74194	£0.87
7413	£0.26	7442	£0.43	7480	£0.48	74110	£0.83	74162	£0.87	74195	£0.85
7414	£0.54	7443	£0.78	7481	£0.92	74111	£0.83	74163	£0.87	74196	£1.13
7415	£0.26	7444	£0.78	7482	£0.71	74118	£0.88	74164	£0.73	74197	£1.13
7416	£0.26	7445	£0.78	7483	£0.93	74119	£1.27	74165	£0.73	74198	£2.00
7417	£0.25	7446	£0.78	7484	£0.96	74121	£0.26	74166	£0.84	74199	£2.00
7418	£0.12	7446	£0.85	7485	£0.73	74122	£0.				

Technologically for sale.

The Mark III FM Tuner

DIY Hi Fi will never seem the same again. Ambit's Mark III tuner system is electrically & visually superior to all others. Some options available, but the illustrated version with reference series modules:

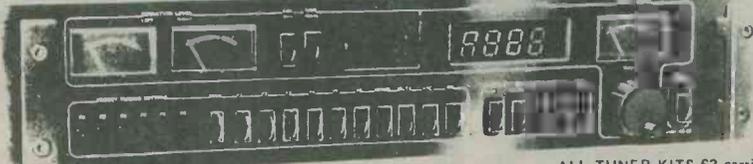£149.00 + £18.62 VAT
With Hyperfi Series modules
£185.00 + £23.12



ALL TUNER KITS £3 carriage

Features of the system:

- * Precision construction & design of all parts
- * Time frequency display
- * State of the art performance with facilities for updates, using modular plug in systems.
- * Deviation level calibrator for recording
- * All usual tuner features

Digital Dorchester All Band Broadcast Tuner: LW/MW/SW/SW/FM stereo

A multiband superhet tuner, constructed using a single IC for RF/IF processing - but with all features you would expect of designs of far greater complexity. The FM section uses a three section (air gang) tuned FET tunerhead, with ceramic IF filters and interstation mute; AM employs a double balanced mixer input stage, with mechanical IF filters - plus a BFO and MOSFET product detector for CW/SSB reception. Styled in a matching unit to the Mark III FM only tuner, employing the same degree of care in mechanical design to enable easy construction. MW/LW reception via a ferrite rod antenna.

Electronics only (PCB and all components thereon) £33.00 + £4.12 VAT
Complete with digital frequency readout/clock timer hardware £99.00 + £12.37 VAT
Complete with MA1023 clock/timer module with dial scale £66.00 + £8.25 VAT
Hardware packages are available separately if you wish to house your own designs in a professional case structure. Please deduct the cost of electronics from complete prices.

LW MW/FM LCD Digital Frequency Display - July PW feature

Update your old radio, or build this into a new design. Or use it as a servicing aid - this low power unit with LCD display reads direct frequency in kHz/MHz, or with usual AM/FM IF offsets for received frequency. Low power LCD means no RF! - 15-20mA at 9v even with the divide by 100 prescaler. FM resolution is 100kHz, AM 1kHz. Sensitivities better than 10mV. Complete kit £19.50 + *£1.56 VAT. Built and tested version £24.00 + *£1.92 VAT. Various other DFM systems described in our catalogue part 2 - including a one chip solution to providing digital display of FRG7 kHz dial, combined with clock/timers etc.



PW SANDBANKS PI METAL LOCATOR

Maintaining our professional approach to home constructor kits, we offer the pulse induction 'Sandbanks'. Now with injection molded casing for greatly improved environmental sealing. £37.00 + *£2.96vat.

VHF MONITOR RX WITH PLESSEY IC

4/9 channel version of the PW design - but using standard 3rd OT crystals, and TOYO 8 pole crystal filter with matching transformers. Coil sets from our standard range to cover bands from 40 to 200MHz. Complete module kit £31.25 + *£3.90vat.

ETI - REMCON RADIO CONTROL

A tried and tested RC system with a full set of supporting hardware from a well known manufacturer. Please send for details - and watch our ads for further news of developments in RC products.

Radio and Audio Modules : The biggest range/ best specs:

EF5801/3/4 6 stage varicap tunerheads with LO feed and various levels of sophistication. New 5804 include pin AGC loop 'on board'. 5801:£17.45+£2.18vat - 5803:£19.75+£2.47vat - 5804:£24.95+£3.18vat. Frequencies in 40-180MHz on apcn. EF5402 4 stage varicap with TDA1062, compound FET/Bipolar input stage, low noise, balanced mixer, pin agc, osc output. A worthy successor to the 5400. £10.75+£1.34vat
The 5402 is available centred on a wide range of frequencies from 30MHz to 180MHz. Non standard units £14.75+£1.84 - 3 weeks. 8319 4 stage varicap tunerhead from Larsholt using MOSFET RF and mixer stages. New temperature compensated oscillator for wide ranges of ambient temperature £13.45+£1.68vat
7252 Complete Larsholt FM tuner less stereo decoder. £26.50+£3.31vat
7253 Stereo FM tuner from Larsholt with FET head. (as 7252)
944378 Hyperfi stereo decoder. The very best. £19.95+£2.19vat
911223 Pilot cancel stereo decoder, priced to make the MC1310 as obsolete as it now deserves to be. £12.50+£1.56vat
Inotec 1-A fully DC tuned and switched LW/MW/FM stereo tuner to interface with synthesiser control etc. A first! Details OA.

COMPONENTS for Radio and Audio ICs, HMOS etc.

The list is too long to attempt here, but AMBIT specializes in all types of semiconductor for radio reception, including devices operating from DC to 5GHz. New low cost SBL1 diode ring mixers (equiv case MD108 etc) - first with HMOS fets, now with a PCB for DC amplifier, and offset sense and protection relay for speakers. See catalogue and updates for most info, please send an SAE for information on anything you cannot find in catalogues.

Radio ICs	cost +vat	Stereo ICs	cost +vat	AF power ICs	cost +vat
CA3089E	1.94 24	MC1310P	1.50 19	LM380N	1.00 12
CA3187E	2.45 30	CA758	2.20 27	TBA810AS	1.09 14
HA1137W	2.20 27	CA390A	2.75 34	TDA2002	1.95 24
SN76660	0.75 9	HA1196	3.95 49	TBA820M	0.75 9
TDA1090	3.35 42	HA11223	4.35 54		
TDA1083	1.95 24	KB4437	4.25 54		
TDA1220	1.40 17	KB2224	2.75 34		
SL6640	2.75 34				
MC3357	3.12 39	Preamp ICs/switches			
HA1197W	1.40 17	TDA1028	3.50 44		
MC1496	1.25 16	TDA1029	3.50 44		
LM373/4	3.75 49	TDA1074	4.14 52		
		KB4438	2.22 28		

from the general list:
LEDs: all colours and low prices
25J48/25K134 HMOS
9.90 + £0.80 vat(Pair)
Signal fets/transistors and TOKO COILS & FILTERS!

OSTS: Remember all OSTs stocks are obtained from BS9000 approved sources - your assurance that all devices are very best first quality commercial types. Some LPSN TTL is presently in great demand, so please check by phone before ordering.

TTL Standard AND LP Schottky

N°	LSN	N°	LSN	N°	LSN	N°	LSN
7400	13	20	7455	35	24	74126	57
7401	13	20	7460	17		74128	74
7402	14	20	7463		124	74132	73
7403	14	20	7470	28		74133	
7404	14	24	7472	28		74135	65
7405	18	26	7473	32	38	74138	
7406	38		7474	27	38	74139	
7407	38		7475	38	40	74141	56
7408	17	24	7476	37	38	74142	265
7409	17	24	7478		38	74143	312
7410	15	24	7480	48		74144	312
7411	20	24	7481	86		74145	65
7412	17		7482	69		74147	175
7413	30		7483A		110	74148	109
7414	51		7484	97		74150	99
7415		24	7485	104	99	74151	64
7416	30		7486		99	74153	64
7417	30		7489	205		74154	84
7420	16	24	7490	33	90	74155	96
7421	29	24	7491	76	110	74156	80
7422	24	24	7492	38	78	74157	67
7423	27		7493	32	99	74158	60
7425	27		7494	78		74159	210
7426	36	27	7495A	65	99	74160	82
7427	27	29	7496	58	120	74161	92
7428	35	32	7497	185		74162	92
7430	17	24	74100	119		74163	92
7432	25	24	74104	63		74164	104
7433	40	32	74105	62		74165	105
7437	40	24	74107	32	38	74166	
7438	33	24	74108	63	38	74167	20
7440	17	24	74110	58	54	74168	
7441	14	24	74111	68		74169	
7442	70	99	74112	38		74170	230
7443	115		74113		38	74172	625
7444	112		74114		38	74173	10
7445	94		74116	198		74174	87
7446	94		74118	83		74175	87
7447	82	89	74119	113		74176	75
7448	56	99	74120	115		74177	78
7449		99	74121	25		74180	85
7450	17		74122	46	57	74181	165
7451	17	24	74123	48	73	74182	160
7453	17		74124		137	74183	
7454	17	21	74125	38	44	74184	210

All prices listed in pence *

CD 4000 CMOS

4000	17p	4059	563p	4522	149p
4001	17p	4060	115p	4523	152p
4002	17p	4063	109p	4528	102p
4006	109p	4066	56p	529	141p
4007	18p	4067	400p	4530	90p
4008	80p	4068	25p	4531	141p
4009	58p	4069	20p	4532	125p
4010	58p	4070	20p	4534	614p
4011	17p	4071	20p	4554	380p
4012	17p	4072	20p	4538	150p
4013	55p	4073	20p	4539	110p
4014	95p	4074	20p	4541	141p
4016	52p	4075	20p	4543	174p
4017	80p	4076	90p	4549	399p
4018	80p	4077	20p	4553	440p
4019	60p	4078	20p	4554	440p
4020	33p	4081	190p	4555	150p
4021	82p	4082	20p	4556	177p
4022	90p	4085	82p	4557	386p
4023	17p	4086	82p	4558	117p
4024	76p	4088	82p	4559	388p
4025	17p	4093	50p	4560	218p
4026	180p	4094	190p	4561	55p
4027	55p	4096	105p	4562	530p
4028	72p	4097	372p	4566	159p
4029	100p	4098	110p	4568	281p
4030	58p	4099	122p	4569	303p
4031	250p	4100	90p	4572	25p
4032	100p	4101	90p	4580	600p
4033	145p	4102	90p	4581	319p
4034	200p	4103	90p	4582	164p
4035	102p	4104	104p	4583	84p
4036	250p	4175	95p	4584	63p
4037	100p	4194	95p	4585	100p
4038	105p	4501	23p		
4039	83p	4502	91p		
4040	90p	4503	69p		
4041	90p	4506	51p		
4042	85p	4507	55p		
4043	85p	4508	248p		
4044	80p	4510	99p		
4045	150p	4511	149p		
4046	130p	4512	98p		
4047	85p	4513	206p		
4048	60p	4514	260p		
4049	65p	4515	300p		
4050	55p	4516	125p		
4051	65p	4517	382p		
4052	65p	4518	103p		
4053	65p	4519	57p		
4054	120p	4520	109p		
4055	135p	4521	236p		

Micromarket

6800 series	8216	1.95	
6800P	6.50	2/08	
6801P	16	2/08	
6805P	2.75	MEMORIES	
6810P	£4		
6852	3.65		
8080 series	2102	£1.70	
8080	6.30	2112	£3.40
8212	2.30	2513	£7.54
		4027	£5.78

MISC. LSI/Scalars/DVMs

NE555	30p	NE556	78p	NE558	180p	
LM3909	72p	95H90UC	£200MHz	£14.95		
IC17208	7 decade	10MHz	DFM/timer	with direct LED drive and all counter features	£19.82	
ICM7217A1B1	4 decade	programmable	cnt	£9.50		
ICM7207	clock	output	IC	£4.95		
ICM7208	7 decade	counter	display	drive	£14.95	
ICM7106CP	LCD	DVM	IC (2 1/2 digit)	£3.55		
ICM7106CP	LCD	DVM	KIT	£24.80		
ICM7107CP	LCD	DVM	IC	£9.55		
ICM7107CP	LCD	DVM	KIT	£20.65		
MSL829	divide	by 100	200MHz	scalar	£4.20	
MSL2318	divide	by 10	to 175MHz	min		
		divide	by 10	to 45MHz	min	£4.70

PLEASE REMEMBER TO ADD 8% VAT TO ITEMS LISTED UNDER OSTs

LINEARS

BIMOS	LM324N	71p
	LM339N	66p
	CA3130T	90p
	LM348N	186p
	LM3900N	60p
	CA3140E	72p
	709HC	1.05
	CA3160E	90p
	CA3160T	99p
	OP amp	
	LM301AH	67p
	LM301AN	30p
	LM308H	121p
	LM308N	97p
	LM318H	279p
	LM318N	224p

OPTO

0.43" High Efficiency HP:	
5082	7650 red CC
5082	7653 red CC
5082	7658 yellow CA
5082	7663 yellow CA
5082	7670 green CA
5082	7673 green CC
0.3" Standard HP	
5082	7740 red CA
5082	7740 red CC
0.5" Fairchild	
FN5050	red CA
FN5057	red CA

Current news: Work continues apace on our HMOS PA kit, and by the time this is published we expect to be about to launch the product in a style that matches the Mark III system. The unit uses separate transformers and power supplies, and includes a DC offset sensing circuit combined with slow switch-on using a relay. We introduce the HyperFi FM IF with this advert and a separate leaflet is available on request with an SAE. All new price lists are also available with an SAE. The Mullard DC controlled tone/volume and switch ICs with a more than HiFi specification are in stock at last - together with reams of data (over 50 pages now). Also, RC enthusiasts will be interested to learn that we are supplying parts for various kits now.

Terms: CWO please. Account facilities for commercial customers OA. Postage 25p per order. Minimum credit invoice for account customers £10.00. Please follow instructions on VAT, which is usually shown as a separate amount. Overseas customers welcome - please allow for postage etc according to desired shipping method. Access facilities for credit purchases. Catalogues: Ambit Part 1 45p, Part 2 50p 90p pair, TOKO Euro shortform 20p, Micrometals toroid cores 40p. All inc PP etc. Full data service described in price list supplements. Hours/phone: We are open from 9am - 7pm for phone calls. Callers from 10am to 7pm. Administrative enquiries 9am to 4.30pm please (not Saturdays). Saturday service 10am to 6pm.

ambit international **2 Gresham Road, Brentwood, Essex.**

AMBIT catalogues are guaranteed to contain the most up-to-date and best informed comment on modern developments and advances in the field of radio and audio. There is no competitive publication that even approaches the broad range of parts/information on modern techniques.

Electronics Constructors — Our component packs save you money!

FREE: with the first order opened this month, worth £15 — A Rockwell Calculator, value £10.95

PACK X101:— Contains 35 mixed capacitors — all good usable values, i.e. 1,500pf/0.01uf/.01uf/.015uf etc. One pack for 45p or two packs for only 82p.

PACK X102:— Contains 50 Germanium Diodes — S1m to OA91 40p per pack or 2 packs for only 77p

PACK X103:— Contains 30 mixed transistors — some new and branded — NPN & PNP silicon and Germanium (most usable) great value at 60p per pack or 2 packs for £1

PACK X104:— Contains 50 silicon diodes, S1m to 1N4148, a real bargain at 46p per pack or 2 packs for 80p

PACK X105:— Contains 50 mixed Wattage resistors. Super value at 40p per pack or 2 packs for only 75p. You can't lose on this pack.

PACK X106:— Contains 20 electrolytic capacitors — ideal for transistor circuits. Values like 10mfd, 50mfd, 220mfd and 100mfd at £1 per pack or 2 packs for £1.75

PACK X107:— Contains 20 ceramic caps — ideal for transistor AF/RF circuits. Values like 150pf/270pf/330pf/22pf/39pf etc. Only 45p per pack or 2 packs for only 80p

PACK X108:— Contains 10 BC107, BC108, BC109 (NPN) transistors all full spec-devices at 95p per pack

SIGTRONIC

* ELECTRONICS *

27 Malvern Street, Stapenhill, Burton-on-Trent, Staffs. DE15 9DY. Tel: (0283) 46868 after 6 pm. Special orders and quotations. All prices include VAT. Add 40p to order for p & p. Cheques/PO's accepted.



Wilmslow Audio

THE firm for speakers!

SEND 15p FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST

AUDAX • AUDIOMASTER • BAKER • BOWERS & WILKINS • CASTLE • CELESTION • CHARTWELL • COLES • DALESFORD • DECCA • EMI • EAGLE • ELAC • FANE • GAUSS • GOODMAN'S • I.M.F. • ISOPON • JR • JORDAN WATTS • KEF • LEAK • LOWTHER • MCKENZIE • MONITOR AUDIO • PEERLESS • RADFORD • RAM • RICHARD ALLAN • SEAS • STAG • TANNOY • VIDEOTONE • WARFEDEALE • YAMAHA • SHACKMAN • TANGENT

WILMSLOW AUDIO DEPT REC

SWAN WORKS, BANK SQUARE, WILMSLOW CHESHIRE SK9 1HF

Discount HiFi Etc. at 5 Swan Street and 10 Swan Street
Tel: 0625-529599 for Speakers, 0625-526213 for HiFi



THIS is the Catalogue you need to solve your component buying problems!



- About 2,500 items clearly listed and indexed
- Profusely illustrated
- 128 A-4 size pages, bound in full-colour cover

- Bargain List of unrepeatabe offers included free
- Catalogue contains details of simple Credit Scheme
- Price includes packing and postage

Send the coupon today with cheque or P.O. for £1.25

Please write your Name and Address in block capitals

NAME _____

ADDRESS _____

HOME RADIO (Components) LTD., Dept. RC
234-240 London Road, Mitcham, Surrey CR4 3HD
Regd. No. 912966, London



HOME RADIO (Components) LTD. Dept. RC, 234-240 London Road, Mitcham, CR4 3HD. Phone: 01-648 8422

STEVENSON

Electronic Components

REGULATORS

78L05 30p	7805 60p	79L05 70p	7912 80p
78L12 30p	7812 60p	79L12 70p	7915 80p
78L15 30p	7815 60p	7905 80p	LM723 35p

HARDWARE


MINIATURE TRANSFORMERS

240 Volt Primary

Secondary rated at 100mA.

Available with secondaries of:

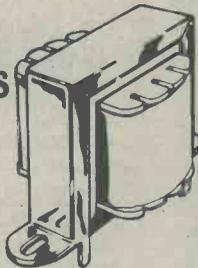- 6 - 0 - 6, 9 - 0 - 9 and
- 12 - 0 - 12. 92p. each.



LOUDSPEAKERS

56mm dia. 8 ohms	70p
64mm dia. 8 ohms	75p
64mm dia. 64 ohms	75p
70mm dia. 8 ohms	100p
70mm dia. 80 ohms	110p



TERMINALS

Rated at 10A. Accepts 4mm plug, black, blue, green, brown and red . . . 22p

SWITCHES

Subminiature toggle. Rated at 3A 250V.

SPDT 70p	SPDT centre off 75p
DPDT 80p	DPDT centre off 95p

Standard toggle

SPST 34p	DPDT 48p
----------	----------

Wavechange switches.

1P12W, 2P6W, 3P4W or 4P3W all 43p ea.

Miniature switches (non-locking)

Push to make 15p Push to break 20p

Slide switches (DPDT)

Miniature 14p	Standard 15p
---------------	--------------

CONTROL KNOBS

Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow and black. 14p



TRANSISTORS

AC127 17p	BCY71 14p	ZTX109 14p
AC128 16p	BCY72 14p	ZTX300 16p
AC176 18p	BD131 35p	2N697 12p
AD161 38p	BD132 35p	3N1302 38p
AD162 38p	BD135 38p	2N2905 22p
BC107 8p	BD139 35p	2N2907 22p
BC108 8p	BD140 35p	2N3053 18p
BC109 8p	BF2448 36p	2N3055 50p
BC147 7p	BFY50 15p	2N3442 135p
BC148 7p	BFY51 15p	2N3702 8p
BC149 8p	BFY52 15p	2N3704 8p
BC148 9p	MJ2955 98p	2N3705 9p
BC177 14p	MPSA06 20p	2N3706 9p
BC178 14p	MPSA56 20p	2N3707 9p
BC179 14p	TIP29C 60p	2N3708 8p
BC182 10p	TIP30C 70p	2N3819 22p
BC182L 10p	TIP31C 65p	2N3904 8p
BC184 10p	TIP32C 80p	2N3905 8p
8C184L 10p	ZTX107 14p	2N3906 8p
BC212 10p	ZTX108 14p	2N4058 12p
BC212L 10p		2N5457 32p
BC214 10p		2N5458 30p
BC214L 10p		2N5459 32p
BC477 19p		2N5777 50p
BC478 19p		
BC479 19p		
BC548 10p		
BCY70 14p		

DIODES

1N914 3p	1N5401 13p
1N4001 4p	BZY88ser. 8p

Full spec. product.
1N4148 £1.40/100. £11/1000

LINEAR

THIS IS ONLY A SELECTION!

CA3140 38p	NE555 21p
LM301AN 26p	NE556 50p
LM318N 85p	NE565 85p
LM324 45p	NE567 170p
LM339 45p	SN76003 200p
LM380 75p	SN76013 140p
LM382 120p	SN76023 140p
LM1830 150p	SN76033 200p
LM3900 50p	SN76477 220p
LM3909 65p	T8A800 70p
MC1496 60p	TDA1022 650p
MC1458 32p	ZN414 75p

CAPACITORS

TANTALUM BEAD each

0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V 8p
4.7, 6.8, 10uF @ 25V 13p
22 @ 16V, 47 @ 6V, 100 @ 3V 16p

MYLAR FILM

0.001, 0.01, 0.022, 0.033, 0.047 3p
0.068, 0.1 4p

POLYESTER

Mullard C280 series

0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1 5p
0.15, 0.22 7p
0.33, 0.47 10p
0.68 14p
1.0uF 17p

CERAMIC

Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF 2p

RADIAL LEAD ELECTROLYTIC

63V 0.47 1.0 2.2 4.7 10 5p
22 33 47 7p
100 13p
220 20p
25V 10 22 33 47 5p
100 8p
220 10p
470 15p
1000 23p

CONNECTORS

JACK PLUGS AND SOCKETS

	screened	unscreened	socket
2.5mm	9p	13p	7p
3.5mm	9p	14p	8p
Standard	16p	30p	15p
Stereo	23p	36p	18p

DIN PLUGS AND SOCKETS

	plug	chassis socket	line socket
2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p

1mm PLUGS AND SOCKETS

Suitable for low voltage circuits, Red & black. Plugs: 6p each Sockets: 7p each.

4mm PLUGS AND SOCKETS

Available in blue, black, green, brown, red, white and yellow. Plugs: 11p each Sockets: 12p each

PHONO PLUGS AND SOCKETS

Insulated plug in red or black	9p
Screened plug	13p
Single socket	7p
Double socket	10p

VERO

Size in.	0.1in.	0.15in.	Veropins—
2.5 x 1	14p	13p	single sided
2.5 x 3.75	42p	40p	per 100
2.5 x 5	52p	50p	0.1in 35p
3.75 x 5	60p	60p	0.15in 40p
3.75 x 17	195p	180p	

BOXES



Aluminum boxes with lid and screws

	Length	width	height	
AL1	3	2	1	48p
AL2	4	3	1 1/2	58p
AL3	4	3	2	65p
AL4	6	4	2	70p
AL5	6	4	3	85p
AL6	8	6	2	116p

THYRISTORS

Plastic cased Thyristors: Texas

	4A	8A	12A
100V	36p	45p	62p
200V	42p	53p	68p
400V	51p	66p	86p

TRIACS

Plastic cased Triacs. Texas. All rated at 400V.

4A 70p	42A 90p	20A 185p
8A 80p	16A 95p	25A 215p


CMOS

4018 55p	4050 25p
4023 12p	4066 35p
4024 40p	4068 18p
4001 12p	4026 90p
4002 12p	4027 30p
4007 12p	4028 48p
4011 12p	4029 50p
4013 28p	4040 60p
4015 50p	4042 50p
4016 30p	4046 90p
4017 48p	4049 25p

FULL DETAILS IN CATALOGUE!

SKTS

Low profile by Texas

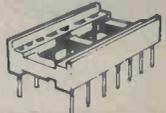

8 pin	9p	16 pin	11p	28 pin	22p
14 pin	10p	24 pin	18p	40 pin	32p

Soldercon pins: 100:50P. 1000:370p

OPTO

LED's	0.125in.	0.2in.	each	100+
Red	TIL209	TIL220	9p	8p
Green	TIL211	TIL221	13p	12p
Yellow	TIL213	TIL223	13p	12p
Clips	3p	3p		

DISPLAYS

DL704	0.3 in CC	130p	120p
DL707	0.3 in CA	130p	120p
FND500	0.5 in CC	100p	80p

RESISTORS

Carbon film resistors. High stability, low noise 5%.

E12 series. 4.7 ohms to 10M. Any mix: each 100+ 1000+

0.25W	1p	0.9p	0.8p
0.5W	1.5p	1.2p	1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £7.50. 0.25W £5.70.

METAL FILM RESISTORS

Very high stability, low noise rated at 1/2W 1%. Available from 51ohms to 330k in E24 series. Any mix: each 100+ 1000+

0.25W	4p	3.5p	3.2p
-------	----	------	------

PLEASE WRITE FOR YOUR FREE COPY OF OUR NEW 80 PAGE CATALOGUE OF COMPONENTS.

CONTAINS OVER 2500 STOCK ITEMS.



WHY NOT VISIT OUR NEW SHOP

We welcome callers at our new premises at the address below (5 mins. from High St.) We are open Mon - Sat, 9am - 6pm. Special offers available.

Express telephone order service. Orders received before 5pm. are shipped first class on that day. Contact our Sales Office now! Tel: 01-464 2951/5770.

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.

BARCLAYCARD & ACCESS WELCOME.

Mail orders to: STEVENSON (Dept RE)

76 College Road, Bromley, Kent, England

TRADE COMPONENTS

PAY A VISIT — THOUSANDS MORE ITEMS BELOW WHOLESALE PRICE. CALLERS PAY LESS ON MANY ITEMS AS PRICES INCLUDE POSTAGE. PRICES INCLUDE VAT AND ADDITIONAL DISCOUNT IN LIEU OF GUARANTEE. GOODS SENT AT CUSTOMERS RISKS UNLESS SUFFICIENT ADDED FOR REGISTRATION OR COMPENSATION FEE POST.

OFFERS CORRECT AT 25/6/79 APPLICABLE TO ORDERS RECEIVED DURING JULY.

VALVE BASES

Printed circuit B/G	7p
Chassis B7-B7G	11p
Shrouded Chassis B7G-B8A	13p
B12A tube. Chassis B9A	13p
Speaker 6" x 4" 5 ohm ideal for car radio	£1.55
4 3/4" diam. 30 Ω	£1.75
2 1/2" diam. 32 or 8 Ω	£1.07

Car type panel lock and key 65p

Transformer 9V 4A £3.78

Aluminium Knobs
for 1/4" shaft. Approx. 3/8" x 7/8" with indicator
Pack of 5 95p

TAG STRIP—6 way 5p 5 x 50pF or 1000 +
8 way 10p Single 2p 300pF trimmers 35p

BOXES — Grey polystyrene 61 x 112 x 31mm, top secured by 4 self tapping screws 57p clear perspex sliding lid, 46 x 39 x 24 mm 15p.

ABS, ribbed inside 5mm centres for P.C.B., brass corner inserts, screw down lid, 50 x 100 x 25mm orange 65p; 80 x 150 x 50mm black 97p; 109 x 185 x 60mm black £1.52.

DIECAST ALI superior heavy gauge with sealing gasket, approx 6 1/2" x 2 3/8" x 1 1/8" £1.50; 3 3/8" x 2 3/8" x 1 1/8" £1.25.

VARIABLE CAMM PROGRAMMER 10, 12 or 15 pole 2 way, 50VAC motor — series with 1mfd, or 3k 10W or 15W pygmy bulb for mains operation. Ex equipment £4.32

SWITCHES

Pole	Way	Type	Price
1	2	Slide	15p
6	2	Slide	24p
2	1	Rotary Mains	28p
2	2	Alternating Micro with roller	30p
2	3	Miniature Slide	20p
2	1	Toggle	42p
1	2	Sub-Min Toggle	75p
2	2	Alternating 2A Mains Push (3/8" hole)	43p
2	2	Alternating Slide	15p

S.P.S.T. 10 amp 240v. white rocker switch with neon. 1" square flush panel fitting 60p; 1 pole 2 way 10 amp oblong clip in mains rocker appliance switch 38p

Standard thumb-wheel switch 0-9 in 1248N or B.C.D., or Comp. 1242 also 2p co. £1.20
Standard Lever Key Switch D.P.D.T. locking plus D.P.D.T. and S.P.S.T. Heavy Duty non latching 82p

AUDIO LEADS

3 pin din to open end, 1 1/2yd, twin screened 45p
5 pin din 180° to 2-phonos 70p
3 pole jack plug to tag ends, 4ft 45p

COMPUTER & AUDIO BOARDS/ASSEMBLIES
VARYING CONTENTS INCLUDE ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKES, INTEGRATED CIRCUITS, ETC.

3lb for £2 7lb for £3.70

1k horizontal preset with knob 10 for 40p	3" Tape Spools 5p
	1" Terry Clips 5p
	12 Volt Solenoid 40p

ENM Ltd. cased 7-digit counter 2 1/4 x 1 1/2 x 1 1/2" approx. 12V d.c. (48 a.c.) or mains £1.10

Auto charger for 12v Nicads, ex-new equipment £5.19

Miniature 0 to 5mA d.c. meter approx 1/8" diameter £1.25
RS Yellow Wander Plug Box of 12 40p
18 SWG multicore solder 3 1/2p foot
SAPPHIRE STYLII. 15 different; dual and single point, current and hard to get types. My mix £2.

BRIAN J. REED

161 ST. JOHNS HILL, BATTERSEA, LONDON SW11 1TQ

Open 10 a.m. till 7 p.m. Tuesday to Saturday, VAT receipts on request.

Terms: Payment with order Telephone: 01-223 5016

JAP 4 gang min. sealed tuning condensers 40p

ELECTROLYTICS Many others in stock

Up to	10V	25V	50V	75V	100V	250V	350V	500V
MFD	6p	7p	7p	10p	13p	15p	26p	32p
10	6p	7p	7p	10p	13p	18p	32p	37p
25	6p	7p	7p	12p	16p	23p	32p	37p
50	6p	7p	7p	12p	16p	23p	32p	37p
100	7p	8p	13p	15p	24p	26p	—	—
250	12p	13p	15p	22p	36p	—	£1.10	£1.30
500	13p	15p	22p	30p	55p	—	£1.48	£1.60
1000	16p	27p	50p	60p	—	£1.05	—	—
2000	28p	47p	55p	93p	£1.20	—	—	—

As total values are too numerous to list, use this price guide to work out your actual requirements
8/20, 10/20, 12/20, 22/50, 47/25. Tub. Tant 24p each 16-32/275V, 100/150V, 100-100/275V
40p 50-50/385V, 2+2/200V non polar, 32-32-50/300V, 20-20-20/350V 0.1+0.1/500V AC 80p
200V, 100-200-60/300V £1.30 100-300-100-16/300V £1.85

RS 100-0-100 micro amp null indicator
Approx. 2" x 1 1/2" x 1 1/2" £1.85

INDICATORS

Bulgin D676 red, takes M.E.S. bulb 38p
12 volt, or Mains neon, red pushfit 23p
R.S. Scale Print, pressure transfer sheet 12p

CAPACITOR GUIDE — maximum 500V

Up to .01 ceramic 4 1/2p. Up to .01 poly 6p
.013 up to .1 poly etc. 7p. .12 up to .68 poly etc. 8p. Silver mica up to 360pF 10p, then to 2,200pF 13p; then to .01 mfd 21p.
1/750 13p. .01/1000, 8/20, 1/900, 22/900, 4/16, 25/250 AC (600v/DC), 3/600 15p.
5/150, 10/150, 40/150 50p.
Many others and high voltage in stock.

SONNENSCHHEIN/POWERSONIC DRI-FIT RECHARGEABLE SEALED GEL (Lead Antimony) BATTERY, 6V 1 amp.hr. (3 3/8" x 2" x 1 1/8") £3.70.
6 amp. hr. (4 1/2" x 2" x 3") £7.60
Ex-equipment, little used.

CONNECTOR STRIP

Belling Lee L1469, 4 way polythene. 9p each

1 1/2 glass fuses 250 m/a or 3 amp (box of 12) 20p
Bulgin 5mm Jack plug and switched socket (pair) 40p

Reed Switch 28mm, body length 11p

Aluminium circuit tape, 1/8 x 36 yards—self adhesive. For window alarms, circuits, etc. 95p

TV MAINS DROPPERS

5 assorted multiple units for 75p

100pF air-spaced tuning capacitor £1.30
5 1/2" x 2 1/2" Speaker, ex-equipment 3 ohm 65p
2 Amp Suppression Choke 10p
3 x 2 1/2 x 1 1/8" } PAXOLINE 5 for 35p
4 1/2 x 1 1/2 x 1 1/8" } 10 for 15p
PVC or metal clip on MES bulb Holder 5 for 30p
VALVE RETAINER CLIP, adjustable 5 for 15p

Sub-miniature Transistor Transformer 35p
Valve type output transformer 90p

POT CORES with adjuster LA2508-LA2519 43p per pair

16 Watt Power Amp. Module 35v 1A power required, giving 16 watt RMS into 8 Ω £3.45

REGULATED TAPE MOTOR Grundig 6V approx., 3" x 1 1/2", inc. shock absorbing carrier, or Jap 9V, 1 1/2" diam. £1.05

3.5mm metal stereo plug 30p
Fane 8 ohm 3" sq. heavy duty communications speaker £1.60

RS neg. volt regulator 103, 306-099 (equiv. MPC900) 10A, 100 watt 4-30 volt. Adjustable short circuit protection. Normally £12.50+ £6.65

Digital count unit. Counts in steps of 1, 2, 5 or 10 with total limit switch (2 x D.I.L. BCD), reed relay remote output. Mains power supply, relay and delay unit. UNUSED. £5.40
Displays on 2 Minitron. 7 segments sold separately.

ACOS DUST JOCKEY Automatic record cleaner £1.30

Mail Order Over £50 deduct 10% Over £100 deduct 20%

RELAY 6 amp changeover. Mains coil 200µA F.S.D. level Meter 1 1/2" x 1 1/2" £1.10 £3.25

McMurdo 4 or 8 way plug and socket ex-equipment 50p

RELAY 6V Capacity 6V 450K. at 10 hour rate. Ex-new equipment £4.11

"Makswitch" 1p 10-way wafer 15p Wood cased 8-12V buzzer £2.50

2.5A r.f. thermo-couple and meter 2 1/4" square £3.80

Crouzet 30-minute timer-programmer, multi-variable contacts £7.50

100 Electrolytics £3.00
 100 Resistors 1W £2.00
 100 Wirewound Resistors £4.50
 Well mixed values and voltages

100 Capacitors £2.50
 100 Resistors up to 1W £1.00
 100 Resistors 2-5W £3.00
 100 1% & 2% Resistors £3.50

Mullard + 12-0-12V 1A, 4A stabilized, regulated, power supply. £12.00
 27V 5A Double section bobbin transformer £4.32

C90 Cassette Tape 62p
 50 ohm BNC through connector or round or flanged chassis socket. TNC plug or N plug or through connector 65p each
 250 Ω, 50 watt + Resistor 40p

SEMICONDUCTORS Full spec. by Mullard etc. Many others in stock

AC126/128/176	20p	BCY70/1/2	14p	BFX12/29/30	23p
ACY20	30p	BCZ11	32p	BFX84/88.89	20p
ACY29	22p	BD113	57p	BFY51	16p
AD161/2 match pr.	85p	BD115	35p	BFY90	57p
ADZ12	£4.00p	BD116(BRC116T)	£1.15	BR101	34p
AF124/6/7	28p	BD130Y	£1.50	BRY39/56	29p
AF139	23p	BD131/2/3	40p	BSV64	36p
AF178/80/81	35p	BD135/6/7/8/9	35p	BSV79/80 F.E.T.s	90p
AF239	35p	BD140/142	35p	BSV81 Mosfet	£1.00
AS27/73	35p	BD201/2/3/4	92p	BSX20/21/78	16p
AU110/113	£2.50	BD232/3/4/5/8	65p	BSY40	30p
BC107/8/9 + A/B/C	8p	BDX77	£1.15	BSY95A	14p
BC147/8/9 + A/B/C	8p	BD437	58p	BU204 + Mount Kit	£1.85
BC157/8/9 + A/B/C	8p	BF115/167/173	18p	BZ208	£2.28
BC178A/B 1798	14p	BF178/9	23p	CV7042 (OC41/44	
HC182/184C/LC	11p	BF180/1/2/3/4/5	18p	ASY63)	12p:
BC186/7	23p	BF194A, 195C	8p	GET111/E112	45p
BC204	12p	BF200 258 324	23p	OC45(ME2)	13p
BC212	13p	BF262/3	35p	ON222	23p
BC213L/214B/238	13p	BF336/274	31p	R2008B/2010B	£2.30
BC327/8 337/8	10p	BFS28 Dual Mosfet	£1.15	TIP30	50p
BC547/8 + A/B/C	13p	BFT61	40p	TIS43 (2N2646)	9p
BC556/7/8/9	11p	BFW10/11 F.E.T.	48p	uA7805	£1.85
BCX32/36	16p	BFW30	£1.15	ZT1486	£1.15
BCY31	90p			ZTX300/341	9p
BCY40	55p			2N393 (MA393)	35p

BRIDGE RECTIFIERS

Amp	Volt		
1	1600	BYX10	34p
1	140	OSH01-200	30p
5	100	Ex Equip	73p
0.6	110	EC433	20p
5	400	Texas	£1.10
2 1/2	100	I.R.	48p
3 1/2	100	B40C 3200	58p

RECTIFIERS

Amp	Volt		
M1	1	68	5p
1N4005/6	1	6/800	8p
1N4007/BYX94	1	1250	8p
BY103	1.5	1500	21p
SR100	1.5	100	9p
SR400	1.5	400	10p
RECS53A	1.5	1,250	16p
LT102	2	30	15p
BYX22-200	1 1/2	300	25p
BYX38-300R	2.5	300	48p
BYX38-600	2.5	600	52p
BYX38-900	2.5	900	60p
BYX38-1200	2.5	1,200	65p
BYX49-300R	3	300	35p
BYX49-600	3	600	42p
BYX49-900	3	900	47p
BYX49-1200	3	1,200	60p
BYX48-300R	6	300	47p
BYX48-600	6	600	60p
BYX48-900	6	900	70p
BYX48-1200R	6	1,200	92p
BYX72-150R	10	150	42p
BYX72-300R	10	300	52p
BYX72-500R	10	500	65p
BYX42-300	10	300	36p
1N5401	3	100	18p
1N5402	3	200	18p
MR856	3	600	24p
BYX42-900	10	900	92p
BYX42-1200	10	1,200	£1.07
BYX46-300R*	15	300	£1.19
BYX46-400R*	15	400	£1.76
BYX46-500R*	15	500	£2.00
BYX46-800*	15	600	£2.30
BYX20-200	25	200	72p
BYX52-300	40	300	£2.06
BYX52-1200	40	1,200	£2.90
RAS310AF*	1.25	1,250	48p

***Avalanche type**

Amp	Volt	TRIACS	
25	900	BTX94-900	£4.50
25	1200	BTX49-1200	£6.75

Diode Characteristic, Equip., and Substitution Book 82p

Transistor equivalents and substitution Book 1 38p Book 2 82p

Chrome Car Radio fascia 28p

Rubber Car Radio gasket 10p

DLI Pal Delayline 90p

Relay Socket miniature 2PCO 20p

28 pin d.i.t. socket low profile 38p

Colour EHT Tray 3000/3500 £5.50

Nylon self-locking, 3 1/2" tie clips 1.5, 10, 22 or 750 μh choke 12p

0-30, or 0-15, black pvc, 360° dial, silver digits, self adhesive 4 1/2" dia. 13p

Mullard Semiconductor, Valve & Component Data Book 1976-78 50p

OPTO ELECTRONICS

Diodes	Photo transistor
BPX40 57p	BPX29 92p
BPX42 92p	OC71 75p
BPY10 92p	

(VOLIAC)

BPY68	92p
BPY69	92p
BPY77	92p

Wire end neons 9p

PHOTO SILICON CONTROLLED SWITCH
 BPX66 PNP 10 amp £1.15

3" red 7 segment L.E.D. 14
 D.I.L. 0-9 + D.P. display 1.9v
 19m/a segment, common
 anode 95p
 RS 0.6in. green £2.25
 Minitoron 0.3in 3015F
 filament £1.25

CQY118 L.E.D.
 Infra red transmitter £1.15
 One fifth of trade

R.S. Battery Holder for
 4 x HP/SP 11 30p

McMurdo PP108 8 way edge plug 12p
 Multicore Solder 1/2kg. 16 or 18 or 20
 s.w.g. 60/40 £5.00
 3 inch 8 Ω speaker £1.15

New unmarked, or marked
 ample lead ex new equipment

ACY17-20	10p	TIC44	28p
AS220	10p	2G240	£1.17
AS221	35p	2G302	6p
BC186	13p	2G401	6p
BCY30-34	24p	2N711	28p
BCY70/1/2	10p	2N2926	6p
BY126/7	5p	2N598/9	8p
HG1005	12p	2N1091	10p
HG5009	4p	2N1302	10p
HG5079	4p	1N1907	£1.17
L78/9	4p	Germ. diode	2p
M3	12p	2N3055	5p
OA81	4p	Motorola	36p
OA47	4p	GET120 (AC128	
OA200-2	4p	in 1" sq. heat	
OC23	27p	sink	22p
OC200-5	24p	GET872	15p
C106 THY	38p	2S3230	34p
		TIS43	25p

MINIATURE EDGE METERS
 100Ω/A f.s.d., scaled 0.5, 12V illuminated
 blue perspex front, 35mm x 14mm £3.45
 200Ω/A level meter, clear front.
 10 x 18mm £1.20

2N1613	24p
2N2401	35p
2N21412	80p
2N2483	28p
2N2904/5/6/7/7A	18p
2N3053	16p
2N3055 R.C.A.	60p
2N3133/4062	24p
2N3553	66p
2N4037	35p
2N5484 FET	39p
2N5956	87p
2SA141/2/360	36p
2SB135/6/457	24p
40250 (2N3054)	35p

CATALOGUE
 38, 11 x 8 Ins illustrated
 sheets, listing approx.
 5,250 items, photo
 printed on day requested,
 from constantly updated
 masters, to ensure latest
 stock position, 75p (re-
 fundable with orders) plus
 24p s.a.e. or label.

TRANSFORMERS
 Ferromag C core. Screens 95-
 105-115-125-200-220-240v
 input output 17v 1/2A, x,
 2 + 24-0-24v 1.04A-20v
 1mA. These current ratings
 can be safely exceeded by
 50%. £4.90
 Cassette Dynamic Micro-
 phone with switch and twin
 plug £1.80
 Telephone Pickup, sucker
 with lead and 3.5 plug.70p

THYRISTORS

Amp	Volt		
	.40	BTX18-200	35p
	400	BTX18-300	41p
	240	BTX30-200	35p
4	500	40506	80p
15	500	BT107	£1.14
6.5	500	BT109-500R/SCR957/BRC4444	£1.14
20	600	BTW92-600RM	£3.40
15	800	BTX95-800R Pulse Modulated	£8.76

PAPER BLOCK CONDENSER
 0.25MFD 800 volt 87p
 1MFD 250 volt 54p
 1MFD 400 volt 85p

TV KNOB
 Dark grey plastic for recessed shaft
 (quarter inch) with free shaft extension
 8p

CHASSIS SOCKETS
 Car Aerial 11p, Coax 8p, 5 pin 180°
 11p, 5 or 6 pin 240° din 8p, speaker
 din switched 13p, 3.5 mm switched
 7p, stereo 1/2" jack enclosed 20p.

SPECIAL OFFERS

2500 mfd. 40v 56p
 0.1 mfd. 350/500v 10 for 50p
 10000 mfd. 15v 3 for £1.16
 6800 mfd. 10v 3 for 90p
 32+32/275v 3 for 90p
 16 + 32/275v 3 for 80p
 8+8 mfd. 375v4 for 90p
 1 mfd. non-polar 350v 10 for £1.19
 25000 mfd. 25v 65p
 12000/12v 3 for £1.16
 G.E.C. 5% Hi-stab
 capacitors 0.13, 0.61, 0.66, 0.69, 0.75, 0.8
 10 for 65p
 AY5 8300 10 for £6
 BC548B 500 for £28.50
 BC556 500 for £28.50
 BCY71 500 for £43.50
 BD437 50 for £13.75
 2N2906500 for £43.50
 TBA920 10 for £11.50
 Ver card handle 10 for 65p
 62 Ω 1/2W Resistor 2,000 for £6.75
 ON222 (superior matched
 BF181) 10 for £1.20
 68 Volt 10 Watt Zener
 Diodes 5 for £2.50

OTHER DIODES

1N916	8p
1N4009	9p
1N4148	4p
BA145	17p
Cartercel	29p
BZY61/BA148/OA81	12p
BB103/110 Varicap	24p
BB113 Triple Varicap	43p
BA182	15p
OA5/7/10	17p
BZY88 up to 43 volt	10p
BZX61 11 volt	17p
AA133	10p
BZY96C 10V	34p
BZY95C 33V or 15V	34p

PVC QUALITY TAPE
 Lasso 10m x 15mm grey
 38p
 33m x 33mm green
 £1.13p
 Trimmer: Post stamp
 type 3-30pF 16p
 10-80pF 19p
 30-140pF 23p

GARRARD
 GCS23T Crystal Stereo
 Cartridge £1.20
 Mono (Stereo compatible)
 Ceramic or crystal £1

INTEGRATED CIRCUITS

TBA920 TCA270	£2.20
TAA700	£2.40
TBA900	£1.24
741/7490/7473	28p
uA702/LM3900	53p
709	40p
74107/74122	38p
SN76228N	£2.03
SN76131/75110	£1.55
SN76013M/ND	£1.40
TAD100 AMRF	£1.22
CA3001 R.F. Amp	£1.58
CA3132	£2.22
74151	45p
CD4069	24p
TAA300 1 wt Amp	£1.15
TAA550 Y or G	26p
TAA263/74LS192	70p
TAA320	£1.15
7400/7401	18p
7402/4/10/20/30	16p
7414/74132N	64p
7438/7474/7432	27p
AY5 8300	£1.00
7483/74S20	79p
7493/CD4013	41p
LM300 2/20V reg	£1.10
LM1303N	£1.15
74154/TBA810	£1.02
TBA5500/74S112	£1.80
2N414	£1

HANDLES

Rigid light blue nylon 6 1/2"
 with secret fitting screws 11p

Belling Lee white plastic
 surface coax outlet box 40p

Miniature Axial Lead Ferrite
 Choke formers 5 for 13p

RS 10 Turn pot 1% 250
 500 Ω 1K. £1.70

Copper coated board
 18" x 2 1/2" 40p

Gearred Knob 8-1 ratio,
 1 1/2" diam., black 93p

KLIPPON 25A 440v
 TERMINAL BLOCKS
 Professional leaf spring
 clamp, twin with clip-over
 cover 11p

Strip of 4, 40A 440V 16p

VAT & POST PAID

MINIMUM ORDER £3 OTHERWISE ADD 50%
 FOR SMALL ORDER HANDLING COSTS (UNDER
 £1.00 TOTAL ALSO INCLUDE 9p S.A.E.)

**NO MORE TO ADD — Prices INCLUDE
 UK VAT and Post/Packing**
**ALL ENQUIRIES, ETC., MUST BE ACCOMPANIED
 BY A STAMPED ADDRESSED ENVELOPE**

THE MODERN BOOK CO

WORLD RADIO TV HANDBOOK 1979 £9.15

THE RADIO AMATEUR HANDBOOK 1979 by ARRL	Price £7.86	UNDERSTANDING DIGITAL ELECTRONICS by Texas Instruments	Price £3.90	ABC'S OF ELECTRONICS by F. J. Waters	Price £4.15
UNDERSTANDING AMATEUR RADIO by J. Rusgrove	Price £4.25	NEWNES RADIO & ELECTRONICS ENGINEER'S POCKET BOOK by Newnes	Price £2.80	BEGINNER'S GUIDE TO HOME COMPUTERS by M. Grosswirth	Price £3.20
SOLID STATE DESIGN FOR THE RADIO AMATEUR by ARRL	Price £6.00	BEGINNER'S GUIDE TO TAPE RECORDING by I. R. Sinclair	Price £3.20	ADVENTURES WITH ELECTRONICS by T. Duncan	Price £2.85
THE A.R.R.L. ANTENNA BOOK by ARRL	Price £4.25	BEGINNER'S GUIDE TO AUDIO by I. R. Sinclair	Price £3.00	PROJECT PLANNING & BUILDING by M. A. Colwell	Price £2.20
FM AND REPEATERS FOR THE RADIO AMATEUR by ARRL	Price £3.50	BEGINNER'S GUIDE TO INTEGRATED CIRCUITS by I. R. Sinclair	Price £3.00	110 COSMOS DIGITAL IC PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston	Price £3.00
REPAIRING POCKET TRANSISTOR RADIOS by I. R. Sinclair	Price £2.50	BEGINNER'S GUIDE TO COLOUR TV by G. J. King	Price £2.50	110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston	Price £2.75
BEGINNER'S GUIDE TO RADIO by G. J. King	Price £3.00	BEGINNER'S GUIDE TO ELECTRIC WIRING by F. Guillou	Price £2.50	TESTING METHODS AND RELIABILITY ELECTRONICS by A. Simpson	Price £4.30
BUILDING & DESIGNING TRANSISTOR RADIOS - A BEGINNER'S GUIDE by R. H. Warring	Price £3.30	THE OSCILLOSCOPE IN USE by I. R. Sinclair	Price £2.75	DIGITAL ELECTRONIC CIRCUITS AND SYSTEMS by N. M. Morris	Price £4.30
OP-AMPS - THEIR PRINCIPLES AND APPLICATIONS by J. B. Dance	Price £2.50	THE CATHODE-RAY OSCILLOSCOPE AND ITS USE by G. N. Patchett	Price £4.00	BEGINNER'S GUIDE TO MICROPROCESSORS by C. M. Gilmore	Price £4.75
ELECTRONICS FAULT DIAGNOSIS by I. R. Sinclair	Price £3.00	INTRODUCING AMATEUR ELECTRONICS by I. R. Sinclair	Price £1.50	GETTING ACQUAINTED WITH MICROCOMPUTERS by L. Frenzel	Price £7.00

* PRICES INCLUDE POSTAGE *

We have the Finest Selection of English and American Radio Books in the Country
19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone: 01-402 9176

BUILD YOUR OWN

40MHz Counter
300MHz Prescaler
Rx Digital Readout



DIGITAL FREQUENCY COUNTER Model RQ-3 and its accessories offer you one of the most versatile combinations available. On its own the RQ-3 incorporates the following features: Mains operation — 40MHz Counting — 8 digit accuracy — 35mV RMS sensitivity — Displays not only FREQUENCY (MHz), but PERIOD (μ s) and WAVELENGTH (Metres) as well
Complete Kit **£44.95 + 15% VAT**

RX DIGITAL READOUT Model RQ-3um. Small additional PCB enables you to modify the RQ-3 Counter to correct for any IF and give you a display of Rx tuning frequency. Makes your inaccurate tuning dial obsolete!
Complete Kit **£9.95 + 15% VAT**

VHF PRESCALER Model RQ-10 Self-contained in its own case with its own power supply. Extends the range of any Frequency Counter to beyond 300MHz.
Complete Kit **£18.95 + 15% VAT**

SIGNAL CLARIFIER Model RQ-9. Truly remarkable multi-function filter and limiter plugs into the output of any receiver and fantastically improves signal readability by suppressing all types of interference. Contains HP, LP, BP and Notch filters in various combinations.
Remarkable value at only **£22.50 + 15% VAT**


CRYSTAL CALIBRATOR Model RQ-1. Outputs on 1MHz, 100kHz and 10kHz either CW or internally modulated with audible tone. Gives harmonics well into VHF.
Complete Kit only **£12.72 + 15% VAT**

BEGINNERS SHORT WAVE RADIO Model RQ-5. Sensitive little radio. Ideal for the budding Dx-er of any age. Reception from all over the world guaranteed. Kit includes a helpful guide to Dx-ing.
Complete Kit **£10.50 + 15% VAT**

MORSE PRACTICE KIT Model RQ-7. Includes key and all necessary components including case and PCB. Ideal beginner's kit.
Complete Kit **£9.50 + 15% VAT**

Send for details — postage appreciated, 9p stamp

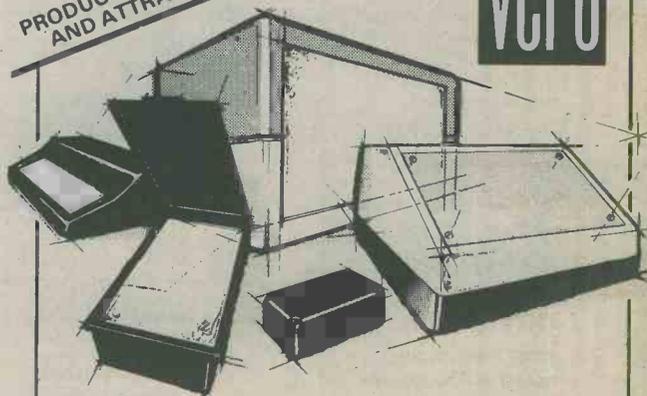OUR RANGE OF
PRODUCTS ARE NOW INDIVIDUALLY
AND ATTRACTIVELY PACKAGED



vero

Our new catalogue lists a whole range of plastic boxes to house all your projects. And we've got circuit boards, accessories, module systems, and metal cases — everything you need to give your equipment the quality you demand. Send 25p to cover post and packing and the catalogue's yours.

VERO ELECTRONICS LTD. RETAIL DEPT.
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR
Telephone Chandlers Ford (04215) 2956

Rocquaine
electronics

Aldebaran, Le Coudre
Rocquaine
GUERNSEY C.I.

PICK-A-PAK

BD187 Full spec. devices new and coded PAK of 4 — 98p	ASSTD. RESISTORS Pak of modern $\frac{1}{8}$ W and $\frac{1}{4}$ W types, brand new PAK of 100 — 65p	NPN/PNP Plastic transistors like BC147/148/149/157/ 158/159. Uncoded, untested 80% good PAK of 50 — 90p	CERAMIC CAPACITORS Asstd. pak, all new and coded types PAK of 40 — 70p
TIP33 Full spec. devices new and coded PAK of 3 — 90p	ZENER DIODES 2 watt metal types Asstd., untested but 80% good PAK of 50 — 85p	C280 CAPACITORS Asstd. Pak new and coded types PAK of 40 — 70p	ASSTD. TRANSISTORS All new and most coded approx 90% good PAK of 50 — 95p
MP8112 Full spec. devices new and coded PAK of 4 — 98p	MP8512 Full spec. devices. New and coded PAK of 4 — 98p	WIREWOUND RESISTORS 2W, 5W, 10 watt types. All new and coded. Modern types PAK of 50 for 95p	PUSH BUTTON SWITCH BANKS All brand new types. Singles, doubles, trebles, etc. PAK OF 5 asstd. banks — 90p
SILICON DIODES Mostly glass types signal, power, etc. Untested, 80% good PAK of 100 — 70p	2N3054 Full spec. devices. New and coded PAK of 3 — 98p	ELECTROLYTIC CAPACITORS All new, modern, coded transistor types PAK of 40 — 85p	BC107/8/9's Transistors, metal cased. Untested, uncoded 80% good PAK of 40 — 75p
E111 N-channel FET's New full spec. Similar to 2N3819 PAK of 4 — 60p	TRIMMERS All new, various types, compression, piston, air etc. PAK of 6 — 85p	I.C. SOCKETS All new low profile d.i.l. types, assortment of 8 pin, 14 pin and 16 pin types PAK of 6 — 80p	THYRISTORS Asstd. types, some coded, all new, untested 80% good PAK of 25 — 70p
PHOTO TRANSISTORS New, some coded, untested 80% good PAK of 5 — 75p	TBA120S I.C.'s F.M. types, new, untested with data PAK of 4 — 70p	POLYSTYRENE CAPACITORS All new, asstd., coded PAK of 50 — 70p	AC128 TRANSISTORS Brand new, coded. Untested 80% good PAK of 40 — 75p
FET's P-channel uncoded but tested O.K. PAK of 4 — 70p	WIDEBAND I.C.'s Untested but new with data PAK of 4 — 70p	HIGH SPEED DIODES BAW62 full spec. types PAK of 12 — 55p	$\frac{3}{16}$ " COIL FORMERS New, with cores PAK of 6 — 50p
FERRITE BEADS New FX1115 types PAK of 12 — 40p	VARI-CAP DIODES New, uncoded, about 500pF, 80% good PAK of 40 — 75p	10K LIN ROTARY POTS New, coded plastic shaft PAK of 6 — 90p	PLASTIC BC107/8/9's Asstd., new, untested 80% good PAK of 40 — 70p
THYRISTORS 1 amp new types, untested 80% good PAK of 30 — 60p	OC71 TRANSISTORS New, marked. Untested 80% good PAK of 40 — 85p	PNP — TRANSISTORS Like AC128, new, untested 80% good PAK of 50 — 65p	S.C.R.'s 5 amp stud mounting, new, untested 80% good PAK of 20 — 80p

Please add 20p extra for post/packing U.K. only, overseas at cost.
 Minimum order value £1.00. Cheques need 8 days to clear.

MAIL ORDER ONLY

We do not have any retail facilities

M. CUTLER

125 HAZLEBURY ROAD, LONDON SW6 2LX



UNDERSTAND DATA PROCESSING

NEW FOURTH EDITION

DATA PROCESSING, by Oliver & Chapman, is now in its Third Edition — first published 1972.

200 pages 9 $\frac{3}{4}$ " x 6 $\frac{3}{4}$ " **PRICE £2.75**

P.&P. 35p

PUBLISHED BY D. P. PUBLICATIONS

The primary aim of this outstanding manual is to provide a simplified approach to the understanding of data processing — (previous knowledge of the subject is not necessary).


The 40 chapters and appendices cover the following topics: Introduction to Data Processing; Organisation and Methods; Conventional Methods; Introduction to EDP and Computers; Hardware; Computer Files; Data Collection and Control; Programming and Software; Flowcharts and Decision Tables; Systems Analysis; Applications; Management of EDP, etc.

A must for Business and Accountancy Students

Available from: **DATA PUBLICATIONS LTD.,**
57 MAIDA VALE, LONDON W9 1SN.

Electronics. Make a job of it....

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

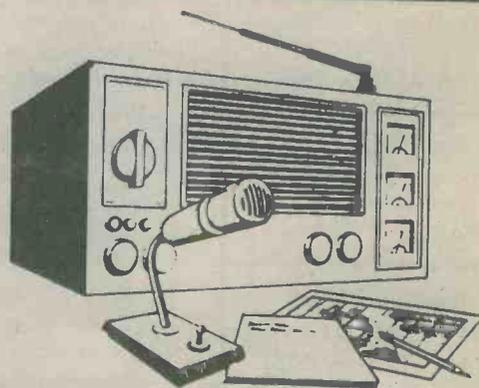

Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Brochure without obligation to:

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

REL 8/79


Block caps please

Free!

APEL POWER SUPPLIES

STABILIZED POWER SUPPLIES WITH ELECTRONIC SHORT CIRCUIT PROTECTION

AL.212 P

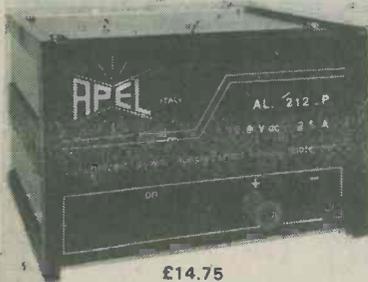

£14.75

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	12.6 V dc
OUTPUT CURRENT MAX	2.5 Amp
LOAD REGULATION	<0.3% 0-2.2 Amp
RIPPLE	<5mV 2.2 Amp
DIMENSIONS (mm)	W140 x H90 x D140
WEIGHT	1,490 Kg.

AL.315 P



£29.50

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	1.7-15 V. dc
LOAD REGULATION	<0.2% 0-2.8 Amp
DIMENSIONS (mm)	W140 x H90 x D155
RIPPLE	3mV 2.8 Amp
WEIGHT	2,330 Kg.

AL.330 P



£46.50

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	3.4-30 V. dc
OUTPUT CURRENT RANGE MAX	3 Amp
LOAD REGULATION	< 5% 0-2.8 Amp
RIPPLE	10mV 2.8 Amp
DIMENSIONS (mm)	W270 x H90 x D155
WEIGHT	4,250 Kg.

STOCKISTS

Alpha Sound Service,
50 Stuart Road, Waterloo, Liverpool L22 4QT.
England.

Anson Electronics,
1133 Hessele High Road, Hull, England.

Amateur Radio Shop,
13 Chapel Hill, Huddersfield, HD1 3ED.
England.

Brent Electronics,
Seaview Street, Cleethorpes,
Lincolnshire, England.

J. Birkett,
26 The Strait, Lincoln, England.

Bradford Consultants Limited,
25 Regent Parade, Harrogate,
Yorkshire, England.

F. Brown & Co. Ltd.,
44/46 George IV Bridge Street,
Edinburgh, Scotland.

N. R. Bardwell Limited,
Sellers Street, Sheffield, England.

Casey Brothers,
235 Boundary Road,
"Saint Helens,"
Lancashire, England.

Electronic Services Limited,
33 City Arcade, Coventry CU11 HX, England.

A. Fanthorpe Limited,
6 Hepworth Arcade, Silver Street,
Hull, England.

G. W. M. Radio,
Portland Road, Worthing, Sussex.

Leeds Amateur Radio,
27 Cookridge Street,
Leeds LS2 3AG, England.

Target Electric Limited
16 Cherry Lane, Bristol, England.

New Cross Radio,
6 Oldham Road, Manchester,
England.

Progressive Radio,
93 Dale Street, Liverpool L2 2JD.
England.

R. E. Pitt Electrical Services Limited,
60/64 Bath Buildings, Mont Pelier,
Bristol, England.

Peats Electronics,
Parnell Street, Dublin.

R. F. Potts,
68 Bobbington Lane, Derby, England.

Brian A. Pearson Limited,
66 Moncur Street, Glasgow, Scotland.

R M E Supplies Limited,
143 Stockwell Street, Glasgow, Scotland.

Stephan James Limited,
Warrington Road, Leigh, Lancashire.

Stewarts Radio,
4 Chance Street, Blackpool, England.

The Radio Shop,
16 Cherry Lane, Bristol BS 3NG,
England.

Q. C. Trading,
1 St. Michaels Terrace, Woodgreen M22 4FT.
England.

AL.1 P5



£78.00

INPUT VOLTAGE	220 \pm 10% 50 Hz
OUTPUT VOLTAGE RANGE	1 \pm 15 V. dc
OUTPUT CURRENT MAX	5 Amp
LOAD REGULATION	< 0.1% 0-4.6 Amp
RIPPLE	< 2mV 4.6 Amp
DIMENSIONS (mm)	W210 x H155 x D250
WEIGHT	5,100 Kg.

AL.212 PS



£18.00

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	12.6 V dc
OUTPUT CURRENT MAX	2.5 Amp
LOAD REGULATION	<0.3% 0-2.2 Amp
RIPPLE	<5mV 2.2 Amp
DIMENSIONS (mm)	W140 x H90 x D140
WEIGHT	1,490 Kg.
AMPEROMETER	

AL.315 P2



£54.00

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	\pm 1.7 \pm 15 V. dc
OUTPUT CURRENT RANGE MAX	3 Amp
LOAD REGULATION	< 0.2% 0-2.8 Amp
RIPPLE	< 3mV 2.8 Amp
DIMENSIONS (mm)	W270 x H90 x D155
WEIGHT	4,140 Kg.

Stan Willets Limited,
37 High Street, West Bromwich.


M/S Waltons,
55a Worcester Street,
Wolverhampton WV2 4LL, England.

Distributed in the UK
and Ireland by:

PEAT'S WHOLESALE LTD.

Chapel Lane, Parnell St., Dublin 1, Ireland.

PHONE 741746-740678-722845. TELEX 31787.

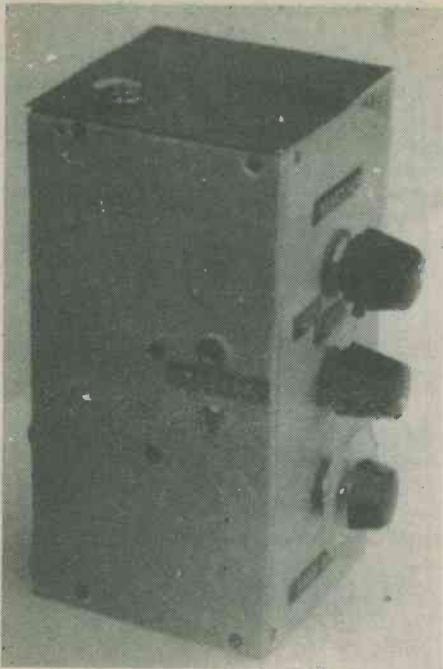

THE "DORIC" 9 WAVEBAND PORTABLE

Part 1

By Sir Douglas Hall, Bt., K.C.M.G.

This opening article describes a complete 6-waveband short wave receiver, to which can be added an amplifier and a tuner covering v.h.f., medium and long waves.

This 4 part series describes a multi-band portable receiver which offers six bandspread short wave ranges covering 13.5 to 52 metres, medium waves, long waves and v.h.f. on Band II. The design can be built in stages, each stage resulting in a complete receiver or amplifier in its own right. The first part of the series commences by dealing with the short wave section which, when assembled, consists of a receiver suitable for use on its own with headphones. The following parts of the series will describe the addition of an amplifier and speaker to this short wave receiver, and further steps which provide for the reception of medium wave, long wave and v.h.f. signals.

SHORT WAVE CIRCUIT

The circuit of the short wave headphone receiver appears in Fig.1. The aerial signal is applied via C1 and VR1 to the emitter of TR1. VR1 is a selectivity control, and can also be used as a vernier reaction control. TR1 amplifies as a common base device, the signal at its collector being passed via C3 to the base of TR2 which, at r.f., is a common collector amplifier. Detection takes place at D1, and the consequent audio signal then passes through TR2 again, working now as a common base amplifier, followed by TR1 as a common emitter amplifier with some negative feedback due to the presence of VR1.

Variable inductance tuning is used, band setting being arranged by having a ferrite rod move into coil L2, the rod movement being controlled by the six positions of rotary switch S1. This has a tuning drive drum fitted to its spindle, and a nylon cord on the drum controls the amount of insertion into the coil of the ferrite rod. At the same time, one set of the switch contacts varies the parallel capacitance across the diode, to give optimum results for each position of the ferrite rod. The associated capacitors, C5 to C8, allow reaction in the Colpitts mode to be obtained. Reaction control is given by varying the impedance of the diode, and hence the damping on the tuned circuit, by altering the direct current which passes through the diode. Panel control VR2 varies this current (which is additional to that passing through TR2) and thereby controls reaction. VR3 is adjusted to compensate for different gain levels in the transistor used in the TR2 position, and D2 and D3 provide voltage stabilization as battery voltage falls with age.

The a.f. output is built up across the large winding of the interstage transformer T1, and high resistance phones (4,000 Ω magnetic or crystal) may be plugged into the lower jack socket. The upper socket is unused with the receiver in its present state of construction, and will be employed when the amplifier to be described next month is added.

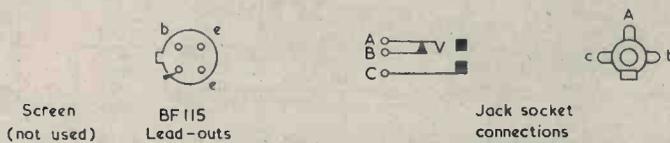
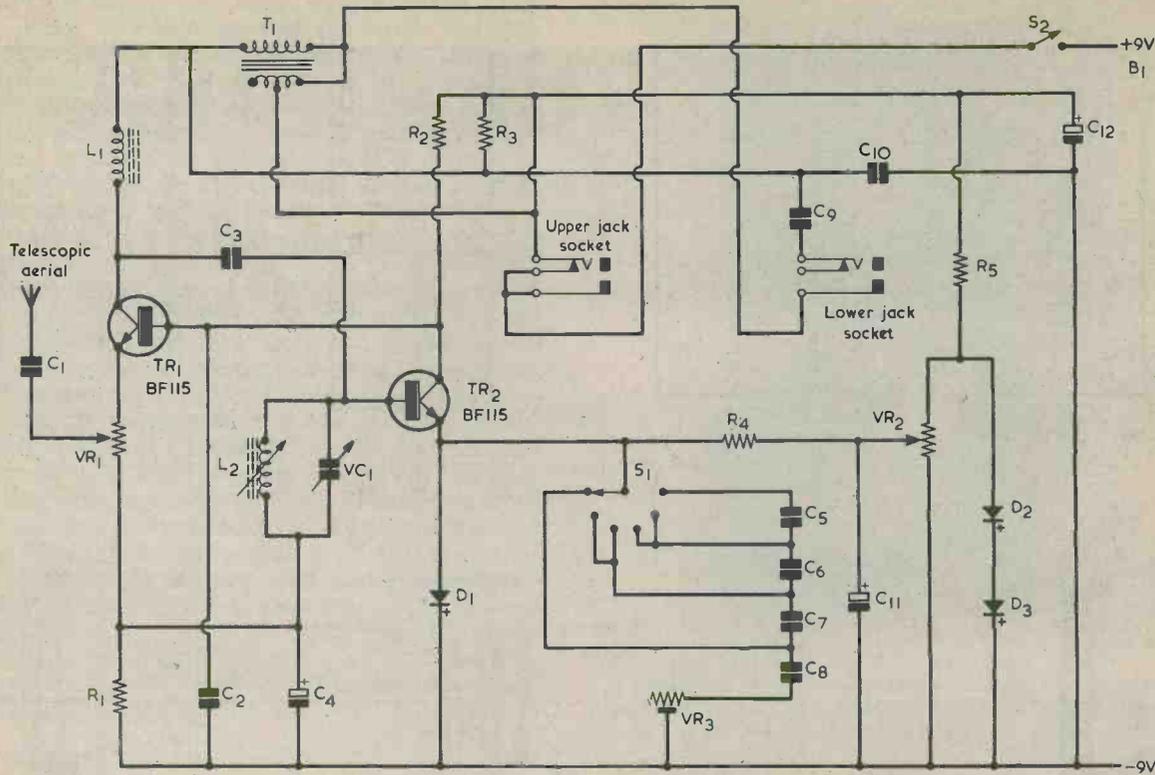


Fig. 1. The circuit of the multi-band short wave receiver. High impedance headphones are plugged into the lower jack socket, whilst the upper jack socket allows interconnection to the amplifier unit which will be described next month. L2 is permeability tuned by a ferrite rod moving to six positions inside the coll, these positions being mechanically controlled by switch S1

Resistors

(All fixed values 1/4 watt 10%)

- R1 1k Ω
- R2 33k Ω
- R3 12k Ω
- R4 1.2k Ω
- R5 8.2k Ω
- VR1 470 Ω potentiometer, linear, type P20 (Electrovalue)
- VR2 4.7k Ω potentiometer, linear, with switch S2, type P20 (Electrovalue)
- VR3 470 Ω pre-set potentiometer, 0.25 or 0.3 watt, horizontal

Capacitors

- C1 100pF silvered mica or ceramic
- C2 1,000pF silvered mica or ceramic
- C3 5.6pF silvered mica or ceramic
- C4 47 μ F electrolytic, 3V. Wkg.
- C5 220pF silvered mica or ceramic
- C6 220pF silvered mica or ceramic
- C7 330pF silvered mica or ceramic
- C8 100pF silvered mica or ceramic
- C9 0.47 μ F polyester
- C10 2,200pF silvered mica or ceramic
- C11 47 μ F electrolytic, 3V Wkg.
- C12 1,000 μ F electrolytic, 10V. Wkg.
- VC1 15pF variable, type C804 (Jackson)

Inductors

- L1 2.5mH r.f. choke (Repanco)
- L2 see text
- T1 transformer type LT44 (Eagle)

Semiconductors

- TR1 BF115
- TR2 BF115
- D1 OA90 or OA91
- D2 1S44
- D3 1S44

Switches

- S1 2-pole 6-way rotary, miniature
- S2 s.p.s.t. toggle, part of VR2

Sockets

- 2-off 3.5mm. jack sockets

Aerial

- Telescopic aerial type TA10 (Eagle-Electrovalue)

Miscellaneous

- 10-way tagstrip (see text)
- 4 control knobs
- Ferrite rod, 4 or 4 1/2 in. by 3/8 in. dia (see text)
- 1 1/2" drive drum (Home Radio)
- 9-volt battery type PP3
- Battery connector
- Nylon cord
- Materials for case and "chassis" assembly


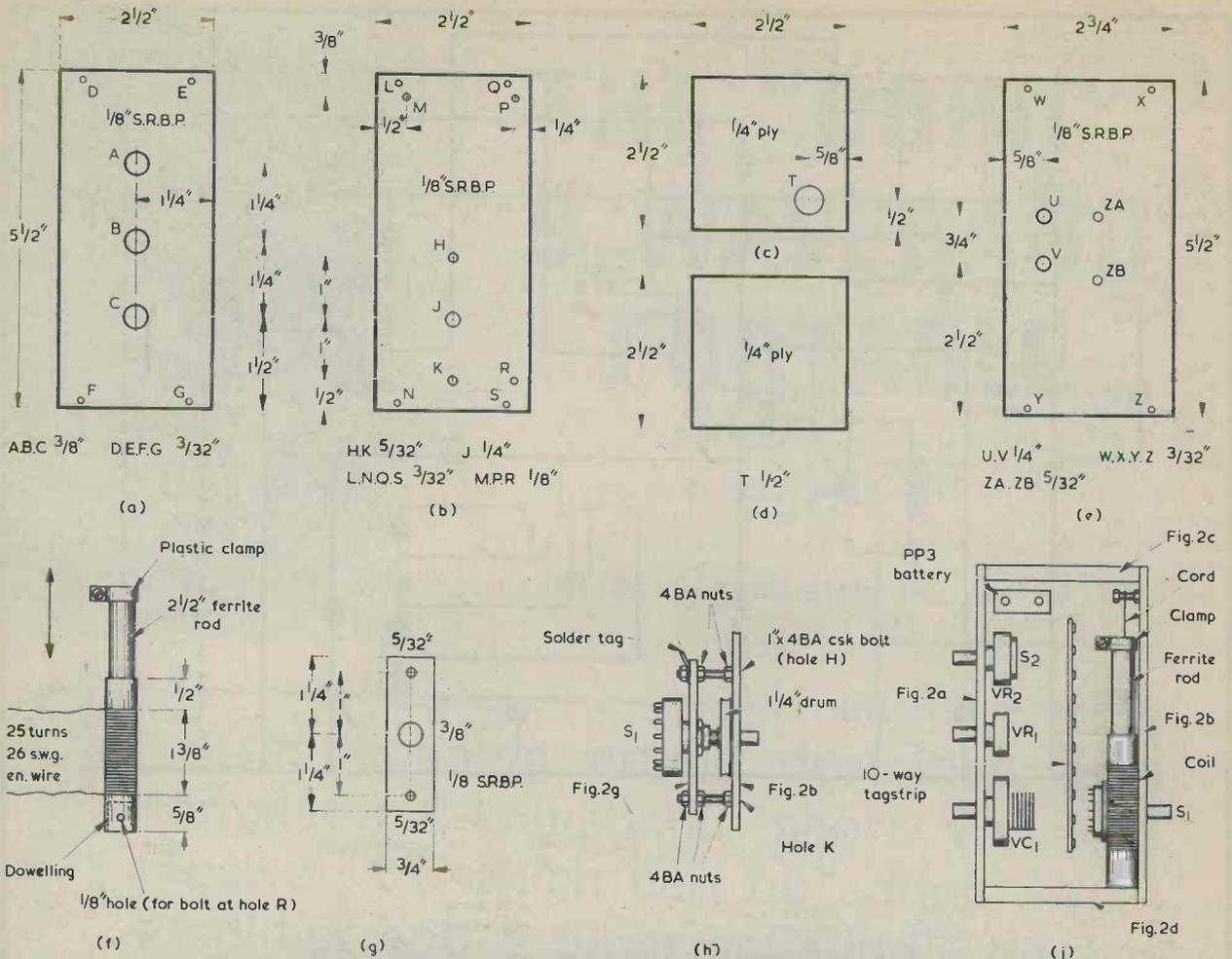


Fig. 2(a) (b) (c) (d) (e). Section of the receiver "chassis" and case (f) Details of the coil, in which the ferrite rod slides to give selection of the six waveranges (g) S.R.B.P. item onto which switch S1 is secured (h). The drive drum is fitted over the spindle of the switch, the spindle passing through hole J of Fig. 2(b) (i) Side view showing the internal assembly of the main parts of the receiver

CONSTRUCTION

Construction commences with the cutting out and drilling of the sections shown in Fig. 2(a) (b) (c) (d) and (e). These provide both the "chassis" and five sides of the case. A second piece of s.r.b.p. should be cut out identical to Fig. 2(e) but without holes U, V, ZA and ZB. This can be fitted opposite Fig. 2(e), forming the sixth side of the case, and can be the side which opens to provide access to the inside of the completed receiver. The small holes, D, E, F, G, and the corresponding four holes in Fig. 2(b) and Fig. 2(e) are for woodscrews used to assemble the parts together. Their exact positioning is not important provided that they are $\frac{1}{8}$ in. from the ends. The woodscrews then pass into the $\frac{1}{8}$ in. plywood edges. The sixth opening side could, instead, be fastened by short lengths of 6BA studding cemented into the plywood, 6BA terminals then securing the side in position. Holes W, X, Y and Z in the sixth side will then need to be $\frac{1}{8}$ in. in diameter. Holes ZA and ZB are for mounting the 10-way tagstrip, the latter being used to mark out their positions.

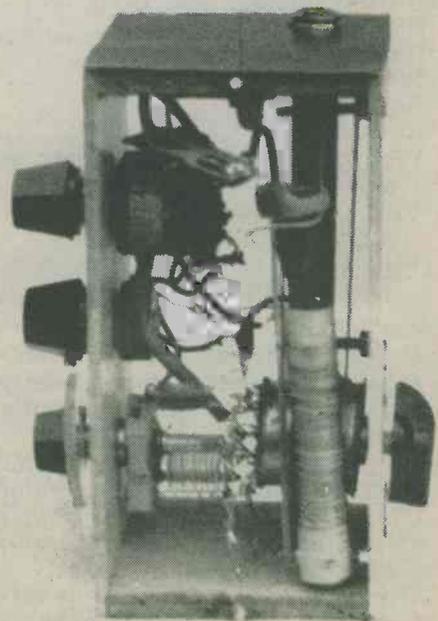The coil is made next. Take a piece of Fablon, or Contact, 4 in. by 2 $\frac{1}{2}$ in., and remove a small strip of




Looking into the receiver with coil L2 nearer the camera

the backing paper, $\frac{1}{4}$ in. wide, at one of the $2\frac{1}{2}$ in. edges. Wrap the Fablon around the ferrite rod with the exposed strip last, so that it secures the tube thus formed. The rod should be able to move in the tube easily but without wobble. Cut a piece of $\frac{3}{8}$ in. wood dowelling $\frac{1}{2}$ in. long, wrap a turn or two of Sellotape around it to ensure that it is a tight fit and insert it at one end of the tube. Drill a $\frac{1}{4}$ in hole through the tube and the middle of the dowelling as shown in Fig. 2(f). Insert the rod into the tube to strengthen it and, starting $\frac{1}{4}$ in. from the end remote from the dowelling, wind onto the tube 25 turns of 26 s.w.g. enamelled wire, spacing out the turns so that the winding ends $\frac{5}{8}$ in. from the dowelling end of the tube. Use Sellotape to secure the winding ends, but not along the coil.

The ferrite rod is orange grade and can be obtained in a 4 or $4\frac{1}{2}$ in. length from Amatronic, 396 Selsdon Road, South Croydon, Surrey CR2 0DE. A $2\frac{1}{2}$ in. length is required, and this is obtained from the longer length supplied by filing round it at the appropriate point and snapping off the excess. If other grades of ferrite are used, some experimenting may be necessary to see whether the number of turns in the coil need to be altered to obtain the required wavelength range.

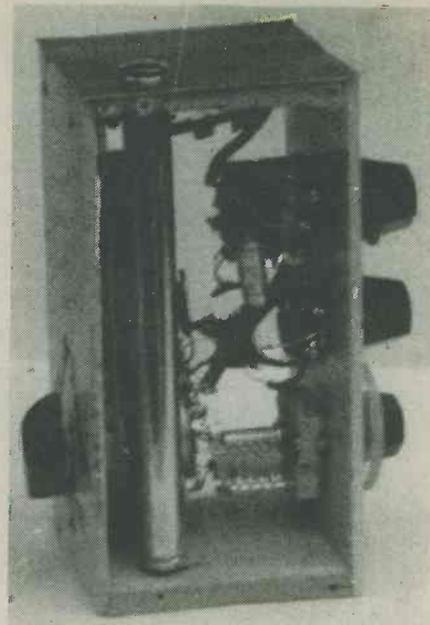Mount VC1, VR1 and VR2/S2 to the item of Fig. 2(a) as shown in Fig. 2(i) and Fig. 3 A piece of



A view from the other side of the receiver. The telescopic aerial is secured to the bottom panel and passes through a hole in the top panel


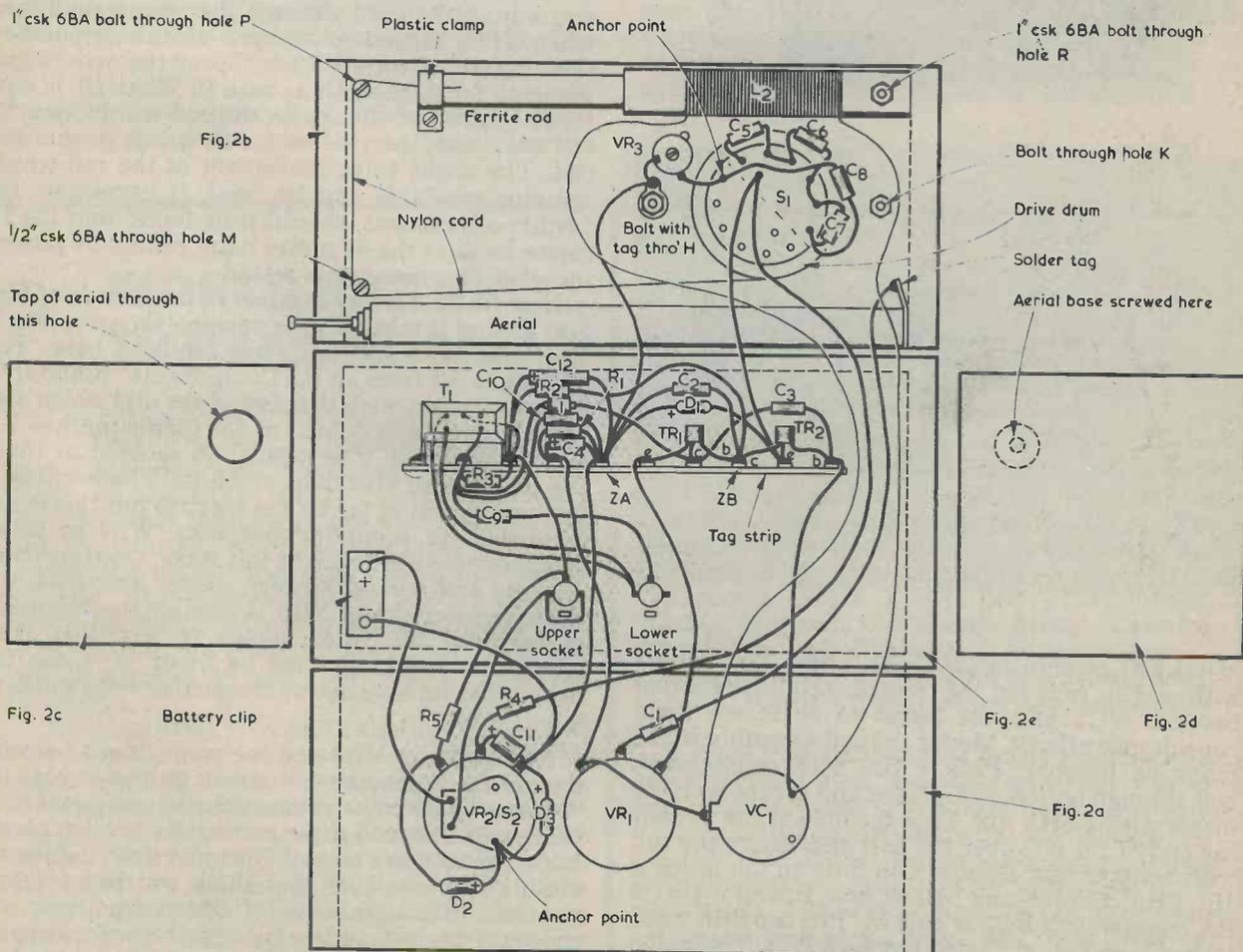
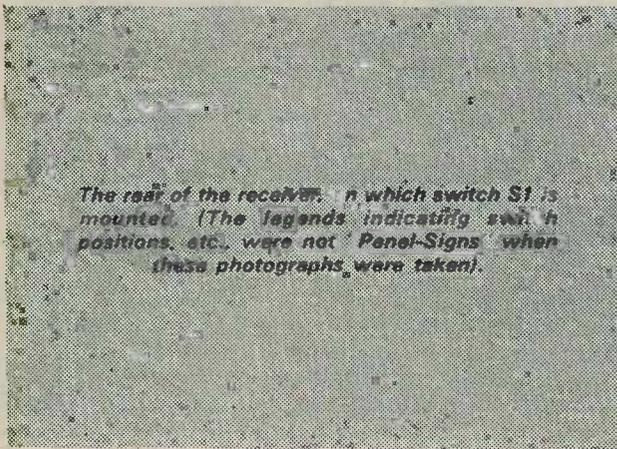


Fig. 3. Assembly and wiring of the components. The item of Fig. 2 (g) is omitted for clarity. Note how each setting of S1 allows the ferrite rod to move to a different position inside the coil. Before wiring to S1 confirm with a continuity tester the six outer tags corresponding to the inner switch arm tag. Similarly check the appropriate tags of S2 before wiring to it.

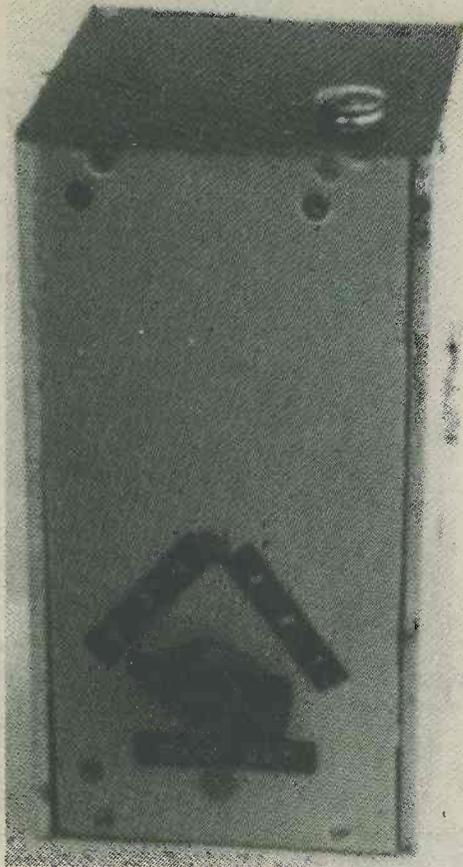

The rear of the receiver in which switch S1 is mounted. (The legends indicating switch positions, etc., were not Panel-Signs when these photographs were taken).

metal foil or thin metal sheet, about 2in. square with a $\frac{3}{8}$ in. hole at the centre, should be fitted between VC1 and the panel to overcome hand capacitance effects. Mount the coil assembly in the following manner. Pass a 1in. 6BA countersunk bolt through hole R of Fig. 2(b) and secure it on the inside with a 6BA nut. Pass the hole at the dowelling end of the coil over the bolt and secure the coil with another nut. Secure with nuts on the inside a 1in. 6BA countersunk bolt at hole P, and a $\frac{1}{2}$ in., 6BA countersunk bolt at hole M. Put two 6BA nuts, locked together, at the end of each bolt. The nylon cord passes over the bolts and the locked nuts prevent it slipping over the bolt ends.

Cut out the item shown in Fig. 2(g) and secure the bush of S1 to this. Fit the $1\frac{1}{2}$ in. drum to S1 spindle with the cord hook away from the switch and

the drum bush well against that of the switch. Make a loop in one end of the nylon cord and pass it through the hole in the side of the drum and over the cord hook. (The cord is fitted to the drum now as it is difficult to reach the hook later). Slip the item of Fig. 2(g) over two 1in. countersunk 4BA bolts passing through holes H and K of Fig. 2(b) and adjust the spacing nuts shown in Fig. 2(h) so that the forward surface of the drum presses lightly against the item of Fig. 2(b). Fit a solder tag over the bolt passing through hole H, then add a third pair of nuts to hold the assembly firm. The pressure on the drum should be just enough to add a little stiffness to the rotation of S1 spindle. The solder tag provides an anchor point, when wiring is carried out, for one of the connections to VR3.

Next required is a plastic clamp to secure the nylon cord to the upper end of the ferrite rod. This is made with a strip of pliant plastic about $\frac{1}{4}$ in. wide and $1\frac{1}{2}$ in. long. This has two holes drilled at the ends such that a 6BA bolt passed through the holes and fastened with a 6BA nut can tighten the clamp so formed on the rod. Take the nylon cord, already fitted to the drum, give it a turn round the drum then lead it over the 6BA bolt in hole M and the 6BA bolt in hole P and then under the ferrite rod plastic clamp. Sufficiently tighten the clamp bolt and nut so that it is just possible to move the cord passing under it. Pass a rubber band over the bolt at hole R and the plastic clamp securing bolt, and adjust the cord through the clamp such that when S1 is turned to its most clockwise position (looking at its spindle) the top of the rod is just about to touch the bolt at hole P. When S1 is now turned fully anti-clockwise the rod will be nearly, but not quite, inserted as far as it can go into the coil. The slight extra movement of the rod which remains available can be used, if necessary, for further adjustment, should it be found that the 13 metre band or the 49 metre band cannot be picked up when the receiver is tested.

Now fit the 10-way tagstrip to the section of Fig. 2(e) so that it takes up the position shown in Fig. 3. Two 4BA nuts and bolts are required here. The tagstrip is cut from an RS Components "Standard" 28-way tagstrip such that two of the tags which also provide mounting appear at the points marked ZA and ZB in Fig. 3. The tagstrip is secured at these two points with 4BA bolts and nuts. There will be a further mounting tag on the tagstrip but this is not employed for mounting purposes. Wire in small components as in Fig. 3, at this stage, omitting components and wiring between panels and, also, the telescopic aerial and VR3. Assemble the "chassis" to take up the form shown in Fig. 2(i). The telescopic aerial can then be fitted. A solder tag held under its base allows connection to be made to it.

Next, wire in VR3 and the connections between the panels. It may be convenient to disassemble the "chassis" and make connections to one panel first, then reassemble and make connections to other panels, but a preliminary assembly as just described is advisable to make sure that there will be no short-circuits. Although some of the components are shown to one side of the tagstrip this is for reasons of clarity only. T1 may, however, be mounted as shown, with its lugs soldered to two of the tags.

When wiring is completed, fit a PP3 battery. A simple home-made clip can be used to hold it in position, though this is not absolutely necessary.

TESTING

Extend the aerial and adjust S1 so that the ferrite rod is fully removed from the coil. Tune with VC1 and check that the 13 metre band is received when the vanes of this capacitor are nearly fully open. Greatest sensitivity is obtained when VR2 is set so that the receiver is just short of the oscillation point. Try all the switch positions and make sure that the 49 metre band is available when S1 is adjusted for the ferrite rod to be fully in the coil. If necessary, adjust the ferrite rod clamp and nylon cord as previously described. Test for overlap between the ranges; this should exist although it will be extremely small. If overlap does not appear at any switch position, this will mean that at that particular setting the turns of the coil are too close, and they should be separated with a small screw-driver. When all is well, put a little clear varnish on the winding.

While testing, use the setting of VR1 which gives the necessary selectivity. Adjustment of VR1 will have some effect on the settings for VC1 and VR2. If it is found that, with certain settings of VC1 and VR1, oscillation cannot be obtained with VR2 at maximum, adjust VR3 to insert less resistance into circuit. Conversely, if oscillation at some settings cannot be controlled, adjust VR3 to insert more resistance. A setting of VR3 to suit all wavebands should be found. So far as is possible, arrange matters so that VR2 never has to be set near its minimum position to prevent oscillation.

Wavebands can be marked, and the control functions indicated, by legends taken from "Panel Signs" Set No. 3 (white) or Set No. 4 (black), available from the publishers of this journal. When completed, the receiver case can be enclosed by the

s.r.b.p. item which was cut out at the same time as that of Fig. 2(e).

EDITOR'S NOTE

The 28-way tagstrip from which the 10-way strip is cut is a "Standard" tagstrip listed by RS Components. In its 28-way form it has a length of 267mm, whereupon the 10-way strip has a length of approximately one-third of this. The tags are vertical to the mounting surface, with every third tag providing a mounting. Other tagstrips of similar dimensions could be employed. RS Components do not supply directly to individuals, and readers wishing to obtain the particular tagstrip used by the author and who do not have access to RS Components will need to obtain it through a retailer. The small radio and television shops, and their service engineers, may be helpful here. RS Components parts may also be obtained from Ace Mailtronix Limited, Tootal Street, Wakefield, West Yorkshire, WF1 5JR, subject to a minimum order of £2. A further section cut from the 28-way strip is employed in the amplifier unit to be described next month.

A second TA10 telescopic aerial is employed in the v.h.f., medium and long wave tuner which concludes the "Doric" series and readers who anticipate making this may, if they wish, obtain the second aerial at the same time as the aerial employed for the short wave receiver which has been described here. The v.h.f., medium and long wave tuner also requires a further 4 or 4½ in. length of orange grade ferrite rod, and this is again available from Amatronix.

(To be continued)

WORLD RADIO TV HANDBOOK

The 33rd edition of "World Radio TV Handbook" has now become available. With 544 pages, the Handbook is crammed with information concerning radio and television transmissions throughout the world, and it lists the frequencies, schedules and other details of virtually every broadcasting station which is on the air. The edition takes in all the changes resulting from the Geneva Medium Wave Plan which came into effect in November 1978, and which applies to all countries outside the Americas.

The Handbook is of particular use to the short wave Dx listener who searches the bands for rewarding long distance reception. In addition to its frequency listings, the Handbook gives information on anticipated reception conditions in 1979, solar activity and similar subjects. Published by Billboard Publications Inc., the "World Radio TV Handbook" 33rd edition is priced at £8.50, and may be obtained from The Modern Book Company, 19-21 Praed Street (Dept. RC), London, W2 1NP. Price £9.15 inclusive of postage and packing.

WILMSLOW AUDIO CATALOGUE

Currently available from Wilmslow Audio Ltd. is their latest 40-page catalogue listing high fidelity speakers for all applications including domestic, group, public address and disco. The products of more than 30 manufacturers are presented in the catalogue, taking in such names as Celestion, Decca, E.M.I., Elac, Fane, Jordan, Watts, Motorola, Richard Allen, Tannoy, Wharfedale and Shackman. Products are illustrated by clear photographs and illustrations. Detailed product specifications are also provided.

It should be noted that Wilmslow Audio Ltd. now offer the widest range of speaker drive units and speaker construction kits in Britain, and have supplied loudspeakers to the BBC, IBA, the Forces, Rolls Royce and many other organisations in addition to individual hi-fi enthusiasts. The catalogue can be obtained from Wilmslow Audio Ltd., Dept. REC, Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF. A charge of 15p is made to cover postage.

A UNIQUE COMPUTERISED SYSTEM

A unique computerised system to expedite the production and lower the costs of making animated films is now being used by the Swedish Broadcasting Corporation (SBC) for its television services.

Conventional methods of preparing animated films are enormously time-consuming. Most of the work is very repetitive since each second of finished film requires from 20 to 25 almost similar drawings.

Under the new system, utilising a SPERRY UNIVAC 1100/11 computer, SBC uses a technique developed by Alan Kitching, an animation and data processing specialist, who manages Grove Park Studios in Camberwell.

The technique, known as ANTICS, begins with a basic drawing being prepared and entered into the computer using a special light pen. By means of special command words and coded direction, speed and position specifications are also inputted into the computer. The basic drawing can then be modified in different ways, for example, it can be shrunk, enlarged, panned, skewed, shaken or reversed.



A technician with the Swedish Broadcasting Corporation uses a new computerised technique to produce an animated film for television.

It can also be induced to rotate, jump, rock, etc. The system now contains some 40 commands but Alan Kitching is working on further expansion.

PORTABLE RADIO TELEPHONE

New from Marconi Mobile Marine is the only Post Office approved radiophone which doubles as a portable. Marconi Mobile Radio, a division of Marconi Communication Systems Limited, is now an approved supplier of equipment to the Post Office Radiophone Service and the new "go-anywhere" telephone, the SV 1320A, opens up new uses for the service.

The equipment is designed to fit in the corner of a car boot with the control unit and handset installed easy-to-hand for the driver or passenger when the vehicle is on the move. By removing the control and radio units from the vehicle, an

operation which takes less than a minute, the equipment becomes completely portable and is ready for use by the swimming pool, on the golf course, in the garden or on the beach.

What has hitherto been a completely impossible use for a telephone has now become feasible. The equipment can, for instance, be used as a temporary telephone on a major construction site until land lines are installed, carried across fields to a temporary remote site, or even brought along when going fishing. Any person required to keep in immediate touch with the office can have the telephone with him or

her wherever located, and the system is completely secure.

The equipment operates from a 12 volt supply and is fitted with rechargeable batteries for use away from the vehicle. In normal operating conditions the batteries will last all day without recharging and, for use away from a vehicle for a long period of time, a desk-top charger is available. The SV 1320A is especially designed and manufactured for Marconi by OY Nokia AB Electronics, Finland, and is marketed exclusively in the UK by Marconi Mobile Radio.

The 9-channel set is fully approved by the Post Office and a new 55-channel set has been submitted for approval.


EXTENSION OF DIECAST RANGE OF BOXES

Recently introduced by BOSS Industrial Mouldings Limited, of 2 Herne Hill Road, London SE24 0AU, is another Diecast Aluminium BIMBOX which, as with all of this family of high quality boxes, is available in either natural or stove enamelled grey hammertone finish.

Measuring 50 x 50 x 31 mm (2" x 2" x 1.2") this latest addition now becomes the smallest of the BIM5000 range of 6 sizes, with the largest being 190 x 110 x 60 mm (7.5" x 4.3" x 2.4").

Being readily drilled or punched, and thereby eminently suitable for prototype and production applications, the natural and hammertone finish versions are capable of withstanding 260°C (500°F) and 90°C (375°F) respectively.

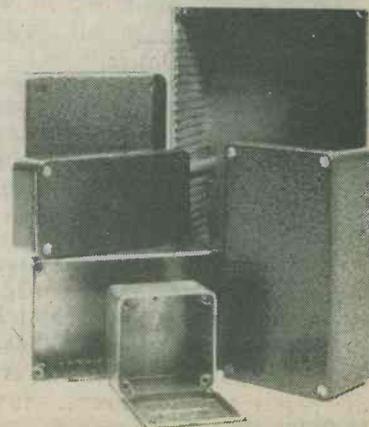The pricing structure of this whole range is very competitive, with the various sized natural versions ranging from £0.69 each to £2.25 each and the grey hammertone finish carrying only a small additional charge.



COMMENT

THE SILENT LISTENERS

Much interest amongst radio amateurs was produced recently by the showing of a T.V. programme by the Norwich BBC T.V. station, made by one of their team, Paul Wright, G3SEM, which dealt with the work done during World War 2, by British radio amateurs enrolled into the Radio Security Service as V.I.s as they were called, which stood for "Voluntary Interceptors".

This story has just been released from its secrecy after 40 years of silence, as all the participants in it had to sign the Official Secrets Act. The film traced the origin of radio intelligence from world War 1 to the establishment of the V.I. service in W.W. 2 and outlines much of the work done by this service in listening to secret radio communications within the enemy's territory and to their agents elsewhere. Much of this listening was done in the V.I.'s own homes using their own radio equipment and few realised just what the messages they were copying were all about!

Amongst those involved with this service were Professor Trevor Roper, Colonel Maltby, Colonel Hornsby, 'Dud' Charman, (G6Cj), Louis Varney (G5RV), Pat Hawker (G3VA), Hugo Lawley (G6ZG) and our own Director, Dr. Arthur C. Gee, (G2UK) who appears quite prominently in the programme, some of which was filmed in his radio shack.

RADIO TRANSMITTERS AND MODULATION TECHNIQUES — I.E.E. CALL FOR PAPERS

The Institution of Electrical Engineers is seeking papers for a Conference on Radio Transmitters and Modulation Techniques" to be held at Savoy Place on 24-25 March 1980. Those wishing to have papers considered should submit a 50-word synopsis to the IEE Conference Department by 3 September 1979.


Subjects to be covered at the Conference include the following: transmitters for communication (fixed and mobile), broadcasting, television, and navigational aid; improvements in transmitting valves; impact of power semiconductors on transmitter designs; new methods of modulation; exploitation of Doherty and pulse-width modulation and other methods for the purpose of higher efficiency; transmitter control/tuning, protection and safety; common antenna working (filters and other means); linearity control; frequency and signal generation; automatic monitoring and correction; and spurious frequencies and noise radiation.

The Conference is being organised in association with the institution of Electronic and Radio Engineers and the Radio Society of Great Britain.

For further information please contact:

Annemarie Cunningham-Swendell, The Institution of Electrical Engineers, Savoy Place, London WC2R 0BL.

AVAILABILITY OF S-DECS

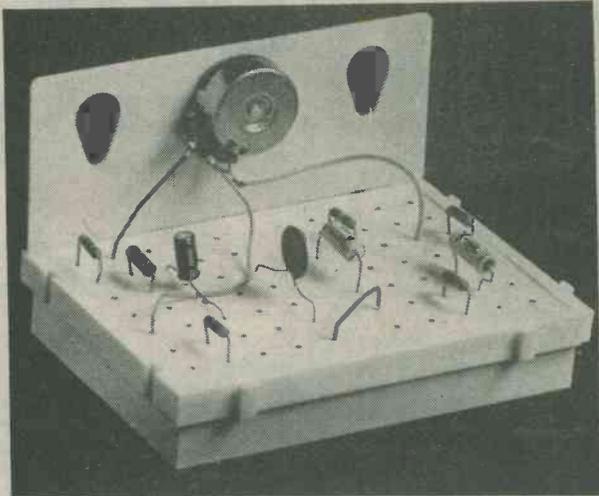

The manufacture and distribution of S-DeCs has now been taken over by Roden Products of 5 High March, Daventry. This photograph (which does not depict the assembly described in the Double Deccer article in this issue) demonstrates the neatness and simplicity which S-DeCs impart to temporary solderless circuits.

Back numbers containing numbers 1-8 of the Double-Deccer series are all still available from the publishers of this magazine.

WHO OWNS THE OLDEST RADIO?

Who owns the oldest radio that's still working? This was a competition organised by one of the BBC's local radio stations in Britain's East Midlands, Radio Leicester. And they got a bit of a surprise when the winning entry turned up.

How old do you think it was? 30 years, 40? No, more than that — there are many 40-year-old radios still in use in Britain today. This particular radio makes 40-year-old sets look like mere striplings — for the winning radio, still working, had seen service in the trenches during World War One (1914-1918) — one of the first valve radio sets ever made.

It still receives perfectly well the BBC's classical music channel and, of course, the local station that was running the competition, Radio Leicester.

It is mounted in a heavy wooden box with a leather carrying strap, and its works are completely exposed when the lid is opened. Inside the lid is a hand-drawn circuit diagram and hand-written instructions, not only telling how to use it for receiving, but also how to transmit in morse code. And the whole thing, with its batteries, is at least as heavy and big as a modern portable TV set.

BBC Radio Leicester presented the old set's proud owner, schoolmaster Gilbert King, with a prize — a new cassette recorder and radio combined.

SUGGESTED CIRCUIT

MULTIPLE 555 CIRCUITS

By G. A. French

The ubiquitous 555 timer i. c. has been employed in many home-constructor projects, featuring mainly as a one-shot timer or as an astable multivibrator. It is also possible to have applications in which one 555 switches on another 555, but these are rarely encountered. This article describes methods by means of which 555 switching of this nature can be carried out, particular emphasis being placed on techniques which result in low power supply current consumption. This last factor can be of considerable importance when the equipment incorporating the 555 is battery operated.

555 SWITCHING

The output of a 555, at its pin 3, can be either high (close to the positive supply rail voltage) or low (close to the negative rail voltage) according to the state of the voltage or voltages at its inputs. When the 555 output is high it can provide

currents up to 200mA through a load connected between the output and the negative rail, and when it is low the output can cause currents up to 200mA to pass through a load returned to the positive rail.

In Fig. 1 (a) the output of ICA controls the operation of ICB, turning on the latter when ICA output is high. The operating current of ICB (and its immediate circuitry) is supplied, when it is turned on, through the output stage of ICA. In Fig. 1 (b) a similar situation is given, except that ICB is turned on this time when the output of ICA is low. Again, the operating current for ICB is provided by way of the output stage of ICA.

At first sight, there may appear to be little to choose between the two modes of operation but, when we look at the internal output stage inside the 555, we find that there are considerable differences. This output stage is shown in Fig. 2. When the 555 output is high, the high

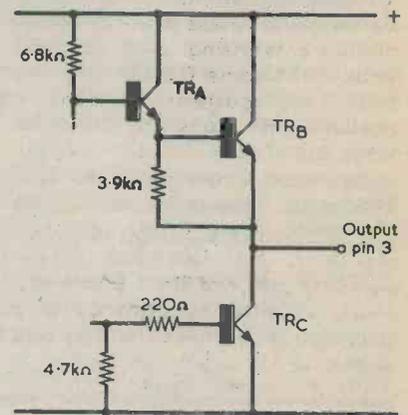


Fig. 2. The internal output stage circuit of the 555. Resistor values are nominal

voltage is maintained by the current passing through the 6.8K Ω resistor into the input base of the Darlington pair consisting of TRA and TRB. The bottom transistor, TRC, is cut off. It will at once be apparent that, even with a negligibly low load current, the output voltage must be less than the positive supply rail voltage by the base-emitter voltage drops in TRA and TRB these drops totalling about 1.2 volts. Further, the output voltage regulation, although quite adequate for normal 555 applications, is by no means perfect, and the output voltage can fall noticeably as load current increases. If, therefore, the switching circuit of Fig. 1 (a) is employed, the supply voltage provided through ICA to turn on ICB will be at least 1.2 volts below the positive rail and can be lower again if ICB draws a high current.

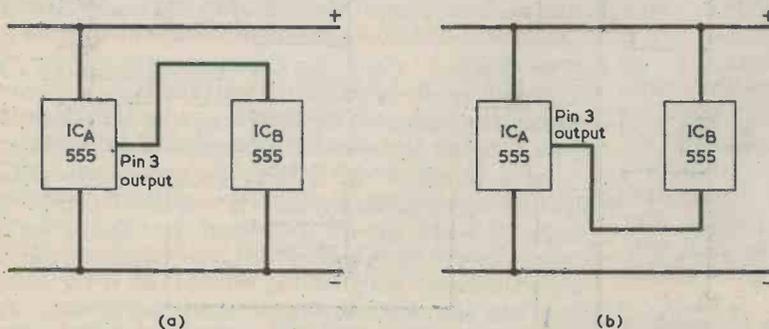


Fig. 1(a). One way of using a 555 i. c. to switch another 555. The second i. c. is turned on when the output of the first goes high

(b). With this alternative method the second i. c. is switched on when the output of the first is in the low state

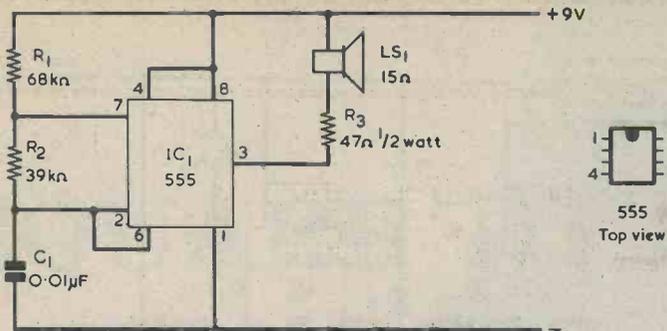


Fig. 3. A typical 555 multivibrator. This produces an a.f. tone with a frequency of 1kHz

Returning to Fig. 2 the output state given when the 555 output is low is provided by having TRA and TRB cut off, and TRC turned hard on. In this case the voltage drop between TRC emitter and collector will be typically less than 0.1 volt at low currents, rising to only slightly higher than some 0.2 volt at quite high load currents. Currently available 555 i.c.'s appear to be particularly good in this respect, those checked by the author exhibiting less than 0.2 volt drop at load currents of the order of 25mA and more. In consequence, the switching circuit of Fig. 1 (b) offers a better potential performance than does that of Fig. 1 (a): it allows very nearly the full supply voltage to be applied to the 555 which is controlled, and the applied voltage has good regulation. A further point not yet considered is that an unwanted amplification loop could be set up between the two i.c.'s when they share a common impedance. In Fig. 1 (b) the common impedance is a transistor which is turned hard on, and this can be almost completely relied on to break such a loop. As we shall see shortly, there can be another reason for preferring the approach shown in Fig. 1 (b).

MULTIVIBRATOR

Fig. 3 shows a standard 555 a. f. multivibrator driving a loudspeaker. The values of the timing components R1, R2 and C1 give a calculated running frequency (using Signetics data) of precisely 1kHz. The 555, when used as an audio oscillator, does not always perform satisfactorily if connected directly to a loudspeaker, and for this reason the 47Ω resistor is inserted in series. The a. f. tone produced is readily audible in normal circumstances. If the speaker is disconnected so that the i. c. oscillates without a load, the current drawn from the 9 volt supply is around 4mA.

The output at pin 3 is high during that part of the cycle when C1 charges via R1 and R2, and is low when C1 discharges through R2 on its own. With the component values shown, the output is high for about 75% of the cycle and is low for about 25% of the cycle. If we were to return the speaker to the negative rail, current would flow through it and through R3 for 75% of the cycle, whereas if we return the speaker to the positive supply, as is done in Fig. 3, the current flows for only 25% of the cycle. The average current drawn from the 9 volt supply will obviously be lower for the second mode of connection, and it is that which is to be preferred. In practice the total current drawn is about 25mA, this being the sum of the 4mA standing current in the i. c. and the average of the intermittent current passed by the speaker and R3.

In Fig. 4 we add a second 555, IC2, to form a 1-second bleeper.

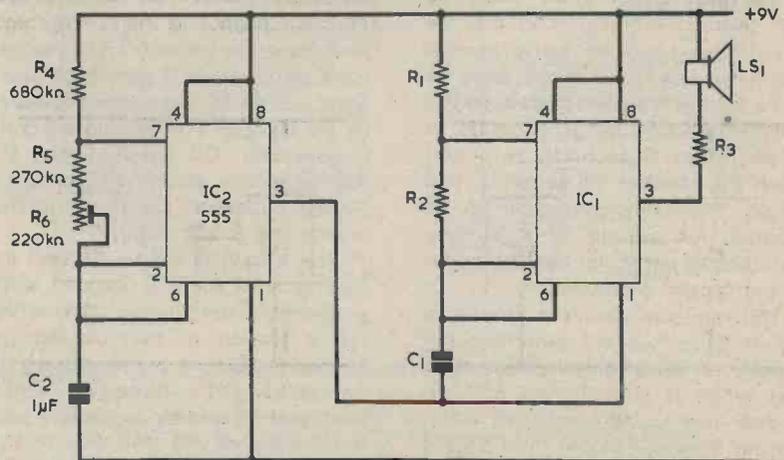


Fig. 4. Here, IC2 switches IC1 of Fig. 3 to form a 1-second bleeper. The average current consumption is considerably lower than that of the multivibrator on its own

The value of C2 is 100 times that of C1, whilst the value of R4 is 10 times that of R1. R5 and R6 in series can be set up to have 10 times the value of R2. With the capacitance value multiplied by 100 and the resistance values multiplied by 10, the frequency is divided by 1,000, whereupon the running frequency of IC2 is 1Hz. As with IC1, the output at pin 3 is high for about 75% of the cycle and low for about 25% of the cycle. If we used the switching circuit of Fig. 1(a), apart from any other difficulties the oscillator would be running for 75% of the time and the average current drawn from the 9 volt supply would be high. The arrangement of Fig. 4 employs the circuit of Fig. 1(b), with the result that the oscillator runs for only 25% of the time. Note that the *whole* of the oscillator circuit, including C1, is fed from the output of IC2. When pin 3 of IC2 is low the 1kHz oscillator draws its 25mA through the output transistor of IC2, and when pin 3 of IC2 is high the 1kHz oscillator draws no current at all.

The total current consumption of the circuit of Fig. 4 is the standing current of about 4mA in IC2 plus the 1kHz oscillator current of 25mA in IC1 for 25% of the time. These currents average out at slightly more than 10mA. So, by using the switching circuit of Fig. 4 we have obtained a bleeper whose average current consumption is two and a half times lower than the actual current drawn by the bleeper audio oscillator on its own! This large saving in current is almost entirely due to the technique of switching on the

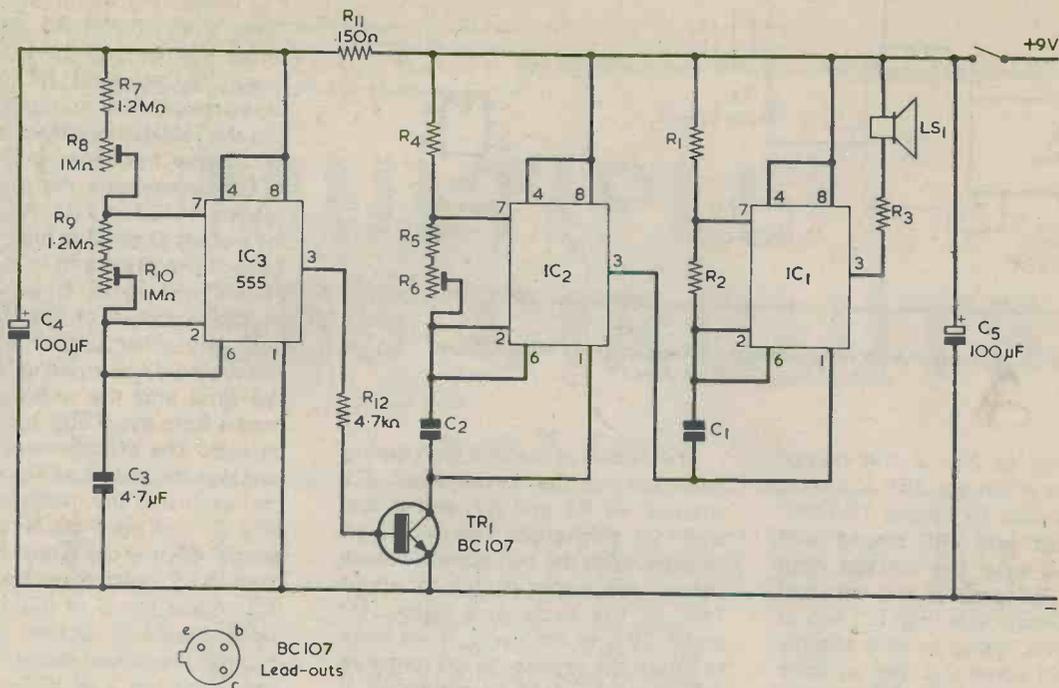


Fig. 5. Yet another 555, IC3, is added to the circuit of Fig. 4. The bleeper is turned off for 5 seconds and is then turned on for 10 seconds, giving a total cycle length of 15 seconds

oscillator from the output of IC2 when that output is in the low state.

In practice, the tolerances in the timing components of IC2 are taken up by adjusting R6 so that the bleeper runs as near to 1Hz as can be arranged. The bleeper can then function as a photographer's metronome or for timing other operations which are carried out in fixed numbers of seconds.

A THIRD 555

The metronome performance would be enhanced if we were to add a further 555 which caused the bleeper to sound for 10 seconds, to be silent for 5 seconds, to sound again for another 10 seconds, and so on. The complete cycle of 15 seconds, or quarter of a minute, would be of particular assistance for timing longer processes.

The requisite circuit is shown in Fig. 5. Since we are switching the bleeper on for a longer period than that when it is switched off, the bleeper has to be turned on when the pin 3 output of the third 555 is high rather than when it is low. The difficulties mentioned earlier will be present if we attempt to supply the bleeper directly from the pin 3 output when it is high, and there is

another problem in the present instance which is due to the switched pulses already present on the positive supply rail. These make it necessary to decouple the positive supply to the third 555 to prevent false triggering. If the bleeper were to draw current from its pin 3 that current would also flow through the decoupling resistor.

In Fig. 5 IC3 turns the bleeper on and off by way of the inverting transistor TR1. When IC3 output is low, TR1 is cut off and the bleeper section draws no current. TR1 is turned hard on when pin 3 goes high and it then passes all the current required by the bleeper. The decoupling components for IC3 are R11 and C4. Although not entirely essential, a bypass capacitor, C5, is also added across the 9 volt supply.

The circuit is set up by first adjusting R10 for a 5 second silent period from the bleeper, after which R8 is set up so that the bleeper produces 10 tone pulses during the period when it is turned on. It may be found necessary to slightly alter the values of R9 and R7. If it is found that the 5 second period is outside the range of R10 the value of R9 may be slightly increased or decreased as necessary. Similarly, the value of R7 may be slightly in-


creased or decreased if the requisite series of 10 bleeps is outside the range of R8. With the prototype, the final settings in R8 and R10 were fairly close to the centres of their slider travel.

The total current from the 9 volt supply is now 4mA in IC3 when the bleeper is silent plus the current drawn by the bleeper and that flowing through R12 when the bleeper is turned on. The average current is therefore about 12mA, a slight increase on the average current of the continually running bleeper on its own.

Apart from R3, all the resistors in the circuits shown are $\frac{1}{4}$ watt, with a tolerance of 5% below 1M Ω and 10% above 1M Ω . Both C2 and C3 should be polyester capacitors. 4.7 μ F polyester capacitors are available from Greenweld, 443 Millbrook Road, Southampton. The three pre-set potentiometers can be 0.1 watt skeleton types.

A final point is that, after switching on the circuit of Fig. 5, the bleeper will produce more than 10 tone pulses before the circuit settles into its cycles of 5 seconds silence followed by 10 bleeps. The extra bleeps immediately after switch-on are given as C3 charges initially from its fully discharged state. ■

SQUARE WAVE

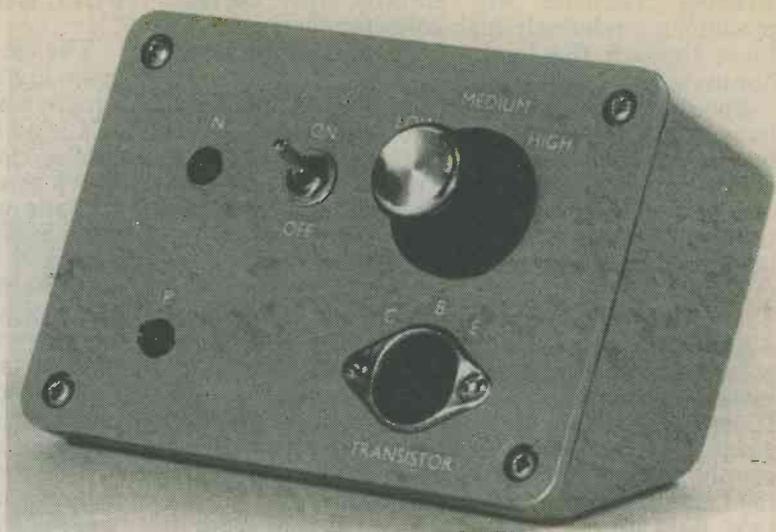

TRANSISTOR TESTER

By R. A. Penfold

N.P.N. AND P.N.P. TESTS WITHOUT POLARITY SWITCHING.

This very simple and handy device is not intended to give accurate measurements of current gain and leakage in transistors, but is meant to give a quick check of whether or not a transistor is serviceable, together with a rough indication of its gain. In most instances this is all that one needs to know about a transistor, and the device has the particular advantage that polarity switching for n.p.n. and p.n.p. transistors is carried out automatically. The unit can also be used to check rectifiers and diodes, and to indicate their polarity.

OPERATING PRINCIPLE

A basic test circuit for an n.p.n. transistor is shown in Fig. 1(a). When only the emitter and collector terminals of the transistor are connected into circuit the test transistor should pass only a very small leakage current. This flows through the light-emitting diode, D1, but will be too small to cause the diode to light up.

If the base terminal is next connected into circuit a small base-emitter current will flow via R1. A ser-

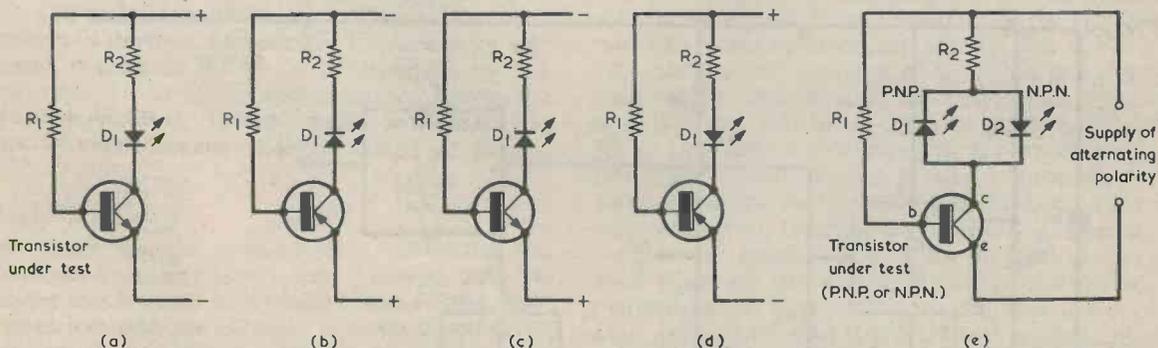


Fig. 1(a). A simple n.p.n. transistor test circuit. The l.e.d. should light when the test transistor is connected into circuit

(b). The supply and l.e.d. polarities have to be reversed for a p.n.p. test transistor
(c). Provided that the supply voltage is low, the l.e.d. will not light if an n.p.n. transistor is connected to the p.n.p. test circuit

(d). Similarly, a p.n.p. transistor will not light the l.e.d. in an n.p.n. test circuit

(e). The circuits of (a) and (b) can be combined in a single circuit powered by an alternating supply

viceable transistor will amplify this current, producing a relatively high collector current which flows through the l.e.d. and causes it to be illuminated.

Should the test transistor not be functional and have a high leakage current or a short-circuit between its collector and emitter, this will be indicated by the l.e.d. lighting up before the connection of the base terminal. An indication that the test transistor is open-circuit will be given if the l.e.d. does not light up when the base is connected to R1.

The same arrangement can be used for checking p.n.p. transistors except, of course, that the polarities of the supply and the l.e.d. have to be reversed. The required circuit is shown in Fig. 1(b). If, as in (c), an n.p.n. transistor is connected in a p.n.p. test circuit, assuming a fairly low power supply voltage, the transistor will not conduct and the l.e.d. will remain extinguished. Neither will the l.e.d. light up if a p.n.p. transistor is connected in an n.p.n. test circuit, as in Fig. 1(d).

These results enable the basic circuits of Fig. 1(a) and Fig. 1(b) to be combined into the single test circuit of Fig. 1(e). Here the supply continually alternates from one polarity to the other and D1 is replaced by two l.e.d.'s connected in parallel with opposite polarities. When a serviceable n.p.n. transistor is connected to the circuit it will pass collector current on the half-cycles when the upper supply rail is positive, and D2 will light up. On the alternate half-cycles, when the upper rail is negative, no current will flow and neither l.e.d. will be alight. Thus, D2 will flash on and off at the frequency of the alternating supply to indicate that the transistor is serviceable and that it is an n.p.n. type. A short-circuited test transistor will cause D2 to flash on and off, and also cause D1 to flash on and off out of phase with D2. A transistor with high leakage current will be indicated by D2 flashing on and off before the base terminal is connected. An open-circuit transistor will result in neither l.e.d. becoming alight.

With a p.n.p. test transistor the circuit will behave in the same way as with an n.p.n. transistor, except that all indications which were previously given by D2 will now be given by D1, and vice versa.

FULL CIRCUIT

The complete circuit of the transistor checker is given in Fig. 2. The alternating voltage is given by a square wave generator comprising IC1 and TR1. IC1 is a 555 operating in the astable mode, and its timing components, R1, R2 and C2, have values which give a running frequency of about 2.3Hz. R2 is made very high in value relative to R1 so that what is virtually a 50:50 square wave is obtained. The 555 output appears at its pin 3 and this provides one of the alternating supply points. Pin 3 also connects to the base of TR1 via current limiting resistor R3, whereupon TR1 functions as an inverter, providing the second alternating supply point at its collector. When pin 3 of the 555 is positive the collector of TR1 is negative, and when pin 3 is negative the collector of TR1 is positive.

Comparing with Fig. 1(e), the supply point at the collector of TR1 connects to the emitter of the test transistor. The supply point at pin 3 of IC1 couples via R5 and the two parallel connected l.e.d.'s to the collector of the test transistor. There are slight differences with Fig. 1(e) in that the single resistor coupling to the base of the test transistor now consists of one of the three resistors selected by S1, and also that these resistors are returned to the junction of R5 and the l.e.d.'s rather than to the upper rail, as in Fig. 1(e). This connection merely means that a slightly lower voltage, of either potential, is applied to the series base resistor.

When pin 3 of the 555 is positive the voltage it provides is about 1.2 volts lower than the positive supply rail. When pin 3 is negative and the collector of TR1 is positive, the positive supply to the test circuit is made via the series resistor R4. With transistors other than open-circuit types connected to the test terminals, there will be a voltage drop of up to some 2 volts in R4. This voltage drop does not affect the basic functioning of the circuit.

Having three resistors in the base circuit enables approximate indications of test transistor gain to be given. R8 gives the highest base current and even a low gain transistor should turn hard on when this resistor is selected. A much smaller base current is provided by R7, and only medium and high gain transistors will cause the appropriate l.e.d. to flash on at full brilliance. R6 gives an even smaller base

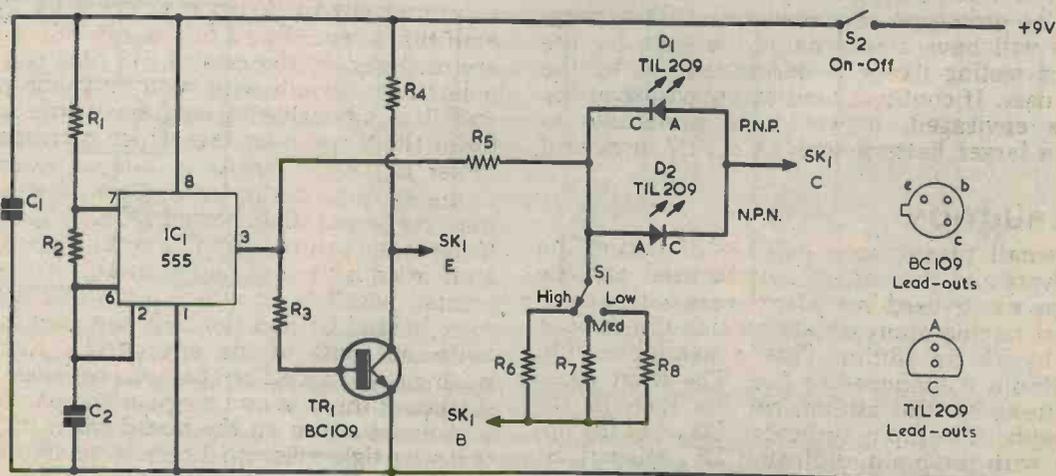


Fig. 2. Full circuit of the transistor tester. One rail of the alternating power supply appears at pin 3 of IC1, the other rail being given, after inversion, at the collector of TR1

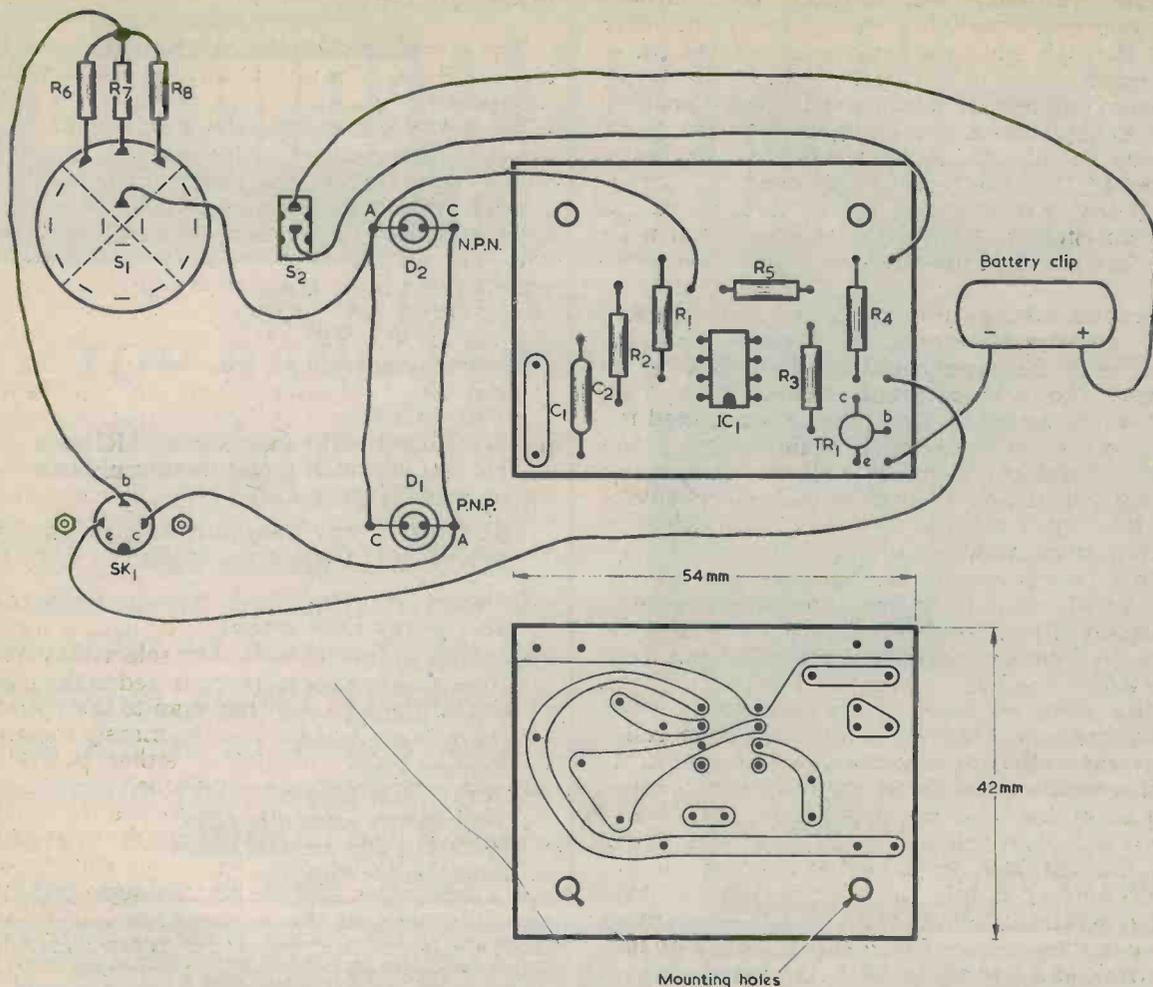


Fig. 3. Preparation of the printed circuit board and the point-to-point wiring in the transistor tester

current, and only high gain transistors will produce full brilliance from the l.e.d. when this resistor is switched in. In consequence, it is possible to obtain a reasonable idea of the test transistor gain by adjusting S1.


S2 is the on-off switch and C1 is a supply decoupling capacitor. The current consumption from the 9 volt battery is of the order of 16 to 18mA. The prototype unit employs a PP3 battery, and this will have a reasonable life span for the transistor testing likely to be carried out by the average user. If continual and extended use of the tester is envisaged, it would be preferable to employ a larger battery such as a PP7 or even a PP9.

CONSTRUCTION

Any small plastic case capable of taking the components and the battery may be used, and the prototype was housed in a plastic case with a sloping panel having approximate outside dimensions of 107 by 75 by 43mm. This is available from Home Radio (Components) Ltd. The front panel layout used by the author can be seen in the photographs. The n.p.n. indicator, D2, is at the upper left, with the p.n.p. indicator, D1, below it. S1 is at upper right with the test transistor socket below it, and S2 appears between D2 and S1. The l.e.d.'s are held in place by panel mounting bushes, and connections are made direct to their lead-outs.

The test transistor socket is a 3-way DIN socket, and many small transistors will plug directly into this. To cater for those which will not it is necessary to make up a test lead set. This simply consists of a 3-way DIN plug to which are connected three flexible leads of different colours terminated in miniature crocodile clips.

Most of the small components are assembled on a printed circuit board measuring 54 by 42mm., and this is reproduced full size in Fig. 3. R6 to R8 are mounted on the tags of S1. This is a 3-way 4-pole rotary switch with with only one pole used, and it is advisable to confirm with a continuity tester the three outer tags which correspond to the inner tag before wiring to this component. With some switches the relative positioning of the tags may vary from that shown in Fig. 3. The mounting holes in the printed circuit are for 6BA or M3 bolts and, when all the wiring is finally completed, the printed board is mounted on the rear panel of the case, behind S1 and the DIN test socket, by short bolts and nuts of the appropriate size. Spacing washers are needed on the bolts between the inside surface of the case and the printed board underside to prevent strain on the board when the nuts and bolts are tightened up. There is plenty of space for the PP3 battery in the remaining space on the rear panel and this can be held in place with a home-made metal bracket. Alternatively, the battery can be secured by a piece of Bostik Blue Tack.

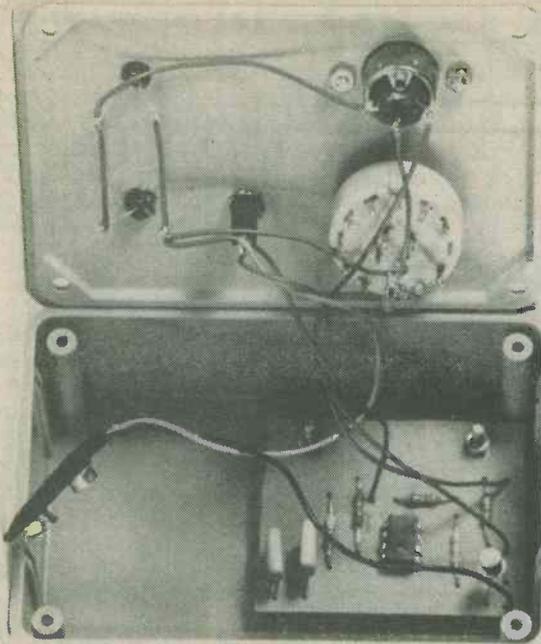


The printed board and the battery are positioned at the rear of the case. The remaining components are mounted on the front panel

USING THE UNIT

After completion the unit should be switched on with no test transistor connected. If either of the l.e.d.'s flashes even dimly there is a wiring error which has to be corrected.

When testing transistors, only the emitter and collector of the test transistor should be initially connected to the unit, whereupon neither l.e.d.'s should light up. Germanium transistors have higher leakage currents than silicon types and it is possible that a functional germanium device may cause one of the l.e.d.'s to light up rather dimly. However, the author tested a number of germanium transistors including small power output types, and none of them exhibited a sufficiently high leakage current to cause a visible glow in either l.e.d. When the base of the test transistor is

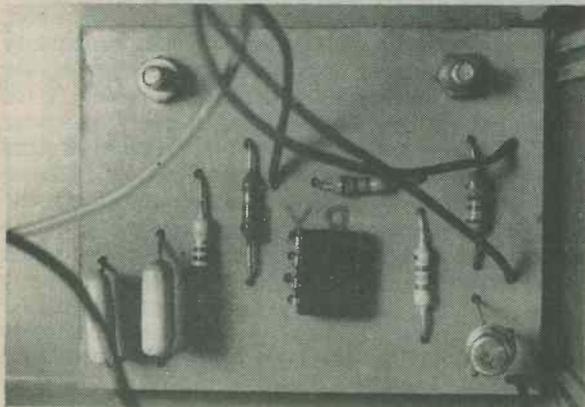

The printed circuit board is quite a simple assembly, with the components arranged as shown here

COMPONENTS

Resistors

(All $\frac{1}{4}$ watt 5% unless otherwise stated)

R1 1.2k Ω	R5 1k Ω
R2 6.8M Ω 10%	R6 1M Ω
R3 15k Ω	R7 100k Ω
R4 560 Ω	R8 10k Ω

Capacitors

C1 0.1 μ F type C280
C2 0.047 μ F type C280

Semiconductors

IC1 555
TR1 BC109
D1 TIL209 with panel-mounting bush
D2 TIL209 with panel-mounting bush

Switches

S1 1-pole 3-way miniature rotary (see text)
S2 s.p.s.t. subminiature toggle

Socket

SK1 3-way DIN socket

Miscellaneous

Plastic case (see text)
9-volt battery type PP3 (see text)
Battery connector
Control knob
3-way DIN plug
3 miniature crocodile clips
Materials for printed board
Nuts, bolts, wire, etc.

connected to the checker, either D1 or D2, as appropriate to the transistor type, should flash on and off at a rate of the order of 2 times a second.

If both l.e.d.'s flash on and off when the emitter and collector terminals are connected to the checker the test transistor is short-circuited and is unusable. Should neither l.e.d. flash when all three terminals are connected then the transistor is open-circuit and is similarly unusable.

For these tests, S1 is always set to the position which brings R8 into circuit. S1 is brought into use when a medium or high gain transistor is suspected of having inadequate gain or when it is desired to select transistors in approximate terms of gain. After confirming the general serviceability of the transistor with R8 selected, S1 then switches in R7 and R6. With R7 in circuit the test transistor needs to have a gain of about 50 times or more in order to bring the appropriate l.e.d. up to about full brightness. A current gain of at least a few hundred times is required for the same indication with R6 selected. On the prototype unit, the corresponding positions of S1 are indicated on the front panel by the legends "LOW", "MEDIUM" and "HIGH". These legends are cut out from "Panel-Signs" Set No. 3, available from the publishers of this journal.


Rectifiers and diodes may also be checked. The cathode (usually marked by a coloured band around the body of the component) is connected to the emitter test point and the anode to the collector test point. This should result in D2 (n.p.n.) flashing on and off. If the connection causes D1 to flash then the cathode has been connected to the collector instead of the emitter test point. If neither l.e.d. flashes the rectifier or diode is open-circuit, and if both l.e.d.'s flash the device is short-circuited. ■

RADIO & ELECTRONICS CONSTRUCTOR

IN OUR NEXT ISSUE TOP BAND FERRITE AERIAL UNIT

Direction reception on
160 metres

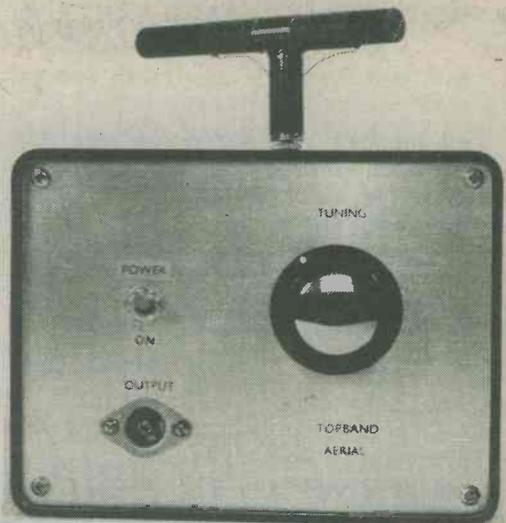This Top Band active ferrite aerial unit incorporates a buffer amplifier to convert the high impedance signal voltages across the aerial to a low impedance suitable for coupling to a short wave receiver. The aerial above the case is free to be rotated.




SILICON DIODE P.I.V. TESTER



Low cost current voltage generator gives safe indications of rectifier breakdown voltage.

A.M. NOISE BLANKER

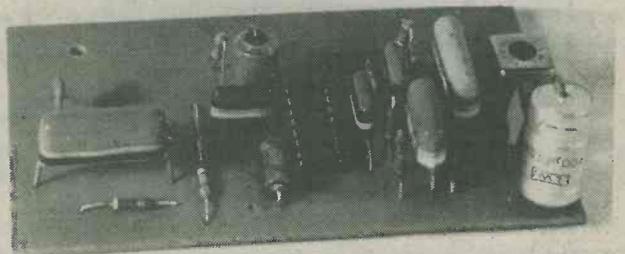How to remove interfering noise spikes in a.m. radio receivers.



*Polarity Protection Circuit
Suggested Circuit*

*Dead Stereo Channel
In Your Workshop*

MANY OTHER ARTICLES

ON SALE 6th AUGUST 1979 Avoid disappointment. ORDER NOW

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 10%)

R1 150k Ω

R2 390 Ω

R3 390 Ω

R4 12k Ω

VR1 2.2M Ω potentiometer, linear

Capacitors

C1 0.47 μ F type C280

C2 10 μ F electrolytic, 16 V. Wkg.

Semiconductors

IC1 CD4011

IC2 CD4022

D1 light-emitting diode, red

D2 light-emitting diode, red

Switch

S1 1-pole 8-way rotary

S2 s.p.s.t., toggle or slide

Miscellaneous

Circuit board

Battery, 6V, 9V or 12V

2 knobs

Case

of G2 is fed to both inputs of G3 which acts as an inverter giving an output signal with steeply rising edges. This output feeds an l.e.d., D2, through a current limiting resistor. The l.e.d. is taken to the positive supply line so that it is on when the output of G3 is low, and therefore when the output of G2 is high. The output of G3 also feeds pin 14 of IC2. IC2 is a divide-by-eight counter with eight decoded outputs and pin 14 is the clock input. To make the counter operate it is necessary to take the clock enable input (pin 13) low, and in this application the enable pin is wired permanently to the negative supply line.

On each rising edge of the clock input the counter advances by one and the corresponding output goes high. The reset pin (pin 15) is switchable between any of these outputs and this has the effect of altering the divide ratio of the counter. Consider what happens if the reset pin is connected to the "4" output. The chip counts from zero to three in the normal manner and then, on the next rising edge of the clock input, the "4" output goes high. This is of course connected to the reset input so the latter is also taken high, setting the counter to zero. Thus the counter spends practically no time with the "4" output high. In all, four pulses on the clock input cause the "0" output to go high once; this means that the counter is operating in a divide-by-four mode.

Now, the "0" output is fed to one of the inputs to G4, whose other input takes the original clock signal from the multivibrator. The output of G4 drives the l.e.d. which indicates the downbeat. Because G4 is a NAND gate, it is again necessary to drive the l.e.d. between the output and the positive supply line, giving inverted operation.

Since the "0" output goes high once per complete cycle, the effect is that D2 flashes at a regular rate, and on every, say, fourth flash D1 flashes with D2,

indicating the downbeat. The fact that when D1 flashes, D2 flashes at exactly the same time gives great visual impact. Naturally, setting S1 to alternative positions controls the number of flashes in D2 for every downbeat flash in D1. With S1 at position "8" the counter itself divides by this number.

CONSTRUCTION

Layout is not critical and the metronome can be built in any way favoured by the constructor. The author's prototype was assembled using plain 0.1 in. perforated board and i.c. sockets, and a wiring pencil dispensing solder-through enamelled wire. Since the integrated circuits are CMOS devices, the sockets enable the wiring to be completed and checked before the i.c.'s are removed from their shorting foam or foil and inserted in their holders.

Switch S1 can be a single pole 12-way rotary type with adjustable end stop set for 8-way operation. The supply voltage may have any value between 6 and 12 volts.

The housing is very much a matter of personal taste, although if the unit is to be used for concerts the traditional pyramidal housing might best be neglected in favour of a more unobtrusive box which can rest on the conductor's podium. Both the tempo control, VR1, and the beats-per-bar switch must be clearly calibrated and easily accessible. The calibration of VR1 is an easy matter, consisting of counting the number of flashes of the faster l.e.d. in a minute at different settings of the potentiometer. This value is the number found on a musical score.


It would be unreasonable to say that a box such as this will ever replace the conductor, but it may help to make his task at least a little less demanding. ■

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is 63p, inclusive of postage and packing.

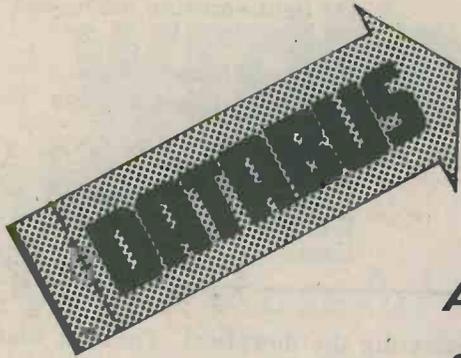Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.



At last! A comprehensive jargon-free guide to digital electronics specifically for the electronics enthusiasts.



PREFACE TO THE SERIES

Have you ever had a guilty feeling that you really ought to know something about microprocessors? Have you then found that all the books and articles you looked at seemed to be written in a foreign language? If so, this series is for you. It's written in English, and the aim is to explain microprocessors from the beginning, for the beginner, rather than from halfway on for the committed micro-nut. We have to assume some starting point, and the one we've taken is that the reader has some clue about digital signals (1 or 0), knows a little about logic gates (AND, OR) and has heard of a shift register. If you're rusty or uninformed on these topics, then you'll find this series a lot easier on the aspirins if you do a little bit of homework on these topics. If you're up to date on these (and we'll remind you about them), then you're ready to start!

The three basic questions that anyone starting to take an interest in microprocessors has to ask are: what are they, what do they do, and how do they work? We can't answer these questions in one part of a series, and the last question couldn't be answered *in detail* even in a large book. The microprocessor has been with us for ten years now, and progress has been really fast so that catching up is a painful process.

It is not helped, either, by some of the books that are around. The genuine manufacturers' databooks are useful, and some of the texts are well put together, but it's only too easy to lash out several pounds for a few scappily-duplicated sheets which tell you very little.

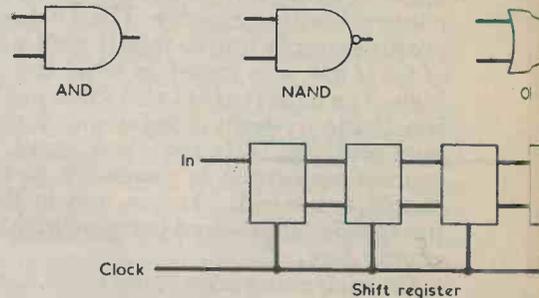


Fig. 1. Standard gate types and a shift register.

WHAT ARE THEY?

This is the easiest of the questions to answer. A microprocessor is a large scale integrated circuit (LSI circuit) which contains logic gates and shift registers arranged so that digital signals can be directed from one part to another under the control of other signal inputs. Let's compare it to something which has been around a bit longer. A telephone exchange exists to direct messages from one place to another by making connections. The connections are made automatically, by dialling a number code which causes the telephone line selectors to operate. You can imagine the microprocessor as a shrunken telephone exchange. The messages are digital signals, each consisting of eight digits or bits, and the code which decides which connections are made is called the program. If you've followed the "Tune-in to Programs" series, you'll know quite a bit about the idea of programming already.

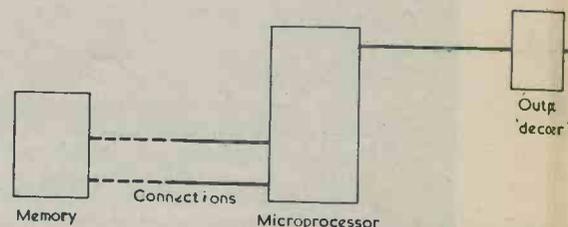



Fig. 2. The hardware surrounding a microprocessor would need at least.

JS No. 1

HOW MICROPROCESSORS WORK

Explanation of microprocessors written
by a person who understands elementary logic.


By Ian Sinclair

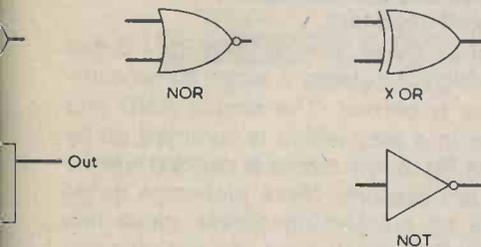

These are the bread and butter components of
circuits

WHAT CAN IT DO?

By itself, it can do practically nothing. A microprocessor by itself is about as useful as a car wiring loom, with no car. To be of any use, the microprocessor needs two important collections of items. One set is called hardware, and it consists of all the i.c.'s, relays, thyristors, motors and other gadgets that are needed to make use of the microprocessor signals. Even if the microprocessor only has to switch on a light, you still need to make the microprocessor signal operate a switch — you can't just connect a microprocessor to a lamp bulb and hope for the best. Similarly, you need i.c.'s to provide the program for the microprocessor, to store any signals that need to be kept in memory, and even to act as input or output stages. After all, you wouldn't buy a radio i.c. without expecting to have to connect an aerial and a loudspeaker!

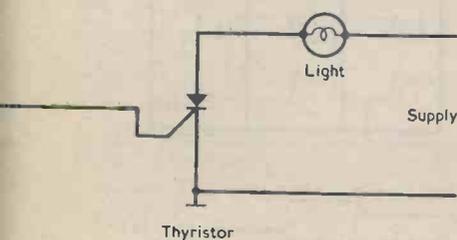

Even to operate a light, a microprocessor
needs the items shown

The other set of essentials is called software, and consists of the program instructions. These might be a set of numbers written down, a tape cassette recorded with signals, punched paper tape, or even an i.c.; but absolutely nothing can happen without these program instructions. There's an important difference here. The hardware items, once designed,

Address	Data
0200	A510
0202	A611
0204	8511
0206	8610
0208	00

Fig. 3. Software — a tiny chunk of program.
This example takes a number from memory and
then returns it

can be churned out by factories in huge quantities and at reasonable prices. Software, even if only a short program, takes hours of thought and effort to develop, is *always* expensive, and must be 100 per cent correct. One single program may cost more than all the hardware put together.

At this point, a small warning is needed. Lots of people are in the business of persuading you to buy microprocessor development kits. There's nothing wrong with these kits as such, they are intended to make life easier for the professional engineer who is writing programs for machine control applications and they are ideal for the job. Unless you have such

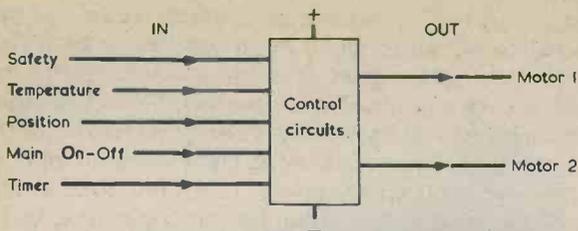


Fig. 4. Logic control. In this example various control signals fed into the controller are used to produce two output signals

a task in mind, though, they aren't so useful unless you really have an interest in programming. The capability of these devices for useful programs isn't a patch on a programmable calculator, and you'll find that even a simple program to add two fairly small numbers together takes a lot of learning.

Of course, many of these kits can be expanded into micro-computers. But do you really need a computer? If you do, then it'll be cheaper in the long run to consult IBM — at least all the snags will be ironed out, and there will be plenty of software at reasonable prices. What you save on hardware by buying or building a computer (which can still cost £400 upwards when all the necessary "extras" are bought) you lose in lashing out £50 or more for each program, or in countless hours of work writing your own. Of course, if you want to learn programming the expensive way, or if you're the only guy in the road without one...

When we're honest with ourselves, very few people *need* a computer, and very few will design control circuits. Nevertheless, we are going to find microprocessors cropping up in useful applications (as distinct from toys and status symbols) and we need to understand them. Just because we couldn't design a TV receiver is no cause for not understanding how it goes about its job, and the same is true for the micro. This series, then, will prepare you for the workshop manuals that will come with the next generation of washing machines, control heating systems and car electrics.

HOW DO THEY WORK?

Now we start on the answer to the third question, the one which will take up all the rest of this 12-part series. To start to understand how a microprocessor works, we really have to go back ten years in time to the events that led to the design of the first microprocessor. Visualise, if you can, the range of control applications for which t.t.l. and CMOS i.c.'s were being used some ten years ago. These applications included the control of machines like lathes, chemical processing plants, some air-conditioning systems and of course, computers; all large and costly machinery. In each case a large number of inputs was taken to a logic circuit, which produced outputs that turned motors or valves on or off, adjusted settings, changed temperatures. These logic circuits consisted of gates, like the familiar AND and OR gates, along with the very useful components called shift registers.

Remember what these components do. Gates give an output which is at logic 1 when some combination of inputs is correct. The simple AND and OR gates behave in a way which is summed up by the truth tables of Fig. 5; the output is decided entirely by what inputs are present. More elaborate gates can all be made by connecting simple gates like these into logic circuits, so that we can design a circuit to have any truth table we choose. For example, the truth table of Fig. 6 can be carried out (or *implemented*) by the circuit of Fig 7; the really complicated truth tables for machine control would, of course, need a large number of logic gates and would take a long time to design.

Shift registers do something quite different — they store a set of binary digits. A binary digit (or bit) is a 0 or a 1, and a set of eight is usually called a byte; these sets of eight are the groups that are used in microprocessors. When a set of bits, which may be any number but is often an 8-bit byte, is loaded into a shift register, it can be stored there. The shift register consists of flip-flops, each of which can be set to give a 1 or 0 output, and which can be clock-

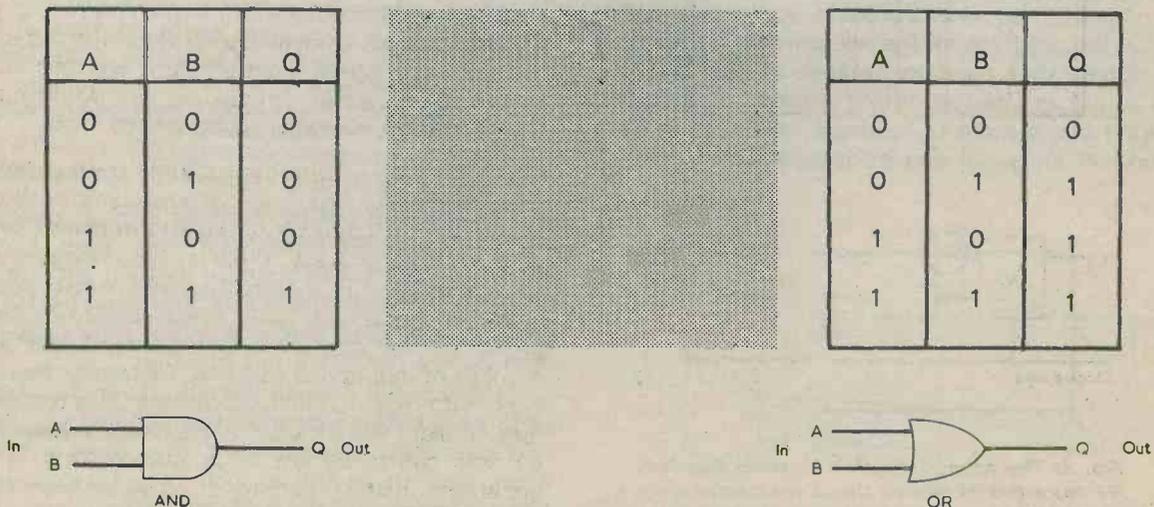


Fig. 5. Two "standard" gate types, and their truth tables. The truth table shows what the output will be for any possible combination of inputs. Two-input gates are shown

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Fig. 6. A truth table which might be needed in a control system. The output is 1 only if at least two of the inputs are at logic 1

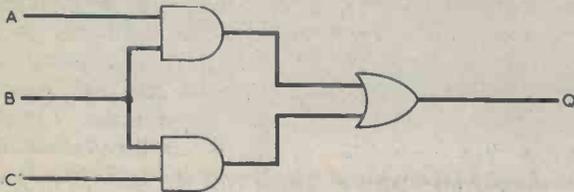


Fig. 7. An arrangement of gates which can produce the truth table of Fig. 6

Pulse No.	Q ₀	Q ₁	Q ₂	Q ₃
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3	0	0	0	1
4	0	0	0	0

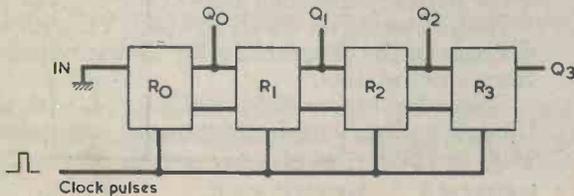


Fig. 8. The action of a shift register. Flip-flop R1 has a 1 at its output, the others have 0's. At each clock pulse, the 1 is shifted right into the next flip-flop. Any pattern of 0's and 1's stored in the flip-flops of the register would also be shifted. Left shift is also possible

ed. "Clocked" means that a clock pulse, a brief pulse repeated at intervals, is applied to each flip-flop in the shift register, causing the bits to shift one place from one flip-flop to the next in line. A direction control can decide whether this shift is to the left or to the right by altering the voltage on one pin of the i.c., perhaps 0 for left, 1 for right. Such a shift register can be filled either by sending a bit to an input pin for each flip-flop, a system called parallel entry, or by feeding a bit in at each clock pulse, a system called serial entry. Similarly, a register can transfer its bits along a set of lines (eight for a byte) in parallel, or one at a time along one line in serial form. If the output of the final flip-flop of the shift register is connected back to the input, then a complete set of clock pulses will leave the register just as it was before the clock pulses, even if each pulse has operated a gate on the way. A complete set of clock pulses means one clock pulse per flip-flop, eight for a byte. The bits can be stored unchanged therefore until a new set of inputs is loaded into the register. Now if all this is new to you, you aren't ready for reading about microprocessors yet. The aim of this very brief summary is to refresh the memory, not to teach from scratch, and to indicate where we start from.

Using shift registers along with gates, we can carry out any operation we like, providing that it can be done using binary digits. We can, for example, add binary numbers, subtract, multiply and divide them, decide when one number is equal to, greater than or less than another. We can also load numbers in, store them, and read them out; anything provided that what we operate on must be binary numbers. All of these operations can be carried out by digital circuits using gates and shift-registers.

Now the more elaborate our requirements to control machines become, the bigger the circuits get. The obvious thing to do, considering how many circuits can be built on a chip, is to make a circuit which has a huge number of gates and shift registers, and use the same chip for all control circuits. You can just imagine what a monstrosity this would be, with several inputs for each gate, and an output, each needing a pin. To use such a chip, we would need to connect the correct pins together to get the logic circuit we wanted. If we then wanted to change what the circuit did, we would need to rewire the connections between the pins.

It's just not on, and the solution to the problem is the device we call the microprocessor CPU (or MPU) chip. It contains gates and registers, but the connections *between them* are also made by gates under the control of a code of one or two bytes. In addition, operations are carried out one at a time rather than altogether, so that we don't need a huge number of inputs and outputs. To ensure that it can cope with really complex problems, it operates on a byte of eight bits at a time. The whole system is timed and controlled by clock pulses from a clock generator, usually running at 1MHz or more, so that a lot of operations can be carried out every second.

What are the advantages? Well, one is that the same component can be put to an incredible variety

of uses. If we want to change the action, we don't have to lift a soldering iron or a pair of cutters, we simply change the program instructions. Working with a complete byte at a time lets it cope with a lot of signal information — if we need larger numbers we can spread it over 2 or more bytes. Incidentally, pocket calculators use only 4 bit units for working with numbers up to 9.9999999×10^{99} — working with large numbers just takes longer.

The sequence of operating means that we can have practically as many inputs and outputs as we


like, providing we don't expect them to be absolutely simultaneous.

The important points about the microprocessor therefore are how we connect it up to other devices (to pass signals in and out) and how we program it to carry out the sequences of operations we want. We'll start next month by looking at some of the chips which are needed to make the microprocessor work, and the first and most important of these is memory.

(To be continued)

SHORT WAVE NEWS

FOR DX LISTENERS

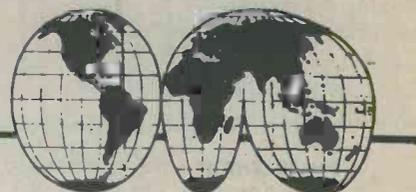

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

●NEWSCASTS FROM INDIA

All India Radio, Delhi, operate a News Broadcasts Service in their Domestic Services, these programmes being in English, English/Hindi or in Urdu. The newscasts last from 5 to 15 minutes at various time periods from 0030 through to 1740 on many differing channels. Reception of some of these broadcasts here in the U.K. would represent quite a feat of Dxing for beginners — 'chasing' these transmissions can provide quite a lot of 'fun and games' — try it and find out!

Listed here are the afternoon transmissions (correct at the time of writing) which are most likely to be heard here in the U.K..

From 1230 to 1240 in English/Hindi on 3235, 3355, 6120, 9575, 9590, 11620, 11735 and on 15430.

From 1430 to 1435 in English on 3255, 3925, 4860, 6145, 7135, 7195, 7280, 7412, 9950 and on 10335.

From 1530 to 1545 in English on 3235, 3255, 3315, 3355, 3925, 4860, 6145, 7135, 7195, 7280, 7415, 9950 and on 10335.

From 1730 to 1740 in English/Hindi on 3255, 3925, 4860, 6145, 7195, 7412 and on 9950.

AROUND THE DIAL

In which are listed some of the transmissions recently logged which we hope will be of interest to many readers.

●LIBYA

Tripoli on 11700 at 1120, OM with Arabic chants in the Domestic Service, scheduled here from 1000 (variable) to 1615. The Foreign Service operates here from 1700 to 2200.

●CLANDESTINE

"Radio Freedom from South Yemen" on a

measured 9953 at 1928, OM with songs in Arabic, local-type music. The schedule is from 1130 to 1430 and from 1630 to 2000 at the time of writing this article.

"Voice of the Malayan Revolution" on 15790 at 1520, childrens choir plus piano, YL with identification at the end of the English programme at 1530. Schedule of the English transmission is from 1450 to 1530 daily.

"Voice of Lebanon" on 6550 at 1932, OM with songs in Arabic, Arabic music. The schedule is from 1900 to 2105 in Arabic (English newscast at 1745).

●CHINA

Radio Peking on 9860 at 1940, YL with Chinese songs in the Portuguese programme to Europe and Africa, scheduled from 1900 to 2000.

Radio Peking on 9880 at 1945, OM with the English programme to North and West Africa, scheduled from 1930 to 2030.

Radio Peking on 9900 at 1900, chimes 'East is Red', identification in the Hausa programme to West Africa, scheduled here from 1900 to 1930.

Radio Peking on 9945 at 1530, YL with song in Chinese in the programme for Vietnam, scheduled from 1500 to 1600.

Radio Peking on 9965 at 1520, YL with song in Chinese in the Bengali programme, scheduled from 1500 to 1600.

●CHINA — REGIONAL

Nanning on 4905 at 2012, YL in Chinese with a relay of Peking 1. The schedule is from 2000 to 2200 (May to October from 2000 to 2300 and 1100 to 1735).

●TAIWAN

BCC Taipeh on 9765 at 1940, YL with the French programme for Europe, the Middle East

and Africa, scheduled from 1930 to 2020. Newscast until 1942 then YL with a song in Chinese.

●NORTH KOREA

Radio Pyongyang on **6600** at 2054, light music Euro-style, 4 low plus 1 high pitched 'pips' time-check at 2100 followed by identification and news in the Korean Domestic Service, also logged in parallel on **11350**. The schedule is from 2000 to 0830 and from 1500 to 1800.

●JAPAN

Tokyo on **9585** at 2104, OM with a newscast in English after station identification, schedule (in English and Japanese) is from 2100 to 2130.

●VATICAN

Vatican City on **9625** at 2001, YL with Rosary to Europe and Africa, scheduled here from 1945 to 2005 and also in parallel on **9645**.

●ISRAEL

Jerusalem on **9815** at 2018, OM with the English programme to Europe, the Middle East, North America and South West Africa, scheduled from 2000 to 2030.

●SEYCHELLES

Mahe (FEBA) on **11860** at 1750, OM with the Arabic programme to North East Africa and the Middle East, YL with identification in this Far East Broadcasting Association transmission scheduled from 1700 to 1800.

●MADAGASCAR

Radio Netherlands Relay on **11730** at 1835, OM with a newscast in the English programme for Africa, scheduled here from 1830 to 1920.

●GREECE

Athens on **11730** at 1546, YL with songs, typical Greek music in the Greek programme to North America, scheduled from 1500 to 1550.

●SPAIN

Madrid on **11840** at 2039, OM with news of local events — including maximum and minimum temperatures at many Spanish resorts — in the English programme for Europe, scheduled from 2030 to 2130.

Madrid on **11880** at 0550, YL with a newscast in the English programme to North America, scheduled from 0515 to 0615.

Madrid on **11920** at 1130, YL with identification and a newscast in the Spanish programme for Latin America, North Africa and the Middle East, scheduled from 1100 to 1235.

●ITALY

Rome on **11800** at 1940, YL with the local news in the English programme for the U.K., scheduled here from 1935 to 1955.

●FINLAND

Helsinki on **11755** at 1930, OM with news of the Nordic Countries in the English programme to Europe and Africa, scheduled from 1930 to 2000.

●KUWAIT

Radio Kuwait on **11990** at 1917, local-type music in the Arabic Domestic Service, scheduled here from 1830 to 2110.

●ROMANIA

Bucharest on **11720** at 0540, YL with the news in the English programme to Africa, scheduled from 0530 to 0600. Also logged in parallel on

11830.

Bucharest on **15335** at 0650, OM and YL alternate with news items in the English programme for the Pacific, scheduled from 0645 to 0715.

●BURUNDI

Bujumbura on **3300** at 1809, OM with the local news in French. This is the Home Service 1 in French and vernaculars, being scheduled here from 0330 to 0600 (Sundays through to 2100) and from 1500 to 2100 weekdays. The power is 25kW but the channel is anything but a good one!

●RWANDA

Kigali on **3330** at 1813, OM with a newscast in French in the Home Service, scheduled here from 0300 to 0600 (Sunday until 0900), 0900 to 1200 (Saturday and Sunday until 2100) and from 1330 to 2100. The power is 5kW.

●ANGOLA

Luanda (R.Nacional) on **3355** at 1919, OM and YL alternate with announcements in Portuguese. The schedule is from 1530 to 2400 and the power is 10kW.

●VENEZUELA

Radio Occidente, Tovar, on **3225** at 0220, religious service in Spanish, extended schedule — which is normally from 1030 to 0200. The power is 1kW.

Radio Universidad, Merida, on **3395** at 0230, OM with identification, jingles, LA music. The schedule is from 1000 to 0400 and the power is 1kW.

●COLOMBIA

Ecos del Combeima, Ibague, on **4875** at 0653, OM with identification as "Radio Super" followed by Sambas etc. The schedule is on a 24-hour basis and the power is 5kW.

Radio Cinco, Villavicencio on **5040** at 0659, OM with a lullaby in Spanish, OM with identification at 0701. The schedule is around the clock and the power is 3kW.

Emisora Nuevo Mundo, Bogata, on **4755** at 0500, OM with full identification followed by a newscast in Spanish. The schedule is around the clock and the power is 1kW.

Ondas del Meta, Villavicencio, on **4885** at 0453, OM with commercials, identification and Sambas etc. The schedule is from 0900 to 0500 and the power is 1kW.

●ECUADOR


Radio Popular, Cuenca, on a measured **4801** at 0507, OM with identification as "Radio Popular" (sometimes identifies as "Radio Amiga Popular de Cuenca"). The schedule is around the clock and the power is 2kW. This one is best received after Radio Lara, Barquisimeto, Venezuela, on **4800** closes at 0400.

Radio Splendit, Cuenca, on **5025** at 0242, OM with a love song in Spanish, OM with announcements and identification at 0245. The schedule of this one is from 0900 to 0500 (variable 0430-0530) and sometimes around the clock. The power is 5kW.

●BRAZIL

Radio Aparecida, Aparicida, on **5035** at 0249, OM with announcements in Portuguese, local-style dance music. The schedule is from 0900 to 0300 and the power is 1kW.

BEGINNER'S MEDIUM

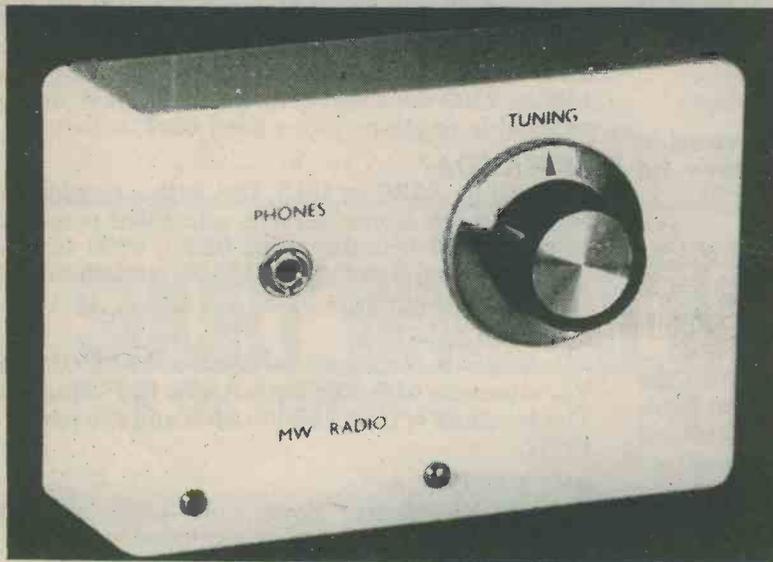

The receiver has only one control, this being for tuning. It switches on automatically when the crystal earpiece plug is inserted in the jack socket

By

I. M. Attrill

This simple receiver is easy to construct and uses readily available components. It is a t.r.f. (tuned radio frequency) design having a single transistor regenerative detector followed by a high gain i.c. audio amplifier stage, and the completed set requires no alignment. The radio is powered by an internal 9 volt battery of PP3 size, which provides many hours of use as the current consumption is only about 3mA. A ferrite rod aerial is employed and gives sufficient sensitivity to receive the local BBC medium wave stations as well as Luxembourg and a few other Continental signals during the hours of darkness. The output is suitable for a crystal earpiece. Magnetic phones or a magnetic earpiece cannot be used.

CIRCUIT DIAGRAM

The full circuit of the "Beginner's Medium Wave Radio" appears in Fig. 1. L1 is the tuned winding of the ferrite aerial, and it can be tuned over slightly more than the medium wave band by means of variable capacitor VC1. The low impedance coupling winding, L2, passes the signal picked up by the tuned winding to the base of the high gain common emitter amplifier, TR1, via C2. R2 provides base bias.

The r.f. collector load for TR1 is R4, which couples to the positive rail via R3 with C3 acting as a bypass capacitor at radio frequencies. TR1 offers greater gain to positive signal half-cycles than it does to negative half-cycles because the positive half-cycles cause it to draw a higher collector current. The result is that the average collector current of TR1 varies with the amplitude of the received signal. Since that amplitude itself varies with the modulating broadcast a.f. signal, it follows that the a.f. modulation is recovered at TR1 collector. The r.f. carrier is present also at TR1 collector

and is prevented from passing further by the filter consisting of R4 and C3. This capacitor has a relatively high reactance at audio frequencies, whereupon a proportion of the recovered a.f. at TR1 collector is passed to the receiver a.f. amplifier via C4.

The collector of TR1 is coupled back to the ferrite aerial tuned circuit by way of R1, the connection being phased so as to give positive feedback. This regeneration considerably improves the sensitivity of the receiver, since it increases the efficiency of TR1 as a detector by enhancing its ability to give increased gain on positive half-cycles. The feedback also improves the selectivity of the set, enabling it to pick out just one of several closely spaced transmissions.

The a.f. output from the detector is still not very great, being typically in the region of 1 millivolt. A large amount of audio amplification must therefore be used to bring the signal up to a sufficiently high level for the crystal earpiece. This amplification is provided by IC1, which is an operational amplifier used in the inverting mode. The non-inverting input (marked with a plus sign) is biased to half the supply voltage by the equal value resistors, R6 and R7. R8 causes the inverting input (marked with the minus sign) to take up the same potential as the non-inverting input and also, with R5, provides a negative feedback network. The two resistors limit the gain of IC1 to a level which is approximately equal to the value of R8 divided by the value of R5. The consequent a.f. gain is 1,000 times, and this high level of amplification ensures that a good volume level is obtained from any signal of reasonable strength.

The earpiece is driven direct from the output of IC1, and as it is a crystal type there is no need for an output d.c. blocking capacitor. The earphone

WAVE. RADIO

A PROJECT WITH PARTICULAR APPEAL FOR THE NEWCOMER.

COMPONENTS

Resistors

(All $\frac{1}{4}$ watt 5% unless otherwise stated)

R1 680k Ω (see text)

R2 2.2M Ω 10%

R3 3.3k Ω

R4 1.2k Ω

R5 10k Ω

R6 22k Ω

R7 22k Ω

R8 10M Ω 10%

Capacitors

C1 100 μ F electrolytic, 10V Wkg.

C2 0.1 μ F type C280

C3 0.047 μ F type C280

C4 0.22 μ F type C280

VC1 300pF variable, "Dilecon" (Jackson)

Inductors

L1, L2 medium wave aerial coil type
MWC2 (see text)

Semiconductors

TR1 BC109C

IC1 CA3140E (8-pin d.i.l.)

Socket

JK1 3.5mm. jack socket (see text)

Miscellaneous

Plastic case (see text)

Veroboard, 0.1in. matrix

Ferrite rod, 9.5mm. diameter (see text)

2 ferrite rod mounting clips (see text)

9-volt battery type PP3

Battery connector

Control knob

Crystal earpiece with 3.5mm. jack plug

8-way d.i.l. i.c. holder (see text)

Wire, solder, etc.


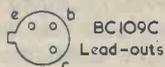
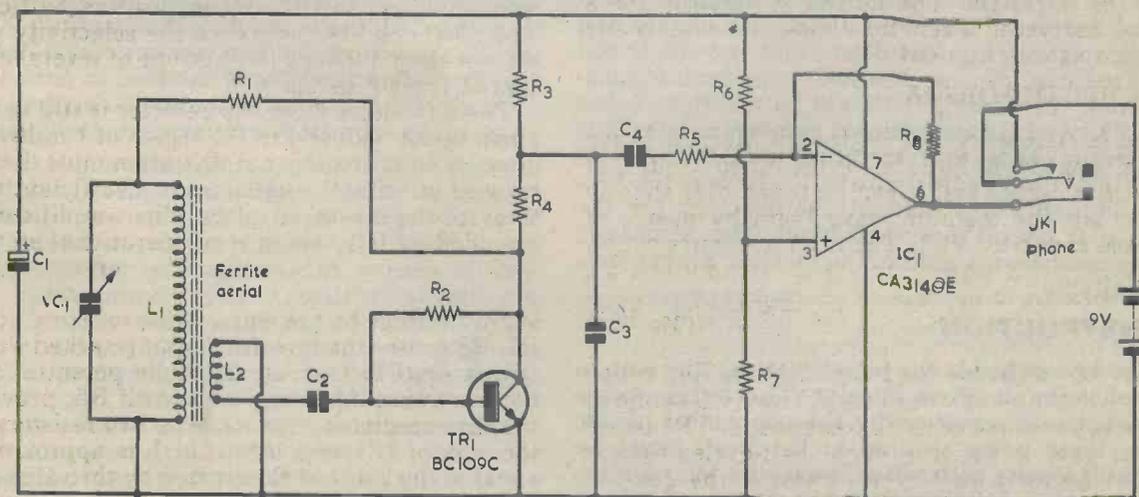


Fig. 1. The circuit of the Beginner's Medium Wave Radio. This drives a crystal earpiece

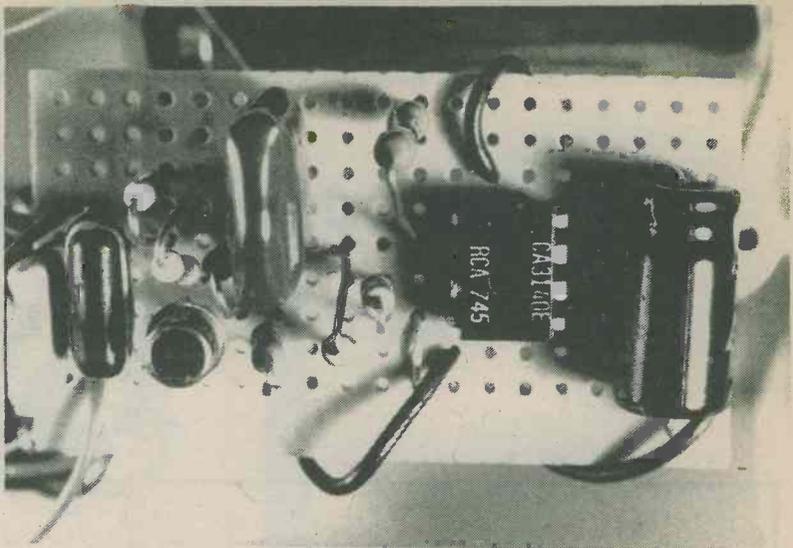The parts which are assembled on the Veroboard component panel. If desired, an i.c. holder may be employed for the CA3140E



jack socket has a "make" contact which automatically switches the set on when the earphone is plugged in, and switches it off again when the plug is removed. There is in consequence no need for an on-off switch.

COMPONENTS

The receiver is housed in a plastic box type PB1, having dimensions of 114 by 76 by 38mm., which is available from Maplin Electronic Supplies. A metal case cannot be used because this would screen the ferrite rod and prevent the reception of signals. It is necessary, also, for VC1 and the phone jack socket to be mounted on an insulated panel because the modification to the phone jack results in its mounting bush having a different potential to that at the mounting bush of VC1. The phone jack should be a type having an "open" construction, i.e. it should not have an insulated body.

The ferrite aerial coil and the CA3140E used for IC1 are both available from Ambit International, who can also supply the two plastic clips which hold the ferrite rod in place. As is described shortly, the ferrite rod will in most instances have to be a longer rod which is cut down, and the longer rod required can also be obtained from Ambit International. (In passing it should be mentioned that the 1978 Ambit International catalogue states that the ferrite aerial coil specified is "not suited to bipolar discrete inputs." However, its characteristics are perfectly satisfactory for the particular circuit described here). The remainder of the components used in the receiver are generally available.

CONSTRUCTION

The layout inside the plastic case can be seen in the photograph of its interior. The ferrite rod is mounted at the bottom by the two Ambit plastic clips, these being secured to the front panel by short 6BA bolts with nuts. The ferrite rod requires a diameter of 9.5mm. and a length of about 100mm., and it is probable that difficulty will be experienced in obtaining a rod of this length. Because of this it may be necessary to obtain the length from a longer rod. The procedure here is to file a fairly deep V-shaped groove all round the rod at the point where it is to be broken and to then

lightly tap the required length of the rod against the edge of a wooden table or bench. It does not matter if there is a rough finish to the rod at the point of the break. Rods with lengths of 140, 160 and 175mm. can be obtained from Ambit International. Since it is not easy to shorten a rod which is only slightly over the required final length, it would be preferable to start off with the 160mm. or 175mm. rod.

The variable tuning capacitor is mounted on the right hand side of the front panel, as viewed from the front, and this requires a mounting hole of 10mm. diameter. The jack socket is fitted to the left of the tuning capacitor and requires a hole with a diameter of about 6.5mm.

The jack socket will normally have contacts which break a circuit when the plug is inserted, these usually being employed to mute a speaker when an earphone is connected. The appearance of the contacts is as shown in Fig. 2(a). It is merely necessary to carefully bend back the thicker fixed contact and then bend it downwards so that it is below the springy moving contact. The fixed contact should be finally positioned so that, without a plug inserted, the moving contact does not touch it. At the same time the two contacts should connect together when the plug is inserted in the socket.

Apart from the battery and its connector, the remaining components are assembled on a

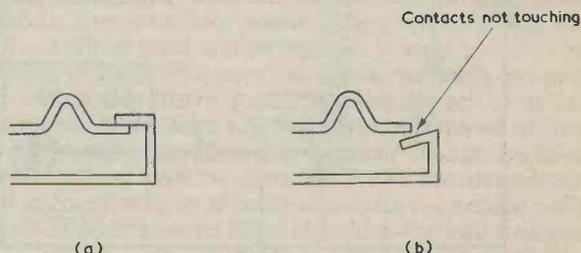


Fig. 2(a). The rear ends of the contacts of the jack socket before modification
(b). One of the contacts is bent so that the two contacts only make when the jack plug is inserted

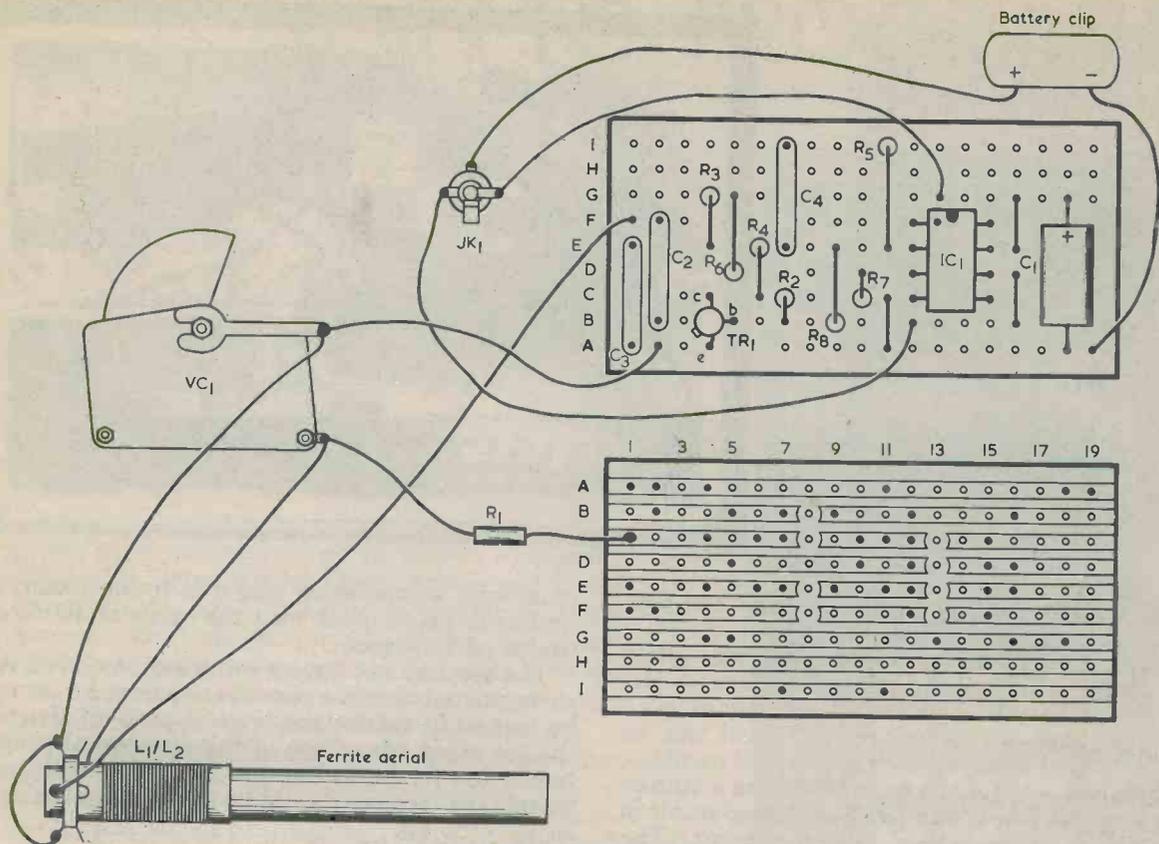


Fig. 3. Component layout on the Veroboard panel and the general wiring of the receiver

Veroboard of 0.1in. matrix having 19 holes by 9 copper strips. Details of this panel are given in Fig. 3, which also illustrates all the point-to-point wiring of the receiver.

Start by cutting out the Veroboard to the correct size using a hacksaw, and then make the eight breaks in the copper strips. The breaks can be made with a Vero spot face cutter or a small twist drill held in the hand. The three link wires and the components should then be soldered to the board at the positions indicated in Fig. 3.

IC1 should be the last component to be soldered to the board. This device has a PMOS input stage and it can be damaged by high static voltages if these should appear at the inputs. The i.c. will almost certainly be supplied with its pins imbedded in a piece of metal foil or conductive foam, and it should not be removed from this until it is time for it to be connected into circuit. All soldering should be carried out with an iron having a reliably earthed bit. Chances of accidental damage are much reduced if an 8-pin i.c. holder is employed. This holder is soldered to the board in place of the i.c., and the latter is then inserted in the holder at a late stage of the construction.

The point-to-point wiring is next carried out, and it should be noted that one lead of R1 is soldered to strip "C" on the copper side of the board. Its other lead connects to the fixed vanes tag of VC1, as shown. The leads to the jack socket, to VC1 and to the aerial coil employ single strand p.v.c. covered wire, and they should be kept short and direct. It

will then be found that they are sufficient to hold the component board in position, making any further mounting unnecessary. The board fits into the space between the jack socket and the ferrite aerial, with the component side towards the aerial and C3 nearest VC1. Its position is clearly shown in the photograph of the inside of the receiver case. The battery is fitted above the phone jack and may be held in place by means of Bostik Blue Tack.

If any difficulty is experienced in identifying the tags of L1 and L2, this should be cleared up by visually inspecting the coil and comparing it with the circuit diagram of Fig. 1. It should then be apparent which two tags connect to the negative supply rail and which connect to VC1 and C2.


ADJUSTMENT

Provided that the aerial coil is positioned right at the end of the ferrite rod the set should work correctly without any alignment. If it does not, switch off at once and check the wiring thoroughly for errors.

It is just possible that the regeneration provided by R1 is too great, causing the detector to oscillate and resulting in a whistle of varying pitch as the set is tuned across a station. This is unlikely but, should it occur, the trouble can be cured by experimentally increasing the value of R1 until satisfactory results are obtained.

It is more likely that the level of regeneration will be below optimum, but this will not prevent the

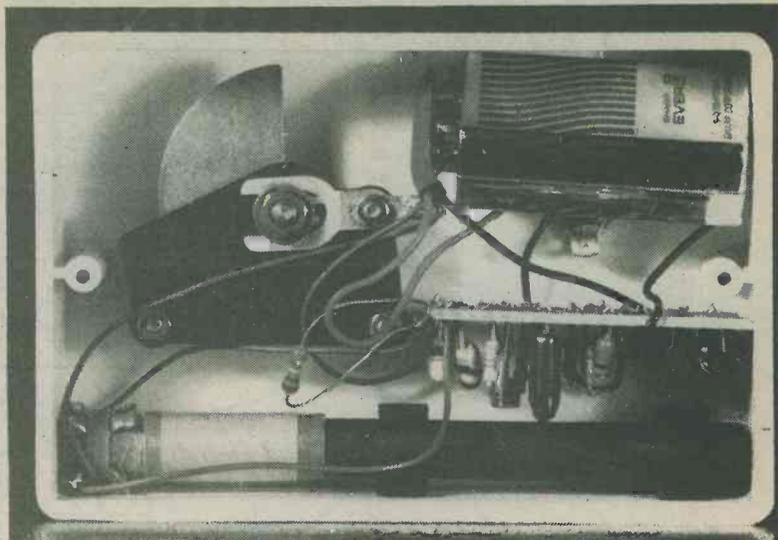The internal layout inside the receiver case. The ferrite rod is secured by two plastic clips, one slightly left of its centre, as shown here, and one near its right-hand end



receiver from exhibiting good selectivity and sensitivity.

Experimentally minded constructors can, if they wish, try the effect of reducing the value of R1, whereupon it may be found that reception of weak signals is improved. However, R1 must not be made too low in value or the detector will oscillate, producing the whistle of varying pitch as a station is tuned in. Too low a value in R1 can also result in the receiver giving a low quality output. The prototype receiver gives good results with less than

maximum regeneration and it is by no means essential to experiment with the value of R1 to optimise performance.

The set does not have a volume control. If a very strong signal should cause overloading the set may be turned to reduce the level of pick-up. Turning the set takes advantage of the directional properties of the ferrite rod aerial. Similarly, with weak signals the receiver should be oriented for strongest signal pick-up.

AN ENTREE TO SOLDERLESS BREAD BOARDING

For those interested in getting their feet wet in solderless breadboarding without wringing their wallets dry, Continental Specialties Corporation recommends their model PB-6 Proto-Board® Kit, low cost (£9.20) way of quickly learning and appreciating the advantages of

the solderless breadboarding approach.


The PB-6 Proto-Board Kit comes complete with a pre-assembled breadboarding socket, two pre-assembled solderless bus strips, four five-way binding posts, a metal ground base plate, non-marring feet

and all required hardware. When complete, its six hundred and thirty tie points permit flexible configurations of as many as six 14-pin DIP ICs.

Despite its low cost, the PB-6 provides a very confident breadboarding base. Of the four binding posts, one is grounded to the ground base plate permitting high distributed capacitance and low distributed inductance for enhanced high-speed circuit operation. The three remaining five-way binding posts can be used to interconnect the circuit on the PB-6 to power and signal lines and the outside world.

Following the easy assembly instructions enclosed, using only pliers and a screwdriver, assembly time for the PB-6 is less than ten minutes.

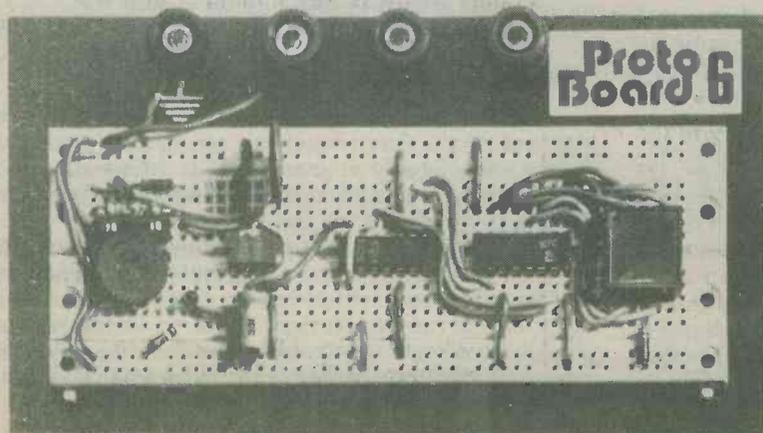For further information, contact Continental Specialties Corporation (U.K.) Ltd., Shire Hill Industrial Estate, Saffron Walden, Essex.



TUNE-IN TO PROGRAMS

PART 7

By
Ian Sinclair

BUG HUNTING

We've all done it — we've written a program, checked it, entered it into the machine and all we get when we run it is a flashing display or a silly answer. Obviously something's wrong, but what? There are several things we can do, some with the calculator, some without, to debug a program, but before we start we should check the following:

1. Is each store loaded up with the numbers that are to be used in the calculation?

2. Is each [STO], [RCL], [GTO], [Lbl] or [SBR] instruction followed by the correct reference number?

3. Have we used an [=] or [()] to complete calculations where these are needed? Some operations, like [1/x], do not need [=], others, like [+], [-], [X], [÷], do. If in doubt, check out a sum with the calculator used simply as a calculator (not running a program).

PROGRAM CHECK

A particularly good way to check a program before running it on the calculator is to imagine yourself as the calculator, writing down the effect of each instruction and acting on the number you have written down with the next instruction. This way, if we do only what the program dictates, we can often spot omitted [=] or other signs which make a calculation impossible or incorrect.

If the program seems perfectly correct (and if it has run before then it must be correct), the next step is to check that this is the program that is actually entered. We may quite easily have missed a step or even added one which was not intended. How, then, do we trace through a program?

The answer is that the TI-57, along with the PR-100, has editing facilities, enabling us to look at each step of a program which is in store. To make use of these facilities load up the memories as required by the program, set up just as you would for running the program, press [RST] so that the program is reset to the beginning, and then press the [LRN] key.

The display then splits off, as in Fig. 1, to show the program step number on the left, along with the code number for the program instruction on the right. Remember your step codings? The code is a



The keyboard of the Texas Instruments TI-57 programmable calculator. Most keys have a second function, whereupon facilities are nearly double the number of keys provided.

two-digit number in which the first digit represents the key row, starting at the display end of the calculator. The second digit represents the key column, starting at the left hand side with number 1, and moving from left to right along the normal functions (the ones printed on the keys) then back again at No. 6 to number the upper functions (marked above the keys and again from left to right). Examples of these key codings are shown in Fig. 2. Any number in addition to the two-digit key code is a reference number such as a memory number, a label number, etc.

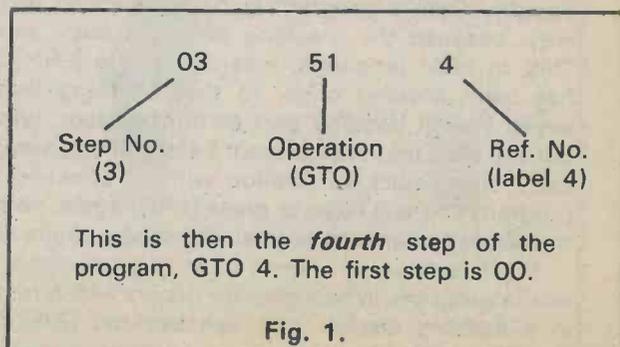


Fig. 1.

[INV] always codes as [-] before the operation code, so that [INV] [SBR] is [-61], [INV] [sin] (or arcsin) is [-28], and so on. Numbers are not coded, but entered normally.

Operation	Code	Operation	Code
Pause	36	y^x	35
GTO	51	sin	28
Dsz	56	cos	29
SBR	61	tan	20
x=t	66	(43
RST	71)	44
R/S	81	÷	45
Lbl	86	X	55
STO	32	-	65
RCL	33	+	75
SUM	34	=	85
x^2	23	+/-	84
\sqrt{x}	24	log	18
1/x	25	antilog	-18

Fig. 2. SOME IMPORTANT KEY CODINGS

In this condition, we can check the program step by step, using the [SST] key. Pressing the [SST] key advances the program by one step, showing the step number and the code for the operation that will be carried out. The [BST] key has a similar effect, but runs the program one step back on each press. Take great care not to press any other key unintentionally while a program is being checked in this way, because the machine is in the *learn* mode. This, in plain language, means that the [LRN] key has been pressed once, so that anything that is keyed in will become part of the program, wiping out the step that was present before. If you want to carry out a quick calculation without affecting the program you will have to press [LRN] again, so that the display returns to normal, showing a single zero.

You may not, of course, have to go through the whole program. When an error occurs which results in a flashing display, you can use the [R/S] and [CLR] (or [CE]) keys to freeze everything, then press

[LRN]. That should get you to the place where things started to go ape, so you can backstep using [BST] until you find what went wrong. Another possibility is that you may have a hunch that the root of the trouble is around step 25. You can get there by the key sequence [GTO] [2nd] [25] [LRN], which will result in the machine showing step 25. Once there, you can [SST] and [BST] your way around until you find the trouble. Note, by the way, that this [GTO] method needs a two-digit number. If, for example, you are looking for step 7 and you press [GTO] [2nd] [7], the machine will look for *label* 7. To get program step 7, you must key in [GTO] [2nd] [07] — the use of two digits makes a great difference.

You still can't see where it's gone wrong? There's still hope for you because we can also check what the calculator does to each number. Enter in a nice easy set of numbers, like 1, 2, 3, into the memories that are to be used. Calculate what the result of each step should be. Now load up the program in the usual way, press [RST] when the machine is out of program mode (after the second press of [LRN]) and, instead of pressing [R/S], press [SST]. What will be displayed this time will be the result of the first step of the program. For example, if the program starts with [RCL] [1], and memory 1 is loaded with the number 1, then pressing [SST] at the start of this program will bring a 1 into the display. The next press of the [SST] key carries out the next instruction. If the next step is [+], [-], [X] or [÷], the display does not change. Instructions like [1/x], [\sqrt{x}] or [x^2] will cause the results of such steps to be displayed. This way, we can [SST] our way through the program looking at the results. Note that [BST] does not work in this mode. The results should agree with the old-fashioned arithmetic which you tried earlier. If it doesn't agree somewhere, you've found the fault.

EDITING

Both the TI-57 and the PR-100 allow a number of editing operations to be carried out on programs which are in store. These operations are insertion, replacement and deletion. Of these, the easiest edit is to write over a program step. You may find, for example, that your written program says [5] [SUM] [2], and the program in the calculator is displayed as 25 32 2, meaning that this is step 25 and that the key strokes programmed were [STO] [2] (since 32 is the code for [STO]). Note that the PR-100 shows these as separate steps since merged codes are not used.

While the calculator is in the [LRN] mode, this incorrect program step can be written over simply by keying in [SUM] [2] in place of the [STO] [2] which was there. Once this is done, the display will show the next step of the program, so that we have to use the [BST] key to go one step back to check that the program is now as we want it.

Another editing step which is sometimes useful is the [Nop] step (obtained by pressing [2nd] [BST]). When the program is being checked in the [LRN] mode, any step can be erased by using [Nop] (No-

Program Example

```
LRN RCL 1 SBR 0 1/x
X ( RCL 2 SBR 0 ) X
RCL 0 = R/S
Lbl 0 X RCL 3 + 1
= INV SBR LRN
```

Program Listing Using SST Key

Press LRN to start, then SST:

00	33	1	11	81	
01	61	0	12	86	0
02	25		13	55	
03	55		14	33	3
04	43		15	75	
05	33	2	16	01	
06	61	0	17	85	
07	44		18	-61	
08	55		19	00	this indicates
09	33	0			the end of the program.
10	85				

Load in the following values: 150 STO 0, 22 STO 1, 125 STO 2, 0.0036 STO 3. With the program loaded and the machine out of LRN mode, the use of SST will now run the program one step at a time, as follows:

22.	1.
22.	1.3435878
22.	1.3435878
0.0036	1.3435878
0.0792	1.3435878
1.	150.
1.0792	201.53818
1.0792	201.53818
0.9266123	201.53818
0.9266123	201.53818
0.9266123	0.0036
125.	0.7255374
125.	1.
125.	1.7255374
0.0036	1.7255374 End
0.45	0 of program.

Fig. 3. USING THE SST KEY

operation), leaving a space which will be skipped when the program runs. A No-operation space can be filled with another instruction later if one is needed.

A very useful editing step is the [Ins], meaning Insert, key, reached by [2nd] [STO]. Using this key shifts all the program steps, leaving a space into which another step can be placed. To use the [Ins]

step, locate the step in the program *after* which you want to add another instruction, then press [Ins]. There is a short delay as all the registers shift the program down, then the display shows a set of zeros after the step number. The new step can then be keyed in. If there's another new step to add, the [Ins] key must be pressed again. Once again, the calculator must be in the [LRN] mode before these operations can be carried out. A point to watch when steps are inserted is the overall length of the program — if the program filled up the calculator previously, using the [Ins] key will cause the last step of the program to be lost.

The final key of the editing set in the TI-57 is the [Del] (Delete) key, obtained by pressing [2nd] [EE]. Pressing this key when the calculator is in the [LRN] mode removes the step which is being displayed, and closes up the gap.

DEBUGGING SUMMARY


1. When a program is first entered by pressing [LRN] and programming, the key codes are *not* displayed.

2. To check key codes, the program must be entered and the machine kept in [LRN] mode. Alternatively, the [LRN] key must be pressed to enter [LRN] mode if the program has been run. The [RST] key must have been used out of [LRN] mode to reset the program, and then the [SST] key can be used to examine the program step by step. The [BST] key also operates in [LRN] mode to backstep the program.

3. The [SST] key works out of [LRN] mode also. Out of [LRN] mode, the [SST] key will run a program step by step, showing the result of each step on the display.

4. The edit keys, [Nop], [Ins] and [Del] can be used in [LRN] mode only.

(To be continued)

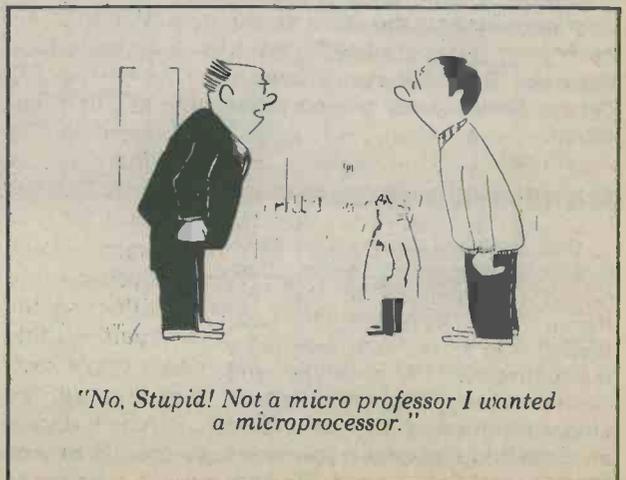

In your workshop -shop

PROBLEMS WITH SYNC

"Our darned bog-roll has gone out of sync again!"

Dick shut the Workshop door behind him noisily and stumped, scowling, over to his bench.

Smithy looked up at him.

"How d'you mean, out of sync?"

"There's something wrong with the perforations," replied Dick aggrievedly. "The perforations in the top layer are displaced by about two inches from the perforations in the bottom layer."

"I can't begin to understand what you get up to out there," remonstrated Smithy mildly. "The bog-roll always seems to be all right for me."

Dick suddenly cast a suspicious glance at the Serviceman.

"Here," he asked, "you haven't been getting in some sub-standard rolls on the cheap, have you?"

"Certainly not," retorted Smithy in a deeply shocked tone. "I would never even dream of skimping on an important item like that. I always get the finest quality two-ply toilet tissue."

"Humph!"

MORE SYNC TROUBLE

Dick slouched down on his stool, looked at his empty bench, then turned his attention to the "For Repair" rack. Resignedly he rose, walked over to the rack, selected a monochrome TV receiver and carried it back to his bench. He next plugged it into the mains, connected an aerial and switched it on. As the sound signal from one of the local

channels became audible from the speaker, he waited for the picture tube to warm up.

The screen flickered into life, to reveal a picture which was completely out of horizontal lock. Dick turned the set round and located the horizontal hold control. Looking at the screen he adjusted the control carefully. He was able to find a critical setting which caused the picture to be momentarily resolved, but it very soon went out of horizontal lock again.

"Just my luck," he grumbled to himself. "I've got another problem with sync now."

Smithy, carrying a serviced

cassette recorder over to the "Repaired" rack, turned round at the sound of his assistant's voice.

"Don't tell me," he said irately, "that you're *still* chuntering on about that sync business."

"It's this TV," stated Dick. "There's not a trace of horizontal sync in it at all."

"Let's have a look."

Smithy walked to Dick's side and, in his turn, experimentally turned the line hold control. He was similarly able to obtain a momentarily resolved picture, which soon fell out of lock once more.

"There's almost certainly a snag in the line flywheel sync circuit," he

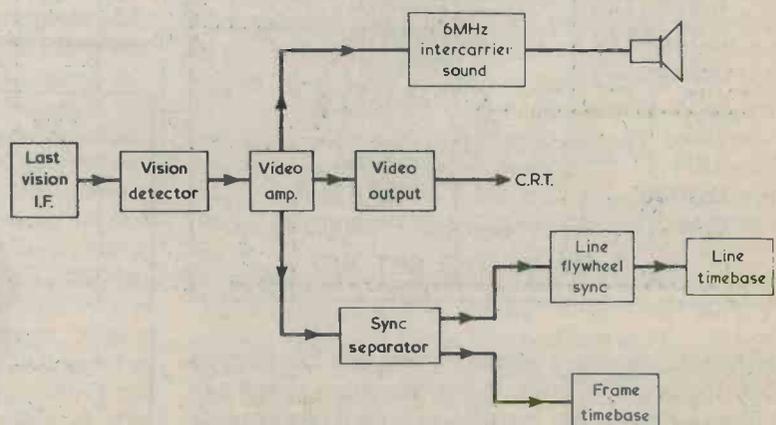


Fig. 1. Typical stage line-up for a monochrome television receiver following the last vision i.f. amplifier. The sync separator provides sync pulses which are applied to the line flywheel sync circuit

pronounced, as he switched off the set. "We're getting a picture and we can hear the intercarrier sound. So there must be a signal getting through all the way to the video output stage. Also, we're getting frame hold, which means that the sync separator circuits are at least passing frame sync pulses to the vertical timebase. Since we're able to get the line timebase on to the correct frequency, even if only momentarily, that timebase can be assumed to be all right. All that's left is the horizontal flywheel sync circuit." (Fig. 1).

"How d'you know that this set has got a flywheel sync circuit? Couldn't it have direct line sync, in which the line sync pulses trigger the horizontal timebase oscillator?" (Fig. 2).

"Direct line sync went out of use ages ago," replied Smithy. "You might come across it in some extremely old valve TV sets, but you certainly won't find it in any solid-state sets like the one you've got there. Apart from some of the most recent sets, which have got the line oscillator and sync stages packed away inside an integrated circuit, line flywheel sync arrangements have become standardised with

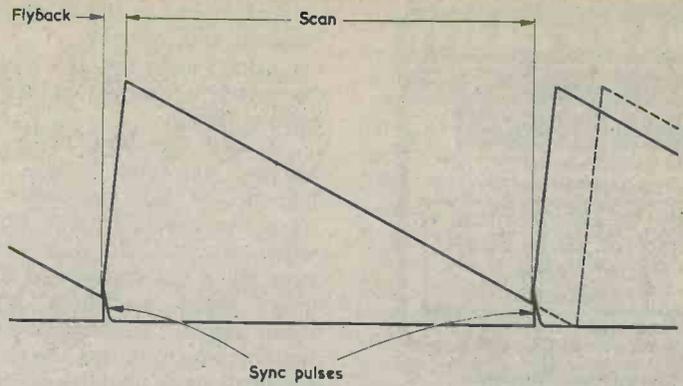


Fig. 2. Graphical presentation illustrating the action of a direct line sync system. The waveform represents a signal in the line timebase oscillator, and the sync pulse initiates the start of the flyback period before it would naturally occur. If the sync pulse were absent the waveform would continue as shown in broken line

time as an inexpensive and reliable circuit which uses two silicon diodes connected in series. These two diodes are caused to become conductive when the transmitted line sync pulses are passed to them. Let's get out the service manual for this set and I'll show you."

Quickly forgetting his complaints about the Workshop's ultra-mural

facilities, Dick rose with alacrity and made his way to the filing cabinet. He soon found the appropriate service manual and brought it back to his bench opening it out at its circuit diagram.

"There you are," said Smithy, pointing to a section of the circuit. "There are the two flywheel sync diodes." (Fig. 3).

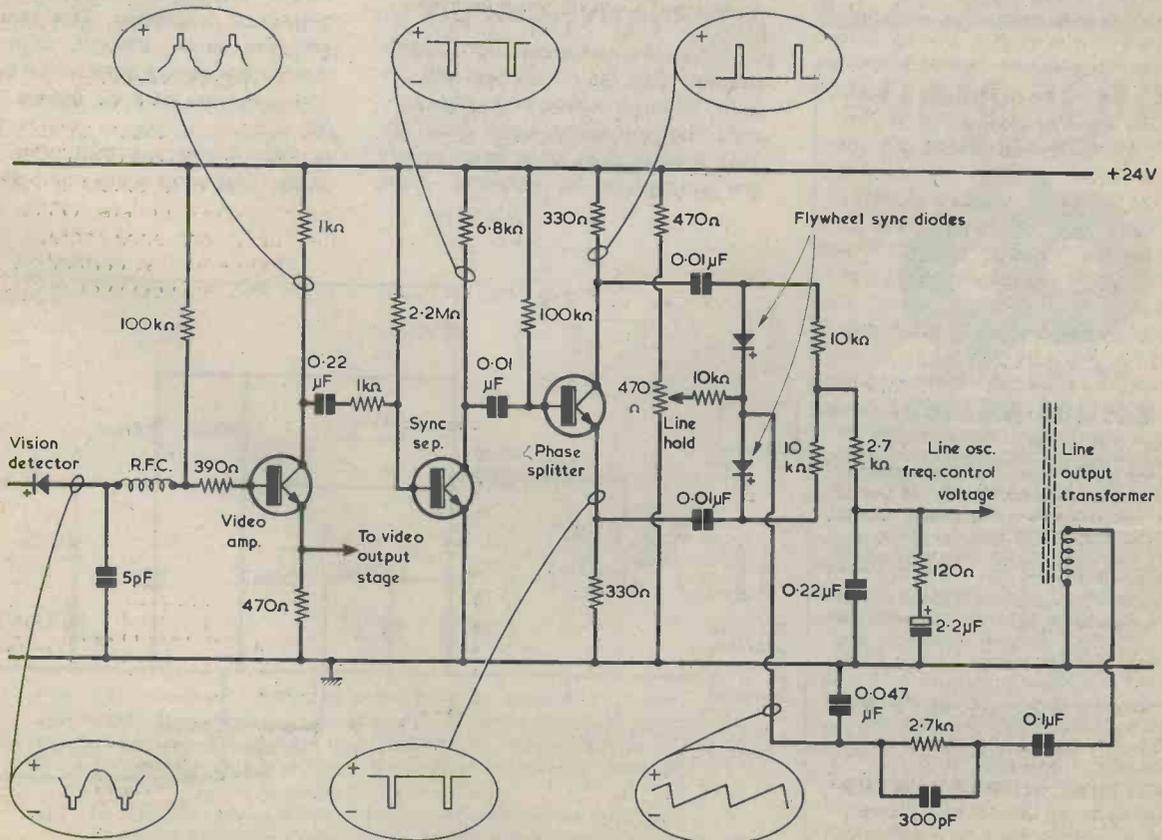


Fig. 3. Slightly simplified circuit representative of monochrome TV practice illustrating how the line sync pulses are fed to the two flywheel sync diodes to turn them on in the presence of the pulses. The components between the line output transformer winding and the sync diodes provide waveform shaping

ing the diodes conductive during sync pulses anyway?"

"When the diodes conduct," said Smithy in reply, "they pass a voltage derived from a winding on the line output transformer to the line timebase oscillator via a sort of smoothing circuit. The smoothed voltage controls the frequency of the line oscillator, which is usually of the blocking oscillator variety. This control voltage normally couples via a series resistor to the base of the blocking oscillator and it then varies the time between one flywheel period and the next."

"I don't quite get that."

"Well," said Smithy, "a blocking oscillator normally has positive feedback given by way of a transformer with a small soft iron core or iron-dust core in it. During

the scan period of the oscillation cycle, the collector or emitter current in one of the windings on the transformer continually increases until the core becomes saturated. The line oscillator then goes into the quick flyback part of the cycle, after which it starts the next scan period. As you can guess, the instant at which core saturation takes place will occur earlier if the control voltage applied to the oscillator base goes more positive. Got it?"

"Yes I have, now. What's this voltage which is derived from the line output transformer?"

"It's a voltage with a waveform like this," replied Smithy.

He took a ball-point pen from his pocket and sketched out the waveform in the margin of the service manual. (Fig. 5(a)).

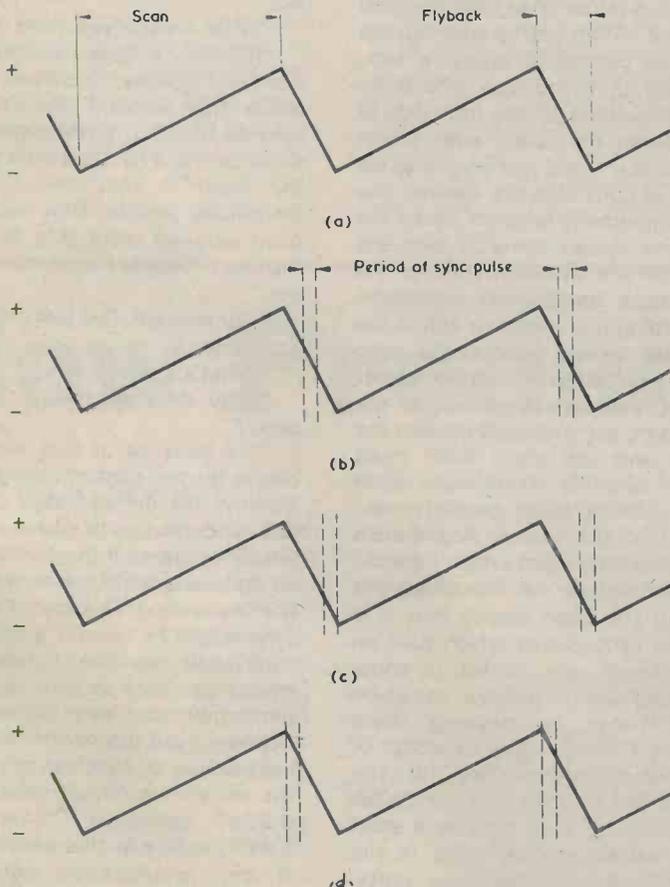


Fig. 5(a). Idealised version of the waveform applied from the line output transformer winding of Fig. 3 to the flywheel sync diodes. (In some receivers the polarity of the waveform is reversed if the line oscillator frequency decreases with a positive-going control voltage)
 (b). The situation given when the sync pulse coincides with the centre of the flyback period of the waveform
 (c). Condition given when the line oscillator tends to run at too high a frequency
 (d). The sync pulse coincides with an early part of the flyback period if the line oscillator attempts to run too slow

"As you can see," he continued, "it has a slowly rising section during the scan period of the waveform and a sharply falling section during the flyback period. What the flywheel sync diodes do is to turn on during the flyback period and pass the voltage present on the waveform at that instant to the smoothing circuit which produces the control voltage for the line oscillator. Now, let's say for argument's sake that the desired line oscillator running conditions are given when the sync pulses coincide with the centre of the flyback period. They will then cause a voltage to be passed to the control voltage smoothing circuit which is just right to keep the line oscillator running in the desired manner."

Smithy added several broken vertical lines to his waveform to indicate the voltage sampling process. (Fig. 5(b)).

"What happens," asked Dick, "if something causes the line oscillator to try to run at a higher frequency?"

"In that case," stated Smithy, "the flyback periods will be produced earlier than they should be, and the turning on of the flywheel sync diodes will coincide with a later part of the flyback section. This will cause the control voltage, after smoothing, to go negative and counteract the tendency of the line oscillator to run at too high a frequency."

Smithy pointed his pen at the appropriate parts of the waveform. (fig. 5(c)).

"This is all making sense now," said Dick thoughtfully. "I suppose that, if the line oscillator tries to run at too low a frequency, the flywheel sync diodes turn on at an early part of the flyback period, causing the voltage applied to the control voltage smoothing circuit to go positive." (Fig. 5(d)).

"That's exactly right," concurred Smithy. "The flywheel sync circuit keeps the line oscillator running at correct frequency provided that the transmitted sync pulses coincide with any part of the flyback period in the line output transformer waveform. In the set we have here the d.c. conditions in the flywheel sync circuit can be varied by adjusting the slider of a 470Ω potentiometer, whereupon this potentiometer acts as the line hold control. It is adjusted to bring the whole circuit into the correct operating state for control to take place. In some sets the d.c. conditions are fixed and the line frequency is controlled by adjusting the position of the core in the line blocking os-

THE
MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country

**19-21 PRAED STREET
LONDON W2 1NP
Tel: 01-402 9176**

**MORSE
IMPROVEMENT**

C90 Cassettes (A) 1-12 w.p.m. with simple exercises. Suitable for R.A.E. preparation. (B) 12-24 w.p.m. computer produced professional level operator material including international symbols.

Price each: complete with instruction and exercise booklets £4.50 including postage. Morse Key and Buzzer Unit suitable for sending practice and DIY tape preparation.

Price £4.50 including postage.
Overseas Airmail £1 extra.

**MHEL ELECTRONICS (Dept. R)
12 Longshore Way, Milton,
Portsmouth (UK), PO4 8LS**

GAREX

V.H.F. Receivers SR-9 for 2-metres F.M., fully tunable 144-146MHz, 2-speed slow-motion dial, also 11 xtal controlled channels. Compact, sensitive, ideal for fixed or mobile listening. Built-in L.S., 12v D.C. operation £57.35 inc. VAT. Crystals, if required: £2.50 each. All popular 2m. channels in stock. Marine band version (156-162MHz) £57.35 (xtals £2.79). Mains psu for above £11.25. Credit terms available, s.a.e. details.

Amplified Mobile Extn. Speaker boosts audio from small receivers. Single compact unit. 12vDC built-in 6W amplifier, with leads and jack plug, 4-8 Ω input £11.25.

Amplifier only from above £2.70.
Neons min wire end 55p/10; £4/100

Slide switches min DPDT 18p ea; 5+: 14p
Resistor Kits E12 series, 22 Ω to 1M Ω

57 values. 5% carbon film, $\frac{1}{2}W$ or $\frac{1}{4}W$ Starter pack, 5 each value (285) £2.95

Mixed pack, 5 each $\frac{1}{2}W$ + $\frac{1}{4}W$ (570) £5.40
Standard pack, 10 each (570) £5.40

Giant pack, 25 each (1,425) £13.25
I.C.'s (new) 7410 25p CD4001AE 25p

SN76660 75p NE555 55p 723(TO5) 75p 709 (TO5). 741 (DIL-8) Op.amps 30p;

BNC Cable mtg socket 50 Ω 20p; 5+: 15p PL259 UHF Plug & Reducer 68p;

5+: 60p; SO239 UHF Socket panel mtd. 55p; 5+: 45p Nicad rechargeables physically equiv. to zinc-carbon types: AAA (U16) £1.64; AA(U7) £1.20, (CU11) £3.15; D(U2) £4.94; PP3 £5.20 Any 5+: less 10%. Any 10+ less 20%.

We stock V.H.F. mobile aeri-als, s.a.e. details.

Distributors for J. H. Associates Ltd. (switches and lamps)

PRICES INCLUDE UK POST, PACKING & VAT
Mail order only

**GAREX ELECTRONICS
7 NORVIC ROAD, MARSWORTH,
TRING, HERTS HP23 4LS
Cheddington (STD 0296) 686864**

cillator transformer. This adjustment then becomes the line hold adjustment."

RANGE OF CONTROL

"There's something here," said Dick, "that's puzzling me a bit."

"What's that?"

"You've just shown me that you can get line synchronism when the line sync pulses coincide with either the beginning, the end or the middle of the flyback period of the line output waveform."

"Yes," said Smithy, "there's quite a wide range over which control is given."

"Well, say the sync pulses coincide with a late part of the flyback period. This could mean that the receiver will have gone into flyback before the end of the transmitted picture information has reached the set."

"That's true," agreed Smithy, "and it's a minor snag with flywheel line sync. When you've adjusted the line hold control to obtain a lock, you find that you can effectively move the whole picture from side to side within the range over which lock occurs. I said just now that we would assume that the desired line hold adjustment is given when the line sync pulses coincide with the centre of the flyback period of the line output transformer waveform. In practice, it is better to adjust the line hold control so that the sync pulses coincide with a rather earlier part of the flyback period in the waveform, say midway between the centre and the start. With most modern sets this will normally result in the picture being properly centralised on the screen. And there's one other little point which I should mention before we finish on this subject. I've been saying that it is the line sync pulses which turn on the flywheel sync diodes. In some sets the sync pulses may be differentiated by passing them through a lowish value capacitor or capacitors before they hit the diodes. The result is that the diodes are turned on each time by a short spike whose leading edge is the leading edge of the sync pulse, rather than by the full sync pulse itself. The result is the same, of course, but the short spike allows the flywheel sync circuit to have increased resolution because a smaller section of the line output transformer waveform is sampled in each cycle."

"Well," said Dick, "that certainly clears up this flywheel sync business."

He scowled as his earlier

grievances rose up in his mind.

"It's a pity," he went on dismally, "that we can't clear up the bog-roll sync problem as easily."

"If you keep on about that," warned Smithy sternly, "I'll get in some of that hard single layer public loo stuff. You won't have any problems with *that* going out of sync."

Dick was aghast.

"You wouldn't," he said in a trembling voice, "do anything like that, would you, Smithy?"

"I will if you don't stop complaining."

"Oh, all right then," grumbled Dick. "I suppose I'd better have a go at repairing this set, then."

He disconnected the receiver from the mains and proceeded to take off its back.

"I should check the sync diodes themselves," suggested Smithy. "One of them may have shorted out."

"What makes you think that?"

"It's only a guess on my part," admitted Smithy. "However, if one diode has shorted out it would provide a circuit path between the slider of the 470 Ω line hold pot and the input to the control voltage smoothing circuit. That would explain why we were able to control the line timebase frequency with the pot."

"Fair enough. I've just thought of something."

"What's that?"

"Why do they call it 'flywheel sync'?"

"It's because of that smoothing circuit for the control voltage," said Smithy. "In the old days of direct line sync, the line timebase could be falsely triggered if the receiver picked up interference pulses, and you'd get line tearing. This meant that line sync would be lost for a number of lines until the line timebase oscillator got back in step again with the transmitted sync pulses. With flywheel sync the control voltage is held steady by the first capacitor in the smoothing circuit, which is the 0.22 μF capacitor following the 2.7k Ω resistor in this particular set. If any interference pulses get through they won't have much effect on the voltage across the capacitor, and that's what gives the flywheel effect." (Fig. 6).

By now, Dick had unhooked the printed board and was examining it closely. He turned his head briefly and looked at the 0.22 μF capacitor in the circuit diagram.

"There's another resistor and capacitor in that circuit," he remarked. "There's a 120 Ω resistor and a

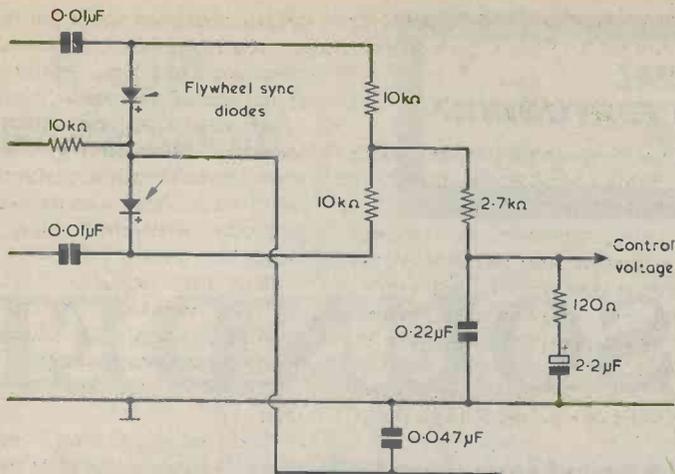


Fig. 6. Detail of the circuit of Fig. 3. The control voltage "smoothing" components are the 0.22μF capacitor, the 120Ω resistor and the 2.2μF capacitor. The last two components also reduce any tendency towards hunting in the sync system

2.2μF electrolytic in series."

"Those are anti-hunt components," said Smithy. "If you just had the 0.22μF capacitor on its own the circuit could have a tendency to hunt around the correct line frequency. It would be the same sort of hunting effect that you get in a servomechanism. The resistor and the capacitor modify the time constant of the flywheel sync loop so that any

hunting that takes place is negligibly low. Have you located those two diodes yet?"

"Yes, I've just found them."

"I should check them both ways round with an ohmmeter," said Smithy. "If my hunch is right you'll soon be able to find the short-circuited one."

And, indeed, Smithy's prediction proved to be correct, and Dick dis-

covered that the lower diode in the circuit diagram was now conducting fully in both directions.

PROBLEM SOLVED

Smithy watched his assistant contentedly as the latter went to the spares cupboard to find a new diode and then soldered it into circuit in place of the faulty one. He waited until Dick had checked the receiver, to find that the horizontal sync circuit was now functioning properly, then quietly made his way out of the Workshop.

Over the years we have followed Smithy into many strange and out of the way places, and modesty would prevent us from accompanying him on his present mission were it not for the fact that his actions solve a minor little mystery. After he had settled himself comfortably, Smithy thoughtfully took the top ply of the paper positioned at his side and passed it once around the roll. The sets of perforations became aligned perfectly. Some time later he just as thoughtfully took the top ply once around the roll again, to give the out-of-sync characteristic which was proving so troublesome to his unsuspecting assistant.

New Product

Z.I.P. D.I.P. SOCKET


The letters Z.I.P. stand for Zero Insertion Pressure and they are applicable to the dual-in-line i.c. holder shown in the accompanying photograph. The socket has been introduced by BFI Electronics Limited, 516 Walton Road, West Molesey, Surrey, KT8 0QF, and is currently available in 16-pin, 24-pin and 40-pin versions will be in production in the near future.

Using the socket is extremely easy. The dual-in-line i.c. is simply dropped into the open socket, after which the small screw at the end is given a quarter turn. This clamps all the i.c. pins inside the socket and ensures excellent mechanical and electrical contact over the life of the i.c. and the socket. The i.c. can be released by turning the screw back to its original position, which will certainly make life easy for service personnel who wish to replace or check the i.c.

Known as the Textool "ECONO

ZIP" socket, the holder is designed as a low cost item with a limited number of clamping operations, but it still incorporates most of the features found in high quality

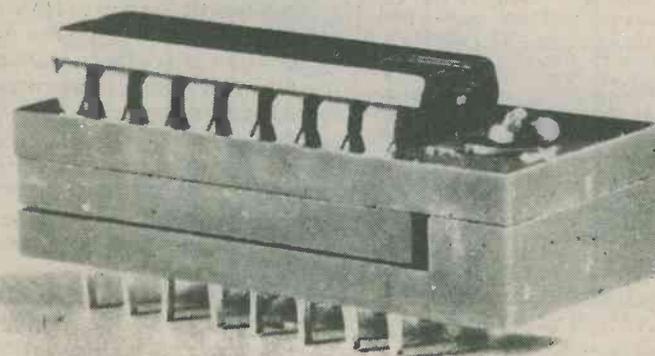"lever-arm" clamping sockets. It is moulded in a UI-approved thermoplastic and its contacts are plated to high standards for maximum life and minimum contact resistance.



The "ECONO ZIP" Zero Insertion Pressure i.c. socket, introduced by BFI Electronics Limited. The socket, which clamps the pins of integrated circuit packages after insertion, is operated by turning the screw head on its upper surface

SIREN SOUNDER

A real attention-catcher

There are simple circuits which can be built on a single S-Dec and which will give a two-tone siren note, but a more difficult proposition is the "sliding-note" siren of the type which is familiar to followers of U.S. Cops and Robbers TV, and which is extensively used in the U.S.A. for emergency vehicles of all sorts. The note from such a siren starts at a high pitch, slides down to a fairly low pitch, then returns to the high pitch again, repeating about twice per second to form a sound that simply cannot be ignored. The circuit of this project provides such a sound pattern, and has enough power output to make a most intrusive noise. It makes an ideal warning sound as well as being extremely useful as a sound effect.

SEVEN TRANSISTORS

The circuit consists of a sawtooth generator, a buffer amplifier and inverter stage, an astable oscillator and an output stage. Six n.p.n. transistors and one p.n.p. transistor are used.

TR1 and TR2 are connected to form an oscillator which simulates the action of a unijunction transistor. TR1 is n.p.n. and TR2 is p.n.p.; their emitters are connected together and there is also a resistive link between the collector of TR1 and the base of TR2. The circuit acts in the following manner. Imagine that the circuit is switched on with C1 discharged. The base of TR1 will then be at the potential of the negative rail, causing TR1 to

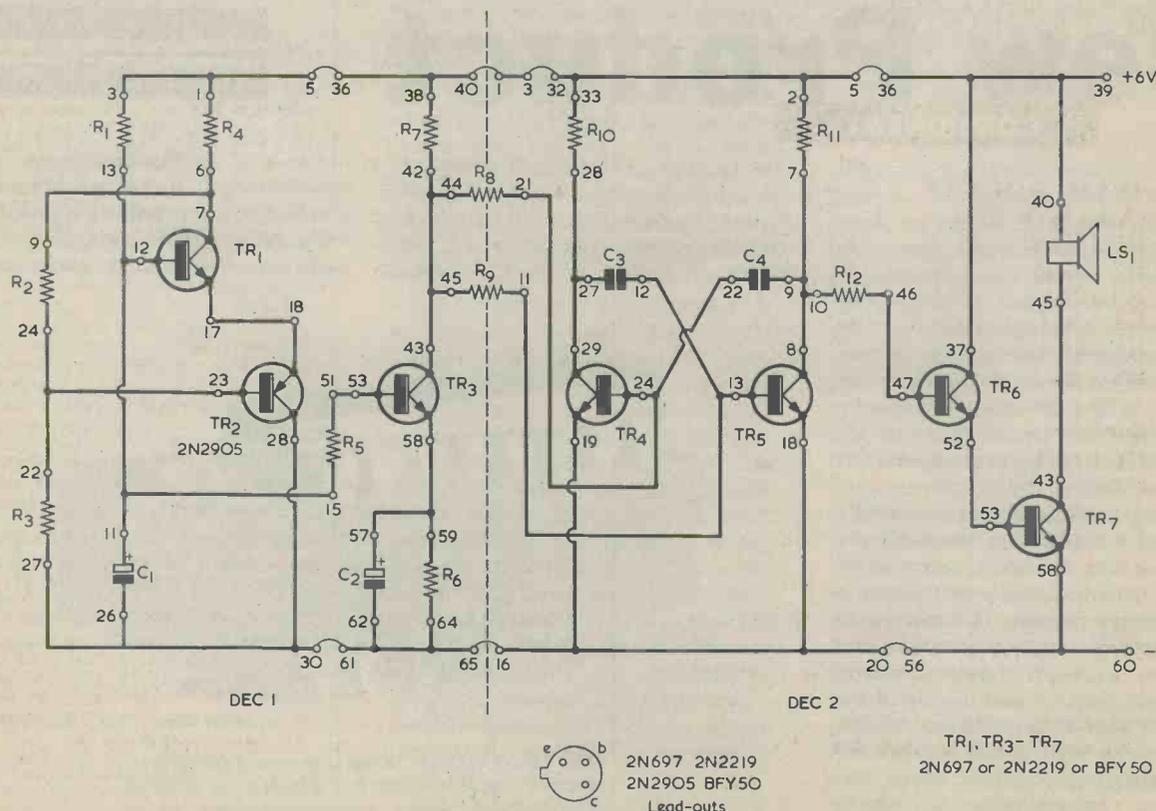


Fig. 1. The circuit of the siren sounder. Component leads and link wires are inserted in the S-DeCs at the numbered points indicated

be cut off. The junction of R2 and R3 will be at about 2 volts positive of the negative rail and TR2 will also be cut off. This is because TR2 is a p.n.p. transistor, which requires the base to be negative of the emitter if it is to conduct.

C1 charges through R1 at a rate determined by the time constant of these two components. When the voltage at point 12 of DeC 1 reaches a level of about 3.2 volts (the 2 volt bias at the base of TR2 plus two base-emitter voltage drops of 0.6 volt each) both TR1 and TR2 start to conduct. With TR1 conducting its collector voltage falls, so that the base voltage of TR2 falls also. The emitter current flowing in the transistors then turns them both hard on. C1 discharges very rapidly through the base-emitter junction of TR1 and through TR2, the voltage across it falling to about 0.8 volt (the base-emitter voltage of TR1 plus a voltage of about 0.2 volt across TR2). The two transistors then turn off, C1 commences to charge again via R1 and another cycle starts.

The waveform at point 12 of DeC 1 is a sawtooth with a positive-going ramp, but we need a negative-going ramp to generate in a multivibrator a note which descends in pitch. We also need rather more amplitude if we are to provide a realistic sound. TR3 is a buffer amplifier which amplifies and inverts the sawtooth. At point 43 of DeC 1, therefore, the waveform is a negative-going sawtooth with a peak-to-peak amplitude of about 6 volts.

ASTABLE OSCILLATOR

TR4 and TR5 form an astable oscillator with cross-coupling capacitors C3 and C4, and collector load resistors R10 and R11. This functions in the familiar multivibrator manner with the capacitors charging through R8 and R9. The rate of charging

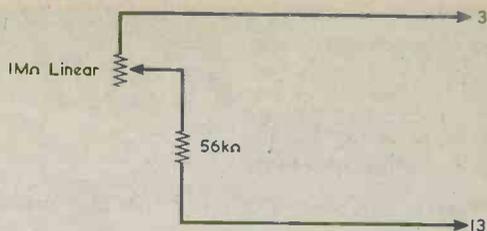


Fig. 2. A variable control of sawtooth frequency can be obtained by replacing R1 with a potentiometer and fixed resistor in series

is faster if the charging resistors are returned to a high voltage, as consequently is the frequency of oscillation. R8 and R9 couple to the collector of TR3 and, at the start of each negative-going ramp of the sawtooth at this collector, the astable frequency will be high. The frequency falls as TR3 collector goes negative until, at the end of each sawtooth ramp, the frequency abruptly goes high again.

The square waves generated by the astable at the collector of TR5 are directly coupled to the output stage, which consists of emitter follower TR6 and the common emitter transistor, TR7. R12 ensures that the astable is not excessively loaded by driving the output stage, and the gain provided by TR6 ensures that TR7 is driven between the fully bottomed and cut-off conditions. The loudspeaker should preferably be a high resistance type, with an impedance of 60Ω to 80Ω. However, a 15Ω speaker can also be used if your ears can stand it!

Several circuit changes can be made if needed. The range of notes can be shifted down in frequency by replacing C3 and C6 with 0.02 μF or 0.05 μF capacitors. The rate of the sawtooth can be increased by connecting another 150kΩ resistor in parallel with R1. The added resistor can be inserted in holes 4 and 14 of DeC1. The rate can be made variable by removing R1 and connecting a 1MΩ potentiometer and a series 56kΩ resistor in its place, as indicated in Fig. 2. The 56kΩ resistor ensures that the potentiometer cannot be adjusted to a low resistance setting which would cause the sawtooth generator to "stick", with both TR1 and TR2 conducting heavily.

CONSTRUCTION

Start construction by clipping two S-DeCs together to form one long DeC. Connect the loudspeaker leads using single-core wire. If stranded wire must be used twist and tin the ends to ensure that there are no loose strands. Plug in the wire links, seven in all, and also the two resistors, R8 and R9, which link the two DeCs together. Next plug in the capacitors, remembering that C1 and C2 are electrolytic and must be connected with correct polarity. The transistors can now be plugged into circuit. TR2 is a p.n.p. type, but its lead-out layout is the same as the other transistors. The assembly of the astable follows the "mirror-image" style, with both emitters connected to the central line of the DeC. Finally, plug in all the remaining resistors.

Add the 6 volt battery leads and prepare to unleash the siren-sound on an unsuspecting world.

COMPONENTS

Resistors

(All ¼ watt 5%)

R1 150kΩ	R7 4.7kΩ
R2 22kΩ	R8 56kΩ
R3 12kΩ	R9 56kΩ
R4 1.8kΩ	R10 1.8kΩ
R5 22kΩ	R11 1.8kΩ
R6 1.8kΩ	R12 56kΩ

Capacitors

C1 10μF electrolytic, 16V Wkg.
C2 10μF electrolytic, 16V Wkg.
C3 0.01μF polyester or mylar
C4 0.01μF polyester or mylar

Semiconductors

TR1 2N697 or 2N2219 or BFY50
TR2 2N2905
TR3-TR7 2N697 or 2N2219 or BFY50

Speaker

LS1 60Ω to 80Ω (see text)

Miscellaneous

2-off S-DeC
6V battery

Radio Topics

By Recorder



HIGH VALUE RESISTORS

Most of us look upon 10M Ω as being the highest value of resistor we're liable to use but, of course, there are applications where much higher resistance values are required. These can be met by a new range of metal glaze resistors announced by SASCO, P.O. Box 2000, Crawley, Sussex, RH10 2RU.

The resistors form the Mullard VR37 Series, and their values range from 1M Ω to 33M Ω . They are designed for applications where high resistance values, high stability and reliability are required. They are also suitable for voltages up to 2.5kV r.m.s.

In their manufacture, a metal glaze is first of all deposited on a high grade ceramic body, the ends of which are then fitted with metal caps to which are welded solder-coated electrolytic copper leads. The required resistance value is obtained by cutting a helical track through the metal glaze. The resistors are protected by multiple coats of a light-blue insulating lacquer, and are colour coded according to E24 preferred values.

Resistance tolerance is 5%, and temperature coefficient of resistance is plus or minus 200 parts per million per degree Centigrade. Maximum power dissipation at an ambient temperature of 70 degrees Centigrade is 0.5 watt and stability is typically within 0.5% over 1,000 hours' operation at 0.5 watt dissipation.

DISPLAY BEZEL

The above photograph illustrates a moulded display bezel, specifically intended for covering unsightly panel cut-out tool marks, which can now be obtained from Vero Electronics Limited. It is available in two sizes and provides an attractive frame as well as highlighting the display behind it. A choice of lenses is offered, these be-



Framing the numeric display at the upper left edge of the panel is the new Vero rectangular display bezel. Simple to fit in place, the bezel not only covers unsightly tool marks but also gives an attractive frame and highlights the display

ing neutral, red and clear, polarised or non-polarised. There is also a full range of compatible mounting boards for both l.e.d. and l.c.d. displays.

The bezel is designed to fit into a single rectangular cut-out. It is positioned in this cut-out by four removable location pegs and is then firmly secured by two moulded-in threaded studs which also hold the display mounting board. Spacers to pass over the studs are provided.

Further details are available from Vero Electronics Limited, Industrial Estate, Chandler's Ford, Eastleigh, Hampshire, SO5 3ZR. Enquiries should refer to the "Display Bezel AB 064".

PETSOFT PROGRAM PACKS

If you want to pamper your Commodore Pet personal computer, Applied Computer Techniques have available a catalogue listing nearly 100 programs as well as Pet Workbooks.



The catalogue is free and is a veritable cornucopia for cost-effective computing. For £8.00 you can buy a discounted cash flow program, sales analysis costs £10.00, while for £25.00 a small business can buy a powerful payroll pack. For those wanting a little fun out of their Pet there are no less than 35 simulation and games programs. For £3.00 you can play noughts and crosses and, for those who prefer more sophisticated board games there is a Super Othello program for £7.00.

Petsoft Limited, a member of the Applied Computer Techniques Group, sells its programs through a nationwide distributor network or even by telephone. Plastic money from any of the credit card companies will normally get a program in the post within 48 hours.

To obtain the free catalogue, apply to Applied Computer Techniques Limited, Petsoft Division, Dudley Road, Halesowen, West Midlands, B63 3NJ. Or you can ring 021-550 7411. ■

DIRECT READER SERVICE

RADIO & ELECTRONICS BOOKS

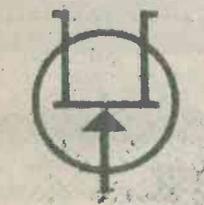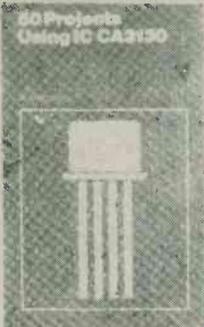

1. **50 PROJECTS USING RELAYS, SCR's & TRIACS**
by F. G. Rayer £1.25
2. **FUN & GAMES WITH YOUR ELECTRONIC CALCULATOR** by J. Vine 90p
3. **50 (FET) FIELD EFFECT TRANSISTOR PROJECTS**
by F. G. Rayer £1.40
4. **DIGITAL IC EQUIVALENTS AND PIN CONNECTIONS**
by Adrian Michaels £2.70
5. **50 SIMPLE L.E.D. CIRCUITS**
by R. N. Soar 90p
7. **THE COMPLETE CAR RADIO MANUAL**
by F. C. Palmer 90p
8. **SOLID STATE NOVELTY PROJECTS**
by M. H. Babani £1.00
9. **28 TESTED TRANSISTOR PROJECTS**
by R. Torrens £1.10
10. **SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS** by R. A. Penfold £1.10
11. **50 PROJECTS USING IC CA3130**
by R. A. Penfold £1.10
12. **50 CMOS IC PROJECTS**
by R. A. Penfold £1.10
13. **HOW TO BUILD ADVANCED SHORT WAVE RECEIVERS** by R. A. Penfold £1.35
14. **BEGINNERS' GUIDE TO BUILDING ELECTRONIC PROJECTS** by R. A. Penfold £1.40
15. **50 CIRCUITS USING GERMANIUM SILICON & ZENER DIODES** by R. N. Soar 90p
16. **LINEAR I.C. EQUIVALENTS AND PIN CONNECTIONS**
by Adrian Michaels £3.00

all prices include postage & packing

To: Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please send me within 21 days copy/copies of

.....
..... No.

I enclose Postal Order/Cheque for £.....

Name

Address

(Block Letters Please)

(We regret this offer is only available to readers in the U.K.)

SMALL ADVERTISEMENTS

Rate: 10p per word. Minimum charge £1.50

Box No. 25p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers. Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. (Replies to Box Numbers should be addressed to: Box No. —, *Radio and Electronics Constructor*, 57 Maida Vale, London, W9 1SN.

SOLAR CELLS: Bits, books and bargains. Send 95p for Solar Cell booklet and Data Sheets or stamp for list. — Edencombe Ltd., 34 Nathans Road, North Wembley, Middlesex HA0 3RX.

COMPLETE REPAIR INSTRUCTIONS for any requested TV, £5 (with diagrams £5.50). Any requested service sheet £1 plus s.a.e. S.a.e. brings free newsletter, details unique publications, vouchers and service sheets from 50p. AUSREC, 76 Church Street, Larkhall, Lanarkshire.

SIGNAL INJECTORS (AF/RF) £2.50 with full instructions. Pin points faults in radios/amps. quickly. Or send s.a.e. for list of low priced test equipment. Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

FOR SALE: Inverter, 12V d.c. to 240V a.c. Suitable running electric shaver, camping, boating, etc. £5.50. Box No. G355.

WANTED: Large and small quantities of transistors, I.C.'s displays, etc., etc. Call any Saturday to: 306 St. Paul's Road, London N.1. Telephone: 01-359 4224.

PARCELS: 200 mixed components £4. 100 £2.75. 10 red LED's 125 90p. 100 mixed branded transistors, new, £2.50. 50 mixed untested i.c.'s 65p. Lists 15p. Sole, 37 Stanley Street, Ormskirk, Lancs., L39 2DH.

2 METRE FM MONITOR RECEIVER MODULE. PCB size 5 in. x 2½ in. 6 channel. Complete kit including prewound coils/transformers and ceramic filters £24.30. Matching scanner, 2 mode kit £7.90 inc. LED's. Receiver crystals £2.50 per channel. Details s.a.e. A. Bailey, G3WPO, 9 Alberta Walk, Worthing, Sussex.

TIRRO'S NEW MAIL ORDER price list of electronic components now available on receipt of S.A.E. — TIRRO Electronics, Grenfell Place, Maidenhead, Berkshire.



THE RADIO AMATEUR INVALID & BEDFAST CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mr. H. R. Boutle, 14 Queens Drive, Bedford.

SOLID STATE INTERCOMS. Call button each end, volume control, and 50 ft. lead. Only £8.95. Refund guarantee. J. Harmsworth, (RE1), 34 Victoria Street, Eccles, Maidstone, Kent.

RADIO, ELECTRONICS, TELEVISION BOOKS. Largest variety. Lowest prices. Write for list. Business Promotion Bureau, 376 Lajpat Rai Market, Delhi 110006, India.

(Continued on page 771)

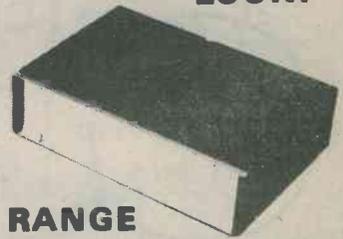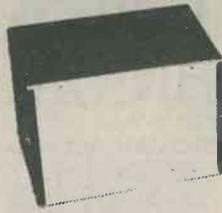DO YOUR PROJECTS LACK THE PROFESSIONAL LOOK?



IF SO, TRY OUR HB RANGE

Instrument cases to give any project a professional look. The four separate top, bottom and end panels are made of black p.v.c. coated steel. Front panel and top and bottom trim are satin anodised aluminium for a neat finish; back panel is in plain aluminium. The whole case, including screws, comes in a flat package and may be assembled in minutes.

Model	DIMENSIONS IN INCHES			Price
	Width	Depth	Height	
HB1	9	6	3	£4.87
HB2	9	6	4½	£5.27
HB3	9	6	6	£5.63
HB4	12	8	3	£5.98
HB5	12	8	4½	£6.80
HB6	12	8	6	£7.26

All prices include V.A.T. and post and packing. Send for free pamphlet on all our instrument cases, boxes and components. Discount on all orders over £10 5%, over £20 10%, over £30 15%.

HARRISON BROS. P.O. Box 55, Westcliff-on-Sea, Essex. SS0 7LQ.
Telephone: Southend-on-Sea (0702) 32338.

A CAREER IN RADIO

Start training *today* and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs — they can do the same for *you*.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

CITY & GUILDS CERTIFICATES

Telecommunications Technicians'
Radio TV Electronics Technicians'
Electrical Installations Technicians'
Electrical Installation Work
Radio Amateurs'
MPT Radio Communications Cert.

**EXAMINATION STUDENTS —
GUARANTEED COACHING
UNTIL SUCCESSFUL**

TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:
Electronic Engineering & Maintenance
Computer Engineering/Programming
Radio, TV & Audio Engineering
& Servicing
Electrical Engineering, Installations & Contracting

COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in

Name

Age

Address

Occupation


ICS

Accredited
by CACC
Member of
ABCC

To
International Correspondence Schools
Dept K278, Intertext House, LONDON
SW8 4UJ or phone 01-622 9911 (anytime)

REVROR OPTICAL & TECHNICAL

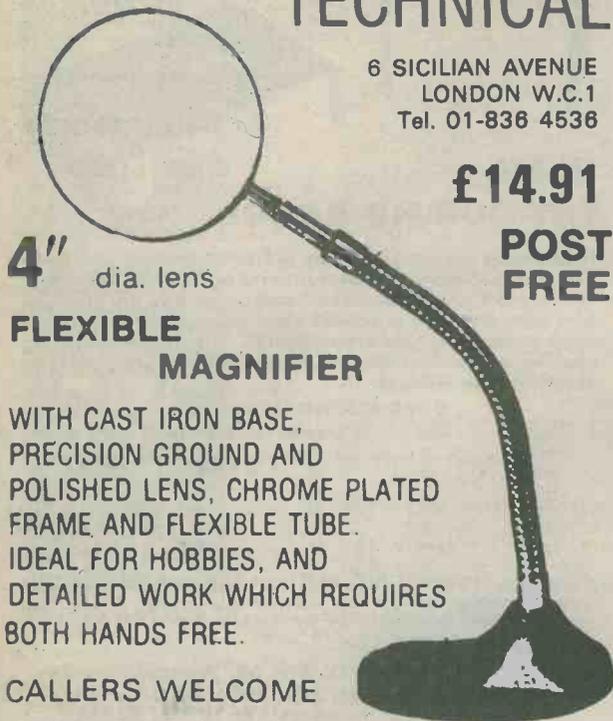6 SICILIAN AVENUE
LONDON W.C.1
Tel. 01-836 4536



4" dia. lens

£14.91

**POST
FREE**

FLEXIBLE MAGNIFIER

WITH CAST IRON BASE,
PRECISION GROUND AND
POLISHED LENS, CHROME PLATED
FRAME AND FLEXIBLE TUBE.
IDEAL FOR HOBBIES, AND
DETAILED WORK WHICH REQUIRES
BOTH HANDS FREE.

CALLERS WELCOME

(Subject to price ruling at the time of issue)

PRINTED CIRCUITS AND HARDWARE

Comprehensive range Constructors' hardware and accessories. Selected range of popular components. Printed circuit boards for individual designs. Drawing materials for printed circuits. Resist coated laminate, epoxy glass for the d.i.y. man. Full processing instructions, no unusual chemicals required.

Send 15p for catalogue

Ramar Constructor Services

Masons Road · Stratford-on-Avon · Warwks CV37 9NF

BUILD YOUR OWN

P.A. GROUP & DISCO SPEAKERS by R. F. C. Stephens

Save money with this practical guide. Plans for 17 different designs, Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

THE INFRA-BASS LOUDSPEAKER by G. Holliman

(full constructional details for versions using 15", 12" and 10" drive units.) £2.95 post free (\$6 overseas).

THE DALESFORD SPEAKER BOOK by R. F. C. Stephens

This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).


VAN KAREN PUBLISHING
5 Swan Street, Wilmslow, Cheshire

Self-Binder

for "Radio & Electronics
Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

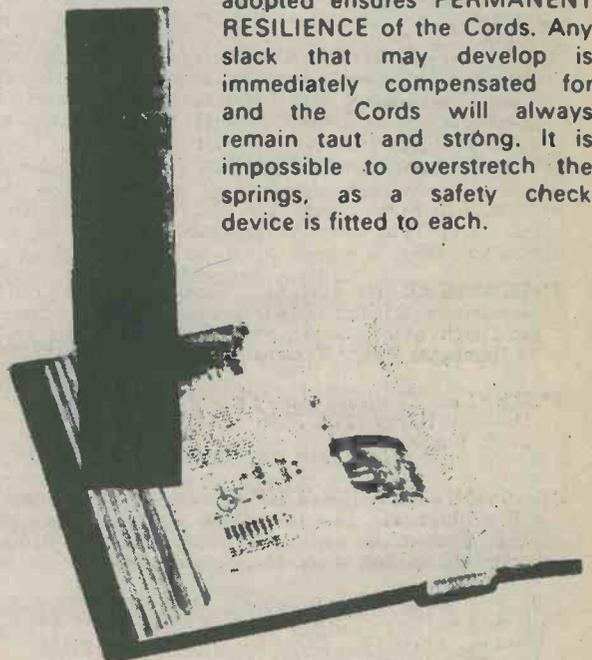

PRICE **£1.95** P.&P. 40p

including V.A.T.

Available only from:—

Data Publications Ltd.

57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 769)

FOR SALE: Single issues of *Radio & Electronics Constructor* covering the period 1955, 1956, 1958, 1959, 1960, 1961, 1967, 1968 and 1976. Not complete years. Cover price asked, plus postage. **WANTED:** Issues for complete years 1947 to 1955, plus December 1972. Marcel Volery, 27 Rue du Grand-Pre, CH-1202 Geneva, Switzerland. Telex 212.

FOR SALE: *Fundamentals of Radio Servicing* by B. W. Hicks, published by Hutchinsons Educational, £2.20 post paid. *Handbook of Satellites and Space Vehicles* by K. P. Haviland, £3.50 post paid. — Box No. G366.

WANTED: FAX equipment, manuals, service sheets, etc. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk. NR32 3PJ.

INTERCOM/BABY ALARM. 50 ft. lead, volume control. Only £7.95. Refund guarantee. J. Harmsworth (RE2), 34 Victoria Street, Eccles, Maidstone, Kent.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. — both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £6.00 per annum. (U.K. and British Commonwealth), overseas \$12.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

FOR SALE: Bush cassette tape recorder, battery driven. Microphone, etc. Excellent condition. £10 plus postage. Box No. G375.

INTERESTED IN OSCAR? Then join AMSAT-UK. Newsletters, OSCAR NEWS Journal, prediction charts, etc. Details of membership from: Ron Broadbent, G3AAJ, 94 Herongate Road, Wanstead Park, London, E12 5EQ.

FOR SALE: "Challenge of the Stars" by Patrick Moore and David A. Hardy £2.00. "Destroyers" by Antony Preston £4.00. Box No. G376.

88-108MHz TRANSMITTERS, built-in battery, mere 25 x 49 x 70mm. £13. 15 x 18 x 40mm. £25. Range up to 500 yards. Transmitter modules £6. Unlicensable U.K. Mail Order. Micro Electronics, 15 New Oxford Street, London W.C.1.

FOR SALE: *Radio & Electronics Constructor*. Seven bound volumes. 1958-1961, 1969-1970, 1971-1972 (Two copies), 1972-1973. Offers? Merseyside. Telephone: 051-426 6767.

COLLECTORS' ITEMS. Nearly 50 copies of Radio Society of Great Britain's *Bulletins* covering period 1945 to 1949. In reasonable condition. Offers to: Box No. G377.

VHF-FM Micro-transmitter. I.C. design. Range 100 yds. 88-110MHz. Built £3.95. Kit £2.95. Both P.&P. 25p. P. Faherty, 4 Angus Drive, South Ruislip, Middlesex.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. — The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

(Continued on page 772)

COMPONENT PACKS

PU1: 50 untested, unmarked t.t.l. i.c.'s (mostly 7400 series) **65p**

PU2: Untested, unmarked silicon diodes, some germanium. Pack of 200 (approx.) **65p**

PT1: Tested, marked selection of popular diodes. Contains: 25 x 1N914, 10 x 1N4002, 5 x BY127 **125p**

PT2: Tested selection of popular electrolytic capacitors. Contains: 5 x 1µF, 5 x 4.7µF, 5 x 10µF, 3 x 100µF **150p**

PT3: Five ¼W 5% resistors of each value from 10 Ω to 1M. Total of 305. Tested. **325p**

PT4: Stranded connecting wire. Five colours each 5 metres. **65p**

PT5: As pack PT4 but solid conductor. **65p**

CAPACITORS

Wide range of polystyrene, polyester, electrolytic etc., too numerous to mention. Prices range from **8p** to **40p**

SEMICONDUCTORS

BC107	12p	7400	12p
BC108	12p	7402	12p
BC109	12p	7408	12p
BC182	12p	741	26p
BC183	13p	ZN414	100p
BC184	13p	BY127	16p
BC212	10p	OA200	20p
BC214	10p	M6800	740p

OPTO-ELECTRONICS

0.125" L.E.D.'s

TIL209 - Red	15p
TIL211 - Yellow	22p
TIL213 - Green	24p
Clips, extra:	2p

Special offer on orders received during July and August. Seven-segment display type DL707. Normal price 90p. Offer price **70p**. Two for **130p**.

POTENTIOMETERS


4.7k - 1M single	28p
100 Ω - 1M horizontal or vertical preset	8p

Mail order only. All prices include VAT. Please add 20p for postage (except component packs). Full list available on receipt of large s.a.e.

T. & J. ELECTRONIC COMPONENTS
98 Burrow Road, Chigwell, Essex IG7 4HB

Understand electronics

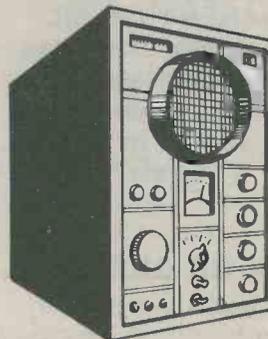Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered using our unique Learn-Kit Course.



- (1) Build an oscilloscope
- (2) Read, draw and understand circuit diagrams.
- (3) Carry out over 40 experiments on basic electronic circuits and see how they work.

FREE

Brochure without obligation to

REF 8/79

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

P.O. Box 156, Jersey, Channel Islands.


NAME _____

ADDRESS _____

PLAIN-BACKED SELF-BINDERS

for your other magazines

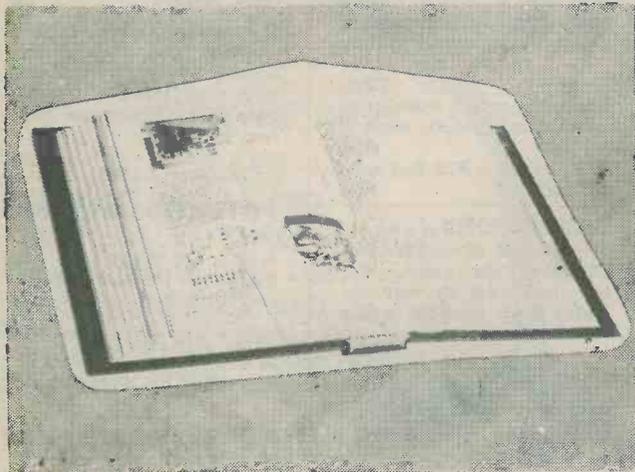(Maximum Format 11 $\frac{1}{4}$ " x 8 $\frac{1}{4}$ ")



The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

COLOURS: MAROON OR GREEN

(If choice not stated, colour available will be sent)

PRICE £1.95 p. & p. 40p
including V.A.T.

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 771)

RECORDS FOR THE RADIO ENTHUSIAST. S.a.e. for details. Atlantis Productions, 13 Clay Road, Caister-on-Sea, Norfolk.

FOR SALE: Telford Communications TC10 "Multiwave" 2 metre transmitter. CW, SSB and FM. S.a.e. for details, price, etc. Box No. G378.

FOR SALE: Eddystone E.C.10 receiver, together with 2 metre converter plus power supply unit. E.C.10 modified for F.M. £90. Box No. G379.

FOR SALE: 5 bound volumes of *Radio & Electronics Constructor*. 1969 to 1972. Offers? Telephone: 01-969 4957.

FOR SALE: 25 mixed voltage 2W zeners 50p. Switch cleaner 50p. P/r cassette mechanisms £10 and £15. S.a.e. for details. Incomplete video tape recorders £50. Closed circuit TV cameras £50. Hearing aid amplifiers £1. Red l.e.d.'s 5p and 10p. 1N914 — 100 — 50p. 10 fuseholders £1. 6 power transistors £1. Miniature relays 25p. Box No. G381.

A FAST INTRODUCTION TO COMPUTING £3.95. Introduction to Microprocessors and Computing £2.75. Both ordered together £6.20. S.A.E. for list of computing books. Dept. RC, Industrial Training Press, 3 Ringwood Way, Winchmore Hill, London N21 2RA.

FOR SALE: Commodore PET Computer £65.00. S.A.E. for booklet. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

NEW SHOP IN EAST KENT. Vast range of electronic components, equipment, hardware. Technocraft, 143 Tankerton Road, Whitstable, Kent. Telephone: 265097. Open Tuesday to Saturday. Easy parking.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

BROADLANDS RESIDENTIAL CLUB for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

FOR HELP with (elementary) Computer, statistical or technical mathematics, send query, s.a.e., paper, P.O. for 50p to: Box No. G380.

SPONSORS required for exciting scientific project Norwich Astronomical Society are building a 30" telescope to be housed in a 20' dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS, Secretary, 195 White Woman Lane, Old Catton, Norwich, Norfolk.

CHI-KUNG for mental/physical health. Discover "Chi" — the life-force/bio-electricity in your body. Send stamp for your Free Literature. The Chi-Kung Society (REC39), 64 Cecil Road, London E13 0LR.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: — The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew., Norwich, NOR 85S.

RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price 50p each, p&p, 13p

Issue(s) required

Annual Subscription

Price **£7.50 inland, £8.50 overseas**

post free, commence with..... issue

Bound Volumes:

Vol. 27. August 1973 to July 1974	Price £3.00 , post & pkg 90p
Vol. 28. August 1974 to July 1975	Price £3.20 , post & pkg 90p
Vol. 29. August 1975 to July 1976	Price £3.50 , post & pkg 90p
Vol. 30. August 1976 to July 1977	Price £3.70 , post & pkg 90p
Vol. 31. August 1977 to July 1978	Price £5.20 , post & pkg 90p

CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,
maroon only

Price **£1.95**, post & pkg 40p

With no title on spine, maroon

Price **£1.95**, post & pkg 40p

With no title on spine, green

Price **£1.95**, post & pkg 40p

Prices include V.A.T.

DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages Price **£1.20**, P. & P. 20p

DB6 Radio Amateur Operator's Handbook,
New edition in course of preparation

DB17 Understanding Television, 504 pages Price **£3.95**, P. & P. 70p

DB19 Simple Short Wave Receivers Price **80p**, P. & P. 20p
140 pages

STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording — White — 6 sheets Price **£1.00**, P. & P. 8p

Set 4: Wording — Black — 6 sheets Price **£1.00**, P. & P. 8p

Set 5: Dials — 6 sheets Price **£1.00**, P. & P. 8p

Prices include V.A.T.

I enclose Postal Order/Cheque for.....in payment for.....

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

*Overseas customers please pay by International Money Order.
All publications are obtainable through your local bookseller*

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS

INDEX TO

VOLUME THIRTY-TWO

September 1978 – August 1979

AMPLIFIERS

High Power Amplifier Modules, <i>by A. P. Roberts</i>	90	Oct.	'78
Noise Reduction Amplifier, <i>by P. R. Arthur</i>	96	Oct.	'78
Testbench Amplifier, <i>by M. V. Hastings</i>	470	Apl.	'79
2 Watt Class A Amplifier, <i>by John Baker</i>	690	July	'79

AMPLIFIER ANCILLARIES

Audio Mixer, <i>by Ian Sinclair</i>	366	Feb.	'79
The ZN424E Operational Amplifier, <i>by P. R. Arthur</i>	25	Sept.	'78

ELECTRONICS

Alternating Voltage Measurements, <i>by F. Bowden</i>	154	Nov.	'78
Bilateral Switch, <i>by F. Bowden</i>	282	Jan.	'79
Car Voltage Monitor, <i>by G. A. French</i>	670	July	'79
CD4017 Musical Box, <i>by G. A. French</i>	152	Nov.	'78
Cunning Light Alarm, <i>by Ian Sinclair</i>	214	Dec.	'78
Digital Dice, <i>by R. A. Penfold</i>	14	Sept.	'78
Discrete Nand Gates, <i>by G. A. French</i>	218	Dec.	'78
Doppler Shift Add-on Unit, <i>by R. A. Penfold</i>	444	Mar.	'79
Electronic "Hangman", <i>by G. A. French</i>	286	Jan.	'79
Enlarger Meter, <i>by M. V. Hastings</i>	558	May	'79
Gas and Smoke Detector — Part 1, <i>by R. A. Penfold</i>	144	Nov.	'78
Gas and Smoke Detector — Part 2, <i>by R. A. Penfold</i>	238	Dec.	'78
Getting Rid of R.F., <i>by R. Webber</i>	372	Feb.	'79
I.C. Morse Practice Oscillator, <i>by I. M. Attrill</i>	424	Mar.	'79
Illuminated Dice, <i>by G. A. French</i>	475	Apl.	'79
Light Change Alarm Unit, <i>by P. R. Arthur</i>	228	Dec.	'78
Logic Level Audible Alarm	677	July	'79
Mains Touch Switch, <i>by A. P. Roberts</i>	672	July	'79
Minimising A.M. Interference, <i>by Ivor N. Nathan</i>	245	Dec.	'78
Multiple 555 Circuits, <i>by G. A. French</i>	734	Aug.	'79
Opto-Isolator A.C. Switch, <i>by John Baker</i>	573	May	'79
Photo Night Light, <i>by Ian Sinclair</i>	156	Nov.	'78
Pinging Bell Circuits, <i>by G. A. French</i>	86	Oct.	'78
Remote Control Garage Light, <i>by G. A. French</i>	606	June	'79
Remote Read-Out Thermometer, <i>by R. A. Penfold</i>	78	Oct.	'78
Scale-of-Two Counter, <i>by Ian Sinclair</i>	304	Jan.	'79
Silicon Controlled Switch Circuits — Part 1, <i>by John Baker</i>	220	Dec.	'78
Silicon Controlled Switch Circuits — Part 2, <i>by John Baker</i>	310	Jan.	'79
Siren Sounder, <i>by Ian Sinclair</i>	764	Aug.	'79
Sleeper-Beeper, <i>by Ian Sinclair</i>	678	July	'79
Sound-Operated Light Switch, <i>by Ian Sinclair</i>	627	June	'79
Sure-Fire CMOS Latches, <i>by G. A. French</i>	348	Feb.	'79
Sustained Alarm Unit, <i>by Vincent S. Evans</i>	545	May	'79
The Decision Maker, <i>by Ian Sinclair</i>	428	Mar.	'79
The Finger Pinger, <i>by G. A. French</i>	417	Mar.	'79
The Sniper — Part 1, <i>by E. A. Parr</i>	550	May	'79
The Sniper — Part 2, <i>by E. A. Parr</i>	629	June	'79
The Swinging Metronome, <i>by R. J. Caborn</i>	172	Nov.	'78
Thyristor Sensitivity Booster, <i>by P. D. Southern</i>	44	Sept.	'78
2-Tone Door Buzzer, <i>by A. P. Roberts</i>	342	Feb.	'79
Touch-Light Circuit, <i>by Ian Sinclair</i>	493	Apl.	'79
Transformer Radio Matching, <i>by D. Snaith</i>	240	Dec.	'78
Tunnel Diode Oscillators, <i>by P. R. Arthur</i>	422	Mar.	'79
Ultrasensitive Ultrasonic Remote Control, <i>by R. A. Penfold</i>	360	Feb.	'79
Visual Metronome With Downbeat, <i>by Paul M. Jessop</i>	742	Aug.	'79
Workshop Power Supply — Part 1, <i>by R. A. Penfold</i>	534	May	'79
Workshop Power Supply — Part 2, <i>by R. A. Penfold</i>	622	June	'79

GENERAL

A Drill For Printed Boards, by <i>I. B. Brodribb</i>	448	Mar.	'79
An Entree To Solderless Breadboarding,	754	Aug.	'79
A Portable Workshop	39	Sept.	'78
Breadboard '78 Exhibition	183	Nov.	'78
Engineer's Hardware Kit	302	Jan.	'79
Fourier Signal Analyzer, by <i>Michael Lorant</i>	184	Nov.	'78
IBA Developments	246	Dec.	'78
Multi Purpose Guillotine	500	Apl.	'79
New Cases For Test Equipment	421	Mar.	'79
New L.F. Signal Analyzer, by <i>Michael Lorant</i>	382	Feb.	'79
Old Timers From The G.E.C., by <i>Ron Ham</i>	351	Feb.	'79
P.C.B. Wiring Jigs, by <i>T. F. Weatherley</i>	704	July	'79
R.S.G.B. National Amateur Radio Exhibition	666	July	'79
Russian Amateur Radio Satellites Launched	350	Feb.	'79
Solid State Telephone Exchanges One Step Nearer	166	Nov.	'78
Sunspots, by <i>Arthur C. Gee</i>	252	Dec.	'78
The 58 Set, by <i>Ron Ham</i>	24	Sept.	'78
The MCR1 Receiver, by <i>Ron Ham</i>	175	Nov.	'78
Waveguide Gas Lasers, by <i>Michael Lorant</i>	19	Sept.	'78
World's Smallest I.F.T.'s	314	Jan.	'79

IN YOUR WORKSHOP

Door Bell Monitor	50	Sept.	'78
Cassette Recorder Fault	114	Oct.	'78
Exclusive-Or Gate	178	Nov.	'78
Computer Subtraction	248	Dec.	'78
Simple Combination Locks	316	Jan.	'79
Video Output Stage Fault	375	Feb.	'79
Stereo Record Player Trouble	438	Mar.	'79
April Fool Circuits	501	Apl.	'79
Valve Hi-Fi Amplifiers	563	May	'79
The "Slow Picture"	632	June	'79
Preventing A.M. Image Interference	696	July	'79
Problems With Sync	758	Aug.	'79

MICROPROCESSORS

Databus No. 1, by <i>Ian Sinclair</i>	744	Aug.	'79
---------------------------------------	-----	------	-----

RECEIVERS

Band II Portable — Part 1, by <i>Sir Douglas Hall, Bt., K.C.M.G.</i>	432	Mar.	'79
Band II Portable — Part 2, by <i>Sir Douglas Hall, Bt., K.C.M.G.</i>	506	Apl.	'79
3 Band Short Wave Superhet — Part 1, by <i>R. A. Penfold</i>	32	Sept.	'78
3 Band Short Wave Superhet — Part 2, by <i>R. A. Penfold</i>	109	Oct.	'78
3 Band Short Wave Superhet — Part 3, by <i>R. A. Penfold</i>	168	Nov.	'78
3 Band Short Wave Superhet — Conclusion, by <i>R. A. Penfold</i>	242	Dec.	'78
Basic Short Wave Radio, by <i>R. A. Penfold</i>	616	June	'79
Beginner's Medium Wave Radio, by <i>I. M. Attrill</i>	750	Aug.	'79
Designing Reflex Circuits — Part 1, by <i>Sir Douglas Hall, Bt., K.C.M.G.</i>	547	May	'79
Designing Reflex Circuits — Part 2, by <i>Sir Douglas Hall, Bt., K.C.M.G.</i>	608	June	'79
Phase Locked A.M. Receiver — Part 1, by <i>M. V. Hastings</i>	296	Jan.	'79
Phase Locked A.M. Receiver — Part 2, by <i>M. V. Hastings</i>	374	Feb.	'79
The "6S3T" Short Wave Receiver, by <i>Sir Douglas Hall, Bt., K.C.M.G.</i>	234	Dec.	'78
The "Doric" 9 Waveband Portable — Part 1, by <i>Sir Douglas Hall, Bt., K.C.M.G.</i>	726	Aug.	'79
The "Hybrid" All Wave Radio — Conclusion, by <i>Sir Douglas Hall, Bt., K.C.M.G.</i>	46	Sept.	'78
V.H.F. Mains Table Radio — Part 1, by <i>R. A. Penfold</i>	487	Apl.	'79
V.H.F. Mains Table Radio — Part 2, by <i>R. A. Penfold</i>	570	May	'79

RECEIVER ANCILLARIES

3 Band Short Wave Preselector, by <i>John Baker</i>	355	Feb.	'79
Car Radio Trim, by <i>R. D. Smith</i>	290	Jan.	'79
"Easi-Build" 100kHz Calibrator, by <i>M. V. Hastings</i>	208	Dec.	'78
F.M. Tuning Indicator, by <i>John Baker</i>	482	Apl.	'79
Phase Locked 200kHz Calibrator, by <i>R. A. Penfold</i>	662	July	'79
PP9 Eliminator Unit, by <i>M. V. Hastings</i>	600	June	'79
Radio 4 Converter, by <i>R. A. Penfold</i>	291	Jan.	'79
9 Volt Eliminator-Speaker Unit — Part 1, by <i>R. A. Penfold</i>	307	Jan.	'79
9 Volt Eliminator-Speaker Unit — Part 2, by <i>R. A. Penfold</i>	370	Feb.	'79

TEST EQUIPMENT

Audio Continuity Tester, by <i>I. M. Attrill</i>	680	July	'79
CMOS Resistance Evaluator, by <i>Bruce Woodland</i>	278	Jan.	'79
Constant Current Transistor Tester, by <i>John Baker</i>	408	Mar.	'79
Electrolytic Capacitance Meter, by <i>G. A. French</i>	542	May	'79
Integrated Circuit Wobblator, by <i>A. P. Roberts</i>	160	Nov.	'78
Musical Voltmeter, by <i>G. A. French</i>	22	Sept.	'78
Square Wave Transistor Tester, by <i>R. A. Penfold</i>	737	Aug.	'79
Ultra-Sensitive OP-AMP Meter, by <i>J. B. Dance</i>	106	Oct.	'78
Variable-C.A.F. Generator — Conclusion, by <i>P. R. Arthur</i>	40	Sept.	'78

TUNE-IN TO PROGRAMS

352	Feb.	'79	419	Mar.	'79	497	Apl.	'79
554	May	'79	610	June	'79	686	July	'79
			755	Aug.	'79			

NEWS AND COMMENT

20	Sept.	'78	84	Oct.	'78	150	Nov.	'78	212	Dec.	'78
284	Jan.	'79	346	Feb.	'79	414	Mar.	'79	480	Apl.	'79
540	May	'79	604	June	'79	668	July	'79	732	Aug.	'79

NEW PRODUCTS

237	Dec.	'78	384	Feb.	'79	495	Apl.	'79
544	May	'79	626	June	'79	763	Aug.	'79

RADIO TOPICS

55	Sept.	'78	119	Oct.	'78	254	Dec.	'78	511	Apl.	'79
			638	June	'79	702	July	'79	766	Aug.	'79

RECENT PUBLICATIONS AND BOOK REVIEWS

113	Oct.	'78	416	Mar.	'79	667	July	'79
-----	------	-----	-----	------	-----	-----	------	-----

SHORT WAVE NEWS

30	Sept.	'78	103	Oct.	'78	176	Nov.	'78	226	Dec.	'78
315	Jan.	'79	380	Feb.	'79	430	Mar.	'79	485	Apl.	'79
568	May	'79	614	June	'79	684	July	'79	748	Aug.	'79

TRADE NEWS

45	Sept.	'78	83	Oct.	'78	217	Dec.	'78
----	-------	-----	----	------	-----	-----	------	-----



ELECTRONICS DATA

No. 37	The Long-Tailed Pair	iii	Sept.	'78
No. 38	The Schmitt Trigger	iii	Oct.	'78
No. 39	The Multivibrator	iii	Nov.	'78
No. 40	Dry Reed Switches	iii	Dec.	'78
No. 41	Relays	iii	Jan.	'79
No. 42	The Moving-Coil Speaker	iii	Feb.	'79
No. 43	Logic Inverters	iii	Mar.	'79
No. 44	Nand Gates	iii	Apl.	'79
No. 45	Nor Gates	iii	May	'79
No. 46	The Triac	iii	June	'79
No. 47	Ferrite Rod Aerials	iii	July	'79
No. 48	Bootstrapping	iii	Aug.	'79

FOR THE BEGINNER

BOOTSTRAPPING



A typical emitter follower audio output stage is shown in (a). In series with the output emitters are two low value resistors which prevent thermal runaway. A further low value resistor (or resistive device) between the output bases prevents crossover distortion. All three resistors may be ignored in the present discussion. The output emitters normally sit at half supply voltage. R_1 is TR_1 collector load resistor. When an input signal causes TR_1 collector to go negative, so also does the base, and consequently the emitter, of TR_3 . When TR_1 collector goes positive so, similarly, does the emitter of TR_2 .

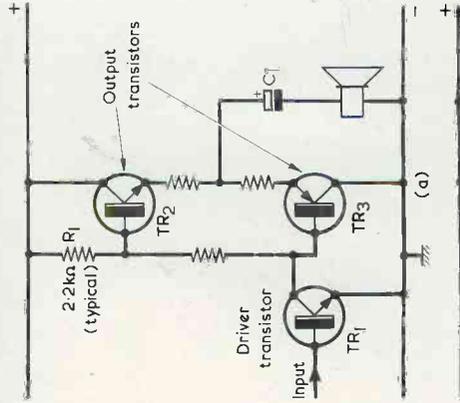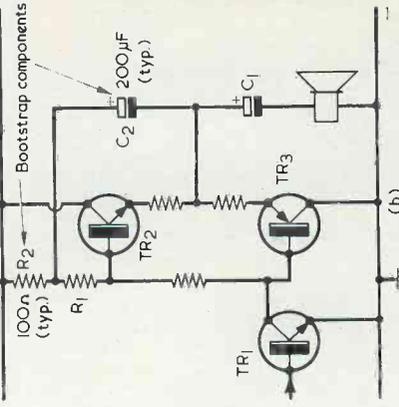

As TR_1 collector goes more and more positive the voltage across R_1 reduces until a level is reached where the current this resistor passes to the base of TR_2 is insufficient to drive the speaker. This constrains the maximum positive excursion of TR_1 collector before the onset of distortion.

Bootstrap components C_2 and R_2 are added in (b). C_2 causes the upper end of R_1 to "follow" the audio output signal so that, if TR_1 collector and TR_2 emitter go highly positive so also does the upper end of R_1 . Ample current is now available for TR_2 base and the only limit to positive excursion at TR_2 collector is the positive supply rail. Since the voltage across R_1 remains virtually unaltered at audio frequencies the resistor offers a very high a.f. resistance and consumes negligible a.f. power, causing the circuit to be more efficient.

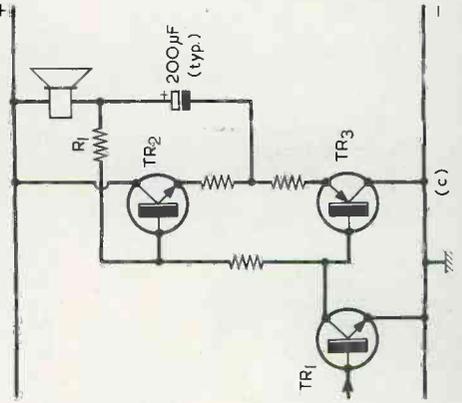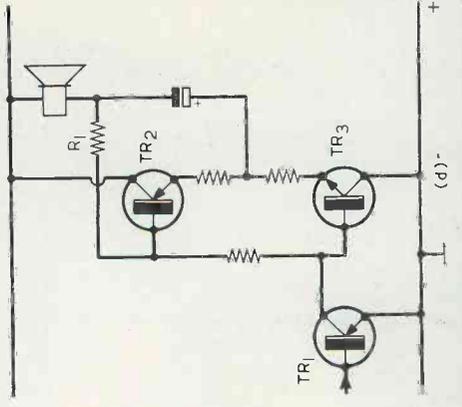A neat version of the bootstrap circuit which saves a capacitor and a resistor is shown in (c). If the upper supply rail is negative all polarities are reversed, as in (d).





Our catalogue even includes some popular car accessories at marvellous prices.



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.



Speakers from 1½ inch to 15 inch, megaphone, PA horns, crossovers, etc. They're all in our catalogue. Send the coupon now!



Our catalogue describes a wide range of plugs and sockets, all at marvellous prices. See cat. pages 114 to 129 for details.



61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



These are just some of the metal cases we stock. These are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop: 284 London Road,
 Westcliff-on-Sea, Essex.
 (Closed on Monday).
 Telephone: Southend (0702) 554000



A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.



A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue - send the coupon now!

Post this coupon now for your copy of our 1979-80 catalogue price 75p.

Please send me a copy of your 280 page catalogue. I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME _____

ADDRESS _____