

RADIO & ELECTRONICS

CONSTRUCTOR

OCTOBER 1979
50p


STYLUS ORGAN



EASY-TO-BUILD MONOPHONIC
ELECTRONIC ORGAN WITH
SWITCHABLE VIBRATO

10watts Vmos AMPLIFIER

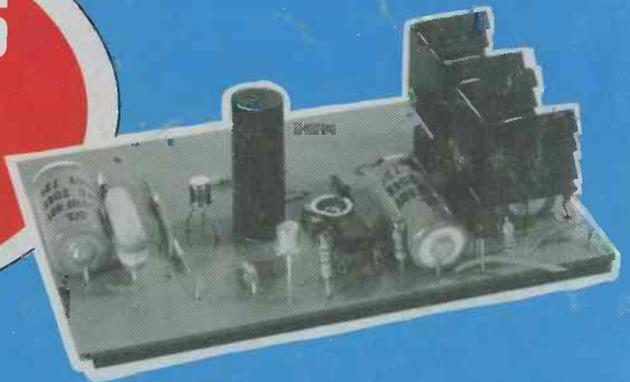POWER F.E.T. CLASS B' OUTPUT WITH
NEGATIVE TEMPERATURE
COEFFICIENT



**ALSO
FEATURED**

ULTRA-SIMPLE QUIZZ SELECTOR

DIODES/ZENERS			
QTY.			
1N914	100v	10mA	.05
1N4005	600v	1A	.08
1N4007	1000v	1A	.15
1N4148	75v	10mA	.05
1N4733	5.1v	1 W Zener	.25
1N4749	24v	1W	.25
1N753A	6.2v	500 mW Zener	.25
1N758A	10v	"	.25
1N759A	12v	"	.25
1N5243	13v	"	.25
1N5244B	14v	"	.25
1N5245B	15v	"	.25
1N5349	12v	3W	.25

SOCKETS/BRIDGES			
QTY.			
8-pin	pcb	.16 ww	.35
14-pin	pcb	.20 ww	.40
16-pin	pcb	.25 ww	.45
18-pin	pcb	.30 ww	.95
20-pin	pcb	.35 ww	1.05
22-pin	pcb	.40 ww	1.15
24-pin	pcb	.45 ww	1.25
28-pin	pcb	.50 ww	1.35
40-pin	pcb	.55 ww	1.45
Molex pins	.01	To-3 Sockets	.35
2 Amp Bridge	100-prv		.95
25 Amp Bridge	200-prv		1.50

TRANSISTORS, LEDS, etc.			
QTY.			
2N2222M (2N2222 Plastic .10)			.15
2N2222A			.19
2N2907A	PNP		.19
2N3906	PNP (Plastic)		.19
2N3904	NPN (Plastic)		.19
2N3054	NPN		.55
2N3055	NPN 15A 60v		.60
T1P125	PNP Darlington		1.95
LED Green, Red, Clear, Yellow			19
D.L. 747	7 seg 5 8" High com-anode		1.95
MAN72	7 seg com-anode (Red)		1.25
MAN3610	7 seg com-anode (Orange)		1.25
MAN82A	7 seg com-anode (Yellow)		1.25
MAN74	7 seg com-cathode (Red)		1.50
FND369	7 seg com-cathode (Red)		1.25

9000 SERIES			
QTY.		QTY.	
9301	.85	9322	.65
9309	.50	9601	.30
		9602	.45

C MOS							
QTY.		QTY.		QTY.		QTY.	
4000	.15	4017	.75	4034	2.45	4069 74C04	.45
4001	.20	4018	.75	4035	.75	4071	.25
4002	.25	4019	.35	4037	1.80	4081	.30
4004	3.95	4020	.85	4040	.75	4082	.30
4006	.95	4021	.75	4041	.69	4507	.95
4007	.25	4022	.75	4042	.65	4511	.95
4008	.75	4023	.25	4043	.50	4512	1.50
4009	.35	4024	.75	4044	.65	4515	2.95
4010	.35	4025	.25	4046	1.25	4519	.85
4011	.30	4026	1.95	4047	2.50	4522	1.10
4012	.25	4027	.35	4048	1.25	4526	.95
4013	.40	4028	.75	4049	.65	4528	1.10
4014	.75	4029	1.15	4050	.45	4529	.95
4015	.75	4030	.30	4052	.75	MC14409	14.50
4016	.35	4033	1.50	4053	.95	MC14419	4.85
				4066	.75	74C151	2.50

CABLE ADDRESS: ICUSD

Telex #697-827 ICUSD SDG

HOURS: 9 A.M. - 6 P.M. MON. thru SUN.

INTEGRATED CIRCUITS UNLIMITED

7889 Clairemont Mesa Blvd. • San Diego, California 92111 U.S.A.

NO MINIMUM

COMMERCIAL AND MANUFACTURING ACCOUNTS INVITED

ALL PRICES IN U.S. DOLLARS. PLEASE ADD POSTAGE TO COVER METHOD OF SHIPPING
ORDERS OVER \$100 (U.S.) WILL BE SHIPPED AIR NO CHARGE.

PAYMENT SUBMITTED WITH ORDER SHOULD BE IN U.S. DOLLARS.

ALL IC'S PRIME/GUARANTEED ALL ORDERS SHIPPED SAME DAY RECEIVED.

CREDIT CARDS ACCEPTED:

Phone (714) 278-4394

BarclayCard / Access / American Express / BankAmericard / Visa / MasterCard

MICRO's, RAMS, CPU's, E-PROMS

QTY.		QTY.	
8T13	2.50		
8T23	2.50		
8T24	3.00		
8T97	1.75		
74S188	3.00		
1488	1.25		
1489	1.25		
1702A	4.50		
AM 9050	4.00		
ICM 7207	6.95		
ICM 7208	13.95		
MPS 6520	10.00		
MM 5314	4.00		
MM 5316	4.50		
MM 5387	3.50		
MM 5369	2.95		
TR 1602B	3.95		
UPD 414	4.95		
Z 80 A	22.50		
Z 80	17.50		
Z 80 P10	10.50		
2102	1.45		
2102L	1.75		
2107B-4	4.95		
2114	9.50		
2513	6.25		
2708	11.50		
2716 D.S.	34.00		
2716 (5v)	69.00		
2758 (5v)	26.95		
3242	10.50		
4116	11.50		
6800	13.95		
6850	7.95		
8080	7.50		
8085	22.50		
8212	2.75		
8214	4.95		
8216	3.50		
8224	4.25		
8228	6.00		
8251	7.50		
8253	18.50		
8255	8.50		
TMS 4044	9.95		

T T L							
QTY.		QTY.		QTY.		QTY.	
7400	.20	7492	.45	74H20	.25	74LS76	.70
7401	.20	7493	.35	74H21	.25	74LS86	.95
7402	.20	7494	.75	74H22	.40	74LS90	.85
7403	.20	7495	.60	74H30	.30	74LS93	.85
7404	.20	7496	.80	74H40	.35	74LS96	2.00
7405	.35	74100	1.15	74H50	.30	74LS107	.90
7406	.25	74107	.35	74H51	.30	74LS109	1.50
7407	.55	74121	.35	74H52	.20	74LS123	1.95
7408	.20	74122	.55	74H53	.25	74LS138	2.00
7409	.25	74123	.55	74H55	.25	74LS151	.95
7410	.20	74125	.45	74H72	.35	74LS153	1.15
7411	.25	74126	.45	74H74	.35	74LS157	1.15
7412	.25	74132	.75	74H101	.95	74LS160	1.15
7413	.45	74141	.90	74H103	.55	74LS164	2.90
7414	.75	74150	.85	74H106	1.15	74LS193	2.00
7416	.25	74151	.95	74L00	.30	74LS195	1.15
7417	.40	74153	.95	74L02	.30	74LS244	2.90
7420	.25	74154	1.15	74L03	.35	74LS259	1.50
7426	.25	74156	.70	74L04	.40	74LS298	1.50
7427	.25	74157	.65	74L10	.30	74LS367	1.95
7430	.20	74161/9316	.75	74L20	.45	74LS368	1.25
7432	.30	74163	.85	74L30	.55	74LS373	2.50
7437	.20	74164	.75	74L47	1.95	74S00	.45
7438	.30	74165	1.10	74L51	.65	74S02	.45
7440	.20	74166	1.75	74L55	.85	74S03	.35
7441	1.15	74175	.90	74L72	.65	74S04	.35
7442	.55	74176	.95	74L73	.70	74S05	.45
7443	.45	74177	1.10	74L74	.75	74S08	.45
7444	.45	74180	.95	74L75	1.05	74S10	.45
7445	.75	74181	2.25	74L85	2.00	74S11	.45
7446	.70	74182	.75	74L93	.75	74S20	.35
7447	.70	74190	1.25	74L123	1.95	74S22	.55
7448	.50	74191	1.25	74LS00	.40	74S40	.30
7450	.25	74192	.75	74LS01	.40	74S50	.30
7451	.25	74193	.85	74LS02	.45	74S51	.35
7453	.20	74194	.95	74LS03	.45	74S64	.15
7454	.25	74195	.95	74LS04	.45	74S74	.70
7460	.40	74196	.95	74LS05	.45	74S112	.60
7470	.45	74197	.95	74LS08	.45	74S114	.85
7472	.40	74198	1.45	74LS09	.45	74S133	.85
7473	.25	74221	1.50	74LS10	.45	74S140	.75
7474	.30	74298	1.50	74LS11	.45	74S151	.95
7475	.35	74367	1.35	74LS20	.45	74S153	.95
7476	.40	75491	.65	74LS21	.45	74S157	.98
7480	.75	75492	.65	74LS22	.45	74S158	.80
7481	.85	74H00	.20	74LS32	.50	74S194	1.50
7482	.95	74H01	.30	74LS37	.45	74S196	2.00
7483	.95	74H04	.30	74LS38	.65	74S257 (8123)	2.50
7485	.75	74H05	.25	74LS40	.70	8131	2.75
7486	.55	74H08	.35	74LS42	.95		
7489	1.05	74H10	.35	74LS51	.75		
7490	.55	74H11	.25	74LS74	.95		
7491	.70	74H15	.45	74LS75	1.20		

I²L, LINEARS, REGULATORS, ETC.

QTY.		QTY.		QTY.	
MCT2	.95	LM320K24	1.65	LM377	3.95
8038	3.95	LM320T5	1.65	LM373	3.95
LM201	.75	LM320T12	1.65	78L05	.75
LM301	.45	LM320T15	1.65	78L12	.75
LM308	.65	LM323K	5.95	78L15	.75
LM309H	.85	LM324	1.25	78M05	.75
LM309 (340K-5)	1.50	LM339	.75	LM380 (8-14 Pin)	1.19
LM310	.85	7805 (340T5)	1.15	LM709 (8-14 Pin)	.45
LM311 (8-14 Pin)	.75	LM340T12	.95	LM711	.45
LM318	1.50	LM340T15	.95	LM723	.40
LM320H6	.79	LM340T18	.95	LM725	2.50
LM320H15	.79	LM340T24	.95	LM739	1.50
LM320H24	.79	LM340K12	1.25	LM741 (8-14)	.45
7905 (LM320K5)	1.65	LM340K15	1.25	LM747	1.10
LM320K12	1.65	LM340K18	1.25	LM1307	1.75
LM320K15	1.65	LM340K24	1.25	LM1458	.65

LM3900	.95
LM75451	.65
NE555	.45
NE556	.85
NE565	1.15
NE566	1.25
NE567	.95
TA7205	6.95
76477	2.95
95H90	9.95

SPECIAL DISCOUNTS

Total Order	Deduct
\$35-\$99	10%
\$100-\$300	15%
\$301-\$1000	20%

RADIO & ELECTRONICS CONSTRUCTOR

OCTOBER 1979
Volume 33
No. 2

Published Monthly
(3rd of preceding Month)

First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone 01-286 6141
Telegrams Databux, London

© Data Publications Ltd., 1979. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £7.50, Eire and Overseas £8.50 (U.S.A. and Canada \$20.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production— Web Offset.

STYLUS ORGAN by M. V. Hastings Easy-to-build monophonic electronic organ with switchable vibrato	78
ULTRA-SIMPLE QUIZZ SELECTOR — Suggested Circuit by G. A. French	84
RECENT PUBLICATIONS	85
NEWS AND COMMENT	86
DOUBLING-AND-HALVING by D. Snaith	88
HOW MICROPROCESSORS WORK — Selection and Bussing — Databus No. 3 by Ian Sinclair	89
IN NEXT MONTH'S ISSUE	93
SHORT WAVE NEWS — For DX Listeners by Frank A. Baldwin	94
10 WATT VMOS AMPLIFIER by R. A. Penfold Power f.e.t. Class B output with negative temperature coefficient	96
ANSWER WINKER — Double Deccer No. 10 by Ian Sinclair	102
CALCULATOR TOPIC by Recorder	104
THE "DORIC" 9 WAVEBAND PORTABLE — Part 3 by Sir Douglas Hall, Bt., K.C.M.G.	105
LOG AND LIN — Notes For Newcomers by R. J. Carborn	112
S-DEC ADAPTOR by A. M. Williams and K. R. Nash	114
DICING WITH TWO I.C.'s — In Your Workshop	116
CAN ANYONE HELP?	121
ELECTRONICS DATA No. 50 TRANSFORMER CURRENTS	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The *Radio & Electronics Constructor* is printed by Swale Press Ltd.

THE NOVEMBER ISSUE
WILL BE PUBLISHED
ON 4th OCTOBER

Technoledgey for sale.

The Mark III FM Tuner

DIY Hi-Fi will never seem the same again. Ambit's Mark III tuner system is electrically & visually superior to all others. Some options available, but the illustrated version with reference series modules: £149.00 + £18.62 VAT

With Hyperfi Series modules £185.00 + £23.12



ALL TUNER KITS £3 carriage

Features of the system:

- * Precision construction & design of all parts
- * Time/frequency display
- * State of the art performance with facilities for updates, using modular plug in systems.
- * Deviation level calibrator for recording
- * All usual tuner features

Digital Dorchester All Band Broadcast Tuner: LW/MW/SW/SW/SW/FM stereo

A multiband superb tuner, constructed using a single IC for RF/IF processing - but with all features you would expect of designs far greater complexity. The FM section uses a three section (air gang) tuned FET tunerhead, with ceramic IF filters and interstation mute; AM employs a double balanced mixer input stage, with mechanical IF filters - plus a BFO and MOSFET product detector for CW/SSB reception. Styled in a matching unit to the Mark III FM only tuner, employing the same degree of care in mechanical design to enable easy construction. MW/LW reception via a ferrite rod antenna.

Electronics only (PCB and all components thereon) £33.00 + £4.95 VAT
Complete with digital frequency readout/clock-timer hardware £99.00 + £14.85 VAT
Complete with MA1023 clock/timer module with dial scale £66.00 + £9.90 VAT

Hardware packages are available separately if you wish to house your own designs in a professional case structure. Please deduct the cost of electronics from complete prices.

PW SANDBANKS PI METAL LOCATOR

Maintaining our professional approach to home constructor kits, we offer the pulse induction 'Sandbanks'. Now with injection molded casing for greatly improved environmental sealing. £37.00+£5.55vat

VHF MONITOR RX WITH PLESSEY IC 4/9

channel version of the PW design but using standard (fundx9) crystals, and TOYO 8 pole crystal filter with matching transformers. Coil sets from our standard range to cover bands from 40 to 200MHz. Complete module kit £31.25 +£3.90vat

MICROMARKET OSTs overflow:

6800P	650p	8212	230p	2102	170p
6820P	600p	8216	195p	2112	340p
6850P	275p	8224	350p	2513	754p
6810	400p	8228	478p	4027	578p
6852	365p	8251	625p	2114	1000p
8080	630p	8255	540p	+15% VAT	

OSTs: Remember all OSTs stocks are obtained from BS9000 approved sources - your assurance that all devices are very best first quality commercial types. Some LPSN TTL is presently in great demand, so please check by phone before ordering.

TTL: Standard AND LP Schottky

All prices listed in pence x

VOLTAGE REGS:		MISCS. Counter/timer, scalar devices.....	
7400	13 20	7412	265
7401	13 20	7413	312
7402	14 20	7414	312
7403	14 20	7415	312
7404	14 24	7416	312
7405	18 26	7417	312
7406	38	7418	312
7409	17 24	7419	312
7410	15 24	7420	312
7411	20 24	7421	312
7412	17	7422	312
7413	30	7423	312
7414	51	7424	312
7415	24	7425	312
7416	30	7426	312
7417	30	7427	312
7420	16 24	7428	312
7421	29 24	7429	312
7422	27	7430	312
7425	27	7431	312
7426	27	7432	312
7427	27 29	7433	312
7428	35 32	7434	312
7430	17 24	7435	312
7432	25 24	7436	312
7437	40 24	7437	312
7438	33 24	7438	312
7440	17 24	7439	312
7441	74	7440	312
7442	70 99	7441	312
7443	115	7442	312
7444	112	7443	312
7445	94	7444	312
7446	94	7445	312
7447	82 89	7446	312
7448	56 99	7447	312
7449	99	7448	312
7451	17 24	7449	312
7453	17	7450	312
7454	17 24	7451	312
7455	35 24	7452	312
7456	17	7453	312
7457	124	7454	312
7463	28	7455	312

Current news: A PCB for the Mullard DC tone and volume control system is now available £3 + 0.45 VAT. HMOS PA modules for 60-100W - kit £14 + £2.10VAT, heatsink £4.10+0.61. FM radio control system crystals £3.75 pair inc VAT (Sept on). MK50366N: static drive clock/timer IC £3.78 + 0.57 VAT, 12.5kHz channel spacing 8 pole 10.7MHz XTAL filter by TOYO type H4402 £15.50 + £2.32VAT. A further updated pricelist is now available, and we would like to remind you that enquiries can only be answered if accompanied either by an official business letterhead, or an SAE. STOP PRESS: TOKO's new split-apart triple AM tuning diodes are in stock £2.45 + 37p VAT, (KV1215). S BL1 diode DBM 1.500MHz - £4.25+0.64p.

Terms: CWO please. Account facilities for commercial customers OA. Postage 25p per order. Minimum credit invoice for account customers £10.00. Please follow instructions on VAT, which is usually shown as a separate amount. Overseas customers welcome - please allow for postage etc according to desired shipping method. Access facilities for credit purchases. Catalogues: Ambit, Part 1 45p, Part 2 50p 90p pair. TOKO Euro shortform 20p. Micrometals toroid cores 40p. All inc PP etc. Full data service described in pricelist supplements. Hours/phone: We are open from 9am - 7pm for phone calls. Callers from 10am to 7pm. Administrative enquiries 9am to 4.30pm please (not Saturdays). Saturday service 10am to 6pm.

LW MW FM LCD Digital Frequency Display - July PW feature

Update your old radio, or build this into a new design. Or use it as a servicing aid - this low power unit with LCD display reads direct frequency in kHz/MHz, or with usual AM/FM IF offsets for received frequency. Low power LCD means no RFI - 15-20mA at 9v even with the divide by 100 prescaler. FM resolution is 100kHz, AM 1kHz. Sensitivities better than 10mV Complete kit £19.50 + £2.93 VAT, built and tested module £27.00 + £4.05VAT



Ambit stocks and distributes a wide range of frequency counter LSI for all types of DFM-part two of the catalogue contains details of the MSM5523/4/5/6 range, and the versatile MSL2318 divide by ten or hundred prescaler IC. The DFM1 combined counter for AM, FM SW and direct/clock/stopwatch/timers - details available, but SAE please!

RADIO AND AUDIO MODULES - Consistently the most advanced FOR FM

EF5801	Dual gate MOSFET RF stages, bipolar mixer	£17.45 + 2.61VAT
5803	Dual gate RF/mixer stages, amplified LO out	£19.75 + 2.97VAT
5804	'Hyperfi' series, with internal PIN diode agc, and ultra wide range tuning system	£24.95 + 3.74VAT
EF5402	4 stage varicap tuner with TDA1062 and LO output. Uses FET/IC input. PDA10eq	£10.75 + 1.61VAT

FOR 30-200MHz series are available on special order to cover bands (usually approx 20% of the centre frequency) in the range described. Details in our price list.

FOR FM IFs at 10.7MHz	7030	single 6 pole linear phase filter IF with HA1137E10.95 + 1.64VAT
	7130	two 6 pole linear phase filter IF with CA3189E £16.25 + 2.44VAT
	7230	Hyperfi IF, switched bandwidth, AGC IF preamp, linear phase ceramic filters with diode switched narrow filter £24.95 + 3.74VAT

DECODERS FOR MPX (STEREO)	Various types, guaranteed the world's biggest and best ranges
LARSCHOLT FM TUNERSSETS	7252 MOSFET front end combined with CA3089 IF £26.50 + 3.97VAT
	7252 JFET front end, combined with IF and decoder £26.50 + 3.97VAT

FM/AM tuning synthesiser, see details elsewhere in this advertisement

COMPONENTS FOR RADIO/COMMUNICATIONS/AUDIO/TV etc.

As usual, Ambit brings you the latest and best, a small selection of which is shown in this advertisement. The Ambit catalogue contains information on most of the devices mentioned here - and an order for the new part three will ensure you stay up with latest developments. Data photocopying service described in pricelist info.

RADIO ICs for FM var	SL1600 series	Audio preamps	var	
CA3089E	1.94 29	LM3811	1.81 27	
CA3189E	2.45 37	LM3821	1.65 25	
HA1137W	2.20 33	KB4438	2.22 33	
HA11225	2.20 33	TDA1028	3.50 53	
SN1660M	0.75 11	TDA1029	3.50 53	
RADIO ICs for AM/FM	SL1621 2.17 33	TDA1074	3.75 56	
TDA1090	3.35 50	Audio power		
TDA1083	1.95 29	SL 624	3.28 49	
TDA1220	1.40 21	SL1625	2.17 33	
IF AMPLIFIERS	SL1626	2.44 37	TBA810AS	0.75 11
KB4406	0.50 07	SL1630	1.62 24	
MC1350	1.20 18	SL1640	1.98 28	
see comms ics also	SL1641	1.89 28	TDA2002	1.00 15
COMMUNICATIONS	SL1660	2.75 41	HA1370	2.99 45
KB4412	2.55 38	MC3357	3.12 47	
KB4413	2.75 41	MC1496	1.25 19	
SD6000	3.75 56	NE544	1.70 25	

CD4000

4000	17	4522	149
4001	17	4528	102
4002	17	4529	141
4006	109	4532	125
4007	18	4538	150
4008	80	4539	110
4009	58	4543	174
4010	58	4549	399
4011	17	4554	153
4012	17	4558	117
4013	55	4560	218
4014	95	4562	530
4015	80	4566	189
4016	52	4568	281
4017	80	4569	303
4018	80	4572	26
4019	60	4584	63
4020	93	4585	100
4021	82		
4022	90		
4023	17		
4024	76		
4025	17		
4026	180		
4027	55		
4028	72		
4029	90		
4030	58		
4035	120		
4040	83		
4042	85		
4043	85		
4044	80		
4046	80		
4048	60		
4049	55		
4050	55		
4051	65		
4052	65		
4053	65		
4059	563		
4060	115		
4063	109		
4065	53		
4068	25		
4069	20		
4070	20		
4071	20		
4072	20		
4073	20		
4075	20		

MORE FROM THE GENERAL AMBIT CATALOGUE RANGES:

Variac tuning diodes for AM/FM/TV - 1.9v AM tuning (Dr 15:1) from TOKO - KV1211 double matched 175p 26p vat	KV1210 triple matched 245p 37p vat	KV1215 triple snap-apt 245p 37p vat	MVM115 single 15v 105p 16p vat	MVM125 single 25v 105p 16p vat	MVM2 double 25v 148p 22p vat	BB204/104 double FM 40p 6p vat	BA102 single AFC etc 30p 4p vat	BA121/TT210 single afc 30p 4p vat	BB105S single UHF 40p 6p vat	PIN DIODES, BANDSWITCH types	BA479 PIN attenuator 35p 5p vat	TDA1061 Pi-front atten. 95p 14p vat	BA182 Bandswitch 21p 3p vat	All RF semiconductor stocks in depth. Please ask for quantity pricing details.
---	------------------------------------	-------------------------------------	--------------------------------	--------------------------------	------------------------------	--------------------------------	---------------------------------	-----------------------------------	------------------------------	------------------------------	---------------------------------	-------------------------------------	-----------------------------	--

LINEARS

CA3130E	84
CA3130T	90
CA3140E	84
CA3140T	72
LM301A	67
LM301AN	30
LM339N	66
LM348N	186
LM3900N	60
709HC	64
709PC	36
710HC	65
710PC	65
723CN	65
741CH	66
741CN	27
747CN	70
748CN	36
NE531N	105


FUTABA FLUORESCENT VACUUM DISPLAYS FOR CLOCKS etc

SLT02	clock display (static drive) with AM/FM flags	£9 + 1.35
SLT03	DFM display for MS1655 LSI counter	£9.45 + 1.42 vat
6LT06	5 digit DFM display (IG AY58100) mpxed	£9.75 + 1.46 vat

TOKO COILS, FILTERS, CHOKES, etc for AM/FM/TV comms -

TYPE	Size	5mm	7mm	10mm	(please add VAT @ 15%)	
AM IF	5p	33p	30p	Various for ICs, transistor etc.		
FM IF	5p	33p	33p	Various for ICs, transistor etc.		
SW coils			33p	Two impedance series		
OSC coils	5p	33p	33p	For LW/MW/SW TV vhf/uf		
			35p			
Various coils in the range 20kHz to 300MHz - see TOKO catalogue						
CERAMIC AND MECHANICAL FILTERS (inc MURATA TYPES)						
CF4458B	CFT455C	60p	CFX014	180p	CFU455C	85p
CF4740	60p	CFU470C	65p			
MURATA CFU455H	and CFU455F	ceramic block filters	1.95ea			
MURATA CFM455 series	ladder filters	D,E,F,G,H	bandwidths available now (20,16,12,8.6 kHz)	£8.35 ea	(metal encapsulated)	
CF2455B	SFD470B	85p ea				
CFM2 series	mechanical elements	types A,B,C,D	(4-10kHz bandwidth)			
SLT03	DFM display for MS1655 LSI counter	£9.45 + 1.42 vat				
CFSE10.7/5E10.7	stereo FM IF ceramic filters (sim FM4 etc)	50p				
CFSE10.7/5E10.7MJ	mono bandwidth ceramic FM IF filters	50p				
CFSE10.7/5E10.7	ultra linear phase stereo ceramic IF filters	70p				
CD10A1.7	10.7MHz ceramic discriminator (for CA3089 etc)	70p				

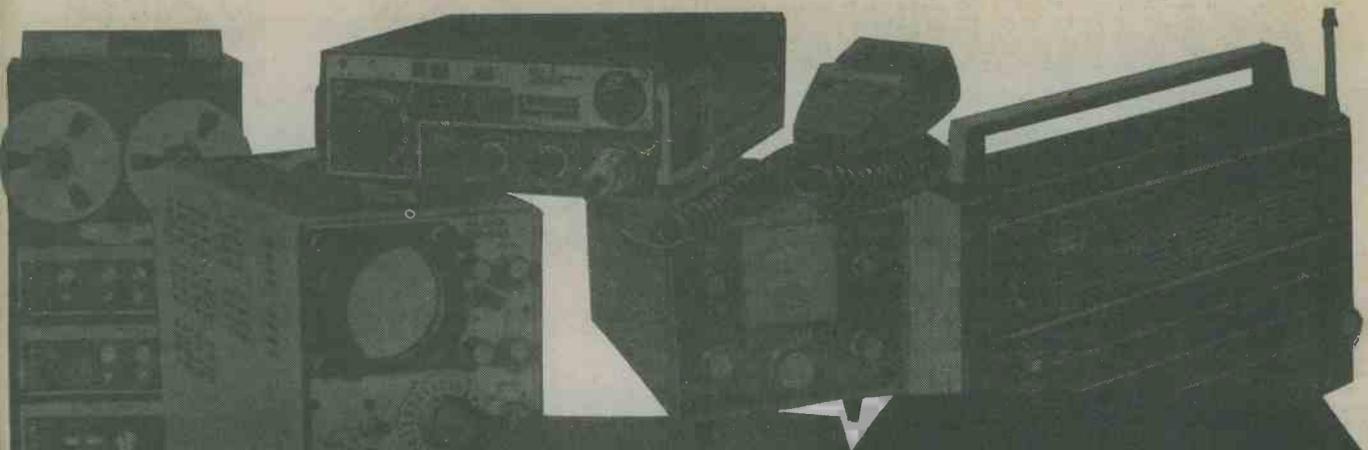IMPORTANT: ALL PRICES SHOWN EXCLUDE VAT - WHICH MUST BE ADDED AT 15% OVERALL. PLEASE NOTE THE REDUCED CMOS/LPSN/TTL RANGES DUE TO CURRENT SUPPLY SHORTAGE



How to make a hobby

The opportunities in electronics, today, and for the future are limitless – throughout the world. Jobs for qualified people are available everywhere at very high salaries. Running your own business, also, in electronics – especially for the servicing of radio, TV and all associated equipment – can make for a varied, interesting and highly remunerative career. There will never be enough specialists to cope with the ever increasing amount of electronic equipment coming on to the world market.


We give modern training courses in all fields of electronics – practical D.I.Y. courses – courses for City & Guilds exams, the Radio Amateur licence and also training for the new Computer Technology. We specialise only in electronics and have over 40 years experience in the subject.

All the training can be carried out in the comfort of your own home and at your own pace.

A tutor is available to whom you can write at any time for advice or help during your work.

and a career.

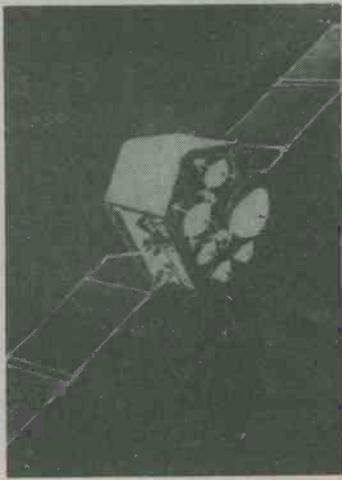- COURSES AVAILABLE
- CITY & GUILDS CERTIFICATES IN TELECOMMUNICATIONS AND ELECTRONICS.
- RADIO AMATEUR LICENCE.
- COMPUTER TECHNOLOGY WITH HOME TRAINING COMPUTER.
- DIGITAL ELECTRONICS.
- BEGINNERS PRACTICAL COURSE.
- RADIO AND TELEVISION SERVICE.
- AND MANY OTHERS.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.



WE ARE AN INTERNATIONAL SCHOOL SPECIALISING IN ELECTRONICS TRAINING ONLY AND HAVE OVER 40 YEARS EXPERIENCE IN THIS SUBJECT.

REC 111

NAME

ADDRESS

.....

Block Caps Please

Post now, without obligation, to:-

BRITISH NATIONAL RADIO and ELECTRONICS SCHOOL P.O. Box 156, Jersey, Channel Islands.

GREENWELD

443G Millbrook Road Southampton SO1 0HX

All prices include VAT at 15% — Just add 30p post

VERO OFFCUTS

Packs of 100 sq ins of good size pieces about 4 x 3" in the following types:

K541 0.1" copper clad **£1.50**
 K542 0.15" copper clad **£1.00**
 K544 0.1" plain **£1.50**

Also pieces 2½x1" — 10/£1.20 100/£9
 17x3½"x0.1" sheets — 10/£16.50

Large range of Standard Veroboard and boxes/cases in stock. Details in catalogue, 45p

SCOOP! Verobox type 2522, unused but has 3 ½" holes in one end and 1 ½" hole the other, so instead of £3.96, we are selling these at **£1.85**

SWITCHES

Push-button banks — 20 types listed on Bargain List No. 8, free with cat (45p) or send SAE. Samples:

W473 3 interlocking 4PCO + 2 independent, **70p**

W481 5 interlocking 4PCO **70p**

Both types supplied with free knobs!

W106 DPCO slide switch 23x15x7mm 10/£1.20; 100/£9

W107 SPCO min slide switch with 2 wires attached. 10/80p 100/£6.

W508 SPCO 5A microswitch with 29mm lever 20x12x6mm **38p** 10/£3.00

W302 Rocker switch on/off 10A white. **22p** 10/£1.80.

W305 Rocker SPCO, centre off, 10A rating, white **30p** 10/£2.30 100/£19.

BUZZERS & MOTORS

Z401 Powerful 6V DC, all metal construction, 50mm dia x 20mm **70p**

Z402 Miniature type, 3-9V, only 22x15x16mm. Very neat **85p**

Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. Only **£1**

Z451 12V high torque motor 30mm dia x 40mm high, with 10mm spindle. **65p**

Z452 6V DC motor with gearbox giving final shaft speed 700 rpm. Spindle is threaded OBA. Ex-equip **£1**

Z453 As above, but 300 rpm and unthreaded spindle **£1**.

TRANSFORMERS

PA 100V line speaker type. Pri tapped 0.625W — 10W in 5 steps. Sec 4 or 8 ohm **£1.75** 10/£15 100/£110

Mains pri, 3 sec windings, 8, 25 and 40V, each at 100mA. A selection of voltages from 8 to 73V is therefore obtainable. 57x48x36mm with flying leads. **£1.50**

Mains pri, sec 40V @ 250mA **£1.75**

AERIALS

X901 Telescopic 8 sections 970mm long extended, 175mm collapsed. Swivel joint. 28A fixing hole in base. **75p**

X904 Ferrite rod 140mm x 9mm LW/MW/coupling coils, each independently moveable **64p**

X905 As above, but LW/coupling coil together on moveable former **55p**

CLOCK CASE BARGAIN

Z472 Oval format, overall size 130x68x87mm deep, with built in stand. Rear panel drilled to accept 4 switches and alarm **60p**

THE AMAZING GREENWELD CATALOGUE

FEATURES INCLUDE:

- 50p Discount Vouchers
 - Quantity prices for bulk buyers
 - Bargain List Supplement
 - Reply Paid Envelope
 - Priority Order Form
 - VAT inclusive prices
- PRICE **30p** + 15p POST

3W AMP MODULE

Ready built and tested, this handy amplifier will prove very useful around the workshop. Just requires 17V ac source (and 8R spkr) as bridge rect and smoothing cap are mounted on the PCB. The 4 transistor circuit provides enough sensitivity for most applications. Supplied complete with circuit diagram and wiring details. Only **£1.75**. Suitable transformer **£2.20**.

LINEAR IC BARGAIN

We have just received a large consignment of popular linear IC's that have failed the manufacturers stringent tests. However, on checking through a few hundred we have found that quite a large proportion tested in a simple oscillator circuit are functional, so are offering them in packs as follows:

TYPE	PACKAGE	%GOOD	QTY	PRICE
702	14DIL	65	25	£1.20
709	8DIL	75	20	£1.20
709	14DIL	50	30	£1.20
710	T099	30	40	£1.20
710	14DIL	30	40	£1.20
720	14DIL	80	20	£1.20
741	T099	40	25	£1.20
748	T099	70	15	£1.20

Connection-data is supplied. One of each pack, **£8.50**

DISC CERAMIC PACK

Amazing variety of values and voltages from a few pF to 2.2uF! 3V to 3kV! 200 **£1** 500 **£2.25** 1000 **£4.00**

DIODE SCOOP!!

We have been fortunate to obtain a large quantity of untested, mostly unmarked glass silicon diodes. Testing a sample batch revealed about 70% useable devices — signal diodes, high voltage rects and zeners may all be included. These are being offered at the incredibly low price of **£1.25/1000** — or a bag of 2500 for **£2.25**. Bag of 10,000 **£8**. Box of 25,000 **£17.50**. Box of 100,000 **£60**.

VU METERS

Voo2 Twin type. 2 meters 40x40mm and driver board, supplied with circuit and connexion data. **£3.50**

Voo3 New type, just in. Twin type moulded in one piece, 80x40mm (No driver board but suitable circuit supplied) **£2.50**

LATEST BOUND VOLUME No. 31 of "Radio & Electronics Constructor"



AUGUST 1977 to JULY 1978

Comprising 768 pages inc. index

PRICE **£5.20 P&P 90p**

BOUND VOLUME No. 27
(August 1973 to July 1974)
Price **£3.00 P&P 90p**

BOUND VOLUME No. 28
(August 1974 to July 1975)
Price **£3.20 P&P 90p**

BOUND VOLUME No. 29
(August 1975 to July 1976)
Price **£3.50 P&P 90p**

BOUND VOLUME No. 30
(August 1976 to July 1977)
Price **£3.70 P&P 90p**

Limited number of these volumes still available.

We regret all earlier volumes are now completely sold out.

Available only from

DATA PUBLICATIONS LTD.,
57 MAIDA VALE, LONDON, W9 1SN

BI-PAK SEMICONDUCTORS

DEPT. RC10, PO Box 6, Ware, Herts. TEL: 0920 3182
 Visit our Shop at: 3 Baldock Street, Ware, Herts. TELEX: 817861

TRANSISTORS

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC126	£0.21	BC148	£0.68	BC550	£0.16	BU105	£1.84	ZTX108	£0.11
AC127	£0.21	BC149	£0.08	BC556	£0.18	BU105/02	£2.24	ZTX109	£0.11
AC128	£0.18	BC157	£0.12	BC557	£0.15	BU204	£1.61	ZTX300	£0.13
AC128K	£0.30	BC159	£0.12	BC558	£0.14	BU205	£1.61	ZTX500	£0.14
AC1304	£0.29	BC167	£0.12	BC559	£0.16	BU208/02	£2.58	2N1613	£0.23
AC131	£0.23	BC168	£0.14	BD115	£0.58	MJE2955	£0.80	2N1889	£0.51
AC141	£0.25	BC169	£0.10	BD116	£0.92	MJ3055	£0.69	2N1890	£0.51
AC141K	£0.38	BC169C	£0.12	BD121	£0.75	MJ3440	£1.04	2N1893	£0.35
AC142	£0.23	BC170	£0.10	BD124	£0.81	MPF102	£0.32	2N1914	£0.86
AC176	£0.21	BC171	£0.10	BD131	£0.40	MPF104	£0.40	2N2148	£0.81
AC176K	£0.30	BC172	£0.10	BD132	£0.40	MPF05	£0.20	2N2160	£1.15
AC179	£0.29	BC173	£0.10	BD133	£0.46	MPSA05	£0.23	2N2192	£0.44
AC180	£0.23	BC173	£0.10	BD135	£0.44	MPSA06	£0.23	2N2193	£0.44
AC180K	£0.32	BC177	£0.18	BD136	£0.40	MPSA55	£0.23	2N2194	£0.44
AC181K	£0.32	BC180	£0.18	BD137	£0.40	MPSA55	£0.23	2N2217	£0.25
AC187	£0.27	BC181	£0.10	BD138	£0.41	OC22	£1.73	2N2218	£0.26
AC187K	£0.32	BC182L	£0.10	BD140	£0.41	OC24	£1.55	2N2218A	£0.23
AC188	£0.21	BC183	£0.10	BD155	£0.92	OC25	£1.15	2N2219	£0.23
AC188K	£0.32	BC183L	£0.10	BD175	£0.89	OC26	£1.15	2N2219A	£0.25
AD112	£0.27	BC184	£0.10	OC28	£0.92	OC28	£0.92	2N2504	£0.23
AD140	£0.69	BC184L	£0.10	OC29	£1.09	OC29	£1.09	2N2904A	£0.24
AD143	£0.86	BC187	£0.23	OC35	£1.03	OC35	£1.03	2N2905	£0.20
AD149	£0.69	BC187L	£0.10	OC36	£1.03	OC36	£1.03	2N2905A	£0.23
AD161	£0.40	BC188	£0.23	OC70	£0.27	OC70	£0.27	2N2905	£0.18
AD162	£0.40	BC188L	£0.10	OC71	£0.17	OC71	£0.17	2N2906A	£0.23
AF124	£0.81	BC189	£0.10	OC72	£1.73	OC72	£1.73	2N2907	£0.23
AF124K	£0.35	BC189L	£0.10	OC73	£1.55	OC73	£1.55	2N2907A	£0.25
AF125	£0.35	BC193	£0.18	OC74	£1.15	OC74	£1.15	2N2966	£0.10
AF126	£0.35	BC207	£0.13	OC75	£1.15	OC75	£1.15	2N2967	£0.10
AF127	£0.35	BC208	£0.13	OC76	£1.15	OC76	£1.15	2N2968	£0.10
AF129	£0.40	BC209	£0.14	OC77	£1.15	OC77	£1.15	2N2969	£0.10
AF186	£0.58	BC212L	£0.10	OC78	£1.15	OC78	£1.15	2N2970	£0.10
AF239	£0.47	BC213	£0.10	OC79	£1.15	OC79	£1.15	2N2971	£0.10
AL102	£1.38	BC213L	£0.10	OC80	£1.15	OC80	£1.15	2N2972	£0.10
AL103	£0.86	BC214	£0.18	OC81	£1.15	OC81	£1.15	2N2973	£0.10
AU104	£1.61	BC215	£0.18	OC82	£1.15	OC82	£1.15	2N2974	£0.10
AU110	£1.61	BC216	£0.18	OC83	£1.15	OC83	£1.15	2N2975	£0.10
AU113	£1.61	BC217	£0.18	OC84	£1.15	OC84	£1.15	2N2976	£0.10
BC107A	£0.09	BC218	£0.18	OC85	£1.15	OC85	£1.15	2N2977	£0.10
BC107B	£0.10	BC219	£0.18	OC86	£1.15	OC86	£1.15	2N2978	£0.10
BC107C	£0.12	BC220	£0.18	OC87	£1.15	OC87	£1.15	2N2979	£0.10
BC108A	£0.09	BC221	£0.18	OC88	£1.15	OC88	£1.15	2N2980	£0.10
BC108B	£0.11	BC222	£0.18	OC89	£1.15	OC89	£1.15	2N2981	£0.10
BC108C	£0.12	BC223	£0.18	OC90	£1.15	OC90	£1.15	2N2982	£0.10
BC109A	£0.09	BC224	£0.18	OC91	£1.15	OC91	£1.15	2N2983	£0.10
BC109B	£0.10	BC225	£0.18	OC92	£1.15	OC92	£1.15	2N2984	£0.10
BC109C	£0.12	BC226	£0.18	OC93	£1.15	OC93	£1.15	2N2985	£0.10
BC147	£0.08	BC227	£0.18	OC94	£1.15	OC94	£1.15	2N2986	£0.10

THYRISTORS

Volts No.	Price
50 THY1A 50	£0.29
100 THY1A 100	£0.32
200 THY1A 200	£0.36
400 THY1A 400	£0.43
600 THY1A 600	£0.51
800 THY1A 800	£0.52
50 THY3A 50	£0.88
100 THY3A 100	£0.34
200 THY3A 200	£0.37
400 THY3A 400	£0.48
600 THY3A 600	£0.57
800 THY3A 800	£0.74
50 THY5A 50	£0.41
100 THY5A 100	£0.51
200 THY5A 200	£0.57
400 THY5A 400	£0.65
600 THY5A 600	£0.79
800 THY5A 800	£0.93
50THY7A 50	£0.55
100 THY7A 100	£0.58
200 THY7A 200	£0.65
400 THY7A 400	£0.71
600 THY7A 600	£0.89
800 THY7A 800	£1.05
100 THY10A 50	£0.58
100 THY10A/100	£0.65
200 THY10A/200	£0.71
400 THY10A/400	£0.89
600 THY10A/600	£1.13
800 THY10A/800	£1.40
50 THY16A 50	£0.62
100 THY16A 100	£0.66
200 THY16A/200	£0.71
400THY16A/400	£0.88
600THY16A/600	£1.03
800THY16A/800	£1.59

SILICON RECTIFIERS

CONTINUED

1.5 Amp	Price
IS015 50v	£0.10
IS021 100v	£0.11
IS021 200v	£0.12
IS023 300v	£0.14
IS025 600v	£0.16
IS027 800v	£0.18
IS029 1000v	£0.23
IS031 1200v	£0.28

3 Amp	Price
IN5400 50v	£0.16
IN5401 100v	£0.17
IN5402 200v	£0.18
IN5404 400v	£0.19
IN5406 600v	£0.24
IN5407 800v	£0.28
IN5408 1000v	£0.34

10 Amp	Price
IS10 50v	£0.21
IS10/100 100v	£0.24
IS10/200 200v	£0.26
IS10/400 400v	£0.40
IS10/600 600v	£0.58
IS10/800 800v	£0.69
IS10/1000 1000v	£0.89
IS10/1200 1200v	£0.79

30 Amp	Price
IS30 50v	£0.64
IS30 100 100v	£0.79
IS30 200 200v	£1.06
IS30 400 400v	£1.43
IS30 600 600v	£2.02
IS30 800 800v	£2.23
IS30 1000 1000v	£2.65
IS30 1200 1200v	£3.31

60 Amp	Price
IS70 50 50v	£0.86
IS70 100 100v	£0.96
IS70 200 200v	£1.38
IS70 400 400v	£2.01
IS70 600 600v	£2.68
IS70 800 800v	£2.87
IS70 1000 1000v	£3.45

SILICON RECTIFIERS

200mA	Price
IS920 50v	£0.07
IS921 100v	£0.08
IS922 150v	£0.09
IS923 200v	£0.10
IS924 300v	£0.11

74 SERIES TTL ICs

Type	Price	Type	Price	Type	Price	Type	Price
7400	£0.10	7426	£0.26	7470	£0.26	74153	£0.71
7401	£0.12	7427	£0.27	7472	£0.23	74154	£0.78
7402	£0.12	7428	£0.29	7473	£0.28	74155	£0.78
7403	£0.12	7430	£0.12	7474	£0.28	74156	£0.89
7404	£0.12	7432	£0.25	7475	£0.33	74174	£0.74
7405	£0.12	7433	£0.34	7476	£0.28	74175	£0.71
7406	£0.25	7437	£0.25	7481	£0.97	74176	£0.86
7407	£0.25	7438	£0.24	7482	£0.78	74177	£0.72
7408	£0.14	7440	£0.12	7483	£0.55	74180	£1.72
7409	£0.14	7441	£0.57	7483	£0.78	74181	£0.68
7410	£0.12	7442	£0.46	7484	£1.01	74182	£0.80
7411	£0.19	7443	£0.80	7485	£0.78	74184	£0.80
7412	£0.17	7444	£0.80	7489	£1.95	74190	£0.78
7413	£0.27	7445	£0.74	7490	£0.36	74191	£0.71
7414	£0.27	7446	£0.89	7491	£0.73	74192	£0.69
7416	£0.26	7447	£0.89	7492	£0.92	74193	£0.68
7417	£0.26	7448	£0.64	7493	£0.34	74194	£0.71
7420	£0.12	7450	£0.12	7494	£0.86	74195	£0.69
7421	£0.23	7451	£0.12	7495	£0.57	74196	£1.20
7422	£0.18	7453	£0.12	7496	£0.57	74197	£1.20
7423	£0.24	7454	£0.12	7497	£0.97	74198	£2.12
7425	£0.21	7460	£0.12	74104	£0.44	74199	£2.12

CMOS ICs

Type	Price	Type	Price	Type	Price	Type	Price
CD4000	£0.16	CD4015	£0.87	CD4026	£1.38	CD4070	£0.19
CD4001	£0.17	CD4016	£0.48	CD4027	£0.57	CD4071	£0.19
CD4002	£0.18	CD4017	£0.86	CD4028	£0.78	CD4072	£0.19
CD4003	£1.05	CD4018	£0.97	CD4029	£0.97	CD4081	£0.10
CD4007	£0.19	CD4019	£0.48	CD4030	£0.55	CD4082	£0.10
CD4008	£1.05	CD4020	£1.03	CD4031	£2.30	CD4050	£1.13
CD4009	£0.51	CD4021	£0.94	CD4035	£1.15	CD4051	£1.09
CD4010	£0.55	CD4022	£1.34	CD4037	£1.09	CD4516	£1.15
CD4011	£0.17	CD4023	£0.17	CD4040	£1.01	CD4518	£1.15
CD4012	£0.18	CD4024	£0.17	CD4041	£0.87	CD4520	£1.13
CD4013	£0.48	CD4025	£0.74	CD4042	£0.87	CD4521	£0.92

LINEAR ICs

Type	Price	Type	Price	Type	Price	Type	Price
CA3011	£0.92	CA3140	£0.80	MC1350	£1.38	709P	£0.29
CA3014	£1.55	LM301	£0.33	MC1352	£1.61	UA710C	£0.46
CA3108	£0.74	LM304	£1.84	MC1469	£3.39	7211B	£0.34
CA3020	£1.95	LM308	£1.15	MC1496	£1.03	UA711C	£0.26
CA3028	£0.92	LM309	£1.72	NE536	£3.05	7211	£0.36
CA3035	£1.61	LM320 5v	£1.72	NE555	£1.09	UA723C	£0.52
CA3036	£1.15	LM320 12v	£1.72	NE556	£0.27	72723	£0.52
CA3042	£1.72	LM320 15v	£1.72	NE556	£0.69	UA741C	£0.27
CA3043	£2.12	LM320 24v	£1.72	NE556	£1.38	72741	£0.27
CA3046	£0.80	LM3900	£0.66	NE566	£1.38	741P	£0.23
CA3052	£1.84	LM3901	£0.97	NE567	£1.95	UA747C	£0.89
CA3054	£1.26						

TRADE COMPONENTS

PAY A VISIT — THOUSANDS MORE ITEMS BELOW WHOLESALE PRICE. CALLERS PAY LESS ON MANY ITEMS AS PRICES INCLUDE POSTAGE. PRICES INCLUDE VAT AND ADDITIONAL DISCOUNT IN LIEU OF GUARANTEE. GOODS SENT AT CUSTOMERS RISKS UNLESS SUFFICIENT ADDED FOR REGISTRATION OR COMPENSATION FEE POST.

OFFERS CORRECT AT 15/8/79 APPLICABLE TO ORDERS RECEIVED DURING SEPTEMBER

VALVE BASES

Printed circuit B7G	7p
Chassis B7-B7G	11p
Shrouded Chassis B7G-B8A	13p
B12A tube. Chassis B9A	13p

Speaker 6" x 4" 5 ohm ideal for car radio	£1.56
4 1/2" diam. 30 Ω	£1.75
2 1/2" diam. 32 or 8 Ω	£1.07

TAG STRIP -6 way 5p	5 x 50pF or 1000 +
9 way 10p Single 2p	300pF trimmers 35p

Car type panel lock and key 65p

Transformer 9V 4A £4.00

Aluminium Knobs for 1/4" shaft. Approx. 5/8" x 7/8" with indicator Pack of 5 95p

BOXES — Grey polystyrene 61 x 112 x 31mm, top secured by 4 self tapping screws 57p clear perspex sliding lid, 46 x 39 x 24 mm 15p.

ABS, ribbed inside 5mm centres for P.C.B., brass corner inserts, screw down lid, 50 x 100 x 25mm orange 65p; 80 x 150 x 50mm black 97p; 109 x 185 x 60mm black £1.52.

DIECAST ALI superior heavy gauge with sealing gasket, approx 6 1/2" x 2 3/8" x 1 3/8" £1.55; 3 1/2" x 2 3/8" x 1 3/8" £1.30.

VARIABLE CAMM PROGRAMMER 10, 12 or 15 pole 2 way, 50VAC motor — series with 1mfd, or 3k 10W or 15W pygmy bulb for mains operation. Ex equipment £4.50.

SWITCHES

Pole	Way	Type	
1	2	Slide	15p
6	2	Slide	24p
2	1	Rotary Mains	28p
2	Alternating	Micro with roller	30p
2	3	Miniature Slide	20p
2	1	Toggle	42p
1	2	Sub-Min Toggle	75p
2	Alternating	2A Mains Push (3/4" hole)	43p
2	Alternating	Slide	15p

S.P.S.T. 10 amp 240v. white rocker switch with neon. 1" square flush panel fitting 60p; 1 pole 2 way 10 amp oblong clip in mains rocker appliance switch 38p

Standard thumb-wheel switch 0-9 in 1248N or B.C.D., or Comp. 1242 also 2p co. £1.20

Standard Lever Key Switch D.P.D.T. locking plus D.P.D.T. and S.P.S.T. Heavy Duty non latching 82p

AUDIO LEADS

3 pin din to open end, 1 1/2yd, twin screened	45p
5 pin din 180° to 2-phonos	70p
3 pole jack plug to tag ends, 4ft	45p

COMPUTER & AUDIO BOARDS/ASSEMBLIES VARYING CONTENTS INCLUDE ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKES, INTEGRATED CIRCUITS, ETC.
3lb for £2.30 7lb for £4.30

1k horizontal preset with knob 10 for 40p	3" Tape Spools 5p
	1" Terry Clips 5p
	12 Volt Solenoid 40p

ENM Ltd. cased 7-digit counter 2 1/4" x 1 1/4" x 1 1/4" approx. 12V d.c. (48 a.c.) or mains £1.10

Auto charger for 12v Nicads, ex-new equipment £5.25

RESISTORS

1-1/2 watt 1 1/2p 10 same value 10p
1 watt 3p 10 same value 20p
1 or 2% 3 times price

RELAYS

RS/Alma reed relay, 1K12v or 3k Ω 18-30v d.c. coil, normally open 45p
12v d.p.c.o. heavy duty octal £1
700Ω, 11-13v Min. Sealed 2 p.c.o. £1.
4 p.c.o. £1.20.

POTS

Wirewound 38p
Log. or Lin., carbon rotary or slide. Single 30p With switch 40p Dual 45p Dual switch 55p 1.5m Edgetype 10 for 40p

Skeleton Presets Slider, horizontal or vertical standard or submin 6p

THERMISTORS and V.D.R.'s

CZ1/2/6/11/14, KR22, KT150, VA1005/6/8/1010/1033/4/7/8/9 1040/1053/5 /1066/7/1074/6/7 / 1082/6/1091/6/7/8 / 1100/3/8/8602. Rod with spot blue/fawn/green.
E299DDP120 / 218 / 224 / 338 / 340 / 350 / 352 / YF020 E220ZZ/02
KR150 All 22p
E23 glass bead 85p
YG150-S534 bead, KB13, E299 DHP230, 116-121 401 (TH7, VA1104, OD10) 35p. R53 Glass £1.20

Miniature 0 to 5mA d.c. meter approx 7/8" diameter £1.25
RS Yellow Wander Plug Box of 12 40p
18 SWG multicore solder 3 1/2p foot
SAPHIRE STYLII. 15 different, dual and single point, current and hard to get types. My mix £2.

BRIAN J. REED

161 ST. JOHNS HILL, BATTERSEA, LONDON SW11 1TO
Open 10 a.m. till 7 p.m. Tuesday to Saturday. VAT receipts on request.
Terms: Payment with order Telephone: 01-223 5016

JAP 4 gang min. sealed tuning condensers 40p

ELECTROLYTICS Many others in stock

Up to 10V	25V	50V	75V	100V	250V	350V	500V
10	6p	7p	7p	10p	13p	15p	26p
25	6p	7p	7p	10p	13p	18p	32p
50	6p	7p	7p	12p	16p	23p	32p
100	7p	8p	13p	15p	24p	26p	—
250	12p	13p	15p	22p	36p	—	£1.10
500	13p	15p	22p	30p	55p	—	£1.48
1000	16p	27p	50p	60p	—	—	£1.05
2000	28p	47p	55p	93p	£1.20	—	—

As total values are too numerous to list, use this price guide to work out your actual requirements 8/20, 10/20, 12/20, 22/50, 47/25. Tub. Tant 24p each 16-32/275V, 100/150V, 100-100/275V 40p 50-50/385V, 2+2/200V non polar, 32-32-50/300V, 20-20-20/350V 0.1+0.1/500V AC 80p 200V, 100-200-60/300V £1.30 100-300-100-16/300V £1.85

RS 100-0-100 micro amp null indicator Approx. 2" x 1 1/2" x 3/4" £1.85

INDICATORS

Bulgin D676 red, takes M.E.S. bulb 38p
12 volt, or Mains neon, red pushfit 23p
R.S. Scale Print, pressure transfer sheet 12p

CAPACITOR GUIDE — maximum 500V Up to .01 ceramic 2p. Up to 0.1 poly etc. 5p. 10 same value 15p. .12 up to .68 poly etc. 8p. Silver mica up to 360pF 10p, then to 2,200pF 13p; then to .01 mfd 21p.

1/750 13p. .01/1000, 8/20, .1/900, .22/900, 4/16, 25/250 AC (600v/DC), 3/600 15p. 5/150, 10/150, 40/150 50p.

Many others and high voltage in stock.

SONNENSCHNEIN/POWERSONIC DRI-FIT RECHARGEABLE SEALED GEL (Lead Antimony) BATTERY, 6V 1 amp.hr. (3 1/2" x 2" x 1 1/4") £2.70
6 amp. hr. (4 1/2" x 2" x 3") £4.25
Ex-equipment, little used.

CONNECTOR STRIP

Belling Lee L1469, 4 way polythene. 9p each

1 1/2 glass fuses 250 mA or 3 amp (box of 12) 20p
Bulgin 5mm Jack plug and switched socket (pair) 40p

Reed Switch 28mm, body length 5p

Aluminium circuit tape, 1/8" x 36 yards—self adhesive. For window alarms, circuits, etc. 95p

TV MAINS DROPPERS

5 assorted multiple units for £75p

100pF air-spaced tuning capacitor £1.30
5 1/4" x 2 1/4" Speaker, ex-equipment 3 ohm 65p

2 Amp Suppression Choke 10p
3 x 2 1/2" x 1 1/2" } PAXOLINE 5 for 35p
4 1/2" x 1 1/2" x 1 1/2" } 10 for 15p

PVC or metal clip on MES bulb Holder 5 for 30p
VALVE RETAINER CLIP, adjustable 5 for 15p

Sub-miniature Transistor Transformer 35p
Valve type output transformer 90p

POT CORES with adjuster LA2508-LA2519 43p per pair

16 Watt Power Amp. Module 35v 1A power required, giving 16 watt RMS into 8 Ω £3.45

REGULATED TAPE MOTOR Grundig 6V approx. 3" x 1 1/2", inc. shock absorbing carrier, or Jap 9V, 1 1/2" diam. £1.05

3.5mm metal stereo plug 30p
Fane 8 ohm 3" sq. heavy duty communications speaker £1.60

RS neg. volt regulator 103, 306-099 (equiv. MPC900) 10A, 100 watt 4-30 volt. Adjustable sort circuit protection. Sacrifice at £2.00

DEAC rechargeable NICAD 450K. Capacity 6V 450 m.a.h. at 10 hour rate. Ex-new equipment £4.15

2.5A r.f. thermo-couple and meter 2 1/4" square £3.86

Wood cased 8-12V buzzer £2.60

"Makaswitch" 1p 10-way wafer 15p

McMurdo 4 or 8 way plug and socket ex-equipment 50p

Mail Order Over £50 deduct 10% Over £100 deduct 20%

ACOS DUST JOCKEY Automatic record cleaner £1.30

Crouzet 30-minute timer-programmer, multi-variable contacts £7.80

Digital count unit. Counts in steps of 1, 2, 5 or 10 with total limit switch (2 x D.I.L. BCD), reed relay remote output. Mains power supply, relay and delay unit. UNUSED. £5.60

Displays on 2 Minitron. 7 segments sold separately.

£1.1, £3.25

RELAY 6 amp changeover. Mains coil 200mA F.S.D. level Meter 1 1/4" x 1 1/4" £1.1, £3.25

100 Electrolytics £3.00
 100 Resistors up to 1W £2.00
 100 Wirewound Resistors £4.50
 Well mixed values and voltages

100 Capacitors £2.50
 100 Resistors up to 1/2W £1.00
 100 Resistors 2-5W £3.00
 100 1% & 2% Resistors £3.50

Mullard +12-0-12V 1A, 4A stabilized, regulated, power supply. September Offer £9.00
 £12.50
 27V 5A Double section bobbin transformer £4.50

50 ohm BNC through connector or round or flanged chassis socket. TNC plug or N plug or through connector 65p each

UK — Postal Orders for same day service. Cheques required — 8 days from a Tuesday banking to ensure clearance. Export banker's draft (sterling) same day service. Foreign currency money orders etc. can lose value and take 4-6 weeks to clear.

250Ω 50 watt + Resistor 40p

SEMICONDUCTORS Full spec. by Mullard etc. Many others in stock

AC126/128/176	16p
ACY20	30p
ACY29	22p
AD161/2 match pr.	85p
ADZ12	£4.00p
AF124/6/7	28p
AF139	23p
AF178/80/81	35p
AF239	35p
ASU27/73	35p
AY110/113	£1.51
BC107/8/9 + A/B/C	8p
BC147/8/9 + A/B/C	5p
BC157/8/9 + A/B/C	5p
BC171B/173	8p
BC178A/B 179B	14p
BC182/184C/LC	5p
BC186/7	23p
BC204	12p
BC212	5p
BC213L/214B/238	13p
BC327/8 337/8	8p
BC547/8 + A/B/C	10p
BC556/7/8/9	11p
BCX32/36	15p
BCY31	5p
BCY40	55p

BCY70/1/2	14p
BCZ11	32p
BD113	57p
BD115	35p
BD116(BRC116T)	86p
BD130Y	£1.50
BD131Z	32p
BD133/5/6/7/8/9	35p
BD137/138 match pr	82p
BD140/142	35p
BD201/2/3/4	86p
BD232/3/4/5/8	45p
BDX77	97p
BD437/438	58p
BF115/167/173	18p
BF178/9	23p
BF180/1/2/3/4/5	18p
BF194/5/6/7	5p
BF194A, 195C	5p
BF258/324	13p
BF262/3	35p
BF336/274	31p
BFS28 Dual Mosfet	£1.15
BF761	40p
BFV10/11 F.E.T	46p
BFV30	£1.15

8FW57/58	21p
8FX12/29/30	23p
8FX84/88.89	20p
8FY50/51	13p
8FY90	50p
BR101	34p
BRV39/56	29p
BSV64	36p
BSV79/80 F.E.T.s	50p
BSV81 Mosfet	75p
8SX20/21/78	16p
BSY40	30p
BSY95A	14p
BU204+Mount Kit	£1.51
BU208	£2.05
ZTX300/341	9p
2N393 (MA393)	35p
2N456A	57p
2N706A	13p
2N918	30p
2N929	16p
2N987	45p
2N1484	£1.15
2N1507/2219	18p

Amp	Volt	8YX10	34p
1	1.600	OSHO1-200	30p
1 1/2	140	Ex Equip	73p
1	100	EC433	20p
0.6	110	Texas	£1.10
5	400	I.R.	48p
2 1/2	100	B40C 3200	58p
3 1/2	100		

BRIDGE RECTIFIERS

8YX10	34p
OSHO1-200	30p
Ex Equip	73p
EC433	20p
Texas	£1.10
I.R.	48p
B40C 3200	58p

RECTIFIERS

Amp	Volt		
M1	68	5p	
1N4004/5/6	4/6/800	8p	
1N4007/BYX94	1250	8p	
BY103	1,500	21p	
SR100	100	9p	
SR400	1,500	10p	
RECS53A	1,250	16p	
LT102	2	30	15p
BYX22-200	3	30	25p
BYX38-300R	2.5	300	48p
BYX38-600	2.5	600	62p
BYX38-900	2.5	900	60p
BYX38-1200	2.5	1,200	65p
BYX49-300R	3	300	35p
BYX49-600	3	600	42p
BYX49-900	3	900	47p
BYX49-1200	3	1,200	60p
BYX48-300R	6	300	47p
8YX48-600	6	600	60p
BYX48-900	6	900	70p
BYX48-1200R	6	1,200	92p
BYX72-150R	10	150	42p
BYX72-300R	10	300	52p
BYX72-500R	10	500	65p
BYX42-300	10	300	36p
1N5401	3	100	13p
1N5402	3	200	15p
MR856	3	600	24p
BYX42-900	10	900	92p
BYX42-1200	10	1,200	£1.07
BYX46-300R*	15	300	£1.19
BYX46-400R*	15	400	£1.75
BYX46-500R*	15	500	£2.00
BYX46-600*	15	600	£2.30
BYX20-200	25	200	72p
BYX52-300	40	300	£2.05
BYX52-1200	40	1,200	£2.90
RAS310AF*	1.25	1,250	48p

OPTO ELECTRONICS

Diodes	Photo transistor
BPX40	57p
BPX42	92p
BPY10	92p
(VOLIAC)	
BPY68	9p
8PY69	14p
8PY77	12p
Wire end neons 4p	2p

L.E.D.'s

.2" Red	9p
TIL209 .125" Red	14p
Green	16p
2" clip	2p

PHOTO SILICON CONTROLLED SWITCH

BPX66 PNP 10 amp £1.15

.3" red 7 segment L.E.D. 14
 D.I.L. 0-9 + D.P. display 1.9v
 19m/a segment, common
 anode 95p
 HP .43 in yellow £1.50
 RS 0.6in. green £2.25
 Minitron 0.3in 3015F
 filament £1.25

CQY11B L.E.D.
 Infra red transmitter £1.15
 H15B Photon coupled isolator
 I.R. diode & NPN Photo-Dar-
 lington amp £1.05
 Data Sheet 10p

2N1613	24p
2N2401	35p
2N2412	27p
2N2483	28p
2N2904/5/6/7/7A	10p
2N3053	16p
2N3055 R.C.A.	60p
2N3133/4062	24p
2N3553	56p
2N4037	39p
2N5484 FET	37p
2N5956	87p

OTHER DIODES

1N916	4p
1N4009	9p
1N4148	17p
BA145	17p
Centercal	29p
BZY61/8A148/OA81	12p
BB103/110 Varicap	24p
BB113 Triple Varicap	43p
BA182	15p
OA5/7/10	17p
BZY88 up to 43 volt	77p
BZX61 11 volt	17p
AA133	10p
BZY96C 10V	34p
BZY95C 33V or 15V	34p

CATALOGUE

38, 11 x 8 ins illustrated sheets, listing approx. 5,250 items, photo printed on day requested, from constantly updated masters, to ensure latest stock position, 75p (refundable with orders) plus 26p a.e.s. or label.

PVC QUALITY TAPE

Lasso 10m x 15mm grey 38p
 33m x 33mm green £1.13p

Trimmer: Post stamp type 3-30pF 16p
 10-80pF 19p
 30-140pF 23p

TRANSFORMERS

Ferromag C core. Screens 95-105-115-125-200-220-240v input output 17v 1/2A x 2 + 24-0-24v 1.04A+20v TmA. These current ratings can be safely exceeded by 50%. £6.00

Cassette Dynamic Micro-
 phone with switch and twin-
 plug £1.80
 Telephone Pickup, sucker
 with lead and 3.5 plug.70p

GARRARD

GCS23T Crystal Stereo
 Cartridge £1.20
 Mono (Stereo compatible)
 Ceramic or crystal £1

THYRISTORS

Amp	Volt		
.40	400	BTX18-200	35p
.40	400	BTX18-300	41p
.240	240	BTX30-200	35p
4	500	40506	80p
1.5	500	BT107	£1.00
6.5	500	BT109-500R/SCR957/BRC4444	£1.14
20	600	BTW92-600RM	£3.40
15	800	BTX95-800R Pulse Modulated	£8.75

PAPER BLOCK CONDENSER

D.I.L. 0-9 + D.P. display 1.9v	87p
0.25MFD 800 volt	87p
1MFD 250 volt	54p
1MFD 400 volt	65p

INTEGRATED CIRCUITS

TBA920 TCA270	£2.00
TAA700	£2.40
TBA800/810	70p
741/7490/7473	25p
uA702/LM3900	53p
709/741	15p
74107/74122	15p
SN76228N	£2.05
SN76131/75110	£1.55
SN76131/ND	£1.40
SN76013N/ND	£1.22
TAD100 AMRF	£1.58
CA3001 R.F. Amp	£1.58
CA3132	£2.22
74151	15p
CD4069	15p
TAA300 1 wt Amp	£1.00
TAA550 Y or G	26p
TAA263/74LS192	70p
TAA320	£1.15
7400/01/06	15p
7402/4/10/20/30	15p
7414/7413N	44p
7438/2/6/32/37	15p
AYS 8300	£1.00
7483/ZN414	26p
CD4013/19	75p
LM3002/20V reg	£1.15
LM1303N	£1.00
CD4040	50p
TBA5500/74S112	£1.80
74154	35p

TV KNOB

Dark grey plastic for recessed shaft (quarter inch) with free shaft extension 8p

CHASSIS SOCKETS

Car Aerial 11p, Coax 8p, 5 pin 180°
 11p, 5 or 6 pin 240° din 8p, speaker
 din switched 13p, 3.5 mm speaker
 7p, stereo 1/2" jack enclosed 20p.

September Offers

SN15809310 for £2.50
 8008MPU £3.50
 40506 5A 500V Thy. 10 for £5.00
 2N5956 10 for £5.00
 74LS00 10 for £1.50
 74LS192 10 for £4.00
 MPC900 - 4 to 30V,
 10A 100 watt regulator £2.00

HANDLES

Rigid light blue nylon 61 1/2" with secret fitting screws 11p

Belling Lee white plastic surface coax outlet box 40p

Miniature Axial Lead Ferrite Choke formers 5 for 13p

RS 10 Turn pot 1% 250 500Ω 1K. £1.70

Copper coated board 18 1/2" x 2 1/2" 40p

Geared Knob 8-1 ratio, 1 1/2" diam., black 93p

KLIPPON 25A 440V TERMINAL BLOCKS Professional leaf spring clamp, twin with clip-over cover 11p
 Strip of 4, 40A 440V 18p

Request Free Catalogue with orders over £10.00

Nixi Tubes 60p
 30pF Beehive Trimmer 10p

Miniature Edge Meters

100uA f.s.d., scaled 0.5. 12V illuminated blue perspex front. 35mm x 14mm	£3.45
200uA level meter, clear front. 10 x 18mm	£1.20

***Avalanche type**

Amp Volt

25	900	BTX94-900	£3.00
25	1200	BTX94-1200	£5.00

Diode Characteristic, Equiv., and -
 Substitution Book 82p

Transistor equivalents and substitution Book 1 38p Book 2 82p
 Chrome Car Radio facia 28p
 Rubber Car Radio gasket 10p
 DLI Pal Delayline 90p
 Relay Socket miniature 2PCO 20p
 28 pin d.i.l. socket low profile Colour EHT Tray 3000/3500 £5.60
 Nylon self-locking, 3 1/2" tie clips 1.5, 10, 22 or 750 µh choke 12p
 0-30, or 0-15, black pvc, 360° dial, silver digits, self adhesive 4 1/2" dia. 13p
 Mullard Semiconductor, Valve & Component Data Book 1976-78 50p

McMurdo PP108 8 way edge plug 12p

Multicore Solder 1kg. 16 or 18 or 20 s.w.g. £5.20
 3 inch 8Ω speaker £1.15

New unmarked, or marked ample lead ex new equipment

ACY17-20	10p	TIC44	17p
ASZ20	10p	2G240	£1.17
ASZ21	35p	2G302	6p
BC186	13p	2G401	6p
BCY30-34	24p	2N711	28p
BCY70/1/2	10p	2N2926	6p
BY126/7	5p	2N598/9	8p
HG1005	12p	2N1091	10p
HG5009	4p	2N1302	10p
HG5079	4p	1N1907	£1.17
L78/9	4p	Germ. diode	2p
M3	12p	2N3055	
OA81	4p	Motorola	36p
OA47	4p	GET120 (AC128	
OA200-2	4p	in 1" sq. heat sink	22p
OC23	27p	GET872	15p
OC200-5	24p	2S3230	34p
C106 THY	28p	TIS43	15p

VAT & POST PAID NO MORE TO ADD — Prices INCLUDE UK VAT and Post/Packing

MINIMUM ORDER £3 OTHERWISE ADD 50% FOR SMALL ORDER HANDLING COSTS (UNDER £1.00 TOTAL ALSO INCLUDING 10p S.A.E.)

ALL ENQUIRIES, ETC., MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE

THE MODERN BOOK CO

PROJECTS IN RADIO AND ELECTRONICS by I. R. Sinclair, Price £2.50

ELECTRONIC PROJECTS IN THE HOME
by O. Bishop Price £2.50

ELECTRONIC PROJECTS IN AUDIO
by R. A. Penfold Price £2.50

OP-AMPS THEIR PRINCIPLES & APPL.
by J. B. Dance Price £2.50

PRINTED CIRCUIT ASSEMBLY
by M. J. Hughes Price £2.10

ELECTRONIC SECURITY DEVICES
by R. A. Penfold Price £1.65

UNDERSTANDING DIGITAL ELECTRONICS
by Texas Inst. Price £4.00

UNDERSTANDING MICRO-PROCESSORS
by Motorola Price £4.30

THE FIRST BK OF MICROCOMPUTERS
by R. Moody Price £3.35

HOW TO BUILD YOUR OWN SOLID STATE OSCILLOSCOPE
by F. G. Rayer Price £1.70

THE OSCILLOSCOPE IN USE
by I. R. Sinclair Price £2.85

AMATEUR RADIO TECHNIQUES
by P. Hawker Price £3.80

THEORY & PRACTICE OF MODEL RADIO CONTROL
by P. Newell Price £4.50

REPAIRING POCKET TRANSISTOR RADIOS
by I. R. Sinclair Price £2.55

MAKING & REPAIRING TRANSISTOR RADIOS
by W. Olivér Price £2.30

WORLD RADIO TV HANDBOOK
by J. M. Frost Price £9.25

PROJECTS IN RADIO & ELECTRONICS
by I. R. Sinclair Price £2.50

ELECTRONIC PROJECTS IN THE HOME
by O. Bishop Price £2.50

SIMPLE CIRCUIT BUILDING
by P. C. Graham Price £2.20

110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR
by R. M. Marston Price £3.20

HAM RADIO
by K. Ulyett Price £5.00

BEGINNER'S GUIDE TO DIGITAL TECHNIQUES
by G. T. Rubarow Price £1.10

UNDERSTANDING SOLID-STATE ELECTRONICS
by Texas Inst. Price £1.80

A SIMPLE GUIDE TO HOME COMPUTERS
by S. Ditlea Price £4.00

HOW TO BUILD A COMPUTER-CONTROLLED ROBOT
by T. Loofbourrow Price £5.30

THE CATHODE-RAY OSCILLOSCOPE & ITS USE
by G. N. Patchett Price £4.00

HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER
by P. J. Guy Price £1.90

A GUIDE TO AMATEUR RADIO
by P. Hawker Price £1.70

RADIO CONSTRUCTION FOR AMATEURS
by R. H. Warring Price £2.80

MAKING TRANSISTOR RADIOS A BEGINNER'S GUIDE
by R. H. Warring Price £2.90

1979 THE RADIO AMATEUR'S H/B
by A. R. R. L. Price £7.86

★ PRICES INCLUDE POSTAGE ★

We have the Finest Selection of English and American Radio Books in the Country
19-21 PRAED STREET (Dept RC) LONDON W2 1NP
Telephone: 01-402 9176

TRANSISTORISED DC TO AC INVERTERS

12v-24v-48v DC input models
110v or 240v AC off load
output models
Square-wave output or
optional filtered models
Frequency 50Hz or 60Hz models
(± 5% typical)



All silicon power transistors
Separate driver and output
transformers
Designed for cool continuous
operation
Aluminium ventilated cased units
DC input fused

12v dc inputs/110v or 240v outputs
50Hz or 60Hz

N12/A — 8" x 6" x 6" 40 watts.....	£18.00
N12/B — 8" x 6" x 6" 60 watts.....	£23.20
N12/C — 8" x 6" x 6" 100 watts.....	£28.10
N12/D — 8" x 6" x 6" 150 watts.....	£34.50
N12/E — 8" x 6" x 6" 200 watts.....	£42.00
N12/F — 8" x 6" x 6" 250 watts.....	£50.60
N12/G — 8" x 6" x 6" 300 watts.....	£58.00
N12/H — 10" x 8" x 6" 400 watts.....	£69.80

Filtered waveform models available at 15% extra.

24v DC inputs/110v or 240v outputs
50Hz or 60Hz

N24/A — 8" x 6" x 6" 40 watts.....	£19.20
N24/B — 8" x 6" x 6" 100 watts.....	£29.00
N24/C — 8" x 6" x 6" 150 watts.....	£36.00
N24/D — 8" x 6" x 6" 200 watts.....	£44.00
N24/E — 8" x 6" x 6" 250 watts.....	£52.50
N24/F — 8" x 6" x 6" 300 watts.....	£60.00
N24/G — 10" x 8" x 6" 400 watts.....	£71.40
N24/H — 10" x 8" x 6" 500 watts.....	£83.00
N24/I — 12" x 8" x 8" 700 watts.....	£101.00
N24/J — 12" x 8" x 8" 1000 watts.....	£150.00

Filtered waveform models available at 15% extra.

48v DC inputs/110v or 240v outputs
50Hz or 60Hz

N48/A — 8" x 6" x 6" 50 watts.....	£20.00
N48/B — 8" x 6" x 6" 100 watts.....	£31.60
N48/C — 8" x 6" x 6" 150 watts.....	£37.00
N48/D — 8" x 6" x 6" 200 watts.....	£45.00
N48/E — 8" x 6" x 6" 260 watts.....	£54.00
N48/F — 8" x 6" x 6" 300 watts.....	£62.00
N48/G — 10" x 8" x 6" 400 watts.....	£73.00
N48/H — 10" x 8" x 8" 500 watts.....	£86.00
N48/I — 12" x 10" x 8" 700 watts.....	£112.00
N48/J — 12" x 10" x 8" 1000 watts.....	£160.00
N48/K — 12" x 10" x 10" 1500 watts.....	£210.00

Filtered waveform models available at 5% extra.

Please add £5.00 carriage per unit U.K. overseas at cost
Delivery 10 to 21 days subject to availability — Cased sizes subject to variations
Callers strictly by appointment — Telephone enquiries 01-748 5778
Business Hours Mon.-Fri. — 9 a.m. to 5 p.m.

ELECTROVANCE

P.O. BOX 191, LONDON SW6 2LS

RADIO AND ELECTRONICS CONSTRUCTOR

STEVENSON

Electronic Components

TTL			
7473	20p	74141	55p
7474	22p	74145	55p
7475	25p	74148	90p
7476	20p	74150	55p
7478	55p	74151	40p
7486	20p	74154	65p
7489	135p	74157	40p
7490	25p	74164	55p
7492	30p	74165	55p
7493	25p	74170	100p
7494	45p	74174	55p
7495	35p	74177	50p
7496	45p	74190	50p
74121	25p	74191	50p
74122	35p	74192	50p
74123	38p	74193	50p
74125	35p	74196	50p
74126	35p	74197	50p
74132	45p	74199	90p

CMOS			
4020	50p	4050	25p
4022	50p	4060	80p
4023	13p	4066	30p
4024	40p	4068	13p
4025	13p	4069	13p
4026	90p	4070	13p
4027	28p	4071	13p
4028	45p	4072	13p
4029	50p	4081	13p
4040	55p	4093	36p
4041	55p	4510	60p
4042	55p	4511	60p
4043	50p	4518	65p
4046	90p	4520	60p
4049	25p	4528	60p

FULL DETAILS IN CATALOGUE!

SKTS



Low profile by Texas

8pin	8p	18pin	14p	24pin	18p
14pin	10p	20pin	16p	28pin	22p
16pin	11p	22pin	17p	40pin	32p

Soldercon pins: 100:50p 1000:370p

PCBS

Size in.	VEROBOARD	VERO
0.1in.	0.15in.	Cutter 80p.
14p	14p	
45p	45p	Pin insertion tool 108p
54p	54p	
64p	64p	
205p	185p	

Single sided pins per 100 40p 40p

Top quality fibre glass copper board. Single sided. Size 203 x 95mm. 60p each.

'Dalo' pens. 75p each.

Five mixed sheets of Alfac. 145p per pack.

OPTO

LED's	0.125in.	0.2in.	each	100+
Red	TIL209	TIL220	9p	7.5p
Green	TIL211	TIL221	13p	12p
Yellow	TIL213	TIL223	13p	12p
Clips	3p	3p		

DISPLAYS

DL704	0.3 in CC	130p	120p
DL707	0.3 in CA	130p	120p
FND500	0.5 in CC	100p	80p

RESISTORS

Carbon film resistors. High stability, low noise 5%.

E12 series. 4.7 ohms to 10M. Any mix: each 100+ 1000+

0.25W	1p	0.9p	0.8p
0.5W	1.5p	1.2p	1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £7.50. 0.25W £5.70.

METAL FILM RESISTORS

Very high stability, low noise rated at 1/2W 1%. Available from 51ohms to 330k in E24 series. Any mix:

0.25W	each	100+	1000+
	4p	3.5p	3.2p



PLEASE WRITE FOR YOUR FREE COPY OF OUR NEW 80 PAGE CATALOGUE OF COMPONENTS. CONTAINS OVER 2500 STOCK ITEMS.

TRANSISTORS

AC127	17p	BCY72	14p	ZTX500	16p
AC128	16p	BD131	35p	2N697	12p
AC176	16p	BD132	35p	2N3053	18p
AD161	38p	BD139	35p	2N3054	50p
AD162	38p	BD140	35p	2N3055	50p
BC107	8p	BFY50	15p	2N3442	135p
BC108	8p	BFY51	15p	2N3702	8p
BC108C	10p	BFY52	15p	2N3703	8p
BC109	8p	MJ2955	98p	2N3704	8p
BC109C	10p	MPSA06	20p	2N3705	9p
BC147	7p	MPSA56	20p	2N3706	9p
BC148	7p	TIP29C	60p	2N3707	9p
BC177	14p	TIP30C	70p	2N3708	8p
BC178	14p	TIP31C	65p	2N3819	15p
BC179	14p	TIP32C	80p	2N3820	44p
BC182	10p	TIP2955	65p	2N3904	8p
BC182L	10p	TIP3055	55p	2N3906	8p
BC184	10p	ZTX107	14p	2N4058	12p
BC184L	10p	ZTX108	14p	2N4547	32p
BC212	10p	ZTX300	16p	2N4549	32p
BC212L	10p			2N5777	50p

DIODES

1N914	3p	1N4006	6p
1N4001	4p	1N5401	13p
1N4002	4p	BZY88 ser	8p
1N4148	-£1.40.100.£11'1000		

LINEAR

THIS IS ONLY A SELECTION!

LM301AN	26p	NE531	98p
LM308	60p	NE555	23p
LM318N	75p	NE567	100p
LM324	45p	RC4136	100p
LM339	45p	SN76477	230p
LM378	230p	SN8000	70p
LM379S	410p	TA810S	100p
LM380	75p	TA1022	620p
LM3900	50p	TL081	45p
LM3909	65p	TL084	125p
LM3911	100p	ZN414	80p
MC1458	32p	ZN425E	39p
MM57160	590p	ZN1034E	200p

CAPACITORS

TANTALUM BEAD

0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V	each	8p
4.7, 6.8, 10uF @ 25V		13p
22 @ 16V, 47 @ 6V, 100 @ 3V		16p

MYLAR FILM

0.001, 0.01, 0.022, 0.032, 0.047, 0.068, 0.1	3p
	4p

POLYESTER

Mullard C280 series

0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1	5p
0.15, 0.22	7p
0.33, 0.47	10p
0.68	14p
1.0uF	17p

CERAMIC

Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF

RADIAL LEAD ELECTROLYTIC

63V 0.47 1.0 2.2 4.7 10	5p
	7p
	13p
	20p
	23p
	47p
	100p
	220p
	330p
	470p
	1000p

CONNECTORS

JACK PLUGS AND SOCKETS

2.5mm	9p	13p	7p
3.5mm	9p	14p	8p
Standard	16p	30p	15p
Stereo	23p	36p	18p

DIN PLUGS AND SOCKETS

2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p

1mm PLUGS AND SOCKETS

Suitable for low voltage circuits, Red & black. Plugs: 6p each Sockets: 7p each.

4mm PLUGS AND SOCKETS

Available in blue, black, green, brown, red, white and yellow. Plugs: 11p each Sockets: 12p each

PHONO PLUGS AND SOCKETS

Insulated plug in red or black	9p
Screened plug	13p
Single socket	7p
Double socket	10p

LOUDSPEAKERS

56mm dia. 8ohms. 70p 64mm dia. 64ohms. 75p
64mm dia. 8ohms. 75p 70mm dia. 8ohms. 100p

Magnetic earpiece including 2.5 or 3.5mm plug. 15p each
Crystal earpiece including 3.5mm plug. 30p each

TRANSFORMERS

All 240V Primary.

0 - 6, 0 - 6 @ 0.5A or 0 - 9, 0 - 9 @ 0.4A	175p
0 - 12, 0 - 12 @ 0.5A or 0 - 15, 0 - 15 @ 0.4A	235p
0 - 9, 0 - 9 @ 1.2A or 0 - 12, 0 - 12 @ 1A	345p
0 - 12 - 15 - 20 - 24 - 30V @ 1.5A.	455p
0 - 20 - 25 - 33 - 40 - 50V @ 1A.	455p
0 - 20 - 25 - 33 - 40 - 50V @ 2A.	585p
0 - 20 - 25 - 33 - 40 - 50V @ 3A.	715p

Miniature type 6 - 0 - 6, 9 - 0 - 9, 12 - 0 - 12 @ 100mA. 95p

SOLDERING IRONS

ANTEX X25 (25W) or ANTEX CX (17W) 390p each
Reel of solder (39.6M) 240p each

POTENTIOMETERS

Single gang Log or Lin 5K - 2M2 28p each
Dual gang Log or Lin 5K - 2M2 80p each
Presets, sub min. type hor. oververt. 100Ω - 2M2 6p each

CONTROL KNOBS

Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow and black. 14p



SWITCHES

Subminiature toggle. SPDT 70p. DPDT 80p.
Standard toggle. SPST 34p. DPDT 48p.

Slide switches (DPDT) miniature or standard 15p.
Push to make switch. 15p. Push to break switch. 20p.
Wavechange switches: 1P12W, 2P6W, 3P4W, 4P3W. 43p



BOXES

Folded construction complete with screws.

3 x 2 x 1	52p	4 x 3 x 2	70p	6 x 4 x 3	95p
4 x 3 x 2	64p	6 x 4 x 2	77p	8 x 6 x 2	125p



We now offer one of the widest ranges of components at the most competitive prices in the UK. See catalogue for full details. We welcome callers at our shop in College Road, Bromley, from Mon - Sat, 9am - 6pm (8pm on Weds. and Fridays). Special offers always available.

We also provide an express telephone order service. Orders received before 5pm are shipped same day. Contact our sales office now with your requirements.

TÉL: 01-464 2951/5770

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.



BARCLAYCARD & ACCESS WELCOME.

ORDERS DESPATCHED BY RETURN POST

Mail orders to: STEVENSON (Dept RE)

76 College Road, Bromley, Kent BR1 1DE.

ALL PRICES INCLUDE 15% V.A.T.

APEL POWER SUPPLIES

STABILIZED POWER SUPPLIES WITH ELECTRONIC SHORT CIRCUIT PROTECTION



AL.212 P

£14.75

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	12.6 V dc
OUTPUT CURRENT MAX	2.5 Amp
LOAD REGULATION	< 0.3% 0-2.2 Amp
RIPPLE	< 5mV 2.2 Amp
DIMENSIONS (mm)	W140 x H90 x D140
WEIGHT	1,490 Kg.



AL.315 P

£29.50

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	1.7-15 V dc
LOAD REGULATION	< 0.2% 0-2.8 Amp
DIMENSIONS (mm)	W140 x H90 x D155
RIPPLE	3mV 2.8 Amp
WEIGHT	2,330 Kg.



AL.330 P

£46.50

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	3.4-30 V dc
OUTPUT CURRENT RANGE MAX	3 Amp
LOAD REGULATION	< 5% 0-2.8 Amp
RIPPLE	10mV 2.8 Amp
DIMENSIONS (mm)	W270 x H90 x D155
WEIGHT	4,250 Kg.

STOCKISTS

Alpha Sound Service,
50 Stuart Road, Waterloo, Liverpool L22 4QT.
England.

Anson Electronics,
1133 Hessle High Road, Hull, England.

Amateur Radio Shop,
13 Chapel Hill, Huddersfield, HD1 3ED.
England.

Brent Electronics,
Seaview Street, Cleethorpes,
Lincolnshire, England.

J. Birkett,
26 The Strait, Lincoln, England.

Bradford Consultants Limited,
25 Regent Parade, Harrogate,
Yorkshire, England.

F. Brown & Co. Ltd.,
44/46 George IV Bridge Street,
Edinburgh, Scotland.

N. R. Bardwell Limited,
Sellers Street, Sheffield, England.

Casey Brothers,
235 Boundary Road,
"Saint Helens",
Lancashire, England.

Electronic Services Limited,
33 City Arcade, Coventry CU11 HX, England.

A. Fanthorpe Limited,
6 Hepworth Arcade, Silver Street,
Hull, England.

G. W. M. Radio,
Portland Road, Worthing, Sussex.

Leeds Amateur Radio,
27 Cookridge Street,
Leeds LS2 3AG, England.

Target Electric Limited
16 Cherry Lane, Bristol, England.

New Cross Radio,
6 Oldham Road, Manchester,
England.

Progressive Radio,
93 Dale Street, Liverpool L2 2JD.
England.

R. E. Pitt Electrical Services Limited,
60/64 Bath Buildings, Mont Pelier,
Bristol, England.

Peats Electronics,
Parnell Street, Dublin.

R. F. Potts,
68 Bobbington Lane, Derby, England.

Brian A. Pearson Limited,
66 Moncur Street, Glasgow, Scotland.

R M E Supplies Limited,
143 Stockwell Street, Glasgow, Scotland.

Stephan James Limited,
Warrington Road, Leigh, Lancashire.

Stewarts Radio,
4 Chance Street, Blackpool, England.

The Radio Shop,
16 Cherry Lane, Bristol BS 3NG,
England.

Q. C. Trading,
1 St. Michaels Terrace, Woodgreen M22 4FT,
England.

AL.1 P5



£78.00

INPUT VOLTAGE	220 \pm 10% 50 Hz
OUTPUT VOLTAGE RANGE	1 \pm 15 V dc
OUTPUT CURRENT MAX	5 Amp
LOAD REGULATION	< 0.1% 0-45 Amp
RIPPLE	< 2mV 4.5 Amp
DIMENSIONS (mm)	W210 x H155 x D250
WEIGHT	5,100 Kg.

AL.212 PS



£18.00

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	12.6 V dc
OUTPUT CURRENT MAX	2.5 Amp
LOAD REGULATION	< 0.3% 0-2.2 Amp
RIPPLE	< 5mV 2.2 Amp
DIMENSIONS (mm)	W140 x H90 x D140
WEIGHT	1,490 Kg.
AMPEROMETER	

AL.315 P2



£54.00

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	\pm 1.7 \pm 15 V dc
OUTPUT CURRENT RANGE MAX	3 Amp
LOAD REGULATION	< 0.2% 0-2.8 Amp
RIPPLE	< 3mV 2.8 Amp
DIMENSIONS (mm)	W270 x H90 x D155
WEIGHT	4,140 Kg.

Stan Willets Limited,
37 High Street, West Bromwich.

M/S Waltons,
55a Worcester Street,
Wolverhampton WV2 4LL, England.




Distributed in the UK.
and Ireland by:

PEAT'S WHOLESALE LTD.

Chapel Lane, Parnell St, Dublin 1, Ireland.

PHONE 741746-740678-722845. TELEX 31787.

<p>MOTORS 1.5-6VDC Model Motors 22p. Sub. Min. 'Big Inch' 115VAC 3 rpm Motors 32p. 12VDC 5 Pole Model Motors 37p. 8 track 12V Replacement Motors 55p. Cassette Motors 5-8VDC ex. equip. 70p. Geared Mains Motors (240V) 2.5 rpm 75p. 115VAC 4 rpm Geared Motors 95p.</p>	<p>JUMPER TEST LEAD SETS 10 pairs of leads with various coloured croc clips each end (20 clips) 90p per set.</p>	<p>PANEL METERS Ferranti 0-600VAC 3.5" square £2.95. Japanese type 60 x 47 x 33mm clear plastic type; 50 micro, 100 micro, 1Ma, 2 amp, 25 volts, 300 VAC, 'S', 'VU', all £5.25 each. Larger type 110 x 82 x 35mm; 50 micro, 100 micro £6.35 each.</p>	<p>AEROSOL SERVICE AIDS, SERVISOL Switch Cleaner 226gm 60p. Freezer 226gm 70p. Silicone Grease 226gm 70p. Foam Cleanser 370gm 60p. Plastic Seal 145gm 60p. Excel Polish 240gm 47p. Aero Klene 170gm 55p. Aero Duster 200gm 70p.</p>	<p>TOOLS SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.99 (spare nozzles 69p each). Antex hest shunts 13p Good Quality snub nosed pliers, insulated handles, 5" £1.45. Antex Model C 15 watt soldering irons, 240VAC £3.95 Antex Model CX 17 watt soldering irons, 240VAC £3.95. Antex Model X25 25 watt soldering irons, 240VAC £3.95. Antex ST3 iron stands, suits all above models £1.65. Antex hest shunts 12p each. Servisol Solder Mop 50p each. Neon Tester Screwdrivers 8" long 43p each. Mlyarna IC test clips 16 pin £1.95.</p>
<p>SEMICONDUCTORS C106D 400V 2.5A SCR 20p. 2N5062 100V 800mA SCR 18p. BX504 Opto Isolator 25p. CA3130 95p. TBA800 50p. 741 22p. 741S 35p. 723 35p. NE555 24p. LM3400 40p. AD161/2 70p. 2N3055 38p. 2N414 75p. BD238 28p. BD438 28p. IN4005 10 for 35p. TIL305 alpha numeric displays £2.50. MAN3A 3mm LED displays 50p. LEDs.0 2" clear 15p, green 12p, red 10p.</p>	<p>TRANSFORMERS All 240VAC Primary (postage per transformer is shown after price). MINIATURE RANGE: 6-0-6V 100mA, 9-0-9V 75mA and 12-0-12V 50mA all 79p each (15p). 12-0-12V 100mA 99p (15p). 0-6V 0-6V, 280mA £1.20 (20p). 0-4-6-9V 200mA these have no mounting bracket, 70p (15p). 12V 500mA 99p (22p). 12V 2 amp £2.75 (45p). 15-0-15V 3 amp Transformer at £2.85 (54p). 30-0-30V 1 amp £2.85 (54p). 20-0-20V 2 amp £3.65 (54p). 0-12-15-20-24-30V 2 amp £4.75 (54p). 20V 2.5 amp £2.45 (54p).</p>	<p>CAR STEREO SPEAKERS Shelf mounting in black plastic pods with 5" 5 watt speaker available in 4 or 8 ohms only £3.95 per pair.</p>	<p>SURPLUS BOARDS No. 1. This has at least 11 C106 (50V 2.5A) plastic SCR's, one relay a unijunction transistor and tantalum capacitors £1.95. No. 2 I.F. Boards, these are a complete I.F. board assembly made for car radios, 465Khz, full set of I.F.'s and oscillator coils, trimmers etc., 40p each. No. 3 Lamp flasher board, suitable for low load 240VAC applications, approx. 1 flash per second but can be varied via preset pot. 38p each.</p>	<p>SWITCHES Sub. miniature toggles: SPST (8 x 5 x 7mm) 52p. DPT (8 x 7 x 7mm) 62p. DPT centre off 12 x 11 x 9mm 77p. PUSH SWITCHES, 16 x 6mm, red top, push to break version (black top) 16p each. SLIDE SWITCHES, all DPDT; 15 x 8 x 12mm 12p, 16 x 11 x 9 12p, 22 x 13 x 8mm 12p, 22 x 13 x 8mm centre off 13p. Multipole slider, double action 12 tags 29 x 9 x 11mm 24p.</p>
<p>PROJECT BOXES Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 54p. 95 x 71 x 35mm 65p. 115 x 95 x 37mm 75p.</p>	<p>TRIAC/XENON PULSE TRANSFORMERS 1:1 (gpo style) 30p. 1:1 plus 1 sub. min. pcb mounting type 60p each.</p>	<p>MURATA MA401 40KHz Transducers. Rec./Sender £3.50 pair.</p>	<p>POWER SUPPLIES SWITCHED TYPE, plugs into 13 amp socket, has 3-4.5-6-7.5 and 9 volt DC out at either 100- or 400mA, switchable £3.45. HC244R STABILISED SUPPLY, 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £3.50.</p>	<p>MICRO SWITCHES Standard button operated 28 x 25 x 8mm make or break, new 15p each. Roller operated version of the latter, New 19p each. Light action micro, 3 amp make or break 35 x 20 x 7mm, 12p each. Cherry plunger operated micro, 2 normally open, 2 normally closed, plunger 20mm long (40 x 30 x 18mm) 25p each.</p>
<p>VERO POTTING BOXES 49 x 71 x 24mm, available in black or white with lid and 4 screws 43p each.</p>	<p>MICROPHONES Min. tie pin. Omni, uses deaf aid battery (supplied), £4.95. ECM105 low cost condenser, Omni, 600 ohms, on/off switch, standard jack plug, £2.95. EM507 Condenser, uni, 600 ohms, 30-18KHz., highly polished metal body £7.96p. DYNAMIC stick microphone dual imp., 600 ohms or 20K, 70-17KHz., attractive black metal body £7.75p. EM506 dual impedance condenser microphone 600 ohms or 50K, heavy chrome copper body, £12.95. DYNAMIC P.A. Microphone mobile radio etc., with thumb switch 50K imp., £3.75. CASSETTE replacement microphone with 2.5/3.5 plugs £1.35. INSERT Crystal replacement 35X10mm 40p. GRUNDIG electric inserts with FET preamp, 3-6VDC operation £1.00.</p>	<p>ELECTRICAL ITEMS 13 amp 3 pin plugs plastic 27p, rubber 62p, 13 amp rubber extension sockets 42p, 12 way flexible terminal blocks; 2 amp 20p, 5 amp 24p, 10 amp 33p, 15 amp 47p. Standard batten (BC lampholders 27p).</p>	<p>AMPHENOL CONNECTORS (PL259)-PLUGS 47p. Chassis sockets 42p. Elbows PL259/SO239 90p. Double in line male connector (2XPL259) 65p. Plug reducers 13p. PL259 Dummy load, 52 ohms 1 watt with indicator bulb 95p.</p>	<p>ROCKER SWITCHES 2 amp SPST, single nut mounting, various colours (red, green, white, blue, yellow, black) 19p each. 250VAC 6amp rocker (all white) 21 x 15 x 13mm 17p each.</p>
<p>VERO 'HAND HELD BOX' White ABS, 2.4" x 3.7" tapered, with screws 68p each.</p>	<p>LIGHT DIMMER 240VAC 800 watts max., wall mounting, has built in photo cell for automatic switch on when dark £4.50</p>	<p>PUSH BUTTON TV TUNERS UHF, not varicap, transistorised new £2.25</p>	<p>BUZZERS MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, four voltage types available, 6-9-12 or 24VDC, 80p each. LOUD 12VDC BUZZER, Cream plastic case, 50mm diam. x 30mm high 63p. GPO OPEN TYPE BUZZER, adjustable works 6-12VDC 27p. 12VDC siren, all metal rotary type, high pitched wall, £7.50p.</p>	<p>TAPE HEADS Mono cassette £1.75. Stereo cassette £3.90. Standard 8 track stereo £1.95. BSR MN1330 1/2 track 50p. BSR SRP9U 1/2 track £1.95. TD10 tape head assembly — 2 heads both 1/2 track R/P with built in erase, mounted on bracket £1.20.</p>
<p>MULTIMETERS NH55 2,000 o.p.v. IKV AC/DC. 100ma DC current, 2 resistance ranges to 1meg. £5.95. MODEL 72606 20,000 opv 1,000 volts AC/DC., 250ma DC current, resistance 3 ranges to 3meg, dimensions 127 x 90 x 32mm, mirror scale £11.75p. HANSEN AT210 100,000 opv 1.2KV AC/DC., 12 amps AC/DC current, resistance to 200 meg in 4 ranges, capacitance 200pf-0.2mfd, 1,00pf-1mfd., decibel range, internal safety fuse, dimensions 160 x 105 x 50mm, an excellent meter, £34.50p.</p>	<p>RIBBON CABLE 8 way single strand miniature 22p per metre.</p>	<p>TELEPHONE PICK UP COIL Sucker type with lead and 3.5mm plug 62p.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.e. for new illustrated lists.</p>	<p>STEREO HEADPHONES 8 ohms adjustable headband with lead and stereo jack, £2.95. CAR AERIAL 5 section telescopic, wing mounting with 2 pull up keys £1.35.</p>
<p>MORSE KEYS Beginners practice key £1.05. All metal fully adjustable type. £2.60.</p>	<p>SPEAKERS 5" Round 8 ohms 5 watts £1.35. 6" round 6 watt 8 ohms with cambric surround £2.75. Elac 8" 8 ohm long throw speaker, 18 watts twin cone £4.75. Mid-Range 5" speaker 850-7Khz 20 watts £1.45.</p>	<p>RELAYS Clare Elliot sub. min. sealed relay 10 x 10mm 2 pole C/O. 1,250 ohm coil, new 75p. Miniature encapsulated reed relay U.1 matrix mounting, single pole make, operates on 12VDC 50p each. Continental series, sealed plastic case relays, 24VDC 3pole change over 5 amp contacts, new 65p. Printed circuit Mtg., Reed relay, single make, 20mm x 5mm, 6-9VDC, coil, 33p each. Metal Cased Reed Relay, 50 x 45 x 17mm, has 4 heavy duty make reed inserts, operates on 12VDC 35p each.</p>	<p>PROGRESSIVE RADIO 31 CHEAPSIDE, LIVERPOOL 2. ALL ORDERS DESPATCHED BY RETURN POST</p>	<p>STEREO HEADPHONES 8 ohms adjustable headband with lead and stereo jack, £2.95. CAR AERIAL 5 section telescopic, wing mounting with 2 pull up keys £1.35.</p>
<p>MINIATURE LEVEL METERS 1 Centre Zero 17 x 17mm 75p. 2 (scaled 0-10) 28 x 25mm 75p. 3 Grundig 40 x 27mm £1.25.</p>	<p>INTERCOM UNITS (can be used as baby alarm) supplied with 60' cable, with call button, 2 station model £5.25, 3 station model £7.25.</p>	<p>DALO 33PC Etch Resist printed circuit maker pen, with spare tip, 79p.</p>	<p>PROGRESSIVE RADIO 31 CHEAPSIDE, LIVERPOOL 2. ALL ORDERS DESPATCHED BY RETURN POST</p>	<p>STEREO HEADPHONES 8 ohms adjustable headband with lead and stereo jack, £2.95. CAR AERIAL 5 section telescopic, wing mounting with 2 pull up keys £1.35.</p>

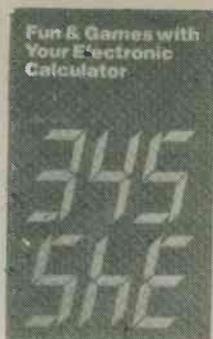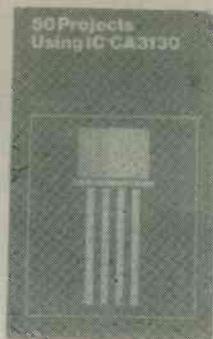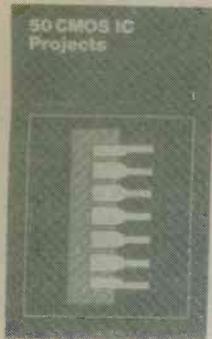

DIRECT READER SERVICE RADIO & ELECTRONICS BOOKS

- | | | | |
|---|-------|--|-------|
| 17. Solid State Power Supply Handbook | 85p | 35. Fun and Games with your Electronic Calculator | 75p |
| 18. 50 Projects Using IC CA3130 | 95p | 36. 50 (FET) Field Effect Transistor Projects | 1.25p |
| 19. 50 CMOS IC Projects | 95p | 37. 50 Simple L.E.D. Circuits | 75p |
| 20. A Practical Introduction to Digital IC's | 95p | 38. How to Make Walkie-Talkies | 1.25p |
| 21. How to Build Advanced Short Wave Receivers | 1.20p | 39. IC 555 Projects | 1.45p |
| 22. Beginners Guide to Building Electronic Projects | 1.25p | 40. Projects in Opto-Electronics | 1.25p |
| 23. Essential Theory for the Electronics Hobbyist | 1.25p | 41. Radio Circuits Using IC's | 1.35p |
| 24. Constructors Manual of Electronic Circuits for the Home | 50p | 42. Mobile Discotheque Handbook | 1.35p |
| 25. 79 Electronic Novelty Circuits | 75p | 43. Electronic Projects for Beginners | 1.35p |
| 26. 52 Projects Using IC741 | 95p | 44. Popular Electronic Projects | 1.45p |
| 27. How to Build Your Own Electronic and Quartz Controlled Watches & Clocks | 85p | 45. IC LM3900 Projects | 1.35p |
| 28. Two Transistor Electronic Projects | 85p | 46. Electronic Music and Creative Tape Recording | 1.25p |
| 29. How to Build Your Own Metal and Treasure Locators | 1.00p | 47. Practical Electronic Calculations and Formulae | 2.25p |
| 30. Electronic Calculator Users Handbook | 95p | 48. Radio Stations Guide | 1.45p |
| 31. Practical Repair and Renovation of Colour TVs (Reprinting) | 95p | 49. Electronic Security Devices | 1.45p |
| 32. Handbook of IC Audio Preamplifier and Power Amplifier Construction | 95p | 50. How to Build Your Own Solid State Oscilloscope | 1.50 |
| 33. 50 Circuits Using Germanium, Silicon and Zener Diodes | 75p | 51. 50 Circuits Using 7400 Series IC's | 1.45p |
| 34. 50 Projects Using Relays, SCR's and TRIACS | 1.10p | 52. Second Book of CMOS IC Projects | 1.50p |
| | | 53. Practical Construction of Pre-Amps, Tone Controls, Fitters & Attenuators | 1.45p |
| | | 54. Beginners Guide to Digital Techniques | 95p |

POSTAGE: 20p PER BOOK. IF MORE THAN 3 BOOKS ORDERED: 10p PER BOOK

To: Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please send me within 21 days copy/copies

..... No.

I enclose Postal Order/Cheque for £


Name

Address

(Block Letters Please)

(We regret this offer is only available to readers in the U.K.)

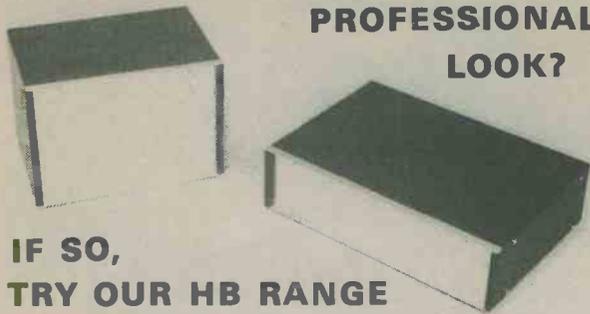DO YOUR PROJECTS LACK THE PROFESSIONAL LOOK?



**IF SO,
TRY OUR HB RANGE**

Instrument cases to give any project a professional look. The four separate top, bottom and end panels are made of black p.v.c. coated steel. Front panel and top and bottom trim are satin anodised aluminium for a neat finish; back panel is in plain aluminium. The whole case, including screws, comes in a flat package and may be assembled in minutes.

DIMENSIONS IN INCHES


Model	Width	Depth	Height	Price
HB1	9	6	3	£4.87
HB2	9	6	4½	£5.27
HB3	9	6	6	£5.63
HB4	12	8	3	£5.98
HB5	12	8	4½	£6.80
HB6	12	8	6	£7.26

ALUMINIUM BOXES


Aluminium box with lid and screws.

Model	Length	Width	Height	Price
AL1	3	2	1	52p
AL2	4	3	1½	62p
AL3	4	3	2	72p
AL4	6	4	2	81p
AL5	6	4	3	94p
AL6	8	6	2	£1.27
AL7	8	6	3	£1.43

(Dimensions in inches)

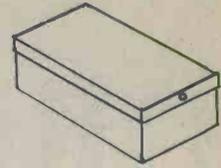

INSTRUMENT CASES

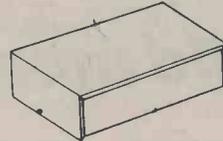

BC Range consists of black P.V.C. coated steel top cover with bevelled front edge, u-shaped aluminium chassis and two fixing screws.

Model	Length	Width	Height	Price
BC1	6	4½	2	£1.61
BC2	6	4	3½	£1.74
BC3	8	5½	2½	£1.99
BC4	10	6½	3	£2.60

(Dimensions in inches)

ELECTROLYTICS

Axial		Radial	
1/25v	4p	1/50v	4p
10/25v	4p	10/50v	4p
22/16v	4p	22/25v	4p
100/10v	5p	33/63v	5p
100/16v	6p	47/16v	5p
220/25v	7p	100/35v	6p
330/25v	8p	220/16v	6p
470/6.3v	8p	220/63v	8p
470/16v	8p	330/25v	8p
1000/16v	16p	470/6.3v	8p
1500/25v	20p	470/16v	8p
2200/10v	20p	1000/25v	16p
3300/16v	25p	1000/35v	20p
4700/10v	30p		
15000µF 10v CAN			Price: 50p

LINEAR I.C.s

LM741	18p	SN76660N	75p
TAA350	£1.00	SN76013	£1.20
TBA120A	50p	SN76023N	£1.20
TBA820	80p	SN76033N	£1.20
T706 BPC		SN76110N	75p
=TBA641	£1.00	SN76131N	£1.30

TRANSISTORS

AD161/2 MP	80p	BC183A	8p	BF194	8p
8C107	8p	BC207B	10p	BF195	8p
8C108A	8p	BC212L	6p	BF198	10p
BC148	6p	BC213LB	6p	BF200	13p
8C149C	7p	BC308	10p	BFY60	13p
8C149S	8p	BC338	8p	BU208	90p
BC171B	8p	BC547	10p	TIP32B	25p
BC172B	7p	BD183	70p	2N2906	10p
BC182LB	8p	BF137	10p	2N3055	65p

DIODES

BZY 88C 6v2	5p	BZY 88C 20v	5p
BZY 83C 6v2	5p	BZY 88C 22v	5p
BZY 88C 7v5	5p	BZY 79C 68v	5p
BZX 83C 7v5	5p	1N914	3p
BZY 88C 8v2	5p	1N4148	2p
BZX 79C 9v1	5p	1N4150	2p
BZY 88C 10v	5p	1N4004	4p
BZY 88C 15v	5p	1N4005	5p
0A91	3p		

HORIZONTAL SUB-MIN PRESETS
100 ohms, 1k, 10k, 470 ohms, 4k7, 22k, 47k.
Price: 4p each

TANTALUM BEAD CAPACITORS

.22/35v	6p	10/16v	8p
.33/35v	6p	15/16v	8p
.47/35v	6p	22/6.3v	8p
6.8/35v	6p	47/6.3v	8p

TTL

7401	8p	7438	25p	74107	16p
7402	8p	7441	25p	74122	25p
7404	9p	7442	34p	74123	42p
7405	9p	7447	25p	74151	32p
7406	16p	7450	9p	74153	29p
7409	9p	7486	14p	74154	35p
7410	6p	7490	32p	74164	35p
7412	12p	7491	18p	74175	35p
7416	14p	7492	23p	74192	33p
7420	9p	7493	18p	74193	38p
7430	9p	7495	45p	74194	33p
		74196	36p		

MIXED PACKS OF COMPONENTS

60 Polyester Caps.	Price: £2.00
100 Electrolytic Caps.	Price: £3.00
Approx. 500 resistors.	Price: £2.50

Standard Rotary Potentiometers. Single with ½ inch white nylon shaft. Values: 5k log, 10k log, 50k log, and 250k log.
Price: 19p each

Standard Rotary Potentiometers. Dual with ½ inch metal shaft. Values: 25k log, 50k log, and 500k log.
Price: 60p each

4mm Banana plugs Red and Black. Price: 11p each
4mm Banana sockets Red and Black. Price: 12p each
8 section Telescopic Aerial with swivel. 38 inches fully extended.
Price: 60p
Anti-surge fuses 20mm 2amp. Price: 5p
4 inch long Heatsink, undrilled, black anodised. Price: 65p
Four buttoned pre-set control panel for vari-cap tuners.
Price: 85p

Single sided, copper clad, printed circuit board. 2½ x 8¼
Price: 10p
4½ x 9
Price: 25p

25 Mixed Rubber Grommets Price 16p
16mm screw-on cab. feet. Set of four
Price: 5p

14mm square self adhesive feet. Set of four
Price: 15p

Din Plugs 5 pin 180° Price 10p
Din Sockets 5 pin 180°. Standard metal type
Price: 10p

Magnetic earpieces with 3.5mm plug
Price: 12p

Reed Switches Price: 5p
Wire Neons 90 volts Price: 4p

75mm diam. 15 ohm Speaker
Price: 60p

125mm x 78mm Oval 50 ohm Speaker
Price: 75p

Latchswitch 2p 2w Price: 10p
DPDT Slide Switches Price: 12p

Green Phono Plugs Price: 6p

Bridge Rectifiers
W005 50v 1A Price: 25p
W04 400v 1A Price: 28p

Red L.E.D.s .2 inch Price: 8p

Ceramic Filters 6MHz, SEF 6.0MB
Price: 20p

Colour T.V. Crystals 4.433619MHz
Price: 90p

PP3 Battery connecting leads Price: 6p
20mm chassis mounting fuse holders
Price: 6p

DL500 Displays Common Cathode
.5 inch displays Price: 75p

1p 12w Rotary Switches Price: 40p

All prices include V.A.T. and post and packing. Send for free pamphlet on all our instrument cases, boxes and components. Discount on boxes and instrument cases only, as follows: Orders over £10 5%, over £20 10%, over £30 15%.

**HARRISON BROS. P.O. Box. 55, Westcliff-on-Sea,
Essex. SS0 7LQ. Telephone: Southend-on-Sea (0702) 32338.**

STYLUS ORGAN

By M. V. Hastings



Easy to build monophonic electronic organ with switchable vibrato

A modern polyphonic electronic organ is quite a complex and expensive piece of equipment, even when special organ i.c.'s are incorporated in the design. However, a simple monophonic instrument which plays only one note at a time can provide many hours of enjoyment, and its construction is considerably eased if it is stylus operated. The design to be described covers the two octaves above Middle C or, if preferred, an octave either side of Middle C. It is completely self-contained and has an integral vibrato circuit which can be switched in or out as desired.

A further facility is the provision of two jack sockets, one coupling to the output of the tone generator and the other to the input of the organ a.f. amplifier. An external envelope shaper can be connected to these sockets to process the signal before it is passed to the a.f. amplifier. An envelope shaper, specifically designed for use with the present organ, will be described in next month's issue. The socket connecting to the output of the tone generator will also take the plug of a crystal earpiece, thereby providing personal listening for practice or simply enjoyment. Inserting the earpiece plug disconnects the tone generator from the a.f. amplifier in the organ.

CIRCUIT DESIGN

The full circuit of the organ is shown in Fig. 1. A BRY39 silicon controlled switch (s.c.s.) connected to operate as a programmable unijunction transistor is connected in a relaxation oscillator circuit which generates the required note. This type of oscillator has been described previously in the article "Silicon Controlled Switch Circuits", Parts 1 and 2, by John Baker, which appeared in the December 1978 and January 1979 issues of *Radio & Electronics Constructor*, and so its functioning will only be described briefly here.

An Envelope Shaper giving a varying amplitude characteristic to the output will be published next month

The GK (gate cathode) terminal of the BRY39 is biased about 2.9 volts positive of the negative supply rail by R6 and R7, and the A (anode) terminal is taken to the positive rail via R8. No connection is made to the GA (gate anode) terminal. Initially, the K (cathode) terminal will be at the positive supply rail potential, since C6 will be discharged. Under these conditions, no current flows through the s.c.s. from anode to cathode. If the stylus connected to the negative rail is now applied to one of the pre-set potentiometers, R12 and R36, C6 commences to charge up by way of R9 and the potentiometer chosen. When C6 has charged to a voltage which causes the cathode of the s.c.s. to be about 0.6 volt negative of the GK terminal, a regenerative action suddenly takes place inside the s.c.s., causing it to turn hard on and quickly discharge C6 through its anode and cathode terminals and through R8. C6 becomes nearly fully discharged, and when the voltage across it becomes insufficient to maintain the s.c.s. in the hard on condition the latter rapidly reverts to the turned off state. C6 is once more free to charge and it does so until once more the s.c.s. turns hard on. The cycles proceed in like manner, a voltage pulse being produced across R8 for each discharge of C6.

The oscillations proceed at an audio frequency whose frequency is controlled by the pre-set potentiometer selected by the stylus, and the stream of pulses produced across R8 form the output signal. These are passed via R10 and d.c. blocking capacitor C7 to jack socket JK1. R10 and C8 attenuate some of the higher frequency harmonics in the signal, giving it a more musically pleasing tone. When no plugs are inserted in JK1 or JK2 the signal is automatically passed to the volume control, VR1, and the subsequent a.f. amplifier. If a jack plug connecting to a crystal earpiece is inserted in JK1 the connection to the volume control is broken and the signal is heard in the earpiece.

The operating frequency of the tone generator depends upon the resistance inserted into circuit by the pre-set potentiometer selected by the stylus, and in practice the 25 potentiometers are set up to provide a full 2-octave scale including semitones, one potentiometer being used to produce each note.


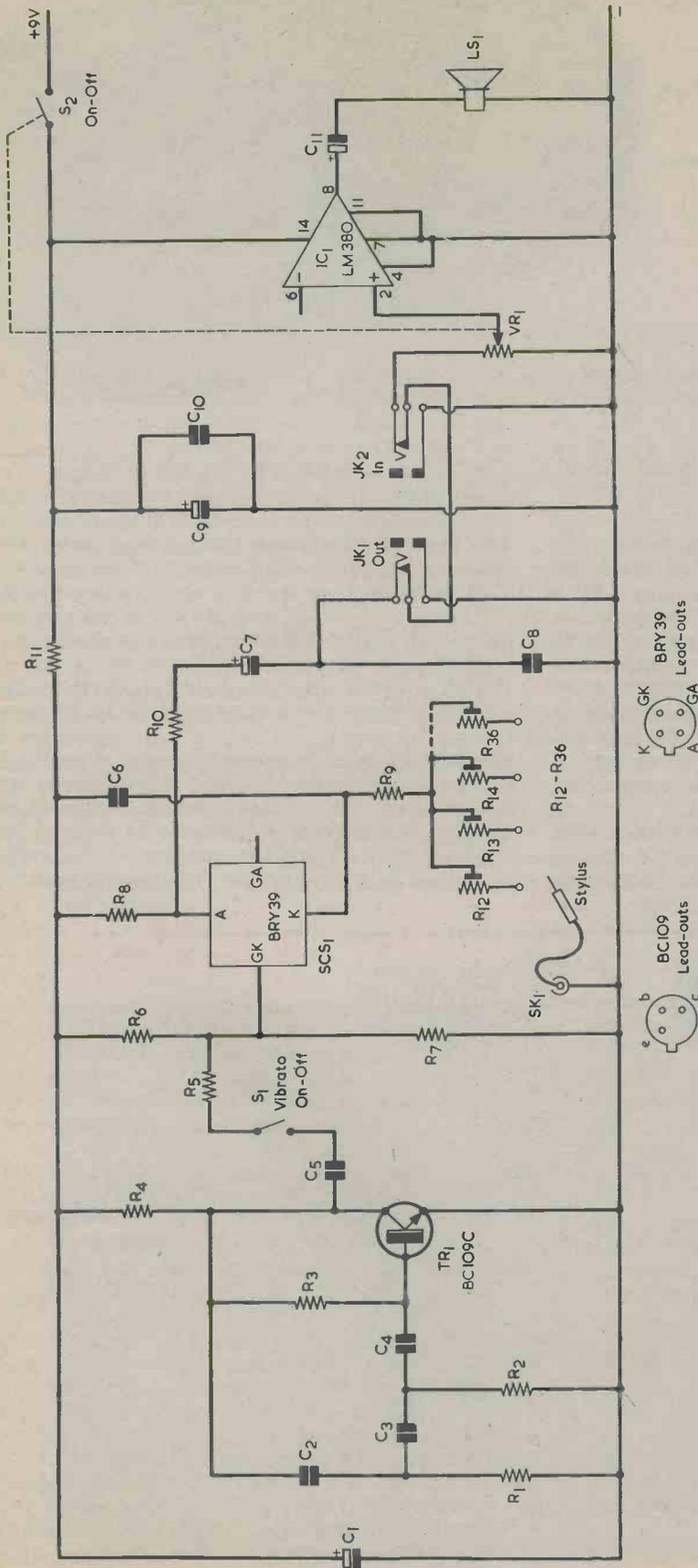


Fig. 1. The circuit of the electronic organ. Each note is played by applying the tip of the stylus to the lower track connection of one of the pre-set potentiometers. R₁₂ to R₃₆. Vibrato can be switched in or out by means of S₁

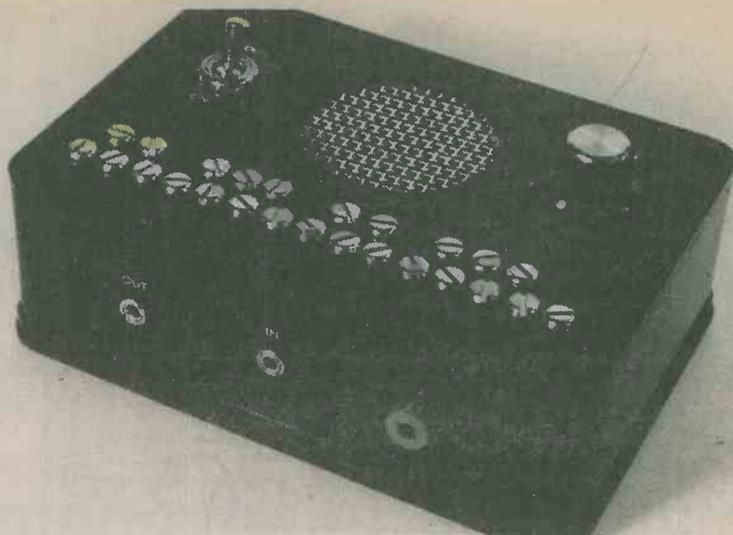Nickel plated screw heads form the keyboard of the organ. These are laid out, in a manner similar to a piano keyboard, to provide two octaves complete with semitones



VIBRATO

A simple tone generator tends to produce a rather monotonous sound, and a much more pleasant and more musical effect can be given by modulating the tone at a low frequency. The modulation can be amplitude modulation (tremolo) in which the volume of the signal is changed, or it can be frequency modulation (vibrato) in which the pitch of the sound is slightly varied on either side of its nominal level. Vibrato offers what is probably the better effect, and frequency modulation is employed in this design.

A phase shift oscillator produces the modulating signal, and incorporates TR1 in the common emitter amplifying mode. A 3-stage phase shift network comprising C2, R1, C3, R2 and C4 couples TR1 collector back to its base, and the 180 degree

phase shift between collector and base which is required for oscillation to occur is given at about 8Hz. The gain of TR1 more than compensates for the losses in the phase shift network. The output from TR1 collector is coupled to the junction of R6 and R7 by way of C5, S1 and R5. S1 is the vibrato on-off switch whilst R5 attenuates the modulation so that it is not excessive.

The effect of the modulating signal is to slightly raise and lower the voltage on the GK terminal of the silicon controlled switch. Raising this voltage reduces the voltage needed across C6 to trigger on the s.c.s., whereupon output frequency increases. Lowering the GK voltage makes it necessary for C6 to charge to a greater voltage and thereby lowers the frequency. Thus, the required vibrato effect is produced in a simple and reliable manner.

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5% unless otherwise stated)

R1 33k Ω	R7 2.2k Ω
R2 33k Ω	R8 680 Ω
R3 2.2M Ω 10%	R9 5.6k Ω
R4 4.7k Ω	R10 47k Ω
R5 220k Ω	R11 680 Ω
R6 4.7k Ω	
R12-R36 47k Ω 0.1 watt pre-set potentiometer, horizontal (25-off)	
VR1 5k Ω potentiometer, log, with switch S2	

Capacitors

C1 100 μ F electrolytic, 10V, Wkg.
C2 0.22 μ F type C280
C3 0.22 μ F type C280
C4 0.22 μ F type C280
C5 0.47 μ F type C280
C6 0.1 μ F type C280 (see text)
C7 10 μ F electrolytic, 10V. Wkg.
C8 2,200 μ F ceramic plate
C9 100 μ F electrolytic, 10V. Wkg.
C10 0.047 μ F ceramic or ceramic plate
C11 330 μ F electrolytic, 10V. Wkg.

Semiconductors

TR1 BC109C
IC1 LM380
SCS1 BRY39

Switches

S1 s.p.s.t. toggle
S2 s.p.s.t. toggle, part of VR1

Sockets

SK1 insulated wander plug socket
JK1 3.5mm jack socket with break contact
JK2 3.5 jack socket with break contact

Speaker

LS1 miniature speaker, 8 Ω to 25 Ω (see text)

Miscellaneous

Plastic case (see text)
Veroboard, 0.1in. matrix
9-volt battery type PP6
Battery connector
Control knob
Test prod, flexible lead and wander plug
Speaker cloth or fret
25-off 6mm. M4 nickel plated panel-head screws
25-off M4 nuts
25-off M4 (or 4BA) solder tags
Wire, nuts bolts, solder, etc.



Fig. 2. The organ keyboard consists of 25 nickel plated screw heads laid out in the manner shown here

AMPLIFIER

An LM380 i.c. forms the a.f. amplifier of the organ. The only discrete components required here are the volume control, VR1, and the output coupling capacitor, C11. An output power of the order of a few hundred milliwatts can be obtained using a speaker having an impedance in the range of 8Ω to 25Ω . The circuit will also work perfectly well with speakers having a higher impedance, but will then give reduced maximum output power.

We have already noted that a crystal earpiece can be plugged into JK1. If it is intended to use the special effects processor which will be described next month, the input of the processor is plugged into JK1 and its output is plugged into JK2. Fitting the plug into JK2 automatically isolates the socket from JK1.


S2 is the on-off switch, and is ganged with the volume control. C1, C9, C10 and R11 are supply decoupling components. The current consumption of the organ is about 10mA at low volume settings, rising to 60mA or more at maximum volume on the higher notes.

CONSTRUCTION


The prototype organ is housed in a black plastic case having approximate outside dimensions of 159 by 108 by 54mm. This is a case type MA1, available from Harrison Bros., P.O. Box 55, Westcliffe-on-Sea, Essex, SS0 7LQ.

The organ keyboard could be made up using printed circuit board techniques, but the simple alternative employed for the prototype is easier to construct and is very effective in practice. It consists of 25 nickel plated 6mm. panel-head M4 screws mounted on the top panel of the case towards the front and laid out in the form of a piano keyboard, as shown in Fig.2 and the photographs. The mounting holes at 4.5mm. in diameter, and a solder tag is secured inside the case, under the nut for each screw. M4 solder tags do not appear to be readily available, but 4BA solder tags will be a satisfactory substitute.

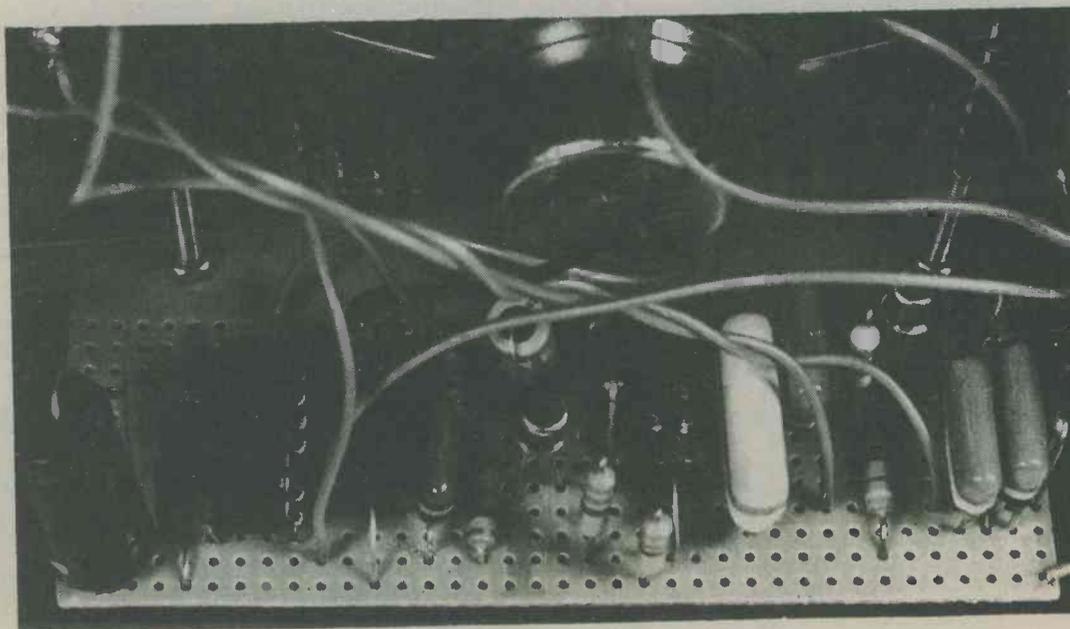A circular cut-out for the speaker is required centrally in the top panel towards the rear, and this can be made with a fretsaw or a round needle file. A piece of speaker cloth or fret is glued in position



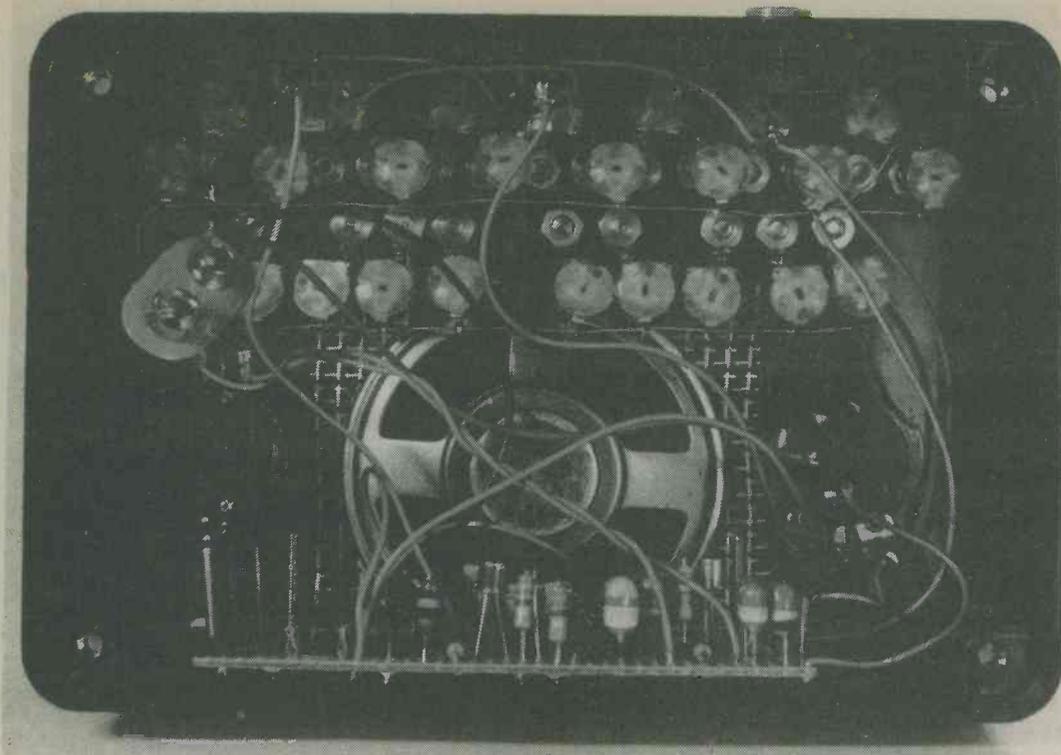Nearly all the small components are wired up on a Veroboard panel which is secured to the inside of the rear panel of the case



The interior of the organ. One pre-set potentiometer has a track tag soldered to each of the keyboard screw solder tags

behind the cut-out. Most miniature speakers do not have provision for screw fixing, and so it will be necessary to carefully glue the speaker in place behind the cloth or fret. A minimal amount of glue should be applied to the front rim of the speaker. Avoid getting any glue on the speaker cone or surround as this could impair the performance of the speaker.

VR1/S2 is mounted to the right of the speaker and S1 to the left. JK1 is mounted on the left hand side of the front panel (looking at the organ from the front) JK2 in the centre and SK1 to the right.

The 25 pre-set potentiometers are mounted on the Keyboard solder tags (one potentiometer to each tag, of course) by one of the track connection tags. The wiper connection tags are wired together by bare tinned copper wires of around 22s.w.g. in size. Three bus-bar wires connect to R9. The photograph of the interior of the organ gives an idea of the positioning of the potentiometers. The job of


mounting the potentiometers is rather fiddly but not too difficult, and the mounting of each potentiometer to its own screw has the advantage of making the identification of the potentiometer for each note readily apparent.

The stylus can be a test prod connected by a flexible insulated lead to a wander plug, which plugs into SE1 when the organ is being used.

CIRCUIT BOARD

The remaining small components are assembled on a piece of 0.1in. Veroboard having 15 copper strips by 37 holes. This is illustrated in Fig. 3. Start by cutting out a board of the required size with a hacksaw, then smooth off any rough edges with a file. Next drill out the two mounting holes, which may be either 6BA or M3 clear, then make the 16 breaks in the copper strips. The various components and the three link wires can then all be

The speaker is mounted centrally behind the keyboard screws, with the vibrato switch to its left and the volume control to its right

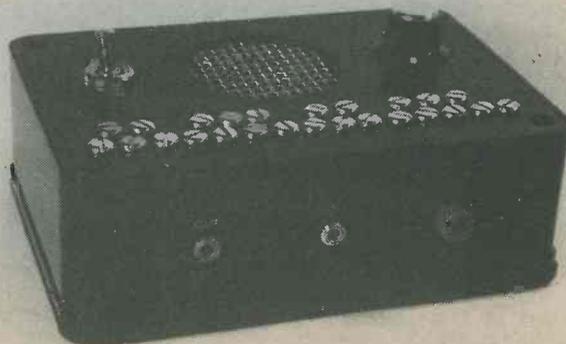

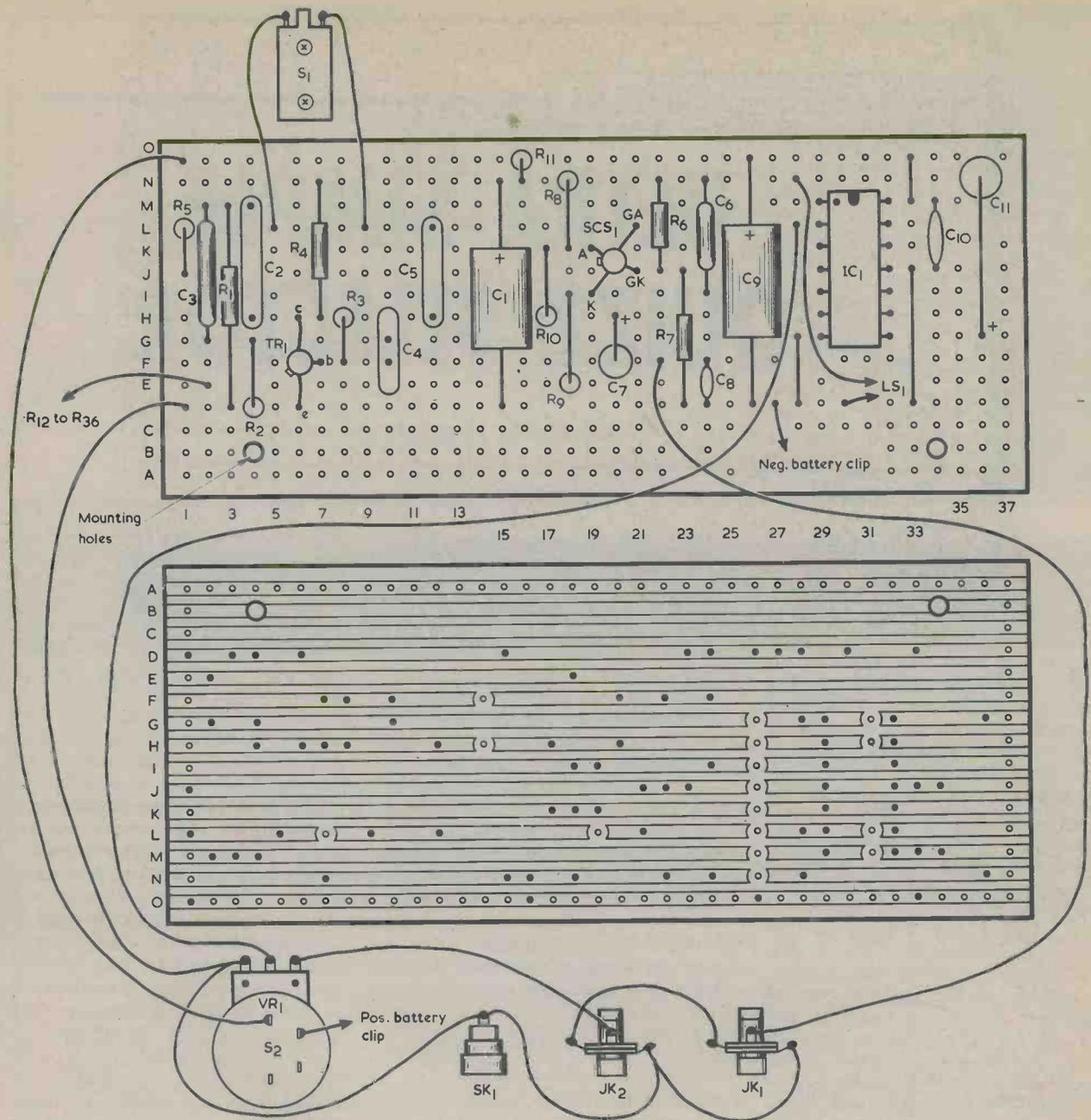


Fig. 3. Layout of components on the Veroboard panel and connections to the components external to the panel

soldered into position. It is only necessary to connect the negative supply rail to pins 4 and 11 of the LM380, as the remaining ground pins, 3, 6, 10 and 12 are internally connected to these inside the i.c.

The completed panel is bolted inside the rear panel of the case, with the mounting holes towards the top. Spacing washers over the mounting bolts between the Veroboard and the inside surface of the case are fitted to prevent strain on the board when the mounting nuts are tightened. The wiring from the board to the external components, also shown in Fig.3, must be completed before the board is finally mounted in place. The organ is powered by a PP6 battery, and there is plenty of space for this below the keyboard.

TUNING

The organ is tuned aurally against a piano or other source of a chromatic scale and, with the component values specified, will tune from Middle C to the C two octaves higher. If preferred, the organ can be given a tuning range of one octave either side of Middle C by increasing the value of C6 to 0.22 μ F. The tuning is largely unaffected by variations in the supply voltage due to battery aging, and once correctly tuned will remain so for a considerable period of time.

An envelope shaper which can be coupled to the organ will be described next month.

SUGGESTED CIRCUIT

ULTRA-SIMPLE QUIZZ SELECTOR

By G. A. French

We are all familiar with broadcast quiz programmes in which each of two contestants has to press a button to indicate that he is ready to answer a question. The quizmaster is provided with two lights to indicate which of the buttons has been pressed first, and these lights function even when one button is pressed only marginally ahead of the other.

A number of circuits which indicate button precedence have appeared in the home-constructor press over recent years, some of these being relatively uncomplicated and others quite complex. The author returns to the theme in the present article only because the circuit to be described is possibly the simplest which can be devised. Acknowledgement for the basic idea is due to the Danish magazine *Populaer Radio*, in the April 1979 issue of which appeared a design incorporating filament bulbs and a somewhat different wiring system ("Enkel Quiz-Markor" by G. Moller-Hansen).

THE CIRCUIT

The circuit of the quiz selector appears in Fig. 1. In this diagram the transistors, resistors, light-emitting diodes and the 9 volt supply are all assembled at a central point, with twin leads, indicated in broken line, passing to the two push-buttons, S1 and S2. When the two push-buttons are open, i.e. not pressed, no current flows in the circuit and both l.e.d.'s are extinguished. If S1 is closed, LED1 lights up and S2 has no effect on the circuit. Similarly, if S2 is pressed, LED2 is illuminated and S1 can exert no control. Thus, the l.e.d.'s indicate which of the two buttons has been pressed first. The

circuit is capable of differentiating between the buttons even when the closure of the first occurs only fractionally before the closure of the second.

Fig. 2 illustrates how the circuit functions. Let us assume that push-button S1 has just been closed. Its contacts connect the emitter of TR1 to the negative supply rail, whereupon a bias current flows via LED2, R4 and R3 into the base of this transistor. An amplified collector current flows through LED1 and R1, causing LED1 to light up. Since TR1 is turned fully on, the voltage between its collector and emitter falls to about 0.2 volt. Subsequently pressing S2 cannot cause TR2 to turn on because, being a silicon transistor, it requires a potential of

around 0.6 volt between its base and emitter before it can pass base bias current. Pressing S1, therefore, not only turns on LED1 but it also causes the flow of base bias current to TR2 to be inhibited. Had it been S2 which was pressed first, it would have been LED2 which became illuminated, with 0.2 volt appearing between the collector and emitter of TR2 to prevent the subsequent turning on of TR1.

Because of the amplification provided by each transistor, the base bias current flowing in the opposite l.e.d. is very much smaller than that flowing in the l.e.d. which lights up. When, for instance, S1 is pressed, the bias current flowing in LED2 is only some 0.25mA whilst that in LED1 is of the order of

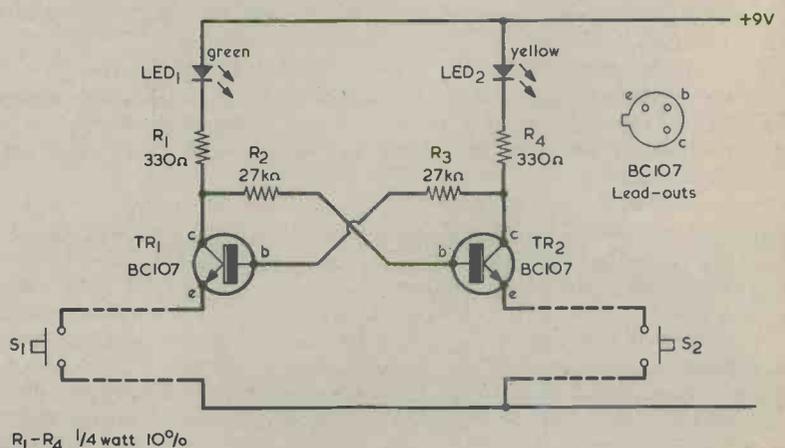


Fig. 1. The circuit of the quiz selector. The two press-to-make push buttons connect to the main part of the circuit via twin leads

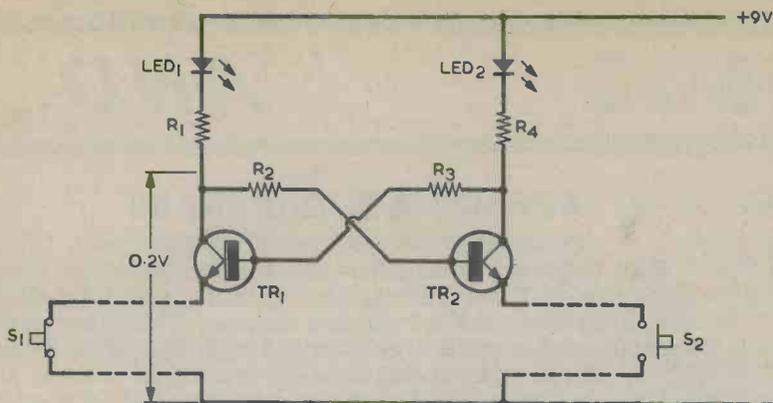


Fig. 2. Illustrating circuit operation when S1 is the button which is pressed first

20mA. The l.e.d. colours are a matter of personal choice although it is better to avoid red, as some of the more sensitive red l.e.d.'s emit a glow which is just visible at 0.25mA and this detracts slightly from the effectiveness of the presentation. For the same reason it is also desirable to avoid using the "extra-bright" l.e.d.'s which are offered by some retailers. Standard green and yellow l.e.d.'s emit no noticeable glow at 0.25mA, and have a satisfactory brightness at 20mA.

There is no need for an on-off switch as the circuit consumes no current when the push-buttons are open. The supply current is 20mA when one of the l.e.d.'s is alight, and a suitable battery would be a PP9 or similar. ■

RECENT PUBLICATIONS



RADIO REPAIR. By Les Lawry-Johns. 95 pages, 165 x 110mm. (6½ x 4¼in.). Published by The Butterworth Group. Price £1.50.

This title appears in the Newnes Technical Books "Questions and Answers" series, and has a format in which questions appear in italics, rather like sub-headings, after which the answers are provided. This is a good method of presenting material on a subject such as radio servicing, since it offers breaks in the text which allow for light occasional reading as well as a continual study of the text.

The author is patently a service engineer of considerable experience and the advice given in the book is always helpful and practical. It is refreshing to see references to that arch-enemy of all serviceman: the "Phantom Dabbler" who attempts to "repair" a receiver and in the process introduces far more faults than were originally in existence.

The contents of the book range from transistor radios to unit audio equipment, including a chapter on car radios. There are also separate chapters on noisy operation and valve radios, of which a surprisingly large number are still in daily use. This will be a rewarding book for anyone starting to work in radio servicing.

YOUR ELECTRONIC CALCULATOR AND YOUR MONEY. By F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., M.B.I.M. 176 pages, 180 x 105mm. (7 x 4¼in.) Published by Bernard Babani (Publishing) Ltd. Price £1.35.

Many of us shy away from calculations when these are not of an obviously simple nature or when they involve such things as multiplications with numbers having more than two or three digits. Nowadays such problems can, of course, be solved in a flash with the aid of a pocket calculator, and yet an inertia still exists which prevents the application of the problem to the calculator.

In the book under review the author deals with the subject of money and shows how inexpensive calculators can be employed to handle money calculations from mortgage repayments to bets on horses. Money is a compelling topic and, when reading the section on electricity charges, this reviewer could not prevent himself from getting out and checking his latest electricity bill! Incidentally, this section of the book also tells the reader how to find the power rating of domestic equipment by observing the number of revolutions of the marked disc in the electricity meter.

The first chapter in the book deals with the arithmetic of money, brushing up what may be a few faded memories on decimals and other mathematical basics. This is followed by a chapter covering domestic expenses, including rates, fuel and decorating, motor car expenses, betting and income tax. Two following chapters then deal with investment and the use of the calculator in a small business. The work concludes with a number of appendices giving tables for conversion factors, compound interest factors, discounted cash flow factors, mortgages, fuel cost comparisons and VAT calculations. Despite the difficulties involved in presenting calculations in print, the text is set clearly and accurately.

LOW-COST LOGIC PROBE



Said to be one half of the cost of any comparable unit, OK's new PRB-1 self-contained digital logic probe greatly simplifies the task of trouble-shooting even the most sophisticated circuits including RTL, DTL, HTL, TTL, MOS, CMOS and microprocessor logic.

Until recently digital electronic servicing had to rely on the oscilloscope for logic level analysis. Although accurate and sensitive, the oscilloscope is also very expensive and not very portable.

However, this new probe is said to rival the best oscilloscopes in performance, yet is completely portable and at £25.93 (Ex. VAT & Packaging) costs a fraction of even the cheapest oscilloscope.

The pen-sized PRB-1 is powered by the circuit under test. Its probe point is steel for durability and is finely sharpened to ensure precise positioning on the circuit or device being examined, as well as to prevent slipping or unwanted shorts.

Another convenience feature of the PRB-1 is that it is permanently adjusted so no recalibration is required. Furthermore, while the PRB-1 is fully compatible with all logic families, no switch resetting or manual adjustments are needed to go from one IC family to another.

The probe body is high impact, and solvent resistant. The light weight power cord is coiled for convenience, detachable, and extends to 6ft (1.8m) if necessary, terminating in mini-alligator clips. The constant brightness LED's are situated for maximum visibility, and a logic truth table is printed above them.

The PRB-1 is manufactured by OK Machine & Tool Ltd., 48a The Avenue, Southampton, Hants. SO1 2SY.

BBC LOCAL RADIO STATIONS

	med. wave	vhf		med. wave	vhf		med. wave	vhf
BIRMINGHAM	206	95.6	HUMBERSIDE	202	96.9	OXFORD	202	95.2
BLACKBURN	351	96.4	LEEDS	388	92.4	SHEFFIELD	290	97.4
BRIGHTON	202	95.3	LEICESTER	189	95.1		—	88.6
BRISTOL	194	95.5	LONDON	206	94.9	SOLENT	300	96.1
CARLISLE	397	95.6	MANCHESTER	206	95.1	(in Bournemouth)	221	—
	206	—	MEDWAY	290	96.7	STOKE-ON-TRENT	200	96.1
CLEVELAND	194	96.6	MERSEYSIDE	202	95.8			
DERBY	269	96.5	NEWCASTLE	206	95.4			
	—	94.2	NOTTINGHAM	197	95.4			

THE STORY OF PYE WIRELESS

The story of Pye Wireless starts in the era when John Scott-Taggart, whose achievements we mention on the next page, was having such an influence on the technically minded public.

A twenty page booklet to mark the 50th anniversary of the formation of Pye Radio Limited is now available to members of the public on application to Pye Limited, Publications Department, 137 Ditton Walk, Cambridge.

The Story of Pye Wireless traces the history of Pye Receivers from when they were originally produced by W. G. Pye & Co. It was from the wireless side of this Company that Pye radio Limited was formed on February 12th, 1929. Written by Gordon Bussey the publication is highly

illustrated with photographs of Pye receivers from 1922 onwards and scenes in the Pye factory in Cambridge during those early years.

"My main source of research was Harold J. Pye," said Gordon, "after discovering his whereabouts I spent many hours talking to him about the early days of Pye and I found him to be a truly fascinating man." After graduating from St. John's College, Cambridge with a BA degree (MA 1930) Harold J. Pye joined his father in the business in 1923 and is the last surviving partner of the original W. G. Pye and Company.

The first public demonstration of wireless equipment made by W. G. Pye & Co., was at the Royal Show held in Cambridge in 1922.

COMMENT

THE PASSING OF A PIONEER

Our older readers will have learned of the recent death of Wing-Comdr John Scott-Taggart, at the age of 82, with almost a sense of personal loss.

He was a radio pioneer who, through his books and magazine articles in the early 1920's, caught the interest of thousands of technically minded people. It was said, at the time, that more than 100,000 amateur radio constructors built radios using his ST100 design. He had however had articles published much earlier, his first published article appearing in 1914.

During the First World War, after serving with the Seaforth Highlanders, he became an instructor in wireless to the army, and in the Second World War, after first commanding a radar station in France, he eventually became responsible at the Air Ministry for all radar training.

Older readers will recall the two magazines he founded — 'Modern Wireless' and 'Wireless Weekly' — which were so very popular between the wars. We like to think that, in our modest way, we have worthily continued in the same tradition.

THE NASCOM STORY

A shining light in the U.K. microcomputer field is Nascom Microcomputers Limited. The history of this company since its inception not only provides a fascinating story in its own right but also aptly demonstrates the meteoric rise of microcomputer development and manufacture over the last year or so.

Nascom Microcomputers Limited was formed in July 1978 following the success of the Mascom-1 microcomputer launched in November 1977 by Nasco Sales Limited. Between then and July 1978 the Nascom-1 was marketed to industrial customers through Nasco Sales and to domestic customers through Lynx Electronic Limited. Both companies are subsidiaries of Nasco Limited, a semiconductor distributor established in 1970.

The Nascom-1 microcomputer was the brainchild of the founders of Nascom Microcomputers, John

Marshall and Kerr Borland, who are Managing Director and Marketing Director respectively. With the concept of a microcomputer that would sell for under £200 and be fully expandable, they engaged London hardware specialists, Shelton Instruments, to design a single board computer around Mostek's Z80 CPU.

The microcomputer was unveiled at a seminar in the Wembley Conference Centre at which 100 to 200 delegates were expected. Such was the interest in a microcomputer which was within the reach of personal finances that nearly 600 delegates attended. By the end of the seminar, 350 orders had been received for the Nascom-1.

Having planned to deliver what was thought to be the optimistic figure of 150 computers in the first three months, Nasco were faced with the immediate problem of gearing up to satisfy these orders. In the following 12 months the order book swelled to over 10,000 units

and reflected a broad cross-section of British industry from Ministries and the G.P.O. through to major industrial companies, universities, colleges, small electronic research laboratories and personal users.

Early in 1978, Nascom set up a network of distributors in the U.K. The network was expanded into Europe, starting with Germany. As with the U.K., the Nascom-1 was an overwhelming success. The distributor network was then increased to take in all of Europe and Scandinavia. Today, 80 per cent of total sales are to these overseas markets.

At the end of 1978, Nascom placed an order for microprocessors with Mostek U.K. valued in excess of 1.5 million dollars. This is the largest order of its kind ever placed by a British company.

Now announced by Nascom Microcomputers is the Nascom-2, this representing a second major step forward in the history of this company's progress. A success story, indeed.

REMOTE CONTROL SWITCH

Suitable for Industrial, Commercial and Domestic use, the Kontite supersonic switch can remotely control any individual piece of electrical equipment up to 2 KW power rating.

The switch consists of two parts — an unobtrusive receiver and a light cordless hand-held transmitter complete with battery.

The input-output cables of the receiver are connected to the appliance to be controlled, using a standard three-pin socket and plug and the transmitter aimed at the receiver. The appliance can now be switched on and off from a distance of up to 30/35 ft.

The Kontite remote control switch can be used in the home, office or factory, anywhere where remote operation is desirable.

For further details contact — Kay & Co. (Engineers) Ltd., Acresfield House, Exchange Street, Bolton BL1 1RS.



Double-and-Halving

By D. Snaith

Multiplication by shift of digits

One way in which a computer can multiply two numbers together is by means of repeated addition. With this process the multiplicand (the number to be multiplied) is fed to an accumulator register initially set to zero and is then repeatedly added to the number in the accumulator until the total number of entries is equal to the multiplier. The final sum in the accumulator is then the multiplicand multiplied by the multiplier.

This is a perfectly rational method of carrying out a multiplication, but it has the disadvantage of requiring a lot of additions which, apart from anything else, take up valuable computer time.

QUICKER METHOD

A quicker approach is to use the doubling-and-halving method. This is quite simple to follow, but it is first of all necessary to see what happens when we double or halve a binary number.

If we multiply a decimal numbers by 10 we move all the digits one place to the left and insert a zero in the space left at the right. 657 multiplied by 10 becomes 6570. Multiply by 10 again and we get 65700. Should we divide 65700 by 10 we move the digits one place to the right, giving 6570. A further division by 10 produces the first number, 657.

Decimal numbers are based on the radix 10, whilst binary numbers are based on the radix 2. Therefore, if we multiply, say, the binary number 101 by 2 we shift the digits one place to the left and insert a zero, to give 1010. Another multiplication by 2 produces 10100. Dividing 10100 by 2 gives 1010, and a further division by 2 results in the original 101. So, doubling a binary number shifts all the digits one place to the left; halving it shifts all the digits one place to the right.

We can now examine the process of multiplication by doubling-and-halving. As a simple example we shall multiply binary 110 (=6) by binary 10101 (=21) and the steps are shown in Fig. 1. The mul-

tiplicand is placed in one register and the multiplier in another register. There is also an accumulator register which is initially set to zero.

The number in the multiplier register is examined and if the least significant digit (that at the extreme right) is 1, the number in the multiplicand register is added to the accumulator. This occurs in the first step of Fig. 1. The multiplicand is then doubled and the multiplier halved, bringing us to the second step. The right hand 1 in the multiplier which was present in the first step is now dropped out of the multiplier register since it has served its purpose, and the least significant digit in the multiplier register is a 0. No action is taken.

Fig. 2.

```

      110
     10101
    -----
      110
     110
    110
   1111110
  
```


On the third step the multiplicand is again doubled and the multiplier halved. The least significant figure in the multiplier register is once more 1, and this results in the number in the multiplicand register being added to the number in the accumulator. The process repeats in the fourth step (no action) and in the fifth step (addition to accumulator), whilst in the sixth step there is no number left in the multiplier register. The result of the multiplication (equal to decimal 126) is then the number which is present in the accumulator.

The doubling-and-halving process of multiplication obviously takes much less time and requires far fewer operations than does repeated addition. Also, shifting digits in a register to the left or to the right is a basic computer operation.

There is no necromancy in Fig. 1, since all we are effectively doing is getting the computer to do the multiplication sum which is shown in Fig. 2. Things get more involved and roundabout when the sum is handled by the computer, but then who ever said that computers are easy?

Multiplicand	Multiplier	Action	Number In Accumulator
110	10 101	Add 110	110
1 100	1 010	No action	110
11 000	101	Add 11 000	11 110
110 000	10	No action	11 110
1 100 000	1	Add 1 100 000	1 111 110
11 000 000	0		1 111 110

Fig. 1.

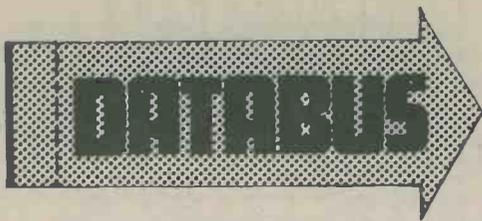

really explains *microprocessors*

series
No. 3

By Ian Sinclair

SELECTION AND BUSSING

This is the third in our 12-part series which takes the lid off microprocessors

In part 2 we looked at memory chips, ROM and RAM. Each memory chip stores a large number of bits, however, so how do we go about selecting one? Take a simple example of two bits only in a ROM (Fig. 1). We could select which one we wanted by using a signal into a gate, 0 for one stored bit and 1 for the other. But suppose we have eight stored bits in a ROM. We now need to be able to select one bit out of eight, and this can be done by gating, this time combined with binary counting, in a circuit called a multiplexer. This particular example will use an 8 to 1 multiplexer, which could be a separate circuit, but is much more useful if it's built into the memory i.c., since this will cut down the number of connections that have to be made outside the i.c. multiplexer. What does it do? There are 8 inputs to the multiplexer, each connected to a stored bit. There's one output and there are three control lines. The way it works is delightfully straightforward. The three control lines can *each* be set to 1 or 0, so that we could use control symbols 001 010, 011, 100 and so on. Now 001 is 1 in binary, and this set of control signals connects bit No. 1 to the output. With 010 (2 in binary) selected, bit No. 2 is connected to the output. With 011 (3) selected, bit No. 3 is connected to the output and so on. Control 000 can be used for bit 8, in this scheme.

ADDRESS LINES

This is a comparatively simple example. The control signal inputs are called address lines, because the digital number which is formed by the bits on these lines is an "address", a code number which

will fetch one bit from memory. Each bit that is stored in the memory has its own address, the combination of signals on the address inputs which makes the gates connect to that particular part of memory.

By using three address lines, we can make connections to eight separate bits in this memory. This way we have avoided using five pin connectors, at the minor expense of more complicated circuits inside the i.c. The savings become a lot more significant when we use larger memories. Four address lines will access (make connection to) sixteen bits of memory, saving 12 pins. Five address lines can access 32 bits of memory — 27 pins saved. Use ten address lines, and the number of stored bits that can be accessed is 1024 — we wouldn't think of using that many pins!

That's all very well, of course, but where do these address line signals come from? The answer is that they are generated inside the microprocessor CPU

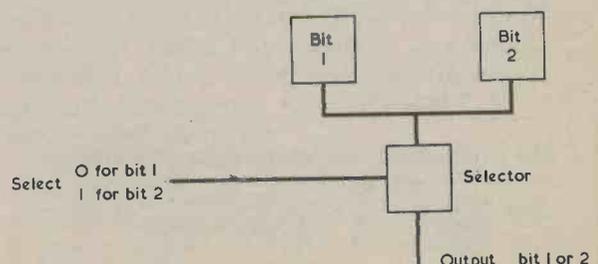


Fig. 1. Selecting one bit from two, using a selector gate switch

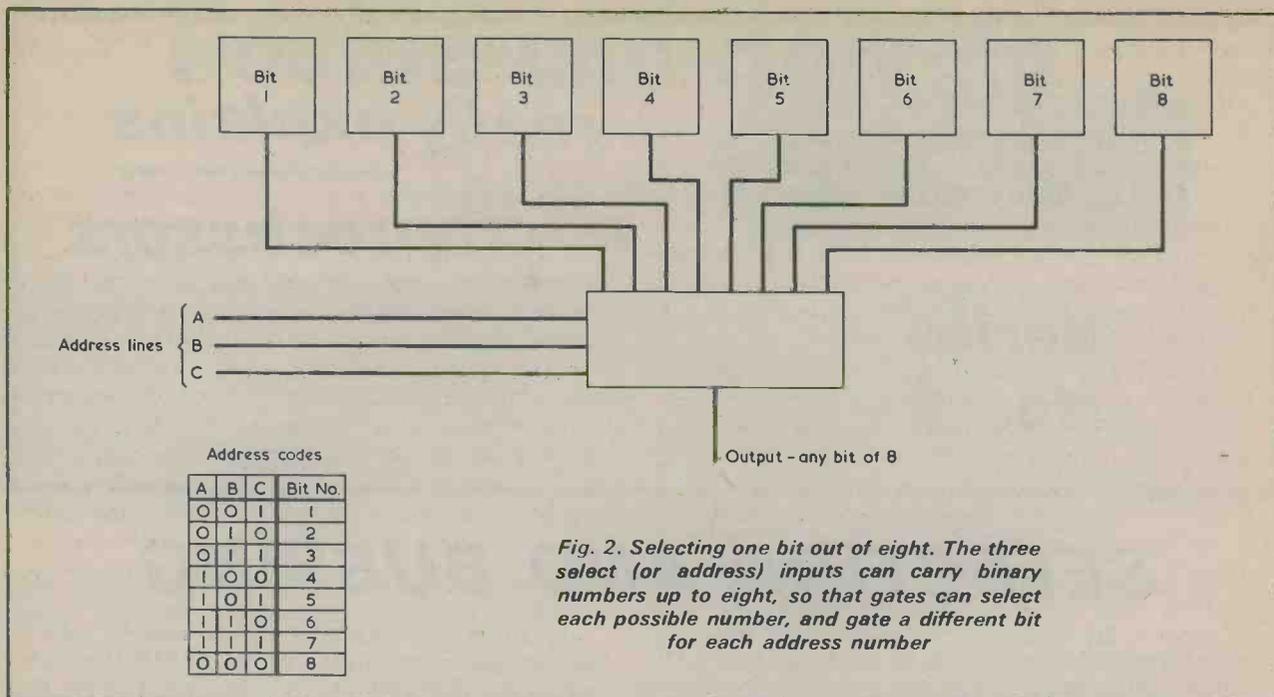


Fig. 2. Selecting one bit out of eight. The three select (or address) inputs can carry binary numbers up to eight, so that gates can select each possible number, and gate a different bit for each address number

itself, some by a simple counting action, and others rather differently as we shall see. Most CPU's, apart from the simpler variety, have sixteen address lines, so that they could address 65536 bits of memory. This is a lot more than is needed for most applications, but it's nice to have in reserve!

A memory i.c., then, will have address pins, so that the signals from the CPU will select the correct part of memory, and one (or more) data pins at which signals will be taken from or passed to the memory. Incidentally, we refer all these operations to the CPU — we use "read" to mean a memory passing data to the CPU and "write" to mean the CPU passing data to the memory. One chip has an output and the other has an input, but the important one is the CPU.

If the memory is a read/write type (RAM) an additional signal is needed. At its simplest, the memory i.c. might use a READ/WRITE pin, with a control signal which might be 0 for read, 1 for write. Where does *that* signal come from? Right again, from the CPU, and the signal has to be generated under the control of the program.

Now you can see why a microprocessor must have a program which is set in a ROM. Without a program, there can be no read or write signals, the address signals would follow a simple sequence (see later, Part 4), and no data signals could be sent out. A very reasonable question to ask at this point is how we can ever start a program running, if we need a program to run the CPU! That's one we'll deal with later; for the moment let's look at some hardware — the connections between the CPU and the memory i.c.'s.

DATA PINS

Microprocessors operate with eight bits, a byte, at a time. To feed in 8 bits need eight pins, called the data pins, at the CPU, and these are both inputs and outputs, unlike the address pins which are for outputs only. When are the data pins used for outputs and when are they used for inputs? They are used as outputs when the CPU is storing bytes into memory, and when this happens there will be a signal from a READ/WRITE pin which switches all

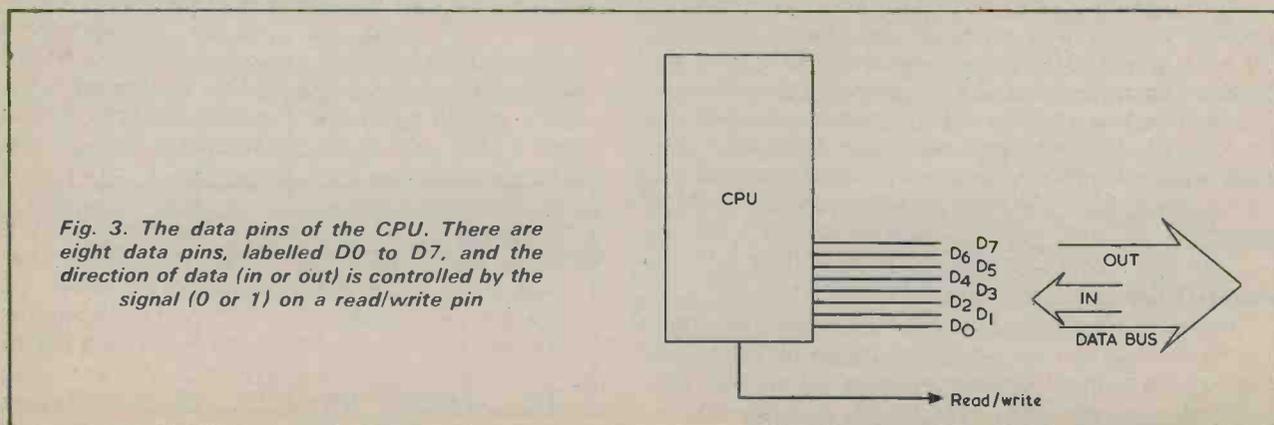


Fig. 3. The data pins of the CPU. There are eight data pins, labelled D0 to D7, and the direction of data (in or out) is controlled by the signal (0 or 1) on a read/write pin

the RAM memory so that data bits can be stored. When the microprocessor needs to take in data from the memory, the read signal is selected by the voltages on the address pins. If, by some mischance, a ROM is selected for write signals, nothing happens, but we should design the system so that the CPU never attempts to write into a ROM.

The next part to note is the way memories are organised inside. Some memory i.c.'s are made so that each address number connects just one single bit to an output/input pin; others connect 2 bits, 4 bits or 8 bits to as many data pins.

The different ways of arranging memories are indicated in the way a memory is described. For example, a 1024 x 1 memory is one which can store 1024 (2^{10}) single bits of memory. Such a memory would have ten address pins, so that a number up to 1024 (in binary) could be selected resulting in a bit, 0 or 1, appearing on the output pin. A 512 x 4 memory, on the other hand, can store 512 sets of four bits. It would use nine address pins (because 512 is 2^9), and would have four data output pins, with a different bit appearing on each pin. A 128 x 8 memory would be able to store 128 complete 8-bit bytes, with seven address pins (because 128 is 2^7) and eight data pins.

which selects the data of byte number 1 and so on. Nothing is lost, the microprocessor simply runs through all the 128 stored bytes again.

ENTER BUSES

What happens, though, if we need more memory and we use four of these 128 x 8 memories? This is where buses come into the picture. A bus is a set of lines, with each line connecting a pin on the CPU to the corresponding pin on other chips. A data bus will need eight lines, and in our example of a CPU connected to four 128 x 8 memories, each line will connect to five pins, one of the CPU and one from each memory. When you think about it, this is the only way it could be done unless we were prepared to have i.c.'s with hundreds of pins. The address pins also are connected to a bus, this time with sixteen lines. Along each one of these lines, a CPU address pin and an address pin of each memory will be connected.

The problem now is, how do we make sure that the signals go the way we want? After all, if we have four 128 x 8 memories, and we ring up number 6 byte by placing 0000110 on the address lines, won't each memory connect up its number 6 byte to

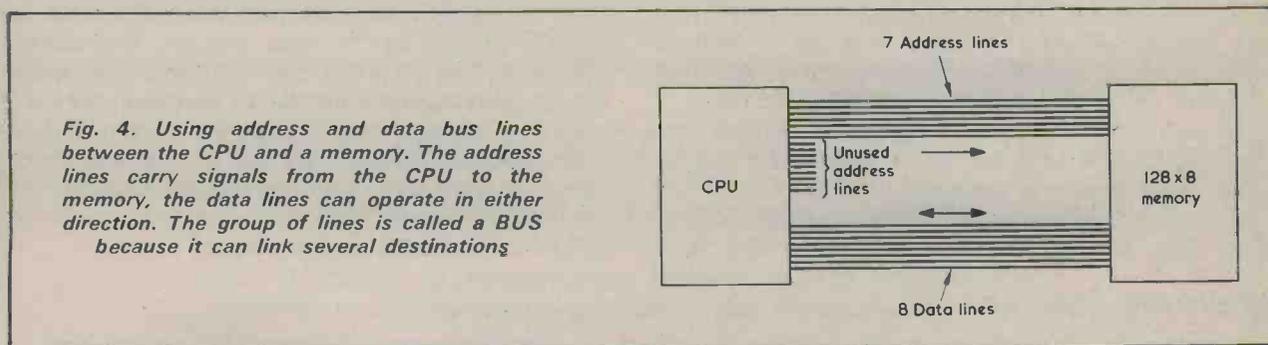


Fig. 4. Using address and data bus lines between the CPU and a memory. The address lines carry signals from the CPU to the memory, the data lines can operate in either direction. The group of lines is called a BUS because it can link several destinations

Now it's easy to see how we could connect a 128 x 8 ROM to the CPU — we would start by connecting the eight data pins of the ROM to the eight data pins of the CPU. The pins are labelled in the same way, so there's not much of a problem about that. How do we connect the address pins, though? A 128 x 8 memory uses only seven address pins, and the CPU has 16, so how do we ensure that the correct connections are made? The answer is simple if only one 128 x 8 memory is connected to the CPU. The seven address lines of the memory are labelled A0, A1 . . . A6 (not to A7, because the first line is, confusingly, A0 rather than A1), and these are connected to the identically labelled pins of the CPU. What about the others? Ignore them! This is possible because with only one ROM, the CPU can count out addresses starting at 0000000 and ending, as far as a 128 x 8 memory is concerned, with 1111111. The next number is 10000000, but the 1 is now on a line which is not connected, and the remaining numbers simply select address 0000000 in the memory. The next count is 100000001,

the data lines?


If this were all there were to it, it would, and the result would be chaos, but there's a way out. It takes the form of a "chip select" signal, which can be as simple as a single pin on the memory i.c., taken to logic 1 if the chip is to be used, and left at logic 0 if the chip is not wanted. With the chip-select pin set to 0, the data output pins are at neither 1 or 0, they are "floating", disconnected, free to take up whatever voltage is on the line to which each one is connected. This sort of system is sometimes called three-state or tri-state logic; as well as 1 and 0 there is an isolated state. This method of switching is extremely useful, as we shall see in other examples.

Returning to the problem of the four 128 x 8 memories, the use of a chip-select pin on each memory allows us to make use of all four memories to give a total of $4 \times 128 = 512$ bytes of memory. The method involves gating, using the outputs of the previously unused address lines. We are using seven address lines, A0 to A6 for the memories, so

RADIO & ELECTRONICS CONSTRUCTOR

IN OUR NEXT ISSUE

SINGLE-CHIP M.W. RADIO

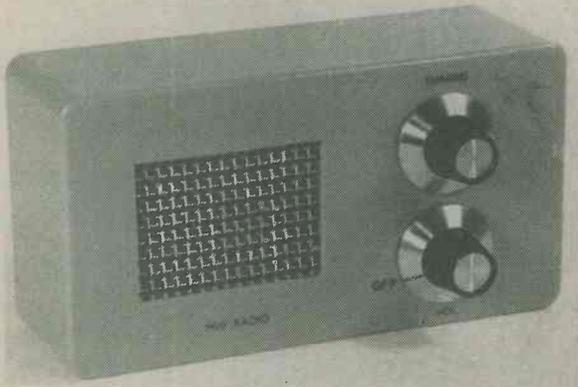

LM389 i.c. gives r.f. gain, a.f. gain and power output

●
Ultra-simple medium
t.r.f. design


●
Easy to construct — Uses
readily available components

●
Inexpensive

PEAK MILLIVOLT ASSESSOR

A.F. Signal Tracer with built-in amplitude assessment

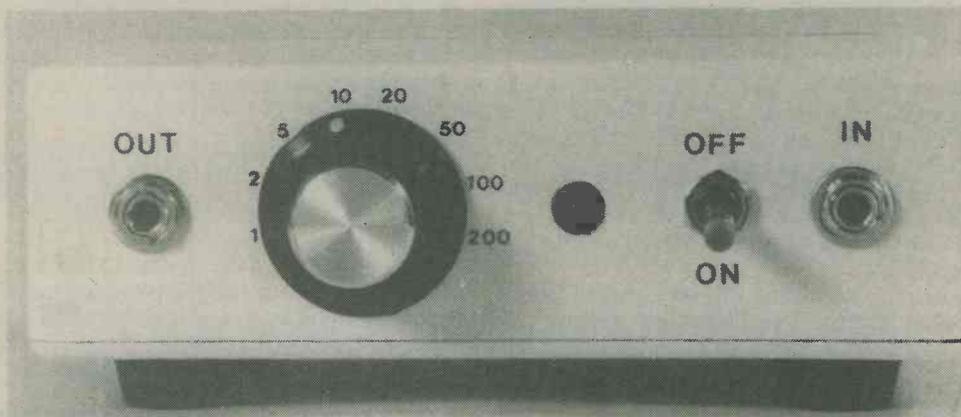This unit is basically a signal tracer but, unlike the normal type of tracer, it incorporates circuitry which enables the operator to assess the amplitude of the input signal.



*CMOS Wire Guard Alarm System
Suggested Circuit*

*Smithy's Reaction Timer
In Your Workshop*


MANY OTHER ARTICLES

ON SALE 4th OCTOBER, 1979

Avoid disappointment — ORDER NOW

SHORT WAVE NEWS

FOR DX LISTENERS

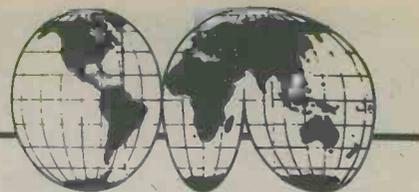

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

What has been happening since last I wrote? Well, apart from some beer brewing and wine making, gardening and watching the local wild life, non-human I hasten to add, some short wave listening was possible at times — but only just!

From correspondence and self observations the country most in the news of late is —

● SOUTH KOREA

My old friend Bob Iball of Worksop has been monitoring Seoul on **6480** for some time and from his observations it seems that Radio Korea operates on this channel from 1600 to 1630 in English to the Middle East and North America; from 1630 to 1700 in French to the Middle East and from 1900 to 1930 in Arabic to the Middle East.

A new correspondent, A. Dupres of Cardiff, reports logging Radio Korea at 2000 on **7550** in English to Africa and Europe and also on **15570** with the Spanish programme to Europe from 2130 to 2200. Just 15 years of age, A.D. is set fair to becoming an experienced SWL and maybe, in time, a good Dxr.

For those of my readers who are interested in logging some of the English transmissions from Radio Korea (afternoon and evening sessions) here is the schedule at the time of writing.

From 1400 to 1430 on **9870**, **11665** and on **12090** to Europe and S.E. Asia; from 1600 to 1630 on **6480**, **9720**, **9870** and on **11830** to the Middle East and N. America; from 1800 to 1830 on **11830** and on **15255** to N. America; from 2000-2030 on **7550**, **9870**, **11525** and on **15570** and from 2300 to 2330 on **7275** and on **7550** to Europe and N. America.

KBS (Korean Broadcasting System) Seoul identifies as "Radio Korea, the Overseas Service of KBS".

● NETHERLANDS ANTILLES

Radio Nederlands Relay, Bonaire, on **9715** at 0550, Dutch pops in a programme for North America (West Coast), scheduled from 0530 to 0625 and also in parallel on **6165**.

● SWITZERLAND

Berne on **9725** at 0606, OM with the French programme to North American (West Coast) scheduled here from 0600 to 0630 and in parallel on **6045**.

● EAST GERMANY

Berlin International on **9730** at 0608, OM with the German programme for East, West and North

West Africa, the Near East and South Arabia, scheduled from 0530 to 0615.

● WEST GERMANY

Berlin on **7285** at 0612, OM with the German programme to South Asia and Australasia, scheduled from 0600 to 0950.

● VATICAN CITY

Vatican on **7250** at 0618, Latin Mass to Europe, scheduled from 0630 to 0700 (to 0715 on Sundays).

● ITALY

Caltanissetta on **7175** at 0622, YL with a talk in a relay of the Domestic Service 2nd Programme to the Mediterranean Basin, scheduled Sundays only on this channel from 0500 to 1300 and from 1330 to 2230. The power is 5kW.

● GREECE

Athens on **7125** at 1923, OM with a local newscast in the English programme for Europe, scheduled from 1920 to 1930 (newscast only).

● CUBA

Havana (via Moscow Relay) on **17710** at 1740, OM and YL alternate with an account of the history of Cuba in the English programme for the Mediterranean Area, scheduled from 1700 to 1800.

● MOROCCO

Rabat on **15155** at 2020, drama in the Arabic Domestic Service, scheduled here from 1900 through to 0100 and in parallel on **21735**.

● IRAQ

Radio Baghdad on **7170** at 2025, OM with a newscast in Arabic in the programme "Voice of Egypt Arabism", scheduled from 2000 to 2200.

● LIBYA

Tripoli on **15100** at 2031, OM with anti-Sadat tirade in Arabic in the programme "Voice of the Arab Homeland" in the External Service, scheduled here from 1700 to 2200. The Domestic Service is relayed here from 0800 to 1700.

● SAUDI ARABIA

Riyadh on **15060** at 1943, OM with a talk about English poets Byron and Shelley in the Arabic Domestic Service, scheduled here from 1500 to 2300.

● KUWAIT

Radio Kuwait on **9840** at 1805, YL with songs then local mx in the Arabic Domestic Service, scheduled from 1600 to 1910 on this channel.

● ISRAEL

Jerusalem on **17630** at 1840, YL with a talk in the Domestic Service Network B programme,

RADIO AND ELECTRONICS CONSTRUCTOR

scheduled here from 0610 to 2310, in Hebrew.

Jerusalem on **17645** at 2002, OM with the English programme for Europe, North America and Africa, news of the peace treaty arrangements. Also in parallel on **17685** but former channel is best for U.K. listeners.

● SOUTH AFRICA

Meyerton on **4835** at 2100, OM with a newscast in English after station identification. The schedule is from 0358 to 0635 (Saturday from 0430, Sunday from 0500), 1520 to 2115 (Saturday until 2205).

● MOZAMBIQUE

Radio Mozambique, Maputo, on **3210** at 2047, YL with folk songs in Portuguese. The schedule is from 0255 to 0530 and from 1630 to 2210 with an English programme from 1800 to 1815. The power is 100kW.

● LIBERIA

ELWA Liberia on a measured **3227** at 2050, OM with a talk in vernacular in the Home Service, scheduled here from 0610 to 0800 and from 1805 to 2220, the power being 10kW.

● MALAGASY

Tananarive on a measured **3287.5** at 2054, piano jazz music in European style. This is the Home Service in French and Malgache, scheduled from 0300 to 0600 and from 1300 to 2100, the power being 100kW.

● GHANA

Accra on a measured **3366** at 2100, African drums, OM with identification and the local news in English. The schedule is from 0530 to 0805 (Saturday and Sunday until 0900), from 1600 to 2305 and the power is 10kW.

● ANGOLA

Radio Nacional, Luanda, on **3375** at 2101, OM in vernacular (presumably the news). The schedule is from 0400 (Sunday from 0430) to 0800 and from 1530 to 2400. This is a Programme in Portuguese except for the period 2100 to 2130 when in Kikongo. The power is 10kW.

● VENEZUELA

Radio Libertador, Caracas, on **3245** at 0223, YL with pop song, OM with announcements in Spanish. The schedule is from 1000 to 0400 and the power is 1kW.

Radio Bolivar, Ciudad Bolivar on 4770 at 0253, Latin American music, OM announcements in Spanish. The schedule is from 1000 to 0300 and the power is 1kW.

Radio La Puerto la Cruz, Puerto la Cruz, on **3365** at 0232, local pops, OM with announcements in Spanish. The schedule is from 1000 to 0400 and the power is 1kW.

● ECUADOR

Radio Iris, Esmeraldas, on **3380** at 0237, pop records local style, OM with announcements in Spanish, several mentions of Esmeraldas (local addresses). The schedule is from 1100 to 0300 (closing time is variable) and the power is 10kW.

Radio Zaracay, Santo Domingo, on **3390** at 0239, local pops on records with OM announcer in Spanish. The schedule of this one is from 1000 to 0500 but the closing time is variable. The power is 10kW.

La Voz de Galapagos, Isla San Cristobal, on **4810** at 0302, OM with love song after OM announcer with identification. The schedule is from 1215 to 1430 and from 2300 to 0400 (but sometimes closes at 0430). The power is 5kW.

La Voz de Los Caras, Bahia de Caraquez, on **4795** at 0417, YL with a song in typical Ecuadorian style — pop version — after OM with identification. The schedule is from 1300 to 0400 (Sunday until 0520 — which is the day I logged it, catching up on lost sleep the same afternoon!) The power is 3kW.

● BRASIL

Radio Rural de Santarem, Santarem, on **4765** at 0250, YL with a religious talk in Portuguese. This one has a schedule from 0800 to 0400 and the power is 10kW.

Radio Brasil Central, Goiania, on **4985** at 0240, OM with guitar and a ballad about unrequited love. This station has a 24-hour schedule and the power is 5kW.

● BOLIVIA

Radio Nueva America, La Paz, on a measured **4797** at 0255, YL with love song in Spanish, orchestral music, identification. The schedule is from 1030 to 1830 and from 2100 to 0400 (Sunday to 0200) and the power is 1kW.

● COLOMBIA

Emisora Meridiano 70, Arauca, on **4925** at 0318, OM with announcements in Spanish, dance music 1930's style, identification 0324 "Somos Emisora Meridiano 70 de Arauca". The schedule is from 1000 to 0330 (Saturday until 0500) and the power is 1kW. The frequency of this one is apt to vary from that above to **4930** and it sometimes identifies as Radio Centro!

● NOW HEAR THIS

Radio Ondas del Huallaga, Huanaco, Peru, on **3330** at 0410, OM with announcements in Spanish, short musical excerpts — more talk than music — mostly noticias. The schedule is from 1015 to 0600 but closing can vary from 0400 to 0900. The power is just 0.5kW.

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is 63p, inclusive of postage and packing.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

10 Watt VMOS Amplifier

By R. A. Penfold

It is now possible to design amplifiers having output stages incorporating VMOS power field-effect transistors in the output stage, and it is a simple VMOS Class B amplifier which is described

Power f.e.t. Class B output with negative temperature coefficient

Virtually all contemporary audio power amplifiers have a Class B bipolar transistor output stage, the main exceptions being a few valve designs and designs which incorporate transistors in modes other than Class B. But it is now possible to design amplifiers having output stages incorporating VMOS power field-effect transistors in the output stage, and it is a simple VMOS Class B amplifier which is described in this article.

TEMPERATURE COEFFICIENT


One of the important advantages of a VMOS device in this type of circuit is its negative temperature coefficient, which gives better thermal stability than is possible with positive temperature coefficient bipolar transistors. Problems with thermal stability arise due to the need for a small quiescent current through the output transistors to combat the effects of crossover distortion. Since bipolar transistors have a positive temperature coefficient, this bias current tends to increase when the amplifier has been in use for a while and the output transistors have become heated up. The increased bias current causes more heating of the output transistors and, in turn, a further increase in the bias current. Unless suitable precautions are taken, this regenerative effect could continue to the point where the dissipation in the output stage becomes excessive, leading even to the possibility of the output transistors becoming destroyed. In order to overcome this thermal runaway problem it is usually necessary to employ what is virtually the

lowest acceptable initial bias current and to incorporate some form of thermal stabilization circuit.

These difficulties do not exist with power f.e.t.'s because a rise in their temperature merely alters the bias characteristic so that there is a marginal reduction in the current flowing under quiescent bias conditions. It is by no means essential to incorporate any thermal stabilization circuitry in an f.e.t. Class B design, nor is it necessary to use a bias which causes a minimal standing current. It is perfectly in order to have a comparatively high initial standing current which falls to a lower but still more than adequate level after the amplifier has been in use for some time.

Another advantage of power f.e.t.'s over bipolar output devices is the far lower drive current requirements of the former compared with the latter. Whereas a simple bipolar Class B amplifier having an output power of, say, 10 watts r.m.s. would need a driver stage operating at a collector current in the region of 50mA, an f.e.t. design could, if desired, operate from a driver stage having a collector current of only a fraction of a milliamp. Darlington pairs or equivalent configurations are often used in output stages to reduce the drive current requirement, but even these need more input current than do power f.e.t.'s.

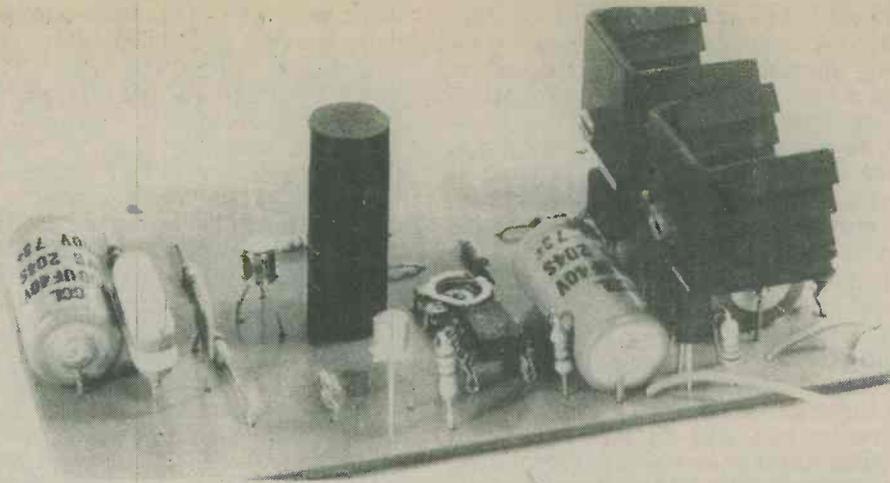There are disadvantages with VMOS devices in Class B audio output stages, one of these being that they are slightly less efficient than bipolar transistors. This is not a major drawback, however, and simply means that the power supply has to provide



The amplifier is assembled on a small printed circuit board having dimensions of $4\frac{1}{2}$ by 3in.

a slightly higher supply voltage to produce the same output power into a given load impedance. A second disadvantage is not due to the power f.e.t. in itself but arises from the present availability of these devices. Only n-channel VMOS devices are generally available at the time of writing, which means that a quasi-complimentary arrangement instead of a true complementary output stage must be used.

QUASI-COMPLEMENTARY CIRCUIT

A representative quasi-complementary circuit which was popular in the earlier days of transistor amplifiers before proper complementary n.p.n. and p.n.p. devices became available is shown in Fig. 1(a). In this diagram, both the output transistors are n.p.n. devices. TR1 is a simple emitter follower which supplies the high output current required by the load on positive-going output excursions. Being

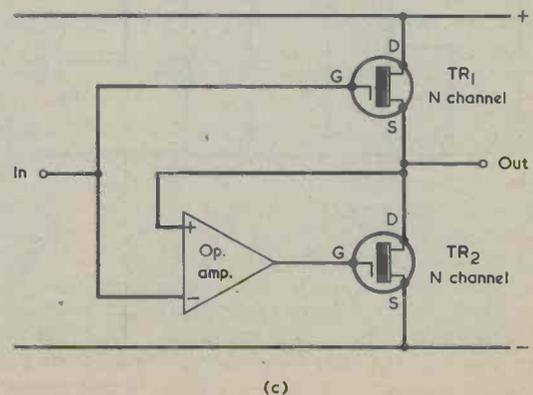
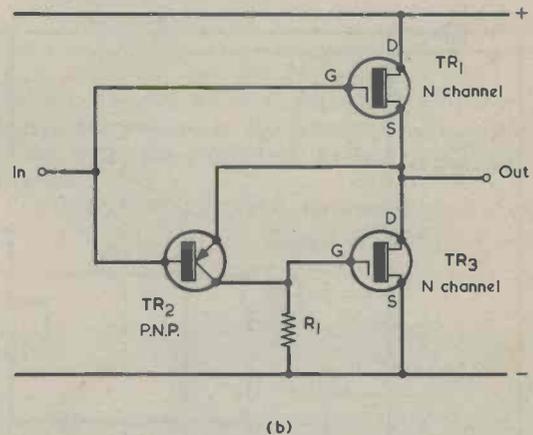
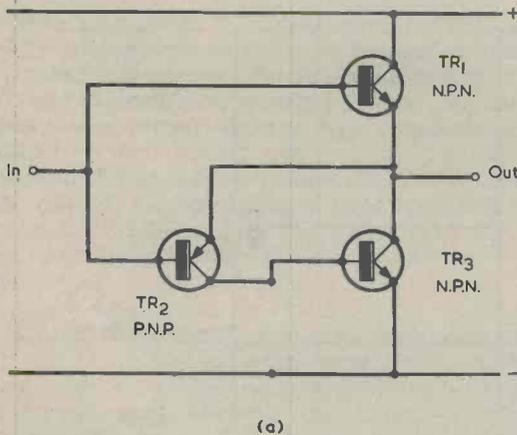


Fig. 1(a) A quasi-complementary a.f. output stage which allows the two output transistors to have the same polarity
 (b) Employing a similar approach when the two output transistors are n-channel VMOS devices
 (c) An alternative method of driving the lower transistor, using an operational amplifier

an emitter follower it has only about unity voltage gain and its input and output are in phase.

It is necessary for the lower half of the output stage to provide a high output current on negative-going excursions and to have the same basic characteristics as an emitter follower. An n.p.n. emitter follower cannot be employed because it would have the wrong polarity. If the lower transistor had its emitter connected to the negative supply rail and its collector connected to the output load the supply polarity would be correct but the transistor would not operate like an emitter follower. Apart from any considerations of gain, the transistor would function in the common emitter mode and its output at the collector would be out of phase with its input at the base.

The configuration can still be made to work, however, by adding another transistor, TR2, ahead of the output transistor. The added transistor is a small p.n.p. type which is also in the common emitter mode and, since both transistors invert the signal the output is now in phase with the input at TR2 base. Also there is 100% negative feedback between TR2 and TR3, so that the two transistors give the same unity voltage gain as does the single emitter follower used in the upper section.

Fig. 1(b) shows the same approach with an output stage having two n-channel VMOS devices, TR1 and TR3, and the p.n.p. bipolar transistor, TR2. TR1 is now a source follower and TR3 a common source amplifier, and at first sight the circuit should function in the same manner as the previous one. R1 is added to provide a collector load resistance for TR2, and is necessary because the input impedance of TR3 is far too high to provide suitable loading.

In practice the arrangement of Fig. 1(b) does not

work very well. This is because on high negative-going current peaks, which are required to be well in excess of 1 amp, the drain of TR3 should fall to about 2 volts positive of the negative rail; whilst the gate voltage needed to produce these current peaks is of the order of 5 to 10 volts positive of the negative rail. Since TR2 collector must always be negative of its emitter the maximum output current from TR3 is limited to a level at which TR3 drain is slightly positive of its gate, and the result is poor efficiency and high dissipation in TR3. This problem does not arise in the circuit of Fig. 1(a) because the bipolar TR3 here can draw a very high collector current when its base is only about 0.7 volt positive of the negative rail.

Attempts made by the author to modify the basic circuit to give an improved performance were not successful, and so the unusual arrangement of Fig. 1(c) was tried instead. Here, the lower output transistor is preceded by an operational amplifier. This circuit provides unity voltage gain due to the 100% negative feedback given by connecting the drain back to the non-inverting input of the op-amp. Note that the signal is inverted in TR2 and so the feedback is applied to the non-inverting input of the op-amp, and not the inverting input as would normally be the case. The input signal is applied to the inverting input, and the dual inversions in the i.c. and in TR2 give the required phase relationship between input and output. The output of the op-amp can swing to virtually the full positive supply rail voltage, which is much more than is required to drive TR2 into saturation.

Although rather novel, the arrangement of Fig. 1(c) is found to give extremely good results in practice, and is that employed in the final amplifier circuit.

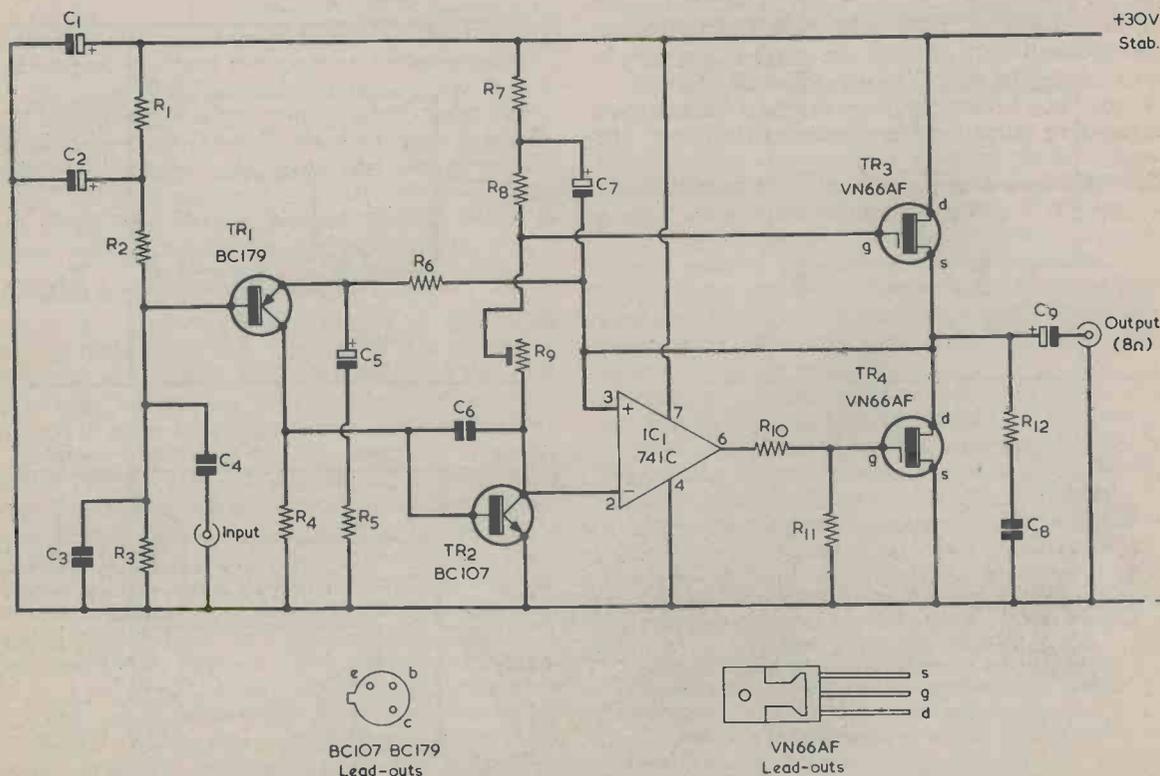


Fig. 2. The circuit of the VMOS Class B amplifier. A stabilized 30 volt supply enables an r.m.s. output power of 10 watts to be given

FULL CIRCUIT

The full circuit of the VMOS amplifier is given in Fig. 2. The output stage is very much as has just been described, the main difference being the inclusion of the potential divider, R10 and R11, between the output of IC1 and the gate of TR4. This potential divider is needed because the negative output swing of the 741 employed is limited to about 2 volts positive of the negative rail which, if applied direct to the gate of an output f.e.t. which happened to have a low gate threshold voltage, could bias the f.e.t. quite hard on. The potential divider ensures that TR4 can be biased to the off state. At the same time, its values are such that TR4 can still be turned hard on when the output of IC1 swings positive.

C9 is the output d.c. blocking capacitor. R12 and C8 form a Zobel network which contributes to the stability of the circuit.

TR1 is a common emitter input transistor which is directly coupled to the common emitter driver transistor, TR2. There is virtually 100% d.c. negative feedback applied to the overall amplifier through R6, with R2 and R3 biasing the input (and consequently the output) to about half the supply voltage. R1 and C2 are smoothing components which prevent hum and noise from the supply being applied to the amplifier input by way of R2 and R3. C4 provides d.c. blocking at the input, and C3 is an r.f. filter capacitor which aids stability. So also does C6, which rolls off the very high frequency response of TR2.

R8 is the main collector load for TR2, whilst pre-set potentiometer R9 is adjusted to provide the desired quiescent bias for the output stage. C7 and R7 are bootstrapping components and they allow the upper end of R8 to go positive of the positive supply rail during positive output voltage excursions. This bootstrapping is essential because, if the positive voltage at TR3 gate were limited to the positive supply rail voltage, the minimum drain-to-source voltage across TR3 would be as high as 8 to 10 Volts. The bootstrapping allows a comfortably high positive output voltage to be available at TR3 source.

Since C5 has a low reactance at audio frequencies, the a.f. feedback components consists of R6

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

- R1 18k Ω
- R2 100k Ω
- R3 100k Ω
- R4 680 Ω
- R5 56 Ω
- R6 1k Ω
- R7 680 Ω
- R8 6.8k Ω
- R9 2.2k Ω pre-set potentiometer, 0.1 watt horizontal.
- R10 4.7k Ω
- R11 5.6k Ω
- R12 2.2 Ω

Capacitors

- C1 100 μ F electrolytic, 40V Wkg.
- C2 100 μ F electrolytic, 40V Wkg.
- C3 180pF ceramic plate
- C4 0.47 μ F type C280
- C5 150 μ F electrolytic, 25V Wkg. (see text)
- C6 10pF polystyrene or ceramic plate
- C7 100 μ F electrolytic, 25V Wkg.
- C8 0.1 μ F type C280
- C9 1,000 μ F electrolytic, 25V Wkg.

Semiconductors

- TR1 BC179
- TR2 BC107
- TR3 VN66AF
- TR4 VN66AF
- IC1 741 in 8-pin d.i.l.

Miscellaneous

- Printed circuit board
- Heatsink (see text)
- Wire, solder, etc.

and R5. The a.c. voltage gain of the amplifier is approximately equal to R6 divided by R5, or about 18 times with the specified values for these components.

With a 30 volt supply the amplifier will give an



The components are laid out neatly on the board without cramping

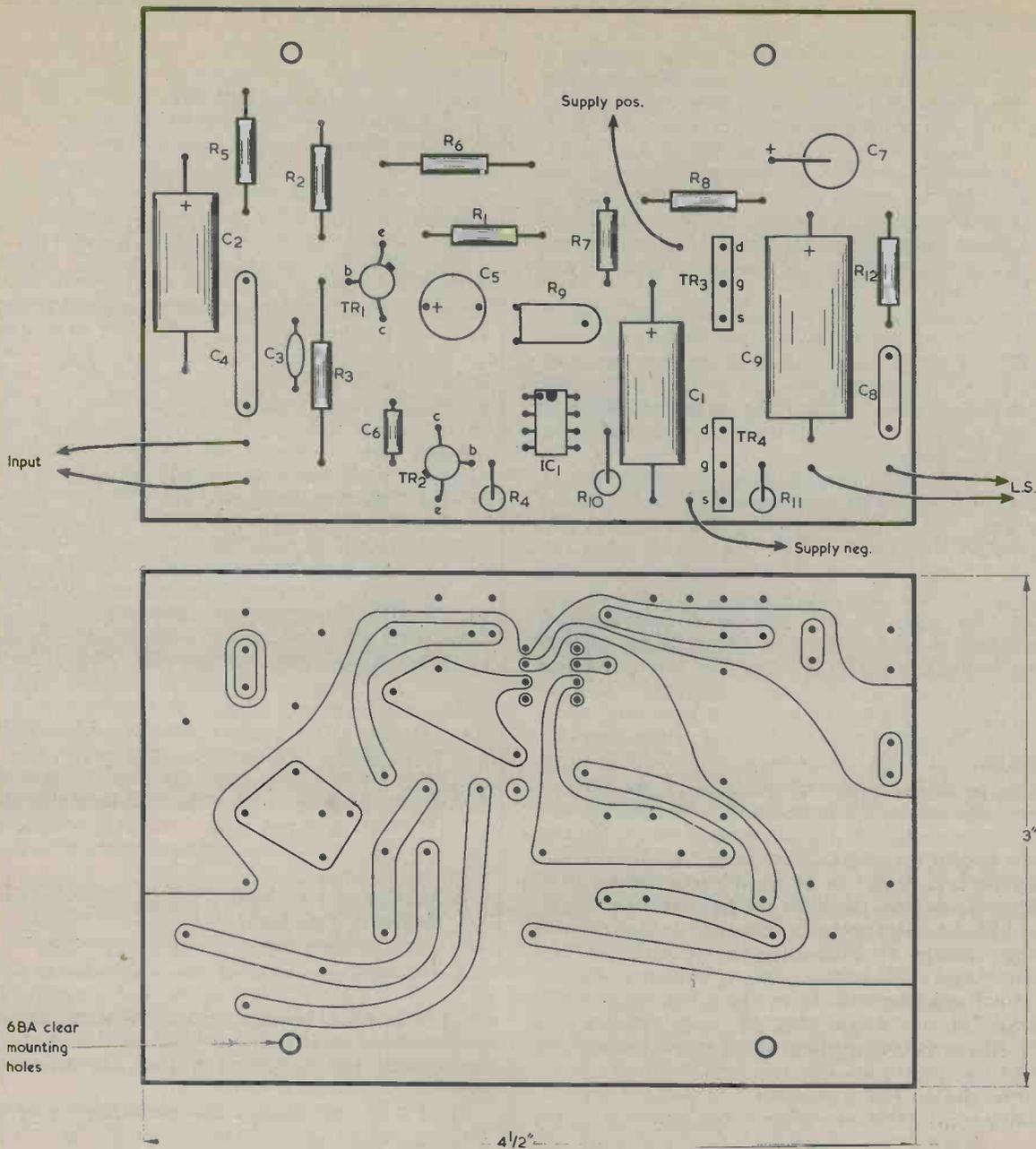


Fig. 3. Component and copper sides of the printed circuit board. This is reproduced fullsize

output of approximately 10 watts r.m.s. into an 8Ω loudspeaker, and about 500mV r.m.s. is needed at the input to fully drive the circuit. The gain can be proportionally increased or decreased by reducing or raising (respectively) the value of R5, but this value should not be greatly altered from the specified figure. Large alterations could result in either instability or a loss of output quality.

The signal-to-noise ratio of the prototype is slightly better than -80dB (unweighted, with input

open-circuit). The distortion performance is roughly comparable to simple Class B bipolar designs with a t.h.d. level of 0.1% or less at most output powers, although it is slightly higher just below the onset of clipping. Of course, as clipping commences the distortion level increases very rapidly.

The VMOS transistors specified for TR3 and TR4 are available from Maplin Electronic Supplies.

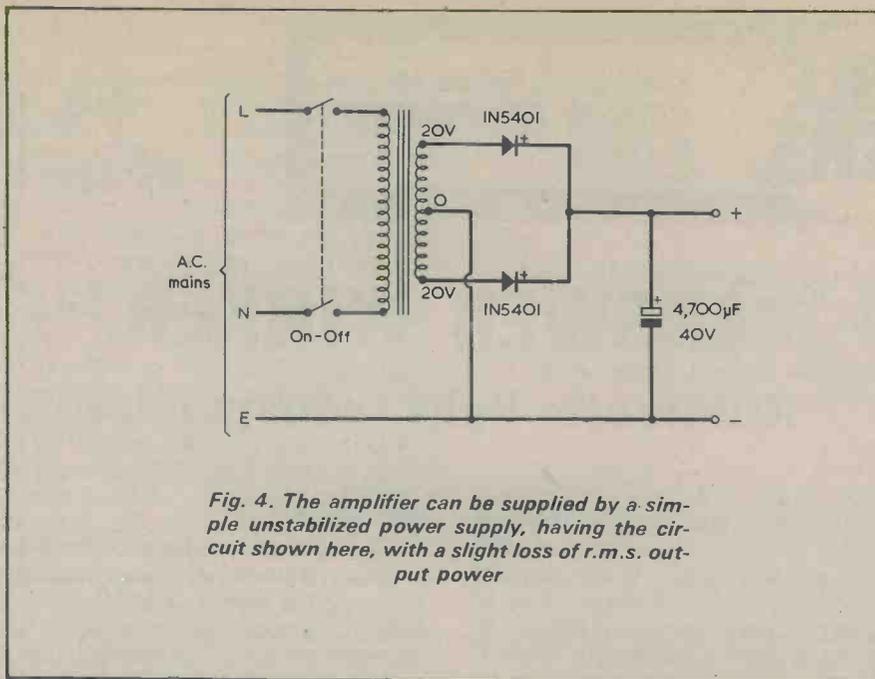


Fig. 4. The amplifier can be supplied by a simple unregulated power supply, having the circuit shown here, with a slight loss of r.m.s. output power

CONSTRUCTION

A suitable printed circuit board design for the amplifier is shown full size in Fig. 3, which illustrates both the component layout and the copper pattern.

TR3 and TR4 require a substantial amount of heatsinking, which can be provided by a large commercially made heatsink. The heat-tabs of the transistors are internally connected to the drain terminals, and so an insulating set or sets will be required if the transistors share a common heatsink. The heatsinks visible in the photographs of the amplifier are type FL57M, available from Maplin Electronic Supplies. These are just adequate with ordinary speech and music signals, but they allow the output transistors to become rather hot when running the amplifier at full power with a sine wave input.

The input leads can be unscreened if they are short and there is no risk of hum pick-up. Most constructors will prefer screened cable here, and the braiding should, of course, connect to the copper area which is common with the negative supply rail, and the centre conductor to C4. If the board is mounted in a metal case, the case should be connected to the negative rail.

The capacitor employed in the prototype for C5 was a "single-ended" type with both lead-outs appearing at one end. A normal capacitor with lead-outs at both ends may be employed instead, if desired, with the negative end nearer the board and the positive lead-out taken down the side of the component.

Before applying power to the completed amplifier, R9 should be set to insert minimum resistance into circuit. This is given when its slider is adjusted fully clockwise. A testmeter switched to a high current range (to avoid the risk of damage to the meter in case of a fault in the amplifier and also to allow for initial surge current when the electrolytic capacitors charge up) is inserted in the

positive supply lead. When indications show that it is safe to do so the testmeter is switched to a range which allows a clear reading of 30mA, after which R9 slider is adjusted in an anti-clockwise direction until 30mA is indicated. The testmeter is removed and the amplifier is then ready for use.

POWER SUPPLY

Ideally, the amplifier should be powered by a stabilized supply offering 30 volts at a mean current of at least 600mA, or 1.2 amps if two amplifiers are used in a stereo system. A non-stabilized supply can be used provided that it gives an output voltage of no more than about 32 to 33 volts under quiescent conditions.

The circuit of a suitable non-stabilized supply is shown in Fig. 4. The transformer secondary should be rated at 1 amp or more and the two diodes provide full-wave rectification. The large-valve reservoir capacitor gives a considerable degree of smoothing and there is a reasonably low ripple content on the output. A suitable mains transformer having two 20 volt 1 amp secondaries is listed in the Maplin Electronic Supplies catalogue.

Since a mains transformer usually offers slightly more than its nominal secondary voltage under low current conditions, the power supply quiescent output voltage will be slightly in excess of 30 volts, this dropping by several volts when the amplifier is fully driven by a sine wave signal. This will cause the amplifier to deliver a little less than 10 watts r.m.s. with a sine wave input, although with a normal music signal the output power will not be significantly different to that obtained when using a 30 volt stabilized supply.

The same power supply may be used for two amplifiers in a stereo system but the mains transformer secondary should then be rated at 2 amps or more.


ANSWER WINKER

Automatic light transponder

The rather unusual circuit described in this last article in the "Double Deccer" series can be used simply as a piece of fun, but it has serious applications because the circuit is a simple type of transponder — a circuit that replies to a signal. In our circuit a light beam from a torch will, when it strikes the photocell, cause the circuit to be triggered and after a short time delay the lamp in the circuit flashes back an acknowledgement. This simple circuit shows the basic principles of transponder action, which was first extensively used in World War II for I.F.F. (Identification, Friend or Foe). With this system a transmitter on a British aircraft sent out a signal which would trigger a transponder on any other British aircraft. The transponder would then send out a coded signal on another frequency, and reception of the correct signal would cause the "friend" signal to light on the equipment. No reply would cause the "foe" warning to be flashed.

PHOTOCELL

The circuit consists of a photocell and amplifier, a delay monostable, a signal monostable and a lamp-driver stage. The photocell is the familiar ORP12 light dependent resistor, which is connected in series with a 10k Ω variable resistor, VR1, acting as the sensitivity control. When the photocell is in darkness its resistance is high, so that TR1 is switched on and bottomed. Resistor R1 ensures that excessive current doesn't flow in VR1 or TR1 if the potentiometer is incorrectly adjusted. In darkness, therefore, the collector voltage of TR1 is very low and, since TR1 collector is directly connected to TR2 base, TR2 will be cut off. Its collector voltage is then high and is at the potential of the positive supply rail. When a beam of light strikes the photocell its resistance decreases, causing TR1 to cut off and its collector voltage to rise. This turns on TR2, causing a rapid drop in the voltage at TR2 collector.

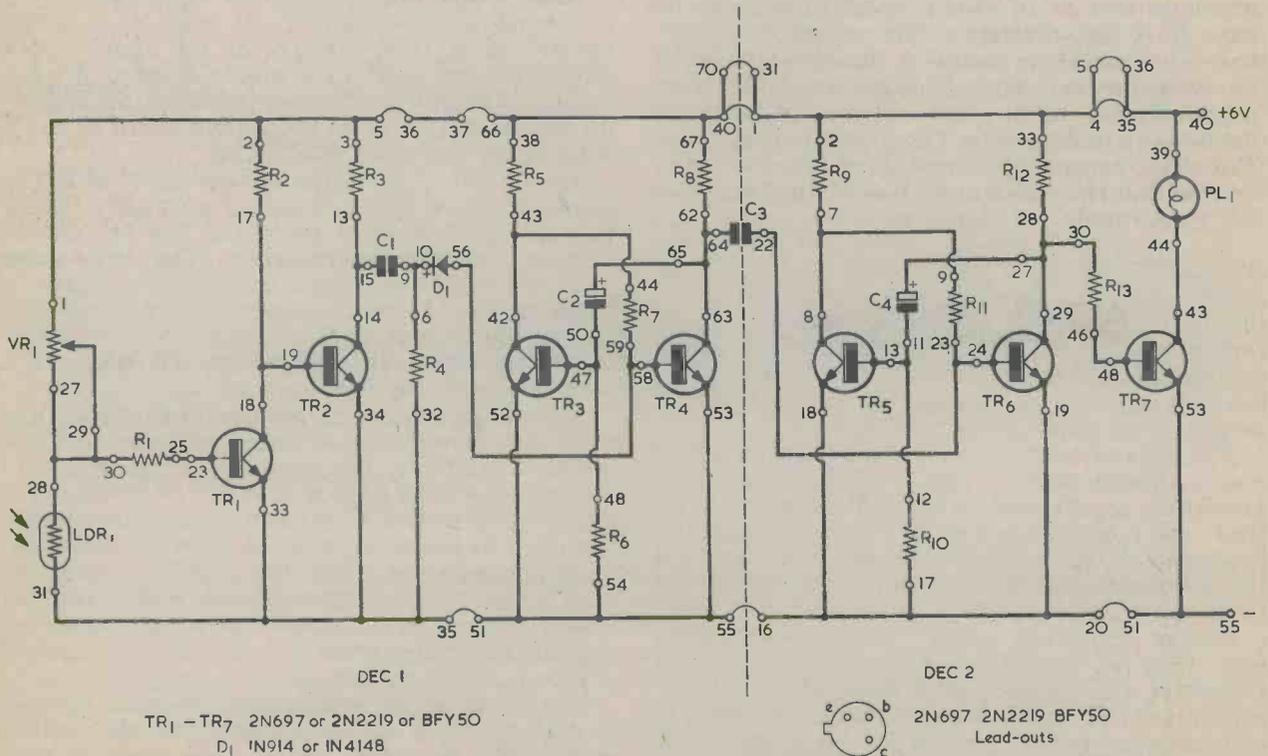

TR₁ - TR₇ 2N697 or 2N2219 or BFY50
D₁ IN914 or IN4148

2N697 2N2219 BFY50
Lead-outs

Fig. 1. Full circuit of the answer winker. This transponds by lighting up PL1 a short time after LDR1 has been interrogated by a light beam

Looking now at the next stage, TR3 and TR4 are connected in a simple monostable circuit. The collector of TR3 is directly coupled through R7 to the base of TR4, so that in the absence of any signals through diode D1, current flows through R5 and R7 into the base of TR4, keeping this transistor turned fully on. The collector of TR4 couples via C2 to the base of TR3. This base is normally held at the potential of the negative rail by R6, causing TR3 to be cut off. In consequence, TR3 collector is at a high voltage, keeping TR4 turned on.

A negative pulse fed into this part of the circuit from the collector of TR2 via C1 and D1 will turn off TR4, so that its collector voltage rises and takes TR3 base positive by way of C2, turning TR2 on. TR3 collector voltage becomes very low, keeping TR4 cut off. If TR2 collector should now happen to go positive it will have no effect on TR4 because D1 will then be reverse biased.

C2 charges through R8, the base-emitter junction of TR3 and R6, and when it has become sufficiently charged the base voltage of TR3 will fall sufficiently for this transistor to cut off again. Its collector voltage rises, allowing TR4 to turn on again, whereupon the charged C2 ensures that TR3 is completely cut off. The positive feedback which is present in all these switching circuits, bistable or astable, causes this changeover to be very rapid. The output of the circuit is therefore a negative-going pulse edge at the collector of TR4. The time preceding the pulse is mainly determined by the values of C2 and R8, and is only slightly affected by the value of R6. After the production of the negative-going pulse, C2 discharges via the fully turned-on TR4 and R6.

SECOND MONOSTABLE

The second monostable stage consisting of TR5 and TR6 is identical, with TR6 being the transistor which is normally turned on. A positive-going pulse edge from TR4 collector has no effect on TR6 because it merely increases its base current due to the consequent charging current through C3. But a negative-going pulse, which appears at the end of the delay period given by TR3 and TR4, will cut off TR6. This causes the second monostable to switch over so that the collector voltage of TR6 goes high for a time mainly dependent on the values of C4

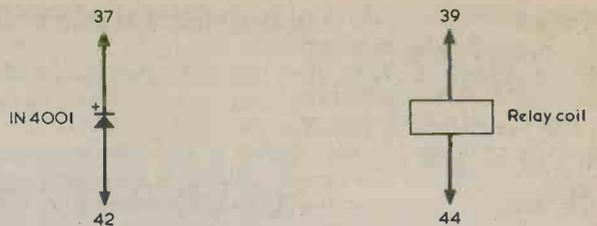


Fig. 2. A relay coil can be connected in place of PL1. It may have an operating current of 12 to 70mA and should energise reliably at 6 volts. Also required with the relay is a protective diode, which must be connected into circuit with correct polarity

and R12. After this period TR6 conducts again, and its collector voltage remains low until the circuit is triggered again.

With TR6 collector voltage in its normal low state no current flows in R13, and TR7 is cut off. When TR6 cuts off, current flows through R12 and R13 into the base of TR7, turning on this transistor and causing the lamp to light. As in previous Double Deccer circuits a relay could also be operated if a different type of response were wanted. The relay coil and protective diode are connected into the circuit as shown in Fig. 2.

The overall action of the complete circuit is, therefore, that a beam of light on the photocell will not produce an immediate effect but, after a short time, will cause the lamp to light. The lamp remains lit for a further short time and then extinguishes. It remains unlit until the photocell is again illuminated, after having been in darkness sufficiently long for the circuit to reset.

CONSTRUCTION

Join the two S-DeCs together to form one long DeC, and insert all the wire links. Capacitor C3, which bridges the two DeCs, should also be inserted at this stage. The front panel of one DeC can be used to take the lampholder and VR1, and these should be connected into the DeCs using single-core wire. The photocell LDR1 can be plugged directly into the S-DeC, with short extension leads

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

- R1 4.7k Ω
- R2 4.7k Ω
- R3 4.7k Ω
- R4 150k Ω
- R5 1.8k Ω
- R6 56k Ω
- R7 56k Ω
- R8 1.8k Ω
- R9 1.8k Ω
- R10 56k Ω
- R11 56k Ω
- R12 1.8k Ω
- R13 4.7k Ω

VR1 10k Ω potentiometer, linear

Capacitors

- C1 0.1 μ F polyester
- C2 470 or 500 μ F electrolytic, 10V. Wkg.
- C3 0.1 μ F polyester
- C4 470 or 500 μ F electrolytic, 10V. Wkg.

Semiconductors

- TR1-TR7 2N697 or 2N2219 or BFY50
- D1 1N914 or 1N4148

Photocell

- LDR1 ORP12

Lamp

- PL1 6V 60mA, m.e.s.

Miscellaneous

- 2-off S-DeC
- 6V battery
- Lamp holder, m.e.s.
- Control knob

soldered on as necessary. Remember that stranded wire must not be inserted into the holes in the S-DeCs unless it has been tightly twisted and soldered to prevent it tangling.

The remaining capacitors and the diode D1 can now be plugged into place. The diode and capacitors C2 and C4 are all polarised components which must be connected the correct way round. The seven transistors can now be plugged into their positions, remembering that the monostables are constructed with the "mirror-image" type of layout in which the emitter leads are inserted in a centre line of the DeC. The resistors can now be added, and the answer winker is ready to transpond.

TESTING

Adjust VR1 so that it inserts maximum

resistance into circuit and take the unit into a dimly-lit room with its light switched off. Connect the battery. There should be no response. Now shine a torch on the photocell or turn the main room light on and off briefly. After a short delay, PL1 should light and stay illuminated for a short time. If there is no response, as may happen if the torch light is not bright enough or the light is some distance from the photocell, then VR1 can be adjusted until the unit triggers on the desired signal. If the room lighting is not particularly dim, VR1 will have to be adjusted to a level where only the torch beam will trigger the circuit. Avoid adjusting VR1 so that it inserts very low values of resistance into circuit if the photocell should happen to be very brightly illuminated, say by direct sunlight. ■

CALCULATOR TOPIC

By Recorder

It is the second calculator which is giving the wrong answer. Not, I must hasten to add, because it is producing a numerical error but simply because it does not possess the logic to deal with mixed additions and multiplications.

When you are confronted with a problem containing additions, subtractions, multiplications and divisions, the multiplications and divisions *must* be completed first before tackling the additions and subtractions. So, with the problem "2 plus 3 times 4 equals" the correct sequence is to multiply 3 by 4, to give 12, and then add the 2, resulting in an answer of 14. The powerful TI-57 has what is described by Texas as "AOS" (which stands for Algebraic Operating System) and the AOS circuits sort out all the multiplications and divisions before even starting on the additions and subtractions.

Not so with the low cost calculator. This inexpensive machine merely does the last thing it has been told to do. When presented with "2 plus 3" its little brain chugs away and produced the answer, 5. If it is next told "times 4 equals", it says to itself: "Well, I've got 5 stored away in my little memory, so if the Master wants this multiplied by 4 I'll do just that for him. No problem." And, obligingly, it displays the number 20.

All this shows that you have to take a little care when working out problems with the more inexpensive type of calculator. If it can't sort out the hierarchy of multiplications, divisions, additions and subtractions, then you have to do the sorting out for it by getting the multiplications and divisions out of the way first. If you present our little problem in the form "3 times 4 plus 2", even the most elementary electronic calculator should give you the correct solution of 14. ■

Swindling a computer appears at first sight to be an awesome task, but it seems that there are quite a few nefarious characters who profit more than adequately from hoodwinking these poor old machines. As if they haven't got enough to do as it is, sorting out all the problems with which they are presented and having nothing better than simple binary to carry out their tasks.

In America (where else?) one gentleman opened a bank account, then proceeded to take away with him a wad of paying-in slips which were left out for the convenience of the bank's customers. The next part of the story becomes a little vague, so far as the more precisely-minded amongst us are concerned, because the procedure adopted is described by non-technical newsmen. At any event, the trickster is reported as having managed to impress on the paying-in slips the magnetic coding corresponding to his own account number. He then returned the paying-in slips and left them lying around in the bank. The slips were next picked up by unsuspecting bank clients who entered on them the details of the amounts they were depositing. But when the paying-in slips were fed into the computer all the deposits were routed into the account of the swindler.

After a sizeable sum had been credited in this manner he simply withdrew a hundred thousand dollars and quietly disappeared back into the woodwork.

Many of us do not have access,

either legally or illegally, to full-sized computers, but a number of us are now playing around with microprocessors, and we nearly all are the proud possessors of pocket calculators.

Is it possible for two different models of calculator to give different answers to the same problem? It quite definitely is, as I've proved to my own satisfaction with a very respectable calculator and another calculator which falls into the bargain basement category. The first calculator is the Texas Instruments Programmable TI-57 (which I acquired after Ian Sinclair's "Tune-In To Programs" series started in this journal) and the second is a much simpler calculator which was on offer at a stationer's for £6.50. That calculator was quite a bargain too, as it happened, since the price included a "mains adaptor" comprising a mains transformer and rectifier for charging the calculator battery. The inexpensive calculator adds, subtracts, multiplies and divides perfectly and, for me, has the great advantage of possessing a square root facility. I shudder to think of the hours I have wasted in the past working out square roots, either the long way or with logs, when sorting out resonant frequencies and things like that.

If I present the simple problem "2 plus 3 times 4 equals" to the Texas calculator it at once tells me that the answer is 14. And if I present the same problem to the £6.50 job it just as quickly flashes up an answer of 20! Which calculator is wrong?

THE "DORIC"

9 WAVEBAND

Part 3

PORTABLE

By Sir Douglas Hall, Bt., K.C.M.G.

Initial steps in constructing the a.m.-f.m. tuner.

Next follows the medium, long and v.h.f. tuner part of the complete "Doric" receiver. This tuner may be employed as a receiver on its own, feeding a pair of standard 8 stereo headphones, or it can be coupled to the amplifier and short wave receiver assembly to produce a comprehensive receiver covering the short wave bands, medium and long waves, and v.h.f. band II.

CIRCUIT DIAGRAM

The circuit of the tuner is shown in Fig. 7, and in this TR7 and TR8 form the reflexed v.h.f. section, and TR5 and TR6 the reflexed medium and long wave section. Both sections use a common emitter follower to couple their outputs to the stereo phones or to the amplifier and short wave receiver

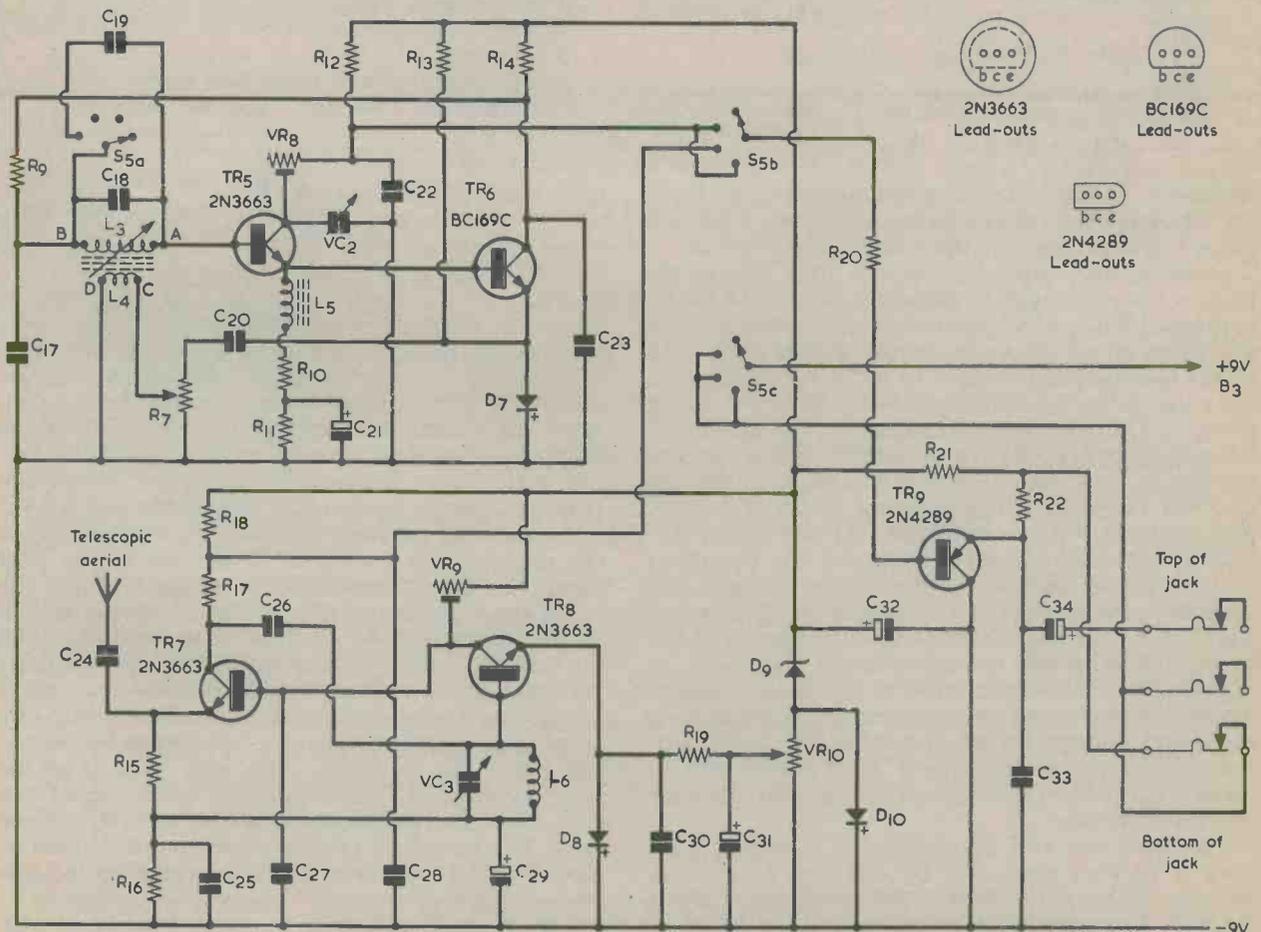


Fig. 7. The circuit of the v.h.f. and medium and long wave tuner. Potentiometers VR7 and VR10 are ganged

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 10%)

R9 10k Ω	R16 3.9k Ω
R10 22 Ω	R17 1k Ω
R11 6.8k Ω	R18 18k Ω
R12 15k Ω	R19 1.2k Ω
R13 39k Ω	R20 27k Ω
R14 47k Ω	R21 1.5k Ω
R15 220 Ω	R22 3.9k Ω

VR7, VR10 4.7k +4.7k Ω dual potentiometer, linear, type JP20 (Electrovalue)

VR8 22k Ω pre-set potentiometer, 0.25 or 0.3 watt, horizontal

VR9 220k Ω pre-set potentiometer, 0.25 or 0.3 watt, horizontal

Inductors

L3, L4 see text

L5 2.5mH r.f. choke (Repanco)

L6 see text

Semiconductors

TR5 2N3663 (Electrovalue)

TR6 BC169C

TR7 2N3663

TR8 2N3663

TR9 2N4289

D7 OA10

D8 OA90 or OA91

D9 BZY88C6V2

D10 1S44

Switch

S5 3-pole 4-way rotary, miniature

Socket

Stereo jack socket (see text)

Capacitors

C17 1,000pF silvered mica or ceramic

C18 47pF silvered mica or ceramic

C19 680pF silvered mica or ceramic

C20 0.01 μ F polyester

C21 22 μ F electrolytic, 3V. Wkg.

C22 1,000pF silvered mica or ceramic

C23 1,000pF silvered mica or ceramic

C24 100pF silvered mica or ceramic

C25 1,000pF silvered mica or ceramic

C26 2.2pF silvered mica or ceramic

C27 1,000pF silvered mica or ceramic

C28 1,000pF silvered mica or ceramic

C29 100 μ F electrolytic, 10 V. Wkg.

C30 6.8pF silvered mica or ceramic

C31 220 μ F electrolytic, 3 V. Wkg.

C32 100 μ F electrolytic, 10 V. Wkg.

C33 1,000pF silvered mica or ceramic

C34 220 μ F electrolytic, 10 V. Wkg.

VC2 20pF mica trimmer

VC3 15pF variable, type C804 (Jackson)

Aerial

Telescopic aerial type TA10 (Eagle-Electrovalue)

Miscellaneous

28-way tagstrip (see text)

6:1 ball drive type 4511/F (Jackson)

3 control knobs

Ferrite rod (see text)

9-volt battery type PP3

Battery connector

Nylon cord

Aerial brackets and clips (see text)

Materials for case and "chassis" assembly

assembly. In the latter case the output signal from the present receiver is linked to the amplifier via the a.f. transformer in the short wave receiver.

Dealing with the v.h.f. section first, the signal from a telescopic aerial passes through C24 to the emitter of TR7, which functions as a common base amplifier at r.f. with the output across R17. The signal then passes via C26 to TR8, operating as a common collector amplifier, with detection being given by D8. The detected signal is then amplified once more by TR8 in the common base mode and applied to TR7 base. C30 acts as a capacitance tap into the tuned circuit consisting of L6 and VC3, and it causes TR8 to oscillate gently at signal frequency and thus allow synchronous f.m. detection to take place. Direct current flows through D8, both from the emitter of TR8 and from the slider of VR10. VR10 is set to reduce the impedance of D8 to a point where a correct state of oscillation is maintained. D10 maintains a stabilized voltage across VR10, and in company with D9 provides a stabilized voltage for all the other reflexed transistors. Pre-set potentiometer VR9 is adjusted to bring TR8 to the required operating conditions for correct oscillation.

The detected and amplified a.f. signal at TR7 base is further amplified by TR7 as a common emitter device with some negative feedback given by R15. The signal finally passes to TR9, which is the emitter follower common to both the a.m. and f.m. tuner sections. TR9 has a low output impedance, and its output is coupled to the upper con-

tact of the stereo jack socket.

The latter is an insulated $\frac{3}{4}$ in. type with three break contacts, such as the Electrovalue type S3BBB. This type of socket has the normal $\frac{1}{4}$ in. aperture at the bush mounting end, but there is also a $\frac{1}{4}$ in. aperture at the other end. The receiver is arranged so that, if the jack plug of a pair of stereo headphones is inserted at the correct end of the socket, it only makes contact at the top 2 contacts, as illustrated in Fig. 7. The two stereo earphones are then connected in series to the output of the tuner. Since the plug does not reach the bottom contact, the 9 volt positive supply is not interrupted and the receiver is switched on and off in the normal way by S5(c). When the stereo plug from the "Doric" amplifier is passed through the top of the amplifier case into the *bottom* of the jack socket, it connects to all three contacts and allows the receiver output to be coupled into the amplifier input via the transformer in the short wave receiver section, and also enables the on-off switch in the amplifier to control the a.m.-f.m. tuner by way of the lower two contacts. The jack plug must be securely pushed home, and the thickness of the a.m.-f.m. receiver base gives the right clearance here. The a.m.-f.m. receiver must be turned off at its own switch when the short wave receiver is turned on, and vice versa.

The medium and long wave section is given by the circuitry around TR5 and TR6. The signal is picked up by L3, which has its inductance varied by a moving ferrite rod. The tuning capacitance is

The a.m.-f.m. tuner mounted in place on top of the short wave receiver and amplifier sections



provided by C18 on medium waves and by C18 and C19 in parallel on long waves. TR5 and TR6 form a "super alpha" pair and detection takes place at D7. This is a low impedance diode whose impedance is made even lower by the direct current flowing through it via R13. TR6 gives a.f. amplification in the common base mode, the a.f. signal at its collector passing through R9 and coil L3 to the base of TR5, which gives further amplification as a common emitter device. Positive feedback for reaction is given by L4, and is controlled by VR7. This potentiometer is ganged with the v.h.f. feedback

control, VR10. The a.f. signal is finally passed to the emitter follower, TR9. VR8 is adjusted to maintain a constant setting in VR7 between about 250 and 500 metres on the medium wave band. A constant setting below 250 metres is achieved by adjustment of the trimmer VC2.



UNDERSTAND DATA PROCESSING

NEW FOURTH EDITION

DATA PROCESSING, by Oliver & Chapman, is now in its Fourth Edition

200 pages 9 $\frac{3}{4}$ " x 6 $\frac{3}{4}$ " **PRICE £2.75**

P.&P. 35p

PUBLISHED BY D. P. PUBLICATIONS

The primary aim of this outstanding manual is to provide a simplified approach to the understanding of data processing — (previous knowledge of the subject is not necessary).

The 40 chapters and appendices cover the following topics: Introduction to Data Processing; Organisation and Methods; Conventional Methods; Introduction to EDP and Computers; Hardware; Computer Files; Data Collection and Control; Programming and Software; Flowcharts and Decision Tables; Systems Analysis; Applications; Management of EDP, etc.

A Manual for Business and Accountancy Students

Available from: **DATA PUBLICATIONS LTD.,**

57 MAIDA VALE, LONDON W9 1SN.

CONSTRUCTION

Construction commences by cutting out the items in Figs. 8 (a), (b), (c), (d), (f), (g), (h) and (j). Two 4BA bolts on either side of the $\frac{1}{4}$ in. hole in Fig. 8(a) take countersunk 4BA bolts which hold the stereo jack socket in place with the aid of the item of Fig. 8(j), as shown in Fig. 8(k). The two 4BA clear holes in Fig. 8(j) match the corresponding holes in Fig. 8(a). Two further 4BA clear holes (C and D) are intended for the telescopic aerial holding assembly in Fig. 8 (l) and the aerial swivel assembly in Fig. 8(m). The two remaining 4BA clear holes in Fig. 8(a) are marked out later with the aid of an item which is not yet prepared. Also required in Fig. 8(a), but not shown in the diagram, is a $\frac{1}{2}$ in. hole for the short wave telescopic aerial.

The lower edge of Fig. 8(a) corresponds with the front edge of the receiver when it is fitted on top of the amplifier and speaker section. Position the item of Fig. 8(a) on top of the amplifier case with the front of the $\frac{1}{4}$ in. "feet" flush with the amplifier front and the sides flush with the amplifier sides. Mark out the centre of the $\frac{1}{4}$ in. hole on the lid of the amplifier case, remove the item of Fig. 8(a), then drill a hole in the amplifier case lid $\frac{3}{8}$ in. in diameter. This accepts the body of the amplifier stereo plug, which passes up into the bottom of the stereo socket.

Place the item of Fig. 8(a) on the amplifier case lid once more and use it to mark out the centres of the two 6BA clear holes on the case lid. Drill these two holes 6BA clear in the lid. The holes will later take 6BA bolts which pass through the lid and the item of Fig. 8(a), with 6BA terminal nuts on the top, thereby securing the a.m.-f.m. tuner to the case when construction of the tuner has been completed. Finally, with the aid of the amplifier case and the short wave receiver section, locate and mark out the centre of the $\frac{1}{2}$ in. hole required in Fig. 8(a) to allow the passage of the short wave telescopic aerial. Drill out this hole in the Fig. 8(a) item.

The pieces of Fig. 8(b), (c) and (d) are screwed together to provide the mounting for VC3 and its epicyclic tuning drive which is shown in Fig. 8(e). The $\frac{1}{4}$ in. rebate in Fig. 8(c) allows room for the body of the drive. The item of Fig. 8(c) is held against the item of Fig. 8(a) by the $1\frac{1}{4}$ in. countersunk 4BA bolt of the telescopic aerial holding assembly. See Fig. 8(1).

The items of Figs. 8(f), (g) and (h) are screwed together in a similar manner to produce the assembly of Fig. 8(i). Note that the assembly leaves room for the PP3 battery, as indicated. The $1\frac{1}{4}$ in. countersunk 4BA bolt for the telescopic aerial swivel assembly, shown in Fig. 8(m), passes

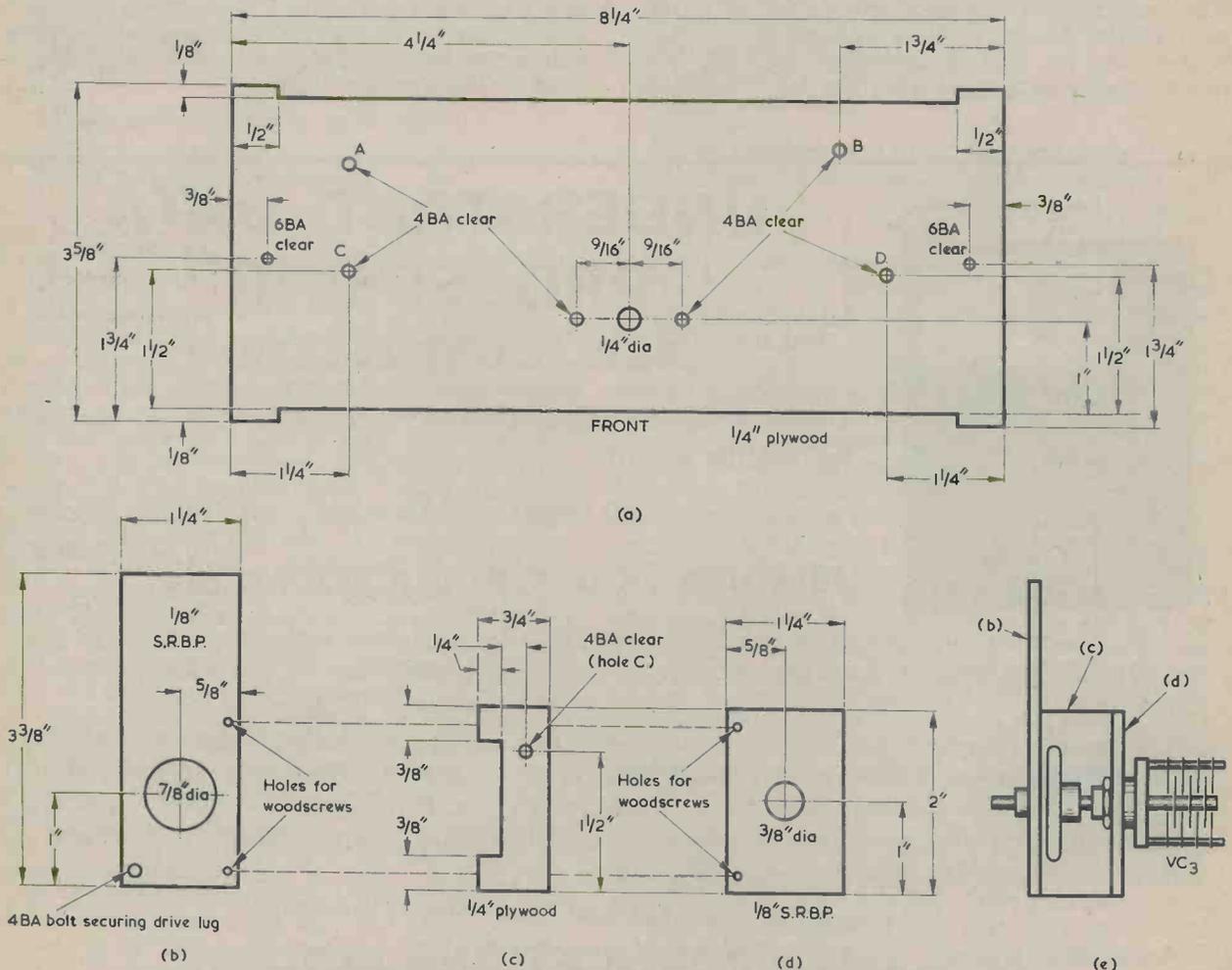


Fig. 8(a). Baseplate of the tuner. This is secured to the top of the amplifier case by screws passing through the two 6BA clear holes, with nuts on the top
(b) (c) (d) (e). Mounting assembly for VC3 and its epicyclic tuning drive

through the items of Figs. 8(g) and (a) as illustrated.

The s.r.b.p. piece of Fig. 8(j) has the outside dimensions shown. The central hole takes the mounting bush of the stereo jack socket. The two remaining holes are 4BA clear and match up with the corresponding 4BA clear holes in Fig. 8(a). When fitting the socket to Fig. 8(a), pass a plug through the $\frac{1}{4}$ in. hole into the socket to ensure that the socket is located correctly. The assembly is illustrated in Fig. 8(k).

The clips and angle brackets in the assemblies of Figs. 8(l) and (m) were Lektrokit type LK2721 and LK2311 in the prototype, but Lektrokit parts are difficult to obtain on the home constructor market at the time being. The clips are $\frac{3}{8}$ in. types whilst the brackets have dimensions of $\frac{1}{2}$ in. by $\frac{1}{8}$ in. by $\frac{3}{8}$ in. The brackets may be home-made from thin metal strip and suitable Terry clips or similar may be obtained from hardware stores. The base of the telescopic aerial fits into the clip of Fig. 8(m), the nuts here being tightened such that the aerial can be swivelled in any direction. When not in use, the aerial is fitted into the clamp of Fig. 8(l) and may then be used as a carrying handle.

COILS

The coils are made next, starting with L6. Cut length, $1\frac{3}{8}$ in. long, from the outer case of a "Bic" ball-point pen. Drill two $\frac{1}{16}$ in. holes in it, each $\frac{3}{16}$ in. from an end. Wind on 6 turns of bare tinned copper wire, the turns being equally spaced, and pass the ends of the coil through the $\frac{1}{16}$ in. holes to anchor them. See Fig. 9(d). The wire should be approximately 22 s.w.g., and normal wiring-up wire stripped of its insulation will do nicely. Ignore the two half-turns given by the wire passing through the two end holes.

L3 and L4 require a 3 in. ferrite rod of $\frac{3}{8}$ in. diameter, and this is obtained by cutting down a 4 or $4\frac{1}{2}$ in. orange grade ferrite rod obtained from Amatronix. Details of cutting down the rod were given in Part 1 of this series. The two windings are made up in a similar manner to the coil which was used for the short wave receiver, also described in Part 1. Make a tube of Fablon by cutting out a piece 4 by $3\frac{1}{2}$ in., and remove the backing paper over a strip $\frac{1}{2}$ in. wide along one $3\frac{1}{2}$ in. side. The Fablon is wrapped around the ferrite rod so that the exposed adhesive comes on last and secures the

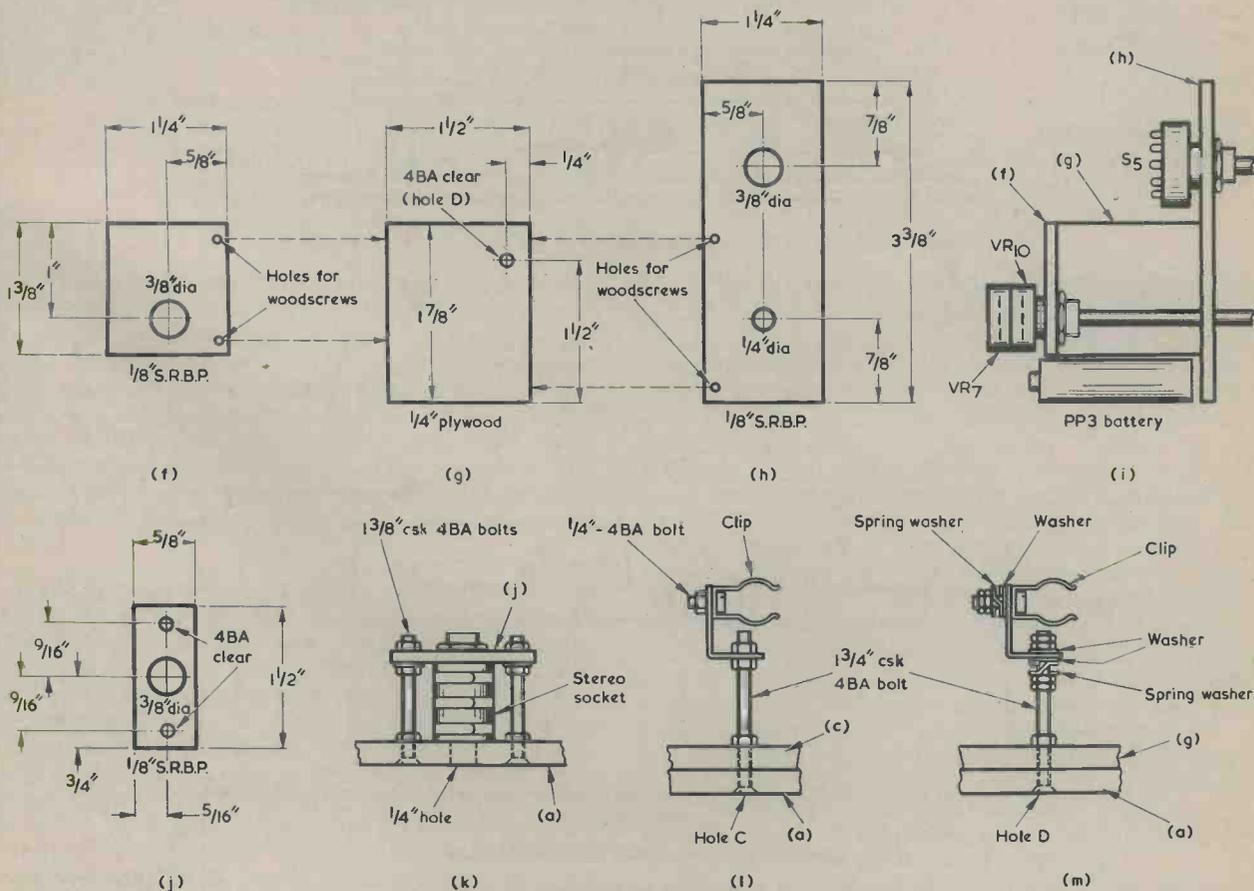


Fig. 8(f) (g) (h) (i). A similar form of mounting assembly is employed for the dual potentiometer VR7/VR10 and S5

(j). Mounting item for the stereo jack socket

(k). The socket is secured to the baseplate as shown here

(l). Telescopic aerial clip assembly

(m). The swivelling clip, into which the base of the telescopic aerial is fitted

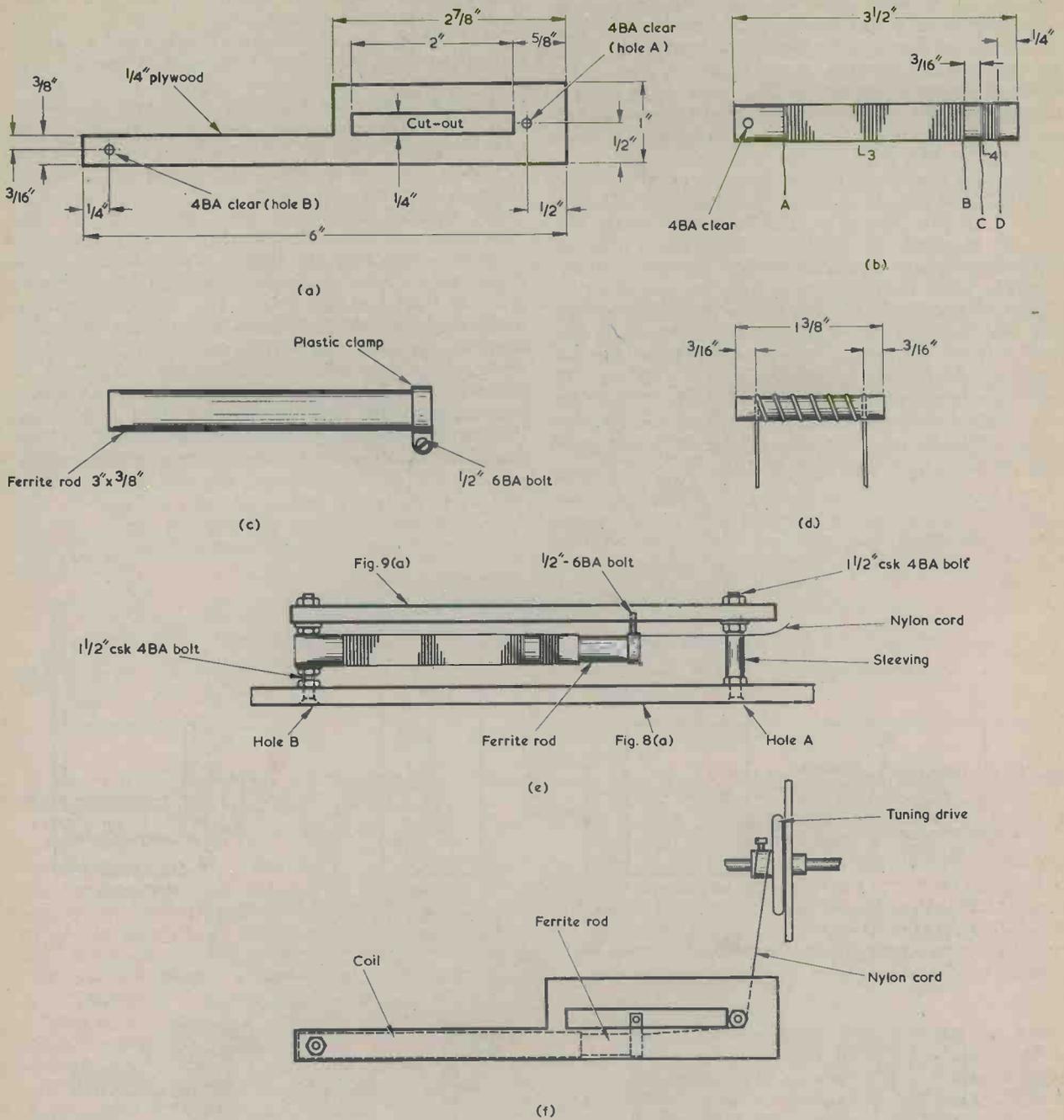


Fig. 9(a). Plywood item which is fitted above the medium and long wave coil and ferrite rod assembly


(b). Details of the medium and long wave coil

(c). The ferrite rod and its plastic clamp


(d). The v.h.f. coil

(e). View from the rear of the receiver illustrating the operation of the ferrite rod. Omitted, for clarity, is the rubber band which draws the rod into the coil

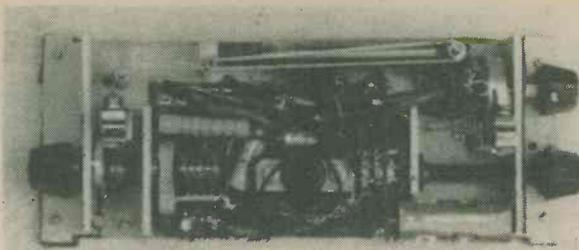(f). Top view, illustrating the nylon cord linkage to the epicyclic tuning device



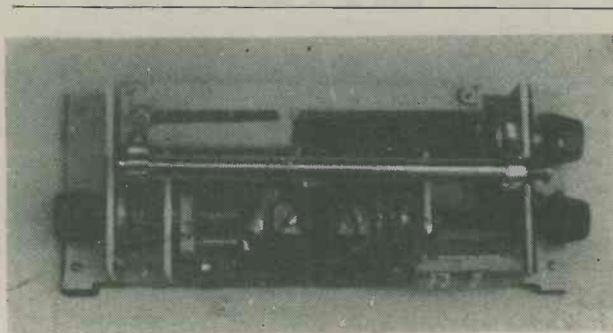The tuner, as assembled without the item of Fig. 9(a)



Here, the Fig. 9(a) item has been fitted, as also has the telescopic aerial

tube. The ferrite rod should be able to slide easily in the tube, but without wobble. A $\frac{1}{2}$ in. length of $\frac{3}{8}$ in. wood dowelling is inserted at one end of the tube, having had a turn or two of Sellotape wrapped around it to make a snug fit. A 4BA clear hole is drilled through the tube and dowelling at the centre of the latter. Insert the rod and wind on L3 and L4 as indicated in Fig. 9(b). L3 consists of 220 turns of 34 s.w.g. enamelled wire, and L4 consists of 15 turns of the same wire. Both coils are close-wound.

Next cut out the item shown in Fig. 9(a). This will be fitted to Fig. 8(a) in the manner shown in Figs. 9(e) and (f). The view in Fig. 9(e) is from the rear of the receiver, and the nearer edge of Fig. 9(a) is directly above the nearer edge of Fig. 8(a). Use the item of Fig. 9(a) to mark out the remaining two 4BA clear holes in Fig. 8(a). Fit two $1\frac{1}{2}$ in. countersunk 4BA bolts to these holes and secure with nuts. Pass a piece of plastic sleeving over one of the bolts, as in Fig. 9(e), and add another nut. Pass a second nut over the other 4BA bolt, then the end of the coil tube and another 4BA nut. Put a rubber band over the bolt, keeping it clear of the other parts for the time being.

Take up the item of Fig. 9(a), lightly countersink the two holes in it on the upper side, then pass it over the two bolts and fit two further nuts on top. Cut out a piece of pliable plastic, $1\frac{1}{4}$ by $\frac{1}{4}$ in., and make two 6BA clear holes in it near its ends. Secure it around the end of the 3in. ferrite rod by passing a

$\frac{1}{2}$ in. 6BA bolt through the holes and fitting this with a 6BA nut, whereupon the plastic functions as a clamp. Tie a length of nylon cord to the plastic clamp and tighten this up on the ferrite rod. Insert the rod in the coil tube and stretch the rubber band over the 6BA bolt at the dowelling end of the tube and the 6BA plastic clamp screw. Tighten up all the nuts shown in Fig. 9(e) so that the assembly is as in the diagram. The ferrite rod is moved inside the tube by the nylon cord, which passes over the plastic sleeve and is then anchored to the epicyclic drive, as shown in Fig. 9(f). The grub screw in this drive is replaced by a standard size screw to enable the cord to be anchored to it. The end of the 6BA screw in the plastic clamp now slides inside the 2in. slot in the item of Fig. 9(a) and acts as a tuning position indicator. Arrange matters such that the VC3 is approximately at half-capacitance when this pointer is at the end of its travel. The rubber band ensures that the ferrite rod is drawn into the coil tube as the tuning control is turned anti-clockwise.

The a.m.-f.m. receiver requires a 28-way tagstrip and this is an RS Components "Miniature" tagstrip, with a length of 194mm, which is mounted flat onto the surface to which it is fitted. Notes on obtaining RS Components products were given at the end of Part 1 of this series. A suitable alternative to the RS Components item is a 28-way tagstrip with 0.25in. tag spacing which is available from Electrovalue.

(To be concluded)

'NOTES FOR NEWCOMERS'

LOG and LIN

By D. Smith

THOSE MYSTERIOUS POTENTIOMETER CLASSIFICATIONS

As anyone who has glanced through components lists in constructional magazines or has scanned the goods offered in mail-order catalogues will be aware, potentiometers come mainly in two types, log and linear. The latter term is frequently abbreviated to "lin".

Why are there these two categories? If we look into the subject we will find that linear potentiometers are very easy to understand whilst the reasons for using log potentiometers are rather more complicated. However, it is not too difficult to obtain a basic understanding of the necessity for log potentiometers, and this we shall do in the present short article.

LINEAR POTS

Linear potentiometers are components in which the percentage of track resistance tapped off by the slider varies directly with the rotation of the potentiometer spindle. If we draw a curve of resistance plotted against effective spindle rotation we get the straight line shown in Fig. 1. At 100% of spindle rotation the slider taps off all the track resistance, at 75% it taps off three-quarters, at 50% it taps off one-half, and at 25% it taps off one-quarter.

Linear potentiometers are used in applications where it is acceptable for the resistance tapped off to vary directly with spindle rotation. There are very many of these applications, ranging from the zero-set potentiometer in a multimeter (where it is actually used as a variable resistor) to the brightness control in a monochrome television receiver (where the potentiometer varies the bias voltage applied to the grid of the cathode ray tube).

Log potentiometers are more specialised components and are primarily intended for use as audio volume controls in radio receivers, television receivers and a.f. amplifiers. They function by having an audio signal applied across the track, the slider then tapping off a proportion of the signal which is passed to the following a.f. stage.

GEOMETRIC RESPONSE

The human ear has an approximately geometric response to the intensity of sounds. If we double the intensity of a sound we may say that we perceive an increase in its volume level. To obtain a further perceived equal increase in volume we have to double the sound intensity once more. For a third apparently equal increase in volume, as heard by the ear, the sound intensity has to be doubled yet again. So, for three *perceived* equal increases in sound volume we have actually increased the sound intensity by 2, then 4 and then 8 times.

Assuming that the sound intensity from the associated amplifier is equal to the resistance tapped off by a potentiometer employed as a



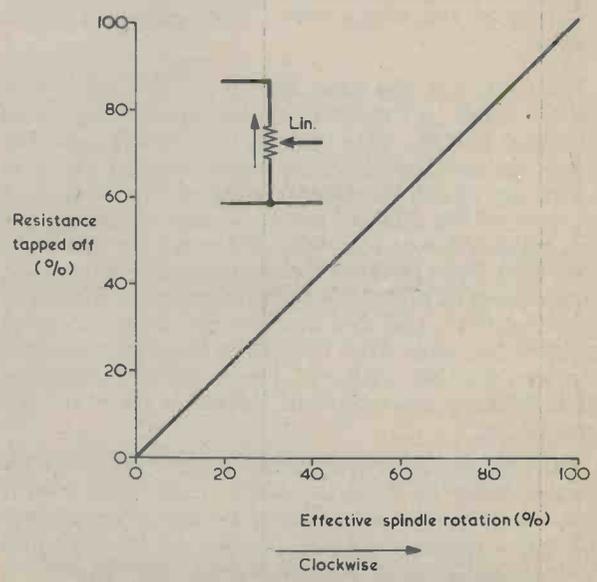


Fig. 1. Characteristic curve showing resistance tapped off plotted against effective spindle rotation for a linear potentiometer

Fig. 2(a). One of the numerous applications for a linear potentiometer is as the zero-set control in an ohmmeter (b). A linear potentiometer may function as the brightness control in a monochrome television receiver. The tube cathode will be held at a positive voltage by its signal input circuit

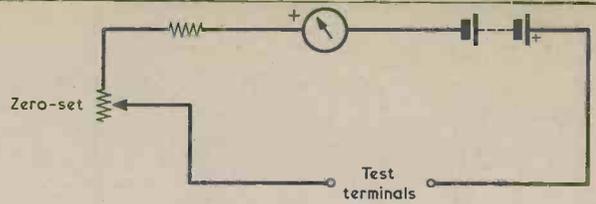

(a)

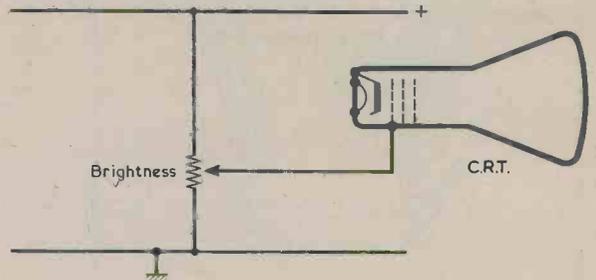

(b)

volume control, the effect of using a linear potentiometer as a volume control is shown in Fig. 3. In this diagram the line representing percentage of effective spindle rotation is divided into "equal units of perceived volume change". One unit is from 100% to 50%, the next is from 50% to 25%, the next from 25% to 12.5%, and so on until the units become too small and crowded to be conveniently drawn in the diagram. It will obviously be difficult to adjust the potentiometer satisfactorily at low volume levels.

"equal unit" sections in Fig. 3 therefore become opened out, allowing the control of volume to be much smoother, particularly at the low volume end of the spindle rotation range. The term "log" arises because, roughly, the spindle rotation has a logarithmic relationship with the resistance tapped off.

You won't blow any fuses by using a linear potentiometer as a volume control, and if you're experimentally minded you might like to try it out in practice. You'll then find you get the effect shown in Fig. 3.

Log potentiometers are employed in other applications where their tapered characteristic gives an apparent smoothness of control. They are,

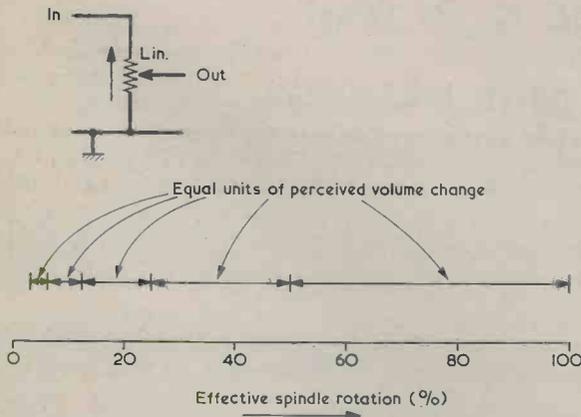


Fig. 3. Assuming that sound intensity is equal to resistance tapped off, a linear potentiometer employed as a volume control gives the effect shown here

LOG TRACK

This is where the log potentiometer comes into use. Fig. 4 shows a typical curve for a log potentiometer and it will at once be seen how it functions. At the anti-clockwise end of the curve, the spindle has to be rotated by a large amount for only a small increase in the percentage of resistance tapped off. Indeed, the spindle has to be rotated to about 80% of its fully clockwise setting before the tapped off resistance reaches 50%. All the crowded


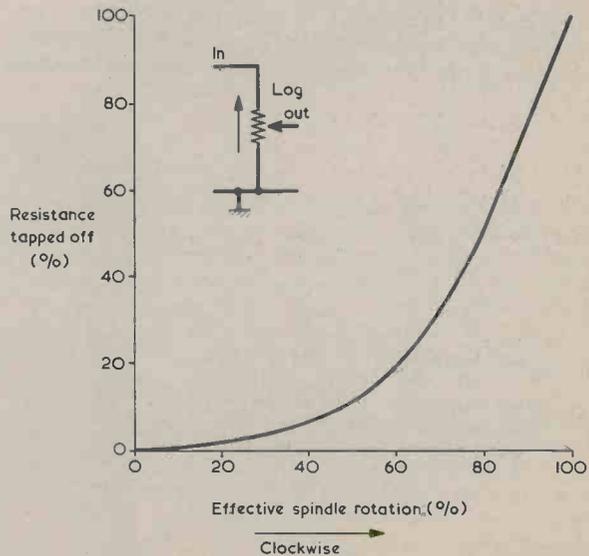


Fig. 4. Typical track characteristic for a log potentiometer

Fig. 5. An anti-log potentiometer has a characteristic which is the reverse of that for the log potentiometer

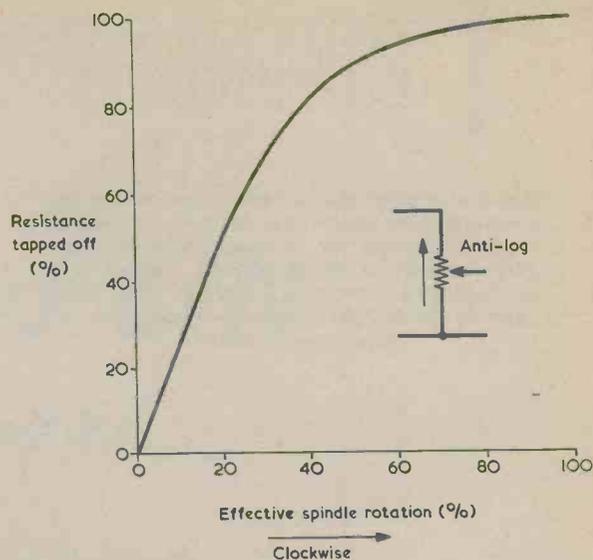

for instance, quite often encountered in tone control circuits. There are, also, anti-log potentiometers. These have a track characteristic which

is the opposite of that shown in Fig. 4, and a typical example is given in Fig. 5. ■

S-DEC ADAPTOR

By


A. M. Williams and K. R. Nash

Home-made adaptor extends usefulness of S-DeC breadboard.

The S-DeC is one of the most popular and inexpensive breadboards presently available. However, it suffers from the disadvantage that its contact

spacing is such that it will not accept d.i.l. integrated circuits. This short article describes a simple adaptor which plugs into an S-DeC and accepts

The i.c. adaptor in use. It is fitted to the centre vertical rows of contact holes in the S-DeC and can accept 8 or 14 pin d.i.l. integrated circuits

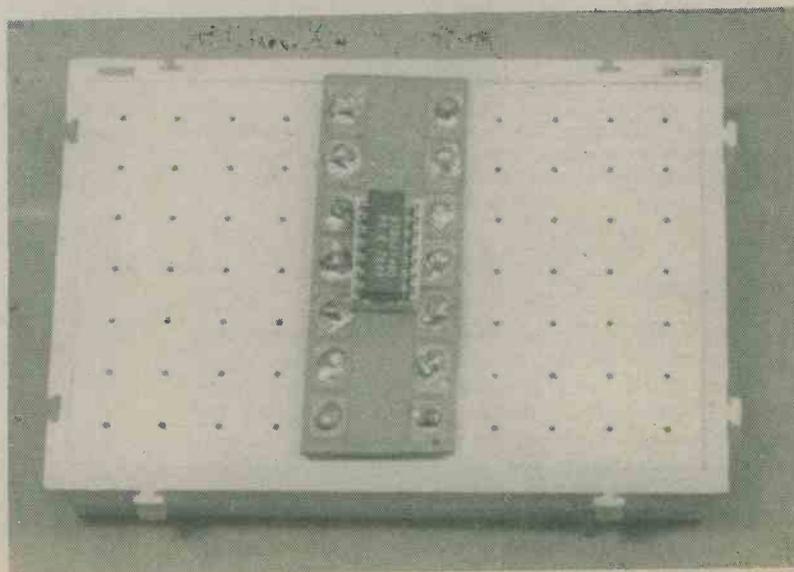

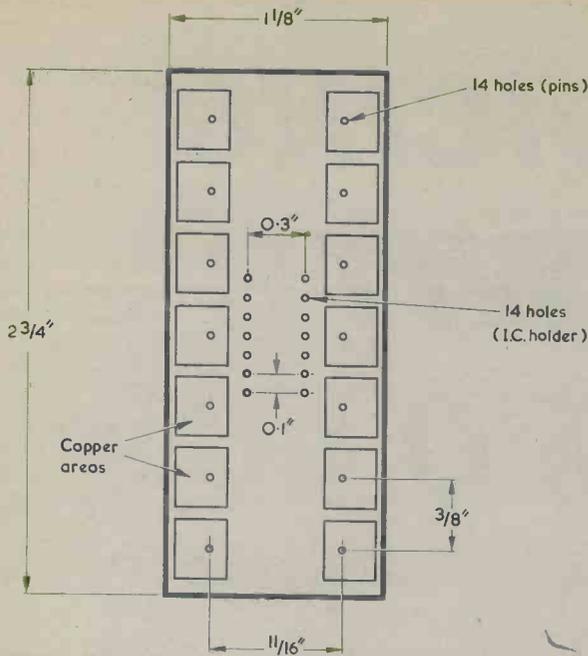


Fig. 1. The copper pattern and holes required in the printed circuit board employed for the adaptor

standard 8 and 14 pin i.c.'s.

CONSTRUCTION

The adaptor is made up with a piece of printed circuit board, a 14-way i.c. holder and 14 ordinary domestic pins.

First, cut out the printed circuit board to the outside dimensions shown in Fig. 1, which is reproduced full size. Then, using standard printed circuit procedure, etch away the copper so that the 14 copper areas shown in the diagram are left. Next, drill out 14 holes in the copper areas at the positions shown, the hole diameters being such that the pins are a fairly firm fit in them. Then drill out the 14 holes in the centre of the board to take the leads of the 14-way d.i.l. holder.

Cut each pin so that its length is a little less than

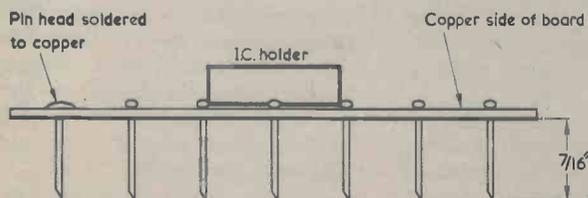


Fig. 2. Side view illustrating the method of assembly. In practice, the i.c. holder is fitted to the board after all the pin heads have been soldered to their copper areas

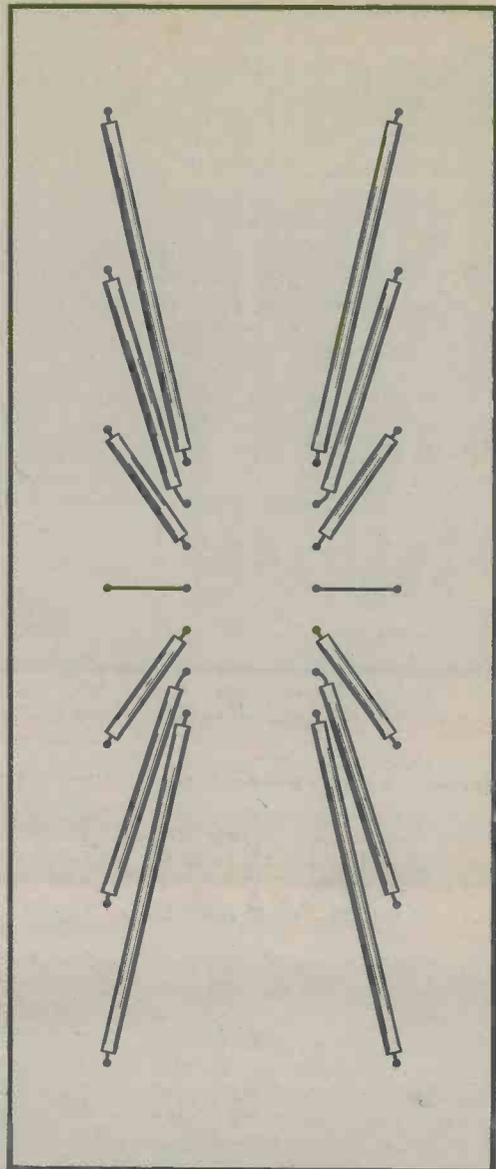


Fig. 3. Final wiring of the i.c. holder leads to the pins. This wiring is carried out on the non-copper side of the board

$\frac{1}{2}$ in. Place the board over an S-DeC, copper side up, and pass the pins through the board into the centre two rows of contact holes in the S-DeC. These are the vertical rows of holes from 5 to 35, and 36 to 66. Push each pin fully home, then solder its head to the copper area through which it passes. The soldering is shown in Fig. 2, and it causes each pin to be firmly held in position.

Remove the board from the S-DeC and fit the i.c. holder to the holes drilled for it. Then, on the non-copper side of the board, wire up the holder leads to the pins as shown in Fig. 3. The two centre leads and pins are connected by bare wire, and the remainder by thin insulated wire. The solder joints at the pins are kept close to the surface of the board. The adaptor is then complete and ready for use.

In your Workshop -Shop

DICING WITH TWO I.C.s

Sometimes you can get too technical ...

"D'you know something, Smithy?"

Smithy leaned back comfortably on his stool and turned his head to look at his assistant.

"No," he replied. "What should I know?"

"That, just for once," stated Dick, "I'm getting a bit fed up with continual servicing."

"Well, that's a surprise coming from you," commented Smithy. "Normally you're pestering me all day long with questions about nothing else except repairing radios and TV's."

"Perhaps that's true," conceded Dick, "but we do now and again have a break from servicing. Like, for instance, when we make up electronic gadgets and things like that."

ELECTRONIC DICE

"Now, it's funny you should mention that," said Smithy, "because it so happens that I've very nearly completed the construction of another little design I dreamed up over the last week or so. It only needs a few more connections to be made to it, and I intended doing these this evening."

He glanced at the Workshop clock.

"There's twenty minutes of lunch-break left," he went on, "so I might as well complete my gadget now. If I haven't made any mistakes and it works first go, I'll be able to demonstrate it to you."

He switched on his soldering iron, then reached into the cupboard

under his bench and drew out a few sheets of notepaper and a small Veroboard panel. He placed the panel on a clean part of his bench, and spread out the notepaper sheets in front of him. These bore circuit diagrams and tables which had obviously been drawn up by Smithy himself.

Eagerly, Dick rose from his stool to examine the Veroboard panel. This was of 0.1 in. matrix and had mounted on it a capacitor, several resistors, a 14-way d.i.l. integrated circuit holder, a 16-way d.i.l. holder, together with seven light-emitting diodes near one corner of the board. These were arranged in a pattern having two vertical columns of three l.e.d.s with a single l.e.d. positioned centrally between them. Also connected to the board were two flexible leads passing to a push-button and two further leads, one red and one black, which were terminated in crocodile clips.

"This Veroboard," remarked Smithy, "is a 5 by 3 $\frac{3}{4}$ inch standard size, which takes all the parts just comfortably. Actually, the layout is of no importance at all, and any other means of assembling and wiring up the components will do equally well."

"What does your gadget do?"

"You'll see," promised Smithy.

"Now, the only parts I've got left to wire in are four 1k Ω resistors which act as current limiting resistors for the l.e.d.s. And I've got these all ready."

Smithy put his hand in the cupboard once more and removed a

small cardboard box. He opened this and took out a $\frac{1}{4}$ watt resistor, then glanced at a circuit diagram on one of the sheets of paper in front of him. He next held the resistor against the Veroboard, bent its two lead-outs through ninety degrees at the points dictated by the requisite holes in the board, then passed the wires through. Turning the board over, he soldered the lead-outs neatly to the copper strips through which they passed and then snipped off the excess wire. He proceeded to deal similarly with three further resistors, after which he examined the underside of the board carefully.

"This looks all okay to me," he pronounced. "All the joints are nice and sound and there's nothing silly like blobs of solder bridging adjacent strips. Right, now I'll plug in the integrated circuits."

He took a 14-pin i.c. from the cardboard box, removed the aluminium foil which short-circuited its pins together, and carefully inserted it into the 14-way d.i.l. holder.

"A CMOS i.c.?" queried Dick.

"A CMOS i.c.," confirmed Smithy. "Both the i.c.'s are CMOS types, which is the main reason why I used i.c. holders. There's no risk of damaging them if I fit them into holders when all the other wiring has been completed."

Quickly, Smithy removed the foil from a 16-way i.c. and then plugged this into the remaining holder. He then reached over towards the back of his bench and picked up a PP9 battery. He connected the crocodile

clip at the end of the black flexible lead to its negative terminal and held the other clip poised over the positive terminal.

"Moment of truth now," he intoned. "Keep your fingers crossed, Dick!"

He connected the crocodile clip to the positive battery terminal. At once, all seven l.e.d.s lit up, glowing with a continual and pronounced flicker. Smithy gave a grunt of satisfaction.

"Right," he said briskly. "You press the push-button, Dick."

Dick picked up the button and pressed it. Three l.e.d.'s extinguished immediately, and the four at the corners of the display lit steadily. Dick released the button, then pressed it again. This time, only the single l.e.d. in the centre of the display remained lit. He released the button and pressed it yet again, to find that the two vertical rows of three l.e.d.'s stayed alight.

"Why, of course," he exclaimed, as realisation suddenly struck him, "it's an electronic dice!"

"That's right," grinned Smithy. "Every time you press the button the l.e.d.'s light up to form a number from 1 to 6, following the dot pattern on an ordinary dice."

"But," protested Dick, "you've got hardly any components at all on that Veroboard! Apart from the seven l.e.d.'s there are just the two i.c.'s, a capacitor and — let me see now — seven resistors only."

"True," agreed Smithy. "That's why I'm rather proud of this little circuit. It *could* be made up with only three resistors, as the four l.e.d. current limiting resistors I wired in just now aren't really essential. However, as you'll see soon, they are worthwhile including because they equalise the brightness of the l.e.d.'s."

ORIGINAL IDEA

"Did you dream this up all on your own?"

"Not entirely," replied Smithy, disconnecting the positive crocodile clip from the PP9 battery. "This gadget is a development from several designs which were presented by an old colleague and friend of many years' standing, G. A. French."

"G. A. French," repeated Dick thoughtfully. "Do you mean the 'Suggested Circuits' geyser?"

"Geyser?" Smithy was profoundly shocked. "You mustn't refer to a person with the experience and ability of G. A. French as a geyser!"

Dick shrugged his shoulders.

"Oh all right then, the guy who does 'Suggested Circuits'."

Smithy glared at his assistant.

"You should have more respect," he said sternly, "for your elders and betters."

"Well, what were the ideas that G. A. French came up with?"

"They were concerned with the CD4018 integrated circuit," replied Smithy, still patently annoyed at his assistant's cavalier references to the author of the 'Suggested Circuit' series. "The CD4018 is a CMOS counter which has five not-Q outputs, and it can be made to divide by 10, 8, 6, 4 or 2 simply by returning the appropriate not-Q output to its data input. The not-Q outputs are numbered 1 to 5 and if, for instance, you want to divide by 10, you connect the not-Q5 output to the data input pin. To divide by 6, it's the not-Q3 output which is returned to the data input."

"Does the electronic dice application require the CD4018 to divide by 6?"

"It does," affirmed Smithy. "The CD4018 is advanced one count by each positive-going pulse edge applied to its clock input. If you apply the pulse edges through a press-to-break push-button you can then

stop the CD4018 count at any one of its six output states, and this forms the basis for the electronic dice."


"Does the generator have to run at a fairly high frequency?"

"Oh yes," confirmed Smithy. "And it then becomes a purely random matter at which instant the push-button is pressed to stop the CD4018 counter."

"How do you manage to get the CD4018 to light up the l.e.d.'s in a dice pattern?"

"Ah," said Smithy, "that's the interesting bit. G. A. French has produced truth tables showing what happens at all of the CD4018 not-Q outputs for each successive count, and he then showed how these outputs could be gated to light up the appropriate l.e.d.'s in an electronic dice. I'm doing the same thing with my own dice design, but I've reduced the gating requirements to what may well be the minimum possible. To start off with, here is the CD4018 truth table when it's set up to divide by 6."

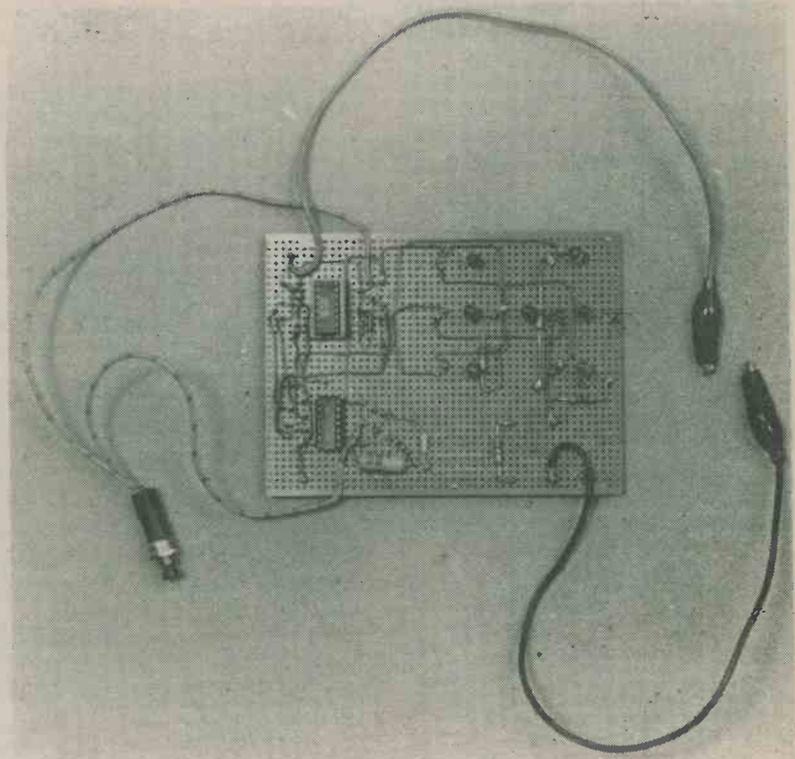Smithy took one of the pieces of notepaper on which he had made out the truth table, and showed this



The electronic dice may be assembled in any manner. Smithy found it convenient to mount all the small components, including the l.e.d.'s, on a standard size of 0.1 in. Veroboard

Count	CD4018 Output				
	Not-Q1	Not-Q2	Not-Q3	Not-Q4	Not-Q5
1	H	H	H	L	L
2	L	H	H	H	L
3	L	L	H	H	H
4	L	L	L	H	H
5	H	L	L	L	H
6	H	H	L	L	L
7	H	H	H	L	L

Fig. 1. Truth table illustrating the states of the CD4018 not-Q outputs over a period of seven counts when the not-Q output is connected to the data input

to Dick. (Fig. 1.)

"After a few counts immediately after switching on," he continued, "the not-Q outputs settle into the pattern shown in this table. The letter 'H' stands for 'High' and indicates a positive output, whilst the letter 'L' stands for 'Low' and means a negative output. As you can see, the highs go progressively across the not-Q outputs followed by the lows. My truth table shows seven counts, and the seventh count is exactly the same as the first count. The eighth count will give the same results as the second count, and so on. The problem then consists of gating these outputs so that they light the right I.e.d.'s in the dice layout. And to do that we have to make up another table."

DICE PATTERN

Smithy selected a further piece of paper, on which he had drawn out the dice I.e.d. layout. (Fig. 2.)

"You've given the I.e.d.'s letters,"

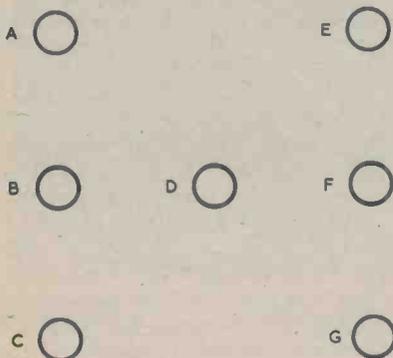


Fig. 2. Seven I.e.d.'s laid out in a pattern which allows them to indicate dice numbers

said Dick, looking down at the paper. "Is this to help you sort out which ones are lit for each number?"

"That's the idea," agreed Smithy. "And here's the table I made up which shows the lit I.e.d.s for each dice number. Number 1 is, of course, simply given by I.e.d. D lit up on its own." (Fig. 3.)

"And 2," chimed in Dick, "will be given when I.e.d.'s C and E are alight."

"3 comes next," said Smithy, "and that's given by I.e.d.'s C, D and E. For 4 we need the four outside I.e.d.'s, A, C, E and G. Add I.e.d. D to these and we've got dice number 5."

"Gosh, this is getting interesting! There's only dice number 6 left, and that must be given by A, B, C, E, F and G."

Dice Number	I.E.D.'s Alight
1	D
2	CE
3	CDE
4	ACEG
5	ACDEG
6	ABCEFG

Fig. 3. Table showing the I.e.d.'s which require to be lit for each dice number

"That's right," said Smithy briskly. "Well, I won't bother you with the details of how I sorted out the gating to light up the dice numbers, apart from telling you it involved a little head-scratching on my part, and I'll go straight on to the arrangements I finally settled for. Our last table shows that I.e.d. D lights up for dice numbers 1, 3 and 5. In my circuit this I.e.d. is driven direct, via a 1kΩ current limiting resistor, from the not-Q4 output of the CD4018 when this output is low. Like this."

Smithy took up a ball-point pen and scribbled out the circuit detail on the paper in front of him. (Fig. 4(a).)

"That means," said Dick slowly, "that I.e.d. D comes on at counts 1, 5 and 6 in the table which shows the not-Q outputs."

"Right! Incidentally, we'll ignore the seventh count in that table because it's the same as the first count. Next come I.e.d.'s A and G. These light up for dice numbers 4, 5

and 6. I've driven them directly from the not-Q2 output, and they light up when *that* output is low."

Smithy again sketched out the arrangement. (Fig. 4(b).)

"Well," said Dick, "these two I.e.d.'s are lit at counts 3, 4 and 5."

"Correct," confirmed Smithy. "After this I had to introduce two NOR gates to handle the remaining four I.e.d.'s. You will note that I.e.d.'s C and E are alight for all the dice numbers apart from number 1. They're driven from the output of a NOR gate whose two inputs connect to not-Q3 and not-Q5."

Smithy drew out the circuit. (Fig. 4(c).)

"Well, the output of that NOR gate," said Dick, staring at the circuit, "will be low when one or both of its inputs is high, and will only go high, to turn off the I.e.d.'s, when the two inputs are low. Now, let's see. Ah yes, the two inputs, from the not-Q3 and not-Q5 outputs, are low only on count number 6."

"You've got it. We are now left with I.e.d.'s B and F. The opposite thing happens here, and these are only turned *on* for one dice number, this being dice number 6. They're fed from the output of a second NOR gate, but in this case they're returned to the negative rail."

Smithy drew the circuit. (Fig. 4(d).)

"The NOR gate input is taken from the not-Q1 and not-Q3 outputs," commented Dick, "and that means the gate output will only go high when its two inputs are low. Which occurs at count number 4?"

"It does," said Smithy. "Now I'll note down the I.e.d.'s corresponding to each count number. At count 1, C, D and E are alight, and at count 2, it's C and E. Count 3 brings on A, C, E and G, count 4 brings on A, B, C, E, F and G, while count 5 brings on A, C, D, E and G. The final count, 6, brings on D only."

Excitedly, Dick took the pen from Smithy's fingers.

"I'll add the dice numbers," he said quickly. "C, D and E obviously give dice number 3, and C and E must give dice number 2."

He quickly jotted the remaining dice numbers on the sheet of paper. (Fig. 5.)

"There you are," grinned Smithy. "How about that, then?"

"The dice numbers don't appear in numerical order," objected Dick. "They appear in the order 3, 2, 4, 6, 5, 1."

"That doesn't matter," said Smithy. "So long as each number appears only once in each 6-count cycle, it doesn't matter what order the numbers are in."

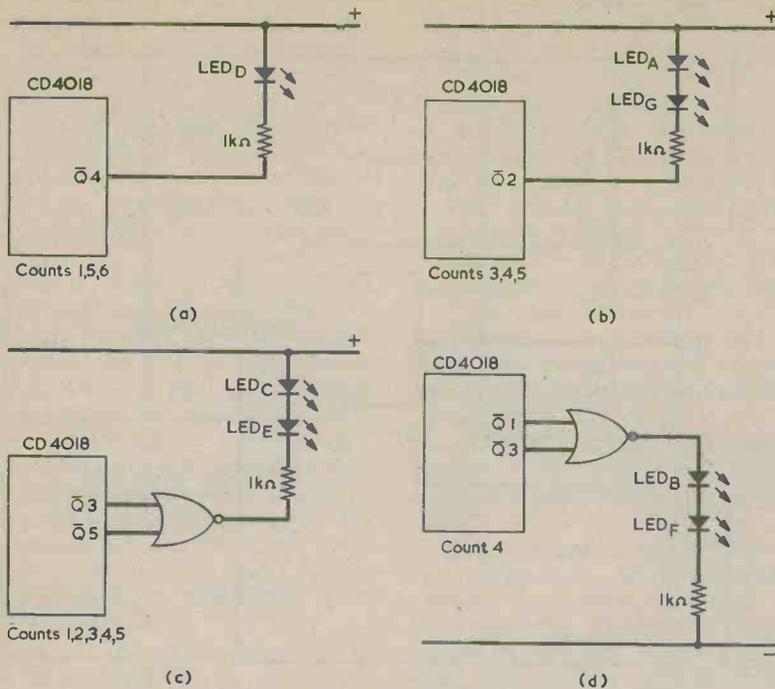


Fig. 4(a). In Smithy's design, l.e.d. D is driven from the not-Q4 output of the CD4018, and it lights up on counts 1, 5 and 6
 (b). The not-Q2 output drives l.e.d.'s A and G
 (c). The not-Q3 and not-Q5 outputs are gated by a NOR gate to l.e.d.'s C and E
 (d). A second NOR gate is used for l.e.d.'s B and F

COMPLETE CIRCUIT

"And all this," queried Dick. "was the result of studying G. A. French's CD4018 truth tables?"

"It was."

"That G. A. French must be a pretty crafty geyser, after all!"

Smithy turned a wrathful look on his assistant.

"It wouldn't half shake you," he snorted, "if all of a sudden a finger came creeping over the edge of the page and dug you one in the ear."

Dick blanched.

"Hey, Smithy," he said, shivering, "don't go saying things like that!"

Count	L.E.D.'s Alight	Dice Number
1	CDE	3
2	CE	2
3	ACEG	4
4	ABCEFG	6
5	ACDEG	5
6	D	1

Fig. 5. Table listing the l.e.d.'s which light up at the counts of Fig. 1, together with the corresponding dice numbers

"You should maintain a civil tongue."

"All right! I'm sorry!"

"Very well, then. I'll now go on to the complete circuit of the electronic dice."

Smithy sorted through the papers, then placed one in front of his assistant. (Fig. 6.)

"Here we are," he remarked proudly. "This is the full circuit. The gating and l.e.d. part of the circuit is to the right of the CD4018, and it follows the lines I've already shown you. The 1kΩ series current limiting resistors simply equalise the brightness of the l.e.d.'s, and make up for the fact that the output current capability of a CD4018 is lower than that of the NOR gates I've used. These are two NOR gates in a quad NOR gate type CD4001. I've made the circuit respectable by giving it an on-off switch, although I didn't bother about this on my own model. Pin number 8 of the CD4018 is the negative supply pin. There are also a number of inputs, a preset enable and a reset, and all their pins are taken to the negative rail as well. Pin 14 is the clock input."

"The not-Q3 output," observed Dick, "is on pin 6, and this is return-

MORSE IMPROVEMENT

C90 Cassettes (A) 1-12 w.p.m. with simple exercises. Suitable for R.A.E. preparation. (B) 12-24 w.p.m. computer produced professional level operator material including international symbols.

Price each: complete with instruction and exercise booklets £4.75 including postage. Morse Key and Buzzer Unit suitable for sending practice and DIY tape preparation.

Price £6.50 including postage.

Overseas Airmail £1.50 extra.

MHEL ELECTRONICS (Dept. R)
 12 Longshore Way, Milton,
 Portsmouth (UK), PO4 8LS

PEATS for PARTS
ELECTRONIC COMPONENTS
RADIO & TELEVISION
For the convenience of Irish enthusiasts we supply:

Radio & Electronics
Constructor Data Books
Panel Signs
Transfers

Also a postal service

peats
 the world of electronics
 25 Parnell Street, Dublin 1. Telephone 749972

GAREX

V.H.F. Receivers SR-9 for 2-metres F.M., fully tunable 144-146MHz, 2-speed slow-motion dial, also 11 xtal controlled channels. Compact, sensitive, ideal for fixed or mobile listening. Built-in L.S., 12v D.C. operation £47.15 inc. VAT. Crystals, if required: £2.60 each. All popular 2m, channels in stock. Marine band version (156 162MHz) £47.15 (xtals £2.90). Mains psu for above £11.95. Pocket VHF Receiver 12 channel xtal controlled complete with nicad and charger. 4MHz bandwidth in range 140-175MHz £57.95. Amateur and Marine xtals in stock, prices as SR-9.

Amplifier module new, fully assembled 6W IC unit, 12v D.C. Low impedance (4-8 Ω) input and output for extn. speaker amplification, with circuit £27.75.

Neons min wire end 70p/10; £4.50/100 Slide switches min DPDT 20p ea; 5+ : 16p Resistor Kits E12 series, 22 Ω to 1M Ω

57 values, 5% carbon film, 1/8W or 1/4W Starter pack, 5 each, value (285) £3.10

Mixed pack, 5 each 1/8W + 1/4W (570) £5.55

Standard pack, 10 each (570) £5.55

Giant pack, 25 each (1,425) £13.60

BNC Cable mtg socket 50 Ω 25p;

5+ : 20p; PL259 UHF Plug & Reducer 75p;

5+ : 67p; SO239 UHF Socket panel mtd.

60p; 5+ : 50p; Nicad rechargeables

physically equiv. to zinc-carbon types: AAA

(U16) £1.80; AA(U7) £1.30; C(U11) £3.35;

PP3 £5.55. Any 5+ : less 10%. Any 10+ less 20%.

We stock V.H.F. & U.H.F. mobile aeri-als.

s.e.e. details.

Access — Barclaycard

PRICES INCLUDE UK POST, PACKING & VAT

Mail order only Sole Address:

GAREX ELECTRONICS

7 NORVIC ROAD, MARSWORTH.

TRING, HERTS HP23 4LS

Chaddington (STD 0296) 668684

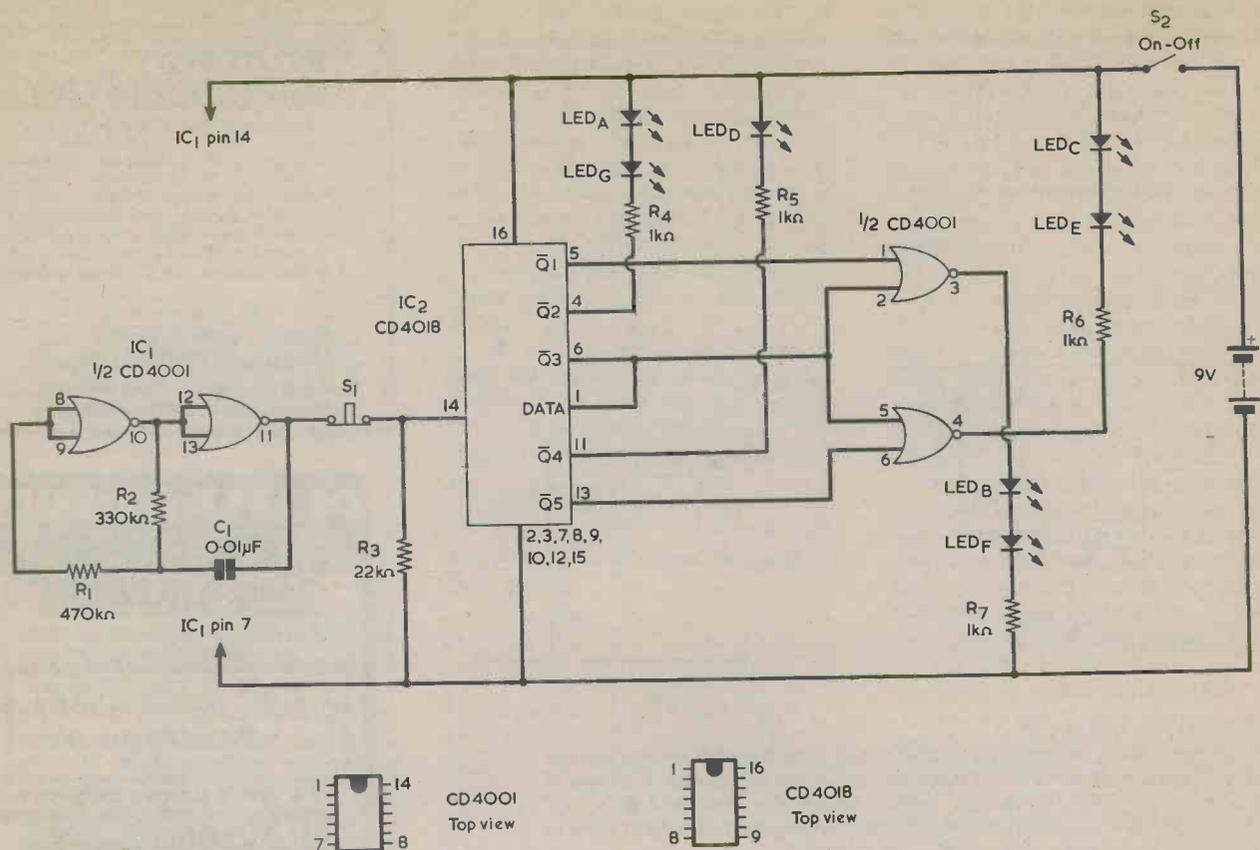


Fig. 6. Complete circuit of the electronic dice. This requires very few components

ed to pin 1 as well as going to the two NOR gates."

"That's right. Pin 1 is the data input pin and the connection to the not-Q3 output gives the CD4018 its divide-by-6 action."

"Is that the pulse generator to the left of the CD4018?"

"It is," said Smithy, "and it uses the remaining two NOR gates in the CD4001. It's a perfectly standard CMOS oscillator, and it has a frequency of about 150Hz. When you press push-button S1 you break the pulse input to the clock pin and R3 causes this pin to be taken to the negative rail. And that's about all there is to say about the circuit. Any reasonable sized 9 volt battery can be used to power the dice, and the current drawn from it varies between about 3mA and 15mA according to the number of l.e.d.'s which are alight."

Dick gazed down at the circuit, then frowned.

"There's one thing about this circuit that's worrying me a bit."

"What's that?"

"How do you *know* that the l.e.d.'s are going through the dice numbers you've just described to

me? The generator is running so fast you can't possibly see that each dice number is appearing properly in its correct order."

"There's a very easy solution to that problem," said Smithy. "We simply slow the generator down! See if you can find a 2.2µF polyester capacitor in the spares cupboard."

Dick rose and proceeded smartly towards the spares cupboard. As he did so, Smithy looked around for a pair of crocodile clip leads. When Dick returned with the capacitor, the Serviceman used the leads to temporarily connect the 2.2µF capacitor in parallel with the 0.01µF capacitor in the pulse generator circuit. (Fig. 7.)

"That," he remarked, "should reduce the generator frequency to rather less than 1Hz. I'll connect the battery again."

He clipped the red lead from the board to the positive terminal of the PP9 battery. The l.e.d.'s of the electronic dice now proceeded to change at a slow rate, and in the correct order. Smithy picked up the push-button and pressed it. The l.e.d.'s stayed at the number they displayed. Smithy released the but-

ton and pressed it again. When he repeated the process a third time the l.e.d.'s jumped to a number which was not that showing when he pressed the button or the one which should have followed it.

"What happened then?"

"It's an effect similar to contact bounce," explained Smithy. "If you press the button when the generator output is high, and if the button contacts don't break cleanly, the CD4018 might hop through

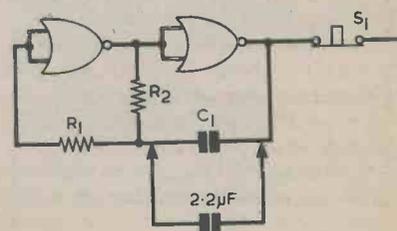


Fig. 7. Temporarily adding a capacitor across C1 slows down the pulse generator and allows circuit operation to be checked

several counts. It's an effect which doesn't worry us with the application we have here, since it can only add a random number to a number which is already random, but I thought I'd show it to you because the effect can be troublesome if the push-button is used in a circuit which has to count accurately."

"Is that the lot on this electronic dice?"

"Pretty well," stated Smithy. "The i.e.d.'s are driven by quite low currents from the CD4018 and the CD4001, and you will get a better visual effect if you use sensitive types. If you look through the mail-order catalogues and advertisements you'll see these described as 'extra bright' or 'ultra bright' or they will have a higher visible light output quoted. However, you don't have to use sensitive i.e.d.'s, as ordinary standard types will work quite adequately."

FINAL POINTS

Smithy unclipped the 2.2μF capacitor, whereupon the pulse generator returned to its previous high frequency, causing the i.e.d.'s to flicker once more. Smithy pressed the push-button and the display steadied at number 5. He released and pressed the button again, whereupon number 5 was once more displayed.

"Hey, that's two 5's in a row!"

"That's all right," said Smithy. "You're liable to get the same number repeating several times with an actual dice also. Now, as I said at the beginning, the layout is not important. You could, for instance, house the electronics in a small box, with the i.e.d.'s and an on-off switch mounted on the front panel."

"Perhaps the box could be a die-cast one," said Dick brightly. "Or, would the risk of short-circuits make an all-metal box too dicey?"

Smithy sighed.

"To be accurate," continued Dick mercilessly, "we should call it a 'die' and not a 'dice', shouldn't we?"

He ignored the groan which arose from Smithy.

"But," concluded Dick triumphantly, "we never say die!"

"Have you finished?"

"If we were Welsh," went on Dick, as a further thought occurred to him, "we could call your gadget a 'Dai-Electric'!"

"That's enough," thundered Smithy. "You and your diabolical puns! Ye gods, you've got me at it now!"

But, fortunately for the peace of the Workshop, Dick's inventive powers were now exhausted, and he and the Serviceman settled down happily to a simple game of dice with Smithy's device of only two i.c.'s. After which they put away the dice and returned to their real and proper world of finding fortuitous faults in randomly chosen radio and television receivers.

EDITOR'S NOTE

Previous articles by G. A. French dealing with the CD4018 were "Illuminated Dice" (April 1979 issue), "Electronic Dice" (February 1978) and "CD4018 Truth Tables" (June 1977).

Copies of the issues containing the above articles are available. Price 63p each, inclusive of postage.

CAN ANYONE HELP?

Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received and to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time.

Tequipment Oscilloscope Model D56 — W. Divine, 17 Firrhill Drive, Edinburgh, EH13 9ES — Circuit diagram or manual required.

'Radio Constructor' Bound Volumes Nos. 1-7 — G. M. Davies, 24 Corporation Street, Chorley, Lancs. PR6 0DP — Wants to buy, if in good condition.

Univox J6 Keyboard Instrument — F. J. Goss, 50 Englefield Road, Theale, Reading, Berks. — Wiring diagram required.

'Radio & Electronics Constructor' December 1977 — J. Tabor, The Rectory, 80 High Street, Northchurch, Berkhamsted, Herts. — Wants to purchase.

PLEASE MENTION RADIO & ELECTRONICS
CONSTRUCTOR WHEN REPLYING TO
ADVERTISEMENTS

ELECTRONIC CONSTRUCTORS

SAVE MONEY!

★ With our BARGAIN PARCEL . . . ★

Contains:

10 x BC107, 10 x BC108, 10 x BC109, 3 x BFY51, 3 x BC172, 3 x BC170 and 10 Mixed Values — ELECTROLYTICS; 10 Mixed Values — CERAMIC CAPS; 20 Mixed Values — FIXED CAPS; 10 DIODES GERMANIUM — Sim, OA91; 10 DIODES SILICON — Sim, IN914; 2 x 741 IC's, 1 2grm PHIAL CYNOACRYLAITE ADHESIVE, VAT inc. in price (all items are brand new).

Buy now — at lower than pre-budget prices Send £5.50 plus 50p p&p

(Cheque, Postal Order, Money Order) to

★ SIGTRONIC ELECTRONICS ★

27 Malvern Street, Stapenhill
Burton-on-Trent, Staffs. DE15 9DY
Tel: (0283) 46868 special orders

THE

MODERN BOOK CO.


Largest selection of English &
American radio and technical
books in the country

19-21 PRAED STREET

LONDON W2 1NP

Tel: 01-402 9176

MORSE MADE EASY

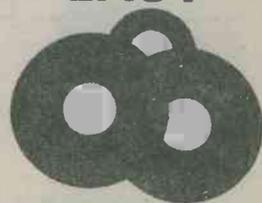

BY THE G3HSC RHYTHM METHOD!

These courses which have been sold for over 23 years, have been proved many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to transkate into letters and words.

Using scientifically prepared 3 speed records you automatically learn to recognise the code, RHYTHM without translating. You can't help it. It's as easy as learning a tune 18 WPM in 4 weeks guaranteed. The Complete Course consists of three records as well as instruction books. For Complete Course send £5.50 (overseas surface mail £1 extra).

THE G3HSC MORSE CENTRE

Box 8, 45 Green Lane, Purley, Surrey.
I enclose £5.50 or s.a.e. for explanatory booklet.

Name

Address

Electronics Constructors — Our component packs save you money!

FREE: with the first order opened this month, worth £11.50 — A Polaroid Super Swinger (Instant) Camera, value £9.95

PACK X101:— Contains 35 mixed capacitors — all good usable values, i.e. 1,500pf/0.01uf/.015uf etc. One pack for 45p or two packs for only 82p.

PACK X102:— Contains 50 Germanium Diodes — S1m to OA91 40p per pack or 2 packs for only 77p

PACK X103:— Contains 30 mixed transistors — some new and branded — NPN & PNP silicon and Germanium (most usable) great value at 60p per pack or 2 packs for £1

PACK X104:— Contains 50 silicon diodes, S1m to 1N4148, a real bargain at 46p per pack or 2 packs for 80p

PACK X105:— Contains 50 mixed Wattage resistors. Super value at 40p per pack or 2 packs for only 75p. You can't lose on this pack.

PACK X106:— Contains 20 electrolytic capacitors — ideal for transistor circuits. Values like 10mfd, 50mfd, 220mfd and 100mfd at £1 per pack or 2 packs for £1.75

PACK X107:— Contains 20 ceramic caps — ideal for transistor AF/RF circuits. Values like 150pf/270pf/330pf/22pf/39pf etc. Only 45p per pack or 2 packs, for only 80p

PACK X108:— Contains 10 BC107 or BC108 or BC109 (NPN) transistors all full spec-devices at £1.10 per pack

SIGTRONIC

* ELECTRONICS *

27 Malvern Street, Stapenhill, Burton-on-Trent, Staffs. DE15 9DY. Tel: (0283) 46868 after 6 pm. Special orders and quotations. All prices include VAT. Add 40p to order for p & p. Cheques/PO's accepted.



FIRST and STILL BEST!

We've been producing our Electronics Components Catalogue for over 20 years. During that time we've learned a lot, not only in the art of catalogue production but in building a business that serves the needs of constructors. Little wonder that we have a reputation *second to none* for our catalogue — *and* for the service that backs it up. Experience both for yourself. Just send £1.25 with the coupon and a catalogue will come by return of post.

- About 2,500 items clearly listed and indexed.
- Profusely illustrated throughout.
- 128 A-4 size pages, bound in full-colour cover.
- Bargain list of unrepeatable offers included free.
- Catalogue contains details of simple Credit Scheme.

HOME RADIO (Components LTD.
Dept. RC., 234-240 London Road, Mitcham, Surrey CR4 3HD

POST. THIS COUPON with cheque or P.O. for £1.25

Please write your Name and Address in block capitals

NAME

ADDRESS

HOME RADIO (Components) LTD., Dept. RC
234-240 London Road, Mitcham, Surrey CR4 3HD

Regd. No. 912966, London




Self-Binder

for "Radio & Electronics Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

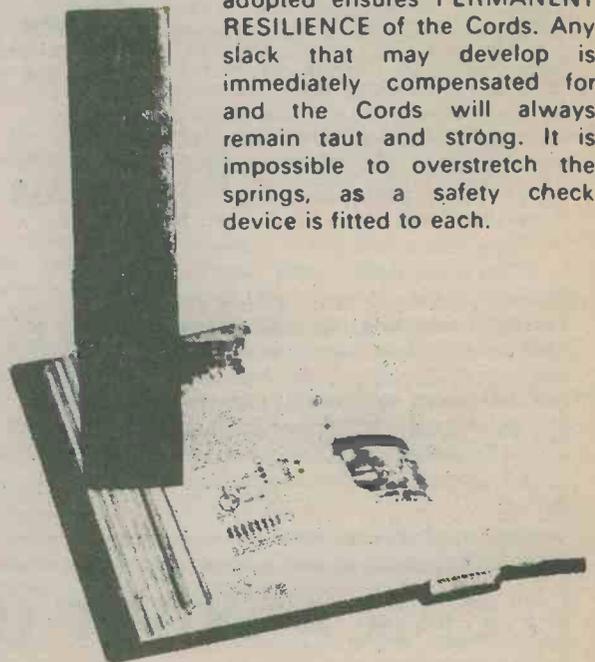

PRICE **£1.95** P.&P. 40p
including V.A.T.

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

RADIO AND ELECTRONICS CONSTRUCTOR

SMALL ADVERTISEMENTS

Rate: 12p per word. Minimum charge £2.00

Box No. 30p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers. Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. (Replies to Box Numbers should be addressed to: Box No. —, *Radio and Electronics Constructor*, 57 Maida Vale, London, W9 1SN.

AERIAL BOOSTERS — B11 VHF/FM Radio — B11A VHF 2 Metre Radio — B45 UHF Television. Price £5. S.A.E. for leaflets, Electronic Mailorder Ltd., Ramsbottom, Bury, Lancs. BL0 9AG.

SOLAR CELLS: Bits, books and bargains. Send 95p for Solar Cell booklet and Data Sheets or stamp for list. — Edencombe Ltd., 34 Nathans Road, North Wembley, Middlesex HA0 3RX.

CONSTRUCTORS 200 mixed components £4. 30W soldering irons £2.60. Full refund guarantees. Lists 15p refundable. Mail only. Components bought. Sole Electronics, 37 Stanley Street, Ormskirk, Lancs.

COMPLETE REPAIR INSTRUCTIONS for any requested TV, £5 (with diagrams £5.50). Any requested service sheet £1 plus s.a.e. S.a.e. brings free newsletter, details unique publications, vouchers and service sheets from 50p. AUSREC, 76 Church Street, Larkhall, Lanarkshire.

FOR SALE: Inverter, 12V d.c. to 240V a.c. Suitable running electric shaver, camping, boating, etc. £5.50. Box No. G355.

WANTED: Large and small quantities of transistors, I.C.'s displays, etc., etc. Call any Saturday to: 306 St. Paul's Road, London N.1. Telephone: 01-359 4224.

P.C.B. DESIGN. Outline p.c.b. drawings, layouts etc., for the amateur. Cost according to circuit complexity. D. G. Harrington, 25 Poynter Road, Bush Hill Park, Enfield, Middlesex.

CONSTRUCT METAL DETECTORS: 1. £120 pulse discriminator (£12 construction cost). 2. £60 model (£6 con/cost). 3. £30 BFO (£3 con/cost). For all three together, written guaranteed d.i.y. plans, send £2. (Dept. RC), J. Lucas, 2 College Road, Grays, Essex. (Established 1973).

PARCELS: 200 mixed components £4. 100 £2.75. 10 red LED's 125 90p. 100 mixed branded transistors, new, £2.50. 50 mixed untested i.c.'s 65p. Lists 15p. Sole, 37 Stanley Street, Ormskirk, Lancs., L39 2DH.

FOR SALE: *Fundamentals of Radio Servicing* by B. Hicks, published by Hutchinsons Educational, £2.20 post paid. *Handbook of Satellites and Space Vehicles* by R. P. Haviland, £3.50 post paid. — Box No. G366.

RADIO, ELECTRONICS, TELEVISION BOOKS. Largest variety. Lowest prices. Write for list, Business Promotion Bureau, 376 Lajpat Rai Market, Delhi 110006, India.

(Continued on page 125)

7400 10p	7432 20p	7482 75p	74126 35p	74155 45p	74181 130p
7401 10p	7433 20p	7483 75p	74128 80p	74156 45p	74182 50p
7402 10p	7437 20p	7484 75p	74130 120p	74157 45p	74184 120p
7403 10p	7438 20p	7485 60p	74131 90p	74180 85p	74185 100p
7404 12p	7440 12p	7486 25p	74132 45p	74181 85p	74188 320p
7405 12p	7441 45p	7489 130p	74135 90p	74182 85p	74190 70p
7406 25p	7442 40p	7490 25p	74136 80p	74183 85p	74191 70p
7407 25p	7443 60p	7491 40p	74137 90p	74184 80p	74192 80p
7408 12p	7444 60p	7492 35p	74138 90p	74185 60p	74193 80p
7409 12p	7445 65p	7493 30p	74141 80p	74186 75p	74194 85p
7410 12p	7446 50p	7494 35p	74142 180p	74187 180p	74195 80p
7411 15p	7447 50p	7495 45p	74143 270p	74170 100p	74196 50p
7412 15p	7448 50p	7496 45p	74144 270p	74173 80p	74197 50p
7413 25p	7450 12p	7497 120p	74146 85p	74174 80p	74198 100p
7414 45p	7451 12p	74100 80p	74147 100p	74175 80p	74199 100p
7416 25p	7453 12p	74104 40p	74148 90p	74178 80p	74203 80p
7417 25p	7454 12p	74105 40p	74150 85p	74177 80p	741500 180p
7420 12p	7460 12p	74107 25p	74151 45p	74178 75p	7451 12 80p
7421 20p	7470 25p	74108 100p	74153 45p	74179 120p	7423 20p
7422 15p	7472 20p	74109 25p	74154 70p	74180 70p	7426 25p
7426 22p	7473 25p	74118 75p	7476 25p	74122 35p	7428 25p
7427 22p	7474 25p	74120 80p	7480 40p	74123 40p	7430 12p
7428 25p	7475 25p	74121 25p	7481 85p	74125 35p	

LINEAR	LM380 60p	SN76013ND	TBA700 180p
AY38500 45p	LM381N 90p	SN76023N 128p	TBA720Q 225p
CA3039 70p	LM382 90p	SN76023N 110p	TBA750Q 200p
CA3046 80p	LM391 180p	SN76023ND 128p	TBA800 80p
CA3060 225p	LM555 25p	SN76033N 180p	TBA810 100p
CA3065 200p	LM709C 40p	SN76227N 180p	TBA820 200p
CA3076 250p	LM710DL 85p	SN76228N 180p	TBA920Q 280p
CA3080 75p	LM723T05 40p	SN76680N 75p	TCA270Q 220p
CA3084 250p	LM723DIL 40p	TAA300 100p	TCA270S 220p
CA3085 85p	LM733 120p	TAA350 190p	TCA760 300p
CA3086 60p	LM741 20p	TAA550 35p	ICA4600A 480p
CA3088 190p	LM748 40p	TAA570 220p	IDA1008 380p
CA3089 160p	LM1303N 100p	TAA651B 140p	IDA1034 480p
CA3090AQ 380p	LM1458 100p	TAA700 350p	IDA2002 300p
CA3123E 130p	LM3080 75p	TAA790 350p	TOA2020 300p
CA3130 100p	LM3900 85p	TAD100 180p	TORA 120p
CA3140 80p	LM3909N 85p	TAD110 130p	XR320 280p
LF356 80p	MC1310P 140p	TAD120T 85p	XR2206 450p
LM211H 250p	MC1312P 150p	TBA120S 80p	XR2208 600p
LM300TRS 170p	MC1314P 190p	TBA480Q 200p	XR2216 850p
LM301AN 30p	MC1315P 230p	TBA520Q 200p	XR2587 280p
LM304 200p	MM50398 680p	TBA530Q 200p	XR4136 180p
LM307N 85p	MM5314 380p	TBA540 200p	XR4202 150p
LM308T05 100p	MM5316 480p	TBA550Q 250p	XR4212 180p
LM308DIL 100p	NE529K 150p	TBA560C 280p	XR4739 180p
LM309K 100p	NE556 25p	TBA641A12 280p	2N414 100p
LM310T05 150p	NE556 80p		95H80 700p
LM311T05 150p	NE5628 400p		
LM317K 325p	SAD1024 1500p		
LM324 70p	SL9175 850p		
LM339 80p	SN76003N 180p		
LM348N 90p	SN76013N 110p		

in 1148 units by L.T.T. (Total 100 for £1.00)
 Silver 250 x 4 bit 100 sets for £1.00 each
 2112 250 x 4 bit 100 sets for £2.00
 More sets available in various quantities. All prices include post and VAT.



T. POWELL

306 ST. PAUL'S ROAD,
HIGHBURY CORNER, LONDON N.1

Telephone: 01-226 1489

ALL PRICES INCLUDE POST AND V.A.T.





Wilmslow Audio

THE firm for speakers!

SEND 30p FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST

AUDAX • AUDIOMASTER • BAKER • BOWERS & WILKINS • CASTLE • CELESTION • CHARTWELL • COLES • DALESFORD • DECCA • EMI • EAGLE • ELAC • FANE • GAUSS • GOODMANS • I.M.F. • ISOPON • JR • JORDAN WATTS • KEF • LEAK • LOWTHER • MCKENZIE • MONITOR AUDIO • PEERLESS • RADFORD • RAM • RICHARD ALLAN • SEAS • STAG • TANNON • VIDEOTONE • WHARFEDALE • YAMAHA • SHACKMAN • TANGENT


WILMSLOW AUDIO

DEPT REC
SWAN WORKS, BANK SQUARE, WILMSLOW CHESHIRE SK9 1HF
 Discount HiFi Etc. at 5 Swan Street
 Tel: 0625-529599 for Speakers, 0625-526213 for HiFi

DIRECT SUPPLY SERVICE TO READERS

TOWERS INTERNATIONAL OPAMP LINEAR-IC SELECTOR

(JUST PUBLISHED)

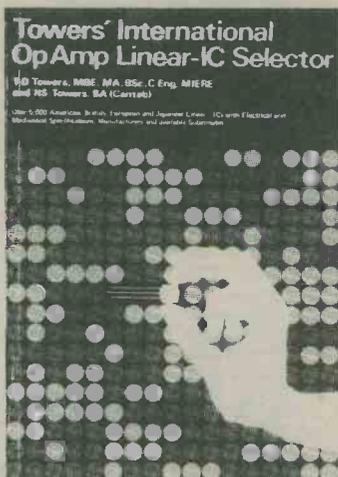

This opamp linear-IC compendium, a comprehensive tabulation of basic specifications for over four thousand opamps, offers information on:

1. Ratings
2. Characteristics
3. Case details
4. Terminal identifications
5. Applications use
6. Manufacturers
7. Substitution equivalents (both European and American)

This work covers not only classical 'pure' opamps, but also several classes of 'quasi-opamps' (i.e. linear-ICs with opamp-like characteristics) such as dc-comparators, operational-transconductance-amplifiers, differential-output amplifiers, current-difference amplifiers, and voltage-follower amplifiers.

The more than 4,000 opamps covered in this self-contained volume are a selection of the more common current and widely-used obsolete types.

The coverage is international in scope and includes opamps not only from the USA and Continental Europe, but also from the United Kingdom and the Far East (Japan).

Price £7.50 inc P&P

(Please allow 21 days for delivery)

**Tower's
International
OpAmp Linear-IC
Selector**

by T. D. Towers
MBE, MA, BSc, C Eng, MIERE
£7.50
inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME

ADDRESS

.....

.....

.....(Block capitals)

TOWERS INTERNATIONAL FET SELECTOR



If you deal with field effect transistors, or fet's — whether as a student, a hobbyist, a circuit engineer, a buyer, a teacher or a serviceman — you often want data on a specific fet of which you know only the type number.

Specifications apart, you may be even more interested in where you can get the device in question. And perhaps more important still (particularly with obsolete devices), you may want guidance on a readily available possible substitute.

This fet compendium, a comprehensive tabulation of basic specification, offers information on:

1. Ratings
2. Characteristics
3. Case details
4. Terminal identifications
5. Applications use
6. Manufacturers
7. Substitution equivalents (both European and American)

The many fet's covered in this compendium are most of the more common current and widely-used obsolete types.

It is international in scope and covers fet's not only from the USA and Continental Europe, but also from the United Kingdom and the Far East (Japan).

Price £4.00 inc P&P

**Tower's
International
FET
Selector**

by T. D. TOWERS
MBE, MA, BSc, C Eng, MIERE
£4.00
inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME

ADDRESS

.....

.....

.....(Block capitals)

SMALL ADVERTISEMENTS

(Continued from page 123)

VHF/FM TRANSMITTER KIT. New silicon chip design means low price (beats anyone else) and better performance. Very small. Fully tuneable 88-108MHz. Instructions etc., all included. **INTRODUCTORY OFFER £1.95 plus 30p P&P.** (Unlicensable). M. Henry, 30 Westholme Gardens, Ruislip, Middlesex.

WANTED: FAX equipment, manuals, service sheets, etc. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk. NR32 3PJ.

FOR SALE: Bush cassette tape recorder, battery driven. Microphone, etc. Excellent condition. £10 plus postage. Box No. G375.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. — both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £6.00 per annum. (U.K. and British Commonwealth), overseas \$12.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

FOR SALE: Copies of *Radio Constructor*, W.W., P.W., P.E., 1956 on, from 5p plus post. S.A.E. enquiries. 1 Hazel Grove, Yelverton, Devon, PL20 6DX.

FOR SALE: "Challenge of the Stars" by Patrick Moore and David A. Hardy £2.00. "Destroyers" by Antony Preston £4.00. Box No. G376.

X-BAND SPECTRUM ANALYSER for sale or exchange for good multimeter. Telephone Swindon 751112.

INTERESTED IN OSCAR? Then join AMSAT-UK. Newsletters, OSCAR NEWS Journal, prediction charts, etc. Details of membership from: Ron Broadbent, G3AAJ, 94 Herongate Road, Wanstead Park, London, E12 5EQ.

DIGITAL MULTIMETER Doram. Cost £68. Also similar multimeter. (Watford) £55. Offers, 4 Riversley Road, Gloucester, GL2 0QT.

COLLECTORS' ITEMS. Nearly 50 copies of Radio Society of Great Britain's *Bulletins* covering period 1945 to 1949. In reasonable condition. Offers to: Box No. G377.

THE RADIO AMATEUR INVALID & BEDFAST CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mr. H. R. Boutle, 14 Queens Drive, Bedford.

SIGNAL INJECTORS (AF/RF) £2.50 with full instructions. Pin points faults in radios/amps. quickly. Or send s.a.e. for list of low priced test equipment. Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

WANTED: WB. HF1016 speaker. State price. Burton, 24 Holly Road, Birmingham, B16 9NH. (Telephone: 021-454-2046).

FOR SALE: 25 mixed voltage 2W zeners 50p. Switch cleaner 50p. P/r cassette mechanisms £10 and £15. S.a.e. for details. Incomplete video tape recorders £50. Closed circuit TV cameras £50. Hearing aid amplifiers £1. Red l.e.d.'s 5p and 10p. 1N914 — 100 — 50p. 10 fuseholders £1. 6 power transistors £1. Miniature relays 25p. Box No. G381.

(Continued on page 127)

COMPONENT PACKS

PU1: 50 untested, unmarked t.t.l. i.c.'s (mostly 7400 series) **65p**

PU2: Untested, unmarked silicon diodes, some germanium. Pack of 200 (approx.). **65p**

PT1: Tested, marked selection of popular diodes. Contains: 25 x 1N914, 10 x 1N4002, 5 x BY127 **125p**

PT2: Tested selection of popular electrolytic capacitors. Contains: 5 x 1µF, 5 x 4.7µF, 5 x 10µF, 3 x 100µF **150p**

PT3: Five 1/4W 5% resistors of each value from 10Ω to 1M. Total of 305. Tested. **325p**

PT4: Stranded connecting wire. Five colours each 5 metres. **65p**

PT5: As pack PT4 but solid conductor. **65p**

BARGAIN SPOT

Whilst stocks last

Money refunded if unavailable

2,200µF 25V electrolytic **38p**

AD142 Transistor **30p**

S.P.S.T. Toggle switch **29p**

SEMICONDUCTORS

BC107	12p	7400	12p
BC108	12p	7402	12p
BC109	12p	7408	12p
BC182	12p	741	25p
BC183	13p	ZN414	100p
BC184	13p	BY127	15p
BC212	10p	OA200	20p
BC214	10p	M6800	740p

OPTO-ELECTRONICS

LEDs	0.125"	0.2"	each
Red	TIL209	FLV117	15p
Yellow	TIL211	FLV310	22p
Green	TIL213	FLV410	24p
Clips, either type, extra			2p
DL707 CA Display			90p

DIN PLUGS AND SOCKETS

	Plug	Socket
2-pin	7p	7p
3-pin	11p	9p
5-pin 180°	13p	10p
5-pin 240°	14p	11p

4mm plugs and sockets. Available in the following colours: Black, Blue, Red, Green, White & Yellow. Plug 10p Socket 11p Terminal 25p

Mail order only. All prices include VAT. Please add 20p for postage (except component packs). Full list available on receipt of large s.a.e.

T. & J. ELECTRONIC COMPONENTS
98 Burrow Road, Chigwell, Essex IG7 4HB

A CAREER IN RADIO

Start training **today** and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs — they can do the same **for you**.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

CITY & GUILDS CERTIFICATES	TECHNICAL TRAINING
Telecommunications Technicians'	ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:
Radio TV Electronics Technicians'	Electronic Engineering & Maintenance
Electrical Installations Technicians'	Computer Engineering/Programming
Electrical Installation Work	Radio, TV & Audio Engineering & Servicing
Radio Amateurs'	Electrical Engineering, Installations & Contracting
MPT Radio Communications Cert	
EXAMINATION STUDENTS — GUARANTEED COACHING UNTIL SUCCESSFUL	

COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in
Name Age
Address
Occupation

ICS

Accredited
by CACC
Member of
ABCC

To
International Correspondence Schools
Dept M278 Intertext House, LONDON
SW8 4UJ or phone 01-622 9911 (anytime)

RADIO MODELLER

ELECTRONIC BOOKS

● MODEL RADIO CONTROL

Detailing both Theory and Practice, this book, by leading authority Paul Newell, has become the standard reference work. A brief historical survey leads up to a detailed description of proportional systems, with over 100 illustrations, including theoretical circuits and p.c. layouts for an advanced digital system.
134 pages

Price £3.35

U.K. Packing
& Postage

32p

theory and
practice of

MODEL RADIO CONTROL

Development of a stem
proportional explained
digital system design
practical examples and
full circuit details

ON SALE NOW
at all leading shops
or direct from:—

**RADIO MODELLER
BOOKS DIVISION,
High Street,
Sunningdale,
Berkshire SL5 0NF.**

REVOR OPTICAL & TECHNICAL

6 SICILIAN AVENUE
LONDON W.C.1
Tel. 01-836 4536

£14.91

**POST
FREE**


4" dia. lens

**FLEXIBLE
MAGNIFIER**

WITH CAST IRON BASE,
PRECISION GROUND AND
POLISHED LENS, CHROME PLATED
FRAME AND FLEXIBLE TUBE.
IDEAL FOR HOBBIES, AND
DETAILED WORK WHICH REQUIRES
BOTH HANDS FREE.

CALLERS WELCOME

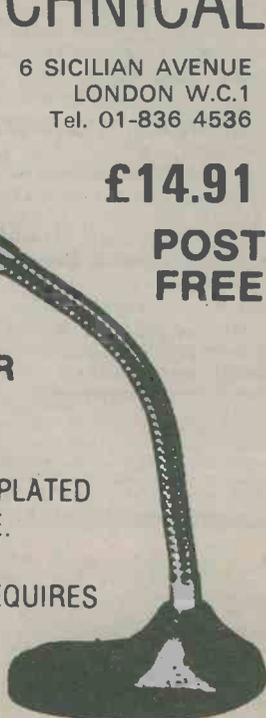
(Subject to price ruling at the time of issue)



PLAIN-BACKED SELF-BINDERS

for your other magazines

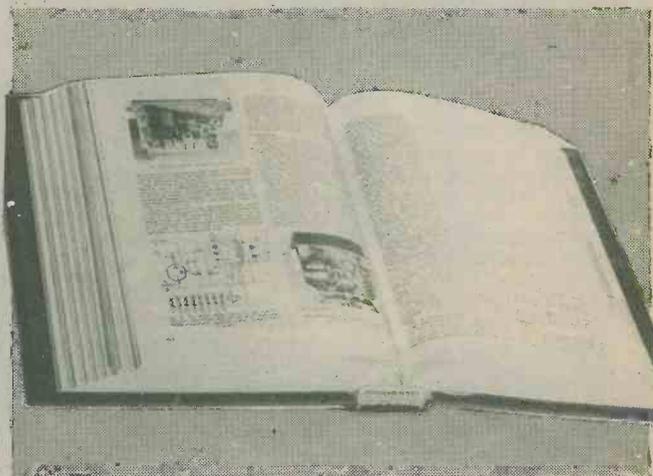(Maximum Format 11 $\frac{1}{4}$ " x 8 $\frac{1}{4}$ ")



The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

COLOURS: MAROON OR GREEN
(If choice not stated, colour available will be sent)

PRICE £1.95 p. & p. 40p
including V.A.T.

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 125)

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. — The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

2 METRE FM MONITOR RECEIVER MODULE. PCB size 5 in. x 2½ in. 6 channel. Complete kit including prewound coils/transformers and ceramic filters £24.30. Matching scanner, 2 mode kit £7.90 inc. LED's. Receiver crystals £2.50 per channel. Details s.a.e. A. Bailey, G3WPO, 9 Alberta Walk, Worthing, Sussex.

FOR SALE Gent's wrist watch, £20. Nurse watch, £12. Box No. G382.

INTERCOM/BABY ALARM. 50 ft. lead, volume control. Only £7.95. Refund guarantee. J. Harmsworth (RE2), 34 Victoria Street, Eccles, Maidstone, Kent.

WANTED: Telford Communications TC10 "Multimode" 2 metre transmitter. Details and price please to Box No. G383.

FOR SALE: *Radio & Electronics Constructor*. Seven bound volumes. 1958-1961, 1969-1970, 1971-1972 (Two copies), 1972-1973. Offers? Merseyside. Telephone: 051-426 6767.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

SPONSORS required for exciting scientific project Norwich Astronomical Society are building a 30" telescope to be housed in a 20' dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS, Secretary, 195 White Woman Lane, Old Catton, Norwich, Norfolk.

FOR HELP with (elementary) Computer, statistical or technical mathematics, send query, s.a.e., paper, P.O. for 50p to: Box No. G380.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: — The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NR0 85S.

CHI-KUNG for mental/physical health. Discover "Chi" — the life-force/bio-electricity in your body. Send stamp for your Free Literature. The Chi-Kung Society (REC39), 64 Cecil Road, London E13 0LR.

BROADLANDS RESIDENTIAL CLUB for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

Give for those who Gave

WINGS APPEAL



During September




Random Electronic EASY DICE

Build your own 'EASY DICE' from the 5 intergrated circuits and full components supplied, including box and descriptive instructions.

Complete
or
Kit



P.C.B.
Layout

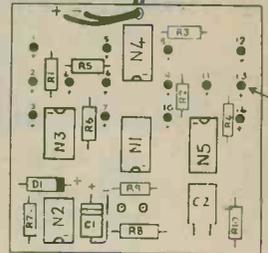

All you need is a soldering iron
TWO DICE FACES TOUCH CONTROL...

- a *Self Assemble Dice £3.95
- b *Ready built Dice £4.75 (INCL. P+P)

Order now from: **Fringewood Electronics Ltd**
1 Hatton Court Ipswich Suffolk O473-210151

Amount enclosed £

Name

Address

please state amount required in appropriate box a b

BUILD YOUR OWN

P.A. GROUP & DISCO SPEAKERS by R. F. C. Stephens

Save money with this practical guide. Plans for 17 different designs, Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

THE INFRA-BASS LOUDSPEAKER by G. Holliman

(full constructional details for versions using 15", 12" and 10" drive units.) £2.95 post free (\$6 overseas).

THE DALESFORD SPEAKER BOOK by R. F. C. Stephens

This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

VAN KAREN PUBLISHING

5 Swan Street, Wilmslow, Cheshire

Build 50 Interesting Projects on a P.C. Chassis with surplus components from your "Spares Box".

EXPERIMENTER'S PRINTED CIRCUIT KIT

Contents: 4 small boards to suit the enclosed designs, etching powder, resist paint, solvent, degreaser and etching instructions. Also 50 Circuit Diagrams, chassis plans and layouts for simple Crystal Sets, Transistor Receivers, Transmitters, Ring Radio Metal Detector, Radio Control, Ultrasonic Alarm, Intercoms, Amplifiers, Instruments, Gadgets, etc. you can build at negligible cost with 'surplus' or reclaimed parts and transistors you already have.

Price: £1.70. Postage & pack. 30p

PHOTOELECTRIC KIT

A kit of basic parts to build a simple, I.R. sensitive photoelectric switch. Contents: phototransistor, transistors, diode, resistors, connector, relay chassis board, case, screws rivets and full instructions. Also plans for Modulated-Light Alarms. Price: £4.50. Postage & pack. 50p.

OPTICAL KIT

A kit of parts of build an I.R. folded-beam projector and receiver to suit the above kit. Contents: 2 lenses, 2 mirrors, 2 45° blocks, infra-red filter, lampholder, building plans, etc. Price: £3.70. Postage & pack. 30p. Both kits together make an efficient Invisible Beam Burglar Alarm.

EXPERIMENTAL ELECTRONICS

335 Battersea Park Road, London S.W. 11 4SL

Send S.A.E. for full details of all kits and circuits

RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price 50p each, p&p 13p

Issue(s) required

Annual Subscription

Price **£7.50 inland, £8.50 overseas (including Eire)**

post free, commence with issue

Bound Volumes:

Vol. 27. August 1973 to July 1974	Price £3.00 , post & pkg 90p
Vol. 28. August 1974 to July 1975	Price £3.20 , post & pkg 90p
Vol. 29. August 1975 to July 1976	Price £3.50 , post & pkg 90p
Vol. 30. August 1976 to July 1977	Price £3.70 , post & pkg 90p
Vol. 31. August 1977 to July 1978	Price £5.20 , post & pkg 90p

CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,
maroon only

Price **£1.95**, post & pkg 40p

With no title on spine, maroon

Price **£1.95**, post & pkg 40p

With no title on spine, green

Price **£1.95**, post & pkg 40p

Prices include V.A.T.

DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages Price **£1.20**, P. & P. 20p

DB6 Radio Amateur Operator's Handbook,
New edition in course of preparation

DB17 Understanding Television, 504 pages Price **£3.95**, P. & P. 70p

DB19 Simple Short Wave Receivers Price **80p**, P. & P. 20p
140 pages

STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording — White — 6 sheets Price **£1.00**, P. & P. 8p

Set 4: Wording — Black — 6 sheets Price **£1.00**, P. & P. 8p

Set 5: Dials — 6 sheets Price **£1.00**, P. & P. 8p

Prices include V.A.T.

I enclose Postal Order/Cheque for in payment for

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable through your local bookseller

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS

TRANSFORMER CURRENTS


In (a) an a.c. generator couples to the primary of an iron-cored transformer, and the secondary connects to a load. An alternating voltage whose magnitude depends on the turns ratio of the transformer appears across the load. The current induced in the secondary flows in the *opposite* direction to that flowing in the primary.

The current directions can be more readily visualised by drawing the primary and secondary on the same side of the core, as in (b). Both windings are wound in the same direction. At an instant when the upper terminal of the generator is positive, current (assumed to flow from positive to negative) flows in the primary as indicated. The induced current in the secondary flows into the load as shown.


This is not an anomalous situation, and it explains the behaviour of transformer windings when connected in series. As can be seen in (c), when the upper end of the primary is positive (current passing in) so also is the upper end of the secondary (current passing out).

In (d) we join the primary and secondary in series, and the voltage from the secondary adds to the voltage from the generator. When connected as in (e) the voltage from the secondary is subtracted from that from the generator.

In the autotransformer of (f), a common section of the winding carries both primary and secondary currents. Since these flow in opposite directions, the actual current is the smaller subtracted from the larger and, for secondary voltages greater than half the primary voltage, is less than the current from the generator. In consequence the common section may be wound with thinner wire than the non-common section above it.

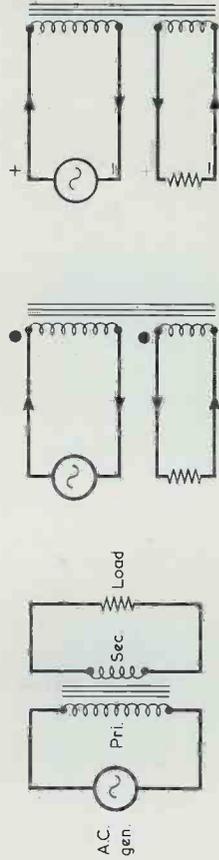


(a)

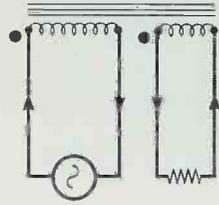


● = winding start

(b)


(c)

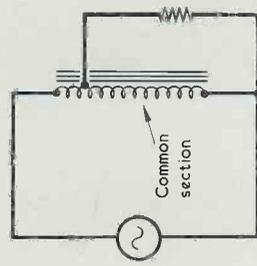

(d)

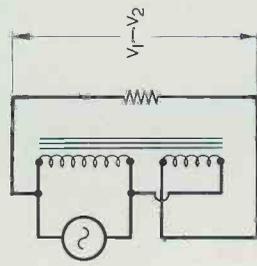

(e)

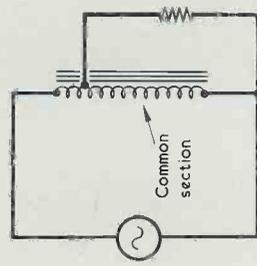

(f)

MAPLIN



This superb organ – build the first working section for just over £100. Full specification in our catalogue.



Touch operated rhythm generator, the 'Drumsette'. Construction details 25p. (Leaflet MES49). Specification in our catalogue.



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.



61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages – some in full colour – it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices; special offers and all the latest news from Maplin.



A range of highly attractive knobs is described in our catalogue. Our prices are very attractive too!



The 3800 synthesiser build it yourself at a fraction of the cost of one ready-made with this specification. Full details in our catalogue.



A pulse width train controller for smooth slow running plus inertia braking and acceleration. Full construction details in our catalogue.



Speakers from 1½ inch to 15 inch; megaphone. PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!

Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 37p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. REC1079 I enclose £1.07.

NAME _____

ADDRESS _____



A wide range of disco accessories at marvellous prices. Our catalogue has all the details.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:—
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop: 284 London Road, Westcliff-on-Sea, Essex
 (Closed on Monday).
 Telephone: Southend (0702) 554000.