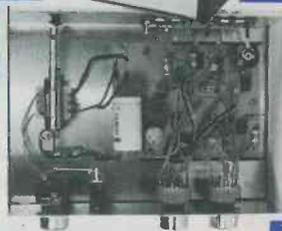


RADIO & ELECTRONICS CONSTRUCTOR

DECEMBER 1980
60p

OPTO- COUPLED



VOLUME EXPANDER

*Increases dynamic
programme range.
Adds realism to
orchestral
music.*

MORSE PRACTICE
BUZZER

An
Invitation
to
Transmit



'K' TONE GENERATOR




AUTOMATIC LOGIC
SENDS A MORSE
'K' AT EACH 'OVER'

ADD-ON CLIPPING MONITOR



MONITOR CIRCUIT
POWERED BY
AMPLIFIER
OUTPUT

MULTI-OPTION
CHIP

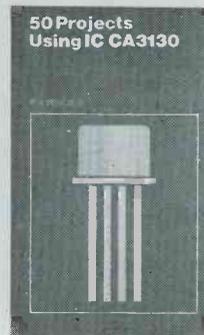

DIRECT READER SERVICE RADIO & ELECTRONICS BOOKS

| | | | |
|---|-------|--|-------|
| 18. 50 Projects Using IC CA3130 | £1.25 | 40. Projects in Opto-Electronics | £1.25 |
| 19. 50 CMOS IC Projects | £1.25 | 41. Radio Circuits Using IC's | £1.35 |
| 20. A Practical Introduction to Digital IC's | 95p | 42. Mobile Discotheque Handbook | £1.35 |
| 22. Beginners Guide to Building Electronic Projects | £1.25 | 43. Electronic Projects for Beginners | £1.35 |
| 23. Essential Theory for the Electronics Hobbyist | £1.25 | 44. Popular Electronic Projects | £1.45 |
| 26. 52 Projects Using IC741 | 95p | 45. IC LM3900 Projects | £1.35 |
| 28. Two Transistor Electronic Projects | 85p | 46. Electronic Music and Creative Tape Recording | £1.25 |
| 29. How to Build Your Own Metal and Treasure Locators | £1.00 | 47. Practical Electronic Calculations and Formulae | £2.25 |
| 30. Electronic Calculator Users Handbook | 95p | 48. Radio Stations Guide | £1.45 |
| 31. Practical Repair and Renovation of Colour TVs | £1.25 | 49. Electronic Security Devices | £1.45 |
| 32. Handbook of IC Audio Pre-amplifier and Power Amplifier Construction | £1.25 | 50. How to Build Your Own Solid State Oscilloscope | £1.50 |
| 33. 50 Circuits Using Germanium, Silicon and Zener Diodes | 75p | 51. 50 Circuits Using 7400 Series IC's | £1.45 |
| 34. 50 Projects Using Relays, SCR's and TRIACS | £1.25 | 52. Second Book of CMOS IC Projects | £1.50 |
| 35. Fun and Games with your Electronic Calculator | 75p | 53. Practical Construction of Pre-Amps, Tone Controls, Fitters & Attenuators | £1.45 |
| 36. 50 (FET) Field Effect Transistor Projects | £1.25 | 54. Beginners Guide to Digital Techniques | 95p |
| 37. 50 Simple L.E.D. Circuits | 75p | 55. 28 Tested Transistor Projects | £1.25 |
| 38. How to Make Walkie-Talkies | £1.25 | 56. Digital IC Equivalents and Pin Connections | £2.50 |
| 39. IC 555 Projects | £1.75 | 57. Linear IC Equivalents and Pin Connections | £2.75 |

POSTAGE: 20p PER BOOK. IF MORE THAN 3 BOOKS ORDERED: 10p PER BOOK

To: Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please send me within 21 days copy/copies

Book Nos:

.

I enclose Postal Order/Cheque for £

Name

Address

.

(Block Letters Please)

(We regret this offer is only available to readers in the U.K.)

RADIO & ELECTRONICS CONSTRUCTOR

December 1980
Volume 34 No. 4

Published Monthly

First published in 1947

Incorporating *The Radio
Amateur*

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone
01-286 6141

Telegrams
Databux, London

© Data Publications Ltd., 1980. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £9.50, Eire and Overseas £10.50 (U.S.A. and Canada \$25.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production – Web Offset.

| | |
|--|-----|
| NEWS AND COMMENT | 206 |
| THE MAGIC HAND – Suggested Circuit – by G. A. French | 208 |
| RECIPROCAL WORKING by G. B. Brown | 210 |
| ADD-ON CLIPPING MONITOR – Monitor Circuit Powered by Amplifier Output, Imposes Negligible Loading – by M. V. Hastings | 212 |
| MORSE PRACTICE BUZZER by P. Fletcher | 216 |
| The INSTRUCTOR – A Practical Introduction to Microprocessors – – Part 5 by Ian Sinclair | 218 |
| IN NEXT MONTH'S ISSUE | 223 |
| OPTO-COUPLED VOLUME EXPANDER – Increases Dynamic Programme Range, Adds Realism to Orchestral Music – by R. A. Penfold | 224 |
| MULTI-OPTION CHIP by R. J. Caborn | 231 |
| TRADE NOTE | 233 |
| SHORT WAVE NEWS – For DX Listeners by Frank A. Baldwin | 234 |
| "K" TONE GENERATOR by Trevor Hopkins | 236 |
| NEW PRODUCT | 239 |
| THE "HAUNTED" RADIO – Novelty Medium Wave Radio Faults – in Your Workshop | 240 |
| NEGLECTED OSCILLATOR by R. S. Burns | 246 |
| RADIO TOPICS by Recorder | 248 |
| VOLTAGE REGULATORS Electronics Data No. 64 | iii |

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The *Radio & Electronics Constructor* is printed by LSG Printers, Portland Street, Lincoln.

OUR NEXT ISSUE
WILL BE PUBLISHED
MID-DECEMBER

Conquer the chip.


Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.




MASTER ELECTRONICS

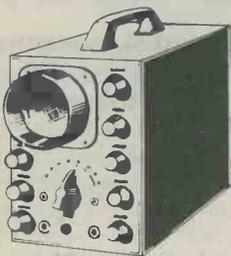

LEARN THE
PRACTICAL WAY BY
SEEING AND DOING

- Building an oscilloscope.
- Recognition of components.
- Understanding circuit diagrams.
- Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.

MASTER COMPUTERS

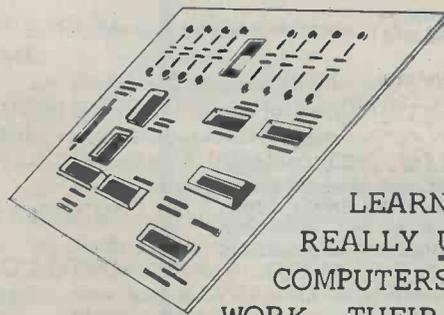

LEARN HOW TO
REALLY UNDERSTAND
COMPUTERS, HOW THEY
WORK - THEIR 'LANGUAGE'
AND HOW TO DO PROGRAMS.

- Complete Home Study library.
- Special educational Mini-Computer supplied ready for use.
- Self Test program exercise.
- Services of skilled tutor available.

MASTER THE REST

- Radio Amateurs Licence.
- Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators - Digital Meters etc.

FREE

Please send your **FREE** brochure without obligation to:—

REC/12/811

Name

Address

BLOCK CAPS PLEASE

I am interested in :-

PRACTICAL ELECTRONICS

COMPUTER TECHNOLOGY

OTHER SUBJECTS

(please state your interest)

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS.

MAGENTA ELECTRONICS LTD.

R.E.C. PROJECT KITS

Make us YOUR No. 1 SUPPLIER OF KITS and COMPONENTS for R.E.C. Projects. We supply carefully selected sets of parts to enable you to construct R.E.C. projects. Project kits include ALL THE ELECTRONICS AND HARDWARE NEEDED - we have even included appropriate screws, nuts and I.C. sockets. Each project kit comes complete with its own FREE COMPONENT IDENTIFICATION SHEET. We supply - you construct. PRICES INCLUDE CASES UNLESS OTHERWISE STATED. BATTERIES NOT INCLUDED. IF YOU DO NOT HAVE THE ISSUE OF R.E.C. WHICH CONTAINS THE PROJECT - YOU WILL NEED TO ORDER THE INSTRUCTIONS/REPRINT AS AN EXTRA - 45p. each.

- LIGHT CHANGE ALARM** Dec. 78. £11.84
In daylight detects someone moving around a room - after dark can be triggered by just torchlight. Units output rs from a relay (included).
- DYNAMIC MIC PRE AMP** Sept. 78 £5.82
Features the ZN424E - with very low distortion and noise.
- ULTRA SENSITIVE ULTRASONIC REMOTE CONTROL** Feb 79 £12.45 and
DOPPLER SHIFT ADD ON UNIT Mar 79. extra £5.22
First part covers the construction of a sensitive remote control switch - an ultrasonic transmitter and receiver. The Doppler Shift add on unit detects movement within the vicinity of the transducers, and so has applications as a burglar alarm.
- RING OF LEDS PRINT TIMER** Jan 80 £11.22.
Unusual display indicates 8 segments of timing period. A ring of 8 leds light progressively. Switch selectable timing periods of 1, 2, 3, and 4 minutes. Very smartly housed in a Vero Case.
- LOGIC TESTER** Jan 80 £5.89.
Detects overload, logic state and pulse voltages in TTL circuits. A piece of veroboard is included - but the layout is left to the constructor. Portable. Battery operated. Supplied with test leads.
- TELEPHONE BELL REPEATER** Feb 80 £7.48.
Includes 2 cases and speakers. Twin fig 8 cable to link units 7p per metre extra. Remote unit warns when the telephone rings. Battery powered.
- INFRA RED INTRUDER ALARM.** Mar 80 £9.98 less cases.
Invisible infra red beam protects property - when the beam is broken the relay in the receiver is activated. Max. range 3 metres. Kit includes relay. Requires 9V supply.
- STEREO MIXER** Mar. 80 £12.73
Mixes high impedance dynamic mic and nurse inputs. Based on 4 LF351 ICs. Two dual pots form the controls for mic. and line. Sockets for inputs and outputs.
- CONSTANT CURRENT NI-CAD CHARGER.** Sept 80. £19.98
Charges up to 10 cells - suitable for all normal ni-cads. Continuously variable output current. Panel meter indicates the output current. Supplied with leads.
- BASIC SHORT WAVE RADIO** June 78 £18.95
3 band trf design covering 1.2 to 24 MHz. Features five front panel controls - wavechange, bandset, bandspread, reaction, and aerial attenuator. Built on a pcb. The frequency range covers all the HF broadcast and amateur bands.
- 3 BAND SHORT WAVE PRESELECTOR** Feb 79 £15.98
Uses a dual gate MOSFET. Tunes from 1.6 to 30 MHz in 3 bands. Adjustable rf gain control. Provides additional selectivity and sensitivity when used with a receiver.
- BEGINNERS MEDIUM WAVE RADIO** Aug. 79. £6.98
Provides crystal earpiece reception of the M.W. band. Crystal earpiece is supplied.
- TOP BAND FERRITE AERIAL UNIT** Sept 79 £8.98
An active tuned and amplified 160 metre band ferrite rod aerial unit. Provides directional reception facilities when used with a 160 metre receiver. Reduces interference and increases sensitivity.
- SINGLE CHIP M.W. RADIO** Sept 79 £11.37
Simple sensitive M.W. receiver with loudspeaker. Uses an LM389 IC for rf gain, af gain and power output. Ideal for beginners.
- SHORT WAVE AERIAL TUNING UNIT** Dec 79 £11.98
Improves receiver performance over 1.6MHz to 30MHz. Provides an increase in signal strength and rejection of strong interfering signals, spurious responses etc.
- SIMPLE SHORT WAVE SUPERHET.** Feb and Mar 80 £27.39
Covers 180 to 20 metres. No alignment problems. Very low battery current. Plug in coils. Uses a dual gate MOSFET as a mixer. Regenerative RIF stage allows reception of a.m., c.w., and s.s.b.
- 80 METRE AMATEUR BAND RECEIVER** July 80 £19.98
Expressly designed for ssb and cw amateur signals. This simple homodyne design provides world wide reception of amateur transmissions. Housed in a smart Vero case.
- PORTABLE SHORT WAVE RADIO** Aug 80. £18.94.
Suitable for beginners. Covers 25, 31, 41, and 49 metre bands. Fitted with telescopic aerial. Use of TBA820M amplifier IC provides loudspeaker output. Regenerative t.r.f. receiver. Smart ABS case.

LATEST KITS: S.A.E. OR 'PHONE FOR PRICES

MAGENTA ELECTRONICS LTD.

RC3, 98 CALAIS ROAD, BURTON-ON-TRENT,
STAFFS., DE13 0UL. 0283-65435. 9-12, 2-5 MON.-FRI.

MAIL ORDER ONLY

ADD 35p. P.&P. TO ALL ORDERS. ALL PRICES INCLUDE 15% V.A.T. OFFICIAL ORDERS FROM SCHOOLS ETC. WELCOME. ENQUIRIES MUST INCLUDE S.A.E. OVERSEAS: SEND ORDER WITH 3 INTERNATIONAL POSTAL COUPONS WE WILL QUOTE EXACT PRICE BY AIR MAIL.

EIRE & BFPO ORDERS
U.K. PRICES - LESS 10%
(COVERS V.A.T. REFUND & EXPORT DOCUMENTS) PAYMENT: STERLING U.K. BANK DRAFT, U.K. POSTAL ORDERS or U.K. CHEQUE.
ENQUIRIES: ENCLOSE 2 INTERNATIONAL POSTAL COUPONS.



80/81 ELECTRONICS CATALOGUE

**KITS
ICs
TRANSISTORS
CAPACITORS**

Hundreds of illustrations, product data, circuits and details of all our kits and educational courses. Up to date price list included. All products are stock lines for fast delivery by FIRST CLASS POST.
Send 6 x 10p stamps for your copy.

**TOOLS
RESISTORS
HARDWARE
CASES**

ADVENTURES WITH ELECTRONICS

by Tom Durcan

An easy to follow book suitable for all ages, ideal for beginners. No Soldering. Uses an 'S Dec' breadboard. Gives clear instructions with lots of pictures. 16 projects - including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec and the components for the projects.
Adventures With Electronics. £1.75.
Component Pack £16.72 less battery.

ADVENTURES WITH MICROELECTRONICS

Same style as above book; 11 projects based on integrated circuits - includes: dice, two-tone doorbell, electronic organ, MW/LW radio, reaction timer, etc. Component pack includes a Bimboard, 1 plug-in breadboard and the components for the projects.
Adventures with Microelectronics £2.35.
Component pack £27.95 less battery.

The INSTRUCTOR A FULLY CONSTRUCTIONAL PROJECT INCORPORATING AN INS8060 MICROPROCESSOR CHIP

- A Practical introduction to microprocessor functioning
- Relatively small number of components required
- An instructional

8 part series. Part 1 in Aug. 80 issue. Reprints of previously published part available. 45p each part.

The Instructor is a low cost assembly which provides a practical introduction to microprocessors and their functions. It is not a computer, but it is a working circuit which allows microprocessor working to be followed, one program step at a time. Build the Instructor and you will gain microprocessor experience. The series is based on the INS8060 microprocessor IC, also known as the SC/MP Mk.2. Circuits are built on a plug in Eurobreadboard. Kit is available with or without the breadboard.
INSTRUCTOR COMPONENT PACK: Including Eurobreadboard £27.85; or less Eurobreadboard £21.65.

HEADPHONES AND EARPIECES.

The short wave radios require a crystal earpiece or high impedance mono headphones.
MONO HEADPHONES £2.98.
High impedance 2k. Sensitive, Lightweight. Adjustable padded earpieces. Fitted with 3.5mm jack plug.
CRYSTAL EARPIECE 56p.
Fitted with lead and 3.5mm jack plug. Top quality.
STETHOSCOPE. 69p.
Optional attachment for use with our earpiece.

TOWERS INTERNATIONAL TRANSISTOR SELECTOR £10.35

- ANEX X25 SOLDERING IRON.** 25W. £4.98.
SOLDERING IRON STAND. £2.03.
SPARE BITS. Small, standard, large. 65p each.
SOLDER. Handy size. 95p.
EUROBREADBOARD. £6.20.
LOW COST LONG NOSE PLIERS. £1.68.
LOW COST CUTTERS. £1.69.
SIREN. 12V. £5.18
P.C.B. ASSEMBLY JIG. £11.98.
P.C.B. ETCHING KIT. £4.98.
MONO HEADPHONES. 2K Padded. Superior, sensitive. £2.98.
STEREO HEADPHONES. 8 ohm. Padded. £4.35.
- DESOLDERING BRAID.** 69p.
HOW TO SOLDER BOOKLET. 12p.
HEAT SINK TWEEZERS. 15p.
SOLDER BOBBIN. 30p.
DESOLDER PUMP. £5.98.
CONNECTING WIRE PACK. 5 x 5 yd coils. 55p.
VERO SPOT FACE CUTTER. £1.21.
VERO PIN INSERTION TOOL. 0.1". £1.66. 0.15" £1.67.
RESISTOR COLOUR CODE CALCULATOR. 21p.
MULTIMETER TYPE 1. 1,000 o.p.v. with probes. 2" x 3 1/2" x 1". £6.66.
MULTIMETER TYPE 2. 20,000 o.p.v. with probes. 5" x 3 1/2" x 1 1/2". £11.52.

MAGENTA gives you FAST DELIVERY BY FIRST-CLASS POST OF QUALITY COMPONENTS AND KITS. All products are stock lines and are new and full specification. We give personal service and quality products to all our customers - HAVE YOU TRIED US?

INTO ELECTRONICS CONSTRUCTION

R.E.C. LATEST KITS

- Tremelo modulation unit Nov 80 £11.27.
CMOS combination switch Nov 80 £7.22.
Coil coupled 5W converter Nov 80 £20.90.
- Go no go transistor tester Oct 80 £7.58.
Personal M.W. Radio, Oct 80. £10.36.

PRICES INCLUDE V.A.T.

MOTORS

1.5-6VDC Model Motors 22p. Sub. Min. 'Big Inch' 115VAC 3rpm Motors 32p. 6 volt standard cassette motors new £1.20. 8 track 12V Replacement Motors 55p. Ex. Equip. BSR record player motors, C129, C197 type, £1.20.

SEMICONDUCTORS

LM340 80p. BY103 10p. 2N5062 100V 800mA SCR 18p. BX504 Opto Isolator 25p. CA3130 95p. CA3020 45p. 741 22p. 7415 35p. 723 35p. NE555 24p. 2N3773 £1.70. NE556 50p. ZN414 75p. BD238 28p. BD438 28p. CB4069 15p. 4" Red Led Displays, c.c. or c.a. 95p. TL209 Red Leds 10 for 75p. Man3A 3mm Led Displays 40p. BY223 20p.

PROJECT BOXES

Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 65p. 95 x 71 x 35mm 75p. 115 x 95 x 37mm 85p.

MOTOROLA PIEZO CERAMIC TWEETERS
No crossover required



2.5" Direct Radiating Tweeter, maximum rating 25 volts R.M.S. 100 watts across 8 ohms. Freq. range 3.8kHz-28kHz, £3.65

TOOL SALE

Small side cutters 5" insulated handles £1. Radiopliers, snipe nosed insulated handles £1. Heavy duty pliers insulated handles £1.10. Draper side cutters spring loaded £1.

HANDY BENCH VICE
1" Jaw opening, £2.95.



Hand drill, double pinion with machine sut gears, 3/16", only £2.75p plus 50p p&p.

MORSE KEYS

Beginners practice key £1.05. All metal full adjustable type. £2.60

MINIATURE LEVEL METERS

1 Centre Zero 17 x 17mm 75p. 2 (scaled 0-10) 28 x 25mm 75p. 3 Grundig 40 x 27mm £1.25.

JVC NIVICO STEREO CASSETTE MECHANISM. Music centre type. Rev. counter, remote operation £13.50 and £1.00 p&p.

JUMPER TEST LEAD SETS

10 pairs of leads with various coloured croc clips each end (20 clips) 90p per set.

TRANSFORMERS

All 240VAC Primary (postage per transformer is shown after price). MINIATURE RANGE: 6-0-6V 100mA, 9-0-9V 75mA and 12-0-12V 50mA all 79p each (15p). 0-6, 0-6V, 280mA £1.20 (20p). 6V 500mA £1.20 (15p). 12V 2 amp £2.75 (45p). 15-0-15V 3 amp Transformer at £2.85 (54p). 30-0-30V 1 amp £2.85 (54p). 20-0-20V 2 amp £3.65 (54p). 0-12-15-20-24-30V 2 amp £4.75 (54p). 20V 2.5 amp £2.45 (54p).

TRIAC/XENON PULSE TRANSFORMERS

1:1 (gpo style) 30p. 1:1 plus 1 sub. min. pcb mounting type 60p each.

MICROPHONES

Min. tie pin. Omni, uses deaf aid battery (supplied), £4.95. ECM105 low cost condenser, Omni, 600 ohms, on/off switch, standard jack plug, £2.95. EM507 Condenser, uni, 600 ohms, 30-18kHz., highly polished metal body £7.92. DYNAMIC stick microphone dual imp., 600 ohms or 20K, 70-kHz., attractive black metal body £7.75. EM506 dual impedance condenser microphone 600 ohms or 50K, heavy chromed copper body, £12.95 CASSETTE replacement microphone with 2.5/3.5 plugs £1.35. INSERT Crystal replacement 35 x 10mm 40p. GRUNDIG electric inserts with FET pre-amp, 3-6VDC operation £1.00.

LIGHT DIMMER

240VAC 800 watts max. wall mounting, has built in photo cell for automatic switch on when dark £4.50

RIBBON CABLE

8 way single strand miniature 22p per metre.

SPECIAL OFFER TAPE HEAD DEMAGNETIZER



240VAC with curved probe suitable for reel to reel or cassette machines, £1.95.

STEREO FM/GRAM TUNER AMPLIFIER CHASSIS, VHF and AM. Bass, treble and volume controls, Gram. 8-track inputs, headphone output jack, 3 watts per channel with power supply. £14.95 and £1.20 p&p

MULTIMETER BARGAINS



Pocket Multimeter, 1,000 opv sensitivity. Ranges 1KV AC/DC Volts, 150ma DC current, resistance 0-2.5K, 0-100K, £4.50




20,000 opv., 1,000 volts AC/DC, DC current to 500ma, 5 ranges, resistance 4 ranges to 6 meg. Mirror scale, carrying handle, £975.

40kHz Transducers. Rec/Sender £3.50 pair.

TELEPHONE PICK UP COIL

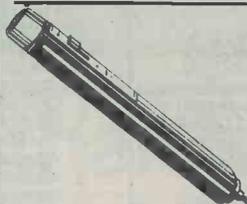Sucker type with lead and 3.5mm plug 62p.



ELECTRET CONDENSER FM

WIRELESS MICROPHONE TX Freq. adjustable between 88-108MHz, field strength 50 micro volt/15 metres, freq. response 50-16,000Hz, supplied with battery, £7.95

Dalo 33PC Etch Resist printed circuit maker pen, with spare tip, 79p.

TERMS:

Cash with order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive.

S.A.E. for illustrated lists



ME502 DIGITAL MULTIMETER

600VDC Max. 1,000VAC, 10 amps d.c., 2 meg., res., with transistor checking facilities, 90 x 171 x 30 m/m, £45.00.

YN360TR MULTIMETER



YN360 M/Meter. 20,000 ohms per volt. 1KV AC/DC volts, 250ma dc current, 4 resistance ranges to 20meg, also has built in transistor tester with leakage and gain ranges. £12.50

CRIMPING TOOL

Combination type for crimping red blue and yellow terminations also incorporates a wire stripper (6 gauges) and wire cutter, with insulated handles only £2.30.

POWER SUPPLIES

SWITCHED TYPE, plugs into 13 amp socket, has 3-4.5-6-7.5 and 9 volt DC out at either 100 or 40 0mA, switchable £3.45. HC244R STABILISED SUPPLY, 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £4.95.

AMPHENOL CONNECTORS

(PL259) PLUGS 47p. Chassis sockets 42p. Elbows PL259/SO239 90p. Double in line male connector (2XPL259) 65p. Plug reducers 13p. PL259 Dummy load, 52 ohms 1 watt with indicator bulb 95p.

BUZZERS

MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, voltage operating 4-15VDC, 75p each. LOUD 12VDC BUZZER, Cream plastic case, 50mm diam. x 30mm high 63p. Carters 12 volt Minimate Alarm sirens £7.65p. 12VDC siren, all metal rotary type, high pitched wail, £6.25.

TOOLS

SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.99 (spare nozzles 69p each).

All Antex irons still at pre increase prices, order now as new stock will be going up next month.

Antex Model C 15 watt soldering irons, 240VAC £3.95

Antex Model CX 17 watt soldering irons, 240VAC £3.95

Antex Model X25 25 watt soldering irons, 240VAC £3.95

ANTEX ST3 iron stands, suits all above models £1.85

Antex heat shunts 12p each.

Servisol Solder Mop 50p each.

Neon Tester Screwdrivers 8" long 59p each.

Miyarna IC test clips 16 pin £1.95

SWITCHES

Sub. miniature toggles: SPST (8 x 5 x 7mm) 42p.

DPDT (8 x 7 x 7mm) 55p.

DPDT centre off 12 x 11 x 9mm 77p. PUSH SWITCHES, 16mm x 6mm, red top, push to make 14p each, push to break version (black top) 16p each.

PACE Mobile SWR metre, with field strength, PL259 connection, £5.95.

RES. SUB BOX



Resistance Substitution Box. Swivelling disc provides close tolerance resistors of 36 values from 5 ohms to 1 meg. £3.95.



Signal Generator. Ranges 250Hz-100MHz in 6 Bands, 100MHz-300MHz (harmonics) internal modulator at 100Hz. R.F. output Max. 0.1vRMS. All transistorised unit with calibrating device. 220-240VAC operation, £48.95.

TAPE HEADS

Mono cassette £1.75. Stereo cassette £3.90.

Standard 8 track stereo £1.95 BSR MN1330 1/2 track 50p.

BSR SRP90 1/2 track £1.95. TD10 tape head assembly — 2 heads both 1/2 track R/P with built in erase, mounted on bracket £1.20

PROGRESSIVE RADIO


31 CHEAPSIDE, LIVERPOOL 2.

ALL ORDERS DESPATCHED BY RETURN POST

DIRECT SUPPLY SERVICE TO READERS

TOWERS INTERNATIONAL TRANSISTOR SELECTOR


(NEW REVISED EDITION)

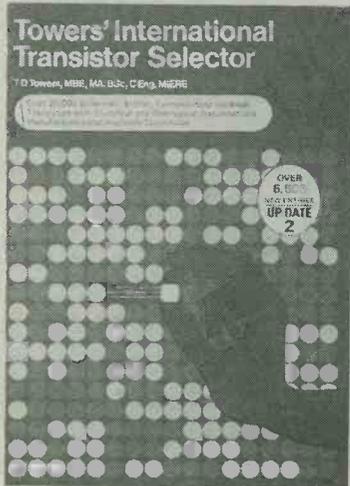

This is dead!



Would this replace it?

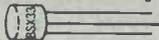


If it takes you longer than 1 minute to find out all about these transistors then you need a copy of TOWER'S INTERNATIONAL TRANSISTOR SELECTOR. It's one of the most useful working books you will be offered this year. And probably the cheapest! In it, you will find a really international selection of 13,000 transistor types — British, Continental European, American and Japanese. And we think that they will solve 90% of your transistor enquiries.

Current and widely used obsolete types were carefully selected and arranged in Numero-Alphabetical order by an author who was uniquely qualified to do the job. With his compendium, all you need to know is the type number and you can learn all about a transistor's specification; who made it and where to contact them; or what to use to replace it.

Price £10.35 inc P&P

TOWERS INTERNATIONAL FET SELECTOR

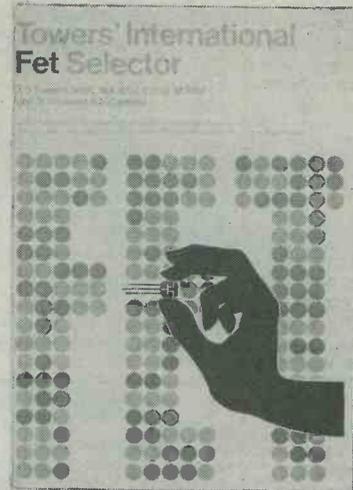

If you deal with field effect transistors, or fet's — whether as a student, a hobbyist, a circuit engineer, a buyer, a teacher or a serviceman — you often want data on a specific fet of which you know only the type number.

Specifications apart, you may be even more interested in where you can get the device in question. And perhaps more important still (particularly with obsolete devices), you may want guidance on a readily available possible substitute.

This fet compendium, a comprehensive tabulation of basic specification, offers information on:

1. Ratings
2. Characteristics
3. Case details
4. Terminal identifications
5. Applications use
6. Manufacturers
7. Substitution equivalents (both European and American)

The many fet's covered in this compendium are most of the more common current and widely-used obsolete types.

It is international in scope and covers fet's not only from the USA and Continental Europe, but also from the United Kingdom and the Far East (Japan).

Price £4.00 inc P&P

(Please allow 21 days for delivery)

Tower's International Transistor Selector by T. D. Towers MBE, MA, BSc, C Eng, MIERE
£10.35 inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies to the address shown below

NAME

ADDRESS

.
.
.

(Block capitals)

Tower's International FET Selector by T. D. TOWERS MBE, MA, BSc, C Eng, MIERE
£4.00 inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies to the address shown below

NAME

ADDRESS

.
.
.

(Block capitals)

SPECIAL CHRISTMAS OFFER

10% DISCOUNT ON ALL ORDERS RECEIVED BEFORE 9-1-81

NEW COMPONENTS

uA723 regulator 60p, uA748 op-amp 40p, LF351 55p, TDA2030 amplifier 180p, BC167, 8, 9, 11p, BC207, 8, 9, 15p, Capacitors 4.7uF 63V 10p, 10uF 16V 9p, Neons 240V 15 x 12mm lens, red or green 35p, round lens 13mm 35p, FULL RANGE OF TTL ICS AVAILABLE, Knobs, various types plastic and metal trims etc, prices from 14p to 50p, Metal and plastic boxes, e.g. Verobox 6" x 3 1/2" x 2 1/2" £3.10, 6" x 3 1/2" x 1 1/2" £2.25. Plastic box 4 1/2" x 3 1/2" x 1 1/2", £1.10. Metal two sections, vinyl covered top and sides, aluminium front and back, 8" x 5" x 2" £2.25, 6" x 4" x 1 1/2" £1.85, 6" x 3 1/2" x 3 1/2" £2.25.

Denco products available, Transistor tuning coils £1.40, MW. 5FR ferrite rod aerial £1.30, most other products available. Jackson Bros. variable capacitors C804 5, 10, 15, 20pF £3.35 each. Dilecon 100, 300pF £2.10, 500pF £2.10.

Many other components and accessories in stock. Please send 30p in stamps for our full lists.

SPECIAL OFFERS (Many half price!)

Transistor sockets T05, T018 6p each. Test probe clips (red or black) 18p. Professional phono single metal socket 13p. Vinyl insulated croc clip 5p. BIB accessories; anti static cleaner 20cc 20p. Cassette title labels 30p. Cassette index cards 15p. Stylus cleaner 22p. Empty library cassette 11p. Component packs; PU9 20 assorted tag strips 30p. PT13 4 off 10k mono slider pots 40p. PT14 10 assorted pots 40p. C60 cassettes, good quality 40p. Money refunded if any of the above special offers are sold out. Special Christmas discount not available on these items.

POSTAGE 30p
KITS 50p
VAT INCLUSIVE

T & J Electronic Components
98 Burrow Road, Chigwell Essex IG7 4HB

NO MINIMUM
ORDER
CHARGE

COMPONENT PACKS

UNTESTED

- PU1: 50 untested, unmarked t.t.l. i.c.s. 65p
PU2: Approx 200 mixed unmarked silicon diodes. 65p
PU4: Resistors, varied selection, approx 100. 65p
PU6: Assorted selection of ceramic, mica, polystyrene etc. Approx 100. 65p

TESTED

- PT1: Tested selection of popular diodes, contains 25 x 1N914, 10 x 1N4002, 5 x BY127 125p
PT3: Five 1/2W resistors of each value from 10 ohms to 1 megohm. 325p
PT16: Assorted selection of nuts, bolts, washers etc. Approx 100 pieces (count by weight) 65p

Many other packs in stock, details in list.

R & EC KITS


| | |
|---------------------------------|--------|
| GO/NOGO TRANSISTOR TESTER | £6.50 |
| 20dB AMPLIFIER (PART ONE) | £4.75 |
| PERSONAL MEDIUM WAVE RADIO | £5.75 |
| CONSTANT CURRENT NI-CAD CHARGER | £12.40 |
| 9 VOLT 1 AMP POWER SUPPLY | £8.80 |
| LABORATORY POWER SUPPLY | £12.80 |
| CAPACITANCE MEASURING ADAPTOR | £8.75 |
| DUAL POLARITY VOLTMETER | £9.60 |
| INFRA-RED INTRUDER ALARM | £6.10 |
| 80M AMATEUR BAND RECEIVER | £21.75 |
| LOGIC TESTER | £3.05 |
| RINGS OF LEDS PRINT TIMER | £7.80 |

The above is only a selection. Please note that some kits exclude certain items, full details on kits since January 1980 are available on receipt of an S.A.E. Please allow 14 days for delivery.

Faster than a scope safer than a voltmeter

See us on
STAND F1 at
LONDON BREADBOARD
EXHIBITION

LOGIC
MONITOR
LM-1

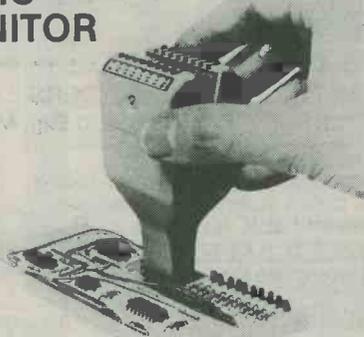

Instant — simultaneous monitoring of the logic state of all IC nodes

Just clip it over your IC

LM-1 Instantly and accurately shows both static and dynamic logic states on a bright 16 LED display.

LM-1 finds its own power.

LM-1 cuts out guesswork, saves time, and eliminates the risk of short circuits.

LM-1 is suitable for all dual-in-line logic ICs LED on = logic state 1 (high), LED off = logic state 0 (low), and each LED is clearly numbered 1 to 16 in the conventional IC pattern.

ONLY £28.70 (Excluding P&P and VAT)
Total £34.44 including box and instruction manual.

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited, Dept. 16S3
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21682
Telex: 817477

C.S.C. (UK) Limited, Dept. 16S3, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.
LM-1 £34.44 (incl. P&P and 15% VAT) Qty. Req'd. For FREE Catalogue tick box

Name Address

I enclose PO/cheque for £..... or debit my
Barclaycard, Access, American Express No.
exp. date

FOR IMMEDIATE ACTION — The C.S.C. 24 hour, 5 day a week service, Telephone: (0799) 21682. and give us your Barclaycard, Access, American Express number and your order will be in the post immediately.

TRANSISTORS

| | | | | | |
|----------------------|-------|----------------------|-------|-----------------------------|-------|
| BD238 | 25p | MJE2371 | 80p | 2N2401 | 71p |
| BD239C | 25p | MJE2901T (Higain) | 25p | 2N2412 | 27p |
| BD240 | 30p | 2955 | 50p | 2N2483 | 28p |
| BD242 | 30p | MJE2955 70v 90w | 50p | 2N2484 | 10p |
| BD242B 90v 40w | 30p | | | 2N2586 | 15p |
| BD246 | 32p | M 15 Russian 25p | 25p | 2N2614 | 4p |
| BD253 | 44p | M 41 Russian 25p | 25p | 2N2887 | 4p |
| BD375 | 35p | MPF131 Dual | 15p | 2N2894 | 11p |
| BD437 | 35p | MOSFET | 15p | 2N2904 | 9p |
| BD438 | 28p | MPU131 Prog. Uni. J. | 15p | 2N2905 | 15p |
| BD597 60v 55w | 36p | | | 2N2906 | 9p |
| BD677 60v 40w | 50p | MRF502 Improved | 15p | 2N2907A | 9p |
| BD678 Pwr. Darl. 50p | 50p | BFY90 | 50p | 2N2926 | 4p |
| BDX33B Pwr Darl 44p | 44p | 16A Russian | 25p | 2N3020 | 25p |
| | | 42A Russian | 25p | 2N3053 | 16p |
| BDX42 60v. Darl. 36p | 36p | NKT A49 | 23p | 2N3055RCA | 35p |
| BDX77 | 50p | NKT B54 | 20p | 2N3133 | 24p |
| BDY20 | 86p | NKT B54 | 20p | 2N3283 | 25p |
| BF115 | 18p | NKT152 | 38p | 2N3418 | 15p |
| BF137 | 11p | NKT153 | 24p | 2N3553 | 56p |
| BF167 | 18p | NKT251 | 26p | 2N3583 | 18p |
| BF173 | 18p | NKT775 | 16p | 2N3645 | 3p |
| BF178 | 23p | NKT775 | 16p | 2N3703 | 3p |
| BF179 | 23p | NKT775 | 16p | 2N3704 | 4p |
| BF180 | 12p | OC41 | 4p | 2N3707 | 3p |
| BF181 | 8p | OC42 | 21p | 2N3711 | 3p |
| BF182 | 18p | OC43 | 55p | 2N3714 80v 150w | 54p |
| BF183 | 18p | OC44 | 4p | 2N3794 | 18p |
| BF184 | 18p | OC45 | 13p | 2N3799 | 18p |
| BF185 | 18p | OC71 | 13p | 2N3823 FET | 25p |
| BF194/A | 5p | OC72 (XK120) | 4p | 2N3906 | 8p |
| BF195/C/D | 5p | OC76 | 15p | 2N4000 | 15p |
| BF196 | 5p | OC77 | 46p | 2N4026 | 15p |
| BF197 | 5p | OC81 (XK122) | 4p | 2N4031 | 15p |
| BF198 | 5p | OC84 | 30p | 2N4062 | 17p |
| BF200 | 13p | OC200 | 41p | 2N4235 | 30p |
| BF224 | 4p | OC201 | 66p | 2N4891 | 30p |
| BF244C FET | 7p | OC202 | 66p | 2N4918 | 15p |
| BF245 | 6p | OC603 | 50p | 2N5058 (BF259) | 11p |
| BF256FET | 4p | OC701 | 50p | 2N5147 | 15p |
| BF256LB/LC FET | 3p | ON222 | 23p | 2N5293 80v 36w | 30p |
| BF257 | 20p | P346A | 24p | 2N5294 80v 36w | 30p |
| BF262 | 29p | P7029 | 30p | 2N5295 60v 36w | 30p |
| BF263 | 29p | PXB103 | 25p | 2N5296 60v 36w | 30p |
| BF274 | 8p | RCP701A/B/D | 10wT | 2N5297 80v 36w | 36p |
| BF324 | 31p | R1039 (2010) | 54p | 2N5449 | 3p |
| BF336 | 16p | R2008B | £1.18 | 2N5484 | 37p |
| BF355 | 15p | R2010B | £1.18 | 2N5492 75v 50w | 36p |
| BF394B | 6p | R2306 100v 40w | 26p | 2N5494 60v 50w | 36p |
| BF451 | 10p | R2540 | £1.70 | 2N5915 (16068) | 45p |
| BF494 | 10p | S3017 | 25p | 450Mhz 6WT R.F. 12v | £2.50 |
| BF495 | 5p | S3017 | 25p | 2N5954 P, 80v, 40w | 36p |
| BF595c FM/AM/9p | 9p | S8240 | 26p | 2N6028 PUJT | 3p |
| BF615 | 27p | SFT357 | 28p | 2N6101 80v 75w | 55p |
| BF617 | 27p | SJE5039 | 8p | 2N6106 80v 40w | 44p |
| BFQ35 | 15p | SL102 | 40p | 2N6109 60v 40w | 44p |
| BFQ37 | 15p | TE886 | £1 | 2N6111 40v 40w | 36p |
| BFQ85 | 15p | TIP29 40v 30w | 22p | 2N61124 | 24p |
| BFR34A | 36p | TIP30 | 22p | 2N6178 100v 25w | 30p |
| BFR38 | 68p | TIP30C 100v 30w | 26p | 2N6181 75v 25w | 30p |
| BFR86 | 19p | TIP31C 100v 40w 26p | 26p | 2N6181 75v 25w | 30p |
| BFS21 FET pair | £3 | TIP32A 100v 40w | 22p | 2N6254 | 36p |
| BFS28 Dual MUS | 50p | TIP32C 100v 40w | 22p | 2N6298 30v 40w | 36p |
| BFT30 | 15p | TIP41 40v 65w | 15p | 2N6390 60v 40w | 30p |
| BFT31 | 15p | TIP42C 100v 65w | 15p | 2N6292 80v 40w | 30p |
| BFT38 | 15p | TIP48 | 33p | 2N6385 Pwr. Darl. 54p | 54p |
| BFT41 | 15p | TIP112 100v 50w 45p | 45p | 2N6486 40v 75w | 36p |
| BFT60 | 6p | TIP117 (Pwr. Darl.) | 45p | 2N6488 90v 75w | 36p |
| BFT61 | 15p | TIS44 VHF switch | 9p | 2S701 | 18p |
| BFT70 | 15p | TIS60GY | 9p | 2SA12 | 42p |
| BFT71 | 15p | TIS61 | 3p | 2SA20 | 36p |
| BFW10 FET | 46p | TIS61 | 3p | 2SA83 | 36p |
| BFW11 FET | 46p | TIS73L | 3p | 2SA142 | 36p |
| BFW30 | 15p | TIS90 | 3p | 2SA142 | 36p |
| BFW31 | 15p | TIS91 UN1 Junc. | 3p | 2SA234 | 50p |
| BFW37 | 18p | TIS92GY | 14p | 2SA235 | 50p |
| BFW58 | 18p | TIS98 | 3p | 2SA354 | 38p |
| BFX12 | 23p | TK24 | 20p | 2SA360 | 34p |
| BFX29 | 11p | V435 | 20p | 2SA367 | 56p |
| BFX30 | 16p | U14710 | 20p | 2SA518 | 38p |
| BFX37 | 20p | ZT403P | 30p | 2SA634 | 80p |
| BFX84 | 20p | ZT1486 | £1.10 | 2SB75 | 25p |
| BFX85 | 14p | ZTX300 | 9p | 2SB77 | 25p |
| BFX88 | 20p | ZTX327 | 18p | 2SB135 | 25p |
| BFY89 | 20p | ZTX341 | 9p | 2SB136 | 25p |
| BFY39 | 15p | 2G103 | 33p | 2SB156 | 60p |
| BFY50 | 15p | 2G302 | 12p | 2SB175 | 20p |
| BFY51 | 15p | 2G309 | 20p | 2SB176 | 20p |
| BFY52 | 15p | 2G339A | 20p | 2SB187 | 25p |
| BFY90 | 40p | 2G371 | 18p | 2SB457 | 25p |
| BLY10 | 23p | 2N456A | 71p | 2SC1061 50v 25w | 50p |
| BR101 } Prog. 20p | 20p | 2N456A | 71p | 2SD234 60v 25w | 50p |
| BR101 } Uni. 29p | 29p | 2N456A | 71p | 2SD315D | 80p |
| BR101 } Junct. 29p | 29p | 2N456A | 71p | 16120 (MPSU55/BD238) | 19p |
| BSV64 | 36p | 2N597 | 16p | 40235 | 19p |
| BSV79 | 50p | 2N598 | 16p | 40250 | 36p |
| BSV80 | 50p | 2N601 | £1.50 | 40250VI (2N3054 + Ht. sink) | 40p |
| BSV81 | 50p | 2N644 | 22p | 40316 40v, 50w | 36p |
| BSX19 | 15p | 2N706A | 101p | 40372 (2N3054 + Ht. sink) | 40p |
| BSX20 VHF Osc. | 7p | 2N708 | 9p | 40349v2 160v 1w | 30p |
| BSX21 | 10p | 2N708 | 9p | 40394 60v 1w | 30p |
| BSX78 | 8p | 2N914 | 15p | 40602 VHF Mosfet | 36p |
| BSY40 | 30p | 2N918 | 12p | 40633 NPN 40w | 36p |
| BSY95A | 10p | 2N929 | 16p | 40911 (2N6261 + Ht. sink) | 40p |
| BU105 | 64p | 2N984 | 28p | | |
| BU105/04 | 78p | 2N987 | 45p | | |
| BU204 | 50p | 2N1091 | 16p | | |
| BU208 | 90p | 2N1132 | 14p | | |
| BUX 66P, 150v, 54p | 54p | 2N1302 | 16p | | |
| D45C2 40v 30w | 30w | 2N1303 | 16p | | |
| 220HF 50MHz | 50p | 2N1395 | 25p | | |
| D1693 | £2.85 | 2N1484 | 36p | | |
| GET102 | 46p | 2N1485 60v 25w | 36p | | |
| GET111 | 45p | 2N1487 | 30p | | |
| GET120 | 30p | 2N1490 | £3 | | |
| M103G MOSFET | 30p | 2N1500 | 30p | | |
| MA393 | 25p | 2N1507 | 18p | | |
| MD7000 | £2.25 | 2N1711 | 13p | | |
| ME2 | 13p | 2N1716 | 13p | | |
| ME0412 | 14p | 2N1748 | 28p | | |
| ME8003 | 20p | 2N192A | 15p | | |
| MJ481 (BDY23) | 23p | 2N2221/A | 9p | | |
| MJE371 | 40p | 2N2222A | 8p | | |
| | | 2N2369 | 10p | | |

1% OR 2% TOLERANCE RESISTORS

UP TO 1WATT 11p
 15, 17, 32, 22, 27, 47, 56, 68, 70, 75, 91, 100, 120, 140, 143, 144.4, 150, 213.4, 220, 250, 270, 330, 390, 470, 590, 600, 634, 680, 820, 850, 1K, 1K2, 1K5, 1K6, 1K8, 2K, 2K2, 2K4, 2K6, 2K7, 3K, 3K3, 3K6, 3K9, 4K7, 5K1, 5K6, 6K8, 7K5, 8K2, 10K, 10K8, 12K, 13K, 15K, 16K, 22K, 23K, 24K, 28K5, 33K, 36K, 39K, 43K, 47K, 56K, 62K, 68K, 72K, 75K, 78K, 82K, 98K, 100K, 120K, 150K, 160K, 180K, 220K, 298K, 330K, 390K, 430K, 470K, 560K, 680K, 800K, 820K, 950K, 1M5.

1 WATT 2p
 15, 68, 70.5, 111, 120, 130, 150, 220, 287, 295, 510, 600, 910, 1K, 1K5, 1K6, 1K8, 2K, 2K2, 2K4, 2K6, 2K7, 3K, 3K3, 3K6, 3K9, 4K7, 5K1, 5K6, 6K8, 7K5, 8K2, 10K, 10K8, 12K, 13K, 15K, 16K, 22K, 23K, 24K, 28K5, 33K, 36K, 39K, 43K, 47K, 56K, 62K, 68K, 72K, 75K, 78K, 82K, 91K, 100K, 110K, 120K, 130K, 150K, 150K, 220K, 240K, 270K, 280K, 300K, 350K, 360K, 390K, 400K, 430K, 470K, 500K, 560K, 620K, 680K, 820K, 850K, 1M, 1M2, 1M5, 2M, 3M, 3M9.

2 WATT 10p
 25, 120, 150, 750, 1K3, 1K5, 2K, 2K4, 3K3, 3K6, 4K7, 5K6, 6K8, 9K1, 10K, 13K, 15K, 16K, 22K, 24K, 33K, 36K, 43K, 47K, 56K, 62K, 68K, 75K, 82K, 91K, 93K7, 100K, 110K, 120K, 130K, 150K, 180K, 220K, 230K, 280K, 330K, 360K, 430K, 470K, 560K, 570K, 680K, 820K, 937K, 4M7, 20M2.

PRECISION 0.1% 1WATT 30p
 1K8, 15K

1% AND 2% WIRE WOUND RESISTORS
 0.025Ω 25watt 96p; 0.1Ω 2 or 5watt 5p; 0.2Ω 5watt 5p; 0.3Ω 25watt 29p; 1, 5watt 10p; 1.075, 5watt 7p; 1.1watt 7p; 1.5, 20watt 96p; 40, 50watt £1.80; 75, 5watt 30p; 95, 5watt 30p; 110, 25watt 96p; 150, 5watt 30p; 300, 5watt 30p; 1K5, 3watt 30p; 27K, 5watt 30p; 100K 9watt 30p; 1M 5watt 5p; 3M9 3watt 30p.

TRIMMER CAPACITORS

- 1 to 60pF tubular 11p
- 2 to 60pF tubular 25p
- 3 to 13pF vane 18p
- 2 to 18pF vane 18p
- 3 to 25pF tubular 25p
- 3 to 30pF beehive 10p
- 3 to 30pF post stamp 10p
- 4 to 40pF tubular 25p
- 5 to 50pF vane 18p
- 6 to 65pF vane 40p
- 8 to 100pF ceramic 30p
- 8 to 115pF ceramic 30p
- 12 to 140pF post stamp 23p
- 1250pF post stamp 35p
- 2000pF post stamp 35p
- 2500pF Hi-volt comp. 35p

MULTIPLE POST STAMP TYPES
 50 + 50 + 50 + 50PF. 35p 1000 + 300PF 35p.
 50 + 50 + 50PF 35p 60 + 60 + 120PF 35p

EGA PLASTIC BOX

Black, 4 corner screws hold lid, 4" x 2 1/2" x 1 1/4" 48p.

NYLON WALL PLUGS.

Expandite fisher, take size 6 to 10 screw 10 for 15p

5 AMP 2 PIN PLUGTOP 19p

White, continental manufacture, but fits British

HUGHES MICRO ELECTRONICS 400MW ZENER DIODES 200 IN CLEAR PLASTIC HINGED LID COMPONENT BOX £2.30
 3V, 3.6V, 3.9V, 4.3V, 4.7V, 11V or 13V

END OF LINE STOCK ITEMS AND COMPUTER & AUDIO BOARDS/ASSEMBLIES WITH VARYING CONTENTS INCLUDE ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOSTS, POT CORES, CHOKES, INTEGRATED CIRCUITS, ETC.
 31b for £2.30 71b for £4.30

MARKED FULL SPEC DIGITAL I.C.'s
 Branded - New 25 for £1 Mixed

7 MILLION CARBON FILM RESISTORS PURCHASED

1/4 - 1/3 - 1/2 - 2/3 - 1 - 1 1/2Wt. Iskra and Pihor, mainly 5%, few 2%. Lucky Dip as the packs come (will not duplicate under 20 packs) due to cartons packed tight and on top of each other in ceiling of warehouse.

PACK OF 100 FOR 25p

PAY A VISIT - THOUSANDS MORE ITEMS BELOW WHOLESALE PRICE. CALLERS PAY LESS ON MANY ITEMS AS PRICES INCLUDE POSTAGE. PRICES INCLUDE VAT AND ADDITIONAL DISCOUNT IN LIEU OF GUARANTEE. GOODS SENT AT CUSTOMERS' RISKS UNLESS SUFFICIENT ADDED FOR REGISTRATION OR COMPENSATION FEE POST.

TRADE COMPONENTS CATALOGUE
 5300 ITEMS AT PRICES YOU WOULD NOT BELIEVE BEFORE INFLATION. YOUR MONEY MUST GO TWICE AS FAR. 75p PLUS 30p POST.

BRIAN J. REED
 ESTABLISHED 23 YEARS
 161 ST. JOHNS HILL, BATTERSEA, LONDON SW11 1TQ
 Open 11 a.m. till 7 p.m. Tues. to Sat. Telephone 01-223 5016
 Terms: Payment with order only. VAT receipts included with goods

PRICES SO LOW, THE POLICE INVESTIGATED ME TWICE

ALL ENQUIRIES, ETC. MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE

VAT & POST PAID

(2nd Class or Parcel)
MINIMUM ORDER £3 (excluding catalogue) OTHERWISE ADD 50% FOR SMALL ORDER HANDLING COSTS (UNDER £1.00 TOTAL ALSO INCLUDE 12p S.A.E.)

UK - Postal Orders for same day service. Cheques require 8 days from a Monday banking to ensure clearance. Export banker's draft (sterling) same day service. Foreign currency not accepted. VAT content becomes documentation charge.

OPTO ELECTRONICS
Photo Diodes: BPX40, BPX42, BPY10, CQY77, CQY17, BPY68, BPY69, BPY77 36p.
Wire end neons 4p.
Photo transistors: BPX43, BP103, 2N5777 Darlington. 36p. OCP71 40p. LED's (Mullard Seimens) Red .2" 8p, .125" 9p; Green .2" 11p; .125" 12p; Micro Yellow LD481 7p.
PHOTO SILICON CONTROLLED SWITCH BPX66 PNP 10 amp 36p
CA3062 Photo Detector and power amp. £1

7 SEGMENT L.E.D. DISPLAYS
.3" Red com. anode 81p
.6" Green R.S.C.A. £1.77
5082-7650 Red com. anode
5082-7653 Red com. cath
5082-7600 Yellow com. anode
H.P. Highbrilliance .43" 72p

HEWLETT PACKARD MULTIPLEXED .12" 7 SEGMENT LED DISPLAYS
3 Digit HP 5082 7413 45p
4 Digit HP 5082 7414 45p
5 Digit HP 5082 7415 45p
Infra red transmit diodes CQY11B or LD27 High power 1.6-2v or 3-3.5v Pulse 32p LD242 36p
H15B Photon coupled isolator I.R. diode and NPN Photo-Darlington amp 26p
CNY17/1 opto coupler 70p
Cold cathode tubes I.T.T. G517A or 5870L 60p

SPECIAL OFFER
IN4004 or IN4006. Sealed manufacturers carton of 300.
£6.75

NON POLAR CAPACITORS 1MF LD UP. PAPER BLOCK
1/250v 70p, 1/1000v £1.
2/200v, 2/250v 80p.
2/500v £1., 7.5/275vac £1.60p.
2+2/200v £1.
0.5+0.5+1+1/350vac £1.50
PAPERCAN
1/350v 12p, 1/450v 50p.
3/500vac 75p, 3/660vac £1.29.
4/200vac £1.10p.
5/150v 60p, 6/450vac 98p.
10/150v £1.50p.
25/440vac £1.85p.
130/125vac £3.25.
CERAMIC
1/50v 8p.
1%-2% HI STAB POLY
1/100v 30p, 5/100v 30p.
TANTELUM
1.1/20v 14p, 1.5/12v/30v 30p, 3.3/6v 30p, 20/120v 12p, 23/6v 12p, 40/15v 12p.
POLY 71p.
0.97/160v 71p.
1/100v/160v/200v/250v 10p, 1/400v 11p, 1/1000v 36p.
1.5/100v 9p.
1.5/250v 22p, 1.5/400v 40p, 2.2/50v/100v 14p, 2.2/250v 20p, 2.2/400v 50p, 3.3/100v 17p, 4/16v 25p, 4.7/63v 16p, 4.7/100v 17p, 4.7/250v 60p, 6.8/63v 19p, 6.8/250v £1.35, 8/20 40p, 10/100v 30p, 10/160v £1.50p, 10/200v 50p, 10/250v £1.90p, 25/50v 19p, 50/12v 50p, 50/25v 80p, 100/6v 50p.

Nickel Cadmium 'D' cell (HP2). Superior vented double insulated 4 1/2 A.H. (1.25v) rechargeable battery. Made by G.E. Ex unused equipment £1.41p.

DIODES

| | | | |
|----------------------|-----|------------------------------|-----|
| AA119 | 7p | MPN3401 | 30p |
| AA133 | 9p | OA5 | 25p |
| AAZ15 | 15p | OA7 | 25p |
| B1 | 11p | OA10 | 25p |
| BA116 | 30p | OA47 | 7p |
| BA128 | 21p | OA70 | 10p |
| BA145 | 21p | OA75 | 11p |
| BA148 | 12p | OA79 | 11p |
| BA182 Varicap | 6p | OA81 | 34p |
| BAX14 | 21p | OA95 | 8p |
| BAX54 | 8p | OA200 | 21p |
| BAY36P | 21p | OA202 | 21p |
| BB103 Varicap | 8p | IGP7 | 11p |
| BB104 Varicap | 16p | IGP10 | 11p |
| BB109 Varicap | 24p | IN662 | 21p |
| BB110B Varicap | 24p | IN914 | 11p |
| BB113 Triple Varicap | 43p | IN916 | 21p |
| | £1 | IN935B | 71p |
| BB139 | 15p | IN937B | 71p |
| BR100 diac | 71p | IN941B | 71p |
| BY206 | 23p | IN942B | 71p |
| BY207 | 21p | IN943B | 71p |
| BY403 | 21p | IN3064 | 21p |
| Centercell | 3p | IN4009 | 21p |
| CG651 | 9p | IN4148 | 1p |
| CRHG3 | 10p | IN4150 | 21p |
| CSD117YLZ | 40p | IN4151 | 21p |
| CV7095 | 21p | IN4446 | 21p |
| CV7098 | 21p | IN4449 | 21p |
| D3202Y Diac. | 11p | IN5456 | 15p |
| DC2845 Microwave | 20p | 5082 2900 RF Schotky Barrier | 20p |
| DOG53 | 11p | | |
| FSY28A | 40p | | |
| HG1012 | 10p | | |
| HS2091 | 11p | | |

RECTIFIERS

| Type | Volt | Amp | Price |
|-------------|------|-------|-------|
| BY127 | 1250 | | 4p |
| BY212 | EHT | | 6p |
| BY235 | 600 | 1 1/2 | 71p |
| BY236 | 900 | 1 1/2 | 71p |
| BY264 | 300 | 3 | 9p |
| BY265 | 600 | 3 | 11p |
| BY266 | 900 | 3 | 15p |
| BY274 | 300 | 5 | 14p |
| BY275 | 600 | 5 | 17p |
| BY277 | 1200 | 5 | 27p |
| BY299 | 800 | 2 | 4p |
| BY1202 | 2kV | 10mA | 6p |
| BYX20-200 | 200 | 25 | 72p |
| BYX22-200 | 300 | 1 1/2 | 25p |
| BYX38-300R | 300 | 2 1/2 | 48p |
| BYX38-600 | 600 | 2 1/2 | 52p |
| BYX38-900 | 900 | 2 1/2 | 60p |
| BYX38-1200 | 1200 | 2 1/2 | 65p |
| BYX42-300 | 300 | 10 | 36p |
| BYX42-600 | 600 | 10 | 46p |
| BYX42-900 | 900 | 10 | 92p |
| BYX42-1200 | 1200 | 10 | £1.07 |
| BYX46-300R | 300 | 15 | £1.19 |
| BYX46-400R | 400 | 15 | £1.75 |
| BYX46-500R | 500 | 15 | £2.00 |
| BYX46-600 | 600 | 15 | £2.30 |
| BYX48-300R | 300 | 6 | 47p |
| BYX48-600 | 600 | 6 | 60p |
| BYX48-900 | 900 | 6 | 70p |
| BYX48-1200R | 1200 | 6 | 92p |
| BYX49-300R | 300 | 3 | 35p |
| BYX49-600 | 600 | 3 | 42p |
| BYX49-900R | 900 | 3 | 47p |
| BYX49-1200 | 1200 | 3 | 60p |
| BYX52-300 | 300 | 40 | £2.05 |
| BYX52-1200 | 1200 | 40 | £2.90 |
| BYX72-150R | 150 | 10 | 42p |
| BYX72-300R | 300 | 10 | 52p |
| BYX72-500R | 500 | 10 | 65p |
| BYX94 | 1250 | 1 | 6p |
| E250C50 | 250 | 1 | 14p |
| KS11394 | 800 | 3 | 23p |
| LT102 | 30 | 2 | 15p |
| M1 | 68 | 1 | 5p |
| MR856 | 600 | 3 | 24p |
| OA210 | 400 | 5 | 33p |
| RAS3 10AF | 1250 | 1 1/2 | 48p |
| REC53A | 1250 | 1 1/2 | 16p |
| S10BR30 | 1000 | 30 | £2.00 |
| SKE4G | 200 | 6 | 30p |
| SR100 | 100 | 1 | 9p |
| SR400 | 400 | 1 1/2 | 10p |
| IN3254 | 400 | 1 | 4p |
| IN4002 | 100 | 1 | 3p |
| IN4004 | 100 | 1 | 4p |
| IN4005 | 600 | 1 | 6p |
| IN4006 | 800 | 1 | 6p |
| IN4007 | 1250 | 1 | 6p |
| IN5059 | 200 | 1 1/2 | 10p |
| IN5401 | 100 | 3 | 10p |
| IS138 | 800 | 4 | 21p |
| IS921 | 100 | 1 | 8p |
| 25G100 | 100 | 60 | £4.35 |
| 3052 | 200 | 3 | 11p |
| 16094P | 900 | 3 | 15p |
| 16492 | 700 | 1 1/2 | 9p |

2N2082 40v 15A 170wt PNP Germanium H.F.E. 70 Ex unused equipment 22 1/2p

BRIDGE RECTIFIERS

| | | |
|----------------------|-----------------|---------|
| 60V | BC30 C350 | 23p |
| 1,600 | BYX10 | 34p |
| 110 | EC433 | 20p |
| 50V | WO05 | 19p |
| 140 | OSH01-200 | 25p |
| 200V | WO2 Ex Equip | 15p |
| 400V | WO4 | 28p |
| 400V | MDA104 | 29p |
| 800V | WO8 | 27p |
| 1000 | W10 | 36p |
| 75V | IBIBY234 | 11 1/2p |
| 150V | IBIBY235 | 15p |
| 100 | I.R. | 40p |
| 350V | 9F2 | 70p |
| 500V | 9E4 | 85p |
| 50 | KBS005 | 30p |
| 100 | KBS01 | 30p |
| 200 | KBS02 | 30p |
| 400 | KBS04 | 30p |
| 600 | KBS06 | 30p |
| 100 | B40C 3200 Texas | 58p |
| 400 | | 85p |
| Miniature Meter Type | | 34p |

Thyristors

| Amp | Volt | Model | Price |
|--------|------|---------------------------|-----------|
| 0.8 | 200 | 2N5064 | 18p |
| 1 | 240 | BTX18-200 | 35p |
| 1 | 240 | BTX30-200 | 35p |
| 1 | 400 | BTX18-300 | 41p |
| 2 | 400 | S2710D with heatsink | 40p |
| 3 | 600 | T3N06C00 | 53p |
| 3 | 100 | T3N1C00 | 36p |
| 4 | 50 | S107F Sensitive Gate | 36p |
| 4 | 50 | S2060F Sensitive gate | 36p |
| 4 | 400 | S2061D Sensitive gate | 38p |
| 4 | 500 | 40506 with heatsink | 58p |
| 4 | 600 | C106M sensitive gate | 36p |
| 4 | 600 | 2N3228 | 36p |
| 5 | 400 | S3700D | 44p |
| 5 | 600 | S5800M | 44p |
| 6.5 | 500 | BT109/SCR957 | 71p |
| 7 | 400 | S2620D | 45p |
| 7 | 600 | S2620M | 45p |
| 8 | 100 | S2800A | 36p |
| 8 | 600 | S122M | 54p |
| 12 | 1000 | CR121103-RB | £8 |
| 15 | 800 | BTX95-800 Pulse Modulated | £1.40 |
| 20 | 600 | BTW92-600RM | £3.40 |
| 75 | 800 | 71C680 | £6 |
| 110 | 20 | 72RC2A | £3 |
| 150 | 1000 | 151RA100 | £10 |
| 150 | 1200 | 151RA120 | £11 |
| BT 106 | | 70p | |
| BT 121 | | 70p | BT 107 £1 |

TRIACS

| Amp | Volt | Model | Price |
|-----|------|--------------|-------|
| 0.1 | 40 | 7W84 | 3p |
| 2.5 | 600 | 2N5757 | 44p |
| 4 | 400 | T2716D/40730 | 74p |
| 6 | 200 | T2500B/41014 | 54p |
| 6 | 400 | T2500D | 72p |
| 8 | 400 | T2850D | 72p |
| 8 | 500 | BT137-500 | 72p |
| 12 | 500 | BT138-500 | 90p |
| 25 | 100 | BTX94-100 | £2.25 |
| 25 | 1200 | BTX94-1200 | £5 |

ZENER DIODES
4/500MW. BZY88, BZX97, etc. 5p
2v. 2v7. 3v. 3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 9v1. 10v. 11v. 12v. 13v. 13v5. 15v. 18v. 20v. 22v. 24v. 27v. 30v. 33v. 43v.
BZY61 Laboratory Standard 400MW 7v5. Voltage Regulator Diode 12p
1.3/1.5WT BZX61, BZY97, etc. 11p
2v4. 2v7. 3v. 3v6. 3v9. 4v3. 4v7. 5v6. 6v2. 6v8. 8v2. 10v. 11v. 12v. 15v. 18v. 27v. 33v.
2.5WT BZX70, etc. 13p
v75. 1v. 2v4. 3v6. 3v9. 5v6. 6v2. 7v. 7v5. 8v. 9v. 10v. 11v. 14v. 15v. (8p). 20v. 22v. 24v. 26v.
5WT BZV40, etc. 15p
3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 8v7. 9v1. 10v. 11v. 12v. 15v. 33v. 68v. 120v.
10WT Z5D, ZX, etc. 20p
4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 11v. 12v. 13v. 16v. 18v. 21v. 22v. 33v. 36v. 39v. 68v. 150v.
15WT BZV15C12R 12volt 37p
20WT BZY93, etc. 44p
8v2. 12v. 39v.

MULTIPLE ELECTROLYTIC CAPACITORS
4+4/250v 30p; 8+8/350-375v 17p, 450v 9p or 19p; 8+16/350v 44p, 450v 50p; 8+32/350v 50p; 16+16/275v 44p, 300v 47p, 350v 55p; 16+32/275v 46p, 350v 60p; 20+20/450v 70p; 25+25/300v 57p, 400v 65p; 32+32/275v 19p, 350v 50p; 50+50/150v 40p, 385v 75p; 60+100/275v 70p, 300v 75p, 450v 95p; 60+250/275v 75p; 100+100/150v 50p, 275v 65p, 500+500/25v 60p; 750+750/15v 60p; 1000+1000/15v 45p, 30v 65p; 1000+2000/35v 35p, 2000+2000/50v 42p; 2500+2500/18v 60p, 30v 80p, 16+25+32/275v 50p; 20+20+20/350v 80p; 32+32+50/300v 80p; 100+32+32/300v 70p; 100+200+32/300v £1.20; 100+200+60/300v £1.20; 330+220+47/250v 33p, 50+50+50+50/55v 85p; 100+300+100+16/300v 85p, 300+300+100+32+32/300v 62p.

BRIAN J. REED


SEE PRECEDING PAGES FOR ORDERING INSTRUCTIONS
Cut out and keep these 3 pages. Over the months they will bring to you some of the 6,000 items stocked.

INTEGRATED CIRCUITS

| | | | |
|-------------------------------|--------|-------------------------------------|--------|
| 371AJ RF/IF Amp | 4p | 74298 | £1 |
| 542 Servo Amp | 18p | 74490 | £1.30 |
| 702 CL | 25p | 7905 - 5v Reg. 1 Amp | £4p |
| 709/72709 OP Amp. | 18p | 8080A C.P.U. | £3.60 |
| 723 Variable Volt Regulator | 36p | 82S129 | £5 |
| 710 | 28p | 9093DC | 4p |
| 724 | 20p | 9112DC | 4p |
| 741 OP Amp | 16p | 93S10 | £1 |
| 747 Dual OP Amp | 44p | 9311 | £1.20 |
| 930DC | 4p | 93L16 | 36p |
| 933DC | 4p | 9370 | 25p |
| 936DC | 4p | 930399-256 Bit Shift Register | 4p |
| 937DC | 4p | 930399-480 Bit Shift Register | 4p |
| 946DC | 4p | 930399-500 Bit Shift Register | 4p |
| 949DC | 4p | AY5-3507 3 1/2 Digit DVM | £1.05 |
| 953 - 42300 Trip. 2 Innard | 4p | AY5-8300 Ch/Time Display | 36p |
| 961DC | 4p | AY58300 Ch/Time Display | 36p |
| 963DC | 4p | BRCM300 Volt Reg. | £1.40 |
| 1315P2 | 36p | BTT822 | £1.25 |
| 2102 Memory | 72p | C500 Calculator | 37p |
| 2716 Eprom | £10.35 | CA139AG Quad Volt Comp. | 54p |
| 3351-2DC 40 x 9 Bit FIFO 2MHz | £1.07 | CA239G Quad volt comparator | 54p |
| 406D Dynamic RAM 300ns | £1.45 | (T)CA270AE | £1 |
| 7400 | 10p | (T)CA270CW/AW | 35p |
| 74H00 | 26p | (T)CA270CE | 36p |
| 74LS00 | 13p | CA758 (MC1311) | 36p |
| 74S00 | 18p | CA920 TV Horiz. system | 72p |
| 7401 | 7p | CA3001 RF Amp | 86p |
| 74H01 | 26p | CA3028A | 75p |
| 7402 | 11p | CA3044 | £1.20 |
| 7404 | 11p | CA3046 Transistor Array | 40p |
| 547406 | 15p | CA3054 | 69p |
| 74LS08 | 15p | CA3060 | 72p |
| 7410 | 10p | CA3065 | 36p |
| 74L10 | 25p | CA3080 OP AMP | 59p |
| 74H10 | 18p | CA3083 | 65p |
| 7411 | 8p | CA3086 | 29p |
| 7414 | 29p | CA3089 | 54p |
| 7420 | 11p | CA3090AQ | 72p |
| 74S20 | 19p | CA3093 | 36p |
| 74S22 | 18p | CA3094 Prog. Sw. Pwr. OP Amp. | 36p |
| 7425 | 18p | CA3123 | 73p |
| 7426 | 16p | CA3132EM | £2.22 |
| 5430 | 12p | CA3146E | 90p |
| 7430 | 11p | CA3183 | 80p |
| 74L30 | 11p | CA3189 | 73p |
| 547437 | 13p | CA3290 Comparator | 59p |
| 7438 | 14p | CA3401 (LM3900) Quad OP Amp | 36p |
| 74H40 | 26p | CD2500E 30mA/Seg DcmI DcmI Dvr | 90p |
| 7442 BCD to Decimal Decoder | 26p | CD4000 Dual 3 input Nor + Inv. | 12p |
| 74LS42 BCD to Decimal Decoder | 40p | CD4002 Dual 4 Input Nor | 12p |
| 7445 | 42p | CD4004 | 56p |
| 7450 | 11p | CD4006 18 Stage Static Shift Reg. | 36p |
| 74H50 | 26p | CD4007 Dual Comp. Pair + Inv. | 12p |
| 7451 | 7p | CD4008 4 Bit Binary Full Adder | 54p |
| 7454 | 11p | CD4010 Hex Buffers | 30p |
| 74L54 | 11p | CD4012 Dual 4 Input Nand | 13p |
| 547472 | 11p | CD4013 Dual D Flip Flop | 36p |
| 74L72 | 17p | CD4014 8 Bit Shift Register | 36p |
| 5473 | 12p | CD4017 Decade Count/Divide | 54p |
| 7473 | 17p | CD4018 Preset Divide N Count | 54p |
| 74H73 | 26p | CD4019 Quad 2 Input Multiplex | 43p |
| 7474 | 13p | CD4020 14 Stage Binary Count | 25p |
| 74L74 | 25p | CD4021 8 Bit Shift Register | 54p |
| 7475 | 24p | CD4022 Divide by 8 Count/Divide | 54p |
| 547476 | 19p | CD4023 Triple 3 Input Nand | 36p |
| 5480 | 22p | CD4024 2-Stage Binary Counter | 19p |
| 7482 | 35p | CD4025 Triple 3 Input Nor | 36p |
| 7483 | 45p | CD4026 Dec. Count + 7 Seg. Out | 14p |
| 74LS83 | 47p | CD4028/MC14028 BCD/Decimal | 72p |
| 547486 | 18p | CD4029 Synch. Preset Bin/Dec | 42p |
| 5490/7490 | 25p | CD4030 Quad Exclusive or | 54p |
| 7493 Binary Counter 4 Bit | 25p | CD4031 64 stage static shift reg. | £1.20 |
| 5474L95 | 25p | CD4032 | 72p |
| 74LS98 | £1.25 | CD4033 Dec. Count. 7 Seg. Output | 72p |
| 74107 | 20p | CD4034 Static shift register | £1.45p |
| 74S112 | 38p | CD4035 4 Bit Par. in out Shift | 54p |
| 74118 | 75p | CD4037 triple and/or B1 Phase pairs | 72p |
| 74121 | 12p | CD4038 | 72p |
| 74122 | 18p | CD4040 14 St. Rip. carry Bin Count | 54p |
| 5474123 | 35p | CD4041 Quad True/Comp. Buffer | 54p |
| 74132 | 44p | CD4042 Quad clocked D type catch | 54p |
| 74141 | 42p | CD4043 Quad Nor R/S Latch | 56p |
| 74LS145 | 93p | CD4044 Quad Nand R/S Latch | 54p |
| 74151 | 32p | CD4045 4 Bit Par. in out shift | 54p |
| 74154 16 Way Dist. | 35p | CD4046 Micro Power PH. Lock Loop | 54p |
| 74155 | 12p | CD4047 monostable | 36p |
| 74157 | 12p | CD4048 Exp 8 input gate | 72p |
| 74165 | 58p | CD4049 Hex Inverter Buffers | 36p |
| 74167 | 23p | CD4051 Analogue Multi/Demulti | 36p |
| 74173 | 44p | CD4052 Analogue Multi/Demultiplex | 56p |
| 74176/8280 | 30p | CD4053 Analogue Multi/Demulti | 54p |
| 74180 | 12p | CD4054 4 LINE LCD driver/count | 72p |
| 74192 | 33p | CD4055 BCD 7SEG. Decode/Drive | 72p |
| 74LS192 | 60p | CD4056 BCD 7SEG decode/drive | 72p |
| 74193 | 38p | CD4061AD 256 word X 1 Bit St. | 72p |
| 74196 | 36p | RAM | £5.30 |
| 74S196/82S90 | 65p | CD4063 4 bit magnitude comparator | 72p |
| 74LS221 Dual Monostable M/VIB | 52p | CD4066 Quad Bilateral Switch | 27p |
| 74LS290 | 47p | CD4067 1.16 MULTIPLEXER | £2.12 |
| 74293 | 80p | | |

| | | | |
|--------------------------------------|-------|------------------------------------|--------------|
| CD4068 8 Input Nand | 20p | SN75451 | 36p |
| CD4069 Hex Inverter | 13p | SN76001 | 36p |
| CD4071 quad 2 input or buffer | 16p | SN76003 5Wt. Amp | 36p |
| CD4076 Quad D Flip-Flop | 54p | SN76013 5Wt. Amp | 36p |
| CD4077 Quad Exclusive Nor | 30p | SN76013N 5 Wt. Amplifier | 92p |
| CD4078 8 Input Nor | 19p | | |
| CD4081 Quad 2 Input and Buffer | 15p | SN76023 5Wt. Amp | 36p |
| CD4086 4 Wide 2 Input and/or Inv. | 54p | SN76110P | 35p |
| CD4094 8 bit ser. par. hold bus reg. | 72p | SN76115N Stereo Decoder | 35p |
| CD4095 J.K. Gated flip flop non Inv. | 72p | SN76131 | 58p |
| CD4096 gated j.k. flip flop | 72p | SN76227 | 59p |
| CD4502 Strobed Hex Inverter | 44p | SN76228N | £1.60 |
| CD4508BF | £1.78 | SN76396 (TBA396) | 35p |
| CD4510 BCD up down count | 72p | SN76620 AN | 18p |
| CD4511 BCD. 7 seg. latch dec/driver | 72p | SN76650N | 50p |
| CD4519/MC14519 | 54p | SN76660N | 35p |
| CD4520 Dual Synch. 4 Bit Binary | 72p | SN76666N | 35p |
| CD4532 | £1.08 | SN158093 | 50p |
| CD4527 | £1.20 | SN158097 | 4p |
| CD4555 | 72p | SN158099 | 50p |
| CD4556 Decoder | 56p | SP4021 high speed dividers | 75p |
| CD22100 | £1.45 | TAA263 Amp | 75p |
| CD40100 32 bit L/R Shift Reg. | £1.78 | TAA300 1Wt. Amp | £1 |
| CD40101 | £1.08 | TAA320 | 35p |
| CD40108 4 x 4 Multiport Reg. | £3.10 | TAA550 Volt Reg. | 104p |
| CD40162 | 72p | TAA700 | £2.30 |
| CD40163 Bin. count synch. clear | 72p | TAD100 AM Radio | £1.22 |
| CD40181BE Quad 2 Input and | £2.12 | TBA120S/CQ/SB/B TV Amp | 25p |
| CD40182 | 72p | TBA240 | £3.90 |
| CD40192 | 72p | TBA395Q | £1.50 |
| CD40194 | 72p | TBA396 Luminance and chrom. | 35p |
| CD40208BF | £2.12 | TBA550Q | £1.25 |
| CDP1833 Cosmac Rom 1824 x 8 | £3.60 | TBA560C | 52p |
| CDP1834 Cosmac Rom 1024 x 8 | £3.60 | TBA800 Amp 5 Watt Audio | 52p |
| CT1012 C Frequency synthesiser | 75p | TBA920 TV Line System | 70p |
| CT1115 Frequency Synthesiser | 75p | TCA2700/SA/AE/OS | £1 |
| CT1119 Frequency Synthesiser | 75p | TCA2705Q synch. demod. | £1.25 |
| D3624 | 36p | TCA440 A.M. Receiver | 55p |
| DM8214 Interrupt (8080 support) | 36p | TCA830S Ex. Equip A.F. Amp. | 18p |
| FCH111 8 input Nand/Nor | 8p | TCA830S A.F. Amp. | 37p |
| FCH201 | 72p | TCA4401 | £1.25 |
| FJ101 | 50p | TCEP100 | £1 |
| FPO/MPQ3725 4 Tr. Array | 45p | TDA/MC1327 Dual Chroma Demod | 18p |
| FZH151 | 18p | TDA2610 6watt audio amp | 71p |
| FZH191 | 18p | TDA2680 | 71p |
| FZH201 | 18p | TDA2690 | 71p |
| ICL 7103 4 1/2 Digit DVM/DPM | £2.04 | TL720 | 28p |
| IM5623 MPU | 36p | TMS4034 Memory | £1.08 |
| LM300 Volt Reg. | 42p | µPD411AC 300ns Dynamic 4096 x 1 | ram |
| LM326 Volt Reg. | 20p | XR215 | £2 |
| LM340T6 6v Reg. | 26p | ZN414 AM Radio Receiver | 79p |
| LM343 Amp | 4p | ZST131A 5 Input Power NOR | 8p |
| LM1303N Dual Stereo Pre Amp | 65p | | |
| LM/MC1458N Dual OP Amp | 19p | | |
| LM3900 (See CA3041) | | | |
| MC830P | 4p | CAN ELECTROLYTIC CAPACITORS | |
| MC833P dual 4 input expander | 4p | 6 VOLT | |
| MC837P Hex invert. fast rise | 4p | 15,000 90p | |
| MC846P | 4p | 10 VOLT | |
| MC862P | 4p | 16,000 1.20 | 39,000 £2.50 |
| MC863P | 4p | 12 VOLT | |
| MC1306P | 40p | 12,000 90p | |
| MC1307P | 35p | 16 VOLT | |
| MC/CA/BRC 1310P St. Dec. | 35p | 3,300 28p | 6,400 £1.10p |
| MC1312P Stereo Decoder | 40p | 4,700 70p | 10,000 36p |
| MC1314P | 35p | 25 VOLT | |
| MC1315P | 35p | 2,000 20p | 3,300 40p |
| MC1350P | 35p | 2,200 40p | 5,000 90p |
| MC1357P | 35p | 3,300 66p | 6,800 70p |
| MC3202 3 1/2 Digit DVM | £1.45 | 4,700 95p | 25,000 50p |
| MC3302L | 75p | 30 VOLT | |
| MC4044P | £1 | 2,000 20p | 3,000 32p |
| MC4344P | £3.50 | 1,000 50p | 10,000 £1.80 |
| MIC7C | 25p | 35 VOLT | |
| MK2686 | 36p | 1,000 50p | 1,250 23p |
| MK4012 Memory | 38p | 40 VOLT | |
| ML237B | £1 | 470 22p | 2,200 25p |
| MM5335D M.P.U. | 36p | 500 22p | 2,500 55p |
| MM8008 M.P.U. | 36p | 800 50p | 3,300 38p |
| MT300 Volt Reg. | 8p | 50 VOLT | |
| MT305 Volt Reg. | 8p | 2,000 35p | 60/64 VOLT |
| MW 4050D Static Ram 200ns | £1.60 | 500. 30p | 1,500 45p |
| MWS 5101 256x4 SOS CMOS RAM | £3.60 | 1,000 52p | 2,200 85p |
| SAA661 | 36p | 70 VOLT | |
| SAA1010 | 34p | 1,000 30p | 1,500 38p |
| SAA1025 | £4 | 100 VOLT | |
| SAS580 | 18p | 200 40p | 500 55p |
| SAS590 | 18p | 250 25p | 1,000 70p |
| SGS308 Op. Amp | 4p | £1 | 2,000 82p |
| SL403A 3Wt. Amp | 38p | 160 VOLT | |
| SL442 | 36p | 330 40p | 500 75p |
| SN7528 | 11p | 200 VOLT | |
| SN15836 | 25p | 700 76p | 1,000 66p |
| SN15845 | 50p | 250 VOLT | |
| SN15846 | 37p | 100 31p | |
| SN15851 | 50p | 275 VOLT | |
| SN15858N | 55p | 100 14p | |
| SN15862 | 6p | 350 VOLT | 500 £1.20 |
| SN75107 Interface | £1.15 | 50 32p | |
| SN75108 | 36p | 450 VOLT | |
| SN75110 | 46p | 32 17p | |
| SN75150 | 18p | | |
| SN75235N | 11p | | |

Here

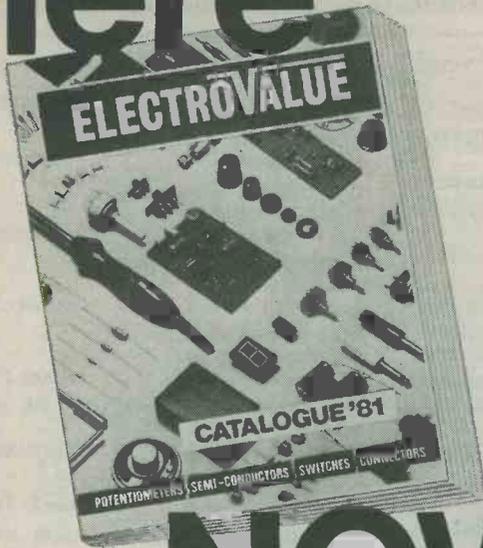

NOW

ELECTROVALUE CATALOGUE '81

as included FREE with December issue of
PRACTICAL ELECTRONICS

It's work-bench size for keeping alongside your favourite journal for instant reference to stock and technical data.

**NEW
LARGE
FORMAT**

With more to choose from than ever - all the items you have learned to depend on being obtainable from Electrovalue PLUS MANY NEW ONES to bring Catalogue '81 bang up to date. The V.A.T. inclusive price list that goes with it will hold for at least 4 months before the next one is issued.

Yes - you will enjoy dealing with Electrovalue - prices are keen - service is tops.

**FREE
FOR THE
ASKING**

Write, phone or call if you haven't yet got Catalogue '81 - and you will receive yours by return. (We pay postage).

AND YOU GET BONUS DISCOUNTS AND FREE U.K. POSTAGE TOO, WHEN YOU BUY FROM ELECTROVALUE.

ELECTROVALUE LTD., (Dept RCE) 28 St. Judes Rd, Englefield Green, Egham, Surrey TW20 0HB. Telephone: (STD 0784) (London 87) 33603 Telex: 264475


Please send me my FREE COPY OF ELECTROVALUE CATALOGUE '81.

Name

Address

(Dept 28(A))

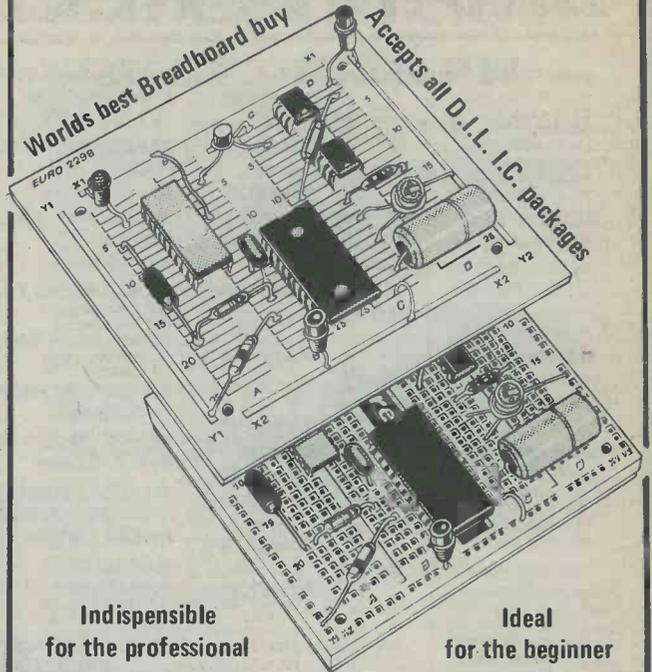First the EuroBreadBoard Now the EuroSolderBoard



Design on a EuroBreadBoard — Instal on a EuroSolderBoard

First the EuroBreadBoard

Will accept 0.3" and 0.6" pitch DIL IC's, Capacitors, Resistors, LED's, Transistors and components with up to .85mm dia leads. 500 individual connections PLUS 4 integral Power Bus Strips along all edges for minimum inter-connection lengths. All rows and columns numbered or lettered for exact location indexing (ideal for educational projects) Long life, low resistance (<10m ohms) nickel silver contacts £6.20 each or £11.70 for 2

Now the EuroSolderBoard

New 100mm square, 1.6mm thick printed circuit board with pre-tinned tracks identically laid out, numbered and lettered to EuroBreadBoard pattern. Four 2.5mm dia fixing holes. £2.00 for set of three ESB's

And don't forget the EuroSolderSucker

Ideal for tidying up messy solder joints or freeing multi-pin IC's, this 195mm long, all metal, high suction desoldering tool has replaceable Teflon tip and enables removal of molten solder from all sizes of pcb pads and track. Primed and released by thumb, it costs only £7.25 including VAT & PP



Snip out and post to David George Sales, Unit 7, Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU

David George Sales,
Unit 7, Higgs Ind. Est., 2 Herne Hill Rd., London SE24 0AU.
Please send me:—

- | | | | |
|-----------------------|----------|-----------------------|--------|
| 1 EuroBreadBoard | @ £ 6.20 | <input type="radio"/> | |
| or 2 EuroBreadBoards | @ £11.70 | <input type="radio"/> | Please |
| or 3 EuroSolderBoards | @ £ 2.00 | <input type="radio"/> | Tick |
| or 1 EuroSolderSucker | @ £ 7.25 | <input type="radio"/> | |

All prices are applicable from Jan. 1st 1980 and include VAT & PP but add 15% for overseas orders.

Name

Company

Address

ERC/12

Tel. No

Please make cheques/P.O. payable to David George Sales and allow 10 days for cheque clearance and order processing

THE MODERN BOOK CO

RADIO & TV SERVICING 1979-1980 Models by R. N. Wainwright £15.50

| | | | | | |
|---|-------------|--|-------------|--|-------------|
| ELECTRONIC FAULT DIAGNOSIS By I. R. Sinclair | Price £3.50 | AUDIO AMPLIFIERS FOR THE HOME CONSTRUCTOR by I. R. Sinclair | Price £3.50 | UNDERSTANDING ELECTRONIC CIRCUITS by I. R. Sinclair | Price £4.50 |
| ELECTRONIC PROJECTS IN AUDIO by R. A. Penfold | Price £2.50 | REPAIRING POCKET TRANSISTOR RADIOS by I. R. Sinclair | Price £2.55 | UNDERSTANDING ELECTRONIC COMPONENTS by I. R. Sinclair | Price £4.50 |
| OP-AMPS THEIR PRINCIPLES & APPL. by J. B. Dance | Price £2.50 | MAKING & REPAIRING TRANSISTOR RADIOS by W. Oliver | Price £2.30 | UNDERSTANDING SOLID-STATE ELECTRONICS by Texas Inst. | Price £3.95 |
| PRINTED CIRCUIT ASSEMBLY by M. J. Hughes | Price £2.10 | WORLD RADIO TV HANDBOOK by J. M. Frost | Price £9.25 | A SIMPLE GUIDE TO HOME COMPUTERS by S. Ditlea | Price £4.00 |
| ELECTRONIC SECURITY DEVICES by R. A. Penfold | Price £1.65 | PROJECTS IN RADIO & ELECTRONICS by I. R. Sinclair | Price £2.50 | HOW TO BUILD A COMPUTER-CONTROLLED ROBOT by T. Loofbourrow | Price £5.30 |
| UNDERSTANDING DIGITAL ELECTRONICS by Texas Inst. | Price £4.00 | ELECTRONIC PROJECTS IN THE HOME by O. Bishop | Price £2.50 | THE CATHODE-RAY OSCILLOSCOPE & ITS USE by G. N. Patchett | Price £4.00 |
| UNDERSTANDING MICRO-PROCESSORS by Motorola | Price £4.30 | SIMPLE CIRCUIT BUILDING by P. C. Graham | Price £2.20 | A GUIDE TO AMATEUR RADIO by P. Hawker | Price £1.70 |
| THE FIRST BK OF MICROCOMPUTERS by R. Moody | Price £3.35 | 110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston | Price £3.20 | MAKING TRANSISTOR RADIOS A BEGINNER'S GUIDE by R. H. Warring | Price £2.90 |
| HOW TO BUILD YOUR OWN SOLID STATE OSCILLOSCOPE by F. G. Rayer | Price £1.70 | HAM RADIO by K. Uilyett | Price £5.00 | | |
| THE OSCILLOSCOPE IN USE by I. R. Sinclair | Price £3.50 | | | | |

We have the Finest Selection of English and American Radio Books in the Country
PRICES INCLUDE POSTAGE

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone: 01-402 9176

DATA PROCESSING

An Instructional Manual for Business and Accountancy Students



UNDERSTAND DATA PROCESSING

NEW FOURTH EDITION

DATA PROCESSING, by Oliver & Chapman, is now in its Fourth Edition

200 pages 9 $\frac{3}{4}$ " x 6 $\frac{3}{4}$ "

PRICE £2.95

P.&P. 48p

PUBLISHED BY D.P. PUBLICATIONS

The primary aim of this outstanding manual is to provide a simplified approach to the understanding of data processing – (previous knowledge of the subject is not necessary).

The 40 chapters and appendices cover the following topics: Introduction to Data Processing; Organisation and Method; Conventional Methods; Introduction to EDP and Computers; Hardware; Computer Files; Data Collection and Control; Programming and Software; flowcharts and Decision Tables; Systems Analysis; Applications; Management of EDP, etc.

A Manual for Business and Accountancy Students


Available from:

DATA PUBLICATIONS LTD.,
57 MAIDA VALE, LONDON W9 1SN.

AND THERES MORE WHERE THIS CAME FROM

It's a long time since one of our adverts was presented in 'list' form - but simply because we do not try to squeeze this lot in every time doesn't mean that it's not available. Our new style price list (now some 40 pages long) includes all this and more, including quantity prices and a brief description. The kits, modules and specialized RF components - such as TOKO coils, filters etc. are covered in the general price list - so send now for a free copy (with an SAE please). Part 4 of the catalogue is due out now (incorporating a revised version of pt.1).

| LINEAR ICs - NUMERIC LISTINGS | | TTL N and LSN | 7443N | 1-15 | 74LS112 | 0-38 | 74LS169 | 2-00 | VARICAP | TRANSISTORS | CAPACITORS | | | | | |
|-------------------------------|------|---------------|-------|--------|---------|-------|---------|---------|---------|-------------|------------|----------|------|-----------------------------|------|---------------------------|
| TLBA120S | 1.00 | KB4413 | 1.95 | 7400N | 0.13 | 7444N | 1.12 | 74LS113 | 0.38 | 74170N | 2.30 | BA102 | 0.30 | BC237 | 0.08 | CERAMIC 50v |
| L200 | 1.95 | KB4417 | 1.80 | 74LS00 | 0.20 | 7445N | 0.94 | 74LS114 | 0.38 | 74LS170 | 2.00 | BAL21 | 0.30 | BC238 | 0.08 | 2B2, 3B3, 4P, 6P8 |
| U237B | 1.28 | TDN4420 | 2.25 | 7401N | 0.13 | 7446N | 0.94 | 74LS115 | 0.83 | 74LS171 | 1.20 | IT210 | 0.30 | BC239 | 0.08 | 8P2, 10P, 15P, 18P, 0.04 |
| U247B | 1.28 | KB4420B | 1.09 | 74LS01 | 0.20 | 7447N | 0.89 | 74LS116 | 0.83 | 74LS172 | 1.10 | BB204B | 0.36 | BC307 | 0.08 | 22P, 27P, 33P, 47P |
| U257B | 1.28 | KB4423 | 2.30 | 7402N | 0.14 | 7448N | 0.56 | 74LS117 | 0.42 | 74LS173 | 0.87 | BB105B | 0.36 | BC308 | 0.08 | 56P, 68P, 82P, 100P, 0.05 |
| U267B | 1.28 | KB4424 | 1.65 | 74LS02 | 0.20 | 7449N | 0.99 | 74LS118 | 0.73 | 74177N | 0.78 | BB109 | 0.27 | BC309 | 0.08 | 150P, 220P, 270P |
| LM301H | 0.67 | KB4431 | 1.95 | 7403N | 0.14 | 7450N | 0.17 | 74LS119 | 1.65 | 74181N | 1.65 | MVM125 | 1.05 | BC413 | 0.10 | 330P, 390P, 470P, 0.05 |
| LM301N | 0.30 | KB4432 | 1.95 | 74LS03 | 0.20 | 7451N | 0.17 | 74LS120 | 0.46 | 74LS182 | 2.10 | BB212 | 1.95 | BC415 | 0.07 | 10N, 2N2, 3N3, 4N7, 0.06 |
| LM308H | 0.96 | KB4433 | 1.52 | 7404N | 0.14 | 7452N | 0.17 | 74LS121 | 0.54 | 74LS183 | 2.00 | KV1210 | 2.45 | BC416 | 0.08 | 10N (0.01uF).....0.05 |
| LM308N | 0.65 | KB4436 | 2.53 | 74LS04 | 0.24 | 7453N | 0.17 | 74LS122 | 0.42 | 74LS184 | 1.35 | KV1211 | 1.75 | BC546 | 0.12 | 22N, 47N.....0.06 |
| LM339N | 0.66 | KB4437 | 1.75 | 7405N | 0.18 | 7454N | 0.17 | 74LS123 | 0.44 | 74LS185 | 1.34 | KV1226 | 1.95 | BC556 | 0.12 | 10N, 220N.....0.09 |
| LM348N | 1.86 | KB4438 | 2.22 | 74LS05 | 0.26 | 7455N | 0.24 | 74LS124 | 0.74 | 74LS190 | 0.92 | KV1225 | 2.75 | BC550 | 0.12 | MONOLITHIC CERAMIC |
| LF351N | 0.38 | KB4441 | 1.35 | 7406N | 0.28 | 7456N | 0.17 | 74LS125 | 0.44 | 74LS192 | 1.80 | KV1225 | 2.75 | BC560 | 0.12 | 10N, 100N.....0.16 |
| LF353N | 0.76 | KB4445 | 1.29 | 7407N | 0.38 | 7457N | 0.28 | 74LS126 | 0.57 | 74193N | 1.05 | TDAL061 | 0.95 | BC639 | 0.22 | FEEDTHRU |
| LM374N | 3.75 | KB4446 | 2.75 | 7408N | 0.17 | 7458N | 0.24 | 74LS127 | 0.78 | 74193N | 1.05 | BC640 | 0.23 | IN SOLDER IN.....0.09 | | |
| LM380N-14 | 1.00 | KB4448 | 1.65 | 7409N | 0.17 | 7459N | 0.28 | 74LS128 | 0.74 | 74194N | 1.05 | 2SC1775 | 0.18 | POLYESTER (SIEMENS) | | |
| LM380N-8 | 1.00 | NE5044N | 2.26 | 7410N | 0.15 | 7460N | 0.17 | 74LS129 | 0.73 | 74196N | 0.99 | 2SB872A | 0.14 | 10mm LEAD SPACING | | |
| LM381N | 1.81 | NE5532N | 1.85 | 74LS09 | 0.24 | 7461N | 0.28 | 74LS130 | 0.60 | 74197N | 1.10 | IN6263 | 0.62 | 10N, 22N, 33N.....0.17 | | |
| ZN419CE | 1.95 | SD6000 | 3.75 | 7411N | 0.20 | 7462N | 0.28 | 74LS131 | 0.78 | 74198N | 1.50 | BA182 | 0.12 | 47N, 68N, 100N.....0.19 | | |
| NE544N | 1.80 | SL6270 | 2.03 | 7412N | 0.17 | 7463N | 0.32 | 74LS132 | 0.78 | 74199N | 1.60 | BA244 | 0.17 | 220N, 470N.....0.22 | | |
| NE555N | 0.30 | SL6310 | 2.03 | 7413N | 0.30 | 7464N | 0.32 | 74LS133 | 0.40 | 74200N | 1.50 | BA379 | 0.35 | 1uF.....0.29 | | |
| NE560N | 0.50 | SL6600 | 3.75 | 7414N | 0.51 | 7465N | 0.32 | 74LS134 | 0.40 | 74201N | 1.50 | TDAL061 | 0.95 | POLYESTER (GENERAL) | | |
| NE560N | 3.50 | SL6640 | 2.75 | 7415N | 0.15 | 7466N | 0.32 | 74LS135 | 0.40 | 74202N | 1.50 | IN4418 | 0.06 | 10mm LEAD SPACING | | |
| NE562N | 4.05 | SL6690 | 2.75 | 7416N | 0.30 | 7467N | 0.32 | 74LS136 | 0.40 | 74203N | 1.50 | IN4001 | 0.06 | 10N, 15N, 22N, 33N.....0.06 | | |
| NE564N | 4.29 | SL6700 | 2.35 | 7417N | 0.30 | 7468N | 0.32 | 74LS137 | 0.40 | 74204N | 1.50 | IN4002 | 0.07 | 47N, 68N, 100N.....0.08 | | |
| NE565N | 1.00 | ICL8038CC | 4.50 | 7418N | 0.48 | 7469N | 0.32 | 74LS138 | 0.40 | 74205N | 1.50 | IN5402 | 1.15 | 22N.....0.11 | | |
| NE566N | 1.60 | MSL9362 | 1.75 | 7419N | 0.15 | 7470N | 0.28 | 74LS139 | 0.40 | 74206N | 1.50 | IN5402 | 1.15 | 22N, 470N, 470N.....0.18 | | |
| NE570N | 3.85 | MSL9363 | 1.75 | 7420N | 0.24 | 7471N | 0.28 | 74LS140 | 0.40 | 74207N | 1.50 | OA91 | 0.17 | 20mm LEAD SPACING | | |
| SL624 | 3.28 | HAL1211 | 1.95 | 7421N | 0.29 | 7472N | 0.28 | 74LS141 | 0.40 | 74208N | 1.50 | AA112 | 0.25 | 22N, 330N, 470N.....0.18 | | |
| TB8651 | 1.81 | HAL1223 | 2.15 | 7422N | 0.29 | 7473N | 0.28 | 74LS142 | 0.40 | 74209N | 1.50 | BRIDGES: | | MYLAR | | |
| uA709HC | 0.64 | HAL1225 | 1.45 | 7423N | 0.27 | 7474N | 0.28 | 74LS143 | 0.40 | 74210N | 1.50 | LA/50V | 0.35 | 5mm LEAD SPACING | | |
| uA709PC | 0.36 | HAL2002 | 1.45 | 7424N | 0.27 | 7475N | 0.28 | 74LS144 | 0.40 | 74211N | 1.50 | 6A/200V | 0.75 | 10N, 10N, 22N, 33N.....0.08 | | |
| uA710HC | 0.65 | HAL2017 | 0.80 | 7425N | 0.27 | 7476N | 0.37 | 74LS145 | 0.97 | 74212N | 1.45 | 2SK135 | 3.75 | 100N.....0.09 | | |
| uA710PC | 0.59 | HAL2402 | 1.95 | 7426N | 0.27 | 7477N | 0.37 | 74LS146 | 0.97 | 74213N | 1.45 | 2SK134 | 3.10 | 20mm LEAD SPACING | | |
| uA714CH | 0.66 | HAL2411 | 1.20 | 7427N | 0.27 | 7478N | 0.37 | 74LS147 | 0.97 | 74214N | 1.45 | 2SK135 | 3.75 | 22N, 470N.....0.17 | | |
| uA714CN | 0.27 | HAL2412 | 1.55 | 7428N | 0.35 | 7479N | 0.37 | 74LS148 | 0.97 | 74215N | 1.45 | 2SK135 | 3.75 | POLYSTYRENE | | |
| uA747CN | 0.70 | LF13741 | 0.33 | 7429N | 0.35 | 7480N | 0.37 | 74LS149 | 0.97 | 74216N | 1.45 | BD535 | 0.52 | 10P, 15P, 18P, 22P | | |
| uA748CN | 0.36 | SN76660N | 0.80 | 7430N | 0.17 | 7481N | 0.48 | 74LS150 | 1.10 | 74217N | 1.45 | BD536 | 0.52 | 27P, 47P, 56P, 68P, 0.08 | | |
| uA753 | 2.44 | | | 7431N | 0.30 | 7482N | 0.69 | 74LS151 | 1.10 | 74218N | 1.45 | BD377 | 0.33 | 100P, 180P, 220P | | |
| uA758 | 2.35 | | | 7432N | 0.25 | 7483N | 0.69 | 74LS152 | 1.10 | 74219N | 1.45 | BD378 | 0.33 | 270P, 330P, 390P.....0.09 | | |
| TB810AS | 1.09 | SAAL056 | 3.75 | 7433N | 0.25 | 7484N | 0.69 | 74LS153 | 0.54 | 74220N | 1.45 | BD165 | 0.30 | 470P, 680P, 820P.....0.10 | | |
| TB820E | 0.75 | SAAL058 | 3.35 | 7434N | 0.40 | 7485N | 0.59 | 74LS154 | 0.54 | 74221N | 1.45 | BD166 | 0.31 | 10N, 10N, 15N, 18N.....0.11 | | |
| TC9A90E | 1.80 | SAAL059 | 3.35 | 7435N | 0.33 | 7486N | 0.59 | 74LS155 | 0.54 | 74222N | 1.45 | BD377 | 0.33 | 2N2, 2N2, 3N3, 3N9.....0.12 | | |
| TDAL028 | 2.11 | LN1C90CD | 14.00 | 7436N | 0.40 | 7487N | 0.59 | 74LS156 | 0.54 | 74223N | 1.45 | BD378 | 0.33 | 4N7, 5N6, 6N6, 10N.....0.13 | | |
| TDAL029 | 2.11 | LM2232 | 19.00 | 7437N | 0.40 | 7488N | 0.59 | 74LS157 | 0.54 | 74224N | 1.45 | BD379 | 0.33 | TANTALUM BEAD CAPS | | |
| TDAL054 | 1.45 | LM2232 | 19.00 | 7438N | 0.33 | 7489N | 0.59 | 74LS158 | 0.54 | 74225N | 1.45 | BD379 | 0.33 | 16v, 0.22, 0.33 | | |
| TDAL062 | 1.95 | LM2232 | 19.00 | 7439N | 0.33 | 7490N | 0.59 | 74LS159 | 0.54 | 74226N | 1.45 | BD379 | 0.33 | 0.68, 1.0.....0.18 | | |
| TDAL072A | 5.04 | MSL2318 | 3.84 | 7440N | 0.17 | 7491N | 0.70 | 74LS160 | 1.30 | 74227N | 1.45 | BD379 | 0.33 | 16v, 2.2, 4.7, 10, 0.10 | | |
| TDAL083 | 1.95 | MSM5523 | 11.30 | 7441N | 0.74 | 7492N | 0.70 | 74LS161 | 0.78 | 74228N | 1.45 | BD379 | 0.33 | 6v3, 2.2, 4.7, 10, 0.10 | | |
| TDAL090 | 3.05 | MSM5524 | 11.30 | 7442N | 0.99 | 7493N | 0.70 | 74LS162 | 1.30 | 74229N | 1.45 | BD379 | 0.33 | 10v, 22, 100.....0.35 | | |
| HAL137 | 1.20 | MSM5525 | 7.85 | 7443N | 0.25 | 7494N | 0.78 | 74LS163 | 1.30 | 74230N | 1.45 | BD379 | 0.33 | ALUMINUM ELECTROLYTICS | | |
| HAL196 | 2.00 | MSM5526 | 7.85 | 7444N | 0.25 | 7495N | 0.65 | 74LS164 | 1.30 | 74231N | 1.45 | BD379 | 0.33 | RAJIAL (VERT. MOUNT) | | |
| HAL197 | 1.00 | MSM5527 | 9.75 | 7445N | 0.25 | 7496N | 0.58 | 74LS165 | 1.04 | 74232N | 1.45 | BD379 | 0.33 | (uF/voltage) | | |
| LM1220 | 1.40 | MSM5527L | 9.75 | 7446N | 0.33 | 7497N | 0.58 | 74LS166 | 1.04 | 74233N | 1.45 | BD379 | 0.33 | 1/63, 2/2, 50, 4/7, 35 | | |
| LM1303 | 0.99 | ICM7106CP | 9.55 | 7447N | 0.33 | 7498N | 0.58 | 74LS167 | 1.04 | 74234N | 1.45 | BD379 | 0.33 | 10/16, 15/16, 22/10 | | |
| LM1307 | 1.55 | ICM7106CP | 9.55 | 7448N | 0.33 | 7499N | 0.58 | 74LS168 | 1.04 | 74235N | 1.45 | BD379 | 0.33 | 33/6, 3.....0.08 | | |
| LM1310P | 1.90 | ICM71217A | 9.50 | 7449N | 0.33 | 7500N | 0.58 | 74LS169 | 1.04 | 74236N | 1.45 | BD379 | 0.33 | 10/16, 15/16, 22/10 | | |
| LM1310P | 1.90 | ICM71217A | 9.50 | 7450N | 0.33 | 7501N | 0.58 | 74LS170 | 1.04 | 74237N | 1.45 | BD379 | 0.33 | 22/16, 33/10 | | |
| LM1310P | 1.90 | ICM71217A | 9.50 | 7451N | 0.33 | 7502N | 0.58 | 74LS171 | 1.04 | 74238N | 1.45 | BD379 | 0.33 | 47/10.....0.09 | | |
| LM1310P | 1.90 | ICM71217A | 9.50 | 7452N | 0.33 | 7503N | 0.58 | 74LS172 | 1.04 | 74239N | 1.45 | BD379 | 0.33 | 10/63, 22/50, 33/50 | | |
| LM1310P | 1.90 | ICM71217A | 9.50 | 7453N | 0.33 | 7504N | 0.58 | 74LS173 | 1.04 | 74240N | 1.45 | BD379 | 0.33 | 47/16, 100/16.....0.10 | | |
| LM1310P | 1.90 | ICM71217A | 9.50 | 7454N | 0.33 | 7505N | 0.58 | 74LS174 | 1.04 | 74241N | 1.45 | BD379 | 0.33 | 47/63, 100/25, 220/16 | | |
| LM1310P | 1.90 | ICM71217A | 9.50 | 7455N | 0.33 | 7506N | 0.58 | 74LS175 | 1.04 | 74242N | 1.45 | BD379 | 0.33 | 470/6, 3.....0.12 | | |
| LM1310P | 1.90 | ICM71217A | 9.50 | 7456N | 0.33 | 7507N | 0.58 | 74LS176 | 1.04 | 74243N | 1.45 | BD379 | 0.33 | 100/6, 3, 470/16 | | |
| LM1310P | 1.90 | ICM71217A | 9.50 | 7457N | 0.33 | 7508N | 0.58 | 74LS177 | 1.04 | 74244N | 1.45 | BD379 | 0.33 | 100/10.....0.18 | | |
| LM1310P | 1.90 | ICM71217A | 9.50 | 7458N | 0.33 | 7509N | 0.58 | 74LS178 | 1.04 | 74245N | 1.45 | BD379 | 0.33 | 1000/16, 470/63.....0.23 | | |
| LM1310P | 1.90 | ICM71 | | | | | | | | | | | | | | |

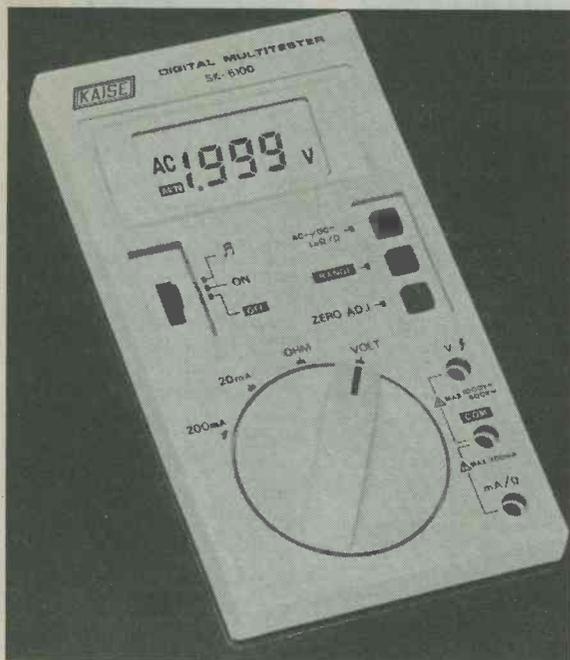

AUTORANGING, AUTO UNIT DISPLAY DMMs for under £40

A major price breakthrough on Autoranging, 3½-digit DMMs with a unique Auto Unit Display has been announced by Maclin-Zand Electronics, with four models selling from only £39.95, inc. VAT.

Hand-held, rugged, and with ergonomically laid out fascias, the four models offer a range of features you'd be hard put to find on DMMs costing two to three times as much. Zero adjustment; 3½-digit LCD with 200 hrs continuous battery life, Full Autoranging; Auto 'Batt' Warning; Auto Unit Display, plus buzzer for Continuity Test and Over Range Indicator on Models 6110 and 6100. Models 6110 and 6220 measure AC/DC current to 10 A, Models 6100 and 6200 to 200mA.

Available only from Maclin-Zand direct, prices are £39.95 for the 6200, £49.95 for the 6220, £64.95 for the 6100 and £74.95 for the 6110. These price include VAT, batteries, pair of test leads, spare fuse and one year guarantee, but exclude p&p, for which £1.15 should be added. Full information and specs on the range are available from Maclin-Zand Electronics, 38 Mount Pleasant, London WC1X 0AP.

GYR AND LANDIS COMMEMORATIVE PRIZE – 1980

The 1980 Karl Heinrich Gyr and Heinrich Landis Commemorative Prize has been awarded by the Institute of Electrical Engineers to Martin Weston of the BBC Engineering Research Department.

Martin Weston has worked at the Research Department for ten years and has spent much of that time developing the techniques of digital television processing. He has been awarded the Prize for his development of the Electronic Zone-Plate which is proving to be a valuable tool in testing and assessing

the performance of digital television systems. The Zone-Plate generates television pictures incorporating periodic gratings of all possible pitches, slopes and rates of movement by electronic means.

The Commemorative Prize won by Martin Weston is awarded annually by the I.E.E. and sponsored by Landis and Gyr Ltd. for practical contributions to the advance of electrical and electronic science and engineering with particular reference to measurement and assessment techniques.

UNIPART AUDIO RANGE

Ten separate Unipart radios, radio/cassette players and cassette players built with technologically advanced quality products that look as good as they should. Each unit is competitively priced and is backed by Unipart's extensive range of accessories, fitting kits and aerials.

The new Unipart audio range consists of:- 1. A manually tuned AM radio. 2. Two five push button AM radios. 3. A six push button AM/FM radio. A prestige 6 push button AM/FM stereo radio. 5. An under dash stereo cassette tape player. 6. Two manually tuned radio combined stereo cassette tape players. 7. A six station pre-selection AM radio combined with a stereo cassette tape player. 8. A six station, pre-selection AM/FM stereo radio combined with a stereo cassette tape player.

Each audio product will be available at 240 BL distributors, 2,000 other UK distributors, 650 Unipart shops and 130 Unipart centres.



RADIO AND ELECTRONICS CONSTRUCTOR

... COMMENT

'THE NIGHTINGALE'S' FIRST BROADCAST

A number of readers were very interested in the article 'First Woman Broadcaster Ever' which appeared in our August 1980 issue.

Many readers will therefore probably be interested to learn of the first broadcast by Dame Nellie Melba, known to the world as 'The Nightingale'. It was made approximately three months after those of Miss Sayer – the first woman broadcaster ever.

The event was advertised widely in the national press and on 15th June 1920 Dame Nellie Melba went to the Chelmsford Works of Marconi to sing.

Completely unaware of how the 'magic' of broadcasting worked, she was shown the site. When told that her voice would go out from the aerial slung some four hundred and fifty feet above her head from two masts, she said to Arthur Burrows (later BBC's first Director of Programmes) "Young man, if you think I'm going to climb up there, you're quite mistaken."

In the event she sang in the transmitter shed, which today is the high-power test area of Marconi Communication Systems Limited.

Amongst those present at her broadcast were William Ditcham, a Marconi engineer, who had made the world's first broadcast, and Miss Winifred Sayer. Miss Sayer, now 82 years old Mrs Winifred Collins, recalled Dame Nellie, who had two accompanists, kicking back the carpet that had been laid on the concrete floor as it spoilt the acoustics. The microphone was a problem, as it did not have an adequate mouth-piece, so one was improvised from the sides of a Havana-cigar box and the contraption was suspended in front of Dame Nellie, who subsequently autographed and dated it. The microphone and its embellishments is still in the possession of The Marconi Company.

Dame Nellie's broadcast was an immediate success. It was followed up over the next few months by further broadcasts using other famous singers. There were also news and current affairs broadcasts as well as instrumental recitals, and in August 1920 the first broadcast to a ship at sea was made, specifically to the ss Victorian which was taking delegates to an international press conference in Canada. They were daily kept informed of news by a bulletin from Chelmsford.

Still experimental, these broadcasts led to the establishment of '2MT Writtle', just outside Chelmsford, in February 1922 and '2LO Strand' in May 1922. '2LO' was later handed over by Marconi to the newly formed British Broadcasting Company in November 1922.

DESIGN OFFICE REFERENCE

Now available from MCP Electronics on behalf of TRW LSI Products is a new 1980 'short form' catalogue offering the immediate answer to what could well be described as hundreds of Digital Signal Processing Design problems.

Copies of the new 1980 short form are available on request from: MCP Electronics Ltd, 38 Rosemont Road, Alperton, Wembley, Middlesex HA0 4PE.

SEALED NICKEL CADMIUM BATTERIES



The 520/8 range of nickel cadmium sealed batteries, style NR-AA, offered by Symot Limited have a nominal voltage 1.2V and a capacity of 500 mAh. The quick charging rate is 4.5 hours at 150 mA and a life of more than 500 cycles of operation, under normal conditions, is claimed.

The volume is 0.51 cubic inches (8.3 cc) giving an energy density rating of 60mAh per cc.

These batteries are suitable for use up to 45deg. C.

The batteries are fitted with flat contact type terminals and weigh 0.74 ounces (21 gm). A re-sealable type of safety vent is fitted.

Full information can be obtained from: Symot Limited, 22a Reading Road, Henley on Thames, Oxon RG9 1AG.

POCKET POWER FROM TANDY

One of the smallest computers on the market, the new Tandy TRS-80 Pocket Computer, should be available by the time these notes appear.

This latest addition to the Tandy TRS-80 range is only 175mm x 70mm x 15mm and will sell for £119 (including VAT).


It is battery powered which means that a number of programmes can be loaded and retained for up to 300 hours (the life of the battery) even when the power is switched off.

Because it does not rely on a mains supply the new TRS-80 Pocket Computer can be carried around and used almost anywhere.

There are already eight packages of software available to cover varying needs. These include civil engineering, aviation, maths drill, business statistics, real estate, personal finance and a games package. These, too, will be in the shops in late autumn at prices ranging from £8.95 to £13.95 (including VAT).

The Tandy Pocket Computer has a 4-bit CPU consisting of two microprocessors. It can carry 1.9K of user memory (RAM) and a total of 11K of ROM – 7K for the BASIC interpreter and approximately 4K for the monitor.

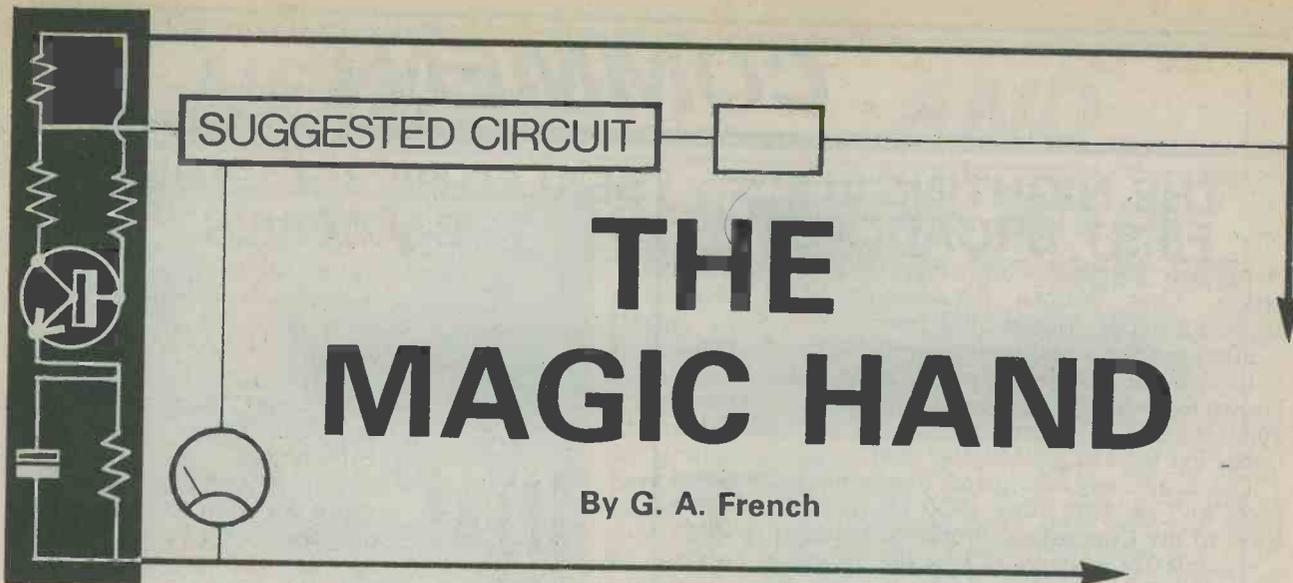Using the cassette interface (£17.95), multiple programmes can be loaded from cassette tape without the previous programme being erased.



THE MAGIC HAND

By G. A. French

This article describes a novelty device which can be both instructive and amusing.

On the surface of a wooden or plastic panel is affixed a piece of card cut out in the shape of a hand. A person being introduced to the device is asked to place his hand flat on the panel, so that the fingers and main part of his hand conform with the cut-out and are positioned within its outline. As soon as the hand is fully placed on the cut-out a circuit is completed, this consisting of the lighting of a lamp, the sounding of a buzzer or any other effect favoured by the constructor. At the same time there are no visible or obvious electrical connections or contacts on the panel which the person's hand can touch.

FOIL CONTACTS

Fig. 1(a) shows the cut-out of the card hand as seen from above. On the underside are glued two pieces of kitchen aluminium foil with the approximate shape and size shown in Fig. 1(b), and having two straight edges at the centre spaced from each other by approximately $\frac{1}{4}$ in. When a hand is placed on the top side of the card,

the increased capacitance between the two pieces of foil activates the circuit which lights the lamp or produces the alternative effect.

The circuit of the device is given in Fig. 2. Here, ICI is a 555 oscillating in the standard astable mode at a frequency of around 200kHz. Its output at pin 3

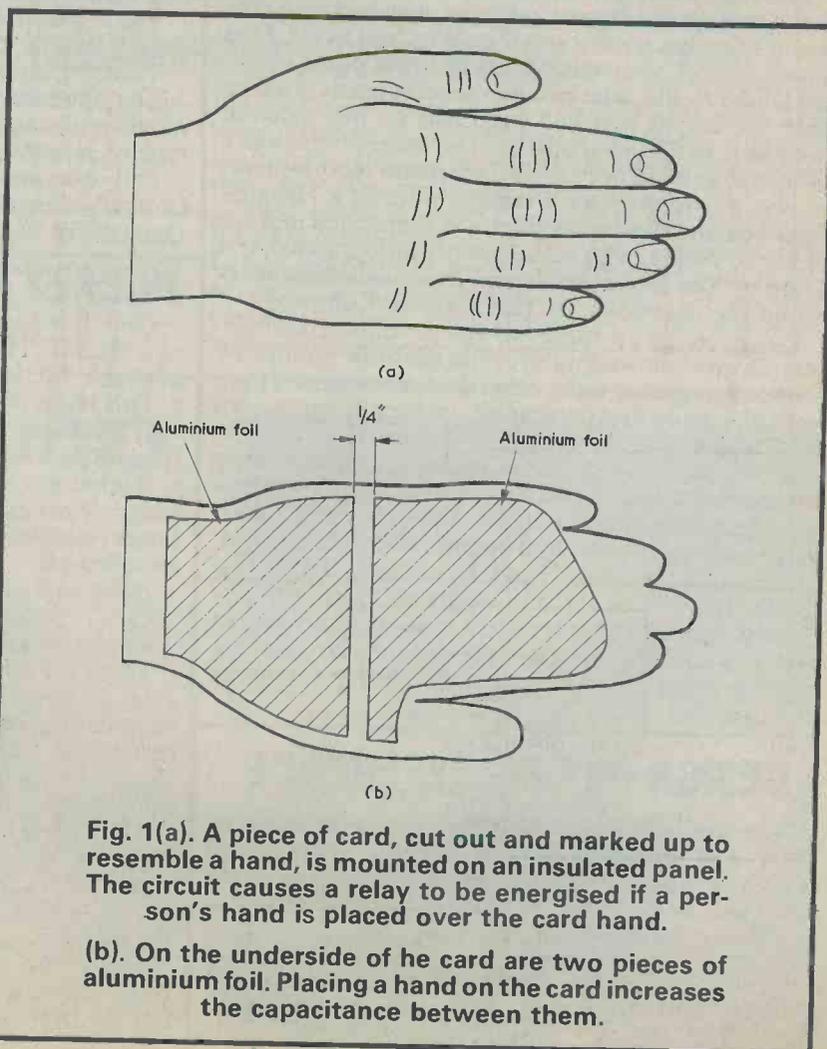


Fig. 1(a). A piece of card, cut out and marked up to resemble a hand, is mounted on an insulated panel. The circuit causes a relay to be energised if a person's hand is placed over the card hand.

(b). On the underside of the card are two pieces of aluminium foil. Placing a hand on the card increases the capacitance between them.

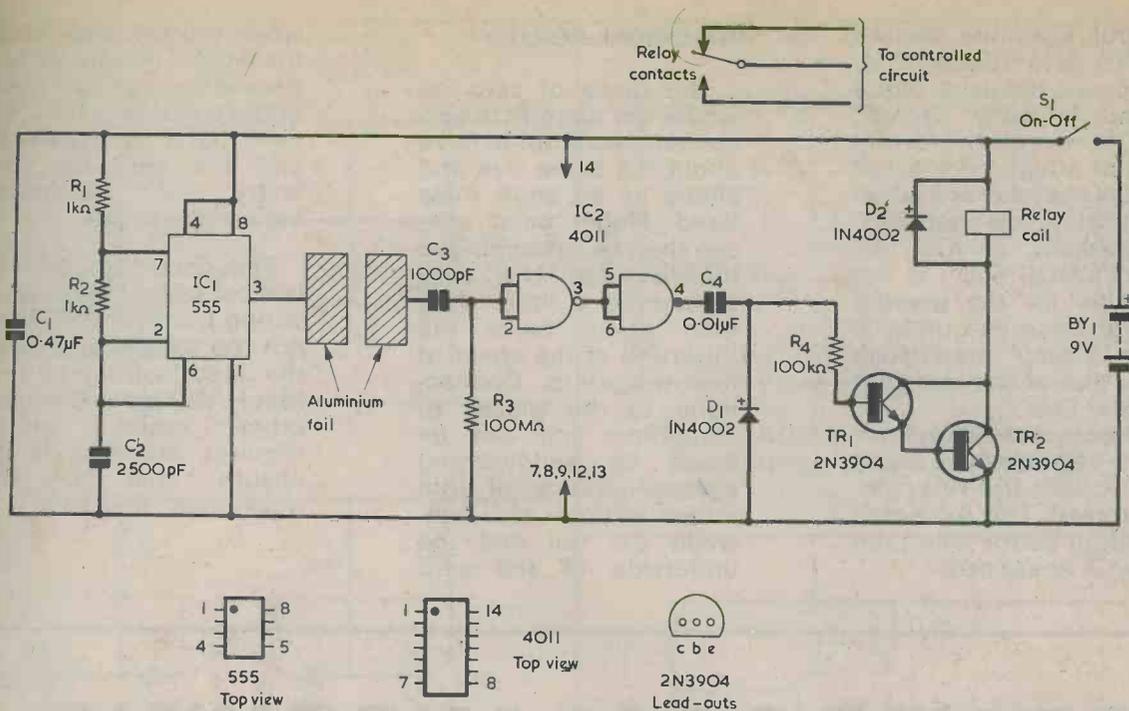


Fig. 2. The circuit of the "Magic Hand". IC1 is a standard 555 oscillator whose output, when the capacitance between the two pieces of foil is sufficiently high, is passed through the two NAND gates of IC2.

connects directly to one of the pieces of aluminium foil shown in Fig. 1(b). The other piece of foil connects via C3 to the inputs of a NAND gate in a CMOS 4011 i.c., the NAND gate output connecting to a second NAND gate. Both gates are employed as inverters. The inputs of the first gate are kept low by R3, and the output of the second gate is similarly low. Normally, the stray coupling between the 555 output and the first NAND gate inputs is too low to have any effect on the NAND gate. When, however, a hand bridges the two pieces of foil, the increased capacitive coupling takes the NAND gate inputs sufficiently high on positive pulses from the 555 to produce corresponding low pulses at the NAND gate output. The output of the first NAND gate is fed to the second NAND gate, which provides any further amplification that may be needed. Thus,

when a hand is placed over the two pieces of foil an output at 200kHz, with the maximum amplitude which a CMOS NAND gate is capable of providing, is produced at the output of the second NAND gate.

The use of the two NAND gates in this manner ensures that, as the capacitance between the two pieces of foil is increased, there is a level of capacitance at which the second NAND gate commences, fairly abruptly, to produce a 200kHz output. There is not a gradual increase in 200kHz output as would be given with a normal linear amplifier.

RECTIFIER CIRCUIT

When it is present, the 200kHz output of the second NAND gate is applied to the shunt rectifier circuit consisting of C4 and D1, and a rectified positive voltage appears at the junction of these two components. This voltage is applied via R4 to the

base of TR1, whereupon TR1 turns on and causes the relay to energise. The relay contacts then switch on the lamp or cause the alternative effect to be given. The relay de-energises again as soon as the hand is taken away from the pieces of aluminium foil.

Apart from R3, the components are all standard types. The author employed ten 10MΩ resistors connected in series to produce the 100MΩ required in R3. Higher value resistors could similarly be connected in series to produce approximately the value required. The relay employed with the prototype circuit was an "Open Relay" with 410Ω coil, and this is available from several suppliers including Maplin Electronic Supplies. The diode specified for D1 has reduced efficiency at 200kHz but it functions adequately in the present circuit where there is a relatively low impedance

output from the second NAND gate. Diode D2 is, of course, the usual diode found in relay circuits, and it prevents the formation of a high back-e.m.f. across the relay coil when the relay de-energises. Incidentally, an ICM7555 (the "CMOS 555") is not suitable for the present circuit since its output is at a higher impedance than that of the standard bipolar 555.

The current drawn from the 9 volt supply is about 15mA with the relay de-energised. This increases to about 35mA when the relay is energised.

PRACTICAL POINTS

The piece of card on which the hand is drawn should be cut out to have about the same size and shape as an adult male hand. Finger nails, etc., can then be inked in. The thickness of the card should be a little more than about twice the thickness of the cover of this magazine. Connections to the pieces of aluminium foil can be made by sandwiching several strands of thin tinned copper wire between the foil and the underside of the card

when the foil is glued to the latter. The wire is then passed through two holes in the panel on which the card hand is mounted, and the electronic circuitry is positioned behind the panel.

The circuit should be laid out so that the output wiring from the 555 does not too closely approach the input wiring to the first NAND gate. The only other point which requires attention is to ensure that C1 is positioned close to IC1.

RECIPROCAL WORKING

By G. B. Brown

Rapid results from your calculator

Even the less expensive general purpose electronic calculators can make short work of solving electronic calculations. What are probably three of the most useful key functions here are the square (x^2), the square root (\sqrt{x}) and the reciprocal ($1/x$) keys. If your calculator has these three keys then it is capable of quickly working out most of the simple electronic problems you are liable to encounter. The key I would like to concentrate on in this short article is the reciprocal key, since it can provide useful short cuts in working out such things as cycle length and frequency in RC oscillators.

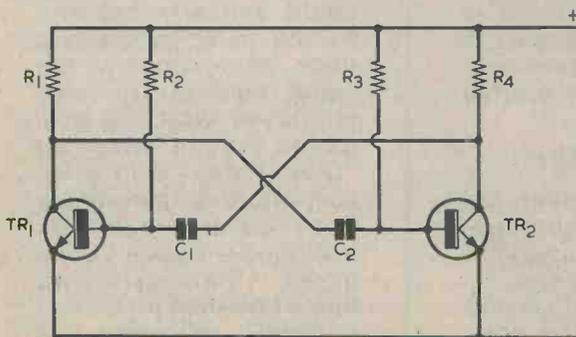


Fig. 1. The standard multivibrator. Frequency is controlled by the values of R2, R3, C1 and C2.

MULTIVIBRATOR

Take the familiar multivibrator of Fig. 1. During the multivibrator cycle TR1 is turned off for part of the time and TR2 is turned off for the remainder of the cycle. The length of time each transistor is turned off depends on the values of the resistor and capacitor connected to its base. Mathematically, the length of time when TR1 is turned off is approximately equal to 0.7 times the time constant of R2 and C1, and the length of time when TR2 is cut off is approximately equal to 0.7 times the time constant of R3 and C2.

Before proceeding further a word of warning. When each transistor is initially turned off in the cycle its base goes negative of the negative rail by nearly the full supply voltage. If this voltage exceeds the transistor base-emitter junction reverse breakdown voltage no harm results, but the junction behaves like a zener diode and upsets the timing calculations. Nearly all modern silicon transistors have base-emitter breakdown voltages of the order of 6 volts or more, so if you want the multivibrator of Fig. 1 to run at around its calculated frequency it's a good idea to use a supply of 6 volts or less. And now to the calculations.

TR1 cut-off time is approximately equal to 0.7 times the time constant of R2 and C1, i.e. it is equal to $0.7 \times R2 \times C1$. Useful units are megohms, microfarads and seconds. Let's say that, as in Fig. 2(a), R2 is 220k Ω (=0.22M Ω) and that C1 is 0.047 μ F. We press the calculator keys to give:

$$0.7 \times 0.22 \times 0.47 =$$

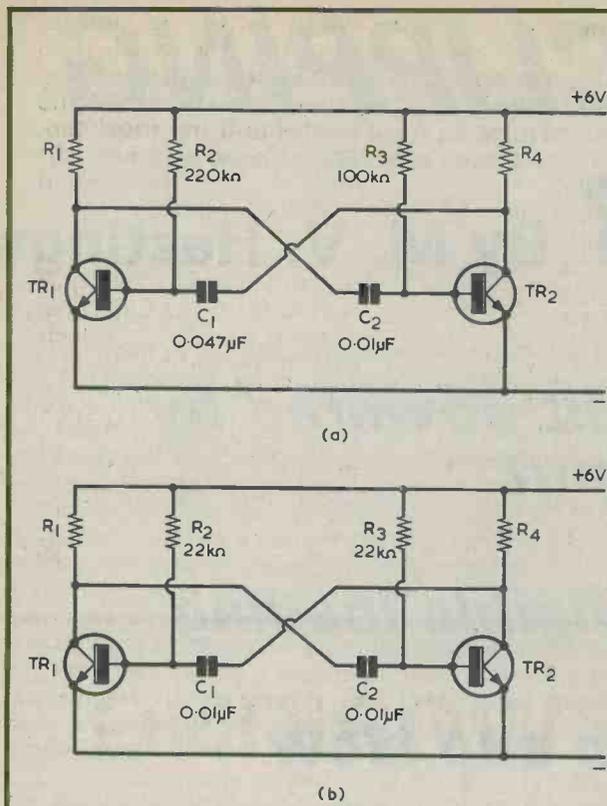


Fig. 2(a). Multivibrator with a calculated frequency of 126Hz (b). Square wave multivibrator having a frequency of 3.25kHz.

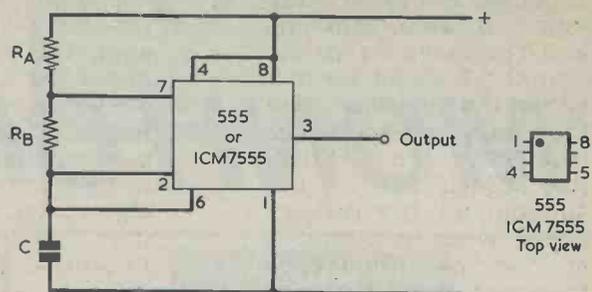


Fig. 3. Astable multivibrator incorporating a 555 or an ICM7555

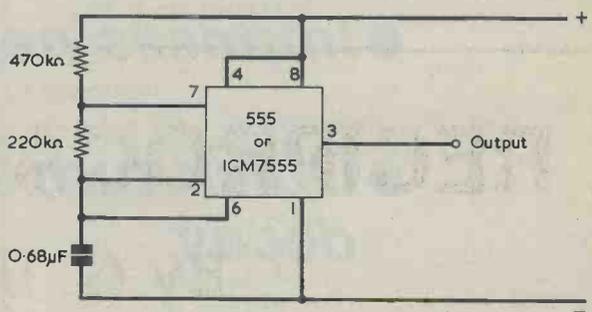


Fig. 4. The astable with typical timing component values.

and we find that the time is 0.00724 second to three significant figures. If we next say that R3 is 100kΩ (=0.1MΩ) and C2 is 0.01μF, the time when TR2 is off calculates as 0.0007 second. Total cycle time is 0.00724 plus 0.0007, which equals 0.00794 second.

And the frequency? Press the 1/x button and you'll find that it is 126Hz to three significant figures.

When R2 equals R3 and C1 equals C2 the total cycle time is approximately 1.4CR. Let's assume that R2 and R3 are 22kΩ (=0.022MΩ) and that C1 and C2 are 0.01μF. See Fig. 2(b). The key sequence:

$$1.4 \times 0.022 \times 0.01 =$$

gives 0.000308 second. Pressing the reciprocal key gives the frequency, which is 3250Hz, or 3.25kHz.

555 AND ICM7555

The usefulness of the reciprocal key becomes more apparent when we deal with oscillators incorporating the 555 and ICM7555. The basic oscillator circuit is shown in Fig. 3 and frequency is given by:

$$f = \frac{1.46}{(RA + 2RB)C}$$

Units can be megohms, microfarads, seconds and Hertz.

Now, the most cumbersome part of the right hand side of the equation is the $(RA + 2RB)C$ and it is a good plan to work this out first. After that we invert it and then multiply by 1.46. Here's the key sequence:

$$2 \times RB = + RA = \times C = 1/x \times 1.46 =$$

The "equals" keystrokes in the middle of the sequence are needed to get the calculation, as it progresses, into the calculator register. Let's try the example of Fig. 4, with RA being 470kΩ (=0.47MΩ), RB being 220kΩ (=0.22MΩ) and C being 0.68μF. We press:

$$2 \times 0.22 = + 0.47 = \times 0.68 = 1/x \times 1.46 =$$

and we arrive at a frequency of w.36Hz.

Using the reciprocal key in this manner takes quantities from below the fraction bar and produces their values when shifted above the fraction bar. If we hadn't used the reciprocal key we would have had to do something like work out $(RA + 2RB)C$, write the result on a piece of paper (or, in a more expensive machine, store it), clear, key in 1.46 and then divide by the result we had noted (or stored).

Reverting to the equation we have just solved, how do we find the total cycle length corresponding to the frequency of 2.36Hz? That's easy. We just press the reciprocal key again, and the calculator tells us that it is 0.424 second. ■

ADD-ON CLIPPING MONITOR

By M. V. Hastings

- *Monitor circuit powered by amplifier output*
- *Imposes negligible loading*
- *Quick turn-on and slow decay.*

If an audio amplifier is overdriven, the output signal becomes distorted due to the inability of the amplifier to provide a sufficiently large output voltage swing. The peaks of the signals are flattened by the overloading, causing a type of distortion which is known as "clipping".

Overdriving an amplifier is unlikely to damage the amplifier itself, although this is still possible with some designs, and the main result is increased distortion. The severity of this distortion depends on how hard the amplifier is overdriven and to a certain extent on the nature of the programme material. Although there may be a significant loss of fidelity, it still may not always be obvious to a listener that clipping is taking place.

One danger given by clipping is that the distortion causes the generation of new signals, most of which will be at high frequencies. If the speakers employed in the system incorporate tweeters, the amount of power fed to the tweeters can be considerably increased by the clipping. It is possible, with the amplifier driving the speakers hard, that the tweeters will be fed with signals approaching or even exceeding the maximum power that they can handle. Indeed, clipping can (and does) sometimes lead to tweeters being burnt out.

OVERLOAD INDICATOR

It is not uncommon these days for an amplifier to be fitted with an output power meter, or i.e.d. overload indicators, either of which give a visual warning when the amplifier is being overdriven. It is not difficult to add clipping indicators to an amplifier which does not already have this facility built in, and a simple add-on clipping monitor forms the subject of this article.


The monitor has two i.e.d. indicators, one to monitor each stereo channel of the amplifier. The appropriate i.e.d. flashes on if clipping occurs in the channel being monitored. The circuit is connected to the two outputs of the amplifier, or across the two speakers, and no other connection is required. Furthermore, the circuit is powered by the signals taken from the amplifier and does not require a battery or other form of power supply. The additional loading imposed on the amplifier by coupling the monitor to it is negligibly low.

The two monitoring channels are identical and are not interconnected with each other in any way. If a mono amplifier is to be monitored, only one monitoring channel needs to be constructed.



The monitor inputs are taken to two 2-way DIN sockets mounted on the rear panel.

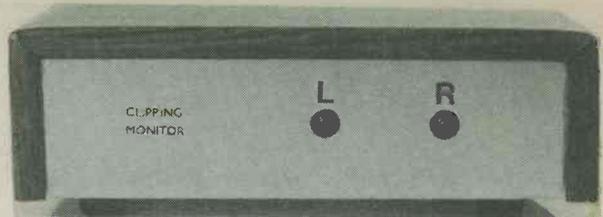The unit is powered by the amplifier output which it monitors, and the only items mounted on the front panel are the two clipping indicator l.e.d.'s.



THE CIRCUIT

The circuit of one monitoring channel is shown in Fig. 1. This breaks down into three basic sections: an adjustable attenuator at the input, a full-wave rectifier which rectifies the output from the attenuator, and a voltage detector flashing circuit which is actuated by the rectified signal voltage.

The output from the amplifier is applied to R1 and R2 in series. R1 is a current limiting resistor which reduces the risk of damage to the amplifier in the event of a fault or constructional error. R2 is adjusted to suit the particular amplifier with which the monitor is to be used and it can be set to the required level for any amplifier having a maximum peak-to-peak output swing of at least several volts. Quite small amplifiers are capable of providing an output of this magnitude.

The signal voltage tapped off at R2 slider is fed to the full-wave rectifier consisting of D1 to D4, the rectified voltage being smoothed to a small extent by the fairly low value reservoir capacitor, C1. Since C1 is charged from a fairly low source impedance the voltage across it quickly responds to any rise in the input voltage. Its discharge path is through the voltage detector section, because discharge back to the input circuit is blocked by the bridge rectifier. If there is a sudden and short increase in signal level, C1 charges quickly and then discharges slowly.

The purpose of the voltage detector flashing circuit is to turn on the l.e.d. indicator D7, when the voltage across C1 exceeds a certain threshold level. It incor-

COMPONENTS

Resistors

(All fixed values ¼ watt 5% unless otherwise stated)

- R1 2-off 10Ω
- R2 2-off 470Ω pre-set potentiometer, 0.25W horizontal
- R3 2-off 3.9MΩ
- R4 2-off 100KΩ
- R5 2-off 390Ω

Capacitors

- C1 2-off 3.3μ electrolytic, 10V Wkg.
- C2 2-off 0.1μ polyester, type C280

Semiconductors

- IC1 2-off ICM7555
- D1-D4 8-off IN4001
- D5 2-off IN4148
- D6 2-off IN4148
- D7 2-off TIL220 (see text)

Sockets

- SK1 2-off 2-way DIN socket

Miscellaneous

- Case (see text)
- Veroboard, 0.1in. matrix
- 2-off panel-mounting bushes (for D7)
- Nuts, bolts, wire, etc.


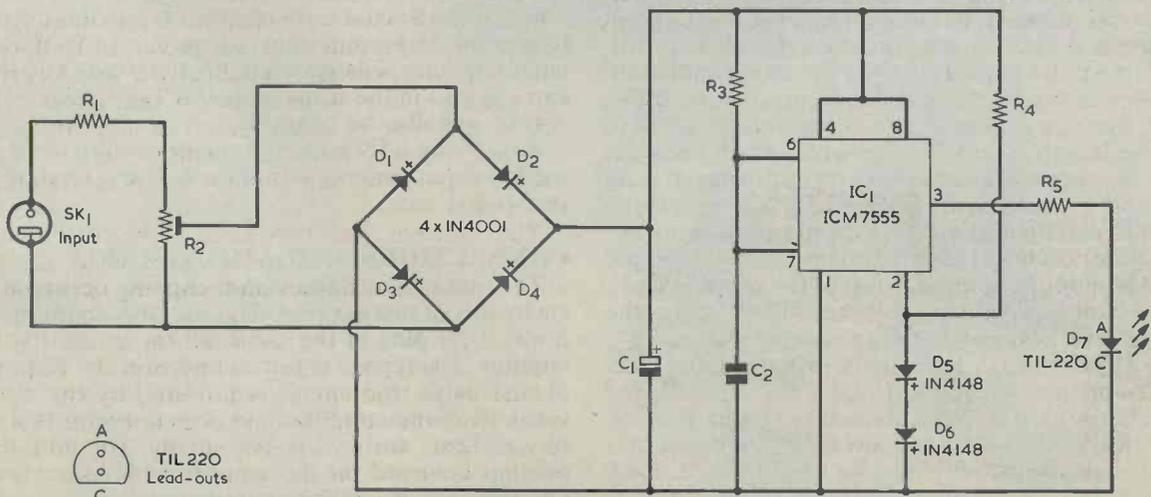


Fig. 1. The circuit of one channel of the clipping monitor. The other channel is identical. R2 is set up such that l.e.d. D7 flashes when the associated amplifier output is at, or very close to, clipping level.

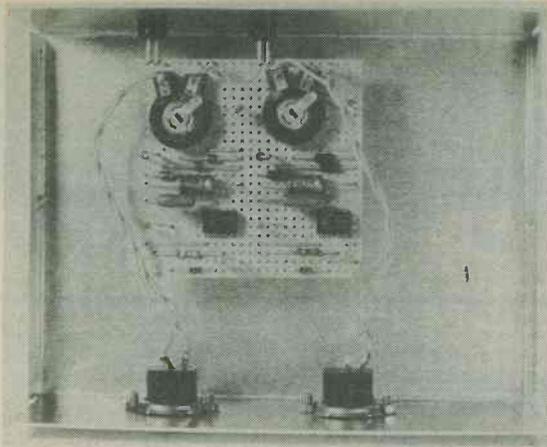

All the components apart from the input sockets are assembled on a Veroboard panel. This is secured inside the case by the front panel mountings for the two l.e.d.'s.

porates an ICM7555, which is the CMOS version of the well-known 555 timer i.c. and has the advantage here of requiring a supply current in the order of tens of microamps. This is very much lower than the current consumption of the standard 555. Only a limited drive current is available from C1 and the use of an ICM7555 ensures that as much of this current as possible is used to drive the l.e.d., with only a very small current being lost in the i.c.

The i.c. is employed in a standard 555 monostable configuration, in which a positive output pulse appears at pin 3 when the trigger input at pin 2 is taken below one-third of the supply voltage. The duration of the output pulse would (with a steady supply voltage to the i.c.) be theoretically 425mS.

The two forward biased silicon diodes, D5 and D6, act as a voltage regulator and apply a voltage of about 1.2 volts to pin 2. If the voltage across C1, which is the supply voltage for the ICM7555, exceeds 3.6 volts the monostable is triggered since pin 2 is then at less than one-third of this supply voltage. Pin 3 goes positive and current flows through the l.e.d. via R5. In practice, the l.e.d. may not always turn on for the theoretical 425mS pulse period given by the monostable timing components, because the l.e.d. current now drawn from C1 may cause the voltage across this capacitor to fall. The length of time during which the l.e.d. stays alight depends on the nature of the input signal from the amplifier but it will still be lit for a long enough period to clearly indicate that clipping has occurred.

R2 is adjusted so that the monostable is triggered when the amplifier output is just at the clipping level. Output voltages which are even slightly below the clipping level will not actuate the monostable.

The ICM7555 i.c. is available from Maplin Electronic Supplies. Two TIL220 l.e.d.'s are required, and these are red l.e.d.'s with a diameter of 0.2in. they are not critical components and any other similar l.e.d.'s of reasonable sensitivity may be used instead. Each l.e.d. requires a panel mounting bush. Capacitor C1 is specified in the Components List as having a working voltage of 10 volts. It will be quite in order here to use a 3.3 μ F electrolytic capacitor having a much higher working voltage, such as 63 volts.

CONSTRUCTION

All the components are assembled on a Veroboard panel of 0.1in. matrix having 25 holes by 25 copper strips. This has to be carefully cut out from a larger size by means of a small hacksaw. (As will be explained shortly, a board having the same number of strips but with more holes and more breaks in the strips may be required if the constructor wishes to adopt a method of mounting which differs slightly from that used by the author.)

The board is next prepared by making the ten breaks in the copper strips which are shown in the layout diagram of Fig. 2. In each channel, four of the breaks isolate the two rows of i.c. pins from each other whilst the fifth break isolates the input connection at R1 from the remainder of the circuit. The components and link wires are then soldered into place, with the i.c.'s being connected last. Although the ICM7555 is a CMOS device it does not need the special handling precautions normally associated with CMOS integrated circuits.

If the unit is to be used with a mono amplifier only one monitor circuit has to be built, and this can be assembled on a board having 25 holes by 12 copper strips.

The completed board is small enough to fit into most small cases. The prototype is housed in a metal case type TP2, available from Maplin Electronic Supplies, which measures approximately 152 by 114 by 44mm. This has a vinyl cover with a teak wood-grain finish which blends well with most hi-fi equipment. As can be seen from the photographs the two l.e.d.'s appear at the front panel, and their bushes are mounted in holes having their centres spaced by 1.3in. The l.e.d. lead-out wires are bent at right angles, so that when the l.e.d.'s are secured to the front panel the Veroboard panel is horizontal. The board is quite light, and the only support provided for it with the prototype was given by way of the l.e.d.'s in their panel-mounting bushes. Constructors who would prefer a further mounting point could initially employ a board with 25 strips by 28 holes, the 3 extra holes extending to the right of the board as it is shown in fig. 2. A third anchoring point could then be given by drilling a 6BA clear hole at the extreme right of strip "M", and then passing a 6BA bolt, with a suitable spacing washer, through a matching hole in the case bottom. A 6BA nut is then fitted on top of the board. It is most important that all parts of the monitor circuit be fully isolated from the metal case and three extra breaks in the strips, at holes "L25", "M25" and "N25" will also be needed.

Two 2-way DIN sockets, one for each channel, are used as input sockets, and these are mounted on the rear of the case.

CONNECTIONS AND ADJUSTMENTS

The unit is connected to the amplifier or the speakers by way of two suitable lengths of twin cable, with a 2-way DIN plug at the cable which connects to the monitor. The type of connector fitted at the other end of each cable must be chosen to suit the amplifier or speakers. Some amplifiers have outputs for two sets of speakers, and if the second pair of outputs is otherwise unused the monitor can be fed from these. On many amplifiers the outputs are taken from screw terminal using spade type connectors, and with these it is usually not difficult to take two connections from each terminal. It is quite common for loudspeakers to have provision for two methods of connection, and


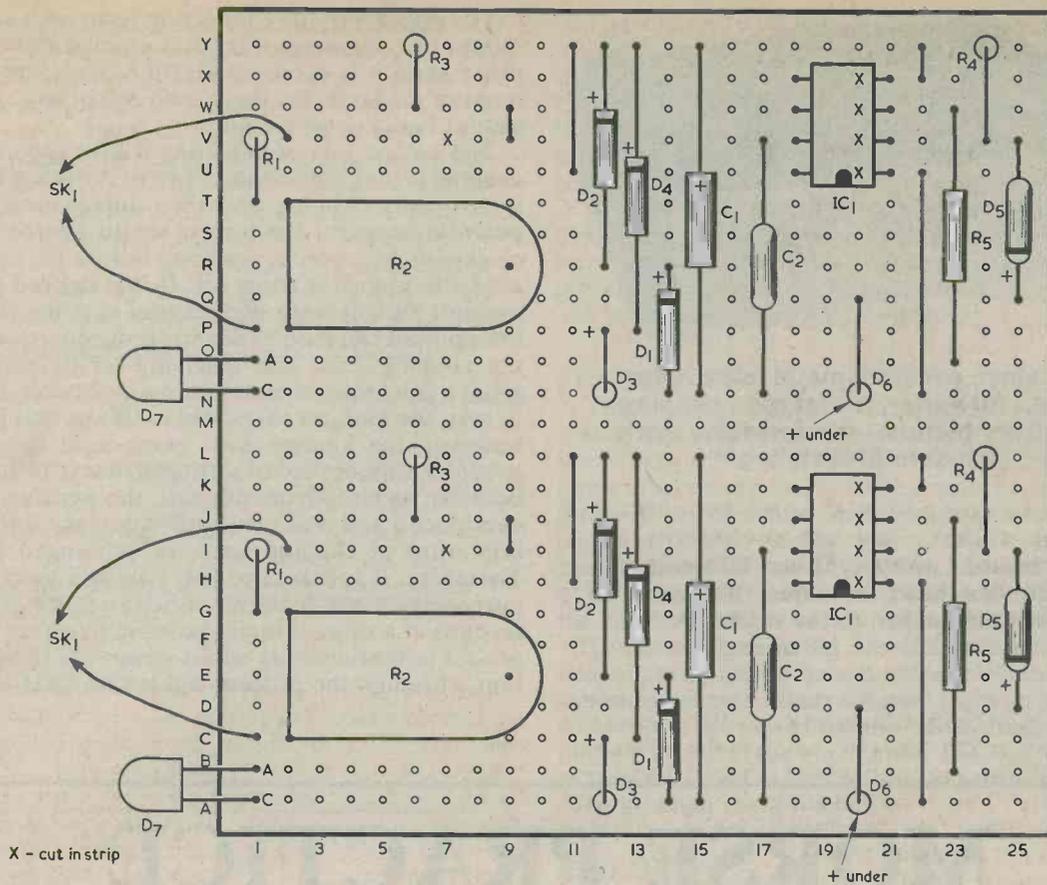


Fig. 2. The components for the two channels are assembled on a Veroboard panel with the layout shown here.

Close up view of the Veroboard assembly.

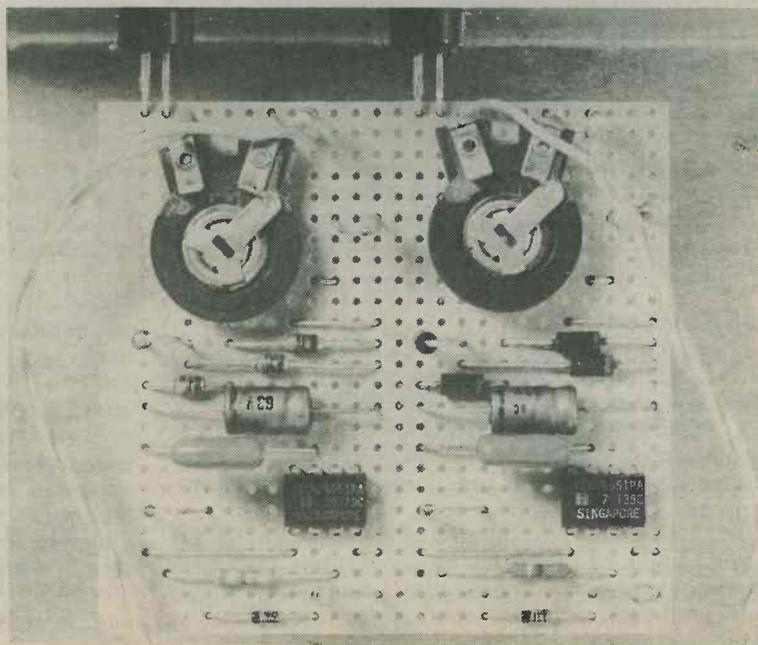



The vinyl covered metal case employed for the prototype clipping monitor blends comfortably with modern hi-fi styling.

they might be fitted with, say, 2-way DIN sockets and screw terminals. If, for example, the input to a speaker is normally taken to the screw terminals, an output for the monitor can be taken from the DIN socket. Finding suitable take-off points from the outputs for the monitor inputs is really a matter of initiative on the part of the constructor.

The polarity of the connection from each amplifier output to each monitor input is unimportant. On the other hand it is essential that the connections to the monitor are such that there is no risk of any amplifier output being short-circuited.

The easiest way of adjusting R2 for each monitor channel is to drive the amplifier to the point where it is obviously clipping and then adjust each pre-set potentiometer for the lowest sensitivity (as far in a clockwise direction as possible) before the appropriate l.e.d. indicator turns off. If it is desired that the monitor should warn of potential clipping the amplifier output can then be slightly reduced to just below the clipping level and each pre-set potentiometer given a final fine adjustment in a clockwise direction to take the monitor threshold to this output level. If, however, the loudspeakers being used incorporate tweeters, this method of setting up has to be modified because, as already mentioned, the tweeters can be overloaded and may even suffer damage if the amplifier runs at clipping level for prolonged periods. Therefore, if speakers of this type are used, do not purposely overdrive the amplifier for more than a few seconds at a time. It is still possible to set up the two pre-set potentiometers whilst observing this precaution, although the process will take a little longer.

MORSE PRACTICE BUZZER

By P. Fletcher

Schmitt NAND gate oscillator.

The circuit shown in Fig. 1 is for a morse code practice oscillator having a frequency of around 1kHz. It can of course function as an oscillator in other applications. Current consumption from the 9 volt battery is about 0.2mA when the key is up, and increases to about 1.7mA with the key down. The second current figure assumes that the headphones have a total resistance of 4,000Ω, i.e. 2,000Ω per phone. Headphones with a total resistance of 2,000Ω can also be used, with a corresponding increase in key-down current. Low resistance headphones should not be used.

OSCILLATOR

The circuit employs two gates of a quad 2-input NAND Schmitt trigger i.c. type 4093, and the oscillator itself is given by the gate associated with pins 1, 2 and 3. Schmitt trigger NAND oscillators are rarely encountered in the pages of this journal and a brief description of oscillator functioning will not, in consequence, be out of place here.

Fig. 2(a) shows pins 1 and 2 of the Schmitt NAND gate coupled to the slider of a potentiometer connected between the supply rails. A voltmeter, M1, is connected between the potentiometer slider and the negative rail, and a second voltmeter, M2, between

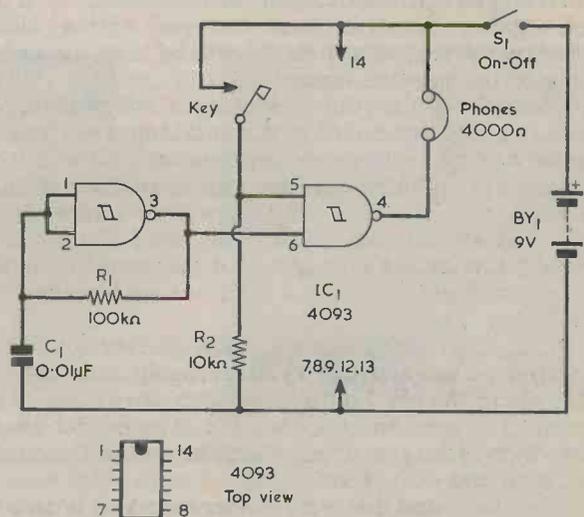


Fig. 1. The circuit of the morse practice oscillator. The headphones are high impedance magnetic types. The oscillator can, of course, be employed in other applications.

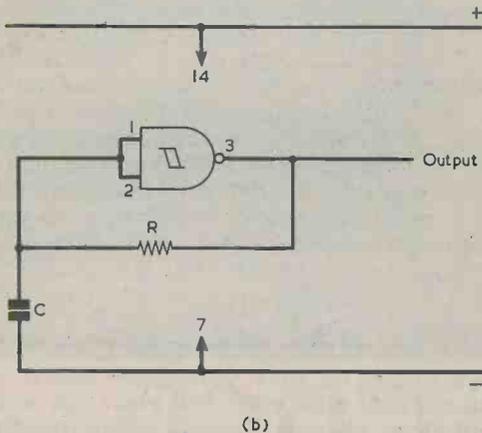
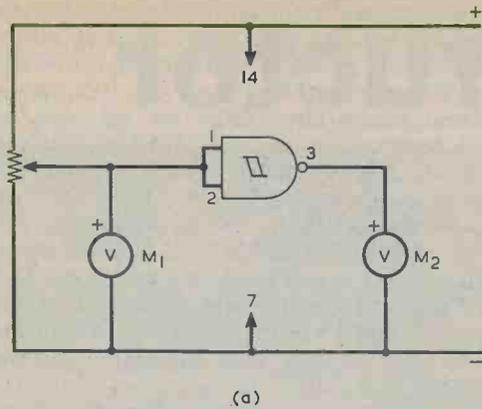


Fig. 2(a) Evaluating the transfer characteristic of the 4093 gate connected to pins 1, 2 and 3.
(b) Adding a resistor and a capacitor makes the gate an oscillator.

the pin 3 output and the negative rail. Since pins 1 and 2 are connected together, the NAND gate functions as an inverter. If the slider of the potentiometer is at the negative end of its track the pin 3 output, indicated by the second voltmeter, will be high, i.e. at or close to the positive supply rail.

The slider of the potentiometer is slowly advanced from the negative end of its track, taking pins 1 and 2 positive. At a certain gate input potential the pin 3 output will suddenly go low, i.e. at or close to the negative rail. This input voltage will be indicated by M1, and we will call it VA. The pin 3 output will remain low as the movement of the potentiometer slider continues, until it is fully at the positive end of the track.

If, next, we slowly take the potentiometer slider negative we will arrive at a voltage, again indicated by M1, where the pin 3 output suddenly goes high. This second voltage can be called VB. The output then stays high as the potentiometer slider continues to the negative end of its track.

It will be found that VB is lower than VA. With a 9 volt supply, VA can typically be of the order of 6 volts and VB of the order of 5 volts, so that there is a difference of about 1 volt between them. This represents the hysteresis effect associated with the classic Schmitt trigger.

In Fig. 2(b) we remove the meters and the potentiometer and add a resistor and capacitor as shown.

We now have an oscillator. At switch-on, the capacitor is discharged so that the gate inputs are low and the gate output is high. The capacitor commences to charge via the resistor until the voltage across it reaches VA, whereupon the pin 3 output suddenly goes low. The capacitor now discharges through the resistor until the voltage across it falls to VB. The pin 3 output then suddenly goes high again and the capacitor once more starts to charge. As a result, we have an oscillator with a near-square wave output at pin 3, and with the capacitor alternately charging to VA and then discharging to VB.

FREQUENCY

The length of the oscillator cycle is very approximately equal to the time constant of the resistor and the capacitor. In seconds, this is the product of resistance in megohms multiplied by capacitance in microfarads. The resistance and capacitance values in the oscillator circuit of Fig. 1 are 100kΩ and 0.01μF, giving a time constant of 0.001 second. The reciprocal of 0.001 is 1,000, and so the oscillator frequency is in the region of 1kHz.

The second gate in Fig. 1 is a buffer amplifier, and it is enabled when the key is closed. When the key is opened, the pin 5 input of the gate is taken low by R2, whereupon the pin 3 output is always high regardless of the voltage on the pin 6 input. The headphones are returned to the positive rail so that they consume no current when the key is up.

ASSEMBLY

There are two remaining gates in the 4093 and their inputs are all taken to the negative rail. Their outputs appear at pins 10 and 11, and no connections are made to these pins.

Pin 5 of the second gate is maintained at a fairly low impedance to the negative rail by R2 but, even so, care should be taken to see that the leads to the key are kept clear of high voltage wiring, such as mains leads. The only other precaution is to ensure that C1 and R1 are positioned fairly close to the i.c. pins to which they connect. As the 4093 is a CMOS device it must be wired into the circuit with a soldering iron having a properly earthed bit.

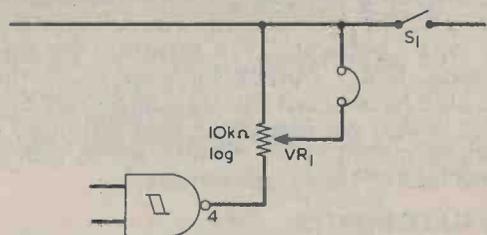


Fig. 3 A volume control can be incorporated between the pin 4 output and the positive rail.


The 1kHz output in the headphones is quite loud and, if desired, a volume control can be added. This simply consists of a 10kΩ log potentiometer, wired up as shown in Fig. 3.

The INSTRUCTOR

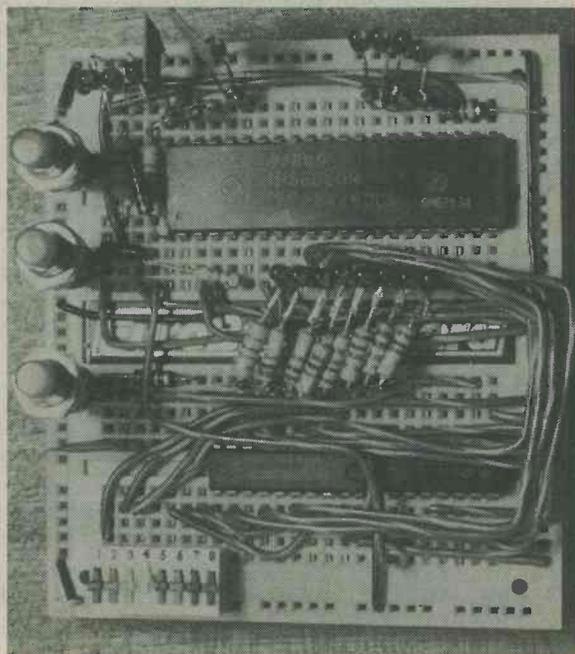Part 5

By Ian Sinclair

A PRACTICAL
INTRODUCTION
TO
MICROPROCESSORS




Universal Logic Operations

An important point about the microprocessor is that it can be used as a "universal logic chip". That needs a fairly detailed explanation. We can build logic circuits using gates and flip-flops to control machines, make calculations and add a form of intelligence (the ability to make decisions) to existing gadgets. These logic circuits can be replaced by a microprocessor system, provided that we can write a suitable program and have enough memory to store it. In other words, anything we can do with "hardware" – gates and flip-flops on a printed circuit board – we can do with "software" – a program for microprocessors. Every microprocessor must therefore be able to carry out the standard logic operations for which we use gates and flip-flops in a hard wired circuit. This month, we're going to look at a few of these operations.

LOGIC GATE INPUTS

Before we start, though, there's one important point. We're fairly accustomed to logic gates with two inputs, like the gates whose symbols are shown in Fig. 1. How do we represent these inputs on the eight data lines of the microprocessor?

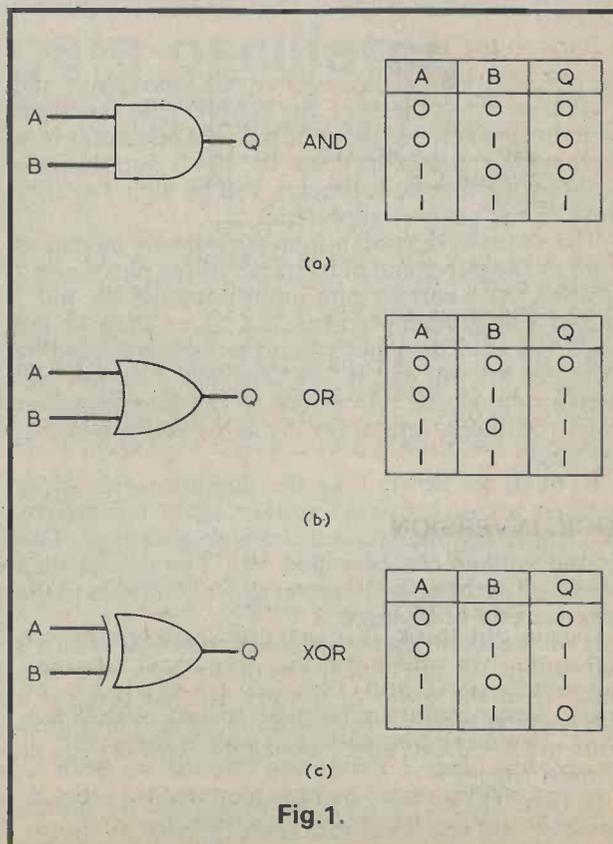The answer is that we use the microprocessor to provide us with eight separate gates, using each data line as a separate gate input. We then simulate the number of inputs to each gate by the number of times we carry out the logic action. Let's make that clearer by an example. Suppose



we want to instruct the microprocessor to "AND" three bits. We choose a data line for the bits, DO will do as an example. We feed in the first of the three bits into DO, using a load immediate, then follow this by an AND instruction, and then the second bit into DO. We then need another AND instruction, and the third bit into DO. When this is displayed, the bit at DO on the readout l.e.d.'s will be the AND of the three bits we have separately fed in. While we're doing this, we can AND seven more lots of bits on the other data lines as well.

Now we can try a two-byte AND. The program in Fig. 2 uses a LDI instruction to load in the byte 11001010, and follows up with AND-immediate (11010100) on the data byte 10111001. Now this isn't arithmetic - it's logical AND, so that there's no carry involved but just the AND-ing of corresponding bits. The law of ANDing is that 1 and 1 gives 1, any other combination gives zero. We can therefore expect the answer at DO to be 0, because the DO bits were 0 and 1 respectively, and so on for each bit separately. We can display the result in the usual way to check what has happened.

AND-ing is a very useful way of comparing patterns. Suppose, for example, you have a set of bits you want to recognise. This might be the correct combination to open a lock, a code for printing the letter B on a video screen, or anything. If you repeatedly AND an input byte with the one you want, the only time that the byte in the accumulator doesn't change is when it is AND-ed with an identical byte, and you can instruct the microprocessor to carry out some action (open the door, activate a character generator) when this happens. Since microprocessors operate fast, you can check a byte against several thousand others in a fraction of a second.

Back to the breadboard. The program in Fig. 3 carries out the OR operation on the two bytes 10011011 and 01000001. The law of the OR gate is that the output is 1 if either or both inputs are at 1, so we expect the answer 11011011.

The simple OR gives a 1 at the output when both inputs are 1, and this is sometimes not wanted. The exclusive OR (XOR) excludes this state and its truth table is as shown in Fig. 1(c). We can carry out XOR operations on bytes in the microprocessor and Fig. 4 shows a program for XOR-ing 10011001 with 11001100. Decide for yourself, using the truth table, what the result of this should be, and then try it out on the program. XOR-ing is very commonly used for pattern recognition, because if a byte is ZOR-ed with itself the result is zero.

LOGIC INVERSION

In quite a lot of logic circuits we find inversion useful, and we make use of NAND and NOR gates. These logic actions are not needed as often as we might think, it's just that these gates are convenient to make and use. For most logic circuits it's the AND and OR which are needed, but it is certainly useful to be able to get NAND and NOR. The NOT part of the action is inversion or complementing, so that we should be able to obtain a NAND result by complementing the output of an AND. The problem is, how do we do it?

```

RESET
LDI      11000100
BYTE    11001010
ANI      11010100
BYTE    10111001
DISPLAY

```

REMEMBER: The display routine consists of setting 11001000 and pressing GO twice. This displays the binary number in the accumulator.

Fig. 2.

```

RESET
LDI      11000100
BYTE    10011011
ORI      11011100
BYTE    01000001
DISPLAY

```

Fig. 3.

```

RESET
LDI      11000100
BYTE    10011001
XRI      11100100
BYTE    11001100
DISPLAY

```

Fig. 4.

Some Ways Of Using AND and XOR

Using XOR

Byte input 11011100
XRI with 11111111
produces 00100011 which is the complement of the first byte.

Using AND

Byte input 11011110
AND with 00001111
produces 00001110 so removing the upper part of the byte (called the upper nibble).

Using XOR

Byte input 10110011
XRI with 10110011
produces 00000000 this is a way of "recognising" a byte; any other input would leave a number in the accumulator.

Fig. 5.

```

RESET
LDI      11000100
BYTE1   11001010
ANI      11010100
BYTE2   10111001
XAE      00000001
CAE      01111000
DISPLAY

```

Fig. 6.

There's no obvious way, until you start to look at the action of the extension register, because the only complementing instructions are the complement and add ones. We can't get the result of an AND operation in the accumulator and then complement it – there's no instruction for doing this directly.

A suggested program is shown in Fig. 6. We reset, so making sure that the extension is reset, and then load in a set of bits to be NAND-ed. We then AND immediately with the other set of bits, so that the accumulator now contains the AND result. Following this with XAE causes the AND result to be loaded into the accumulator. Now if we use the instruction CAE (01111000) we can complement the number in the extension register, so producing the NAND, and add it to the number (which is zero) in the accumulator. We can display the result and satisfy ourselves that it is the result of a NAND.

Two points have to be watched carefully here. One is that the extension must be cleared before this program starts, because any number which is present in the extension register will be added in to the result at the CAE stage. We've cleared the extension by resetting before the start of the program, but at other times we might not be able to do this and we would have to clear the extension register by loading a byte of zeros into the accumulator and exchanging with the extension. The other point is that the final operation is a complement and add, so that the carry/link bit will be automatically added in. Once again this has not affected us, because we had reset, but in the middle of a long program we would need to clear the carry/link bit before starting the NAND operation. Now try for yourself to write and test a program to give the NOR operation, which is OR followed by NOT. If you're a glutton for punishment, you can follow that up by an XNOR, which is the XOR followed by NOT.

We've dealt now with all the immediate instructions, meaning all the double byte instructions which are followed immediately by the data to which they refer. That doesn't mean that we're finished with double byte instructions because there's quite a number of these we shall be returning to. Before we start on the single byte instructions, though, there's one unusual instruction, which as far as I know, is peculiar to the 8060. It's the DLY instruction, which simply lets the microprocessor tick away for some time before going to the next step. In other words, it introduces a time delay. On other microprocessors this has to be done by a procedure called a "counting loop". In a counting loop a number is

loaded into the accumulator and is decremented (meaning 1 is subtracted) on the next step. The number is then checked, and if it isn't zero it's decremented again and compared. This is done over and over again until zero is reached, then the microprocessor goes to the next program step. On the 8060, the DLY instruction does this for you. It's a double byte instruction, with the second byte measuring the amount of delay. The rules for finding the delay are a bit complicated (Fig. 7), but the important point is that the greater the size of the number which follows the DLY instruction, the longer is the delay before the microprocessor goes to the next step.

If the clock frequency crystal is controlled, we can use the delay for time measurement, producing time readings in hour, minutes and seconds, providing of course we have the memory and the program set up to do so. On our machine we can make use of DLY to measure the clock frequency, so providing the way to a useful method of measuring frequency without the use of an oscilloscope. The program is shown in Fig. 8. The DLY instruction is loaded and then the data switches set to 11111111, so as to load in the number 255 (unsigned numbers are used here) whenever the GO button is pressed. Now if we start a stopwatch at the instant when we press GO, or press GO just as the seconds indicator of a watch is at zero, we'll find that the address l.e.d.'s go out when the GO switch is pushed and don't come back on until the delay is finished. Stop the watch or note the number of seconds when this happens, and you have the total delay time. To find the frequency, divide 524332 by the delay time and the answer is frequency in Hertz!

The reasons are not too complicated. The 255 (decimal) byte causes a delay of 524332 clock cycles, and dividing this by the time taken gives the number of clock cycles per second, which equals frequency. If the clock is a fast one, of

Calculating the delay time for the INS8060: If (AC) is the number in the accumulator and (disp) is the displacement number (the second byte of the instruction) then the delay is:

$$13 + 2 \times (AC) + 2 \times (disp) + 512 \times (disp) \text{ microcycles.}$$

The time of a microcycle (the unit used by the microprocessor) is 4 clock cycles. If, for example, a 1MHz clock is used, the clock cycle time is 1 microsecond, and the microprocessor microcycle time is 4 microseconds.

Fig. 7.

```

RESET
DLY      10001111
Disp     11111111

```

Now find out how long it takes before the address l.e.d.'s come on again!

Fig. 8.

SINGLE-BYTE INSTRUCTIONS

| Mnemonic | Code | Meaning |
|----------|----------|--|
| LDE | 01000000 | Load accumulator from extension register |
| XAE | 00000001 | Exchange contents of accumulator and extension |
| ANE | 01010000 | AND extension with accumulator, result in accumulator |
| ORE | 01011000 | OR extension with accumulator, result in accumulator |
| XRE | 01100000 | XOR extension with accumulator, result in accumulator |
| DAE | 01101000 | Decimal-add extension to accumulator, result in accumulator |
| ADE | 01110000 | Binary-add extension to accumulator, result in accumulator |
| CAE | 01111000 | Complement-and-add extension to accumulator, result in accumulator |
| SIO | 00011001 | Serial input and output |
| SR | 00011100 | Shift contents of accumulator right one place |
| SRL | 00011101 | Shift right with link |
| RR | 00011110 | Rotate right |
| RRL | 00011111 | Rotate right with link |
| HALT | 00000000 | Pulses halt signal (no effect unless gating arranged) |
| CCL | 00000010 | Clear carry/link bit in status register |
| SCL | 00000011 | Set carry/link bit |
| DINT | 00000100 | Disable interrupt |
| IEN | 00000101 | Enable interrupt |
| CSA | 00000110 | Copy status register to accumulator |
| CAS | 00000111 | Copy accumulator to status register |
| NOP | 00001000 | No operation (used to leave spaces in a program so that additions can be made later) |

NOTE: Three sets of single-byte operations (pointer-register operations) have been omitted from this list – they will be dealt with later.

Fig. 9.

course, there may not be time to operate a stopwatch but for low frequencies it works quite well. We're not stuck with the frequency which the microprocessor generates for itself, either, because if we remove the oscillator components and connect XIN on the 8060 to the output of gate 3, then a frequency fed in at one input of gate 3 (with the other input connected to +5V) will clock the microprocessor. The 8060 is one of the few microprocessors which will operate at frequencies as low as 100Hz or so – and if you used the full delay at this frequency you would have to wait almost nine minutes! The upper limit is 4MHz, but at that frequency you couldn't time even a full delay with a stopwatch. In a microprocessor system with a memory this is easily solved by following one delay instruction with another. The delay is a favourite method of using the 8060 to generate musical notes. This is done by setting a bit in the status register to 1, delaying, setting the bit to zero, delaying, then starting over again. This sets and resets the bit at a rate decided by the delay, so generating a frequency which can be amplified and fed to a speaker.

THE CAS INSTRUCTION

Now to other matters. We have to start looking at some of the single byte instructions which we've neglected so far. Quite a few single byte-ers have appeared, and NOP, CAE, CCL and SCL have all been used in programs. Fig. 9 reminds

you of these. There's another, CAS, which is used to copy the byte in the accumulator into the status register without erasing the byte in the accumulator.

Now the CAS instruction is a particularly useful one, for reasons which you'll not appreciate unless you know several types of microprocessor i.c. fairly well. On a lot of microprocessors the only way you can get a useful output is by connecting up another i.c. to the data lines. The 8060 allows us to take three single bit outputs from the status register to pins labelled FLAG 0, FLAG 1, FLAG 2. these are, as you would expect, the bits at positions 0, 1 and 2 in the status register. If we want the voltage at the FLAG 0 pin to go to 1, we load the number 00000001 into the accumulator, and then follow with CAS, which copies this pattern into the status register, setting all the bits which can be set (see later on this one!) to zero, but bit 0 is set to 1.

Similarly, loading 00000010 will set bit 1, and 00000100 will set bit 2. Since there are three outputs, we can even switch eight circuits! How? The circuit of Fig. 10 shows how – the three flag outputs feed an octal counter, so that any combination of 1's and 0's on the flags produces a 1 on one of the counter output pins!

We can try out the flag operation by using our spare I.e.d. and the program in Fig. 11. Start by using the spare I.e.d. to monitor FLAG 0; this is done by linking B2 on the Eurobreadboard to B21.

STATUS REGISTER

Bit: 7 6 5 4 3 2 1 0
 Use: Carry/link Overflow SB SA IE F2 F1 F0

To set flags (example): LDI 0000101
 CSA (this sets flags 2 and 0)

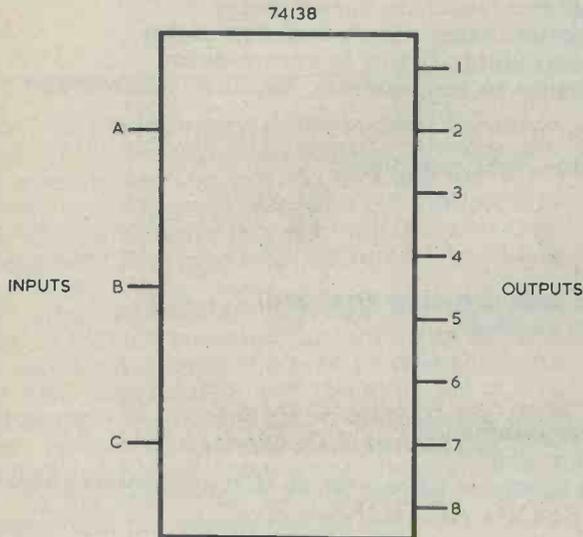


Fig. 10.

| | |
|-------|----------|
| RESET | |
| LDI | 11000100 |
| BYTE1 | 00000001 |
| CAS | 00000111 |
| LDI | 11000100 |
| BYTE2 | 00000010 |
| CAS | 00000111 |

(Use the spare l.e.d. to monitor the FLAG outputs.)

Fig. 11.

A long link wire can be used and it doesn't need to hug the board. Now load in the number 00000001 and follow up with CAS (00000111). The l.e.d. should light and stay lit. Unlike some outputs, which load for only one clock cycle, the bits of the status register are latched, so they'll stay at their 1 or 0 setting until the setting is changed. Now load in 00000010 and CAS again, as shown. The l.e.d. will go out, but when the far end of the link wire is moved from B2 (the FLAG 0 output) to A1 (the FLAG 1 output), the l.e.d. lights, showing that FLAG 0 has been reset to zero, and FLAG 1 set to 1. When 00000100 is loaded and CAS'd, then FLAG 1 will go out, but shifting the link to A2 will


show that the FLAG 2 output is at 1. Check for yourself that all three flag outputs are at 1 when the number 00001111 is loaded in and copied to the status register.

One instruction we'll spend no time over is HALT. This is a byte of zeros, and it doesn't stop the microprocessor working! What it does do is to cause a 1 to appear on the D7 line at a time when the microprocessor is neither reading nor writing memory. At the same time, a negative pulse appears on the pin marked NADS. If we gate and latch these two outputs, we can cause the microprocessor to halt when this instruction appears by wiring the latch to the CONT input. With CONT low the microprocessor stops without resetting any registers. With CONT taken high again the microprocessor starts operating once more. Few microprocessor units use the HALT instruction because, at the end of the program, the microprocessor has to be kept running in order to display the results.

Next month – Shifting, Rotating and Serial input/output.

(To be continued)

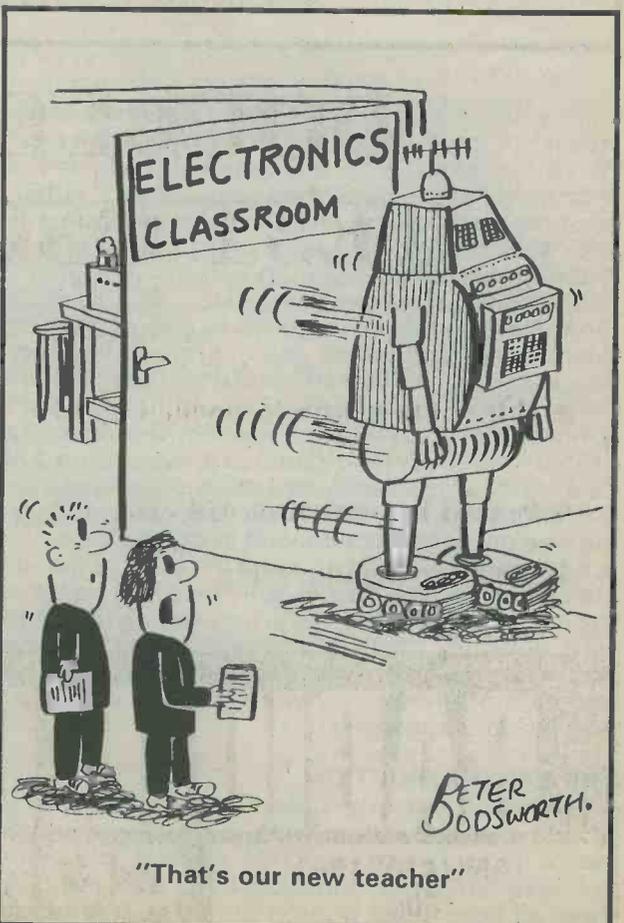
The previous series on Microprocessors by Ian Sinclair, Databus series 1-11, appeared in our issues August 1979 to July 1980. Copies are still available from our Back numbers Department.



"That's our new teacher"

IN OUR NEXT ISSUE


FUZZ BOX

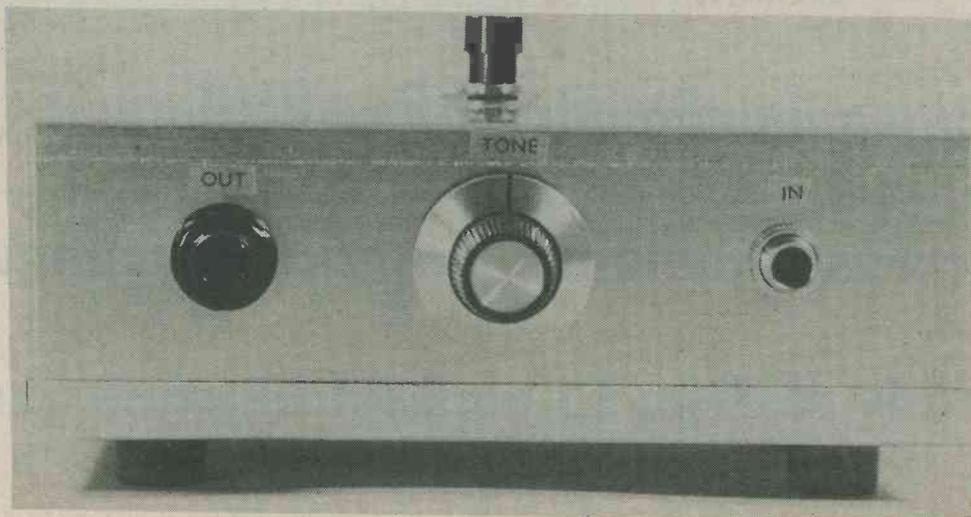

- ★ SILICON DIODE CLIPPING ACTION
- ★ VERY LOW NOISE LEVEL
- ★ VARIABLE OUTPUT FILTER

DOUBLE OUTPUT TEST OSCILLATOR

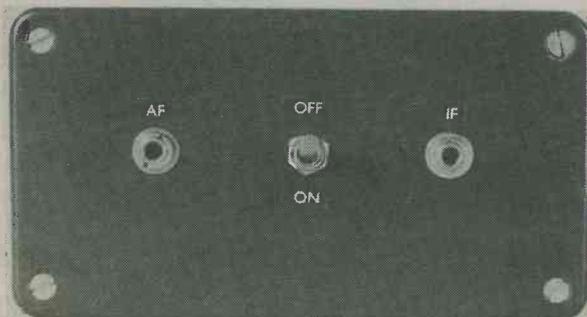- 1kHz output with harmonics up to several MHz
- Peaked i.f. output at 470 kHz
- Ideal for signal tracing



RADIO & ELECTRONICS
CONSTRUCTOR

JANUARY 1981
60p

OPTO COUPLED VOLUME EXPANDER


By R. A. Penfold

Increases dynamic programme range.

Adds realism to orchestral music.

Although a volume expander may be an unfamiliar item of equipment to many readers, it is by no means a new or even recent invention. The purpose of a volume expander is to increase the dynamic range (the difference between maximum and minimum signal levels) of a processed audio signal. In other words, an expander causes quiet passages to be made quieter and loud passages to be made louder.

This is not a gimmick but represents a serious attempt to compensate for loss of dynamic range during a recording or a transmitting process. The type of audio signal which suffers most, with which a volume expander offers its most useful effect, is classical orchestral music which, in its original form, can have a dynamic range of over 70dB. This dynamic range has to be reduced if the signal is to be recorded or transmitted in order that the quiet passages are adequately greater than noise level and the loud passages do not overload and cause distortion in the recording or transmitting channel. Popular recording and transmitting mediums can handle a dynamic range of about 60dB, and the range is only a little higher than 50dB for a good non-Dolbyised cassette.

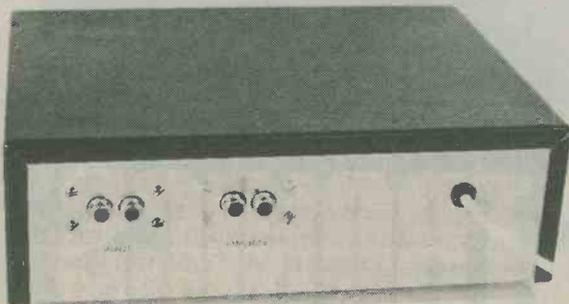


The rear panel of the expander. The input and outputs appear at dual phono sockets.

With a professional recording the reduction in dynamic range, or "compression", is provided manually by the recording engineer. For amateur recordings it is more usual for an automatic recording level circuit or an audio limiter to provide the compression. However skilfully or otherwise the compression is applied, the result must have an adverse effect on the signal because of the reduction in contrast between quiet parts of the performance and loud climaxes.

Volume expansion is the opposite of compression and enhances the level of loud musical passages. Noise level is at the original level with quiet passages and increases with loud passages but this is not noticeable because it is masked by the loud passages themselves. An effective increase in subjective signal-noise ratio results.

It must be stressed that a volume expander cannot restore the dynamic levels to precisely their original values as this would require an expansion law which exactly reciprocated the compression law. Since the latter is unknown and is probably different for each recording or transmission, an exactly correct expansion law is not practicable. However, even though an expander provides only approximate correction it can still give effective and acceptable results in practice. For best results it should give little or no expansion at low dynamic levels, and the expansion should be smoothly introduced and increased over the medium and high dynamic levels. Normally, the reproducing amplifier volume control is set to a lower level than would be appropriate for non-expanded music. As a result, the quieter passages are reproduced at a lower level whilst the expansion increases the volume of the louder passages.

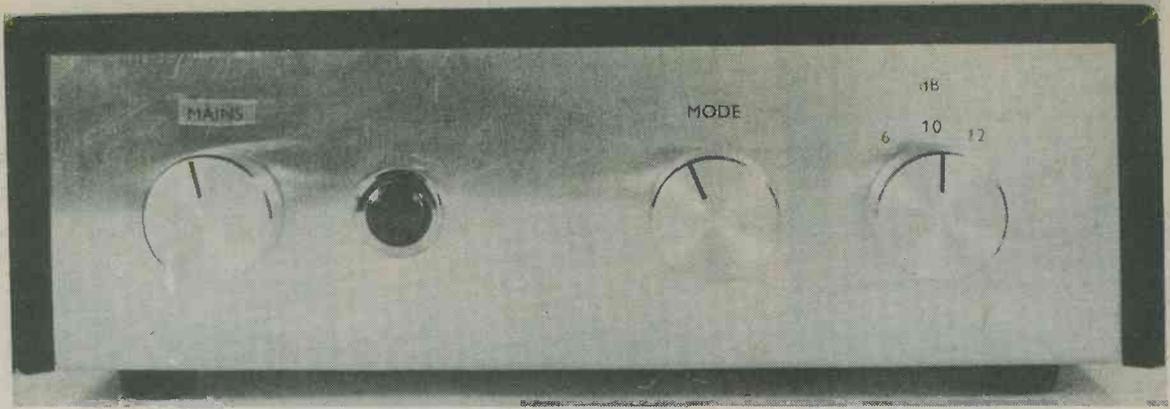The earliest form of volume expander, employed with valve amplifiers, merely consisted of a light bulb connected across the loudspeaker! The bulb filament had a low resistance with quiet passages because it was fairly cool, and the amplifier output was reduced because of the extra loading. At higher volume levels



The front panel layout of the volume expander. The mains on-off switch is to the left, with PL1 on its right. The remaining two controls are S1 and S2.

atched expansion selected 6dB, 10dB and 12dB.

the bulb's filament heated up and its resistance increased, resulting in reduced loading on the amplifier and an increased output. Such an arrangement could not be employed with modern transistor amplifiers, which have extremely low output impedances and with which the output voltage is only affected marginally by output loading. Also, in order to give truly acceptable results an expander needs to respond very rapidly to changes in dynamic level, and a light bulb type of expander tends to be too slow due to the thermal inertia of the filament.

VOLTAGE CONTROLLED AMPLIFIER

Somewhat more sophisticated circuitry is therefore required and the block diagram of Fig. 1 shows the arrangements employed in the expander described in this article.

The broken line in Fig. 1 encloses a voltage controlled amplifier or v.c.a. This incorporates an operational amplifier with the signal input applied via a cadmium sulphide photocell to its inverting input and with a feedback resistor, R1, from the output to the inverting input. The voltage gain of the amplifier is equal to R1 divided by the resistance of the photocell.

The input signal is also applied to an active rectifier followed by a buffer stage. The active rectifier both half-wave rectifies the signal and amplifies it, and the resultant d.c. signal is applied to the l.e.d. and its series resistor, R2. Under low signal conditions the l.e.d. will either fail to light or will glow very dimly. In either instance it will have no effect on the photocell resistance which, under these conditions, can be assumed to be approximately equal to the value of R1. (In the practical circuit the photocell is shunted by a resistor having the same value as R1.) The operational amplifier therefore has a voltage gain of approximate unity. Higher signal levels cause the l.e.d. to light up quite brightly, with a consequent decrease in photocell resistance and increase in

operational amplifier voltage gain. Thus, the gain of the v.c.a. is controlled by the voltage applied to the l.e.d. and R2.

As will be gathered, the increase in gain is dependent upon the input signal amplitude and so a full expansion effect is provided. Greatest expansion occurs when the buffer stage offers its full voltage output and this results in an operational amplifier gain of about 4 times. In consequence, the unit can give a maximum expansion of some 12dB, and this is about the highest level of expansion that can be usefully provided in practice.


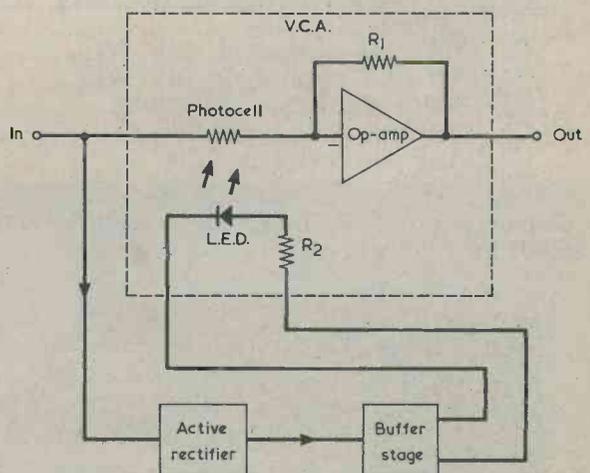


Fig. 1. Basic operation of the volume expander. The voltage gain of the op-amp is equal to R1 divided by the resistance of the photocell. When increased voltage is applied to the l.e.d. and R2, the l.e.d. glows more brightly and causes the resistance of the photocell to decrease.

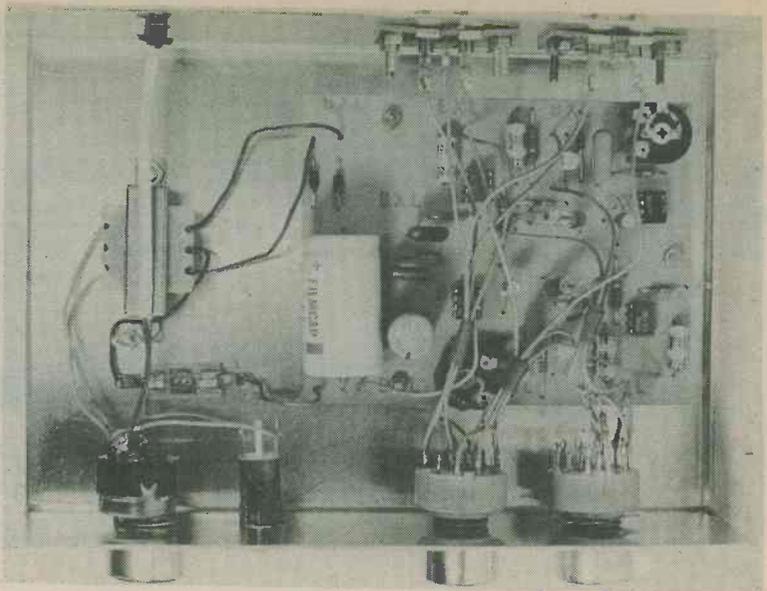The layout inside the metal instrument case.



COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

- R1 2-off 150 Ω
- R2 2-off 100k Ω pre-set potentiometer, 0.25 watt horizontal
- R3 2-off 180k Ω
- R4 2-off 18k Ω
- R5 2-off 47k Ω
- R6 2-off 120k Ω
- R7 2-off 22k Ω
- R8 2-off 22k Ω
- R9 2-off 120k Ω

Capacitors

- C1 2-off 0.22 μ F polyester, type C280
- C2 2-off 0.47 μ F electrolytic, 10V. Wkg. (see text)
- C3 2-off 10 μ F electrolytic, 10V. Wkg.
- C4 2-off 10 μ F electrolytic, 10V. Wkg.
- C5 1000 μ F electrolytic, 25V. Wkg.
- C6 0.1 μ F polyester, type C280
- C7 0.1 μ F polyester, type C280
- C8 100 μ F electrolytic, 25V. Wkg.

Semiconductors

- IC1 2-off CA3140E in 8 pin d.i.l.
- IC2 2-off 741C in 8 pin d.i.l.
- IC3 7812
- TR1 2-off BC108
- D1 2-off TIL220
- D2 1N4001
- D3 1N4001

Transformers

T1 mains transformer, secondary 12-0-12V. at 100mA

Photocell

PCC1 2-off ORP61

Switches

- S1 4-pole 3-way miniature rotary with adjustable end stop (set for 2-way)
- S2 4-pole 3-way miniature rotary (only 2 poles used)
- S3 d.p.s.t. rotary toggle

Fuse

FS1 100mA cartridge fuse, 20mm.

Neon

PL1 panel-mounting neon with integral series resistor

Sockets

- SK1 dual phono socket
- SK2 dual phono socket

Miscellaneous

Metal instrument case (see text)
 Chassis-mounting fuseholder, 20mm.
 3 control knobs
 Printed circuit board
 Nuts, bolts, wire, etc.

The volume expander should have a fast attack rate so that it responds quickly to rises in dynamic level, and a slightly slower (although still quite fast) decay time. A quick reduction in resistance and a slightly slower increase in resistance are innate characteristics of the cadmium sulphide photocell employed, and

these comfortably meet the attack and decay requirements. A simplification of the circuit results because there is then no need to incorporate timing components. A further advantage of the opto-coupled circuit is that it introduces negligibly low quantities of noise and distortion.

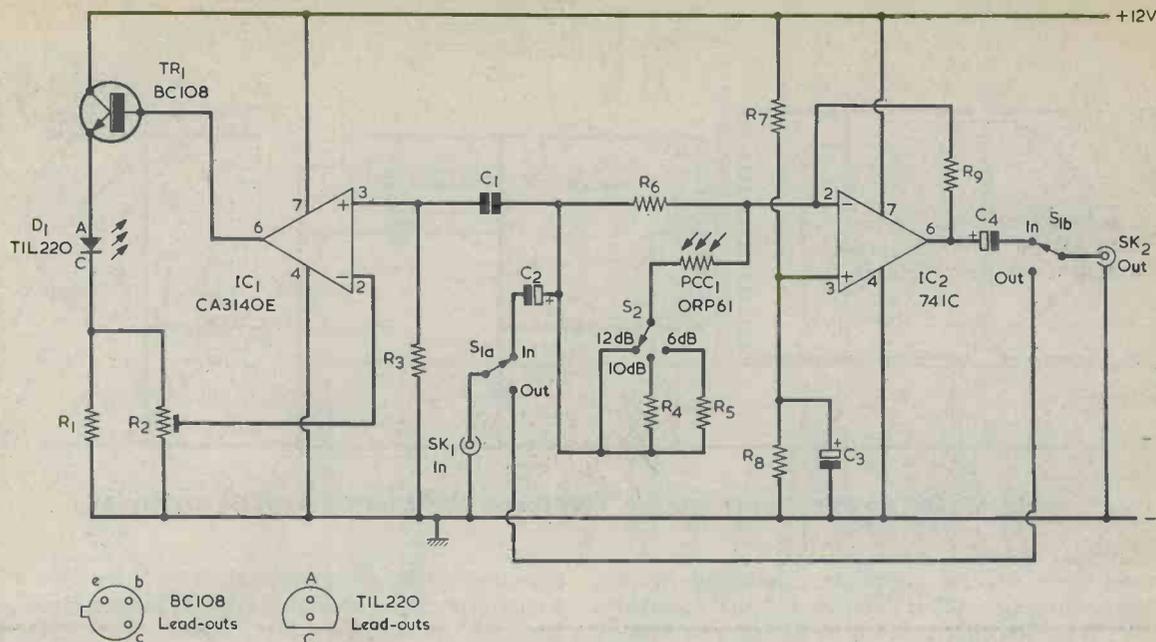


Fig. 2. The circuit for one channel of the volume expander. The other channel is identical.

THE CIRCUIT

The expander is intended to handle stereo signals and the circuit for one of the two channels is given in Fig. 2. It is normal practice for the two channels of the stereo signal to be processed separately.

IC2 is the inverting mode operational amplifier of Fig. 1 and its non-inverting input is biased to half the supply voltage by R7 and R8. C3 filters out any hum or noise which might otherwise be applied to the non-inverting input.

Under low signal conditions the photocell, PCC1, has a resistance of many megohms, whereupon the voltage gain of IC2 is determined by the equal value resistors R9 and R6. The voltage gain is therefore unity. At high signal levels the resistance of PCC1 falls to about 40kΩ, boosting the voltage gain in IC2 by about 4 times, or 12dB. The full level of expansion is not always required, and S2 can be adjusted to insert either R4 or R5 in series with PCC1, whereupon the boost is reduced to approximately 10dB or 6dB respectively.

C2 and C4 provide input and output d.c. blocking. S1(a)(b) can be set to bypass the expander, if desired, so that normal operation can be obtained without having to disconnect the expander from the hi-fi system.

IC1 is the active rectifier. The input signal is applied to its non-inverting input via C1, and this input is biased to the negative supply rail by R3. As a result, IC1 amplifies positive-going half-cycles only. The i.c. output connects to the emitter follower, TR1, which drives the l.e.d., D1. Negative feedback to the inverting input is obtained from the slider of R2. This feedback path is chosen because it is necessary to take the base of TR1 positive by about 2.2 volts to overcome the forward voltage drop in its base-emitter junction and the forward voltage drop in the l.e.d. if the latter is to light up. Low level input signals are

therefore given a high degree of amplification until the output of IC1 takes the base of TR1 up to the 2.2 volt level. The feedback circuit then takes over and limits the gain to a level dependent upon the setting of R2 slider. The circuit permits the illumination level in the l.e.d. to follow signal amplitude smoothly. If the negative feedback had been taken from the output of IC1, there would have been an abrupt signal level at which the l.e.d. commenced to light up.

The curve of Fig. 3 shows the expansion characteristic of the prototype with S2 in the "12dB" position. The precise characteristic obtained will, of course, vary slightly between different units, and it also varies considerably with different settings in R2.

The TIL220 employed for D1 is a red l.e.d. with a diameter of 0.2in. It is available from a number of suppliers. The ORP61 required for PCC1 can also be

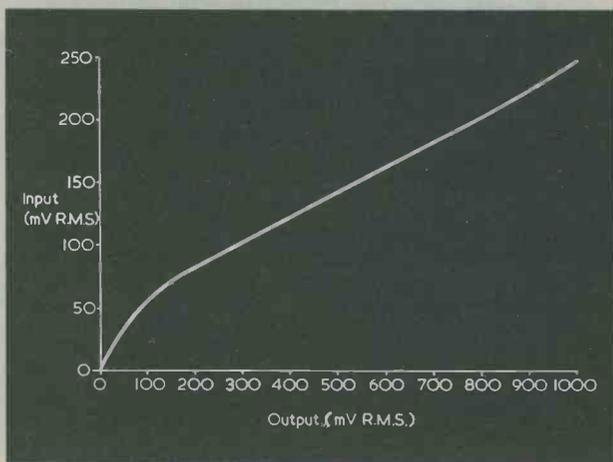


Fig. 3. Curve showing the expansion characteristics given by the prototype.

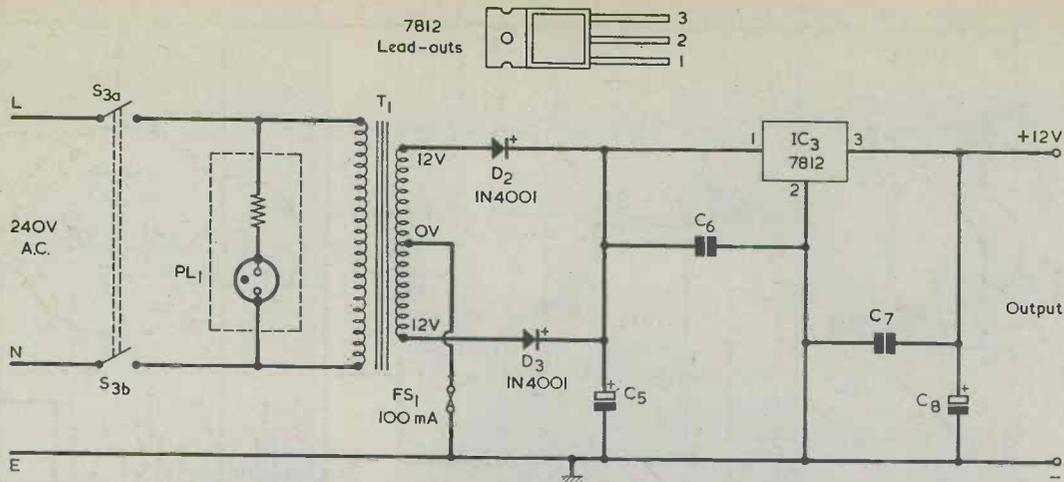


Fig. 4. The power supply section. This feeds both channels of the expander.

obtained from several suppliers, including Maplin Electronic Supplies. C2 is listed as 0.47 μ F electrolytic. 10V. Wkg. In practice it will be in order to employ a 0.47 μ F electrolytic capacitor having a much higher working voltage than this, even as high as 250 volts.

POWER SUPPLY

A well smoothed 12 volt supply is required, and the maximum mean current consumption is about 50mA. This is obtained with the regulated circuit of Fig. 4. The mains on-off switch is S3(a)(b) and PL1 is a panel-mounting neon indicator with integral series resistor intended for 240 volt a.c. operation.

The transformer secondary voltage is full-wave rectified by D2 and D3, with C5 providing a considerable amount of smoothing. Protection is provided by fuse FS1, which is rated at 100mA. Although there is an initial surge of current at switch-on as C5 charges, it was found with the prototype that a quickblow type of fuse was quite suitable and seemed to be perfectly capable of withstanding the surge. IC3 is a 12 volt voltage regulator which provides an extremely well smoothed output. C6 and C7 provide stability and ensure a good transient response, and C8 gives final smoothing of the output. IC3 does not require a heat sink in this circuit.

CONSTRUCTION


The author's unit was housed in a metal instrument

case measuring approximately 8 by 5½ by 2½in. This is a case type BC3, available from Harrison Bros., P.O. Box 55, Westcliff-on-Sea, Essex, SS0 7LQ. It is advisable to obtain the mains transformer, or at least ascertain its dimensions, before ordering the case, to ensure that it can be accommodated. The front panel layout can be seen in the photographs. S3 is mounted on the left, with PL1 to its right. Balancing these on the right are S1 and S2, with S2 being at the extreme right. On the rear panel are the two input sockets (one for each channel) and the two output sockets, with the input sockets on the left as seen looking at the rear panel. Dual phono sockets are used. A hole on the right hand side of the rear panel is fitted with a grommet and takes the 3-core mains cable. The cable must be secured inside the case by a suitable plastic or plastic-faced clamp.

The photograph of the interior shows the layout of components. The mains transformer and fuseholder are secured to the case bottom, with a solder tag under one of the mains transformer mounting nuts. If the transformer has tags on the top of its body, and if there is any risk of these closely approaching the inside surface of the case lid, a piece of thin s.r.b.p. should be glued to the inside of the lid at the appropriate position.

Fig. 5 shows the wiring inside the case. Except for the power supply components, there are 2-off of each

A view of the interior from the rear.

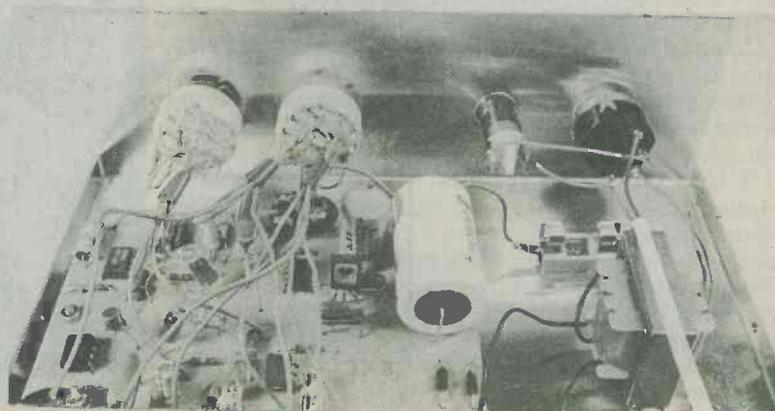

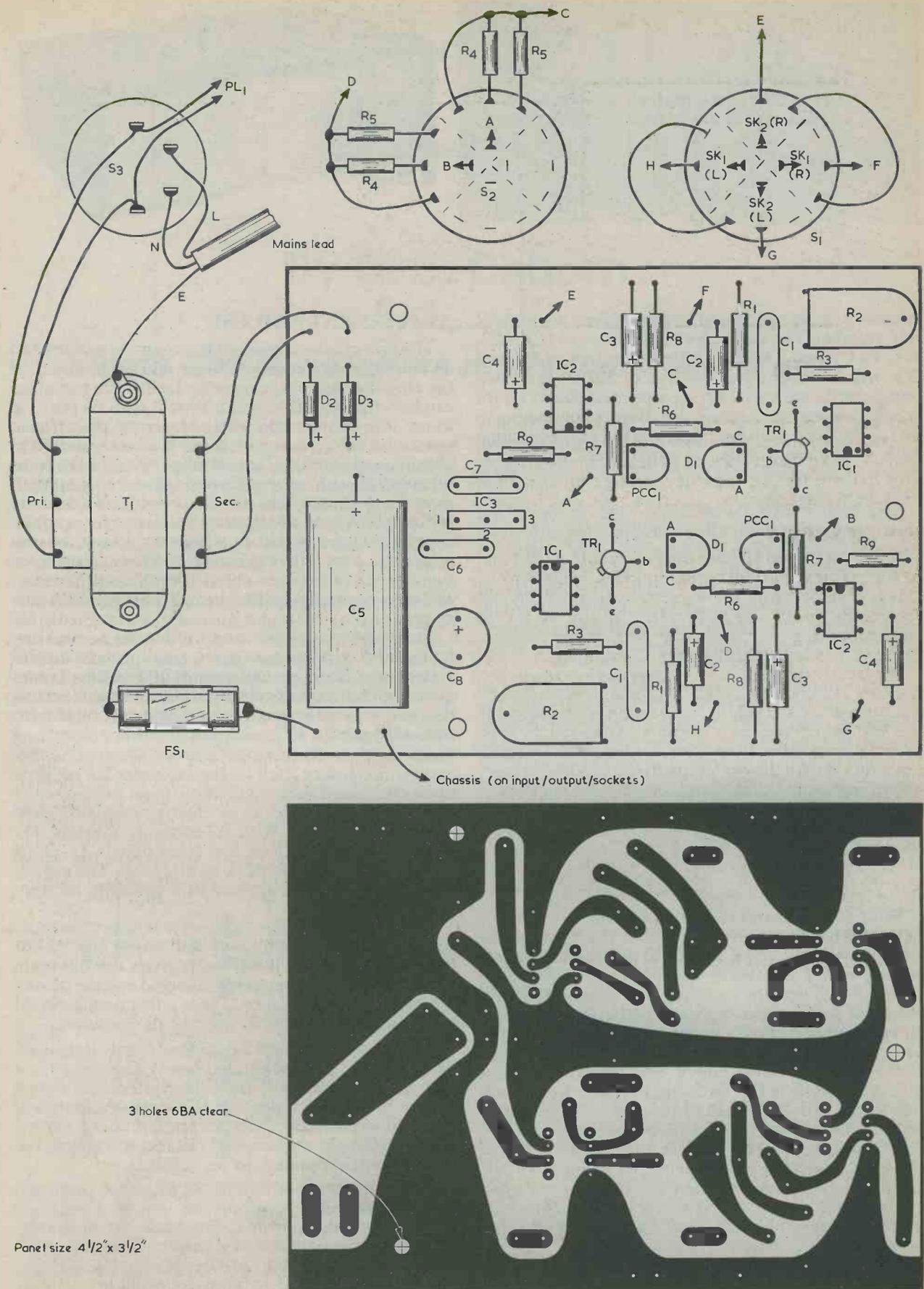


Fig. 5. Wiring up and details of the printed circuit board.

The ready-made instrument case ensures that mechanical construction requirements are kept to a minimum.



resistor and capacitor, and both are given the same R or C number. The same comment applies to IC1, IC2, D1, PCC1 and TR1. With the exception of R4 and R5, which are fitted at the tags of S2, all the small components are wired up on a printed circuit board which is reproduced actual size. Before connecting to any of the three switches, ascertain the tag positioning with a continuity tester or ohmmeter. With some switches the relative tag positioning may differ from that shown in Fig. 5.

The printed board is secured to the bottom of the case by means of three 6BA bolts and nuts with metal spacing washers. Two of these washers provide a chassis connection to the board. There is also a wired chassis connection from the board to the chassis tags on the input and output sockets. The board should not be finally mounted in place until all the connections from it to external components have been completed.

Components on the board which require special mention are the CA3140E i.c.'s, the l.e.d.'s and the photocells. The CA3140E has a PMOS input stage which is susceptible to damage by high static voltages. It should be kept in its protective packaging until it is to be wired into circuit and it should then be handled as little as possible. Preferably, the two CA3140E's should be the last items to be fitted to the board and they should be soldered into circuit with an iron having a reliably earthed bit. Alternatively, i.c. holders can be soldered to the board and the CA3140E's fitted into these afterwards.

With each pair of D1 and PCC1, the two components should be positioned so that the light output from the l.e.d. is aimed directly at the photo-sensitive surface of the photocell. The photocell has side-on illumination, and the sensitive side is indicated by a coloured dot on the component body. The photosensitive element is clearly visible above this, well to the top of the component. The l.e.d. has what is effectively a built-in lens, and it emits maximum light energy forward in the direction opposite to its lead-out wires. It is quite easy to position each l.e.d. and photocell at 45 degrees to the board surface, so that they are at right angles to each other with the end of the l.e.d. as close to the sensitive element of the photocell as is possible. Their alignment is not especially critical as the l.e.d. is a large component which gives a strong light output over a comparatively large area.

Unscreened wires connect the tags of S1 to the input and output sockets. These are designated "L" and "R" in Fig. 5. Connections may be made to the corresponding left and right sockets as seen looking at the rear of the case.

ADJUSTMENT AND USE

The unit can be connected between a tape deck and an amplifier, or between a tuner and an amplifier. If the amplifier has a tape monitor facility the expander can be wired into this, and it should then be possible to use it in conjunction with any normal programme source including a record deck. It is not possible to obtain good results by connecting the unit between a record deck with magnetic cartridge and an amplifier. Acceptable results here can only be given if a suitable pre-amplifier is used ahead of the expander, and the expander output is fed to a high level input on the amplifier. The unit works satisfactorily with input signal levels of between about 100mV and 1V r.m.s., and so is compatible with virtually any standard hi-fi system.

Empirical means are used to find the best setting for each R2. If the potentiometer is adjusted too far in a clockwise direction the gain of IC1 will be inadequate and full expansion will not be obtained. Setting the potentiometer too far anti-clockwise will give excessive gain in IC1, with full expansion occurring too abruptly and at too low a level. The first adjustment will manifest itself by the expander having little or no effect, and the second adjustment will cause the action of the expander to be clearly audible on most programme sources. With R2 correctly adjusted, D1 should light up dimly on low level signals, reaching full brightness only on peak level signals. The expansion should then be applied in a smooth and non-obvious manner.

When used in a stereo system it is best to initially connect up one channel only and adjust the R2 for that channel. When it has been given the optimum setting, the other channel is connected and the second R2 set for correct balance. These adjustments should be carried out with S2 in the "12dB" position.

The expander will not function correctly if the case lid is removed and the printed board is subjected to a high ambient light level, since the photocells will then be too brightly illuminated. However, the unit will work quite normally with the printed board shaded from bright light sources, and this fact will enable the two R2 potentiometers to be adjusted.

In use, the best position for S2 with each particular programme source can only be found by trial and error. It should be borne in mind that not all sources will benefit from the use of expansion, and that only a few really need the full 12dB expansion. Using excessive or unnecessary expansion can result in the music sounding unnatural. As was stated at the beginning of this article, the programme source most likely to benefit is classical orchestral music. ■

MULTI-OPTION CHIP

By R. J. Caborn

Single CMOS i.c. offers many logic functions.

When we deal with CMOS digital i.c.'s we expect a single device to offer exactly what it is designed to do. For instance a 4011 contains four 2-input NAND gates and that's all we anticipate finding in it. The only time we don't use the gates as NAND gates is when we connect their inputs together and use them as inverters. NAND gates are NAND gates, and that's that!

But there is one CMOS i.c. lurking in the lists which can provide a multiplicity of functions. It can be used as a triple inverter, it can be used as a single high current inverter, and it can be employed to drive separate loads from single f.e.t.'s inside the chip. Not only are these functions readily available but the chip will also act as a 3-input NOR gate or as a 3-input NAND gate. All these applications are available by simply choosing the requisite interconnections between the i.c. pins.

VERSATILE CHIP

The versatile chip with all these options is the 4007, and it has the internal circuitry shown in Fig. 1. Its official title is "Dual Complementary Pair Plus Inverter". The two complementary pairs are TRA, TRD and TRB, TRE. The inverter is given by TRC and TRF and employs normal CMOS operation. When the inverter input at pin 10 is high, i.e. close to or at the positive supply rail, TRC is turned off and TRF is turned on, resulting in a low output at pin 12. And when pin 10 is low, i.e. close to or at the negative rail, TRF is turned off and TRC is turned on, producing a high output at pin 12.

Whatever the function, pin 14 of the device always connects to VDD, the positive supply rail. Similarly, pin 7 always connects to the negative supply rail, or VSS.

TRA, TRB and TRC are P-channel f.e.t.'s, and TRD, TRE and TRF are N-channel f.e.t.'s. The thin line at the left of each f.e.t. symbol is the gate, and the centre of the three thick line rectangles is the f.e.t. substrate. As can be seen, all the P-channel substrates connect internally to pin 14, and all the N-channel substrates connect internally to pin 7. This is exactly what is required for correct f.e.t. functioning and from now on we can forget about the substrates, knowing that these are all properly connected, and concentrate on device functioning in terms of the remaining f.e.t. electrodes, the drains and the sources.

TRIPLE INVERTER

What is probably the most obvious application for the 4007 is to use it to give three inverters. One inverter, employing TRC and TRF, is already there. If we join together pins 13 and 8, TRA and TRD give us another inverter. Joining pins 1 and 5 produces a third inverter incorporating TRB and TRE. We also need to connect together pins 14, 2 and 11, to give a positive supply to all the inverters. And, finally, we have to join pins 7, 4 and 9 to provide the negative supply.

All these interconnections are illustrated in Fig. 2, with the interconnected pin numbers being shown in brackets. To use the first inverter we apply an input at pin 6 and obtain an output at either pin 13 or pin 8. The second inverter takes an input at pin 3 and gives an output at pin 1 or pin 5.


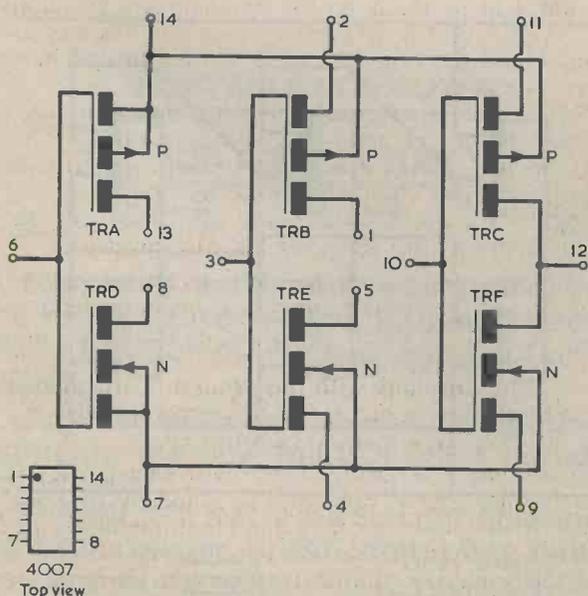


Fig. 1. The internal circuitry of the CMOS 4007 Dual Complementary Pair Plus Inverter i.c.

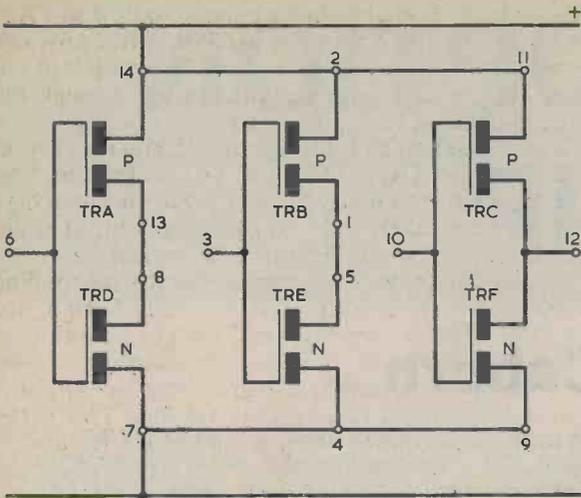


(14-2-11)(13-8)
(1-5)(7-4-9)

Fig. 2. Connecting the 4007 pins together in the manner shown here results in a triple inverter circuit.

The output impedance for each inverter, in either the high or low state, is 500Ω typical with a supply of 10 volts. So, if we draw from any output a current of 2mA (which is a reasonable current near the maximum for a digital CMOS output) the voltage dropped in the i.c. will be about 1 volt.

Connecting the 4007 as in Fig. 3 provides a single super-current inverter. All three inverter inputs are connected together, as are all three inverter outputs. An input at pin 6 produces an inverted output at pin 12. The output impedance is now in the order of one-third of 500Ω, and we can expect to draw output currents up to 6mA for a voltage drop in the i.c. of 1 volt. It is quite in order to connect the inverter outputs together in this manner, and the circuit of Fig. 3 has the blessing of the i.c. manufacturer.

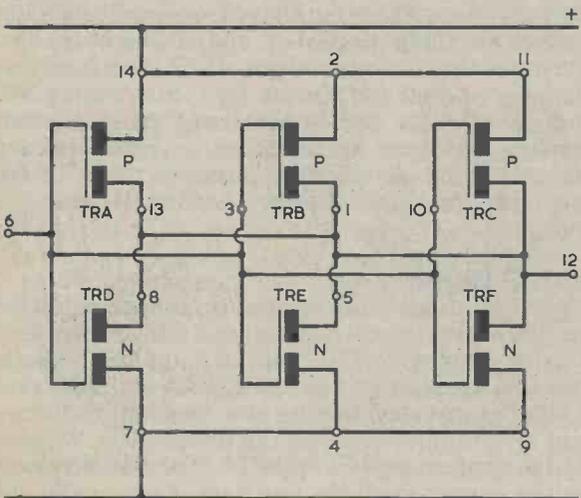

(14-2-11)
(13-8-1-5-12)
(6-3-10)
(7-4-9)

Fig. 3. With the three inverters in parallel, a single inverter with a high output current capability is produced.

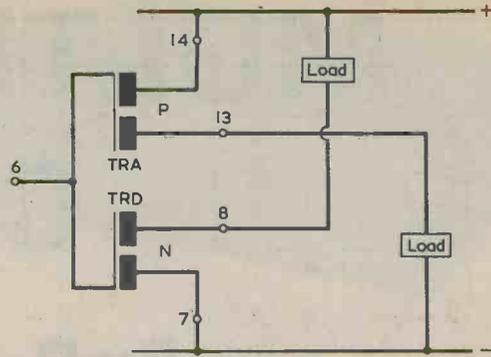


Fig. 4. The open-ended outputs of the 4007 can be used to drive separate loads in the manner shown here.


OPEN-ENDED OUTPUTS

Open-ended f.e.t. outputs are available at pins 13, 8, 1 and 15, and we can use these outputs in the manner illustrated in Fig. 4. If, in this example, pin 6 is taken high TRD is turned on, and it will drive a load connected between pin 8 and the positive rail. Taking pin 6 low causes TRD to turn off, and no current flows through the load.

At the same time, taking pin 6 low turns on TRA, and this can then cause current to pass through quite a separate load connected between pin 13 and the negative rail. The load current ceases when pin 6 is taken high.

NOR GATE

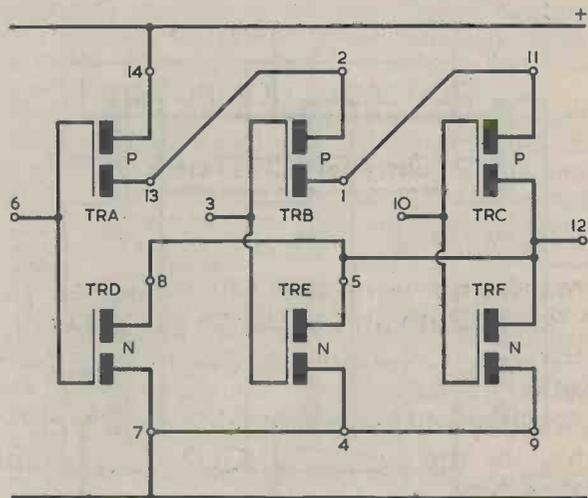
An application which may not be so obvious at first sight of the i.c. circuitry is shown in Fig. 5. Here, the 4007 is connected to function as a 3-input NOR gate. Examination of the diagram shows that the drains and sources of TRA, TRB and TRC are connected in



(13-2) (1-11)
(8-5-12) (7-4-9)



Fig. 5. The interconnections illustrated in this circuit allow the 4007 to function as a 3-input NOR gate.

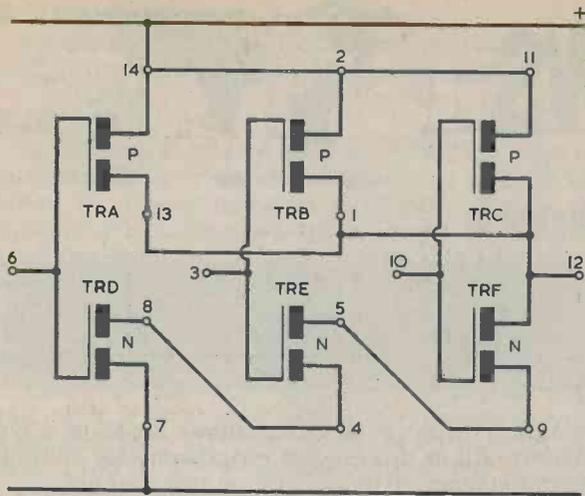

(14-2-11) (3-1-12)
(8-4) (5-9)



Fig. 6. Another configuration for the multi-option 4007. This time it operates as a 3-input NAND gate.

series between the positive supply input at pin 14 and the output at pin 12. At the same time the drains and sources of TRD, TRE and TRF are all connected in parallel. The three NOR gate inputs are at pins 6, 3 and 10.

Let's see what happens if we take all the input pins low. First, TRD, TRE and TRF are all turned off.

TRA is turned on and allows current to flow to TRB, which is also turned on. In its turn, TRB provides current for TRC, again turned on. The output at pin 12 is high, with output current passing through the three P-channel f.e.t.'s in series.

If pin 6 is taken high TRA turns off, and the current chain through TRA, TRB and TRC is broken. The current chain is similarly broken if pin 3 is taken high or if pin 10 is taken high. To get a high output at pin 12, all three of the P-channel f.e.t.'s *must* be on.

Taking an input high causes the corresponding N-channel f.e.t. to turn on. With pin 6 high, for instance, TRD is turned on and the pin 12 output is low. So, the NOR gate output is low if any one or two, or all three of the inputs is high. The gate output is high only when all three inputs are low. This is the performance required from a 3-input NOR gate.

NAND GATE

The interconnections shown in Fig. 6 result in a 3-input NAND gate. Fig. 6 is really the NOR gate of Fig. 5 turned upside-down. This time it is TRD, TRE and TRF which are connected in series, with TRA, TRB and TRC in parallel.

The output is low only when all three inputs are high, so that TRD, TRE and TRF are all turned on. The output at pin 12 is high for all the other input combinations, given by one input low, two inputs low or all inputs low. A fully serviceable NAND gate results.

The 4007 doesn't seem to have received the attention in the constructional press which it fairly deserves. As you can see, it is an exceptionally versatile chip and is capable of carrying out many more different tasks in logic than can its fixed-purpose partners in the current CMOS listings. ■

TRADE NOTE

PORTABLE COMPUTER

FOR AGRICULTURE

A marketing agreement was signed at the Royal Bath and West Show between Microdata Computers and Agriday Computers.

Agriday will have exclusive distribution rights for the new MICROLINK 1 portable computer system within the agricultural community.

The MICROLINK is the first portable computer to include a keyboard, plasma display, acoustic coupler, BASIC interpreter, bubble memory, real time clock and text processor, and is manufactured in Hayes, Middlesex.

In addition to the agricultural software to be supplied by Agriday, programme packages will be available to meet the needs of accountants, engineers, stocktakers, insurance brokers and salesmen.



SHORT WAVE NEWS

FOR DX LISTENERS



By Frank A. Baldwin

Times = GMT

Frequencies = kHz

The items presented here are for the general guidance of readers who wish to tune over the short wave bands, some of the loggings will interest the short wave listener whilst others may catch the attention of the Dixer. All details are correct at the time of writing.

● PAKISTAN

Radio Pakistan on **17910** at 1548, local-style songs and music in the "World Service" programme in Urdu intended for the Middle East and the Persian Gulf areas, scheduled from 1330 to 1600. A newscast read at slow speed in English followed at 1600, this for the Middle East and East Africa.

● VIETNAM

Hanoi on a measured **15009.5** at 2120, a programme all about life in Hanoi now that peace reigns, in the English transmission directed to Europe, scheduled from 2030 to 2130.

● JAPAN

Tokyo on **21610** at 0800, station identification, time and frequency details followed by a newscast of local affairs – all in the English programme for Europe, scheduled from 0800 to 0830. Also logged in parallel on **17855**.

● NORTH KOREA - 1

Radio Pyongyang on **11350** at 1315, music and songs in the Korean Domestic Service, scheduled here from 2000 to 0300, 0400 to 0900 and from 1500 to 1800.

● PORTUGAL

Radio Renascenca on **9670** at 1504, station identification and announcements in Portuguese to Europe, scheduled from 1500 to 1530 – a relay from Radio Trans Europe, Sines, Portugal for Portuguese Catholics away from home.

● CANADA

RCI (Radio Canada International), Montreal, on **5995** at 2029, YL (Young Lady = female announcer) with station identification and programme details at the end of the English programme for Africa and Europe, scheduled from 2000 to 2030. Into the French programme at 2023. All this from the BBC relay station at Daventry.

● PORTUGAL

Lisbon on **6025** at 2040, YL with a newscast of both local and world events, followed by station identification. This was followed by OM (Old Man = male

announcer) with the Dx programme for short wave listeners. All in the English programme for Europe scheduled from 2030 to 2100 on this channel.

● SEYCHELLES

FEBA (Far East Broadcasting Association), Mahe, on **11860** at 1638, chimes interval signal, OM with station identification as "Halkani wa FEBA Seychelles" – at least according to my tape recorder!

● AUSTRALIA

Melbourne on **6035** at 1700, OM with station identification and a newscast of world events in English.

Melbourne on **9570** at 0804, OM with both world and local newscast, this transmission in English to Asia.

Melbourne on **11865** at 1635, OM with local weather forecasts in an English programme directed to Asia.

Melbourne on **21570** at 0805, OM with news report in English, followed by a review of Australian business affairs.

● FINLAND

Helsinki on **6120** at 2135, OM with the English programmed "Northern Report" in a transmission to Europe, North West Africa and South America, scheduled from 2130 to 2200. "Compass North" commenced at 2140.

● CLANDESTINE

A Voz de Verdade on **4950** at 1820, OM with a tirade in Portuguese about Angola and UNITA. This is a pro-UNITA transmitter broadcasting to Angola.

● NAMIBIA

Windhoek on **4965** at 1721, OM in vernacular. This is a new transmitter which commenced operations in early October. The evening transmission on this channel is scheduled from 1515 to 2200.

● EQUATORIAL GUINEA

Radio Ecuatorial, Bata, on **4925** at 2020, a programme of local songs and music in typical style. This one seems to have abandoned **5005** for the time being.

Malabo on **6250** at 2022, YL with announcements in Spanish, short excerpts of classical music.

● KENYA

Nairobi on a measured **4934** at 0314, YL with announcements in vernacular, African drums. This is the North Eastern Service operating from 0250 to 0630 and from 1400 to 2015. The power is 100kW.

● **SIERRA LEONE**

Freetown on **5980** at 2225, local pops on records, OM in vernacular, just audible under QRM.

● **UGANDA**

Soroti on a measured **5027** at 1928, U.K. pops on records, OM with station identification at 1933 followed by a local newscast in English. This is the National Programme in English, French and Swahili, operating from (weekdays) 1300 to 2100; Saturdays and Sundays from 0300 to 0545 and from 1400 to 2100 (Sundays from 1430). The power is 250kW.

● **ZIMBABWE**

Gwelo on **3396** at 1735, OM in vernacular, songs and music in local style. This is the General Service, scheduled from 0350 (Sundays 0500) to 0545 and from 1500 to 2200 (Sundays 2105). The power is 100kW but it operates on 10kW only from 0545 to 0615, additional to the foregoing schedule.

● **CHINA**

CPBS Peking on **4905** at 2035, YL announcer, Chinese classical music in the Domestic Service 1 programme, operating from 2000 to 2300 and from 1100 to 1735. Also logged in parallel on **7504**.

Radio Peking on **7035** at 2050, Chinese music in the Standard Chinese programme intended for Europe and North Africa, scheduled here from 2000 to 2100.

Wuhan, Hypeh, on **3940** at 2150, OM and YL in Chinese, orchestral music local style. Schedule is from 2100 to 0100 and from 0300 to 1605.

Hohhot, Neimenggu, on **4000** at 2153, Chinese classical music. The schedule is from 2145 to 0555 and from 0900 to 1520.

Lanzhou, Gansu, on **4865** at 2211, OM with a talk in Chinese, The schedule is from 2145 to 0100 (Sundays to 0600), from 0320 to 0600 and from 1000 to 1600.

Nanning, Guangxi, on **5010** at 2215, YL announcer, Chinese music. This is Guangxi 2 operating from 2115 to 2200 and from 0950 to 1530.

Harbin, Heilongjiang, on **4840** at 2052, YL in Chinese with short periods of Chinese classical music. This one operates in Chinese from 2040 to 0630 and from 0830 to 1530, except in Korean from 0300 to 0400 and an English language lesson from 2130 to 2200.

● **MALAYSIA**

Kuala Lumpur on **4845** at 2257, OM and YL with songs, Indian-type music in the Tamil programme. The schedule is from 2130 to 0130 and from 1545 to 1530 Monday to Friday, from 2130 to 0330 and from 0545 to 1530 on Saturdays (2130 to 1530 on Sundays). The power is 50kW.

● **NORTH KOREA - 2**

Radio Pyongyang on **4770** at 2208, OM and YL in Korean in the Home Service 2, operating on this channel from 2200 to 2230 and from 1000 to 1045 irregularly. The power is 120kW but the channel suffers from QRM.

● **MONGOLIA**

Ulan Bator on **4830** at 2202, four-note tuning signal repeated several times, National Anthem, OM and YL in Mongolian. This is the Home Service, scheduled from 2200 to 0100 and from 1030 to 1500.

The power is not known.

● **SRI LANKA**

Colombo on **4902** at 1829, religious chants on full moon day. This is the Home Service 1 in Sinhala, timed from 0000 to 0230 and from 1000 to 1745. On full moon days additionally from 1600 to 2400.

● **COLOMBIA**

La Voz del Cinaruco, Arauca, on **4865** at 0010, OM with newscast of local events in Spanish (the language not the events!). Many mentions of Colombian place-names. This one operates from 0900 to 0330 and the power is 1kW.

La Voz del Norte, Cucuta, on **4875** at 0505, OM with the local news. Still there at 0526 retune but this time with a political harangue, complete with cheers and jeers of the audience! The schedule is 0930 to 0500 but has been reported closing as late as 0630 on occasions. The power is 5kW.

● **ECUADOR**

Radio Popular Independients, Cuenca, on a measured **4801.5** at 0447, OM with announcements in Spanish, YL With folk songs. The schedule is from 1000 to 0530 but the frequency can vary from **4800** to **4802**. It also identifies sometimes as "Radio Amiga Popular de Cuenca". The power is 2kW and this one is heard only after Radio Lara, Barquisimeto, Venezuela closes at 0400.

La Voz de los Caras, Bahia de Caragues, on **4795** at 0420 the usual mix of local music and songs. OM with clear and full identification at 0434. The schedule is from 1100 to 0430 and the power is 3kW.

Radio Nacional Espejo, Quito, on a measured **4679.4** at 0438, OM with song in Spanish, local-style pops. The schedule is form 0800 to 0600 but sometimes around the clock and the power is 5kW.

● **BOLIVIA**

Radio Cobija, Cobija, on **4855** at 0406, OM with a political talk in Spanish. Local music and songs from 0430 after clear station identifications at 0415 and 0418. Gone at 0500 retune. This one operates irregularly from 1000 to 0300 and is seldom reported in the SWL press. The power is 1kW.

Radio Difusora Christal, La Paz, on a measured **5006** at 0024, choral folk song, OM with announcements in Spanish. Tentative logging - no identification heard despite several later observations.



"K" TONE GENERATOR

By
Trevor P. Hopkins



The author's "K" tone generator. Screening is desirable, and all the components are housed in a metal case.

Automatic logic sends a morse "K" at each over

When working s.s.b. Dx, on both the h.f. and v.h.f. bands, it is often very difficult to determine exactly when the other station's over has been completed. This point is especially true when the signal is very weak or during contest operation.


One technique to overcome this problem is to use a "pip"-tone generator which produces a short tone every time the Push-To-Talk (P.T.T.) switch is released. However, this can occasionally be confusing and a better method is to send a "K" in morse code (dah-di-dah) at the end of each over. The letter "K" is usually used during c.w. operation to mean "Invitation to transmit". The device to be described will provide this "K" function and is easily connected in the microphone lead of most transceivers.


CIRCUIT OPERATION

The complete circuit of the "K" tone generator is given in the accompanying diagram. Assuming that the function switch, S3(a) (b), is in the "Automatic" position, the following sequence takes place. When the P.T.T. switch is closed, a logic "0" is applied to pins 1, 2 and 5 of IC1. The output of IC1(b) then turns on transistor TR2, which energises a miniature reed relay RLA. Contacts RLA1 close the original P.T.T. line, so that the transceiver goes into the transmit mode. LED2 lights up to indicate this state.





When the P.T.T. switch is released, pin 3 of IC1(a) reverts from logic "1" to logic *0*. The negative-going edge is differentiated by C2 and R3, and the resulting negative pulse triggers the latch consisting

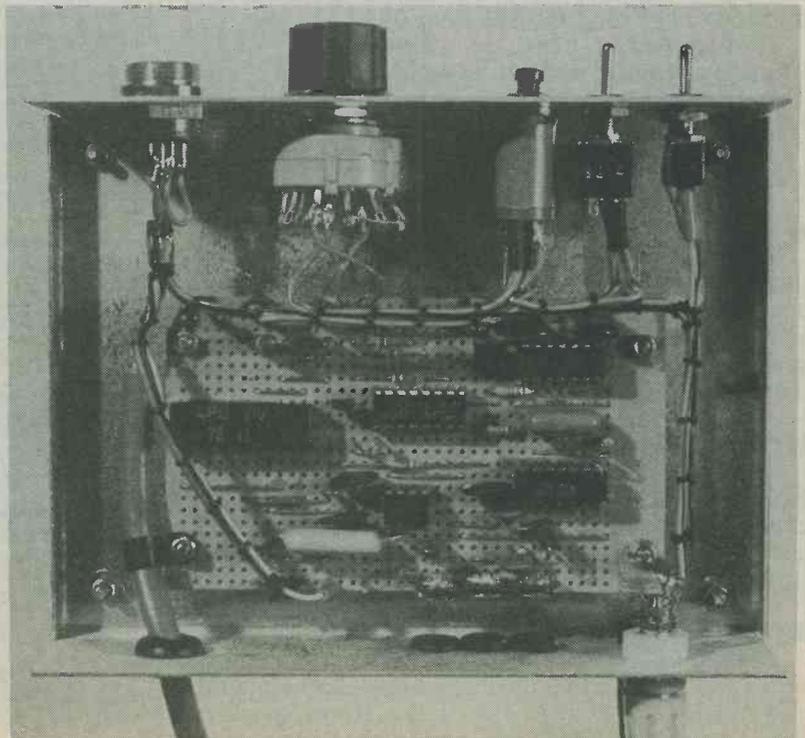The method employed for assembly is left to the constructor. Most of the components in the prototype generator are wired up on a Veroboard panel.




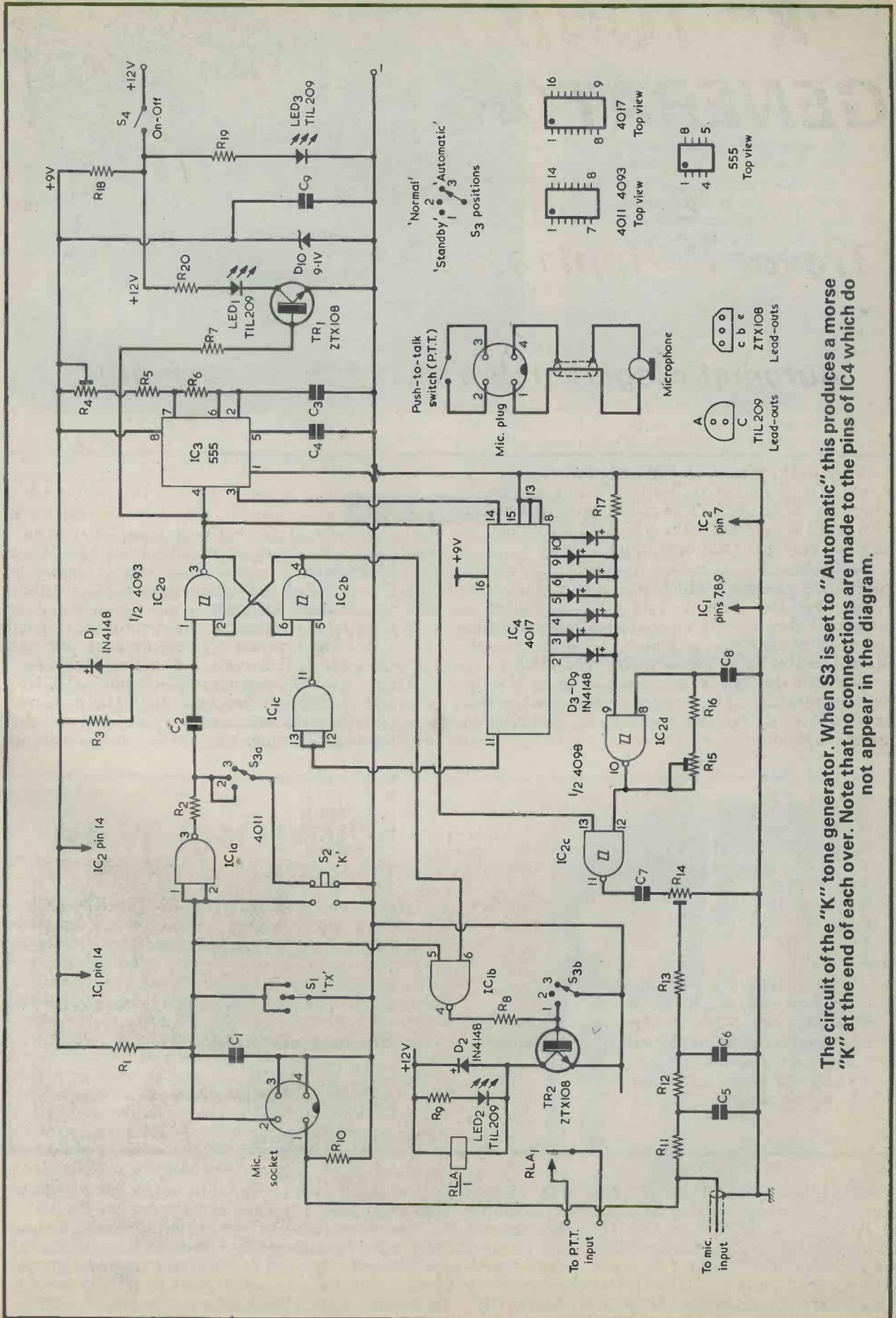

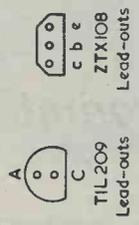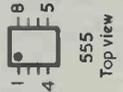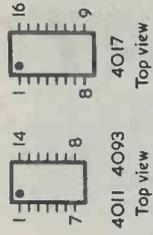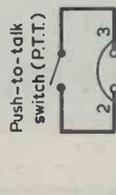'Normal' 1
'Standby' 2
'Automatic' 3
S3 positions



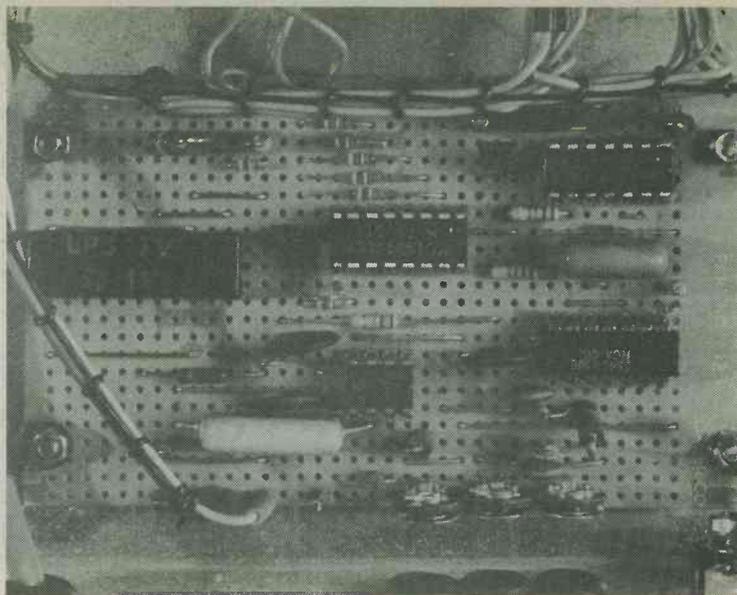A closer look at the Veroboard panel. The miniature reed relay is at centre left, and the three preset variable resistors are mounted at the right near the bottom edge.



COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

| | |
|-----|--|
| R1 | 10k Ω |
| R2 | 15k Ω |
| R3 | 680k Ω |
| R4 | 22k Ω preset potentiometer, 0.1 watt. |
| R5 | 82k Ω |
| R6 | 10k Ω |
| R7 | 15k Ω |
| R8 | 15k Ω |
| R9 | 1k Ω |
| R10 | 1.2k Ω |
| R11 | 1.2k Ω |
| R12 | 15k Ω |
| R13 | 15k Ω |
| R14 | 10k Ω preset potentiometer, 0.1 watt |
| R15 | 22k Ω preset potentiometer, 0.1 watt |
| R16 | 82k Ω |
| R17 | 15k Ω |
| R18 | 390 Ω |
| R19 | 1k Ω |
| R20 | 1k Ω |

Switches

| | |
|----|---|
| S1 | s.p.d.t. toggle, centre off, biased one way |
| S2 | s.p.d.t. push-button |
| S3 | 2-pole 3-way, miniature rotary |
| S4 | s.p.s.t. toggle |

Capacitors

| | |
|----|------------------------|
| C1 | 0.047 μ F ceramic |
| C2 | 0.22 μ F polyester |
| C3 | 0.47 μ F polyester |
| C4 | 0.01 μ F ceramic |
| C5 | 0.047 μ F ceramic |
| C6 | 0.047 μ F ceramic |
| C7 | 2,200pF ceramic |
| C8 | 2,200pF polystyrene |
| C9 | 0.047 μ F ceramic |

Semiconductors

| | |
|-------------|-----------|
| IC1 | 4011 |
| IC2 | 4093 |
| IC3 | 555 |
| IC4 | 4017 |
| TR1 | ZTX108 |
| TR2 | ZTX108 |
| D1 - D9 | 1N4148 |
| D10 | BZY88C9V1 |
| LED1 - LED3 | TIL209 |

Relay

RLA miniature reed relay, 12 volt coil.

Miscellaneous

Metal case
Control knob
Microphone socket, etc.

of IC2(a) and IC2(b). Pin 3 of IC2 goes to "1" and pin 4 to "0", and there are four results. First, the output of IC1(b) stays at "1", so that the relay remains energised and the transceiver stays in the transmit mode. Second, transistor TR1 turns on and illuminates LED1 to indicate that a "K" is being produced. Third, the reset pin of the 555, IC3, is taken to "1",

allowing pulses to appear at its output pin 3. Finally, pin 13 of IC2(c) is taken to "1".

The pulses from the 555 are fed to the clock input of the 4017 decade counter/divider, IC4. Diodes D3 to D9 form a logic OR gate and take pin 9 of IC2(d) to logic "1" on the counts 012 - 4 - 678. IC2(d), which is a Schmitt trigger hysteresis a.f. oscillator, is thus

enabled to produce a tone having the correct dash-dot-dash pattern for the letter "K". IC2(c) gates the oscillator output when the latch is set and feeds the "K" audio tone to the passive filter R13, C6, R12, C5, and thence to the transmitter microphone input.

After the last "K" forming pulse from IC4, its pin 11 goes to logic "1" and IC1(c) resets the latch to its previous state. The 555 is inhibited, TR2 is turned off and relay RLA releases, thereby opening the transceiver P.T.T. line. Preset resistor R4 sets the speed at which the "K" is transmitted, R15 adjusts the tone frequency and R14 allows its audio level to be set.

Switch S1 is the transmit switch and allows the transceiver to transmit continuously. In the prototype, S1 was a single pole changeover toggle type with a centre-off position and biased one way only. This enables the same switch to be used for both momentary or continuous operation.

S3 is the mode switch. In the "Standby" position, transmission is disabled; and in the "Normal" position no "K" tone is generated. Putting S3 to "Automatic" causes the "K" tone to be generated at the end of each over. Pressing S2 allows a morse "K" to be transmitted in the "Normal" mode. S4 is the on-off switch, and LED3 lights up to indicate that the 12 volt supply is switched on.

OPTIONS

As just described, the "K" tone generator can be constructed as a self-contained unit. However, the maximum current consumption is approximately 50mA, mainly due to the l.e.d.'s, and the prototype was powered by the transceiver power supply. If desired, the l.e.d.'s can be omitted along with TR1, D10, R7, R9, R18, R19 and R20, and RLA replaced by a 6 volt type. The generator will then operate from a 9 volt dry battery and will have a very low standby current consumption. The circuit may be further simplified by removing all the switches, and in this form could be incorporated inside many transceivers.

CONSTRUCTION

The layout of the circuit is not critical and any convenient method of construction may be used. The prototype components were assembled on a piece of 0.1in. Veroboard measuring 4 by 2½in., and were housed in a proprietary metal case measuring 6 by 4½ by 1½in. (152 by 114 by 44mm.). The preset resistors were vertical types mounted at one edge of the board, and holes were drilled in the rear of the case, and fitted with grommets, to allow adjustment. The microphone plug and socket were chosen to suit the author's transceiver. Other arrangements can be made to suit other transceivers.

SETTING UP AND TESTING

It is suggested that the output of the generator be connected to a suitable audio amplifier for initial testing. All three preset resistors should be set to their centre positions and a microphone connected to the input. Connect a suitable 12 volt supply and switch on. With S3 in the "Normal" position, operating the microphone P.T.T. switch or the transmit switch S1 should actuate relay RLA and light LED2. Set S3 to "Automatic" and press and release the P.T.T. switch. Both LED1 and LED2 should light and a morse "K" should be heard. Adjust R4 and R15 respectively for suitable speed and tone. Speak normally into the microphone and adjust R14 until the audio levels are the same. Final adjustments should be carried out "on-air", using a monitor receiver or by requesting a critical report. Ensure that the audio level does not overdrive the transmitter as this will cause severe distortion and interference.

No r.f. interference problems with the control logic were experienced with the prototype, although the use of a metal box is to be recommended. If r.f.i. problems do arise, 1,000pF decoupling capacitors and ferrite beads should be used on inputs and outputs.


NEW PRODUCT


The new Model SB 3M oscilloscope from Albol Electronic will serve most purposes required by industrial and service and hobby engineers, and yet manages to keep on the right side of the significant £100 price barrier. With a bandwidth of 0 to 3 MHz at -3 dB (extending to 6 MHz at -6 dB), the SB 3M breaks new ground, in its class, by offering time-base automatic triggering by IC comparator control of the type usually fitted only to luxury 'scopes' A 10 mV signal is all that is needed for a firmly locked and triggered time-base.

Albol say that this is an ideal personal oscilloscope for use by hobbyists, laboratory engineers and production-line testers, and for use as a garage diagnostic instrument, where it is complementary to the recently-announced Albol SD-80 petrol engine test and monitoring equipment.

The SB 3M takes about 20 watts from the 240 V mains, weighs 4.5 kg, and measures 150 mm wide by 340 mm deep by 280 mm high. Price: £99.00 plus VAT; delivery ex-stock.

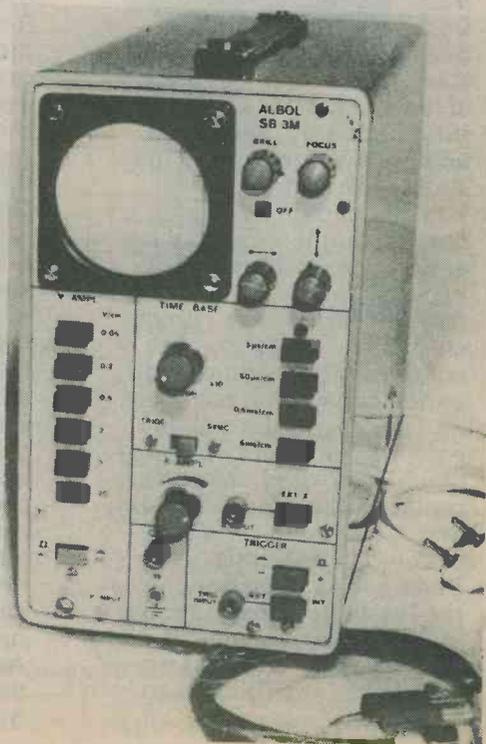Albol Electronic & Mechanical Products Ltd., 3 Crown Buildings, Crown St., London SE5 0JR.



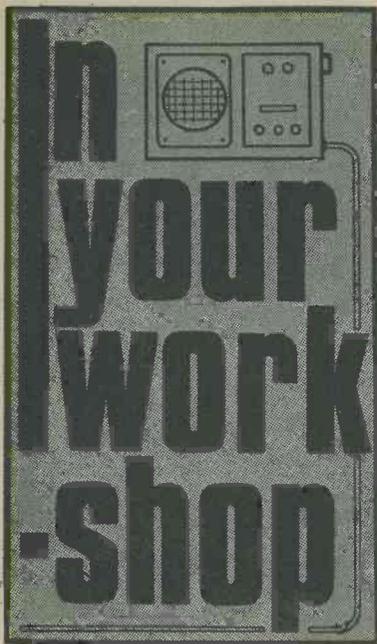

The "Haunted" Radio

The set which always worked
for Smithy, but never for Dick.

Had you chanced to enter the Workshop on the morning when our story commences you might well have thought yourself taken back through time by at least several decades when, first, you caught sight of Smithy the Serviceman delving into the interior of a mains valve radio with a cabinet styling dating from the early 50s. But this is the Age of the Antique, when almost anything which has survived at least a quarter of a century suddenly seems to acquire a value grossly in excess of its true worth. The owner of the old radio had sought Smithy's assistance in bringing it back to working order, and Smithy was now checking through the components, removing paper capacitors and fitting more modern polyester components in their place. He had already replaced the electrolytics and, indeed, there seemed very little else that needed to be done to the radio, whose aged valves gave evidence of a cathode emission which was so prolific as to be almost unseemly.

VINTAGE YEARS

Had you then carried on to observe Smithy's assistant, Dick, your reaction might well have been that the tapestry of the years had been drawn back even further, and you could in fact have wondered whether you were in an electronic servicing establishment at all. For Dick was carrying over from the "For Repair" rack a small shiny model of a truly vintage car which, since you are undoubtedly up on these things, you would at once have identified as a Rolls-Royce "Silver Ghost".


But things these days are rarely what they seem. The model of that prestigious car, which Dick was now placing on his bench, had two adjuncts which could never have existed on the original. Just visible above the running board on the right projected the milled edge of a flat circular knob, whilst a similarly positioned knob rim could be seen on the left hand side of the model. And, of course, you would have realised that the model was not just a

model of a vintage motor car, attractive in its own right as it might be. It was also a radio, with one of the knobs being the tuning control and the other the combined volume control and on-off switch.

Dick sat down on his stool and turned the model over. A leaflet slipped out from the driving seat and fluttered onto the bench surface. Dick put down the car and examined the leaflet. Some unknown and helpful hands in far-off sunny Hong Kong had not only printed an illustration showing the positions of the battery cover, speaker and controls, but had also appended the circuit diagram of the radio as well. (Fig. 1.)

Dick picked up the model and again turned it over. A grille on the underside was obviously the aperture for the speaker. Dick turned one of the knobs, and there was a mechanical click as the radio became turned on. He then experimentally turned the tuning control, but there was no sound from the speaker. He held the model close to his ear. He could detect

MORSE MADE EASY

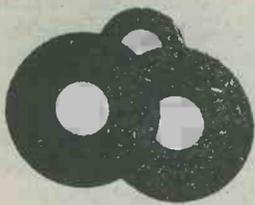

BY THE G3HSC RHYTHM METHOD!

These courses which have been sold for over 25 years, have been proven many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words. Using scientifically prepared 3 speed records you automatically learn to recognise the code, RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 WPM in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books. Complete Course £5.50 U.K. p/p 75p. (Overseas postage sufficient for 750grm). Details only s.a.e.

THE G3HSC MORSE CENTRE

S. Bennett, (Box 8), 45 Green Lane, Purley, Surrey.

Name

Address

THE

MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET
LONDON W2 1NP
Tel: 01-402 9176

Please mention
Radio & Electronics
Constructor when
replying to
advertisements

works of Bach.

"That must be Radio 3 on 247 metres," commented Smithy. "Let's see what else we can get."

He adjusted the tuning control. The strains of Bach disappeared, to be replaced after some moments by strident pop music.

"And that," Smithy pronounced, "can only be Radio 1 on 285 metres."

He continued to turn the tuning knob and the car-cum-radio emitted the unmistakable tones of Jimmy Young.

"And that," said Smithy finally, "will quite certainly be Radio 2 on 330 metres. Well there doesn't seem to be very much wrong with this set."

He switched off the radio, replaced it on Dick's bench and walked back to his own bench.

INTERMITTENT

Scowling, Dick picked up the radio and turned it on. Apart from the faint hiss, it was completely dead.

"Hey, Smithy," he called out, "what did you do with this set? I can't get a peep out of it!"

Smithy returned to Dick's side and picked up the model car. He turned one of the knobs, remembered that it was the tuning control, and then rotated the other. Once again the radio worked quite satisfactorily.

Smithy tuned through Radio 3 on 247 metres, Radio 1 on 285 metres and, finally, Radio 2 on 330 metres. He switched the radio off and handed it back to his assistant.

"It's working all right as far as I can see," he remarked. "Try it for yourself."

Bemusedly, Dick turned on the radio again. As before, it was completely dead. He adjusted the tuning control but to no avail. The set stubbornly refused to pick up any signals whatsoever.

"This is crazy," mut-

tered Dick as he switched the radio off. "Here, you try it again, Smithy."

Smithy took up the radio and switched it on. A little distorted, because the Radio 3 signal was slightly mistuned, the efforts of the string ensemble as they worked their way through their Bach repertoire at once became audible. Smithy tuned in the signal properly and then tuned, respectively, to Radios 1 and 2. He switched the radio off and replaced it on Dick's bench.

Dick picked it up and turned it on. No matter how he adjusted the tuning control the radio simply refused to reproduce the vaguest suspicion of a signal.

"This," moaned Dick as he switched off the set, "just cannot be true! We've got a simple medium wave radio here, admittedly in an unusual housing, and it's only got two controls. If I pick it up and switch it on it refuses to work. And yet when you pick it up it works perfectly. Here, do it again!"

Smithy took up the radio and turned it on. As he turned the tuning control the sounds of Bach, pop music and Jimmy Young issued successively from the speaker inside the model vintage car. He switched the radio off and placed it in front of Dick.

Dick looked bleakly at the model car and shuddered.

"I'm getting to the point where I daren't even touch the darned thing," he wailed. "That radio's got a spell on it. I bet there's someone in the factory out at Hong Kong who puts an old Chinese curse on these sets just to put the frighteners on young foreign devils like me!"

"Well," admitted Smithy, "I must confess that it's a bit odd that the radio works every time with me but never for you. Give it another try."

Dick reached out a faltering hand to switch on the radio and then adjusted the tuning.

As before, the set stayed completely dead.

"What did I tell you?" he stuttered. "The flaming thing's bewitched!"

"Nonsense," snorted Smithy. "It must have an intermittent fault of some sort which will show up after a bit of straight-forward fault finding. Can you get the printed board out, Dick?"

Dick examined the bottom of the model car closely.

"There are four screws holding the bottom plate on," he said. "Let's take these out."

Dick removed the screws, to find that the whole radio section came out neatly as one module.

"Obviously," remarked Smithy, "we haven't got a service manual for this job."

"We've got a circuit," said Dick. "I forgot to tell you that there was a leaflet with the model car which showed the circuit of the radio."

Dick picked up the leaflet and passed it over to Smithy, who examined it carefully.

CIRCUIT DIAGRAM

"You know, Dick," he remarked after some moments, "you've got to take off your hat to the people who design and manufacture these novelty medium wave radios. Everything is tidy and functional and yet the circuit uses the bare minimum of components."

"That circuit may be tidy and functional with you," complained Dick, "but it certainly isn't functional so far as I'm concerned!"

"Well, let's just take a butcher's at it," pronounced Smithy. "If we work back from the speaker it's very easy to follow. There's the usual Class B output stage preceded by the driver trans-

sistor. As almost always with these little radios, a.f. transformers are used instead of the more modern a.f. amplifier arrangements which don't require transformers."

"Before the driver transistor," put in Dick, "there's the third i.f. transformer and the diode detector which feeds into the volume control."

"That's right," agreed Smithy. "The volume control is also the diode load, and you'll notice that the diode is connected so that the top end of the volume control track goes more negative as signal strength increases. The voltage at the top of the volume control track is fed back via a 33kΩ resistor to the base of the first i.f. transistor to give automatic gain control."

"There isn't an i.f. transformer between the two i.f. transistors," put in Dick, "they're coupled together by a 0.005μF capacitor."

"True," confirmed Smithy. "So the coupling between these two transistors is untuned. But there are two i.f. transformers between the mixer-oscillator transistor and the first i.f. transistor. These are coupled together by a 2pF capacitor to form a band-pass pair. So there are still three tuned circuits in the i.f. amplifier." (Fig. 2.)

"All that seems fair enough," commented Dick. "What about the mixer part?"

"That uses a very simple circuit arrangement," stated Smithy. "Since the set only tunes over the medium wave band very few components are needed here. A coupling winding on the ferrite rod aerial couples into the base of the mixer transistor. The mixer collector connects through a coupling winding on the oscillator coil to the first i.f. transformer, and the

PEATS for PARTS

ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish enthusiasts we supply:

Radio & Electronics
Constructor Data Books
Panel Signs Transfers

Also a postal service

peats

the world of electronics

25 Parnell Street, Dublin 1. Tel 749972

ELECTRONIC

TUTOR KITS

Learn electronics the effective way by experiments. Each kit contains an illustrated handbook, which takes you step by step through the fundamentals of electronics, plus all the components needed. No soldering. Safe and instructive for even the young enthusiast. Kit 1, £5.85. Kit 2, £5.95. Kit 3, £6.15. SAE for leaflets on this and other RXG products.

RXG ELECTRONICS LTD.

15 Walnut Tree Crescent,

Sawbridgeworth, Herts, CM21 9EB.

GAREX

V.H.F. Receivers SR-9 for 2-metres F.M., fully tunable 144-146MHz, 2-speed slow-motion dial, also 11 xtal controlled channels. Compact, sensitive, ideal for fixed or mobile listening. Built-in L.S., 12v D.C. operation £47.15 inc. VAT. Crystals, if required: £2.60 each. All popular 2m. channels in stock. Marine band version (156 162MHz) £47.15 (xtals £2.90). Mains psu for above £11.95. Pocket VHF Receiver 12 channel xtal controlled complete with nicad and charger. 4MHz bandwidth in range 140-175MHz £57.95. Amateur and Marine xtals in stock, prices as SR-9.

Amplifier module new, fully assembled 6W IC unit, 12v D.C. Low impedance (4-8Ω input and output for extn. speaker amplification, with circuit £2.75.

Neons min wire end 70p/10: £4.50/100

Slide switches min DPDT 20p ea; 5 plus: 16p

Resistor Kits E12 series, 22Ω to 1MΩ 57 values, 5% carbon film, 1/4W or 1/2W Starter pack, 5 each, value (285) £3.10

Mixed pack, 5 each 1/4W plus 1/2W (570) £5.55

Standard pack, 10 each (570) £5.55

Giant pack, 25 each (1,425) £13.60

BNC Cable mtg socket 50Ω 25p; 5 plus: 20p;

PL259 UHF Plug and Reducer 75p; 5 plus: 67p;

SO239 UHF Socket panel mtd. 60p; 5 plus: 50p;

Nicad rechargeables physically equiv. to zinc-carbon types: AAA (016) £1.80; AA(U7) £1.30;

C(U11) £3.35; PP3 £5.55. Any 5 plus: less 10%. Any 10 plus less 20%.

We stock V.H.F. & U.H.F. mobile aeriols

s.a.e. details.

Access - Barclaycard

PRICES INCLUDE UK POST,
PACKING & VAT

Mail order only

Sole Address

GAREX ELECTRONICS
7 NORVIC ROAD, MARSWORTH.
TRING, HERTS HP23 4LS
Cheddington (STD 0296) 668684

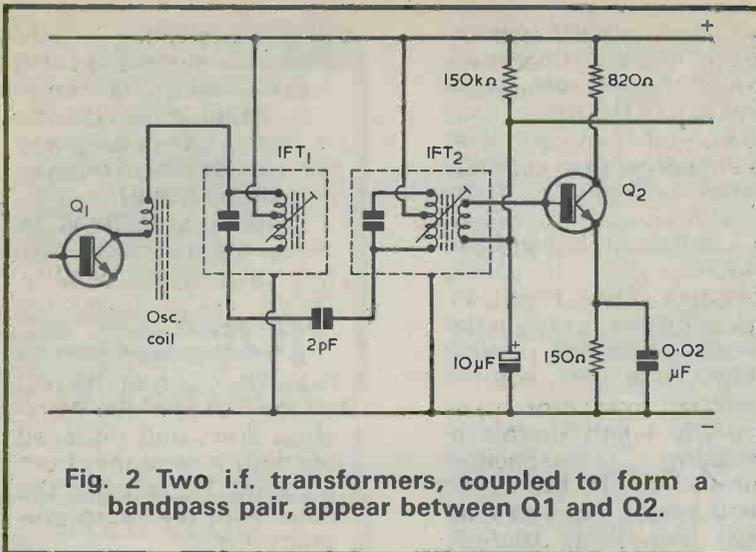


Fig. 2 Two i.f. transformers, coupled to form a bandpass pair, appear between Q1 and Q2.

oscillator tuned coil has a tap which connects to the mixer emitter. So the oscillator feedback is from the mixer collector back to its emitter." (Fig. 3.)

Smithy put the leaflet with the circuit diagram back on Dick's bench.

"Right," he said briskly, "to business! Did you notice anything about the set when you switched it on and it didn't pick up signals?"

Dick thought for a moment.

"Well, there was a quiet hiss."

"Was there? Can you switch on the set now you've got the board out?"

"Oh yes."

Dick rotated the volume control knob to turn on the set, then rotated the tuning control. As on all the previous occasions, the radio doggedly refused to function for him.

"Signal genny next!" said Smithy. "Bring it over and set it up for around 465kHz."

Dick pulled his battered signal generator over and switched it on. As he set up its frequency, Smithy searched through a cardboard box of spares on his assistant's bench and found a 0.01 μF capacitor. He next coupled the earthy output lead of the

signal generator to the negative battery clip and clipped the 0.01 μF capacitor to the non-earthly output lead. He next examined the little printed board and traced the printed wiring from the ferrite aerial coupling coil through its coupling capacitor to the base of the mixer transistor, then applied the free end of the 0.01 μF capacitor to that base. (Fig. 4.)

SIGNAL INJECTION

The 400Hz modulation of the signal generator was at once audible from the speaker of the radio.

Smithy increased the signal generator attenuation until the modulation could just be heard and then adjusted the generator frequency for maximum output. After that he removed the 0.01 μF capacitor and the signal generator earthy lead from the radio, then glanced at the generator frequency scale.

"The i.f. amplifier," he remarked in a satisfied tone, "is peaking nicely at 470kHz, and the i.f. stages seem to be giving plenty of amplification. I thought I'd start off by checking the i.f. amplifier as a whole rather than inject a signal at each stage and work back to the mixer. I had a hunch, inspired by your remark about the hiss, that the whole i.f. amplifier would be all right, and so it has turned out to be."

"So," said Dick slowly, "let's see what we've got up to now. I've switched on the set and, as always, it refuses to pick up any signals for me. And yet the i.f. amplifier is all right. There must be a fault in the ferrite aerial circuit, then."

"There could be," agreed Smithy, frowning. "Or it could be that the mixer isn't oscillating."

"Not oscillating?"

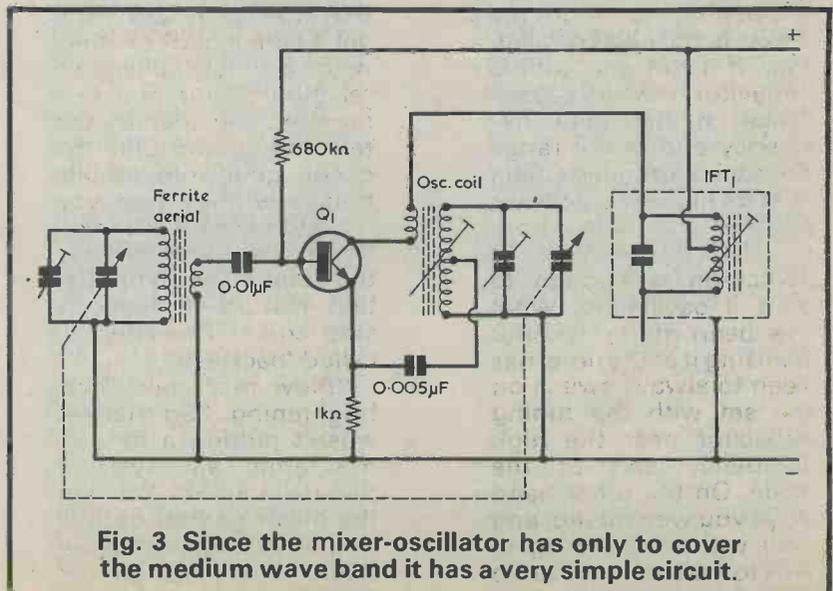


Fig. 3 Since the mixer-oscillator has only to cover the medium wave band it has a very simple circuit.

repeated Dick. "Well, why won't it oscillate for me and yet oscillate for you?"

"I don't know," replied Smithy slowly. "Hang on a jiffy though, I've got a glimmering of an ideal! When I switched the set on, didn't I always tune in the Radio 3 signal first?"

"I can't remember," said Dick dolefully.

Smithy leaned forward, switched off the radio, set the tuning capacitor to the high frequency end of its range and switched on again. He then slowly adjusted the tuning capacitor, and a signal almost immediately became audible. It was a talk on social proclivities in Outer Mongolia. Johann Sebastian Bach must have won and Radio 3 was now continuing with its next programme, cutting its own narrow swathe through the airwaves of England.

"Ye gods," said an aghast Dick. "Even when its out of its case that darned radio will still only work for you!"

Smithy proceeded to turn the tuning control, passing yet again through Radio 1 and Radio 2. After tuning in this last station he switched off the radio and turned it on again. And the radio remained silent.

"It's the oscillator that's wrong," stated Smithy triumphantly. "What's happening is that the mixer is only just oscillating. If I set the tuning capacitor to a low capacitance at the high frequency end of the range the oscillator tuned circuit is at its highest efficiency, so that the little shock given to the oscillator at switch-on is enough to start it oscillating. What I've been doing, without realising it at the time, has been to always switch on the set with the tuning capacitor near the high frequency end of the scale. On the other hand what you were doing, and also without knowing it, was to switch on the radio with the tuning capacitor

set to a greater capacitance. With the reduced tuned circuit efficiency which resulted, the switch-on shock just wasn't enough to start the oscillator."

"But you got the mixer to oscillate at those lower frequencies."

"Only after I'd initially got it to start at the high frequency. This quite often happens with a reluctant oscillator, particularly when there's a coupling capacitor somewhere in the feedback circuit. As you can see, there's a $0.005\mu\text{F}$ coupling capacitor in the emitter circuit. When the oscillator is caused to start at the high frequency it settles down to proper working and it will then

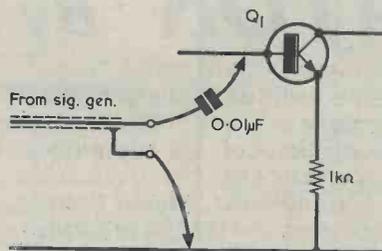


Fig. 4 Checking the i.f. and a.f. stages by injecting a modulated i.f. signal into the base of Q1.

continue to oscillate even when you take it down to frequencies lower than that at which it starts. You get a similar sort of effect with a badly designed reaction circuit in a t.r.f. receiver. You advance the reaction control until the circuit goes into oscillation, and then find you have to back off the reaction control well beyond the point at which oscillation started to make it stop again. The effect is called 'backlash'."

"Blow me," said Dick, brightening. "So that set wasn't putting a hex on me after all. Wait a minute, though. You got the mixer to start oscillating by tuning around the Radio 3 wavelength of 247 metres, and it then

kept oscillating right down to Radio 2 on 330 metres, which is nearly 100 metres down the scale. Isn't that a long way for your backlash thing to remain effective?"

"Not if you think in terms of oscillator frequency," stated Smithy. "Now, let me consult my newspaper."

Smithy walked over to his coat, hung on its peg on the inside of the Workshop door, and retrieved his daily newspaper from a pocket. He selected the page with the radio programmes.

"We're more than a bit old-fashioned in this country," he remarked, "because we still tend to keep talking about station wavelengths on medium and long waves. Now my very superior newspaper not only gives station wavelengths but it also gives frequencies, and it tells me that the Radio 3 frequency is 1,215kHz whilst the Radio 2 frequency is 909kHz."

"That's still," objected Dick, "a ratio of something like 3 to 2."

"Ah yes," agreed Smithy, "but don't forget that oscillator frequency is higher than signal frequency by the intermediate frequency, which, with this set, is 470kHz."

Smithy took out a pen and proceeded to jot some figures in the margin of the circuit diagram leaflet. (Fig. 5.)

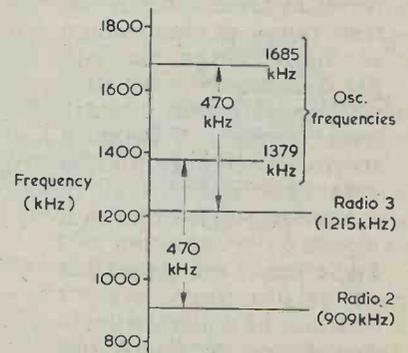


Fig. 5 The oscillator frequencies corresponding to the signal frequencies of Radio 3 and Radio 2.

"The oscillator frequency for Radio 3 is 1,215 plus 470kHz," he went on, "which comes to 1,685kHz. And the oscillator frequency for Radio 2 is 909 plus 470kHz, which works out as 1,379kHz. The ratio between these two frequencies is not 3 to 2 but is less than 5 to 4, which is quite low enough for a backlash effect to take place."

NEW TRANSISTOR

Smithy was right, of course.

A few quick checks

showed that the resistors and capacitors around the mixer transistor were as they should be, whereupon the fault could lie in the oscillator coil or in the mixer transistor itself. Smithy plumped hopefully for the latter which, the little leaflet told him, was a 9011G. Even Maplin don't list this one so Smithy consulted the Workshop copy of the invaluable **Towers' International Transistor Selector—Up Date 2** to find that this was a silicon transistor with a quoted hFE of 72 to 108. A BC107A

seemed a reasonable substitute and this, with due attention to its different lead layout, was ceremoniously installed by Dick.

And, with its new transistor, the little radio worked perfectly regardless of whether Smithy or Dick switched it on. It would probably even have worked for Jimmy Carter. Every cloud has its silver lining, and the silver lining in this case was that the radio was not after all haunted despite its silver ghostly housing. ■

NEGLECTED OSCILLATOR

By R. S. Burns

When the ICM7555 (the "CMOS 555") came on the scene we looked upon it as the latest thing in low supply current operation. Having all the attributes of the 555, apart from output current capability, the ICM7555 could run as an oscillator requiring only about 40 to 50µA from a 9 volt supply.

But a CMOS digital device which can function as an oscillator with even lower current consumption was already sitting in the lists before the appearance of the ICM7555. This digital device is the 4047 Low-Power Monostable/Astable Multivibrator.

4047 PINOUT

The 4047 has the pinout shown in Fig. 1, and a simplified block diagram representing its internal logic is given in Fig. 2. As can be seen, it includes a low power astable multivibrator whose output passes to pin 13. The multivibrator output is also fed into a frequency divider which divides it by 2, with a Q output at pin 10, and a not-Q output at pin 11. There are a number of inputs, most of which are concerned with monostable functioning. The astable and not-astable inputs at pins 5 and 4 respectively do, however, control the i.c. in astable operation.

Fig. 3 shows the 4047 connected for free-running astable operation. You can take an output at multivibrator frequency from pin 13, or an output at half multivibrator frequency either from pin 10 or from pin 11. The two divided outputs are guaranteed square waves. Frequency is controlled by the values of R and C.

Fig. 4 shows the output waveforms at pin 13 and pin 10 relative to each other. The pin 13 output is not a guaranteed square wave because its duty cycle depends upon the transfer characteristic of the f.e.t. inside the i.c. which follows pin 3. The pin 10 output changes state on every positive-going pulse edge of the pin 13 waveform. Since each half-cycle of the pin 10 output has the same length as a whole pin 13 cycle,

the pin 10 output has to be a true square wave.

The cycle length of the pin 10 waveform is specified as being typically:

$$T = 4.40 RC$$

where T is in seconds, R is in ohms (or megohms) and C is in farads (or microfarads). Interestingly enough, this equation for typical cycle length represents the minimum time within tolerance. If the transfer characteristic of the multivibrator input f.e.t. shifts in either direction to its specification limits the maximum cycle length is given by:

$$T = 4.62 RC$$

4.62 is 4.40 plus 5%. So you can calculate cycle length by using the 4.40 figure, and this will give you the actual cycle length within -0% and + 5%. To take an example, let's say that R in Fig. 3 is 470kΩ and that C is 0.0022µF. The typical cycle length at the pin 10 output is then:

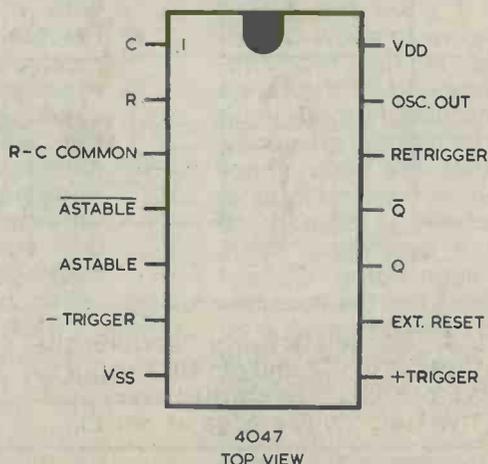


Fig. 1. Pin functions for the 4047 monostable/astable multivibrator.

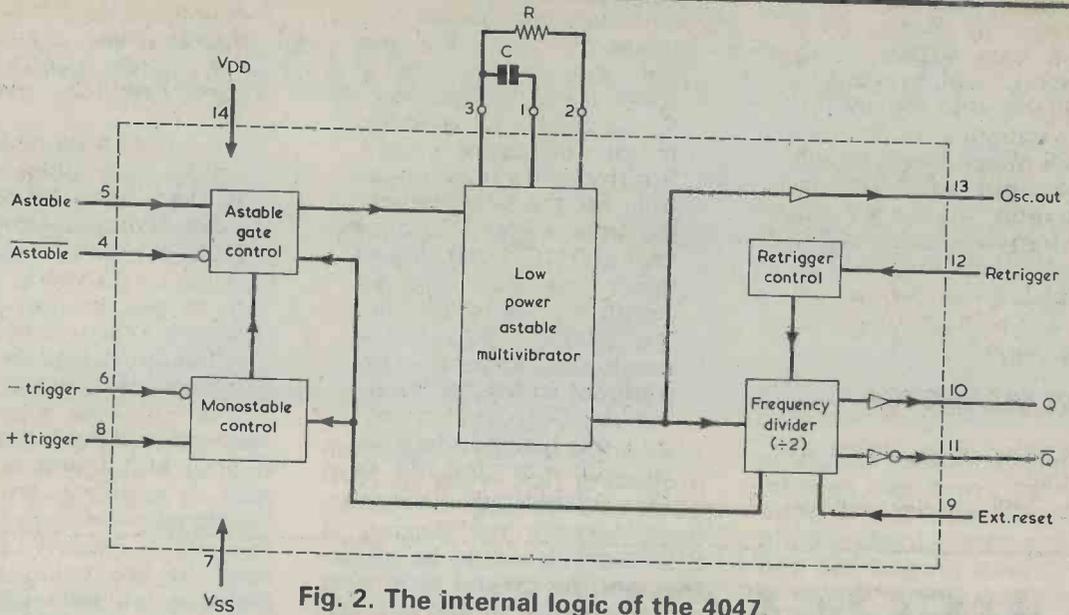


Fig. 2. The internal logic of the 4047.

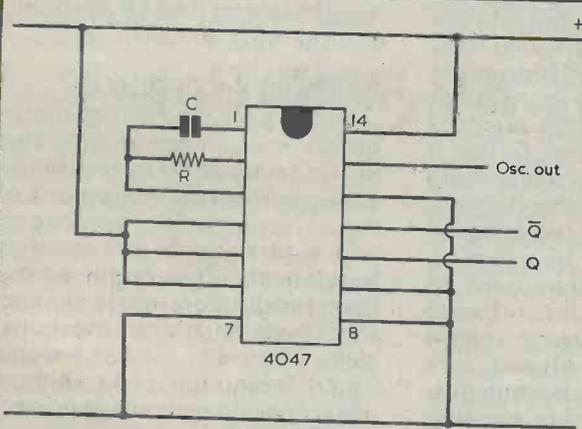


Fig. 3. Connecting up the 4047 as a free-running multivibrator. There are three outputs, one at multivibrator frequency, and two at half multivibrator frequency.

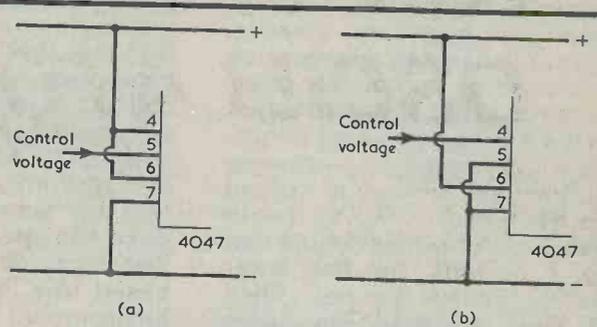


Fig. 5(a). When pins 4, 5 and 6 are connected as shown here, the multivibrator runs when pin 5 is high and stops when it is low.
 (b). With this alternative method of connection, the multivibrator runs when pin 4 is low and stops when pin 4 is taken high.

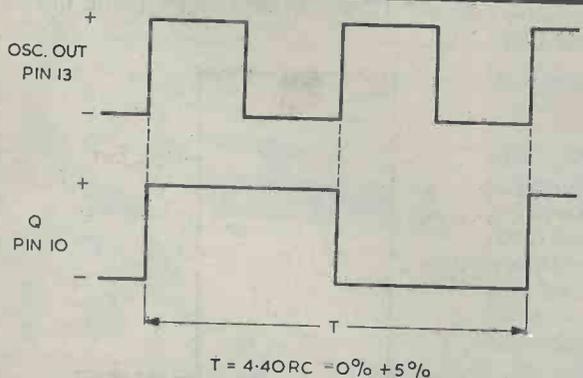


Fig. 4. The relationship between the outputs at pin 13 and pin 10. The pin 10 waveform changes state at every positive-going pulse edge at pin 13.

LIMITING VALUES

The manufacturer's limiting values for the timing components, R and C, state that the resistance must lie between 10k Ω and 1M Ω , whilst the capacitance must have a minimum value of 100pF with no limit on maximum value.

Current consumption, when employed as a free-running multivibrator, depends almost entirely upon the value of the timing resistor. When this is 1M Ω the current drawn from a 9 volt supply is less than 25 μ A, and when it is 100k Ω the current is less than 45 μ A. With a 10k Ω timing resistor the current at 9 volts is much higher, being in the region of 600 to 800 μ A. So, provided the timing resistance is 100k Ω or more, a 4047 oscillator draws less current from its supply than does an ICM7555 oscillator.

The 4047, when free-running, can be controlled by voltages at the astable and not-astable inputs. If pins 4, 5 and 6 are connected as shown in Fig. 5(a), the multivibrator runs when pin 5 is high and stops when pin 5 is low. With the pins connected as in Fig. 5(b), the multivibrator runs when pin 4 is low and stops when it is taken high.

$4.40 \times 0.47 \times 0.0022$
 which calculates as 0.00455 second. The reciprocal, which gives the frequency, is 220Hz.

Radio Topics



By Recorder

So far as Mother Nature is concerned I'm a real townie, and my concept of the good earth is a nice shiny brass pin on a 13 amp plug at the end opposite to where the wire goes in. But I recently had to assume responsibility for a small plot of ground measuring some 6 feet by 4 feet which had become completely overgrown. I could either donate it to the nation as an area of outstanding natural free-growing flora or get to work in pulling up the weeds. I like to live in peace with my neighbours and so I decided on the latter course. Believe it or not, I filled at least a dozen bin liners before I had the area reasonably well cleared.

THE TREE

Normal weeds were easy enough but the ground also supports a little tree of such abundant fecundity that it's beginning to dog my dreams. The roots go under some concrete and so I just contented myself with cutting it down. But I only have to turn my back on it for a couple of days to find that it has pushed out a whole new system of branches all covered with bright chlorophyll laden leaves. And, of course, the branches and leaves exactly reflect the basic make-up of the tree, which I assume to be a member of the *genus Quatermass*.

Now, it occurs to me that this abundantly productive tree is carbon based, and that it should not be beyond the capabilities of our experimental biologists to create a silicon based form of plant life. Just imagine the benefits to modern technology which would accrue. We could, for instance,

raise 4001 or 4011 trees, each producing rich crops of NOR gates and NAND gates respectively just for the picking. A BC109 shrub would be attractive, and by careful grooming and selection it should be possible to cultivate three individual plants which fell into the BC109A, BC109B and BC109C categories. As our silicon plant cultivators became more adept we could have a 555 bush or even an MC6800 tree. In fact it is in the microprocessor field that my scheme should produce the greatest awards. In just the same way as a carbon based tree interfaces with its environment the silicon based microprocessor plant could interface with its own source of nutrient, with each branch providing its own data bus coupling it with the main trunk.

I think I'll take another look at that prolific tree of mine. Ord-

nary sand is a good source of silicon, and I see no reason why I couldn't try copper nitrate as a fertilizer. So watch this space. Even if I only succeed in producing a 1N914 plant, it will still be quite a major step forward. But with my gardening luck I'll probably end up with an OA70 bush.

ASSEMBLY STATION

In the accompanying photograph you can see an operator at the factory of Oxford Medical Systems assembling one of the firm's tape recorders, which are used to monitor heart beats. This is not a flow line production system, and the operator builds the complete assembly. She is helped by a "Trescomp" independent assembly station designed and produced by Link-Hampson Ltd., 5 Bone Lane, Newbury, Berkshire, RG14 5TD.



In this assembly station at Oxford Medical Systems the operator builds the complete product. Components are brought forward as required by a Link-Hampson "Trescomp" motorised conveyor.



The Link-Hampson "Trescomp" independent assembly station is part of an integrated parts handling system which can provide increased levels of production over more conventional factory flow lines. Oxford Medical Systems were one of the first firms to install these stations, and they report an increase of 40% over the previous flow line system. At their Abingdon based factory, where tape recorders for monitoring heart beats and associated analysis equipment are produced, "Trescomp" stations are used to complete the different assemblies. The products are constructed from a mix of electro-mechanical and electronic components and individual operators are responsible for complete assemblies.

Each assembly station has a motorised conveyor which supports rows of trays with sufficient capacity to carry 153 different components. Before the assembly work commences the trays are loaded with all the required components in a pre-planned sequence. The operators then follow a pre-determined order of assembly. When a new component is needed, the conveyor is activated by a foot switch and the appropriate component moves into position.

By employing independent stations it is found that not only does production output increase but improved reliability also results from greater operator responsibility. This is



The Klippon cable insulation stripper. This deals with all types of insulation having an outer sheath diameter of 4.5 to 28.5mm.

because each operator builds up a complete assembly and any defect that occurs can then be rectified by the person concerned. As can be readily visualised, there is less personal association with a completed product when it is assembled using the flow line system, with defects being rectified by a special repair section employing different staff.

CABLE STRIPPER

The second photograph shows the Type AMI insulation stripper which has been introduced by Klippon Electricals Ltd., Terminal Works, Power Station Road, Sheerness, Kent, ME12 3AB. This is suitable for use with round cables having an outer sheath diameter of 4.5 to 28.5mm. The AMI is a com-

pact and easily held hand-tool, yet it is very robust and will give many years of trouble-free use.

The insulation cutting blade can be adjusted with a simple thumbscrew to obtain the correct cutting depth, and the tool firmly grips the cable during the rotary cutting action. To complete the cutting operation, the blade is rotated by means of a push-button to enable an axial cut to be made.

In cases where the insulation is extra thick or difficult to remove, the tool features an integral hook-blade cutter which can be pulled along the initial axial cut to ensure easy removal of the insulation. The AMI is made of steel and high strength thermoplastic and measures a mere 5½ by ¾ in. ■

We regret that owing to pressure on space, the article entitled *Experimental Electronics* has been held over to our next issue.

Mail Order Protection Scheme

The publishers of this magazine have given to the Director General of Fair Trading an undertaking to refund money sent by readers in response to mail order advertisements placed in this magazine by mail order traders who have become the subject of liquidation or bankruptcy proceedings and who fail to supply goods or refund money. These refunds are made voluntarily and are subject to proof that payment was made to the advertiser for goods ordered through an advertisement in this magazine. The arrangement does not apply to any failure to supply goods advertised in a catalogue or direct mail solicitation.

If a mail order trader fails, readers are advised to lodge a claim with the Advertisement Manager of this magazine within 3 months of the appearance of the advertisement.

For the purpose of this scheme mail order advertising is defined as:

"Direct response advertisements, display or postal bargains where cash has to be sent in advance of goods being delivered."

Classified and catalogue mail order advertising are excluded.

ELECTRONICS

A NEW AND EXCITING HOBBY!!

BIG, WELL ILLUSTRATED BOOK

Ideal for beginners – gives lots of general information – explains how to build lots of projects: intercom, Rain Alarm, Radios, Organ, Parking Light etc. All parts supplied and can be re-used on special deck provided, so **NO SOLDERING** is required. Just needs 4½V battery.



£17.50 inc. VAT & Post

Also

ADVENTURES WITH MICROELECTRONICS

– Explore the world of silicon chips – All components & Deck, £27.95 inc VAT & Post.

Component Catalogue & Bargain List 75p

GREENWELD

443G Millbrook Road, Southampton SO1 0HX

A CAREER IN RADIO

Start training *today* and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs – they can do the same for *you*.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

CITY & GUILDS CERTIFICATES

Telecommunications Technicians' Radio TV Electronics Technicians' Electrical Installations Technicians' Electrical Installation Work Radio Amateurs' MPT Radio Communications Cert

EXAMINATION STUDENTS – GUARANTEED COACHING UNTIL SUCCESSFUL

TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including: Electronic Engineering & Maintenance Computer Engineering/Programming Radio, TV & Audio Engineering & Servicing Electrical Engineering Installations & Contracting

COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in

Name Age

Address

Occupation

ICS

Accredited by CACC Member of ABCC

To International Correspondence Schools Dept 278B, Intertext House, LONDON SW8 4UJ or phone 01-622 9911 (anytime)

TUNE IN to the new-look

JANUARY 1981

Practical Wireless

65p

8 EXTRA PAGES OF PROJECTS & FEATURES

tape-slide controller



& **DXTV**

8 EXTRA PAGES OF PROJECTS AND FEATURES

PLUS **PW NIMBUS** Back-up Power Supply

● DX TV – THE BASICS

Find out how to get started in long-distance television reception with Roger Bunney, an acknowledged expert in the field. Propagation, receivers, amplifiers and aerials for the VHF and UHF TV bands are all covered.

● TAPE/SLIDE CONTROLLER

Build your holiday slides up into an audio-visual show with this versatile tape/slide controller. The unit incorporates microphone pre-amp and mixing facilities for use with tape recorders lacking these features.

● PW 'NIMBUS' SCANNING MODULE

● PORTABLE RADIO BACK-UP POWER SUPPLY

Practical Wireless

JANUARY ISSUE ON SALE FRIDAY DECEMBER 5 65p

SMALL ADVERTISEMENTS

Rate: 12p per word. Minimum charge
£2.00
Box No. 30p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of Advertisers.

Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. Replies to Box Numbers should be addressed to: Box No. —, Radio and Electronics Constructor, 57 Maida Vale, London, W9 1SN.

BURGLAR ALARM COMPONENTS. PVC coated steel bell box £8.74. 6in. masterbell £13.53. 106dB sounder £11.53. Latching personal attack button £2.95. Surface contact £1.28. Flush contact £1.28. Large pressure pad £2.85. Stair tread pad £2.00. 20m range infra red beam £46. Mains/battery alarm control module £17.20 or send for our free component catalogue and price list. All prices inclusive. Sigma Security Systems, 13 St. Johns Street, Oulton, Leeds, W. Yorks. LS26 8JT.

BIGGEST RANGE SERVICE SHEETS/MANUALS. Any published sheet £1. plus s.a.e. Repair data any named TV £5.50 (with circuit set £7). S.A.E. newsletter, quotations, bargains. G.T., 76 Church Street, Larkhall, Lanarkshire.

WANTED: FAX equipment, manuals, service sheets, etc. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk. NR32 3PJ.

BOOKS FOR SALE: *Experiments with Operational Amplifiers*, by George B. Clayton. £3.75. *Digital I.C. Equivalents & Pin Connections*, by Adrian Michaels, £1.20. *Experimenting with Electronic Music* by Brown & Olsen. £1.20. *Electric Model Car Racing* by Laidlaw-Dickson. 60p. *Understanding & Using Modern Signal Generators* by Charles Gilmore. £1.20. *Electronics Unravalled* by Kyle, £1. *How to Use your VOM VTVM Oscilloscope*, by Clifford, £1. *Modern Radio Repair Techniques*, by Art Margolis, £1. Box No. 394.

ZX80 PEOPLE. Free leaflet explains how to overcome load problems, ½-price memories, etc., supplied with four games on cassette. Send £3 or s.a.e. for details. Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

25 MIXED I.C.'S £1.50. 100 mixed transistors £3.50. Valves. Early radios. Electronic bargains. Interesting lists 15p. Sole Electronics, REC, 37 Stanley Street, Ormskirk, Lancs, L39 2DH.

(Continued on page 252)



Wilmslow Audio


THE firm for speakers!

SEND 50p FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST

AUDAX ● AUDIOMASTER ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMAN'S ● HARBETH ● ISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● MCKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANNOY ● VIDEOTONE ● WHARFEDALE ●

WILMSLOW AUDIO DEPT REC
35/39 CHURCH STREET, WILMSLOW
CHESHIRE SK9 1AS.

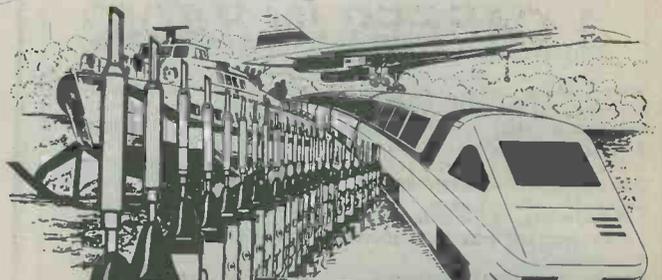Tel: 0625-529599 for Mail Order & Export of Drive Units, Kits, etc.,
Tel: 0625-526213 (Swift of Wilmslow) for Hi-fi and complete speakers




The MIGHTY MIDGETS SOLDING IRONS AND ACCESSORIES

| | RETAIL PRICE each inc. v.a.t. | POSTAGE extra |
|---|--|------------------|
| 18 WATT IRON FITTED WITH NO. 20 BIT AVAILABLE IN: 12V, 110V, or 240V | £4.95 | 28p |
| SPARE BITS | 69p | — |
| STANDS | £4.49 | 80p |
| SOLDER: SAVBIT 20' | 70p | 12p |
| " 10' | 40p | 8p |
| LOWMELT 10' | 80p | 12p |
| I.C. DESOLDERING BIT | £1.27 | 12p |
| BIT SIZES: | NO. 19 (1.5mm) NO. 20 (3mm) NO. 21 (4.5mm) NO. 22 (6mm) | |

From your Local Dealer or Direct from Manufacturers

S & R. BREWSTER
LIMITED

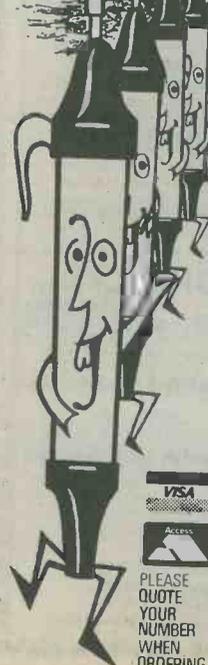86-88 UNION ST. PLYMOUTH PL1 3HG
Tel: 0752 65011 TRADE ENQUIRIES WELCOME



VSA
Access
PLEASE QUOTE YOUR NUMBER WHEN ORDERING

Strip-fix Plastic PANEL SIGNS



- ★SET 3-Wording-WHITE
- ★SET 4-Wording-BLACK

Over 1,000 words and symbols,
covering more than 300 terms, in
each set

Illustration of actual size equals RADIO

★SET 5-DIALS

6 sheets containing one Large and two
Medium scales, Large Horizontal Tuning
scale, Frequencies, 12 Control Panels

6 SHEETS IN EACH SET

PRICE: **£1.50** per set including VAT.
p.&p. 11p per set.

To DATA PUBLICATIONS LTD.,
57 Maida Vale, London, W9 1SN

Please supply Panel Signs as follows: Set 3.....Set 4.....Set 5.....

I enclose cheque/crossed postal order for
(Tick which set is required)

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

SMALL ADVERTISEMENTS

(Continued from page 251)

FOR SALE: Wide angle 9.5mm cine equipment:
camera, projector, screen, etc. Also several
other 9.5mm cine cameras. S.A.E. for details
Box No. G388.

MODULES. Mullard LP1164 AM/FM i.f. Unused
and guaranteed £1.50. P.P. C.W.O. BA screws,
hardware, components, Manufacturers' clear-
ance. S.A.E. lists. Tennex Ltd., Stock Road,
Southend-on-Sea, Essex.

U.K. AIRCRAFT frequencies list £1. U.K. marine
frequencies list £1. Including HF VHF. P.L.H.
Electronics, 20 Vallis Road, Frome, Somerset.

JOIN THE INTERNATIONAL S.W. LEAGUE.

Free services to members including Q.S.L.
Bureau, Amateur and Broadcast Translation,
Technical and Identification Dept. - both
Broadcast and Fixed Stations, DX Certificates,
contests and activities for the SWL and transmit-
ting members. Monthly magazine, *Monitor*,
containing articles of general interest to Broad-
cast and Amateur SWLs, Transmitter Section
and League affairs, etc. League supplies such as
badges, headed notepaper and envelopes, QSL
cards, etc., are available at reasonable cost. Send
for League particulars. Membership including
monthly magazines, etc., £6.00 per annum.
(U.K. and British Commonwealth), overseas
\$12.00. Secretary ISWL, 1 Grove Road, Lyd-
ney, Glos., GL15 5JE.

FOR SALE: A number of "D & S" three pin,
fused, mains plugs and fuses. S.A.E. for details.
Box No. G396.

12 UNUSED RECHARGEABLE Gel type Lead
Acid Batteries. 12V 1.5 A.H. £4 each. R. Garas,
147 Seaforth Avenue, New Malden, Surrey.

USE OPTICAL FIBRES TO CARRY LIGHT.

Tough, wire-like strands that are excellent for
communications, lighting, electrical isolation,
etc. Introductory pack totals sixteen feet of four
assorted types, plus twenty page illustrated
guide. Send £3.55 inclusive to Quantum Jump
Ltd., 53 Marlborough Road, Tuebrook, Liver-
pool L13 8EA.

BOOKS FOR SALE: *Amateur Radio Antennas* by
Harry Hooton, £1. *Ham Antenna Construction
Projects* by J. A. Stanley, 75p. *All about Cubical
Quad Antennas* by W6SAI, £1. *Radio
Astronomy for the Amateur* by Dave Heiser-
man, £2. *HAM-RTTY* by W2NSD, 50p. *Radio
Control for Model Yachts* by C. R. Jeffries,
£1.00. All plus postage. Box No. G397.

INTERESTED IN OSCAR? Then join
AMSAT-UK. Newsletters, OSCAR NEWS
Journal, prediction charts, etc. Details of mem-
bership from: Ron Broadbent, G3AAJ, 94
Herongate Road, Wanstead Park, London, E12
5EQ.

(Continued on page 253)

SMALL ADVERTISEMENTS

(Continued from page 252)

THE RADIO AMATEUR INVALID & BLIND CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. F. E. Woolley, 9 Rannoch Court, Adelaide Road, Surbiton, Surrey, KT6 4TE.

FOR SALE: KW2000 B Transceiver with trapped dipole antenna to match. £150. Prefer buyer collects. George Oxby, G3RRX, 36 Denmark Road, Beccles, Suffolk. Telephone: 0502-715322.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

FOR SALE: Photographic enlarging equipment: Vivitar enlarger. Model E.36 with 50mm f. 3.5 and 75mm f.3.5 lenses. Kodak safety light. Kodak contrast filter set. 11 in. x 14 in. printing frame with copying facilities. Measuring flask. Three trays, three tweezers. Three plastic bottles. Clips. Printing paper. Antistatic brush for cleaning negatives. Kodak Photoguide Booklet. Man's protective apron. £75 o.n.o. Pair of Goodman's speakers 8 ohms, 15 watts, £50 o.n.o. R. L. Gee, 3 Longfellow Drive, Hutton, Essex, CM13 2QQ.

INTERESTED IN RTTY? You should find the "RTTY Journal" of interest. Published in California, U.S.A., it gives a wide outlook on the current RTTY scene; RTTY-DX; DXCC Honour Roll; VHF RTTY news; and up to date technical articles are included. Specimen copies 35p from: The Subscription Manager, RTTY Journal, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk, NR32 3PJ.


LEARN-KIT OSCILLOSCOPE, etc. £50. Telephone: Newcastle-Upon-Tyne 862813.

THE BRITISH AMATEUR ELECTRONICS CLUB for all interested in electronics. Four Newsletters a year. Library of technical books and magazines. Help for members by experts. U.K. & Eire £4.50. Europe £6. Airmail £7.50:- Sterling per year. Details from Hon. Sec., J. G. Margetts, 3 Bishopstone Close, Golden Valley, Cheltenham, Glos.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

(Continued on page 255)

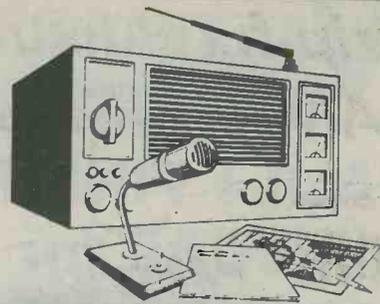

BECOME A RADIO AMATEUR

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

No previous knowledge required.

Brochure without obligation to :-

British National Radio & Electronic School

4 Cleveland Road, Jersey, Channel Islands.

Name

Address

REC/12/815

BLOCK CAPS PLEASE

MARCO TRADING

To obtain a free copy of our 35 page list simply send a 20p postage stamp or a large SAE. This advertisement shows only a part of our range. (Our new list includes Tants, Electrolytics, Disc ceramics, etc.)

400m/w ZENER DIODES

Low Price
3V6, 3V9, 4V3, 4V7, 5V1, 5V6, 6V2, 6V8, 7V5, 8V2, 9V1, 10V, 11V, 12V, 13V, 13V5, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V
Price: 8p each 100 any mix £6.00

RESISTORS

1/4W at 40°C 5% tol., 2.2 Ω to 2M2, E12 2p each.
Resistor Pack - 2.2 Ω - 2M2, 10 each value (730 resistors) £6.00

1 watt ZENER DIODES

3V3 to 200V Full range
I.C. Sockets
Price 15p each 100 any mix £12.50
8 DIL 10p 22 DIL 23p
14 DIL 13p 24 DIL 24p
16 DIL 15p 28 DIL 28p
18 DIL 18p 40 DIL 40p
20 DIL 22p

TANT. BEAD CAPS

| | | | |
|----------|-----|---------|-----|
| 0.1/35v | 12p | 4.7/35v | 12p |
| 0.22/35v | 12p | 33/6.3v | 25p |
| 1.0/35v | 12p | 47/10v | 30p |

SUB. MIN. TOGGLE SWITCHES

| | |
|--------|-----|
| SPST - | 70p |
| SPDT - | 78p |
| DPDT - | 82p |
| DPDT - | 90p |



BRIDGE RECTIFIERS

| | | | |
|-------------|-------|-------------|-------|
| 2.5 Amp 50V | 32p | 400V | 50p |
| 400V | 43p | 6.0 Amp 50V | 70p |
| 800V | 58p | 200V | 78p |
| 2.0 Amp 50V | 35p | 400V | 85p |
| 100V | 42p | 25 Amp 100V | £2.41 |
| 25 Amp 50V | £2.38 | | |

VEROBOARD (Copper Clad)

| | | |
|------------|------|------|
| Size Inch | 0-1" | 0.15 |
| 2.5 x 1 | 20p | N/A |
| 2.5 x 5 | 55p | 56p |
| 2.5 x 3.75 | 46p | 50p |

Speakers 8" x 5" x 3 ohm £1.50 each.

CONNECTING CABLE

Black. Blue. Green. Grey. Orange. Pink. Red. White. Violet. Yellow. Brown.
Singles 5p per metre
7/0.2mm 5p per metre
16/0.2mm 8p per metre

SPECIAL OFFERS

BRAND NEW METAL SLIDER POTENTIOMETERS

| | | | | |
|-------------------|-----|------|--------------------------|--------------------------|
| 60mm TRACK | 1+ | 100+ | Mains Rocker switch with | BZY96 ZENERS (21W) - 6V2 |
| 500 ohm Lin. Mono | 35p | 28p | Neon 10A. | 1+ 20p each |
| 50K Log. Stereo | 40p | 30p | D.P.S.T. | 100+ 12p each |
| 100K Lin. Stereo | 40p | 30p | 65p each | |
| 1 Meg Log. Stereo | 40p | 30p | | |

Other values available in 45mm track - send for list.

Send your orders to:

DEPT DP11, MARCO TRADING, THE OLD SCHOOL, EDSTAGON, Nr. WEM, SHROPSHIRE SY4 5RJ

Tel: Whixall (094872) 464/465

Please add 30p postage and packing to each order and add 15% VAT to your total order. Export add NO VAT but add postage. Air/Sea at cost.

TV

FAULT FINDING MANUAL for 405/625 LINES



£1.20

P. & P. 27p

REVISED & ENLARGED EDITED BY J. R. DAVIES

132 pages

Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

UNDERSTANDING TELEVISION

by

J. R. DAVIES



Over 500 pages
300 diagrams

£3.95

P. & P. £1.00

UNDERSTANDING TELEVISION deals with:

- Principles of 405 line reception
- Principles of 625 line reception
- Nature of the television signal
- Receiver tuner units
- A.F. and video amplifiers
- Deflector coil assemblies
- Automatic gain and contrast control
- Receiver aerials
- The cathode ray tube
- Receiver i.f. amplifiers
- Vertical and horizontal timebases
- Synchronising
- Power supply circuits
- Colour television
- **COLOUR TELEVISION** – 80 page comprehensive introduction to the subject

The reader is required to have only a basic knowledge of elementary radio principles. The treatment is non-mathematical throughout, and there is no necessity for any previous experience in television whatsoever. At the same time UNDERSTANDING TELEVISION is of equal value to the established engineer because of the very extensive range it covers and the factual information it provides

To Data Publications Ltd., 57 Maida Vale, London, W9 1SN

Please supply the 4th revised edition of TV FAULT FINDING, Data Book No. 5

Please supply UNDERSTANDING TELEVISION, Data Book No. 17

I enclose cheque/crossed postal order for (Tick which book is required)

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

SMALL ADVERTISEMENTS

(Continued from page 253)

BROADLANDS RESIDENTIAL CLUB for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: - The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NR8 8SS.

SPONSORS required for exciting scientific project Norwich Astronomical Society are building a 30" telescope to be housed in a 20" dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, 195 White Woman Lane, Old Catton, Norwich, Norfolk.

NORTHAMPTON: Television and Electrical Goods and Repairs. Old established business in freehold premises retail shop - well known local name. For Sale as a going concern plus s.a.v. Price £22,000 includes Shop, small workroom, private car park. Very busy main road position between public house and car showrooms. Apply:- Jackson-Stops & Staff, 20 Bridge Street, Northampton.

SITUATION VACANT

WANTED: Representatives to sell Electronic Components to shops and industries on good commission basis. Please send full details of experience to: Sunmit Electronics, 96 Peel Road, Wembley, Middlesex. Telephone: 01-904-6792.

PRINTED CIRCUIT BOARDS FOR "RADIO & ELECTRONICS CONSTRUCTOR" PROJECTS.

"Two 20dB amplifiers" Board for part 1 68p plus 25p P&P
Board for part 2 62p plus 25p P&P

All boards ready for use, roller tinned and drilled, glassfibre.

Trade enquiries welcome. Highly competitive prices. Write now for quote To:

BRB PRINTED CIRCUITS (REC)

109, Potter Street, Worksop,
Notts. S80 2HL.

DURRANT RADIO

(Electronic Components)

9 St. Mary's Street, Shrewsbury SY1 1EB.
Tel. 61239

Prices include V.A.T. Please add 35p P&P.

100 Cable ties 50p. 100 Assorted resistors 60p.
100 Assorted resistors 60p. 100 P.C.B. spacers 40p
100 Assorted capacitors £1.50. 100 Rivets mixed 35p.
100 Lengths of Heat Shrink Sleeving 40p.
50 Micro switches (mixed) £2.50
100 Self tapping screws 50p. 100 8 BA Bolts mixed 50p.
100 4 BA Bolts mixed 50p. 100 6 BA Bolts mixed 50p.
50 Solder tags 25p. 50 Reed switches £2.00
100 Presets mixed £2.00. 50 Fuses 250 ma 1 1/2in. £1.50
100 P-Clips mixed £1.00. 10 OA91 Diodes £1.10.
10 Nixie tubes on panels £1.25. 50 Rubber Grommets 40p.
10 P.C.Bs with markings for P.S.U. panels 80p.
10 Mullard OC 71 Transistors £2.20.
10 Assorted Micro switches 60p. 100 Brass eyelets 25p.
100 .022 mfd Polyester Capacitors £2.00.
.047 mfd Polyester C280 Capacitors 4p each £3.00 100.
470 K. Lin Pots with 1/2in. dia. shaft 40p. each.
1N4001-7 Diodes 8p each or 50p. per 10.
Diodes 1amp 300 volts 40p per 10.
8 way Terminal blocks 20p each.
Rotary switches 1p 2w Centre off 25p each.
1N4148 Diodes 5p each. 1N914 Diodes 6p each.
Panels with 2 phono sockets & 1 d.i.n. socket 40p each.
28 Volt Les Bulbs 8p each. Spade connectors 15p doz.
Relays 24v D/P C/O plug in type 50p each.
32 mfd 450 v Can type capacitors 40p each.
Multi-turn presets 5k 25p each.
Presets 250k 5p each. 2.5m Presets 5p each.
Electro magnets (works from 1 1/2 to 6 volts) 40p each.
Tag strip 7 way 8p each. Fuseholders 9p each.
Ferrite rods 6in 35p each. 50 Circlips mixed 25p.
Resistors 1/2 watt 2p each. 1/4 watt 3p each.
C-Mos 4013 I/Circuits flip-flops 20p each.
LEDs. .125" 14p each, .2" 15p each.
BC107-8-9 Transistors 10p each.
Capacitors 32 x 32 MFD 450v 45p. each.

We stock 1000s of components too numerous to list.
Why not pay us a visit when in the Shrewsbury area.

AERIAL SPLITTERS

2-UHF Televisions from one aerial.
Price £1.70.
10-Moulded Co-ax Plugs £1.20.
Low loss Co-ax Cable white 15p
per metre.

100 MULLARD C280/C281 CAPACITORS

Values from .01uf to 1.5uf 250V/W, our choice, good mixed selection. Price per 100 £2.00

AERIAL AMPLIFIERS

Aerial amplifiers can produce remarkable improvement on the picture and sound in fringe or difficult areas.
B45 - for mono or colour this is tunable over complete UHF television band.
B11 - for stereo or standard VHF/FM radio.
B11A - 2 metres Aircraft bands.

All amplifiers are complete and ready to use.

(Battery type PP3 or 8v to 18v ac, next to the set type fitting. Prices £6.70 each.

SIGNAL INJECTORS with (pre-set) variable AF, which emits RF harmonics into the UHF band. Protected up to 300 volts dc. Complete with leads £5.70 each.
All prices include VAT at 15% P&P per order 30p. S.A.E. for leaflets. Access cards.

ELECTRONIC MAILORDER LTD,

62 Bridge Street, Ramsbottom,
Via Bury, Lancs. BL0 9AGC. Tel. Ramsbottom 3036

BUILD YOUR OWN

P.A., GROUP & DISCO SPEAKERS by R. F. C. Stephens
Save money with this practical guide. Plans for 17 different designs. Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

THE INFRA-BASS LOUDSPEAKER by G. Holliman
(full constructional details for versions using 15", 12" and 10" (drive units). £2.95 post free (\$6 overseas).

THE DALESFORD SPEAKER BOOK by R. F. C. Stephens
This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

VAN KAREN PUBLISHING
5 Swan Street, Wilmslow, Cheshire

RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price 60p each, p&p 18p

Issue(s) required

Annual Subscription

Price £9.50 inland, £10.50 overseas (including Eire)

post free, commence with issue

Bound Volumes:

| | | |
|----------|-------------------------------|-------------------------------|
| Vol. 27. | August 1973 to July 1974 | Price £3.00, post & pkg £1.30 |
| Vol. 28. | August 1974 to July 1975 | Price £3.20, post & pkg £1.30 |
| Vol. 29. | August 1975 to July 1976 | Price £3.50, post & pkg £1.30 |
| Vol. 30. | August 1976 to July 1977 | Price £3.70, post & pkg £1.30 |
| Vol. 31. | August 1977 to August 1978 | Price £5.20, post & pkg £1.30 |
| Vol. 32. | September 1978 to August 1979 | Price £5.50, post & pkg £1.30 |

CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,

maroon only

Price £2.25, post & pkg 50p

With no title on spine, maroon

Price £2.25, post & pkg 50p

With no title on spine, green

Price £2.25, post & pkg 50p

Prices include V.A.T.

DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages

Price £1.20, P.&P. 27p

DB6 Radio Amateur Operator's Handbook,

New edition in course of preparation

DB17 Understanding Television, 504 pages

Price £3.95, P. & P. £1.00

DB19 Simple Short Wave Receivers

Price 80p, P. & P. 27p

140 pages

STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording - White

- 6 sheets

Price £1.50, P. & P. 11p

Set 4: Wording - Black

- 6 sheets

Price £1.50, P. & P. 11p

Set 5: Dials

- 6 sheets

Price £1.50, P. & P. 11p

Prices include V.A.T.

I enclose Postal Order/Cheque for in payment for

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable through your local bookseller

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS


VOLTAGE REGULATORS

A voltage regulator is intended to provide a nearly constant supply voltage for a load despite varying load current and varying regulator input voltage. In (a) the zener diode is a reverse biased silicon diode which is designed to break down at a specific voltage. The voltage-current characteristic is shown in (b). As the reverse voltage approaches the breakdown zener voltage reverse current starts to flow and, after some curvature, produces nearly a straight line graph. V_s divided by I_s is the zener "slope resistance". The value of R in (a) is chosen to ensure that, within its permitted dissipation figure, the zener diode functions on the straight part of its characteristic at all load currents and unstabilized input voltages.

In (c) the added emitter follower carries nearly all the load current, so that variations in the latter have only a small effect on zener diode current.

The forward biased light-emitting diode of (d) drops a voltage of typically 1.6 volts which increases only slightly with increasing forward current. It may in consequence be used as a voltage regulator. So also, as in (e), may a series chain of forward biased silicon diodes, each of which drops around 0.6 volt, again with a zener-type voltage-current characteristic.

An amplified voltage regulator is illustrated in (f). A reference voltage from the zener diode is applied to the non-inverting input of the amplifier whilst a fraction of the regulated output voltage is applied to the inverting input, giving the relationship shown. Any very small change in regulated voltage at once produces an amplified correcting voltage in the opposite direction at the amplifier output, and a very high level of voltage regulation results.

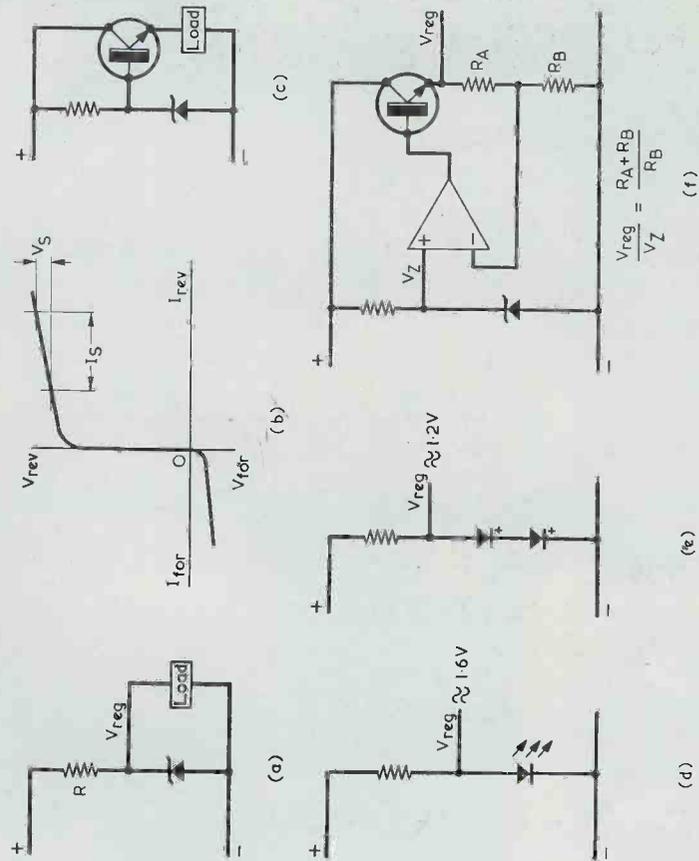

The new MAPLIN CATALOGUE is out on December 5th

A massive new catalogue from Maplin that's bigger and better than ever before. If you ever buy electronic components this is the one catalogue you must not be without. Over 300 pages, it's a comprehensive guide to electronic components with thousands of photographs and illustrations and page after page of invaluable data. We stock just about every useful component you can think of. In fact, well over 5000 different lines, many of them hard to get from anywhere else. Hundreds and hundreds of fascinating new lines, more data, more pictures and a new layout to help you find things more quickly.

MAPLIN

Maplin Electronic Supplies Ltd.
All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 554155. Sales (0702) 552911.
Shops:
159-161 King Street, Hammersmith, London W6. Telephone: (01) 748 0926.
284 London Road, Westcliff-on-Sea, Essex. Telephone: Southend (0702) 554000.
Both shops closed Mondays.



On sale
in all branches
of W H Smith
from Dec 5th
price £1

Breadboard 1980

26th to 30th November
Open 10 a.m. till 6 p.m. (and till
8 p.m. Thursday, 4 p.m. Sunday)
Royal Horticultural Halls,
Elverton Street, London
(Nr. St. James's Park Underground)
Visit our huge stand and
see our new 'single-chip' organ,
a new sequencer/composer,
and lots more.
Don't miss it!!

Post this coupon now for your copy of our 1981 catalogue price £1.

Please send me a copy of your 320 page catalogue. I enclose £1 (Plus 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.68 or 12 International Reply Coupons.

I enclose £1.25

Name _____

Address _____

REC 12-80