

WILLIAMS



# RADIO & ELECTRONICS

## CONSTRUCTOR


JANUARY 1981  
60p
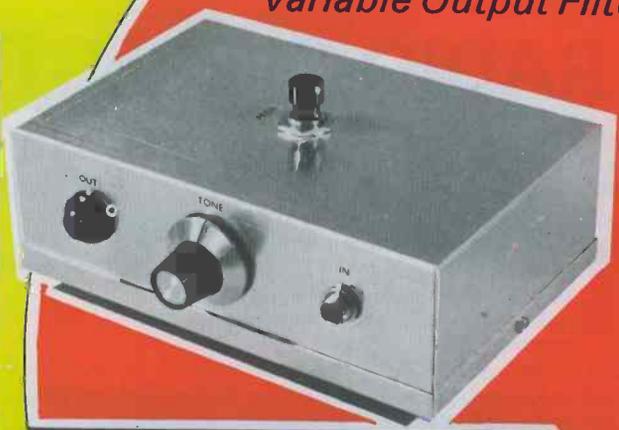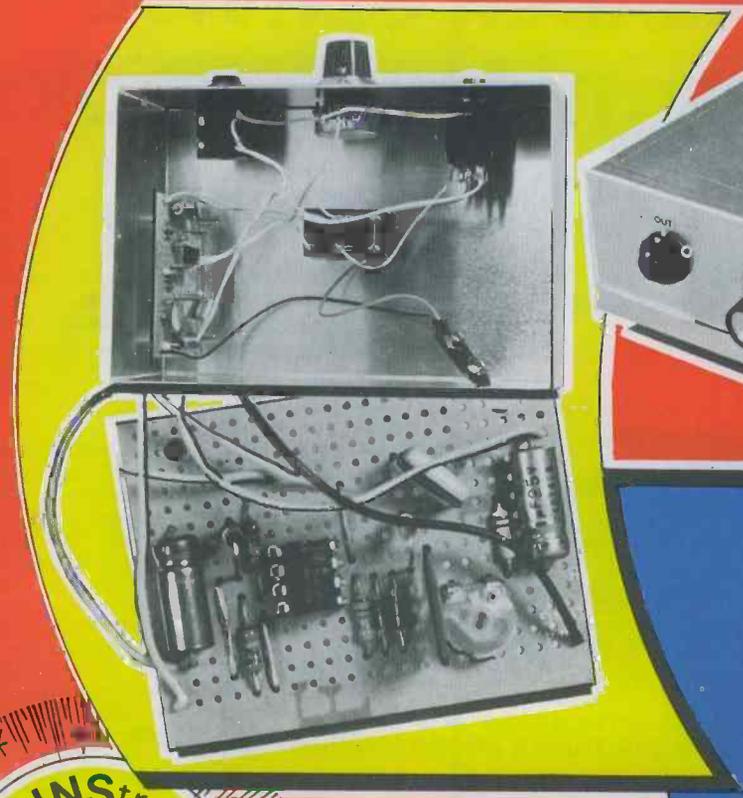
# FUZZ BOX

SILICON DIODE  
CLIPPING ACTION  
*Variable Output Filter*




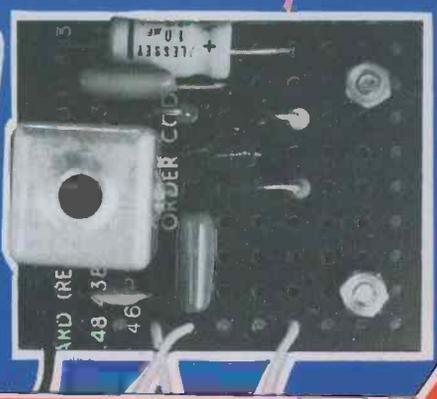The **INSTRUCTOR**  
LEARN ABOUT  
MICRO-  
PROCESSORS  
**SERIES 6**



IDEAL FOR SIGNAL TRACING

## DOUBLE OUTPUT TEST OSCILLATOR

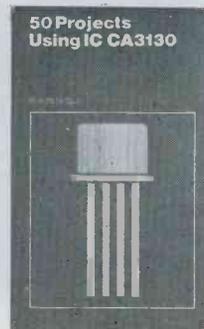

# DIRECT READER SERVICE RADIO & ELECTRONICS BOOKS

18. 50 Projects Using IC CA3130	£1.25	40. Projects in Opto-Electronics	£1.25
19. 50 CMOS IC Projects	£1.25	41. Radio Circuits Using IC's	£1.35
20. A Practical Introduction to Digital IC's	95p	42. Mobile Discotheque Handbook	£1.35
22. Beginners Guide to Building Electronic Projects	£1.25	43. Electronic Projects for Beginners	£1.35
23. Essential Theory for the Electronics Hobbyist	£1.25	44. Popular Electronic Projects	£1.45
26. 52 Projects Using IC741	95p	45. IC LM3900 Projects	£1.35
28. Two Transistor Electronic Projects	85p	46. Electronic Music and Creative Tape Recording	£1.25
29. How to Build Your Own Metal and Treasure Locators	£1.00	47. Practical Electronic Calculations and Formulae	£2.25
30. Electronic Calculator Users Handbook	95p	48. Radio Stations Guide	£1.45
31. Practical Repair and Renovation of Colour TVs	£1.25	49. Electronic Security Devices	£1.45
32. Handbook of IC Audio Pre-amplifier and Power Amplifier Construction	£1.25	50. How to Build Your Own Solid State Oscilloscope	£1.50
33. 50 Circuits Using Germanium, Silicon and Zener Diodes	75p	51. 50 Circuits Using 7400 Series IC's	£1.45
34. 50 Projects Using Relays, SCR's and TRIACS	£1.25	52. Second Book of CMOS IC Projects	£1.50
35. Fun and Games with your Electronic Calculator	75p	53. Practical Construction of Pre-Amps, Tone Controls, Fitters & Attenuators	£1.45
36. 50 (FET) Field Effect Transistor Projects	£1.25	54. Beginners Guide to Digital Techniques	95p
37. 50 Simple L.E.D. Circuits	75p	55. 28 Tested Transistor Projects	£1.25
38. How to Make Walkie-Talkies	£1.25	56. Digital IC Equivalents and Pin Connections	£2.50
39. IC 555 Projects	£1.75	57. Linear IC Equivalents and Pin Connections	£2.75

POSTAGE: 20p PER BOOK. IF MORE THAN 3 BOOKS ORDERED: 10p PER BOOK

To: Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please send me within 21 days . . . . . copy/copies

Book Nos: . . . . .

. . . . .

I enclose Postal Order/Cheque for £ . . . . .

Name . . . . .

Address . . . . .

. . . . .

(Block Letters Please)

*(We regret this offer is only available to readers in the U.K.)*

# RADIO & ELECTRONICS CONSTRUCTOR

**JANUARY 1981**  
**Volume 34 No. 5**

**Published Monthly**

*First published in 1947*

**Incorporating The Radio  
Amateur**

*Editorial and Advertising Offices*  
**57 MAIDA VALE LONDON W9 1SN**

*Telephone*  
01-286 6141

*Telegrams*  
Databux, London

©Data Publications Ltd., 1980. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

**Annual Subscription:** £9.50, Eire and Overseas £10.50 (U.S.A. and Canada \$25.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

**Technical Queries.** We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

**Correspondence** should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

**Opinions** expressed by contributors are not necessarily those of the Editor or proprietors.

**Production** – Web Offset.

<b>TRANSISTOR GAIN METER – Suggested Circuit</b> by G. A. French	270
<b>CAR VOLTAGE MONITOR</b> BY I. Peterson	273
<b>NEWS AND COMMENT</b>	274
<b>EXPERIMENTAL ELECTRONICS</b> by R. J. Caborn	276
<b>DOUBLE OUTPUT TEST OSCILLATOR</b> by R. A. Penfold	278
<b>MEDDLE MONITOR</b> by F. Bowden	282
<b>AMATEUR RADIO SATELLITES</b> Report by Arthur C. Gee	284
<b>SHORT WAVE NEWS – For DX Listeners</b> by Frank A. Baldwin	285
<b>FUZZ BOX</b> by I. M. Attrill	288
<b>The INSTRUCTOR – A Practical Introduction to Micro-processors – Part 6</b> by Ian Sinclair	293
<b>MEASURING ELECTROLYTICS</b> by T. H. Reynolds	297
<b>A CENTURY OF GMT – BBC World Service Report</b>	299
<b>NEW PRODUCTS</b>	300
<b>OHMS PER VOLT – Notes For Newcomers</b> by D. Snaith	301
<b>REGULATOR CIRCUITS</b> by D. H. Trent	302
<b>RADIO TOPICS</b> by Recorder	304
<b>THE TRANSFORMER WITH A MEMORY – In Your Workshop</b>	307
<b>CURRENT CHECKERS</b> by P. G. Smith	312
<b>TRADE NEWS</b>	313
<b>TRUTH TABLES</b> Electronics Data No. 65	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The *Radio & Electronics Constructor* is printed by LSG Printers, Portland Street, Lincoln.

**OUR NEXT ISSUE  
WILL BE PUBLISHED  
MID-JANUARY**

### BOOKS BY BABANI

BOOK NO	DESCRIPTION	£ p
BP6	Engineers & Machinists Ref. Tables	0.75
BP14	2nd Book Transistor Equivs & Subs	1.10
BP24	52 Projects Using IC741 (or equiv)	0.98
BP26	Radio Antenna Book Long Distance Reception & Transmission	1.00
BP27	Giant Chart of Radio Electronic Semi-conductor & Logic Symbols	0.60
BP32	Build Metal Treasure Locators	1.00
BP34	Practical Repair & Renovation of Colour TVs	1.25
BP35	Handbook of IC Audio Pre-amplifier	1.25
BP36	50 Ccts use Germ/Sil/Zener Diodes	0.75
BP37	50 Projects using Relays / SCRs / Triacs	1.25
BP39	50 Field Effect Trans Projects	1.25
BP40	Digital IC Equivs & Pin Connection	2.60
BP41	Linear IC Equivs & Pin Connection	2.75
BP43	How to make Walker Talkies	1.90
BP44	IC5555 Projects (Revised & Enlarged Edition)	1.75
BP45	Projects on Opto-electronics	1.25
BP46	Radio Circuits using ICs	1.35
BP47	Mobile Discotheque Handbook	1.35
BP48	Electronics Projects for Beginners	1.35
BP49	Popular Electronic Projects	1.45
BP50	IC LM3900 Projects	1.35
BP51	Electronic Music & Creative Tape Recording	1.25
BP52	Long Distance Television Reception (TV-DX) For the Enthusiast	1.95
BP53	Practical Electronic Calculations & Formulae	2.25
BP55	Radio Stations Guide	1.45
BP56	Electronic Security Devices	1.45
BP57	How to Build Your Own Solid State Oscilloscope	1.90
BP58	50 Circuits using 7400 Series ICs	1.35
BP59	Second Book of CMOS IC Projects	1.60
BP60	Practical Construction of Pre-amps / Tone Controls / Filters & Atn	1.45
BP61	Beginners Guide to Digital Techniques	0.85
BP62	Elements of Electronics — Book I	2.25
BP63	Elements of Electronics — Book II	2.25
BP64	Elements of Electronics — Book III	2.25
BP65	Single IC Projects	1.90
BP66	Beginners Guide to Microprocessors & Computing	1.75
BP67	Circuit driver & numeral Display projects	1.75
BP68	Choosing & Using your Hi-Fi	1.85
BP69	Electronic Games	1.75
BP70	Transistor Radio Fault-Finding Chart	0.80
BP180	Coil Design & Construction Manual	0.75
BP202	Handbook of Integrated Circuits Equivs & Substitutes	1.00
BP211	First Book of Diode Characteristics & Equivalents	1.25
BP213	Electronic Circuits for Model Railways	1.00
BP215	Shortwave Circuits & Gear for Experimenters & Radio Hams	0.85
BP221	28 Tested Transistor Projects	1.25
BP224	50 CMOS IC Projects	0.95
BP226	Build Advanced Short wave receivers	1.20
BP227	Beginners Guide to Building Electronic Projects	1.25
RCC	Resistor Colour Code Disc	0.20

### BRACKETS

Right-angle mounting brackets. Ideal for mounting PCB panels at cetera into boxes and cases.

18SWG — Mild steel — short face has slotted hole 6.5cm x 3.7cm long face has 3.7cm diam hole

O/NO 1726 Height 15cm, length 15cm, width 10cm £0.06

O/NO 1727 Height 25cm, length 15cm, width 10cm £0.07

### SWITCHES

Description	No.	Price
DPDT miniature slide	1973	£0.18
DPDT standard slide	1974	£0.17
Toggle switch SPST 1 1/2 amp 250V ac	1975	£0.38
Toggle switch DPDT 1 amp 250V ac	1976	£0.48
Rotary on/off mains switch	1977	£0.58
Push switch — Push to make	1978	£0.16
Push switch — Push to break	1979	£0.21

ROCKER SWITCH	Colour	No.	Price
A range of rocker switches SPST — moulded in high insulation material available in a choice of colours ideal for small apparatus	RED	1980	£0.35
	BLACK	1981	£0.35
	WHITE	1982	£0.35
	BLUE	1983	£0.35
	YELLOW	1984	£0.35
	LUMINOUS	1985	£0.35

Description	No.	Price
Miniature SPST toggle 2 amp 250V ac	1958	£0.81
Miniature SPST 2 amp 250V ac	1959	£0.86
Miniature DPDT toggle 2 amp 250V ac	1960	£0.92
Miniature DPDT toggle centre off 2 amp 250V ac	1961	£1.09
Push-button SPST 2 amp 250V ac	1962	£1.04
Push-button SPST 2 amp 250V ac	1963	£1.09
Push-button DPDT 2 amp 250V ac	1964	£1.38

**MIDGET WAFER SWITCHES**  
Single bank wafer type — suitable for switching at 250V ac, 100mA or 150V dc in non-reactive loads make before-break contacts. These switches have a spindle 0.25 in dia and 30 indexing.

Description	No.	Price
1 pole	1965	£0.55
2 pole	1966	£0.55
3 pole	1967	£0.55
4 pole	1968	£0.55

Micro Switches	No.	Price
Plastic button gives simple 1 pole change over action Rating 10 amp 250V ac	1970	£0.29

### ANTEX IRONS

1943	15 watt iron element ceramic fitted with 3/32" bit	£5.12
1947	Replacement element for 1943 iron	£2.33
1944	Iron coated bit 3/32" for 1943 iron	£0.58
1945	Iron coated bit 1/8" for 1943 iron	£0.58
1946	Iron coated bit 3/16" for 1943 iron	£0.58
1948	General purpose 18 watt iron fitted with iron coated bit	£5.12
1952	Replacement element for 1948 iron	£2.22
1949	Iron coated bit 3/32" for 1948 iron	£0.58
1958	Iron coated bit 1/8" for 1948 iron	£0.58
1951	Iron coated bit 3/16" for 1948 iron	£0.58
1931	Highly popular 25-25 watt quality iron ceramic shafts to provide near perfect insulation breakdown voltage of 1500 volts AC and a leakage current of only 3.5uA and another shaft of stainless steel to ensure strength	£5.12
1935	Replacement element for 1931 iron	£2.22
1932	Iron coated bit 1/8" for 1931 iron	£0.58
1933	Iron coated bit 3/16" for 1931 iron	£0.58
1934	Iron coated bit 1/2" for 1931 iron	£0.58
1953	SK1 kit contains 15 watt iron with a 3/16" bit plus two spare solder, heat-sink and a booklet 'How to solder', in presentation display box	£7.28

### VEROBOARD

2201	2.5" x 5" .1 Copper	£0.71	2211	2.5" x 2.5" .15 Copper	£0.63
2202	2.5" x 3.75" .1 Copper	£0.81	2212	3.75" x 17" .15 Copper	£2.39
2203	2.5" x 17" .1 Copper	£2.14	2213	3.75" x 5" .15 Copper	£0.99
2204	3.75" x 3.75" .1 Copper	£0.71	2217	3.75" x 17" .1 Plain	£1.78
2205	3.75" x 17" .1 Copper	£2.78	2218	3.75" x 2.5" .1 Plain	£0.44
2207	4.75" x 17" .1 Copper	£3.61	2219	5" x 3.75" .1 Plain	£0.60
2208	2.5" x 1" .5 lb pack	£0.85	2223	2.5" x 5" .15 Plain	£0.37
2210	3.75" x 5" .1 Copper	£0.79	2225	2.5" x 3.75" .15 Plain	£0.56
2212	2.5" x 5" .15 Copper	£0.64			

### BIB HI-FI ACCESSORIES

806	J Compact tape head cleaning kit	£1.22
810	23 Tape Editing kit	£2.85
811	24 Cassette Tape editing and joining kit	£2.76
813	29A Splice cassette	£0.81
814	31 Cassette Head cleaning tape	£0.71
817	36A Record & Stylus cleaning kit	£0.48
818	41 B-track Cartridge tape head cleaner	£1.24
819	42 Groove Klean auto metal record cleaner	£2.65
826	52A Cassette storage tray (holds 10)	£0.92
827	53 Hi-Fi stereo test cassette	£3.17
829	60 Chrome finish Groove Klean (plastic)	£2.12
834	69 Anti-static Hi-Fi cleaning liquid	£0.38
838	78 Cassette hand tape winder	£1.50

### WIRE CONNECTORS

Entirely new range of connectors for discrete wire. Uniquely designed Wirepac is soldered to the P.C. Board. A pre-stripped wire is inserted into the connector and easily locked by pressing the housing down. The wire is alternatively removed by lifting the housing. Tin alloy plated contacts ensure good as gold performance.

Housing consists of Thermo plastic polyester

1728	Single connector in red/black or white	£0.12 inc VAT
1729	Two-way connector black ONLY	£0.23 inc VAT
1730	Four-way connector black ONLY	£0.28 inc VAT

### FUSE HOLDERS AND FUSES

Description	No.	Price
20mm x 5mm chassis mounting	506	£0.18
1/4in x 1/4in chassis mounting	507	£0.14
1/4in car inline type	508	£0.18
Panel mounting 20mm	509	£0.23
Panel mounting 1/4in	510	£0.37

QUICK-BLOW 20mm	Type	No.	Type	No.	Type	No.		
150mA	611	7p	1A	615	8p	3A	619	8p
250mA	612	8p	1.5A	616	7p	4A	620	10p
500mA	613	8p	2A	617	6p	5A	621	8p
800mA	614	8p	2.5A	618	7p			

ANTI-SURGE 20mm	Type	No.	Type	No.	Type	No.
100mA	622	1A	625	2.5A	628	
250mA	623	2A	626	3.5A	629	
500mA	624	1A	627	5A	630	

QUICK-BLOW 1/4in	Type	No.	Type	No.	Type	No.
250mA	631	500mA	632	800mA	634	

Type	No.	Type	No.	Type	No.
1A	635	2.5A	638	4A	641
2A	637	3A	639	5A	642

### NUTS AND BOLTS

**BA BOLTS** — packs of BA threaded cadmium plated screws slotted cheese head. Supplied in multiples of 50

Type	No.	Price	Type	No.	Price
1/4in DBA	839	£1.38	1/4in 4BA	846	£0.37
1/4in DBA	840	£0.88	1/4in 4BA	847	£0.28
1/4in 2BA	842	£0.75	1/4in 6BA	848	£0.46
1/4in 2BA	843	£0.52	1/4in 6BA	849	£0.24
1/4in 2BA	844	£0.60	1/4in 6BA	850	£0.29
1/4in 4BA	845	£0.51			

**BA NUTS** — packs of cadmium plated full nuts in multiples of 50

Type	No.	Price	Type	No.	Price
DBA	855	£0.83	4BA	857	£0.35
2BA	856	£0.55	6BA	858	£0.28

**BA WASHERS** — flat cadmium plated plain stamped washers supplied in multiples of 50

Type	No.	Price	Type	No.	Price
DBA	859	£0.16	4BA	861	£0.14
2BA	860	£0.14	6BA	862	£0.14

**SOLDER TAGS** — Hot tinned supplied in multiples of 50

Type	No.	Price	Type	No.	Price
DBA	851	£0.46	4BA	853	£0.25
2BA	852	£0.32	6BA	854	£0.25

### AUDIO LEADS

No.	Type	Price
107	FM indoor Ribbon Aerial	£0.89
113	3.5mm Jack plug to 3.5mm Jack plug Length 1.5m	£0.85
114	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5 Length 1.5m	£0.88
115	5 pin DIN plug to 3.5mm Jack connected to pins 1 & 4 Length 1.5m	£0.98
116	Car aerial extension Screened insulated lead Fitted plug and socket	£1.44
117	AC mains connecting lead for cassette recorders and radios 2 metres	£0.78
118	5 pin DIN phono plug to stereo headphone Jack socket	£1.21
119	2+2 pin DIN plugs to stereo Jack socket with attenuation network for stereo headphones Length 0.2m	£1.04
120	Car stereo connector Variable geometry plug to fit most car cassettes B-track cartridge and combination units Supplied with inlined fuse power lead and instructions	£0.69
123	6 pin Coded Guitar Lead Mono Jack plug to Mono Jack plug Black	£1.73
124	3 pin DIN plug to 3 pin DIN plug Length 1.5m	£0.86
125	5 pin DIN plug to 5 pin DIN plug Length 1.5m	£0.88
126	5 pin DIN plug to Tinned open end Length 1.5m	£0.88
127	5 pin DIN plug to 4 Phono Plugs All colour coded Length 1.5m	£1.50
128	5 pin DIN plug to 5 pin DIN socket Length 1.5m	£0.92
129	5 pin DIN plug to 5 pin DIN plug mirror image Length 1.5m	£1.21
130	2 pin DIN plug to 2 pin DIN inline socket Length 5m	£0.78
131	5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5 Length 1.5m	£0.95
132	2 pin DIN plug to 2 pin DIN socket Length 10m	£1.13
133	5 pin DIN plug to 2 Phono plugs Connected pins 3 & 5 Length 1.5m	£0.88
134	5 pin DIN plug to 2 Phono sockets Connected pins 3 & 5 Length 23cm	£0.78
135	5 pin DIN socket to 2 Phono plugs Connected pins 3 & 5 Length 23cm	£0.78
136	Coded stereo headphone extension lead Black Length 6m	£2.01
178	AC mains lead for calculators, etc	£0.52

### TRANSFORMERS

MINIATURE MAINS Primary 240V		Price
No.	Secondary	
2021	6V-0.6V 100mA	£1.04
2022	9V-0.9V 75mA	£1.04
2023	12V-0.12V 100mA	£1.29

MINIATURE MAINS Primary 240V with two independent secondary windings		Price
No.	Secondary	
2024	MT280 6V-0.6V 6V RMS	£1.84
2025	MT150 0-12V 0-12V RMS	£1.84

1 AMP MAINS Primary 240V		Price
No.	Secondary	
2026	6V-0.6V 1 amp	£2.88 P & P 45p
2027	9V-0.9V 1 amp	£2.30 P & P 45p
2028	12V-0.12V 1 amp	£2.99 P & P 55p
2029	15V-0.15V 1 amp	£3.18 P & P 65p
2030	30V-0.30V 1 amp	£3.97 P & P 85p

STANDARD MAINS Primary 240V		Price
No.	Rating	
2031	1/2 amp	£3.81 P & P 85p
2032	2 amp	£5.06 P & P 85p
2033	2 amp	£6.27 P & P 11

2035 240V Primary 0.55V @ 2A Secondary £7.30 P & P 11

### CASES AND BOXES

# AND THERE'S MORE WHERE THIS CAME FROM

It's a long time since one of our adverts was presented in 'list' form - but simply because we do not try to squeeze this lot in every time doesn't mean that it's not available. Our new style price list (now some 40 pages long) includes all this and more, including quantity prices and a brief description. The kits, modules and specialized RF components - such as TOKO coils, filters etc. are covered in the general price list - so send now for a free copy (with an SAE please). Part 4 of the catalogue is due out now (incorporating a revised version of pt.1).

LINEAR ICs - NUMERIC LISTINGS		TTL N and LSN		7443N 1.15		74LS112 0.38		74LS169 2.00		VARICAP TUNING DIODES		TRANSISTORS AUDIO DEVICES		CAPACITORS	
TBA120S 1.00	KB4413 1.95	7400N 0.13	7444N 1.12	7444N 1.12	74LS113 0.38	74170N 2.30	74LS120 2.00	BAL02 0.30	BC237 0.08	All 5mm or less spacing		CERAMIC 50V			
L200 1.95	KB4417 1.80	74LS00 0.20	7445N 0.94	7445N 0.94	74LS114 0.38	74170N 2.30	74LS121 1.20	BAL21 0.30	BC238 0.08			2P2, 3P3, 4P7, 6P8			
U237B 1.28	TDA4420 2.25	7401N 0.13	7446N 0.94	7446N 0.94	74LS118 0.83	74171N 1.20	74LS122 0.46	ITT210 0.30	BC239 0.08			8P2, 10P, 15P, 18P...0.04			
U247B 1.28	KB4420B 1.09	74LS01 0.20	7447N 0.89	7447N 0.89	74120N 1.15	74175N 0.87	74LS123 0.73	BB204B 0.36	BC307 0.08			22P, 27P, 33P, 47P			
U257B 1.28	KB4423 2.65	7402N 0.14	7448N 0.56	7448N 0.56	74121N 0.42	74175N 1.10	74LS124 1.75	BB105B 0.36	BC308 0.08			56P, 68P, 82P, 100P...0.05			
U267B 1.28	KB4424 1.65	74LS02 0.20	7449N 0.99	7449N 0.99	74122N 0.46	74177N 0.78	74LS125 0.44	BB109 0.27	BC309 0.08			150P, 220P, 270P			
LM301H 0.67	KB4431 1.95	7403N 0.14	7450N 1.17	7450N 1.17	74123N 0.73	74178N 1.65	74LS126 0.57	MVM125 1.05	BC413 0.10			330P, 390P, 470P...0.055			
LM301N 0.30	KB4432 1.95	74LS03 0.20	7451N 0.17	7451N 0.17	74124N 1.75	74181N 1.35	74LS127 0.44	KV1210 2.45	BC414 0.11			1N0, 2N2, 3N3, 4N7...0.06			
LM308H 0.96	KB4433 1.52	7404N 0.14	7452N 0.17	7452N 0.17	74125N 0.38	74181N 1.35	74LS128 0.57	KV1215 2.75	BC415 0.07			10N (0.01uF)...0.05			
LM308N 0.65	KB4436 2.53	74LS04 0.20	7453N 0.17	7453N 0.17	74126N 0.44	74185N 1.34	74LS129 0.74	KV1225 2.55	BC416 0.08			22N, 47N, ...0.06			
LM339N 0.66	KB4437 1.75	7405N 0.18	7454N 0.24	7454N 0.24	74127N 0.57	74185N 1.34	74LS130 0.73	KV1226 1.95	BC417 0.10			100N, 220N, ...0.09			
LM348N 1.86	KB4438 2.22	74LS05 0.26	7455N 0.24	7455N 0.24	74128N 0.74	74189N 1.05	74LS132 0.73	KV1225 2.55	BC418 0.08			MONOLITHIC CERAMIC			
LF351N 0.38	KB4441 1.35	7406N 0.28	7456N 0.17	7456N 0.17	74129N 0.73	74192N 1.80	74LS133 0.60	KV1225 2.55	BC419 0.12			10N, 100N, ...0.16			
LF353N 0.76	KB4445 2.75	7407N 0.38	7457N 0.38	7457N 0.38	74130N 0.73	74193N 1.05	74LS134 0.60	KV1225 2.75	BC500 0.12			FEEDTHRU			
LM374N 3.75	KB4446 2.75	7408N 0.17	7458N 0.24	7458N 0.24	74131N 0.73	74193N 1.05	74LS135 0.60	SWITCHING AND PIN DIODES	BC501 0.12			1N0 SOLDER IN...0.09			
LM380N-14 1.00	KB4448 1.65	7409N 0.17	7459N 0.24	7459N 0.24	74132N 0.73	74194N 1.05	74LS136 0.60	SHOTTKY DIODES	BC502 0.12			POLYESTER (SMDs)			
LM380N-8 1.00	NE5044N 2.26	74LS08 0.24	7460N 0.17	7460N 0.17	74133N 0.73	74194N 1.05	74LS137 0.60	IN6263 0.62	BC503 0.12			10mm LEAD SPACING			
LM381N 1.81	NE5044N 2.26	7409N 0.17	7461N 0.17	7461N 0.17	74134N 0.73	74196N 0.99	74LS138 0.60	BAL82 0.19	BC504 0.12			30P, 390P, 470P...0.17			
ZN419CE 1.95	SD6000 3.75	74LS09 0.24	7462N 0.24	7462N 0.24	74135N 0.73	74196N 0.99	74LS139 1.10	BA244 0.17	BC505 0.12			47N, 68N, 100N, ...0.19			
NE544N 1.80	SL6270 2.03	7410N 0.15	7463N 0.24	7463N 0.24	74136N 0.73	74199N 1.60	74LS140 1.10	BA244 0.17	BC506 0.12			220N, 470N, ...0.22			
NE555N 0.30	SL6310 2.03	74LS10 0.24	7464N 0.28	7464N 0.28	74137N 0.73	74199N 1.60	74LS141 0.56	BA379 0.35	BC507 0.12			1uF, ...0.29			
NE556N 0.50	SL6600 3.75	7411N 0.20	7465N 0.38	7465N 0.38	74138N 0.73	74199N 1.60	74LS142 0.56	TD1061 0.95	BC508 0.12			POLYESTER (GENERAL)			
NE560N 3.50	SL6640 2.75	74LS11 0.24	7466N 0.37	7466N 0.37	74139N 0.73	74199N 1.60	74LS143 0.56	SIGNAL DIODES & RECTIFIERS	BC509 0.12			10mm LEAD SPACING			
NE562N 4.05	SL6690 3.20	7412N 0.17	7467N 0.38	7467N 0.38	74140N 0.56	74199N 1.60	74LS144 0.56	LN4148 0.06	BC510 0.12			10N, 15N, 22N, 33N...0.06			
NE564N 4.29	SL6700 2.35	74LS12 0.24	7468N 0.48	7468N 0.48	74141N 0.56	74199N 1.60	74LS145 0.97	LN4148 0.06	BC511 0.12			47N, 68N, 100N, ...0.08			
NE565N 1.00	ICL8038CC 4.50	7413N 0.30	7469N 0.48	7469N 0.48	74142N 0.56	74199N 1.60	74LS146 0.97	LN4148 0.06	BC512 0.12			22N, ...0.11			
NE566N 1.60	MSL9362 7.50	7414N 0.51	7470N 0.86	7470N 0.86	74143N 0.56	74199N 1.60	74LS147 0.97	LN4148 0.06	BC513 0.12			20mm LEAD SPACING			
NE570N 3.85	MSL9363 1.75	74LS15 0.24	7471N 0.86	7471N 0.86	74144N 0.56	74199N 1.60	74LS148 0.97	LN4148 0.06	BC514 0.12			10N, 15N, 22N, 33N...0.18			
SL624 3.28	HAL1211 1.95	7416N 0.30	7472N 0.86	7472N 0.86	74145N 0.56	74199N 1.60	74LS149 0.97	LN4148 0.06	BC515 0.12			MYLAR			
TB6651 1.81	HAL1223 2.15	7417N 0.30	7473N 0.86	7473N 0.86	74146N 0.56	74199N 1.60	74LS150 0.97	LN4148 0.06	BC516 0.12			5mm LEAD SPACING			
UA709HC 0.64	HAL1225 1.45	7418N 0.30	7474N 0.86	7474N 0.86	74147N 0.56	74199N 1.60	74LS151 0.97	LN4148 0.06	BC517 0.12			1N0, 10N, 22N, 33N...0.08			
UA709PC 0.36	HAL1202 1.45	74LS20 0.24	7475N 0.86	7475N 0.86	74148N 0.56	74199N 1.60	74LS152 0.97	LN4148 0.06	BC518 0.12			100N, ...0.09			
UA710HC 0.65	HAL1207 0.80	7421N 0.29	7476N 0.37	7476N 0.37	74149N 0.56	74199N 1.60	74LS153 0.97	LN4148 0.06	BC519 0.12			20mm LEAD SPACING			
UA710PC 0.59	HAL1202 1.45	74LS21 0.24	7477N 0.86	7477N 0.86	74150N 0.56	74199N 1.60	74LS154 0.97	LN4148 0.06	BC520 0.12			22N, 470N, ...0.17			
UA711HC 0.66	HAL1241 1.20	7423N 0.27	7478N 0.86	7478N 0.86	74151N 0.56	74199N 1.60	74LS155 0.97	LN4148 0.06	BC521 0.12			POLYSTYRENE			
UA711CN 0.27	HAL1242 1.55	7425N 0.27	7479N 0.86	7479N 0.86	74152N 0.56	74199N 1.60	74LS156 0.97	LN4148 0.06	BC522 0.12			10M, 15P, 18P, 22P,			
UA714CN 0.70	LF13741 0.33	7427N 0.27	7480N 0.86	7480N 0.86	74153N 0.64	74199N 1.60	74LS157 0.97	LN4148 0.06	BC523 0.12			27P, 47P, 56P, 68P...0.08			
UA748CN 0.36	SN7666CN 0.80	7428N 0.35	7481N 0.69	7481N 0.69	74154N 0.64	74199N 1.60	74LS158 0.60	LN4148 0.06	BC524 0.12			100P, 180P, 220P...0.08			
UA753 2.44		74LS28 0.32	7482N 0.78	7482N 0.78	74155N 0.54	74199N 1.60	74LS159 2.10	LN4148 0.06	BC525 0.12			270P, 330P, 390P...0.09			
UA758 2.35		7430N 0.17	7483N 0.53	7483N 0.53	74156N 0.80	74199N 1.60	74LS160 1.30	LN4148 0.06	BC526 0.12			470, 680P, 820P...0.10			
TBA10AS 1.09		74LS30 0.24	7484N 0.78	7484N 0.78	74157N 0.87	74199N 1.60	74LS161 0.78	LN4148 0.06	BC527 0.12			1N0, 1N2, 1N5, 1N8...0.11			
TBA20M 0.75		7432N 0.25	7485N 0.65	7485N 0.65	74158N 0.60	74199N 1.60	74LS162 1.30	LN4148 0.06	BC528 0.12			2N2, 2N7, 3N3, 3N9...0.12			
TC9A90E 1.80	SAAL056 3.75	74LS32 0.24	7486N 0.65	7486N 0.65	74159N 2.50	74199N 1.60	74LS163 0.78	LN4148 0.06	BC529 0.12			4N7, 5N6, 6N8, 10N...0.13			
TDA1028 2.11	SAAL058 3.35	7433N 0.40	7487N 0.86	7487N 0.86	74160N 0.82	74199N 1.60	74LS164 1.30	LN4148 0.06	BC530 0.12			TANTALUM BEAD CAPS			
TDA1029 2.11	SAAL059 3.35	7434N 0.40	7488N 0.69	7488N 0.69	74161N 0.92	74199N 1.60	74LS165 1.30	LN4148 0.06	BC531 0.12			16V, 0.22, 0.33,			
TDA1054 1.45	11C90DC 14.00	7435N 0.33	7489N 0.65	7489N 0.65	74162N 0.92	74199N 1.60	74LS166 1.30	LN4148 0.06	BC532 0.12			16V, 2.2, 4.7, 10...0.19			
TDA1062 1.95	LAN232 19.00	7436N 0.33	7490N 0.65	7490N 0.65	74163N 0.92	74199N 1.60	74LS167 1.30	LN4148 0.06	BC533 0.12			6V3, 22, 47, ...0.30			
TDA1072 2.69	LAN242 19.00	7437N 0.40	7491N 0.76	7491N 0.76	74164N 0.92	74199N 1.60	74LS168 1.30	LN4148 0.06	BC534 0.12			10V, 22, 100, ...0.35			
TDA1074A 5.04	MSL2318 3.84	7438N 0.33	7492N 0.78	7492N 0.78	74165N 0.78	74199N 1.60	74LS169 2.00	LN4148 0.06	BC535 0.12			ALUMIN ELECTROLYTICS			
TDA1083 1.95	MSM5523 11.30	7439N 0.33	7493N 0.53	7493N 0.53	74166N 0.92	74199N 1.60	74LS170 2.00	LN4148 0.06	BC536 0.12			RADIAL (VERT. MOUNT)			
TDA1090 3.05	MSM5524 11.30	7440N 0.17	7494N 0.65	7494N 0.65	74167N 0.92	74199N 1.60	74LS171 1.20	LN4148 0.06	BC537 0.12			(uF/voltage)			
HAL137 1.20	MSM5525 7.85	74LS38 0.24	7495N 0.65	7495N 0.65	74168N 0.92	74199N 1.60	74LS172 1.20	LN4148 0.06	BC538 0.12			1/63, 2/250, 4/7/35			
HAL196 2.00	MSM5526 7.85	7441N 0.74	7496N 0.65	7496N 0.65	74169N 0.92	74199N 1.60	74LS173 1.20	LN4148 0.06	BC539 0.12			10/16, 15/16, 22/10			
HAL197 1.00	MSM5527 9.75	7442N 0.70	7497N 0.86	7497N 0.86	74170N 2.30	74199N 1.60	74LS174 1.20	LN4148 0.06	BC540 0.12			33/6, 33/10, ...0.08			
TDA1220 1.40	MSM5527L 9.75	74LS42 0.99	7498N 0.65	7498N 0.65	74171N 1.20	74199N 1.60	74LS175 1.20	LN4148 0.06	BC541 0.12			22/16, 33/10,			
LM1303 0.99	ICM7106CP 9.55	7443N 0.85	7499N 0.78	7499N 0.78	74172N 1.20	74199N 1.60	74LS176 1.20	LN4148 0.06	BC542 0.12			47/10, ...0.09			
LM1307 1.55	ICM7107CP 9.55	4044 0.80	7480A/2 7.50	7480A/2 7.50	74173N 1.20	74199N 1.60	74LS177 1.20	LN4148 0.06	BC543 0.12			10/63, 22/50, 33/50,			
LM1310P 1.90	ICM7216B 19.25	4046 1.30	8212 2.30	8212 2.30	74174N 1.20	741									

# THE MODERN BOOK CO

## RADIO & TV SERVICING 1979-1980 Models by R. N. Wainwright £15.50

<b>ELECTRONIC FAULT DIAGNOSIS</b> By I. R. Sinclair	Price £3.50	<b>AUDIO AMPLIFIERS FOR THE HOME CONSTRUCTOR</b> by I. R. Sinclair	Price £3.50	<b>UNDERSTANDING ELECTRONIC CIRCUITS</b> by I. R. Sinclair	Price £4.50
<b>ELECTRONIC PROJECTS IN AUDIO</b> by R. A. Penfold	Price £2.50	<b>REPAIRING POCKET TRANSISTOR RADIOS</b> by I. R. Sinclair	Price £2.55	<b>UNDERSTANDING ELECTRONIC COMPONENTS</b> by I. R. Sinclair	Price £4.50
<b>OP-AMPS THEIR PRINCIPLES &amp; APPL.</b> by J. B. Dance	Price £2.50	<b>MAKING &amp; REPAIRING TRANSISTOR RADIOS</b> by W. Oliver	Price £2.30	<b>UNDERSTANDING SOLID-STATE ELECTRONICS</b> by Texas Inst.	Price £3.95
<b>PRINTED CIRCUIT ASSEMBLY</b> by M. J. Hughes	Price £2.10	<b>WORLD RADIO TV HANDBOOK</b> by J. M. Frost	Price £9.25	<b>A SIMPLE GUIDE TO HOME COMPUTERS</b> by S. Ditlea	Price £4.00
<b>ELECTRONIC SECURITY DEVICES</b> by R. A. Penfold	Price £1.65	<b>PROJECTS IN RADIO &amp; ELECTRONICS</b> by I. R. Sinclair	Price £2.50	<b>HOW TO BUILD A COMPUTER-CONTROLLED ROBOT</b> by T. Loofbourrow	Price £5.30
<b>UNDERSTANDING DIGITAL ELECTRONICS</b> by Texas Inst.	Price £4.00	<b>ELECTRONIC PROJECTS IN THE HOME</b> by O. Bishop	Price £2.50	<b>THE CATHODE-RAY OSCILLOSCOPE &amp; ITS USE</b> by G. N. Patchett	Price £4.00
<b>UNDERSTANDING MICRO-PROCESSORS</b> by Motorola	Price £4.30	<b>SIMPLE CIRCUIT BUILDING</b> by P. C. Graham	Price £2.20	<b>A GUIDE TO AMATEUR RADIO</b> by P. Hawker	Price £1.70
<b>THE FIRST BK OF MICROCOMPUTERS</b> by R. Moody	Price £3.35	<b>110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR</b> by R. M. Marston	Price £3.20	<b>MAKING TRANSISTOR RADIOS A BEGINNER'S GUIDE</b> by R. H. Warring	Price £2.90
<b>HOW TO BUILD YOUR OWN SOLID STATE OSCILLOSCOPE</b> by F. G. Rayer	Price £1.70	<b>HAM RADIO</b> by K. Uilyett	Price £5.00		
<b>THE OSCILLOSCOPE IN USE</b> by I. R. Sinclair	Price £3.50				


We have the Finest Selection of English and American Radio Books in the Country  
PRICES INCLUDE POSTAGE

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone: 01-402 9176
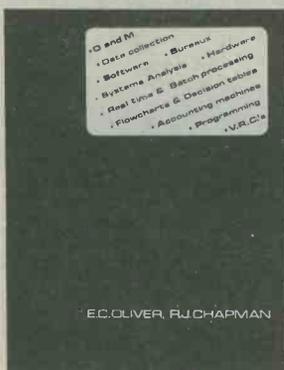
### DATA PROCESSING

An instructional Manual for Business and Accountancy Students



## UNDERSTAND DATA PROCESSING

NEW FOURTH EDITION

DATA PROCESSING, by Oliver & Chapman, is now in its Fourth Edition

200 pages 9½" x 6½"

PRICE £2.95

P.&P. 48p

PUBLISHED BY D.P. PUBLICATIONS

The primary aim of this outstanding manual is to provide a simplified approach to the understanding of data processing – (previous knowledge of the subject is not necessary).

The 40 chapters and appendices cover the following topics: Introduction to Data Processing; Organisation and Method; Conventional Methods; Introduction to EDP and Computers; Hardware; Computer Files; Data Collection and Control; Programming and Software; flowcharts and Decision Tables; Systems Analysis; Applications; Management of EDP, etc.


A Manual for Business and Accountancy Students

Available from:

**DATA PUBLICATIONS LTD.,**  
57 MAIDA VALE, LONDON W9 1SN.

# IT'S AS EASY AS A,B,C...

# ...ASK OUR DEALERS.

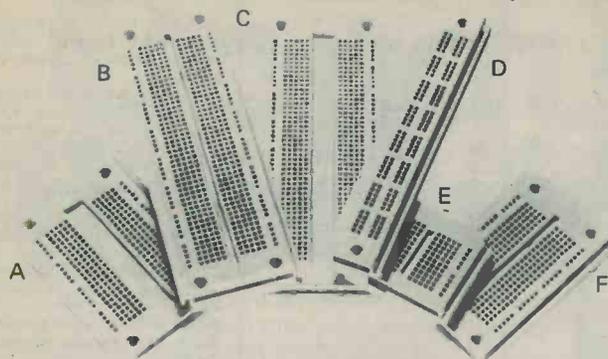

- A EXP 650 For microprocessor chips. **£3.60**
- B EXP 300 The most widely sold breadboard in the UK; for the serious hobbyist. **£5.75**
- C EXP 600 6" centre channel makes this the Microprocessor Breadboard. **£6.30**
- D EXP 4B An extra 4 bus-bars in one unit. **£2.30**
- E EXP 325 Built in bus-bars accepts 8, 14, 16 and up to 22 pin ICS. **£1.60**
- F EXP 350 270 contact points, ideal for working with up to 3 x 14 pin DIPS. **£3.15**
- G PB6 Professional breadboard in easily assembled kit form. **£9.20** (Not illustrated.)
- H PB 100 Kit form breadboard recommended for students and educational uses. **£11.80** (Not illustrated.)

### & IT'S AS EASY AS 1,2,3 with THE EXPERIMENTOR SYSTEM

- SCRATCHBOARD
- BREADBOARD
- MATCHBOARD

1. EXP 300PC which includes one item. A matchboard pre-drilled PCB - **£1.32**
2. EXP 302 which includes three items. Three 50-sheet scratchboard workpads - **£1.68**
3. EXP 303 which includes three items. Two matchboards and an EXP 300 solderless breadboard - **£8.60**
4. EXP 304 which includes four items. Two matchboards and EXP 300 breadboard and a scratchboard workpad - **£9.30**

The above prices do not include P&P and 15% VAT

## TOMORROW'S TOOLS TODAY

CONTINENTAL SPECIALTIES CORPORATION

C.S.C. (UK) Limited, Dept. 1600  
Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex CB11 3AQ.  
Tel: Saffron Walden (0799) 21682.  
Telex: 817477.



NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

I enclose cheque/PO for £ \_\_\_\_\_  
or debit my Barclaycard, Access, American Express card  
No. \_\_\_\_\_ Exp. date \_\_\_\_\_  
or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

A EXP 650 £5.00	Qty. Reqd.	B EXP 300 £7.76	Qty. Reqd.
C EXP 600 £8.39	Qty. Reqd.	D EXP 4B £3.50	Qty. Reqd.
E EXP 325 £2.70	Qty. Reqd.	F EXP 350 £4.48	Qty. Reqd.
G PB6 £11.73	Qty. Reqd.	H PB 100 £14.72	Qty. Reqd.

#### Experimentor System

1 EXP 300 PC £2.38	Qty. Reqd.	2 EXP 302 £2.79	Qty. Reqd.
3 EXP 303 £11.04	Qty. Reqd.	4 EXP 304 £11.85	Qty. Reqd.

Boxed prices include P & P and 15% VAT  
If no dealer in your area contact CSC direct. FREE catalogue tick box

Continental Specialties Corporation (UK) Limited, Dept. 1600  
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

AITKEN BROTHERS,  
35 High Bridge, Newcastle Upon Tyne, NE1 1EW.  
Tel: 0632 26729.

ARROW ELECTRONICS LTD.,  
Leader House, Coptfold Road, Brentwood, Essex.  
Tel: 0277 226470.

BASIC ELECTRONICS LTD.,  
18 Epsom Road, Guildford, Surrey, GU1 3JN.  
Tel: 0483 39984.

BI-PAK SEMICONDUCTORS,  
P.O. Box 6, Ware, Herts.  
Tel: 0920 3442.

F. BROWN & CO.,  
45 George IV Bridge, Edinburgh, EH1 1EJ, Scotland.  
Tel: 031 225 3461. Telex: 922131.

THE CHILDRENS SHOP & TACKLE BOX,  
73-75 High Street, Ryde, Isle of Wight.  
Tel: 0983 63437.

CUBEGATE LTD.,  
301 Edgware Road, London, W2 1BN.  
Tel: 01 724 3565.

ETESON ELECTRONICS,  
15b Lower Green, Poulton-Le-Fylde, Blackpool, FY6 7JL.  
Tel: 0253 885107.

H. GEE ELECTRONIC SUPPLIES,  
94a Mill Road, Cambridge, CB1 2BD.  
Tel: 0223 358019.

LEEDS AMATEUR RADIO,  
27 Cookridge Street, Leeds, LS2 3AG.  
Tel: 0532 452657.

MARSHALLS,  
108A Stokes Croft, Bristol.  
Tel: 0272 426801.

85 West Regent Street, Glasgow, G2, Scotland.  
Tel: 041 332 4133.

325 Edgware Road, London, W2.  
Tel: 01 723 4242.

40 Cricklewood Broadway, London, NW2 3ET.  
Tel: 01 452 0161.

RASTRA ELECTRONICS LTD.,  
275-281 King Street, Hammersmith, London, W6.  
Tel: 01 748 3143. Telex: 24443 RASTRA G.

SHUDEHILL SUPPLY COMPANY,  
53 Shudehill, Manchester, M4 4AW.  
Tel: 061 834 1449.

SPECTRON ELECTRONICS (M/C) LTD.,  
7 Oldfield Road, Salford, M5 4NE.  
Tel: 061 834 4583.

SWANLEY ELECTRONICS,  
32 Goldsel Road, Swanley, Kent, BR8 8EZ.  
Tel: 0322 64851.

TECHNOMATIC LTD.,  
17 Burnley Road, London, NW10 1ED.  
Tel: 01 452 1500. Telex: 922800.

## TOMORROW'S TOOLS TODAY

Also ask your local stockist.  
If no dealer in your area, contact CSC direct.

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited, Dept. 1600  
Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex CB11 3AQ.  
Tel: Saffron Walden (0799) 21682  
Telex: 817477

### MOTORS

1.5-6VDC Model Motors 22p. Sub. Min. 'Big Inch' 115VAC 3rpm Motors 32p. 6 volt standard cassette motors new £1.20. 8 track 12V Replacement Motors 55p. Ex. Equip. BSR record player motors, C129, C197 type, £1.20.

### SEMICONDUCTORS

LM340 80p. BY103 10p. 2N5062 100V 800mA SCR 18p. BX504 Opto Isolator 25p. CA3130 95p. CA3020 45p. 741 22p. 741S 35p. 723 35p. NE555 24p. 2N3773 £1.70. NE556 50p. ZN414 75p. BD238 28p. BD438 28p. CB4069 15p. 4" RedLed Displays, c.c. or c.a. 95p. TIL209 Red Leds 10 for 75p. Man3A 3mm Led Displays 40p. BY223 20p.

### PROJECT BOXES

Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 65p. 95 x 71 x 35mm 75p. 115 x 95 x 37mm 85p.

### MOTOROLA PIEZO CERAMIC TWEETERS

No crossover required



2.5" Direct Radiating Tweeter, maximum rating 25 volts R.M.S. 100 watts across 8 ohms. Freq. range 3.8kHz-28kHz, £3.65

### TOOL SALE

Small side cutters 5" insulated handles £1. Radiopliers, snipe nosed insulated handles £1. Heavy duty pliers insulated handles £1.10. Draper side cutters spring loaded £1.

### HANDY BENCH VICE

1" Jaw opening, £2.95.



Hand drill, double pinion with machine sut gears, 1/16", only £2.75p plus 50p p&p.

### MORSE KEYS

Beginners practice key £1.05. All metal full adjustable type. £2.60

### MINIATURE LEVEL METERS

1 Centre Zero 17 x 17mm 75p. 2 (scaled 0-10) 28 x 25mm 75p. 3 Grundig 40 x 27mm £1.25.

JVC NIVICO STEREO CASSETTE MECHANISM. Music centre type. Rev. counter, remote operation £13.50 and £1.00 p&p.

### JUMPER TEST LEAD SETS

10 pairs of leads with various coloured croc clips each end (20 clips) 90p per set.

### TRANSFORMERS

All 240VAC Primary (postage per transformer is shown after price). MINIATURE RANGE: 6-0-6V 100mA, 9-0-9V 75mA and 12-0-12V 50mA all 79p each (15p). 0-6, 0-6V, 280mA £1.20 (20p). 6V 500mA £1.20 (15p). 12V 2 amp £2.75 (45p). 15-0-15V 3 amp Transformer at £2.85 (54p). 30-0-30V 1 amp £2.85 (54p). 20-0-20V 2 amp £3.65 (54p). 0-12-15-20-24-30V 2 amp £4.75 (54p). 20V 2.5 amp £2.45 (54p).

### TRIAC/XENON PULSE TRANSFORMERS

1:1 (gpo style) 30p. 1:1 plus 1 sub. min. pcb mounting type 60p each.

### MICROPHONES

Min. tie pin. Omni, uses deaf aid battery (supplied), £4.95. ECM105 low cost condenser, Omni, 600 ohms, on/off switch, standard jack plug, £2.95. EM507 Condenser, uni, 600 ohms, 30-18kHz., highly polished metal body £7.92. DYNAMIC stick microphone dual imp., 600 ohms or 20K, 70-kHz., attractive black metal body £7.75. EM506 dual impedance condenser microphone 600 ohms or 50K, heavy chromed copper body, £12.95 CASSETTE replacement microphone with 2.5/3.5 plugs £1.35 GRUNDIG electric inserts with FET pre amp, 3-6VDC operation £1.00

### LIGHT DIMMER

240VAC 800 watts max. wall mounting, has built in photo cell for automatic switch on when dark £4.50

### RIBBON CABLE

8 way single strand miniature 22p per metre.

### SPECIAL OFFER TAPE HEAD DEMAGNETIZER



240VAC with curved probe suitable for reel to reel or cassette machines, £1.95.

STEREO FM/GRAM TUNER AMPLIFIER CHASSIS, VHF and AM. Bass, treble and volume controls, Gram. 8-track inputs, headphone output jack, 3 watts per channel with power supply. £14.95 and £1.20 p&p

### MULTIMETER BARGAINS



Pocket Multimeter, 1,000 opv sensitivity. Ranges 1KV AC/DC Volts, 150ma DC current, resistance 0-2.5K, 0-100K, £4.50




20,000 opv., 1,000 volts AC/DC, DC current to 500ma, 5 ranges, resistance 4 ranges to 6 meg. Mirror scale, carrying handle, £975.

40kHz Transducers. Rec/Sender £3.50 pair.
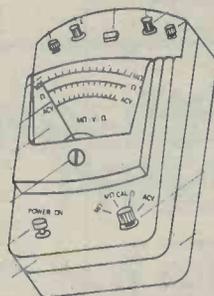
### TELEPHONE PICK UP COIL

Sucker type with lead and 3.5mm plug 62p.



500v electronic megger, push button operation. Ranges:—LO ohm Range 0 - 100Ω (MW scale 5Ω) 0 - 100MΩ Mid scale 5MΩ) £46.75p

Dalo 33PC Etch Resist printed circuit maker pen, with spare tip, 79p.

### TERMS:

Cash with order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive.

S.A.E. for illustrated lists

### MULTI-TESTER



KRT5001 50k/v range doubler multimeter, 0-1kv (125mv LO range) 0-1kv AC. 0-10amp DC. 0-20MΩ res. (LO ohm 0-2k range) 170 x 124 x 50mm £15.50.

### YN360TR MULTIMETER



YN360 M/Meter. 20,000 ohms per volt. 1KV AC/DC volts, 250ma dc current, 4 resistance ranges to 20meg, also has built in transistor tester with leakage and gain ranges. £12.50

### CRIMPING TOOL

Combination type for crimping red blue and yellow terminations also incorporates a wire stripper (6 gauges) and wire cutter, with insulated handles only £2.30.

### POWER SUPPLIES

SWITCHED TYPE, plugs into 13 amp socket, has 3-4.5-6-7.5 and 9 volt DC out at either 100 or 40 0mA, switchable £3.45. HC244R STABILISED SUPPLY, 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £4.95.

### AMPHENOL CONNECTORS

(PL259) PLUGS 47p. Chassis sockets 42p. Elbows PL259/SO239 90p. Double in line male connector (2XPL259) 65p. Plug reducers 13p. PL259 Dummy load, 52 ohms 1 watt with indicator bulb 95p.

### BUZZERS

MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, voltage operating 4-15VDC, 75p each. LOUD 12VDC BUZZER, with, metal case. 50mm diam. x 30mm high 63p. Carters 12 volt Minimate Alarm sirens £7.65p. 12VDC siren, all metal rotary type, high pitched wall, £6.25.

### TOOLS

SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.99 (spare nozzles 69p each).

All Antex irons still at pre increase prices, order now as new stock will be going up next month.

Antex Model C 15 watt soldering irons, 240VAC £3.95

Antex Model CX 17 watt soldering irons, 240VAC £3.95

Antex Model X25 25 watt soldering irons, 240VAC £3.95

ANTEX ST3 iron stands, suits all above models £1.65

Antex heat shunts 12p each.

Servisol Solder Mop 50p each.

Neon Tester Screwdrivers 8" long 59p each.

Mlyarna IC test clips 16 pin £1.95

### SWITCHES

Sub. miniature toggles: SPST (8 x 5 x 7mm) 42p. DPDT (8 x 7 x 7mm) 55p. DPDT centre off 12 x 11 x 9mm 77p. PUSH SWITCHES, 16mm x 6mm, red top, push to make 14p each, push to break version (black top) 16p each.

PACE Mobile SWR metre, with field strength, PL259 connection, £5.95.

### RES. SUB BOX



Resistance Substitution Box. Swivelling disc provides close tolerance resistors of 36 values from 5 ohms to 1 meg. £3.95.



Signal Generator. Ranges 250Hz-100MHz in 6 Bands, 100MHz-300MHz (harmonics) internal modulator at 100Hz. R.F., output Max. 0.1vRMS. All transistorised unit with calibrating device. 220-240VAC operation, £48.95.

### TAPE HEADS

Mono cassette £1.75. Stereo cassette £3.90. Standard 8 track stereo £1.95 BSR MN1330 1/2 track 50p. BSR SRP90 1/2 track £1.95. TD10 tape head assembly — 2 heads both 1/2 track R/P with built in erase, mounted on bracket £1.20

# PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL 2.

ALL ORDERS DESPATCHED BY RETURN POST

# Conquer the chip.


Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.




## MASTER ELECTRONICS

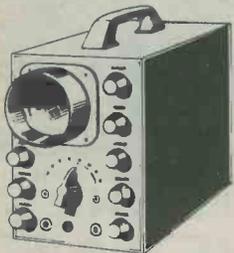

LEARN THE  
PRACTICAL WAY BY  
SEEING AND DOING

- Building an oscilloscope.
- Recognition of components.
- Understanding circuit diagrams.
- Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.

## MASTER COMPUTERS

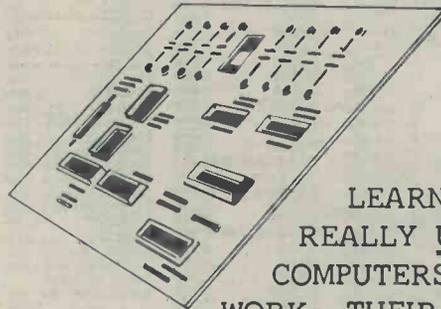

LEARN HOW TO  
REALLY UNDERSTAND  
COMPUTERS, HOW THEY  
WORK - THEIR 'LANGUAGE'  
AND HOW TO DO PROGRAMS.

- Complete Home Study library.
- Special educational Mini-Computer supplied ready for use.
- Self Test program exercise.
- Services of skilled tutor available.

## MASTER THE REST

- Radio Amateurs Licence.
- Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators - Digital Meters etc.

**FREE**

Please send your **FREE** brochure without obligation to:-

Name .....

Address .....

BLOCK CAPS PLEASE

REC/1/811

I am interested in :-

PRACTICAL ELECTRONICS .....

COMPUTER TECHNOLOGY .....

OTHER SUBJECTS .....  
(please state your interest)

.....

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**

4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS.

## TRANSISTORS

AC126	16p	BD233	20p	MA393	25p	2N1490	£3
AC127	16p	BD235	35p	MD7000	£2.25	2N1500	30p
AC128	5p	BD238	25p	ME2	13p	2N1507	18p
AC153	11p	BD239C	29p	ME0412	14p	2N1711	13p
AC176	11p	BD240	30p	ME8003	20p	2N1716	15p
AC188	10p	BD241 45v 40w	22p	MJ481 BDY23	23p	2N1748	28p
ACV20	20p	BD242B 90v 40w	30p	MJE371	40p	2N192A	15p
ACV28	22p	BD246	32p	MJE2371	80p	2N2212A	9p
AD161/162	match pair	BD253	44p	MJE2901T (Higain)	80p	2N2222A	8p
AF119	75p	BD375	35p	MJE2955	50p	2N2359	10p
AF124	27p	BD437	35p	MJE2955 70v 90w	50p	2N2401	7.5p
AF126	27p	BD438	28p	MJ15 Russian	25p	2N2412	27p
AF127	27p	BD597 60v 55w	36p	M041 Russian	25p	2N2483	28p
AF139	23p	BD677 60v 40w	50p	MPF131 Dual	25p	2N2484	10p
AF178	35p	BDX33B Pwr. Darl.	44p	MOSFET	15p	2N2586	15p
AF181	33p	BDX42 60v. Darl.	15p	MPU131 Prog. Uni J.	15p	2N2614	4p
AF239	35p	BDX77	36p	BRF502 Improved	15p	2N2887	£2
ASV60	35p	BDY20	50p	BFY90	90p	2N2894	11p
ASV63	4p	BF115	18p	016A Russian	25p	2N2905	9p
ASV73	35p	BF137	11p	042A Russian	25p	2N2906	9p
ASZ21	4p	BF167	18p	NKT49	23p	2N2907/A	9p
AU110	£1.43	BF178	23p	NKT452	20p	2N2926	4p
AU113	£1.03	BF180	23p	NKT454	20p	2N3020	25p
AU107A/B	7p	BF181	8p	NKT455	20p	2N3053	16p
BC108/A/B/C	7p	BF182	8p	NKT456	20p	2N3054	35p
BC109B	7p	BF183	18p	NKT457	20p	2N3055	35p
BC125B	3p	BF184	18p	NKT458	20p	2N3056	35p
BC140	15p	BF185	18p	NKT459	20p	2N3057	35p
BC141	11p	BF194A/B	5p	NKT460	20p	2N3058	35p
BC147/A/B/C	5p	BF195/C/D	5p	NKT461	20p	2N3059	35p
BC148/A/B/C	5p	BF196	5p	NKT462	20p	2N3060	35p
BC149/A/B/C/S	5p	BF197	5p	NKT463	20p	2N3061	35p
BC154	7p	BF198	5p	NKT464	20p	2N3062	35p
BC157/A/B	5p	BF200	13p	NKT465	20p	2N3063	35p
BC159/B/C	5p	BF204	4p	NKT466	20p	2N3064	35p
BC171B	4p	BF244 FET	71p	NKT467	20p	2N3065	35p
BC172	61p	BF245	6p	NKT468	20p	2N3066	35p
BC172c	71p	BF256FET	4p	NKT469	20p	2N3067	35p
BC173	4p	BF256LB/LC FET	4p	NKT470	20p	2N3068	35p
BC177A	10p	BF257	20p	NKT471	20p	2N3069	35p
BC178A/B/C	10p	BF262	29p	NKT472	20p	2N3070	35p
BC179B	14p	BF263	29p	NKT473	20p	2N3071	35p
BC182/AL	5p	BF274	4p	NKT474	20p	2N3072	35p
BC182L	3p	BF324	31p	NKT475	20p	2N3073	35p
BC183A/AL/LC	3p	BF336	18p	NKT476	20p	2N3074	35p
BC184L	5p	BF355	15p	NKT477	20p	2N3075	35p
BC186	21p	BF394B	3p	NKT478	20p	2N3076	35p
BC187	3p	BF451	6p	NKT479	20p	2N3077	35p
BC204	11p	BF494	10p	NKT480	20p	2N3078	35p
BC212L/B	5p	BF495	5p	NKT481	20p	2N3079	35p
BC213L	5p	BF595c Fm/AM/GP	5p	NKT482	20p	2N3080	35p
BC213LB	4p	BF615	91p	NKT483	20p	2N3081	35p
BC214B	8p	BF624	27p	NKT484	20p	2N3082	35p
BC214L	31p	BF735	15p	NKT485	20p	2N3083	35p
BC237A	71p	BFQ35	15p	NKT486	20p	2N3084	35p
BC238	71p	BFQ85	15p	NKT487	20p	2N3085	35p
BC238B/C	71p	BF34A	36p	NKT488	20p	2N3086	35p
BC239C	71p	BFR38	68p	NKT489	20p	2N3087	35p
BC251	71p	BFR86	19p	NKT490	20p	2N3088	35p
BC258B/C	71p	TIP29 40v 30w	22p	NKT491	20p	2N3089	35p
BC259C	71p	TIP29 40v 30w	22p	NKT492	20p	2N3090	35p
BC302	15p	TIP30C 100v 30w	22p	NKT493	20p	2N3091	35p
BC304	15p	TIP31C 100v 40w	26p	NKT494	20p	2N3092	35p
BC307	7p	TIP32C 100v 40w	26p	NKT495	20p	2N3093	35p
BC308B/C	71p	TIP32A 60v 40w	22p	NKT496	20p	2N3094	35p
BC309B	71p	TIP32C 100v 40w	26p	NKT497	20p	2N3095	35p
BC327	5p	TIP41 40v 65w	26p	NKT498	20p	2N3096	35p
BC328	8p	TIP42C 100v 65w	26p	NKT499	20p	2N3097	35p
BC337	5p	TIP48	33p	NKT500	20p	2N3098	35p
BC338L	71p	TIP48	33p	NKT501	20p	2N3099	35p
BC384B	71p	TIP110 60v 50w Darl.	30p	NKT502	20p	2N3100	35p
BC546	5p	TIP112 100v 50w	45p	NKT503	20p	2N3101	35p
BC547/A/B	5p	TIP117 Pwr Darl	45p	NKT504	20p	2N3102	35p
BC548/A/B/C	5p	TIS44 VHF switch	91p	NKT505	20p	2N3103	35p
BC549C	5p	TIS60GY	3p	NKT506	20p	2N3104	35p
BC556	5p	TIS81	3p	NKT507	20p	2N3105	35p
BC557/B	5p	TIS91	3p	NKT508	20p	2N3106	35p
BC558A	5p	TIS93	3p	NKT509	20p	2N3107	35p
BC559	5p	TIS94	3p	NKT510	20p	2N3108	35p
BC612L	4p	TIS95	3p	NKT511	20p	2N3109	35p
BCX33 60v 750m.w.	10p	TIS96	3p	NKT512	20p	2N3110	35p
BCX32	10p	TIS97	3p	NKT513	20p	2N3111	35p
BCX34	10p	TIS98	3p	NKT514	20p	2N3112	35p
BCX36	10p	TIS99	3p	NKT515	20p	2N3113	35p
BCY11	28p	TIS100	3p	NKT516	20p	2N3114	35p
BCY31	59p	TIS101	3p	NKT517	20p	2N3115	35p
BCY56	10p	TIS102	3p	NKT518	20p	2N3116	35p
BCY70	8p	TIS103	3p	NKT519	20p	2N3117	35p
BCY71	8p	TIS104	3p	NKT520	20p	2N3118	35p
BCY72	8p	TIS105	3p	NKT521	20p	2N3119	35p
BCY79B	15p	TIS106	3p	NKT522	20p	2N3120	35p
BCZ11	32p	TIS107	3p	NKT523	20p	2N3121	35p
BD113	57p	TIS108	3p	NKT524	20p	2N3122	35p
BD115	35p	TIS109	3p	NKT525	20p	2N3123	35p
BD(BRC)116	35p	TIS110	3p	NKT526	20p	2N3124	35p
BD132	15p	TIS111	3p	NKT527	20p	2N3125	35p
BD133	28p	TIS112	3p	NKT528	20p	2N3126	35p
BD135	22p	TIS113	3p	NKT529	20p	2N3127	35p
BD136	14p	TIS114	3p	NKT530	20p	2N3128	35p
BD137	28p	TIS115	3p	NKT531	20p	2N3129	35p
BD138	28p	TIS116	3p	NKT532	20p	2N3130	35p
BD137/8 mch pr	60p	TIS117	3p	NKT533	20p	2N3131	35p
BD140	26p	TIS118	3p	NKT534	20p	2N3132	35p
BD142	35p	TIS119	3p	NKT535	20p	2N3133	35p
BD156	50p	TIS120	3p	NKT536	20p	2N3134	35p
BD182p 70v 117w	44p	TIS121	3p	NKT537	20p	2N3135	35p
BD201	86p	TIS122	3p	NKT538	20p	2N3136	35p
BD202	86p	TIS123	3p	NKT539	20p	2N3137	35p
BD203	86p	TIS124	3p	NKT540	20p	2N3138	35p
BD204	86p	TIS125	3p	NKT541	20p	2N3139	35p
BD232	34p	TIS126	3p	NKT542	20p	2N3140	35p

## RELAYS

CONTINENTAL SERIES. 7000 24v 4pco 62p; 7000 12v 4pco 75p; 520 3/6v 2pco 75p; 520 3/6v 4pco 75p; 1250 12v 2pco 75p; 9000 2pco 75p; 12500 14pco 1.2500 12v 2pco 75p; 9000 2pco 75p; 12500 14pco 2pco 75p; 12500 24v 2pco 75p; 7000 11/31v 2pco 75p; 10000 12v 2pco 95p;

REED RELAYS. Alma DR1. 1" x 1/4" diam. 12500 S.P. 12volt 50p. D.I.L. 5000 3.7/10volt S.P. £1. ALMA 38mm x 11mm x 13mm 1K0/12v S.P. 36p, 3K0 18/30v S.P. 36p, 2K70 12/24v S.P.C.O. 65p. Reed switches normally open 28mm sp. Colls 6-12-24volt 28p. 6/12v 2pco £1.45; 12v 3pco £2.

HEAVY DUTY SERIES. 6500 12/24v 4pco 75p 6700 12v 4pco 75p; 110v 4pco 62p; 3250 12v 3pole £1.15p; 110/130vac spco 75p; 6/12vdc/24vac 3pco 10amp 75p; 2800 12v D.P. 95p.

OPEN STYLE. 240vac 3pco, 2pco or 1pco £1.20, 110vac. 3pco or 4pco 75p; 115vac 1pco 75p.

MINIATURE OPEN STYLE HI-SPEED. 54000 S.P.C.O. 24v 6p; 45000 20v S.P.C.O. 60p.

HIGH SPEED OPEN STYLE DUAL COIL. Wire as 625, 1250 or 25000 11-12v coil S.P.C.O. Heavy Duty contacts 75p.

G.P.O. 1000/3000 series. 12v 2pco 81p; 12v S.P.C.O. £1.05. 3K00 centre tapped 4pco 63p. 1700 3pco + 2p. 80p. Clare 11k0 4pco 63p; 4K50 + 5K0 4pco 63p.

PLUG IN 8/11 PIN. 3360 12v S.P.C.O. 80p; 53300 S.P.C.O. 80p; 10,2500 S.P.C.O. 80p; 110 12v 2pco £1; 4750 24v 2pco 80p; 40/52v 2pco 80p; 36v 2pco 60p; 24v 3pco 89p; 50vac (1MFD series for mains) 3pco 80p; 6v. 2880 S.P. 75p.

COAXIAL 7000 14/30v 500 Impedance S.P.C.O. £2.

SEALED METAL CASED HEAVY DUTY MULTI CONTACT. 12v £1.40; 18/24v £1.30; 8pco 12v £1.30p; 48v 17000 + 17000 S.P.C.O. 66p.

THERMAL DELAY. Amperite 115 no2, 26c5, 1CC10T, 26 no5, 6 no2. 60p each. Silic-on-netic 36v 90 second 2pco 90p.

LOW PROFILE. 4pco 24v 12000 95p.

Continental series CONTINENTAL SERIES SOCKETS 2 or 4pco 10p. 11 pin ex-equipment 18p.

## TRIACS

Amp	Volt	Part No.	Price
0.1	40	7W84	3p
2.5	600	2N5757	44p
3.5	400	T2710D	58p
4	400	T2716D/40730	74p
6	200	T2500B/41014	54p
6	400	T2500D	72p
8	400	T2850D	72p
8	500	BT137-500	72p
12	500	BT138-500	90p
25	100	BTX94-100	£2.25
25	1200	BTX94-1200	£5

## HUGHES

MICRO ELECTRONICS 400MW ZENER  
DIODES 200 IN CLEAR PLASTIC HINGED LID  
COMPONENT BOX £2.30  
3V, 3.6V, 3.9V, 4.3V, 4.7V, 11V, or 13V.

END OF LINE ITEMS AND COMPUTER & AUDIO BOARDS/ASSEMBLIES WITH VARYING CONTENTS INCLUDE ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKES, INTEGRATED CIRCUITS, ETC.

3lb for £2.30 7lb for £4.30

MARKED FULL SPEC DIGITAL I.C.'s  
Branded - New 25 for £1 Mixed

7 MILLION CARBON FILM RESISTORS  
PURCHASED

1/4 - 1/3 - 1/2 - 3/4 - 1 - 1 1/2 Wt. Iskra and Pihor, mainly 5%, few 2%. Lucky Dip as the packs come (will not duplicate under 20 packs) due to cartons packed tight and on top of each other to ceiling of warehouse.

PACK OF 100 FOR 25p

PAY A VISIT - THOUSANDS MORE ITEMS BELOW WHOLESALE PRICE. CALLERS PAY LESS ON MANY ITEMS AS PRICES INCLUDE IN POSTAGE. PRICES INCLUDE VAT AND ADDITIONAL DISCOUNT IN LIEU OF GUARANTEE. GOODS SENT AT CUSTOMERS' RISK UNLESS SUFFICIENT ADDED FOR REGISTRATION OR COMPENSATION FEE POST.

TRADE COMPONENTS CATALOGUE

5300 ITEMS AT PRICES YOU WOULD NOT BELIEVE BEFORE INFLATION. YOUR MONEY MUST GO TWICE AS FAR. 75p Plus 30p Post.

ESTABLISHED 23 YEARS

BRIAN J. REED

161 ST. JOHNS HILL, BATTERSEA, LONDON SW11 1TO  
Open 11 a.m. till 7 p.m. Tues. to Sat. Telephone 01-223 5016  
Terms: Payment with order only. VAT receipts included with goods

**PRICES SO LOW, THE POLICE INVESTIGATED ME TWICE**  
ALL ENQUIRIES, ETC. MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE

**VAT & POST PAID**  
(UK 2nd Class or Parcel)  
MINIMUM ORDER £3 (excluding catalogue) OTHERWISE ADD 50% FOR SMALL ORDER HANDLING COSTS (UNDER £1.00 TOTAL ALSO INCLUDE 12p S.A.E.)

UK - Postal Orders for prompt service. Cheques require 8 days from a Monday banking to ensure clearance. Export - banker's draft (sterling) prompt service. Foreign currency not accepted. VAT content becomes documentation charge. Add additional postage.

**OPTO ELECTRONICS**

Photo Diodes: BPX40, BPX42, BPY10, CQY77, CQY17, BPY68, BPY69, BPY77 36p  
Wire end neons 4p.  
Photo transistors: BPX43, BP103, 2N5777, Darlington, 36p. LED's (Mullard Seimans) Red 2" 8p, 125" 9p; Green 2" 11p; 125" 12p; Micro Yellow LD481 72p.  
PHOTO SILICON CONTROLLED SWITCH BPX66 PNP 10 amp 36p.  
CA3062 Photo Detector and power amp. £1

**7 SEGMENT L.E.D. DISPLAYS**

3" Red com. anode 81p  
6" Green R.S.C.A. £1.77  
5082-7650 Red com. anode.  
5082-7653 Red com. cath  
5082-7600 Yellow com. anode.  
H.P. Highbrilliance 43" 72p

**HEWLETT PACKARD MULTIPLEXED 12" 7 SEGMENT LED DISPLAYS**

3 Digit HP5082 7413 45p  
4 Digit HP 5082 7414 45p  
5 Digit HP 5082 7415 45p  
Infra red transmit diodes CQY11B or LD27 High power 1.6-2v or 3-3.5v Pulse 32p  
LD242 36p  
H15B Photon coupled isolator I.R. diode and NPN Photo-Darlington amp 26p  
CNY17/1 opto coupler 70p  
Cold cathode tubes I.T.T. G517A or 5870L 60p

**SPECIAL OFFER**

IN4004 or IN4006 Sealed manufacturers carton of 300. £6.75

**BULGIN 5amp 240vac in line 3 pin plug and socket 75p pair.**

**T.V. DROPPERS**

266+ 14+ 193Ω  
15+ 23+ 26Ω  
108+ 24+ 9Ω  
66+ 66+ 137Ω  
66+ 66+ 158Ω  
285+ 575+ 148+ 35Ω  
25+ 35+ 97+ +59 30Ω  
30+ 60Ω  
all 11p each plus 59p

**UNISELECTOR**

5 pole 25 way 24v coil £3.50

**TOGGLE SWITCHES**

Double Pole 40p. Bulgin 3 amp 250v S.P. 42p with free panel plate 13amp 250v S.P. 36p. 13amp 250v S.P.C.O. centre off 39p. 3amp 250v S.P. Biased 50p. S.P.C.O. biased 50p. D.P. biased 3amp 250v 60p. S.P.C.O. centre off 10a 250v biased 75p. 10/15amp 4 pole C.O. centre off £1.20. 10/15amp 3 pole C.O. centre off 98p. Sub miniature S.P.C.O. 53p.

**ROTARY MAINS SWITCH**

1/2" or 4mm Spindle D.P.S.T. 20p. Bulgin 5amp S.P. 35p.

Rada + SLR EMERGENCY LIGHT 8" diam x 5" deep. 4 hour unit fit and forget. Auto switch on if mains fail. switches off and recharges when mains restored complete - Boxed - £26.50.

**DIODES**

AA119	7p	MPN3401	30p
AA133	9p	OA5	25p
AAZ15	15p	OA7	25p
B1	11p	OA10	25p
BA116	30p	OA47	7p
BA128	21p	OA70	10p
BA145	21p	OA75	11p
BA148	12p	OA79	11p
BA182 Varicap	6p	OA81	31p
BAX14	21p	OA95	8p
BAX54	8p	OA200	21p
BAY36P	21p	OA202	21p
BB103 Varicap	6p	IGP7	11p
BB104 Varicap	16p	IGP10	11p
BB109 Varicap	24p	IN662	21p
BB110B Varicap	24p	IN914	11p
BB113 Triple Varicap	43p	IN916	71p
		IN935B	71p
BB139	£1	IN936B	71p
BR100 Diac.	15p	IN937B	71p
BY206	71p	IN941B	71p
BY207	23p	IN942B	71p
BY402	21p	IN943B	71p
BY403	21p	IN943B	71p
BY403	21p	IN943B	71p
Centercell	3p	IN4009	21p
CG651	9p	IN4148	1p
CR HG/3	10p	IN4150	21p
CSD117YLZ	40p	IN4151	21p
CV7095	21p	IN4146	21p
CV7098	21p	IN4449	21p
D3202Y Diac.	11p	IN5456	15p
DC2845 Microwave		5882 2900 RF Schotky Barrier	20p
DOG53	11p		
FSY28A	40p		
HG1012	10p		
HS2091	11p		

**RECTIFIERS**

Type	Volt	Amp	Price
BY126	650	1	5p
BY127	1250	1	4p
BY212	15kv	500ma	6p
BY235	600	1 1/2	71p
BY236	900	1 1/2	71p
BY264	300	3	9p
BY265	600	3	11p
BY266	900	3	15p
BY274	300	5	14p
BY275	600	5	17p
BY277	1200	5	27p
BY299	800	2	4p
BY1202	2kv	10mA	6p
BYX20-200	200	25	72p
BYX22-200	300	1 1/2	25p
BYX38 300R	300	2 1/2	48p
BYX38 600	600	2 1/2	52p
BYX38 900	900	2 1/2	60p
BYX38 1200	1200	2 1/2	65p
BYX42 300	300	10	36p
BYX42 600	600	10	46p
BYX42 900	900	10	92p
BYX42 1200	1200	10	£1.07
BYX46 300R	300	15	£1.19
BYX46 400R	400	15	Avalanche £1.75
BYX46 500R	500	15	£2.00
BYX46 600	600	15	£2.30
BYX48 300R	300	6	47p
BYX48 600	600	6	60p
BYX48 900	900	6	70p
BYX48 1200R	1200	6	92p
BYX49 300R	300	3	35p
BYX49 600	600	3	42p
BYX49 900R	900	3	47p
BYX49 1200	1200	3	60p
BYX52 300	300	40	£2.05
BYX52 1200	1200	40	£2.90
BYX72 150R	150	10	42p
BYX72 300R	300	10	52p
BYX72 500R	500	10	65p
BYX94	1250	1	6p
E250C50	250	1	14p
KS11394	800	3	23p
LT102	30	2	15p
M1	68	1	5p
MR856	600	3	24p
OA210	400	5	33p
RA53 10AF	1250	1 1/2	41p
Avalanche			
REC53A	1250	1 1/2	16p
S10BR30	1000	30	£2.00
SKE4G	200	6	30p
SR100	100	1 1/2	9p
SR400	400	1 1/2	10p
IN3254	400	1	4p
IN4002	100	1	3p
IN4004	400	1	41p
IN4005	600	1	6p
IN4006	800	1	6p
IN4007	1250	1	6p
IN5059	200	1 1/2	10p
IN5401	100	3	10p
IS138	800	1	21p
IS921	100	1	8p
25G100	100	60	£4.35
3052	200	3	11p
16094P	900	3	15p
16492	700	1 1/2	91p

24 MEG 1 watt 5% High Voltage resistor 10 for 25p.

**BRIDGE RECTIFIERS**

60V	BC30 C350	23p
1,600	BYX10	34p
110	EC433	20p
50V	WO05	19p
140	OSH01-200	25p
200V	WO2 Ex Equip	15p
400V	WO4	28p
400V	MDA104	29p
800V	WO8	27p
1000	W10	36p
75V	IBIBY234	11 1/2p
150V	IBIBY235	15p
100	I.R.	40p
350V	9F2	70p
500V	9E4	85p
50	KBS005	30p
100	KBS01	30p
200	KBS02	30p
400	KBS04	30p
600	KBS06	30p
100	B40C 3200	58p
400	Texas	85p
Miniature		34p
Meter		
Type		

**THYRISTORS**

Amp	Volt	Price
0.8	200	2N5064 18p
1	240	BTX18-200 35p
1	240	BTX30-200 35p
1	400	BTX18-300 41p
2	400	S2710D with heatsink 40p
3	600	T3N06C00 53p
3	100	T3N1C00 36p
4	50	S107F Sensitive Gate 36p
4	50	S2060F Sensitive Gate 36p
4	400	S2061D Sensitive Gate 38p
4	500	40506 with heatsink 58p
4	600	C106M Sensitive Gate 36p
4	600	2N3228 36p
4	600	GAK 36p
5	400	S3700D 44p
5	400	S5800D/R 36p
5	600	S5800M 44p
6.5	500	BT109/SCR957 71p
7	400	S2620D 45p
7	600	S2620M 45p
8	100	S2800A 36p
8	600	S122M 54p
12	1000	CR121103-RB £8
15	800	BTX95-800 Pulse Modulated £1
20	600	BTW92-600RM £3.40
75	800	71CG80 £6
110	20	72RC2A £3
150	1000	151RA100 £10
150	1200	151RA120 £11
BT106		70p
BT121		70p
BT107		£1

**ZENER DIODES**

4/500MW. BZY88, BZX97, etc.	5p
2v. 2v7. 3v. 3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 9v1. 10v. 11v. 12v. 13v. 13v5. 15v. 18v. 20v. 22v. 24v. 27v. 30v. 33v. 43v.	
BZY61 Laboratory Standard 400MW 7v5. Voltage Regulator Diode	12p
1.3/1.5WT BZX61, BZY97, etc.	11p
2v4. 2v7. 3v. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 8v2. 10v. 11v. 12v. 15v. 18v. 27v. 33v.	
2.5WT BZX70, etc.	13p
v75. 1v. 2v4. 3v6. 3v9. 5v6. 6v2. 7v. 7v5. 8v. 9v. 10v. 11v. 14v. 15v. (8p). 20v. 22v. 24v. 26v.	
5WT BZV40, etc.	15p
3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 8v7. 9v1. 10v. 11v. 12v. 15v. 33v. 68v. 120v.	
10WT Z50, ZX, etc.	20p
4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 11v. 12v. 13v. 16v. 18v. 21v. 22v. 33v. 36v. 39v. 68v. 150v.	
15WT BZV15C 12R 12volt	37p
20WT BZY93, etc.	44p
8v2. 12v. 39v.	

**COMPUTER GRADE ELECTROLYTICS Single ended. High ripple screw terminals**

4/6 VOLT		9/10 VOLT		13/15 VOLT	
22,000	£1.70	10,000	£1.40	7,200	£1.40
25,000	£1.70	11,000	£1.40	8,000	£1.40
36,000	£1.70	12,000	£1.07	10,000	£1.50
66,000	£2.20	15,500	£1.70	12,500	£1.60
		19,000	£1.70	15,000	£1.70
		90,000	£1.85	16,000	£1.70
				17,000	£1
5,500	£1	3,500	£1	22,000	£1.50
11,500	£1.50	4,000	£1.20	33,000	£1.40
17,000	£1	7,500	£1.50	36,000	£2.50
35,000	£3	10,000	£1.50	54,000	£3.25
		11,000	£1.50	70,000	£4
		12,000	£1.50	90,000	£1.85
2,500	£1	12,000	£1.50	110,000	£1.85
4,000	£1.50	30,000	£3.50		
5,500	£1.70	32,000	£3.50		
7,100	£2	47,000	£3	40,000	£1.85
1,300	£1	50,000	£1.85	60,000	£1.60
		71,000	£1.85		
				160 VOLT	
60 VOLT		100 VOLT		820	£1
2,000	60p	400MFD	85p	1,200	£1.90
8,000	£2.50	300/325 VOLT		2,200	£2.50
		3,100	£3.50		

Some are scruffy looking - but O.K.

# BRIAN J. REED

SEE PRECEDING PAGES FOR ORDERING INSTRUCTIONS  
Cut out and keep these 3 pages. Over the months they will bring to you some of the 6,000 items stocked.

## INTEGRATED CIRCUITS

326 2, 2, 3, 3 Input Nand	20p	74LS290	47p	CD4068 8 Input Nand	20p	SN75108	36p
371AJ RF/IF Amp	4p	74293	80p	CD4069 Hex Inverter	13p	SN75110	46p
542 Servo Amp	18p	74298	£1	CD4070 Quad 2 Input exclusive or	15p	SN75150	18p
702 CL	25p	74490	£1.30	CD4071 quad 2 input or buffer	16p	SN75235N	11p
709/72709 OP Amp	19p	7905 - 5v Reg. 1 Amp	54p	CD4072 dual 4 input or	15p	SN75451 interface	36p
723 Variable Volt Regulator	36p	8080A C.P.U.	£3.60	CD4076 Quad D Flip-Flop	54p	SN76001	36p
710	26p	825129	£5	CD4077 Quad Exclusive Nor	30p	SN76003 5Wt. Amp	36p
724	26p	9093DC	4p	CD4078 8 Input Nor	19p	SN76013 5Wt. Amp	36p
741 OP Amp	16p	9112DC	4p	CD4081 Quad 2 Input and Buffer	15p	SN76013N 5 Wt. Amplifier	82p
747 Dual OP Amp	44p	93510	£1	CD4082 Dual 4 Input and	15p	SN76023 5Wt. Amp	36p
930DC	4p	9311	£1.20	CD4085 Dual 2 in. 2 wide and/or inv.	72p	SN76110P	35p
933DC	4p	93116	36p	CD4086 4 Wide 2 Input and/or Inv.	54p	SN76115N Stereo Decoder	35p
936DC	4p	9370	36p	CD4093 quad 2 Input Nand S.T.	54p	SN76131	58p
937DC	4p	930399-256 Bit Shift Register	4p	CD4094 8 bit ser. par. hold bus reg.	72p	SN76227	59p
946DC	4p	930399-480 Bit Shift Register	4p	CD4095 JK. Gated flip flop non Inv.	72p	SN76228(BTA396)	£1.60
949DC	4p	930399-500 Bit Shift Register	4p	CD4096 gated JK flip flop	72p	SN76396	35p
961DC	4p	AY5-3507 3 1/2 Digit DVM	£1.65	CD4502 Strobed Hex Inverter	44p	SN76620 (AN)	18p
963DC	4p	AY5-8300 Ch/Time Display	36p	CD4508BF	£1.78	SN76650N	50p
963DC	4p	AY58300 Ch/Time Display	36p	CD4510 BCD up down count	72p	SN76660N	35p
1315P2	36p	AY58300 Ch/Time Display	36p	CD4511 BCD 7 seg. latch dec./driver	72p	SN76666N	35p
2102 Memory 1024 static 450ns	73p	BRCM300 Volt Reg.	£1.40	CD4517 2x64 bit Shift Register	£3.60	SN76803	50p
2107B see µPD411AC	-	BT7822	£1.25	CD4519/MC14519	54p	SN158097	4p
2/4/7116 see µPD416C	-	C500 Calculator	37p	CD4520 Dual Synch. 4 Bit Binary	72p	SN158099	50p
2125 1024x1 Static 125ns RAM	£1.25	CA139AG Quad Volt Comp.	54p	CD4532	£1.08	SP4021 high speed dividers	75p
2708 Eprom	£2.60	CA239G Quad volt comparator	54p	CD4537	£1.20	TAA263 Amp	75p
2716 Eprom	£5.00	(T)CA270AE	£1	CD4555	72p	TAA320	35p
3351-2DC 40 x 9 Bit FIFO 2MHZ	£1.07	(T)CA270CWW/AW	35p	CD4556 Decoder	56p	TAA550 Volt Reg.	10p
4060 Dynamic RAM 300ns	£1.45	(T)CA270CE	36p	CD22100	£1.45	TA4700	£2.30
7400 Quad 2 Input	16p	CA2758 (MC1311)	36p	CD40100 32 bit L/R Shift Reg.	£1.78	TAI100 AM Radio	£1.22
74H00 Positive Nand	10p	CA3200 TV Horiz. system	72p	CD40101	£1.08	TBA120S/CO/SB/B TV Amp	25p
74LS00 Gates	13p	CA3201 RF Amp	86p	CD40108 4 x 4 Multiport Reg.	£3.10	TBA240	£3.90
74S00	18p	CA3028A	75p	CD40160 Dec. Count. Async. clear	72p	TBA395Q	£1.50
7401 Quad 2 input pos	71p	CA3044	£1.20	CD40162	72p	TBA396 Luminance and chrom.	35p
74H01 Nand + O/C out	26p	CA3045 Transistor Array	£1.43p	CD40163 Bin. count synch. clear	72p	TBA550Q	£1.25
7402 quad 2 In pos nor	11p	CA3046 Transistor Array	40p	CD40181BE Quad 2 Input and	£2.12	TBA560C	52p
7404 Hex. Inverter	11p	CA3054	69p	CD40182	72p	TBA800 Amp 5 Watt Audio	52p
54/7406 Hex. Inv./Buff/Drive	15p	CA3060 Variable OP AMP	72p	CD40192	72p	TBA920 TV Line System	70p
74LS08 Quad 2 in pos. and	15p	CA3065	36p	CD40194	72p	TCA2700/SA/AE/OS	£1
7410 Triple 3 Input	10p	CA3065	36p	CD40208BF	£2.12	TCA2705Q synch. demod.	55p
74L10 Positive Nand	25p	CA3080 OP AMP	59p	CD40257 Data Selector	£1.15	TCA440 A.M. Receiver	£1.25
74H10 Gates	28p	CA3083	65p	CDP1833 Cosmac Rom 1824 x 8	£3.60	TCA8305 Ex. Equip A.F. Amp.	18p
7411 Triple 3 In. Pos. and.	8p	CA3086	29p	CDP1834 Cosmac Rom 1024 x 8	£3.60	TCA8305 A.F. Amp.	37p
7414 Hex. Schmitt trig. Inv.	29p	CA3089	54p	CT1012 C Frequency synthesiser	75p	TCA4401	£1.25
7420 Dual 4 Input	11p	CA3090AQ	72p	CT1115 Frequency Synthesiser	75p	TCEP100	37p
74S20 Positive Nand Gates	19p	CA3093	36p	CT1119 Frequency Synthesiser	75p	TDA0470 Organ	31p
74S22 Dual 4 In. Pos. Nand o/c	18p	CA3094 Prog. Sw. Pwr. OP Amp.	36p	D3624	36p	TDA2610 6watt audio amp	71p
7425	18p	CA3123	36p	DM8214 Interrupt (8080 support)	36p	TDA2680	71p
7426 Quad 2 In 15v Interface	16p	CA3132EM	73p	FCH1118 input Nand/Nor	8p	TDA2690	71p
5430	12p	CA3146E	£2.22	FH201	18p	TDA25A 16 diode array	4p
7430 8 In. Pos. Nand	11p	CA3183	90p	FCJ101	50p	TLµA720 AM Radio RF/IF Amp	73p
74L30	11p	CA3189	80p	FQJ/MPO3725 4 Tr. Array	45p	TM54034 Memory	£1.08
54/7437 Quad 2 In. Pos. Nand. Buf.	13p	CA3290 Comparator	73p	FZH151	18p	µPD411AC 300ns Dynamic 4096 x 1	ram
7438	14p	CA3401 (LM3900) Quad OP Amp	36p	FZH191	18p	µPD416C 16384 x 1 Dynamic MOS RAM	£1.30
74H40 Dual 4 In. Pos. Nand. Buf.	26p	CD2500E30mA/Seg Demul Point Dvr	90p	FZH201	18p	300ns	£1.30
7442 BCD to Decimal Decoder	26p	CD4000 Dual 3 Input Nor + Inv.	12p	ICL7103 4 1/2 Digit DVM/DPM	£2.04	XR215	£2
74LS42 BCD to Decimal Decoder	40p	CD4002 Dual 4 Input Nor	12p	IM5623 MPU	36p	ZN414 AM Radio Receiver	79p
7445 BCD Decimal Decoder	42p	CD4004	56p	LM300 Volt Reg.	42p	ZST131A 5 Input Power NOR	8p
Expandable Dual 2		CD4006 18 Stage Static Shift Reg.	36p	LM340T6v Reg.	38p		
74H50 Wide 2 Input and/or Inv.	26p	CD4007 Dual Comp. Pair + Inv.	12p	LM345 Amp	4p		
7451 Dual 2 Wide/In. and/or Inv.	7p	CD4008 4 Bit Binary Full Adder	54p	LM1303N Dual Stereo Pre Amp	65p		
7454 4 Wide 2 In. and/or Inv.	11p	CD4010 Hex Buffers	30p	LM/MC1458N Dual OP Amp	19p		
74L54	11p	CD4012 Dual 4 Input Nand	13p	LM3900 (See CA3041)			
54/7472 And Gated JK Master	17p	CD4013 Dual D Flip Flop	36p	MC8300	4p		
74L72 Slave F.F. Preset + Clear	25p	CD4014 8 Bit Shift Register	36p	MC833P dual 4 input fast rise	4p		
5473 Dual JK Master	25p	CD4017 Decade Count/Divide	54p	MC837P Hex invert. expander	4p		
7473 Slave Flip Flops	17p	CD4018 Preset Divide N Count	54p	MC848P	4p		
74H73 with Clear	26p	CD4019 Quad 2 Input Multiplex	25p	MC862P	4p		
7474 Dual D. Pos. Trig	13p	CD4020 14 Stage Binary Count	54p	MC863P	4p		
74L74 FF 2/Preset + Clear	25p	CD4021 8 Bit Shift Register	54p	MC1306P	40p		
7475	24p	CD4022 Divide by 8 Count/Divide	56p	MC1307P	35p		
54/7476 Dual JK Mas./SL Flip Flop	19p	CD4023 Triple 3 Input Nand	19p	MC/CA/BRC 1310P St. Dec.	35p		
5480	22p	CD4024 2-Stage Binary Counter	36p	MC1312P Stereo Decoder	40p		
7482 2 Bit Binary Full Adder	35p	CD4025 Triple 3 Input Nand	14p	MC1314P	35p		
7483 4 Bit Binary full	45p	CD4026 Dec. Count + 7 Seg. Out	72p	MC1315P	35p		
74LS83 Add + Fast carry	47p	CD4028/MC14028 BCD/Decimal	42p	MC1350P	35p		
54/7486	18p	CD4029 Synch. Preset Bin/Dec	42p	MC1357P	35p		
5490/7490 Decade Counter	25p	CD4030 Quad Exclusive or	36p	MC3302L	75p		
7493 Binary Counter 4 Bit	25p	CD4031 64 stage static. shift reg.	£1.20	MC4044P	£1		
54/74L95 4 Bit Ser./Par. In Out	25p	CD4032	72p	MC4344P	£3.50		
74LS98	£1.25	CD4033 Dec. Count. 7 Seg. Output	72p	MIC7C	25p		
74107 Dual JK Flip Flop Clear	20p	CD4034 Static shift register	£1.48p	MK2686	36p		
74S112	38p	CD4035 4 Bit Par. in out shift	54p	MK4012 Memory Static Shift Reg	38p		
74118	75p	CD4036 Word Buff. Store/decode	£2.90	ML237B	£1		
74121 Monostable Multivib.	12p	CD4037 triple and/or B1 Phase pairs	72p	MM5395D M.P.U.	36p		
74122	18p	CD4038	54p	MM8008 M.P.U.	36p		
54/74123 Dual Retrigger. Multivib.	35p	CD4041 Quad True/Comp. Buffer	54p	MP3202 3 1/2 Digit DVM	£1.45		
74132	44p	CD4042 Quad clocked D type catch	56p	MT300 Volt Reg.	8p		
74141 BCD To Decimal Dec/Dr.	42p	CD4043 Quad Nor R/S Latch	54p	MT305 Volt Reg.	8p		
74LS145	93p	CD4044 Quad Nand R/S Latch	54p	MW4050D Static Ram 200ns	£1.60		
74151 1 of 8 Data Sel/Multi	32p	CD4045 4 Bit Par. in out shift	54p	MW55101 256x4 SOS CMOS RAM	£3.60		
74154 16 Way Dist.	35p	CD4046 Micro Power PH. Lock Loop	36p	SA0661	36p		
74155	12p	CD4047 monostable	72p	SA01010	34p		
74157 Quad 2 line to 1 Data	12p	CD4048 Exp 8 input gate	36p	SA01025	£4		
74165	58p	CD4049 Hex Inverter Buffers	36p	SA580	18p		
74167 Synch. Dec. Rate Mult.	23p	CD4051 Analogue Multi/Demulti	36p	SA5590	18p		
74173	44p	CD4052 Analogue Multi/Demulti	36p	SGS308 Op. Amp	4p		
74176/8280 Pre-set 35MHZ Dec.	30p	CD4053 Analogue Multi/Demulti	36p	SL403A 3 Wt. Amp.	38p		
74180	12p	CD4054 4 LINE LCD driver/count	72p	SL442	36p		
74192 Synch. Dec. Up/Down	33p	CD4055 BCD 7SEG. Decode/Drive.	72p	SN7528	11p		
74LS192 Count + Dual Clock	60p	CD4061 AD 256 word X 1 Bit St. RAM	£5.30	SN15836	25p		
74193	38p	CD4063 4 bit magnitude comp.	72p	SN15845	50p		
74196 Pre-set 50MHZ	36p	CD4066 Quad Bilateral Switch	27p	SN15846	50p		
74S196/82S90	52p	CD4067 1.16 MULTIPLEXER	£2.12	SN15851	37p		
Decade Count/Latch	65p			SN15858N	55p		
74LS221 Dual Monostable M/VIB	52p			SN15862	6p		
				SN75107 Interface	£1.15		

## FUSES

PLUGTOP			
10 amp 3p. 13amp 30p. Box 10 3 amp 50p.			
QUICKBLOW			
20mm		1 1/2"	
150ma	2p	60ma	3p
250ma	2p	100ma	3p
500ma	2p	250ma	3p
1a	2p	12 for	12p
2a	2p	2a	3p
5a	2p	3a	3p
5/8"		12 for	
100ma	3p	5a	3p
250ma	3p	10a	3p
4a	3p	25a	4p
		35a	4p
ANTI SURGE			
20mm		1 1/2"	
50ma	5p	100ma	5p
80ma	7p	150ma	5p
400ma	50p	250ma	5p
Pack of 10	50p	500ma	5p
500ma	5p		
1a	5p		
2.5a	5p	500ma	5/8"
4a	5p		
Pack of 10	50p		
TERMINAL BLOCKS			
Grelco Black solid 15amp 6-8 or 10 way. 24p. Klippon 12 way 20amp with wire protection leaf.Rigid. 32p			
Vidor VT3 9v battery 37p. Long life calculator version 39p.			
Low resistance screened wire. (As used by A.F.A. for alarm systems), drums vary 250 to 280 yds. £4.45p.			
CIRCUIT BOARDS unused top quality fibreglass and paxoline. Many varied circuit patterns and sizes, some precious metal coated. Circuit groupings ideal for experiments or non complex projects 10p, 16p, and 27p.			

# Self-Binder

for "Radio & Electronics Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.



**PRICE £2.25** P. & P. 50p  
including V.A.T.


**For your other magazines**  
Plain-backed in Maroon or Green  
(Please state colour choice)

**PRICE £2.25** P. & P. 50p  
including VAT

Available only from:—

**Data Publications Ltd.**  
**57 Maida Vale London W9 1SN**
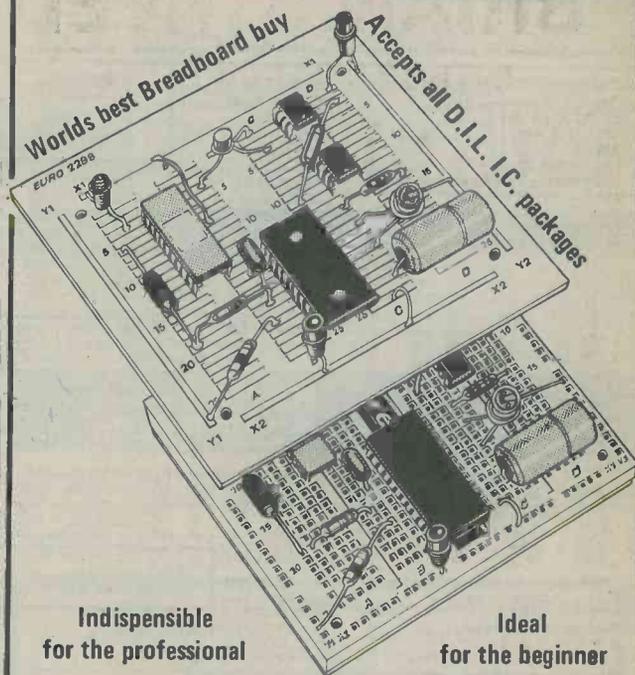
## First the EuroBreadBoard Now the EuroSolderBoard



Design on a EuroBreadBoard — Instal on a EuroSolderBoard

### First the EuroBreadBoard

Will accept 0.3" and 0.6" pitch DIL IC's, Capacitors, Resistors, LED's, Transistors and components with up to .85mm dia leads. 500 individual connections PLUS 4 integral Power Bus Strips along all edges for minimum inter-connection lengths. All rows and columns numbered or lettered for exact location indexing (ideal for educational projects) Long life, low resistance (< 10m ohms) nickel silver contacts £6.20 each or £11.70 for 2

### Now the EuroSolderBoard

New 100mm square, 1.6mm thick printed circuit board with pre-tinned tracks identically laid out, numbered and lettered to EuroBreadBoard pattern. Four 2.5mm dia fixing holes. £2.00 for set of three ESB's

### And don't forget the EuroSolderSucker

Ideal for tidying up messy solder joints or freeing multi-pin IC's, this 195mm long, all metal, high suction desoldering tool has replaceable Teflon tip and enables removal of molten solder from all sizes of pcb pads and track. Primed and released by thumb, it costs only £7.25 including VAT & PP



Snip out and post to David George Sales,  
Unit 7, Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU

David George Sales,  
Unit 7, Higgs Ind. Est., 2 Herne Hill Rd., London SE24 0AU.  
Please send me:—

- |                       |          |                       |        |
|-----------------------|----------|-----------------------|--------|
| 1 EuroBreadBoard      | @ £ 6.20 | <input type="radio"/> |        |
| or 2 EuroBreadBoards  | @ £11.70 | <input type="radio"/> | Please |
| or 3 EuroSolderBoards | @ £ 2.00 | <input type="radio"/> | Tick   |
| or 1 EuroSolderSucker | @ £ 7.25 | <input type="radio"/> |        |

All prices are applicable from Jan. 1st 1981 and include VAT & PP but add 15% for overseas orders.

Name .....  
Company .....  
Address .....

..... ERC/1  
Tel. No .....  
Please make cheques/P.O. payable to David George Sales and allow 10 days for cheque clearance and order processing

<b>BATTERIES</b> NICAD rechargeable 1. (AA) £1.50 2. (C) £2.50 3. (D) £4.50		<b>CAPACITORS</b> Ceramic - Auto Insertion Types tol 10% 400v IN PFCs PCM 5mm		<b>RESISTORS</b> E12 IN OHMS 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 227A Carbon Film 1W5% 9 x 3mm 250v 10R-1 MEG E12 1p 227B Metal Film 1W5% 10 x 3mm 350v 10R-1 K E12 2p. By Electrofil/Welwyn. When ordering resistors state qty, item no and resistance value. Minimum quantity per value, 10																																																																																																																
<b>CABLE</b> PVC round Grey 4. Audio screened overall 2 core 7/20mm 20p MTR 5. Mains 3 core 3 amp 12p MTR 6. TV Downlead 6p MTR 7. 16/2mm x 15' 1 each in Black Red, Yellow Sp lot.		<table border="1"> <tr><td>8</td><td>10</td><td>2p</td><td>12</td><td>47</td><td>2p</td><td>15</td><td>150</td><td>4p</td><td>20</td><td>680</td><td>5p</td></tr> <tr><td>9</td><td>15</td><td>3p</td><td>13</td><td>56</td><td>2p</td><td>17</td><td>220</td><td>4p</td><td>21</td><td>1K</td><td>5p</td></tr> <tr><td>25</td><td>33</td><td>13 x 6</td><td>3p</td><td>31</td><td>47</td><td>19 x 10</td><td>15p</td><td>36</td><td>10/63v</td><td>C</td><td>12 x 8</td><td>3p</td></tr> <tr><td>27</td><td>47</td><td>13 x 6</td><td>5p</td><td>32</td><td>100</td><td>31 x 13</td><td>20p</td><td>37</td><td>22/35v</td><td>M</td><td>13 x 8</td><td>4p</td></tr> <tr><td>28</td><td>6.8</td><td>13 x 7</td><td>9p</td><td>33</td><td>220</td><td>31 x 13</td><td>25p</td><td>38</td><td>47/95v</td><td>S</td><td>12 x 10</td><td>4p</td></tr> <tr><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td>39</td><td>100/25v</td><td>M</td><td>13 x 10</td><td>5p</td></tr> <tr><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td>40</td><td>220/35v</td><td>M</td><td>17 x 10</td><td>7p</td></tr> <tr><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td>41</td><td>470/63v</td><td>+</td><td>20 x 10</td><td>9p</td></tr> </table>		8	10	2p	12	47	2p	15	150	4p	20	680	5p	9	15	3p	13	56	2p	17	220	4p	21	1K	5p	25	33	13 x 6	3p	31	47	19 x 10	15p	36	10/63v	C	12 x 8	3p	27	47	13 x 6	5p	32	100	31 x 13	20p	37	22/35v	M	13 x 8	4p	28	6.8	13 x 7	9p	33	220	31 x 13	25p	38	47/95v	S	12 x 10	4p									39	100/25v	M	13 x 10	5p									40	220/35v	M	17 x 10	7p									41	470/63v	+	20 x 10	9p	<table border="1"> <tr><td>42</td><td>W005</td><td>18p</td></tr> <tr><td>43</td><td>W02</td><td>20p</td></tr> <tr><td>44</td><td>W04</td><td>24p</td></tr> </table>		42	W005	18p	43	W02	20p	44	W04	24p
8	10	2p	12	47	2p	15	150	4p	20	680	5p																																																																																																									
9	15	3p	13	56	2p	17	220	4p	21	1K	5p																																																																																																									
25	33	13 x 6	3p	31	47	19 x 10	15p	36	10/63v	C	12 x 8	3p																																																																																																								
27	47	13 x 6	5p	32	100	31 x 13	20p	37	22/35v	M	13 x 8	4p																																																																																																								
28	6.8	13 x 7	9p	33	220	31 x 13	25p	38	47/95v	S	12 x 10	4p																																																																																																								
								39	100/25v	M	13 x 10	5p																																																																																																								
								40	220/35v	M	17 x 10	7p																																																																																																								
								41	470/63v	+	20 x 10	9p																																																																																																								
42	W005	18p																																																																																																																		
43	W02	20p																																																																																																																		
44	W04	24p																																																																																																																		

<b>CAPACITORS</b> ELECTROLYTIC TOL - 10% + 50% IN MFDS SIZES IN MM. AXIAL TUBULAR  ALL 53V  PLUG IN  LEADS .7 x 5mm		<b>BRIDGES</b> By GI, ME																																																																											
<table border="1"> <tr><td>24</td><td>1</td><td>13 x 8</td><td>9p</td><td>29</td><td>10</td><td>19 x 7</td><td>9p</td><td>34</td><td>2.2/63v</td><td>+</td><td>11 x 5</td><td>2p</td></tr> <tr><td>25</td><td>2</td><td>13 x 6</td><td>9p</td><td>30</td><td>100</td><td>19 x 9</td><td>12p</td><td>35</td><td>4.7/63v</td><td>P</td><td>11 x 8</td><td>3p</td></tr> <tr><td>26</td><td>3</td><td>13 x 6</td><td>9p</td><td>31</td><td>47</td><td>19 x 10</td><td>15p</td><td>36</td><td>10/63v</td><td>C</td><td>12 x 8</td><td>3p</td></tr> <tr><td>27</td><td>4</td><td>13 x 6</td><td>5p</td><td>32</td><td>100</td><td>31 x 13</td><td>20p</td><td>37</td><td>22/35v</td><td>M</td><td>13 x 8</td><td>4p</td></tr> <tr><td>28</td><td>6.8</td><td>13 x 7</td><td>9p</td><td>33</td><td>220</td><td>31 x 13</td><td>25p</td><td>38</td><td>47/95v</td><td>S</td><td>12 x 10</td><td>4p</td></tr> </table>		24	1	13 x 8	9p	29	10	19 x 7	9p	34	2.2/63v	+	11 x 5	2p	25	2	13 x 6	9p	30	100	19 x 9	12p	35	4.7/63v	P	11 x 8	3p	26	3	13 x 6	9p	31	47	19 x 10	15p	36	10/63v	C	12 x 8	3p	27	4	13 x 6	5p	32	100	31 x 13	20p	37	22/35v	M	13 x 8	4p	28	6.8	13 x 7	9p	33	220	31 x 13	25p	38	47/95v	S	12 x 10	4p	<table border="1"> <tr><td>42</td><td>W005</td><td>18p</td></tr> <tr><td>43</td><td>W02</td><td>20p</td></tr> <tr><td>44</td><td>W04</td><td>24p</td></tr> </table>		42	W005	18p	43	W02	20p	44	W04	24p
24	1	13 x 8	9p	29	10	19 x 7	9p	34	2.2/63v	+	11 x 5	2p																																																																	
25	2	13 x 6	9p	30	100	19 x 9	12p	35	4.7/63v	P	11 x 8	3p																																																																	
26	3	13 x 6	9p	31	47	19 x 10	15p	36	10/63v	C	12 x 8	3p																																																																	
27	4	13 x 6	5p	32	100	31 x 13	20p	37	22/35v	M	13 x 8	4p																																																																	
28	6.8	13 x 7	9p	33	220	31 x 13	25p	38	47/95v	S	12 x 10	4p																																																																	
42	W005	18p																																																																											
43	W02	20p																																																																											
44	W04	24p																																																																											
BY ELNA MULLARD RUBYCON, PLESSEY 5PRAGUE 40. 220/35v M 17 x 10 7p 41. 470/63v + 20 x 10 9p		<table border="1"> <tr><td>390</td><td>DIN plug 5 pin</td><td>18p</td></tr> <tr><td>391</td><td>DIN chassis SKT</td><td>15p</td></tr> <tr><td>392</td><td>Jack plug stereo</td><td>15p</td></tr> <tr><td>393</td><td>Jack chassis SKT</td><td>15p</td></tr> <tr><td>394</td><td>main plug</td><td>39p</td></tr> <tr><td>395</td><td>rubber white 3 pin</td><td>13p</td></tr> <tr><td>396</td><td>pin</td><td>56p</td></tr> </table>		390	DIN plug 5 pin	18p	391	DIN chassis SKT	15p	392	Jack plug stereo	15p	393	Jack chassis SKT	15p	394	main plug	39p	395	rubber white 3 pin	13p	396	pin	56p																																																					
390	DIN plug 5 pin	18p																																																																											
391	DIN chassis SKT	15p																																																																											
392	Jack plug stereo	15p																																																																											
393	Jack chassis SKT	15p																																																																											
394	main plug	39p																																																																											
395	rubber white 3 pin	13p																																																																											
396	pin	56p																																																																											

<b>SCRS</b> 228 BT106 (TA) 1 700 70p 230 2N4644 B 600 90p 232 2N5062 (TA) .25 v 100 18p 229 C106D 1 400 35p 231 2N5061 25 60 12p		<b>TAPES</b> MAGNETIC TOK Item 233. ADC 90 85p.	
--	--	---	--

<b>CAPACITORS</b> POLYESTER PLUG IN RECT BOK STYLE TOL 10% IN MFDS BY EVOX MULL PLESSEY ROEDSTEIN SIEMENS		<b>CONNECTORS</b> 390 DIN plug 5 pin 18p 391 DIN chassis SKT 15p 392 Jack plug stereo 15p 393 Jack chassis SKT 15p 394 main plug 39p 395 rubber white 3 pin 13p 396 pin 56p																																																																													
<table border="1"> <tr><td>45</td><td>.001/400v</td><td>10</td><td>2p</td><td>53</td><td>.068/100v</td><td>10</td><td>3p</td></tr> <tr><td>46</td><td>.0022/400v</td><td>10</td><td>2p</td><td>54</td><td>.1/250v</td><td>10</td><td>3p</td></tr> <tr><td>47</td><td>.0033/400v</td><td>10</td><td>2p</td><td>55</td><td>.22/250v</td><td>15</td><td>5p</td></tr> <tr><td>48</td><td>.0047/400v</td><td>10</td><td>2p</td><td>56</td><td>.33/100v</td><td>15</td><td>7p</td></tr> <tr><td>49</td><td>.01/250v</td><td>10</td><td>3p</td><td>57</td><td>.47/250v</td><td>22</td><td>10p</td></tr> <tr><td>50</td><td>.022/250v</td><td>10</td><td>3p</td><td>58</td><td>.68/100v</td><td>15</td><td>15p</td></tr> <tr><td>51</td><td>.033/100v</td><td>10</td><td>3p</td><td>59</td><td>1/100v</td><td>15</td><td>15p</td></tr> <tr><td>52</td><td>.047/100v</td><td>10</td><td>3p</td><td>60</td><td>1.5/100v</td><td>22</td><td>20p</td></tr> </table>		45	.001/400v	10	2p	53	.068/100v	10	3p	46	.0022/400v	10	2p	54	.1/250v	10	3p	47	.0033/400v	10	2p	55	.22/250v	15	5p	48	.0047/400v	10	2p	56	.33/100v	15	7p	49	.01/250v	10	3p	57	.47/250v	22	10p	50	.022/250v	10	3p	58	.68/100v	15	15p	51	.033/100v	10	3p	59	1/100v	15	15p	52	.047/100v	10	3p	60	1.5/100v	22	20p	<table border="1"> <tr><td>61</td><td>2.2/100</td><td>22</td><td>25p</td></tr> <tr><td>62</td><td>3.3/100</td><td>22</td><td>50p</td></tr> <tr><td>63</td><td>4.7/100</td><td>22</td><td>50p</td></tr> </table>		61	2.2/100	22	25p	62	3.3/100	22	50p	63	4.7/100	22	50p
45	.001/400v	10	2p	53	.068/100v	10	3p																																																																								
46	.0022/400v	10	2p	54	.1/250v	10	3p																																																																								
47	.0033/400v	10	2p	55	.22/250v	15	5p																																																																								
48	.0047/400v	10	2p	56	.33/100v	15	7p																																																																								
49	.01/250v	10	3p	57	.47/250v	22	10p																																																																								
50	.022/250v	10	3p	58	.68/100v	15	15p																																																																								
51	.033/100v	10	3p	59	1/100v	15	15p																																																																								
52	.047/100v	10	3p	60	1.5/100v	22	20p																																																																								
61	2.2/100	22	25p																																																																												
62	3.3/100	22	50p																																																																												
63	4.7/100	22	50p																																																																												

<b>TRANSISTORS</b> all at 6p each		all at 19p each																																																																																																																																																																																																																																																																																																																												
<table border="1"> <tr><th>Case</th><th>VC</th><th>EO</th><th>L</th><th>IC Max</th><th>P Tot</th><th>FT Min</th></tr> <tr><td>234 BC134</td><td>TO106</td><td>45</td><td>N</td><td>200</td><td>200</td><td>200</td></tr> <tr><td>235 BC147</td><td>TO176</td><td>45</td><td>N</td><td>200</td><td>350</td><td>150</td></tr> <tr><td>236 BC148</td><td>SO176</td><td>30</td><td>N</td><td>200</td><td>350</td><td>150</td></tr> <tr><td>237 BC148</td><td>SO176</td><td>30</td><td>N</td><td>200</td><td>350</td><td>150</td></tr> <tr><td>238 BC157A</td><td>TO176</td><td>45</td><td>P</td><td>300</td><td>350</td><td>130</td></tr> <tr><td>239 BC158A</td><td>SO176</td><td>30</td><td>P</td><td>200</td><td>350</td><td>100</td></tr> <tr><td>240 BC158A</td><td>SO176</td><td>30</td><td>P</td><td>200</td><td>350</td><td>100</td></tr> <tr><td>241 BC171B</td><td>TO32</td><td>45</td><td>N</td><td>200</td><td>300</td><td>100</td></tr> <tr><td>242 BC172B</td><td>TO32</td><td>25</td><td>N</td><td>200</td><td>300</td><td>100</td></tr> <tr><td>243 BC182A</td><td>TO32</td><td>60</td><td>N</td><td>200</td><td>300</td><td>150</td></tr> <tr><td>244 BC183A</td><td>TO32</td><td>30</td><td>N</td><td>200</td><td>300</td><td>150</td></tr> <tr><td>245 BC184</td><td>TO32</td><td>30</td><td>P</td><td>200</td><td>300</td><td>150</td></tr> <tr><td>246 BC129B</td><td>TO32</td><td>60</td><td>P</td><td>200</td><td>300</td><td>200</td></tr> <tr><td>247 BC213B</td><td>TO32</td><td>30</td><td>P</td><td>200</td><td>300</td><td>200</td></tr> <tr><td>248 BC214B</td><td>TO32</td><td>30</td><td>P</td><td>200</td><td>300</td><td>200</td></tr> <tr><td>249 BC237A</td><td>TO32</td><td>45</td><td>N</td><td>100</td><td>625</td><td>150</td></tr> <tr><td>250 BC337</td><td>TO32</td><td>45</td><td>N</td><td>800</td><td>625</td><td>60</td></tr> <tr><td>251 BC347</td><td>TO32</td><td>80</td><td>N</td><td>200</td><td>625</td><td>100</td></tr> <tr><td>252 BF393</td><td>TO32</td><td>300</td><td>N</td><td>500</td><td>625</td><td>80</td></tr> <tr><td>253 TI390</td><td>TO32</td><td>40</td><td>N</td><td>800</td><td>625</td><td>100</td></tr> <tr><td>254 TI391</td><td>TO32</td><td>40</td><td>N</td><td>800</td><td>625</td><td>100</td></tr> <tr><td>255 2N3702</td><td>TO32</td><td>25</td><td>P</td><td>200</td><td>350</td><td>100</td></tr> <tr><td>256 2N3704</td><td>TO32</td><td>30</td><td>N</td><td>800</td><td>350</td><td>100</td></tr> <tr><td>257 2N3706</td><td>TO32</td><td>30</td><td>N</td><td>800</td><td>625</td><td>100</td></tr> <tr><td>258 2N3711</td><td>TO32</td><td>30</td><td>N</td><td>300</td><td>350</td><td>100</td></tr> </table>		Case	VC	EO	L	IC Max	P Tot	FT Min	234 BC134	TO106	45	N	200	200	200	235 BC147	TO176	45	N	200	350	150	236 BC148	SO176	30	N	200	350	150	237 BC148	SO176	30	N	200	350	150	238 BC157A	TO176	45	P	300	350	130	239 BC158A	SO176	30	P	200	350	100	240 BC158A	SO176	30	P	200	350	100	241 BC171B	TO32	45	N	200	300	100	242 BC172B	TO32	25	N	200	300	100	243 BC182A	TO32	60	N	200	300	150	244 BC183A	TO32	30	N	200	300	150	245 BC184	TO32	30	P	200	300	150	246 BC129B	TO32	60	P	200	300	200	247 BC213B	TO32	30	P	200	300	200	248 BC214B	TO32	30	P	200	300	200	249 BC237A	TO32	45	N	100	625	150	250 BC337	TO32	45	N	800	625	60	251 BC347	TO32	80	N	200	625	100	252 BF393	TO32	300	N	500	625	80	253 TI390	TO32	40	N	800	625	100	254 TI391	TO32	40	N	800	625	100	255 2N3702	TO32	25	P	200	350	100	256 2N3704	TO32	30	N	800	350	100	257 2N3706	TO32	30	N	800	625	100	258 2N3711	TO32	30	N	300	350	100	<table border="1"> <tr><th>Case</th><th>VC</th><th>EO</th><th>L</th><th>IC Max</th><th>P Tot</th><th>FT Min</th></tr> <tr><td>308 2N696</td><td>TO5</td><td>40</td><td>N</td><td>500</td><td>500</td><td>40</td></tr> <tr><td>310 2N698</td><td>TO5</td><td>60</td><td>N</td><td>500</td><td>800</td><td>40</td></tr> <tr><td>311 2N830</td><td>TO18</td><td>45</td><td>N</td><td>30</td><td>300</td><td>30</td></tr> <tr><td>312 2N1513</td><td>TO5</td><td>50</td><td>N</td><td>600</td><td>800</td><td>80</td></tr> <tr><td>313 2N1871</td><td>TO5</td><td>50</td><td>N</td><td>600</td><td>800</td><td>70</td></tr> <tr><td>314 2N1890</td><td>TO5</td><td>60</td><td>N</td><td>800</td><td>800</td><td>60</td></tr> <tr><td>315 2N2218</td><td>TO5</td><td>30</td><td>N</td><td>800</td><td>800</td><td>250</td></tr> <tr><td>316 2N2219</td><td>TO5</td><td>30</td><td>N</td><td>800</td><td>800</td><td>250</td></tr> <tr><td>317 2N2221</td><td>TO18</td><td>30</td><td>N</td><td>800</td><td>500</td><td>250</td></tr> <tr><td>318 2N2222</td><td>TO18</td><td>30</td><td>N</td><td>600</td><td>400</td><td>200</td></tr> <tr><td>319 2N2905</td><td>TO5</td><td>40</td><td>P</td><td>600</td><td>600</td><td>200</td></tr> <tr><td>320 2N2906</td><td>TO18</td><td>40</td><td>P</td><td>600</td><td>400</td><td>200</td></tr> <tr><td>321 2N2907</td><td>TO18</td><td>40</td><td>P</td><td>600</td><td>400</td><td>200</td></tr> <tr><td>322 2N3011</td><td>TO18</td><td>12</td><td>N</td><td>200</td><td>350</td><td>400</td></tr> <tr><td>323 2N3053</td><td>TO5</td><td>40</td><td>N</td><td>700</td><td>1W</td><td>100</td></tr> <tr><td>324 2N3638</td><td>TO105</td><td>25</td><td>N</td><td>500</td><td>300</td><td>100</td></tr> <tr><td>325 2N3647</td><td>TO18</td><td>10</td><td>N</td><td>200</td><td>350</td><td>300</td></tr> <tr><td>326 2N5550</td><td>TO32</td><td>140</td><td>N</td><td>600</td><td>310</td><td>100</td></tr> </table>		Case	VC	EO	L	IC Max	P Tot	FT Min	308 2N696	TO5	40	N	500	500	40	310 2N698	TO5	60	N	500	800	40	311 2N830	TO18	45	N	30	300	30	312 2N1513	TO5	50	N	600	800	80	313 2N1871	TO5	50	N	600	800	70	314 2N1890	TO5	60	N	800	800	60	315 2N2218	TO5	30	N	800	800	250	316 2N2219	TO5	30	N	800	800	250	317 2N2221	TO18	30	N	800	500	250	318 2N2222	TO18	30	N	600	400	200	319 2N2905	TO5	40	P	600	600	200	320 2N2906	TO18	40	P	600	400	200	321 2N2907	TO18	40	P	600	400	200	322 2N3011	TO18	12	N	200	350	400	323 2N3053	TO5	40	N	700	1W	100	324 2N3638	TO105	25	N	500	300	100	325 2N3647	TO18	10	N	200	350	300	326 2N5550	TO32	140	N	600	310	100
Case	VC	EO	L	IC Max	P Tot	FT Min																																																																																																																																																																																																																																																																																																																								
234 BC134	TO106	45	N	200	200	200																																																																																																																																																																																																																																																																																																																								
235 BC147	TO176	45	N	200	350	150																																																																																																																																																																																																																																																																																																																								
236 BC148	SO176	30	N	200	350	150																																																																																																																																																																																																																																																																																																																								
237 BC148	SO176	30	N	200	350	150																																																																																																																																																																																																																																																																																																																								
238 BC157A	TO176	45	P	300	350	130																																																																																																																																																																																																																																																																																																																								
239 BC158A	SO176	30	P	200	350	100																																																																																																																																																																																																																																																																																																																								
240 BC158A	SO176	30	P	200	350	100																																																																																																																																																																																																																																																																																																																								
241 BC171B	TO32	45	N	200	300	100																																																																																																																																																																																																																																																																																																																								
242 BC172B	TO32	25	N	200	300	100																																																																																																																																																																																																																																																																																																																								
243 BC182A	TO32	60	N	200	300	150																																																																																																																																																																																																																																																																																																																								
244 BC183A	TO32	30	N	200	300	150																																																																																																																																																																																																																																																																																																																								
245 BC184	TO32	30	P	200	300	150																																																																																																																																																																																																																																																																																																																								
246 BC129B	TO32	60	P	200	300	200																																																																																																																																																																																																																																																																																																																								
247 BC213B	TO32	30	P	200	300	200																																																																																																																																																																																																																																																																																																																								
248 BC214B	TO32	30	P	200	300	200																																																																																																																																																																																																																																																																																																																								
249 BC237A	TO32	45	N	100	625	150																																																																																																																																																																																																																																																																																																																								
250 BC337	TO32	45	N	800	625	60																																																																																																																																																																																																																																																																																																																								
251 BC347	TO32	80	N	200	625	100																																																																																																																																																																																																																																																																																																																								
252 BF393	TO32	300	N	500	625	80																																																																																																																																																																																																																																																																																																																								
253 TI390	TO32	40	N	800	625	100																																																																																																																																																																																																																																																																																																																								
254 TI391	TO32	40	N	800	625	100																																																																																																																																																																																																																																																																																																																								
255 2N3702	TO32	25	P	200	350	100																																																																																																																																																																																																																																																																																																																								
256 2N3704	TO32	30	N	800	350	100																																																																																																																																																																																																																																																																																																																								
257 2N3706	TO32	30	N	800	625	100																																																																																																																																																																																																																																																																																																																								
258 2N3711	TO32	30	N	300	350	100																																																																																																																																																																																																																																																																																																																								
Case	VC	EO	L	IC Max	P Tot	FT Min																																																																																																																																																																																																																																																																																																																								
308 2N696	TO5	40	N	500	500	40																																																																																																																																																																																																																																																																																																																								
310 2N698	TO5	60	N	500	800	40																																																																																																																																																																																																																																																																																																																								
311 2N830	TO18	45	N	30	300	30																																																																																																																																																																																																																																																																																																																								
312 2N1513	TO5	50	N	600	800	80																																																																																																																																																																																																																																																																																																																								
313 2N1871	TO5	50	N	600	800	70																																																																																																																																																																																																																																																																																																																								
314 2N1890	TO5	60	N	800	800	60																																																																																																																																																																																																																																																																																																																								
315 2N2218	TO5	30	N	800	800	250																																																																																																																																																																																																																																																																																																																								
316 2N2219	TO5	30	N	800	800	250																																																																																																																																																																																																																																																																																																																								
317 2N2221	TO18	30	N	800	500	250																																																																																																																																																																																																																																																																																																																								
318 2N2222	TO18	30	N	600	400	200																																																																																																																																																																																																																																																																																																																								
319 2N2905	TO5	40	P	600	600	200																																																																																																																																																																																																																																																																																																																								
320 2N2906	TO18	40	P	600	400	200																																																																																																																																																																																																																																																																																																																								
321 2N2907	TO18	40	P	600	400	200																																																																																																																																																																																																																																																																																																																								
322 2N3011	TO18	12	N	200	350	400																																																																																																																																																																																																																																																																																																																								
323 2N3053	TO5	40	N	700	1W	100																																																																																																																																																																																																																																																																																																																								
324 2N3638	TO105	25	N	500	300	100																																																																																																																																																																																																																																																																																																																								
325 2N3647	TO18	10	N	200	350	300																																																																																																																																																																																																																																																																																																																								
326 2N5550	TO32	140	N	600	310	100																																																																																																																																																																																																																																																																																																																								

<b>CAPACITORS</b> TANT BEAD TOL 20% IN MFDS PCM 5mm 54. 2.2/20v 9p. 55. 4.7/25v 9p. 56. 22/25v 12p. 57. 47/63 18p.		<b>TANT SOLID</b> LARGE SELECTION AVAILABLE																																																																																																																											
<b>DIODES</b> BY ITT, MULL, SESCOSEM, TEXAS, etc. All coded.		<table border="1"> <tr><td>68</td><td>AA119</td><td>35mA 45v</td><td>8p</td><td>76</td><td>BY255</td><td>3A 1300v</td><td>10p</td><td>84</td><td>IN4004</td><td>1A 400v</td><td>3p</td></tr> <tr><td>69</td><td>BA182</td><td>100mA 35v</td><td>5p</td><td>77</td><td>QA47</td><td>48mA 30v</td><td>5p</td><td>85</td><td>IN4148</td><td>75mA 75v</td><td>1p</td></tr> <tr><td>70</td><td>BA183</td><td>75mA 50v</td><td>1p</td><td>78</td><td>DA30</td><td>10mA 30v</td><td>5p</td><td>86</td><td>IN4151</td><td>150mA 75v</td><td>2p</td></tr> <tr><td>71</td><td>BA186</td><td>200mA 150v</td><td>4p</td><td>79</td><td>DA31</td><td>50mA 115v</td><td>7p</td><td>87</td><td>IN5414</td><td>3A 400v</td><td>10p</td></tr> <tr><td>72</td><td>BA198</td><td>115mA 50v</td><td>6p</td><td>80</td><td>DA200</td><td>80mA 50v</td><td>6p</td><td>88</td><td>IN5407</td><td>3A 800v</td><td>12p</td></tr> <tr><td>73</td><td>BY126</td><td>1A 650v</td><td>7p</td><td>81</td><td>IN814</td><td>75mA 100v</td><td>2p</td><td>89</td><td>IS923</td><td>220mA 200v</td><td>2p</td></tr> <tr><td>74</td><td>BY127</td><td>2A 1250v</td><td>11p</td><td>82</td><td>IN916</td><td>75mA 100v</td><td>2p</td><td></td><td></td><td></td><td></td></tr> <tr><td>75</td><td>BY206</td><td>400mA 350v</td><td>20p</td><td>83</td><td>IN4002</td><td>1A 100v</td><td>2p</td><td></td><td></td><td></td><td></td></tr> </table>		68	AA119	35mA 45v	8p	76	BY255	3A 1300v	10p	84	IN4004	1A 400v	3p	69	BA182	100mA 35v	5p	77	QA47	48mA 30v	5p	85	IN4148	75mA 75v	1p	70	BA183	75mA 50v	1p	78	DA30	10mA 30v	5p	86	IN4151	150mA 75v	2p	71	BA186	200mA 150v	4p	79	DA31	50mA 115v	7p	87	IN5414	3A 400v	10p	72	BA198	115mA 50v	6p	80	DA200	80mA 50v	6p	88	IN5407	3A 800v	12p	73	BY126	1A 650v	7p	81	IN814	75mA 100v	2p	89	IS923	220mA 200v	2p	74	BY127	2A 1250v	11p	82	IN916	75mA 100v	2p					75	BY206	400mA 350v	20p	83	IN4002	1A 100v	2p					<table border="1"> <tr><td>84</td><td>IN4004</td><td>1A 400v</td><td>3p</td></tr> <tr><td>85</td><td>IN4148</td><td>75mA 75v</td><td>1p</td></tr> <tr><td>86</td><td>IN4151</td><td>150mA 75v</td><td>2p</td></tr> <tr><td>87</td><td>IN5414</td><td>3A 400v</td><td>10p</td></tr> <tr><td>88</td><td>IN5407</td><td>3A 800v</td><td>12p</td></tr> <tr><td>89</td><td>IS923</td><td>220mA 200v</td><td>2p</td></tr> </table>		84	IN4004	1A 400v	3p	85	IN4148	75mA 75v	1p	86	IN4151	150mA 75v	2p	87	IN5414	3A 400v	10p	88	IN5407	3A 800v	12p	89	IS923	220mA 200v	2p
68	AA119	35mA 45v	8p	76	BY255	3A 1300v	10p	84	IN4004	1A 400v	3p																																																																																																																		
69	BA182	100mA 35v	5p	77	QA47	48mA 30v	5p	85	IN4148	75mA 75v	1p																																																																																																																		
70	BA183	75mA 50v	1p	78	DA30	10mA 30v	5p	86	IN4151	150mA 75v	2p																																																																																																																		
71	BA186	200mA 150v	4p	79	DA31	50mA 115v	7p	87	IN5414	3A 400v	10p																																																																																																																		
72	BA198	115mA 50v	6p	80	DA200	80mA 50v	6p	88	IN5407	3A 800v	12p																																																																																																																		
73	BY126	1A 650v	7p	81	IN814	75mA 100v	2p	89	IS923	220mA 200v	2p																																																																																																																		
74	BY127	2A 1250v	11p	82	IN916	75mA 100v	2p																																																																																																																						
75	BY206	400mA 350v	20p	83	IN4002	1A 100v	2p																																																																																																																						
84	IN4004	1A 400v	3p																																																																																																																										
85	IN4148	75mA 75v	1p																																																																																																																										
86	IN4151	150mA 75v	2p																																																																																																																										
87	IN5414	3A 400v	10p																																																																																																																										
88	IN5407	3A 800v	12p																																																																																																																										
89	IS923	220mA 200v	2p																																																																																																																										

all at 29p each																																																																																																																																																																								
<table border="1"> <tr><td>327</td><td>AC153K</td><td>18</td><td>P</td><td>2A</td><td>1W</td><td>1</td></tr> <tr><td>328</td><td>AD161</td><td>S055</td><td>20</td><td>P</td><td>1A</td><td>4W</td><td>1</td></tr> <tr><td>329</td><td>AD162</td><td>S055</td><td>20</td><td>P</td><td>1A</td><td>6W</td><td>1</td></tr> <tr><td>330</td><td>AF139</td><td>TO22</td><td>15</td><td>P</td><td>10</td><td>10</td><td>275</td></tr> <tr><td>331</td><td>BD116</td><td>TO38</td><td>180</td><td>P</td><td>150</td><td>6W</td><td>80</td></tr> <tr><td>332</td><td>BD118</td><td>TO3</td><td>60</td><td>P</td><td>3A</td><td>10W</td><td>60</td></tr> <tr><td>333</td><td>BD111</td><td>TO126</td><td>50</td><td>N</td><td>3A</td><td>10W</td><td>60</td></tr> <tr><td>334</td><td>BD132</td><td>TO126</td><td>45</td><td>P</td><td>3A</td><td>11W</td><td>60</td></tr> <tr><td>335</td><td>BD176</td><td>TO126</td><td>45</td><td>P</td><td>3A</td><td>30W</td><td>3</td></tr> <tr><td>336</td><td>BD242</td><td>TO126</td><td>300</td><td>N</td><td>150</td><td>1W</td><td>10</td></tr> <tr><td>337</td><td>BD236</td><td>TO126</td><td>60</td><td>P</td><td>2A</td><td>25W</td><td>3</td></tr> <tr><td>338</td><td>BS238</td><td>TO126</td><td>100</td><td>P</td><td>200</td><td>25W</td><td>40</td></tr> <tr><td>339</td><td>BC459</td><td>TO126</td><td>300</td><td>N</td><td>100</td><td>5W</td><td>40</td></tr> <tr><td>340</td><td>BSX29</td><td>TO18</td><td>12</td><td>P</td><td>200</td><td>360</td><td>20</td></tr> <tr><td>341</td><td>OC45</td><td>TO18</td><td>12</td><td>P</td><td>200</td><td>360</td><td>20</td></tr> <tr><td>342</td><td>TP41A</td><td>TO220</td><td>60</td><td>N</td><td>6A</td><td>55W</td><td>3</td></tr> <tr><td>343</td><td>TP42A</td><td>TO220</td><td>60</td><td>P</td><td>6A</td><td>65W</td><td>3</td></tr> <tr><td>344</td><td>TP3056</td><td>TO3</td><td>60</td><td>N</td><td>15A</td><td>40W</td><td>3</td></tr> <tr><td>345</td><td>2N3019</td><td>TO3</td><td>75</td><td>N</td><td>1A</td><td>800</td><td>100</td></tr> <tr><td>346</td><td>2N5320</td><td>TO39</td><td>75</td><td>N</td><td>2A</td><td>1W</td><td>50</td></tr> <tr><td>347</td><td>2N5322</td><td>TO39</td><td>75</td><td>P</td><td>2A</td><td>1W</td><td>50</td></tr> </table>		327	AC153K	18	P	2A	1W	1	328	AD161	S055	20	P	1A	4W	1	329	AD162	S055	20	P	1A	6W	1	330	AF139	TO22	15	P	10	10	275	331	BD116	TO38	180	P	150	6W	80	332	BD118	TO3	60	P	3A	10W	60	333	BD111	TO126	50	N	3A	10W	60	334	BD132	TO126	45	P	3A	11W	60	335	BD176	TO126	45	P	3A	30W	3	336	BD242	TO126	300	N	150	1W	10	337	BD236	TO126	60	P	2A	25W	3	338	BS238	TO126	100	P	200	25W	40	339	BC459	TO126	300	N	100	5W	40	340	BSX29	TO18	12	P	200	360	20	341	OC45	TO18	12	P	200	360	20	342	TP41A	TO220	60	N	6A	55W	3	343	TP42A	TO220	60	P	6A	65W	3	344	TP3056	TO3	60	N	15A	40W	3	345	2N3019	TO3	75	N	1A	800	100	346	2N5320	TO39	75	N	2A	1W	50	347	2N5322	TO39	75	P	2A	1W	50
327	AC153K	18	P	2A	1W	1																																																																																																																																																																		
328	AD161	S055	20	P	1A	4W	1																																																																																																																																																																	
329	AD162	S055	20	P	1A	6W	1																																																																																																																																																																	
330	AF139	TO22	15	P	10	10	275																																																																																																																																																																	
331	BD116	TO38	180	P	150	6W	80																																																																																																																																																																	
332	BD118	TO3	60	P	3A	10W	60																																																																																																																																																																	
333	BD111	TO126	50	N	3A	10W	60																																																																																																																																																																	
334	BD132	TO126	45	P	3A	11W	60																																																																																																																																																																	
335	BD176	TO126	45	P	3A	30W	3																																																																																																																																																																	
336	BD242	TO126	300	N	150	1W	10																																																																																																																																																																	
337	BD236	TO126	60	P	2A	25W	3																																																																																																																																																																	
338	BS238	TO126	100	P	200	25W	40																																																																																																																																																																	
339	BC459	TO126	300	N	100	5W	40																																																																																																																																																																	
340	BSX29	TO18	12	P	200	360	20																																																																																																																																																																	
341	OC45	TO18	12	P	200	360	20																																																																																																																																																																	
342	TP41A	TO220	60	N	6A	55W	3																																																																																																																																																																	
343	TP42A	TO220	60	P	6A	65W	3																																																																																																																																																																	
344	TP3056	TO3	60	N	15A	40W	3																																																																																																																																																																	
345	2N3019	TO3	75	N	1A	800	100																																																																																																																																																																	
346	2N5320	TO39	75	N	2A	1W	50																																																																																																																																																																	
347	2N5322	TO39	75	P	2A	1W	50																																																																																																																																																																	

<b>DIODES ZENER</b> BY MOTOROLA, MULLARD, SESCOSEM BZX79/BZV88C 400mW 5%		<b>LEDS</b> 2mm TIL 209C 90. GR 13p 91. RED 9p 92. YEL 15p.																																
<table border="1"> <tr><th>ITEM</th><th>3V3</th><th>4V7</th><th>5V1</th><th>5V6</th><th>6V8</th><th>9V1</th><th>10</th><th>15</th><th>18</th><th>5p</th></tr> <tr><td>BZX79/BZV88C</td><td>93</td><td>94</td><td>95</td><td>96</td><td>97</td><td>98</td><td>99</td><td>100</td><td>101</td><td></td></tr> </table>		ITEM	3V3	4V7	5V1	5V6	6V8	9V1	10	15	18	5p	BZX79/BZV88C	93	94	95	96	97	98	99	100	101		<table border="1"> <tr><td>90</td><td>GR</td><td>13p</td><td>91</td><td>RED</td><td>9p</td><td>92</td><td>YEL</td><td>15p</td></tr> </table>		90	GR	13p	91	RED	9p	92	YEL	15p
ITEM	3V3	4V7	5V1	5V6	6V8	9V1	10	15	18	5p																								
BZX79/BZV88C	93	94	95	96	97	98	99	100	101																									
90	GR	13p	91	RED	9p	92	YEL	15p																										
<table border="1"> <tr><th>ITEM</th><th>102</th><th>103</th><th>104</th><th>105</th><th>106</th><th>107</th><th>108</th><th>109</th><th>110</th><th>8p</th></tr> <tr><td>BZX61/85C 1W3 5%</td><td>5/8</td><td>9/1</td><td>10</td><td>12</td><td>15</td><td>18</td><td>20</td><td>22</td><td>24</td><td></td></tr> </table>		ITEM	102	103	104	105	106	107	108	109	110	8p	BZX61/85C 1W3 5%	5/8	9/1	10	12	15	18	20	22	24												
ITEM	102	103	104	105	106	107	108	109	110	8p																								
BZX61/85C 1W3 5%	5/8	9/1	10	12	15	18	20	22	24																									

all at 39p each																																																																																																																																									
<table border="1"> <tr><td>348</td><td>ACV17</td><td>TO8</td><td>32</td><td>P</td><td>500</td><td>260</td><td>4</td></tr> <tr><td>349</td><td>ACV18</td><td>TO5</td><td>30</td><td>P</td><td>500</td><td>280</td><td>1</td></tr> <tr><td>350</td><td>ACV22</td><td>TO5</td><td>15</td><td>P</td><td>500</td><td>280</td><td>1</td></tr> <tr><td>351</td><td>ASV27</td><td>TO5</td><td>15</td><td>P</td><td>200</td><td>150</td><td>8</td></tr> <tr><td>352</td><td>BCV33</td><td>TO5</td><td>25</td><td>P</td><td>100</td><td>250</td><td>25</td></tr> <tr><td>353</td><td>BD112</td><td>TO20</td><td>60</td><td>N</td><td>12A</td><td>20W</td><td>3</td></tr> <tr><td>354</td><td>TP427</td><td>TO32</td><td>250</td><td>N</td><td>1A</td><td>40W</td><td>10</td></tr> <tr><td>355</td><td>TP110</td><td>---</td><td>60</td><td>P</td><td>2A</td><td>50W</td><td>---</td></tr> <tr><td>356</td><td>TP118</td><td>---</td><td>60</td><td>P</td><td>2A</td><td>50W</td><td>---</td></tr> <tr><td>357</td><td>TP2955</td><td>TOP3</td><td>---</td><td>P</td><td>15A</td><td>30W</td><td>3</td></tr> <tr><td>358</td><td>2N1304</td><td>TO5</td><td>20</td><td>N</td><td>300</td><td>150</td><td>4</td></tr> <tr><td>359</td><td>2N1305</td><td>TO5</td><td>20</td><td>P</td><td>300</td><td>150</td><td>4</td></tr> <tr><td>360</td><td>2N1308</td><td>TO5</td><td>18</td><td>P</td><td>300</td><td>150</td><td>12</td></tr> <tr><td>361</td><td>2N1309</td><td>TO5</td><td>15</td><td>P</td><td>300</td><td>150</td><td>12</td></tr> <tr><td>362</td><td>2N3056</td><td>TO6</td><td>60</td><td>N</td><td>15A</td><td>115W</td><td>2</td></tr> <tr><td>363</td><td>2N3056</td><td>TO3</td><td>60</td><td>N</td><td>15A</td><td>115W</td><td>2</td></tr> <tr><td>364</td><td>2N3440</td><td>TO5</td><td>250</td><td>N</td><td>1A</td><td>1W</td><td>15</td></tr> </table>		348	ACV17	TO8	32	P	500	260	4	349	ACV18	TO5	30	P	500	280	1	350	ACV22	TO5	15	P	500	280	1	351	ASV27	TO5	15	P	200	150	8	352	BCV33	TO5	25	P	100	250	25	353	BD112	TO20	60	N	12A	20W	3	354	TP427	TO32	250	N	1A	40W	10	355	TP110	---	60	P	2A	50W	---	356	TP118	---	60	P	2A	50W	---	357	TP2955	TOP3	---	P	15A	30W	3	358	2N1304	TO5	20	N	300	150	4	359	2N1305	TO5	20	P	300	150	4	360	2N1308	TO5	18	P	300	150	12	361	2N1309	TO5	15	P	300	150	12	362	2N3056	TO6	60	N	15A	115W	2	363	2N3056	TO3	60	N	15A	115W	2	364	2N3440	TO5	250	N	1A	1W	15
348	ACV17	TO8	32	P	500	260	4																																																																																																																																		
349	ACV18	TO5	30	P	500	280	1																																																																																																																																		
350	ACV22	TO5	15	P	500	280	1																																																																																																																																		
351	ASV27	TO5	15	P	200	150	8																																																																																																																																		
352	BCV33	TO5	25	P	100	250	25																																																																																																																																		
353	BD112	TO20	60	N	12A	20W	3																																																																																																																																		
354	TP427	TO32	250	N	1A	40W	10																																																																																																																																		
355	TP110	---	60	P	2A	50W	---																																																																																																																																		
356	TP118	---	60	P	2A	50W	---																																																																																																																																		
357	TP2955	TOP3	---	P	15A	30W	3																																																																																																																																		
358	2N1304	TO5	20	N	300	150	4																																																																																																																																		
359	2N1305	TO5	20	P	300	150	4																																																																																																																																		
360	2N1308	TO5	18	P	300	150	12																																																																																																																																		
361	2N1309	TO5	15	P	300	150	12																																																																																																																																		
362	2N3056	TO6	60	N	15A	115W	2																																																																																																																																		
363	2N3056	TO3	60	N	15A	115W	2																																																																																																																																		
364	2N3440	TO5	250	N	1A	1W	15																																																																																																																																		

<b>FUSES</b> DC 20mm x 5mm 395 100mA 4p. 396 500mA 4p. 397. 1A 4p. 398 2A 4p. MAINS 1" x 1" 399 3A 5p. 400 5A 5p. 401 13A 5p.		<b>ICs</b> DIL PINNING (-) 111 301 (8) 112 380 (14) 113 556 (8) 144 709 (8) 115 723 (14) 116 741 (8) 117 CA3130 (8) 20p 48p 18p 18p 24p 18p 96p	
---	--	---	--

all at 19p each		all at 89p each																																																																																			
<table border="1"> <tr><td>279</td><td>AC107</td><td>TO1</td><td>15</td><td>P</td><td>10</td><td>80</td><td>1</td></tr> <tr><td>280</td><td>AC127</td><td>TO1</td><td>12</td><td>N</td><td>500</td><td>340</td><td>15</td></tr> <tr><td>281</td><td>AC128</td><td>TO1</td><td>16</td><td>P</td><td>1A</td><td>287</td><td>1</td></tr> <tr><td>282</td><td>AC141B</td><td>TO1</td><td>15</td><td>N</td><td>1A2</td><td>1W</td><td>1</td></tr> <tr><td>283</td><td>AC142</td><td>TO1</td><td>20</td><td>P</td><td>2A2</td><td>1W</td><td>1</td></tr> <tr><td>284</td><td>AC153</td><td>TO1A</td><td>18</td><td>P</td><td>2A</td><td>1W</td><td>1.5</td></tr> <tr><td>285</td><td>AC176</td><td>TO1</td><td>20</td><td>N</td><td>1A</td><td>1W</td><td>1</td></tr> <tr><td>286</td><td>AC187</td><td>TO1</td><td>15</td><td>N</td><td>2A</td><td>1W</td><td>1</td></tr> <tr><td>287</td><td>AC188</td><td>TO1</td><td>15</td><td>P</td><td>2A</td><td>1W</td><td>1</td></tr> <tr><td>288</td><td>BC140</td><td>TO39</td><td>40</td><td>N</td><td>1A</td><td>3W7</td><td>50</td></tr> <tr><td>289</td><td>BC141</td><td>TO39</td><td>60&lt;/</td></tr></table>		279	AC107	TO1	15	P	10	80	1	280	AC127	TO1	12	N	500	340	15	281	AC128	TO1	16	P	1A	287	1	282	AC141B	TO1	15	N	1A2	1W	1	283	AC142	TO1	20	P	2A2	1W	1	284	AC153	TO1A	18	P	2A	1W	1.5	285	AC176	TO1	20	N	1A	1W	1	286	AC187	TO1	15	N	2A	1W	1	287	AC188	TO1	15	P	2A	1W	1	288	BC140	TO39	40	N	1A	3W7	50	289	BC141	TO39	60</
279	AC107	TO1	15	P	10	80	1																																																																														
280	AC127	TO1	12	N	500	340	15																																																																														
281	AC128	TO1	16	P	1A	287	1																																																																														
282	AC141B	TO1	15	N	1A2	1W	1																																																																														
283	AC142	TO1	20	P	2A2	1W	1																																																																														
284	AC153	TO1A	18	P	2A	1W	1.5																																																																														
285	AC176	TO1	20	N	1A	1W	1																																																																														
286	AC187	TO1	15	N	2A	1W	1																																																																														
287	AC188	TO1	15	P	2A	1W	1																																																																														
288	BC140	TO39	40	N	1A	3W7	50																																																																														
289	BC141	TO39	60</																																																																																		

# MAGENTA ELECTRONICS LTD.

## R.E.C. PROJECT KITS

Make us YOUR No. 1 SUPPLIER OF KITS and COMPONENTS for R.E.C. Projects. We supply carefully selected sets of parts to enable you to construct R.E.C. projects. Project kits include ALL THE ELECTRONICS AND HARDWARE NEEDED - we have even included appropriate screws, nuts and I.C. sockets. Each project kit comes complete with its own FREE COMPONENT IDENTIFICATION SHEET. We supply - you construct. PRICES INCLUDE CASES UNLESS OTHERWISE STATED. BATTERIES NOT INCLUDED. IF YOU DO NOT HAVE THE ISSUE OF R.E.C. WHICH CONTAINS THE PROJECT - YOU WILL NEED TO ORDER THE INSTRUCTIONS/REPRINT AS AN EXTRA - 45p. each.

## 80/81 ELECTRONICS CATALOGUE

**KITS  
ICs  
TRANSISTORS  
CAPACITORS**

Hundreds of illustrations, product data, circuits and details of all our kits and educational courses. Up to date price list included. All products are stock lines for fast delivery by FIRST CLASS POST. Send 6 x 10p stamps for your copy.

**TOOLS  
RESISTORS  
HARDWARE  
CASES**

## ADVENTURES WITH ELECTRONICS

by Tom Duncan

An easy to follow book suitable for all ages, ideal for beginners. No Soldering. Uses an 'S Dec' breadboard. Gives clear instructions with lots of pictures. 16 projects - including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec and the components for the projects. Adventures With Electronics. £1.75. Component Pack £16.72 less battery.

## ADVENTURES WITH MICROELECTRONICS

Same style as above book; 11 projects based on integrated circuits - includes: dice, two-tone doorbell, electronic organ, MW/LW radio, reaction timer, etc. Component pack includes a Bimboard, 1 plug-in breadboard and the components for the projects. Adventures with Microelectronics £2.35. Component pack £27.95 less battery.

### LIGHT CHANGE ALARM Dec. 78. £11.84

In daylight detects someone moving around a room - after dark can be triggered by just torchlight. Units output rs from a relay (included).

### DYNAMIC MIC PRE AMP Sept. 78. £5.82

Features the ZN424E - with very low distortion and noise.

### ULTRA SENSITIVE ULTRASONIC REMOTE CONTROL Feb 79 £12.45 and DOPPLER SHIFT ADD ON UNIT Mar 79. extra £5.22

First part covers the construction of a sensitive remote control switch - an ultrasonic transmitter and receiver. The Doppler Shift add on unit detects movement within the vicinity of the transducers, and so has applications as a burglar alarm.

### RING OF LEDS PRINT TIMER Jan 80 £11.22.

Unusual display indicates 8 segments of timing period. A ring of 8 leds light progressively. Switch selectable timing periods of 1, 2, 3, and 4 minutes. Very smartly housed in a Vero Case.

### LOGIC TESTER Jan 80 £5.89.

Detects overload, logic state and pulse voltages in TTL circuits. A piece of veroboard is included - but the layout is left to the constructor. Portable. Battery operated. Supplied with test leads.

### TELEPHONE BELL REPEATER Feb 80 £7.48.

Includes 2 cases and speakers. Twin fig 8 cable to link units 7p per metre extra. Remote unit warns when the telephone rings. Battery powered.

### INFRA RED INTRUDER ALARM. Mar 80 £9.98 less cases.

Invisible infra red beam protects property - when the beam is broken the relay in the receiver is activated. Max. range 3 metres. Kit includes relay. Requires 9V supply.

### STEREO MIXER Mar. 80 £12.73

Mixes high impedance dynamic mic and nurse inputs. Based on 4 LF351 ICs. Two dual pots form the controls for mic, and line. Sockets for inputs and outputs.

### CONSTANT CURRENT NI-CAD CHARGER. Sept 80. £19.98

Charges up to 10 cells - suitable for all normal ni-cads. Continuously variable output current. Panel meter indicates the output current. Supplied with leads.

### BASIC SHORT WAVE RADIO June 78 £18.95

3 band trf design covering 1.2 to 24 MHz. Features five front panel controls - wavechange, bandset, bandspread, reaction, and aerial attenuator. Built on a pcb. The frequency range covers all the HF broadcast and amateur bands.

### 3 BAND SHORT WAVE PRESELECTOR Feb 79 £15.98

Uses a dual gate MOSFET. Tunes from 1.6 to 30 MHz in 3 bands. Adjustable rf gain control. Provides additional selectivity and sensitivity when used with a receiver.

### BEGINNERS MEDIUM WAVE RADIO Aug. 79. £6.98

Provides crystal earpiece reception of the M.W. band. Crystal earpiece is supplied.

### TOP BAND FERRITE AERIAL UNIT Sept 79 £8.98

An active tuned and amplified 160 metre band ferrite rod aerial unit. Provides directional reception facilities when used with a 160 metre receiver. Reduces interference and increases sensitivity.

### SINGLE CHIP M.W. RADIO Sept 79 £11.37

Simple sensitive M.W. receiver with loudspeaker. Uses an LM389 IC for rf gain, af gain and power output. Ideal for beginners.

### SHORT WAVE AERIAL TUNING UNIT Dec 79 £11.98

Improves receiver performance over 1.6MHz to 30MHz. Provides an increase in signal strength and rejection of strong interfering signals, spurious responses etc.

### SIMPLE SHORT WAVE SUPERHET. Feb and Mar 80 £27.39

Covers 180 to 20 metres. No alignment problems. Very low battery current. Plug in coils. Uses a dual gate MOSFET as a mixer. Regenerative RIF stage allows reception of a.m., c.w., and s.s.b.

### 80 METRE AMATEUR BAND RECEIVER July 80 £19.98

Expressly designed for sbb and cw amateur signals. This simple homodyne design provides world wide reception of amateur transmissions. Housed in a smart Vero case.

### PORTABLE SHORT WAVE RADIO Aug 80. £18.94.

Suitable for beginners. Covers 25, 31, 41, and 49 metre bands. Fitted with telescopic aerial. Use of TBA820M amplifier IC provides loudspeaker output. Regenerative t.r.f. receiver. Smart ABS case.

LATEST KITS: S.A.E. OR 'PHONE FOR PRICES

## MAGENTA ELECTRONICS LTD.

RC3, 98 CALAIS ROAD, BURTON-ON-TRENT, STAFFS., DE13 0UL. 0283-65435. 9-12, 2-5 MON.-FRI.

MAIL ORDER ONLY

ADD 35p. P.&P. TO ALL ORDERS. ALL PRICES INCLUDE 15% V.A.T. OFFICIAL ORDERS FROM SCHOOLS ETC. WELCOME. ENQUIRIES MUST INCLUDE S.A.E. OVERSEAS: SEND ORDER WITH 3 INTERNATIONAL POSTAL COUPONS WE WILL QUOTE EXACT PRICE BY AIR MAIL.

EIRE & BFPO ORDERS U.K. PRICES - LESS 10% (COVERS V.A.T. REFUND & EXPORT DOCUMENTS) PAYMENT: STERLING U.K. BANK DRAFT, U.K. POSTAL ORDERS or U.K. CHEQUE. ENQUIRIES: ENCLOSE 2 INTERNATIONAL POSTAL COUPONS.



Tremelo modulation unit Nov 80 £11.27.  
CMOS combination switch Nov 80 £7.22.  
Coil coupled 5W converter Nov 80 £20.90.

Go no go transistor tester Oct 80. £7.58.  
Personal M.W. Radio, Oct 80. £10.36.

## INTO ELECTRONICS CONSTRUCTION

### R.E.C. LATEST KITS

## TOWERS INTERNATIONAL TRANSISTOR SELECTOR £10.35

ANTEX X25 SOLDERING IRON. 25W. £4.98.

SOLDERING IRON STAND. £2.03.

SPARE BITS. Small, standard, large. 65p each.

SOLDER. Handy size. 95p.

EUROBREADBOARD. £8.20.

LOW COST LONG NOSE PLIERS. £1.88

LOW COST CUTTERS. £1.69.

SIREN. 12V. £5.18

P.C.B. ASSEMBLY JIG. £11.98.

P.C.B. ETCHING KIT. £4.98.

MONO HEADPHONES. 2K Padded. Superior, sensitive. £2.98.

STEREO HEADPHONES. 8 ohm. Padded. £4.35.

DESOLDERING BRAID. 69p.

HOW TO SOLDER BOOKLET. 12p.

HEAT SINK TWEEZERS. 15p.

SOLDER BOBBIN. 30p.

DESOLDER PUMP. £5.98.

CONNECTING WIRE PACK. 5 x 5 yd coils. 55p.

VERO SPOT FACE CUTTER. £1.21.

VERO PIN INSERTION TOOL. 0.1". £1.66. 0.15" £1.67.


RESISTOR COLOUR CODE CALCULATOR. 21p.

MULTIMETER TYPE 1. 1,000 o.p.v. with probes. 2" x 3/4" x 1". £6.66.

MULTIMETER TYPE 2. 20,000 o.p.v. with probes. 5" x 3/4" x 1 1/2". £11.52.

MAGENTA gives you FAST DELIVERY BY FIRST-CLASS POST OF QUALITY COMPONENTS AND KITS. All products are stock lines and are new and full specification. We give personal service and quality products to all our customers - HAVE YOU TRIED US?

PRICES INCLUDE V.A.T.

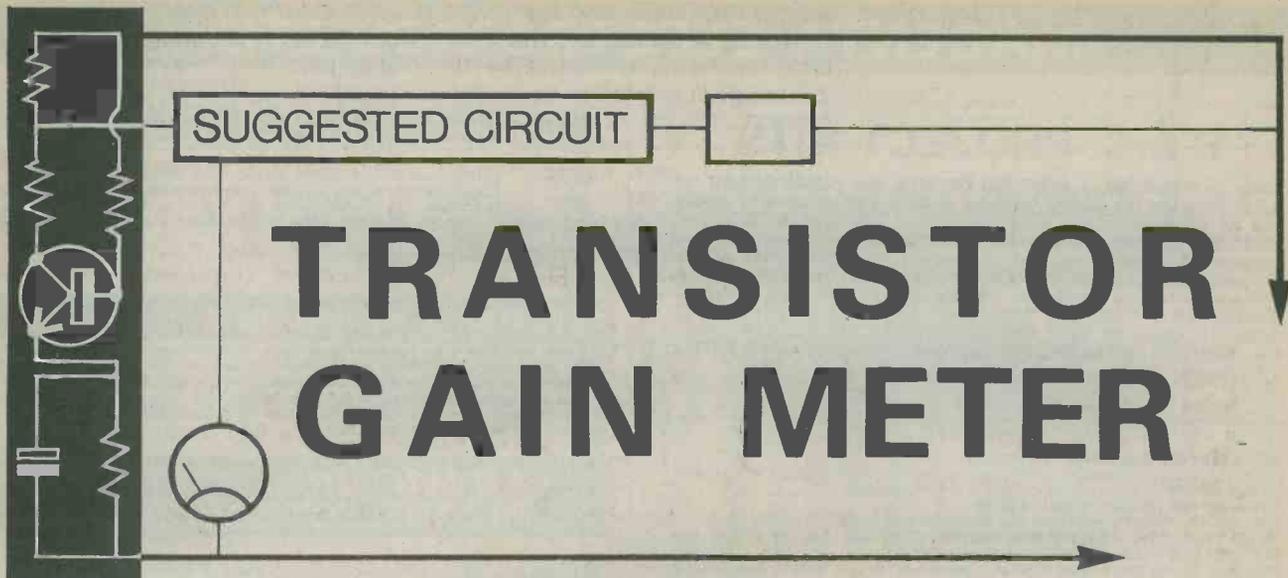

# TRANSISTOR GAIN METER

By G. A. French

The instrument described in this article is intended to measure the  $h_{FE}$ , or d.c. current gain, of n.p.n. or p.n.p. transistors. The measurement range is from 30 to 1,000 times, and readings are taken at a collector current of slightly more than 10mA. Since a transistor gain meter is not normally used extensively in the amateur workshop, care has been taken to keep the component count low without sacrificing accuracy. The circuit requires one voltmeter for transistor gain evaluation, and this can be any multimeter, set to a low d.c. volts range, which is connected to the gain meter when required. Thus, no expensive meter movement is permanently tied up with the instrument.

The gain meter is primarily intended for checking silicon transistors, although it can also be employed with the now obsolescent germanium types. The description of the circuit assumes that it is silicon transistors which are being checked.

## BASIC CONFIGURATIONS

To understand how the meter functions, let us first examine the circuit of Fig. 1 (a). In this a p.n.p. silicon transistor is connected as an emitter follower, with the emitter current flowing through resistor  $R_A$ . The voltmeter monitors the voltage across this resistor.

Base bias for the transistor is applied via the variable resistor  $R_B$ , and the circuit is powered by a 5 volt stabilized supply.

As the resistance inserted into circuit by  $R_B$  is reduced, the transistor base current increases as also does the amplified emitter current and the voltage dropped across  $R_A$ . If  $R_B$  is adjusted so that the voltage across  $R_A$  (as indicated by the voltmeter) is equal to 2.2 volts, the situation shown in Fig. 1(b) is set up. Here, 2.2 volts appear across  $R_A$  with approximately 0.6 volt being dropped across the base-emitter junction of the transistor. The remaining 2.2 volts must then appear across  $R_B$ . Since the same voltage

appears across  $R_A$  and  $R_B$ , the currents flowing in them are inversely proportional to their values. Thus, if  $R_B$  inserts a resistance which is 100 times the value of  $R_A$ , the current flowing in  $R_A$  is 100 times the current flowing in  $R_B$  and the transistor has a base-to-emitter current gain of 100 times.

The circuit of Fig. 1 (b) makes it possible to measure the base-to-emitter current gain of any small p.n.p. silicon transistor. After the transistor has been connected into the circuit,  $R_B$  is adjusted until the voltmeter reads 2.2 volts. The gain is then found from a previously calibrated scale fitted behind the control knob of  $R_B$ .


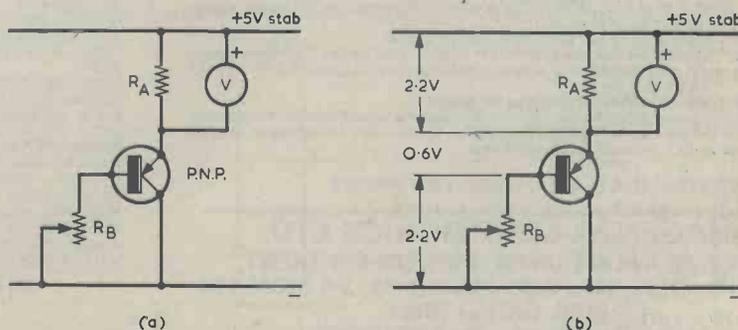


Fig. 1(a). A circuit which is capable of evaluating the base-to-emitter current gain of a p.n.p. silicon transistor.

(b). If  $R_B$  is adjusted for a reading of 2.2 volts in the voltmeter, the voltage distribution in the circuit is as shown here.

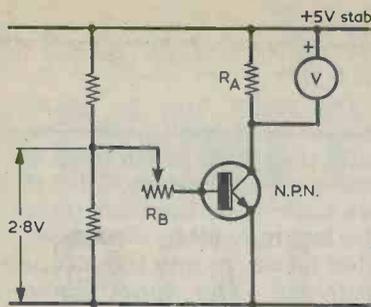

**Fig. 2.** This circuit can be used to measure the base-to-collector gain of a silicon n.p.n. transistor. RB is adjusted for an indication of 2.2 volts in the voltmeter, and this voltage also appears across RB.

The base-to-emitter current gain is not precisely the same as hFE, which is the base-to-collector current gain, because the emitter current is the sum of the collector and the base currents. However, the base current is very much smaller than the collector current and little error is introduced, particularly at the higher gain figures, if its presence is ignored. The circuit of Fig 1(b) can in consequence be looked upon as a practical arrangement capable of assessing the hFE of a p.n.p. transistor.

To ease polarity switching requirements, it is desirable to have a basic circuit very similar to that of Fig 1(b) for the evaluation of n.p.n. transistors. This circuit is shown in Fig. 2, where the emitter of the n.p.n. transistor is connected to the negative rail and the collector is connected to RA. RB is not now returned to the negative rail but connects instead to a potential divider which offers a voltage which is 2.8 volts positive of the negative rail. The standing current flowing through the two potential divider resistors is very much higher than any current which is likely to be drawn by RB, and so the 2.8 volt point may be considered as having virtually the same level of voltage stabilization as has the 5 volt positive rail.

As with Fig. 1(a), RB is again adjusted so that the voltage across RA is 2.2 volts. Since about 0.6 volt is dropped

across the base-emitter junction of the transistor, the voltage across RB will then also be 2.2 volts. The base-to-collector current gain will be equal to the resistance inserted by RB divided by the resistance of RA, and the gain calibration given to RB for Fig. 1(b) will be equally applicable to the gain measuring circuit of Fig. 2.

### COMPLETE CIRCUIT

The two basic circuits of Fig. 1(b) and Fig. 2 are combined in the complete working circuit of Fig. 3. RA now appears as the 200Ω resistor, R4, and the voltmeter connected across it is a multimeter plugged into sockets SK4 and SK5. RB is replaced by R3 in series with VR1 or VR2 according to the position of switch S2. When S2 is in position "1", VR1 is in circuit and provides current gain readings from 30 to 100 times. A gain of 30 is indicated when R3 plus the resistance inserted by VR1 is equal to 30 times 200Ω, or 6kΩ. A transistor current gain of 100 is indicated when R3 and VR1 insert 100 times 200Ω, or 20kΩ. Setting S2 to position "2" allows gain measurements from 100 to 1,000, these figures corresponding to resistances in R3 plus VR2 of 20kΩ and 200kΩ respectively.


The potential divider of Fig. 2 is given by R1 and R2. These are connected in series when S1 is set to "N.P.N." and the voltage at their junction calcu-

lates at almost exactly 2.8 volts positive of the negative rail. The standing current in the potential divider is 18.5mA.


Putting S1 to "P.N.P." opens the potential divider circuit and returns R3 to the negative rail, to give the same circuit conditions as existed in Fig. 1(b). S1 provides the only polarity switching required. Further polarity changes are automatically given at the three test sockets. An n.p.n. test transistor has its collector connected to SK1 and its emitter to SK3, whilst a p.n.p. test transmitter has its emitter connected to SK1 and its collector to SK3. With both transistor types, the base connects to SK2.

Since R4 has a value of 200Ω, the collector or emitter current which flows in this resistor after VR1 or VR2 has been adjusted for the voltage reading of 2.2 volts is 11mA.

R3 is a current limiting resistor. With S1 in the "P.N.P." position, a combination of possible short-circuits in the test connections at SK1 and SK2, and at SK4 and SK5, could cause the full 5 volts of the supply to appear across R3 and VR1 or R3 and VR2. The more vulnerable component here is VR2. This is a standard ½ watt potentiometer, and the current which flows through its track must not exceed 1.5mA. R3 ensures that the maximum possible current which can flow is 5 volts divided by 3.9Ω, or 1.3mA.

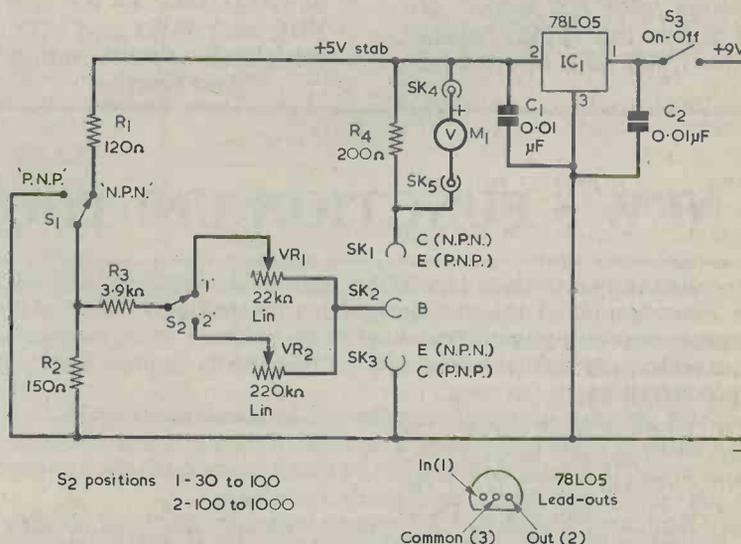

**Fig. 3.** The complete circuit of the transistor gain meter. C1 and C2 ensure stability in IC1, and should be positioned close to its lead-outs.

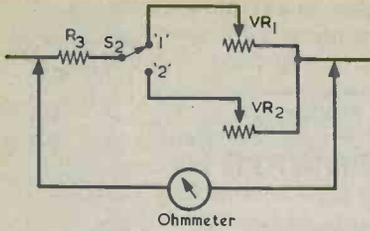

**Fig. 4.** VR1 and VR2 are calibrated for gain figures by connecting an ohmmeter in the manner illustrated here.


### CALIBRATION

VR1 and VR2 are calibrated by connecting an ohmmeter as shown in Fig. 4, and setting S2 to position "1" or position "2" for each range. No power is applied to the gain meter and no connection is made to SK2. Temporary scales are fitted behind the potentiometer knobs, which must of course be pointer types, and these are marked up with gain figures corresponding to the resistances indicated by the charts in Fig. 5. VR2 will normally have a tolerance on value of 20% and if it is at or very close to the minimum value within tolerance it may not be possible to obtain a calibration for gain figures above 900. However the probability, in practice, will be that most potentiometers likely to be encountered will provide resistances, in series with R3, which are well above the 200kΩ needed for the 1,000 gain figure calibration.

### COMPONENTS

All the components are readily obtainable. As already mentioned, VR2 is a standard sized potentiometer rated at ½ watt. VR1 is a similar type of potentiometer. All three switches are toggle types. The fixed resistors are ½ watt 5% components. A slight increase in accuracy will, however, be given if R4 is 2% or 1%, rather than 5%. IC1 is a standard 78L05 voltage regulator with a maximum rating of 100mA. In the inset view of its lead-outs in Fig. 3 the lead-outs are pointing towards the reader.

The current consumption from the 9 volt supply is equal to the emitter current of the test transistor when S1 is set to "P.N.P.". To this current is

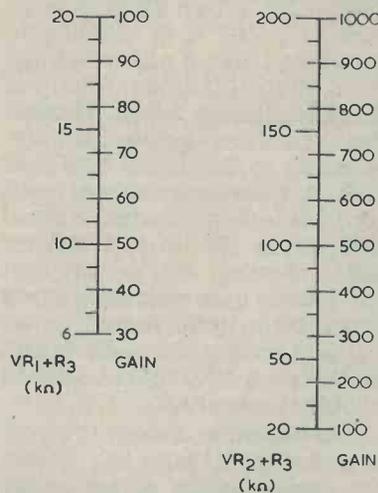

**Fig. 5.** Charts showing resistance in the series combinations of R3 and VR1, and of R3 and VR2, with the corresponding gain figures.

added the 18.5mA flowing in R1 and R2 when S1 is put to "N.P.N.".

The tester may be assembled in any small plastic case with the three switches, the two potentiometers and the five sockets on the front panel. The last may all be 4mm. insulated types, or any other types preferred. The most convenient method of making connections to the test transistors will be given by three short flexible leads, plugging into SK1, SK2 and SK3, these leads being terminated in miniature crocodile clips with vinyl sleeves.

When the gain meter is to be used, a multimeter is connected to SK4 and SK5 and is switched to a suitable low d.c. volts range. The test transistor is connected to SK1, SK2 and SK3, and S1 is put to the transistor polarity applicable. Both VR1 and VR2 should be at their maximum gain figure settings. S2 is set to position "2" and S3 is then closed to apply power. The resistance inserted by VR2 is slowly reduced until the multimeter indicates 2.2 volts, whereupon the transistor gain figure is read from the scale at VR2. If the gain is lower than 100 times, S2 is put to position "1" and the process repeated with VR1.

The gain meter is primarily intended for silicon transistors. It can give results which are nearly as accurate with germanium transistors but, in this case, VR1 and VR2 are adjusted for a reading of 2.5 volts in the meter.


## NEW 5 FUNCTION UNI-TOOL

Recently introduced by BOSS Industrial Mouldings Ltd is a new 5 function Uni-Tool which although orientated to the needs of power and automotive electrical engineers working both in-house and on-site is, nevertheless, equally useful to most engineers and 'Do It Yourselfers'.

Of primary importance is the spade terminal crimping facilities where, by utilising 2 separate sections of the tool both the conductor wire and the outer sleeving can be firmly crimped to the appropriate part of all commonly used spade terminals.

Both wire cutting and 0.75mm to 6mm wire stripping facilities are also incorporated, as are M2.6 to M5 bolt shearing capabilities.

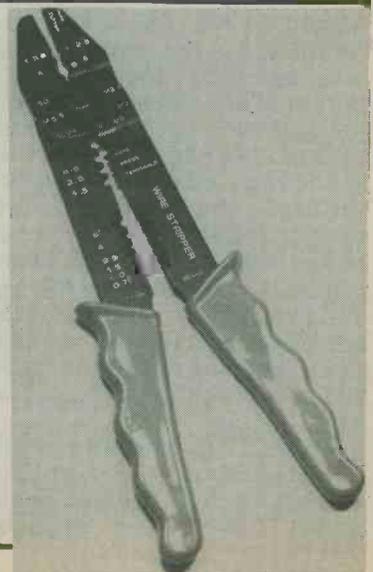Selling for only £2 this new Uni-Tool is a must for all self respecting engineers tool kits.



# CAR VOLTAGE MONITOR

By I. Peterson

This low cost unit has simple and robust circuitry, and is thereby well fitted for installation in a car. Its function is to monitor the battery voltage in 12 volt systems and it does this by means of three light-emitting diodes. When no diode is illuminated, the battery voltage is below 10.5 volts. One diode lit up indicates a voltage of 10.5 volts or more, two diodes a voltage of 12 volts or more and three diodes a voltage of 13.5 volts or more. As a result, the car driver can tell at a glance whether his battery is fully charged, whether it is running at nominal voltage and whether its voltage is at or below the discharged level.

## CIRCUIT OPERATION

The circuit appears in the accompanying diagram, in which the light-emitting diodes are LED1, LED2 and LED3. These diodes are fed by TR1, TR2 and TR3 respectively, the emitters of which are all returned to the stabilized voltage appearing across the forward biased silicon diodes, D1 to D4. The voltage across these diodes under low forward voltage conditions is almost exactly 2.4 volts.


The voltage being monitored is applied to the potential dividers coupling to the transistor bases. Roughly one-quarter of the nominal 12 volts is applied to each base, whereupon the transistors turn on much more abruptly as battery voltage rises than would occur if their emitters were returned direct to the negative rail. In the latter case each potential divider would need to apply approximately 0.6 volt to the base it connects to in order to turn the transistor on. Such a voltage is only one-twentieth of the nominal 12 volts.

## VOLTAGE LEVELS

When the battery voltage is below 10.5 volts all of the three transistors are turned off and no l.e.d. is alight. If the battery voltage rises to 10.5 volts the voltage applied to TR1 base by way of R1 and R2 is just sufficient to turn on the transistor, and LED1 commences to glow. It stays illuminated at all higher voltages. The values of R4 and R5 allow TR2 to turn on at a battery voltage of 12 volts, whereupon LED2 lights up at this and higher voltages. R7 and R8 cause TR3 to turn on at 13.5 volts, with the result that all three l.e.d.'s are then alight.

The voltage across D1 to D4 increases by about 0.2 volt as each l.e.d. is turned fully on, and this fact is reflected in the resistor values specified for the potential dividers. With the prototype circuit each l.e.d. becomes illuminated at precisely the voltage ascribed to it, as accurately as can be judged with an analogue voltmeter.

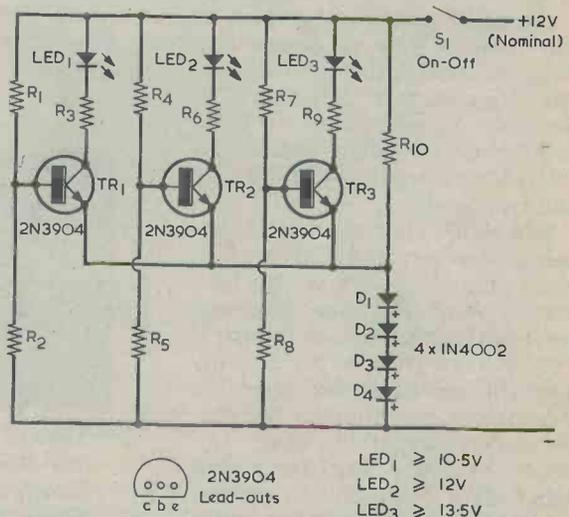All the components are standard types. Resistors with a tolerance of 5% will be accurate enough for practical requirements. The 7.5k $\Omega$  resistor required for R4 may only be available in  $\frac{1}{2}$  watt from some suppliers, and it is, of course, perfectly in order to use



The circuit of the battery voltage monitor. Voltage is indicated by the number of l.e.d.'s which are alight.

## COMPONENTS

### Resistors

(All  $\frac{1}{4}$  watt 5%)

R1	6.8k $\Omega$	R6	1.5k $\Omega$
R2	2.7k $\Omega$	R7	6.8k $\Omega$
R3	1.5k $\Omega$	R8	2.2k $\Omega$
R4	7.5k $\Omega$	R9	1.5k $\Omega$
R5	2.7k $\Omega$	R10	4.7k $\Omega$

### Semiconductors

TR1-TR3 2N3904  
D1-D4 1N4002  
LED1-LED3 see text

### Switch

S1 s.p.s.t. toggle

the higher wattage resistor. The three l.e.d.'s should be red or "extra bright" types.

The unit couples into the car electrical system at any convenient point. With no l.e.d. alight the standing current is of the order of 4 to 6mA, and it increases by about 5mA as each l.e.d. becomes illuminated. Such currents are negligible when compared with those normally provided by a car battery.

To prevent short-circuits to the car metalwork the unit should be completely enclosed in a small plastic case, this being situated at a convenient point in front of the car driver. On its front panel are mounted the three l.e.d.'s and the on-off switch. When not in use, the monitor can be turned off by means of the switch.

# NEWS . . . AND

## TELETEXT ADAPTOR RECEIVES DEPARTMENT OF INDUSTRY SUPPORT

Actual production samples of the Teletext Adaptor shown and demonstrated at the Viewdata 80 exhibition by Ayr Viewdata Ltd, Surbiton, Surrey, have now been produced for distribution to selected organisations in the UK and overseas.

Mr. H. O. Thomas, Ayr's Managing Director, said that this had been made possible by the enthusiastic support received from the Department of Industry. "They have given every encouragement and assistance in getting this British invention to the pre-production stage," he said.

Mr. Thomas explained that although a reduction in picture quality is expected when using an adaptor, this has been shown to be of a very minor, hardly discernible degree when using the Ayr adaptor.

The unit is compatible with most modern television receivers, which are automatically converted to remote control operation by means of the hand held infra-red key pad used for remote operation of the adaptor. It will enable viewers with standard TV



sets to take full advantage of the written-word information services provided by the BBC1 and BBC2 Ceefax and ITV Oracle systems. Of particular help to the hard of hearing, these systems will give general news, stock

exchange prices, financial information, weather forecasts, travel and other special interests.

When in production, the Ayr Teletext Adaptor is expected to have a retail price tag of not more than £150, including VAT.

exchange prices, financial information, weather forecasts, travel and other special interests.

## HIPFI - THE HI-FI AT YOUR HIP

Selfridges at their Oxford Street Store have the exclusive selling rights for a new product from Binatone International. As far as is known there is only one other such product on the market.

While you can carry around a portable radio or stereo it is very difficult to get true hi-fi reproduction. The problem is resolved with Hipfi, which can be worn as shown in the photograph.

The unit includes a leatherette carrying case, shoulderstrap, spare cassette pouch, batteries, featherlight hi-fi stereo headphones and even a pre-recorded demonstration tape for instant music.

Full facilities including separate volume controls for each channel, a tone control, facility for add-on second headphones (optional extra), fast forward and rewind with cueing and reviewing facility for locating the required piece of music.

The entire unit weighs 390 grms and while 3 alkaline pencil batteries will provide approximately 8 hours of music - it has facilities for an add-on mains adaptor (optional extra) for use at home.

It has a talk-line whereby simply pressing a button switches the listener to the outside world so he can converse with others without having to remove the headphones.



## IBA's small-dish digital-video satellite first

The first successful transmission of digital-video colour television pictures through a European space satellite using compact small-dish terminals at both ends of the link has been achieved at the IBA Engineering Centre at Crawley Court, Winchester.

This follows experiments earlier this year in which the IBA small-dish receive terminal was used to receive digital video signals transmitted from British Telecom's large 14 GHz space terminal at Goonhilly Downs, Cornwall.

The new series of experiments, again carried out with the co-operation of British Telecom and the European EUTEL-SAT organisation, passed digital signals through the 120-MHz-bandwidth transponder on the OTS satellite launched in May 1978.

The digital test signals, using the IBA-developed experimental 60Mbit/s digital encoder-decoder, were sent and received at Crawley Court, using the 14 GHz 2.5-metre dish 'up-link' terminal (about 1.5 kW transmitter power) and the 3-metre dish receive-terminal.

During preliminary tests using pseudo-random digital signals error rates of the order of only one error in each 10-million bits were recorded. When 625-line colour television pictures were transmitted through the system no degradations, other than those inherent in the experimental 60Mbit/s digital system, could be observed.


For these experiments, a conventional 625-line analogue television picture was encoded and transmitted through the 120MHz-bandwidth OTS transponder using a bandwidth of some 40MHz and modulated by means of quadrature phase-shift keying. The pictures were initially sampled at four times the frequency of the colour sub-carrier (142Mbit/s) and then digitally converted to the equivalent of twice sub-carrier frequency sampling (71 Mbit/s). This data rate is then further reduced by means of bit-reduction techniques including the use of differential pulse code modulation and, when error-protection and 'house-keeping' bits are added the system has a bit rate of 60Mbit/s.

The digital sampling rate and techniques used in these trials are for experimental purposes only and are not being proposed as an international standard. The IBA work however is showing that digital-video transmission would have useful advantages for news-gathering and national and international distribution links via space satellites.

SEASONAL  
GREETINGS

TO ALL OUR READERS
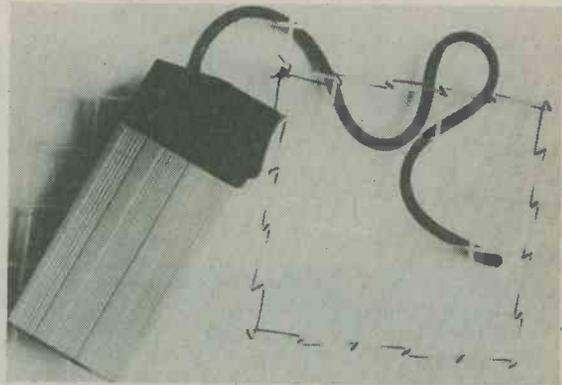
## FIBRE OPTIC LIGHT 'SEES' ROUND CORNERS



Edward Fletcher and Partners have announced a new, British-made, Light Probe.

Comprising a small hand-held torch and a 9" long, 3mm. diameter, flexible Fibre Optic Light Guide, the Light Probe can be used for illumination and inspection in inaccessible areas, or wherever a direct light source will not penetrate. By using Fibre Optics, the light from the torch is transmitted along the fibres and can be 'bent' round corners as required. If necessary, the Fibre Optic Light Guide can be detached and the torch used in the conventional manner.

The Light Probe also makes an ideal gift or novelty item for Christmas for adults, or children, as an introduction to the new technology of Fibre Optics. A small magnet can be attached to the end of the Light Guide for retrieval of metal objects in hard-to-reach places.

Only available from the manufacturers:-

Edward Fletcher & Partners, 25 West Park Road, Kew, Richmond, Surrey TW9 4DB. The price of the Light Probe is under £2.00.

Broadcast Training and Services Ltd of 2 Hills Road, Cambridge, have recently completed Sound Reinforcement Systems for both the Chapel and Hall of St John's College, Cambridge and for Chelmsford Cathedral.

In St John's, loudspeakers were successfully camouflaged so that they are virtually invisible in the context of the gilded and panelled 16th Century Hall, without impairing the high quality reproduction. Mixing facilities for several microphones and other sources were provided with provision also to record from the system.

The system installed in the very reverberant Chapel makes use of highly directional BTS loudspeakers with three circuits so that the sound always appears to come from the person speaking even when the speaking points are widely separated. The directional properties are important to prevent the excitation of unwanted reverberation and the sound coverage achieved varies by less than 2 dB throughout the listening areas.

A similar approach has been adopted in Chelmsford Cathedral.

# EXPERIMENTAL ELECTRONICS

By  
R. J. Caborn

## Tips for the venturesome

Many constructors obtain their pleasure in the successful assembly of projects, following the instructions which are given in this magazine. A growing number like to design their own projects as well, using their knowledge to work out the project circuits, checking out the circuits experimentally and, when a circuit has been proven in practice, assembling it in its final permanent form. The intermediate experimental stage is almost mandatory for all but the simplest circuits; a circuit diagram may look great in theory but there are many pitfalls between that theory and actual practical working. In the theoretical circuit a transistor may be biased incorrectly, there may be a hidden positive feedback route which will cause instability, component values may not be at their optimum and some could even be downright wrong. The list of possible snags which can beset a seemingly perfect theoretical circuit is a long and sorry one.

So the experimental electronic hobbyist (and, incidentally, the professional engineer) carries out the following procedure. First, he works out the initial circuit of the project; second, he checks it out in a quick experimental test mock-up; third, he builds it in its properly constructed permanent form.

### EXPERIMENTAL APPROACH

Here are some hints gleaned from those who test new circuits, either professionally or as a hobby.


First, choose the method of experimental assembly. There are two basic approaches here: either use a breadboard having rows of holes with internal contact springs, or use tagboards, tagstrips or other forms of terminal, and solder all connections. With the breadboard most (but not all) soldering processes are eliminated, whilst the second approach means soldering all the way. Assembly with breadboards is 2-dimensional, whilst with all-soldering it is 3-dimensional. Veteran experimenters can solder up test circuits very quickly. Provided you don't cut the

leads too short, resistors and capacitors can be used over and over in all-soldered hook-ups, just as they can be used over and over again in breadboard layouts.

What are the essentials for experimental working? The first and most obvious is a multimeter. You **have** to know what voltages and currents exist in the experimental hook-up. In many cases we don't insert a meter into circuit to measure current. If the current flows through a known resistance it is usually much quicker to measure the voltage across the resistance and deduce the current from Ohm's Law. With electronics we nearly always have to think in terms of milliamps and microamps. 9 volts across  $1k\Omega$  means a current of 9mA; 9 volts across  $1M\Omega$  indicates a current of  $9\mu A$ .

Not essential but very, very useful are crocodile clip leads. The best clips to use are the miniature ones with a clip length of about 35mm. and a flexible vinyl sleeve, as are retailed by Maplin Electronic Supplies and others. Make up some ten of these leads with varying lengths, as in Fig. 1(a). If you are going in for breadboard have half a dozen of the leads with one end of the wire tinned to form a single strand which will plug into one of the breadboard holes. See Fig. 1(b). (Never push stranded wire into breadboard holes; there is too great a risk of the strands separating, whereupon they can upset the spring contact action and cause short-circuits.)


It is best to draw your initial circuit on a large (8 by 10in. or more) notepad or sheet of paper. Use both a blue and a red ball-point pen. The initial circuit is drawn in blue. If it is amended during the experiments, scribble over the unwanted circuit section with red and then draw in the new section in blue. The final, tested, circuit will then be all-blue. Unless you're very familiar with the transistors and other multi-lead devices you are using, draw their pin layouts on the same paper as the initial circuit.

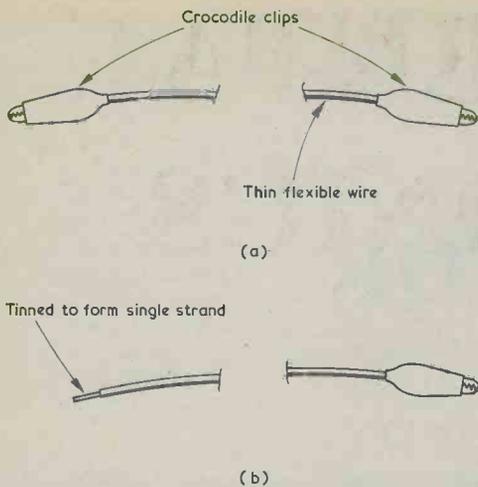

**Fig. 1(a).** Very useful for experimental work are crocodile clip leads. A range can be made up with wire lengths varying from some 4 to 7in.  
**(b).** One end of the lead can be tinned to form a single strand which can be inserted in a breadboard hole.

### FINDING RESISTANCE VALUES

Some component values may have to be finalised in the experimental mock-up. The base bias resistor required in Fig. 2(a) to make the transistor collector sit at exactly half-supply voltage may not be known. One simple way of finding the required value is to use two of the crocodile clip leads to connect to a potentiometer, and adjust this for the required collector voltage, as in Fig. 2(b). The potentiometer is then removed, its resistance measured, and a fixed resistor of that value inserted in the circuit. The collector load in our example is  $1k\Omega$ , and a suitable potentiometer value would be  $470k\Omega$  linear. A word of caution here: always start with the potentiometer inserting maximum resistance and then reduce that resistance

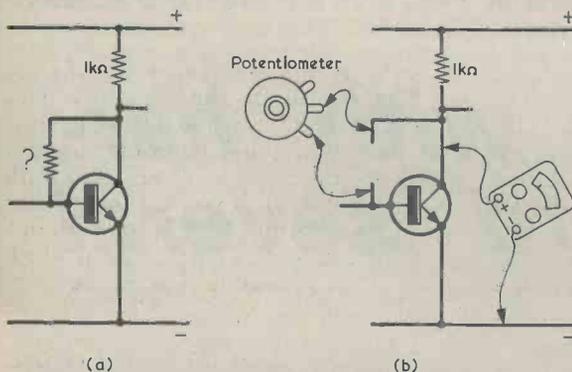

**Fig. 2(a).** In an experimental circuit the bias resistor, whose value is unknown, is required to have a value which causes the transistor collector to be at mid-supply potential.  
**(b).** The collector voltage is monitored by a testmeter switched to a volts range, and a potentiometer is coupled into the circuit by two crocodile clip leads. The potentiometer is adjusted for the required collector voltage.

**TABLE**  
**Maximum permitted potentiometer track currents (mA)**

Resistance	0.25W	0.5W	1W
100Ω	50	70	100
220kΩ	33	47	67
470kΩ	23	32	46
1kΩ	15	22	31
2.2kΩ	10	15	21
4.7kΩ	7.0	10	14
10kΩ	5.0	7.0	10
22kΩ	3.3	4.7	6.7
47kΩ	2.3	3.2	4.6
100kΩ	1.5	2.2	3.1
220kΩ	1.0	1.5	2.1
470kΩ	0.72	1.0	1.4
1MΩ	0.50	0.70	1.0

slowly. If the potentiometer inserts too low a resistance an excessive current can flow in its track and it will be damaged. Remember that a potentiometer wattage rating applies to its whole track. The accompanying Table shows maximum permitted track currents for potentiometers of different values and wattage ratings.

A pocket calculator can be very useful, and this can be an inexpensive model with the four arithmetic functions, a reciprocal function ( $1/x$ ), a square function ( $x^2$ ) and a square root function ( $\sqrt{x}$ ). We tend to get into the habit of using calculators for solving ridiculously simple problems, but this is not all bad as it gets us calculator-oriented for the more complicated ones. Tastes vary, but a good choice is a calculator with a nice bright l.e.d. display and rechargeable facilities, i.e. a socket in the side into which the mains "adaptor" for the calculator can be plugged. L.E.D. display calculators burn up a lot of current but this is no problem when their batteries can be readily recharged from the mains.

Whether the breadboard or all-soldering approach is used, the resulting experimental assembly will almost certainly look untidy, to say the least. This doesn't matter if it proves the circuit. Longish leads are not normally liable to cause trouble in a.f. or logic circuits but it pays to keep wiring to op-amp non-inverting inputs short and to keep compensating and bypass capacitors close to op-amps, voltage regulators and other i.c.'s.

Even with an experimental circuit there can be hidden snags. You may get a circuit to work fine when it's supplied by a mains power supply, after which it does horrible things when connected to a battery of the same voltage. Reason? The power supply had a fat electrolytic across its output terminals which acted as a supply bypass for the experimental circuit!

There are, of course, many other aspects to be considered when undertaking experimental electronic work, but those which have been covered in this short article make up the basic essentials. There's a lot of fun to be had with experimenting and, once you catch the bug, you'll find yourself learning all the way as you advance in this fascinating branch of electronics. ■

# DOUBLE OUTPUT TEST OSCILLATOR

By  
R. A. Penfold




The test oscillator can be housed in any small plastic case which can accommodate the components

***1kHz output with harmonics up to several MHz.***

***Peaked i.f. output at 470kHz.***

***Ideal for signal tracing.***

**Fig. 1** The circuit of the test oscillator. Despite its simplicity this produces an a.f. output with modulated harmonics up to several MHz as well as a modulated i.f. signal peaked at 470kHz

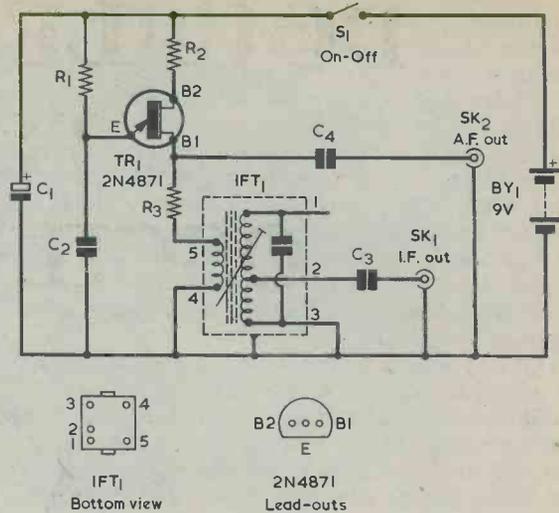

This very inexpensive item of test equipment can be very useful when troubleshooting audio or radio equipment. It can be used as a wide band signal injector providing an audio tone which is rich in harmonics up to frequencies of a few MHz. It is therefore suitable for checking the r.f. and i.f. stages of a.m. radios as well as audio equipment. It also has an i.f. output at the normal a.m. intermediate frequency of 470 kHz and can be used as an i.f. alignment oscillator for newly constructed a.m. radios or for commercially made radios having this intermediate frequency.

The circuit is very simple and employs only one active device (a unijunction transistor) together with a few passive components. Power is obtained from an internal 9 volt battery, and running costs are low since the current drain is only about 1.5mA.

### THE CIRCUIT

In the circuit diagram of Fig. 1, TR1 is the unijunction transistor. This functions in the following manner. At switch-on, capacitor C2 is discharged, and it begins to charge via R1. The transistor presents a resistance between its base 2 and base 1 which allows a small current to flow in R2 and R3. (The winding of IFT1 between R3 and the negative rail has a low resistance, and has little effect on oscillator operation.) When the voltage across the capacitor reaches the triggering level for the transistor a regenerative effect takes place which causes a very low impedance to be given between the emitter and the base 1. The capacitor rapidly discharges into R3. It then commences to charge again via R1 and the voltage across it increases until it once more reaches triggering level and discharges into R3. The circuit continues to oscillate in this manner and causes the appearance of positive-going spikes at the base 1 of the transistor. These spikes are coupled to the a.f. output via C4.

The component values in the circuit cause the spikes to have a fundamental frequency of about 1kHz, although this may vary slightly with different unijunction transistors. The a.f. output is very rich in harmonics and produces signals, spaced at the 1kHz fundamental frequency, up to several MHz. If these signals are applied to an a.m. detector, the fundamental frequency is given in the detector output. Thus, the a.f. output can be used for r.f. and i.f. signal injection as well as for audio checking.

## COMPONENTS

### Resistors

(All  $\frac{1}{4}$  watt 5%)

R1	33k $\Omega$
R2	120 $\Omega$
R3	100 $\Omega$

### Capacitors

C1	10 $\mu$ F electrolytic, 10V. Wkg.
C2	0.022 $\mu$ F type C280
C3	47pF ceramic plate
C4	0.1 $\mu$ F type C280

### Inductor

IFT1	i.f. transformer type IFT13-470kHz (Denco)
------	--

### Semiconductor

TR1	2N4871
-----	--------

### Switch

S1	s.p.s.t. sub-miniature toggle
----	-------------------------------

### Sockets

SK1	3.5mm jack socket
SK2	3.5mm jack socket

### Battery

BY1	9-volt battery type PP3
-----	-------------------------

### Miscellaneous

Plastic case (see text)  
 Veroboard, 0.15 in. matrix  
 Veropins, single ended, for 0.15in. Veroboard  
 Battery connector  
 Test prod  
 Crocodile clip  
 3.5mm jack plug  
 Nuts, bolts, wire, etc.

Although the winding of IFT1 between R3 and the negative rail has little effect on oscillator operation it still allows the current spikes at 1kHz to be coupled into the second winding, which is tuned to 470kHz by the parallel capacitor. This capacitor is an integral part of the i.f. transformer and the tuned circuit filters out the fundamental and harmonics other than those which are at or very close to its resonant frequency. An output is taken from a tap in the tuned winding, to ensure that there is little loading on the resonant circuit, and is coupled to the i.f. output socket via C3. This output can be used for i.f. alignment purposes.

There is only one control in the circuit, this being the on-off switch, S1.

If difficulty is experienced in obtaining the component specified for IFT1, it may be purchased direct from the maker at Denco (Clacton) Limited, 357/9 Old Road, Clacton-on Sea, Essex, CO15 3RH.

### ASSEMBLY

Any small plastic case capable of taking the parts may be used to house the oscillator, and that employed by the author had approximate dimensions of 118 by 84 by 38mm. Switch S1 is mounted centrally on the lid, which now becomes the front panel, with SK2 mounted on its left and SK1 on its right. The two sockets are positioned symmetrically on each side of the switch.

Apart from the battery, the remaining components are assembled on a Veroboard of 0.15in. matrix having 11 copper strips by 9 holes. This has to be cut out from a larger board by means of a small hacksaw. The single break in the strips and the two 6BA clear holes are then made at the points indicated in Fig. 2, which shows the component and copper sides.

The first item to be soldered in place is IFT1. This is not mounted directly in the Veroboard holes but has its tags soldered to single-ended Veropins which are first soldered in at holes C6, B4, A5 and A6. Tags 5, 2, 3 and 4, and the can mounting lug between tags 3 and 4 are then generously tinned with solder, after which it will be found they can be easily soldered to the Veropin heads. Note that no connections are




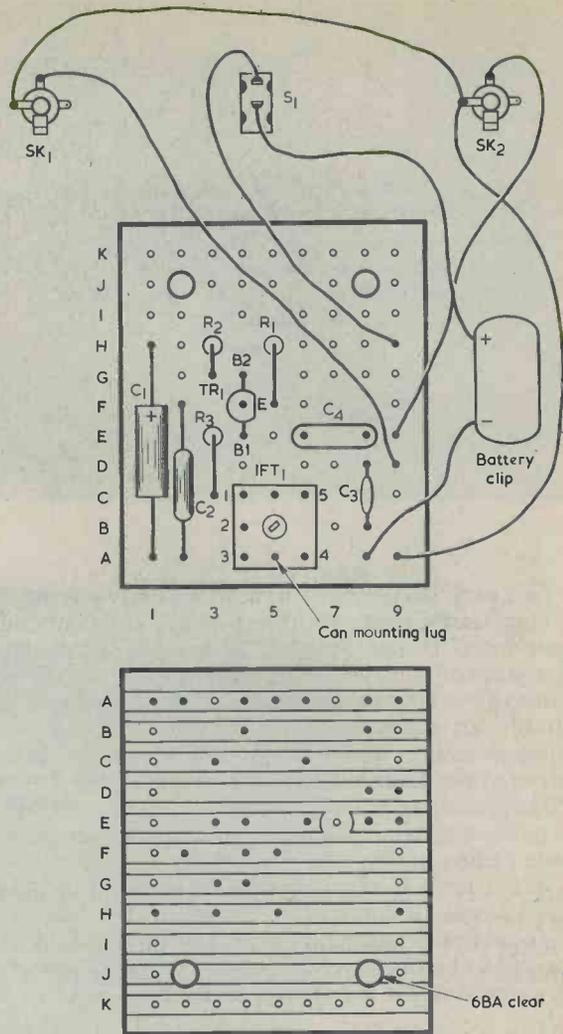


Fig. 2. The wiring on and around the Veroboard. IFT1 is soldered in place first, using a procedure which is described in the text

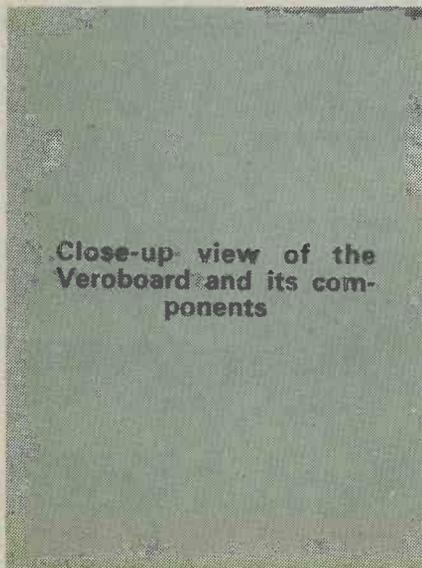

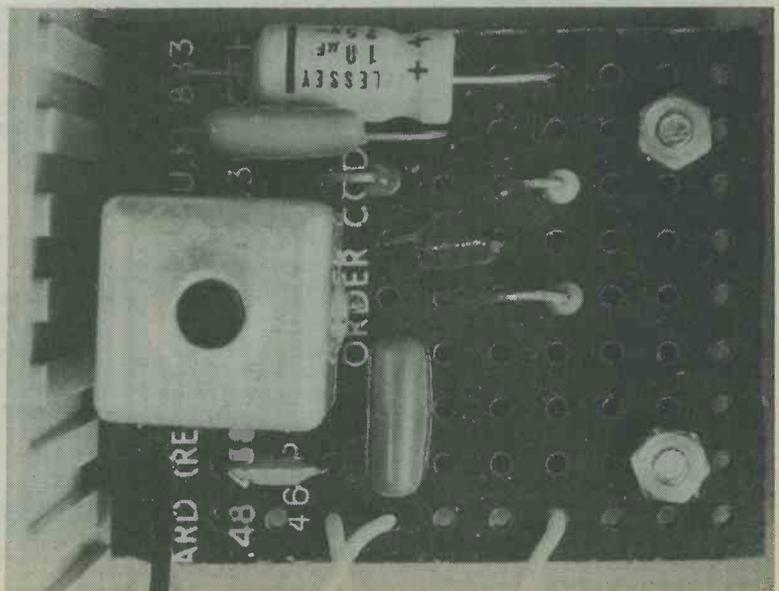Close-up view of the Veroboard and its components



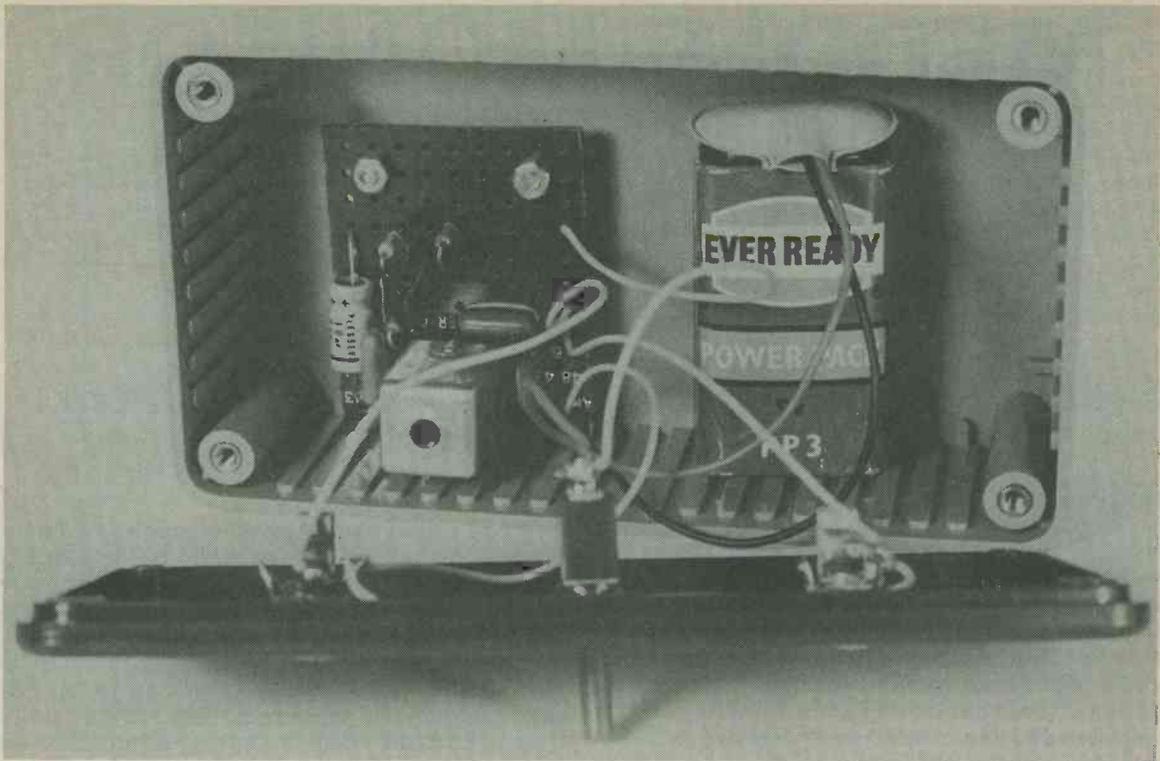

The Veroboard assembly is secured to the rear panel at the left, with the battery to the right

made to tag 1 and the remaining can mounting lug of the component.

After IFT1 has been soldered into circuit the remaining components are mounted and soldered to the board. So also are the leads which connect to S1, the two sockets and the battery clip. All wiring external to the board is shown in Fig. 2.

The board is secured to the left hand side of the rear panel, as indicated in the photograph of the interior, using two 6BA bolts and nuts with spacing washers. There should be adequate clearance with the backs of the sockets and on-off switch when the front panel is screwed in place. The 9 volt battery is positioned to the right of the board and it can be held in place by a home-made clamp or, more simply, by a piece of plastic foam sandwiched between the front panel and the battery.

### USING THE OSCILLATOR

When completed the oscillator is ready for use. If suitable test gear is available, IFT1 can if desired be peaked up to 470kHz, whereupon it is essential that a proper trimming tool (such as the Denco TT5) be used. The core can easily break if an attempt is made

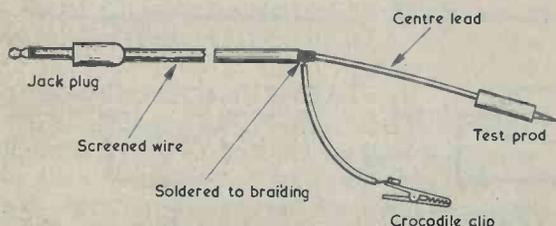


Fig. 3. Making up the test lead. This is plugged into SK1 or SK2 according to the function required

to adjust it with an incorrect tool such as a small screwdriver. However, no adjustment is really necessary because the transformer is pre-aligned at the factory and will provide an output frequency of adequate accuracy.

A short screened test lead is required and this can consist of flexible audio cable connected to a 3.5mm jack plug. At the other end the braiding is connected to a wire terminated in a crocodile clip and the centre conductor to a test prod, as shown in Fig. 3.

For a.m. receiver i.f. alignment purposes the test prod can be applied to the collector of the mixer transistor and the i.f. transformers can then be adjusted, working backwards from the last i.f. transformer. In this case there should be no necessity to connect the test clip to the receiver chassis, and sufficient signal will be given simply by connecting the test prod on its own. For this purpose the test lead is plugged into SK1.

For signal injection purposes with an a.m. receiver the test lead is plugged into SK2, and it will be necessary to connect the test clip to the receiver chassis. The test prod is then first applied to the non-earthly tag of the speaker, and this should produce a low volume tone from the speaker if this is functioning. (Try out the oscillator initially with one or more serviceable speakers to gain an idea of the performance to be expected here.) The prod is next applied to the output transistor bases, the driver transistor base, the base of the a.f. amplifier input stage, the i.f. amplifier bases and so on, working back towards the mixer base. The approximate location of the fault is found when the audio tone fails to be produced by the speaker, and it lies either in the immediate circuitry at the last test point, or between that test point and the previous one. The same working-back technique can be used when fault-finding on audio equipment. ■

# MEDDLE MONITOR

By

F. Bowden

## Security device incorporates AND gate latch.

We have become used, over recent years, to CMOS latches employing two inverters. A typical instance is given in Fig. 1(a), where two 2-input NAND gates are connected as inverters. If the input of the latch is taken momentarily to the positive rail the output goes positive as well, whereupon it holds the input positive via resistor R when the temporary connection is removed. The circuit remains latched in this condition. Should the input be momentarily connected to the negative rail the output goes negative and the circuit latches in this alternative state.

The resistor between input and output limits the current drawn from the output of the second gate during a transition and, in most practical applications, may have a value lying between some 10 k $\Omega$  and 1M $\Omega$ . Two 2-input NOR gates could be employed instead of the two NAND gates shown.

### AND GATE

AND gates can also be employed as latches. In Fig. 1(b) a 2-input AND gate is used in a latch circuit having the same performance as the latch of Fig. 1(a). When the input goes positive, so also does the output, and when the input goes negative the output similarly becomes negative. Again, the circuit can latch into either of these two stable states.

The fact that a single AND gate carries out the same function as two NAND gates or two NOR gates can represent an advantage in some circuit applications. A particularly useful i.c. here is the 4081 quad 2-input AND gate which contains four gates. This is a readily available and inexpensive i.c., and has the internal circuitry shown in Fig. 2.

To give an idea of the manner in which AND gates may be employed, the remainder of this article is devoted to the security device indicated by its title.

### SWITCHING MONITOR

When prized mains-driven equipment is left unattended for relatively long periods the owner frequently wishes to assure himself that it has not been switched on and meddled with during his absences. A similar situation can arise with unoccupied premises, and it is comforting if a check can be made to ascertain whether an intruder has switched on any electrical equipment or appliances. The security device is connected to the mains circuitry to be monitored after its on-off switch, and will indicate at any later time whether or not that switch has been closed.

The circuit of the monitor appears in Fig. 3. Here, the latching gate is the gate associated with pins 1, 2 and 3 of IC1, which is a 4081. The 240 volt primary of transformer T1 is connected to the mains circuit being monitored, and it has a 6 volt secondary. To set up the monitor, S3 is closed to switch on the 9 volt supply with the 240 volt a.c. mains connected to T1 primary switched off. The "Reset" button, S1, is then pressed to ensure that the input and output of the latching gate are negative.

If at any subsequent time the 240 volt a.c. mains is switched on, even if momentarily only, the voltage across T1 secondary is applied to TR1 base via R1, causing TR1 to turn on for part of the alternate a.c. half-cycles when the lower end of T1 secondary is negative. The upper end of R2 is then taken positive and causes the AND gate latch input and output to go positive also. The gate latches in this state during the periods when TR1 is non-conductive because current from the gate input to R2 is blocked by D1. Thus, a momentary, or continuous, application of the a.c. mains to T1 primary causes the gate input and output to go positive and stay positive. The function of C1 is to prevent possible switching transients in the mains

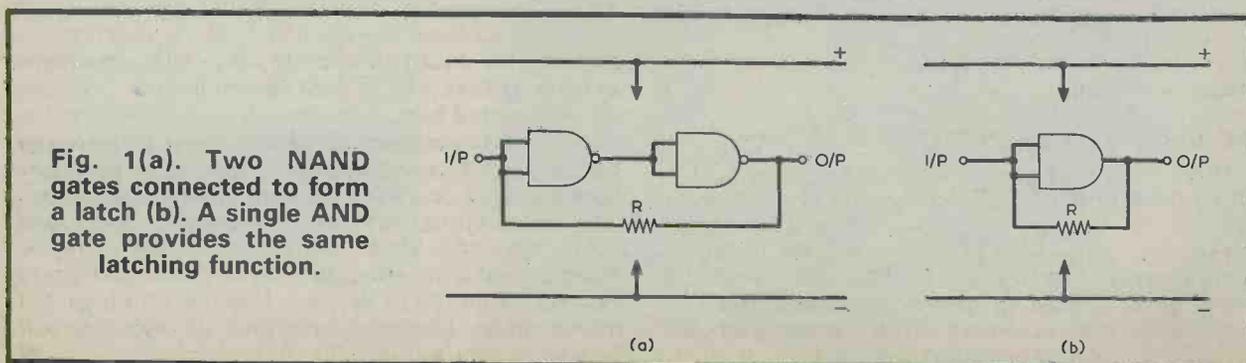


Fig. 1(a). Two NAND gates connected to form a latch (b). A single AND gate provides the same latching function.



# AMATEUR RADIO SATELLITES

Report by Arthur C. Gee

Readers will know from the note in 'News and Comment' June 1980 issue, that the satellite Oscar 9 was lost at launching; the only failure in ten years of amateur orbiting satellites.

Hopes were expressed then, that it might be possible to build a replacement and find a launching opportunity in the not too distant future. Doubts were also expressed that, due to the heavy expenditure of time and money that would be involved in creating a replacement, it might not be possible.

It is pleasing to report that the West German Amateur Radio Satellite Construction Group, led by Dr. Karl Meinzer who in conjunction with Jan King of Amsat was responsible for much of the construction and design of Oscar 9, have been negotiating with the European Space Agency for a further launch facility. As a result it is reported that such an opportunity may be available early in 1982. If this opportunity is to be taken up much work has to be done and a very large sum of money raised. It has been estimated that approximately £80,000 will be required, and it is hoped that half of the amount required will be raised in Europe.

AMSAT-UK has undertaken to spearhead the drive for this fund raising effort, and readers who would like to contribute should contact the AMSAT-UK

---

**OSCAR 9, before its completion, being wired up by Marie Marr, AMSAT'S Aerospace Technician. The replacement will be almost identical to that shown with just a few modifications resulting from the experience gained during the construction of the first model.**

Secretary, Ron Broadbent, 94 Herongate Road, Wanstead Park, London E12 5EQ.

The failure of the Ariane LO2 launched on 23rd May last, was due to combustion instability which occurred in one of the four first stage engines about six seconds after ignition.

This extremely violent phenomenon which lasted only three tenths of a second, abruptly altered the characteristics of the injector, which promptly led to the destruction of that engine. The fire that then broke out in the propulsion bay caused the vehicle to be destroyed 108 seconds after take off.

As can be imagined, much meticulous work was needed to narrow down the range of possible causes of the failure and to reproduce on the test-stand the behaviour of the faulty engine. This involved analysing the telemetry recordings, inspecting the damaged rocket recovered from the sea, static firings of the engines, acoustic simulation and an investigation of manufacturing and inspection processes.

In particular, it has been proved that the cause of the engine failure could not have been external to the engine itself, and the hypothesis of the presence at ignition of a foreign body, e.g. an identification tag or metal filings, has been eliminated.

The conclusion was reached that the combustion instability of the engine was caused by a combination of factors in the system for injecting fuel into the combustion chamber. These most probably resulted from slight variations in the manufacture of successive units, such that very small variations in geometrical characteristics resulted in sufficient variations in the engines to cause failure.


The engine injectors are extremely complex, some 1000 injection orifices are provided in order to deliver 250 Kgs of fuel and oxidant per second into the combustion chamber.

In order to solve the problem, it has been decided to adjust the manufacturing tolerances for the injectors and to select those actually used by means of static firings on the engine test stand. Provided that the test schedules from now until the end of the year are satisfactory, this programme should enable Ariane LO3 to be equipped with injectors thus selected, in time for a launch in the second fortnight of March 1982.



# SHORT WAVE NEWS

## FOR DX LISTENERS

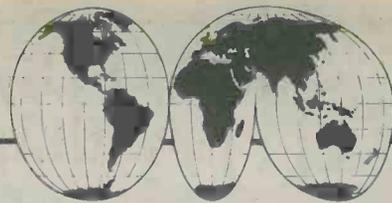

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

A lot to report this month, so without more ado – and less verbiage – your attention is drawn to the following loggings, presented here for guidance. Select your item and ‘have a go’.

### ●INDONESIA

RRI (Radio Republik Indonesia) Jakarta on a measured **11791.2** at 1430, OM (OM = male announcer) with station identification in English after a musical interlude in the English programme for South East Asia and the Pacific, scheduled from 1400 to 1500.

RRI Yogyakarta on **5046** at 1514, OM in Indonesian, orchestral music slow and rhythmic in the local style. This one operates from 0100 to 0300, 0455 to 0800 and from 0955 to 1700. The power is 5kW.

RRI Padang on a measured **4002** at 1536, YL’s (YL = Young Lady - female) with a soft lilting song and guitar-type music. The schedule here is from 2230 to 0100 and from 1000 to 1600. The power is 10kW.

RRI Bukittinggi on a measured **4827** at 1525, OM with a song in Indonesian, local-type music. The schedule is from 2300 to 0300, 0500 to 0715 and from 0930 to 1600. The power is just 1kW.

### ●BURMA

BBS Rangoon on **4725** at 1524, YL with a talk – presumably in Burmese. Rangoon is scheduled on this channel from 1030 to 1545 but the signing-off time can vary from as early as 1445. The power is 50kW.

### MALAYSIA

Kuala Lumpur on **4845** at 1520, OM and YL in Malay at termination of transmission. National Anthem and off at 1532. The schedule is from 2130 to 0130 and from 0545 to 1530 Mondays to Fridays; Saturdays from 2130 to 0330 and from 0545 to 1530; Sundays from 2130 to 1530. The power is 50kW and the programme languages are Indian.

Kuching, Sarawak, on **4950** at 1533, plaintive tune on a local wind instrument, weird and wailing! Fair signal under a running teletype transmitter. The schedule is from 2200 to 0100 and from 0800 to 1600. The power is 10kW.

### ●NEPAL

Jawalakhal on **5005** at 1520, OM in Nepalese, OM song, music in Indian-style. This is the Home Service radiated from 0020 to 0350; from 0720 to 0950 and from 1150 to 1720. The power is 100kW. This one can also be logged in parallel on **3425**.

### ●CHINA

Wuhan, Hubei, on **3940** at 2214, OM and YL in Chinese, logged under severe CW (Morse) interference. The schedule is from 2100 to 0100; from 0300 to 0740 and from 0855 to 1605.

Xizang, Tibet, on **4750** at 0046, OM AND YL alternate in Chinese. This one is scheduled from 2230 to 0645 (March to September from 2300) and from 1000 to 1545. Ensure you are listening to this one by tuning to the channel after 0000 for the reason that Hailaer, Heilongjiang is on this frequency from 2120 to 2400; also from 0355 to 0600 and from 0925 to 1500.

Wulumqi, Xinjiang, on **5060** at 0058, Chinese classical music, 5 pips time-check at 0100, OM station identification in Mongolian. Wulumqi is on the air from 2330 (from February to September from 0000) to 0555 and from 1100 to 1625.

Kumming, Yunnan, on **4760** at 2348, OM with a talk in Chinese. This is Yunnan 1, on the air from 2150 to 0600 (Tuesdays until 0800) and from 0920 to 1600.

Xizang, Tibet, on **4035** at 2342, Chinese classical music then YL with songs in the Tibetan Service, scheduled here from 2230 to 0645 and from 1000 to 1545.

Xining, Qinghai, on **3950** at 0003, OM with a talk in Chinese. Xining is scheduled from 2150 to 0100 and from 0930 to 1525.

### ●ITALY

Rome on **7275** at 1950, YL and OM announcers with the programme in English for the U.K., scheduled on this channel from 1935 to 1955.

### ●NIGERIA

Lagos on **15120** at 0651, OM with a newscast in English, all about local affairs in a programme directed to North Africa and “Overseas”, scheduled from 0600 to 0800.

## ● MALTA

Radio Mediterranean on 5960 at 1840, YL with a newscast in English, followed by station identification in English.

## ● AUSTRALIA

Melbourne on 17890 at 0112, OM with a talk in English about foreign affairs as represented in the Australian press in a programme entitled 'Editorial Opinion'.

## ● TAIWAN

CBS Taipei on 11905 at 1410, YL with songs in Chinese, light music local-style in a broadcast presumably for South East Asia.

## ● SINGAPORE

BBC Kranji on 11955 at 1615, OM with comments on USSR domestic affairs followed by a reading from 'The Invisible Man' by H. G. Wells.

## ● NEW ZEALAND

Wellington on 15485 at 0700, 6 pips time-check, station identification in English after a programme of soft-sounding Polynesian melodies from 0655 tune-in.

## ● MALAYSIA - 2

Kuala Lumpur on 15295 at 0713, OM with station identification, frequencies and times announcement in English.

## ● NEW CALEDONIA

Radio Noumea on 11710 at 0732, choral song to a Polynesian drum-beat, OM with announcements in French. A weak signal but audible on a clear channel.

## ● PHILIPPINES

Tinang (VOA) on 11965 at 1350, OM and YL with an English language lesson in a programme intended for China.

## ● CLANDESTINE

Voice of the Malayan Revolution on 15789 at 1403, military music, OM with a harangue in (presumably) Tamil. This station follows a pro-Peking line and is anti-Malaysia and Singapore Governments. The transmitter is thought to be located near Changsha in the Hunan Province of China.

## ● ECUADOR

HCJB Quito on 9535 at 0300, YL with station identification followed by a programme in Russian for Europe, scheduled from 0230 to 0400.

## ● MONGOLIA

Ulan Bator on 4830 at 2355, OM and YL in Mongolian followed by a programme of folk music. Also logged on the parallel channel of 4763 at 2210 on a differing occasion, OM in Mongolian. This is the Home Service, scheduled from 2200 to 0100 and from 1030 to 1500.

## ● UGANDA

Soroti on a measured 5026.5 at 0331. OM with news of African affairs in Swahili in the National Programme scheduled from 1300 to 2100 weekdays and from 0300 to 0545 and from 1400 to 2100 on Saturdays and Sundays. The power is 250kW.

## ● TANZANIA

Dar-es-Salaam on 5050 at 0325, African drums interval signal, OM with announcements in Swahili at 0330 when opening transmission. The schedule is from 0300 to 0700 and from 1500 to 2015 weekdays. Presumably they commence later on Sundays! The power is 10kW.

## ● SWAZILAND

TWR (Trans-World Radio) Mpangela on 4790 at 0319, YL's with an African song in the Afrikaans programme, radiated at this time of the year from 0300 to 0345. The power is 30kW.

## ● INDIA

AIR (All India Radio) Bombay on 4840 at 1549, OM in Hindi in the Domestic programme, scheduled on this channel from 0230 to 0400 and from 1230 to 1740. The power is 10kW.

AIR Delhi on 3925 at 1541, OM with a newscast in English in the Home Service, scheduled from 1300 to 1600 and from 1730 to 1740 (Tuesdays, Saturdays and Sundays continuous until 1735). The English newscasts are as follows - from 0030 to 0035; 1430 to 1435; 1530 to 1545 and from 1730 to 1735. The power is 10kW.

## ● CAPE VERDE

Voz de Sao Vicente on a measured 3931 at 2359, OM with announcements in Portuguese, the National Anthem and sign-off. This station is on the air irregularly and when transmitting is scheduled from 2000 to 2400 (Saturdays from 1630, Sundays from 1600). The power is 10kW.

## ● NAMIBIA

Windhoek on 4965 at 1721, OM in vernacular. The schedule is from 1515 to 0615. Power unknown.

## ● ANGOLA

Luanda on 4820 at 1815, OM with a long harangue in vernacular (not Portuguese) all about Angola and UNITA. The schedule is from 0430 to 0630 and from 1500 to 2400. The power is 10kW.

## ● SAO TOME

Radio Nacional de Sao Tome on a measured 4807 at 1755, choral songs then OM with announcements in Portuguese. The schedule is from 0530 to 2300 and the power is 10kW.

## ● AFGHANISTAN

Kabul on 4740 at 0138, OM with announcements in Pashto, 3 long pips at 0130 then OM with religious chants, all in the Home Service 1, scheduled from 0125 to 0330 and from 1340 to 1920. The power is unknown.

## ● COLOMBIA

Radio Super, Medellin, on 4875 at 0509, OM with a newscast in Spanish with many mentions of Colombian place-names. Full station identification as "Radio Super" at 0517. The schedule is around the clock and the power is 2kW.

Radio Neiva, Neiva, on 4855 at 0456, OM with announcements in Spanish then the National Anthem and off. Radio Neiva operates irregularly and is reported to be on the air at times from 2300 to 0530 and the power is 1 kW.


# RADIO & ELECTRONICS

FEBRUARY 1981

# CONSTRUCTOR

## IN NEXT MONTH'S ISSUE

### REVERBERATION UNIT

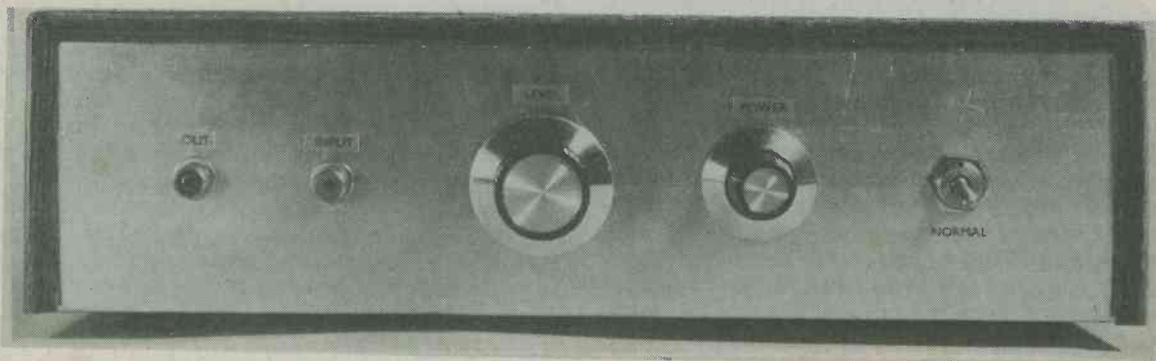

- ★ SELF-CONTAINED SELF-POWERED UNIT
- ★ REVERBERATION AMPLITUDE CONTROL
- ★ SWITCHING OPTION FOR REVERBERATION ONLY. The unit is powered by a PP6 size 9 volt battery.

### ELECTRONIC DOOR BUZZER

LOW CONSUMPTION UNIT PRODUCES DISTINCTIVE TWO-NOTE TONE.

### “OWIZZEE”

HOW TO PLAY CRICKET IN COMFORT

## PLUS MANY OTHER ARTICLES

# FUZZ BOX

## Silicon diode clipping action.

### Very low noise level.

### Variable

Although it has been in use for many years now the "fuzz" musical effect is still one of the most popular. It is primarily employed with electric guitars (although of course it can be used with electronic organs and other instruments) and consists of distorting the processes signal to produce strong harmonics of the signal frequency. These harmonics are multiples of the input frequency, so that a 500Hz signal would have added to it signals at 1kHz, 1.5kHz, 2kHz and so on. Thus, the output signal tends to have a much higher treble content than the input signal, giving a "sharper" and more "brilliant" sound than would otherwise be obtained.

#### CLIPPING

There are several ways in which the fuzz effect can be given, but by far the most common method is to use a clipping circuit. With this type of circuit a sine wave input, as in Fig. 1(a), is greatly amplified and then fed to a diode clipping circuit which, if silicon diodes are used, limits the maximum peak signal level to plus and minus 0.6 volt. Since the input signal would normally have a peak-to-peak amplitude of several volts, the clipping considerably flattens the signal peaks, so that the sine wave of Fig. 1(a) would be changed to the near square wave of Fig. 1(b). A square wave signal is rich in harmonics, and the fuzz effect is thereby given.

When used with a guitar the clipping circuit can also produce a "sustain" effect. The output from the guitar initially has a high amplitude which rapidly decays. When there is a high level of amplification before the clipping diodes the decaying signal can still reach clipping level, so that the clipped output is maintained at full amplitude for several seconds.

Although a fuzz unit can sustain a note, it has the obvious disadvantage of producing distortion products as well. This problem can be overcome to some extent by using a low pass filter at the output, thereby giving the signal a more rounded waveform. The filter can give quite good results, but it will not greatly reduce intermodulation distortion products as many of these occur at middle and low audio frequencies. In practice dissonant results are much less noticeable if only one note is played at a time.

The fuzz box described here is designed to connect between an electric guitar and a guitar amplifier, and by employing a low noise bifet operational amplifier it has an excellent signal-to-noise ratio. An adjustable low pass filter is included at the output so that the fuzz effect can be varied to suit individual tastes. The unit is self-contained, being powered by its own PP3 9 volt battery. This will give many hours of operation before a replacement is required, as the circuit has a current consumption of only about 3mA.

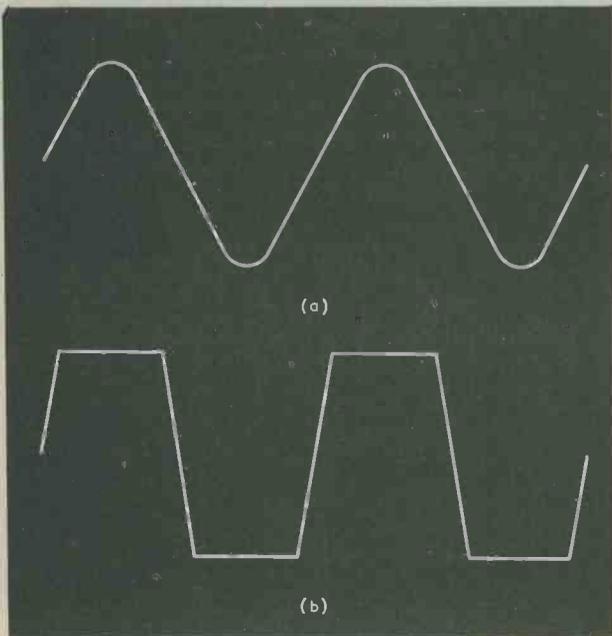


Fig. 1(a). The input waveform before clipping  
(b). After amplification and clipping, the waveform is converted to a nearly square wave.

By  
I. M. Attrill



The completed fuzz unit in its aluminium case. The successional action foot operated switch on the top panel switches the fuzz effect in and out.

### THE CIRCUIT

The full circuit of the fuzz box is shown in Fig. 2. IC1 is a Texas Instruments operational amplifier which is designed to give minimal audio frequency noise at its output. The i.c. also has an excellent distortion performance, although this is obviously of no great importance in the present application!

The non-inverting input of the i.c. is biased to half the supply voltage by R2 and R3, and the input signal passes through C2 and R1 to the inverting input. R4 and R1 form a standard negative feedback circuit and allow the i.c. to have a voltage gain, for very low level signals, equal to R4 divided by R1, or approximately 47 times. If, however, an input signal causes the peak i.c. output to exceed 0.6 volt the two diodes commence to conduct. Their forward resistance is very much lower than the resistance of R4, with the result that the amplifier gain is considerably reduced.

As signal amplitude increases a point is reached where the diodes cause the amplifier to have a gain which is less than unity. This gives the desired clipping effect, with the amplifier output being limited to about 1.2 volts peak-to-peak.

The low pass filter is given by R5, C3 and VR1. The filter has no significant effect when VR1 inserts maximum resistance into circuit and gives its full high frequency cut when VR1 inserts minimum resistance. VR1 can be set up to give the level of filtering which is desired. R6 and R7 form an output attenuator, and the output signal level can be adjusted by means of R7. This potentiometer is set up so that the output levels with or without fuzz are comparable, whereupon the switching in or out of the fuzz effect can be reasonably unobtrusive. This switching is achieved by S1(a)(b), which is a successional action push-button switch intended for foot

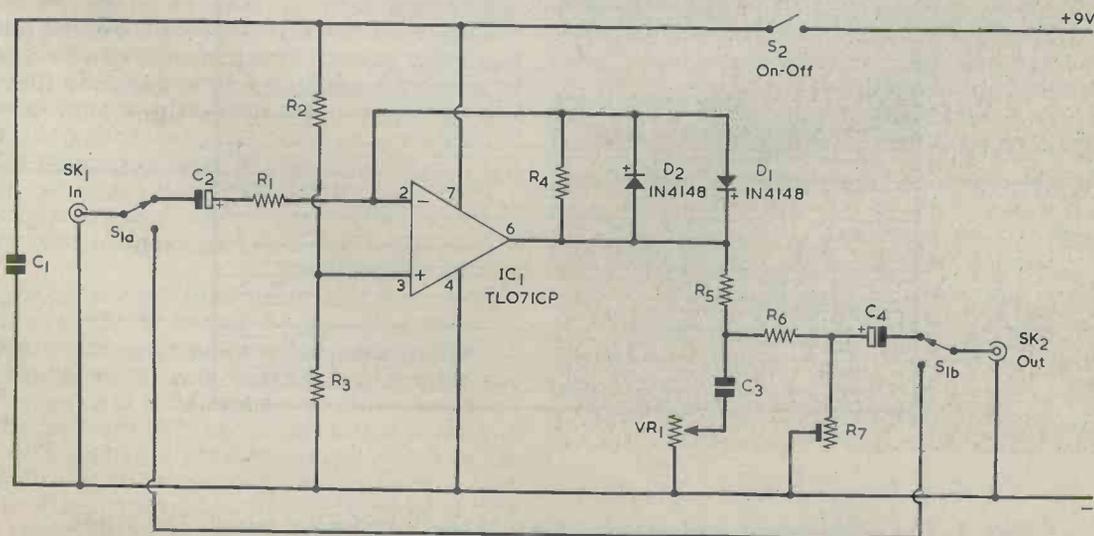


Fig. 2. The circuit of the fuzz box. Clipping is achieved by the two diodes in the feedback loop around IC1.

The Veroboard assembly is mounted on one of the side panels of the case

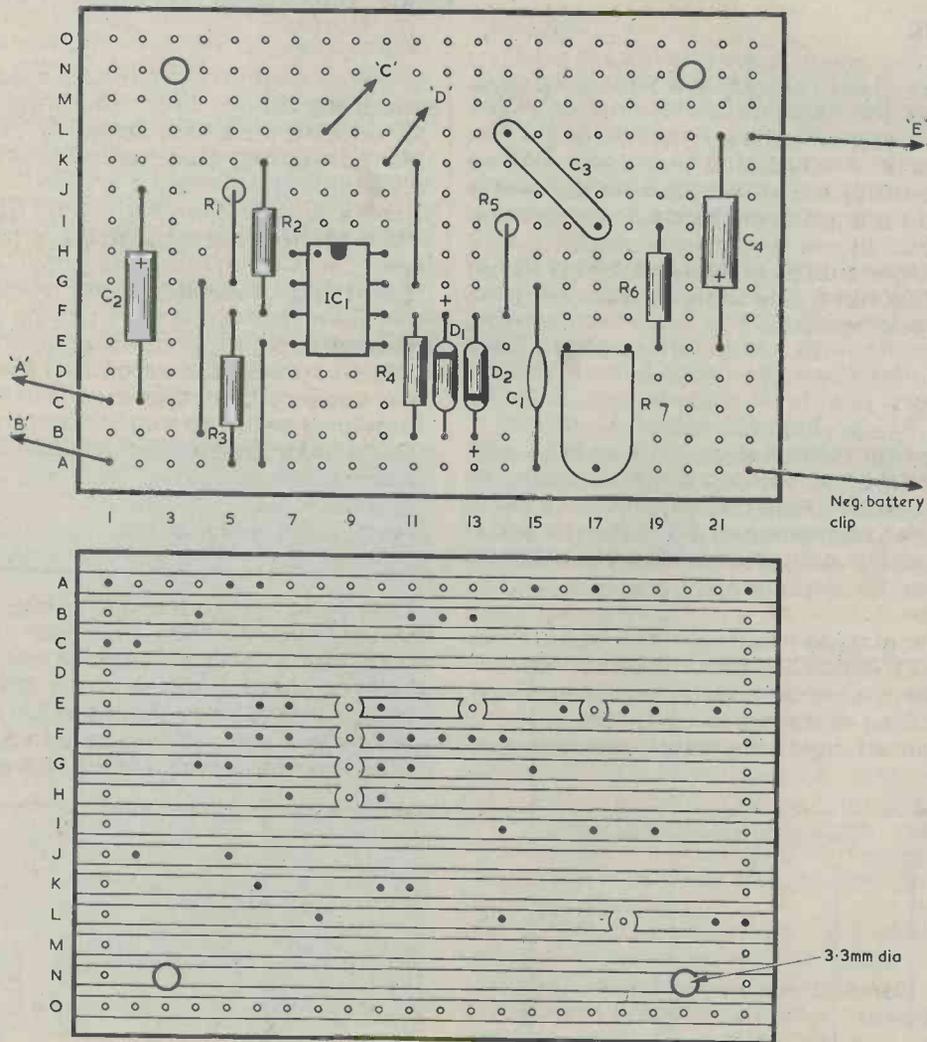
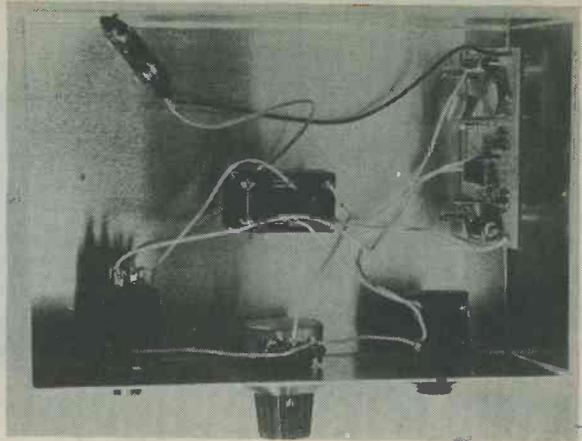


Fig. 3. The component and copper sides of the Veroboard panel. The wires designated "A" to "E" connect to the similarly identified points in Fig. 4.

operation. A suitable switch is available from Maplin Electronic Supplies.

The only other control is the on-off switch S2. In the prototype this is part of the input socket SK1, which has d.p.d.t. contacts, insulated from the jack contacts, which are operated when the jack plug is inserted. This socket is also available from Maplin Electronic Supplies. A separate on-off switch can be alternatively employed, if desired.

The TL071CP specified for IC1 is available from several suppliers. The two electrolytic capacitors are specified as having a working voltage of 10 volts. It will be perfectly in order to use capacitors having a much higher working voltage than this, and it can be as high as 100 volts.

## CONSTRUCTION

The fuzz unit must be housed in a robust metal box, which provides screening and which also has to withstand rough handling. A diecast aluminium box would be ideal, but these are relatively expensive. It was found that a simple aluminium box measuring about 152 by 102 by 51 mm. (6 by 4 by 2 ins.) was quite adequate, and cases of this type are readily available at reasonably low cost.

The box is used inverted so that the lid is at the bottom. This lid is fitted with four large cabinet feet near the corners. S1 is mounted at the centre of what is now the top of the box, so that it can be foot operated. VR1 is mounted at the centre of one of the larger side panels, with SK2 on its left and SK1 on its right. The general layout can be seen in the photographs.

## VEROBOARD PANEL

The majority of the components are assembled on a piece of Veroboard of 0.1 in. matrix having 22 holes by 15 copper strips. This is shown in Fig 3. The board has to be cut down from a larger piece, after which the two mounting holes are drilled and the seven breaks in the copper strips made. The components and link wires are then soldered in place. Finally to be fitted are the negative battery lead and five flexible insulated leads for connection to the components external to the board. These can all be around 8 in. long, being cut to their final length when the other ends are connected.

## COMPONENTS

### Resistors

(All fixed values  $\frac{1}{4}$  watt 5% unless otherwise stated)

- R1 47k $\Omega$
- R2 22k $\Omega$
- R3 22k $\Omega$
- R4 2.2M $\Omega$  10%
- R5 5.6k $\Omega$
- R6 100k $\Omega$
- R7 47k $\Omega$  pre-set potentiometer, 0.1 watt horizontal
- VR1 22k $\Omega$  potentiometer, linear

### Capacitors

- C1 0.047 $\mu$ F ceramic plate or type C280
- C2 1 $\mu$ F electrolytic, 10V. Wkg. (see text)
- C3 0.047 $\mu$ F type C280
- C4 1 $\mu$ F electrolytic, 10V Wkg. (see text)

### Semiconductors

- IC1 TL071CP
- D1 IN4148
- D2 IN4148

### Switches

- S1(a)(b) d.p.d.t. (see text)
- S2 part of SK1 (see text)

### Sockets

- SK1  $\frac{1}{2}$  in. jack socket with d.p.d.t. contacts (see text)
- SK2  $\frac{1}{2}$  in. jack socket


### Miscellaneous


- Aluminium case (see text)
- Veroboard, 0.1 in. matrix
- 9 volt battery type PP3
- Battery connector
- Control knob
- 4 cabinet feet
- Nuts, bolts, wire etc.

The completed Veroboard panel is mounted to the side panel at the SK2 end of the case by means of two 6BA or M3 bolts and nuts. Spacing washers about 12.5mm. long are used on the bolts to ensure that the underside of the board is well clear of the metal case panel.

The point-to-point wiring shown in Fig. 4 is

Fig. 4. Connections to the front panel components and the foot operated switch.

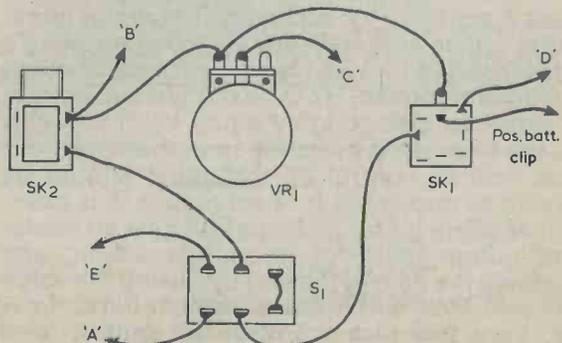

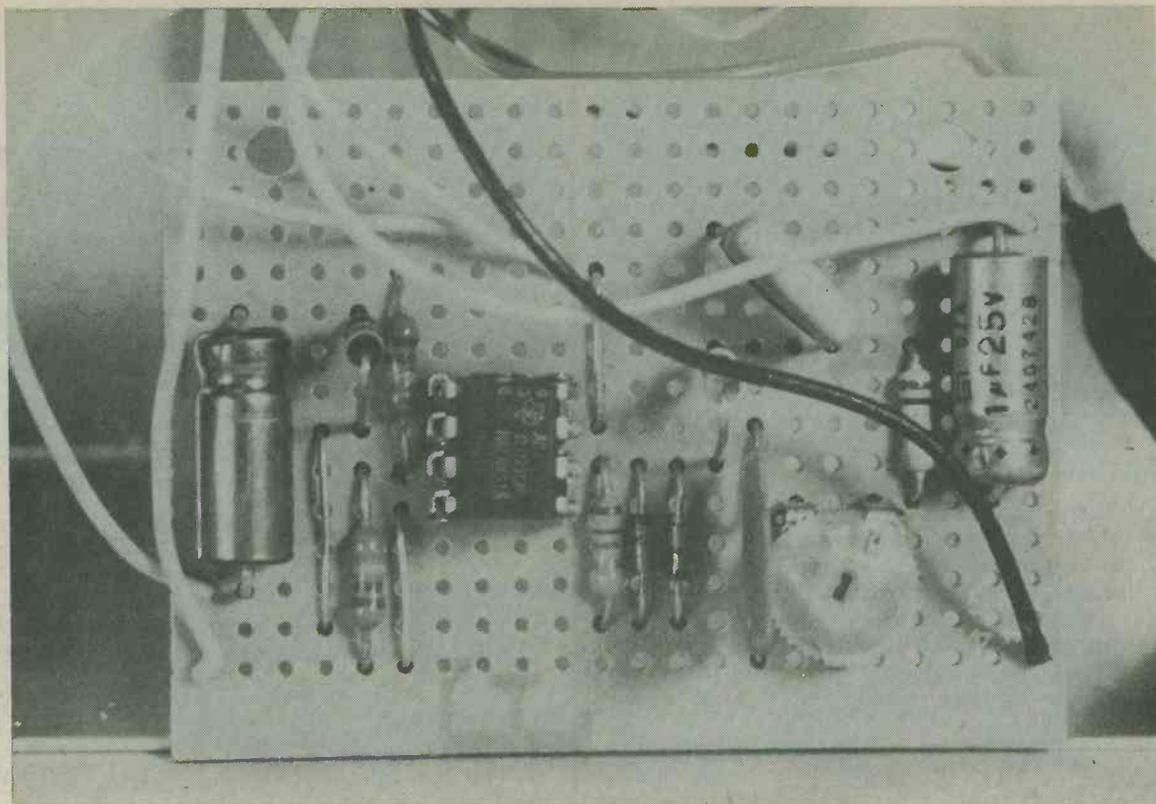

Component layout on the Veroboard panel

then carried out. Confirm with an ohmmeter or continuity tester the tags on the \$K1 assembly which connect to S1 before wiring to these tags. A jack socket with an insulated housing was used in the prototype for \$K2. If an open type of socket is used here (or in the \$K1 position) the connections to it will be obvious from the circuit of Fig. 2.

There is plenty of space for the PP3 battery. This can be held on place with a simple clip or can be secured by sponge plastic when the case lid is screwed on.

### TESTING

After a final and thorough visual check of the wiring, the fuzz box is ready for testing. A screened lead must be used for the connection between its output and the guitar amplifier to prevent pick-up of hum and other electrical noise. Unless a separate on-off switch has been fitted, the unit will be automatically switched on when a plug is inserted into \$K1, and switched off when the plug is removed. R7 is next adjusted, by trial and error, to give roughly equal volume levels with the fuzz effect switched in and out.

The volume control on the guitar should be adjusted to maximum for best results. It is possible that some guitar pick-ups will give an inadequate output level for good fuzz action, and increasing the gain of the unit by raising the value of R4 to 4.7M $\Omega$  should be of benefit here. However, very few pick-ups have an output level which is low enough to make this modification necessary. ■




"Coo Mister! Have you come to fix our tele?"

# The INSTRUCTOR

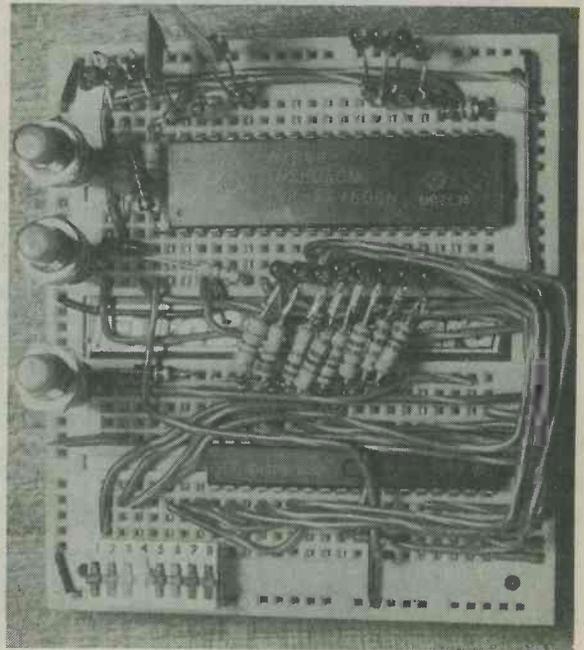Part 6

By Ian Sinclair

A PRACTICAL  
INTRODUCTION  
TO  
MICROPROCESSORS



## *Shifting, Rotating and Serial input/output*

The next family of single-byte instructions we're going to look at carries out the usual action of a shift register, and allows us to program for multiplication among other things. The shift right (SR) instruction acts on the byte in the accumulator and has the effect of shifting each bit into the next place on the right. What happens to the D7 position of the register, and the DO bit? Try it and see, using the program in Fig. 1. We start with the byte 10010001, and end with the displaced byte 01001000. What's happened is that a zero has been shifted into the D7 place, and the 1 has dropped out of the DO place in the register. Each shift instruction causes one more shift, so that if the GO button is pressed twice with the SR instruction set up on the data switches, the byte in the accumulator will be shifted right, twice—try it.

### WITH LINK

There's a variation on this theme which causes the carry/link bit to be fed into the D7 position of the accumulator. This is the shift-right-with-link step (SRL), and it's this use of the carry bit to link into the shift operation which is responsible for the name "link" appearing along with "carry". A program which makes use of the link is shown in Fig 2. The carry/link is set using SCL, and the byte 01100100 is loaded into the accumulator. This is shifted right twice, with the link fed in, by setting up the SRL code 00011101 and pressing GO twice. What do you end up with? Has the carry/link been cleared by the first shift?

The shift-right instruction, with or without link, is sometimes useful, but the rotate right (RR) is even more so. In a rotate instruction, the bits in

```
RESET
LDI    11000100
BYTE   10010001
SR     00011100
DISPLAY
```

Fig. 1

```
RESET
SCL    00000011
LDI    11000100
BYTE   01100100
SRL    00011101
DISPLAY
```

Fig. 2

RESET	
LDI	11000100
BYTE	01100101
RR	00011110
DISPLAY	

Fig. 3

RESET	
LDI	11000100
BYTE	00010101
XAE	00000001
SIO	00011001

(Observe the l.e.d. - see text)

Fig. 4.

the register are shifted right as before, but the bit which drops out of the DO position is shifted into the D7 position. Practically speaking, what has happened is that the serial output of the register is connected to its serial input. Fig 3 shows a program example, setting up 01100101 and rotating right so as to produce 10110010 in one rotation.

We can also bring the carry/link into this operation, using the RRL instruction (00011111). When this is done, the DO bit shifts into the carry/link bit, and the bit which was in the carry/link shifts into D7, with the rest of the bits shifted right one place as before.

One example of the use of the rotate right instruction is the entry of a four bit number from a keyboard. The circuit of the microprocessor system will be arranged so that the four bit number appears in the lower half byte of the accumulator. Before the next number is loaded in, the accumulator must be rotated four times, so that the first number is now in the upper four bits, and the second number can be loaded into the lower four bits.

Shift and rotate instructions are used on all microprocessors, but the next instruction, SIO is another one which is peculiar to the INS8060. SIO means Serial Input/Output, and this means shifting bits into or out of the microprocessor one at a time, rather than in eights. If, for example, you want to record a program or a set of data bytes on a cassette, the eight data lines are not of much use to you because you don't have an eight-track recorder! What is done is to shift the bits, one by one, in a series, to the recorder. When we want to replay the procedure is the same - we shift the bits in one by one and assemble them into bunches of eight for use. This is a simple system which, as it stands, offers no protection against a bit which goes astray - it's left to the program which controls the serial input and output to identify the bits correctly and to feed them out and in at the correct speed. Once again, most other microprocessors need another i.c. connected to the data lines to carry out this action.

In the 8060, the serial input and output acts on the extension register, and does not affect the accumulator. The serial output is taken from a flip-flop fed from the EO end of the extension register to the START pin and the input is taken at the SIN (Serial IN) pin on the microprocessor. On our board, there's a push-button switch at the SIN input, and an l.e.d. hooked to the output, so we can put information in and read it out. The switch earths the serial input when the button is pushed, so that the arrangement is that the input will be 1 unless the switch is pushed. Remember, though, that there are no serial inputs or outputs unless the SIO program instruction is being carried out.

## XAE INSTRUCTION

Take a look at the output first, using the program in Fig. 4. This loads the byte 00010101 into the accumulator, and then uses the XAE instruction to exchange the accumulator and extension registers. With the byte in the extension register, the SIO instruction (00011001) can be set up on the data switches, and we're ready for serial outputs. Watch the serial output l.e.d. and press the GO switch once. This should shift the lowest order bit of the accumulator (A1) to the serial output, causing the l.e.d. to light. At the same time, a 1 will be shifted into the E7 position of the extension register, because the SIN switch is open, allowing the serial input to stay at logic 1. The next press of GO (without altering the settings on the data switches) will cause the next bit to be shifted out. Since this is zero, the l.e.d. will extinguish. The next press of GO will light the l.e.d. again, because of the 1 which started in the E2 position, and so on. After the GO button has been pushed eight times, the l.e.d. will remain lit continually, because the extension register is full of 1s, which were fed in from the SIN switch. Without resetting, hold the SIN switch pressed, and push the GO switch eight times. This should load the extension register with 0s, so that the l.e.d. goes out and will stay out for the next eight presses of the GO button. Try alternately pushing and releasing the SIN switch as you push GO, and then see the effect on the l.e.d.

There are a number of single byte instructions which act on the accumulator, but use the extension register as the source of the bytes. These were listed in Fig. 9 of Part 5 of this series. In each case the numbers which are processed are the bytes in the extension and in the accumulator, and the result is stored in the accumulator. For example, the AND-extension (ANE) will AND the byte in the extension with the byte in the accumulator and store the result in the accumulator. In this way, numbers which have been assembled for the serial input, or which have been taken from the accumulator at an earlier stage, can be fed back into the main accumulator register.

## DOUBLE-BYTE INSTRUCTIONS

Now we have to pop back to look at some more double-byte instructions again, and it's an important group. So far, each load, add, AND or similar instruction which we've used has been immediate - the byte to be processed has followed the instruction. If we'd been following address numbers, for example, we would find that a LDI (load immediate) instruction at address 0001 was followed by the number to be loaded at address 0010. This can be useful, but it's much more likely

RESET

LD 11000000 Note the address number.

DISP 00000011 Note the address number.

The number displayed by the data l.e.d.'s is not important in this example, what we are looking for are the address changes. In the examples which follow the address changes are also the important point.

Fig. 5

that we'll want to load a number which appears at some quite different address – how do we do that? The most common method of loading from a different address is *program-relative displacement*, and we can most easily illustrate what happens by a program example which you can try out. In this example and the ones which follow ignore what the data l.e.d.'s are doing, and concentrate entirely on the address l.e.d.'s. Fig. 5 shows the routine. Remember that the address l.e.d.'s always show the address of the step which you are about to make, so that when we read the l.e.d.'s we're actually reading the address for the next instruction. We start off with the address l.e.d.'s at 0001, and we set the data switches to a load instruction – not load immediate this time, but a PC relative load. PC means program counter, and relative means that the address of the number we want to load is given by adding a byte to the value of the program count. The binary code of this one is 11000000, so when GO is pressed the next address is 0010. We now set up the displacement byte – in this example 00000011 (decimal 3) and press GO again. Now in the programs we've been stepping through up to now, this would result in the address shifting to the next number, 0011 – but that's not what the address l.e.d.'s are reading now! What has happened is that this second byte has been added to the program counter address, to produce the new address 0101 (decimal 5). In a fully-fledged system, then, the number which is to be loaded in is fetched from memory position 0101 instead of being loaded immediately after the load instruction. We wouldn't usually, of course, make such a small jump forward to find a number in memory, because if we had 1024 steps of program in a read-only memory, then we might want to start loading the numbers from a read/write memory which started with its first address at 1025.

Wait a moment, though. How far can we "displace" from the program address? One byte can be a number as large as 11111111, which is 255 – or is it? Try it out as in Fig. 6. Reset and, with the address 0001 shown, set the data switches to load 11000000 and push GO. Then set to 11111111, check that the address which is showing is 0010, and push GO again. The normal step forward

would bring the address to 0011. What does it actually show? Whatever it does, 11111111 doesn't put the program 255 steps on. Can it be that the microprocessor is arranged to read this as a signed number? To check this, repeat the load operation, but this time use 11111110 as the displacement. What address does this cause?

These displacements are limited, then, to seven bit numbers, with the highest order bit indicating sign. We can displace only 127 steps on, or 128 steps back. Now that may not sound very much and it certainly doesn't solve the problem of getting to a memory location which is several thousand steps away, but for a lot of programming it's quite enough. The reason is that most programs are written as short "blocks" of only a few steps, and so the displacements that are needed are only of a few steps. For larger displacements – stay with us.

#### LARGE DISPLACEMENTS

All the functions which are available as "immediate" or as "extension" are also available as PC relative displacements, so that we can load AND, OR, XOR, DECIMAL ADD, ADD, complement-and-add numbers which are taken from an address given by the program count plus a signed displacement. Next question is: what happens after that? The program of Fig. 7 answers that in a practical way. We've set up to load, specified a displacement of 00000101 and then, having got there, loaded the number 00000001. What is the address showing now? It is, as we might suspect, the next address that the microprocessor would have gone to if we had not used the displacement. That, in fact, is one of the very useful features of this method of loading a byte from another address – you don't have to do anything special to be sure of returning to your normal address afterwards. As well as loading into the accumulator there is an instruction, STORE (ST), which is found only in this displacement form (there's no store immediate, for example). We've used this to display numbers, and we can now clear up a mystery which has been with us since Part 3. When we display, the routine we've used has been to set the store code

RESET

LD 11000000 Note address.

BYTE 11111111 Note address.

What address is caused by this displacement number? Try 11111110 as a displacement also.

Fig. 6.

```

RESET
LD      11000000
DISP   00000101    Note address.
BYTE   00000001    Note address.
Note the final address.

```

Fig. 7.

RESET		Address
LDI	11000100	000000000001
BYTE	11000100	000000000010
ST	11001000	000000000011
READ	11001000	000000000100

The resulting address is 11111001100

**WHY?** The last address in the program counter before the "READ" part of the store instruction was completed was 000000000100, which is decimal 4. The displacement byte was 11001000, which is in decimal -56. The resulting address should be  $4 - 56 = -52$  in decimal. Because 12 address lines are used, this causes all the higher lines to be set - the reason can be seen if we work out the sum in binary, using twelve bits:

-52 in decimal becomes	000000110100
Complemented, this is	111111001011
Add 1 to get	111111001100,
which is the address put out on the lines.	


Fig. 8.

11001000 and press GO twice. Now the first press of GO loads in the instruction to store, and the second loads in 11001000, which is taken by the microprocessor as a negative number (decimal -56). This subtracts 56 (decimal) from the address, causing the odd effects which manifest themselves as the A11 i.e.d. lighting. This is because the 8060 uses 12 address lines, which can address  $2^{12}$ , equal to 4096, memory locations. The normal number of address lines is 16, and the 8060 has the other four but they have to be gated and latched, they're not available on pins. This type of arrangement is called paging—the 8060 has an address page of 4096 bytes, and the number of pages is 24 (the four higher order bits), equal to 16, making a grand total of 65536 bytes which can be addressed. Now these upper few bits aren't affected by anything that happens to the 12 lower address lines, so that one lot of 4096 addresses is separate from another lot. When we use a negative displacement number which is greater than the program address, we run backwards "across the page". Fig. 8 helps to explain this.

The result is that the high order address lines set to 1, causing an address number which we wouldn't normally expect, since it seems to be much larger than we could get from a displacement of +127. This, incidentally, is one way of getting displacements greater than +127 relative

to the program counter, but it's not mentioned in any of the manufacturer's data books!

(To be continued)

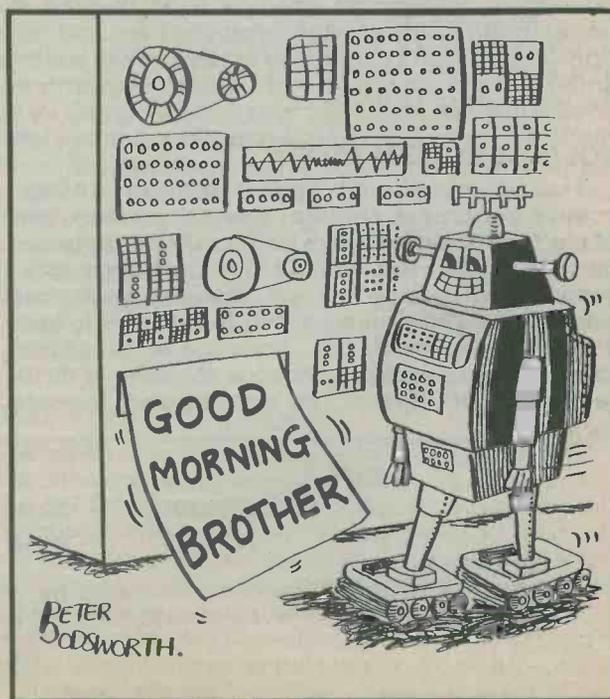

# MEASURING ELECTROLYTICS

By  
T. H. Reynolds

## *Inexpensive capacitance measuring circuit*

In Fig. 1(a) a resistor  $R$  and capacitor  $C$  are in series, and are connected to a source of supply via a switch. The switch is open and the capacitor is discharged. When the switch is closed the capacitor charges via the resistor and the voltage across it increases. After a period of time equal to the time constant of the resistor and the capacitor, the voltage across the capacitor will have reached 63% of the supply voltage. The time constant, in seconds, is equal to the value of  $C$  in microfarads multiplied by the value of  $R$  in megohms. The capacitor still continues to charge after the time constant level, of course, and the voltage across its plates eventually becomes equal to the supply voltage.

In Fig. 1(b) the positions of the capacitor and resistor are reversed. If the capacitor is discharged and the switch is closed the voltage across the capacitor increases as before, but this time its lower plate is going negative with respect to the positive rail. The voltage across the capacitor will once again equal 63% of the supply voltage after the time constant of the resistor and capacitor has elapsed.

### VOLTAGE COMPARATOR

The circuit of Fig. 1(b) forms the basis of an inexpensive instrument, capable of measuring the values of electrolytic capacitors, which forms the subject of this article. As used normally the instrument gives approximate indications, but these are more than adequate for components having the very wide tolerances on value which are common with electrolytic capacitors. In any case, quite accurate measurements can be obtained if extra time is employed in carrying them out.

The full circuit of the capacitance measuring instrument is given in Fig. 2, and it will be seen that this incorporates an ICM7555. The ICM7555 is the CMOS version of the 555 and offers very high input impedances at the trigger and threshold inputs, at pins 2 and 6 respectively.

When S2 is in the Off position the capacitor being measured is short-circuited via the current limiting resistor R8, and has zero voltage across it. Putting S2 to On takes the short-circuit off the capacitor and

applies power to the circuit. The test capacitor then begins to charge via whatever resistor is brought into circuit by the Range switch S1. At the instant of putting S2 to the On position, pins 2 and 6 of IC1 are held at the same potential as the positive rail by the discharged test capacitor and the output at pin 3 is low. LED1, in consequence, lights up. The l.e.d. remains alight until the voltage on the lower plate of the test capacitor falls to one-third of the supply voltage. At this voltage the pin 3 output of IC1 goes abruptly high, and the l.e.d. extinguishes. It stays extinguished as the voltage across the charging capacitor continues to increase. The ICM7555 is therefore employed as a voltage comparator.

The length of time during which the l.e.d. is alight is equal to the time needed for the voltage across the test capacitor to reach two-thirds, or 67%, of supply voltage. There was a similar charging circuit in Fig. 1(b) when we noted that the voltage across the test capacitor reached 63% of supply voltage after a period equal to the time constant of  $R$  and  $C$  had


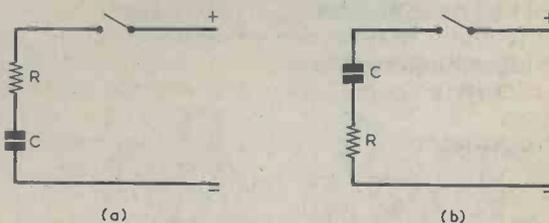


Fig. 1(a). When the switch is closed the voltage across the capacitor rises and reaches 63% of the supply voltage after a period equal to the time constant of the resistor and the capacitor (b). With this circuit the voltage across the capacitor increases in the same way after the switch closes, but the voltage on the lower plate is now negative-going

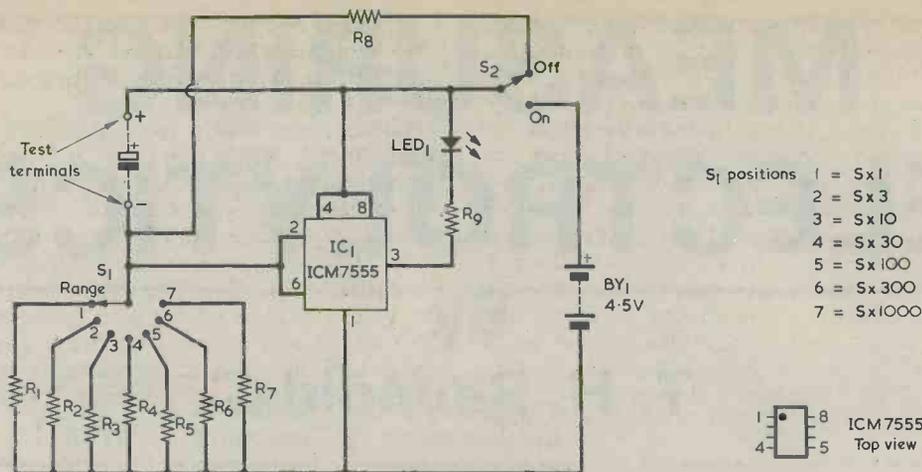

**Fig. 2. The circuit of the capacitance measuring instrument. The test capacitance, in microfarads, is equal to the number of seconds the l.e.d. is alight multiplied by the appropriate figure for the setting of Range switch S1**

elapsed. We shall not be introducing more than a slight error if we assume that the period during which the l.e.d. is alight in Fig. 2 is equal to the time constant

of the capacitor and whatever resistor is brought into circuit by S1. Since we know the value of the resistor we can then find the value of the test capacitor by measuring the length of the period when the l.e.d. is alight. The process is quite easy to carry out and involves no complicated mathematics. The basic principle behind the circuit is not new, and was employed in G. A. French's "Suggested Circuit" in the May 1979 issue. This version used the old 555, employed a different switching arrangement and had the test capacitor charging from the negative rail. The present design has the capacitor charging from the positive rail because the ICM7555 output is then low during the initial charging period and is capable of illuminating an l.e.d. brightly. The ICM7555 output, in the high state, has a useful current capability of a few milliamps only, this being particularly the case with the present low supply voltage of 4.5 volts only.

## COMPONENTS

### Resistors

(All  $\frac{1}{4}$  watt 5%)

- R1 1M $\Omega$
- R2 330k $\Omega$
- R3 100k $\Omega$
- R4 33k $\Omega$
- R5 10k $\Omega$
- R6 3.3k $\Omega$
- R7 1k $\Omega$
- R8 10 $\Omega$
- R9 220 $\Omega$

### Semiconductor

IC1 ICM7555

### Light-Emitting Diode

LED1 red l.e.d.

### Switches

- S1 1-pole 7-way rotary
- S2 s.p.d.t. toggle

### Battery

BY1 4.5 volt battery

### Miscellaneous

- 2 insulated terminals
- Control knob
- Small plastic case
- Wire, etc.

## TIME MEASUREMENT

The period during which the l.e.d. is alight after operating S2 is measured by observing the seconds display on a digital watch or the sweep second hand of an analogue watch. If the watch is held fairly close to the l.e.d. it is a simple matter to observe the seconds readings whilst keeping the l.e.d., which offers a relatively bright light, within the field of vision. Useful indications are possible for timing periods of 2 seconds or longer.

IF S1 is in position 1 it selects the 1M $\Omega$  resistor R1. Should the test capacitor have a value of 5 $\mu$ F the l.e.d. will stay alight for 5 seconds. Thus, test capacitance values, in microfarads, on position 1 of S1 are directly equal to the number of seconds. R2 has a value which is one-third of R1, whereupon test capacitances are equal to the number of seconds multiplied by 3. If the time period is 4 seconds on this range the test capacitance is 12 $\mu$ F. R3 is one-tenth the value of R1 and the seconds multiplier becomes 10. The following resistors, R4 to R7 inclusive, follow the same pattern and the corresponding multipliers are listed in Fig 2.

To measure an unknown capacitor, this is connected to the test terminals and S1 is initially set to position 7. S2 is put to On. If the illumination of the l.e.d. is too brief to measure, the process is repeated with S1 at position 6. S1 is advanced one step at a time until the illumination period becomes sufficiently long to measure comfortably, and the test capacitance is then evaluated. Quite accurate measurements are possible if S1 is put to a lower setting to give illumination periods in the order of 15 to 40 seconds, although these will naturally take longer to carry out. In many instances a reasonable guess at the value of the capacitor will be possible by a consideration of its size, whereupon S1 can be initially put to a setting lower than 7. The minimum value which can be reasonably well measured is  $2\mu\text{F}$  with S1 at position

1. There is really no limit to the maximum capacitance which can be evaluated. With S1 at position 7 a  $10,000\mu\text{F}$  capacitor will cause the l.e.d. to be illuminated for 10 seconds.

The current drawn from the 4.5 volt battery is about 10mA when the l.e.d. is alight and falls to approximately  $40\mu\text{A}$  when the l.e.d. is extinguished. An initial charging current of about 4.5mA flows when S1 is set to position 7. The battery can consist of three HP7 cells in series or a "flat" torch battery, Ever Ready No. 1289. The low battery voltage allows any electrolytic capacitor with a working voltage of 4.5 volts or more to be measured. The switch employed for S1 can be a single pole 12 way rotary switch with adjustable end stop set for 7 way operation. ■

## A CENTURY OF GMT

### BBC World Service Report

The method of time-keeping known as Greenwich Mean Time was one hundred years in 1980. The BBC World Service recently looked back over its past history origins.

In pre-industrial times most craftsmen in Britain were self-employed and decided themselves when to start work, but the growth of the factory system meant that labour had to be organised more systematically. Some of the early factories had clocks, but as the number of clocks increased it became impossible to decide which one was the most accurate.

Adding to the confusion, each locality kept its own time, usually based on the position of the sun at noon. So there could be variations of up to ten or sixteen minutes between different places in the country. Then came the advent of the railway and the need for a uniform time scale throughout the country.

In 1880, Parliament passed the 'Definition of Time' Act. This followed the installation of an electric clock by the Post Office at Greenwich from which an automatic signal was transmitted at exactly 10.00am every day to every telegraph office in the country. Because of the existence of this clock, Greenwich time was defined in 'The Definition of Time Act' as the time to which all the country's clocks should be set.

But although this act established Greenwich time as the legal standard in Britain, clocks in other parts of the world, of course, told a different time and there was no one standard time against which they could be set. This was particularly confusing to mariners travelling from one time zone to another.

In 1884 it was agreed at an international convention that all longitudes and time zones would be based on the Greenwich meridian and Greenwich time. The equipment for keeping the world on time is housed in gleaming aluminium and brick buildings.

Inside one is the 28 inch Isaac Newton telescope, the largest in Western Europe. Another building houses chronometers and computers, and in a nearby aluminium shed stands the masterclock of the world – an instrument known as the photographic zenith tube.

It stares straight up at the sky, photographing and clocking the stars that traverse its field; and the scientists at Greenwich who look through it are able to mark the passage of the universe every thousandth of a millionth of a second.

It is they who provide the BBC with pips heard all over the world to mark the passing of each hour. The BBC keeps two landlines open to the Royal Observatory 24 hours a day, and the pips are transmitted from Greenwich to the BBC at 15 minute intervals.

Sadly however, Greenwich Mean Time has fallen out of favour, for the fact is that the earth is slowing down by about one second a year. Experiments in radio astronomy, geophysics and satellite communication systems demand even greater accuracy. So GMT has been superseded by the atomic clock which measures a second in terms of the number of vibrations of an atom.

But whilst scientists split time to a billionth of a second, for most of us the pips of the Greenwich Time signal are sufficient.



# New Products




## FIXOTAPE CASSETTE ACCESSORY

An answer to the perennial problem of tangled cassette tapes, faced by anyone interested in recording or recordings, is provided by Fixotape, a new device just launched by Jorephani Exports of Park Lane, Corsham, Wilts.

Simple in action, Fixotape snap-fixes to any table edge or shelf. The Cassette is pushed into it, the tape fed through a guide and at the turn of a handle any tangled, twisted, creased or knotted tape is freed within seconds.

Fixotape can also be used as the basis of a mini-workshop, because it is invaluable for editing, cleaning or repairing tapes. Simple, durable and always handy, Fixotape is now being patented worldwide. It is being sold through normal retail trade outlets, particularly hi-fi and record shops, but in the event of difficulty, can be obtained direct from Jorephani Exports, price £1.99 including post and packaging (with a money-back undertaking).

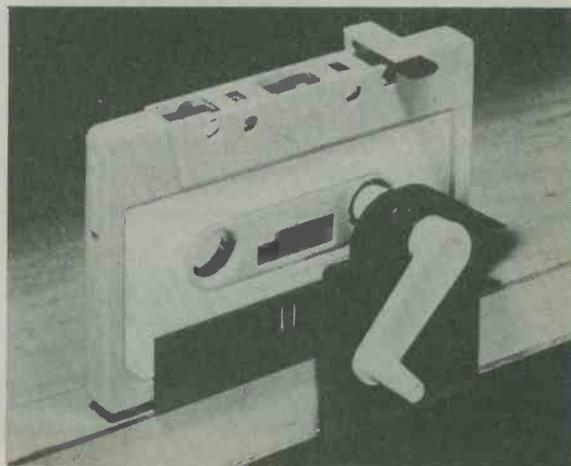

## Built-in advantages in new clock radio

Eagle International have just launched a digital alarm clock radio which has been specially designed to be mounted neatly into a bedhead, kitchen unit or other site in the house where maximum advantage may be taken of its comprehensive facilities.

The RCA 20 has a removable back panel which, when unscrewed, leaves a fully enclosed unit that can be fitted into a prepared aperture. It is complete with all necessary mounting brackets and screws to enable a simple and neat installation. However, if the outer back panel is left in place, the slim-cased RCA 20 may be used free-standing in the conventional way.

The clock radio embodies an unusual variety of facilities for its price - retailing at around £44 (inc.

VAT). The "touch-snooze" plate, as well as serving the late-night and early-morning listener, offers a timer facility for the busy cook, who can set the alarm for any period up to 59 minutes. It can be programmed, in fact, to give the listener up to half-a-dozen calls within the hour. The RCA 20 can be mounted in a kitchen unit fascia, conveniently away from working surfaces.

The alarm function can be set for any desired time or radio station (both Medium wave and FM), and this automatically switches on the radio with or without a "warble" call as desired. The green LED time readout has a fully adjustable brightness control.

Further details can be obtained from:

**Eagle International,  
Precision Centre,  
Heather Park Drive,  
Wembley HAO 1SU.**

## Mail Order Protection Scheme

The publishers of this magazine have given to the Director General of Fair Trading an undertaking to refund money sent by readers in response to mail order advertisements placed in this magazine by mail order traders who have become the subject of liquidation or bankruptcy proceedings and who fail to supply goods or refund money. These refunds are made voluntarily and are subject to proof that payment was made to the advertiser for goods ordered through an advertisement in this magazine. The arrangement does not apply to any failure to supply goods advertised in a catalogue or direct mail solicitation.

If a mail order trader fails, readers are advised to lodge a claim with the Advertisement Manager of this magazine within 3 months of the appearance of the advertisement.

For the purpose of this scheme mail order advertising is defined as:

"Direct response advertisements, display or postal bargains where cash has to be sent in advance of goods being delivered."

Classified and catalogue mail order advertising are excluded.

# NOTES FOR NEWCOMERS

## OHMS PER VOLT

By D. Snaith

### Explaining a commonly encountered phrase

Digital multimeters, with readings given by an i.e.d. or liquid crystal display, are becoming more and more common. Unfortunately, they still tend to remain rather expensive and we can only hope that, like pocket calculators and digital watches, they will eventually start reducing in price. Whereupon, for the time being those of us with short pockets will continue to use the trusty old analogue multimeter with its pointer and scales.

#### METER RESISTANCE

What can be puzzling to the beginner in electronics is that the sensitivity of analogue multimeters on their voltage ranges is specified in terms of "ohms per volt". To understand how this expression arises we have first to examine what constitutes an analogue voltmeter.

In Fig 1(a) we have the basic meter movement for an analogue meter and, to choose a nice easy figure, this could have a full-scale deflection current (i.e. the current at which the needle indicates maximum on its scale) of 1mA. The meter movement will be a moving-coil type in which a coil having many turns of thin wire is pivoted to turn in a magnetic field. That coil is bound to have a significant resistance and a typical figure could be  $170\Omega$ . This is known as the "internal resistance of the meter movement.

Let's say that we want to use this meter in a voltmeter having a full-scale deflection of 1 volt. We do this by adding a resistor,  $R_1$ , in series, as in Fig. 1(b). What is the value of this resistor? Well, we know from Ohm's Law that, if we apply a voltage of 1 volt across a resistance of  $1k\Omega$  the current which flows in the resistance is 1mA. Should we make the series resistor of Fig. 1(b)  $1k\Omega$  then? No, we can't do that because

there is already  $170\Omega$  in the meter coil, and so we make the series resistor  $1k\Omega$  minus  $170\Omega$ , or  $830\Omega$ , as in Fig 1 (c). The total resistance between the voltmeter terminals is now  $1k\Omega$  and so if we apply 1 volt to those terminals 1mA of current will flow and the meter will indicate full-scale deflection, or "f.s.d." for short.

Let's next say that we want to add two more ranges to the voltmeter, to give f.s.d. readings at 5 volts and at 20 volts. This we start to do in Fig. 2(a). A current of 1mA will flow when 5 volts are applied to a resistance of  $5k\Omega$ . We already have  $1k\Omega$  in the meter movement coil plus  $R_1$ , so we only need to add

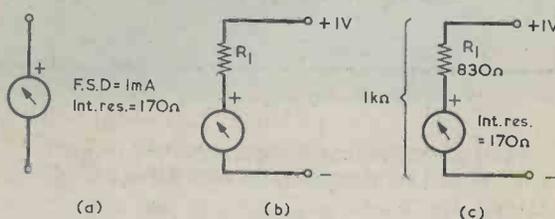


Fig. 1(a). A 0–1mA moving-coil meter movement. This can, typically, have an internal resistance of  $170\Omega$   
(b) Adding a resistor,  $R_1$ , to produce a 0–1 voltmeter. What should be the value of  $R_1$ ?  
(c) Since the total resistance must be  $1k\Omega$ ,  $R_1$  requires a resistance of  $830\Omega$

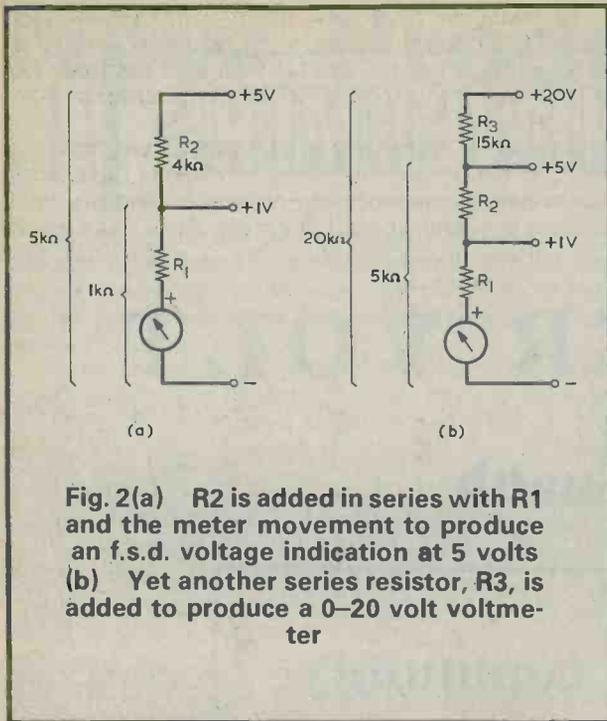


Fig. 2(a) R2 is added in series with R1 and the meter movement to produce an f.s.d. voltage indication at 5 volts  
 (b) Yet another series resistor, R3, is added to produce a 0-20 volt voltmeter

another series resistor, R2, which has a resistance of 4kΩ. We advance to the 20 volt range in Fig. 2(b). Here we want 20kΩ for a current of 1mA to flow at f.s.d., and we add a further series resistor, R3, having a value of 15kΩ. So the grand total of resistance on the 20 volt range is 20kΩ.

### SENSITIVITY

Summing up, we have 1kΩ voltmeter resistance on the 1 volt range, 5kΩ voltmeter resistance on the 5 volt range and 20kΩ voltmeter resistance on the 20 volt range. In other words we have a voltmeter with a sensitivity of 1kΩ per volt or, to make it sound grander, 1,000Ω per volt.

If our basic meter movement had an f.s.d. sensitivity of 100μA, which is one-tenth of 1mA, the total resistance values become multiplied by 10. On a 1 volt range we would have a total resistance (meter coil plus series resistor) of 10kΩ, on the 5 volt range a total of 50kΩ and on the 20 volt range a total of 200kΩ. So, a basic meter movement with an f.s.d. sensitivity of 100μA permits us to make up a voltmeter with a resistance of 10,000Ω per volt. If the meter movement had an f.s.d. sensitivity of 50μA we could make up a voltmeter with a resistance of 20,000Ω per volt.

We have used voltage ranges of 1 volt, 5 volts and 20 volts in our example but the same results apply to other voltage ranges. Thus, if a voltmeter with a sensitivity of 10,000Ω per volt has a 10 volt range, the total resistance presented on that range would be 100kΩ.

Expressing voltmeter sensitivity in terms of ohms per volt is not an engineer's idea for making things difficult for newcomers. It is a very useful method of showing how much loading a voltmeter will place on a circuit being checked. If our particular voltmeter is stated to be 10,000Ω per volt and we switch it to a 50 volt range to take a reading, we know that the voltmeter will load the circuit being checked with a resistance of 50 times 10,000Ω, or 500kΩ. ■

# REGULATOR CIRCUITS

By  
**D. H. Trent**

# Fixed and variable voltage regulators

The 78L05 is a small 5 volt regulator with a maximum output current of 100mA. It is in a T092 encapsulation and the lead-out inset in Fig. 1 shows a bottom view with the lead-outs pointing towards the reader. Fig. 1 also shows the manner in which the regulator is normally connected into circuit. The unregulated input voltage should be at least 2 volts higher than the stabilized output voltage. The two bypass capacitors ensure stability and should be wired close to the device. The 78L05 does not have output short-circuit protection, and output currents should not be allowed to exceed 100mA.

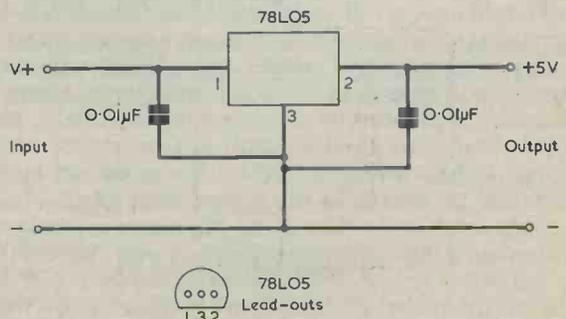
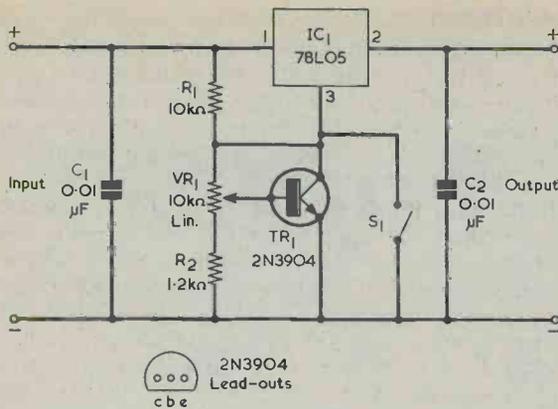


Fig. 1. The normal circuit in which the 78L05 voltage regulator is employed.

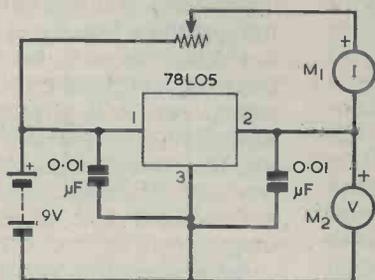


**Fig. 2.** With this circuit the stabilized output voltage may be varied from about 5.6 to slightly more than 10 volts by adjusting VR1. Closing S1 produces a 5 volt stabilized output.

### VARIABLE VOLTAGE

If the common lead-out, pin 3, is taken positive of the negative rail the stabilized output voltage is 5 volts positive of the pin 3 voltage. Fig. 2 shows a variable voltage stabilized power supply which takes advantage of this effect. The collector voltage of TR1 is that which causes about 0.6 volt to be applied to its base so that, when VR1 slider is at the top of its track, approximately 0.6 volt appears across the transistor. When VR1 slider is at the bottom of its track, a voltage slightly in excess of 5 volts (assuming VR1 and R2 have their nominal values) is given across the transistor. Intermediate settings of VR1 give intermediate voltages.

The output voltage can, in consequence, be varied by VR1 over a range of around 5.6 volts to slightly more than 10 volts, all voltages having good stabilization up to 100mA. In practice the maximum voltage may vary from the calculated figure. This is mainly because of variations of value in VR1, which will in



**Fig. 3.** An experimental circuit in which current is drawn from the regulator output in the opposite direction to normal.


most instances be a 20% component. Switch S1 is closed to cause the regulator to give a 5 volt output. If this facility is not required, S1 may be omitted. The unstabilized input voltage can be of the order of 14 to 18 volts.

Resistor R1 is not essential, but it gives a marginal improvement in performance by causing the transistor to pass a collector current greater than the small current available at pin 3 of the regulator. As a result, the voltage across the transistor is maintained at a more stable level.

### REVERSE CURRENT

It is frequently of interest to try devices in circuit applications for which they are not primarily intended, and the author has checked out 78L05 performance in the test set-up of Fig. 3. The regulated output is 5 volts as before, but current is drawn from it not towards the negative rail but in the opposite direction. The current is monitored by the milliammeter M1, and is varied by the potentiometer coupling to the positive terminal of the battery. M2 is a very high resistance voltmeter.

Fig. 4 shows the graph obtained by plotting output voltage against the "reverse output current". The voltage remains steady at 5 volts until the current rises to some 0.5mA above which it starts to rise, reaching some 7.5 volts around 2mA. In consequence, and maintaining a safety factor, it would seem that the 78L05 is capable of maintaining its regulated output voltage for "reverse output currents" up to at least 0.3mA.

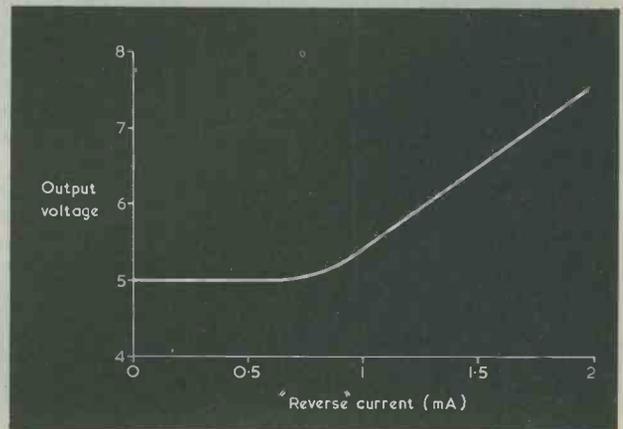

**Fig. 4.** Output voltage - current curve given with the test circuit of Fig.3.

A current of 0.3mA is very small in terms of power supplies but it nevertheless allows the regulator to provide a useful reference voltage in high impedance circuits, and it would be sufficient to drive, say, an emitter follower which itself passed some 50mA.

The variable voltage supply circuit of Fig. 2 is also capable of providing low "reverse output currents" without any change in output voltage. It can, therefore, provide a reference voltage adjustable within its range and having a source capability of 100mA and a sink capability of at least 0.3mA. ■

# Radio Topics



By Recorder

There are always new people entering any pursuit, and it would seem that our particular hobby, that of constructing electronic projects, is becoming more and more favoured by those who wish to expand their experience and acquire assembly skills, as well as extract quite a lot of enjoyment from the process. Newcomers do not, obviously, know all the ropes, and there are almost always some hurdles which appear insurmountable at first until, magically, they have been successfully cleared.

The brand-new beginner in electronics will, of course, follow his own inclinations, and he may tackle quite ambitious projects right from the start. Others may prefer to gain confidence by constructing simpler designs. When it is found that these work after they have been completed, the new enthusiast can then carry on to more complex equipment.

## MAIL ORDER SHOPPING

One continuing problem which besets the beginner is the purchasing of components. Not all of us have the good fortune to live near a well-stocked electronic component shop, and even then it is almost certain that such a shop will not have available some of the more out-of-the-way components that occasionally turn up in projects. The only recourse, then, is to obtain the parts required by mail order. If you

look through the advertising pages of *Radio & Electronics Constructor* you will find listings of available parts by suppliers together with quite simple instructions for their purchase through the mail.

The newcomer will be even better served if he obtains component catalogues, as also advertised in this journal. Many suppliers have stocks which are so large and varied that they could not possibly be listed in magazine advertisements, and the only way to find out what items can be obtained is to send off for their catalogues. The catalogues are often full of extremely useful descriptions of the parts on offer, and the catalogues themselves may even contain basic constructional information for their use.

With a few catalogues in front of you, you can quickly find all the components you require for a particular constructional exercise and you can also, where there is a choice, pick the least expensive. Half an hour with the catalogues can enable you to order very many parts, and the only minor snag is that you have to wait a few days for the components to come through to you after you have posted off your order.

So, if you are embarking on electronic construction as the pleasurable pursuit that it is, do give serious consideration to

obtaining mail order catalogues. They are interesting, instructive and can save you no end of time!

## COLLECTING SPARES

The beginner will probably find, after he has spent some months at construction, that he is beginning to acquire quite a collection of odd components together with nuts, bolts and other hardware. Some components such as small resistors can be so cheap, even for these days, that it hardly seems worth buying just one of a particular value when that is all that is called for in a project. So you may order say, five, and keep the spare resistors on one side for possible future use. Again some items, especially hardware, are on sale in packets rather than singly. Sometimes you may strip down a project whereupon, provided they have been treated carefully, quite a few if not all of the components can be used all over again. However it happens, you will almost inevitably find that you are becoming the owner of quite a large number of items, all of them serviceable and all ready for use.

As soon as this stock of spare parts begins to become large it is a very good idea to keep the items sorted out. Small glass or clear plastic jars are surprisingly useful here because you can see the contents, and if

they have screw-on caps they are even more useful. The last thing I would want to do is influence your family's eating habits but you may find it worth-while, the next time you are in your local supermarket, to look around for items of food which are sold in transparent containers that would be just right for your spare parts collection.

### COMPONENT MARKINGS

A good way of keeping spare resistors sorted out is to put them in groups corresponding to the third colour in their colour coding. Thus, all resistors graded orange would be in the range 10k $\Omega$  to just short of 100k $\Omega$ , those graded yellow would run from 100k $\Omega$  to less than 1M $\Omega$ , and those in the green grade would be single figure megohm values. Keeping resistors sorted out in this way saves a lot of searching when you need a value in a hurry.

Capacitors can be sorted out in terms of type. Silvered-micas could constitute one group, polystyrenes another group, and so on. Take care with capacitors having printed values because the printing can become rubbed off very easily.

Because of the impermanence of the markings on some semiconductors, it is very advisable to have a container for each type. Otherwise, you might find yourself soldering into circuit a 78L05 voltage regulator in the happy belief that it is a BC184L, or a ZN4114 radio i.c. instead of a BC109C. Incidentally, you can't blame the manufacturers if the marking on some semiconductor devices soon becomes smudged or erased. In normal use the devices would simply be soldered to a printed board at some factory, and the markings would be perfectly able to withstand the small amount of handling then involved.

So you may well find yourself collecting more and more items without even seriously attempting to do so. These are then immediately available for experimental work, which can be even more fun than assembling published projects.

### POCKET MAGNETOMETERS

The hand-held meter you can see in the photograph is not the sort of instrument you encounter every day. It isn't even an electrical instrument. It is a magnetometer and its function is to measure residual magnetism in steel parts, to measure magnetic polarity and to compare magnetic fields. The model shown is capable of measuring gauss up to plus or minus 5 gauss and has 0.5 gauss scale units.

The instrument is dual purpose and has an outer black scale and an inner red scale. The black scale gives direct gauss readings for a uniform magnetic field oriented parallel with the centre line on the scale. That centre line is immediately below the pointer pivot and has an arrow pointing directly downwards. The red scale is used to determine the magnitude and direction of a magnetic field which is parallel with the pointer.


There is a range of 12 similar models, with type numbers from LR77/1 to LR77/12 and these provide sensitivities from plus or minus 0.5 gauss up to plus or minus 100 gauss. Made in the USA by Annis, the meters are supplied by Leavers-Rich Equipment Limited, 319 Trinity Road, Wandsworth, London SW18 3SL.

### MARCONI UMBRELLAS

Local a.m. radio stations have their problems, particularly with respect to finance. A considerable expense can be incurred with the provision of a suitable aerial system which, normally, requires to be about one quarter wavelength in height. So, if you set up a transmitter at around 400 meters you could need an aerial which is 100 metres, or nearly 110 yards high.

New medium wave "Umbrella Antennas" made by Marconi Communications Systems Limited overcome the problem, and these are being supplied to the Independent Broadcasting Authority. Following the successful commissioning of one such aerial for the IBA's local radio station in Cardiff, two further aerials have been ordered from the Marconi Antenna Systems Division for installation at the new Independent local radio stations at Aberdeen and Inverness. Marconi is also to provide the IBA with a transportable version for use as a standby.

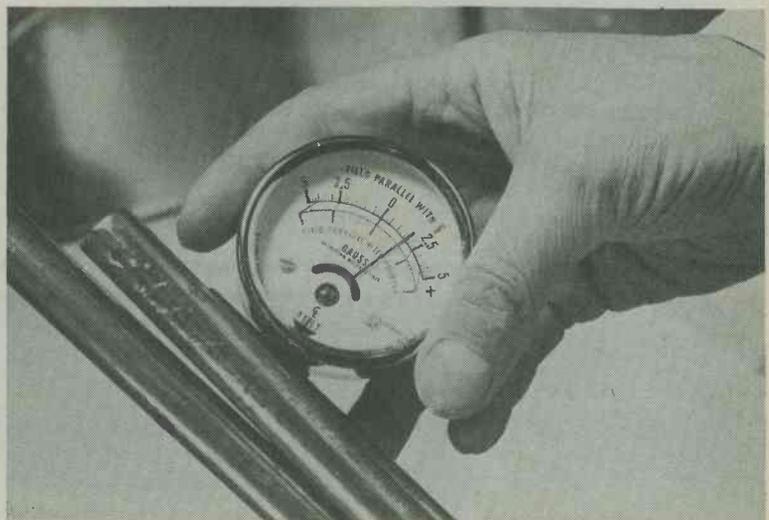The requirements of operators of local radio stations, and the problems they face, have resulted over the years in the development of a number of solutions. Of these, what must undoubtedly be one of the most innovative is the Marconi Umbrella Antenna




A pocket magnetometer available from Leavers-Rich Equipment Limited. This measures from -5 to +5 gauss in 0.5 gauss stages.

system. Basically, the operator requirements are to keep costs to a minimum while still providing a satisfactory coverage and, since aerials tend to be large and unsightly, to reduce environmental problems to a minimum.

With standard quarter-wave aerials, the cost of the basic structure at medium wave frequencies is disproportionately large in comparison with the cost of the transmitter itself. The Marconi Umbrella system, in which the aerial is "folded" so as to reduce its height, is less than half the size of conventional systems and makes a very considerable saving on the cost of installation. Furthermore the systems provided for Cardiff, Aberdeen and Inverness are such that the transmitter can be matched directly to the aerial without the need for an expensive aerial tuning unit.

Marconi Umbrellas are to be found all round the world and the company, which has almost one hundred years experience in aerial development, can well be considered a world leader in this field. Ranging from l.f. to s.h.f., Marconi aerials are used in satellite communications networks, tropospheric scatter, broadcasting, military and civil communications systems from Bahrein to the West Indies, and from Hong Kong to Norway.

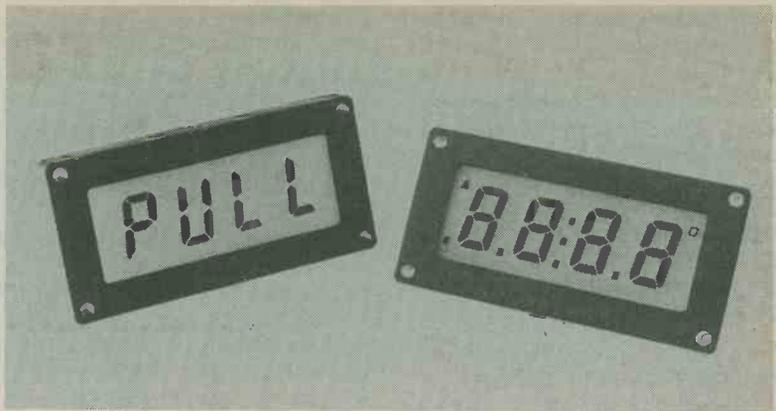

Two of a new range of four combined data decoder and liquid crystal display modules available from Ambit International.

#### LCD DISPLAY MODULES

The second photograph shows two of a new range of miniature combined data decoder and liquid crystal display modules available from Ambit International, 200 North Service Road, Brentwood, Essex, CM14 4SG. These are types DM180 to DM183 and they provide ideal solutions to many m.p.u. data output decoding and display requirements.

Two versions, the DM180 and the DM181, which are based on the ICM7211 (DF411), provide simultaneous decod-

ing and display from multiplexed BCD inputs. Additional options provide for either HEX or Code B displays. The DM180 and DM181 operate from 3.5 to 6 volts at typically only 20 $\mu$ A consumption.

The DM182 and DM183 provide decoding and display using serial data inputs compatible with most types of m.p.u. Consumption from 3 to 15 volts is typically 60 $\mu$ A only.

All the modules measure 60 by 30 by 7mm., and can be supplied with a panel mounting bezel if required.

---

From time to time we try to set aspects of our hobby in a wider context.

Recently there was an article in the *Financial Times* describing the new industries which are developing in Japan and will, in time, be more important to the Japanese than their traditional industries such as shipbuilding and car manufacturing.

According to the article new industries use a new

"basic" raw material, namely Integrated Circuits. Japan is only second to the U.S.A. in producing I.C.s and it is anticipated that they will play a very big part in the Japanese economy during the 1980s.

These new industries will almost certainly be successful and, apparently, video tape already earns them more foreign exchange than do colour TVs.


---

#### BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is 78p, inclusive of postage and packing.

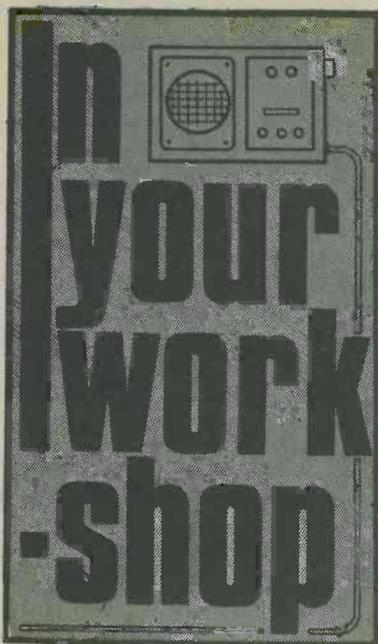Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.



# The transformer with a memory

Even ohmeter tests  
can lead you astray

The little monochrome TV in the smart white cabinet was the last set remaining on the "For Repair" rack. At its front, to the right of the screen, was the loudspeaker grille, and there was a rotary channel selector tuning control above this and a combined volume control and on-off switch below. Above the rear to the right projected an adjustable single wire loop aerial, and this had been pushed down flat over the top of the case.

Dick looked at the set cheerfully. He and Smithy had had a good day, and they had successfully cleared up a record quantity of faults, all obvious and all easy to repair. The life of a service engineer cannot always consist of frustration following frustration and the Fates had smiled fondly at the pair, presenting them with a succession of snags which were almost vying with each other in calling attention to their location. A noisy volume control, a wire adrift at a 2-way DIN plug, a 6-volt battery holder with one HP7 cell inserted wrong way round, a broken tuning drive cord, an unserviceable coaxial socket which had probably suffered from the repeated plugging and unplugging of a TV, game, a worn-out black and white cathode ray tube

to which Smithy had given a further lease of life by application of his secret cathode emission rejuvenator. These were amongst the many elementary faults which had been triumphantly tackled and treated on this happy and halcyon day.

Dick picked up the little TV set, carried it over to his bench, pulled its loop aerial to a vertical position and plugged it into the mains. He rotated the volume control, and there was a click as the on-off switch operated.

## MAINS INPUT RESISTANCE

The set remained silent. Dick waited patiently for the c.r.t. screen to light up but it stayed completely blank. He turned the volume control to its maximum setting and experimentally adjusted the tuning control. There was not even a hiss from the speaker, nor was there any glimmer of light from the tube.

If the form already established for the day was to continue, the fault would probably be nothing more complicated than an open-circuit fuse in the 13 amp mains plug. Dick pulled the plug of the TV set from the bench mains socket, switched his testmeter to a high resistance range, zeroed it and applied the test clips to the live and neutral pins of the plug.

The needle moved over to indicate a resistance which was too low to be read from the meter scale. Dick switched to the lowest ohms range on his meter and re-zeroed it. He then applied the test clips once more to the live and neutral pins of the mains plug. (Fig. 1.)

With a surprising sluggishness, the meter needle moved to the right, to finally settle at a reading of about  $40\Omega$ . Dick disconnected one test clip from the mains plug and then reconnected it. The meter needle advanced, much more quickly, to the  $40\Omega$  reading.

Dick scratched his head. The TV set was still switched on and that  $40\Omega$  reading must almost certainly be the resis-

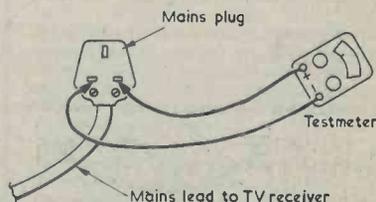


Fig. 1. Dick applied the leads of his testmeter, switched to a low ohms range, to the live and neutral pins of the mains plug connected to the television receiver he was examining.

tance of a mains transformer primary inside the set. So, at least, there were no blown fuses. But the behaviour of his testmeter was puzzling. Why should the needle have moved sluggishly the first time and then relatively rapidly the second time? Dick disconnected the test clip and reconnected it again. The meter needle moved over, with the same speed as on the last occasion, to the reading of  $40\Omega$ .

Frowning, Dick considered the situation. Could there be some peculiar type of capacitor connected across the mains input in the TV set which varied the rate at which the meter needle moved? Could the fact that the needle had moved so much more quickly on the second and third occasions indicate that the capacitor had acquired a charge from the testmeter ohms range battery during the first resistance reading? It was all very mysterious. Struck by a sudden inspiration, Dick removed the test clips from the mains plug pins and reconnected them the other way round. (Fig. 2.)

The meter needle rose sluggishly to indicate about  $100\Omega$  and then crept, quite slowly indeed, to the final reading of  $40\Omega$ . The total time needed to arrive at the final setting was much longer than the fairly extended period when Dick had first applied the testmeter, switched to its low ohms range, to the mains plug pins. Extremely puzzled now, Dick disconnected one test clip and re-applied it to its mains plug pin. The meter needle advanced to the  $40\Omega$  setting at the same relatively rapid speed as on the second and third occasions.

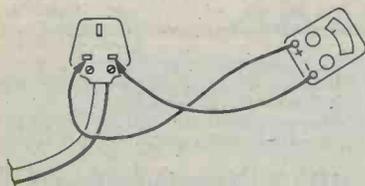


Fig. 2. Puzzled by the resistance readings he obtained, Dick changed over the testmeter leads - to obtain even more puzzling readings!

With trembling fingers, Dick disconnected the test clips, changed them over again and reconnected them. The meter needle rose sluggishly to the  $100\Omega$  calibration point and then crawled, quite slowly indeed, to its ultimate destination of  $40\Omega$ . Worried, Dick gazed at the meter scale. He removed the test clips and started to reconnect them, reversed yet again, to the live and neutral plug pins. After he had connected one clip a thought occurred to him and he switched off the TV set by rotating its volume control fully anti-clockwise. He then connected the remaining test clip to the plug.

The meter needle rose sluggishly to around  $100\Omega$  and then moved, quite slowly indeed, to its final setting of  $40\Omega$ .

#### MYSTERY OHMS

"Oh, no!"

Stricken, Dick slouched back on his stool and gazed apprehensively at the TV set and testmeter in front of him. A low moan escaped his lips.

"What on earth is the matter with you?"

Dick looked up at the sound of Smithy's voice.

"I've got a real enema over here, Smithy," he replied dolefully.

"A real *what*?"

"A real enema."

"Well, I've given a few bad names to some of the snags I've encountered over the years, but I've never had any reason to call a fault that! What's the trouble?"

"It's too difficult to explain," said Dick. "Come on over and I'll show you."

Smithy rose from his stool and walked over to Dick's side.

"This TV came in dead," continued Dick, "and so I thought I'd just do a quick resistance check across its mains input. And I found that I got a slow movement in the testmeter needle when I first connected the test leads and a much quicker movement when I connected them again. Then, when I swapped the test leads over I got a *really* slow needle movement first time off and then the quick movement on connecting up once more. After this, the very slow movement came back at first when I changed the leads back

to their original state. And the meter needle movement keeps on like that each time I connect it. What's more, the effect is still there even when the set is switched off!"

Dick demonstrated the behaviour of the meter needle with the test leads connected one way and then reversed. As he did so, a slow smile spread over Smithy's face.

"There you are," wailed Dick in conclusion, "A right enema!"

He turned round to face the Serviceman.

"Hey, he remarked suspiciously, "what are you grinning at?"

"Your mysterious effect. What do you call it?"

"An enema," repeated Dick. "Something which just cannot be explained."

Smithy burst into laughter.

"You great steaming nit," he roared. "The word is 'enigma'!"

"Oh, all right then, said Dick crossly. "There's no need to take the mickey out of me just because I'm not so - what's the word for being good at words?"

"Erudite?"

"Come off it, Smithy, that's for sticking things together. Well, perhaps I'm not so *learned* as you are with words. But there's still that queer ohmmeter business. If you're so clever, perhaps you can explain that."

Smithy beamed at his assistant.

"You're miffed," he pronounced cheerfully. "I can see that you're quite definitely miffed. Well, it's been such a good and successful day today that I can't let it finish with you in a state of advanced miffedness. So hang on a jiffy."

Smithy walked over to his spares cupboard and rummaged around inside. Eventually he returned and placed a large mains transformer on Dick's bench. He indicated two tags on a tagstrip mounted on top of the transformer.

"Those look to me," said Dick cautiously, "like the primary tags."

"They are," stated Smithy. "Now connect your testmeter clips to these two tags, first one way round and then the other way round."

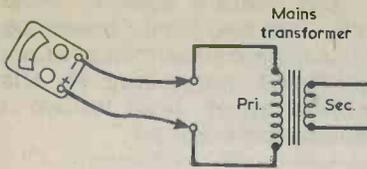


Fig. 3. Smithy used a mains transformer with no connection made to its secondary to demonstrate the types of resistance reading which can be obtained at the primary.

Dick did as he was told. He got precisely the same slow and fast needle movements that he had encountered at the mains input pins for the television receiver. The only difference was that the final resistance reading with this particular transformer was around 25Ω. (Fig. 3.)

#### MEMORY EFFECT

"I don't get it," he said helplessly as he laid his test leads down on his bench. "I just don't get it."

"What you've been seeing," said Smithy, "is a magnetic memory effect which can be quite readily observed with fairly large inductors having laminated iron cores. For the effect to be really noticeable you need to have an iron-cored inductor with a low resistance, and you can get this with the primary of a mains transformer designed to handle some 20 watts or more. Also, you need an ohmmeter which causes a current of at least 10mA to pass through the inductor when the resistance reading is being taken."

"How do you know what current the ohmmeter provides?"

"You can get a rough idea," said Smithy, "from the ohms figure which appears at the mid-scale point of the ohms scale of the meter. Rough check, if the mid-scale ohms figure is around 25Ω or less, the ohmmeter will pass the necessary current through the mains transformer primary. I'm speaking now of analogue meters, of course, and not digi-

tal meters. And when I talk of ohmmeters I'm referring to multimeters which are switched to an ohms range."

Dick looked down at his meter.

"On the low ohms range I switched my meter to," he said, "the mid-scale resistance figure is 20Ω."

"Fair enough," said Smithy, pleased at this confirmation of his comments. "Now, let's look at what happens when you apply the ohmmeter leads to the transformer primary. The basic property of inductance is that it opposes change in the current flowing through it. This is why the initial movement of the ohmmeter needle is fairly slow. When the needle settles at its final position a current in the order of tens of milliamps flows in the mains transformer primary, and it causes the laminations to become magnetised. When you remove the ohmmeter test leads the laminations retain some of the magnetisation which has been induced in them. The result is that if you apply the test leads again with the same polarity the meter needle rises more quickly to the final reading. This is because there's less magnetisation of the laminations to be carried out."

"Humph," grunted Dick dubiously. "Well, I'll have to agree that what you've just said did take place. Go on, Smithy."

"Right," said Smithy briskly. "If, next, you reverse the ohmmeter leads and apply them to the transformer primary once more, the current in the primary is flowing in the opposite direction. The increase in current as the meter needle rises is slowed down not only due to the inductance of the primary but also because the laminations have to be demagnetised from their previous state and magnetised again with opposite polarity. The whole process takes longer than the first application of the ohmmeter leads, which merely took the laminations from an unmagnetised state, because this time you're taking the laminations from magnetisation with one polarity to magnetisation with the opposite polarity. Subsequent applications of the ohmmeter leads

## GAREX

V.H.F. Receivers SR-9 for 2-metres F.M., fully tunable 144-146MHz, 2-speed slow-motion dial, also 11 xtal controlled channels. Compact, sensitive, ideal for fixed or mobile listening. Built-in L.S., 12v D.C. operation £47.15 inc. VAT. Crystals, if required: £2.60 each. All popular 2m. channels in stock. Marine band version (156 162MHz) £47.15 (xtals £2.90). Mains psu for above £11.95. Pocket VHF Receiver 12 channel xtal controlled complete with nicad and charger. 4MHz bandwidth in range 140-175MHz £57.95. Amateur and Marine xtals in stock, prices as SR-9.

Amplifier module new, fully assembled 6W IC unit, 12v D.C. Low impedance (4-8Ω) input and output for extn. speaker amplification, with circuit £2.75.

Neons min wire end 70p/10: £4.50/100

Slide switches min DPDT 20p ea; 5 plus: 16p

Resistor Kits E12 series, 22Ω- to 1MΩ 57 values, 5% carbon film, 1/4W or 1/2W Starter pack, 5 each, value (285) £3.10

Mixed pack, 5 each 1/4W plus 1/2W (570) £5.55

Standard pack, 10 each (570) £5.55

Giant pack, 25 each (1,425) £13.60

BNC Cable mtg socket 50Ω 25p; 5 plus: 20p;

PL259 UHF Plug and Reducer 75p; 5 plus: 67p;

SO239 UHF Socket panel mtd. 60p; 5 plus: 50p;

Nicad rechargeables physically equiv. to zinc-carbon types: AAA (018) £1.80; AA(U7) £1.30;

C(U11) £3.35; PP3 £5.55. Any 5 plus: less 10%. Any 10 plus less 20%.

We stock V.H.F. & U.H.F. mobile aerials s.a.e. details.

Access - Barclaycard


PRICES INCLUDE UK POST, PACKING & VAT

Mail order only

Sole Address

GAREX ELECTRONICS  
7 NORVIC ROAD, MARSWORTH.  
TRING, HERTS HP23 4LS  
Cheddington (STD 0296) 668684

## MORSE MADE EASY

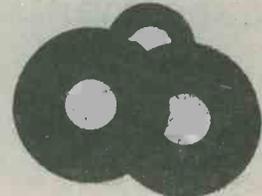

### BY THE G3HSC RHYTHM METHOD!

These courses which have been sold for over 25 years, have been proven many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words. Using scientifically prepared 3 speed records you automatically learn to recognise the code, RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 WPM in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books.

Complete Course £5.50 U.K. p/p 75p. (Overseas postage sufficient for 750grm). Details only s.a.e.

### THE G3HSC MORSE CENTRE

S. Bennett, (Box 8), 45 Green Lane, Purley, Surrey.

Name .....

Address .....

THE  
**MODERN BOOK CO.**

*Largest selection of English & American radio and technical books in the country.*

19-21 PRAED STREET  
LONDON W2 1NP  
Tel: 01-402 9176

**ELECTRONIC  
TUTOR KITS**

Learn electronics the effective way by experiments. Each kit contains an illustrated handbook, which takes you step by step through the fundamentals of electronics, plus all the components needed. No soldering. Safe and instructive for even the young enthusiast. Kit 1, £5.85. Kit 2, £5.95. Kit 3, £6.15. SAE for leaflets on this and other RXG products.

RXG ELECTRONICS LTD.  
15 Walnut Tree Crescent,  
Sawbridgeworth, Herts, CM21 9EB.

Please mention

**Radio &  
Electronics  
Constructor**

when replying to  
advertisements

**PEATS for PARTS**

**ELECTRONIC COMPONENTS  
RADIO & TELEVISION**

*For the convenience of Irish enthusiasts we supply:*

Radio & Electronics  
Constructor Data Books  
Panel Signs Transfers

*Also a postal service*

**PEATS**

the world of electronics  
25 Parnell Street, Dublin 1. Tel 749872

give quick rises in meter needle movement. But if you swop the ohmmeter leads over again you get the considerably slowed down rise in needle movement at the first application."

"It sounds," said Dick, "almost as though the laminations have a memory."

"That's precisely what they do have. They remember the polarity with which they were magnetised last."

"But," protested Dick, "a mains transformer is supposed to work with alternating current at 50 cycles in one second! It's not going to follow changes in current direction which take place at 50Hz if the laminations spend all their time remembering what was the last type of magnetisation they had!"

"It's because they *do* remember," replied Smithy, "that laminated core mains transformers have losses. If you take a mains transformer and, with nothing connected to its secondary or secondaries, connect the primary to the a.c. mains a small alternating current flows. This is loosely referred to as 'magnetising current' and is partly due to the fact that the primary does not have an infinite inductive reactance and so some normal inductive current must flow. But quite a sizeable proportion of that 'magnetising current' consists of the current which is needed to take the laminations from magnetisation with one polarity to magnetisation with the opposite polarity."

"Well, stap me," stated Dick. "I've never heard of that before. I've always looked upon mains transformers as being almost perfect components."

"A well-designed transformer is not all that far from being perfect," said Smithy. "With a good transformer, the magnetising current is much smaller than the ordinary primary current which flows when the secondary or secondaries are loaded."

Dick's thoughts turned to the TV set on his bench.

"There must obviously," he remarked, "be the primary of a mains transformer inside that TV at the end of the mains input lead."

"No doubt of it."

"But there's another mystery," stated Dick, frowning. "The transformer must have still been connected to the mains input lead when I switched the set off."

**MAINS INPUT CIRCUIT**

"Ah," said Smithy. "Now we're dealing with quite a different matter. Let's see if I can find the service manual for that TV."

This time Smithy walked over to the filing cabinet, from which he returned with a service sheet. He opened this out on Dick's bench and the pair of them looked at the circuit diagram. Dick's attention at once became centred on the power supply section. (Fig. 4.)

"Blow me," he gasped. "There's no on-off switch in the mains input circuit at all. The mains goes through a fuse straight into the mains transformer primary!"

"That's right," confirmed Smithy. "This set is one of those which can work either from the mains or from a 12 volt car battery. The on-off switch for the set appears after the mains rectifier circuit and after the 12 volt car battery input socket."

"But," objected Dick, "that means that as soon as you plug the set into the mains and switch on at the mains socket the mains transformer and rectifier circuit are live."

"It does," agreed Smithy. "The power consumed by the transformer and rectifier circuit when the set is switched off will be negligibly low and will almost certainly hardly be enough to make that little wheel in the electricity meter on the wall even think of turning round. Incidentally, this business of having part of a TV still running when it's supposed to be switched off is by no means new. In some TV sets the tube heater is run at a reduced voltage when the receiver on-off switch is turned off, so that there is a quick warm-up when the set is switched on again. Indeed, it is sometimes stated that keeping the tube heater warm during switch-off can even extend the life of the tube, because the thermal shock at the tube heater is less when it changes from a warm to a hot state than

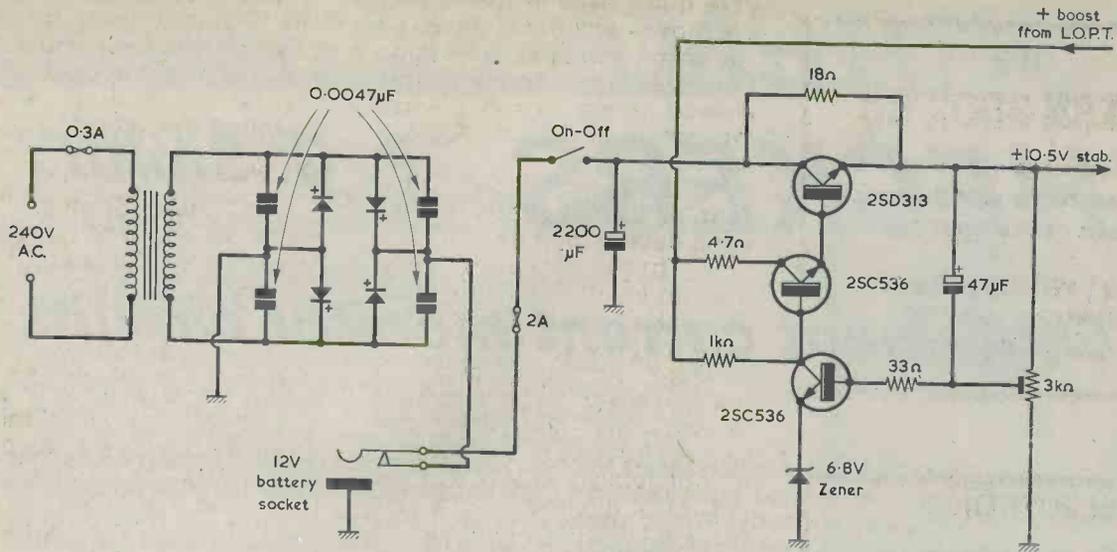


Fig. 4. The circuit of the power supply section of the television receiver. The rectified voltage from the bridge rectifier passes through a normally closed contact on the battery socket to the receiver on-off switch, and thence to the 3-transistor voltage regulator. This circuit is employed in the Sanyo Model 12-T280.

when it changes from a cold to a hot state."

"The fire chiefs are right, then."

"Fire chiefs? What fire chiefs?"

"The fire chiefs who give warnings every now and again about turning off TV sets. They say you should always switch off at the mains socket instead of just switching off at the set."

"Switching off at the mains socket," said Smithy, "would certainly ensure that there were no fire hazards from TV sets which aren't fully turned off by their own switches. Anyway, we'd better see what's wrong with this set now."

"As I said earlier on, it's completely dead," stated Dick. "No sound, no vision, nothing. That's why I started checking for continuity at the mains plug input pins to see if any fuses had blown. After which I got caught up with this mains transformer memory thing!"

"Well, apart from that," commented Smithy, "things have been very simple today. So let's see if our luck holds out with this set."

He turned the set round and took a cursory look at its back. Suddenly his eyes narrowed and he reached down and pul-

ed a small plug out of a socket near the set bottom.

"Try it now, Dick," he said.

Dick took up the receiver mains plug and inserted it into the socket at the rear of his bench once more. He turned the volume control clockwise, whereupon a loud hiss became audible from the speaker. He next adjusted the tuning control and almost immediately picked up one of the three local transmissions. This gave perfectly acceptable vision and sound. The same results, after further adjustments of the tuning control, were available from the other two local stations.


### SUCCESS AGAIN

"It's at times like these," said Smithy, "that I feel I'm picking up money under false pretences. All that was wrong with this set was that someone had inserted the 12 volt battery plug into the battery socket. The contact at the battery socket had then automatically broken the circuit from the mains rectifiers to the on-off switch. Which means that we've cured this particular fault without even having to take the set back off. Things have certainly been good and easy today."

"Apart," commented Dick a little ruefully, "from that enigma of mine."

"Ah yes, your enigma," grinned Smithy. "What did you call it again?"

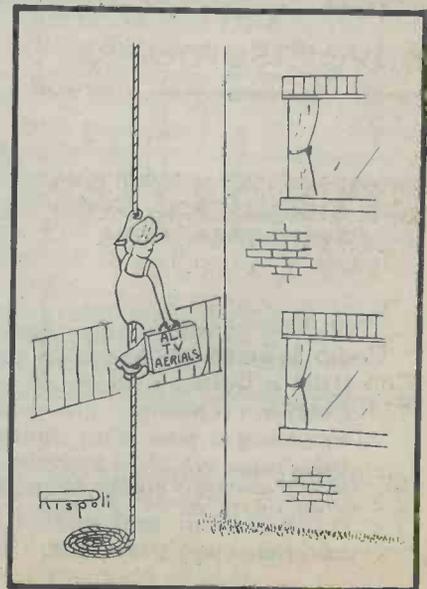But Dick was not to be drawn by Smithy's taunts. And, knowing Smithy as we do, Dick was wise. Much as we appreciate the Serviceman's utterances, we have to admit that there are times when it is difficult to know whether his jibes are intended to be taken in jocular vein or in jugular vein. ■



# CURRENT CHECKERS

By  
P. G. Smith

## Equipment current monitor circuits.

It is sometimes desirable to be able to measure the current drawn by battery operated equipment to ensure that it is functioning correctly. Where such current checks are to be made as a matter of routine it can be helpful to provide the equipment concerned with a means of carrying out a quick connection without the fuss of opening the case and making what, with some battery clips, can be quite fiddling connections to get the meter in series with one of the battery leads.

### CURRENT SOCKET

A very simple method of providing current measuring connections is to fit the equipment with a jack socket employing the circuit shown in Fig. 1(a). The socket is in series between the negative battery terminal and the equipment (shown as a "load") and, when no jack plug is inserted, its contacts complete the supply circuit.

A test lead assembly is made up consisting of two wires which connect at one end to a jack plug and, at the other end, to the terminals of a testmeter switched to a suitable current range. The positive meter terminal connects via the test lead assembly to the jack plug tip and the negative terminal to the jack plug sleeve. The equipment is switched on and the jack plug is then inserted to take the current reading. This method of working has the advantage that any electrolytic capacitors across the equipment supply rails will be charged before the connection is made and there will be no charging current surge in the meter.

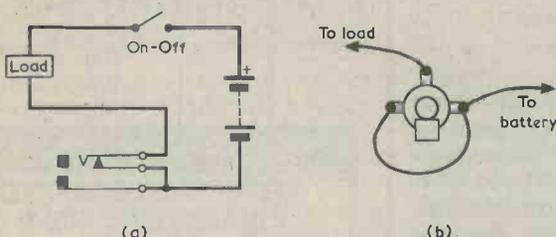


Fig. 1(a). Connecting a jack socket in series with the negative supply in an item of battery operated equipment. Current readings are obtained by inserting a jack plug connected to a testmeter which is switched to a suitable current range.

(b). A 3.5mm. jack socket is suitable and takes up little space. The wiring to it is as illustrated here.

The jack socket can be a standard 3.5mm. socket, and its tags are wired into circuit as shown in Fig. 1(b).

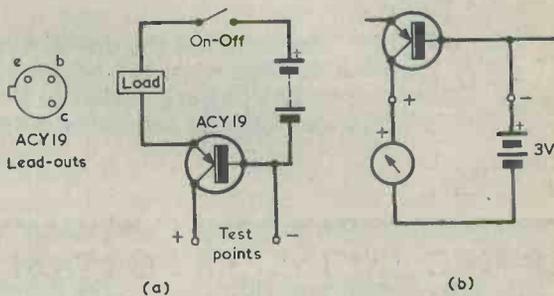


Fig. 2(a). A more unusual approach. The base-emitter junction of a p.n.p. transistor is permanently connected in the negative supply line.

(b). A current-reading meter and a 3 volt battery are connected to the test points with the polarities shown. The meter (a testmeter switched to a current range) indicates the current drawn by the equipment without altering its functioning in any way.

### TRANSISTOR CIRCUIT

A more unusual circuit is shown in Fig. 2(a), in which the base-emitter junction of a transistor is permanently in series with the negative supply to the equipment. This time, two terminals are provided for current measurements.

The current reading meter, and a 3 volt battery, are connected to the test terminals as illustrated in Fig. 2(b), whereupon the meter indicates the current flowing in the base-emitter junction of the transistor! How is this achieved? The transistor is connected in the common base mode and has an emitter-to-collector current gain which is just slightly less than unity.

To keep voltage drop low, the transistor has to be an old-fashioned germanium type. This should be no problem to many constructors having a junk box of a few years' standing. In any case the transistor specified is still quite widely available, although it is getting a little pricey. Suitable alternatives, with the same lead-out layout, are ACY18, ACY20, and ACY21. All these, including the ACY19, have maximum base-emitter current ratings of 0.25 amp.

# TRADE NEWS

## INEXPENSIVE HI-FI

From DIY Hi-Fi comes a new idea to give everyone the chance of bringing the luxury of high quality stereo sound into their homes at a low cost.

The 'CECILIA' is a unique bookshelf loud-speaker system which can be built in a weekend for around £35, the pair.

One of the main contributing factors to the low cost is that there are no electronic components, such as crossovers etc., except for the drive units themselves, (one in each cabinet). The drive unit is the readily available Pioneer TS.107. It was originally developed for the car, and can be purchased at most car radio centres, but DIY-HiFi have found it a perfect match for their new speaker design.

Efficient, yet small (only 17ins high), the 'CECILIA' is deceptively powerful and will produce over 91.5 decibels at one watt/metre with a maximum power handling of 20 watts each, more than enough for most domestic situations!

You build it yourself, using the step-by-step guide and full size plans which are clear and easy to follow. Only the simplest skills and tools are required. All the components and materials are readily available and should be found in your local high street.

For your complete construction guide pack, send only £2.50 (including P & P) to: D-I-Y Hi-Fi, York House, Swan Street, West Malling, Kent.



## SERVICE ENGINEERS' PORTABLE CABINET AND TOOL CASE



Link-Hampson's multiple service cabinet and tool case is destined to suit the needs of service engineers who work on light engineering, instrumentation and electronics equipment.

The Link-Hampson multiple service cabinet and tool case is a portable unit which is easily carried when making equipment servicing calls. It is ideal for servicing television, radio and typewriters in the domestic and commercial markets and electronic equipment in the industrial sphere. A further field of application is within the manufacturing environment by factory service engineers with responsibility for maintaining instrumentation and electronic control gear.

The internals are basically the same as the firm's 200 series cabinet with external dimensions of height 380mm, width 317mm and depth 203mm. A lift up top flap gives easy access to the tool carrying tray. The front panel also folds down, thus exposing the clear plastic pull-out component drawers: these comprise eight small trays 37 x 70 x 155mm, two of 37 x 140 x 155mm, a drawer of 37 x 280 x 155mm and the bottom drawer which measures 81 x 280 x 155mm.

To allow for alternative sizes Link-Hampson provide a selection of drawer dividers. The outer case has an attractive appearance, being made of black simulated leather, with a moulded carrying handle. Extra strength is given to the case by incorporating reinforcing side straps.

Link-Hampson's recommended selling price is £29.95 and the cabinet on its own is £10.00. Their address is 5 Bone Lane, Newbury, Berks.

## DELAYED ORDERS

Messrs. Brian J. Reed of 161 St. Johns Hill, Battersea, London, SW11 1TQ., have asked us to express their regrets to readers whose orders were not completed promptly in the period from mid-October

to mid-November. The cause was staff shortage due to an outbreak of influenza. Normal service has now been resumed.


## RADIO & ELECTRONICS Constructor Projects

BASIC MEDIUM WAVE RADIO	£3.50
TWO 20dB AMPLIFIERS (Part 2)	£6.25
TREMOLO MODULATION UNIT	£9.50
CMOS COMBINATION SWITCH	£5.00
CONSTANT CURRENT NI-CAD CHARGER	£12.40
LABORATORY POWER SUPPLY	£12.80
PASSIVE LOGIC PROBE	£2.50
DUSK TO DAWN SWITCH	£8.50
9V 1A POWER SUPPLY	£8.80

For a complete list of the kits we have produced for 1980, send an SAE.

**COMPONENTS** - Remember we also stock a wide range of components and accessories. Send 30p in stamps for all our lists to date. All kits include parts as specified in the article except where stated (P.C.B.s are not included). Batteries are not included. Please add 50p postage per kit. Allow 14 days for delivery.

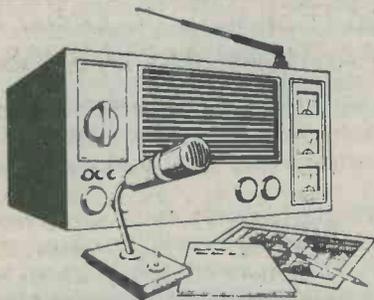**T & J ELECTRONIC COMPONENTS**  
98 Burrow Road, Chigwell, Essex. IG7 4HB.



## BECOME A RADIO AMATEUR

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

No previous knowledge required.

Brochure without obligation to :-

**British National Radio  
& Electronic School**

4 Cleveland Road, Jersey, Channel Islands.

**Free!**

Name .....

Address .....

REC/1/815

BLOCK CAPS PLEASE

## Strip-fix Plastic PANEL SIGNS



★SET 3-Wording-WHITE  
★SET 4-Wording-BLACK

Over 1,000 words and symbols,  
covering more than 300 terms, in  
each set

Illustration of actual size equals RADIO

★SET 5-DIALS

6 sheets containing one Large and two  
Medium scales, Large Horizontal Tuning  
scale, Frequencies, 12 Control Panels

6 SHEETS IN EACH SET

PRICE: **£1.50** per set including VAT.  
p.&p. 11p per set.

**To DATA PUBLICATIONS LTD.,  
57 Maida Vale, London, W9 1SN**

Please supply Panel Signs as follows: Set 3.....Set 4.....Set 5.....

I enclose cheque/crossed postal order for  
(Tick which set is required)

NAME .....

ADDRESS .....

(BLOCK LETTERS PLEASE)

## SMALL ADVERTISEMENTS

Rate: 12p per word. Minimum charge  
£2.00  
Box No. 30p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of Advertisers.

Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. Replies to Box Numbers should be addressed to: Box No. —, Radio and Electronics Constructor, 57 Maida Vale, London, W9 1SN.

### ANY SINGLE SERVICE SHEET £1 plus S.A.E.

Thousands of different service/repair manuals/sheets in stock. Repair data your named TV £6 (with circuits £8). S.A.E newsletter, price lists, quotations. (0698-883334). Ausrec, 76 Churches, Larkhall, Lanarkshire.

U.K. AIRCRAFT frequencies list £1. U.K. marine frequencies list £1. Including HF VHF. P.L.H. Electronics, 20 Vallis Road, Frome, Somerset.

**LEARN ELECTRONICS FAST.** New, unique, brilliantly simple Tutronik system. Selected by BBC TV. No-soldering, 30-kwikbuild electronics projects. Learn fast to identify components, read circuit diagrams, break the colour code and connect circuits that really work. Kit complete with simple-to-follow instructions, circuit plans, components and Tutronic connection system in compact presentation wallet. Only £12.95 plus 75p p. & p. UK (£2.75 p. & p. elsewhere). Available only from Dept. RE, Technocentre Ltd., 140 Norton Road, Stockton-on-Tees, TS20 2BG.

**BOOKS FOR SALE:** *Experiments with Operational Amplifiers*, by George B. Clayton. £3.75. *Digital I.C. Equivalents & Pin Connections*, by Adrian Michaels, £1.20. *Experimenting with Electronic Music* by Brown & Olsen. £1.20. *Electric Model Car Racing* by Laidlaw-Dickson. 60p. *Electronics Unravalled* by Kyle, £1.10. *6 Easy Electronics Projects — Beyond the Transistor*, by Rufus p. Turner. £1.20. *Auto Electronics Simplified*, by Tab Books, £1.20. *Practical Solid-State DC Power Supplies*, by T. D. Towers, £1.00.

**BURGLAR ALARM COMPONENTS.** PVC coated steel bell box £8.74. 6in. masterbell £13.53. 106dB sounder £11.53. Latching personal attack button £2.95. Surface contact £1.28. Flush contact £1.28. Large pressure pad £2.85. Stair tread pad £2.00. 20m range infra red beam £46. Mains/battery alarm control module £17.20 or send for our free component catalogue and price list. All prices inclusive. Sigma Security Systems, 13 St. Johns Street, Oulton, Leeds, W. Yorks. LS26 8JT.

(Continued on page 316)

# Here



# NOW

## ELECTROVALUE CATALOGUE '81

as included FREE with December issue of  
**PRACTICAL ELECTRONICS**

It's work-bench size for keeping alongside your favourite journal for instant reference to stock and technical data.



With more to choose from than ever - all the items you have learned to depend on being obtainable from Electrovalue PLUS MANY NEW ONES to bring Catalogue '81 bang up to date. The V.A.T. inclusive price list that goes with it will hold for at least 4 months before the next one is issued.

*Yes - you will enjoy dealing with Electrovalue - prices are keen - service is tops.*



Write, phone or call if you haven't yet got Catalogue '81 - and you will receive yours by return. (We pay postage).

**AND YOU GET BONUS DISCOUNTS AND FREE U.K. POSTAGE TOO, WHEN YOU BUY FROM ELECTROVALUE.**

ELECTROVALUE LTD., (Dept RCE) 28 St. Judes Rd, Englefield Green, Egham, Surrey TW20 0HB. Telephone: (STD 0784) (London 87) 33603 Telex: 264475

Please send me my FREE COPY OF ELECTROVALUE  
CATALOGUE '81.

Name .....

Address .....

(Dept 28(A))

# A CAREER IN RADIO

Start training *today* and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs — they can do the same for *you*.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

## CITY & GUILDS CERTIFICATES

Telecommunications Technicians'  
Radio TV Electronics Technicians'  
Electrical Installations Technicians'  
Electrical Installation Work  
Radio Amateurs'

MPT Radio Communications Cert  
**EXAMINATION STUDENTS —  
GUARANTEED COACHING  
UNTIL SUCCESSFUL**

## TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:  
Electronic Engineering & Maintenance  
Computer Engineering/Programming  
Radio, TV & Audio Engineering  
& Servicing  
Electrical Engineering Installations  
& Contracting

## COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in .....

Name ..... Age .....

Address .....

Occupation .....



Accredited  
by CACC  
Member of  
ABCC

To  
International Correspondence Schools  
Dept 278C Intertext House, LONDON  
SW8 4UJ or phone 01-622 9911 (anytime)

## REHOR OPTICAL & TECHNICAL

6 SICILIAN AVENUE  
LONDON W.C.1  
Tel. 01-836 4536



**PRICED  
FROM  
£148.75**

### Stereomaster

This microscope's working distance and field of view is relatively large; this feature ensures convenience to the operator who works with both hands while assembling precision mechanisms.

IDEAL FOR  
PRINTED CIRCUITS  
AND OTHER  
DELICATE WORK.

COMES  
COMPLETE WITH

built-in x 10 Mag.  
Objectives x 20  
Objectives x 35  
At extra cost

We stock one of the largest selections of second hand microscopes and optical magnifiers, on and off stands. Please phone for details.

## SMALL ADVERTISEMENTS

(Continued from page 315)

**WANTED:** FAX equipment, manuals, service sheets, etc. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk. NR32 3PJ.

**FOR SALE:** A number of "D & S" three pin, fused, mains plugs and fuses. S.A.E. for details. Box No. G396.

**THE RADIO AMATEUR INVALID & BLIND CLUB** is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. F. E. Woolley, 9 Rannoch Court, Adelaide Road, Surbiton, Surrey, KT6 4TE.

**ZX80 PEOPLE.** Free leaflet explains how to overcome load problems, ½-price memories, etc., supplied with four games on cassette. Send £3 or s.a.e. for details. Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

**FOR SALE:** Damaged repairable cassette recorder and 10 cassettes. £15.00. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

**INTERESTED IN OSCAR?** Then join AMSAT-UK. Newsletters, OSCAR NEWS Journal, prediction charts, etc. Details of membership from: Ron Broadbent, G3AAJ, 94 Herongate Road, Wanstead Park, London, E12 5EQ.

**25 MIXED I.C.'S** £1.50. 100 mixed transistors £3.50. Valves. Early radios. Electronic bargains. Interesting lists 15p. Sole Electronics, REC, 37 Stanley Street, Ormskirk, Lancs, L39 2DH.

**12 UNUSED RECHARGEABLE** Gel type Lead Acid Batteries. 12V 1.5 A.H. £4 each. R. Garas, 147 Seaforth Avenue, New Malden, Surrey.

**JOIN THE INTERNATIONAL S.W. LEAGUE.** Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. — both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £6.00 per annum. (U.K. and British Commonwealth), overseas \$12.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

**RADIO & ELECTRONICS CONSTRUCTOR** 1969-1975, P.W./P.E. 1964-1970. 50p each. S.A.E. for refund if sold. C. Redwood, 45a Lulworth Avenue, Poole, Dorset, BH15 4DH.

(Continued on page 317)

**SMALL ADVERTISEMENTS**  
(Continued from page 316)

**FOR SALE:** Photographic enlarging equipment: Vivitar enlarger. Model E.36 with 50mm f. 3.5 and 75mm f.3.5 lenses. Kodak safety light. Kodak contrast filter set. 11 in. x 14 in. printing frame with copying facilities. Measuring flask. Three trays, three tweezers. Three plastic bottles. Clips. Printing paper. Antistatic brush for cleaning negatives. Kodak Photoguide Booklet. Man's protective apron. £75 o.n.o. Pair of Goodman's speakers 8 ohms, 15 watts, £50 o.n.o. R. L. Gee, 3 Longfellow Drive, Hutton, Essex, CM13 2QQ.

**POSTAL ADVERTISING?** This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

**USE OPTICAL FIBRES TO CARRY LIGHT.** Tough, wire-like strands that are excellent for communications, lighting, electrical isolation, etc. Introductory pack totals sixteen feet of four assorted types, plus twenty page illustrated guide. Send £3.55 inclusive to Quantum Jump Ltd., 53 Marlborough Road, Tuebrook, Liverpool L13 8EA.

**INTERESTED IN RTTY?** You should find the "RTTY Journal" of interest. Published in California, U.S.A., it gives a wide outlook on the current RTTY scene; RTTY-DX; DXCC Honour Roll; VHF RTTY news; and up to date technical articles are included. Specimen copies 35p from: The Subscription Manager, RTTY Journal, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk, NR32 3PJ.

**PRINTED CIRCUIT BOARDS FOR "RADIO & ELECTRONICS CONSTRUCTOR" PROJECTS.**

OCT. 20dB amp. Part 1 68p plus 25p P&P

NOV. 20dB amp. Part 2 62p plus 25p P&P

NOV. Basic Med. Wave radio 69p plus 25p P&P

DEC. Volume Expander £2.25 plus 25p P&P

All boards ready for use, roller tinned and drilled, glassfibre.


Trade enquiries welcome. Highly competitive prices. Write now for quote To:

**BRB PRINTED CIRCUITS (REC)**  
109, Potter Street, Worksop,  
Notts. S80 2HL.

(Continued on page 319)

**ELECTRONICS**  
A NEW AND EXCITING HOBBY!!

BIG, WELL ILLUSTRATED BOOK

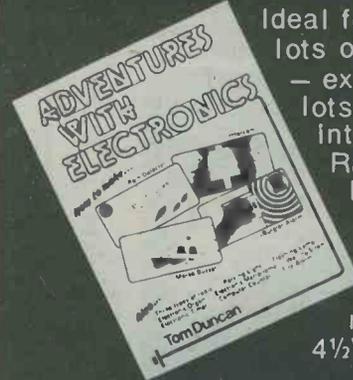

Ideal for beginners - gives lots of general information - explains how to build lots of projects: intercom, Rain Alarm, Radios, Organ, Parking Light etc. All parts supplied and can be re-used on special deck provided, so **NO SOLDERING** is required. Just needs 4½V battery.

**£17.50** inc. VAT & Post

Also

**ADVENTURES WITH MICROELECTRONICS**

- Explore the world of silicon chips -

All components & Deck, £27.95 inc VAT & Post.

Component Catalogue & Bargain List 75p

**GREENWELD**

443G Millbrook Road, Southampton SO1 0HX



**Wilmslow Audio**

*THE firm for speakers!*

**SEND 50p FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST**

- AUDAX ● AUDIOMASTER ● BAKER ● BOWERS &
- WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMAN'S ● HARBETH ● ISOPHON ● I.M.F. ●
- JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● MCKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANNOY ● VIDEOTONE ● WHARFEDALE ●


**WILMSLOW AUDIO** DEPT REC

35/39 CHURCH STREET, WILMSLOW  
CHESHIRE SK9 1AS.

Tel: 0625-529599 for Mail Order & Export of Drive Units, Kits, etc.,  
Tel: 0625-526213 (Swift of Wilmslow) for Hi-fi and complete speakers

# DIRECT SUPPLY SERVICE TO READERS

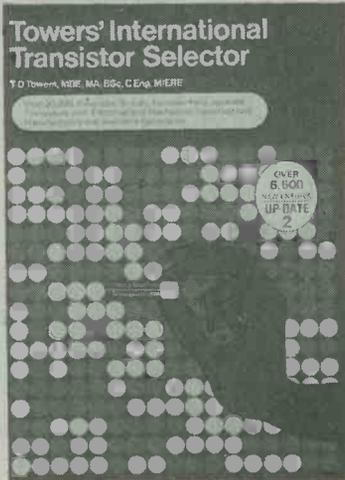
## TOWERS INTERNATIONAL TRANSISTOR SELECTOR (NEW REVISED EDITION)



This is dead!



Would this replace it?

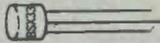

If it takes you longer than 1 minute to find out all about these transistors then you need a copy of TOWER'S INTERNATIONAL TRANSISTOR SELECTOR. It's one of the most useful working books you will be offered this year. And probably the cheapest!

In it, you will find a really international selection of 13,000 transistor types — British, Continental European, American and Japanese. And we think that they will solve 90% of your transistor enquiries.

Current and widely used obsolete types were carefully selected and arranged in Numero-Alphabetical order by an author who was uniquely qualified to do the job. With his compendium, all you need to know is the type number and you can learn all about a transistor's specification; who made it and where to contact them; or what to use to replace it.

Price **£10-70** inc P&P

## TOWERS INTERNATIONAL FET SELECTOR



If you deal with field effect transistors, or fet's — whether as a student, a hobbyist, a circuit engineer, a buyer, a teacher or a serviceman — you often want data on a specific fet of which you know only the type number.

Specifications apart, you may be even more interested in where you can get the device in question. And perhaps more important still (particularly with obsolete devices), you may want guidance on a readily available possible substitute.

This fet compendium, a comprehensive tabulation of basic specification, offers information on:

1. Ratings
2. Characteristics
3. Case details
4. Terminal identifications
5. Applications use
6. Manufacturers
7. Substitution equivalents (both European and American)

The many fet's covered in this compendium are most of the more common current and widely-used obsolete types.

It is International in scope and covers fet's not only from the USA and Continental Europe, but also from the United Kingdom and the Far East (Japan).

Price **£4-60** inc P&P

(Please allow 21 days for delivery)

**Tower's  
International  
Transistor  
Selector** by T. D. Towers  
MBE, MA, BSc, C Eng, MIERE  
**£10-70**  
inc. post and packing

To:—DATA PUBLICATIONS LTD.  
57 MAIDA VALE  
LONDON W9 1SN

Please send me . . . . . copy/copies  
to the address shown below

NAME . . . . .

ADDRESS . . . . .

. . . . .

. . . . .

. . . . . (Block capitals)

**Tower's  
International  
FET  
Selector** by T. D. TOWERS  
MBE, MA, BSc, C Eng, MIERE  
**£4-60**  
inc. post and packing

To:—DATA PUBLICATIONS LTD.  
57 MAIDA VALE  
LONDON W9 1SN

Please send me . . . . . copy/copies  
to the address shown below

NAME . . . . .

ADDRESS . . . . .

. . . . .

. . . . .

. . . . . (Block capitals)

## SMALL ADVERTISEMENTS

(Continued from page 317)

### PERSONAL

**JANE SCOTT FOR GENUINE FRIENDS.** Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

**IF YOU HAVE ENJOYED A HOLIDAY** on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: - The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NR8 8SS.

**BROADLANDS RESIDENTIAL CLUB** for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

**SPONSORS** required for exciting scientific project Norwich Astronomical Society are building a 30" telescope to be housed in a 20" dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, 195 White Woman Lane, Old Catton, Norwich, Norfolk.

### SITUATION VACANT

**WANTED:** Representatives to sell Electronic Components to shops and industries on good commission basis. Please send full details of experience to: Sunmit Electronics, 96 Peel Road, Wembley, Middlesex. Telephone: 01-904-6792.

### BUILD YOUR OWN

**P.A., GROUP & DISCO SPEAKERS** by R. F. C. Stephens

Save money with this practical guide. Plans for 17 different designs, Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

**THE INFRA-BASS LOUDSPEAKER** by G. Holliman

(full constructional details for versions using 15", 12" and 10" (drive units). £2.95 post free (\$6 overseas).

**THE DALESFORD SPEAKER BOOK** by R. F. C. Stephens

This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

**VAN KAREN PUBLISHING**

5 Swan Street, Wilmslow, Cheshire

## MARCO TRADING

To obtain a free copy of our 35 page list simply send a 20p postage stamp or a large SAE. This advertisement shows only a part of our range. (Our new list includes Tants, Electrolytics, Disc ceramics, etc.)

### 400m/w ZENER DIODES

#### Low Price

3V6, 3V9, 4V3, 4V7, 5V1, 5V6, 6V2, 6V8, 7V5, 8V2, 9V1, 10V, 11V, 12V, 13V, 13V5, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V  
Price: 8p each 100 any mix £6.00

### RESISTORS

1/4W at 40°C 5% tol., 2.2 Ω to 2MΩ, E12 2p each.  
Resistor Pack - 2.2 Ω - 2MΩ, 10 each value (730 resistors) £6.00

### 1 watt ZENER DIODES

3V3 to 200V Full range

#### I.C. Sockets

Price 15p each, 100 any mix £12.50  
8 DIL 10p 22 DIL 23p  
14 DIL 13p 24 DIL 24p  
16 DIL 15p 28 DIL 28p  
18 DIL 18p 40 DIL 40p  
20 DIL 22p

### VEROBOARD (Copper Clad)

Size Inch 0-1" 0.15  
2.5 x 1 20p N/A  
2.5 x 5 55p 56p  
2.5 x 3.75 46p 50p  
Speakers 8" x 5" 3 ohm £1.50 each.

### CONNECTING CABLE

Black. Blue. Green. Grey. Orange.  
Pink. Red. White. Violet. Yellow.  
Brown. Singles 5p per metre  
7/0.2mm 5p per metre  
16/0.2mm 8p per metre

### SPECIAL OFFERS

#### BRAND NEW METAL SLIDER POTENTIOMETERS

60mm TRACK	1+	100+	Mains Rocker	BZY96 ZENERS
500 ohm Lin. Mono	35p	28p	switch with	(21W) - 6VZ
50K Log. Stereo	40p	30p	Neon 10A.	1+ 20p each
100K Lin. Stereo	40p	30p	D.P.S.T.	100+ 12p each
1 Meg Log. Stereo	40p	30p	65p each	

Other values available in 45mm track - send for list.

Send your orders to:

DEPT DP11, MARCO TRADING, THE OLD SCHOOL,

EDSTASTON, Nr. WEM, SHROPSHIRE SY4 5RJ

Tel: Whixall (094872) 464/465

Please add 30p postage and packing to each order and add 15% VAT to your total order. Export add NO VAT but add postage. Air/Sea at cost

### TANT. BEAD CAPS

0.1/35v	12p	4.7/35v	12p
0.22/35v	12p	33/6.3v	25p
1.0/35v	12p	47/10v	30p

### SUB. MIN. TOGGLE SWITCHES

SPST -	70p	
SPDT -	78p	
DPDT -	82p	
DPDT -	90p	


### BRIDGE RECTIFIERS

2.5 Amp 50V	32p	400V	50p
400V	43p	6.0 Amp 50V	70p
800V	58p	200V	78p
2.0 Amp 50V	35p	400V	85p
100V	42p	25 Amp 100V	
25 Amp 50V	£2.38		£2.41

### 0.1W SUB. MINIATURE PRE-SETS

100 Ω to 1 Meg Vertical or Horizontal  
Price: 6p each, 100 any mix £4.50

AC12B 20p	BC125 10p	BC184 9p
AD149 58p	BC147 8p	ZN3055 48p
BC107 10p	BC153 10p	BY127 12p
BC108 10p	BC172 8p	IN4007 8p
BC109 10p	BC183 9p	IN4148 2p
BYF90 90p	BC212 9p	BC160 37p
BR101 32p	BC214 9p	CMOS
741 20p	BC140 32p	4011 20p

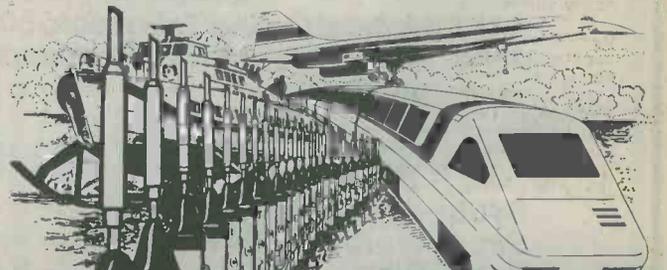

## The MIGHTY MIDGETS SOLDERING IRONS AND ACCESSORIES

	RETAIL PRICE (each inc. V.A.T.)	POSTAGE (extra)
<b>18 WATT IRON</b> FITTED WITH NO. 20 BIT AVAILABLE IN: 12V, 110V, or 240V	£4.95	28p
<b>SPARE BITS</b>	69p	—
<b>STANDS</b>	£4.49	80p
<b>SOLDER: SAVBIT 20'</b>	70p	12p
" 10'	40p	8p
<b>LOWMELT 10'</b>	80p	12p
<b>I.C. DESOLDERING BIT</b>	£1.27	12p
<b>BIT SIZES:</b>	NO. 19 (1.5mm) NO. 20 (3mm) NO. 21 (4.5mm) NO. 22 (6mm)	

From your Local Dealer or Direct from Manufacturers

## S & R BREWSTER LIMITED

86-88 UNION ST. PLYMOUTH PL1 3HG  
Tel: 0752 65011 TRADE ENQUIRIES WELCOME



PLEASE QUOTE YOUR NUMBER WHEN ORDERING

# RADIO & ELECTRONICS CONSTRUCTOR

## Single Copies

Price 60p each, p&p 18p

Issue(s) required . . . . .

## Annual Subscription

Price £9.50 inland, £10.50 overseas (including Eire)

post free, commence with . . . . . issue

## Bound Volumes:

Vol. 27.	August 1973 to July 1974	Price £3.00, post & pkg £1.30
Vol. 28.	August 1974 to July 1975	Price £3.20, post & pkg £1.30
Vol. 29.	August 1975 to July 1976	Price £3.50, post & pkg £1.30
Vol. 30.	August 1976 to July 1977	Price £3.70, post & pkg £1.30
Vol. 31.	August 1977 to August 1978	Price £5.20, post & pkg £1.30
Vol. 32.	September 1978 to August 1979	Price £5.50, post & pkg £1.30

## CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,  
maroon only

Price £2.25, post & pkg 50p

With no title on spine, maroon

Price £2.25, post & pkg 50p

With no title on spine, green

Price £2.25, post & pkg 50p

Prices include V.A.T.

## DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages

Price £1.20, P.&P. 27p

DB6 Radio Amateur Operator's Handbook,

New edition in course of preparation

DB17 Understanding Television, 504 pages

Price £3.95, P. & P. £1.00

DB19 Simple Short Wave Receivers  
140 pages

Price 80p, P. & P. 27p

## STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording - White

- 6 sheets

Price £1.50, P. & P. 11p

Set 4: Wording - Black

- 6 sheets

Price £1.50, P. & P. 11p

Set 5: Dials

- 6 sheets

Price £1.50, P. & P. 11p

Prices include V.A.T.

I enclose Postal Order/Cheque for . . . . . in payment for . . . . .

NAME . . . . .

ADDRESS . . . . .

(BLOCK LETTERS PLEASE)

*Postal Orders should be crossed and made payable to Data Publications Ltd.*

*Overseas customers please pay by International Money Order.*

*All publications are obtainable through your local bookseller*

Data Publications Ltd., 57 Maida Vale, London W9 1SN

**PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS**

## TRUTH TABLES

Truth tables are employed to define the performance of logic circuits. With the commonly accepted positive logic, the figure "1" corresponds with a high (positive) voltage and the figure "0" to a low voltage.

In the symbol for the inverter, or NOT gate, of (a) the circle at the output indicates inversion. In the equation, the bar over A signifies NOT. The truth table below shows that the output is high when the input is low, and is low when the input is high.

The right hand side of the AND gate equation in (b) infers a multiplication between A and B. In Boolean algebra this indicates AND. The truth table shows that the output is high only when all inputs are high.

A NAND gate appears in (c). The performance is the same as the AND gate with the output inverted, so that the output is low only when all inputs are high.

An OR gate is shown at (d), and in the equation the plus sign signifies OR. The truth table shows that the output goes high when either one input goes high or both inputs go high. The output is low only when all inputs are low.

In (e) the device is a NOR gate. The output is the inverse of the OR gate output, and goes low when one or both inputs go high.

The gate in (f) is an exclusive-OR, or XOR gate. Its output goes high when one input goes high but goes low when both inputs are high. The equation states that the output equals (A and not-B) or (not-A and B).



$$Y = \bar{A}$$

A	Y
0	1
1	0



$$Y = AB$$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1



$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

(a)

(b)

(c)



$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

(d)



$$Y = \overline{A + B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

(e)



$$Y = AB + \bar{A}\bar{B}$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

(f)

# The new MAPLIN CATALOGUE is out on December 5th

A massive new catalogue from Maplin that's bigger and better than ever before. If you ever buy electronic components this is the one catalogue you must not be without. Over 300 pages, it's a comprehensive guide to electronic components with thousands of photographs and illustrations and page after page of invaluable data. We stock just about every useful component you can think of. In fact, well over 5000 different lines, many of them hard to get from anywhere else. Hundreds and hundreds of fascinating new lines, more data, more pictures and a new layout to help you find things more quickly.

# MAPLIN

Maplin Electronic Supplies Ltd.  
All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR.  
Telephone: Southend (0702) 554155. Sales (0702) 552911.  
Shops:  
159-161 King Street, Hammersmith, London W6. Telephone: (01) 748 0926.  
284 London Road, Westcliff-on-Sea, Essex. Telephone: Southend (0702) 554000.  
Both shops closed Mondays.



On sale  
in all branches  
of W H Smith  
from Dec 5th  
price £1

**PLUS LOW PRICES**  
such as  
Resistors from 1½p  
Multimeters from £4.25  
Ni-Cads from £1.15  
Stereo Headphones from £3.49  
Radios from £2.95  
Over 300 Books  
21 Different ranges  
of capacitors, etc.,  
etc., etc.,

Post this coupon now for your copy of our 1981 catalogue price £1.

Please send me a copy of your 320 page catalogue. I enclose £1 (Plus 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.68 or 12 International Reply Coupons.

I enclose £1.25

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

REC181