

ANNUAL TELEVISION NUMBER

JANUARY 1952


RADIO - ELECTRONICS

LATEST IN TELEVISION • SERVICING • AUDIO

HUGO GERNSBACH, Editor

NEW MILITARY USE FOR TV

SEE TELEVISION SECTION

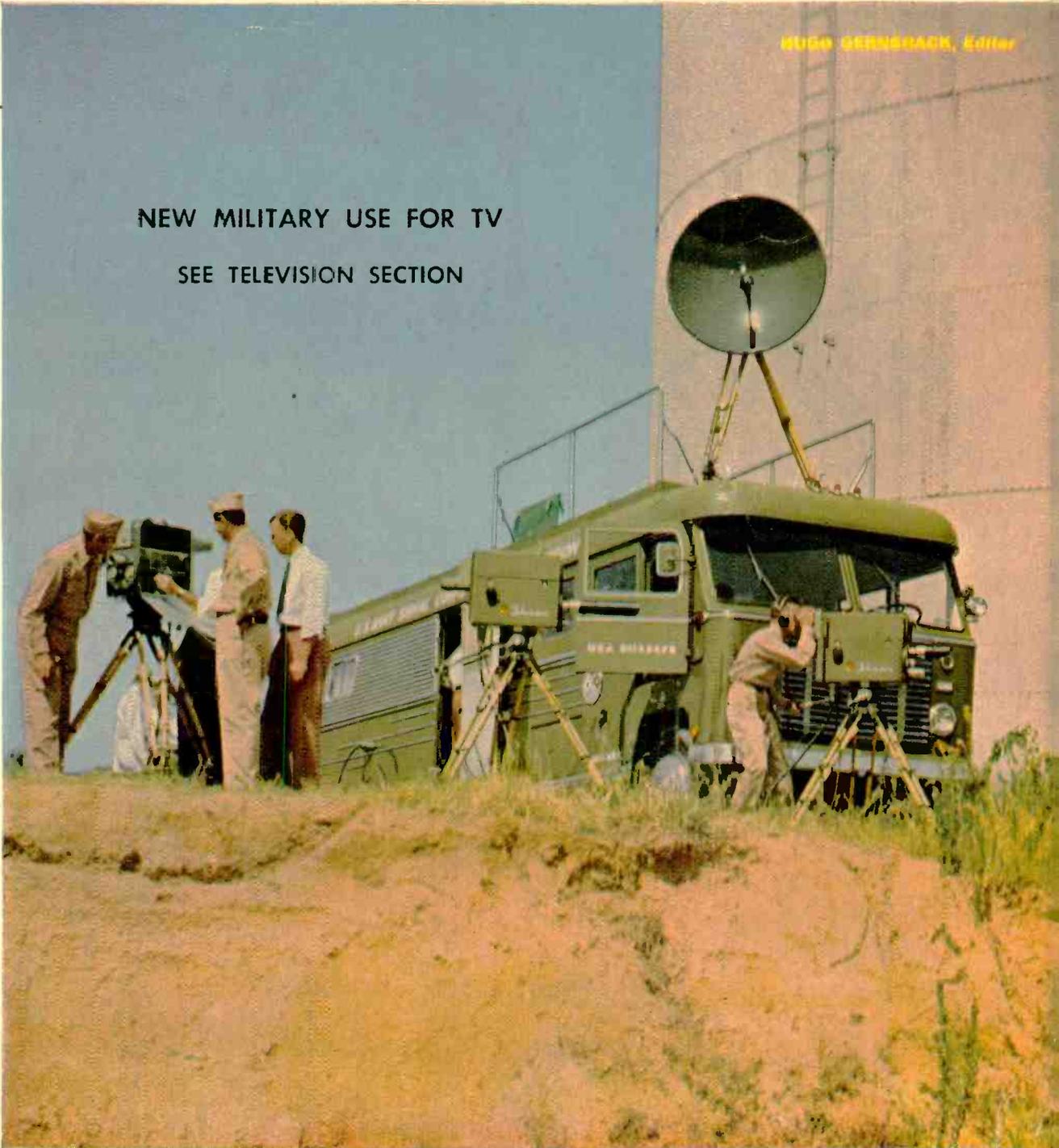


50¢
U.S. and
CANADA

***In this Issue:* TV receiver, antenna and booster directories
U.h.f. antennas • TV servicing articles**

guaranteed
for

6

months from date of installation

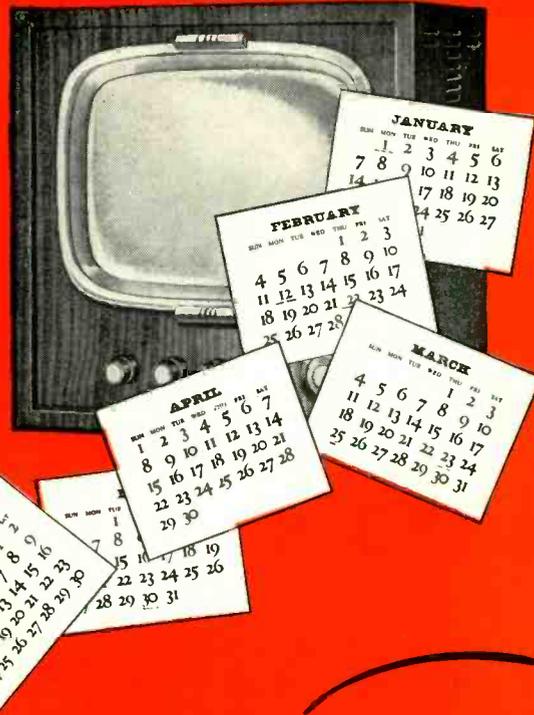

REGISTRATION
No. 10861

USER'S REGISTRATION

IMPORTANT

DUMONT
REPLACEMENT TELETRON WARRANTY

Teletron Serial Number _____
Purchased From _____ (Name of dealer) _____
User's Signature _____
Street Address _____
City _____

Teletron Type Number _____
On _____ (Date) _____
City _____
State _____
Teletron purchased for repair
replacement conversion replacement Indicate one.

USER—COMPLETE, SIGN AND MAIL THIS SECTION IMMEDIATELY AFTER YOUR PURCHASE. UNLESS YOU DO SO YOUR WARRANTY IS NOT VALID.

Write for complete information
on the Du Mont tube line.



Here is a warranty with sales appeal — with your customer participating in the registration of his Teletron. A series of three cards are supplied with each Teletron. One copy is retained by you, a second is retained by the set owner and the third is sent to Du Mont providing complete protection for the set owner for a period of six months from the date of installation against any defects in the Teletron.

* TRADE MARK

CATHODE-RAY TUBE DIVISION, ALLEN B. DU MONT LABORATORIES, INC., CLIFTON, N. J.

J. E. SMITH,
President,
National Radio
Institute,
Wash., D. C.

I Will Show You How to Learn RADIO-TELEVISION

by Practicing at Home in Spare Time




You Practice **SERVICING** with Equipment I Furnish

You build the modern Radio (at left) as part of my Servicing Course. I send you speaker, tubes, chassis, transformer, loop antenna, everything you need. You use it to make many tests, get practical experience you need to make EXTRA money fixing Radios. I send you many other kits of parts with which you build other circuits common to Radio and Television, some of which are pictured on the next page. All equipment is yours to keep. See and read about them in my FREE 64-PAGE BOOK. Mail card below.



You Practice **COMMUNICATIONS** with Equipment I Furnish

As part of my Communications Course I send you kits of parts to build the low power broadcasting transmitter shown at the right and many other circuits common to Radio and Television. You use this equipment to get practical experience putting a station "on the air," performing procedures demanded of Broadcast Station operators. I train you for your FCC Commercial Operator's License that puts you in line for good pay in Radio or Television Broadcasting. Mail card below.

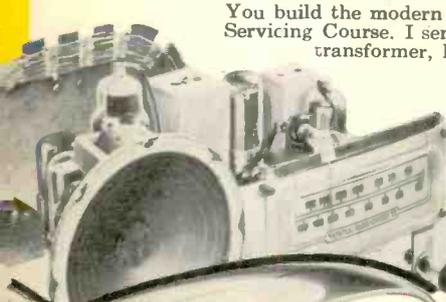

NEW! Advanced Television Practice!

New, special TV kits furnished to build high-def. monitor SCOPE... RF OSCILLATOR with flyback power supply... complete TV SET... many other units. You see pulse, trapezoidal, saw-tooth wave forms. Get valuable PRACTICAL EXPERIENCE locating and correcting TV troubles. Mail coupon for facts, pictures and prices!

CUT OUT AND
MAIL CARD
NOW!

SEE OTHER SIDE THE TESTED WAY
TO BETTER PAY

NO POSTAGE NEEDED

Both FREE



Sample Lesson & 64-Page Book

ACT NOW! Send for my DOUBLE OFFER FREE. This card entitles you to Sample Lesson on Servicing; shows how you learn Radio-Television at home. You'll receive my 64-page Book, "How To Be a Success in Radio-Television." Mail card now! No postage needed. J. E. SMITH, President, National Radio Institute, Washington 9, D. C. Our 38th year.

Mr. J. E. SMITH, President, Dept. 2 ARR
National Radio Institute, Washington 9, D. C.

Mail me Sample Lesson and 64-Page Book, "How to Be a Success in Radio-Television." (No Salesman will call. Please write plainly.)

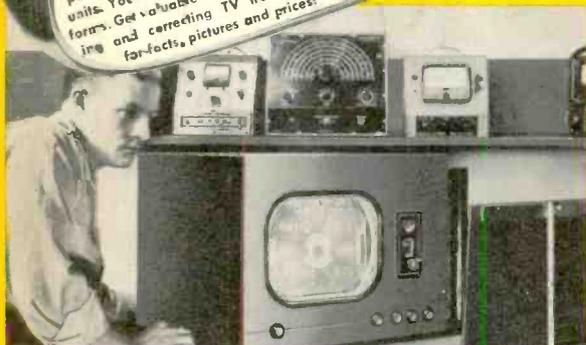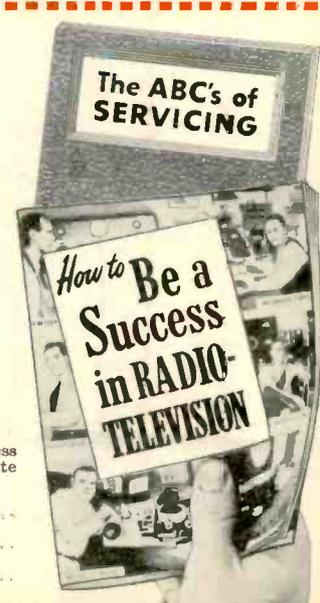NAME AGE.....
ADDRESS.....
CITY.....ZONE.....STATE.....



Television Is Today's Good Job Maker

In 1946 only 6,000 TV sets sold. In 1950 over 5,000,000. By 1954, 25,000,000 TV sets estimated. Over 100 TV Stations now operating. Authorities predict 1,000 TV Stations. This means more jobs, good pay for properly trained men. Mail this Postage-Free card NOW for FREE book and sample lesson.

BE A RADIO-TELEVISION TECHNICIAN

Train at Home in Spare Time



J. E. SMITH, President,
National Radio Institute,
Washington, D. C.

There's a Bright Future For You In America's Fast Growing Industry

Do you want good pay, a job with a bright future and security? Would you like to have a profitable shop or store of your own? If so, find out how you can realize your ambition in the fast growing RADIO-TELEVISION industry. Even without Television, the industry is bigger than ever before. 90 million home and auto Radios, 3,100 Broadcasting Stations, expanding use of Aviation and Police Radio, Micro-Wave Relay, Two-Way Radio for buses, taxis, etc. are making opportunities for Servicing and Communications Technicians and FCC Licensed Operators.

You Learn by Practicing with Kits I Furnish

With both my Servicing Course and my NEW Communications Course I send you many Valuable Kits of Parts. They "bring to life" theory you learn in my

illustrated texts. Some equipment from both courses is shown below and on previous page. All equipment I send is yours to keep. Among equipment you build is a Tester. Use it to make extra money fixing neighbors' sets while training. Special booklets show you how.

Training Features Television

Both my Servicing and Communications training include up-to-date lessons on TV principles. Throughout the country my graduates are filling jobs, making good money in both Radio and Television. Remember the way to a successful career in Television is through experience in Radio.

Send NOW for 2 Books FREE— Mail Card

Send the Postage-Free card now for my FREE DOUBLE OFFER. You get Sample Servicing Lesson to show you how you learn at home. Also my 64-page book, "How to Be a Success in Radio-Television." Read what my graduates are doing, earning; see equipment you practice with at home. Mail card now. We pay postage. J. E. SMITH, President, National Radio Institute, Washington 9, D. C. Our 38th Year.

Read What Successful NRI Graduates Say:



Radio Operator with ABC

"I was a bookkeeper with a hand-to-mouth salary. Now, a Radio Operator." — N. H. Ward, Ridgefield Park, N. J.



Can Step Into FM, Television

"When I enrolled with N.R.I., was a laborer. Now I have a position paying over \$10 a day." — R. Ford, Phila., Pa.



Is Broadcasting Operator

"Now employed at station WHAW as operator. I have also opened my own Radio business." — R. J. Bailey, Weston, W. Va.



\$10 Week In Spare Time

"Before finishing your course, I earned \$10 a week in Radio servicing in my spare time." — S. J. Pet-ruff, Miami, Fla.



\$10 to \$15 Week Spare Time

"4 months after enrolling averaged \$10-\$15 a week spare time servicing Radios. Now have business." — W. B. Weyde, Brooklyn, N. Y.



Lost Job, Now Has Own Shop

"Got laid off. Best thing that ever happened as I opened a Radio shop." — E. T. Slate, Corsicana, Texas.

Make Extra Money While Learning

Keep your job while training. Learn Radio-Television principles from illustrated lessons. Get Practical Experience experimenting with circuits common to Radio and Television. Many students make \$5, \$10 a week extra fixing neighbors' Radios in spare time while learning. I send you special booklets that start teaching you the day you enroll.



IMPORTANT!
See Other Side

**Extra Pay in Army,
Navy, Air Force**
Knowing Radio, TV, Electronics can help you get extra rank, extra prestige, more interesting duty at pay up to several times a private's base pay. You are also prepared for good Radio-TV jobs upon leaving service. Mail Coupon NOW.

You Build These and many more for Practical Experience



MAIL POSTAGE FREE CARD TODAY

Want Your Own Business?



Let me show you how you can be your own boss. Many N.R.I.-trained men start their own business with capital earned in spare time. Robert Dohmen, New Prague, Minn., whose store is shown at right, says, "Am now tied in with two television outfits and do warranty work for dealers. Often fall back to N. R. I. textbooks for information on installing Television sets."

FIRST CLASS
Permit No. 20-R
(Sec. 34.9 PL & R)
Washington, D. C.


BUSINESS REPLY CARD

No Postage Stamp Necessary If Mailed In The United States

4c POSTAGE WILL BE PAID BY
NATIONAL RADIO INSTITUTE

16th and U Sts. N. W.

Washington 9, D. C.

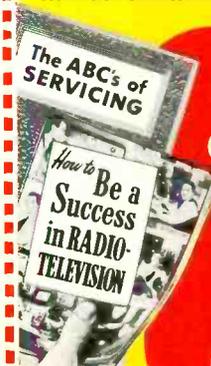

**SAMPLE LESSON
and 64-PAGE BOOK
Both FREE**

Cut out and mail
postage-free card now!

Be Sure of Your Installations . . .


Use

Aptitude-Tested

MULTIPLE CONDUCTOR CABLE

• You know what you are doing when you use Belden Multiple Conductor Cables — they're aptitude rated. They are designed to provide desirable electrical characteristics, and rigid control assures constant quality.

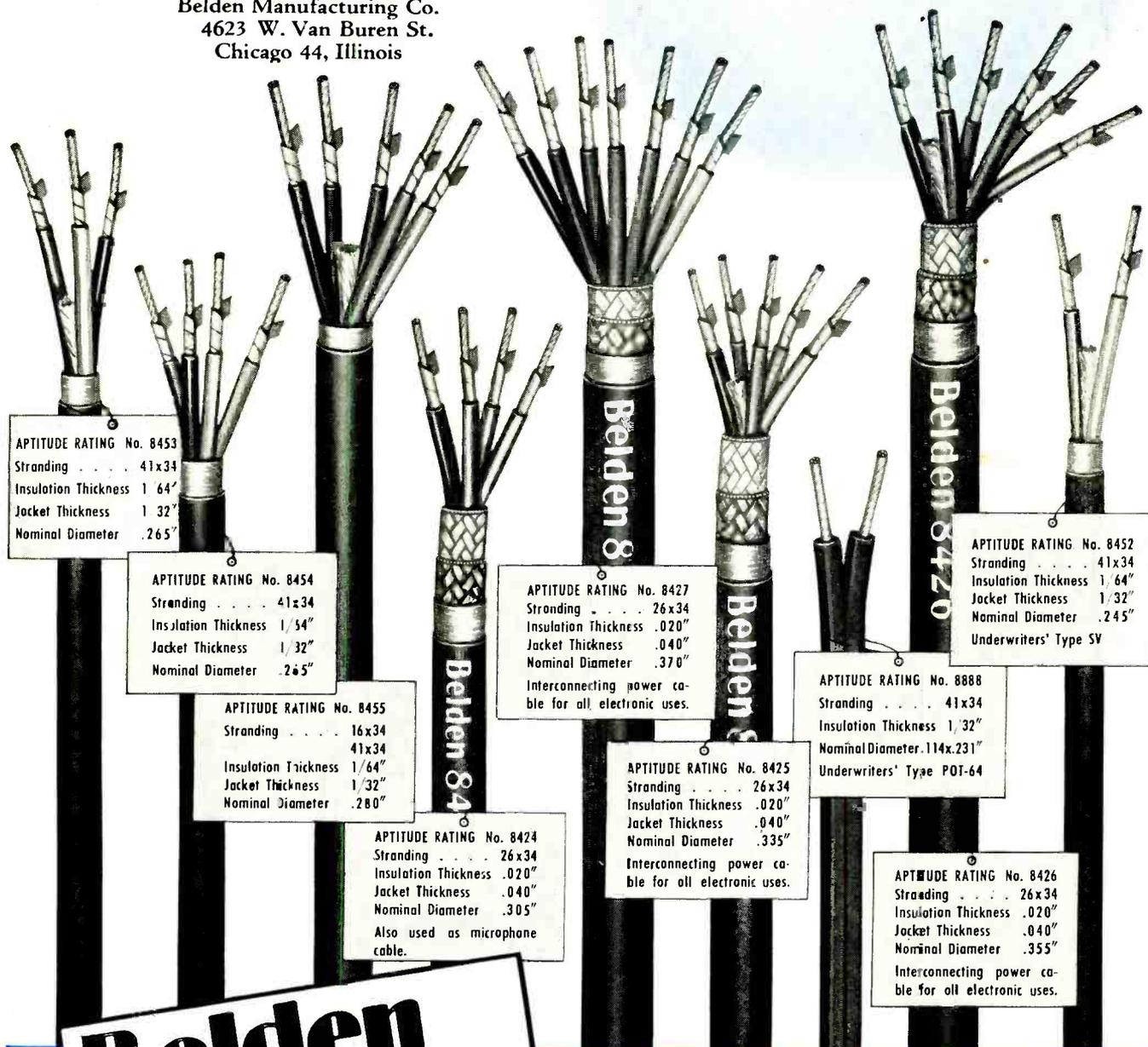Specify Belden Radio Wires.
Belden Manufacturing Co.
4623 W. Van Buren St.
Chicago 44, Illinois



Belden Radio WIRE

The Aptitude-Tested LINE

RADIO - ELECTRONICS

Formerly RADIO-CRAFT • Incorporating SHORT WAVE CRAFT • TELEVISION NEWS • RADIO & TELEVISION*

Hugo Gernsback,
Editor-in-Chief

M. Harvey Gernsback
Editorial Director

Fred Shunaman
Managing Editor

Robert F. Scott
W2PWG, Technical Editor

I. Queen
Editorial Associate

Angie Pascale
Production Manager

Wm. Lyon McLaughlin
Tech. Illustration Director

Lee Robinson
General Manager

John J. Lamson
Sales Manager

G. Aliquo
Circulation Manager

Robert Fallath
Promotion Manager

ON THE COVER:

The television truck designed to increase the number of students who might be able to "see" a military problem under actual field conditions. (Color photo courtesy of RCA.)

CONTENTS

JANUARY 1952

Editorial (Page 25)

Television at the Crossroads.....by Hugo Gernsback 25

Television (Pages 26-74)

Fair Weather Ahead.....by Raymond F. Guy 26
 Novel 1952 TV Circuits.....by Robert F. Scott 30
 TV Microwave Relay..... 33
 New Ideas in U.H.F. Antennas..... 34
 U.H.F. Reception on V.H.F. Receivers.....by Rudy Frank 36
 44-Mc I.F. Amplifiers for TV.....by David T. Armstrong 38
 TV Dx in 1951.....by Edward P. Tilton 40
 New Military Use for TV (Cover Story)..... 43
 The Toughest Customer.....by Guy Slaughter 44
 TV Distribution System..... 47
 Fringe Area Performance.....by Edward M. Noll 48
 New Idea in TV Antennas..... 49
 Servicing Horizontal Locks.....by Matthew Mandl 50
 Television Service Clinic.....Conducted by Matthew Mandl 52
 TV Distribution Amplifier.....by Edwin Bohr 54
 630 to 17 Inches.....by T. E. Cantor 56
 Picture Tube Replacement Guide.....by E. Wm. Scott 58
 Television Antenna Products Directory..... 60
 Boosters 62
 Directory of TV Receiver Characteristics..... 65

Audio (Pages 76-94)

Electronics & Music, Part XIX.....by Richard H. Dorf 76
 Remote Controlled Amplifier.....by Paul W. Streeter 86

Servicing—Test Instruments (Pages 98-118)

Multi-Unit Signal Generator.....by Joseph Marshal 98
 V.T.V.M. in PA Work.....by A. T. Parker 105
 Safety First & TV Antennas..... 116
 Use Wire Tables in Service Work.....Vergniaud H. Richard 117

Electronics (Pages 119-125)

Timer for Long Intervals.....by Fred Upton 119
 Electrostatic Precipitation.....by Ed Bukstein 121
 Counting Rate Instrument.....by I. Queen 125

Amateur (Pages 126-127)

Useful Phone—C. W. Monitor.....by John E. Pitts, W6CQP 126

New Design (Pages 133-134)

Tube of the Month..... 133
 Small, Chatter-proof Interruptor Meets Special Switching Needs..... 134

Departments

The Radio Month..... 12	New Patents..... 136	Technotes..... 150
Radio Business..... 16	Try This One..... 140	People..... 152
New Devices..... 95	Radio-Electronic Circuit..... 143	Miscellany..... 154
With the Technician..... 128	Question Box..... 147	Communications..... 158
		Book Reviews..... 159

MEMBER Audit Bureau of Circulations • *Trademark registered U.S. Patent Office

January, 1952

RADIO-ELECTRONICS

Vol. XXIII, No. 4

Published monthly by Radcraft Publications, Inc., at Erie Ave., F to G Streets, Philadelphia 32, Pa.

EXECUTIVE, EDITORIAL and ADVERTISING OFFICES: 25 West Broadway, New York 7, N. Y. Telephone REctor 2-8630. Hugo Gernsback, President; M. Harvey Gernsback, Vice-President; G. Aliquo, Secretary.

SUBSCRIPTIONS: Address Correspondence to Radio-Electronics, Subscription Dept., Erie Avenue, F to G Sts., Philadelphia 32, Pa., or 25 West Broadway, New York 7, N. Y. When ordering a change please furnish an address stencil impression from a recent wrapper. Allow one month for change of address.

SUBSCRIPTION RATES: In U. S. and Canada, in U. S. possessions, Mexico, South and Central American countries, \$3.50 for one year, \$6.00 for two years; \$8.00 for three years; single copies 30c. All other foreign countries \$4.50 a year, \$8.00 for two years; \$11.00 for three years. Entered as second class matter September 27, 1948 at the post office at Philadelphia, Pa., under the Act of March 3, 1879. Printed in U. S. A. Copyright 1951 by Radcraft Publications, Inc. Text and illustrations must not be reproduced without permission of copyright owners.

BRANCH ADVERTISING OFFICES: Chicago: 520 N. Michigan Ave. Telephone Superior 7-1796. Los Angeles: Ralph W. Harker, 1127 Wilshire Blvd., Tel. MA 6-1271. San Francisco: Ralph W. Harker, 582 Market St., Tel. GARfield 1-2481. FOREIGN AGENTS: Great Britain: Atlas Publishing and Distributing Co., Ltd., London E.C.4. Australia: McGill's Agency, Melbourne. France: Brentano's, Paris 2e. Holland: Trillectron, Heemstede. Greece: International Book & News Agency, Athens. So. Africa: Central News Agency, Ltd., Johannesburg. Capetown: Natal Universal Book Agency, Johannesburg. Middle East: Steimatzky Middle East Agency, Jerusalem. India: Broadway News Centre, Dadar, Bombay 711. K. L. Kannappa Mudalliar, Madras 2. Pakistan: Paradise Book Stall, Karachi 3.

POSTMASTER: If undeliverable send form 3578 to: RADIO-ELECTRONICS, 25 West Broadway, New York 7, N. Y.

RADIO-ELECTRONICS for

TRAIN

for Security! Good-Paying Jobs!

MAKE THE MONEY YOU'VE ALWAYS DREAMED OF!



You get all the parts—even tubes!— for this modern Superheterodyne Receiver. You learn to build it step by step. And you keep it! Get all the facts. Mail coupon now.

LEARN RADIO -TELEVISION

AND ELECTRONICS BY EASY SHOP METHOD TRAINING AT HOME!

Let **NATIONAL SCHOOLS**—a resident-training school for nearly 50 years—train you at home for today's unlimited opportunities in Radio-Television-Electronics. National Schools is one of the largest schools of its kind. It is located in Los Angeles—the center of Radio and TV world! It has four large buildings of modern shops and labs. Its faculty is considered top in the business.



You learn from lessons prepared by experienced instructors and engineers. Men who are successful Radio and Television technicians. Men who have trained 1000's of men like YOU!



FREE BOOK TELLS YOU HOW!

Page after page—in color—tells you everything you want to know. Mail the coupon. Get this valuable book today. And if you hurry—YOU GET A FREE SAMPLE LESSON, TOO! Shows how easy National Schools Home Training is. Mail the coupon today.

Today's Shortage of Trained Technicians Creates Chance of a Lifetime For You!

Think of it! With guided missiles, radar, and other electronic devices so important to national defense! With big, new developments in TV. With over 90,000,000 home and auto radios, over 12,000,000 TV sets. With more than 3100 radio stations...over 100 TV stations—and more building every day...yes, imagine the great opportunity you have today! YOU are wanted in Radio-Television-Electronics! America's fastest-growing field. High-pay jobs—the kind you've always wanted—are waiting for YOU!

Job Security! Big Money! For YOU! in Today's Expanding Industries!

Trained Radio and Television technicians really make important money these days. Thousands of National Schools graduates—men just like you—are earning good money all over the country. Why not you? And—National Schools graduates get the personal satisfaction of being highly-skilled technicians. Men people respect. Men who enjoy their work—rather than having to drag along in just any old job.

National Schools Has Trained 1000's of Successful Men! Why Not YOU?

In almost every state—and many foreign countries—National Schools graduates are filling big jobs with famous companies. Or running their own successful businesses. What are YOU waiting for? National Schools training is complete training. So when you graduate you can take advantage of today's big opportunities in Radio-Television-Electronics—fast.


You Train At Home—In Your Spare Time

National Schools Shop Method Home Training gives you basic and advanced instruction in all phases of Radio-TV-Electronics. And remember—your training is based on resident school training principles. You learn fast from hundreds of diagrams and pictures. All instructions are written by experienced technicians who work in Radio and TV every day. All instructions have been developed and tested in National Schools' own labs and studios, which are equipped with the latest RCA equipment. No wonder this National Schools course is so up-to-date, practical, interesting. And so easy to learn! And no wonder it is held in such high regard by leaders of American industry! Approved for eligible Veterans.

We Teach You How To Make Welcome Extra Money—While You Learn!


Many National Schools students—men like you—make plenty of extra dollars each week in spare time! Fixing neighbors' radios, appliances—and other ways we teach you. You start learning and earning from the day you enroll. From the very first lesson!

WE SEND YOU LOTS OF PARTS LIKE THIS!

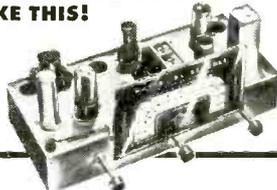

With National Schools Shop Method Home Training, you get basic principles and plenty of practical training. You learn by doing. No wonder you learn so fast! We send you many parts—all of professional, modern quality. You do lots of practical experiments. You advance day by day, step by step. Until you can even build the modern Superheterodyne Receiver you see above—plus other important testing units. The free book tells you all about it. The free sample lesson shows how easy the training is. Use the coupon. Send today—without fail!

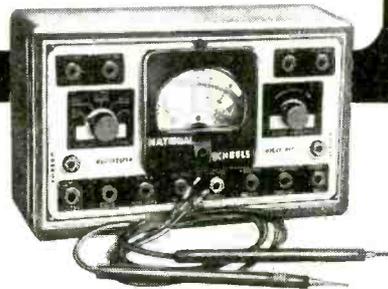DON'T PUT IT OFF! GET THE BIG SALARY YOU HAVE ALWAYS WANTED!



Only National Schools Gives You This Professional Multi-Tester!

You get this amazing, new testing instrument—factory-made and tested—complete—ready to use! Simple to operate. Accurate and dependable. An instrument every Radio-TV man needs. Light enough to carry around—so you can use it at home or on service calls. You'll be proud to own this valuable equipment.

Here are only a Few of the Good-Paying Jobs You Can Choose

Radio Station Engineer, District Service Manager, Aircraft Radio Inspector, Own Your Own Repair Shop, Inspector Technician, Service Specialist, Special Government Jobs, Complete TV Service, Sound Truck Operator. Many more! National Schools graduates have secure, good-paying jobs like these! So don't wait—mail the coupon today. Now—while you're thinking about it!

Attention! Men Going into Service Soon!

National Schools' course quickly prepares you for many important jobs in the Armed Services. With National Schools Training you have an opportunity to get into special service classifications—with higher pay and grade—immediately!

FREE SERVICE FOR GRADUATES

National Schools uses its great influence and prestige to help you find your place in the field of your choice. Don't put it off! Start yourself toward a skilled trade! Get the big pay you've always wanted!

NATIONAL SCHOOLS

LOS ANGELES 37, CALIFORNIA • ESTABLISHED 1905

MAIL THIS COUPON TODAY—WITHOUT FAIL!

NATIONAL SCHOOLS, Dept. GR-12
4000 South Figueroa Street
Los Angeles 37, California

Mail in envelope or paste on penny post card.

Mail me FREE the book mentioned in this ad. Also a free sample lesson. I understand no salesman will call on me.

NAME _____ AGE _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Check here if you were released from the Service less than 4 years ago.



**A SERVICE DEALER
IS ONLY AS GOOD AS
HIS WORK**



Today's wary customers are more interested in the *business ethics* of a Television and Radio Service Dealer than they are in his *technical ability*.

They look for a Service Dealer who will treat them fairly, a Service Dealer whose guarantee is sound, and then take it for granted that the results will be satisfactory.

The RAYTHEON *Bonded* Electronic Technician Pro-

gram gives customers just what they are looking for. If you can qualify as a Raytheon *Bonded* Electronic Technician your 90-day guarantee on service and parts is cash-protected by a *bond* issued by the American Mutual Liability Insurance Company. You are presented with a Registered Bond Certificate, Creed Displays and Identification Cards all featuring an 8-point Code of Ethics that will convince the most skeptical customers of your integrity and ability.



Back up your business with the Raytheon *Bond*. Ask your Raytheon Tube Distributor if you qualify for this exclusive business asset. It's yours *at no cost*, if you can.

RIGHT... FOR SOUND AND SIGHT®




RAYTHEON MANUFACTURING COMPANY

Receiving Tube Division,
Newton, Mass., Chicago, Ill., Atlanta, Ga., Los Angeles, Calif.

Excellence in Electronics

RECEIVING AND PICTURE TUBES • RELIABLE SUBMINIATURE AND MINIATURE TUBES • GERMANIUM DIODES AND TRANSISTORS • RADIAC TUBES • MICROWAVE TUBES

RADIO-ELECTRONICS for

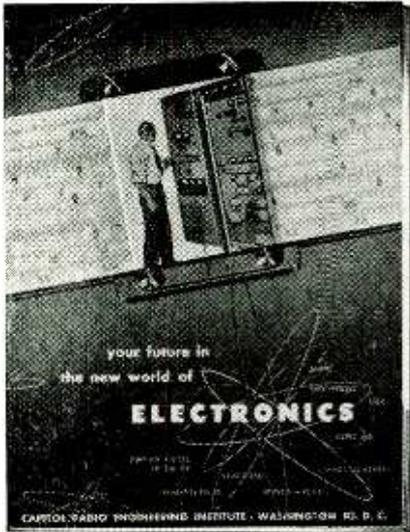

*How far ahead can you be
next year . . .*

IN TV AND ELECTRONICS?

◀ **Send for this free CREI booklet today . . .
and find out!**

This booklet can mean the difference between small, w-i-d-e-l-y s-p-a-c-e-d salary increases—and rapid advancement. Between routine work—and challenging opportunity. Between constantly defending your job against better-trained men—and dynamic confidence. Between short-circuited hopes—and high-powered ambition.

An exciting new world has opened up with such super-speed that even the most optimistic electronic experts fall short in their predictions of expansion.

Think of the 1,500 TV stations within the next 5 years and the 2,500 stations within 10 years, as predicted by the Chairman of the FCC. Think of the 14,496,000 TV sets now in use. *Remember that we weren't supposed to reach that figure until 1954.* Think of the 100,000,000 radios in current operation. (95% of the nation's homes have one or more sets.) Think of the tremendous defense orders now being placed for electronic equipment and installations.

Think of the thousands of radio-equipped fire and police departments throughout the U.S. Of the many radio-equipped railroads, of the hundreds of cities with 2-way radio service for cars and cabs. Think of the wide-ranging field of aviation communications—radio-controlled aircraft, navigation-and-traffic control, airport stations.

Think of the maritime world with its navigational aids, fathometers, ship-to-shore and ship-to-ship communications and radar. Think of electronic heating, fax and ultra-fax, of electronic medicine, and all the other applications of electronic know-how.

Countless positions must be filled—in development, research, design, production, testing and inspection, manufacture, broadcasting, telecasting and servicing. Who will get those positions? You—if you prepare today—if you are alert and have the ambition to advance your knowledge. You—if you take 2 minutes to send for a free copy of "Your Future in the New World of Electronics."

This helpful book shows you how CREI Home Study leads the way to greater earnings through the inviting opportunities described above.

However, being an accredited technical school, CREI does not promise you a "bed-of-roses." You have to translate your willingness to learn into saleable technical knowledge

—via *study*. Since its founding in 1927, CREI has provided thousands of professional radiomen with technical educations. During World War II, CREI trained thousands for the Armed Services. Leading firms choose CREI courses for group training in electronics at company expense, among them United Air Lines, Canadian Broadcasting Corporation, Trans Canada Airlines, Sears Roebuck & Co., Bendix Products Division, All-American Cables and Radio, Inc., and RCA-Victor Division.

CREI courses are prepared by recognized experts, in a practical, easily-understood manner. You get the benefit of time-tested materials, under the personal supervision of a CREI Staff Instructor. This complete training is the reason why CREI graduates find their diplomas keys-to-success in Radio, TV and Electronics. CREI alumni hold top positions in America's leading firms.

At your service is the CREI Placement Bureau, which finds positions for students and graduates. Although CREI does not guarantee jobs, requests for personnel currently exceed supply by far.

Talk to men in the field and check up on CREI's high standing in electronics instruction. Determine for yourself right now that your earnings are going to rise with your knowledge—and that you get your rightful place in the Age of Electronics. All this CREI can promise you, provided you sincerely want to learn. Fill out the coupon and mail it today. We'll promptly send you your free copy of "Your Future in the New World of Electronics." The rest—the future—is up to you.

MAIL COUPON FOR FREE BOOKLET

CAPITOL RADIO ENGINEERING INSTITUTE
 Dept. 141D, 16th & Park Rd., N.W., Washington 10, D. C.
 Send booklet "Your Future in the New World of Electronics" and course outline.

CHECK TV, FM & Advanced AM Servicing Aeronautical Radio Engineering
FIELD OF Practical Television Engineering
GREATEST Broadcast Radio Engineering (AM, FM, TV)
INTEREST Practical Radio Engineering

Name.....
 Street.....
 City..... Zone..... State.....
 If residence school in Wash., D. C. preferred, check here

NO MATTER HOW YOU LOOK AT IT...



the **TURNER** is a better **BOOSTER!**

From every angle the new Turner Model TV-1 Booster is the finest on the market today. Under the worst possible fringe area receiving conditions, the TV-1 consistently produces sharper, clearer pictures and crisper, more natural sound.

There are many reasons for the superiority of the Turner Booster, but the two most important are advanced electronic engineering and finest construction using only high quality component parts.

Turner's low-noise-level cascode circuit stabilizes the picture, reduces noise and snow to a minimum... makes viewing a real pleasure.

The Turner TV-1 is simple in operation. A single tuning knob permits fine adjustment for the best reception of picture and sound over all 12 TV channels. And because it tunes continuously from 54 to 216 megacycles, you can use the TV-1 to amplify FM, aviation and mobile radio signals. Three position control switch turns on the TV set only, the TV set and Booster, or shuts off both set and Booster.

The unit is quickly and easily installed. Attaches to any television set. Attractive styling and neutral finish harmonize with any furniture design.

CHECK THESE SUPERIOR FEATURES

Continuous Tuning - single knob control for finest adjustment to permit best possible reception of both picture and sound.

Cascode Circuit - inherent low noise level circuit with great stability and high signal-to-noise ratio.

Construction - finest quality materials carefully assembled to rigid Turner standards assure years of continuous, repair-free use.

Appearance - handsome cabinet designed to harmonize with any furniture design and finish.

Uses - amplifies FM, mobile and aviation radio signals as well as TV.

Results - most important, the Turner TV-1 produces an excellent picture under conditions which nullify the best efforts of many other boosters.

List Price\$57.50

FOR THE BEST POSSIBLE TV RECEPTION, TURN TO

THE **TURNER** **BOOSTER**

THE **TURNER** COMPANY, 933 17th Street, N. E. Cedar Rapids, Iowa

Toronto, Ont., and Branches
In Canada: Canadian Marconi Co.,

Export: Ad. Auriema, Inc.
89 Broad St., New York 4

RADIO-ELECTRONICS for

Want To Double Your Pay?



How To Pass **FCC** **COMMERCIAL** **RADIO OPERATOR** **LICENSE** **EXAMINATIONS**

**MONEY MAKING
FCC LICENSE
INFORMATION**

**TELLS HOW YOU CAN GET A
FREE TELEVISION
ENGINEERING
COURSE**

GET THIS AMAZING NEW BOOKLET FREE!

TELLS HOW—

WE GUARANTEE

TO TRAIN AND COACH YOU AT HOME
IN SPARE TIME UNTIL YOU GET
YOUR FCC LICENSE

If you have had any practical experience—Amateur, Army, Navy, radio repair, or experimenting.

TELLS HOW— Employers make
JOB OFFERS Like These
to Our Graduates Every Month!

Letter, October 11, 1951, from Chief Engineer, Broadcast Station, North Carolina. "Need men with radiotelephone 1st class licenses, no experience necessary. Will learn more than at average station for we are equipped with Diesel Electric power, transmitting and studio equipment".

Telegram, October 2, 1951, from Chief Engineer, Broadcast Station, Wyoming. "Please send latest list available first class operators. Have November 10th opening for two combo men".

Letter, October 8, 1951, from Chief Engineer, Broadcast Station, Texas. "Please send list of latest licensed graduates".

These are just a few examples of the job offers that come to our office periodically. Some licensed radioman filled each of these jobs . . . it might have been you!

HERE'S PROOF FCC LICENSES ARE OFTEN SECURED IN A FEW HOURS OF STUDY WITH OUR COACHING AT HOME IN SPARE TIME

Name and Address	License	Lessons
Lee Worthy 2210 1/2 Wilshire St., Bakersfield, Calif.	2nd Phone	16
Clifford E. Vogt Box 1016, Dania, Fla.	1st Phone	20
Francis X. Foerch 38 Beucler Pl., Bergenfield, N. J.	1st Phone	38
S/Sgt. Ben H. Davis 317 North Roosevelt, Lebanon, Ill.	1st Phone	28
Albert Schoell 110 West 11th St., Escondido, Calif.	2nd Phone	23

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
Desk RE-37, 4900 Euclid Bldg., Cleveland 3, Ohio

TELLS HOW—

Our Amazingly Effective JOB-FINDING SERVICE

Helps CIRE Students Get Better Jobs

Here are a few recent examples of Job-Finding results:

GETS CIVIL SERVICE JOB
"Thanks to your course I obtained my 2nd phone license, and am now employed by Civil Service at Great Lakes Naval Training Station as an Equipment Specialist." Kenneth R. Leiser, Fair Oaks, Md. Del., McHenry, Ill.

GETS STATE POLICE JOB
"I have obtained my 1st class ticket (thanks to your school) and since receiving same I have held good jobs at all times. I am now Chief Radio Operator with the Kentucky State Police." Edwin P. Healy, 264 E. 3rd St., London, Ky.

GETS BROADCAST JOB
"I wish to thank your Job-Finding Service for the help in securing for me the position of transmitter operator here at WCAE, in Pittsburgh." Walter Koschik, 1442 Ridge Ave., N. Braddock, Pa.

GETS AIRLINES JOB
"Due to your Job-Finding Service, I have been getting many offers from all over the country, and I have taken a job with Capital Airlines in Chicago, as a Radio Mechanic." Harry Clare, 4537 S. Drexel Blvd., Chicago, Ill.

OURS IS THE ONLY HOME STUDY COURSE WHICH SUPPLIES FCC-TYPE EXAMINATIONS WITH ALL LESSONS AND FINAL TESTS.

Your FCC Ticket is always recognized in all radio fields as proof of your technical ability.



MAIL COUPON NOW

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
Desk RE-37—4900 Euclid Bldg.
Cleveland 3, Ohio
(Address to Desk No. to avoid delay.)

I want to know how I can get my FCC ticket in a minimum of time. Send me your FREE booklet, "How to Pass FCC License Examinations" (does not cover exams for Amateur License), as well as a sample FCC-type exam and the amazing new booklet, "Money-Making FCC License Information."

Tell me how I can get your Free Television Course.

Name

Address

City Zone State

Paste on penny postcard or send air mail.

MERIT

TV full-line* Components For
Improvement, Replacement, Conversion



SELL IMPROVED RECEPTION

MERIT "TV" Kit #1000 for edge to edge focus—contains MFD-70 Cosine Yoke, HVO-7 Universal Flyback and MWC-1 Width Linearity Control. Keep a Kit handy—you'll get plus business and a reputation for "know-how."



MFD-70... original of the "cosine" series—low horz. high vert inductance. Used by such famous sets as Radio Craftsman. Cosine Yokes will improve 19,000,000 sets now in use!

MERIT... HQ for TV Service Aids

MERIT's 1952 Catalog #5211 now available... introducing MERIT IF-RF Coils, includes Coil & Transformer data, listings. Other MERIT service aids: TV Repl Guide #404, Sept. '51 issue—covers 3000 models, chassis of 82 mfrs; Cross Ref Data on IF-RF Coils, Form #14. Write: Merit Coil and Transformer Corporation, 4425 North Clark Street, Chicago 40.

These three MERIT extras help you:

• Exclusive: Tape-marked with specs and hook-up data



• Full technical data packed with every item

Listed in Howard Sams Photo-facts



*Merit is meeting the TV improvement, replacement and conversion demand with a line as complete as our advance information warrants!

BURTON BROWN ADVERTISING

IRE ELECTED Dr. Donald B. Sinclair as president, and Harold L. Kirke, vice-president for the 1952 term.

Dr. Sinclair is noted for his work in the development of high-frequency measuring instruments. He received the President's Certificate for merit for outstanding services during World War II for his work in the guided missile division of the National Defense Research Committee.

Harold L. Kirke is currently the assistant chief engineer of the British Broadcasting Corp. His election to office maintains the traditional recognition of the international nature of the Institute's membership and activities.

The newly elected directors are John D. Ryder, professor and head of the electrical engineering department of the University of Illinois, and Ernst Weber, professor and head of the electrical engineering department of the Polytechnic Institute of Brooklyn.

Regional directors elected for the new term are: Region 1, Glenn H. Browning, president of Browning Laboratories; Region 3, Irving G. Wolff, director of the Radio Tube Research Laboratory, RCA Laboratories Division; Region 5, Alois W. Graf, patent lawyer, Region 7, Karl Spangenburg, professor of electrical engineering.

IRE AWARDS for 1952 will be conferred upon a number of noted men for outstanding contributions in the diversified field of radio technology: Dr. William Shockley, of Bell Telephone Laboratories, will be awarded the Morris Liebmann Memorial Prize "in recognition of his contributions to the creation and development of the transistor." B. D. Loughlin, of Hazeltine Electronics Corporation, will receive the Vladimir K. Zworykin Television Prize Award for outstanding technical contributions toward fully electronic television. H. W. Welch, Jr., research physicist at the University of Michigan, will receive the Browder J. Thompson Memorial Prize for the best combination of technical contribution and presentation in his paper entitled "Effects of Space Charge on Frequency Characteristics of Magnetrons." Jerome Freedman, of Watson Laboratories, Griffis Air Force Base, will be granted the Editor's Award for good English in technical writing in his paper "Resolution in Radar Systems."

Presentation of the awards will be made by the president at the IRE Annual Banquet at the Waldorf-Astoria during the 1952 IRE National Convention in New York City on March 3 to 6.

A LIGHT AMPLIFIER is television's greatest present need, according to David Sarnoff. Speaking at a gathering commemorating his 45th year of service in radio and renaming the RCA Laboratories at Princeton "the David Sarnoff Research Center," General Sarnoff said: "... an electronic amplifier of light will do for television what the amplifier of sound does for radio broadcasting. ... An amplifier of sound gave

radio a loudspeaker, and an amplifier of light would give television a 'big-looker.'"

Two other needed inventions, he said, are a television recorder that would record the video signals of television on an inexpensive tape, and an electronic air-conditioner for the home that would operate with tubes, or possibly through the action of electrons in solids, and without moving parts.

General Sarnoff requested that the three inventions, which he called *Magnalux*, *Videograph*, and *Electronair*, be developed by scientists of the Research Center by the time of his 50th anniversary in radio, in 1956.

A TV CODE OF ETHICS has been formulated by the members of NARTB (The National Association of Radio and Television Broadcasters). Representatives of 61 TV broadcasters throughout the nation accepted and recommended for adoption by the directors of NARTB a set of guiding principles or code governing: acceptability, presentation, and the time allocation of advertising; acceptability of program material and decency in its production; coverage and treatment of news events; time for religious programs and requests for time for airing views on controversial issues.

A Television Code Review Board of six members will be established upon ratification of the code. Five members of the Review Board shall be selected from the NARTB membership with Judge Justin Miller, chairman of the board of directors, serving as ex-officio member.


NOVICE, TECHNICIAN HAMS

have been authorized to join the Military Amateur Radio System (MARS). The prospective member must either be in the Armed Services or Reserves, or a civilian 21 years or older and possessing the necessary equipment to operate on the military frequency of 3497.5 kc. He must operate (while on the MARS frequency) at such time and in such manner as the MARS Command Director may direct, and using the special military call signs assigned to him. The Army and Air Force jointly determine MARS policy but operational procedures are separate. Hams desiring more information are invited to write to MARS Headquarters (Army, Office of the Chief Signal Officer; Air Force, Director of Communications, AF), Washington 25, D. C.

A TV PACT affecting the assignment of channels along the U.S.-Mexican border has been concluded after two years of negotiations between the two countries. The assignment plan agreed that stations within 250 miles of the border were not to exceed an effective radiated power of 100 kilowatts for the lower band and 200 kilowatts for the upper band. The assignments which would be affected under the assignment plan are: (in the United States) Arizona, 15; California, 10; Nevada, 5; New Mexico, 10; Texas, 23; (in Mexico) Baja California, 16; Chihuahua, 7; Coahuila, 11.

RADIO-ELECTRONICS for

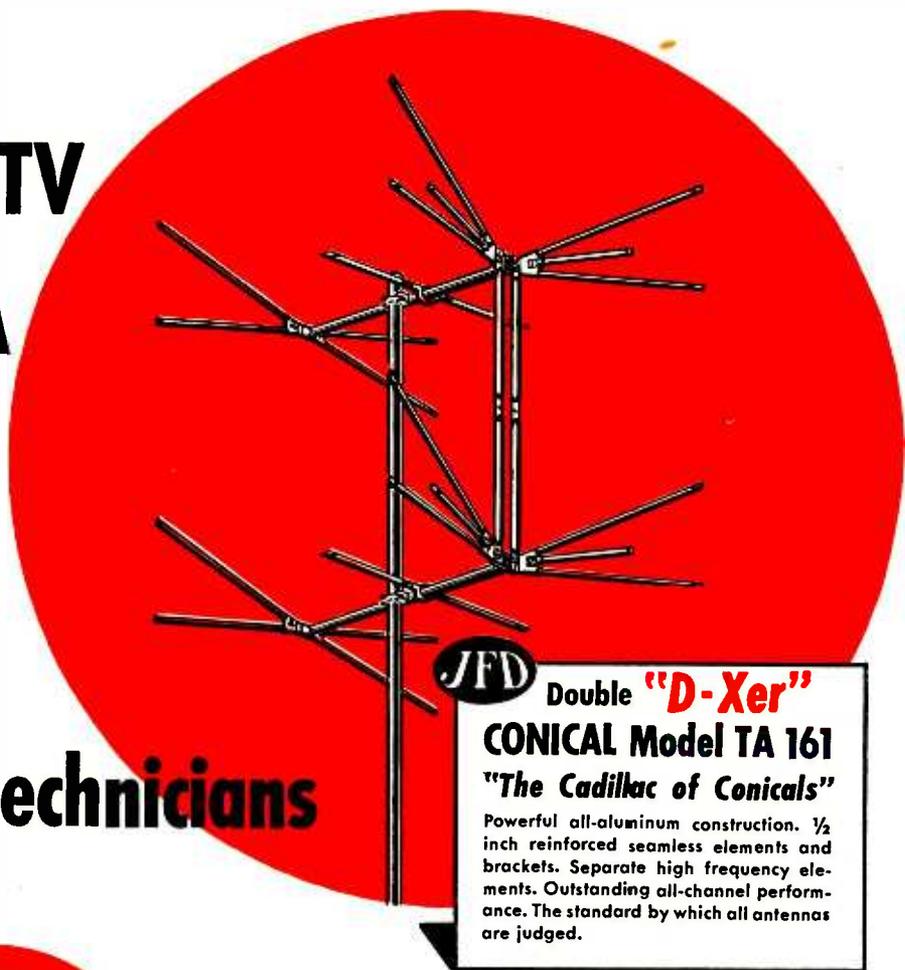
**For the right TV
ANTENNA
to fit the
Location and
the Need....
Installation Technicians
Prefer—**



JFD Double **"D-Xer"**
CONICAL Model TA 161
"The Cadillac of Conicals"
Powerful all-aluminum construction. 1/2 inch reinforced seamless elements and brackets. Separate high frequency elements. Outstanding all-channel performance. The standard by which all antennas are judged.



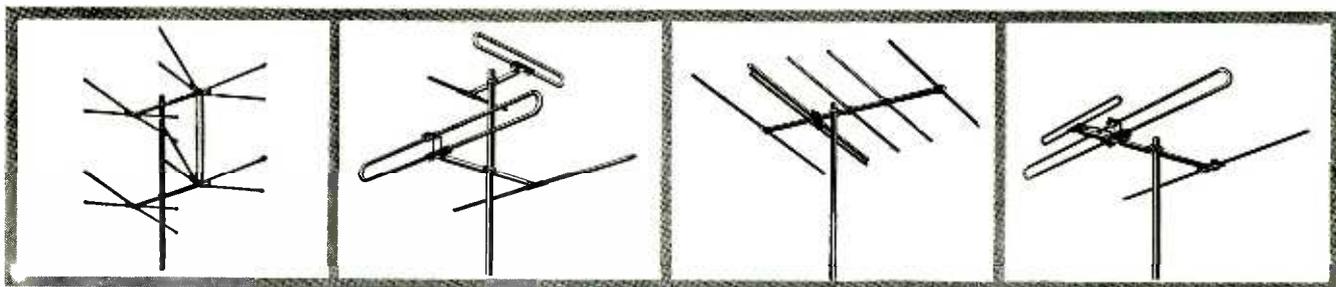**Emblem of Performance
and Profit Leadership!**




JFD "Commandair" Stacked Conical. More than ever before... The lowest-priced, highest-value conical on the market. Model C661 series.

JFD "Plug-In" HiLo Folded Dipoles array. The fastest selling antenna in its class! Model PL5 series.

JFD 5-Element "Corsair" Low-Band Yagi. Pre-assembled. Super-high gain! Model 5Y2-13 series.

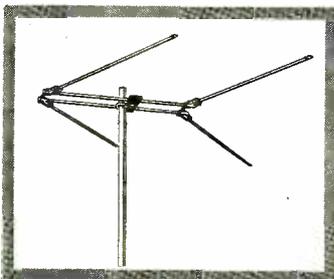JFD "Plug-In" Inline Array. Built to outlast! Designed to outperform! Model PL150 series.




JFD "Vee-Beam" Antenna. Setting new performance records! Model C800 series.

The Most Widely Demanded Line In The Country!

Send today for complete catalog No. 68G. Dept. 01



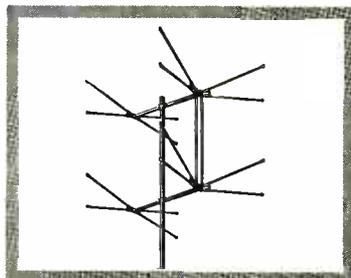MANUFACTURING CO., Inc.
6129 16th Avenue, Brooklyn 4, N. Y.




JFD "Commandair Special" . . . Greatest value in aluminum conical history! Model C261 series.

FIRST IN TELEVISION ANTENNAS AND ACCESSORIES.

TUNG-SOL[®]

for
Uniformity
and
Dependability

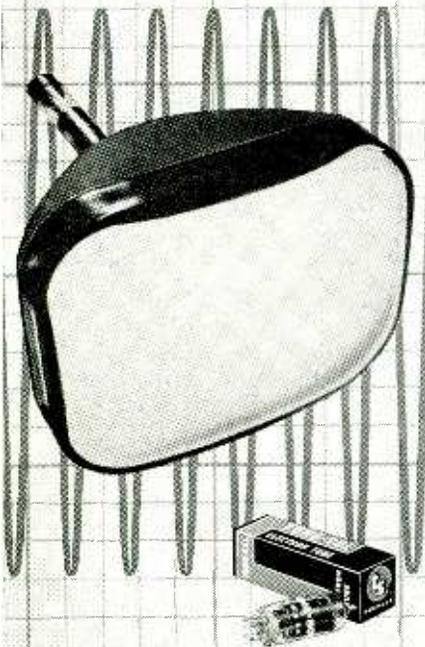

REPLACEMENT:

Tung-Sol tubes keep service standards up to set manufacturers' specifications.

INITIAL EQUIPMENT:

Tung-Sol tubes meet the highest performance requirements of set manufacturers.

TUNG-SOL
RADIO, TV TUBES, DIAL LAMPS

TUNG-SOL ELECTRIC INC., NEWARK 4, N. J.
Sales Offices: Atlanta • Chicago • Dallas • Denver
Detroit • Los Angeles • Newark

ALSO AUTO. LAMPS, ALL-GLASS SEALED
BEAM LAMPS AND SIGNAL FLASHERS

TV RECORDING direct on magnetic tape was demonstrated last month by Ampex Co., the electronic division of Crosby Enterprises, Inc. This may well be the "Videograph" envisioned by David Sarnoff as television's most-needed invention.

The recorder, according to press reports, uses standard Scotch magnetic recording tape. At present the picture is "rather fuzzy" but it is expected to be improved greatly before public demonstrations are staged about six months from now.

If the recorder becomes commercially practical, it should reduce greatly both the cost and complexity of TV recording. Optical methods must be used at present, the screen being photographed with a moving-picture camera.

NEW RECORD SPEED has been announced by the Wagner Research Corporation of New York City. Their records will play at the hitherto-unheard-of speed of 16 revolutions per minute. It will be possible to play the new records on a standard 33 $\frac{1}{3}$ r.p.m. player with the help of a simple attachment.

The new records, of thin vinylite 4 $\frac{1}{4}$ inches in diameter, will have 448 grooves to the inch and will play more than an hour (one-half hour per side).

The new records are intended to be used for transcribing readings of classical literature, rather than for music. Work with the blind, according to the company's president, Robert Wagner, inspired the development.

The company intends to market the records for about a dollar each, and a kit containing two records and the attachment for a 33 $\frac{1}{3}$ r.p.m. player will probably cost about \$12. Mr. Wagner said that the latest Zenith phonographs are also capable of playing at 16 r.p.m. but will require a special stylus.

HARBOR RADAR TESTS conducted by the Port of New York Authority have been extended for another six months according to Howard S. Cullman, chairman of the agency. Commencing last March with equipment donated by Raytheon Manufacturing Co. and Sperry Gyroscope Co. some 60 large ships have participated closely

with the radar crews at the Fort Wadsworth installation.

Recently developed electronic identification devices will also be tested in the winter months ahead under conditions of heavy fog, rain and snow. An additional \$30,000 has been appropriated by the board for these continued tests which will allow data over a whole year's operation to be accumulated. Definite and considerable reduction in time and money lost in ship delays caused by bad visibility and navigation hazards are expected if a permanent installation is found to be practical and feasible.

UNDERSEA TELEVISION may be used by the Navy to protect divers and to aid them in their work, Admiral Homer N. Wallin, Chief of the Navy Bureau of Ships, discloses. The new underwater TV cameras enable viewers to explore the ocean floor and study it for conditions dangerous to divers. When working at 200 feet or more, divers spend more time descending and ascending than they do on the bottom. Actual working time is short. Cameras can be lowered and raised much quicker than a diver and can be operated for long periods. Remote-control circuits provide for camera adjustments.

FINAL TV ALLOCATIONS are believed to be in the offing according to observers. Recent developments tending to substantiate this view have been noted. WSB-TV (formerly WCON-TV) has been granted a temporary authorization to operate on a commercial basis with modification in power for not later than February 15, 1952. The FCC has assigned at least 15 staff members to the necessary task of reading and evaluating the hundreds of sworn statements filed in connection with the TV allocation proceedings. The FCC postponed the theatre TV proceedings from November to February 25, 1952 with an opinion and order which stated that the TV allocations necessitated the postponement. Also cited was the speech by vice-chairman Paul A. Walker in which he expressed indications of TV coverage of the whole nation in the near future.

—end—



Photo of a 16-r.p.m. record and adapter on a standard Dynavox record player.

Courtesy Wagner Research Corp.

RADIO-ELECTRONICS for

**IN STOCK AT
ALLIED**

EICO

Test Instrument Kits
Lab Precision Quality at Lowest Cost
Quick and Easy to Assemble



221-K Vacuum Tube Voltmeter. 15 ranges; 26 meg DC input res. Zero center $4\frac{1}{2}$ " meter; ranges: AC-DC volts, 0-5-10-100-500-1000; res., 0-1000 ohms and 0-1-10-100-1000 meg.; db, -20 to +16. With all tubes and parts ready to wire. $6\frac{1}{2} \times 9\frac{1}{2} \times 5$ ". Shpg. wt., 10 lbs. **83-152. Only. \$25.95**



526-K Standard Multimeter. 1000 ohms-per-volt; 31 ranges; $3\frac{1}{2}$ " meter. Ranges: AC-DC volts, 0-1-5-10-50-100-500-5000 at 1000 ohms/volt; res., 0-700, 0-100,000 ohms, 0-1 meg; AC and DC current, 0-1-10 ma, 0-0.1-1 amps; 6 db ranges, -20 to +69. Accuracy: AC $\pm 5\%$, DC $\pm 3\%$. Ready to wire. $6\frac{1}{4} \times 3\frac{3}{4} \times 2$ ". Shpg. wt., 3 lbs. **83-166. Only. \$13.90**



555-K 20,000 Ohms-Per-Volt Multimeter. $4\frac{1}{2}$ " meter, 50 micro-amp D'Arsonval movement. 31 ranges: DC, AC and output volts, 0-2.5-10-50-250-1000-5000 (DC at 20,000 ohms/volt); 5 db ranges: -12 to +55; res., 0-2000-200,000 ohms, 0-20 meg; DC current, 0-100 micro-amps, 0-10-100-500 ma, 0-10 amps. Ready to wire. $6\frac{3}{4} \times 5\frac{1}{4} \times 3$ ". Shpg. wt., 4 lbs. **83-167. Only. \$29.95**




511-K Volt-Ohm-Milliammeter. 3" meter; germanium crystal for AC. Ranges: DC volts, 0-5-50-250-500-2500; AC, output volts, 0-10-100-500-1000; DC current, 0-1-10-100 ma, 0-500-100,000 ohms, 0-1 meg; db, -8 to +55. Complete, ready to wire. $8 \times 4\frac{1}{2} \times 3$ ". Shpg. wt., $3\frac{1}{2}$ lbs. **83-153. Only. \$14.95**



145-K Multi-Signal Tracer. Traces audibly all IF, RF, video and audio circuits in AM, FM and TV sets. Built-in 4" PM speaker; panel jacks for use of VTVM; germanium crystal diode probe. Response to over 200 mc. Complete, ready to wire. $10 \times 8 \times 4\frac{1}{4}$ ". Shpg. wt., 9 lbs. **83-158. Only. \$19.95**

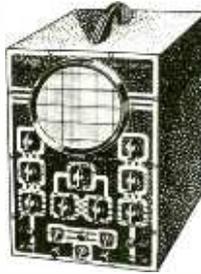425-K 5" Oscilloscope. For AM, FM, TV alignment; push-pull deflection. Sensitivity .05 to .1 rms volt/inch. Range, 5 cps to 500 kc. Wide-range multi-vibrator sweep circuit 15-75,000 cps. Provision for ext. sync. Z-mod. and direct input to CR tube plates. With all tubes and parts, ready to wire. $8\frac{1}{2} \times 17 \times 13$ ". Shpg. wt., 30 lbs. **83-155. Only. \$44.95**



320-K RF Signal Generator. Uses Hartley oscillator. Covers 150 kc to 34 mc on fund., to 102 mc on harmonics. Unmodulated or 400 cycle AM modulated output. Dial calibrated in 7 bands. Quickly aligns AM, FM sets; aligns RF with any standard AM set. Ready to wire. $10\frac{1}{2} \times 8\frac{3}{4}$ ". Shpg. wt., 10 lbs. **83-154. Only. \$19.95**



322-K RF-AF Signal Generator. Improved 150 kc to 34 mc instrument, with individual calibration for each of 5 bands. Selects pure RF, mod. RF, or pure AF. Colpitts audio osc. generates 400 cy. pure sine wave voltage. Ready to wire. **83-168. Only. \$23.95**

315-K DeLuxe RF Signal Generator. For AM, FM, TV work. 1% accuracy. Freq. range, 75 kc to 150 mc in 7 calibrated bands; vernier micro-cycle band; volt.-reg. power supply. 400 cycle sine wave modulation, less than 5% distortion. Complete, ready to wire. $12\frac{1}{2} \times 13\frac{7}{8}$ ". Shpg. wt., 20 lbs. **83-162. Only. \$39.95**



625-K Tube Tester. Tests all standard AM, FM and TV tubes, including 9-pin miniatures. $4\frac{1}{2}$ " meter; illuminated chart shows test settings. Tests for shorts and open elements; spare socket for new tubes; built-in power supply. Ready to wire. $12\frac{1}{2} \times 9\frac{1}{2} \times 4\frac{1}{4}$ ". Shpg. wt., 13 lbs. **83-161. Only. \$34.95**



360-K Sweep Generator. Use with any standard scope for visual TV-FM alignment. Covers 500 kc-228 mc. Variable sweep, 0-30 mc. Crystal marker osc. with variable amp; external marker can be injected; phasing control; each TV channel center marked on front panel. Ready to wire. $10\frac{1}{2} \times 8\frac{3}{4}$ ". Shpg. wt., 12 lbs. **83-159. Only. \$34.95**



950-K Resistance-Capacitance Bridge. Measures, tests all resistors, 0.5 ohms to 500 meg., and all condensers, 10 mmfd. to 5000 mfd. Also gives instant R-C-L comparison with any ext. component as standard. 0-500 DC v. source. Tests for leakage, polarization, power factor. Magic eye indicator. Ready to wire. $10\frac{1}{2} \times 4\frac{3}{4}$ ". Shpg. wt., 10 lbs. **83-164. Only. \$19.95**



1171-K Resistance Decade Box. Supplies resistance values from 0 to 99,999 ohms with $\frac{1}{2}\%$ precision. Has 5 separate 10-position switches. Includes comparator position and binding posts for instant substitution of actual equivalent component. Complete with all parts, ready for wiring. $3\frac{1}{2} \times 12 \times 3$ ". Shpg. wt., 3 lbs. **83-165. Only. \$19.95**




1040-K Battery Eliminator and Charger. For charging and all auto radio testing. Gives 0-13 v. output. Has 4-stack rectifiers in full-wave bridge. 10,000 mfd condenser for well-filtered output. Delivers 10 amps DC at 5-8 volts continuously, 20 amps intermittently. Meter measures current and voltage output. Ready to wire. $10\frac{1}{2} \times 7\frac{3}{4} \times 8\frac{3}{4}$ ". Shpg. wt., 15 lbs. **83-163. Only. \$25.95**



EICO PROBE KITS

With Germanium crystal; for signal tracing and measurement up to 200 mc; $6\frac{1}{2} \times 1\frac{1}{2}$ ". **83-156.** P75-K RF Probe for 221-K VTVM. **\$3.75**
83-157. P76-K RF Probe for 425-K Scope. **\$3.75**
83-160. High-voltage probe HVP-1. Adapts Eico 221-K VTVM, Eico 555-K or any other VTVM or 20,000/ohm/V VOM to read up to 30,000 v. 10×2 ". **\$6.95**

ALL OF THE ABOVE UNITS ARE ALSO AVAILABLE FACTORY-WIRED AND TESTED—SEE YOUR ALLIED CATALOG OR WRITE FOR PRICES

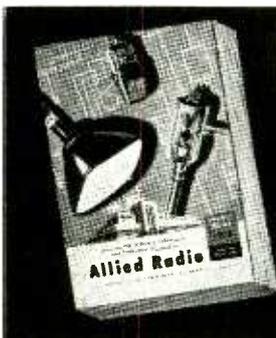

FREE 212-PAGE 1952 CATALOG

Send today for ALLIED's authoritative, complete buying guide to all electronic supplies. ALLIED offers the world's largest stocks of tubes, parts, test instruments, audio equipment, industrial components—complete quality lines at lowest prices. Get every buying advantage—speedy delivery, expert personal help, complete satisfaction on every order. Send for your FREE ALLIED Catalog today.

ALLIED RADIO

ALLIED RADIO CORP., Dept. 2-A-2
833 W. Jackson Blvd., Chicago 7, Ill.

Please ship the following Eico Kits.

\$ enclosed. Full Pay. Part Pay (Bal. C.O.D.)
 Send FREE 1952 212-Page Catalog.

Name _____

Address _____

City _____ Zone _____ State _____

HERE'S THE "SECRET!"

Solder-seal construction formerly used only in costly, large metal-encased capacitors.

This exclusive hollow eyelet terminal permits OIL impregnation after the capacitor is molded.

Sprague dry molding keeps the high purity paper and foil windings uncontaminated during manufacture.

Enlarged cut-away view of Sprague Telecap.

..... that makes
SPRAGUE TELECAPS[®]
outperform and outlast
other molded tubulars

Actual, on-the-job performance *proves* the superiority of Sprague "Black Beauties" beyond question. To find the secret that explains just why they're so much better, however, you've got to see inside of a Telecap itself.

The big feature is that every Sprague Telecap is molded into its sturdy Bakelite phenolic shell while its windings are still *dry*. Any chance of contamination by moisture or dust during manufacture is avoided. After molding, the capacitor is vacuum-impregnated with mineral oil through a tiny eyelet. The lead is then inserted, the terminal is solder-sealed—and you have a capacitor that has maximum resistance to heat and moisture... extra high insulation resistance and superior capacitance stability. *In short, a capacitor that brings you premium quality at no extra cost!*

... And that's the secret behind the fact that Sprague Telecaps are more widely used by leading television set makers... and why they're first choice of service technicians who value their reputations for good work!

Write for "Telecap" Bulletin. It's free!

SPRAGUE PRODUCTS CO.

81 Marshall Street
NORTH ADAMS MASSACHUSETTS

SPRAGUE

BLACK BEAUTY TELECAPS[®]

TELEVISION'S MOST WIDELY USED
MOLDED TUBULARS

Merchandising and Promotion

Merit Transformer Corp., Chicago, is shipping its No. 1,000 TV kit to distributors. The kit contains three major components for conversion and replacement: The HVO-7, a 77J-1 type flyback transformer with universal mounting brackets; an MWC-1 width-linearity coil with a.g.c. winding; and an MDF-70 cosine-wound deflection yoke. The kit also contains data sheets.

Bendix Radio Division of Bendix Aviation Corp., Baltimore, published a cartoon booklet, the "Blue Book of TV Servicing." The booklet humorously presents the "dos and don'ts" for TV service technicians in their relations with the public.

Erie Resistor Corp., Erie, Pa., designed a new "Breakaway" package consisting of two drawer trays and a sleeve. The sleeve may be broken apart so that each half of the package makes a complete drawer tray unit containing Erie Ceramicons of five different capacitances.

Circle-X Antenna Corp., Perth Amboy, N. J., launched a \$100,000 sales campaign, "The Circle-X Round-Up," offering incentive merchandise to distributors' salesmen to promote the sale of its antennas.

The RCA Tube Department, Harrison, N. J., inaugurated a sales promotion campaign to familiarize the names and services of RCA tube distributors in the minds of their broadcast and industrial customers. Built around the "forget-me-not" theme, the campaign offers a wide variety of useful items imprinted with the distributor's name. The give-away merchandise includes such items as a three-year wall calendar, an electric clock, an automatic pencil, the RCA reference book, and a tie or a money clip. The Tube Department is also offering, free, a three-ring leatherette binder through its distributors to service technicians who purchase at least \$10 worth of RCA Victor service data.

Belmont Radio Corp., Chicago, manufacturers of Raytheon TV receivers, prepared a service manual and presentation which directs TV service technicians to study the picture for clues to circuit troubles. Titled "How to Interpret What You See," the presentation, under the direction of Carroll Hoshour, Belmont service manager, was shown to 850 TV technicians in Philadelphia and Chicago and has now become a "road show."


Allen B. Du Mont Laboratories' Electronic Parts Department is sponsoring a campaign by which service technicians may offer their customers a trade-in allowance on their present tuners if they purchase a Du Mont Inputuner. The plan is meant to reduce the customer's cost of converting a straight TV receiver to an FM-TV combination. The plan will be in effect for a limited time only.

Jensen Industries, Inc., Chicago, released a circular describing its needle kits and new cutting needles, and also
(Continued on page 20)

RADIO-ELECTRONICS for

ANCHOR Boosters

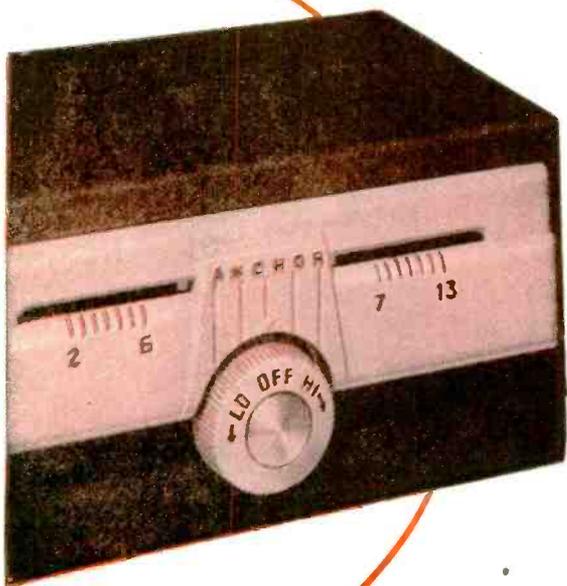**First in Preference!
First in Fringe
Reception!**



REACHING NEW

horizons

*Anchor engineering
always a year ahead!*

ANCHOR RADIO CORP.


2215 SOUTH ST. LOUIS AVENUE
CHICAGO 23, ILLINOIS



Each crystal is enclosed in a cylindrical oven which holds the crystal temperature to within 1/100 of a degree.

At the A. T. & T. building at 195 Broadway, New York, passersby set watches by the world's most accurate public clock, which is controlled by the master standard.

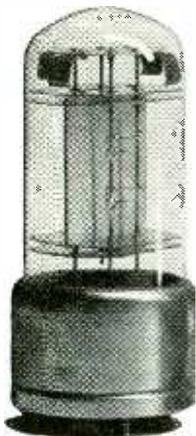▲ Front of the new frequency-time standard at Bell Telephone Laboratories. In the rear there are 600 electron tubes and 25,000 soldered connections. Room temperature is maintained within two degrees.



The controlling quartz crystal vibrates in vacuum at 100,000 cycles per second. The standard is powered by storage batteries, with steam turbo-generator standing by, just in case of emergency.

A vibrating crystal keeps master time

Ever since Galileo watched a lamp swinging in the Cathedral of Pisa three centuries ago, steady vibration has provided the practical measure of time. In the 1920s Bell Laboratories physicists proved that the quartz crystal oscillators they had developed to control electrical vibration frequency in your telephone system could pace out time more accurately than ever before.

The Laboratories' latest master standard keeps an electric current vibrating at a frequency that varies only one part in a billion, keeping time to one ten-thousandth second a day.

Through secondary standards, a master oscillator governs the carrier

frequencies of the Bell System's ship-to-shore, overseas and mobile radio-telephone services, the coaxial and *Radio-Relay* systems which transmit hundreds of simultaneous conversations, or television. In the northeastern states, it keeps electric clocks on time through check signals supplied to electric light and power companies.

The new standard also provides an independent reference for time measurements made by the U. S. Naval Observatory and the National Bureau of Standards. Thus, world science benefits from a Laboratories development originally aimed at producing more and better telephone service.

BELL TELEPHONE LABORATORIES



Improving telephone service for America provides careers for creative men in scientific and technical fields.

RADIO-ELECTRONICS for

NOW... GET EVERYTHING YOU NEED TO LEARN AND MASTER TELEVISION RADIO-ELECTRONICS ...AT HOME!

Use REAL commercial-type equipment to get practical experience

Your future deserves and needs every advantage you can give it! That's why you owe it to yourself to find out about one of the most COMPLETE, practical and effective ways now available to prepare AT HOME for America's billion dollar opportunity field of TELEVISION-RADIO-ELECTRONICS. See how you may get and keep the same type of basic training equipment used in one of the nation's finest training laboratories... how you may get real STARTING HELP toward a good job or your own business in Television-Radio-Electronics. Mail the coupon today for complete facts — including 89 ways to earn money in this thrilling, newer field.

D.T.I., ALONE, INCLUDES BOTH MOVIES and HOME LABORATORY In addition to easy-to-read lessons, you get the use of HOME MOVIES — an outstanding training advantage — plus 16 big shipments of Electronic parts. Perform over 300 fascinating experiments for practical experience. Build and keep real commercial-type test equipment shown at right

Get BOTH of these information packed publications FREE!

89 WAYS TO EARN MONEY IN TELEVISION RADIO-ELECTRONICS

YOU GET ALL 6

MODERN LABORATORIES

If you prefer, get all your preparation in our new Chicago Training Laboratories—one of the finest of its kind. Ample instructors, modern equipment. Write for details!

MILITARY SERVICE!

If you're subject to military service, the information we have for you should prove very helpful. Mail coupon today.

ACT NOW! MAIL COUPON TODAY!

DE FOREST'S TRAINING, INC. Dept. RE-1-1
2533 N. Ashland Ave., Chicago 14, Ill.

Without obligation, I would like your Opportunity News Bulletin showing "89 Ways to Earn Money in Television-Radio-Electronics"; also, the folder showing how I may prepare to get started in this thrilling field.

Name.....Age.....
Address.....Apt.....
City.....Zone.....State.....



ABOVE: Build and keep a real 17 INCH commercial TV receiver. Optional after completing regular training at moderate added cost.

**Here's the REAL THING!
SET UP YOUR OWN HOME LABORATORY**



R-F Signal Generator

Oscilloscope

6-Tube Radio

Home Movies

Multimeter

"ONE OF AMERICA'S FOREMOST TELEVISION TRAINING CENTERS"


De FOREST'S TRAINING, INC.
CHICAGO 14, ILLINOIS
A De VRY INSTITUTION

AMAZINGLY VERSATILE NEW ASTATIC L-12-U CRYSTAL CARTRIDGE

Leave condenser
harness on for low
output (1.2 volts) . . .
or slip it off for high
output (4.0volts)
to replace over
125 standard
78 RPM Cartridges



LIST PRICE . \$4.95
Code ASWSF

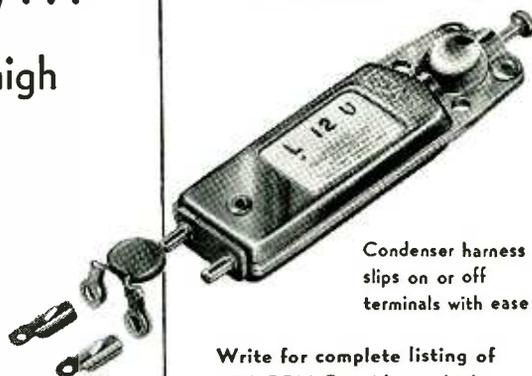

Condenser harness
slips on or off
terminals with ease

Write for complete listing of
78 RPM Cartridges which
the L-12-U replaces.

AT LAST, here is the first completely satisfactory answer to a long-felt need! You can now replace most standard 78 RPM cartridges with one, single model . . . and get reproduction guaranteed to better or equal the previous unit. It's the newly perfected Astatic Dual-Output L-12-U Crystal Cartridge which puts this modern replacement magic at your fingertips. Think of the savings in time and trouble . . . the streamlining of old problems, all the way from inventory to installation! Try the new Astatic L-12-U at the first opportunity . . . you'll adopt it at once as your number one standby.

FEATURES:

1. Stamped steel housing.
2. Needle chuck limiting feature which restricts motion of the chuck both radially and lengthwise, prevents dislocation of chuck, and protects against crystal breakage from rough handling and when changing needle.
3. Dual-output; 1.25 or 4.0 volts at 1,000 c.p.s.
4. Range to 5,000 cycles.
5. Minimum needle pressure, 1 oz.
6. Net weight, 19 grams.
7. Furnished with complete installation instructions and listing of cartridges the L-12-U replaces.



Astatic Crystal Devices manufactured under Brush Development Co. patents.

showing electrotypes of cuts of its products available for distributor catalogs.

Production and Sales

The NBC TV Sales Planning and Research Department reported that there were 14,555,800 TV sets installed in the United States as of November 1. New York City led with 2,630,000, followed by Los Angeles with 1,045,000, Chicago 1,020,000, Philadelphia 940,000 and Boston 809,000.

The RTMA reported that receiving-tube sales for September had increased to 27,946,193 over the 23,761,253 sold in August. Of the September sales, 16,176,604 tubes were for new sets, 7,363,721 for replacement, and the balance for export and Government agencies. The sales of TV picture tubes to TV set manufacturers also increased during September—294,951 units were sold compared to 210,043 in August. Of the picture tubes sold in September, 97% were 16 inches or larger and 98% were rectangular.

Allen B. Du Mont Laboratories' president, Dr. Allen B. Du Mont, estimated that the company's sales during 1952 would be at least 25% more than any previous year due to the increase of defense orders.

RTMA president Glen McDaniel predicted that the industry would not be able to produce more than 1,000,000 to 1,250,000 TV sets during the fourth quarter of 1951, which would bring the total output for 1951 to between 5,000,000 and 5,250,000 sets as compared with 7,400,000 in 1950.

New Plants and Expansions

Haydu Brothers, Plainfield, N. J., completed a two-story building in connection with its main plant at Mount Bethel, N. J. The need for the new plant was dictated by the company's Government program for the production of electronic assemblies and parts for the Air Force and Signal Corps.

Budelman Radio Corp., Stamford, Conn., was formed as a new manufacturing and engineering corporation for radio and electronic equipment.

Astron Corp., East Newark, N. J., signed a long-term lease for additional space, virtually doubling its production facilities for its line of capacitors and r.f. interference filters.

Shallcross Manufacturing Co., Collingdale, Pa., is nearing completion of its building program which includes a new wing on its main factory, expansion of its instrument laboratory, and a large component development laboratory.

TV-"Q" Custombilt Corp. moved its plant and offices to new quarters in Hawthorne, N. J.

Business Briefs

. . . Jensen Manufacturing Co., Chicago, announced that its Viking loudspeakers would now be identified by the phrase, "Viking by Jensen." It was formerly a private brand line for low-cost replacement. The brand will be given extensive publicity and promotion.

—end—

RADIO-ELECTRONICS for

You'll see better..

NATIONAL
TELEVISION



Demand the N.V.C. trade mark on every picture tube.

*America's largest
Independent*
Manufacturer*

**PRODUCING THE WORLD'S
FINEST TELEVISION TUBES**

*Independent sound engineering, carefully selected quality materials and tightly controlled precision workmanship make N.V.C. television tubes the finest—for at N.V.C. all efforts, all personal attention is given to a single thing alone—better tubes designed for conversion and replacement in every standard set to give a *better, more clearer* picture.

Write for name of Representative nearest you
3019 West 47th Street, Chicago, Ill.

Three plants with over 17 acres of coordinated machinery and personnel, producing the world's finest television picture and receiving tubes.



National Video Corporation

3019 W. 47th St.
Chicago

Grays Lake
Illinois


901 W. Huron St.
Chicago

RADIO-ELECTRONICS for

.. You'll see more....

V **VIDEO** **W** **ORPORATION**

PICTURE TUBES

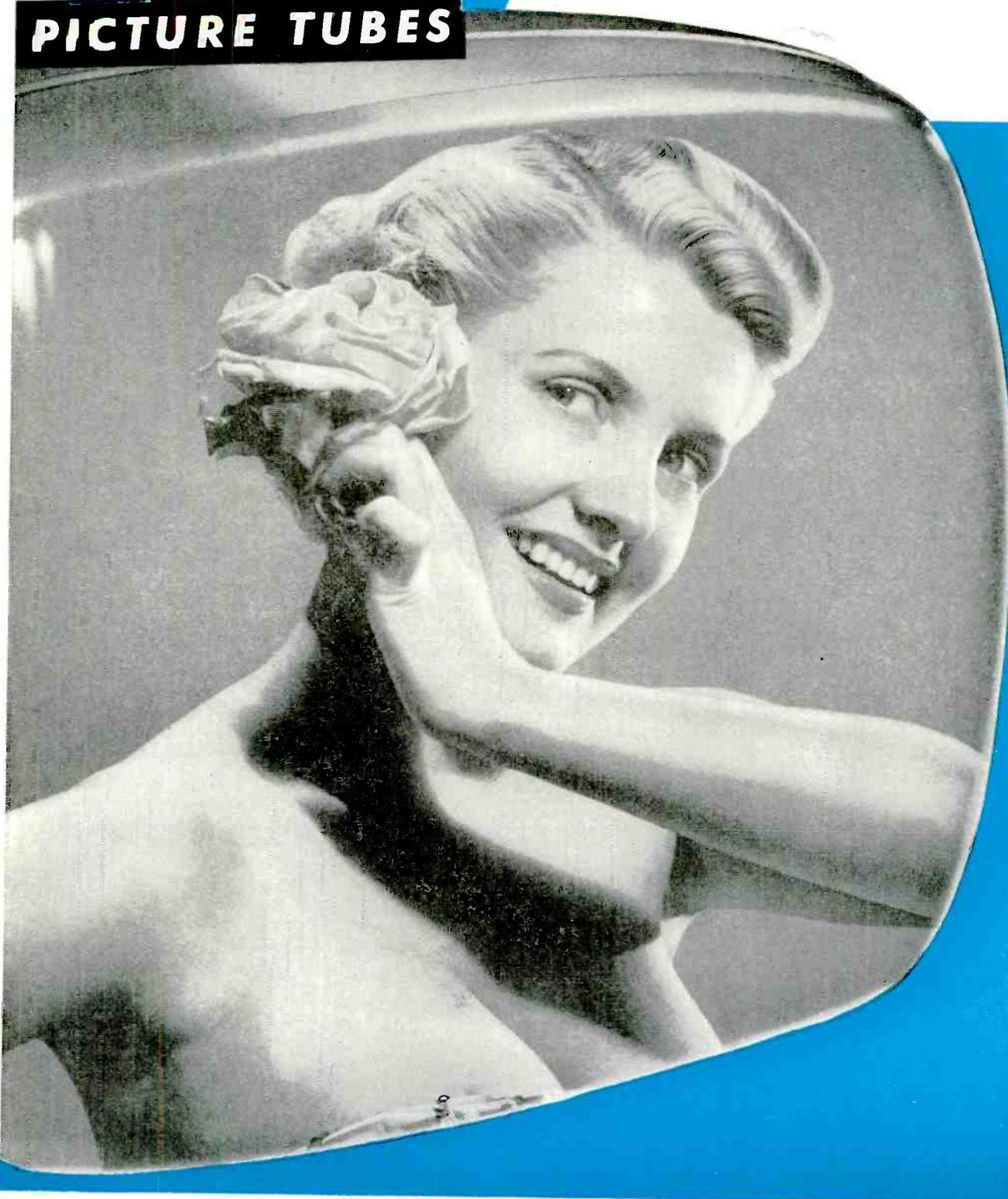

JANUARY, 1952

EICO
TEST INSTRUMENTS

Guard

CBS-Columbia Inc.
HIGH STANDARDS OF
TELEVISION PRODUCTION QUALITY



In the CBS-Columbia design laboratories, Al Goldberg takes some important readings with the EICO Model 221 Vacuum Tube Voltmeter and Model 555 Multimeter, as Harry R. Ashley looks on.



Mr. Al Goldberg, Assistant Chief Engineer of CBS-Columbia, and Harry R. Ashley, President of EICO, inspecting the use of the EICO Model 221 Vacuum Tube Voltmeter and Model HVP-1 High Voltage Probe at the Sweep Frequency Troubleshooting Position on the CBS-Columbia Television production lines.



NEW
221K VTVM KIT \$25.95
WIRED \$49.95



HIGH VOLTAGE
PROBE \$6.95

KITS
WIRED INSTRUMENTS



NEW 555K MULTIMETER
KIT \$29.95. WIRED \$34.95
20,000 ohms/volt



320K SIG.
GEN. KIT \$19.95. WIRED \$29.95

NEW 322K SIG. GEN.
KIT \$23.95. WIRED \$34.95



NEW 950K P.C. BRIDGE &
R-C COMP. KIT \$19.95
WIRED \$29.95



NEW 104CK BATTERY ELIM.
KIT \$25.95. WIRED \$34.95



311K VOM
KIT \$14.95
WIRED \$17.95



NEW 520K MULTI-
METER KIT \$13.90
WIRED \$16.90
1000 ohms/volt



NEW 1171K RES
DECADE BOX KIT
\$19.95
WIRED \$24.95



NEW 315K DELUXE SIG.
GEN. KIT \$39.95
WIRED \$59.95




145K SIG.
TRACER KIT
\$19.95
WIRED
\$28.95



NEW 625K
TUBE TESTER KIT \$34.95
WIRED \$49.95



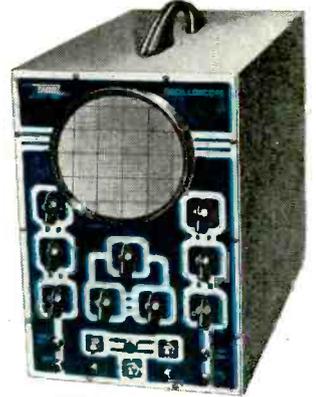360K SWEEP GEN. KIT \$34.95
WIRED \$49.95



NEW 425K 5" PUSH-PULL
SCOPE KIT \$44.95. WIRED \$79.95

*For Laboratory Precision at Lowest Cost—
the Leaders Look to EICO!*

WHY does CBS-Columbia, Inc., another one of America's leading TV manufacturers, use EICO Test Instruments on both its production lines and in its design laboratories?

BECAUSE — like Emerson, Tele-King, Tele-Tone, Majestic, and many another famous TV manufacturer coast to coast, CBS-Columbia knows that . . . *Only EICO Test Equipment*

delivers All 10 EICO nomical Features!

1. Laboratory Precision
2. Lowest Cost
3. Lifetime Dependability
4. Speedy Operation
5. Rugged Construction
6. Quality Components
7. Latest Engineering
8. Super-Simplified Assembly and Use Instructions
9. Laboratory-Styled Appearance
10. Exclusive EICO Make-Good Guarantee

Before You buy any higher-priced equipment, be sure You look at the EICO line—in *Wired* as well as *Kit form!* Each EICO product is jam-packed with unbelievable value. YOU be the judge—compare, see EICO instruments today — in stock at your local jobber — and SAVE! Write NOW for FREE newest Catalog 1-C.

FOLLOW THE LEADERS . . . INSIST ON EICO!

EICO

ELECTRONIC INSTRUMENT CO., Inc.
276 NEWPORT STREET, BROOKLYN 12, NEW YORK

©1951, Electronic Instrument Co., Inc.
Price \$5 Higher on West Coast Due to unstable conditions, prices and specifications are subject to change without notice.

Television at the Crossroads

. . . . "Television is about to enter a new cycle"

By HUGO GERNSBACH

The television industry is about to undergo a new and far-reaching upheaval, beginning some time in 1952. It is perhaps the most important change that the industry has faced since its beginning.

We are not referring to color television, which has been frozen for the time being by the NPA, due to strategic shortages of materials. We refer to the imminent end of the television freeze order of the Federal Communications Commission—the freeze having been in effect for some three years. The FCC realized, back in 1948, that unless drastic steps were taken, new television stations would have continued to swamp the country, with mutual interference to such an extent that good reception for a large part of the country would have been impossible.

Unfortunately, the country started out on the wrong foot by adopting v.h.f. (very high frequency) transmission when we should have had u.h.f. (ultra high frequency), which is just now about to be opened up.

According to Curtis P. Plummer, chief of the FCC's Broadcasting Bureau, the new schedule will work somewhat as follows:

1. Between February 1 and March 1, 1952, the present freeze, in all probability, will be lifted.
2. About April 1, 1952, the Commission will begin granting new u.h.f. station permits.
3. About July, 1952, there is a possibility that some eighty new stations will have been authorized.
4. About the middle of 1953, these new stations should be on the air.

While it is most desirable and necessary that the country have new television stations to open up territories not served at the present time, the industry faces a number of formidable difficulties, which so far have not been ironed out.

The trouble stems from the fact that some time during 1952 there will be in existence over 19,000,000 television receivers. Not all of these will be in use, as perhaps a half-million or more of them may still be in warehouses, stores, etc. These receivers are all designed for v.h.f. and the majority of them cannot receive u.h.f. signals when the new stations go on the air. It is true that the owner of the present day v.h.f. television set can get ultra high frequency reception by an external converter or u.h.f. strips in his present receiver's tuner. This, however, isn't the most satisfactory means of getting reception, as at best, converters are makeshifts.

The industry also faces a technical difficulty in equipping the new u.h.f. television sets with efficient tuning devices. So far, no manufacturer has placed one on the market. It is, however, probable that con-

tinuous tuners, rather than the step-by-step type we now have on most receivers will be used. The continuous tuner will be similar in operation to what we have in our present day radios (and some TV sets), and there is a strong possibility that this will be the best solution.

If such a device proves satisfactory—and most engineers feel that it will be—the majority of the new television sets will be thus equipped. That means that the new sets then will receive both v.h.f. and u.h.f., enabling reception in the present bands as well as the new one. The sets may become known as *All-Frequency TV receivers*.

How many of the new type television sets will be manufactured in 1952 is anyone's guess, due to the critical shortage of materials and the uncertainty of their allotments to manufacturers by the government.

As it seems to be probable that sooner or later all of the television stations will transmit on u.h.f., it follows that some 19,000,000 or more present-day sets eventually will become obsolete. This does not mean that they will be obsolete in the near future, as the v.h.f. stations will probably continue broadcasting for many years to come, but taking a long range view, it would appear that by 1970 or thereabouts, nearly all stations will be u.h.f.

By that time existing sets will be obsolete anyway, and will certainly have outlived their utility.

The newer television receivers several years hence will also have to be able to receive either black-and-white or color, and will do so without the necessity of requiring a separate receiver for color.

It is therefore to be hoped that the FCC will clear up the problems of color "compatibility" so that all u.h.f. receivers can receive *all* transmissions in black-and-white, at least.

From this it will be seen that the television picture for the near future looks complicated, but it need not necessarily remain so if vigorous action is taken by all concerned at the earliest opportunity.

Another minor factor also bothers the industry. That is that the antenna requirements for u.h.f. are quite a bit different from v.h.f., at least at the present.

This, however, is a technical point that can be overcome, as similar technical difficulties have been overcome in the history of radio. It too, in its heyday, had similar difficulties, some of them looking more insurmountable than the television problems which we face today. Technical ingenuity overcame all of them and we feel sanguine that whatever technical problems there are now in television will be solved in due time.

—end—

EXACTLY 100 years ago, the Congress of the United States was dissuaded from building a chain of semaphore stations from Washington to New Orleans for "rapid" communications. They were dissuaded by Samuel F. B. Morse, a "dreamer" of his day, who not only had faith and conviction in electrical wire telegraphy, but also had some powers of persuasion. Only about 50 years ago, radio for the first time was usefully employed for telegraphing from point to point. Not until 1921 did transmission of speech and music reach the stage where its technical development could be combined with vision and enterprise to create the sound-broadcasting industry which in its day revolutionized our habits and thinking. Modern broadcasting has become a Colossus by comparison with the imaginative concepts of those of us who developed it from the beginning, as witnessed by the more than 90 million home receivers and the 2,900 stations devoted to sound broadcasting. A great new revolution is now taking place as a result of the combination of sight and sound which can be delivered with a high degree of perfection into our living rooms.

Only six years ago television had its great opportunity to expand and provide an outlet for the imagination and enterprise of those with unshakeable confidence in its tremendous future. The 6,000 television receivers which constituted our complete national inventory of five years ago have skyrocketed to 14,000,000 upon the stimulus provided by only 108 television stations, a great many of which duplicate their services in individual areas. What of the future?

The coming expansion

One must give reign to his imagination in prophecy. During television's lean years in the late 1930's and through the war, those of us who were intricately involved in it were frequently reluctant to express fully our prophecies because they sounded like wild dreams. But wild as they seemed, they have been proven to have been conservative. The readers of these pages have cause to be pleased with the opportunities which television has already made bountiful. But an insatiable public appetite for television service—held in leash only by the current television freeze—will require a phenomenal growth of television facilities throughout our country to feed upon.

In years to come, our present 108 television stations may grow to 3,000 or even more. Our present 14,000,000 receivers may grow to 50,000,000 or more, and the widespread use of color television a few years hence will present to the manufacturer, the broadcaster, and the service technician an opportunity to profitably serve the public to an exciting and stimulating degree. Unfreezing the construction of new v.h.f. stations in itself will provide

*Manager, Radio and Allocations Engineering, National Broadcasting Company.



AIR WEATHER AHEAD

By **RAYMOND F. GUY***

television service to many millions of persons now without it. The addition of 70 new u.h.f. channels will insure television service to all parts of our country where there are people to support it.

In 1945, following the postwar all-service frequency allocation hearings, it was apparent that the number of channels available for television would not give service throughout all of the communities of our country. To provide for future expansion, the u.h.f. block from 470 to 890 mc was earmarked for television use. But in 1945, those concerned with allocation and transmission problems had insufficient knowledge of, and experience with, u.h.f. propagation to permit the wise formulation of rules and standards. It was necessary to know how to calculate and determine the area which a u.h.f. station could serve. It was necessary to know the minimum co-channel station separation necessary to prevent destructive interference. It was necessary to know more about receiver characteristics so that minimum adjacent-channel separation could be determined. It was necessary to study the problems created by oscillator radiation and the establishment of suitable intermediate frequencies in receivers, and to allocate channels in specific areas to avoid the obvious difficulties which could arise without adequate provision against such effects. Recognizing these needs, RCA, NBC, and various other groups in the industry established research programs and through the ensuing years have been contributing information to the FCC.

A u.h.f. laboratory

In particular, the NBC experimental u.h.f. station at Bridgeport (RADIO-ELECTRONICS, August, 1950) has been referred to by the press as "The nursery of u.h.f." In operation nearly two years, this station carries the full program service of WNBT. Seventy manufacturing companies have taken advantage of this prototype operation to familiar-

ize themselves with various aspects of u.h.f. performance. Of this number many have field-tested their designs of u.h.f. receivers and converters, and demonstrated them to dealers, to service organization representatives, and to the Federal Communications Commission. Those interested in a comprehensive report of the NBC investigations of u.h.f. transmission and reception, may find information of the apparatus utilized and the propagation studies referred in papers by the author in the *RCA Review* issues of March, 1950, and March, 1951.

We are now on the threshold of the long-awaited unfreezing, with assurance that when allocation of frequencies and construction of facilities is resumed, it will be on a solid foundation of technical facts and considered judgment.

Television's tremendous national impact has been felt despite the fact that at present:


- 15 states have no stations,
- 10 states have only one station each,
- 14 states have only two stations each,
- 2 states have only three stations each.

The remaining 64 stations are concentrated in only 7 states and the District of Columbia.


A total of 65 cities at present have stations. But under the proposed FCC plan 558 v.h.f. stations may be built in 342 cities. And, combining u.h.f. and v.h.f. in the new proposals, 1,916 stations are specifically provided for, without making allowance for possible expansion of the specified list. A presentation of the proposed United States television assignments appears in map form on pages 28 and 29 of this issue of RADIO-ELECTRONICS.

TV technicians needed

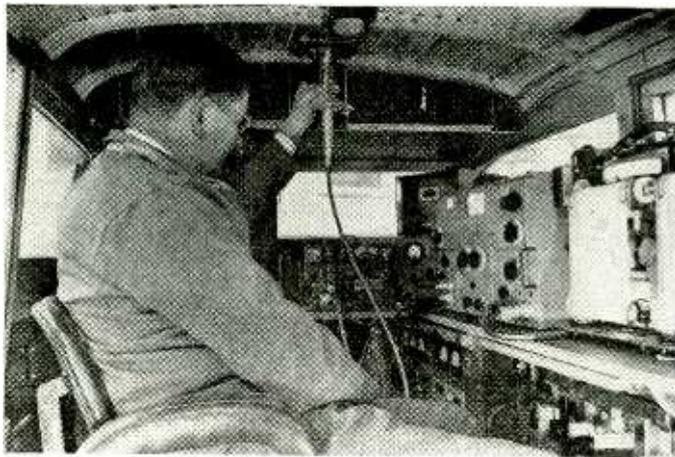With a total of 14,000,000 existing receivers, and a probable growth to at least 50,000,000, it seems inevitable that 36,000,000 new receivers will be pur-



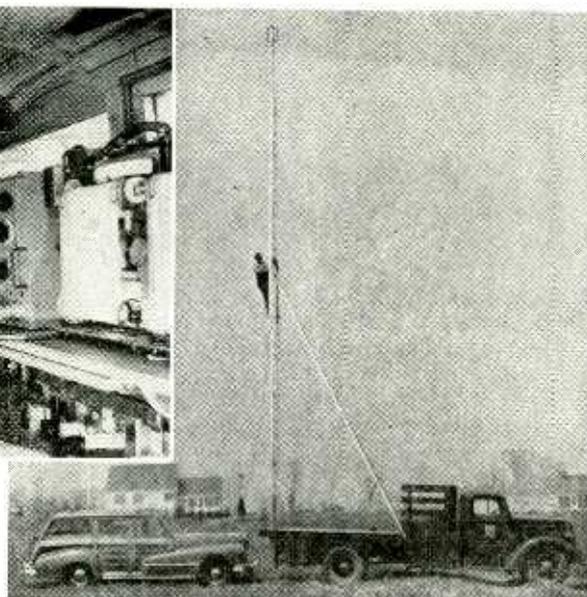Above—Interior of the NBC engineering car used in making the tests and measurements. Right—A mobile antenna rig used in making the tests described in the two charts, as well as checking antenna types, etc.



chased. Add to this the replacement demand for larger-screen sets and the millions of color receivers which the public will demand a few years hence, and the future appears exciting indeed. But it also presents a challenge.

It is authoritatively estimated that over 90,000,000 radio receivers are in use in the United States, nearly two per home. But this growth has extended over 30 years since about a dozen persons—including your author—launched the world's first broadcasting service. Television, on the other hand, has attained its great growth during the last five or six years, during three of which the FCC freeze has prohibited construction of new stations. This freeze, coupled with the tremendous unsatisfied public demand for television in unserved areas, has created a situation which is analogous to a coiled spring. A new "TV day" is imminent when the issuance of new TV station construction permits will be resumed by the FCC; nation-wide construction of new TV stations will be undertaken and millions of families will represent a virgin market for television receivers.

The Bell Telephone System is rapidly extending its microwave and coaxial cable facilities throughout the nation to meet the demand for TV network connections. Superb network program service is already available. And the manufacturers of transmitting and receiving equipment are completing their designs and preparations to supply the apparatus which will be needed.

Of particular significance to the readers of these pages is the coming concentrated demand for the services of competent and well-equipped installation and maintenance men in thousands of communities which will for the first time have television service, as well as those obtaining more adequate service. To meet this demand will be a challenge to the skill and resourcefulness of the servicing industry. It portends for the foreseeing and pre-

pared dealers and service technicians a bright prospect for new business, with fine opportunities and ample rewards for business enterprise and services rendered. And it presents to the technical schools an opportunity to train the thousands of men who will require knowledge of u.h.f. and v.h.f. receivers and antennas and of the intricacies of vertical and horizontal synchronizing circuits and frequency converters, of the importance of optimum antenna location, particularly in marginal receiving areas and more particularly in u.h.f. where wave interference patterns are somewhat more complex.

There is little productive reward for the amateur receiver repair man in television. The competent and well-equipped professional is indispensable. And therein lies an added responsibility and opportunity. Television receivers are more complex and costly than sound-broadcasting receivers, and maintenance, installation, and repair costs are correspondingly higher. It appears axiomatic that the service technician will assume higher stature in fact and in the customer's estimation for these reasons. He must have greater knowledge and skill, and thereby will do more business and become a more important and integral part of his community.

Propagation peculiarities

Certain phases of the knowledge gained in the Bridgeport project will be of particular interest to service technicians. It is well known that effective reflection of radio waves requires that a reflecting surface shall have dimensions not smaller than some function of a wavelength. There is no abrupt discontinuity, and for illustrative purpose we will assume one-half wavelength. For channel 5 such a surface would be about 6.5 feet square. For a u.h.f. station on 770 mc it would be about 8 inches square. It follows that a given sized surface will produce more distinct reflection at the short wavelengths

(higher frequencies). Hence, in residential areas characterized by homes, power and telephone lines, and other objects, the field of a u.h.f. station may vary over a wide range within distances of a few feet because of the random combination of the direct field and indirect fields reflected from nearby surfaces or reradiated by wires. Knowledge of this effect gives the installation technician a useful tool with which to work.

This effect was investigated in scores of actual home installations and also by a more precise statistical analysis of field intensity measurements. In the latter analysis an antenna at an altitude of 30 feet was moved through a horizontal range of 5 or more feet as the field intensity was recorded on charts. This was done at 91 locations. The averaged results are shown on Fig. 1. The field intensity varied over a range of as much as 7 to 1 within a few feet and at 10% of the locations it was 3 to 1. This study, combined with experience in installing about 100 receivers or converters in homes, illustrates the importance of exploring the area of the proposed antenna location to take

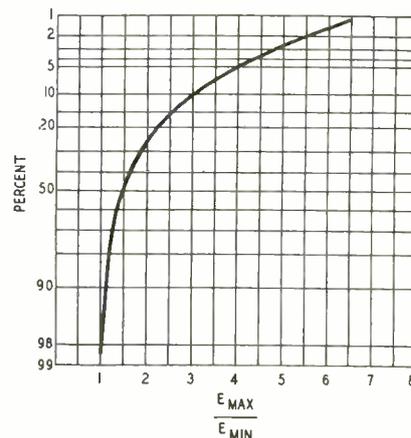


Fig. 1—Percentage of locations varying from standard and amount of variation.

maximum advantage of this effect. A threefold increase in signal intensity obtained by such an exploration would be equivalent to increasing the power of the transmitting station 900%.

At Bridgeport, such exploration was conducted by two men, one at the receiver and one on the roof. With communication by interphone, optimum antenna location was found easily by visual inspection of the picture or maximum indication on a meter. In marginal locations where the efforts are warranted this exploration may be fruitfully conducted in various areas on top of homes. In most cases where a reasonably strong signal is received, the antenna location is not so critical as to prevent its being located in the desired location.

Studies of signal intensity variations in the horizontal plane have been mentioned. Similar studies were conducted of the relationship of u.h.f. signal intensity and antenna height at 107 locations in the service area of the Bridgeport station. Measurements at individual locations also show the effects of random reflections from the earth and other objects, and of local shadowing. Integrating the results of the 107 sets

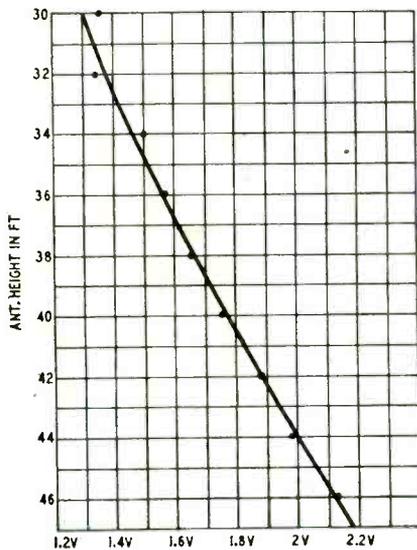


Fig. 2—Voltage increase over 10-foot height exceeded at 50% of the locations.

of measurements, as shown on Fig. 2, shows that on the average the field intensity increases with antenna height. But ordinarily it is not possible accurately to predict the optimum antenna height in specific locations. Here again, knowledge provides the installation technician with a useful tool by which he may take advantage of these effects.

Interference to u.h.f. reception from neighborhood sources, such as diathermy and automobile ignition systems, is almost completely absent. And multipath images may be expected to be at a minimum because the greater directivity afforded by u.h.f. receiving antennas of practical dimensions provides greater discrimination against reflected signals from random directions.

—end—



TELEVISION, U. S. A.

Present and proposed network routes (Bell coaxial, Bell microwave and independent) and present and future television allocations as envisioned by present FCC plans. Allocations are approximate only, the plans being so made as to provide flexibility.

- EXISTING 1951 TV NETWORK ROUTES
- - - PROPOSED 1952 TV NETWORK ROUTES
- EXISTING OR PROPOSED VHF ALLOCATIONS
- PROPOSED UHF ALLOCATIONS
- VHF AND UHF ALLOCATIONS, EXISTING OR PROPOSED

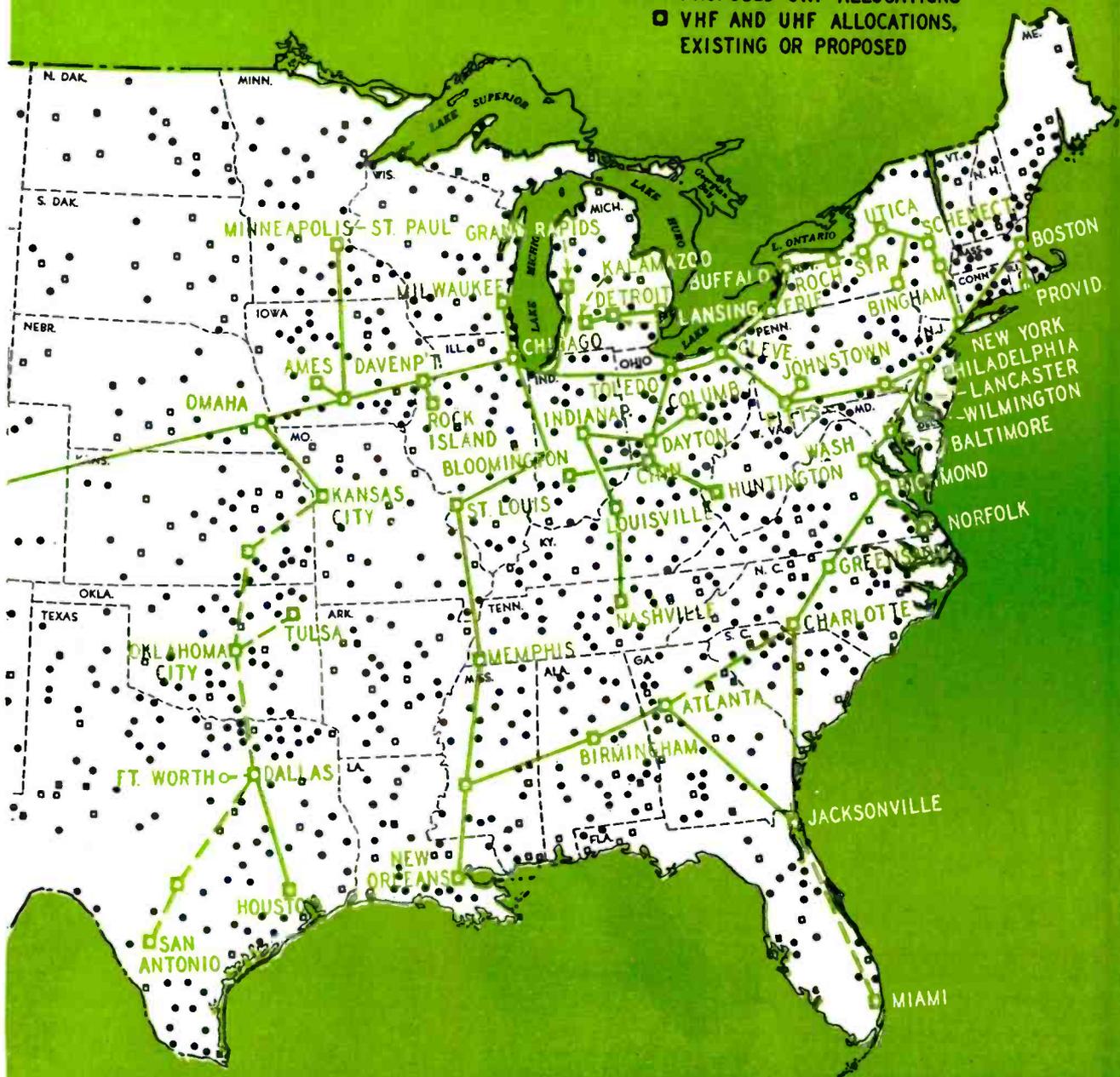


Fig. 3—An interesting sound i.f. circuit is found in the General Electric model 24C101.

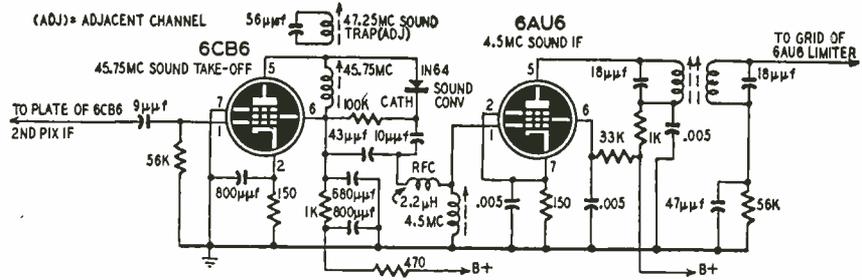


Fig. 4—Typical focusing circuits as found in some of the Zenith receivers. High-voltage focusing is used.


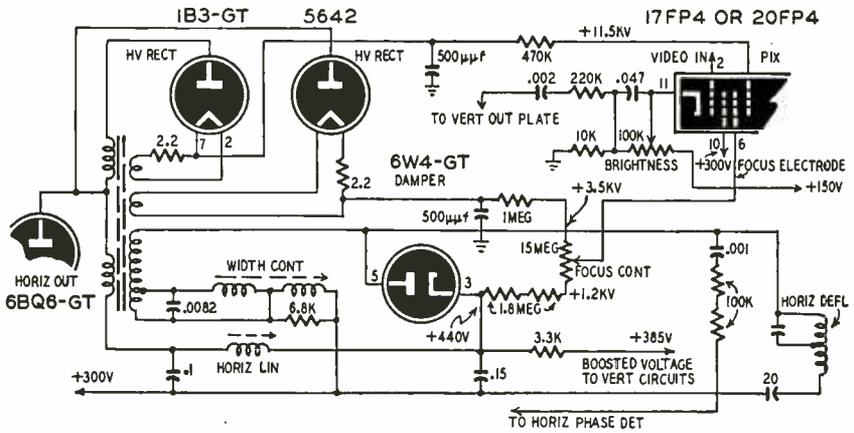


Fig. 5—The circuit of one of the newer low-voltage focusing tubes. Voltage of focus electrode is 440.

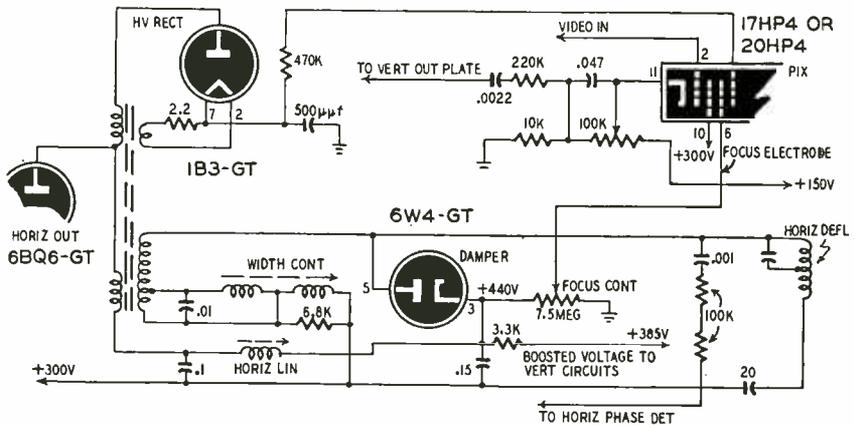

mately 18 db of inverse feedback is applied from one side of the voice coil to the cathode circuit of the 6AU6 first a.f. amplifier.

Note that the cathode of the 6W6-GT output tube is approximately 150 volts positive. Heater-to-cathode breakdown is minimized by connecting one side of the filament winding to the cathode. Breakdown between heater and cathode of the damper tube, a.g.c. keyer tube, and the second video i.f. amplifier is minimized by supplying these heaters from the same filament winding supplying the a.f. output tube.

The first and second video i.f. stages are connected in series with approximately 285 volts applied to the plate and screen of the second stage. The cathode of this stage is approximately 145 volts positive and is used as a source of supply voltage for the plate and screen of the first stage. This connection effects a further reduction in

current drain from the power supply by eliminating the plate and screen currents drawn by one stage. With this circuit arrangement, the over-all impedance is very high, yielding greater gain and making it possible to obtain wider bandwidth.

Since the two stages are in series, their cathode currents are equal. Both can be controlled by a.g.c. voltage merely by applying a.g.c. bias to the first stage. This is possible because any change in the cathode current of the first stage will be automatically reflected to the second.

Novel G-E circuit

G-E comes up with more complete trapping in their new receivers. The circuit of the video i.f. strip of the 24C101 is shown in Fig. 2. Parallel-tuned adjacent-channel sound traps are in the grid and plate circuits of the first video i.f. amplifier stage. The third video i.f.


amplifier has a 39.75-mc adjacent-channel picture trap in the cathode circuit and a 41.25-mc parallel-tuned trap in its plate circuit to absorb accompanying sound carrier. The plate circuit of the fourth i.f. stage has two traps. One is tuned to 39.75 mc for the adjacent-channel picture carrier and the other to 41.25 mc to trap out any sound carrier of the channel being tuned in which has leaked through. A 4.5-mc trap is in series with the signal lead to the cathode of the picture tube. This removes the 4.5-mc beat, indicated by picture hash, between the sound and picture carriers.

After glancing over the sound i.f. section of this set, we immediately pegged it as a split-carrier model because the sound take-off preceded the video detector. The second glance showed that the set has a 4.5-mc ratio detector, which by most standards would make it an intercarrier model. It

TV MICROWAVE RELAY


Stretching 3,000 miles from New York to San Francisco, the Bell System microwave link is communications electronics' greatest achievement. Its 107 towers are placed on an average of 30 miles apart (not in a straight line but staggered slightly so that beams do not overlap and interfere). They range from a mere 14 feet high on the flats west of Great Salt Lake to 427 feet at Des Moines and 450 feet at the New York home station. Operating frequency is 3,700 to 4,200 mc, a bandwidth of 500 *megacycles* which

permits carrying thousands of simultaneous telephone conversations as well as the east-west and west-east television channels. Together with the coaxial cable link, this microwave system ties all important television cities in the United States into one network, so that an important East Coast news event or a Hollywood opening can be viewed instantaneously on the television screens of the audience on the opposite coast as during the recent cross-country Presidential telecast.

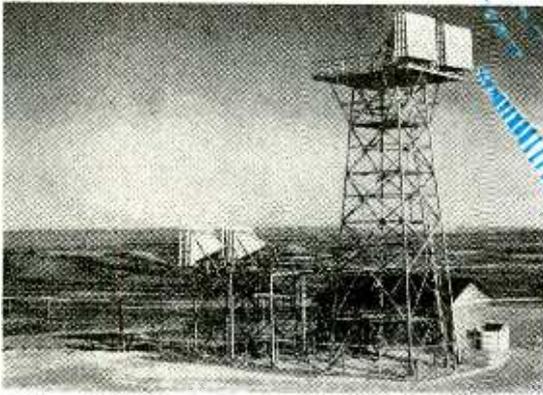


Continental Divide station at Creston, Wyoming.

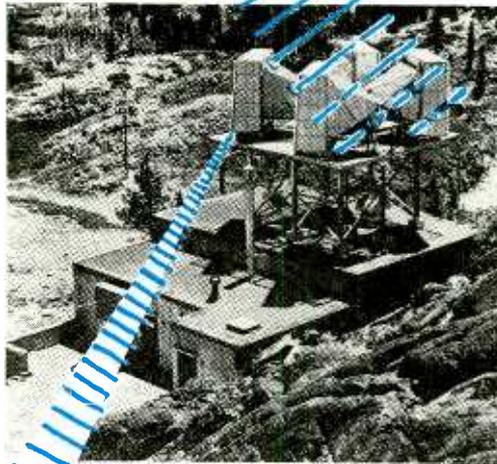
The microwave nets have solved the contradiction between coverage of vast areas and short transmission ranges. They bridge distances and serve regions that else might wait years for a coaxial line.



Relay station at Cisco Butte, California.

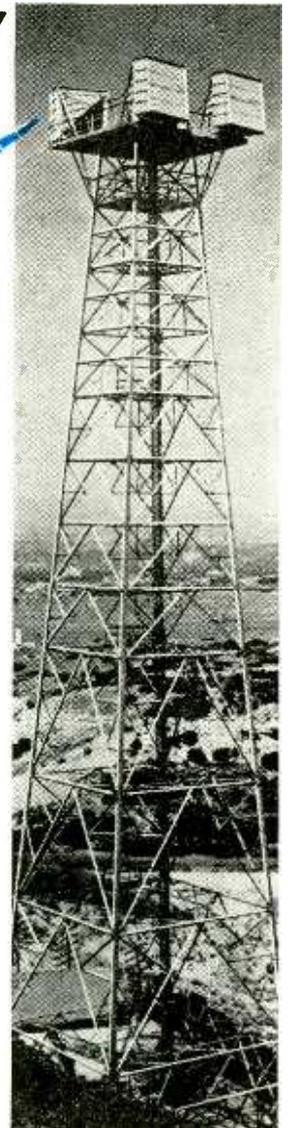


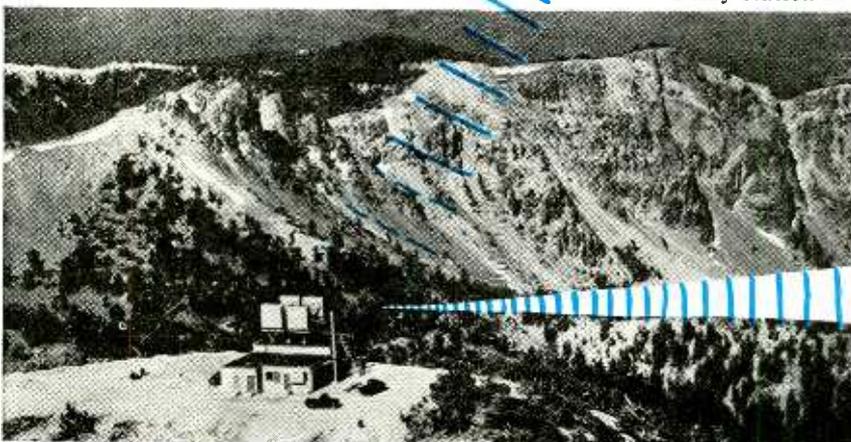The 200-foot steel tower at Salt Lake City, Utah.





System's highest station, at Mt. Rose, Nevada, is 10,000 feet above sea level.

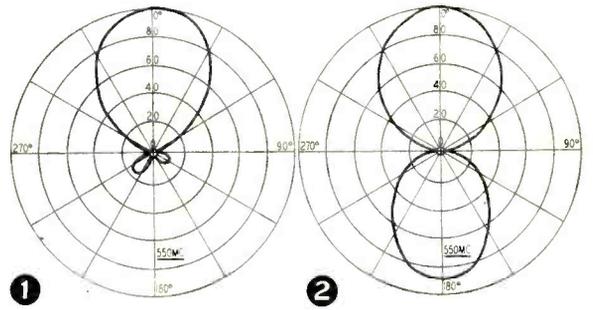All photographs courtesy Long Lines Dept., American Telephone & Telegraph Company.



**NEW
IDEAS
IN
U.H.F.
ANTENNAS**

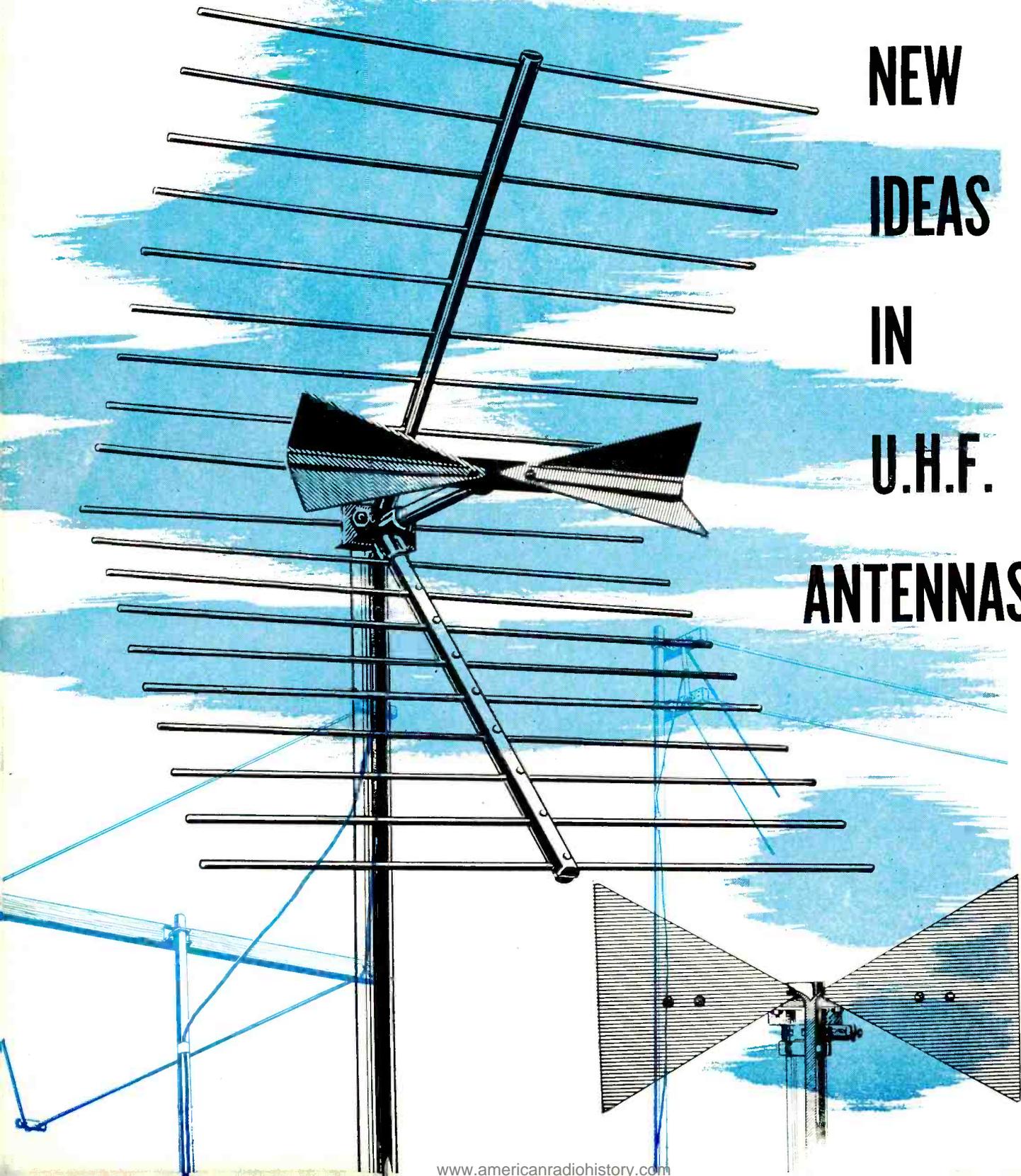

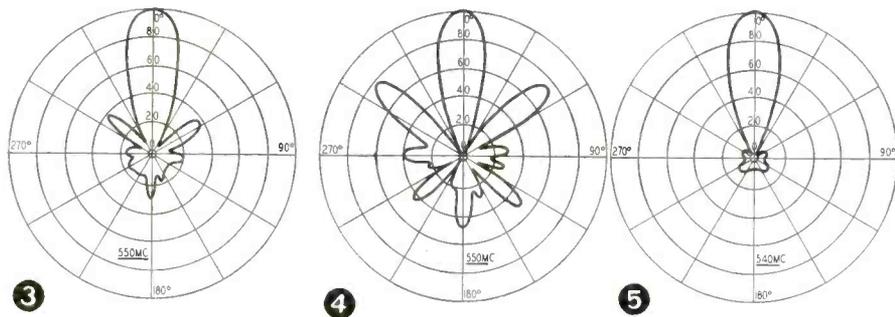

THE installation technician will have a new world of antennas to conquer when u.h.f. receivers reach the customer. While cut-down versions of v.h.f. antennas will operate well, the need for excellent signal pick-up and the possibility of using types that would be cumbersome at lower frequencies will without question create new favorite types.

A number of these are forecast in a report by E. O. Johnson, of the Advanced Development Section, RCA Victor Home Instrument Department, and J. D. Callaghan, of the RCA Service Co. Their report, based on actual experience in the service area of NBC's u.h.f. station at Bridgeport, Conn., is unusually complete and is illustrated with photos of the various antennas tried.

One of the most useful of the new types is the corner reflector, an antenna which is so cumbersome at lower frequencies that it is not commonly used. The horizontal directivity pattern is shown in polar pattern 1 above, and

the gain and bandwidth in graph 1. A simple dipole, or a fan dipole, may be placed in the focus of the reflector.

The fan dipole will probably be the most popular antenna in medium- or strong-signal areas. It is a slight modification of the standard dipole, and has somewhat greater gain and roughly the same directivity. See polar pattern and graph 2.







The rhombic, illustrated in the lower left corner and described in pattern and graph 3, is another high-gain antenna whose size limits its use on v.h.f. On the u.h.f. it can come into its own, and will probably be the preferred antenna where great gain, high directivity, and broad-band response must be combined.


The V antenna is theoretically a half rhombic and combines efficiency with simplicity and ease of installation. It lends itself well to stacking, as shown in the photo, and its gain increases with frequency (see graph 4), which is a very desirable feature at u.h.f. Graph and pattern 4 are for the stacked V.

Stacking can be used with excellent results for other types of u.h.f. antennas. The rhombic can be stacked for greater vertical directivity, as can the dipole.

The old standard Yagi is more than ever valuable in cases where bandwidth can be sacrificed for high gain. Used to receive a single channel, it produces more gain and has higher directivity than any antenna of comparable cost. See polar pattern and graph 5.

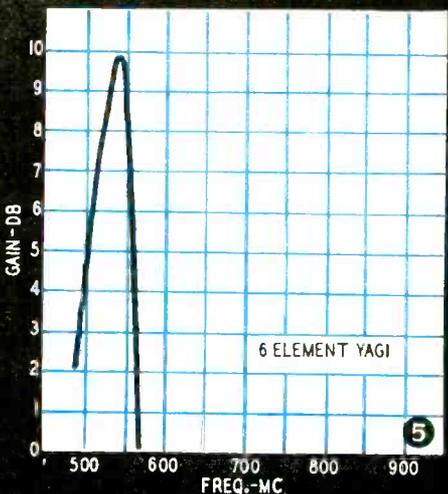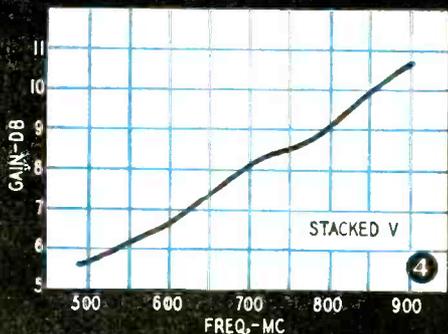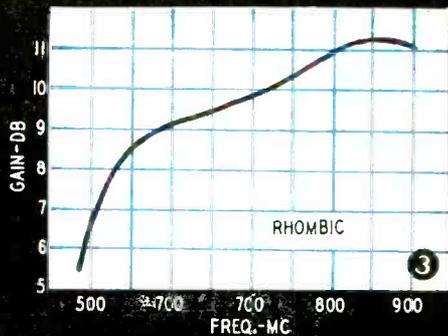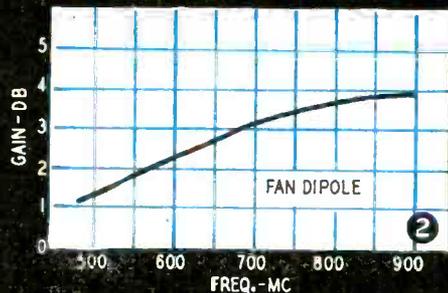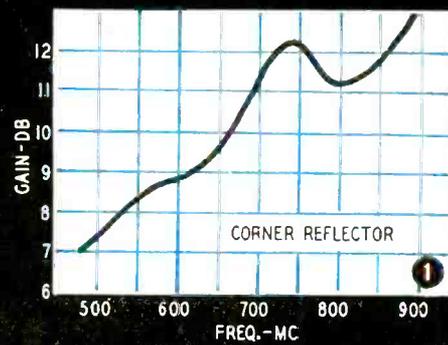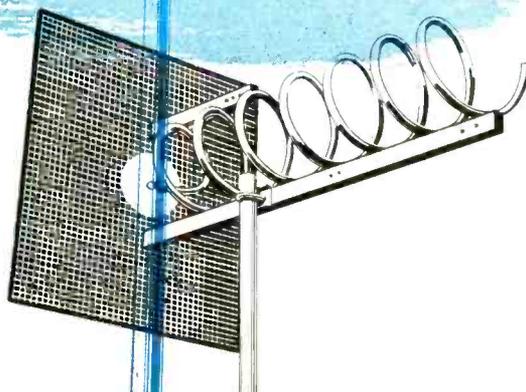A number of other types, such as the helical antenna illustrated here, are likely to be used. Some of them, such as the billboard, parabolic, and slot antennas, are modifications of equipment used in v.h.f. and v.h.f. broadcast work. Actual experience under varied conditions will determine if they will compete with the types already described.



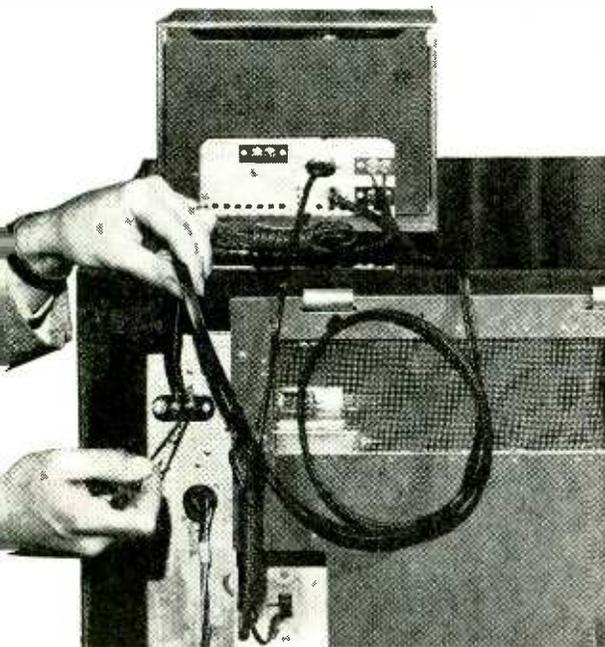


*Within two years we may have
1337 new television stations on
the air. Set owners will universally
want to have u.h.f. converters
and antennas installed*

By RUDY FRANK

U.H.F. Reception on V.H.F. Receivers

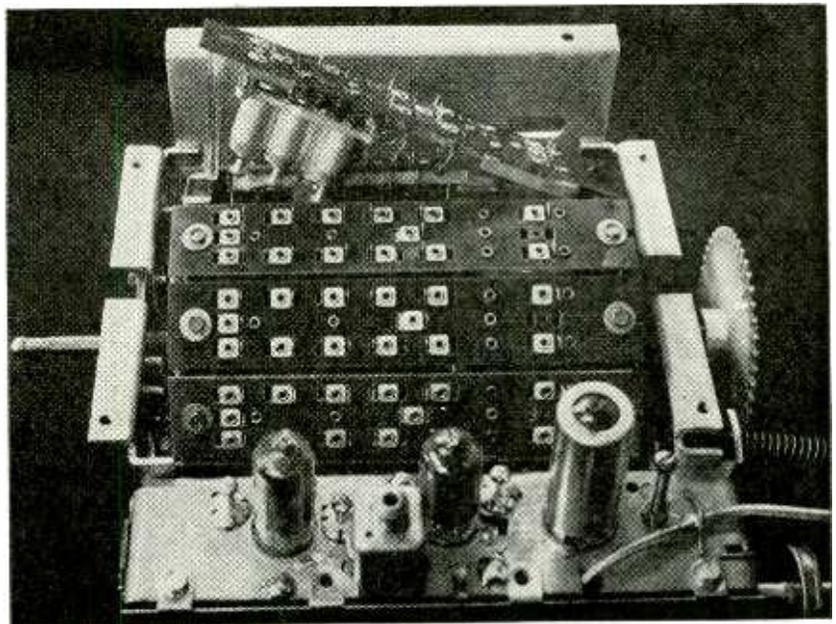Above — Installing an external u.h.f. converter is as simple as adding a booster. Right — U.h.f. strip as used in Zenith and other front ends.



THIRTEEN hundred and thirty-seven new television stations will go on the air within two years after the lifting of the freeze on the ultra-highs. With this distribution of u.h.f. TV stations to every nook and corner of the United States, service technicians may look forward to a bonanza. Set owners will universally want to have u.h.f. converters and antennas installed so they can avail themselves of the signals from the new stations in their communities.

The author has observed transmission from the experimental u.h.f. television station KC2XAK at Stratford, Connecticut, ever since it first went on the air in early 1950. After many tests and observations under all sorts of con-

ditions we are satisfied that u.h.f. television is commercially practical and in some ways a service superior to the present v.h.f. type of transmission. Manufacturers came to this conclusion early in the NBC-RCA experiment at Stratford and have developed u.h.f. converters which undeniably may be greatly improved upon in the future, but which are commercially practical for home installations right now.

There are two main ways in which the problem of u.h.f. conversion has been approached. One, which uses a separate external converter, is employed by manufacturers such as RCA-Victor, Crosley, Stromberg-Carlson, General Electric, Philco, and Westinghouse. With this type of conversion, the entire

u.h.f. band from 470 to 890 megacycles is made available to the set owner. Stations are tuned continuously on the converter. The second approach to the problem is employed by manufacturers who use the turret-type front end. Tuned, movable strips are supplied for the various ultra-high frequencies available in any given community. This method is of course limited in the number of stations which may be received to the number of positions on the turret-tuner. Two leading manufacturers will make this type of conversion available to set owners who have their receivers. One is Zenith which manufactures its own 13-position tuners. The other is the Standard Coil Corporation which although not a manufacturer of receivers

RADIO-ELECTRONICS for

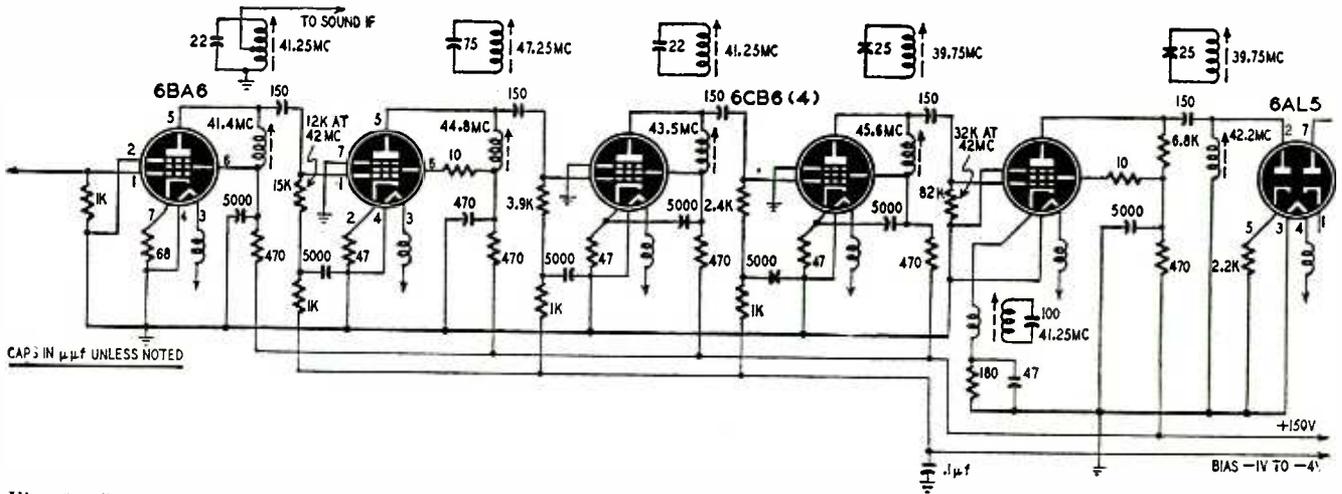


Fig. 2—One version of RCA's stagger-tuned 44-mc video i.f. strip. The 6AU6 is the converter; 6CB6's are amplifiers. Two 41.25-mc parallel-resonant circuits trap out the accompanying sound channel while the 47.25-mc circuit traps out the adjacent-channel sound. Two 39.75-mc circuits are included in the third and fourth stages to trap adjacent-channel video.

strip. RCA uses the 6CB6, and G-E the 6BC5.

4, *Servicing*: The higher i.f. makes servicing a more serious matter. Location of a ground is important. Placement of a bypass capacitor can affect performance. Replacement with exact duplicate parts is desirable. Alignment is more frequently necessary after servicing (even when only a tube is replaced), particularly with permeability slugs. Where any direct i.f. interference is a problem installing an i.f. trap in the antenna lead-in usually corrects the condition.

Circuit considerations

A suitable television i.f. amplifier tube requires high transconductance for high gain and low grid-plate capacitance for low feedback. The combination of reduced grid-plate capacitance and high transconductance of the 6CB6 make it possible to obtain higher gain with this tube than with others.

Note the over-all gain as well as the effective stage gain for the tubes listed in Table II. The 6CB6 tube is highly suited for both the 24- and 44-mc i.f. band. The separate grid No. 3 connection of the 6CB6 makes it possible to use an unbypassed cathode resistor to reduce variations in input capacitance and conductance with changes in bias.

Because the only capacitance in the tuned circuits of most television i.f. amplifiers is that of the tube electrodes and associated wiring, a large increase in output capacitance causes a decrease in plate circuit impedance and a consequent loss in gain. The maximum grid-plate capacitance for the 6CB6 is 0.020 μ f and its output capacitance is only 1.9 μ f.

When the grid bias of an i.f. amplifier is changed to vary the gain, both input capacitance and input conductance of the tube vary also, and the shape of the pass band is changed. In a TV receiver employing a.g.c. the i.f. response will vary. To compensate for changes in input capacitance and input conductance an unbypassed cathode resistor should be used with the 6CB6 because of its separate grid No. 3 connection. A

47-ohm resistor is just about optimum, but because it is too small to provide proper bias, it must be supplemented with fixed bias, or with additional cathode bias supplied by a 130-ohm bypassed resistor. The circuit shown in Fig. 2 requires fixed bias of -1 to -4 volts.

Because tube capacitance varies slightly from tube to tube, retuning is necessary when tubes are changed to obtain the same bandpass characteristics. At frequencies higher than 30 mc it becomes difficult to ground the

screen grid effectively because of the inductance of its leads and those of the bypass capacitor. It may be necessary to adjust the lead inductances so that they are in series resonance with the bypass capacitor to ground the screen grid effectively.

These remarks apply specifically to the circuit shown in Fig. 2, which is an RCA development of a 44-mc i.f. circuit designed around the characteristics of their 6CB6.

—end—

TABLE I

Channel	Channel band in mc.	Picture carrier frequency	Sound carrier frequency	21.25-mc i.f. sound; osc. above on all channels	41.25-mc i.f. sound; osc. above on all channels	41.25 mc-i.f. sound; osc. above on channels 2-6 and below on channels 7-13
2	54-60	55.25	59.75	81.0 ¹	101.0 ⁴	101.0 ⁴
3	60-66	61.25	65.75	87.0 ²	107.0	107.0
4	66-72	67.25	71.75	93.0	113.0	113.0
5	76-82	77.25	81.75	103.0	123.0	123.0
6	82-88	83.25	87.75	109.0	129.0	129.0
7	174-180	175.25	179.75	201.0 ³	221.0	138.5 ^{5,6}
8	180-186	181.25	185.75	207.0 ³	227.0	144.5 ⁶
9	186-192	187.25	191.75	213.0 ³	233.0	150.5 ⁶
10	192-198	193.25	197.75	219.0	239.0	156.5 ⁶
11	198-204	199.25	203.75	225.0	245.0	162.5
12	204-210	205.25	209.75	231.0	251.0	168.5
13	210-216	211.25	215.75	237.0	257.0	174.5


NOTES:

- ¹ There may be channel 5 interference as a result of oscillator radiation. FM stations may also be received on the image frequency.
- ² There may be oscillator radiation interference on channel 6.
- ³ There is likely to be oscillator radiation interference on channels 11, 12, and 13.
- ⁴ In some localities there may be image interference from 144-mc amateurs.
- ⁵ There may be image interference from channel 6.
- ⁶ There may be image interference from FM broadcast stations.

TABLE II

4-TUBE COMPLEMENT FOR STAGGER-TUNED I.F. AMPLIFIER

Tube	Over-all Gain	Effective Average stage gain	Interelectrode capacitances			
			input μ f	output μ f	g-p μ f	gm μ mhos
24 mc only						
6BA6	1,300	6.0	5.5	5.5	0.0035	4400
6AU6	3,000	7.5	5.5	5.0	0.0035	5200
6AG5	6,500	9.0	6.5	1.8	0.025	5100
24 or 44 mc						
6AK5	10,000	10.0	4.0	2.8	0.02	5100
6CB6	14,500	11.0	6.3	1.9	0.020	6200

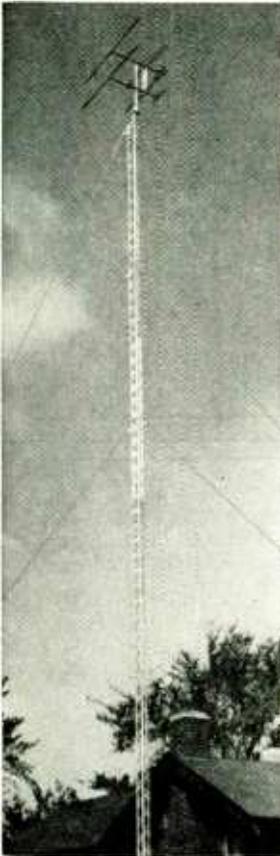

The antenna of observer M.C. Butler of Burlington, Iowa.

TV DX IN

1951

By

EDWARD P. TILTON*

An analysis of the year's reports, with a glance at the possibilities for 1952.

ONE June day back in the early 1930's, hams working the 5-meter band in the cities of the Eastern Seaboard were amazed to hear interfering signals from midwestern stations breaking through. The frequency band used was 56 to 60 mc, now the upper two-thirds of TV channel 2. Amateurs had been developing interest in this band for

*V.h.f. editor, QST.

several years. There had been scattered reports of 1,000-mile dx as far back as 1926, but few workers placed much faith in them. After all, didn't the best authorities in the propagation field state that there could be no ionospheric reflection of frequencies higher than about 30 mc or so?

Many, including myself, felt that they were being tricked, and were a bit reticent about discussing their experiences, for fear of being laughed down if they showed any signs of "falling for it." But as they began to compare notes, principally through the reports published in the magazine QST, it became apparent that dx on "5" was an accomplished fact.

What a tantalizing will-of-the-wisp it was! Appearing out of nowhere, the dx stations would boom in for a few minutes and then, with a precipitate fade quite unlike anything in previous dx experience, drop out again, perhaps to be replaced by signals from another section of the country in a matter of minutes. What manner of dx was this? After nearly 20 years of observation and study we still don't have all the answers, but we have learned quite a bit. Detailed observation by amateurs and TV dx enthusiasts¹ has been very useful in formulating some rules and predictions.

It is now generally accepted that this reflection back to earth of signals that otherwise would dissipate into space is

the result of patches of dense ionization in the E-layer region of the ionosphere, some 50 miles above the earth's surface. We know that there are two definite times when such dx is most likely to occur: one period from May through July, and the other period around the end of the year. We also know that despite this well-defined pattern, TV dx can take place at any season. We observe a general diurnal pattern, with peaks in the morning and early evening hours, but it does not always work that way. The usual dx range is between 600 and 1,200 miles, but signals have been received as close as 300 miles—the maximum dx is largely a matter of conjecture. We have evidence that sporadic-E dx is associated with solar phenomena, but attempts at direct correlation with sunspot observations have been largely unsuccessful.

This still rather unpredictable nature of sporadic-E dx is a considerable factor in the popularity of this hobby. Considerable interest has been evidenced by the receipt by RADIO-ELECTRONICS in recent months of hundreds of individual observations of TV dx from 33 states, the District of Columbia, 3 Canadian provinces, and Mexico. These reports have been (and are still being) studied for possible new light on this intriguing phenomenon.

What the observations show

The seasonal nature of this dx is indicated by the charts of Fig. 1. The

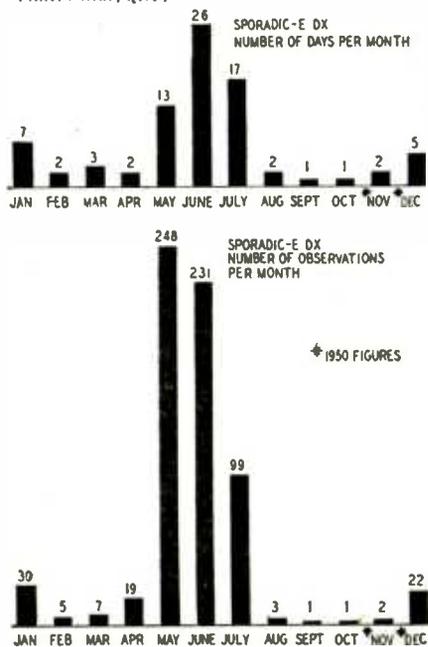


Fig. 1—Periodicity of dx-time is obvious.

¹Tilton: "What's The Mystery behind Television DX?" RADIO-ELECTRONICS, May, 1951, Page 28.

upper one, giving the number of days in each month when dx was observed, shows June as the top month for TV dx. Note that only four days showed no dx report, and on at least two of these observations by amateurs working on 50 mc (not included in the chart) suggest that TV dx might have been possible. Yet we still encounter individuals who regard TV dx as something rare or freakish!

The lower chart indicates the number of reports for each month. The apparently contradictory reports for May and June in these graphs is probably the result of an especially favorable condition on May 30, a holiday when more than the usual number of daytime observations would be made.

Reports for 1950 are used to illustrate the minor year-end peak: because the autumn figures are not complete as this material is being prepared for publication.

The inverse relationship between transmitter frequency and E-layer dx is shown graphically in Fig. 2. Here we see that low-end channel 2, with only 12% of the stations, accounted for nearly 28% of the reports. The champion dx station of the country, KPRC, Houston, Texas, was reported no less than 71 times—nearly as many loggings as for all 30 stations on channels 5 and 6 combined! From the tabulation of stations it may be seen that all known stations on channels 2 and 3 were logged. Of 28 stations on channel 4, all but 2 were reported. Four channel 5 stations eluded the dx'ers, and only 6 out of 11 stations on channel 6 made the grade. The remaining stations; WNHC, WHAM, WTVN, WFIL, and WTVR are all fair game and make nice targets for avid TV dx'ers.

The data on Fig. 2 agrees well with a similar chart in the May issue that was prepared from the much smaller number of 1950 observations. The slight disparity in station totals is the result of the inclusion in this year's analysis of stations in Cuba, Mexico, and Brazil.

Obviously, a station in the center of the country has a better chance of running up an impressive total than one in a coastal area. Nonetheless the greater prevalence of sporadic-E in southern latitudes can be seen from the tabulation of dx reports by station and channel.

The impressive record of KPRC is, certainly at least in part, the result of a combination of these factors; but notice the preponderance of southern stations in the upper brackets of dx reports. Only on channel 3, which has no representative in the Deep South, is the lead held by a Midwestern station, KMTV of Omaha, Neb. The top ten listings for channel 4 shows no station above the Mason-Dixon line. WBAP of Fort Worth, Texas almost monopolizes the channel 5 score, and CMQ of Havana, Cuba, KOTV of Tulsa, Okla., and WDSU of New Orleans, La., seem to dominate on channel 6.

JANUARY, 1952

Some outstanding records

With reports running into the hundreds for the more active months, it is obviously impossible to publish them all in detail. Several deserve special mention, however. Observer Canning, of Halifax, Nova Scotia, is the proud possessor of the verification from PRF-3, Sao Paulo, Brazil, reproduced on page 31 of the October issue of RADIO-ELECTRONICS. This record of reception over a distance of nearly 5,000 miles is shared by observer Jordan, of Grand Rapids, Mich., who also picked up PRF-3 on June 11. This is one TV dx record that has no counterpart in amateur two-way v.h.f. communication. No U.S. or Canadian amateur has yet contacted Brazil on 50 mc. Observer Canning also claims one of the longest distances ever logged for a U. S. station, with KPRC of Houston, Texas—over 1,900 miles.

Worthy of note is the unusually complete and concise log of D. V. Dixon, of the Service Appliance Co., Deming, New Mexico. Despite a high noise level, Dixon was able to log dx on 31 out of 67 days from May 23 to August 1. On several other days there was intermittent dx that was not identifiable.

Down in Miami, observer Hall was able to pick up dx almost daily after the latter half of April. On July 9 and 10 he logged 26 different stations in a period of less than 24 hours, including Mexico City and San Francisco. The latter is the only transcontinental TV dx reported to date. The log of Jim Morrow of Brantford, Ontario, contains 41 different calls.

The reports of the more than 100 other keen observers listed at the end of this article were extremely helpful, and their co-operation is appreciated.

What about the high channels?

The foregoing is all very well for channels 2 through 6, but where do the more than 35 different stations now tele-

casting on channels 7 through 13 come in? The answer is that they don't—at least as far as ionospheric dx is concerned. The absolute limit for the reflection of signals from the E-layer is not precisely known, but indications point to a frequency well below channel 7.

As pointed out in the May article, signals on the higher channels have a pretty good chance of being received at distances of a few hundred miles as a result of the greater ease with which they are refracted by temperature and humidity variations in the lower atmospheric strata. Since this bending takes place in the first few thousand feet above the ground level, the resultant dx is more an extension of the normal coverage than the ionospheric skip effect as observed in the reports.

A typical example is reported by observer Canning, who has picked up WJAR, Providence, R. I., on channel 11, and by observer Smith of Hampton, Va., who has logged the same station when weather conditions were favorable. The distances involved were 400 miles or more. Such reception of high-band signals over distances of 500 miles and more is fairly common in areas where stable stratifications occur frequently in the lower atmosphere. The "smoke bar" over the Great Lakes or a river valley at dusk, with thin over-running high cloudiness, are two usually favorable signs. Undoubtedly many observers have achieved excellent results on these frequencies, but these instances of high-band dx have gone unreported, because the distances involved are not quite so spectacular as those reported for the lower channels.

Prospects for 1952

There is as yet no magic formula with which we can make detailed predictions for E-layer dx a year in advance. Analysis of the data in Fig. 1 however, will enable us to get a fair idea of what is in prospect. Careful ob-

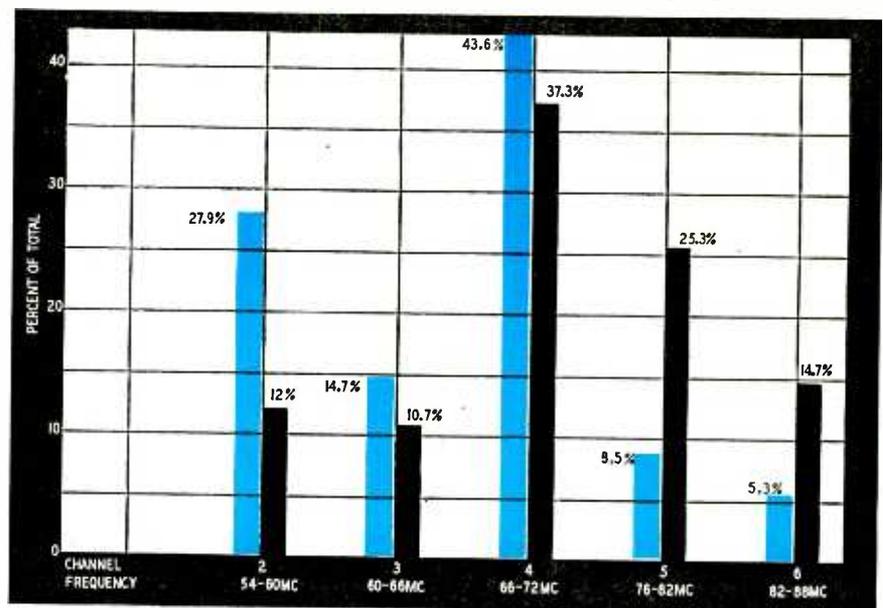


Fig. 2—Blue columns indicate reports, black columns stations, on each channel.

servation of weather conditions at the beginning of the dx season should furnish a few clues as to the periods when the biggest skip reception opportunities will develop. (The 27-day cycle becomes a useful rule-of-thumb.)

The variation from year to year seems to be a matter of degree. It is well known that there is more dx some years than others, but we're not sure just why. There is some indication that sporadic-E dx is more prevalent in years of low sunspot numbers (which should make 1952 a good year). Unfortunately the long interruption of amateur v.h.f. operation during the war years cost us our first chance to observe the workings of a complete 11-year solar cycle.

There are, however, some important compensations: Receivers and antenna designs are improving, particularly for the high bands. Transmitters are being licensed for higher effective radiated power, so signals will be carrying somewhat farther. New dual-triode front-end designs effect as much as 10 db improvement in the signal-to-noise ratio of some 1952 receivers. By using some really high-gain antenna arrays designed especially for the high channels we should be in for some dx surprises.

Of course there's also the prospect of u.h.f. TV. Barring unfavorable international or economic conditions we'll probably have some commercial exploitation of the u.h.f. band before 1952 is over. Many receivers, at first, will be makeshifts, incapable of making full use of the u.h.f. possibilities. But they will improve, just as today's receivers are so tremendously advanced over those of a few years ago. Activity in the u.h.f. field will be a bonanza for the inventive experimenter. It would not surprise me if next year's Television Issue of RADIO-ELECTRONICS included some u.h.f. dx reports!

LIST OF OBSERVERS

Alday, Carl, Lamar, Ohio
 Allen, James P., Fayette, Miss.
 Alverman, H. W., Toledo, Ohio
 Anderson, Clarence, Burlington, Kan.
 Anderson, John, Centerville, Iowa
 Austin, G. R., Shawnee, Okla.
 Barr, Robert L., Canton, N. Y.
 Bashta, William, Los Alamos, N. Mex.
 Baxter, R. H., Logtown, Miss.
 Beverlin, R. S., Toledo, Ohio
 Billings, Ray A., Shira, Texas
 Boyce, Jack, Green Bay, Wis.
 Brenner, Syd, Montreal, Quebec
 Brewer, Elmo M., Crossville, Tenn.
 Brookner, Stephen, Providence, R. I.
 Brown, Pvt. Maurice, Camp Pickett, Va.
 Brown, N. L., St. Johnsville, N. Y.
 Butlerbaugh, Ralph, New Philadelphia, Ohio
 Callan, Olive M., Altoona, Pa.
 Canning, L. A., Halifax, N. S.
 Champlin, C. E., Lyons, Mich.
 Christy, John, Sherman Oaks, Cal.
 Calbert, Ralph, South Bend, Ind.
 Coover, Richard, Willard, Ohio
 Culmer, Thad W., II, Robinson, Ill.
 DeGroat, F. E., Salamanca, N. Y.
 DePeter, R., Harrisburg, Pa.
 Dixon, D. V., Deming, N. Mex.
 Dull, Rex, Washington, D. C.
 Dunn, John L., Springfield, Mo.
 Durrell, Bruce, Knowlton, Quebec
 Elwell, James L., Italy Valley, N. Y.
 Everist, O. G., Easton, Ill.
 Forshay, E. P., Amite, La.
 Foster, E. G., Goodland, Kan.
 Garvey, Walter H., Andover, Ohio
 Germain, J., Opa Locka, Fla.
 Gervais, Gerry, Mairo, N. Y.
 Glahe, Fred R., Cookeville, Tenn.
 Goldmeister, Morris, Gaylord, Minn.

Good, Wendell, Erie, Pa.
 Greynolds, Mrs. Earl, Adamay, W. Va.
 Grout, Robert M., Medina, N. Y.
 Groves, A. L., Brooke, Va.
 Gummo, Mrs. Wm. L., Harrisburg, Pa.
 Gunderson, Alfred, Savanna, Ill.
 Hall, E. R., Miami, Fla.
 Hapman, R. C., Portsmouth, Ohio
 Harpole, Tony H., Clinton, Ky.
 Haugland, B. W., Pequot Lakes, Minn.
 Hiatt, Richard L., Portsmouth, Ohio
 Higginson, Howard, Blytheville, Ark.
 Holmes, Ira, DeLand, Fla.
 Horn, Mac, Los Angeles, Cal.
 Hubbell, Courtland G., Ashburnham, Mass.
 Huff, Hadley, Leesburg, Ohio
 Johnson, Ronald E., Webster, Ohio
 Jordan, Frank, Grand Rapids, Mich.
 Kastner, R. W., New Braunfels, Texas
 Keyser, R. W., Van Wert, Ohio
 Knutson, George, Pequot Lakes, Minn.
 Kravitz, Herbert, Atlantic City, N. J.
 LaBrecque, Leon J., Lincoln, N. H.
 Langlois, Darius, Ste. Marie Cte Beauce, Quebec
 Laskaris, Leon, Warren, Pa.
 Lazarus, Billy, Houston, Texas
 Lofgren, R. L., Rush City, Minn.
 Lundy, Robert, Findlay, Ohio
 Malwitz, Harry A., Sheboygan, Wis.
 Manning, G. N., Dalton, Ga.
 Martin, Jack H., Port Credit, Ont.
 Matz, Dr. Homer F., Ash Grove, Mo.
 Maupin, Ted, Yuba City, Cal.
 McCall, Leland W., Woodston, Kan.
 McCollon, Lt. V. L., Atlantic, Va.
 McLaughlin, C. F., Birmingham, Ala.
 Meares, C. B., Enka, N. C.
 Meyer, Julien, Benson, Minn.
 Miller, Albert A., Palm Beach, Fla.
 Miller, C. L., Chattanooga, Tenn.
 Millott, Don, Hopkins, Minn.
 Mitchell, A., Fallbrook, Cal.
 Morrow, Jim, Brantford, Ont.
 Murphy, William, Granite City, Ill.
 Needy, W. H., Hagerstown, Md.
 Newton, Reed, Greenville, Ill.
 Nichols, Den, Mason, Mich.
 Oyamburu, Francisco, Mexico City

Parrott, C. M., Houston, Texas
 Pate, Rembert, Clio, S. C.
 Patterson, N. Gentry, Sedalia, Mo.
 Penc, Stanley J., Utica, N. Y.
 Pigen, Gordon, Madoc, Ont.
 Pyrow, Earl, Athens, Ga.
 Randall, John, Hanover, Mass.
 Rowley, David, High Point, N. C.
 Robarge, R. J., Chicopee Falls, Mass.
 Robbins, Howard L., Tampa, Fla.
 Robinson, Clair, Rush City, Minn.
 Robson, C. A., Cedar Rapids, Iowa
 Roeder, Jack, Spencerville, Ohio
 Rutledge, Jerry, Waseca, Minn.
 Sagel, Leslie, Wildwood, N. J.
 Schield, Richard K., Scranton, Pa.
 Scherf, Paul, Andalusia, Ala.
 Schmidt, W. H., Washington, D. C.
 Scholey, W. B., Toronto, Ont.
 Shreve, Joe, Flint, Mich.
 Simons, Donald, Winsted, Conn.
 Smith, Sterling, Hampton, Va.
 Smith, William, Strabane, Pa.
 Sparks, Coy M., Alice, Texas
 Spencer, Verne, Jeanette, Pa.
 Staner, M. C., Tulsa, Okla.
 Stanley, P. J., Minneapolis, Minn.
 Stevenson, E. N., Decatur, Ill.
 Stevenson, M. L., Wichita, Kan.
 Storch, Clarence, San Antonio, Texas
 Swanson, Earl, Rockford, Ill.
 Symons, Arthur, Larksville, Pa.
 Thomson, W. H., Peoria, Ill.
 Troyan, James A., Youngstown, Ohio
 Upholster, Russell, Latrobe, Pa.
 Vail, Joe F., Indianapolis, Ind.
 Vanderfelt, Paul, Muskegon Hts., Mich.
 Van Hook, Donald, Tecumseh, Mich.
 Ventolo, Joseph, Jr., Enon, Ohio
 Wallace, W. H., Santa Anna, Texas
 Ward, John F., Jr., Norfolk, Va.
 Whiteside, Richard, Corcoran, Cal.
 Whitfield, L. A., Altoona, Pa.
 Wilcox, W. W., Richmond, Va.
 Willis, J. E., St. Petersburg, Fla.
 Wilson, R. P., Toronto, Ont.
 Wnukowski, P. P., Kingston, Pa.
 Yeager, Claude C., Wichita, Kan.

TABULATION OF DX REPORTS BY STATION AND CHANNEL

Channel 2, 54-60 Mc., 9 stations

KPRC	Houston, Texas	71	WFMY	Greensboro, N. C.	14
WMAR	Baltimore, Md.	24	KTSL	Los Angeles, Cal.	11
WJBK	Detroit, Mich.	19	XETV	Mexico City	4
WCBS	New York City	19	XEW	Northern Mexico	3
			K12XBN	Atlanta, Ga.	3

Channel 3, 60-66 Mc., 8 stations

KMTV	Omaha, Neb.	22	WTMJ	Milwaukee, Wis.	7
WPTZ	Philadelphia, Pa.	18	WDTV	Pittsburgh, Pa.	6
WBTY	Charlotte, N. C.	17	WKZO	Kalamazoo, Mich.	3
WLW-C	Columbus, Ohio	13	PRF-3	Sao Paulo, Brazil	2

Channel 4, 66-72 Mc., 28 stations

WKY	Oklahoma City, Okla.	27	WOI	Ames, Iowa	6
WMBR	Jacksonville, Fla.	24	WRGB	Schenectady, N. Y.	6
WQAI	San Antonio, Texas	23	WBEN	Buffalo, N. Y.	5
WDAF	Kansas City, Mo.	21	WBZ	Boston, Mass.	5
KRLD	Dallas, Texas	20	WSM	Nashville, Tenn.	4
CMUR	Havana, Cuba	19	KRON	San Francisco, Cal.	4
XHTV	Mexico City	18	WNBW	Washington, D. C.	4
WMCT	Memphis, Tenn.	17	WNBK	Cleveland, Ohio	2
WTVJ	Miami, Fla.	16	KNBH	Los Angeles, Cal.	2
WTAR	Norfolk, Va.	9	WNBT	New York City	2
WTCN	Minneapolis, Minn.	8	WLW-T	Cincinnati, Ohio	2
WHBF	Rock Island, Ill.	8	WWJ	Detroit, Mich.	1
WBRC	Birmingham, Ala.	6	KDYL	Salt Lake City, Utah	1

Channel 5, 76-82 Mc., 19 stations

WBAP	Ft. Worth, Texas	17	KSL	Salt Lake City, Utah	2
KEYL	San Antonio, Texas	5	WEWS	Cleveland, Ohio	2
WOC	Davenport, Iowa	5	WABD	New York City	1
KPIX	San Francisco, Cal.	4	WTTG	Washington, D. C.	1
KTSP	St. Paul, Minn.	3	KSD	St. Louis, Mo.	1
WNBQ	Chicago, Ill.	3	KTLA	Los Angeles, Cal.	1
WAGA	Atlanta, Ga.	2	KPHO	Phoenix, Ariz.	1
			WSAZ	Huntington, W. Va.	1

Channel 6, 82-88 Mc., 11 stations

CMO	Havana, Cuba	15	WFBM	Indianapolis, Ind.	2
KOTV	Tulsa, Okla.	6	WOW	Omaha, Neb.	2
WDSU	New Orleans, La.	5	WJIM	Lansing, Mich.	1

—end—

New Military Use for TV

THE 31-foot television truck on our cover represents possibly the boldest stroke in education by television ever made. The Army Signal Corps will use it to televise intricate military exercises and maneuvers, transmitting the signals back to base where they can be viewed on television screens by much larger numbers than could see them on the spot.

Not only can instruction in field problems be revolutionized by actually televising them on the field, but the camera will make visible "all the little things you wouldn't see if you *were* there," as one fan put it when describing a televised football game. Instruction can be more intensive as well as extensive.

The "caravan", as it has been called, consists of four special 10-ton 6-wheel coaches, each 31 feet long. The first contains the camera pickup and transmitting unit. It is equipped with three complete TV field camera chains, a microwave transmitter for transmitting the video signals, and a 45-watt FM transmitter for the sound signals.

The second mobile unit contains the power supply for the transmitting equipment. This consists of two 15-kva gas-driven generating units, each of which supply 120/208, 3-phase, 4-wire, 60-cycle power. One of the generators is designated for standby use, or for supplying power to special lighting equipment for illuminating the scene to

be televised. By a switching arrangement, the truck batteries are able to supply power to the two-way radio communication system when the caravan is in motion and the generators are not in use.

Receiving coaches

The receiver-display unit is the third coach in the caravan. In addition to housing the FM and microwave receiving equipment, it contains ten 16-inch picture monitors, a 16-mm TV projector and film camera, slide projector, and a large-screen television projector.

This equipment is so interconnected that TV picture and sound received by microwave can be switched to the ten monitors, or if desired, film can be used on the 16-mm TV projector and the picture and sound fed to the monitors or to the large-screen projector, which can be set up in a nearby building or shelter. The monitors are 16-inch TV receivers modified to receive only the video signal. Individual cables 500 feet in length for the ten receivers are stored on reels installed inside the vehicle. During setup, these cables are pulled out through small doors in the side of the coach and connected between the receivers and a distribution box. Two cables are required for each receiver. One carries the audio and video, the other is an a.c. power cable. Special dollies stored in compartments can be

quickly attached to the receivers for mobility over the viewing area.


The fourth coach contains a 15-kva gas-engine generator of the same type used in the transmitting unit. This generator supplies a.c. for the receiving equipment.

Microwave visual system

The RCA microwave transmitting and receiving system which handles the visual part of the TV signal is identical to that supplied by RCA to TV broadcast stations for studio-to-transmitter link and relay purposes. The 4-foot parabola provides a gain of 5,000 which—multiplied by the 100-milliwatt output of a klystron oscillator which feeds it—provides an equivalent power output of 500 watts. Since a 7,000-mc frequency is used, transmission is limited to a line-of-sight path. The parabolas at the transmit and receive positions are beamed toward each other to provide a high-intensity signal path. Transmitter and receiver units are mounted directly on the transmitting and receiving parabolas. In addition to these, control units for the transmitter and receiver are rack-mounted in the coaches. The control unit for the transmitter contains a video amplifier and modulator which frequency-modulates the klystron by varying the voltage on the repeller plate.

—end—

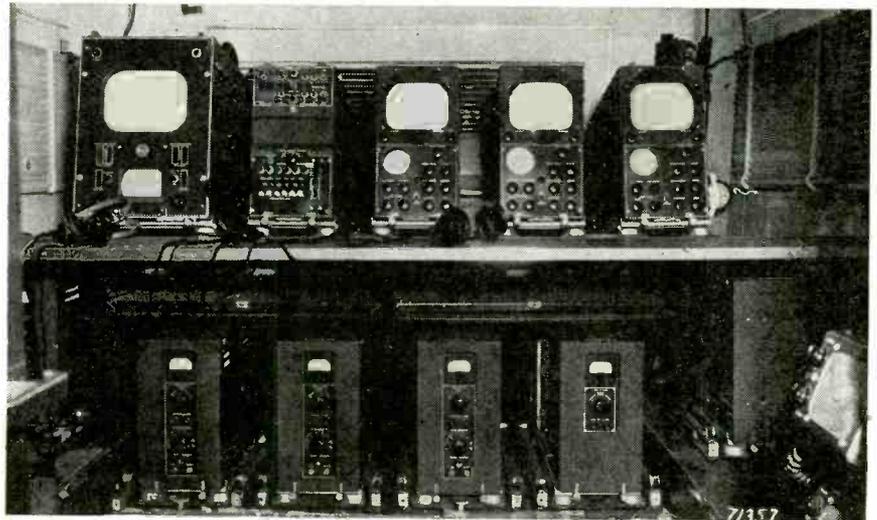Right—The desk mounted units in the transmitting coach are from left to right the master monitor, field switcher, and three field-type camera controls. Below these are the three field-type power supplies and a sync generator. Below—Transmitting truck with parabolic reflector and its companion power generating equipment truck.



Customer relations are certainly the most important thing in the TV service business. But they can be important in the technician's personal life, too. . . .



The Toughest Customer

By GUY SLAUGHTER

RADCLIFFE Bowman Junior surveyed the forest of antenna masts and guy wires dejectedly, shivered in the freezing wind, and softly cursed the fate that put him up on other people's roofs in the dead of winter. Then he singled out one of the antennas that looked unfamiliar to him, and eyed it closely.

"Nope," he said aloud. "Not mine." He followed the twisting ribbon of its transmission line across the roof to the parapet running around its edge, and leaned far out to look down. The transmission line entered a window several stories below, and he took a bearing on it. "Third window from the left," he muttered, "four stories down. That'd be the fourth floor." He picked up his tool

kit and headed for the roof door, hunching up against the icy wind.

The third window from the left on the fourth floor proved to belong to apartment 4D. "Miss Nancy Hammond," the little card said. Rad leaned on the doorbell, hoping she wouldn't be an unreasonable old hag. When the door opened he saw she was neither old nor haggy, and she didn't look unreasonable. She looked, instead, young and luscious. Her eyes were warm and her figure precisely filled her swishy housedress. She cocked an inquiring eyebrow at him.

"I represent Bowman Radio Service," Rad said in his best business voice. "I'm investigating the complaints of several of my customers here in the Brumley Apartments."

"How nice for them," Nancy Hammond said, her smile growing wide. "And there's something I can do?"

"Yes," Rad said, "there is something you can do."

"Well, come in." She swung the door wider. "Tell me about it."

"How long have you had your TV set?"

"About a week." She pursed her lips thoughtfully. "But if you're looking for business I'm afraid I haven't any. My set works fine. You can leave your card, though, and if I ever do have trouble I can call you."

"Thanks," Rad said. "But that isn't what I had in mind. Is your picture okay during the daytime?"

She shrugged. "I never use it during

RADIO-ELECTRONICS for

the day."

Rad nodded thoughtfully. The interference came only at night, according to his complaint cards; and it had begun just about a week ago.

"Would you mind turning your set on?"

"Not at all." She swished over to the disguised-plywood console, flipped a knob, and smiled back at him over her shoulder. "It takes a minute to warm up," she confided.

"Yeah, I know. Have you got a telephone?"

She pointed at the handset on the little table near the door, and a look of puzzlement crossed her features.

"Thanks," Rad said. He flipped one of the complaint cards from his pocket, found a number, dialed it. The handset buzzed in his ear, crackled, and then a voice grunted at him. "This is Bowman Radio Service," he said into the mouthpiece. "Is your TV set on now? Well, turn it on, will you? Yes. To the channel that's been giving you trouble. Yes, I'll wait." He turned to the girl. "Will you switch to the channel you use most, please?"

The girl frowned at him in mystification, shrugged, and flipped the selector switch. A swarthy-faced tenor filled the screen with teeth and the room with an aria. Rad put his finger to his lips, and she turned the volume down to a mere whisper.

"What's this all about?" she asked.

"What have you got?" Rad spoke into the telephone. "Wavy lines, huh? Sort of a moving herringbone suit? Like a rumpled pair of tweeds? Yeah. Well, watch now." He put his hand over the mouthpiece. "Turn it off, please."

The girl, looking more mystified than ever, snapped the switch, and the screen went blank.

"How now?" Rad asked the telephone.

"Yeah? Okay, thanks." He hung up, and turned to the girl again. "Your set radiates," he mourned.

"Huh?"

"Your TV set. It radiates a signal. It's lousing up my installations. I've got nine sets here in the building, and yours sabotages all of them."

Nancy Hammond's demeanor changed abruptly. Her chin thrust out belligerently, and her hands went to her hips. She was breathing hard, and from her eyes lightning flashed. For an instant Rad thought he heard the ominous rumble of rolling thunder.

"Just a darn minute," she was saying. "Who do you think you are, coming into my apartment like this and accusing my set of . . . of . . . of whatever you're accusing it of? It's a perfectly good set, and I get a good picture, and . . . and I think you're mean!"

She was advancing on him now, the lightning flashing more dangerously. He put up his hands and backed toward the door.

"Wait a minute," he said hoarsely. "Don't get me wrong. I . . . you . . . it's not your fault. It's just that it's a cheap set. You got gypped! You can't. . . ." He broke off as she seized

a bronze bookend from atop a handy table and heaved it at his head. He ducked, whirled, grabbed his tool kit, and ran for the door. Something heavy splintered the panels as he slammed it shut behind him. He raced down the hall to the elevator, dove inside the cage, and slid the gate closed before he dared take a breath. He fumbled in his pocket for his handkerchief, and mopped his sodden brow. "Wow!" he said aloud. "Is that dame a heller!" And then a mental image of her formed in his mind, and he sighed deeply. "But berrother, what a dish. . . ."

He pondered his dilemma all the way back to the shop. Here was a girl—and what a girl—with a bargain TV set that radiated like WLW and fouled up nine of his installations. The logical approach was to convince her of the fact, and then work the set over; shield the front end, maybe install a booster, whatever it took to kill the radiation. But judging from the lightning in her eyes, the bookend she had thrown, the heavy object that had all but broken the door down behind him—she wouldn't convince. He sighed, manhandled the truck into a parking place in front of the shop and climbed out, shaking his head wearily.

Bill Samples, his big, red-headed bench man listened to his troubles sympathetically. Then he waved a hand.

"A tough customer, huh?" He shrugged. "Call her up. Reason with her. Threaten her with the FCC if you have to. She can't throw anything at you over the phone line."

"Yeah," Rad breathed happily. "Sure. Bill, you're a genius. How'd you happen to think of that?"

"Aw," the red-head said modestly, turning back to the bench. "It just came to me." He dove into an upturned chassis and began snipping wires.

Rad went through the phone book feverishly, stabbed the number with a shaking finger, and dialed it wrong twice before he got the call through. His eagerness was natural enough, he told himself. He was merely anxious to serve his nine customers. The fact that the girl was a knockout had nothing to do with it. Nothing at all!

"Hello," he said cautiously into the mouthpiece when the click came through. "This is Radcliffe Bowman Junior, of Bowman Radio Service. Remember me?"

"Of course," she said softly. "I'm sorry I lost my temper, Mr. Bowman. You see I . . ."

"Think nothing of it," Rad said magnanimously. "All my fault." He gulped, swallowed. "And call me Rad."

"Thank you, Rad," she purred. "You're sweet."

"About your television set," he continued. "It does radiate, you know. Something fierce. I . . ." He paused, listening to a pretty dead wire. Muttering under his breath, he dialed the number again and talked fast when the click sounded. "Would you like to go to a movie with me this evening? I mean. . . . You would? I'll pick you up

about seven? Okay. Bye." He cradled the phone and stood a minute lost in thought.

Bill Sample's sarcastic voice broke into his reverie. "Fine way to out-manuever a tough customer, that is," he snickered. "Boy, what a general you'd make."

"If you can't lick 'em, join 'em," Rad countered. "It was an inspiration, regular fifth column stuff. I'll get to know her better, and then I can talk her into letting me work her set over."

"Nuts," the bench man drawled. "If you'd handled her right in the first place all this wouldn't be necessary. Where's your customer psychology? You know you can't tell a person his stuff's no good, especially a *dame*." He giggled. "Boy, you were really usin' the old brain when you called her set a cheapie."

"Yeah," Rad agreed. "But I can recover that fumble. If I take her out tonight she can't play her TV set and those other nine people *won't* be bothered with the interference." He nodded thoughtfully. "Yeah . . . I'll keep her out 'til after the stations are off for the night."

It was long after the final sign-off of the latest-running TV station in the area when Radcliffe Bowman Junior said his final goodnight to Nancy Hammond. The next morning when he got down to the shop he felt fine.

"Hi, General," Bill Samples said drily. "What a skirmish you must've had last night." He leered at Rad, winked owlishly. "I haven't heard you whistling like that since the day we got the Hotel Griffin installation contract."

"It's a nice day," Rad said cautiously. "I feel good. Any reason why I shouldn't whistle?"

"Yup. Seven reasons." He held up a handful of complaint cards. "Got seven calls from that apartment house so far this morning. There's still two to go—but it's early yet."

"Go on," Rad said incredulously, "you're kidding."

"Nope. Same old story. Interference patterns lousing up all seven sets most of the evening." His cheery smile irked Rad no end.

"But . . . but she wasn't home," Rad said. "How could. . . ?"

The red-head shrugged, his grin growing.

"Maybe it ain't her set after all."

"It's her set all right," Rad insisted. "I'll bet she forgot to turn it off when I called for her." He nodded sagely. "That must be it. I'll check it myself, tonight."

"Tonight?" Bill echoed, his grin fading.

"Tonight," Rad said firmly.

Radcliffe Bowman Junior floated through the evening in a rapturous daze, smugly reflecting that while he was enjoying Nancy's company he was serving the best interests of his customers as well. His nine clients in the Brumley apartments would be pleasantly entertained by the programs of their choice, unmarred by lines or patterns. While Nancy was getting her coat

from the closet he had scrupulously made it a point not only to turn off her set, but even to pull the power plug from the wall receptacle so that there would be no mistake. Furthermore, he intended to keep her out until the programs ended—strictly for his customers' sake.

The next morning he couldn't believe his eyes when he walked into the shop and saw Bill Samples gleefully waving aloft a handful of complaint cards for his inspection.

"Hi, General," Bill leered, "the war ain't over yet."

Rad stared at the cards belligerently, grabbed them, and leafed through them. There were eight of them today, all from the Brumley Apartments. Every blessed one complained of severe and lasting interference last night. Five of the cards bore notations to the effect that Bowman Radio had better either fix their sets or come and get them. Rad reached for a handful of hair, found it, and tugged wildly.

"It can't be," he moaned. "I checked every other possible source in the building, and her set is the one. Besides I didn't take her home 'til long after midnight."

"Maybe she's got company," Bill leered. "Maybe the iceman cometh in and uses her set while you're out with her."

"Yeah," Rad said doubtfully. "Maybe an uncle or a cousin. . . ."

"Or a boy friend," Bill finished. "Got a date tonight?" Rad nodded. "Fine," the red-head continued, winking, "I'll head up there while you two are out and see who's home. It'll be sort of a flank strategy. Okay, General?"

Rad nodded, wordlessly.

"And if someone *is* home," the bench man went on smugly, "I'll use customer psychology." He winked again. "With the right approach I'll be able to look the set over and do whatever I want to do, no questions asked."

"The cousin or uncle or whoever it is will heave you out," Rad said. "It's a tough family, if they're all like Nancy." Then he set his jaw and clenched his fists. "I'll win this battle myself. I'll put it up to her tonight. I'll tell her what would happen if I had to take back nine TV sets and refund the customers' money. I'll convince her she should cooperate and let me iron out the trouble." He took a deep breath. "I think we're well enough acquainted now." He looked at the floor, flushing modestly. "I figure she's pretty much interested in my welfare."

"Forget that angle," Bill Samples said cynically, shaking his head. "She's a dame, ain't she?"

"Yeah," Rad breathed enthusiastically. "And how. . . ."

The evening had gone well, so far. The movie had been good, the popcorn dripping with butter, and here in the restaurant the juke box was moaning soft music as they chomped contentedly at their hamburgers. Radcliffe Bowman Junior finished his, automatically noting the juke's hum-level, wondered how long

those filters had been in and wiped his mouth on a paper napkin. He drained that last drop of his coffee, and cleared his throat.

"Uh, Nancy," he coo-ed. "Uh, there's something I've been meaning to say."

"Yes?"

"I. . . well, the fact is, your TV set radiates," he began diplomatically.

"Yes?" Something in her tone sounded a little alarm in the back of his head, but he ignored it and plunged on, staring at the table cloth.

"I've got nine customers in your building and if you don't let me fix your set they'll make me take their sets back, and there's really nothing wrong with them. Nine TV sets cost an awful lot of money, and. . . ." He broke off, sensing her movement, and looked up. Nancy Hammond was standing up, her chin outthrust, her hands on her hips, breathing heavily.

"So that's why you've gotten so chummy," she snapped. "I should have known. You've been dating me every evening just so I couldn't play my set. And you're the one who unplugged it last night. My father thought it was broken when he came home from work and if he hadn't just happened to notice the plug out he wouldn't have been able to use it all evening!" Her voice shrilled higher and higher, and every customer in the place started goggling at them.

"I. . . I. . . ." Rad began, and then he saw her grab the heavy glass ashtray off the table and hurl it at his head. He tried to duck. Thunk. Something exploded inside his brain, and he was up on a high roof in a cold wind, dodging under guy wires, reaching for a mast, twisting it with a pipe wrench so that the dipole high above his head swung forty-five degrees around. Then he fell off the roof, drifting slowly down past hundreds of windows out of which hundreds of beautiful Nancy Hammonds winked invitingly at him, and landed on his head in a soft, warm snowdrift.

He opened his eyes, looked foggily about, surprised to find himself still in the restaurant, stretched out on the floor. His head thumped like a jungle tom-tom, but he didn't mind—it was cradled in a soft lap, and above the lap, next to his ear, there rose a waist, and above the waist there was a face, and in the face the eyes were brimming with tears. A voice floated down to him.

"Oh, Rad," it was saying between sobs. "I'm so sorry I hurt you. I lost my temper when I found out you didn't really like me for myself. . . ."

"Nonsense!" Radcliffe Bowman Junior said gallantly. He started to sit up, and on second thought, settled back into the lap again. He flicked a hand at the people crowding around them. "Beat it! Can't a couple have any privacy around here?" The crowd dispersed, and he looked up into the face again, making his voice come out stern and determined. "I'll not have any more of these childish temper tantrums, do you hear? And you're not to throw things, ever again!"

"Yes, Rad," Nancy Hammond said,

and her voice was tiny and obedient. . . .

"Hi, General," grunted Bill Samples dispiritedly, holding one hand over his left eye, when Radcliffe Bowman Junior entered the shop the next morning. "We lost the war."

"We did?" Rad murmured airily.

"Yup. Her old man's the bozo that plays the set at night. He lives with her, and he won't listen to reason. Most unreasonable man I ever saw. Used my best customer psychology, too. I told him he'd won a booster in a drawing we'd held, and tried to install it for him, figuring it would kill the radiation by isolating the antenna from the front end of the set." He sighed deeply. "But the old guy wasn't having any. Said it took extra current, ran up the light bill, and didn't help the picture anyway."

"Too bad," sympathized Rad.

"Yeah, but that ain't all. I got mad and told him he had a bargain set that radiated, and he bopped me. See?" He dropped his hand to display a beautiful shiner neatly outlining his left eye, and shrugged disconsolately. "He's a toughie."

"Yeah," Radcliffe Bowman Junior said cheerfully. He paused. "You could have gone up on the roof and rotated the antenna until the signal pick-up fell off, and *then* brought in your booster." He cocked a quizzical eyebrow at his bench man.

"Hey!" Bill said admiringly, a sickly grin showing on his face. "Good strategy, General. Then the old man could see an improvement in his picture, and he'd be tickled to have the booster."

"Roger," confirmed Rad. He sighed contentedly. "But you can forget the booster business."

"How come?" The red-head's grin faded.

"I met Mr. Hammond last night, too. Along about midnight. And I twisted his antenna around when I left. As soon as he calls up tonight complaining of weak signals and bad pictures, you rush him out a new set to use. Bring his old one in. And don't forget to re-orient the antenna when you get the new set hooked up."

"What makes you think he'll call us?" Bill demanded, mouth agape.

"He'll have to. I left our card on the table, and stole his phone directory."

"Even so," Bill persisted, "I thought he was mad at Bowman Radio."

"Not any more. All is forgiven. We won the war, Corporal. Strategic tactics did it." He paused, smiled condescendingly, went on. "We'll loan Mr. Hammond a new set, and you can work over his old one while I'm gone. A little front end shielding ought to do the trick."


"Yeah," Bill Samples said uncertainly. "Where. . . where you going?"

Radcliffe Bowman Junior bestowed a look of pity on his slow-witted employee, and dropped one eyelid in a slow wink.

"If you can't lick 'em, join 'em," he said expansively. "To City Hall to get a marriage license, bonehead. Where did you think?"



—end—

TV DISTRIBUTION SYSTEMS

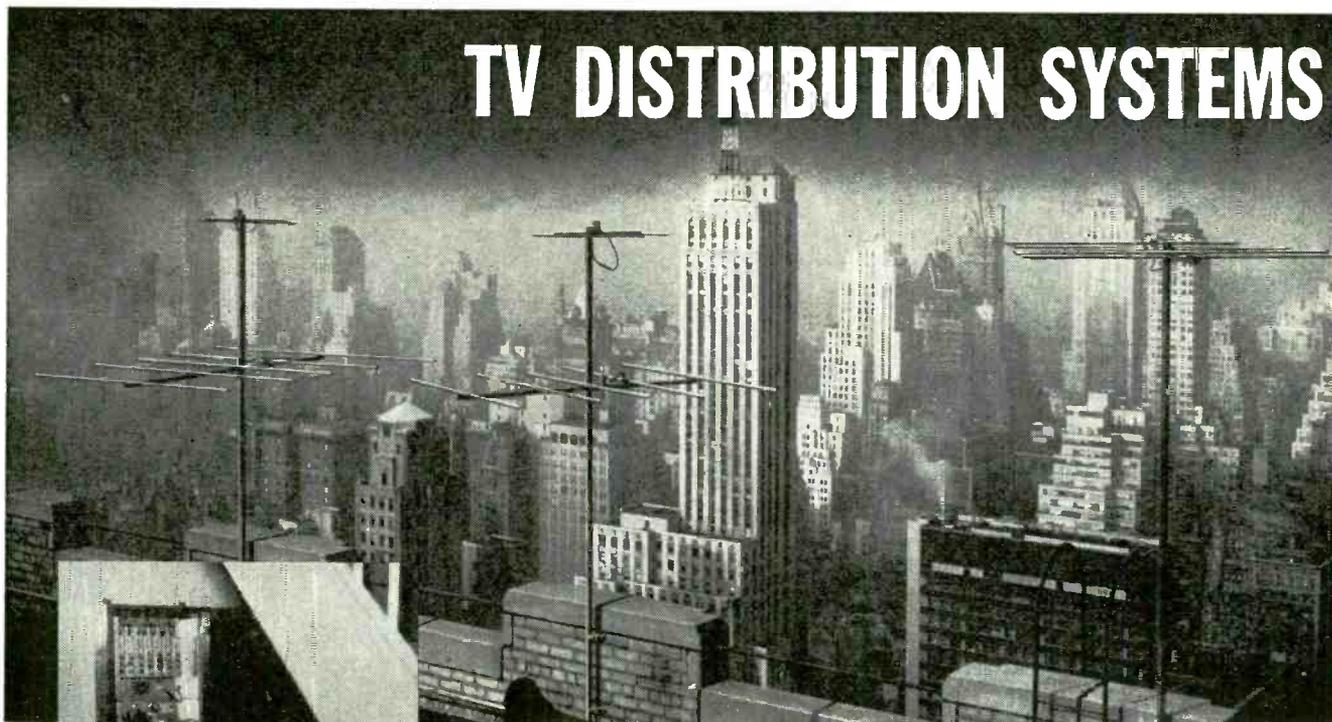

These installations, bringing TV to "hidden valley" communities and the steel-shielded and interference-ridden caves of urban cliff-dwellers, are becoming increasingly important to the industry.

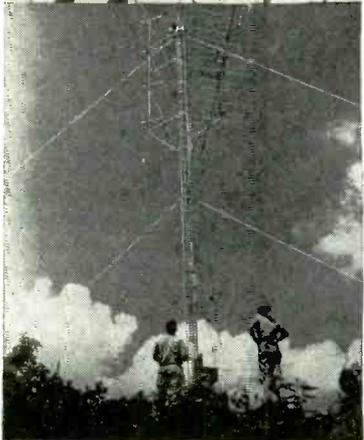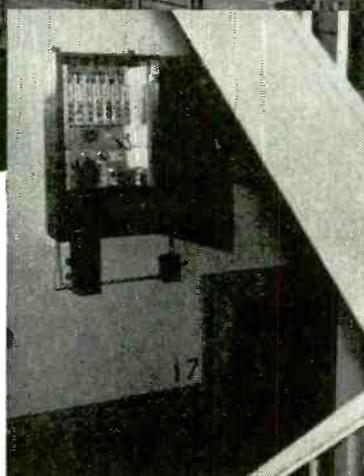Above — Part of antenna system on the Hotel Waldorf-Astoria, as seen against New York's skyline. Note that leads come down through mast and into conduit, making this a completely shielded installation. Below — Part of 3,000 feet of Gonsset line which brings signals from a 1,000-foot-high antenna to televiewers in the village of Hazard, Kentucky.



Top — Sub-system amplifier on the 17th floor of the Hotel Waldorf-Astoria.
Middle — Tapping subscriber's line off the feeder in a community TV system.
Bottom — Mountain-top antenna of the Hazard, Ky., TV distribution system.

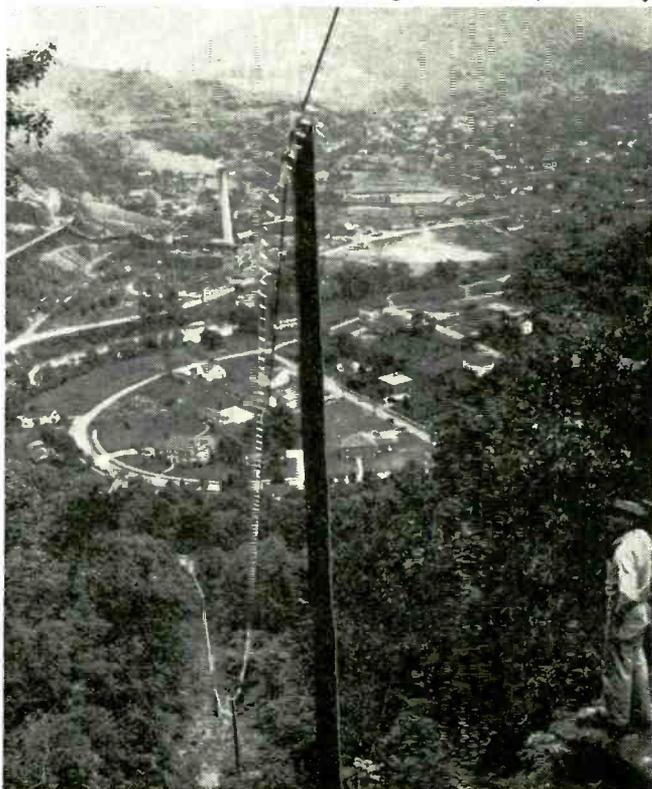


Photo credits: General Electric Co., RCA, Jerrald Electronics

FRINGE AREA

PERFORMANCE

By EDWARD M. NOLL

FFRINGE-AREA performance is judged on the basis of four considerations:

Gain and sensitivity of antenna system and receiver.

Clarity and minimum background noise in picture.

Rejection of signal interference.

Influence of impulse and signal interference on synchronization.

Not so long ago gain and sensitivity were the only major concerns in fringe-area reception. The appearance of a picture on the screen accompanied with a very tolerant attitude on the part of the viewer as to how often the picture would flop, tear, and become obscured by noise constituted acceptable fringe-area reception. Thanks to extensive research on this problem developments that improved fringe-area results rapidly emerged—higher-sensitivity tuners and antenna systems, peaked alignment, horizontal sync control systems that minimized picture tear, fact-acting a.g.c. systems that minimized influence of impulse noises (particularly aircraft flutter). Additional improvements have been made recently in the form of low-noise tubes and amplifier circuits, and better vertical-deflection circuits with improved noise immunity. A more complete knowledge of the factors which improved antenna system and booster performance has contributed markedly to this over-all advance. How do these developments affect fringe-area performance?

Snow-effect

Snow in a fringe area picture is caused by high noise level in the tuner or booster, inability to apply enough signal to receiver input to permit signal domination over noise (antenna system or fringe propagation conditions), antenna system with a high noise level, or one that through mismatch or reactive effects increases the noise output of booster or tuner.

To improve the quality of a picture it is necessary to increase the signal level and at same time keep the noise level at a minimum. The following suggestions, singly or in combination, help to improve the fringe-area picture.

1. Choose a receiver that uses a low-noise-level tuner. Modified cascode triode types using the new 6BK7 or 6BQ7 dual triodes have excellent signal-to-noise ratios. Fig. 1 is a diagram of a commercial circuit using these tubes.

2. Choose a booster with low-noise-level features. A high-noise-level booster used with a low-noise-level receiver results in a stronger signal but more snow in the picture. Cascode and push-pull triode types are preferred.

3. For reception of a limited number of channels in far fringe areas, an antenna-mounted booster permits signal-to-noise improvement because the signal dominates transmission-line noise pickup and the input noise level of tuner.

4. Use an antenna system of high gain and low noise content. Perform-

ance of the antenna should be based on the channel or channels desired. For single-channel operation (or perhaps reception of two or three adjacent channels) the Yagi is a preferred type. When wide-band performance particularly on low-band channels, the Directional, fanned, double-v's, or conical types, though they do not have peak gain of the Yagi, are preferred in fringe operations.

Co-channel interference

A very trying fringe problem in many areas is co-channel interference (two stations on same channel). Solution to the problem, or at least a reduction of the interference, is strictly an antenna-system problem.

1. Use a high-gain single-lobe antenna such as the Yagi to minimize sensitivity of the antenna in all directions except the desired one.

2. If co-channel interference enters from back of the antenna, screening can be useful. The screen should be at least $3/2$ wavelength square to be effective at all.

3. If co-channel interference arrives from almost the same direction as the desired signal, the collinear arrangement of the Yagis can be used to sharpen the horizontal sensitivity pattern, as suggested in Fig. 2.

4. If interference is on a high-band channel, avoid use of antennas that have multi-lobes on these channels (low-band cut elements).

5. Use a length of tin foil on the transmission line. Adjust its position for best relative phasing between the competing signals by observing the screen with co-channel interference present.

Adjacent channel interference

Still another difficult problem to solve is adjacent channel interference. This is particularly trying in an area where the desired station is weak and the adjacent channel station very strong. Such is the case in the area northeast of Philadelphia. In this area, reception of channels 2 and 4 from New York is hampered by a strong Philadelphia channel 3; channel 5, by a strong 6; and channels 9 and 11, by a strong 10.

There are two ways that an adjacent channel can cause trouble. A signal on a given channel can be interfered with by the picture carrier of the next highest channel or the sound carrier from the next lower channel. For example, channel 4 is affected by channel 3 sound and channel 2 by channel 3 picture signal.

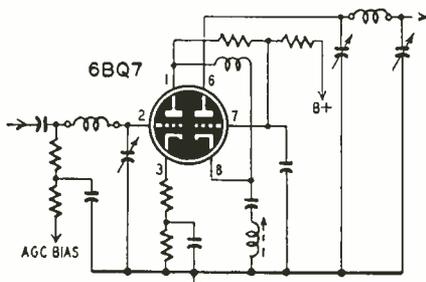


Fig. 1—The cascode r.f. amplifier.

These factors can be minimized by following these instructions:

1. Adjust adjacent-channel sound traps of the receiver under actual reception conditions. For example, set receiver on channel 4, and adjust traps for minimum sound bars and very best picture. Needless to say, if the tuner is not properly aligned or the i.f. strip has no traps, elimination of adjacent-channel interference is greatly hampered.

Due to the wide-band nature of pic-

ture carrier interference (channel 3 picture on channel 2) its elimination is difficult. Adjust trap slowly as channel 2 picture is observed. It is advisable to switch back to channel 3 frequently and observe picture resolution. If trap adjustment is carried too far it disturbs the low-frequency end of the i.f. amplifier response and can put broad echoes in the picture.

2. Choice of a proper antenna will minimize adjacent-channel sensitivity. For example in one test using a channel 2 Yagi, the received signal was strong but interference from channel 3 was severe. When a single fan and reflector was used on channel 2, the channel 2 signal was weaker but interference from channel 3 was reduced and a better over-all picture was obtained. Upon consulting an antenna dimension chart it was found that a channel 2 cut director has the same length as a channel 3 cut reflector. Consequently, a channel 2 Yagi would show good sensitivity in the opposite direction on channel 3 and would undesirably boost adjacent-channel sensitivity. (Increasing the length of the director by 5% and decreasing the spacing between reflectors by 10% should narrow the antenna bandpass and attenuate the higher frequency adjacent-channel response.—Editor)

Local oscillator interference

Local oscillator interference in fringe areas is particularly objectionable because desired signals are weak and local oscillator interference levels remain unchanged. Again its elimination is primarily an antenna problem, although a direct solution would be the installation of traps or a booster at the offending receiver.

1. Use an antenna with a highly directional pattern in the desired direction. A switched-beam or motor-rotated antenna can be oriented away from interference.

2. If the interference comes from the same direction as the desired signal, a change in antenna height often helps.

3. The added selectivity of a booster and tuning the transmission line with

stubs or tin foil helps the signal to override interference.

4. An antenna-installed booster can reduce the effects of local oscillator radiation pickup by the lead-in.

Vertical instability

The modern television receiver has high sensitivity and an improved horizontal synchronization system. In fact, impulse noises and interference are likely to affect the vertical synchronization,

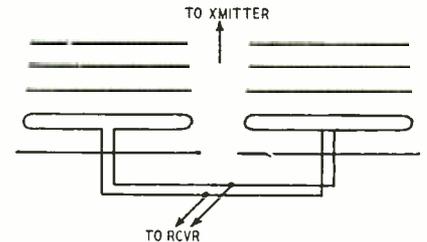


Fig. 2—Colinear antennas are used to greatly increase horizontal directivity.

with consequent flipover and loss of interlace, more readily than other sections of the receiver.

1. Use stacked antenna systems because they exhibit weak sensitivity to ground level pickup. If noise sources are very close by, use well-shielded and properly routed transmission line.

2. The added selectivity of a booster can make a signal dominate the noise level to a greater degree—particularly an antenna-mounted installation. With the newer, more sensitive receivers a fine picture can be obtained without any booster if a.g.c. is set at its least active position. This method of operation permits a good picture but does make the receiver more vulnerable to impulse noises, when present, due to the weaker a.g.c. action. Use of a booster, although it does not appreciably improve the picture, makes the receiver less susceptible to impulse noises because a.g.c. action can be turned up and contrast control reduced when receiving stronger signals.

3. Use a receiver with two or three sync amplifier-separator stages, multi-section integrator network, and vertical retrace line suppressor circuit.

—end—

NEW IDEA IN TV ANTENNAS

A new and highly original television antenna was exhibited at the 1951 Cleveland show of the National Electronic Distributors Association by Fretco Television Company, of Pittsburgh, designers and manufacturers of special antennas. Because of its numerous unique features, the new antenna merits description in considerable detail. The sales engineer of Fretco explains it as follows:

"This super outfit features a polystyrene intensifier rod that doubles the signal every time the signal passes.

"The expert amateur signal getters in Pittsburgh found out that a light bulb hooked up with an antenna would give a lot more signal, so we incor-


porated that idea. The light also keeps airplanes from landing on the antenna.

"Two folded dipoles have more gain than one, so the antenna has two vertical dipoles and one horizontal high and one horizontal low. The tail assembly was patterned after the P80 *Shooting Star*. It has a vertical stabilizer to stabilize any signal that happens to come by. Naturally *Fretline* is used to transmit the signal from one part to another. For strong-signal reception the antenna is equipped with a spigot or throttle to turn the signal down. For normal cruising it is recommended that the spigot be closed. 200 miles or more from the station, open it a little.

"We are now working on a new and

improved model that will do everything—manufacture its own signal, show the picture—this might even do away with television receivers!"

—end—

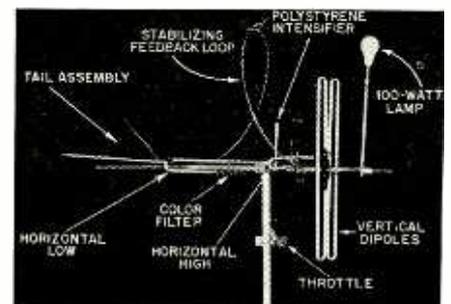

SERVICING HORIZONTAL LOCKS

By MATTHEW MANDL

WHILE the latest type of horizontal lock systems use fewer tubes than the older ones, the circuits are still complex and give rise to many of the troubles which occur in television receivers. Common defects are:

- Horizontal pull or weaving
- Foldover
- Intermittent instability
- Total horizontal sync loss
- Picture shift
- Inadequate hold control range

These faults are usually caused by changes of parts values and tube characteristics, slight maladjustments. If the system was properly adjusted, the horizontal hold control range is usually adequate for quite some time and only decided tube aging and part value change would prevent good synchronization.

The older "synchrolock" and "phase detector" systems used several tubes to secure good lock, and adjustments were rather simple. Modern systems use fewer tubes but adjustment procedures are much more exacting, and complex, and only by critical alignment procedures will stable sync be secured.

The two systems generally used with new receivers are the phase detector system and the synchroguide method. The synchroguide system is by far the most popular and used in numerous receivers including RCA, Admiral, DuMont, Hallicrafters, and a host of others. The primary advantage of the synchroguide is that only a single 6SN7-GT tube need be used for both the control circuit and the sweep oscillator.

The phase detector system is used by Westinghouse in a number of their models, as well as by Motorola in their later receivers. While slight variations exist among different models, the one shown in Fig. 1 is typical of the phase detector system and represents that used by Motorola in their TS-216 chassis.

The phase detector consists of one-half of a 6SN7-GT tube and compares the sync pulses from the sync clipper with the sawtooth developed in the horizontal output. By such phase comparison a correcting voltage (which restores proper phase relationship) is generated and applied to the grid of the horizontal oscillator.

The oscillator is a conventional cathode-coupled multivibrator with a stabilizing coil (L16). This stage also uses a 6SN7-GT tube and the second triode section feeds the horizontal output tube. The waveshapes shown in Fig. 1 apply to any such system,

though relative voltage amplitudes will vary from one manufacturer to another.

In order to facilitate adjustment of the horizontal sweep system a test socket is provided on the rear of the receiver chassis. (Several other manufacturers are including test terminals on their receivers for easy accessibility and rapid checking.) The test socket shown in Fig. 1 provides:

A simple means of shorting the oscillator coil during lock adjustments by putting a jumper from pin 1 to pin 6.

A check on B+ voltage (pins 1 or 8). Provision for checking video output (pin 7 connects to the output of the video amplifier).

Phase system alignment

If instability is present or if the hold control range is inadequate, the entire system should be adjusted. The procedures are not as complicated as with the synchroguide; for the phase detector shown in Fig. 1, the following are typical step-by-step adjustments:

- a. Use a jumper to short out the oscillator coil (L16).
- b. Adjust horizontal centering control so that the right-hand edge of the raster is visible.
- c. Adjust horizontal hold control to the approximate middle of its range and note width of the blanking bar at the right edge of raster.
- d. Remove jumper from oscillator coil.
- e. Adjust horizontal oscillator coil slug until the blanking pulse which now appears has the same width as was seen in step "c" above.
- f. Vary hold control and change stations to check general stability. Repeat above procedures if necessary.
- g. Readjust centering control for proper picture masking.

Modern synchroguide

The synchroguide type of horizontal lock systems is not strictly new, but like the phase detector system previously described, the latest versions are simpler and have greater stability.

A typical modern version of the synchroguide is shown in Fig. 2. It is the system used in the latest Hallicrafters receivers (Models 815, 822, etc.). This circuit is basically identical to those used by many other manufacturers.

In the synchroguide the first triode section of the 6SN7-GT tube acts as the control tube. The second section is a conventional blocking oscillator circuit using a transformer for plate to grid feedback. At the transformer tap a coil and capacitor (C148) form a

resonant section for increased stability.

As with the phase detector, the synchroguide gives good stability, when properly adjusted, for most of the middle range of the horizontal hold control. At one extreme setting sync will be lost immediately, while at the other extreme setting of the hold control sync will only be lost during station change (or momentary removal of sync pulses during station break). In a misadjusted system, or one in which component parts values have changed materially, there will be a gradual narrowing down of the stability range of the hold control, and readjustment becomes necessary. The following instructions apply in general to all synchroguide systems, though some manufacturers give only a condensed version in their service notes.

Synchroguide alignment

- a. Turn the horizontal hold control fully clockwise and adjust the horizontal range adjustment (Fig. 3) (so that the picture displaces to the right) until a vertical bar appears. This procedure must be done with a station tuned in. A station pattern is preferable and a fairly strong signal is desirable.
- b. Turn hold control fully counterclockwise. Use the station selector knob and turn to another channel, then switch back again. Three or four horizontal or slanting bars should then appear on the screen. If too many or too few bars appear, adjust the horizontal lock trimmer (see Fig. 2), until only three or four bars are present.
- c. Repeat step "a" after which center the hold control and check lock-in and general sync stability on all local stations. (Weak stations may give some sync instability) Repeat these steps if sync is not sufficiently stable.
- d. If sync stability is still poor connect an oscilloscope to point C as shown in Fig. 3. Adjust the tertiary waveform slug until the wave form shown at B of Fig. 3 has equal amplitudes. That is, the broad peak P1 should be as high as the sharp peak P2. Adjustment of the tertiary slug will throw sync out and it must be restored by adjusting the horizontal range slug each time. The lead to the vertical amplifier of the scope should be unshielded to minimize effect of probe capacity.
- e. Remove the scope and check general sync stability and range of lock-in. Repeat steps "a" and "b" if necessary. The waveform peak adjustment is very important with any synchroguide

Television Service Clinic

Conducted By **MATTHEW MANDL**

WE wish to extend to the readers of our Clinic the hope that the forthcoming year will prove to be a prosperous one for them, whether they are engaged in television servicing or in other technical endeavors. The art is still growing and with it the inevitable opportunities for expansion in activities and acquisition of new concepts and techniques. The prospect of ultra-high-frequency station allocations has already influenced design in new television receivers.

Many of these receivers are designed for subsequent u.h.f. reception with converters or by insertion of special u.h.f. coils in drum-type tuners. The increased popularity of the latter type has been of advantage to the servicing technician because such tuners lend themselves readily to repair.

Fig. 1 illustrates the printed-circuit tuner used by Hallicrafters. Removal of wire springs at each end of the tuner permits withdrawal of the entire drum and shaft section from the housing. A similar arrangement is employed in the Standard tuner and others used in modern receivers.

With the drum removed all parts are exposed and can be checked or replaced with ease. The phosphor bronze springs which make contact with the coil terminals can be cleaned, lubricated, and bent upward to insure good contact and eliminate noisy or intermittent operation.

Not only can u.h.f. coils be inserted into the drum, but the present v.h.f. ones are readily removed and replaced when defective. This feature is a welcome change from the complexity of earlier tuners, in which it was virtually impossible to replace a defective capacitor or resistor without tearing the entire unit apart. With those, most technicians were forced to take out the entire tuner with considerable loss of time in wiring and retracking the replacement tuner.

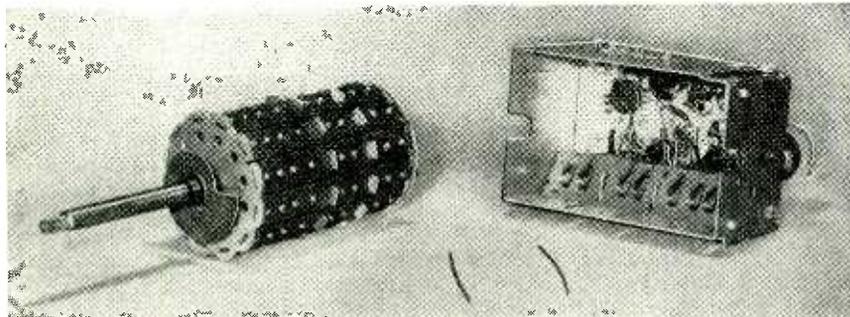


Fig. 1—This Hallicrafters turret is a typical printed circuit front end.

It is gratifying to note that even the new wafer-tier tuners in the newer receivers are far less complex than their older counterparts and also exhibit certain advantages in maintenance work. Let's hope that such progressive thinking will be applied to other circuits in the television receiver.

White line at top of picture

A short while after replacing the vertical output transformer in a Bendix receiver a bright white line appeared across the top of the picture. Adjustment of controls did not help, nor did replacement of tubes. I've taken voltage and resistive checks, but values seem close to normal. The transformer was not an exact replacement, but was one designed for a similar circuit. G. K. Baltimore, Md.

The characteristics of the new transformer may be sufficiently different from the original to cause this trouble. The white line indicates crowding of the initial vertical sweep trace and possible transient oscillations in the vertical system. Make several checks to verify if the transformer is the offender before replacing it.

First of all, check the network of resistors and capacitors (the integrator circuit) feeding the vertical oscillator. If these components check okay use your scope to observe waveform linearity at the input and output of the vertical amplifier. This will help you to determine where the nonlinearity occurs and so localize the trouble.

Crowding at right

I replaced the yoke on an RCA type 630 chassis with the new type designed to give full focus. Since then I've been unable to correct for crowding on the right-hand side of the picture. Replacing tubes didn't help and all parts check all right. Is it possible that the new yoke does not match the flyback transformer? J. S., Long Island, N. Y.

A compressed right side of the picture, as shown in Fig. 2, could very well be caused by a mismatch. For good results in terms of linearity and general performance, both the horizontal output transformer and horizontal deflection coils should be matched.

Try adjusting linearity, drive and width controls, readjusting each one slightly after changing the other. Also try different values of capacitors in the linearity filter of the damper-tube.

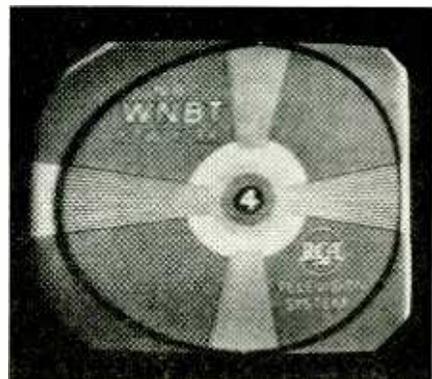


Fig. 2—Compression at picture's right.

If these measures do not yield satisfactory horizontal linearity, you will have to get a matching output transformer for the yoke, or vice versa.

Booster overload

I am located in a fringe area, and in using a booster with an Admiral 17K12 there is a noticeable pulling and distortion of the picture when the booster is tuned for maximum signal strength. I can eliminate this condition by reducing booster output through detuning, but lose picture quality. How can I get maximum signal without distortion? W. A. R., Hazleton, Pa.

Severe pulling is usually indicative of clipped sync, an overloaded a.g.c. system, or an oscillating stage in either booster or receiver due to excessive signal amplitude.

Your symptoms indicate excessive output from the booster because the trouble disappears when you detune. Inasmuch as most boosters have no means of controlling gain you should provide a means for varying booster bias, or use low-value resistors across the transmission line (values determined experimentally). If pulling occurs for all stations you can increase booster-tube bias by increasing cathode resistor value until output is at the desired level.

Picture weave at top

On a converted RCA 721 a slight vertical tremor exists, the picture is bent slightly at the top and weaves on the point of tearing. I have replaced all integrator capacitors, have made a.f.c. adjustments according to the manufacturer's manual, and have checked vertical and horizontal sweep-circuit tubes. S. R., Bergenfield, N. J.

Bending at the top of the picture, as shown in Fig. 3, indicates insufficient sync pulse amplitude and possibly a change of sweep-circuit operating characteristics.

Try a new V104B, 6AL5 sync-limiter tube as well as a new 6SN7-GT sync amplifier-separator. A change of characteristics in the 12AU7 video amplifier (dual video amp) can also clip the sync pulses even though the tube checks O.K. in an ordinary tester.

Check for proper plate voltages at both sweep oscillators, particularly for



Fig. 3—Bending at top of the picture is the result of insufficient sync pulse and trouble in the sweep circuit.

increases in voltage boost brought on by conversion. Improper alignment of video i.f. stages can also cause the symptoms you describe because it can contribute to poor low-frequency response and thus decrease sync amplitude.

Interlock fuse trouble

I have had persistent trouble with a Philco 51-T1870 in which the interlock fuse burns out on an average of once a week. I've measured the line voltage where the receiver is used and it reads 125 volts consistently. How can I remedy this situation? E. S., Havana, Cuba.

Inasmuch as most receivers are designed for operation from 110 to 117 volts a.c. the high line voltage you mention would increase the voltages in the receiver and thus cause abnormal current drain. A heavier fuse could be installed but it would not decrease excessive screen and plate voltages in the receiver. You can use a line-voltage-dropping resistor provided that its wattage rating is adequate in dissipating the heat developed by the current through it. A more expensive but highly satisfactory solution is to use one of the voltage-control transformers sold by a number of manufacturers—RCA Isotap

WP-25A, Sola CVA constant voltage transformer, or UTC Varitran, or an equivalent type.

Increasing fringe gain

I have used good high-gain antennas to receive the four television stations from Chicago, which is 100 miles from here, with pretty good results when using a booster. I have been thinking of building an elaborate booster, similar to the Jervold master booster used with their community antenna systems, in order to assure consistently good reception. I intend using this for a single receiver only, not community work, and would appreciate your comments on this. E. B., Wauwatosa, Wis.

Inasmuch as your results are almost what you desire we would not advise going to the trouble of building a complex booster. Instead, why not try increasing signal pickup by using two boosters in series? These, if properly tuned, will give substantial signal increase. You could also use open-wire line, for this has less loss than the flexible solid plastic types. Also increase antenna height, if possible.

You could install four Yagi antennas (5-element affairs) which should give you a gain of around 10 db. You would have to run four transmission lines to the receiver and use a switching arrangement. While slightly inconvenient, this is less expensive than the complex booster you propose.

Each Yagi, of course, should be designed for the single channel it is to pick up and must be oriented carefully. Yagi antennas have not only extremely narrow band response (good for only one or two channels) but a sharp unidirectional pickup lobe which steps up both gain and selectivity.

Ineffective horizontal hold

I've encountered some trouble lately with two Bendix model 2051 receivers in which the horizontal sync drifts and requires constant resetting of the horizontal hold during the first hour. After that time the hold control is set at the extreme end and horizontal sync is no longer possible. How can I remedy this? A. S., Laurel, Md.

These receivers use a phase detector and a blocking oscillator type of sync-lock system. Other than the hold-control adjustment, no means are provided for correct alignment when loss of horizontal sync occurs.

Try several 6SN7-GT tubes in the horizontal oscillator-phase detector circuit to see if one gives better stability than the other. Some 6SN7-GT tubes have sufficiently different characteristics to make considerable difference in horizontal stability range.

Check for incorrect value resistors in the plate circuit of the 6SN7 section which is connected to the hold control. If necessary check all sweep circuit parts and replace those components which do not test within 5% of the schematic values.

A.c.-d.c. receiver conversion

What suggestions do you have for converting a Belmont 10DX22 (a.c.-d.c. model) to a 14- or 20-inch tube? I would like to leave the a.c.-d.c. feature undisturbed. H. C., Detroit, Mich.

This receiver uses three horizontal output tubes (50B5) and an r.f. type of high-voltage supply with dual 35L6-GT tubes. Conversion to the rectangular tubes or any others having a high deflection angle is not recommended because of the extensive changes which would be necessary. Inasmuch as you do not want to disturb the general features of the receiver, you could use any of the 12-inch tubes without making major changes. Depending on the choice of tube type minor changes in the ion trap or 2nd anode plug for the picture tube may have to be made. Sixteen-inch round tubes having small deflection angles such as the 16LP4, 16MP4, and the 16ZP4 (the latter using a single ion trap) can also be used. Others could also be used but some have no outer conductive coating such as your present 10BP4 tube and would require the addition of another h.v. filter capacitor. Still others are metal and require special precautions and high-voltage insulated mountings.


Decreased brilliancy

When I turn the brightness control on my receiver, the brilliancy increases up to a certain point. When I turn the control farther, the brilliancy actually decreases instead of getting better. At full setting of the control the picture is much dimmer than at half-setting. R. W., Chicago, Ill.

Often a decrease in brightness for an advance of the brilliancy control is due to a faulty 1B3 high-voltage rectifier. When the 1B3 emission falls off and the high voltage is slightly reduced the symptoms you describe will occur. As the brilliancy control is advanced it increases the electron stream within the tube and the space charge effects around the tube phosphor increase also. With reduced velocity (due to lower high voltage) there isn't sufficient force to dislodge a proportionate number of electrons by the secondary emission process and the result is decreased instead of increased brilliancy. Substitute a new 1B3 tube and also check horizontal output and damper tubes, as well as the ion trap setting.

Note: Letters addressed to this Clinic are answered directly and those of general interest are published. When writing to this department enclose a self-addressed envelope and give model number of receiver, manufacturer, chassis number, and tube complement. List all of the symptoms pertinent to reliable evaluation and accurate diagnosis. Include such information as antenna type, channel numbers of stations which can be received in your area, and what preliminary checks you have undertaken prior to writing us.

—end—

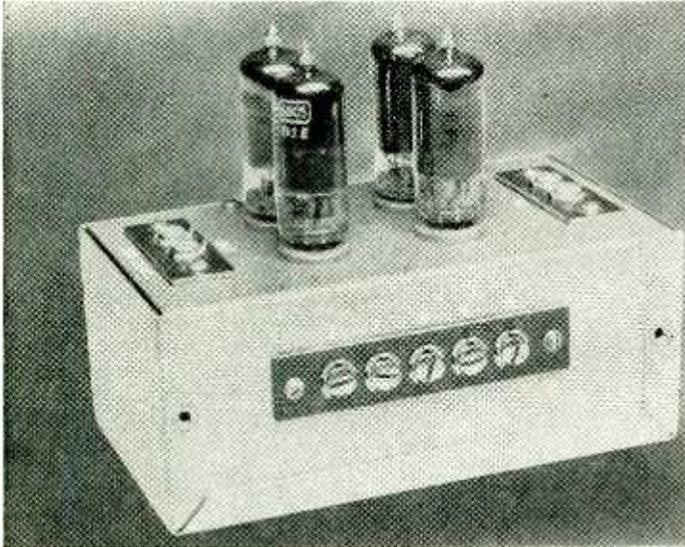

Symmetry is the fundamental feature of the amplifier. A maximum of three receivers may be used with this unit.

A device which makes it possible to use two or three receivers on one antenna without loss of signal strength

By EDWIN BOHR

TV DISTRIBUTION AMPLIFIER

IN SERVICE shops, in homes with more than one TV set, and in fringe areas, it is often desirable to operate several receivers from a single master antenna system. Here is a distribution unit that will operate as many as three TV receivers from a single antenna, and with additional stages will provide as many additional outlets as are needed.

The distribution amplifier consists of push-pull 6BC5 stages arranged along a 300-ohm artificial transmission line. A single pair of 6BC5 tubes serve each distribution outlet. At first glance this may seem poor economy in tubes, but it results in some very worthwhile features.

First: It results in greater dependability since the failure of one tube does not cause a complete signal loss. The signal is lowered only slightly at one outlet when a tube fails. This is important when the distribution amplifier is placed in remote locations, and as many as 10 or more outlets are used.

Second: The push-pull circuit results in greater bandwidth, better r.f. bypassing with better line balance and impedance match.

The gain of each stage is approximately unity over the entire range of TV channels and the FM band. Bandwidth is extremely broad by virtue of the low value of load resistance used in each plate—300 ohms plate-to-plate.

Artificial line

The heart of the distribution amplifier is the 300-ohm artificial line. Amplifier tubes are connected at intervals along this line, distributing the signal to other

points. The artificial line behaves just as a regular transmission line, but in a regular transmission line the impedance is determined by the *distributed* capacitance and inductance of the two parallel conductors. In the artificial line the capacitance and inductance is not distributed but *lumped*.

This lumped inductance is furnished by the coils L1, L2, L3, and L4 (see Fig. 1); and the capacitance is supplied by the grid-to-cathode capacitance of the tubes connected to these inductance coils. Since the input capacitance of the tubes is actually part of this low-impedance line, the tubes produce only a very small disturbing effect on the signal as it is propagated down the line.

Here is what happens: The signal

arriving at the "300-ohm in" terminals is fed to the artificial 300-ohm line. As the signal travels along the line, it reaches the first pair of 6BC5 tubes and is fed to the first outlet. The signal reaches the second stage and is fed to the second outlet. When the signal arrives at the end of the line it can be used to supply a third receiver or can be fed to another distribution unit. If only two outlets are needed, the signal can be terminated in a 300-ohm carbon resistor connected across the "300-ohm out" terminals.

Construction

Since the amplifier is constructed on a small aluminum utility box, the size of the chassis in terms of signal wave-


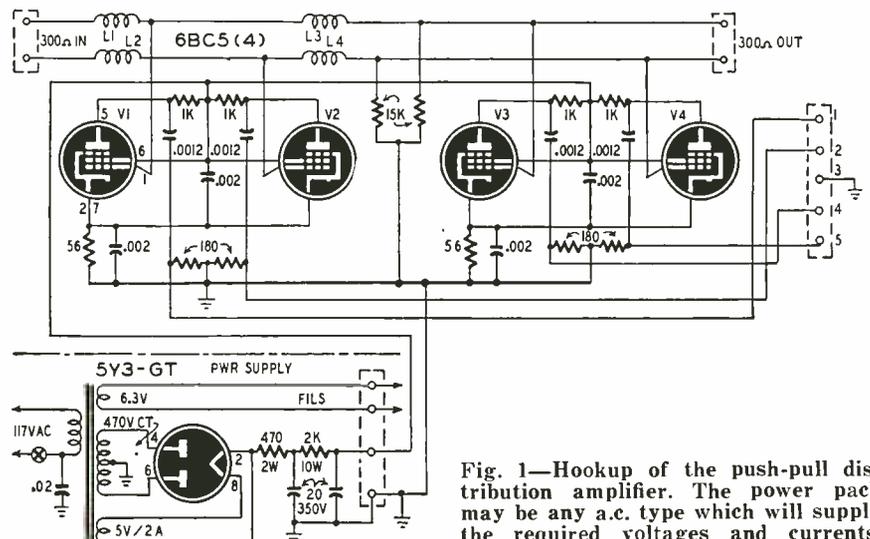


Fig. 1—Hookup of the push-pull distribution amplifier. The power pack may be any a.c. type which will supply the required voltages and currents.

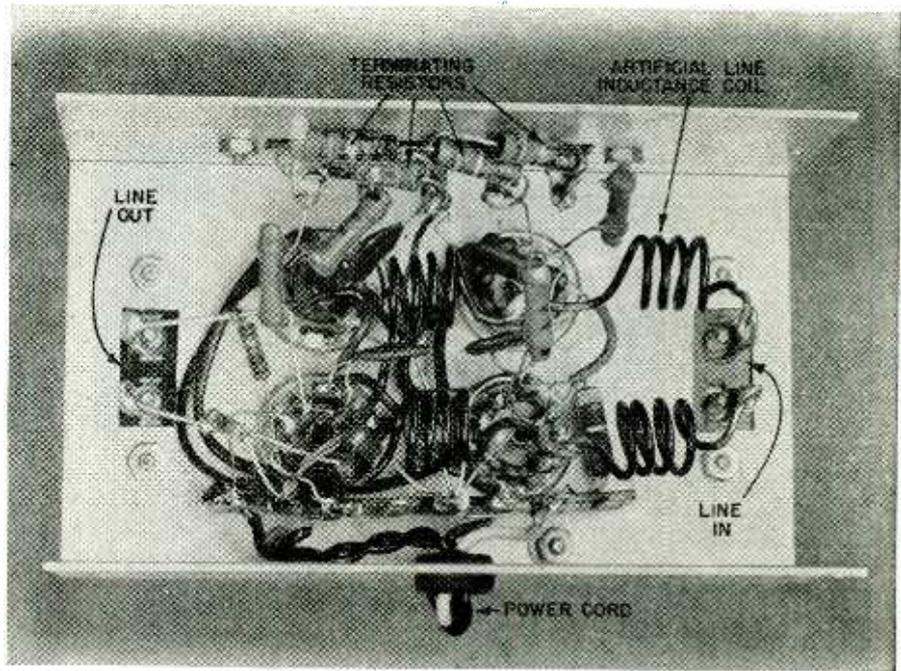

Underchassis view gives a good idea of the symmetrical placement of the artificial transmission lines and terminating resistors.

length is small. This, in addition to the push-pull feature, reduces bypassing problems. Be sure to use physically small capacitors and to trim the lead wires until they are just sufficiently long to reach from one connection to another.

Wire in the artificial line coils first because these are the least easily deformed and rearranged. The 15,000-ohm resistors from each side of the artificial line to ground simply prevent the 6BC5 grids from floating.

No power supply is built into the amplifier. This design is more flexible and allows a smaller and better shielded r.f. chassis. Any power supply that will provide from 110 volts to 125 volts d.c. at 40 milliamperes and 6.3 volts at 1.2 amperes will work. If extra outlet stages are added it will take an extra 10 milliamperes plate current and 0.3 amperes filament current for each additional tube.

Applications

Since its voltage gain is approximately unity, the unit is actually a power amplifier—the same signal voltage is developed across several 300-ohm loads. If a booster is presently used ahead of a single TV set the same booster should be used ahead of the distribution amplifier. See Figs. 2-a and 2-b. When several TV stations are received from the same direction a broad-band high-gain antenna system, such as a rhombic or conical, may be fed to the distribution amplifier for all-channel operation. In this case, if a booster is needed between the antenna and distribution unit, all-band boosters that require no tuning should be used.

Two separate single-channel antennas and boosters can be connected to the distribution unit as shown in Fig. 2-c. Two boosters can be paralleled with quarter-wave crossover sections of 300-ohm line. According to Fig. 2-c, best

match for channel "Y" will be obtained by pruning the lead from the channel "X" booster and vice versa. In other words, the lead from each booster acts as a stub for the other booster.

Fig. 2-d shows how two units may be connected in series for additional outlets. Theoretically, the number of receivers that may be added is limitless, and if an odd number of receivers is to be used in the system, one of them can take the place of the resistor.

If no-loss signal distribution is desired and isolation is needed between receivers to reduce interference, this feed system is just the thing. FM receivers can be fed with TV receivers,

making possible universal TV and FM outlets for several service benches in a repair shop. With experience other uses for the broad-band amplifier will suggest themselves to the experimenter- constructor.

Materials for distribution unit


Resistors: 2—56, 2—15,000, 4—180, 4—1,000 ohms (all 1/2 watt).

Capacitors: 4—.002 uf, disk ceramic; 4—.0012 uf, tubular ceramic.


Inductors: L1, L2, L3, L4: Four turns No. 14 enameled copper wire, 3/8-inch diameter, spaced out to 3/4-inch length.

Miscellaneous: 4—6BC5 tubes, aluminum box chassis, 3 screw terminal strips, 1 4-lug tie strip, 4 tube sockets, hookup wire, assorted hardware.

—end—

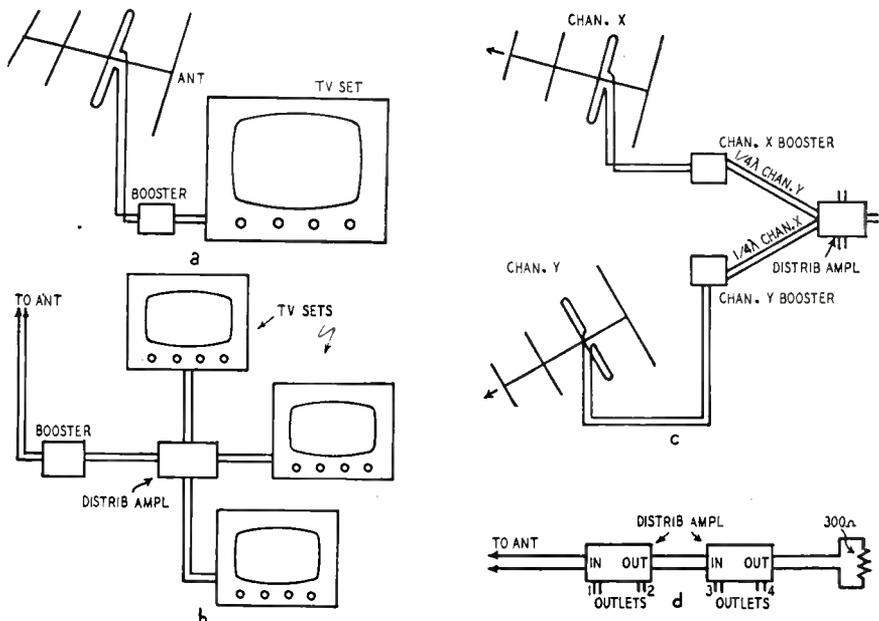

Figs. 2-a and 2-b—If a booster is used, the same booster will amplify equally for all three receivers if placed where indicated. (It may also be placed in any one of the three leads if only one set requires a booster.) Fig. 2-c—If two antennas are used, they may be hooked up as shown, using the lead from the one channel as a tuning stub for the other. Fig. 2-d—If any even number of receivers are connected to one antenna, a 300-ohm resistor terminates the OUT lead.

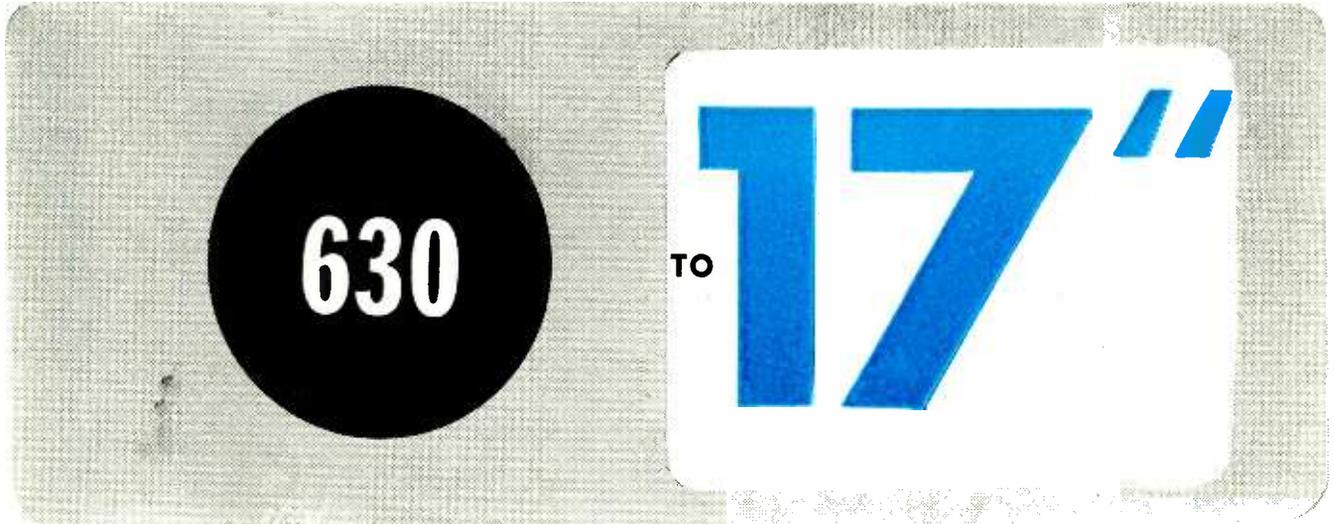

By T. E. CANTOR

THE 630-type TV chassis, manufactured by most companies since 1947, is considered one of the best chassis in the field and is still featured as a fringe-area and custom model by many firms. Since the initial cost of the 10-inch 630 model was higher than many large-screen console models today, the owners are reluctant to part with their fine performing but small-screen sets for the few dollars of trade-in allowed them toward a 17- or 20-inch rectangular-tube model.

The technician who is on his toes can show the set owner how he may "have his cake and eat it too," by converting his old 630.

The argument may have been offered that the chassis will be overloaded in providing the extra sweep and high voltage required for the rectangular tubes. This is a fallacy since the use of a high-efficiency ferrite-core flyback transformer and yoke and the elimination of the 5,300-ohm resistor shunting

the 5V4-damper tube will enable the deflection circuit to deliver more high voltage and deflection power at no increase in B-plus drain. The Du Mont H1A1 ferrite yoke provide edge-to-edge sharpness on 70° tubes. They are mechanically interchangeable with the original components and perform well in 630 conversions.

When the 630 is fully converted according to the instructions given here, the reserve of high voltage and deflection power is so great that it is possible to interchange 14-, 16-, 17-, 20-, and 24-inch rectangular tubes directly in the same chassis. Resetting the horizontal drive control is the only adjustment required.

Horizontal output modifications

Fig. 1 shows the horizontal deflection circuit of the typical 630-type receiver. Original wiring and components are

shown in BLACK and components or wiring which must be added or changed are shown in BLUE.

The diagram is divided into two sections by a dashed line just to the left of the 6BG6-G. The 12 steps required for successful modification of the horizontal circuit of most sets are applied to the section of the circuit on the right of the dashed line. Make these changes first:

1. Remove the original yoke and flyback transformer. The original linearity and width coils may be used.
2. Remove 6,300-ohm damping resistor, connected between plate and cathode of the 5V4-G damper tube.
3. Replace the high-voltage filter capacitor with one rated for 20 kv. Connect the negative side to the plates of 5V4-G damper tube instead of to ground as in the original circuit. This adds the boosted voltage in series with the high voltage, raising it about 1.5 kv.

If an insulated mounting is not provided for the high-voltage filter capacitor, construct one from bakelite sheet and fasten it across the punched hole in the chassis where the original capacitor was mounted. This is shown at *a* in Fig. 2. An alternate method is to support the bakelite sheet on two bakelite or ceramic standoff insulators as at *b* in Fig. 2. In either case, take care that the positive terminal of the capacitor is at least 1 inch away from any low-potential points, and the negative terminal at least 3/8 inch away.

4. When converting doubler circuits, disconnect one rectifier tube socket and wire up the other for single rectifier operation. The high-efficiency components provide more high voltage with better regulation than the original doubler circuit.

5. Fasten the new flyback transformer to the chassis in the mounting holes of the original transformer.

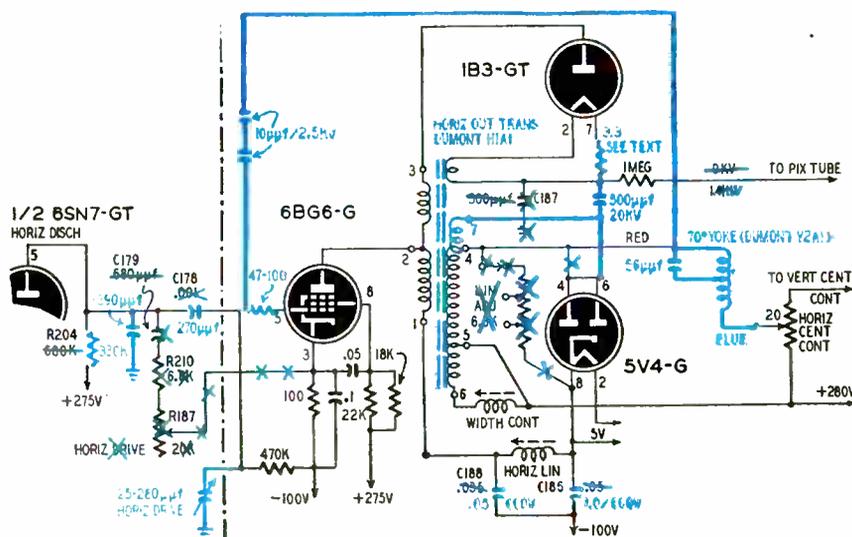


Fig. 1—The required modifications for the 630 conversion are indicated in blue.

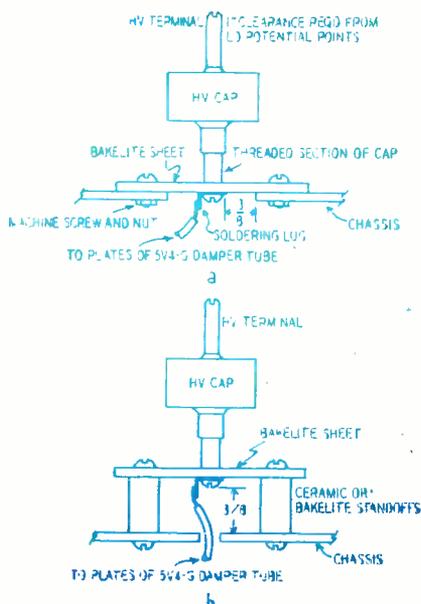


Fig. 2—Ways of mounting h.v. filter

6. Omit the 3.3-ohm series resistor if the flyback transformer has a one-turn filament winding. Solder the filament leads directly to pins 2 and 7 on the 1B3-GT socket. The resistor must be used if the transformer has two filament turns.

7. Connect a wide-angle ferrite yoke as in the original circuit except for the following change: Connect the red horizontal lead to terminal 4 alone of the flyback transformer and disconnect the damper plates.

8. Connect terminal 7 of the flyback transformer to the plates of the 5V4-G damper tube and connect terminal 5 to B-plus. Connect terminal 1 to the end of the linearity coil that connected to terminal 1 of the original flyback transformer.

9. Connect the width coil across to terminals 5 and 6 of the flyback transformer. Omit the width coil if maximum width is desired.

10. Insert a 47- to 100-ohm, 1/2-watt parasitic suppressor resistor in series with the 6BG6-G grid if not already in the circuit.

11. Change the values of C186 and C188 (bypassing the linearity coil) to 1.0 and .05 μf respectively. Use 600-volt units.

12. Connect two 10- μf , 2,500-volt capacitors in series from terminal 4 of the flyback transformer to the grid of the 6BG6-G. This provides feedback which produces additional sweep and high voltage.

Increasing horizontal drive

If still more horizontal sweep and high voltage are required make the changes shown in RED left of the dashed line dividing Fig. 1. The following changes will increase the horizontal drive.

1. Change resistor R204, in the plate circuit of the 6SN7-GT horizontal discharge tube from 680,000 to 330,000 ohms, and the .001- μf coupling capacitor C178 to 270 μf .

2. Remove the original horizontal drive circuit consisting of C179 (680 μf), R210 (6,800 ohms), and the 20,000 ohm drive potentiometer R187.

3. Add a 25-280- μf padder capacitor from the grid resistor of the 6BG6G to ground, and a 390- μf discharge capacitor, in the plate circuit of the 6SN7-GT horizontal discharge tube. These changes provide more than enough horizontal drive. Coupling capacitor C178 was changed to 270 μf to bring the drive down to a usable range. Use the original value (.001 μf) if maximum drive is required.

4. Use the padder capacitor as the drive control. Turn the adjusting screw counterclockwise until white overdrive lines appear on the screen, then clockwise until the lines just fade out. This is the point of maximum usable drive.

Vertical sweep circuit

The increased high voltage makes it necessary to provide more vertical sweep than it is possible to obtain with optimum adjustment of the vertical height and linearity controls. In this case, make the changes shown in red in Fig. 3 and described in detail below.

1. Substitute a 6V6 for the 6K6 vertical output tube.

2. Increase the voltage on the plate of the vertical output tube by reducing the value of resistor R179 (in series with the red primary lead of the vertical output transformer) from 10,000 to 5,000, 2,000, or 1,000 ohms as in Fig. 3, connection A. Use the highest resistance that will provide sufficient vertical sweep with good linearity.

3. If still more vertical sweep is desired, then disconnect the red lead of the vertical output transformer from B-plus and connect it to the boosted voltage at pin 1 of the flyback transformer through 10,000 to 5,000 ohms, as in Fig. 3, connection B. Be sure the 10- μf , 450-volt decoupling capacitor C221C is NOT disconnected. Use the highest resistance that will provide good vertical linearity and sufficient sweep, as this connection loads down the boost voltage and reduces the high voltage about 1 kv.

Foldover

The large distributed capacitance of the high-efficiency yokes and flyback transformers often increases the horizontal retrace time to 10-15 microseconds, resulting in one side of the picture being folded over.

Adjusting the phasing slug (underneath the chassis) of sync discriminator transformer may make it possible to position the foldover off the screen. If the condition is still evident, then the negative pulse which produces the retrace may be applied directly to the screen grid of the kinescope to blank out the screen during the retrace. See Fig. 4. The screen grid (pin 10 on the kinescope socket) is the red lead in the

kinescope cable. The 50- μf coupling capacitor may be varied from 20 to 100 μf

Focusing

Remove the 1,800-ohm resistor R183, shunted across the focus coil as in Fig. 5. This provides the higher focusing current required for the higher anode voltage. If the proper focusing range is still not available, then substitute an RCA 202D2 or RTMA-JETEC109 focus coil. These units have a resistance of 470 ohms and a somewhat different mounting, but are electrically interchangeable with the original focus coil.

Elimination of arcing and corona

The majority of converted sets were designed originally for voltage of 7-10 kv. It will be necessary to take special precautions to avoid corona or arc-over in the high-voltage cage. Be sure all connections on the high-voltage rectifier socket are rounded and free from sharp points. If arcing occurs from the rectifier socket to ground, insert a sheet of bakelite 1/8 inch to 1/4 inch thick, or layers of rubber tape, on the chassis directly under the socket to effectively insulate it from ground. If arcing occurs from the cap of the rectifier tube to the top of the high-voltage cage, replace the spring clip on the cap with an Alden or Warren type plastic cap or cut out a section of the cage directly above the cap. If corona is present, apply a thick coat of Amphenol polystyrene dope to all high-voltage surfaces. Be sure the dope is completely dry before applying power, as its solvent is inflammable.

—end—

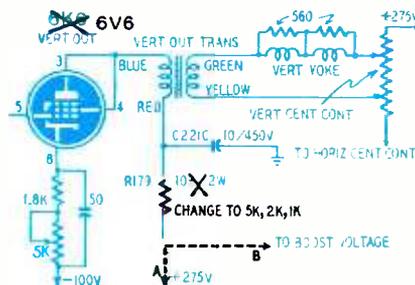


Fig. 3—Make changes shown in black if greater vertical sweep range is needed.

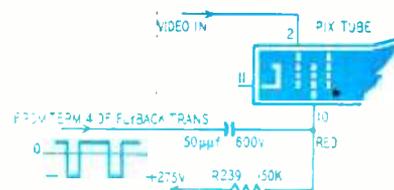


Fig. 4—Circuit for reducing foldover.

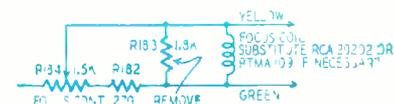


Fig. 5—Remove R183 to improve focus.

PICTURE TUBE REPLACEMENT GUIDE

By E. WM. SCOTT

THIS tabulation of picture-tube characteristics is prepared to assist the technician and tube salesman in selecting the tube best suited for a particular job. Tubes are listed in groups according to size, shape, construction (metal or glass), method of focusing, and deflection angle. Tubes having the same electrical and physical characteristics and differing only in the type of face plate are completely interchangeable without modifying the circuit or cabinet. For example: the 19AP4, 19AP4-A, 19AP4-B, 19AP4-C, and 19AP4-D are identical except for the treatment of the face plate. All types employ magnetic focusing except where specified in heading in the table.

Picture tubes can be divided roughly into two classes according to their deflection angles. The first covers tubes from 50 to 60 degrees and the second includes the wide-angle 66- to 70-degree types. Rectangular tubes which have 50-degree vertical and 65- to 66-degree horizontal deflection angles are listed according to the diagonal deflection angle (70 degrees) in accordance with the method which seems almost universal among tube manufacturers and the TV service industry. A new deflection yoke and possibly a new high-voltage and deflection transformer will be required when replacing a 50- to 60-degree tube with one of the 70-degree types.

The new electrostatically focused picture tubes are available in three types. In one type, the focusing anode must be supplied with a potential of 2,000 to 5,000 volts. This type requires a separate high-voltage rectifier to supply the focusing potential. A second type requires focusing voltages between 0 and 500. The newest of the electrostatically focused types have a new electron gun designed so the electron beam is always focused without special focusing potentials. In fact, these tubes do not even have an outside terminal connection for the focusing electrode.

Operating voltages must be considered when converting a set to use a picture tube several inches larger than the original. The circuit changes required can be minimized by observing the operating potentials on the original tube and selecting a replacement tube which will provide satisfactory service under similar conditions. As a rule, a difference of 15% in operating voltages can be tolerated. Maximum accelerator (grid No. 2) voltage is 410 for most tubes regardless of size—except for the 10EP4 and 12AP4 whose maximum voltages are 330 and 250 respectively.

The maximum anode voltage is approximately 1,000 volts for each inch of screen diameter or width in rectangular

Tube type	Bulb diameter or diagonal (inches)	Over-all length	Ion trap type	Base diagram Fig. No.	Anode connector	notes
10-inch glass round, 50 degrees						
10BP4	10 1/2	17 5/8	Double	1	Cavity	
10EP4	10 1/2	17 5/8	Double	1	Ball	
10FP4	10 1/2	17 5/8	None	1	Cavity	
10MP4	10 1/2	17	Single	2	Cavity	
10CP4	10 1/2	16 5/8	None	1	Ball	
10-inch glass round, 50 degrees, electrostatic focus						
10DP4	10 1/2	17 5/8	None	5	Cavity	a
12 1/2-inch glass round, 50 degrees						
12LP4	12 7/16	18 3/4	Double	1	Cavity	
12TP4	12 7/16	18 3/4	Double	1	Cavity	a
12CP4	12 1/16	18 5/8	None	3	Cavity	a, b, c
12VP4	12 7/16	18	Single	2	Cavity	
12WP4	12 7/16	17 3/4	Single	7	Special	
12KP4	12 7/16	17 5/8	None	1	Cavity	
12QP4	12 7/16	17 1/2	Single	1	Ball	
12JP4	.12	17 1/2	None	1	Ball	d
12RP4	.12	17 1/2	Single	1	Ball	d
12 1/2-inch glass round, 40 degrees, electrostatic focus						
12AP4	12 3/16	25 3/8	None	4	Cap	a, c
12 1/2-inch metal round, 54 degrees						
12UP4	12 7/16	18 5/8	Double	1	Cone lip	a
14-inch glass rectangular, 70 degrees						
14BP4	13 11/16	16 13/16	Double	1	Cavity	
14EP4	13 11/16	16 13/16	Double	1	Cavity	
14CP4	13 11/16	16 3/4	Single	1	Cavity	
14DP4	13 11/16	16 3/4	Double	1	Cavity	
14-inch glass rectangular, 70 degrees h.v. electrostatic focus						
14GP4	12 21/32	17 3/16	Single	5	Cavity	
15-inch glass round, 50 degrees						
15CP4	15 3/4	21 7/8	Double	1	Cavity	a
15-inch glass round, 57 degrees						
15AP4	15 3/4	20 7/8	None	1	Ball	a
15DP4	15 3/4	20 7/8	Single	1	Cavity	a
16-inch glass rectangular, 70 degrees						
16QP4	16 1/8	19 1/8	Double	1	Cavity	a, e
16KP4	16 1/8	18 3/4	Single	1	Cavity	
16RP4	16 1/8	18 3/4	Single	1	Cavity	
16XP4	16 1/8	18 3/4	Double	1	Cavity	a
16UP4	17 1/8	18 1/8	Single	1	Cavity	a
16TP4	16 1/8	18 1/8	Single	1	Cavity	
16-inch glass round, 50-60 degrees						
16LP4	15 7/8	22 1/4	Double	1	Cavity	f, g
16MP4	16 1/8	21 3/4	Double	1	Cavity	
16CP4	15 7/8	21 1/2	Double	1	Cavity	a, f, g
16FP4	16 1/8	21 1/4	Single	1	Ball	a
16HP4	15 7/8	21 1/4	Double	1	Cavity	f
16JB4	16 1/8	20 3/4	Double	1	Cavity	
16DP4	15 7/8	20 3/4	Double	1	Cavity	a
16-inch glass round, 70 degrees						
16ZP4	15 7/8	22 1/4	Double	1	Cavity	h
16WP4	15 7/8	17 3/4	Double	1	Cavity	a, h
16SP4	15 7/8	17 5/16	Single	1	Cavity	h
16YP4	15 7/8	17 5/16	Single	1	Cavity	h
16VP4	15 7/8	17 3/16	Single	1	Cavity	a
16-inch metal round, 53 degrees						
16AP4	15 7/8	22 5/16	Double	1	Cone	a
16-inch metal round, 60 degrees						
16EP4	15 7/8	19 5/8	Double	1	Cone	a
16-inch metal round, 70 degrees						
16GP4	15 7/8	17 11/17	Single	1	Cone	a, f
16-inch glass round, 60 degrees, self-focus						
16ACP4	15 7/8	20 7/8	Single	6	Cavity	
17-inch glass rectangular, 70 degrees						
17BP4	16 5/8	19 5/8	Single	1	Cavity	
17AP4	16 5/8	18 5/8	Single	1	Cavity	



Fig. 1



Fig. 2



Fig. 3



Fig. 4

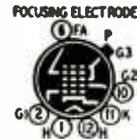


Fig. 5



Fig. 6



Fig. 7

Tube type	Bulb diameter or diagonal (inches)	Over-all length	Ion trap type	Base diagram Fig. No.	Anode connector	notes
17-inch glass rectangular, 70 degrees h.v. electrostatic focus						
17FP4	16 3/4	19 5/8	Single	5	Cavity	
17-inch glass rectangular, 70 degrees, i.v. electrostatic focus						
17HP4	19 3/16	16 5/8	Single	5	Cavity	
17-inch metal rectangular, 70 degrees						
17CP4	17	19	Single	1	Cone	a
17-inch metal rectangular, 70 degrees h.v. electrostatic focus						
17GP4	15 17/16	18 1/16	Single	5	Cone	a
17-inch glass rectangular, 70 degrees, self-focus						
17KP4	16 5/8	19 1/4	Single	6	Cavity	
17RP4	16 5/8	19 1/4	Single	6	Cavity	
17SP4	16 5/8	19 3/16	Single	6	Cavity	
17-inch metal rectangular, 70 degrees, i.v. electrostatic focus						
17TP4	16 13/16	19 5/16	Single	5	Cone	a
19-inch glass round, 66 degrees						
19FP4	18 7/8	22	Double	1	Cavity	a
19DP4	18 7/8	21 1/2	Double	1	Cavity	e
19GP4	18 7/8	21 1/4	Single	1	Cavity	a
19-inch metal round, 66 degrees						
19AP4	18 3/4	22	Single	1	Cone	a
19-inch glass rectangular, 70 degrees						
19JP4	18 5/8	21 3/16	Single	1	Cavity	a
19EP4	17 1/8	21 1/2	Double	1	Cavity	
20-inch glass round, 54 degrees						
20BP4	20 3/8	28 3/4	None	1	Cap	a
20-inch glass rectangular, 70 degrees						
20DP4	20 3/32	21 7/8	Single	1	Cavity	
20CP4	20 3/32	21 7/16	Single	1	Cavity	
20-inch glass rectangular, 70 degrees, h.v. electrostatic focus						
20FP4	20 3/32	22 1/8	Single	5	Cavity	
20GP4	20 3/32	22 1/8	Single	5	Cavity	
20-inch glass rectangular, 70 degrees, i.v. electrostatic focus						
20HP4	20 3/32	21 3/4	Single	5	Cavity	
20-inch glass rectangular, 70 degrees, self-focus						
20JP4	20 3/32	21 3/4	Single	6	Cavity	
21-inch metal rectangular, 70 degrees						
21AP4	20 3/4	22 5/16	Single	1	Cone	a
21-inch glass rectangular, 70 degrees						
21EP4	21 7/32	23 3/8	Single	1	Cavity	
21-inch glass rectangular, 70 degrees, self-focus						
21KP4	21 7/32	22 7/8	Single	6	Cavity	
22-inch metal round, 70 degrees						
22AP4	21 11/16	22 7/8	Single	1	Cone	a
24-inch metal round, 70 degrees						
24AP4	24 1/8	23 15/16	Single	1	Cone	a
24-inch metal round, 70 degrees, i.v. electrostatic focus						
24BP4	24 1/8	24 1/4	Single	5	Cone	
30-inch metal round, 90 degrees						
30BP4	30 1/8	23 9/16	Single	1	Cone	a

tubes. For typical operation, anode voltages range from 9,000 to 11,000 for 10- to 12-inch tubes, up to 12 kv for 14- to 16-inch types, and 12,000 to 16,000 for tubes up to 24 inches. The 30BP4 has a maximum anode voltage of 30,000, with 23,000 being typical in practice.

Self-focusing and low-voltage electrostatically focused tubes can, in some instances, replace magnetically focused types. High-voltage types can be used in conversions where the high-voltage transformer is replaced. Typical circuits employing electrostatically focused tubes are shown in Figs. 4 and 5 of the article "Novel 1952 TV Circuits" in this issue. These circuits show Zenith's method of supplying operating voltages to the focusing electrodes. Other manufacturers may use slightly different circuits.

We have listed only magnetically deflected tubes of 10 inches and larger. There are only a few electrostatically deflected types. These are not readily replaced by electromagnetic types. In each particular group of tubes, the types are listed in descending order of size. Thus, when substituting a tube of the same screen size as the original or when selecting a tube for a conversion job, a tube low on the list is preferable to any of the types above it when best utility of small cabinet size is an important factor in the selection. For example, if you are looking for a 12-inch tube to squeeze into a 10-inch cabinet, a 12JP4 or 12RP4 will be more likely to fit than a 12LP4 or 12TP4 because the former types are 1 1/4 inches shorter and about 1/2 inch smaller in diameter than the latter types.

Footnotes:

a—Tube has no exterior conductive coating. Add 500-μmf, high-voltage filter capacitor when using tube as replacement for type having exterior coating. When this type is replaced by tube having outside coating, ground the coating to the chassis.

b—Triode-type tube. Has no No. 2 grid. For circuitry, refer to diagrams of sets using triode- and tetrode-type tubes. Alter circuits where necessary to permit use of tube being used as replacement.

c—This tube has 2.5-volt, 2.1 ampere heater. All others have 6.3-volt, 600 ma heaters.

d—Face-plate curvature has 20-inch radius; all others in this group have 40-inch radius.

e—Requires JETEC-RMA 106 focus coil. Others in this group use type 109 focus coil.

f—Face-plate curvature has 56-inch radius; others in this grouping have 27-inch radius.

g—Deflection angle is 50 degrees. The deflection angle is 60 degrees for other tubes in this group.

h—Radius of face-plate curvature is 56 inches.

i—Radius of face-plate curvature is 40 inches; all others in this group have 27-inch radius.

j—17BP4-A and -B have outside conductive coatings; 17BP4 has not.

Tube types printed in light-face type (12AP4, 12CP4), are obsolete.

—end—

TELEVISION ANTENNA

Alliance Mfg. Co.
Alliance, Ohio

Antenna rotators. Three models.

All Channel Antenna Corp.
70-07 Queens Blvd.

Woodside, N. Y.

Super-fan conical antennas, double-V's, Yagis, folded and straight high-low antennas, window antennas. Masts and other accessories.

Alproco, Inc.
Kempton, Ind.

Mineral Wells, Tex.

Telescoping test tower. Permanent aluminum towers. Three models.

American Phenolic Corp.
1830 S. 54 Ave.

Chicago 50, Ill.

In-line antennas, single-bay and stacked arrays, piggy-back, indoor antennas. Eleven models. Rotators, lightning arrester, standoff insulators, and mast sections.

Antenna Products

3628 N. Lincoln Ave.

Chicago 13, Ill.

Dual and single-channel Yagi arrays, conical Yagi arrays. High- and low-band folded dipole arrays. Chimney mounts, wall mounts, vent mounts, and accessories. Twenty-nine antenna models.

Baker Mfg. Co.

Evansville, Wis.

Forty-foot tower, 30- and 20-foot telescopic masts, 10-foot plain mast sections, 10-foot fitted-end mast sections, and foot mounts.

Beacon Corp.

2846 Milwaukee Ave.

Chicago 18, Ill.

Spiral-type horizontal-element indoor antenna.

Blonder-Tongue Laboratories

38 N. Second Ave.

Mount Vernon, N. Y.

TV preamplifiers, line amplifiers, master antenna system, 2-outlet and 8-outlet distribution amplifiers.

Brach Mfg. Corp.

Division of General Bronze Corp.

200 Central Ave., Newark, N. J.

Four- and 6-element conicals and 2- and 4-bay stacked conicals, in-line types, bow-tie V, FM crossed dipoles, indoor antennas. Nine models. Master antenna system, amplified and nonamplified. Two- and 4-set couplers, coaxial plugs, boosters, lightning arresters, masts, mast mounts, and mast bases.

Bud Radio, Inc.

2118 E. 55th St.

Cleveland 3, Ohio

Adjustable chimney mounts, universal and heavy-duty wall mounts, corner mounting brackets, guying clamps, mast couplers, and towers.

Camburn, Inc.

32-40 57th St.

Cleveland 3, Ohio

Telescoping indoor antennas, outdoor conical arrays, straight and folded high-low dipoles, window antennas, and Yagis. Masts, rubber standoffs, swivel-base brackets, lightning arresters, guy-wire rings, and other accessories.

Channel Master Corp.

Elienville, N. Y.

Fan, conical, Yagi, in-line, V, high-low antennas for single-channel and broad-band use. More than 50 models. Twenty, 30, 40 and 50-foot telescoping masts. Couplings, guy rings, wall mounts, roof mounts, base mounts, and other accessories. Aluminum and steel triangular towers with associated mounts and brackets.

Circle-X Antenna Corp.

500 Market St.

Perth Amboy, N. J.

Broad-band Circle-X antennas, conical V's, and folded dipoles. Twenty-seven models. Masts, guy wires, ground rods.

Cornell-Dubilier Electric Corp.

South Plainfield, N. J.

Conical, high-low, indoor, super-V, Yagi, straight-line antennas. Seventeen models. Antenna rotators, four models. Chimney mounts, lightning arresters.

Crown Controls Co.

124 S. Washington St.

New Bremen, Ohio

Rotators. Two models. Roller-bearing guy ring.

Delson Mfg. Co.

126 Eleventh Ave.

New York 11, N. Y.

Window and indoor antennas. Five models. Two-set couplers.

R. L. Drake Co.

11 Longworth St.

Dayton 2, Ohio

TVI filters. Nine models.

Easy-Up Tower Co.

427 Romaine Ave.

Racine, Wis.

TV towers, roof mounts, rotating and fixed-pole rings, guy-wire clamps, and twin-line testers. Eleven models.

Electronic Indicator Co.

259 Green St.

Brooklyn, N. Y.

Conical, folded dipole, Yagi, and double-V antennas. Chimney mounts and accessories.

Energy Farm Equipment Co.

Monticello, Iowa

All-hydraulic sectional TV mast, extended height about 60 feet.

Ferro Electric Products, Inc.

Kirkland, Ill.

Single-, 2-, and 4-bay conical antennas. Nine models. Accessories, ground rods, etc.

Fretco Television Co.

1041 Forbes St.

Pittsburgh 19, Pa.

Straight and folded dipoles. Three-, 4-, 5-, 6-element Yagis cut to channel. In-line folded high-low with directors and reflector. Conicals, collinear arrays, super-loop, broad-side arrays, phased arrays, custom-built arrays. "Fretline" open wire transmission line. TV lights. Seventy-seven models.

Gadgets, Inc.

3629 N. Dixie Drive

Dayton, Ohio

Indoor circular dipole.

Gee-Lar Mfg. Co.

1330 10th Ave.

Rockford, Ill.

Single-, 2-, and 4-bay conical antennas. Three models.

General Cement Mfg. Co.

919 Taylor Ave.

Rockford, Ill.

Single-, 2-, and 4-bay conical antennas. Indoor dipole. Chimney mounts, wall mounts, standoff insulators, lightning arresters, and other accessories.

Gonset Co.

72 E. Tujunga Ave.

Burbank, Calif.

Radar-type arrays, including dipole mattress types and quadrature-phased dipole curtain types; high-low-band and all-channel models. Telescopic masts. Low-loss open-wire line.

Don Good, Inc.

1014 Fair Oaks Ave.

South Pasadena, Calif.

Low-loss perforated TV lead-in wires. High-pass filters, TVI traps. Seven models.

Haygren Electronic Mfg., Inc.

436 18th St.

Brooklyn 15, N. Y.

Chimney mounts, wall brackets, clamps, insulators, and other accessories.

Hi-Lo TV Antenna Corp.

3540 N. Ravenswood Ave.

Chicago 13, Ill.

Indoor, outdoor spiral antennas. Two models.

Hy-Lite Antennae, Inc.

242 E. 137th St.

New York 51, N. Y.

Yagi, folded dipole, straight dipole, in-line, conical, bat-wing, V, and double-V antennas. Thirty models.

Insuline Corp. of America

36-02 35th Ave.

Long Island City, N. Y.

Wide-band systems, including conical and biconical single, double, and quadruple arrays in standard and heavy-duty models, folded dipoles and indoor-outdoor folded dipoles; 5-element Yagi types; kits and preassembled units. Forty-eight models. Masts, brackets, arresters, mounts, and other accessories.

JFD Mfg. Co.

6101 16th Ave.

Brooklyn, N. Y.

Multielement and multibay dipoles, folded dipoles, and conicals with various modifications; Yagis, window and indoor antennas, boosters. One hundred thirty-five models. Antenna kits, filters, masts, extensions, turnbuckles, cables, guy wires and rings, cable clamps, and other accessories.

Jerrold Electronics Corp.

26th and Dickinson Sts.

Philadelphia 46, Pa.

Master antenna systems for apartment houses, dealers, and communities.

Kay-Townes Antenna Co.

Box 32

Rockmart, Ga.

High-gain, all-band, fringe-area antennas. Twelve models. Cast-aluminum-chimney mounts.

Kenwood Engineering Co., Inc.

Kenilworth, N. J.

TV antenna mounts, including eave, all-position, and parapet mounts; two sizes of wall brackets.

Knepper Aircraft Service Co.

Aero Television Tower Div.

1016-24 Linden St.

Allentown, Pa.

Tubular steel towers and poles. Ten-foot components, 20-foot one-piece tower and pole. Four tower models. Six pole models.

La Pointe-Plascomod Corp.

(Vee-D-X)

Windsor Locks, Conn.

Seven types of Yagi, two of collinear. Six series of Yagis, single-channel, two types of Yagi for multichannel use, three collinear antennas, conicals, folded dipoles and reflectors, dipoles and reflectors. Towers, boosters, lightning arresters, switches, and other accessories.

Louis Brothers

3543 E. 16th St.

Los Angeles 23, Calif.

Wide- and narrow-band arrays, masts, accessories. Seven models.

Milner Mfg. Co.

4359 Northview Drive

Jackson, Miss.

All-aluminum mast for 10- to 100-foot installations. Accessories.

National Electronic Mfg. Corp.

42-08 Vernon Blvd.

Long Island City, N. Y.

Wide-band antenna systems, including conical and quadruple arrays in standard and heavy-duty models; folded dipoles and arrays, window antennas; indoor dipoles and indoor-outdoor folded dipoles; 5-element Yagi types; kits and preassembled units. Forty-seven models. Masts, brackets, arresters, mounts, and other accessories.

Oak Ridge Products

37-01 Vernon Blvd.

Long Island City 1, N. Y.

High- and low-band antennas, straight and folded dipoles, in-line, conicals, fan-type arrays and Yagi arrays for all channels. Thirteen models.

Ohio Aerial Co.

4553 Lewis Ave.

Toledo, Ohio

Conical antennas. Two models. Accessories.

Walter E. Peek, Inc.

132 E. 44th St.

Indianapolis 5, Ind.

Six, 12-, and 16-element arrays with telescopic elements. Five models. Broad-band, double-stacked, collinear-dipole conical. One model.

Peerless Products Industries

812 N. Pulaski Road

Chicago 51, Ill.

Indoor brass dipoles. Two models.

Penn Boiler & Burner Mfg. Corp.

Lancaster, Pa.

Triangular and rectangular towers and poles, in various lengths, both guyed and self-supporting. Tower-top rotating motor mounts, concrete base blocks, pole bases, and associated hardware.

PRODUCTS DIRECTORY

Penn Television Products Co.
3336-40 Frankford Ave.
Philadelphia 34, Pa.

Two- and 3-channel switches. Two-set coupler; base, chimney, roof-peak mounts. Guy-wire rings, collars, and clamps. Twelve models.

Philco Corp.
A St. and Allegheny Ave.
Philadelphia 34, Pa.

Fan, V, and double-V broad-band antennas. Folded high-low antennas, Yagis, cut to channel. Master antenna system. Lightning arresters, two models. TV booster, one model. Chimney, roof, and wall mounts, eight models. Steel masts, two models. Insulators, guy wire, coaxial cable.

Philson Mfg. Co., Inc.
60 Sackett St.
Brooklyn 31, N. Y.

Wide- and narrow-band arrays, conical, Yagi, indoor, and V antennas. Masts, chimney mounts, wall mounts.

Phoenix Electronics, Inc.
Lawrence, Mass.

Yagi, in-line, conical, folded dipole, and stacked antennas. Over 60 models. Chimney, roof, wall, vent-pipe, eave, and universal mounts. Ten models. Standoff insulators and other accessories.

Price Tenna-Trailer Co.
Waukegan, Ill.

Portable TV demonstrating unit. TV masts.

Radelco Mfg. Co.
7580 Garfield Blvd.
Cleveland 25, Ohio

Folded dipoles, conicals, tri-channel and preassembled Yagis and indoor antennas. Twenty models. Stacking kits, wall and chimney mounts, and other accessories.

The Radiart Corp.
3571 W. 62nd St.
Cleveland 2, Ohio

Indoor antennas, conical, all-channel, single- and double-stacked units, folded dipoles and reflectors, high-low, and straight-line antennas. Yagis cut to channel. Twenty-one models. Stacking kits for conicals, super-V's, straight-line antennas, and Yagis. Mounting equipment, standoff insulators, lightning arresters, transmission line, masts.

Radio Corp. of America
Electronic Components
Harrison, N. J.

Unidirectional all-channel antennas, lobe-switching, reversible-beam, unidirectional arrays, V attachments. Lightning arresters, guy rings, and mounting brackets.

The Radion Corp.
1130 W. Wisconsin Ave.
Chicago, Ill.

Indoor dipoles, printed-circuit, and window antennas, high-low folded dipoles, conicals, and Yagis. Base mounts.

Radio Merchandise Sales, Inc.
1165 Southern Blvd.
New York 59, N. Y.

Corner arrays, Yagis, folded dipoles, combinations, in-line, conicals, super-conicals, indoor and window antennas. Masts, lightning arresters, boosters; open transmission line.

Ramsey Radio & Television Co.
Box 297
Ramsey, Ill.

Tubular steel towers in 10-foot sections; 27-foot roof-mounting tower with telescoping mast.

Ray Mfg. Co.
441 Summit
Toledo, Ohio

Conical antennas, motorless, "rotating," double-stacked conicals.

Walter L. Schott Co. (Walsco)
3225 Exposition Place
Los Angeles 18, Calif.

Conicals, double-V's, in single-, 2-, and 4-bay stacks. Yagis. Stacking kits, mast bases, guy rings, guy wire, standoff insulators, feed-through bushings.

Snyder Mfg. Co.
22nd and Ontario
Philadelphia, Pa.

Conicals, folded and straight dipoles. Yagis, window, indoor, and outdoor antennas. Clamps, guy rings, brackets, standoff insulators, and other accessories.

South River Metal Products Co., Inc.
377-379 Turnpike
South River, N. J.

Chimney-mount antenna bases. Five models. Wall brackets, vent-pipe mounts, roof mounts, eave mounts, guy clamps, universal guy rings, screw eyes, adjustable mast standoffs, snap-ons.

Spirling Products Co., Inc.
62 Grand St.
New York 13, N. Y.

Indoor and outdoor antennas. Yagis, conicals, single, and stacked. Eight models.

Square Root Mfg. Corp.
391 Saw Mill River Road
Yonkers 2, N. Y.

Outdoor antennas, built-in quadruphased antennas, indoor and window antennas.

Tele-Matic Industries, Inc.
1 Joralemon St.
Brooklyn, N. Y.

Conicals, 1 bay, 2-stacked, 4-stacked, straight and folded high-low, straight low-folded high; in-line; broad-band Yagis, narrow-band Yagis; square-corner reflectors; high-gain narrow-beam vector antenna double-V, 1-bay, 2-stacked, 4-stacked; double-driven single-channel Yagis, double-driven 2-channel Yagis. Twenty-four models.

T.V. Development Corp.
2024 McDonald Ave.
Brooklyn 23, N. Y.

Indoor antennas. Four models.

T-V Products Co.
152 Sandford St.
Brooklyn 5, N. Y.

Yagis, V's, in-lines, straight and folded dipoles, conical antennas. Roof, chimney, and wall mounts. Masts and joiners. Fifty-four models.

Taylor Mfg. Co.
P.O. Box 851
Lima, Ohio

Antenna mast mountings, chimney, wall, and roof types. Mast couplers and guy-wire clamps. Eleven models.

Technical Appliance Corp. (Taco)
Sherburne, N. Y.

Broad-band, all-channel antennas, conical and high-low types. Yagis, twin-driven 5-element, indoor, dipole, and folded dipole antennas. Sixty models. Accessories, mast mounts, lightning arresters, antenna amplifiers, master antenna distribution systems.

Tel-A-Ray Enterprises, Inc.
P.O. Box 332
Henderson, Ky.

Five-element, wide-spaced Yagis, cut to single channel. Thirteen models. Three-element wide-spaced Yagis, cut to single channel. Thirteen models. Antenna-mounted preamplifier.

Television Laboratories, Inc.
5045 W. Lake St.
Chicago 44, Ill.

Printed-circuit and under-rug antennas. Thirteen models.

Telrex, Inc.
Asbury Park, N. J.

Conical V beams, all-band arrays, indoor, outdoor, window, and Yagi antennas. Thirty-one models.

Tempo T-V Products
2450 Ramona Blvd.
Los Angeles 33, Calif.

Eighteen sizes of steel telescopic masts, from 20 to 70 feet. Steel bases and guy rings.

Thomas Mold & Die Co.
Box 126
Wooster, Ohio

Forty-, 60-, 80-, and 100-foot telescopic masts. Two models. Truck and trailer mounts.

Towers Corp.
3332 E. 55th St.
Cleveland 27, Ohio

Towers, mast extensions, guy rings, and hardware.

Triercraft Products Co.
1535 N. Ashland Ave.
Chicago 22, Ill.

Loaded dipoles, high-low folded dipole and reflector, single and stacked conical, cut-to-channel Yagis, all-wave Yagis, indoor and window antennas. Masts, kits, and accessories. Twenty-six models.

Trio Mfg. Co.
Griggsville, Ill.

Single and 2-channel double-dipole Yagi arrays. Phasing units, rotators, aluminum towers, and accessories. Thirteen antenna models.

Veri-Best Electronics Co.
655 Main St.

Westbury, Long Island, N. Y.

Conical, straight and folded dipoles, Yagi, V and H types, Bazuka antennas, window Bazuka antennas, in-line and barrage antennas. Single-channel, pre-tuned boosters, 2-set couplers, inductive couplers, high-pass filters, chimney and wall mounts, masts, base mounts.

Walnut Machine Co.
1525 S. Walnut St.

South Bend 14, Ind.

Stacked array with aluminum phasing harness. Antenna mount.

Ward Products Corp.—
Div. of The Gabriel Co.

1523 E. 45th St.
Cleveland 3, Ohio

Installation kits, Para-Cons, Yagis, high-low, in-line, Permatube. Twenty-one models.

Warren Mfg. Co., Inc.
250 East St.

New Haven, Conn.

Conical, indoor, Yagi, high-low straight and folded dipole, single and stacked V antennas. Thirty-two models. Chimney, swivel, and eave mounts. Wall brackets, guying and mast clamps, and extenders.

Wells and Winegard
323 S. 8th St.

Burlington, Iowa

Combination-channel Yagi antennas. Four models. Boosters.

Western Coil & Electrical Co.
215 State St.

Racine, Wis.

TV towers, sixteen models. Partially telescoping masts. 19 to 46 feet high, four models. Guy rings, insulators, and other accessories.

Wincharger Corp.
East 7th at Division St.
Sioux City 2, Iowa

Guyed and self-supporting towers. Insulated and noninsulated uniform, triangular cross-section, guyed towers.

Wind Turbine Co.
266 E. Market St.

West Chester, Pa.

Masts, guyed; steel ladder towers, antenna support brackets. Twenty-five models.


The Workshop Associates—
Div. of The Gabriel Co.

135 Crescent Road



Needham Heights 94, Mass.

Double-V all-channel antennas, cut-to-channel beams. Matching transformers, coaxial switches, connectors, and other accessories.

—end—

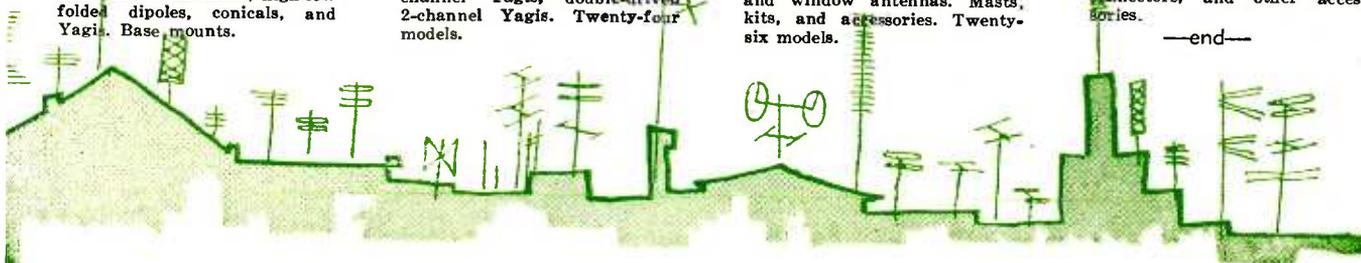

BOOSTERS

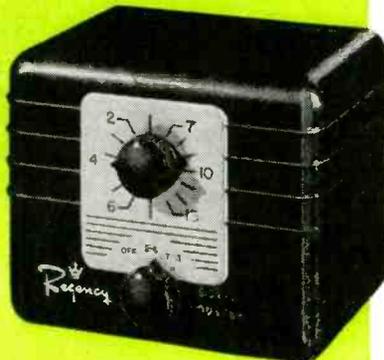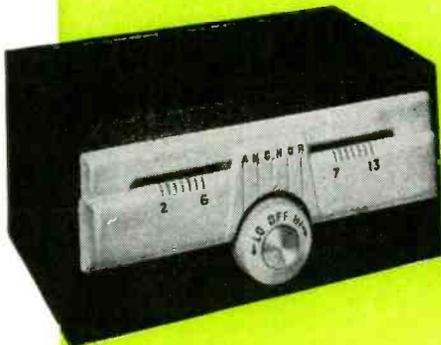

THE TV technician may sometimes solve reception problems by installing a booster. In fringe areas, they may raise signal strength enough to bring in a viewable picture. In city locations where outside antennas are sometimes prohibited, a booster and an indoor antenna may bring in a usable signal not obtainable with the indoor antenna alone. A booster may improve the signal-to-noise ratio enough at bad locations to raise a poor picture to an enjoyable level. Under some circumstances a booster may also be useful in reducing interference.

Boosters fall into four groups: The standard type which mounts beside or on top of the set; the booster mounted on the rear of the cabinet; the antenna-mounted type; and the i.f. booster.

The r.f. booster is far more common than the i.f. type, and of the r.f. boosters the single-tube (usually 6J6) unit is most popular. These usually have switches to change from high- to low-band coils (or portions of the same coil) and slug-tuning to select channels within each band. The circuit is tuned-plate-tuned-grid, neutralized or "balanced" to prevent oscillation. Boosters with capacitor tuning can be found, and one (the DeciMeter Professional) uses switching for each channel, all fine adjustments being factory preset.

The next most common type is the wide-band booster. Its tuning circuits are designed to resonate over a wide range of frequencies—across either the high or low television band. Some of these boosters use separate amplifiers for the high and low bands, with input coils so arranged that no switching is necessary. Others switch to high or low bands, using either a single amplifier or occasionally two separate ones. In some cases the booster will accommodate separate high- and low-band antennas.

The hideaway type of booster, designed to mount on the back of the cabinet, invariably has a thermal or magnetic relay which puts it into operation when the receiver switch is turned on. This automatic feature is found in some standard boosters, as well as a semiautomatic variation in which the receiver is turned on with the booster switch.

The antenna-mounted booster follows standard circuitry. At least two companies use identically the same hookup for their antenna-mounted booster that they use with their regular unit. Power is supplied along the transmission line, with filters at the power supply and booster to keep the TV signal from dissipating into the power circuits. An automatic switch cuts off power to the booster when the TV set is turned off. Antenna boosters designed for commercial 24-hour use have a separate power lead and a manual switch.

Other variations are the single-channel unit, which is just a special kind of tuned booster; the continuous-tuning type, which usually has a Mallory In-

(Turn to page 64)

RADIO-ELECTRONICS for

Manufacturer	Model	Band selection	Channel tuning	Tube(s)	Circuit	Installation	Other features
Alliance Manufacturing Co. Lake Park Blvd., Alliance, Ohio	Tenna-Scope AB	Switching sep. amps	Slug	2-6J6	T.p.t.g.	St.	Auto.
Anchor Radio Corporation 2215 So. St. Louis Ave. Chicago 23, Ill.	ARC-101-75	All-channel switching	Slug	1-6AK5	T.p.t.g.	St.	
	ARC-101-100	All-channel switching	Slug	2-6AK5	2-stage		
Approved Electronic Inst. Corp. 142 Liberty St., New York, N. Y.	A-TV B	Chan. 12-13	Untuned	2-6J6	2-stage	St.	
The Astatic Corp. Conneaut, Ohio	AT-1	Switching sep. amps	2 capacitor conts.	4-6AK5	2-stage	St.	
	BT-1 & BT-2 ¹	Continuous	Inductuner	1-6AK5	T.p.t.g.	St.	
Blonder-Tongue Labs. 38 North 2nd Ave. Mount Vernon, N. Y.	HA-2-M Antensifier	All-channel wide-band	Untuned	3-6J6 1-12AV7	4-stage	St.	Auto.
David Bogen Co., Ltd. 663 Broadway, New York, N. Y.	BB1 and BB2 ²	Switching sep. amps	Slug	2-6J6	T.p.t.g.	St.	Auto.
Brach Manufacturing Corp. 200 Central Ave., Newark, N. J.	50825	Sep. amps wide-band	Slug adjust.	1-6AK5 1-6CB6	T.p.t.g.	St.	
DeciMeter, Inc. 1430 Market St., Denver 2, Colo.	"Professional"	All-channel with switches	Switch-tuned	4-6J6	2-stage	St.	
Electro-Voice, Inc. Buchanan, Mich.	3000	Sep. amps wide-band	Untuned	4-6J6	2-stage	St.	Auto. 1 or 2-ant. input
	3002	Sep. amps wide-band	Untuned	2-6BK7	1-stage broad-band	St.	Auto.
	3010	Sep. amps wide-band	Untuned	4-6J6	2-stage broad-band	Ant.	Auto. 1 or 2-ant. input
I.D.E.A. Inc. 55 No. New Jersey St. Indianapolis 4, Ind.	Regency DB-410	All-channel switching	Slug	1-6J6	T.p.t.g.	St.	
Industrial Television, Inc. 359 Lexington Avenue Clifton, N. J.	IT-75A ³	Sep. amps wide-band	Slug adjust.	1-6AK5 1-6CB6	T.p.t.g.	Rear	Auto. 1 or 2-ant. input
	IT-96A	Single channel	Fixed	2-6CB6	2-stage	Rear	Auto. adj. gain
	IT-90A	Sep. amps wide-band	Untuned	1-6AK5 1-6CB6 1-6BQ7 1-6X4	2-stage cascode	Rear	Auto. adj. gain 1 or 2-ant. input
J F D Manufacturing Co. 6101-23 Sixteenth Ave. Brooklyn 4, N. Y.	VB (channel No.) ⁴	Single channel	Factory preset	1-6J6	T.p.t.g.	Rear	
	SW (channel No.)	Single channel	Factory preset	1-6J6	T.p.t.g.	Rear	Bypassing switch
The La Pointe-Plascomold Corp. Windsor Locks, Conn.	Vee-D-X Outboard Vee-D-X Rocket	Single channel Single channel	Slug adjust. Slug adjust.	1-6J6 1-6J6	T.p.t.g. T.p.t.g.	Rear Ant.	Auto. Auto.
Masco Electronic Sales Corp. 32-28 49th St. Long Island City 3, N. Y.	Sky Chief	All-channel switching	Slug	2-6J6	T.p.t.g.	St.	
	Super Sky Chief	All-channel switching	Slug	4-6J6	T.p.t.g.	St.	
National Co. Inc. 61 Sherman St., Malden, Mass.	TVB-2B	All-channel turret	Capacitor	1-6AK5	T.p.t.g.	St.	Separate output tuning control
Oak Electronics 150 Oak St., Buffalo, N. Y.	Oak	Continuous 54-220 mc	Inductuner	1-6AK5 1-6AG5	T.p.t.g.	St.	Auto.
Radio Merchandise Sales, Inc. 1165 Southern Blvd. New York 59, N. Y.	SP-5	All-channel switching	Slug	1-6AK5	T.p.t.g.		
Regency—See I.D.E.A.							
Sonic Industries Inc. 221 W. 17th St., New York, N. Y.	Super Sonic	Continuous 50-220 mc	Spiral	1-6J6	T.p.t.g.	St.	
Standard Coil Products Co. 2329 No. Pulaski Rd. Chicago 39, Ill.	B-51	All-channel wide-band	Untuned	1-6AK5	T.p.t.g.	St.	
Sutton Electronics Co. 426 West Short St. Lexington, Ky.	16B	All-channel switching	Slug	1-6J6	T.p.t.g.	St.	
Tech-Master Products Co. 443 Broadway, New York, N. Y.	TVB	All-channel switching	Capacitor	1-6AK5	Tuned plate	St.	Kit form
Technical Appliance Corp. Sherburne, N. Y.	Taco 1628	Single channel	Factory preset	1-6AK5	T.p.t.g.	Ant.	Auto.
Tel-A-Ray Enterprises, Inc. Box 332, Henderson, Ky.	TB (channel No.)	Single channel	Fixed	1-6J6	T.p.t.g.	Ant.	Auto., separate power lead
The Turner Company Cedar Rapids, Iowa	TVI	Continuous 54-216 mc	Inductuner	1-12AT7	Cascode	St.	Auto.

Footnotes

¹ BT-1, wooden; BT-2, plastic cabinet.

² BB1, metal cabinet; BB2, wood cabinet.


³ IT-75A Autobooster is a home type; Multibooster a

commercial type amplifier designed for 24-hour use in distribution systems.

⁴ These are made for all TV channels. In addition

there are four two-channel models and one for the FM band.

BOOSTERS

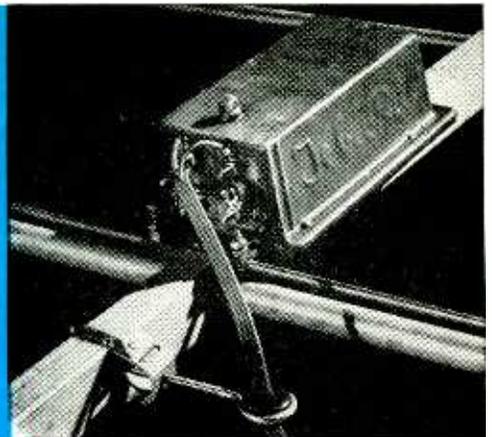

ductuner and is useful across the FM band; and the multistage amplifier, whose tuning systems may be any one of those already described.

The table on page 63 presents the characteristics of all boosters on which we have been able to obtain data. As used in the table, the term "wide-band" refers to an amplifier which operates over one or both of the TV bands without tuning. Some of those with separate amplifiers for high and low bands need neither tuning nor switching. The term "switching," under the heading "Band selection," refers to an amplifier which switches from low to high bands, whether it has a single amplifier or one for each band. "Standard" ("St." in the table) simply means the common type of installation in which the booster is mounted beside or on top of the receiver. "Auto," refers to automatic turning on and off with the receiver, and "T.p.t.g." means tuned-plate-tuned-grid circuit. All other terms are probably self-explanatory.

A close relative of the standard booster is the commercial r.f. amplifier. These in some cases may differ from the home booster only in their more careful design and rugged construction. The Blonder-Tongue CA-1-M is simply the commercial version of the home booster HA-1-M (now superseded by the HA-2-M). The ITI Multibooster is a commercial form of the Auto booster, and differs from it in that it has a gain control and lacks the automatic on-off feature. Since commercial boosters are often designed for 24-hour use, a manual switch is sufficient. One of the JFD antenna-mounted jobs is built to commercial as well as to consumer specifications, and the Brach 01630 is another of the commercial amplifier group.

Distribution systems

An important kind of booster is the *television distribution system*. These are arrays of equipment in which the signal from one antenna is amplified and fed to a number of sets. They may be elaborate sets like those of Jerrold (Philco), TACO, or RCA, intended for apartment houses but actually capable of supplying large villages with other-



wise unobtainable television signals. On the other hand, they may be small two-output jobs, such as the Blonder-Tongue DA2-1-M.

The two-output and eight-output boosters of the smaller multiple-unit systems can be hooked together with these single-output jobs to form multiple installations for stores or small buildings. The large distribution systems for apartment-house use have multitube amplifiers for each channel, often combined with single-output boosters in the line when twin-lead runs are long. Each installation job—whether small or large—is a problem in itself, and the installer should check his own ideas and calculations with those of the manufacturer's engineers before buying a number of units.

A less common type of booster adds another i.f. stage to the receiver. Such boosters are made by Barb City Industries of DeKalb, Ill., Grayburne Corporation of Yonkers, N. Y., and—in a specialized form—by Raytheon. The booster is constructed to plug into one of the i.f. sockets. The i.f. tube which was removed is then plugged back into one of the booster sockets and an additional tube of the same type plugged into an additional socket mounted above it. The additional i.f. tube is the same type as those in the set, if the receiver's filaments are wired in parallel. For series-wired sets, two 6BJ6 or 6BH6's are used in parallel to draw the standard 0.3 ampere. Trimmers to tune the additional stage to the common TV intermediate frequencies are provided.

The Raytheon i.f. booster is intended for the sound channel of certain receivers in the Raytheon-Belmont line, to adapt them to rural fringe-area

reception, where the excellent video i.f. succeeds in picking up a good picture beyond the receiver's sound range.

Making the installation

Installation procedure for standard boosters is simple. The manufacturer's literature often assumes that the set owner will install his own booster. However, the service technician will be called on to make many installations of boosters—some with the original sale of the set, some for those who have sets but prefer not to do any work on their receivers.

It is worth while to note that the instructions often overlook important points. A number of manufacturers urge that the leads to the set be as short as possible. One supplies a pre-cut booster-receiver connection. A few suggest matching antenna to booster and booster to set by running the hand—or sliding the familiar piece of tin foil—along the line till the picture is brightest. The lead may then be cut and the equipment attached at that point, or the tin foil may be secured with tape and left there. At least one manufacturer emphasizes that the point of maximum satisfaction will be true for one channel only, and suggests the set and booster should be matched to the weakest channel, or the particular one to be favored. Rear-mounted boosters require the same care in matching as the standard type, plus tuning adjustments and occasionally gain adjustments.

Attenuators may in some cases be required if the booster is being used to improve selectivity in strong-signal areas. A booster, of course, requires service the same as any other piece of television equipment. —end—

Directory of TV Receiver Characteristics

JANUARY, 1952

Manufacturer	Model	Chassis number	Cabinet or chassis type	AM-FM-SW	C-R tube size (inches) & type	C-R tube anode kilovolts	Number of tubes	Inter-carrier sound	Type of AGC	Video i.f. stages	Video i.f. megacycles	Provision for u.h.f.	Speaker type and size (inches)	Type of tuner	Accessories
Admiral Corp. 3800 West Cortland St. Chicago 47, Ill.	15K21	20T1	T	No	14CP4	12	20	Yes	Ord	3	25.75	Yes	5PM	Tur	No
	17K22, 17M16	21P1, -F1	T	No	17BP4 ¹²	14	21	Yes	Key	3	25.75	Yes	5PM	Tur	No
	27K85, 27K86, 27K87	21P1, -F1	T	No	17BP4 ¹²	14	21	Yes	Key	3	25.75	Yes	10PM	Tur	No
	37K55, 37K56, 37K67	21G1, -Q1	C	AM	17BP4 ¹²	14	21	Yes	Key	3	25.75	Yes	8PM	Tur	Ph
	37F55, 37F56, 37F67	21G1, -Q1	C	AM-FM	17BP4 ¹²	14	21	Yes	Key	3	25.75	Yes	8PM	Tur	Ph
	121K15, 121K16, 121K17	21M1	T	No	20CP4 ⁶	14	21	Yes	Key	3	25.75	Yes	5 or 6 PM	Tur	No
	221K45, 221K46, 221K47	21M1	C	No	20CP4 ⁶	14	21	Yes	Key	3	25.75	Yes	8PM	Tur	No
	321F65, 321F66, 321F67	21N1	C	AM-FM	20CP4 ⁶	14	21	Yes	Key	3	25.75	Yes	10PM	Tur	Ph
	321K65, 321K66, 321K67	21N1	C	AM	20CP4 ⁶	14	21	Yes	Key	3	25.75	Yes	10PM	Tur	Ph
	17RO		T	No	17	19	Yes	Ord					6		
17CD, 17CR		C	No	17	19	Yes	Ord					6			
20RO		T	No	20	19	Yes	Ord					6			
20CD, 20CR		C	No	20	19	Yes	Ord					6			
Affiliated Retailers, Inc. (Artone) 855 6th Ave. New York, N. Y.	Brewster C-VL-17	VL-17	C	FM	17CP4	13.5	23	No	Key	4	26.2	No	12PM	Con	No
	Caronia CO-VL-19	VL-19	C	AM-FM	16AP4	14	29	No	Key	4	26.2	No	12PM	Con	Ph
	Pleewood CO-VL-16	VL-16	C	FM	16GP4	13.5	26	No	Key	4	26.2	No	10PM	Con	Ph
	Gotham T-VL-17	VL-17	T	FM	17CP4	13.5	23	No	Key	4	26.2	No	7PM	Con	No
	Sutton C-VL-16	VL-16	C	FM	16GP4	13.5	26	No	Key	4	26.2	No	12PM	Con	No
Arvin Industries, Inc. Columbus, Ind.	5170, 5171, 5171TM, 5172, 5173	TE302	T	No	17BP4	12	26	Yes	Key	4	45.75	Yes	6D	Sw	PJ-LD
	5204, 5206	TE300	C	No	20CP4 ⁶	13	26	Yes	Key	4	45.75	Yes	10D	Sw	PJ-LD
	5210, 5211, 5212, 5212CFP	TE315	C	No	21AP4	15	26	Yes	Key	4	45.75	Yes	10D	Sw	PJ-LD
	5116R & 5160	4	C	No	17BP4	14	21	Yes	Ord	3	25.75	Yes	10	Tur	No
	5217	4	T	No	17BP4	14	21	Yes	Ord	3	25.75	Yes	6	Tur	No
Automatic Radio Mfg. Co., Inc. 122 Brookline Ave., Boston 15, Mass.	5220	4	C	No	20CP4	14	21	Yes	Ord	3	25.75	Yes	12	Tur	No
	5220T	4	T	No	20CP4	14	21	Yes	Ord	3	25.75	Yes	6	Tur	No
	170C, 170HD, 170FD	630	C	No	17	13.5	30	No	Key	4	25.75	Yes	12		PJ
	170TM	630	T	No	17	13.5	30	No	Key	4	25.75	Yes	5x7		PJ
	20C	630	C	No	20	13.5	28	No	Key	4	25.75	Yes	12		PJ
Race Television Corp. Green and Lenning Sts. South Hackensack, N. J.	20RCH	630	C	No	20	13.5	28	No	Key	4	25.75	Yes	12		PRC
	Club 24	630	C	No	24	13.5	28	No	Key	4	25.75	Yes	12		RC
	R916	1631	T	No	16DP4	10	31	No	Key	4	25.75	No	12PM	Tur	RC
	R920	1930	T	No	20CP4	12	30	No	Key	4	25.75	No	12PM	Tur	RC
	R924	1930	T	No	24AP4A	15	30	No	Key	4	25.75	No	12PM	Tur	RC
Bell Television, Inc. 552 W. 53rd St. New York 19, N. Y.	1720	17AY27	C&T	AM	17BP4	12	22	Yes	Key	4	26.75	Yes	6PM	Con	3PI
	C1714	17AY21	C&T	No	17BP4	12	22	Yes	Key	4	26.75	Yes	6PM	Con	No
	C1715	17AY21	C	No	17BP4	12	22	Yes	Key	4	26.75	Yes	6PM	Con	No
	C1724	17AY21	C	No	17BP4	12	22	Yes	Key	4	26.75	Yes	10PM	Con	No
	C2001, C2002, C2006	20AY21	C	No	20CP4	17	25	Yes	Key	4	26.75	Yes	10PM	Con	No
	M1711, M1712, M1725 ³	17AY21	T	No	17BP4	12	22	Yes	Key	4	26.75	Yes	6PM	Con	No
	M2007, M2008 ³	20AY21	T	No	20CP4	17	25	Yes	Key	4	26.75	Yes	10PM	Con	No
	RC-1718, RC-1720 ³	17AY21	C	AM	17BP4	12	22	Yes	Key	4	26.75	Yes	6PM	Con	3PI
	RC-2005 ³	20AY21	C	AM-FM	20CP4	17	25	Yes	Key	4	26.75	Yes	6PM	Con	3PI

Manufacturer	Model	Chassis number	Cabinet or chassis type	AM-FM-SW	C-R tube size (inches) & type	C-R tube anode kilovolts	Number of tubes	Intercarrier sound	Type of A(G)	Video i.f. stages	Video i.f. megacycles	Provision for u.h.f.	Speaker type and size (inches)	Type of tuner	Accessories
Bendix Radio Baltimore 4, Md.	C172, C182, C200	T9	C	No	17BP4 ⁸	11	22	Yes	Key	3	25.75	Yes	12PM	Sw-Tur	No
	C174, C176B	T5	C	No	17BP4	11	17	Yes	Ord	2	25.75	Yes	12PM	Sw-Tur	No
	T170, T173, T190	T5	T	No	17BP4	11	17	Yes	Ord	2	25.75	Yes	8PM	Sw-Tur	No
	T171	T9	T	No	17BP4 ⁴	11	22	Yes	Key	3	25.75	Yes	8PM	Sw-Tur	No
Cadillac Electronic Corp. 19 West 26th St. New York 10, N. Y.	1651		T	No	16		19	Yes	Ord			Yes	12	Tur	No
	1652, 1654		C	No	16		19	Yes	Ord			Yes	12	Tur	No
	1653		C	No	20		19	Yes	Ord			Yes	12	Tur	No
Capehart-Farnsworth Corp. 3702 E. Pontiac Ave. Ft. Wayne, Ind.	920B, 920M, 921R, 921M	CX-33	T	No	17	11	23	Yes	Ord	3	25.75	Yes	6PM	Tur	No
	922RAB, 922RAM, 924M,	CX-33	C	No	17	11	23	Yes	Ord	3	25.75	Yes	12PM	Tur	No
	924RB, 924AF	CX-33	C	No	20	11	23	Yes	Ord	3	25.75	Yes	12PM	Tur	No
	925M, 928, 939, 940, 941	CX-33	C	AM-FM	17	11	21	Yes	Ord	3	25.75	Yes	12PM	Tur	3PI
	928M	CX-33	C	AM-FM	17	11	21	Yes	Ord	3	25.75	Yes	12PM ¹	Tur	3PI
	937CN, 937M	CX-33	C	AM-FM	19	11	21	Yes	Ord	3	25.75	Yes	12PM	Tur	3PI
	937RCM, 937RM	CX-33	C	AM-FM	20	11	21	Yes	Ord	3	25.75	Yes	12PM	Tur	3PI
Cascade Television Company 153 Chestnut Ave. Irvington 11, N. J.	508	630K3C	C	No	17BP4	14.5	30	No	Key	4	26.25	Yes	12	Tur	PJ
	LD24	630K24	WC	No	24AP4	16	36	No	Key	4	26.25	Yes	12	Tur	RC
	F42-4X3	630K	C	No	5TP4 ⁰	25	42	No	Key	4	26.25	Yes	12	Tur	RC
Certified Radio Laboratories 5507 13th Ave. Brooklyn 19, N. Y.	4920	4920	K	No	16HP4	11	20	Yes	Ord	4	25.75	Yes	4x6	Tur	No
	5120	5120	WC	No	20CP4	14	20	Yes	Ord	4	25.75	Yes	12	Tur	No
Conrac, Inc. 19217 E. Foothill, Glendora, Cal.	27M40, 27W40, 28B40	40	C	No	20CP4	13.5	24	No	Ord	4	25.75	Yes	12PM	Tur	PJ
	32M44, 33B44, 34P44	44	C	No	24AP4	16	24	No	Ord	4	25.75	Yes	12PM	Tur	PJ
Covideo, Inc. 212 Broadway, New York, N. Y.	T-2020		T	No	20	11	20	Yes	Ord	3	25.75		5		CO
	DU17TOR, -TOL, -TOM	356-1	T	No	17BP4A	12	19	Yes	Key	4	26.4	Yes	5 1/4PM	Con	No
Crosley Division Avco Mfg. Corp. 1325 Arlington St. Cincinnati 25, Ohio	DU17CDB, -CDM, -CHB, -CHM, -CHN, -COR, -COM	356-1	C	No	17BP4A	12	19	Yes	Key	4	26.4	Yes	10PM	Con	No
	DU17PDM, -PDB	359	C	No	17BP4A	12	19	Yes	Key	4	26.4	Yes	10PM	Con	Ph
	DU17PHB, -PHM, -PHN	359	C	AM	17BP4A	12	19	Yes	Key	4	26.4	Yes	6x9PM	Con	Ph
	DU20CDM, -CHM, -COR, -COM	357	C	No	20CP4	12	19	Yes	Key	4	26.4	Yes	10PM	Con	No
	DU20PDM	363	C	AM-FM	20CP4	12	19	Yes	Key	4	26.4	Yes	10PM	Con	Ph
	ET140	ET140	T	No	14CP4	11.5	20	Yes	Ord	4	21.75	Yes	6PM	Con & Tur	No
De Wald Radio Mfg. Corp. 35-15 37th Ave. Long Island City, N. Y.	ET170	ET170	T	No	17BP4	11.5	20	Yes	Ord	4	21.75	Yes	6PM	Con & Tur	No
	ET171	ET171	C	AM	17BP4	11.5	20	Yes	Ord	4	21.75	Yes	10PM	Con & Tur	Ph
	ET172	ET172	C	No	17BP4	11.5	20	Yes	Ord	4	21.75	Yes	10PM	Con & Tur	No
	ET190	ET190	C	No	20CP4	11.5	20	Yes	Ord	4	21.75	Yes	10PM	Con & Tur	No
	ET1020	ET1020	T	No	10BP4	11.5	20	Yes	Ord	4	21.75	Yes	6PM	Con & Tur	No
	Allen B. Du Mont Laboratories, Inc. 35 Market St. East Paterson, N. J.	RA147A	RA147A	C	FM	17BP4	10	23	No	Ord	4	26.25	EC	10PM	Con
East Paterson, N. J.	RA112A	RA112A	C	FM	19AP4A	13	25	No	Ord	4	26.25	EC	10PM	Con	TE-PJ-VJ
	RA113B	RA113B	C	FM	17BP4	13	25	No	Ord	4	26.25	EC	10PM	Con	TE-PJ
	RA117A	RA117A	T	No	17BP4	10	23	No	Ord	4	26.25	EC	5PM	Con	TE-PJ-VJ
	RA109A	RA109A	C	FM	19AP4	16	34	No	Ord	4	26.25	CMC	10PM	Con	TE-PJ
Park Lane, Strathmore	RA117A	RA117A	C	No	17BP4	10	23	No	Ord	4	26.25	EC	10PM	Con	TE-PJ-VJ

Manufacturer	Model	Chassis number	Cabinet or chassis type	AM-FM-SW	C-R tube size (inches) & type	C-R tube anode kilovolts	Number of tubes	Intermediate sound	Type of AGC	Video i.f. stages	Video i.f. megacycles	Provision for u.h.f.	Speaker type and size (inches)	Type of tuner	Accessories	
The Hallicrafters Co. 4401 W. Fifth Ave. Chicago, Ill.	17905	L1000S	T	No	16RP4	12	17	Yes	Ord	2	26.25	Yes	5PM	Tur	No	
	17906	P1000D	T	No	17BP4A	12	22	Yes	Ord	3	26.25	Yes	5PM	Tur	No	
	17907	S1000D	T	No	16RP4	12	22	Yes	Ord	3	26.25	Yes	5PM	Tur	No	
	17908	E1000D	T	No	17BP4	12	22	Yes	Ord	3	26.25	Yes	5PM	Tur	No	
	17922	E1000D	C	No	17BP4	12	22	Yes	Ord	3	26.25	Yes	5PM	Tur	No	
	17922CD	T1000D	C	No	17CP4	12	22	Yes	Ord	3	26.25	Yes	8PM	Tur	No	
	17930, 17931, 17932	N1000D	C	No	17CP4	12	22	Yes	Ord	3	26.25	Yes	8PM	Tur	No	
	17933, 17934	M1000D	C	No	17CP4	12	22	Yes	Ord	3	26.25	Yes	8PM	Tur	No	
	21923	Q1000D	C	No	20BP4	12	22	Yes	Ord	3	26.25	Yes	5PM	Tur	No	
	21928	K1000D	T	No	20BP4	12	22	Yes	Ord	3	26.25	Yes	5PM	Tur	No	
	21939	G1000D	C	No	21AP4	12	22	Yes	Ord	3	26.25	Yes	8PM	Tur	No	
	21940	Q1000D	C	No	20BP4	12	22	Yes	Ord	3	26.25	Yes	8PM	Tur	No	
	21941	C1000D	C	AM	21AP4	12	22	Yes	Ord	3	26.25	Yes	8PM	Tur	Ph	
	21943	G1000D	C	No	21AP4	12	22	Yes	Ord	3	26.25	Yes	10PM	Tur	No	
	21980	D900D	C	No	19AP4	12	22	Yes	Ord	3	26.25	Yes	10PM	Tur	No	
	Hoffman Radio Corp. 3761 So. Hill St. Los Angeles, Calif.	636, 637	183	T	No	17BP4A	14	23	No	Key	4	26.1	No	6x12PM	Tur	No
		880, 881, 882, 883, 884, 885,														
886, 887		183	C	No	17AP4A	14	23	No	Key	4	26.1	Yes	12PM	Tur	No	
893, 894, 895		185	C	No	20CP4	14	23	No	Key	4	26.1	Yes	12PM	Tur	No	
896, 897		185	C	No	19AP4A	14	23	No	Key	4	26.1	Yes	12PM	Tur	No	
933, 954		184	C	AM-FM	17BP4A	14	23	No	Key	4	26.1	Yes	12PM	Tur	Ph	
963, 964, 965		186	C	AM-FM	20CP4	14	23	No	Key	4	26.1	Yes	12PM	Tur	Ph	
24B707, 24M708		187	C	No	22AP4 ¹⁴	15.5	23	No	Key	4	26.1	Yes	12PM	Tur	No	
Industrial Television, Inc. 359 Lexington Ave. Clifton, N. J.		Century 776	IT76R	T	No	17R		20	Yes	Ord	3	21.25	No	8PM	Tur	No
		Century 1176	IT76R	C	No	17R		20	Yes	Ord	3	21.25	No	8PM	Tur	No
	Century 1376	IT76R	C	No	20R		20	Yes	Ord	3	21.25	No	8PM	Tur	No	
	Century 379	ITS7R & IT79R	C	No	20R		27	No	Ord	3	21.25	No	12PM	Tur	RC	
	Industrial IT-82R	ITS7R	Tablet-ern	No	20R		27	No	Ord	3	21.25	No	12PM	Tur	RC	
International Television Corp. 238 William St. New York, N. Y.	E-16	None	T	No	16RP4	11	20	Yes	Ord	3	25.75	Yes	6PM	Tur	No	
	F-16	None	T	No	20RP4	11	20	Yes	Ord	3	25.75	Yes	12PM	Tur	No	
			C	No	16RP4	11	20	Yes	Ord	3	25.75	Yes	6PM	Tur	No	
			C	No	20RP4	11	20	Yes	Ord	3	25.75	Yes	12PM	Tur	No	
Jackson Industries, Inc. 500 E. 40th St. Chicago, Ill.	17XT, 17XC, 1700T	117H	C	No	17BP4	12	20	Yes	Ord	3	25.75	Yes	10PM	Tur	No	
	1700C, 3170	117H	T	No	17BP4	12	20	Yes	Ord	3	25.75	Yes	10PM	Tur	No	
	20XT, 20XC, 2000C, 5120	120H	C	No	20CP4	12	20	Yes	Ord	3	25.75	Yes	10PM	Tur	No	
		120H	T	No	20CP4	12	20	Yes	Ord	3	25.75	Yes	10PM	Tur	No	
Kaye-Halbert Corp. 3555 Hayden Ave., Culver City, Cal.	Console	253	C	No	24AP4	16	25	No	Key	3	25	Yes	12	Tur	No	
	Table Model	253	T	No	20CP4	14	25	No	Key	3	25	Yes	5	Tur	No	
Lytle Engineering and Mfg. Co. 4721 N. Kedzie Ave. Chicago 25, Ill.	20" Combination	CTV-222A	C	FM	20CP4	11	18	No	Ord	3	25.75	No	12	Lytle	Ph	
	16" Combination	CTV-220A	C	FM	16RP4	11	15	No	Ord	3	25.75	No	6x9	Lytle	Ph	
	16" Television	CTV-216A	C	No	16RP4	11	18	No	Ord	3	25.75	No	8	Lytle	Ph	
Majestic Radio & Television Division of the Wilcox-Gay Corp. 385 Fourth Ave. New York 16, N. Y.	17C62, 700, 701, 712	106	C	No	17BP4	12	19	Yes	Ord	3	24.75	Yes	10PM	Tur	No	
	17T62, 17T6A1, 17T6B1,															
	70, 72, 73	106	T	No	17BP4	12	19	Yes	Ord	3	24.75	Yes	5PM	Tur	No	
	20C82, 20C83	108	C	No	20CP4	12	19	Yes	Ord	3	24.75	Yes	10PM	Tur	No	
20T8A1, 20T82, 20T83	108	T	No	20CP4	12	19	Yes	Ord	3	24.75	Yes	5PM	Tur	No		

Manufacturer	Model	Chassis number	Cabinet or chassis type	AM-FM-SW	C-R tube size (inches) & type	C-R tube anode kilovolts	Number of tubes	Intercarrier sound	Type of AGC	Video i.f. stages	Video i.f. megacycles	Provision for u.h.f.	Speaker type and size (inches)	Type of tuner	Accessories	
Philmore Mfg. Co., Inc. 113 University Place New York 3, N. Y.	CP731D		WC, K, T	FM ¹³	16 to 24	15	31	No	Key	4	25.75	Yes	12PM	Tur	Ph	
	CP730S		WC, K, T	FM ¹³	16 to 24	16	30	No	Key	4	25.75	Yes	12PM	Tur	Ph	
	TV-167B		C	FM	16TP4	13	25	Yes	Ord	4	25.75	Yes	12PM	Con	PJ	
	TV-191, TV-192		C	FM	19AP4	13	25	Yes	Ord	4	25.75	Yes	8PM	Con	PJ	
	TV-271		T	No	17BP4A	14	25	Yes	Ord	4	25.75	Yes	12PM	Con	PJ	
	TV-273		C	No	17BP4A	14	25	Yes	Ord	4	25.75	Yes	12PM	Con	PJ	
	TV-283		C	No	20DP4A	14	25	Yes	Ord	4	25.75	Yes	12PM	Con	PJ	
	17T153, 17T154, 17T155		T	No	17GP4	13.5	23	Yes	Key	4	40	Yes	8PM	Sw	PJ	
	17T160, 17T162, 17T172, 17T174		C	No	17GP4	13.5	23	Yes	Key	4	40	Yes	8 or 12PM	Sw	PJ	
	21T176, 21T177, 21T178, 21T179		C	No	21AP4	17.5	25	Yes	Key	4	40	Yes	12PM	Sw	PJ	
Pilot Radio Corp. 37-06 36th Street Long Island City, N. Y.	4T101		T	No	14BP4	10.1	23	No	Ord	4	25.5	No	5x7PM	Sw	PJ	
	7T103, 7T104		T	No	17GP4	12	23	No	Ord	4	25.5	No	8PM	Sw	PJ	
	7T111		T	No	17GP4	12	23	Yes	Ord	4	25.5	No	12PM	Sw	PJ	
	7T112		C	No	17GP4	12	23	No	Ord	4	25.5	No	12PM	Sw	PJ	
	7T112-1C		C	No	17GP4	12	23	Yes	Ord	4	25.5	No	12PM	Sw	PJ	
	7T122-1C		C	No	17GP4	12	23	No	Ord	4	25.5	No	12PM	Sw	PJ	
	7T123		C	No	17GP4	12	23	Yes	Ord	4	25.5	No	12PM	Sw	PJ	
	7T123-1C		C	No	17GP4	12	23	No	Ord	4	25.5	No	12PM	Sw	PJ	
	7T132		T	No	17GP4	12	23	No	Ord	4	25.5	No	8PM	Sw	PJ	
	9T105		T	No	19AP4A	12	23	No	Ord	4	25.5	No	8PM	Sw	PJ	
The Radio Craftsmen, Inc. 4401 N. Ravenswood Ave. Chicago, Ill.	9T105-1C		T	No	19AP4A	12	23	Yes	Ord	4	25.5	No	8PM	Sw	PJ	
	9T126, 9T126-1C		C	No	19AP4A	12	23	Yes	Ord	4	25.5	No	12PM	Sw	PJ	
	16T152		T	No	16GP4	12	22	Yes	Ord	4	25.5	No	8PM	Sw	PJ	
	C101		WC	No	24AP4 ⁸	16	24	No	Key	4	26.1	Yes	None ²⁰	Tur	No	
	C200		WC	FM	24AP4 ⁸	16	28	No	Key	4	26.1	No	None	Con	PJ	
	C201		WC	No	24AP4 ⁸	16	27	No	Key	4	26.1	Yes	None	Tur	No	
	See Belmont Radio															
	Regal Electronics Corp. 605 West 130th St. New York, N. Y.	17C22N		C	No	17BP4	13	22	Yes	Ord	4	25.7	Yes	8 PM	Tur	No
		17T22N		T	No	17BP4	13	22	Yes	Ord	4	25.7	Yes	5x7PM	Tur	No
		20C22N		C	No	20CP4	14	22	Yes	Ord	4	25.7	Yes	8PM	Tur	No
20T22N			T	No	20CP4	14	22	Yes	Ord	4	25.7	Yes	5x7PM	Tur	No	
20S1			WC	No	17 to 24	16	31	No	Key	4	25.2	Yes	12PM	Tur	No	
20S6			WC	No	17 to 24	16	31	No	Key	4	25.2	Yes	12PM	Tur	PJ	
Scott Radio Laboratories, Inc. 4541 Ravenswood Ave. Chicago 40, Ill.	AC17 Ravenswood		C	No	17BP4	12	21	Yes	Ord	4	26.1	Yes	12PM	Sw	No	
	AT17 Ravenswood		T	No	17BP4	12	21	Yes	Ord	4	26.1	Yes	8PM	Sw	No	
	310TS Stuart		C	AM-FM	17BP4	12	21	Yes	Ord	4	26.1	Yes	12PM ¹⁵	Sw	Ph	
	510TC-3 Cressy		C	AM-FM	20DP4	12	21	Yes	Ord	4	26.1	Yes	12PM ¹⁵	Sw	Ph	
	924W Wellington		C	No	24AP4	15	21	Yes	Ord	4	26.1	Yes	12PM	Sw	No	
	1000TC Chippendale 1510TA Ashby		C	AM-FM	20AP4 24DP4	15 12	21 21	Yes Yes	Ord Ord	4 4	26.1 26.1	Yes Yes	15PM ¹⁵ 12PM ¹⁵	Sw Sw	Ph Ph	
Sentinel Radio Corp. 2100 Dempster St. Evanston, Ill.	438-TV.M, 438-TV.B		T	No	17BP4A	14	21	Yes	Ord	4	25	Yes	6	Sw	No	
	439-C.V.M, -C.V.B		C	No	17BP4A	14	21	Yes	Ord	4	25	Yes	8	Sw	No	
	440-C.V.B, 441-C.V.M, -C.V.B		C	No	17BP4A	14	21	Yes	Ord	4	25	Yes	8	Sw	No	

Model	Company	Class	Power	Frequency	Bandwidth	Modulation	Antenna	Height	Service	Notes	Year	Price	Availability
443-CVM, 443-CVB	Setchell Carlson, Inc. New Brighton, Minn.	C	No	11	21	Yes	Ord	4	4	25	Yes	10	No
444-CVM, 444-CVB		C	No	14	21	Yes	Ord	4	4	25	Yes	10	No
446-TVM		T	No	14	21	Yes	Ord	4	4	25	Yes	8	No
151-A17	Sheraton Television Corp. 2061 Broadway New York 23, N. Y.	T	AM	14.5	23	Yes	Key	2	2	26.1	Yes	6	No
151-A17LR		T	No	14.5	23	Yes	Key	2	2	26.1	Yes	6	No
151-B17		C	AM	14.5	23	Yes	Key	2	2	26.1	Yes	6	No
151-B17LR		C	No	14.5	23	Yes	Key	2	2	26.1	Yes	6	No
151-B20		C	AM	14.5	23	Yes	Key	2	2	26.1	Yes	6	No
151-B20LR		C	No	14.5	23	Yes	Key	2	2	26.1	Yes	6	No
151-C20	C	AM	14.5	23	Yes	Key	2	2	26.1	Yes	10	Ph	
Super Video DX Console, Sussex Super Video DX Table Windsor	Sightmaster Corp. New Rochelle, N. Y.	C	No	14.5	26	No	Key	4	4	26.25	Yes	12PM	PJ
17E52		T	No	14	24	No	Key	3	3	26.75	No	8	No
20K52		C	No	16	24	No	Key	3	3	26.75	No	8	No
P520		C	SW-FM	27	37	No	Ord	5	5	26.1		12	No
1230		T	SW-FM	10	31	No	No	5	5	26.1		12	No
1630		C	SW-FM	10	31	No	No	5	5	26.1		12	No
1930		C	SW-FM	10	31	No	No	5	5	26.1		12	No
1321		T	No	10	21	Yes	Ord	3	3	25.75		10	No
1621		C	No	10	21	Yes	Ord	3	3	25.75		10	No
1921		C	No	10	21	Yes	Ord	3	3	25.75		10	No
M-PJ-521	P	No	30	21	Yes	Ord	3	3	25.75		10	No	
17BM1, 17TW, 17BG-1, 17C1, 17C2, 17C3, 17CG, 17CD, 17CD-B 20TW, 20TG, 20C, 20C1, 20CP, 20CD A17BM1, A17TW, A17TG-1, A17C1, A17C2, A17C3, A17CG, A17CD, A17CD-B	Starrett Television Corp. 601 West 26th St. New York 1, N. Y.	C, T	No	13	20	Yes	Ord	3	3	26.1	No	5PM	Ph
12S1		C, T	No	13	20	Yes	Ord	3	3	26.1	No	5PM	Ph
17S1		C, T	No	12	19	Yes	Ord	3	3	26.1	No	5PM	No
9121-A		C	AM-FM	26	26	Yes	Key	4	4	26.1	Yes	6x9PM	3PJ
9121-E		C	No	26	26	Yes	Key	4	4	26.1	Yes	12PM	3PJ
9122-A		C	AM-FM	26	26	Yes	Key	4	4	26.1	Yes	12PM	PJ
9124-A		C	AM-FM	26	26	Yes	Key	4	4	26.1	Yes	12PM	PJ
9126-A		T	No	26	26	Yes	Key	4	4	26.1	Yes	6PM	No
9126-B, 9126-C		C	No	26	26	Yes	Key	4	4	26.1	Yes	6x9PM	No
9127-A		C	No	26	26	Yes	Key	4	4	26.1	Yes	6x9PM	No
9202-C, 9202-F	C	No	19	19	Yes	Ord	3	3	25.75	Yes	6x9PM	No	
9202-E	C	No	19	19	Yes	Ord	3	3	25.75	Yes	6x9PM	No	
9202-DA, 9202-DB, 9202-DD	T	No	19	19	Yes	Ord	3	3	25.75	Yes	6PM	No	
9202-DAX, 9202-DDX	C	No	19	19	Yes	Ord	3	3	25.75	Yes	6PM	No	
9204-A	C	No	19	19	Yes	Ord	3	3	25.75	Yes	6x9PM	No	
17C2M	Stromberg-Carlson Co. 100 Carlson Road Rochester 7, N. Y.	C	No	12	26	Yes	Key	4	4	26.4	Yes	12PM	PJ
24CM		C	No	16	30	Yes	Key	4	4	26.4	Yes	12PM	PJ
24RPM		C	AM-FM	16	30	Yes	Key	4	4	26.4	Yes	12PM	3PJ
119CDM, 119CM		C	No	13.5	29	Yes	Key	4	4	26.4	Yes	12PM	3PJ
119M5M, 119RPM		C	AM-FM	13.5	29	Yes	Key	4	4	26.4	Yes	12PM	3PJ
317C5D, 317CO		C	No	15	23	Yes	Key	4	4	26.4	Yes	12PM	3PJ
317M20, 317RPM		C	AM	15	24	Yes	Key	4	4	26.4	Yes	12PM	3PJ
317RPM4		C	AM	15	24	Yes	Key	4	4	26.4	Yes	12PM	3PJ
317TM		T	No	15	23	Yes	Key	4	4	26.4	Yes	5 1/2 PM	3PJ
321C2M, 321CD2M, 321CF		C	No	17	23	Yes	Key	4	4	26.4	Yes	12PM	PJ
324C5M, 324CDM	C	No	17	23	Yes	Key	4	4	26.4	Yes	12PM	PJ	

Manufacturer	Model	Chassis number	Cabinet or chassis type	VAC-PM-SW	C-R tube size & type (inches)	C-R tube mode (kilovolts)	Number of tubes	Intermediate sound	Type of AGC	Video I.F. stages	Video I.F. megacycles	Provision for h.f.	Speaker type and size (inches)	Type of tuner	Accessories
Sylvania Electric Products, Inc. Radio & Television Division 254 Rano St. Buffalo 7, N. Y.	22	1-387	T	No	20DP4A	15	25	Yes	Ord	4	21.9	Yes		Con	Ph
	25	1-507-1	C	No	20BP4	13	24	Yes	Ord	3	21.9	Yes		Con	No
	24	1-387-2	C	No	20DP4A	15	25	Yes	Ord	4	21.9	Yes		Con	Ph
	25	1-387-1	C	No	20DP4A	15	25	Yes	Ord	4	21.9	Yes		Con	Ph
	72	1-366	T	No	17BP4	13	25	Yes	Ord	4	21.9	Yes		Con	No
	73	1-366	C	No	17BP4	13	25	Yes	Ord	4	21.9	Yes		Con	No
	74	1-437-1	C	No	17BP4A	13	25	Yes	Ord	4	21.9	Yes		Con	Ph
	75	1-437-1	C	No	17BP4A	13	25	Yes	Ord	4	21.9	Yes		Con	Ph
	7111	1-366	T	No	17BP4	13	25	Yes	Ord	4	21.7	Yes		Con	No
	7130	1-366	C	No	17BP4	13	25	Yes	Ord	4	21.7	Yes		Con	No
Tech Master Products Co. 443 Broadway New York 13, N. Y.	2430	2430	WC	No	16 to 24	16	30	No	Key	4	25.75	Yes	5x7	Tur	No
	2431C	2431C	WC	No	16 to 24	16	31	No	Key	4	25.75	Yes	12PM	Con	No
	2431P	2431P	WC	No	16 to 24	16	31	No	Key	4	25.75	Yes	12PM	Tur	No
	5116	5116	K	No	10 to 16	9	17	Yes	Ord	3	25.75	Yes	4x6PM	Tur	No
	5120	5120	WC	No	14 to 20	11	20	No	Ord	3	25.75	Yes	4x6PM	Tur	No
	630D19 & 630S19	4	K	No	12 to 20	14	30	No	Key	4	25.75	Yes	5x7PM	Tur	No
	K21	TVJ7	T	No	20CP4	14.5	18	Yes	Ord	3	25.1	No	4x6PM	Sw	No
	K72, K73L	TVJ7	T	No	17BP4	14.5	18	Yes	Ord	3	25.1	No	4x6PAL	Sw	No
	KC2L, KD21M, KD22B	TVJ7	C	No	20CP4	14.5	18	Yes	Ord	3	25.1	No	10PM	Sw	No
	KC71	TVJ7	C	No	17BP4	14.5	18	Yes	Ord	3	25.1	No	8PM	Sw	No
KD71, KD72B	TVJ7	C	No	17BP4	14.5	18	Yes	Ord	3	25.1	No	10PM	Sw	No	
Telequip Radio Co. 601 W. 26th St. New York, N. Y.	C317MF, C517M, C517B, C617M, C617B, C320MF, C720M, C720B, C820M, C820B	All use Chassis 5060	C&T	No	17 & 20	12	19	Yes	Ord	3	26.1	Yes	5, 8, 10	Tur	Ph
	T217L, T417M, T417L, T417MF, T417B, T520MF, T620M														
	TV357, TV365, TV379	8009	T	No	17BP4	12	21	Yes	Key	3	37.3	Yes	6	Sw	No
	TV383	8009	C	No	17BP4	12	21	Yes	Key	3	37.3	Yes	10	Sw	No
	TV385	8009	T	No	20CP4	14	21	Yes	Key	3	37.3	Yes	6	Sw	No
TV386	8009	C	No	20CP4	14	21	Yes	Key	3	37.3	Yes	10	Sw	No	
Tele-Vogue, Inc. (Muntz) 1735 W. Belmont Ave. Chicago 13, Ill.	2053A, 2056A	1712	C	No	20CP4	16	16	Yes	Ord	3	25.75	Yes	10PM	Tur	RC ³
	2055A	1712	T	No	20CP4	16	16	Yes	Ord	3	25.75	Yes	5 1/2 PM	Tur	RC ³
	2457A	1714	C	No	24AP4	16	16	Yes	Ord	3	25.75	Yes	10PM	Tur	RC ³
	T1720	T-20-D	T	No	17CP4	13.5	21	No	Ord	3	25.75	Yes	5PM	Tur	No
C2020	T-20-E	C	No	20CP4	13.5	21	No	Ord	3	25.75	Yes	8PM	Tur	No	
C2420	T-20-E2	C	No	24AP4	14	21	No	Ord	3	25.75	Yes	10PM	Tur	No	
Transvision, Inc. 460 North Ave. New Rochelle, N. Y.	A4 Standard	None	C, WC, T	No	17RP4 or 20RP4	14	25	No	Ord	3	26.4	No	6x9PM	Sw	RC-Ph
	A4 De Luxe	None	C, WC, T	FM	17RP4 or 20RP4	14	25	No	Ord	3	26.4	No	6x9PM	Sw	RC-Ph
Trans-Vue Corp. 58 East Cullerton St. Chicago, Ill.	1400T, 1400TB	114H	T&C	No	14BP4	11	20	Yes	Ord	3	25.75	Yes	6 & 10	Tur	No
	1700B, 1700C, 1700T, 17XC, 17XT, 1700TB	117H	T&C	No	17BP4	11	20	Yes	Ord	3	25.75	Yes	6 & 10	Tur	No
	20XT, 20XC, 200C, 2000CB	120H	T&C	No	20CP4	11	20	Yes	Ord	3	25.75	Yes	6 & 10	Tur	No



NOW-Be a Fully Trained, Qualified RADIO TELEVISION TECHNICIAN IN JUST 10 MONTHS OR! LESS!

**I Send You
18 BIG
KITS
OF RADIO-
TELEVISION
EQUIPMENT**

**TRAIN AT
HOME IN
SPARE HOURS!**

**New "Package" Unit Training Plan
PAY AS YOU LEARN-YOU SET THE PACE!**

**No Monthly Payment Contract
to Sign!**

Now . . . be ready for Radio-Television's big pay opportunities in a few short MONTHS! Frank L. Sprayberry's completely new "Package" training unit plan prepares you in just 10 MONTHS . . . or even less! Equally important, there is NO monthly payment contract to sign . . . thus NO RISK to you! This is America's finest, most complete, practical training—gets you ready to handle any practical job in the booming Radio-Television industry. In just 10 months you may start your own profitable Radio-Television shop . . . or accept a good paying job in this fascinating expanding field at work you've always wanted to do. Mr. Sprayberry has trained hundreds of successful Radio-Television technicians—and stands ready to train you in less than one year, even if you have no previous experience. You learn by DOING . . . actually working with your hands with equipment of special design to illustrate basic theory instead of relying on books alone.

VALUABLE EQUIPMENT INCLUDED WITH TRAINING

The new Sprayberry "package" plan includes many big kits of genuine, professional Radio-Television equipment. While training you actually perform over 300 demonstrations, experiments and construction projects. In addition, you build a powerful 6-tube standard and short wave radio set, a multi-range test meter, a signal generator, signal tracer, many other projects. All equipment is yours to keep . . . you have practically everything you need to set up your own service shop. The interesting Sprayberry book-bound lessons and other training materials . . . all are yours to keep.

EARN EXTRA MONEY WHILE YOU LEARN!

All your 10 months of training is AT YOUR HOME in spare hours. Keep on with your present job and income while learning . . . and earn EXTRA CASH in addition. With each training "package" unit, you receive extra plans and ideas for spare time Radio-Television jobs. Many students pay for their entire training this way. You get priceless practical experience and earn generous service fees from grateful customers. Just one more reason why the Sprayberry new 10 MONTH-OR-LESS training plan is the best Radio-Television training in America today. If you expect to be in the armed forces later, there is no better preparation than good Radio-Television training.

FREE 3 BIG RADIO-TELEVISION BOOKS

I want you to have ALL the facts about my new 10-MONTH Radio-Television Training—without cost! Act now! Rush the coupon for my three big Radio-Television books: "How to Make Money in Radio-Television," PLUS my new illustrated Television Bulletin PLUS an actual sample Sprayberry Lesson—all FREE with my compliments. No obligation and no salesman will call on you. Send the coupon in an envelope or paste on back of post card. I will rush all three books at once!

**Mail
Coupon
Today!**

**NO OBLIGATION
No Salesman
Will Call**

**SPRAYBERRY ACADEMY OF RADIO, Dept. 20E
111 North Canal St., Chicago 6, Ill.**

Please rush to me all information on your 10-MONTH Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me.

Name..... Age.....

Address.....

City..... Zone..... State.....

Please check Below About Your Experience


Are You Experienced? No Experience

**IF YOU ARE
EXPERIENCED IN RADIO**

Men already in Radio who seek a short intensive 100% TELEVISION Training with FULL EQUIPMENT INCLUDED are invited to check and mail the coupon at the right.

A Guiding Beacon For
Quality Electronic Parts

Your Local
RADIART
Distributor

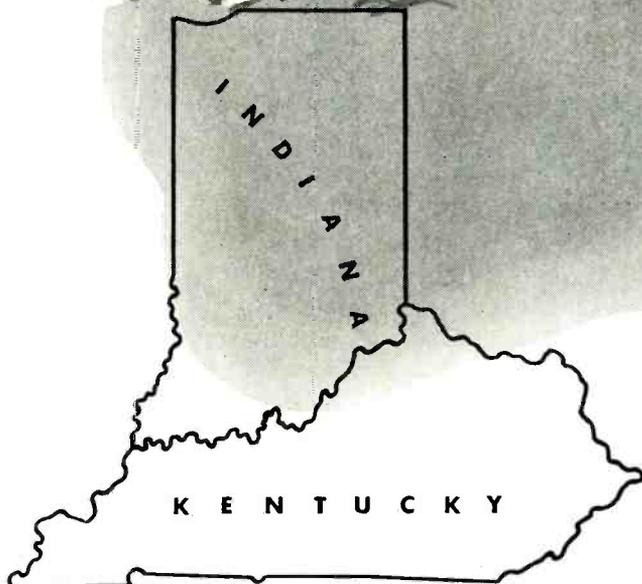

These Are The Cities With
RADIART Distributors in Indiana and Kentucky
Served by **HOEMIG SALES CO.**
Fort Wayne, Indiana

INDIANA


- ANDERSON
- ANGOLA
- BLOOMINGTON
- EIKHART
- EVANSVILLE
- FORT WAYNE
- GARY
- HAMMOND
- INDIANAPOLIS

- LAFAYETTE
- MARION
- MUNCIE
- RICHMOND
- SOUTH BEND
- TERRE HAUTE

KENTUCKY

- OWENSBORO
- PADUCAH

BUY OF THE MONTH

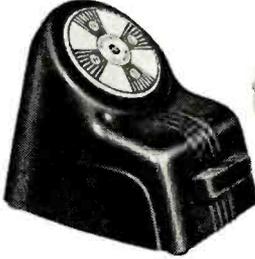


The RADIART "TELE-ROTOR" is the most POWERFUL ... most DEPENDABLE TV antenna rotator you can buy! It offers power when and where you need it ... to turn any TV antenna array under all weather conditions! Model TR-2 ... complete rotator with "COMPASS CONTROL" cabinet having illuminated "perfect pattern" dial - (uses 8 wire cable) .. \$49.95
See your Radiart distributor, or write us.

FOR NAME OF YOUR NEAREST RADIART DISTRIBUTOR
USE COUPON BELOW

HOEMIG SALES CO. 1730 Clover Lane, Fort Wayne 7, Indiana

..... Please send names of the Radiart Distributors in my area stocking the following Radiart products in which I am interested: Tele-Rotors, Vibrators, TV and FM Antennas, "Spee-Dee" Chimney Mounts, Lightning Arresters, Auto Aerials, Power Supplies
..... Please have a Radiart Distributor call on me.

Name

Address

City State



THE RADIART CORPORATION CLEVELAND 2, OHIO

VIBRATORS • AUTO AERIALS • TV ANTENNAS • ROTATORS • POWER SUPPLIES



ELECTRONICS and MUSIC

part XIX

More on the Baldwin...

Tone coloring and note blending circuits

By **RICHARD H. DORF**

IN THE Baldwin electronic organ, as well as in pipe organs, two classes of organ tones are extremely important in addition to those discussed last month. These are the diapason family and the "stopped" tone colors. Both

have the peculiarity of having prominent odd harmonics, with even harmonics fairly subdued. Even harmonics do appear with some effect in the diapasons, but they are almost completely missing in the stopped colors. These

tones have a hollow kind of sound like those produced by a clarinet when played in the low register.


To produce the stopped tones it is necessary not only to pass them through formant filters like other types of tones but to begin with a generator waveform which has almost entirely odd harmonics. The sawtooth has both odd and even, and an ingenious system is used in the Baldwin to eliminate the evens. It is done by mixing octave-related sawtooth waves to produce a square wave which, being symmetrical, is composed almost entirely of odd harmonics which create that pleasing tone effect.

The mixing process is illustrated graphically in Fig. 1. When a given key on the swell manual is pressed, an 8-foot and a 4-foot tone are switched into their respective networks and emerge through the network outputs. They have approximately the same amplitude, a sawtooth waveshape, and are in phase.

A special outphasing circuit is employed for the mixing, and *a* of Fig. 1 shows how the waves are mixed. A is the 8-foot, or lower-frequency, wave. B is the 4-foot wave, one octave above wave A. Wave A has been reversed in phase before the mixing and wave B has been reduced to half the amplitude of A. Now, by simple graphical analysis, it can be seen that the resultant is a square wave, as in *b* of Fig. 1.

The mid-point or average value of instantaneous values of waves A and B, when added graphically or algebraically, produces or defines the resultant square wave. The reader can prove this for himself. At each of several points in *a* of Fig. 1, place a point at the resultant value of voltage. This point is halfway between the individual values of the two waves. When all the points are connected the result will be a square wave.

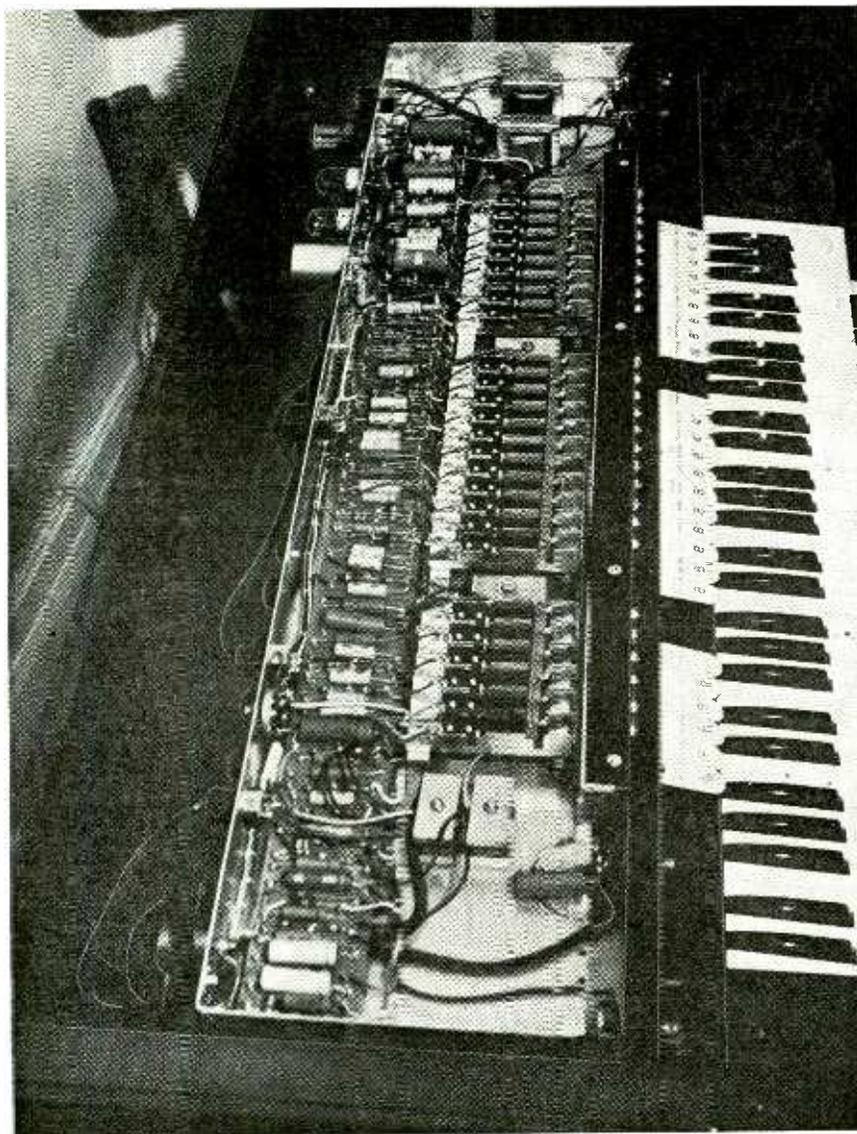Let's look at it in another way. We start with an 8-foot tone of, let us say, 1,000 cycles. Its second, third, and fourth harmonics are 2,000, 3,000, and 4,000 cycles. We mix with it a 4-foot tone of 2,000 cycles, in phase opposition. Each harmonic of the second tone will buck out any harmonic of the first tone whose frequency coincides, since the



A side, top view of the tone-color box of the Baldwin Organ containing all the filter elements for the stops, the stop switches, outphaser, and the preamplifier.



Announcing a new service that only RIDER could bring you!

TEK

IT'S COMPACT!



FILE

IT'S FACTORY AUTHORIZED!




Now—the new Rider TV8 Manual available two ways. First as the standard single volume—or the sensational, new Tek-File way!

For the first time you can have the complete Rider TV data you need . . . bound separately by individual manufacturers. You order only what you need—when you need it . . . at a low, low price that will amaze you!

Tek-File comes in individual sealed, tamper-proof boxes. Each box contains a minimum of 128, 8½" x 11" pages folded and bound in one or more standard folders for easy filing. The folders are indexed by manufacturers . . . for quick, easy reference. Ideal for service calls and for separate set servicing in the shop.

See your jobber today. Learn how Tek-File can make your servicing job—faster—easier—more profitable!

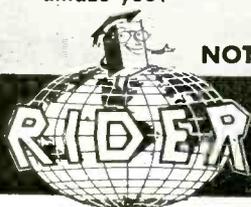NOTE: Starting in November all RIDER TV data will be available the new TEK-FILE way!



JOHN F. RIDER Publisher, Inc.
480 Canal Street, New York 13, N. Y.

two are in phase opposition. The coinciding frequencies are all the even harmonics of the lower-frequency tone, leaving only the odd-numbered frequencies, 1,000, 3,000, 5,000, etc. The result is a practically square wave of the 8-foot fundamental frequency. The circuit which does the outphasing appears in Fig. 4, which will be explained later

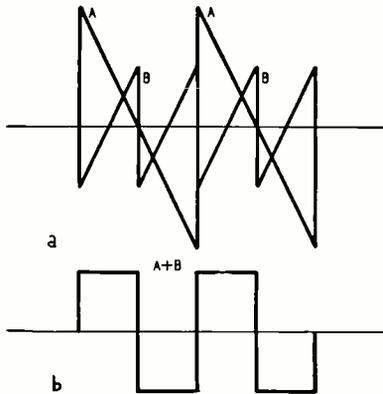


Fig. 1—To produce the “hollow” woodwind effect, even harmonics are phased out by mixing 8-foot and 4-foot tones in correct ratios and phase relations.

Fig. 7 of last month’s article showed the keying circuit with which all the tones of the generators are keyed and channeled through successive attenuator networks to their outputs. The illustrations on these pages show what happens next to these tones.

The tone-color box

The tone-color box is shown in the photograph. It is a shallow metal “tray” containing all the R-C-L filters which form the tone colors for the various stops in accordance with the formant principle discussed last month. The box is just under the top cover of the organ console. Its components can be reached by first removing the wooden top, then unscrewing and removing the metal top of the box itself.

The tone-color box also contains three tubes—one for the outphasing circuit and two for the preamplifier which follows all the filters. Along its front edge are ranged all the stop switches. These are gradual-contact switches of the same type used for keying. Circuit-wise

they follow each filter. For simplicity they are shown as ordinary s.p.s.t. switches in the diagrams of Figs. 2, 4, and 5. The resistor R preceding each one is the 5,000-ohm printed-circuit resistance between the input terminal of each switch and the leaf contactor.

Fig. 2 shows the tone-coloring system for the pedal clavier. There are two outputs from the pedal switching system—8-foot and 16-foot. The pedal 8-foot FLUTE stop is a soft-voiced one, used to add clarity to the pedal in soft music. Let us briefly analyze the filter which produces it to show how the system works.

The filter is made up of three L-section R-C filters in cascade, each giving, theoretically, an attenuation of about 3 db per octave above its turnover frequency. The 47,000-ohm resistor and .01- μ f capacitor have a turnover frequency of about 320 cycles. The next two sections have turnovers of about 160 and 65 cycles, respectively. The resultant curve of the entire filter has low-pass action, with a slope carefully engineered to produce the most lifelike and pleasing tone. The spectrum of this curve agrees closely with the typical flute spectrum shown in Fig. 10 of last month’s article.

Most of the stop filters do not have attenuation curves as steep as that of the 8-foot pedal FLUTE, and the curves vary widely. In general, however, most do have low-pass action. While this attenuates harmonics of each generated tone to form the correct spectrum characteristic, it also has the effect of attenuating the fundamentals of the generated tones as the tones become higher in pitch. The attenuator network following the switches, shown in Fig. 7 last month, partially offsets this. The outputs of the switching networks are taken from the high-frequency end, which means that the higher tones are initially louder. If this were not done, some of the higher notes would be barely audible. As each of the stop qualities is described below, examine the filter and note now the effect is achieved.

The 8-foot pedal CELLO is a string-type stop, moderately voiced and somewhat like the orchestral cello. The diapason family is the backbone of the organ, not imitative of any orchestral

instrument. The pedal 16-foot OPEN DIAPASON is voiced rather loud. Notice that it has a fairly large harmonic content, with only a single-section R-C filter from the 16-foot sawtooth source. Note, too, that it has a certain amount of 8-foot tone added. As with a few other stops, a dual switch is required to avoid disturbing the busses. As with all the stops, the loudness of a particular tone quality is governed by the resistor which follows the filter, just preceding R (as well as by the filter itself, of course).

The 16-foot BOURDON is a softly voiced stop of the flute family, with great depth and clarity. The 16-foot pedal DULCIANA is as the name implies, a very soft tone, and belongs to the diapason family. The output lead of the pedal department (marked W) goes to the preamplifier.

The great manual is the lower one and its filter schematic appears in Fig. 3. The 16-foot GREAT BOURDON is a soft flute stop which adds body to an ensemble.

Note that the 4-foot CLARION filter is fed from the low-frequency end of the 4-foot great switching network. This is because it is a high-pass filter and deals with high-pitched tones. If it were fed from the high-frequency end, the higher notes would be too pronounced and the lows would almost disappear.

The remainder of the great stops have two inputs each. One is from the 8-foot or 4-foot great switching network, as shown, but the other is from lead X in the pedal department, where one of the stop switches is labeled “8’ GREAT TO 8’ PEDAL.” This is a coupler, and when the switch is closed the tones coming from the 8-foot pedal switching network pass not only through the pedal stops but also through whatever great stops have been selected. Thus the resources of the great can be made available to the pedal as well. The great also has a coupler (Fig. 3), Swell to GREAT 8’. This coupler sends 4-foot great tones to the 4-foot swell stops and 8-foot great tones to the 8-foot swell stops. Thus when playing on the great manual the swell stops can be used in addition to the great stops. The swell has no couplers and when playing on the swell manual the player can use only the swell stops.

The great 4-foot CLARION is a very keen reed tone of great brilliance. It has a definite formant range in which fundamentals and harmonics are greatly emphasized, due to the resonant L-C filter. The great 4-foot VIOLINA is a string-type stop with a high-pass characteristic. The OCTAVE is a diapason tone in the 4-foot register.

The 8-foot TRUMPET is a loud, heavy-voiced reed, again with a resonant filter. It is a surprisingly good imitation of the orchestral trumpet when played in certain ways. The 8-foot great DULCIANA is much like the pedal DULCIANA, but in a higher register. The 8-foot MELODIA is a soft flute-type tone. The 8-foot OPEN DIAPASON possesses the tone quality of which the average person


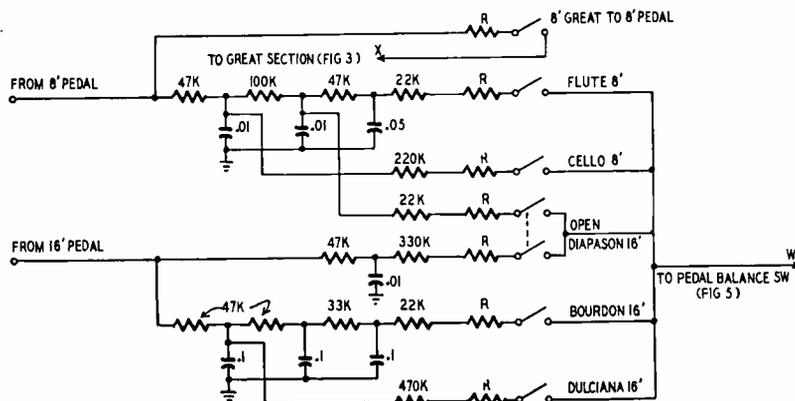


Fig. 2—The resources of the pedal department include five stops and a coupler.

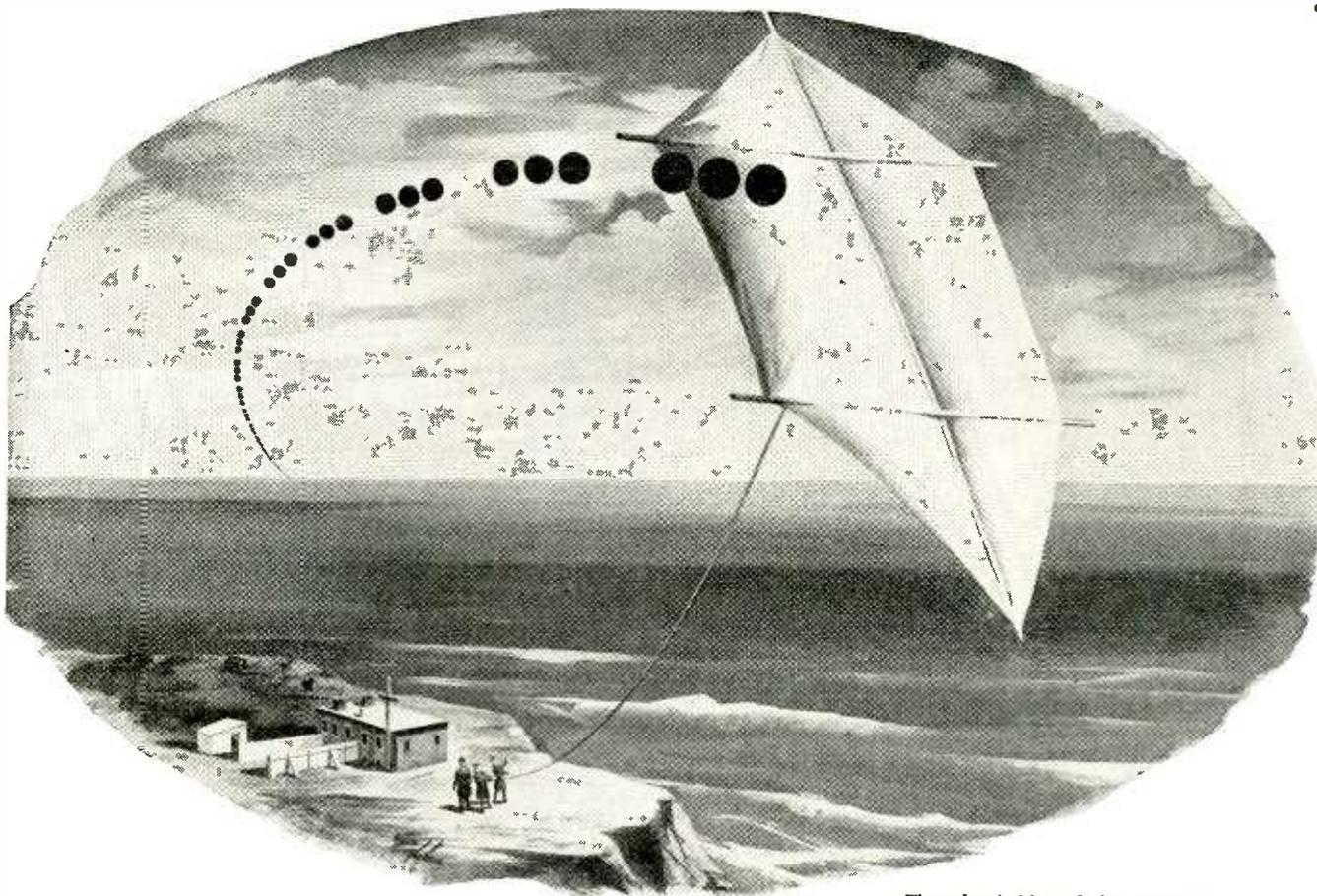

Three dots in Morse Code—sent from England and received by Marconi in Newfoundland—proved that wireless signals could span the Atlantic.

Three dots that opened a new era!

When Marconi, on December 12, 1901, heard a "3-dot" radio signal—the letter "S" in Morse Code—across 1,800 miles of sea, it was an experimental triumph that opened a new era in communications.

Before this historic event, wireless telegraphy had been limited primarily to communications between the shore and ships at sea. Marconi's success, however, was the forerunner of many other developments which led eventually to RCA world-wide radiotelegraph service that now operates more than 80 direct circuits to 66 countries.

As radio progressed, its usefulness was ex-

panded by invention and development of the electron tube, the harnessing of short waves which made world-wide transmission a reality, and the automatic transmission and reception of messages at high speed.

Radio, with its magic of spoken words and music broadcast over the world . . . television, the miracle of pictures in motion transmitted through the air . . . these mediums of modern communication have added notable links in the chain of electronic advances first forged in 1901 from the mere sound of three dots.


See the latest wonders in radio, television, and electronics at RCA Exhibition Hall, 36 West 49th St., N. Y. Admission is free. Radio Corporation of America, RCA Building, Radio City, N. Y. 20, N. Y.




Today RCA Communications sends and receives about 81 million words each year across the Atlantic; the messages are automatically recorded on tape, for error-free transmission.



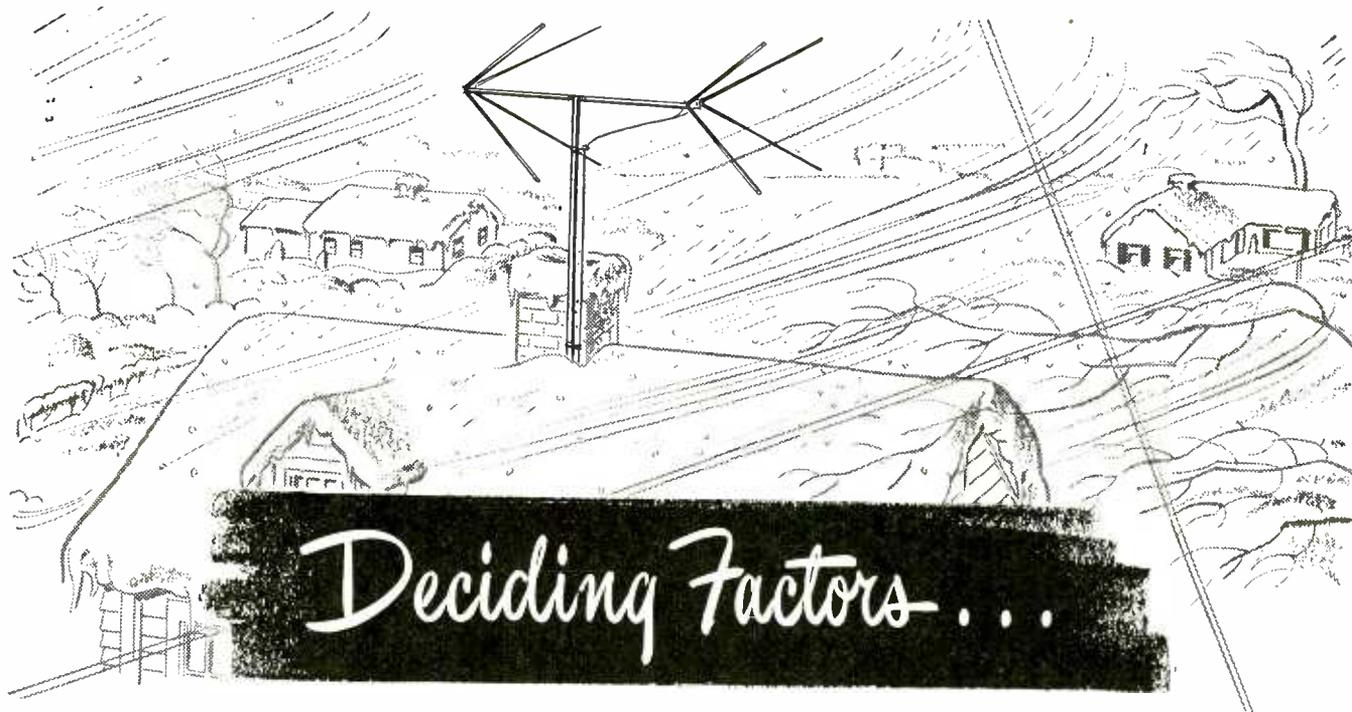RADIO CORPORATION of AMERICA
World Leader in Radio—First in Television



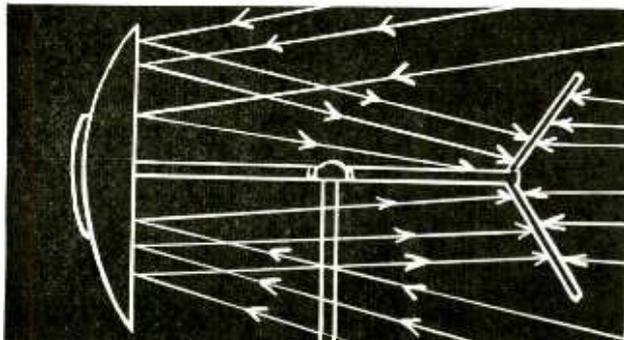WITH **WARD** ANTENNAS INSTALLATIONS *Stay Put!*



Diagrammatic sketch showing how parabolic reflectors gather in and concentrate energy on conical elements.

WARD ANTENNA INSTALLATION KITS . . . time savers . . . money makers . . . cut the cost of stocking and storing parts . . . give everything you need at your fingertips at installation time. **KIT MODELS TV-105 and TV-103** contain necessary 6 element Ward Conical bays, including mast, base, stand-offs, lead-in, lag bolts all in one kit. Write for catalog.

Ward mechanical superiority is a deciding factor weighing heavily with men in the field. Ward installations "stay put" . . . eliminate call-backs.

WARD PARA-CON* Antenna not only combines parabolic and conical principles to assure maximum picture clarity on all channels in most reception areas—but it features a material and structural strength that defies the elements, and assures a permanent installation. Aluminium tubing, molded plastic insulators, heavy duty crossarm and other construction features make for rugged strength and unsurpassed durability. Write for catalog.

As the oldest, largest exclusive antenna manufacturer, Ward combines a complete, widely-diversified line of Radio and TV antennas. A single source of supply gives you every advantage and every superiority that means satisfied customers and bigger profits to retailers and service technicians.

WARD

**WORLD'S OLDEST AND LARGEST
EXCLUSIVE MANUFACTURER OF**

ANTENNAS

THE WARD PRODUCTS CORPORATION

Division of The Gabriel Co.

1523 East 45th Street • Cleveland 3, Ohio

In Canada: Atlas Radio Corp., Ltd., Toronto, Ont.

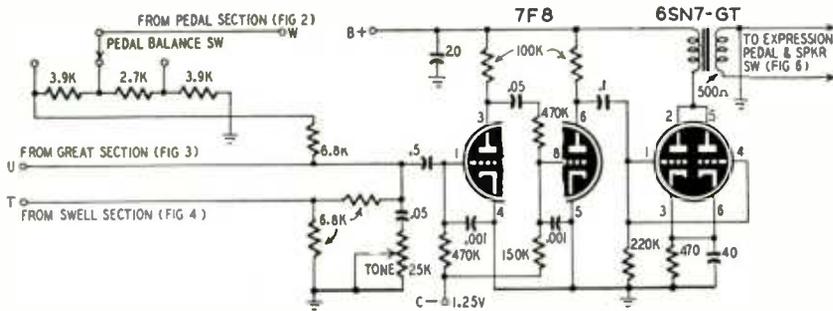


Fig. 5—The preamplifier, located in the tone color box, has 3 separate inputs.

triode, both from the swell key network and from the swell-to-great coupler. At the output of the first triode the phase is reversed. The tones are then fed through the second triode, along with 4-foot tones mixed in, at the proper strength, between the two stages. The output, consisting of 8-foot tone with even harmonics very much attenuated, is fed to the next three stop filters.

The STOPPED FLUTE is a fairly heavy flute tone. Since only odd harmonics are

ceived in organ tradition as imitating the human voice, is a reed stop of unusual quality. In the Baldwin this is produced by the outphaser and by the fact that it has two distinct formants, one around 600 cycles and the other in the neighborhood of 2,000 cycles.

Preamplifier circuit

The output of each of the three departments goes to the preamplifier diagrammed in Fig. 5, in the tone-color box. Lead W from the pedal department goes to the arm of a voltage-divider switch so that the volume of the pedal tones can be adjusted during installation. The pedal clavier controls some fairly loud tones as low as 32 cycles. At this low frequency sound diffuses extensively, and windows, fixtures, and furnishings may tend to vibrate. The setting of the pedal balance switch depends on the acoustics of the room or hall in which the organ is located.

Lead T from the swell section enters the preamplifier through a simple isolating network, while lead U from the great department enters without any isolation resistor of its own, the isolation of the other two inputs being sufficient. The .05- μ f capacitor and variable 25,000-ohm resistor between preamplifier grid and ground make up a tone control. With the resistor at maximum resistance, the capacitor has least shunting effect and tone is most bril-

liant. As the resistor value is reduced, more and more of the higher tones and harmonics are shunted to ground. The setting of this control, which is on the front of the console panel, depends somewhat on the acoustics of the room or hall, but is often varied during playing. It is seldom left at the full brilliant position, especially when, as in some cases, special speaker systems with high-efficiency tweeters are used. The preamplifier terminates in a 500-ohm transformer.

Two additional controls appear on the organ console. The first is the usual expression or swell pedal which controls volume. The pedal operates a potentiometer (Fig. 6), which is connected to the preamplifier output and returns through a tone-compensating and limiting network to ground. The 22- and 220-ohm resistors and the 10- μ f capacitor constitute a lower net impedance for high frequencies than for lows. When the potentiometer arm is at the bottom the proportion of middle and high frequencies appearing at the output of the attenuator network is less than the lows. This compensates to some extent for the characteristic of the human ear which hears less bass when volume is low. It is, in effect, a simple loudness control, or compensated volume control of the type used on many receivers. The attenuator output goes to a panel switch with three positions.

In pipe organs one set of pipes, known as the echo organ, is sometimes located at a distance from the others so that the effect is that of having tones float in from a distance. The effect is especially marked in a very large church with strongly reflective walls. This effect can be produced in the Baldwin by adding a separate set of loudspeakers and a power amplifier at some distance. The switch of Fig. 6 connects the attenuator output to either the main speakers or the echo speakers, or to both. When only one set is being used, a 1,000-ohm resistor shorts the line to the other set preventing an open-ended line.

Tone cabinets

Several different styles of tone cabinets containing loudspeakers and power amplifiers are available. At least two 15-inch loudspeakers are used in all of them. It is possible, however, to employ any amplifier and speaker combination desired and some installations are very elaborate indeed. Two amplifier models are supplied, one with 20-watt maximum output and the other with 40-watt. The 40-watt amplifier is diagrammed in Fig. 7. It is simple but quite adequate. It has only two stages, an input and phase-inverter stage combined, and a paralleled push-pull output, with inverse feedback from output transformer secondary to the input triode cathode. So-called high fidelity is not a requirement in an organ from a frequency response standpoint, although freedom from intermodulation is. There is, however, a very marked difference

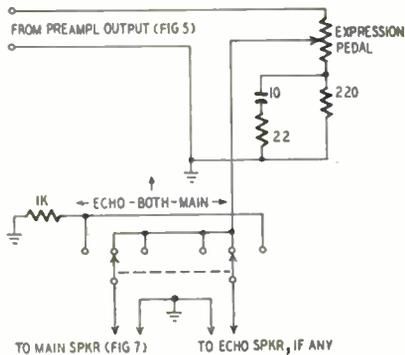


Fig. 6—Preamplifier output goes to the expression pedal, and speaker switch.

heard it has a hollow sound peculiar to woodwind instruments and to organ pipes with one closed end. The CLARINET is much like the orchestral instrument, again with the typical hollow, woodwind sound. The VOX HUMANA, originally con-

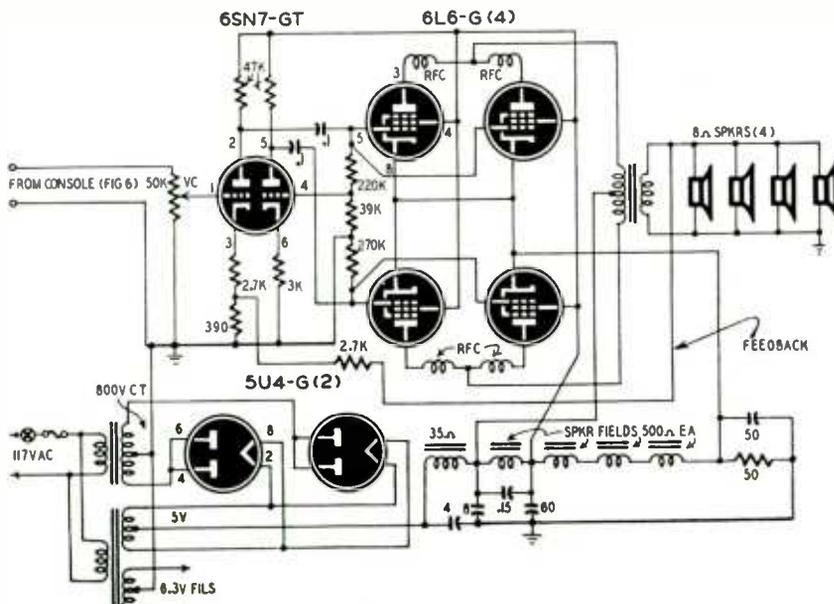


Fig. 7—The Baldwin uses 20- or 40-watt speaker systems. This is the 40-watt unit.

The SUPERIOR Line

We have been manufacturing Test Equipment for twenty years . . . rugged instruments designed for all 'round use—in the shop—in the basement—in the house. Our units can be piled in the back of your car with the rest of your gear. Accurate? We must make our units accurate to required tolerances to stay in this business. Not the

1/10th of 1% required by laboratory technicians but the 2% accuracy required for service work. Price? Compare the dealer's price of any model in our line with the price of any comparative unit. Ours is always lower priced.



Superior's TELEVISION BAR GENERATOR

THROWS AN ACTUAL BAR PATTERN ON ANY TV RECEIVER SCREEN!!

- Two Simple Steps**
1. Connect Bar Generator to Antenna Post of any TV Receiver.
 2. Plug Line Cord into A.C. Outlet and Throw Switch.

RESULT: A stable never-shifting vertical or horizontal pattern projected on the screen of the TV receiver under test.

SPECIFICATIONS:

Power Supply: 105-125 Volt 60 Cycles
 Power Consumption: 20 Watts
 Channels: 2-5 on panel, 7-13 by harmonics
 Horizontal lines: 4 to 12 (Variable)
 Vertical lines: 12 (Fixed)
 Vertical sweep output: 60 Cycles
 Horizontal sweep output: 15,750 Cycles

FEATURES:

1. Provides linear pattern to adjust VERTICAL linearity, height, centering.
2. Provides linear pattern to adjust HORIZONTAL drive, width, peaking, linearity, centering.

3. Provides vertical sweep signal for adjusting and synchronizing vertical oscillator discharge and output tubes.
4. Provides vertical signal to replace vertical oscillator to check vertical amplifier operation.
5. Provides horizontal sweep signal for adjusting and synchronizing horizontal oscillator A.F.C. and output tubes.
6. Provides horizontal sweep signal to check H.V. section of fly-back and pulse operating power supplies.
7. Provides signal for testing video amplifiers.
8. Can be used when no stations are on the air.

TV Bar Generator comes complete with shielded leads and detailed operating instructions. Only

\$39⁹⁵
NET

Superior's new model 770

AN ACCURATE POCKET-SIZE

VOLT-OHM MILLIAMMETER

(SENSITIVITY—1000 OHMS PER VOLT)

- ★ Compact—measures 3 1/8" x 5 7/8" x 2 1/4".
- ★ Uses latest design 2% accurate 1 Mil. D'Arsonval type meter.
- ★ Same zero adjustment holds for both resistance ranges. It is not necessary to readjust when switching from one resistance range to another. This is an important time-saving feature never before included in a V.O.M. in this price range.
- ★ Housed in round-cornered, molded case.
- ★ Beautiful black etched panel. Depressed letters filled with permanent white, insures long-life even with constant use.

SPECIFICATIONS

6 A.C. VOLTAGE RANGES:
 0-15/30/150/300/1500/3000 VOLTS
 6 D.C. VOLTAGE RANGES:
 0-7.5/15/75/150/750/1500 VOLTS
 4 D.C. CURRENT RANGES:
 0-1.5/15/150 M.A. 0-1.5 AMPS.
 2 RESISTANCE RANGES:
 0-500 OHMS 0-1 MEGOHM

The Model 770 comes complete with self-contained batteries, test leads and all operating instructions.

\$14⁹⁰
NET

Superior's new model TV11

TUBE TESTER

SPECIFICATIONS:

- ★ Tests all tubes including 4, 5, 6, 7, Octal, Lock-in, Peanut, Bantam, Hearing Aid, Thyatron, Miniatures, Sub-Miniatures, Novals, Sub-minars, Proximity fuse types, etc.
- ★ Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to the pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-11 as any of the pins may be placed in the neutral position when necessary.
- ★ The Model TV-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.
- ★ Free-moving built-in roll chart provides complete data for all tubes.
- ★ Newly designed Line Voltage Control compensates for variation of any Line Voltage between 105 Volts and 130 Volts.
- ★ **NOISE TEST:** Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.



★ **EXTRA SERVICE**—The Model TV-11 may be used as an extremely sensitive Condenser Leakage Checker. A relaxation type oscillator incorporated in this model will detect leakages even when the frequency is one per minute.

★ The Model TV-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a beautiful hand-rubbed oak cabinet complete with portable cover


\$47⁵⁰
NET

Superior's new model 670

SUPER-METER

A COMBINATION VOLT-OHM MILLIAMMETER PLUS CAPACITY REACTANCE INDUCTANCE AND DECIBEL MEASUREMENTS

SPECIFICATIONS:
 D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts
 A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
 OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
 D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5 Amperes
 RESISTANCE: 0 to 500/100,000 Ohms 0 to 10 Megohms
 CAPACITY: .001 to .2 Mfd. .1 to 4 Mfd. (Quality test for electrolytics)
 REACTANCE: 700 to 27,000 Ohms 13,000 Ohms to 3 Megohms
 INDUCTANCE: 1.75 to 70 Henries 35 to 8,000 Henries
 DECIBELS: -10 to +18 +10 to +38 +30 to +58

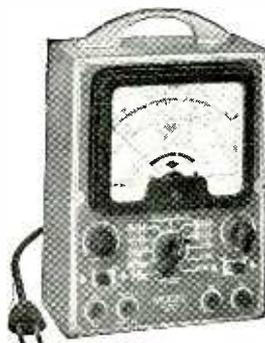

ADDED FEATURE:

The Model 670 includes a special GOOD-BAD scale for checking the quality of electrolytic condensers at a test potential of 150 Volts.

The Model 670 comes housed in a rugged, crackle-finished steel cabinet complete with test leads and operating instructions. Size 5 1/2" x 7 1/2" x 3".

\$28⁴⁰
NET

Superior's new model 660

An AC Operated

SIGNAL GENERATOR

Provides Complete Coverage for A.M.-F.M. and TV Alignment

SPECIFICATIONS:

- ★ Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 240 Megacycles on powerful harmonics.
- ★ Accuracy and stability assured by use of permeability trimmed Hi-Q coils.
- ★ Built-in 400 Cycles sine wave audio oscillator used to modulate the R.F. signal also available separately for audio testing of receivers, amplifiers, etc.
- ★ Oscillator Circuit: Uses a miniature high frequency type of acorn triode in a Hartley circuit to insure a high degree of stability. By using the same type of triode as a buffer amplifier, complete and positive isolation between the R.F. oscillator and the attenuator is attained.
- ★ Attenuator: A 3 step ladder type of attenuator is used. Each step of the attenuator is controlled by a separate attenuator control thus providing intermediate level steps.
- ★ Tubes used: 955, as R.F. Oscillator, 955 as Modulated Buffer Amplifier, 6SN7 as Audio Oscillator and Power Rectifier. The Model 660 comes complete with coaxial cable test lead and instructions



\$42⁹⁵
NET

Write Dept. RC-1 For Catalog of Complete Line.

AT YOUR
RADIO PARTS JOBBER



Manufactured and Guaranteed by
SUPERIOR INSTRUMENTS CO.
 227 Fulton Street • New York 7, N. Y.

Examine FREE



**Prentice-Hall
ELECTRONICS &
UHF LIBRARY**

Edited by
W. L. EVERITT

5 VOLUMES 1662 ILLUSTRATIONS
Pay Easy Installments If You Keep the Set

Turn to this new, up-to-date Library with complete confidence, for dependable facts on any phase of modern electronic theory and practice. These volumes, by outstanding authorities, give you thorough guidance—clearly written, logically arranged, profusely illustrated.

Electronic Fundamentals and Applications
By Prof. John D. Ryder, Univ. of Illinois

Complete, logical, easy-to-follow treatment of (a) physical principles underlying electron tubes, (b) characteristics of vacuum tubes, (c) all basic tube circuits. Includes: Electron Ballistics, Cathode-Ray Tubes, Emission of Electrons, Space Charge in Vacuum Tubes, Diode Rectifiers, Triodes, Multi-Element Tubes, Small-Signal Amplifier Circuits, Audio-Frequency Amplifiers, Radio-Frequency Amplifiers, Oscillator Circuits, Modulation Systems, Wave-Shaping Circuits, Gaseous Conduction, Gas Diodes, Gas Control Tubes and Circuits, Photoelectric Cells, Solid-State Electronics.

Electromagnetic Waves and Radiating Systems
By Prof. Edward C. Jordan, Univ. of Illinois

Covers entire field of electromagnetic engineering. Includes propagation as well as radiation and transmission. Full treatment of UHF transmission lines, wave guides, antennas, slot antennas, radiation and diffraction, ground-wave and sky-wave propagation.

Ultra High Frequency Engineering
By Thomas L. Martin, Univ. of New Mexico

Theory and technique of ALL the new fields of electronic engineering: Radar, Telemetry, Electronic Computing, Facsimile, Television, Blind landing systems, Pulse-time modulation, Ionosphere measurements . . . and the others.

Networks, Lines and Fields
By Prof. John D. Ryder, Univ. of Illinois

Network transformations and theorems, Resonance, Impedance transformation and coupled circuits, Filters, General transmission line, High-frequency line, Equations of the electromagnetic field, Radiation, Transmission and reflection of plane waves at boundaries, Guided waves between parallel planes, Wave guides.

Elements of Television Systems
By George E. Anner, New York University

Complete basic theory, plus current practice, covering: Closed TV systems, Commercial Teletexting Systems, Color TV Systems. Gives clear exposition of all phases of picture transmission, including the new technique of dot interlace.

SEND NO MONEY — EXAMINE FREE

Just mail coupon below to get complete 5-Volume Set on 10 DAYS' FREE TRIAL. If not completely satisfactory, return in ten days and owe nothing. Or keep the set and pay only \$5.35 down and \$8 a month for five months until full price of \$45.35 is paid. Decide for yourself without risk or obligation—just mail coupon to examine Library ten days free.

Prentice-Hall, Inc., Dept. M-RE-152
70 Fifth Avenue, New York 11, N. Y.

Send me the Prentice-Hall **ELECTRONICS & UHF LIBRARY** (5 Volumes) for ten days' free examination. If fully satisfied in ten days I will send you \$5.35 plus few cents postage and then \$8 a month for five months until full price of \$45.35 is paid. Or I will return the Library in ten days and owe nothing.

Name

Address

City and State

in the way the tone colors come out when various amplifiers and speaker systems are used. This is not surprising in view of the formant principle, in which any element of the system which affects the spectrum or frequency-response characteristic alters the tone quality.

Fixed bias of a sort is used in the amplifier; the speaker fields across the power supply form a voltage divider with the 50-ohm resistor at the bottom. The 19 volts appearing across this resistor is fed to the 6L6 cathodes.

A bleeder current of about 200 milliamperes flows through the speaker fields. This is roughly equivalent to the current drain of the push-pull parallel 6L6 output tubes and serves to stabilize the bias on these tubes.

As with any musical instrument, the acoustics of the installation are of paramount importance. The ideal installation includes a tone chamber for the loudspeaker units. The speakers can be faced toward one of the hard walls of the chamber so that when the sound emerges it has diffused to some extent. In addition, the multiple reflections from the walls and ceiling cause some phase shift among the tones, changing with frequency. These effects, as well as a certain amount of reverberation in the hall, are very desirable in eliminating the point-source effect of loudspeakers and the undesirable perfection of electronically generated tones. Straight speaker cabinets, when they are placed properly can also be used with good effect. The company has established a number of rules of thumb and procedures to help the installers in this respect.

When correctly installed, the Baldwin organ is a fine musical instrument—entirely aside from the ingenuity which has gone into its design. It is suited not only for church work, but has been widely accepted for concert performance in both the baroque and modern styles and is equally suitable for theater and radio music. While not superior to a really good pipe organ, it is better than most. It represents a truly happy wedding of the art of the electronic engineer and the music-maker.

—end—

**CARTOON IDEAS
NEEDED**

This magazine can use several cartoons on technical electronic, radio and television subjects per month. Ideas are invited and will be paid for at our best rates. Cartoon ideas must be original and they must be funny. It is not necessary to draw a sketch—just get the idea down so our artist can draw it. We can also use finished cartoons from skilled cartoonists. Please submit roughs.

Address: **Cartoons**


RADIO-ELECTRONICS
25 West Broadway New York 7, N. Y.

**Operate 2 sets
from 1 Antenna**

with the

**TELE Matic
ADD-A-SET**

TV Receiver Coupler

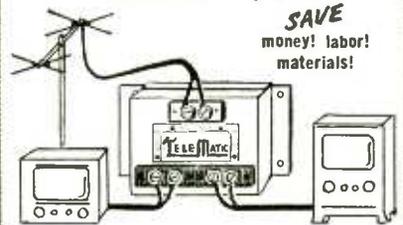

- Highest efficiency transformers used.
- Operates in fringe areas.
- High pass filter action.
- No inter-set coupling.
- Eliminates soldering, screw terminal.
- Compact, mounts inside cabinet.

Sold by leading Jobbers Everywhere
Send for FREE booklet on TV INTERFERENCE




**GET YOURS
FREE NOW!**

JUST OFF THE PRESS!
Value-Packed, JANUARY
F. Y. I. BULLETIN

Published Monthly To
Keep You Up-To-Date On
• Latest & Greatest Values!
• Newest Equipment & Designs!
WRITE TODAY! FYI Dept.

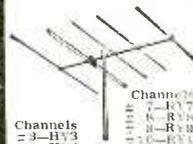**Snyder's Powerful 5 Element
YAGI TELEVISION
ARRAYS**



Channels
3—HY3
4—HY4
5—HY5
6—HY6

Channels
7—RV7
8—RV8
9—RV9
11—RV11
12—RV12
13—RV13

\$7.95

\$4.95

For Fringe & Ultra Fringe

Highly directional and closely tuned to each channel. Cuts interference and noise to a minimum. Five elements: one folded dipole, three directors and one reflector. Individual array for each channel. Specify model desired.


Tie rods for stacking 2 yagi arrays. Specify by # to band . . . 85c pr.

Address orders to Dept. RE-1 or Call MUIberry 2134

**WHOLESALE
RADIO PARTS CO., Inc.**
311 W. Baltimore St.
BALTIMORE 1, MD.

AUDIO CONSTRUCTION TIP

When constructing high-gain audio amplifiers and similar equipment, it is desirable to keep the grid of the input stage isolated from the other circuits to minimize hum and feedback. It is easy to isolate the control grid and input circuit of double-ended tubes such as the 6J7 and 6F5 but the usual construction methods do not take full advantage of the tube. The usual arrangement is shown at *a* in the illustration. The grid lead is comparatively long and must be well shielded to avoid hum and feedback. A suitable shield on the grid lead increases the input capacitance of the circuit and can cause loss of highs.

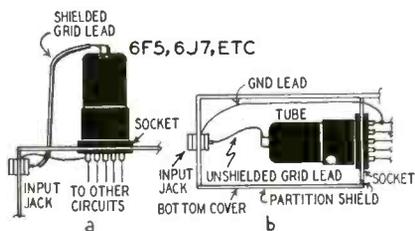

A better layout is shown at *b*. The tube is mounted under the chassis in a partition shield which effectively isolates the tube and its input circuit from the circuits on the rest of the chassis. With this arrangement the grid lead can be short and unshielded, thus decreasing stray capacitance and increasing high-frequency response.

The usual precautions in low-level amplifiers—placing the tube and shield away from the magnetic fields of power transformers and filter chokes as well as the output transformer and its leads—of course apply.

Replacing the tube is a little more difficult than when the conventional mounting is used, but since replacements are infrequent, the inconvenience is of little consequence. It is advisable to drill a few 1/4-inch holes in the chassis above the tube to allow for air circulation and heat dissipation.—*Charles Erwin Cohn*

DISTORTION IN PHONOS

Distortion which cannot be traced to the amplifier or which occurs only when using the phonograph section of a combination can often be traced to the record-player unit. In most instances, distortion is of two types.

Distortion caused by a bad crystal is usually accompanied by low output. It clears up when the defective crystal is replaced with a new one.

Distortion due to motor rumble or wow is usually more noticeable when the needle nears the center of a record—particularly on LP types. Some motors develop enough vibration to cause distortion by modulating the crystal output at the frequency of the vibration. The solution to this problem is to tighten the motor mounting or change the motor. *Do not increase needle pressure by reducing the weight of the counterweight.* This practice shortens the life of needle and records.—*Admiral Service Bulletin*



Balanced
tone

... from the flashing sunlight of Mozart to the storm of Shostakovich



PERMOFLUX ROYAL EIGHT" WITH THE FAMOUS BLUE CONE


Permoflux ROYAL EIGHT"

AUDIOPHILES the country over acclaim the clean, brilliant, life-like musical reproduction of the Permoflux Royal Eight" ... the 8" Speaker comparable to any 12"! Combined with the new Permoflux Corner Baffle, Model CB-8-M, the Royal Eight" re-creates original programs with even superior sensitivity and fidelity—every instrument in full-range tonal balance. Here's Big Speaker Performance in a small, easy-to-install frame at a sensible price. \$22.50 List, less Baffle).

See your Radio Parts Distributor or write to Permoflux today for full information about the complete Royal Blue Line of 6" to 15" Speakers and Baffle Combinations. Ask for Permoflux Catalog J-202.

"Sound in Design!... Sound in Price!"

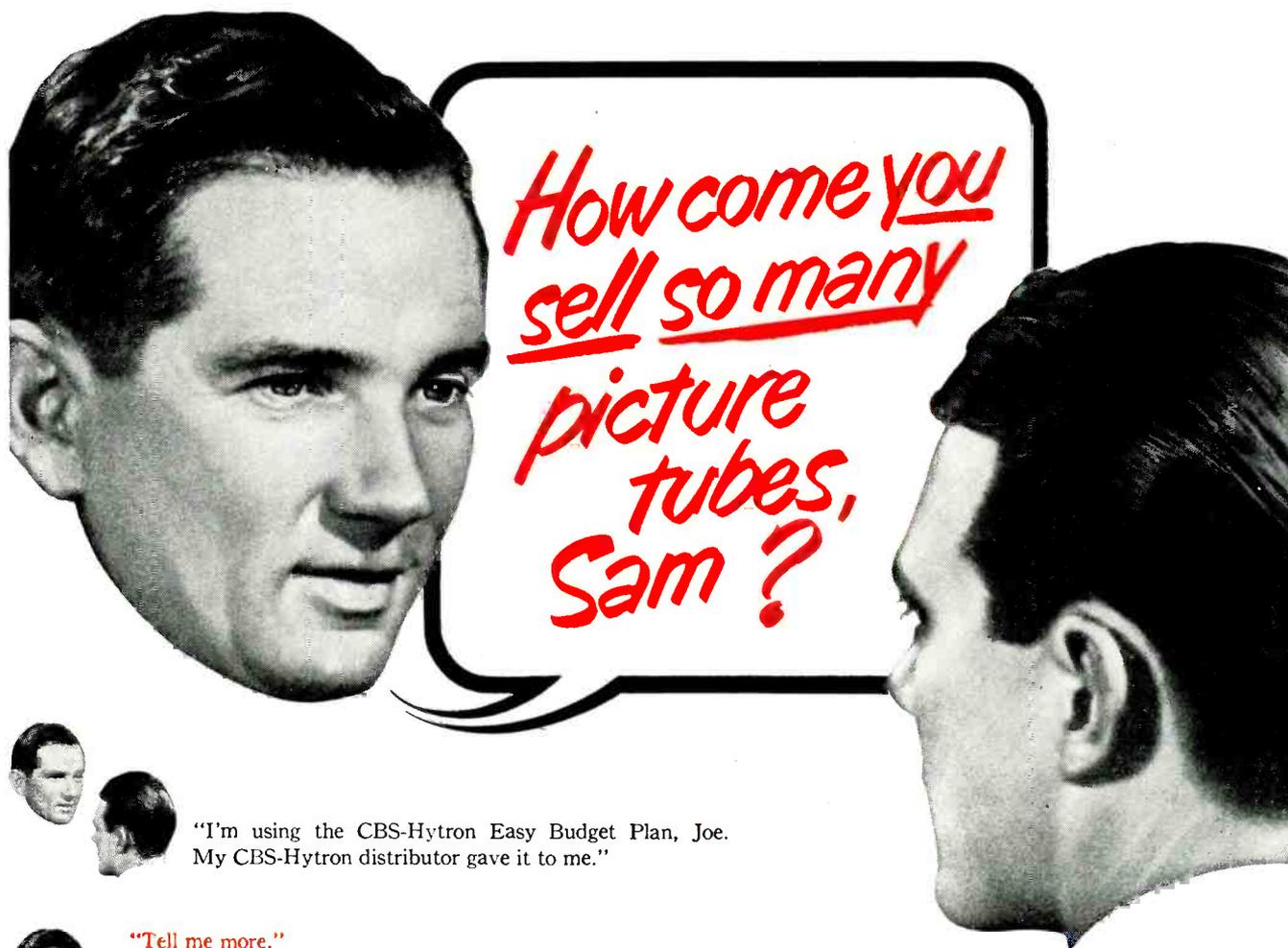PERMOFLUX CORPORATION 4912-A W. GRANE AVE., CHICAGO 39, ILL.
236 S. VERDUGO RD., GLENDALE 5, CALIF.
Canadian Licensee—Campbell Mfg. Company, Toronto, Canada



"I'm using the CBS-Hytron Easy Budget Plan, Joe. My CBS-Hytron distributor gave it to me."



"Tell me more."

"Well, CBS-Hytron's Plan helps me sell TV picture tubes and service to many a customer who just doesn't have \$50 cash. My customer now pays for the job painlessly a few dollars a month. Yet I get my cash right away."




"Fine! How does it work, Sam?"

"Simple. I introduce my customer to the finance company authorized by CBS-Hytron. The finance company does the rest . . . acts as my credit department . . . arranges all details. My customer gets his tube and I get my cash — at once."



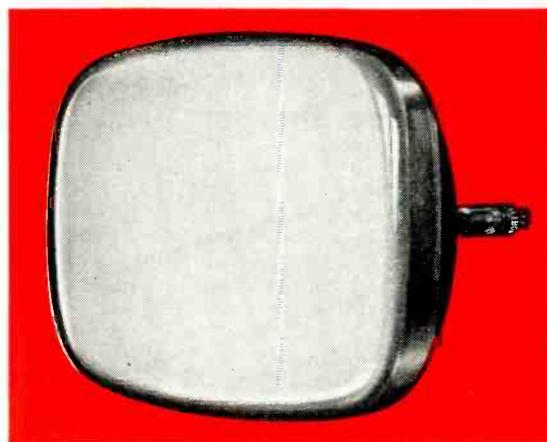"That's swell, Sam! I've sure been losing sales I shouldn't. I need that CBS-Hytron Easy Budget Plan. CBS-Hytron tubes are tops, too. Thanks for the tip. I'll see my CBS-Hytron distributor today."



SAVE THE SALE No need for you to miss a single profitable picture-tube sale . . . just because your customer does not have the cash. Get the details on this original CBS-Hytron service for you. See your CBS-Hytron jobber . . . or mail this coupon . . . today!



MAIN OFFICE: SALEM, MASSACHUSETTS

HYTRON RADIO & ELECTRONICS CO.
SALEM, MASSACHUSETTS

Please rush me details on the CBS-Hytron Easy Budget Plan.

NAME.....
(Please print)

STREET.....

CITY.....STATE.....

LOOK—NO NOISE!

Boosts the signal . . .
not local lead-in noise!

Gives higher signal-to-
overall-noise ratio!

Exclusive broadband
circuit gives uniformly
high all-channel gain!

Eliminates
effect of
external
interference

**Tenna-Top
TV BOOSTER**

AUTOMATIC SELF-TUNING

SINGLE TWIN-LEAD LINE*
CARRIES POWER UP—
AND SIGNAL DOWN

Pictures are Sharper, Brighter! Sound is Clearer!

You can *see* and *hear* the difference when you hook up the TENNA-TOP. Because it is mounted at the antenna ahead of the lead-in...it amplifies only the wanted TV signals, not any local noise interference produced by automobile ignition systems, neon signs, diathermy, or other external noise picked up by the lead-in. You have the further advantage of E-V low-noise circuit. All this guarantees the best possible results with any TV set anywhere...even in toughest fringe areas or in all noisy locations. The TENNA-TOP is completely automatic. Turns "On" or "Off" with the TV receiver switch. It is easy to install, highly stable, trouble-free.

Model 3010 Tenna-Top TV Booster. List Price . . . \$89.50



Tuneo-Matic TV BOOSTER

Famous E-V broadband booster—proved in thousands of installations! Uniform high gain—low noise circuit. Automatic self-tuning for all channels. Easily concealed.

Model 3000, 4-stage, List \$59.50
Model 3002, 2-stage, List \$39.50

Electro-Voice

TV BOOSTERS • MICROPHONES • HI-FI SPEAKERS • PHONO-PICKUPS

Send for Free Bulletin

Electro-Voice, Inc., Dept. E-152
421 Carroll St., Buchanan, Michigan
Send Free Bulletin No. 163

Name _____ (PLEASE PRINT)

Address _____

City _____ Zone _____ State _____

Serviceman Installer Dealer TV Fan

*Patent Pending

ating conditions, but under full volume becomes seriously overloaded. Two tubes should be used for dependable results. Since considerable heat is developed by these tubes, good steatite sockets should be used to avoid breakdown. We tried phenolic sockets and found that they would not stand up under the heat and vibration.

The amplifier was built on a chassis 7 x 9 x 2 inches. The completed amplifier, without cabinet, is just over 7½ inches high. All parts should be laid out on the chassis and all mounting holes marked and drilled before any wiring is attempted, since the underchassis parts occupy most of the available space and can easily be damaged by later drilling. It will be advantageous to lay out the 6AU6 and the 6J6 tube sockets with just enough space between them so that the plate-to-grid coupling capacitors can be wired in place and will lie flat against the underside of the chassis with very short leads to the socket.

The 6AU6 tubes are mounted along the left front of the chassis and the 6J6 tubes are placed behind them. Enough space should be left for the master gain controls and their respective input coupling capacitors, between the front of the chassis and the 6AU6 sockets.

The two 6AQ5 tubes are mounted in the rear right corner, between the output transformer and the filter choke. All the power-supply components—except the filter choke—are mounted on the right front side of the chassis and covered with a shield can. In addition, the leads which will run from the power transformer to the vibrator and the rectifier-tube plates on the underside of the chassis should be enclosed with a small metal shield. It will save time if these cans are made up and the necessary holes for mounting them drilled before any parts are installed.

Dimensions of these shields are not critical. Probably—if parts are carefully placed—they can be made of available discarded shield cans originally used for other purposes.

Wiring the amplifier

A piece of solid, bare No. 14 copper wire should be spot-soldered to the underside of the chassis in the form of a U, starting directly under the center of the power transformer and proceeding along the front to the opposite side; then to the rear edge of the chassis; then back to a point directly under the output transformer. All ground-return leads are brought to the nearest point on this wire; except that all leads from the power-supply components should be fastened to the wire where it is placed under the power transformer.

Tube sockets and master gain controls can be mounted on the chassis first and all filament wiring completed; then the shielded leads from the master gain controls installed. We used ordinary pushback hookup wire loosely inserted in woven shielding removed from phonograph pickup wire. The metal backs of the gain controls should


RADIO-ELECTRONICS for

TRIPLETT

Load-Chek

introduces
Servicing
 by
Power
Consumption

MODEL 660

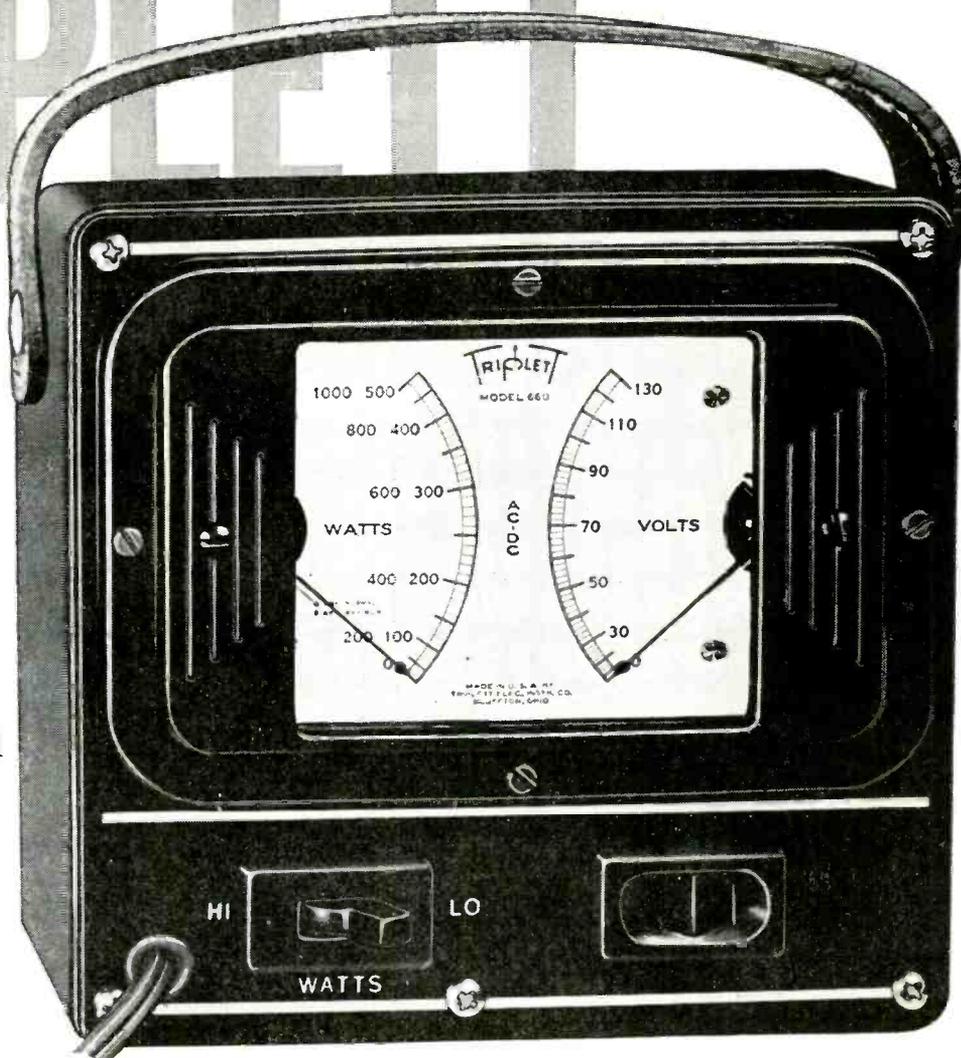

LOAD-CHEK for the first time makes it possible for every technician to utilize what is perhaps the simplest and quickest of all service methods—Servicing by Power Consumption Measurements.

Power consumption measurement has long been proved by auto-radio servicemen as a rapid method of localizing troubles in auto radios. But Triplet's new **LOAD-CHEK** is the first Wattmeter to be produced at moderate cost, and with the proper ranges, to bring this short-cut method within the reach of every radio and TV service man.

Basis of the **LOAD-CHEK** method is the tag or label on every radio and TV chassis which shows the normal power consumption. The following examples are only two of many time-saving uses of this new instrument.

LOCATING A SHORT—The chassis tag may show a normal consumption of 225 Watts. Simply plug the power cord of the chassis into **LOAD-CHEK** (there are no loose ends to connect or be in the way). Note the reading—which should be possibly 350 Watts. By removing the

rectifier tube you can determine at once which side of the tube the short is on. With a soldering iron and long-nosed pliers you can check through the chassis, locate and correct the trouble without having to lay down tools or to check with lead wires!

REPLACING BURNED OUT RESISTORS—With the chassis to be repaired plugged into a **LOAD-CHEK MODEL 660**, note the wattage reading with the burned out resistor circuit open. Now replace the resistor. Should the increase in watts be greater than that of the resistor rating being installed, it indicates that an extra load has caused the trouble which has not been cleared.

LOAD-CHEK is made-to-order for the busy service man and can help stop costly "come back" repair jobs. It's a profit-maker because it's a Time-Saver. And at its moderate cost **LOAD-CHEK** can be standard equipment on every service bench. By all means, inspect this versatile instrument at your distributor and place your order, for under present conditions we must fill all orders on a basis of "First Come, First Served."

SEE MODEL 660 LOAD-CHEK AT YOUR DISTRIBUTOR'S

FOR THE MAN WHO TAKES PRIDE IN HIS WORK

Triplet

TRIPLETT ELECTRICAL INSTRUMENT COMPANY - BLUFFTON OHIO U S A

THERE'S Fun AND Profit IN Magnetic Recording



A complete guide
to better
recording for
higher fidelity
reproduction

by S. J. Begun
300 pages, 6 x 9,
130 illustrations

Price only \$5

A HOW-TO-DO-IT BOOK FOR REAL RESULTS!

Beginning with the history and theory of the art, this fascinating book, MAGNETIC RECORDING, brings you accurate data on every detail of modern magnetic recording equipment and how to use it for best results. From home entertainment to motion pictures, broadcasting, professional and amateur radio to special applications such as secret communications (speech scrambling) you get the latest, most comprehensive data on all phases of recording by magnetic methods.

ALL ABOUT FUNDAMENTALS COMPONENTS and EQUIPMENT

Whether you do recording as a hobby or as a business, this great book will prove invaluable. Included are clear explanations of acoustic and magnetic factors, reproducing heads, drive mechanisms, recording media and the methods of recording, reproduction and erasing.

Standard equipment is fully discussed along with instruments needed to evaluate recording performance. Subjects covered include:

- | | |
|---|--|
| 1—History of Magnetic Recording | 6—Magnetic Recording Equipment |
| 2—Acoustic Factors | 7—Applications of Magnetic Recording |
| 3—Magnetism | 8—Instrumentation and Recording Measurements |
| 4—Theory of Magnetic Recording | 9—The Magnetic Phonograph |
| 5—Components of a Magnetic Recording System | 10—General Glossary |

READ IT 10 DAYS . . . at our risk!

Dept. RE-12, RINEHART BOOKS, Inc.,
Technical Division,
232 Madison Ave., New York 16, N. Y.

Send MAGNETIC RECORDING for 10-DAY FREE EXAMINATION. If book is O.K. I will then promptly remit \$5.00 in full payment. If not, I will return book postpaid in good condition and owe you nothing.

Name.....

Address.....

City, Zone, State.....

Employers' Name & Address.....

Price outside U.S.A. \$5.50—cash only. Money back in 10 days if you return book.

be grounded directly to the chassis, together with one end of each shielding. Most controls have removable backs held in place with small metal tabs. One of these tabs on each control should be bent out with the blade of a knife until it contacts the chassis, and secured in place with a small spot of solder.

Next, capacitors and resistors should be installed. Careful layout of these parts will result in easy wiring, in spite of the close quarters around tube sockets. It will help if alternate socket prongs are spread outward on the 6AU6 and the 6J6 sockets, to allow more room for the soldering iron. Solder must be used sparingly on all tube-socket prongs. Rosin-core solder and a small hot iron—or transformer-type soldering gun—should be employed. Make all connections mechanically tight before applying any solder, and depend on the solder *only* for a tight electrical connection. This can best be done by looping the wire through the hole in the socket prong and closing the loop with needle-nose pliers before applying the solder.

Wire the plate-to-grid coupling capacitors in place with short leads and so that they lie flat against the chassis. The B-supply resistors for the 6J6's and the screen resistor of the 6AQ5's may be mounted on a small bakelite strip near the second 6J6 tube socket to save space and for ease in wiring.

Input coupling capacitors for inputs 1 and 2 are installed at the microphone input connectors and wired to the 6AU6 No. 1 grids with shielded flexible leads. The grid resistors in these circuits are connected from the socket pins directly to the grounding copper bus with *very short* leads at the grid end of the resistors. The phonograph input circuit is made up similarly, with the input resistors and capacitor mounted at the input jack and a shielded lead to the tube socket with the grid resistor direct to ground from the grid pin of the socket.

The three r.f. chokes in the power supply should be made of No. 14 d.c.c. solid wire. Each choke consists of 24 turns, close-wound in one layer on a piece of 3/8-inch dowel. After winding, the dowel is removed and the choke is tied with strong thread to hold its shape. These chokes are mounted by their own leads.

Transformer and vibrator

The vibrator power transformer should be one capable of delivering 300 volts at 100 ma each side of center-tap. The transformer we selected was a Stanecor P-6131. It is designed to operate with a vibrator whose reed frequency is 115 cycles. We selected a Cornell-Dubilier CS15 vibrator to use with it. If other transformers that will deliver the above mentioned voltage and current are available, they can be used successfully, but be careful not to pick a transformer designed to be used at a higher frequency than the vibrator will deliver, or that will otherwise mismatch the units. Since considerably more current is needed than that furnished by

the average auto radio power pack. Synchronous vibrators should be avoided because of the higher "hash" level in the output. Battery polarity becomes a problem when using sync vibrators, too.

In general, a transformer that meets the above specifications may be used with an appropriate nonsync vibrator with no trouble if the frequency of the transformer and the vibrator are matched, and are 115 cycles or more. Some vibrators and transformers now on the market are designed for frequencies as high as 180 cycles.

After all possible underchassis wiring has been completed, mount and wire the components on top of the chassis. The r.f. choke connected to the vibrator transformer center-tap and the two capacitors between its terminal and ground are wired to mounting strips placed on top of the power transformer. Take care that they are so placed that they will not interfere with the shield that will be installed over them. The resistor across the vibrator transformer primary should be wired directly across the vibrator socket contacts, and then the vibrator transformer secondary capacitor should be jumpered across the 6X4 sockets with leads as short as possible (the leads can be used to jumper each socket's No. 1 and No. 6 pins).

When all wiring is completed, double-check for accuracy and tightness, and place a drop of bright-colored paint on each soldered connection. This paint will often be an aid in detecting a later developed poor connection (caused by vibration) since the paint will flake and fall away if any looseness develops. It also serves as a check.

The remote control unit (Fig. 2-a) consists of three volume controls mounted compactly in a small box suitably arranged for mounting on the steering column or under the instrument panel of the car. The box we used measured 2 3/4 x 5 x 3/4 inches. It is bolted under the car instrument panel, just to the left of center, within easy reach of the driver. The leads from the remote-control unit consist of a shielded 7-wire cable terminating in a 7-prong plug which can readily be inserted in the amplifier's remote-control socket. After assembly the control box was given two coats of black crackle finish and a dial plate and knobs were installed.


If desired, the remote control may be omitted, and a dummy plug can be made up as shown at *b* in Fig. 2, and inserted in the amplifier socket. The master gain controls will then be used to control volume level. Such a plug is also handy for checking the amplifier when removed from the car for servicing.

After all wiring has been completed, install tubes and shield covers. Before the amplifier is placed in the cabinet, however, it is advisable to drill the cabinet for the mounting bolts and also lay out and drill similar holes for mounting the equipment in the car. Any paint around these holes should be scraped away to make a good electrical

(Continued on page 94)

New Arrival

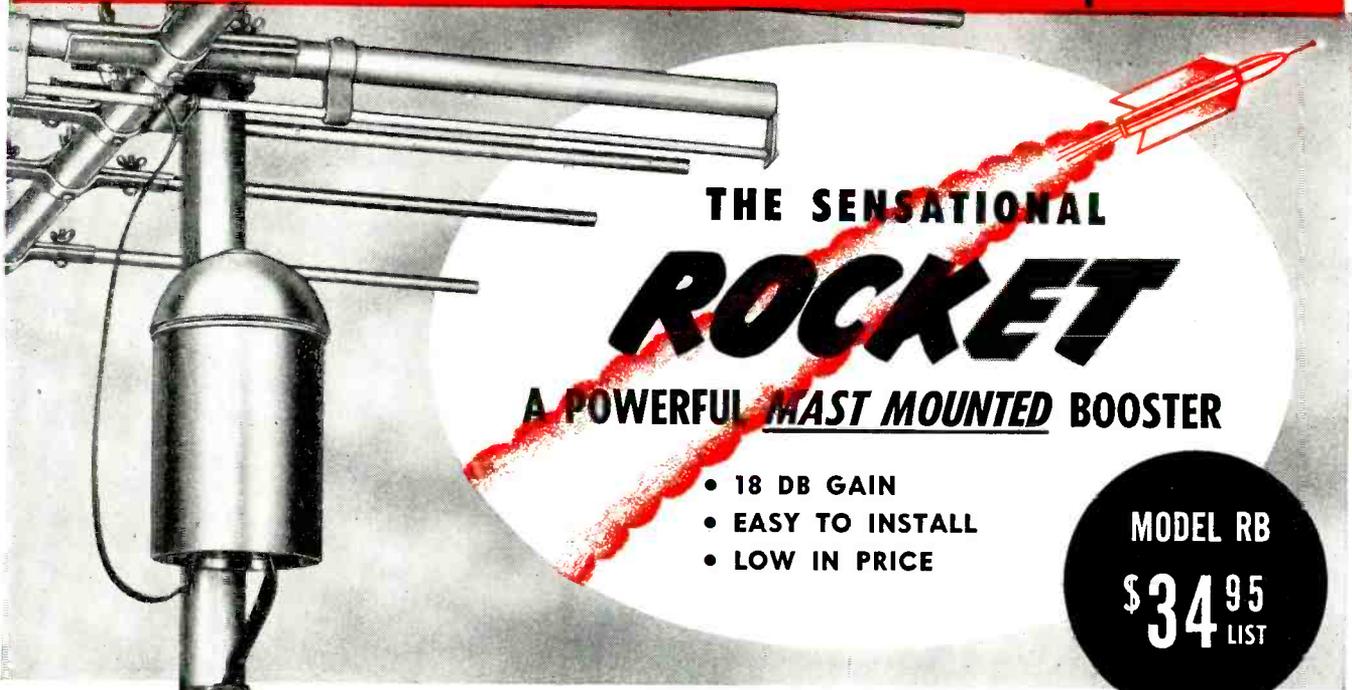**GIVES SINGLE CHANNEL RECEPTION
A BIG BOOST IN PICTURE QUALITY
AT GREATER DISTANCES**



THE SENSATIONAL **ROCKET**

A POWERFUL MAST MOUNTED BOOSTER

- 18 DB GAIN
- EASY TO INSTALL
- LOW IN PRICE

MODEL RB
\$34⁹⁵
LIST

**Pre-amplifies Signal at Antenna Height — Prior to Line Loss
— Where Most Favorable Signal-to-Noise Ratio Exists**



The control unit is quickly attached to back of TV receiver and provides exact voltage needed for any length of transmission line.

The Rocket Booster is utterly new by every standard of comparison and is destined to further revolutionize single channel television reception at far greater distances. Research and laboratory tests have long proved that the best point to boost a TV signal is at the antenna — prior to line losses — where the most favorable signal-to-noise ratio exists — not at the TV receiver after the transmission line has picked up noise and interference. It remained, however, for VEE-D-X engineers to perfect this mast mounted booster that is high in performance — easy to install — low in price — and using only the single standard 300 ohm transmission line. The Rocket Booster has two components — 1) the booster itself which is mounted directly on the mast below the antenna and 2) the control unit. The Rocket is extremely powerful, delivering an 18 db gain with full 5 megacycle band width. It is factory pre-set for peak performance on any desired channel and once installed needs no further adjustments. For complete information on the sensational new Rocket Booster see your distributor or write direct.

Another Great Product by

VEE-D-X

THE LaPOINTE-PLASCOMOLD CORPORATION, WINDSOR LOCKS, CONNECTICUT

SYLVANIA NATIONAL ADVERTISING

**5 Stars Endorse
Your Business in these
Smashing Magazine
ads**

Jane Russell says:

"For the finest radio and television service, I advise my friends to depend on the man who displays the Sylvania sign. Believe me, he's a past master at keeping sets in splendid shape."



RADIO TELEVISION SERVICE
SYLVANIA RADIO TUBES

SYLVANIA
RADIO AND TELEVISION PICTURE TUBES

Sylvania Electric Products Inc., 1740 Broadway, New York 19, N. Y.

June Haver says:

"I've made a wonderful discovery. When I have trouble with my radios or TV set, I simply call the man who displays the Sylvania service sign. He gives me prompt, courteous and competent repair service. Try him and see if you don't agree."



RADIO TELEVISION SERVICE
SYLVANIA RADIO TUBES

SYLVANIA
RADIO AND TELEVISION PICTURE TUBES

Sylvania Electric Products Inc., 1740 Broadway, New York 19, N. Y.

says Leo Durocher:

"Laraine and I don't fool around with just any radio and TV service. We like an expert who knows how to call things right. That's why we call the man who shows the Sylvania sign."



RADIO TELEVISION SERVICE
SYLVANIA RADIO TUBES

SYLVANIA
RADIO AND TELEVISION PICTURE TUBES

Sylvania Electric Products Inc., 1740 Broadway, New York 19, N. Y.

says Ann Blyth

"I've found a man who knows all the answers—at least to radio and TV troubles. He's the man who displays the Sylvania radio and television service sign. No matter I'm in Hollywood or in New York, I look for this sign for dependable service."



RADIO TELEVISION SERVICE
SYLVANIA RADIO TUBES

SYLVANIA
RADIO AND TELEVISION PICTURE TUBES

Sylvania Electric Products Inc., 1740 Broadway, New York 19, N. Y.


Every one of your prospects will see and read these appealing ads in famous national magazines. These ads recommend your service . . . when you display the Sylvania Service Emblem, shown above. So, make sure these emblems are on your doors, your windows, and trucks. They're FREE from your Sylvania Tube Distributor NOW!

These ads will appear in the 4 famous magazines your prospects read most!



Will Sell Your RADIO-TV SERVICE in '52

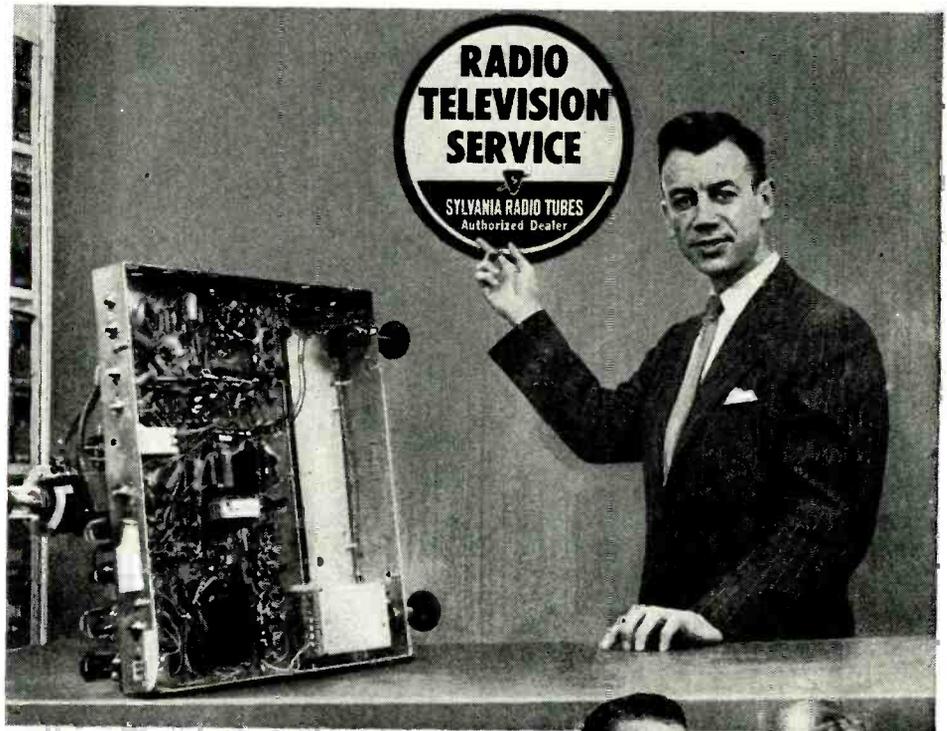Nation-wide weekly TV Show "BEAT THE CLOCK" will sell your service to every TV set owner



You're an "expert, reliable service-man who does a tough job well," Bill Shipley, crack CBS-TV announcer, tells your prospects. And, he adds: "Always look for that Sylvania Service Emblem." That's how the hard-hitting, full-minute commercials on Sylvania's CBS-TV show, "Beat the Clock," put Bill Shipley, Roxanne, and Bud Collyer on your sales staff.

Roxanne and Bud Collyer are seen weekly over CBS-TV in 35 cities... selling your service... when you display the Sylvania Service Emblem.



Make this great national ad campaign pay off in your store

Mail the coupon below for FREE, full-color folder giving complete details about Sylvania's compelling Spring Service Dealer Advertising Program. It contains everything to identify you unmistakably as the dealer advertised in Sylvania's magazine and TV advertising. If you want more business, you can't afford to miss it. But, time's awastin'... get that coupon in the mail NOW!



SYLVANIA

RADIO TUBES; TELEVISION PICTURE TUBES; ELECTRONIC PRODUCTS; ELECTRONIC TEST EQUIPMENT; FLUORESCENT TUBES, FIXTURES, SIGN TUBING, WIRING DEVICES; LIGHT BULBS; PHOTOLAMPS; TELEVISION SETS

Sylvania Electric Products Inc.
Dept. R-2701, Emporium, Pa.


Please send me full details about Sylvania's powerful business-building campaign for Service Dealers.

Name _____

Street _____

City _____ Zone _____ State _____

AVOID RESISTOR BREAKDOWNS

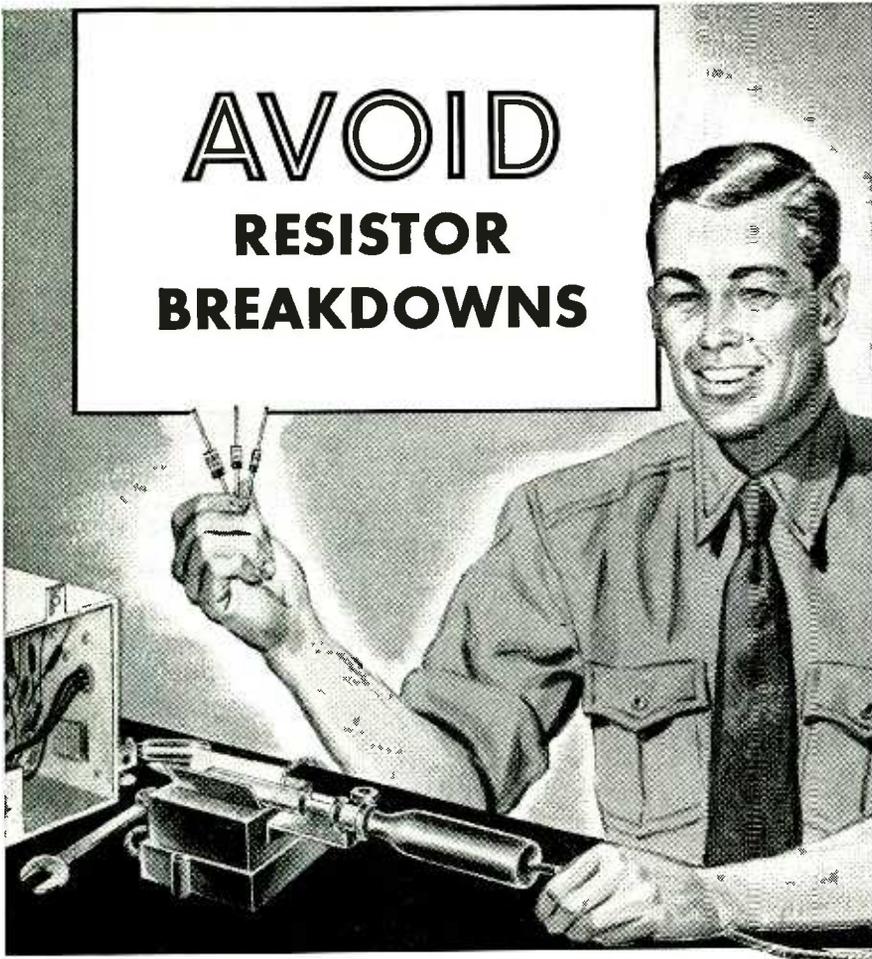

OHMITE Little Devil Resistors Provide EXTRA MARGIN of SAFETY

Although they are tiny in size, Ohmite Little Devil molded composition resistors have unusual ruggedness, stability, and current-carrying capacity. For example, they are rated at 70C instead of the usual 40C. They meet all test requirements of JAN-R-11, including salt water immersion and high humidity tests without wax impregnation. In addition to conventional color coding, the resistance value and wattage are clearly marked on each unit.

Available in 1/2, 1, and 2-watt sizes with $\pm 5\%$ or $\pm 10\%$ tolerance, in standard RTMA values—10 ohms to 22 megohms. The 1-watt size, $\pm 10\%$ tolerance, comes in values as low as 2.7 ohms.



Available Only
From Your
Distributor

OHMITE MANUFACTURING CO.
4894 Flournoy St., Chicago 44, Ill.

Be Right with **OHMITE**

RHEOSTATS • RESISTORS • TAP SWITCHES

connection between the car and the case.

Test and operation

The amplifier can be easily checked before installation in the car. One terminal of a 6-volt storage battery should be connected to the hot lead of the amplifier and the other connected to the case. Polarity is not important. Any good high-impedance crystal or dynamic microphone will serve and should be connected to the microphone input connector of the stage under test. A speaker rated at 15 watts or more should be connected to the amplifier output. With the master gain control about halfway on, fairly high output should be obtained when the remote control is turned all the way up. With similar control settings, each input should give substantially the same output.

In use, the master gain controls on the amplifier can be left on and each channel can be individually regulated by the remote control unit. The remote gain controls of those inputs which are

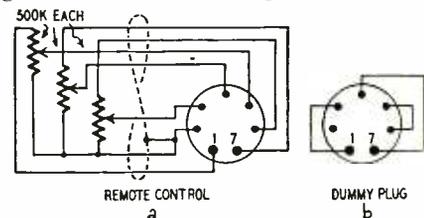


Fig. 2-a—Detail of remote-control unit.
Fig. 2-b—Remote socket dummy plug.

not being used should be kept turned off. The controls are available, however, to allow any combination of mixing or fading of the various inputs.

No audio amplifier should ever be operated without adequate speaker loading. This one is no exception. If operated without a suitable output load, high audio voltages in the final-amplifier plate circuit will cause insulation breakdown in the output transformer, in the final-amplifier tube sockets, or in the power-supply components. For that reason, always check the speaker connections before operating the amplifier. Be sure they are tight.

If more than one speaker is used, connect the speakers in parallel and properly phase for maximum output. Most of the 25-watt driver units available today have 15-ohm voice coils. Two such units will match the 8-ohm winding of the amplifier's output when paralleled. The amplifier will provide sufficient drive for two speakers to be heard for distances up to a half mile or more if straight or re-entrant horns are employed.

Materials for amplifier

Resistors: 1—220, 1—10,000, 3—33,000, 1—47,000, 3—100,000, 4—470,000 ohms, 1—3.3 megohms, 1/2 watt; 2—1,000, 1—1,800, 2—2,700, 3—47,000, 3—100,000, 3—270,000 ohms, 1 watt; 1—10,000 ohms, 2 watts; 1—200, 1—5,000 ohms, 5 watts; 1—0.25-megohm, 6—0.5 megohm volume controls.

Capacitors: (Paper) 1—0.1, 1—0.15, 1—0.1, 2—0.5 μ f, 200 volts; 1—0.02, 1—0.02, 6—0.05, 2—0.1 μ f, 400 volts; 1—0.006 μ f, 1,600 volts. (Mico) 3—0.005 μ f. (Electrolytic) 1—20 μ f, 25 volts; 3—10 μ f, 50 volts; 4—10 μ f, 450 volts.


Miscellaneous: 1—Stancor A3311 output transformer; 1—Stancor P-6131 vibrator transformer (see text); 1—Stancor C-2305 or equivalent 5-henry, 100-ma filter choke; 1—vibrator, C-D CS15 (see text); 1—fuse, 6-volt, 14-ampere type; 1—switch, s.p.s.t., 20-ampere type; r.f. chokes, self-wound (see text); chassis, case, miscellaneous hardware, wire, etc.

—end—

RADIO-ELECTRONICS for

LINE TRANSFORMERS

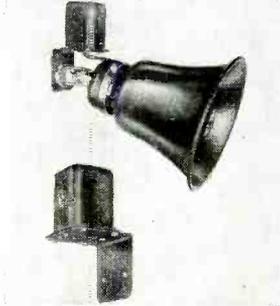Atlas Sound Corp., 1449 39th St., Brooklyn 18, N. Y., has developed two new weatherproof line-matching transformers designed to match their dual-projector and paging and talk-back speakers to either constant-voltage (70-volt line) or constant-impedance systems. Transformer tops are marked so as to eliminate complex computations. The units are rated at 12 watts and have 4- and 8-ohm secondaries.




The model T-11 has a 2,000-ohm primary tapped at 1,500, 1,000, and 500 ohms. The T-12 has a 45-ohm primary. The frequency response of these units is shaped to insure efficient operation over the range required for public address work.

These transformers are mounted in heavy steel housings which prevent mechanical and atmospheric damage. The mounting brackets are integrated with the speaker mounting brackets so that no extra fastenings are required.

TV DEFLECTION YOKES

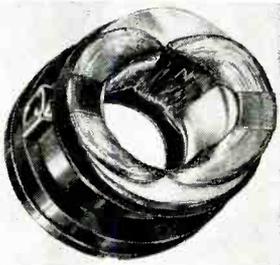Standard Transformer Corp., 3580 Elston Ave., Chicago 18, Ill., has recently added the type DY-8 and DY-9 deflection yokes to their line of TV replacement components. Both units have cosine-type windings and ferrite cores




All specifications given on these pages are from manufacturers' data.

and are designed for 70-degree deflection. The inductance of the horizontal coil is 8.5 and 13.5 mh for the DY-8 and DY-9, respectively. Vertical coil inductance is 50 mh in each.

ALL-CHANNEL TV ANTENNA


The Brach Mfg. Corp., 200 Central Ave., Newark, N. J., announces its new Air Special all-channel TV antenna. The length and forward tilt of the elements is designed to provide maximum forward gain with a single-bar reflector. The reflector is adjustable for peaking on channels 2 through 6. The single-bay unit is the model TA-462 and the stacked model shown is the TA-464. Both antennas match 300-ohm lines.

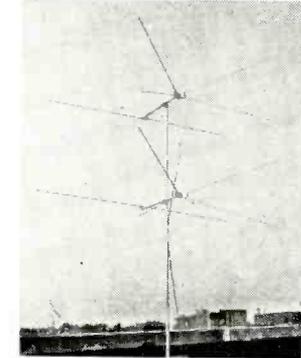

PHONO CARTRIDGE

The Astatic Corp., Conneaut, Ohio, announces the new L-12-U dual-voltage phonograph cartridge which is designed as a replacement for more than 125 different standard 78-r.p.m. cartridges. The L-12-U is supplied with a capacitor-harness fitted over its output terminals.

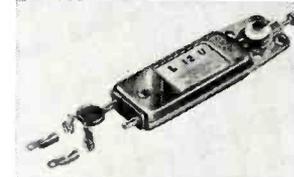
Removing the harness raises the output from a low of 1.2 volts (at 1,000 cycles) to a high of 4 volts. The range of the L-12-U is to 5,000 cycles. The cartridge weighs 19 grams; minimum needle pressure is 1 ounce.



Seletron SELENIUM RECTIFIERS

May be up your alley, too!

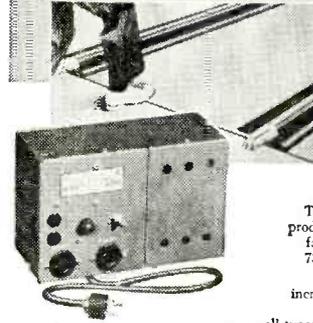... AS THEY ARE FOR THE BRUNSWICK-BALKE-COLLENDER COMPANY



Illustrated above is the "Tel-E-Foul" control box. When the bowler oversteps the foul line the electronic beam emits an impulse causing a light to flash above the alley. A 75 MA SELETRON miniature is built into the control box on each bowling lane.

The new "Tel-E-Foul," photo-electric Foul Indicator produced by The Brunswick-Balke-Collender Company, famous manufacturer of bowling equipment, includes 75 MA SELETRON miniatures in its electronic circuits.

SELETRON Selenium Rectifiers are the choice of an increasing number of manufacturers in diversified fields because they are so thoroughly dependable under all types of grueling conditions. SELETRON is available in the miniature sizes required for radio, TV and other electronic circuits, all the way up to heavy duty power stacks used in a wide range of industrial applications.

Whenever you meet up with a power conversion problem, no doubt SELETRON engineers can be of substantial assistance in recommending the right rectifier for your needs. Write us today!




SELETRON DIVISION
RADIO RECEPTOR COMPANY, INC.

Sales Dept.: 251 W. 19th St., New York 11, N. Y. • Factory: 84 N. 9th St., Brooklyn 11, N. Y.

RADIO-ELECTRONICS is paying highest rates for good articles on television and AM servicing. Stories must be authentic and must either give new information or have an original slant

Largest Selling Booster

AT ANY PRICE !

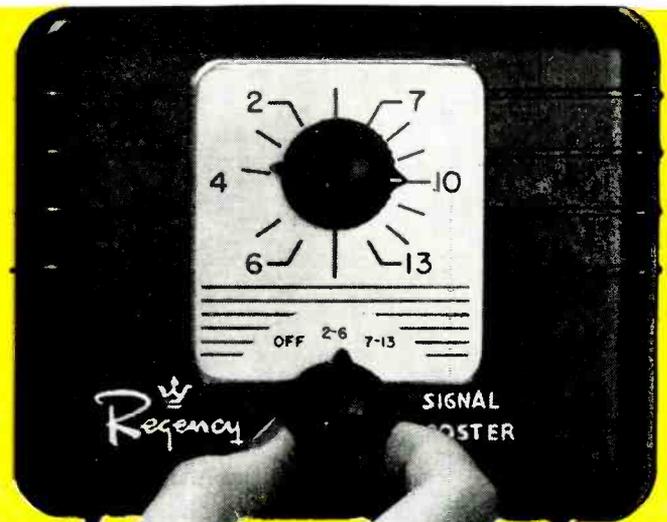

Regency

Be Sure

OF YOUR ANTENNA INSTALLATION FROM ROOF TOP TO TV SET...

AMPHENOL INLINE ANTENNA

A broadband antenna with a single, strong forward lobe that permits receiving the strongest, clearest TV signal with the least amount of objectionable interference or reflected images. Its clean design and rugged construction of half-hard aluminum is neither too hard and brittle nor too soft and bendable. It will repeatedly stand winds of 70 miles per hour and ice loadings of one-half inch without bending or breaking.

AMPHENOL "AUTO-DIAL" ROTATOR

This rotator permits you to literally probe the sky with your antenna for the best TV signal. So accurate is the rotator that the best position for each channel can be logged and returned to at any time by a simple setting of the "Auto-Dial." The Amphenol "Auto-Dial" Rotator is sturdily constructed and will support a two bay stacked array.

AMPHENOL LIGHTNING ARRESTOR

Guard against fire hazard caused by lightning by installing an Amphenol Lightning Arrestor on your TV outdoor antenna. This type of arrestor is recommended by the National Electric Code. The Amphenol Lightning Arrestor is approved by Underwriters' Laboratories. Installation is easy, the arrestor is small and compact and there is no cutting or splicing of transmission line necessary.




send 10¢

for this 20 page book containing complete information on all the factors determining . . .

- . . . Better TV Picture Quality
- . . . Secure Antenna Installation


AMPHENOL

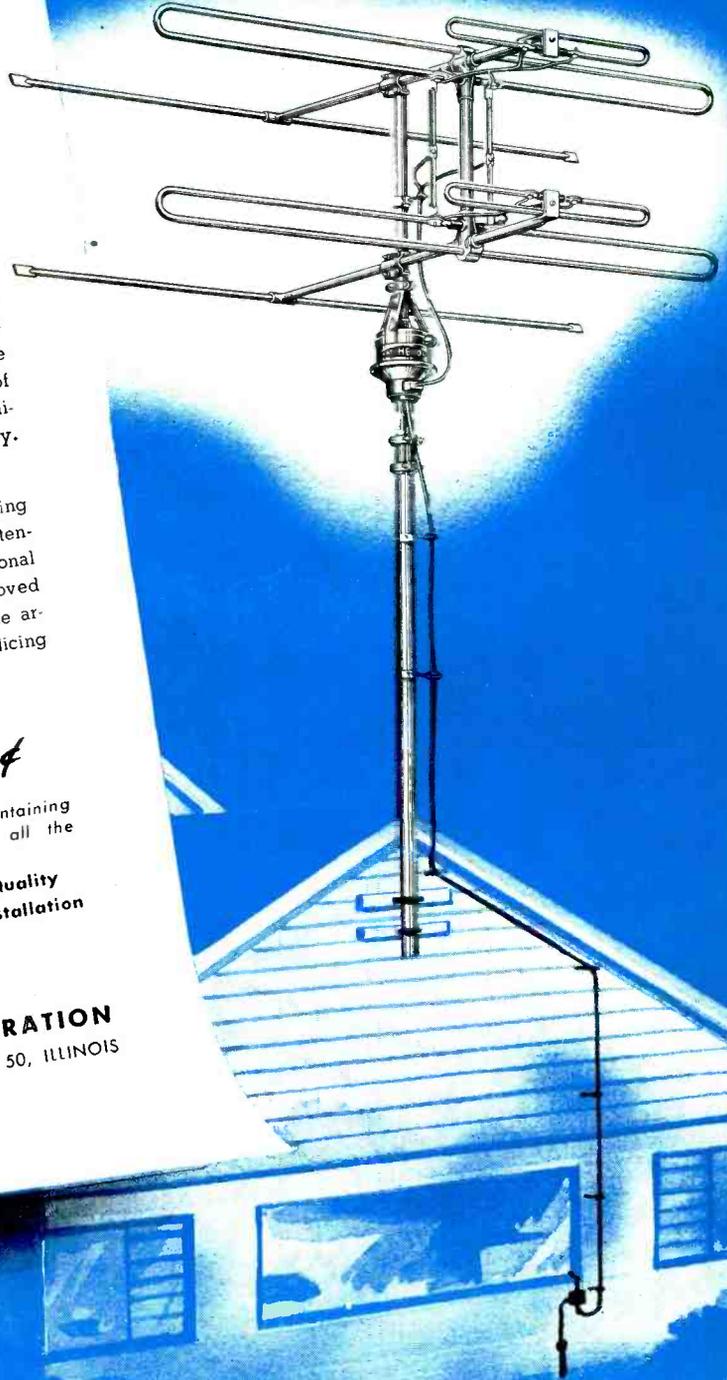AMERICAN PHENOLIC CORPORATION
1830 SOUTH 54TH AVENUE • CHICAGO 50, ILLINOIS



TV CRYSTAL OSCILLATOR

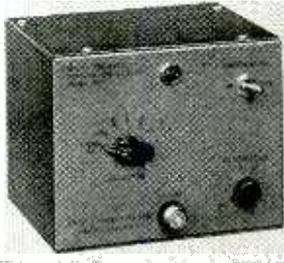Crest Laboratories, Whitehall Bldg., Far Rockaway, L. I., N. Y., announces the new model 50 multi-frequency, high-output crystal-controlled signal generator for spot frequency alignment of TV and military receivers. Compact in size, it provides five spot frequencies in the 4.5 to 50 mc range. Maximum output is 1 volt from the



72-ohm terminated probe. It uses five harmonic-type crystals which are available as accessories. Internal 400-cycle modulation is available. The unit incorporates a transformer-type power supply which operates from 117-volt, 60-cycle lines.

HEATHKIT V.T.V.M.

The Heath Co., Benton Harbor 20, Mich., announces its new model V-5 v.t.v.m. featuring a new cabinet design which is smaller and more professional in appearance than the earlier model. The 4 1/2-inch, 200- μ a meter has a shatterproof plastic face and a two-color scale. The instrument reads a.c. and d.c. with full scale ranges of 3, 10, 30, 100, 300, and 1,000 volts; resistance from 0.1 to 1 billion ohms; and decibels from minus 20 to plus 15. Controls include d.c. polarity reversing switch and zero centering.


The kit comes complete with all parts including tubes, meter, transformer, test leads, cabinet, etc. Construction

manual includes step-by-step assembly instructions, pictorials, schematic, and circuit description.



C-R TUBE REACTIVATOR

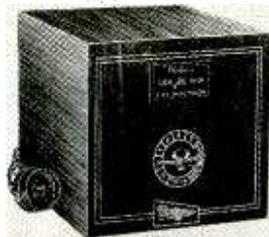Transvision Inc., 460 North Ave., New Rochelle, N. Y., announces the release of its new C-R tube reactivator. It is a line-operated instrument which can be used in the customer's home without removing the picture tube from the TV set. The reactivator will not work on tubes having shorted elements, open heaters, or broken glass.



KIT OR WIRED V.T.V.M.

Precise Development Corp., 999 Long Beach Road, Oceanside, L. I., N. Y., is producing its new model 907 vacuum-tube voltmeter as a kit and a wired model. The instrument features a 7 1/2-inch easy-to-read meter. It measures d.c. and a.c. with full-scale ranges of 5, 25, 250, 500, and 1,000 volts, decibels from minus 20 to plus 55, and resistances from 0 to 1 billion ohms in five ranges. When measuring d.c. voltages, polarity can be reversed simply by throwing the function switch.

High-voltage and r.f. probes—available as accessories—are used to increase the frequency range to over 250 mc and the voltage range to over 30,000 volts.

The model 907 is available in two cabinet styles which make it possible for the prospective owner to select the style which fits more readily into his tool bag or into available space in the test panel above the workbench. One is assembled in a case 16 inches wide, 8 inches high, and 5 inches deep. The style shown in the photo is in a case 8 inches wide, 16 inches high, and

and is delivered complete with test leads, wire, and batteries.

VACUUM TUBE VOLTMETER

Electronic Measurements Corp., 280 Lafayette St., New York 12, N.Y., announces the model 106 v.t.v.m., the latest addition to the EMC line of electrical testing equipment. Designed



for field alignment of radio and television sets, the 106 is completely electronic on all functions and ranges and has five a.c.-d.c. and ohms ranges. The instrument includes a special zero-center scale and centering control which are useful in aligning AFC, and FM discriminator circuits. Featuring a 1 1/2-volt range for both a.c.-d.c. volts, this instrument is housed in a molded bakelite case that measures 7 1/4 x 5 1/4 x 2 3/8 inches with a net weight of three pounds.

NEW TV ANTENNAS

The Walter L. Schott Co., 3225 Exposition Pl., Los Angeles 18, Cal., introduces its new model M antenna which is constructed largely of chromate-coated magnesium which is one-third lighter than aluminum and almost as strong as steel. The antenna has a director which minimizes ghosts and improves gain on the high channels.

—end—

FREE Yours For Examining This New 6-Volume **TV-RADIO LIBRARY** **7 DAYS FREE**

BOOK OF TV-RADIO PATTERNS & DIAGRAMS

150 Radio Patterns and Radio-TV Diagrams Explained

1951 EDITION

Now! Get this sensational new TV-Radio servicing book, "150 PICTURE PATTERNS & RADIO-TV DIAGRAMS EXPLAINED," absolutely FREE! Shows actual TV picture tube patterns and wave forms as well as Radio and TV set diagrams. Clearly explains how to use them to analyze and service sets faster. If you act now, you can get this book FREE, just for asking to examine Coyne's 6-volume TV-RADIO LIBRARY on 7 days FREE TRIAL!

More Earning Power For You With The COYNE LIBRARY!

You'll get into the big money faster in TELEVISION-RADIO if you know where to find the answer to servicing problems. Coyne's great new 6-volume library gives you all the answers—quickly! For basic "know-how" that is easy to understand, you'll find everything you want in volumes 1 to 5 which contain over 5000 practical facts and data. They cover every step from principles to installing, servicing, trouble-shooting and aligning all types of radio and TV sets. So up-to-date it includes COLOR TV and UHF, adapters and converters.

And then, for speedy on-the-job use, you get volume 6—the famous Coyne TELEVISION CYCLOPEDIA. It answers today's television problems on servicing, alignment, installation and others; PLUS tomorrow's problems on COLOR TV and

UHF. In easy-to-find ABC order, cross indexed. Use this 6 volume TV-RADIO LIBRARY free for 7 days; get the valuable Servicing Book ABSOLUTELY FREE!

ACT NOW . . . OFFER LIMITED!

Fill out and mail coupon for 6-volume library on 7 days free trial. We'll include book of TV-Radio Patterns & Diagrams. If you keep the set, pay \$3 in 7 days and \$3 per month until \$23.00 plus postage is paid. (Cash price \$22.) Or you can return the library at our expense in 7 days and owe nothing. YOU BE THE JUDGE. Either way, the book of TV-Radio Patterns is yours FREE to keep! Offer is limited. Act NOW!

SEND NO MONEY—MAIL COUPON NOW!

COYNE ELECTRICAL & TELEVISION-RADIO SCHOOL, Dept. 12-T1
500 S. Pauline St., Chicago 12, Ill.

YES! Send 6-volume TV-RADIO LIBRARY for 7 days FREE TRIAL per your offer. Include TV-RADIO PATTERNS & DIAGRAM BOOK as my FREE GIFT.

Name..... Age.....

Address.....


City..... Zone..... State.....

Where Employed.....

() Check here if you want library sent COD. You pay postman \$22 plus COD postage on delivery. 7-day money-back guarantee.

COYNE ELECTRICAL & TELEVISION-RADIO SCHOOL
500 S. Pauline St., Dept. 12-T1, Chicago 12, Ill.

The Manhattan

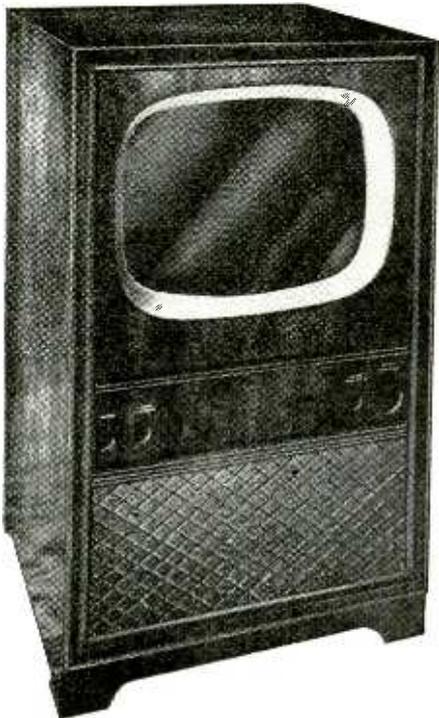

CUSTOM-BUILT CABINET For #630 AND ALL OTHER TV SETS

From Factory—To You
The MANHATTAN has everything
STYLE ... QUALITY ... PRICE

STYLED—to blend with any furniture setting, it's a best seller.

QUALITY—constructed of genuine mahogany or walnut, handrubbed to a fine piano finish.

LOW PRICE—made possible by our huge commitments and a special deal to ship directly from factory to you

THE MANHATTAN—takes any TV set. The knob-panel and shelf are either, drilled for a #630 chassis, or left blank for any other TV set. The picture tube cutout is any size you order (12½" to 24") and the mask and safety glass are included.

EVERYTHING NECESSARY—for an easy, perfect installation is included—assembling instructions, picture tube mounting brackets, hardware, backboard, and as a finishing touch we even include a backup for recessing the picture tube neck.


EACH CABINET—is carefully packed in an air cushioned carton & shipped F.O.B. factory, N.Y.
\$59.37 cab., size H-41", W-25", D-24", wt. 56 lbs.
\$86.22 cab., size H-46", W-27", D-24", wt. 78 lbs.

MANHATTAN to fit any size CRT **\$59.37**
12½", 14", 16", 17", 19" or 20"

Manhattan also available for the **\$86.22**
24" picture tube

Blonde 10% extra

#630 SUPER DELUXE 31-TUBE TV CHASSIS

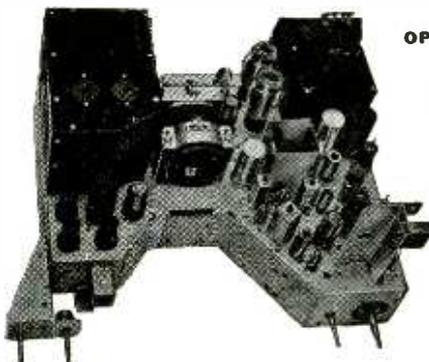

OPERATES ALL 16" TO 24" PICTURE TUBES

Engineered in strict adherence to the genuine RCA #630, plus added features ★★★★★

NOTHING BETTER AT ANY PRICE!

- Standard Turret Tuner (Cascade)
- Original 630 Synch. Chain for Stability
- 16.5 KV for Clarity and Brilliance
- Peak Sensitivity for Fringe Areas
- 4 Megacycle Bandwidth for Definition
- Larger Power Trans. & Voltage Doubler
- Fast Action Pulse Keyed AGC
- Large Concert-tone 12" PM Speaker

KNOWN MFR... LICENSED BY RCA Complete ready to play with all tubes, hardware, knobs, etc. (less CRT) **\$167.97**

FINEST STANDARD GUARANTEED PICTURE TUBES

Most desirable sizes. Choice of DUMONT 6-mos. guaranty or SHELDON blue label 1-yr. guaranty.

17" Rect. **\$34.63**

20" Rect. **\$49.74**

24" Round **\$79.49**

SPECIAL COMBINATION OFFERS

CABINET, CHASSIS & 17" CRT* (featured above) **\$235.78**

CABINET, CHASSIS & 20" CRT* (featured above) **249.37**

CABINET, CHASSIS & 24" CRT* (featured above) **298.24**

* CRT is the abbreviation for picture tube

DOLLAR FOR DOLLAR WE BRING YOU YOUR BEST BUYS IN TV!

WE ARE HEADQUARTERS FOR #630 TELEVISION CHASSIS, KITS & PARTS . . . All Items are STANDARD BRANDS . . . All Prices Are WHOLESALE (FEDERAL TAXES PAID) . . . Do Not Be Misled By Any Lower Offers!

BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N. Y. TELEPHONE COrtlandt 7-2359

GOOD NEWS For #630 TV BUILDERS

Just Released . . . A New Edition
OF THE

#630 TV BUILDERS INSTRUCTION PACKAGE

Complete from the authentic RCA #630 STANDARD (10" to 12½") 29-tube TV RECEIVER, to the present #630 DELUXE (16" to 24") 31-tube TV RECEIVER.

LIFE SIZE—Everything from chassis pan, to part, to tube, to wire is life-size, you just can't make mistakes.

NO MORE FUMBLING—The diagrams, layouts, and easy to follow step by step instructions are all neatly arranged on 25" x 38" charts eliminating the old fashioned method of looking and craning from booklet to diagram.

Popular priced at only **\$2.49**

#630 TELEVISION PARTS

RCA FRONT END TUNER, compl. w/tubes.	\$22.49
STANDARD TURRET TUNER, com. w/tubes.	22.49
ESCUTCHEON PLATE, for either tuner.	.69
COMPLETE SET OF KNOBS, incl. decals.	1.34
POWER TRANSFORMER, 295ma.	2.49
VERTICAL OUTPUT TRANS. 204T6.	9.97
VERTICAL BLOCKING TRANS. 204T2.	2.69
HORIZONTAL OUTPUT TRANS. 211T3.	1.32
HORIZONTAL OUTPUT TRANS. 211T5.	2.98
FOCUS COIL, 247 ohms.	3.98
FOCUS COIL, 470 ohms.	2.29
DEFLECTION YOKE, 60°	202D2. 3.42
DEFLECTION YOKE, 70°	201D1. 2.97
HORIZONTAL DISCRIM. TRANS. 206D1.	3.98
FILTER CHOKE, 62 ohms.	208T8. 1.49
WIDTH CONTROL COIL.	201R1. 1.47
WIDTH CONTROL COIL, keyed AGC.	.44
HORIZONTAL LINEARITY COIL, 201R3.	.79
ION TRAP BEAM BENDER, (single) 203D1.	.39
ION TRAP BEAM BENDER, (double) 203D3.	.79
AUDIO OUTPUT TRANSFORMER (6K6)	.98
HV RECTIFIER, SOCKET ASSEMBLY, single.	.69
HV RECTIFIER, SOCKET ASSEMBLY, double	.79
PUNCHED CHASSIS PAN, cadmium plated	1.37
630KIT, screws, nuts, rivets, washers.	.39
TV 6' LINE CORD, with both plugs.	1.69
CATHODE RAY TUBE SOCKET, 18" leads.	.29
VAL PM SPEAKER, 5"x7"	.39
8" PM SPEAKER, heavy alnico #5 magnet.	2.49
12" PM SPEAKER, heavy alnico #5 magnet.	3.97
	6.94

#630 PARTS - COMPLETE SETS

VIDEO AND I.F. KIT, 19 items.	7.84
ELECTROLYTIC CONDENSER KIT, 6 Cond.	7.37
TUBULAR CONDENSER KIT, 37 condensers.	4.28
CERAMIC CONDENSER KIT, 28 condensers.	3.37
MICA CONDENSER KIT, 11 condensers.	1.38
CARBON RESISTOR KIT, 107 resistors.	6.98
WIREWOUND RESISTOR KIT, 4 resistors.	2.31
OCTAL WAFER SOCKET KIT, 13 sockets.	.72
MIN. WAFER SOCKET KIT, 10 sockets.	.63
MIN. MOLDED SOCKET KIT, 2 sockets.	.22
BRACKET AND SHIELD KIT, 18 items.	8.63
TERMINAL STRIP KIT, 9 controls.	.59
VARIABLE CONTROL KIT, 29 tubes.	5.83
COMPLETE SET OF TUBES, 29 tubes.	30.31

#630 STANDARD TV KIT

COMPLETE SET OF PARTS
for the FAMOUS ORIGINAL RCA #630
29-TUBE 10" TO 12½" CHASSIS

Complete with all tubes, hardware and instructions, (less CRT & wire) **\$119.74**

#630 SUPER DELUXE TV KIT

COMPLETE SET OF PARTS
for the 31-TUBE 16" to 24" CHASSIS


Complete with all tubes, hardware and instructions. (less CRT & wire) **\$146.49**

(Same as chassis featured to left)



● THAT CAN'T BE DUPLICATED

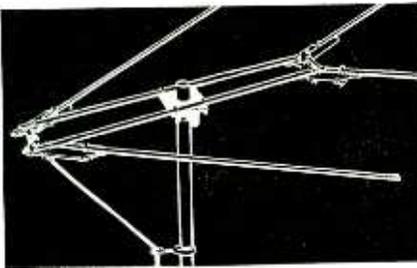Workshop Associates' pioneering leadership individualizes all products to a superlative degree that defies duplication. Laboratory-tested engineering confirmed by field technicians everywhere. Like fingerprints, you can always tell the difference.



the WORKSHOP DUBL-VEE TV ANTENNA

Developed and Patented by Workshop

Widely imitated . . . never equalled . . . preferred everywhere. Rugged, durable, extra strength to withstand the toughest weather conditions . . . assures clearer pictures . . . higher gain . . . high signal strength . . . no ghosts. Write for catalog.

Specialists in High Frequency Electronics



**THE
WORKSHOP
ASSOCIATES**


Division of the Gabriel Co.
135 Crescent Road
Needham Heights 94, Mass.

There is one inconvenience: it takes two switches to cover all the ranges. This is more than made up for by the performance of the unit. Thanks to the mechanical rigidity, the size of the frequency-determining tank, the low temperature rise due to excluding the power supply from the case, and the use of the very stable cathode-coupled circuit, the stability obtained is remarkable. Even the highest range which has the poorest L-C ratio is astonishingly stable. The lower ranges will maintain frequency with a variation of less than 50 cycles for hours from a cold start. The reset accuracy is also excellent. The dial is not calibrated, and tuning is facilitated by calibrated charts. However, when the errors of plotting, reading, and setting are combined, it is still possible to reset the oscillator to within extremely close limits.

Incidentally, a similar tuning unit would make an excellent v.f.o. for ham transmitters. Using the Clapp circuit with the three capacitors in series, a range of from 1500 to 2000 kc over 800 dial divisions with very high stability and reset accuracy would be provided. The remainder of the case could be used for frequency-multiplying stages. We are at present planning a unit along this line.

It will be noted that the v.f.o. is modulated in the second grid circuit by the variable audio oscillator. It will be noted, also, that the r.f. output is taken from this same grid and out of the same jack as the audio. This is a desirable feature approaching the electron-coupled-oscillator type of circuit in the isolation it provides. In actual operation the frequency varies only very slightly when the oscillator is loaded.

Rapid signal tracing is aided by using the same output jack for both audio and v.f.o. output. For initial trouble-shooting the audio oscillator is set to 1,000 cycles and the v.f.o. to the i.f. of the receiver on test. The output probe is then systematically moved from the audio amplifier toward the front end of the receiver. No changes in the setting of the oscillators are needed. The a.f. responds only to the a.f. component of the signal; the i.f. will respond to the modulated r.f. The receiver is then tuned to the second or third harmonic of the intermediate frequency. The probe is advanced toward the antenna

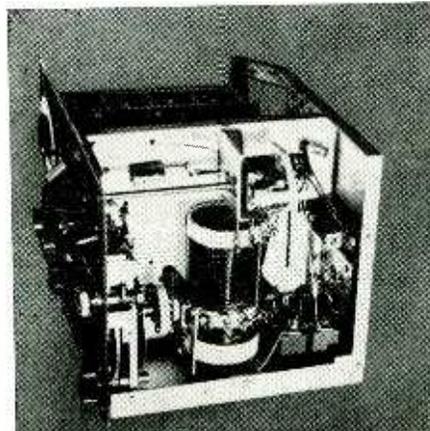

The VFO section is sturdily constructed.

until the signal stops or is greatly reduced. This pins down the stage in which trouble exists.

For rapid and accurate alignment of all-wave receivers on the short-wave bands the quickly switched crystal oscillator with a choice of correct test frequencies cannot be surpassed. The middle section of this signal generator consists of a simple crystal oscillator accommodating 11 crystals in the 100- to 10,000-kc range. Any clean crystal will oscillate satisfactorily in this circuit. It uses a 9001 in a Pierce oscillator with the output from the plate but the feedback from the screen. A 2-pole 2-position switch changes components to provide good oscillation at both low and high frequencies.

The output of the crystal oscillator goes to a binding post on the panel. For ease in operation we use a short telescoping antenna in this binding post. This allows using the generator without any direct connection to the receiver under test and offers a simple means of attenuation. The antenna radiates enough signal to be picked up by any receiver with a foot or so of antenna. With the antenna extended to its full length of about 1 foot the radiated signal is about R9 plus 20 db on most communication receivers. Retracted to its shortest length (6 inches) the radiation gives an R9 signal. With the oscillator antenna removed and the radiation confined entirely to the small binding post, the input strength at the receiver approximates 5 microvolts, which is just right in aligning for weak signal levels.

The crystal oscillator in this specific instrument was built around the switch and chassis assembly of the surplus CGQ crystal calibrator. The switch and assembly was simply removed from the old CGQ case and mounted in the new case. However, any 11-point, 2-pole switch and a number of different crystal sockets can be wired up to duplicate this arrangement. A slotted-shaft 50- μ f midget variable capacitor, with the slot accessible from the panel, makes possible a slight change in the frequency of the crystals so that a 500-kc crystal, for instance, can be set to exact frequency by zero-beating with WWV.

For our purpose we use a 455- and a 500-kc crystal in the low position. The 475-kc crystal is not usually used for actual alignment but rather to spot the correct frequency for the v.f.o. The 500-kc crystal is used for dial calibration and for checking tracking on the short-wave band.

A group of high-frequency crystals provides test signals for aligning the r.f. end of all-wave receivers. Crystals cut to around 2000, 3000, 3500 and 5000 kc will provide enough check points, using fundamental and harmonics, to align upper and lower ends of the short-wave bands.

The third harmonic of a 3570-kc crystal is used for alignment of 10.7 FM i.f.'s; 3545- and 3595-kc crystals, also using the third harmonic, for markers at the extreme ends of the linear portion of the S-shaped curve of the de-

RADIO-ELECTRONICS for

Rauland—the Original

LOW FOCUS VOLTAGE ELECTROSTATIC TUBE

**Perfected in Rauland Electronics Laboratories,
this tube that gives edge-to-edge sharpness of focus
without coils and magnets is proved and ready
as the materials pinch becomes painful**

BETTER in all ways! Gives better over-all focus—hair-line sharpness from edge-to-edge—with **NO** critical materials for focusing . . . and **STAYS SHARP** under considerable variation in line voltages.

REQUIRES NO re-engineering of present television chassis . . . **NO** added high voltage focus circuit . . . **NO** added receiver tubes . . . **NO** additional components except an inexpensive potentiometer or resistor.

FOCUSES by using D.C. voltage already available in the receiver.

ELIMINATES focusing coils and magnets . . . saves critically scarce copper and cobalt.

• • •

This new Rauland development is now available in substantial quantities in 17 and 20 inch rectangular tubes. For further information, address . . .

THE RAULAND CORPORATION



Perfection Through Research

4245 N. KNOX AVENUE • CHICAGO 41, ILLINOIS



Sensational TV BARGAINS!

Rocket YAGI


5 ELEMENT TV ANTENNA Excellent Pictures in Fringe Areas

HIGH GAIN. Clearer, sharper, steadier pictures. **PERFECT PICTURES IN FRINGE AREAS.** Minimum interference from ghosts and noise due to a directive pattern. Five elements include one folded dipole, three directors, and one reflector. Supplied less mast. **MATCHES 300 OHMS IMPEDANCE.** Molded insulator provides additional strength. Exclusive design mast clamp prevents antenna tumbling or cutting under any conditions. **STURDY, TROUBLE-FREE CONSTRUCTION.** No return calls. No broken elements. Stands the test of severest weather. Elements of extra heavy aluminum-clamped top and bottom. **QUICK RIG.** Completely pre-assembled. Just swing elements into line and tighten wing nuts. Simple to install or remove. **easy.** Available for any channel, high or low band.

Channels 2 and 3 **\$7.95** each
Channels 4, 5, and 6 **\$6.95** each
Channels 7 to 13 **\$3.95** each

EACH CHANNEL requires a DIFFERENT Yagi. When ordering specify exact channel number desired.
SOLD ONLY BY MAIL BY NATIONAL ELECTRONICS

Rocket DIRECTRONIC MOTORLESS TV ANTENNA

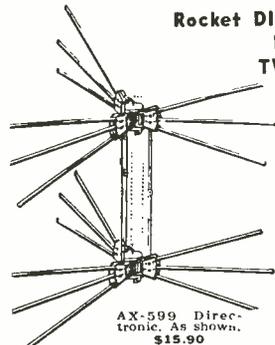

360°
Electrically Switched Beam
● No Motors
● No Roof
● Orientation
● No Electric
● No Ghosts


The Directronic 18 element, 360° antenna is the finest for ultrawide or metropolitan reception. The HI-PAC molded insulator is a material of extreme tensile strength not affected by weather or temperature, either electrically. Included in the AX-599 "Service-men's Array" are:

- 18 hi-tensile aluminum alloy elements
- 1 set of connecting studs (3)
- Universal U Clamps for masts to 1 1/2"
- Directronic Beam Selector
- 75 feet of Tri-X Cable
- 5 stacked array per carton

AX-56 Directronic, 6 element Single \$ 9.05
AX-56B Directronic, 12 element Stacked..... 14.25
AX-59 Directronic, 9 element Single..... 9.95
All above antenna prices include Tri-X Cable and Switch.

SOLD ONLY BY MAIL BY NATIONAL ELECTRONICS

Rocket ALL CHANNEL CONICALS

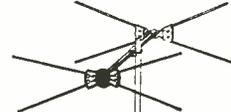

This sturdy, all-aluminum constructed TV antenna is designed for broad-band reception on all TV channels, plus FM. High Gain, 4 to 1 front to back ratio. All channels 2-13. Uni Directional. Maximum signal to noise ratio. For use with 72-150-300 ohm lines. Low reception angle. Complete with all hardware—less mast.

Single Bay Stacked Array with Rods \$3.75 each
The Rods..... \$8.20 each
SOLD ONLY BY MAIL BY NATIONAL ELECTRONICS

- 1 1/2" O.D. Mast Steel (Dualcoated) 5' crimped \$1.05
- Mast Steel (Dualcoated) 10' \$1.95
- Mast Steel (Zinc plated) 10' \$1.59
- Mast Connectors for 1 1/2" O.D. Mast—10' long..... 49c
- 3 Conductor Motor Wire 3c ft.
- 4 Conductor Motor Wire 4c ft.
- Peak Roof Saddles (Will take up to 1 1/2" O.D.) \$1.49
- Twin Lead 300 Ohm—7/6 Mil—Solid 2 1/2c ft.
- Twin Lead 300 Ohm—2 55/60 Mil—7/28 Stranded 3c ft.
- Double Stacking Assembly for stacking \$1.70 set
- 2-X Arrays \$6.95
- Aluminum Guy Line 7/18—Stranded 300 ft. coil..... \$4.95
- Arrestors (TV-Lighting) \$1.19
- Chimney Mount—Complete with Straps \$1.19
- Coxs—72 Ohm 6 1/2c ft.
- Guy Wire—Galvanized—4 strand 20 1/2c ft.
- Guy Wire—Galvanized—5 strand 20 3/4c ft.
- Guy Wire—Galvanized—11 strand 20 1 1/2c ft.
- Boosters—Anchor—101-75 \$22.50
- Tec—S-505 \$2.75 C
- Stand-off Screw Insulators—3" for 300 ohm..... \$5.50 C
- Stand-off Screw Insulators 7" for 300 Ohm..... \$8.50 C
- Strab Clamp Stand-off Insulators—3"..... \$2.75 C

PRICES SUBJECT TO CHANGE WITHOUT NOTICE
ALL PRICES F.O.B. CLEVELAND, OHIO

Do not remit more than complete purchase price. Pay shipping charges on receipt of goods. 25% Deposit on C.O.D. orders, please. Money Back guarantee

For Faster Service, Address Desk RE-1

National Electronics
OF CLEVELAND
THE HOUSE OF TV VALUES
Delco Building • Cleveland 3, Ohio

detector output when aligning the discriminator and ratio detectors. These crystal values (obtainable from surplus) are useful for 80-meter ham operation, and may be purchased for far less than crystals cut to the high frequencies. An 8800-kc crystal is used for FM r.f. alignment, providing check points at 88, 96.8, and 105.6 mc. Since my area has not been blessed with television coverage yet, no crystals are listed for TV service. However, the circuit could be copied for supplying television test frequencies.

The crystal oscillator is very slightly modulated by the audio oscillator through the common plate-supply coupling. The modulation is just sufficient to make the signal recognizable when tuning a receiver.

Audio Oscillator

The audio oscillator is a simple version of the R-C or Wien bridge type of oscillator. It uses only two 6C4 tubes. The tuning capacitor is a 3-gang 15-500-µuf capacitor obtained from surplus. Only two gangs are used. If care is taken in wiring to keep the stray capacitance low, it is possible to cover a 10-to-1 frequency ratio. A 2-gang 365-µuf capacity could be used, although it will probably not yield a 10-to-1 ratio. If the attained ratio is only 8 to 1 or so, it should still be satisfactory for test purposes.

We did not use precision resistors but selected matched pairs of carbon resistors with a Wheatstone bridge. We found that out of any 10 resistors of a given value, it was possible to find one pair which balanced to about 1% and produced the desired frequency to within 5%. Resistor balance is more important—in order to produce constant amplitude and good waveform—than exact value. Precision resistors will insure the multiplication of the scale exactly in the four ranges. However, the carbon resistors provide a multiplication exact enough for practical use. We felt that waveform and constant amplitude were more important than exact calibration.

A third section of the range switch cuts in separate feedback controls for the high and low frequencies, in order to stabilize output over the whole range. With a single feedback ratio it is difficult to maintain constant output at the extreme ends of the range. By providing separate controls for the two extreme ranges, and one for the mid-ranges, we attained an output which was constant to plus 1 db. This variation occurs in the upper one-third of each range and is constant throughout the four ranges. With due allowance, the oscillator can be used as a substantially constant-amplitude oscillator.

A series feedback control, which can be cut in and out by means of a toggle switch, provides for a choice of either sine-wave or square-wave output. With the switch open, adjust the 5,000-ohm potentiometer across it till a good square wave is produced. Check with a scope. All feedback controls are mounted on the chassis and are used only for initial calibration. Only the


main tuning dial, the range switch, and the output attenuator are on the panel. For TV the wave-shaper toggle switch may also be mounted on the panel. Feedback is adjusted by observing the waveform of the oscillator on an oscilloscope. The range switch is turned to one of the mid-frequencies and the capacitor is opened all the way. The mid-range feedback control is adjusted to give the best possible sine-wave shape. The switch is turned to the low-est range and the capacitor is turned to the maximum capacitance position. Now the low-range feedback control is adjusted to give good waveform and amplitude equal to that at mid-range. The capacitor is turned to minimum and the trimmer on its upper section adjusted to give good waveform and proper output with the lowest possible capacitance. Next the range switch is turned to the highest range and the feedback control of this range is adjusted to give an output as nearly equal to the other ranges as possible.

The calibration of the Wien bridge oscillator has been covered in other articles of this magazine.*

A simpler method using a frequency test record and feeding both the record and the oscillator output into a common audio amplifier and loudspeaker allows quick calibration. The easiest range to calibrate is the 100- to 1,000-cycle range. It will be found that as the variable oscillator approaches the test-record frequency a beat note will be set up in the ear. It is possible to zero-beat the variable oscillator roughly to the record frequency. Once this range is calibrated, the other ranges will be multiples of it, if the resistors are accurately selected. This method of calibration is not as accurate as the oscilloscopic one, but will be adequate for test purposes. Exact frequency is very seldom important in audio servicing. It is the over-all response which is important; and an oscillator which is calibrated plus or minus 10% will often do as well as one more accurately calibrated.

The output is taken from the cathode of the second tube. This produces very little loading of the oscillator and makes it possible to use shielded output cable with no signal attenuation. The maxi-

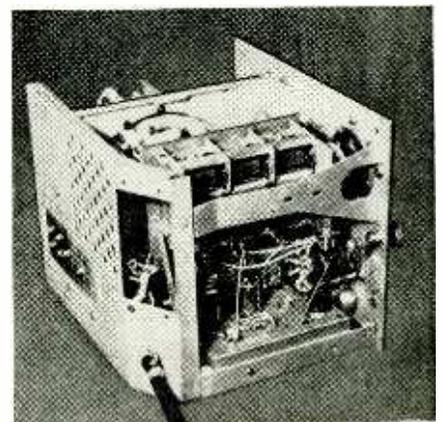*"Calibrating Audio Oscillators," by R. D. Henry, RADIO-ELECTRONICS, October, 1948.



Ganged capacitor is on a Masonite board.

Tel-a-Ray's

BIG


FOUR

of TV reception

For television that's
bright and clear
Wherever you are . . .
far or near




Good reception up to 200 miles or more!

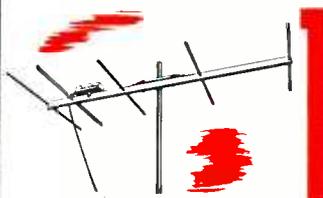


Models T and TD Antennas . . . famous for providing clear, stable, interference-free reception at almost unbelievable distances. With the Pre-Amplifier, they give up to an amazing 300 times gain over dipole. Rugged, weatherproof construction.

Signal amplification without noise!

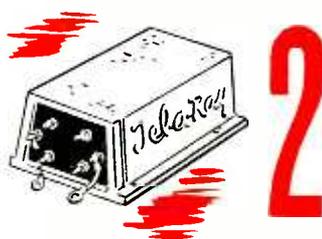


The unique, research-perfected Pre-Amplifier . . . the only device of its kind . . . an antenna- or mast-mounted installation that dramatically multiplies the signal gain while keeping noise at a minimum. Eliminates snow and makes signals strong and stable. Sold as a weather-sealed unit and guaranteed against weather damage.

Middle-distance champions!

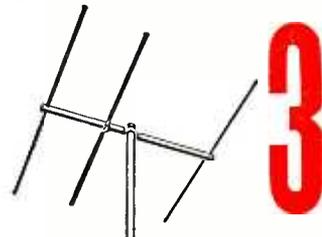

Models R and RD Antennas . . . designed to give the finest TV reception to the outer service areas at low cost . . . America's champion middle-distance performers. Same quality construction features as Models T and TD.

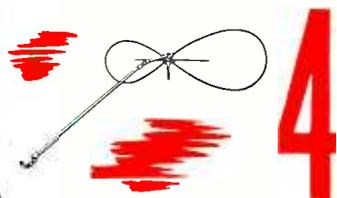Now, primary area reception benefits from Tel-a-Ray Antenna know-how!



Butterfly Swivel-Positioned TV Antenna . . . low cost, high gain . . . easy to adjust for best primary area reception . . . self-mounted on three-way bracket for quick installation almost anywhere . . . an all-channel antenna designed and priced for the mass market.

HOW TO INCREASE VOLUME AND PROFITS NOW

A huge market is opened up for you by Tel-a-Ray long-distance antennas and the Pre-Amplifier. With them, you can sell television in areas where it could not otherwise be sold successfully. For the big, established primary area market, the Butterfly has the features needed for capturing replacement sales . . . for building profits and volume against the strangest competition. These are products of the finest construction and appearance . . . ruggedly made of corrosionproof materials and unconditionally guaranteed against wind and weather damage. Let us send you full details.

Tel-a-Ray, America's most progressive antenna manufacturer, has applied to the FCC to operate a UHF television station on Channel 50 . . . Tel-a-Ray's research engineer is keeping pace with America's fastest-growing industry, has developed an effective UHF antenna. Such progress assures you finer television.

Send the coupon

for full information and
free sales literature

Tel-a-Ray ENTERPRISES, INC. P. O. Box 332E, Henderson, Kentucky


Yes . . . send me full information and descriptive literature on
 Models T and TD Antennas; Models R and RD Antennas;
 Butterfly Swivel-Positioned Antenna; The Pre-Amplifier.

NAME.....

COMPANY.....

ADDRESS.....

for Radio and
Television

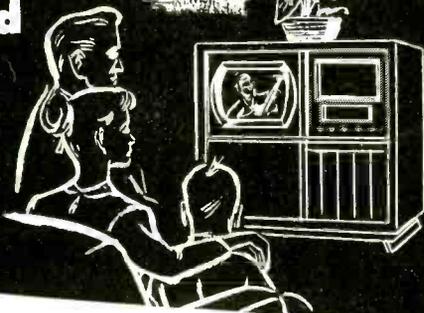

it's
OXFORD
Speakers

Preferred for original equipment
... Proven for replacement!

Other Oxford Speakers for:
Portable Sets • Auto Radios • P.A. Systems • Out-
door and Weatherproof Applications • High Fidelity • Intercom

OXFORD
ELECTRIC CORPORATION
3911 S. Michigan Ave. • Chicago 15, Ill.
EXPORT: ROBURN AGENCIES, NEW YORK CITY

A copy of our
latest catalog
will be sent
upon request.

Available at
leading jobbers!



mum output is about 2 volts. All leads and components to grids and plates should be kept well away from the chassis to insure low stray capacitance. Bus-bar wiring is recommended. The capacitor, of course, must be insulated from the chassis. It is mounted on a piece of masonite which serves also as a partition between this section and the crystal-oscillator section.

Heating and consequent frequency drift are minimized by using an external power supply. Any power supply capable of delivering 150 to 300 volts can be used, but a regulated 150 volts for the two r.f. oscillators and 250 volts for the audio oscillator gives the best all-around results.

Several filters and shielded leads are used to keep the power-supply cable from radiating. Each of the r.f. oscillators has a single-section filter, and all three units are fed through a common two-section filter.

The care employed in shielding and construction resulted in gratifyingly low signal leakage. It amounts to about 1 microvolt for the v.f.o. and about 5 microvolts for the crystal oscillator, the latter being accounted for by binding-post radiation.

Mechanically the construction was determined by the original layout of the tuning unit. The velvet vernier dial and the insulated coupling were left in place and used for the audio-oscillator tuning control. A paper calibrated scale was added to the dial for direct reading. The 4-position ceramic switch had to be mounted in the middle section. The layout of panel controls, while not entirely what might be desired from the standpoint of appearance, is functionally sound.

The 11-position switch, marked CRYSTAL FREQUENCY, is located in the lower center part of the panel. Since completion of the unit I have added a 10.7- and a 21.25-mc crystal and labeled these two extra frequencies on the panel. The R-C values for the audio-frequency generator, though calculated for the 8-80, etc., range, proved to give a range of 10-100, 100-1,000, etc. (The exact ranges are determined by circuit-wiring capacitance, resistor and capacitor tolerance, and tuning capacitor characteristics.) The 4-position capacitor switch is the basic r.f. range selector, but the settings on the inductor tap switch allow an electronic band-spread of from 50 to 500 kc. Originally, the jack between the v.f.o. range switches was used for r.f. output, but subsequent check showed that taking audio or r.f. signals from one output was quite feasible.

The original panel was a very thin piece of aluminum which was easily removed. Upon completion of the instrument the underlying panel was labeled with Techni-cals which gave the job that "dressed up" look.

The total cost of the instrument was about \$30, including crystals. We've never obtained so much usefulness per dollar in any instrument before.

—end—

RADIO-ELECTRONICS for

V.T.V.M. in PA Work

By A. T. PARKER

THE vacuum-tube voltmeter is a most useful and versatile tool to the service technician who deals with public address and audio systems. With a little imagination and ingenuity mixed with a knowledge of the methods of applying the v.t.v.m., the most difficult problems can be solved.

The modern v.t.v.m. measures either a.c. or d.c. voltages. It requires essentially no power from the circuit to which it is connected, thus enabling measurement of true r.m.s. voltages in high-impedance circuits and true d.c. voltages in complicated series circuits.

Fig. 1 illustrates a typical phase inverter and output stage as found in

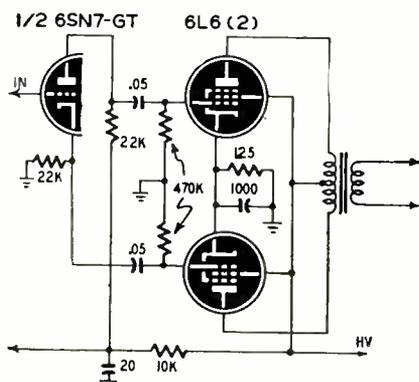


Fig. 1—Idealized a.f. phase inverter.

many high-quality amplifiers. The v.t.v.m. can be used to check the balance of the audio voltages applied to the output-tube grids. In this circuit it is particularly important that the value of the cathode resistor in the phase inverter match that of the plate resistor. With a constant audio signal applied to the input of the amplifier from an oscillator, the audio (a.c.) voltage appearing on one output-tube control grid should be identical with that on the other tube's control grid. If the voltages from each grid to chassis differ by more than a few percent, the quality of the amplifier will be seriously impaired.

There are several possible causes of unbalance in the circuit shown. Values of the grid resistors in the output stage should be the same. They should be checked with an ohmmeter and replacements selected which match in value. The value of the coupling capacitor in series with each output grid will affect the balance at low audio frequencies. For best results, these should be the same. The capacitance of the coupling capacitor is chosen to have negligible reactance at the lowest frequency the amplifier is required to produce. The .05- μ f capacitors in Fig. 1 have a reactance of approximately 31.850 ohms at 100 cycles per second.

At any given frequency of operation

the capacitor can be considered a resistor in series with the grid resistance. The reactance of the capacitor is thus indicated as R1 in Fig. 2. The grid resistor is R2. This simplified diagram shows how the reactance of the capacitor forms a voltage-dividing network, with the grid resistor as the output portion. Since the reactance of a capacitor varies inversely with frequency, it can be seen that the voltage at the grid of the tube would suffer if the capacitor value were too low and its reactance high at the lower frequencies of operation.

Coupling and bypass capacitors

The effectiveness of the coupling capacitor at all frequencies of operation can be measured with the v.t.v.m. Connect an audio oscillator to the input of the amplifier and measure the audio voltage to chassis on both sides, the input and output sides, of the coupling capacitor. Write down the voltage measured on each side, using different audio frequencies from the audio oscillator. As the frequency is made lower and lower, the difference between the voltages measured on the input and output sides of the capacitor will become greater. The low-frequency response of the amplifier can be improved, of course, by using bigger coupling capacitors.

If the coupling capacitor is leaky and permits d.c. to pass, the v.t.v.m. will detect it. Set it up to measure d.c. and connect it to the output side of the coupling capacitor. With the following tube removed, there should be no d.c. present unless the capacitor is defective. Replacement coupling capacitors

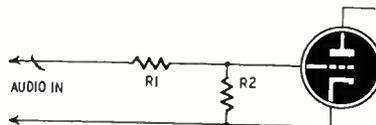


Fig. 2—R1 indicates coupling reactance.

should be high quality, mica or paper insulated, with a voltage rating several times that of the d.c. on the plate of the preceding tube.

The effectiveness of bypass capacitors can be checked simply with the v.t.v.m. and an audio oscillator. With the oscillator connected as shown in Fig. 3, from grid to chassis (adjusted

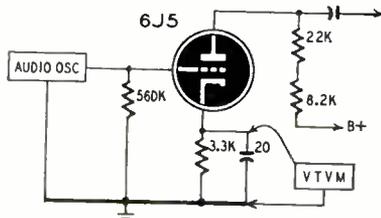


Fig. 3—V.t.v.m. checks cathode bypass.

INDISPENSABLE! PHOTOFACT BOOKS



Photofact Television Course. Covers TV principles, operation and practice. 216 pages; profusely illustrated; 8 1/2 x 11". Order **TV-1**. Only **\$3.00**

Television Antennas. New 2nd edition. Describes all TV antenna types; tells how to select, install, solve troubles. Saves time; helps you earn more. 200 pages; illustrated. Order **TAG-1**. Only **\$2.00**

Television Tube Location Guide. Volume 2. Accurate diagrams show position and function of all tubes in hundreds of TV sets; helps you diagnose trouble without removing chassis. 224 pages; pocket-size. Order **TGL-2**. Only **\$2.00**

Television Tube Location Guide. Vol. 1. Over 200 pages of TV receiver tube position diagrams on hundreds of models. Order **TGL-1**. Only **\$1.50**

Making Money in TV Servicing. Tested proved methods of operating a profitable TV service business. Covers all important phases. Authoritative, valuable guide to success. Over 130 pages. Order **MM-1**. Only **\$1.25**

Servicing TV in the Customer's Home. Shows how to diagnose trouble using capacitor probe and VTVM. Short-cut methods help save time, earn more on outside service calls. Order **TC-1**. Only **\$1.50**

1949-1950 Record Changer Manual. Vol. 3. Covers 44 models made in 1949, including multi-speed changers and wire and tape recorders. Original data based on actual analysis of equipment. 286 pages; 8 1/2 x 11", paper-bound. Order **CM-3**. Only **\$3.00**

1948-1949 Changer Manual. Vol. 2. Covers 45 models made in 1948-49. Paper bound. Order **CM-2**. Only **\$4.95**

1947-1948 Changer Manual. Vol. 1. Covers 40 post-war models up to 1948. Order **CM-1**. Only **\$3.95**

Recording & Reproduction of Sound. A complete authoritative treatment of all phases of recording and amplification. 6 x 9". Order **RR-1**. Only **\$5.00**



Audio Amplifiers. Vol. 3. Clear, uniform, accurate data on 50 important audio amplifiers, plus full coverage of 22 FM and AM tuners, produced during 1950. 362 pages, 8 1/2 x 11". Order **AA-3**. Only **\$3.95**

Audio Amplifiers. Vol. 2. A complete analysis of 104 well-known audio amplifiers and 12 tuners made 1949-50. 368 pages, 8 1/2 x 11". Order **AA-2**. Only **\$3.95**

Audio Amplifiers. Vol. 1. 102 amplifiers and FM tuners made through 1948. 352 p. Order **AA-1**. Only **\$3.95**

Auto Radio Manual. Complete service data on more than 100 post-war auto radio models. Covers over 24 mfrs. 350 pages, 8 1/2 x 11". Order **AR-1**. Only **\$4.95**

Communications Receiver Manual. Complete analysis of 50 popular communications models. 246 pages, 8 1/2 x 11". Order **CR-1**. Only **\$3.00**

Radio Receiver Tube Placement Guide. Accurate diagrams show where to replace each tube in 5500 radio models, covering 1938-1947 receivers. 192 pages, pocket-size. Order **TP-1**. Only **\$1.25**


Dial Cord Stringing Guide. Vol. 2. Covers receivers made from 1947 through 1949. Shows you the one right way to string a dial cord in thousands of models. Pocket-size. Order **DC-2**. Only **\$1.00**

Dial Cord Guide. Vol. 1. Covers sets produced 1938 through 1946. Order **DC-1**. Only **\$1.00**

Order from your Parts Jobber or write direct to
HOWARD W. SAMS & CO., INC., 2201 E. 46th St., Indianapolis 5, Indiana
HOWARD W. SAMS & CO., INC.



**VIKING
SPEAKERS**
by **Jensen**

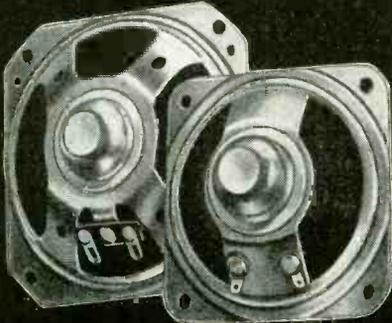

**low cost
replacement
speakers
by Jensen
...foremost
in advanced-
design
loudspeakers**

Manufactured especially for low-cost replacement and utility applications by Jensen—World's foremost producer of advanced-design loudspeakers—VIKING speakers embody the same engineering and production skills which go into every Jensen product.

Ask for VIKING by Jensen when you need dependable performance at lowest cost—line includes 12 models from 3½" to 12" with 4" x 6", 5" x 7" and 6" x 9" ovals, all P. M. Accessory bracket set solves service installation problems.



Jensen
MANUFACTURING COMPANY
Division of the Muter Company
Export Department at the Factory
6601 S. Laramie • Chicago 38, Illinois

BURTON BROWNE ADVERTISING

to an output voltage less than the d.c. bias on the grid) and the v.t.v.m. across the cathode bypass capacitor, no audio voltage should be indicated. This test should be conducted at the lowest frequency the amplifier is expected to reproduce. If audio voltage is shown, the stage will be degenerative at that fre-

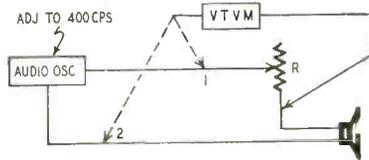


Fig. 4—Checking voice-coil impedance.

quency and all lower frequencies. To improve the low-frequency response, replace the bypass with a larger one. The reactance of a 20- μ f capacitor at 100 cycles is 80 ohms. Since this is small compared with the value of the cathode resistor, 3,300 ohms, the amplifier's response at 100 cycles should be good.

Loudspeaker and gain

Determining the voice-coil impedance of a loudspeaker to be used in public address systems is often a problem. Many speakers are not marked and the information is not readily available. An audio oscillator is connected to the

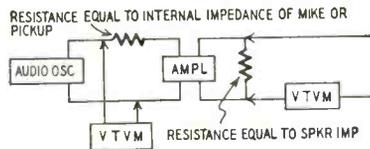


Fig. 5—Measuring a.f. amplifier gain. speaker as shown in Fig. 4. An adjustable resistor with a maximum value of 20 or 25 ohms is connected in series with the voice coil across the oscillator.

One terminal of the v.t.v.m. is connected to the midpoint of the two. The other connection to the v.t.v.m. is alternately shifted from point 1 to point 2. The resistor R is adjusted until the v.t.v.m. reads the same voltage at both points. Measure the resistance value of R with an ohmmeter. If the audio oscillator is adjusted to 400 cycles for this test, the value of R is equivalent to the impedance of the voice coil when the voltages are equal.

The gain of an amplifier is easily measured with the v.t.v.m. The input power and output power as measured by it are converted to *decibels of gain*. Set up the amplifier as shown in Fig. 5 with resistors to simulate the input and output devices. Adjust the volume control for maximum gain. If the resistor in the input is intended to simulate the internal impedance of a dynamic microphone it will be approximately 25,000 ohms. (It is best to get exact data on the internal impedance of a microphone or pickup from the manufacturer.) Adjust the output of the audio oscillator to one volt as indicated by the v.t.v.m. The input power is then found by the formula:

$$W = E^2/R.$$

Since E, the voltage is 1, E² is 1 x 1 or 1. Dividing by 25,000 gives an input power of .00004 watts. For convenience, this might be called .04 milliwatt.

Supposing the output load resistor is made equal to a speaker impedance of 8 ohms, the output power can be computed in the same way. If the v.t.v.m. reads, say, 13 volts across the 8 ohms, the power output is 13 x 13 (or 169) divided by 8. This gives 21 watts out. t.

The output power divided by the input power is the "power ratio" and will (Continued on page 115)

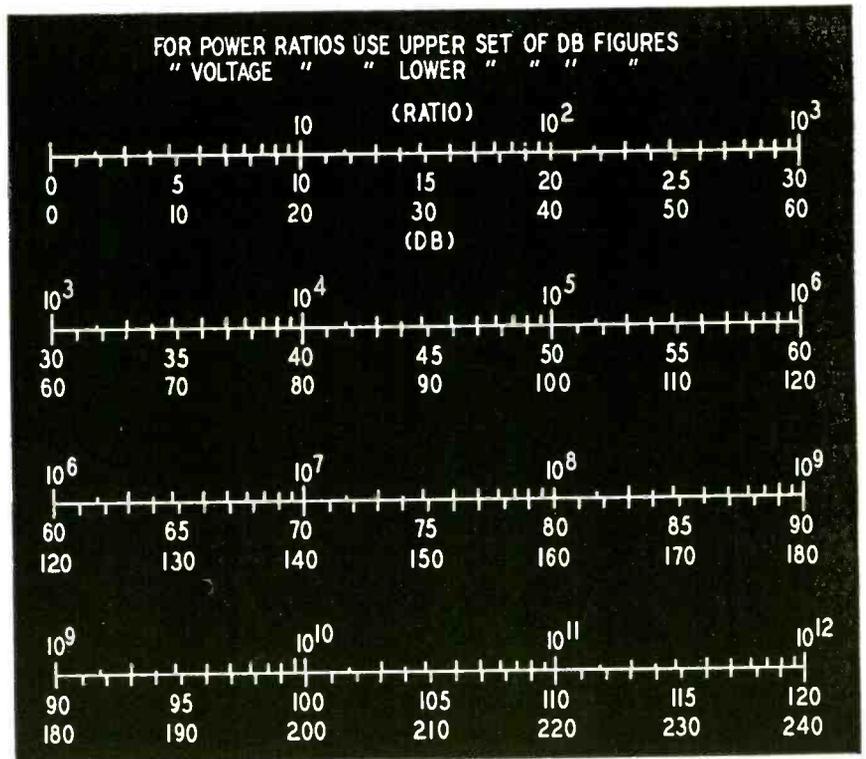



Fig. 6—This chart simplifies conversion of power and voltage ratios to decibels.

Features OF THE NEW 1952




PROOF OF THE NEW O-7 OSCILLOSCOPE'S OUTSTANDING PERFORMANCE

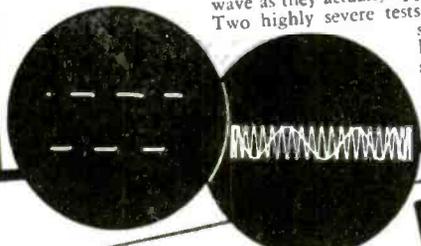Below are actual, unretouched photographs showing the outstanding frequency response characteristics of the NEW 1952 HEATHKIT OSCILLOSCOPE, MODEL O-7. To the left is a 10 KC square wave — to the right a 4 MC sine wave as they actually appear on the screen. Two highly severe tests to make on any scope (only the best of scopes will show traces like these) — and the O-7 really comes through.




COMPANION VACUUM TUBE VOLTMETERS

Here are the two NEW 1952 VACUUM TUBE VOLTMETER COMPANION PIECES. Matched instruments of new design to open up the whole field of DC, AC, and resistance measurements for you. The new greatly reduced size combines style, beauty, and compactness — The V-5 and AV-1 have the new panel and cabinet construction as shown on the right. A tremendous pair of voltmeters. Small in size but virtual giants in the range of measurements they make.

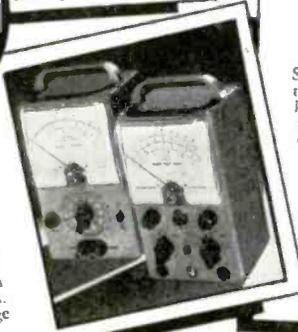

NEW STYLE AND BEAUTY

Style that's modern, yet functional — that's the trend of today — and Heathkits are right up to the minute. Note the cut showing the new V-5 and AV-1 cabinet and panel construction. The front panel and rear cover slide right over the recessed flange of the case thereby eliminating sharp edges and pointed corners. The voltmeter kits aren't "shelf" or "mounted" instruments — they're moved about on the bench a lot and thus the new compact size and specially designed cabinets — Another 1952 Heathkit feature.

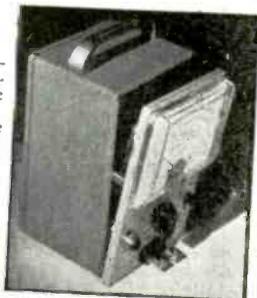

A STATEMENT FROM SIMPSON ELECTRIC CO.

In choosing Simpson Meters for their Heathkit VTVM, the Heath Co. has set a new high standard of kit meter quality. The same high quality of material, workmanship and design that has given Simpson the reputation for building "Instruments That Stay Accurate" is found in the Heathkit Meter Movement.

SIGNED
SIMPSON ELECTRIC CO.



A STATEMENT FROM CHICAGO TRANSFORMER

It is indeed gratifying to note the outstanding sales records you are building with you Heathkits.

This sales success is readily understandable, since we are cognizant of the high quality standards you have established for your component suppliers.

We at Chicago Transformer are proud that our product has contributed to the recognized quality and increasing popularity of Heathkits.


CHICAGO TRANSFORMER DIVISION
Essex Wire Corporation

L. S. RACINE *L. S. Racine*
Vice-President and Sales Manager



HEATHKIT PRECISION RESISTORS

Where exact resistance values are required for instrument accuracy, the Heath Co. has spared no effort in supplying the finest resistors available. Precision resistors as manufactured by Continental Carbon Inc., and Wilcor Corp., meet the rigorous JAN (Joint Army-Navy) specifications and are small in size, extremely non-inductive, highly stable, have a low temperature coefficient, and can be held to great accuracy. You'll find quality components in Heathkits.

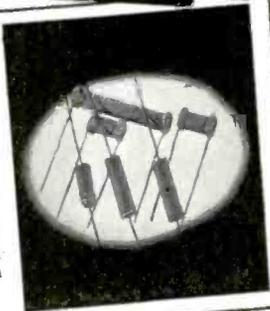

COLLEGES USE HEATHKITS

Colleges and Universities throughout the country are using Heathkits in their electrical engineering, radio, and physics laboratories — Heathkits are the answer to good test equipment at lower cost, plus being rugged, dependable, and accurate. Trade schools are having their students build Heathkits to obtain a first hand working knowledge of test equipment and to get the practical experience gained by construction. Heathkits fill school needs.



YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

REPORT AGENT
ROCKE INTERNATIONAL CORP.
12 E. 40th ST.
NEW YORK CITY 17 (16)
CABLE: ARLAB-N.Y.

The HEATH COMPANY

... BENTON HARBOR 20, MICHIGAN

THE *New* 1952
Heathkit
**OSCILLOSCOPE
 KIT**

MODEL O-7
 SHIPPING WEIGHT 24 LBS.

\$43⁵⁰

Features

- New "spot shape" control for spot adjustment — to give really sharp focusing.
- A total of ten tubes including CR tube and five miniatures.
- Cascaded vertical amplifiers followed by phase splitter and balanced push-pull deflection amplifiers.
- Greatly reduced retrace time.
- Step attenuated — frequency compensated — cathode follower vertical input.
- Low impedance vertical gain control for minimum distortion.
- New mounting of phase splitter and deflection amplifier tubes near CR tube base.
- Greatly simplified wiring layout.
- Increased frequency response — useful to 5 Mc.
- Tremendous sensitivity .03V RMS per inch Vertical — .6V RMS per inch Horizontal.
- Dual control in vernier sweep frequency circuit — smoother acting.
- Positive or negative peak internal synchronization.

NEW INEXPENSIVE *Heathkit*
ELECTRONIC SWITCH KIT

The companion piece to a scope — Feed two different signals into the switch, connect its output to a scope, and you can observe both signals — each as an individual trace. Gain of each input is easily set (gain A and gain B controls), the switching frequency is simple to adjust (coarse and fine frequency controls) and the traces can be superimposed for comparison or separated for individual study (position control).


Use the switch to see distortion, phase shift, clipping due to improper bias, both the input and output traces of an amplifier — as a square wave generator over limited range.

The kit is complete; all tubes, switches, cabinet, power transformer and all other parts, plus a clear detailed construction manual.



Model S-2
 Shipping Wt. 11 lbs.

Only
\$19⁵⁰

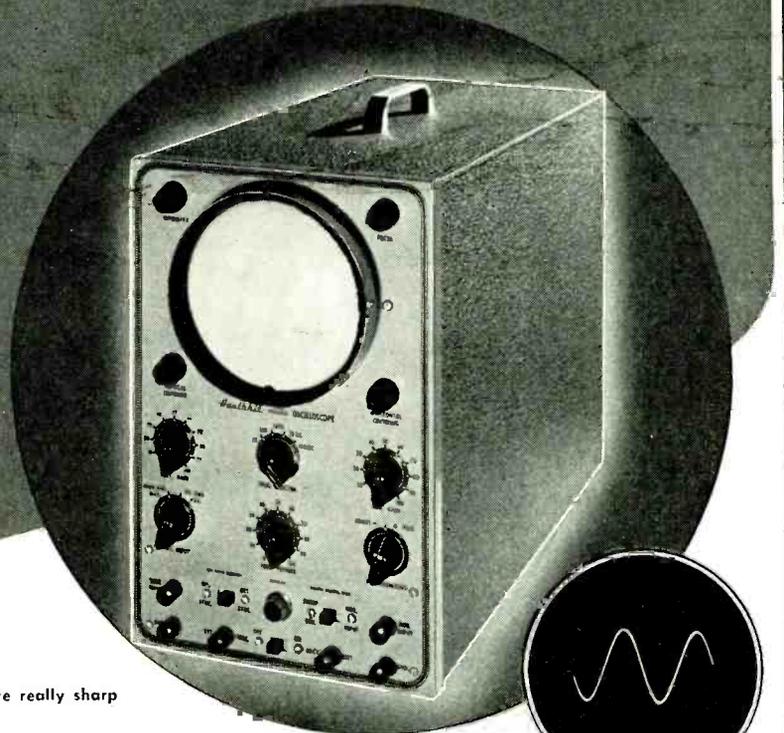

The performance of the NEW, IMPROVED, HEATHKIT 5" OSCILLOSCOPE KIT is truly amazing. The O-7 not only compares favorably with equipment costing 4 and 5 times as much, but in many cases literally surpasses the really expensive equipment. The new, and carefully engineered circuit incorporates the best in electronic design — and a multitude of excellent features all contribute to the outstanding performance of the new scope.

The VERTICAL CHANNEL has a step attenuated, frequency compensated vertical input which feeds a cathode follower stage — this accomplishes improved frequency response, presents a high impedance input, and places the vertical gain control in a low impedance circuit for minimum distortion. Following the cathode follower stage is a twin triode — cascaded amplifiers to contribute to the scope's extremely high sensitivity. Next comes a phase splitter stage which properly drives the push-pull, hi gain, deflection amplifiers (whose plates are directly coupled to the vertical deflection plates). This one tube lineup and circuitry give a sensitivity of .03V per inch RMS vertical and useful frequency response to 5 Mc.

The HORIZONTAL CHANNEL consists of a triode phase splitter with a dual potentiometer (horizontal gain control) in its plate and cathode circuits for smooth, proper driving of the push-pull horizontal deflection amplifiers. As in the vertical channel, horizontal deflection amplifier plates are direct coupled to the CR tube horizontal deflection plates (for improved frequency response).

The WIDE-RANGE SWEEP GENERATOR circuit incorporates a twin triode multivibrator stage for producing a good saw-tooth sweep frequency (with faster retrace time). Has both coarse and vernier sweep frequency controls.

And the scope has internal synchronization which operates on either positive or negative peaks of the input signal — both high and low voltage rectifiers — Z axis modulation (intensity modulation) — new spot shape (astigmatism) control for spot adjustment — provisions for external synchronization — vertical centering and horizontal centering controls, wide range focus control — and an intensity control for giving plenty of trace brilliance.

The Model O-7 EVEN HAS GREAT NEW MECHANICAL FEATURES — A special extra-wide CR tube mounting bracket is provided so that the vertical cascade amplifier, vertical phase splitter, vertical deflection amplifier, and horizontal deflection amplifier can mount near the base of the CR tube. This permits close connection between the above stages and to the deflection plates; distributed wiring capacity is greatly reduced, thereby affording increased high frequency response.

The power transformer is specially designed so as to keep its electrostatic and electromagnetic fields to a minimum — also has an internal shield with external ground lead.

You'll like the complete instructions showing all details for easily building the kit — includes pictorials, step-by-step construction procedure, numerous sketches, schematic, circuit description. All necessary components included — transformer, cabinet, all tubes (including CR tube), completely punched and formed chassis — nothing else to buy.

YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
 13 E. 40th ST.
 NEW YORK CITY (16)
 CABLE: ARLAB-N.Y.

The **HEATH COMPANY**

... BENTON HARBOR 20, MICHIGAN

RADIO-ELECTRONICS for

THE *New* 1952

Heathkit VTVM KIT

MODEL V-5
SHIPPING WT. 5 LBS.

\$24.50

Features

- New styling, — formed case for beauty.
- New truly compact size. Cabinet 4 1/8" deep by 4-11/16" wide by 7 3/8" high.
- Quality 200 microamp meter.
- New ohms battery holding clamp and spring clip — assurance of good electrical contact.
- Highest quality precision resistors in multiplier circuit.
- Calibrates on both AC and DC for maximum accuracy.
- Terrific coverage — reads from 1/2V to 1000V AC, 1/2V to 1000V DC, and .1 to over 1 billion ohms resistance.
- Large, clearly marked meter scales indicate ohms, AC Volts, DC Volts, and DB — has zero set mark for FM alignment.
- New styling presents attractive and professional appearance.

A real beauty — you'll have only highest praise for this NEW MODEL VACUUM TUBE VOLTMETER. Truly a beautiful little instrument — and it's more compact than any of our previous models. Note the new rounded edges on the front panel and rear cover. The size is greatly reduced to occupy a minimum of space on your workbench — yet the meter remains the same large size with plainly marked scales.

A set of specially designed control mounting brackets permit calibration to be performed with greatest ease — also makes for ease in wiring. New battery mounting clamp holds ohms battery tightly into place, and base spring clip insures a good connection to the ohms string of resistors.

The circuitry employs two vacuum tubes — A duo diode operating when AC voltage measurements are taken, and a twin triode in the circuit at all times. The cathode balancing circuit of the twin triode assures sensitive measurements, and yet offers complete protection to the meter movement. Makes the meter burn-out proof in a properly constructed instrument.

Quality components are used throughout — 1% precision resistors in the multiplier circuit — conservatively rated power transformer — Simpson meter movement — excellent positive detent, smooth acting switches — sturdy cabinet, etc.


And you can make a tremendous range of measurements — 1/2V to 1000V AC, 1/2V to 1000V DC, .1 to over 1 billion ohms, and DB. Has mid-scale zero level marking for quick FM alignment. DB scale in red for easy identification — all other scales a sharp, crisp black for easy reading.

A four position selector switch allows operator to rapidly set the instrument for type or reading desired — positions include ACV, DC+V, DC-V, and Ohms. DC — position allow negative voltage to be rapidly taken. Zero adjust and ohms adjust controls are conveniently located on front panel.

Enjoy the numerous advantages of using a VTVM. Its high input impedance doesn't "load" circuits under test — therefore, assures more accurate and dependable readings in high impedance circuits such as resistance coupled amplifiers, AVC circuits, etc. Note the 30,000 VDC probe kit and the RF probe kit — available at low extra cost and specially designed for use with this instrument. With these two probes, you can make DC voltage measurements up to 30,000V, or make RF measurements — added usefulness to an already highly useful instrument.

The instruction manual is absolutely complete — contains a host of figures, pictorials, schematic, detailed step-by-step instructions, and circuit description. These clear, detailed instructions make assembly a cinch.

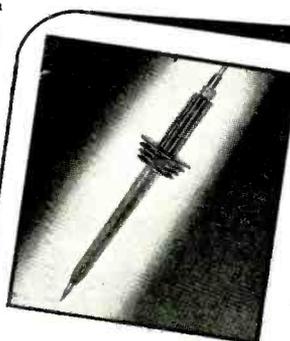And every part is included — meter, all controls, pilot light, switches, test leads, cabinet, instruction manual, etc.



Heathkit 30,000V DC PROBE KIT

A new 30,000 V DC Probe Kit to handle high voltages with safety. For TV service work and all other high voltage applications. Sleek looking — and guard — jet black plastic — Red body with connector, cable, and PL55 type plug. Plugs into Heathkit VTVM so that 300V scale is conveniently multiplied with any standard 11 megohm VTVM.

\$5.50


No. 336 High Voltage Probe Kit
Shipping Wt. 2 lbs.

Heathkit RF PROBE KIT

This RF Probe Kit comes complete with probe housing, crystal diode detector, connector, lead and plug and all other parts plus clear assembly instructions. Extends range of Heathkit VTVM to 250 Mc. ± 10%. Works on any 11 megohm input VTVM. Specify No. 309 RF Probe Kit.

\$5.50

Ship. Wt. 1 lb.

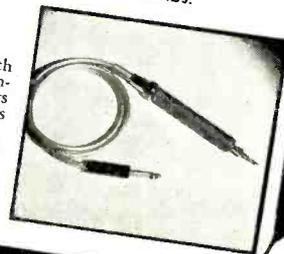

YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
131 E. 40th ST.
NEW YORK CITY (16)
CABLE: ARLAB-N.Y.

The HEATH COMPANY

... BENTON HARBOR 20, MICHIGAN

Heathkit SIGNAL GENERATOR KIT

Model SG-6
Shipping Wt. 7 lbs.

The new Heathkit Signal Generator Kit has dozens of improvements. Covers the extended range of 160 Kc to 50 megacycles on fundamentals and up to 150 megacycles on useful calibrated harmonics; makes this Heathkit ideal as a marker oscillator for TV. Output level can be conveniently set by means of both step attenuator and continuously variable output controls. Instrument has new miniature HF tubes to easily handle the high frequencies covered.

Uses 6C4 master oscillator and 6C4 sine wave audio oscillator. The kit is transformer operated and a husky selenium rectifier is used in the power supply. All coils are precision wound and checked for calibration making only one adjustment necessary for all bands.

New sine wave audio oscillator provides internal modulation and is also available for external audio testing. Switch provided allows the oscillator to be modulated by an external audio oscillator for fidelity testing of receivers. Comes complete, all tubes, cabinet, test leads, every part. The instruction manual has step-by-step instructions and pictorials. It's easy and fun to build a Heathkit Model SG-6 Signal Generator.



Heathkit CONDENSER CHECKER KIT

Only
\$19.50

Model C-2
Shipping Wt. 6 lbs.



Checks all types of condensers — paper — mica — ceramic — electrolytic. All condenser scales are direct reading and require no charts or multipliers. Covers range of .00001 MFD to 1000 MFD. A Condenser Checker that anyone can read. A leakage test and polarizing voltage for 20 to 500 V provided. Measures power factor of electrolytics between 0% and 50% and reads resistance from 100 ohms to 5 megohms. The magic eye indicator makes testing easy.

The kit is 110V 60 cycle transformer operated and comes complete with rectifier tube, magic eye tube, cabinet, calibrated panel and all other parts. Has clear detailed instructions for assembly and use.

NEW Heathkit SIGNAL TRACER AND UNIVERSAL TEST SPEAKER KIT

\$19.50

Model T-2
Shipping Wt. 7 lbs.



The popular Heathkit Signal Tracer has now been combined with a universal test speaker at no increase in price. The same high quality tracer follows signal from antenna to speaker — locates intermittents — finds defective parts quicker — saves valuable service time — gives greater income per service hour. Works equally well on broadcast, FM, or TV receivers. The test speaker has an assortment of switching ranges to match either push-pull or single output impedances. Also tests microphones, pickups and PA systems. Comes complete: cabinet, 110V and detailed instructions for assembly and use.



Model TC-1
Shipping Wt. 12 lbs.

\$29.50

Heathkit TUBE CHECKER KIT

The Tube Checker is a MUST for radio repair men. Often customers want to SEE tubes checked, and a checker like this builds customer confidence. In your repairing, you will have a multitude of tubes to check — quickly. The Heathkit tube checker will serve all these functions — it's good looking (with a polished birch cabinet and an attractive two color panel) — checks 4, 5, 6, 7 prong Octals, Loctals, 7 prong miniatures, 9 prong miniatures, pilot lights, and the Hytron 5 prong types. AND IT'S FAST TO OPERATE — the gear driven, free-running roll chart lists hundreds of tubes, and the smooth, acting, simplified switching arrangement gives really rapid set-ups.

The testing arrangement is designed so that you will be able to test new tubes of the future — without even waiting for factory data — protection against obsolescence.

You can give tubes a thorough testing — checks for opens, shorts, each element individually, emission, and for filament continuity. A large BAD-?-GOOD meter scale is in three colors for easy reading and also has a "line-set" mark.

You'll find this tube checker kit a good investment — and it's only \$29.50.

YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CABLE: ARLAB-N.Y.

The **HEATH COMPANY**

... BENTON HARBOR 20, MICHIGAN

RADIO-ELECTRONICS for

New LABORATORY LINE HEATHKITS



NEW *Heathkit*
A.C. VACUUM TUBE
VOLTMETER KIT

Now — as a Heathkit — at a price anyone can afford, an AC VTVM. A new kit to make possible those sensitive AC measurements required by audio enthusiasts, laboratories, and experimenters. Here is the kit that the audio men have been looking for. Its tremendous range of coverage makes possible measurements of audio amplifier frequency response — gain or loss of audio stages — characteristics of audio filters and attenuators — hum investigation — and literally a multitude of others. Ten ranges consisting of full scale .01, .03, .1, .3, 1, 3, 10, 30, 100, 300 volts RMS assure easy and more accurate readings. Ten ranges on DB provide for measurements from -52 to +52 DB. Frequency response within 1 DB from 20 cycles to 50 KC.

The ingenious circuitry incorporates precision multiplier resistors for accuracy, two amplifier stages using miniature tubes, a unique bridge rectifier meter circuit, quality Simpson meter with 200 microampere movement, and a clean layout of parts for easy wiring. A high degree of inverse feedback provides for stability and linearity.

Simple operation is accomplished by the use of only one control, a range switch which changes the voltage ranges in multiples of 1 and 3, and DB ranges in steps of 10.

The instrument is extremely compact, cabinet size — 4 1/8" deep x 4-11/16" wide x 7 3/8" high, and the newly designed cabinet makes this the companion piece to the VTVM. For audio work, this kit is a natural.

MODEL AV-1
Shipping weight 5 lbs.

\$29⁵⁰

NEW *Heathkit*
AUDIO FREQUENCY METER KIT

MODEL AF-1
Shipping weight 12 lbs.



A NEW Heathkit Audio Frequency Meter — the ideal instrument for determining frequencies from 20 cycles to 100 KC. Set the selector switch to the proper range — feed the signal into the input terminals — and read the frequency from the meter — completely simple to operate, and yet dependable results.

Quality Simpson 200 microampere meter has two plainly marked scales (0-100 0-300). These scales, read in conjunction with the seven position selector switch, give full scale readings of 100, 300, 1000, 3000, 10,000, 30,000, and 100,000 cycles. Convenient ranges for fast and easy readings.

For greatest accuracy, the 1-3-10 ratio of ranges is maintained and each range has individual calibrating control.

Input impedance is high (1 megohm) for negligible circuit loading. A signal and a change in signal voltage between 2 and 300V can be fed directly into the instrument reading. In addition, input wave shape is not critical (the unit will read the frequency of either sine wave or square wave input).

The tube complement consists of a 6SJ7 amplifier and clipper, 6V6 amplifier and clipper, 6HG meter pulse rectifier, 6X5 power supply rectifier, and OD3/VR150 voltage regulator.

Construction is simple, and quality components are used throughout.

NEW
Heathkit SQUARE WAVE
GENERATOR KIT

The new Heathkit Square Wave Generator Kit with its 100 KC square wave opens an entirely new field of audio testing. Square wave testing over this wide range will quickly show high and low frequency response characteristics of circuits — permit easy adjustment of high frequency compensating networks used in video amplifiers — identify ringing in circuits — demonstrate transformer characteristics, etc.

The circuitry consists of a multivibrator stage, a clipping and squaring stage, and a cathode follower output stage. The power supply is transformer operated and utilizes a full wave rectifier tube with 2 sections of LC filtering.

As a multivibrator cannot be accurately calibrated, a provision is provided to allow the instrument to be accurately synchronized with an accurate external source when extreme accuracy is required.

The low impedance output is continuously variable between 0 and 25 volts and operation is simple. You'll really appreciate the wide range of this instrument, 10 cycles to 100 kilocycles — continuously variable. Kit is complete with all parts and instruction manual, and is easy to build.

NEW *Heathkit*
**INTERMODULATION
ANALYZER KIT**

Intermodulation testing of audio equipment is rapidly being accepted by more and more engineers and audio experts as the best way to determine the characteristics of audio amplifiers, recording systems, networks, etc. — shows up those undesirable characteristics which contribute to listening fatigue when all other methods fail.

The Heathkit Intermodulation Analyzer supplies a choice of two high frequencies (3000 cycles and a higher frequency) and one low frequency (60 cycles). Both 1:1 or 4:1 ratios of low to high frequencies can be set up for IM testing, and the ratios are easily set by means of a panel control and the instrument's own VTVM. An output level control supplies the mixed signal at the desired level with an output impedance of two thousand ohms. The Analyzer section has input level control and proper filter circuits feeding the instrument's VTVM to read intermodulation directly on full scale ranges of 30%, 10% and 3%. Built-in power supply furnishes all necessary voltages for operating the instrument.

You won't want to be without this new and efficient means of testing.



MODEL IM-1
Shipping wt. 18 lbs.

\$39⁵⁰



MODEL SQ-1
Shipping wt. 14 lbs.

\$29⁵⁰

YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
12 E. 40th ST.
NEW YORK CITY (16)
CABLE MAILER-N.Y.

The **HEATH COMPANY**

... BENTON HARBOR 20, MICHIGAN

Heathkit IMPEDANCE BRIDGE KIT



Model 1B-1B
Shipping Wt. 15 lbs.

\$69⁵⁰

This Impedance Bridge Kit is really a favorite with schools, industrial laboratories, and serious experimenters. An invaluable instrument for those doing electrical measurements work. Reads resistance from .01 Ohms to 10 meg., capacitance from .00001 to 100 MFD, inductance from 10 microhenries to 100 henries, dissipation factor from .002 to 1, and storage factor from 1 to 1000. And you don't have to worry about selecting the proper bridge circuit for the various measurements—the instrument automatically makes the correct circuit when you set up for taking the measurement you want. Bridge utilizes Wheatstone, Hay, Maxwell, and capacitance comparison circuits for the wide range and types of measurements possible. And it's self powered—has internal battery and 1000 cycle hummer. No external generator required—has provisions for external generator if measurements at other than 1000 cycles are desired. Kit utilizes only highest quality parts, General Radio main calibrated control, Mallory ceramic switches, excellent 200 microamp zero center galvanometer, laboratory type binding posts with standard 3/4 inch centers, 1% precision ceramic-body type multiplier resistors, beautiful birch cabinet and ready calibrated panel. (Headphones not included.)

Take the guesswork out of electrical measurements—order your Heathkit Impedance Bridge kit today—you'll like it.

Heathkit LABORATORY RESISTANCE DECADE KIT



\$19⁵⁰

Shipping Wt. 4 lbs.

An indispensable piece of laboratory equipment—the Heathkit Resistance Decade Kit gives you resistance settings from 1 to 99,999 ohms IN ONE OHM STEPS. For greatest accuracy, 1% precision ceramic-body type resistors and highest quality ceramic wafer switches are used.

Designed to match the Impedance Bridge above, the Resistance Decade Kit has a beautiful birch cabinet and attractive panel. It's easy to build, and comes complete with all parts and construction manual.

Heathkit LABORATORY POWER SUPPLY KITS

Limits:

No load.....	Variable 150-400V DC
25 MA.....	Variable 30-310V DC
50 MA.....	Variable 25-250V DC
Higher loads: Voltage drops off proportionally	



\$29⁵⁰

Model PS-1.....Ship. Wt. 20 lbs.

Every experimenter needs a good power supply for electronic setups of all kinds. This unit has been expressly designed to act as a HV supply and a 6.3 V filament voltage source. Voltage control allows selection of HV output desired (continuously variable within limits outlined), and a Volts-Ma switch provides choice of output metering. A large plainly marked and direct reading meter scale indicates either DC voltage output in Volts or DC current output in Ma. (Range of meter 0-500V D.C., 0-200 Ma. D.C.) Instrument has convenient stand-by position and pilot light.

Comes with power transformer, filament transformer, meter, 5Y3 rectifier, two 1619 control tubes, completely punched and formed chassis, panel, cabinet, detailed construction manual, and all other parts to make the kit complete.

Heathkit ECONOMY . . . 6 WATT AMPLIFIER KIT



Model A-4
Ship. Wt. 8 lbs.

\$12⁵⁰

No. 304 12 inch speaker . . . \$6.95

This fine Heathkit Amplifier was designed to give quality reproduction and yet remain low in price. Has two preamp stages, phase inverter stage, and push-pull beam power output. Comes complete with six tubes, quality output transformer (to 3-4 ohm voice coil), husky cased power transformer and all other parts. Has tone and volume controls. Instruction manual has pictorial for easy assembly. Six watts output with response flat $\pm 1\frac{1}{2}$ db from 50 to 15,000 cycles. A quality amplifier kit at a low price. Better build one.

Heathkit HIGH FIDELITY . . . 20 WATT AMPLIFIER KIT



\$33⁵⁰

Shipping Wt. 18 lbs.

Our latest and finest amplifier—the model A-6 (or A-6A) is capable of a full 20 Watts of high fidelity output—good faithful reproduction made possible through careful circuit design and the use of only highest quality components. Frequency response within ± 1 db from 20-20,000 cycles. Distortion at 3 db below maximum power output (at 1000 cycles) is only .8%. The power transformer is rugged and conservatively rated and will deliver full output and filament supply with ease. The output transformer was selected because of its exceptionally good frequency response and wide range of output impedances (4-8-16-150-600 ohms). Both are Chicago Transformers in drawn steel case for shielding and maximum protection to windings. The unit has dual tone controls to set the output for the tonal quality desired—treble control attenuates up to 15 db at 10,000 cycles—bass control gives bass boost up to 10 db at 50 cycles. Tube complement consists of 5U4G rectifier, 6SJ7 voltage amplifier, 6SN7 amplifier and phase splitter, and two 6L6's in push-pull output. Comes complete with all parts and detailed construction manual. (Speaker not included.)

MODEL A-6: For tuner and crystal phono inputs. Has two position selector switch for convenient switching to type of input desired.

MODEL A-6A: Features an added 6SJ7 stage (preamplifier) for operating from variable reluctance cartridge phono pickup, mike input, and either tuner or standard crystal phono pickup. A three position selector switch provides flexible switching. **\$35.50**
Shipping Wt. 18 lbs.

YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CABLE: AR148-107

The **HEATH COMPANY**

. . . BENTON HARBOR 20, MICHIGAN

RADIO-ELECTRONICS for



NEW 1952 *Heathkit*
**BATTERY ELIMINATOR
KIT**

- Can be used as battery charger.
- Continuously variable output 0 - 8 Volts — not switch type.
- Heavy duty Mallory 17 disk type magnesium copper sulfide rectifier.
- Automatic overload relay for maximum protection. Self-resetting type.
- Ideal for battery, aircraft and marine radios.
- Dual Volt and Ammeters read both voltage and amperage continually — no switching.

The new Heathkit Model BE-2 incorporates the best. Continuously variable output control is of the variable transformer type with smooth wiper type contacts.

There are no switches or steps and voltage between 0 and 8 Volts is available at 10 Amperes continuous and 15 Amperes intermittent. Maximum safety from overloads and shorts provided by automatic overload relay which resets itself when overload is removed.

The new rectifier is a 17 plate Mallory magnesium copper sulfide type. This is the most rugged type available for long trouble-free use.

Output is continuously metered by both a 0 - 10 Volt Voltmeter and a 0 - 15 Amp Ammeter. Shorted vibrators indicated instantly by ammeter.

Equip now for all types of service — aircraft — marine — auto and battery radios — this inexpensive instrument vastly increases service possibilities — better be ready when the customer walks in.

Model BE-3
Shipping Wt. 17 lbs.

NEW *Heathkit*
**SINE AND SQUARE WAVE
AUDIO GENERATOR KIT**

Designed with versatility, usefulness, and dependability in mind, the AG-7 gives you the two most needed wave shapes right at your fingertips — the sine wave and the square wave.

The range switch and plainly calibrated frequency scale give rapid and easy frequency selection, and the output control permits setting the output to any desired level.

A high-low impedance switch sets the instrument for either high or low impedance output — on high to connect a high impedance load, and on low to work into a low impedance transformer with negligible DC resistance.

Coverage is from 20 to 20,000 cycles, and distortion is at a minimum — you can really trust the output wave shape.

Six tubes, quality 4 gang tuning condenser, power transformer, metal cased filter condenser, 1% precision resistors in the frequency determining circuit, and all other parts come with the kit — plus, a complete construction manual — A tremendous kit, and the price is truly low.



Model AG-7
Shipping Wt. 15 lbs.

\$34.50

THE NEW *Heathkit*
HANDITESTER KIT

A precision portable volt-ohm milliammeter. Uses only high quality parts — All precision 1% resistors, three deck switch for trouble-free mounting of parts, specially designed battery mounting bracket, smooth acting ohm adjust control, beautiful molded bakelite case, 400 micro-amp meter movement, etc.

DC and AC voltage ranges 10 - 30 - 300 - 1000 - 5000V. Ohms range 0 - 3000 and 0 - 300,000. Range Milliamperes 0 - 10 Ma, 0 - 100 Ma. Easily assembled from complete instructions and pictorial diagrams.



\$13.50

Model M-1
Shipping Wt. 3 lbs.

NEW *Heathkit*

T.V. ALIGNMENT GENERATOR KIT

Here is an excellent TV Alignment Generator designed to do TV service work quickly, easily, and properly. The Model TS-2 when used in conjunction with an oscilloscope provides a means of correctly aligning television receivers.

The instrument provides a frequency modulated signal covering, in two bands, the range of 10 to 90 Mc. and 150 to 230 Mc. — thus, ALL ALLOCATED TV CHANNELS AS WELL AS IF FREQUENCIES ARE COVERED.


An absorption type frequency marker covers from 20 to 75 Mc. in two ranges — therefore, you have a simple, convenient means of frequency checking of IF's, independent of oscillator calibration.

Sweep width is controlled from the front panel and covers a sweep deviation of 0-12 Mc. — all the sweep you could possibly need or want.

And still other excellent features are: Horizontal sweep voltage available at the front panel (and controlled with a phasing control — both step and continuously variable attenuation for setting the output signal to the desired level — a convenient instrument stand-by position — vernier drive of both oscillator and marker tuning condensers — and blanking for establishing a single trace with base reference level. Make your work easier, save time, and repair with confidence — order your Heathkit TV Alignment Generator now!

Model TS-2
Shipping Wt. 20 lbs.

\$39.50

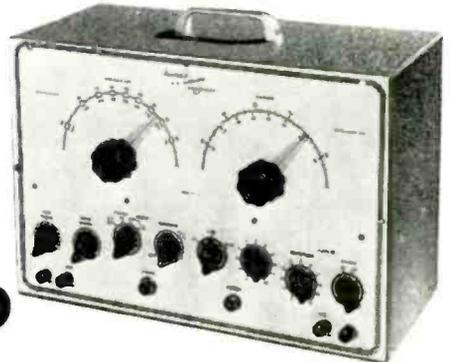


YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CABLE: ATLAN-N.Y.

The **HEATH COMPANY**

... BENTON HARBOR 20, MICHIGAN

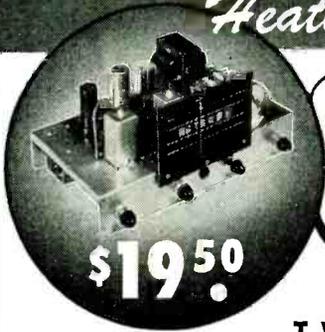Heathkit RECEIVER & TUNER KITS for AM and FM



Model BR-1 Broadcast Model Kit covers 550 to 1600 Kc. Shipping Wt. 10 lbs.

\$19⁵⁰




Model AR-1 3 Band Receiver Kit covers 550 Kc. to over 20 Mc. continuous. Extremely high sensitivity. Shipping Wt. 10 lbs.

\$23⁵⁰

TWO HIGH QUALITY *Heathkit* SUPERHETRODYNE RECEIVER KITS

Two excellent Heathkits. Ideal for schools, replacement of worn out receivers, amateur and custom installations. Both are transformer operated quality units. The best of materials used throughout—six inch calibrated slide rule dial—quality power output transformers—dual iron core shielded. I.F. coils—metal cased filter condenser. The chassis has phono input jacks. 110 Volt output for phono motor and there is a phono-radio switch on panel. A large metal panel simplifying installation in used console cabinets is included. Comes complete with tubes and instruction manual incorporating pictorials and step-by-step instructions (less speaker and cabinet). The three band model has simple coil turret which is assembled separately for ease of construction.

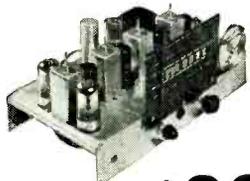

Model FM-2
Ship. Wt. 9 lbs.

\$22⁵⁰

TRUE FM FROM *Heathkit* FM TUNER KIT

The Heathkit FM Tuner Model FM-2 was designed for best tonal reproduction. The circuit incorporates the most desirable FM features—true FM.

Utilizes 8 tubes: 7E5 Oscillator, 6SH7 mixer, two 6SH7 IF amplifiers, 6SH7 limiter, two 7C4 diodes as discriminator, and 6X5 rectifier.

The instrument is transformer operated making it safe for connection to any type receiver or amplifier. Has ready wound and adjusted RF coils, and 2 stages of 10.7 Mc IF (including limiter). A calibrated six inch slide rule dial has vernier drive for easy tuning. All parts and complete construction manual furnished.



MAIL TO THE
HEATH COMPANY
BENTON HARBOR 20,
MICHIGAN

ORDER BLANK

From _____

- SHIP VIA
- Parcel Post
 - Express
 - Freight
 - Best Way

Quantity	Item	Price	Quantity	Item	Price
	Heathkit Oscilloscope Kit — Model O-7			Heathkit H.V. Probe Kit — No. 336	
	Heathkit VTVM Kit — Model V-5			Heathkit R.F. Signal Gen. Kit — Model SG-6	
	Heathkit FM Tuner Kit — FM-2			Heathkit Condenser Checker Kit — Model C-2	
	Heathkit Broadcast Receiver Kit — Model BR-1			Heathkit Handitester Kit — Model M-1	
	Heathkit Three Band Receiver Kit—Model AR-1			Heathkit Power Supply Kit — Model PS-1	
	Heathkit Amplifier Kit — Model A-4			Heathkit Resistance Decade Kit — Model RD-1	
	Heathkit Amplifier Kit — Model A-6 (or A-6A)			Heathkit Impedance Bridge Kit — Model IB-1B	
	Heathkit Tube Checker Kit — Model TC-1			Heathkit A.C. VTVM-KIT — Model AV-1	
	Heathkit Audio Generator Kit — Model AG-7			Heathkit Intermodul. Analyzer Kit—Model IM-1	
	Heathkit Battery Eliminator Kit — Model BE-2			Heathkit Audio Freq. Meter Kit — Model AF-1	
	Heathkit Electronic Switch Kit — Model S-2			Heathkit Square Wave. Gen. Kit — Model SQ-1	
	Heathkit T.V. Alignment Gen. Kit — TS-2				
	Heathkit Signal Tracer Kit — Model T-2				
	Heathkit R.F. Probe Kit — No. 309				

On Parcel Post Orders, include postage for weight shown and insurance. (We insure all shipments.)

On Express Orders, do not include transportation charges—they will be collected by the Express Agency at time of delivery.

Enclosed find Check Money Order for _____

Please ship C.O.D. Postage enclosed for _____ lbs.

ALL PRICES SUBJECT TO CHANGE WITHOUT NOTICE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th St.
NEW YORK CITY (16)
CABLE: ARLAS N.Y.

The HEATH COMPANY

... BENTON HARBOR 20, MICHIGAN

RADIO-ELECTRONICS for

give the gain of the amplifier in decibels by the formula:

$$db = 10 \log_{10} \times \text{power ratio.}$$

A decibel chart

Rather than go to the trouble of finding the *log* and working this out the hard way, the chart of Fig. 6 is supplied to make it simple. Locate the power ratio on the upper scale and read opposite it the gain in db. For power ratios, read the upper set of db figures. For the example we have chosen, the power ratio is 21 divided by .00004, or 525,000 to 1. Find 525,000 on the second scale and read opposite it approximately 57.3 db. The gain of the amplifier is 57.3 db. For convenience, the equivalent values of powers of ten are shown in Table I.

If the amplifier has the same impedance at both input and output, such as the 600 ohms used commonly in line amplifiers, the task of determining gain is considerably simpler. The gain of such an amplifier can be figured from the ratio of the *voltages* appearing across the input and output without converting to power ratios. Using the same setup as shown in Fig. 5, measure the two voltages. Divide the larger voltage by the smaller one. This data can be used to determine gain by the formula:

$$db = 20 \log_{10} \times \text{voltage ratio.}$$

Again, instead of working it out, refer to Fig. 6. Using the lower set of db figures, read the gain opposite the voltage ratio. For example, if the voltage across the input is 1 volt and the voltage across the output is 200, the voltage ratio is 200/1 or 200. Locating this ratio in the chart will show a gain of 46 db opposite the ratio.

The over-all fidelity of the amplifier can be measured by plotting the gain as measured by these methods at a number of frequencies. For example, plot the gain at:

100 cycles	1,000 cycles	7,000 cycles
300	1,500	10,000
500	3,000	15,000
700	5,000	20,000

The variations in gain in db with reference to the gain at 1,000 cycles indicate the over-all fidelity of the system.

As indicated briefly in this article, the uses of the v.t.v.m. in servicing and designing public address systems are many. The enterprising service technician can use it to determine the effectiveness of negative feedback, the response and gain of amplifiers, stages or transformers, to measure hum, measure the effectiveness of bypass and coupling capacitors, measure power output, and for other needs.

Table I

Powers of Ten	Numerical Value
10 ¹	10
10 ²	100
10 ³	1,000
10 ⁴	10,000
10 ⁵	100,000
10 ⁶	1,000,000
10 ⁷	10,000,000
10 ⁸	100,000,000
10 ⁹	1,000,000,000
10 ¹⁰	10,000,000,000
10 ¹¹	100,000,000,000
10 ¹²	1,000,000,000,000

—end—

KON-TIKI

Thousands read the best-seller! Millions have seen and will see the thrilling movie!

NATIONAL

SW-54
\$49⁹⁵

by the makers of professional radio
equipment for the

greatest adventure of our time!

Despite 101 days of salt spray and even total immersion, a National transmitter and receiver kept the world-famed Kon-Tiki Expedition in touch with the world! Now the same rugged dependability is yours in the amazing SW-54, the "Mighty Midget" broadcast and shortwave receiver (540 kcs. to 30 mcs.). Measures only 11" x 7" x 7". Write for details and name of nearest supplier!



TV CONVERSION ARTICLES APPEARING IN PAST ISSUES OF R-E

Replacing Picture Tubes in Television Receivers	Oct., 1949, p. 28
Revamping a 630-Type TV Set	Jan., 1950, p. 38
Big-Tube Conversions are Profitable	Jan., 1951, p. 50
Video Slave for Remote Televiewing	April, 1951, p. 24
Converting to Bigger TV Tubes	May, 1951, p. 24
Slave Unit Simplifies 7-inch Conversion Jobs	Aug., 1951, p. 22
Special Problems in TV Conversions	Aug., 1951, p. 26
Profitable Conversions with Rectangular Tubes (Part I)	Aug., 1951, p. 28
Profitable Conversions with Rectangular Tubes (Part II)	Sept., 1951, p. 22
TV Conversion Components	Aug., 1951, p. 30
Conversion—A Practical Approach	Sept., 1951, p. 24

Safety First and TV Antennas

The need for forethought and care in TV antenna installations is dramatically illustrated in the photos

SAFETY precautions often take second place to signal strength when a television antenna is installed. The accompanying photographs show that "safety first" is just as applicable to television antennas as to any of the other appliances and equipment with which we have to live. Even less excusable are the cases where an antenna is installed dangerously because of carelessness or the pure ignorance and incompetence of inexperienced workers.

The antenna pictured in Photo A was mounted on a tall pole and not properly guyed. A moderate storm was sufficient to cause it to fall into the electric wires running past the house. Considerable damage was done to the side of the building, as shown in Photo B, and the lady of the house was severely burned on the face and arms as she was standing in front of the sink in Photo C. (Investigators believe the current was trying to reach ground through a path from the sanitary stack vent pipes to the water pipes, causing the flashover at the sink.)

These photographs are the highlights of a booklet published by the National Fire Protection Association of 60 Battery March St., Boston, Mass., and illustrate only one of the ways that hazards of death may be introduced into a television antenna installation. Next to mechanical risks, such as attaching to chimneys in such a way that antenna and chimney are likely to come down together in the next severe storm—lightning is probably the greatest danger. Arresters and ground wires are very frequently so installed as to make them useless or worse. For example, "grounding" to the top of a sanitary stack vent pipe may result in serious life and fire hazards. Arresters can be so installed as to give adequate protection, or in such a way as to be almost useless, or even to expose at least the receiver to severe damage. The booklet, which sells at 25¢, is well worth the attention of all television installation men and television service contractors.

—end—

RADIO-ELECTRONICS for

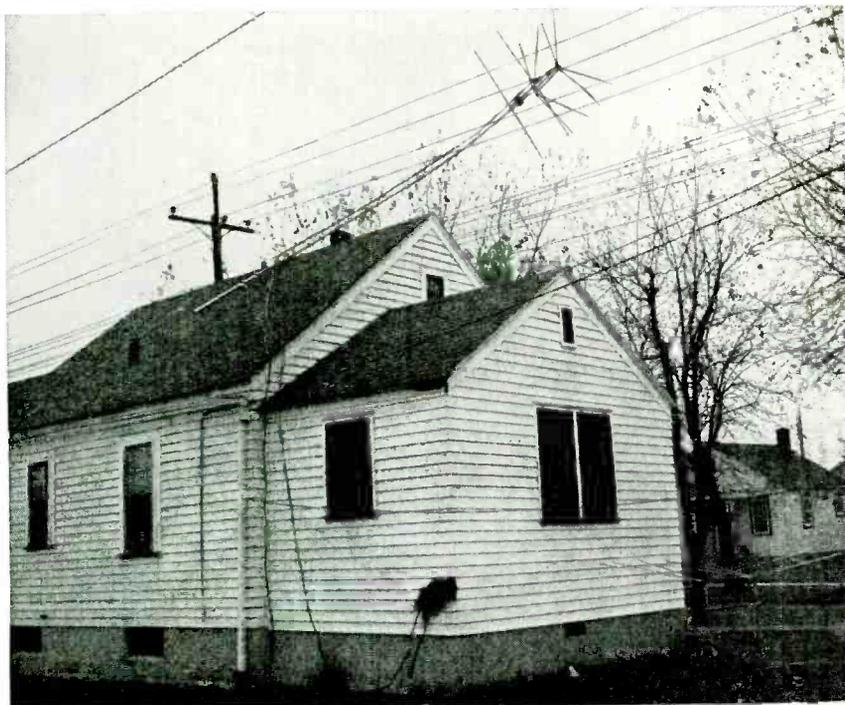


Photo A—Inadequate guying, despite its height and weight-adding rotator, caused this mast to fall across power wires, causing both injury and damage.

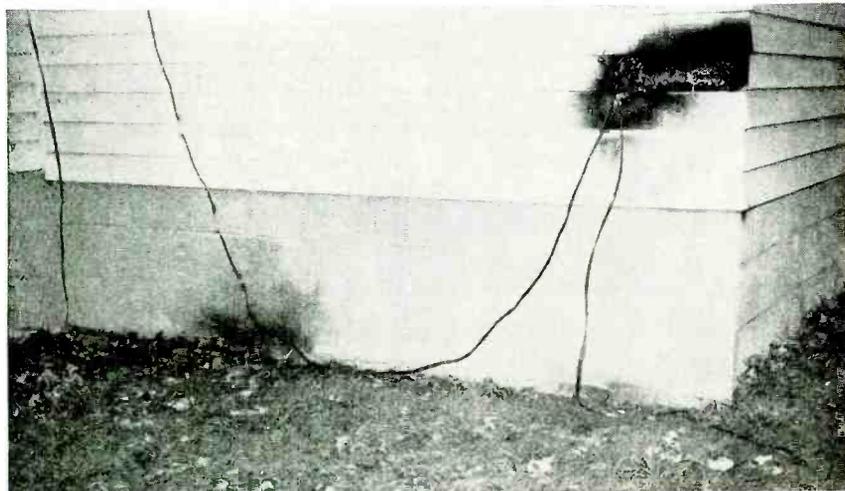


Photo B—Building narrowly escaped fire. Line at right is rotator control cable.

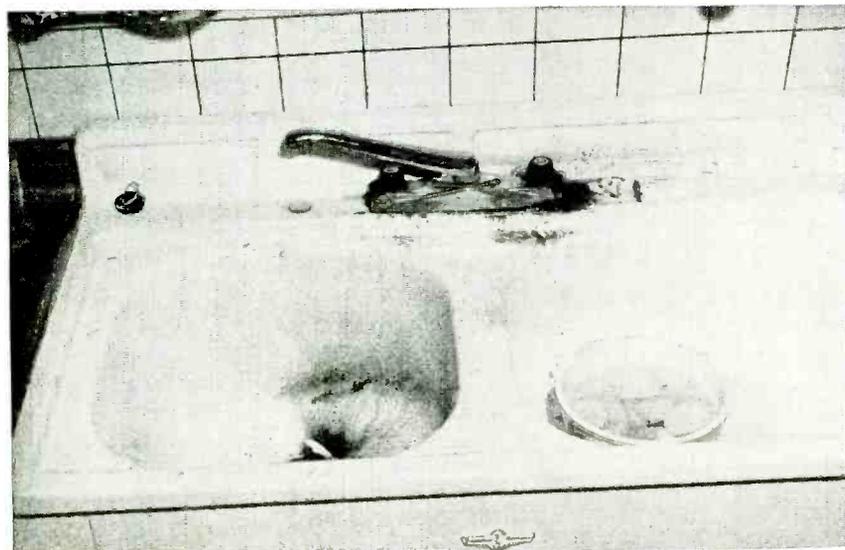


Photo C—Where injury took place. Flashover could well have had fatal results.

All photos courtesy National Fire Protection Association

Use Wire Tables In Service Work

By VERGNIAUD H. RICHARD

Many service technicians believe that the only information they can get out of a wire table is that relative to sizes, current-carrying capacities, and types of insulation of wires for coil and transformer design. The wire table, they feel, was made up originally for electricians and only mere gleanings are useful to the radioman. A great deal more can be gotten out of wire tables. How much depends entirely upon the kind of table used and the ingenuity of the service technician.


The helpful wire table gives, in addition to the usual data (gauge number, diameter in mils, circular mils area, type of insulation, current-carrying capacity, feet per pound), turns per linear inch and per square inch and ohms per 1000 feet for the different sizes of wires and types of insulation. The following are some cases in which the table will come in handy for computations and calculations:

1. We have on hand a 0-1 ma meter whose range is to be increased to 10 milliamperes. Upon calculation, we find that the required shunt must have a resistance of 3 ohms. The uninventive man will be stuck if he does not have some resistance wire, whereas if he consults a good wire-table he will be rewarded for his investigation. Assume further that we find in the usual junk box some No. 38 enamel wire. The table reveals that 1,000 ft. of No. 38 wire has a resistance of 672.6 ohms. The resistance being proportional to the length, our shunt is then: $1000 \times 3/672.6 = 53 \frac{17}{32}$ inches long. Now we must find out if our wire is capable of carrying the 9 milliamperes without undue heating. Upon consultation the table says O.K. and there is our shunt. (The nearer the maximum current-carrying capacity of the wire is to the required ma range, the less bulky will be the shunt.)

2. Having a certain quantity of wire of unknown size taken from an old transformer, we decide to use it to build a coil. How can we find the wire size, no micrometer and no wire gauge being handy? Here again the table comes to the rescue. All we have to do is to wind, closely, enough turns on a pencil or other convenient dowel to fill in one inch (previously marked off). Suppose we find x turns and our wire is enamel coated. The wire table will specify that the enamel wire whose turns per linear inch amount to x is No. y . If the wire is very fine, some convenient fraction of an inch should be chosen to save time and avoid eye strain and confusion.

(The technician or experimenter may wish to build up a library of pieces of

SENSATIONAL RESULTS!

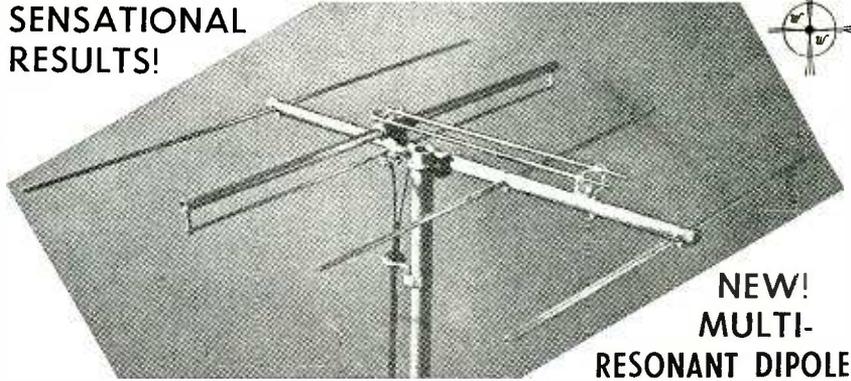

**NEW!
MULTI-
RESONANT DIPOLE**
PAT. PENDING

THE ONLY TRUE

COMBINATION YAGI ANTENNA

Now! for the first time—a TV antenna with all these powerful advantages.

- Just a few Yagi antennas cover the entire high and low bands.
- All the elements work in their true fashion and do not double in purpose, such as a driven element acting as a parasitic with a loss of efficiency.
- When the multi-resonant dipole is incorporated in the Yagi antenna as a driven element the antenna assumes the aspect of two or more separate Yagi antennas in one.
- It eliminates troublesome and frequency sensitive phasing lines.
- It can be peaked in performance to any number of channels if desired, since it is not restricted to just a few channels as is the case of modified designs.
- In relation to size and gain, it is unequalled.
- It is light, rigid, and easy to install.


The following models and their peaked channels are K-36 (channels 3 & 6); K-45 (channels 4 & 5); K-79 (channels 7 & 9); K-113 (channels 11 & 13). This antenna also responds to adjacent channels. Additional channels combinations can be made with the same outstanding features, to meet the requirements of almost any territory.

The Multi Resonant Dipole Combination Yagi Antenna is the only true answer to difficult reception problems. Order today from your jobber or write for prices and descriptive folder.

WELLS & WINEGARD TELEVISION ACCESSORY MFGS.
BURLINGTON, IOWA

THE JUNIOR SUPER-METER

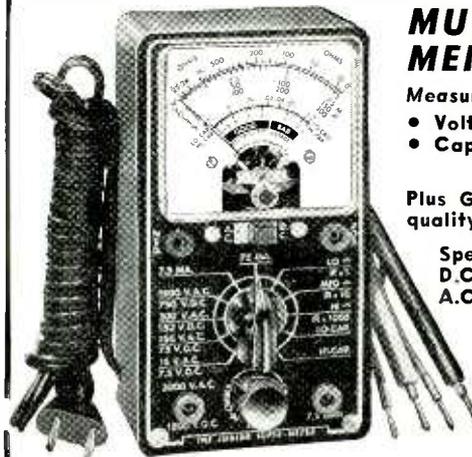THE MOST COMPLETE AND COMPACT MULTI-SERVICE INSTRUMENT EVER DESIGNED!



Measures:

- Voltage
- Current
- Resistance
- Capacity
- Reactance
- Inductance
- Decibels

Plus Good-Bad scale for checking the quality of electrolytic condensers.

Specifications:

- D.C. Volts: 0-7.5/75/150/750/1500 Volts.
- A.C. Volts: 0-15/150/300/1500/3000 Volts.
- Resistance: 0-10,000/100,000 ohms. 0-10 Mgms.
- D.C. Current: 0-7.5/75 Ma. 0-7.5 amps.
- Capacity: .001 Mfd.—2 Mfd. .1 Mfd.—20 Mfd.
- Electrolytic Leakage: Reads quality of electrolytics at 150 Volt test potential.
- Decibels: -10 Db. to +18 Db. +10 Db. to +38 Db. +38 Db. to +58 Db.
- Reactance: 15 ohms—25 K ohms 15 K ohms—2.5 Megohms.
- Inductance: .5 Henry—50 Henries 30 Henries—10 K Henries.

Handsome round cornered molded bakelite case 3 1/8" x 5 7/8" x 2 1/4" complete with all test leads and instructions.

\$21.40

SOLD ON EASY PAYMENTS AT THE NET CASH PRICE

No interest or carrying charges added. Simply remit \$5.40 with order, pay balance \$4.00 per month for four months.

MOSS ELECTRONIC DIST. CO., INC.

Dept. B-8, 38 Murray St., New York 7, N. Y.



Like the proverbial mouse trap, a better ion trap is bound to be popular. INDIANA'S E-ZEE-ON Ion Traps are better too. Servicemen like them because E-ZEE-ON can be slipped on the tube neck and adjusted in seconds with just one hand. There's no manual clamp—just one compact piece of permanently magnetized Cunife that grips snug and stays put.

E-ZEE-ON provides an even magnetic field pattern that results in brighter, more uniform picture definition. They fit any picture tube neck and function efficiently on large and small tubes. E-ZEE-ON Ion Traps are ideal for servicing older sets or for conversion jobs. They are already standard equipment on many new TV sets.

EASY TO CARRY

Each E-ZEE-ON Ion Trap is protected in a compact package that takes but little space in your service kit. An instruction sheet is included with each unit.

Your jobber now has these better ion traps; look for the colorful E-ZEE-ON counter-top display carton. Write for descriptive folder. E-ZEE-ON Ion Traps are made by the world's largest producer of permanent magnets . . .



THE INDIANA STEEL PRODUCTS COMPANY

Specialists in Packaged Energy Since 1908

VALPARAISO, INDIANA

wire of known sizes, either discovered by the method above or taken from a marked spool. These can be cemented at one end to a piece of white card and wire of unknown size calibrated by holding it parallel and close to the known pieces for comparison. It is surprising how much difference there is between No. 36 and No. 38 when both are held close together.—*Editor*)

3. Coils in the high-frequency stages of receivers usually have such low resistance as to be continual puzzles to the service technician unless he has a diagram of the set with these resistances indicated. In close-wound single-layer coils the problem is solved without a circuit drawing. First the size of the wire is found as above, by measuring the length of the coil and counting the number of turns. The next step is to calculate the length of the wire by multiplying the circumference of the coil by the number of the turns. This done, we refer again to the table which gives us the resistance per 1,000 feet for that size of wire, and compute the ohmic value for the given length. The result is then compared with the ohm-meter's reading and we have an exact idea of the coil's condition.

4. The table is again useful in replacing filament, bleeder, cathode, and other resistors of low values. Calculate the resistance and wattage required. The necessary data are the following: voltage of the source, voltage and current ratings of the load. It is understood, naturally, that the source is able to furnish the required energy. The resistance being calculated according to Ohm's law, the next step is to find what size wire is capable of handling the amperage without overheating. Then the length is easily computed.

5. The wire table and a quantity of wire of small sizes may help—in an emergency—to recalibrate cheap instruments using carbon resistors. If the original resistors are burned out or are far from their original values, the wire-wound calibrating resistors should be used in their stead.

6. The table again can help find the internal resistance of meters. Carbon resistors being unreliable on account of their tolerances, wires of sufficient resistance are preferable. Use is then made of the formula:

$$R_m = R_s \times n - 1,$$

where R_m = the internal resistance of the meter that it is required to find, R_s = the resistance of a piece of wire calculated with the the help of the table, and n = the number of times that the meter's reading is multiplied. If a piece of wire is cut which will exactly double the meter reading, $n = 2$, and R_s then equals $2 - 1$ (in other words, has the same resistance as the meter).

(Wire also has a certain tolerance in its manufacture, especially in the smaller sizes, therefore precision results are not to be expected from calculated wire resistors. Shunts of copper wire should be of a wire large enough to avoid heating in normal use. The resistance of copper changes appreciably with heat.—*Editor*)

—end—

OPPORTUNITY AD-LETS

Advertisements in this section cost 35c a word for each insertion. Name, address and initials must be included at the above rate. Cash should accompany all classified advertisements unless placed by an accredited advertising agency. No advertisement for less than ten words accepted. Ten percent discount six issues, twenty percent for twelve issues. Objectionable or misleading advertisements not accepted. Advertisements for Feb. issue must reach us not later than December 21, 1951. Radio-Electronics, 25 W. Broadway, New York 7, N. Y.

DO 1/4" SHEET METAL SCREWS GIVE YOU TROUBLE? Our special 1/4" Driver Wrench fits those undersize 1/4" heads. Ppd. \$1.00. Benson, 749 Palisade Ave., Yonkers 3, N. Y.

WE REPAIR, EXCHANGE, SELL ALL TYPES OF electrical instruments, tube checkers and analyzers. Hazleton Instrument Co. (Electric Meter Laboratory), 140 Liberty Street, New York, N. Y. Telephone—BArclay 7-4239.

"ELECTRONIC CALCULATORS", "ELECTRONIC Mathematics", "Audio Engineering", data sheets 50¢

each or 3 for \$1 postpaid. Technical Question Answering Service \$1 per letter. Willard R. Moody, Consulting Electronics Engineer, 5705 Carters Lane, Riverdale, Maryland.

WANTED: THE FOLLOWING SETS, PARTS OR Equipment associated with: BC-611 Handle-Talkies; ARC-1; ARC-3; ARN-7; BC-342, 312; R-89B/ARN-5; T-47, 47A/ART-13 & Dynamotor; F-21/ARA-9 Audio Filter; RT-TA/APN-1; APN-2; APN-9; BC-348; MG-149; BC-733D; BC-966A; DM-32A; BC-453B; CRT-3; SCR-529; plus all types test equipment. Top Dollar paid. Write: ROBERT SANETT, 4668 Dockweiler, Los Angeles, California.

RG-8-U, RG-11-U, RG-59-U COAXIAL CABLE. ANY lengths, any quantities. Write: Television Service Co., 249 North 48 St., Lincoln, Neb.



AMATEURS—RADIO ENGINEERING QUESTIONS Answered \$1.00 With Schematics \$2.50. Henry Twillmann, R. R. #1, Chesterfield, Missouri.

TV AND FM ANTENNAS, YAGI BEAMS, STACKS, Mounts, wire, accessories. Wholesale Supply Co., Lunenburg 2, Mass.

You can't beat
Radio-Electronics
for complete coverage of
RADIO, TELEVISION and AUDIO

Timer for Long Intervals

By FRED UPTON

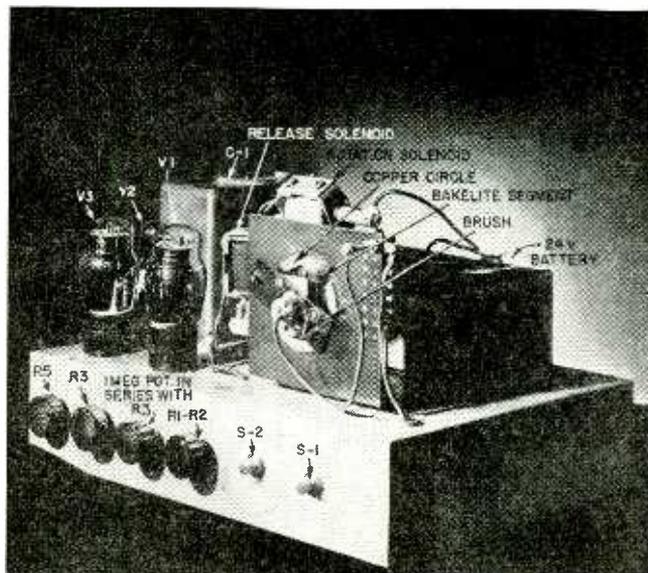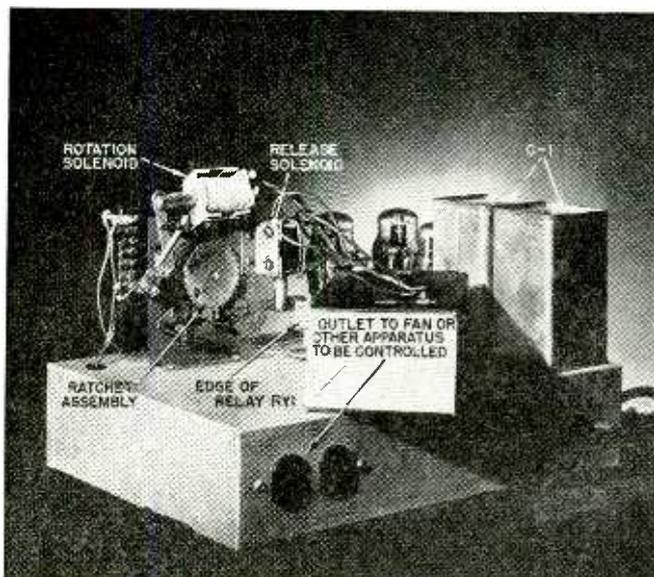

Rear of timer (left) shows ratchet relay on left and battery in foreground. Front view (right) shows the brush and commutator added to the relay. A second 43 tube replaced the 25Z5 (see Fig. 1) as a line dropping resistor on the 117-volt line.

IN ALMOST every home there is a use for a timing device such as this. The one I have constructed is used for cutting off a window fan after a definite time interval.

This eliminates an unnecessary, groping trip out of bed, and allows me to slumber undisturbed.

The timer is very simple and not very expensive. I used only three tubes in its construction. See Fig. 1. V3 could be omitted by substituting a 220-ohm resistor in place of R8. The timer can be set for intervals from a fraction of a second to approximately 25 minutes by adjusting R1, R2, R7, and R5.

V2 is used to obtain positive voltage for the plate and screen of V1 and negative voltage for charging C1 (two 8- μ f oil-filled, 600-volt capacitors wired in

parallel) and biasing the grid of V1 beyond cutoff. R5 varies the voltage supplied to the grid of V1.

The operation of the basic timer follows: When the grid of V1 is at zero or above cutoff the tube conducts, causing the relay RY1 to operate. The bottom contacts of RY1 close and a negative voltage is applied to the grid of V1 and C1 through R3. The time it takes to charge C1 to cutoff is dependent on the capacitance of C1, the resistance of R3, and the applied negative voltage as determined by the setting of R5. C1 should be a high-quality paper or oil-filled capacitor to minimize leakage. I used oil-filled capacitors because I had them on hand. As soon as C1 has charged to a negative voltage sufficient to cutoff V1, RY1 releases and the top

contacts close. A 40- μ f electrolytic capacitor (C4) was used across the RY1 winding to prevent chatter. The negative charge on the grid of V1 leaks off through R7, R1, R2, hence their value (in addition to the settings of R3 and R5) determine the timing interval. For greater control, another 1-meg pot was added in series with R3. It appears in the photo but not the schematic.

RY2 is a ratchet-type relay. It cuts off the current to the electric fan and inactivates the timer after a predetermined number of pulses. When the relay RY1 is operated it closes the battery circuit to the rotation solenoid, causing it to operate and remain operated until RY1 releases. This causes the ratchet assembly to move forward one step for each timed interval (which I have set

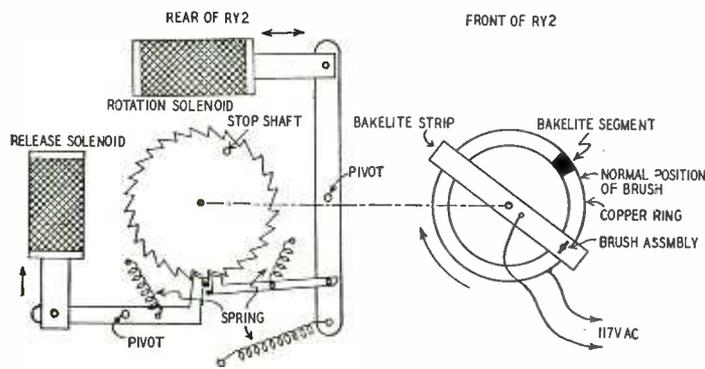
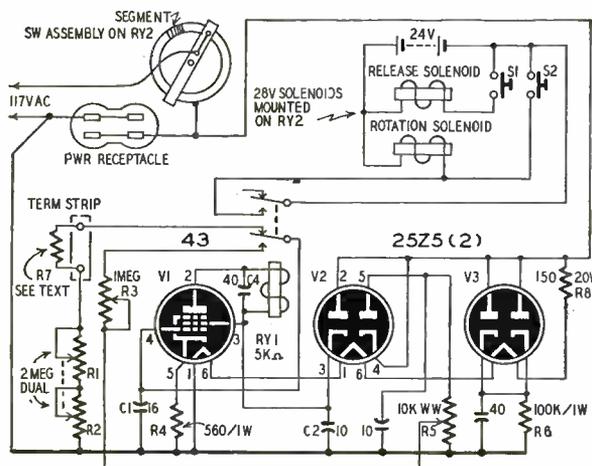


Fig. 1—Timer diagram. To omit V3, change R8 to 220 ohms. Fig. 2—Drawings showing construction of ratchet relay.

Snyder
PHILADELPHIA

YEARS AHEAD

Directronic
MOTORLESS
TV AERIAL SYSTEMS

360° ELECTRONICALLY SWITCHED BEAM

GIVES SAME CLEAR PIX AS MOTOR
DRIVEN AERIALS AT $\frac{1}{3}$ THE COST

SIMPLE FLICK OF SWITCH
CLEARS PICTURE **INSTANTLY**
NO WAITING

OPENS BIGGEST
REPLACEMENT MARKET
IN **TV** HISTORY

FREE

T

TENNA TIPS

PRICE 50¢

MAIL THIS COUPON TO-DAY!



SNYDER MFG. CO.
23rd & Ontario Sts., Phila. 40, Pa.

Please send me free copy of authoritative
booklet **TENNA TIPS** on Directronic and
all other types of aerials, plus catalogs.

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

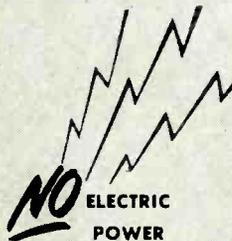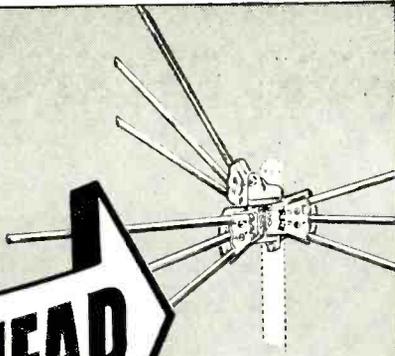

for 20 minutes in my case by using 40 megohms of resistance as R7). There are 27 step positions on this relay and 26 twenty-minute intervals allow a timing period of almost nine hours. The twenty-seventh notch is aligned with the bakelite segment of the ring assembly used to cut off the a.c. supply. The release solenoid is used to prevent the ratchet assembly from returning to normal except when the solenoid is energized. When it is energized by pressing S1, the ratchet returns to normal through the action of a spring coil mounted on the assembly.

The switch assembly on RY2 uses a carbon or metal brush mounted on a bakelite strip firmly mounted to the other end of the ratchet wheel shaft. This is shown in Fig. 2. The brush presses against a copper circle from which a segment has been cut and replaced by bakelite. When the brush steps to the position of the bakelite the a.c. is cut off to both the fan and the timer. The a.c. remains off until S1 is pressed, operating the release solenoid, which in turn allows the spring coil mounted on the ratchet assembly to return the brush to normal, and the a.c. is again applied.

R3 and R5 should be set so that RY1 is held energized for only a short period of time since the rotation solenoid draws almost 3 amperes when operating. The relay in this particular unit operates for only a fraction of a second, and the battery has held up very well. A low-voltage, dry rectifier supply could easily replace the batteries. The relay RY2 is surplus but the copper circle and brush assembly is my own modification. The versatility of this equipment can be enhanced by additional copper rings cut into different segments. S2 is used to step the ratchet assembly to the desired position before the timing cycle starts. V3 is used primarily as a filament-dropping resistor, but may furnish useful plate power to some other piece of equipment. The complete assembly including battery space, was built on a 10 by 14-inch chassis.

Materials for timer

Resistors: 1—560, 1—100,000 ohm, 1 watt; R7 value as desired, 40 megohms for 20 minutes time interval, 1—150 ohm wirewound, 20 watts; (potentiometers) 1—10,000 wirewound, 2—1 megohm, 1—dual, 2 megohm.

Capacitors: 2—8 µf 600 volt, oil-filled (in parallel), 2—10 µf 150 volt electrolytic, 2—40 µf 150 volt electrolytic.

Relays: 1—ratchet relay to be used on 24 volt battery or other power source, 1—5,000 ohm plate coil d.p.d.t. throw.


Miscellaneous: 2—pushbutton switches s.p.s.t., 2—25Z5 tubes, 1—43 tube, dual female power receptacle, chassis, hardware, hookup wire, etc.

—end—

Gambling curbs are demanded in an FCC-sponsored bill under consideration by the Senate Interstate and Foreign Commerce Committee. The Commission bill would prohibit the publishing by newspapers and broadcasting by radio of betting odds and prices paid on any sporting event. FCC Chairman Wayne Coy in testimony before Congress indicated that "undue hardship" would result from adoption of the proposal of the Senate Crime Investigation Committee to license all carriers of sports information.

RADIO-ELECTRONICS for

ELECTROSTATIC PRECIPITATION

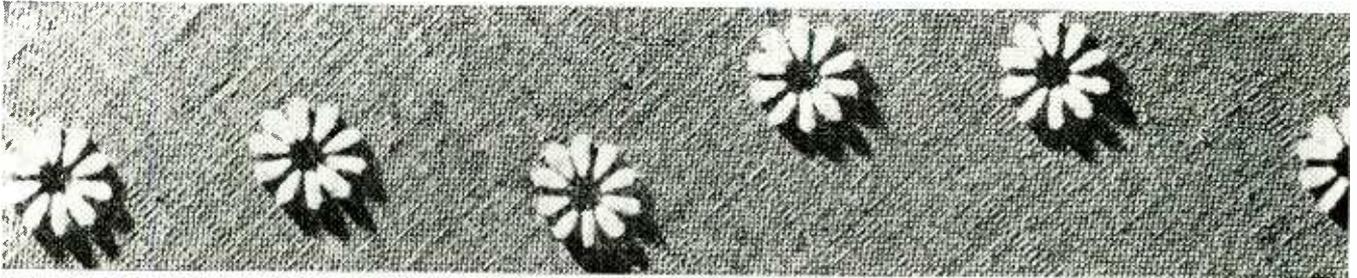

Sample of a fabric with raised design produced with short textile fibers in a precipitation process superior to weaving.

By ED BUKSTEIN

Using a principle known for thousands of years, the modern high-voltage precipitator is giving yeoman service in the home, industrial plant and hospital.

HOW cleanse the air of cigarette smoke particles though these particles may be less than a hundredth of a thousandth of an inch in diameter? How recover minute particles of valuable chemicals that might otherwise go up as waste through factory chimneys? How make a spray of paint follow curved paths so that it coats the back of the object to be painted? The solution is—electrostatic precipitation, a branch of industrial electronics dealing with the control of minute particles of matter.


Electrostatic attraction has been known for at least 25 centuries. Thales of Miletus, philosopher and mathematician of ancient Greece, observed that dried leaves and light straws were attracted to a piece of amber which had been rubbed with silk. Radio students have rubbed a glass rod with a piece of silk and noted that the glass attracts small bits of paper. A hard rubber comb, after being passed through the hair, likewise attracts paper.

These experiments are generalized in the well-known law of charges: like charges (two positives or two negatives) repel each other, and unlike charges attract. To control a small particle of matter it is necessary only to give that particle an electric charge. The particle will then be attracted to a collector plate bearing an opposite charge.

Service technicians are familiar with the phenomena in practical radio work. The face plate of a picture tube, if not sealed, collects dust. Dust also collects

on the high-voltage winding of the flyback transformer in TV sets. Both

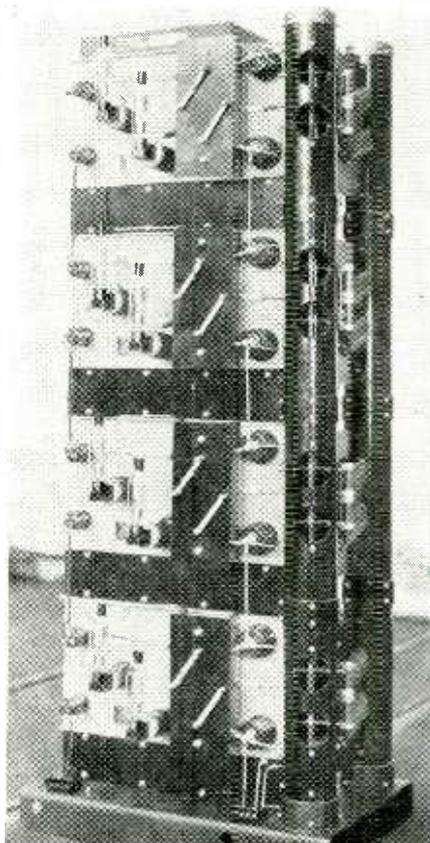of these conditions are caused by electrostatic precipitation.



A commercial two-stage precipitator.

Precipitation action

The underlying principle of electrostatic precipitation is illustrated in Fig. 1. The output of a high-voltage power supply is connected to a thin wire and a flat metal plate. Because of the high potential, the air around the wire is ionized. This is *corona discharge*; it appears as a faint glow around the *wire*. The air is thus broken down into positive and negative ions. The positive ions are attracted to the nearby wire, and the negative ions must travel across the gap to the plate. As a result, the space between the wire and the plate is filled with negative ions.

The air to be filtered is passed between the wire and the plate. Air-borne particles of dust, smoke, soot, etc., collide with the negative ions. They become charged. The *negatively* charged particles are then attracted to the *positive* plate, and the air emerges clean and ready for reuse. The collector plate is cleaned at regular intervals by rapping, washing, or scraping away the accumulated waste.

Pipe type (a) and plate type (b) precipitators (Fig. 2) are used in practice. The pipe type consists of a number of hollow cylinders with a thin wire running coaxially through each. Dust-laden air is passed through these cylinders, and the dust collects on the inner walls of the cylinders. The plate type

free send for it

212-PAGE
ALLIED Catalog

Everything in Radio, Television and Industrial Electronics

Allied Radio
431 WEST JACKSON BLVD. CHICAGO 7, ILLINOIS

the only complete up-to-date catalog for Everything in Radio, Television & Industrial Electronics

Send for the Buying Guide that's used daily by thousands of service technicians, engineers, Amateurs, sound men, builders and experimenters. Make your selections from the world's largest stocks of quality equipment—at lowest money-saving prices. Get every buying advantage at ALLIED—speedy delivery, expert personal help, and complete satisfaction on every order. Make ALLIED your single, dependable source for electronic supplies.

SEND FOR FREE CATALOG

ALLIED RADIO

ALLIED RADIO CORP., Dept. 2-AA-2
833 W. Jackson Blvd., Chicago 7, Ill.

Send FREE 212-Page ALLIED Catalog

Name _____
Address _____
City _____
Zone _____ State _____

consists of a number of flat metal plates with the wires spaced in between them. These plates can be arranged either horizontally or vertically, depending on the particular installation.

Commercial types

The precipitators in Fig. 2 are one-stage types and are used in small units such as those for the home. The two-stage precipitator, Fig. 3, is used in large, industrial installations. This type has two sections, the ionizer or dust charger and the collector cell.

The ionizer is made of thin wires spaced between larger diameter rods. Rods and wires are alternately negative and positive. The high voltage applied to the ionizer produces corona discharge and causes the air between the wires and the rods to become ionized. As the dust-laden air passes through this ionized region, its particles become positively charged.

The second section of the two-stage precipitator consists of two sets of oppositely charged plates. As the positively charged particles enter the collector cell, they are repelled by the positive plates and attracted by and adhere to the negative plates. Periodically, the plates of the collector cell are cleaned, either manually or automatically.

Power requirements

Depending upon its size and purpose, an electrostatic precipitator will require potentials from 10,000 to 100,000 volts. The current drain may range from 10 to 250 ma. Both electronic and mechanical rectifiers have been used in practice. The electronic types consist of conventional half-wave, full-wave, or voltage-doubler rectifiers. Voltage-doublers are sometimes cascaded when extremely high voltages are required.

The mechanical rectifier is a motor-driven switch which reverses the load connections at each reversal of the power-line polarity. The motor is a synchronous type to "keep step" with the line-voltage alternations. The mechanical rectifier is similar in appearance and function to the commutator of a d.c. generator.

In practice, electronic rectifiers are more popular than the mechanical types. This greater popularity results from the well-known advantages of the electronic rectifier. It is quiet in operation, it has no moving parts to wear out, and it does not generate noise

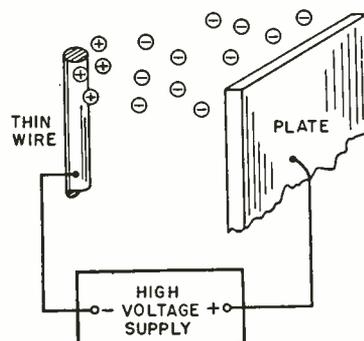


Fig. 1—The basic cell used in all units.

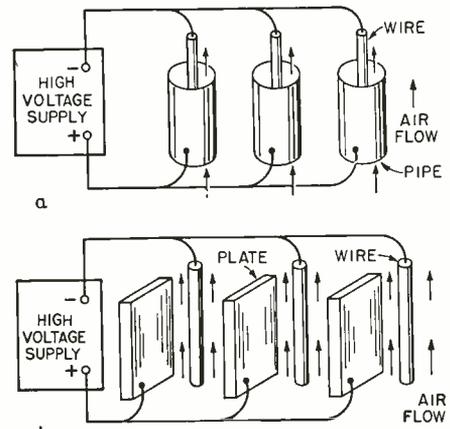


Fig. 2—One-stage type in home units.

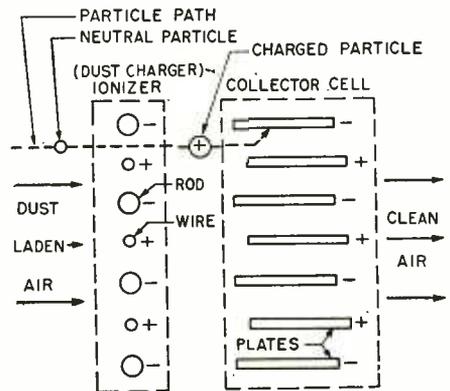


Fig. 3—Type of heavy duty two-stage unit used in industrial installations.

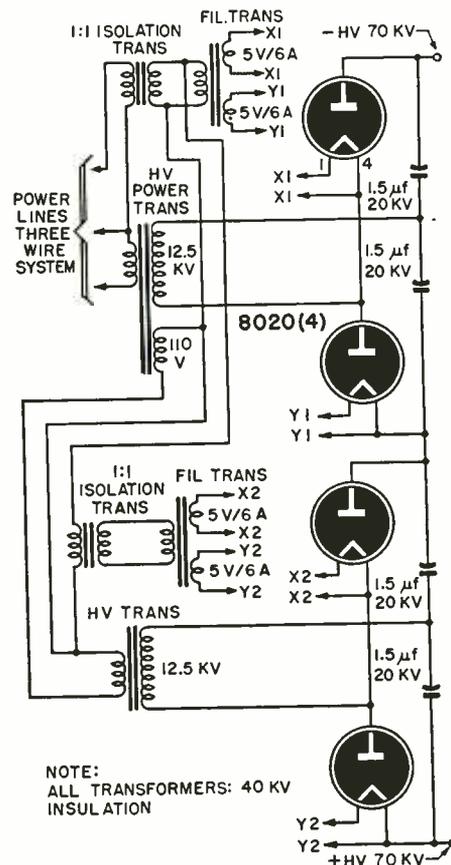


Fig. 4—Power supply for industrial unit employs cascaded voltage doubler.

voltages to interfere with radio reception. Fig. 4 is a simplified schematic of a two-unit cascade rectifier. Each unit is a voltage doubler and is rated at 35,000 volts, 30 milliamperes.

Nuisance abatement

No other practical system of air cleaning compares with the efficiency of electrostatic precipitation. It cleanses the air of particles as small as 1/250,000 inch in diameter, which would pass through ordinary mechanical filters. Electrostatic air filters trap over 90% of the air-borne particles; mechanical systems operate at about 10 to 20% efficiency. Commercially available precipitators range in capacity from the 1,200 cubic-feet-per-minute home unit, to the larger industrial types capable of handling 40,000 cubic feet of air per minute.

Electrostatic precipitators are often used to remove particles of cigarette smoke. In night clubs, restaurants, offices, and homes, this produces a healthier and more pleasant atmosphere. It also reduces laundering, cleaning, and decorating costs. Curtains, draperies, and furniture remain fresh and clean for longer periods, and mirrors and glassware do not become clouded with the familiar blue haze.

Industry has often adopted the electrostatic dust and smoke eliminator as an aid to better public relations. Many communities have instituted nuisance abatement ordinances and will not issue building permits for cement plants, blast furnaces, refineries, etc. unless electrostatic precipitation is included in the plans.

Precision industry

Some industries require a dust-free atmosphere as essential to the quality of the product. In the manufacture of delicate watch movements or electrical instruments, for instance, microscopic particles of dust can produce wear and inaccuracies. Manufacturers of photographic film, precision optical instruments, electron tubes, drugs and pharmaceuticals, and many other products employ electrostatic precipitators.

In machine shops and other industrial plants employing high-speed machinery, large quantities of oil coolant are used. Friction-generated heat transforms the liquid coolant into mist-fine particles of oil suspended in the air. This oil mist covers windows and lighting fixtures, cutting down illumination. It attacks the rubber insulation on electrical wiring. It makes pulley belts slippery, and it coats the floor with a slippery film. Electrostatic precipitation has successfully solved the oil-mist problem. Not only is the nuisance of oil-mist eliminated, but the reclaimed oil can be used over again.

Food products

Food product manufacturers find improved quality and reduced wastage results when electrostatic precipitation is used. In the manufacture of powdered milk, for instance, the elimination of

JANUARY, 1952

"CONICAL-V-BEAMS" REGISTERED TRADE MARK

Keep in Step

WITH

ANTENNA PROGRESS


-INSTALL *Telrex*

"CONICAL-V-BEAMS"

for finer TV performance in every type of signal area!



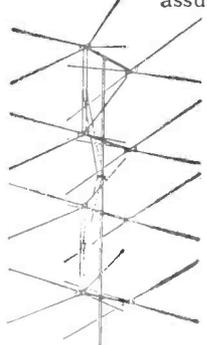Near or far, you can rely on Telrex "Conical-V-Beams" for full audio and video bandpass, high gain and high signal to noise ratio. Telrex quality of construction assures a lasting installation, full customer satisfaction and a minimum of service callbacks. Don't settle for less than the best! Check with Telrex on your next antenna requirements. Write for latest catalogs.



TELREX MODEL 8X-TV Famous for high gain. Will out-perform any other type antenna. "If the 8X-TV does not provide a usable signal, TV reception is impractical."

"CONICAL-V-BEAMS" are produced under Re-issue Patent No. 23,346

THE SKILL TO DESIGN..
THE FACILITIES TO PRODUCE..
THE ABILITY TO DELIVER

Telrex INC.

CONICAL-V-BEAMS

AMERICA'S STANDARD OF COMPARISON

ASBURY PARK 9, NEW JERSEY

Over 43,000 Technicians Have Learned

HOW TO GET THE MOST OUT OF BASIC TEST EQUIPMENT

Why Not You, Too?

SERVICING by SIGNAL SUBSTITUTION


A BEST SELLER FOR OVER 9 YEARS! (NEW, UP-TO-DATE, 12TH EDITION)

The Simple, Modern, Dynamic Speed Approach To Receiver Adjustment and Alignment Problems, AM-FM-TV.

- Nothing complex to learn
- Universal — non-obsolescent
- No extra equipment to purchase
- Employs Only Basic Test Equipment

Ask for "S.S.S." at your local Radio Parts Jobber or order direct from factory.

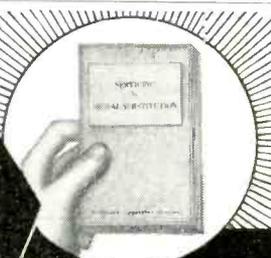
PRECISION APPARATUS COMPANY, INC. 92-27 Horace Harding Blvd., Elmhurst 4, N. Y.



only 40¢

100 pages. Invaluable information that will help you re-double the value of your basic test equipment.

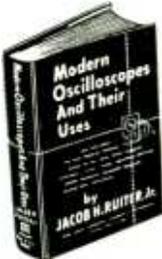NOW YOU'LL Really Know How to Use 'Scopes!



Don't let the oscilloscope "stump" you! Learn to use it fully on all sorts of jobs—and watch your efficiency soar!

MODERN OSCILLOSCOPES AND THEIR USES

BY JACOB H. RUITER, Jr.
of Allen B. DuMont Laboratories, Inc.
326 pages, 370 illustrations, \$6.00

Here at last is a book that makes it easy for you to become expert in the many uses of the greatest, most versatile service instrument of all—the oscilloscope! It contains no involved mathematics. First, the author explains oscilloscopes fully—then gets right down to earth in telling exactly how to use them on AM, FM and TV service work . . . from locating receiver troubles to aligning and adjusting the most complicated circuits.

HOW THEY WORK

Expert knowledge of oscilloscopes helps you work faster, far more accurately and more profitably on all sorts of service and laboratory jobs. Basic subjects covered include:

- 1—Introduction to Oscilloscopes; 2—History of the Oscillograph; 3—Development of the Cathode Ray Tube; 4—Principles of Cathode Ray Tube Operation; 5—Details of the Modern Cathode Ray Tube; 6—The General-Purpose Oscilloscope; 7—Power-Supply Circuits; 8—Amplifiers, Attenuators and Positioning Circuits; 9—Time-Base Circuits.

HOW TO USE OSCILLOSCOPES ON ALL TYPES OF JOBS

Each operation is carefully explained including the making of connections, adjustment of circuit components, setting the oscilloscope controls and analyzing patterns. About 400 illustrations including dozens of pattern photos make things doubly clear. Here are the specific how-to-do-it subjects covered: 10—Operation; 11—Interpretation of Basic Patterns; 12—Auxiliary Equipment; 13—Typical Applications in Electronics; 14—Servicing A-M Receivers; 15—Servicing F-M Receivers; 16—Television Receiver Servicing; 17—Use of the Radio Transmitter; 18—Using the Oscilloscope in Teaching; 19—Additional Industrial Uses; 20—Photographing Cathode Ray Tube Patterns; (a) Glossary. **Send coupon today!**

READ IT 10 DAYS . . . at our risk!

Dept. RE-12, RINEHART BOOKS, Inc., Technical Division, 232 Madison Avenue, New York 16, N. Y.

Send MODERN OSCILLOSCOPES AND THEIR USES for 10-DAY FREE EXAMINATION. If book is satisfactory, I will then send you \$6.00 promptly in full payment. If not, I will return book postpaid in good condition and owe you nothing.

Name.....
Address.....
City, Zone, State.....
Employers' Name and Address.....

Price outside U.S.A. \$6.50, cash only. Money back if you return book within 10 days.

bacteria-laden dust helps the product withstand extreme temperatures. Geographical distribution is thus greatly extended. Meat packers have solved the problem of moldy bacon by eliminating air-borne bacteria from the slicing rooms. In breweries, precipitation equipment prevents mold spores from entering the fermentation vats.

Material recovery

Nuisance abatement is not the only reason for the use of precipitation equipment in industrial plants. In many cases, the recovered particles are of considerable value. This is particularly true in smelting and refining plants. Particles of gold, silver, cadmium, lead, mercury, etc., that might otherwise be lost as chimney waste are reclaimed and used again. Single precipitator installations have recovered as much as \$1,000,000 a year.

Spray painting

In the field of spray painting, electrostatic precipitation has effected many advantages in quality and economy. The object to be painted is connected to the positive terminal of a high-voltage power supply. The negative terminal is connected to a screen mesh containing many sharp points to aid corona discharge.

Paint particles sprayed into the electrostatic field become negatively charged and are attracted to the positively charged object. Paint particles which, because of their initial velocity, travel past the object will reverse their direction and return. This feature provides a convenient method of painting the back of the object without rotating it and without moving the spray gun.

Overspray reduction results in considerable savings. With ordinary spraying methods, only about 50% of the paint reaches the work. Precipitation equipment increases the efficiency to 95%. Ventilation problems are reduced, and fewer guns and operators can handle the same volume of work.

Material deposition

In the manufacture of sandpaper and emery cloth, grains of abrasive material are electrostatically deposited on the glued backing. These grains tend to align themselves with the electrostatic field, and are deposited with their sharp points outward. This improves the abrasive quality of the product.

Electrocoating of fabrics is also being practiced. A design is printed with adhesive material on a cloth backing. Short pieces of textile fiber, known as flock, are electrostatically impelled against the backing cloth. The fibers not only stick to the adhesive, they actually penetrate the backing cloth, giving the appearance of a woven fabric. Rugs manufactured by this method are easier to produce and have greater durability. More than a quarter of a million fibers per square inch can be deposited in this manner. This is a fiber density about ten times greater than can be achieved by ordinary weaving methods.

—end—

TUBES at Mfr's. COST

Standard Brands—Unbranded—Guaranteed			
*1B3	\$1.35	8BF5	\$6.60
1L4	.60	8B06G	1.48
1L6	.60	8B06	.94
*1L6S	1.05	6C4T	.39
1M5	.60	6CR8	.56
1U4	.60	6C06G	1.93
1U5	.60	6C06	.75
*2A3	1.45	6J5T	.44
*2X2	.60	*6J5M	.65
3A4	.66	6J6	.73
3V4	.62	*6J6	1.04
*5V4	1.20	*6K6	.85
*5Y30T	.33	*6K7M	.85
*5Z3	.85	*6J7GT	.85
*6AC7	1.25	6L6	1.05
6AG5	.57	6L6A	1.05
*6AC7	1.65	*6R6	1.50
*6AM6	1.75	6S4	.51
6AR5	1.10	*6S7M	1.05
6AL5	.44	*6S7	1.10
6AU5	.51	*6S7J	.70
6AT6	.40	6K7GT	.53
6AU6	.45	6S7GT	.85
6AVE	.40	6S7GT	.58
*6AS5 6N5	1.25	6T8	.86
6RA6	.48	6V8T	.51
6BC5	.36	6W4GT	.49
6BE6	.49	6X4	.36
6X5		*7AD7	5.36
*12A6		*12A6	1.25
*12AT6		*12AT6	.70
*12AT7		*12AT7	.75
12AU6		12AU6	.46
12AU7		12AU7	.38
12AV7		12AV7	.75
12AX7		12AX7	.65
12AY7		12AY7	4.95
12BA6		12BA6	.48
12BE6		12BE6	.48
*12BSM		*12BSM	.70
12SK7GT		12SK7GT	.53
12SN7GT		12SN7GT	.58
12SR7		12SR7	.65
19T8		19T8	.84
25L6GT		25L6GT	.50
35L6GT		35L6GT	.53
35W4		35W4	.37
6000		6000	1.39
9002		9002	1.50
9003		9003	1.75
9005		9005	1.75
6X4		6X4	4.95
6X5		6X5	7.99
6X6		6X6	7.99
6X7		6X7	7.99
6X99		6X99	7.99
6X00		6X00	7.99

UNBRANDED—*STANDARD BRANDS
Minimum Order \$15.00

SPECIAL PURPOSE TUBES

1N36	\$9.95	350B	\$5.50	5749	\$4.95
1N23A	2.75	194A	5.50	5814	4.95
1N23B	4.95	703A	2.48	8025	5.75
2C3	5.95	715E	15.00	9001	1.75
2E25	5.95	721A	3.95	9002	1.50
2D21	1.55	723AH	14.50	9003	1.75
2B29	21.95	819	7.50	9004	1.75
304TL	12.49	813	7.50	CK70	4.95
304TH	12.49	829B	13.95	CK1005	7.99
304T	3.10	832A	11.00	8W4	1.90
3C24 24E	1.50	837	1.95	T20	2.25
8J3	6.75	931A	6.75	T200	16.95
8J4	6.75	932A	6.75	YU720	3.95
211C/VT4C	95	9670	5.95	T220	2.25
				T240	3.25

IMMEDIATE DELIVERY!
Write for quotations, many other types available. 20% Deposit with order, balance C.O.D. All tubes subject to prior sale.
WRITE, WIRE, CALL—TODAY!
We Buy Anything in Electronics—large or small Quantities!

Nat Adelman
168 Washington St. New York 6, N. Y.
CO. 7-6091

THE RADIUM ATOMIC SPINTHARISCOPE



THE SPINTHARISCOPE is one of the most amazing scientific instruments ever invented. The SPINTHARISCOPE demonstrates that radium actually destroys atoms. Look into the SPINTHARISCOPE and you see a whole firmament lit up like a brilliant night sky. You observe thousands of "stars" and untold bright flashes similar to showers of shooting stars. Every flash is the result of the destruction of one atom of radium. These fast moving Helium atoms (also called Alpha rays) produce a minute flash of light when they strike a crystal of zinc sulphide contained in the SPINTHARISCOPE. The magnifying lens of the instrument makes these flashes visible to your eye. The action keeps on going for over 1800 years. Our SPINTHARISCOPE actually contains a small quantity of radium. If you want to see a most awe-inspiring sight, witness the actual destruction of thousands of worlds (atoms are miniature worlds), by simply looking through the lens of the instrument.

See RADIUM DISINTEGRATED AND DESTROYED RIGHT BEFORE YOUR EYES!

The RADIUM SPINTHARISCOPE
Item No. 190
Price, Postpaid 75c
HUDSON SPECIALTIES CO., 40 West Broadway, New York 7, N. Y.

Please mention
RADIO-ELECTRONICS
when you write
to advertisers


RADIO-ELECTRONICS for

COUNTING RATE INSTRUMENT

By I. QUEEN

A new idea in electromechanical counting-rate meters is used in the Berkeley Scientific Corp.* model 1600 computer. The instrument has rapid response, wide counting range and high accuracy.

In the circuit shown, C1 and C2 are matched. A ganged rotary switch connects C1 to a source of regulated d.c. through a resistor, while C2 is across a voltmeter. This switch is controlled by a scaler or divider. As an example, the scaler might provide a single pulse for every 100 pulses from a Geiger counter. Then, after every 100 counts from the Geiger, the switch is flipped from A to B (or from B to A) by the scaler.

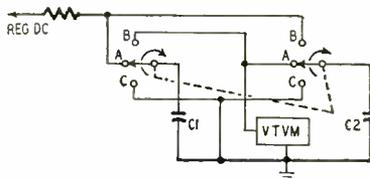

While one capacitor is being charged, the other is being tested by the v.t.v.m. If it should require 10 seconds for the Geiger count to reach 100, the switch will remain in the same position for 10 seconds. If it should require 30 seconds, for example, a much greater charge will accumulate on the charging capacitor before the switch is flipped. The meter scale is calibrated in reverse (like a series ohmmeter) since a rapid rate corresponds to a small deflection.

Each capacitor is shorted to ground by momentary contact with grounded terminal C after its charge is measured.

Each measurement is independent of previous ones, since the capacitor charge is shorted out after a reading. Since there are two capacitors which are measured alternately, there is no interruption. The greater the counting rate, the more often a reading is taken. The maximum number of readings is 400 per minute.

*Richmond, Cal.


ELECTRONIC EYES NEEDED

Electronic eyes and brains will have to take over in flying supersonic planes that travel 1,800 miles per hour, Dr. Richard A. Byrnes told the Aero Medical Association at a meeting in Denver recently.

Dr. Byrnes, of the U. S. Air Force School of Aviation Medicine, illustrated his point with this example: A plane traveling at 1,800 miles per hour will go about a fifth of a mile before it is even seen, because the eye and brain take between three-hundredths to three-tenths of a second to see at all. But in that distance the brain will not recognize the object as a plane. The aviator would not know he was seeing a plane until the supersonic plane had gone a half mile. While the brain is deciding what to do, the plane would have traveled almost a mile.

—end—

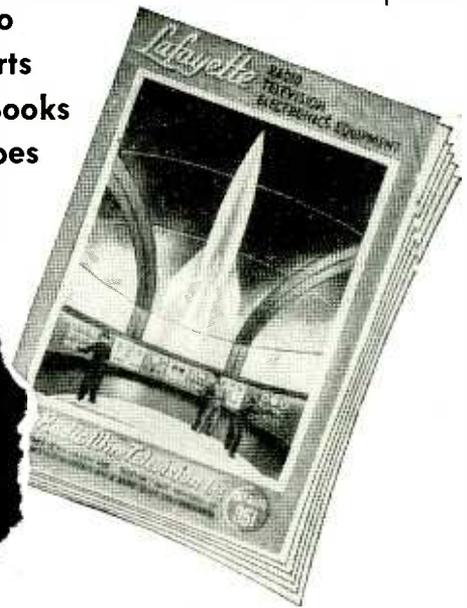High-Fidelity • TV • Radio
Phonographs • P.A. • Parts
Test Equipment • Tools • Books
Ham Gear • Electronic Tubes



FREE

31st year

New Lafayette Catalog NOW READY!

IMMEDIATE SHIPMENTS
★
COMPLETE STOCKS
★
TECHNICAL SERVICE
★
30-DAY MONEY BACK GUARANTEE
★

A practical encyclopedia used by economy-minded servicemen, hams and technicians throughout the world because they know they have a complete "one-source" guide. For quality equipment, for hard-to-get items, for nationally-advertised merchandise, for low prices, it's Lafayette.



RUSH THIS COUPON AT ONCE

VISIT LAFAYETTE SHOPPING CENTERS at
100 Sixth Ave. New York 13, N. Y.
•
110 Federal St. Boston 10, Mass.
•
24 Central Ave. Newark 2, N. J.
•
542 E. Fordham Rd. Bronx 58, N. Y.

Lafayette Radio, Dept. JA
100 Sixth Avenue
New York 13, N. Y.



I need the 1952 catalog. Please rush!

Name.....

Address.....

City..... Zone.....State.....

PASTE ON POSTCARD



It's the newest convenience in soldering. *Twin Spotlights* on your new 135-watt WELLER Soldering Gun completely eliminate shadows; you see clearly even in the darkest classis. Pull the trigger of your WELLER Gun, heat and light come on *together*—in just 5 seconds! No more waiting, wasted current, or blind soldering. Your WELLER Gun pays for itself in a few months!



Specially Designed for TV and Radio Work


- **DUAL SOLDERLITE**—Two prefocused spotlights completely eliminate shadows — let you see clearly what you are soldering.
- **OVER/UNDER DESIGN**—Tube construction braces tip and improves visibility.
- **5-SECOND HEATING**—No waiting. Saves power. Pull the trigger and you solder!
- **LONGER REACH**—Slides easily into deep chassis, reaches the tightest corners.
- **GREATER CAPACITY**—Smaller, lighter, with greater soldering capacity.
- **TRIGGER-SWITCH CONTROL**—Adjusts heat to the job. Saves current—no need to unplug gun between jobs.
- **DUAL HEAT**—Single heat 100 watts; dual heat 100/135 watts; 120 volts, 60 cycles. Handles all light-duty soldering.

See new Models WS-100 and WD-135 at your distributor, or write for bulletin direct.

- **SOLDERING GUIDE**—Get your new copy of "Soldering Tips"—revised, up-to-date and fully illustrated 20-page booklet of practical soldering suggestions. Price 10¢ at your distributor, or order direct.



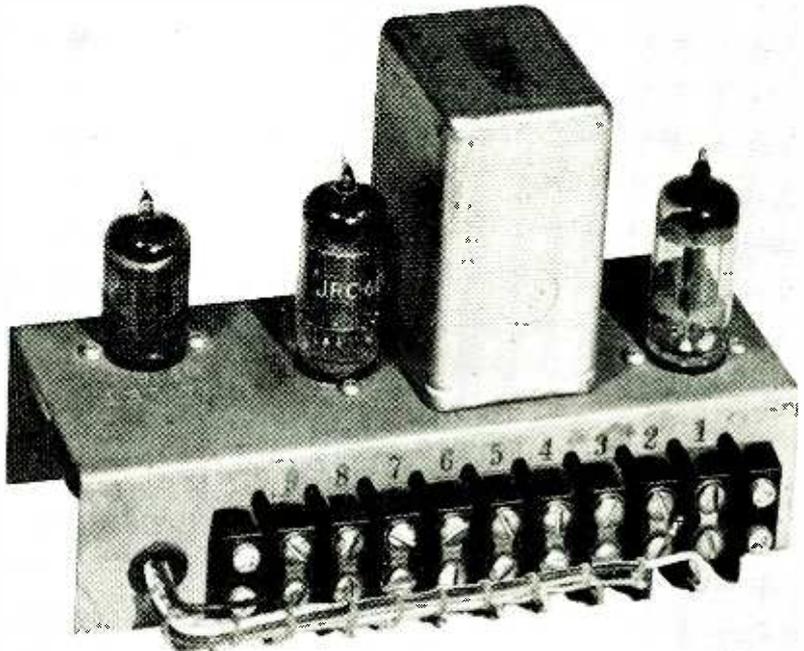WELLER
ELECTRIC CORP.
828 Packer Street, Easton, Pa.



The high utility value and modest dimensions justify a spot on the ham shelf.

Useful Phone-C.W. Monitor

By JOHN E. PITTS, W6CQP

WHETHER a ham operates on phone or c.w. he should know at all times how his voice or his keying sounds to the other fellow, and not have to ask the traditional question, "Cw's by bodulajun, Ode Ban?"


The monitor described here was designed to be as uncomplicated as possible, yet operate satisfactorily on either phone or c.w., being switched with the transmitter PHONE-C.W. switch to either type of emission. It was built on a piece of scrap sheet steel, 6 inches long, 2 inches wide, and with sides bent to give a height of 1½ inches. All external connections are made to a 9-terminal strip (see photos).

It comprises a 6AL5 duo-diode to provide plate voltage from the rectified transmitter carrier for the series-fed

Hartley oscillator. Phone carriers are demodulated by the other half of the 6AL5. The 6C4 amplifier is used to build up the output level enough to give a comfortable signal in the phones.

How it operates

With the PHONE-C.W. switch of the transmitter set to C.W., the 1-7 pin section of the 6AL5 receives r.f. from the antenna. The cathode of the 6AL5 supplies a slight positive voltage to the center tap of the oscillator transformer, causing the 6C4 oscillator to oscillate. The diode's d.c. return is through the 2.5-mh r.f. choke. The frequency of oscillation can be set over a moderate range by the capacitor across the center-tapped winding. In the instance here, a value of 100 µf produces a tone of about 800 cycles.

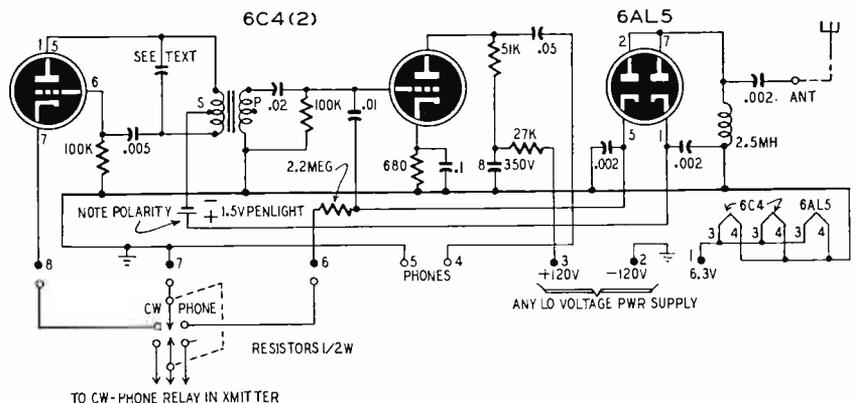

This circuit monitors phone signals and provides keyed tones when used on cw. RADIO-ELECTRONICS for

The Original!
LOW LOSS OPEN WIRE LINE
 (lowest loss lead-line m.f.d.)

"GONSET LINE"

- 1/6 THE LOSS OF NEW MOLDED RIBBON
- 0.5 DB LOSS PER 100 FT. AT 200 M.C.
- POLYSTYRENE SPACERS

Ideal for

- TELEVISION
- AMATEUR
- COMMERCIAL
- FRINGE AREAS
- LONG RUNS
- BEACH AREAS

send for latest bulletin

GONSET CO., BURBANK, CALIF.
 72 E. TUJUNGA AVE.

Model 200
AM & FM SIGNAL GENERATOR

Specifications: • **R. F. FREQUENCY RANGES:** 100 Kilocycles to 150 Megacycles. • **MODULATING FREQUENCY:** 400 Cycles. May be used for modulating the R.F. signal. Also available separately. • **ATTENUATION:** The constant impedance attenuator is isolated from the oscillating circuit by the buffer tube. Output impedance of this model is only 100 ohms. This low impedance reduces losses in the output cable. • **OSCILLATORY CIRCUIT:** Hartley oscillator with cathode follower buffer tube. Frequency stability is assured by modulating the buffer tube. • **ACCURACY:** Use of high-Q permeability tuned coils adjusted against 1/10th of 1% standards assures an accuracy of 1% on all ranges from 100 Kilocycles to 10 Megacycles and an accuracy of 2% on the higher frequencies. • The Model 200 operates on 110 Volts A.C. Comes complete with output cable and operating instructions.

\$21.85 NET

Sold on Money-Back-If-Not-Satisfied Guarantee.

We carry a complete line of test equipment. Write for FREE Catalog

GENERAL ELECTRONIC DISTRIBUTING CO.
 Dept. RE-1 98 Park Place, New York 7, N. Y.

The output of the oscillator is amplified by the second 6C4, being coupled to the amplifier grid through the .02- μ f capacitor. Terminals 4 and 5 may be connected in parallel with the high-impedance output of the station's receiver or by any other suitable means to the phones.

It will be noted that a 1.5-volt penlite cell is connected in *reverse* polarity in the plate lead to the oscillator. This was found necessary because the oscillator was sufficiently sensitive to oscillate weakly on the contact potential of the 6AL5 diode, probably not more than a few hundredths of a volt. The reverse potential cured the oscillation.

For phone operation, the PHONE-C.W. switch of the transmitter is set at PHONE. This breaks the cathode circuit of the 6C4 oscillator, and makes the return circuit of the 5-2 pin diode section of the 6AL5 through the 2.2-meg diode load resistor. The varying audio across the 2.2-meg resistor is impressed on the grid of the 6C4 amplifier through the .01- μ f capacitor. An exact replica of the modulation as heard at the other fellow's station is produced in the phones, as actually a minute portion of the carrier is sampled and demodulated at the station.

This monitor will not check for chirps on c.w., or out-of-band operation. But every station is supposed to have a reliable frequency-measuring device, is it not? However, any a.c. modulation of the c.w. signal will produce modulation of the audio tone heard from the oscillator, and will give a good check on the purity of the emitted signal.

The length of antenna connected to terminal 9 will be determined by the power output of the station's transmitter, of course. Used with the author's transmitter, running a kilowatt to a pair of 304TL's, only 4 inches of antenna gives a good signal on either phone or c.w.

(The monitor will be more convenient to use if you connect a 0.5 megohm potentiometer across terminals 4 and 5 and run a shielded lead from the variable arm to the hot side of the receiver's volume control and adjust the monitor level to the customary receiver level. With this connection, it will not be necessary to use an extra pair of phones for the monitor. An audio voltage divider may be inserted to reduce the monitor output to the level of the second detector in the set. If the send-receive switch breaks the B-minus lead in the set, rewire it so it is in series with the B-plus lead to the r.f. and i.f. circuits, leaving B-plus applied to the audio circuits of the set. With this connection, you won't have to reset the volume control each time you switch from send to receive.—Editor)

Materials for monitor

- Capacitors: (paper) 3—.002, 1—.005, 1—.01, 1—.02, 1—.05, 1—0.1 μ f. (electrolytic) 1—8 μ f.
 Resistors: 1—680, 1—27,000, 1—51,000, 2—100,000 ohms, 1—2.2 megohms.
 Tubes: 2—6C4, 1—6AL5.
 Miscellaneous: 1—push-pull interstage or input audio transformer; 1 s.p.d.f. relay (part of d.p.d.f. relay in transmitter) 1—RFC, 2.5 mh; 1 penlite cell; tube sockets; terminal strip; chassis; phones; accessories; wiring.

—end—

USE PHOTOFAC
 the world's best Radio-TV service data—it pays for itself every working day



Try PHOTOFACT!

FREE We'll send you any Photofact Folder listed in the Photofact Cumulative Index*

WE'LL PROVE YOU'LL SAVE TIME and EARN MORE WITH PHOTOFACT

NOW—learn for yourself—at our expense—how PHOTOFACT makes your Radio and TV work *quicker, easier, more profitable!* Examine an actual PHOTOFACT Folder. Use it. You'll learn first-hand why over 35,000 successful service technicians use PHOTOFACT daily. You'll learn that no other service gives you PHOTOFACT'S completeness, accuracy, uniformity, and lowest cost. PHOTOFACT is the *only* radio and TV service data prepared from laboratory analysis of the actual equipment. Know the facts—get your FREE Folder now. Examine, use, compare—learn why no modern service shop can afford to be without PHOTOFACT!

* Except those followed by asterisk (*) or letter A.

WRITE FOR FREE INDEX **PAY AS YOU EARN!** Ask your distributor about this amazing plan. Only \$18.39 puts the entire profit-boasting Photofact library in your shop now!

NOTE: Our FREE Folder offer is limited to Service Technicians only. Attach coupon below to your letterhead and mention your jobber's name. If you have no letterhead, send coupon to your jobber. Experimenters and others may obtain the Photofact Folder by remitting amount shown below.

HOWARD W. SAMS & CO., INC.
 2201 E. 46th St., Indianapolis 5, Ind.

- Send FREE Photofact Cumulative Index
- Send Full Easy-Pay Details

I am a Service Technician:

- Send FREE Folder for set model.....

I am an Experimenter: Enclosed \$.....

- Send Folder for set model.....

TV-\$1.00. Record Changer or Comm. Receiver-75c. AM/FM-50c

Name.....

Address.....

City.....Zone...State.....

It's a shame ...



Yes, sir, it's a downright shame and pity that every service technician and dealer in the country can't sit in on the rigid, comprehensive tests we conduct on TARZIAN Tubes.

You could see first-hand how the high standards of quality control in TARZIAN production assures customer satisfaction . . . always.

Qualitywise . . . performancewise . . . and pricewise, there is no better tube than the TARZIAN Illuminized Tube with the metalized screen. TARZIAN Tubes are available all sizes—round and rectangular—for original use or replacements. Write for technical information.

SARKES TARZIAN, Inc., Sales Division, Bloomington, Ind.

TARZIAN MADE PRODUCTS

Tubes

Air Trimmers

Selenium Rectifiers

Cathode-Ray and Receiving Tubes

STATIONS WTTT (5000 WATTS) AND WTTV (CHANNEL 10)
OWNED AND OPERATED BY SARKES TARZIAN IN BLOOMINGTON

ACTIVITIES OF NETSDA AND ITS LOCAL CHAPTERS

The National Electronic Technicians and Service Dealers Association (NETSDA) held its annual meeting in the Hotel Stacy Trent in Trenton, New Jersey on November 11, 1951. E. W. Merriam, Service Manager for the Radio Television Manufacturers Association, was guest speaker. He gave an outline of his proposed plans to forward the proposals presented by NETSDA at the Chicago meeting of the Radio Television Manufacturers Association's Service Committee.

At the close of Mr. Merriam's talk, the score or more delegates present from the various chapters presented a series of questions to Mr. Merriam, who tried to answer as many as possible. A series of requests and demands was also given to Mr. Merriam to present to the RTMA Service Committee at its next meeting. The delegates then voted to give all the cooperation necessary to Mr. Merriam in helping him to promote a concrete program for the servicing industry.

The National Electronic Technicians and Service Dealers Association's delegates voted to hold a national meeting of representatives of all servicing associations throughout the country. The meeting was tentatively set for May 1952, at which time, representatives of the manufacturers, distributors, broadcasters, and sales representatives will also be requested to attend. A definite date and location has not been selected as yet, but will be after a survey is made among all radio and television technicians and service dealers associations in the U.S.A.

A national code of ethics was adopted by the body and will be presented for vote and ratification by all Chapters. The Federation of Radio Servicemen's Associations of Pennsylvania (FRSAP) met in Scranton, Pa. October 21, 1951. Delegates from all chapters were present. In addition, representatives from the Southern Pennsylvania Radio and Television Technicians Association (of York, Pa.), headed by their president, Mr. Sheffer, presented their application for membership to the state group which was voted upon and accepted. This makes the tenth chapter in the state federation.

Officers of the new association are: Carl Sheffer, president; Eugene Klinedinst, vice-president; Joseph Hauser, secretary; James Geiselman, treasurer; and Gerald Dean, public relations.

The new organization has applied for membership in the Federation of Radio Servicemen's Associations of Pennsylvania.

The 50-point program as prepared by delegates of the Federation and presented to the RTMA, National Electronic Distributors Association, and set distributors association, was thoroughly covered at this meeting.

Each year, as in the past four years, the Federation appoints a committee to arrange for a statewide vote in all Chapters to select the individual, organization, or the publication who has made

★ **WANTED** WE NEED YOUR SURPLUS ELECTRONIC EQUIPMENT ★
★ **WE PAY TOP \$\$\$ FOR:** ★
★ RADIO RECEIVERS ★ CLAMPS ★
★ TRANSMITTERS ★ PLUGS ★
★ ARC-1 ★ CORDS ★
★ ARC-3 ★ RELAYS ★
★ ART-13 ★ TELEPHONE ★
★ CONTROL BOXES ★ MATERIALS ★
★ INDICATORS ★ WE BUY ANYTHING!! ★
★ AN CONNECTORS ★
★ **Write, Wire Today!** ★
★ Tell us what you have ★
★ **TALLEN COMPANY, INC.** ★
★ Dept. RE, 159 Carlton Ave. ★
★ Brooklyn 5, New York ★
★ *****

500 FORMULAS TO SUCCESS

MANY million dollar firms started with a single formula, for which they paid a big price. Here you have 500—no less—tried and tested formulas, recipes and processes for making things . . . all at the ridiculously low price of 25c. Here is your opportunity to start business with but a few dollars' capital and with undreamed of profits in prospect. You can also use these formulas in your own home to cut household expenses to the bone. Or you can put them to use in your workshop to cut costs as much as 100%. Quit paying out many dollars in profits to manufacturers, wholesalers, and dealers, when you can make the same thing yourself for a few cents. It's so easy when you follow our simple instructions.

66 PAGES. 47,000 WORDS IN TEXT
Send for "500 FORMULAS AND RECIPES" today. Enclose 25c, that's all! You won't be asked for another cent now or later. Sold on a money-back guarantee.

NATIONAL PLANS COMPANY
1966R Broadway, New York 23, N. Y.

an outstanding contribution to the servicing industry. For this, the Federation awards its annual plaque. The committee appointed this year is the delegation from Altoona. The new speaking schedule for 1952 will include John Rider, nationally known publisher, and speakers from Capehart-Farnsworth, Howard W. Sams, and Motorola.

The Radio Servicemen's Association of Luzerne County is carrying on with a full line of business and social activities, with lectures and demonstrations on TV receivers and circuitry, u.h.f., better business methods, and other subjects. The local Association is looking forward to the future lectures which have been arranged by the State Federation and is at present doing its part in promoting licensing.

September 16, 1951, the annual basket picnic was held at Toby Park, Blakeslee. Prior to the basket picnic, the annual sponsorship of a Grove Theater play, "Dark of the Moon" took place on Tuesday, August 28, 1951.

Max Liebowitz, president of the Associated Radio-Television Servicemen of New York (City) has recently arranged for a series of articles in the local daily newspapers on the need for licensing. He has also supplied a story entitled "Here's A Law to Protect You." to the TV Guide whose circulation in New York City runs into many thousands. On November 12, Mr. Liebowitz appeared as a guest on a program on WCBS-TV in New York City, at which time, he presented the service technicians' views on licensing.

Oak Ridge Products Co. will supply necessary test equipment for ARTSNY's clubroom. A committee has been appointed to select nominees for election to offices for 1952.

The Radio Servicemen's Association of Trenton, New Jersey, has arranged a series of technical and business lectures to promote a more progressive and active program within the association for the benefit of its members. They will be held in the studios of the local broadcasting stations.

Gibson Grandly of Trenton has been appointed chairman of the new membership committee and already good results have been obtained. Membership is now open to all radio and television technicians and service dealers in the area.

The Long Island Television and Radio Technicians Guild president Eugene Laper has appointed a nominating committee to select officers for 1952. A series of lectures are being arranged for by the Educational Committee on television and radio servicing as a business.

The Guild has decided to make a bigger effort to take a more active part in the Empire State Federation and in the NETSDA.

The Kingston Radio Servicemen's Association officers, under leadership of their President, Raymond E. Trumpait, will undertake a campaign to visit all technicians and service dealers in the area to obtain additional membership. A series of lectures and social events are being scheduled for 1952.

GET YOUR **BIG, NEW 1952**
CONCORD Catalog



FREE!
Send for it NOW!

ALL-NEW COMPLETE BUYING GUIDE for Every Need!

FAMOUS PRODUCTS—VAST STOCKS—LOWEST PRICES

TV • RADIO • ELECTRONICS

You save time and money—with this bigger, better 1952 Buying Guide! Here is page-after-page full of the latest and greatest values in Television, Radio and Electronics. It brings right to your finger tips one of the world's largest stocks of nationally known guaranteed quality parts and equipment. You find it quick and easy to get whatever you need—at the very lowest prices! Send for your FREE Concord Catalog today! Have it handy for quick reference!

Supplies for Industry, TV and Broadcast Stations, Schools, Servicemen, Hams, Government, Experimenters and Builders

CONCORD RADIO

901 W. JACKSON BLVD. • CHICAGO
Over 30 Years of Service to the Radio World

CONCORD RADIO CORP., Dept. JA-52
901 W. Jackson Blvd., Chicago 7, Illinois

Rush FREE Big, New 1952 CONCORD Catalog No. 95

Name _____
Address _____
City _____ Zone _____ State _____

- HIGH FIDELITY TV & RADIOS
- PHONOS & RECORDERS
- SOUND SYSTEMS
- HAM GEAR
- TEST EQUIPMENT
- ELECTRONIC TUBES
- PARTS, BOOKS, KITS

FAST DELIVERY
Large and varied stocks insure quick shipment on thousands of items.

HELPFUL SERVICE
Our technical experts give personal attention to your problems!

INDUSTRIAL DIVISION
Experienced staff and centralized efficiency speed service on supplies to Industry!

HIGH FIDELITY
Complete systems and custom components for finest reproduction!

EXPORT DIVISION
Special Export Division gives prompt service on orders and inquiries.

POSITIVE SATISFACTION
CONCORD'S policy of quality and value assures you of complete satisfaction!

FREE SEND FOR IT TODAY!



THOUSANDS ARE RAPIDLY LEARNING ABOUT ITS OUTSTANDING FEATURES

SUCH AS:

SHARP, CLEAN "SNOW-FREE" PICTURES

And

- Correct impedance for "ghost-free" reception. Nominal 300 ohms.
- Lower in cost than other leadlines purported to accomplish same results.
- Correct spacing for minimum radiation loss. Less than 1% of operating wave length.
- Fully insulated—approved by safety experts.
- Pure, unadulterated polyethylene insulation—specially treated by our chemists for extreme weather.
- High-efficiency conductors: Flexible, stranded—to insure long life.
- Easily installed—with standard insulators.
- Packaged in convenient lengths: 100', 250', 500', 1,000', 2,500'.
- AT YOUR DEALERS, or Write For Free Samples and Literature.

*Patent Pending *Trade Mark U.S. and Foreign Patents Pending
EXCLUSIVE LICENSEE AND SOLE MANUFACTURER

Don Good, INC.

1014 FAIR OAKS AVENUE
 SOUTH PASADENA, CALIFORNIA

OTHER OUTSTANDING GOODLINE PRODUCTS:

VARIABLE TELETRAPS—2: Highly effective for *eliminating interference* from FM STATIONS, and DIATHERMY and AMATEUR SIGNALS within its tuning range.

HI-PASS FILTER: *Eliminates or greatly reduces interference* picked up by I. F. AMPLIFIER or TV RECEIVER—interference arising from strong, local low-frequency fields: X-Ray, Diathermy Equipment, Neon Lights, Etc., Etc.

HAVE YOU A JOB FOR A TRAINED TECHNICIAN?

We have a number of alert young men who have completed intensive training in Radio and Television Repairing. They learned their trades thoroughly by working on actual equipment under personal, expert supervision. If you need a trained man, we invite you to write for an outline of our course, and for a prospectus of the graduate. No fees, of course. Address:

Placement Manager, Dept. P108-1

COMMERCIAL TRADES INSTITUTE

1400 Greenleaf

Chicago 26

NEW CONDENSER TESTER

**Finds Intermittent
 Condensers Instantly**
 NET



Pres-probe's sliding tip with variable resistance prevents condenser heating. Tests with power on. Requires no adjustment. Stops guesswork. Saves time. Convenient probe size (7 1/2" long). Satisfaction guaranteed.

See Your Dist. or Order Direct

PRES-PROBE CO.

4034 N. Sixth St., Milwaukee 12, Wisc.

795
 Postpaid
 U. S. A.

Philadelphia Radio Servicemen's Association is preparing a program of public relations to be carried directly to the homes of the thousands of customers serviced daily by Association members. The magazine committee is now completing the mailing list which will include most of the four thousand members in the State Federation and the officers of a hundred or more individual Radio and Television technicians and service dealers' associations throughout the country. *PR.S.M.A. News*, which is the voice of the local service technicians will, therefore, be available to all those interested. Copies can be obtained by writing Mr. Stan Myers, 1643 S. Wilton Street, Philadelphia 43, Pennsylvania.

Mid-State Radio Servicemen's Association members attended a series of technical lectures at Harrisburg, sponsored by RCA in September, General Electric in October, and Raytheon in November. The Raytheon lecture was one of the finest the local technicians have heard in a long time. In addition to the hundred or more members, scores of invited technicians from Harrisburg and surrounding areas were present.

The Lackawanna Radio Technicians Association is contemplating a new advertising and publicity campaign for its entire membership through newspapers and radio ads. The election of new officers at the last meeting and the committee heads will again promote an active program for the Lackawanna technicians.

Blair County Association of Radio Service Engineers, through the promotion of its technical talks to the technicians in the surrounding area, has obtained over thirty-five new members in the past six months. Delegates to the State Federation have brought in additional business and technical programs to round out the balance of the year. A publicity campaign to promote the association emblem to the public is now under consideration.

LICENSE BILL PASSED

Television technicians and contractors of New York City will require licenses or permits to work after February first, according to the terms of a bill passed by the City Council in November.

Television contractors would be licensed in two groups. The "A" contractors would include those considered financially able to carry out their obligations and to refund balances of contract payments if for any reason they should not be able to complete the contracts. The "B" group would not have to show the same financial strength, but would have to satisfy the license board of their dependability as service concerns.

Technicians now working as such would be issued a permit until such time as they can sit for an examination for a technician's license. All technicians would be expected to take an examination before July 1, 1953, and after that date none but licensed technicians will be permitted to do service work on television or radio-TV combinations.

RADIO-ELECTRONICS for

Fees of \$15 are to be charged for technician permits or licenses, with an annual \$5 renewal fee. A less skilled group is to be given apprentice permits at a \$5 fee, also with a \$5 yearly renewal.

The law will be administered by a city commissioner, with the help of an eight-man board, consisting of one member from the city's law department, one from its Board of Education, an electronic engineer, a service technician, a service contractor, a television dealer, a receiving set distributor, and a parts distributor.

A mixed reaction to the bill was noted. The press generally welcomed it as protection for the TV set owner. The president of ARTS.NY, Max Liebowitz, points out "The bill is for the protection of the public, but is in the best interests of the service industry." On the other hand, officials of large service companies and the spokesman of a dealer's association believe that "the bill will not be effective," that it will not cure all the industry's evils (a reasonable assumption, indeed!) or even that "It's another racket to get more money for the city." One of the four councilmen who voted against it felt that it restricted honest service people who have been doing ethical business for a long time. It should be noted that the bill covers licensing of television service only.

COLUMBUS ADVERTISES

The Associated Radio-Television service Dealers of Columbus, Ohio, have been running a series of ads in the local *Sunday Citizen*, on the Radio-Television page. Effect has been good, in the opinion of members.

BALTIMORE UNITES

A new service association to be known as the Certified Television and Electronics Association (CTEA) of Maryland, has been formed in Baltimore. Twenty-seven members were reported to have signed up.

Speakers at the organization meeting included Frank Moch, president of the National Alliance of Television and Electronic Service Associations (NATESA) and Mal Parks, Chicago radio and television editor. Mr. Moch discussed the parts warranty problem and Western Union's plan to handle radio and television servicing. Mr. Parks talked on servicing prospects and problems, among other things urging that all service companies return to the service contract system, and criticizing present manufacturing standards. Out of a recent check of 60 sets, he stated, 40 were missing a tube, or connections had not been properly soldered.


LICENSES FOR SHOPS

Los Angeles County will license all television shops in unincorporated parts of the county (those outside the city of Los Angeles) under a recently passed ordinance. The bill makes no provision for examination and licensing of technicians, but is confined to service shops not engaged in selling new sets. Fee will


Now BLONDER-TONGUE BRINGS YOU FOR THE FIRST TIME IN TV HISTORY

An ALL-CHANNEL MASTER ANTENNA SYSTEM that YOU can install—in a matter of minutes—that is guaranteed to out-perform any other system.

... AND AT THE LOWEST COST!

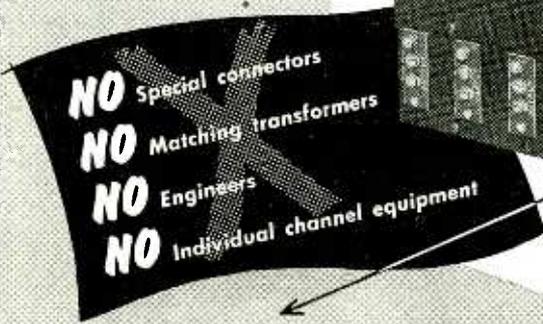

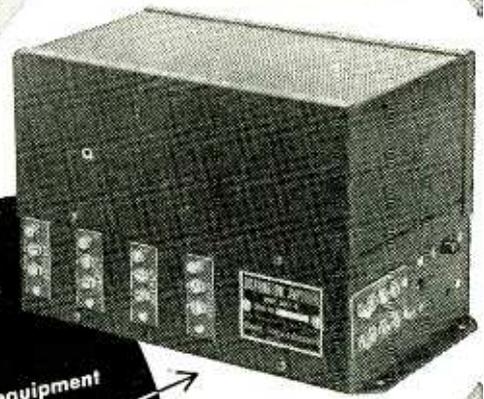
Distribution Amplifier
8 TV Outlets at Lowest Cost




Model #DA8-1-M
\$87.50

Model #DA8-1-M Distribution Amplifier

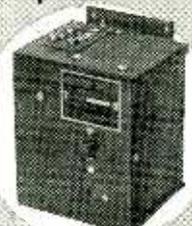Full electronic isolation (min. 35db. between outlets). Amplifies as it distributes... Variable Gain Control. No signal loss. Automatic All-Channel transmission. Ordinary screw terminals assure faster, simpler installation.



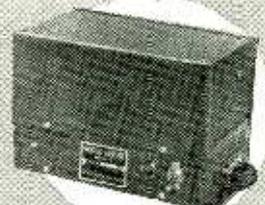MODEL #DA2-1-M
List Price \$39.50
Distribution Amplifier
2 TV Set Outlets



Model #CA-1-M. List Price \$77.50. Commercial Antensifier (30 Times Gain). Use As Pre-Amplifier, Line Amplifier or de-luxe Booster.

Combine these B-T units to serve up to 2,000 TV sets from 1 antenna.



Literature on Request write Dept. C-1
Mt. Vernon, N.Y.

Model #HA-2-M
HOME ANTENSIFIER — Fully automatic, all-channel TV booster. 16 times gain. In metal cabinet. 57.50



COLOR TONE TELEVISION

ON FOUR

Simply attach TELECOLOR FILTER to front of set and enjoy programs in glorious color tones instead of dull black and white. GUARANTEED to give genuine color tone. Can also be used with any other filter. Once tried, you will never go back to old black and white. Write for FREE information. ORDER BY MAIL. NEW REDUCED PRICES!

Send check, M.O., cash, COD to Dept. RE-3

10 in.....\$1	16, 17 in.....\$3
12, 14 in. \$2	19, 21 in.\$5

HARVARD LAB 659 FULTON ST. BROOKLYN, N.Y.

EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes for beginner's alphabet to typical messages on all subjects. Speed range 3 to 40 WPM. Always ready—no QRM.

ENDORSED BY THOUSANDS!


The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

INSTRUCTOGRAPH COMPANY

4701 Sheridan Rd., Dept. RC, Chicago 40, Ill.

The New Precision Engineered **OAK BOOSTER!**

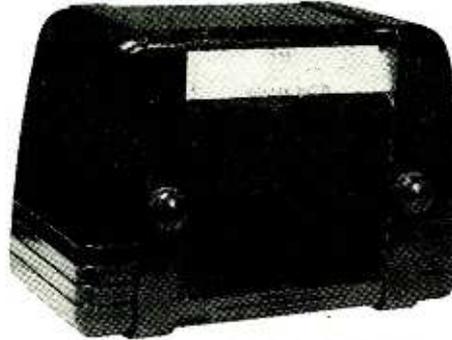for **TV-FM**
by **OAK ELECTRONICS**
\$39.95



▲ **KNOB DOES IT:**

- A. Turns on Booster & TV set.**
- B. Changes "Q" of circuit from 50 to 300 thru new "Q" multiplier circuit (See May "Electronics")**
- C. Varies bandwidth from 0.5 MC. to 12 MC.**
- D. Allows gain to be controlled from a low value comparable to any other booster, to a high value no other booster can match.**

The booster that finally satisfies your demands by succeeding where others have failed. The OAK BOOSTER uses Mallory INDUCTUNER same as used in Dumont, Crosley and Stromberg Carlson TV sets) in a newly engineered circuit on which patent is pending. Provides variable bandwidth to control adjacent channel interference and reduce noise to a minimum. Uses new "Q" multiplier circuit to increase gain enormously.

Only Oak has all the features that count

FEATURES	BOOSTER CHECK LIST						
	Oak Booster	A	B	C	D	E	F
Automatic On-Off	Yes	Yes	Yes	No	No	No	No
Variable Bandwidth	Yes	No	No	No	No	No	No
Amplifies Fm	Yes	Yes	Yes	No	No	No	No
75 or 300 Input	Yes	No	No	No	No	No	No
Variable Sensitivity	Yes	No	No	No	No	No	Yes
Highest Gain 2-6	Yes	Yes	Yes	No	No	No	No
Highest Gain 7-13	Yes	Yes	Yes	No	No	No	No
75 or 300 Output	Yes	No	No	No	No	No	Yes
Widest bandwidth of any booster	Yes	No	No	No	Yes	No	Yes
Square Wave Type Band Pass Characteristic	Yes	Yes	No	No	Yes	No	Yes

No untuned boosters are rated, as performance is not equal to any tunable boosters.

Other boosters use this knob only for On-Off switch, or to switch from low to high channels. OAK REALLY USES THIS KNOB.

- ✓ **Highest gain of any booster**
- ✓ **Dual Input**
- ✓ **Dual Output**
- ✓ **Gain adjustable from front knob**
- ✓ **Automatic On-Off**
- ✓ **Variable bandwidth controllable from front panel**

Order Oak Booster from your jobber today
SALES REPRESENTATIVES

- Atlanta, Ga. — HENRY BURWELL Co.
- Chicago, Ill. — JEROME KLEKER Co.
- Cleveland, O. — EDWARDS & LOHSE
- Fort Wayne, Ind. — WALTER BIEBERICH
- Houston, Tex. — H. H. WILLISON
- Los Angeles — CARL A. STONE ASSOCIATES
- San Francisco — RUSS HINES
- New York City — BURLINGAME ASSOCIATES
- Bronx, N. Y. — V. SALES Co.
- New Jersey — JACK BROWN

Write for specifications and discounts

OAK ELECTRONICS
150 Oak Street, Buffalo, N. Y.

be \$36 per year.

According to County Sheriff Biscailuz, "The background of each repairman will be investigated, and . . . a dishonest one will not be licensed for business."

A conference was proposed by the county supervisors, with the idea of exploring the possibilities of examining and granting certificates to individual repairmen, with the idea of protecting the public against incompetent service as well as the protection against dishonesty expected to result from the ordinance already passed.

NETSDA'S PROPOSED CODE

The following Code of Ethics was adopted by the National meeting of NETSDA at Trenton, N. J. It has been sent to member chapters for approval or further suggestions.

I pledge myself:

1. To at all times perform my work to the best of my ability and knowledge. In addition, to make a sincere effort to improve my knowledge of the technical and business requirements of my profession, thereby enabling me to render more competent service.
2. To use whenever possible, original factory replacement parts. Where this is impractical, to use parts of equivalent or better quality.
3. To exercise special care in handling customers' property.
4. To guarantee all service performed and parts replaced by me for a period of 90 days (unless otherwise specified).
5. To charge a fair and just price for all work, and to display these prices prominently.
6. To refrain from unfair or unethical practices, untruthful advertising, unreliable statements, unjust or unfair criticism of other technicians, or any conduct which might lead to lack of confidence in my self or in my fellow technician.

NATESA MEETING

The 1951 Convention of the National Alliance of Television and Electronic Service Associations (NATESA) was held in Chicago November 18, 1951. Nineteen members were present, representing five states, and proxies for three more member associations were voted. In addition, visitor representatives from five states were also present.

Six new associations affiliated with NATESA during the convention. These were the Associated Radio & Television Service Dealers, Columbus, Ohio; Television Service Engineers, Inc., Kansas City, Mo.; California TV Service Dealers Association Inc., Hollywood, Calif.; Certified Television Electronics Association, Baltimore, Md.; Radio Service Dealers Association of Kansas, Inc., Wichita, Kan.; and the Radio Television Service Association, Minneapolis, Minn.

E. W. Merriam, the Service Secretary of the RTMA, and Mal Parks, of *What's New in Television*, addressed the gathering. Major problems such as parts warranty, procurement, and Western Union, were discussed, and a new constitution for the Alliance was adopted.

—end—

FIND THIS MAN!

NAME: Len Leonard. Age: 31. Height: 5' 10". Hair: black. Eyes: brown.

ALIASES: "Moneybags Leonard."

WANTED: This man is urgently wanted by his wife, Leona and two children.

RECORD: For months he has been paying the highest, most ridiculous prices ever offered for new or used radio equipment. He buys anything in electronics from hams anywhere—and dishes out dough like it grew on trees.

IMPORTANT: You can get rich too! Sell your new and used radio gear to Len Leonard at—

COLUMBIA ELECTRONICS SALES

522 S. San Pedro St. Los Angeles 13, Calif.

WANTED TO BUY

Large and small quantities of new or used electronic government or manufacturers' surplus tubes and equipment. Highest prices paid. State quantity, condition and best price in first letter.

Box No. F-2 c/o Radio-Electronics
25 West Broadway
New York 7, N. Y.

TUBE OF THE MONTH

A new all-glass rectangular 21-inch TV picture tube has been released for replacement or original manufacturer equipment by the Cathode-ray Tube Division of the Allen B. Du Mont Laboratories, Inc.

The tube, the 21KP4A, features a picture area of 242 square inches (more than previous metal-cone 21-inch tubes). A filter-glass face plate improves contrast and cylindrical face surface minimizes reflections by scattering incident



The base connections of the 21KP4A light upward and downward, away from the eyes of the viewer.

The new 21KP4A is a Selfocus type and does not require a focus control or associated circuitry. It may replace electromagnetically or electrostatically focused picture tubes, usually without circuit change.

It is provided with an external conductive coating and the standard 5-pin duodecal base. The overall dimensions are 23 inches with a 70° diagonal deflection angle. Heater rating is the usual 6.3 volts at 0.6 amperes with maximum recommended voltages of 500 for first anode and 18 kv for second anode.

—end—

Be precise!
Buy **PRECISE** you'll save with these top quality kits

The New **PRECISE** Vacuum Tube Voltmeter with the famous **PRECISE** Reflex Circuit for increased stability and greater accuracy.

By comparison, your best value! 1% Ceramic resistors; Etched panel; Amphenol connectors; Separate 5 V., AC scale; Tubes: 6AL5, 6X5, 6SN7; True zero adjust; 4 1/2" Meter; Three-color rapid construction book explains each step. Complete with btry. & test lead.

Ranges: +DC: 0-5-25-250-500-1000 V.
-DC: 0-5-25-250-500-1000 V.
AC: 0-5-25-250-500-1000 V.
Ohms: Rx1, Rx10, Rx100, Rx10,000, Rx1,000,000 ohms.
DB: From -20 to +55 DB.

PRECISE Kit Model **\$2598***
909-K
Factory
wired, Model 909. \$44.98*

NO OTHER PROBE OFFERS SO MUCH... all **PRECISE** exclusives... make it the most practical, foolproof and sturdy High Voltage Probe in the industry today.

Multiple insulation; Mechanically shockproof construction; Interchangeable tips; Swivel Lead connection; Interchangeable resistors; Triple flash guards; Sturdy, non-porous shell construction.

PRECISE Model 999 **\$698***
(Wired only) Complete

PRECISE DeLuxe V.T.V.M. ... Build it horizontally or vertically to fit your own bench requirements. Large 7 1/2" meter for better visibility—greater accuracy.

All the unusual features and ranges of the **PRECISE** Model 909 V.T.V.M. in a DeLuxe version. Complete with btry. & test lead.

PRECISE Kit Model **\$3898***
907-K
Factory Wired.
Model 907 \$57.98*

New R.F. PROBE Lowest Price in the field! Leads in Value!

Time-tested circuit; Special non-porous case; Uses germanium crystal rectifier up thru 250 megs. Probe handle terminated in an amphenol connector—other end of shielded cable available in either amphenol, phone plug or phone tip type fitting at no added charge.

PRECISE Model 912 **\$425***
(Wired only)

All instruments carry the **PRECISE** Guarantee, components protected by the R.M. Warranty. Write for FREE Catalog E-11. SEE THE COMPLETE **PRECISE** LINE AT YOUR JOBBER NOW! *Prices slightly higher in the West.

EXPORT DEPT.: 15 Moore St., New York, N. Y. Cable "Mintlhorne."

PRECISE **PRECISE DEVELOPMENT CORP.**
An Engineered Product Oceanside, L. I., New York

FIX ANY RADIO

Amazing New Invention

Find radio faults with a new simplified method. Repair all radios in minutes instead of hours. Revolutionary, different Comparison technique permits you to do expert work almost immediately. Most repairs can be made without test equipment. Simplified point-to-point, cross-reference, circuit suggestions locate faults quickly and easily.




NO TESTERS NEEDED

This newly developed method tells you how to locate the source of trouble in any radio set without equipment. Make needed tests, measure voltage, trace the signal, by using only a 5¢ resistor, small condenser, and a crystal detector. Inject signals without any signal generator. Test parts by the new Comparison method. Test tubes without equipment. Repair any radio expertly following simplified picture plans. Improve your radio servicing ability. Data on all sets, portables, FM, AC-DC, P.A., and television. Send coupon below.

CHARTS, BLUE-PRINTS, TESTS

Learn time-saving trouble-shooting short-cuts: find any radio fault with ease. Follow the tests shown on 24 large circuit blue-prints. Gives over 1,000 practical repair hints. For all types of radios. Hundreds of simplified tests using a 5¢ resistor and any filter condenser. Introductory material to help beginners. Several chapters on test equipment. Complete plan in manual form. 61 job-sheets, data on all tubes, 92 large pages, 8 1/2 x 11 in. Schematics, pictures, charts. Sold on no-risk trial. Price, only \$1.50.

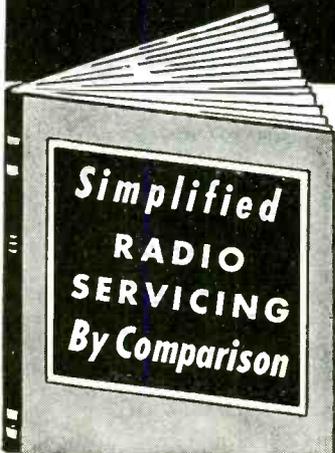

Supreme Radio & TV Manuals

Your complete source of all needed RADIO and TV diagrams and service data. Most amazing values. Still sold at pre-Korean prices. Only \$2 for most volumes. Every Radio manual contains large schematics, all needed alignment facts, parts lists, voltage values, trimmers, dial stringing, and service hints. Each TV manual is a practical treatise on servicing the year's sets, with giant blueprints, patterns, waveforms, charts, suggested changes. See coupon at right for a complete list of these low-priced manuals.

NO-RISK TRIAL ORDER COUPON

SUPREME PUBLICATIONS, 3727 W. 13 St., Chicago 23, ILL.

Send the manuals checked below and at right. You guarantee satisfaction or money back.

- Simplified Radio Servicing by Comparison... \$1.50
- New 1951 Television Service Manual... \$3.
- 1950 Television Manual, \$3. 1949 TV, \$3.
- 1948 TV, \$3. 1947 TV & FM, only \$2.

Radio Diagram Manuals
 New 1951 Manual } Each Only
 1950 Radio Manual } **\$2.50**
 1949 Radio Manual

RADIO MANUALS
 1948
 1947
 1946
 1942
 1941
 1940
 1939
 1926-1938 Manual. \$2.50

PRICED AT ONLY \$2 EACH

I am enclosing \$..... Send postpaid.
 Send C.O.D. I am enclosing \$... deposit.

Name:

Address:


Supreme Publications

Sold by All Leading Radio Jobbers

IF YOU SERVICE IN ANY OF THESE AREAS . .

BINGHAMTON, BIRMINGHAM, BLOOMINGTON, BUFFALO, CHARLOTTE, DAVENPORT, ERIE, GRAND RAPIDS, INDIANAPOLIS, JOHNS-TOWN, KANSAS CITY, LANCASTER, NEWARK, NEW HAVEN, PROVIDENCE, RICHMOND, ROCHESTER, ROCK ISLAND, ST. LOUIS, SAN DIEGO, SCHENECTADY, SEATTLE, TOLEDO, TULSA, UTICA AND WILMINGTON . . .

or in areas
fringe to these cities . . .

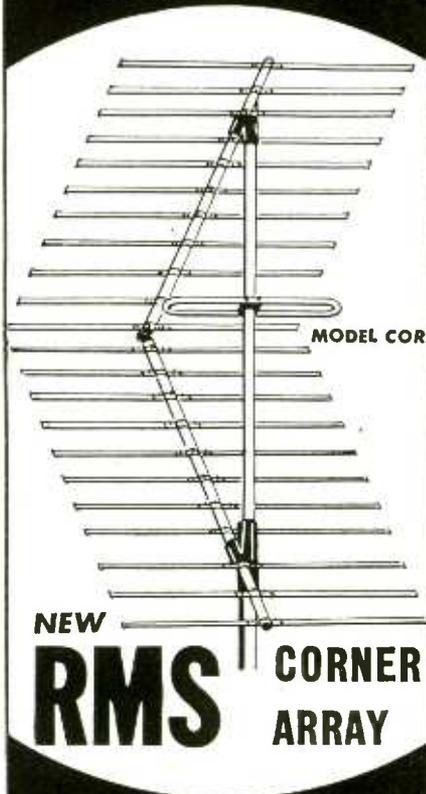

WILL GIVE YOU AMAZING TV RECEPTION RESULTS!


fringe and extreme fringe areas of these cities and similar locations throughout the country can now obtain snow-free television pictures with the Corner Array.

doubles television entertainment by producing sharp pictures from signals of a station fringe to these cities.

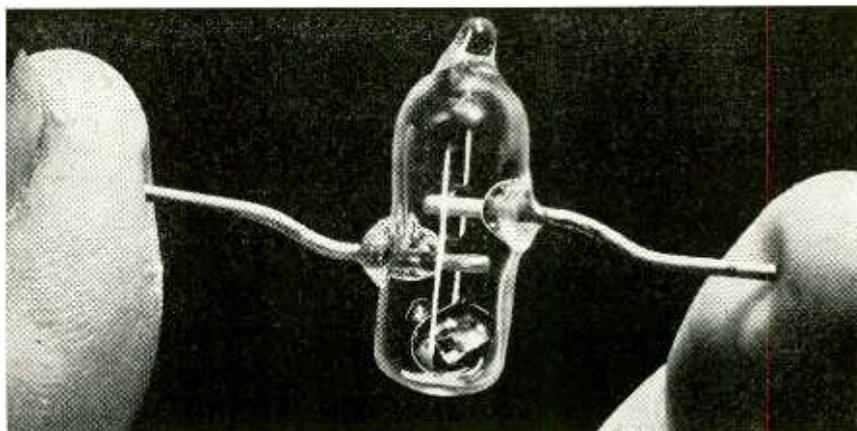Example: adds channel 13 (Johnstown) to the TV fare of Pittsburgh set owners.



RADIO MERCHANDISE SALES, INC.
NEW YORK 59, N. Y.



The large mercury globule insures positive, but momentary, contact across leads.

Small, Chatter-proof Interruptor Meets Special Switching Needs

Mercury contacts have proven their reliability for many years. From the control of refrigerators to oil burners, from operating the light in the glove compartment of automobiles to making a host of other contacts, mercury switches are an accepted and trustworthy element of construction.


Essentially all mercury contacts known heretofore either make or interrupt the electric current. A new contacting device has now been developed by Dr. Erwin J. Saxl, of the Saxl Instrument Company of Harvard, Mass., whereby the arrangement of electrodes and mercury is such that under no condition can the electrodes remain permanently connected in the pool of mercury.

Like all basic developments, his design is simple, as shown in the schematic patent drawing. The drop of mercury is at one end of a glass tube which is evacuated or filled with the proper gas for avoiding oxidation of the contacts. Upon tilting the glass tube, the mercury runs along it toward the other end. In doing so it passes by two electrodes adequately spaced from each other. During the short time while the mercury runs between them, both electrodes are connected and temporary contact is established. No possibility exists that the contact will remain closed. The contact is first established and positively extinguished thereafter, since the drop of mercury irrevocably passes beyond the contacting leads.

This device is self-healing. Having made and broken electric contact, the mercury accumulates at the other end of the tube and is ready for operation again.

The new contactor has a wide range of possible applications, which are best understood if we think of it as a relay turned inside out, in which a small amount of mechanical power releases a large pulse of electric power. As such, it may be used to make more efficient watt-hour meters—in which electric

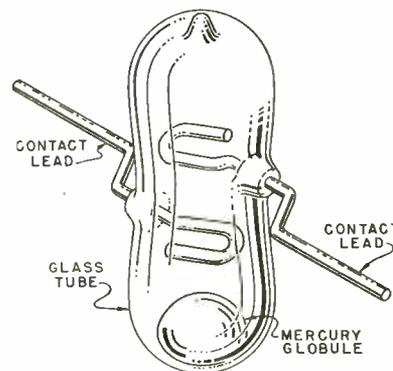pulses replace gearing—and has applications in counters and other equipment. It covers the gap between the heavy switching arrangement of electromechanical construction on one hand and photoelectric or electronic equipment on the other hand.



The new mercury momentary contactor.

As a speed governor the mercury contactor may be mounted with the axis of its electrodes at right angles to the axis of rotation of the member to be controlled. When the rotational speed diminishes to the point where the force of gravity exceeds the centrifugal force acting on the globule the liquid runs past the electrodes, makes contact, and allows energizing impulses (through a suitable electromechanical system) to be applied to the rotating member such as to bring it out of its stalling or dragging, overloaded condition.

Since under no conditions can the mercury remain between the two electrodes, interruption as well as contact is sharp and positive. Vibrating or frozen contacts are impossible. This may make it useful for vending machines, electrical coin changers, and other devices in which sticking or chattering contacts may result in loss or danger.

—end—

RADIO-ELECTRONICS for



LEARN PRACTICAL RADIO AT HOME!

Build 15 Radios

Build a Professional Signal Tracer
Build a Code Oscillator
and Learn Code!

COMPLETE, FOR ONLY

\$19⁹⁵

FREE!

• ELECTRICAL AND RADIO TESTER • RADIO TELEVISION SERVICING LESSONS • BOOK ON TELEVISION • MEMBERSHIP IN RADIO-TELEVISION CLUB • ELECTRIC SOLDERING IRON • CONSULTATION SERVICE • QUIZZES

10-DAY MONEY BACK GUARANTEE

ABSOLUTELY NO PREVIOUS TRAINING NEEDED • FREE TOOLS • NO ADDITIONAL PARTS REQUIRED
YOU KEEP ALL PARTS, TOOLS, INSTRUCTIONS • AN EXCELLENT BACKGROUND FOR TELEVISION

LEARN TROUBLE SHOOTING . . . THEORY . . . WIRING . . . CODE!

WHAT THE NEW IMPROVED 1952 PROGRESSIVE RADIO "EDU-KIT" OFFERS YOU

The Progressive Radio "Edu-Kit" offers you a home study course at a rock bottom price. Our kit is designed to train Radio Technicians, with the basic facts of Radio Theory and Construction Practice expressed simply and clearly. You will gain a knowledge of basic Radio Principles Involved in Radio Reception, Radio Transmission and Audio Amplification. You will learn how to identify Radio Symbols and Diagrams; how to build radios, using regular radio circuit schematics; how to mount various radio parts; how to wire and solder in a professional manner. You will learn how to operate Receivers, Transmitters, and Audio Amplifiers. You will learn how to service and trouble-shoot radios. In brief, you will receive a basic education in Radio exactly like the kind you would expect to receive in a Radio Course costing several hundreds of dollars.

THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The Kit has been used successfully by young and old in all parts of the world. It is not necessary that you have even the slightest background in science or radio.

The Progressive Radio "Edu-Kit" is used by many Radio Schools and Clubs in this country and abroad. It is used by the Veterans Administration for Vocational Guidance and Training.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions are included. All parts are individually boxed, and identified by name, photograph and diagram. Every step involved in building these sets is carefully explained. You cannot make a mistake.

THE PROGRESSIVE RADIO "EDU-KIT" IS COMPLETE

You will receive every part necessary to build 15 different radio sets. This includes tubes, tube sockets, variable condensers, electrolytic condensers, mica condensers, paper condensers, resistors, tie strips, coils, tubing, hardware, etc. Every part that you need is included. In addition these parts are individually packaged, so that you can easily identify every item.

TROUBLE-SHOOTING LESSONS

Trouble-shooting and servicing lessons are included. You will be taught to recognize and repair troubles. While you are learning in this practical way, you will be able to do many a repair job for your neighbors and friends, and charge fees which will far exceed the cost of the Kit. Here is an opportunity for you to learn radio and have others pay for it. You build a professional Signal Tracer which alone is worth more than the price of the complete Kit.

THE PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" comes complete with instructions. These instructions are arranged in a clear, simple and progressive manner. The theory of Radio Transmission, Radio Reception, Audio Amplification and Servicing by Signal Tracing is clearly explained. Every part is identified by photograph and diagram; you will learn the function and theory of every part used.

The Progressive Radio "Edu-Kit" uses the principle of "Learn By Doing." Therefore you will build radios to illustrate the principles which you learn. These radios are designed in a modern manner, according to the best principles of present-day educational practice. You begin by building a simple radio. The next set that you build is slightly more advanced. Gradually, in a progressive manner, you will find yourself constructing still more advanced radio sets, and doing work like a professional Radio Technician. Altogether you will build fifteen radios, including Receivers, Amplifiers, Transmitters, Code Oscillator & Signal Tracer.

THE PUBLIC APPROVES!

COMMENTS FROM SATISFIED USERS OF THE PROGRESSIVE RADIO "EDU-KIT"
VETERANS ADMINISTRATION,
PHYSICAL MEDICINE REHABILITATION SERVICE,
WASHINGTON, D. C.

"This morning I was showing the Progressive Radio 'Edu-Kit' to one of our representatives from our Branch Office in Richmond, and already he wants me to purchase some for his hospital. . . . As indicated in previous correspondence, I took the Progressive Radio 'Edu-Kit' to our Veterans Administration Hospital at Fort Thomas, Kentucky. Both instructors and patients worked them, and they proved quite satisfactory."

ROBERT L. SHUFF,
1534 Monroe Ave., Huntington, W. Va.

"Thought I would drop you a few lines to say that I have bought a Progressive Radio 'Edu-Kit' and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and radio-phonographs. Friends were really surprised to see me get into the swing of it so quickly. The trouble-shooting tester that came with the kit is really swell, and finds the trouble if there is any to be found. Everything you say about your kit is true."

DOMINICK STRAUZZA,
111 Clarence St., London, Ontario

"I am very satisfied with the Progressive Radio 'Edu-Kit' which I bought from you. I did not know anything about radio, but now I feel as though I have been in the radio business for years. Your kit is simple and educational. I enjoy working with it."

Order your Progressive Radio "EDU-KIT" Today, or send for further information.

Postage prepaid on cash orders—C.O.D. orders accepted in U. S. A.

COMPLETE, FOR ONLY

\$19⁹⁵

BECOME A RADIO AMATEUR



GET A WELL-PAYING JOB



GO INTO A PROFITABLE BUSINESS




PROGRESSIVE ELECTRONICS CO.

497 UNION AVE., DEPT. RE-55

BROOKLYN 11, N. Y.


FOR PERFECT PICTURE CENTERING IN ELECTRO-STATIC TUBES

Use the **NEW** PERFECTION *Kine-Center*

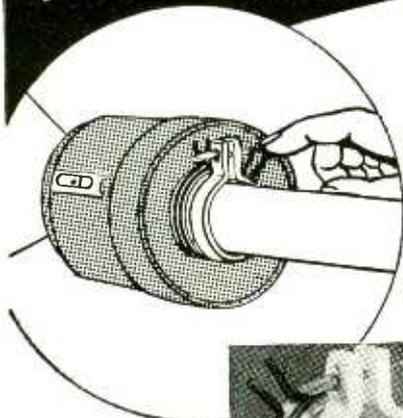

Here is the simplest of all centering devices for the new electrostatic tubes. It is also the most efficient and positive—as your own tests will prove.

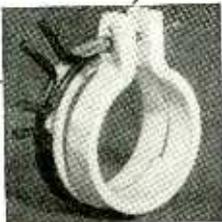- **Quickly Mounted.** Slip the Kine-Center over the tube neck and tighten the holding screw. It stays firm. No wobble. No wiggle.
- **Finger-Tip Control.** Picture is centered by rotating the two rings either independently or together.
- **Positive Centering.** Once adjusted, the rings stay put.
- **No Distortion of Focus** as with many other centering devices.




MORE EFFICIENT

Rings are closer to deflection yoke (the most effective operating area) and to the tube neck. They are stabilized magnetically.

Order today from your supplier!

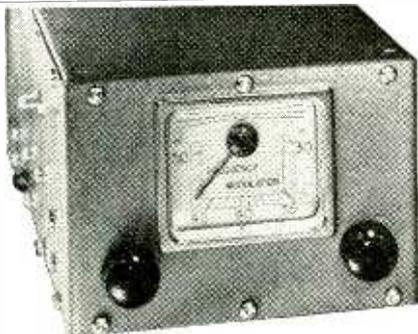PERFECTION ELECTRIC COMPANY
2635 South Wabash Avenue, Chicago 16, Illinois
MAKERS OF PERFECTION SPEAKERS AND TELEVISION COMPONENTS



**Model
M-51**

for emergency communications

USED BY HUNDREDS OF MUNICIPALITIES FROM BOSTON, MASS., TO ALHAMBRA, CAL.

POLICALARM MONITORADIO

Says S. L. Grant, City Manager, Winchester, Virginia . . .

"I think you have a receiver that is well built, and I see no reason why it should not be in demand by all public works departments that have a transmitter available."



Users of FM 2-Way Radio Communications equipment throughout the entire nation, find Polic-Alarm and Monitoradio a welcome innovation to low-cost mobile communications radio .

5 Models For All Systems
6 VOLT MOBILE

- M-51 Tuneable 30-50 MC
- M-101 Tuneable 152-163 MC

- 115 VOLT AC-DC
- PR-31 Tuneable 30-50 MC
- PR-8 Tuneable 152-163 MC
- AIRCRAFT
- AR-1 AM Tuneable 108-132 MC
- 115 Volt AC-DC

For Complete Information: See Your Jobber—Or Write Us Today

RADIO APPARATUS CORPORATION

55 N. NEW JERSEY ST., INDIANAPOLIS 4, IND., PHONE: ATLANTIC 1624


PHASE SPLITTER

Patent No. 2,571,431
Kurt Enlein, Rochester, N. Y.

(Assigned to Stromberg-Carlson Co.)

The 6BN6 tube is a gated-beam type. Its operation was described on page 78 of the Feb. 1951 issue. The tube is used here as a phase-splitter.

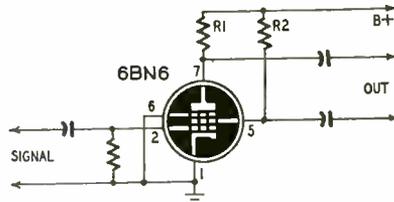The electron beam of the 6BN6 is focused to a narrow stream. Electrons pass through the control grids (pins 2 and 6) on the way to the plate. The tube construction is such that electrons cannot return to the cathode even when they are repelled by the grids. Those electrons which are prevented from reaching the plate are diverted to the accelerator, pin 5.



In this circuit, only the first grid is used to control the electron beam. When the r.f. or a.f. signal drives the grid negative, fewer electrons land on the plate but more are available at the accelerator. Plate output is out-of-phase with the control grid. Accelerator output is in phase.

To compensate for the lower Gm of the accelerator element, R2 is made larger than R1. The signals at each output terminal can be made equal as well as opposite in polarity.

TRANSISTOR FLIP-FLOP

Patent No. 2,569,345

Richard F. Shea, Syracuse, N. Y.
(Assigned to General Electric Co.)


Transistors make ideal flip-flop elements. Two transistor multivibrators were described on page 92 of the Sept., 1951, issue. A new circuit is even simpler and more effective because it contains no time-constant networks. It requires a pair of transistors in grounded-base circuits.

A transistor conducts when its base is *negative* with respect to its emitter. The transistor is blocked when its base is sufficiently *positive*. In this multivibrator, the base of each transistor is coupled to the collector of the other unit.

Initially, assume that TR1 tends towards *less* conduction for some reason. The negative voltage on C1 tends to approach the battery value, -45 volts. The increase in negative voltage is fed to B2. A more negative base permits greater conduction in TR2, so its collector passes more current. The negative voltage at C2 (and B1) is reduced. Therefore TR1 has a more positive base and it conducts even less. In a very short time TR1 is completely blocked and TR2 conducts fully. The multivibrator remains in this condition until it is disturbed by a positive pulse at A.

The pulse appears at the anodes of two rectifiers, X1 and X2. The first of these is biased beyond cutoff by the positive base, B1. The cathode of the second rectifier X2 is connected to B2 which is negative. Therefore X2 can conduct the positive pulse to B2. Now the transistors reverse action. TR2 conduction decreases towards cut-off and forces TR1 towards full conduction.

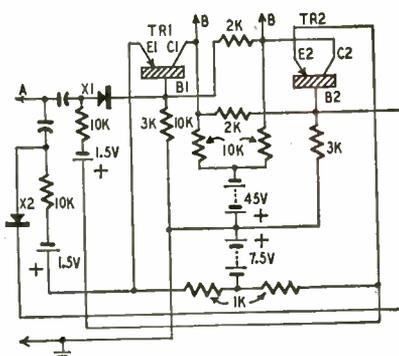The next positive pulse at A finds X2 blocked and X1 able to conduct. Therefore the pulse can affect only TR1. It blocks TR1 so that TR2 can conduct fully. Successive pulses trigger the multivibrator. If pulses are equally spaced, output (from terminals B) is a symmetrical square wave.



RADIO-ELECTRONICS for

Now! LONG DISTANCE TV RECEPTION
... from any direction
with the Flick of the switch


NEW 4 WAY TRIPLEX Wavemaster TV ANTENNA

Complete with:
 Antenna Mast • Ray-x Control Box
 125 ft. 300 ohm Lead-in Wire

\$15.45 Single Lots
\$14.45 Lots of Three

20% Deposit on C.O.D. Orders

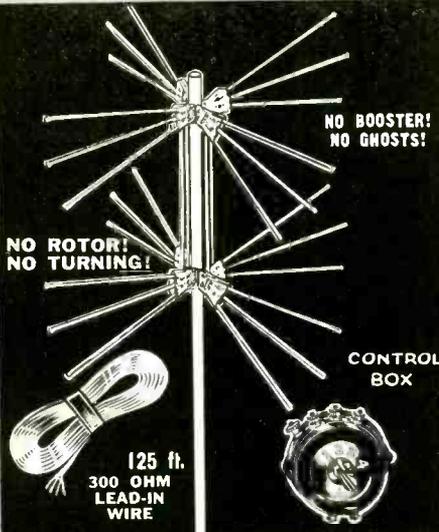Simply place control box near your TV set. Each of 4 positions opens up one complete antenna in the direction you want. Strong reception on all channels, eliminates ghosts, cuts down interference.



NO BOOSTER! NO GHOSTS!
NO ROTOR! NO TURNING!
CONTROL BOX
125 ft. 300 OHM LEAD-IN WIRE


"DIRECT FROM MANUFACTURER"

RAY CO.

WRITE • WIRE • CALL

441 Summit St.
 Toledo, Ohio
 Phone FA. 9171

3 New Custom-Built Deluxe TV Chassis

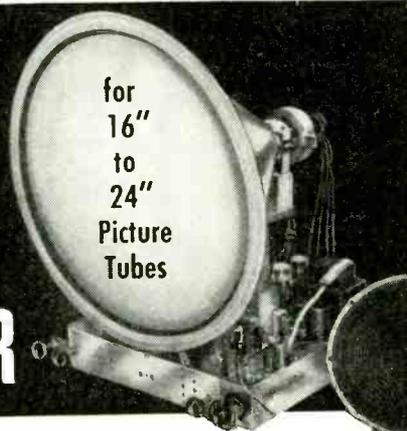

for 16" to 24" Picture Tubes

by **TECH-MASTER**

MODEL 2430—Designed specifically for all picture tubes requiring from 65 to 70 degrees horizontal deflection, (such as 24AP4, 20CP4, 19AP4, etc.) Supplied with quality PM speaker, and Universal Picture Tube Mounting Brackets & Phono Jack. \$189.50

MODEL 2431P—Similar to model 2430, but with Push-Pull Audio, True Fidelity Output and Universal Picture Tube Mounting Brackets. \$199.95

MODEL 2431C—Basically same as Model 2430 but with Continuous Tuner, Push-Pull Audio, True Fidelity Output and Universal Picture Tube Mounting Brackets. Allows complete coverage of both TV and F.M. bands. \$199.95

The new **Gold Medal Series** incorporates all the latest Tech-Master features which have made this improved 630 type chassis the standard by which custom-built TV is measured... performance and service are assured because Tech-Master design and construction are **as fine as human hands and brains can produce**. All chassis are supplied completely wired, aligned and tested with all tubes (less picture tube).

LOOK for your Tech-Master registration and guarantee card attached to each chassis... it is your assurance that you are buying a genuine Tech-Master receiver.

See the Gold Medal Series and other quality Tech-Master products at your favorite Radio Parts Jobber or write direct to Tech-Master Products Co., Dept. RE-1 for complete descriptive literature.




TECH-MASTER PRODUCTS CO.
 443-445 Broadway • New York 13, N. Y.

METER DAMPING CIRCUIT

Patent No. 2,567,688

John E. Bigelow, Schenectady, N. Y.
 (Assigned to General Electric Co.)

The damping of a d.c. meter determines how its indicator deflects. If the damping is high, the needle moves slowly towards its final position. If too low, the needle may oscillate before coming to rest. When damping is optimum, the needle deflection occurs in the shortest possible time and without oscillation. Damping is often controlled by a resistor shunting the meter. A low shunt provides heavy damping, and vice versa. Unfortunately,

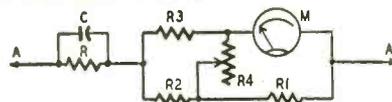

a change in shunt resistance affects the meter calibration. In the new circuit, damping is adjusted as desired without affecting the calibration.

The circuit includes a balanced bridge network with meter M as one of the arms. A paralleled R-C network is added in series with the bridge as shown. R and C are used to speed the initial deflection. When d.c. is fed between terminals A, a relatively large current charges C and flows into M. This "kicks" the needle and speeds it on its way.

The slowing down process is a question of damping. Since the bridge is balanced, no current flows through R4. This resistor may be adjusted without upsetting balance or the calibration of the meter. R4 controls damping, however, since it determines the total resistance shunting M.

R1 should be relatively low. It should provide more than sufficient damping when R4 is zero. Then, with the resistance of M and R1 known, the other bridge arms are chosen for balance. Finally, R4 is adjusted for desired damping.


REVOLUTION COUNTER

Patent No. 2,566,868

Domenico J. Allia, Worcester, Mass.

This instrument counts the revolutions of a disc or wheel without loading down the motion. It is applicable to testing watt-hour meters and similar equipment.

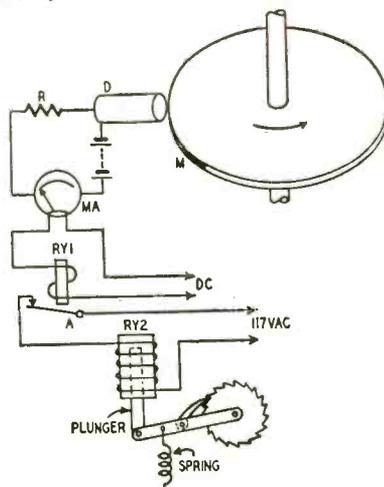A speck of radioactive material M is placed at the rim of the disc. D, a radiation detector, is positioned near the rim. At each revolution of the disc, the detector is energized once as M passes by. The detector output feeds a microam-



meter relay MA which closes a d.c. circuit containing RY1. RY1 attracts armature A.

When A closes its contact, RY2 is energized from the a.c. line. This lifts the plunger and advances a calibrated ratchet wheel.

RATE OF CHANGE METER

Patent No. 2,564,829


Leslie Herbert Bedford, London, and John Bell and Eric Miles Langham, Teddington, England.
 (Assigned to A. C. Cossor, Ltd., London)

This instrument indicates the rate at which a direct current is increasing or decreasing. If

RADIO-ELECTRONICS for

... is measured, a rectifier and filter are needed. In addition, a polarizing voltage may be added to prevent a change in polarity of the signal.

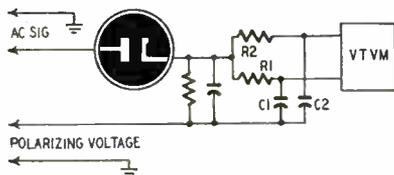The d.c. is impressed on R1, C1 and R2, C2, the first of which has a smaller time-constant than the second network. If the d.c. remains constant, C1 and C2 charge to the same voltage. When the meter remains at rest. Preferably the a.t.v.m. is of the center-zero type.



If the d.c. increases, C1 charges before C2 and the meter shows a deflection in one direction. A decrease in voltage causes C1 to discharge before C2. Therefore the meter needle deflects in the opposite direction. In either case a more rapid range is shown by a greater deflection.

IMPROVED FACSIMILE TRANSMISSION

Patent No. 2,564,556


Maurice Artzt, Princeton, N. J.

(Assigned to Radio Corp. of America)

This invention eliminates distortion due to telephone lines. Relatively high frequencies, say 20,000 cycles, travel much more slowly than those of a few hundred cycles. This factor is negligible on voice communication, but facsimile and telephoto images are seriously affected.

The figure shows a transmitter and a receiver (not shown), connected by telephone wires. A facsimile image is placed around a revolving drum (not shown). A light beam scans the image as the drum rotates. The density changes modulate the reflected light which is focused on a PE cell. Output frequencies extend from 1,000 cycles to 0.

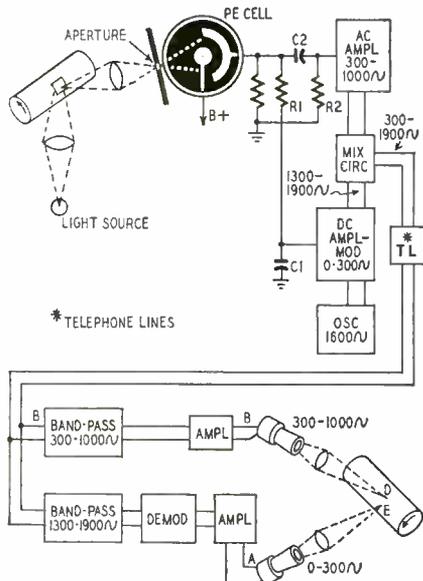
A low-pass filter, R1, C1, transmits 0-300 cycles which is marked band A. The high-pass filter R2, C2, transmits band B, from 300-1,000 cycles. A 1,600-cycle oscillator heterodynes with A. The beat (1,300-1,900 cycles) combines with B and both are fed to the phone lines. The transmitted range lies between 300-1,900 cycles.



At the receiver, the signal is divided as shown. Band B is amplified and fed to a recording lamp focused at point D on the rotating drum. The frequency portion between 1,300-1,900 cycles is demodulated to give band A. This is focused at point E by a second recording lamp. Note that E is ahead of D on the drum.


Band A is carried on the telephone lines by a carrier of 1,600 cycles. Therefore the time-delay in transmission is greater than for band B. This lag is balanced out by adjusting point E ahead of D. When the adjustment is correct, distortion is minimum.

—end—

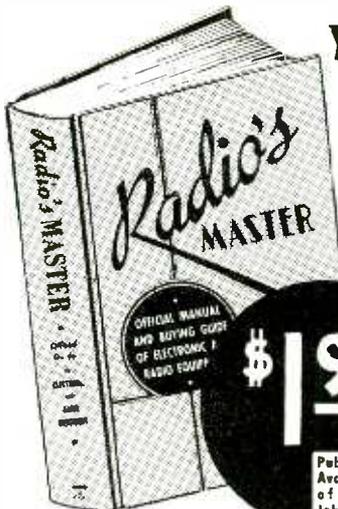

You'll find it **FASTER** in the **MASTER**

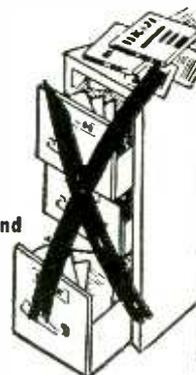No More Files of Small Catalogs and Loose Literature



Publisher's price \$6.50. Available at special price of \$1.95 thru Parts Jobbers who absorb part of cost for privilege of printing ad on cover.

Industry's OFFICIAL Buying Guide of Radio-Electronic-Television parts and equipment.

- 1100 Pages
- Hard Cover
- Fully Indexed
- Over 75,000 Items
- Over 7000 illustrations
- Weight—5 lbs.
- Size—8¼ x 10¾"
- Serving the Industry 16 years

When you **BUY--SELL--SPECIFY** you must have the **MASTER**

This single volume replaces all other small catalogs


Over 90% of the products manufactured in the Radio-Electronic-Television Parts and Equipment Industry are catalogued in this BIG 1100 page MASTER Buying Guide. Complete descriptions, with specifications and illustrations are written and compiled by each manufacturer covering such products as: tubes, instruments, TV parts, transformers, capacitors, resistors, test equipment, relays, coils and antenna equipment. Also, recording and PA systems, intercoms, tools, hardware, switches and thousands of associated products. IT'S YOUR "RADIO BIBLE"—SAVES YOU TIME AND MONEY.

BE MASTER-Minded—GET your copy NOW

NEW — 16th Edition available from local Parts Distributor at the special \$1.95 price.

UNITED CATALOG PUBLISHERS, INC. 110 Lafayette St., New York 13, N. Y.

OAK RIDGE CRT TESTER

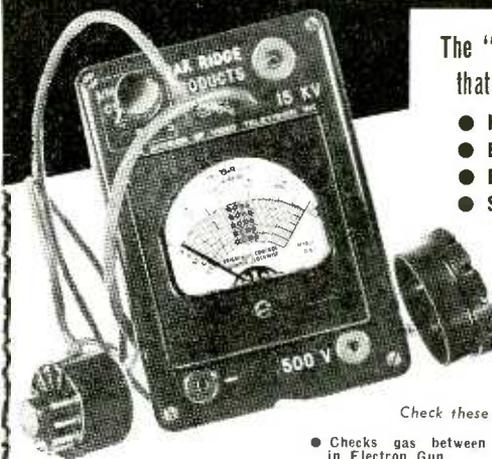

The "CATHETTE" is the ONLY CRT Tester* that checks ALL the following:

- HIGH VOLTAGE BREAKDOWN
- BEAM CURRENT MEASUREMENT
- ELECTRON GUN CONDUCTANCE
- SHORTS BETWEEN ANY ELEMENTS

Ask to see this INDISPENSABLE new tool at your nearest jobber. You'll agree that it's a MUST for every TV Serviceman today!

MODEL 106 "CATHETTE" CRT Tester, net. **\$29.95**

*Pat. applied for.

Check these additional "Cathette" Features:

- Checks gas between elements in Electron Gun
- Checks gas between High Voltage Anode and Electron Gun
- Checks conductance between Cathode, Control Grid, and Screen Grid
- Checks filament continuity
- Checks high voltage on Anode
- Checks Screen to Control Grid voltage from set
- Checks Control Grid to Cathode voltage from set
- Checks leakage
- Tests and positions Ion Trap
- Checks brightness control voltage
- Easy-to-read calibrated DC Voltage scales (0-500V, 0-15KV)
- Easy-to-read tube test scales
- Supplied with duo-decal plug and socket. (Special adaptors available as accessories)
- Pocket size: 5½x3¾x2¼". Shil. wt. 3 lbs.

MODEL 108 POWER SUPPLY (Pocket size, same as above.) Used in conjunction with Cathette CRT Tester, permits testing of Picture Tubes in carton! **\$19.95** net

Send NOW for your copy of our complete, new catalog, illustrating and describing the above equipment, as well as all other OAK RIDGE TV Test Instruments. Cable Address: "UNIONTEX" N.Y.

OAK RIDGE PRODUCTS
37-01 Vernon Blvd. Long Island City 1, N. Y.
Mfg Division of VIDEO TELEVISION, INC.

Oak Ridge Products, Dept. C
37-01 Vernon Blvd., Long Island City 1, N. Y.
Please send your complete new OAK RIDGE Catalog at once, to:

Name.....
Address.....
City..... State.....



for flawless reproduction
**NO OTHER CARTRIDGE CAN
 PERFORM LIKE A PICKERING**

Pickering patented design
 provides **DYNAMIC COUPLING***
 throughout the entire audible range

*** DYNAMIC COUPLING ASSURES**

- constant stylus contact with the record grooves over the entire audio spectrum (20-20,000 cps)
- full frequency response
- full transient response

**NO RESONANCES
 NO MISTRACKING
 NO GRINDING OF GROOVE WALLS**

Well-informed engineers and technicians, schooled in the science of electro-mechanics, know that only wide-range frequency response provides full transient response; the electronic phenomena which enables the reproduction of orchestral music with all the subtle sounds that give each musical instrument its individual character.

Pickering engineers and designers have but one objective . . . to produce products that will please the music lovers' insatiable appetite for the flawless recreation of recorded music . . . for the utmost in quality insist upon Pickering Audio Components.


Pickering Cartridges transmit all of the sounds in the musical spectrum, without loss of definition, just as a fine optical lens passes all of the colors in the rainbow.

For literature address Dept. p



AMPLIFIER FOR TV AUDIO

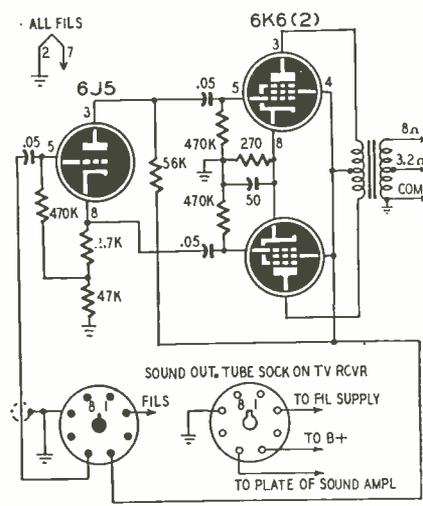Television service technicians and set owners have long bemoaned the fact that the sound systems of most TV sets leave much to be desired. The compact little amplifier illustrated offers a rather novel solution to this deficiency. The amplifier (small enough to be mounted in most cabinets) employs a pair of 6K6 tubes in push-pull driven by a 6J5 cathode-follower.



Power is obtained through a cord and plug which is inserted in the final audio stage of the TV set. Provision is made on the unit for 3.2- or 8-ohm voice coils. The leads from the speaker voice coil to the old output transformer are disconnected and transferred to the output of the unit. Field coil leads, of course, remain undisturbed. (This unit is not usable on sets where output tube currents flow through the focus coil or where the audio output cathode supplies bias or operating voltage for other stages.—*Editor*)

For best results the makers of the device, Vidair Electronics Manufacturing Company, suggest replacing the old speaker with a large good-quality one.

HANDY TEST-LEAD SWITCHING

We often see radio and TV service benches cluttered with snarls of test leads dangling from a number of different test instruments. You can eliminate this by using one set of test leads and a 2-circuit rotary switch having at least as many positions as there are test instruments. The negative test lead connects to the arm of one switch section and the positive lead to the other. The negative or ground leads from the various instruments connect to the taps on the section of the switch connected to the negative test lead, and the positive or hot leads connect to taps on the remaining section of the switch.

I have seven instruments connected in this way to an 8-position switch. The unused position disconnects the test leads from all instruments. This system saves wear and tear on test leads, but it does not work out well when two instruments are needed at the same time. —*R. C. Sandison*

RADIO-ELECTRONICS for

TUBES Every Critical Type

WE BUY FIRST QUALITY TUBES FOR CASH!

Fully Guaranteed • Brand New • Immediate Delivery

.59	.69	.79	.99	1.29
5U4G 5Y3GT 6AL5 6AU6 6AV6 6BE6 6J5GT 6K5GT 6K6GT 6W4GT 35W4 35Z5GT	1R5 1U4 354 3V4 6BA6 6SA7GT 6SK7GT 6SN7GT 6V6GT 6X5GT 6B86 12AT6	1B3GT 3Q4 12AU7 12SA7GT 12SK7GT 12SN7GT 12SQ7GT 35L6GT 50L6GT 6CB6 6BH6 25L6GT	1X2A 5V4G 6BC5 6AG5 6AC7 6J6 6T8 6AB4 12AV7 12BH7 12SC7 12SG7	6AH6 6BG6 6CD6 6BQ6 6BN6 6AK5 12AT7 19C8 19T8 25BQ6 19BG6 70L7GT

300-ohm twin lead, pure copper and polyethylene, \$19.50 per thousand feet, 1500 feet to a roll.

TERMS: Orders for less than \$25.00, add 10% to above prices. 25% deposit with order, balance C.O.D. F.O.B. New York City.

All Merchandise Subject to Prior Sale.

Supreme Radio & Television Co.
 136 Liberty Street, New York 6, N. Y.

RADIO ENGINEERING DEGREE IN 27 MONTHS

Intensive, specialized course including strong basis in mathematics and electrical engineering, advanced radio theory and design, television. Modern lab. Low tuition. Self-help opportunities. Also 27-month courses in Aeronautical, Chemical, Civil, Electrical, and Mechanical Engineering. Approved for G.I.'s. Enter, March, June, Sept., Dec. Catalogue.

INDIANA TECHNICAL COLLEGE
 151 E. Washington Blvd., Fort Wayne 2, Indiana

SENDING CODE RECEIVING SPEED

Be a "key" man. Learn how to send and receive messages in code by telegraph and radio. Commerce needs thousands of men for jobs. Good pay, adventure, interesting work. Learn at home quickly through famous Candler System. Qualify for Amateur or Commercial License. Write for FREE BOOK.

CANDLER SYSTEM CO.
 Dept. 3-A, Box 928, Denver 1, Colo., U.S.A.

CABINETS!! CABINETS!!

Sturdy wood; slide-rule dial onp.
 Type "A"—Ivory. Inside: 10 1/4"x6 3/4"x5 1/2".....\$1.49
 Dial: 1 3/4"x6 3/4"
 Type "B"—Mahog. Inside: 17 7/8"x10 1/4"
 Dial: 1 1/2"x10 3/8"..... 2.49
 Type "C"—Mahog. Inside: 14 1/4"x6 3/4" sq.
 Dial: 1 3/4"x6"..... 1.95
 Type "D"—MIDGET CABINET & CHASSIS. Pol.
 Walnut Ideal for Small Radio, Amplif., Oscill.,
 Intercom., Test Equip., etc. Inside: 7 3/8"x5 1/2"x4"
 Ready-punched 4 mini-tube chassis.....set 1.49

Leotone

Philco LP Cartridge . . . moulded bakelite, 3/4" sq. x 3 1/8".....\$1.49
 3/16" Sheet Felt (36" wide) . . . 35c sq. ft.
 DM-36 Dynamotors . . . 24V-220V, 80ma. 2.95
 TU-17A Tuning Units (BC223) . . . 2-3Mc. 2.49
 BC-746A Tuning Units (SCR-511) . . . 3655 or 4780 Kc. Less stals. Either. 69c 3 1.98

"Alnico Magnet" Special . . . Set of two 5/8" O.D. Bar magnets, 4 1/4" & 1-5/16" in wood box. \$2.29

AC-DC Blower (Delco) . . . 5400 RPM, 27V, 1 1/2A, Shunt, 3" fan blade, 1/4" dbie. shaft, 4 3/4" l. . . \$3.95
 RPD Bat Toggles (AHI) 49c 6 2.49
 6A/125V 49c 6 2.49
 20 Push-Back Wire . . . Red, Yel., Blue, or Black . . . 100 ft. / .89
 MS-53 Mast Sections . . . fit to any lgh. . . 39c 6 1.98
 Selenium Rect. . . F.W. Bridge, 600ma, 18V AC 1.29
 Cabinet Draw Slides . . Ball-bearing; 13" (8V ext.) . . \$2.10; 15" (11") \$2.25; 16 1/2" (12 1/2") . . . 3.25
 Heavy duty, all-steel 16 1/2" (12 1/2") . . . 3.25
 Cabinet Lid Support (stay hinge) . . . Holds at any angle to 70°. Bronze finish. 49c 6 2.49

1" Jewel Ass'bly . . . amber, DC bay. 6/51.98
 W-110B Field Wire . . . 1/2 MILE coils, Exc. condition. Shpg. wt. 70 lbs. Several lghs. coil. . . 5.95
 Nichrome Heater Elements . . . 660W. . . 2.3c 5 1.00
 1/2 Meg. Controls & Switch . . . 1/4" shaft. 39c 6 1.98
 50W. Rheostats . . . 1250 or 1800 ohms. Each. . . 1.69
 50W-15 Ohm Rheostat 69c 10 6.50
 25W-350 Ohm Rheostat . . . steel case; brass knob 1.89
 Crystals . . . IN21. 69c 10 6.50
 IN23 \$1.29 10 10.00

!! BARGAIN KITS !! . . . NEW "JUMBO RADIO PARTS KIT"—17 FULL LBS. OF: COILS, WIRE, RESISTORS, SOCKETS, CONDENSERS, CHASSIS, SWITCH, ETC., ETC. Shpg. wt. 21 lbs. . . . \$3.95
 Moulded Bakelite Condensers 0.00001 to .02 mfd. 200-900V. Kit of 30 ass'd. 1.98
 Rotary Selector Switches . . . multi-deck, multi-contact. Kit of 6 ass'd. 1.75
 Knobs . . . spring, setscrew. Kit of 25 ass'd. 98
 Water Sockets . . . 4 to 8 pin. Kit of 12 ass'd. 49
 Radio Hardware Treasure . . . FULL LB. of: Nuts, Screws, Washers, Lugs, etc. . . . 69c 3 lbs. 1.98
 Mica Padders & Trimmers . . . Kit of 15 ass'd. 79

(WRITE FOR "ALNICO MAGNET" SUPPLEMENT)
 "FACTORY SPEAKER REPAIRS SINCE 1927"
 Min. Order \$3.00 . . . 20% deposit on all COD's
 Please add sufficient postage—excess refunded
 Full remittance with foreign orders

LEOTONE RADIO CORP.
 67 Dey Street
 New York 7, N. Y.

DID YOU GET IT? IF NOT
SEND NOW FOR B-A's 136 BIG PAGE FREE CATALOG

RADIO TELEVISION ELECTRONICS
 1952

B-A

INCLUDING 21 PAGES OF DOLLAR-SAVING BARGAINS!

BURSTEIN-APPLEBEE CO.
 1012-14 McGee St.
 Kansas City 6, Mo. **FREE**


Send your 1952 catalog to:

Name.....
 Address.....
 City..... State.....

BURSTEIN-APPLEBEE CO.

FLUX SAVER

Most radio service technicians have a can of soldering paste on the workbench for those tough soldering jobs. A brand new can of flux is always a pleasure to use because it is nice and clean. But it doesn't take long for the flux to become contaminated with dirt and small pieces of wire and solder because it seems that most technicians are always *too* busy to replace the cover when the job is completed.

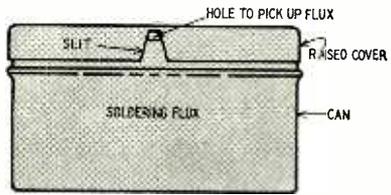


A simple solution to the problem is to cut a slit in the side of the cover (see drawing) so it can be left on the can in the raised position. This allows solder to be inserted to pick up flux and transfer it to the work. Besides keeping out dirt, the slit prevents picking up too much paste. Too much paste can do more harm than good. It produces a messy job and is often the cause of leakage, noisy contacts, intermittents, and other troubles.—George H. Hague

V.H.F. ANTENNA TERMINALS

After a few months exposure to the elements, terminals on TV and other v.h.f. antennas usually are so badly corroded that they cannot be loosened. To eliminate this trouble and to avoid high-resistance connections, I coat all terminals, nuts, and bolts with battery-terminal sealing compound. This protects the terminals against weathering and the coating is easy to strip off when necessary. It can be purchased at most automotive supply stores.—Leonard Pfeiffer


IMPROVING A.C.-D.C. FILTERS

A high residual hum level is one of the undesirable characteristics of most inexpensive a.c.-d.c. radios and phonographs. If the set has an electromagnetic speaker, the 60- or 120-cycle component in the d.c. feeding the speaker field coil will produce hum in the output. If there is ripple on the d.c. line feeding the plate of the output tube, it will produce a pulsating magnetic field which may affect the field of a PM speaker, which is usually placed close to the output tube.

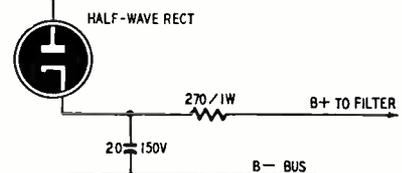

Note that in either case the hum is caused by d.c. ripple rather than a.c. pickup from the power line or heater string. Hum of this type can be greatly reduced or eliminated by attenuating the ripple component of the d.c. supply. The simplest method of doing this is to install a simple R-C filter right at the

Become an **Electrical Engineer**

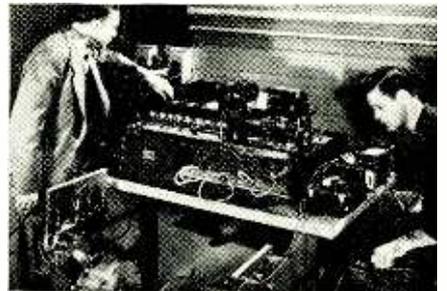

MAJOR IN ELECTRONICS

- B. S. Degree in 36 Months
- Radio-Television Technician Certificate in 18 Months

Experts predict that by 1954 there will be at least two positions for every engineering and technician graduate. This College offers a tested plan that permits you to enter these vast employment opportunities at an early date. First — you save a valuable year through optional year-round study. Second — you can receive advanced credit for prior training gained in the armed forces, other schools or field experience.

Enter Both Radio and Television Through This Plan

12 months or one-third of the B. S. degree course (Electronics major) — also brings you the Radio Technician's certificate. An added 6-month course qualifies you for the Radio-TV Technician's Certificate.

The Famous "UNIT CHASSIS SYSTEM"



of teaching was developed here. It "breaks down" the TV set by stages. You learn every component of all types and makes — and are prepared for future design changes, including the advent of color.

SPECIAL! Television Clinics

Ambitious Radio and TV Servicemen can enrol now in special one-month spring or summer clinics — to handle latest field service problems. Write for full details. Over 48,000 former students from all states and 23 overseas countries. Faculty of trained specialists. Modern laboratories and equipment. Nonprofit technical institute and college in its 49th year.

MILWAUKEE SCHOOL OF ENGINEERING

Terms open April, July, October, January
 FREE — Write for "Occupational Guidance Bulletin," "Your Career" booklet, and Catalog.

Milwaukee School of Engineering
 Dept. RE 152, 1025 N. Milwaukee
 Milwaukee, Wisconsin

Without obligation send Catalog for
 Electrical Engineering, B. S. Degree,
 Major in Electronics Power "Your Career"
 Occupational Guidance Bulletin on: Radio-TV Electrical Power Welding Heating, Refrigeration Air Conditioning.
 TV Service Clinic.

Name..... Age.....
 Address.....
 City..... Zone..... State.....
 If veteran, indicate date of discharge.....

4 SENSATIONAL VALUES

for immediate delivery from stock

NOT KITS but completely wired and factory guaranteed instruments


TEST-CRAFT Model TC-10 Quality Multitester



Only \$12.85

AC and DC Voltage Ranges: 0-5/15/150/1500/3000 Volts. DC Current Ranges: 0-5/50 ma. 0-1.5 Amps. Resistance Ranges: 0-100 ohms, 0-100 K. Size: 6"x3 1/2"x2". Complete with batteries and full instructions.

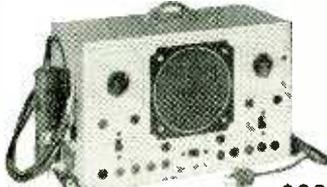
TEST-CRAFT Model TC-75 Combination Test Speaker and Signal Tracer



Only \$29.50

plus speaker substitution plus resistor tester plus condenser tester plus output indicator. plus field substitutor plus voice coil substitution. Complete with full instructions.

TEST-CRAFT Model TC-50

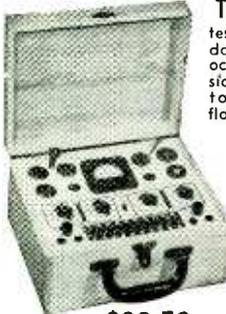

Tube and Set Tester tests all tubes up-to-date incl. 4, 5, 6, 7L, octals, loctals, television, magic eye, thyratrons, single ended, floating filament, mercury vapor, new miniatures, etc.

Multimeter Specifications: AC and DC Voltage Ranges: 0-1-100-1000-5000 DC Current Ranges: 0-10/100/1 Amp. Low Resistance Range: 0-10,000 Ohms. Medium Resistance Range: 0-100,000 Ohms.

Only \$39.50

High Resistance Range: 0-1 megohm. Complete with test leads and full instructions

MODEL 999 Combination Television, F.M. and A.M. Signal Generator and Signal Tracer



Only \$28.85

Generates R.F. frequencies from 150 kilocycles to 50 megacycles. Battery operated, no external source of current required. Positive action attenuator provides effective output control at all times. R.F. is obtainable separately or modulated by the Audio Frequency. Complete with test leads and full instructions 25% with order, balance C.O.D. or full check with order.

METROPOLITAN ELECTRONICS & INSTRUMENTS CO.
Dept. E
106 Fifth Ave., New York, N.Y.


cathode of the rectifier—ahead of any other filter components. A typical R-C filter is shown in the diagram. The filter should consist of the largest capacitance which can be used without raising the peak voltage or current to dangerous proportions and the highest resistance which can be employed without causing a noticeable reduction in the d.c. supply voltage at the output of the filter.

The values which produce the most effective filtering in most cases are 20 μ f and 270 ohms. Adding a simple filter of this type will greatly decrease the hum level of almost all a.c.-d.c. sets—even new ones.—David Gnessin

AMPLIFIER MODIFICATIONS

Many low-power PA systems—particularly those of prewar vintage—are equipped with electrodynamic speakers connected to the amplifier through a three-wire cable connected as shown at *a*. The disadvantage of this system is that all the speaker leads are at B-plus potential. There is a constant danger of someone being shocked or the power supply being short-circuited should one of the cables or connectors become exposed. This happens quite frequently in portable equipment where the cables are often laid out on the ground or floor where they are subjected to rubbing and scuffing.

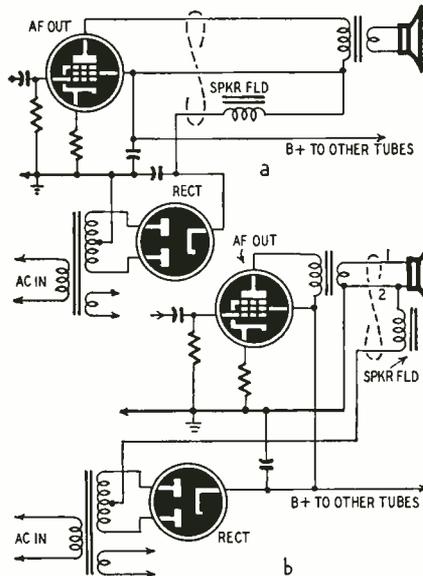The possibility of one receiving a shock or of short-circuiting the power supply can be eliminated by rewiring the circuit as shown at *b*. Here, the output transformer is moved to the amplifier end of the cable and the speaker field is connected in series



with the negative leg of the power supply. The three leads are at or near ground potential. An added advantage of this arrangement is that one side of the voice coil is grounded and the other is convenient for connecting an inverse-feedback network. This would not be possible with the arrangement at *a* without running two extra leads in the speaker cable.—Charles Erwin Cohn

—end—

NEW!



MOSLEY ROOF-THRU

The Leak-Proof Roof Entrance for TV and FM Transmission Line and Rotator Control Cable

Here's the new ROOF-THRU, another MOSLEY product for BETTER TV PICTURES Through More Efficient Installation. ROOF-THRU provides the easiest and most practical method of bringing in lead-in for concealed-in-wall installations using MOSLEY Flush Mounted Sockets.

Why the ROOF-THRU Way Is Best:

- Permits shorter lead-in line resulting in less loss of signal energy—less interference pick-up!
- Copper flashing and plastic bushing provides perfect seal against leaks!
- Prolongs life of transmission line by keeping it out of weather!
- Eliminates unsightly wires on outside of house!
- Long lasting—weather can't hurt ROOF-THRU!
- Easy to install on new or old buildings!

Cat. No. 624 MOSLEY ROOF-THRU

List Price \$5.84

See the ROOF-THRU and MOSLEY Flush Sockets at your jobber

MOSLEY ELECTRONICS
2125 Lockland Road, Overland, Missouri

AUDIO TRANSFORMERS

AT-501	Hi-Fi Special: PRI: 3000 ohms I P/Sec: 4/16/12/70-00 ohms 60-10,000 Cy—1 lb 50W as shown \$3.49	
AT-152	Hi-Fi Driver PRI: 10,000 ohms sec: 40,000 ohms PU grids 50-15 KC—1 lb 1.49	
AT-063	Output to I.S. or Line PRI: 14,200 ohms SEC: 8000/600 ohms	1.19
AT-666	Intercom Input: Spkr. (-4-8 ohms) to Grid (250,000 ohms)	.69
AT-415	Plate (18,000 ohms C.T.) to Line (125 ohms) 175 Watts—500-600 Cy	1.95
AT-858	Plate (10,000 ohms C.T.) to Line & V.C. 500/125/30 ohms HI-FI—50W	6.95
AT-070	Mike-or-Line (250 ohms) to Grid (250,000 ohms C.T.)	1.29
AT-765	Mike-or-Line (600 ohms) to Grid (50,000 ohms C.T.)	.89
AT-449	HI-FI Driver (5000 ohms) 100-10,000 Cy, 10 Watts. 6V6 to PP805's	2.39

B-19 MK II TRANS. RECEIVER	ARC5 MODULATOR MD7/ARC5 Plate Modula for w/dyna motor complete w/Tubes 1-1213 2-1625 1-VR50. Good cond.	Price \$7.95
Less Power Pack. \$32.50		
B-19 Power Pack. 8.95		
ID-24 ARN-9		
Dual 0-300 Micro-amp Movement in 3' Case IIS Equipment \$6.95		

F. W. BRIDGE SELENIUM RECTIFIERS

UP TO 18 VAC IN—UP TO 14 VDC OUT	UP TO 36 VAC IN—UP TO 28 VDC OUT
2A \$2.50	1A \$3.00
1A 4.00	2A 4.00
5A 6.00	4A 8.00
10A 7.50	10A 14.50
15A 9.00	12A 18.00
21A 18.00	24A 36.00
Hi-Current Chokes	
1 HY—12 Amp—16 Ohms \$14.95	
01 HY—15 Amp—2.25 Cased \$3.75	
Low-Voltage Transformers	
Primaries 115v. 60 Cycle	
36V-40V at 3.75 amps \$3.75	
24V 1.5A 1.95	2A \$11.00
8v 1.5A .98	10A 48.00
16v 3A 3.75	12A 60.00
	UP TO 54 VAC IN—UP TO 42 VDC OUT
	2A \$6.50
	4A 8.50
	UP TO 120 VAC IN—UP TO 100 VDC OUT

Rated Concerns Send P.O. Minimum Order \$3.00
Send M.O. or CHK. Mds. Guard. Shpg. Charges
Sent C.O.D. Price F.O.B. N.Y.C. Phone Di. 9-4124
COMMUNICATIONS EQUIPMENT CO.
131 Liberty St. Dept. C-1 New York City 7, N. Y.

7 HARD TO GET ITEMS AT BIG SAVINGS TO YOU

AMAZING BLACK LIGHT



250-watt ultra-violet light source. Makes fluorescent articles glow in the dark. Fits any lamp socket. For experimenting, entertaining, unusual lighting effects. Ship. wt. 2 lbs.
ITEM NO. 87
A SAVING AT **\$2.45**

POWERFUL ALL PURPOSE MOTOR



Sturdy shaded pole A.C. induction motor. 15 watts, 3000 rpm. 3"x2"x1 1/4"; 4 mounting studs; 7/8" shaft, 3/16" diameter; 110-120 volts. 50-60 cycles. A.C. only. When geared down, this unit can operate an 18" turntable with a 200 lb. dead weight. Use it for fans, displays, timers and other purposes. Ship. wt. 2 lbs.

ITEM NO. 147
UNUSUAL BUY **\$2.45**

WATTHOUR METER

Leading makes — completely overhauled ready for service. 100-110 volts, 60 cycles, 2-wire A.C. 5 amp. Heavy metal case 8 1/2" x 6 1/4" x 5". Easy to install. Ship. wt. 14 lbs.



ITEM NO. 33
NOW ONLY **\$4.50**

WESTERN ELECTRIC BREAST MIKE

Lightweight 1 lb. carbon microphone. Aircraft type. Breastplate mounting, adjustable 2-way swivel. Easily fastened straps. For home broadcasts, communications etc. Complete with 6 foot cord, hard rubber plug. Sherardized plate, non-rusting finish. Ship. wt. 2 lbs.
ITEM NO. 152
NEW LOW PRICE **\$1.75**

TELEPHONE TRANSMITTERS

Genuine transmitters made by Kellogg Western Electric Stromberg Carlson Work on two dry cells For P.A. systems, intercoms, other practical uses. Shipping weight 1 lb.



ITEM 160
REAL VALUE **\$2.45**

250 POWER TELESCOPE LENS KIT

Make your own high powered 6 ft. telescope! Kit contains 3" diam. 75" focal length, ground and polished objective lens and necessary eye pieces. Magnifies 50x to 250x. Full instructions. Ship. wt. 1 lb.
ITEM NO. 123
YOU SAVE AT **\$2.95**



HUDSON SPECIALTIES CO.
40 West Broadway, Dept. RE-1-52
New York 7, N. Y.

I am enclosing full remittance for items circled below. (Be sure to include shipping charges.)

OR, my deposit of \$..... Ship balance C.O.D.
MINIMUM C.O.D. ORDER \$5.00.
C.O.D. ORDERS ACCEPTED ONLY WITH 20% DEPOSIT
INCLUDE SHIPPING CHARGES.
Circle Items Wanted
87 147 33 152 160 123


Name..... Please Print Clearly
Address.....
City..... Zone..... State.....

Please mention
RADIO ELECTRONICS
when writing to advertisers

LOW-BAND TV BOOSTER

After reading and hearing a lot about the advantages of triodes over pentodes in TV boosters, I decided to construct one using push-pull triodes. The unit shown in the diagram and photos is my version of the booster described on page 64 of the March, 1949, issue and page 79 of the November, 1950, issue.

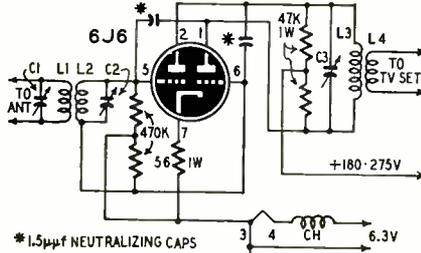I constructed the unit in a surplus jack box with a lucite platform at one end for mounting the antenna input terminals and trimmer capacitor C1.



*1.5µmf NEUTRALIZING CAPS
C1, C2, C3 = 3-30µmf
Other modifications include the use of National AR-5 coils for L2 and L3. L1 and L4 are 2 or 3 turns of insulated hookup wire wound in the grooves around L2 and L3. The unit is tuned with three 30-µmf air trimmers fitted with pointer knobs which make it easy to return to the correct settings for FM and low-band TV stations. Short lengths of No. 24 insulated wire twisted together were used as substitutes for the 1.5-µmf neutralizing capacitors shown in the schematic.

If you need a high-gain booster for the lower television band or for FM reception, you will probably find this one satisfactory in all respects.—*Augustine Mayer.*

SYNTHETIC BASS CIRCUIT

Various types of circuits have been designed to produce synthetic bass response from small, poorly baffled speakers by generating or emphasizing harmonics of low-frequency notes which are below the range of the amplifier or which cannot be handled adequately by the speaker and its enclosure. The ear, upon hearing the harmonics, is tricked into supplying the missing fundamental tone.

A novel means of producing artificial bass is described in *Wireless World* (London, England). The circuit is shown on page 144.

The audio signal applied to the input is amplified by V1, a 6SF5, one-half a 12AX7, or similar high-mu triode, and fed to the grids of V2 and V3. V2 is a conventional voltage amplifier having tone controls R1, R2, and R3 in its grid circuit to adjust the levels of the high medium, and low frequencies. A linear negative feedback voltage is fed to the cathode of V2 from the secondary of the output transformer.

V3 is the high-mu triode which may be of the same type as V1. It is fed through a low-pass filter which cuts off at about 100 cycles. V3 operates with zero bias and a high plate-load resistance. This condition produces grid-circuit distortion which results in the production of the desired harmonics.



2000 TV STATIONS SOON TO BLANKET NATION!

Get In On The Ground Floor Now!

LEARN TELEVISION BROADCASTING



2,000 new TV stations will urgently need trained men for Video Engineers, Technical Directors, Cameramen, Micro-Wave Engineers, Audio Engineers, Projectionists, Lighting Engineers, Remote Engineers

and other important TV Broadcasting jobs. They'll pay **BIG MONEY** for these men. NOW is the time for YOU to train for TV station jobs with this NEW course!

TRAIN AT HOME for BIG PAY and SECURITY!

You learn every phase of telecasting — operation, maintenance, installation—at home, in your spare time. You don't have to leave your present job and you learn the *right* way with T.C.I.'s non-mathematical *practical* training. Here's the *only* course all on technical and operational instruction.

COMPLETE, PRACTICAL TRAINING

You learn all circuits—RCA, Dumont, GE and others. You learn Micro-Wave relays, COLOR TV, UHF, Industrial TV, FCC Engineering Standards, Broadcasting Techniques, Network Operations and more. Lessons are written in language you know —without mathematics. You learn as fast or as slow as you like. Benefit by unique **FREE** Employment Service, **FREE** Consultation Service. Get details of T.C.I. TV Broadcasting training AT once!

FCC LICENSE GUARANTEE
T.C.I. positively guarantees to continue your training until you get your FCC license, no matter how long this may take.

T.C.I. ALSO OFFERS HOME-STUDY TRAINING IN TV SERVICING

You learn by doing! Course includes set conversion, master antenna installation, COLOR TV and CONVERSION, field servicing short cuts. You learn to test, trouble-shoot and repair. **Train on your own large screen TV receiver, furnished with course.** Get two weeks real field experience with Chicago's largest independent servicing organization (optional). **Age no barrier!** Get free facts on TV Servicing Course!

MAIL NOW FOR FREE FACTS

TELEVISION COMMUNICATIONS INSTITUTE

205 W. Wacker Drive, Dept. RE-7, Chicago 6, Ill.
Rush **FREE** facts on the course checked below! I am under no obligation. No salesman will call.

TV Broadcasting TV Servicing
 Pre-TV Radio for Beginners

Name.....
Address.....
City..... Zone..... State.....



Clearer, Brighter Pictures

when these transformers match antenna impedance to line, or line to TV receiver. Signal input may be improved as much as four times! Designed to couple low-impedance antenna to standard 300-ohm line; or 300-ohm antenna to 72-ohm twin-lead or low-loss 52-ohm coaxial cable. At receiver, low-impedance line matched to standard 300-ohm input. Housed in impregnated, weather-tight aluminum shield.

Dimension: 3/4" by 3/4" by 1-3/4"

Cat. No.	Impedance Ratio	List Price
6161	52/300 or 300/52	\$2.75
6162	72/300 or 300/72	2.75



See your Wholesaler or write us for literature

J. W. MILLER COMPANY
5917 S. Main St., Los Angeles, Calif.

• BUILDERS OF QUALITY RADIO INDUCTANCES SINCE 1924


The output of V3—those frequencies below 100 cycles plus the harmonics of each—is fed to the grid of V4, the power-amplifier tube. The signal which reaches the speaker is a mixture of the input signal—as shaped by the tone controls—and the artificial bass produced by V3. A switch is provided for cutting out V3 when desired.

This circuit works best when used with a speaker having bass resonance below 60 cycles. Resonance at about 30 cycles provides cleanest low-frequency output. The optimum size of the capacitor between grid and cathode of V3 varies with the type of speaker and the area of the front of the baffle. A 0.1- μ f unit is used with baffles in excess of 4 square feet. A .03- μ f unit should be tried if the baffle area is 1 square foot or less, and a .05- μ f for baffle areas between 1 and 4 square

feet. Increase the value of this capacitor if distortion is noticed with the middle-frequency tone control turned down.

V4, the power-amplifier tube, is British EL33. Its plate resistance is 50,000 ohms and load resistance 7,000 ohms, with 6 volts bias and 250 volts on plate and screen. Plate and screen-grid currents are 36 and 4 ma, respectively. Its transconductance is 9,000 ohms. Power output is 4.5 watts. An equivalent American-type power-amplifier tube may be used.

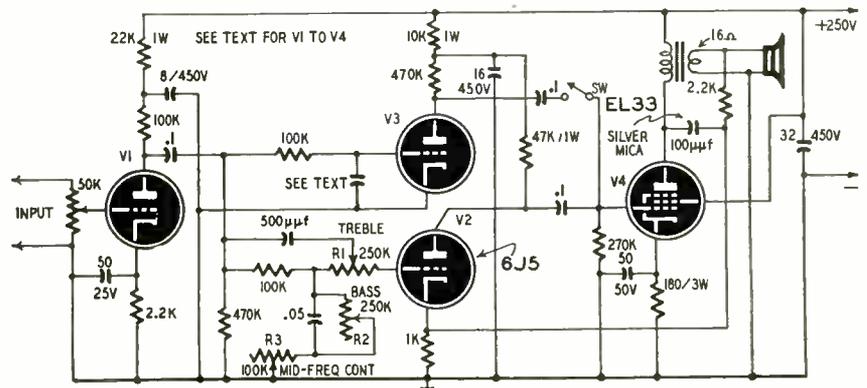The 2,200-ohm, 1-watt resistor in the feedback network is used with 16-ohm speakers and a 6SF5 or equivalent for V2. Try other values for best results. The 100- μ f capacitor between the cathode of V2 and plate of V4 compensates for leakage inductance of the output transformer at high frequencies.



ELECTRIC SOLDERING IRON

ROSE Co's SENSATIONAL FREE GIFT OFFER

TUBES SPECIAL SAVINGS ON ALL NUMBERS

RMA GUARANTEED—STANDARD BRANDS ONLY		SPECIAL SAVINGS ON ALL NUMBERS	
024	\$.59	6B07	\$.29
1A5	.89	6B08	.79
1A7	1.09	6B06	.89
1B3	1.19	6CD6	2.69
1H5	.79	6D6	1.09
1L5	1.19	6J5	.69
1R5	.99	6J6	1.29
1T4	.99	6K6	.79
1U4	.89	6L5	1.79
1V2	.69	6Q7	.99
1X2A	1.19	6S4	.79
3Q5	1.19	6S8	1.29
5U4	.79	6SA7	.79
5Y3	.49	6SK7	.79
6A6	1.19	6SN7	1.09
6AB4	.89	6SQ7	.69
6AC7	1.39	6T8	1.39
6AG5	1.19	6V6	.89
6AH6	1.89	6W4	.79
6AK5	1.89	6W6	.99
6AL5	.79	6X4	.69
6AQ5	.89	7C4	.89
6AT6	.89	7C5	.89
6AU5	1.29	7F8	1.59
6AU6	.79	12AL5	.69
6AV5	1.29	12AT6	.69
6BA6	.89	12AT7	1.29
6BC5	.89	12AU6	.89
6BE6	.89	12AU7	1.19
6BG6	1.39	12AV6	.69
6BH6	.89	12AV7	1.29
6BL7	.89	12AW6	1.29
6BN6	1.39	12AX4	1.09
6BQ6	1.49	12AX7	1.19
		12Y7	3.69

TV PICTURE TUBES

Full Year's Guarantee—Not Pre-Rent
Black Face—Brand New—Standard Brands—Sealed Cartons

10BP4	\$24.95	16GP4	\$31.95	19AP4A	\$37.95
12LP4	24.95	16HP4	33.95	20CP4	37.95
14BP4	24.95	17BP4	29.95	24AP4	69.95

ELECTROLYTIC CONDENSERS
All Guaranteed Fresh Stock

20x20-150 V.	\$.39	50x30-150 V.	\$.45
40x40-150 V.	.45	50x30-150 V.	.45
50x30-150 V.	.45	40x40x20-150 V.	.69
50x30x20-150 V.	.69	50x30x20-150 V.	.69
50x30-150 V. (200-25 V.)	.79	25-25 V.	.19
25-25 V.	.19	20-250 V.	.29
20-250 V.	.29	8-150 V.	.39
8-150 V.	.39	10-450 V.	.39
10-450 V.	.39	16-450 V.	.59

May be Ass't. for 100 Lot Price!



FREE This Superior Electric Soldering Iron. What every serviceman needs! Yours absolutely FREE! * Nickel Chrome Wire Heating Element * Handsomely Plated Shaft * U.L. & C.S.A. Approved

For a limited time, the ROSE Co. is offering, absolutely FREE, this wonderful new soldering iron to its customers. With each order of \$25, you get FREE this 75 Watt electric soldering iron. A \$50. order brings you a 100 Watt Soldering Iron or two (2) 75 Watt Irons. A 75W. iron for each \$25. order. Be sure to mention which iron you want with your order. Act quickly—order Now! **GET THIS SUPERIOR ELECTRIC SOLDERING IRON NOW—ABSOLUTELY FREE!** We're sorry that this offer cannot include TV chassis, Picture Tubes, or complete radios.

630 Super Chassis Bargain Priced for Terrific Savings! 30-Tubes—RCA lic.—For 16" to 24" Picture Tubes. * High efficiency high voltage circuit

- Keyed AGC
- Automatic brightness control
- Special extra-high gain standard coil tuner
- Directly adaptable for color
- 12" Quality speaker
- Factory wired, aligned & tested
- Complete, ready to play
- Including hardware & knobs **\$144.50** (less CRT)




630DX Chassis, 3-times normal reception of regular chassis. Needs no complicated antenna or booster. Reduced to (less CRT) **\$159.50** FREE OFFER: Schematic diagram FREE with any chassis ordered!

NOW AVAILABLE... FREE! Write for new catalog including complete listings of tubes, parts, accessories for radio and TV and special test equipment catalog for instruments and kits! MINIMUM ORDER \$5.00. 25% deposit with order, balance C.O.D. Include postage with order. All merchandise subject to prior sale. F.O.B. New York, N.Y. Price's subject to change without notice.

THE ROSE COMPANY 100 Park Place Dept. E-1, New York 7, N. Y. Cortland 7-6195

AUTOMATIC SQUELCH CIRCUIT

The squelch circuits shown are designed for use in sensitive receivers which have a high background noise level when no signal is being received. This *codan*—carrier-operated device, antinoise—was described by G. A. French in *Radio Constructor* (London, England). The circuit shown at *a* is designed for use with a plate-circuit relay having a 1,000- to 5,000-ohm coil and normally closed contacts. The relay is in the plate circuit of a relay-control tube which may be any convenient triode or triode-connected pentode. The grid of the tube is connected to the a.v.c. line of the receiver, and the relay contacts are connected in series with the plate of the first a.f. amplifier tube and B-plus. When no signal is being re-

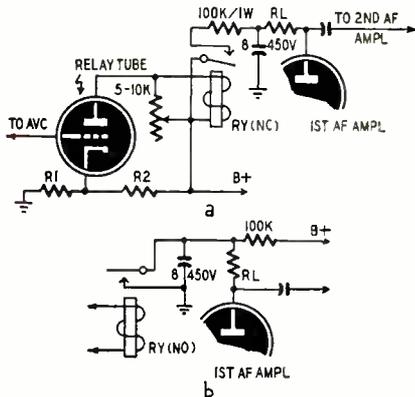

ceived, the a.v.c. voltage is low, permitting the control tube to draw sufficient current to excite the relay and open its contacts, thus breaking the plate-supply circuit to the a.f. amplifier. When a signal comes in the a.v.c. line goes negative, cutting off the relay tube and closing the circuit to the a.f. tube.

In some sets, there may be sufficient noise pickup to make the a.v.c. line a few volts negative at all times, in which case cathode resistor R1 may be made very small or eliminated entirely. If a cathode resistor is required to prevent the tube from operating without bias, and normal relay operation requires a value greater than 300 ohms, reduce the value of R1 to about 200 ohms and add R2 of sufficient value to provide normal operation. A potentiometer of 5,000 to 10,000 ohms may be required across the relay to control its sensitivity.

A time-delay circuit is provided by the 100,000-ohm resistor and 8- μ f capacitor. The capacitor charges and discharges slowly so there is no abrupt "pop" when the squelch cuts in and out.

The circuit at *b* is used with a normally open relay. With no signal input, the relay contacts close and ground the d.c. plate-supply voltage for the a.f. amplifier tube.

PREAMP FOR SCOPE OR VTVM

Very often service technicians and experimenters have difficulty measuring very low a.c. voltages on a scope or v.t.v.m. Such voltages can be measured accurately and easily by using a suitable preamplifier ahead of the scope or meter. A preamplifier designed for



NEW 1952 MODEL

INCLUDING COLOR ADAPTER INPUT

(COLOR ADAPTER NOT INCLUDED)

16"-20" TV RECEIVER

Completely Wired, Aligned and Tested—Ready to Install With Big 12" High Quality PM Speaker.

- 30 TUBES (including 3 Rectifiers)!
- High Efficiency High Voltage Circuit!
- Advanced Model 12 Channel Tuner!
- AGC for Fringe Area Reception!
- Magnificent TV Performance!



ONLY 139⁹⁵
Less Kinescope
ORIGINAL 630TS TYPE

DOES YOUR TV DROOP FROM TVI* BLOOP?



BANISH INTERFERENCE WITH NIAGARA'S FAMOUS HIGH PASS FILTER

Positive protection against interference from amateur transmitters, diathermy, and all other devices generating radio frequency interference below 40 MCS. Designed for 300 ohm leadin. No loss in brightness or clarity.

Wired and tested. \$2⁹⁵ EA.
Postpaid if entire amount is included with order.
* Television interference

NEW MODEL 100-75 WEBSTER-CHICAGO

AUTOMATIC RECORD CHANGER




Fine, new record changers at less than regular manufacturer's cost. Made by Webster-Chicago and only introduced on the market a few months ago as one of their latest models. Plays 12, 10 or 7 inch records at 33 1/3, 45, or 78 R. P. M. New spindle carefully lowers unplayed record stack. Balanced arm assures light needle pressure and long wear. Needle-tip (included) for standard or micro-groove records. Inside-out records played without any adjustment. Pickup arm comes to rest position after last record has played. Complete factory packed and sealed record changers, normally listing at \$47.50—While they last. **\$2485**
Shipping Wgt.

ASTATIC BOOSTER

MODEL BT-1

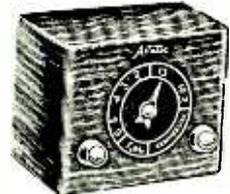A simplified high gain booster using the famous Mallory inducto-tuner for continuous tuning over entire TV and FM spectrum. Gives exceptional improvement on all channels. Single tuning knob. Mahogany finished metal case. Low noise. For either 72 or 300 ohm line. Wgt. 5 lbs.



SPECIAL! \$18.45

MODEL AT-1

Astatic four-tube deluxe models—no other booster can do so much in improving TV picture contrast and clarity, in improving sound, in eliminating interference. Feature exclusive variable gain control and dual-tuning. Model AT-1 in fine furniture finish mahogany.

Special \$29.10

ALLIANCE TENNA-ROTOR TV ANTENNA ROTATOR

New Alliance Rotator, completely remote controlled. Automatic rotation control shows exact position of antenna at all times. Moving light shows position while ant. is rotating. Set pointer to position desired and antenna automatically turns to that position and stops. 1 RPM instantly reversible. Weather proof construction. Lifetime lubricated. Fits masts up to 1 3/4". Includes 4 wire control line. Less cable, instructions. Shpg. wgt. 14 lbs. **\$25.95**



4 Wire control ribbon for Rotator 100 ft.—\$4.50; Per Foot. \$05
THRUST BEARING SUPPORTS UP TO 200 lbs. \$4.95

ONE OF AMERICA'S GREAT RADIO STORES
Niagara
RADIO SUPPLY CORP. Dept. 1-E2
160 Greenwich Street, New York 6, N. Y.

Digby 9-1132-3-4

It's NEW... It's a MONEY MAKER for Every Serviceman!
2 Service Instruments for the price of 1



TRANSVISION CR TUBE TESTER-REACTIVATOR

performs 2 vital functions:

- Tests Picture Tubes
- Renews Brightness of Many Dim Picture Tubes

It's a TESTER:

Without removing picture tube from set, you apply this precise instrument to:—

- Measure Cathode emission
- Locate shorts between elements
- Locate high resistance shorts or leakage as high as 3 megohms

It's a REACTIVATOR

for dim CR Picture Tubes

Revives dim TV Picture Tubes, without removal of tubes from sets. Works on a great many tubes with low light output, if there's no mechanical defect in tube. 110 V—60 cycles. Portable, weighs only 3 lbs. One or two applications pays for instrument.

SATISFACTION GUARANTEED \$19.95 NET
 or money refunded if you return the instrument in 10 days in good condition.

RUSH THIS COUPON—
TRANSVISION, INC.
DEPT. RC NEW ROCHELLE, N. Y.

Send me ___ CR Tube Tester-Reactivator(s).

Enclosed find \$___ deposit. Balance C.O.D.

Enclosed find \$___ in full. Send prepaid.


Name _____

Address _____

City _____ State _____

this purpose is described in *Sylvania News*. The circuit shown is designed especially for use with Sylvania polymeters and scopes but is of course suitable for use with equipment of other makes.

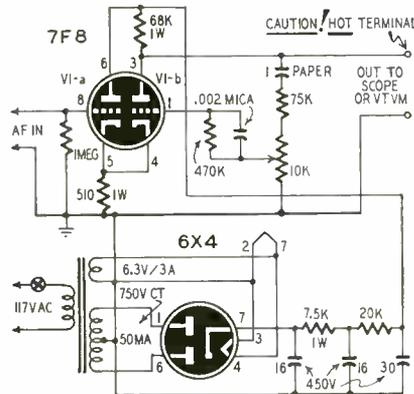The preamplifier provides a voltage gain of 10 with inputs from .001 to 1.5 volts in the frequency range of 20 to 50,000 cycles. One unit will provide a full-scale range of 0.3 volt for a meter whose lowest full-scale range is 3 volts. Two preamplifiers in series will reduce the full-scale range to .03 volt, and thereby increasing its sensitivity one hundred times.



VI-a is a cathode follower used to maintain a high input impedance. VI-b amplifies the signal and feeds it to the output terminals which connect to the scope or meter. The circuit is stabilized, noise is suppressed, and over-all gain is reduced to exactly 10 times by employing inverse feedback between the plate and grid of VI-b.

When wiring the unit, isolate the power supply and a.f. stages, use twisted pair for the heater leads, ground pin 2 of the 7F8, and use a common ground return. This practice minimizes noise which causes errors when measuring low voltages. Note that there is no blocking capacitor between the plate of VI-b and the output terminal. One is not used in the circuit because most scopes and v.t.v.m.'s have blocking capacitors in their input circuits.

The ungrounded output terminal is HOT with approximately 250 volts on it. Use insulated terminal jacks and always be sure to disconnect the test lead from the preamp before disconnecting it from the scope or meter.

To calibrate the preamplifier, connect a 10-to-1 resistive voltage divider (use carbon or noninductive resistors) across the output of a convenient source of audio voltage—you can use 60 cycles from a filament transformer—and adjust the output of the source so it is delivering exactly 1 volt to the divider network. One-tenth of this voltage is fed to the preamplifier. Switch the meter to the output of the preamp and adjust the 10,000-ohm potentiometer so the meter again reads exactly 1 volt.

Carefully made and calibrated, this instrument is a valuable addition to any experimenter's lab.

—end—


TRANSVISION
Sensational Offer!
2 YEAR GUARANTEE
on PICTURE TUBES
Direct from Factory!



Pro-Rated
 Transvision is the first and only manufacturer to offer you this amazing 2 year guarantee. Top quality rectangular and round tubes; all sizes.

Write for NEW LOW PRICES

FEED Up to 5 TV SETS from 1 Antenna with

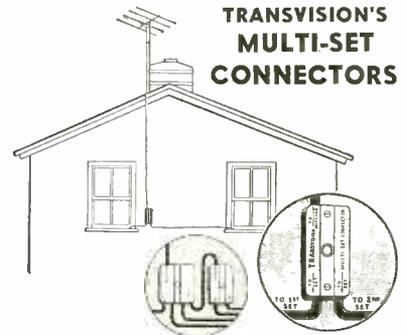

Increase Sales with Multi-Set Connectors. Ideal for homes, garden apartments, TV dealers, bars, etc. Big savings in time and labor. Guaranteed!

PRICES: Multi-Set Conn. for 2 sets, \$4.95 list.* Multi-Set Conn. for 3 or 4 sets, \$7.95 list.*

*Dealers, write for discounts

TRANSVISION'S FIELD STRENGTH METER at NEW LOW PRICE:

\$59 net



Improves TV Installations; saves half the work. Model FSM-1, complete with tubes, \$59 net.

Write for details on amazing Transvision **FACTORY AGENT PLAN!**

FREE: Sample copy of "TV and Electronics Notes." Or send 50c to cover cost of addressograph plate and mailing for **FREE** Subscription. Monthly issues are gold mines of info on color, conversion, sales, service, etc. **WRITE FOR IT TODAY!**


TRANSVISION, INC.

Dept. RC NEW ROCHELLE, N. Y.

SPEAKER SWITCHING SYSTEM

? I have an amplifier with an 8-ohm output, and three 8-ohm speakers with matching L pads. I want to install two of the speakers in one room and the third in another. Please design a switching system which will permit me to select the speakers in either room or to use them simultaneously.—R. W. H., Pittsburgh, Pa.

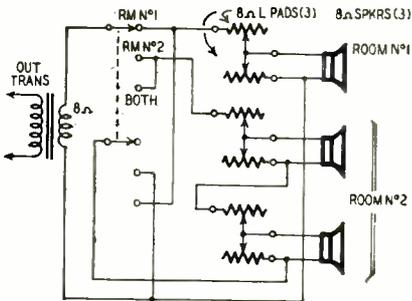A. One method of switching the speakers is shown in the diagram. The match to the output of the amplifier will be




perfect only when the single speaker is used. The speakers are mismatched when two or three are connected in series across the load. This causes a reduction in the maximum power which is available from the amplifier. However, this will be of little consequence if you do not normally operate the amplifier at more than about half its full output. Full output can, of course, be obtained when working into the single speaker.

VARIABLE-SELECTIVITY I.F.

? I have started constructing the variable-bandwidth AM tuner described in the November, 1950, issue. I'm being held up because I cannot find a variable-bandwidth i.f. transformer. Can you give me the make and type number of the one used by Mr. Drenner?—V. M. S., Grangeville, Idaho.

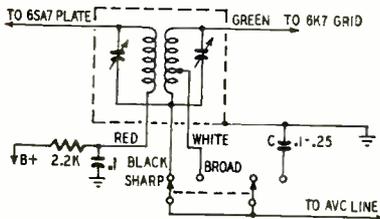A. The variable-selectivity transformer used in the original tuner was a Meissner type 17-7412 or 17-7416. We



have been advised that these types have been discontinued. However, you may be able to find one by shopping around among local and mail-order radio supply houses. You can substitute a Miller type F-512-C1 or F-612-C1 transformer. The 512 is an air-core unit while the 612 has a powdered-iron core. Either will work.

These transformers have only two selectivity positions; one sharp and the other broad. The circuit shows how they may be connected. Experiment with the value of capacitor C to minimize flutter when the switch is in the broad position.

Our New Year's Resolution to You . . . HIGHEST QUALITY AT LOWEST PRICES!

Make Steve-El your headquarters for everything in electronics . . . and save big money!

BRAND NEW STANDARD BRAND TUBES—World's Finest

Individually Boxed and Guaranteed

OZ4	.59	6BH6	.86	7G7	1.21
1A3	.89	6BN6	1.32	7J7	1.19
1A6	.89	6BQ6	1.44	7K7	1.19
1A7	.98	6C4	.76	7L7	1.19
1B3	1.02	6C5	.79	7N7	.99
1B5/25S	1.09	6C6	.85	7Q7	.89
1H5	.89	6CB6	.86	7T7	1.19
1J6	.74	6CD6	2.49	7Y4	.86
1L4	.74	6D6	1.09	7Z4	.84
1LA4	1.12	6D8	1.39	12A6	.79
1LA6	1.12	6F6	.88	12A8	.86
1LC5	1.12	6F8	1.49	12A15	.86
1LC6	1.12	6H6	.76	12AT6	.65
1LD5	1.12	6J5	.59	12B6	.79
1LN5	1.12	6J6	1.09	12A06	.89
1N5	.87	6J7	.81	12AU7	.96
1R5	.82	6K6	.66	12AV6	.79
1S5	.79	6K7	.74	12AV7	1.24
1T4	.85	6L5	1.39	12AX7	.99
1U4	.79	6L6GA	.89	12B6	.79
1U5	.78	6L7	1.19	12BE6	.79
1V2	.69	6N7	1.19	12H6	.89
1X2A	.96	6Q7	.88	12J5	.79
2A4G	.84	6S4	.76	12Q7	.79
2A5	.84	6SA7	.76	12SA7	.77
3A4	.89	6SF7	.99	12S17	.78
3Q4	.89	6SG7	.99	12SK7	.77
3Q5	1.02	6SH7	.89	12SL7	1.09
3S4	.88	6SJ7	.76	12SN7	1.09
3V4	.99	6SK7	.79	12SQ7	.68
5U4	.65	6SL7	1.19	14A7	1.03
5V4	1.10	6SN7	.89	14B6	1.03
5W4	.83	6SR7	.86	14B8	1.03
5Y3	.47	6SQ7	.72	14N7	1.05
5Y4	.75	6T8	1.19	14R7	1.02
5Z3	.89	6V6	1.69	14W7	1.09
5Z4	1.12	6V6GT	.86	19T8	1.34
6A3	1.59	6W4	.66	50B5	1.09
6AB7	1.39	6W6	.89	25BQ6	1.49
6AC7	1.21	6X4	.74	25L6	.85
6AF6	1.18	6X5	.74	25W4	.88
6AG5	.86	6Y6	.96	25Z6	.74
6AC7	1.59	7A4	.89	32L7	1.49
6AH6	1.49	7A5	.99	32L6	.86
6AK5	1.49	7A6	.86	35W4	.58
6AL5	.68	7A7	.86	35Y4	.86
6AQ5	.72	7AD7	1.92	35Z5	.57
6AR5	.67	7AF7	.89	47	1.34
6AS5	.99	7AG7	1.05	50A5	.96
6AS7	5.39	6W4	1.09	50B5	.86
6AT6	.68	7B6	.89	50C5	.86
6AU5	1.59	7B8	.99	50L6	.72
6AV6	.76	7C4	.79	50Y6	.99
6AV6	.67	7C5	.89	56	.66
6BA6	.69	7C6	.99	70L7	1.69
6BA7	1.16	7E6	.99	77	.89
6BC5	.86	7E7	.99	80	.79
6BE6	.82	7F7	.99	117Z3	.78
6BG6	1.76	7H7	.96	2051	1.22
				117N7	1.79

All American 5 Tube Kit

50L6, 35Z5, 12SA7, 12SQ7, 12SK7
Standard Brands only . . \$3.60 complete

TV PICTURE TUBES

All black faced—Non glare. SHELDON, ZETKA, and other famous makes. All Guaranteed.

10BP4	21.95	17B4	22.90
12LP4A	22.95	17HP4	24.95
14BP4	21.95	19AP4	32.95
16HP4	28.95	19EP4	32.95
16KP4	28.95	19DP4	39.50
16GP4	30.95	20CP4	32.95
16LP4	32.95	24AP4	65.50

SPECIAL MONEY-SAVING BONUS FOR QUANTITY PURCHASES
5% off on 25 tubes or more
10% off on 100 tubes or more

Model 175 TV & FM BOOSTER



Dimensions: Height 5 1/2" — Width 7 3/8" — Depth 7".
SIMPLE TO OPERATE
ALL 12 TV CHANNELS
ONE KNOB CONTROL
EASY TO INSTALL
CONTINUOUS TUNING

- Improves TV reception in weak signal area
- Permits use of indoor antenna in many locations
- Reduces noise and "snow" effects
- Reduces electrical and diathermy interference
- Minimizes "Ghosts"

List Price \$32.95 **\$15.95**

FREE — WRITE FOR OUR NEW BARGAIN CATALOG

Terms: 20% cash with order, balance C.O.D. Prices F.O.B. N. Y. City warehouse. Min. order \$5. (Allow for postage). Prices in this ad supersede all others published.

STEVE-EL ELECTRONICS CORP.

Dept. E-1 61 Reade St., N. Y. 7, N. Y. COrtlandt 7-0086

Visit Our New Store

TELEVISION RECEIVER

\$141.50

LESS C.R.T.



The Famous 630 TV CHASSIS

The New and Improved Super Famous "630" T.V. Chassis is a 30 tube high quality television receiver (including 3 rectifiers) manufactured under license by the Radio Corporation of America. The "630" Television Chassis is universally recognized by leading electronic engineers as the highest standard of television excellence. This chassis is the standard by which all other T.V. chassis are measured.

Standard R.M.A. Guarantee! FREE replacement on all defective tubes and parts.

- FEATURES:** 1. Full channel coverage. 2. Discriminator-type FM sound system. 3. Improved picture brilliance. 4. AFC horizontal hold. 5. Keyed AGC. 6. Stabilized vertical hold. 7. 3 stage sync. separator and clipper. 8. Automatic brightness control. 9. 4Mc band width. 10. Highest quality parts used. All tubes standard nationally. 11. Finest for Fringe area reception. Focus: adapted for all Cathode Ray tube sizes and types. Sweep Deflection: For 16", 17", 19", 20", 24" Tubes. Perfect for Fringe Area Reception—Will work where most sets fail to operate.

With HiGain standard coil tuner and R.C.A. Hi-Fi 12" Speaker. Complete with knobs and hardware. Complete with Fed. Taxes Paid. Less Cathode Ray Tube **\$141.50**

630 DX Chassis—Extra power for fringe areas. Can be operated without booster or complicated antenna. Complete with Fed. Taxes Paid. **\$151.50**
Less Cathode Ray Tube

Chassis Mounting Brackets when ordered with chassis **\$4.95**




WEBSTER CHICAGO AUTOMATIC RECORD CHANGER Series 100

Made by Webster-Chicago and only introduced on the market a few months ago as one of their latest models. Plays 12, 10 or 7 inch records at 33 1/3, 45 or 78 R.P.M. New spindle carefully lowers unplayed record stack. Balanced arm assures light needle pressure and long wear. Needle-tip (included) for standard or micro-groove records. Inside-out records played without any adjustment. Pickup arm comes to rest position after last record has played. Complete factory packed and sealed record changers. normally listing at \$47.50.

LIMITED QUANTITIES **\$24.79**

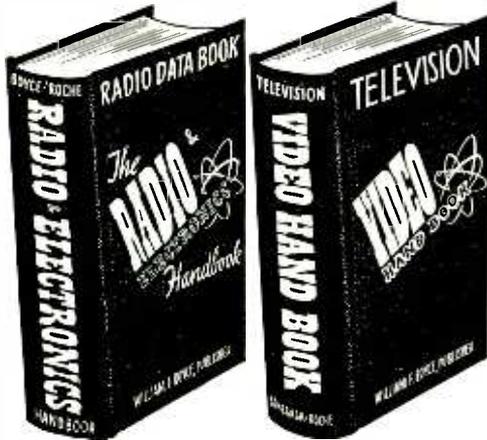**ARMY—NAVY
AIR FORCE—MARINES
SERVICEMEN
TECHNICIANS
Here's Help!**



**Now in 1800 PAGES
THE BASIC KNOWLEDGE
AND DATA OF
RADIO & TELEVISION
DIGESTED INTO 32 SECTIONS
... IN A COMPLETE, QUICK-
TO-FIND, EASY-TO-READ
HANDBOOK FORM.**

You can plan every operation in TV—Radio & Electronics with the Library Set. These handbooks are your lifelong tools—use them every day on the board, at the bench, or in the field—for construction, production, servicing, installation or operation—for adjusting, troubleshooting, measuring and testing. Your invaluable aid in service, research, development, design, manufacturing and maintenance. With all data & servicing procedures, these handy books work better, faster and easier.

In addition, you get complete coverage of everything you need in TV, Radio & Electronics—in practical form—everything presented in plain talk, all terms explained; schematics, working diagrams and pictures all clearly illustrated for your quick and easy reference.

These books are works of complete authority prepared by the well known engineers, Joseph J. Roche and Morton Scheraga, under the direction of William F. Boyce, famous for the preparation of hundreds of handbooks and manuals for the U. S. Signal Corps, U. S. Navy, U. S. Air Force, Western Electric Co., General Electric Co., Bell Laboratories, National Radio Co. and many others.

These Handbooks are endorsed by leading schools for instruction and reference. The armed services make them available to their technicians in libraries, schools, and in the field. Engineers, Draftsmen, Laboratory and Production men in every industry have purchased over 50,000 of these books for use in their work.

500 Radio jobbers keep them constantly in stock for the convenience of their service and industrial customers. These are the most commonly used books in Radio & TV.

Whether you use these Handbooks for general reference, scientific instruction or education, one thing is certain; the practical help, the daily usefulness you will derive from them will prove to be worth many times their price.

Contents are too long & complete to describe here, so see the books at your Radio Jobber, your bookstore, or

**SEND FOR TEN DAY
FREE TRIAL EXAMINATION.**

RADIO ELECTRONICS HANDBOOK\$7.00
VIDEO HANDBOOK\$7.00

SAVE \$2.00—Both Books Above\$12.00

**BOYCE-ROCHE BOOK CO.
Caldwell 31, New Jersey**

Send Library Set (both books) @ \$12.00
 Radio Electronics Handbook @ \$7.00
 Video Handbook @ \$7.00

In ten days I will send price plus postage, or I will return books postpaid.
(Offer good in U.S.A. and to men in Armed Services overseas only.)

Name.....

Address.....

Employed by.....


Save postage—we pay postage and packing if you send money NOW. Money back on same return privilege.

RECORDING-LEVEL INDICATORS

? I have a Masco MA-17 amplifier and a G.I. basic disc recording unit. Please show how I can connect these along with the necessary switching circuits for recording, playback, and monitoring. Show two neon lamps as level indicators.—L. L., Struthers.

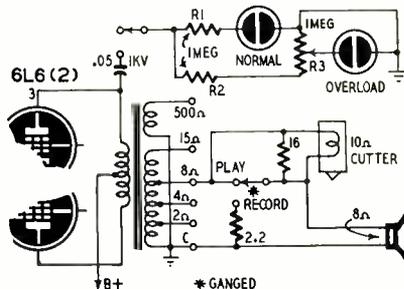A. The circuit shows how a 10-ohm magnetic cutter and an 8-ohm speaker can be connected to the output of the amplifier. The monitoring level is about 10 db below the recording level.

Values of R1, R2, and R3 are approximate and should be determined accurately by experimenting. Make a test record and determine the minimum vol-




ume which will produce good results. Adjust the value of R1 so the NORMAL lamp remains lighted most of the time that sound is fed into the input of the amplifier. Now, turn up the gain control to the point where a further increase results in overloading and distortion. Adjust the value of R2 and the setting of R3 so the OVERLOAD lamp is out or flashes only at rare intervals.

COMBINATION INPUT

? I have a direct-coupled all push-pull amplifier with which I would like to use the preamplifier described on page 27 of the February, 1951, issue. The preamplifier has single-ended output, the amplifier push-pull input. I wish to connect them—C.S., Los Angeles, Cal.

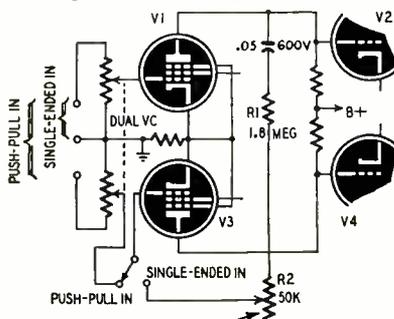A. The circuit shows how the input of a push-pull amplifier stage can be modified to provide for single-ended inputs. The output of V1 appears across a



ADJ FOR EQUAL SIGS ON GRIDS OF V2 & V4

.05 capacitor and resistors R1 and R2 in series. The voltage across this combination is 180 degrees out of phase with the signal applied to the grid of V1. A portion of the voltage appearing across R2 is tapped off and fed to the grid of V3 which acts as a phase inverter when the switch is in the SINGLE-ENDED INPUT position. Adjust R2 for equal signals on the grids of V2 and V4 with the switch set for single-ended input.

—end—

**The Book that takes
Drudgery out of
Mathematics**
Only **\$1.** postpaid
SOLVES EVERYDAY PROBLEMS HELPS YOU GET AHEAD IN LIFE

How many times have you lost money because of a mistake in figuring? Do you know how to figure quickly and correctly? Can you figure discounts, interest rates, taxes and all the other calculations you meet up with in your daily life?

Are you having trouble qualifying for Civil Service Exams or Armed Services Promotions, because you're not up on mathematics?

ILLUSTRATED

Here is the book that gives you a good background in mathematics; that takes all the irritation and drudgery out of it. You don't need to be scared of mathematics, because here's the subject explained without frills, without useless computations. Here's the book for men in radio jobs; for business men; technicians and craftsmen, explaining and answering everyday mathematic problems in easy-to-understand words and illustrations.

**A BOON TO EVERY
RADIOMAN**

The Radio Technician will find information on the following: Ohm's Law—Resistance—Reactance—Capacities—Inductances.

The valuable tables are multiplication and division table. Squares; Square Roots; Cubes and Cubic Roots Tables. Areas of Circles Table. Common Fractions reduced to Decimal Table. Factors and Prime Numbers Table. Table of Multiples.

Yes, it's the key to a simple understanding of mathematics. It's a real home-study course in mathematics for the man who's alert to its importance in the world today.

ELEMENTARY MATHEMATICS

• EASY — SIMPLIFIED — PRACTICAL •

CONTENTS OF BOOK

- CHAPTER I. Arithmetic—Addition—Subtraction—Multiplication—Division.
- CHAPTER II. Factoring and Cancellation—Fractions—Decimals—Percentage—Ratio—and Proportion.
- CHAPTER III. The Metric System.
- CHAPTER IV. How to Measure Surfaces and Capacity (Geometry).
- CHAPTER V. Powers and Involution—Roots and Evolution.
- CHAPTER VI. Mathematics for the Manual and Technical Craftsman—Thermometer conversions—Graphs or Curve Plotting—Logarithms—Use of the Slide Rule.
- CHAPTER VII. Special Mathematics for the Radio Technician.
- CHAPTER VIII. Commercial Calculations—Interests—Discounts—Short Cut Arithmetic.
- CHAPTER IX. Weights and Measures—Useful Tables.

ONLY **\$1.** POSTPAID

STAMPS, CASH OR MONEY ORDER ACCEPTED

Send Today for Your Copy of This Indispensable Book. It Can Be Carried Readily in Your Pocket. (Size 6 x 9 in.)

TECHNIFAX, 520 N. Michigan Ave. Chicago 11, Ill.

Enclosed find \$1.00 for which send me ELEMENTARY MATHEMATICS prepaid.


Name.....

Address.....

City & State.....

RE-1-52

NEXT MONTH — AND

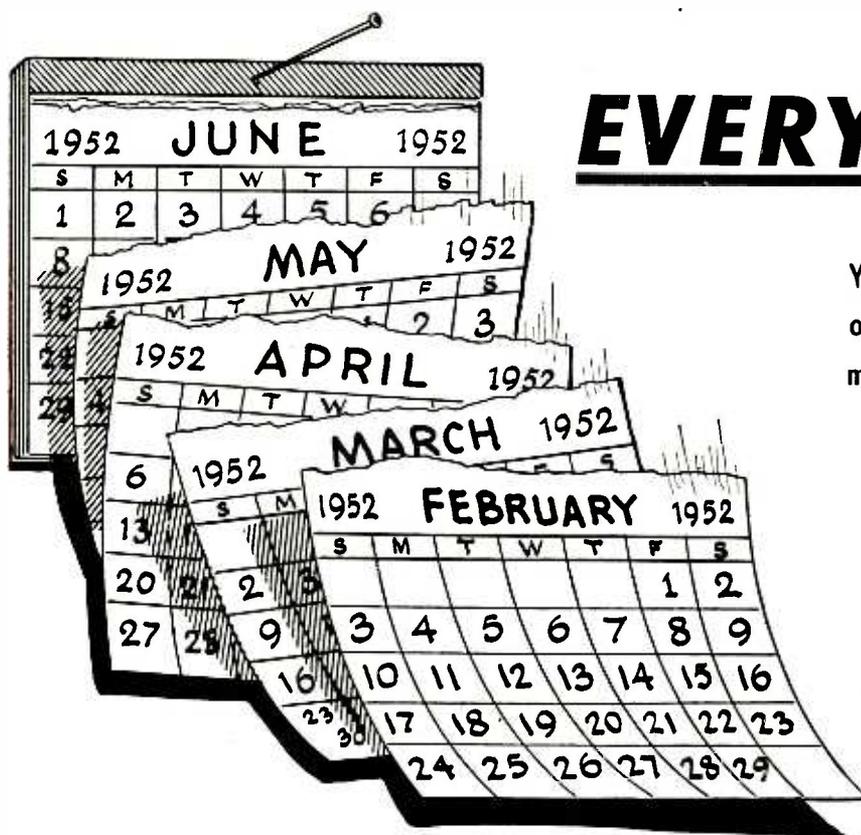

EVERY MONTH!

You can be sure of getting top coverage on servicing, installation, new developments and every other important phase of

- TELEVISION
- RADIO
- AUDIO

If you subscribe now to

RADIO-ELECTRONICS

Save up to eight cents a copy over the newsstand price at these low

SUBSCRIPTION RATES

Three Years **\$8.00**

Two Years **\$6.00**

One Year **\$3.50**

Check list of top-flight features scheduled for publication in future issues.

- ✓ New TV Front Ends
- ✓ Direct Reading Frequency Meter
- ✓ Constant Voltage Audio Systems
- ✓ VFO Design
- ✓ Broadband Chain Amplifiers
- ✓ Electronic Controls in Industry
- ✓ Adjusting TV Controls
- ✓ Untuned Preampifier for Superhets

25 West Broadway

New York 7, N. Y.

JANUARY, 1952

for dependable sound,
INDUSTRY relies on

ATLAS



DR Double-Reentrant Projectors



Paging & Talk-Back Speakers



ALNICO-V-PLUS Driver Units



Dual Speakers



FULL-GRIP, VELVET-ACTION Mike Stands

DEPENDABLE QUALITY:

The latest electro-acoustic research and engineering—and over 20 years of manufacturing know-how—are behind every ATLAS product.

DEPENDABLE SERVICE:

Coast-to-coast and around the world today—in every Industrial, Marine, Railroad, Military, Educational, Civic, U.S. and Foreign Government application—under every kind of climate and noise condition—ATLAS sound equipment is famous for highest efficiency and durability. That's the proof of ATLAS performance dependability.

DEPENDABLE DELIVERY:

Yes, ATLAS gives our Government highest priority. And yes, we too feel the pinch of material shortages. But our customers will continue to get our usual dependable delivery—because we believe in equitable and dependable distribution to all ATLAS users.

DEPENDABLE PROFITS:

Completeness of line, excellence of product, dependable delivery, right prices—that's the ATLAS combination that means high, steady Industrial Sound profits for you!

JUDGE for yourself, COMPARE ATLAS at your local Jobber today. See why ATLAS is the preferred line for utmost dependability. Write NOW for FREE latest Catalog 551.

ATLAS SOUND CORP.
1443-39th Street, Brooklyn 18, N. Y.
In Canada: Atlas Radio Corp., Ltd., Toronto, Ont.

Immediate Delivery of SCARCE RADIO-TV TUBES

TUBES BOUGHT, SOLD and TRADED Send Your Want and Trade List!


Complete Line of TELEVISION PICTURE TUBES

Radio and TV service men, experimenters, amateurs... we have many types of scarce tubes ready for immediate shipment. Don't use make-shifts or spend valuable time looking for tube sources. Try Electro FIRST... and get the tubes you need without delay. Get complete list and Electro's low prices. It's FREE... write today!

ELECTRO SALES, 425 W. Randolph St., Chicago 6, Ill.

SYLVANIA RETRACE BLANKING

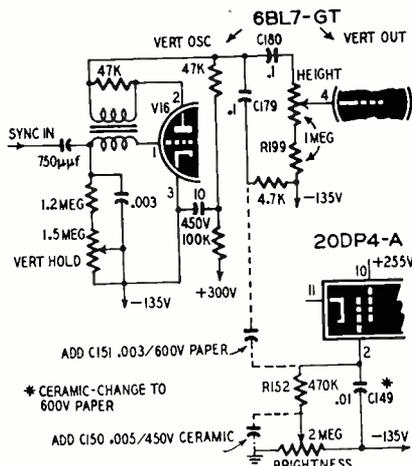The changes shown in the diagram have been added to the Sylvania 1-387 chassis to suppress vertical retrace



lines. The changes have been made in chassis bearing codes C03 and later. They can be made in earlier chassis.—*Sylvania Service Notes*

BENDIX 3001U TV SET

Loss of horizontal sync can be traced to a change in the value of the screen-dropping resistor for the 6BG6-G horizontal output tube. This resistor is made up of three series-connected 4,700-ohm resistors which have a total nominal value of 15,000 ohms. A pulse is taken off between the first and second resistor and applied to the phase detector in the a.f.c. circuit. A change in value of any of these components will usually cause the sync circuit to fail. The three resistors should be replaced.—*James Moudry*

TV TUBE SUBSTITUTION

During a temporary shortage of 6BQ6-GT's, I tried 6W6-GT's as replacements in several sets and found that they worked nicely. The latter type is a single-ended tube so I wired the plate-cap lead to pin 3 on the socket. No other changes were needed.

The 6W6-GT heater draws 50 ma more than the 6BQ6-GT, and its plate, screen, and bias voltages are lower, so it is advisable to study the circuit, tube characteristics, and operating voltages before making the substitution.—*Edward Tanrath*

MAGNAVOX CT-273CA

The complaint was tearing out of several lines when the controls were set for normal picture contrast. Using a scope to examine the composite sync in the clipper stage, we found that the horizontal sync was being wiped out over a portion of each field. Moving the scope to the output of the video amplifier showed a 60-cycle sine wave superimposed on the signal although there was no characteristic shading in the picture.

Further investigation revealed a 4-megohm leakage between filament and grid in the 6CB6 first i.f. amplifier. Replacing this tube cleared up the trouble.—*Arthur D. Marikle*

★ BUY WITH CONFIDENCE ★
★ 5 DAY MONEY BACK GUARANTEE ★
★ **ELECTRONIC SURPLUS MATERIALS** ★
★ **QUALITY KITS AT BARGAIN PRICES** ★

- ★ 100 INSULATED RESISTORS—name brands RMA color coded, 1/4, 1/2, 1, 2 Watt, many 5%, Over 50 values, \$2.75 ★
- ★ 100 CARBON NON-INSUL. RESISTORS RMA color coded, 1/4 to 2 watt, contains over 50 values, 1.75 ★
- ★ 50 RF CHOKE COILS—all sizes for plate, grid, fil. circuits Xmitter, TV, Oscill., etc., 1.75 ★
- ★ 50 MICA CONDENSERS—over 20 values, incl. popular silver mica types, 1.95 ★
- ★ 25 PRECISION WIRE WOUND RESISTORS—name brands, Over 20 values, 2.95 ★
- ★ POTENTIOMETER KIT—13 types, Carbon & W.W. S.D. & shaft types. Includes 1/2 & 1 meg. with switches, 2.25 ★
- ★ 50 CERAMIC CONDENSERS—Over 25 values, Color coded, 2.45 ★
- ★ 50 BY-PASS CONDENSERS—Tubular Popular values, 400 and 600 wdg. volts, 2.75 ★
- ★ 20 ELECTROLYTIC CONDENSERS—Tubular, FP & upright types. Popular values for service or set building, 2.95 ★
- ★ 40 TUBE SOCKETS—4-5-6-7-8 prg., Ceramic, molded & bakelite wafer types, 7 pin miniature, neon, klystron, etc., 1.95 ★
- ★ 50 TIE POINT STRIPS—2-3-4-5-6-7-8 terminals, Ideal shop assortment, 1.45 ★
- ★ 20 BATHUB CONDENSERS—assorted values, voltages, terminals, 1.95 ★
- ★ HOOKUP WIRE ASSORTMENT—Cut lengths, 27 to 127 Stripped ends, some tinned, mixed colors, 2 lbs., approx. 400 ft.,89 ★
- ★ EXTRA BONUS—1 wire kit free with 5 assorted kits.

No C.O.D.'s. Please Include Postage. Excess refunded.
ELECTRONIC SPECIALTY SUPPLY CO.
★ 56 Lispenard Street New York 13, N. Y. ★
★ Dept. RE-1 ★

YOUR COPY of
NEW 1952 COMPLETE
GREYLOCK
CATALOG

IS NOW READY!
Send for it Today!

68 pages
Crammed full of Radio—Electronic—Television quality merchandise at terrific savings! Many standard lines carried. High quality Greylock Tubes still available at some of Today's best prices. If you sell or service Radio, TV or Electronics equipment, you can't afford to be without this GREAT BUYING GUIDE! Write NOW for your copy (unless already on our mailing list).
Dept. C-1

GREYLOCK ELECTRONICS SUPPLY CO.
115 Liberty Street • New York 6, N. Y.

TELEVISION RECEIVER—\$1.00

Complete instructions for building your own television receiver. 16 pages—11"x17" of pictures, pictorial diagrams, clarified schematics, 17"x22" complete schematic diagram & chassis layout. Also booklet of alignment instructions, voltage & resistance tables and trouble-shooting hints.—All for \$1.00. Write for free catalogue.


CERTIFIED TELEVISION LABORATORIES
Dept. C, 5507-13th Ave., Brooklyn 19, N. Y.

Another Outstanding Jobber
Almo Radio Co.
1123-37 Maddon Ave., Camden, N. J.

EICO has all 17 KITS & INSTRUMENTS in stock!

755 E. 4th Street, St. Louis 95 See EICO ad on Page 24

AUTOMATIC M-90 AUTO RADIO

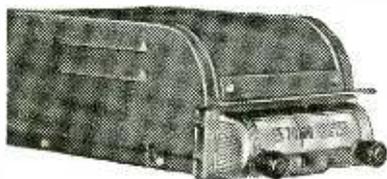

- Six Tube Superheterodyne • Three Gang Condenser • Powerful, Long-Distance Reception • Fits All Cars, Easy Installation
 - Mounting Brackets Included
 - 6 Tube model M90 *\$33.87
 - 5 Tube Model A-15 \$28.76
- *Above price includes Federal Excise Tax
Approx. shipping weight either radio (11) eleven pounds


MAIL US YOUR ORDERS

All orders filled within 24 hours.
Standard Brand tubes 50% off list

Bill Sutton's Wholesale Electronics
Fifth at Commerce Fort Worth, Texas

UNUSUAL MIXER CIRCUIT

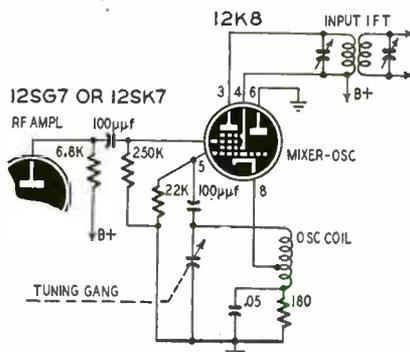The model FS-16 radio set distributed by McGee Radio Co. uses the rather unusual mixer-oscillator circuit shown in the diagram. The converter tube is 12K8 with its hexode section connected in a circuit similar to that used with 6A7's and similar tubes. The triode plate is grounded.



Problems of poor sensitivity can be handled simply by disconnecting the triode plate (pin 6) from ground and leaving it floating or connecting it to the screen grid (pin 4).

Although this circuit is comparatively rare, it is not confined to the FS-16. A similar circuit is used in an old 6-tube Philco which uses a 6K8 as the converter tube.—G. P. Oberto

ALIGNMENT HINT

When a set becomes unstable or breaks into oscillation when you attempt to align it, check the filter capacitors for reduced capacitance. A reduction in capacitance may produce a considerable increase in r.f. impedance without being sufficient to raise the hum level. The increased impedance causes r.f. feedback and oscillation.

Try to keep this hint foremost in your mind because it is so easy to overlook a source of trouble such as this when working on the r.f. or i.f. end of a set.—C. E. L. Payne

TRANSFORMERLESS TV SETS

This set was one of the transformerless Emerson models which uses a flock of selenium rectifiers in the power-supply circuit. It worked O.K. with the exception that the picture was distorted and too narrow. The defect seemed to be in the horizontal output stage. Replacing tubes, checking voltages and resistances, and a thorough visual examination showed nothing wrong. We tried a new deflection yoke and a substitute low-voltage supply without success. As the last resort, we replaced the horizontal output transformer. The set worked perfectly. Apparently, a few turns had shorted out in the secondary of the transformer. This trouble can occur in most TV sets, so if you have the same symptoms and everything checks O.K., try a new horizontal output transformer.


Incidentally, if you are not familiar with the voltage-multiplier circuits used in transformerless TV sets, voltage checks will produce some surprising figures. Always use the service manual when there is any doubt whatever.—Jacob Dubinsky

Customer Satisfaction

WINCHARGER

Antenna Support Towers

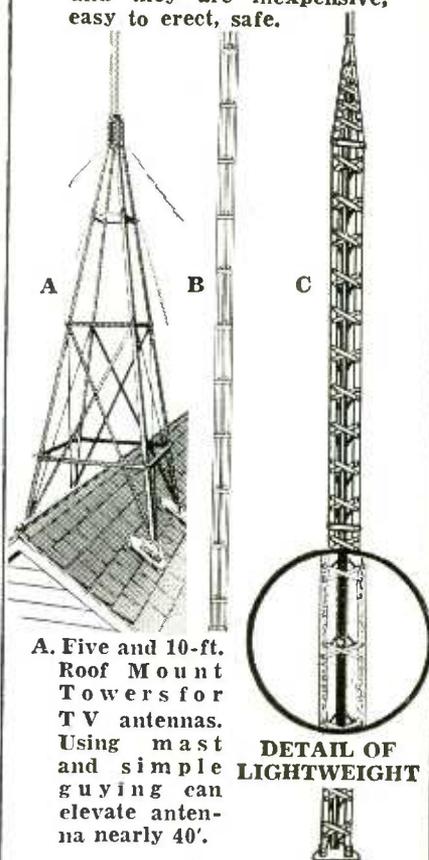The stronger the signal, the more satisfied your TV customers will be. Wincharger Support Towers are a real aid to a stronger signal. Here are three different models that have proved to be ideal for every installation... and they are inexpensive, easy to erect, safe.



A. Five and 10-ft. Roof Mount Towers for TV antennas. Using mast and simple guying can elevate antenna nearly 40'.

B. Lightweight Towers has hinged base. In 10' sections. With simple guying will support 4-bay stack at 40'.

C. Self-Supporting. Slender, attractive design—no guys. Will support antenna with maximum wind thrust of 100 pounds. Cement base.

Wincharger Corp.
Dept. 81 Sioux City 2, Iowa

LOW FACTORY PRICES

Let Us Put This NEW 1952 **MIDWEST TELEVISION or RADIO**

In Your Home on **30 DAYS TRIAL**

Mammoth **20-INCH** Rectangular PICTURE



EASY TERMS

You be the judge! See and hear Midwest Television in your own home. You must be 100% satisfied or your money back. Send for 1952 Catalog of the finest Midwest line in 32 years.

FACTORY-TO-YOU Low Factory Prices.



LOW FACTORY PRICES

WE PAY TRANSPORTATION CHARGES.

Special Bonus Gift!



Illuminated TELEVISION CLOCK
Given With Every Purchase of a **MIDWEST RADIO or TELEVISION**
LIMITED TIME ONLY!

Phone For **FREE 1952 MIDWEST CATALOG**
IN NEW YORK M Urray Hill 2-6810 IN CHICAGO State 2-5600
IN CLEVELAND Prospect 1-7450 IN PITTSBURGH Grant 1-0609
IN DETROIT Woodward 3-1233 IN ST. LOUIS Grand 1161
IN PHILADELPHIA Locust 4-1035 ... or send coupon below

SEND THIS COUPON For **FREE MIDWEST 1952 Catalog**

MIDWEST RADIO & TELEVISION CORP.
Dept. 386, 909 Broadway, Cincinnati 2, Ohio

NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____


TUBE BARGAINS

* 5U4G	.65	6AU6	.62	*
* 5Y3GT	.49	6BC5	.67	*
* 5Z4	.90	12AU6	.67	*
* 6AL5	.55	12AU7	.82	*
* 6AK5	.85	12BE6	.60	*

All tubes standard brands, guaranteed. Write for prices on other types

SUPREME 542 RCP 442 & TRIUMPH MULTIMETERS

made for U. S. Army

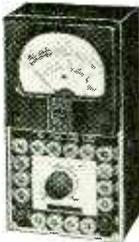

- * 5000 ohms per volt, 3" meter, 24 ranges, only 5 7/8" x 3 1/16" x 2 1/8"
- * 4 DC MIL RANGES 0/0.3/6/30/150
- * 4 DC VOLT RANGES 0/6/150/300/1500
- * 4 ohm ranges 0 2K/20K/200K/2 meg
- * 4 AC VOLT RANGES 0/6/30/150/300
- * 1 OUTPUT RANGES 0/6/30/150/600
- * 4 DB RANGES -6/+10/+8/+24,+22/+38,+34/+450

\$15.95

- * Complete with battery, test leads & 90 day GUARANTEE
- * 3" Sq 0-50 ua meters \$12.95
- * 3" Rnd 0-30 (Sp. Scale) 2.25
- * 3" Rnd 30-0-30 Amp DC 5.50
- * 2" 0-30 Amp DC (aircraft type) 1.98

COMPONENT BARGAINS

- * TS-13 Handset \$4.95, National type N dial .. 3.25
- * Dual 10 Amp, 115 V, 60 Cy. circuit breaker .. 2.95
- * 5 screw terminal strip (6/32 screw) .. 1.20
- * Barrier Strip, Yellow Bakelite, 6 term .. 1.50
- * Mitten terminal strip 37104 .. 1.40
- * 9 pin min. water socket, base shield .. 1.75
- * 7 pin min. molded sock, base shield .. 2.50
- * 7 pin min. Steatite sock, base shield .. 1.50
- * Octal sock, Steatite .. 1.00
- * 4 prong steatite socket .. 1.00
- * 6 prong, MIP 6 socket .. .85
- * Amph. 61M, 15A 125V plug & 61-61 shell .. .25
- * Amph. 61P, 15A 125V Recept. & 61-61 shell .. 1.99
- * 7 ft. rubber line cord & mold. plug .. 1.07
- * 1" green 110V Pilot Light assembly .. .39
- * SPST 6A 125V, H & H Box Handle Toggle Sw. .. .25
- * C-H Luminous tip bat handle Aircraft Toggle Sw. .. .25
- * SPST 5A 125V .. .25
- * SPDT as above .. .35
- * SPST as above, momentary only .. .25
- * SPDT as above, neutral center .. .49
- * SPST Rotary Switch, water type .. .25
- * Ceramic Battery Switch .. .59
- * 50 or 200 ohm 10W WW Res. .. .15
- * IRC 800 ohm 50 W WW Res. .. .75
- * IRC 10K 50W WW Res Adj. .. .59
- * IRC 10K 100W WW Res. .. .59
- * IRC 50K 100W 2.5K 100W Adj. pair .. .75
- * Rheostats-50 ohm 2.5K, 100 ohm 2.5V .. .59
- * Veeley Root 4 digit counter (A1142) .. 1.75
- * Millen Flex. coup (39002) .. 1.50
- * PL-55 plugs 525 .. 1.25
- * JK34 Jack (PL55), 18c, JK33 (PL-68) .. .25
- * 3 digit counter dials, 1/2" shafts .. .59
- * HI-IMPED. Phones 2k ohms less h-band .. 9.95
- * Control Box C254AR/AIC-13 & plug, New .. .05
- * 2 cell penlite bulbs (222) .. .05
- * Grain of Wheat 3V bulb 100 GE 257, 12V .. .10
- * Mazda S-6 115V 6W bulb .. .10
- * 3000 MF 3V electrolytic capacitor .. .21
- * STRAIGHT Plate Caps-807 175, 806 .. .85
- * Johnson 210 sock, 65c, 211 sock .. .85
- * AN PRS-1 mine detector .. 39.50

CO-AXIAL RELAYS

- * Allied Control Type RA, SPDT, 6VDC, Uses Standard Co-Ax Connectors .. \$5.95
- * NEW STEEL TABLE RACK CABINETS, 60x4 1/2 x 19 1/2 x 13 1/2, Black Crackle Finish, Hinged Top with Lock, 2" opening in rear for cable Connections. Shipped via Ry. Xpr. .. \$5.95
- * RCA 12 inch PM Speaker, New .. \$3.95

CHOKES

- * 6HY 50MA .. \$.59
- * 9HY 90MA .. 1.49
- * 125MA Cased .. .85
- * 1-28HY 130MA Cased .. 1.69
- * 6HY 150MA 140 OHM .. 5.10
- * 6HY 200MA Cased .. 3.49
- * 1-6HY 200MA 140 OHM Cased .. 1.39
- * 3HY 250MA 15 OHM Cased .. 6.50
- * 3-25HY 300MA 85 OHM Cased .. 5.00
- * 3HY 300MA 85 OHMS Cased .. 5.00

115V FILAMENT TRANSFORMERS 60 CY

- * 2.5 VCT 10A, 19 KV Insulation .. \$4.50
- * 2.5 V @ 6A, 2.5 V @ 6A, Cased .. 3.45
- * 5VCT 2A, 2.5 KV Insulation .. 2.45
- * 5 V @ 3A, 6.3 VCT @ 3.5A, 5V 3A .. 2.95
- * 5 VCT 12A, 4.5 KV Insulation .. 6.85
- * 5 VCT 20A, 2.5 KV Insulation .. 2.49
- * 6.3 VCT 1A, 2.5 KV Insulation .. 2.95
- * 6.3 VCT 3A, 2.5 KV Insulation .. 2.49
- * 6.3 V @ 4A, 6.3 V @ 4A, Cased .. 2.95
- * 6.3 V 6A, 5V 3A .. 2.75
- * 6.3 VCT @ 6A, 2.5 KV Insulation .. 3.95
- * 6.3 V 10A, Cased .. 6.00
- * 6.3 V 12A, 6.3 V 2A Herm. Seal .. 3.95
- * 10 VCT 10A, 2.5 KV Insulation .. 3.95
- * 12 V 1A, 2 KV Insulation .. 2.49
- * 32 V 1A, 2 KV Insulation .. 2.49

115V POWER TRANSFORMERS 60 CY

- * 68 to 83 V Half Wave, 1.5A .. \$1.25
- * 300 V 20 MA (Half Wave) .. 2.95 ea. 2/
- * 435 VCT 1.45 MA, 6.3 V 3A, 5V 3A .. 2.95
- * 600 VCT 40 MA, 6.3 V 2A, 5 V 2A .. 3.25
- * 680 VCT 200 MA, 6.3 V 3A, 5 V 3A .. 3.50
- * 700 VCT 70 MA, 6.3 V 3A, 5 V 3A .. 3.50
- * 700 VCT 90 MA, 6.3 V 3A, 5 V 3A .. 5.95
- * 740 VCT 185 MA, 6.3 V 4A, 5 V 4A .. 9.50
- * 800 VCT 200 MA, 6.3 V 3A, 5 V 3A .. 9.50
- * 800 VCT 300 MA, 6.3 V 10A, 5 V 6A, 5 V 2A .. 9.95
- * 750-600-0-600-750 VDC, 225 MA .. 9.95

SEND FOR "POLY-GRAM"

POLY-TECH, N.Y.

919 Dawson St., New York 59, N. Y.
Tel. Murray Hill 6-2650

Rear-Admiral Stanley F. Patten, U.S.N. (Ret.) was elected vice-president of ALLEN B. DU MONT LABORATORIES, INC. Admiral Patten has been with Du Mont since 1947 as assistant to the president. Du Mont also announced the appointment of Keeton Arnett as general assistant to the president. He comes to the company from the Fred Eldean public relations firm.



S. F. Patten



K. Arnett

H. Laurence Kunz was promoted to the position of general manager of the Capacitor Division of the SANGAMO ELECTRIC CO., Springfield, Ill. He will make his headquarters at the factory in Marion, Ill. Mr. Kunz had been sales manager of the division for the past six years.



H. L. Kunz

Louis Martin joined STANDARD COIL PRODUCTS CO., INC., Chicago, in the newly created position of general sales manager. He was formerly sales manager of the General Instrument Corp.



L. Martin

W. D. (Bill) Renner was upped to the position of manager of sales engineering for HOWARD W. SAMS & CO., Indianapolis, publishers of Photofact folders. He was formerly chief field engineer and technical advisor.

Robert J. Reigel joined the STANDARD TRANSFORMER CORP. as distributor sales co-ordinator. He comes to the company from the Thordarson-Meissner Division of Maguire Industries where he had been sales manager.



R. J. Reigel


Obituaries

Allen D. Cardwell, inventor and founder of the electrical instrument manufacturing company which bore his name, died in Nassau Hospital, Mineola, N. Y. Ernest H. Scott, founder and former president of SCOTT RADIO LABORATORIES, died in Victoria, B. C.

Personnel Notes

... William F. E. Long was appointed as the first director of statistics of the

PERFORMANCE Not Size IS WHAT COUNTS

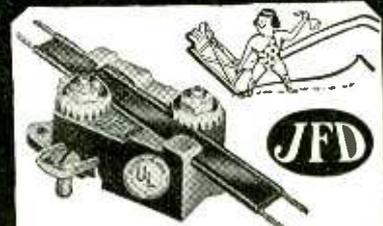

"LITTLE GIANT" LIGHTNING ARRESTER

PROTECTS Against Lightning Hazards

No. AT 105 For ribbon-type and oval jumbo twin lead. **\$1.25 LIST**

ONLY JFD Lightning Arresters offer you these exclusive patented features...

1. Strain-relief Retaining Lip prevents pulling or straining of lead against contact points.
2. You actually see positive contact made with lead-in wire.
3. No wire stripping or cutting.

Write for Form No. 84 showing the damage lightning can do to a Television installation.

JFD MANUFACTURING CO., Inc.
6101-A 10th AVENUE, BROOKLYN 4, N. Y.
FIRST in Television Antennas and Accessories



EVERY RADIOMAN Can Use These SERVICE HINTS!

Valuable Manual Yours—FREE!

Every page of "How to Simplify Radio Repairs" is packed with on-the-bench, practical ideas. Contains photos, charts, diagrams—no fluff—no vague theory. In plain every-day language it gives you priceless suggestions, new servicing ideas. You'll use and benefit from the experience of experts. Partial list of contents: How to Localize Trouble; How to Service Amplifiers; How to Test for Distortion; How to Test Audio Circuits; How to Test Speakers; How to Find Faults in Oscillators; How to Test Radio Parts—and it's all yours—FREE! No obligation.



SEND COUPON OR PENNY POSTCARD FOR YOUR FREE COPY TODAY!

FEILER ENGINEERING CO., Dept. IRC
8026 N. Monticello Ave.
Skokie, Ill. (Suburb of Chicago)
Please RUSH my FREE copy of "How to Simplify Radio Repairs."
Name.....
Address.....
City.....Zone.....State.....

HELP THE DEFENSE EFFORT by turning over old copies of RADIO-ELECTRONICS and all other waste paper to paper collecting agencies in your community.

PLATT WISHES YOU ALL A
HAPPY NEW YEAR
 ... and to make it happier, Platt offers this sensational bargain sale!
 5% OFF any price in this ad

20 POUNDS OF ASSORTED RADIO PARTS ONLY \$2.79



The last time PLATT offered this terrific bargain he was sold out—but not this time! You won't want to pass up this buy—so order today to be sure you get your supply.

WELL KNOWN MAKE TAP SWITCHES

5, 6, 7, 8, 9, 10, 11 POSITION All Porcelain—Vitreous Enamelled. 50 and 100 watters. ... \$1.29
 5, 6, 7, 8 POSITION ... \$1.69
 9, 10, 11 POSITION ... \$1.69

HEADSET H-16/U
 8,000 ohms with adjustable head band and ear cups. ONLY \$3.95

HEADSET ADAPTER MC-385
 Used with headsets HS-33 or HS-38, raising the impedance from low to high. Comes complete with PL55 Plug. ONLY 49¢

HEADSETS

HS-33 low impedance with cord and plug, used, fine condition. \$1.89
 HS-23 high impedance, BRAND NEW with ear pads. 3.95
 HS-33 low impedance, BRAND NEW with ear pads, cord and PL54 plug. 4.95
 HS-30 with ear plugs, low impedance, used, good condition. 1.69
 CD-307A Cords, 6 ft., NEW.89

TIME CLOCKS

12 and 24 hour cycle timing. UNLIMITED USES. Needs minor repairs. AN EXCELLENT BUY. HOW CAN YOU GO WRONG! ONLY \$9.95

BC-348 RECONDITIONED GUARANTEED LIKE NEW

All letters, Frequency Range 200 to 500 KC. 1 1/2 to 18 meg. OLD RELIABLE OF WORLD WAR II. SPECIAL! \$179.50

PRE-AMPLIFIER MODEL K-1

The K-1 is used to amplify output level for microphones and phonographs. Operates on 24-28 VDC, can be converted to 110 VAC. Comes complete with PL 55 plug and 2 foot 119-B cord. 2 terminal blocks and instruction book. \$4.95 BRAND NEW.

BEACON RECEIVER BC-1206-C
 Manufactured by Setchell-Carlson

Frequency Range—195 KC to 420 KC. IF Frequency—195 KC. Receiver Sensitivity—2 Microvolts for 10 Milliwatts output. Output Impedance—300 Ohms and 4000 Ohms to be selected inter alia. Power Output—230 Milliwatts. Volume 4 to 10 dB Gain Control, Power Supply—24-28 Volts Accumulator Battery, Current—75 Amperes. BRAND NEW—ONLY \$10.95

MN-26Y INSTALLATION

MN-26Y RECEIVER—Remote control commercial type navigational. Indicates direction of any deflected transmitting station. 3 bands—frequency range 150 KC to 1500 KC. has 12-6 V type tubes. BRAND NEW (Original Cost \$600.) \$15.95

MINIMUM ORDER \$2.00
 Immediate Delivery—Send 25% deposit on c.o.d. orders. All shipments F.O.B., N.Y.C. (N.Y.C. residents add sales tax to your remittance.)

PLATT ELECTRONICS CORP.
 Dept. B, 489 Broome St., N. Y. 13, N. Y.
 PHONES: WO 4-0827 and WO 4-0828

RTMA. He had been director of the Statistical Division of the National Paint, Varnish and Lacquer Association.

... William W. Taylor, for several years a member of the SANGAMO ELECTRIC Co.'s advertising, sales research and publicity division at Springfield, Ill., handling capacitor advertising and promotion, was advanced to the position of sales promotion manager, Capacitor Division, with complete charge of all phases of capacitor advertising activities. His headquarters are to be at the Sangamo capacitor plant located in Marion, Ill.

... Dr. Lan Jen Chu, internationally known physicist, joined the GABRIEL Co., Cleveland, as director of research. Gabriel is the parent company of the Ward Products and Workshop Associates Divisions.

... Harry Ehle, vice-president of INTERNATIONAL RESISTANCE Co., Phila., was honored recently upon the occasion of his 20th Anniversary with the company.

... Frederic J. Robinson was appointed director of the International Sales Division of SYLVANIA ELECTRIC PRODUCTS. He was formerly Sylvania's sales manager for Latin America. The company also announced the appointment of C. J. Luten as editor of *Sylvania News*. He succeeds Robert A. Penfield who was promoted to Advertising and Sales Promotion supervisor.

... Henry F. Argento was elected an assistant vice-president of RAYTHEON MANUFACTURING Co., Waltham, Mass., and appointed assistant manager of the Power Tube Division in which he held the position of sales manager since 1941.

... Leonard F. Cramer was appointed assistant general manager of the CROSLY DIVISION of AVCO MANUFACTURING Co. He was previously executive vice-president and director of Allen B. Du Mont Laboratories.

... Dr. Constantin S. Szegho, director of research of the RAULAND CORP., was awarded the grade of Fellow in the I.R.E.

... George W. Henyan, manager of GENERAL ELECTRIC Industrial and Transmitting Tube operations, accepted a temporary appointment as chief of the components branch of the NPA. G-E also announced the appointments of D. S. Beldon and D. E. Weston, Jr., as national account sales manager and radio sales manager respectively of General Electric's Receiver Department.

... Frank K. Spiro joined JFD MANUFACTURING Co., Brooklyn, N. Y., as assistant advertising manager. He was formerly with Fawcett Publications and Kenyon & Eckhardt Advertising Agency.

... W. H. Garrett, Victor Williams, C. A. Brokaw, and W. H. Allen were promoted to newly created posts as district managers of the RCA Tube Department Renewal Sales field activities in the company's Central, Southeastern, Western, and Eastern districts, respectively.

PROFESSIONAL-TYPE TAPE RECORDER
 Uses Your Amplifier!

COMPLETELY PORTABLE



The tape Master NET \$89.95 LESS MIKE

Own a better tape recorder—at a tremendous saving! By using the tapeMaster with your own audio amplifier, you get professional-type performance—economically! Built to RTMA standards. 7 1/2" per sec. tape speed. Fidelity equal to professional recorders. Fast forward and rewind. Complete master switching. Full monitoring. Inputs for Radio-Phono and Mike. Outputs to Amplifier and Headphones. Push-Pull Supersonic Bias and Erase. Neon Record Level Indicator. One Knob Mechanism Control.

ORDER NOW ON 15-DAY TRIAL. MONEY BACK if not fully satisfied.

WEXCO, INC., Dept. B52
 54 W. Illinois St., Chicago 10, Ill.

Rush tapeMaster to me.
 Enclosed \$ _____ Ship C.O.D.
 Send full information on tapeMaster

Name _____
 Address _____
 City _____ Zone _____ State _____

LEARN

Television-Radio Electricity

REFRIGERATION-ELECTRONICS

IN THE GREAT SHOPS OF **COYNE**

TRAIN QUICKLY! OLDEST, BEST EQUIPPED SCHOOL of ITS KIND in U.S.
 Young and Older Men

Come to the Great Shops of Coyne in Chicago. Get practical training in TELEVISION-RADIO or ELECTRICITY—vital in Defense Program. Prepare now for a better job or better service rating.

START NOW—PAY LATER
 You can finance most of your tuition, pay for it later in easy monthly payments. Special plan for men of Draft Age. Part time employment service available.

FREE BOOK Clip coupon for Big Free Illustrated Book. Indicate below, course that interests you. No salesman will call. Act NOW.

COYNE SCHOOL B. W. Cooke, President
 A TECHNICAL TRADE INSTITUTE CHARTERED NOT FOR PROFIT
 Established 1895
 500 S. Paulina, Chicago

ELECTRICITY ★ TELEVISION RADIO ★ REFRIGERATION ★ ELECTRONICS

B. W. COOKE, Pres.
 COYNE School
 500 S. Paulina St., Chicago 12, Ill. Dept. 12-81H

Send FREE BOOK and full details on:
 TELEVISION-RADIO ELECTRICITY

NAME _____
 ADDRESS _____
 CITY _____ STATE _____

SURPLUS JANUARY BARGAIN SPECIALS

- 30 amp plug fuse, house type 100 for \$3.00**
A WONDERFUL BUY
- 15 amp 3AG fuses 100 for **\$2.00**
 - 50 amp 5AG type HBR 100 for **2.95**
 - 40 amp 5AG type HBR 100 for **2.95**
 - 40 amp 4AG type 100 for **2.95**
 - 35 amp 4AG type 100 for **2.95**
 - 20 amp 4AG type 100 for **2.95**
 - 15 amp 4AG type 100 for **2.95**
 - 10 amp 4AG type 100 for **2.95**
 - 1 amp 4AG type 100 for **2.00**
 - 4 amp 3AG type 100 for **2.00**
 - 1 amp 3AG type 100 for **2.00**
 - 1/2 amp 3AG type 100 for **2.95**
 - 275 amp HJR type 100 for **2.95**
 - 70 amp HBR type 100 for **2.95**
 - 70 amp ACL type 100 for **2.95**

ANTENNA INSULATORS



A specially designed insulator that provides great tensile strength 10 for **60c**

- Open circuit jacks 10 for **\$1.50**
- JK 26 and PL 54 per set **49c**
- 3 AG fuse post **25c** each
- 4 AG fuse post **25c** each
- 3 AG type HJM **25c** each
- 30 ft. hook-up wire **10c**
- 6AK5, new, boxed **\$1.19**

2 MFD 600 volt oil condensers, round can **89c** each
LUMINOUS PAINT KIT **79c** each
For Dusting, Painting or Mixing To Suit
Your Requirements GLOWS IN THE DARK
1250 ft. of 2 cond. twisted stranded wire.... **\$3.95**



MUELLER CLIP JUMPER

A complete jumper, ready to use. Two No. 21-A clips and 14" of insulated wire. Packed 10 in a box. **19c** each Lots of 10 **\$1.50**

3HK4970-3 Regulator: Carbon Pile; 80V A.C.; Leland #B2475 (76 carbon discs 0.1968" ID; 0.1968" thk; 0.432" OD; solenoid contained in base; 2 5/16" diameter by 15/16" high; mounted by a strap fastened around solenoid portion; overall dimension 2.469" diameter by 3 3/4" high.



\$3.95
EACH

- J 41 A Telegraph Keys **\$.89** each
- J 5 A Telegraph Keys **.95** each
- J38 Telegraph Keys **1.25** each

- 50 watt burn back tube sockets **95c** each
- 3" round Weston meters; Model 467. 0 to 150 volts A.C. **\$5.95** each
- Removed from new surplus equipment
- 2 MFD 4000 volt D.C., G.E. 23 F 47 Prynol . . . **\$7.95**
- 90 MFD 120 volt A.C., 3 phase G.E.
- 26 F 685 Prynol **\$7.95**
- Edwards Lungen Buzzers Type O. #15. 12 volt. Works on 6 volts DC. New **69c** each
- Dual Variable Midget Condenser **\$1.49**
- 35 mmd. per section
- PL 68 covers only **5c** each
- 6 ft. cord with PL 55 plug. **59c**
- Head phones, high impedance (Used. Good condition.) **\$1.69**
- 250 ft. rolls phosphorus bronze ship-type antenna wire. Seven strands #18 **\$6.95** roll
- Vertical Antenna Mast Kit Fully adjustable 5 to 35 ft. easy to set up for fringe area FM, Television or rotary mast beam **\$12.95**



DRY AIR PUMPS

Hand Pump CPR-10198-B with 30 lb. Shallcross Gauge, Tank for silica gel, 2 bottles of gel, air hose, shut-off valve. Used for drying coax lines, instruments, etc. NEW INDIVIDUALLY BOXED. **\$4.95**

Write for Our Bargain Bulletin
DOW RADIO, INC.

1759 E. Colorado St.

Pasadena 4, Calif.

\$2.00 min. order

PHONE: SYcamore 3-1196

25% deposit with orders

Send full remittance to save C.O.D. charges.

All merchandise fully guaranteed. Subject to prior sale.

ELECTRONIC LITERATURE

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. All literature offers void after six months.

SOUND EQUIPMENT CATALOG

The Bell line of sound equipment is described in their catalog No. 5152 which has just been released. Equipment listed includes high-fidelity and public address amplifiers, industrial-type apparatus for plant broadcasting and paging, tape and disc recorders, intercoms, microphones, speakers, and accessories.

Interested parties may obtain copies of the catalog by writing to Bell Sound Systems, 555 Marion Road, Columbus 7, Ohio. Gratis.

HEATHKIT CATALOG

The new Heathkit catalog describes the full line of kits for constructing a variety of test equipment, audio amplifiers, power supplies, AM receivers and FM tuners.

Write to The Heath Co., Benton Harbor 20, Mich. for copies of the catalog. Gratis.

TV CONTROL SUPPLEMENT

Clarostat is offering a supplement to their TV control replacement manual issued last spring. The supplement gives manufacturers' part numbers and numbers of exact-duplicate replacement units. It also lists by manufacturer, the frequency of use of the various controls. Thus, the technician can stock the replacement controls needed to service the prevailing makes of receivers in his territory.

Available through Clarostat jobbers. Gratis.

TV STATION BOOKLET

Du Mont is distributing to TV station managers and engineers, a new booklet, *Station Planning*, which explains the facilities and functions of all equipment required for normal operation of a TV station. Suggested equipment layouts, floor plans, and exploded views are included in the booklet.


The booklet will be sent to all TV station managers and engineers requesting it on their company letterheads. Send request to Television Transmitter Division of Allen B. Du Mont Laboratories, Inc., 1000 Main Ave., Clifton, N. J.

GENERAL CEMENT CATALOG

General Cement's catalog No. 155 is just off the presses. Listing the full GC line of radio chemicals, alignment and repair tools, and radio and TV parts and hardware, the catalog is made available to all radio and TV service technicians who request a copy from General Cement Mfg. Co., 919 Taylor Ave., Rockford, Ill. Gratis.

RADIO-ELECTRONICS for

Send for New
1952 Catalog

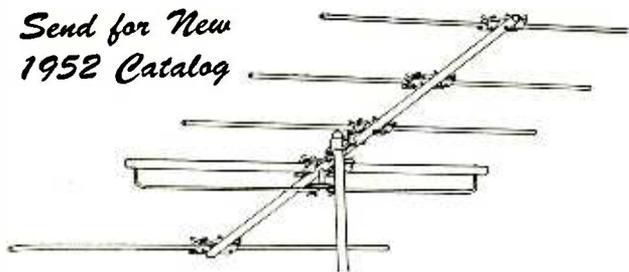

Phoenix

the One BEST Source
for All the BEST
in...

SPEED • TENNAS
• MOUNTS
• CESSORIES

PHOENIX ELECTRONICS, INC., LAWRENCE, MASS.


ANTENNAS



MOUNTS



ACCESSORIES

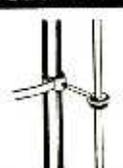

CAPACITOR BULLETIN

A new booklet (Bulletin GEC-808) describes the new G-E Tantalytic capacitors designed for low-voltage d.c. applications where small size and long life are major considerations. The Tantalytic capacitor is a foil-type, tantalum electrode, electrolytic capacitor offering greater capacitance per unit volume and longer minimum shelf-life than similar aluminum units.

Bulletin GEC-808 may be obtained from General Electric Co., Schenectady 5, N. Y. Gratis to interested parties.

POWER RECTIFIER CATALOG

Sarkes Tarzian has just released a new catalog (No. PR1) covering power-type selenium rectifiers. It contains numerous performance charts showing the effects of temperature and frequency on forward voltage drop, reverse current, and output voltage. It also lists electrical and mechanical specifications for the various power-type selenium rectifiers made by the firm.

Available upon request from Sarkes Tarzian Inc., Rectifier Division, 415 N. College Ave., Bloomington, Ind. Gratis.

TV ANTENNA CATALOG

A catalog covering the Speed line of TV antennas, mounts, and accessories is available gratis from Phoenix Electronics, Inc., Lawrence, Mass.

Radio Thirty-Five Years Ago

In Gernsback Publications

HUGO GERNSBACK	
Founder	
Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some of the larger libraries still have copies of ELECTRICAL EXPERIMENTER on file for interested readers.

**JANUARY, 1918
ELECTRICAL EXPERIMENTER**

- Raising Sunken Treasures, by H. Gernsback
- Fog Warning by Radiophone, by George Holmes
- Ground Telegraphy in War, by H. Gernsback
- The "Electro-Magnetic Depth Bomb" Modern Physics and the Electron
- "Electrician—Radio U. S. N.," by Willard Connely, U. S. N. R. F.
- Measurements of Radio Antennae on Shipboard
- The "Smallest Audion"
- French Aeroplane Radio Great Aid to Artillery
- A Short-Cut to Code-Learning, by Thomas Reed
- "Ham" Aerials, by W. J. Howell
- A Mechanical Inductance Changer, by Frederick J. Schlink
- A High Potential Storage Battery, by Thomas Lewis Herren
- Method for Increasing Sensitiveness of Silicon and Galena, by Robert W. Jaeger

—end—

JANUARY, 1952

Practical, Popular-priced Books on
RADIO•AUDIO•SERVICING



A NEW BOOK ON RADIO TUBES!

RADIO TUBE FUNDAMENTALS—No. 45. By George J. Christ. 96 pages, 74 illustrations. Just off the press—the first and only low-priced book to give you such a complete picture of the how, what and why of radio tubes—the heart of any set. The author, an engineer and teacher, gives the radio man the information he wants about tubes in the way he's accustomed to using it. Here's a practical book that will increase your understanding of radio whether you're a 25-year man or just starting out. Covers tubes from the electron theory to a working analysis of the different types of tubes. You'll find this new Gernsback Library Book as valuable as your soldering iron! Order your copy today. Only \$1.00.

TWO TOP FLIGHT \$1.00 BOOKS

MODEL CONTROL BY RADIO—No. 43. By Edward L. Safford, Jr., 112 pages. An authority in the field of radio control gives you the first complete book on the subject. For beginner and expert. Tells you what radio control is, how it works and how to construct not only component parts but a complete system as well. Illustrations explain each step.

HIGH-FIDELITY TECHNIQUES—No. 42. By James R. Langham, 112 pages. You've never seen a technical book like it! Just as he'd talk to you across the work bench, RADIO-ELECTRONICS' popular audio writer tells you how to design your own equipment and how to get top performance from it. Takes the double talk out of high-fidelity work.



THREE IMPORTANT 75¢ BOOKS



PUBLIC-ADDRESS GUIDE—No. 41. 80 pages. This handy book shows the service technician the way to extra income in big-paying PA work. Covers installation, maintenance and construction.

THE CATHODE-RAY OSCILLOSCOPE—No. 40. 112 pages. A "must" for servicing TV, FM and AM receivers and in amateur operation! Tells in simple, but technically sound language, how the scope works and how to use it.

PRACTICAL DISC RECORDING—No. 39. 96 pages. Tells you how to make good disc recordings. Covers every phase, theory as well as technique. A full chapter is devoted to each component.

9 POPULAR 64-PAGE BOOKS — 50¢ EACH

HANDY KINKS AND SHORT CUTS—No. 29. A treasury of time savers! Antennas, power supplies, test equipment, phonographs, amplifiers. Easy reference. Illustrated.

UNUSUAL PATENTED CIRCUITS—No. 30. A gold mine of important hook-ups. Control circuits, detectors, amplifiers, power supplies, foreign circuits.

RADIO QUESTIONS & ANSWERS—No. 31. Answers the tough ones on circuit diagrams, amplifiers, receivers, transmitters, meters and test equipment.

ADVANCED SERVICE TECHNIQUE—No. 32. A "must" for the advanced service technician! Covers specialized problems of servicing not usually found in ordinary textbooks.

AMPLIFIER BUILDER'S GUIDE—No. 33. For the designer and builder of audio equipment.

Covers a variety of amplifiers with power outputs from 8 to 30 watts.

RADIO-ELECTRONIC CIRCUITS—No. 34. For the experimenter—circuit diagrams of intercom systems, power supplies, voltmeters, electronic relays, receivers, etc.

AMATEUR RADIO BUILDER'S GUIDE—No. 35. For the "ham" who builds his own. Receivers, transmitters, antennas, converters, etc. Practical construction data.

RADIO TEST INSTRUMENTS—No. 36. Practical construction data on signal tracers, capacity meters, portable and bench multi-checkers, voltmeters, etc.

HOW TO BUILD RADIO RECEIVERS—No. 38. Describes 18 modern sets including short wave, broadcast, vhf, portable, ac-operated, ac-dc, miniatures—types for every fan.

THE GERNSBACK LIBRARY

SEE YOUR DISTRIBUTOR OR MAIL THIS COUPON TODAY

RADCRAFT PUBLICATIONS, INC. Enclosed is \$..... for which please send me postpaid, the books checked below.
25 West Broadway, New York 7, N. Y.

- 29 30 31 32 33 34 35 36
- 38 39 40 41 42 43 45

Name.....
Street.....
City..... Zone..... State..... 12



Frank J. Moch

president of the
National Alliance of Television
and Electronics Service Associa-
tions.

says:
"there is no other
Oscilloscope like the

Simpson MODEL 476 MIRRORSCOPE

Simpson Model 476 MIRRORSCOPE reflects the 5-inch cathode ray tube image on a high grade mirror mounted in the cover allowing the tube to be vertically mounted which reduces bench space requirements to 9" x 8" and brings the viewing surface to eye level. The upright construction permits location of controls and connections for maximum convenience and allows for internal cathode ray tube connections at the front of the panel. The unique construction and superior specifications of the Model 476 make it worthy of leading experts' recommendation for all phases of TV receiver service including observation and diagnosis of Sync. signals. For complete information see your Parts Jobber or write: SIMPSON ELECTRIC CO., 5200 W. KINZIE ST., CHICAGO 44. COLUMBUS 1-1221.



BURTON BROWNE ADVERTISING

SOCIAL SECURITY

Are you working for yourself as the owner of a trade or business? If so, you may be one of the 4½ million individuals who became covered for the first time under the Social Security Act on January 1, 1951. Until this year, it was not possible for a self-employed individual to earn credits toward old-age and survivor's insurance benefits.

Under the provisions of the new act, you may collect up to \$80 per month on your retirement at 65; or after your death, your widow, if she has minor children or is over 65, may collect up to \$60. This may be increased to as much as \$150 if there are two or more minor children.

Steps should be taken now so that your self-employment income will be credited to your account at the proper time. The first thing to do is to be sure you have a social security card. If you have had a card before and lost it, get a duplicate card at your nearest field office. If you have never had a card, the field office will assign one to you.

Self-employed individuals make only one report each year to the Social Security Administration regarding their net earnings. This report will be filed with the regular Income Tax return.

Self-employed individuals, with the exception of farm operators and certain professional groups listed below who were excluded by law, are covered on a compulsory basis. Only two requirements are to be met. One is that the business or profession is not one of the excepted groups listed below. The other is that the individual have net earnings from self-employment of at least \$400 during the taxable year. All individuals who meet these two requirements are covered and will be required to file an annual report on their net earnings. You should not report your earnings on any quarterly report you file for your employees.

The law specifically exempts from coverage:

- | | |
|----------------|----------------------------------|
| Farm operators | Veterinarians |
| Lawyers | Architects |
| Dentists | Certified, licensed, registered, |
| Physicians | or full time accountants |
| Osteopaths | Christian Science practitioners |
| Chiropractors | Professional engineers |
| Optometrists | Funeral directors |
| | Naturopaths |

If any individual in the above category is employed by someone else, he would, of course, be reported as an employee on his employer's regular quarterly tax return.

Unless you have net earnings from self-employment of at least \$400 for a calendar or taxable year beginning on or after January 1, 1951, it is not necessary for you to make the report at the end of the year. However, if your net earnings are \$400 or more, you must report and pay the social security tax of 2¼% on the first \$3600.


Any Social Security Administration office will assist you on Social Security matters, whether it be to issue a Social Security card or to furnish information or a booklet to you.

—end—

**STAN-BURN
E-P-A-R-K-E**

- | | |
|---------------------------|--------------------|
| ● Condenser Specials | ● Speaker Specials |
| BY PASS | ALL GUARANTEED |
| ● ALL GUARANTEED | |
| ● 20x20-150 Stan Burn .41 | 4" P.M. \$1.64 |
| ● 50x30-150 Stan Burn .49 | 5" P.M. 1.75 |
| ● 20x150 Stan Burn .32 | 6" P.M. 2.41 |
| ● 8-450 Stan Burn .41 | 8" P.M. 3.41 |
| ● 16-450 Stan Burn .49 | 12" P.M. 6.33 |
| ● 4 Prong Vibrators | 4 x 6 P.M. 2.19 |
| ● Lots of 12 or more 1.19 | 6 x 9 3.73 |
| ● Turret TV | 5 x 7 3.43 |
| ● Tuners \$18.95 | 10" P.M. 5.48 |

NEW for '51 AUTOMATIC RADIOS

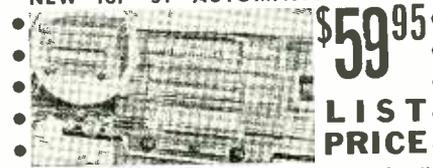

\$59.95
LIST PRICE.

- Each auto radio is specifically designed to fit all 1949, 1950 and 1951 cars for Ford, Plymouth, Dodge, Chevrolet, Hudson, Henry J and Studebaker. All incorporate the same outstanding features: Six-tube superheterodyne. Six-volt storage battery operation. Two dual-purpose tubes. Eight-tube performance. Installation in a few minutes. Three-gang tuning condenser and tuned R.F. stage for extreme sensitivity. Permanent magnetic dynamo speaker with Powerful Auto #5 magnet. Low battery drain. Weight 10 lbs.

ATTRACTIVE DISCOUNTS TO DEALERS

CHASSIS 630 K3B Video Product \$139.50

CATHODE RAY TUBE SPECIALS	
● 7JP4	\$15.00
● 10BP4	14.95
● 12LP4	19.95
● 14BP4	19.95
● 16DP4A	26.00
● 16GP4	33.00
● 16AP4A	39.00
● 16RP4A	26.00
● 17BP4A	27.00
● 20CP4	39.95
● 19AP4A	47.95
● 19DP4A	47.95
● 24AP4A	73.00
● Single Ion traps39
● Double Ion traps59

- | | |
|----------------------------|------------------------|
| ● RAM TRANSFORMERS | 70° DEFLECTION |
| RCA type for 16" to 24" | YOKES |
| ● X032 | \$3.85 |
| ● G.E. Type for 16" to 24" | |
| ● X045 | \$3.85 |
| ● These are very special | Todd wired replacement |
| ● prices while they last! | Special \$3.85 |

- ANTENNAS**
- Conicals, less mast, 10 element
 - Circle V, less mast
 - Chimney Mounts—1-12 .95 12 or more
 - 100 ft. roll strapping
 - Mast standoffs
 - 10 ft. masts, each
 - 12 or more, each
 - 55 mil. 300 ohm wire white or black, 1000 ft.

AUTHORIZED DISTRIBUTORS for: General Electric, Kenrad, Tung-Sol, National Union, Jewel, De Wald, Regal, Automatic and Setchel Carlson.

We carry a complete line of popular makes of Radio and TV tubes, at 50% discount. Also many other special purpose and transmitting types, and all electronic parts and equipment at lowest prices. Send us a list of your requests for quantities and prices. Terms: 20% with order. Balance COD All prices FOB New York Warehouse, Minimum order \$5.00 Write for our latest price list to Dept. RE-1

STAN-BURN RADIO and ELECTRONICS CO.
(C.B.S. THEATRE BLDG.)
1697 BROADWAY • NEW YORK 19, N.Y.

RHOMBIC TV ANTENNAS

Power Gains of 400 and More for consistent extreme fringe area reception. BUILD YOUR OWN—USE OUR RHOMBIC TV ANTENNA BOOK

- Complete Simplified Building instructions and drawings for 24 sizes.
- Use and Design of open wire lines.
- Information on Stacked Rhombics.

\$1.50 Richard J. Buchan
Postpaid WOTJF Bricelyn, Minn.

SURPLUS
BOUGHT & SOLD
GOULD GREEN 252 Greenwich St. Worth 4-8044—NYC 7

TWIN-TRAX* TAPE RECORDERS



...give you more

MORE MODELS
the most complete variety of recorders for professional, semi-professional and experimenter use.

MORE FEATURES
for better quality, smoother performance and easier operation.

MORE VALUE
because our direct sales policy saves you dealer markups.

Send today for our catalog 5109 which lists complete technical specifications and performance ratings for all recorder models and accessories.*Trademark Reg.

AMPLIFIER CORP. OF AMERICA
398 Broadway New York 13, N. Y.

WHEN WRITING TO ADVERTISERS PLEASE MENTION RADIO ELECTRONICS

SHOOT TV TROUBLE FAST!

With H. G. Cisin's Copyrighted Rapid "TV TROUBLE SHOOTING METHOD"

Without experience or knowledge, this guaranteed new method of servicing TV sets enables you to DIAGNOSE TV troubles as rapidly as an expert. NO THEORY—NO MATH—you can locate all faults in record-breaking time, regardless of make or model.

"TV TROUBLE SHOOTING METHOD" is the most valuable aid to TV servicing ever written. Be a TV Trouble Diagnostician. Increase your present earnings. Open your own Profitable Business or get a high-paying skilled job.

It's all in this book . . . Nothing more to Pay—Nothing else to Buy

Alphabetically listed, there are 85 picture troubles, over 58 raster and IT sound troubles and by this unique copyrighted method you know EXACTLY WHERE the trouble is; plus step-by-step instructions, including 69 RAPID CHECKS, enabling you to find the faulty part.

13 IMPORTANT PRELIMINARY CHECKS NEED NO INSTRUMENTS! Of the 69 Rapid Checks, OVER 65 ALSO REQUIRE NO INSTRUMENTS! Rapid checks include emergency checks for distorted pictures, defective tubes including PIX tube, plus 57 others. ALL EXPLAINED IN SIMPLE LANGUAGE. PERFORMED WITHOUT INSTRUMENTS. MANY CHECKS USE THE PICTURE TUBE AS A GUIDE

H. G. Cisin, the author, is the inventor of the AC/DC midjet radio. He licenses RCA, AT&T, etc. He has also trained thousands of technicians now owning their own prosperous TV service organizations or holding highly paid TV positions. His years of experience are embodied in this remarkable new TV TROUBLE SHOOTING METHOD. Guaranteed. Money Back in 5 Days if Not Satisfied!

If you use coupon below you will receive, ABSOLUTELY FREE, a copy of H. G. Cisin's new book "TV Terms Simply Explained including Picture Guide" which sells for \$1. ACT NOW and get both books postpaid at the cost of only one.

\$1
Post-paid

RUSH COUPON NOW!

H. G. CISIN—CONSULTING ENGINEER
(Dept. E-9), 200 Clinton St., Brooklyn 2, N. Y.

Name.....
Address.....
City.....Zone.....State.....

A BANKER'S VIEWPOINT

Dear Editor:

That you may know a little about me I wish to inform you that by profession I am a banker, that as a hobby I follow electronics with a deep interest in television and radio. It has been my privilege to have contacts with the businesses selling these products and with individuals and shops doing service work.

In RADIO-ELECTRONICS for August 1951 appeared your article "Service Technicians' Trials," which I read with much pleasure. I surmise, however, that the circulation of your magazine is among persons interested in the radio, television and electronics field from the angles of industry, science and hobby, and that it does not reach a vast majority of the service technician's problem children. The article thereby becomes one of consolation or eulogy to those who already and long have known the story. Every service technician has experienced what you have written.

Your story should be in every newspaper in the country and along with it should be some convincing evidence that there are many capable service technicians who render efficient service and are entitled to adequate compensation for the service they render. Permit a little pun, sir. In television as in the case of a wife, it's not the initial cost that hurts, it's the upkeep.

Who is gypping the public—the manufacturer, the dealer or the service technician? I believe that the skilled technician operating in the field is doing all that he can to maintain satisfied customers. I believe that dealers and merchants, vendors of general merchandise, have been granted the opportunity to sell an intricate device of which they know nothing, the complexities of which are far greater than the intricacies of any purely mechanical device on the market, and their ignorance and irresponsibility has been blithely pushed off as a problem of the service industry. But, let's not call them "gyps" but just plain greedy.

If "gypping" exists, responsibility must be laid in the lap of the manufacturer, for it is in his power to correct any injustices that may exist:

- First, by a process of franchising qualified service shops to perform service work either under guarantees or under customer contracts.
- Second, by supplying the franchised shop with full data, schematics, parts lists, changes and so on, relating to the units manufactured.
- Third, that an adequate supply of the parts peculiar to their units, be made available at the shop at all times, availability to be on consignment basis subject to audit accounting.
- Fourth, all sales contracts ultimately to be in the hands of service technicians too. * * * *

R. A. C.

Lorain, Ohio

**SPECIAL!!
6 TUBE AC-DC KIT**

At Last! A low-priced kit designed for high sensitivity, excellent selectivity and good tone quality. Uses 25L6, 25Z6, 6SQ7, 6SA7, 6SK7, 6SK7 in an easily constructed circuit. The 6 Tube Kit is shipped with all parts, including punched chassis, resistors, condensers, coil, sockets, PM Speaker, hardware, etc.

And at a closeout price of only **\$6.95**

X182 less tubes and cabinet
X183 Extra for matched set of six tubes for kit **\$3.25**

5 TUBE AC-DC SUPERHET KIT

Five tube superheterodyne kit, A.C.-D.C. contains all components required to construct this latest design, highly sensitive superheterodyne broadcast receiver complete with black bakelite cabinet (excludes wire and solder) Price **\$7.95**

Extra for a kit of 5 tubes (12AT6, 12BA6, 12BE6, 35WA, 50C5). Price **\$3.25.**

YOUR MONEY RETURNED IN FULL—

If the New Regency Television Booster fails to improve your television enjoyment! Bring your picture out of the snow and reduce interference!

- Push-Pull Neutralized triode design assures high gain without adding snow.
- No external impedance matching devices required.
- Inductive tuning assures same high-gain wide-band operation on all channels.
- Single knob tuning control.
- Underwriters approved with 90 day RMA guarantee.

LOWEST Price—ONLY **\$19.11**

MODEL NFRD—RADIO NOISE FILTER

If it doesn't work, send it back!

We absolutely guarantee that our Model NFRD will eliminate all line noises when properly connected to radios, television sets, short wave sets, motors, electric shavers, refrigerators, vibrators, oil burners, transmitters, and all other sources of interference. This unit will carry up to 12 amperes or 1 1/2 KW of power and may be used right at the source of interference or at the radio.

Small size only 2 1/2" x 1 3/4" x 4 1/2". Very low price only **Each \$1.95**

A SCIENTIFICALLY DESIGNED PHONO SCRATCH FILTER

Resonated at approximately 4500 cycles effectively reducing objectionable needle scratch without altering the brilliancy of reproduction.

Contains a HI-Q SERIES resonated circuit. Tested by means of an audio oscillator and an oscilloscope to give 22 db attenuation with very low signal loss.

EASY TO ATTACH

Just two wires to clip on. Compact **\$1.98**

Price

THREE TUBE PHONO AMPLIFIER

An assembled unit ready for installation using tone and volume control and six feet of rubber **\$2.95**

cord

(Not including Tubes)

With Complete Set of Tubes..... **\$3.95**

PHONO OSCILLATOR

Wireless phono oscillator transmits recording for crystal pick-ups or voice from carbon mike through radio without wires. Can also be used as an inter-comm by using P.M. speaker as mike. Price (excluding tubes)..... **\$2.95**

With Complete Set of Tubes..... **\$3.95**

Grab Bag Special, 10 pounds of Misc. Electronic Material—Transformers, Condensers, resistor, wire, etc. Price **\$1.95 ea.**


Satisfaction guaranteed on all merchandise. All prices subject to change without notice.

RADIO DEALERS SUPPLY CO.

154 Greenwich St. New York 6, N. Y.

RADELCO

LIGHTNING ARRESTOR

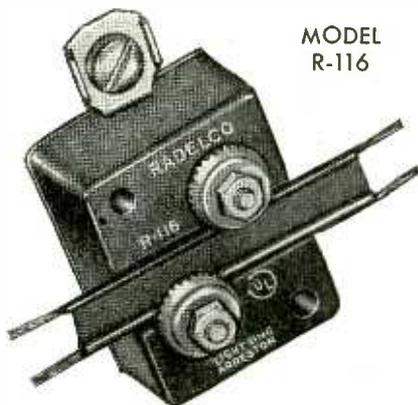

MODEL R-116

IT'S THE LOWEST PRICE UNDERWRITERS' LISTED ARRESTOR ON THE MARKET

ORDER FROM YOUR NEAREST PARTS JOBBER LIST PRICE **90¢**

AMPERITE

Studio Microphones at P.A. Prices

Ideal for BROADCASTING RECORDING PUBLIC ADDRESS

"The ultimate in microphone quality," says Evan Rushing, sound engineer of the Hotel New Yorker.
 • Shout right into the new Amperite Microphone—or stand 2 feet away—reproduction is always perfect.
 • Not affected by any climatic conditions.
 • Guaranteed to withstand severe "knocking around."



Models RBLG—200 ohms RBHG—Hi-imp. List \$42.00



"Kontak" Mikes Model SKH, list \$12.00 Model KKH, list \$18.00

Special Offer: Write for Special Introductory Offer, and 4-page illustrated folder.

AMPERITE Company, Inc.
 561 BROADWAY • NEW YORK 12, N. Y.
 Canada: Atlas Radio Corp., Ltd., 360 King St. W., Toronto

ULTRAHIGH FREQUENCY ENGINEERING, by Thomas L. Martin, Jr. Published by Prentice-Hall, Inc., 70 Fifth Ave., New York N. Y. 5 1/2 x 8 1/4 inches, 456 pages, Price \$8.00.

This text is intended for senior college students, but will be understood by technicians who know algebra and calculus. There are separate chapters on wave-shaping, trigger circuits, waveguides, klystrons, and magnetrons. The subjects are presented logically and clearly.

The author has a flair for bringing out less obvious facts. Often he approaches his subject from more than one viewpoint, to the advantage of the reader.

Unfortunately, symbol co-ordination is lacking in a number of places. For example, R_1 and R_T are used interchangeably in one discussion. An equation refers to e_c , but the corresponding diagram shows e_r . The symbol r is used in several places to represent the *voltage* of a capacitor. Capacitor polarity is shown indiscriminately. These are minor errors but they may slow up the reader who likes to follow through solidly.

ELECTRONICS, by Jacob Millman, Ph.D. and Samuel Seely, Ph.D. Second Edition. Published by McGraw-Hill Book Co., Inc., 330 West 42 St., New York, N. Y. 6 x 9 inches. 598 pages. Price \$7.25.

This is the new edition of a well-known text. Much of the material has been clarified and modernized. Knowledge of calculus is assumed, but physical explanations are given throughout.

The book begins with analysis of the path and motion of an electron in a field. This leads to oscilloscopes, magnetrons, cyclotrons and betatrons. Next follows the behavior of electrons in metals, for an understanding of semiconductors, contact potential, cathodes, and similar subjects. There are several chapters on electrons in gases. Technicians will find this section interesting because it deals with characteristics of thyratrons, ignitrons, fluorescent lamps, mercury vapor and similar types.


Problems and references are given at the end of chapters.

WIRELESS SERVICING MANUAL (Eighth Edition) by W. T. Cocking. Published for Wireless World by Iliffe & Sons, Ltd., Dorset House, Stamford Street, London S.E. 1, England. 4 1/4 x 7 inches, 296 pages. Price 12s. 6d.

This manual has aided service technicians since 1936. This latest edition covers modern servicing of AM receivers, broadcast and short wave. There is also an introduction to TV servicing. The author shows how to locate and cure various troubles in amplifiers, converters, a.f.c. and other circuits. Motorboating, instability, hum, whistles and distortion are discussed. Much space is devoted to capacitor ganging in t.r.f. and superhet receivers. Some information is also given on meters, oscilloscopes, signal generators and tube testers.

In spite of space limitations the manual contains clear and useful information. The appendix has wire tables, formulas, and color codes.—IQ

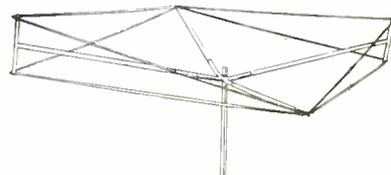CASH IN ON FRINGE AREA SALES with the sensational



DAVIS SUPER RHOMBIC ANTENNA

- Eliminates ghosts!
- Eliminates costly stacked arrays!
- Gives all-channel coverage with gain of over 12 DB!
- Features exclusive 15-degree tilt to take advantage of horizontal wave lengths.
- Extensively lab and field tested. Constructed with aluminum alloy elements that out-perform copper wire rhombics.
- Space tapered elements construction gives automatic match to all commonly used lead-ins without matching transformer.
- Super-sensitive 12-degree directivity for maximum distance (DX) reception and ghost elimination.
- Pre-assembled, lightweight construction cuts installation time to minutes!

TO: DAVIS ELECTRONICS 1-2
 3047 W. Olympic Blvd., Los Angeles 6, California
 Sir: Rush information to me as checked below:
 Send free technical data on Super Rhombic Antenna.
 Send name and address of nearest jobber.


Name _____
 Street _____
 City _____ State _____

GIVE Voluntarily TO MARCH OF DIMES JANUARY 2-31

JANUARY

	1	2	3	4	5
6	7	8	9	10	11
12	13	14	15	16	17
18	19	20	21	22	23
24	25	26	27	28	29
30	31				

Cash in on TV Service Profits!

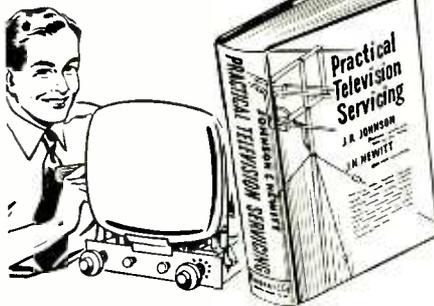

PRACTICAL TELEVISION SERVICING

By J. R. JOHNSON and J. H. NEWITT
375 pages, 230 illustrations, \$4.00

Good training for television service doesn't need to cost you a lot of money! This great book at only \$4.00 is a complete guide that tells you step by step just what to do, what mistakes to avoid, what tools, parts and equipment to use—in short, how to handle every phase of television receiver servicing promptly, efficiently and profitably.

LEARN FAST! . . . LEARN RIGHT!

The authors of PRACTICAL TELEVISION SERVICING actually operated a TV service shop to get the specific, how-to-do-it information they now pass along to you in easily understood form. In addition to a clear explanation of how television work differs from radio, they show exactly how to perform all operations in trouble-shooting, diagnosing and remedying television troubles. No needless theory! They show you exactly how to do the work!

CHOCK FULL OF HELPFUL CASE HISTORIES AND SERVICE HINTS

Dozens of actual TV servicing case histories and service hints make the book literally worth its weight in gold.

Subjects include: TV System Fundamentals; R-F, I-F and Detector Sections; Video Amplifiers; Cathode Ray Tubes; Synchronizing and Sweep Circuits; Power Supplies; Antenna & Wave Propagation; TV Receiver Installation; Test Equipment and Alignment; Wiring and Repair Techniques; Color Television; Receiver Layout Diagrams—and dozens more. In addition there are countless tips on such things as getting better fringe area reception; improving picture linearity; checking video response with a square wave; getting signals over a mountain and numerous others. Send coupon today for 10-day examination.

READ IT 10 DAYS . . . at our risk!

Dept. RE-12, RINEHART BOOKS, Inc.,
Technical Division,
252 Madison Avenue, New York 16, N. Y.

Send PRACTICAL TELEVISION SERVICING for 10-DAY FREE EXAMINATION. If book is O.K. I will then promptly remit \$4.00 in full payment. If not, I will return book postpaid in good condition and owe you nothing.

Name _____

Address _____

City, Zone, State _____

Employers' Name & Address _____

Price outside U.S.A., \$4.50—cash only. Money back in 10 days if you return book.

RADIO SCHOOL DIRECTORY

F.C.C. COMMERCIAL RADIO OPERATORS LICENSE

CRITICAL SHORTAGE OF LICENSED OPERATORS EXISTS!!!

A wonderful future is yours with an F.C.C. commercial radio telephone or telegraph operators license, leading to top-salaried jobs in aviation, broadcasting, transportation and Civil Service. Sensational new simplified HOME STUDY course teaches you in the shortest possible time at lowest possible cost. NO OTHER COURSE LIKE IT! Proven valuable during World War II in speedily training thousands of men, eliminates tedious schooling, exam papers, wading through books. Each page of text directly related to official F.C.C. exam. questions, thus assuring you of all theory requirements.

The entire up-to-date course, nothing else to buy, containing 230 pages of complete material, diagrams, etc., yours for only \$9.95. Send check or money order; or pay postman \$9.95 upon receipt; plus C.O.D. charges. Complete satisfaction or money refunded within ten days.

STREAMLINED SELF STUDY COURSES
509 5th Ave. Dept. A New York, N. Y.

AUDIO (SOUND) ENGINEERING COURSE HOME STUDY TRAINING

Prepare yourself, in your spare time for a BIG PAY JOB as an AUDIO ENGINEER. Practical, easy-to-understand lessons, written by nationally recognized Audio Engineers and Educators.

Prepare for a SUCCESSFUL CAREER in the TELEVISION, RADIO, DISC AND TAPE RECORDING, ELECTRONICS AND MOTION PICTURE INDUSTRIES.

Training will not interfere with present employment.

EARN WHILE YOU LEARN
WRITE FOR COMPLETE DETAILS—TODAY

B. M. Klekner, D.Sc., Ph.D.

President

HOLLYWOOD TECHNICAL INSTITUTE
3359 Cahuenga Boulevard
Hollywood 28, California

TELEVISION

Big demand for graduates

B.S. degree in 27 mo. in radio including TV engineering—VHF, UHF, AM and FM. New TV lab. Over \$100,000 worth of equipment. Also new modern physics lab. Intense specialized course includes strong basis in mathematics, advanced design in radio and in TV.

Hundreds of young men each year are earning engineering degrees in this recognized institution. Start any quarter. Many earn a major part of expenses in this industrial center. Low tuition. Competent instruction. Thorough, intense, practical program.

Also B.S. degree in 27 mo. in Aeronautical, Chemical, Civil, Electrical and Mechanical Engineering. Approved for veterans. Enter March, June, Sept. and Dec. Send for free catalog. ENROLL NOW

INDIANA TECHNICAL COLLEGE
1712 E. Washington Blvd., Fort Wayne 2, Indiana

RADIO ENGINEERING FM—Television—Broadcast

Police Radio, Marine Radio, Radio Servicing, Aviation Radio and Ultra High mobile applications. Thorough training in all branches of Radio and Electronics. Modern laboratories and equipment. Old established school. Ample housing facilities, 7 acre campus. Small classes, enrollments limited. Our graduates are in demand. Write for catalog.

Approved for Veterans

VALPARAISO TECHNICAL INSTITUTE
Dept. C VALPARAISO, INDIANA

RADIO COURSES

- RADIO OPERATING • CODE
- RADIO SERVICING • ELECTRONICS
- F.M. TELEVISION

Preparation for Civilian, Maritime, Army and Navy license requirements.

Write for Catalog TE

YMCA

TRADE & TECH. SCHOOL
15 W. 63 St., N. Y. 23
ENcl. 2-8117

RADIO ENGINEERING

B. S. DEGREE IN 27 MONTHS
Complete Radio Engineering course incl. Telev., U.H.F. and F.M. BS Degree Courses also in Mech., Civil, Elect., Chem. and Aero Eng.; Bus. Adm., Acct. Extensive campus, modern buildings, well equipped labs. Low cost. Prep. courses. Personalized instruction. Heavy demand for graduates. Placement service. Founded in 1884. Prepare now for the civil and military opportunities ahead. Enter Jan., March, June, Sept. Write for Catalog.

TRI-STATE COLLEGE
2412 COLLEGE AVE. ANGOLA, INDIANA

ATTENTION...

A NEW department of the DON MARTIN SCHOOL OF RADIO AND TELEVISION ARTS AND SCIENCES . . . for instruction and training in—TELEVISION—incorporating:

Production: Writing, Directing, Producing, Acting, Staging, Lighting.

Engineering: Transmission, Receiving, Camera and Studio, Operation, Theory of Video, Pickup and Reproduction.

Approved for veterans.

THE DON MARTIN SCHOOL OF RADIO AND TELEVISION ARTS AND SCIENCES

1655 No. Cherokee, Hollywood 28, Calif. HU. 23281.

RADIO COURSES

Preparatory Mathematics, Service, Broadcast, Television, Marine Operating, Aeronautical, Frequency Modulation, Radar.

Classes now forming for the
Mid-Year term beginning Feb. 1, 1952
Entrance exam. Jan. 21, 1952
Veterans. Literature.

COMMERCIAL RADIO INSTITUTE
(Founded 1920)
38 West Biddle Street, Baltimore 1, Md.

COMPUTING MACHINERY COURSES

(Math and other subjects)

Guided study for the beginner or advanced student with 100% cooperation from the instructor when needed. Write us for complete information on our courses. Cost, \$9 to \$35.

EDMUND G. BERKELEY AND ASSOCIATES
MAKERS OF SIMON AND SQUEE
Small Electric Robots
36 West 11 Street, R1, New York 11, N. Y.


RADIO and TELEVISION ELECTRONICS

Thorough Training For Men and Women in All Technical Phases
New Classes (Day & Eve.) Start NOVEMBER 30, 1951
FREE PLACEMENT SERVICE FOR GRADUATES
For Free Catalog Write Dept. RC-52

RCA INSTITUTES, Inc.
A Service of Radio Corporation of America
350 WEST 4TH STREET NEW YORK 14, N. Y.

SCIENCE FICTION

— at its best!

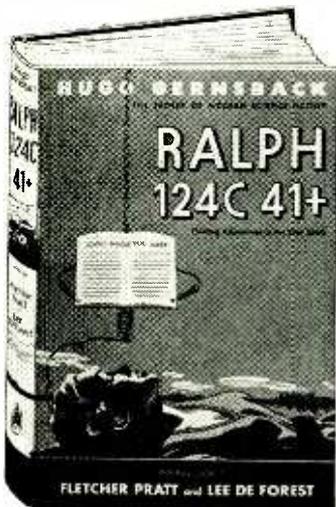

By HUGO GERNSBACK
Father of Modern Science Fiction

Dr. Lee de Forest calls RALPH 124C 41+ the greatest science fiction novel in two generations

Originally written in 1911, it predicted in accurate detail—

- Radar
- Television
- Wire recording
- Learning while you sleep
- Blood transfusions
- Many other developments which have become part of every day living

One of the most amazing books ever written—a slam-bang adventure story of the year 2660—but much more than just another action story! The plot is interwoven with the most startlingly accurate scientific prophecies ever described in a single book—not fantasy or flights of imagination, but the logical projection of established scientific facts! Many of the things predicted, scoffed at in 1911 when the book was written, have become necessities today. Many others will surely become fact in the years to come.

WRITTEN FOR RADIO-TV MEN

Hugo Gernsback originally wrote RALPH 124C 41+ as a serial in the world's first radio magazine. At the time it served as an inspiration for many young men who have become top engineers and scientists in electronics today. Now when science novels have gained a new popularity, RALPH 124C 41+, in this new second edition, is regarded as the classic in the field. No one interested in electronics, no true science-fiction fan can afford to miss it. **THE SUPPLY IS LIMITED.** Order your copy today—only \$2.50 postpaid.

MAIL THIS COUPON TODAY

RADIO PUBLICATIONS
25 West Broadway, New York 7, N. Y.
Gentlemen:
Send me a copy of RALPH 124C 41, postpaid, at once. My remittance of \$2.50 is enclosed.

NAME.....
STREET.....
CITY..... ZONE..... STATE.....

RADIO COMMUNICATION AT U.H.F., by John Thomson. Published by John Wiley & Sons, Inc., New York, N. Y. 5 1/4 x 8 1/2 inches, 203 pages. Price \$5.50.

This book is definitely not for the radio beginner or the practical service technician. It deals with more advanced concepts of u.h.f. circuits and tubes. The material is unusually concise. Little space is wasted on details or information which an experienced engineer may himself possess or derive. The language is largely mathematical. Informative charts and tables are included.

The text is based on the postwar experience of the author and his associates. Among the chapters are: traveling wave tubes, magnetrons, noise, mixers and oscillators, control by molecular absorption, and frequency control.

ROCKETS, MISSILES, AND SPACE TRAVEL, by Willy Ley. Published by The Viking Press, 18 East 48th Street, New York, N. Y. 6 x 8 1/2 inches, 436 pages. Price \$5.95.

Here is a documented, exciting account of the history of rockets from their early use as weapons of war to the more intriguing prospective applications in space travel. The gradual evolution of the space rocket is covered in considerable detail. The question of space travel is not one of derring-do, but rather of mathematical travail. Space travel, when it comes, must be based on taking advantage of well-established natural laws. The problems of space travel may be reduced through the use of multiple-step rockets and space terminals, both are discussed.

For rocket enthusiasts the primary concern is space travel itself. The assumption is made that existing methods of communication and space navigation by radar would be satisfactory, hence present no insoluble difficulties. The author does discuss these topics very briefly and passes along the novel idea of having a system of three space stations, revolving around the earth for world-wide radio and TV coverage.

Based on the author's many years of experience with rocket theory and experiment, on the surface more fantastic yet ultimately more believable than science fiction, Willy Ley's very authentic book props up the old cliché about truth being stranger than fiction.—MC

DESIGN, CONSTRUCTION AND OPERATING PRINCIPLES OF ELECTROMAGNETS FOR ATTRACTING COPPER, ALUMINUM AND OTHER NONFERROUS METALS, by Leonard R. Crow. Published by Scientific Book Publishing Co., Vincennes, Indiana. 5 1/2 x 8 1/2 inches, 38 pages. Price \$1.00 paper binding, \$1.25 cloth binding.

This educational booklet, which should interest experimenters and students, uses text, photographs, and diagrams in a study of practical magnetism. Step-by-step, the subject matter progresses from ordinary magnets to a special unit which attracts nonferrous metals. The special electromagnet operates on the same principle as that of a shaded-pole motor.



MODEL 106

Vacuum Tube Voltmeter
✓CHECK THESE FEATURES

Specially designed for field alignment of television and radio sets. Uses dual triode balanced bridge circuit. All functions and ranges completely electronic—meter cannot burn out. Zero center position for FM discriminator alignment. Uses 1% precision resistors for voltage multipliers. 5 DB ranges. Full scale deflection of 1 1/2 volts for both AC-DC volts. Measures resistance in 5 ranges from .2 ohm to 1000 megs. 1 Meg isolating resistor in probe.

SPECIFICATIONS

DC VOLTAGE: Input resistance 16.5 megs or 1 1/2 megohms per volt. Ranges: 0 to 1.5, 10, 100, 300, 1000 up to 30,000 volts (with accessory probe.)

AC VOLTAGE: Input resistance 2 megohms. Ranges 0 to 10, 100, 300, 1000. Frequency response flat from: 25-100,000 cycles.

OHMS: 1000 — 10,000 — 100,000 — 10 megohms, 1000 megohms. Compact, portable bakelite case measures 4 1/4" x 5 1/4" x 2 7/8".

MODEL 106.....\$35.90

In Kit form.....\$23.90

MODEL HVP 30,000 Volt Probe for Model 106.....\$8.75

Write Dept'RE1 for latest FREE Catalog and Jobber Discount



ON-THE-SPOT BATTERY RECORDER

WALKIE-RECORDALL 8 lb. miniature BATTERY RECORDER-PLAYBACK
Continuous, permanent, accurate, indexed recording at only 5c per hr. Instantaneous, permanent playback. Picks up sound up to 60 ft. Records conferences, lectures, dictation, 2-way phone & sales talks; while walking, riding or flying. Records in closed briefcase with hidden mike! Write for details.

MILES REPRODUCER CO., INC.
812 BROADWAY Dept'RE-1 NEW YORK 3, N. Y.

Another Outstanding Jobber.
EASTERN RADIO CORP.
1055 MAIN AVE., CLIFTON, N. J.
EICO has all 17 KITS & INSTRUMENTS in stock!
721K VTM Kit \$25.95 See EICO ad on Page 24

TAB That's A Buy!

NEW THRIFT-LITE LIFETIME PHOTO-FLASH
 Not a kit, Incl Pwr pck, Life gtd Lamp, Rfctr & 15' cord 1/1000 Sec flash every 7sec. True daylight color. Usable in any camera over 1/4" x 1 1/4" w/Type AC40. \$41.98
 Complete Outfit for AC & Battery op. Incl AC40&BP2, portopak & all accessories. \$69.98
 KODAK & COMPUR Shutters. \$69.95
 Write for Complete "THRIFT-LITE" Data Booklets, Ext. Lists, Units for Focal plane shutters & accessories.
E. BUY, SELL & SWAP

TAB "SUN-FLASH" LAMPS

No.	Replaces	Max. W-sec.	Each
U10	GE FT114	100	\$ 9.98
No. 1	AMGLO5804X	100	10.98
23ST	GE FT210	200	10.98
53GT	GE FT403	500	16.98
VA	SYLV. 4330	500	16.98
23MT	FT114	200	10.98
22ST	FT110	200	10.98
353GT	FT503	5000	\$36.98
R4340	FLAS-TIME-Tab Special		\$36.00
X-400 AIR CORPS Lamp			\$14.98

"WILLIAMSON" 10W HI-FI KIT
 10 to 20000 cycles with Ease! Internationally Famous; For HiFi enthusiasts. Incl Pwr supply, RCA chassis, Less Pre-Amp & output Xfmr. Pre-selected parts. Balanced resistive pwr supply & 5 tubes. \$29.95
 Wmson Pre-Amp Kit & Tone boost Amplifier, chassis, parts, pwr supply and 5 tubes. \$34.95
SUPER-Wide-Range HI-FI 10W KIT
 10 to 20000 cycles, 6B4G's Max Harmonic Distortion 1 1/2% at full output & only 1/2% at 5W output. Includes Bass & Treble tone boost and Tone ckt's. 4 Pre-Gonset ch. Pickup dual & 2 output (7) tubes, Parts, RCA chassis & info., less output xformer. \$29.95
 UTC Hi-Fi Output Xfmr for P.P. 275V, 6.3V, 5 & 6.4V. Cgd cap 30W. Sec. 5 taps. 2 1/2 to 250 ohms. 6.98
 GE Relec Cartridge perm. needle. 7.29
 GE Dual Relec Cartridge RFX 055. 7.29
 GE S1201 Hi-Fi Hvy duty 12" PM Spkr. 18.98
 Sensational 10" HI-FI Spkr Ideal 10 Watt Home Size. Concentric, Separable, 275V, 6.3V, 5 & Horn Drive. Tweeter-30 to 16000 cps Range. 18.98
 Electro Voice EV16H dual twill Cart. 3.98
 Extra dual needle for TWB Cart. 1.99
 1N34 static fluid good 1000 plays. .69
 1N34 static fluid good 1000 plays. .69

SNOOPERSCOPE
 Image-Converter Tube Hi-Sensitivity simplified design 2" dia. Willemite screen—Resolution up to 350 lines/in. Complete data & tube. \$4.98; 2 for. \$9.49
SPECIAL
 RADIOACTIVE MARKERS 1 1/2" OD; 5 for. .25
 DIAG CUTTERS 6 1/2" Hvy duty Eng. Shld steel. 1.69
 1N34 static fluid good 1000 plays. 1.20
 1N34 static fluid good 1000 plays. 1.20
 1N34 static fluid good 1000 plays. 1.20

TRANSFORMERS
 TV & CR Pwr Xfmr for 7" to 20" Tubes, Hi VOLTS to 20KV w/quadripler ckt. ALL Tubes, Pl. & Fil. windgs. (w/rgs.) 300 V. 275V, 6.3V, 5 & 6.4V.
 10.3A, 5.4V/8A, 5.5V/3A, Hypersil Core. Oil impreg. \$7.98
 2500V for CRT, 6.3V/6A, 2.5V/1.75A Cgd. \$7.98
 1400V/90ma, 6.3V/3A, 5V/3A H'sid. \$5.98
 1320V & 375VCT/110ma, 5V/3A, 2.5V/3.25A, 6.4V/3A, H'sid. H'Windgs. \$5.98
 1000V/150ma, 300V Bias 6.3/5A, 5V/3A, 286.3V/.65A, 6.3/1.25A H'sid. \$4.98
 1000V/45ma, 590V/80ma & 360V/55ma, 6.3V/3A, 6.3V/1A, 6.3V/7/3A Cgd, HiWindgs, USN. can be used 2X Rating Hypersil Core. 1800V V. Dbl. twd. 900V/35ma, 282.5V/2A, Excellent. \$4.98
 2x2 fil. windgs. H'sid. H'Vins. \$4.98
 840V/110ma & 530VCT/21ma, 285V/3A, 6.3V/1A, 6.3V/3A Cgd H'Vins Raytheon. \$3.98
 700VCT/125ma, 6.3V/4A, 5V/3A. \$3.98
 570V/150ma 5V/3A, 12V/4A, H'sid. \$4.49
 420VCT/90ma, 6.3V/1.0a w/imp's 6-12-24-115Vdc & 115 230vac. \$1.98

FILAMENT TRANSFORMERS
 6.3Vct/4A (rud. 6.3H'sid H'Vins. \$2.69
 6.3V/2A, \$1.39; 6.3V/1A, \$1.98
 2.5V/2A, 79c; 7Vct/12A H'Vins 15KV. \$10.98
 12.6Vct/1.25A, \$1.98; 24V/2a cgd. \$1.98

PLATE TRANSFORMERS
 7500V or 15000 V Dbl. 25M. \$19.95
 3000V/10ma, Cgd H'Vinsul. 8.95

NEW TV COMPONENTS
 HV Horiz & Def Output Xformer Sim RCA \$1.98
 Width Control Sim 2" dia. \$1.98
 UTC 86662 VBOXfmr H'sid. \$1.69
 HV Cndsr 500mmf 15KV. \$1.98
 JEFERS Cndsr 500mmf 20KV. \$1.98
 Ion Trap Dem. Magnet type. .89
 12 or 12 1/2" Tube Picture Frame Mask. .59

COMPLETE YOUR INVENTORY AT GREAT SAVINGS. TELL US YOUR NEEDS.

FULL WAVE BRIDGE RECTIFIERS

18VAC INPUT	14VDC OUTPUT
2 Amps. \$2.40	8 Amps. \$5.65
4 Amps. 3.85	12 Amps. 7.50
6 Amps. 5.49	24 Amps. 14.00

36VAC INPUT 28VDC OUTPUT

1.2 Amps. \$2.75	8 Amps. \$9.95
2 Amps. 3.75	12 Amps. 14.98
4 Amps. 7.00	24 Amps. 27.00

We specialize in Rectifiers & Power Supplies to your specifications. Immediate deliveries.

RHEOSTATS
 6-Ohm 25W standard brand Model LH. \$1.98
 15 Ohm 25W Ward Leonard w/Hub. 1.98
 100 Ohm 50W standard brand Model K. 2.25
 300 Ohm 200W standard brand Model F. 5.49
 500 Ohm 25W Servo Driver Shaft \$ 29.93; 3 for 20.00
 1500 Ohm 0000 Ohm 25W Screw Driver \$ 79; 3 for 20.00
 250 Ohm 25W Hardwick Handle \$1.39; 4 for. 5.00

SELSONS
 2J1G1 GE As Is. No Returns. 2 for \$0.49
 2J1H1 GE Selysins. 2 for 6.98
 2J1F3 GE 115V/40CY. Brand New. 2 for 6.98
 C78248 Synchro Trans. 115V/60CY. 2 for 18.00
 C78259 Synchro Diff. 115V/60CY. 2 for 18.00
 C69405 2 Svc Trans Type 1-1. Brand New. 27.50
 Synchro Repeater 115V/60CY. Type 11-4. Brand New @ \$13.95. 2 for 25.00

866A KIT and XFORMER
 2 Tubes, Sekts, xmr 115V 60cye Inpt. output 2.5Vct/10a/10KVins. \$6.98

DIODE PROBE TUBE!
 Unexcelled for NO-LOSS UHF Testing. Ultra-Sensitive Sub-Miniature—Envelope App. 1 1/4"x3/8". Element & Probe at Tip. Low Pwr. Htr. BRAND NEW w. Data. \$1.98; 2 for. 2.5c; 5 for \$1.98
 \$5 Min. 25% Dep. F.O.B. NYC. Prices Subject to Change.

Dept. IRE, 6 Church Street
 New York 6, N. Y., U. S. A.
 Cor. Church & Liberty Sts.
 Room 200. Phone Worth 2-7230

ADVERTISING INDEX

Adelman, Nat	124
Acro Tower	137
Allied Radio Corp.	15, 122
Almo Radio	96
American Corp.	175
Amperite Company, Inc.	159
Amplifier Corporation of America	17
Anchor Radio	175
Astafik Corporation	20
Atlas Sound Corp.	150
Audal Publishers	127
Barry Electronics Corp.	162
Belden Mfg. Co.	18
Bell Telephone Labs.	131
Benson Radio	148
Boyer-Roche Book Co.	163
Brook Electronics, Inc.	93
Brooks Radio & Television Corp.	156
Buchan, Richard J.	141
Burstein-Appelbe Co.	140
Candler System Co.	9
Central Radio Engineering Institute	150
Certified Television Labs.	158
Cisair, H. G.	158
Cleveland Radio Electronics	130
Columbia Electronics Sales	132
Commercial Trades Institute	142
Communications Equipment Co.	129
Concord Radio Corp.	97, 153
Coyne Electrical & TV Radio School	159
Davis Electronics	19
DeForest Training Institute	154
Dow Radio, Inc.	154
DuMont Labs., Inc. Allen B.	Inside Front Cover
Eastern Radio	61
Electro Sales	150
Electro-Voice, Inc. Co. Inc.	88
Electronic Instrument Co. Inc.	24
Electronic Measurements Corp.	161
Electronic Specialty Supply Co.	150
Feiler Engineering Co.	152
General Electric Distributing Co.	127
General Test Equipment	157
Gensler, B. N.	157
Good, Inc.	130
Gonset Company	127
Gould Green	156
Grylock Electronic Supply Corp.	130
Hawley Laboratories	131
Heath Company	107, 108, 109, 110, 111, 112, 113, 114
Hudson Specialties	87
Hytron Radio & Electronics Co.	118
Indiana Steel Products Co.	87
Indiana Technical College	146
International Telegraph Company	131
JFD Manufacturing Co., Inc.	13, 152
Jensen Manufacturing Co.	106
Lafayette Radio	125
La Pointe-Plasticmold Corp.	91
Leotone Radio Co.	141
Mallory & Co., Inc. P. R.	Inside Back Cover
McGraw-Hill Book Co.	163
Merit Transformer Corp.	142
Metropolitan Electronics & Instrument Co.	151
Midwest Radio & Television Corp.	115
Miles Reproducer Co., Inc.	161
Miller Company, J. W.	144
Milwaukee School of Engineering	141
Mosley Electronics	142
Moss Electronics	117
National Company, Inc.	102
National Electronics	128
National Plans Company	3, 4
National Radio Institute	3, 4
National Schools of Electronics	22, 23
National Video Corp.	142
Niagara Radio Supply Corp.	142
Oak Electronics	139
Oak Ridge Products	139
Omrite Manufacturing Co.	104
Oxford Electric Corp.	118
Opportunity Adults	136
Perfection Electric Co.	154
Permutex Corporation	154
Phoenix Electric, Inc.	152
Pickering & Company	140
Platt Electronics	152
Poly-Tech	133
Precision Development Corp.	123
Precision Apparatus Co., Inc.	123
Prentiss-Hall, Inc.	84
Pres-Probe Co.	130
Progressive Electronics Co.	21
RCA Institutes, Inc.	159
RCA Victor Division (Radio Corporation of America)	Back Cover
Radelco Manufacturing Corp.	75
Radiant Corporation	136
Radio Apparatus Corp.	136
Radio City Products	157
Radio Corporation of America	128
Radio Dealers Supply	134
Radio Merchandise Sales, Inc.	95
Radio Receptor Co., Inc.	95

RADIO SCHOOL DIRECTORY

(Page 160)

Berkeley & Associates, Edmund C.	163
Commercial Radio Institute	163
Hollywood Technical Institute	163
Indiana Technical College	163
Martin School, Don	163
RCA Institutes, Inc.	163
Streamlined Self-Study Courses	163
Tri-State College	163
Valparaiso Technical Institute	163
YMCA Trade & Tech. Schools	163
Ram Electronics Sales Co.	101
Rauland Corporation	138
Ray Company	138
Raytheon Manufacturing Co.	95
Regency Div. (I.D.E.A., Inc.)	164
Relay Sales	164
Rider, John F., Publisher Inc.	90, 124, 160
Rose Company	144
Sams & Co., Inc., Howard W.	105, 127
Simpson Electric Co.	120
Snyder Manufacturing Co.	120
Sprague Products Co.	16
Sprayberry Academy of Radio	156
Stark-Burn Radio & Electronics Corp.	147
Steve-EI Electronics Corp.	147
Superior Instrument Co.	83
Supreme Publication	133
Supreme Radio & Television Co.	140
Sutton's Wholesale Electronics, Bill	151
Sylvania Electric Products, Inc.	92, 93
Tab	128
Tallen Co., Inc.	162
Tarzan, Inc., Sarkes	138
Tech-Master Products Co.	138
Technifax	148
Technical Appliance Co.	129
Tel-A-Ray Electronics, Inc.	103
Telematic Industries, Inc.	84
Television Communications Institute	143
Telrex, Incorporated	123
Transvision, Inc.	146
Triplet Electrical Instrument Co.	89
Tung-Sol Electric Co.	10
Turkey Company	139
United Catalog Publishers	11
Use-D-X	81
Ward Products	81
Weller Electric Corp.	126
Wells & Winegard	117
Wesco, Inc.	153
Wholesale Radio Parts Co., Inc.	84
Wincharger Corporation	151
Workshop Associates	160

QUALITY, TESTED TUBES

New and guaranteed in stock now; many others not listed—complete line of receiving tubes at low prices. Submit your requirements on any types for our quotation. Call us on WESTINGHOUSE & other types of Industrial & Special-purpose Tubes.

0A2	\$1.00	6BQ6GT	\$.90	12AV6	\$.55
0B2	1.10	6C4	.65	12AY7	3.00
0Z4A	.65	6CB8	.70	12BA6	.70
1B3GT	1.05	6CB6	.85	12BA7	.90
1N21	.85	6CD6G	1.75	12BE6	.70
1N21B	3.50	6F8G	.98	12BH7	1.00
1N23	1.45	6H6	.75	12SH4	.95
1N23A	2.50	6J5GT	.75	12SL7	.75
1N23B	3.75	6J6	1.10	12SL7	.75
1N34	.68	6J7	.95	12SQ7	.75
1R5	.65	6K6GT	.79	25B06GT	.98
1U4	.65	6K7	.75	25L6GT	.65
2B7	.75	6K8	.80	35C5	.60
3A4	.85	6L7	.98	35Z5GT	.55
3A5	1.10	6R8	.90	50C5	.60
3D6	.50	6SA7	.75	50L6GT	.60
3Q4	.55	6SF5	.85	80	.60
354	.90	6SG7	.98	304TH	11.50
5F7	1.95	6SH7	.70	304TH	11.50
5U4G	.59	6SK7GT	.75	717A	.98
5V4G	1.05	6SL7GT	.75	807	1.65
5X4G	.85	6SN7GT	.70	813	7.75
5Z3	.95	6S07	.75	866A	1.50
6AC7	.98	6T8	1.25	872A	2.25
6AG5	.85	6U4GT	.80	955	.45
6AH6	1.50	6V6GT	.60	956	.37
6AJ5	1.95	6V6M	1.50	1616	.75
6AK5	1.25	6W4GT	.50	1624	1.40
6AK6	1.30	6X4	.45	1625	.40
6AL5	.55	6X5GT	.45	1626	.40
6AU6	.65	6Y6G	.75	1629	.30
6AV6	.55	7H7	.80	5686	3.95
6B4G	1.25	12A6	.75	5910	.75
6BA6	.70	12C8	.85	9004	.44
6BE6	.70	12AT7	1.00	9005	1.50
6BG6G	1.20	12AU7	.75	9106	.44
				9106	1.25

• Carter, 6 V. Dynamotrons, in original cartons. Brand new—400 VDC @ 375 ma. List Price \$71.40—Special \$28.00

• TV "CHEATER" CORD—6 Ft. Complete—U.L. App'd. Reg. Net 59¢—Special 39¢

• ART-I—75 Meter Deluxe Mobile Am XMTR—Complete—NEW @ \$25.00

• ART-II Complete, Ultra Compact XMTR-RCVR—Write For Details

• SPECO SIGNAL—TRACER KIT
 • Complete with 3 tubes, steel case, all parts, cabinet, easy instructions, less batteries. only \$9.45

• 300 ohm quality twinlead—Pure Poly.—55 ga.—#20 wire—all tinned strands—1,000 ft. roll \$20.00

• RG 59/U—73 OHM. CO-AX. CABLE... \$55.00/M FT.

ELECTROLYTIC CONDENSERS
 All Guaranteed Fresh Stock

lots of 100	lots of 1000
20X20-150 V. \$0.39	\$3.70 \$34.95
40X40-150 V.45	4.30 39.95
50X30-150 V.45	4.30 39.95
50X30-150 V.49	4.50 41.95
40X40X20-150 V.69	6.70 59.95
50X30X20-150 V.69	6.70 59.95
50X50-150 V.79	7.70 69.95
(200-25 V.)39	3.69 32.50

• PM SPEAKERS—NEW, BOXED
 3" 1.60 Imported English Hi-Fi Speakers
 4" 1.65 5" 2.15
 5" 1.75 6" 3.50
 6" 1.89 8" 4.50
 12" 5.95 (RCA) 10" 5.50

• NEW, SELENIUM RECTIFIERS, TRANSFORMERS
 Pri: 110 V, 60 cycle In. 4 amps. \$7.75
 Sec: 18, 24, and 36 volts. 12 amps. 14.75
 24 amps. 33.75
 Designed for bridge or center-tap use. These transformers are not surplus, but are made to our specs by a leading m'fr.
 • 110V. pri.—36V. 50 amp secondary XFMR. Special. \$39.95

• 110 V. Selenium Rectifier Specials
 1/2 wave 65 ma. only 59¢ ea.
 1/2 wave 450 ma. only \$1.65 ea.

SELENIUM RECTIFIERS—FULL-WAVE BRIDGE TYPES

Current (cont.)	18/14 Volts	36/28 Volts	54/40 Volts	54/40 Volts
1 Amp.	\$1.98	\$1.98	\$1.98	\$1.98
2 Amps.	\$2.40	\$3.75	\$6.95	\$10.50
4 Amps.	3.85	7.00	9.00	
6 Amps.	5.65	9.00		
8 Amps.	6.95	10.95		48.00
12 Amps.	7.50	14.00		58.00
20 Amps.	13.25	20.00		
24 Amps.	14.00	26.00		
30 Amps.	19.00	30.00		
36 Amps.	25.50	35.00		

All our rectifiers are new & guaranteed one year. We manufacture special types of rectifiers and rectifier supplies to your specs. FAST DELIVERY.

BARRY ELECTRONICS CORP.

136 Liberty Street, N. Y. 6, N. Y. Rector 2-2563
 Terms: 25% with order, balance C. O. D. —Send a few cents for postage—All merchandise guaranteed. F. O. B. N. Y. C.

NOW! BECOME EXPERT AT RADIO-TELEVISION IN 4 EASY STEPS!



Complete Self-Training Course in RADIO and TV by Famous Experts—Takes You BY SIMPLE STEPS From Basic Theory to Problems of Repair, Installation, Color TV, etc.

NOW you can do ANY Radio-TV installation, service, or repair job like an expert; operate field-testing equipment; understand problems of TV, FM-AM transmission, etc. Step into a good-paying job—or start your own service business. Train yourself AT HOME . . . IN SPARE TIME . . . with the McGraw-Hill Basic Course in Radio and TV.

2296 Pages—1611 Illustrations

The men who wrote this complete 4-volume course are among the outstanding radio and TV instructors in America today. Every detail is clearly explained in over TWO THOUSAND PAGES of step-by-step instruction and over SIXTEEN HUNDRED "how-to-do-it" illustrations, cross-section diagrams, etc. The review questions and answers "nail down" everything you learn. At a glance "trouble-shooting" charts show how to diagnose instantly any radio or TV breakdown . . . and how to repair it expertly and quickly.

The course will pay for itself many times over. It can qualify a beginner for FCC's 1st-Class License test; gives an experienced technician more confidence and skill.

SEND NO MONEY

Mail coupon below to examine complete four-volume course FREE for 10 days. No obligation. Or you may examine individual books FREE for 10 days by checking the proper boxes in coupon.

PARTIAL CONTENTS ESSENTIALS OF RADIO.

300 pages, 433 illus. Circuit Analysis • Vacuum Tubes • Circuits • Detector • Amplifier • Tube Oscillator • Power Supply • Transmitting, Receiving • Etc.

ELEMENTS OF RADIO SERVICING. 475 pages, 375 illus. Multimeters • AC Power Supply • Speakers • Antennas • Auto Radios • Push-Pull Output Stages

BASIC TELEVISION. 592 pages, 415 illus. Scanning • Synchronizing • Video Signal • Brightness Control • DC Retention • Picture • FM Alignment • Picture Tubes • VHF and UHF transmission • Reception

TELEVISION SERVICING. 429 pages, 388 illus. Antennas • Transmission Lines • Test-pattern and Picture Analysis • Localizing Reception Troubles • Interference Remedies • Deflection Circuits

AND MUCH MORE!

FREE 10-DAY TRIAL COUPON

McGraw-Hill Book Co., Inc., Dept. RE-1-52, 327 West 41st St., New York 18, N. Y.

Send me for 10 day free examination the Basic Course in Radio and TV, 4 Vols. (Regular retail price is \$23.75; Special Course Price only \$19.95 in easy installments.) If not satisfied with Course, I will return it, pay nothing. Otherwise, I'll send \$1.95 plus delivery then and only \$3.00 in monthly installments.

If you wish to examine any of these books individually, check below the ones you wish us to send you for 10 Days' FREE EXAMINATION:

Essentials of Radio, \$6.50
 Elements of Radio Servicing, \$4.75
 Basic Television, \$6.50
 Television Servicing, \$6.00

For any book I keep, I'll send \$2.00 plus delivery in 10 days, balance in easy monthly installments.

Name.....
 Address.....
 City..... Zone..... State.....
 Position.....
 Company..... RE-1-52

WE PAY FOR DELIVERY if you send first payment of \$1.95 when ordering Course or full price when ordering individual books (prices above). Same return privilege.

ELEMENTS OF TELEVISION SYSTEMS, by George E. Anner. Published by Prentice-Hall, Inc., 70 Fifth Ave., New York, N. Y. 5 1/2 x 8 1/2 inches. 804 pages. Price \$10.35.

This volume packs much TV information for the service technician, transmitter operator, and hobbyist. Scanning, camera tubes, synchronization, and stagger tuning are some of the important subjects described in detail. There are also chapters on televising of motion pictures, antennas, color TV, etc.

Much of the treatment is nonmathematical. However, many equations, charts, and diagrams are provided. Practical and detailed numerical examples show how to design multivibrators, compensated video amplifiers, and other circuits.

The basic information given here will remain useful for years to come. Nevertheless, the rapid changes in TV are apparent. Schematics are supplied for several 7, 10, and 12-inch kinescope receivers. There is nothing on the modern high-voltage supplies or the larger size kinescopes.

MATERIALS TECHNOLOGY FOR ELECTRON TUBES, by Walter H. Kohl. Published by Rheinhold Publishing Corporation, 330 W. 42nd Street, New York, N. Y. 6 1/4 x 9 1/4 inches, 493 pages. Price \$10.00.

Vacuum tube designers and manufacturers, or electronic technicians are provided with a wealth of data and techniques in this book which endeavors to include in one text most of the pertinent research work in high vacuum construction work. Data on the characteristics of nickel, tungsten, molybdenum, tantalum, copper, ceramics, and glass used in the art are presented. The coverage on different glasses is unusually comprehensive.

A broad index of authors and reviewers permit the worker seeking specialized data on processes and applications to pinpoint additional search. A review of atomic theory, classification of crystals, and an outline of the salient factors of the phase rule, high vacuum technique, and thermionic emission provide a theoretical basis for the mechanical and chemical processes described in the text. Soldering, brazing and advanced welding techniques used with the many alloys listed are presented at length. Many graphs and illustrations are presented with each chapter and reinforce the text content. A large index allows quick reference to any of the varied topics discussed.

RESPONSE OF PHYSICAL SYSTEMS, by John D. Trimmer. Published by John Wiley & Sons, Inc., 440 Fourth Ave., New York 16, N. Y. 5 3/8 x 8 3/8 inches, 268 pages. Price \$5.00.

This book offers aid to workers in such fields as physics, sociology, biology, mechanics, etc., by applying cybernetic concepts to problems in instrumentation. A working knowledge of calculus and differential equations is needed for successful application of mathematics to physical systems.

—end—

THE BROOK

High Quality
AUDIO AMPLIFIER
ALL TRIODES

Distortion and intermodulation extremely low
 Wide frequency range, flat from 20 to 20,000 cycles within .5 db
 Attractive remote-control pre-amplifier
 Compensation for various inputs; Phono, Tuner, Television or Microphone
 Exclusive BROOK circuits and transformers

Yes. All These Features
 but primarily
LISTENING PERFORMANCE
 heretofore not achieved

Write for free Technical Bulletin, detailed Distortion Analysis & booklet "Better Listening". Dept. EA-2

BROOK ELECTRONICS, INC.
 34 DeHART PLACE, ELIZABETH 2, N.J.

14 Ram Parts

Exact Replacement:
 You need only 14 Ram parts to cover over 94% of TV sets now in the country—because Ram specifications are identical to those of the original parts!

Flybacks

Performance-Proved:
 Ram makes transformers, yokes, and coils for such leading TV set manufacturers as DuMont, CBS-Columbia, Olympic, Tele-Tone, Majestic, Fada, Silverstone, Starrrett, Regal, DeWald, etc.—surpasses their every laboratory, production and field test!

Yokes

TV replacement

Lowest-Priced:
 for highest profits for you.


width coils
 linearly coils

SIMPLIFY your TV parts stock with Ram's complete, universal line! Ask your distributor for Ram components—today! Write NOW for FREE latest TV Replacement & Conversion Guide, #E-1.

Ram ELECTRONICS SALES CO.
 51 South Buckhout St.
 Irvington-on-Hudson, N. Y.
 IRVINGTON 9-5700

TEST-PATTERN TESTED COMPONENTS FOR TV

TELEPHONE TYPE RELAYS

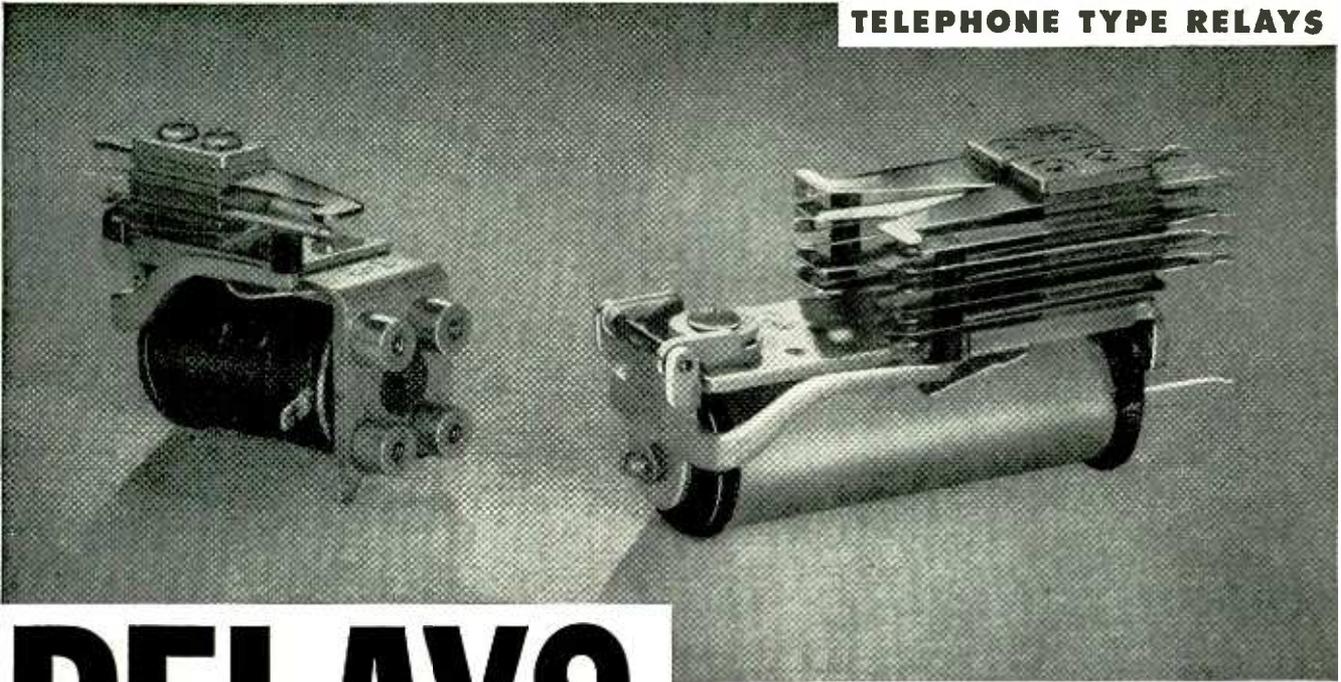

RELAYS

This list represents only a small part of more than a million relays in our stock—one of the world's largest. All relays are standard, brand new in original packing, and fully guaranteed by Relay Sales. Send us your relay requirements. If the items are in stock we can make immediate delivery at substantial savings in cost to you.

STANDARD TELEPHONE RELAYS

STK. NO.	VOLTAGE	OHMAGE	CONTACTS	UNIT PRICE
R-806	115 VAC	900	1A	\$2.05
R-161	6 VDC	10	2B&1A	1.10
R-873	6 VDC	12	3C-3A MICALEX	3.00
R-305	12 VDC	50	2A Split Cerm.	1.35
R-360	24 VDC	200	1C	1.50
R-484	24 VDC	200	2A, 1C	1.35
R-337	24/48 VDC	1200	1A, 2B Split	2.65
R-101	24 VDC	1300	2A	2.50
R-868	30/162 VDC	3300	1C	1.90
R-365	52/162 VDC	3300	4C	3.95
R-518	85/125 VDC	6500	1C	3.60
R-918	52/228 VDC	6500	1C	3.60
R-852	52/228 VDC	6500	1C, 1A	3.00
R-341	75/228 VDC	6500	4C @ 4 Amps	3.65
R-633	180/350 VDC	10,000	1C @ 5 Amps	2.90
R-344	72/300 VDC	11,300	3A, 1B	2.45
R-332	100/350 VDC	40,000	2A	3.50
R-664	110 VAC	...	2B&1A/OCT.SOCKET	2.45
R-667	6 VDC	.75	1B/10AMP. 1A/3AMP.	1.45
R-632	6 VDC	12	5A&1C	3.25
R-154	6/12 VDC	200	1A	1.50
R-517	12 VDC	250	2A	1.50
R-116	85 VDC	3000	1B	3.05
R-631	100/125 VDC	3300	2A	1.90
R-545	110/250 VDC	7000	1C	2.40
R-124	300 VDC	12,000	1A	1.55
R-511	24 VDC	200	W/MICRO N.O.	3.05
R-160	6 VDC	12	3C&3A	3.00
R-851	52/228 VDC	6500	1C, 1A	3.00
R-591	6 VDC	40	1B&1C	1.35
R-155	12 VDC	100	4A&4B	1.45
R-520	200/300 VDC	14,000	2C	3.45
R-159	6 VDC	50	2A	1.35
R-158	6 VDC	50	4A Cerm.	1.85
R-381	6/8 VDC	100	1A Split	2.50
R-382	6/12 VDC	200	1B Split	2.50
R-153	12 VDC	200	1C&1A	1.55
R-304	12 VDC	200	4A Split Cerm.	2.50
R-383	6/12 VDC	500	1A Split	2.50
R-385	6/12 VDC	500	1B Split	2.50
R-384	6/12 VDC	500	3A Split	3.00
R-576	12 VDC	200	2A	2.50
R-316	24 VDC	200	1C	1.50

SHORT TELEPHONE RELAYS

STK. NO.	VOLTAGE	OHMAGE	CONTACTS	UNIT PRICE
R-635	12 VDC	100	1C&1B	\$1.35
R-308	12 VDC	100	2C @ 4 Amps	1.85
R-343	12 VDC	100	1C	2.00
R-826	12 VDC	150	2C, 1B	1.55
R-770	24 VDC	150	1A/10 Amps	1.45
R-368	8/12 VDC	200	1B	1.40
R-771	24 VDC	200	1A/10 Amps	1.45
R-603	18/24 VDC	400	2A	1.55
R-575	24 VDC	500	2C	2.40
R-764	48 VDC	1000	1C&2A	2.00
R-417	5.5 ma	5800	2C	2.50
R-563	60/120 VDC	7500	1A	2/3.10
R-213	5/8 VAC 60 Cy.	2A	2.50
R-801	115 VAC	NONE	1.45
R-589	12 VDC	125	2A	1.30
R-113	12 VDC	150	4A	1.55
R-689	12/24 VDC	255	1C	1.55
R-799	24 VDC	500	NONE	1.00
R-115	24 VDC	500	1C	1.70
R-110	24/32 VDC	3500	1C	2/3.45
R-121	150 VDC	5000	2A&1C	2.05
R-122	150 VDC	5000	2C/Octal Base	2.50
R-634	150/250 VDC	6000	1A&1B	2.45
R-369	8/12 VDC	150	2A, 2B	1.60
R-908	6 VDC	15	4A @ 4 Amps	1.50
R-800	12 VDC	150	2C&1A	1.55
R-537	12/24 VDC	150	2C&1B	2.00
R-750	24 VDC	400	1A	1.60
R-367	10/16 VDC	195	2C	2.50
R-335	20/30 VDC	700	2A, 1C	2.00
R-366	30/120 VDC	4850	1C	2.50

OTHER RELAY TYPES IN STOCK

- Keying Relays
- Voltage Regulators
- Rotary Relays
- Differential Relays
- Contactors
- Sealed Relays
- Midget Relays
- Special Relays



Manufacturers and Distributors:
Write for the new Relay Sales Catalog.

Telephone
Seeley 8-4146

833 W. CHICAGO AVE., DEPT. Y, CHICAGO 22, ILL.



Preferred by Servicemen everywhere . . .

MALLORY VIBRATORS

There are three big reasons why servicemen prefer Mallory vibrators over all other brands combined. They count on Mallory vibrators for long dependable service because they give . . .

- 1— Slow contact impact for minimum wear
- 2— High contact pressure for low resistance
- 3— Fast contact break for reduced arcing, pitting

That combination—available only from Mallory, with its patented, tuned mechanism—means real performance for you and your customers. That's why more Mallory vibrators are used as original equipment than all other makes combined. Put these features to work for you. When you order vibrators . . .



Service 47 Radio Makes
With ONE of Mallory's
Special Vibrator Deals

Ask your distributor about these Mallory specials. They help keep your inventory down. You can service 47 radio makes with the 6 Mallory vibrators in one of these deals. And you get a handy parts cabinet at no additional cost when you buy at your regular discount price. Call your distributor today for details.

Make Sure! Make it Mallory!

P. R. MALLORY & CO. Inc
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
• RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

THE QUALITY OF RCA TUBES IS UNQUESTIONED



Extra Performance

as a matter of course...with RCA tubes


The RCA-developed "A" frame construction—used in 6 of the metal-type r-f amplifiers—is one of the many improvements that contribute to the *extra* performance of RCA tubes.

The "A" frame—shown in red—consists of a top member, two vertical members, and a bottom cross member. The ribbed uprights are welded to the cross member... the feet of the uprights are welded to the grounded metal header. In effect a truss, this rigid "A" frame acts as the supporting member for the tube elements. Its increased resistance to vibration reduces the possibility of electrode displacement due to wear on the holes in the mica spacers... and thereby

plays an important role in reducing microphonics and maintaining uniform tube characteristics.

In addition to imparting rigidity to the tube elements, the top and bottom members of the "A" frame serve as shields. The two ears on the top member add to its effectiveness in reducing grid-to-plate capacitance... the tab on the lower member—which extends down to the stem—provides additional shielding between grid and plate leads.

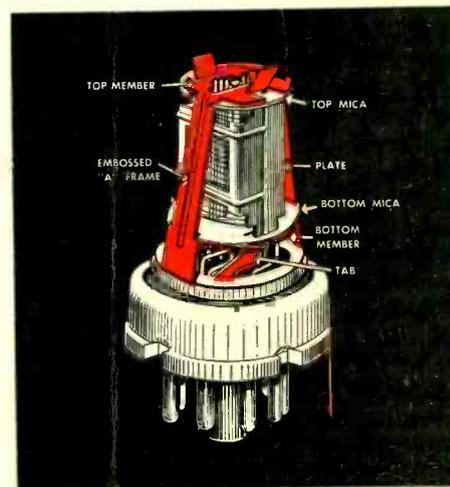The *extra* performance built into RCA tubes accounts for their high quality, long life, and dependability. They cost no more. Why not use them for your daily tube requirements?



Keep informed—keep in touch with your RCA Tube Distributor



RADIO CORPORATION of AMERICA
ELECTRON TUBES
HARRISON, N. J.