

PROJECTS – Binary counter & experimental mini-tenna

60c ■ FEB. 1968

# Radio-Electronics

TELEVISION · SERVICING · HIGH FIDELITY

GERNSBACK  
PUBLICATION

## AUDIO

Build an Electronic Tremolo

How to Measure Reverberation

Audio Levels on Long Lines

## SERVICE

Solid State TV  
(see page 35)


Pulses & Circuits

Noise Limiters

## PLUS

Numbers

Labels

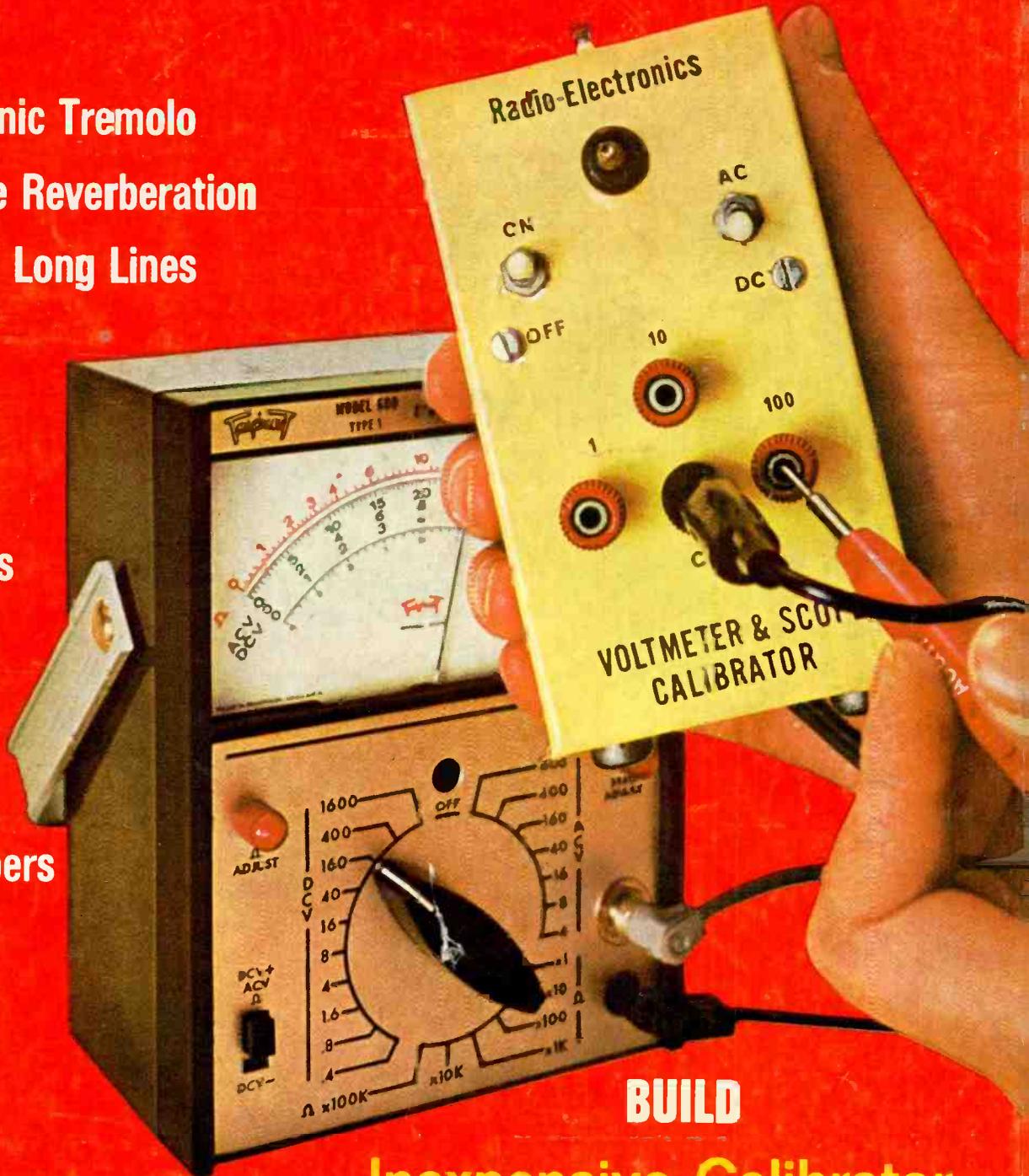


**BUILD**
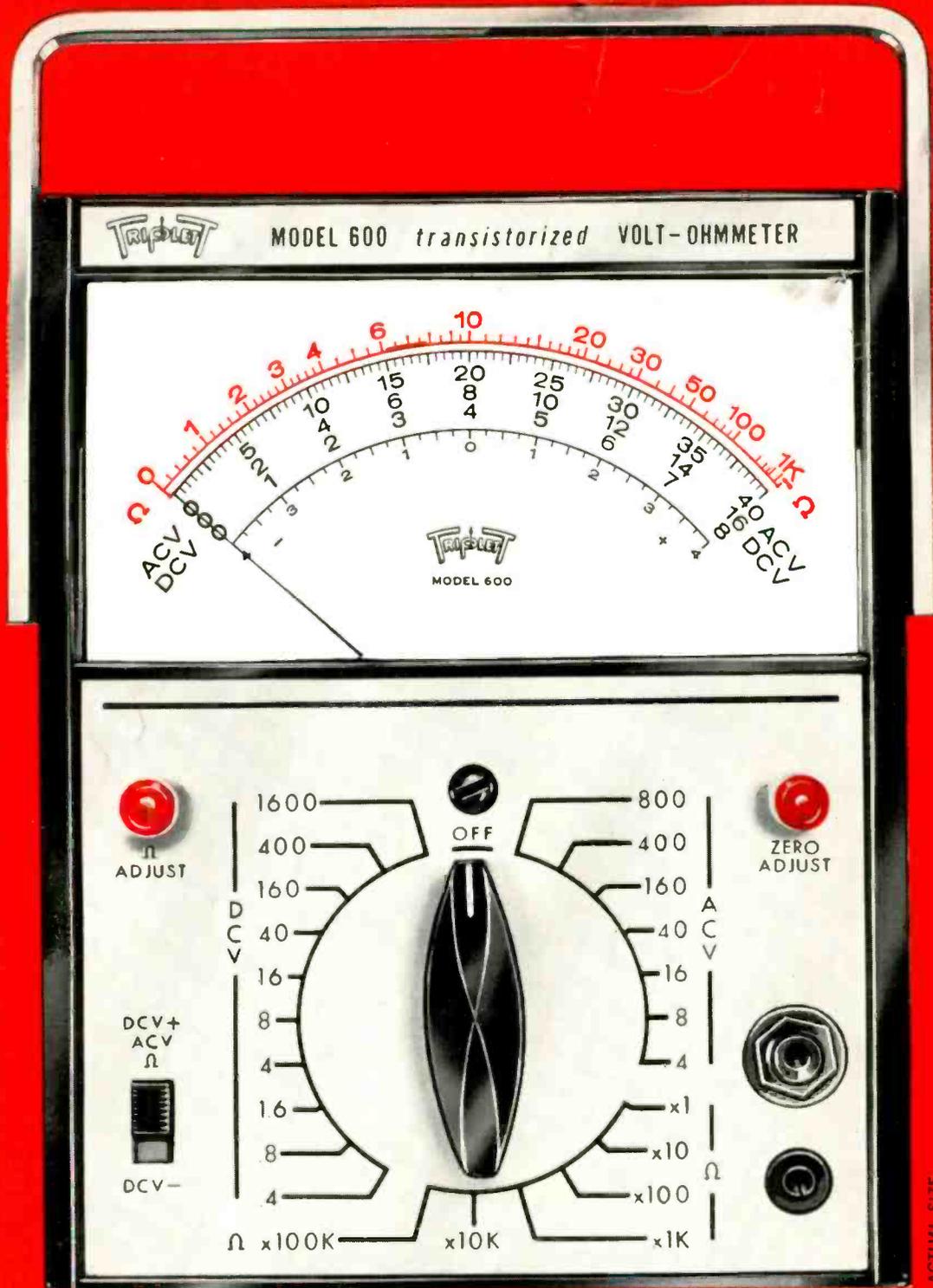
### Inexpensive Calibrator for Scope & Voltmeter

(see page 42)

A0768 5100768LU0220D0A52  
A L BALUKA  
220 DOWNING DR  
FLORISSANT MO 63031



ACTUAL SIZE

# NEW SOLID STATE VOLT-OHMMETER

1. F-E-T Circuitry—Battery Operated with 11 Megohm Input Impedance (Field Effect Transistor).
2. 400 DC MV range at 2.7 Megohm Impedance for Solid State circuit testing.
3. One Selector Switch with 23 ranges plus a Polarity Reversing Switch.




Model 600 on stand handle leather case \$14.70

Model 600 TVO  
(Transistorized Volt-Ohmmeter)

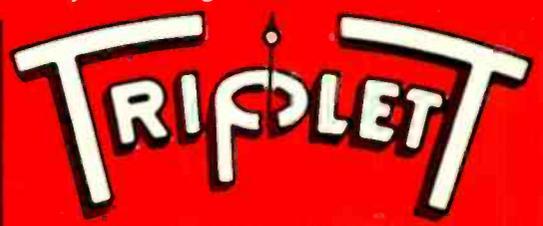**\$82.**

Suggested U.S.A. User Net  
Available Now At Your  
Local Distributor



ELECTRICAL INSTRUMENT COMPANY  
BLUFFTON, OHIO

# F.C.C. COMMERCIAL OPERATOR LICENSE

## Training

is part of the Grantham

## A. S. E. E.


### DEGREE CURRICULUM

In today's world of electronics employment, an FCC license is important — sometimes essential — but it's not enough! Without further education, you can't make it to the top. Get your FCC license without fail, but don't stop there. To prepare for the best jobs, continue your electronics education and get your Associate Degree in Electronics.

This is good common sense for those who want to make more money in electronics. It also makes sense to prepare for your FCC license with the School that gives degree credit for your license training — and with the School that can then take you from the FCC license level to the Degree level.

The first two semesters of the Grantham degree curriculum prepare you for the first class FCC license and radar endorsement. These two semesters, in addition to other parts of the Grantham

This booklet  
**FREE!**

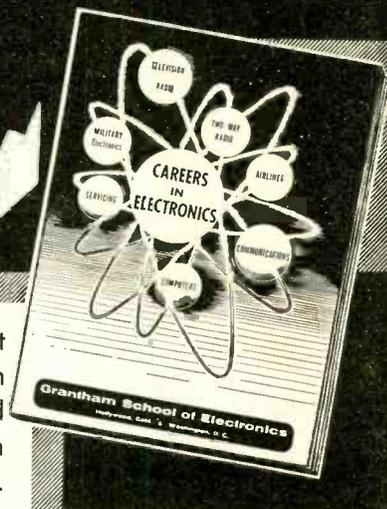

This free booklet explains what an FCC license and ASEE degree can do for your future.

degree curriculum, are available by correspondence\* at very reasonable tuition. *The ASEE Degree can be earned by correspondence with a minimum of one semester in residence.*

#### Accreditation, and G.I. Bill Approval

Grantham School of Electronics is *accredited* by the Accrediting Commission of the National Home Study Council, and is *approved* for both correspondence and resident training under the G.I. Bill. Mail the coupon, or simply write or telephone for your free copy of our Associate Degree Bulletin which gives complete details of our educational program.



## GRANTHAM School of Electronics



\*Semesters 1, 2, and 3 of the Grantham electronics curriculum are available *also in resident classes* at our Washington, D.C. school — at the address shown below.

• Established in 1951 •

### Grantham School of Electronics

1505 N. Western Ave.  
Hollywood, Calif. 90027

or

818 18th Street, N.W.  
Washington, D.C. 20006

Telephone:  
(213) 469-7878

Telephone:  
(202) 298-7460

**Grantham School of Electronics** RE-2-67  
1505 N. Western Ave., Hollywood, Calif. 90027


Please mail me your free catalog, which explains how Grantham training can prepare me for my FCC License and Associate Degree in electronics. I understand no salesman will call.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

# NEWS BRIEFS

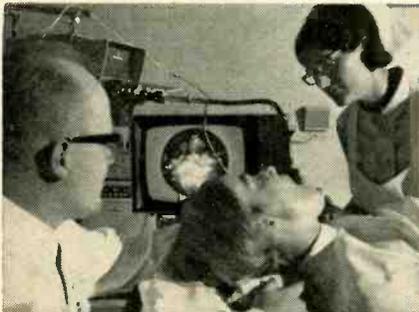

**LIVING STOMACH IN LIVING COLOR**—Flexible glass fiber-optics tube picks up optical image inside patient's stomach, transmits it to Siemens color TV camera. Physician watches monitor, makes accurate diagnoses.




**IMPROVED VIDEO TELEPHONE**—Currently under test is Bell Lab's new Picturephone for see-while-you-talk communication. System is scheduled for field tests between Pittsburgh and New York City in September.

## COMPUTER TO SPAN U.S.A.


Honeywell Inc. plans to install 40 terminal units next year at plants from Florida to California and Boston to Seattle that will be able to feed technical data on a cyclical time-sharing basis into three computers at the firm's Minneapolis headquarters. It will be able to handle 48 users simultaneously, when eight other remote terminals are installed later.

The effect of the new system


will be the same as installing a computer at each of the company's engineering locations coast to coast. Engineers will be able to enter their problems directly in any of three computer languages—Fortran IV, in an interpretive algebraic language, or in a special scientific language. The system uses three computers, teletype terminals, and two tape units and two disc packs capable of storing up to 14 million bits of information.

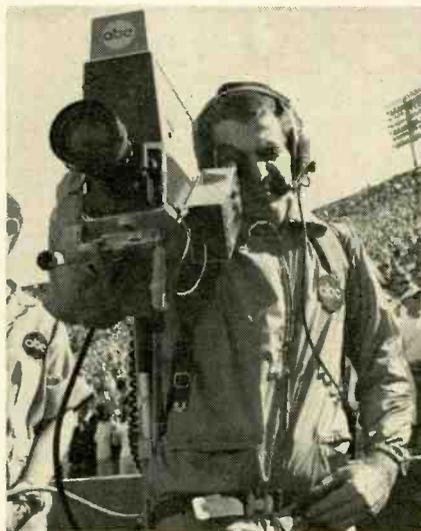

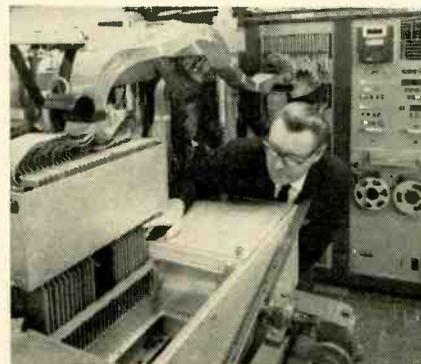**ONE-MAN COLOR TV CAMERA**—Weighing only 35 lbs, this color camera—developed by Ampex for ABC—offers closeup coverage of sports, conventions, news events.



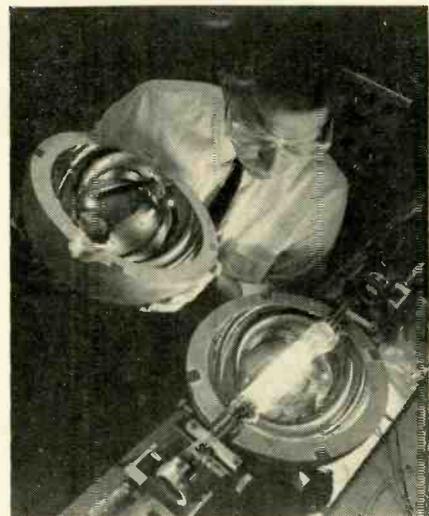**FAST WIRING CHECKER**—A man would need 10 years to verify by hand the wire connections in computerized defense equipment. Hughes Aircraft's FACT (Flexible Automatic Circuit Tester) tests connections of 10,000 wires in 30 minutes.



**BALL-OF-LIGHT LASER**—New kind of laser pump uses highly-polished bowl-like spherical mirrors to stimulate more efficient laser action. Pump was developed by Westinghouse Labs.



**LARGE-SCALE 3-D PHOTOS**—New RCA laser advance makes possible holograms of scenes up to 6 feet deep. System overcomes previous limit of inches-deep scene, may make 3-D window displays possible.

## SOLID-STATE SALES

US manufacturers' sales of transistors during the first 9 months of 1967 declined 21%, according to EIA. This figure applies to total transistor sales. The surprise was the field-effect transistor. FET sales during the same period were up 23%. **R-E**

RADIO-ELECTRONICS

# Radio-Electronics

February 1968 • Over 55 Years of Electronics Publishing

## CONSTRUCTION PROJECTS

- Build a Mini-Tenna** ..... **32** James A. Gupton, Jr.  
*An experiment and a challenge*
- Build AC/DC Calibrator for Scope and Voltmeter** ..... **42** Peter E. Sutheim  
*1% accuracy with a "hot" neon lamp*
- Binary Count Demonstrator** ..... **62** Russel Ayers  
*One plus one equals three*

## AUDIO

- How to Measure Reverberation Time** ..... **50** Don Davis  
*Be an echo expert*
- Build an Electronic Tremolo** ..... **53** R. H. Keenan  
*Step up to the big sound*
- Audio Levels on Long Communications Lines** ..... **60** Eugene Austin  
*Telephone techniques tame two-way radio*

## SERVICING


- In the Shop . . . With Jack** ..... **14** Jack Darr  
*Service Clinic*
- Update Your Solid-State TV Servicing** ..... **35** Matthew Mandl  
*Practical info in a palatable portion*
- Ultrasonics: New Tool for Industry** ..... **58** Pat McDonald  
*Your chance to clean up*
- The Technician Who Knew Too Much** ..... **68** Wayne Lemons  
*Who condemned the CRT?*

## GENERAL ELECTRONICS


- Pulses and Pulse Circuits You Should Know** ..... **38** Robert G. Middleton  
*No respectable TV set is without them*
- Quiet-Noise Limiters at Work** ..... **44** John D. Lenk  
*Down with QRM*
- The Useful Decibel** ..... **54** Eric Leslie  
*Look . . . no logarithms*
- Imaginary Numbers Are a Cinch** ..... **56** Norman H. Crowhurst  
*Part 3 . . . filter design*
- Equipment Reports: Dynamic Instrument** . . . **70**  
    **Plug 'N Play PNP-10** . . . . . **86**  
    **Shure M68** . . . . . **86**  
    **Microphone Mixer**

## DEPARTMENTS


- |                              |    |                          |    |                       |    |
|------------------------------|----|--------------------------|----|-----------------------|----|
| Correspondence               | 4  | New Literature           | 84 | Noteworthy Circuits   | 96 |
| Miss-Q                       | 83 | New Products             | 77 | Technotes             | 92 |
| New Audio Equipment          | 79 | New Tools                | 80 | Try This One          | 97 |
| New Communications Equipment | 81 | New Tubes for Television | 94 | Reader's Service Page | 74 |
|                              |    | News Briefs              | 2  |                       |    |

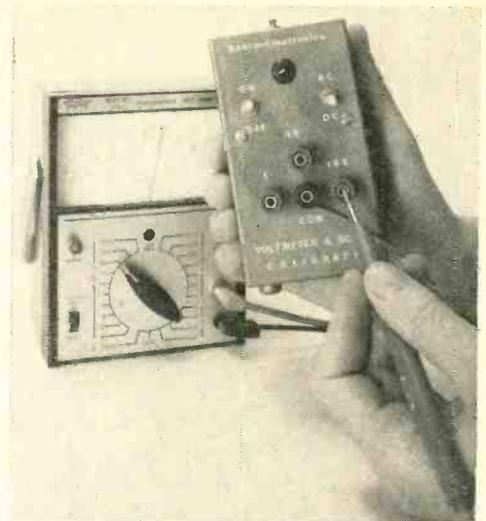

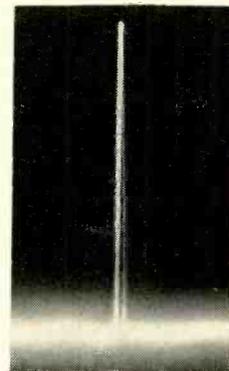Handy voltmeter and scope calibrator, covers both ac and dc, with calibrating voltages of 1, 10 and 100. Uses only a handful of parts. Meter shown is a Triplet 600 transistORIZED volt, ohmmeter. See page 42



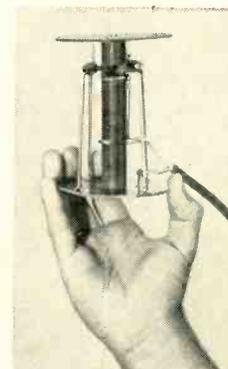Pulses are used everywhere in electronics. How much do you know about them? Find the answers and enlarge your electronics knowledge. See page 38



Transistors become part of the antenna elements in this experimental device you can build. It's tiny and it's broadband. How well does it work? See page 32

RADIO-ELECTRONICS, FEBRUARY 1968, Volume XXXIX, No. 2.  
Published monthly by Gernsback Publications, Inc., at Ferry St., Concord, N. H. 03302.  
Editorial, Advertising, and Executive offices: 154 West 14th Street, New York, N. Y. 10011. Subscription Service: Boulder, Colo. 80302.  
Second-class postage paid at Concord, N. H. Printed in U.S.A. One-year subscription rate: U. S. and possessions, Canada, \$5.  
Pan-American countries, \$6. Other countries, \$6.50. Single copies: 60c. ©1968, by Gernsback Publications, Inc. All rights reserved.  
POSTMASTER: Notices of undelivered copies (Form 3579) to Boulder, Colo. 80302.



Member,  
Institute of High Fidelity.  
Radio-Electronics is indexed in  
*Applied Science & Technology Index* (formerly *Industrial Arts Index*)

## SOME SHOP OWNERS DO MORE BUSINESS THAN OTHERS BY DOING BASIC THINGS LIKE THESE:



1 Reading what's new in leading technical magazines.



2 Keeping their trucks ready to roll at a moment's notice.



3 Arranging to have their phones answered promptly.



4 Making sure their caddies are organized and properly stocked.



5 Keeping accurate track of their time on each job.



6 Smiling . . . often . . . both on and off the job.



DIFILM® BLACK BEAUTY® . . .  
Ultimate in molded tubulars

DIFILM® ORANGE DROP® . . .  
The world's finest radial-lead capacitor

### 7 INSTALLING SPRAGUE DIFILM® CAPACITORS

These two great Sprague capacitors are expressly made for men who are in the TV service business to do business . . . as it should be done. Both feature the ultimate in tubular capacitor construction to keep you out of call-back trouble:

- Dual dielectric . . . combine best properties of both polyester film and special capacitor tissue.
- Impregnated with HCX® to provide rock-hard capacitor section.
- Because impregnant is solid, there's no oil to leak, no wax to drip.
- Designed for 105°C (220°F) operation without voltage derating.

#### DIFILM® ORANGE DROP® Dipped Tubular Capacitors

A "must" for applications where only radial-lead capacitors will fit. Perfect replacements for dipped capacitors used in most leading TV sets. No other dipped tubular capacitors can match them. Double-dipped in rugged epoxy resin for positive protection against extreme heat and humidity.

#### DIFILM® BLACK BEAUTY® Molded Tubular Capacitors

World's most humidity-resistant molded capacitors. Feature tough, protective outer case of non-flammable molded phenolic . . . which cannot be damaged in handling or installation. Will withstand the hottest temperatures of any radio or TV set . . . even in the hottest, most humid climates.

For complete listings, ask your Sprague distributor for Catalog C-617, or write to Sprague Products Company, 81 Marshall Street, North Adams, Massachusetts 01247.

**DON'T FORGET TO ASK YOUR CUSTOMERS  
"WHAT ELSE NEEDS FIXING?"**



#### HIGHER FI?

You really do have a first-class magazine! This has impressed me particularly at this moment, as I have had to go through quite a few back numbers. Somehow you manage to couple the practical with theory, or future developments in such a way that it not only makes for good reading, but keeps one up to date in the field. In this line: How about a thorough treatment of the operational amplifier, either IC or not? I suppose I cheat in looking to you for simple explanations to give to other people. Not that I want to enter any audio controversy with Peter Sutheim's article, "The Wider the Band the Higher the Fi?" (October 1967) but he appears to have overlooked the fact that while he knows all about the bandwidth of his amplifiers, he does not give as much information about his speakers, the cartridge or the recording equipment. After all, if only 15 kHz are recorded, one is not likely to hear 20 +.

JOSEPH G. BRADLEY, JR.  
New York, N.Y.



*Mr. Sutheim's contention is that one is not likely to hear 20+ regardless of what is recorded. We have an article in the works on operational amplifiers.*

#### MANUFACTURERS AS VILLAINS?

After being in this business as an electronic technician and following every bit of Mr. Gernsback's writings since 1938, I was shocked at your reply to V. N. Everts' letter (December 1967). A pat on the back for Mr. Evert for speaking out; more electronic technicians should come forward on this issue. It is the service technicians who keep the manufacturers in business. A fourth of my calls is to correct mistakes of the manufacturer and to try to explain why a customer's 10-year-old set, with a good picture, had to be repaired only three or four times in the past 5 years, when their new set has gone out three times in the first 3 months. Do you really think this is progress? We in the service business

# LOOK!
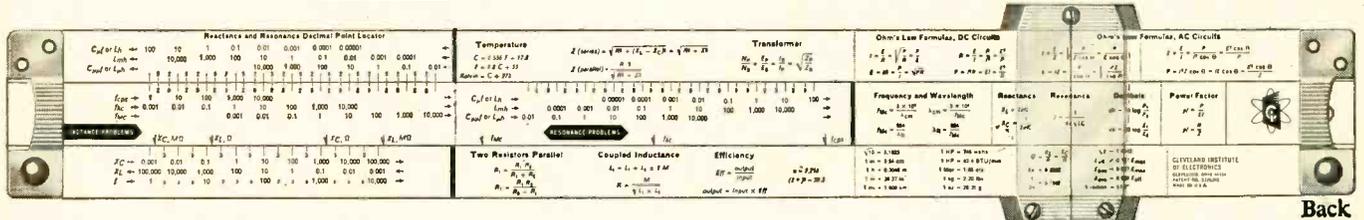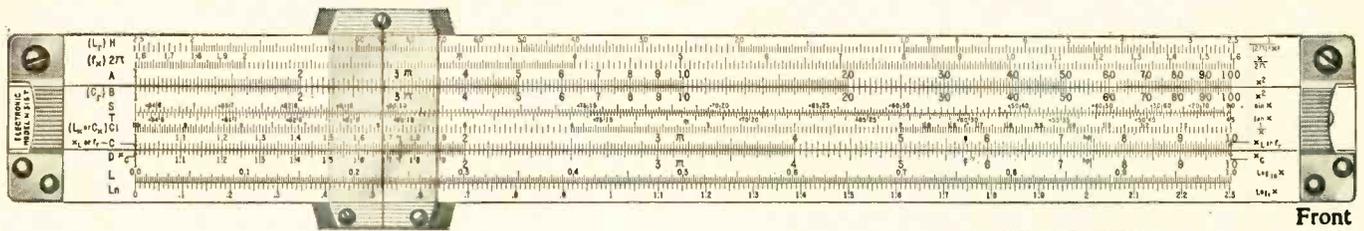
## A New Electronics Slide Rule with Instruction Course




This amazing new "computer in a case" will save you time the very first day. CIE's patented, all-metal 10" electronics slide rule was designed *specifically* for electronic engineers, technicians, students, radio-TV servicemen and hobbyists. It features special scales for solving reactance, resonance, inductance and AC-DC circuitry problems . . . an exclusive "fast-finder" decimal point locator . . . widely-used formulas and conversion factors for instant reference. And there's all the standard scales you need to do multiplication, division, square roots, logs, etc.

Best of all, the CIE Slide Rule comes complete with an Instruction Course of four **AUTO-PROGRAMMED** lessons. It includes hundreds of illustrations, diagrams and practice problems. You'll learn ingenious short cuts . . . whip through exacting electronics problems quickly and accurately. This course alone is worth far more than the price of the entire package!

Electronics Slide Rule, Instruction Course, *and* handsome, top-grain leather carrying case . . . a \$50 value for less than \$25. Send coupon for **FREE** illustrated booklet and **FREE** heavy vinyl Pocket Electronics Data Guide. Cleveland Institute of Electronics, 1776 E. 17th St., Dept. RE-149, Cleveland, Ohio 44114.

\*TRADEMARK

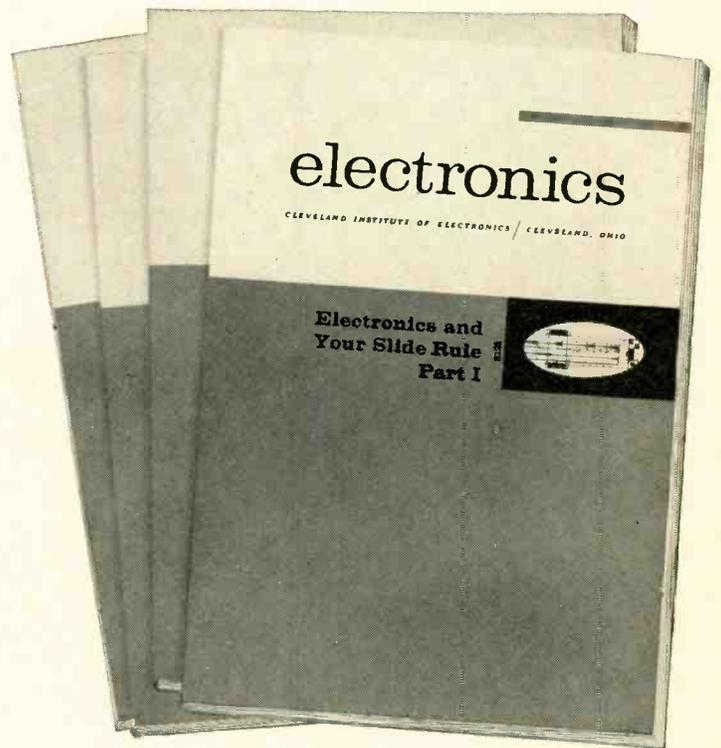

**GET BOTH FREE!**



**Cleveland Institute of Electronics**

1776 E. 17th St., Dept. RE-149, Cleveland, Ohio 44114

Please send **FREE** Illustrated Booklet describing your Electronics Slide Rule and Instruction Course.

**SPECIAL BONUS!** Mail coupon promptly . . . get **FREE** Pocket Electronics Data Guide too!


Name \_\_\_\_\_

Address \_\_\_\_\_ (PLEASE PRINT) \_\_\_\_\_ County \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

A leader in Electronics Training . . . since 1934.

Circle 9 on reader's service card

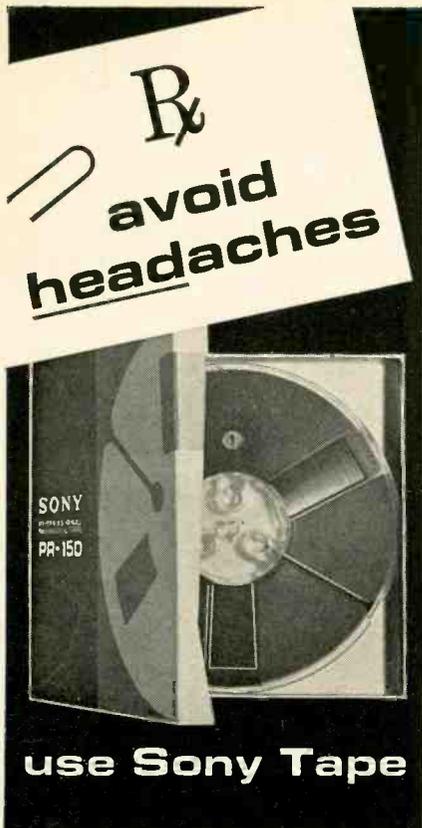

If you've been using any of the so-called bargain tapes, chances are you should have your heads examined. The odds are good that the heads are excessively worn and you're not getting the most out of your recorder. If you want to keep "factory-fresh" sound to your recorder—and avoid future "headaches" and keep it that way—Here's the prescription—buy Sony Professional-quality Recording Tape. Sony Tape is permanently lubricated by the exclusive Lubri-Cushion process. Sony's extra-heavy Ox-Coating won't shed or sliver and is applied so evenly that recordings made on Sony Tape are not subject to sound dropouts. Sony Tape captures and reproduces the strength and delicacy of every sound—over and over again. There's a bonus, too, with every 5" and 7" reel of Sony Tape—a pair of Sony-exclusive "Easy Threader" tabs to make tape threading the easiest ever. And Sony reels are a sturdier, heavier gauge plastic for protection against possible warping. It's just what the "Doctor" ordered and yours for just pennies more than "bargain" tape.

**SONY** **SUPERSCOPE**  
 SUN VALLEY, CALIFORNIA • 91352  
 Circle 10 on reader's service card

**CORRESPONDENCE** *continued*

have enough to do on well-built sets where at the very least we can get at the parts. I use the very best equipment I can get and yet on these "Mickey Mouse" sets it is impossible to get at the parts even with medical tools. I would just love to see a factory service technician replace a transistor in a small TV tuner sealed with a spot weld on the side.

MARV POOLEY, WA0SDL  
 Mitchell, S. Dak.

**DUST COLLECTOR WANTED**

I am in need of schematic diagrams and information pertaining to the design of (1) a static-dust collector as used in small family dwellings and (2) a metal locator used to find small coins, jewelry, etc. at beaches.

WALTER BAER  
 Mineola, N.Y.

*Walter, you'll find a metal locator in the November 1967 issue. As for a static dust collector, we don't have any (except for some old AM radios). Perhaps one of our enterprising contributors of electronic project articles, after reading this letter, will submit a workable project we can publish.*

**FM STEREO ADAPTER**

I am interested in building the "Modern FM Stereo Adapter" (August 1967) but I am puzzled by one thing which appears to be an omission from the schematic diagram. I do not see any supply-voltage connection for transistors Q5 and Q6.

C. L. PARRISH  
 Melbourne, Fla.

*Good catch C. L. The emitter of Q6 should also be connected to 14 volts. Should you desire to use a ready-made printed circuit board for this project, you can get one from Transitek Co., PO Box 205, Des Moines, Wash., 98016. Send \$4.15 and ask for part No. MD116.*

**MAGNETRON MODULATION**

While reading the article, "Creative Electronic Servicing" (September 1967) I was a little surprised to see Mr. Larry Allen's block diagram of a radar transmitter (page 40). I have worked on many types of radar but never ran across one where the magnetron feeds the modulator. In my opinion a pulsed radar transmitter can-

(continued on page 12)

**Radio-Electronics**

154 WEST 14TH STREET  
 NEW YORK, N. Y. 10011

HUGO GERNSBACK (1884-1967)  
 editor-in-chief and founder  
 M. HARVEY GERNSBACK, publisher  
 ROBERT CORNELL, editor  
 Robert F. Scott, W2PWG, senior editor  
 Thomas R. Haskett, managing editor  
 Jack Darr, service editor  
 Peter E. Suteim, audio editor  
 I. Queen, editorial associate  
 Matthew Mandl, contributing editor  
 Linda Albers, assistant to editor  
 Wm. Lyon McLaughlin,  
 technical illustration director  
 Bruce Ward, production manager  
 Adelaide Cassity, production assistant  
 G. Aliquo, circulation manager  
 Cover by Harry Schlack

RADIO-ELECTRONICS is published by Gernsback Publications, Inc.  
 President: M. Harvey Gernsback  
 Vice President-Secretary: G. Aliquo

**ADVERTISING REPRESENTATIVES**

**EAST**  
 John J. Lamson,  
 RADIO-ELECTRONICS, 154 West 14th Street,  
 New York, N. Y. 10011, 212-255-7755

**MIDWEST/N.&S. Car., Ga., Tenn.**  
 Robert Pattis, the Bill Pattis Co., 4761 West Touhy Ave., Lincolnwood, Ill. 60646, 312-679-1100

**W. COAST/Texas/Arkansas/Oklahoma**  
 J. E. Publishers Representative Co., 8380 Melrose Ave., Los Angeles, Calif. 90069, 213-653-5841; 420 Market St., San Francisco, Calif. 94111, 415-981-4527

**UNITED KINGDOM**  
 Publishing & Distributing Co., Ltd., Mitre House, 177 Regent St., London W.1, England

**SUBSCRIPTION SERVICE:** Send all subscription correspondence and orders to RADIO-ELECTRONICS, Subscription Department, Boulder, Colo. 80302. For change of address, allow six weeks, furnishing both the old and new addresses and if possible enclosing label from a recent issue.

**MOVING?** Or writing about subscription? Be sure to fill out form below.

For FASTEST service on address change, missing copies, etc., attach old mailing label in first space below. Otherwise please print clearly your address as we now have it.

OLD ADDRESS (Attach old label if available)

Name .....

Address .....

City ..... State .....

Zip Code .....

**NEW ADDRESS**

Name .....


Address .....

City ..... State .....


Zip Code .....

Mail to: **RADIO-ELECTRONICS**  
 Subscription Dept. Boulder, Colo. 80302
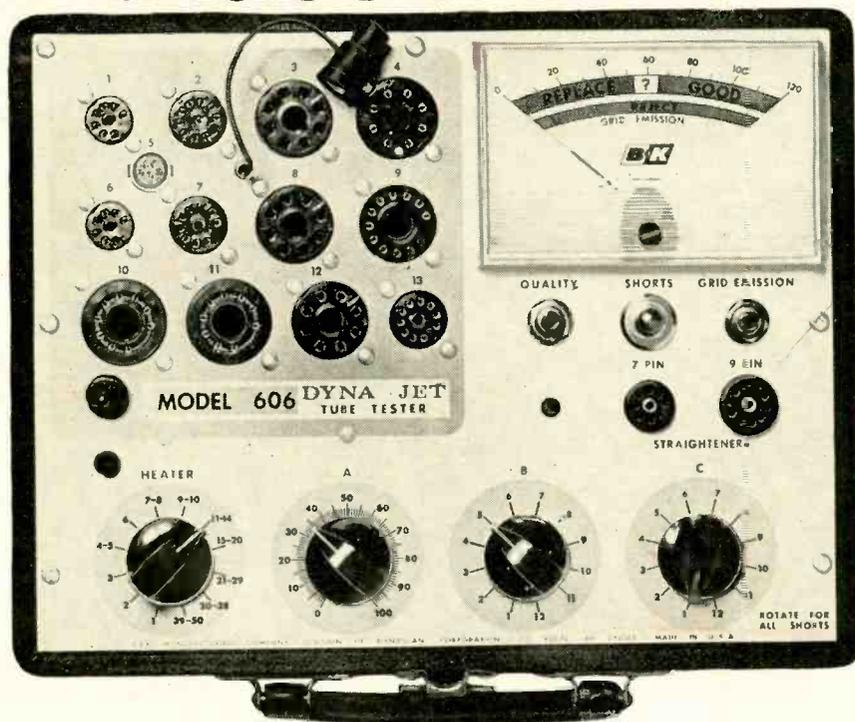
# fast. accurate. versatile. what else would you want from a tube tester?



## money, of course.

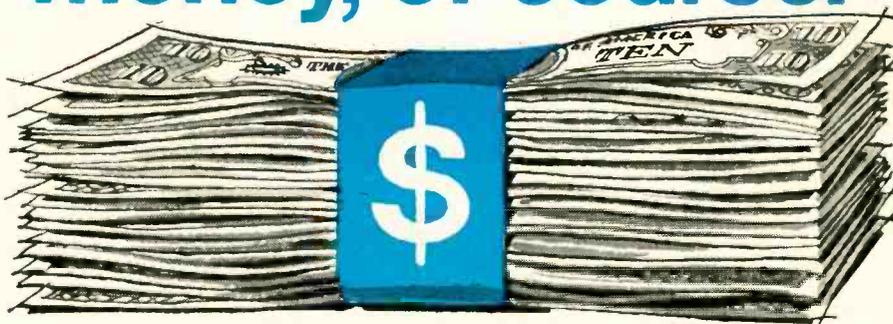

We know that swift and sure tube testing makes servicing more profitable. So we created the Dyna-Jet 606 Tube Tester, the professional portable loaded with the most-wanted features. Multiple 13-socket design means only 4 test settings, yet it tests the latest miniature and color receiving tubes as well as older types.

It tests for all shorts, grid emission, leakage, gas. Checks cathode emission the accurate way—under simulated load conditions. Checks each section of multi-section tubes. And the 606's exclusive front panel adjustable grid emission test spots the "tough dogs" and the weak ones. With the 606, good tubes aren't rejected, bad ones show up fast. That means less callbacks, more tube sales, better profit . . . MORE MONEY!

Few test instruments pack the profit-per-square-inch as does the Dyna-Jet 606. It's another product of B & K electronic innovation . . . of B & K's policy to provide maximum value and maximum quality. And the B & K Professional Servicing Equipment emblem assures you . . . and your customers . . . that you use the finest equipment available. Model 606 Net: \$79.95



**A DIVISION OF DYNASCAN CORPORATION**


1801 W. Belle Plaine, Chicago, Illinois 60613

WHERE ELECTRONIC INNOVATION IS A WAY OF LIFE

Canada: Atlas Radio Corp., Ltd., 50 Wingold Avenue, Toronto 19, Ontario. Export: Empire Exporters, Inc., 123 Grand Street, New York, N.Y. 10013.

Circle 11 on reader's service card

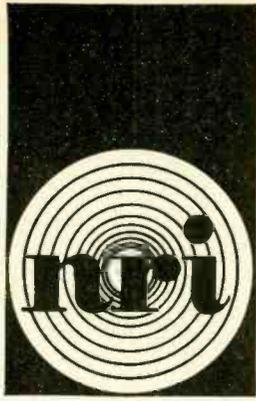[www.americanradiohistory.com](http://www.americanradiohistory.com)



***Learning electronics at home is faster, easier, more interesting with new achievement kit***


Only NRI offers you this pioneering method of "3 Dimensional" home-study training in Electronics, TV-Radio . . . a remarkable teaching idea unlike anything you have ever encountered. Founded more than half a century ago—in the days of wireless—NRI pioneered the "learn-by-doing" method of home-study. Today, NRI is the oldest, largest home-study Electronics school. The NRI staff of more than 150 dedicated people has made course material entertaining and easy to grasp. NRI has simplified, organized and dramatized subject matter so that any ambitious man—regardless of his education—can effectively learn the Electronics course of his choice.

**DISCOVER THE EXCITEMENT OF NRI TRAINING**

Whatever your reason for wanting knowledge of Electronics, you'll find the NRI "3 Dimensional" method makes learning exciting, fast. You build, test, experiment, explore. Investigate NRI training plans, find out about the NRI Achievement Kit. Fill in and mail the postage-free card. No salesman will call. NATIONAL RADIO INSTITUTE, Electronics Division, Washington, D. C. 20016

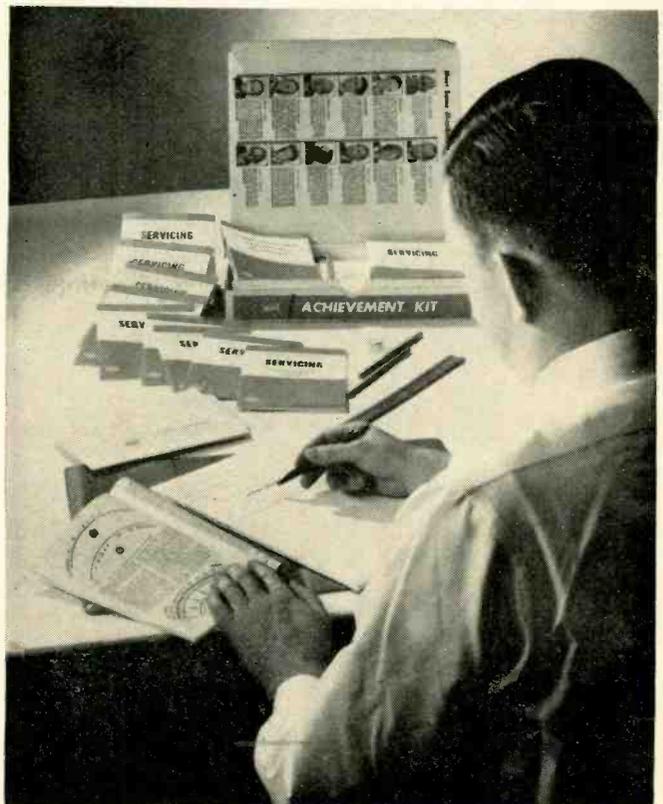**GET A FASTER START IN THE COURSE YOU CHOOSE WITH NRI'S REMARKABLE ACHIEVEMENT KIT**

When you enroll with NRI we deliver to your door everything you need to make a significant start in the Electronics field of your choice. This remarkable, new starter kit is worth many times the small down payment required to start your training. And it is only the start . . . only the first example of NRI's unique ability to apply 50 years of home-study experience to the challenges of this Electronics Age. Start your training this exciting, rewarding way. No other school has anything like it. What do you get? The NRI Achievement Kit includes: your first set of easy-to-understand "bite-size" texts; a rich, vinyl desk folder to hold your training material in orderly fashion; the valuable NRI Radio-TV Electronics Dictionary; important reference texts; classroom tools like pencils, a ball-point pen, an engineer's ruler; special printed sheets for your lesson answers—even a supply of pre-addressed envelopes and your first postage stamp.



## ELECTRONICS COMES ALIVE AS YOU LEARN BY DOING WITH CUSTOM TRAINING EQUIPMENT

Nothing is as effective as learning by doing. That's why NRI puts so much emphasis on equipment, and why NRI invites comparison with equipment offered by any other school, at any price. NRI pioneered and perfected the use of special training kits to aid learning at home. You get your hands on actual parts like resistors, capacitors, tubes, condensers, wire, transistors and diodes. You build, experiment, explore, discover. You start right out building your own professional vacuum tube voltmeter with which you learn to measure voltage and current. You learn how to mount and solder parts, how to read schematic diagrams. Then, you progress to other experimental equipment until you ultimately build a TV set, an actual transmitter or a functioning computer unit (depending on the course you select). It's the practical, easy way to learn at home—the priceless "third dimension" in NRI's exclusive Electronic TV-Radio training method.


## SIMPLIFIED, WELL-ILLUSTRATED "BITE-SIZE" LESSON TEXTS PROGRAM YOUR TRAINING

Lesson texts are a necessary part of training, but only a part. NRI's "bite-size" texts are as simplified, direct and well-illustrated as half a century of teaching experience can make them. The amount of material in each text, the length and design, is precisely right for home-study. NRI texts are programmed with NRI training kits to make things you read come alive. As you learn, you'll experience all the excitement of original discovery. Texts and equipment vary with the course. Choose from major training programs in TV-Radio Servicing, Industrial Electronics and Complete Communications. Or select one of seven special courses to meet specific needs. Check the courses of most interest to you on the postage-free card and mail it today for your free catalog.


Available Under  
**NEW  
GI BILL**

If you served since  
January 31, 1955, or  
are in service, check GI  
line in postage-free card.
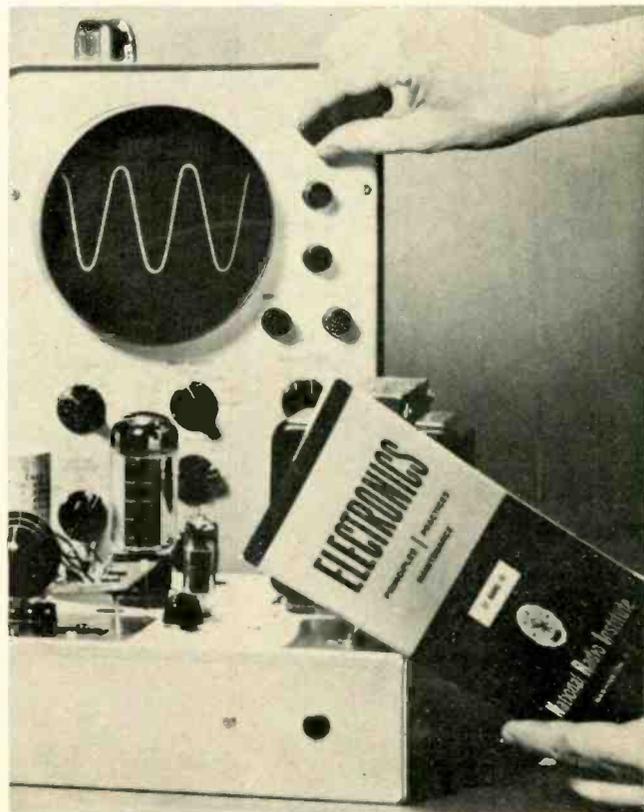
## *custom training kits "bite-size" texts*


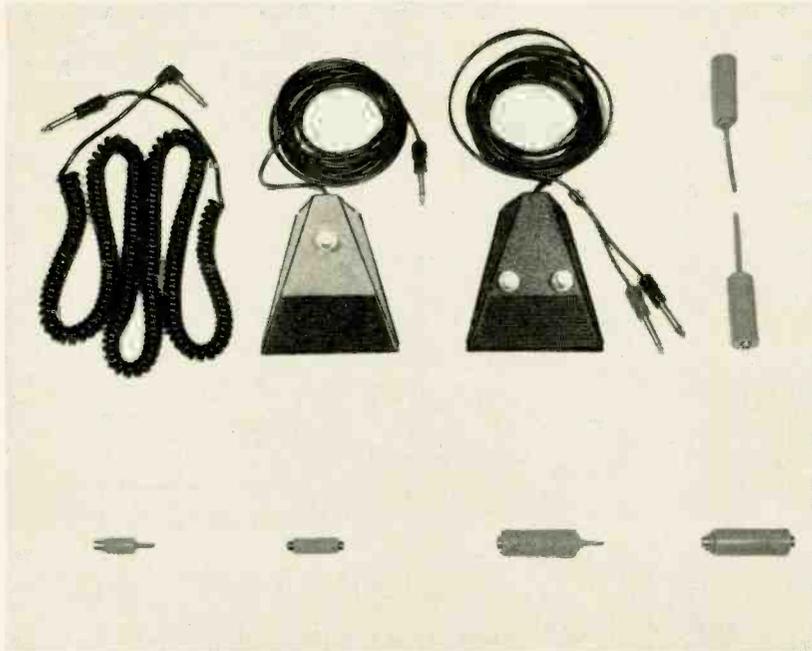
# If a plug or accessory from BARKER is not shown here – it's in our catalog!




ABOVE: from left to right. First row. Guitar coil cord 20' RSP-RE in six colors—White—Beige—Grey—Red—Black—Blue. FS-1 Foot switch single—designed for amplification Shut-off. FS-2 Foot switch—dual—designed for amplifier and reverberation. PJ-PJ Phone Plug to phone plug adapter.

Second row. ATF "Molded on" Adapter—Adapts phono pin plug to miniature two (2) conductor phone plug. AFF Phono jack to Phono jack. PJT phone jack to mini-plug, PJJ Phone jack to Phono jack.

BELOW: from left to right. First row. PJM Phone jack to Phono plug. APF Phono jack to Phone plug. M-FF 2 phono jacks connected in parallel to phono plug, 4" shielded cables. F-MM Phono Jack connected to 2 phono plugs 4" shielded cables.

Second row. M-MM 3 phono plugs connected in parallel 4" shielded cables. D4 2 individually shielded cables with phono plugs each end color coding positively identifies each circuit 36"—72" & 12'. 20' 3LP-3PJ "Molded On" three (3) conductor phone plug one end of 20' three conductor cable—Other end a "Molded On" three (3) conductor phone jack—For stereo head set application. FM-1 Twin lead FM Antenna Dipole type for indoor use—Has 6 Foot Lead-in with spade lugs.

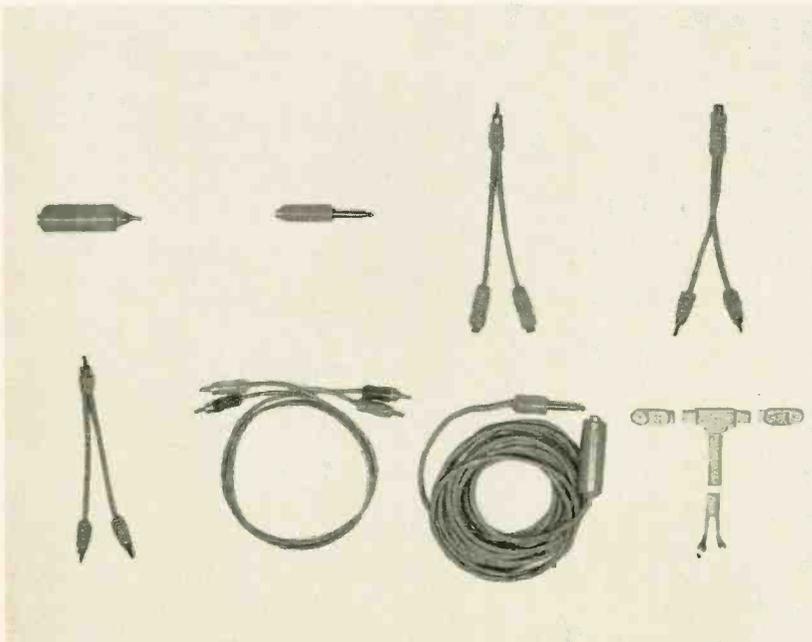

Manufacturers, distributors and dealers: write for our latest catalog. All our products made on our U.S.A. premises. Circle Reader's Service # for our latest catalog. For speedier service, write us direct.

## BARKER PRODUCTS COMPANY

344 Central Street, Saugus, Mass. 01906 Telephone: 617-233-6676

Subsidiary of Component Manufacturing Service, Inc.

## CORRESPONDENCE

(continued from page 6)

not be easily compared with a TV transmitter or any other CW transmitter.

BOB L. RUCKER  
Wichita, Kans.

Okay, Bob, just flip the magnetron and modulator labels on the block diagram in Fig. 3. Also show the pulse generator going to the modulator and not to the magnetron. Mr. Allen was attempting to show that troubleshooting complex electronic equipment can be simplified.

## PARTS FOR TREASURE FINDER

I am interested in building the Treasure Finder (November 1967). Can you tell me where I can buy a kit of parts?

M. E. LONG  
Alameda, Calif.

Except for loop L1, which you make yourself, all parts are standard. No kit is available for this particular project. You should not have too much difficulty getting all these parts. You may have to try more than one supplier, in your area.

## JACK DARR DOES NICE THINGS

Thank you very much for your (Jack Darr's) letter of Nov. 30 and the information about the Stromberg Carlson CD 20 TV models that you sent. Your kindness in sending it was one of the nicest things that has happened to me in a long time—and boosted my faith in humanity many points.


F. M. JACOBSEN  
Whiting, Ind.

## CONSTRUCTION VS. SERVICE ARTICLES

I've been a continuous subscriber since age 14 (1943 when it was Radio-Craft), so perhaps I have some right to voice my opinions. You might best label me an advanced experimenter—lots of construction skill but limited electronic design capability. I've depended on R-E (and R-C) for schematics for many projects. But you've steadily abandoned this type of reader in favor of the service technician. In short, I'd like to see much more in the way of construction articles of all kinds.


M. D. RATCLIFF  
Vero Beach, Fla.  
R-E

# If you're looking for trouble,

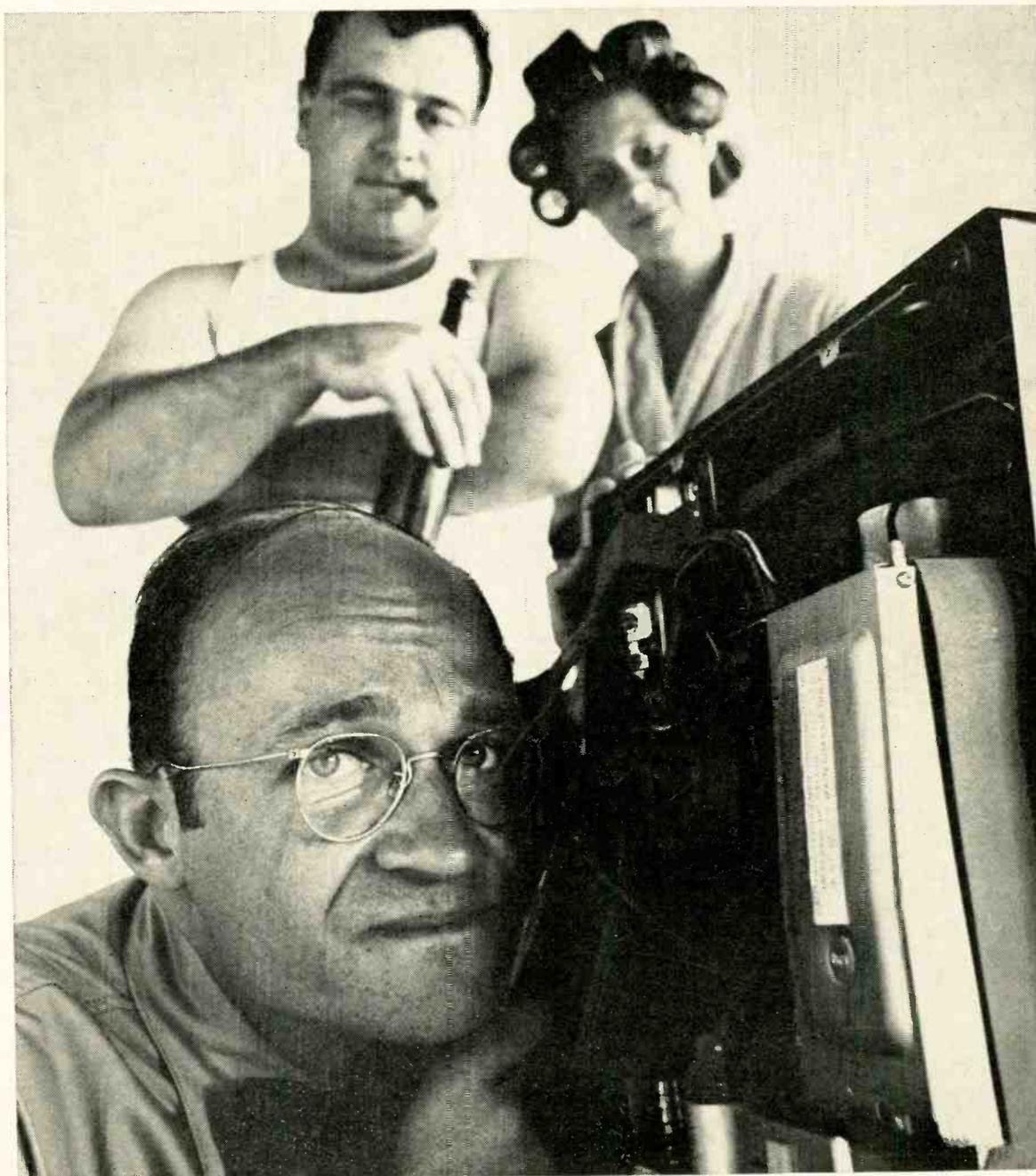
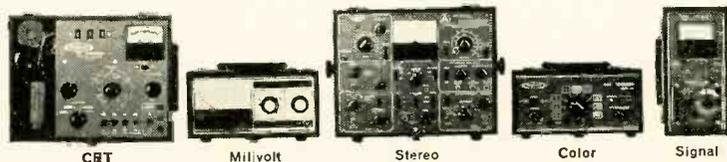
## you'll find it fast.

That's what Amphenol test equipment is all about. The CRT Commander. The Milivolt Commander. The Signal Commander. The Color Commander. The Stereo Commander. They're all time savers. With them you can test any TV, radio or stereo set. They let you find trouble, fix it, then get out of there. See your Amphenol distributor. Or write us direct. Amphenol Corporation, Department RE-28, 2875 South 25th Avenue, Broadview, Illinois 60153.



**AMPHENOL**

Circle 13 on reader's service card

Who  
stocks  
replacements  
for  
Valvo Tubes\*  
in  
your area?

Your local  
Amperex  
distributor.

And he stocks the full line of Valvo receiving tubes, not just the "most-called-for" types. With this new, off-the-shelf convenience, you can forget about any problem of immediate availability of replacements for your servicing jobs on imported radios and hi-fi components.

For names and addresses of the Amperex (and Valvo) distributors in your area, write: Amperex Electronic Corporation, Distributor Sales Dept., Hicksville, Long Island, N. Y. 11802

\*All Valvo replacement tubes sold in the U.S.A. are branded Amperex and are packaged in Amperex cartons.

**Amperex**<sup>®</sup>

TOMORROW'S THINKING IN TODAY'S PRODUCTS

Circle 14 on reader's service card

## In the Shop . . . With Jack

By JACK DARR

### CASE OF THE DISORGANIZED ORGAN

THERE ARE TIMES, IN THE ELECTRONICS repair business, when we run into things which "don't make sense". We get that "Now, why did it do that?" reaction. Things happen that seem to violate the laws of electronics. They don't, of course, but they seem to—they can throw you a curve. So, we have to keep up a kind of mental agility while we're working—be ready to admit any possibility, no matter how remote it might seem. If we freeze on one line of thinking, we've had it. We'll be there all night!

Here's a case in point. A big old Baldwin electronic organ was acting up. It was an oscillator-frequency-divider type, with one tone generator for each note. An oscillator generated the highest frequency, then a succession of blocking oscillators divided this by two, for the similar notes in each of the other octaves.

So, any trouble usually showed up as a "burble" or flutter in the faulty note, and in all the similar notes in the octaves below. All you had to do was count down to the note in the highest octave that was burbling—say the third from the top—and go into that divider stage. Leaky capacitors, drifted resistors, etc., would make the divider misfire or run off frequency.


Now, though we were stuck. The highest "C" was okay, but all the rest were burbling, indicating trouble in the first divider stage. However, everything in that stage checked out okay. A couple of dubious capacitors were replaced, with no results. All of the other notes on the organ worked beautifully.

Finally, we made a mock-up and

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge, and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. Write: Service Editor, Radio-Electronics, 154 West 14th Street, New York 10011.

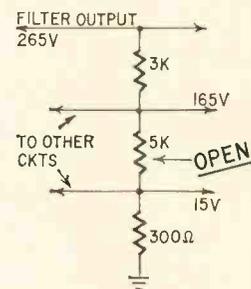hooked the tone generator up on the bench, using the same voltages found in the organ. Now, we could check it with a scope. Setting the sweep to show 4 cycles at the oscillator frequency, the first divider should show 2, the next 1 and so on. However, the



first divider showed 4 cycles, jittering. This was the burble we'd been hearing.

Experimenting desperately, we found that varying the plate voltage

had little effect or none. However, a +15-volt applied bias was fed to the divider cathodes, and varying this did have an effect! Most definitely it did. Now, we checked the "service data."

This showed us what was happening. The bias voltage held the dividers at cutoff unless there was a drive signal from the oscillator. This voltage set the firing point of the blocking oscillators. By varying this bias, we could make the first divider trigger beautifully, and all the rest as well.

Hmmm. The schematic showed +165 volts on the plate and +15 volts of bias. We had read +200 volts and +10 volts at the church where the organ was used. This much variation was out of tolerance. We pulled the power supply, which had not been considered as a source of trouble, because all the other notes were working.

Power supply very ordinary. Rectifier, filter, bleeder resistors, etc. okay, although the supply was pretty complex, with so many stages to feed. Our tone-generator supply had a 3-resistor bleeder/voltage divider. From the +265 volt source, there were 3000, 5000 and 300 ohms to ground, with the voltages shown.

The 5000-ohm resistor was open. Parallel paths in the circuitry kept the voltage from disappearing entirely, but it wasn't at the right value by a long shot. We replaced the open resistor, and all voltages went back to normal. So did the C generator! Now,

# COLOR GENERATORS FOR EVERY NEED

4 reasons why Sencore is your best buy  
in professional test instruments

1

### LOBOY CG10

America's lowest priced professional quality standard color bar generator. All solid state. Battery powered for maximum portability.

\$89.95



2

### LOBOY CG12

AC operated version of the CG10. Also has 4.5 MHz crystal controlled signal for fine tuning adjustment.

\$109.95



3

### COLOR KING CG141

Absolute stability assured by exclusive "Temp Control" and new timer circuitry. All standard patterns, plus new movable single dot and single cross. Analyzing features too.

\$149.95



4

### COLOR ANALYZER CA122B

The complete analyzer for color and B&W—far more than just a color generator. Has variable RF and IF outputs, composite video, chroma, and horizontal and vertical sync pulses.

\$187.50



Whatever the need, Sencore has the color generator that is just right for you. Each has the built-in quality you expect from Sencore. Each has standard RCA licensed color bar patterns.

Each is triple tested for guaranteed accuracy. Each is steel encased with chrome panel. See your distributor for more reasons why Sencore is your best buy, always.



## SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT  
426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 15 on reader's service card



Get Top **PERFORMANCE** from



your Car! **Buy The Best!**  
**DELTA'S Remarkable, Proven**

# MARK TEN CAPACITIVE DISCHARGE IGNITION SYSTEM

ONLY  
**\$44.95**  
 ppd.

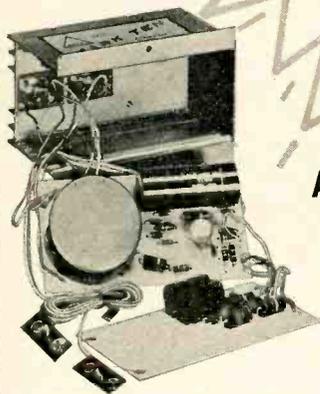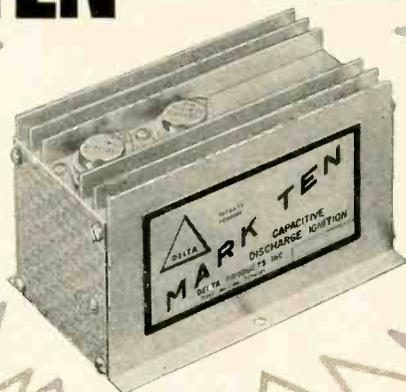

Available in Easy-to-Build

## DELTAKIT® ONLY

ASSEMBLE IT  
 YOURSELF!

**\$29.95**  
 ppd.

You've read about the Mark Ten in Radio Electronics, Electronics World, Mechanix Illustrated, Electronics, Popular Mechanics and other leading publications! Now discover what dramatic improvement in performance with capacitive discharge ignition is yours for your car, truck, jeep, boat — any vehicle! Delta's remarkable electronic achievement — on the market since 1963 and so unique that a patent has been granted — saves on gas, promotes better acceleration, gives your car that zip you've always wanted. Even Detroit has finally come around. Delta's Mark Ten, the original, the proven winner from Sebring to Suburbia, has set new records of ignition benefits attested to by thousands of satisfied purchasers. No re-wiring necessary. Works on literally any type of gasoline engine. Satisfaction guaranteed.

Order from coupon below, specifying car make, voltage and polarity. Like to build your own? Order a Deltakit® and save!

### COMPARE THESE PROVEN BENEFITS!...

- ▲ DRAMATIC INCREASE IN ACCELERATION
- ▲ LONGER POINT AND PLUG LIFE
- ▲ IMPROVED GASOLINE MILEAGE
- ▲ MORE COMPLETE COMBUSTION
- ▲ SMOOTHER PERFORMANCE

Order Your Mark Ten Today! Shipped Postpaid at Once.



## DELTA PRODUCTS, INC.

P.O. BOX 1147 RE — GRAND JUNCTION, COLORADO 81501

Enclosed is \$ \_\_\_\_\_

Ship prepaid.  Ship C.O.D.

Mark Tens (Assembled) @ \$44.95

Mark Tens (Deltakit®) @ \$29.95

(12 volt positive or negative ground only)

Specify  6 Volt: Negative Ground only.

12 Volt: Specify  Positive Ground  Negative Ground

Car Year \_\_\_\_\_ Make \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City/State \_\_\_\_\_

Zip \_\_\_\_\_

Circle 16 on reader service card

In the shop . . . With Jack

(continued from page 14)

all notes played as sweet as a bird!

Now, there was the problem. With about 16 tone generators, counting sharps and flats, why did this loss of voltage affect *only the one*? The same power supply fed all of the rest, in parallel! The best guess that we could make was that this one was affected first because of its high frequency, or because its parts were right on the limit of tolerance (or something!)


The moral of this, of course, is: "Check everything!" This includes the power supply to the thing being tested. This ought to be checked first no matter what kind of gizmo you're working on.

### Limiting Amplifier for Taping Speech

I record speech on a miniature tape recorder. Later, this is re-recorded on a larger machine, where the problems set in. Because of the necessary mike placement, I get some voices very loud and others very low, and on the re-recording, it sounds awful! Is there any way that I could equalize the voice level?—A.W., Newark, N.J.

There is one thing you might try first: Place the mike farther from the people if you can't locate it in a central position. Mikes will pick up sound from much greater distances than most people believe. Turn the record gain

(continued on page 22)

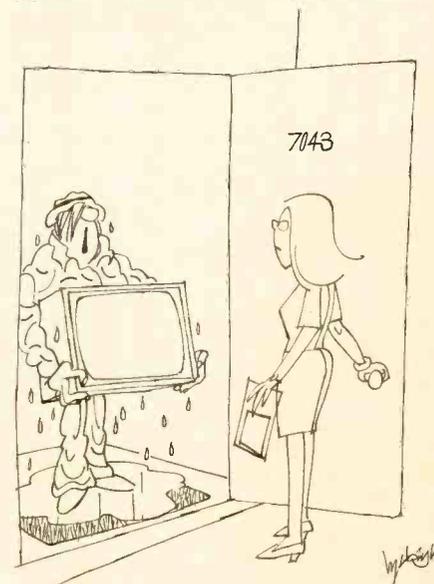


"When did you put in the swimming pool?"

# Now...in every price range, every tracking force range

from \$67.50 to \$25.00...

from  $\frac{3}{4}$  grams to 5 grams

With the introduction of our extremely low cost new M32E elliptical stylus cartridge (\$25.00 net,  $2\frac{1}{2}$  to 5 gms. tracking, 20 to 17,500 Hz), and M31E elliptical stylus cartridge (\$27.50 net, 1 to 2 gms. tracking, 20 to 18,000 Hz), you can now get Shure quality in the broadest possible spectrum of prices and specifications. Given our "druthers", we would prefer you bought the Shure V-15 Type II Super Trackability cartridge at \$67.50. We feel it's the world's finest cartridge, and independent critics the world over agree with us. However, if your equipment or your exchequer dictates another cartridge, be assured that Shure makes a really complete line of best-in-their-price-class cartridges. Note for instance, the impressive line-up of elliptical styli cartridges below. Detailed literature on the *complete* Shure group with the reason for each is available at no cost: Shure Brothers, Inc., 222 Hartrey Ave., Evanston, Illinois, 60204.

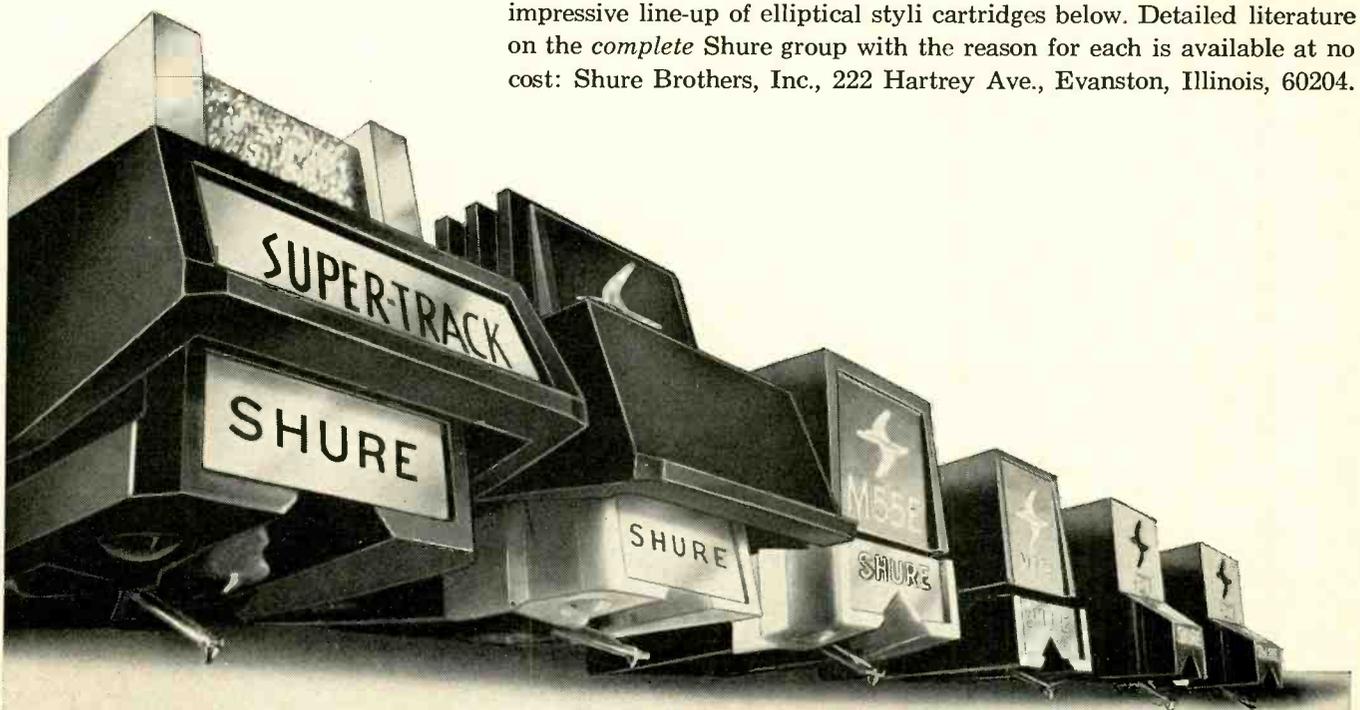

V-15 TYPE II  
\$67.50  
 $\frac{3}{4}$  to  $1\frac{1}{2}$  gms.

M75E  
\$39.50  
 $\frac{3}{4}$  to  $1\frac{1}{2}$  gms.

M55E  
\$35.50  
 $\frac{3}{4}$  to  $1\frac{1}{2}$  gms.


M44E  
\$34.50  
 $1\frac{1}{4}$  to 4 gms.

M31E  
\$27.50  
1 to 2 gms.

M32E  
\$25.00  
 $2\frac{1}{2}$  to 5 gms.

© 1967 Shure Brothers, Inc.

Circle 17 on reader's service card

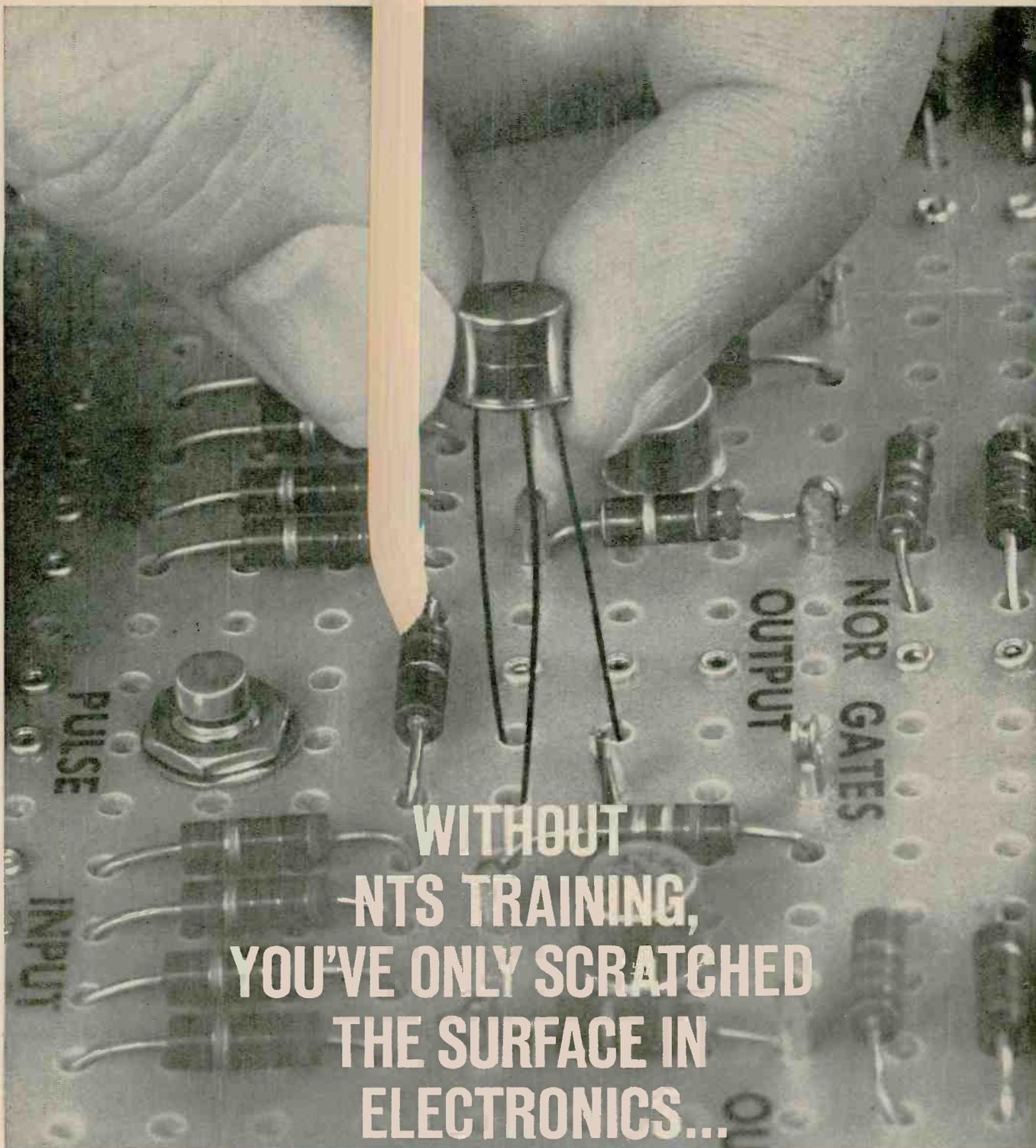

Only NTS penetrates below the surface. Digs deeper. Example? Take the above close-up of the first transistorized digital computer trainer ever offered by a home study school.

It's called The Compu-Trainer®—an NTS exclusive. Fascinating to assemble, it introduces you to the exciting world of computer electronics. Its design includes advanced solid-state NOR circuitry,

flip-flops, astable multivibrators and reset circuits. Plus two zener and transistorized voltage-regulated power supplies. The NTS Compu-Trainer® is capable of performing 50,000 operations per second.

Sound fantastic? *It is!* And at that, it's only one of many *ultra-advanced* kits that National Technical Schools offers to give you incomparable, in-depth career training.

**PROVE IT YOURSELF. SEND FOR OUR NEW CATALOG. SEE THE LATEST, MOST ADVANCED KITS AND COURSES EVER OFFERED BY A HOME STUDY SCHOOL.**

## NTS...THE FIRST HOME STUDY SCHOOL TO OFFER LIVE EXPERIMENTS WITH INTEGRATED CIRCUIT KITS

You build a computer sub-system using the new, revolutionary integrated circuits. Each one, smaller than a dime, contains the equivalent of 15 resistors and 27 transistors.

And your kits come to you at no extra cost. These kits are the foundation of the exclusive *Project-Method* home study system...developed in our giant resident school and proven effective for thousands of men like yourself.

With Project-Method, all your kits are carefully integrated with lesson material. Our servicing and communication kits are *real* equipment—not school-designed versions for training only. As you work on each of the projects, you soon realize that even the most complicated circuits and components are easy to understand. You learn *how* they work. You learn *why* they work.

NTS Project-Method is a practical-experience approach to learning. The approach that works *best!* An all-theory training program can be hard to understand — difficult to remember. More than ever before you need the practical experience that comes from working with real circuits and components to make your training stick.

### NTS SENDS YOU KITS TO BUILD THESE IMPORTANT ELECTRONICS UNITS!

- ◆ 25" COLOR TV
- ◆ 21" BLACK & WHITE TV
- ◆ SOLID-STATE RADIO
- ◆ AM-SW TWIN-SPEAKER RADIO
- ◆ TUBE-TESTER
- ◆ TRANSCEIVER
- ◆ COMPU-TRAINER®
- ◆ VTVM
- ◆ SIGNAL GENERATOR

See them all illustrated in  
the new NTS Color Catalog.

**CLASSROOM TRAINING AT LOS ANGELES:** You can take classroom training at Los Angeles in sunny California. NTS occupies a city block with over a million dollars in facilities devoted exclusively to technical training. Check box in coupon.

# NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

4000 So. Figueroa Street, Los Angeles, Calif. 90037

**APPROVED FOR VETERANS**



Accredited Member: National Home Study Council  
Accredited Member: National Association of  
Trade and Technical Schools

FEBRUARY 1968




### COMMUNICATIONS

This transceiver is included in Communications courses. You build it. With it, you easily prepare for the F.C.C. license exam. You become a fully-trained man in communications, where career opportunities are unlimited.
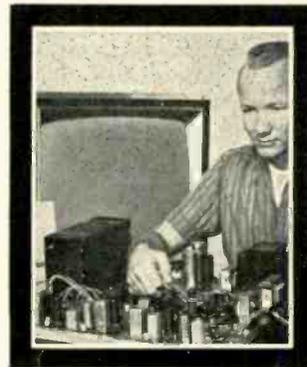
### 25" COLOR TV ▼

Included in Color TV Servicing Courses. With it you advance yourself into this profitable field of servicing work. Color is the future of television, you can be in on it with NTS training.



### YOUR OPPORTUNITY IS NOW

New ideas, new inventions, are opening whole new fields of opportunity. The electronic industry is still the fastest growing field in the U.S. There's a bigger, better place in it for the man who trains today. So, whatever your goals are — advanced color TV servicing, broadcasting, F.C.C. license, computers, or industrial controls, NTS has a highly professional course to meet your needs.

GET THE FACTS! SEE ALL NEW COURSES AND KITS OFFERED IN THE NEW NTS COLOR CATALOG. SEND THE CARD OR COUPON TODAY!



There's no obligation. We have no salesmen. That means lower tuition for you.

DEPT. 206-28

### NATIONAL TECHNICAL SCHOOLS

4000 S. Figueroa St., Los Angeles, Calif. 90037

Please rush Free Color Catalog and Sample Lesson, plus information on field checked below. No obligation.

- |   |  |
|---|--|
| <input type="checkbox"/> MASTER COURSE IN COLOR TV SERVICING        | <input type="checkbox"/> PRACTICAL TV & RADIO SERVICING    |
| <input type="checkbox"/> COLOR TV SERVICING                         | <input type="checkbox"/> FCC LICENSE COURSE                |
| <input type="checkbox"/> MASTER COURSE IN TV & RADIO SERVICING      | <input type="checkbox"/> INDUSTRIAL & COMPUTER ELECTRONICS |
| <input type="checkbox"/> MASTER COURSE IN ELECTRONIC COMMUNICATIONS | <input type="checkbox"/> STEREO, HI FI & SOUND SYSTEMS     |
|   | <input type="checkbox"/> BASIC ELECTRONICS                 |

NAME \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Check if interested in Veteran Training under new G.I. Bill.

Check if interested ONLY in Classroom Training at Los Angeles.

**In the shop . . . With Jack**

*(continued from page 16)*

up to compensate for the lower level.

Otherwise, you might get hold of one of the *speech compressors* used with CB transmitters. There are quite a few of these being made now, at different prices. These are actually simply *limiting amplifiers*, which have avc. A portion of the output signal is rectified, and applied as bias to the input or second stage. If the gain goes

too high, it cuts itself down. Similar equipment is used in most radio and TV stations, too.


You could get a compressor, put it between the mini recorder output and the bigger one's input, and then set it so that the overall output would be more uniform.

**Uncontrollable brightness**

*The intensity control on my EICO 460 scope won't change the brightness of the trace. I don't have too much brightness as it is. I get -1500 volts on pin 2*

*of the 5U1 and it doesn't vary with the intensity control. What's the matter?—L.G., Jersey City, N.J.*

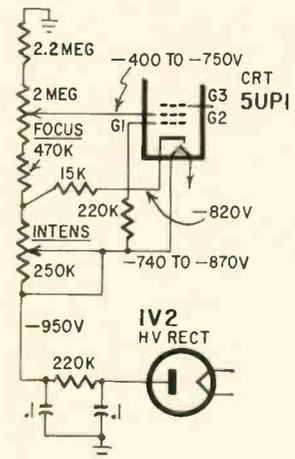You've got an open resistor somewhere in the voltage divider. The diagram shows how this works; your operating voltages are taken from the high-voltage rectifier cathode (1V2), and they're all too high, indicating that the divider is not loading the HV supply enough.



Normal voltages are shown in the diagram; notice that your total HV should be -950 volts, and you've got -1500. The cathode and grid voltages should vary as shown. However, if the divider is open, they won't! Crystal-ball diagnosis: One of the resistors "above" the controls is bad.

**Organ trouble**

*I'm working on a middle-aged electronic organ. At first, none of the C notes worked. A new 0.051-μF capacitor in the C-oscillator stage fixed that. Now, the C's work, but only if I leave the vibrato off! I get a "warble" tone, and the note comes up to pitch very slowly, if I hold the key down. What's causing this?—J.M., Odenton, Md.*

Basics: This type of organ uses an oscillator stage which is tuned to the

*See* **ELECTRONIC CORRESPONDENCE SCHOOL**



*"To Mr. John A. Cook, Alameda, New Mexico. Dear Mr. Cook: Yes, you may put in the plug."*

**Want the sharpest, clearest color reception**

**this side of the studio?**



*Get it with*



**Saxton COLOR POWER TV ANTENNA WIRE**

The exclusive "Magic Membrane" makes the difference!

Any engineer will tell you. There is only one theoretically perfect medium for transmitting color TV signals from antenna to set . . . and that's the air itself. But, this isn't practical or possible! So now, Saxton has engineered a "practically perfect" answer for sharper, clearer color reception . . . the exclusive "Magic Membrane" (pat. appl. for). Saxton encapsulates its copper conductor wire with layers of exclusive air-foam polyethylene sub-

stances for superior transmission. This "Magic Membrane" development helps send color signals directly from antenna to set with minimum leakage or loss. What's more, it offers extra protection against electrical interference, reflected TV signals, adverse weather conditions. You can even run the No. 1041 Shielded Model down a drain pipe for easy, out-of-sight installation! And, best of all, it's guaranteed for 20 years.

From \$2.59 and up . . . in Model 1041 Shielded Wire for city; Model 1037 for country; Model 1043—Economy


Available at the following dealers:

Almart Stores, 2 Guys from Harrison, Lafayette Radio Stores, Allied Radio Stores, Radio Shack Stores, Olson Electronics, Pergament Stores.

Manufactured by SAXTON PRODUCTS, INC. CONGERS, N.Y.

Circle 18 on reader's service card
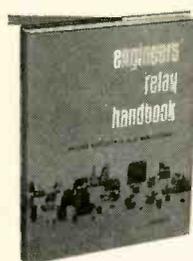
# Special Introductory Offer to new members of the electronics and control engineers' book club




**Pub. Price**  
\$11.95  
**Club Price**  
\$10.15

Engineers' Relay Handbook by the National Association of Relay Manufacturers. Code #171




**Pub. Price**  
\$18.00  
**Club Price**  
\$15.30

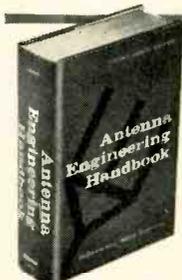Pulse, Digital, and Switching Waveforms by J. Millman and H. Taub. Code #381



**Pub. Price**  
\$26.50  
**Club Price**  
\$18.95

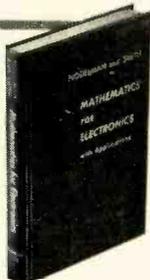Antenna Engineering Handbook by Henry Jasik. Code #290




**Pub. Price**  
\$7.00  
**Club Price**  
\$5.95

Mathematics for Electronics with Applications by H. M. Nodelman. Code #850



**Pub. Price**  
\$16.75  
**Club Price**  
\$14.25

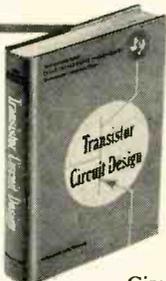Electronic and Radio Engineering by F. E. Terman. Code #509



**Pub. Price**  
\$15.00  
**Club Price**  
\$12.75

Transistor Circuit Design by the Engineering Staff of Texas Instruments, Inc. Code #737



**Pub. Price**  
\$29.50  
**Club Price**  
\$25.00

System Engineering Handbook edited by R. E. Machol. Code #371



**Pub. Price**  
\$14.00  
**Club Price**  
\$11.90

Radio Transmitters by L. Gray and R. Graham. Code #240



Special \$1.00 bonus book comes to you with your first club selection

## SAVE TIME AND MONEY BY JOINING THE electronics and control engineers' book club

Here is a professional club designed specifically to meet your day-to-day engineering needs by providing practical books in your field on a regular basis at below publisher prices.

**HOW THE CLUB OPERATES.** Basic to the Club's service is its publication, the *Electronics and Control Engineers' Book Club Bulletin*, which brings you news of books in your field. Sent to members without cost, it announces and describes in detail the Club's featured book of the month as well as alternate selections which are available at special members' prices.

When you want to examine the Club's feature of the month, you do nothing. The book will be mailed to you as a regular part of your Club service. If you prefer one of the alternate selections — or if you want no book at all for that month — you notify the Club by returning the convenient card enclosed with each *Bulletin*.

As a Club member, you agree only to the purchase of four books over a two-year period. Considering the many books published annually in your field, there will surely be at least four that you would want to own anyway. By joining the Club, you save both money and the trouble of searching for the best books.

## MAIL THIS COUPON TODAY

**electronics and control engineers' book club**  
582 PRINCETON ROAD  
HIGHTSTOWN, N. J. 08520

Please enroll me as a member of the Electronics and Control Engineers' Book Club and send me the two books indicated below. You will bill me for my first selection at the special Club price and \$1 for my new membership book, plus local tax where applicable, and a few additional cents for delivery costs. These books are to be shipped on approval, and I may return them both without cost or further obligation. If I decide to keep the books, I agree to purchase as few as four additional books during the next two years at special Club prices (approximately 15% below list).

Write Code # of your \$1 bonus book

Write Code # of your first selection



NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_ ZIP \_\_\_\_\_

COMPANY \_\_\_\_\_

(This offer good in United States only) E33043

# MACHINE SCREW and NUT ASSORTMENT

A size for every need!



CATALOG No. 9199  
Suggested Net \$4.98

Here it is, a choice selection of screws and nuts in a single carton. This working assortment, containing over 375 items, represents a complete range of Nos. 4, 6, and 8 round-head machine screws and matching hex nuts, all the popular sizes commonly used in the electronics field. These items, like all GC electronic hardware, reflect the quality materials and precision manufacture preferred by government and industry alike. Check this hand-picked assortment today, it's sized right and priced right for every electronic technician's service kit.

Always insist on **GC** ...  
you'll get more for your money every time!

**GC ELECTRONICS**  
A DIVISION OF HYDROMETALS, INC.  
MAIN PLANT: ROCKFORD, ILL. U.S.A.



Giant FREE Catalog...

Only GC gives you everything in electronics ... has for almost 40 years. Match every part and service need from over 10,000 quality items. Write for your copy today!

Circle 19 on reader's service card



has  
everything  
in  
**ELECTRONIC  
HARDWARE**



"99" WASHER  
ASSORTMENT  
Variety of metal  
and fibre washers in  
plastic box.  
Cat. No. 9119  
Suggested Net \$1.08



"99" SOLDER LUG  
ASSORTMENT  
A variety of sizes  
and shapes for  
every need.  
Cat. No. 9116  
Suggested Net \$1.08



RUBBER GROMMET  
ASSORTMENT  
200 in reusable  
plastic box ... a  
size for every need.  
Cat. No. 32-618  
Suggested Net 99¢



In the shop . . . With Jack

(continued from page 22)

highest note on the keyboard. Then this signal goes to a series of frequency dividers; each makes the "next lowest note" (one octave down in musical notes means half the frequency).


A true vibrato means a slight change in frequency; it swings back and forth around the original pitch. Many organ circuits use a dual triode tube in each tone generator: One is the tone oscillator, the other a very-low-frequency oscillator, down around 4-6 cycles per second. This signal is fed to the tone oscillator in such a way that it swings the frequency back and forth. Does it by varying grid bias.

Look for something like a coupling capacitor with a very small dc leakage, a resistor which has drifted far above normal value, or even a slight leakage across the socket through dirt accumulation. Watch for anything which would throw the vibrato oscillator off frequency, and cause it to affect the operation of the tone oscillator when it shouldn't. Most of the troubles in these circuits are due to bad capacitors or resistors.
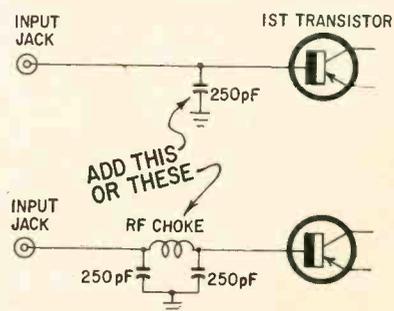
### Rf noise in stereo amplifier

*I have a new V-M 20097 amplifier that's noisy. Another one like it picks up signals from a two-way radio in the owner's car when he gets close to his home. The volume control won't cut this out.—B.S., Sabattus, Me.*

Your main problem here is that the amplifiers are too sensitive. They're picking up rf noise, CB radio signals and all kinds of electrical interference,



in their input circuits. Since the volume control in these is in the input, naturally it will have no effect on this kind of pickup.

The cure is to kill the rf signals at the input, without affecting the audio input. Try connecting a small capacitor, say about 250 pF, directly from base to ground of the input transistor on each channel. This being stereo, you'll have to fix both channels!

Anyone can build  
a column speaker.

We've built  
something better.

A new Line  
Radiator.

The LR4SA.

**(EY)** Column speakers look simple. Do it yourself? Why not!

Just hammer up a long box, grab a handful of radio-set speakers and a few feet of wire, and hook them up. Now cover the face with a couple of yards of hi-fi grille cloth and you're done. And it may even work.

Of course it won't be perfect.

It will be very heavy.

It won't be weatherproof.

Its polar pattern will be irregular — high frequency output lobes may appear almost anywhere (with at least one off the ends or back, right where you need a quiet spot for a microphone).

And finally, it may sound like nothing more than a long, narrow table radio. Or worse.

The new LR4SA Line Radiator\* was designed to combat the many ills of hit-or-miss column speaker construction.

Start with the housing. We use a single channel of extruded aluminum, plus cast end caps. Very light. Weatherproof. Much stronger pound-for-pound than wood or steel. With no maintenance needed — indoors or out.


The grille is equally unusual. Acoustifoam®. We developed this foam plastic to be completely transparent to sound — yet act as a solid barrier to water!

And the LR4SA sounds better. You get solid coverage of a wide area with flat response. Unwanted lobes of energy at the backs and sides are sharply suppressed. It's quite a trick — and very useful to you.

It's accomplished in the LR4SA with very special 3" x 5" speakers, chosen for rising response, teamed with electrical filtering that progressively rolls off highs at the ends of the column. This "contouring" of the response of every speaker is the basic difference between column speakers and a Line Radiator.

The next time you face a job that calls for a column — try the LR4SA Line Radiator instead. It can make your day!

\*T.M.

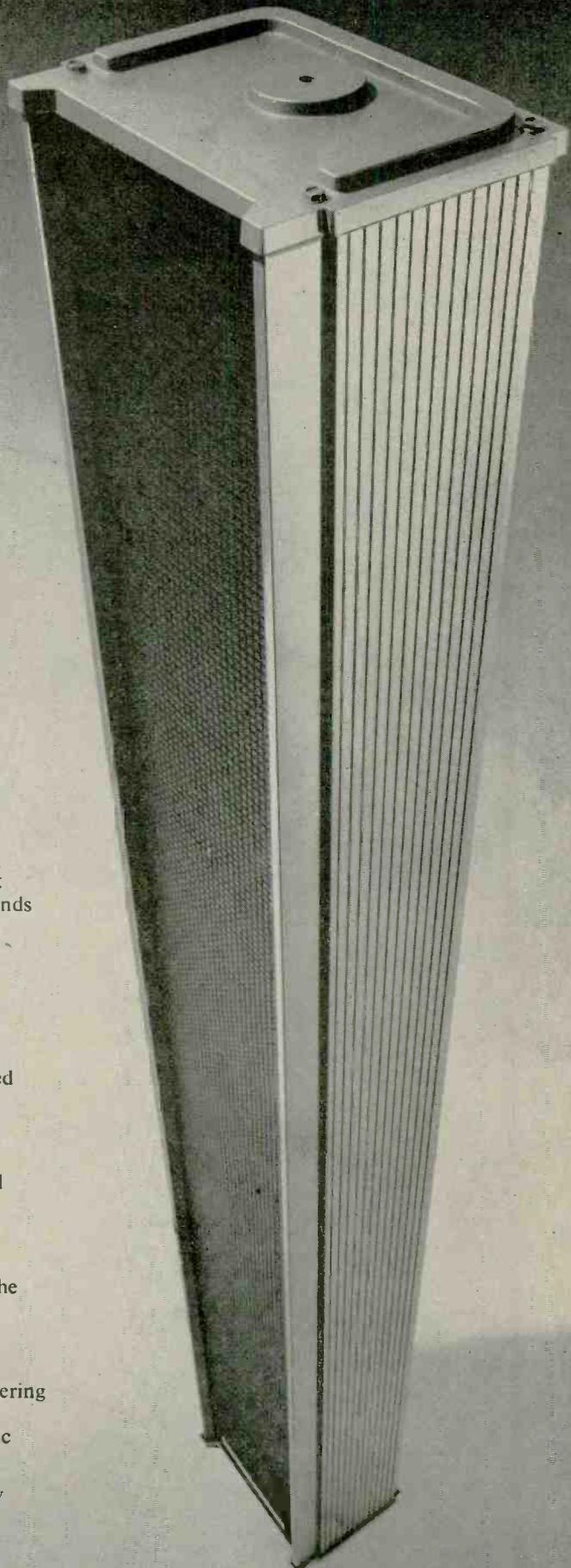


Specifications: Frequency Response 200 to 10,000 Hz; 80 Watts Peak Power; Dispersion 160° Horiz. 30° VerL; Net Weight 25 lbs.; Size 48-3/8" L x 6-5/8" W x 4-7/8" D; \$150.00 List (less normal trade discounts).

high fidelity systems and speakers • tuners, amplifiers, receivers • public address loudspeakers  
microphones • phonograph needles and cartridges • organs • space and defense electronics

**Electro-Voice®**

Electro-Voice, Inc., Dept. 286E, 613 Cecil Street, Buchanan, Michigan 49107
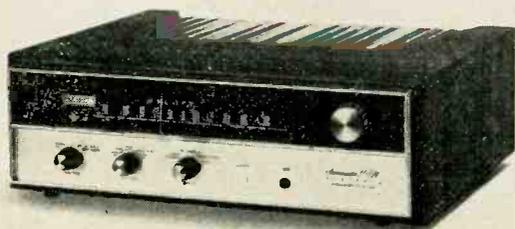
# Popular Science Top-Rates Scott's Stereo Tuner Kit (THERE'S A SOUND REASON.)



Popular Science magazine's reviewer said, "I rate the LT-112-B as one of the finest FM tuners available — in or out of kit form." All of this fabulous tuner's critical circuitry comes pre-wired, pre-tested, and pre-aligned . . . and the full-size, full-color instruction manual makes the rest simple. In just eight hours, you'll have it completed. Again, in the reviewer's words: "Stereo performance is superb, and the set's sensitivity will cope with the deepest fringe area reception conditions . . . drift is non-existent." See your Scott dealer and review the new LT-112B-1 for yourself. Only \$199.95.



©Copyright 1967, H.H. Scott, Inc.

H.H. Scott, Inc., Dept. 570-02, Maynard, Mass. 01754. Export: Scott International, Maynard, Mass. 01754  
Circle 100 on reader's service card

## In the Shop . . . With Jack

(continued from page 24)

If this doesn't get rid of it completely, add a very small rf choke in series with the input lead, right at the base of this transistor, and put a 250-pF capacitor to ground from either side of the choke, as in the diagram.

You can get small chokes already made, say about 15–20  $\mu$ H, or wind one up out of about No. 30 enameled wire. About 20 turns on a 1/8-inch form ought to do; self-supporting. These parts are so small (electrically) that they'll have no effect on the audio signals, but they should shunt out the radio-frequency signals so that they can't get into the amplifier.

Check the ac line input to the power supply; you may have to add a pair of line bypass capacitors, about .05  $\mu$ F, from each side of the ac line to chassis. This will help to keep interfering signals from being carried inside the shielding through the power line.

### Turns-per-volt ratio

*I've got an old TV power transformer, and I want to wind on some special secondaries. How do I figure out the turns-per-volt ratio?—A. B., Lynchburg, Va.*

Take the "shells" off, pull the laminations (carefully!) and locate a winding of known voltage; the easiest one is usually the 5.0-volt 5U4 filament winding (yellow wires). Now, unwind this, counting the turns. Divide this by 5, and there you are.

For instance, if you get 25 turns all together, then it has a 5 turns per volt ratio. This will hold for any other windings you want to put on. **R-E**

## People who built their own Schober Organs wrote this ad

Here's what they say about the pleasure of assembling the Schober Electronic Organ from kits . . . and enjoying the magnificent sound of an instrument they've created in their spare time.

### Building was fun

*"Building it was at least as much fun as playing it!"*

Mr. Lester F. Schwartz,  
Somerset, N. J.

### So proud I could pop

*"I've done over 90 per cent of the work on this organ myself—and I'm so proud I could about pop!"*

Mrs. V. P. Allbert,  
Topeka, Kansas

### Nothing as fine under \$5,000

*" . . . I could not find any organ that sounded as fine as the Schober under \$5,000."*

Mr. Jerome J. Fraenkel,  
Franklin Square, N. Y.

### Proud to own

*"I am proud to own such a valuable instrument."*

Mr. Jean J. Juteau,  
Montreal, Canada



The NEW Schober THEATRE ORGAN—  
one of four models available

### Most cherished possession

*"My spinet has become the most cherished possession in our home—fabulous, indeed."*

Mr. Frank J. Marion,  
North Bergen, N. J.

### Tremendous sound

*"The sound is conservatively, tremendous."*

Mr. Paul DeForest Wren,  
Westbrook, Conn.

### Unbelievably easy to build

*"When we ran out of instruction, the organ was finished . . . To me it was unbelievable!"*

Mr. Ted Sowinski,  
Chicago, Illinois

Thousands of music lovers in every walk of life—from teen-agers to grandmothers, from people who are "all thumbs" to electronic engineers—have enjoyed the pleasure of assembling, playing and hearing the magnificent sound of the Schober organ. Whether you favor Bach or Bop, there is a Schober organ that gives you full range of expressional and tonal quality—so like a fine pipe organ that many listeners can't tell the difference. You can build a Schober organ for as little as \$645. And—even if you've never played a note before—Schober's self-teaching courses give you immediate musical results.

Over 50% of Schober Organ owners never handled an electronic job before and didn't play a note, yet assembled some of the best organs ever designed and get a daily thrill from making their own music. Isn't it time for you to take this cost-saving road to greater musical

pleasure—and enjoy the satisfaction of doing it yourself?

**Free Information and Demonstration Recording**  
Send today for your free copy of Schober's 16-page, full color booklet, plus 7" free recording.

The Schober Organ Corp., Dept. RE-54  
43 West 61st Street, New York, N. Y. 10023

- Please send me Schober Organ Catalog and free 7-inch "sample" record.
- Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME \_\_\_\_\_


ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_



*"For what you want to spend I can sell you a black and white set in a color cabinet."*

# New **B&K** Dynamic Transistor Analyst

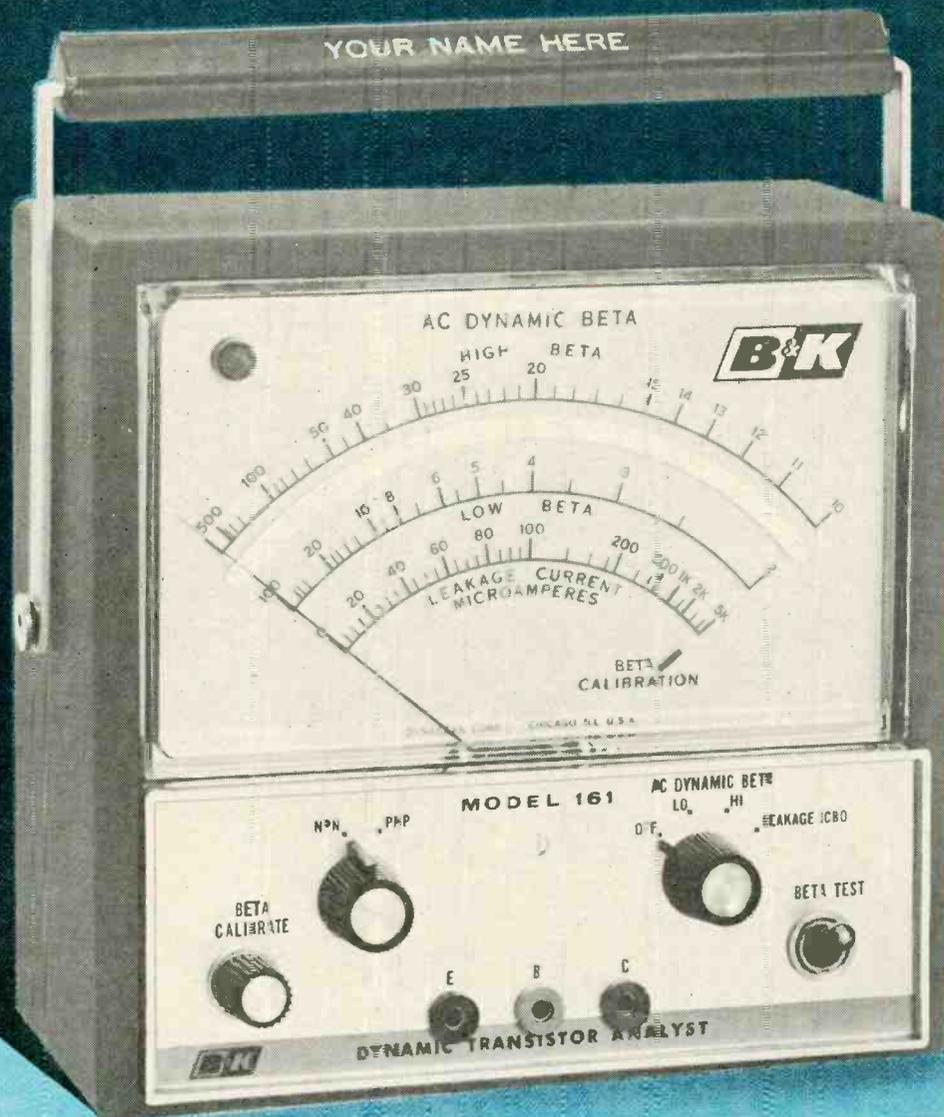

**Simple to operate... fast ... safe to use.  
In-Circuit Transistor Tester.  
Personalized for professional pride.**

B&K ends the mystery, fears and misunderstanding surrounding transistor servicing, application and theory. With every Model 161 Transistor Analyst, you get *two free reference manuals*: the new edition of Howard W. Sams' Transistor Specification Handbook, plus the all-new, years-ahead B&K Basic Course on Transistors — everything you need to know to test and service unfamiliar solid-state sets. You get ahead of your competition and stay ahead of the market.

The new B&K 161 means fast, accurate, *in-circuit* testing of transistors for AC Beta. With the same simple procedures, the 161 makes out-of-circuit tests, too, including Icbo (current leakage) and front-to-back conduction of diodes and rectifiers. There's no chance of damaging transistors or components; special circuitry protects all parts, even if leads are connected incorrectly. The huge 7" mirrored meter insures accurate readings on three separate scales. Two ranges check AC Beta: 2 to 100; 10 to 500. For leakage tests, Icbo

range is 0 to 5000 microamps on an expanded scale for better readability. A flick of the switch checks polarity. It's so simple, you don't need any set-up book.


To stay ahead of the game, get the B&K Model 161 with a scuff-proof case and the two exclusive B&K Transistor reference manuals. A complete transistor service package with all leads included and your personalized name plate — for only \$89.95.

B&K Division of Dynascan Corporation  
1801 W. Belle Plaine • Chicago, Illinois 60613



Where Electronic Innovation Is A Way Of Life

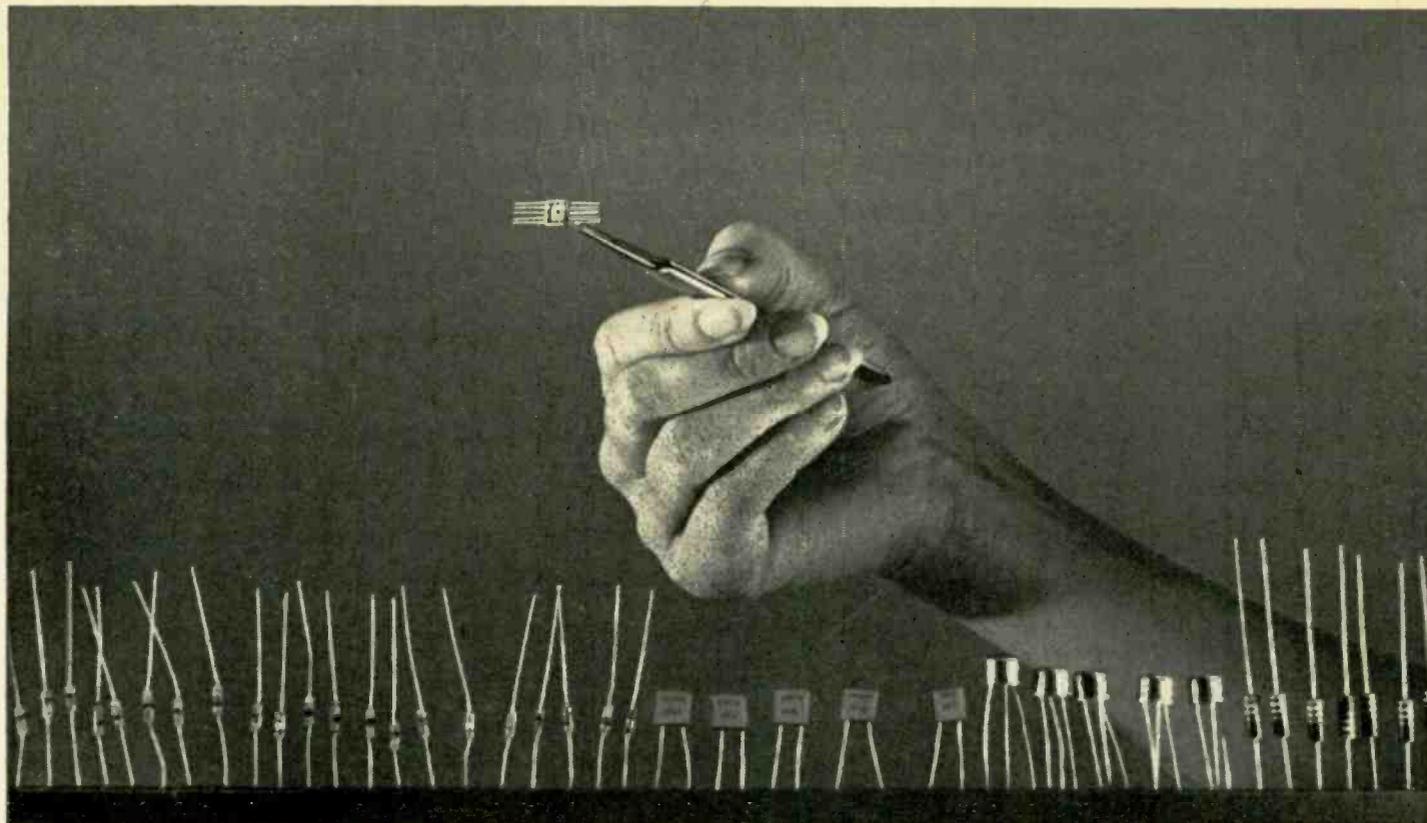Circle 23 on reader's service card  
[www.americanradiohistory.com](http://www.americanradiohistory.com)



*50 functions in a single chip. The functions of 50 separate transistors, diodes, resistors and capacitors can now be formed by the tiny dot in the center of the integrated circuit held by the tweezers.*

# The "Chip"

## ...will it make or break your job future?

THE DEVELOPMENT OF INTEGRATED CIRCUITRY is the dawn of a new age of electronic miracles. It means that many of today's job skills soon will be no longer needed. At the same time it opens the door to thousands of exciting new job opportunities for technicians solidly grounded in electronics fundamentals. Read here what you need to know to cash in on the gigantic coming boom, and how you can learn it right at home.

**T**INY ELECTRONIC "CHIPS," each no bigger than the head of a pin, are bringing about a fantastic new Industrial Revolution. The time is near at hand when "chips" may save your life, balance your checkbook, and land a man on the moon.

Chips may also put you out of a job...or into a better one.

"One thing is certain," said *The New York Times* recently. Chips "will unalterably change our lives and the lives of our children probably far beyond recognition."

A single chip or miniature integrated circuit can

perform the function of 20 transistors, 18 resistors, and 2 capacitors. Yet it is so small that a thimbleful can hold enough circuitry for a dozen computers or a thousand radios.

### Miniature Miracles of Today and Tomorrow

Already, as a result, a two-way radio can now be fitted inside a signet ring. A complete hearing aid can be worn entirely inside the ear. There is a new desk-top computer, no bigger than a typewriter yet capable of 166,000 operations per second. And it is almost possible to put the entire circuitry of a color television set inside a man's wrist-watch case.

And this is only the beginning!

Soon kitchen computers may keep the housewife's refrigerator stocked, her menus planned, and her calories counted. Her vacuum cleaner may creep out at night and vacuum the floor all by itself.

Money may become obsolete. Instead you will simply carry an electronic charge account card. Your employer will credit your account after each week's work and merchants will charge each of your purchases against it.

When your telephone rings and nobody's home, your call will automatically be switched to the phone where you can be reached.

Doctors will be able to examine you internally by watching a TV screen while a pill-size camera passes through your digestive tract.

### New Opportunities for Trained Men

What does all this mean to someone working in electronics who never went beyond high school? It means the opportunity of a lifetime—if you take advantage of it.

It's true that the "chip" may make a lot of manual skills no longer necessary.

But at the same time the booming sales of articles and equipment using integrated circuitry has created a tremendous demand for trained electronics personnel to help design, manufacture, test, operate, and service all these marvels.

There simply aren't enough college-trained engineers to go around. So men with a high school education who have mastered the fundamentals of electronics theory are being begged to accept really interesting, high-pay jobs as engineering aides, junior engineers, and field engineers.

### How To Get The Training You Need

You can get the up-to-date training in electronics fundamentals that you need through a carefully chosen home study course. In fact, some authorities feel that a home study course is the best way. "By its very nature," stated one electronics publication recently, "home study develops your ability to analyze and extract information as well as to strengthen your sense of responsibility and initiative." These are qualities every employer is always looking for.

If you do decide to advance your career through spare-time study at home, it makes sense to pick an electronics school that specializes in the home study method. Electronics is complicated enough without trying to learn it from texts and lessons that were designed for the classroom instead of correspondence training.

The Cleveland Institute of Electronics has everything you're looking for. We teach only electronics—no other subjects. And our courses are designed especially for home study. We have spent over 30 years perfecting techniques that make learning electronics at home easy, even for those who previously had trouble studying.

Your instructor gives your assignments his undivided personal attention—it's like being the only student in his "class." He not only grades your work, he analyzes it. And he mails back his corrections and comments the same day he gets your lessons, so you read his notations while everything is still fresh in your mind.


### Always Up-To-Date

Because of rapid developments in electronics, CIE courses are constantly being revised. Students re-
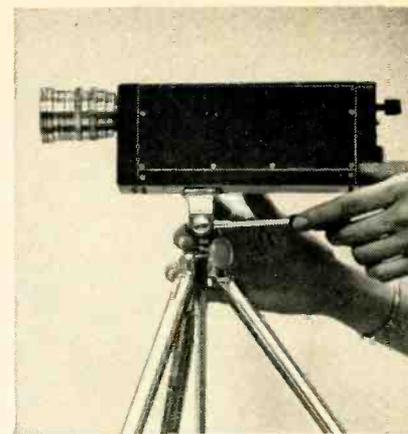
#### ENROLL UNDER NEW G.I. BILL

All CIE courses are available under the new G.I. Bill. If you served on active duty since January 31, 1955, or are in service now, check box on reply card for G.I. Bill information.

**Tiny TV camera** for space and military use is one of the miracles of integrated circuitry. This one weighs 27 ounces, uses a one-inch vidicon camera tube, and requires only four watts of power.



ceive the most recent revised material as they progress through their course. This year, for example, CIE students are receiving exclusive up-to-the-minute lessons in Microminiaturization, Logical Troubleshooting, Laser Theory and Application, Single Sideband Techniques, Pulse Theory and Application, and Boolean Algebra. For this reason CIE courses are invaluable not only to newcomers in Electronics but also for "old timers" who need a refresher course in current developments.

### Praised by Students Who've Compared

Students who have taken other courses often comment on how much more they learn from CIE. Mark E. Newland of Santa Maria, California, recently wrote: "Of 11 different correspondence courses I've taken, CIE's was the best prepared, most interesting, and easiest to understand. I passed my 1st Class FCC exam after completing my course, and have increased my earnings \$120 a month."

### Get FCC License or Money Back

No matter what kind of job you want in electronics, you ought to have your Government FCC License. It's accepted everywhere as proof of your education in electronics. And no wonder—the Government licensing exam is tough. So tough, in fact, that without CIE training, two out of every three men who take the exam fail.

But better than 9 out of every 10 CIE-trained men who take the exam pass it.

This has made it possible to back our FCC License courses with this famous Warranty: you *must* pass your FCC exam upon completion of the course or your tuition is refunded in full.

### Mail Card For Two Free Books

Want to know more? The postpaid reply card bound in here will bring you a free copy of our school catalog describing today's opportunities in electronics, our teaching methods, and our courses, together with our special booklet on how to get a commercial FCC License. If card has been removed, just send us your name and address.




# CIE

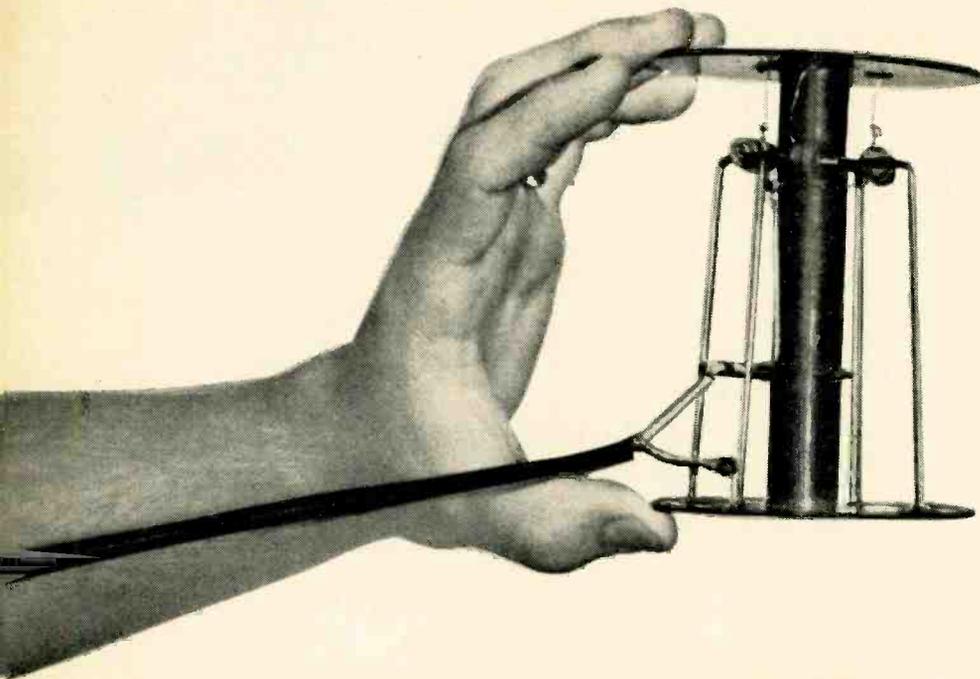**Cleveland Institute of Electronics**

1776 E. 17th St., Dept. RE-45, Cleveland, Ohio 44114

Accredited Member National Home Study Council  
A Leader in Electronics Training... Since 1934





# BUILD A MINI-TENNA

By JAMES A. GUPTON, JR.

Here's a construction project designed around one of the most controversial recent developments in electronics—the *Subminiature Integrated Antenna*, or SIA. You can build it in less than an hour, for only a few dollars. And you'll be learning something about the latest state-of-the-art development in antennas.

## Background of SIA

In the spring of 1967 a new military communications development was revealed.\* Researched and built by the US's Edwin M. Turner and Germany's Dr. Hans Meinke, the SIA was branded with an astounding claim—only 1/50 wavelength long, it can perform as well as a conventional quarter-wavelength model.

Normally, a small antenna (with respect to wavelength) has little capture area, hence doesn't pick up much rf signal. Thus gain is low and the antenna is inefficient. At frequencies above about 30 MHz, moreover, the signal-to-noise ratio of a small antenna is poor. Generally, then, an antenna should be a quarter-wavelength or

longer in size to provide a clean signal.

In the SIA, transistors are connected *directly* to antenna elements. Thus the transistor multiplies the rf current in the antenna element by a factor equal to the gain of the transistor. Another way of looking at the situation: In a passive (conventional) antenna, resonant frequency depends solely on element length (unless electrically altered by inserting capacitance or induc-

used is a low-impedance device, an SIA usually needs no special matching circuit to drive coaxial cable directly.

Some antenna engineers, however, question the value of SIA. The same results could be obtained, they say, by using an ordinary passive antenna with a booster. Transistor noise levels, they note, can also limit performance of the SIA. And no study has been made of crossmodulation in the new device.

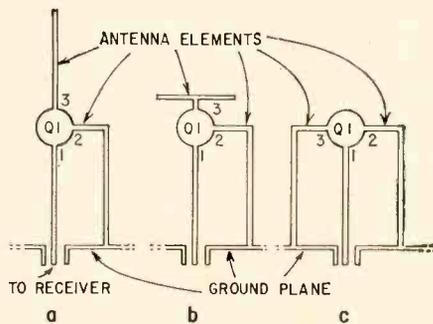


Fig. 1—Secret of SIA is that transistor becomes integral part of antenna.

tance). But the SIA's transistors *lower* the resonant frequency. They also make the frequency response quite broad, so a few inches of wire will have good response.

Its developers claim that the SIA can operate over a wide frequency band—from a ratio of 2:1 to perhaps 50:1. Because the bipolar transistor


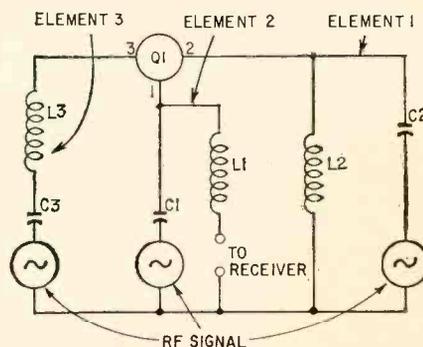


Fig. 2—Equivalent circuit of SIA's shown in Figs. 1-a and 1-b. RF signal is picked up by all antenna elements.

The controversy grew when some predicted a 2-inch-long SIA for home TV receivers would obsolete rabbit ears and rooftop antennas. But it mustn't be overlooked that the tiny antenna was developed for military use

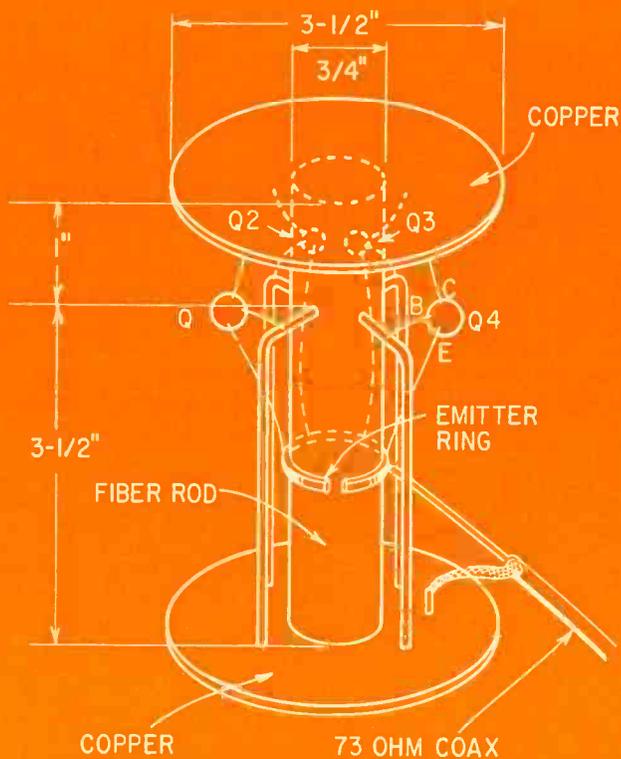
\* See "Major Antenna Breakthrough?" in News Briefs, RADIO-ELECTRONICS, July 1967.



*New experimental antenna blends solid-state elements with conventional skywire in new approach.*

*Fig. 5—(left) Construction uses capacitance of top and bottom "hats" for wide frequency response.*


*Fig. 6—(below) Diagram shows dc and mechanical circuit, but not distributed capacitance and inductance.*

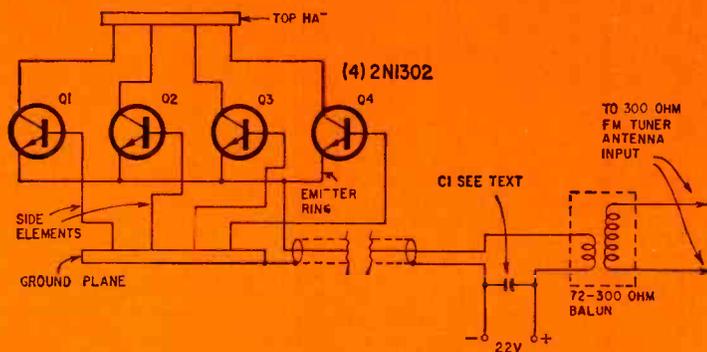

where large antennas simply can't be used and where some inefficiency must be tolerated.

### How It Works


The simplest form of an SIA is merely a transistor connected to antenna elements in any one of three basic forms (Fig. 1). The ground plane is connected to one side of the lead-in,

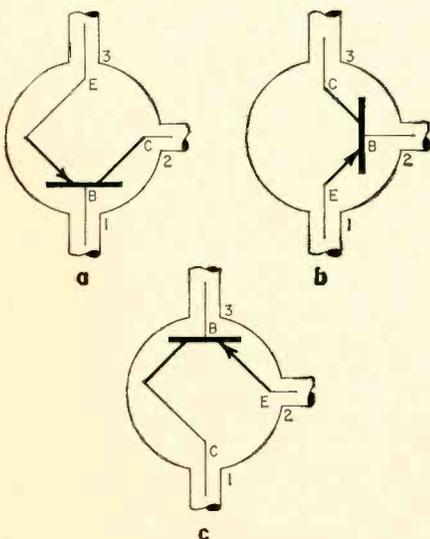

*Fig. 3—Three transistor elements may be connected three ways in the SIA.*

and a transistor lead to the other side.

In Fig. 2 you can see the equivalent circuit of antennas B and C of Fig. 1. Generator symbols represent the rf signal picked up by the three antenna elements. Distributed capacitance and inductance are shown, as well as the transistor and the lead-in terminals. Note that antenna elements 1 and 2 form loops, and respond to the magnetic rf field. All three elements

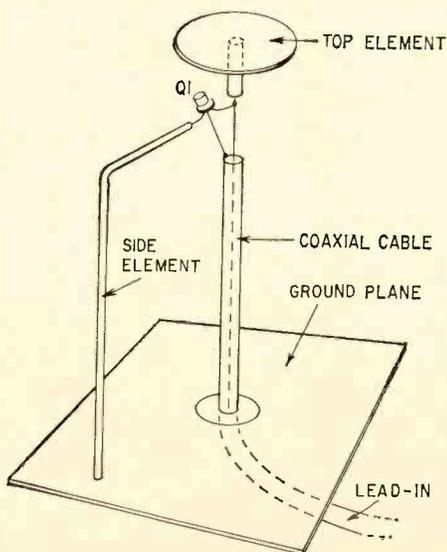

*Fig. 4—Developmental version of SIA shows practical method of connections.*

respond to the electric field.

There are also three ways to connect a transistor to the antenna elements (Fig. 3). The emitter-base lead-in connection (B) seems the most likely to match low-impedance coaxial cable and receiver inputs. A practical model of this antenna might look somewhat like Fig. 4.

### FM Mini-Tenna

My choice for an experimental model of an SIA was what I call a Mini-Tenna, for it stands only 4½ inches high and is 3½ inches in diameter.

You can see the simple construction in Fig. 5. A ¼-inch-diameter fiber rod forms the main support (you can also use Lucite, wood or any nonconductor here). At each end of the rod is a 3-inch-diameter round piece of copper-clad print board (a piece of sheet metal will do)—one forms the top hat, the other the ground plane. The copper sides of the boards face inward. Four lengths of No. 10 copper wire form the side elements, and another section of wire forms the emitter ring.

The electrical circuit, shown in Fig. 6, is just as simple. *Not* shown here are the distributed capacitances and inductances in the metallic elements. Battery bypass capacitor C1 is merely a

gimmick with a value of a few picofarads. You can solder a short piece of hookup wire to each battery terminal, then twist the insulated ends together to form the gimmick.

Mini-Tenna's dimensions are cut to about 1/35 wavelength (at 100 MHz). I tried a 1/50-wavelength model, but the present antenna performs better. Since the antenna isn't

sharply resonant, but is broad-band, exact dimensions don't seem too important. In fact, the larger the antenna, the more capture area, and the more signal.

## Mini-Tenna Performance

Two RADIO-ELECTRONICS editors borrowed author Gup-ton's small antenna to evaluate its performance. Their reports follow.

I compared the Mini-Tenna pickup capability with that of a dipole. The reference antenna was a 50-inch, 72-ohm open dipole, gamma-matched to 72-ohm coaxial cable. I oriented the dipole horizontally, north-south, and placed it 7 feet above the floor of my ground-floor apartment in Manhattan, at a location where the field intensity of the stronger local FM stations is approximately 250 to 500 mV/m.

The coax was fed through a 72-to-300-ohm balun into my mono Eico HFT-90 FM tuner. In the tuner, the age network was disabled and all stages run at constant gain. The limiter grid voltage was monitored by a Heathkit IM-25 solid-state vom with 11 megohms input resistance. This monitored dc grid voltage was then essentially proportional to received signal intensity.

First I made a control run, measuring limiter grid voltage for signals from 14 local FM stations. Later measurements were plotted against this reference run.

Next I physically removed the dipole from its mounting at the end of the coax, and inserted a 4½-inch stub of wire in the coax plug; I oriented the wire vertically. The stub represented the Mini-Tenna reduced to the bare minimum. By remeasuring the same 14 FM stations, and plotting the differences against the reference dipole readings, I got curve (A) (see graph).

Then I mounted the Mini-Tenna in place of the wire stub—at the same point the dipole had been. With a 22-volt battery and a bypass capacitor in place, the "active" curve (B) was obtained. Next I removed the battery and placed a jumper across the break in the coax shield; this produced "passive" curve (C). Finally, all transistors were removed from their sockets and a short jumper was placed between the emitter ring (at the point where the coax ties to it) and the top hat. This gave curve (D), or "shorted."

As the graph indicates, there seems little difference in the pickup of the wire stub, the shorted or passive Mini-Tenna. It appears that the mass of metal in the Mini-Tenna, as well as

the unpowered transistors themselves, contribute little or nothing to signal pickup.

The active Mini-Tenna, however, seems to produce some significant improvement over the other modes of operation. It hasn't the pickup of a dipole, but it did produce fully quieted signals on local stations. The Mini-Tenna seems essentially nondirectional, but this might or might not be an advantage in metropolitan receiving locations. I did not evaluate this antenna for stereo.—Thomas R. Haskett


I found the Mini-Tenna to have no discernible effect (good or bad) on stereo FM reception at my apartment in Brooklyn. Presumably the broad-band character of the antenna makes it frequency-flat and phase-flat over the

necessary range of frequencies, so that stereo separation isn't affected.

However, like all more-or-less omnidirectional antennas, this one may intercept delayed reflections of signals just as well as it intercepts the direct signal from the transmitter; hence it may give distorted reception or poor separation on some FM stereo stations.

Signal strength was higher with the battery jumper open than with it closed (when the battery was not used). The gimmick had no noticeable effect. A 0.001-μF disc ceramic bypass capacitor connected in place of the jumper had the same (negative) effect as closing the jumper. (The reactance of 0.001 μF at 100 MHz is approximately 1.5 ohms.) This suggests that the gimmick has no significant bypassing effect. I estimate its reactance (100 MHz) at 1000-2000 ohms—vastly greater than the impedance of the battery or that of any other component in the system.

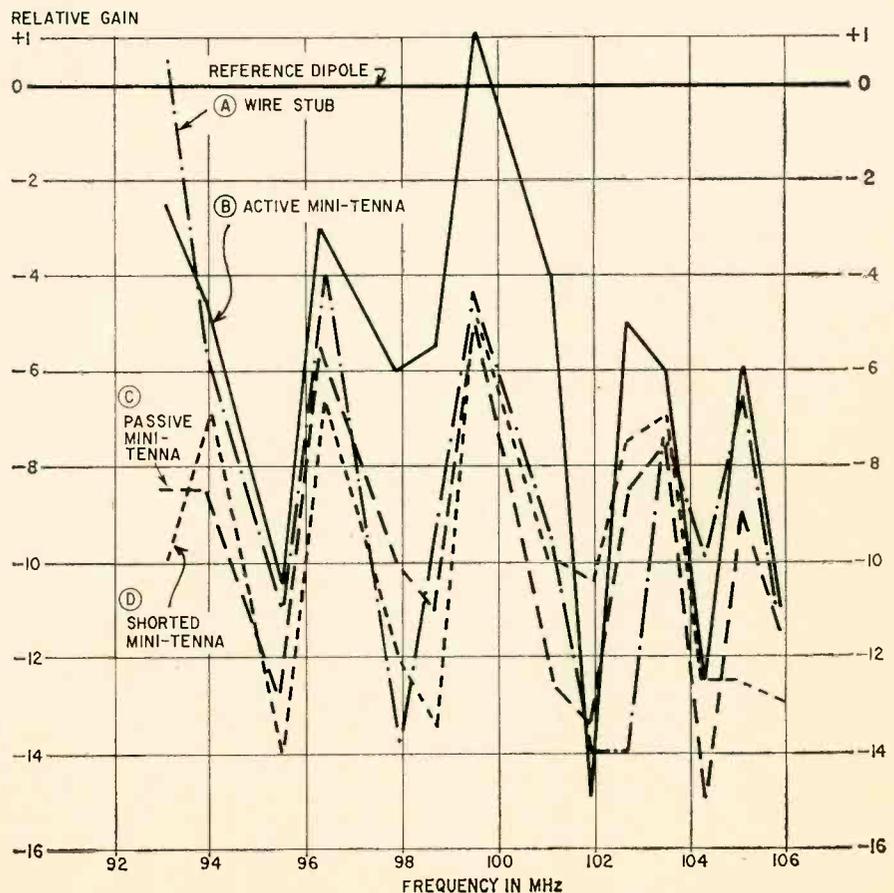In short, the Mini-Tenna seems to perform about as well as a small piece of wire.—Peter E. Sutheim R-E



Response curves of Mini-Tenna vs reference dipole.

# Update Your Solid-State TV Servicing

Increased popularity  
of transistor TV  
receivers demands  
solid know-how

By MATTHEW MANDL

SERVICE TECHNICIANS ARE ALREADY familiar with some solid-state repair because transistor radios and hi-fi amplifiers have been with us for some time. You yourself have probably run across a few transistor circuits in hybrid TV sets and have had some experience with transistor portables.

In contrast to what they do in radios and hi-fi amps, solid-state circuits in TV must handle high-frequency video signals, pulse signals and sweep waveforms. TV troubles are often more complex. It is vital to follow certain precautions in solid-state servicing, not only to cut down on repair time, but to prevent damage to transistors.

To do an A-1 job in solid-state TV repairs we must also keep in mind the bias relationships between pnp and npn transistors. When we look at a manufacturer's schematic, the bias voltages don't always seem to follow textbook rules. We can best learn how to reconcile theory and practice by re-

tor, but since reverse bias is necessary, the collector is made negative. These bias relationships are shown in Fig. 1-a, where +2 volts is present at the emitter, -3 volts at the base, and -10 volts at the collector.

For the npn, shown in Fig. 1-b, the first two letters np denote that forward bias means negative emitter and positive base. The final n for the collector indicates, as before, that the collector-base junction would be forward biased with a negative voltage on the collector; but since that junction must be reverse-biased, it gets a positive voltage. If you apply forward bias between emitter and base as well as between base and collector, the transistor will burn out. It will conduct too much current.

Fig. 1-c is a typical video i.f. stage of a solid-state TV receiver (Sylvania AO4-1,2 chassis). Here it *appears* that our rule does not hold, because the emitter is positive. Actually, the rule is still followed because the emitter is negative with respect to the base by 0.8 volt, because the base is more positive than the emitter, making the emitter negative with respect to the base. If you read a voltage at test point 1 as shown, the reading is +2.3 volts.

At test point 2, however, we would read 0.8 volt, with the minus probe at the emitter as shown. Thus, test point 2 is the place to read the actual forward bias on the transistor. Reading from emitter to ground would show +1.5 volts, which is not the true bias. Collector voltage can be read from collector to ground as shown at test point 3, but if the reverse bias is to be checked the reading must be taken between emitter and collector. For this case it would be 6.5 volts.

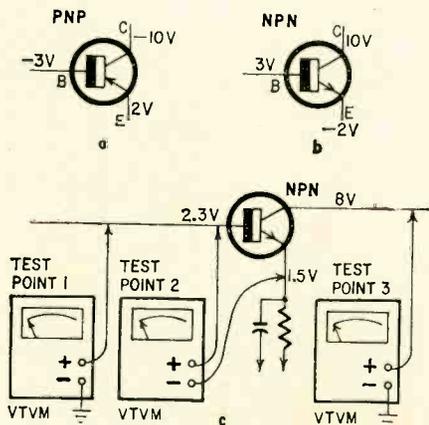


Fig. 1—Getting straight this matter of transistor bias voltages. It's easy.

examining bias rules and relating them to an actual TV circuit. Later, we'll examine some servicing procedures.

The rule for class-A amplification in any transistor is *forward bias between emitter and base, and reverse bias between emitter and collector*. This holds for either the pnp or npn. If it's a pnp, the first letter p indicates a *positive emitter*, the second letter n a *negative base* and hence forward bias. The final letter p relates to the collec-

## Practical matters

In Fig. 2 the complete three-stage i.f. section of the Sylvania receiver is shown. A number of factors must be considered when servicing or checking such stages besides the bias testing just described. Often the transistor types are not given in the schematic, only the manufacturer's part number. Just because each stage performs the same

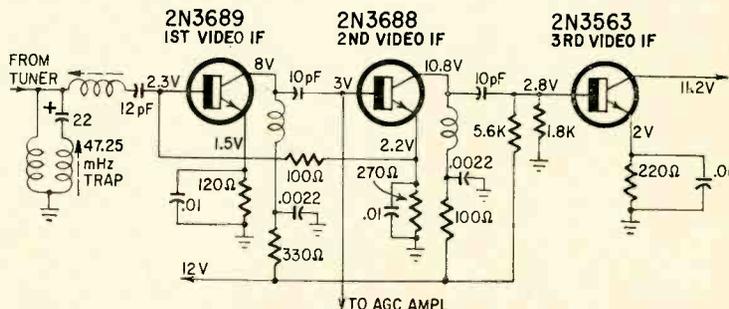


Fig. 2—Video i.f. stages from a Sylvania AO4-1. Note untuned, capacitive coupling between stages. Leakage in coupling capacitors can overbias the following stage.

function, don't assume the transistors are alike. Note the different types used for each stage in Fig. 2 to take care of gain and bandwidth considerations. When replacement is necessary, make sure you use an exact replacement.

When replacing transistors make sure the set's power is off. In i.f. stages, clip the transistor leads to the same length as the originals to maintain the same lead inductance. When soldering, hold the transistor lead with long-nose pliers to absorb excessive heat. Make sure terminals are clean and solder as fast as possible while still making a good joint. This is particularly important when the transistor is mounted on a printed-circuit board. Avoid excessive heat to prevent damage to both the transistor and the printed wiring.

If a transistor is found to be defective, check associated parts to make sure they are not the cause. Transistors often can't take even moderate overloads. Even test equipment which is not

and video signals are lost. The collector resistor will also heat up—a sure clue to a shorted capacitor or possibly a transistor.

Generally resistors give little trouble, though routine checks should be made when circuit troubles are evident. Make voltage checks first and, if a resistor is suspected, unsolder one end and take an accurate ohmmeter reading. When making voltage checks with power on, set contrast and brightness at a minimum unless otherwise specified in the manufacturer's notes.

### Scope tests

Too many service technicians still do not use their scopes enough in troubleshooting. Either they don't understand the scope or they feel it's too much trouble to set up. But a scope can save you so much time and pinpoint troubles so precisely that it's foolish not to use it. You are practically

in Fig. 4 and is a typical sawtooth signal. For this set the waveform should be 7 volts peak-to-peak. More than a ½-volt difference indicates a decrease from normal stage gain.

Because direct coupling is used, the only capacitors are those involved with the linearity-control feedback loop. Hence, low gain is often caused by a defective driver transistor.

Insufficient vertical oscillator signal could, of course, be a contributing factor. Thus, a scope reading should be taken between the base of the vertical driver and ground. The peak-to-peak voltage should be approximately 3.2. The waveform would be opposite in phase to that shown in Fig. 4.

### Scope measurements

A good scope accurately calibrated to read peak-to-peak voltages is very helpful for signal waveform observation and voltage measurements. A poor scope may suffice for signal tracing, where the absence of presence of the signal is all we need to check. For pulse and sawtooth waveforms, however, the high-frequency signal components will be diminished in a scope having poor response, and the waveform will then be distorted.

Note the waveform shown in Fig. 5, taken with a scope having poor response. The long, sloping trace (sawtooth sweep) has a long rise time and hence shows up well on this scope. The sudden drop from the high to the low level, however, is too fast and the scope is unable to respond as well; hence the trace is fuzzy compared with that of Fig. 4. Also, note the presence of the scope's retrace line in Fig. 5, which can be blanked out on better scopes as shown in Fig. 4. The sawtooth scan in Fig. 5 shows some traces of nonlinearity in the upper portion and you're never sure, with a cheap scope, whether this is in the TV circuit or in the scope. (The number of cycles shown depends on the setting of the scope's horizontal frequency control.)

The horizontal driver and output stages of the Magnavox T021 receiver are shown in Fig. 6. This set uses a 9XP4 picture tube and is all solid-state. Note the low voltage (−11.6) at the damper collector, compared to the high boost voltages in tube dampers. Where normally we would not take scope readings on the horizontal output section of a tube-type receiver, we can safely take readings on the solid-state units. A scope pattern taken at the emitter of the horizontal output transistor is shown in Fig. 7. It should have an amplitude of 80 volts peak-to-peak on your scope.

In making voltage checks on these circuits, note that the driver and

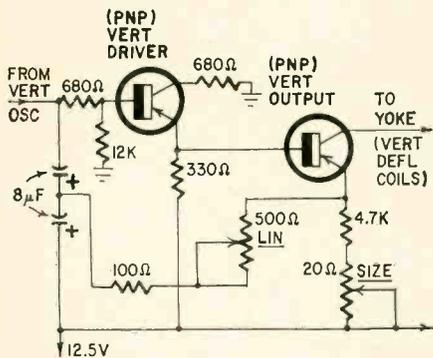


Fig. 3—Vertical sweep amplification in Motorola TS-460. In direct-coupled circuits like this one, excessive leakage or a short in one transistor will often affect voltages around the other and destroy it.

well isolated from the power line can ruin a transistor.

Forward bias can be upset by a leaky coupling capacitor between the collector of one stage and the base of another. Note the third i.f. stage in Fig. 2, for instance. Here the emitter is +2 volts and the base +2.8, providing a forward bias of 0.8 volt. If the 10-pF coupling capacitor is leaky, some of the 10.8-volt collector potential can get to the base and increase forward bias.

Increased forward bias on a transistor increases current flow and can cause overloading. Read the voltage between base and emitter. If it is more than 1 volt when the schematic calls for 0.8, check parts for defects.

Note the 0.0022-μF decoupling capacitors across the series resistors in the collector circuits. If these open, signal cross-coupling between stages can occur with consequent oscillations. This can cause interference lines on the screen. If these capacitors short, the collector voltage is shorted to ground

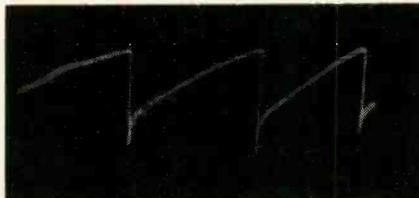


Fig. 4—Correct vertical driver pattern for the circuit described in Fig. 3.

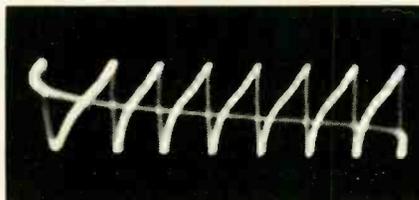


Fig. 5—Cheap scopes often produce fuzzy patterns with prominent retrace lines, especially at higher frequencies and with high horizontal-sweep rates.

working blind if you don't use it.

Take the case of sweep drivers in most solid-state TV sets. These drivers or amplifiers are used between the sweep generators and the output stages. It is important that they provide sufficient gain, or height and width will suffer. If trouble is suspected it is much easier to take a scope reading than to check components and transistors. If the peak-to-peak waveform voltage is below the recommended value, much time is saved in pinpointing the defective stage.

A typical vertical driver circuit is shown in Fig. 3 (Motorola TS-460 chassis). Here an emitter-follower circuit is used, directly coupled to the vertical output stage. Since the collector is not bypassed, however, it makes a good check point for the scope connection. The waveform obtained here is shown

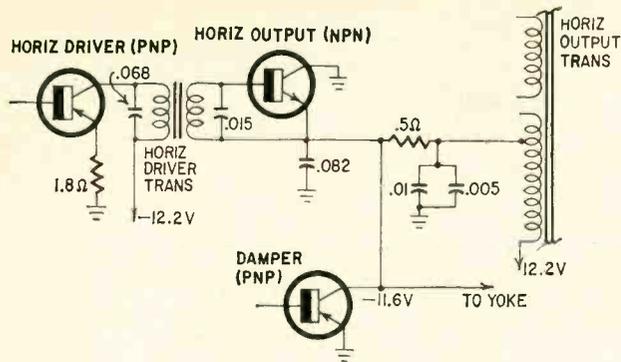


Fig. 6—Magnavox T921's horizontal output. Maximum peak-to-peak voltages in this circuit range around 80, and are perfectly safe to measure with ordinary instruments. Note the pnp driver and damper versus the npn output transistor.

damper transistors are pnp types and the horizontal output is an npn type. For this receiver the positive potential is at ground level, hence the emitters of the driver and damper have the proper polarity. For the output transistor emitter, however, we have a common minus-voltage linkage between it and the collector of the damper. To check the amount of drive, observe the peak-to-peak waveform at the collector of

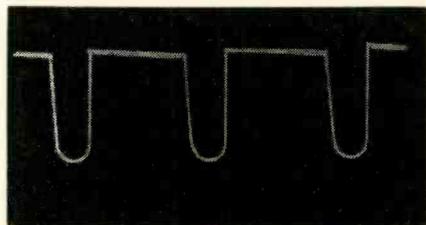


Fig. 7—A scope at the emitter of the horizontal output transistor in Fig. 6 should show the above waveform when the circuit is operating in a normal manner.

the driver. The correct potential should be 20 volts peak-to-peak.

Because of the direct coupling, horizontal-output transistor troubles can affect the damper circuit and vice versa. Both transistors should be checked if troubles are evident.

Because of their low impedance, the sweep output transistors can be connected directly (or via a capacitor) to the deflection coils without transformers. In the horizontal system the transformer is used only to generate the high voltage for the picture tube.

When replacing any power transistor, apply silicone grease to the mica insulator and the bottom of the replacement transistor. Without the grease the thermal resistance of the heat sink increases and the transistor may overheat and have a shorter life.

When servicing any transistor circuits, don't bridge a suspected capacitor with another capacitor while the set is turned on. When you shunt one capacitor with another you can damage a transistor easily because of the surge voltages set up in the circuit. This practice, even in tube sets, will tell you only if a capacitor is open. If a capaci-

tor is shorted, shunting it with another is of no help.

### Low-voltage troubles

In some solid-state TV receivers elaborate precautions are taken in the low-voltage supply to keep it steady. This assures constant bias for transistors even with line-voltage variations.

A typical system is shown in Fig. 8. It is used in the General Electric TC

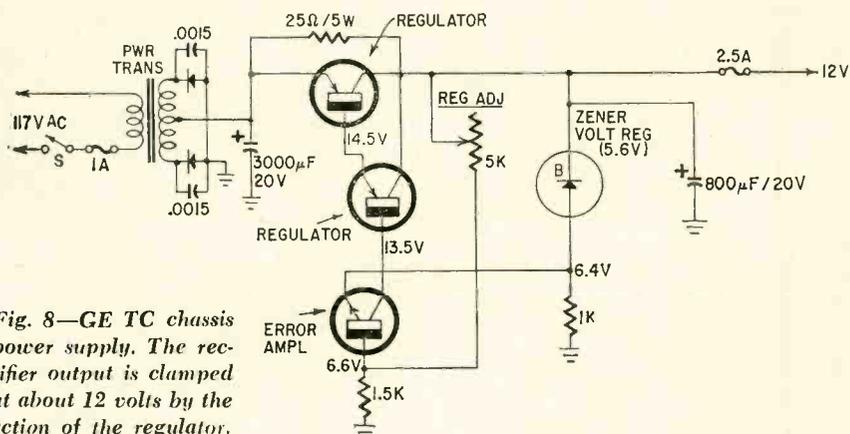


Fig. 8—GE TC chassis power supply. The rectifier output is clamped at about 12 volts by the action of the regulator.

chassis receiver. (The same principles are also used in the Westinghouse V-2483-1 chassis and the Zenith 1M30T20 chassis.) Three transistors supplement the Zener-diode voltage regulator. This voltage-regulation method is particularly useful in sets which combine line-voltage input with battery-charger facilities.

The top regulator transistor acts as a dynamic resistor in series with the load and regulates current flow. The resistance of this transistor is controlled by its bias voltage which is developed across the other regulator transistor (preregulator). The preregulator in turn is controlled by the error amplifier. The error amplifier senses the voltage drop across the 1000-ohm resistor, and makes the system responsive to small changes.

(Note that the emitter of the error amplifier is connected to the junction of the 5.6-volt Zener diode and the 1000-ohm resistor. These two components act as a voltage divider across the output which is to be regulated.

Any variation in the voltage on this line varies the current flowing through the divider. The voltage drop across the Zener is constant at 5.6, this in effect, puts the full error voltage across the resistor.)

An increase in voltage either at the source or due to a lighter load tends to increase the voltage drop across the 1000-ohm resistor. This puts a more positive voltage on the emitter of the error amplifier in opposition to its forward bias and effectively increases its dynamic resistance. The higher voltage developed across the error amplifier increases the voltage on the base of the preregulator which tends to cut down its current flow (effectively increasing its dynamic resistance) and increases the positive voltage applied to the base of the top regulator and tends to "pull" the output voltage down to normal. A lower than normal voltage at the source or the output will cause a reverse action. The Regulator

Adjust Control sets up the center of operations for this solid state voltage-divider network.

When replacing a defective Zener, make sure you wire it in with the same polarity as the original, and that it has the same voltage rating as the original. The replacement can be of larger wattage, but must have the same voltage rating as the original.

In Fig. 8 the 5000-ohm potentiometer sets the bias voltage for the error-amplifier transistor by increasing or decreasing the voltage drop across the 1500-ohm base resistor. As this voltage is raised it approaches that of the emitter and decreases bias. If any regulator transistor is replaced, set the regulator adjustment control for the voltages specified by the manufacturer.

For the General Electric set shown, the base of the error amplifier should have 6.6 volts, and the emitter 6.4 volts. If the other regulating transistors are all right, 13.5 volts should appear at the base lead of the lower

(continued on page 93)

# Pulses and Pulse Circuits You Should Know

Differentiate and integrate to keep in sync

By **ROBERT G. MIDDLETON**

ANYONE SERIOUSLY INVOLVED WITH electronics should be vitally concerned with pulsed circuit action. Unfortunately, many technicians are hampered by an incomplete or inaccurate understanding of pulses and pulse-forming circuits. For example, the pulse voltage in Fig. 1 produces zero reading on a dc voltmeter, in spite of the fact that the positive-peak is greater than the negative-peak voltage. The reason is simply that the pulse waveform contains equal quantities of positive and negative electricity (current  $\times$  time). Since a dc voltmeter is a current instrument—albeit a *small-current* instrument—the equal positive and negative quantities cancel each other and give a zero reading.

### Polarity reversal of a pulse

When a "positive" pulse is passed through an amplifier stage (a video amplifier, for example) it becomes a "negative" pulse (Fig. 2); a sine wave passed through a similar amplifier

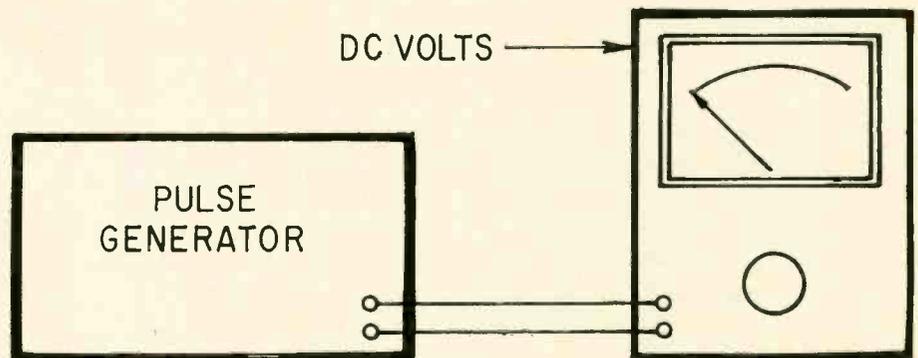
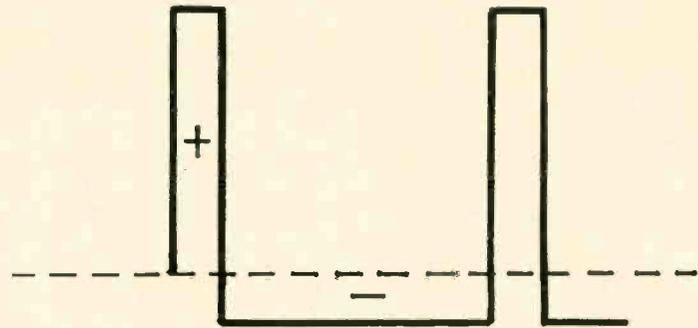


Fig. 1—Since a dc voltmeter actually reads average current, the pulse shown will cause no indication on the meter . . . average dc voltage and current is zero.



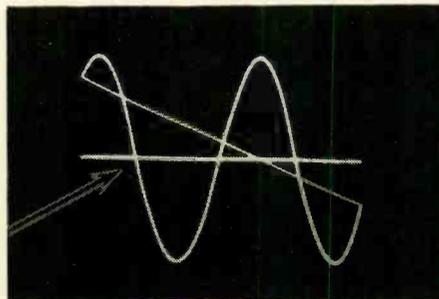
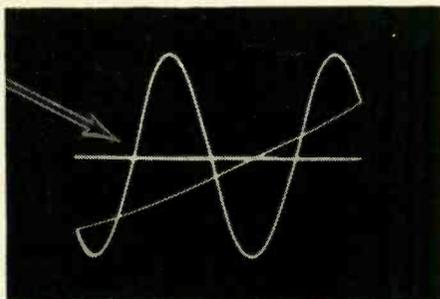
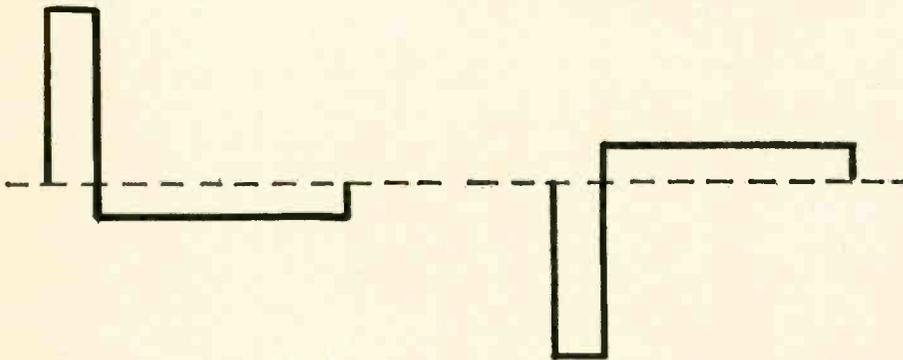


Fig. 2—Waveforms, whether pulses or sine waves, are inverted by an amplifier stage. The terminology, however, is different for the two types of waves.

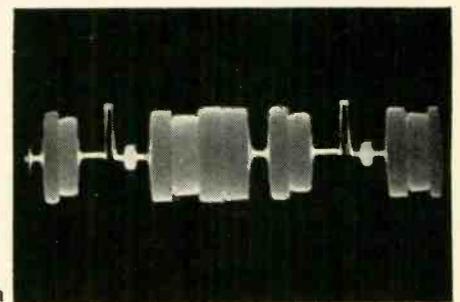

a

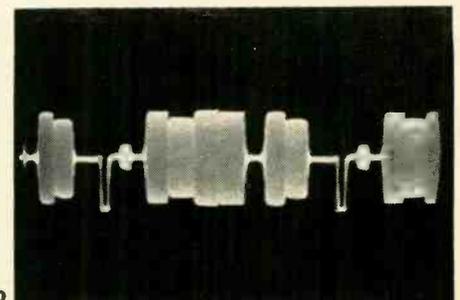

b

Fig. 3—Color-bar video waveform in positive (a) and negative (b) modes.

stage is shifted in phase  $180^\circ$ . These two facts are equivalent. The sine wave also can be regarded as being inverted in polarity. Since both half-cycles of a sine wave are symmetrical, however, one half-cycle is not distinguishable from another. The amplifier action is thus described as a  $180^\circ$  phase shift.

Polarity reversal of a complex waveform is illustrated in Fig. 3, the examples taken from a color-bar generator provided with a video-polarity switch. When the switch is in the positive position, the horizontal-sync pulse is positive (Fig. 3-a). When the switch is thrown to the negative position, the sync pulse is negative (Fig. 3-b). The chroma bars (blocks of 3.58-MHz sine waves) come after the color burst signal which comes after the sync pulse.

What really happens when we pass a chroma-bar signal through a stage of amplification? Recalling the sine wave of Fig. 2, we'd expect the 3.58-MHz sine waves to be shifted  $180^\circ$  in phase. This means that  $R - Y$  will be changed to  $-(R - Y)$ , and  $B - Y$  will be changed to  $-(B - Y)$ , etc.

The color burst has the  $-(B - Y)$  phase. Hence, if the color burst is

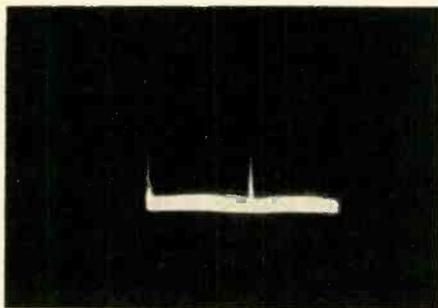


Fig. 4—Narrow vertical pulses appear dimly on the screen of a service scope.

passed through a stage of amplification, it changes to the  $B - Y$  phase. Note that the burst is a complex type of pulse waveform having a complete envelope. This results from a sine wave of the  $-(B - Y)$  phase being modulated by a pulse which has the same width as the horizontal-sync pulse. The chroma-bar signals also form pulse envelopes, but the modulating pulses are wider than a horizontal-sync pulse.

#### Display of pulse waveforms

The horizontal-sync pulses of Fig. 3 are clearly visible, primarily due to the comparatively slow rise and fall time of the sync pulse and the appreciable width of the pulse. On the other hand, consider the pulse in Fig. 4. This pulse, generated by a white-dot generator, has a fast rise and fall, and the pulse is also comparatively narrow. As a result, it can be displayed only with difficulty on the screen of a service-

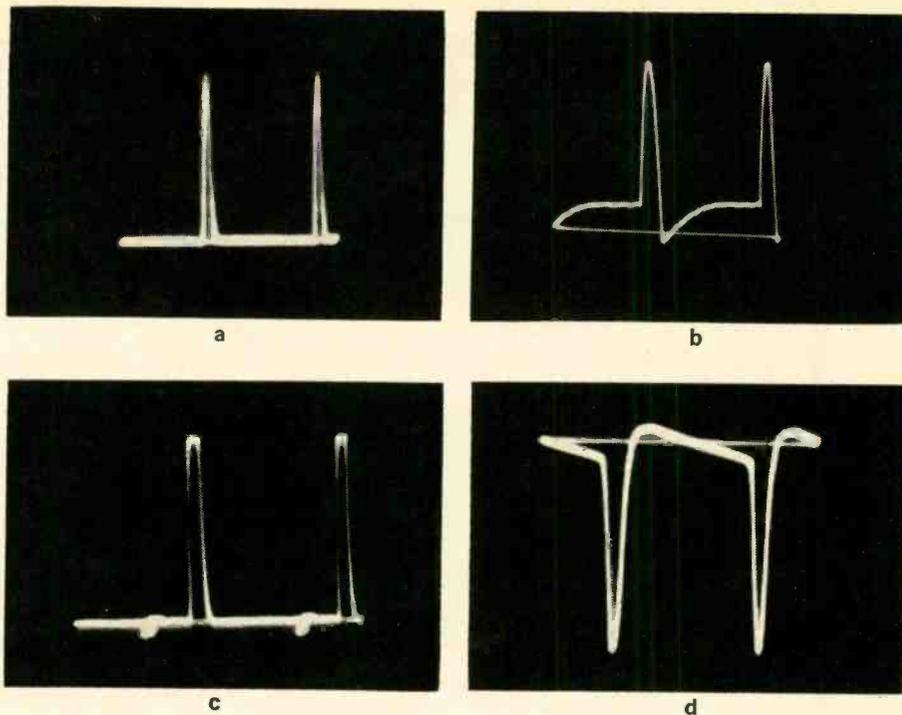


Fig. 5—These various waveforms may all be properly classified as true pulses.

scope—the vertical deflection of the beam is so rapid that the pulse is quite dim. In some cases, a white-dot pulse is so narrow that it is completely invisible in the scope pattern, and it could be falsely concluded that the generator was not supplying pulses.

To display very narrow fast-moving pulses satisfactorily, you need to use a lab-type scope. Lab scopes also have

beam-unblanking circuitry which intensifies the relative brightness of the pulse.

#### Pulse classification

Some familiar waveforms are clearly classified as pulses, while analysis of others can be difficult. For example, there is no hesitation in describing the waveforms in Fig. 5 as pulses. Although three of the photos exhibit un-

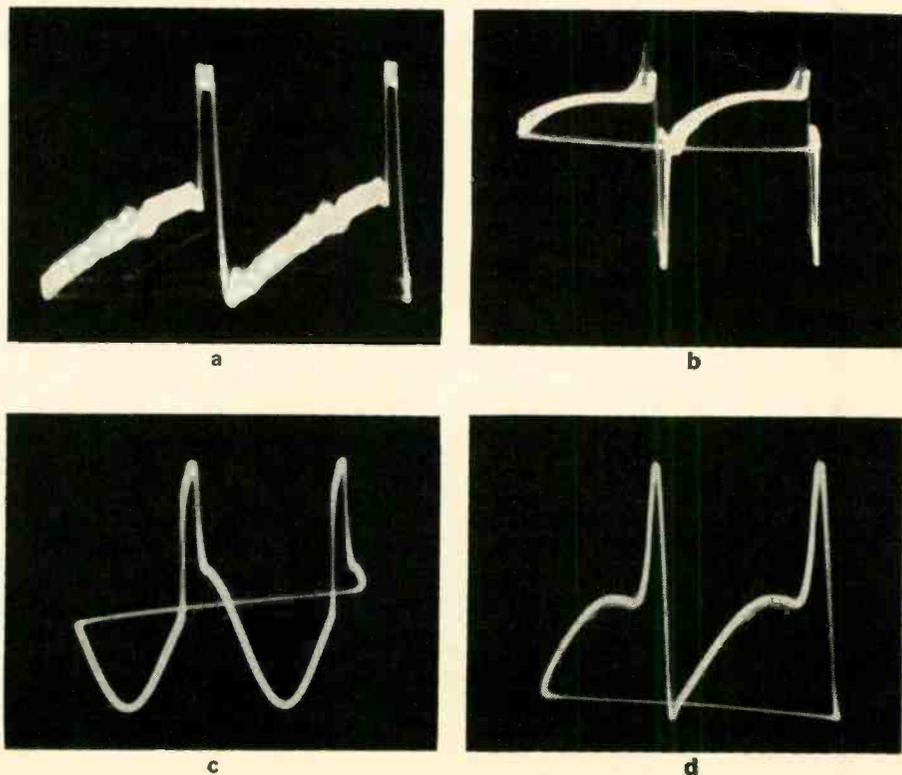


Fig. 6—These waveforms may be regarded either as pulses or as complex waves.

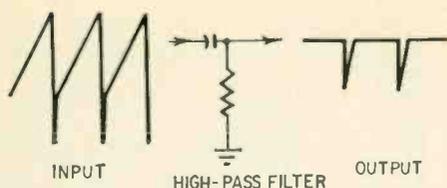


Fig. 7—Differentiator passes only high-frequency harmonics of peaked sawtooth.

even base lines, the pulse component in each waveform is dominant and unmistakable. The base lines could be described as sloping in Figs. 5-b and -d.

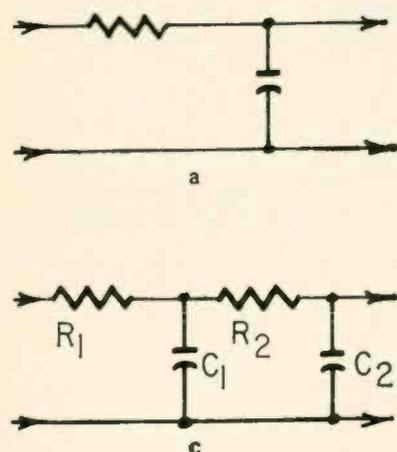


Fig. 8—When low-pass filters are used with pulses, they build up a waveform.

In Fig. 5-c, an irregularity can be noted in the base line. On the other hand, the waveforms illustrated in Fig. 6 can be called pulses only when the pulse component is of chief concern. Otherwise, they will be termed complex waveforms.

The waveform in Fig. 6-a is fully described as a peaked-sawtooth wave. You could also include mention of the residual video signal riding on the sawtooth component. Again, the waveform in Fig. 6-c is fully described as a pulse-and-sine wave: you could also state that the pulse appears near the positive peak of the sine wave. Distorted peaked-sawtooth waveforms are shown in Figs. 6-b and -d.


In each of these waveforms, the pulse has a certain amplitude relative to the sawtooth or other portion of the waveform. Furthermore, the peak-to-peak voltage is tied closely with circuit action. For example, a sync clipper does not operate as intended unless the input waveform has a peak-to-peak voltage that lies within certain specified limits.

### Waveshaping circuits

To change a peaked-sawtooth waveform into a pulse (differentiate), a high-pass filter is used. A simple differentiating circuit is shown in Fig. 7.

The pulse component of the waveform contains harmonics much higher in frequency than the sawtooth component itself. Hence, when suitable values of capacitance and resistance are chosen, the pulse is passed and the sawtooth is rejected. The simple RC configuration works best for peaked-sawtooth waveforms having comparatively narrow pulses.

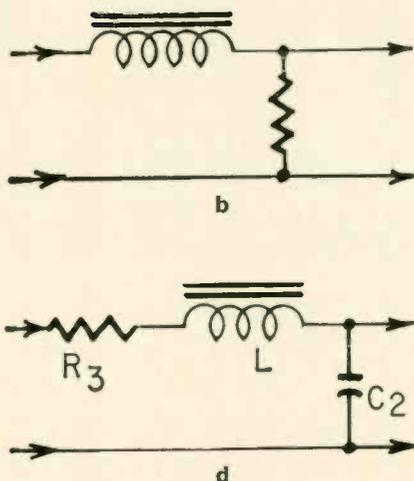Low-pass filters also are used as waveshaping circuits; Fig. 8-a shows a single-section RC integrating circuit. Integration is a process of addition or



accumulation, and requires a storage device such as a capacitor. In a TV set the 60-Hz sync pulse is developed by a

series of 6 relatively wide square wave pulses transmitted between the equalizing pulses in the composite video signal. The low-pass filter type of action prevents the relatively short duration pulses from building up a signal voltage at the output of the integrator. Figure 8-c is a 2-section network.

Another possible integrator circuit configuration is shown in Fig. 8-d. However, this circuit may not always work.

The RL circuit of Fig. 8-b is also an integrating circuit; if you choose suitable values of R and L, it offers the same waveshaping action as Fig. 8-a.

Practical difficulties in specific cases are due to the distributed capacitance of coil windings, which makes coils self-resonant at some frequency. If the input waveform contains strong harmonics near the resonant frequency, the output waveform will be distorted. Not only will the waveshape be different than anticipated, but "ringing" distortion can also occur.

### Small pulse components

Familiar waveforms sometimes have comparatively small pulse components, which are nevertheless essential for normal circuit action. In an afc circuit, for example, the horizontal-sync pulse appears as a component of slight amplitude riding on the sawtooth comparison wave (Fig. 9-d). The pulse is halfway up the sawtooth wave, which corresponds to a picture that is split horizontally on the screen. If the pulse is weak or absent, there is a complete loss of horizontal locking. Another ex-

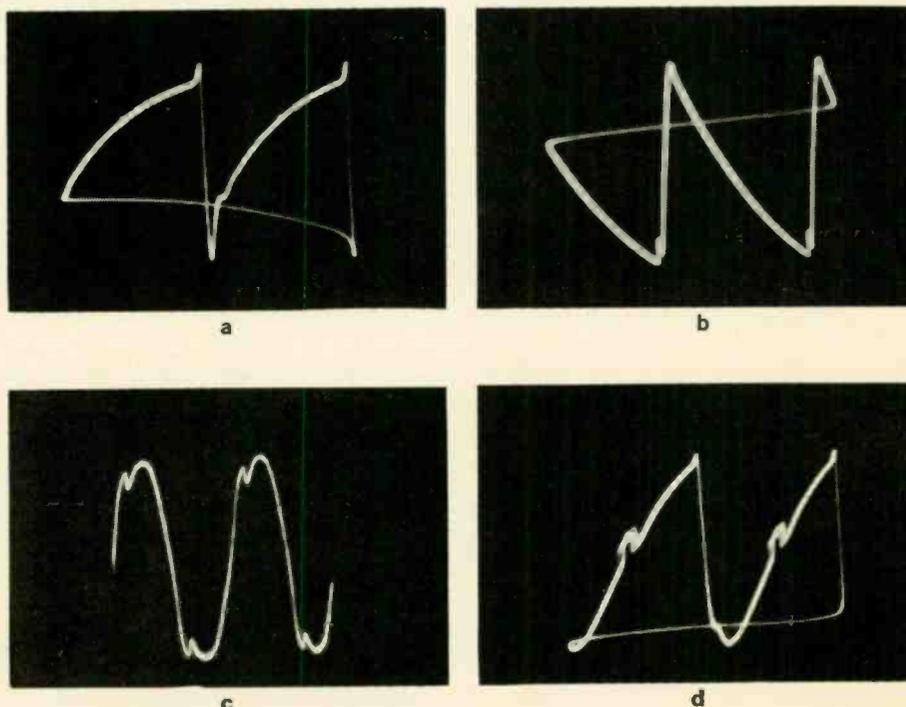


Fig. 9—Pulses can appear on various parts of a waveform. Sometimes they are hidden and sometimes they are very prominent. They can also increase or decrease amplitude.

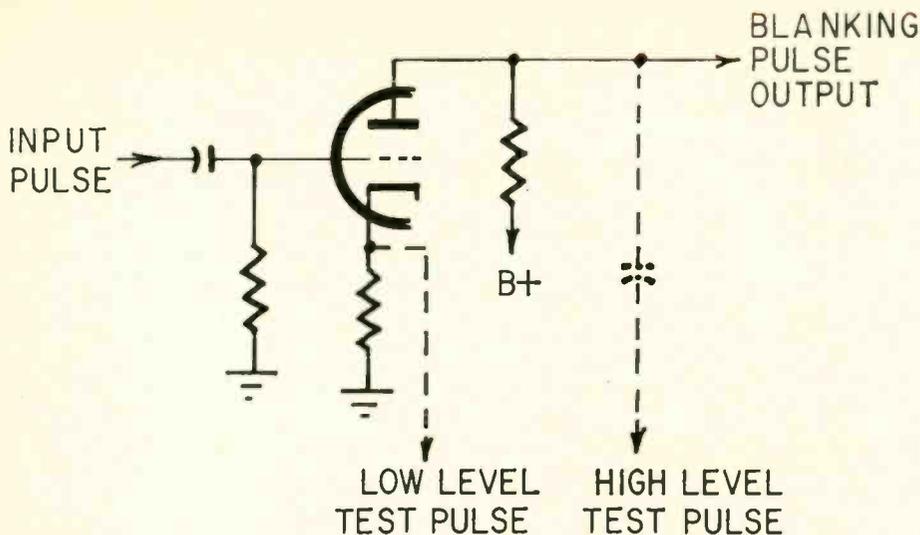


Fig. 10—Ringing-test pulse may be taken from blanking-amplifier output on scope.

ample of a minor pulse component is seen in Fig. 9-c; this is the voltage across the primary winding of a small 60-Hz transformer. Excessive current is being drawn, and the core is saturating during the pulse intervals. The pulse component is a clue to abnormal current flow. As saturation is approached, the sine wave becomes flattened.

In Fig. 9-b, the pulse starts at the negative peak of the sawtooth waveform, and its shape is obscured by the ensuing retrace interval of the sawtooth. The opposite aspect is seen in Fig. 9-a; here, the pulse is negative-going and increases the amplitude of the sawtooth component. A smaller positive-going pulse at the top of the waveform also increases the total amplitude. Various pulse-and-sawtooth waveforms are used in the horizontal-afc and sweep sections of many TV receivers, and analysis of waveform distortion with measurements of peak-to-peak voltages can be of considerable assistance in practical troubleshooting procedures.

### Test-pulse source

Electronic technicians use pulse generators to make tests of coils and transformers as well as audio amplifiers and other equipment. A scope is a convenient source of test pulses. For example, most modern scopes have blanking amplifiers similar to that in Fig. 10. The output from the blanking amplifier is a pulse waveform used for retrace blanking, which can be tapped to provide a test pulse as shown in the diagram. If you use a trimmer capacitor in the pulse-takeoff circuit, you can adjust the trimmer for the sharpest pulse consistent with sufficient amplitude. If the pulse is differentiated, it becomes narrower and its amplitude will be decreased simultaneously.

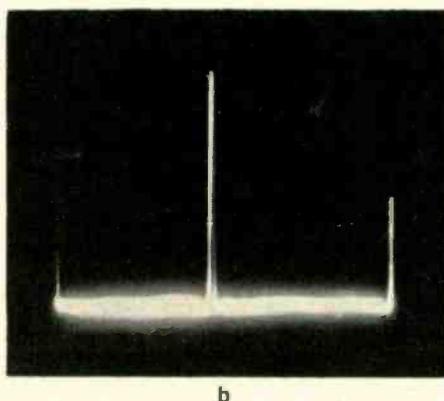
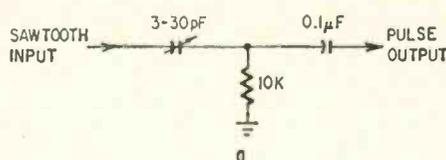


Fig. 11—Differentiating circuit used to shape the sawtooth taken from the scope. At (b), differentiator output waveform.

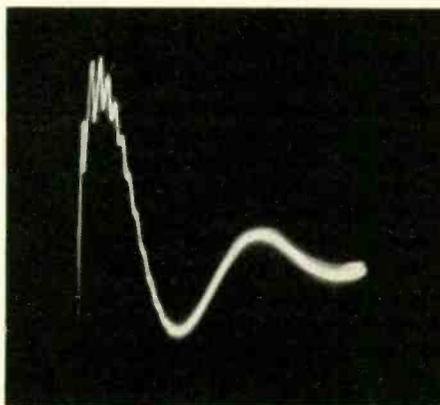




Fig. 12—Some typical ringing waveforms found across iron-cored audio transformers, and setup used to obtain them.

If your scope has no blanking amplifier, you still can obtain a test-pulse output. Simply couple the sawtooth sweep voltage through a small capacitor to a suitable differentiating circuit such as that in Fig. 11-a. If you use the horizontal sawtooth as a pulse source, the pulse amplitude will vary with the setting of the horizontal-gain control. However, this is not a disadvantage in most cases, because the gain control is usually set for nearly full screen width, and the pulse amplitude is ample.

This type of test pulse ordinarily is used for ringing tests of coils or transformers. Fig. 12 shows typical ringing waveforms, and the test setup. In case the pulse is too weak, connect the pulse lead directly to the vertical-input terminal of the scope. The ringing test is a comparison type in which the waveform produced by a known-good transformer is compared with the waveform produced by a transformer suspected of having any kind of defect.

Test pulses also are useful for checking the transient response of audio amplifiers. Some modern scopes have horizontal-sweep rates up to 500 kHz and will provide pulse repetition rates up to 500 kHz. While test pulses from a scope are less versatile than those obtained from a regular pulse generator, many useful applications are possible.

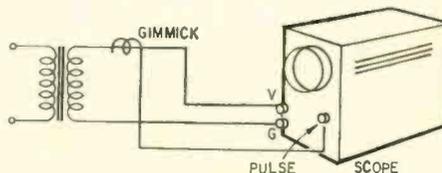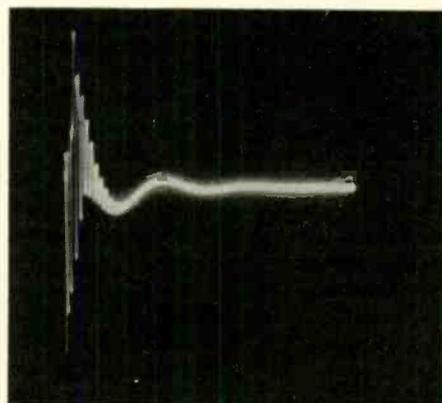
In just about every phase of electronics, pulses are an integral part of the operation of many circuits. When you know what normal pulse action is in a given situation, you will be able to recognize a faulty waveform. The trick then is to know what to do about it. **R-E**



# BUILD
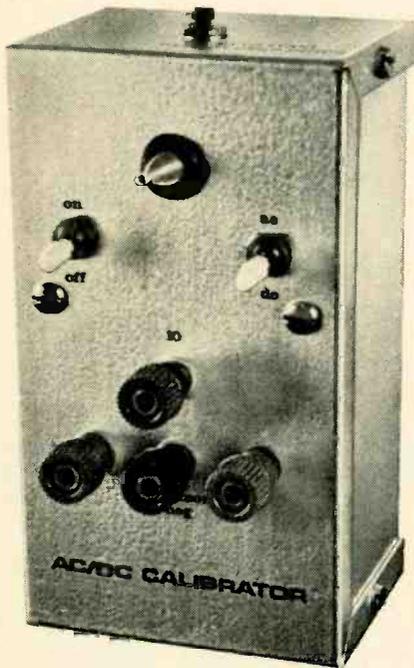
## AC/DC Calibrator for

*Inexpensive voltage reference sports 1% to 2% accuracy on 3 ranges*



*Panel Layout is designed for ease of operation. Neon lamp containing radioactive material serves as a 1% reference voltage standard and as a pilot light.*

IT'S SURPRISING HOW MANY PEOPLE own several hundred dollars' worth of test equipment and use it daily—perhaps to make a living—and yet don't own a single item for calibrating all that stuff! Are you one of them?

I was. I have to laugh (or cry) at the amount of blind faith I used to have in my meter readings. When something was really in doubt, I would buy a mercury cell and use it to calibrate my dc instruments. But ac? Well, when I finally got a dc scope I evolved a tedious way of calibrating by using it. This method turned out to be inaccurate because the scope's response (unknown to me) was down some 3 dB at dc compared to the response at 60 Hz! That put my ac instruments about 30% high!

Imagine my delight when I discovered a 100-volt neon lamp, accurate to within 1 volt (that's 1%). The calibrator shown here is the result. It has one extra wrinkle—a chopper to make ac out of dc—for which credit is due Leslie Spaiser, a young technician in a neurology lab at Mount Sinai Hospital, New York City.

### Peak to peak

I had been hunting around for some way to get an accurate 100 volts peak to peak for ac calibration. Signalite makes an ac version of the 100-volt 1% neon, but its waveform is tricky to use because it begins with a spike about 40% higher than the rest of the wave. Leslie suggested the simple chopper I used (Fig. 1)—it works.

From the 100 volts available across the neon lamp, you have to subtract the saturation drop across the transistor (about 0.25 volt), and to the zero you'd expect when the transistor is cut off you must add the voltage drop in the divider string due to transistor leakage (about 0.25 volt). These are small to begin with, making the peak-to-peak amplitude of the resulting square wave about 99.5 volts. It turns out that they are cancelled almost perfectly by the slightly increased drop across the neon under the lighter load caused by the action of the chopper.

The calibrator provides three voltages: 1, 10 and 100. The negative terminal floats (there is no connection to the case). The accuracy of the 100-volt output is  $\pm 1$  volt, or 1%. The accuracy of the other taps is decreased, by the inaccuracy of the divider string resistors, to roughly 2%. These figures are good only when the current drawn from the divider is negligible.

The resistance of any device connected to the 10- and 1-volt terminals should be 100,000 and 10,000 ohms minimum, respectively, to keep the loading error to 1%. The load on the 100-volt terminal can be heavier; resistances as low as 10,000 ohms can be connected with less than 1% drop in terminal voltage as long as the neon lamp is not extinguished. This means that even 1000 ohms/volt vom's can be calibrated directly on their 100- or 150-volt ranges.

### Construction

Parts placement is shown in the photo. The switches used in the original are little d.p.d.t.'s, with only the necessary terminals used. They are tiny and very attractive, but relatively expensive (about \$1.50 each), and you may prefer to use less-expensive switches.

Don't try to substitute parts that are different electrically from the ones called for in the parts list. The transformer voltage, the values of C1, R2, R4, R5 and R6 and the transistor all affect the accuracy or stability of the output voltages. R1 and R3 are not particularly critical. Values within 20% of those shown will work as well.

A 2N398 or 2N398-A can be used in place of the 2N398-B shown, but the B version has lower leakage and lower saturation resistance, which makes it preferable.

Be sure to connect the lead of the Z100R12 neon lamp with the red dot near it to the positive side of the power supply.

The binding-post terminals on the front of the calibrator are all of the "jack-top" type and will accept bare wire, spade lugs, banana plugs or alligator clips. They are spaced so that

# Scope and Voltmeter

the 1-, 10- and 100-volt terminals are exactly  $\frac{3}{4}$  inch from the common (negative) terminal. This permits the use of dual banana plugs, of which I have a great many. (The dual banana is sometimes called a "GR" plug, for General Radio Co., because they developed them. The plugs are also made by E. F. Johnson, Pomona; H. H. Smith and probably others.)

Nothing much needs to be said about using the calibrator for dc. Treat it as you would a battery: connect the device you want to calibrate and adjust the device to read exactly 1, 10 or 100 volts. Just be sure you don't connect heavier loads (lower resistances) than the limits mentioned earlier.

## Operation

You need operate the START button only on dc. On ac, the "chopped" load of the divider string due to the action of Q1 is quite light. On dc the loading is twice as great, and the drop across R2 is enough to keep NE1 from igniting. A momentary push is enough. Don't hold the button down, because NE1 will be overloaded and eventually damaged.

On ac, remember that the values 1, 10 and 100 are *peak-to-peak* voltages. You should see exactly those figures on a peak-reading indicator such as a peak-reading vtm or an oscilloscope. Average or rms instruments will *not* indicate 1, 10 or 100. An ac instrument calibrated to read rms values of sine waves (this includes the vast majority of service-type ac instruments, such as amplifier/rectifier type audio millivoltmeters and the ac ranges of vom's) should read 0.50, 5.00 or 50.0 volts, depending on which terminal of the calibrator is used.


The slight slope of the square waveform should give no trouble when the calibrator is used for an oscilloscope. Use the height of the leading edge of the trace as 100 volts.

Another way of checking instruments designed to indicate rms voltages is to set up a scope to display one or two cycles of the square wave from the calibrator on about  $\frac{2}{3}$  the screen

height. Mark the height of the leading edge with a sharpened crayon or use appropriate graticule lines. Disconnect the calibrator and instead connect to the scope a sine-wave source. Adjust it so that the peaks of the sine wave coincide exactly with the marks. You now have a 1- (or 10- or 100-) volt *peak-to-peak* sine wave. Its rms value is very nearly 0.354 volt (or 3.54 or 35.4). Adjust an rms-reading instru-

ment to indicate accordingly, when measuring the sinewave.

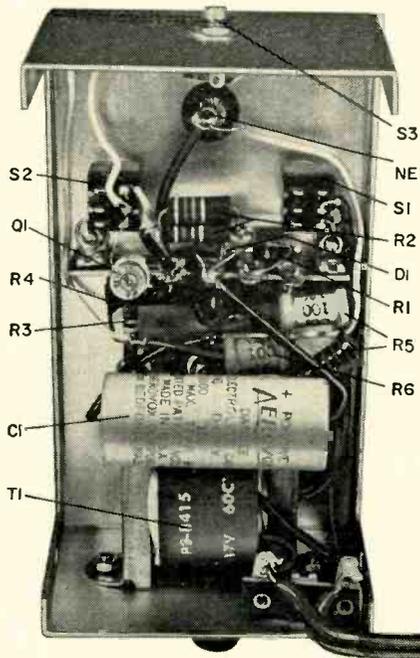For the most accurate and stable readings, the calibrator should be left to stabilize at least 2 minutes before using it. Nothing will be gained by leaving it on permanently, although the life expectancy of the Z100R12 is around 30,000 hours (over 4 years). It is normal for the neon lamp to get too warm to hold comfortably. **R-E**



Center the neon lamp inside the grommet and cement in place. Observe lamp "polarity." Construction is not critical.

## PARTS LIST

- C1—80- $\mu$ F, 150-volt electrolytic capacitor
- D1—Silicon rectifier, 400 volts minimum, any current rating (1N1695, 1N3194, 1N4004, etc.)
- J1, J2, J3—Red jack-top ("5-way") binding posts
- J4—Black jack-top binding post
- NE-1—100-volt, 1% neon reference lamp, Signalite Z100R12, available only from Signalite, Inc., (Attn. Mr. Donald J. Furfaro) 1933 Heck Ave., Neptune, N.J., for \$3.50 plus postage, and only if you mention this article and RADIO-ELECTRONICS.
- Q1—2N398-B transistor
- R1—100-ohm,  $\frac{1}{2}$ -watt resistor
- R2—2400-ohm, 2-watt resistor (or two 4,700-ohm, 1-watt resistors in parallel)
- R3—330-ohm,  $\frac{1}{2}$ -watt resistor
- R4—9000-ohm, 2-watt, 1% resistor
- R5—900-ohm,  $\frac{1}{2}$ - or 1-watt, 1% resistor (100-ohm and 800-ohm resistors, in series)
- R6—100-ohms,  $\frac{1}{2}$ -watt, 1% resistor
- S1—Miniature s.p.s.t. toggle switch
- S2—Miniature s.p.d.t. toggle switch
- S3—Momentary pushbutton, normally closed switch
- T2—Power transformer, 125-volt, 15mA primary and 6.3V, 0.6A secondaries (Stancor PS-8415, Knight 54 B 1410, or similar)
- Two-piece aluminum box,  $2\frac{1}{2}$  x 3 x  $5\frac{1}{4}$  in. (Bud CU-3006-A or similar)
- Misc.—Terminal strips, grommets, rubber feet, etc.


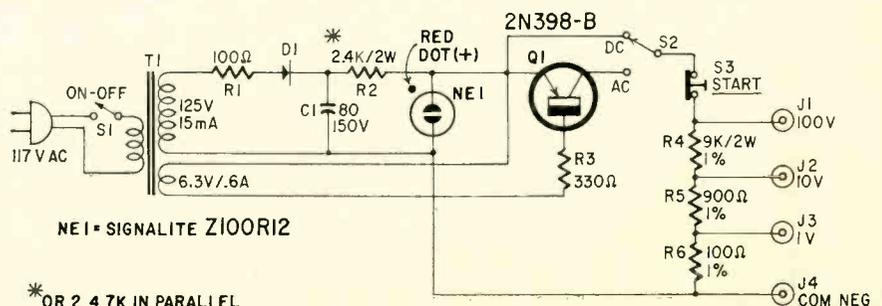


Fig. 1—Neon lamp (NE1) regulates output for 100-volts dc. Transistor Q1 chops this dc to develop the ac voltage. The resistor string sets up 2 more ac and dc ranges.

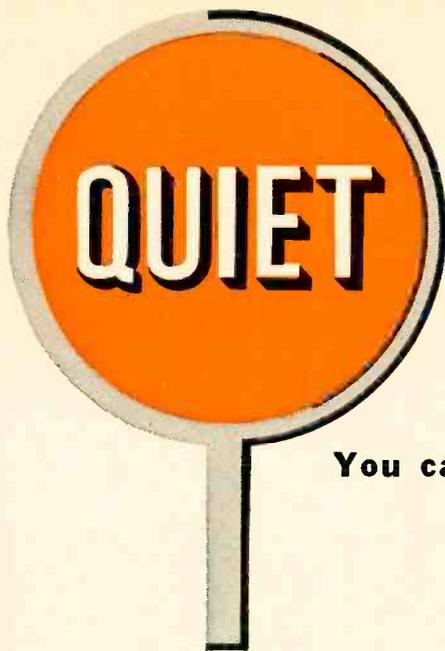

# NOISE LIMITERS AT WORK

You can cut some of the QRM without pulling the plug

By JOHN D. LENK

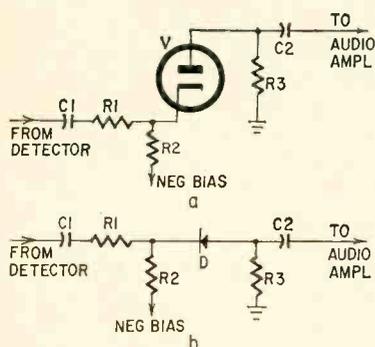


Fig. 1-a—Tube version; b—solid-state version of half-wave series limiter.

IN A RADIO RECEIVER A NOISE LIMITER reduces or eliminates rf impulses which interfere with desired signals. The operation of automatic noise limiter (ANL) circuits is based on the fact that undesired rf noise has two characteristics which make it different from intelligible audio modulation. Most rf noise is shorter in duration and greater in amplitude than the desired signals.

Most noise-limiter circuits are designed to *reduce* the noise pulses, rather than eliminate them. The circuits can be divided into several broad classifications, such as peak limiters and rate-of-change limiters. There is also the twin noise squelch (TNS) that blocks all sound during noise pulses.

Peak limiters are relatively simple. They "chop" off the tops of the noise pulses so that the noise is no louder than the signal. Rate-of-change limiters "chop" out noise, such as ignition pulses, which change polarity rapidly. The rate-of-change circuits are new compared to peak limiters.

## Peak limiters

There are two types of series peak limiters—half-wave and full-wave. Both

clip the peaks of noise pulses, to keep noise level from exceeding signal level. The full-wave noise limiter operates on positive and negative noise pulses, while the half-wave limiter restricts positive or negative peaks only.

A basic half-wave limiter circuit is shown in Fig. 1. The cathode is normally biased negative with respect to the plate—even during positive audio signals from the detector. Under these conditions, V (Fig. 1-a) or D (Fig. 1-b) conducts, allowing audio from the detector to pass to the audio amplifier in the normal manner. An abnormally large positive signal, such as a noise pulse drives the cathode of V positive with respect to the plate. Current can no longer flow, so V does not conduct the noise pulse to the amplifier. Usually, the noise pulse is of very short duration. As soon as it is over, the cathode again becomes

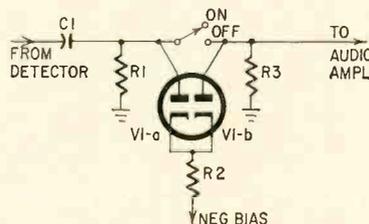


Fig. 2—The full-wave series limiter is more effective at removing the noise.

negative with respect to the plate (or anode), V (or D) conducts, and normal operation is restored.

The basic series full-wave limiter circuit is shown in Fig. 2. Both cathodes are normally biased negative with respect to their corresponding plates, as long as the signal is less than a certain peak-to-peak voltage. Under this condition, audio passes from the detector to the amplifier without change. When there is a strong negative noise pulse across C1, the plate of V1-a is driven

negative and it stops conducting, blocking the noise. As soon as the plate is positive with respect to the cathode, V1-a again conducts, permitting passage of audio.

Positive noise pulses are clipped in a similar manner by V1-b, since this half of the tube cannot conduct when a noise pulse drives the cathode positive. The two diodes in combination remove noise pulses from the audio output.

A series limiter breaks the audio path between detector and audio amplifier. A shunt limiter, on the other hand, shorts the noise peaks to the ground. This is the simplest form of limiting circuit and can be added to almost any receiver. The basic half-wave shunt limiter is shown in Fig. 3. Capacitor C1 charges to the average signal level through D2. At this point, the voltages on both sides of D2 are approximately equal, and the diode no longer conducts. Audio then passes from the detector to the audio amplifier. However, an abnormally strong signal biases D2 into conduction, and this pulse is absorbed by C1. The charge gradually leaks off C1 through R1 at a rate determined by the C1-R1 time constant.

It is possible to place two half-wave shunt limiters across an audio line with the diode polarities reversed, forming a full-wave shunt limiter. However, such a circuit can cause audio distortion if the capacitor values are not proper, or if the diode characteristics are not correct. Hence, full-wave shunt limiters

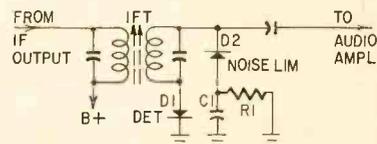


Fig. 3—Shunt limiter bypasses noise spikes without interrupting the signal.

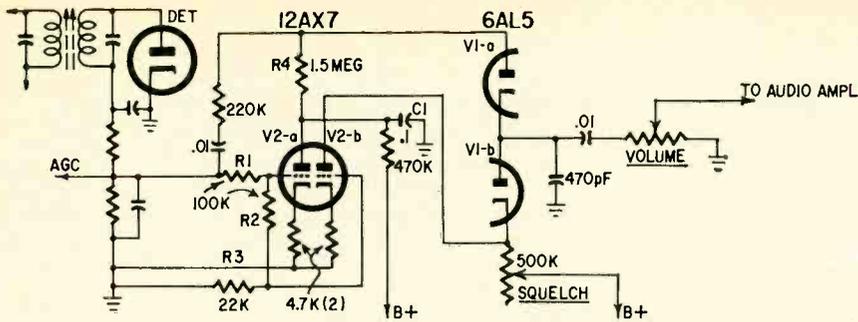


Fig. 4—Twin noise squelch has two actions. It keeps the receiver silent until a normal signal comes along, and cuts the receiver out again in the presence of noise.

are rarely used in audio stages, although they are sometimes found in i.f. stages of single-sideband receivers.

### Twin noise squelch

This circuit is a combination squelch and noise limiter. As seen in Fig. 4, detector output consists of audio and a dc voltage produced by carrier rectification. This mixture is applied across voltage divider R1, R2 and R3. The divider is tapped so the grid of V2-a receives more detector output than the grid of V2-b. The audio signal is amplified by V2-b and goes through gating diode V1-a before it reaches the volume control and the audio amplifier.

A signal can pass through V1-b and V1-a only when each plate is positive with respect to its cathode. The voltage on the cathode of V1-b is controlled by the plate voltage of V2-b. Similarly, the voltage on the plate of V1-a is controlled by the plate voltage of V2-a.

Under no-signal conditions, the grids of V2-a and V2-b are zero-biased; both tubes are conducting. The SQUELCH control (supplying B+ to V2-b) can be set so the cathode of V1-b is sufficiently positive to cut off gating tubes V1-a and V1-b. When there is a signal from the detector, the grid voltage of V2-a drops faster than that of V2-b. Consequently, the plate voltage of V2-a rises faster than that of V2-b. This signal biases V1-a and V1-b into conduction, and the audio signal goes through the volume control.

When a noise pulse is received, it is applied to the grids of both V2-a and V2-b, causing their plate voltages to rise. However, the time constant of R4-C1 in the V2-a plate circuit slows down

that plate's voltage rise, as well as that of the plate of V1-a. This means the plate voltage of V2-b (and the cathode voltage of V1-b) rises faster. Thus V1-a and V1-b are biased to cutoff, preventing audio from passing for the duration of the noise pulse. This hole is not audible, however, since the noise pulse is usually very short.

The TNS circuit is more effective than peak limiters. Its only drawback is distortion on very strong audio signals when the circuit is added to certain receivers. Even then the problem can be cured by a slight modification, described by the circuit manufacturer.

### I.f. noise limiters

In a single-sideband receiver it is desirable for the limiter to work on noise pulses before they reach the detector. This is because the beat-frequency oscillator (bfo) used for sideband reception produces an artificial carrier much stronger than the actual received carrier. If the limiter used the bfo carrier as reference, the limiter would have very little effect on noise pulses. A practical solution is to use a full-wave shunt limiter—similar to that shown in Fig. 5—in the first i.f. stage.

In this circuit, known as an IFNL, the plate current of an i.f. amplifier varies with the incoming signal; stronger signals produce greater variations. Capacitors C1 and C2 are charged to the average value of this varying i.f. voltage. Since D1 and D2 are reversed, C1 and C2 are charged by both positive and negative swings of i.f. plate current. C3 and R1 aid the voltage-averaging process.

When C1 and C2 are charged to the average value, the voltages on both sides of diodes D1 and D2 are approximately the same, and the diodes do not conduct. This allows the normal plate-current variations to appear across the i.f. transformer primary. When there is an abnormally strong signal (noise pulse), the voltage is considerably different from that of C1 and C2, creating a voltage differential across D1 and D2. One of the diodes then conducts and creates a virtual short across the i.f. transformer primary. This prevents any

signal from passing through the i.f. stage. Once the noise pulse drops back to the average i.f. level, the voltage differential across the diodes is removed, and the circuit is restored to normal operation.

### Rate-of-change limiters

Unlike peak limiters, rate-of-change limiters sense the speed at which the instantaneous detector output voltage is varying, not just the amplitude of change. In the presence of a rapidly changing detector output (such as a noise pulse), the rate-of-change limiter remains inactive up to a certain point. As the output swings above that point, the limiter substitutes its own output signal for that of the detector.

A typical rate-of-change limiter circuit is shown in Fig. 6. The base-emitter junction of a transistor is used as a diode. The voltages at the base and emitter of Q are determined by the audio signal. The base is connected at the junction of R1 and R2, and the emitter voltage is taken from the junction of R4 and C4. The values of R1, R2, R4 and C4 are chosen so the emitter is normally less positive (or more negative) than the base. This causes Q to pass audio from the detector to the volume control. With normal audio variations (no rapid changing of amplitude or polarity) both the base and emitter follow the audio signals.

When there is a noise pulse, or any signal that changes rapidly, the base of Q instantly swings negative. The emitter of Q also swings negative, but not as rapidly as the base, because of the time needed for C4 to charge. Therefore the base is more negative than the emitter during the noise pulse. This condition cuts off Q, preventing audio from passing to the volume control. The low charging voltage of C4 is substituted for normal audio.

When the noise pulse has passed, the base of Q returns to the normal voltage, Q starts conducting, and normal audio passes.

Most rate-of-change limiters obtain voltage from the detector load resistor (through a filter) and take the audio signal from a tap on this resistor. This makes the rate-of-change limiter self-adjusting for varying signal strengths. R-E

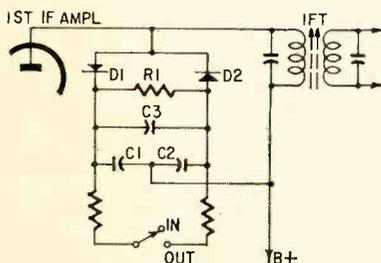


Fig. 5—Many single-sideband receivers use this special type of i.f. noise limiter.


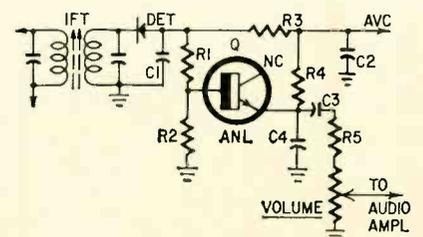


Fig. 6—Solid-state rate-of-change limiter.

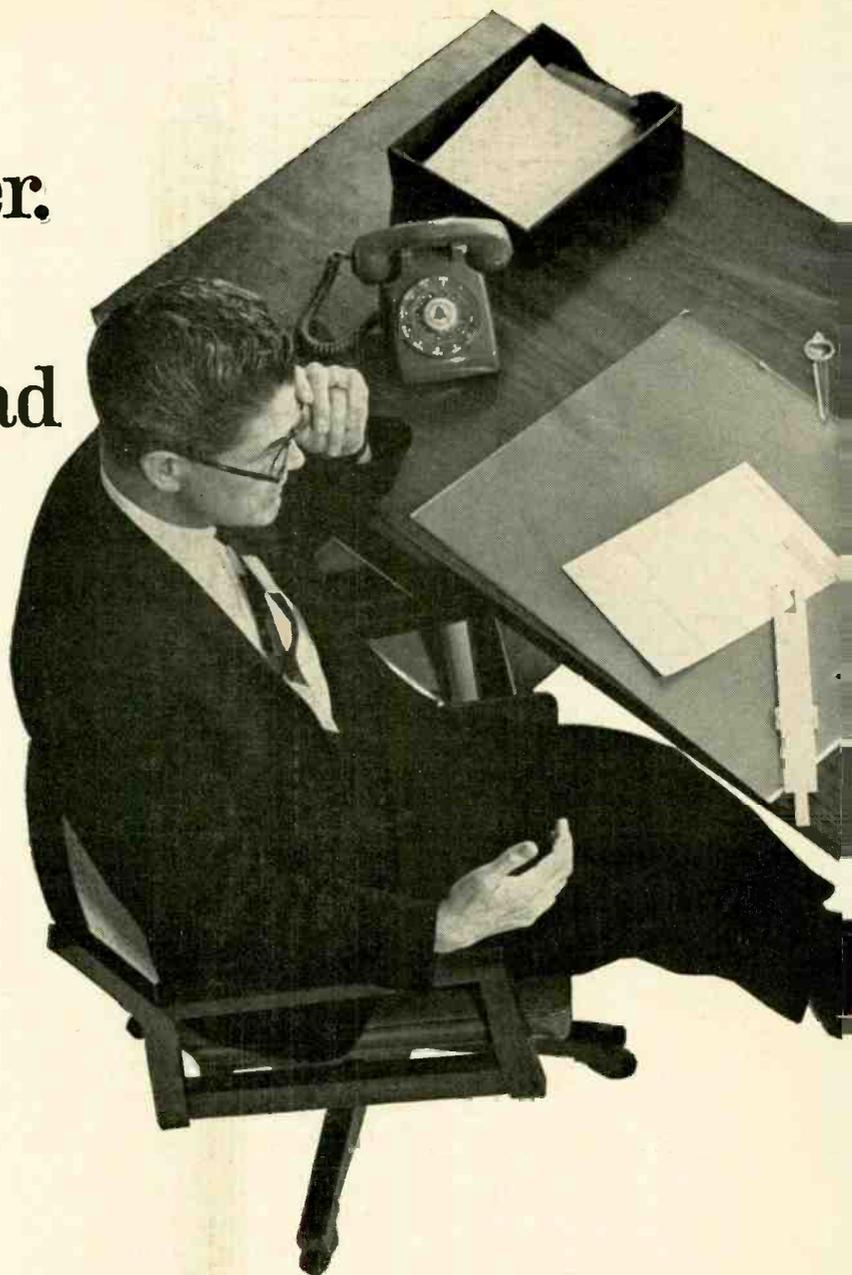**“He’s a good worker.  
I’d promote him  
right now if he had  
more education  
in electronics.”**



## **Could they be talking about you?**

You'll miss a lot of opportunities if you try to get along in the electronics industry without an advanced education. Many doors will be closed to you, and no amount of hard work will open them.

But you can build a rewarding career if you supplement your experience with specialized knowledge of one of the key areas of electronics. As a specialist, you will enjoy security, excellent pay, and the kind of future you want for yourself and your family.

Going back to school isn't easy for a man with a

full-time job and family obligations. But CREI Home Study Programs make it possible for you to get the additional education you need without attending classes. You study at home, at your own pace, on your own schedule. You study with the assurance that what you learn can be applied to the job immediately.

CREI Programs cover all important areas of electronics including communications, radar and sonar, even missile and spacecraft guidance. You're sure to find a program that fits your career objectives.



You're eligible for a CREI Program if you work in electronics and have a high school education. Our FREE book gives complete information. Airmail post-paid card for your copy. If card is detached, use coupon at right or write: CREI, Dept. 1402G, 3224 16th St., N.W., Washington, D.C. 20010.



**The Capitol Radio Engineering Institute**  
*A Division of McGraw-Hill, Inc.*  
**Dept. 1402G, 3224 Sixteenth Street, N.W.**  
**Washington, D.C. 20010**

Please send me FREE book describing CREI Programs. I am employed in electronics and have a high school education.

NAME \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP CODE \_\_\_\_\_

EMPLOYED BY \_\_\_\_\_

TYPE OF PRESENT WORK \_\_\_\_\_  G.I. BILL

I am interested in  Electronic Engineering Technology  
 Space Electronics  Nuclear Engineering Technology  
 Industrial Electronics for Automation  
 Computer Systems Technology

**APPROVED FOR TRAINING UNDER NEW G.I. BILL**

# How To Measure Reverberation Time

Measuring reverb time is as important to the sound-system designer as selecting the equipment **By DON DAVIS\***

MODERN HALLS ARE TOO BIG AND TOO expensive for architects and acoustics consultants to rely on hunches.

Designing or modifying the acoustics of a huge auditorium is a complex and fascinating job. It can be every bit as exciting and romantic as building a suspension bridge.

If you've ever strained to understand train announcements in the main waiting room of a city railroad station, you know that loudness alone is

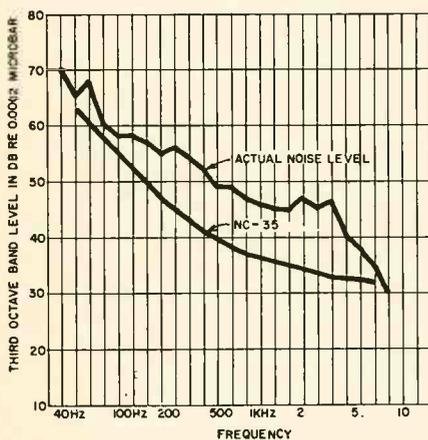


Fig. 1—Noise measurements of the hall.

not enough to make a sound system adequate. Why? If the *reverberation time* of the room is too long (or, as most people would say, if there's too much echo), the sound issuing from the PA speakers at any instant is blurred by earlier sound as it reverberates from the walls, floor and ceiling of the room. For a large, hard-surfaced room, 7 to 8 seconds is not at all uncommon for "echo" duration. With a reverberation time that long, loud speech becomes completely gar-

bled. The louder the sound, the worse the situation gets, since the reflected sound increases with incident sound.

A method called Boner equalization (developed by Dr. C. P. Boner) permits the frequency response of a sound reinforcement system to be altered to suit particular reverberant-room characteristics. (See "Custom Equalization Enhances PA Sound," R-E, November 1966.) But that isn't the whole answer. It aids intelligibility, but it isn't suitable for high-quality sound assist in concert halls.

**Basic terms.** Reverberation time is defined as the time it takes for the rms sound-pressure level in a room to drop by 60 dB after having been allowed to reach a steady value. What this means in practical terms is simply the time it takes for one sound to drop to inaudibility (or very nearly so) so that it can't interfere with the next sound.

If no other frequency figure is given, one can assume that the measurement was made at 512 Hz.

Wallace Clement Sabine, the father of modern architectural acoustics, was the first to reduce reverberation time to a workable formula. Around the beginning of the 20th century, in a series of brilliant experiments and deductions, he described reverberation time and plotted its dependence on the absorptive properties of the materials in the room.

By bringing cushions from an acoustically acceptable hall into an acoustically unacceptable hall he was able to plot the curve that characterizes reverberation time in a live hall:

$$T = \frac{.05V}{S\alpha}$$

where T = reverberation time in sec-

onds, V = room volume in cubic feet, S = total surface area in square feet, and  $\alpha$  = average absorption coefficient of the surfaces in the hall.

Sabine's work gave rise to a unit of acoustical absorption (now called the *sabin* in his honor): 1 sabin is the equivalent of 1 square foot of a per-



Hall after treatment. Dark area of dome is flocked for greater sound absorption. The nearer speaker is fed delayed audio.

fectly absorptive surface. (Sabine's choice of a perfectly absorptive surface was a window opening out into free space.)

It's obvious from the formula that reverberation time increases directly in proportion to room volume and inversely with absorptivity. Rule of thumb: Big room and hard surfaces mean trouble!

**A typical case.** A number of years ago a sound contractor and I were driving through a small city in the

\*Author of *Acoustical Tests and Measurements*, published by Howard W. Sams & Co., Inc.

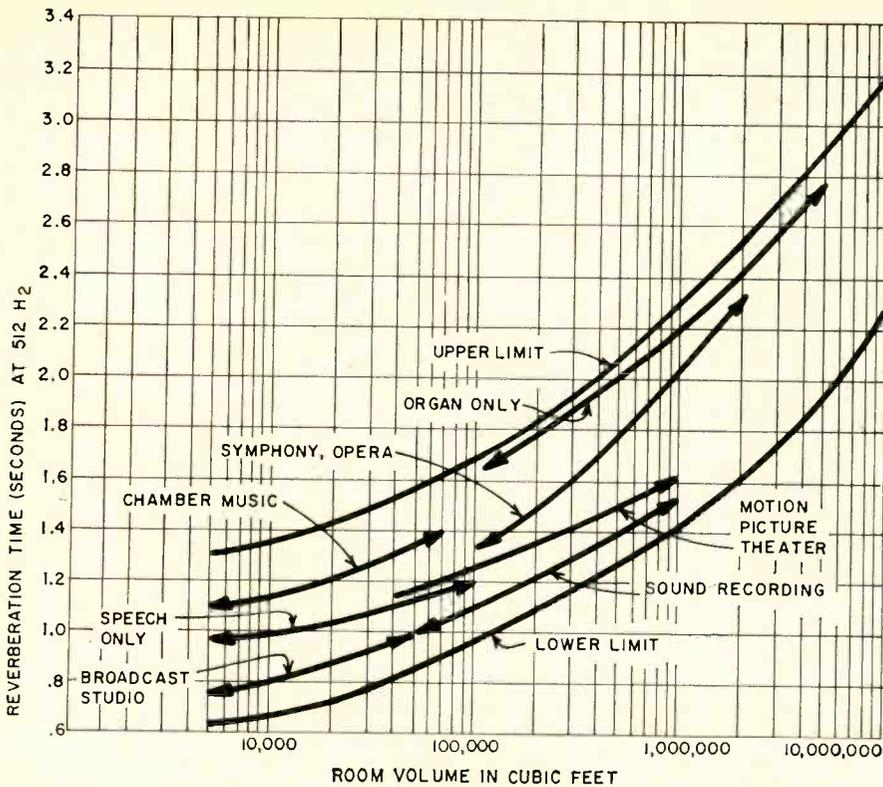


Fig. 4—An assortment of optimum reverberation times for various rooms and uses.

middle west when we noticed a large domed auditorium that had just been completed. Because of its size (over 370 feet in diameter) we were consumed with curiosity about its acoustical properties. Inquiries soon led us to the owners of the auditorium. When they heard we were in the sound-system business they unburdened themselves of an acoustical tale of woe. They had gone from cones to columns to confusion. It seemed that the auditorium had an interior volume of

1,500,000 cu ft, and not only were all surfaces hard but they were also concave. A handclap lasted a good ¼ minute, and stamping the feet created a roaring sound that rolled around and around the interior. The sound system was a "package deal" amplifier driving four low-cost column (line-source) speaker systems. Speech from the speaker's platform could not be heard clearly at any of the 7,600 seats.

We were taken to the architect's office. He asked us point blank if we

could provide a sound system to correct the situation. We replied that at the moment we didn't know, but we could do a complete acoustical survey of the auditorium, and from the data we gathered we could give a definite answer.

A short time later the contractor and I arrived back in town with approximately \$7,000 in measuring equipment. With this equipment we measured:

1. Ambient noise levels by frequency in the auditorium.
2. Reverberation time at 1/3-octave intervals from 40 to 10,000 Hz.
3. Frequency response and dynamic range of the sound system installed in the auditorium.
4. The harmonic distortion of the sound system at key frequencies in the speech range.
5. The reflection patterns in the auditorium when excited by the sound system.

The technique that's least familiar to someone who isn't a member of the club is the one used to measure reverberation time, and that's what this article is all about. So we'll concentrate on that.

The test apparatus was set up on an 8-foot table and allowed to warm up for an hour. Our big test speaker, used to excite the room with random noise, was aimed toward the center of the auditorium.

The first test run was a measurement of the ambient noise level in the auditorium. This we did, not only to analyze the noise sources in the room, but to let us know how high a sound-pressure level (SPL) we would need from our test speaker for enough dynamic range to guarantee a true picture of the decay slope (at least 20 dB of decay is highly desirable). At low frequencies in this large auditorium it was necessary to achieve at least 90-dB SPL of noise at the measuring microphone before the noise source is silenced. Fig. 1 indicates the result of the measurements in this large auditorium.

To make these measurements, we placed our sound-level meter (slm) in the center of the auditorium. The slm's output was connected by a long cable to the input of the 1/3-octave band analyzer. This analyzer can be read directly from its own meter, or its output can be connected to the input of the chart recorder for automatic plotting. All lights, fans, blowers, etc. normally on when the building is used were on for our tests. Our measurements were taken *without* an audience. An audience would have appreciably

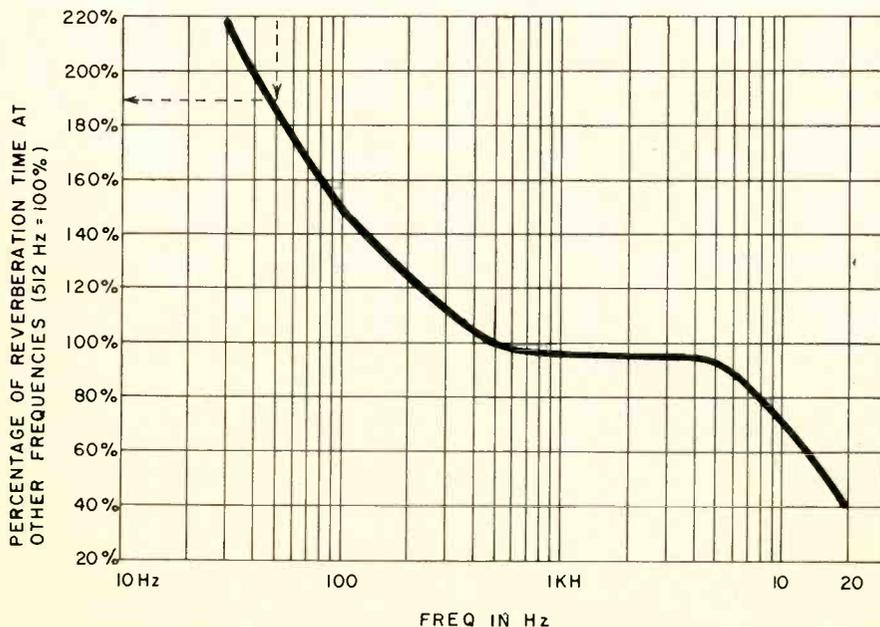


Fig. 5—Conversion chart for computing optimum reverb time versus frequency.



Quite an impressive table full of equipment is needed for professional measurement of reverberation. Permanent sound-system console at left is part of hall.

increased these noise levels.

After we were satisfied that the noise levels were overcome, we set our test speaker and its 175-watt amplifier to deliver a 126-dB SPL at 4 feet, or 96 dB at 128 feet. The hookup of the test equipment is shown in Fig. 2. We closed S1, tuned the 1/3-octave analyzer No. 2 to 40 Hz and started the graphic level (chart) recorder running at 75 in./min, or 300 div/min (5 div/sec) paper speed. We set the pen speed to its fastest setting (in this case 20 in./sec). Then we opened S1. The level recorder pen traced the decaying sound picked up by the slm's microphone.

Fig. 3 shows two decays, at 1,000 and 2,500 Hz. Here's how to read a curve like that:

1. Draw an average-decay-rate line through the decay slope.

2. Count off the number of horizontal divisions crossed by this average line in 20 dB of slope. (On this paper, 20 dB is 2 vertical divisions.)
3. Multiply the counted divisions by 3.
4. Each division represents 1 second.

This process is repeated for each of the 1/3-octave-band center frequencies. All the individual curves were recorded on the overall chart.

**Criteria.** Once you have a decay curve for each of the 1/3-octave bands on the chart, what do you do with them?

In the 60-plus years since Sabine's epochal work, literally thousands of rooms all around the world have been measured. Gradually people's subjective

judgments of these rooms (good, bad, fair, etc.) have been compared with the reverberation curves they exhibited. While no one has found an absolute correlation between reverberation time and subjective opinion, it has been found that whenever a certain broad set of criteria is violated, listeners are invariably annoyed.

As room volume increases, slightly more reverberation time is usually tolerated. That works out happily: Remember V in the formula and how much surface absorption would be required to divide into it if it became a large number. Fig. 4 shows a chart that plots the optimum reverberation time against room volume and program type. There's a great difference of opinion about optimum reverberation, but most authorities agree that if you get beyond either of the two limit

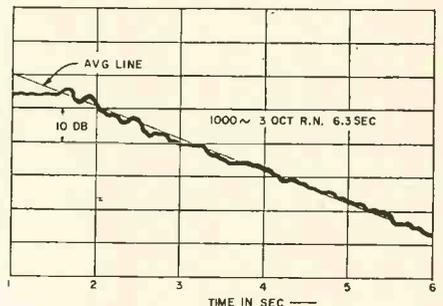
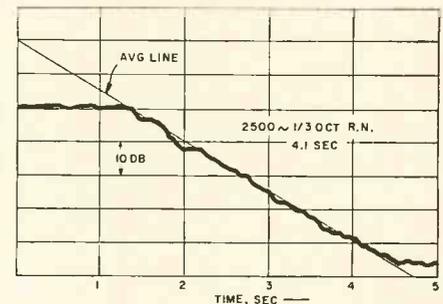


Fig. 3—Two sample decay-time measurements. Checks are made at several points.

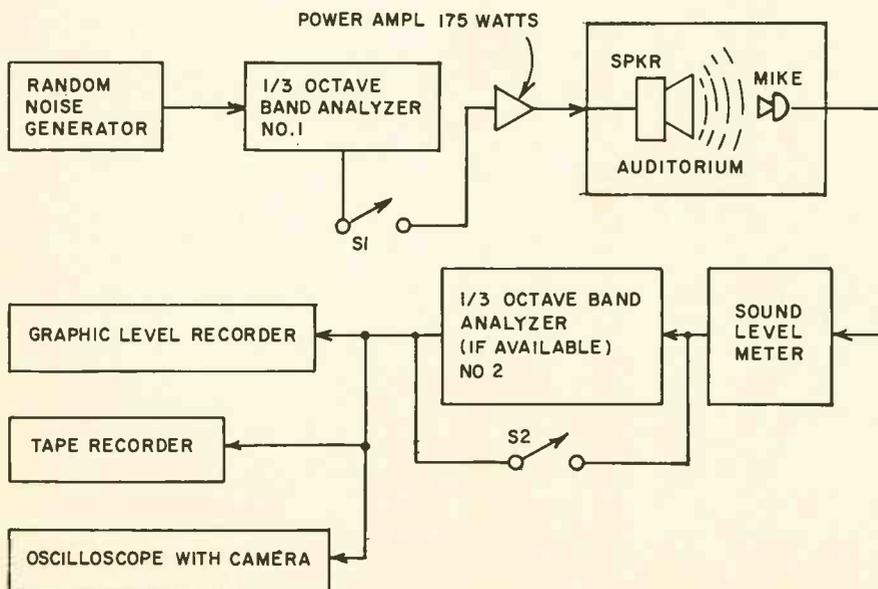


Fig. 2—Interconnection of the equipment used to measure hall reverberation time.

lines on the chart you can expect difficulties.

Once you have a feeling for the range of acceptable criteria at 512 Hz, the chart in Fig. 5 gives the percentage of increase or decrease in reverberation time for other frequencies. It is important to note that, at very low frequencies, reverberation times often double compared with 512 Hz.

**Data used for correction.** When the measurements were concluded, the sound contractor was asked to install a sound system in the room. On the basis of the evidence from the tests he demurred until the builders engaged an acoustical consulting firm. All the charts and tests were made available

(continued on page 81)

# Build An Electronic Tremolo

Build this add-on unit for today's way out electronic music

By R. H. KEENAN

AN EFFECT COMMON TO MOST KINDS of classical and popular music is *tremolo*: periodic, fairly rapid variation in loudness. It is particularly common in wind instruments, even including the pipe organ. What it amounts to is amplitude modulation of the musical note by a low-frequency, subaudible signal (usually around 5 to 8 cycles per second). In conventional musical instruments it can be produced by varying the wind pressure applied to them.

Tremolo is *not* the same thing as *vibrato*, which is slow frequency modulation (FM) and sounds quite different. Pipe organs never have vibrato. The two words are often confused.

Tremolo (AM) is easy to add to

an existing music source. The simple device described here can be used with electronic guitars, organs or other instruments, or with recorded music or noise to produce special effects for electronic music or sound-and-light shows. The circuit is simple and can be added quickly to any amplifier or tape recorder.

## How it works

The subaudible tremolo signal is produced by Q1, a unijunction transistor, used in a simple relaxation oscillator (Fig. 1). Q2 amplifies the signal and drives lamp LMI, which flickers at the rate set by the oscillator. The varying light falls on cadmium-sulfide photocell PC1, causing its resistance to vary accordingly. The photocell is part

of the series arm of a voltage divider (attenuator), so the audio level varies periodically as the oscillator swings. R3 is the tremolo RATE control; R5 controls the depth of modulation.

The photocell and lamp (see parts list) are placed end to end and rolled together into a strip of black

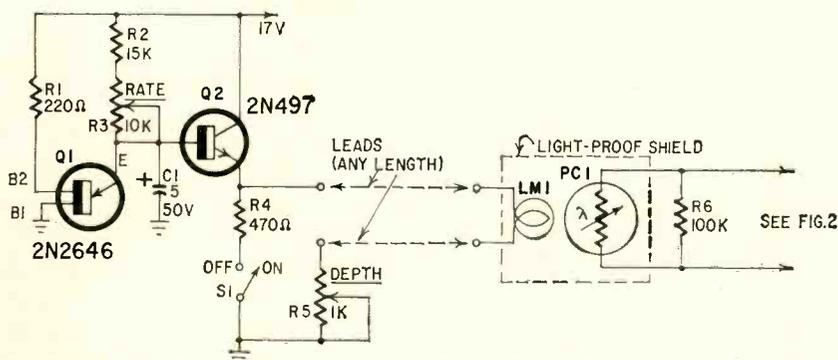


Fig. 1—Two 9-volt transistor batteries in series will power the tremolo nicely. You can install the lamp and photocell any convenient distance from controls.

## PARTS LIST

C1—5- $\mu$ F, 50-volt electrolytic capacitor  
 R1—220-ohm resistor  
 R2—15,000-ohm resistor  
 R3—10,000-ohm potentiometer (RATE)  
 R4—470-ohm resistor  
 R5—1000-ohm potentiometer (DEPTH)  
 R6—100,000-ohm resistor for shunting PC1 (you may need to select best value from 47,000 to 470,000 ohms)

PC1—Photocell (Clairex CL607)  
 LM1—Incandescent lamp, 28 volts, 40 mA (G-E 327 or similar)  
 Q1—Unijunction transistor (2N2646)  
 Q2—Large-signal npn transistor (2N497 or similar)  
 S1—S.p.s.t. switch of any convenient kind. Case and perforated board or other means for mounting Q1-Q2 circuitry.

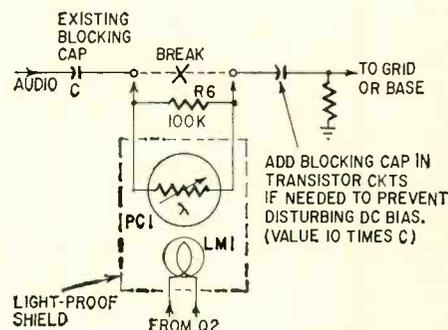


Fig. 2—Insert the photocell between amplifier stages as shown. Be sure to use blocking capacitors to avoid dc through the photocell and changing bias.

plastic electrician's tape, making a single, lightproof unit with leads coming out the ends. Total current drain for the circuit shown, including the lamp, is about 20 mA. The circuit will probably work with other transistors; Q1 is a 2N2646, a common and inexpensive unijunction, and Q2 is a 4-watt npn 2N497, used because it was handy. The circuit could be rearranged for use with a pnp transistor as Q2. This transistor should have fairly high beta ( $h_{FE}$ ) and be capable of dissipating at least 200 mW.

## Circuit connection

Connect the tremolo device between amplifier stages, either tube or transistor, as in Fig. 2. You may want (continued on page 83)

# The Useful Decibel

Everywhere in electronics you find dB's—now learn them the painless way—without logarithms!

By ERIC LESLIE

MUCH NONSENSE, AND WORSE—A LOT of incomprehensible sense—has been written about the decibel, probably the most useful unit of measurement in electronics. Yet in spite of that usefulness, too many technicians don't understand it. Why? Because most articles on the how and why of the decibel do more talking about logarithms than about decibels. That's fine, if you know logs. But if you don't, you have to learn logarithms and decibels, both at the same time.

## Nonlinear measurement

How did the decibel come about? It was devised to measure nonlinear quantities. Did you know your ear does not have linear response to changes in sound volume? This is the reason you can hear a whisper across a quiet room, and also tolerate the blare of auto horns or the roar of a subway express train.

Suppose you're listening to an amplifier with a wattmeter across the output. First you hear a 1-watt sound; then you crank up the gain to 2 watts. Does the speaker output sound twice as loud? No—it just sounds a little bit louder. You have to turn up the gain until you increase power output 10 times—to 10 watts—before you hear twice as much audio as you did at the 1-watt level. That, briefly, is the way your ear works.

To describe this interesting system, the 10-to-1 power relationship was described mathematically and called a *bel* (in honor of Alexander Graham Bell). For more precise measurements, a tenth-of-a-bel unit—the decibel—was put in service.

The decibel, then, is a measure of power *ratio*. It doesn't matter whether you increase or decrease the power—dB's work both way. Double the power, and you've increased it by 3 dB. Cut the power in half, and you've decreased it by 3 dB. Check this with the table. In column B find the ratio of power increase—2.0. Opposite this point in col-

umn E you'll find 3—the number of dB's of change.

Decibels can also be used to measure the ratio between two voltages or between two currents. Since power equals voltage times current, though, voltage dB's come out differently than power dB's. Look at the chart again. Increase voltage by ratio of 2 (2.0 in column B) How many dB's of voltage increase? In column A you'll find 6.

Here's why: Put 1 volt across a 1-ohm resistor. Since  $P = \frac{E^2}{R}$  or  $\frac{1^2}{1}$ , power is 1 watt. Now increase voltage 3 dB. The chart says that a 3-dB voltage in-

crease is a ratio of 1.4 to 1. So now

what's the power?  $P = \frac{E^2}{R}$  or  $\frac{(1.4)^2}{1}$ , or

about 2 watts. Power has *doubled*—and according to the chart, that is 3 dB of power gain. (The same figures work for current, by the way.)

## How to use dB's

Using dB's to measure changes in power, voltage or current makes difficult jobs easy. As an example, suppose you want to install a master antenna system in a large 40-unit apartment building. You make a diagram—like Fig. 1—

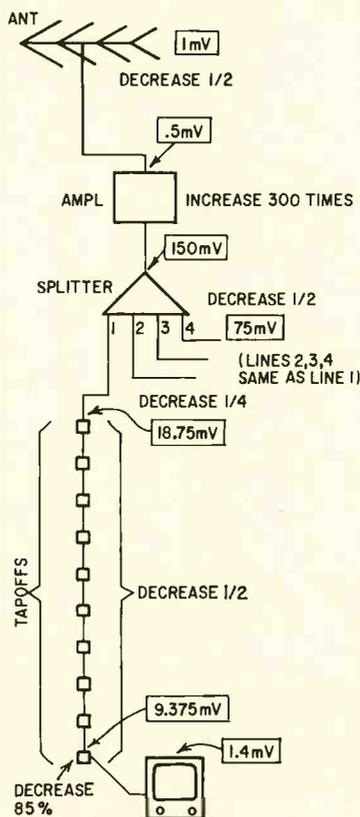


Fig. 1—Functional diagram of typical MATV system, with signal levels in volts. Boxed figures are absolute values.

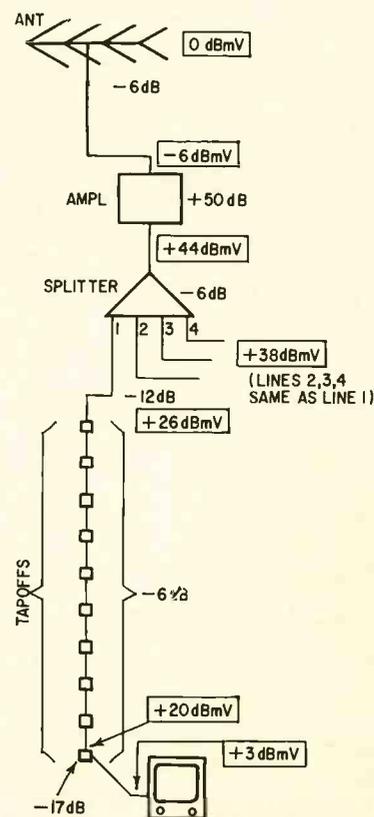


Fig. 2—Same system, using dB's. Again, signal levels are shown in boxes; gains and losses are not. See text for details.

of the equipment. Then you figure how to get enough signal to each TV to furnish an acceptable picture.

Assume you've got a 1-mV signal at the rooftop antenna, and you want no less than 1 mV at each receiver. From the antenna, the signal goes through coaxial cable, dropping to half the voltage ( $\frac{1}{2}$  of 1 mV is 0.5 mV) by the time it arrives at the amplifier, where it's stepped up 300 times (300 times 0.5 mV is 150 mV). From the amplifier, the signal divides at a four-way splitter, and each output has half the voltage of the input ( $\frac{1}{2}$  of 150 mV is 75 mV).

Next there's more coax, dropping signal voltage to  $\frac{1}{4}$  ( $\frac{1}{4}$  of 75 mV is 18.75 mV). The 10 receiver tapoffs in series cut the signal in half again ( $\frac{1}{2}$  of 18.75 mV is 9.375 mV).

The last receiver is isolated from the line by the tapoff, and this isolation drops the signal again—to perhaps 15% of the line signal (15% of 9.375 mV is about 1.4 mV). That's what the last receiver gets.

If you *like* to multiply, as we've done, you're welcome to the method. There is an easier system, though—using decibels.

But first we've got to have a reference point. A dB figure is only a measure of the *ratio* between two power or voltage levels. It does not refer to an absolute value. In TV antenna work, 1 mV (or 1,000  $\mu$ V) has become the reference point, because it is often the lowest signal that should be delivered to a receiver. Therefore, 1 mV is called "0 dBmV."

Now look at Fig. 2, where 0 dBmV is beside the antenna, to show that's the signal available there. Coax drops the signal in half, and from the table you'll find that's a 6-dB loss, so write that down and subtract it from 0 dBmV, getting -6 dBmV. (The minus sign here indicates the signal is 6 dB *below* 0 dBmV.)

Next convert the 300-times gain of the amplifier to the nearest value in the table, or 50 dB. Add +50 dB to -6 dBmV, getting +44 dBmV. (You can also do it by subtracting -6 dBmV from +50 dB; the result is the same. The plus sign here shows the signal is 44 dB *above* 0 dBmV.)

Continue through the diagram, using the table to convert voltage increases or decreases to dB gain or loss. Eventually you'll find you have about +3 dBmV at the last receiver. From the chart, you see that's about 1.4 mV.

Sure, you've had to do a lot of converting and using the table to work with dB's in this example—and it has been a nuisance. *But you don't have to do it in practice.* If manufacturers of amplifiers, splitters, tapoffs and cable told you only that their equipment would amplify a signal "300 times" or attenuate it "by 15%" you'd have to multiply and divide

to lay out a master antenna system. They don't do that, however. They give you dB gain or loss figures, and all you have to do is *add and subtract* them.

Assume you've made a plan of the apartment building. From equipment catalogs, you obtain the following figures—all the losses in your system:

Cable (ant to amp)	-6 dB
Splitter	-6 dB
Cable (spltr to last rcvr)	-12 dB
10 splitters in series	-6 dB
1 splitter as isolation	-17 dB
Total loss	-47 dB

You determine the signal at the antenna is 0 dBmV. Since you also want 0 dBmV at the last receiver, it's obvious you need at least 47 dB of gain from the amplifier. You buy the nearest thing—a 50-dB unit. See how simple it is?

### Other dB uses

Decibels aren't used solely in antenna work. Various reference levels are used in other areas of electronics. In broadcasting and recording studios, "0

dBm" is defined as 1 mW in 600 ohms of impedance. Years ago telephone companies and some radio stations used a 0-dBm reference point of 6 mW in 500 ohms. For higher-power applications, such things as "0 dBW" (1 watt) and "0 dBK" (1 kW) are used. There is even "0 dBV" (1 volt).

Notice that 0 dBm means 1 mW *only* in 600 ohms. Impedance is defined because radio, television and recording studios have standardized on 600-ohm inputs, outputs and lines. A similar situation exists in master-antenna computations involving voltage. Hence, 0 dBmV means 1 mV (or 1,000  $\mu$ V) across 75 ohms of impedance, since that's the common type of coax used.

You can't use dB's to compare voltage differences unless the two voltages are across the same value of impedance.

So you see, the dB is really not too difficult to work with. As a stranger, it's an unknown, perhaps incomprehensible element. Once you get to know it, the decibel will become a valuable tool in your electronics work. **R-E**

Decibel Table

A	B	C	D	E
dB of Voltage or current gain or loss	Ratio of increase (to 1.0)	Ratio of decrease (to 1.0)	Attenuation or loss in %	dB of Power gain or loss
0	1.0	1.0	0	0
1	1.1	0.98	11	
2	1.3	0.79	21	1
3	1.4	0.71	29	
4	1.6	0.63	37	2
5	1.8	0.56	44	
6	2.0	0.50	50	3
7	2.2	0.45	55	
8	2.5	0.40	60	4
9	2.8	0.36	64	
10	3.2	0.32	68	5
11	3.6	0.28	72	
12	4.0	0.25	75	6
13	4.5	0.22	78	
14	5.0	0.20	80	7
15	5.6	0.18	82	
16	6.3	0.16	84	8
17	7.1	0.14	86	
18	8.0	0.13	87	9
19	9.0	0.11	89	
20	10	0.10	90	10
21	11	.089	91.1	
22	13	.079	92.1	11
23	14	.071	92.9	
24	16	.063	93.7	12
25	18	.056	94.4	
26	20	.050	95.0	13
27	22	.045	95.5	
28	25	.040	96.0	14
29	28	.036	96.4	
30	32	.032	96.8	15
31	36	.028	97.2	
32	40	.025	97.5	16
33	45	.022	97.8	
34	50	.020	98.0	17
35	56	.018	98.2	
36	63	.016	98.4	18
37	71	.014	98.6	
38	79	.013	98.7	19
39	89	.011	98.9	
40	100	.010	99.0	20
42	130	.0079	99.21	21
44	160	.0063	99.37	22
46	200	.0050	99.50	23
48	250	.0040	99.60	24
50	320	.0032	99.68	25
52	400	.0025	99.75	26
54	500	.0020	99.80	27
56	630	.0016	99.84	28
58	790	.0013	99.87	29
60	1,000	.0010	99.90	30

# Imaginary numbers are a cinch

Want a low- or high-pass filter? Find out how to design your own

By NORMAN H. CROWHURST

WHEN I NEXT DROPPED BY GEORGE'S lab, he'd been doing his homework on imaginary numbers. He'd made a neat tabulation of all the results he could find about the simple two-element low-pass filter we had been working with and started extending it to a three-element type. Now he wanted to know more.

"I think I could go ahead with more complicated low-pass filters, with a little trial and error," he said. "I suppose you can apply the same method to high-pass filters, but I couldn't see it."

"Let's just reason it out as we did for the low-pass." I sketched a high-pass circuit and started translating its per-

formance into an equation (Fig. 1). "The output is an inductor in shunt with the terminating resistor, and its normalized value is unity. We let the inductive reactance be represented as  $b$  units at cutoff frequency, as we did with the shunt capacitor of the low-pass filter. Should these units represent reactance or susceptance really, at cutoff frequency?"

"That's what had me stymied," admitted George.

"You can use either, with the proper care," I went on. "I find it simpler to use *susceptance* for all shunt elements and reactance for all series elements. Then we show its variation with frequency and phase of the elements by where we write  $x$  and  $j$ ."

"So the susceptance of the inductor will be  $jb/x$ ?" queried George, who

had obviously been thinking about this.

"Last week we set a standard about phase for this kind of calculation," I reminded him. "It was that a  $+j$  means the quantity *leads* the reference quantity. Here, reference quantity is voltage across both the output resistance and the shunt inductor, so the  $j$  applies to the inductor current."

"And current lags voltage in an inductance," went on George, "so it should be  $-j$ , right?"

"Right. But an easier way is to just remember that the  $j$  and  $x$  always go together; this automatically takes care of the sign." I showed him that  $b/jx$  is the same as  $-j(b/x)$ . He was already figuring out the expression for this high-pass filter.

George was taking to the use of  $j$  like a duck takes to water. In short order, he had the phase and amplitude expressions figured out, as well as values for  $a$  and  $b$  for the constant-resistance type. He set these down alongside those he had tabulated for the low-pass unit.

"Hey," he said, "the values and, when you make  $ab = 1$ , the phase angles are the same for both, except for the sign. What does that mean?"

"Simply that the transfer phase of these two filters is  $180^\circ$  apart at all frequencies, when they use the same cutoff frequency as in a crossover."

"Can you also show from this that a crossover like these makes constant resistance and delivers constant total power?"

"For power, take the reciprocals of the amplitude-squared expressions, and add them," I suggested, which he did (Fig. 2) almost as quickly as I said it, and found the answer reduced to  $1/1$ .

"Does that prove the constant-resistance property as well?"

"Not directly, you need to figure out the input admittance of each filter and then add the two together." I showed him step by step how to do this for the low-pass (Fig. 3). He did the same for the high-pass, converted to

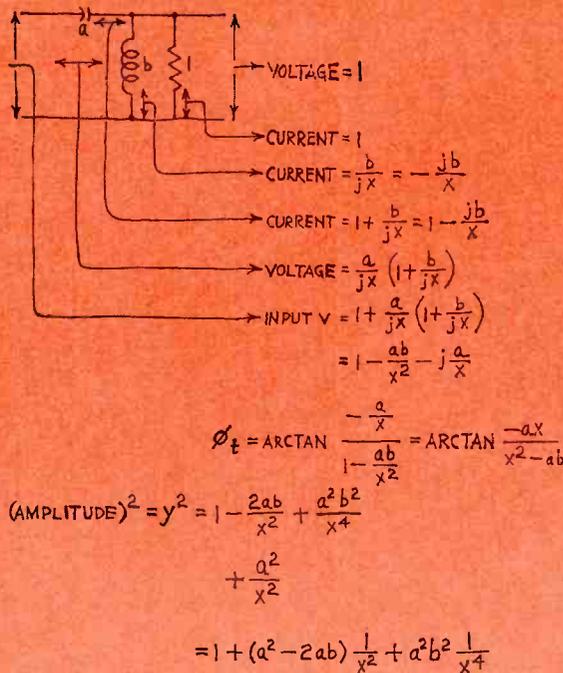


Fig. 1—Diagram of a high-pass filter, and what it does in simple math terms.

FOR  $90^\circ$  AT CUTOFF:  $ab = 1$   
 FOR 3db AT CUTOFF:  $a = \sqrt{2} = 1.414$ ;  $b = .707$   
 EACH REACTANCE IS 1.414 TIMES TERMINATING RESISTANCE AT CUTOFF

x instead of 1/x as the variable in this case, added them, and found the sum was again equivalent to 1/1.

"Show me a three-element low-pass design," George asked. I drew the design (Fig. 4-a). I put in a, b, and c to represent the normalized reactance and susceptance of the elements at cutoff, and we started figuring.

"The voltage across the output inductor is jcx," said George, "so the total voltage at the mid-point capacitor is (1 + jcx), isn't it?" I nodded, so he went on, "Then the current through the capacitor is . . ." and he wrote it out: jbx (1 + jcx). "Now what?"

"What's the current through the input inductor?" I suggested.

"It's the current through the capacitor, plus that going to the output—is output current I?" he asked. I nodded, so he wrote, for current in the input inductor: 1 + jbx(1 + jcx). "Then the voltage across the input inductor is . . ." and he wrote out:

$$jax \{ 1 + jbx (1 + jcx) \}$$

"Now you just add the voltages together to get the input voltage," I suggested, sketching in the voltages on the schematic. By this time George was working it, to come up with the answer:

$$1 + jcx + jax \{ 1 + jbx (1 + jcx) \}$$

"Yuk," he commented, so I took over and removed the parentheses, till we had:

$$1 - abx^2 + j(a + c)x - jabcx^3$$

"Now what?" asked George. "Just solve for a, b, and c, I suppose you'll say."

"That isn't as difficult as you might think, for the constant-resistance or maximal-flatness case. First, let's figure out the amplitude-squared expression."

George squared the real and imaginary parts and added the terms in x<sup>2</sup> and x<sup>4</sup> to come up with

$$1 + [(a + c)^2 - 2ab]x^2 +$$

$$[a^2b^2 - 2abc(a + c)]x^4 + a^2b^2c^2x^6$$

which evoked another "Yuk!" when he'd finished.

"Well, we can simplify that somewhat," I said. "First we want the rolloff asymptotic to cutoff, so the coefficient of x<sup>6</sup> must be one."

"Come again," said George, confused by the abstract math terms.

So I sketched out the response on log/linear paper (Fig. 4-b). I explained that the 1 of the amplitude-squared expression represents the horizontal part of the response in the passband, while the x<sup>6</sup> of the last term represents an 18-dB-per-octave slope, crossing the zero line at cutoff frequency.

"So that means abc must equal 1," George promptly made that substitution

by crossing out abc and a<sup>2</sup>b<sup>2</sup>c<sup>2</sup>.

"Next, for maximal flatness, the terms in x<sup>2</sup> and x<sup>4</sup> have to disappear," I told him.

"So the whole thing boils down to just (1 + x<sup>6</sup>)?" asked George, and added, "Oh, I see now what you meant by its being asymptotic."


I nodded. "The curve approaches

a straight line, but never quite gets there."

"That's negotiable," he said, writing out (a + c)<sup>2</sup> - 2ab = 0 for x<sup>2</sup> and a<sup>2</sup>b<sup>2</sup> - 2(a + c) = 0 for x<sup>4</sup> (Fig. 5). Then he looked stumped.

"Because abc = 1, how about writing 1/c for ab?" I suggested, which he

(continued on page 71)

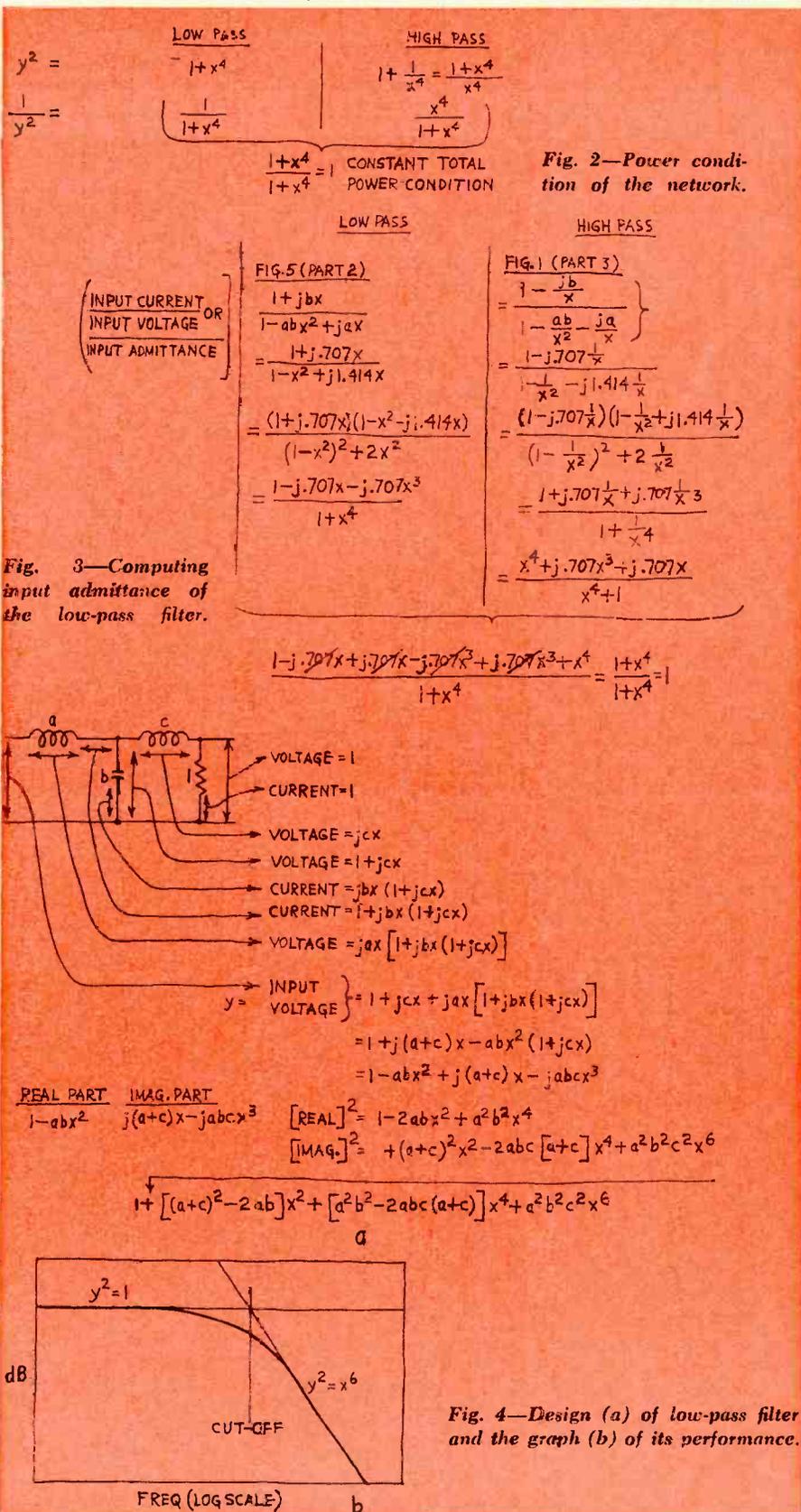


# ULTRASONICS

## NEW TOOL
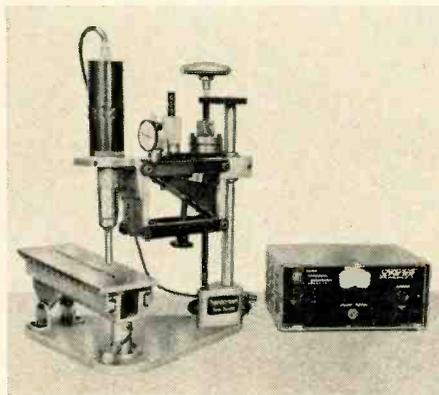
## FOR INDUSTRY

There are more technical applications for ultrasonics than you may realize By PAT MCDONALD



(Courtesy Branson Instruments)

An ultrasonic welder speeds fabrication of plastic containers, etc., providing a continuous welded seam at 100 ft/min.

MOST RADIO AND TV SERVICE TECHNICIANS have some knowledge of simple ultrasonic devices. The remote-control channel changer supplied with many TV receivers, for example, is a very basic ultrasonic generator. Watchmakers and auto mechanics may have in their shops ultrasonic units designed for degreasing and super cleaning; most technicians and experimenters are at least aware that such devices exist. But do you know that other industrial applications employing ultrasonic waves include welding, atomizing, mixing, polishing, flaw detection in metals, and gas-and-liquid flow-monitoring devices, among many others? Because electronic circuitry is so much a part of ultrasonic devices (sound waves behave very much like electrical and radio-frequency waves) technicians will find much that's familiar in such equipment.

From frequencies as low as 20 kHz to an upper limit of several-hundred GHz or more, ultrasonic energy offers an expanded horizon for technicians and industrial engineers.

Ultrasonic devices fall into two principal categories: one employs sound energy directly as a power source to perform useful work; the other uses the high-frequency sound waves as a signal source for sensing, measuring, or carrying information.

In nearly every application, ultrasonic generators and transducers (devices which transform electrical energy into mechanical force) are part of a more complex electroacoustic system.

### Soldering and welding

Straightforward soldering techniques are used for joining many metals. Aluminum, however, cannot be soldered using familiar practices, because of the oxide film which forms a barrier to fluid-metal bonding. Abrasive removal of the oxide barrier and the use of corrosive



however, permits bonds to be made on difficult-to-solder metals such as aluminum, as easily as brass or tin can be soldered using conventional techniques.

In ultrasonic soldering, vibrations are applied through a transducer to the tip of the iron or, as in the case of a dipping bath, to the vessel containing the molten solder. The ultrasonic energy produces a violent agitation, the action of which removes the oxide film and allows a "wetting" action to take place, thus permitting a bond. No flux is required, and the danger of corrosion due to flux remaining in the joint is avoided. Fluxless soldering on delicate silicon and germanium surfaces in semiconductors can be accomplished readily.


Welding metal foils ordinarily is difficult, because thin-film metals are extremely delicate. An ultrasonic foil welder incorporated into automated foil-packaging machines, however, effectively eliminates foil damage and provides an hermetic seal. Such a welder may be added to systems using fixed or movable welding heads.

fluxes generally are required to obtain a satisfactory metallic bond. Even then, the work is slow, the joints sometimes marginal.


Ultrasonic soldering equipment,

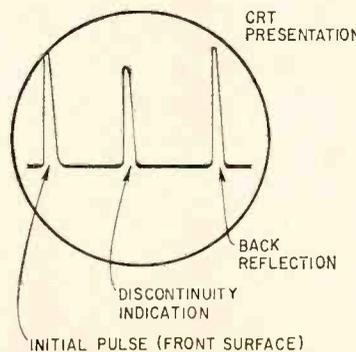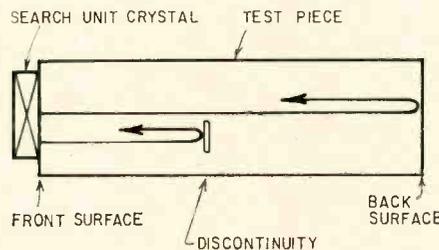

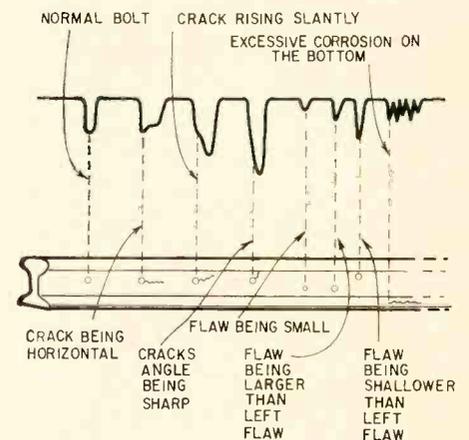Similarity of ultrasonic flaw detection to radar echo ranging is easily seen. Scope presentation also is much the same.



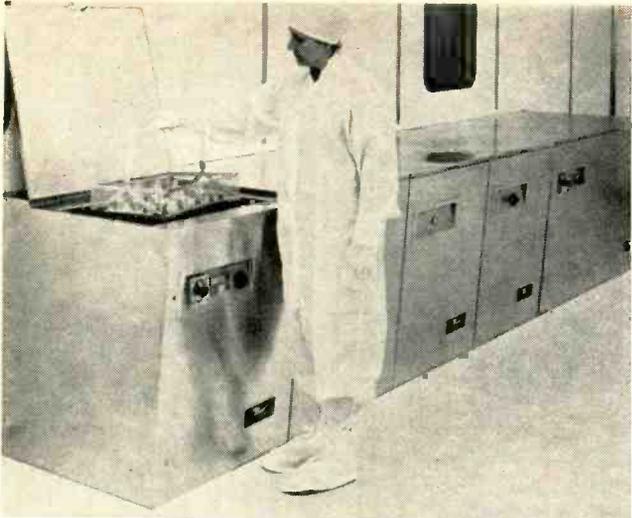Plotted curve of signal current of track flaw detector indicates response to various types of commonly encountered flaws.



(Courtesy Bendix Corp.)

*Industrial ultrasonic cleansing baths have become common in spaceage and defense work where absolutely clean parts are needed.*

A similar technique also may be applied to most thermoplastic materials—Mylar, polypropylene, polyethylene, Nylon and Dacron. Here, as in metal bonding, the plastic material remains cool, regardless of how long the welder tip remains in contact with it. Continuous welding can be carried out at rates as high as 100 ft/min, depending upon the type of material and its thickness. Since there is no heat, flammable materials can be welded or encased in plastic containers without risk of fire.

#### **Nondestructive testing**

Ultrasonic material-testing techniques have given industrial quality-control and inspection technicians a valuable tool. Using ultrasonic inspection procedures, it's possible to detect flaws that cannot be uncovered by any other nondestructive method.

This testing technique uses short bursts of ultrasonic energy (sonic wave trains) generated by a piezoelectric element and transmitted by contact into the material under test. Any discontinuity in the structure of the material represents an acoustic barrier. Some of the sound energy will be reflected to the source, in a manner not at all unlike the echo responses obtained in various types of radar and sonar systems.

The piezoelectric transducer or "search" unit also may be used to convert the reflected ultrasonic energy into electrical energy, so that echo amplitude and return time may be indicated. The interval is proportional to the distance between the flaw and the entry surface.

Energy also will be returned from the opposite surface of the material and may be used to indicate the actual length of the part being examined. Such measurements obtained on calibrated instruments can determine the thickness of a wide variety of products; cathode-ray tubes and other electronic devices are used to display the information.

A thoroughly practical flaw-detection device has been designed to prevent train accidents due to rail fractures. The system is able to detect cracks and other structural flaws before they become serious enough to endanger passenger safety. To obtain an analysis of the rails, frequency-modulated ultrasonic waves are projected into the rail surface at right angles to the lay of the track. The frequency of the ultrasonic energy is resonant to the mechanical cross-section of the rail. Any change in the resonant frequency as a result of a structural discontinuity due to the presence of cracks or other flaws is detected visually by means of a meter and aurally by headphones.

#### **Leak detection**

The usual method of detecting pressure leaks in industrial gas systems is to apply a soap solution to various systems components and connections and watch for bubbles caused by a leak. A much more modern and effective technique is to use an ultrasonic translator to detect ultrasonic sound pressures escaping from the system. Typical translators can detect pressure leaks at distances greater than 50 ft. This distant-detection capability, combined with the use of a directional probe, permits locating leaks without a minute examination of the entire system.

#### **Ultrasonic sensing**

Ultrasonic transducers can be used in place of electric-eye sensing devices to detect a wide variety of objects. Since the ultrasonic beam can "see" in darkness and in spite of dust, smoke, steam, fog, high ambient light levels, humidity, vibration or contamination, most of the electric eye's shortcomings are thereby eliminated.


Using a direct beam, transmitting and receiving transducers (sensors) can be positioned to face each other for di-

rect ultrasonic energy transfer. In cases where the sensors might be damaged or otherwise adversely affected when positioned near moving material (as in bin-leveling applications), reflective-beam operation is best. In either, a relay can be made to drop out or pick up upon beam interruption.
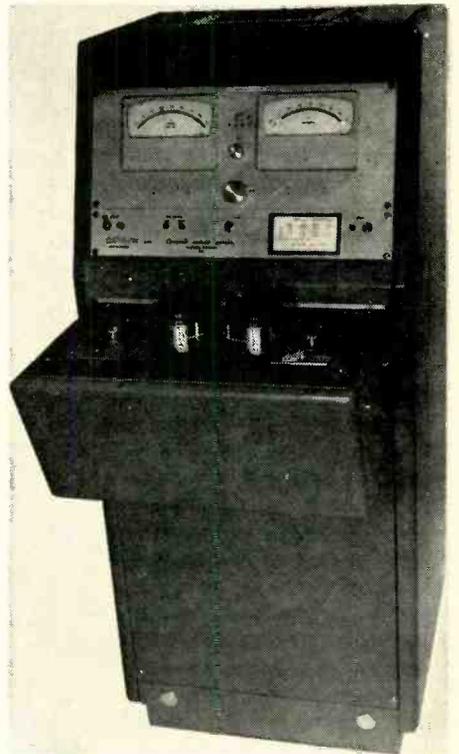
#### **Cleaning**

The "scrubbing" action of liquids agitated by ultrasonic waves makes it possible to use ultrasound to clean objects which otherwise would require extensive soaking, boiling, and scrubbing. The action of countless tiny bubbles in the cleaning solution literally "scrubs away" dirt, grease, and almost any other contaminant.

The intensive, deep cleaning obtainable through the use of ultrasonic



(Courtesy Chesapeake Instrument Corp.)


*Almost instantaneous readout of butterfat percentage and SNF percentage is possible using this dairy-industry ultrasonic unit.*

techniques has proved especially valuable in medical technology and aerospace operations, situations where absolute cleanliness is required to avoid contaminating human life or a multimillion-dollar space probe that could infect an entire planet or stellar system.
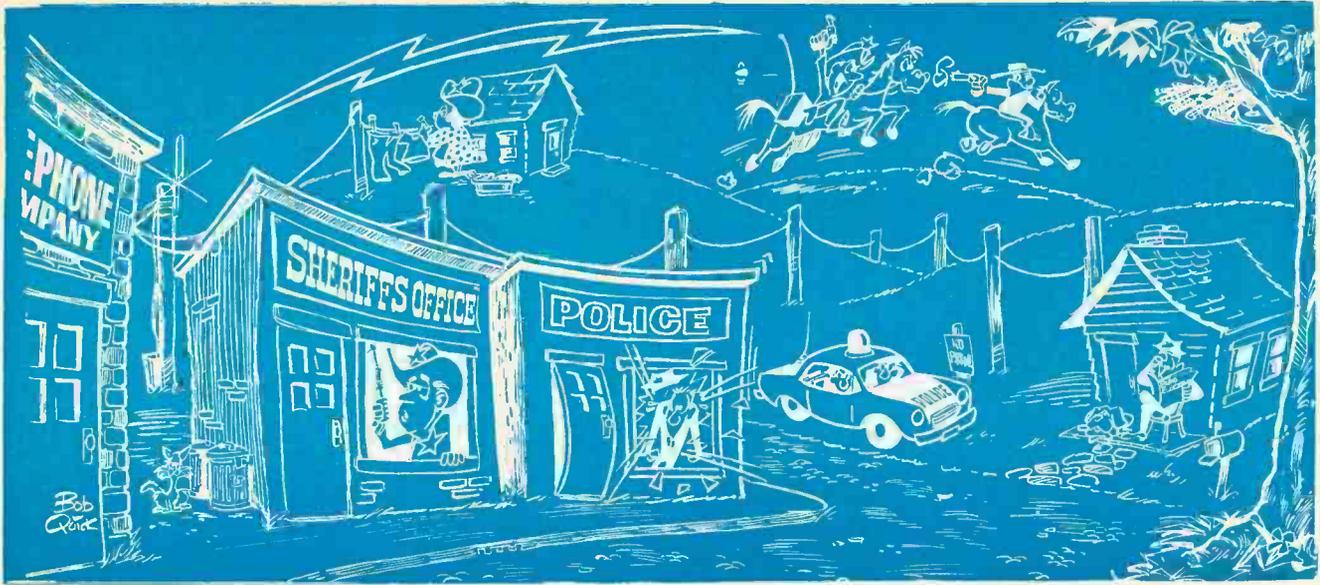
#### **Chemical action**

Many chemical reactions are accelerated by ultrasonic energy, while others are inhibited. Solutions also can be mixed or homogenized efficiently through various high-frequency agitation procedures.

The vaporization of many liquids  
(continued on page 82)



# Audio Levels on Long Communications Lines

When several dispatch points are used in a two-way radio system and audio levels to the transmitter aren't the same, here's how to equalize them **BY EUGENE AUSTIN**

BACK IN THE OLD DAYS, INSTALLING A TWO-WAY SYSTEM meant plunking down a tin box and a mike on the sheriff's desk, hanging an antenna from the chimney, bolting a couple of boxes and a whip on his car, and then you were in business.

In recent years, I found myself ordering progressively more sophisticated equipment, and more of it. A short time ago, I loaded up a truck to the roof with mobile transceivers, and spent the next week installing them. In the meantime, the rest of the crew had loaded up a tin outhouse, carried it out on top of that big hill way out in the boondocks, and bolted it down on a cement pad at the foot of a 100-foot-plus tower.

Then they hooked up one end of a network of leased telephone lines and ran all over town hooking remotes to all the other ends.

And that's where we all came a cropper!

When they got done, I ran out and sent in a 0-dBm signal from all remotes, and thought we were ready for business. Trouble was the police dispatcher climbed down my throat because he could hear the sheriff's office perfectly, but the sheriff's house was so far down in the mud nobody could find him. If they turned up the volume to hear the sheriff's house, the first car that came on the air could be heard in the city clerk's office—seven doors down the hall.

Out in the cars it was even worse. If I set the modulation up for the police department, no sheriff's house. If I set up for the sheriff's house, the police dispatcher sounded like he had just swallowed a hot soldering iron. Also, we could hear every dog barking, every kid screaming, and every horn honking for two blocks around.

Having worked one summer on toll telephone systems, I took one look at a block diagram of the phone lines, and knew what I had on my hands. It was a network of bridged (paralleled) telephone lines that looked like it

had been spun by a drunken spider. Every segment was a different length, and the loss figures varied over 10 dB from one to another. Einstein would have choked trying to figure out loss figures with a pencil.

I studied the thing for all of ten minutes, and threw up my hands. It looked like the best bet was to set up to deliver consistent audio to the transmitter—thus keeping

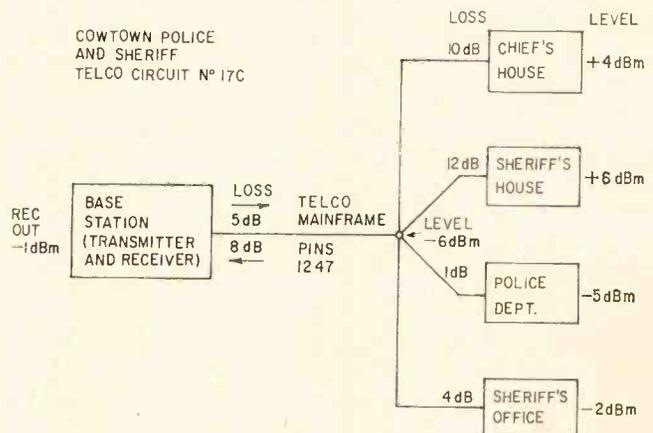


Fig. 1—Signal levels and line losses through typical system.

the FCC off the customers' backs. At the time, I was convinced that Satan himself couldn't control the blasting between remotes.

Soooo—I made sure all the equipment was connected, and stationed a man at the transmitter with a high-impedance dB meter. Then I went around to each remote and put 0-dBm into the line, at 1 kHz. The other man measured the loss, and noted it on a circuit card similar to that shown in Fig. 1.

That done, I called the phone company, and learned that their maximum permissible level was +6 dBm (or 6 dB above 1 mW).

After studying the block diagram, I realized that, to deliver consistent levels to the transmitter, the remote on the end of the longest segment would have to transmit the highest level, because it had to overcome more loss than any other segment. Sure, that was a lot like signals in a CATV system—only backward.

I arbitrarily assigned the line segment with the highest loss—the sheriff's house—the maximum permissible level of +6 dBm.

I took my measured loss figures and figured what level

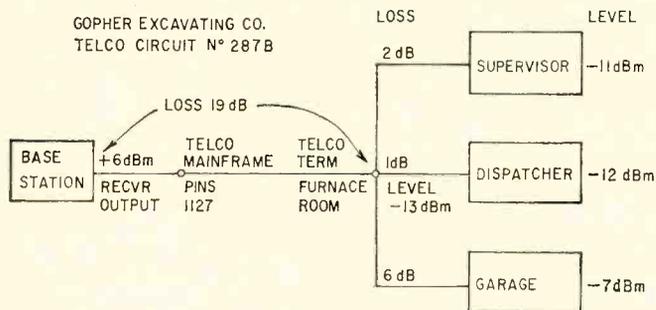


Fig. 2—Sometimes there are two common points within a single system. Levels at each should be maintained the same.

this +6 dBm from the sheriff's house would push through the transmitter. With a total line loss of 20 dB, the transmitter would receive -14 dBm.

I then figured backward and determined what level would be necessary for each remote to deliver -14 dBm to the transmitter. For the chief's house, with a loss of 18 dB, a transmit level of +4 dBm was necessary. For the police department, with only a 9-dB loss, a much lower transmit level of -5 dBm was necessary.

I set up each line in the system this way, adjusted modulation, listened to the various remotes on the monitor, and called it done.

I hadn't any more than hit the shop when the police dispatcher called. "Boy," he said, "this is more like it! I can't tell whether the sheriff's talking from his house or his office, they're that much alike. That's the way it ought to have been in the first place."

I mumbled something or other, hoping to convince him that I had planned it that way, and hung up quick. I sat down and asked myself: "What happen? What'd I do?" I got out the circuit card, looked at it for a while with a completely blank mind, then something snapped between my ears, and a great light dawned.

I had set up to deliver consistent audio to the base. Since all audio came together at a common gathering point on the telephone company's main frame and traveled down a common line from there to the transmitter, it followed that I had also unknowingly set up to deliver consistent audio to the common point. It came out to -6 dBm.

Look at it from the police department's viewpoint: If all three of the other remotes delivered a consistent audio to the common point at -6 dBm, this signal would travel down the common line to the police-department remote, losing about 1 dB on the way, and arrive there at a still-consistent level of -7 dBm. (Each remote station receives any audio on the network, whether from the base-station receiver or from another remote station.) All we had to do then was adjust the police-department input level to -7 dBm and we were set.

Or take the sheriff's house: If all three other remotes delivered a consistent signal of -6 dBm to the common

point, this audio would travel down a common line to the sheriff's house, dropping about 15 dB on the way, and arrive there at the still-consistent level of -21 dBm. So all we had to do then was to adjust the sheriff's level for -21 dBm and his station received properly.

Realizing that all I had to do was set the receiver up the same way, I went back and measured the loss from the receiver to the common point. I got 5 dB loss, so I set the receiver to send -1 dBm down the line.

We did some later testing, and found that there wasn't the slightest sign of blasting anywhere. We decided we had somehow overlooked one key fact: The transmit level from any particular remote has no effect on blasting on that remote, because the receiving circuits in it are cut off during transmit. Obviously, blasting is strictly an incoming-signal problem. We could juggle transmit levels all over the place without causing local blasting.

Since that time, I've worked out a cut-and-dried setup procedure that works about 75% of the time. Specifically, it works on the 75% or so of all multiple-remote systems that have their lines tied together at a common point somewhere in the system.

Here's my technique:

1. Make sure all equipment is in place and connected. Two reasons: First, an unconnected end will not show working load, and will throw the whole system out of balance when finally connected. Second, the open end of a long telephone line will introduce all kinds of crosstalk and hum. If you absolutely must set up part of a system, have the phone company tie in the unused segments. Then, go out and connect a 600-ohm resistor across each end where a remote will eventually be installed. Leave it there until the equipment actually replaces it.

2. Make up a circuit card, like Fig. 1. Essentially, this is just a glorified block diagram, with telco circuit numbers and frame-connection locations added. You'd be surprised

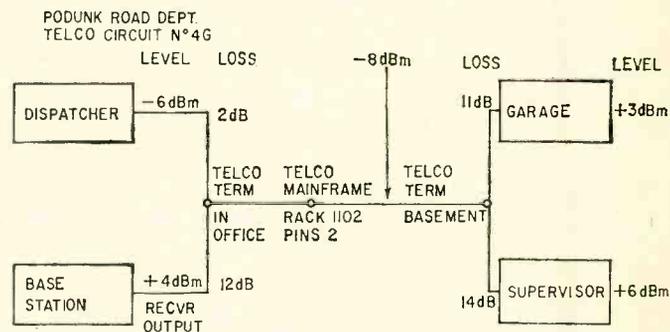


Fig. 3—If there's no actual common point in the system, you'll just have to set up for uniform audio level at the transmitter.

how much this information helps when you have to test a line in the middle of the night. I like to use the cardboard shirt stiffeners that come in my laundry. They are big enough to hold a lot of information without crowding, they just fit a file folder, and they are durable enough to lug around in the truck without getting dog-eared.

3. Send a man with a high-impedance dB meter (or audio vtm) and the circuit card to the common point. Be sure the meter is high-impedance. Some dB meters, intended for toll telephone work, have a 600-ohm resistor across the input. Such a meter loads down the line and gives false readings.

4. Go around to every remote point and to the base, and put a 0-dBm, 1-kHz signal into the line for the other man to measure and note. Two precautions: First, always

(continued on page 73)

# BINARY COUNT DEMONSTATOR

Simple neon-lamp flip-flops demonstrate binary counting

By RUSSEL AYERS

AT THE REQUEST OF ONE OF OUR LOCAL teachers, I undertook to prove to his students that, believe it or not, 10 equals 2 and 100 equals 4.

No, there was nothing erratic about the request nor my immediate willingness to take on the project. In point of fact, I was being asked to develop a simple binary counter. And, in binary notation, as will be explained further in the article, these examples are correct.

When this neon-lamp counter was suggested as a classroom visual aid, I thought of the numerous articles on relaxation oscillators, flashers and such which would make the device comparatively easy for me to assemble. However, I quickly realized that there were a few more problems than I had anticipated, to say the least.

Certainly, flip-flops and triggering circuits employing neon lamps had been published by the dozens. But nowhere could I find a description of one that generated enough output power to trigger reliably another stage following. Only one or two even purported to. None actually did. And this is the one feature absolutely essential to a binary series or operation.

A hard look at the problem led me to see that what power there was being generated in the normal neon flip-flop tended to expend itself around its own internal loop. I divided the standard commutating capacitor in two, returning each half to the more stable mid-load point, and succeeded in getting more of the switching kick channeled out to trigger succeeding stages. Four well-demarcated stages were constructed and tacked in series.

The results were unexpected and disappointing. The best stability I could get was with a Variac at the line input to the doubler supply. This showed that each stage tended to settle down at one certain voltage. None, however, were the same as any other. Pots were put in all four of the decoupling networks. This permitted each stage to be adjusted to its most stable point. Things did settle down considerably, but double-tripping

took over as the general order. That is, a trigger was produced at the following stage on the flip as well as on the flop.


Some random single-excursion triggering did occur, though—enough to indicate that proper switching should be attainable. Matching lamps for ionization points and sustaining voltages had seemed an obvious precaution at the start. Now I found, confoundingly, that substituting lamps that did not match quite so well often produced better triggering action.

More pots were installed. This time in the common negative leg. They appeared to help. But it was only after

more lamp substitutions—plus a few other experimentations, as a result of nothing in particular—that all at once a proper binary sequence began to click off. Through all four stages. From the first pulse, nicely right out through binary 15 (1111) and back to zero, or 16 if you prefer, it carried.

Five minutes later it quit. Perverse-ly, it began double-tripping again. And it persistently avoided another correct sequence the rest of that session.

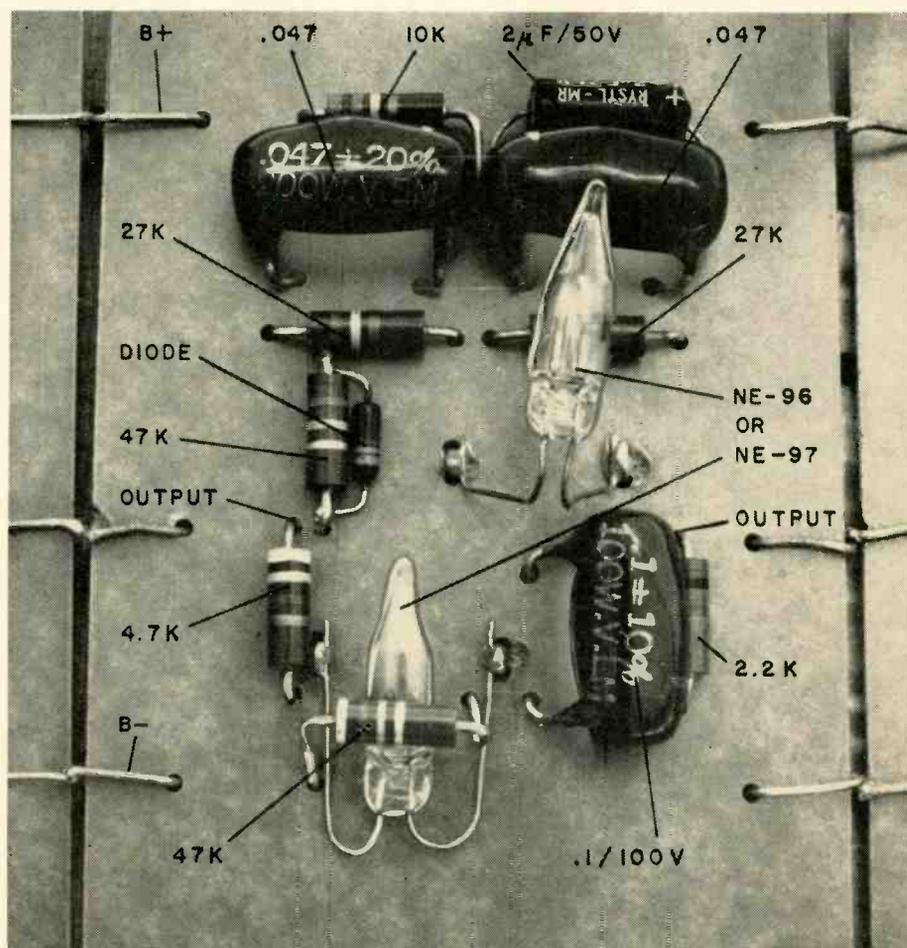At the next session more lamp interchanging brought back periods of stable switching. Still, one lamp after another would fire out of sequence.



An experimental flip-flop mounted on a board (one of several sections in unit).

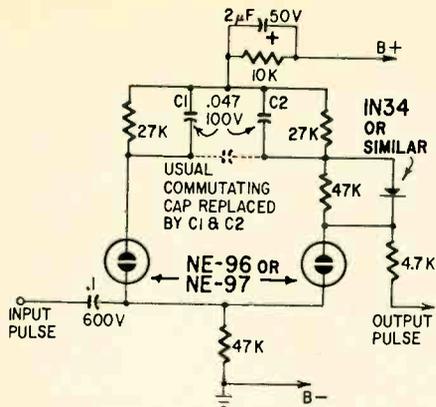


Fig. 1—One section of the flip-flop counter circuit which divides by two.

Then, and for no apparent reason, one of the lamps showed a very pale purple glow. This was quite different from the normal rich orange glint.

The oscilloscope showed that, not only was there high-frequency oscillation in this one lamp, but nearly every other lamp was producing heavy transients of the same sort. It was caused by the unbroken lineup of capacitors and lamps, bridged by other capacitors and lamps, that extended down through the entire string of flip-flops. That glut of reactances being stabbed by every voltage shift anywhere created the wild transients and ringing.

Isolating resistors were inserted to act as dampers. A 4,700-ohm resistor in the output pulse lead serves that purpose in the finished unit (Fig. 1). Now and then a very touchy lamp will need more than 4,700 ohms. The neon flip-flop shown in the photo also had 2,200-ohm isolating resistors in the input leads. You can omit either the output or input isolators in most instances.

With isolation, a much greater measure of reliable triggering could be maintained. Still, it held only within very narrow limits. And having a closely regulated supply for this simple little rig made no sense at all. Double-triggering kept creeping in. The trigger of undesired polarity was finally suppressed by a diode-resistor combination, placed just back of the isolating resistor.

### Latitude and stability

Thus the circuit attained an appreciable degree of working latitude. So, at this juncture, the whole thing was gone over. All-round stability got a big boost. Even lamps stopped being so terribly critical. And the common circuit you see became feasible.

A number of interesting experiences deserve recounting: 1. Use NE-96's. Not NE-2's. They are 20 cents each against 10 cents. But you will hunt through 20 of the cheaper ones finding one workable lamp pair. 2. Put the eas-

iest-to-ionize pair at the input. A safer way to do this is to connect the finished unit, except for the pulse leads. Then advance the power-supply pot (Fig. 2) slowly, and observe the order in which each flip-flop becomes a free-running multivibrator. Reconnect them in that order, the first going at the input. 3. Put a 200-volt zener diode across the power supply output (with a heatsink) to minimize adjusting the 10,000-ohm pot.

Fig. 3 is the circuit of a relaxation oscillator that you can use to drive the flip-flops when used as a demonstration counter. With the R-C values shown, the oscillator delivers one trigger pulse every 4 seconds. You can throw S1 to MANUAL and then use switch S2 for manual control.

Do not merely shift the lamps. Lamps that ionize a test a little before another pair may not do so when in the working circuit. Nor will lamps shifted from one working circuit to another hold their order. Even the best 5% resistors and capacitors have enough variance to effect these changes. Actually, closely matched pairs will interchange

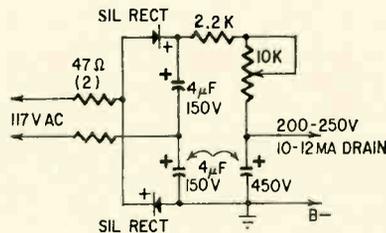


Fig. 2—Power supply for demonstrator.

without impairing switching. But a pair that ionizes 4 or 5 volts ahead of another might trigger right through a slower pair, which offers not a flicker.

Each flip-flop uses two neon lamps but only one is used as a count indicator. These are the ones visible in the photo. The other six are hidden behind the numbered plastic panels. The indicators are called "up" lamps.

Investigation of such things as optimizing frequency response would have been clearly immaterial as a training aid. As the counter stands now, even industrial applications such as batching counters would not tax it.

Say objects were coming off a production line too fast to count, but a record was to be kept of the dozen-per-minute rate. Watching for the "up" lights on the last two flip-flops ("4" and "8") would do it. A reset to zero would be needed, to keep the count from going on out to 16 each cycle. The "8" and "2" "up" lamps would obviously batch 10's. This is done all the time in automation, with standard transistor modules, though it is usually much too fast to see. A running count is always decimal, so

binary-to-decimal conversion is done at every stage in automation. Computers do it only at the final readout.

Which brings us to those who may not yet have fully penetrated binary. This too-often-misrepresented, super-scientific system of counting can be cut down to size this way. Binary is cloven-hoof counting. People, having 10 fingers at hand, quite as naturally keep count in tens. They just do not group things in pairs or multiples of pairs.

### High-speed computers

But computers do. And the flip-flop circuit is the element that forces them to do it. It kicks from this side to that side, and then back to this side again. And that is all. Trying to make it switch in some other fashion would tend to create confusion. Let it simply flip, and flop back, and it can rather easily be set to do this a million times in one second without a bobble. Moreover, setting either its flip or its flop to trigger another just like it is equally easy. One unit counts pairs. The next triggered unit counts pairs of pairs, or 4s. Then 8s. And we come out with a simple doubling progression.

The notation for binary is really simple. A zero is used to indicate a double. Start with 1. Add a zero and you double to 2. Add another, it is 4. It looks like 10 and 100. But it is actually two doubles. Add another and you are up to 8. It has grown to eight more counts and the input flip-flop would have to tick off to double again. You reach 16, and you have a five-figure term: 1 and 0000. But consider 1 and 000000. It looks like a million. It is actually only 64.

Very properly, the binary system can be regarded as a clumsy notation,

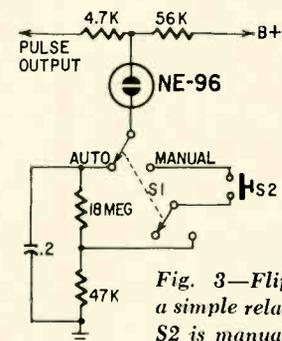


Fig. 3—Flip-flop driver is a simple relaxation oscillator. S2 is manual trigger switch.

and a clumsy way to count. But a computer can trip along to a million before you can jot down 64 in the normal way. By the time present-day second graders are grown, binary will be pre-eminent. But there is no real cause for alarm. Recently, a couple of second-graders, children of an old friend, had it down pat in 15 minutes, studying the rough little demonstrator in the photo.

R-E

## **Confused by all the ads for home training in electronics?**

### **find out what it's really all about from the leader...**

With RCA Institutes Home Training Programs you get:

- As many as 24 valuable kits at no extra cost.
- The AUTOTEXT programmed method of learning electronics faster, easier, almost automatically.
- A unique easy-pay Tuition Plan.


CLASSROOM TRAINING ALSO AVAILABLE. For special catalog and full information, simply check the appropriate box on the attached card.


All courses approved under the new G.I. Bill.  
Accredited Member National Home Study Council.

RCA INSTITUTES, DEPT. RE-28  
320 West 31st Street, New York, N.Y. 10001



The Most Trusted Name in Electronics

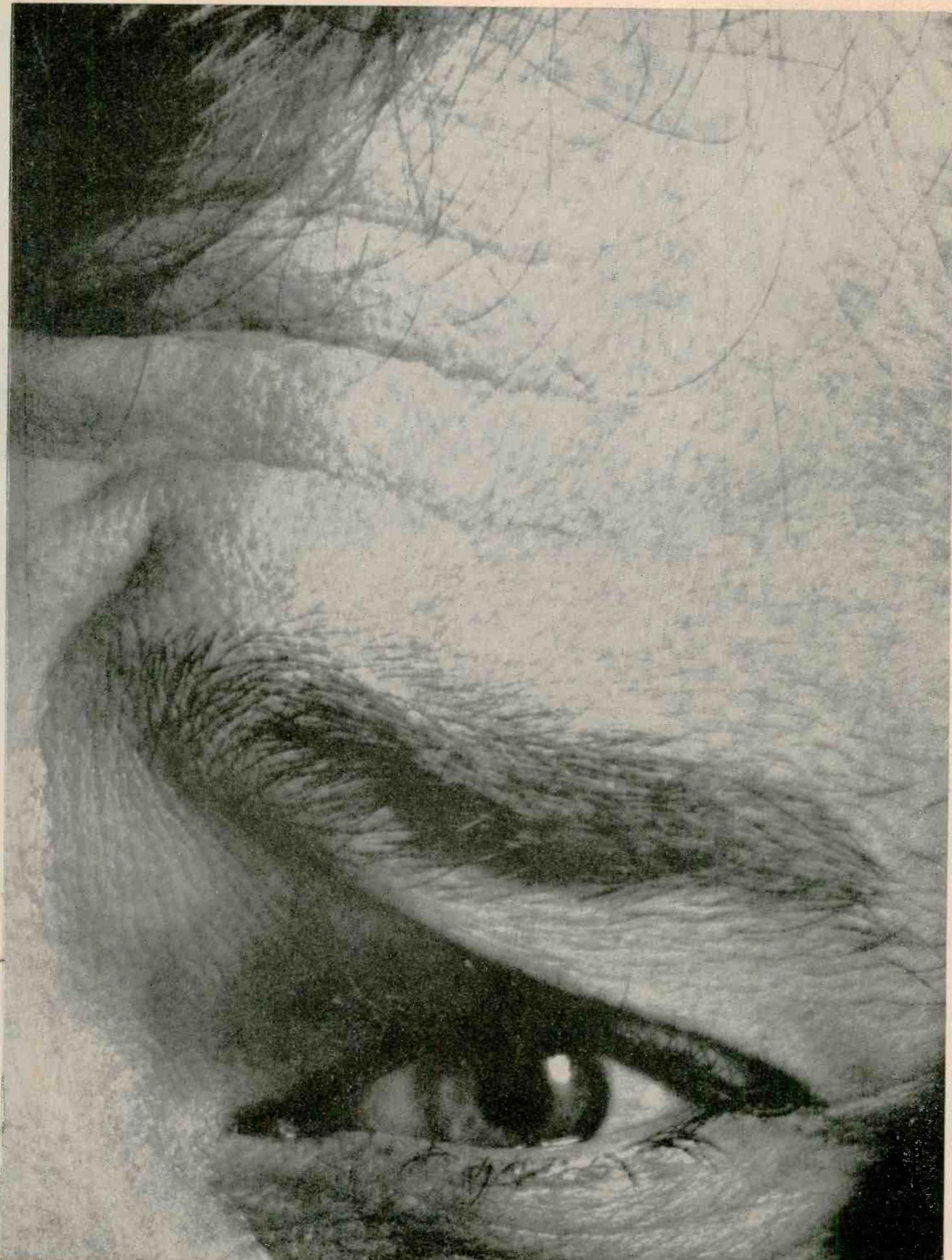

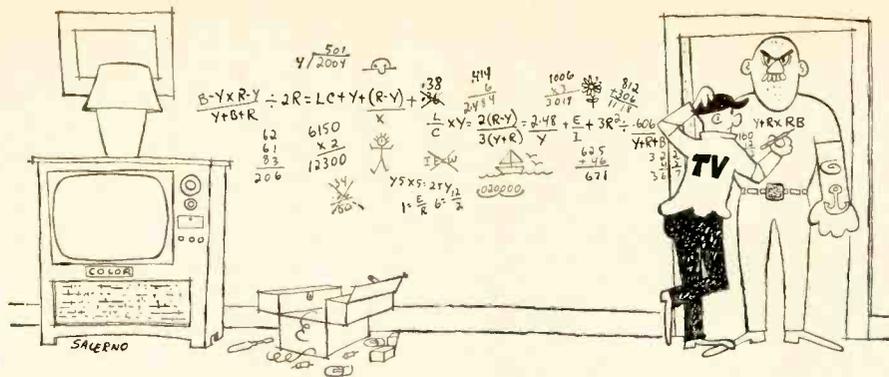

Illustrated by Frank Salerno

# The Technician Who Knew Too Much

Or, don't sell the newcomer short

By WAYNE LEMONS

"IT COULD BE THE PICTURE TUBE," Jack said, "but I don't think so. It does have the characteristic blink that a black-and-white tube gets when the cathode opens intermittently, but since the color stays and since a color tube has three cathodes I'm pretty sure they're not open and certainly not all of them."

Jack Cline—a tall, almost skinny, red-headed TV technician—was talking to a customer. Jack is known as a good technician.

He belongs to a local civic club, takes part in the PTA, goes to church on Sunday and yells good-naturedly at the referees at ball games. But Jack has never forgotten that his chosen trade is electronic servicing and that he has to keep learning all the time.

And today, Jack would soon be wondering if he shouldn't go back to school to learn more about throwing stones in glass houses.

An old friend (or at least that's what he'd always thought) had taken his color set to the new technician in town. This guy had been a shop apprentice in the next county and had just opened a place around the corner from Jack's. And Jack, with more work than he could do, was happy for the competition.

## Bad picture tube

The new man had diagnosed the trouble as a bad picture tube. Now Jack's "friend" wanted an expert diagnosis . . . "after all a picture tube costs a lot of money!"

Jack had stifled a natural inclination to sarcasm as to why he hadn't been consulted first and continued, half to himself, "The video, all of it, is dropping out and the only thing left is the color."

Jack turned down the color con-

trol to make a b-w picture; the picture blinked off and on but there was no change in color or brightness. Or, if there was, it was so slight as to go unnoticed.

"Can't you check the tube on your picture-tube checker?" his customer asked. "The other guy didn't have one."

"I could," Jack agreed, "and I will, but don't expect too much. When it's an intermittent condition you can't always depend on a test to find it. Mainly because a picture-tube checker just doesn't put the tube under exactly the same stresses that it gets in the circuit."

Jack got out the tester, set it up and made the checks on each gun. The tube checked okay. Tapping the tube produced not even a flicker on the short-indicating neons. The meter reading the emission of each gun held steady.

"Yes, I'd say the picture tube is

good," Jack said. "Not just because of the tester but because it seems impossible to me that anything in the tube could cause all the video to drop out and yet the colored portions of the picture be okay. And especially since the screen background color doesn't change and the brightness stays normal. I'll get out the scope and see where we're losing the video."

Jack studied the circuit to decide where the best place to hook the scope would be. The set was a Curtis Mathes with an RCA-type video-amplifier circuit; it was dc-coupled all the way. This meant there just weren't too many things that could cause a loss of video without also affecting the screen brightness.

One thing that might cause it, Jack decided, was leakage—perhaps between the grid and cathode of a video amplifier. This would reduce the video level by reducing grid bias. Even

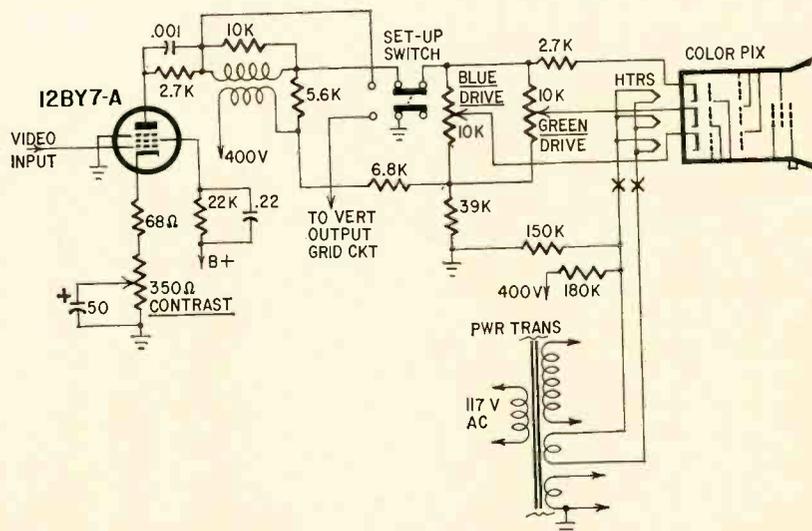


Fig. 1—Jack scoped the grid, then the plate, of the 12BY7-A. Signal on the grid was clean and steady; on the plate, it blinked. Could this be a bad CRT?

this, Jack realized, was far-fetched. But he tried the tubes. The blinking continued intermittently.

Perhaps an open cathode-bypass capacitor? This would reduce the video without affecting the plate current of the tube. Maybe an open screen bypass?

Jack decided to start by connecting the scope to the third video amplifier grid (Fig. 1). The pattern was clean. When the blinking on the picture tube occurred, the grid signal did not change. The trouble was isolated to the last video stage or (heaven forbid!) the picture tube.

He moved the scope to the plate circuit of the third video amplifier. The trouble cleared itself suddenly, but Jack knew the whimsy of circuits; the hiding out of the culprit when the police get on the trail. He waited. The blinking returned and at the same time the scope pattern blinked, becoming reduced in size and distorted. What could cause the trouble? Perhaps it was a screen bypass. He bridged a new one in. No change. Ditto with the cathode bypass.

He checked voltages on the plate, screen and cathode of the 12BY7 third video amplifier. There was virtually no change when the blinking occurred.

### Jiggle the switch

Jack pored over the schematic. Could it be trouble in the set-up switch? He reached over and jiggled it a couple of times. This seemed to have no effect on the blinking, except that the trouble would clear for several seconds; but that happened no matter *how* you disturbed the circuit. "And even if the setup switch was removing the video," Jack reasoned. "It shouldn't have much effect on the plate signal."

Something had to be causing a loss of video without affecting the circuit dc paths. A capacitor to ground somewhere? To probe this idea a little, Jack shunted a 0.01- $\mu$ F capacitor from the plate of the 3rd video tube to ground. This nearly duplicated the symptom on the screen and the pattern on the scope. The video blinked off and the scope pattern took a distorted dive downward.

But where was the capacitive leakoff of the signal? He followed the video circuit from the plate to the picture tube. There was no wayward capacitor from some other circuit causing the trouble. No leakage paths. It was another dead end.

"Oh no," Jack groaned, half aloud. "It probably *is* the picture tube."

The picture was blinking off and on regularly now, sometimes staying off for several seconds. Jack eased the picture-tube socket off. The scope pattern

on the plate of the 12BY7 returned to normal size and shape. It stayed that way for 5 minutes. The blinking was gone. Was it circuit whimsy or was it the picture tube?

He gently replaced the picture-tube socket. The picture stayed on 30 seconds after the tube warmed up—then started to blink again.

"It's *got* to be the picture tube," Jack concluded. "But how? How is it possible for a picture tube to lose all the video without losing the color or even changing background color?"

He studied the circuit—all of it. Then it came to him. That had to be it. He took a jumper and shorted two terminals going to the picture tube. It exactly duplicated the trouble. The question, dear reader, is: What did Jack do and what was the trouble inside the picture tube?



*The cathode is shorted to the filament, and we've got to separate them.*


Jack used a jumper to short one of the cathodes to the heater circuit. This recreated the trouble. There can be no brightness change because the heater is biased by a bleeder on the B+ line so that it is near the same voltage as the cathodes. But the video is skimmed off by the capacitance of the heater transformer windings to ground.

"Is there anything you can do, old friend?" his customer asked.

"I'll see if I can burn out the short, but I've never had too much luck with heater-cathode shorts," Jack said.

Jack looked at the circuit. Why not just ground the heater circuit? This would place quite a lot of voltage between the cathodes and the heater. Maybe the short would burn open.

Instead, something happened, but

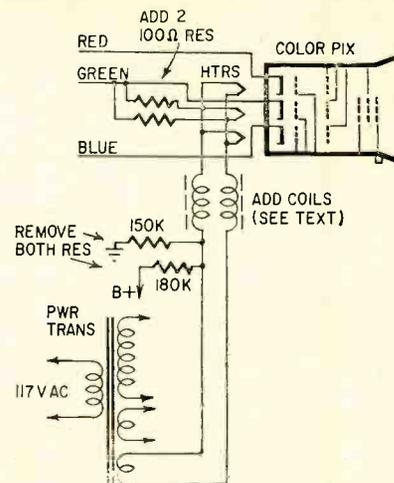

*Fig. 2—Jack's solution to the green heater-cathode short; isolation coils.*

not what he had exactly hoped for. The short became permanent. You could even measure it with an ohmmeter. It was the green cathode shorted to its heater . . . now solid and tight.

"Not much I can do except put in a new picture tube," Jack said, "but for a really good friend who might have to tolerate just a little drop in video quality I can install a circuit that will make this old tube work pretty well, perhaps."

"Go to it," his customer said.

Jack wound two coils of No. 20 enamel-coated wire in a single layer on a ferrite core taken out of an old radio antenna circuit. Each coil was about 2¼ inches long. He inserted them in series with the heater windings at point "X" (Fig. 2). He removed the heater-biasing resistors and tied the green cathode through 100-ohm resistors to each side of the heater circuit. (He couldn't tie the cathode direct to the heater because the short inside the tube was not at the end of the heater winding. But the short might not be permanent. Should it remove itself the 100-ohm resistors would keep the heater winding biased.) The ferrite coils would pass the heater current and at the same time keep the video from being bypassed to ground.

The new circuit worked even better than Jack had dared hope. Jack thought about the new technician. He knew that the guy had instinctively but *accidentally* arrived at the correct diagnosis. He wondered if sometimes you "knew" too much for your own good. One thing was consoling though: Jack was pretty sure the new guy couldn't have salvaged the old tube.

And Jack, still a little rankled because his friend had gone to the new guy first, almost wished the jerry-built circuit hadn't worked. But then he smiled to himself . . . of such things are reputations made. **R-E**



**NEW** □ □ □

## a really versatile bench supply

- \* 0-34 volts at 1.5 amps!
- \* 0.005% or 1 MV regulation!
- \* Ripple — 250 microvolts!
- \* Short circuit proof!
- \* Price — just \$143.00 complete  
f.o.b. Hackensack, N. J.

Hard to believe? Then see for yourself. Write today for complete information on this handy supply that uses the fabulous POWER/MATE CORP., UNI-88 supply. We think you'll agree — it's a buy that can't be beat.




**POWER/MATE CORPORATION**  
163 Clay Street, Hackensack, N. J. 07601

Circle 25 on reader's service card

## EQUIPMENT REPORT

### Dynamic Instrument Plug 'N Play PNP-10

Circle 20 on reader's service card

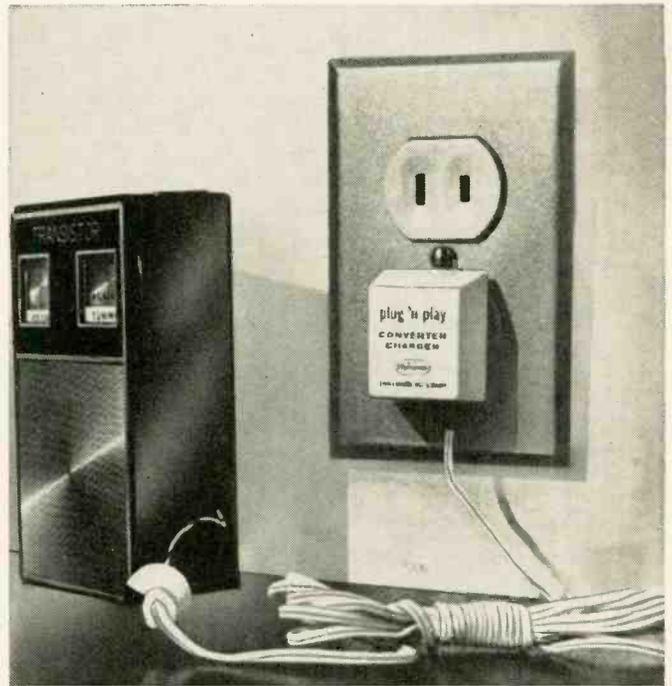

REPLACING BATTERIES IS A NUISANCE YOU TOLERATE IN transistor radios because you can use the radio anywhere. But, at a fixed location why not use the ac line and save money?


One device for doing this is the Plug 'N Play—a receiver accessory with two features. It converts ac to dc to run the radio off the line; it also recharges the battery and permits you use of the radio as a portable.

As the diagram shows, the circuit is simple—a step-down transformer, half-wave rectifier, and filter capacitor. Output voltage is 12.5 unloaded and about 6.5 across a 325-ohm load. You must leave the battery in the radio when using the PNP-10; thus the cell(s) limit voltage to the radio.

Whether a zinc-carbon or a mercury battery can be recharged is debatable. Call it recharging, rejuvenating, or depolarizing, I found the PNP-10 made a mercury battery last about 5 times longer than normal.

To experiment, I used 6 mercury cells—Mallory TR-146X (NEDA 1604M). They are rated at about 575 mA-hr, or about 48 hours to a 5.4-volt end point at 12 mA (which is what my AM-FM portable nominally draws). I ran batteries 1, 2 and 3 through normal duty cycles of a few hours each day, without recharging. Each began at a fresh terminal voltage of 8.0 under load, and each was retired at 7.0—the point where FM afc became touchy and audio peaks distorted. The three batteries averaged 46

(continued on page 86)

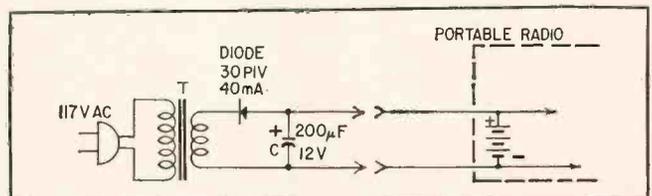

# FREE!



## BRAND NEW EDITION SPRING & SUMMER RADIO-TV ELECTRONICS CATALOG

THE WORLD'S MOST  
FAMOUS CATALOG OF  
ELECTRONIC EQUIPMENT!

YOUR BUYING GUIDE FOR:

- Stereo & Hi-Fi Systems & Components
- Tape Recorders
- Electronic Parts, Tubes, Tools
- Phonos & Records
- Ham Gear
- Test Instruments & Kits
- Cameras & Film
- PA
- Citizens Band
- Radio & TV Sets
- Musical Instruments

SEND FOR YOURS TODAY!

MAIL TODAY TO:

**BURSTEIN-APPLEBEE**

Depl. REN, 1012 McGee, Kansas City, Mo. 64106

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip Code \_\_\_\_\_

DO YOUR FRIEND A FAVOR... ALSO INCLUDE HIS NAME AND ADDRESS IN ENVELOPE WHEN MAILING YOUR REQUEST

Circle 26 on reader's service card

## Numbers are a cinch

(continued from page 57)

immediately did.

"From the  $x^4$  equation,  $2(a+c) = 1/c^2$ , so  $(a+c) = 1/2c^2$ , right?" he asked. I nodded. "So I can substitute this in the  $x^2$  equation to find  $c$ ?"

He was doing it and came up with the conclusion  $c = 1/2$ , followed by  $ab = 2$ , then  $a = 1.5$ , and finally  $b = 4/3$ .

"Now we know the coefficients, let's

REDUCE PRODUCT OF FIG. 4-a TO  $1+x^6$

$$\textcircled{1} a^2 b^2 c^2 = 1$$

$$abc = 1$$

$$ab = \frac{1}{c}$$

$$\textcircled{2} \text{ FOR } x^2 \text{ TO DISAPPEAR } (a+c)^2 = 2ab = \frac{2}{c}$$

$$\textcircled{3} \text{ FOR } x^4 \text{ TO DISAPPEAR } a^2 b^2 = 2abc(a+c)$$

$$\frac{1}{c^2} = 2(a+c) \quad a+c = \frac{1}{2c^2}$$

$$\text{SO } (a+c)^2 = \frac{1}{4c^4} = \frac{2}{c}$$

$$\frac{1}{c^3} = 8 \quad \frac{1}{c} = 2 \quad c = \frac{1}{2}$$

$$ab = 2$$

$$2(a+c) = \frac{1}{c^2} \quad 2(a+\frac{1}{2}) = 4$$

$$2a+1=4 \quad 2a=3 \quad a=1.5$$

$$1.5b=2 \quad b = \frac{2}{1.5} = \frac{4}{3}$$

$$y = 1 - 2x^2 + j2x - jx^3$$

$$y^2 = 1 + x^6$$

$$\phi_t = \text{ARCTAN } \frac{2x - x^3}{1 - 2x^2}$$

Fig. 5—How to make  $X^2$  and  $X^4$  disappear.

look at phase," I suggested. George had the expressions for  $y$ ,  $y^2$  and  $\phi_t$  with values of  $a$ ,  $b$  and  $c$  substituted to give a simple numerical result (Fig. 5).

"One element shifts  $45^\circ$  at cutoff, two elements make it  $90^\circ$ , does the third element shift it to  $135^\circ$ ?" He crossed out the  $x$ 's in the arctan expression and found it simplified down to  $-1$ , which is the tangent of  $135^\circ$ . Then he spotted that  $90^\circ$  would be where the denominator is zero, or  $x^2 = 1/2$  and  $x = 0.707$ , while  $180^\circ$  would be where the numerator is zero, or  $x^2 = 2$  and  $x = 1.414$ .

"The whole thing looks easier by the minute," he commented. "Don't bother with the high-pass section, I'll work that some other time, for my own amusement. What I want to get to is that filter you designed that started us off on all this. Can you show me that?"

"Well, that's a little different," I admitted. "In the first place, all the filters we've discussed so far are 'ideal' designs: they are exactly what we want them to be—constant resistance, uniform total power. But there is no such thing as a perfect linear-phase filter, so we have to find what is the best we can do with a given number of components. Sometimes calculus will help, sometimes it's a matter for trial and error, with diminishing deviations. So I think we should look at that kind of problem first."

"Oh yes, you were going to show me how calculus helps," George commented. "Can you give me a quick example?"

"Calculus deals with slopes," I explained. "It's not too easy to work out for phase response, but it's easy with amplitude response and we use the same principles for phase. Suppose you have a response with rolloff something like this," and I sketched it out (Fig. 6). "Detailed analysis shows its amplitude expression is of the form  $(1+x^2+x^4)$  which yields a 4.77-dB loss at the  $90^\circ$  point, where  $x = 1$ . Suppose we want to add a circuit that will reduce the loss to zero at this frequency, with minimum deviation up to this frequency."

"Sounds difficult. How do you go about it?"

"First step is to cook up the required overall amplitude-squared response, for which two requirements will set maximum flatness: boost equaling attenuation at  $x = 1$  (4.77 dB for both); and, slope at the same point equal and opposite to that of the existing circuit, both measured on a dB/log frequency scale." I sketched in how this worked.

"As we're interested in frequencies up to the normalizing point of  $x = 1$ ," I went on, "it's easy and useful to work in that reference, and find out how good the result is when we get through. The attenuation of 4.77 dB ( $\log 3 = 0.477$ ) merely means that  $1+x^2+x^4$  is 3 when  $x = 1$  (which is fairly obvious). We use a two-reactance filter that provides a peak before rolloff, which means its amplitude response will be of the form  $y^2 = 1 - ax^2 + bx^4$ . We must solve for the two conditions: boost equal to attenuation, and equal, but opposite slopes; both at  $x = 1$ , to find  $a$  and  $b$ . Then we can convert this information into a designable filter circuit, by use of the  $j$  operator."

"I get the idea," said George, "but it's not all clear yet. For boost to equal attenuation, the amplitude-squared expression should be the reciprocal at  $x = 1$ , shouldn't it?" I nodded. "So  $(1-a+b)$  must have a value of  $1/3$ ," he went on. "But how do you figure out the equal-slope part?"

"That's where calculus comes in," I replied. "The slope we are interested in is plotted on log frequency and log amplitude (dB) scales, so the slopes we want are expressed by  $\frac{d \log y}{d \log x}$ , writing  $y$  for the amplitude. Because we use expressions for

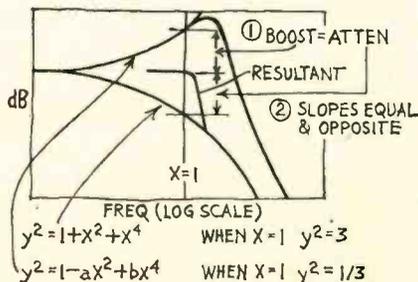


Fig. 6—Changing slope curve by calculus.

Fig. 7—Transform math into a filter.

amplitude squared, it's easier to work in  $y^2$  and  $x^2$  as variables, so we'll use that form." Showing him the standard differentials in a handbook he had, I wrote the conversion

$$\frac{d \log y^2}{d \log x^2} = \frac{x^2}{y^2} \times \frac{dy^2}{dx^2}$$

For the first expression,  $y^2 = 1 + x^2 + x^4$ . I figured this out to

$$\frac{x^2(1 + 2x^2)}{1 + x^2 + x^4}$$

Making  $x = 1$  reduces this to a simple  $3/3 = +1$ . For the expression  $y = 1 + ax^2 + bx^4$ , the slope figures out to

$$\frac{x^2(-a + 2bx^2)}{1 - ax^2 + bx^4}$$

Making  $x = 1$  in this expression reduces it to  $\frac{-a + 2b}{1 - a + b}$ , which needs to be  $-1$ .

So the equation for equal slopes may be written:  $a - 2b = 1 - a + b$ , which rearranges to  $2a - 3b = 1$ . And the amplitude requirement equation reduces to  $a - b = 2/3$ .

George soon had these solved, to  $a = 1$ ,  $b = 1/3$ . "But how do you make that into a filter?" he wanted to know.

"Assume it's of this configuration," and I drew it out (Fig. 7), using  $c$  and  $d$  as constants for the inductor and capacitor. "Then you solve for values of  $c$  and  $d$  that make the amplitude-squared equation come out to

$$y^2 = 1 - x^2 + \frac{1}{3}x^4."$$

George was glad of the exercise in using  $j$  and in short order had equations in  $c$  and  $d$  that made  $a = 1$  and  $b = 1/3$ . Together we solved them, using a slide-rule to get approximate values of  $c = 0.395$  and  $d = 1.462$ . Using the reciprocal of  $d$ , which is  $0.685$ , we could use a reactance chart to design such a filter for any terminating resistance and cutoff frequency.

"How good is the correction this

filter makes?" George wanted to know next.

"We can use calculus for that too. The maximum error will be a stationary point on the graph of the amplitude-squared equation, which means the slope of the graph is zero." I sketched this.

"Just a minute there," interjected George, "you've lost me, momentarily."

I showed him (Fig. 8) that a point moving along a curve can go up or down; or it can momentarily do neither, in which case it is stationary at the top of a peak or at the bottom of a dip. I pointed out that an amplitude-squared response with terms in  $x^2$  and  $x^4$  can have one stationary point (a peak) if the coefficient of  $x^2$  is negative.

Thus, the combined response after "correction" can have three stationary points, one at zero frequency, followed

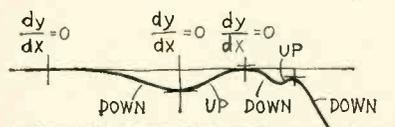


Fig. 8—Movement of point on a curve.

by a dip and a peak before final rolloff. "To find these points, we differentiate the amplitude-squared expression, for convenience using  $x^2$  as the variable

$$y^2 = [1 + x^2 + x^4] [1 - x^2 + \frac{1}{3}x^4] = 1 + \frac{1}{3}x^4 - \frac{2}{3}x^6 + \frac{1}{3}x^8$$

$$\frac{dy^2}{dx^2} = \frac{2}{3}x^2 - 2x^4 + \frac{4}{3}x^6$$

$$x^2 = 0, \text{ LEAVING } \frac{2}{3} - 2x^2 + \frac{4}{3}x^4 = 0$$

$$2x^4 - 3x^2 + 1 = 0 \quad 2x^2 = 1 \quad (x^2 = \frac{1}{2})$$

$$\text{OR } x^2 = 1$$

$$\text{WHEN } x^2 = 1 \quad y^2 = 1 + \frac{1}{3} - \frac{2}{3} + \frac{1}{3} = 1 \quad (\text{AS REQUIRED})$$

$$\text{WHEN } x^2 = \frac{1}{2} \quad y^2 = 1 + \frac{1}{12} - \frac{1}{12} + \frac{1}{48} = \frac{49}{48}$$

rather than  $x$ , and equate to zero (for zero slope).

"The overall amplitude-squared equation is . . ." George began, when he'd grasped this, and he wrote it out to

$$y^2 = 1 + \frac{1}{3}x^4 - \frac{2}{3}x^6 + \frac{1}{3}x^8$$

I differentiated it (not bothering with log terms, because a stationary point has zero slope no matter which scale is used) and got (see Fig. 9)

$$\frac{dy^2}{dx^2} = \frac{2}{3}x^2 - 2x^4 + \frac{4}{3}x^6$$

Equating this to zero,  $x^2$  must be zero, or  $1/2$ , or  $1$ . The point at which  $x^2 = 1$  is the point for which we de-

signed. The point where  $x^2 = 1/2$ , at 0.707 below cutoff, represents a dip. Substituting  $x^2 = 1/2$  into the amplitude-squared expression gives the fraction  $49/48$ . Taking 10 times the logarithm of  $49/48$  gives the deviation in dB as .089.

George was impressed with how small a deviation this correction could achieve — less than 0.1 dB. Before I left, he wanted to know what else operator  $j$  could be used for.

I suggested it could be used to analyze anything that uses vectors. We had discussed vector analysis before.


George was convinced his new knowledge of how to use operator  $j$  was going to prove a very useful tool. **R-E**

Fig. 9—Overall amplitude-squared math expression.
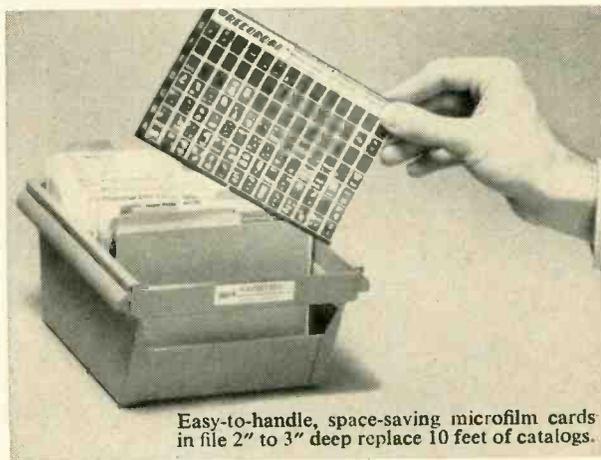
# Why not sell the best

Now... get genuine Zenith parts three ways faster—with ZIP!

Your Zenith Distributor has a revolutionary new system to speed your replacement parts ordering. Called "ZIP" (Zenith Instant Parts), it gives you much improved service.



Easy-to-handle, space-saving microfilm cards in file 2" to 3" deep replace 10 feet of catalogs.

1. Looking up parts numbers is 100% quicker than before. Because parts lists and schematics for the past ten years are now microfilmed on compact, easily-handled filmcards.
2. "Out-of-stocks" are cut down. The new ZIP program helps your Zenith distributor keep tighter inventory controls and maintain a more complete stock.
3. Factory special orders are shipped faster. Under the new ZIP program, the Zenith factory is geared to ship orders without delay.

Order from your Zenith Distributor for "Zenith Instant Parts" service on all genuine Zenith replacement parts and accessories.

**ZENITH®**  
The quality goes in before the name goes on

Circle 27 on reader's service card

## Audio Levels on Long Communication Lines

(continued from page 61)

send the signal from the remote to the common point. These systems typically show different loss figures with direction of transmission. Second: All dB meters, and the line math on which they are based, are designed around a 1-kHz signal. There are capacitive effects on long phone lines that will cause any other frequency to give misleading readings.

5. Call the phone company, and ask for their maximum permissible level. This could be anywhere from 0 dBm to maybe +10. It will vary from town to town, depending on the age and condition of the cable system. Your best authority is normally the wire chief. However, in larger places, you will have to run down somebody from the engineering department.

6. Select the line segment with the highest loss figure and arbitrarily assign that remote a transmit level equal to the maximum level. Reasons were given earlier. In Fig. 1, this would be the sheriff's house, with a loss of 12 dB, and an arbitrarily assigned level of +6 dBm.

7. Figure what level that remote, transmitting at its assigned level, will deliver to the common point. In Fig. 1, the sheriff's house, transmitting at +6 dBm, will drop 12 dB getting to the common point, and arrive there at -6 dBm. Note this figure on the card at the common point.

8. Figure backward and determine what level is necessary for each remote to deliver this same level to the common point. In Fig. 1, the base receiver will drop 5

dB getting to the common point, so it has to put out -1 dBm. The police department, with a loss of only 1 dB, only needs an output of -5 dBm. Continue like this around the system.

Variations of the leased-line systems have common points at places other than the telephone company's main frame. Fig. 2 illustrates; setup is exactly the same as before.

There are some systems—about 25% around here, to be exact—that have no common point (Fig. 3). In these systems, you will have blasting among the remotes no matter what you do. I set them up to deliver consistent audio to the transmitter. At least the FCC traveling monitors don't hear stinky signals.

There is also one special case, the repeater system, which requires additional work.


Repeaters feed receiver audio to the transmitter for retransmission, as well as down the phone line to the remotes. All the repeaters I've worked on have receiver-to-receiver attenuators, put there specifically for adjustment to prevent local blasting.

To set them up, you begin by making one additional loss measurement, from the common point to the transmitter. Do this in repeater mode (not remote-transmit mode).

Add together the two loss figures from the base-station segment of the line. In Fig. 1, this would be 13 dB.

Set the receiver-to-transmitter attenuator to this figure. I replaced the fixed resistors that come with these rigs with an adjustable wirewound resistor; the size depends on the particular equipment. That way, I don't have to spend an hour or more fooling with a box of resistors, and I got a more exact setting. **R-E**

# electronic technicians: take note.

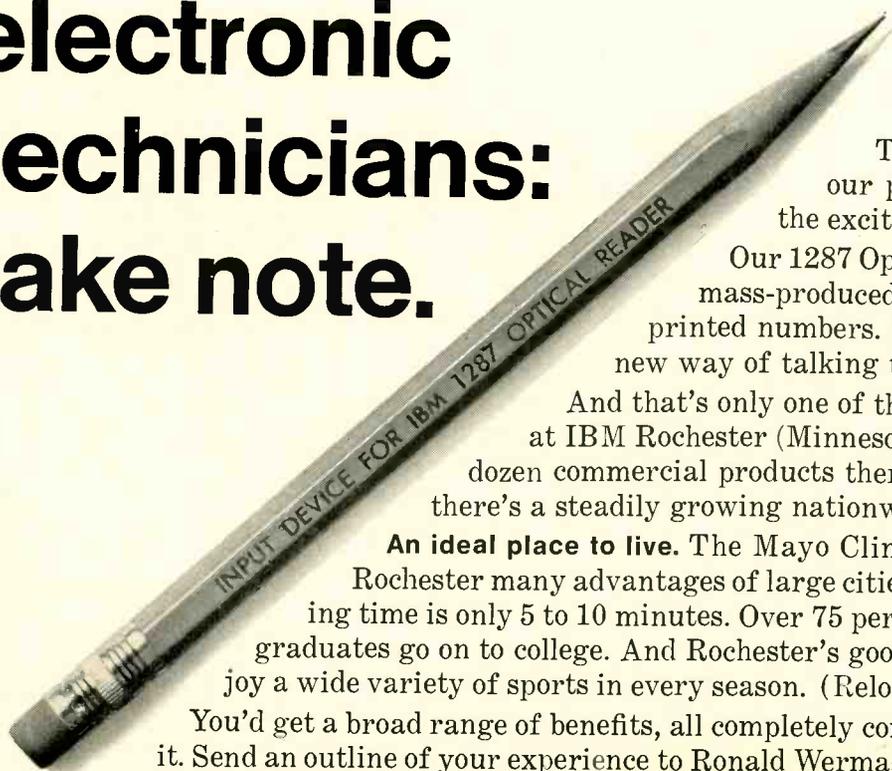

That little message on our pencil says a lot about the exciting projects at IBM.

Our 1287 Optical Reader is the first mass-produced machine to read hand-printed numbers. It gives people a whole new way of talking to computers.

And that's only one of the challenging projects at IBM Rochester (Minnesota). We make over two dozen commercial products there. Products for which there's a steadily growing nationwide demand.

**An ideal place to live.** The Mayo Clinic and IBM help give Rochester many advantages of large cities, yet typical commuting time is only 5 to 10 minutes. Over 75 percent of the high school graduates go on to college. And Rochester's good weather lets you enjoy a wide variety of sports in every season. (Relocation expenses paid.)

You'd get a broad range of benefits, all completely company paid. Look into it. Send an outline of your experience to Ronald Wermager, IBM Corporation, Dept. QD7-O, Highway 52 and N. W. 37th St., Rochester, Minn. 55901.

An Equal Opportunity Employer

**IBM**<sup>®</sup>

## RADIO-ELECTRONICS READER'S SERVICE

Here's how you can get manufacturers' literature fast:

1. Tear out the post card on the facing page. Clearly print or type your name and address.

**Include zip code! Manufacturers will not guarantee to fill your requests unless your zip code is on the reader service card!**

2. Circle the number on the card that corresponds to the number appearing at the bottom of the **New Products, New Literature or Equipment Report** in which you are interested.

For literature on products advertised in this issue, circle the number on the card that corresponds to the number appearing at the bottom of the advertisement in which you are interested. Use the convenient index below to locate quickly a particular advertisement.

3. Mail the card to us (no postage required in U.S.A.)

**Advertisements in this issue offering free literature (see the advertisements for products being advertised):**


ALLIED RADIO CORP. (Pg. 84)	Circle 116
AMPEREX ELECTRONIC CORP. (Pg. 14)	Circle 14
AMPHENOL CORPORATION (Pg. 13)	Circle 13
ARCTURUS ELECTRONICS CORP. (Pg. 98)	Circle 142
B & K (Division of Dynascan Corporation) (Pg. 7)	Circle 11
B & K (Division of Dynascan Corporation) (Pg. 27)	Circle 23
BARKER PRODUCTS CO. (Subsidiary of Component Manufacturing Service, Inc.) (Pg. 12)	Circle 12
BROOKS RADIO & TV CORP. (Pg. 94-95)	Circle 127
BURSTEIN-APPLEBEE CO. (Pg. 70)	Circle 26
CASTLE TV TUNER SERVICE, INC. (Pg. 78)	Circle 107
CLEVELAND INSTITUTE OF ELECTRONICS (Pg. 5)	Circle 9
CLEVELAND INSTITUTE OF ELECTRONICS (Pg. 28-31)	Circle 24
CORNELL ELECTRONICS CO. (Pg. 100)	Circle 146
CORTLANDT ELECTRONICS (Pg. 92)	Circle 123
DATAK CORPORATION, THE (Pg. 78)	Circle 108
DELTA PRODUCTS, INC. (Pg. 16)	Circle 16
EDMUND SCIENTIFIC CO. (Pg. 99)	Circle 143
ENTERPRISE DEVELOPMENT CORP. (Pg. 84)	Circle 115
GC ELECTRONICS CO. (Pg. 24)	Circle 19

HEALD COLLEGES (Pg. 97)	Circle 131
HEATH COMPANY (Pg. 88-91)	Circle 122
INTERNATIONAL CRYSTAL MFG. CO. (Pg. 102)	Circle 148
JERROLD ELECTRONICS CORPORATION (Distributor Sales Division) (Pg. 86)	Circle 118
JFD ELECTRONICS CO. (Pg. 77)	Circle 106
MICROFLAME, INC. (Pg. 86)	Circle 119
MULTICORE SALES CORP. (Pg. 94)	Circle 126
MUSIC ASSOCIATED (Pg. 97)	Circle 129
OLSON ELECTRONICS, INC. (Pg. 93)	Circle 125
POLY PAKS (Pg. 101)	Circle 147
POWER/MATE CORPORATION (Pg. 70)	Circle 25
QUIETROLE CO. (Pg. 93)	Circle 124
READING IMPROVEMENT PROGRAM (Pg. 97)	Circle 130
RYE INDUSTRIES, INC. (Pg. 87)	Circle 120
SAMS & CO., INC., HOWARD W. (Pg. 80)	Circle 110
SAXTON PRODUCTS, INC. (Pg. 22)	Circle 18
SCHOBER ORGAN CORP., INC. (Pg. 26)	Circle 22
SCOTT, INC., H. H. (Pg. 26)	Circle 100
SENCORE (Pg. 15)	Circle 15
SENCORE (Pg. 83)	Circle 114
SENTRY MANUFACTURING COMPANY (Pg. 96)	Circle 128
SHURE BROS. (Pg. 17)	Circle 17
SOLID STATE SALES (Pg. 99)	Circle 144
SONAR RADIO CORPORATION (Pg. 82)	Circle 113
SPRAGUE (Pg. 4)	Circle 8
SONY/SUPERSCOPE (Pg. 6)	Circle 10
TAB BOOKS (Pg. 85)	Circle 117
TRIPLETT ELECTRICAL INSTRUMENT COMPANY (Second Cover)	Circle 7
VACO PRODUCTS COMPANY (Pg. 79)	Circle 109
WARREN ELECTRONIC COMPONENTS (Pg. 100)	Circle 145
XCELITE, INC. (Pg. 81)	Circle 111
ZENITH (Pg. 72)	Circle 27
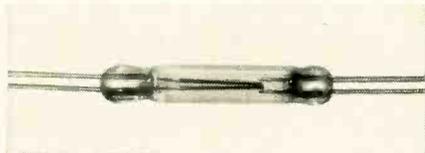
# NEW PRODUCTS

More information on new products is available free from the manufacturers of items identified by a Reader's Service number. Turn to the Reader's Service Card facing page 74 and circle the numbers of the new products on which you would like further information. Detach and mail the postage-paid card.


**MINIATURE DRY-REED SWITCH, Quad-Reed.** Enclosed in glass, four elements are arranged for a variety of switching uses. Contact resistance and



bounce have been reduced and voltage break-down level increased. The multi-element design eliminates need for several switch types.—Caton Industries, Inc.

Circle 46 on reader's service card

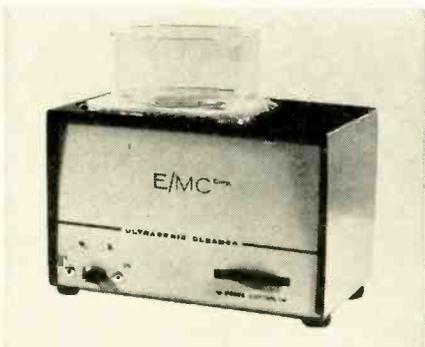
**ULTRASONIC CLEANER, Model LP-2.** Operates at 90,000 Hz on 115 volts. Turns off automatically before it can over-heat. All metal and stainless steel cabinet



with crystal beaker. Can be filled, emptied, and objects rinsed without moving the cabinet. \$39.95—Electromation Components, Inc.

Circle 47 on reader's service card

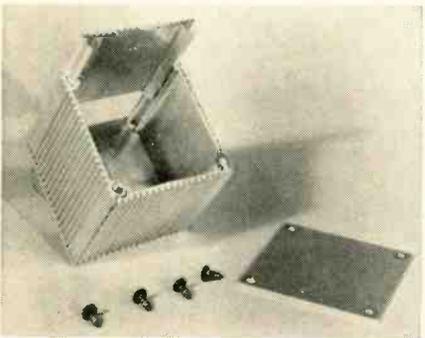**ELECTRONIC CIRCUITRY ENCLOSURES, MINI-COOL.** Constructed to contain cable junctions, plug boxes,



control modules, transformers, circuitry, solid-state devices, meters and amateur radio gear. Can withstand a force of 3

tons. The six flat sides are made of light-weight extruded aluminum. Features a lock joint at each corner, which tightens when the screws are installed. Also available with integral heat sink walls. 21 sizes range from 2" x 2" x 1 1/2" to 2.6" x 2.6" x 10". Price from \$ .62 to \$2.40, depending on size and quantity ordered.—Sarex Corp.

Circle 48 on reader's service card


**ROSIN FLUX REMOVER, Sprayon No. 2009 Freon T.M.C. Cleaner.** Removes rosin flux from printed circuits, electrical relays, and semiconductors



without harming plastics and elastomers. Nonflammable and non-toxic, it comes in the 16-oz. size can with an extension tube for delicate work.—Industrial Supply Div./Sprayon Products, Inc.

Circle 49 on reader's service card

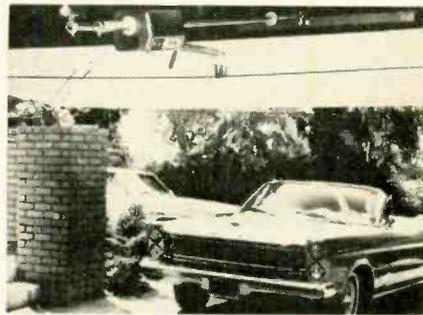
**GARAGE DOOR OPENER, Electro-Lift.** A cigarette-package-size control unit sends a silent but powerful burst of radio waves to the motor and a 150-lb. door opens on command. Triple coding eliminates accidental operation by other openers in the neighborhood. Completely




streamlined with no exposed wires or gears, the wall-mounted radio receiver is accessible for ready maintenance. Instant-stop control automatically stops the door when an obstacle is encountered and when started again it reverses direction. Additional information available.—Perma-Power Co.

Circle 50 on reader's service card

## JFD® V/U/FM Couplers have muscle!

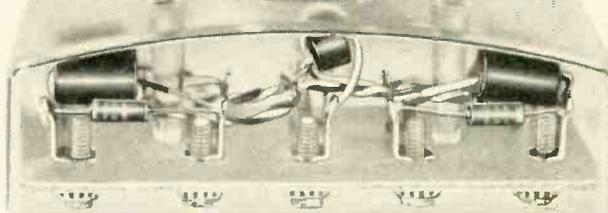

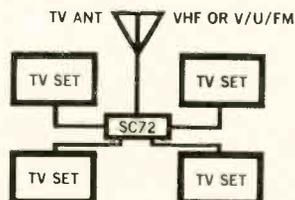DESIGNED BETTER!  
BUILT BETTER!  
FOR COLOR-PERFECT HOME DISTRIBUTION SYSTEMS



Model SC72 4-Set V/U/FM COUPLER  
Model SC62 3-Set V/U/FM COUPLER  
Model SC42 2-Set V/U/FM COUPLER

world's largest manufacturer

**JFD ELECTRONICS CO.**

1462 - 62 Street Brooklyn, N.Y. 11219  
of TV/FM antennas and accessories.

- COUPLES up to 4 sets to a single V/U/FM antenna with lowest possible loss—only 6.0 db maximum.\*\*
- CONSTANT inter-set isolation—20 db minimum across all VHF, UHF and FM frequencies.\*\*
- OPTIMUM VSWR of 1.2:1—both forward and backward—for noise-free color.\*\*
- FLAT response ( $\pm 1/4$  db per 6 MHz channel) for perfect chroma registration.\*\*
- MATCHED quality components, operating well below rated parameters, insure long-life reliability.
- NO-STRIP terminals make positive contact, eliminate 300 ohm twin lead stripping or splicing.
- COMPLETE with hardware and adhesive Insta-Mount for quick and convenient indoor installations.
- ATTRACTIVE non-breakable housing sheds rain and moisture.

\*\*For model SC72, 4-set coupler.

Solve all reception problems permanently and profitably with the couplers, splitters, combiners, antennas, transformers and amplifiers that have muscle. Now at your JFD distributor. Write for brochure 834.

**COMPLETE TUNER OVERHAUL**

**995**

**ALL LABOR AND PARTS (EXCEPT TUBES & TRANSISTORS)\***

VHF UHF COLOR U-V TRANSISTOR

**COLOR TUNERS** GUARANTEED ALIGNMENT ADDITIONAL COLOR MD CHARGE

Simply send us the defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warranted for 90 days. UV combination tuner must be single chassis type; dismantle tandem UHF and VHF tuners and send in the defective unit only. Exact Replacements are available for tuners unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.) And remember—for over a decade Castle has been the leader in this specialized field . . . your assurance of the best in TV tuner overhauling.

**CASTLE**  
TV TUNER SERVICE, INC.

5715 N. Western Ave., Chicago 45, Illinois.  
41-96 Vernon Blvd., Long Island City 1, N. Y.

For service in Canada write to Chicago or use reader service card in this magazine.  
\*Major parts are charged extra in Canada.

Circle 107 on reader's service card

Because you've got to SEE it to BELIEVE it  
.....we will send you a FREE sample!

**instant lettering**®

**DATAMARK**  
— the easy new way to label your projects!

Just rub over the pre-printed words or symbols with a ballpoint pen and they transfer to any surface — looks like finest printing! Label control panels, meter dials, letter on anything!

LOOK FOR **instant lettering**®

**DATAMARK SETS** only \$1.25 each  
— at leading electronic distributors

**DATAMARK SETS AVAILABLE FOR:**

- Amateur Radio, CB
- Audio, Hi-Fi, TV
- Experimenter Home Intercom
- Industrial Test Equipment
- Switch & Dial Markings
- Alphabets & Numerals in 1/8", 1/4" and 1/2"

— each set has black, white, and gold

SEND FOR FREE SAMPLE RE-28

**THE DATA CORPORATION**  
85 HIGHLAND AVENUE • PASSAIC, N. J. 07055  
Circle 108 on reader's service card

**5-BAND PORTABLE RADIO, Model 10 J 4362X.** Receives AM or FM standard broadcasts, international SW (5-12 MHz), airport and airplanes (108-142.70 MHz), police, fire, radio-telephone, commercial and public service vehicles (143.80 to 177.38 MHz). Oper-



ates from "C" cell batteries or from a built-in 117-Vac adapter. Uses 15 transistors, 6 diodes and a thermistor and has a built in antenna for AM and SW and a 25" telescoping antenna for FM and vhf reception. An earphone is supplied. Leatherette-covered case. \$59.50 with batteries, earphone and built-in AC adapter.—Allied Radio Corp.

Circle 51 on reader's service card

**FIELD-EFFECT VOM, FE14.** With 15-megohm input resistance on dc and 10-megohm input impedance on ac, measures voltages with a minimum of circuit loading. Has ac and dc voltage ranges from 1.0 to 1000-V full scale. An optional high-voltage probe extends the dc



range to 30 kV. Frequency response is up to 10 MHz. A zero center scale of 0.5 volt simplifies testing of transistor circuits. Direct current ranges are 0 to 100 μA, and 1, 10 and 100 mA. Operates on small 9-V and 1.5-V batteries. Complete with test leads, less batteries. \$59.95—Sencore

Circle 52 on reader's service card

**PROGRESS IN AN EXPLODING TECHNOLOGY**

**EXHIBITS**  
NEW YORK COLISEUM

**TECHNICAL SESSIONS**  
NEW YORK HILTON


Monday through Thursday

- 48 GENERAL SESSIONS at the New York Hilton. Hours: 10:00-12:30; 2:00-4:30.
- FOUR FLOORS OF EXHIBITS at the N. Y. Coliseum including over 750 firms. Hours: 10 a.m.-8 p.m. 4 Days.
- GALA ANNUAL BANQUET—Wednesday 7:15 p.m. N. Y. Hilton Grand Ballroom—\$16.00.
- FREE SHUTTLE BUSES between the Hilton and the Coliseum—every few minutes.
- REGISTRATION—Good all days—General Sessions and exhibits. In and out privileges.—IEEE Members \$3.00. Non-members \$6.00. Ladies \$1.00. High School Students \$3.00 if accompanied by an adult—One student per adult; Thursday only—limit of 3 students per adult.
- REG-IDENT CARD speeds request for exhibitors' literature. Ask for one when registering.
- ESCALATORS/EXPRESS ELEVATORS to the Fourth Floor.

**IEEE Exhibition MARCH 18-21, 1968**
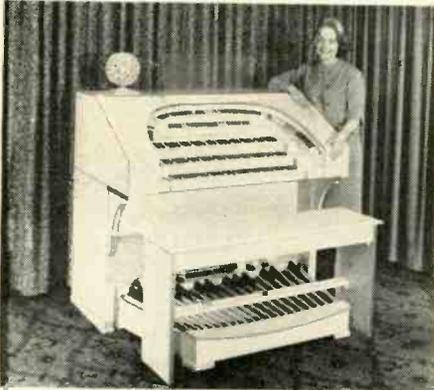
# NEW AUDIO EQUIPMENT


**IMPERIAL KIT ORGAN.** Theater-type organ is designed to look and sound like the consoles of the silent-movie era. The actual tone of theater pipes is reproduced by employing many sets of transistor oscillators plus special voicing filters.



This is one of 12 models now available for home builders. No previous kit-building experience is required. The *Imperial* is available in several woods and optional finishes; custom-built or in kits at 50% savings.—Artisan Organs

Circle 53 on reader's service card

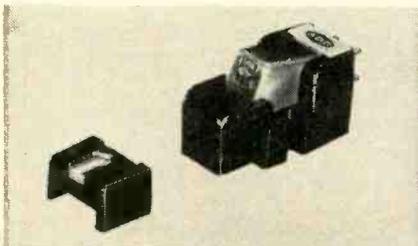**MAGNETIC PHONO CARTRIDGE 10/E-Mark II.** Increased resiliency, greater stylus deflection and greater shock absorbency. Uses elliptical stylus, tracks at up to 1½ grams. Moving mass is far below



record groove yield for clean tonal rendition. Replacement stylus will fit both 10/E and 10/E-Mark II cartridges. Three-year free inspection service. \$59.50—Audio Dynamics Corp.

Circle 54 on reader's service card

**STEREO RECEIVER, SX-300T.** 40-watt AM/FM/FM-multiplex receiver with 41 transistors and 26 diodes. Channel




separation is better than 35 dB at 1 kHz. **FM Section:** 3 µV sensitivity, 52 dB image rejection at 1000 kHz, signal-to-noise ratio of 55 dB. **AM Section:** 28 µV sensitivity, 33 dB image rejection, built-in

ferrite loopstick antenna, transistorized protection circuit to insure against damage to output transistors. Rear of chassis has standard terminals and switches. Coded plugs are provided for the speaker leads. Additional details and specs available. Oiled walnut cabinet optional.—Pioneer Electronics U.S.A. Corp.

Circle 55 on reader's service card

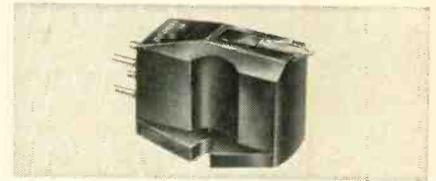**PHONO CARTRIDGE, SL-15.** Small size, 7 grams, output impedance 2 ohms, stylus pressure 1-2 grams, output 0.04, mV/cm/sec., channel separation 20-30



dB. Fits all transcription pickuparms, mounts easily in all better quality automatic turntables. \$60.00 without external transformers, \$75.00 with external transformers—Elpa Marketing Industries, Inc.


Circle 56 on reader's service card

## Blinded by hat pin performance...

By rivets that hold only part of the time? Then open your eyes to a NEW blind rivet... the VACO POW'RIVET... in oversized holes, always just tight and water tight, low profile on both sides. Only four sizes replace 11 sizes of old fashioned types. See your local distributor for a startling demonstration of the VACO POW'RIVET, the fastener that eliminates "hat pin" performance.
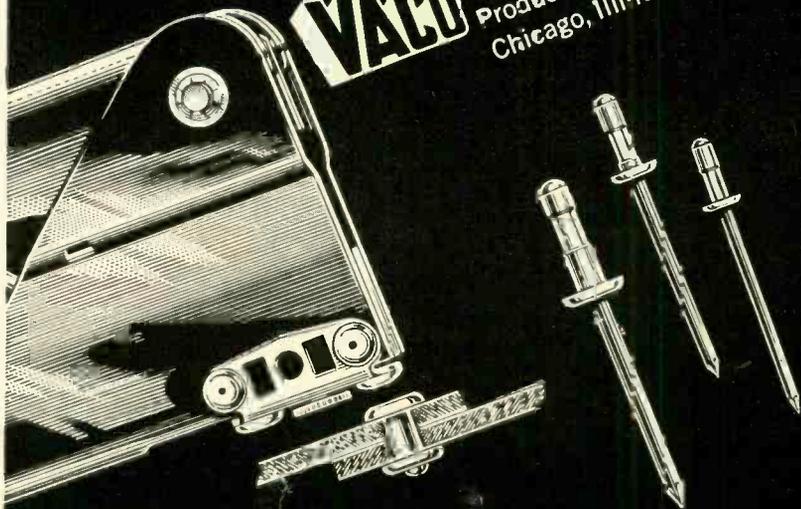
### VACO®

Products Co. 510 N. Dearborn St.  
Chicago, Illinois 50610



U. S. Patent  
No. 3,286,580

Circle 109 on reader's service card

# new Sams books

## So You Want to Be a Ham. 4th Ed.

by Robert Hertzberg, W2DJJ. Completely revised and updated to include full information on changes introduced by the new incentive licensing. Here is everything you need to know to get into Amateur radio; chapters are devoted to the code, the receiver, the antenna, kits, getting the ticket, going on the air, going mobile, how to be a good operator, test equipment and safety measures, etc. Describes modern equipment, operating procedures; gives helpful guidance on passing the FCC exam. A "must" book for anyone out after the ham ticket. 192 pages; 5½ x 8½". \$3.95  
Order 20607, only.....

## FET Principles, Experiments & Projects

by Edward M. Noll. The field-effect transistor is coming into wide acceptance in industry, and is beginning to appear in electronic products for home use. Low-cost FET types are now available for the build-it-yourselfer. This book by a well-known authority clearly explains the unique FET principles of operation, provides data for circuit designs, and includes experiments demonstrating the operating characteristics of field-effect transistors. Practical projects using FET's are also included; simple circuits can be constructed on pegboards or inexpensive chassis. Has chapter on FET math. A fascinating book for audio, amateur, short-wave, CB and do-it-yourself fans. 256 pages; 5½ x 8½". Order 20594, only..... \$4.95

## Outboard Motor Service Manual. 4th Ed. (In 2 Volumes)

Vol. 1. Complete service data for motors under 30 HP, covering models made by 37 leading manufacturers.

Vol. 2: Comprehensive maintenance and repair information for motors of 30 HP and over; covers models made by 21 manufacturers.

Each volume includes design fundamentals (engine types, fuel, ignition, and cooling systems); drive-unit fundamentals (propeller, gearcase, and lower housing); service fundamentals, troubleshooting, maintenance, and general repairs. Volumes are 8½ x 11½".

Vol. 1. 240 pages. Order 20598, only..... \$4.95  
Vol. 2. 208 pages. Order 20599, only..... \$4.95

## Inertial-Guidance Systems

by Training & Retraining, Inc. Explains the importance of these unique systems which are completely self-contained, require no outside stimulus, and are isolated from all external influences of electromagnetic radiation. Inertial-guidance systems are used in all U.S. ballistic missiles and in such space projects as Gemini and Apollo; the same principles and equipment techniques are being increasingly utilized in major aircraft operations. The book explains basic theory, coordinate systems and earth effects, inertial sensors, the inertial-measurement unit, the guidance computer, and system operation. Includes review summaries and instructive self-test feature. 176 pages; 5½ x 8½". Order 20605, only..... \$4.95

## RECENT BESTSELLERS

### Modern Dictionary of Electronics

New 3rd edition. Now defines approximately 16,500 terms; includes pronunciation guide, most widely used symbols and abbreviations, new terms in latest specialized fields. The most complete and authoritative electronics dictionary available. 608 pages; 6 x 9"; hardbound. \$9.95  
Order 20600, only.....

### Stereo/FM

Bestselling book value for everyone interested in stereo, hi-fi, and FM. Highlights components, consoles, tape recorders, auto stereo, and tape recorder/player systems. Includes buyer's guide for all types of equipment. \$1.25  
Order 50012, only.....

These and over 300 other SAMS Books are available from your local Electronics Parts Distributor . . .


HOWARD W. SAMS & CO., INC.

4300 WEST 62nd ST. • INDIANAPOLIS, INDIANA 46226

Circle 110 on reader's service card
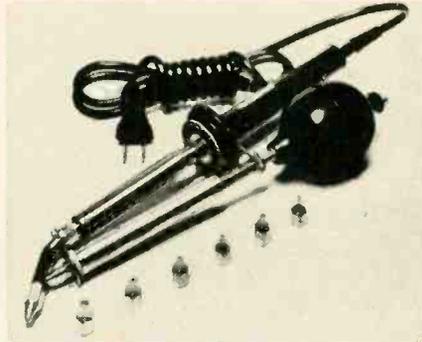
# NEW TOOLS


**DESOLDERING IRON TIPS** add new uses for Model 100-A Endeco desoldering iron. They bring to six the number of tip sizes available for the iron. Hollow tips fit over leads or around con-



nections to remove all solder. Tip openings are 0.046" and 0.067". Packaged in clear plastic, they come 3 of each size to a package, or 6 sizes for both model irons.—Enterprise Development Corp.

Circle 57 on reader's service card

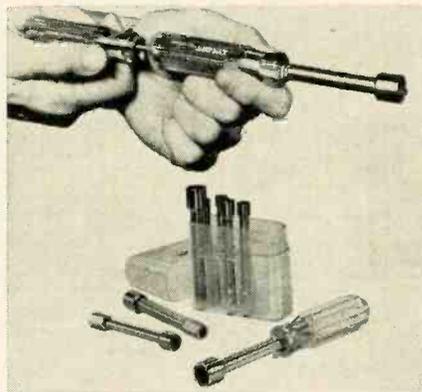
**NUTDRIVER SET No. HSC-1** features drilled handle. By passing an 8-inch or longer round-shank screwdriver blade through the center of the handle and the



hollow nutdriver shaft, you can quickly and easily set the combination locknut and screw adjustments. Eight interchangeable shafts with hex openings from 3/16" to 9/16" are included.—Xcelite Inc.

Circle 58 on reader's service card

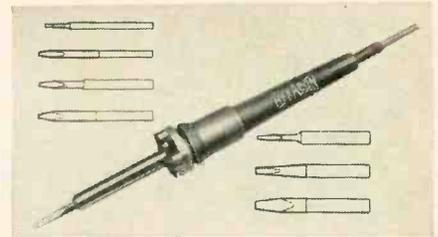
**MINIATURE SOLDERING IRONS, Slim-Line.** Ruggedly constructed to withstand heavy production use without bending or loosening, these small tools afford maximum visibility of work and directional control. White-room handles are slim, extra cool and well balanced. Long-life tips are available in a wide selection (3/16" to 3/8") of shapes and are non-



scaling and nonfreezing. Wattages range from 15 to 60 watts.—Hexacon Electric Co.

Circle 59 on reader's service card

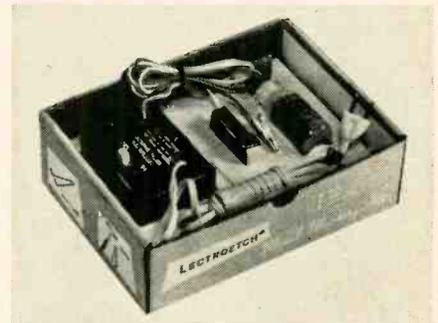
**METAL MARKING KIT, Electroetch.** Permanently marks identification on any clean, bare metal surface. Complete with 110-volt power supply which is transformed to 2 amps—10 volts. Marks



are permanent. Complete instructions and suggested applications included. Additional supplies are furnished in the MK-1A Accessory Kit. Money-back guarantee. \$14.95.—Davidson Enterprises

Circle 60 on reader's service card

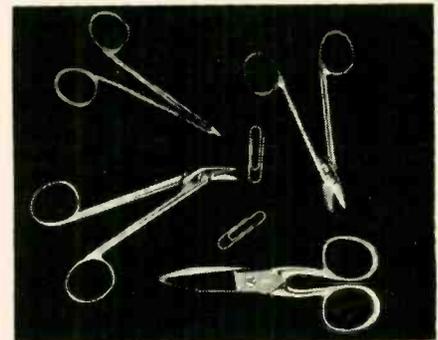**ELECTRONIC SCISSORS** come in five styles and are helpful in a variety of ways for electrical and electronic work. Assemblers, production workers, model-shop men, technicians, research and de-




velopment people find them ideal for cutting fine wires, springs, foil, insulation, gaskets, etc. Small size lets them get into tight places. Specs on each of the five models are available.—Telvac Instrument Co.

Circle 61 on reader's service card
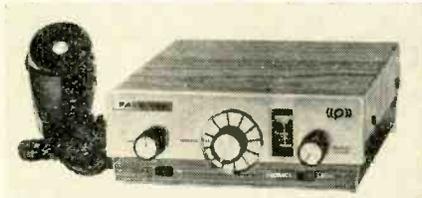
## New Communications Equipment


**CB TRANSCEIVER, PACE 200.** A 12-channel unit designed to complement the decor of modern cars. Meter indicates relative incoming signal strength in S-units and dB over S9. Transmitter rated



at 5 watts and operates at 100% modulation. Receiver has a single-crystal tolerance of 0.0033%. Brackets provided for mounting on car or boat. \$159—Pace Communications

Circle 62 on reader's service card

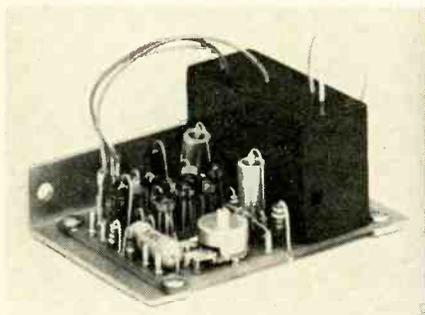
**TONE SQUELCH ENCODER, Series 260 SUB-TONE.** Generates between 67 and 250 Hz without use of a mechanical resonant reed. Easily adaptable to almost any two-way radio, the silicon, solid-



state circuit withstands severe mobile conditions. Six tunable plug-in frequency control networks. Dc supply is 10 to 18 volts and output level adjustable from 0 to 2 volts.—Mu-Western, Inc.

Circle 63 on reader's service card

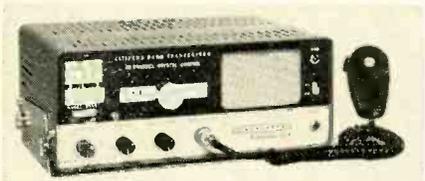**CB TRANSCEIVER, Comstat 25A.** 23-channel transceiver has a 5-watt transmitter, dual-conversion receiver and 2.5-kHz fine-tuning control. Features S/PRF meter, public-address switch and external speaker jack. Has a built-in TVI antenna



trap, 117 Vac and 12 Vdc transistorized power supply. 11 tubes, 2 transistors and 11 diodes. All crystals are supplied. Comes with mounting bracket and ceramic push-to-talk microphone.—Lafayette Radio Electronics Corp. R-E

Circle 64 on reader's service card

## How to Measure Reverberation Time

(continued from page 52)

to the firm. They recommended spraying the domed ceiling with absorptive asbestos flocking. The second plotting in Fig. 6, made after treatment, shows the change in the reverberation time as a result of the flocking.

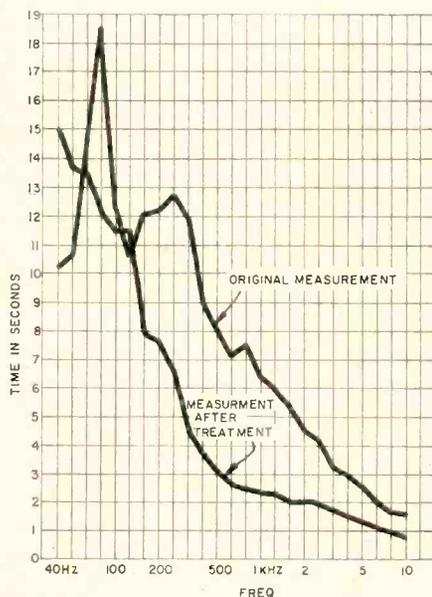


Fig. 6—"Before" and "after" curves of the hall described in this article.

After this correction was made it was possible to install two large speaker arrays carefully designed to distribute high-level sound reinforcement evenly to every seat in the hall. The array mounted in the center is time-delayed to allow for the fact that sound travels far more slowly than electric currents to a speaker. Otherwise, the amplified sound would reach the listener before the direct sound.

The acoustical tests and measurements in this case were useful to the architects in another way. They were able to use them to prove to the ceiling-material supplier that the results he had guaranteed had not come about. The material had failed to reduce reverberation time properly.

Once a sound engineer has measured a number of auditoriums he finds that he gradually develops a feel for the kinds of spaces that are going to cause troubles. Eventually he can recognize them at the drawing board stage. Then he becomes very valuable. If you're a sound contractor, you'd be well advised to look into acoustical tests and measurements. The professional jobs of the future will fall to the professional who starts today. R-E

# have you any idea how many ways you can use this handle?



as a screwdriver...



for slotted, Allen hex, Phillips, Frearson, Bristol, Clutch Head, Scrulox® screws

as a nutdriver...



for hex nuts, screws, and bolts

as an awl/scraper and reamer



It accommodates 49 interchangeable blades of various types and sizes.

Its patented spring device permits quick blade insertion and removal.

It's shockproof, breakproof (UL) plastic. Comes in three sizes—regular, junior, stubby—also Tee type.

It's available in a great variety of sets from 39-piece roll kits to compact, pocket cases.

For information on time-saving, space-saving Xcelite "99" tool kits and sets, request Catalog 166.



# XCELITE

XCELITE, INC., 10 Bank St., Orchard Park, N. Y. 14127  
In Canada contact Charles W. Poynton, Ltd.  
Circle 111 on reader's service card



**DUAL CONVERSION  
SMALL SIZE • LOW POWER DRAIN  
• HIGH STABILITY • CRYSTAL CONTROLLED**

Specifically designed for simplicity of operation... efficiently engineered to give you years of service. Fits the smallest auto yet powerful enough to deliver a clear signal. Operates on 6 crystal controlled frequencies. Dual limiter & Foster Seely discriminator. Quadruple tuned RF stage for greater image rejection. Noise Free squelch, PLUG IN crystals for instant frequency change. Compatible with major continuous tone systems. Operates on 117VAC and 12VDC. Size: 6 7/8" x 2 5/8" x 8 1/2". Wt. 3 lbs. 8 oz.

**FR-104** (25-50 MHz) **\$1400** Complete with AC and DC power cables, mounting bracket, less crystals.  
**FR-105** (150-175 MHz) Crystals \$5.00 ea.

**SONAR RADIO CORPORATION**  
73 Wortman Ave., Bklyn, N. Y. 11207 Dept. 597  
Please send me information on Model FR-104/105 FM Monitor Receivers.

Name .....  
Address .....  
City ..... Zone ..... State .....

Circle 113 on reader's service card

**LISTEN TO:  
POLICE, FIRE and  
WEATHER REPORTS!**



Perfect for Industrial, Commercial, Utility and Government Use  
**SONAR SENTRY  
VHF MONITOR  
RECEIVERS**

Designed and engineered for simplicity of operation, compact enough to fit a shirt pocket yet powerful enough to deliver a clear clean signal—it's dependable • Operates on two crystal controlled VHF channels plus broadcast band • Completely solid state for long life use • Visible battery indicator to show battery condition at all times • Built in antenna • 5 7/8" H x 2 1/2" W x 1 3/8" D. Wt. 11 oz.

**\$39.95**  
**FR-103** 150-175 MHz With Battery, Earphone, & less Crystals  
**FR-106** 25-50 MHz Crystals \$5.00 ea.

**SONAR RADIO CORPORATION**  
73 Wortman Ave., Bklyn, N. Y. 11207 Dept. 597  
Please send me information on Model VHF Monitor Receivers.

Name .....  
Address .....  
City ..... Zone ..... State .....

Circle 113 on reader's service card

## ULTRASONICS

(continued from page 59)

ordinarily is very difficult; it is even more difficult to generate droplets of a desired size. This job is accomplished easily using ultrasonic waves, since this type of energy can be controlled precisely so that the particle size of the vaporized liquid is determined by the frequency and amplitude of the ultrasonic wave used.

Typical applications of such ultrasonic vaporizing include control of fuel-burning rates, carburetion, agricultural-chemical dispersion, and painting. The efficiency of heat exchangers used to heat and refrigerate closed areas also is greatly increased by applying ultrasonic waves to the interface between fluids and the heating or cooling surface.

The strength and other working properties of metals are directly dependent on their grain structure. Ultrasonic waves applied during crystallization are capable of altering basic grain orientations, creating entirely new classes of alloys and improving existing metals.

### Ultrasonics in the dairy

In the dairy industry, ultrasonic testing obsoletes the laborious methods of determining butterfat content and the percentage of other solids or solids-not-fat (SNF). One instrument includes a computer section that gives rapid, automatic, and simultaneous measurement both of solids-not-fat and butterfat in samples of fresh milk.

The time required for an ultrasonic pulse to travel through a typical milk sample is approximately 50  $\mu$ sec; the exact speed of the pulse depends on the concentration of suspended and dissolved substances and on the temperature. The presence of butterfat lowers the speed, while that of solids-not-fat raises the speed. The exact time is measured electronically and fed to the computer which determines the effect of either variable on the pulse speed. Computed values of butterfat and solids-not-fat are then displayed on meters in direct percentages.

In this introduction to a few of the present uses of ultrasonic energy, the wide range of possible applications remains largely unexplored. Certainly ultrasonic technology today is in its infancy—perhaps as much so as was electronics when de Forest was perfecting the vacuum tube. Look for new and unusual uses of ultrasound to improve existing methods of measurement, cutting, heating, cooling, and many other areas of industrial- and consumer-oriented interest. Ultrasonic devices may turn up where you'd least expect to find them. **R-E**

## COMING NEXT MONTH

**BUILD**—An IC crystal calibrator using an 80-cent integrated circuit, a crystal and a few other parts costing about \$15 has near-lab accuracy. Useful for receiver and scope calibrating.

**SERVICE**—A pH meter, used throughout industry to measure acidity, is similar to a vtvm, and just as easy to understand and troubleshoot.

**AUDIO**—Tips on how to use a tape recorder and how to get the most out of it. Learn the tricks the experts use.

**BUILD**—An adaptor for your vom that lets you measure 0.1 ohm with ease. Useful for checking ground connections, relay contacts, etc.

**SPECIAL FEATURE**—Several articles dealing with antennas and reception-improving devices. TV/FM antennas are bigger and better than ever. Homes are being outfitted with multiple TV set installations. Get the lowdown.

**BUILD**—A wideband field-strength meter using a new FET for best performance. Useful for checking transmitters in all common radio services—ham, CB, commercial two-way.

**RFI**—Radio interference is a growing problem... learn how to cope with it, in easy steps. Corrective measures you can take to reduce noise in radio and TV receivers are described.

**BUILD**—Analyzer to troubleshoot intermittent series heater strings. There's no reason to let those blinking filaments tie you up. This simple device speeds those would-be tough dogs away from your door. Yes, all this and more... in the next issue

**of RADIO-ELECTRONICS.**

## Versatile Electronic Tremolo

(continued from page 53)

to trim the 100,000-ohm resistor, depending on the values of the resistors in the circuit. Keep the leads on the photocell short, else they may pick up hum. The leads to the lamp may be any length; this means that the unit containing Q1 and Q2 can be put in any convenient place.

When the tremolo is used with an electronic organ, it is usually desirable to keep tremolo off the pedal tones (tremolo in low bass notes just doesn't sound right). Thus you may want to insert the photocell in the lead that carries signals from one or more manuals only, before the pedal tones are mixed in (Fig. 3). For more specific information, consult the diagram of your organ.

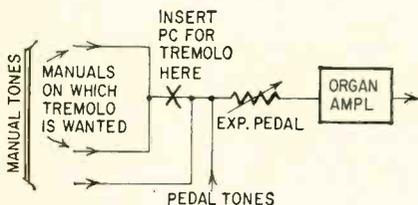


Fig. 3—You may want to split-feed an electronic organ, adding tremolo to only certain manuals, and not to others. See organ manual before attempting this.

Pipe organs generally do not have tremolo on all manuals. The *great* almost never has it, the *swell* does frequently. You may want to arrange your electronic organ similarly.

### Controls

Potentiometer R3 is for rate, R5 for depth. Although electrically the two controls are quite independent, psychologically there seems to be some interaction between rate and depth adjustments. You may want to rig up a switch with two or three values of fixed resistance so that you can select quickly, while playing, different rates or depths of tremolo.

To check out the circuit, connect an ohmmeter across the leads of PC1. If the circuit is oscillating and the lamp is glowing, the needle should fluctuate.

The 2N2646 is fairly easily damaged by heat, so use heat-sink clips when soldering, and solder quickly. Its case is connected internally to base 2, so be sure the case doesn't come into contact with any alien wires. A one-turn wrap of tape or a tight-fitting plastic tubing will prevent mishaps. **R-E**

## EDISON TECH Graduates in Demand

Why not? They are trained to be skilled technicians—in demand by industry since 1945. Industry-recognized courses in Electronics, TV, Drafting. Why not earn credits towards an Associate in Science degree while learning a vocational skill? Long-term USAF tuition loans—start repaying ten months after graduation at only 3% interest. Veterans training under GI Bill also eligible. Investigate—no obligation. Write for catalog.

**EDISON TECHNICAL COLLEGE RE-2**  
4629 Van Nuys Blvd., Van Nuys, California 91403

### MISS-Q

“A Modern FM Stereo Adapter” (August 1967) schematic on page 32 should show that the collector of Q6 is also connected to the 14-volt supply. The printed circuit board (see Correspondence Column) is correctly wired.

### COMMUNICATION RECEIVER

RCAP GR-10 COMMUNICATION RECEIVER: 115 Volt 25-60 cycle 8 Bands; 195 to 410 KC & 1400 to 31000 KC, electric band spread, var. selectivity, adj. crystal filters, noise limiter, AVC, carrier strength meter, crystal control on any one freq. to 6.8 MC. temp. & voltage reg. of oscillator, sensitivity better than 5 Mic. V. 2:1 sig. to noise ratio. Max. undistorted output 3 watts. With Tubes: 3/6SK7, 1/6K8, 1/6H6, 1/6SJ7, 1/6SQ7, 1/6F6G, 1/5Y3G & 1/4X-105. Beat freq. osc. control & prov. for speaker & headset. Size: 10 1/2 x 20 x 11 1/2".—Wt.: 85 lbs.

Prices: Used—Not Checked ..... \$209.95  
Used—Checked ..... \$99.95

### TRANS-REC. W/S CDN #29 "B" SET

Approx. 230 to 240 MC. with 12/24 VDC Power Supply self contained, and Tubes: 4/6AG5, 2/6AK6, 2/6C4, & 3/6J6. Two preset channels in the freq. range. (Ideal set for local netting on 1 1/4 meters.) Size: 4 1/2 x 8 x 11 1/2"; Wt.: 18 lbs. Price: Used ..... \$18.95

Prices F.O.B. Lima, O. — 25% Deposit on COD's — BIG FREE CATALOG — Send for your copy now. Dept. RE

### FAIR RADIO SALES

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

# NO MORE GUESSWORK!



AMERICA'S MOST RELIABLE TUBE ANALYZER

## CONTINENTAL

You don't need three guesses to tell if a tube is bad—or why. With the new Sencore MU140 Continental, you **know**. Right now. And you simply can't go wrong. Because it's a complete tube analyzer for 4-way testing—true mutual conductance (using exclusive 5000 hertz square wave), full cathode emission, 100 megohm grid leakage, and internal shorts. Tests all tubes, including foreign—over 3000 in all. Obsolescent-proof, too—with “new socket” panel, and controls so standard the switch numbers correspond to the pin numbers in any tube manual.

If it's reliability you want—for years to come—you need the Continental. It's the best way to be sure—

for only

**\$179<sup>50</sup>**

See America's most complete line of professional test instruments—at your Distributor now.



## SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT  
426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 114 on reader's service card

# NEW!

A BETTER WAY TO REPLACE SOLDERED COMPONENTS

LENGTH 8" WEIGHT 3 1/2 OZ.

**ENDECO**

**Pencil Desoldering Iron**  
MODEL 300

Now—remove miniature soldered components in seconds—without damage


Hollow tip fits over connection; vacuums all solder for easy removal of component. Leaves terminals and mounting holes clean. Then, with 360° contact, it resolders even faster and better than regular irons. Handles miniature and standard components in printed circuit boards and conventional wiring. Self-cleaning. All parts replaceable. 40 watts, 115-v. 5 tip sizes. Pays for itself in time saved. \$9.95 net East of the Rockies.

Larger model available. See your distributor or write:

ENTERPRISE DEVELOPMENT CORPORATION  
5157 E. 65th · INDIANAPOLIS, IND. 46220

Circle 115 on reader's service card

# FREE!

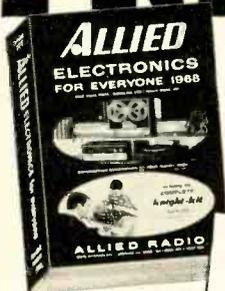

**ALLIED**  
NEW 1968  
CATALOG

518  
PAGES

SAVE ON:

- Famous Knight-Kits®
- Stereo Hi-Fi
- Tape Recorders, Tape
- CB 2-Way Radios
- Walkie-Talkies
- FM-AM & AM Radios
- Shortwave Receivers
- Portable TV
- Phonographs
- Amateur Gear
- Intercoms & PA
- Automotive Electronics
- Test Instruments
- TV Antennas & Tubes
- Power Tools, Hardware
- Tubes, Transistors
- Parts, Batteries, Books

TOP SAVINGS ON THE BEST IN ELECTRONICS FOR EVERYONE

Shop by mail and save at Allied, world's largest electronics headquarters. Hundreds of money-saving values. NO MONEY DOWN. Up to 2 years to pay!

MAIL COUPON BELOW

ALLIED RADIO, Dept. 2B  
P.O. Box 4398, Chicago, Ill. 60680

NAME (Please Print)

ADDRESS

CITY

STATE

ZIP

Circle 116 on reader's service card

## NEW LITERATURE

All booklets, catalogs, charts, data sheets and other literature listed here with a Reader's Service number are free for the asking. Turn to the Reader's Service Card facing page 74 and circle the numbers of the items you want. Then detach and mail the card. No postage required!

**1968 ELECTRONICS CATALOG, No. 270**  
518-page book gives information on the newest hi-fi components and tape recorders; videotape recorders, monitors and cameras; transistorized AM/FM and shortwave radios; phonographs and turntables; TV sets; car radios and stereo tape players; walkie-talkies and Citizens Band 2-way radios and accessories. Also lists sound equipment, ham gear, audio equipment, motorcycle accessories, test instruments, and includes complete Knight-Kit catalog.—Allied Radio Corp.

Circle 65 on reader's service card

**RESISTANCE SOLDERING & THERMAL WIRESTRIPPING EQUIPMENT.** Covers power-control units ranging from three-power through infinitely variable to multipurpose, timed consoles. Hand pieces include a microsoldering probe for 1/64" solder pad connections, and miniature tweezer-type strippers through heaviest-duty types, accessories and replacement electrodes and elements. There is a question-and-answer section for user's guidance.—American Electrical Heater Company

Circle 66 on reader's service card

**ISOTHERM MATCHED THERMISTORS, Bulletin MTM 141.** Dual-purpose matched thermistors can be used wherever resistance vs temperature-curve matching is required. 4-page booklet contains comprehensive resistance vs temperature table for interchangeable thermistors. Describes electrical characteristics and gives design criteria. Illustrated with performance curves and typical performance tables.—Victory Engineering Corp.

Circle 67 on reader's service card

**PHOTOGRAPHIC EQUIPMENT, 180 pages.** Incorporates a complete listing of the latest professional-quality photographic equipment, including lenses, cameras, lights and dark-room equipment. Lists everything from a complete color lab to a lens brush.—Burke and James, Inc.

Circle 68 on reader's service card

**ADJUSTABLE CRIMPING TOOLS.** Illustrated 6 page bulletin, No. TA 100, describes a new line of eight-indent, cycle-controlled crimping tools. Includes adjustable standard and miniature microcrimp tools and the crimping tool kit which contains the tool with two turret head assemblies, socket-head screw key, service inspection gauge, and 9-page set of instructions, all housed in a metal box.—Buchanan Electrical Products Corp.

Circle 69 on reader's service card

**MEASURE NOISE-POWER DENSITY, Application Note AN-63C.** 6 pages. Presents procedure for measuring noise-power density with model H10-851B/8551B spectrum analyzer (10.1 MHz-40 GHz). Provides instructions for calibrating noise bandwidth and power density, and performing the actual measurement. Appendix gives theoretical considerations.—Hewlett-Packard Co.

Circle 70 on reader's service card

**AMATEUR ANTENNAS, No. H-174.** 26-page catalog of antennas, beams, beam-conversion kits, stacking kits, verticals, dipoles, ground planes, mobile and receiving antennas and amateur accessories. Includes specs and features, model numbers and nearest stores for ordering convenience. Flyers also available.—Mosley Electronics, Inc.

Circle 71 on reader's service card

**PLASTIC TRANSISTOR SELECTION GUIDE.** Contains a replacement table, all major device parameters, voltage-vs-current selection and parameter interrelationship table. Npn and pnp types are included in this 6-page guide.—Motorola Semiconductor Products, Inc.

Circle 72 on reader's service card

**TOOL CATALOG, NC Flasher.** Features small tools such as the metric tap and die set, vacuum tweezers for handling delicate miniature parts, a small gas welding torch, belts for movie projectors, horn anvils, automatic wire strippers and angle-crown scissors. Prices specs and model numbers given.—National Camera, Inc.

Circle 73 on reader's service card

**1968 CATALOG.** Contains 740 pages of products, prices and technical data. Features 160 pages of integrated circuit listings and a complete semiconductor directory. 350 manufacturers' lines are covered. Contains product, MIL spec and manufacturer's indexes.—Newark Electronics Corp.

Circle 74 on reader's service card

**ELECTRONICS AND TELECOMMUNICATIONS.** This 32-page brochure is of interest to the electronic- or communications-minded. It describes the role in these fields of such NEC products as electron tubes and lasers, integrated circuits, and electric household appliances. Well-done and interesting, this brochure is worth reading.—Nippon Electric Co.

Circle 75 on reader's service card

**SHIELDING PRODUCTS AND SERVICES.** New 16-page catalog covers EMI materials and magnetic shielding alloys. Contains a variety of wire mesh constructions, wire and elastomer combinations, RFI ventilation panels, and gasket formations. Includes magnetization curves on shielding alloys with high permeability and high saturation.—Primec Corp.

Circle 76 on reader's service card

**STEREO CONSOLES.** 24-page 1968 brochure features new line of stereo consoles in decorator-styled room settings. Includes articles on hi-fi music in the home, choosing a console to match room decor, and non-technical explanations of the technical aspects of stereo consoles.—H. H. Scott, Inc.

Circle 77 on reader's service card

**SEALED NICKEL-CADMIUM CELLS, No. BA-112.** This 12-page booklet tells about the origin, electrical characteristics, charging capacities, specs, and makeup of the sealed nickel-cadmium cell. Illustrations.—Sonotone Corp.

Circle 78 on reader's service card

Write direct to the manufacturer for information on the item listed below:

**TUBE APPLICATION REPORT, No. P-111.** 19-page booklet contains a complete discussion of Thyratron tubes with useful information and data on their design and application. Gives operating fundamentals, circuit considerations, installation tips, definitions of ratings, and operating characteristics. Amperex Electronic Corp., Product Manager, Industrial Tubes, Hicksville, N.Y. 11802. **R-E**

# Be Sure and See These Brand-New G-V-TAB Books at Your Parts Distributor!



**PRACTICAL COLOR TV SERVICING TECHNIQUES:** Loaded with easy methods and dozens of case histories on locating and repairing problems in both old and new color sets. Discusses new portables and solid-state receivers only recently introduced! Learn new techniques for isolating troubles. 304 pps.; 230 illus.; 8-p. schematic foldout; Dozens of full-color photos. Order No. 436 only \$4.95



**EASY WAY TO SERVICE RADIO RECEIVERS:** A long-needed new book devoted exclusively to servicing standard AM receivers. Tells how to diagnose and correct troubles in any kind of tube or transistor set. Virtually every possible circuit defect is included on dead sets, noisy reception, hum, distortion, and intermittents. 192 pps.; 10 Ch.; over 100 Schematics & photos. Paper. Order No. 429 only \$3.95



**NEW WAYS TO DIAGNOSE ELECTRONIC TROUBLES,** by Jack Darr. Looking for new ways to diagnose trouble in radio, TV, and electronics circuits? Well, here they are—condensed into a 256-page volume! You'll literally chop troubleshooting time to the bone when you put these new methods into action. 256 pps.; 15 ch; Heavily illus. Paper. Order No. 427 only \$4.95



**HOW TO USE YOUR VOM-VTVM & OSCILLOSCOPE:** 3 books in ONE! Ideal guide for anyone who wants to brush up on the VOM, VTVM, and scope. Whether you want to know just how each instrument works, or how it can be used most effectively in everyday applications, this volume contains the answers. 160 pps.; 13 Chapters; scores of illus. Paper. Order No. 438 only \$3.95



**PIN-POINT TV TROUBLES IN 10 MINUTES:** A MAMMOTH, quick-answer guide to over 700 TV circuit troubles. Contains 63 large-size photos of different picture-troubles, keyed to trouble-finding charts to help you pinpoint over 700 probable defects, you can pinpoint almost any TV circuit for probable causes for defects. 372 pps., 394 illus. 160 waveforms; 18 Ch. Hardbound. Order No. 428 only \$6.95



**PINPOINT TRANSISTOR TROUBLES IN 12 MINUTES:** A GIANT of a book—495 pages—a virtual library of practical data of value to everyone who works with transistor circuits. Here is a unique servicing text you can put to immediate use on home-entertainment or industrial type equipment. A servicing reference for all types (over 100) of transistor circuits. Hardbound. Order No. 430 only \$6.95



**FET APPLICATIONS HANDBOOK:** Chock-full of current, practical FET circuit design data! Includes latest info on FET types, parameters, and characteristics, and operational modes. Covers linear applications, chopper and switching circuits, integrated circuits, and photo-FETS. Includes many basic circuit descriptions. 23 Chapters; 228 pages; 225 illus. Hardbound. Order No. 240 only \$12.95



**RADIO-CONTROL MANUAL (REVISED EDITION)** By Edward L. Safford, Jr. Completely revised with 70% new material, this long-time favorite has been brought up-to-date. Principles of radio-controlling model planes, boats, cars, etc., from super simple to super sophisticated. Circuits (tubes and transistor) that you can build and use. 192 pages. Paper. Order No. G-91 only \$3.95



**TEN-MINUTE TEST TECHNIQUES FOR ELECTRONICS SERVICING:** Describes how trouble in any piece of electronic equipment may be pinpointed quickly and easily. Step-by-step techniques for localizing trouble to an improperly operating stage and then to the defective component itself, using a minimum of test equipment. 176 pps., 125 illus. Paper. Order No. 424 \$2.95



**TV TROUBLESHOOTER'S HANDBOOK:** A carefully-planned reference source of over 350 different, tried and tested solutions to "tough-dog" TV servicing problems. A complete digest of late-model TV receiver troubles and cures, new and unusual circuits and descriptions of how they work, field and factory changes, recurring defects, etc. 125 illus. Paper. Order No. T-401 \$2.95



**TV RECEIVER CIRCUITS:** Just the kind of "how-to-do-it" handbook every practicing TV service technician should have. Contains the TV service data most needed for troubleshooting both monochrome and color receivers, all in one handy volume. Practical used in the home or at the service bench. 224 pps. Paper. Order No. 414 \$2.95



**ELECTRONIC ENGINEERING MEASUREMENTS FILEBOOK:**—A single source of measurement principles and practices. Describes detailed techniques, complete with test setups, waveforms, mathematical analyses, etc., for measuring. One of the most complete collections of its type available today, containing 60 complete "How-to-Measure" sections. 256 pps. Paper. Order No. T131 \$4.95



**ELECTRONIC DESIGNER'S HANDBOOK:** A 296-p. practical guide to transistor circuit design—the best ever written for the engineering tech. Contains much unpublished material. 200 illus. Hardbound. No. 228 only \$8.95



**THE MAN BEHIND THE MIKE:** 288 page guide to professional broadcast announcing. Contains literally hundreds of practical, down-to-earth pointers—offers practical help on every phase of announcing! Hardbound. No. 266 only \$9.95



**CATV SYSTEM ENGINEERING:** 2nd Edit. of the accepted technical standard on CATV—all about planning, designing and operating CATV. Covers newest solid-state eqpt. 224 pps.; 140 illus.; 13 Chapters. Hardbound. No. T-98 only \$12.95



**CATV SYSTEM MAINTENANCE:** Covers all phases of maintaining a CATV system—from the antenna thru construction techniques, troubleshooting, eliminating interference, etc. Hundreds of tips! 192 pps. Comb-bound. No. T-82 only \$12.95



**CONNECTING DIAGRAMS FOR INDUCTION MOTORS:** Contains 72 connection diagrams for practically any type of lap-wound induction motor. Tells how to rewind and reconnect induction motors! 27 Ch. No. T-96 only \$5.95



**ELECTRIC MOTOR TEST & REPAIR:** A practical, time-saving workshop book of essential data on all phases of re-winding and testing fh motors. A must for motor repairmen! 160 pps. Order No. T-97 only \$6.95




**PROCEEDINGS OF 1967 NAB ENGR. CONFERENCE:** Vital source of ideas to help radio and TV broadcasters keep pace with tomorrow. Covers eqpt., measurements, color TV, maintenances. 256 pps; 8 1/2" x 11". No. T-140 only \$10.00



**BROADCAST ANTENNA SYSTEMS HANDBOOK:** Practical guide to all type and styles of broadcast antennas. Covers preparing FCC data, designing, engineering, improving coverage, measurements, etc. Comb-bound. No. T-44 only \$7.95



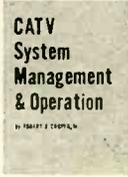**FM RADIO STATION OPERATIONS HANDBOOK:** Complete guide to FM station engineering, operation and management. Covers automation, studio design and operation, remote control, recording, etc. 192 pps. 25 Ch. No. T-94 only \$9.95



**CATV SYSTEM MANAGEMENT & OPERATION:** Complete guide to CATV—from locating new CATV situations thru financing, acquiring franchises, budgeting, opening a system, etc. 250 pps. Comb-bound. No. T-100 only \$12.95



**RADIO PROMOTION HANDBOOK:** Complete guide on ways to develop better ratings, improve results and increase sales. Jam-packed with 100's of ideas on on-air and off-air promotions! Comb-bound. No. 267 only \$9.95



**CATV OPERATOR'S HANDBOOK:** New, practical guide to all phases of CATV—franchising, planning, financing, selling hookups, local program origination, etc. 160 pps. Comb-bound. Order No. T-73 only \$7.95

**TAB BOOKS**  
Gernsback Library  
Winter 1967



## FREE Catalog

Over 100 quality books on the subjects shown below are described in our brand-new catalog. Send for your FREE copy today.

- Radio and TV Servicing
- Electrical Motor Repair
- Electronics Technology
- Electronic Hobbies
- Electronic Engineering
- Broadcasting and CATV

**NO RISK COUPON — MAIL TODAY**

TAB Books, Blue Ridge Summit, Pa. 17214  
Please send me the books listed below:

I enclose \$..... (Save postage by remitting with order)

Please invoice on 10-day FREE trial

Name .....

Company .....


Address .....

City ..... State ..... Zip .....


My distributor is: ..... RE 28

# JERROLD

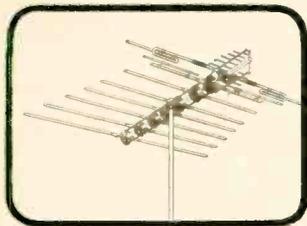
## Focusing on one thing... better reception




Outdoor antennas

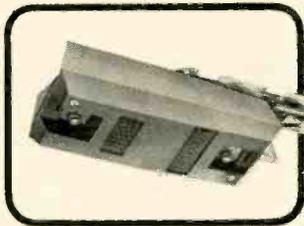


Home preamplifiers

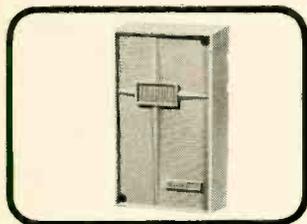

Distribution equipment

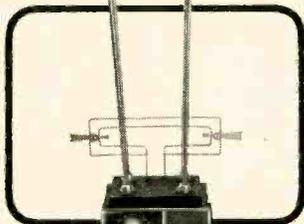

Indoor antennas

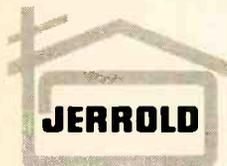


### Jerrold Electronics Corporation

Distributor Sales Division  
401 Walnut St., Philadelphia, Pa. 19105

Circle 118 on reader's service card

## GAS WELDING TORCH

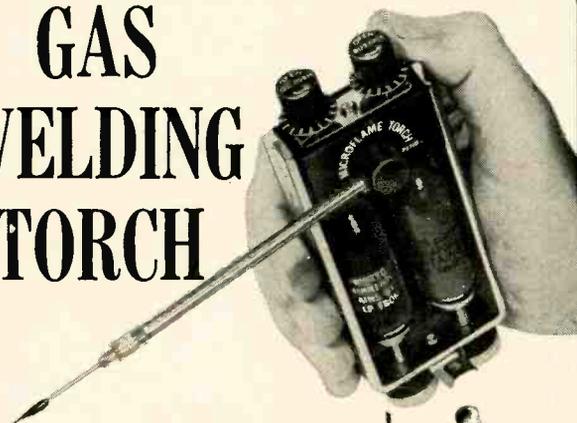

Uses **OXYGEN**  
and **LP GAS**

- Completely self-contained.
- Produces 5000° pin-point flame.
- Welds, brazes, solders.
- Hundreds of lightweight uses.
- Suggested list — \$19.95.

GET COMPLETE DETAILS AT MOST INDUSTRIAL DISTRIBUTORS, OR WRITE TO MICROFLAME, INC.



HOME WORKSHOP



TECHNICIANS



REPAIR AND SERVICE SHOPS

### MICROFLAME, INC.

7800 COMPUTER AVENUE  
MINNEAPOLIS, MINNESOTA 55424

Circle 119 on reader's service card

## EQUIPMENT REPORT

(continued from page 70)

hours of useful life. (Of course, current varied with volume setting.)

Then I ran battery 4 several hours per day in the radio, and recharged it equal time with the PNP-10. Out to 50 hours battery voltage remained constant at 8.0. After that, it would drop after a few hours of use, and I had to limit playing time to about 5 hours—followed by recharging. Otherwise the voltage might have fallen so far the battery couldn't be recharged. I reached the point of no return at about 200 hours, when the battery died. I got similar life from batteries 5 and 6.

I paid \$1.31 for a TR-146X. Without recharging, each battery lasted 46 hours for a cost of 2.86 cents per hour. With recharging, life was 200 hours, for a cost of 0.655 cent per hour.

I pay 4 cents per kilowatt-hour to the power company and, allowing for 50% charging efficiency, the PNP-10 probably doesn't draw more than 0.2 watt. Hence I paid all of .0008 cent per hour for the current the recharger drew. To recharge a TR-146X for 200 hours costs \$0.0016, which you can just about forget.

The actual battery cost had thereby dropped 1/5—from \$1.31 to \$0.26—for a saving of \$1.05 on each battery. Considering the PNP-10 cost, I figure that after using and recharging 6 batteries the device will have paid for itself.

Of course, if you want to run your radio off the ac line exclusively, your battery life will equal shelf life. And the cost of the ac will never break you!


I didn't try zinc-carbon cells, so I don't know what savings you'd get with them.—*Thomas R. Haskett*

Price: \$5.95
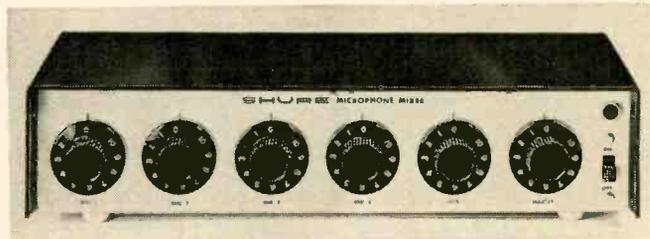
### Shure M68 Microphone Mixer

Circle 21 on reader's service card

THIS EXCELLENT MIXER FOR PUBLIC ADDRESS AND SERIOUS amateur recording work meets or exceeds all its specs. I found distortion at rated output somewhat lower than specified: 0.2% for 1 volt output into high impedance at 1 kHz, rising to 0.4% at 20 kHz, and to 1% at 3.5 volts, 1 kHz. This last figure was measured with 50 mV input—roughly a hundred times the voltage produced by a low-impedance mike.



The M68 has four mike-input channels, all switchable from high-impedance unbalanced to low-impedance balanced or unbalanced with a tamper-resistant switch over each input connector on the back. All mike connectors are male Cannon XLR-3-14's, the three-prong positive-locking types used in almost all broadcast and recording studios.

An additional input accepts signals at a slightly higher

level, from a tuner or tape or phono preamp. Its input impedance is fixed at 50,000 ohms. (The input may be somewhat too sensitive for many applications, but that can be taken care of by inserting an extra resistor of 150,000 or so ohms in series with the input right at the jack.)

Control interaction was low enough, I found, for non-critical speech or music mixing. With any one control at midposition, turning any other control from zero to full on produced a 1-dB drop in output. Interaction is worst at low settings of each control, and decreases as the control is turned up.

Three kinds of output are available from the M68. The output Cannon connector can be switched to produce an average output of about a millivolt for feeding to the low-impedance mike input of a recorder or console. The same connector can be switched for unbalanced high-impedance feed (typically about 20 mV) for the high-impedance mike input of a recorder or amplifier.

Third, an ordinary phono jack provides a level on the order of a volt or two for feeding "high-level," "line" or "auxiliary" inputs of recorders or amplifiers. This output can also be connected to the auxiliary input of another M68, giving a stacked mixer good for eight microphone channels and one high-level auxiliary input.

The noise level of the M68 is low enough for all PA work, and for all but highly critical serious recording. The mixing circuitry is relatively conventional. Each mike input, after going through a matching transformer, is amplified by one transistor, which feeds a current-divided mixer control through an isolation resistor (to reduce interaction).

The controlled outputs are "collected" along a mixing bus. The AUX input feeds the bus directly, unamplified, through a 47,000-ohm resistor. A two-transistor amplifier feeds the outputs, via the MASTER gain control.

The M68 is about as small as it can be made without making the knobs too small to get hold of. Professionals who are accustomed to 2- and 3-inch knobs are going to be annoyed with these, but most people will find the compactness of the M68 a joy.

It's pretty rugged inside and out, and should take quite a bit of banging around in the back of a sound truck. Nothing about the unit is delicate. Inside, all transistors, resistors and capacitors are rigidly mounted to terminal strips. The channel-form chassis and its cover brace each other when assembled.

A device like this should never need servicing, but if it does, everything is instantly accessible by removing the cover (four screws).


Finally, the M68 can be powered from the ac line (built-in transformer power supply) or from an external 22- to 28-volt supply. An export model, the M68-2, offers a choice of 155- or 230-volt power-line inputs.

A lab prototype of this unit which I saw about a year and a half ago had a steel cover that fitted over the control panel and could be padlocked in place. This production model doesn't have that. It seemed a good idea, since the mixer then becomes quite safe for unsupervised operation. The controls can be set by the sound man, then locked behind the cover beyond the reach of people of the twiddling kind. Perhaps Shure will decide to make such a cover available as an option.—Peter E. Suthain

#### MANUFACTURER'S SPECIFICATIONS


Frequency response:  $\pm 2$  dB, 30 to 20,000 Hz  
 Hum, noise: 70 dB below rated output  
 Equivalent input noise: 123 dB below 1 volt, 150-ohm source  
 Output clipping levels: 60mV at low-Z mic. output; 850 mV at hi-Z mike. output; 4 volts at AUX hi-Z output  
 Distortion: less than 1% total harmonics when low-Z mic output is 20 mV, hi-Z mike output is 200 mV, AUX output is 2 V.  
 Weight: 4 lb  
 Price: \$75.00

R-E

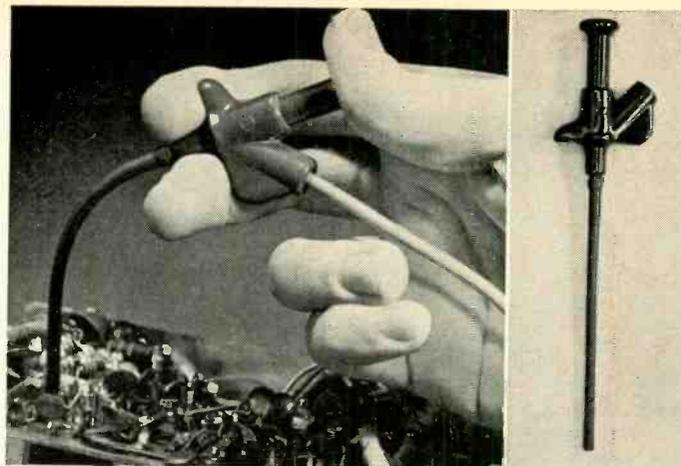
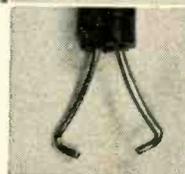
## Clever Kleps 30

Push the plunger. A spring-steel forked tongue spreads out. Like this Hang it onto a wire or terminal, let go the plunger, and Kleps 30 holds tight. Bend it, pull it, let it carry dc, sine waves, pulses to 5,000 volts peak. Not a chance of a short. The other end takes a banana plug or a bare wire test lead. Slip on a bit of shield braid to make a shielded probe. What more could you want in a test probe?



**\$147**



Available through your local distributor, or write to:

**RYE INDUSTRIES INC.**  
 126 Spencer Place, Mamaroneck, N.Y. 10543

Circle 120 on reader's service card

Designed and manufactured in U.S.A.

## NEVER A BURNOUT

IN 6 EMC DIODE-PROTECTED VOMS

NOBODY ELSE BUT EMC DESIGNS IN SO MUCH VALUE!  
 • Professional quality and versatility • Lifetime protection against electrical abuse • No meter burn-out, needle damage, or fuse replacement

#### VOLOMETER

Model 109A Factory Wired & Tested **\$28.35**  
 Model 109AK Easy-to-Assemble Kit **\$21.15**  
 20,000  $\Omega/v$  DC sens. 10,000  $\Omega/v$  AC sens. 4 1/2", 40  $\mu$ a meter. High impact bakelite case. 5 DC voltage ranges: 0-6-60-300-600-3000v. 5 AC voltage ranges: 0-12-120-600-1200-3000v. 3 DC current ranges: 0-6-60-600ma. 3 AC current ranges: 0-30-300ma; 0-3A. 3 resistance ranges: 0-20K, -200K, -20 megs. 5 db ranges: -4 to +67db. With carrying strap. 5 1/4" W x 6 3/4" H x 2 7/8" D.

#### VOLOMETER

Model 103A Factory Wired & Tested **\$20.75**  
 Model 103AK Easy-to-Assemble Kit **\$16.80**  
 4 1/2", 2% accurate, 800  $\mu$ a D'Arsonval type meter. One zero adjustment for both resistance ranges. High impact bakelite case. 5 AC voltage ranges: 0-12-120-600-1200-3000v. 5 DC voltage ranges: 0-6-60-300-600-3000v. 5 db ranges: -4 to +64db. 5 AC current ranges: 0-30-150-600ma. 4 DC current ranges: 0-6-30-120ma; 0-1.2A. 2 resistance ranges: 0-1K, 0-1 meg. 5 1/4" W x 6 3/4" H x 2 7/8" D.

#### POCKET SIZE VOLOMETER

Model 102A  
 Factory Wired & Tested **\$16.95**  
 Model 102AK Easy-to-Assemble Kit **\$14.40**  
 3 1/2", 2% accurate 800  $\mu$ a D'Arsonval type meter. One zero adj. for both res. ranges. High impact bakelite case. 5 AC voltage ranges: 0-12-120-600-1200-3000v. 5 DC voltage ranges: 0-6-60-300-600-3000v. 3 AC current ranges: 0-30-150-600ma. 4 DC current ranges: 0-6-30-130ma; 0-1.2A. Resistance: 0-1K, 0-1 meg. 3 3/4" W x 6 1/4" H x 2" D.



EMC, 625 Broadway, New York 12, N.Y.

Send me FREE catalog of the complete value-packed EMC line, and name of local distributor.

NAME \_\_\_\_\_ RE-2

ADDRESS \_\_\_\_\_


CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

**EMC**

ELECTRONIC MEASUREMENTS CORP.  
 625 Broadway, New York 12, New York  
 Export: Pan-Mar Corp., 1270 B'way, N.Y. 1
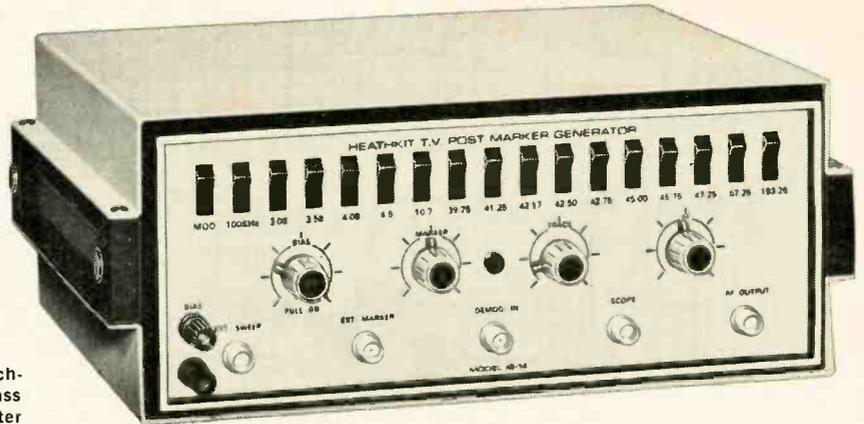
# 8 NEW KIT IDEAS FROM HEATH . . .

**Attention TV Servicemen!**  
**Introducing The All New Heathkit**  
**Solid-State Crystal-Controlled Post**  
**Marker Generator . . . The Most**  
**Important Instrument You Can Own For**  
**Color TV And FM Alignment . . . Now**  
**At A Fraction Of The Usual Cost**



IG-14  
**\$99.95**  
 no money dn., \$10 mo.

- 15 crystal-controlled marker frequencies • Switch-select picture and sound IF frequencies, color bandpass and trap frequencies, 6 dB points, plus FM IF center frequency and 100 kHz points • Use up to six markers simultaneously for faster TV alignment • Birdie-type markers • Trace and Marker amplifiers and size controls • 400 Hz modulator • Variable bias supply • All solid-state, 22 transistors, 4 diodes • Circuit boards

**Fast, Accurate Color Alignment.** Speed and accuracy are important in today's service work . . . important to your customers, important to your profits. Speed and accuracy are what the new Heathkit IG-14 gives you . . . plus features usually costing five to ten times as much.

**Just Push A Button.** That's all it takes to set a frequency . . . no dial to twiddle, no searching, no resetting problems. Fifteen switch selected crystal-controlled markers. Nothing could be easier or more accurate. The IG-14 has input and output connections so that it can be used with any sweep generator and scope. Also an external marker input. BNC connectors are used throughout.

**No Trace Distortion.** One of the big values to using a post marker generator like the IG-14 is that markers are injected after the sweep signal passes through the set being tested, thereby eliminating the 'scope trace distortion usually found when injection or absorption type marker generators are used.

**Crystal-Controlled Markers For Any TV Alignment Task.** Four marker frequencies are provided for setting color bandpass, one marker for TV sound, eight at the IF frequencies between 39.75 and 47.25 MHz, and markers for channel 4 and channel 10 picture and sound carriers for checking tuner RF response. With the ability to use up to six markers at once, such as picture and color carriers at 6 dB points, corner marker and trap frequencies, alignment is fast and precise. Trap alignment is just a matter of selecting the appropriate trap frequency, applying the 400 Hz modulation, and tuning the trap for minimum audio on a scope or meter.

**Easy FM IF and Discriminator Alignment.** The IG-14 provides visible markers at the 10.7 MHz center frequency plus 100 kHz markers on each side . . . visible because they are applied to the trace after detection and so are not attenuated by the discriminator. Use of harmonics, fully explained in the manual, provide tracking markers as well.

**Trace and Marker Amplitude Controls . . .** on the front panel permit using a regular service type 'scope instead of a wide-band, ultra-sensitive model . . . and stage by stage alignment is easier.


**Variable Bias Supply . . .** 0 to 15 VDC @ 10 milliamps is isolated from chassis so you can use positive or negative bias.

**New Look . . . Circuit Board Construction.** Handsome low profile, "stackable" cabinets in the new look of Heath instruments . . . finished in beige and black. Easy-to-build layout with two circuit boards.


**Save Hundreds of Dollars.** Until now, an instrument with these features cost much more. Order the IG-14 now . . . it's the best investment in alignment facilities you can make.

Kit IG-14, 8 lbs., no money dn., \$10 mo. . . . . **\$99.95**

**IG-14 SPECIFICATIONS—Crystal Marker Frequencies:** 3.08, 3.58, 4.08, 4.5, and 10.7 MHz @ .01%; 39.750, 41.250, 42.170, 42.500, 42.750, 45.000, 45.750, 47.250, 67.250, and 193.250 MHz @ .005%. **FM Bandwidth Marker:** 100 kHz. **Modulation:** 400 Hz. **Input Impedance:** External sweep, 75 ohm; External marker, 75 ohm; Demodulation input, 220K ohm. **Output Impedance:** RF output, 75 ohm; Scope output, 22K ohm. **Bias Output Voltage:** Variable from 0 to 15 VDC @ 10 MA. Isolated from chassis for either negative or positive bias. **Type of Marker:** "Birdie." **Controls:** Bias voltage with AC on/off; Trace size; Marker amplitude; RF output; Modulation on/off; Markers, individual switches for each frequency. **Semiconductors:** Transistors: (16) 2N3692; (6) 2N3395; (3) Silicon diodes; (1) Zener diode, 13.6-V. **Power requirements:** 105-125 volts, 50/60 Hz AC @ 7.5 watts. **Net weight:** 8 lbs.

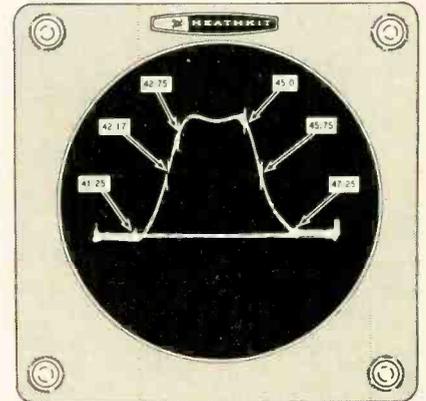

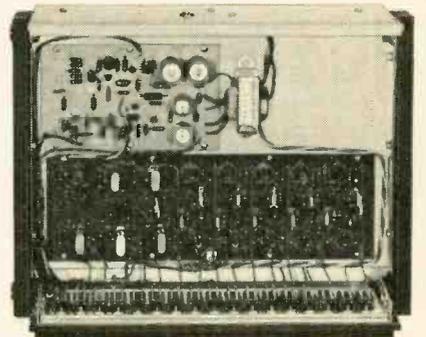**SIX MARKERS SIMULTANEOUSLY.** The scope trace above shows how six markers can appear at the same time. Note the trap markers, 6 dB points, and picture and sound carriers . . . all on one trace with the IG-14.



**EASY TO BUILD.** Note how everything except the front panel switches and controls mount on two circuit boards . . . even the crystals.



IO-17  
**\$79.95** no money dn., \$8 mo.

## NEW Heathkit 5 MHz 3" Compact 'Scope - Only \$79.95

**Destined To Set The Value Pace . . .** the new Heathkit IO-17 with its superior response and sensitivity, professional features, compactness, handsome new styling, and low cost . . . will find its way into shops and labs the world over. It's your best wide-band 'scope buy!

Kit IO-17, 17 lbs.,  
 no money dn., \$8 mo. . . . . **\$79.95**

**IO-17 SPECIFICATIONS — VERTICAL CHANNEL:** Input impedance: 1 megohm shunted by 25 pF; x50 attenuator position

1 megohm shunted by 15 pF. **Sensitivity:** 30mV P-P/div. (uncalibrated). **Frequency response:** 5 Hz to 5 MHz  $\pm 3$  dB. **HORIZONTAL CHANNEL:** Input impedance: 10 megohm shunted by 15 pF. **Sensitivity:** 300 mV P-P/div. **Frequency response:** 2Hz to 300 kHz  $\pm 3$  dB. **HORIZONTAL SWEEP GENERATOR:** Sweep generator: Recurrent type. **Frequency:** 20 Hz to 200 kHz in four overlapping ranges. **Retrace:** Blanked by a pulse from blanking amplifier. **Synchronization:** Automatic type. **GENERAL:** Tube complement: (1) 3RP1 cathode ray tube, medium persistence, green trace; (3) 12AU7; (1) 12AX7; (1) 6GH6; (1) 6BH6; (1) 6BQ7. **Power requirements:** 105-125 volts 50/60 Hz or 210-250 volts 50/60 Hz. **Power consumption:** 60 watts. **Overall dimension:** 9 $\frac{1}{2}$ " H x 5 $\frac{1}{2}$ " W x 14 $\frac{1}{8}$ " L. (Dimensions include handle, knobs, etc.). **Net weight:** 12 lbs.

# USE COUPON BELOW TO ORDER NOW

## NEW! VOX "Jaguar" Transistor Combo Organ By Heathkit



Kit TO-68  
**\$349.95**  
\$35 dn., \$30 mo.

Save Up To \$150 on the world's most popular combo organ with this new Heathkit version. Features the most distinctive sound of any combo organ. Has a special bass output that gives a brilliant stereo bass effect when played through a separate or multi-channel amplifier, 4 complete octaves, vibrato, percussive effects and reversible bass keys. Includes hand crafted orange and black cabinet, fully plated heavy-duty stand, expression pedal and waterproof carrying cover and case for stand. Requires a bass or combo amplifier like Heathkit TA-17 (opposite page).

Kit TO-68, 80 lbs. . . . \$35 dn., \$30 mo. . . . . **\$349.95**

## NEW! Deluxe Solid-State Combo Amplifier & Speaker System . . . Choose Kit Or Factory Assembled

Amplifier  
Kit TA-17  
**\$175**  
\$17 mo.  
(Assembled  
TAW-17 \$275)

Speaker System  
Kit TA-17-1  
**\$120**  
\$11 mo.  
(Assembled  
TAW-17-1 \$150)

**Special  
Combination Offer**  
Amplifier & Two  
Speaker Systems  
Save \$20  
Kit TAS-17-2  
**\$395**  
\$40 dn.  
\$34 mo.  
(Assembled  
TAW-17-2 \$545)



All the "big sound" features every combo wants . . . tremolo, built-in "fuzz", brightness, reverb, separate bass and treble boost and more. Delivers a shattering 120 watts EIA music power (240 watts peak power) through two TA-17-1 speakers . . . or 90 watts through one TA-17-1 speaker. Features 3 independent input channels, each with two inputs. Handles lead or bass guitars, combo organ, accordion, singer's mike, or even a record changer. All front panel controls keep you in full command of all the action.

Speaker system features two 12" woofers, special horn driver and matching black vinyl-covered wood cabinet with casters & handles for easy mobility.

## NEW! Lowest Cost Solid-State Stereo Receiver

Kit AR-17  
**\$72.95**  
(less cabinet)  
\$8 mo.



Features wide 18-60,000 Hz response @ ±1 db at full 5 watts RMS power per channel . . . 14 watts music power . . . inputs for phono and auxiliary . . . automatic stereo indicator . . . outputs for 4 thru 16 ohm speakers . . . adjustable phase for best stereo . . . flywheel tuning . . . and compact 9 3/4" D. x 2 7/8" H. x 11 3/4" W. size. 12 lbs. Optional factory assembled cabinets (walnut \$7.95, beige metal \$3.50).

Kit AR-17, (less cab.) 12 lbs. . . . no money dn., \$8 mo. . . . **\$72.95**  
Kit AR-27, 7-Watt FM Mono Only Receiver (less cab.)  
9 lbs. . . . no money dn., \$5 mo. . . . . **\$49.95**



Kit AR-15  
**\$329.95**  
(less cabinet)  
\$28 mo.  
Assembled  
ARW-15 \$499.50  
(less cabinet) \$43 mo.

## World's Most Advanced Stereo Receiver

Acclaimed by owners & experts for features like integrated circuits & crystal filters in IF amplifier; FET FM tuner; 150 watts music power; AM/FM and FM stereo; positive circuit protection; all-silicon transistors; "black magic" panel lighting; and more. Wrap-around walnut cabinet \$19.95

Kit AR-15 (less cab.), 34 lbs. . . . \$33 dn., \$28 mo. . . . **\$329.95**  
Assembled ARW-15, (less cab.), 34 lbs. . . . \$50 dn.,  
\$43 mo. . . . . **\$499.50**

## Professional 10-Band Shortwave Receiver

Kit SB-310  
**\$249**  
\$23 mo.



Covers 49, 41, 31, 25, 19 & 16 meter shortwave . . . 80, 40 & 20 meter ham . . . 11 mete CB Includes 5 kHz crystal filter for AM, SSB and CW listening. Features selectivity that slices stations down to last kHz; 11-tube circuit; crystal-controlled front-end and more. 20 lbs. SB-600 8 ohm 6" x 9" speaker in matching cabinet \$18.95.

## NEW! Solid-State Portable Volt-Ohm-Meter

Kit IM-17  
**\$19.95**

So Handy, So Low Cost we call it "every man's" meter. Just right for homeowners, hobbyists, boatowners, CBER's, hams . . . it's even sophisticated enough for radio & TV servicing! Features 12 ranges . . . 4 AC & 4 DC volt ranges, 4 ohm ranges; 11 megohm input on DC, 1 megohm input on AC; 4 1/2" 200 uA meter; battery power; rugged polypropylene case and more. Easy 3 or 4 hour kit assembly. Ideal gift for any man! 4 lbs.



## NEW FREE 1968 CATALOG!

Now with more kits, more color. Fully describes these along with over 300 kits for stereo/hi-fi, color TV, electronic organs, electric guitar & amplifier, amateur radio, marine, educational, CB, home & hobby. Mail coupon or write Heath Company, Benton Harbor, Michigan 49022.

**HEATH COMPANY, Dept. 20-2**  
Benton Harbor, Michigan 49022  
In Canada, Daystrom Ltd.

Enclosed is \$ \_\_\_\_\_, including shipping.

Please send model (s) \_\_\_\_\_

Please send FREE Heathkit Catalog.

Please send Credit Application.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

Prices & specifications subject to change without notice.

CL-316

CORTLANDT STREET (New York City) is now the World Trade Center. 102 story twin-towers (\$535,000,000) are rising on what was for 47 years the Electronic Bargain Center of the country. We moved one street north to 44 DEY ST, where over the counter service and Mail Orders are skilfully processed. We have always sold on a Money-Back Guarantee. Just a few items are listed below. Inquiries on parts, components, equipment and Industrial Tubes answered promptly. If we cannot serve you we will suggest who can.




COMPUTER BOARDS from IBM. Ten boards have over 35 transistors, plus over 135 parts as diodes, caps., resistors, chokes. 10 for \$1.00 . . . CLOCK MOVEMENTS: Westclox 115 VAC includes Auto-on-off, also doze light, complete with face and clock hands (no case) \$2.25 . . . TELECHRON, complete with face and clock hands, includes on-off-auto and sleep-switch \$2.30 . . . WESTCLOX Cordless Alarm Clock, battery operated, in high impact, white case 5" long, 3" wide x 3" high. Shatterproof crystal, clear bell alarm, 7 Jewels quiet tick, sweep alarm indicator, raised gold numerals, padded base. Operates one year on "C" flashlight battery. Regular 90 day factory guarantee by Westclox \$8.45 . . . TRANSISTORS: RCA 2N404, Syl. 2N229, UST 2N43A, UST 2N44 & IBM 015 (PNP-40 MHz) each 25¢ . . . SPEAKERS, Jap. 2" - 2 1/2" diam., 8 or 40 ohm, includes safety screen to protect cone 50¢ . . . HARNESS Battery Cable and clips for 9 V. Battery, 10¢ ea., \$1 doz. . . PHONO JACKS—RCA type, single + 2-3-4 gang @ 6¢ to 24¢ . . . CAPACITORS, MYLAR (yellow), .001 thru .018 mf.—100 WV @ 5¢ ea. . . .02 mf thru .22 mf.—100 WV @ 10¢ ea. . . .47-100 WV @ 15¢ . . .67 mf-100 V @ 20¢ . . .1 mfd-400 WV @ 22¢ . . . TANTALUM CAPACITORS: .0015 Mf. thru .0082 Mf-35 WV @ 10¢ ea. . . .from .01 to .1 mf. @ 15¢ ea. . . .15 to .47 mf. 20 WV @ 20¢ ea. . . .And from .47 to 50.0 Mf. at very low prices . . . POTS: AB type "J" stripped from new equipment, linear, 1/2" shaft, 2500, 5000, 10,000, 25,000, 100K, 500K ohms. Special 65¢ ea. . . .Also AB type "G" 100 ohms, thru 2.5 megohms special \$1.95 ea. . . .CIRCUIT BREAKERS: Heineman 120 VAC, SPST-5 Amps. 65¢ . . .6 Amps. 75¢ . . .10 Amps. (2 HP) \$1.00 . . .15 Amp. \$1.05 . . .West 20 Amp. SP \$1.95 . . .G.E. 2P-100 Amp. 240 VAC \$2.00 . . .R.F. Choke—1 Ma. Xmt. NATIONAL boxed, ceramic SA-8459, 5 pies, 3"TLx1" Diam. end, mtg 1 1/2" bet. holes 50¢ ea. . . .BUD 4.3 MH 12 ohm CH-569 45¢ ea. . . .RECTIFIER BRIDGE, 20 Amp. studs (N1186) 200 PRV, plates 3" sq, overall 5 1/2" L x 4" W x 3 3/8" H; Westinghouse #508C575G(H) 04-2C; for 125 V. two phase or three phase. Value \$24.00, our LOW PRICE \$8.95 . . . BRIDGE RECTIFIER, IBM, 6 Amp. 200 PIV, four studs on two copper plates, super for battery charger, compact 8" x 2" \$1.50 set . . . TOP HAT Silicon Rectifiers; quality control, inspection, conservatively rated 750 Ma. 400 PIV, 1 1/4" leads, 35¢ ea., \$24.00 per 100 . . . DUAL BANANA PLUG, GR #274-MB, black, standard 3/4" spacing 60¢ . . . PLUG (1/4" Switchcraft) & Jack (1/4" mount hole, closed circuit, impor) miniature 45¢ pr., ea. 25¢ . . . TWO-WAY SPEAKER CROSS-OVER, crosses at 2500 cycles with 8 ohm speakers, 3500 cycles at 16 ohms. Size: 2 1/2" H x 2 1/2" W x 5 1/2" L, 9" leads. Contains woofer choke and non-polarized SPEAKER CROSSOVER. Made by UNIVERSITY. Crosses at 2500 cycles with 8 ohm speakers. Includes "L" pad, "brilliance" control and "squeak" filter, with toggle switch. Special \$2.45 . . . STEPPER SWITCH (Relay) by C. P. Clare, 21 steps, 6 stacks, 55 VDC coil, spring-driven pawl (circuit open during wiper-arm movement) govt mil specs, \$8.80 . . . HAM SPECIAL! SOLID-STATE VIBRATOR ELIMINATOR. Heavy duty both 6 and 12 V. up to 25 watts. For most popular transceivers and communication equipment. Socket supplied, 4 pin plug-in; full instructions and diagrams. Housed in finned aluminum heat sink. 1 1/2" H x 2" diam. \$2.80 . . . TV Picture Tube Brighteners series 6 wire, and parallel 5 wire (TELEMATIC) 45¢ . . . FILTER CHOKES, laminated, open frame—75 ohm (3x2x1/2") \$1.25 . . .3000 ohm 1 3/4" L, 1 3/8" core, leads 40¢ . . .1 ohm 3/4" core, 2" leads 75¢ . . .0.1 ohm 20 Amp. 4 lbs. \$2.50 . . .45 ohm 2 1/4" L x 1" core, 1 1/4" lb. 80¢ . . .60 ohm 7 1/2" H, 400 Ma. \$2.00 . . .300 ohm 22 Hy. 100 Ma. (IBM power spec) \$2.60 . . .200 ohm, 20 Hy. 100 Ma. \$2.25 . . . MARKER CRYSTAL: 1.000 MHz (HOFFMAN) flat mounting, 3/4" sq. x 1/4" H. 100% guaranteed \$1.50 . . . PANEL METERS: ALL BRAND NEW! 10 Ma. DC Bakelite Case, 3 1/2" diam. \$2.75 . . .10 Ma. DC WESTINGHOUSE, 2" Bakelite NX-33 \$2.50 . . .20 Ma. DC, Sealed case, 2" diam. \$2.40 . . .50 Ma. DC, ROLLER-SMITH 3" Diam. Bakelite \$2.95 . . .100 Ua. DC, DE-JUR, 1 1/2" diam. metal case, special photo-light scale, black face, \$1.00 . . .DB Black face, sealed 3" diam. marked 10—0—6 (F.S. 15 V.) MARION \$1.95 . . .1 Ma. DC (800 V. scale) type RX-33, includes 800K w.w. multiplier \$3.50 . . .10 Ma. AC (200 Ma. DC) 2" sq. plastic modern case, white face marked, "replace? good" \$1.00 . . .1 Ma. DC—Dual scale marked 500 VDC & 140 Ma. DC. G.E. type DW-41, 2" bakelite, includes multiplier and shunt, \$2.85 . . .Extra multipliers available at 20¢ each for 14 v., 140 v., 50 v., etc. SENSITROL WESTON model #705 relay, 5 uA. SPDT, ext. electrical reset \$3.75 . . .Variable capacitor; 100 Pf; 14 plate 1/4" shaft 1/2" L. BUD #MC-1855 \$1.00 . . .APC type, var. air capacitors in stock. WRITE FOR LOW PRICES! RELAYS: Sensitive rugged, 20-30 VDC; 5.6 Ma. 4500 ohm coil, SPST, contacts 2 A. 24 VDC. (115 VAC), plug-in 7 pin tube socket, sealed can, 3/4" dia. x 2" L. 25¢ . . .115 VAC coil SPST—10 Amp. 1 1/2" x 1" x 1 1/4" SPECIAL 75¢ . . .Sensitive Swivel, 20-28 VDC., 4500 ohms 4 ma. SPST 90¢ . . .SIGMA #95740-5A for in-line (in series with equipment) SPST 5 Amp. \$1.00 . . .115 VAC or DC (all frequencies) built-in rectifier bridge, sealed 5000 ohm 20 ma. coil; contacts 3 A. 28 V. (115 VAC) compact 99¢ . . .SPDT—8 ma. 5000 ohms 24 VDC. 3/4" cube, contacts 250 ma., neomatic 35¢ . . .MERCURY WETTED RELAYS, CLARE #HG-1023, DPDT, 36 to 90 VDC, 4000 ohms. \$1.95 . . .CLARE #HB-1012, 130 ohms 39 ma., 5/2 to 16 VDC \$1.95 . . .PRECISION RESISTOR KIT; 1/2%—1%, 1/2 watt, 1 W. 2 W. values between 1 ohm and 100 megohms. No two alike. Includes refresher instruction for series, parallel combinations, 100 for \$1.50 . . .PRECISION RESISTORS—1% wirewound your choice of any value 10¢ each . . .RESISTOR KITS, Carbon 5%, 10%, 1/2 W. 1 W. 2 Watts, between 5 ohm and 100,000 ohm, 100 asstd. \$1.00 . . .between 100 K and 27 megohms, 100 asstd. for 50¢ . . .RESISTORS; CARBON, 1/2-1-2 watt to your specifications, from 6.8 ohm to 22 megohms, 5% 4¢ ea., 10% 3¢ ea. . . .POWER WIREWOUND RESISTORS, 10 watt, 4 ohm, 20, 35, 50, 220, 310, 470, 2200, 4000 ohms, each 20¢, (100 asstd. \$15.00) . . .Also 20 watt, 50, 300, 15,000, 5,000, 20,000, 22,500 & 60 K, ea. 30¢ . . .POWER RESISTORS, 5 W. to 500 watts. WRITE . . .POWERSTAT Var. XFR. 12 V. 60 cy. 0-3.5 V. 2 Amp., sec. 2 1/2" diam. 2 1/2" L. \$2.50 . . .STEP DOWN (UP) Xfr. 230V-115 V. 60 cy. 1/2 Amp. (50 watt) 2 1/2 x 2 1/2 x 2 1/4" w. open strap 4 leads, \$1.85 . . .TRANSISTOR POWER SUPPLY. Conventional full-wave bridge with 10 ohm bleeder resistor and two—8 Mfd. 150 Wv. electrolytics. For up to 115 VAC input. Output 1 Amp. Includes heat sinks. Size: 3" x 3 1/2" x 1" w. Made for Dictaphone equipment (NEW) \$1.35.

Mail check or M.O. net cash, small COD deposit; FOB our store.  
10 day money-back guarantee. Send for Our Large Bargain Catalog.

**CORTLANDT ELECTRONICS, Inc.**  
Store: 44 DEY STREET, N.Y.C. Tel. (212) 964-8044  
(one block north of Cortlandt St.) Box 553, New York, N. Y. 10008  
Circle 123 on reader's service card

# TECHNOTES

## MOTORS IN AUTO TAPE PLAYERS

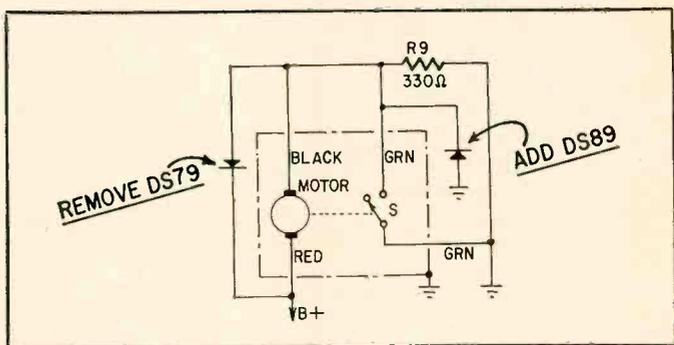

A slow tape-player motor doesn't necessarily have to be replaced. If it runs slow at 10.5 volts but is OK at 14.5, don't replace it. Cure it this way (see diagram).

1. Remove diode DS79, shunting the motor.
2. Operate the player on 16 volts dc for 5 to 15 minutes. (Applying 16 volts with spike suppressor diode DS79 removed cleans the contact points.)
3. Check the player operation periodically by listening to a tone such as Program 2 on the Delco test tape and applying between 10.5 and 16 volts. The contacts are clean when the tone is constant as the voltage is varied.
4. Install a 24-volt Zener diode (DS89). The Zener diode provides "point-cleaning" voltage and permits the player to operate at lower voltages. (Note well that this repair is not required on all tape-player motors.)—*Delco Testing Tips*

R-E

## COLOR TV AGC ADJUSTMENTS

Always readjust the AGC control after installing or repairing a color TV set. You must make this adjustment while receiving the strongest station on the customer's antenna. Improperly adjusted AGC can cause poor sync, overloading, insufficient contrast, sync buzz or horizontal pulling and results in complaints and callbacks. The correct procedure for adjusting the AGC control is:

- 1) Turn set on and warm up for 5 minutes.
- 2) Tune in strongest station in the area.
- 3) Turn CONTRAST control fully clockwise and turn BRIGHTNESS control clockwise until picture is bright but not blooming.
- 4) Slowly turn the AGC control counterclockwise just to the point where the picture weakens and begins to lose contrast.
- 5) Adjust vertical and horizontal hold controls for a steady picture. Vertical lines must not bend at the top.
- 6) Turn the AGC control clockwise very slowly until the picture bends, tears or shifts or until buzz is heard in the sound. Then, turn the control counterclockwise slowly until bending, tearing, shifting and buzz stop.
- 7) Turn the control an additional 10 degrees counterclockwise.
- 8) Check the picture at maximum contrast on all channels. Picture should not overload and should reappear immediately after changing channels.—*Admiral Service News Letter*

R-E

## Solid-State TV Servicing

(continued from page 37)

regulator (preregulator) and 14.5 at the base of the upper regulator.

Note the extremely high capacitance of the filter capacitor at the output of the rectifiers. A 3000- $\mu$ F capacitor is used, and an additional 800 at the output of the supply. These assure substantially ripple-free dc for minimum hum transistor operation. In some receivers, transistors are used in ripple-filter networks to permit use of lower-value capacitors.

The circuit used in the Sears-Silvertone model 7122 solid-state receiver is shown in Fig. 9. Any ripple

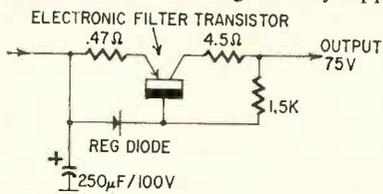


Fig. 9—The value of filter capacitor is multiplied by transistor current gain.

voltage behaves as a signal input to the base-emitter junction of the filter transistor. The collector signal that develops is out of phase with the input signal. This out-of-phase signal is applied to the output line and partially cancels the ripple from the rectifier.

Excessive ripple in the power supply will produce hum from the speaker (even with the volume control turned down) as well as hum bars on the screen. If such symptoms appear in a solid-state TV set, make sure you check filter transistors and regulator circuits in addition to the usual filter capacitors.

### Standard precautions

When working on transistor sets, keep in mind the standard precautions for all circuit testing. If you are using probes with the set turned on, watch out for possible shorting of transistor collector to base by the probe tip. Avoid temporary shorting of low or high voltages. Don't shunt in-circuit capacitors with test external capacitors while the power is on.

Keep the yoke connected all the time the set is in operation to prevent damage to the sweep output transistors. (This also applies to the speaker—keep it in the circuit whenever the set is turned on.)

As a final "don't"—don't believe the old adage that rules are made to be broken. If you don't follow the rules in solid-state TV servicing you might end up with more damaged components than you had when you began. Respect transistors and other solid-state devices. They are physically rugged, yet electronically delicate. **R-E**

# ...JUST WHAT THE TV PROBLEM ORDERED! QUIETROLE

- Lubricates and Cleans
- Apply With Spray or Dropper
- Non-inflammable . . . Non-conductive . . . Non-corrosive
- Harmless to plastics & metal — zero effects on capacity & resistance — "for color & black & white".

Quietrole is preferred by manufacturers and servicemen alike. Quiets noisy TV and radio controls. Mark-II for tuners, Spray-Pack for controls & switches, Silitron for general use.



At Your Distributor . . . Ask for Quietrole by Name.

manufactured by  
**QUIETROLE CO.**  
Spartanburg, South Carolina

Circle 124 on reader's service card

## SCHOOL DIRECTORY

### ENGINEERING MATHEMATICS

**NOW! A NEW WAY TO LEARN—I. H. S. I. WAY.** A complete home study course in engineering math to help you get the position you want—**MORE MONEY—MORE RESPECT.**

**COURSE PREPARED BY COLLEGE PROFESSORS**

who have lectured to thousands of men on math and engineering. You learn at home quickly, easily—**AS FAST** as you want.

**YOU SIGN NO CONTRACTS**

Pay only if satisfied—you owe it to yourself to examine the **INDIANA HOME STUDY INSTITUTE COURSE IN ENGINEERING MATH.**

**FREE BONUS**—if you join now, a refresher course in basic arithmetic.

Write for Brochure—No Obligation.

**THE INDIANA HOME STUDY INSTITUTE**  
Dept. RE-2, P.O. Box 1189  
Panama City, Fla. 32401

Learn Electronics for your  
**SPACE-AGE EDUCATION**  
at the center of  
America's aerospace industry

No matter what your aerospace goal, you can get your training at Northrop Tech. in sunny Southern California.


**COLLEGE OF ENGINEERING.**

Get your B.S. degree in engineering in just 36 months by attending classes year round. Most Northrop Tech graduates have a job waiting for them the day they're graduated!

**A & P SCHOOL.** Practical experience on real aircraft. One-year course prepares you for F.A.A. A & P certificate. **WRITE TODAY FOR CATALOG.**

**NORTHROP INSTITUTE OF TECHNOLOGY**

1199 W. Arbor Vitae, Inglewood, Calif.

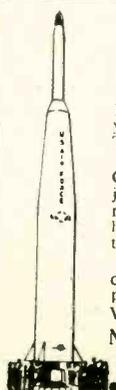







**FREE**

Fill in coupon for a **FREE** One Year Subscription to **OLSON ELECTRONICS'** Fantastic Value Packed Catalog—Unheard of **LOW, LOW PRICES** on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, Hi-Fi's, and thousands of other Electronic Values. Credit plan available.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

GIVE ZIP CODE \_\_\_\_\_

If you have a friend interested in electronics send his name and address for a **FREE** subscription also.

**OLSON ELECTRONICS, INC.**

808 S. Forge Street Akron, Ohio 44308

Circle 125 on reader's service card



### LEARN TECHNICAL WRITING

for prestige, high pay, advancement

**WRITE YOUR WAY TO SUCCESS.** Electronics, aerospace, glamour industries need trained writers now. Technical Writing is one of the highest paying careers **NOT** requiring college. The demand for trained writers is growing with thousands needed in all areas.

**ATWS WILL TRAIN YOU AT HOME AT LOW COST.** ATWS home training is fast moving, fascinating, easy-to-follow. Includes

everything you need to become a top notch Tech Writer. Low cost. Send today for free career book and sample lesson. No salesman will call. **APPROVED FOR VETERANS.**

**AMERICAN TECHNICAL WRITING SCHOOLS, Dept. RE-28**  
5512 Hollywood Boulevard, Hollywood, California 90028

### distinguished graduates


hold important engineering and business administration posts throughout U.S. Professionally-oriented college with outstanding placement record. Four-quarter year permits degree in three years. Fine faculty. Modern labs. Small classes. 300-acre campus. Accredited. Approved for vets. Modest costs. Enter March, June, Sept., Jan. For Catalog, write Admissions Director.

**TRI-STATE COLLEGE**  
2428 College Avenue, Angola, Indiana 46703

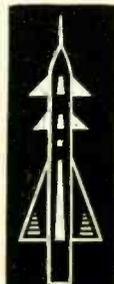
### GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic & advanced courses in theory & laboratory. Electronic Engineering Technology & Electronic Technology curricula both available. Associate degree in 28 mos. B.S. also obtainable. G.I. approved. Graduates in all branches of electronics with major companies. Start Feb., Sept. Dorms, campus. High school graduate or equivalent. Catalog.

**VALPARAISO TECHNICAL INSTITUTE**  
Dept. C, Valparaiso, Indiana 46383



**WORLD'S FINEST 5-CORE SOLDER**

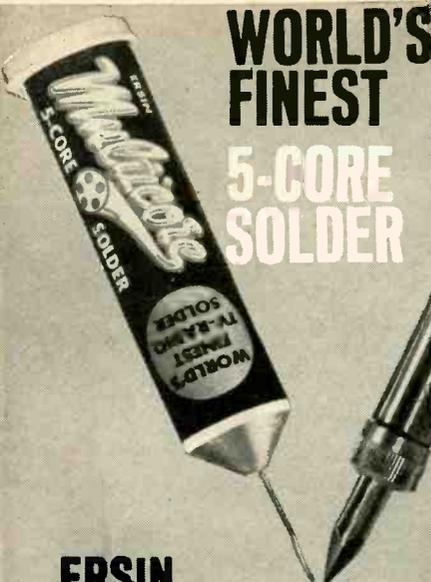

**ERSIN MULTICORE**

**NEW EASY DISPENSER PAK ONLY 69¢**


BUY IT AT RADIO-TV PARTS STORES

MULTICORE SALES CORP. WESTBURY, N.Y. 11590  
Circle 126 on reader's service card

# New Tubes
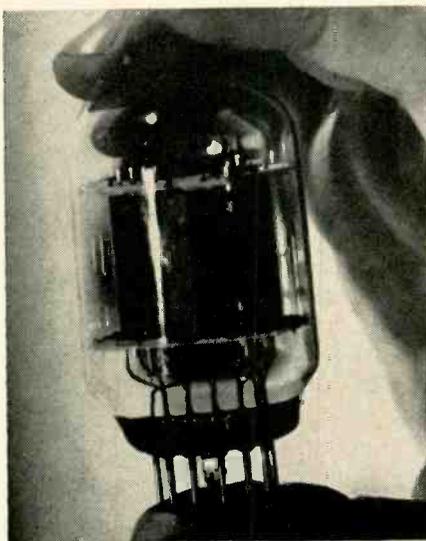
## DOUBLE-TRIODE PENTODE COMPACTRONS

The G-E 6AK9 and 16AK9 are double-triode-pentode compactrons for color TV sets. The pentode section



is suitable for use as a vertical amplifier and is particularly suited for use in sets having only 270 volts B+. Triode 1 has an amplification factor of 43 which makes it ideal for sync-clipper applications or other general-purpose uses. Triode 2 has an amplification factor of 20 and is especially suited for use in vertical oscillator circuits.

The 6AK9 has a 6.3-volt, 1.6-amp heater. The 16AK9 has a 16.4-volt, 600-mA heater for use in transformerless color TV sets.

## NEW PICTURE TUBES FOR COLOR TV

The 22JP22 and 22KP22 are designed for compact console and console color TV receivers with a picture size of 20 inches diagonal (227 square inches). The 22JP22 has a bonded etched faceplate as protection against the dangers of possible implosion. The 22KP22 does not have the

# THE PURCHASING POWER OF THE DOLLAR

At BROOKS is even GREATER than PRE-WAR ★★☆☆ THE PRICES SPEAK FOR THEMSELVES!

FREE \$1 BUY WITH EVERY 10 YOU ORDER Only applies to "\$1" Buys FREE GIFT WITH EVERY ORDER

<p><b>RCA 110° FLYBACK TRANSFORMER</b></p> <p>We scooped the Market Latest type — standard for all 110° TV's</p> <p>RCA's design of large Coil produces 18KV — assuring adequate width Inel Schematic Diagram application for any TV</p> <p>List price \$13.90</p> <p><b>Slashed to .. \$1 THIS MONTH ONLY</b></p>	<p><input type="checkbox"/> 2 — POWER TRANSISTORS Re- place 2N155, 2N176, 2N301, etc. \$1</p> <p><input type="checkbox"/> 20 — ASST. DIODE CRYSTALS fine assortment, popular types \$1</p> <p><input type="checkbox"/> 70 — BRASS FAHNESTOCK CLIPS popular type &amp; size \$1</p> <p><input type="checkbox"/> 10 — SPEAKER PLUG SETS deluxe type, 2 conductor \$1</p> <p><input type="checkbox"/> 10 SETS — DELUXE PLUGS &amp; JACKS asst. for many purposes \$1</p> <p><input type="checkbox"/> 10 — SETS PHONO PLUGS &amp; PIN JACKS RCA type \$1</p> <p><input type="checkbox"/> 10 — SURE-GRIP ALLIGATOR CLIPS 2" plated \$1</p> <p><input type="checkbox"/> 50 — RADIO &amp; TV SOCKETS all type 7 pin, 8 pin, 9 pin, etc. \$1</p> <p><input type="checkbox"/> 50 — ASSORTED PRINTED CIRCUIT SOCKETS best types \$1</p> <p><input type="checkbox"/> 100 — STRIPS ASSORTED SPAGHETTI handy sizes \$1</p> <p><input type="checkbox"/> 50 — ASSORTED PRINTED CIRCUIT SOCKETS best types \$1</p> <p><input type="checkbox"/> 10 — ASSORTED VOLUME CONTROLS less switch \$1</p> <p><input type="checkbox"/> 7 — ASSORTED VOLUME CONTROLS with switch \$1</p> <p><input type="checkbox"/> 50 — BALL POINT PENS Retractable, assorted colors \$1</p>	<p><input type="checkbox"/> HEARING AID AMPLIFIER Incl. 3 Tubes, Mike, etc. (as is) \$1</p> <p><input type="checkbox"/> 50 — ELECTROLYTIC CONDENSERS 25mfd-6v, top quality \$1</p> <p><input type="checkbox"/> 10 — 7" TAPE REELS all you want, 3000 in stock \$1</p> <p><input type="checkbox"/> TV TUNERS asst. all standard all complete (less Tubes) \$1</p> <p><input type="checkbox"/> 3—ELECTROLYTIC CONDENSERS 250/200/50mfd — 175/175/175v \$1</p> <p><input type="checkbox"/> 5—ELECTROLYTIC CONDENSERS 15/15/15mfd — 450/250/100v \$1</p> <p><input type="checkbox"/> UNIVERSAL 2" PM SPEAKER Alnico 3 magnet, quality tone .. 19¢</p> <p><input type="checkbox"/> UNIV. 3" x 5" PM SPEAKER Best type for Radios, TV, Etc. .. 59¢</p> <p><input type="checkbox"/> 15 — ASST. RADIO ELECTROLYTIC CONDENSERS \$1</p> <p><input type="checkbox"/> 15 — ASST. ROTARY SWITCHES all popular types \$20 value \$1</p> <p><input type="checkbox"/> 20 — ASST. DUAL CONTROLS for Radio, TV, Hi-Fi, Stereo, etc. \$1</p> <p><input type="checkbox"/> 5 — ASSORTED TRANSFORMERS Radio, TV and Industrial \$1</p> <p><input type="checkbox"/> 4 — AUDIO OUTPUT TRANSFORMERS asst. 6L6, 50L6, 6K6, 3Q4 \$1</p>	<p><input type="checkbox"/> TRANSISTOR RADIO asst type \$1.50 good, bad, broken, as-is, potluck</p> <p><input type="checkbox"/> TAPE RECORDER — assorted types \$4 good, bad, broken, as-is, potluck ..</p> <p><input type="checkbox"/> TELEPHONE RECORDING DEVICE place it under telephone .. \$1</p> <p><input type="checkbox"/> CRYSTAL LAPPEL MICROPHONE high impedance, 200-6000 cps .. 59¢</p> <p><input type="checkbox"/> \$4 ELECTRIC FOOT SWITCH deluxe type for any equipment .. \$1</p> <p><input type="checkbox"/> 10 — TRANSISTOR RADIO EARPIECES wired complete with plug \$1</p> <p><input type="checkbox"/> \$15.00 RADIO PARTS "JACK-POT" handy assortment .. \$1</p> <p><input type="checkbox"/> 500 — ASSORTED SCREWS 6/32, 8/32, 5/40, 4/40, Etc. 50¢</p> <p><input type="checkbox"/> 3-1/2 MEG VOLUME CONTROLS with switch, 3" shaft .. \$1</p> <p><input type="checkbox"/> 50 — TUBE CARTONS (colored) assorted sizes for Popular Tubes .. \$1</p> <p><input type="checkbox"/> 10 — ASSORTED TUBES Radio, Television and Industrial .. \$1</p> <p><input type="checkbox"/> ALL AMERICAN TUBE KIT Top Standard Brand — 12BA6, 12BE6, 12AV6, 50C5, 35W4 .... \$2</p> <p><input type="checkbox"/> 3 — TOP BRAND 35W4 TUBES \$1</p>
--	---	--	---

IMMEDIATE DELIVERY . . . Scientific light packing for safe delivery at minimum cost. HANDY WAY TO ORDER: Pencil mark or write amounts wanted in each box, place letter F in box for Free \$1 BUY. Enclose with check or money order, add extra for shipping. Tearsheets will be returned as packing slips in your order, plus lists of new offers.

Name .....

Address .....

Cost of goods .....

Shipping .....

Estimated .....


TOTAL .....

Please specify refund on shipping overpayment desired:  CHECK  POSTAGE STAMPS  MERCHANDISE (our choice) with advantage to customer

**BROOKS RADIO & TV CORP., 487 Columbus Ave., New York, N. Y. 10024** TELEPHONE 212-874 5600

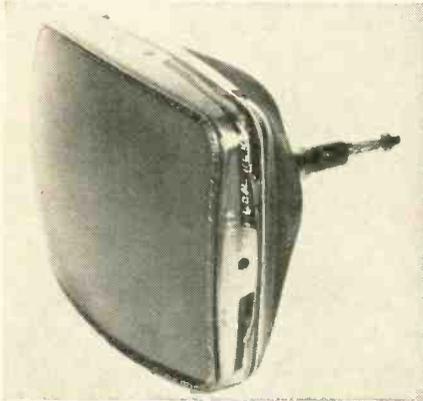
# for Television

integral faceplate and requires a separate safety glass as implosion protection. Further details on these two




tubes can be obtained from Westinghouse Electronic Tube Division, Elmira, N.Y. 14902.

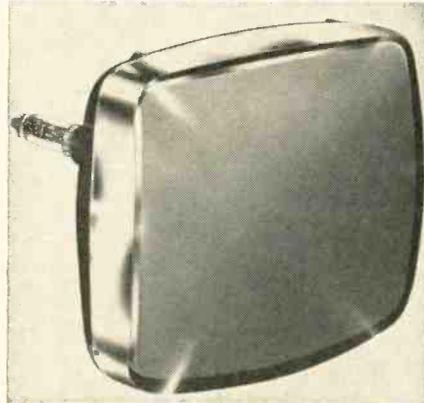The 15LP22 (right) is an RCA 14-inch diagonal 90° color picture tube featuring improved rare-earth



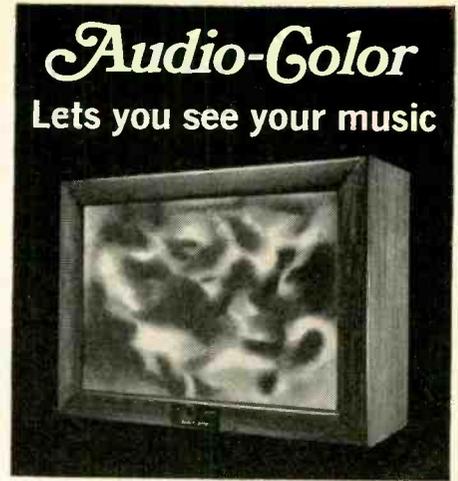red phosphor material and sulfide red and green phosphors to provide equal cathode currents. An added feature is the einzel-lens focusing system (see "How We See Color", January 1966, page 35) that eliminates the need for a separate focus rectifier. The tube is designed for operation with the blue gun down (anode contact on top) to provide the best freedom from pin-cushion distortion. **R-E**



**ASSEMBLED** \$54.95  
**KIT FORM** \$44.95  
**\$5 DOWN — \$5 MONTH**

Walnut finished cabinet included  
Shipped REA Collect

Easy to build, easy to install. All transistor AUDIO-COLOR adds a visual dimension to musical enjoyment. A brilliantly moving panorama of color casts dancing images on a soft frosted screen, reflecting rising and falling volume with each beat of the music. Here's a truly unique and exciting new musical experience. Make check or money order to CONAR.

**SEND FOR FREE CONAR CATALOG**

**CONAR** Division of National Radio Institute  
Dept. BC8C, 3939 Wisc. Ave., Washington, D.C. 20016

**CANADIANS: Ordering is easy . . . we do the paperwork . . . try a small order**

**SARKES TARZIAN TV TUNER 41mc**  
Latest Compact Model—for all 41 mc TV's.  
**NEW—MONEY BACK GUARANTEE**

Parallel filament  
**COMPLETE with Tubes & Schematic** \$7.95

Same TUNER as above (series fit.) \$7.95

**STANDARD TV TUNER** \$7.95  
Popular type for many TV's

**Mastercraft RADIO**

We tested hundreds of brands of 6 Transistor Radios side-by-side and picked the:

- **BEST STYLE**
- **BEST VALUE**

Red, White, Blue, Black

**\$3.99** Complete  
Price slashed to

**MYLAR TAPE**

3"	— 225'	.. \$ .17
3 1/4"	— 600'	.. .49
5"	— 600'	.. .52
5"	— 900'	.. .67
7"	— 1200'	.. .69
7"	— 1800'	.. .99
7"	— 2400'	.. 1.59
7"	— 3600'	.. 2.97

**CASSETTE 1 hr. 1.00**

**IBM COMPUTER SECTIONS**

8 assorted Units we sell for \$1 are loaded with over 150 valuable parts.

Incl. — Transistors  
Condensers, Resistors, Heat Sinks, Diodes, Etc.

**8 for \$1**  
**100 for \$10**


**HARDWARE SPECIALS**  
ANY 6 FOR \$5

<input type="checkbox"/> 1000 — ASST. HARDWARE KIT screws, nuts, washers, rivets, etc. \$1	<input type="checkbox"/> 100 — ASST. RADIO KNOBS all selected popular types \$1	<input type="checkbox"/> 1 — LB SPOOL ROSIN-CORE SOLDER 40/60 top quality \$1	<input type="checkbox"/> 10 — STANDARD TRANSISTORS NPN & PNP 2N404, 2N414, etc. \$1
<input type="checkbox"/> 300 — ASSORTED HEX NUTS 2/56, 4/40, 5/40, 6/32, 8/32 \$1	<input type="checkbox"/> 100 — ASST. TUBULAR CONDENSERS .001 to .47 to 600v. \$1	<input type="checkbox"/> 2 — G.E. PIECES OF EQUIPMENT stacked with over 200 useful parts \$1	<input type="checkbox"/> 10 — ASSORTED DIODE CRYSTALS 1N34, 1N48, 1N60, 1N64, etc. \$1
<input type="checkbox"/> 250 — ASST. SOLDERING LUGS best types and sizes \$1	<input type="checkbox"/> 3 — ELECTROLYTIC CONDENSERS most popular number 50/30—150v \$1	<input type="checkbox"/> 15 — G.E. 6X5GT TUBES Neon Glow Lamp for 101 uses \$1	<input type="checkbox"/> 50 — ASSORTED MYLAR CONDENSERS popular selected types \$1
<input type="checkbox"/> 250 — ASST. WOOD SCREWS finest popular selection \$1	<input type="checkbox"/> 3 — ELECTROLYTIC CONDENSERS 1000/1000/500mfd — 35/35/20v \$1	<input type="checkbox"/> 2 — G.E. 6X5GT TUBES brand new, individually boxed \$1	<input type="checkbox"/> 3 — TOP BRAND SILICON RECTIFIERS 1 amp, 1000 PIV \$1
<input type="checkbox"/> 250 — ASST. SELF TAPPING SCREWS #6, #8, etc. \$1	<input type="checkbox"/> 20 — EXPERIMENTER'S COIL "JACKPOT" assorted for 101 uses \$1	<input type="checkbox"/> 10 — G.E. SAPPHIRE NEEDLES 4G, VR-11, etc. (\$25.00 value) \$1	<input type="checkbox"/> 100 — ASST 1/4 WATT RESISTORS stand. choice ohmages, some in 5% \$1
<input type="checkbox"/> 150 — ASST. 6/32 SCREWS and 150 6/32 HEX NUTS \$1	<input type="checkbox"/> CHAPT ZU DI MITZIA "JACKPOT" double your money back if not completely satisfied \$1	<input type="checkbox"/> 50 — FEDERAL SELENIUM RECTIFIERS new Tubular Type #15A2HS1 \$1	<input type="checkbox"/> 100 — ASST 1/2 WATT RESISTORS stand. choice ohmages, some in 5% \$1
<input type="checkbox"/> 150 — ASST. 8/32 SCREWS and 150—8/32 HEX NUTS \$1	<input type="checkbox"/> 50 — ASST. TERMINAL STRIPS all types, 1-lug to 6-lug \$1	<input type="checkbox"/> 20 — ASST. PILOT LIGHTS #44, 46, 47, 51, etc. \$1	<input type="checkbox"/> 70 — ASST 1 WATT RESISTORS stand. choice ohmages, some in 5% \$1
<input type="checkbox"/> 150 — ASST. 2/56 SCREWS and 150—2/56 HEX NUTS \$1	<input type="checkbox"/> 25 — INSTRUMENT POINTER KNOBS selected popular types \$1	<input type="checkbox"/> 50 — ASSORTED #3AG FUSES popular ampere ratings \$1	<input type="checkbox"/> 35 — ASST 2 WATT RESISTORS stand. choice ohmages, some in 5% \$1
<input type="checkbox"/> 150 — ASST. 4/40 SCREWS and 150—4/40 HEX NUTS \$1	<input type="checkbox"/> 5 — I.F. COIL TRANSFORMERS sub-min for Transistor Radios \$1	<input type="checkbox"/> WIRE "JACKPOT" good variety \$1	<input type="checkbox"/> 50 — PRECISION RESISTORS asst. list-price \$50 less 98% \$1
<input type="checkbox"/> 150 — ASST. 5/40 SCREWS and 150—5/40 HEX NUTS \$1	<input type="checkbox"/> 5 — AUDIO OUTPUT TRANSFORM Sub-min for Trans Radios \$1	<input type="checkbox"/> 4 — 50' HANKS HOOK-UP WIRE assorted colors \$1	<input type="checkbox"/> 20 — ASSORTED WIREWOUND RESISTORS, 5, 10, 20 watt \$1
<input type="checkbox"/> 500 — ASSORTED RIVETS most useful selected sizes \$1	<input type="checkbox"/> 4 — TOGGLE SWITCHES SPST, SPDT, DPST, DPDT \$1	<input type="checkbox"/> 150' — BUSS WIRE #20 tinned for hookups, special circuits, etc. \$1	<input type="checkbox"/> 100 — ASST. MICA CONDENSERS some in 5% \$1
<input type="checkbox"/> 500 — ASSORTED WASHERS most useful selected sizes \$1	<input type="checkbox"/> 32' — TEST PROD WIRE deluxe quality, red or black \$1	<input type="checkbox"/> 10 — ASSORTED SLIDE SWITCHES SPST, SPDT, DPDT, etc. \$1	<input type="checkbox"/> 5 — PNP TRANSISTORS general purpose, TO-5 case \$1
<input type="checkbox"/> 100 — ASST. RUBBER BUMPERS for cabinet bottoms & other uses \$1	<input type="checkbox"/> CLEAN UP THE KITCHEN "JACKPOT" Big Deal only one to a customer \$1	<input type="checkbox"/> BONANZA "JACKPOT" not gold, not oil, but a wealth of Electronic Items—Money-Back-guarantee \$5	<input type="checkbox"/> 5 — NPN TRANSISTORS general purpose, TO-5 case \$1
<input type="checkbox"/> 100—ASSORTED RUBBER GROMMETS best sizes \$1			<input type="checkbox"/> 50 — ASST. DISC CERAMIC CONDENSERS popular numbers \$1
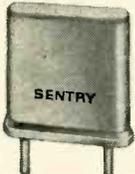
# PEED

24 HOUR DELIVERY

We guarantee that we will ship all orders for 10 crystals or less within 24 hours of receiving the order.



Buy The Best

SEND FOR OUR 1968 CATALOG OF PRECISION QUARTZ CRYSTALS AND ELECTRONICS FOR THE COMMUNICATIONS INDUSTRY



**SENTRY MANUFACTURING COMPANY**  
1634 Linwood Boulevard - Oklahoma City, Oklahoma 73106  
PHONE: 405-232-1431-TELEX: 071-361-TWX: 010-831-3178

Circle 128 on reader's service card

## U.S. GOV'T ELECTRONIC SURPLUS

Nationally Known-World Famous SURPLUS CENTER offers finest, most expensive, Government Surplus electronic units and components at a fraction of their original acquisition cost.

ORDER DIRECT FROM AD or WRITE FOR CATALOGS

### STANDARD DIAL TELEPHONE

(ITEM #715) - Standard, commercial telephone same as used throughout U.S.A. Attractive polished black, like new condition. Use as extension phone to private systems or connect several phones together for local intercom system. Full instructions are furnished. Wt. 9 lbs. Original Cost \$24.50.



F.O.B. \$7.50

### STEP-BY-STEP AUTOMATIC SWITCH

(ITEM #738) - Amazing "up-and-around", electro-magnetic telephone switch. Dial any bank pair from 1 to 100. Make your own telephone system. Can also be used to remotely control up to 100 circuits over a single pair of wires.




Complete: Switch, cover, dial, line bank, instructions..... F.D.B. \$9.95

### TYPICAL BUYS FROM OUR 1968 CATALOGS

- \$ 350.00 - Geared 2-hp Battery Golf Car Motor ..... \$26.95
- \$ 15.00 - Westinghouse DC Ammeter, 0 to 300 ..... \$ 7.11
- \$ 40.00 - Vacuum/Pressure Pump, 12-VDC ..... \$11.95
- - - 80-MW Walkie-Talkies, Per Pair ..... \$19.60
- - - Deluxe, Multi-Range, AC/DC Tester ..... \$ 8.98
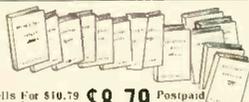
### SPECIAL SALE

Correspondence Course In ELECTRICAL ENGINEERING



Sells For \$10.79 Postpaid In U.S.A. \$8.79

(ITEM #A181) - Wonderful chance to obtain technical training at Amazing Low Cost! Lincoln Engineering School has suspended its Correspondence Course because of increased operating costs. We offer a limited number of the school's complete Electrical Engineering Course but without the examination paper grading service. The course consists of 14 lesson unit books. Each book has the regular exams, and in a separate section, "Standard Answers" to each exam question.

Course is well written, easy to understand, profusely illustrated. Reader's Digest size, easy to carry and study in spare time. Many Lincoln Engineering School students holding excellent jobs as a result of L.E.S. training. Course contains latest information on transistors, silicon diodes, etc. Additional book on how to build and operate a "Home Laboratory and Experimental Bench" furnished with each course.

SEND 25c COIN OR STAMPS FOR 3 MAIN CATALOGS

All Items FOB Lincoln Money Back Guarantee

**SURPLUS CENTER**

DEPT. RE-028 LINCOLN, NEBR. 68501

# NOTEWORTHY CIRCUITS

## FUZZ BOX FOR ELECTRIC GUITARS

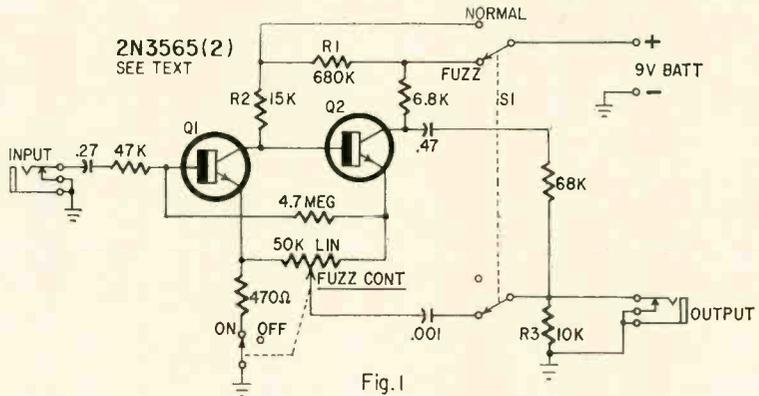


Fig. 1

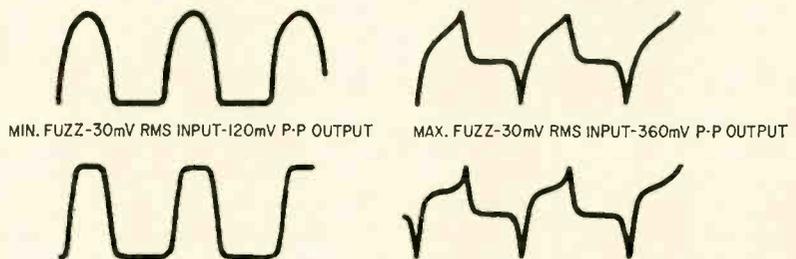


Fig. 2

A number of readers have asked for the circuit of a "fuzz box"—a device used with electric guitars to produce strident tones similar to some reed instruments. Generally, fuzz tones are produced by clipping the positive and negative peaks of the signal waveform. This generates multiple harmonics which intermodulate the original tone to give it the distinctive "fuzz".

The diagram in Fig. 1, taken from *Electronics Australia*, shows a fuzz box designed to be connected between the guitar and the amplifier input. The circuit consists of a pair of 2N3565 (Raytheon) or MPS6514 (Motorola) npn transistors connected as a direct-coupled amplifier.

When switch S1 is in the FUZZ position, Q1's load resistor consists of R1 and R2 in series. With this value of collector load resistance and forward bias, the first stage is near current saturation. The base of Q2 is direct-coupled to Q1's collector so it is held near cutoff. The positive peaks of the incoming signal are clipped by Q1 as it is driven to saturation. The negative peaks are clipped as Q2 is driven to cutoff. This results in out-of-phase square wave pulses appearing at the collec-

tor and emitter of Q2.

The high-frequency components of the distorted signal at the emitter are taken off through the .001  $\mu$ F capacitor and added to the signal from the collector appearing across output resistor R3. This produces an output waveform with spikes on the trailing edges of each square wave. The FUZZ control determines the amount of the emitter signal that is fed to the output. Fig. 2 shows the waveforms available.

When S1 is in the NORMAL position, R1 is switched to the collector load of Q2, the emitter-signal circuit is disconnected and both transistors operate as linear amplifiers. Circuit gain is about 1.5 for both modes of operation.


The original unit was built into a small metal box which resembles a sloping-panel meter case laid on its back. The foot-operated FUZZ-NORMAL switch—a heavy-duty d.p.d.t. pushbutton type—is mounted on the sloping surface that rests under the player's foot. The ON-OFF switch is on the top, and input and output jacks are on the rear.

You can also construct the fuzz box on a small circuit board and mount it on the body of the guitar. R-E

# TRY THIS ONE
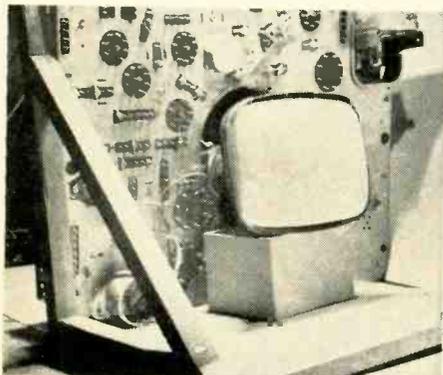
## "L" BRACKET HOLDS VERTICAL CHASSIS FOR REPAIRS


Many vertical TV chassis are difficult to hold upright for repairing. From wood, construct a large "L" bracket and platform. The TV chassis rests against the "L" bracket and on the



wooden platform. A small CRT can be plugged in and the chassis can be checked from either side. Not only is it easy to check voltages and locate defective parts, but small parts will not be bumped and accidentally broken by laying the chassis down.—*Homer L. Davidson*
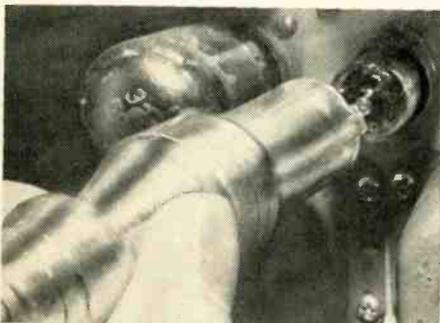
## TUBE PULLER PULLS SHIELDS


A 9-pin tube puller fits a 7-pin tube shield! This can be useful when you work with crowded aircraft equipment, where the shield is almost as hard to re-



move as the tube. I have tried a 9-pin puller on various types of 7-pin shields, and it fits them all. This idea is handy for radio and TV sets too. When replacing a shield with the puller, it is necessary only to twist the puller to remove it from the shield.—*Robert E. Kelland R-E*

Enjoy the "music-only" programs now available on the FM broadcast band from coast to coast.

- NO COMMERCIALS •
- NO INTERRUPTIONS •

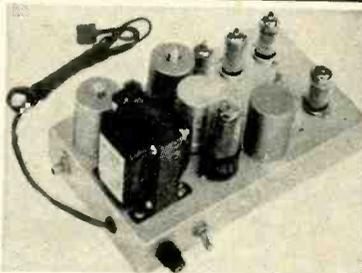

It's easy! Just plug Music Associated's Sub Carrier Detector into multiplex jack of your FM tuner or easily wire into discriminator. Tune through your FM dial and hear programs of continuous commercial-free music you are now missing. The Detector, self-powered and with electronic mute for quieting between selections, permits reception of popular background music programs no longer sent by wire but transmitted as hidden programs on the FM broadcast band from coast to coast. Use with any FM tuner. Size: 5 1/2" x 9". Shipping weight approx. 7 lbs.

**KIT \$4950**

(with pre-tuned coils, no alignment necessary)

**WIRED \$7500** (Covers extra \$4.95 ea.)

Current list of FM Broadcast stations with SCA authorization \$1.00

### MUSIC ASSOCIATED

65 Glenwood Road, Upper Montclair, N. J.  
Phone: (201)-744-3387 07043

Circle 129 on reader's service card

# Why Do You Read So Slowly?

A noted publisher in Chicago reports there is a simple technique of rapid reading which should enable you to double your reading speed and yet retain much more. Most people do not realize how much they could increase their pleasure, success and income by reading faster and more accurately.

According to the publisher, anyone, regardless of his present reading skill, can use this simple technique to improve his reading ability to a remarkable degree. Whether reading stories, books, technical matter, it becomes possible to read sentences at a glance and entire pages in seconds with this method.

To acquaint the readers of this publication with the easy-to-follow rules for developing rapid reading skill, the company has printed full details of its interesting self-training methods in a new booklet, "How to Read Faster and Retain More" mailed free to anyone who requests it. No obligation. Send your name, address, and zip code to: Reading, 835 Diversey Parkway, Dept. 684-012, Chicago, Ill. 60614. A postcard will do.

Circle 130 on reader's service card

1968 Consumer Electronics Show has been scheduled for June 23 to 26 in New York City. Exposition will include new exhibits from manufacturers of television, radio, phonographs, magnetic tape gear, and accessories for these products.

Show will occupy space in four hotels in New York—Americana, City Squire Motor Inn, New York Hilton, and Warwick Hotel.

# ELECTRONICS

## Engineering-Technicians

**Bachelor of Science Degree, 30 Months  
Save Two Years' Time**

- Radio-Television Plus Color Technician (12 Months)
- Electronics Engineering Technology (15 Months)
- Electronics Engineering (B.S. Degree)
  - Electrical Engineering (B.S. Degree)
  - Mechanical Engineering (B.S. Degree)
  - Civil Engineering (B.S. Degree)
  - Architecture (B.S. Degree) (36 Months)

The Nation's increased demand for Engineers,

Electronic Technicians, Radio TV Technicians is at an all time high. Heald Graduates are in demand for

Preferred High Paying Salaries. Train now for a lucrative satisfying lifetime career.

**Approved for Veterans  
DAY AND EVENING CLASSES**

Write for Catalog and Registration Application.  
New Term Starting Soon.

Your Name .....

Address .....

City .....

State .....



1243 Van Ness Avenue  
San Francisco, California

Circle 131 on reader's service card

# MARKET CENTER

## GENERAL

CONVERT ANY TELEVISION to sensitive Big-Screen Oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. RELCO-A25, Box 10563, Houston 18, Texas

TV SERVICE ORDER BOOKS for use with your rubber stamp. Duplicate or triplicate. Low cost. Write for FREE 32 PAGE CATALOG and Special Rubber Stamp Offer. OELRICH PUBLICATIONS, 6556 W. Higgins, Chicago, Ill. 60656

FREE ELECTRONICS (new and surplus) Parts catalog. We repair multimeters. BIGELOW ELECTRONICS, Bluffton, Ohio 45817

## "ARCTURUS" SALE

- Tube Bargains, to name just a few:
 

#6146... \$2.95	#5725/6AS6... 59¢	#6AQ5... 56¢
#6360... 3.50	#5842/417A... \$2.50	#6BQ7... 84¢
#6688... 3.50	#5847/404A... 2.50	#6CG7... 59¢
#6939... 3.50	#1AX2... 49¢; 5 for 2.00	#616... 49¢
#7025... .59	#6K7... 39¢; 3 for 1.00	#6T8... 84¢
#7788... 3.75	#12BN6 39¢; 3 for 1.00	#6U8... 77¢
#2D21... .49	#25L6... 59¢; 3 for 1.49	#12A U7... 59¢

Any unlisted receiving tubes 75% discount off list prices.

- Tube Cartons: GAUG etc. size. \$1.75 per 100. GSN7 etc. size. \$2.10 per 100. 5U4GB size, \$2.50 per 100. 5U4G size, 03¢ each.
- Obsolete Tubes: #UX200, \$1.69; #80, \$1.20; #10Y, 69¢ etc.

- 7 inch 90 degree TV bench test Picture Tube with adapter. No ion trap needed. Cat. #7BP7, \$6.99.

- Silicon Rectifier octal-based long-life replacement for 5U4, 5Y3, 5AS4, 5AW4, 5T4, 5V4, 5Z4. With diagram. Cat. # Rect 1, 99¢ each.

- OZ4 Silicon Rectifier replacement, octal based. Cat. # Rect 2, 99¢ each.

- 10 Flameless Rectifiers, 1 amp, 400 to 1000 p.i.v. Cat. # RS10, \$2.98.

- 10 Silicon Rectifiers, 750 AM., 50 to 300 p.i.v. Cat. # 330F, 99¢ each.

- Condensers: 50-30 MFD at 150 v., 39¢ each, 3 for \$1.00. Cat. # 80; 850-400-100-15 MFD at 16-16-4-115 v., 3 for 79¢. Cat. # 82Y.

- 2 Silicon Controlled Rectifiers, 1 amp, general purpose units with instructions. Cat. # SCR 1, \$1.00.

- 5 Transistor Circuit Boards containing up to 6 transistors, plus diodes, resistors, capacitors, etc. Cat. # TB10, 99¢.

- Needles: values such as # AS22 Sapphire, 39¢; Diamond, 99¢.

- Color Yokes, 70 Degree for all round color CRT's. Cat. # XRC70, \$12.95. 90 degree for all rectangular 19 to 25 inch color CRT's. Cat. # SRC90, \$12.95.

- Transistorized U.H.F. Tuners used in 1965 to 1967 TV sets made by Admiral, RCA, Motorola, etc. Removable gearing may vary from one make to another. Need only 15 volts d.c. to function. No filament voltage needed. Easy replacement units. Cat. # U.H.F. 567, \$4.95.

- General Electric U.H.F. miniature Transistorized Tuner. G.E. Part # ET85X-33. Cat. # GE85, \$4.95.

- F.M. Tuner, Hi-Fi amplifier tuning unit complete with diagram. 2 tubes. Sam's Photofacts # 620 lists 2 applications. Cat. # FM20, \$3.98.

- Flyback Transformer in original carton. Made by Merit or Todd. Most with schematic drawing of unit. Please do not request specific type. Cat. # 506, 99¢ each.

- Flyback Transformer Kits, 2 flybacks per kit. # 502E, Emerson; # 502Y, Silvertone; # 502W, Westinghouse; # 507, Philco; # 502, RCA. Any kit, \$2.99.

- Kit of 30 tested Germanium Diodes. Cat. # 100, 99¢.
- Kit of 10 NPN Transistors. Cat. # 371, 99¢. 10 PNP Transistors. Cat. # 370, 99¢. All tested.

Send for our Free Catalog listing thousands of similar best buys in tubes, parts, kits, transistors, rectifiers, etc. Orders under \$5.00, add 50¢ handling charge. Include 4% of dollar value of order for postage.

## ARCTURUS ELECTRONICS CORP.

502-22nd St., Union City, N.J. 07087 Dept. MRE  
Phone: 201-UN 4-5568

Circle 142 on reader's service card

TREASURE HUNTERS! PROSPECTORS! Relco's new instruments detect buried gold, silver, coins. Kits, assembled models. Transistorized. Weighs 3 pounds. \$19.95 up. Free catalog. RELCO-A25, Box 10839, Houston, Texas 77018

BACK-ISSUES, Electronic, Scientific Magazines. SEMCO, Box 130, Roxboro, Quebec, Canada

MAGNETS. ALL TYPES. Specials—20 disc magnets, or 2 stick magnets, or 10 small bar magnets, or 8 assorted magnets, \$1.00. MARYLAND MAGNET COMPANY, 5412-G Gist, Baltimore, Maryland 21215

LAMPKIN 103-B FREQUENCY METER \$110.00 Prepaid U.S.A. cabinet, instructions included D. CLUNE, 1106 Boulevard, New Milford, N. J. 07646

LAMP PARTS—New 1968 catalogue listing all parts, sockets—cords—pipe etc. 25¢. SECO, 109 South 20th Street, Birmingham, Alabama 35233

### ROTRON 100 CFM FANS

Sentinal—4 11/16 sq x 1 1/2 D, 115 V, 60 cy. . .	Each \$7.95
Sentinal—4 11/16 sq x 1 1/2 D, 220 V, 60 cy. . .	9.95
Gold Seal—4 11/16 sq x 1 1/2 D, 115 V, 60 cy. . .	6.95
4 Pole Single Throw Contactor—115 V 60 cy 15 Amps MFG AH & H, ROWAN, etc. . . . . \$9.95 each	
All in fine condition, working, removed from equipment. Ship post paid anywhere Continental United States.	
Leads Radio, 57RE Warren St., N.Y.C., N.Y. 10007	

### World Famed BREVETTATA TEAR GAS PISTOL

Appearance of this fine tear gas weapon is similar to real gun. It is ideal for people who work in lonely dark locations and require protection. Men give this gun to wives and daughters for night security. Many industrial applications. Shooting of gun stops aggressor without permanently injuring him. It fires six cartridges without reloading. Each gun comes with six tear gas shells and six blanks for practice and is shipped prepaid. Gun unit prices include 12 shells and all shipping costs, and this pistol is not intended for sale or possession in any locality where it is prohibited by law. Not sold to minors.



- 1 Gun-unit at . . . . . (\$11.43 ea.) \$13.07
  - 2 Gun-units at \$22.86 . . . . . (\$11.43 ea.)
  - 3 Gun-units at \$29.94 . . . . . (\$9.98 ea.)
  - 4 Gun-units at \$35.16 . . . . . (\$8.79 ea.)
- Extra boxes of ten tear gas shells at \$1.50 per box (prepaid with gun orders). Extra boxes of blanks at \$1.25 per box.

### MEREDITH SEPARATOR CO.

Dept. REL 310 W. 9th St., Kansas City, Mo. 64105

### CHEMTRONICS

## COLOR-LUBE

SPECIALLY FORMULATED TUNER CLEANER FOR COLOR TV TUNERS

Accept no substitutes



### TUNAVERTERS

POLICE, FIRE, AIR-CRAFT, MARINE AND AMATEUR CALLS ON YOUR BROADCAST RADIO! Tunable RF converters. 6-1 reduction tuning.

See complete listing in Dec. 1967 RE  
HERBERT SALCH & CO., WOODSBORO RE-2, TEX. 78393

## ADVERTISING INDEX

RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.

Allied Radio Corp. . . . .	84
American Basic Science Club, Inc. . . . .	Third Cover
Amperex Electronic Corp. . . . .	14
Amphenol Corporation . . . . .	13
Arcturus Electronics Corp. . . . .	98
B & K (Division of Dynascan Corporation) . . . . .	7, 27
Barker Products Co. (Subsidiary of Component Manufacturing Service, Inc.) . . . . .	12
Brooks Radio & TV Corp. . . . .	94-95
Burstein-Applebee Co. . . . .	70
Capitol Radio Engineering Institute, The . . . . .	46-49
Castle TV Tuner Service, Inc. . . . .	78
<b>CLASSIFIED</b>	
Cleveland Institute of Electronics . . . . .	5, 28-31
Conar (Div. of National Radio Institute) . . . . .	95
Cornell Electronics Co. . . . .	100
Cortlandt Electronics . . . . .	92
Data Corporation, The . . . . .	78
Delta Products, Inc. . . . .	16
Edison Technical College . . . . .	83
Edmund Scientific Co. . . . .	99
Electronic Measurement Corp. (EMC) . . . . .	87
Electronics and Control Engineers' Book Club . . . . .	23
Electro-Voice, Inc. . . . .	25
Enterprise Development Corp. . . . .	84
Fair Radio Sales . . . . .	83
GC Electronics Co. . . . .	24
Grantham School of Electronics . . . . .	1
Heald Colleges . . . . .	97
Heath Company . . . . .	88-91
IBM Corporation . . . . .	73
I.E.E.E. . . . .	78
International Crystal Mfg. Co., Inc. . . . .	102
Jerrold Electronics Corporation (Distributor Sales Division) . . . . .	86
JFD Electronics Co. . . . .	77
Microflame, Inc. . . . .	86
Multicore Sales Corp. . . . .	94
Music Associated . . . . .	97
National Radio Institute . . . . .	8-11
National Technical Schools . . . . .	18-21
Olson Electronics, Inc. . . . .	93
Poly Paks . . . . .	101
Power/Mate Corporation . . . . .	70
Quietrol Co. . . . .	93
RCA Electronic Components and Devices Tubes . . . . .	Fourth Cover
RCA Institutes . . . . .	64-67
Reading Improvement Program . . . . .	97
Rye Industries, Inc. . . . .	87
Sams & Co., Inc., Howard W. . . . .	80
Saxton Products, Inc. . . . .	22
Schober Organ Corp., Inc. . . . .	26
Scott, Inc., H. H. . . . .	26
Scenore . . . . .	15, 83
Sentry Manufacturing Company . . . . .	96
Shure Bros. . . . .	17
Solid State Sales . . . . .	99
Sonar Radio Corporation . . . . .	82
Sony/Superscope . . . . .	6
Sprague . . . . .	4
Surplus Center . . . . .	96
TAB Books . . . . .	85
Triplett Electrical Instrument Company . . . . .	Second Cover
Vaco Products Co. . . . .	79
Warren Electronic Components . . . . .	100
Xcelite, Inc. . . . .	81
Zenith . . . . .	72
<b>MARKET CENTER</b> . . . . .	98-101
CeCo	
Chemtronics	
Kenzac	
Lead's Radio	
McGee Radio	
Meredith Separator Co.	
Salch & Co., Herbert (Marketing Division of Tompkins Radio Products)	
<b>SCHOOL DIRECTORY</b> . . . . .	93
American Technical Writing Schools	
Indiana Home Study Institute, The	
Northrop Institute of Technology	
Tri-State College	
Valparaiso Technical Institute	

## WANTED

QUICK CASH . . . for Electronic EQUIPMENT, COMPONENTS, unused TUBES. Send list now! BARRY, 512 Broadway, New York, N. Y. 10012, 212 WALKER 5-7000

## ELECTRONICS

BARGAINS in Canadian Electronic equipment and surplus. Send \$1.00 for giant catalogs. ETCO, Box 741, Dept. R, Montreal, Canada

TUBES, "Oldies", latest. Lists free. STEINMETZ, 7519 Maplewood, Hammond, Indiana 46324

RECEIVING & INDUSTRIAL TUBES, TRANSISTORS, All Brands—Biggest Discounts, Technicians, Hobbyists, Experimenters—Request FREE Giant Catalog and SAVE! ZALYTRON, 469 Jericho Turnpike, Mineola, N.Y. 11501

Discharge IGNITION, PHOTOFLASH. Free catalog parts, kits. TRANSPARK, Carlisle, Mass. 01741

RADIO & TV TUBES 33¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. CORNELL, 4217-E University, San Diego, California 92105

MESHNA'S TRANSISTORIZED CONVERTER KIT Converts car radio to receive police & fire. 35-50Mc or 100-200Mc. (one Mc tuning) with simple step instructions \$5.00. MESHNA, No. Reading, Mass. 01864

GIANT JAPANESE ELECTRONICS CATALOG. #1. DEE, 10639A Riverside, North Hollywood, Calif 91602

BRAND NEW TUBES. World's lowest prices on Radio, TV-industrial-special purpose tubes. Write for free parts catalog. UNITED RADIO CO., Newark, N.J. 07101

CATHODIC protection instructions \$1.00. F. F. KNAPP, P. O. Box 854, Scottsdale, Arizona 85252

TV CAMERA KITS for experimental and industrial applications. Starter kits \$18.95 up! Catalog free. ATV RESEARCH, Box 453-R, Dakota City, Nebr. 68731

CALEMCO. Manufacture and design of general purpose and specialized transformers. P.O. Box 585, San Fernando, Calif. 91341

INTEGRATED CIRCUIT KITS; COMPUTER LOGIC KITS; Others. Free catalog. KAYE ENGINEERING, Box 3932-D, Long Beach, Calif. 90803

USED TV TEST INSTRUMENTS. Free list. RALPH TOLBERT, Route 1, Fayetteville, Pa. 17222

HOME ELECTRONICS Course only \$26.95. Free Literature. EDU-KITS, Departments 258G, Hewlett, New York 11557

KITS! Unusual solid-state amplifiers, mikes, power units, controls. Amazingly low-priced quality products. Free Brochure. COSMOSE ENTERPRISES, 507 Fifth Avenue, New York, N.Y. 10017

"COIL WINDING" Handbook—50¢. Experimenter's catalog includes 250 exclusive items—25¢, refundable. LABORATORIES, 12041-B Sheridan, Garden Grove, Calif. 92640

HAMMOCK REVERBERATION! New mechanism—\$4. CAL'S, Box 133, Dearborn, Michigan 48121

## AUDIO - HI-FI

RENT STEREO TAPES—over 2,500 different—all major labels—free brochure. STEREO PART I, 1616-R Terrace Way, Santa Rosa, Calif. 95404

WRITE for highest discounts on components, recorders, tapes, from franchised distributors. Send for FREE monthly specials. CARSTON, 1686-R Second Ave. N.Y.C. 10028

HI-FI COMPONENTS, Tape Recorders, at guaranteed "WE will not be undersold" prices. 15-day moneyback guarantee. Two-year warranty. NO Catalog. Quotations Free. HI-FIDELITY CENTER, 239R East 149th St., N.Y., N.Y. 10451

TAPE RECORDER SALE. Brand new, latest models, \$10.00 above cost. ARKAY SALES, 1028-E Commonwealth Ave., Boston, Mass. 02215

STEREO TAPES. Save 30% and up; no membership or fees required; postpaid anywhere USA. FREE 70-page catalog. We discount batteries, recorders, tape/accessories. Beware of slogans, "not undersold" as the discount information you supply our competitor is invariably reported to the factory. SAXITONE, 1776 Columbia Road, N.W., Washington, D.C. 20009

SPEAKER REPAIR. Hi-Fi, guitar, organ speakers reconed good as new at fraction of new speaker price. For details write WALDOM ELECTRONICS, INC. 9155-4, Dept. RE 4625 W. 53rd St., Chicago, Ill. 60632

## INVENTIONS & PATENTS

INVENTIONS-IDEAS developed: Cash/Royalty sales. Member: UNITED STATES CHAMBER COMMERCE, Raymond Lee, 230-U Park Avenue, New York City 10017

## BUSINESS AIDS

JUST STARTING IN TV SERVICE? Write for FREE 32 PAGE CATALOG of Service Order books, invoices, job tickets, phone message books, statements and file systems. OELRICH PUBLICATIONS, 6556 W. Higgins, Chicago, Ill. 60656.

1,000 Business Cards, "Raised Letters" \$3.95 postpaid. Samples. ROUTH, 5717 Friendswood, Greensboro, N. C. 27409

TWO-WAY RADIO SERVICE INVOICE FORMS—Detailed. Free Samole Form No. 50 and Catalog. OELRICH PUBLICATIONS, 6554 W. Higgins, Chicago, Ill. 60656

Attention: TV Service Dealers. HIGHLY DETAILED TV SERVICE ORDER FORM STOPS PRICE COMPLAINTS BEFORE THEY START. FREE CATALOG AND SAMPLE NO. 206. OELRICH PUBLICATIONS, 6554 W. Higgins, Chicago, Ill. 60656

## YOUR SERVICE AND QUALITY LEADER

Our semiconductors have full factory length leads, are American made, unused, and in good physical condition. Our technical descriptions and pictures are accurate.

We promise to supply you with the highest quality products at the most attractive prices with the fastest service in the industry.

### ZENERS

1 Watt 6-33V	\$ .50
10 Watt 6-200V	\$ .75
50 Watt 7-200V	\$ 1.75

### 1 AMP Top Hat & Epoxy

PRV	AMP	PRV	AMP
100	.07	1000	.35
200	.09	1200	.50
400	.12	1400	.65
600	.18	1600	.80
800	.22	1800	.90

## TRIACS

TO-66  
5 AMPS



POST OFFICE BOX 74D  
SOMERVILLE, MASS. 02143  
TELEPHONE (617)547-4005

Send For Our Latest Catalog Featuring Transistors, Rectifiers And Components  
328 Elm Street, Cambridge, Mass.

SIM TO 2N3429 (NPN) SI, 7/8" stud, min Hfe of 30, 7.5 amps, 175 watts, Vce of 75. \$2.75

SILICON BILATERAL SWITCH. Replaces two SCR's by firing in either direction when breakdown voltage is exceeded. Used in light dimmers, etc. 2/\$1.00

1000 PRV at 3A full wave bridge \$3.50

NEON LIGHT of NIXIE TUBE DRIVERS. An NPN, TO-18, Si Transistor with a V<sub>CB0</sub> of 120 3/\$1.00

500 Hfe PLASTIC TRANSISTORS (NPN) TO-18, S1 unit sim to 2N3565. 3/\$1.00

SIM. to 2N2875 (PNP). Silicon 20 watts with 30 MHz cut off \$ .75

HIGH-VOLTAGE NPN 150V V<sub>CB0</sub> at 2.5A, hi gain in TO-66 pack \$ .75

### Silicon Power Rectifiers

PRV	3A	12A	20A	40A
100	.09	.30	.40	.75
200	.16	.50	.60	1.25
400	.20	.70	.80	1.50
600	.30	1.00	1.20	1.80
800	.40	1.25	1.50	2.30
1000	.55	1.50	1.80	2.70

## INTEGRATED CIRCUITS



SR FLIP FLOPS	\$.90
JK FLIP FLOPS	\$1.15
DUAL NAND NOR GATES	\$1.00
SR CLOCKED FLIP FLOPS	\$1.15
SRT FLIP FLOPS	\$1.15
8 INPUT NAND NOR GATES	\$1.00
OVAL AND GATE	\$1.00
QUAD NAND NOR GATES	\$1.00

TO-85 flat pack with holder. Guaranteed to work. They come complete with schematic, elect. characteristic sheet and some typical applications.

CADMIUM SELENIDE PHOTO CONDUCTIVE CELLS. Dark resistance of 500 megohms. Sensitivity of 1-4.99  $\mu$ a/ft candle with data sheet \$1.25

### Silicon Control Rectifiers TO-66 pack Studs

PRV	3A	7A	20A
50	.35	.45	.70
100	.50	.65	1.00
200	.70	.95	1.30
300	.90	1.25	1.70
400	1.20	1.60	2.10
500	1.50	2.00	2.50
600	1.80	2.40	
700	2.20	2.80	
1000		4.00	

Terms: FOB Cambridge, Mass. Send check or Money Order. Rate companies 30 days net. Include Postage, Average Wt. per package 1/2 lb. Allow for C.O.D. Minimum Order \$3.00

## UNUSUAL BARGAINS

... MANY U.S. GOV'T SURPLUS

### FLY 9-FT. HOT AIR BALLOON

9 Ft. tall. Rises to amazing heights on just hot air. Supplied with tether attached, so can be used over and over. Easy to make, launch, fly. Loads of fun. Great for celebrations, science fairs, plain fun. Will lift model gliders, parachutes, instruments, etc.—anything up to 1/2 lb. Approx. 5 ft. diam. when fully inflated. Kit contains 10 pre-cut red & white gores (No. 1 model paper), 6 ft. 14-gauge wire for bottom ring, top, "tie-off" cord, complete instructions. Stock No. 60, 691EH \$2.00 Ppd.

### NICKEL-CADMIUM BATTERY BARGAINS

Terrific value—used government surplus. Quick-charge, lightweight 6-volt nickel-cadmium battery. 4-amp. hour capacity. Almost unlimited life—thousands of discharge-charge cycles with minute deterioration. Charges fully in approx. 1 hr. with Edmund Charger Kit. Hundreds of uses for hobby, photography, model building, industry, etc. Only few drops of water yearly for full maintenance. Req. minimum of electrolyte-sealed to prevent loss. Delivers nearly 100% output at below freezing. Maintains constant voltage through major portion of capacity. Five vented 1/2 cell straps in 3 polypropylene bands. 3 1/2"x2"x6". 10 & "Jumbo" 275 Ampere Hour Batteries also available. Write for info.

Stock No. 70,942EH \$15.00 Ppd.  
1.2 VOLT NICKEL-CADMIUM CELL  
Stock No. 41,109EH \$ 3.95 Ppd.

CHARGE KIT FOR 6-VOLT BATTERY  
Stock No. 70,807EH \$ 8.00 Ppd.

Order by Stock No. Check or M. O.—Money-Back Guarantee.  
EDMUND SCIENTIFIC CO. 300 EDCORP BUILDING  
BARRINGTON, N.J. 08007

## CLIP AND MAIL COUPON TODAY

EDMUND SCIENTIFIC CO. 300 EDCORP BLDG.  
BARRINGTON, N.J. 08007

### SEND FOR FREE CATALOG "EH"

Completely new 1968 edition. New item categories, illustrations. Dozens of electrical and electromechanical parts, accessories. Enormous selection of Astronomical Telescopes, Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Many war surplus items: for hobbyists, experimenters, workshop, factory. Mail coupon for catalog "EH".



NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Circle 143 on reader's service card

Circle 144 on reader's service card

# SILICON RECTIFIER SALE

IMMEDIATE DELIVERY  
FULLY GTD AMERICAN MADE  NEWEST TYPE FULLY TESTED

## 1 AMP TOP HAT AND EPOXIES

PIV	SALE	PIV	SALE	PIV	SALE
50	.05	800	.19	1800	.87
100	.07	1000	.31	2000	1.45
200	.08	1200	.44	3000	1.80
400	.11	1400	.62	4000	2.30
600	.16	1600	.72	—	—

## "SILICON POWER DIODE STUD MOUNT"

PIV	3A	6A	12A	50A	100A	160A
50	.07	.18	.22	.50	.85	2.25
100	.09	.24	.29	.73	1.05	2.65
200	.15	.37	.48	1.23	1.60	3.50
400	.19	.48	.68	1.45	2.50	4.25
600	.28	.72	.95	1.75	3.75	6.50
800	.38	.87	1.15	2.20	—	—
1000	.53	1.10	1.40	2.60	—	—

## "SCR" SILICON CONTROLLED RECT "SCR"

PRV	7 AMP	16 AMP	25 AMP	PRV	7 AMP	16 AMP	25 AMP
50	.45	.60	.70	400	1.60	1.85	2.10
100	.65	.85	1.00	500	1.95	2.35	2.50
200	.95	1.20	1.30	600	2.35	3.50	3.75
300	1.25	1.45	1.70	700	2.75	4.25	—

### SPECIALS!

Westinghouse 160 AMP, 500 PIV SILICON HI-POWER STUD RECTIFIER IN1666. **\$5.10 ea. 10 for \$45.00**  
Limited quantity.

100 Different Precision Resistors 1/2—1—2 Watt 1/2%—1% TOL **\$1.25**

Asst transistor Kit. P.N.P.—N.P.N. All popular types. Unchecked **100 for \$2.95 500 for \$9.95**

Computer Grade Condenser 15,500 MFD 12 VDC American Mfg. **.75 ea.**

NEW DIODE KIT ALL POPULAR TYPES IN34, IN34A, IN48, IN60, IN64 etc. **100 for \$ 4.00 BEST QUALITY 500 for \$15.00**

Money Back guarantee. \$2.00 min. order. Include additional \$ for postage. Send check or money order. C.O.D. orders 25% down.

Warren Electronic Components

230 Mercer St., N. Y., N. Y. 10012 • 212 OR 3-2620

Circle 145 on reader's service card

# MARKET CENTER

Attention: TV Service Dealers. TV SERVICE CONTRACTS FORMS. Free Catalog and Samples No. 105. OELRICH PUBLICATIONS, 6554 W. Higgins, Chicago, Ill. 60656

"PROFIT GUARD" BOOKKEEPING SYSTEM FOR TV SERVICE. Complete—easy to use. Free Catalog and Sample No. 1800 Page. OELRICH PUBLICATIONS, 6554 W. Higgins, Chicago, Ill. 60656

REGISTRY AND JOURNAL for TV APPLIANCE AND EQUIPMENT DEALERS. Keeps record of daily sales by make, model, serial, etc. Stops inside theft. Provides quick reference. Free catalog and sample page No. 1700. OELRICH PUBLICATIONS, 6554 W. Higgins, Chicago, Ill.

WRITE NOW FOR 1968 SENT FREE **McGEE'S CATALOG**  
**1001 BARGAINS IN**  
SPEAKERS—PARTS—TUBES—HIGH FIDELITY COMPONENTS—RECORD CHANGERS—Tape Recorders—Kits—Everything in Electronics  
1901 McGee Street, Kansas City (RE), Missouri 64108

## EDUCATION/ INSTRUCTION

LEARN TECHNICAL WRITING—at home. High paying prestige careers not requiring college. Growing demand, all industries for tech writers now. Low monthly tuition. Easy to understand. FREE career book, sample lesson. APPROVED FOR VETERANS. AMERICAN TECHNICAL WRITING SCHOOLS, Dept. REC-28, 5512 Hollywood Blvd., Hollywood, Calif. 90028

COMPUTER LOGIC. Design new "electronic brains"! Rewarding careers! Free homestudy brochure. COMPUTER SCIENCES INSTITUTE, 11727G Mayfield, L. A., Calif. 90049

88-108 MC F.M. RECEIVER  
10 TUBE CRYSTAL CONTROLLED F.M. RECEIVER WITH TUBES VOLUME TONE CONTROLS 4 WATT OUTPUT. 115 V 60 CYCLE. METAL CABINET 8H x 10D x 12W. WITH DIAGRAM LESS CRYSTAL AND SPEAKER. REMOVED FROM SERVICE BY STORECAST OUTFIT THAT WENT SOLID STATE. \$14.50 EA: 2 for \$25.00 PLUS SHIPPING.  
LEED'S RADIO, 57RE WARREN ST., N.Y.C. 10007

# CORNELL One Year TUBES Guaranteed

Tubes are new or used and so marked.

Lab-tested. Individually Boxed. Branded and Code Dated.

OZ4	3B26	6AB4	6AT6	6BA6	6BQ6	6CG7	6EA7	6K7	6SN7	6X4	12AD6	12BE6	12SQ7	77
1B3	3DG4	6AC7	6AT8	6BC5	6BQ7	6CG8	6EM5	6Q7	6SQ7	6X8	12AE6	12BF6	25L6	78
1J3/1K3	5U4	6AG5	6AU4	6BD6	6BZ6	6CM7	6F6	6S4	6SR7	7A7	12AF6	12BH7	25Z6	84/624
1H5	5U8	6AK5	6AU5	6BG6	6C4	6CZ5	6GH8	6SA7	6U7	7AB	12AT7	12BL6	35W4	5687
1L4	5V4	6AL5	6AU6	6BJ6	6C6	6D6	6H6	6SH7	6U8	7B6	12AU7	12BY7	35Z3	6350
1T4	5Y3	6AN8	6AV6	6BL7	6CB6	6DA4	6J5	6SJ7	6V6	7C5	12AX7	12C5	50L6	6463
1U4	6A6	6AQ5	6AW8	6BN4	6CD6	6DE6	6J6	6SK7	6W4	7N7	12BA6	12CA5	24	7044
1X2	6AB	6AS5	6AX4	6BN6	6CF6	6DQ6	6K6	6SL7	6W6	7Y4	12BD6	12SN7	27	

Other tubes and CRT's at low prices—send for free list

NO SUBSTITUTIONS WITHOUT YOUR PERMISSION • YOUR ORDER FREE IF NOT SHIPPED IN 24 HRS.

## TRANSISTORS

FAIRCHILD SEMICONDUCTOR

FOR—RADIO—TV—HI-FI—REPAIRS

ORDER CORNELL PART NO.	FAIRCHILD	REPLACEMENT FOR
79-79	2N434A	6X4
69-69	2N435A	6X4
69-69	2N436A	6X4
79-79	2N437A	6X4

Prestige & Success are yours as an ELECTRONIC EXPERT



COMPLETE RADIO SERVICING AND REPAIR COURSE ONLY \$3.00  
BASIC ELECTRONICS COURSE ONLY \$3.00  
NEW PRACTICAL TV TRAINING COURSE ONLY \$3.50  
Both above courses \$6.00

## TUBE CARTONS

HIGH GLOSS RED & BLACK With built in Diagonal Partitions  
CLAY COATED

SIZE	FOR TUBE SIZE	PRICE PER 10 CARTONS	PRICE PER 100 CARTONS
MIN.	6AU6	.29	2.59
GT.	6SN7	.39	3.49
LG. GT	5U4GB	.59	5.29
G.	5U4G	.89	7.99

Special! With every \$10 Order **25¢** per tube (No Limit) from this list.

6AG5 6SN7  
6AQ5 6CB6 6S4  
6AU6 6J6 6W4

FREE

Send for CORNELL'S NEW 1968 CATALOG!!!

PICTURE TUBES!

MANY NEW ITEMS!!!

FREE

all purpose ELECTRONIC CLEANER **89¢**



# CORNELL

Dept. RE-2—4217 UNIVERSITY AVE.  
SAN DIEGO, CALIFORNIA 92105

TERMS: ORDERS OVER \$5.00: Add 3c per tube shipping. Prepay in full and avoid C.O.D. charges. Send \$3.00 deposit on C.O.D. orders. No 24 hr. free offer on personal checks orders. ORDERS UNDER \$5.00: Add 3c per tube shipping plus 50c handling. CANADIAN AND FOREIGN ORDERS: Add approximate postage. No C.O.D. orders. COMBINE VARIED ITEMS TO BRING YOUR ORDER OVER \$5.00

Circle 146 on reader's service card

LEARN ELECTRONIC ORGAN SERVICING. New home study course covering all makes electronic organ including transistors. Experimental kits—schematics—trouble-shooting. Accredited NHC-GI Approved. Write for free booklet. NILES BRYANT SCHOOL, 3631 Stockton Blvd., Dept. F, Sacramento 20, Calif.


WANTED! TV-RADIOMEN to learn aircraft electronics servicing. Numerous job openings everywhere. Write: ACADEMY AVIONICS, Reno/Stead Airport, Reno, Nevada

HIGHLY EFFECTIVE HOME STUDY COURSE in Electronics Engineering Mathematics with circuit applications. Earn your Associate in Science degree. Free literature. COOK'S INSTITUTE OF ELECTRONICS ENGINEERING, P.O. Box 36185, Houston, Texas 77036 (Established 1945.)

HIGHLY EFFECTIVE HOME STUDY REVIEW for FCC commercial phone exams. Free literature. COOK'S SCHOOL OF ELECTRONICS, P.O. Box 36185, Houston, Texas 77036

FCC First Class License in six weeks—nation's highest success rate—approved for Veterans Training. Write ELKINS INSTITUTE, 2603E Inwood Road, Dallas, Texas 75235

**LIKE MUSIC WITHOUT COMMERCIALS?**

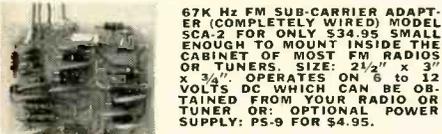

67K HZ FM SUB-CARRIER ADAPTER (COMPLETELY WIRED) MODEL SCA-2 FOR ONLY \$34.95 SMALL ENOUGH TO MOUNT INSIDE THE CABINET OF MOST FM RADIOS OR TUNERS. SIZE: 2 1/2" x 3" x 3/4". OPERATES ON 6 to 12 VOLTS DC WHICH CAN BE OBTAINED FROM YOUR RADIO OR TUNER OR: OPTIONAL POWER SUPPLY: PS-9 FOR \$4.95.

The SCA-2 sub-carrier adapter makes it possible for you to enjoy the background music transmitted on a 67KHz sub-carrier on many FM stations. (These programs cannot be heard on a FM set without an adapter.) In the US there are approximately 400 FM stations authorized by the FCC to transmit the 67KHz programs. If you are within 50 miles of a city of 100,000 or more, it is probable that you are within the satisfactory reception range of one or more of these stations. If in doubt write for a list of such stations in your area. The SCA-2 requires only four connections to your FM receiver or FM tuner/amplifier. These are: Multiplex output, audio input, and DC power. If your FM set does not have a multiplex output jack, we supply instructions of where to connect.

**ONE YEAR FACTORY GUARANTEE**  
THE SCA-2 IS A STABLE, EXTREMELY LOW NOISE UNIT REQUIRING NO FIELD ADJUSTMENT. Available in General Electric Model T2230 table radio. This is an AC operated, 13 transistor, AM/FM radio with a four inch speaker, for \$84.95. Send order to: KENZAC, P.O. B. 66251, Houston, Tex. 77006.

Top Paying Jobs—Guidance Manual \$1. CANADIAN INSTITUTE OF SCIENCE & TECHNOLOGY, 263E Adelaide St. W., Toronto

"SLEEP-LEARNING." Send for free brochure, "What's It All About." TAPES, Box-190RE, Quincy, Mass. 02169

WATCH REPAIRING. Learn to repair American and Swiss watches in spare time at home. Tuition \$5 monthly. Diploma awarded. Free sample lesson. No obligation. CHICAGO SCHOOL, Dept. REO, Fox River Grove, Illinois 60021

**GOVERNMENT SURPLUS**

72 page illustrated Government Surplus Radio, Gadgeteers Catalog 25¢. MESHNA, Nahant, Mass. 01908

**BC-603 FM RECEIVER**

20 TO 27.9 MC.

ONLY \$29.95

Excellent Used



Write for quantity discounts—  
10 Channel, pushbutton tuning or continuous tuning. Complete with speaker, tubes, squelch.  
12 or 24V Dynamo for Above  
Exc. Used 4.95

AC POWER SUPPLY FOR BC603, 683 Interchangeable, replaces dynamotor. RECVR. CHANGE NEEDED. Provides 220 VDC @ 80 Ma. 24VAC @ 2 Amps. \$7.95

FREE—Ham tube catalog  
120 W. 18th St., New York, N. Y. 10011 212-242-7400

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services): 60¢ per word . . . minimum 10 words.

NON-COMMERCIAL RATE (for individuals who want to buy or sell personal items) 30¢ per word . . . no minimum.

Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. Misleading or objectionable ads not accepted. Copy for May issue must reach us before March 10th.

**CLASSIFIED ADVERTISING ORDER FORM**

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

No. of Words { @ .30 Non-Commercial Rate } = \$  
{ @ .60 Commercial Rate }

Total Enclosed \$

Insert \_\_\_\_\_ time(s)

Starting with \_\_\_\_\_ issue

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

SIGNATURE \_\_\_\_\_

MAIL TO: RADIO-ELECTRONICS, CLASSIFIED AD DEPT., 154 WEST 14TH ST., NEW YORK, N.Y. 10011

Payment must accompany order unless placed through accredited advertising agency 28

**DOUBLE BONUS**  
\$25 WORTH OF TRANSISTORS RECTIFIERS RESISTORS CONDENSERS DIODES ETC.  
Add 25¢ for handling  
**BOTH FREE WITH ANY \$10 ORDER**

PLUS CHOOSE ANY \$10 ITEM FREE


**FACTORY TESTED \$1 SEMI-KON-DUCTORS**



- 2—85 WATT 2N424 PLANAR, silicon, TO-53 npn \$1
- 3—40W NPN SILICON MESA, 2N1648, transistor \$1
- 4 2N170 TRANSISTORS, by GE, npn for gen'l rf \$1
- 15 3 Amp RECT's, studs, silicon, to 800V no test \$1
- 4—2N255 POWER TRANSISTOR EQUALS . . . \$1
- 10 PNP SWITCHING TRANS'TRS, 2N404, no test \$1
- 4 GE 2N43 OUTPUT TRANSISTORS pnp, TO3 . . . \$1
- 5 2N107 TRANS'TRS, by GE, pnp, pop. audio pak \$1
- 4—2N1613 NPN SIL. 120 mc, by "Rheem" TO-46 \$1
- 3—45 AMP POWER RECTIFIERS, stud, silicon . . . \$1
- 5 2N706 500MW, 300 MC NPN transistors, TO-18 \$1
- 10PNP SWITCHING TRANSISTORS, no test, TO-5 \$1
- 25 TOP HAT RECTIFIERS, silicon, 750 ma, no test \$1
- 4 BIDIRECTIONAL TRANSISTORS, 2N1641 . . . \$1

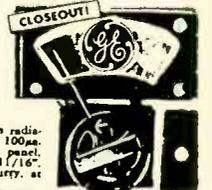**100 MICROAMP PANEL METER**

Made in U.S.A. D'Arsonval Meter Movement **2.99 ea**



New! Originally designed to be used with radiation detector! Basic meter movement, 100µa, 2 mounting holes for easy installation in panel. Size: 2 1/2" x 3/4". Mounting centers: 1-1/16". Ideal for builders, hobbyists, labs, etc. Hurry, at this fantastic price they won't last long!

- 10 NPN SWITCHING TRANS'TRS, 2N388 no test . \$1
- 15 PNP TRANS'TRS, CK722, 2N35, 107, no test . \$1
- 15 NPN TRANSISTORS, 2N35, 170, 440, no test \$1
- 30 TRANSISTORS, rf, if, audio osc-ifs, TO5 no test \$1
- 4—"EPOXY" TRANSISTORS 2N3563, 600 MC . . . \$1
- 4—"EPOXY" TRANSISTORS 2N3643 by Fairchild \$1
- 3 EPOXY TRANSISTORS 2N4265 by Motorola . . . \$1
- 4 EPOXY TRANSISTORS 400 HFE by Fairchild . . \$1
- 5—1 Amp 800 PIV EPOXYS, submini . . . . . \$1
- 2 2N918 TRANSISTORS 1000MC npn TO18 . . . . \$1
- 3—5-WATT EPOXY B-5000 Bendix transistors . . \$1
- 2 PHOTO ELECTRIC CELLS by GE Very High Z . . \$1
- 2 FETS FOR HOBBYIST, EXPERIMENTERS . . . . . \$1
- 3—2 AMP 1000 PIV, axial leads silicon . . . . . \$1
- 10—10-AMP SILICON RECTIFIERS, studs, ASST . . . \$1

**MOTOROLA HIGH POWER**  
**3 for \$1**  
PNP 100Watt/15 Amp HiPower  
T036 Case1 2N441, 442, 277,  
278. DS501 up to 50 Volts

G.E. 1 AMP	PIV	Sale	PIV	Sale
MICROMINIATURE	50	5¢	600	19¢
SILICON RECTIFIERS	100	7¢	800	27¢
	200	9¢	1000	39¢
	400	13¢		

**Stereo PREAMP 4.95**  
★ 8 TRANSISTORS  
★ Ready to Play thru tape Amplifier, radio, TV  
★ Volume, Tone, Controls sw

**2N3235 NPN SILICON**  
(Watts) 115  
BV C80 100  
(AMP) 15 **\$2.25**

**1 AMP TOP HAT AND EPOXIES**


PIV	Sale	PIV	Sale	PIV	Sale
50	5¢	800	21¢	1800	75¢
100	6¢	1000	32¢	2000	1.10
200	8¢	1200	45¢	4000	1.50
400	11¢	1400	55¢		
600	17¢	1600	65¢		

**POLY PAKS**  
P.O. BOX 942R  
SO. LYNNFIELD, MASS. 01940


TERMS: add postage; rated; net 30 days. COD's 25%  
"SPRING" BARGAIN CATALOG **10¢**

# WHERE RELIABILITY & ACCURACY COUNT

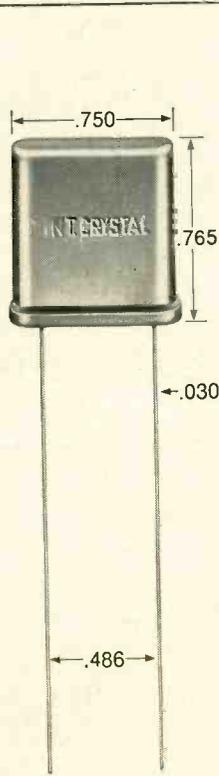
## INTERNATIONAL PRECISION RADIO CRYSTALS 70 KHz to 160 MHz



F-700

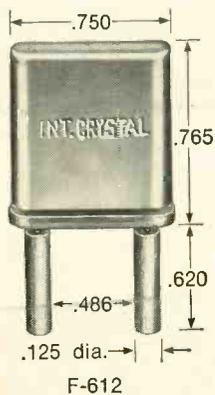


F-612

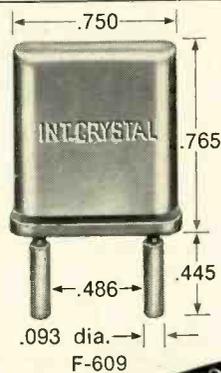


F-609


### HOLDER TYPES

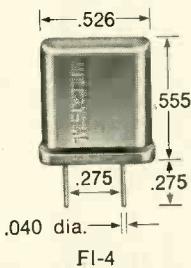



FI-4

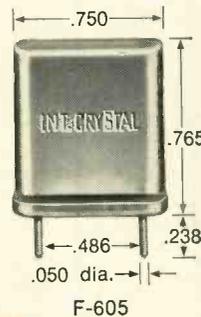

F-605

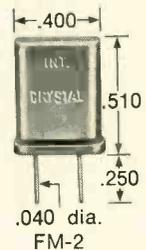

FM-2

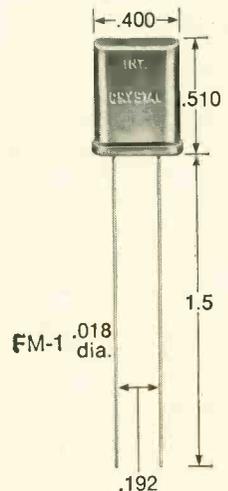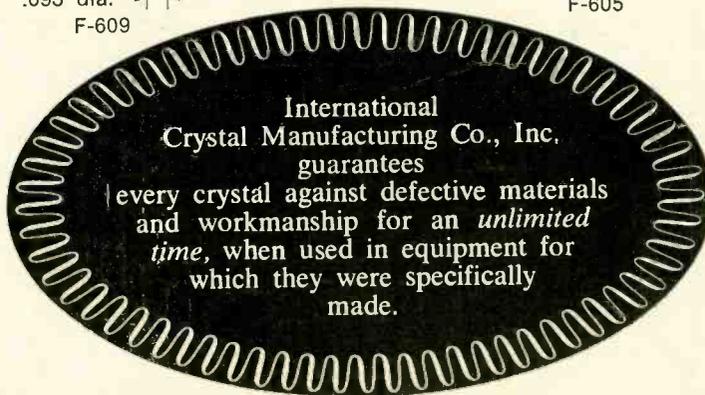

FM-1

### Crystal Types:

- (GP) for "General Purpose" applications
- (CS) for "Commercial" equipment
- (HA) for "High Accuracy" close temperature tolerance requirements

International Crystals are available from 70 KHz to 160 MHz in a wide variety of holders.


Crystals for use in military equipment can be supplied to meet specifications MIL-C-3098C

WRITE FOR COMPLETE CATALOG.



**INTERNATIONAL**  
CRYSTAL MFG. CO., INC.  
10 NO. LEE • OKLA. CITY, OKLA. 73102

F-13

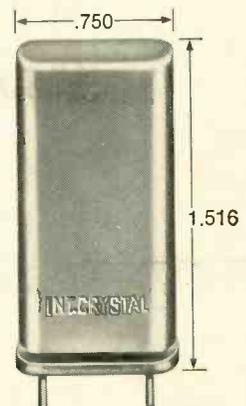



# We can't leave well enough alone...

...so we redesigned the RCA-6BK4A to improve its capability in shunt regulator circuits of high voltage power supplies in color TV receivers. Always the best tube to do the job, the RCA-6BK4B is now even better.

An improved plate provides highly efficient heat radiation and uniform temperature distribution...and permits a 40 W max. plate dissipation rating. This rating is especially important in present-day color receivers. An increased peak

negative heater-cathode voltage capability of 450 V max. results from better heater insulation and tighter processing controls. A redesigned top cap reduces strain on dome of the glass envelope for greater strength and reliability.

Innovations and improvements that make your service operation more reliable, efficient and profitable are our constant aim. So see your local Authorized RCA Tube Distributor for quality RCA receiving tubes.



RCA Electronic Components and Devices, Harrison, N. J.



The Most Trusted Name in Electronics